



Why does a DC Power Supply need a Power Sink

Modern Loads and Test-Systems become more demanding

In the past a DC power supply only needed to *deliver* power, now loads can *return* power. The only way to cope with this new challenge is integrating an electronic load in the power supply, called a Power Sink. Without the sink-capability the output voltage will start rising and get out of control.

Reverse Current

DC Motors are more and more controlled by a PWM (Pulse Width Modulation) circuit; the advantage is a flexible loss-less speed control. Car makers make use of this technique to make new solutions possible for pumps, electric steering, brakes, windscreen wipers, hybrid cars and more. Also energy is conserved, this means less heat dissipation. The special behaviour of a PWM controlled motor is the return of power during a braking action. In fig. 1 you can see the typical load current, in phase I the motor accelerates; in phase II it has constant speed with a certain load and in phase III the motor brakes and the current becomes negative.

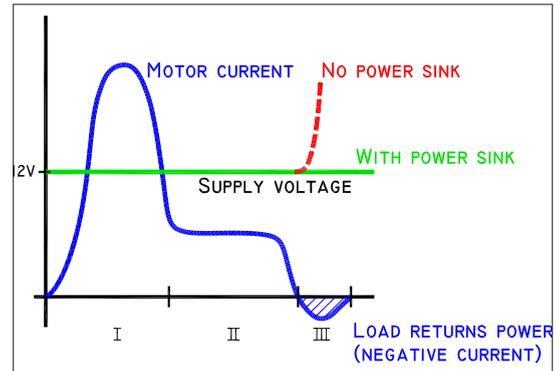


Fig. 1
 Typical load current
 PWM - controlled DC motor

Output under control

Normally the output circuit of a power supply is not designed to absorb current returned by the load; see the simplified circuit in fig. 2. The only path left for the negative load current is into the output capacitor C_o , so it will charge and the voltage will rise without any control from the power supply, following the formula $dv/dt = i/C$. To solve this problem a Power Sink is added, symbolised by the transistor in fig. 3, and integrated in the voltage control of the power supply. So the output voltage is kept to the desired voltage, whether the operation mode is sink or source. Dynamically the system reacts fast, see fig. 5. In this example the load current is switched between positive and negative (a harsh condition). On the output voltage only a slight variation is visible (upper trace). On a normal unit the voltage would rise uncontrolled, see fig. 4.

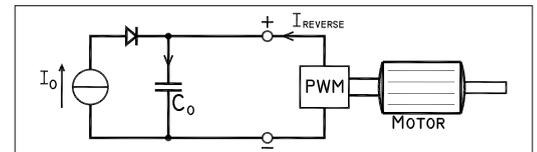


Fig. 2
 Simplified output circuit normal power supply.
 Braking power of motor charges
 output-capacitor

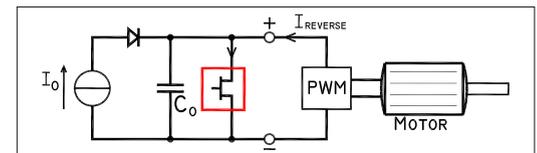


Fig. 3
 Braking power of motor absorbed by power sink
 equipped power supply.
 No voltage rise

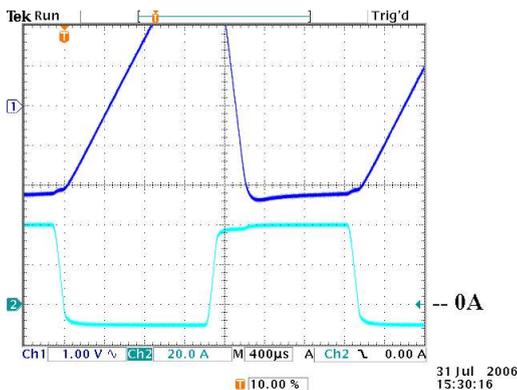


Fig. 4
 Without power sink
 Uncontrolled voltage rise when the load current
 goes negative

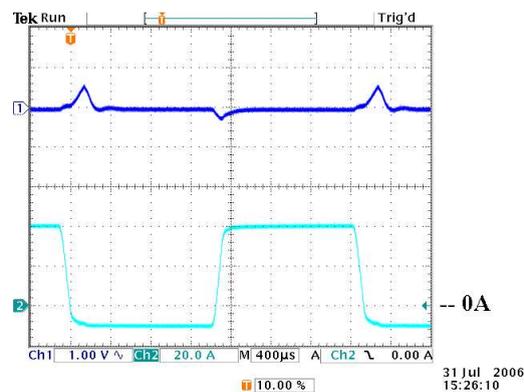


Fig. 5
 Dynamic reaction of power sink
 Load current switches between positive and
 negative

Fast Down Programming & Automotive

Test Systems require a test-time as short as possible. For each new item to be tested the voltage often has to be programmed down to zero. A normal power supply has a problem because it cannot quickly discharge the output capacitor C_o . The circuit in fig. 6 shows that only the load can discharge C_o .

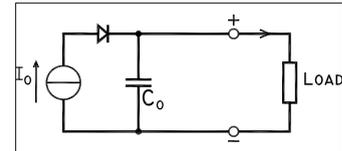


Fig. 6
Simplified output circuit
Normal power supply

A Power Sink as in fig. 7 will make it possible to do fast down-programming at light or no-load conditions. See fig. 8 and 9 to compare the results. Also for generating fast simulation voltages, like the battery voltage of a starting car (ISO7637), a Power Sink is indispensable.

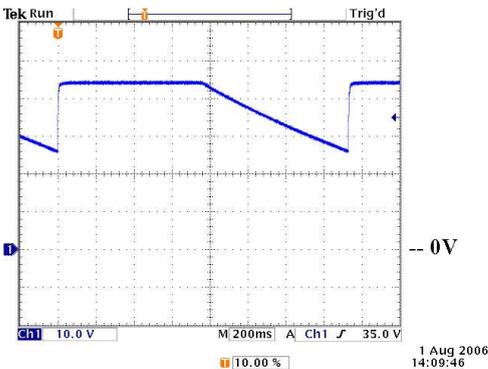


Fig. 8
Down programming at no load
Normal power supply
Voltage falls very slowly

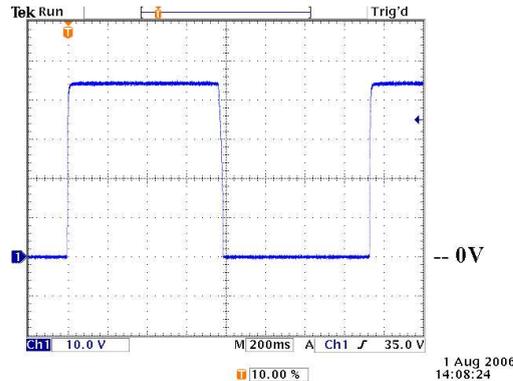


Fig. 9
Down programming at no load
Power sink equipped power supply
Short fall-time

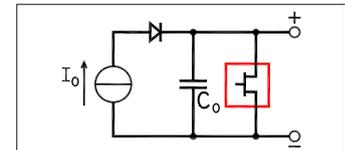


Fig. 7
Simplified output circuit
Power sink equipped power

Delta Elektronika Power Sinks

See table below for available Delta Elektronika Power Supplies with Power Sink option. All Power Sinks have electronically limited peak power and maximum current. The module shuts down in case of thermal overload (the unit itself continues operation). The overload condition is indicated with a LED on the front panel and with a status output.

SM700 - series Power Sink Peak Power / Maximum current	SM1540-D option P140 70W / 18A	SM7020-D option P141 70W / 18A	-	-	-
SM800 - series Power Sink * NEW NEW Peak Power / Maximum current	SM7.5-80 option P245 140W / 36A	SM18-50 option P246 140W / 36A	SM70-AR-24 option P247 140W / 25A	SM400-AR-4 option P248 140W / 5A	-
SM1500 - series Power Sink Peak Power / Maximum current	SM15-100 option P202 200W / 40A	SM35-45 option P203 200W / 40A	SM52-30 option P204 200W / 30A	SM52-AR-60 option P205 200W / 40A	SM70-22 option P206 200W / 30A
SM3000 - series Power Sink Peak Power / Maximum current	SM15-200D option P127 300W / 70A	SM30-100D option P128 300W / 70A	SM45-70D option P129 300W / 70A	SM70-45D option P130 300W / 45A	-
SM6000 - series Power Sink ** NEW NEW Peak Power / Maximum current	SM15-400 option P230 700W / 140A	SM30-200 option P231 700W / 140A	SM45-140 option P232 700W / 140A	SM60-100 option P233 700W / 100A	SM70-90 option P234 700W / 100A

* = available mid 2007 ** = available first quarter 2007



SM52-AR-60, 1500W power supply from Delta Elektronika, with optional Power Sink