

Using a Network and Impedance Analyzer to Evaluate 13.56 MHz RFID Tags and Readers/Writers

Application Note

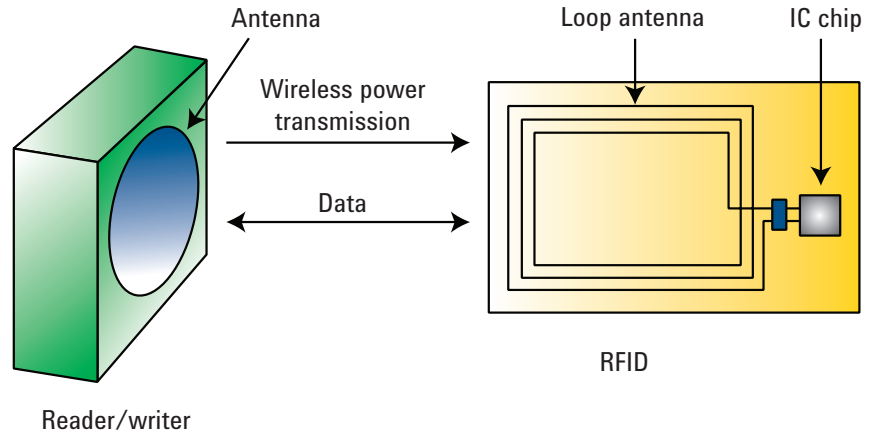


Figure 1. Simplified RFID system

Introduction

RFIDs, also called non-contact IC cards or ID tags, are devices that make it possible to detect the presence of objects and verify their identification without contacting them. RFIDs have been used since the 1980's but initially their use was limited to maritime transports, traffic information systems, and other special applications. Since the middle of 1990's, RFIDs have been miniaturized at an accelerated rate and they are now widely used. Currently, a number of standards exist that define the frequencies, communication methods, and purposes of RFIDs. This document gives an overview of how to evaluate the electrical characteristics of mass-produced 13.56 MHz RFID tags and readers/writers and their components.

Overview of an RFID

Figure 1 shows a simplified RFID system. The loop antenna in the reader/writer communicates with the loop antenna in the RFID tag; these are electromagnetically coupled. The reader/writer outputs RF signals, which are received by the RFID tag via its loop antenna. The RFID tag gains power by detecting DC signals through a detector circuit integrated in its IC chip. This power is used to drive the IC chip.

Typically, data communications between readers/writers and RFID tags use ASK modulation at a frequency of 13.56 MHz.



Evaluating RFID Tags

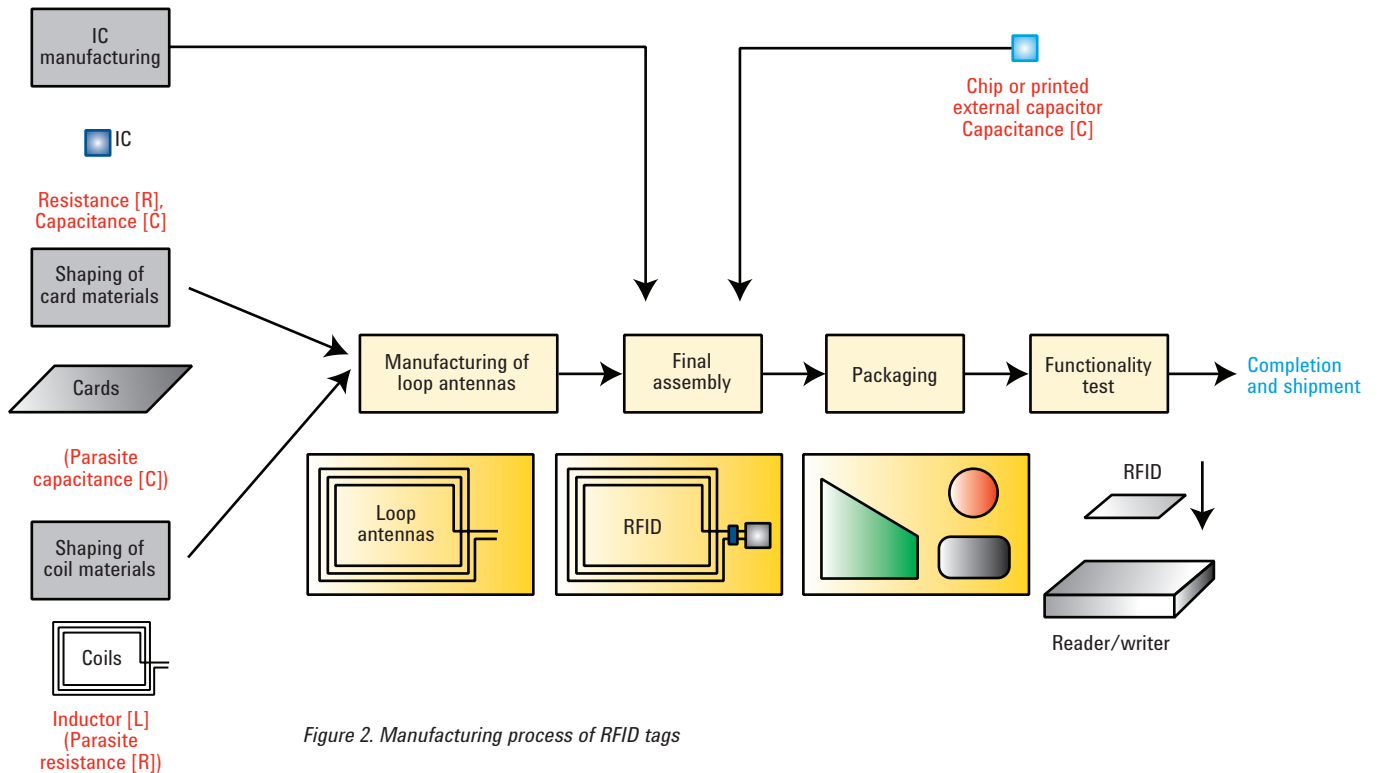


Figure 2. Manufacturing process of RFID tags

Figure 2 shows a typical manufacturing process of card type RFID tags. This process involves printing or otherwise forming a loop antenna on the card and subsequently placing an IC chip and chip capacitor on the same card. Printing may also be used to form the capacitor on the card. Finally, the tag is appropriately packaged and tested before shipping.

Figure 3 is a circuit diagram which represents a completed RFID tag. Basically, an RFID tag consists of an L-C-R parallel circuit (where “L” stands for a loop antenna, “C” for a chip capacitor, and “R” for an IC chip). The resonant frequency of an RFID tag, f_0 , is given by the expression $1/(2\pi\sqrt{LC})$. If an RFID tag has a resonant frequency close to 13.56 MHz, then the RFID tag is considered to communicate well with a reader/writer. It is very important to verify that the completed tag in its entirety resonates at 13.56 MHz.

Also, measuring the characteristics of L and C component parts will help improve the yield of completed RFID tags.

Another consideration is the sharpness of resonance (communication bandwidth), which is determined by the R value of the IC chip or the parasitic resistance, “R”, of the loop antenna. An excessively high sharpness of resonance makes

communications difficult when the modulation signal bandwidth is wide; on the other hand, an excessively low sharpness of resonance results in worsened communication distance characteristics. It is important to measure the resonance characteristics of the completed tag in its entirety, and measuring these resistance values on a part by part basis will help improve the communication performance of the RFID tag.

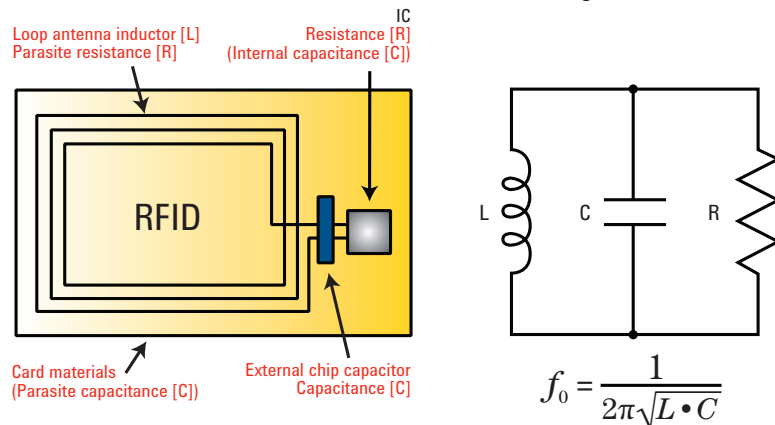


Figure 3. RFID tag components and its equivalent circuit

Component-Level Measurements

Agilent solution - impedance measurement instruments




4294A precision impedance analyzer + 42941A impedance probe kit

E5061B ENA network analyzer


E5061B-3L5 LF-RF network analyzer with option 005

E5072A ENA network analyzer

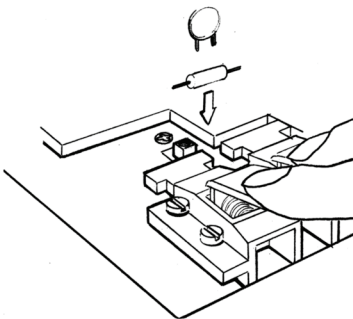
Agilent solution - impedance measurement test fixtures



For axial-lead components

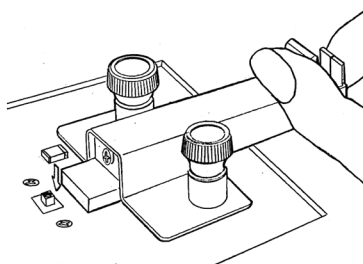


For SMD components

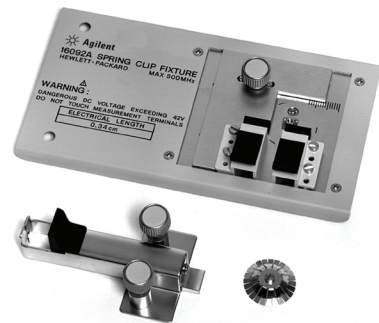

Choose an appropriate test fixture along with the DUT dimension

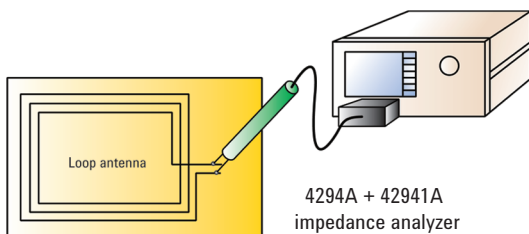Agilent solution - impedance measurement probes




E5061B-3L5/005 + SMA cable + 42941-6002 pin probe

4294A + 42941A impedance analyzer or



42941A impedance probe kit for 4294A

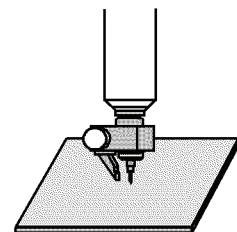


pin probe (42941-60002) for either 4395A or network analyzers

Figure 4. Recommended instruments and accessories

Basic components of L, C, and R make up an RFID tag as well as the RF portion of a reader/writer. The 4294A impedance analyzer is an optimum choice for measuring the electrical characteristics of these components.

You may also want to use the E5061B-3L5 LF-RF network analyzer with option 005 impedance analysis function. If you do not need the wide impedance measurement range provided by an impedance analyzer you can use a network analyzer instead.

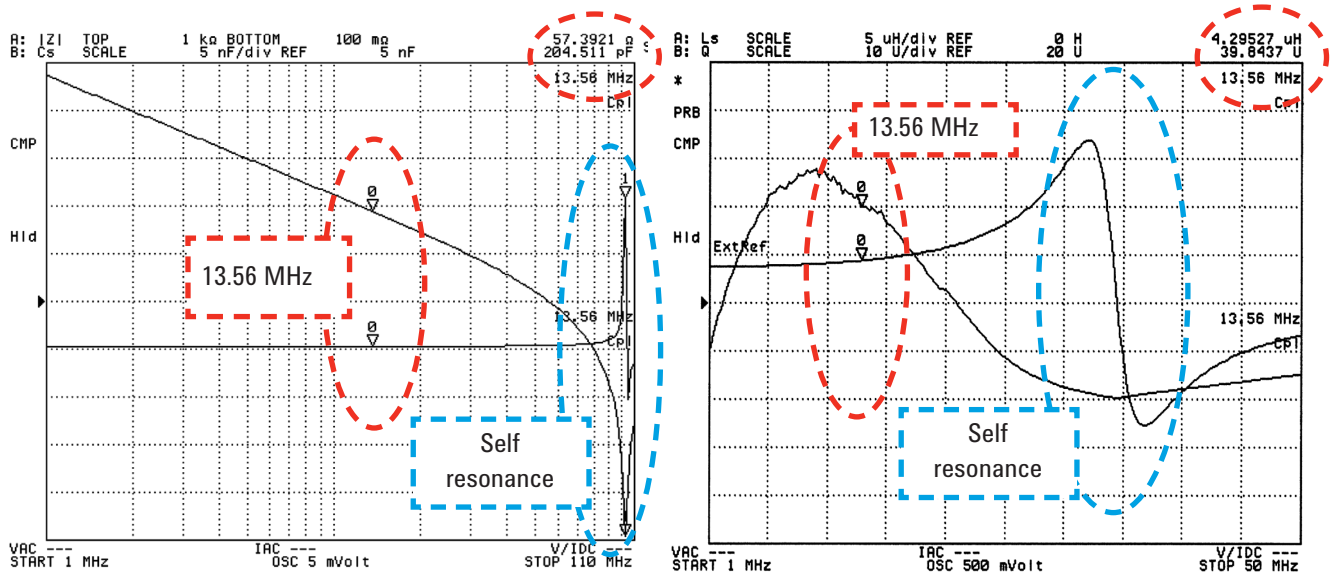RFID tags do not have coaxial connectors, instead, many of their components have electrodes or lead terminals. Therefore, you should use a test fixture that matches the shape of the tag to connect the RFID tag under test to the analyzer. If the RFID tag has a loop antenna formed on the card, you should use a probe to connect the tag to the analyzer.



Example: Chip capacitor characteristics measured with the 4294A

Example: Loop antenna characteristics measured with the 4294A

Figure 5. Examples of measurements

Figure 5 shows examples of measurements carried out on a chip capacitor and a loop antenna. The two graphs indicate that the chip capacitor and loop antenna resonate at approximately 100 MHz and 30 MHz, respectively.

Each of these components can only be used at or below the resonant frequencies indicated. Also, the results obtained at 13.56 MHz for these components are:
 C = approximately 204 pF and
 L = approximately 4.3 uH. These values determine the resonant frequencies.

After testing each component, you can use a probe to measure the resonance characteristics of the entire RFID tag complete with all its components.

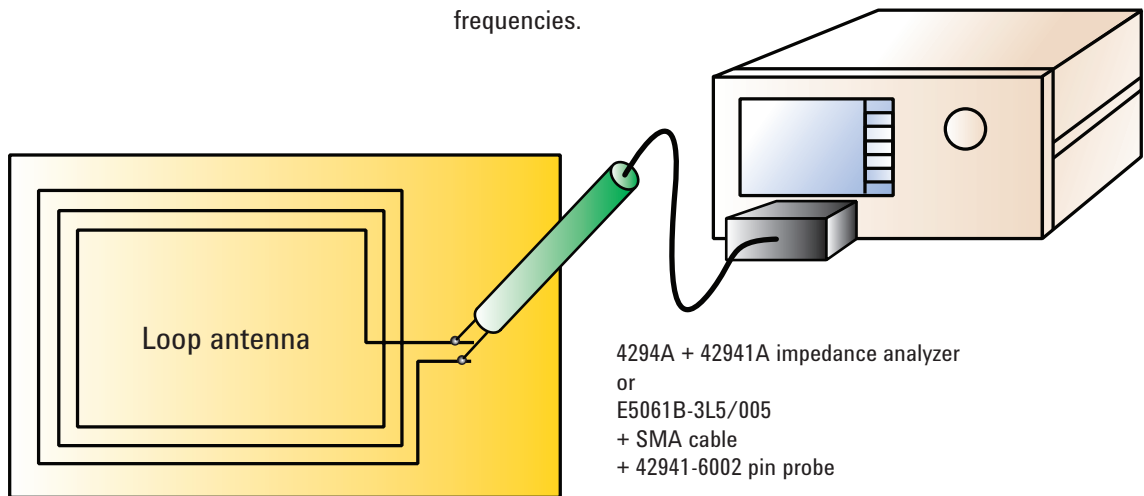


Figure 6. RFID measurement with impedance probe

Non-Contact Measurements of Resonant Frequencies

Once an RFID tag is packaged, you cannot test it with a probe. You can, however, use a non-contact measuring method. In this method you hold an RFID tag in front of a loop antenna connected to an analyzer. This allows you to measure the resonant frequency of an RFID tag without having to disassemble the RFID tag. Non-contact measurements are typically carried out with a network analyzer. The resonant peak is generally evaluated by measuring the negative peak of the reflection coefficient S_{11} or the positive peak of the impedance real part R with the non-contacting measurement configuration. In some case, the non-contacting resonant peak evaluation is performed with the S_{21} transmission measurement.

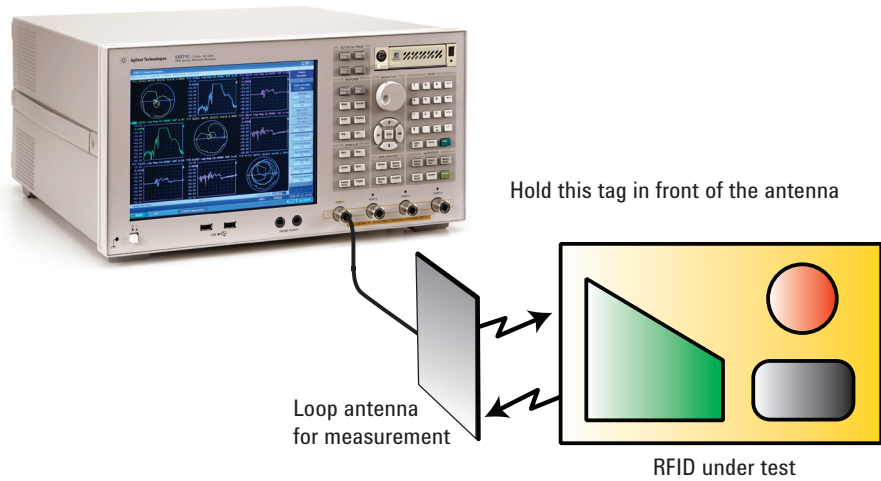


Figure 7. Non-contact measurements of resonant frequencies

Up to +20 dBm Source Power

The resonance characteristics of RFID tags often change depending on the RF power transmitted from the loop antenna, and it is desired that the network analyzer can provide high source power level up to nearly +20 dBm, which is not available with most of conventional network analyzers. The E5072A network analyzer is an optimum choice for this purpose.

The E5072A delivers source power level up to +20 dBm in frequency range of 300 kHz to 1 GHz. This enables you to perform high-power S_{11} and impedance measurements for RFIDs even without using an external booster amplifier. Not just S_{11} , the impedance $R-X$ can be measured by using the impedance conversion function (Z:Reflection). To measure S_{11} or $R-X$ by applying the high power up to +20 dBm, it is recommended to connect 6 dB attenuators to the

direct access port of the reference and test receivers (RCVR R1 IN and RCVR A IN) as shown in figure 8, so that the receivers operate in the linear region. This is critical especially when measuring impedance because the S_{11} measurement error due to the receiver compression can be significantly expanded when it is converted to impedance.

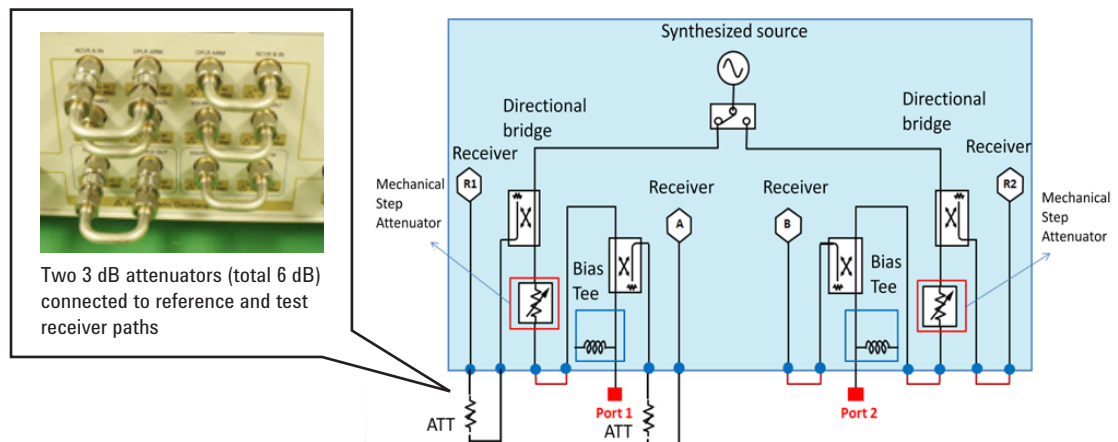


Figure 8. High power configuration of ENA network analyzer

Evaluating a Reader/Writer

Figure 9 is a simplified circuit diagram of an RFID reader/writer. The impedance of the power amplifier contained in a reader/writer should match that of the loop antenna so that the power amplifier can effectively transmit the power to the loop antenna. When the power amplifier's output impedance (Z_{pa}) is $R-jX$, you should adjust the loop antenna's impedance (Z_{in}) to $R+jX$. A typical setting is: $Z_{pa}=Z_{in}=50\Omega$.

The goal is to determine the capacitors values by adjusting values on both $C1s$ and $C2p$ to achieve impedance matching. You should connect capacitors to the loop antenna in serial or parallel, and adjust the capacitance values of these capacitors so that impedance matching is achieved. It is common practice to use an analyzer or simulator program in Smith Chart mode while measuring and adjusting the capacitance values of these capacitors.

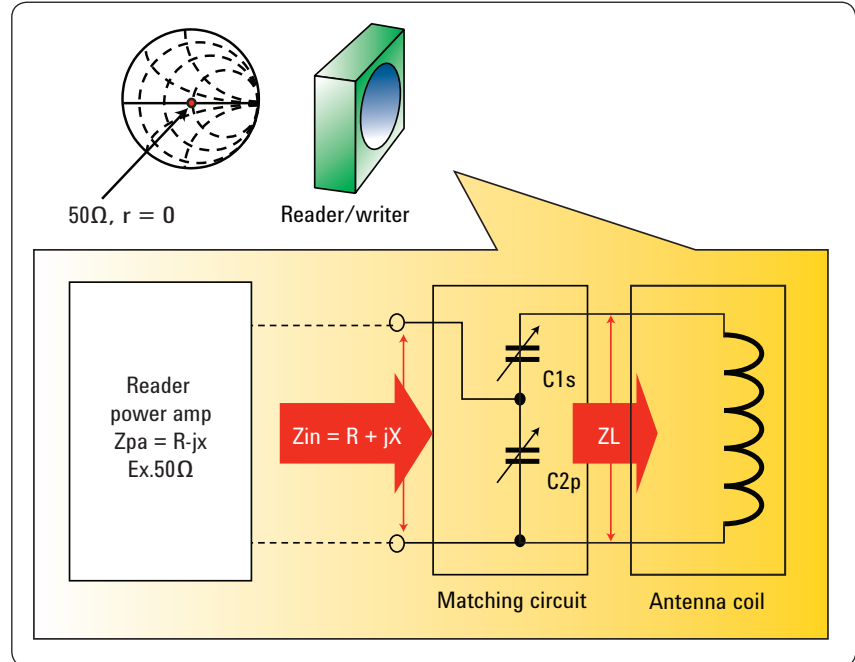


Figure 9 Simplified circuit diagram of an RFID reader/writer

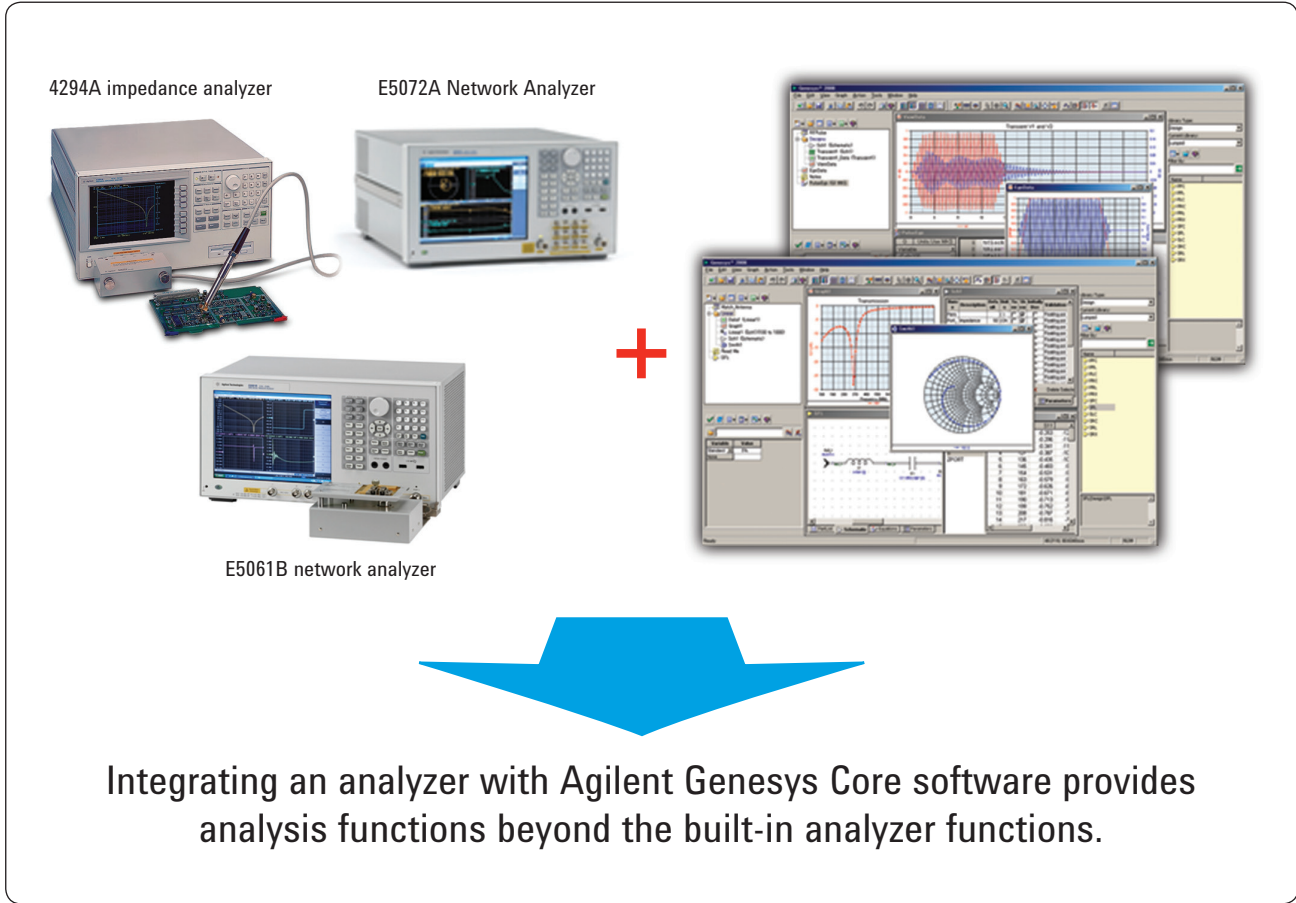


Figure 10. Design integration with Genesys

When your desired analysis is not available on your analyzer, you can use an inexpensive software simulation program called Genesys Core. Easily perform various types of measurement analysis by transferring measurement results to Genesys Core installed on a PC. For example, the 4294A impedance analyzer is not able to display a Smith chart, but you can generate one by just transferring measurement results to Genesys Core.

Note: The E5061B and E5072A analyzers come with built-in Smith Chart mode.

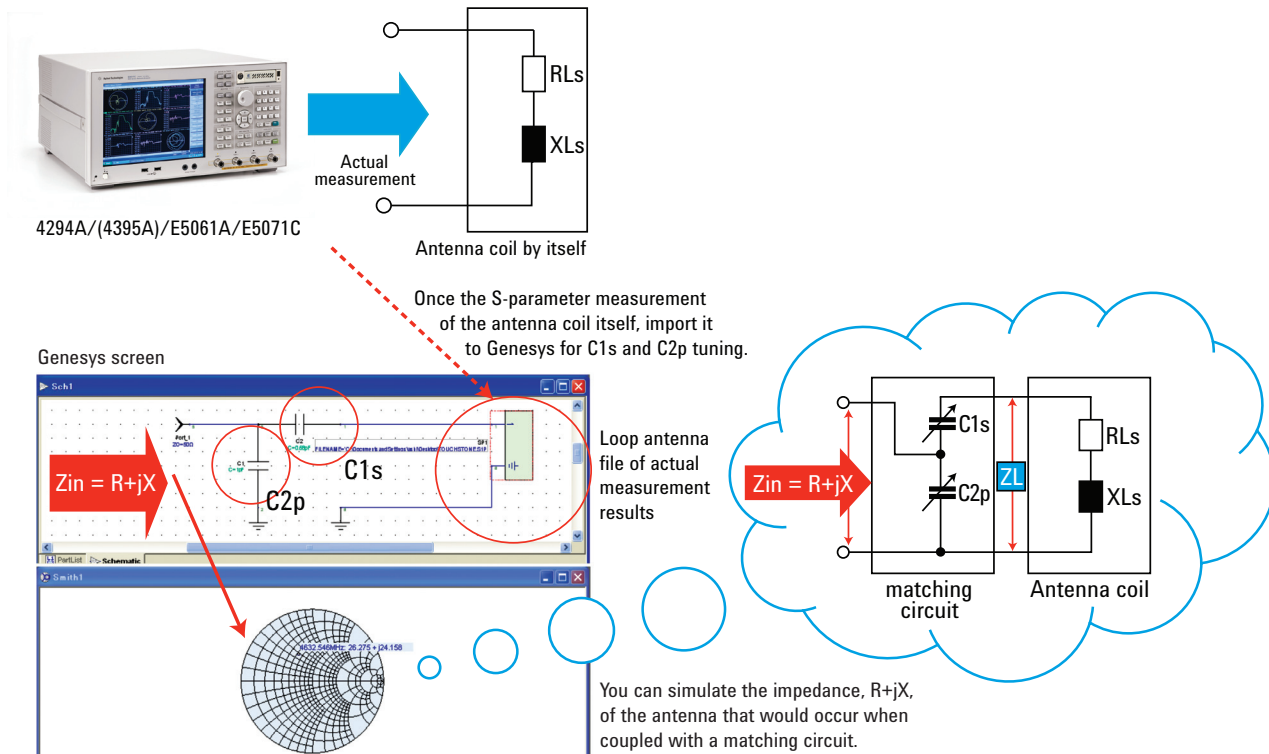


Figure 11. Matching circuit simulation using Genesys

For example, suppose you measure the characteristics of a loop antenna without a matching circuit using your analyzer. You can then transfer the measurement results to Genesys to simulate how the loop antenna would behave when coupled with a certain matching circuit. Thus the simulator program allows you to

estimate what characteristics will be obtained with each of possible circuit configuration without having to create different matching circuits by repeatedly rebuilding the actual circuit. By combining an impedance analyzer with Genesys, you can also perform different types of analysis on the electrical characteristics of RFID tags and readers/writers.

Selection Guide Summary

Table 1 show the summary of RFID application and recommend product model.

	Hand-probing loop antenna impedance measurement	Non-contacting RFID resonance measurement	Non-contact RFID resonance measurement with high-power	Reader/writer matching evaluation
4294A impedance analyzer (40 Hz to 110 MHz)	Yes (Provides very high accuracy.)	No	No	No
E5061B-115/215/135/235 50 ohm RF options (100 k to 1.5/3 GHz)	No	Yes (The best solution for manufacturing tests due to affordable prices.)	No	Yes
E5061B-3L5 & 005 LF-RF option with Z-analysis function (5 Hz to 3 GHz)	Yes	Yes	No	Yes
E5072A (30 k to 4.5/8.5 GHz)	No	Yes	Yes (Provides up to 20 dBm source power.)	Yes

Related literature

Non-Contact measurement method of 13.56 MHz RFID using the ENA/ENA-L Application Note, 5990-3443EN

Genesys Software

<http://eesof.tm.agilent.com/products/genesys>



Agilent Email Updates

www.agilent.com/find/emailupdates

Get the latest information on the products and applications you select.



www.lxistandard.org

LAN eXtensions for Instruments puts the power of Ethernet and the Web inside your test systems. Agilent is a founding member of the LXI consortium.

Agilent Channel Partners

www.agilent.com/find/channelpartners

Get the best of both worlds: Agilent's measurement expertise and product breadth, combined with channel partner convenience.



Agilent Advantage Services is committed to your success throughout your equipment's lifetime. To keep you competitive, we continually invest in tools and processes that speed up calibration and repair and reduce your cost of ownership. You can also use Infoline Web Services to manage equipment and services more effectively. By sharing our measurement and service expertise, we help you create the products that change our world.

www.agilent.com/find/advantageservices



www.agilent.com/quality

www.agilent.com
www.agilent.com/find/ENA

For more information on Agilent Technologies' products, applications or services, please contact your local Agilent office. The complete list is available at:

www.agilent.com/find/contactus

Americas

Canada	(877) 894 4414
Brazil	(11) 4197 3600
Mexico	01800 5064 800
United States	(800) 829 4444

Asia Pacific

Australia	1 800 629 485
China	800 810 0189
Hong Kong	800 938 693
India	1 800 112 929
Japan	0120 (421) 345
Korea	080 769 0800
Malaysia	1 800 888 848
Singapore	1 800 375 8100
Taiwan	0800 047 866
Other AP Countries	(65) 375 8100

Europe & Middle East

Belgium	32 (0) 2 404 93 40
Denmark	45 45 80 12 15
Finland	358 (0) 10 855 2100
France	0825 010 700*
	*0.125 €/minute
Germany	49 (0) 7031 464 6333
Ireland	1890 924 204
Israel	972-3-9288-504/544
Italy	39 02 92 60 8484
Netherlands	31 (0) 20 547 2111
Spain	34 (91) 631 3300
Sweden	0200-88 22 55
United Kingdom	44 (0) 118 927 6201

For other unlisted countries:

www.agilent.com/find/contactus

Revised: January 6, 2012

Product specifications and descriptions in this document subject to change without notice.

© Agilent Technologies, Inc. 2012
Published in USA, February 8, 2012
5990-3442EN



Agilent Technologies