

The most general uniform linear transmission line has four primary descriptive constants:

1. The loop resistance per unit length, R .
2. The loop inductance per unit length, L .
3. The shunt conductance per unit length, G .
4. The shunt capacitance per unit length, C .

If there is a voltage e between conductors and it is changing at a rate $\frac{\partial e}{\partial t}$ there will be a shunt current di_s in a length dx given by $di_s = (Ge + C \frac{\partial e}{\partial t}) dx$.

This current is robbed from the current entering the element dx . Hence for the current, i , in the line we have

$$\frac{\partial i}{\partial x} = - \frac{\partial i_s}{\partial x} = - (Ge + C \frac{\partial e}{\partial t}) \quad (1)$$

Similarly, the current i in the line, changing at a rate $\frac{\partial i}{\partial t}$ causes a series voltage de_s in the length dx given by

$$de_s = (Ri + L \frac{\partial i}{\partial t}) dx.$$

The voltage at the output of dx is the input voltage to dx less this series voltage. Thus for the voltage, e , between conductors we have

$$\frac{\partial e}{\partial x} = - \frac{\partial e_s}{\partial x} = - (Ri + L \frac{\partial i}{\partial t}) \quad (2)$$

By differentiating (1) and (2) and substituting we find:

$$\frac{\partial^2 e}{\partial x^2} = LC \frac{\partial^2 e}{\partial t^2} + (RC + LG) \frac{\partial e}{\partial t} + RGe \quad (3)$$

$$\frac{\partial^2 i}{\partial x^2} = LC \frac{\partial^2 i}{\partial t^2} + (RC + LG) \frac{\partial i}{\partial t} + RGi \quad (4)$$

Equations (3) and (4) are one dimensional wave equations the direct general solution of which is difficult. However, two cases admit simple solutions:

- a) The "distortionless" case, where $\frac{R}{L} = \frac{G}{C}$
- b) The "harmonic" case, where the excitation is sinusoidal.

The harmonic solution then permits complete specific solutions since the spectrum of the wave can be found at any point on the line if the input spectrum is known, and the spectrum defines the time function. However, let us first consider the "distortionless" case (a).

- a) (3) and (4) are of the same form, so let's just talk about (3). The general solution of (3) under the condition $\frac{R}{L} = \frac{G}{C}$ is:

$$e = A e^{-\alpha x} f(x-vt) + B e^{\alpha x} f(x+vt) \quad (5)$$

where $\alpha = \sqrt{RG}$, $v = \frac{1}{\sqrt{LC}}$, and A and B are arbitrary. This solution can be verified by substitution.

What does (5) say? The first term represents a wave traveling to the right (x increasing) at a velocity v and dying out at a rate determined by α , but without changes in shape. Similarly, the second term represents a wave traveling to the left (x decreasing) at a velocity v , and also dying out at a rate determined by α , and also without change of shape. Hence the name "distortionless" for this case. Since the wave shape doesn't change, the spectrum amplitude merely decreases with distance equally for all frequencies; i. e., the line attenuation is independent of frequency, the phase shift linear.

Associated with each of these voltage waves is a current wave of the same shape, i. e.:

$$i = C e^{-\alpha x} f(x-vt) + D e^{\alpha x} f(x+vt). \quad (6)$$

Substitution in (1) and (2) will reveal that

$$\frac{A}{C} = -\frac{B}{D} = \sqrt{\frac{L}{C}} \quad \left(= \sqrt{\frac{R}{G}} \right) \quad (7)$$

Thus, for the distortionless line the ratio of instantaneous voltage to instantaneous current for any wave is a resistance $Z_0 = \sqrt{\frac{L}{C}}$.

- b) Things aren't too different in the harmonic case.

$$\begin{array}{l} \text{We let} \\ e = E e^{j\omega t} \\ i = I e^{j\omega t} \end{array} \quad \text{so that} \quad \begin{array}{l} \frac{de}{dt} = (j\omega)e \\ \frac{di}{dt} = (j\omega)i \end{array}$$

And get

$$\frac{dE}{dx} = (R + j\omega L) I \quad (8)$$

$$\frac{dI}{dx} = (G + j\omega C) E \quad (9)$$

$$\frac{d^2E}{dx^2} = [RG + j\omega(RC + LG) - \omega^2LC] E \quad (10)$$

$$\frac{d^2I}{dx^2} = [RG + j\omega(RC + LG) - \omega^2LC] I \quad (11)$$

We then find as the solutions:

$$E = A e^{-\gamma x} + B e^{\gamma x} \quad (12)$$

$$I = C e^{-\gamma x} + D e^{\gamma x} \quad (13)$$

Where

$$\begin{aligned} \gamma^2 &= [RG + j\omega(RC + LG) - \omega^2LC] \\ &= (R + j\omega L)(G + j\omega C). \end{aligned}$$

That is

$$\begin{aligned} \gamma &= \sqrt{(R + j\omega L)(G + j\omega C)} \\ &= \alpha + j\beta \end{aligned} \quad (14)$$

γ is called the propagation constant. It tells what happens to the amplitude and phase of a sinusoid as it propagates down the line. It consists of two parts: α , the attenuation constant (nepers/unit length)

β , the phase constant (radians/unit length).

Thus:

$$e^{-\gamma x} = e^{-\alpha x - j\beta x} = e^{-\alpha x} \times e^{-j\beta x}$$

\uparrow \uparrow
 Attenuation Phase shift
 with distance with distance.

In general, α and β are very complicated expressions of R, L, C, G ; but for the case $\frac{R}{L} = \frac{G}{C}$, we have

$$\alpha = \sqrt{RG}, \quad \beta = \omega \sqrt{LC};$$

while for the "low loss" case: $R \ll \omega L, G \ll \omega C$, we have

$$\left. \begin{aligned} \beta &\approx \omega \sqrt{LC} \\ \alpha &\approx \frac{1}{2} \left[R \sqrt{\frac{C}{L}} + G \sqrt{\frac{L}{C}} \right] = \frac{1}{2} \left(\frac{R}{Z_0} + G Z_0 \right). \end{aligned} \right\} \quad (15)$$

Substitution of (12) and (13) in (8) and (9) shows that

$$\frac{A}{C} = -\frac{B}{D} = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = Z_c \quad (16)$$


Z_c is the characteristic impedance of the line. For the distortionless case $\frac{R}{L} = \frac{G}{C}$, we have

$$Z_c = \sqrt{\frac{L}{C}} = \sqrt{\frac{R}{G}} = Z_o$$

For the "low loss" case ($R \ll \omega L$, $G \ll \omega C$), we have

$$Z_c \approx \sqrt{\frac{L}{C}} \left[1 + j \frac{1}{2} \left(\frac{R}{\omega L} - \frac{G}{\omega C} \right) \right] \approx \sqrt{\frac{L}{C}} = Z_o \quad (17)$$

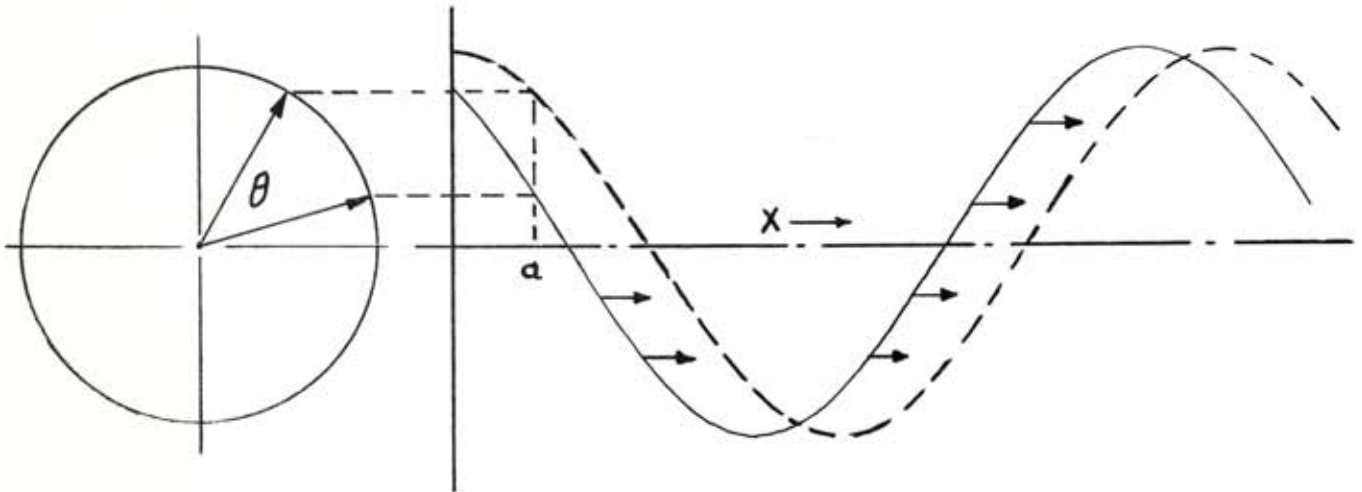If the transmission line extends from $x=0$ to $x=\infty$ and the excitation is by a generator at $x=0$, the solution will consist of only the first term in (5) and (6) or in (12) and (13). With no loss the voltage conditions in the harmonic case are as shown below.



The solid line shows the wave now ($t = 0$).

The dotted line shows the wave later ($t = t_0$).

The voltage at $x = 0$ is the generator voltage.

The voltage now (solid) at $x = a$ is the generator voltage at the earlier time $t = -t_0$.

The voltage later (dotted) at $x = a$ is the generator voltage now. As we move from $x = 0$ to $x = a$ the voltage we see is exactly as if we had stayed at $x = 0$ and the generator had dropped back in phase by an angle $-\theta$. If we move a distance λ , $-\theta = 2\pi$. Hence

$$-\theta = \frac{2\pi}{\lambda} x = \frac{2\pi f}{v} x = \frac{\omega}{v} x.$$

But $v = \frac{1}{\sqrt{LC}}$, so $-\theta = \omega \sqrt{LC} x = \beta x$.

If we look at any point on the infinite lossless line we will see the generator voltage delayed by an angle $-\theta = \beta x$. That is

$$E = E(0) e^{j\theta} = E(0) e^{-j\beta x}.$$

When the line is lossy a similar picture is obtained. The difference is that as we advance down the line the voltage is the generator voltage delayed by angle $-\theta$, and decreased in amplitude by a factor $e^{-\alpha x}$. That is

$$E(x) = E(0) e^{-\alpha x} e^{-j\beta x} = E(0) e^{-\alpha x}.$$


As a result we can represent the voltage (or current) for a wave traveling to the right as a vector which rotates clockwise uniformly and decreases exponentially in length with increasing x . The locus of the tip of this vector is a logarithmic spiral

$$E = E(0) e^{\left(\frac{\alpha}{\beta}\right)\theta}$$

where θ is measured counterclockwise. The ratio $\frac{\alpha}{\beta} \approx \frac{1}{\omega} \sqrt{\frac{RG}{LC}}$ is a measure of the lossiness of the line. For $\frac{\alpha}{\beta} \ll 1$. The locus is nearly circular and the loss per wavelength is small.


Similarly a wave traveling to the left can be represented as a vector which rotates clockwise and decreases exponentially with decreasing x .

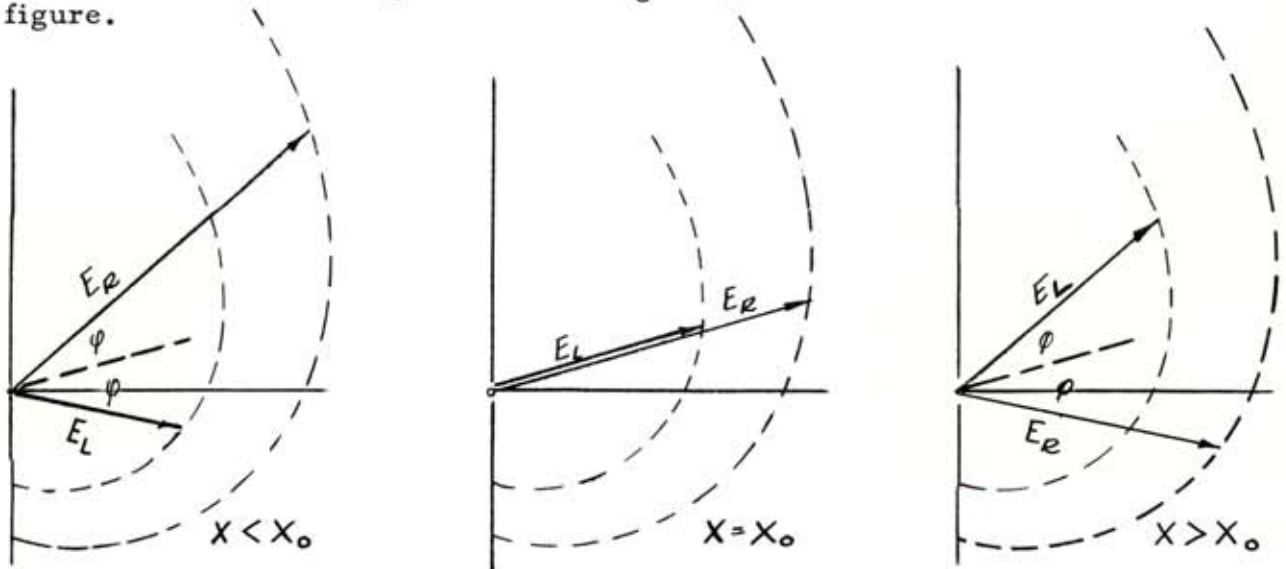Thus consider two voltages which happen to be in phase at $x = x_0$, as shown in the center figure below. If one voltage E_R is from a wave propagating to the right, the other E_L from a wave propagating to the left, then at $x < x_0$ the picture will be as shown in the left figure. For $x > x_0$ the picture will be as shown in the right figure.




Termination, Reflection, Standing Waves

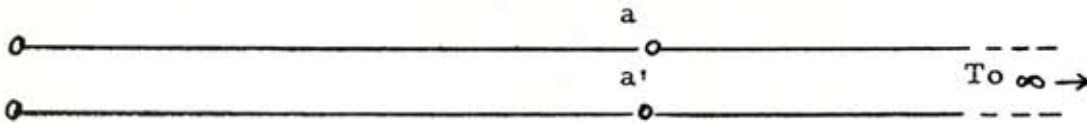Consider any two points a-a' on the conductors of an infinite line.



To a wave incident on these points from the left, the line to the right merely looks like an impedance Z_0 connecting a and a'. If we chop the line off at a-a' and connect an impedance Z_0 across a-a' then so far as the line to the left is concerned, Z_0 just looks like more line. Waves coming from the left will be totally absorbed by the connected impedance. We say such a line is "terminated in a matching impedance", or "matched", or simply "terminated". Regardless of length, such a line looks infinite to the generator which sees the impedance Z_0 .

If we now terminate the line in an impedance Z_L , different from Z_0 , a reflected wave is produced. To see how this happens, first consider the relative polarities of the incident and reflected voltages and currents. If the voltage on a conductor is positive and the current in it at the same instant is to the right, the wave is traveling to the right. If either E or I is of opposite sign, the wave is to the left. Hence the following polarities and senses are consistent for our case:

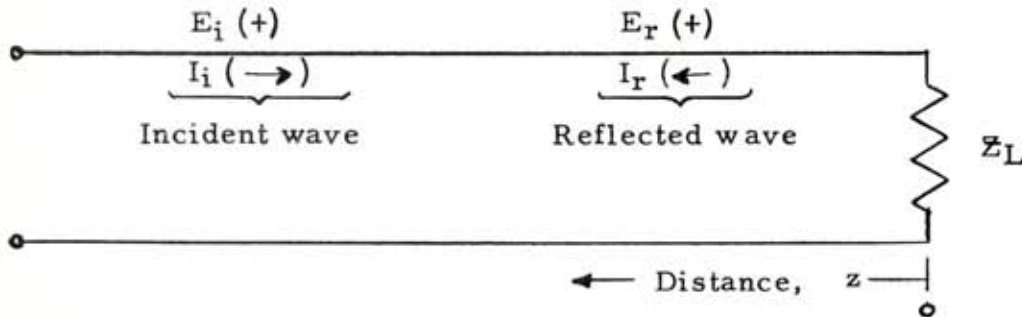

For convenience, let us measure distance from the load. Then at the load we have

$$E_L = E(0) = E_i(0) + E_r(0)$$

$$I_L = I(0) = I_i(0) - I_r(0)$$

But $Z_L = \frac{E_L}{I_L}$ while $\frac{E_i}{I_i} = \frac{E_r}{I_r} = Z_0$. Hence

$$Z_L = \frac{E_i(0) + E_r(0)}{I_i(0) - I_r(0)} = Z_0 \frac{1 + \frac{E_r(0)}{E_i(0)}}{1 - \frac{I_r(0)}{I_i(0)}}$$

$$\frac{Z_L}{Z_0} = \frac{1 + \frac{E_r(0)}{E_i(0)}}{1 - \frac{I_r(0)}{I_i(0)}} \quad (18)$$

If we now let $\rho = \frac{E_r(0)}{E_i(0)} = \frac{I_r(0)}{I_i(0)}$ we have

$$\frac{Z_L}{Z_0} = \frac{1 + \rho}{1 - \rho} \quad (19)$$

Or, turning things around

$$\rho = \frac{\frac{Z_L}{Z_0} - 1}{\frac{Z_L}{Z_0} + 1} = \frac{Z_L - Z_0}{Z_L + Z_0} \quad (20)$$

ρ is called the reflection coefficient. It is the (complex) ratio of the amplitude of the reflected wave to the amplitude of the incident wave. We shall represent its magnitude by r . This is $\rho = r e^{j\phi}$.

The voltage at the load is

$$E_L = (1 + \rho) E_i(0) = \frac{2Z_L}{Z_L + Z_0} E_i(0)$$

The current at the load is

$$I_L = (1 - \rho) I_i(0) = \frac{2Z_0}{Z_L + Z_0} I_i(0) = \frac{2E_i(0)}{Z_L + Z_0}$$

The ratio of reflected power to incident power is given by

$$\frac{P_r}{P_i} = |\rho|^2 = r^2$$

The return loss is this ratio expressed in db. Thus

$$\begin{aligned} \text{Return Loss} &= -10 \log \frac{P_r}{P_i} \\ &= -20 \log r. \end{aligned}$$

The remainder of the power is absorbed by the load so we have

$$\frac{P_L}{P_i} = 1 - r^2$$

The reflection loss is the ratio expressed in db. Thus

$$\text{Reflection Loss} = 10 \log (1-r^2) \approx 4.343r^2 \text{ for } r \ll 1.$$

If there is reflection at the receiving end of the line, the reflected wave amplitude (current or voltage) will add vectorially to the incident wave amplitude. If there is no loss, the incident and reflected vectors merely rotate in opposite directions as we move along the line. At a point where E_i and E_r are in phase the total voltage will have the magnitude $(1+r)E_i$. As we move toward the generator a distance Δz from this point E_i will advance in phase an amount $\beta\Delta z$ while E_r will retard the same amount. The total angle between them is thus $2\beta\Delta z$. When

$$2\beta\Delta z = \pi$$

$$\Delta z = \frac{\pi}{2\beta} = \frac{\pi V}{2\omega} = \frac{V}{4f} = \frac{\lambda}{4}$$

The two vectors will be opposed and the total voltage will have the magnitude $(1-r)E_i$. The action repeats cyclically, maxima and minima occurring alternately every quarter wavelength. The ratio of maximum to minimum is called the standing wave ratio. Evidently:

$$\text{SWR} = \frac{1+r}{1-r} \quad (21)$$

By comparing (19) and (21) we see that a resistance termination produces a standing wave ratio which is its normalized value or the reciprocal. Thus a 50^ω line terminated in a resistance of 100^ω (or 25^ω) will have a 2 to 1 SWR.

Equation (21) may be inverted to give

$$r = \frac{\text{SWR} - 1}{\text{SWR} + 1} \quad (22)$$

Standing wave measurements thus indicate (1) the frequency and (2) the degree of match at the load.

Input Impedance of Mis-terminated Lines

The impedance looking into a line of length l terminated in Z_L may be written merely by adapting equation (18) to the point $z = l$, rather than $z = 0$.

Thus

$$\frac{Z}{Z_0} = \frac{1 + \frac{E_r(l)}{E_i(l)}}{1 - \frac{I_r(l)}{I_i(l)}}$$

Now

$$\frac{E_r(l)}{E_i(l)} = \frac{I_r(l)}{I_i(l)} = \frac{E_r(0)}{E_i(0)} e^{-2\gamma l} = \rho e^{-2\gamma l}$$

So

$$\frac{Z}{Z_0} = \frac{1 + \rho e^{-2\gamma l}}{1 - \rho e^{-2\gamma l}} \quad (23)$$

Now substitute $\rho e^{j\phi}$ for ρ and let $\theta = \phi - 2\beta l$ and we find

$$\frac{Z}{Z_0} = \frac{1 + r e^{-2\alpha l} e^{j\theta}}{1 - r e^{-2\alpha l} e^{j\theta}} \quad (24)$$

For lossless lines $\alpha = 0$ and (24) becomes

$$\frac{Z}{Z_0} = \frac{R}{Z_0} + j \frac{X}{Z_0} = \frac{1 + r e^{j\theta}}{1 - r e^{j\theta}} \quad (25)$$

Equation (25) is the equation of the Smith Chart. The equation is of the form

$$w = \frac{1 + z}{1 - z}$$

where $w = u + jv$, and $z = x + jy$ are complex numbers. Such an equation is known as a bilinear transformation and is characterized by the fact that lines of constant u or constant v plot as circles in the z -plane. Since in our case $r = |z| \leq 1$, the entire plot lies within the unit circle $r = 1$.

The Smith Chart

We see from equation (25) that the Smith Chart is essentially a plot of normalized resistance and reactance as a function of magnitude and phase of reflection coefficient. In fact:

1. Distance from the center of the chart is proportional to magnitude of reflection coefficient, r .

2. Angles about the center of the chart (read on the peripheral angle scale) are the angle of the reflection coefficient ϕ , if the plane is that of the load ($z = 0$); or the effective angle, θ , if the plane is $z = l$.
3. The lines of constant normalized resistance $\left(\frac{R}{Z_0}\right)$ and reactance $\left(\frac{X}{Z_0}\right)$ form a set of curvilinear coordinates from which the impedance corresponding to any magnitude and phase of reflection coefficient may be read; or vice versa.

Now the convenient thing about the Smith Chart is this: In a lossless line, as we see from eq. (25), the input impedance change with line length is equivalent to a change in the phase of the reflection coefficient only. Hence as we change line length the input impedance will describe a circular path about the center of the Smith Chart. Since

$$\Delta\theta = 2\beta\Delta l = \frac{2\omega}{v} \Delta l = 4\pi \frac{\Delta l}{\lambda}$$

changing l by $\frac{\lambda}{2}$ takes us completely around the circle. For convenience, a second angle scale calibrated in terms of fractions of a wavelength is provided around the periphery. With a Smith Chart you don't need tables of hyperbolic functions to compute transmission line problems; all you need is a ruler and compass. (In fact, you usually don't need the compass.) This sounds easy enough, let's try an example.

Example 1: A 50ω line is terminated in a resistance of 30ω in series with a capacitive reactance of 40ω .

- a) What is the reflection coefficient?
- b) What is the SWR?
- c) What is the input impedance if $l = 0.1\lambda$?
- d) What lengths of line make the input impedance resistive and what is the resistance?

Solution: $\frac{30 - j40}{50} = 0.6 - j0.8$ so we enter the chart at $\frac{R}{Z_0} = 0.6$,

$\frac{X}{Z_0} = 0.8$, marking point A.

- a) The distance of point to the center is 0.5. Radial line through A to angle scale shows $\phi = -90^\circ$. Thus $\rho = 0.5 \angle -90^\circ$
- b) Draw the circle of constant $r = 0.5$ through point A. This circle intersects the $\frac{X}{Z_0} = 0$ line on the $\frac{R}{Z_0} > 1$ side at $\frac{R}{Z_0} = 3$ (Point B). This is the SWR. (This is the $\frac{R}{Z_0}$ which would produce the same r as the actual load, and for $\frac{R}{Z_0} > 1$, $\frac{R}{Z_0} = \text{SWR}$).

- c) Radius through A intersects wavelength scale ("toward generator" scale) at 0.375λ . (This is just an arbitrary starting point. On fancy Smith charts, wavelength scale can be rotated to put index here.) Proceed 0.1λ toward generator - you're going away from load, aren't you? -- to 0.475 . Draw radius. Intersects circle (Point C) at $0.336 - j 0.144$ or $16.8 - j 7.2$ ohms.
- d) Impedance will be real at Points D and B. Takes $0.5\lambda - 0.375\lambda = \frac{\lambda}{8}$ to get to D from A. Another $\frac{\lambda}{4}$ to get to B. Resistance at D is $50 \times 0.333 \dots = 16.67$ ohms. Resistance at B is $50 \times 3 = 150\omega$.

Referring to equation (25) we see that changing θ by π inverts the expression. Thus points diametrically opposite each other on the Smith Chart are inverses of each other with respect to Z_0 , i.e. $\frac{Z_1}{Z_0} = \frac{Z_0}{Z_2}$ or $Z_1 Z_2 = Z_0^2$. This illustrates the impedance inverting property of a quarter wave (or $\frac{(2n-1)\lambda}{4}$) line, since it takes a quarter wavelength to go halfway around the chart. Further, since

$$\frac{Z_0}{Z} = \frac{Y}{Y_0}$$

the point diametrically opposite a given normalized impedance point is the normalized admittance representation. Thus the Smith Chart can be used equally well on an impedance or admittance basis. In the latter case one merely uses the $\frac{R}{Z_0}$ scale as $\frac{G}{Y_0}$ and the $\frac{X}{Z_0}$ scale as $\frac{B}{Y_0}$.


The voltage maxima along a line occur at the point where $\frac{Z}{Z_0}$ is greatest, i.e., where ρ is real and positive; the minima where $\frac{Z}{Z_0}$ is least, i.e., where ρ is real and negative. Thus the maxima are where the r-circle intersects the $\frac{X}{Z_0} = 0$ line where $\frac{R}{Z_0} > 1$ and the minima at the intersection where $\frac{R}{Z_0} < 1$.

A standing wave measurement suffices to determine the magnitude of the reflection coefficient, r , of an unknown load. To complete the picture the phase (referred to some reference plane) must also be found. This can be done by measuring the position of the minima of the SW pattern with the unknown, relative to their positions with a load having known reflection phase, and is usually carried out as follows:

1. Locate a voltage minimum with the actual load. (Any minimum near the middle of the slotted section will do.)

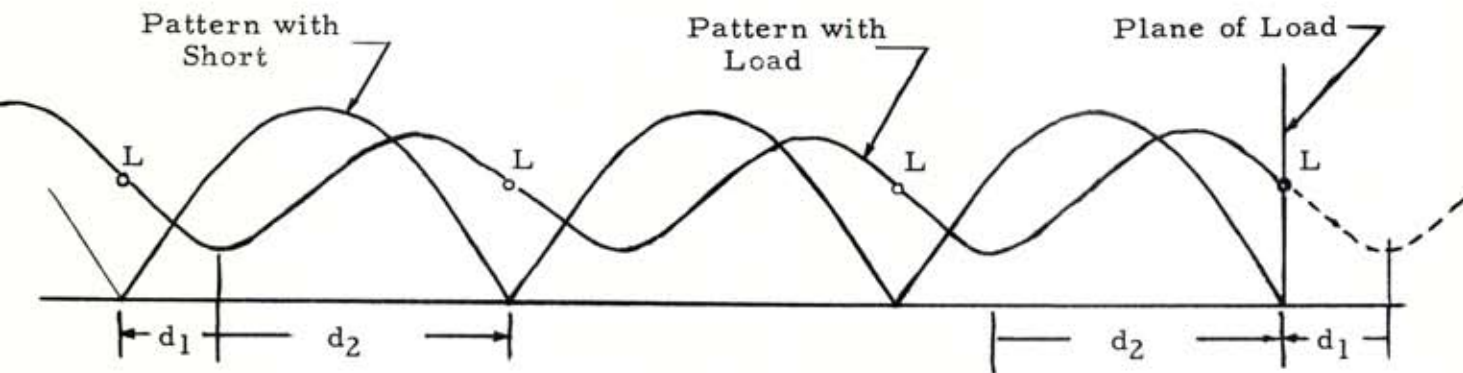2. Replace the load with short circuit.
3. Locate a nearby new null and express in wavelengths the distance you moved (toward generator or toward load) from the old minimum. Draw this radial line on the Smith Chart, using the wavelength scales (with their zeros opposite $\frac{Z}{Z_0} = 0$).
4. Draw the circle representing the measured SWR and read the impedance where it intersects the radial line.

The impedance so obtained is referred to the plane of the short. The reason the method works may be seen from the drawing below.



Input Impedance = Load Impedance at Points Marked "L".

Since the input impedance of the line is equal to the load impedance for a line any number of half wavelengths long, and since these half wavelength multiples occur at the nulls with a short, the input impedance will equal the load impedance either a distance d_1 toward the generator or a distance d_2 toward the load from the observed minimum. Now the input impedance at the observed minimum occurs on the $\frac{X}{Z_0} = 0$ line for $\frac{R}{Z_0} < 1$ on the chart. This happens to be the zero axis for the wavelength scale (as printed) so all we do is go toward the generator a distance d_1 on our r-circle or toward the load a distance d_2 . Since $d_1 + d_2 = \frac{\lambda}{2}$ we will end up at the same point on the chart.

Additional radial scales are often provided on the Smith Chart. Some of these and their uses are listed below:

1. Voltage or Current Limits

(Max. and Min.) These are scales of $\sqrt{\text{SWR}}$ and $\frac{1}{\sqrt{\text{SWR}}}$ respectively.

They are used to find the maximum and minimum voltages or currents on a line when the line impedance and load power are known, using the relations:

$$E_{\max} = \sqrt{P Z_0 (\text{SWR})} \quad I_{\max} = \sqrt{P(\text{SWR}) / Z_0}$$

$$E_{\min} = \sqrt{P Z_0 / (\text{SWR})} \quad I_{\min} = \sqrt{P / Z_0 (\text{SWR})}$$

2. Voltage or Current Ratios -

(Max. and Min. and db) These are scales of SWR and $20 \log \text{SWR}$.

3. Reflection Loss (db) -

This is a scale of $-10 \log (1 - r^2)$, i.e. the load mismatch loss in db.

4. S. W. Loss Coefficient -

This is a scale of $\frac{1 + r^2}{1 - r^2}$ which is the factor by which the actual power dissipation in the line is increased by the SWR.

5. "1 db Steps" (or 1/2 Return Loss) -

This is a scale which can be used to compute or to take account of line loss as explained below. If each step is taken as 2 db, starting with the outside mark as 0 db, the scale becomes a scale of return loss ($-10 \log r^2$).

Use of Smith Chart with Lossy Lines

So far our discussion of the Smith Chart has assumed a lossless line. The locus of input impedance as line length varies is then a circle, as we have seen.

Referring to equation (24) we see that if $\alpha \neq 0$ then the effective reflection coefficient not only changes in angle (θ) but also decreases exponentially in magnitude as we progress toward the generator. The Smith Chart can still be used to convert between input and load impedances, but the loci along which impedances move with l are now logarithmic spirals, not circles. However, if the attenuation per wavelength is known the process is not difficult.

The losses are most simply taken into account with the aid of an additional radial scale marked off in 1 db steps, the use of which is best illustrated by example. Suppose the line in Example 1 had a loss of 5 db per wavelength. Then the answer to part (c) would be obtained as follows.

1. We would first pretend the line had no loss and obtain point C, as before.
2. Since we have moved away from the load, the effect of line loss will be to make the input impedance nearer the characteristic impedance than would be the case without loss. The total intervening attenuation has been 0.1 wavelength x 5 db per wavelength or 0.5 db. Accordingly, we move inward radially from point C by 0.5 db on the 1 db steps scale to obtain point E. This point is the normalized input impedance with the lossy line.

Since the 1 db steps are farthest apart for $r \approx 1$, we see that corrections for loss will have the greatest effect on impedances when the SWR is high.

The attenuation of a lossy line can be determined by a measurement of SWR of shorted length of line. Since the reflection coefficient of the load is unity, the reflection coefficient at $z = l$ will be $r = e^{-2\alpha l}$. Hence we have

$$\begin{aligned} \alpha l &= -\frac{1}{2} \ln r = \frac{1}{2} \ln \left(\frac{\text{SWR} + 1}{\text{SWR} - 1} \right) \quad (\text{nepers}) \\ &= -4.343 \log r = 4.343 \log \left(\frac{\text{SWR} + 1}{\text{SWR} - 1} \right) \quad (\text{db}) \end{aligned}$$

This quantity (in db) can be read directly from the "1 db steps" radial scale as the number of db from $r = 1$ ($\text{SWR} = \infty$) to the point opposite the measured r (or SWR).

The load need not be a short, though this is best. With less than unity reflection at the load one takes the difference on the db steps scale between the point for r (or SWR) as measured at the load and the point for r (or SWR) as measured through the line.

The measurement of attenuation using the "db steps" scale is not very accurate for very low or very high attenuation. However, with a slotted line, the expression

$$\alpha l = 4.343 \log \left(\frac{\text{SWR} + 1}{\text{SWR} - 1} \right) \quad (\text{db})$$

is quite accurate for low attenuations. For high attenuations a transmission measurement is preferable.

ELECTRONIC INSTRUMENTATION SALES AND SERVICE

UNITED STATES

ALABAMA

P.O. Box 4207
2003 Byrd Spring Road S.W.
Huntsville 35802
Tel: (205) 881-4591
TWX: 810-726-2204

ARIZONA

3009 North Scottsdale Road
Scottsdale 85251
Tel: (602) 945-7601
TWX: 910-950-1282

232 South Tucson Boulevard
Tucson 85716
Tel: (602) 623-2564
TWX: 910-952-1162

CALIFORNIA

3939 Lankershim Boulevard
North Hollywood 91604
Tel: (213) 877-1282
TWX: 910-499-2170

1101 Embarcadero Road
Palo Alto 94303
Tel: (415) 327-6500
TWX: 910-373-1280

2591 Carlsbad Avenue
Sacramento 95821
Tel: (916) 482-1463
TWX: 910-367-2092

1055 Shafter Street
San Diego 92106
Tel: (714) 223-8103
TWX: 910-335-2000

COLORADO

7965 East Prentice
Englewood 80110
Tel: (303) 771-3455
TWX: 910-935-0705

CONNECTICUT

508 Tolland Street
East Hartford 06108
Tel: (203) 289-9394
TWX: 710-425-3416

111 East Avenue
Norwalk 06851
Tel: (203) 853-1251
TWX: 710-468-3750

DELAWARE

3941 Kennett Pike
Wilmington 19807
Tel: (302) 655-6161
TWX: 510-666-2214

FLORIDA

Suite 106
9999 N.E. 2nd Avenue
Miami Shores 33138
Tel: (305) 758-3626
TWX: 810-848-7262

P.O. Box 20007
Herndon Station 32814
621 Commonwealth Avenue
Orlando
Tel: (305) 841-3970
TWX: 810-850-0113

P.O. Box 8128
Madeira Beach 33708
410 150th Avenue
St. Petersburg
Tel: (813) 391-0211
TWX: 810-863-0366

GEORGIA

P.O. Box 28224
2340 Interstate Parkway
Atlanta 30328
Tel: (404) 436-6181
TWX: 810-766-4890

ILLINOIS

5500 Howard Street
Skokie 60076
Tel: (312) 677-0400
TWX: 910-223-3613

INDIANA
4002 Meadows Drive
Indianapolis 46205
Tel: (317) 546-4891
TWX: 810-341-3263

LOUISIANA

391 Grand Avenue
1942 Williams Boulevard
Kenner 70062
Tel: (504) 721-6201
TWX: 810-955-5524

MARYLAND

6707 Whitestone Road
Baltimore 21207
Tel: (301) 944-5400
TWX: 710-862-0850

P.O. Box 727
Twinbrook Station 20851
12303 Twinbrook Parkway
Rockville
Tel: (301) 427-7560
TWX: 810-928-9684

MASSACHUSETTS

Middlesex Turnpike
Burlington 01803
Tel: (617) 272-9000
TWX: 710-332-0382

MICHIGAN

24315 Northwestern Highway
Southfield 48075
Tel: (313) 353-9100
TWX: 810-232-1532

MINNESOTA

2459 University Avenue
St. Paul 55114
Tel: (612) 645-9461
TWX: 910-563-3734

MISSOURI

9208 Wyoming Place
Kansas City 64114
Tel: (816) 333-2445
TWX: 910-771-2087

2812 South Brentwood Blvd.
St. Louis 63144
Tel: (314) 644-0220
TWX: 910-760-1670

NEW JERSEY

391 Grand Avenue
Englewood 07631
Tel: (201) 567-3933
TWX: 710-991-9707

NEW MEXICO

P.O. Box 8366
Station C 87108
6501 Lomas Boulevard N.E.
Albuquerque
Tel: (505) 255-5586
TWX: 910-989-1665

156 Wyatt Drive
Las Cruces 88001
Tel: (505) 526-2485
TWX: 910-983-0550

NEW YORK

1702 Central Avenue
Albany 12205
Tel: (518) 869-8462

1219 Campville Road
Endicott 13760
Tel: (607) 754-0050
TWX: 510-252-0890

236 East 75th Street
New York 10021
Tel: (212) 879-2023
TWX: 710-581-4376

82 Washington Street
Poughkeepsie 12601
Tel: (914) 454-7330
TWX: 510-248-0012

39 Saginaw Drive
Rochester 14623
Tel: (716) 473-9500
TWX: 510-253-5981

1025 Northern Boulevard
Roslyn, Long Island 11576
Tel: (516) 869-8400
TWX: 510-223-0811

5858 East Molloy Road
Syracuse 13211
Tel: (315) 454-2486
TWX: 710-541-0482

NORTH CAROLINA

P.O. Box 5187
1923 North Main Street
High Point 27262
Tel: (919) 884-6873
TWX: 510-926-1516

OHIO

5579 Pearl Road
Cleveland 44129
Tel: (216) 884-9209
TWX: 810-421-8500

2460 South Dixie Drive
Dayton 45439
Tel: (513) 298-0351
TWX: 810-459-1925

OREGON

Westhills Mall, Suite 158
4475 S.W. Scholls Ferry Road
Portland 97225
Tel: (503) 292-9171
TWX: 910-464-6103

PENNSYLVANIA

2500 Moss Side Boulevard
Monroeville 15146
Tel: (412) 271-0724
TWX: 710-797-3650

144 Elizabeth Street
West Conshohocken 19428
Tel: (215) 248-1600, 828-6200
TWX: 510-660-8715

TEXAS

P.O. Box 7166
3605 Inwood Road
Dallas 75209
Tel: (214) 357-1881
TWX: 910-861-4081

P.O. Box 22813
4242 Richmond Avenue
Houston 77027
Tel: (713) 667-2407
TWX: 910-881-2645

GOVERNMENT CONTRACT OFFICE

225 Billy Mitchell Road
San Antonio 78226
Tel: (512) 434-4171
TWX: 910-871-1170

UTAH

2890 South Main Street
Salt Lake City 84115
Tel: (801) 486-8166
TWX: 910-925-5661

VIRGINIA

P.O. Box 6514
2111 Spencer Road
Richmond 23230
Tel: (703) 282-5451
TWX: 910-956-0157

WASHINGTON

11656 N.E. Eighth Street
Bellevue 98004
Tel: (206) 454-3971
TWX: 910-443-2303

FOR AREAS NOT LISTED, CONTACT: Hewlett-Packard; 1501 Page Mill Road, Palo Alto, California 94304; Tel: (415) 326-7000; TWX: 910-373-1267; Telex: 34-8461

CANADA

ALBERTA

10010 - 105th Street
Edmonton
Tel: (403) 424-0718
TWX: 610-831-2431

BRITISH COLUMBIA

Hewlett-Packard (Canada) Ltd.
2184 West Broadway
Vancouver
Tel: (604) 738-7520
TWX: 610-922-5050

NOVA SCOTIA

7001 Mumford Road
Suite 356
Halifax
Tel: (902) 455-0511
TWX: 610-271-4482

ONTARIO

Hewlett-Packard (Canada) Ltd.
880 Lady Ellen Place
Ottawa 3
Tel: (613) 722-4223
TWX: 610-562-1952

Hewlett-Packard (Canada) Ltd.

1415 Lawrence Avenue West
Toronto
Tel: (416) 249-9196
TWX: 610-492-2382

QUEBEC

Hewlett-Packard (Canada) Ltd.
275 Hymus Boulevard
Pointe Claire
Tel: (514) 697-4232
TWX: 610-422-3022
Telex: 01-2819

FOR AREAS NOT LISTED, CONTACT: Hewlett-Packard Inter-Americas; 1501 Page Mill Road, Palo Alto, Calif. 94304; Tel: (415) 326-7000; TWX: 910-373-1267; Telex: 034-8461; Cable: HEWPACK Palo Alto

CENTRAL AND SOUTH AMERICA

ARGENTINA

Mauricio A. Suárez
Telecomunicaciones
Carlos Calvo 224
Buenos Aires
Tel: 30-6312, 34-9087
Cable: TELEPILOT Buenos Aires

CHILE

Héctor Calcagni
Casilla 13942
Santiago
Tel: 490.505, 393.119

COLOMBIA

Instrumentacion
Henrik A. Langebaek & Cia. Ltda.
Cra. 7A N° 48-51/59
Apartado Aereo 6287
Bogota, 1 D.E.
Tel: 45-78-06, 45-55-46
Cable: AARIS Bogota

COSTA RICA

Lic. Alfredo Gallegos Guardián
Apartado 3243
San José
Tel: 21-86-13
Cable: GALGUR San José

ECUADOR

Laboratorios de Radio-Ingeniería
Calle Guayaquil 1246
Post Office Box 3199
Quito
Tel: 12496
Cable: HORVATH Quito

EL SALVADOR

Electrónica
27 Avenida Norte 1133
Apartado Postal 1589
San Salvador
Tel: 25-74-50
Cable: ELECTRONICA
San Salvador

GUATEMALA

Olander Associates Latin America
Apartado 1226
7a. Calle, 0-22, Zona 1
Guatemala City
Tel: 22812
Cable: OLALA Guatemala City

MEXICO

Hewlett-Packard Mexicana,
S.A. de C.V.
Eugenia 408, Dept. 1
Mexico 12, D.F.
Tel: 43-03-79

NICARAGUA

Roberto Terán G.
Edificio Terán
Apartado Postal 689
Managua
Tel: 3451, 3452
Cable: ROTERAN Managua

PANAMA

Electrónica Balboa, S.A.
P.O. Box 4929
Ave. Manuel Espinosa No. 13-50
Bldg. Alina
Panama City
Tel: 30833
Cable: ELECTRON Panama City

PERU

Fernando Ezeta B.
Av. Petit Thouars 4719
Miraflores
Casilla 3061
Lima
Tel: 50346
Cable: FEPERU Lima

PUERTO RICO

San Juan Electronics, Inc.
P.O. Box 5167
Ponce de León 150, Stop 3
Puerta de Tierra Santa
San Juan 00906
Tel: (809) 725-3342
Cable: SATRONICS San Juan

URUGUAY

Pablo Ferrando
S.A. Comercial e Industrial
Avenida Italia 2877
Casilla de Correo 370
Montevideo
Tel: 40-3102
Cable: RADIUM Montevideo

VENEZUELA

Citec, C.A.
Edif. Arisan-Of. #4
Avda. Francisco de Miranda
Apartado del Este 10934 Chacaito
Caracas
Tel: 71.88.05
Cable: CITECAL Caracas

FOR AREAS NOT LISTED, CONTACT: Hewlett-Packard Inter-Americas; 1501 Page Mill Road, Palo Alto, Calif. 94304; Tel: (415) 326-7000; TWX: 910-373-1267; Telex: 034-8461; Cable: HEWPACK Palo Alto

ELECTRONIC INSTRUMENTATION SALES AND SERVICE

EUROPE

AUSTRIA
Unilabor H.m.b.H.
Wissenschaftliche Instrumente
Rummelhardtgasse 6/3
P.O. Box 33
Vienna IX/71
Tel: 425 181
Cable: LABORINSTRUMENT
Vienna

BELGIUM
Hewlett-Packard Benelux S.A.
20-24 rue de l'Hôpital
Brussels
Tel: 11 22 20
Cable: PALOBEN Brussels

DENMARK
Tage Olsen A/S
Rønnegade 1
Copenhagen 0
Tel: 29 48 00
Cable: TOCOPEN Copenhagen

FINLAND
INTO O/Y
Meritalinkatu 11
P.O. Box 10153
Helsinki 10
Tel: 51 133
Cable: INTO Helsinki

FRANCE
Hewlett-Packard France
2 rue Tête d'Or
Lyon, 6 - Rhône
Tel: 52 35 66
Hewlett-Packard France
150 Boulevard Massena
Paris 13e
Tel: 707 97 19
Cable: HEWPACK Paris

GERMANY
Hewlett-Packard Vertriebs-GmbH
Lietzenburger Strasse 30
1 Berlin W 30
Tel: 24 86 36

Hewlett-Packard Vertriebs-GmbH
Herrnberger Strasse 110
703 Bablingen, Württemberg
Tel: 07031-6971
Cable: HEPAG Bablingen

Hewlett-Packard Vertriebs-GmbH
Achenbachstrasse 15
4 Düsseldorf 1
Tel: 68 52 58/59

Hewlett-Packard Vertriebs-GmbH
Kurfürstenstrasse 95
6 Frankfurt 50
Tel: 52 00 36
Cable: HEWPACKSA Frankfurt

Hewlett-Packard Vertriebs-GmbH
Beim Strohhause 26
2 Hamburg 1
Tel: 24 05 51/52
Cable: HEWPACKSA Hamburg

Hewlett-Packard Vertriebs-GmbH
Reginfriedstrasse 13
8 Munich 9
Tel: 69 51 21/22
Cable: HEWPACKSA Munich

GREECE
Kostos Karayannis
18, Ermou Street
Athens 126
Tel: 230 301
Cable: RAKAR Athens

IRELAND
Hewlett-Packard Ltd.
224 Bath Road
Slough, Bucks, England
Tel: Slough 28406-9, 29486-9
Cable: HEWPIE Slough

ITALY
Hewlett-Packard Italiana S.p.A.
Viale Lunigiana 46
Milan
Tel: 69 15 84
Cable: HEWPAKIT Milan

Hewlett-Packard Italiana S.p.A.
Palazzo Italia
Piazza Marconi 25
Rome - Eur
Tel: 591 2544
Cable: HEWPAKIT Rome

NETHERLANDS
Hewlett-Packard Benelux, N.V.
de Boelelaan 1043
Amsterdam, Z.2
Tel: 42 77 77
Cable: PALOBEN Amsterdam

NORWAY
Morgenstjerne & Co. A/S
Ingeniofirma
6 Wessels Gate
Oslo
Tel: 20 16 35
Cable: MOROF Oslo

PORTUGAL
Teleclra
Rua Rodrigo da Fonseca 103
P.O. Box 2531
Lisbon 1
Tel: 68 60 72
Cable: TELECLRA Lisbon

SPAIN
Ataio Ingenieros
Urgel, 259
Barcelona, 11
Tel: 230-69-88
Ataio Ingenieros
Enrique Larreta 12
Madrid, 16
Tel: 235 43 44
Cable: TELEATAIO Madrid

SWEDEN
HP Instrument AB
Hagakersgatan 7
Mölnådal
Tel: 031 - 27 68 00
HP Instrument AB
Centralvägen 28
Solna
Tel: 08 - 83 08 30
Cable: MEASUREMENTS
Stockholm

SWITZERLAND
HEWPAK AG
Zurcherstrasse
8952 Schlieren
Zurich
Tel: (051) 98 18 21
Cable: HEWPAKAG Zurich

TURKEY
Telekom Engineering Bureau
P.O. Box 376 - Galata
Istanbul
Tel: 49 40 40
Cable: TELEMATIK Istanbul

UNITED KINGDOM
Hewlett-Packard Ltd.
224 Bath Road
Slough, Bucks
Tel: Slough 28406-9, 29486-9
Cable: HEWPIE Slough

YUGOSLAVIA
Belram S.A.
83 avenue des Mimosas
Brussels 15, Belgium
Tel: 35 29 58
Cable: BELRAMEL Brussels

FOR AREAS NOT LISTED, CONTACT: Hewlett-Packard S.A.; 54 Route des Acacias; Geneva, Switzerland; Tel: (022) 42 81 50; Telex: 2.24.86; Cable: HEWPACKSA Geneva

AFRICA, ASIA, AUSTRALIA

AUSTRALIA
Hewlett-Packard Australia
Pty. Ltd.
22-26 Weir Street
Glen Iris, S. E. 6
Victoria
Tel: 20-1371 (4 lines)
Cable: HEWPAK Melbourne
Hewlett-Packard Australia
Pty. Ltd.
4 Grose Street
Glebe, New South Wales
Tel: 211-2235, 211-2888
Cable: HEWPAK Sydney

CEYLON
United Electricals Ltd.
P.O. Box 681
Yahala Building
Staples Street
Colombo 2
Tel: 5496
Cable: HOTPOINT Colombo

ETHIOPIA
African Salespower & Agency
Private Ltd., Co.
P. O. Box 718
Addis Ababa
Tel: 44090
Cable: ASACO Addisababa

HONG KONG
Schmidt & Co. (Hong Kong) Ltd.
P.O. Box 297
1511, Prince's Building
10, Chater Road
Hong Kong
Tel: 240168, 232735
Cable: SCHMIDTCO Hong Kong

INDIA
The Scientific Instrument
Co., Ltd.
6, Tej Bahadur Sapru Road
Allahabad 1
Tel: 2451
Cable: SICO Allahabad
The Scientific Instrument
Co., Ltd.
240, Dr. Dadabhai Naoroji Road
Bombay 1
Tel: 26-2642
Cable: SICO Bombay
The Scientific Instrument
Co., Ltd.
11, Esplanade East
Calcutta 1
Tel: 23-4129
Cable: SICO Calcutta
The Scientific Instrument Co., Ltd.
30, Mount Road
Madras 2
Tel: 86339
Cable: SICO Madras

The Scientific Instrument Co., Ltd.
B-7, Ajmeri Gate Extn.
New Delhi 1
Tel: 27-1053
Cable: SICO New Delhi

IRAN
Telecom, Ltd.
P. O. Box 1812
Teheran
Tel: 43850, 48111
Cable: BASCOM Teheran

ISRAEL
Electronics & Engineering
Div. of Motorola Israel Ltd.
16, Kremenski Street
Tel-Aviv
Tel: 35021/2/3
Cable: BASTEL Tel-Aviv

JAPAN
Yokogawa-Hewlett-Packard Ltd.
Shinhankyu Building
No. 8, Umeda
Kita-ku, Osaka City
Tel: 0726-23-1641
Yokogawa-Hewlett-Packard Ltd.
Ito Building
No. 59, Kotori-cho
Nakamura-ku, Nagoya City
Tel: 551-0215

Yokogawa-Hewlett-Packard Ltd.
Ohashi Building
No. 59, Ichome, Yoyogi
Shibuya-ku, Tokyo
Tel: 370-2281
Cable: YOKOHEWPAK Tokyo
Telex: 232-2034

KENYA
R. J. Tilbury Ltd.
P. O. Box 2754
Suite 517/518
Hotel Ambassador
Nairobi
Tel: 25670, 26803, 68206
Cable: ARJAYTEE Nairobi

KOREA
American Trading Co., Korea, Ltd.
Seoul P. O. Box 1103
112-35 Sokong-Dong
Jung-ku, Seoul
Tel: 3.7049, 3.7613
Cable: AMTRACO Seoul

LEBANON
Constantin E. Macridis
Clemenceau Street
Clemenceau Center
Beirut
Tel: 220846
Cable: ELECTRONUCLEAR Beirut

MALAYSIA
MECOMB Malaysia Ltd.
2 Lorong 13/6A
Section 13
Petaling Jaya, Selangor
Cable: MECOMB Kuala Lumpur

NEW ZEALAND
Sample Electronics (N.Z.) Ltd.
8 Matipo Street
Onehunga S.E. 5
Auckland
Tel: 667-356
Cable: ELPAS Auckland

PAKISTAN (EAST)
Mushko & Company, Ltd.
31, Jinnah Avenue
Dacca
Tel: 80058
Cable: COOPERATOR Dacca

PAKISTAN (WEST)
Mushko & Company, Ltd.
Oosman Chambers
Victoria Road
Karachi 3
Tel: 51027, 52927
Cable: COOPERATOR Karachi

SINGAPORE
Mechanical and Combustion
Engineering Company Ltd.
9, Jalan Kilang
Singapore, 3
Tel: 642361-3
Cable: MECOMB Singapore

SOUTH AFRICA
F. H. Flanter & Co. (Pty.), Ltd.
Rosella House
Buitencingle Street
Cape Town
Tel: 3-3817
Cable: AUTOPHONE Cape Town

F. H. Flanter & Co. (Pty.), Ltd.
104 Pharmacy House
80 Jorissen Street
Braamfontein, Johannesburg
Tel: 724-4172

TAIWAN
Hwa Sheng Electronic Co., Ltd.
P. O. Box 1558
21 Nanking West Road
Taipei
Tel: 46076, 45936
Cable: VICTRONIX Taipei

THAILAND
The International
Engineering Co., Ltd.
P. O. Box 39
614 Sukhumvit Road
Bangkok
Tel: 913460-1-2
Cable: GYSOM Bangkok

VIETNAM
Landis Brothers and Company,
Inc.
P.O. Box H-3
216 Hien-Vuong
Saigon
Tel: 20.805
Cable: LANBROCOMP Saigon

FOR AREAS NOT LISTED, CONTACT: Hewlett-Packard Export Marketing; 1501 Page Mill Road; Palo Alto, California 94304; Tel: (415) 326-7000; Telex: 034-8461; Cable: HEWPAK Palo Alto