



**Agilent Technologies**

**Increasing MMIC Yield  
with  
Advanced Statistical Design Methods**

**November 8, 2001**

*presented by:*


**Jack Sifri**

# Agenda

- **Initial Design Process of X-band LNA**
  - *X-band LNA Elements*
  - *Programmable Optimization*
  - *Yield Analysis*
- **Statistical Tools for Robustness**
  - *Yield Sensitivity Histograms*
  - *Sensitivity Analysis*
  - *Design of Experiments*
  - *Yield Optimization (Design Centering)*
- **Final LNA Design**



# MMIC Statistical Design Process

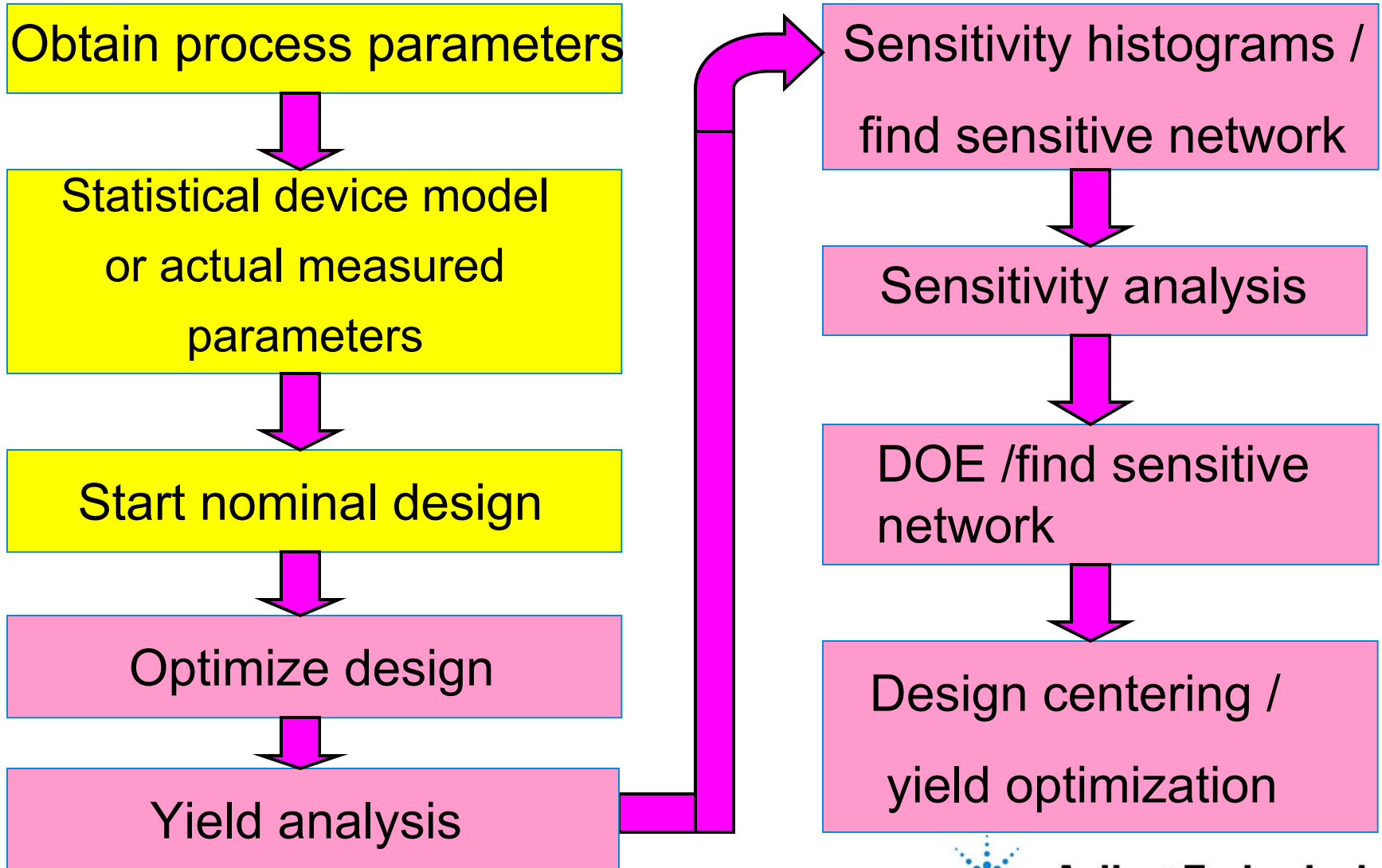


# X-Band LNA Specifications

|                                   |                      |
|-----------------------------------|----------------------|
| • <b>Center frequency (Fc)</b>    | <b>8 GHz</b>         |
| • <b>Bandwidth (20%)</b>          | <b>7.2 - 8.8 GHz</b> |
| • <b>Gain (S21)</b>               | <b>&gt; 14 dB</b>    |
| • <b>Noise figure (NF)</b>        | <b>&lt; 3 dB</b>     |
| • <b>Output return loss (S22)</b> | <b>&lt; -14 dB</b>   |




# X-Band LNA Top-Level Schematic

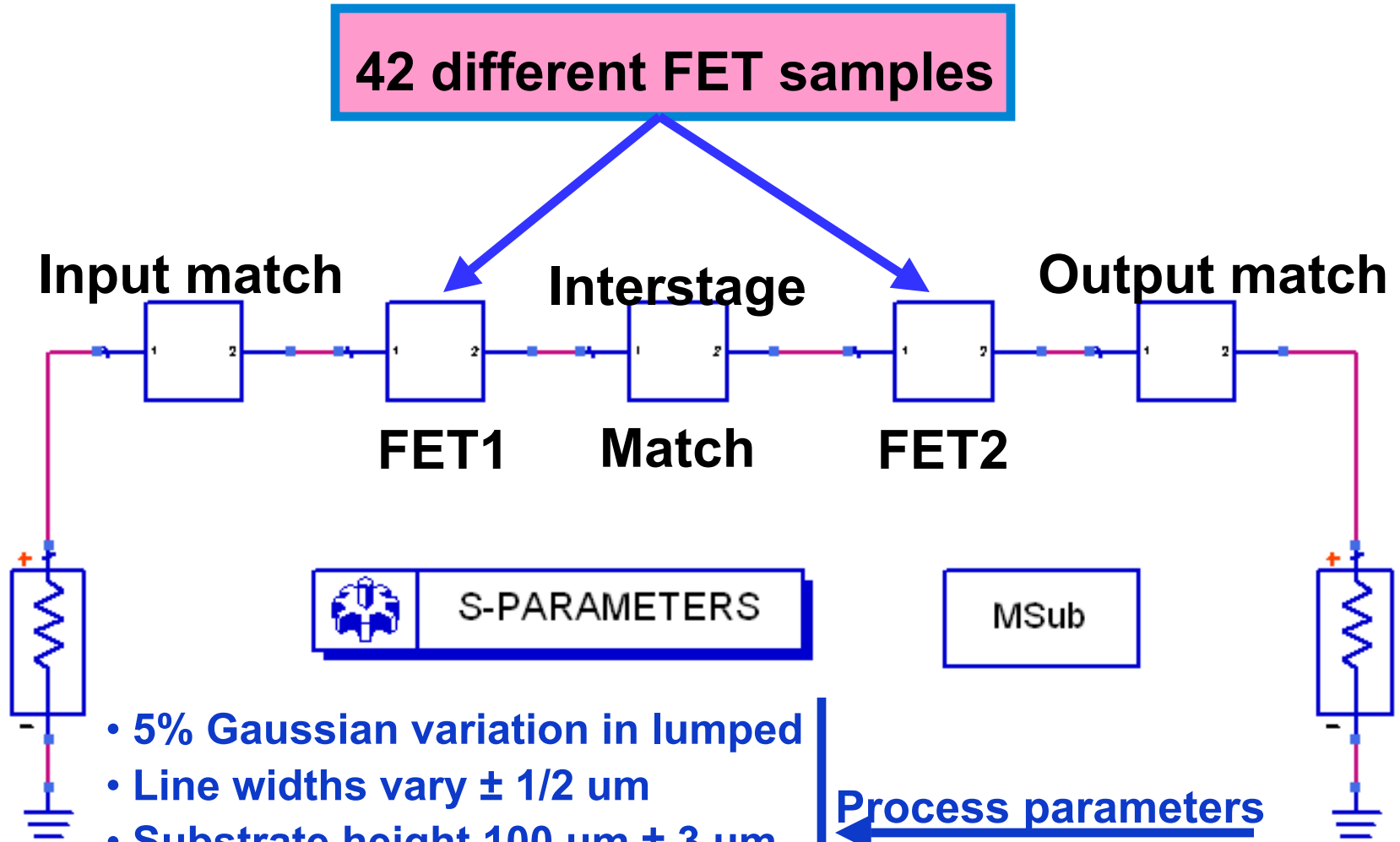

- 5% Gaussian variation in lumped
- Line widths vary  $\pm 1/2$   $\mu\text{m}$
- Substrate height  $100 \mu\text{m} \pm 3 \mu\text{m}$
- Substrate  $\epsilon_r$   $12.9 \pm 5\%$
- 42 FET samples




# Input Matching Network for Noise

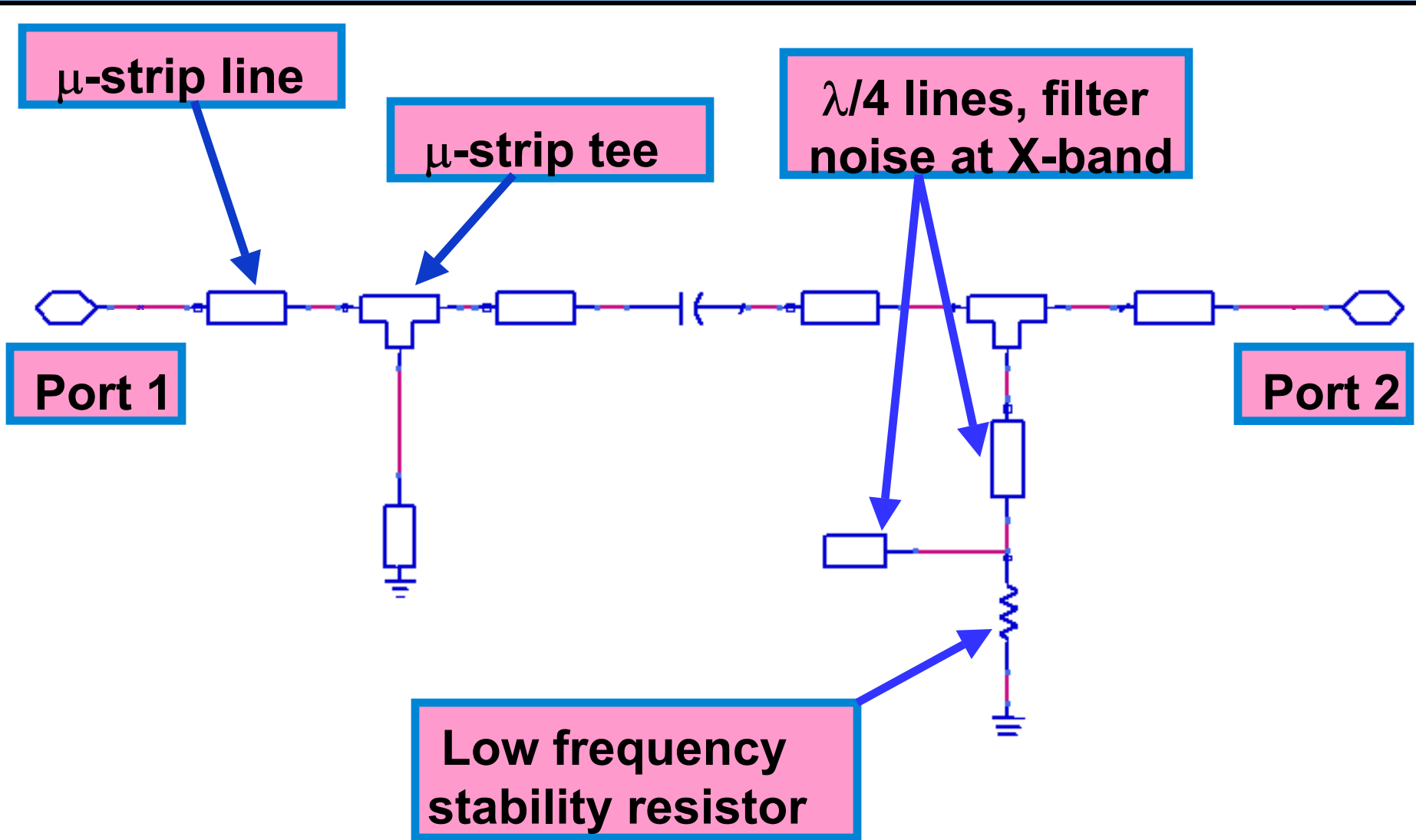

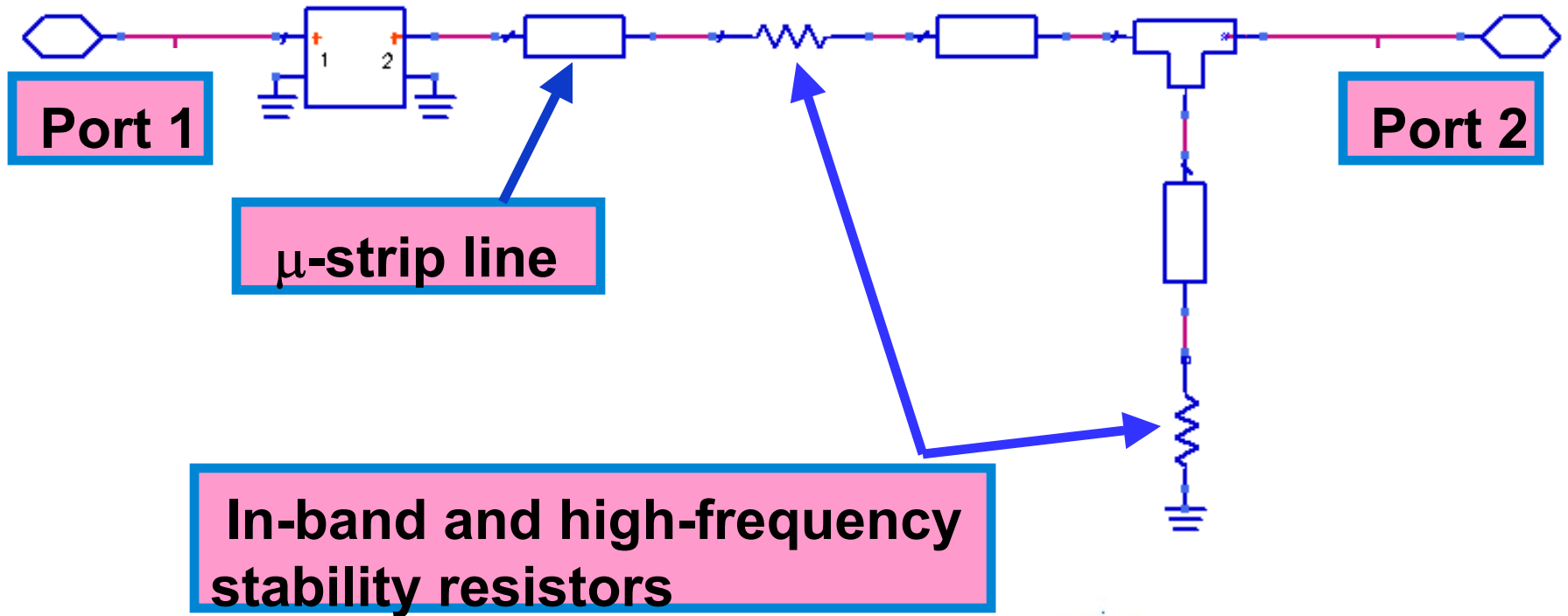
# FET1 Structure with Stability Resistors

This 2-port data-access block reads in a file that contains 42 MESFET samples of noise and s-parameter



# Interstage Matching Network

A more accurate “high-frequency momentum” EM model is also available

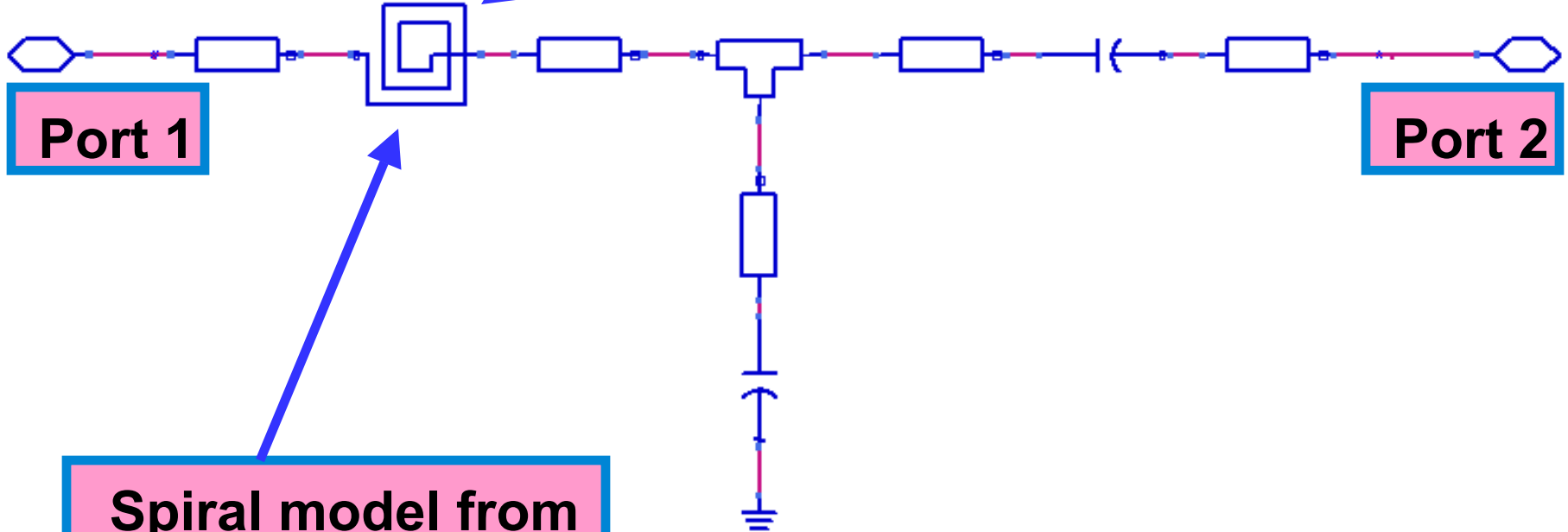

Port 1


Port 2

Spiral model from standard library.





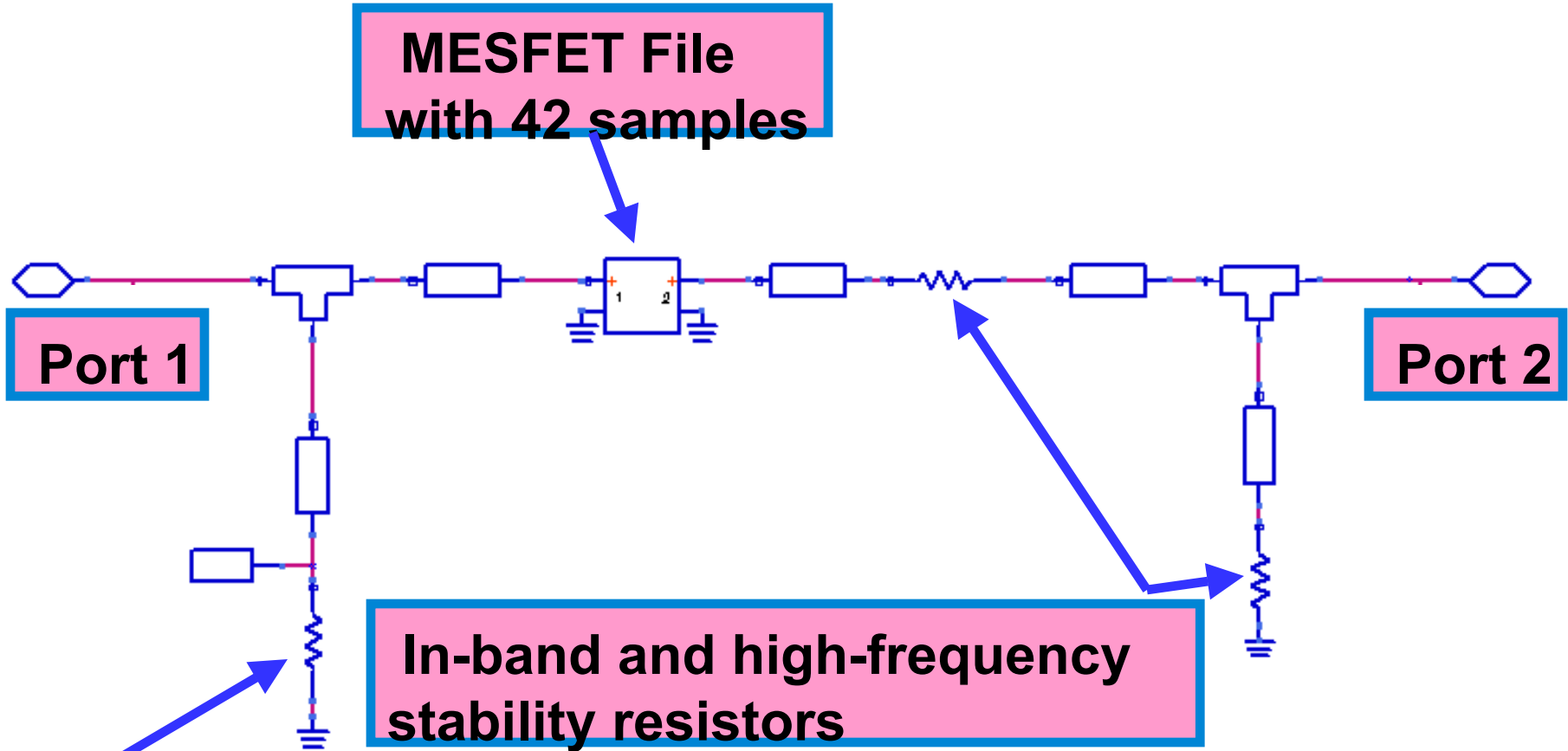
# FET2 Structure with Stability Resistors




Low frequency stability resistor



# Output Matching Network

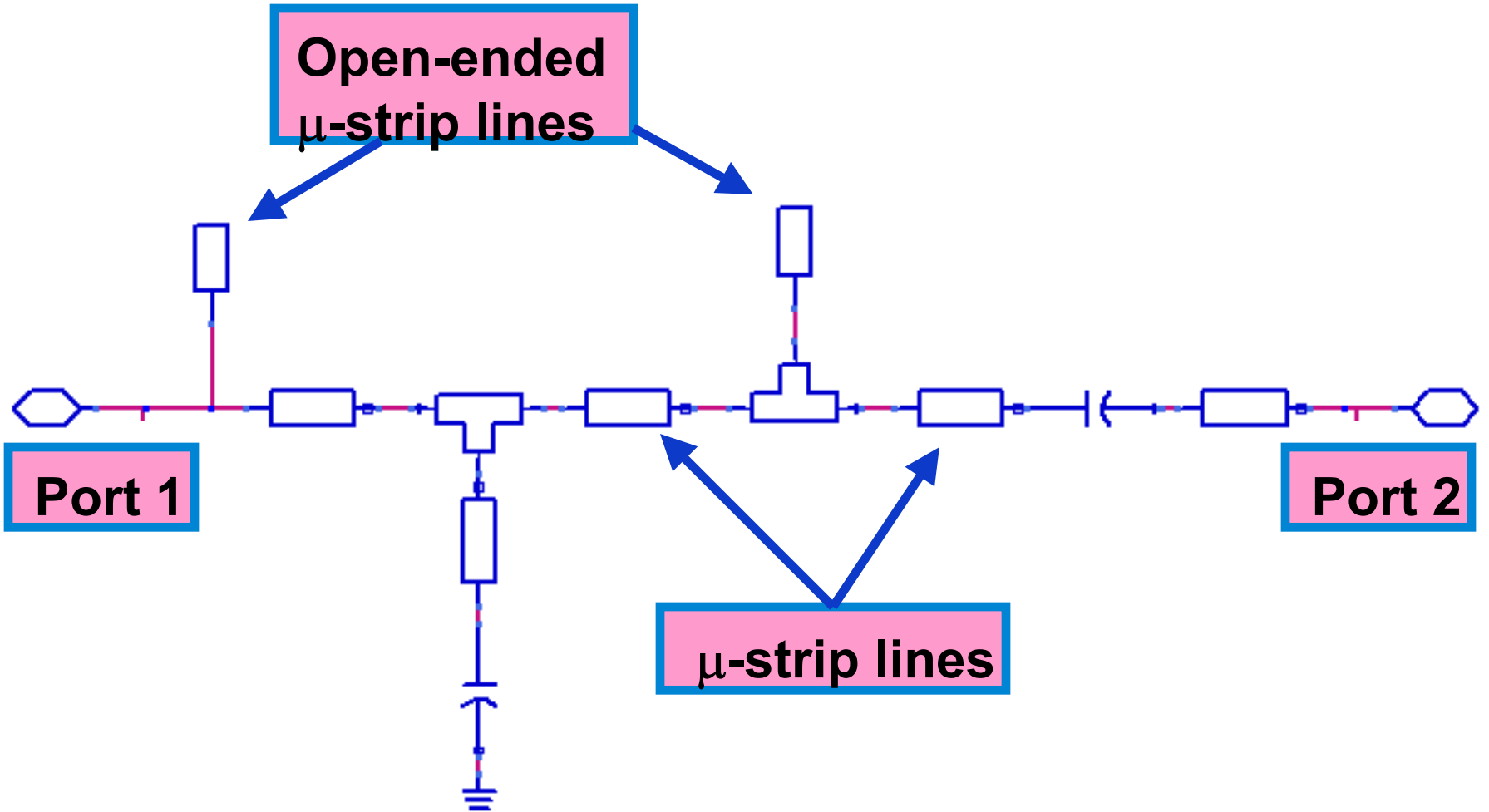

# MMIC Statistical Design Process

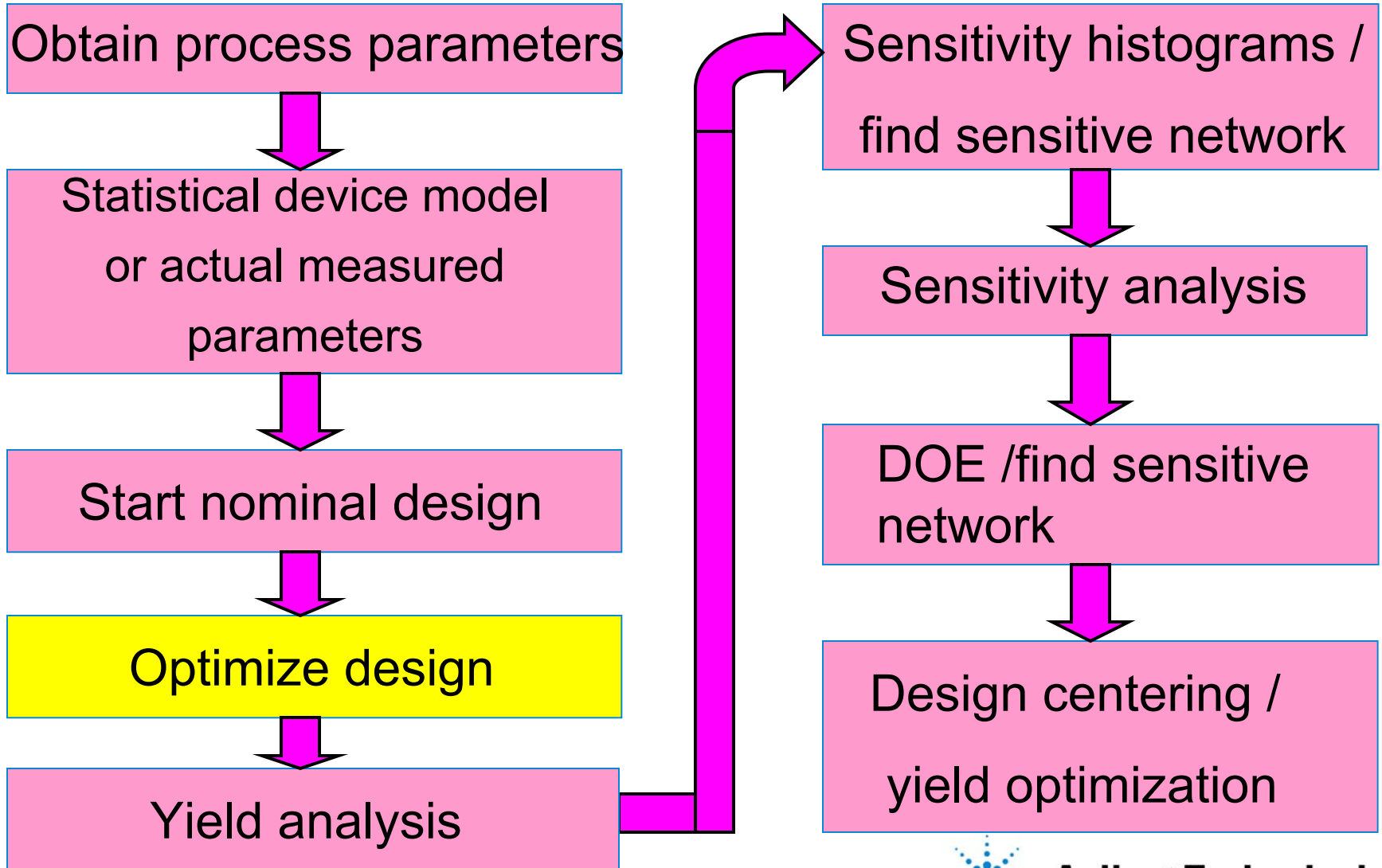

# Programmable Optimization Setup in ADS

**Start here**

**PARAMETER SWEEP**

```
ParamSweep
Sweep1
SweepVar=
SimInstanceName[1]="InitialAnalysis"
SimInstanceName[2]="NFOpt"
SimInstanceName[3]="AmpOpt"
SimInstanceName[4]="FinalAnalysis"
SimInstanceName[5]=
SimInstanceName[6]=
Start=1
Stop=10
Step=1
```

**S-PARAMETERS**

```
S_Param
InitialAnalysis
Start=1.0 GHz
Stop=11.0 GHz
Step=.25 GHz
```

**Step 1**

**Step 2**

**OPTIM**

```
Optim
NFOpt
OptimType=Gradient
MaxIters=50
DesiredError=0.0
StatusLevel=4
SetBestValues=yes
SaveOptimVars=yes
UpdateDataset=yes
UseAllOptVars=no
OptVar[1]="Inp_C1"
OptVar[2]="Inp_L3"
OptVar[3]="Inp_W2"
OptVar[4]="Inp_L1"
OptVar[5]="Inp_L2"
UseAllGoals=no
GoalName[1]="NFGoal"
```

**First optimization sequence optimizes only on the input matching network parameters for noise figure spec only**

**Step 4**

**Step 3**

**S-PARAMETERS**

```
S_Param
FinalAnalysis
Start=1.0 GHz
Stop=11.0 GHz
Step=.25 GHz
```

**OPTIM**

```
Optim
AmpOpt
OptimType=Gradient
MaxIters=50
DesiredError=0.0
StatusLevel=4
SetBestValues=yes
Seed=
SaveOptimVars=yes
UpdateDataset=yes
SaveAllIterations=yes
UseAllOptVars=yes
UseAllGoals=yes
```

**Start optimization using best values obtained from first optimization**

**Second optimization sequence optimizes the whole amp parameters for noise figure, gain and S22 specs**

**Step 2a**

**S-PARAMETERS**

```
S_Param
OptSweep
Start=7.0 GHz
Stop=9.0 GHz
Step=.2 GHz
```

**Step 3a**

**GOAL**

```
Goal
GainGoal
Expr="dB(S21)"
SimInstanceName="OptSweep"
Min=14.0
Max=
Weight=
RangeVar[1]="freq"
RangeMin[1]=7.0 GHz
RangeMax[1]=9.0 GHz
```

**GOAL**

```
Goal
S22Goal
Expr="dB(S22)"
SimInstanceName="OptSweep"
Min=
Max=-14
Weight=9
RangeVar[1]="freq"
RangeMin[1]=7.0 GHz
RangeMax[1]=9.0 GHz
```


**GOAL**

```
Goal
NFGoal
Expr="nf(2)"
SimInstanceName="OptSweep"
Min=
Max=2.8
Weight=
RangeVar[1]="freq"
RangeMin[1]=7.0 GHz
RangeMax[1]=9.0 GHz
```




# Programmable Optimization Setup


**Start here**

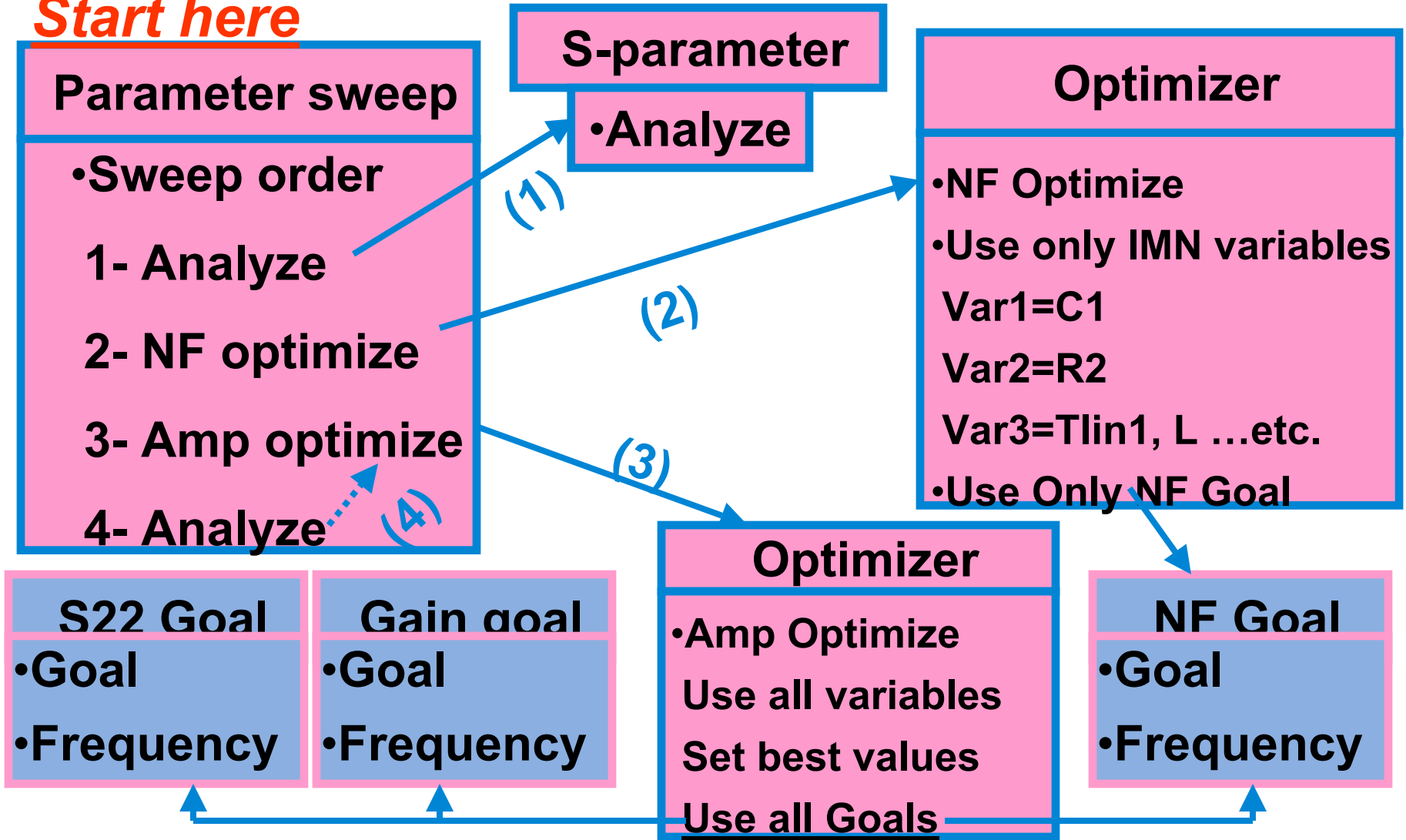

# LNA Response after Optimization

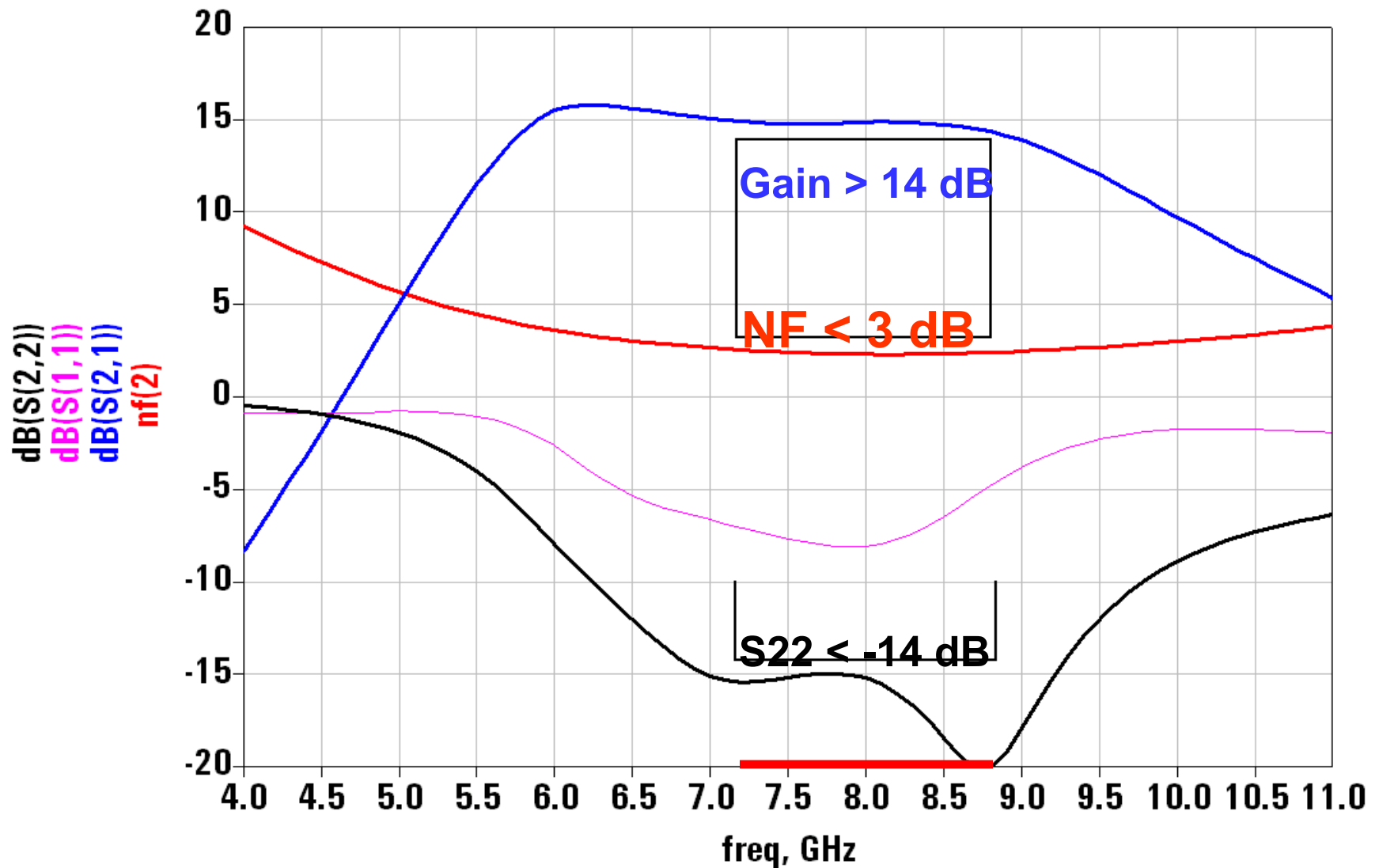

# MMIC Statistical Design Process

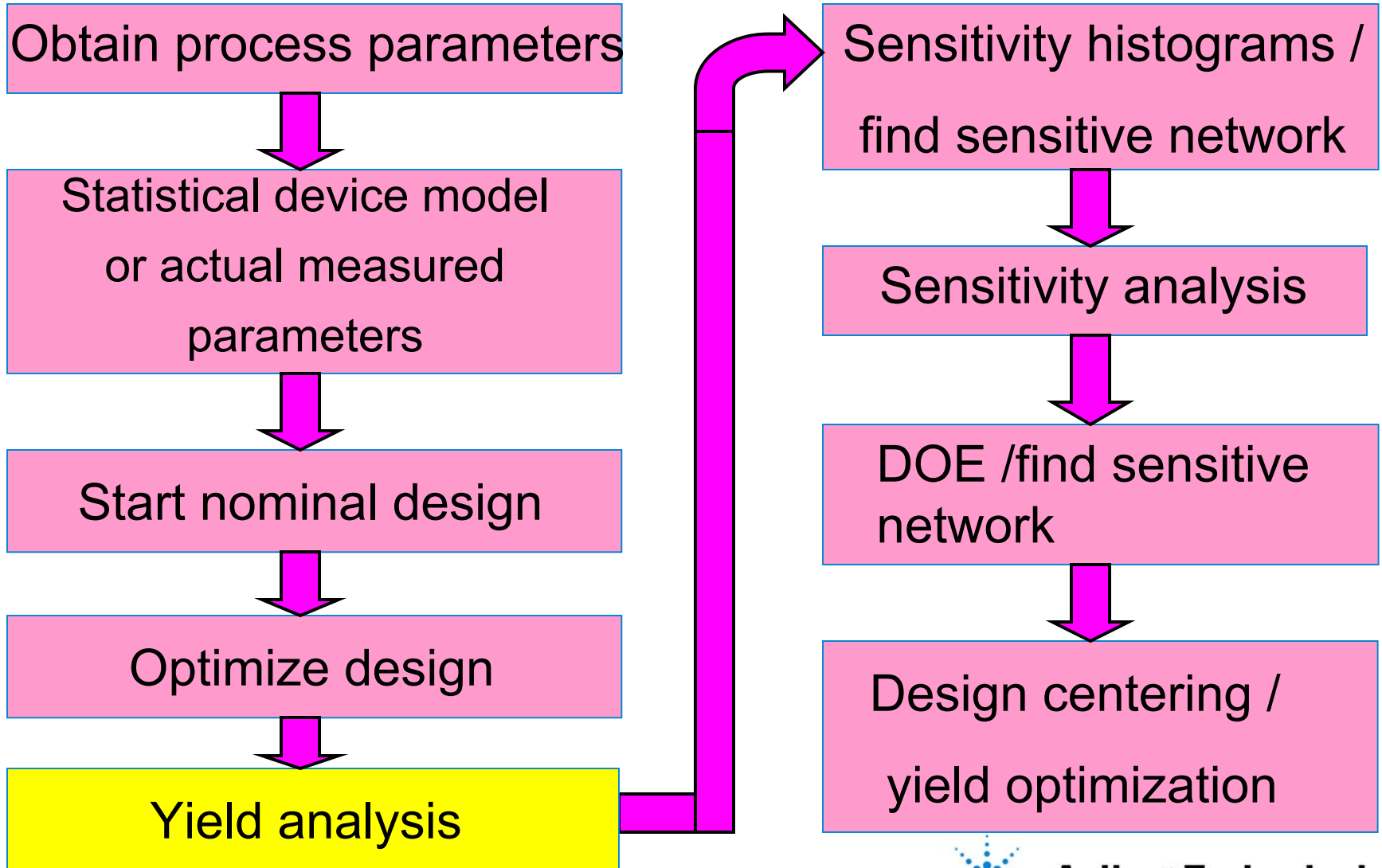

# Yield Analysis in ADS

## YIELD

```
Yield
Yield1
NumIters=200
PPT_Mode=none
ShadowModelType=none
Seed=
SaveSolns=yes
SaveSpecs=yes
SaveRandVars=yes
UpdateDataset=no
SaveAllIterations=yes
UseAllSpecs=yes
StatusLevel=2
```

## YIELD SPEC

```
YieldSpec
NF_Spec
Expr="max(nf(2))"
SimInstanceName="YldSweep"
Min=
Max=2.8
Weight=
Save=
RangeVar[1]=
RangeMin[1]=
RangeMax[1]=
```

## VAR

```
VAR2
Inp_L2=17.2666 opt{ 10 to 100 }
Inp_L1=1064.12 opt{ 800 to 1300 }
Inp_WW2=14.3175 opt{ 5 to 25 } stat{ uniform +/- .5 }
Inp_WW3=5.75363 opt{ 5 to 25 } stat{ uniform +/- .5 }
Inp_L3=268.891 opt{ 100 to 550 }
Inp_C1=4.20706 opt{ .1 to 6 } stat{ uniform +/- 5 % }
Inp_R1=27.9732 opt{ 25 to 30 } stat{ uniform +/- 5 % }
```

## S-PARAMETERS

```
S_Param
YldSweep
Start=7.2 GHz
Stop=8.8 GHz
Step=.2 GHz
```

## YIELD SPEC

```
YieldSpec
Gain_Spec
Expr="min(dB(S21))"
SimInstanceName="YldSweep"
Min=14.0
Max=
Weight=
Save=
RangeVar[1]=
RangeMin[1]=
RangeMax[1]=
```

## VAR

```
VAR5
FET2_L1=261.487 opt{ 10 to 550 }
FET2_WW1=10.0692 opt{ 5 to 50 } stat{ uniform +/- .5 }
FET2_WW2=9.12953 opt{ 5 to 50 } stat{ uniform +/- .5 }
FET2_WW4=10.2946 opt{ 5 to 50 } stat{ uniform +/- .5 }
FET2_WW3=7.74289 opt{ 5 to 50 } stat{ uniform +/- .5 }
FET2_R1=29.3678 opt{ 25 to 30 } stat{ uniform +/- 5 % }
FET2_R2=20 opt{ 20 to 25 } stat{ uniform +/- 5 % }
FET2_R3=165.472 opt{ 150 to 200 } stat{ uniform +/- 5 % }
FET2_L2=178.628 opt{ 10 to 250 }
FET2_L3=24.7259 opt{ 2 to 250 }
FET2_L4=98.0301 opt{ 2 to 250 }
```

## YIELD SPEC

```
YieldSpec
S22_Spec
Expr="max(dB(S22))"
SimInstanceName="YldSweep"
Min=
Max=-14
Weight=
Save=
RangeVar[1]=
RangeMin[1]=
RangeMax[1]=
```

Page 17 has an easier-to-read diagram





# Yield Analysis (Simplified Setup)

**Yield**  
# iterations=1000  
use all specs=yes  
...etc.

**S-parameters**  
Yield sweep  
start = 7 GHz  
stop = 9 GHz  
step = .1 GHz

**Yield spec**  
NF spec  
max NF = 3 dB  
use yield sweep

**Yield spec**  
Gain spec  
min gain=14 dB  
use yield sweep

**Yield spec**  
S22 spec  
max S22=-14 dB  
use yield sweep






# Yield after Optimization : 8.8 %

## Statistical Analysis of LNA Performance

- 5% Gaussian variation in lumped
- Line widths vary  $\pm 1/2 \mu\text{m}$
- Substrate height  $100 \mu\text{m} \pm 3 \mu\text{m}$
- Substrate Er  $12.9 \pm 5\%$
- 42 FET samples

| NumFail | NumPass | Yield |
|---------|---------|-------|
| 912.00  | 88.00   | 8.80  |

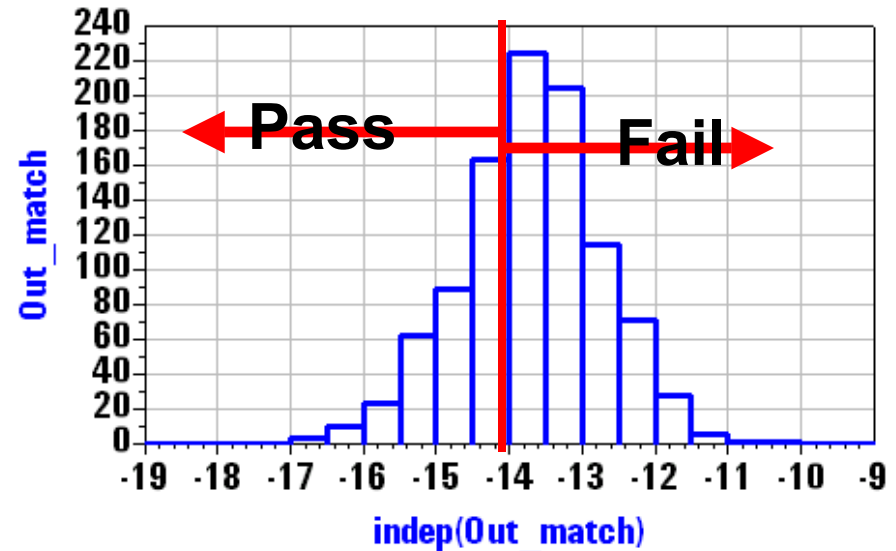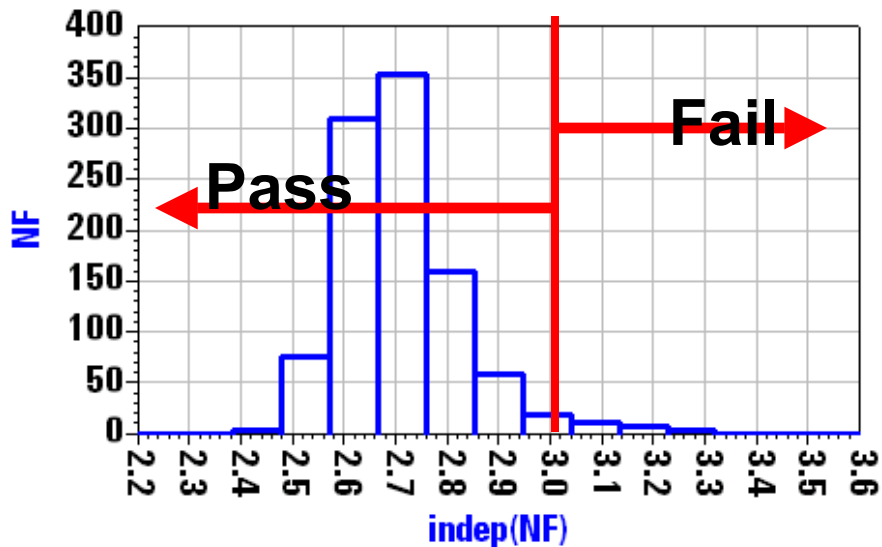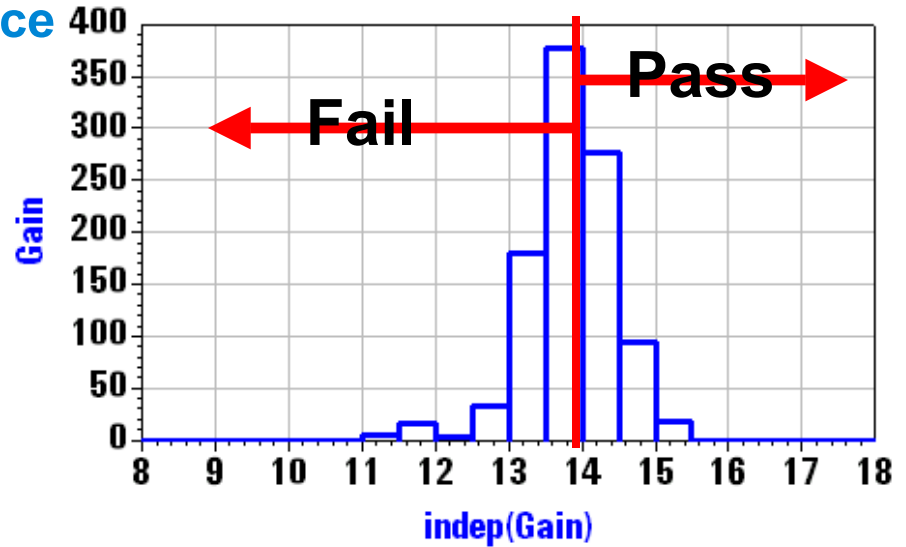


# LNA Yield / Versus Variation in Each Section

| <u>Element name</u>             | <u>Yield</u> |
|---------------------------------|--------------|
| Input matching network          | 100 %        |
| Interstage matching network     | 100 %        |
| Output matching network         | 70 %         |
| FETs (42 samples)               | 25 %         |
| Er (dielectric constant)        | 87 %         |
| H (substrate height)            | 100 %        |
| Overall yield (vary everything) | 8.8 %        |



# MMIC Statistical Design Process

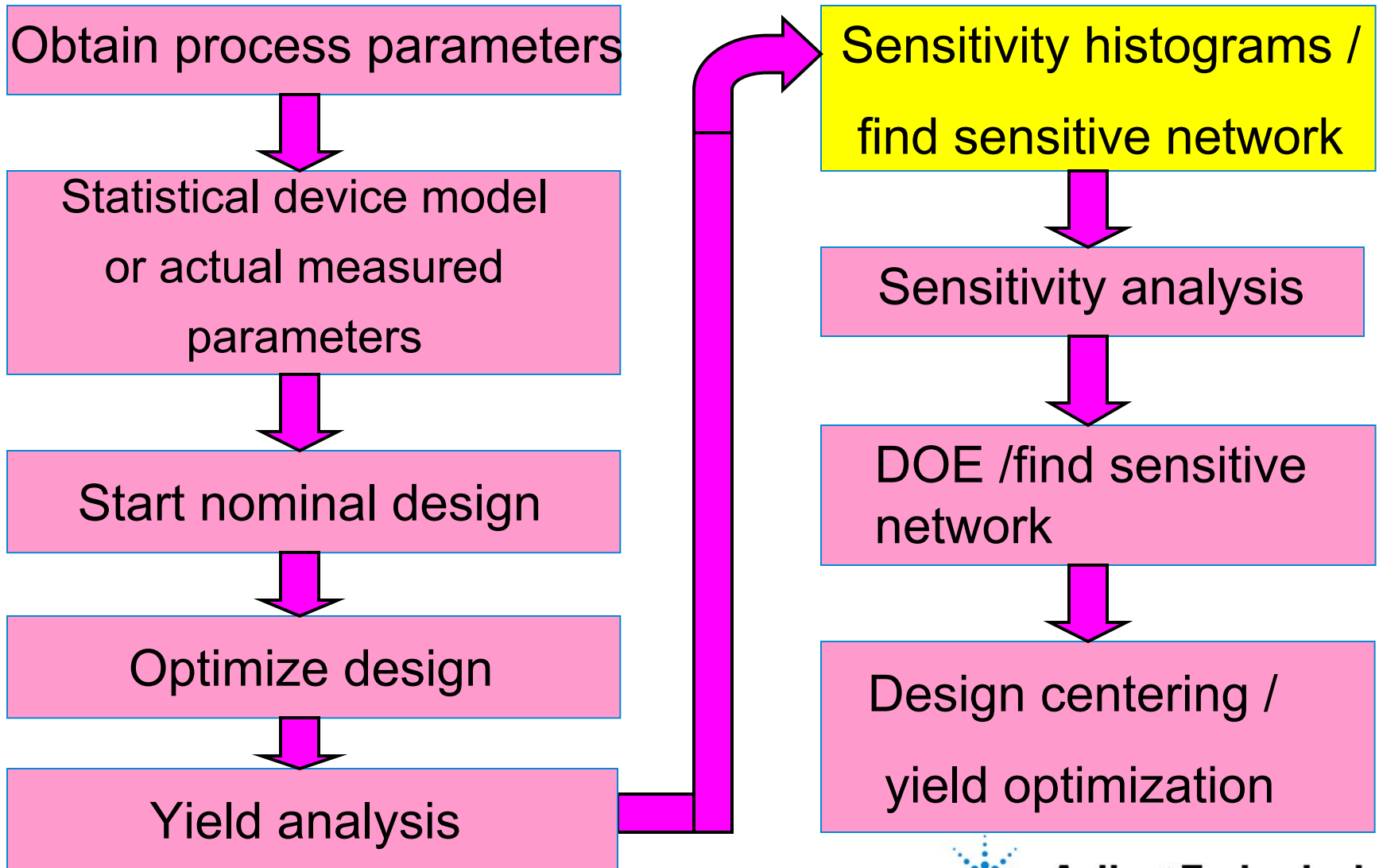


# Yield Sensitivity Histograms (YSH)


- Data that are stored from a yield analysis run are post processed via built-in AEL Expressions to extract and display results
- YSH display yield with respect to each element variation.
- YSH provide insight to how sensitive the design specs are with respect to each of the design's elements.
- YSH help designers to pinpoint the sensitive parts in their designs. As a result, designers make decision to replace these parts with “tighter tolerance parts” in Board application (OR) create “less sensitive matching networks” in IC designs.
- YSH also allow designers to manually adjust the nominal values of design elements in order to increase the yield.



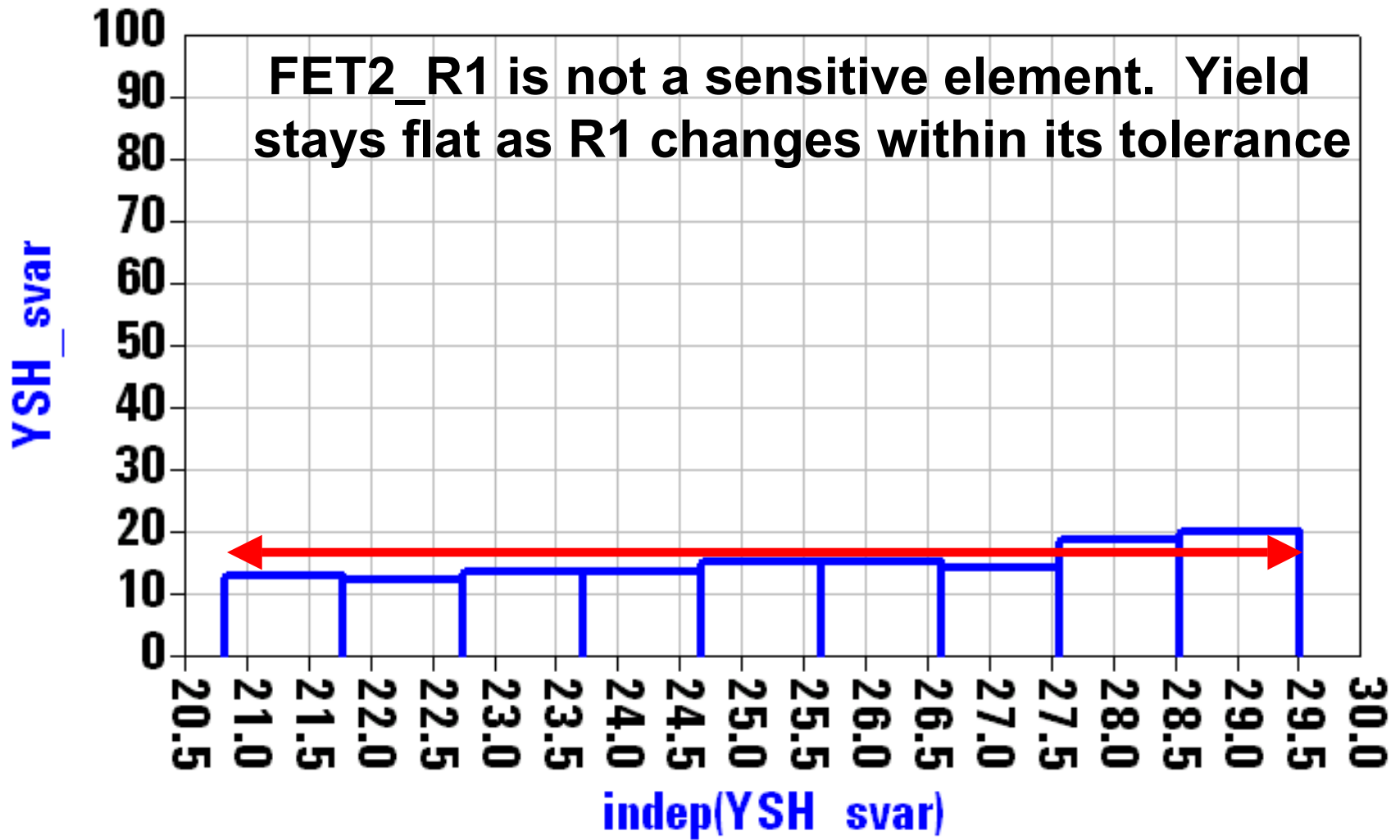
# Yield Sensitivity with Respect to FET2\_R1


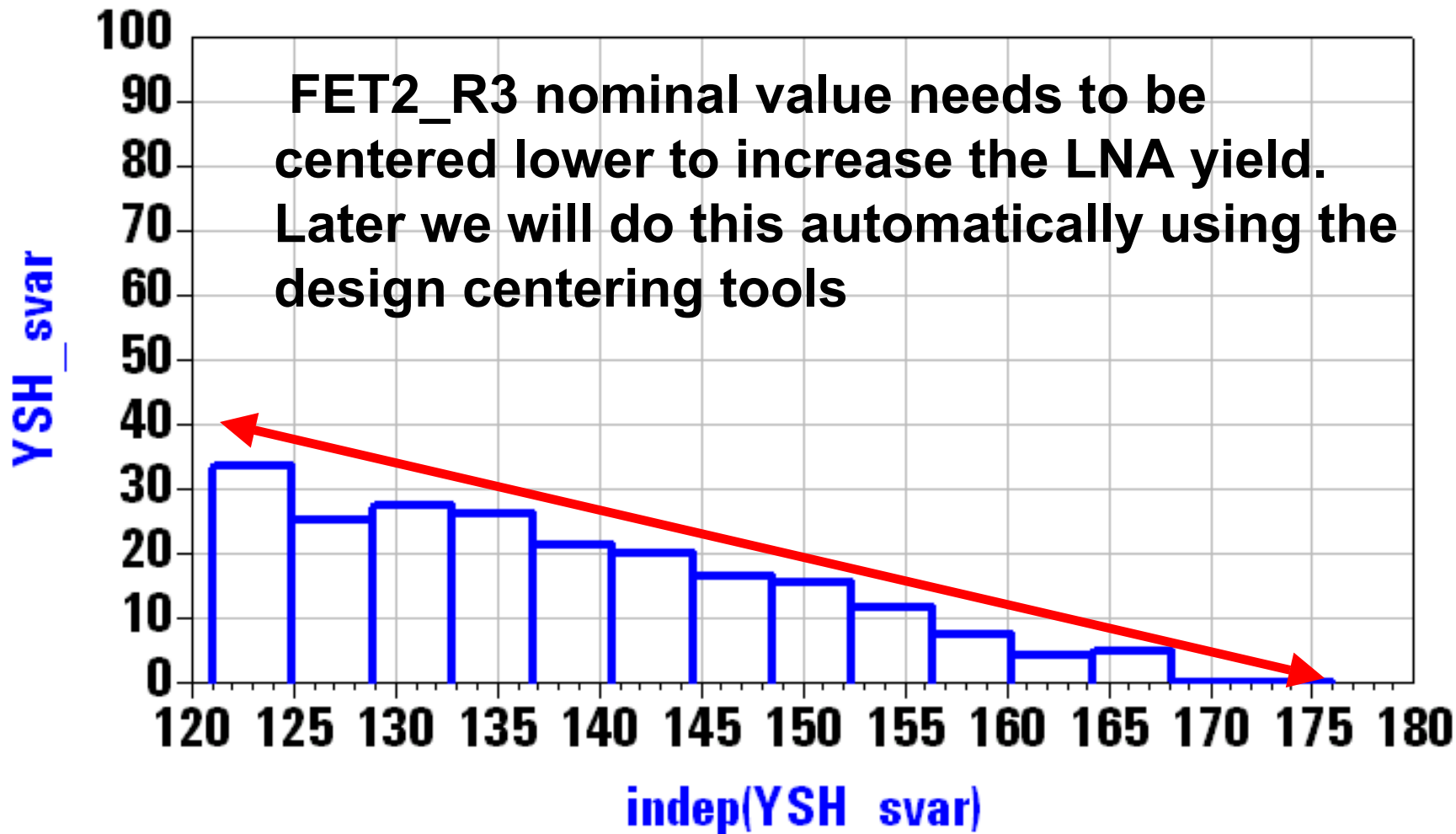
# Yield Sensitivity with Respect to FET2\_R3



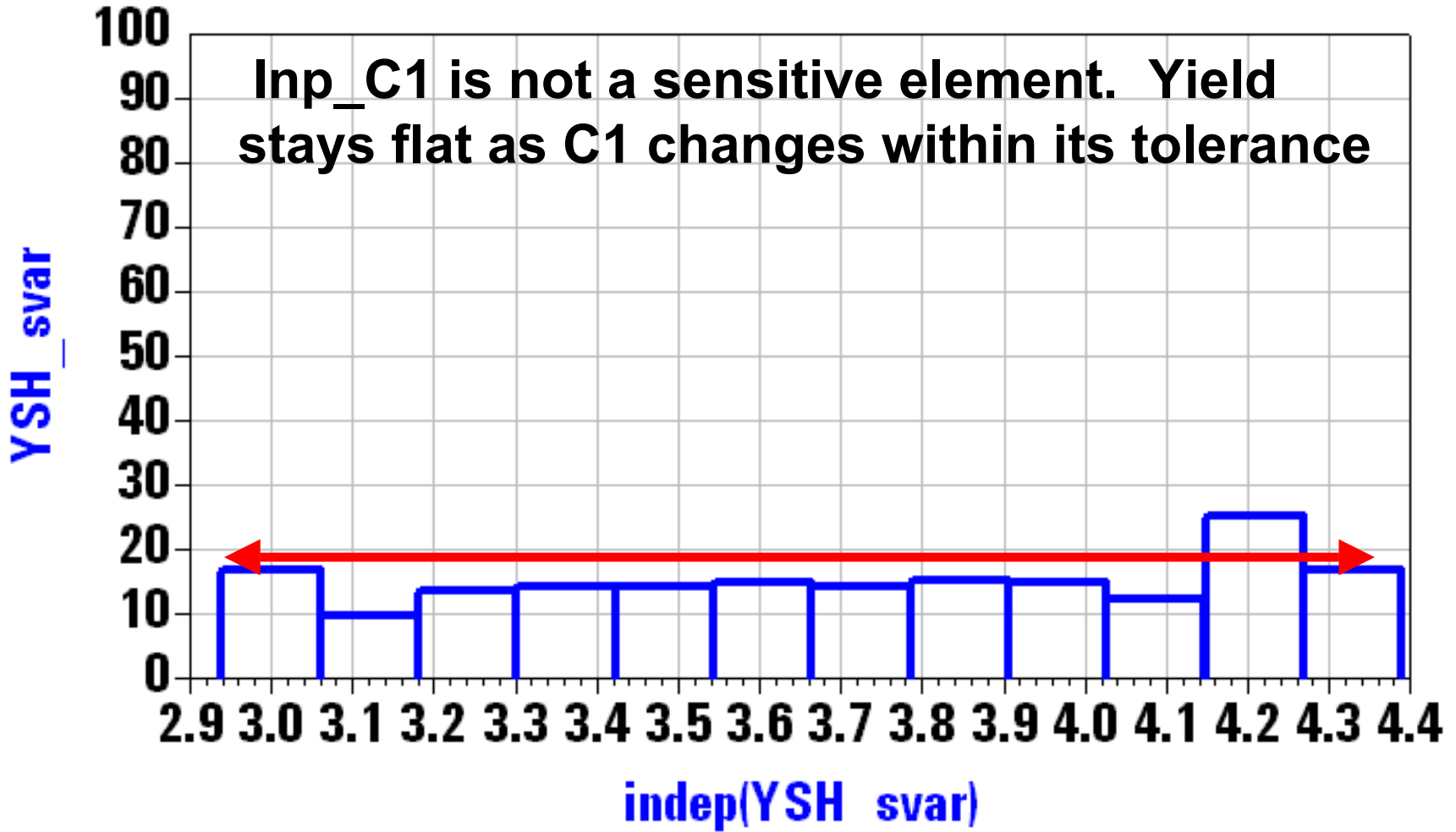
# Yield Sensitivity with Respect to Inp\_C1





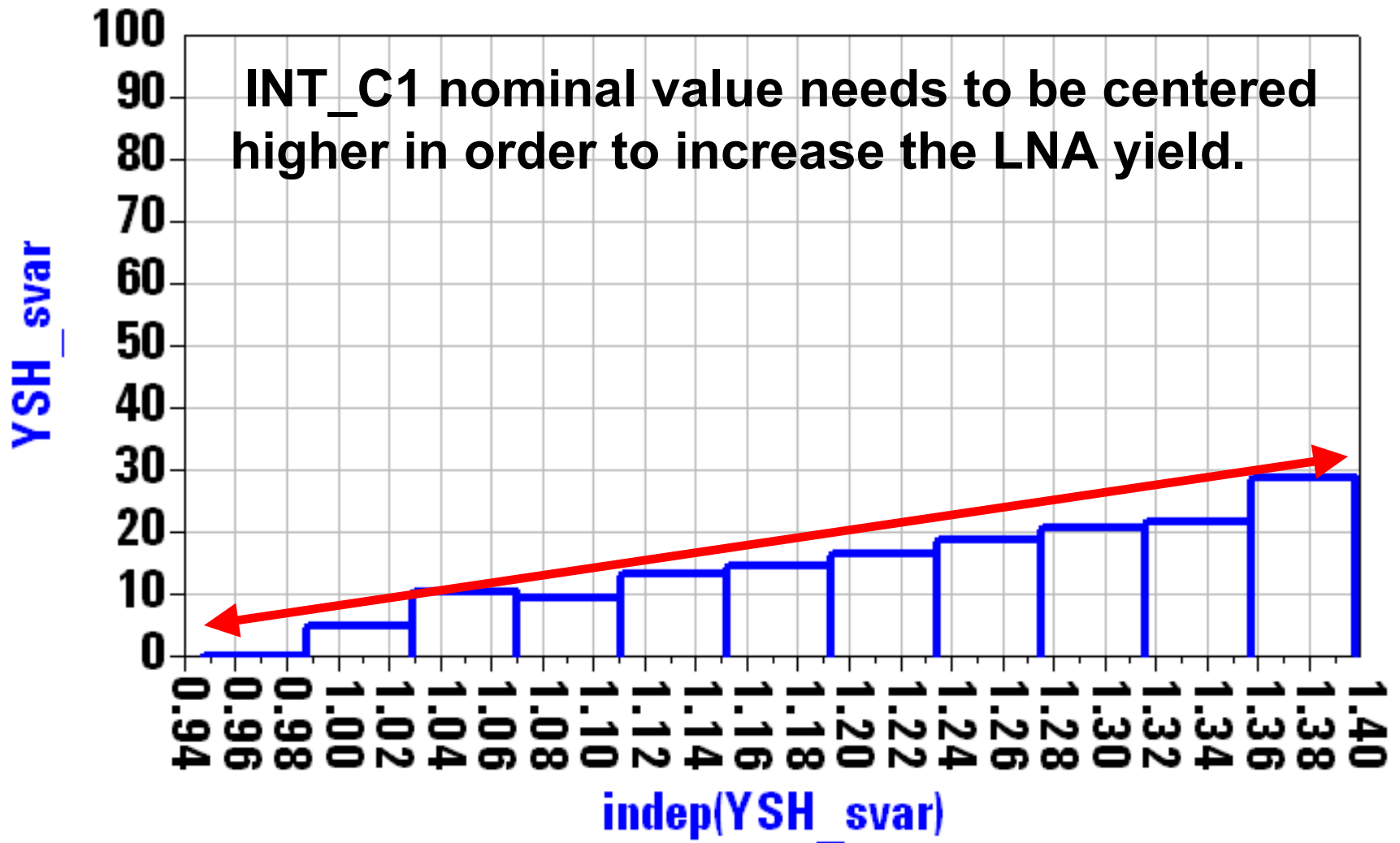
# Yield Sensitivity with Respect to INT\_C1


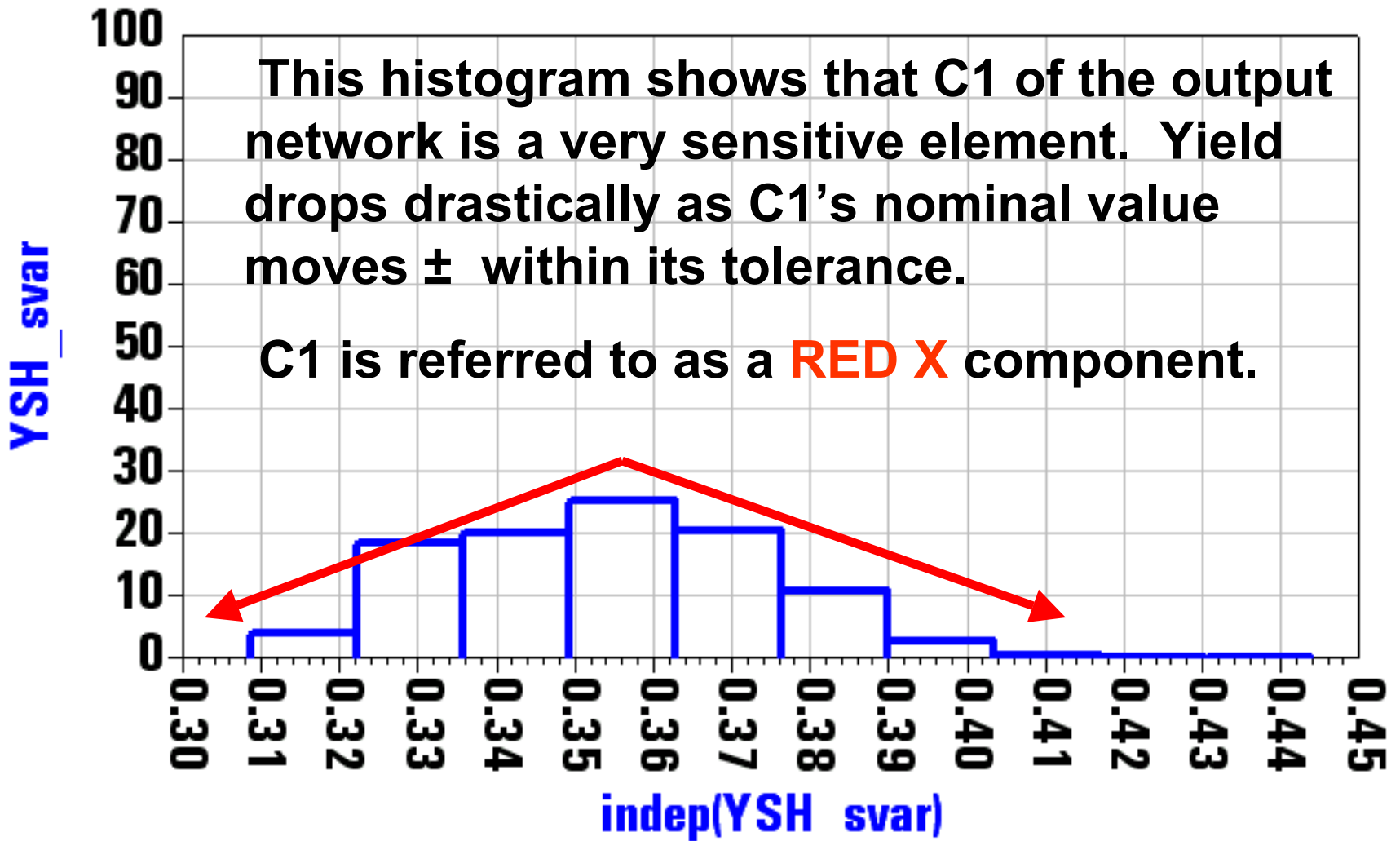
# Yield Sensitivity with Respect to OUT\_C1




# Break for Questions and Answers

**Q & A**




# MMIC Statistical Design Process

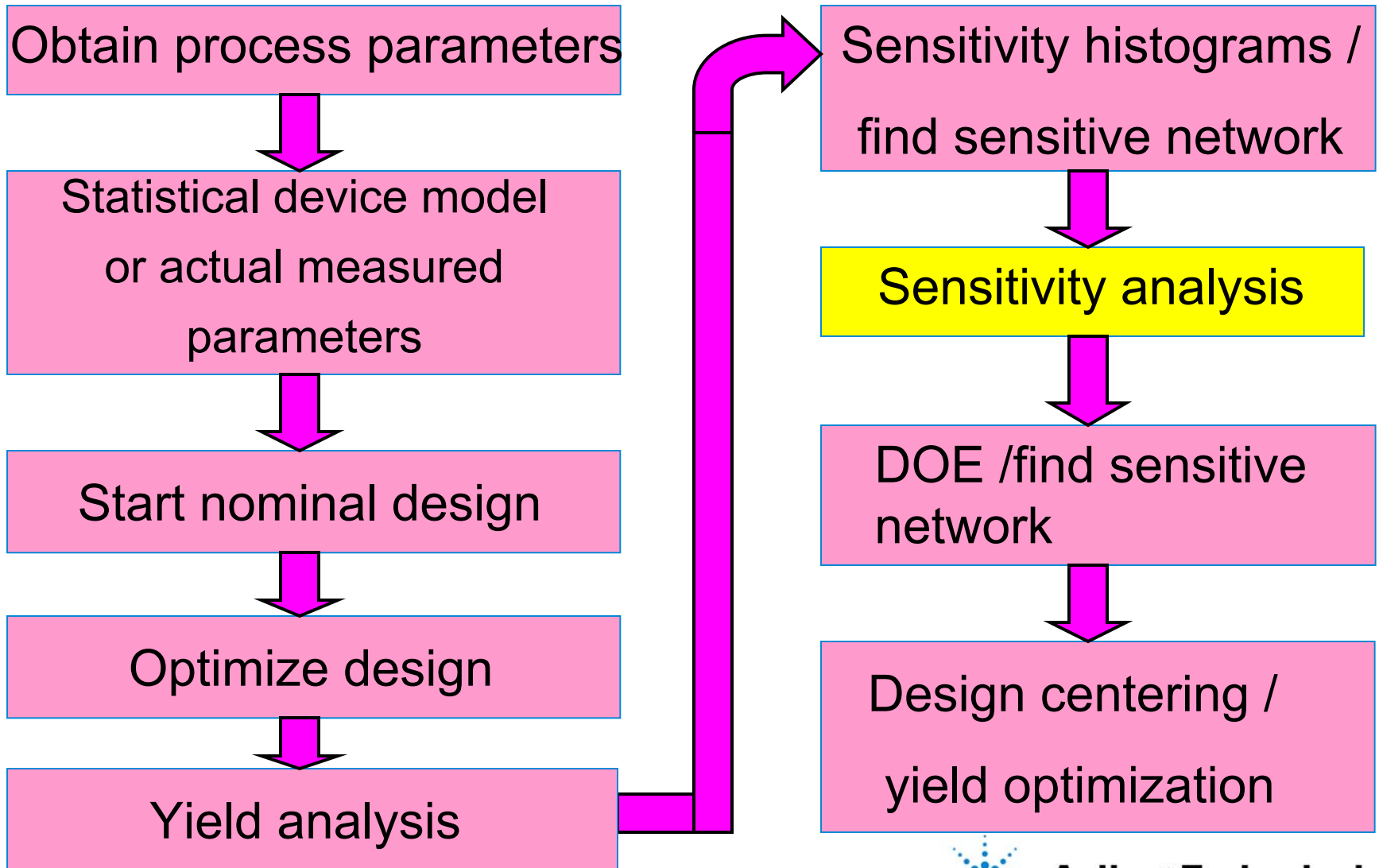
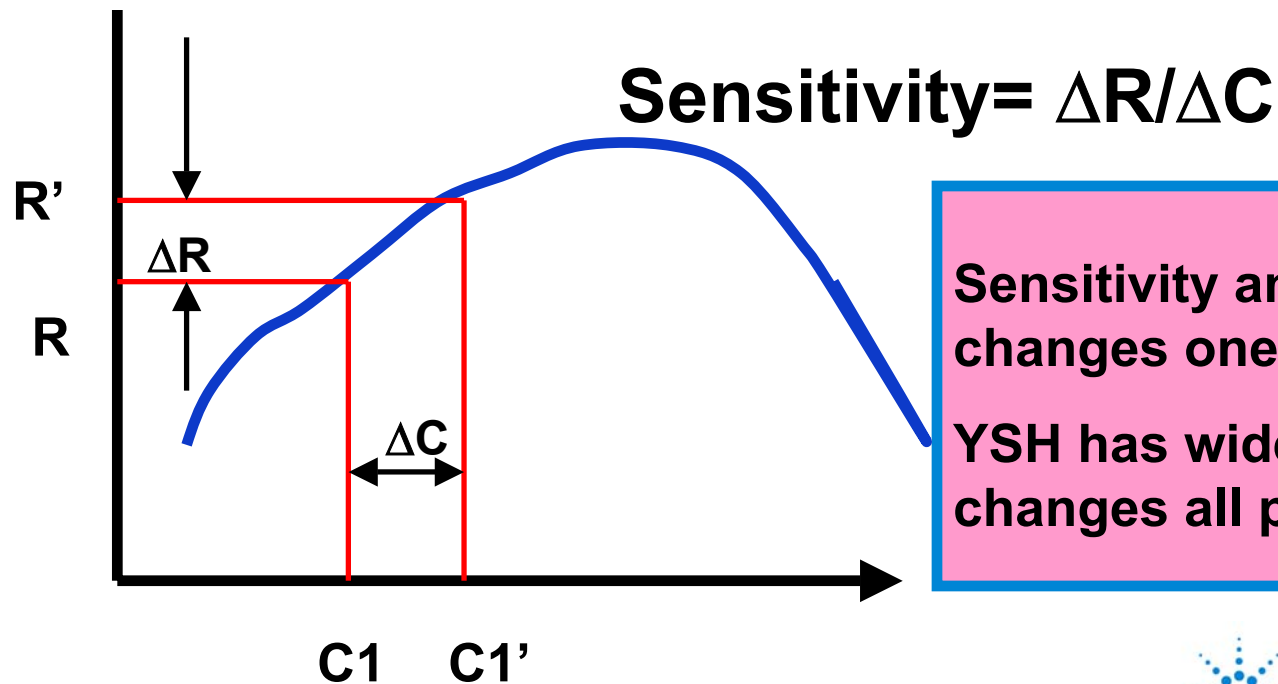
# Sensitivity Analysis – How Does it Work?

- Change the part's nominal value by  $1e-6$  and monitor the change in the response (R).
- Example for capacitor, C1 with response R
- Perturb C1 by a small delta:  $C1' = C1(1+1e-6)$




Sensitivity analysis is local. It changes one part at a time.

YSH has wider variation and changes all parts together.



# Sensitivity Analysis to NF Setup

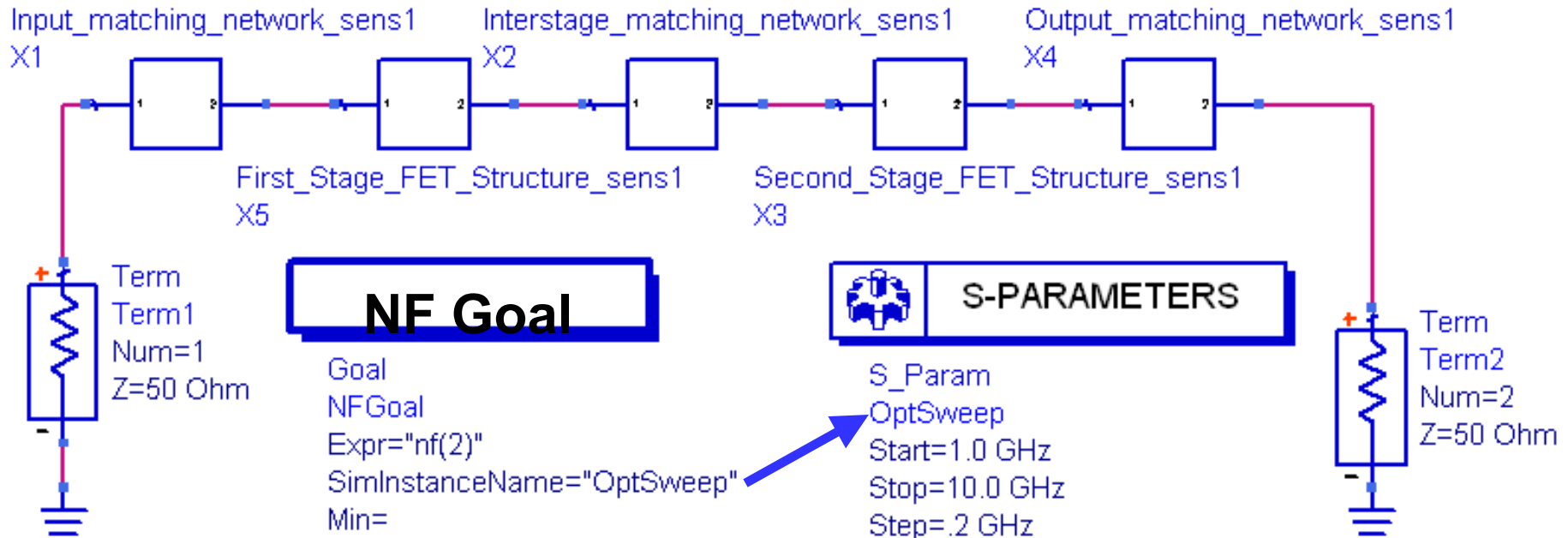

## NF Goal

Goal  
NFGoal  
Expr="nf(2)"  
SimInstanceName="OptSweep"  
Min=  
Max=2.0  
Weight=  
RangeVar[1]="freq"  
RangeMin[1]=7.0 Ghz  
RangeMax[1]=9.0 Ghz

## S-PARAMETERS

S\_Param  
OptSweep  
Start=1.0 GHz  
Stop=10.0 GHz  
Step=.2 GHz


## OPTIM

Optim  
InOpt  
OptimType=Sensitivity  
StatusLevel=4  
UseAllOptVars=yes  
UseAllGoals=yes


**Sensitivity analysis is accessed from the optimization controller**



# Sensitivity Analysis to NF Spec

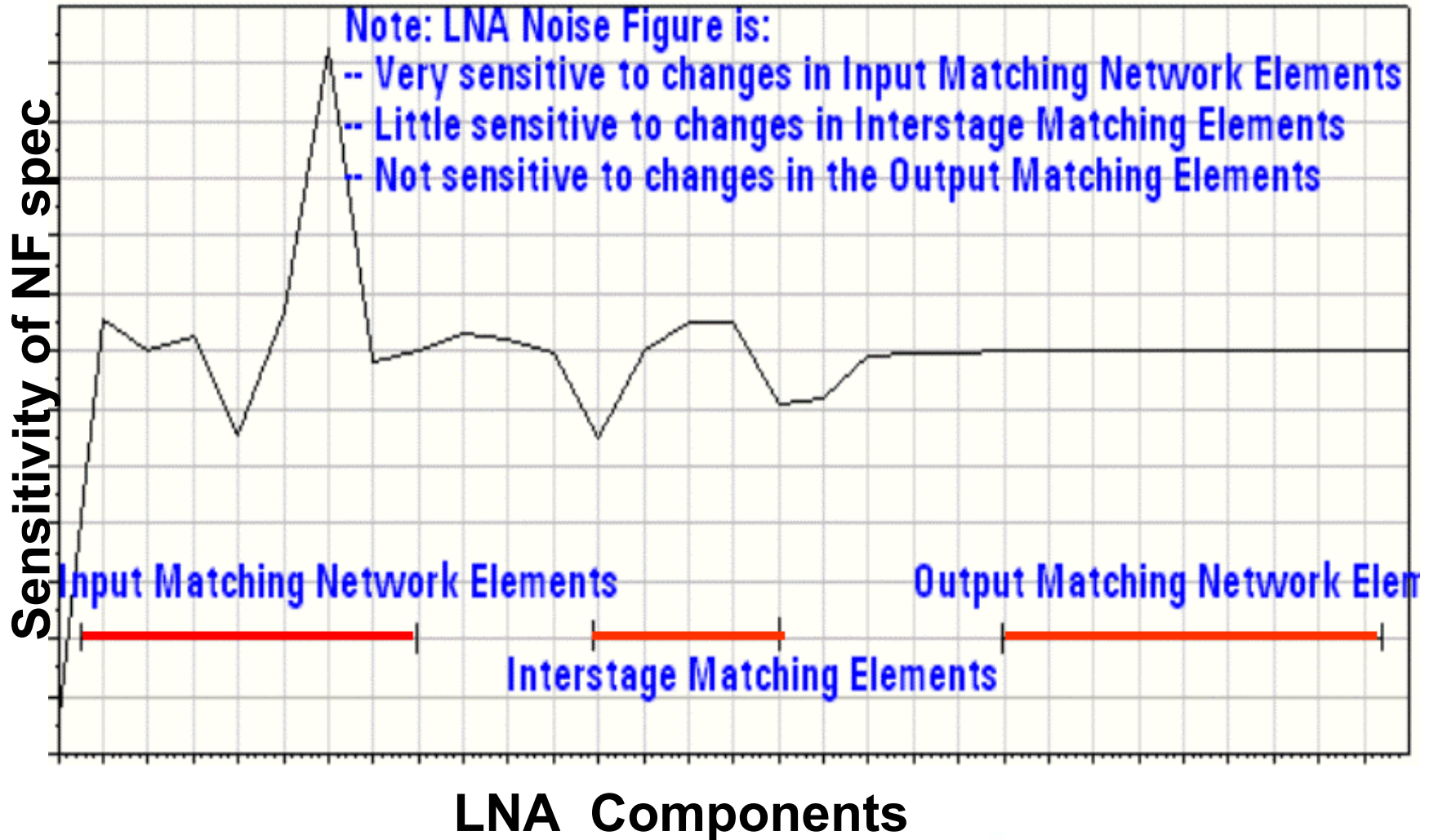


# Sensitivity Analysis to S22 Spec

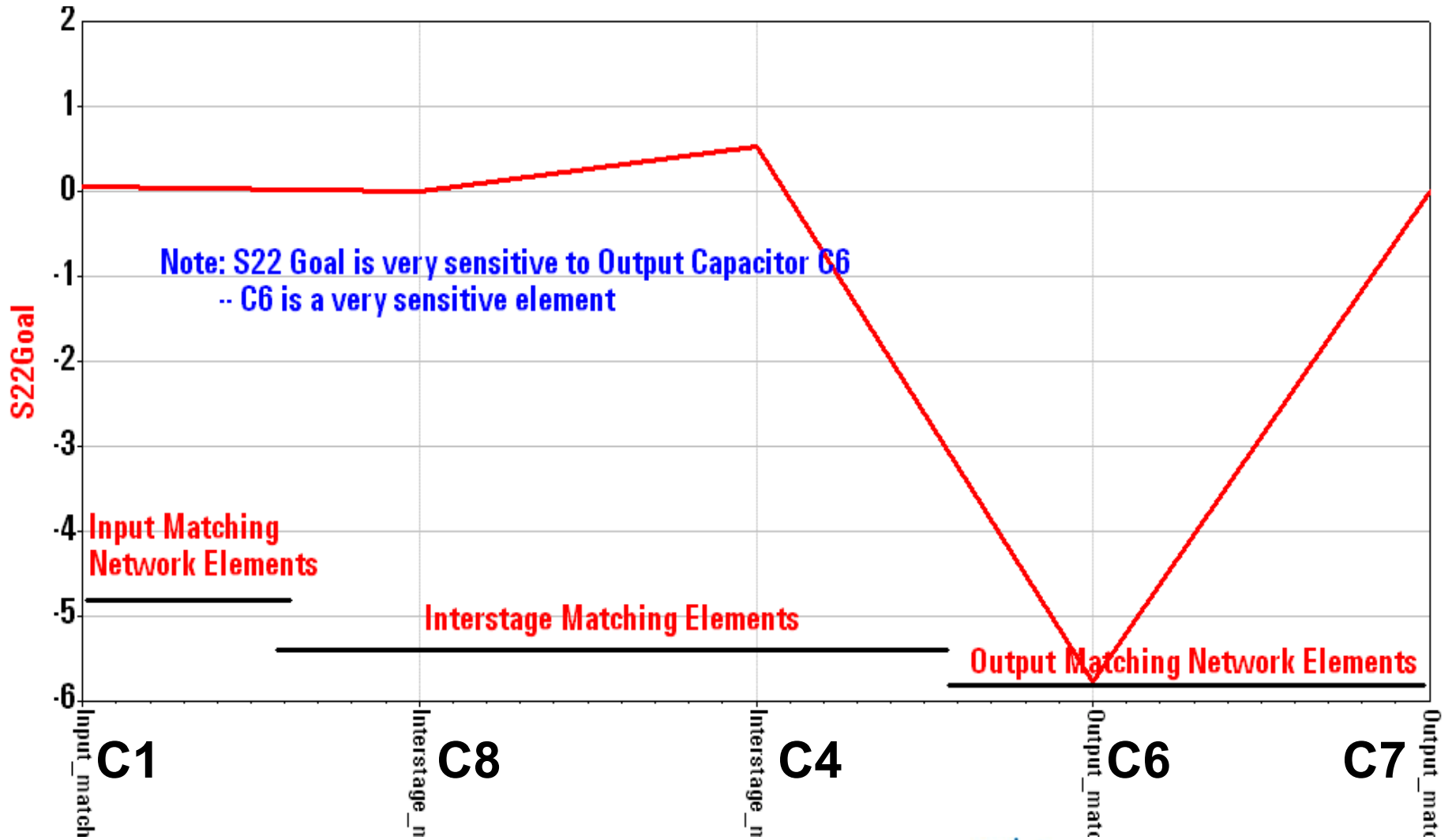



# MMIC Statistical Design Process

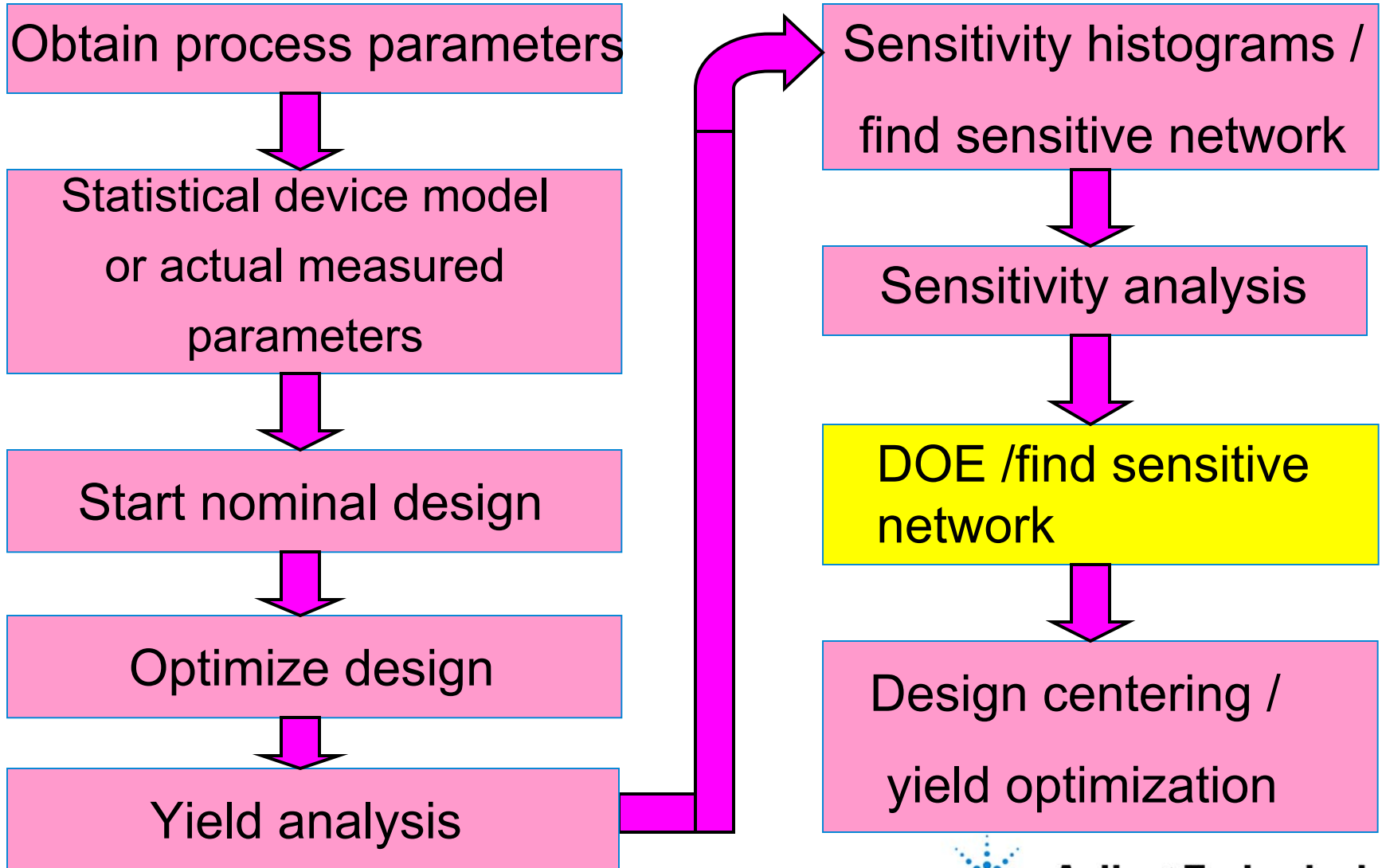

# Design of Experiments (DOE) on the LNA

- Lump all input matching network elements together and vary them with a steering variable **(d\_inp)  $\pm 5\%$**
- Do the same with the interstage and output
- DOE variables are then **d\_inp, d\_int, and d\_out**
- This should provide us with more information on the sensitivity of the matching networks.
- The 3 variables require 8 simulation runs = **(2<sup>3</sup>)**



# How Does Steering Variable d\_inp Work ?

**Example:**

**For input matching network variables C1, R1, W1**

**Set the following variables:**

$$C1 = 5 \text{ pF} * (1+d\_inp)$$

$$R1 = 20 \text{ ohm} * (1+d\_inp)$$

$$W1 = 10 \text{ um} * (1+d\_inp)$$

$$d\_inp = 0 \text{ DOE}(\pm 5\%)$$

**d\_inp steers all “input matching variables” as it changes from -5% to +5% for the DOE**



# Input and Output Variables of DOE

Get the output values at center frequency (8 GHz), or use the worst response across the frequency band

| d_inp | d_int | d_out | Gain | NF | S22 |
|-------|-------|-------|------|----|-----|
| 1     | 1     | 1     |      |    |     |
| 1     | 1     | -1    |      |    |     |
| 1     | -1    | 1     |      |    |     |
| 1     | -1    | -1    |      |    |     |
| -1    | 1     | 1     |      |    |     |
| -1    | 1     | -1    |      |    |     |
| -1    | -1    | 1     |      |    |     |
| -1    | -1    | -1    |      |    |     |




# DOE Results on Gain

## Nominal Response


| freq     | dB(S(2,1)) |           |           |           |           |           |           |           |           |
|----------|------------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|
|          | doelter=0  | doelter=1 | doelter=2 | doelter=3 | doelter=4 | doelter=5 | doelter=6 | doelter=7 | doelter=8 |
| 7.200GHz | 14.889     | 15.861    | 14.577    | 15.649    | 14.930    | 15.876    | 14.613    | 15.656    | 15.301    |
| 7.300GHz | 14.809     | 15.834    | 14.521    | 15.634    | 14.820    | 15.822    | 14.528    | 15.616    | 15.241    |
| 7.400GHz | 14.756     | 15.824    | 14.480    | 15.628    | 14.743    | 15.794    | 14.463    | 15.593    | 15.199    |
| 7.500GHz | 14.712     | 15.820    | 14.451    | 15.627    | 14.682    | 15.778    | 14.418    | 15.582    | 15.172    |
| 7.600GHz | 14.682     | 15.822    | 14.438    | 15.632    | 14.642    | 15.775    | 14.396    | 15.583    | 15.159    |
| 7.700GHz | 14.669     | 15.829    | 14.436    | 15.637    | 14.624    | 15.782    | 14.391    | 15.590    | 15.159    |
| 7.800GHz | 14.670     | 15.836    | 14.445    | 15.638    | 14.626    | 15.794    | 14.401    | 15.596    | 15.170    |
| 7.900GHz | 14.680     | 15.835    | 14.463    | 15.630    | 14.640    | 15.800    | 14.424    | 15.596    | 15.187    |
| 8.000GHz | 14.702     | 15.826    | 14.492    | 15.614    | 14.669    | 15.800    | 14.460    | 15.588    | 15.204    |
| 8.100GHz | 14.691     | 15.756    | 14.485    | 15.532    | 14.668    | 15.736    | 14.463    | 15.513    | 15.178    |
| 8.200GHz | 14.682     | 15.663    | 14.478    | 15.431    | 14.668    | 15.648    | 14.466    | 15.415    | 15.135    |
| 8.300GHz | 14.662     | 15.535    | 14.456    | 15.289    | 14.658    | 15.520    | 14.452    | 15.271    | 15.076    |
| 8.400GHz | 14.631     | 15.373    | 14.423    | 15.116    | 14.633    | 15.351    | 14.424    | 15.090    | 14.984    |
| 8.500GHz | 14.581     | 15.169    | 14.374    | 14.910    | 14.585    | 15.133    | 14.376    | 14.870    | 14.864    |
| 8.600GHz | 14.515     | 14.932    | 14.300    | 14.662    | 14.516    | 14.877    | 14.298    | 14.601    | 14.708    |
| 8.700GHz | 14.419     | 14.651    | 14.198    | 14.375    | 14.410    | 14.569    | 14.185    | 14.288    | 14.507    |
| 8.800GHz | 14.286     | 14.324    | 14.063    | 14.051    | 14.261    | 14.212    | 14.032    | 13.932    | 14.267    |



# DOE Pareto Chart (Effects on Gain)

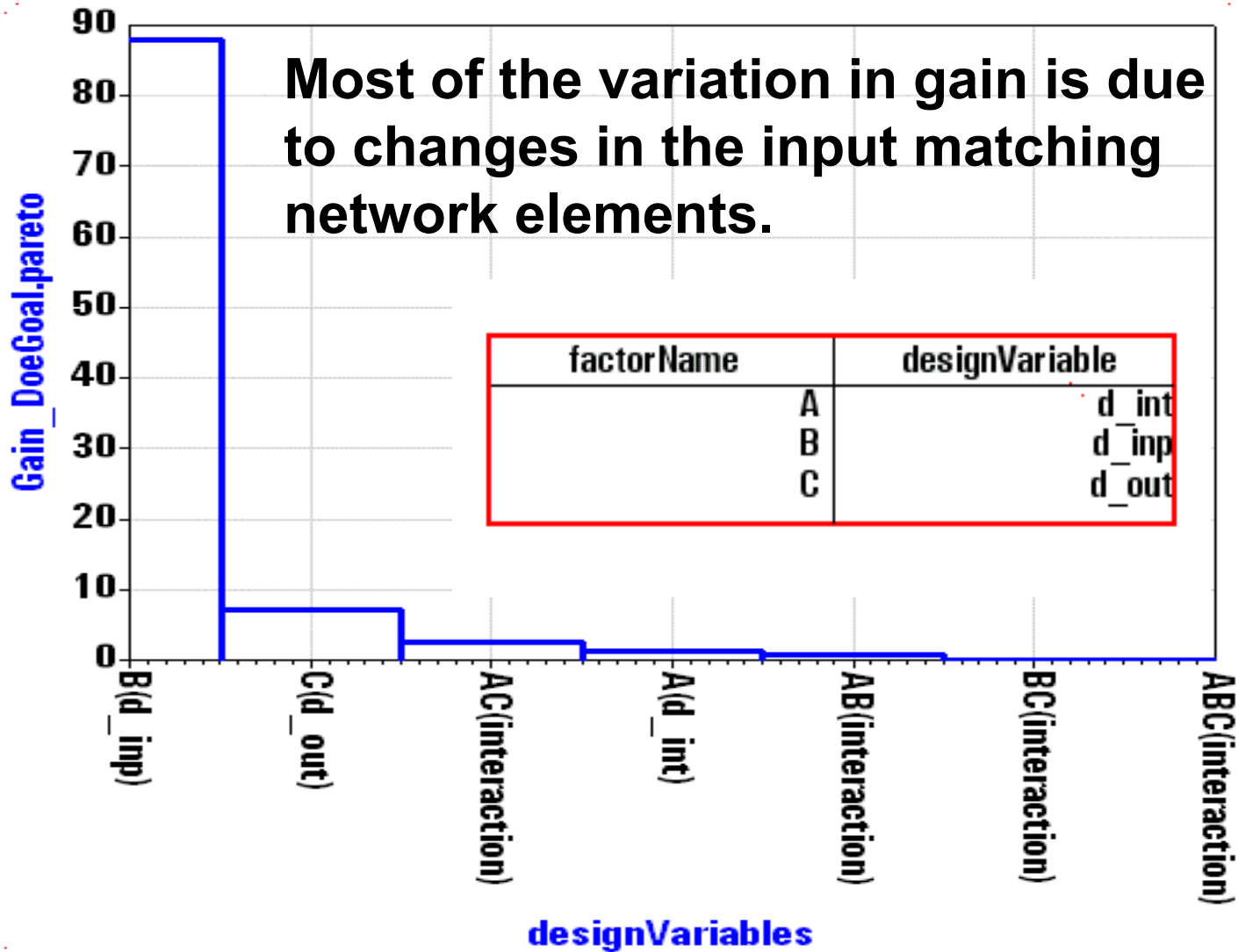
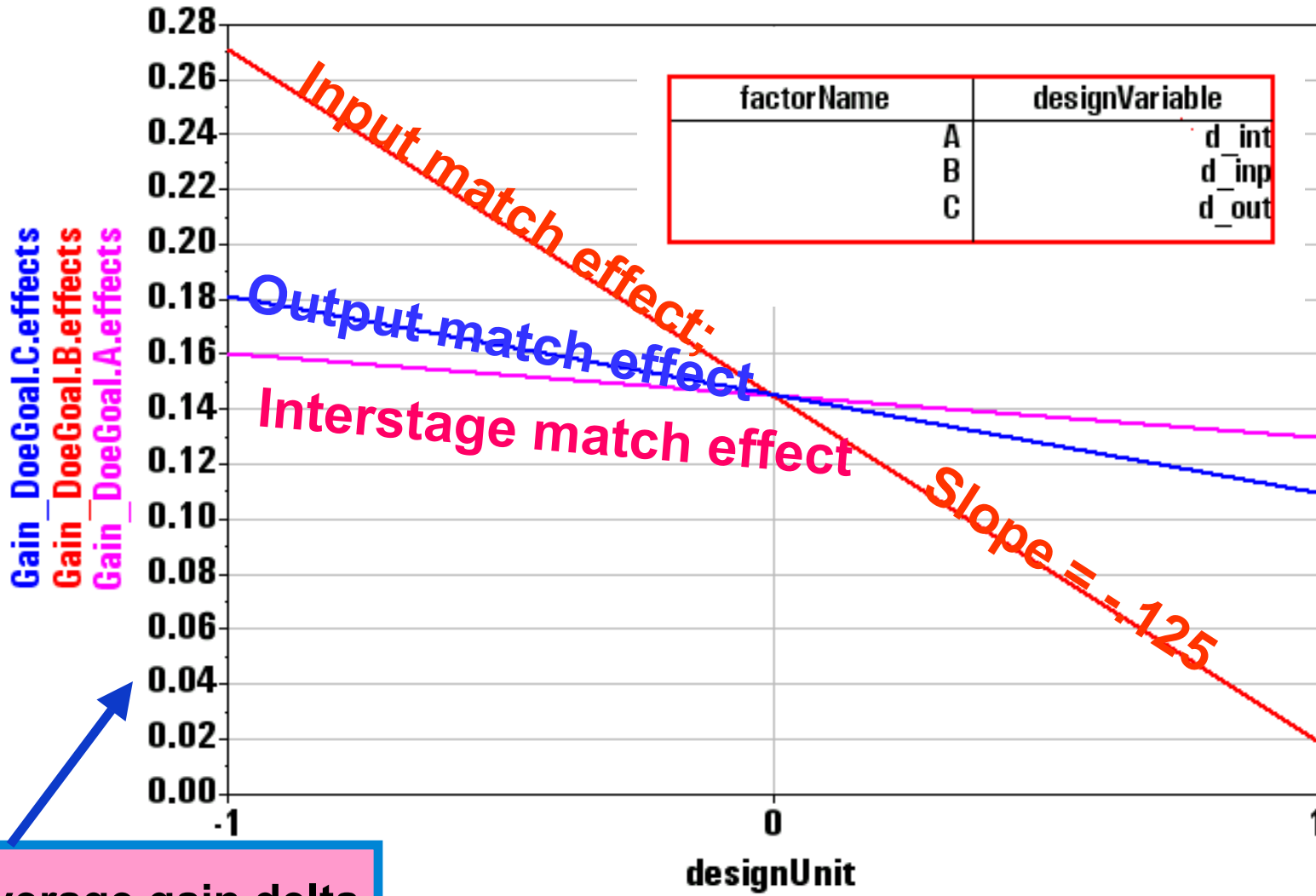
# DOE Effects of Inp, Int, and Out on Gain



Average gain delta response from the 14 dB spec




# DOE Results on NF

| freq     | nf(2)     |           |           |           |           |           |           |           |           |
|----------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|
|          | doelter=0 | doelter=1 | doelter=2 | doelter=3 | doelter=4 | doelter=5 | doelter=6 | doelter=7 | doelter=8 |
| 7.200GHz | 2.548     | 2.500     | 2.455     | 2.392     | 2.545     | 2.498     | 2.452     | 2.389     | 2.463     |
| 7.300GHz | 2.499     | 2.444     | 2.420     | 2.349     | 2.497     | 2.442     | 2.417     | 2.347     | 2.419     |
| 7.400GHz | 2.460     | 2.397     | 2.391     | 2.312     | 2.457     | 2.395     | 2.388     | 2.310     | 2.379     |
| 7.500GHz | 2.422     | 2.352     | 2.366     | 2.278     | 2.420     | 2.350     | 2.363     | 2.276     | 2.344     |
| 7.600GHz | 2.390     | 2.311     | 2.346     | 2.250     | 2.387     | 2.309     | 2.343     | 2.248     | 2.313     |
| 7.700GHz | 2.363     | 2.275     | 2.330     | 2.226     | 2.360     | 2.274     | 2.328     | 2.225     | 2.288     |
| 7.800GHz | 2.341     | 2.246     | 2.320     | 2.207     | 2.339     | 2.245     | 2.317     | 2.206     | 2.268     |
| 7.900GHz | 2.325     | 2.221     | 2.314     | 2.193     | 2.323     | 2.220     | 2.312     | 2.193     | 2.253     |
| 8.000GHz | 2.314     | 2.202     | 2.312     | 2.185     | 2.312     | 2.202     | 2.311     | 2.185     | 2.244     |
| 8.100GHz | 2.310     | 2.191     | 2.316     | 2.183     | 2.308     | 2.190     | 2.315     | 2.183     | 2.240     |
| 8.200GHz | 2.311     | 2.185     | 2.324     | 2.185     | 2.310     | 2.186     | 2.323     | 2.186     | 2.242     |
| 8.300GHz | 2.317     | 2.187     | 2.338     | 2.194     | 2.317     | 2.187     | 2.337     | 2.195     | 2.249     |
| 8.400GHz | 2.330     | 2.194     | 2.356     | 2.208     | 2.329     | 2.195     | 2.355     | 2.210     | 2.263     |
| 8.500GHz | 2.347     | 2.208     | 2.377     | 2.228     | 2.347     | 2.210     | 2.377     | 2.230     | 2.281     |
| 8.600GHz | 2.369     | 2.228     | 2.403     | 2.253     | 2.370     | 2.230     | 2.404     | 2.255     | 2.304     |
| 8.700GHz | 2.396     | 2.254     | 2.434     | 2.284     | 2.397     | 2.257     | 2.435     | 2.286     | 2.334     |
| 8.800GHz | 2.429     | 2.287     | 2.469     | 2.320     | 2.430     | 2.290     | 2.471     | 2.323     | 2.368     |






# DOE Pareto of Effects on NF

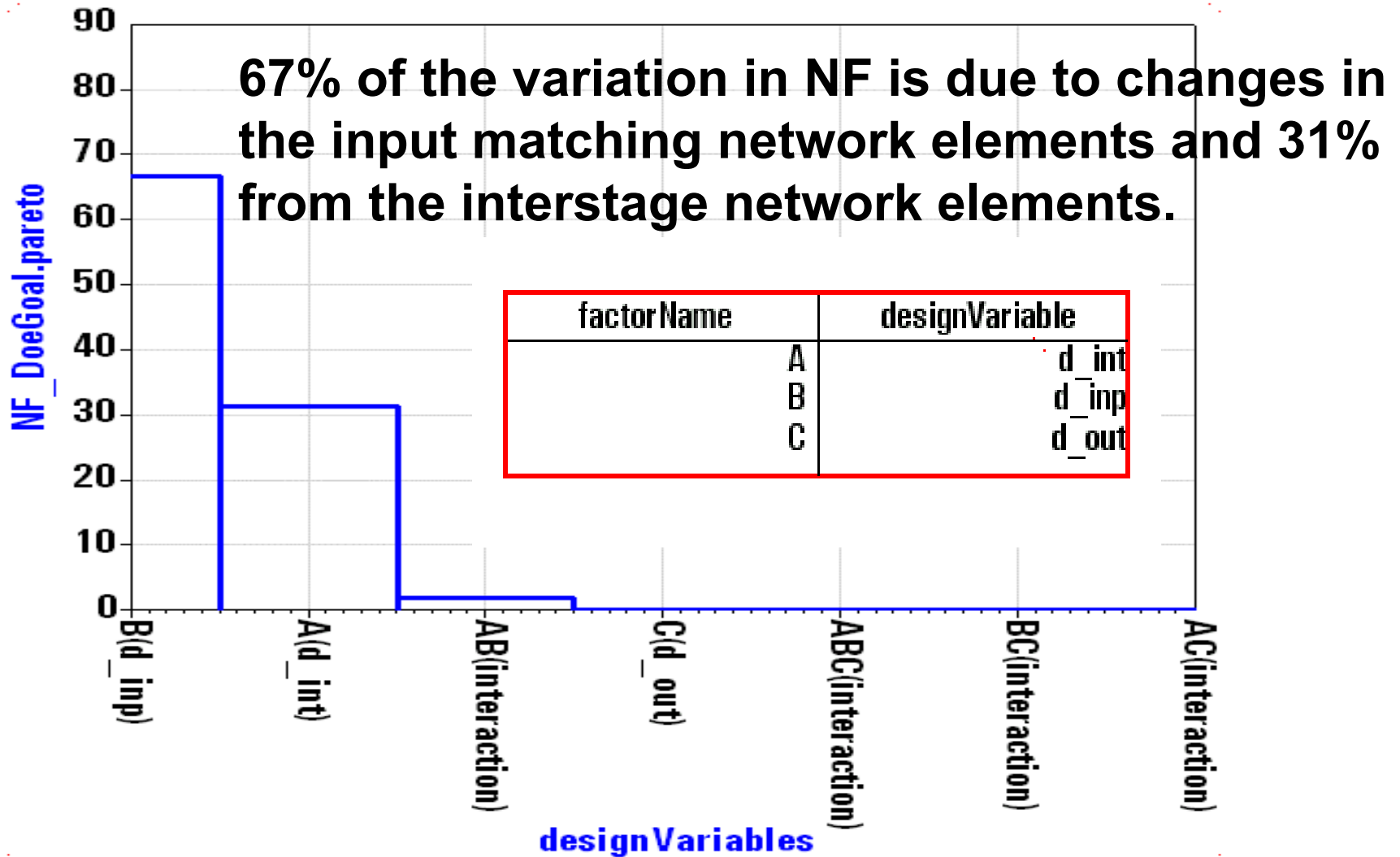

# DOE Effects of Inp, Int, and Out on NF

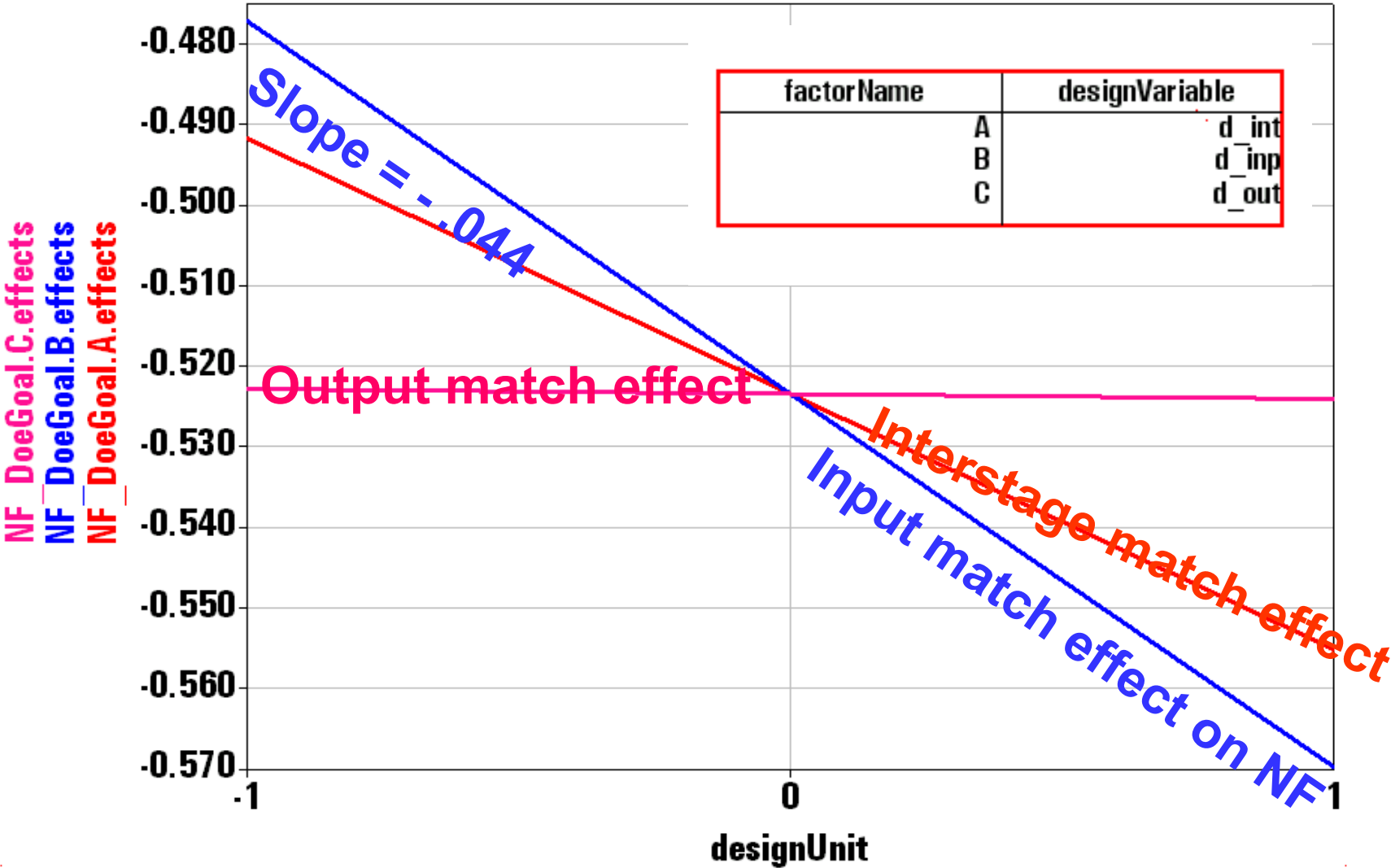


# DOE Results on S22


| freq     | dB(S(2,2)) |           |           |           |           |           |           |           |           |
|----------|------------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|
|          | doelter=0  | doelter=1 | doelter=2 | doelter=3 | doelter=4 | doelter=5 | doelter=6 | doelter=7 | doelter=8 |
| 7.200GHz | -14.187    | -16.167   | -14.117   | -16.219   | -12.094   | -12.947   | -11.905   | -12.777   | -14.013   |
| 7.300GHz | -14.645    | -16.784   | -14.582   | -16.819   | -11.926   | -12.820   | -11.771   | -12.692   | -13.956   |
| 7.400GHz | -14.957    | -17.152   | -14.903   | -17.173   | -11.790   | -12.749   | -11.667   | -12.668   | -13.866   |
| 7.500GHz | -15.134    | -17.297   | -15.088   | -17.297   | -11.695   | -12.757   | -11.606   | -12.724   | -13.777   |
| 7.600GHz | -15.196    | -17.262   | -15.156   | -17.243   | -11.654   | -12.860   | -11.598   | -12.876   | -13.719   |
| 7.700GHz | -15.175    | -17.121   | -15.148   | -17.098   | -11.677   | -13.079   | -11.656   | -13.149   | -13.716   |
| 7.800GHz | -15.114    | -16.948   | -15.105   | -16.937   | -11.776   | -13.436   | -11.793   | -13.571   | -13.788   |
| 7.900GHz | -15.054    | -16.809   | -15.066   | -16.814   | -11.970   | -13.975   | -12.026   | -14.178   | -13.961   |
| 8.000GHz | -15.023    | -16.730   | -15.056   | -16.753   | -12.271   | -14.726   | -12.367   | -15.001   | -14.256   |
| 8.100GHz | -15.087    | -16.830   | -15.149   | -16.880   | -12.718   | -15.777   | -12.862   | -16.148   | -14.725   |
| 8.200GHz | -15.240    | -17.040   | -15.329   | -17.107   | -13.323   | -17.187   | -13.516   | -17.660   | -15.387   |
| 8.300GHz | -15.512    | -17.362   | -15.640   | -17.450   | -14.139   | -19.117   | -14.403   | -19.750   | -16.261   |
| 8.400GHz | -15.918    | -17.752   | -16.082   | -17.841   | -15.225   | -21.756   | -15.570   | -22.561   | -17.425   |
| 8.500GHz | -16.481    | -18.147   | -16.669   | -18.204   | -16.689   | -25.163   | -17.124   | -25.886   | -18.893   |
| 8.600GHz | -17.193    | -18.417   | -17.422   | -18.441   | -18.676   | -27.061   | -19.279   | -26.729   | -20.663   |
| 8.700GHz | -18.069    | -18.456   | -18.325   | -18.430   | -21.569   | -24.293   | -22.443   | -23.515   | -22.493   |
| 8.800GHz | -19.063    | -18.175   | -19.315   | -18.103   | -26.232   | -20.746   | -27.641   | -20.186   | -23.413   |



# DOE Pareto of Effects on S22

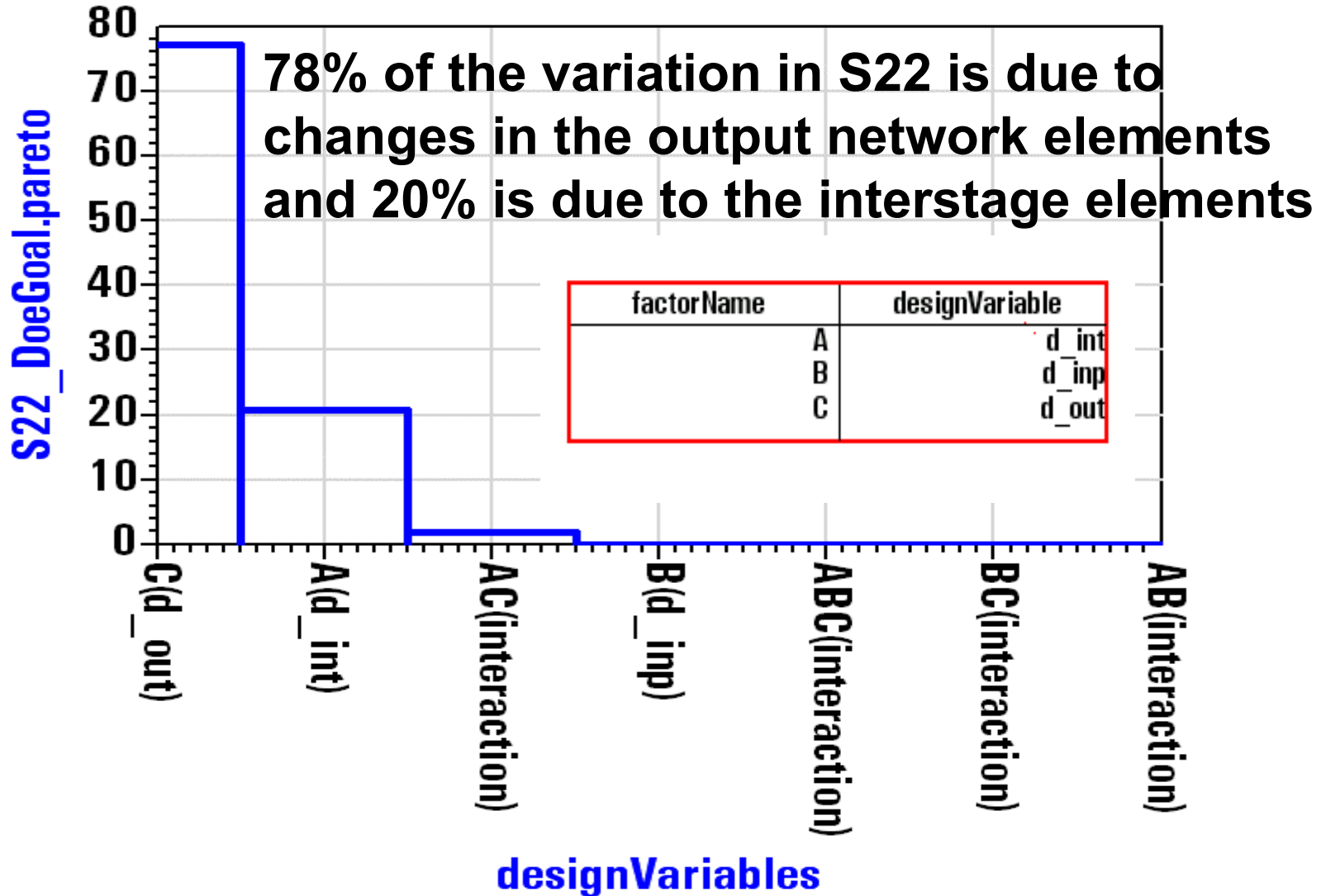
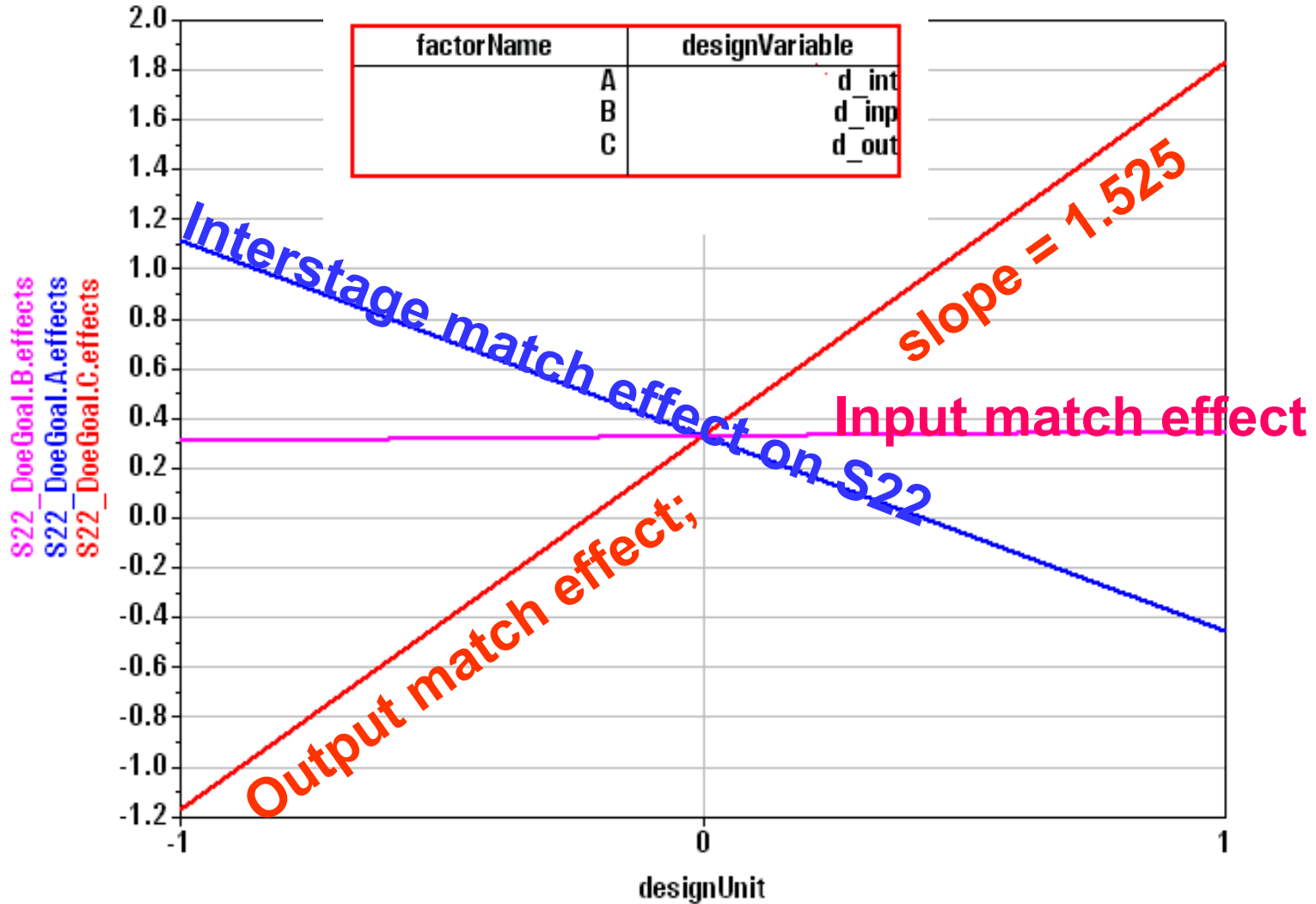
# DOE Effects of Inp, Int, and Out on S22




# DOE Conclusion

- **Output matching network is sensitive to the output match spec and is contributing significantly to the low yield**
- **Interstage matching network is also contributing to the low yield**




# Action: Redesign the Output Match

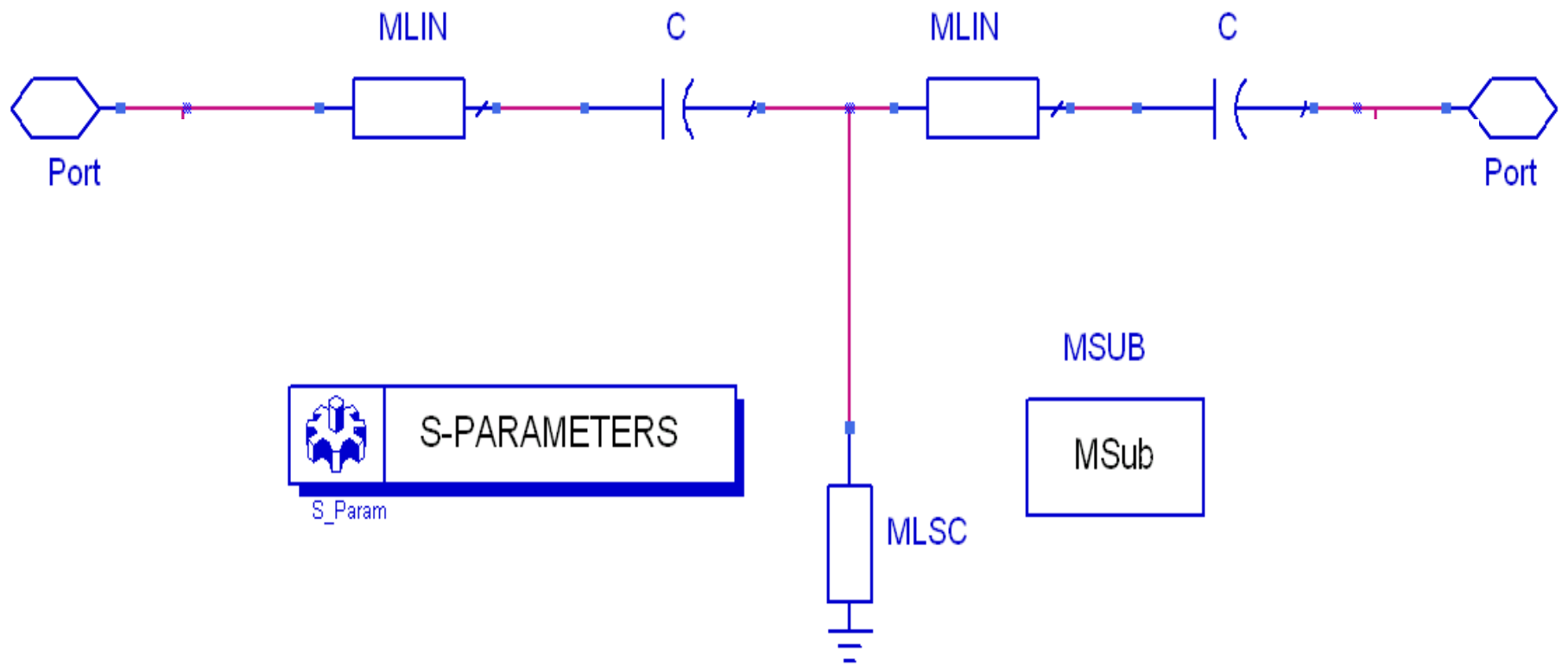

 S-PARAMETERS  
S\_Param

# LNA Response with New Output Network

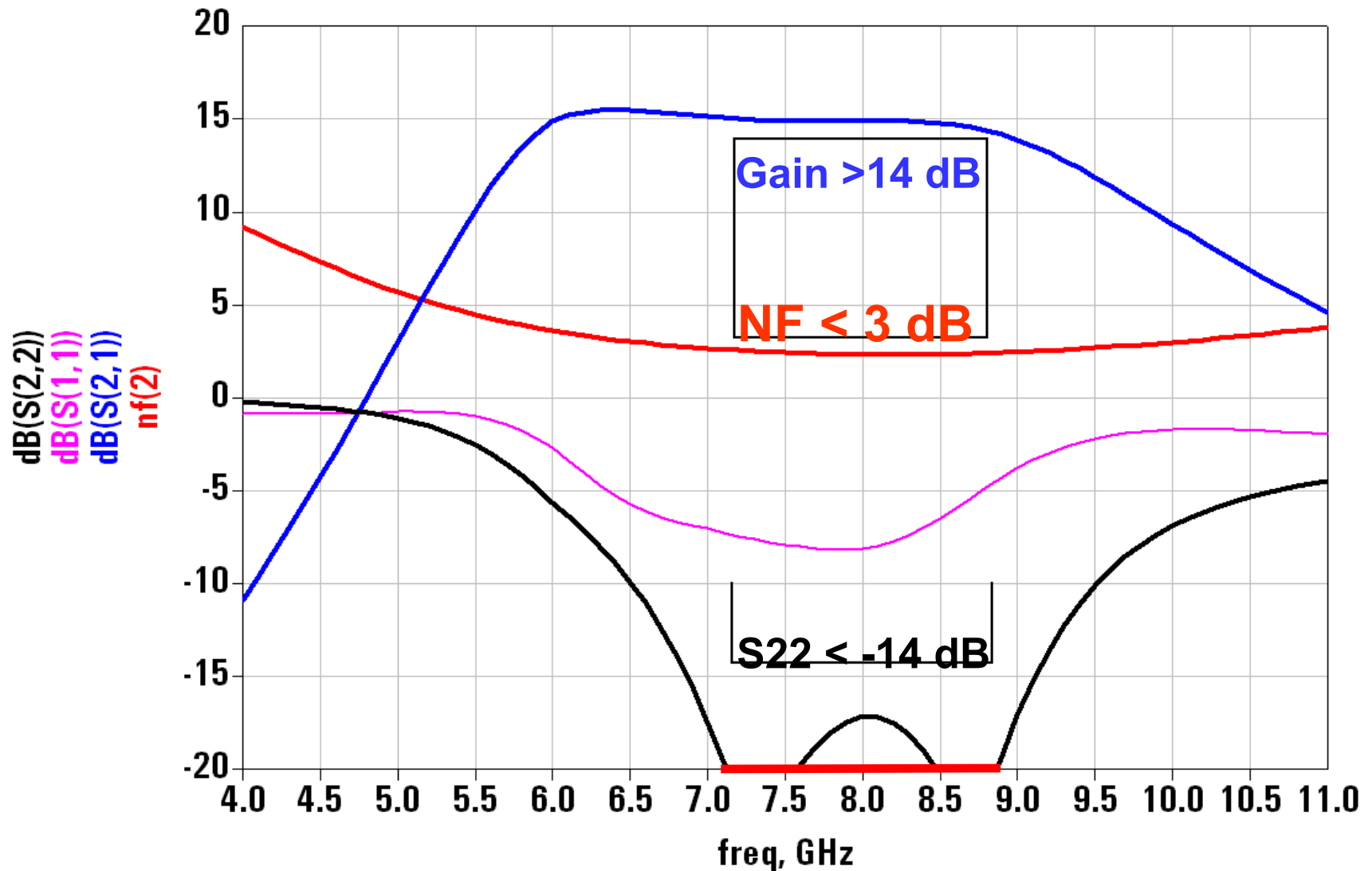






# New Overall Yield of LNA : 39.5%


## Statistical Analysis of LNA Performance

- 5% Gaussian variation in lumped
- Line widths vary  $\pm 1/2$   $\mu\text{m}$
- Substrate height  $100 \mu\text{m} \pm 3 \mu\text{m}$
- Substrate  $\epsilon_r$   $12.9 \pm 5\%$
- 42 FET samples

| NumFail | NumPass | Yield |
|---------|---------|-------|
| 121.00  | 79.00   | 39.50 |

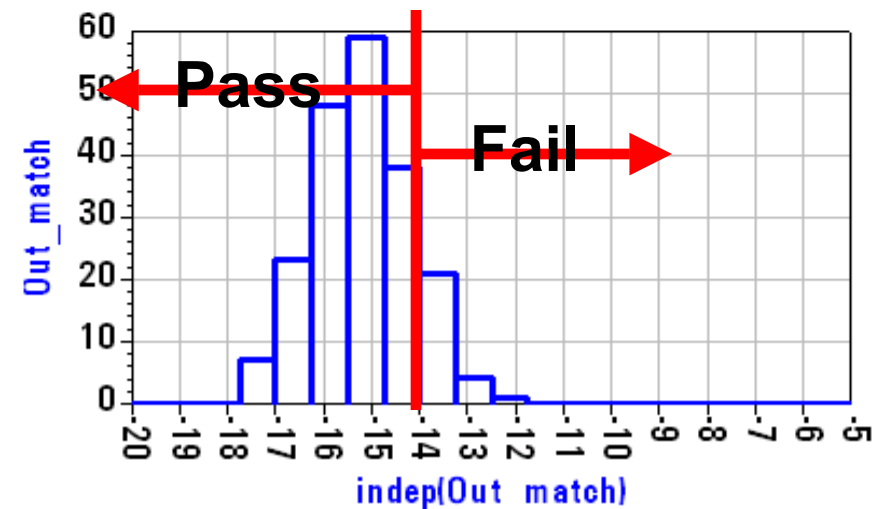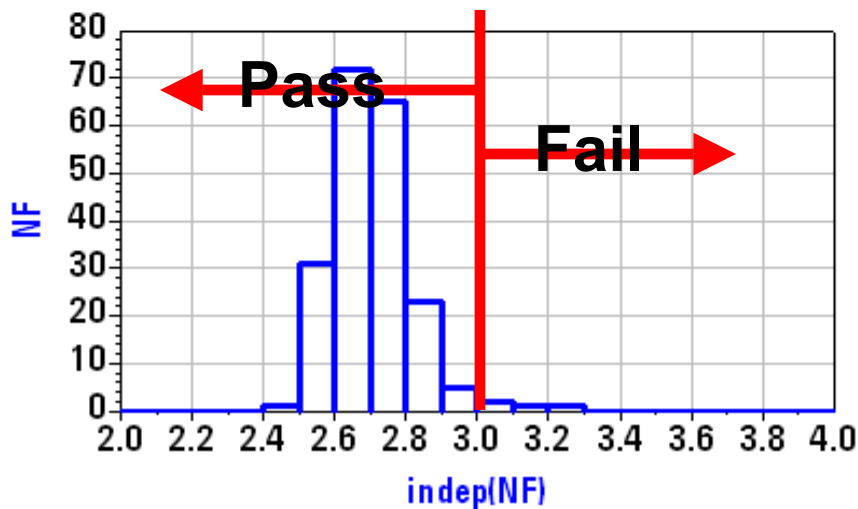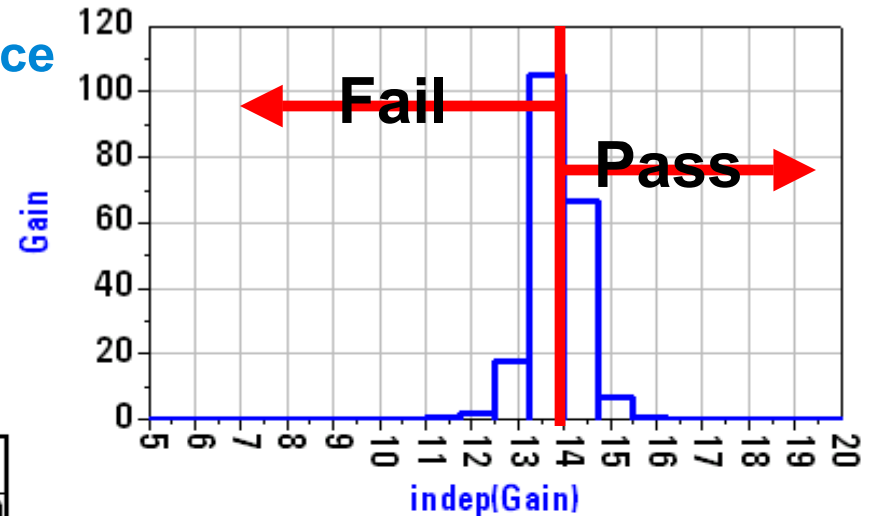

# MMIC Statistical Design Process

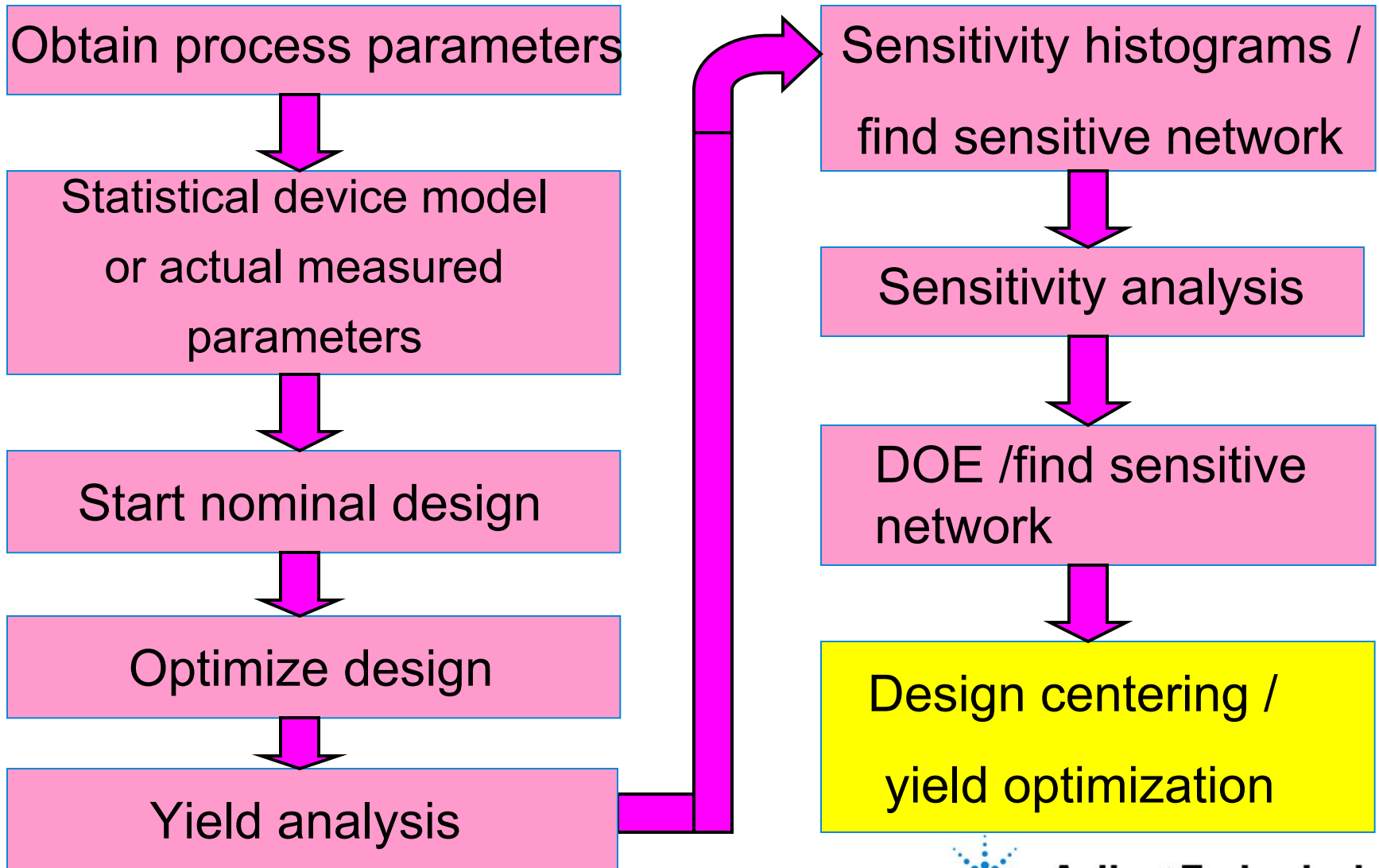

# Yield Optimization (Design Centering)

## A Recap:

- We have reduced the sensitivity by redesigning the output matching network.
- The new matching network has also helped to reduce the output response variability span.
- Next we need to center the design for maximum yield using the yield optimization tool (also called design centering).



# “Design Centering” – Simplified Setup

**Yield optimization**  
# iterations=50  
use all specs=yes  
...etc.

Yield optimization runs optimization and yield together and optimizes for maximum yield

**S-parameters**  
Yield sweep  
start = 7 GHz  
stop = 9 GHz  
step = .1 GHz

**Yield spec**  
NF spec  
max NF = 3 dB  
use yield sweep

**Yield spec**  
Gain spec  
min gain=14 dB  
use yield sweep

**Yield spec**  
S22 spec  
max S22=-14 dB  
use yield sweep






# Final Yield after Design Centering: 97.4%

## Statistical Analysis of LNA Performance

- 5% Gaussian variation in lumped
- Line widths vary  $\pm 1/2 \mu\text{m}$
- Substrate height  $100 \mu\text{m} \pm 3 \mu\text{m}$
- Substrate  $\epsilon_r$   $12.9 \pm 5\%$
- 42 FET samples

| NumFail | NumPass | Yield |
|---------|---------|-------|
| 26.00   | 974.00  | 97.40 |

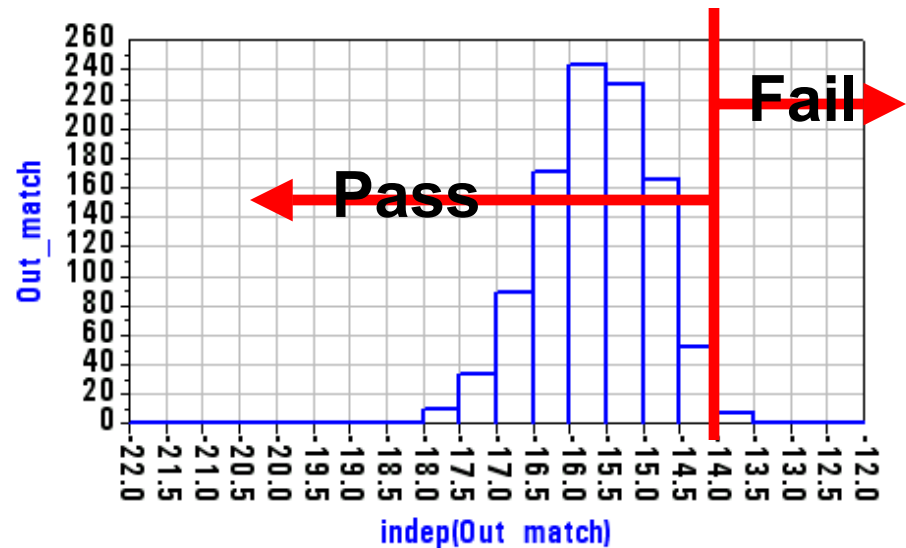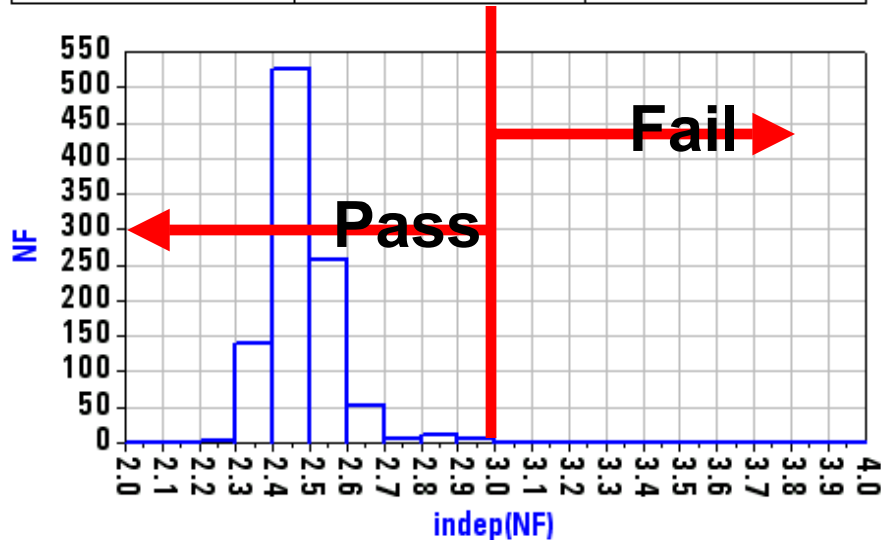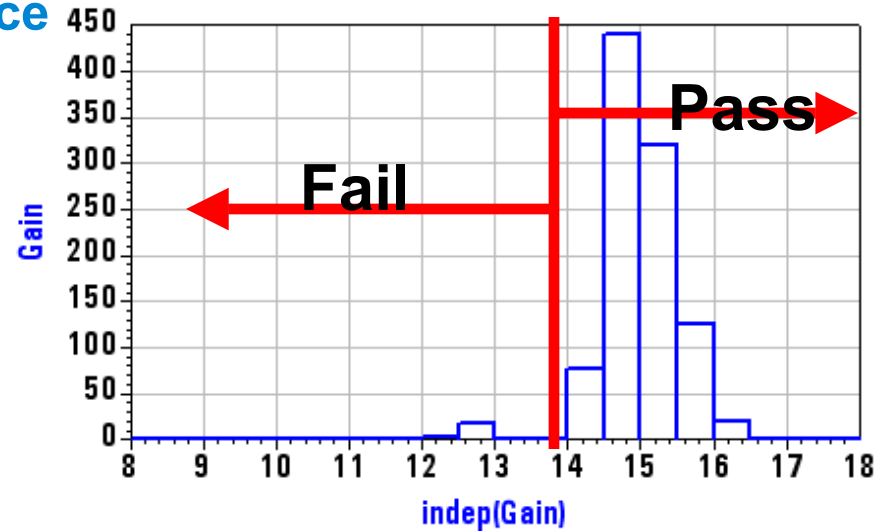


# Response of Yield Trials


## Statistical Analysis of LNA Performance

- 5% Gaussian variation in lumped
- Line widths vary  $\pm 1/2 \mu\text{m}$
- Substrate height  $100 \mu\text{m} \pm 3 \mu\text{m}$
- Substrate  $\epsilon_r$   $12.9 \pm 5\%$
- 42 FET samples


| NumFail | NumPass | Yield |
|---------|---------|-------|
| 26.00   | 974.00  | 97.40 |

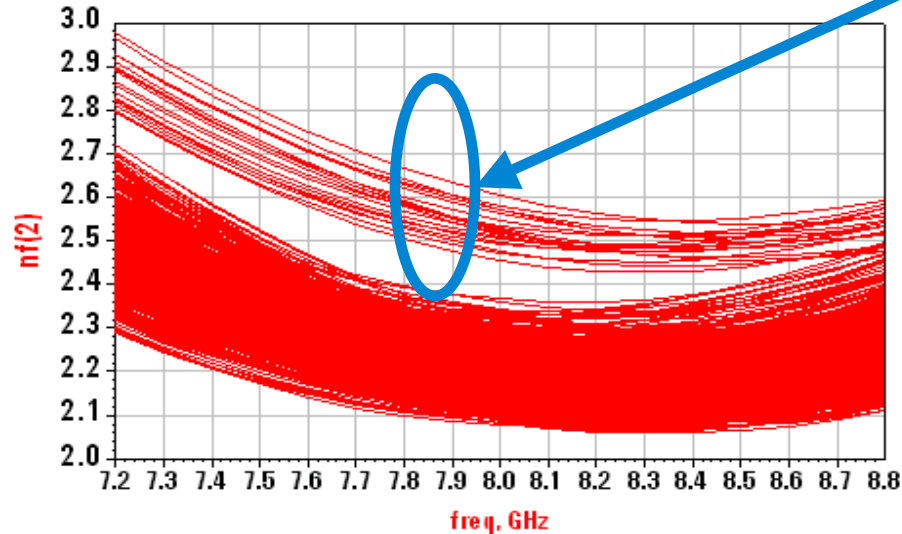

**Note: Low-performance devices**

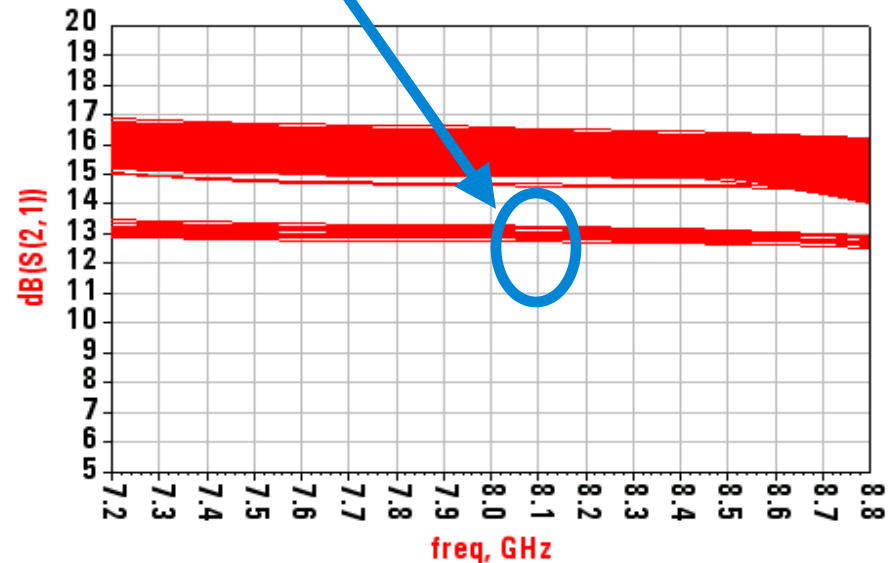
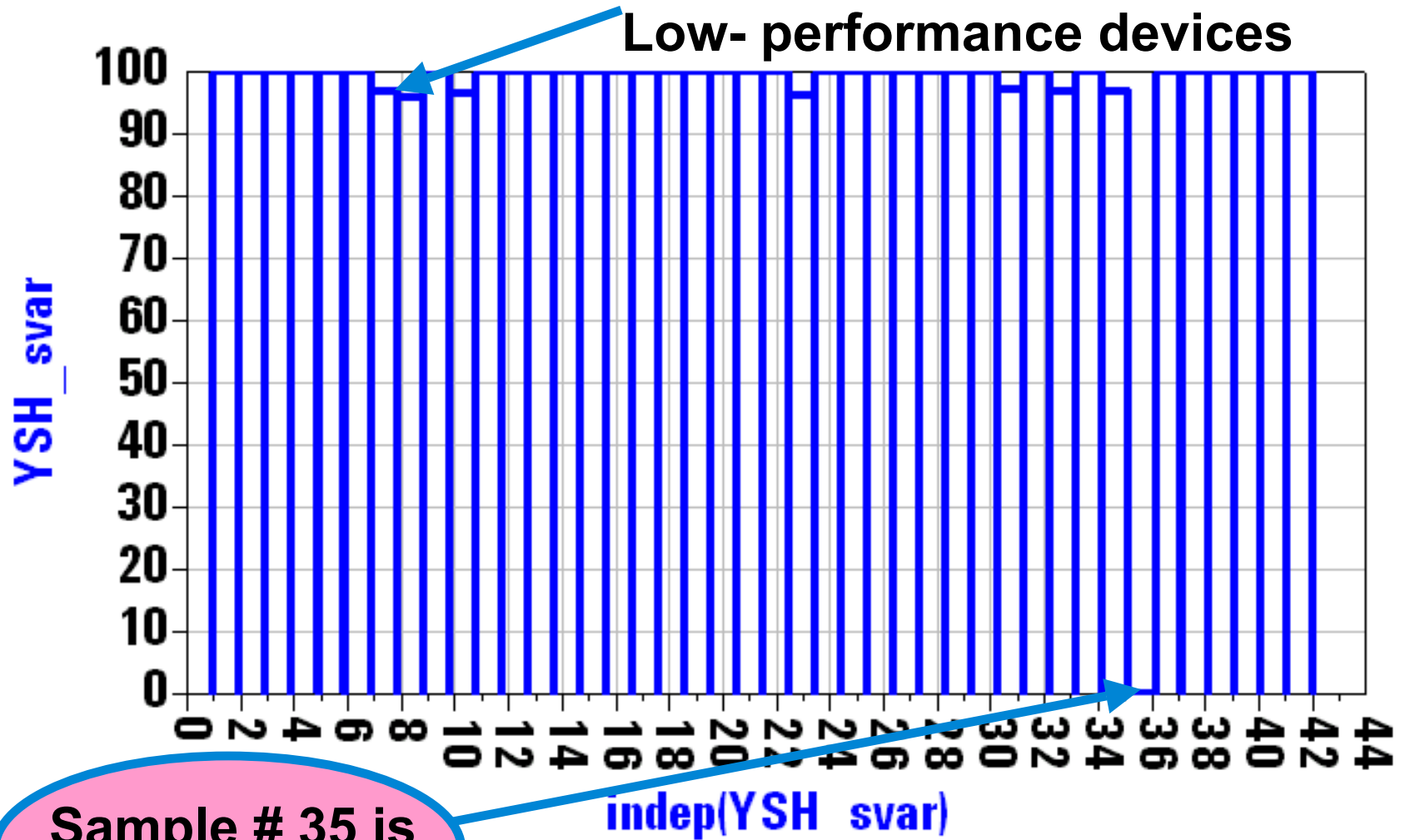
# Yield Sensitivity with Respect to Sample




Sample # 35 is a bad sample




# Yield Sensitivity with Respect to FET1\_R1

Yield now is not sensitive to FET1\_R1

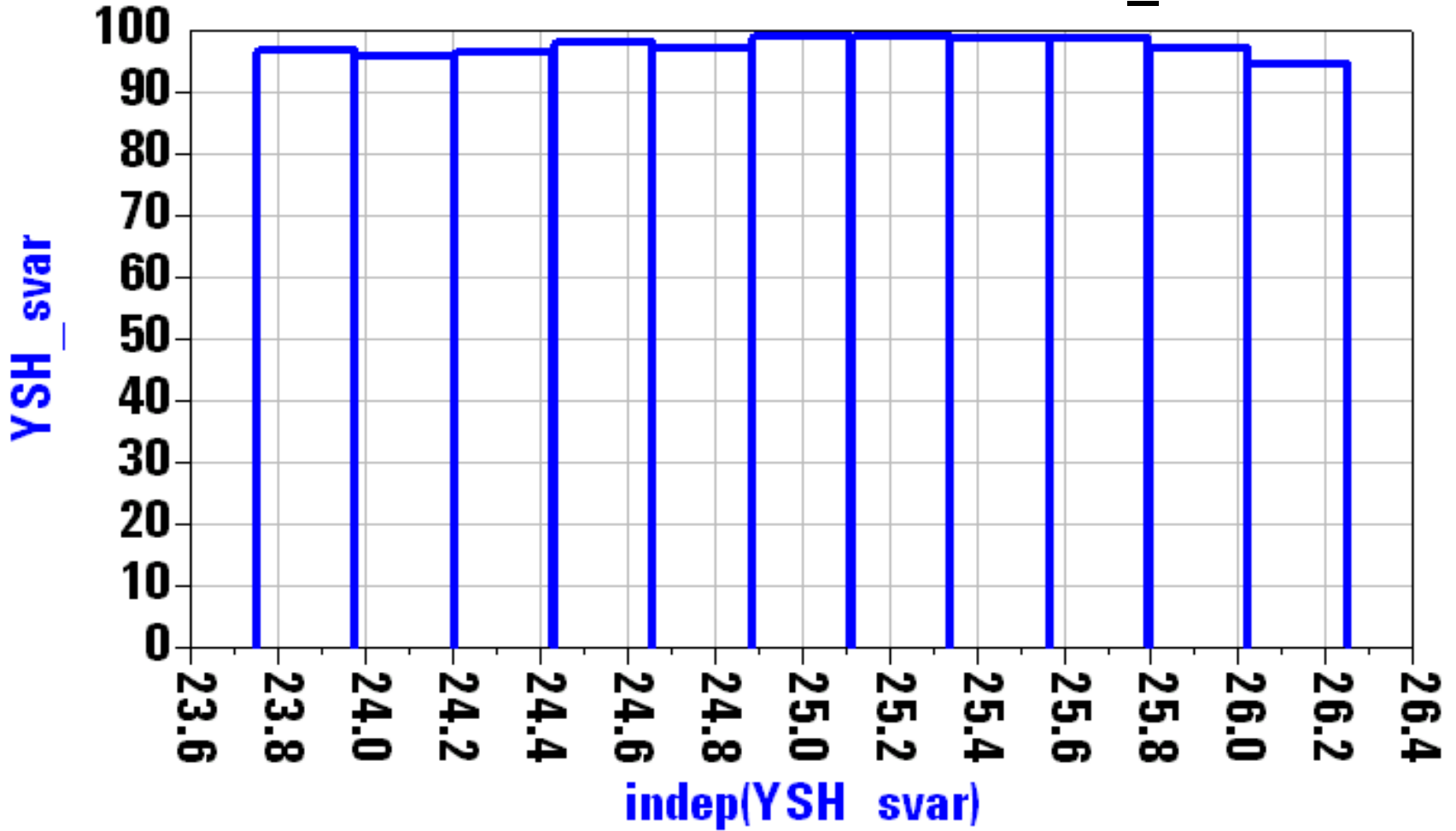




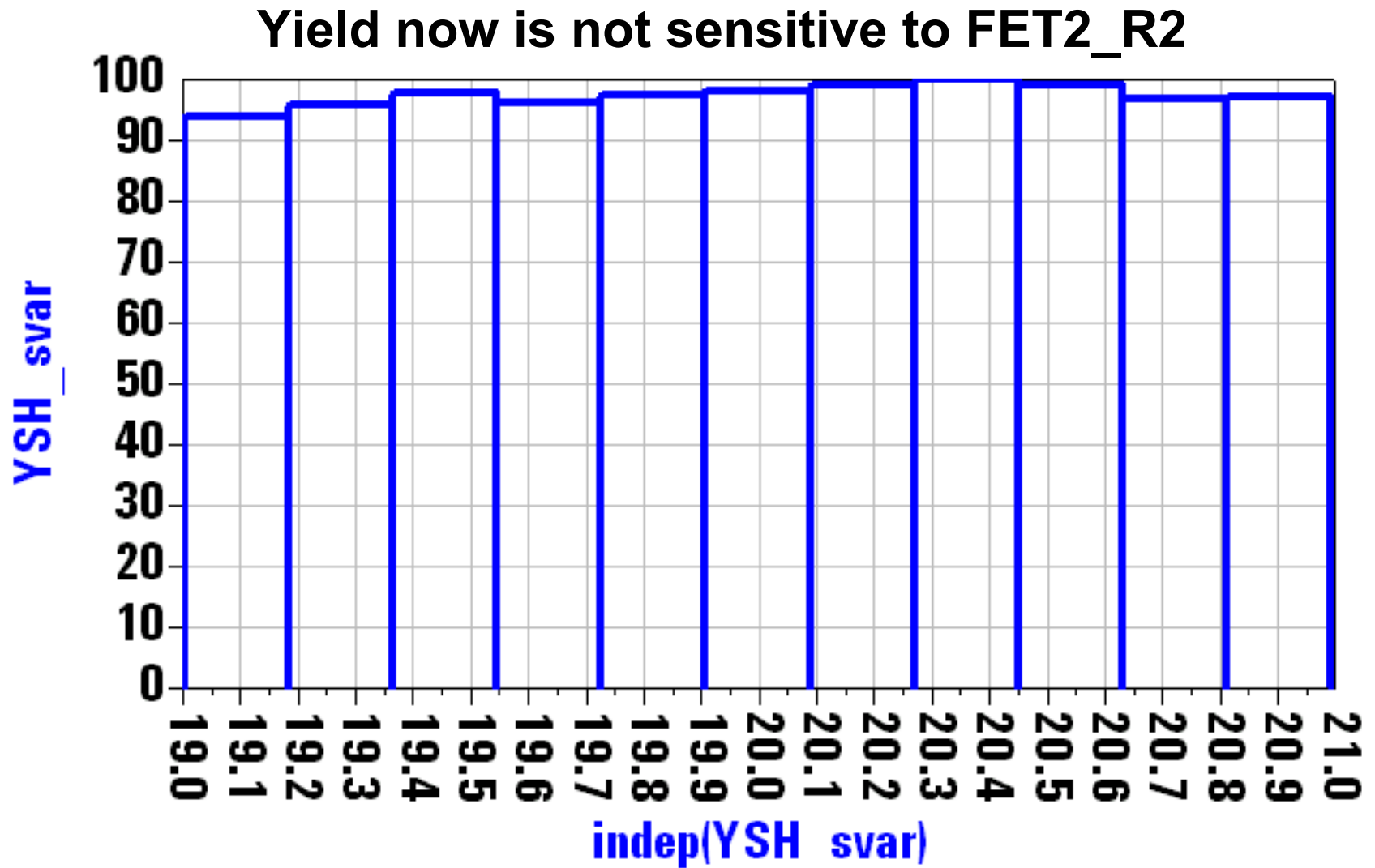
# Yield Sensitivity with Respect to FET2\_R2



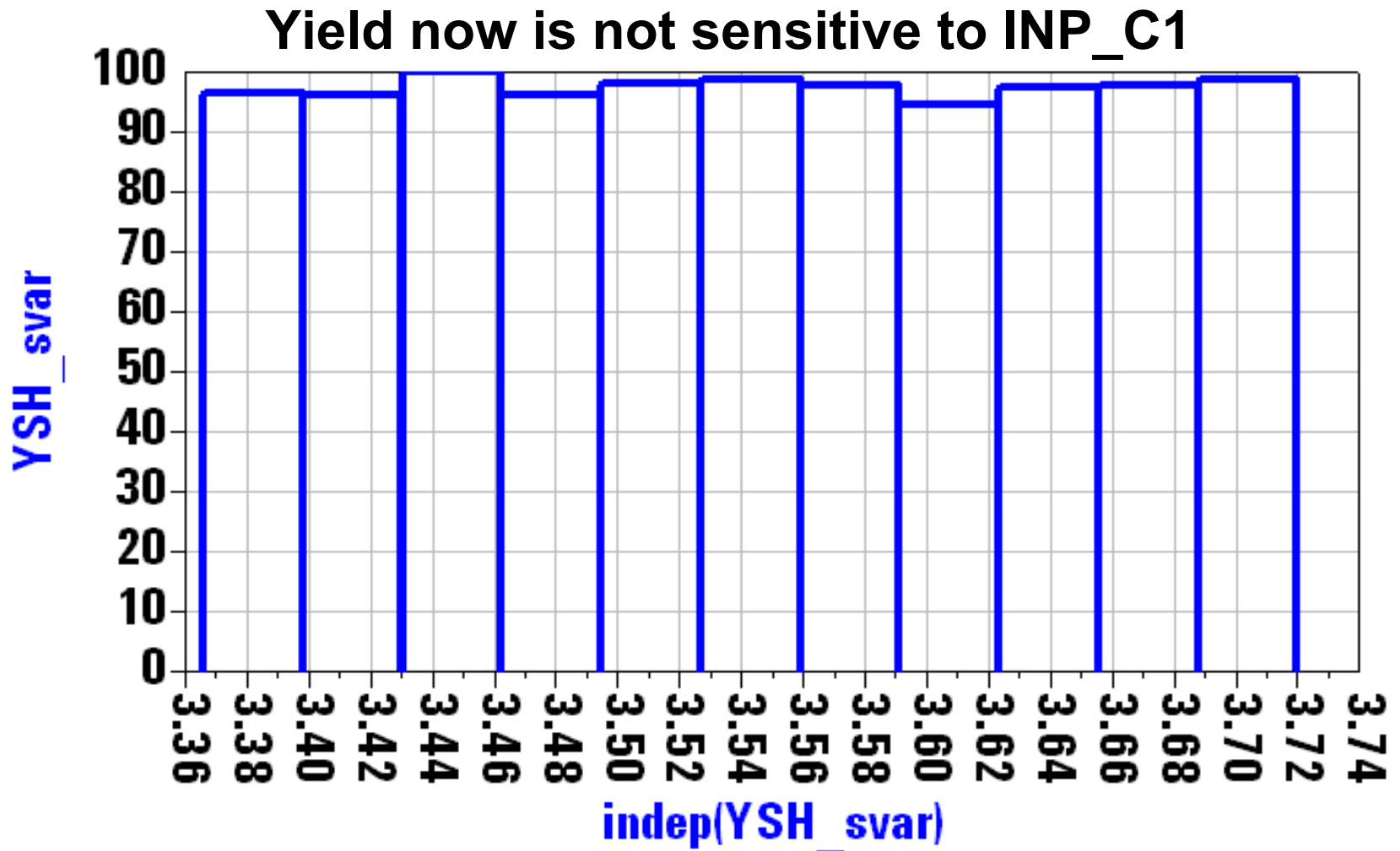
# Yield Sensitivity with Respect to INP\_C1



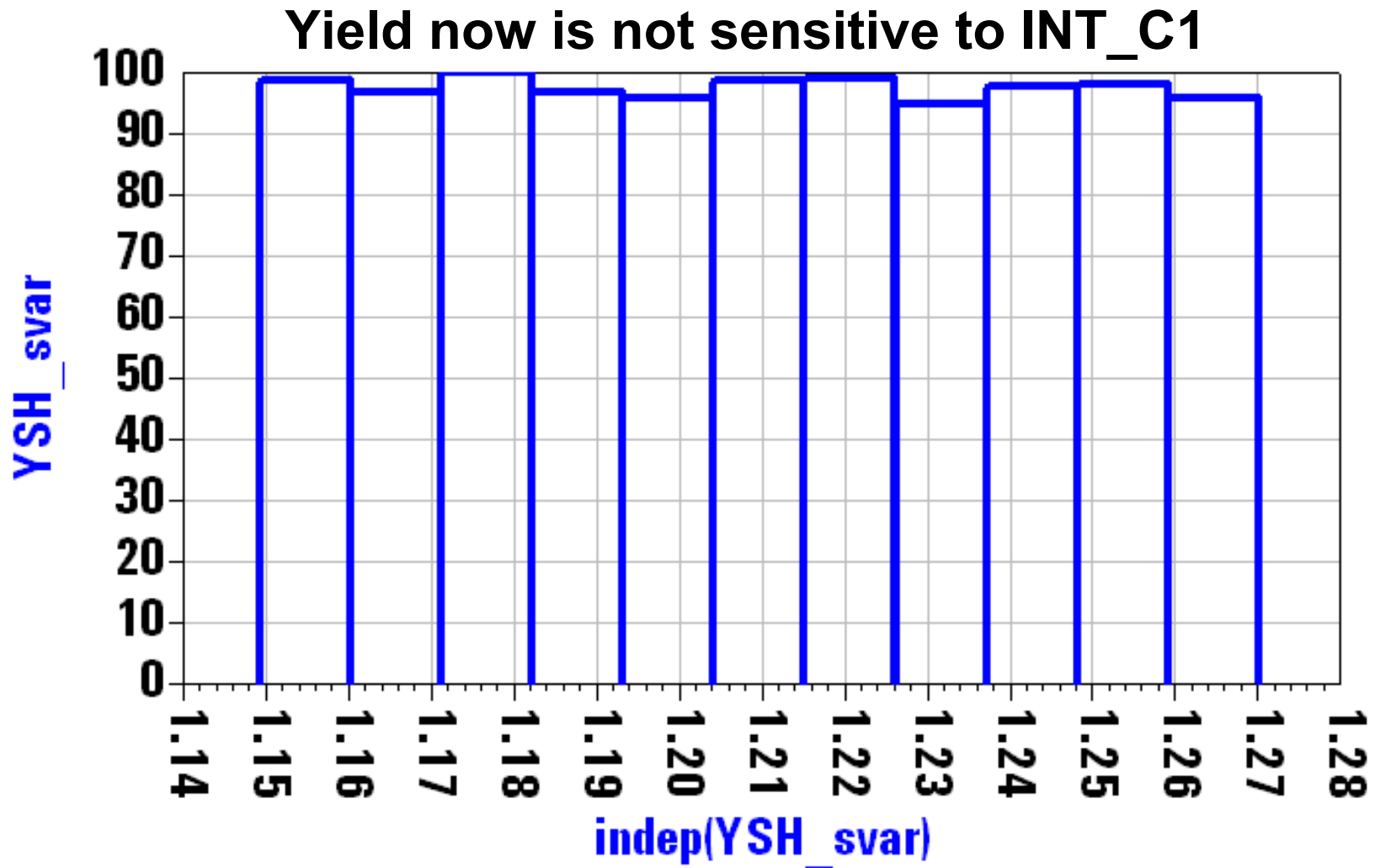
# Yield Sensitivity with Respect to INT\_C1



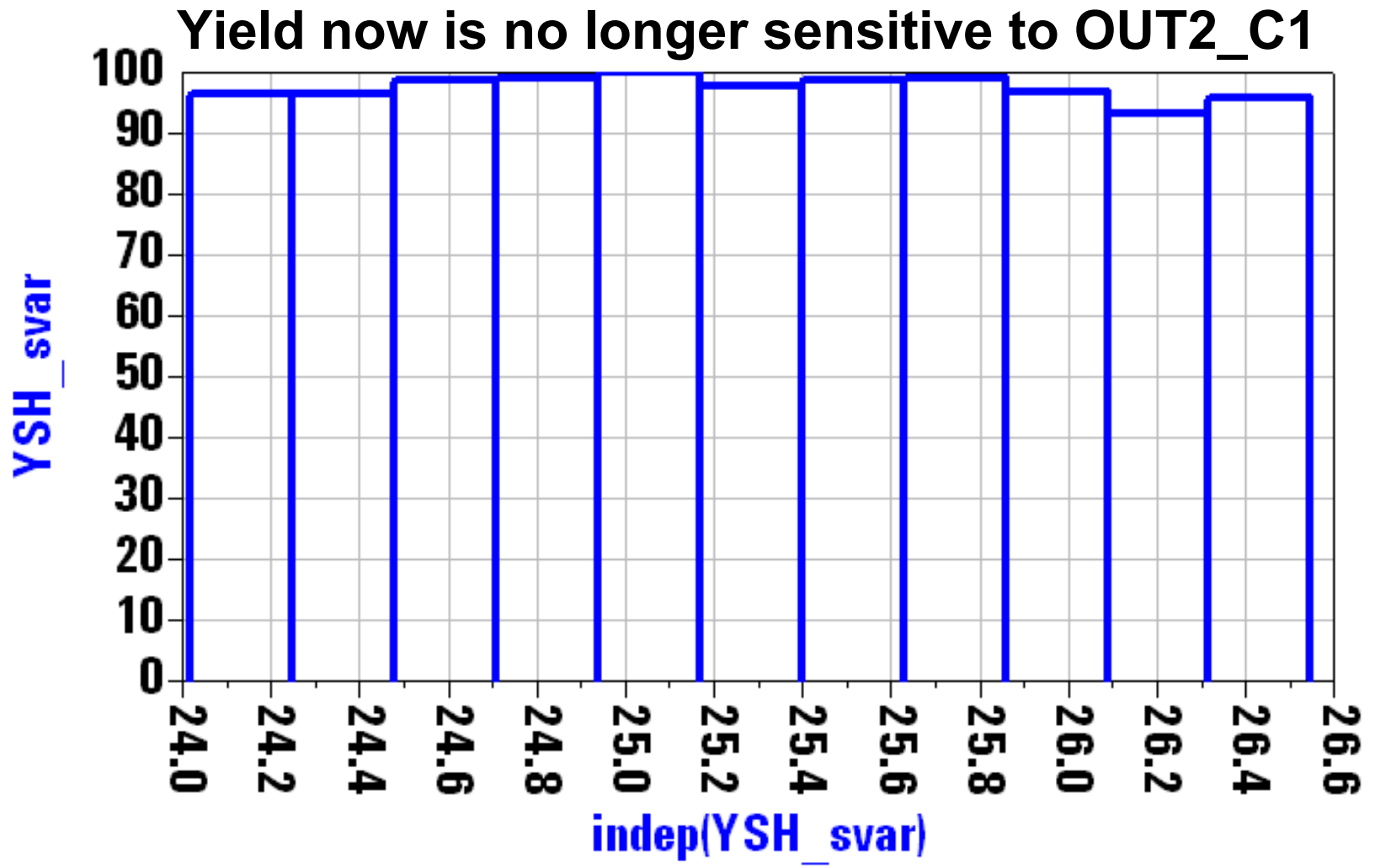
# Yield Sensitivity with Respect to OUT2\_C1


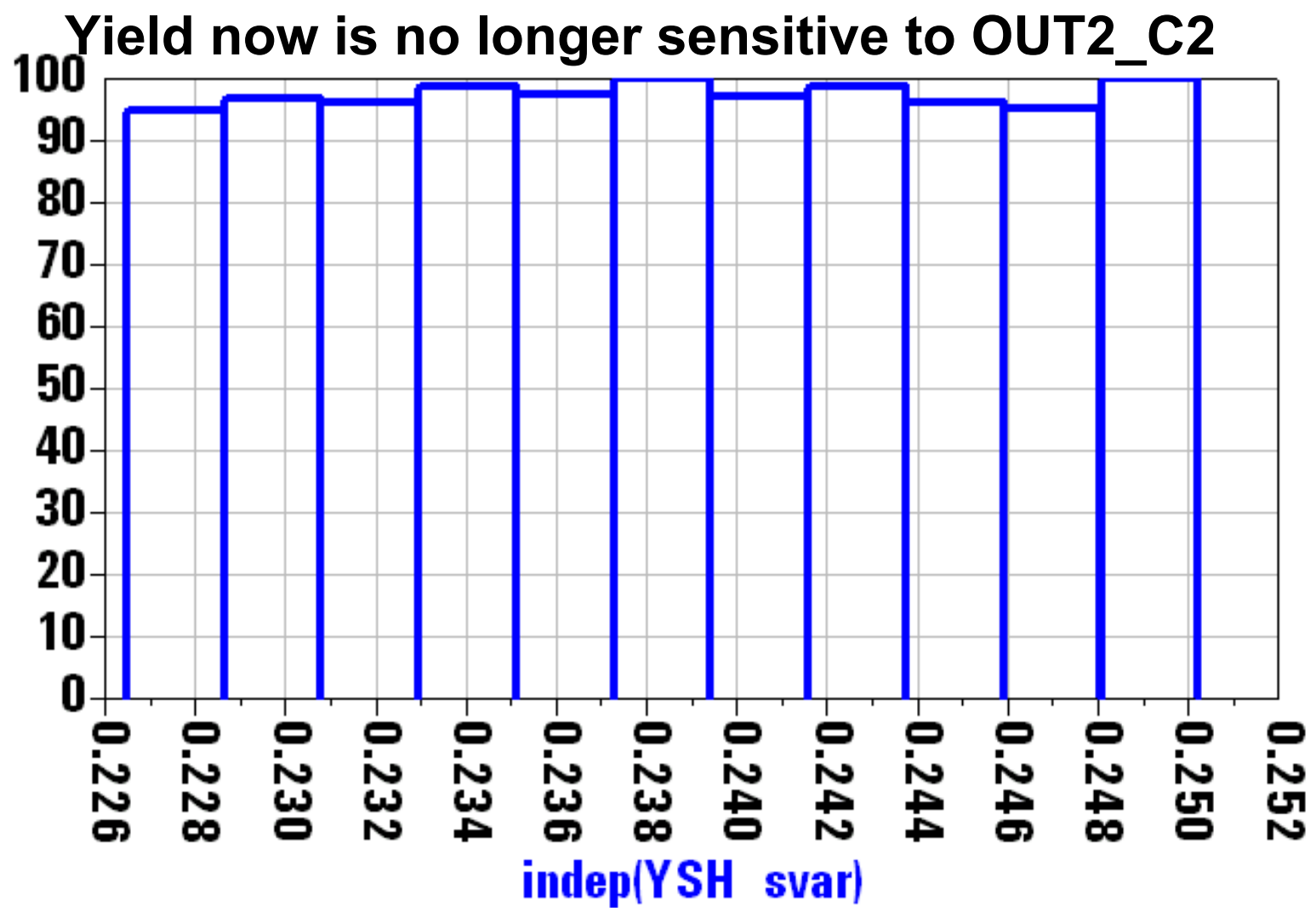
# Yield Sensitivity with Respect to OUT2\_C2



# Recap: MMIC Statistical Design Process

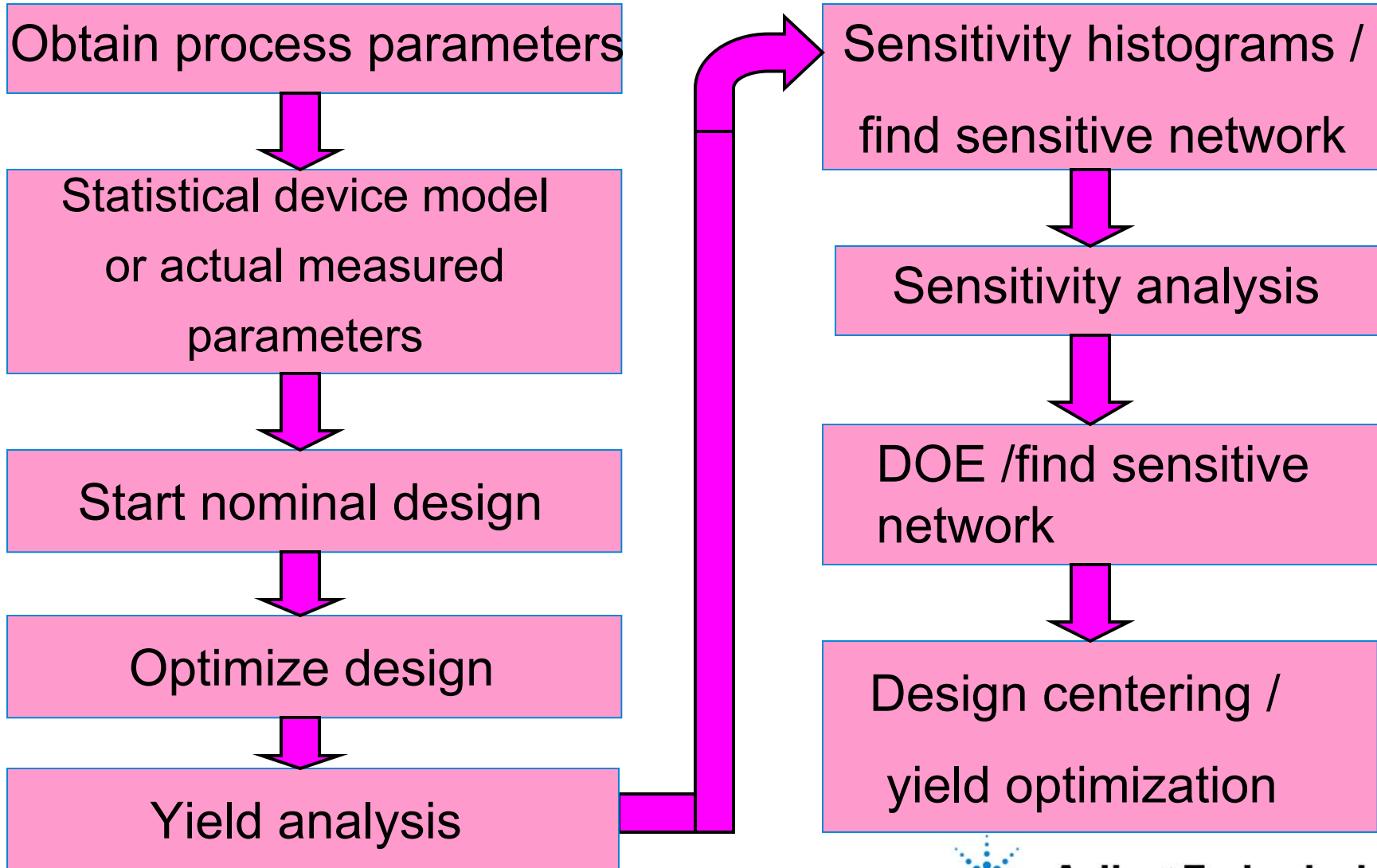

# Conclusion (ADS 2001 Statistical Design Package)

- **Advanced optimization technique**
- **Yield analysis**
- **Yield optimization or design centering**
- **Sensitivity analysis**
- **Design of experiment (DOE) with full supporting plots.**
- **Yield sensitivity histograms.**
- **Correlation analysis with any kind of distribution, including log normal distribution, which is heavily used in RFIC design.**
- **Mismatch models statistical analysis of devices from different sites on the wafer, from different wafers, and from different lots.**



## **A Brief Tutorial on Design of Experiments (DOE)**





# DOE – A Brief Tutorial

Start by choosing variables that affect the response

**Choose three variables with their +1 and -1 :**

Width of lines (W)

$$W = W_{\text{nom}} \pm .5 \text{ um}$$

Resistors (R)

$$R = R_{\text{nom}} \pm 5\%$$

Capacitors (C)

$$C = C_{\text{nom}} \pm 5\%$$

Example: For W

-1 corresponds to 9.5 um

+1 corresponds to 10.5 um

0 corresponds to nominal value, 10um



# Main Effect of Capacitors, C on Gain

| W  | R  | C  | Gain  |
|----|----|----|-------|
| -1 | -1 | -1 | 12.85 |
| 1  | -1 | -1 | 13.01 |
| -1 | 1  | -1 | 14.52 |
| 1  | 1  | -1 | 14.71 |
| -1 | -1 | 1  | 12.93 |
| 1  | -1 | 1  | 13.09 |
| -1 | 1  | 1  | 14.61 |
| 1  | 1  | 1  | 14.81 |

Average gain for C=-1

13.7725 dB (yellow)

Average gain for C=1

13.86 dB (blue)

Slope= .044



# Main Effect of Resistors, R on Gain

| W  | R  | C  | Gain  |
|----|----|----|-------|
| -1 | -1 | -1 | 12.85 |
| 1  | -1 | -1 | 13.01 |
| -1 | 1  | -1 | 14.52 |
| 1  | 1  | -1 | 14.71 |
| -1 | -1 | 1  | 12.93 |
| 1  | -1 | 1  | 13.09 |
| -1 | 1  | 1  | 14.61 |
| 1  | 1  | 1  | 14.81 |

Average gain for R=-1

12.97 dB (blue)


Average gain for R=1

14.6625 dB (green)

Slope = .85



# Plotting Main Effects of C and R

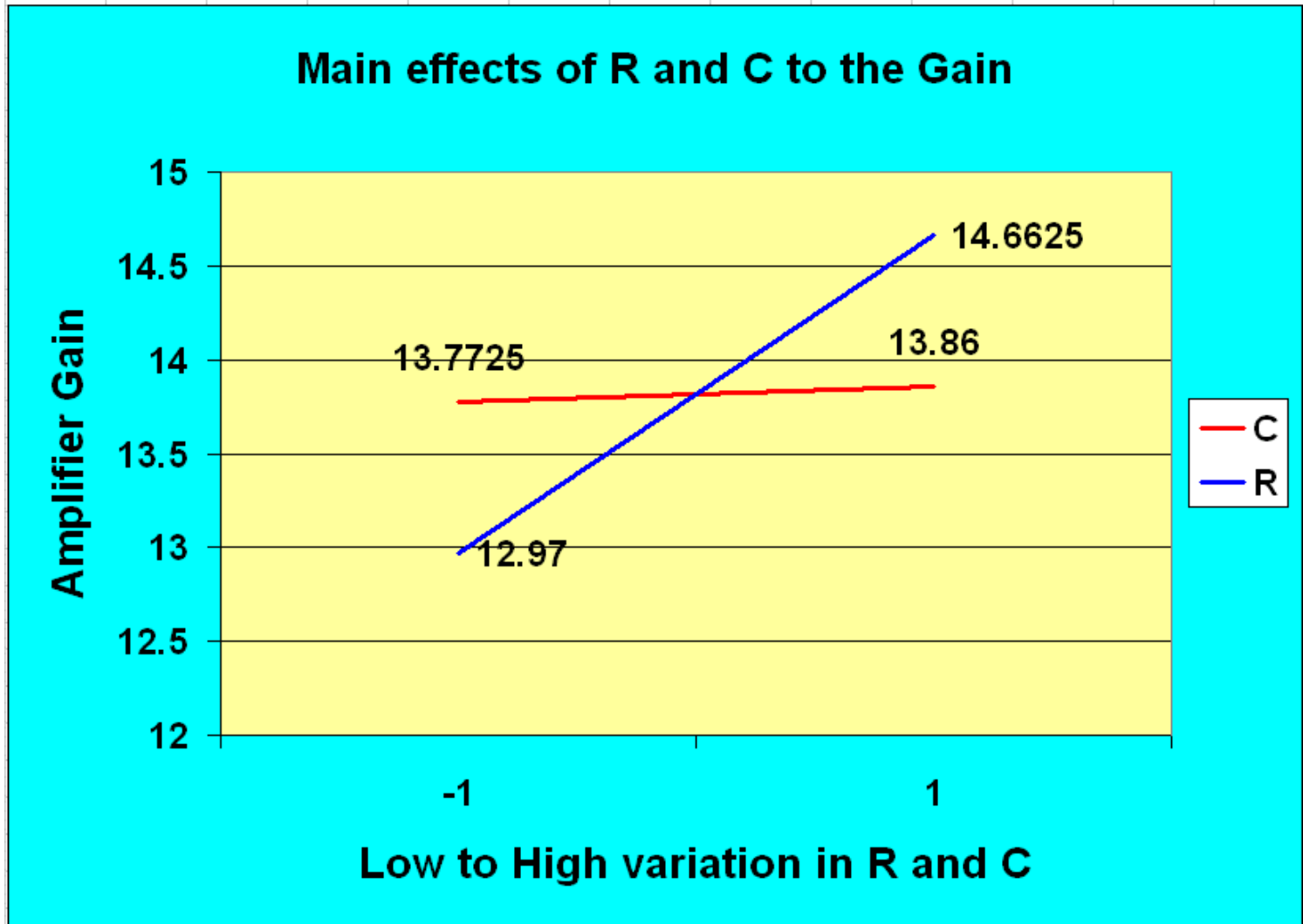

# Interaction Effect of (W and R) on Gain

| W  | R  | C  | Gain  |
|----|----|----|-------|
| -1 | -1 | -1 | 12.85 |
| 1  | -1 | -1 | 13.01 |
| -1 | 1  | -1 | 14.52 |
| 1  | 1  | -1 | 14.71 |
| -1 | -1 | 1  | 12.93 |
| 1  | -1 | 1  | 13.09 |
| -1 | 1  | 1  | 14.61 |
| 1  | 1  | 1  | 14.81 |

Average gain for  $W \cdot R = -1$

13.8075 dB (blue)


Average gain for  $W \cdot R = 1$

13.825 dB (pink)

Slope = .0088


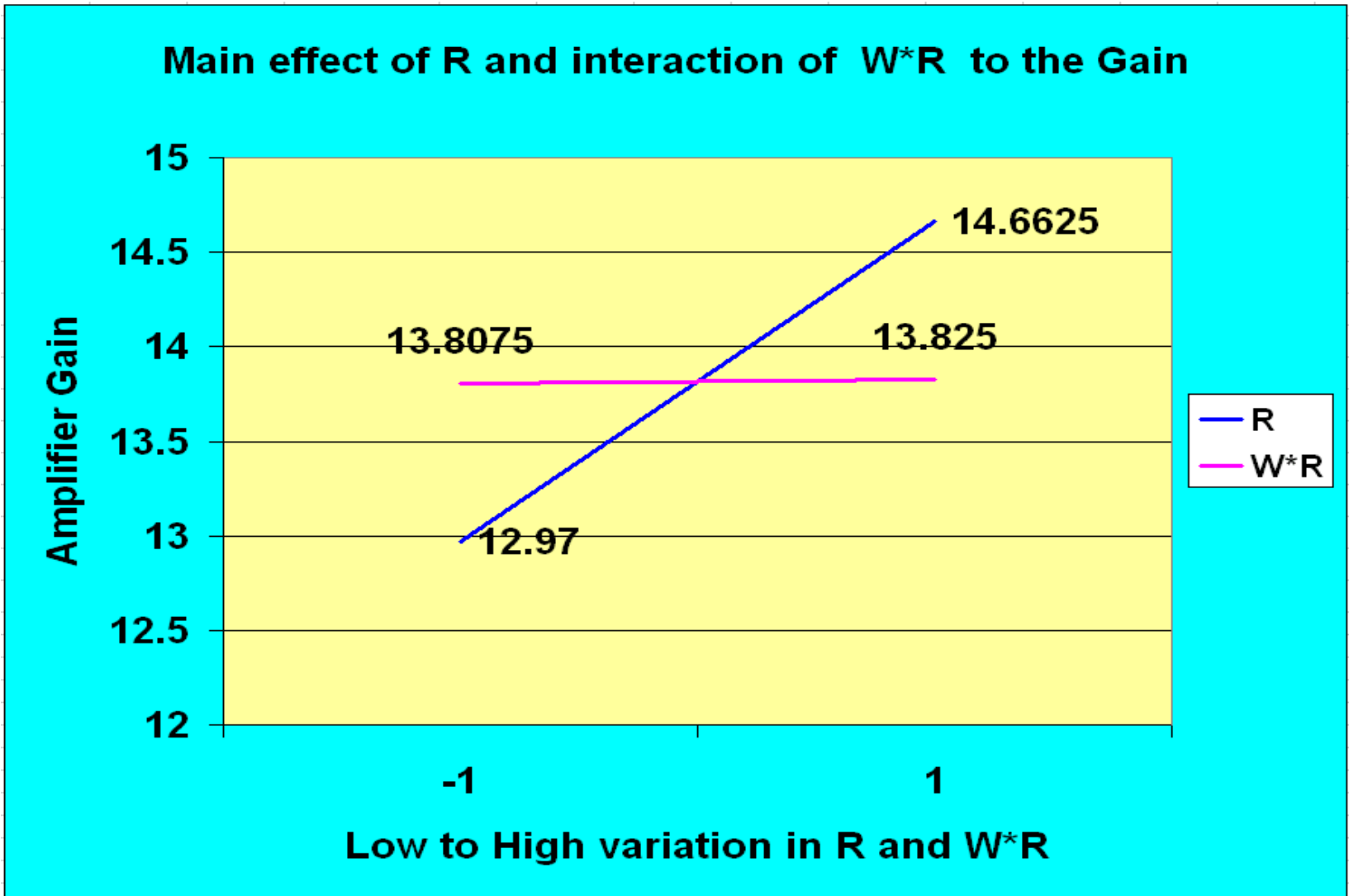
# Plotting Interaction Effects of W and R



# Obtaining the Rest of the Coefficients

| <u>Term</u>             | <u>Coefficient</u> |
|-------------------------|--------------------|
| Constant (nominal gain) | 13.8               |
| W                       | .09                |
| R                       | .85                |
| C                       | .044               |
| W*R                     | .0088              |
| W*C                     | .0013              |
| R*C                     | .0050              |
| W*R*C                   | 0.0025             |


We calculated these three coefficients in the previous slides

Construct a linear equation to represent the experiment results.

$$\text{Gain} = 13.8 + .09W + .85R + .044C + .0088WR + \dots \text{etc.}$$



# Display All Effects on a Pareto Chart

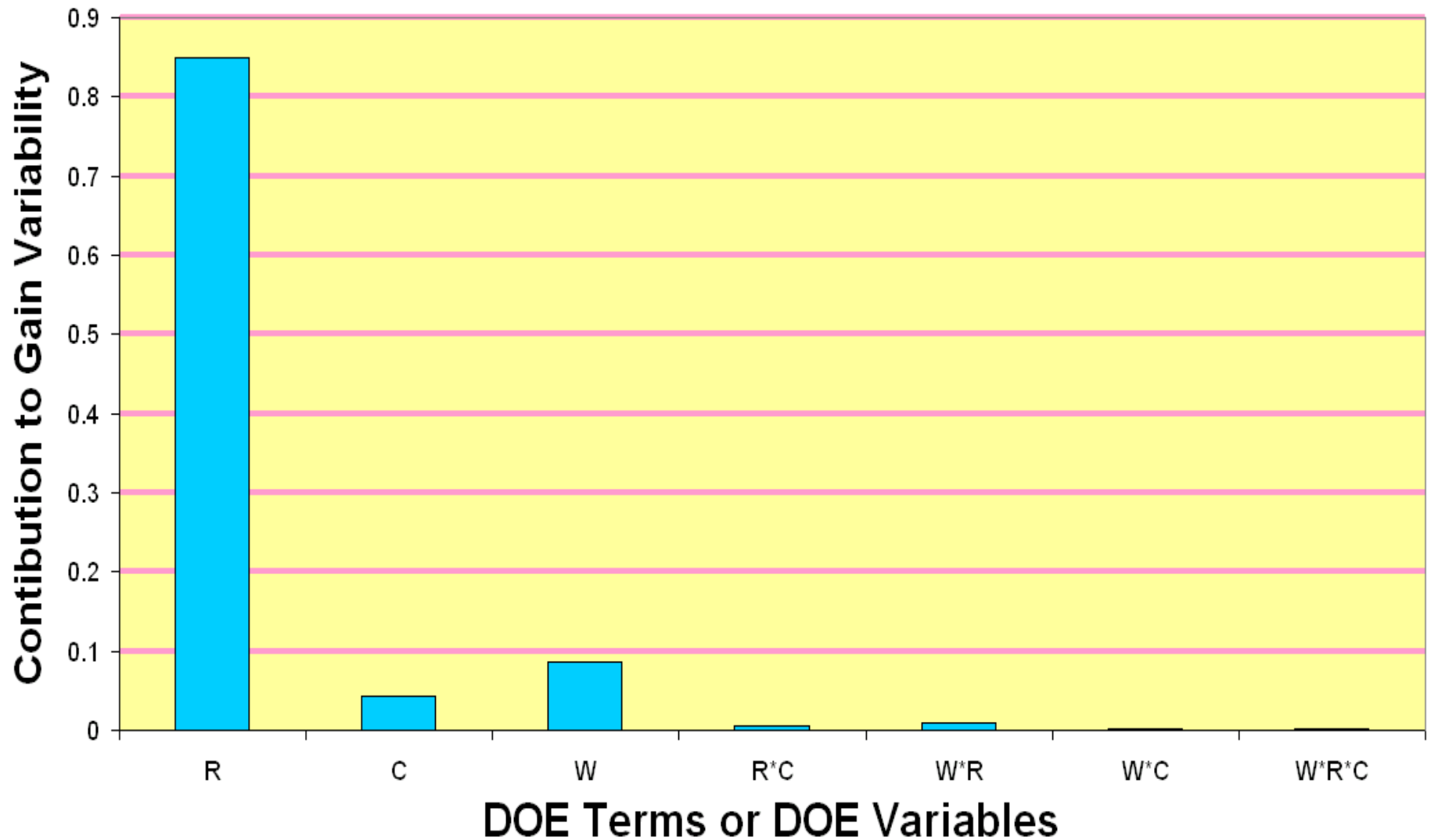



## Yield Sensitivity Histograms Used in Trade-off Study




# Start with This Scenario

- **System people are badly in need of an X-band LNA immediately**
- **An old design is available, but it might not meet the required specs**
- **Run yield analysis on the existing design**
- **Use the yield sensitivity histograms to make wise decisions about how to use this design.**


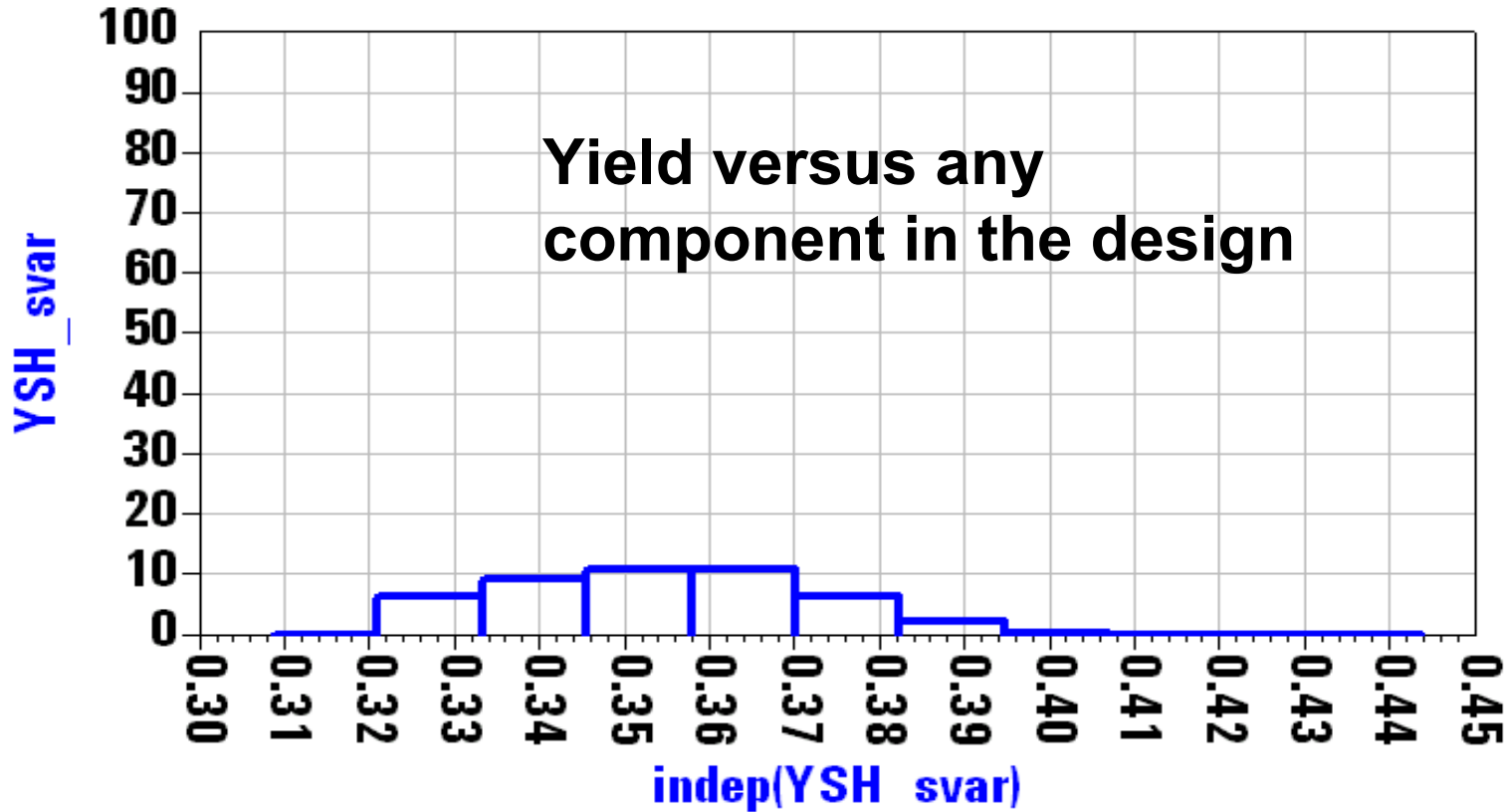
# Existing Amp Has Low Yield to the Specs



**Eqn** NF\_Spec\_Min=0

**Eqn** NF\_Spec\_Max = 2.8

**Eqn** Gain\_Spec\_Min = 14.0

**Eqn** Gain\_Spec\_Max=100


**Eqn** S22\_Spec\_Min=-100

**Eqn** S22\_Spec\_Max=-14

Initial  
specs


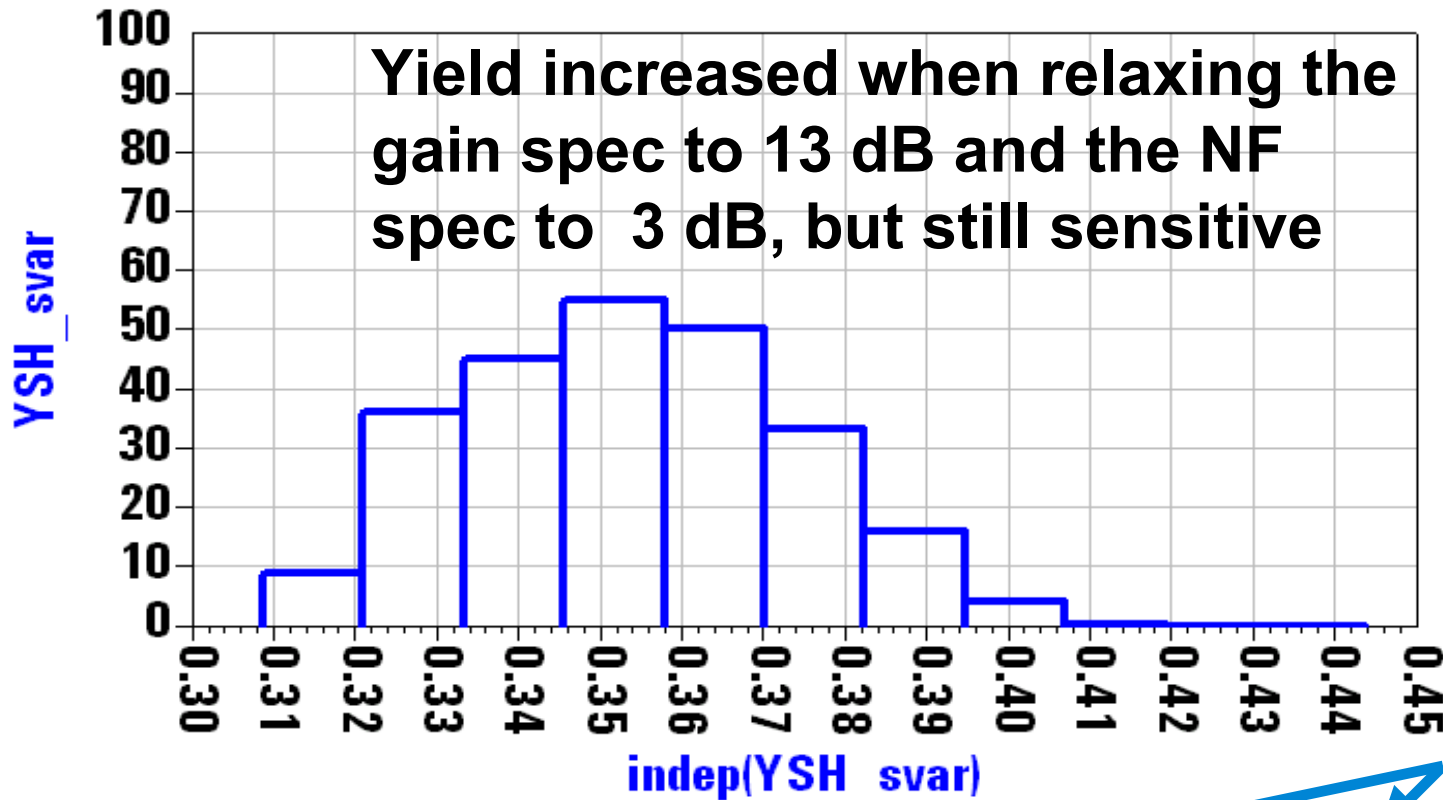
# Relax the NF Spec to 3 dB and Gain to 13 dB



**Eqn** NF\_Spec\_Min=0

**Eqn** Gain\_Spec\_Min = 13.0

**Eqn** S22\_Spec\_Min=-100

**Eqn** NF\_Spec\_Max = 3.0


**Eqn** Gain\_Spec\_Max=100

**Eqn** S22\_Spec\_Max=-14

Change specs slightly and watch the corresponding yield immediately



# Drop S22 Spec and Use Amp as Balanced

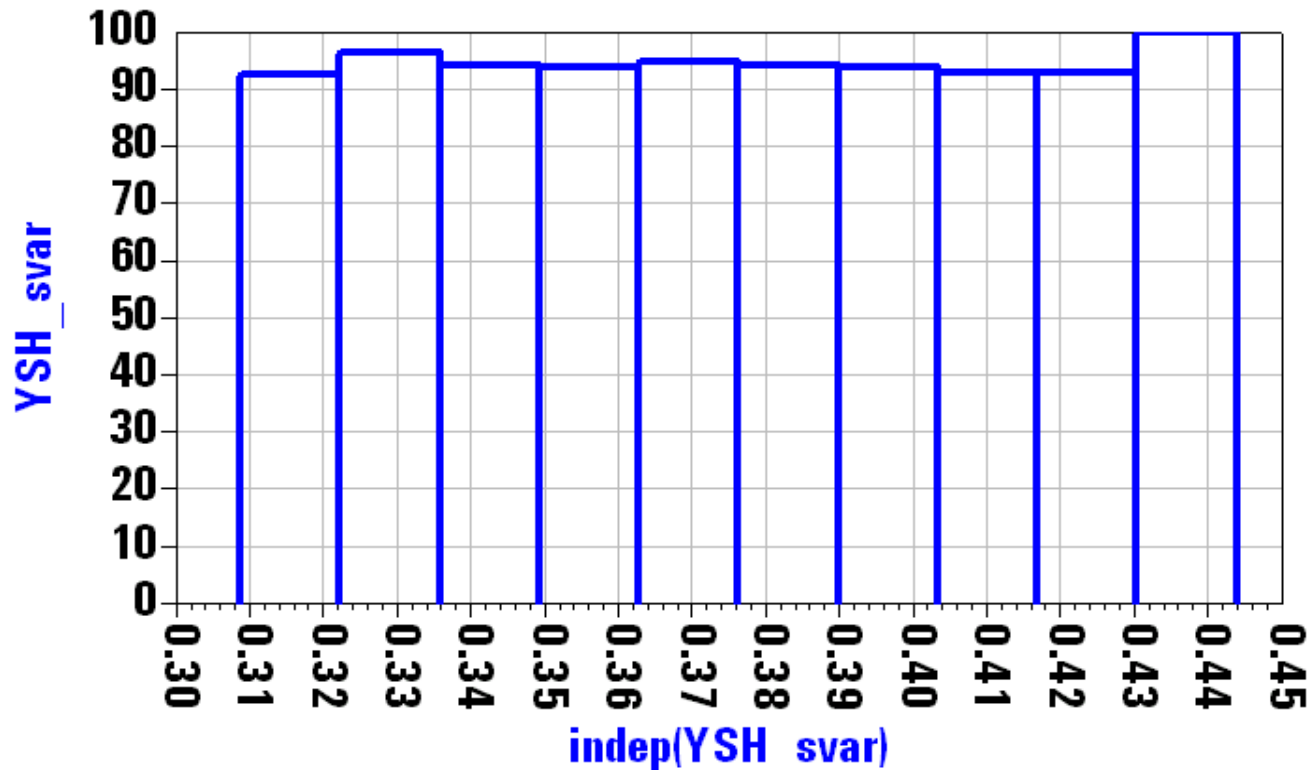

**Eqn** NF\_Spec\_Min=0

**Eqn** NF\_Spec\_Max = 3.0

**Eqn** Gain\_Spec\_Min = 13.0

**Eqn** Gain\_Spec\_Max=100

If we drop the S22 spec, yield goes up to >90.

This means that we can successfully use the LNA if we use it in a balanced configuration with Lange couplers.

