



### Lab #4 Pre-Lab Assignment


By: Larry Dunleavy  
Wireless and Microwave Instruments  
University of South Florida

#### Pre-Lab Assignment


The input reflection coefficient for a 50 ohm low loss (assume lossless) transmission line terminated in a short circuit been measured at 3GHz to be  $\Gamma_{in} = 1 \angle 140^\circ$ .

A. Fill in the blanks below to derive three different, but equivalent representations for the shorted transmission line.


**i) Electrical length.**

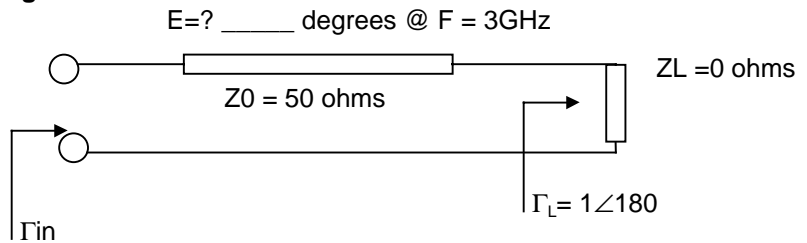

**ii) Physical length, air-line**

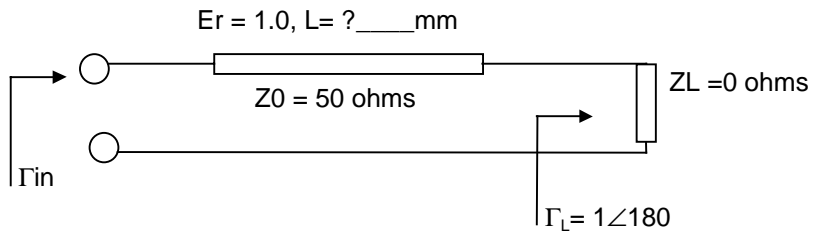

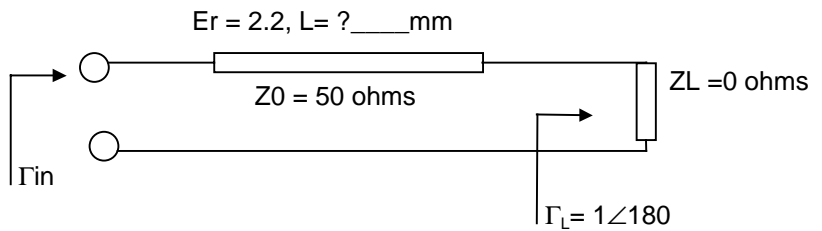**iii) Physical length, teflon dielectric.**





- B. Assuming a fixed physical length, use MATHCAD to plot  $\Gamma_{in}$  vs. frequency on a polar chart or Smith Chart over the frequency range from 300kHz to 3000MHz for the 1-port network below. Also plot the phase of  $\Gamma_{in}$  on a rectangular plot over the same frequency range. [Hint: See Mathcad example from lecture and/or web page for guidance on setup of plot].

