



## Experiment 10 — Superposition

### EL 111 - DC Fundamentals

**By:** Walter Banzhaf, E.K. Smith, and Winfield Young  
University of Hartford  
Ward College of Technology

#### Objectives:

1. For the student to calculate circuit voltages and currents, when more than one voltage source is present, by the process of superposition and verify calculations by measurements.

#### Equipment and parts:

Meters: Digital Multimeter (DMM);  
Milliammeter or Handheld MM such as the Agilent 971A

Power Supply: Agilent E3631A Triple Output DC Power Supply (0-20  $V_{DC}$ , +5 $V_{DC}$ )

Resistors: 1 - 3 k $\Omega$ , 1 - 1.2 k $\Omega$ , 1 - 1.6 k $\Omega$

Misc: Component Board

#### Information:


Superposition is a process for calculating currents and/or voltages for a component in a circuit which has more than one source.

The superposition techniques involve the following steps:

- Step 1 Remove all sources except one. You elect which one remains since eventually each existing source will be the stand-alone source before the analysis is complete. Replace the removed sources with their internal resistances. (Note: for this lab you will use voltage sources with a resistance of zero and will be instructed to replace the source with a *short*). Calculate the current(s) and/or voltage(s) with the one remaining source in the circuit for the resistor(s) in which you have an interest. Record the amount and direction of current and/or the magnitude and polarity of voltage across each resistor of interest.
- Step 2 Remove the source used in Step 1 and replace another source previously removed. Calculate the current(s) and/or voltage(s) of interest, recording directions, polarities and magnitudes of the current and voltage of interest.
- Step 3 Repeat Step 2 until all sources in the original circuit have been used.
- Step 4 The actual current and/or voltage for any one resistor will be the algebraic sum of the currents and/or voltages found above for that particular resistor.

#### Procedure:

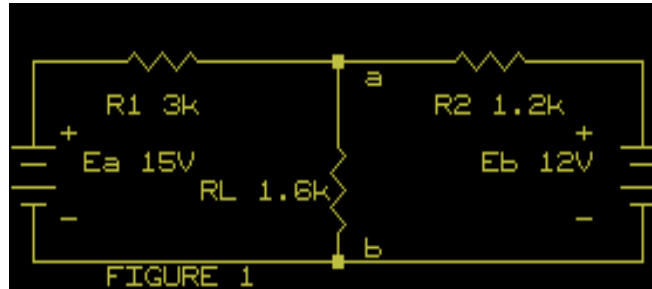1. Refer to Figure 1. **Use the following steps to calculate the current through and the voltage across  $R_L$  (the resistor of interest) by superposition techniques.**




**Step 1**  $E_a$  is present,  $E_b$  is removed. Refer to figure 2. Remove  $E_b$ , and replace it with a short. (This assume that the voltage source has no internal resistance.) Solve for the magnitude and direction of the current through  $R_L$  in figure 2. Calculate the voltage drop across  $R_L$ . Determine the polarity of the voltage drop. Record the current, its direction, the voltage drop and the polarity on figure 2. Show your calculations in space provided.

Calculations ( $E_b$  removed):

$I_{RL}$  \_\_\_\_\_


$E_{RL}$  \_\_\_\_\_

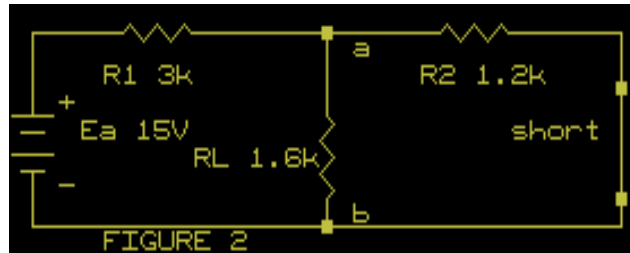

**Step 2** Refer to figure 3. Remove the short and replace  $E_b$ . Refer to figure 3. Remove  $E_a$  and replace it with a short. Solve for the magnitude and direction of the current through  $R_L$  in figure 3. Calculate the voltage drop across  $R_L$ . Determine the polarity of the voltage drop. Record the current, its direction, the voltage drop and the polarity on figure 3. Show your calculations in space provided.

Calculations ( $E_a$  removed):

$I_{RL}$  \_\_\_\_\_

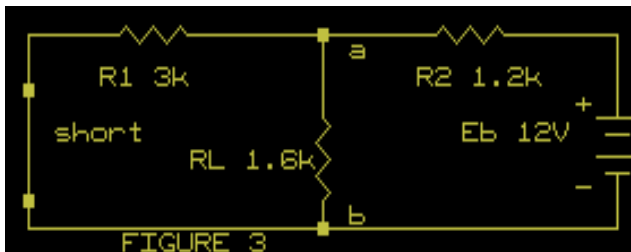

$E_{RL}$  \_\_\_\_\_



Step 3 The actual current through and voltage across  $R_L$  WILL BE the ALGEBRAIC SUM of the results obtained in steps 1 and 2. Do these summations below and record the resultant current and its direction and the voltage drop and its polarity on Figure 1 on page two.

Algebraic addition:  $E_{RL} = \underline{\hspace{2cm}} + \underline{\hspace{2cm}} = \underline{\hspace{2cm}}$

$$I_{RL} = \underline{\hspace{2cm}} + \underline{\hspace{2cm}} = \underline{\hspace{2cm}}$$

**2. Verify the results of the superposition calculations by circuit measurement.**

- a) Connect the circuit of Figure 1. NOTE: Make sure that the DMM common is at point b.
- b) Measure the following:

$E_{RL} = \underline{\hspace{2cm}}$ , and point  $\underline{\hspace{1cm}}$  is positive in respect to point  $\underline{\hspace{1cm}}$ .

$I_{RL} = \underline{\hspace{2cm}}$ , current flows from point  $\underline{\hspace{1cm}}$  to point  $\underline{\hspace{1cm}}$ .

- c) If the calculated results are not reasonable close to the measured results, check your calculations and measurements to find the error.

3. On a separate sheet of paper, repeat Procedures 1 and 2 except **reverse the polarity of  $E_a$** . Show all three circuit diagrams and all calculations as contained in Procedures 1 and 2 of this experiment.