

# BENCH BRIEFS

SERVICE INFORMATION FROM HEWLETT-PACKARD

JANUARY-FEBRUARY 1975

## ALL ABOUT POWER SUPPLIES

by Dick Gasperini, Editor

Virtually every piece of electronic gear has a power supply so the probability of having to repair a failure is rather high. Therefore, knowledge of power supply operation is essential for repair personnel.

A power supply that may look familiar is in Figure 1. It will convert the AC line voltage to a DC voltage, say 175 volts, for our load, lumped here as a single resistor  $R_L$ .

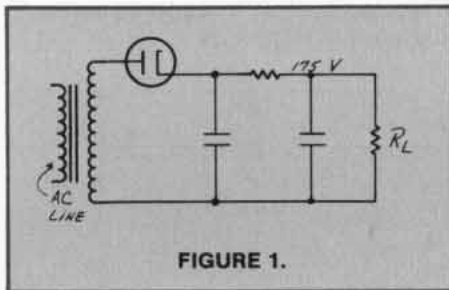


FIGURE 1.

This type of power supply has several shortcomings. Since this supply can be looked upon as an ideal battery with a resistor in series, it becomes clear that the output voltage will change if the load changes. See Figure 2.

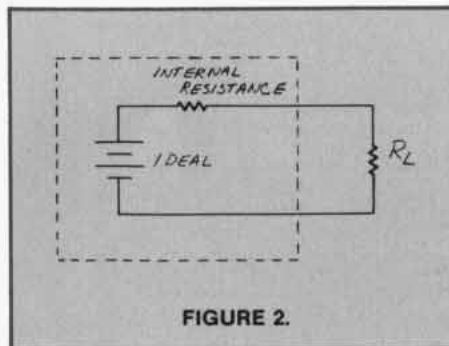


FIGURE 2.

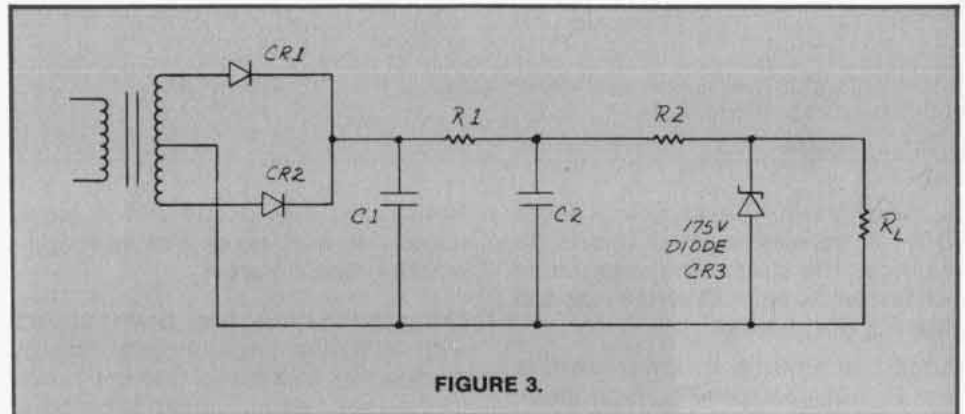


FIGURE 3.

This change of output voltage with a change in load ("load regulation") would not be a problem if we always had a fixed load that demanded a constant amount of current. Most times, though, a load is not constant. Therefore, the power supply voltage will change and this may be undesirable.

Also, what happens if the line voltage varies by 20%? In this supply the output voltage will again vary. This supply lacks "line regulation".

To obtain a more stable voltage we will want an improved supply.

One improvement is to change to solid state and to a full wave circuit. This gives a lower internal impedance and therefore better load regulation. (This also has other benefits, like reduced ripple.) A bigger improvement, though, will result from using a breakdown diode. See Figure 3.

The breakdown diode will start drawing current when its breakdown voltage is reached. Thus, as the output voltage starts to rise above 175V, the breakdown diode will conduct heavily, causing more voltage to be dropped across  $R_2$ . If the output voltage were to start to drop below 175V, the diode would conduct less, dropping less voltage across  $R_2$ . Thus, the diode

helps to stabilize the output voltage.

This technique does have its limitations. Assume that  $CR_3$  is rated at 20 mA. We would select the value of  $R_2$  so that 10 mA of current flowed thru  $CR_3$ . If the load were reduced by 10 mA, the voltage would tend to rise and  $CR_3$  would conduct more current, keeping the voltage at 175V. Similarly, if the load were to draw more current, less current would be drawn by  $CR_3$ , again stabilizing the voltage. But we are very limited in the load variation that can be compensated with a breakdown diode.

The output voltage is also changing somewhat during this process.

### IN THIS ISSUE

- POWER SUPPLY THEORY
- ISOLATING POWER SUPPLY DRIFT
- NEW SERVICE NOTES
- MORE ON TRANSISTOR CHECKER

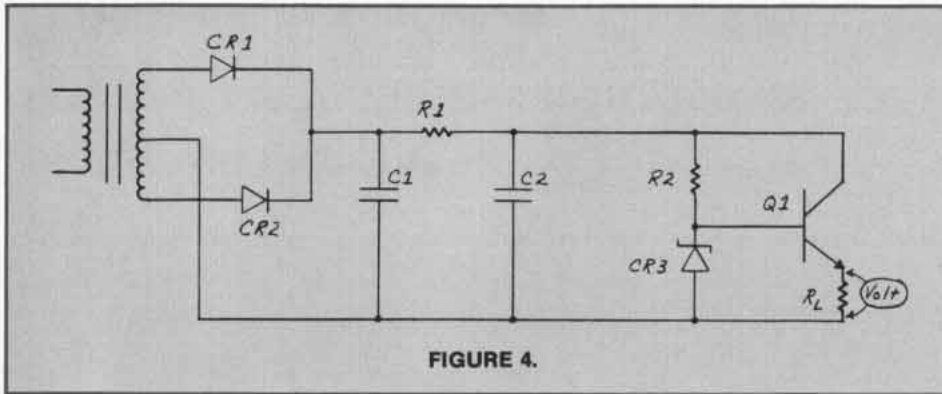


FIGURE 4.

A breakdown diode has about  $10\Omega$  of resistance, and this is, in essence, the output impedance of our power supply. This may be too high for our needs.

Putting an emitter follower on this circuit will reduce the impedance by about the gain ( $\beta$ ) of the transistor. See Figure 4.

This circuit operation can be understood easily by recognizing that the base of Q1 will have a fairly constant voltage on it (developed across CR3). If the output voltage (emitter of Q1) drops more than one diode drop (0.6V for silicon, 0.2V for germanium) below the base, Q1 will tend to turn on harder, raising the output voltage. If the output voltage were to rise, Q1 will be biased off. Thus, the output voltage is fixed at the breakdown voltage of CR1 minus one diode drop (B-E drop of Q1).

If this power transistor has a gain of 10, the output impedance is now about 1 ohm (that is, 1 mA change in load current will cause a 1 mV change in output voltage). This is still too high for many circuits, so we can add another emitter follower. See Figure 5.

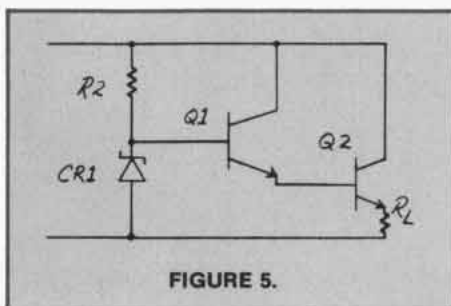


FIGURE 5.

Redrawing this circuit in the more usual way may make it more recognizable. See Figure 6.

Current limiting has been added with a series resistor and several diodes. As increased current flows in the load, additional voltage drop is realized across R3. When the drop across R3 starts to exceed one diode drop, CR4, CR5 and CR6 will start to conduct, robbing base-emitter current away from Q1, causing it to conduct less. This limits the current flow, and the output voltage will drop somewhat.

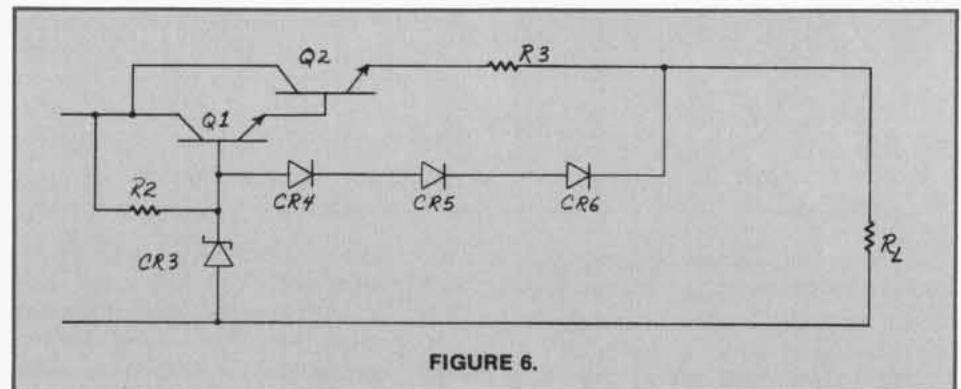


FIGURE 6.

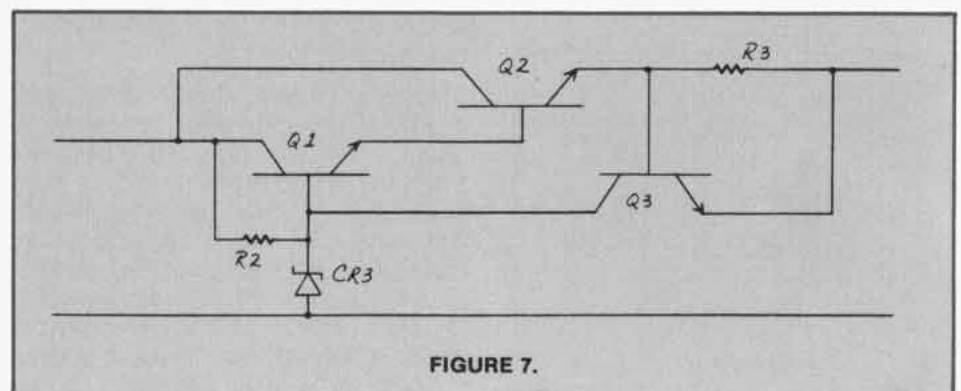


FIGURE 7.

The resistance of R3 will determine the current limiting point.

It is interesting to note, however, that the circuit has stabilized at maximum current and nearly normal output voltage. Therefore, the power dissipated in the power supply circuit and the load is very high.

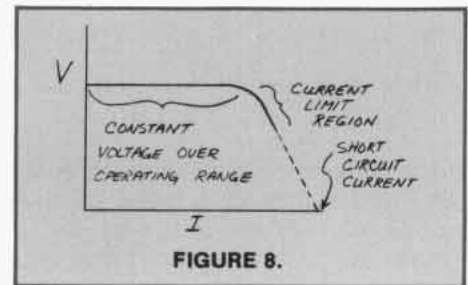


FIGURE 8.

Sharper turnoff can be achieved by adding a transistor to the current limit circuit. See Figure 7. We still will have a high level of power dissipation since enough current must be flowing in R3 to keep Q3 conducting.

A typical plot of voltage vs current is shown in Figure 8.

### FOLDBACK

Since current limiting comes into play when there is a failure (or other abnormality), it may be advantageous to be able to shut off the power supply circuit, rather than continue to dissipate all that power. This technique is called foldback and is shown graphically in Figure 9. In the +180V supply in Figure 10, once the Q2 circuitry is turned on, it will continue to conduct, holding Q1 off.

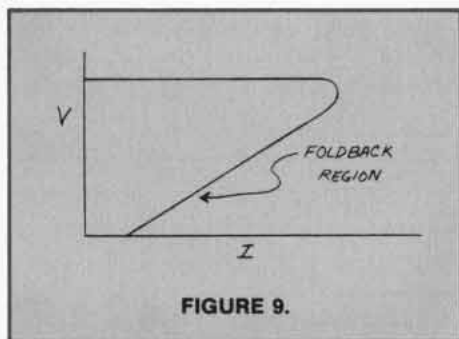


FIGURE 9.

Notice that the +5V regulator circuitry is integrated into a TO3 package. While this package looks like an ordinary power transistor, it contains the series pass transistor(s), breakdown reference diode and associated circuitry needed for proper regulation. These fixed voltage regulators can be purchased for the more commonly used power supply voltages such as 5V and 12V. Some are available with current limit capability.

### RIPPLE

Modern electronic circuits require very clean (ripple-free) power supplies. Looking back at Figure 4, we see that the output voltage is very dependent on the voltage dropped across CR3. But this will vary slightly with the current through it (recall that a breakdown diode has a nominal internal resistance of about  $10\Omega$ ). Therefore if the line voltage increases, the voltage on C2 will increase, resulting in increased current through CR3 and an increase in the output voltage. Also the voltage on C2 varies during each rectification cycle. The peak of the rectified sine wave (ripple) will be passed through Q1 to some extent. Since even this small variation in the output voltage may be undesirable, you may see power supply circuits with a constant current source for CR3. See Figure 11.

In essence, a constant voltage is

dropped across diodes CR7 and CR8. This limits the B-E current of Q4, resulting in a constant current through CR3.

In actuality, the voltage across CR7 and CR8 will vary slightly and the next evolution would be a constant current source for them. This can be done easily with two transistors. See Figure 12. Transistor Q4 receives a constant bias from the drop across Q5. This gives a constant current through R5, which keeps a constant bias on Q5 and a constant current through CR3.

### PROTECTION

Current limiting may not be enough protection for the load. What happens if there is a failure in the power supply circuit, such as a shorted Q2? The output would rise to the full unregulated voltage.

If this were the +5 volt supply for all the IC's in an instrument, most of the IC's would very likely be destroyed. Therefore, it may be

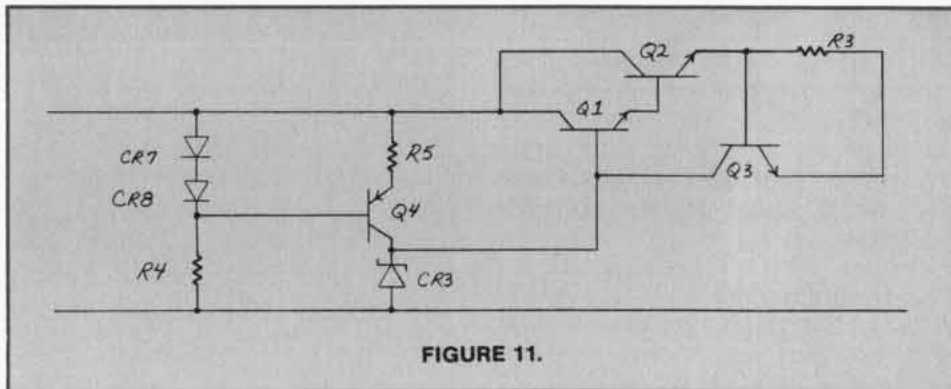


FIGURE 11.

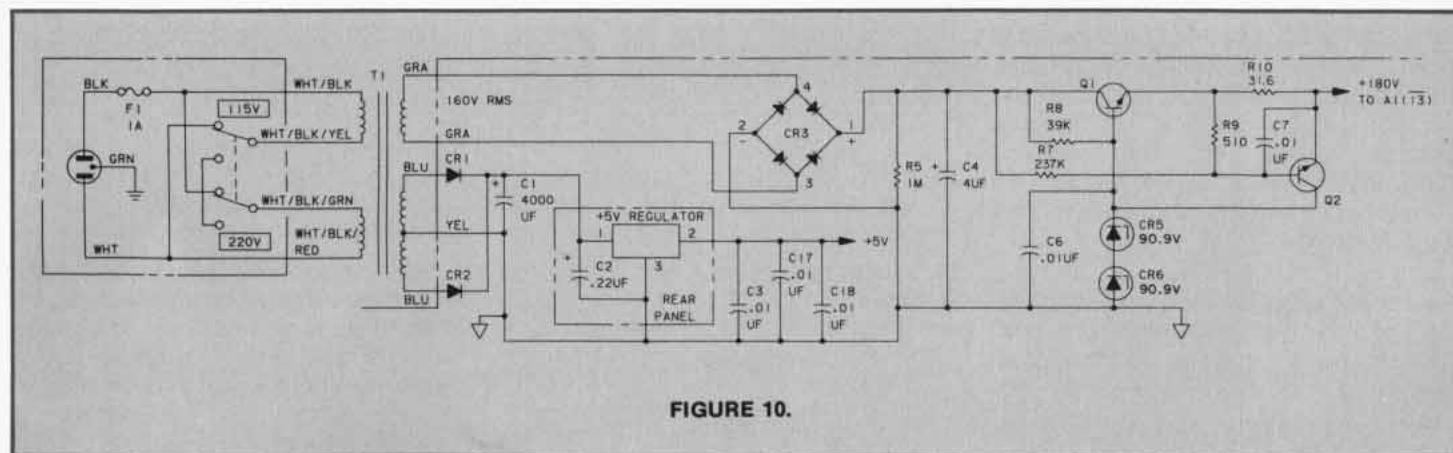


FIGURE 10.

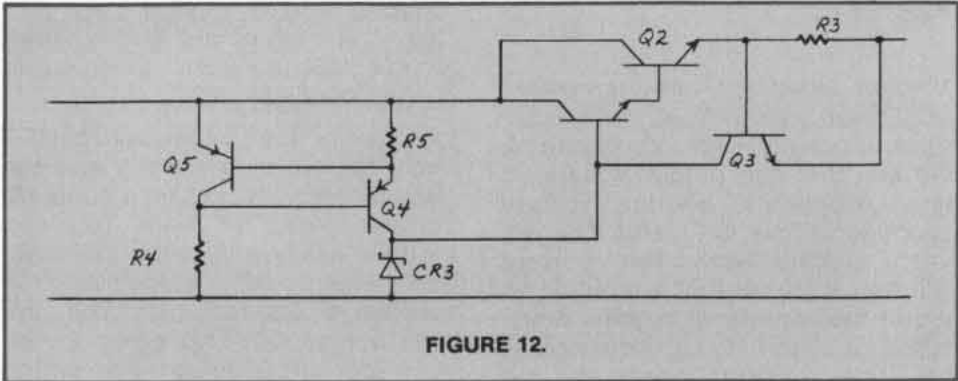


FIGURE 12.

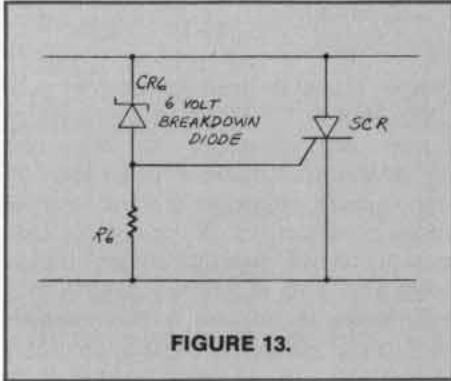


FIGURE 13.

advisable to build in additional protection in the form of a "crowbar circuit". This is generally an SCR that monitors the output volt-

age and shorts it to ground if the voltage rises too high. See Fig. 13. If the supply voltage rises above 6 volts, CR9 would start to conduct,

developing a voltage across R6. This would cause the SCR to fire, shorting out the power supply line (and hopefully blowing a fuse).

**ISOLATING POWER SUPPLY DRIFT**


by John Whidden

What is the most effective way to isolate a drift problem in a power supply?

To answer that question, let's look at how a power supply normally operates.

The programming input to a power supply consists of a resistive divider (R<sub>R</sub> and R<sub>p</sub>) connected between reference zener and -S terminal. (Refer to figure.) The common point of R<sub>R</sub> and R<sub>p</sub> is the input to the amplifier and is called the summing point. When the power supply is operating properly, the output voltage equals the sum of voltage across R<sub>p</sub> plus the offset voltage. Therefore, variation in either of these will cause a change in the output voltage.

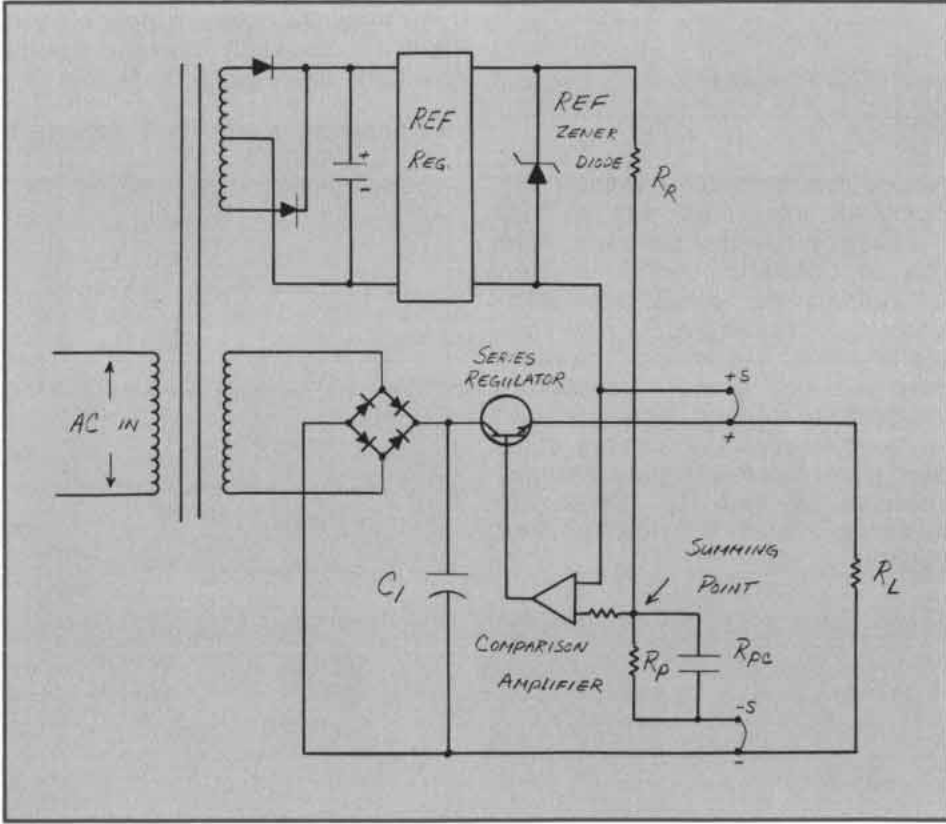
The most effective way to isolate a drift problem is measure and record the reference supply voltage, the summing point voltage and the output voltage at any convenient interval (such as every half hour).



- Measure and record the following voltages:
1. +S to -S (output)
  2. +S to summing point (offset)
  3. +S to reference zener (reference)

The important thing is not how often the measurements are made but that they are made in the same manner and with the same equipment. Usually only 3 or 4 sets of measurements are necessary to evaluate the power supply.

The following algorithm may be useful to narrow the trouble:

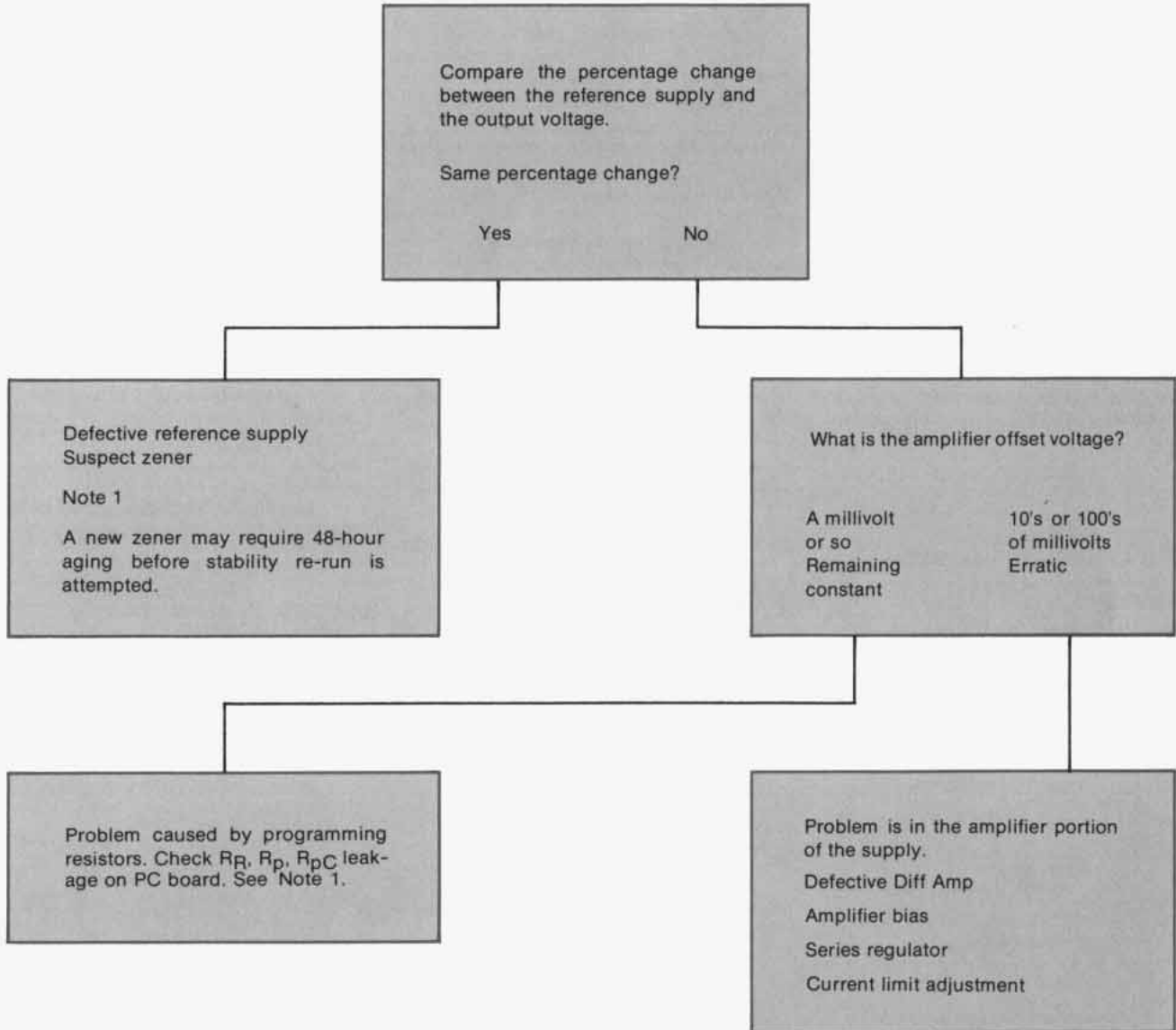

**Note 1.** Circuit coolant sprayed on individual 20PPM resistors will generally cause 0.25 and 0.5% change in the output. A defective resistor might cause a 1% to even 25% change.

*John Whidden joined HP in 1961 and became involved with power supply service and applications for field service and customer training. John now provides factory back up for field service and prepares service information for instruction manuals and service notes.*

supplement to

# BENCH BRIEFS SERVICE NOTE INDEX

## NEED ANY SERVICE NOTES?

Here's the latest listing of Service Notes available for Hewlett-Packard products. To obtain information for instruments you own, remove the order form and mail it to the HP distribution center nearest you.

### 211B SQUARE WAVE GENERATOR

211B-3. All serials. Improved reliability of 600 ohm output.

### 425A/AR DC MICROVOLT-AMMETER

425A-7. Elimination of potential shock hazard.

### 1208A DISPLAY

H11-1208A-9. All serials. Preferred replacement for A6Q3.

### 1220A DUAL CHANNEL OSCILLOSCOPE, 15 MHz

1220A-13. All serials. Troubleshooting tips. 1220A-14. Serial numbers 1416A02656 to 1416A02760. Sweep problems in the 1  $\mu$ sec to 50 sec range.

1220A-15. All serials. Insulator caps.

1220A-16. All serials. Service kit.

1220A-17. Serial numbers below 1416A03150. H.V. board modification.

1220A-18. All serials. Antistatic solution.

### 1221A SINGLE CHANNEL OSCILLOSCOPE, 15 MHz

1221A-5. All serials. Troubleshooting tips.

1221A-6. All serials. Service kit.

1221A-7. All serials. Antistatic solution.

### 1308A EIGHT CHANNEL MONITOR

1308A-9. All serials. Preferred replacements for A4Q3, A4Q4, A4Q9, and A4Q10.

### 1309A X-Y MONITOR

1309A-9. All serials. Preferred replacements for A4Q3, A4Q4, A4Q9, and A4Q10.

### 1331A/C X-Y DISPLAY, STORAGE

1331A/C-12. 1331A serial prefix 1424A through 1448A; 1331C serial prefix 1426A and below. Intermittent erasing. Supersedes 1331C-3.

1331A/C-13. 1331A serial prefix 1424A and below; 1331C serial prefix 1426A and below. Modification to add pattern correction adjustment.

1331A/C-14. All serials. Intermittent blowing of +50V fuse.

### 1810A 1 GHz DUAL CHANNEL SAMPLER

1810A-2. Serial prefix 1308A and below. Reduced minimum delay drift.

1810A-3. Serial prefix 1308A and below. Reduced trigger circuit lock-up.

### 1811A 18 GHz SAMPLER

1811A-2. Serial prefix 1309A and below. Reduced trigger circuit lock-up.

### 1915A VARIABLE TRANSITION TIME OUTPUT

1915A-12A. Serial prefix 1143 and above. Three preferred replacements. Supersedes 1915A-12.

### 3330A/B AUTOMATIC SYNTHESIZER

3330A/B-5. All serials. Replacement part numbers for LED displays.

### 3403A/C TRUE RMS VOLTMETER

3403C-3. Part numbers 5060-9131/32/33. Replacement part numbers for LED displays.

### 3469A/B MULTIMETER

3469B-3. Part numbers 5060-9131/32/33. Replacement part numbers for LED displays.

### 3480C/D DIGITAL VOLTMETER

3480C/D-1. All serials. Replacement part numbers for LED displays.

### 3490A MULTIMETER

3490A-9. All serials. Replacement part numbers for LED displays.

### 3570A NETWORK ANALYZER

3570A-5. All serials. Replacement part numbers for LED displays.

### 3575A GAIN PHASE-METER

3575A-2. Part numbers 5060-9131/32/33. Replacement part numbers for LED displays.

### 3690A INSTRUMENTATION TAPE RECORDERS

3690A-24. Serial prefix 1422A only. Option 050 (remote control) wiring error.

### 5055A DIGITAL RECORDER

5055A-2. Serial number 1316A02635 and below. Transistor change to prevent failures in A2 driver board assembly.

### 5477A SYSTEM CONTROL

5451B-7/5477A-1. All serials. Field preventive maintenance procedure.

### 5500A/B LASER HEAD

5525A/B-3. All serials. Laser tube safety.

### 6940/6941A MULTIPROGRAMMER

6940A-1. Serial number 1321A00476 and below. Added protection on the -12V line.

6941A-1. Serial number 1242A00290 and below. Added protection on the -12V line.

### 7130A/B and 7131A/B STRIP CHART RECORDERS

7130A/B-2, 7131A/B-2. All serials. Disposable pen conversions.

### 7155A PORTABLE STRIP CHART RECORDERS

7155A-1. Serial prefix 1432 and below. Battery charging circuit modification to prevent possible oscillation.

7155A-2. All serials. Modification to Option 005 right hand zero.

### 7200/7202/7203A GRAPHIC PLOTTERS

7200A-12/7202A-11/7203A-11. All serials. EIA RS232C interfacing instructions and information.

7200A-13/7202A-12. All serials. Correct character register (A3), servo preamplifier (A7), and pen control assembly (A8) board combinations for proper plotter operation.

7203A-10. Serial prefixes before 1433A. Component change on interface board.

### 7210A DIGITAL PLOTTER

7210A-12. All serials. Interface/conversion kit for operating 7210A plotters with HP 2100 series computers.

### 7260A OPTICAL MARK READERS

7260A-9. Serial prefixes before 1436A. New A4 serial interface board.

7260A/7261A-10. Serial prefixes before 1444A. -19V regulator change.

### 8012/8013A PULSE GENERATORS

8012A-4. All serials. Recommended replacements.

8013A-4. All serials. Recommended replacements.

### 8445A AUTOMATIC PRESELECTOR

8445A-1. All serials. Replacement YIG filter assembly.

### 8551A/B SPECTRUM ANALYZER RF SECTION

8551A/B-9. All serials. RF input attenuator replacements.

### 8552B SPECTRUM ANALYZER, IF SECTION

8552B-9. Serial number 1437A07061 to 1437A07210. Prevention of power supply failures due to shorted series regulators Q23 and Q24.

### 8555A SPECTRUM ANALYZER

8555A-3. Serial number 1434A04235 and below. Improved 500 MHz local oscillator.

### 8605A COMMUNICATION SWEEP OSCILLATOR

8605A-4. Serial prefix 1403A and below. Replacement of A2 and A3 YIG oscillator driver assemblies.

### 8620A/B SWEEP OSCILLATOR

8620A-6. Serial prefix 1332A and below. Modification required for 86290A. 2.0-18.0 GHz plug-in compatibility.

8620B-3. All serials. Modification required for 86290A. 2.0-18.0 GHz plug-in compatibility.

### 8640A/B AM-FM SIGNAL GENERATOR

8640A-11A/8640B-12A. All serials. RF on/off switch modification.

### 8660A/B SYNTHESIZED SIGNAL GENERATOR

8660A-24. Serial numbers below 1145A00691. Digital I.C. replacement.

8660A-25. All serials. Mainframe calibration quick check.

8660B-23. Serial number 1439A00960 and below. 1820-0450 I.C. replacement.

8660B-25. All serials. ROM input assembly compatibility.

8660B-26. All serials. Mainframe calibration quick check.

### 9869A CALCULATOR CARD READERS

9869A-5. Serial prefixes below 1434A. New calculator I/O and mother boards.

9869A-6. Serial prefixes below 1444A. -19V regulator change.

### 10230A/B PROBES

10230A/B-1. Replacement wire kit 10231-68702. Supersedes 1601A-2.

10231A/B-1. Replacement wire kit 10231-68702. Supersedes 1601A-2.

### 10579A STRAIGHTNESS ADAPTER

10579A-1. Serial prefix 1328 only. Improved frequency multiplier board.

### 11661A FREQUENCY EXTENSION MODULE

11661A-5A. Serial prefix 1431A and below. Improved sum loop locking. Supersedes 11661A-5.

11661A-6. Serial prefix 1430A and below. YIG pretune improvement.

11661A-7. Serial prefix 1433A and below. Improved cooling.

### 29400 SERIES RACK CABINETS

29400-2. Instrument slide alignment.

### 34703A DCV/DCA/OHM METER

34703A-4. Serial numbers below 1251A01500. Improvement of reliability when measuring high voltage inputs.

34703A-5. Serial numbers below 1251A01500. Elimination of potential intermittent logic problems.

### 86601/86602A RF SECTION FOR 8660A/B

86601A-7. Serial number 1443A00781 and below. Attenuator driver assembly.

86602A-6. Serial number 1444A01011 and below. Attenuator driver assembly.

# ORDER FORM

Please print your name and address clearly.  
This will be used as a shipping label. ▶

Check here to receive a qualification form for  
a free subscription to Bench Briefs.

NAME \_\_\_\_\_

COMPANY NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_

STATE \_\_\_\_\_ ZIP \_\_\_\_\_

Please  check below the numbers of any desired service notes:

Cut off this page and return to:

Hewlett-Packard  
195 Page Mill Road  
Palo Alto, California 94306

- |                                     |                                    |
|-------------------------------------|------------------------------------|
| <input type="checkbox"/> 1331A/C-13 | <input type="checkbox"/> 8013A-4   |
| <input type="checkbox"/> 1331A/C-14 | <input type="checkbox"/> 8445A-1   |
| <input type="checkbox"/> 1810A-2    | <input type="checkbox"/> 8551A/B-9 |
| <input type="checkbox"/> 1810A-3    | <input type="checkbox"/> 8552B-9   |
| <input type="checkbox"/> 1811A-2    | <input type="checkbox"/> 8555A-3   |

For European customers (ONLY),  
please send it to:

Hewlett-Packard  
Central Mailing Dept.  
P.O. Box 7550  
Freeport Building  
SCHIPHOL - Centrum  
The Netherlands

- |                                    |  |
|------------------------------------|--|
| <input type="checkbox"/> 1915A-12A | <input type="checkbox"/> 8605A-4             |
| <input type="checkbox"/> 3330A/B-5 | <input type="checkbox"/> 8620A-6             |
| <input type="checkbox"/> 3403C-3   | <input type="checkbox"/> 8620B-3             |
| <input type="checkbox"/> 3469B-3   | <input type="checkbox"/> 8640A-11A/8640B-12A |
| <input type="checkbox"/> 3480C/D-1 | <input type="checkbox"/> 8660A-24            |
| <input type="checkbox"/> 3490A-9   | <input type="checkbox"/> 8660A-25            |
| <input type="checkbox"/> 3570A-5   | <input type="checkbox"/> 8660B-23            |
| <input type="checkbox"/> 3575A-2   | <input type="checkbox"/> 8660B-25            |
| <input type="checkbox"/> 3690A-24  | <input type="checkbox"/> 8660B-26            |
| <input type="checkbox"/> 5055A-2   | <input type="checkbox"/> 9869A-5             |

- |                                      |   |                                     |
|--------------------------------------|---|-------------------------------------|
| <input type="checkbox"/> 211B-3      | <input type="checkbox"/> 5451B-7/5477A-1      | <input type="checkbox"/> 9869A-6    |
| <input type="checkbox"/> 425A-7      | <input type="checkbox"/> 5525A/B-3            | <input type="checkbox"/> 10230A/B-1 |
| <input type="checkbox"/> H11-1208A-9 | <input type="checkbox"/> 6940A-1              | <input type="checkbox"/> 10231A/B-1 |
| <input type="checkbox"/> 1220A-13    | <input type="checkbox"/> 6941A-1              | <input type="checkbox"/> 10579A-1   |
| <input type="checkbox"/> 1220A-14    | <input type="checkbox"/> 7130A/B-2, 7131A/B-2 | <input type="checkbox"/> 11661A-5A  |

- |                                   |   |                                   |
|-----------------------------------|---|-----------------------------------|
| <input type="checkbox"/> 1220A-15 | <input type="checkbox"/> 7155A-1                        | <input type="checkbox"/> 11661A-6 |
| <input type="checkbox"/> 1220A-16 | <input type="checkbox"/> 7155A-2                        | <input type="checkbox"/> 11661A-7 |
| <input type="checkbox"/> 1220A-17 | <input type="checkbox"/> 7200A-12/7202A-11/<br>7203A-11 | <input type="checkbox"/> 29400-2  |
| <input type="checkbox"/> 1220A-18 | <input type="checkbox"/> 7200A-13/7202A-12              | <input type="checkbox"/> 34703A-4 |
| <input type="checkbox"/> 1221A-5  |   | <input type="checkbox"/> 34703A-5 |
|                                   |   | <input type="checkbox"/> 86601A-7 |
|                                   |   | <input type="checkbox"/> 86602A-6 |

- |                                     |   |
|-------------------------------------|---|
| <input type="checkbox"/> 1221A-6    | <input type="checkbox"/> 7203A-10       |
| <input type="checkbox"/> 1221A-7    | <input type="checkbox"/> 7210A-12       |
| <input type="checkbox"/> 1308A-9    | <input type="checkbox"/> 7260A-9        |
| <input type="checkbox"/> 1309A-9    | <input type="checkbox"/> 7260A/7261A-10 |
| <input type="checkbox"/> 1331A/C-12 | <input type="checkbox"/> 8012A-4        |

Please photocopy this order form if  
you do not want to cut the page  
off.

# READERS CORNER

Here's your chance to share your ideas and views with other *Bench Briefs* recipients. In Reader's Corner, we will print letters to the Editor, troubleshooting tips, modification information, and new tools and products that have made your job easier. In short, Reader's Corner will feature anything from readers that is of general interest to electronic service personnel.


If there is something you have to share with other *Bench Briefs* readers, let us hear from you.

Mr. Stanley:

The transistor checker (Sept-Oct '74 and Nov-Dec 74) can also be used for impedance matching by the following alteration:

Also by use of AF or RF generator, I assume the checker can be used to show faulty transistors which instead of bad junctions the  $h_{fe}$  has deteriorated. I am going to pursue this but my scope is only good to 10 Mc which handicaps my results. Perhaps you might try it.

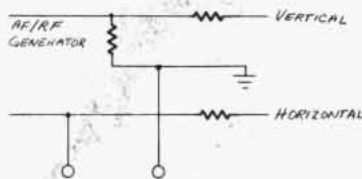Incidentally, the checker obviously can be used to locate bad connections, open PC patterns, open lamps, poor solder connections (especially if they exhibit resistance or



act as a diode), and any other applications where continuity is required.

After locating the area of the failure, I immediately switch to the checker and appear to cut servicing by at least 75% total time. I found the circuit in *Radio-Electronics* magazine about 3 years ago, but your

articles have allowed expansion of the use as now I know WHY it works as it does.

Sincerely,

J.R. Chamberlin  
R7 School District  
Lee's Summit, Missouri

$h_{fe}$  rarely deteriorates as it is primarily set by the doping ratios which do not change easily. However, leakage can change which causes an operating point shift. Also,  $h_{fe}$  decreases with frequency and this is why the data sheet value is given at a specific frequency. Any external (or internal) capacitance change will thus cause a change in this high frequency value of  $h_{fe}$ .

George Stanley

## More on Transistor Checker

The resistance values for the transistor checker (Figure 8) in the November-December issue are slightly different than those shown in the September-October issue. The two circuits are electrically identical for all practical purposes. In one case, the switch shorts out a resistor and in the other case it adds a resistor in parallel. Incidentally, in the November-December issue, the output voltage of the transformer (Figure 8) is not shown. It is 6 volts AC --- the same as in the September-October issue.

We're thinking of running a series of pictures on the interpretation of transistor checker waveforms. Some are mighty strange especially when doing incircuit testing. Even an out-of-circuit germanium power transistor can show an unusual collector-base waveform because of its relatively high  $I_{CEO}$  leakage current.

George Stanley

## HEWLETT-PACKARD COMPANY

195 Page Mill Road  
Palo Alto, California 94306

### BENCH BRIEFS

JANUARY-FEBRUARY 1975  
Volume 15 Number 1

*Bench Briefs* is published periodically by Hewlett-Packard for customers engaged in Repair, Calibration, Maintenance, Test and related areas. To obtain a qualification for a free subscription, send your request to the above address. Requests for Service Notes should also be mailed to the above address.

Customers in Europe (ONLY) should instead send all correspondence to:

Hewlett-Packard Central Mailing Dept  
P.O. Box 7550, Freeport Building  
Schiphol-Centrum  
The Netherlands

Reader comments or technical article contributions are welcomed. Please send them to the correct address for your area.

#### Staff for this issue:

Editor: Dick Gasperini, HP Palo Alto, California  
Contributing Author: John Whidden, HP New Jersey  
Layout and make-up: Christina Cruz, HP Palo Alto, California  
Typesetting: Kathy Aquino, HP Santa Clara, California

Bulk Rate  
U.S. Postage  
PAID  
Menlo Park, CA.  
Permit No.  
317

Address Correction Requested

Printed in U.S.A.