


## **Application Note**

## **Digibridge and Battery Measurements**

The QuadTech Digibridge instruments (1659, 1689, 1689M, 1692, 1693, 1710 and 1750) are particularly well suited to measure the internal impedance of batteries. The advantages are:

- □ **Automatic** Measurement
- □ The Digibridge measures the **AC resistance**. The battery voltage would effect a DC resistance measurement.
- $\Box$  The Digibridge measures capacitance well when  $D_f$  is large.
- □ The **4-Terminal Kelvin Connection** makes it easy to block the DC voltage without effecting the measurement.

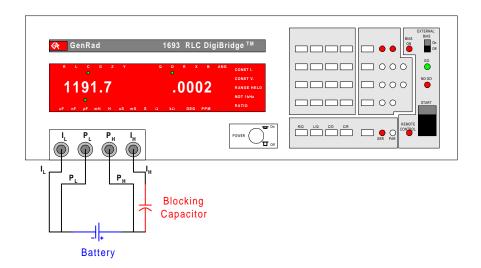A blocking capacitor is required in the **IH** lead to avoid battery discharge into the instrument. The capacitor should be installed into the test fixture and should have a reactance of less than  $10\Omega$  at the test frequency (160  $\mu$ F @ 120Hz).



For faster and more accurate testing, build a test fixture and mount the blocking capacitor in this test fixture. The test fixture should provide four terminal connection to the digibridge instrument. A 1689-9602 4-BNC to 4-BNC test cable can be used to connect the fixture to the instrument when using a 1689M, 1693, 1710 or 1750 Digibridge.

The information presented here is subject to change and is intended for general information only

©QuadTech, Incorporated
Telephone: 1-800-253-1230, Website: www.quadtech.com

Printed in U.S.A. PN 035079 May, 2000