

ELECTRONICTM

Servicing & Technology

NOVEMBER 1983/\$2.25


How to service Sharp's sweep circuits

Understanding decibels and time constants

Learning about electronics


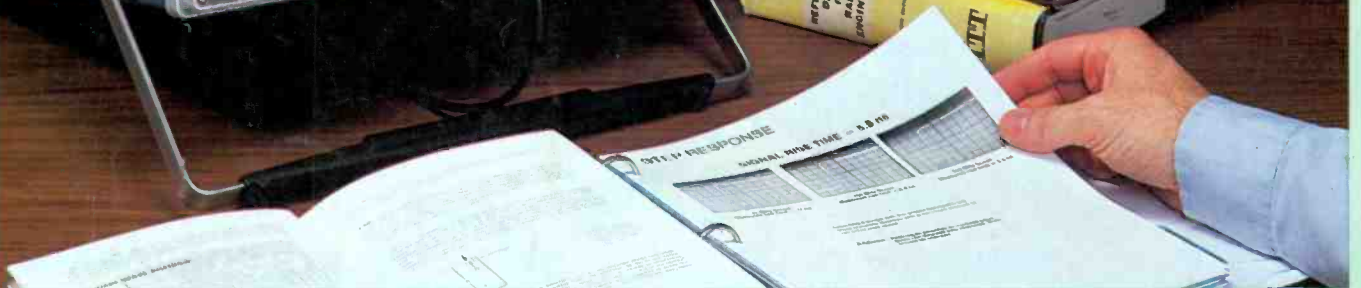
$$T_r(\text{nanoseconds}) = \frac{350}{\text{BW}(\text{MHZ})}$$



PTS Corporation
P.O. Box 272
Bloomington, IN 47402

PTS Availability

All makes/All models
available at over
1500 locations
nationwide.

**Reach for PTS quality
rebuilt tuners and modules.**

Pick up the tuners and modules you need
in one stop at PTS Servicenters and distributors
nationwide. Either way, you'll get PTS quality
that meets or exceeds all manufacturers'
specifications. Plus automatic updates for
superior performance.

Circle (1) on Reply Card



PTS CORPORATION


MCM ELECTRONICS

THE ONLY ELECTRONIC PARTS COMPANY YOU'LL EVER NEED*

QUALITY PARTS AT EVERYDAY LOW PRICES

3 1/2 DIGIT L.C.D. MULTIMETER

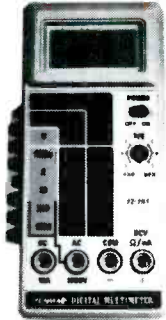.5" display 10 MEG input imp Auto polarity .1 ohm resolution overload protected. DC current 200u, 2 m, 20 m, 200 m, 10 A. Ohm 2K, 20K, 200K. 2M—1 yr. Warr.



#72-050
(Formerly DVM-1)

\$49⁹⁵

DIGITAL CAPACITANCE METER

1 pF to 1999 uF accuracy .5%, 3 1/2 digit .5" 8 ranges full scale 200 pF to 2000 uF .1 pF resolution .5 sec. sampling time crystal OSC time base 1 yr. warranty.



#72-040 **\$69⁹⁵**
(Formerly DCM-1)

AC VARIABLE TRANSFORMER

Has a built-in AMP Meter which shows excessive current draw to check for shorts before they can cause costly component failure 0-140 volts 10 AMPS.



#72-110 **\$89⁹⁵**
(Formerly AT-3)

SANYO FOCUS BLOCK

Sanyo Part #ESPA-98-F1 #Z0064



#33-748 **\$23⁹⁵ \$19⁹⁵**
(1-9) (10-up)

NEW! TOUCH TONE* TELEPHONE

Attractive modern design ■ High quality durable ABS plastic ■ Bell type ringer ■ Wall or desk phone ■ Last number redial ■ FCC approved ■ Available in Ivory or Brown ■ Tone-dial, access computers and MCI type long distance carriers ■ Available mid-August.



*TOUCH TONE is a registered trademark of AT&T

#36-240 **\$23⁹⁵ \$19⁹⁵**
(1-2) (3-up)

MCM NOW CARRIES



FLYBACKS & YOKES
50% OFF LIST
on in-stock items

Ask for your **FREE** Replacement Guide with order.

UNIVERSAL BEHIND THE SET

■ 5 section, dual VHF antenna



#30-070 **\$3³⁰ \$2⁹⁰ \$2⁴⁵**
(Formerly U-38) (1-9) (10-49) (50-up)

SHARP FLYBACK TRANSFORMERS

Sharp #RTRNF2037TAZZ

Sharp #RTRNF1106CEZZ



#33-655 **\$22⁵⁰ \$19⁹⁵**
(1-9) (10-up)



#33-750 **\$28⁹⁵ \$25⁹⁵**
(1-9) (10-up)

2SC1308K — ORIGINAL SANYO!

Most reliable horizontal output sold today, replaces ECG® 238, 165 and most other outputs.

1500v **\$1⁹⁹ \$1⁸⁵**
7a (10-99) (100-up)



T-WIK SPECIAL

■ Tenma brand braided solder remover ■ 5 ft.

#21-327

74¢
(Min. 10 pcs.)

8 VOLT FUSE TYPE LAMPS

8 volt 250 MA 1 1/4" x 1/4"



#25-090 **29¢**
(min. 100)

AGC FUSES



Buy any AGC Fuse for **4¢ ea.**
(min. 100, no mixing)

F-59 ALM



#33-410 (min. 10)

24¢ 21¢ 18¢
(10-99) (100-499) (500-up)

F-81 FEMALE SPLICE



#33-460 (min. 10)

26¢ 24¢ 19¢
(10-99) (100-499) (500-up)

CONNECTORS

GROUNDING BLOCK



#33-470

50¢ 40¢ 35¢
(1-9) (10-99) (100-up)

MATCHING TRANSFORMER


75-300 Ohm


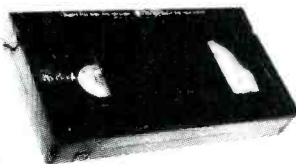
#33-050 (min. 100) **34¢**

2-4-6 HOUR VHS VIDEO TAPE

■ Top quality video tape. ■ Made in USA ■ VHS T-120. ■ Attractive packaging for display. Comes with heavy cardboard case.



#38-090

\$7⁹⁵
(1-9)

\$6⁹⁵
(10-49)

\$5⁹⁵
(50-up)

COTTON SWABS

■ Great for tape machine maintenance ■ 6" wooden stick for getting into tight places ■ 100 per bag

#21-060 **85¢**
(1-49 bags)

70¢ 65¢
(50-99 bags) (100 bags-up)

VCR FOAM SWABS

■ Absorbent foam material. Perfect for delicate cleaning jobs. Will not separate or leave fibers on the VCR head ■ 50 per bag

#21-050 **\$1⁶⁰**
(1-49 bags)

\$1⁵⁰ \$1³⁵
(50-99 bags) (100 bags-up)

HIGH GAIN DELUXE VHF TO UHF 40 CHANNEL CABLE CONVERTER

+ 5 to + 8 db GAIN!

■ Amplifies low level CATV lines []. Includes mid and superband channels. FULL FEATURES ■ Uses your UHF tuner to access cable TV channels ■ Channel conversion chart included ■ Front fine tuning adjustment ■ + 5 to 8 db UHF gain ■ Wide input range ■ Flat frequency response ■ Easy installation ■ High reliability ■ Compatible with built-in remote tuning systems ■ Accessible master oscillator control for entire band adjustment for multiple STV applications

#32-100

\$23⁹⁵ \$19⁹⁵
(1-9) (10-up)



mcm
ELECTRONICS
RIGHT PARTS, RIGHT PRICE,
SHIPPED RIGHT AWAY.

*Call Today for Your **FREE** 96-pg. Summer Catalog #6 and see our complete line of over 4,000 parts.

CALL TOLL **FREE 1-800-543-4330**

(In Ohio 1-800-762-4315)

858 E. CONGRESS PARK DR. CENTERVILLE, OH 45459


Circle (4) on Reply Card

The how-to magazine of electronics...

ELECTRONIC

Service & Technology

November 1983
Volume 3, No. 11

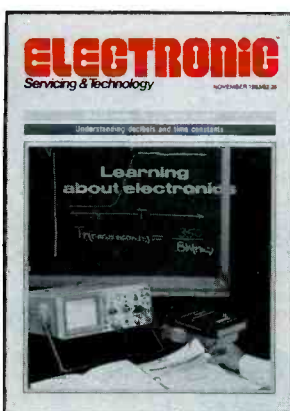

Electronics manuals, spec sheets and specific instruction handbooks are ideal sources for updating your electronics knowledge. For other methods of expanding your knowledge, see "Learning about Electronics" on page 24. (Cover photo courtesy of Tektronix.)

10 How to service Sharp's sweep circuits

By Homer Davidson

Most service problems originate in the sweep circuit of color TV receivers. By knowing symptoms and cures for these problems, Davidson focuses on some symptoms and provides the cures for the supply, horizontal and vertical sweep problems.

24 Learning about electronics

By Conrad Persson, editor

In today's rapid pace of electronics, keeping up with all of the electronics developments is of prime concern for the consumer. For the service technician, it is just as vital to keep updated and educated on troubleshooting techniques and repair methods.

40 Using linear ICs

By Joseph Carr

The author discusses the construction of linear ICs, how they are used and how to troubleshoot circuits that might be defective.

48 Test your electronic knowledge

By Sam Wilson, IS CET test director

See how you would do on the Certified Electronic Technicians' test. This month's questions cover power supply.

50 Decibels and time constants

By Sam Wilson, IS CET

The relationship of logarithms and the number called epsilon help in explaining the equation for decibels and time constants.

52 Symmetrical output circuits

By Bud Izen, CET/CSM


Three basic variations of the complementary type of audio output circuit are examined as well as their advantages and disadvantages in practical applications.



Departments

- 4 Editorial
- 6 Technology
- 22 Books
- 26 Feedback
- 28 Troubleshooting Tips
- 29 Profax
- 38 Readers' Exchange
- 56 Symcure
- 58 Products
- 61 Literature

Page 6

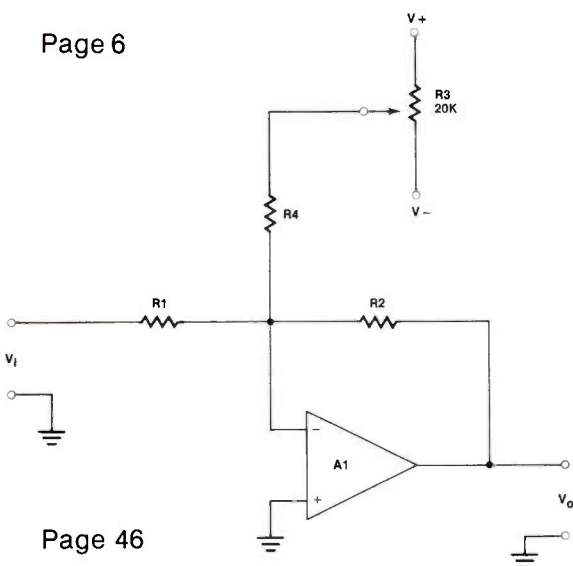

Page 46



Page 22

Next month...

One of the more common items we see on the audio servicing bench is the cassette recorder. Although most repairs are the garden variety of clean-and-lube routines, occasionally we have to change a head or readjust the internal controls to get the machine back up to its operating potential. Kirk Vistain describes some of the adjustments that most commonly require attention.

Kill the umpire?

One of the problems with athletic events is that judging is done by mere humans, who are fallible. Even when officials are totally unbiased, they occasionally make mistakes. And have you noticed that when they make a bad call it always goes against your team?

In international athletic competition, the difficulties are compounded by nationalistic fervor. For example, according to researcher Joan de Regt of International Resource Development, an independent consulting firm in Norwalk, CT, "Political controversies often arise when you have a Yugoslavian judge who awards a Soviet gymnast an undeservedly high score, while an American judge might give that same gymnast an undeservedly low score. With the final outcomes of these events often decided by fractions of a point, it's a shame to see prejudice or political haggling obscure true athletic accomplishment."

How do you eliminate the human factor in judging events such as this? Why, turn it over to that electronic marvel, the computer, of course. It would work something like this. Computerized images for the ideal moves for the events would be recorded and made part of a computer database. When the athlete performs in competition, the performance would be recorded and transformed into computerized images, which would be compared with the record of the ideal routine. The score would be determined on the basis of this comparison.

According to de Regt, the use of such a system is likely to occur "sometime within the next four or five Olympiads," or roughly by the year 2000.

"It's not such a giant step to take," she says. "Many physicians are already using such imaging systems to analyze the mechanical factors involved

in sports injuries."

This conjures up images of what might eventually be if this type of judging system were to be exploited to the fullest in all sports.

Just imagine in football, for example. We could put an electronic device inside the football and install sensors in the field. There would be no question of whether the offense had made the first down, or whether the ball had broken the plane of the goal line for a touchdown.

But it's in baseball that electronics could really do the job. Wouldn't it be great to eliminate all the umpires? For starters it would be a simple matter to get rid of the guy behind the plate. We'd replace home plate with a bar-code reading device like at the grocery store, and put bar codes on the baseballs and bats. Not only would you know if the ball was in the strike zone, you'd be able to detect whether the pitch was a fastball, curve, slider or sinker. You could also tell how fast the pitch was and if the batter swung early, late, high or low, or where he met the ball if he made contact. Sensors along the foul lines and base paths and at bases could take care of questions of fair or foul and safe or out.

But then, who would fans have to boo when a call went the wrong way? And who would Billy Martin kick sand on when he got frustrated? Baseball just wouldn't be the same without those men in blue whom fans just love to hate.

In this increasingly automated and computerized world, some jobs are best left to humans.

Nils Conrad Persson

ELECTRONIC

Servicing & Technology

Editorial, advertising and circulation correspondence should be addressed to: P.O. Box 12901, Overland Park, KS 66212-9981 (a suburb of Kansas City, MO); (913) 888-4664.

EDITORIAL

Bill Rhodes, *Editorial Director*
Nils Conrad Persson, *Editor*
Carl Babcoke, *Consumer Servicing Consultant*
Rhonda Wickham, *Managing Editor*
Tina Thorpe, *Associate Editor*
Jane Cigard, *Associate Editor*

ART

Kevin Callahan, *Art Director*
Jonl Harding, *Graphic Designer*

CIRCULATION

John C. Arnst, *Director*
Evelyn Rogers, *Manager*
Dee Manies, *Reader Correspondent*

ADMINISTRATION

R. J. Hancock, *President*
Cameron Bishop, *Publisher*
Eric Jacobson, *Associate Publisher*

ADVERTISING

Greg Garrison, *National Sales Manager*
Liz Turner, *Production Manager*
Robyn Kahn, *Marketing Coordinator*



Member, Audit Bureau
of Circulation



Member, American
Business Press

ELECTRONIC SERVICING & TECHNOLOGY (USPS 462-050) (with which is combined Electronic Technician/Dealer) is published monthly by Intertec Publishing Corp., 9221 Quivira Road, P.O. Box 12901, Overland Park, KS 66212-9981. Second Class Postage paid at Shawnee Mission, KS 66201. Send Form 3579 to P.O. Box 12952, Overland Park, KS 66212-9981.

ELECTRONIC SERVICING & TECHNOLOGY is the "how-to" magazine of electronics. It is edited for electronic professionals and enthusiasts who are interested in buying, building, installing and repairing home-entertainment electronic equipment (audio, video, microcomputers, electronic games, etc.).

SUBSCRIPTION PRICES: one year \$15, two years \$26, three years \$34 in the USA and its possessions. Foreign countries: one year \$20, two years \$30, three years \$40. Single copy price \$2.25; back copies \$3.00. Adjustment necessitated by subscription termination to single copy rate. Allow 6 to 8 weeks delivery for change of address. Allow 6 to 8 weeks for new subscriptions.

PHOTOCOPY RIGHTS: Permission to photocopy for internal or personal use is granted by Intertec Publishing Corp. for libraries and others registered with Copyright Clearance Center (CCC), provided the base fee of \$2 per copy of article is paid directly to CCC, 21 Congress St., Salem, MA 01970. Special requests should be addressed to Cameron Bishop, publisher. ISSN 0278-9922



INTERTEC PUBLISHING CORP.

©1983 All rights reserved.

The Digital vs. Analog battle is over.

\$85* buys you the new champion. **The new Fluke 70 Series.**

They combine digital and analog displays for an unbeatable two-punch combination.

Now, digital users get the extra resolution of a 3200-count LCD display.

While analog users get an analog bar graph for quick visual checks of continuity, peaking, nulling and trends.

Plus unparalleled operating ease, instant autoranging, 2,000+ hour battery life and a 3-year warranty.

All in one meter.

Choose from three new models. The Fluke 73, the ultimate in simplicity. The feature-packed Fluke 75. Or the deluxe Fluke 77, with its own multipurpose protective holster and unique "Touch Hold" function (patent pending) that captures and holds readings, then beeps to alert you.

Each is Fluke-tough to take a beating. American-made, to boot. And priced to be, quite simply, a knockout.

For your nearest distributor or a free brochure, call toll-free anytime **1-800-227-3800, Ext. 229**. From outside U.S., call 1-402-496-1350, Ext. 229.

FROM THE WORLD LEADER IN DIGITAL MULTIMETERS.



Fluke 73

\$85*

Analog/digital display
Volts, ohms, 10A, diode test

Autorange

0.7% basic dc accuracy

2000+ hour battery life

3-year warranty

Fluke 75

\$99*

Analog/digital display
Volts, ohms, 10A, mA, diode test

Audible continuity

Autorange/range hold

0.5% basic dc accuracy

2000+ hour battery life

3-year warranty

Fluke 77

\$129*

Analog/digital display
Volts, ohms, 10A, mA, diode test

Audible continuity

"Touch Hold" function

Autorange/range hold

0.3% basic dc accuracy

2000+ hour battery life

3-year warranty

Multipurpose holster

* Suggested U.S. list price, effective October 1, 1983.





Liquid-crystal technology colors display capabilities

Tektronix' new color display system does not use shadow masks or penetration phosphors. Based on a combination of liquid-crystal and CRT technologies, the system combines a monochrome CRT and liquid-crystal "color switch" to produce a high-resolution, field-sequential color display.

Because no shadow mask or patterned phosphors are used, the resolution can be as high as any monochrome CRT. This is a particular advantage in small display sizes where high-resolution color has not been practical before. Other advantages are inherent convergence (because only one electron beam is used), excellent contrast in high ambient light, and ruggedness, due to the absence of any fragile shadow mask or complex electron gun.

Previous attempts at producing a field-sequential system have suffered from the lack of a suitable fast color switch. The Tektronix liquid crystal color display uses a new, proprietary, fast liquid crystal optical switch combined with a monochrome CRT.

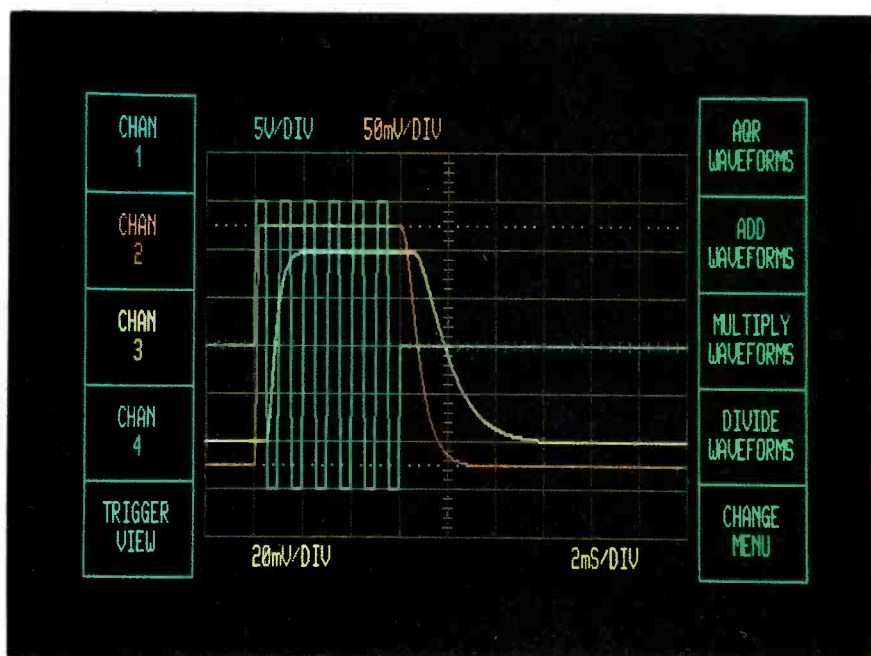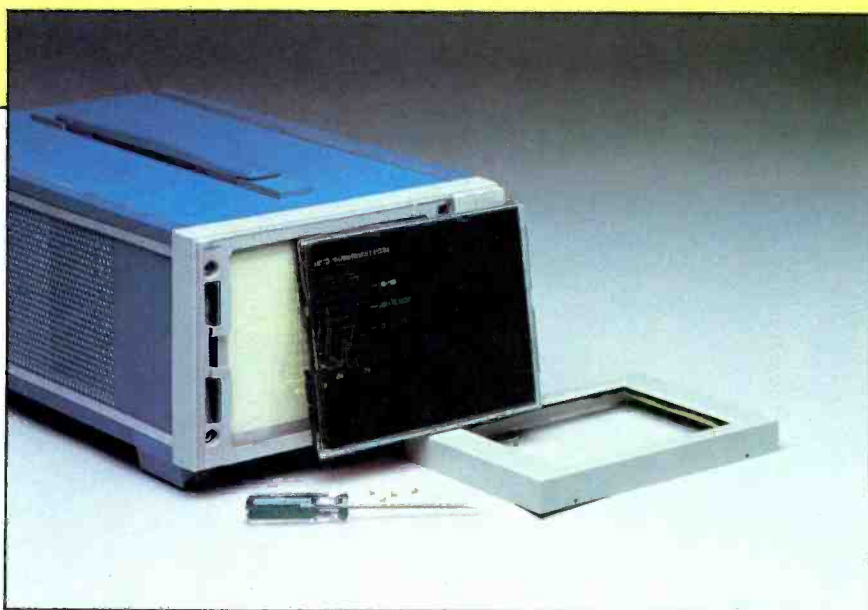The assembly consists of a sandwich of special polarizers and Tektronix' proprietary liquid crystal π -cell. The liquid crystal color shutter acts similar to a



(Information and photos courtesy of Tektronix)

REACH FOR RELIABILITY



REPLACEMENT
★ SK ★
SOLID STATE

RCA

RCA Distributor and
Special Products Division,
Deptford, NJ 08096

filter that switches between two states, one allowing primary color #1 to pass and the other passing primary color #2. The shutter switches between the two states in a few milliseconds upon the application of a low voltage electrical drive signal.

The CRT has a simple phosphor with two separate emission peaks that are typically, but not limited to, red and green. The phosphor does not require any patterning or special process steps. In any one field, the information written on the screen appears only in the color selected by the electronic switch. Each color is repeated at a 60Hz rate, requiring the 2-field system to run at a 120Hz rate. This field-sequential system can provide all possible mixtures of

the two primary colors contained in the phosphor.

Research is continuing to extend the concept to three fields, with three primary colors, which will produce a full color gamut comparable to or better than conventional color display technologies.

Examples of where this new technology can provide color capability where it has not been practical before include:

- Small instrument displays, such as oscilloscopes, logic analyzers and spectrum analyzers. In the past, the need for high resolution to present waveform information has been a drawback. Now, Tektronix' liquid crystal color display's ability to function in

both refresh vector and raster display modes makes new design breakthroughs possible.

- Small process control displays, such as those included on vacuum systems, can now include color for highlighting special situations and warnings.
- Computer workstations, where high-resolution is important.
- Word-processing equipment, where monochrome displays have been typically used because high-resolution color displays have either not been possible or too expensive. Tektronix' liquid crystal color display technology allows the addition of color without any resolution penalty.

ES&TTM

Order Your INTERTEC Mailing Labels NOW and **SAVE!**

To take advantage of these savings, your list rental must be completed and billed by **December 31, 1983**, or discount offers do not apply.

- 1. 10% DISCOUNT FOR USE OF UP TO 10,000 SUBSCRIBER NAMES**
 - 5,000 name minimum
 - Sample mailing piece required
- 2. LARGER 15% DISCOUNT WHEN YOU RENT MORE THAN 10,000 NAMES**
 - Sample Mailing piece required.

Because we want your business NOW, we're making you an offer we've never made before. INTERTEC PUBLISHING CORP. has successfully served various markets (including this one) for over 95 years. Each magazine's subscriber list offers unparalleled direct marketing opportunities.

List of Publications: **Broadcast Engineering, Electronic Servicing & Technology, Grounds Maintenance, Implement & Tractor, Land Mobile Product News, Lawn & Garden Marketing, Video Systems.**

For further information, call Rosanne Navran, Directing Marketing Co-ordinator, TODAY!



INTERTEC
PUBLISHING
CORP.

(913) 888-4664

P.O. BOX12901
OVERLAND PARK, KS 66212

We've got it all together.



Weller



Weller



Xcelite



Wiss



Nicholson



Boker

Boker[®]
Crescent[®]
Lufkin[®]
Nicholson[®]
Plumb[®]
Weller[®], Wiss[®]
Xcelite[®]



Lufkin



Crescent



Plumb

Take a good look round this ad and you'll agree that "All together" is no exaggeration. Whether you're making or mending, cutting or joining, striking, measuring or stripping, there's a Cooper tool that's just right for the job. Don't take chances on tools. Specify Cooper and get 'em right the first time!



The Cooper Group PO Box 728 Apex NC 27502 USA Tel (919) 362-7510 Telex 579497

CooperTools

Circle (7) on Reply Card

www.americanradiohistory.com

How to service Sharp's sweep circuits

By Homer L. Davidson

In color TV receivers, most service problems originate in the sweep circuits or the power supplies. This certainly is true in 13in and 19in models by Sharp.

These models (Photofact 1959-2, for example) have several dc-voltage supplies produced by rectification of horizontal-sweep pulse or scan peaks. These voltage sources are stabilized by regulation of the +120V that is supplied to the horizontal-output transistor. However, the situation is complicated by two limitations. At turn-on, no horizontal sweep is generated, although it is necessary for proper operation of the +120V supply. This same +120V is essential for proper operation of the horizontal sweep. These contradictions are resolved through a series of small steps. An insufficient +120V supply at turn-on allows the horizontal sweep to operate weakly. The weak sweep increases the +120V actual voltage, which in turn strengthens the sweep, until the sweep is maximum and the regulated voltage is +120V. You must consider this interdependence of horizontal sweep and regulated voltage in troubleshooting of these two basic systems.

Low voltage and regulation

Figure 1 shows the complete low-voltage sources and +120V regulation for Sharp model C1935 (Photofact 1959-2). In normal operation of this circuitry, the full +164V from the bridge rectifier is applied to the SCR701 anode. SCR701 is gated into conduction by the I701 power-regulator IC at a time during each horizontal-sweep cycle as required to provide a constant +120V at integrating capacitor C708. An SCR, once it is gated on, continues conduction un-


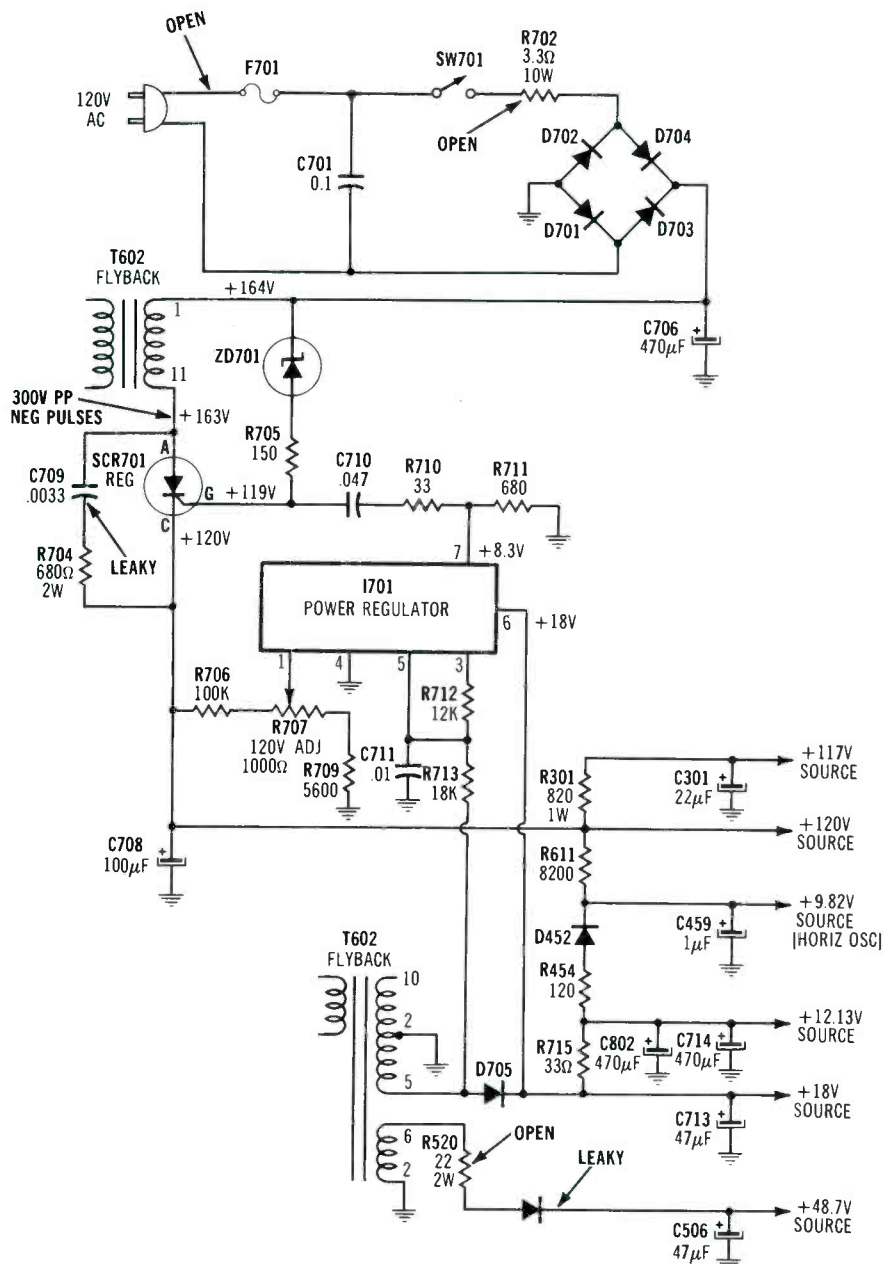


Figure 1. A bridge rectifier and C706 produce a filtered +164V supply that is regulated to +120V by SCR701 and I701.

THINKING TVRO?

Take A Look At Winegard!

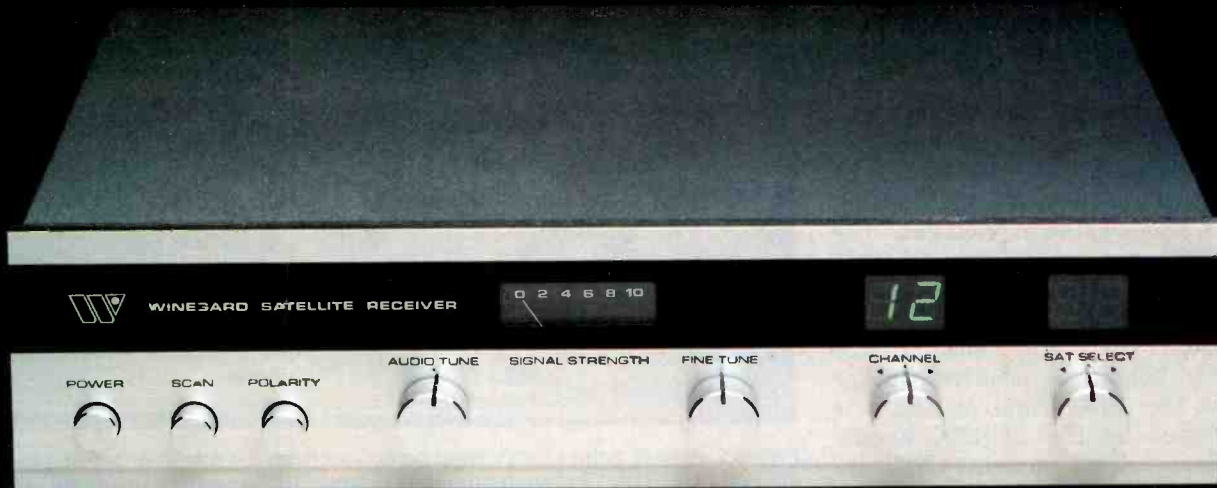

Excellent picture quality and low cost. That's what you get with Winegard's SC-5000S home satellite television system.

You'll discover that Winegard's 8-foot package incorporates all the latest in TVRO solid-state design and engineering for a dramatic difference in satellite TV reception. All the features that your customers want are there!



Why Buy Winegard Home Satellite TV Reception Products?

All Your Satellite Product Needs From One Source • Competitive Pricing • Easy to Handle, Ship and Inventory • All Satellite Products Backed By A Full-Year Warranty • Easy-To-Install • Complete And Professional Factory Support And Service • Rigid Quality Control Standards For Satellite TV Products

SC-7032S RECEIVER FEATURES:

- Rapid Scan Control
- Fine Tune
- Polarity Switch
- Channel Select Control
- Audio Tune
- Satellite Select
- Signal Strength Meter
- Remote Control Optional

SC-8009 ANTENNA FEATURES:

- 8-ft. Durable Spun Aluminum Reflector with Weather Resistant White Epoxy Finish
- Easy Handling and Shipping
- Complete Arc Coverage
- Choice of Rugged Pedestal or Post Polar Mounts
- Prime Focus Feed with Automatic Electronic Polarity Switching
- 90mph Wind Survival

WINEGARD
SATELLITE SYSTEMS

WINEGARD COMPANY • 3000 KIRKWOOD STREET • BURLINGTON, IOWA 52601 • (319) 753-0121

Write for information about SASA, the professional satellite TV installers network.

til the anode voltage becomes negative relative to the cathode. Negative-going horizontal-sweep pulses from the flyback (pins 1 and 11) turn off SCR701. Power is applied to C708 from SCR701's rectification of these same negative-going pulses as well. Of course, all SCRs can be efficient rectifiers when supplied with proper gating and anode/cathode voltages. The +164V applied to the SCR701 anode changes the zero-voltage point of the anode negative-going pulses. Therefore, most of the pulse height is positive (rather than the usual negative) and it is rectified by the SCR701 anode/cathode diode action. C708 integrates these two source voltages (gated dc from the +164V plus rectified dc from the SCR) into an average voltage. When SCR701 is gated-on at the proper time during each horizontal cycle, a constant regulated voltage is produced.

It should be clear now why an insufficient voltage of about +76V is obtained from the +120V supply when there is no horizontal sweep: Without the SCR701 anode pulses, one of the power sources is missing, and the regulator gates-on the SCR at incorrect times.

Of course, the +120V regulator cannot operate correctly unless it is supplied with +164V from the bridge diodes that rectify the 60Hz line power. You should verify the presence of +164Vdc at the SCR701 anode before you waste too much time checking the regulator circuit.

A lower-than-normal supply voltage is obtained for the horizontal-oscillator circuit through R611 from the +120V source during start-up (or when the horizontal-sweep system is dead). When correct start-up activates the +18V source (from rectified horizontal-sweep power), D452 is forward biased and the oscillator voltage comes through R454, producing +9.82V supply for the oscillator. In other words, oscillator supply voltage comes through R611 during *start-up* and through R454 during normal *run* operation.

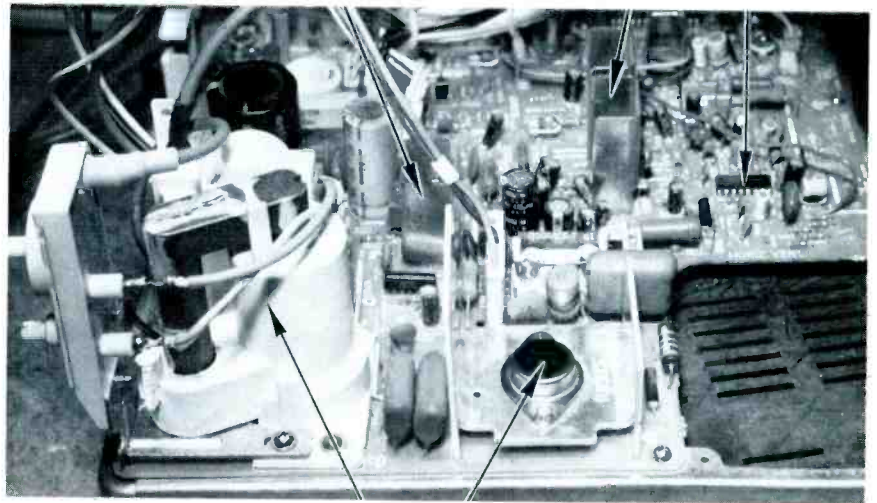


Figure 2. Arrows point to important components on the circuit board of a Montgomery Ward GSK12981B manufactured by Sharp. Clockwise from upper left, arrows indicate SCR701 heat sink, heat sinks for vertical output Q502 and Q503, I501, Q602 horizontal output, and the T602 flyback with focus and screen controls.

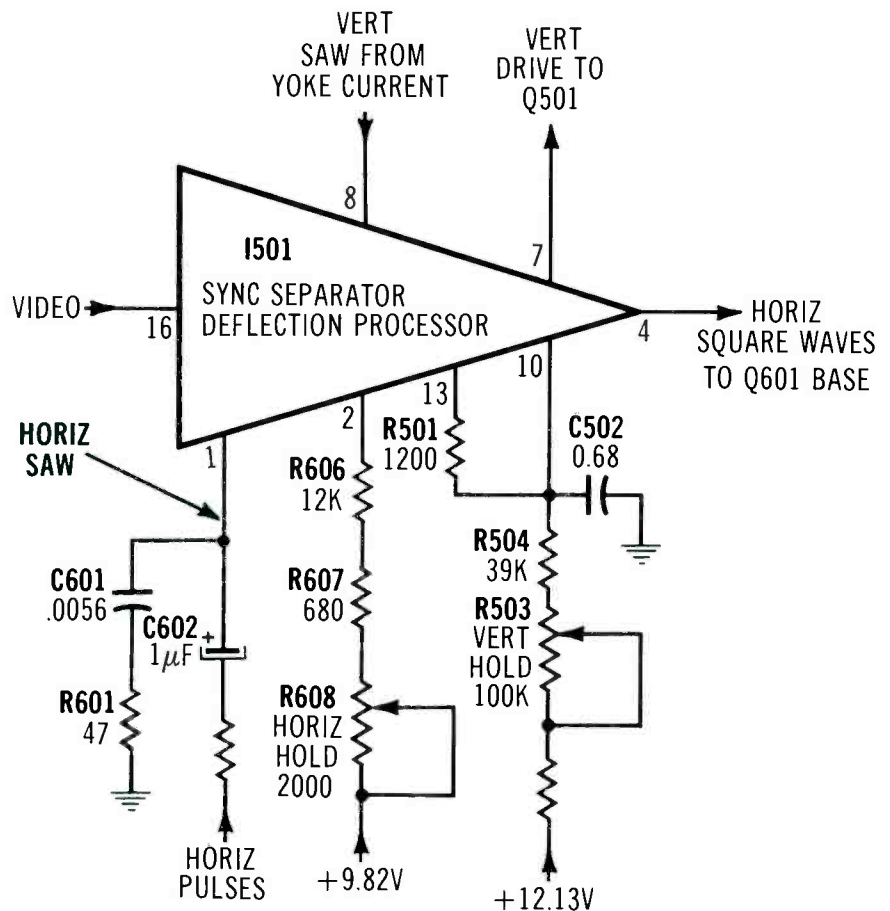


Figure 3. Solid-state components for sync separation, horizontal phase detector, horizontal oscillator and vertical oscillator are inside IC I501.

The dc power for the horizontal-driver and horizontal-output transistors comes from the +120V

source at all times. However, at turn-on before start-up is complete, this voltage is less than

+80V. The low oscillator, driver and output start-up voltages can produce only weak sweep, even with a non-defective receiver. If start-up is not completed because of a sweep defect (or if start-up is followed immediately by shut-down), some of these stages might have a weak signal plus typically low start-up dc voltages.

The following are helpful suggestions for analyzing supply problems:

- Loss of horizontal sweep at the T602 flyback eliminates the high voltage, CRT screen voltage, CRT focus voltage, +171V boost supply, +12.13V source, +18V source and the +48.7V source.
- Loss of all +120V source also eliminates the +117V source and the horizontal oscillator start-up source voltage.
- The +117V source supplies only the sound-output transistors.
- The +171V boost source supplies only the red, blue and green output transistors that drive the CRT cathodes.
- The +120V regulated source supplies the horizontal-output transistor directly, the driver transistor through a dropping resistor, the +117V source through a resistor and the oscillator start-up voltage through R611.
- The horizontal oscillator operates after start-up from the +9.82V source.
- The +12.13V source supplies the vertical oscillator, some video and chroma stages and the IF stages.
- The +18V source supplies the sound IF stages and some chroma functions. Also, it supplies the +12.13V source (through resistors) and the horizontal oscillator start-up voltage.
- Two vertical-output transistors operate from the +48.7V source.

Servicing power supplies

Higher-than-normal voltages in the +120V source can be caused by leakage in SCR701 or C709

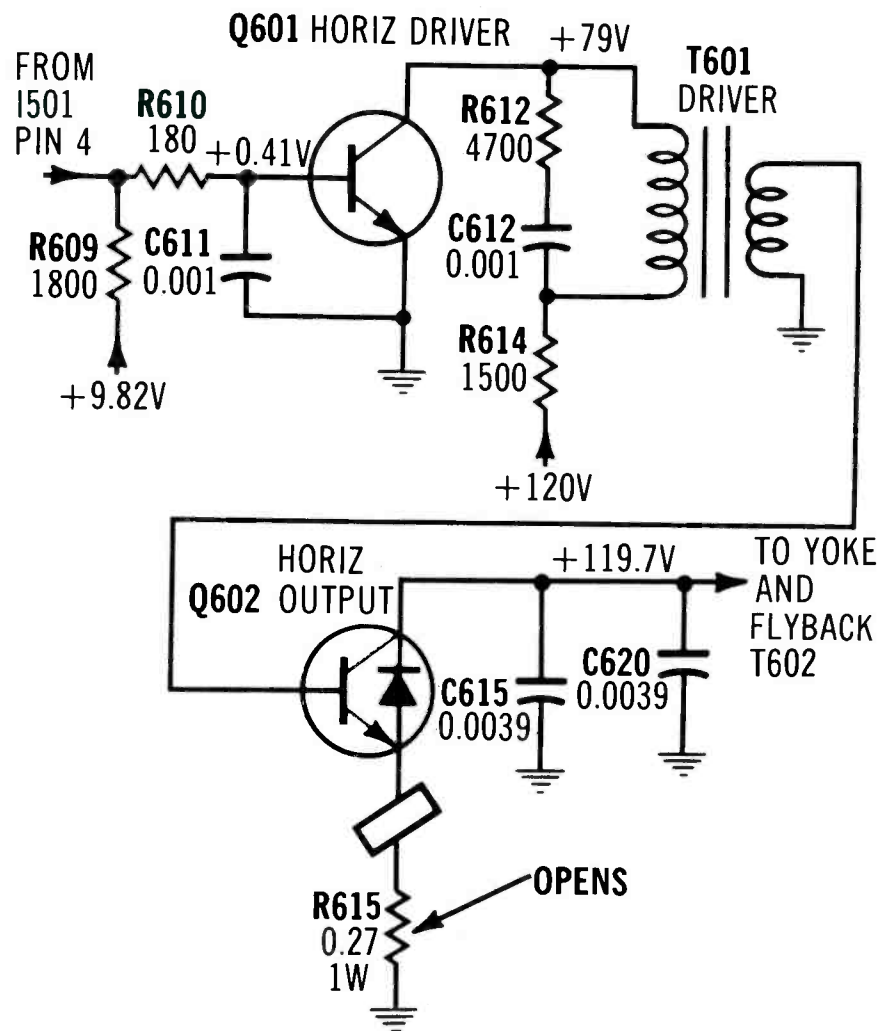


Figure 4. The horizontal driver and output stages are not unusual, except for the damper diode inside the Q602 transistor case and emitter resistor R615, which sometimes causes a motorboating of the +120V supply.

(0.0033 μ F), which feeds a steady current from the +164V supply to the +120V supply. A shorted ZD701 zener can maintain SCR701 in constant conduction. Also, a defective I701 regulator IC can produce excessive +120V source voltages, although this is rare. Another possibility is increased resistance in R706 (Figure 1).

Most SCR701 leakages can be found with a high-power ohmmeter (low-power mode voltage is not sufficient to check gate-to-cathode diode action), however the SCR should be removed from the circuit during the tests. Normal resistance between gate and cathode might measure 50 Ω to perhaps 900 Ω , depending on the

ohmmeter used. Notice, however, that the ohmmeter polarity must apply the positive polarity to the gate and the negative probe to the cathode. Resistances between anode and cathode or gate should be very high, perhaps above 5M Ω .


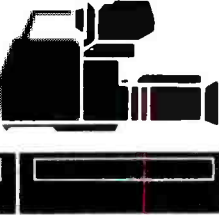

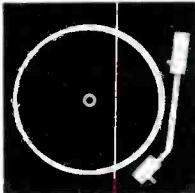

Low voltage from the +120V supply can be caused by these conditions: a low +164V line-rectified supply voltage, an increased resistance in R709, decreased R706 resistance or a loss of horizontal sweep.

Always remember that no more than +76V can be obtained from the +120V source unless the horizontal sweep is operating correctly.

Loss of all voltage in both the

SPECIAL PUBLICATIONS NOW AVAILABLE FROM SONY!

- A collection of books on key concepts, in-depth theory of circuit operation and troubleshooting-aid for the following three categories of Sony products: AUDIO, BETAMAX, TV.
- The material is presented concisely. These books, although written for the average to advanced technicians, can be used as a self-help guide by anyone who is interested in Sony consumer products.

	MODEL & DESCRIPTION	PART NUMBER	PRICE
	TV Products		
	Alpha-1 Chassis New Circuit Operation	2CTV480-2	\$5.00
	Alpha-1 Chassis Troubleshooting Guide	2CTV1080-1	5.00
	30P Chassis New Circuit Operation	2CTV681-1	7.00
	30P Chassis Troubleshooting Guide	2CTV1181-1	7.00
	Betamax Products		
	SL-5400 System Control and Troubleshooting Guide	2BETA180-1	\$3.00
	SL-2500 New Circuit Operation	2BETA982-1	5.00
	SL-5800 New Circuit Operation	2BETA681-1	3.00
	AG-400 Auto Changer Circuit Operation	2BETA1182-1	3.00
	HVC-2000 Circuit Operation	2CC1281-3	10.00
	HVC-2400 Circuit Operation	T-999-714-31	5.00
	Trinicon Color Cameras	2CC383-1	10.00
	Audio Products		
		PS-X65, -X75 Circuit Operation and Troubleshooting Guide	2HF181-5
PS-X700, -X500, -LX5 Circuit Operation and Troubleshooting Guide		2HF1282-2	5.00
	CRF-1 Theory of Operation	2HF1082-4	3.00
	STR-VX6, -VX5, -VX4, -VX3, -VX2, -VX1 Circuit Operation	2HF1181-1	5.00
	STR-V55, -V45, -V35, -V25 Circuit Operation	2HF481-2	5.00
	ST-J75 Circuit Operation and Troubleshooting Guide	2HF781-4	5.00
	RS-20 Circuit Operation	2HF782-1	3.00
	PCM-F1 Troubleshooting Guide	9-959-013-11	3.00
	CDP-101 Troubleshooting Guide	9-959-021-11	3.00
	Miscellaneous		
	RF Interference Handbook	2TV990-1177-1	\$5.00
	Digital Electronics	2G183-1	8.00
	Remote Control System	2RM383-1	3.00

SONY®

TO ORDER: Send check or money order payable to "Sony Corporation of America" and mail to: Sony National Parts Center, 8281 NW 107th Terrace, P.O. Box 20407, Kansas City, MO 64153

FOR FURTHER INFORMATION: Contact Lloyd Barningham,

Tel. (816) 891-7550

Circle (10) on Reply Card

November 1983 *Electronic Servicing & Technology* 15

+164V and +120V sources usually indicates that a strong overload (such as a shorted horizontal-output transistor) has blown the F701 4A fuse, or opened 3.3Ω R702. A shorted bridge rectifier also can ruin these two components, as can a shorted C706 main filter capacitor.

Horizontal-sweep problems

I501 deflection-processor IC (Figure 2, arrow at far right) contains the solid-state transistors for the horizontal and vertical oscillator circuits. A partial schematic is shown in Figure 3. Composite video comes into I501 at pin 16. The sync is separated inside I501 and applied to an internal phase detector. Horizontal pulses are integrated into sawteeth by R602, C602, C601 and R601. These sawteeth enter I501 at pin 1 where they are applied to the horizontal phase detector. Remember that sync and horizontal sawteeth are equally essential for solid locking and correct frequency. Whenever horizontal frequency is unstable, scope these signals at pins 16 and 1.

Horizontal-frequency square waves exit I501 at pin 4 and are applied to the Q601 base (Figure 4) as input signal and dc positive forward bias. Q601 inverts and amplifies the drive signal, and this stronger signal is coupled and impedance-matched by T601 driver transformer, which in turn drives the base of Q602, the horizontal-output transistor. Q602 then supplies sweep power to the deflection yoke and the T602 flyback.

Notice that the horizontal-output transistor is not a conventional type, but it has the damper diode inside the transistor case. Do *not* attempt to substitute a common type that does not have the diode. The transistor will fail when there is no damper diode. If possible, replace Q602 with the original 25D870 or 25D869 component.

All signals of the Figure 3 and Figure 4 circuits can be scoped safely, which makes the scope the instrument of choice for testing

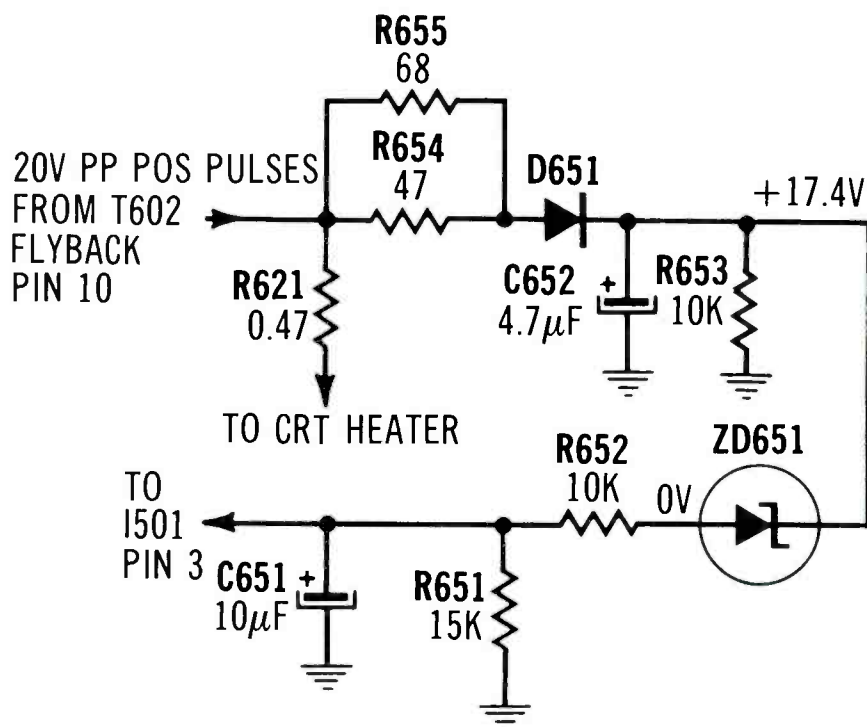


Figure 5. Horizontal pulses from the T602 flyback are rectified by D651, and the positive voltage is stored in C652. When the pulse amplitude (and the high voltage) is not excessive, the dc voltage does not exceed the 20V ratings of the ZD651 zener diode so no positive voltage passes through R652 to reach I501 pin 3. When the high voltage is excessive, voltage passes through ZD651, making pin 3 positive and the IC latches to remove the horizontal-drive square waves. Without drive to the Q601 driver transistor, the horizontal sweep is killed, and this also removes all scan-rectified power sources, eliminating the picture and sound.

these horizontal stages. Scope the horizontal signal path starting with I501 pin 4 and continuing to the Q601 base, the collector of Q601, the Q602 base and finally the Q602 collector. When you locate the first missing or distorted waveform, you have isolated the problem to the circuit stage just prior to that point.

In a number of sets, resistor R614 (Q601 collector voltage, Figure 4) has become open, removing the collector voltage and signal. A dc-voltage reading of about +9V without any square waves at I501 pin 4 usually indicates that the IC is defective and should be replaced. Low dc voltage readings at other I501 pins also can point to a defective IC.

Frequently, when a Q602 output transistor shorts, emitter resistor R615 burns from the overload. After a new Q602 is installed, the weakened resistor can cause a pulsating voltage in all supplies

taken from horizontal-sweep power.

Horizontal shut-down operation

In theory, any time the high voltage becomes dangerously high (producing X-rays), an X-ray protection circuit should immediately reduce the high voltage to a safe value. However, none of the late-model color receivers do that. Instead, the horizontal sweep is eliminated, along with the high voltage, the raster and the picture. Most circuits maintain this condition until the power is shut off. If the overvoltage condition that triggered the shut-down is not permanent, the performance can be restored by turning off the receiver power for a minute and then switching it back on. Of course, if the overvoltage condition is still present, the start-up will be followed instantly by shut-down.

A schematic of the Sharp shut-

The complete library of replacement semi's.



Here's the one guide that has it all—the new ECG® Master Guide. It's 545 pages, packed with over 3000 ECG semiconductors that replace over 200,000 industry numbers. And our replacements meet or exceed the specs of the original parts. So if it's ECG, you can count on it to fit and work.

Reduce equipment downtime and save yourself endless hours of parts hunting. For everything from analog amplifiers to zener diodes, go with replacement semiconductors from ECG. Get your new ECG Master Guide and our "Counterpoints" product updates from your nearest distributor. For his name and number, call 1-800-225-8326 toll-free (in Massachusetts, dial 1-617-890-6107). Or just send \$3.25 for your ECG Master Guide to Philips ECG, Inc., Dept. EST, 70 Empire Drive, West Seneca, NY 14224.

**If it's ECG, it fits.
And it works.**

Philips ECG

A North American Philips Company

down circuit is shown in Figure 5. Pulses from the flyback winding that supplies CRT-heater power are rectified by diode D651, producing about +17V to +18V. C652 acts as a peak-reading filter capacitor and also stores the voltage for a time to prevent erratic operation. Unless the flyback pulses are abnormally high, the C652 dc voltage does not go anywhere, because the 20V rating of zener diode ZD651 is not exceeded. Therefore, the zener anode and I501 pin 3 have zero volts, permitting normal oscillator operation.

If the flyback-pulse amplitudes increase abnormally for any reason (such as an open retrace-tuning capacitor or excessive regulated voltage), the ZD651 zener voltage is exceeded, forcing positive voltage through ZD651, R652 and I501 pin 3. This eliminates the output square waves at I501 pin 4. Without a drive signal, the horizontal-sweep circuit stops all operations, which eliminates raster, picture and sound; the receiver becomes totally dead.

A receiver that appears to be in shut-down mode presents several problems to technicians. The first decision is whether the shut-down action has occurred because the flyback pulses were excessive (the only valid reason for shut-down), or whether the shut-down circuit itself has a defect that triggers shut-down when no problem exists with excessive high voltage or pulse amplitude.

It is easy to defeat the shut-down circuit (*but this is not recommended, as it could result in damage to the set*). Turn off the ac power, ground pin 3 of I501 and turn on the ac power. That's all. If the receiver previously had been in shut-down because of a defect in the shut-down circuit, the receiver now should operate correctly, including all supply voltages and the high voltage.

If excessive high voltage had caused the shut-down, the receiver should operate, but with possible danger from picture-tube damage

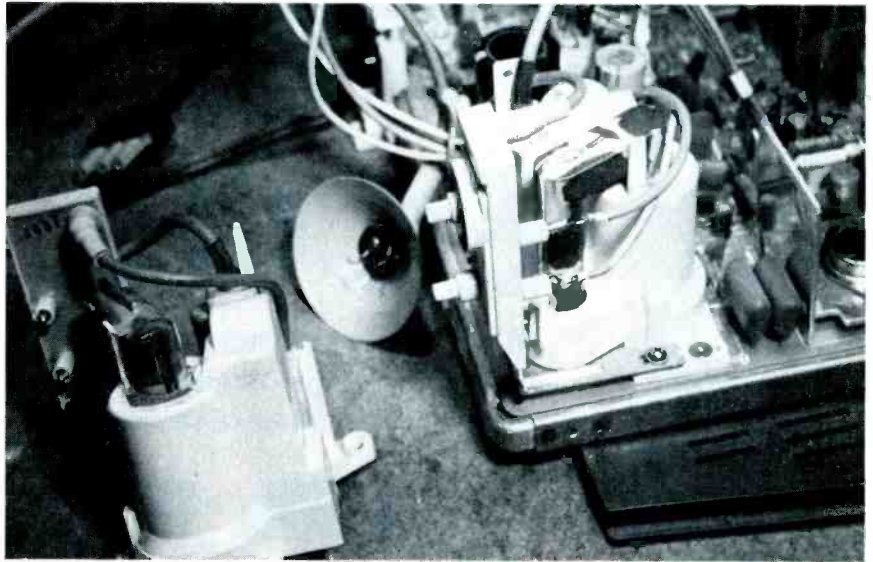


Figure 6. The new T602 flyback is shown mounted on the Sharp chassis, while the old flyback is at the left. Use only original-type replacements.

before the power can be turned off. If you are willing to take that chance, and the receiver has sound and soon shows a picture, quickly test for +120V at the collector (case) of Q602 and then measure the high voltage. In case both voltages are normal, the problem evidently is a defect in the shut-down circuitry. Measure all shut-down components, particularly D651 and zener ZD651.

A safer method for proving whether or not shut-down is occurring and if it is from excessive high voltage is to operate the chassis from a variable-voltage 60Hz transformer. Start with about 50Vac and slowly increase the voltage until picture and sound are obtained. Again, slowly increase the ac voltage and notice if shut-down occurs (and at what line voltage). A normal receiver should withstand up to almost 130V before the shut-down activates. Shut-down at 90V to 100V hints at excessive +120V regulated supply, while shut-down at 100V to 110V might be caused by an open capacitor such as C615 and C620 in Figure 4.

When the +120V supply voltage cannot be adjusted by R107 to the correct voltage, R107 might be defective. With power off, rotate it

and check the resistance.

No sound, no horizontal sweep

When the receiver is completely dead, check the Q602 collector voltage. A reading of less than +70V hints at a defective bridge-rectified +164V supply, while a +76V or +78V reading indicates the horizontal sweep is not operating (the low voltage is caused by the lack of horizontal pulses at the SCR701 anode).

An open Q602 output transistor with an ohmmeter can have complications because of the internal damper diode. First, a voltage-drop diode tester or a high-power ohmmeter should be used to check the transistor out-of-circuit.

When the horizontal-output transistor does not have an internal damper diode, the resistance reading between collector and emitter should be high, regardless of probe polarity. But the damper diode in Q602 should give a typical silicon diode reading when the positive probe touches the emitter and the negative ohmmeter probe touches the collector. With the probes reversed, the reading should be in the megohms. Lower readings should arouse suspicions about the transistor.

The base/emitter and base/col-


FOUR GREAT REASONS TO USE N.A.P. FACTORY REBUILT MODULES.

1. ONLY N.A.P. rebuilt modules are always updated by our engineers to incorporate the most recent factory modifications.
2. ONLY N.A.P. guarantees genuine, factory approved replacement parts—pre-tested to exacting quality control standards before installation in modules.
3. ONLY N.A.P. provides modules tested to demanding factory quality assurance standards.
4. ONLY N.A.P. guarantees rebuilt modules that perform to rigid factory specifications. Our One-Year Warranty proves it.

Product Services Organization
P.O. Box 555, Dept. 741
Jefferson City, TN 37760
1-615-475-3801, Ext. 7348



**PRODUCT
SERVICES
ORGANIZATION**

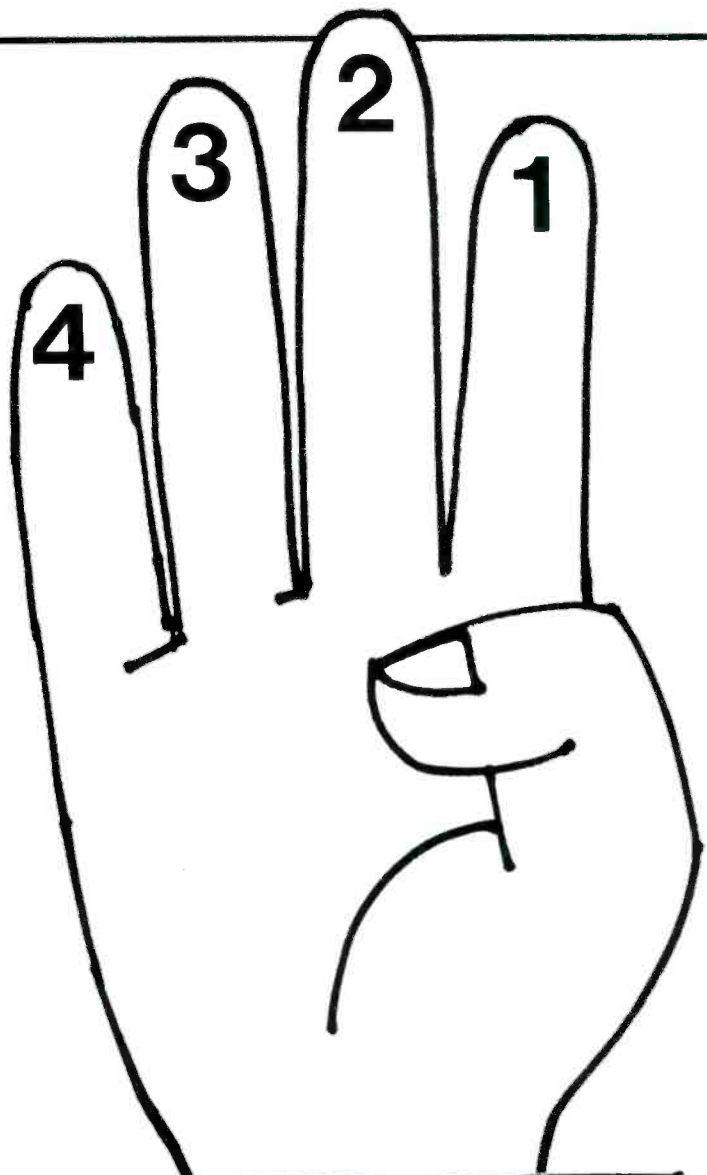

**MAGNAVOX
ODYSSEY
PHILCO
SYLVANIA**
AUDIO • VIDEO

A North American Philips Company

Circle (11) on Reply Card

November 1983 *Electronic Servicing & Technology* 19

lector junctions should be checked with both polarities in the same way. Forward-biased junctions should show typical resistances for the meter used, while reverse-bias polarity should produce resistance readings approaching infinity.

If Q602 tests normal, but the horizontal sweep is dead, check all significant dc voltages followed by scope analysis of any or all waveforms in the horizontal system. These measurements and some logical thinking locate the problem area.

Check all connections of the T602 flyback transformer on the circuit board's bottom side. Poor connections, particularly pins 1 and 11 for the SCR pulses, have been found there. Flybacks may require replacement (Figure 6).

Motorboating

When the +120V regulated supply voltage varies significantly at a slow rate, causing a motorboating sound in the speaker and a synchronized slow variation of picture width, replace resistor R615, the Q602 emitter-to-ground resistor (Figure 4). R615 is likely to need replacement after Q602 has shorted and been replaced. Use a 0.27Ω, 1W replacement for R615.

Vertical-sweep problems

Transistors for the vertical oscillator are inside I501. These are followed by a driver transistor and two NPN power transistors that supply vertical power to the yoke. It is important to note that the driver transistor is external to the IC in Sharp models (Figure 7A), while the transistor is inside the IC in similar models manufactured by Sharp for Montgomery Ward and K-Mart (Figure 7B). Pin numbers for the vertical-hold control and drive-signal output are different for the two versions, as shown.

Scope waveforms can prove the presence or absence of signal from I501 on to the yoke, and this is valuable. However, defects often distort the waveforms, making analysis difficult. Lack of a drive waveform at the proper pin (accor-

ding to the circuit variations) might indicate a defective I501. Before removing the IC, measure the supply voltages at the input to R502 (at the vertical-hold control; +12.13V expected) and at I501 pin 15 (expect +9.82V). If these two voltages are within tolerance and there is low dc voltage and signal level at the output pin (pin 2 or 7), I501 should be replaced.

Output transistors Q502 and Q503 have been known to cause intermittent height when they open erratically. These intermittent transistors cannot always be found by in-circuit or out-of-circuit tests. Therefore, if they are suspected, replace both of them at the same time. Use the exact replacement, or use ECG373 universal transistors (Figure 8).

Erratic height also can be caused

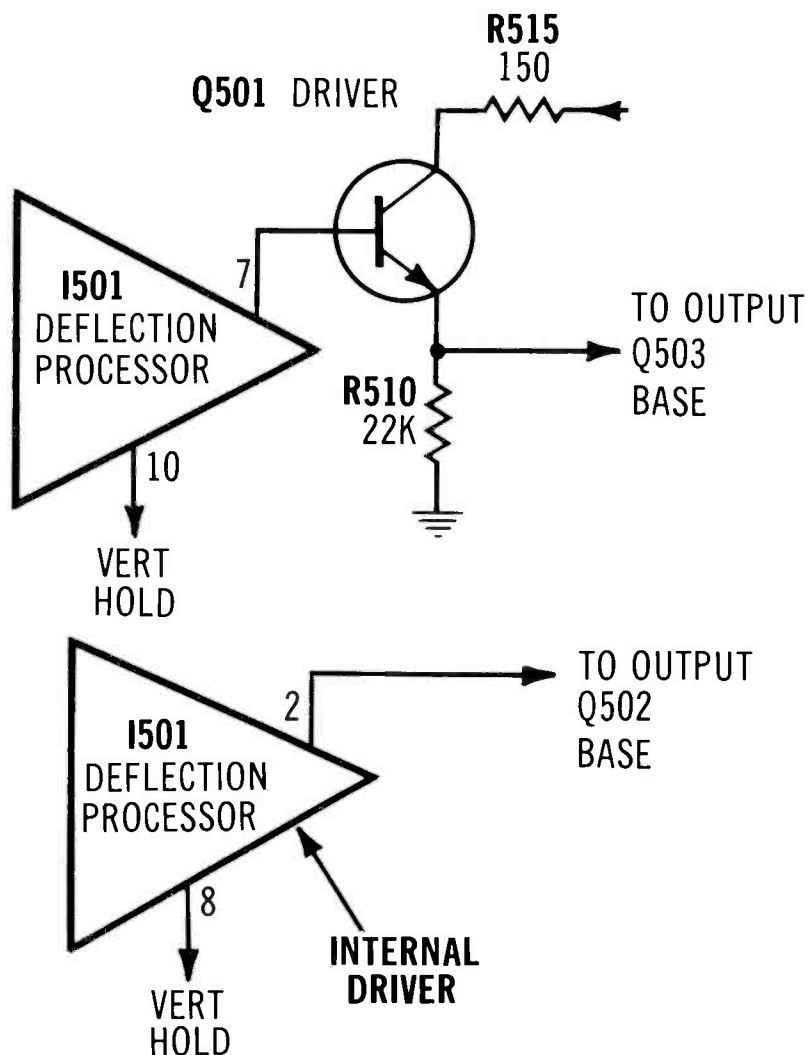


Figure 7. (A) In Sharp chassis, the vertical driver transistor (Q501) is external to I501, while Montgomery Ward and K-Mart color receivers made by Sharp (B) include the driver transistor inside I501. Notice the different pin numbers.

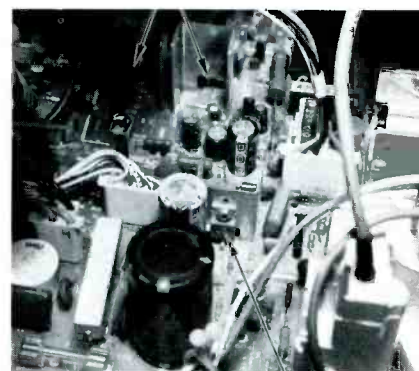


Figure 8. (Arrows at the top point to vertical-output transistors Q502 and Q503. At the bottom, an arrow points to SCR701 on its heat sink.)


by corrosion on the vertical hold-control element. Spray the inside with tuner cleaner and rotate the control several times. If this reduces the erratic action, you should replace the control.

OMNITRON CHRISTMAS SPECIALS

USE * NUMBERS FOR SPECIALS

Silicon H.V. Triplers HIGH VOLTAGE MULTIPLIERS

Minimum 3/may asst.

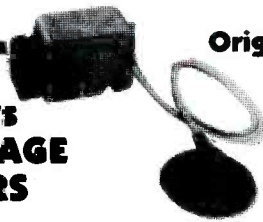

Original ECG SYLVANIA Triplers

ECG-500A ECG-523 ECG-526A

212-139	212-141	212-141-02
212-139-01	212-141-01	212-141-03
212-139-02	212-141-01	212-141-04
#ETD-20	#ETD-21	#ETD-22
\$10.99	\$10.99	\$10.99

SANYO

TOSHIBA



2SC1308K
#ETD-5B

2SC1172B
#ETD-5C

\$1.49 /50 up
\$1.69 10-49

Cordless Telephone

X-18 **\$99.95**

X-19 **\$79.95**
less intercom



- Range 600 ft. with 2-way intercom
- Both receive and send calls from remote location
- High-Low rechargeable battery indicator

Econ-O-Phone

\$129.95



- X-20
- Economical desk or wall phone—2 in 1!
- Last number redial
- Mute Switch
- Works with push button and rotary systems

Jerrold 60 Channel Cordless Cable TV Converter

reg. \$189.95
\$89.95
MODEL DRX3-105



X-2100

BK PRECISION 3 1/2 Digit DMM

\$63.75

Reg. \$75.00
Model 2806

X-25

- 0.7% DCV accuracy
- 500 hours continuous battery life
- Auto-ranging/manual ranging in Volt and Ohm scales
- 10 A AC and DC ranges
- 3 1/2 digit LCD display with annunciators
- Single rotary switch operation
- Low battery indicator
- Diode check
- Audible continuity check
- Transient and overload protected
- High energy fuse
- Ruggedized case with safety designed test lead system
- Complete with test leads, batteries, spare fuse, and instruction manual

NEW!



BK PRECISION 3 1/2 Digit DMM

\$97.75

Reg. \$115.00
Model 2807

X-26

- 0.5% DCV accuracy
- 500 hours continuous battery life
- Auto-ranging/manual ranging on Volt and Ohm scales
- 10 A AC and DC ranges
- Convenient single rotary switch function/range selector
- 3 1/2 digit LCD display with annunciators
- Low battery indicator
- Diode check
- Audible continuity check
- Transient and overload protected
- High energy fuse
- Ruggedized case with safety designed test lead system
- Complete with test leads, batteries, spare fuse, and instruction manual

NEW!



Beckman DMM

\$59.95

Model DM-15

NEW!

- 10 amps
- 24 ranges
- 0.8% basic Vdc Accuracy
- Separate diode Test Function

X-30




10 MHz Dual Trace Scope

\$435.00 BK PRECISION

Reg. \$545.00
Model 1476A

- dual trace
- 10mV/div sensitivity
- video sync separators
- includes probes

X-28

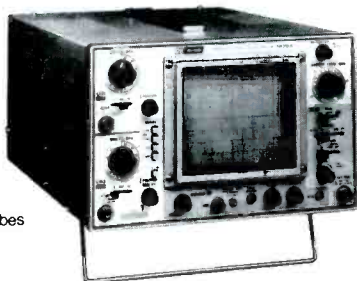

30 MHz Dual Trace Scope

\$635.00 BK PRECISION

Reg. \$795.00
Model 1479B

- dual trace
- 5mV/div sensitivity
- 10:1 reference/direct probes included

X-29




X-22

Weller/Xcelite Tool Kit

\$329.95

Reg. \$499.95
Model TC-100/ST

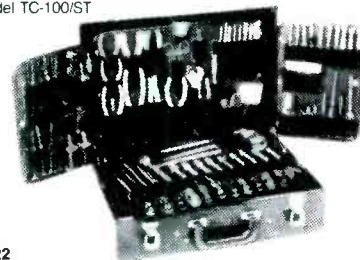

Send Purchase Order. Check, Money Order or C.O.D.

or Call Toll Free
800-223-0826

in N.Y. State (212) 865-5580

SHIPPING CHARGES

For Orders	ADD
\$25-100	\$6.50
\$100 - \$500	\$8.50
\$500 - \$750	\$10.50
\$750 - and up	\$15.00

MASTER CARD • VISA

Write for FREE 112 page Catalog

OMNITRON

ELECTRONICS

770 Amsterdam Ave., NY 10025

Circle (12) on Reply Card

November 1983 Electronic Servicing & Technology 21

Books

Editor's note: Periodically *Electronic Servicing & Technology* features books dealing with subjects of interest to our readers. Please direct inquiries and orders to the publishers at the address given for each book, rather than to us.

Electronic Miniatures – A Buyer's Guide, by S.E. Harris; Tab Books; 304 pages; \$17.95 hardbound, \$12.95 paperback.

This guide book tells what is on the market in miniature electronic gadgetry—cameras and tape recorders, electronic games, medical devices, computers, radios, televisions and more. The book covers the evolution of electronic miniatures, microelectronics, repair of microelectronic circuits, miniature television circuits, cassette recorders, miniature entertainment systems, miniature broadcast receivers, calculators, pocket computers, clocks and watches, microprocessors and assorted miniature gadgets.

Also included are electronic drill presses, personal smoke alarms, blood pressure/pulse monitors, radar detectors and a sports forecasting kit.

Published by Tab Books, Blue Ridge Summit, PA 17214.

Fundamentals of Stereo Servicing, by Joel Goldberg; Prentice Hall, Inc.; 299 pages; \$22.95.

This working handbook covers stereo repair and troubleshooting techniques and includes block diagrams, schematics and in-depth circuit coverage. Guidelines are given for complete professional servicing of transformers, rectifier systems, bridge output systems, low-level amplifiers, AM and FM tuners, matrix decoders, switching decoders, cassette systems, cartridge systems, reel-to-reel systems, and discrete and IC circuits. The handbook gives professional safety precautions, step-by-

The regulator circuit uses the principle pioneered by RCA: Power from the +164V supply is released to C708 in timed bursts, with one pulse of dc current during each horizontal cycle. This is a practical example of *time constant* at work. C708 integrates the dc pulses. Heavier loads on the C708 filter require the dc pulses to be widened. The I701 circuit determines from the C708 voltage when during each horizontal cycle the SCR conduction should begin, and a positive pulse is applied to the SCR gate at that time.

Once started, the current conduction continues until the negative-going flyback pulses at the SCR anode become negative relative to the dc voltage at the SCR cathode. Conduction ceases at the same point during

each horizontal cycle. *Rectification of the anode pulses adds voltage to the +120V regulated supply.* Notice that the horizontal driver and output transistors are powered directly from the +120V supply, so they are ready when the oscillator begins operation. During start-up, however, the oscillator receives a lower voltage from R611, thus forcing the sweep system to operate weakly. After start-up is finished and the sweep is operating at full power, the oscillator dc supply voltage comes through D452 and R454 from the +18V supply. Notice that all dc sources (except four operating from +120V) are generated by rectification of horizontal power. Therefore, these supplies will be dead when the horizontal sweep is dead.

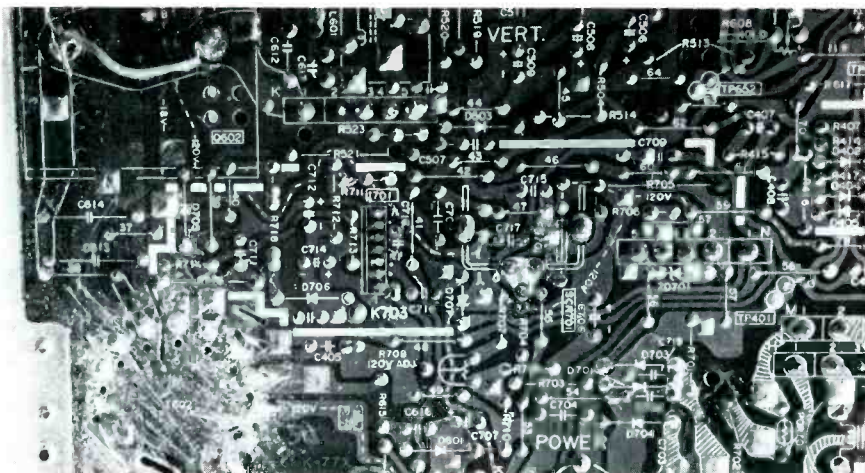


Figure 9. Locations of many components are printed on the bottom of the circuit board, and wider lines show the general areas for power, vertical and other systems.

One of the first tests when the height is insufficient involves measuring the dc voltages at the two vertical output power transistors. If these voltages are low, check 1K Ω R513 (brings +48.7V supply to R512 and C504) and 56 Ω R516 that brings supply voltage to the Q502 collector. When yoke-coupling 470 μ F C507 is partially open, there will be no height.

Of course, defects in the supply voltages can produce height problems. Loss of +48.7V supply

(Figure 1) might be caused by a leaky D503 that has burned open 22 Ω R520. Replace both if D503 is defective. Also, remember D503 must be suitable for operation at 15,734.4Hz horizontal frequency. Do not use a 60Hz top-hat type.

The location of many circuit-board components are marked on the board's bottom (Figure 9). In addition, wide lines show limits of the principal areas, such as vertical and power.

ES&T

step troubleshooting methods and how-tos for using test equipment.

The book shows how to identify input and output connections for each type of amplifier circuit, anticipate the approximate size and shape of input and output waveforms, pinpoint how input and output transducers help to produce a signal voltage and determine which type of tuner develops the audio signal from the modulated RF signal being transmitted.

Published by Prentice-Hall, Inc., Englewood Cliffs, NJ 07632.

The Video Guide, by Charles Bensinger; Howard W. Sams & Company; 255 pages; \$18.95.

This survey of current video equipment, trends, techniques and programs provides the reader with a general overview of the video industry today. Topics include cameras, VTRs, videotape monitors, projectors, videocassette systems, the video portapak, ENG systems, maintenance, troubleshooting and purchasing equipment.

Published by Howard W. Sams & Company, 4300 W. 62nd St., Indianapolis, IN 46268.

Concepts of Digital Electronics, by Harry M. Hawkins; Tab Books; 196 pages; \$17.95 hardbound, \$11.95 paperback.

This book shows how anyone can understand and use low-cost 7400 series integrated circuits to produce working digital devices including a power supply and a breadboard experimenter. Written in an easy-to-follow-and-understand style, the book shows how clocks, flip-flops, shift registers, logic gates and other digital devices function and explains how to use them in a variety of practical applications.

Several digital electronics concepts are introduced including the different number systems – binary, decimal, octal and hexadecimal. BCD, Baudot and ASCII codes and fundamental digital operations including AND, NAND, OR, NOR and Exclusive OR are covered. The author has included hands-on information on the basic principles of digital electronics experimentation and how-tos for troubleshooting digital circuits.

Published by Tab Books, Blue Ridge Summit, PA 17214.

Meet the New Low-Cost Simpson 470™!



**Full-Function
3½ Digit
Hand-Held
DMM**



**High-Impact
Molded Case—**
Choice of two-tone
Brown or two-tone Gray

Complete with battery,
test leads and manual



- Professional-Grade Design and Construction
- Full Measurement Capability — 100 μ V to 1000 V DC, 100 μ V to 750 V AC, 0.1 Ω to 19.99 M Ω up to 10 A AC/DC Current
- 0.15% DC V Accuracy
- 0.5" High-Contrast LCD Display
- Low Battery Indication
- UL Recognized Test Leads
- Wide Temperature/Humidity Operating Range
- Audible Tone and Diode Test
- Transient Protection and Double Fusing
- Tilt Stand and Anti-Skid Pads
- Convenient Thumbwheel Range and Function Knobs
- One-Year Battery Life (average use)
- Full Line of Optional Accessories

AVAILABLE NOW AT LEADING ELECTRICAL/ELECTRONICS DISTRIBUTORS WORLDWIDE



SIMPSON ELECTRIC COMPANY
A Katy Industries, Inc. Subsidiary
853 Dundee Avenue, Elgin, IL 60120
(312) 697-2260 • Telex 72-2416

Circle (37) on Reply Card

Learning about electronics

By Conrad Persson, editor

The rapid pace of the electronics "revolution" has been much celebrated in the press, on television and in general conversation. Its effect on the lives of all of us has been profound. To many it means improved communications, expanded entertainment choices or electronic help in calculating and computing. To others it means a threat of unemployment as computers and robots perform more and more routine tasks.

To yet others, servicing technicians and electronic enthusiasts for example, it means still more to learn about electronic theory, practical applications of electronics and servicing, and repair of electronic products. Whether learning about this new electronic technology is an intellectual challenge or a drudge depends upon an individual's attitude, and of course whether or not he simply wishes to study or if he is obliged to study. Whatever the case, there is plenty of new material to study in electronics with more generated every day.

Several avenues

There are two pivotal decisions to be made when you're deciding about further education: What, precisely, do you need to learn and how will you learn it?

It's important to do a thorough analysis of exactly what it is you want to learn. I occasionally hear someone say, "I want to learn about computers," or something equally vague. The question that needs to be answered is, "What do you want to learn about computers?" The answer might be something like, "I want to take an introductory course in computers so I can understand the jargon and know how hardware and software interrelate, so that I can know what further courses to take to

learn servicing." That doesn't pin it down completely, but it does state some specific goals.

Once the specific goals are set, the next consideration becomes how to achieve them. One simple but effective method might be to contact other technicians in your area. If you have a skill that they lack and vice-versa, why not arrange for a session in which you educate each other.

Self study

Another simple but less effective method is to buy a book on the subject and study it yourself. Depending upon a number of factors, including the complexity of the subject, the quality of the book, and your own self discipline, this experience might bring anything from complete understanding to fruitlessness. Home-study courses offer a major improvement over studying from books. The material is broken down into study units, someone tells you what is expected of you, and you get feedback through regular tests.

Schools and seminars

If time and money permit, a more effective way to learn is through structured class and lab courses. Here again there are many avenues. Public and private technical schools throughout the country offer a selection of courses from the most elementary introductory courses to detailed theory and design. If you have the time and the budget to travel, manufacturers of home electronic equipment offer to servicing technicians seminars on the operation and servicing of specific items.

Identifying the available resources

A local school may have just the course you need listed in its catalog. One of the book publishers

might have just the book or series of books to fill in the gaps in your knowledge. One of the associations related to home electronics equipment manufacturing sales or service may have just the item of information you need or be able to point you in the right direction.

The following text lists a number of correspondence schools, book publishers and associations whom you might want to contact for further information on what educational opportunities they have to offer.

Trade associations

Electronic Industries Association (EIA)
Consumer Electronics Group
2001 Eye St., N.W.
Washington, DC
202-457-4919

Electronic Representatives Association (ERA)
20 East Huron Street
Chicago, IL 60611
312-649-1333


Electronic Technicians Association (ETA)
RR3, Box 564
Greencastle, IN 46135

National Association of Television & Electronic Servicers of America (NATESA)
5930 S. Pulaski Road
Chicago, IL 60629
312-582-6350

National Association of Retail Dealers of America (NARDA)
2 North Riverside Plaza
Chicago, IL 60606
312-454-0944

National Association of Recording Merchandisers (NARM)
1060 Kings Highway North
Suite 200
Cherry Hill, NJ 08034
609-795-5555

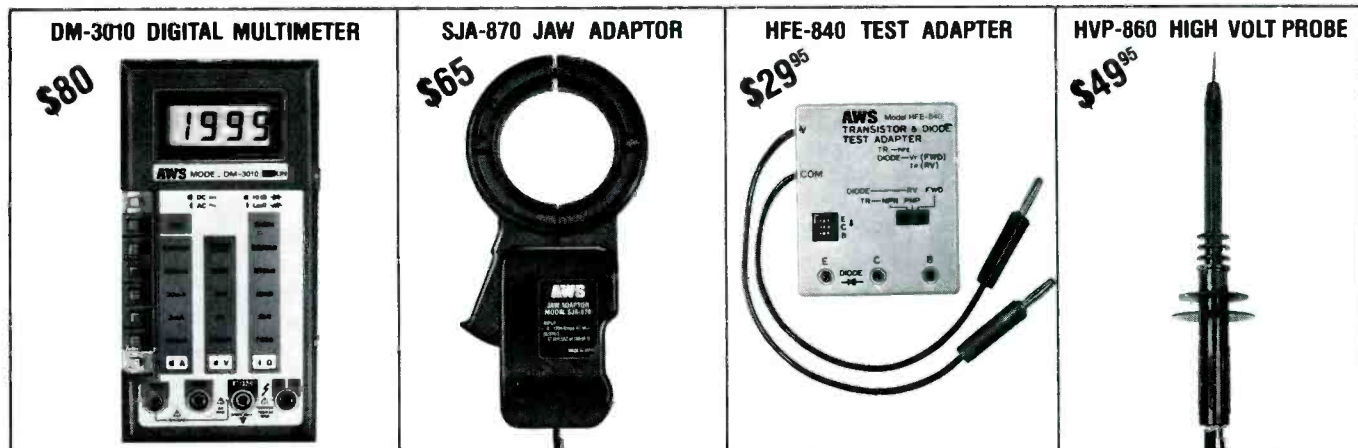The new AWS DM-3010. It's not just another DMM. It's a complete electrical/electronic testing system.



Today's electrical and electronic testing requirements call for equipment that can handle a wide range of applications. That's why now more than ever you need the new AWS DM-3010 Testing System.

To start off with, the **DM-3010 Digital Multimeter** has an unbelievable \$80 price tag. It offers 34 ranges with push-button control plus features usually found in much more expensive models such as: 10 Amp AC/DC range; UL1244 type test leads; overload protection on all ranges; Hi and Low power ohms in all resistance ranges and more.

Complete the system by simply adding the following accessories as you need them...

SJA-870 Snap-Around Jaw Adaptor. Reads 0-1200 Amps AC. Its large jaws fit easily around any conductor up to 2-15/16" in diameter.

HFE-840 Test Adapter. If your work requires transistor and diode testing, this pocket-size adapter is a must.

HVP-860 High Voltage Probe. Provides safe, easy and reliable readings of 0-50KVDC on low power high impedance circuits.

So compare the DM-3010 Testing System for yourself. You'll find that no other company offers a comparable system at these low prices.

For more information on the AWS DM-3010 Testing System, see your local distributor today or contact A.W. Sperry Instruments Inc., P.O. Box 9300, Smithtown, N.Y. 11787. Call Toll-Free 800-645-5398 (N.Y., Hawaii, Alaska call collect 516-231-7050).

A.W. SPERRY INSTRUMENTS INC.

Circle (13) on Reply Card

National Electronic Distributors Association (NEDA)
1420 Renaissance Drive
Park Ridge, IL 60068
312-298-9747

National Electronic Service Dealers Association (NESDA)
2708 W. Berry St.
Ft. Worth, Texas 76109
817-921-9061

Recording Industry Association of America, Inc. (RIAA)
888 Seventh Ave.
New York, NY 10106
212-765-4330

Technical book publishers
Hayden Book Company
Rochelle Park, NJ 07662

McGraw-Hill Book Company
1221 Avenue of the Americas
New York, NY 10020

Prentice-Hall
Englewood Cliffs, NJ 07632

Howard W. Sams & Company
4300 W. 62nd St.
P.O. Box 558
Indianapolis, IN 46206

Tab Books
Blue Ridge Summit, PA 17214

Van Nostrand Reinhold Company
135 W. 50th St.
New York, NY 10020

Home study
Cleveland Institute of Electronics
1776 E. 17th St.
Cleveland, OH 44114

Cook's Institute of Electronics Engineering
Desk 15
P.O. Box 20345
Jackson, MS 39209

Electronic Institute of Brooklyn
4823 Avenue N
Brooklyn, NY 11234

Grantham College of Engineering
2500 S. La Cienega Blvd.
Los Angeles, CA 90034

Heath Company
Benton Harbor, MI 49022

National Institute of Technology
1701 W. Eules Blvd.
Eules, TX 76039


National Technical Schools
456 W. Santa Barbara Ave.
Los Angeles, CA 90037

NRI Training for Professionals
McGraw-Hill Continuing Education Center
3939 Wisconsin Ave.
Washington, DC 20016

Trade schools
National Association of Trade and Technical Schools
2021 K Street, N.W.
Washington, DC 20006

ES&T

INTRODUCING

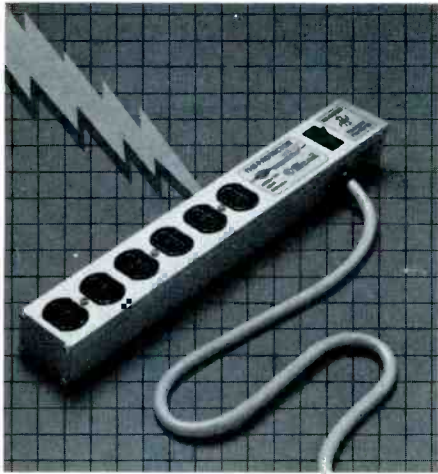

THE PROTECTOR 6000™

TOTAL PROTECTION FOR YOUR SENSITIVE ELECTRONIC EQUIPMENT.

Something that you can't even see may be slowly but surely killing your expensive electronic equipment. It's transient voltage, and it can be fatal to computers, medical equipment, electronic games, videotape recorders, electronic test equipment, electronic cash registers — almost any of today's sophisticated solid state equipment.

THE TRANSIENT VOLTAGE PROBLEM.

Most of this modern electronic equipment uses LSI and MOS semiconductor devices which are extremely sensitive to voltage transient surges or "glitches." In fact, a large percentage of equipment failures can be directly linked to the damaging effects of over-voltage line transients to unprotected, highly fragile components.

THE PROTECTOR 6000™ SOLUTION.

Not to be confused with other transient voltage protection units available today, THE PROTECTOR 6000 uses state-of-the-art solid state components and exclusive circuitry to provide you with complete and total protection from transient voltage surges of up to 6,000 volts. THE PROTECTOR 6000 uses silicon PN junction devices — proven to provide the fastest response to surges! They have a statistical life expectancy of over 20 years. THE PROTECTOR 6000 has a maximum clamping voltage of only 335 volts, well below the voltage rating of other transient protection devices which commonly use much less effective MOV's or gas discharge tubes. It also provides full protection from electro-magnetic and radio frequency interference. The unit operates in both common and differential modes, and is outfitted with a circuit breaker to guard against severe current overloads over 15 amps.

Why take chances with your expensive electronic equipment? For full details contact your local NTE distributor or write:



NEW-TONE ELECTRONICS, INC.

44 Farrand St., Bloomfield, NJ 07003

THE PEOPLE WHO BRING YOU THE TCG LINE OF SEMICONDUCTORS.

© 1983 New-Tone Electronics, Inc.



Leakage testing

In response to the letter in June 1983 Feedback, I would like to add one item. Our shop does many repairs on line-operated musician's equipment. It is common to find some sort of capacitor from 0.05 to 0.3 μ F from one side of the line to the chassis, with both 2- and 3-wire line plugs right from the factory. The 2-wire types are common in older units, and you may find a switch to allow the hot side of the capacitor to be to either line side. The result is that:

- To properly measure leakage, you must be sure that if a third (neutral) is used it is operational.
- You will probably have to check both (or all 3) switch positions, and you may have to repeat this with the line cord in the case of a 2-conductor plug.
- A value of 0.05 μ F allows about 2mA of ac 60Hz to flow, far in excess of the typically allowed 0.5mA of ac. Therefore, the older units may not pass today's leakage test, and no leakage specs exist on them anyway.

I highly recommend that any shop that sees a piece of line-operated musician's equipment not let one out of the shop without asking the customer about installing a 3-wire line and plug. Musicians are used to receiving shocks from equipment, but the liability situation is questionable. I make them sign a waiver. And no, you cannot remove the capacitor, because the musician may complain he cannot get rid of the "hum" problem.

R. Fleischer
South Lake Tahoe, CA

Capacitor cautions

I have just read Mr. Honey's article on capacitors ("Special Capacitors for Television, May 1983 ES&T) and did enjoy his knowledge of them, and found the article interesting and informative. I found myself driven to

write to you about a serious bit of advice that he gives concerning the 4-legged capacitor used in many horizontal output stages.

He says "I prefer the separate capacitors instead of one large one for retrace use...I do not normally replace the 22-5001 capacitors (Zenith part number) capacitors with a 4-legged one...I replace the original part, usually with a better quality replacement...The reasons I prefer separate capacitors are simple. First, one large capacitor (4-legged or not) holds more heat internally and can accelerate failure."

While he is basically correct in his assumptions, his advice is totally incorrect and could bring lawsuits to anyone following it. The federal government has mandated that parts within critical areas are not to be modified in any way. Replacement of the 4-legged capacitor with several single capacitors is definitely modifying the circuit and makes you responsible for what you have done.

His knowledge of the circuit or his encouraged modification of it is wrong because of the legality of it — not the performance of the circuit. I do agree with his circuit logic but know your magazine or any other cannot support the advice he has given.

George Savage, CET
Doniphan, NE

Honey's reply

I believe Mr. Savage has misinterpreted my article, or perhaps I didn't express my thoughts clearly.

At no time have I advocated modifying "critical areas" with substandard parts. I also never implied that I replaced the 4-legged capacitor with several single capacitors, even though such a mod would be safer and more reliable.

I did suggest that "better than original parts be used" and that even when the manufacturer supplied a mod kit consisting of a 4-legged capacitor, I didn't use it. A circuit can be "redesigned" or repaired in any way I see fit, as long as safety factors are maintained or improved.

The replacement parts I suggested in all cases were better than the original. The whole point

of the article was to supply enough information so that anyone could determine what type of capacitor would make an adequate replacement.

No law exists that says that "only the manufacturers original parts or part numbers must be used in repairing television sets." Anything can be used as long as it is equal to or better than the original OEM part.

Incidentally, a good way to test the 22-5001 Zenith capacitors to see if one or more are open, is to cut one loose while monitoring the high voltage (be sure set is off while cutting). If no voltage change is apparent when the set is turned on again, the capacitor is open. If the voltage changes 1 to 2kV, the capacitor was probably good. Replace the lead and continue. In this way, the bad ones can be weeded out a little faster if proper test equipment is not available.

C. A. Honey
Ontario, CA



Want MORE Information on Advertised Products?

Just refer to the Bingo # beneath each ad. Circle the appropriate number on the Reader Service Card in the back of this issue. Complete the remaining information and mail!



One source for thousands of VCR parts.

RCA VCR parts are available from more than 600 authorized RCA parts distributors. See your local RCA distributor for RCA's new VCR parts kits — they're easy to use and reuse. Each package has a handy slide top — and features detailed cross-references to other manufacturers' model numbers and stock numbers.

One more thing. Kit prices are lower than the total cost of the individual parts. So see your RCA distributor today. Also ask for a copy of the VCR Parts Cross Reference of more than 8000 VCR parts (Form 1F6627) and VCR Tool Catalog (Form 1F6857). Or write: RCA Distributor and Special Products Division, 2000 Clements Bridge Road, Deptford, NJ 08096.

Service more than 95 RCA and other brand models with these VCR Parts Kits:

199094 and 199095 Belt Kits, 199096 Lamp Kit, 199097 Fuse Kit, 199300 IC Kit

RCA VCR Parts

SOLTEC® OSCILLOSCOPES


Model No.	Description	Price
5100	100 MHz, Quad Trace, Portable	\$1,995.00
560	60 MHz, Triple-Trace, Portable	1,695.00
540P	40 MHz, Triple-Trace, Portable	1,295.00
540D	40 MHz, Triple-Trace, Desk Top	1,295.00
540M	40 MHz, Triple-Trace with Built-in DMM, Portable	1,995.00
540C	40 MHz, Triple-Trace with Built-in Counter/Timer, Portable	1,995.00
530	30 MHz, Dual-Trace, Portable	895.00
520	20 MHz, Dual-Trace, Portable	695.00
515-2	15 MHz, Dual-Trace, Portable	595.00
515-1	15 MHz, Single-Trace, Portable	495.00
512-2	12 MHz, Dual-Trace, Portable	545.00
512-1	12 MHz, Single-Trace, Portable	445.00

CALL NOW

for the name of the distributor in your area and a color catalog with full details TOLL FREE

800 - 423-2344

MODEL 5100

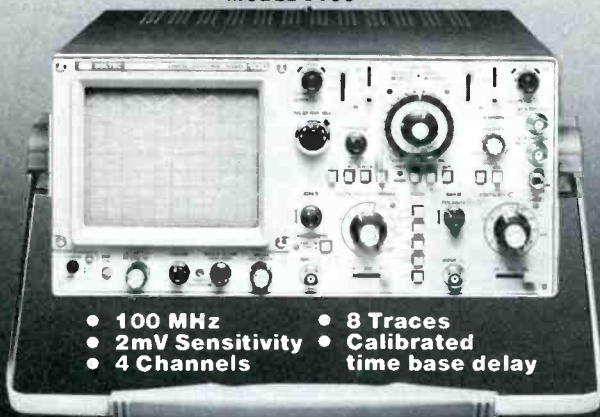

- 100 MHz
- 2mV Sensitivity
- 4 Channels
- 8 Traces
- Calibrated time base delay

No other manufacturer offers comparable quality, design features and proven performance in a 100 MHz Scope at this price. Let us prove it to you!

Two Probes Included

NOW 100 MHz
\$1,995.00!

- 1500 hrs. MTBF
- Glass epoxy circuit boards
- 2 year warranty on all parts and labor

**SOLTEC®
CORPORATION**

11684 Pendleton Street
Sun Valley, California 91352
213 - 767-0044

Circle (14) on Reply Card

Troubleshooting Tips


No sound and no picture Sony KV-1711 chassis SCC-63A (Photofact 1503-1 or 1625-2)

A customer who brought the Sony TV receiver to me explained that another shop had given up trying to repair it after six weeks. They had installed several F602 4A line fuses, an unidentified electrolytic capacitor and the D517 damper diode.

Usually, I carefully check all previous repairs, because mistakes often kept the previous technician from completing the repair. Unfortunately, I forgot to check this time.

A resistance check of the regulated +130V supply showed a 26Ω short to ground, which is sufficient to blow the line fuse. Rapid in-circuit tests of the bridge rectifiers and all transistors on the power-supply board did not locate any defects. I disconnected the wires from the audio-output and the horizontal-sweep circuits, and the short was gone from the +130V supply. Additional tests proved the short was in the horizontal circuit, so I reconnected the audio wire, leaving the horizontal wire disconnected. When 120V power was applied, the fuse did not blow, but R617 in the power supply began smoking from overload. I put aside the R617 question until later.

I tested all horizontal diodes and transistors by the voltage-drop function of my DMM, but none appeared to be bad. I tested the yoke, flyback and other components by resistance measurements, but found no defects. The 26Ω short remained as I unsoldered each flyback pin in turn until pin 10 of T501 was disconnected, eliminating the short. The +130V for the Q510 horizontal-output devices comes through R904 (10Ω) to pin 10. Next, I noticed a

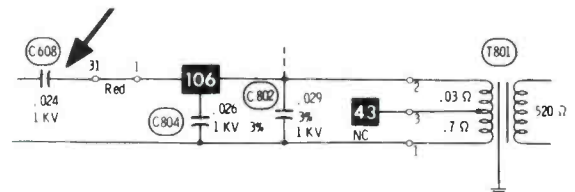

jumper on the yoke plug that (when the plug is removed) opens the circuit between Q510 and T801, the high-voltage transformer. By opening the jumper, I proved the short was on the T801 leg of the wiring. The wire went back to the power-supply board, which held L601, L602 and C608. I was relieved to measure a 14Ω short in C608 (0.024μF 1000V) that coupled sweep power to the T801 primary. The primary low end is connected to the cathode of Q510 which is grounded through a 1.8Ω resistor. Therefore, C608 was responsible for the overloaded +130V supply.

After I replaced C608 and restored all connections, the short was gone, so I switched on the 120V

power; F602 blew instantly. Then I remembered the D517 damper diode had been replaced by the previous technician. The soldering of D517 appeared to be satisfactory. I decided to re-install the old damper diode, because it tested fine externally and not all replacement parts will operate correctly in Sony machines. After one end of the new damper was unsoldered, I noticed the polarity was reversed. Of course, this connected its anode to the B+ through the flyback, producing a short when the voltage was higher than 0.7V. I re-installed the old damper diode.

When the receiver power was applied next time, the sound had a loud hum and the picture showed two wide black bars. I installed a new R617 (which I had forgotten to do earlier) and measured +158V at the +130V regulated supply. Junction tests of all regulator transistors revealed Q601 had an open base-to-collector junction and Q602 was shorted between emitter and collector. After these transistors were replaced and the regulated voltage adjusted for +130V, the receiver operated normally.

This case illustrates some of the complications from two separate defects, and the dangers of not checking all previous repairs for mistakes.

Phillip M. Jones
Martinsville, VA

Poor focus

Admiral 19C8248L

(Photofact 1766-1)

A blurred picture and lack of visible scanning lines indicated a problem with focusing. When I opened the receiver, I found that someone had butchered the focus-divider network, evidently in a misguided attempt at forcing the circuit to give better focus. I installed a new network, but this did not improve the focus. At CRT socket pin 9, the focusing voltage tested below 1kV, far below the expected 5kV.

High voltage at the CRT anode was satisfactory. A check of the focus control showed some roughness, so I installed a replacement component. Again, there was no improvement.


The focus voltage at the tripler measured about right. When I disconnected the wire to CRT-socket pin 9, the voltage at the wire jumped up to almost 5kV. This made me suspect that excessive picture-tube current was loading down the focus voltage. The CRT tested normal on a CRT tester.

I removed the socket from the CRT base and tested for leakage between pin 9 and all other socket pins. I found no leakage. I repeated all the previous tests and examined the schematic carefully, but without success.

Finally, I remembered that the only component not tested completely was the picture-tube socket. After I dismantled it, I noticed that the spark gap didn't look right, although it didn't test shorted. In desperation, I installed a new socket, and this cured the focus problem.

Although no arcing had been seen or heard, it was clear that the spark gap had been breaking down under the focus voltage. This is one lesson I will remember for a long time.

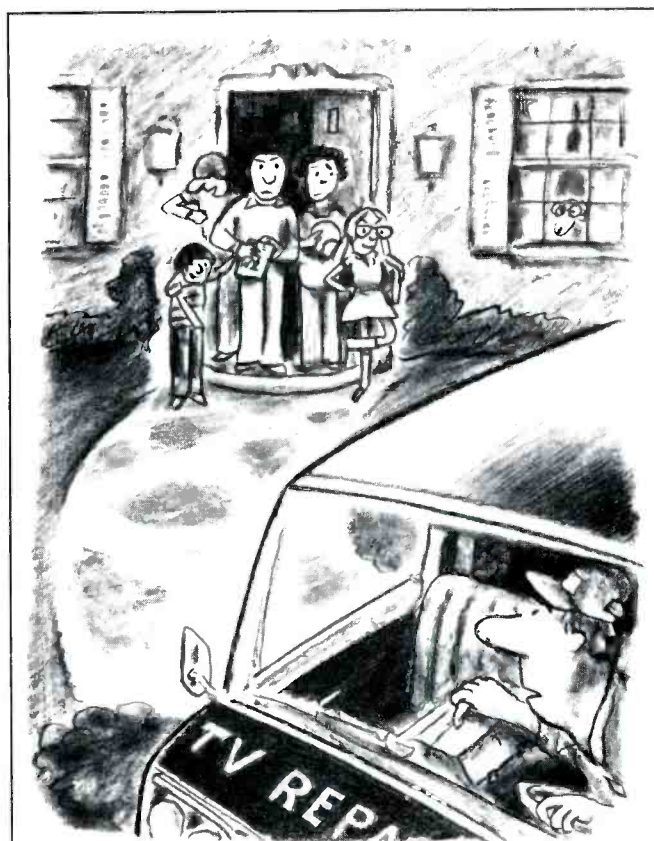Mike B. Danish
Aberdeen Proving Ground, MD



*"If it's not a GE, I think
I'll just stay in the truck."*

In this business, you never know what you'll run into. So it's always nice to run into a GE color TV, packed with its own Mini-Manual, including a schematic, parts list and troubleshooting guide. Since 1977 we've put a Mini-Manual inside every color set we make. Look for it every time that you're servicing a GE color TV. And use our toll-free numbers for parts orders and technical assistance. You'll have a good reception the next time your GE customer needs service.



We bring good things to life.

GENERAL  ELECTRIC

Readers' Exchange

For sale: Electronic Servicing, 1968-1980, \$50 plus shipping; Sams 38-700, \$400 plus shipping; B&K 1076 TV analyst, \$175. *Paul S. Funk, 607 E. Cherry Lane, Souderton, PA 18964; 215-723-2355.*

For sale: FM stereo pack, model CU-951UA with service manual, for Panasonic car radio, \$15. *Al Crispo, 3225 Chipmunk Drive, New Port Richey, FL 33552.*

Needed: IC for Philco television, #1C5/46-5002-5, or Motorola HEP6077P. *Wizard Electronics, Rt. 5, Box 522, Renick, WV 24966; 804-497-2066.*

Needed: Electronic Measurements Corporation (EMC) construction manual for model 801 comparator bridge and in-circuit capacity checker. Send photocopy or original COD. *Max Emerson, 1923 N. Texas, Weslaco, TX 78596; 512-969-3913.*

Needed: Service manual (in English) for NordMende Electronics (German) KM-394 distortion analyzer; working NordMende SRG-389 sine/square generator; parts/service manual for Sansui SD-7000 R-R tape deck (1971). *Steve Bender, Bengrun Research Labs, Box 23360, Queens Village, NY 11428; 212-776-2909.*

Needed: Simpson 498 field-strength meter, VHF-UHF tube type, and Hickok model 235A field-strength meter, VHF-UHF tube type. Batteries not needed; ok if inoperative. *Jim Shoemaker, 600 First St., Leechburg, PA 15656; 412-842-8321.*

Needed: High-voltage cup and socket for Panasonic color television, model CT-21P. State price. *George Saylor, 2319 Parrish St., Philadelphia, PA 19130.*

Needed: Service manual/schematic for model 1700, 115V, 60CPS, 21W Magnus organ. Will pay reasonable price. *Wilks Radio & Electric, 6056 Steubenville Road, SE, Amsterdam, OH 43003.*

Needed: Up-to-date tube layout charts for Mercury model 300 tube tester or address of company. *Earl P. Anderson, 1828 W. Jewell Ave., Milwaukee, WI 53221.*

Needed: Schematic diagram and power transformer for Marquette engine analyzer, model 40-175. *Ed Peterson, 751 Jakway, Benton Harbor, MI 49022.*

Needed: Sencore VA48, Sencore TF46 and Sencore UPS164. *Rod Wells, 4528 N. Dearing St., Fresno, CA 93726; 209-291-5071.*

Needed: Adapter cables for Sylvania Check-a-Color CK 1500X rig, transverter, matching cords and other updating equipment. *A. Johnston's Electronics, 14 Waldwick Court, Toms River, NJ 08757.*

Needed: Sencore LC53 *Nate Lilienthal, 29515 Quailwood Drive, Palos Verdes, CA 90274; 213-377-9913.*

Needed: Power transformer for Hewlett-Packard model 130A scope; P/N 910-148 replaced by P/N 9100-0078. *Dewey Landis, 2712 Mayfair N., Seattle, WA 98109; 206-282-2624.*

Needed: Service manual or schematic for Sears b&w television, model 5025, chassis 562.10453, 110Vac and 12Vdc, and same for Candle b&w television, model MT510 or MT510A, 110Vac and 12Vdc. *John R. Andrade, Rt. 1, Box 40, San Gregorio, CA 94074.*

Needed: IC ECG 782 and picture tube 370 AUB22 for Philco 13in color television. *J. Rosenblatt, 2063 E. 56 St., Brooklyn, NY 11234.*

Needed: Parts or a complete Hallicrafter model SX-62 receiver. *Paul Capito, 637 W. 21 St., Erie, PA 16502.*

Needed: Service manual and operator's manual for HyGain VHF marine transceiver, model 655. *Mark Moorman, P.O. Box 2923, Greenville, NC 27834.*

Needed: Tekfax volumes 101-105 and Supremes TV volumes 1-4, and 11. *C. T. Huth, 146 Schonhardt St., Tiffin, OH 44883.*

Needed: Instruction manual and schematic for Robyn CB transceiver tester, model MT-701. Will buy or copy and return. *Hubert McGraw, 10136 Renfrew Drive, El Paso, TX 79925.*

For sale: Sencore VA48, mint condition, with manual and probes, \$800. *Robert L. Blount, 40 S.W. 8th Ave., Delray Beach, FL 33444.*

Needed: Sencore LC-53 Z-meter and Sencore VA48 analyzer. Both must be in A-1 condition. *David A. Tabor, Box 56, Killdeer, ND 58640; 701-764-5017.*

Needed: Schematic for Columbian Hydrosonics Aqua Probe, model CH-363. Will buy or copy and return. *Robert A. Ports, 1420 Appian Drive, Punta Gorda, FL 33950.*

For sale: Heathkit VTVM model 1M-5228. Includes probes, manual and extra 50kV probe; new and accurate; asking half of kit price. *C. Gillow, P.O. Box 177, Springer, NM 87747; 505-483-2363.*

For sale: 1600 Sams Photofact folders from 1 to 1850, \$15. *Don's TV, 119 Lisann St., Tallmadge, OH 44278.*

For sale: Sencore VA48 analyzer; used less than 20 hours; \$850. *Ron Carron, Box 365, Highland, KS 66035; 913-442-3255.*

For sale: New and used TV tubes, many boxed; 30 cents each plus \$1.50 postage. Send stamped envelope for list. Will buy or trade for TV solid-state troubleshooting flow charts and books. *R. Stanley, 428 W. Roosevelt Blvd., Philadelphia, PA 19120.*

For sale: Two B&K 415 sweep/marker generators; one new, \$250, one used, \$100. *Jim Moyer, 417 E. Elm St., Tamaqua, PA 18252; 717-668-2607.*

For sale: Sencore VA48 analyzer and Sencore RC167 substitution box R/C. Both units, with manuals, \$800. *Raoul Vazquez, 7251 S.W. 9 St., Miami, FL 33144; 305-264-6785.*

For sale: Sencore VA48 video analyzer, \$825, manuals and probe included. Excellent condition; price includes shipping. *George Lazoryszak, George's TV, 4432 N. Chadwick St., Philadelphia, PA 19140.*

For sale: TV parts and equipment at good discounts. Send SASE. *Marvin Warmbrand, 8 Dusk Drive, Centereach, NY 11720.*

For sale: Avantek 120-degree LNA, \$375, and Sa-TEC R2B receiver, \$375. *WSEP, Sparta, WI; 608-269-2392.*

For sale: RCA junior volt ohmst with probes and service manual, \$50; high-voltage probe, \$15. *Al Crispo, 3225 Chipmunk Drive, New Port Richey, FL 33552.*

For sale: Sencore CR143 CRT tube tester, \$125; Anders CM-100 capacitance meter, \$60, used less than two hours. Buyer pays UPS postage. *Walter Fiscus, Audio Repair Service, Route 1, Box 345, Oxford, NC 27565; 919-693-1066.*

For sale: Jackson model 523 oscillograph and Jackson model 420 universal oscillator, manuals included. Manufactured in 1937 by the Jackson Electrical Instrument Company, Dayton, OH. These instruments are operable. *J. L. Carter, Box 464, Hooker, OK 73945; 405-652-2049.*

For sale: Sencore CB41 and CB42 CB analyzer in like-new condition. Includes manuals and test leads; \$525 or best offer. *Martin Major, 15810 Sapwood St., Tampa, FL 33624; 813-961-7303.*

For sale: Sencore TF46 Super Cricket transistor FET tester, new, \$145; B&K model 466 picture tube tester rejuvenator, used only on service calls, \$65; Conar model 311 resistor capacitor tester, \$25. All with manuals. *Paul's TV, 260 Main Cross, Charlestown, IN 47111; 812-256-3119.*

For sale: EICO model 145 multisignal tracer, \$75; EICO model 944 flyback/yoke tester; Precision Tube master series 10-2 tube and battery tester, wood dovetail box, antique, \$150. *Ed Barlow, Box 29, Tweed, Ontario, Canada K0K 3J0.*

For sale: Hewlett Packard model HP608D signal generator, \$220; B&K model 2040 CB generator, \$185; RCA 10J106 TV test jig, with cables, \$215. *Jeffrey Jeffers, 337 Lambert Ave., Groveport, OH 43125; 614-836-5368.*

For sale: B&K model 1077B TV analyst, \$300; B&K model 467 CRT restorer and tester, \$300; Triplett 5in VTVM, \$75. *J. L. Bachelor, 2538 Tam O'Shanter Drive, Cleveland, TN 37311; 615-472-8726.*

For sale: B&K 1077B TV analyst, \$200; B&K 415 solid-state sweep/marker generator, \$200. Both like-new condition; manuals and leads/probes included. *Tom's TV & Sound Service, 412 Grand Mesa Ave., Grand Junction, CA 81503; 303-243-1324.*

For sale: Heathkit model 1GB-1023 RF signal generator, \$35; Heathkit model 10-101 vector scope, with manuals, hardly used, \$65. Both for \$100 plus shipping. *Don Kerkhoff, 1266 Vermont St., Quincy, IL 62301.*

For sale: B&K 1077B analyst, used only three times, \$350. *H. Solano, P.O. Box 1074, Bricktown, NJ 08723.*

For sale: 85 books on radio and television and some on video; mostly hard-back, all in excellent condition; \$200 for all. *Daniel Seidler, 5827 S. Campbell Ave., Chicago, IL 60629.*

For sale: Hickok model 536 vacuum tube tester; Hickok model 209A VTVM; and Hickok model 675A oscilloscope. All probes and manuals included. *Edward H. Frazier, R. R. #2, Box 632, Brownsville, TX 77520.*

For sale: Sencore SC60 scope, \$1150; Sencore CA55 capacitor analyzer, \$275; and Leader LDM851 multimeter, \$65. *Val Obal, 3201 S. 73 St., Omaha, NE 68124.*

For sale: Sencore LC53 Z-meter, like new; B&K model 1477 dual-trace, trigger-sweep oscilloscope, like new; Bell & Howell complete 16-volume TV course with or without hardware. Best offer for one or all; write for complete list. *Rod Wells, 4528 N. Dearing St., Fresno, CA 93726; 209-291-5071.*

For sale: Hundreds of old radio and TV tubes (boxed) for \$1 each plus postage. Also old issues of *Radio News*, *Electronic World*, *Radio Craft*, *Audio Craft*, *PF Reporter*, *Electronic Servicing*, *Radio Electronics*, etc., \$2 a copy plus postage; special price for whole lot. *J. R. Blundin, 151 W. 3 St., Mt. Carmel, PA 17851; 717-339-0402.*

For sale: Hammarlund SP-600 receiver, B&K model 470 CRT tester, and two teletypewriters. *W. A. Frederickson, 3103 W. 12 Ave. Ct., Broomfield, CO 80020.*

For sale: Tektronix model 212 scope, portable ac/NiCads, \$600 or best offer; B&K 1476 scope, LN, with probes, \$300 or best offer; and Wavetech model VCG116 function generator, general purpose, \$400 or best offer. All working and with manuals; COD/UPS. *A&B Electric Company, 1883 E. Main, Rochester, NY 14609; 716-288-1520.*

For sale: Six like-new Admiral 3M2D chassis, \$25 each; set of six DK3 6CW6 and 6LU8 tubes, \$750. *Jenkins Service, 9 Airline, Bridgeton, MO 63044.*

For sale: Sams CB Photofacts in intermittent sequence 1 through 257 (125 volumes). \$250 plus shipping. *Richard E. Wood, Box 338, Lenn Road, Newburgh, IN 47630.*

Wanted: Good, used b&w CRT 16VDGP4 and Zenith flyback 95-3332-01. Miscellaneous recent Sams Photofacts for sale. *M. B. Danish, P.O. Box 217, Aberdeen Proving Ground, MD 21005.*

Needed: Schematic for a Panasonic AM/FM stereo receiver (model RE 8126). Inform me of your terms. *Thomas Lutz, Consumer Electronics, 614 Edwards St., Aurora, IL 60505.*

Needed: CK3000 Sylvania test jig; picture tube 490BLB22 or 19HNP22, used; yoke for a Sears color TV 80-77-4D or Y-268, used. *Richard Salazar, 10940 Sunnyslope Drive, Riverside, CA 92505.*

Needed: Service manual (in English) for NordMende Electronics (German) KM-394 Distortion Analyzer; a working NordMende SRG-389 Sine/Square generator; parts/service manual for Sansui SD-7000 R-R tape deck (circa 1971); service manual/owner's manual/parts for Acrosound ST-120 power amp (circa 1958). *Steve Bender, Bengrun Research Labs, Box 28360, Queens Village, NY 11428.*

For sale: B&K Model 415 solid state sweep/marker generator and B&K model 1077 TV analyst, both complete with cables, owner's manuals and schematics; both for \$150 plus UPS delivery charges. *William D. Fowble, 217 W. Desoto Drive, Harbour Heights, FL 33950.*

Needed: Chroma IC Philco P/N 46-5002-5 or -21 or Sylvania ECG 782 or GEIC-224 or Workman 2057. Will pay going rate and shipping. *Bud TV & Stereo, 18480 S.W. TV Highway, Aloha, OR 97006.*

Needed: Schematic and parts list for Supreme Instruments Corporation tube and set tester, model 504A. Will purchase copy or original, or will copy and return. *Harold J. Helm, Economy Sales and Service, 40 Monument St., Freehold, NJ 07728.*

Needed: Sencore VA-48 TV analyzer, Sencore SG-165 stereo analyzer with original box and manuals. *Chuck Vostry, 111 Grenadier, Franklin, TN 37064.*

Wanted: Good NTSC generator. *Linear Audio, 3155 N. Long, Chicago, IL 60641.*

For sale: Commodore Vic 20 computer game cassettes, large selection, low prices. Send SASE for list. *Don Maurer, 2352 Grace Ave., Lebanon, PA 17042.*

For sale: TV test equipment. Send large SASE for list. *Maurer TV, 2a S. 4 St., Lebanon, PA 17042.*

**DESOLDER-IT,
CLEAN-IT, COAT-IT,
FREEZ-IT...SEND FOR IT!**

Our new electronic problem solving catalog
and Free Chem-Wik® samplers!



Chemtronics
661 Old Willets Path
Hauppauge, NY 11788
800-645-5244
In NY 516-582-3322
Telex 968567

Circle (15) on Reply Card

SAVE TIME

For fast, accurate service, please remove the Peel-Off Label (which is used to address your magazine) and affix it to the Fast Fact Card, the Address Change Card, or to any correspondence you send us regarding your subscription.

ES&T

Linear ICs show analog can do the job

by Joseph J. Carr

Some people are under the impression that analog circuits are dead and gone, having been completely displaced by digital electronics. Makers of linear ICs can attest that the analog world is not only alive but thriving. Even many digital instruments require an analog subsystem for data acquisition. There are cases where linear IC devices will do a job better or cheaper than a digital circuit, while in still other cases the analog linear IC is the only way to do the job. This article will cover linear ICs, how they are used and how to troubleshoot those you suspect are bad in a circuit. The ubiquitous operational amplifier (op-amp) is a good place to start.


Op-amp basics

The operational amplifier was originally designed to perform mathematical *operations* in analog computers. Although analog computers aren't used today, the properties that made the op-amp suitable for that application also make it highly useful in a wide variety of dc and ac circuits. Some modern instruments, incidentally, are little more than fixed-program analog computers.

Figure 1 shows two different circuit symbols commonly used for operational amplifiers. The version in Figure 1a is the one most commonly encountered, while Figure 1b is used by a few companies and is technically the *of-*

ficial symbol. The only significant difference, however, is that one has a straight back, and the other has a curved back. The terminals are the same on both. The pinouts shown in Figure 1a are the so-called industry standard. They don't fit all op-amps, but they are sufficiently common to warrant comment. Originally they were used on the 741 device but are now found on op-amps of all quality levels.

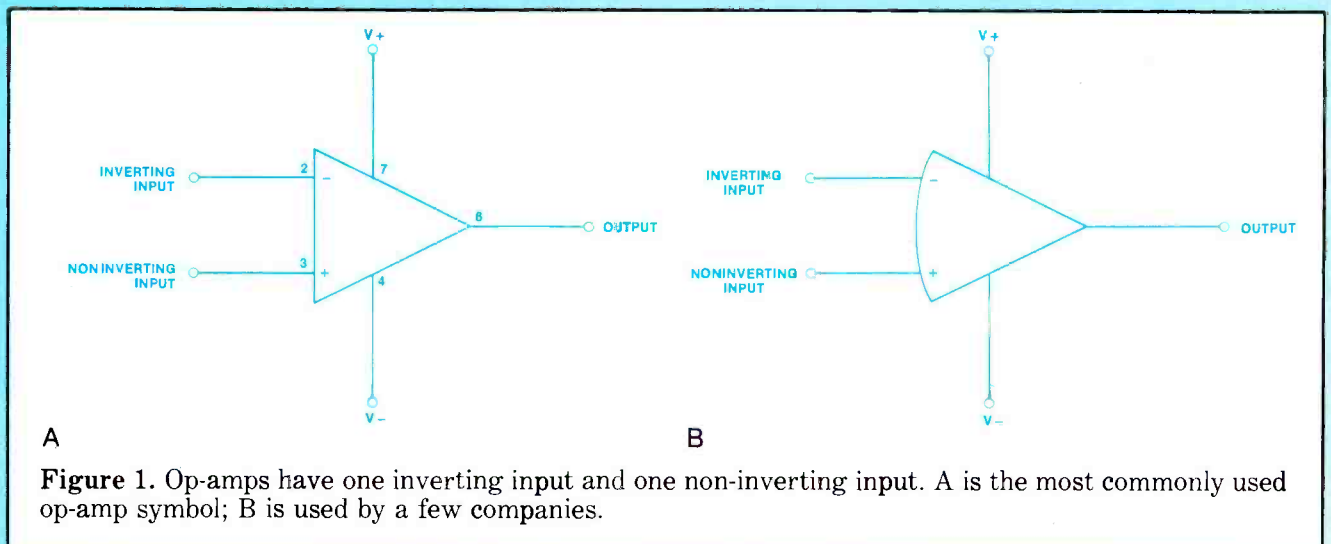The $V+$ and $V-$ terminals are the power connections. Note that there is no ground terminal on the op-amp. The $V+$ is an independent power supply that is positive with respect to ground, while $V-$ is negative with respect to ground,



A

B

Figure 1. Op-amps have one inverting input and one non-inverting input. A is the most commonly used op-amp symbol; B is used by a few companies.

Maybe We're Too Discrete About Our Discrete Products

Diode Specials

In Lots of 100

1N4148	\$3.60/100	1N4004	\$3.60/100
1N4001	3.00/100	1N4005	4.00/100
1N4002	3.25/100	1N4006	4.50/100
1N4003	3.40/100	1N4007	5.50/100

Transistor Specials

PN2222A	\$8.00/100	2N3906	\$12.00/100
PN2907A	8.00/100	2N3055	.65 ea.
2N3904	12.00/100		

Carbon Film Resistors

1/4 Watt 5% Tolerance

Now Only \$1.50/100

All 5% Values Available

Specializing in:

Resistors

Transistors

Diodes

SCRs

Full Wave Bridges

STOCKED
IN
DEPTH

And the Old and Exotic!


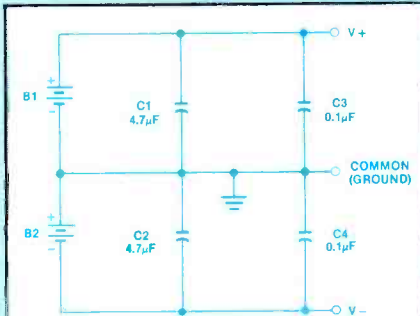


Figure 2. The power supply used for an op-amp must be bipolar.

Call Liz and ask about her parts today!

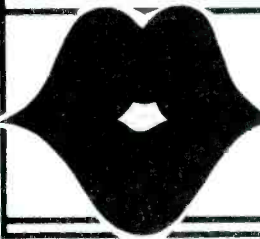We also purchase excess inventories. Call Martha about your parts today!



"Have You Kissed Your Computer Lately?"

Components Express, Inc.

1380 E. Edinger • Santa Ana, Calif. 92705 • 714/558-3972

TWX 910-595-1565 • ADVACON SNA • International Orders Welcome

Terms of Sale: Cash, Checks, Credit Cards, M.O., C.O.D. FOB Santa Ana.

Calif. residents add 6% sales tax.



Circle (16) on Reply Card

even though no separate ground connection exists on the op-amp.

The output terminal is self-explanatory. The output signal will swing positive or negative between certain limits less than V^- and V^+ .


The inputs on almost all op-amps consist of a pair of differential inputs. In theory, only the inverting input is needed, but all common op-amps also have the noninverting input.

The difference between the two inputs is a matter of *phase*. The inverting input produces an output signal that is 180° out of phase with the input signal. In other words, a *positive* voltage applied to the *inverting* input produces a *negative* output voltage (the inverting input is marked with a minus sign). The noninverting input, which is marked with a plus sign, produces an output that is in phase with the input signal. A *positive* voltage applied to the *non-inverting* input will produce a *positive* output voltage.

Since the op-amp output may have to swing either positive or negative, a bipolar dc power supply is needed. Figure 2 shows a typical power supply for an op-amp circuit. Although batteries are shown here, in most cases electronic power supplies will be used. Note that there are two separate

BELT IT TO 'EM

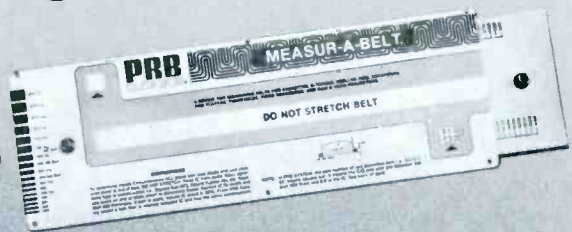SELL BELTS AT A PROFIT USING THE PRB SYSTEM



IT'S EXCLUSIVE!

Only PRB's copyrighted system puts the profit back into selling projector and recorder belts. Because the PRB stock number actually describes the belt you want. Measure a belt and find it instantly, without time-consuming references and cross-references.

FREE WITH A \$50 ORDER

You can get a wealth of valuable information — not just for belts, but for other components, too — free from PRB. Ask how you can get the PRB Technician's Reference Library.

For profitable products — and the references you need to make them even more profitable — call PRB. 1-800-558-9572

In Wisconsin: 1-800-242-9553
Business Number: 1-414-473-2151

TLX: 4994411 PRB USA

In Canada call collect: 1-613-225-5003

PROJECTOR RECORDER BELT
200 Clay Street
Whitewater, WI 53190



Circle (17) on Reply Card

power supplies: $V+$ and $V-$. The $V+$ supply is positive with respect to common, while $V-$ is negative with respect to common. The power-supply common is also used as the signal common, and may also be the ground (chassis) connection.

The capacitors shown in Figure 2 are not always used, but are needed in many cases for power-supply decoupling. The capacitors are always good practice and are especially needed in multi-stage cascade circuits, when high frequency (uncompensated) op-amps are used, or where the power supply lines may be noisy.

There are two capacitors on each line in Figure 2. The high-value type is used for low frequencies, while the low-value one is for high frequencies. The low-value capacitor should be mounted as close to the body of the op-amp as possible. If multiple op-amps are used, a separate pair of $0.1\mu\text{F}$ capacitors is needed for each op-amp.

The one case where the capacitors are not always used is on frequency-compensated (unconditionally stable) devices such as the 741. Those types of op-amps trade off frequency response in favor of stability, so they will only operate properly to 8 or 10kHz.

Ideal op-amps

An ideal op-amp would exhibit the following properties:

- zero noise contribution
- infinite frequency response
- infinite open-loop gain
- zero output impedance
- infinite input impedance
- differential inputs "stick together"

The first two ideal properties are never approached, but are thrown in for benefit of the purists who would insist, correctly, that such factors affect performance.

The third property tells us that there is no limit to gain. In real

devices, open-loop voltage gains (A_{VOL}) range from 200,000 to more than 1,000,000. An implication of this condition is that closed-loop gain is controlled totally by the feedback network.

Zero output impedance ($Z=0$) means the output will function as an ideal voltage source. Real devices usually have Z values of less than 100Ω .

If infinite input impedance could be achieved, neither input would either sink or source current. Real devices have Z_{in} value of $1M\Omega$ to $10^{12}\Omega$, and so will be considered ideal in most cases.

The final condition requires some explanation. The differential inputs must be treated mathematically as if they were at the same potential. If a voltage is applied to the noninverting input, for example, the same potential will be found on the inverting input. This is not just some theoretician's concept, but can actually be measured with a voltmeter. The property is the most frequently used in our simplified circuit analysis.

Inverting followers

Figure 3 shows the op-amp configuration called the *inverting* follower. The noninverting input is

grounded and so is at zero potential. The signal is applied to the input resistor, R_1 .

Because of Kirchoff's Current Law (KCL), we know in Figure 3 that $I_2 = I_1$ (the ideal op-amp does not draw current). We also know from Ohm's law that

$$I_1 = V_{in}/R_1$$

$$\text{and}$$

$$I_2 = V_{out}/R_2$$

KCL tells us that these equations are equal:

$$V_{out}/R_2 = -V_{in}/R_1$$

The *transfer function* of a circuit is the ratio of the output voltage to the input voltage (V_{out}/V_{in}), and is called the *gain* (A_v). Solving for this ratio yields:

$$-V_{out}/V_{in} = R_2/R_1$$

$$\text{or}$$

$$-A_v = R_2/R_1$$

These equations tell us that the gain is set only by the ratio of R_2 to R_1 . The minus sign indicates that phase reversal takes place.

An example

Suppose we need a gain of -100 , and an input impedance of $10K$.

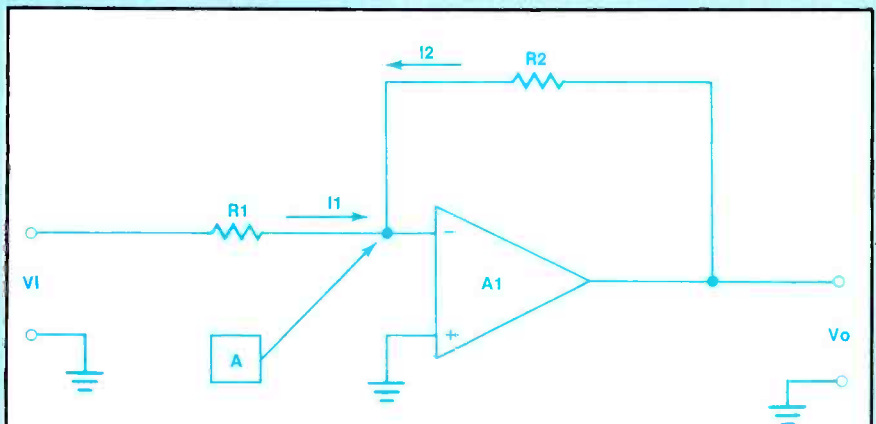


Figure 3. The gain of the op-amp inverting follower circuit is set by the ratio R_2/R_1 .

WE HAVE A LOT TO BRAG ABOUT AT ORA ELECTRONICS

ONE HOUR SHIPPING



Other companies brag about 24-hour shipping, but we at ORA Electronics have the best shipping time in the industry. ONE HOUR — that means that you can have that important part in your hands as early as the next day.

HIGH IN-STOCK RATIO

**95%
IN
STOCK**

ORA Electronics has the highest "in stock" ratio in the industry (95%). The average stocking ratio in the business is 75%. That means less back orders or "out of stock" items when you order from us!

BETTER SERVICE



Nobody offers better service than ORA Electronics — that includes packing, order handling, customer service and quality control. Our employees are highly trained and experienced to better serve you.

LOWER PRICES



Other companies lower the price on some items and advertise them heavily. We at ORA Electronics have a lower overall price—and yes, you'll like OUR total better!

FREE SHIPPING



Only ORA Electronics offers free shipping for prepaid orders (in the continental U.S.A.). For COD, charge and open account orders, we charge only actual shipping costs, no handling charges whatsoever!

TWO YEAR WARRANTY



All ORA Electronics' semiconductors and many other products are guaranteed for two full years. ORA Electronics has the longest warranty in the industry because we know what we sell: prime grade parts, and they are tested for quality.

ORIGINAL PARTS



ORA Electronics offers you only original semiconductors, no "replacements" or "substitutes" or "almost the same" parts. Some other companies re-label their parts. When you order from us, you can be sure that every semiconductor you buy is a prime grade, ORIGINAL, tested part.

POPULAR CATALOG



ORA Electronics' catalog is the most copied catalog in the industry. It's the easiest to follow, the prices are not confusing, and a comprehensive index is included. Send for your free copy today!

Call toll free: (800) 423-5336.
Calif. toll free: (800) 382-3663.
Non-order info: (213) 701-5850.
Local: (213) 701-5848.

ORA
ELECTRONICS
A DIVISION OF ALLIANCE RESEARCH CORPORATION

"OUR SERVICE MAKES THE DIFFERENCE"
18215 PARTHENIA ST., NORTHridge, CA 91325

Rearranging the equation for A_v will allow us to find R_2 that will yield a gain of -100 .

$$\begin{aligned} R_2 &= -A_v R_1 \\ R_2 &= -(-100)(10K) \\ R_2 &= 1000K = 1M\Omega \end{aligned}$$

In the example above, we used the value of R_1 as the amplifier input impedance. This is true because point A is essentially at ground potential due to the grounding of the noninverting input. Even though point A of Figure 3 is not actually grounded, it behaves as if it were grounded. This situation is called a *virtual ground*.

A problem with the inverting follower circuit is that the maximum input impedance is limited to the value of R_1 . In some practical circuits, this value can be somewhat low. A solution to the problem is the noninverting follower circuit.

Noninverting followers

The noninverting follower circuits of Figure 4 apply the signal to the noninverting input of the operational amplifier. There are two configurations: the unity gain (4a) and with gain (4b).

The unity-gain noninverting follower of Figure 4a has a voltage gain of one because it uses 100% negative feedback. Uses of this circuit include buffering with neither loss of voltage amplitude nor change of phase, and impedance transformation made possible because of the high input impedance and low output impedance.

Because $V_{out} = V_{in}$, and the output impedance is very low, we must conclude that the unity-gain noninverting follower does offer power gain, even though voltage gain is unity.

The circuit in Figure 4b is a noninverting follower with gain. Using an analysis similar to that

used above for the inverting case, but taking into account that point A is at a potential equal to V_{in} rather than ground, we arrive at the following gain equation:

$$A_v = R_2/R_1 + 1$$

The gain version of the circuit can be used for exactly the same

applications as the unity-gain version, but with voltage gain as well as power gain.

Op-amp problems

Practical op-amps do not match the idealized version. One major problem is output offset voltages. This term means that the output voltage will be nonzero at a time

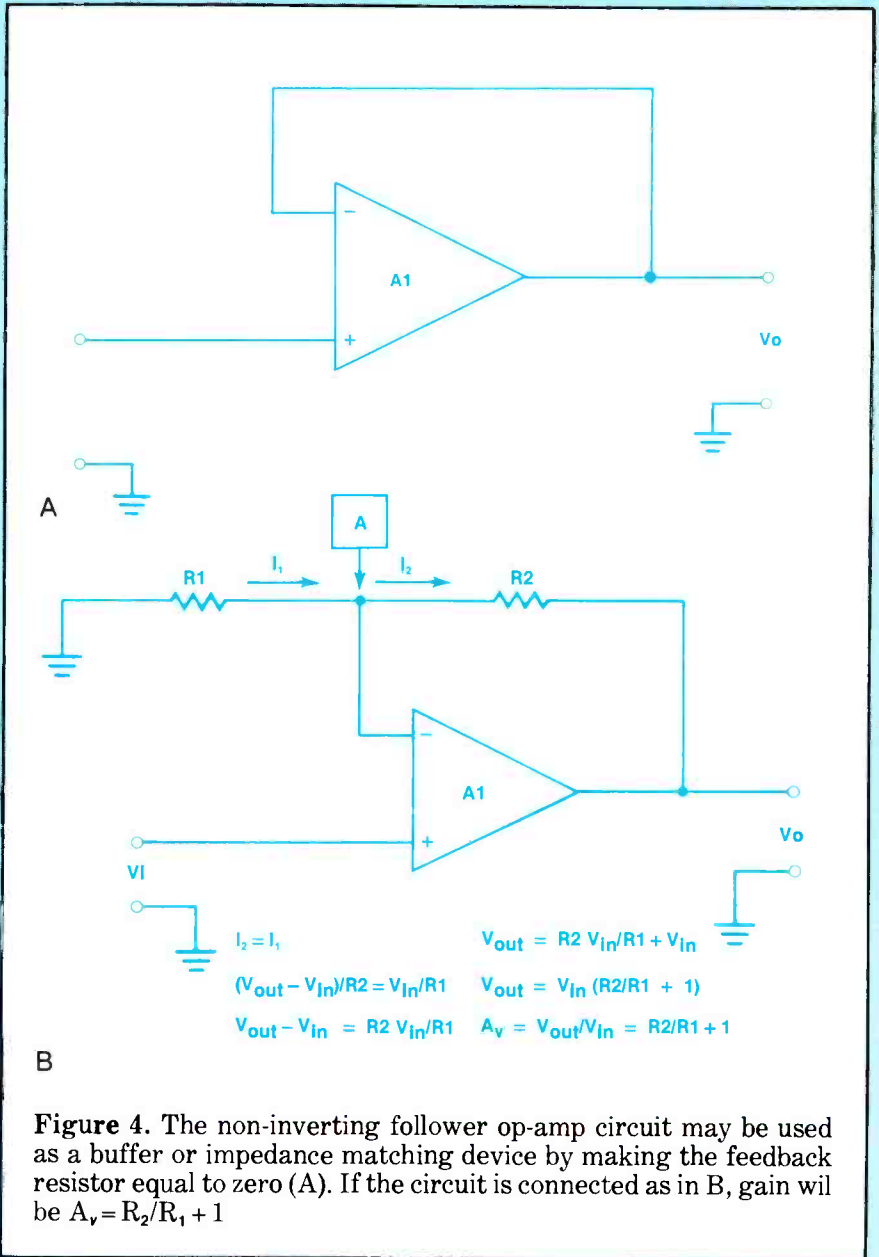


Figure 4. The non-inverting follower op-amp circuit may be used as a buffer or impedance matching device by making the feedback resistor equal to zero (A). If the circuit is connected as in B, gain will be $A_v = R_2/R_1 + 1$

when it should be zero. For example, if $V_{in} = 0$, then V_{out} should also be zero. In many cases, however, it will not be zero.

There are several causes of output offset voltages; among them are the input bias currents. If bipolar transistors are used in the input stage, their bias currents will be available at the (-) and (+) input terminals. In that case, the input impedance is not infinite. Figure 5 shows a simple method for reducing the effect of this current. The output offset is caused by current from the (-) input flowing in R_1 and R_2 , creating an input offset voltage that is amplified by the gain. If we force the bias current from the (+) input to flow in the same resistance, it will produce an equal but opposite offset voltage, and the two cancel each other. The net result is zero. Resistor R_3 in Figure 5 is called a *compensation resistor* and serves this purpose. Resistor R_3 has a value equal to the parallel combination of R_1 and R_2 .

The method of Figure 5 solves only one form of output offset voltage problems. Those of Figure 6, however, solve all forms of normal output offset voltage problems, including that caused by input bias currents.

Figure 6a shows a circuit that is used when the op-amp is equipped with a pair of *offset null* terminals (not all so equipped). A potentiometer is connected between the offset null terminals, and its wiper is connected to the $V-$ power supply terminal. This potentiometer is adjusted to produce $V_{out} = 0$ when the V_{in} input is shorted to ground (or common). Alternatively, the potentiometer is sometimes adjusted for $V_{out} = 0$ when the (-) and (+) inputs are shorted together.

A more universal scheme is shown in Figure 6b. Here we null the natural output offset by using the potentiometer to introduce a counter-offset of a magnitude and polarity to completely cancel the offset voltage. Adjustment of the

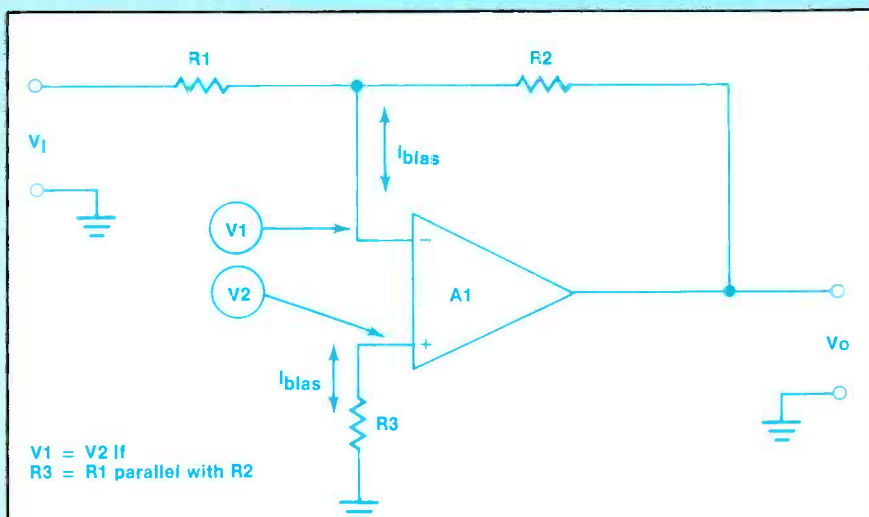


Figure 5. If bipolar transistors are used in the input stage of the op-amp, their bias currents will cause an output offset voltage. Addition of R_3 , equal to the parallel combination of R_1 and R_2 will compensate for this offset.

New! 80MHz B&K-PRECISION multi-function counter does it all...

FREQUENCY PERIOD TOTALIZE



B&K-PRECISION
Model 1805 \$290

Now you can have one counter that handles most every need, at an affordable price. Conservatively rated at 80MHz, the 1805 is not just another frequency counter. In addition to measuring frequency, it also measures period and totalizes, so it's ideal for many industrial and service industry applications. To best resolve your measurement questions, the 1805 displays input signals to full eight digits on a bright LED display. Resolution is up to 0.1Hz.

For accurate measurement of low frequency signals when high-frequency noise may be present, a low pass input filter may be selected. Other features include a switchable input attenuator and a stable timebase.


Further separating the 1805 from other counters in its price class is the display hold feature. A touch of a button freezes any displayed reading and holds it—even after the input signal has been removed.

The new B&K-PRECISION Model 1805 is available for immediate delivery at your local distributor. For the name of your nearest distributor or for additional information, call:


B&K PRECISION
DYNASCAN
CORPORATION

6460 West Cortland Street
Chicago, Illinois 60635 • 312/889-9087
International Sales: 6460 W. Cortland St., Chicago, IL 60635
Canadian Sales: Alias Electronics, Ontario
South and Central American Sales,
Emoire Exporters, Plainview, NY 11803

Circle (18) on Reply Card

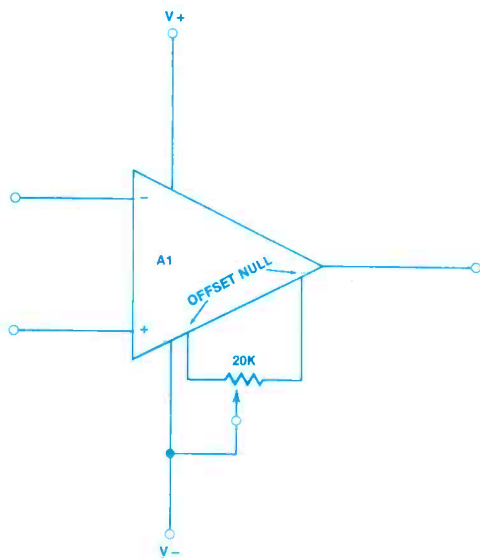


A

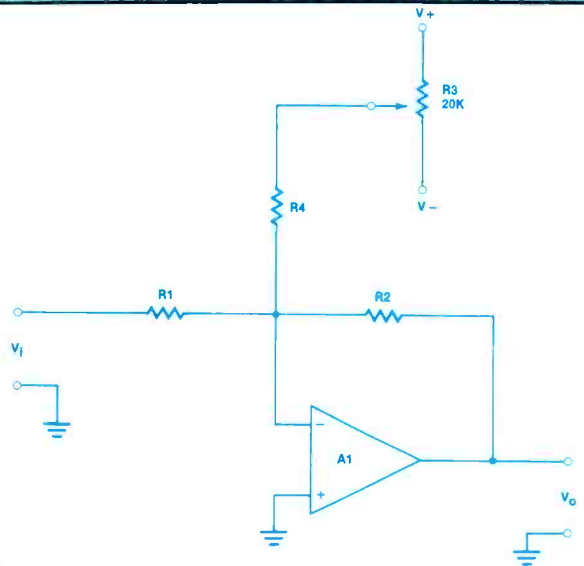


B


Figure 6. Some op-amps are provided with a set of offset-null terminals to provide for output-offset compensation.

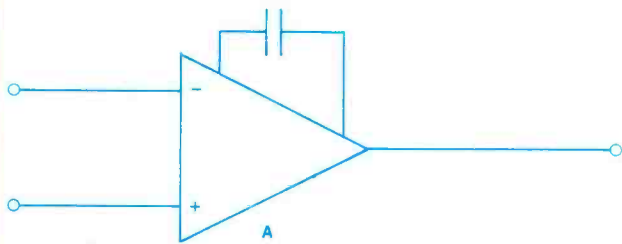


A

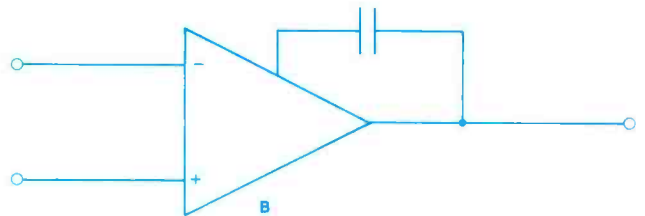

B

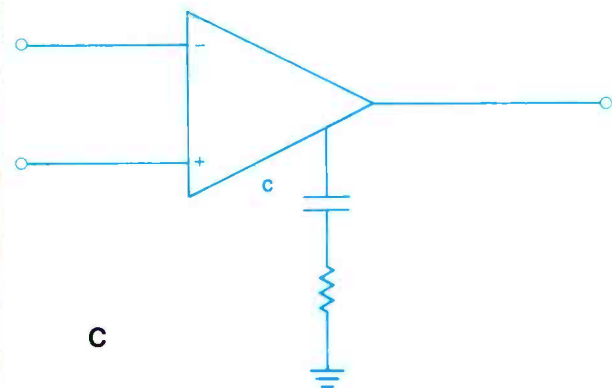

C

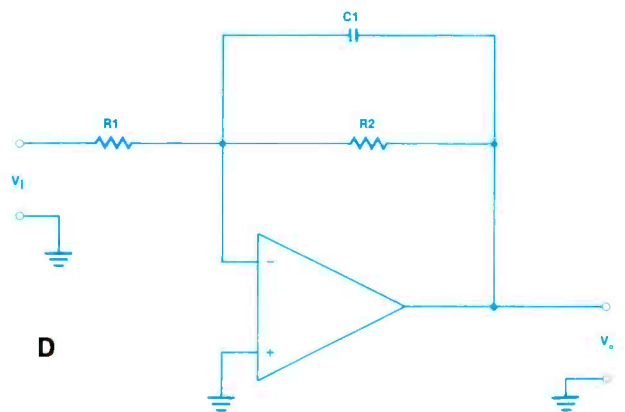

D

Figure 7. Op-amps will oscillate under some conditions. It may be necessary to limit the frequency of the op-amp by adding external components in order to preclude oscillation.

potentiometer is accomplished by setting the input voltage to zero (shorting the input(s) to ground). The potentiometer is then adjusted for an output voltage of zero.

Frequency compensation

Some operational amplifiers have such limited frequency response that they are said to be *unconditionally stable*. A 741 device, for example, operates only to a few kilohertz. Others, however, have much wider bandwidths, and under some circumstances will oscillate at some

natural frequency. For these amplifiers, other means must be found. Figure 7 shows several methods for reducing the frequency response.

Figure 7a shows the use of a capacitor across a pair of frequency compensation terminals (which are also sometimes the dc offset terminals). Typical values for the capacitor are 10pF to 1000pF. Figure 7b shows a feed-forward capacitor between a compensation terminal and the output terminal. In Figure 7c we have an RC network between the compensation

terminal and ground. The final method, in Figure 7d, shows a capacitor shunting the feedback resistor. At low frequencies, where X_c is much higher than R_2 , the gain is essentially R_2/R_1 , or $(R_2/R_1 + 1)$ in noninverting followers. At higher frequencies, the gain falls off at a rate of -6dB/octave . The frequency at which the gain starts falling off is measured from the -3dB frequency as defined by:

$$f = 1/2\pi R_2 C_1$$



TECHNICIANS & SERVICEMEN
COMPONENTS FOR YOUR MAINTENANCE & REPAIR WORK
SPECIAL: OUR LOW LOW PRICES
REPLACEMENT FOR ECG® TYPES

TYPE NO.	YOUR COST	TYPE NO.	YOUR COST
85	FOUR for .99	125	SEVEN for .99
102A	THREE for .99	159AP	FOUR for .99
123A	FIVE for .99	177	EIGHT for .99
123AP	SIX for .99	199	FIVE for .99

SUPER SPECIAL (MIN. 5 PC. EACH)

TYPE NO.	YOUR COST	TYPE NO.	YOUR COST	TYPE NO.	YOUR COST
124	.85	165	2.25	375	.90
128	.45	171	.65	506	.55
129	.45	184	.45	500A	8.95
130	.80	185	.45	523	9.95
152	.40	238	2.25	526A	10.20
153	.40	276	6.95	529	13.75
154	.60	291	.95	712	1.25

JAPANESE TYPES (MIN. 5 PC. EACH)

2SC867A	2.75	HA1366W	1.85	STK0029	3.80
2SC1114	3.25	HA1377A	2.90	STK0080	9.99
2SC1308K	1.95	LA4102	1.25	TA7205AP	1.50
AN214Q	1.45	M51515BL	2.95	TA7208P	1.85
AN239A	4.60	STK433	3.95	TA7222AP	1.95
BA532	1.80	STK435	3.95	UPC1181H	1.25
GH3F	.99	STK437	6.25	UPC1182H	1.25
HA1342A	2.30	STK439	6.50	UPC1185H	2.99

COD ORDERS WELCOME (\$25 MIN. ORDER)
For Complete Component Catalog Call or Write
DIGITRON ELECTRONIC
110 HILLSIDE AVENUE, SPRINGFIELD, N.J. 07081
Toll Free: 800-526-4928 In NJ: 201-379-9016

*ECG IS A TRADE MARK OF PHILIPS ECG.
DIGITRON ELECTRONIC IS NOT ASSOCIATED IN ANY WAY WITH PHILIPS ECG.

OPTIMA ELECTRONICS
TO ORDER CALL TOLL FREE 1-800-327-0224
G.E., SYLVANIA, ZENITH, RCA, 75% OFF LIST NEW-BOXED

<input type="checkbox"/> 3A3	5 FOR \$15.75	<input type="checkbox"/> 6LF6	5 FOR \$34.44
<input type="checkbox"/> 6MJ6	5 FOR \$34.88	<input type="checkbox"/> 6LB6	5 FOR \$31.50
<input type="checkbox"/> 6JE6	5 FOR \$32.75	<input type="checkbox"/> 6CJ3	5 FOR \$14.69
<input type="checkbox"/> 3DJ3	5 FOR \$17.44	<input type="checkbox"/> 6JS6	5 FOR \$29.00
<input type="checkbox"/> 6GH8	5 FOR \$12.44	<input type="checkbox"/> 6BL8	5 FOR \$12.25

All Tubes Not Advertised, Write in at 75% Off List.
Sleeves Only, Singles 72% Off List

HORIZONTAL OUTPUT TRANSISTORS **REPLACEMENT TRIPLERS**

<input type="checkbox"/> RKS1172B	<input type="checkbox"/> RKS238	<input type="checkbox"/> 500A	\$11.95	<input type="checkbox"/> 526A	\$14.95
<input type="checkbox"/> RKS1308K	<input type="checkbox"/> RKS165	<input type="checkbox"/> 522	\$11.95	<input type="checkbox"/> 529	\$15.50
		<input type="checkbox"/> 523	\$13.95	<input type="checkbox"/> 539	\$15.75

TRANSISTORS & I.C.'s...MIN. 10, CAN MIX

T.V. #'s	Pop. I.C. #'s	STEREO #'s			
<input type="checkbox"/> 2SC1114	\$3.75	<input type="checkbox"/> 712	\$1.50	<input type="checkbox"/> DM133	\$5.95
<input type="checkbox"/> MN8303	\$3.95	<input type="checkbox"/> 713	\$1.50	<input type="checkbox"/> DA101	\$5.75
<input type="checkbox"/> 2SC1034	\$5.95	<input type="checkbox"/> 714	\$1.50	<input type="checkbox"/> HA1377A	\$3.25
<input type="checkbox"/> 2SC867A	\$3.50	<input type="checkbox"/> 731	\$1.50	<input type="checkbox"/> HA1388	\$5.25
<input type="checkbox"/> 2SD870	\$4.75	<input type="checkbox"/> 790	\$1.50	<input type="checkbox"/> HA1396	\$5.50
<input type="checkbox"/> 2SD871	\$5.50	<input type="checkbox"/> 791	\$1.85	<input type="checkbox"/> HA1398	\$4.95
<input type="checkbox"/> AN5210	\$6.50	<input type="checkbox"/> 793	\$1.95	<input type="checkbox"/> UPC1181	\$1.25
<input type="checkbox"/> AN5310	\$3.95	<input type="checkbox"/> 819	\$2.25	<input type="checkbox"/> UPC1182	\$1.25
<input type="checkbox"/> AN5320	\$3.25	<input type="checkbox"/> 820	\$2.25	<input type="checkbox"/> UPC1185H	\$3.50
<input type="checkbox"/> AN5435	\$2.95	<input type="checkbox"/> 821	\$2.00	<input type="checkbox"/> UPC1367	\$3.25
<input type="checkbox"/> LM1818	\$3.25	<input type="checkbox"/> 822	\$2.75	<input type="checkbox"/> UPC1368H2	\$3.95

GENERAL

<input type="checkbox"/> Exact Rep. for SG613	5 for \$35.00
<input type="checkbox"/> HI DIV-3 (800-616 equiv.) focus block div.	10 for \$35.00
<input type="checkbox"/> 6 ft. Cheater Cords SPT2 (Heavy Duty - UL App. 7 Amp. 125V. P & NP)	10 for \$ 7.95
<input type="checkbox"/> Solder Wick	10 for \$6.95
<input type="checkbox"/> BSR Changers	\$32.95
<input type="checkbox"/> Replacement Tone Arms (mono & stereo)	5 for \$6.00
<input type="checkbox"/> Speaker Wire-50ft. 24 gauge	5 for \$5.00
<input type="checkbox"/> Fiberglass Align Tool Set (5 pcs)	5 for \$4.00
<input type="checkbox"/> 2.5 Amps 1000 PIV Rectifiers	100 for \$8.95

Quantity Prices Available
Letters of credit and all checks placed on deposit with Bank of Hallendale, FL. VISA & Master Charge accepted. Min. order \$75. FOB Dania, FL. Catalog \$3, refundable upon order.

SEND CHECK OR MONEY ORDER TO:
OPTIMA ELECTRONICS
2022 Tigertail Blvd., Dania, FL 33004
Phone (305) 920-3550 TOLL FREE: 1-800-327-0224

Circle (19) on Reply Card



Circle (20) on Reply Card

Test your electronic knowledge

By Sam Wilson, IS CET test director


These questions are similar to questions used on the various CET tests. All questions on the actual CET test are multiple choice, and a grade of 75% or better is required for passing. This month's questions are all about power supply. (Answers on page 57)

- Which of the following is true regarding the rectifier diodes in Figure 1?
 - The diode-resistor combination doesn't make sense.
 - The combination assures equal forward voltages across the resistors.
 - The combination assures equal reverse voltages across the resistors.
 - The PIV of the combination is the same as the lowest PIV rating of the three diodes.
 - The PIV rating of the combination is the same as the highest PIV rating of the three diodes.

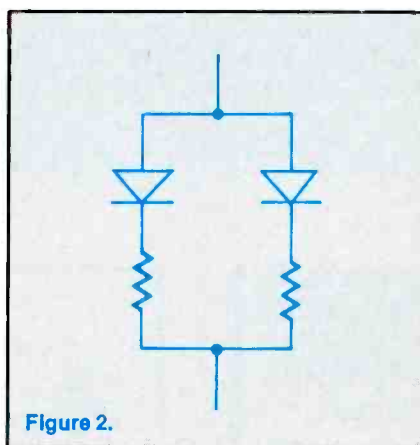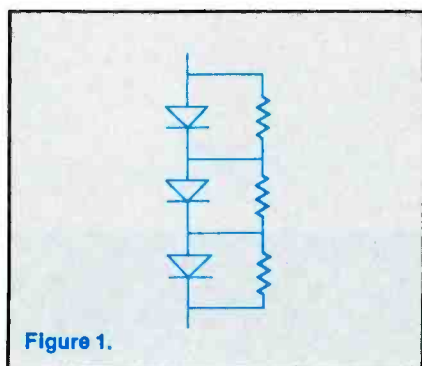

- Which of the following is the purpose of the resistor in the rectifier diode-resistor combination of Figure 2?
 - Limit the forward current through the diodes.
 - Assure that both diodes will conduct.
- Which of the following is true regarding the rectifier diodes in Figure 2?
 - The diode-resistor combination doesn't make sense.

- The combination assures equal forward voltages across the resistors.
 - The combination assures equal reverse voltages across the resistors.
 - The PIV of the combination is the same as the lowest PIV rating of the two diodes.
 - The PIV rating of the combination is the same as the highest PIV rating of the two diodes.
- The circuit of Figure 3 is
 - a discriminator.
 - a ratio detector.
 - a full wave rectifier.
 - a voltage doubler.
 - two half-wave rectifiers.
 - The broken line between the primary and secondary windings in Figure 3 represents
 - a self-resonating transformer.
 - a saturable reactor.
 - an auto transformer.
 - Faraday shield.
 - a phase shifter.

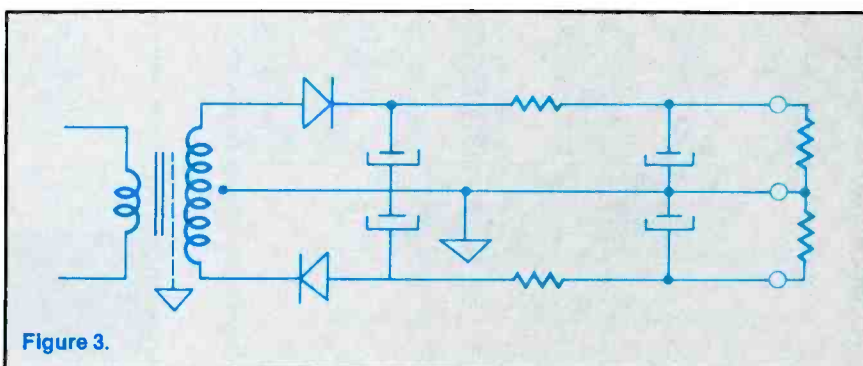

6. The purpose of the 4.7Ω resistor in Figure 4 is
- to limit the output voltage to a given value.
 - to improve the supply regulation.
 - to protect the diode.
 - to protect the output load resistance.
 - None of these choices is correct.
7. The output voltage of the supply in Figure 4 should be about
- 140V.
 - 100V.

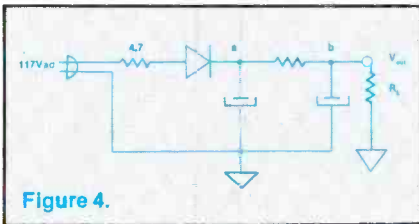


Figure 4.

8. In the circuit of Figure 4 you will find the audio power amplifier connected to which point?
- a
 - b

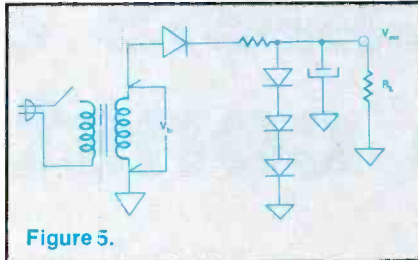


Figure 5.

9. All of the diodes in the circuit of Figure 5 are silicon types. Which of the following is true regarding this circuit?
- The output is short circuited.
 - The diodes are connected in the reverse direction.

- The diode current must be equal to the load current.
- In order for the circuit to work properly, V_{IN} must be at least 25V.
- The output voltage is about 2.1V.

10. The circuit in Figure 6 is
- a short circuit across the secondary.
 - a bridge rectifier.
 - an open circuit.
 - a preregulating circuit and full-wave rectifier.
 - ok if all of the diodes are reversed.

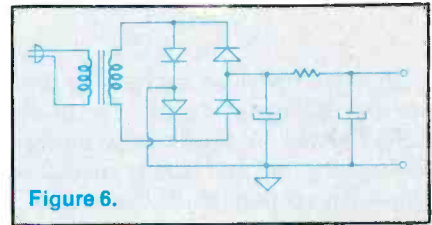


Figure 6.

ES&T

COMPACT ECONOMICAL DESOLDERING

It's so Dependable, there's a Two-Year Warranty on the Pump. The EX-525 may be A.P.E.'s lowest-cost portable solder extractor, but it's full of features: • easily descenders components from multi-layer PC boards • pump is vibration-isolated for quiet operation • Model 550 for use with shop air • EX-1000 handpiece is non-clogging and temperature-regulated by panel controls.

You need the A.P.E. EX-525 in your shop. Call or write today for all the details. **Automated Production Equipment Corp.**, 142 Pecanic Ave., Medford, N.Y. 11763 • 516-654-1197, TWX: 510-228-2120

DEPEND ON A.P.E.

Circle (21) on Reply Card

FINALLY. COMPUTERS AS A NEW TOOL FOR T.V. REPAIR.



Primefax puts computer-assisted repair capability in your shop today.

Primefax drastically reduces the number of sets requiring extensive trouble-shooting procedures. Through the use of today's technology, Primefax maintains—in a central computer—a database of problem-solving solutions for television set malfunctions. Primefax is a compilation of the most current, applicable technical information acquired from hundreds of valuable sources . . . and updated daily.

With a Primefax Computer Terminal installed in your shop, you can do your job more quickly and more

accurately. You have more satisfied customers, and your profits are increased substantially.

Reduced call backs • faster turn-around • reduced chance of repeated failure • more thorough service and complete repair at reasonable cost.

The more Primefax is used, the more profit you realize.

CALL US OR WRITE. No matter how you compute it, Primefax means profit for you. It's worth looking into.

In Texas, call (512) 344-5999 • Out of Texas, call 800-531-5953

Primefax

4825 Fredericksburg Road • San Antonio, Texas 78229

Circle (22) on Reply Card

Understanding decibels and time constants

By Sam Wilson, ISCET test director

The two previous articles in this series (August and October **ES&T**) have covered the invention of logarithms and their relationship with epsilon (e). In this article, we will show how epsilon is related to the charge of a capacitor.

Why study math?

Mathematics is a shorthand method of expressing relationships in electrical and electronic circuits. Technicians should think of mathematics as being an aid (rather than a hindrance) to analyzing electronic circuits and systems. Unfortunately there is so much new technology to be learned that the importance of basic mathematics relationships is often underestimated.

I have heard technicians boast that they have worked many years in electronics and never even used Ohm's Law.

Suppose a technician measures the voltage across a resistor and finds that voltage is too low according to the manufacturer's specifications. He immediately knows that the current or resistance (or both) is too low. He knows that because he knows Ohm's Law. He knows that the voltage across a resistor depends directly upon the current and resistance. In other words, he knows that $V = I \times R$.

Every time a student learns an equation, he is learning a shorthand method of remembering relationships in circuits. Imagine try-

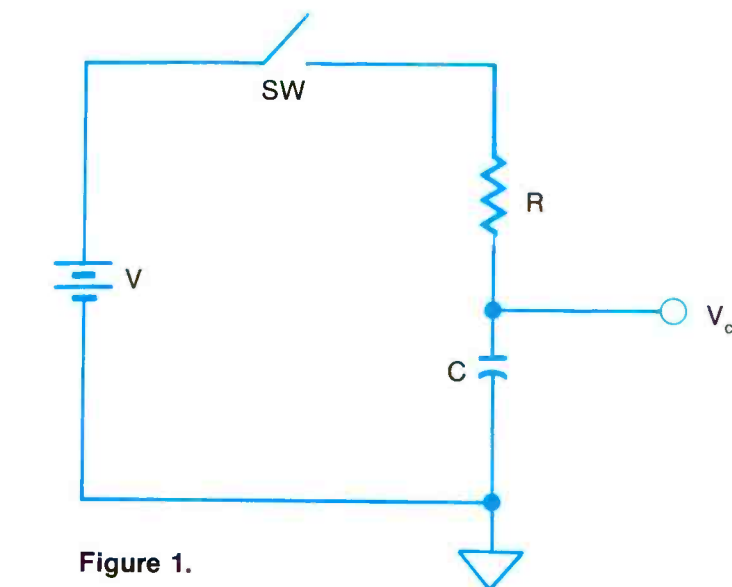


Figure 1.

ing to learn about electronics by dealing with Ohm's Law stated, "The amount of voltage drop across a resistor is dependent upon the amount of current flowing through that resistor, and it is also directly dependent upon the amount of resistance of that resistor."

Can you imagine having to learn 20 or 30 laws similar to that before you could begin to understand basic electric circuits? Fortunately you don't have to. The simple equation $V = IR$ tells it all.

Time constants

How was the time constant

equation ($T = RC$) obtained? Consider the circuit of Figure 1. The capacitor is discharged. It will start to charge the instant the switch is closed. The mathematical equation for the voltage across the capacitor (v_c) at any instant of time after the switch is closed (t) is:

$$v_c = \left(1 - \frac{1}{e^{t/RC}}\right) V$$

Where V is the applied voltage, R and C are the resistance and capacitance in ohms and farads respectively, and e is epsilon (2.71828).

A special case occurs when t is made equal to $R \times C$.

$$\frac{t}{RC} = \frac{RC}{RC} = 1$$

For $t = RC$, the equation becomes:

$$\begin{aligned} v_c + (1 - \frac{1}{e^{t/RC}})V \\ = (1 - \frac{1}{e^1})V \\ = (1 - \frac{1}{2.71828})V \end{aligned}$$

$$v_c = 0.632V, \text{ or, } v_c = 63.2\% V$$

This equation shows that the voltage across the capacitor is 63.2% of the applied voltage when $t = RC$. That is the reason that the voltage on the capacitor after *one time constant* equals 63.2% of the applied voltage.

An important thing to note from this discussion is that e is a factor in calculating the growth of voltage across a charging capacitor. This peculiar number (2.71828) is related to many fields other than electronics and biology.

The time constant equation ($T_c = R \times C$) is useful when you want to find how long it takes a capacitor to charge to 63.2% of the applied voltage. But how do you find the voltage across the capacitor for some other value of time? If you have a calculator, it is a simple matter to use the equation for v_c . If you do not have a calculator, follow the step-by-step procedure to increase your insight into the time constant.

Sample problem

In the circuit of Figure 1, the following values apply: $V = 5V$, $R = 1M\Omega$ and $C = 1\mu f$.

What is the value of v_c 0.5s after the switch is closed? (For this type of problem, always assume the

capacitor is discharged to start.)

Solution

The time (t) is 0.5s, and the value of $R \times C$ is:

$$R \times C = 1 \times 10^6 \times 1 \times 10^{-6}$$

$$\text{or } R \times C = 1s$$

The equation can now be solved:

$$v_c = (1 - \frac{1}{e^{t/RC}})V$$

$$= (1 - \frac{1}{e^{0.5/1}}) \times 5$$

$$V_c = 1.97V$$

So, in 0.5s the voltage across the capacitor has increased to slightly less than 2V.

The equation for v_c can be used for many practical problems. However, in technicians' books, $T_c = R \times C$ is often given as the only time constant equation. And for full charge of the capacitor, the equation is given as $T_c = 5 \times R \times C$.

Is the capacitor really charged to the full supply voltage in five time constants? Not quite. If you use $t = 5$ in the equation for v_c , you will find that the voltage across the capacitor is 99.3% of the supply voltage at the end of five time constants.

So when does the capacitor actually become fully charged? Never. You can raise e to any large number and if your calculator can work with that number, you will find that the capacitor is not quite charged to the full supply voltage.

The value of five time constants for full charge was chosen because, for all practical considerations, the capacitor is fully charged after that amount of time.

Arriving at the equations

How did they arrive at the equation for decibels, time constants and Ohm's Law? The curve for the response of the human ear to loudness and the curve that shows

the voltage across a capacitor during charge are both logarithmic.

If you were an early experimenter working on hearing measurement and graphed your results, you would soon come to the conclusion that the general shape of the curve is the same for all people with normal hearing. If you had a basic math background, you would recognize that you are dealing with a logarithmic response, so you would write an equation that involved logs for the hearing response.

The process of writing an equation from a curve is called *curve fitting*. This is not to play down the valuable contribution of the people who did this important work. But, technicians are sometimes puzzled about where certain equations come from.

You could not derive the equation for decibels without first making a lot of measurements to see what type of response you are dealing with. Equations that are derived this way from data are called *empirical equations*.

The equation for V_c was derived the same way. Data was taken and curves were drawn, then the equation that fit that curve was written. Therefore, V_c is an empirical equation.

It is interesting to note that Ohm's Law ($V = IR$) was derived empirically. Georg Ohm lived in the shadow of his brother, who was a famous biologist in Europe.

Ohm studied the relationship between voltage and current, then wrote an equation that related the two. His first published paper gave an equation that was not correct. Fortunately, he reworked the equation and soon published it in the form we use today.

So far in this series we have talked about the concept of decibels and time constants. In a future issue, we will continue with the time constant equations and then give examples of practical problems that can be solved with the equations discussed up to this point.

ES&T

Troubleshooting symmetrical output circuits

By Bud Izen, CET/CSM

The most common type of audio-output circuit uses two transistors in what is commonly called a push-pull or complementary arrangement. There are many specific examples of circuits of this type, but fortunately only three basic variations on the theme. These are the push-pull transformer-coupled type, the true output-transformerless (OTL) type and the most common of the three, the quasi-complementary type.

The easiest to understand is the garden-variety transformer-driven output stage (Figure 1). You will come across this circuit or its close cousins in all tube circuits, older transistorized products and less-expensive products. Because a majority of the products in the service market now are solid state, we'll just look at transistor circuits, but the exact same analysis applies to tube circuits.

The output transformer is driven by both Q1 and Q2. The signal inverter make the top and bottom signals fed to each device a mirror image of each other because they are 180° out of phase. Each device is biased into cut-off either half of the time (pure class B operation) or slightly less than half of the time (class AB operation). This overlap in conduction is created in order to eliminate *crossover distortion*, which can occur if one device turns on as the other turns off. This can be easily observed on the scope as a "notch" appearing as the waveform crosses the zero-conduction point.

When either transistor conducts, it induces a voltage across the entire transformer primary, which is then coupled to the trans-

former secondary and therefore appears across the speaker. Depending on the design choice made by the manufacturer, the out-of-phase signals used to drive each device may be furnished by a single inverter stage, which affects only one of the output devices (the bias makes sure when each one starts to conduct), or may be fed by an input transformer. Such a transformer provides two signals, each 180° out of phase with the other (Figure 2).

Transformer coupling

The disadvantages of using transformers are phase distortion due to the reactance of the transformer, loss of low-frequency response due to core loss, weight increase, increased cost and the resulting increase in product size, and energy consumption due to transformer inefficiency. The main advantage of using transformers is ease of design, and a lesser advantage is that short circuits in the driver stage are isolated from the output stage and vice versa. For this reason, troubleshooting is fairly straightforward.

A more complex circuit

Neither of the circuits of Figures 1 or 2 are practical enough to work, yet they are not far from being usable. A realistic circuit using a single transistor as a phase splitter is shown in Figure 3. The signal at the collector of Q1 is 180° out of phase with that on the base, which can be treated as being in common emitter configuration. The signal at the emitter is in phase with that at the base, and

can be thought about as being in common-collector, or emitter-follower configuration.

The gain of the Q1 stage is set by the ratio of R3 divided by R4, and is adjusted so that the signals from collector to ground and emitter to ground are essentially equal, and opposite in polarity. Q1 and Q2 are then biased into class B or AB operation by resistors R5 and R6. Capacitors C1, C2 and C3 are necessary in order to avoid quiescent operating point shift. Although more parts are required to accomplish this design than the previous one, frequency response is better and the cost is lower.

The complementary output circuit

Figure 4 shows a somewhat more complicated design that requires neither a phase-splitting device nor a transformer. By using one NPN and one PNP device (each the other's complement), push-pull action occurs without any external help. The two transistors are placed in series across the dc power supply. Resistors R3 and R4 provide fuse protection and some amount of thermal stability. R1 and R2 provide base current paths at the proper time.

Diodes D1 and D2 (often part of a single unit) provide bias stability in the following manner. Under normal conditions, the two transistor bases are about 1.2V apart. In an NPN device, the base is normally 0.6V more positive than the emitter, while in a PNP device the base is 0.6V more negative than the emitter. Ignoring the small drop across R3 and R4, the bases should measure normally about

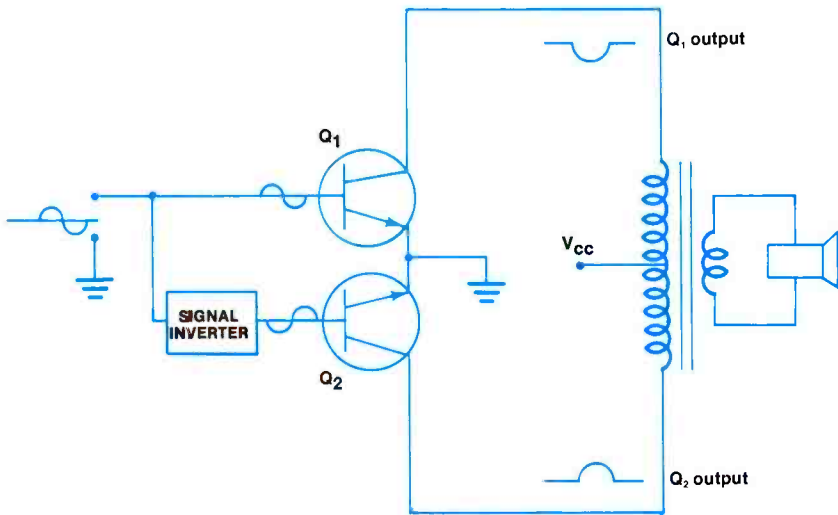


Figure 1. A push-pull output driven by a signal inverting stage.

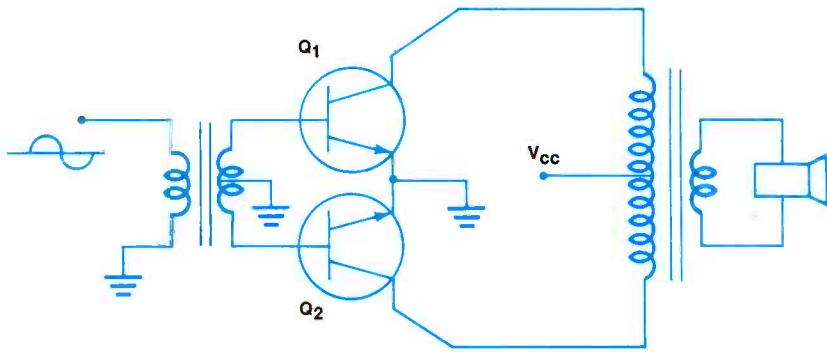


Figure 2. A push-pull output driven by a phase-splitting driver transformer.

1.2V apart constantly because the emitters are essentially tied together.

The diodes are mounted very near the output transistors, often secured to them or mounted on the same heat sink. The temperature response of the diodes is matched to that of the transistors. As the temperature of the devices increases, causing the transistors to increase in conduction, the voltage across the diodes decreases, limiting base current. Therefore, thermal runaway can be controlled.

Avoiding a critical error

A word of caution is necessary at this point. Because the diodes are matched to the output devices, if it is ever necessary to replace the diodes, use only exact replacements. Also, if new output devices are required in circuits like this, it is wise to order the diode unit(s) as well. In the case of a part number or type change when the ordered parts are received, this will ensure that a repair brings the unit back to specs without worry or unnecessary delay. There is nothing more annoying than to install substitute devices with different numbers than the original parts and have the unit fail because the temperature characteristics of the diode are not the same as that of the replacement device.

Obviously, the same caution applies when using general substitutes for original parts. They may or may not work, even if the

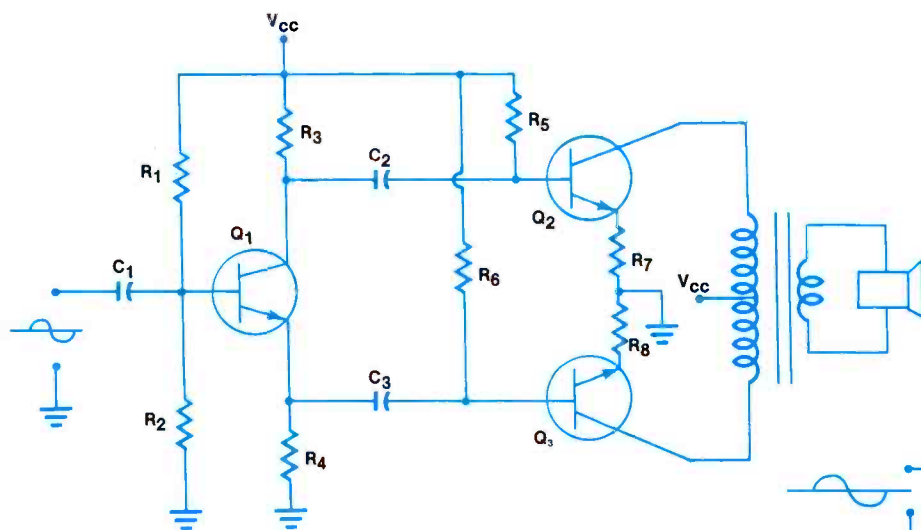


Figure 3. A circuit using a single transistor as a phase splitter.

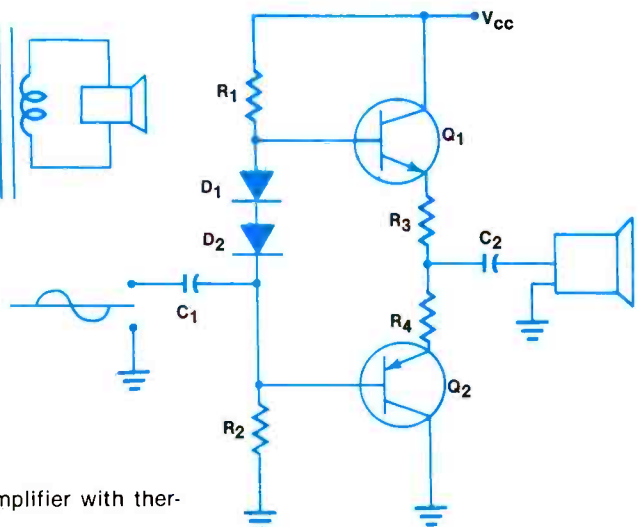


Figure 4. A basic complementary-symmetry amplifier with thermal stabilization.

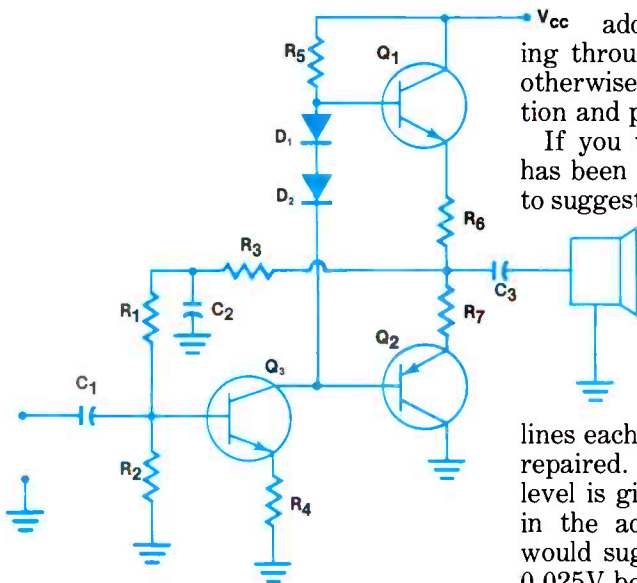


Figure 5. The circuit of Figure 4 preceded by a class-A voltage amplifier.

manual says they will. In general, you will always be better off replacing output devices with exact replacements. The higher the power of the amplifier, the more likely this is to be true. If the amplifier is direct-coupled, this will be crucial in avoiding disaster.

To illustrate this, the service manager of a local branch of a chain stereo store told me that one day a local servicer came in to drop off an amplifier. The servicer complained that the "darn thing just wasn't any good," and was "impossible to fix." He had replaced virtually every transistor in the unit with a well-known general substitute device.

Unfortunately, the amplifier was completely direct coupled. All it took was a little bias shift, and every single substitute device was destroyed. Replacement of the transistors with exact replacements and output current adjustment was all it took to repair the unit.

The analysis continues

Because the output of the circuit in Figure 4 is taken from the emitters, no matching transformer is needed. However, because the design requires that half of the dc supply voltage be dropped across each device, steps must be taken to keep dc out of the speaker. C2 is

added to block dc from passing through the voice coil, which otherwise would cause core saturation and possible coil burnout.

If you work on a speaker that has been burned out, don't forget to suggest to the customer that the amplifier should be checked for possible dc presence. Likewise, it is always necessary to check for presence of excessive dc on speaker lines each time an output circuit is repaired. Usually a maximum dc level is given on the schematic or in the adjustment procedures. I would suggest that no more than 0.025V be present.

Becoming more practical

The circuit of Figure 4 is still not quite practical, but is close. Because Q1 and Q2 are emitter-followers, the output stage has a voltage gain of slightly less than one. It is therefore necessary to provide at least one stage of voltage gain before the output. Figure 5 shows the circuit of Figure 4 redesigned with Q3 added as a pure class-A voltage amplifier. R3 and R1 couple back negative feedback to stabilize the gain of Q3 by monitoring a rise in voltage at

the junction of C3, R6, R7 and R3. The Q3 operating bias is obtained through that same source, while obtaining collector bias from R5, D2 and D1. C2 is provided to eliminate any signal voltage feedback. This circuit is now practical enough to find application in many sorts of products, but it can be refined further.

Disadvantages of coupling capacitors

Coupling capacitors have several undesirable characteristics. They cause phase distortion because they have more reactance at low frequencies than at high frequencies. Coupling capacitors that are used to couple the signal from output devices to speakers while blocking dc must be very large in size (often thousands of microfarads) because of the low impedance nature of output circuits. In order to avoid pronounced phase shift and accompanying voltage-divider action, the capacitive reactance should be no more than 10% of the speaker load resistance at the lowest operating frequency. If such is not the case, loss of bass response is often the result. Physically large capacitors are expensive and limit the overall compactness of the amplifier.

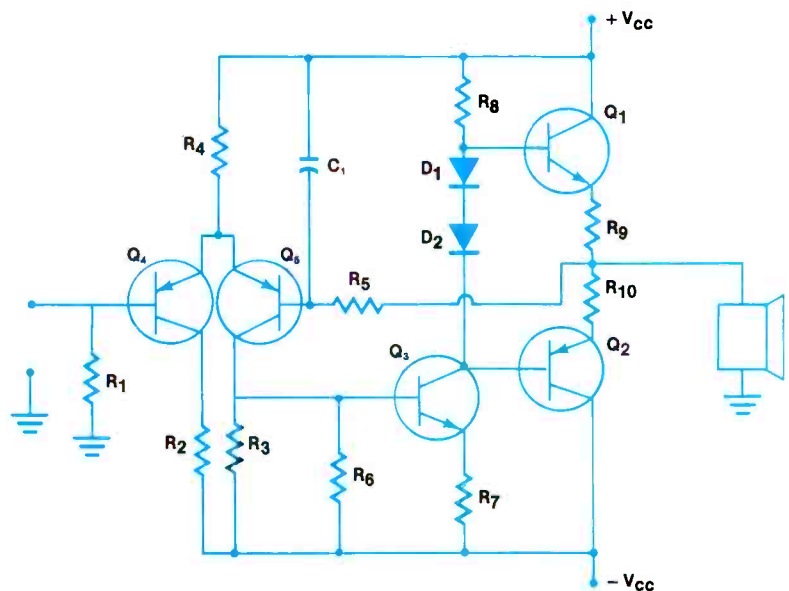


Figure 6. dc-coupled complementary amplifier.

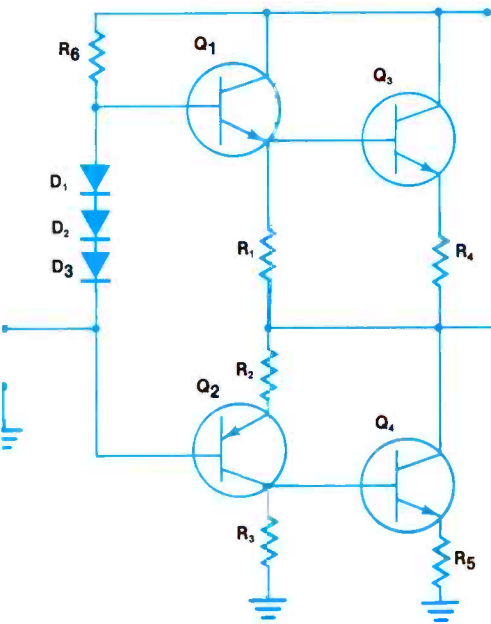


Figure 7. Quasi-complementary symmetry.

A solution to the problems

Figure 6 shows the circuit of Figure 5 modified to eliminate the need for all coupling capacitors. Instead of using one source of Vcc, the original Vcc is divided into two supplies, one negative and one positive. Initial engineering of the output transistor biasing will ensure that the speaker output line will have essentially 0Vdc on it. Transistors Q4 and Q5 are added as a differential pair. As long as the speaker line remains at 0Vdc, Q5 essentially does nothing. If the voltage on the speaker line rises (in either the positive or negative direction), Q5 will change conduction so as to restore balance. R4 serves as a constant current source for Q4 and Q5, allowing this action to occur.

The voltage on the speaker line is referred to as the *offset* voltage. The offset voltage is monitored by the current flowing through R5. The dc levels can then be altered, depending upon the direction of offset shift.

Troubleshooting analysis

As an example, let's examine what would happen if the offset voltage increased negatively. Q5 would turn on harder, its collector voltage would fall, increasing the

drop across R3. The voltage at the base of Q3 would be less negative, turning on Q3 more and lowering its collector voltage. In turn Q1 would turn on harder and Q2 would conduct less, regaining zero offset. In order to analyze the reverse situation, a positive increase in offset voltage, merely change the words in the above analysis. Change up to down, fall to rise, less to more, harder to less hard and lowering to raising. The final result is the same: restoration of zero offset.

Improving damping factor

The application of a concept called *damping factor* is a major concern to users and manufacturers alike. In order for the amplifier to be able to control speaker cone movement, the ratio of speaker impedance to amplifier output resistance must be fairly high. Elimination of the output capacitor improves that ratio as the capacitive reactance increases the output impedance when such a capacitor is used. Because the circuit of Figure 6 accomplishes this task, you will find its application in many high-quality amplifiers. Circuits such as these produce damping factors from 20 to 50 and above.

More power needed

Unfortunately, with few exceptions, complementary NPN-PNP pairs are hard to match for high-power applications. Above 10W or so, NPN power types become expensive, too. Factors like temperature coefficient and beta drift become critical in high-power applications, and slight discrepancies in such characteristics usually result in catastrophic failure. When high power is needed, a complementary pair is often used as a driving stage, while two NPN types are used to actually provide the power. This type of circuitry is commonly called *quasi-complementary symmetry*. Circuits combining the features of both circuits in Figures 6 and 7 are common.

Figure 7 shows a typical, simplified but accurate representation of such an output configuration. When a positive voltage is present

to the base of Q1, increased conduction takes place in both Q1 and Q3. Notice how the collectors of Q1 and Q3 are tied together and that the emitter of Q1 feeds the base of Q3. This is called a Darlington-pair configuration. Sometimes manufacturers provide such a pair in a single conventional 3-lead package. Watch out for this in making substitutions. The net result is that Q1 and Q3 act together to simulate a high-power NPN device.

Similarly Q2 and Q4 are connected to simulate a high-power PNP device. When a negative signal is presented at the base of Q2, it turns on, making the voltage on its collector less positive and causing Q4 to conduct harder.

In order to stabilize the voltage drop between the bases of Q1 and Q2, diodes D1 through D3 are used, often integrated into a single package as previously discussed. Three diodes are needed because there are now three junctions to stabilize (Q1, Q2 and Q3). Resistors R1 through R5 are used to provide thermal stability and fuse protection. They are not always used in such circuits. In all respects, these types of circuits can be analyzed just the same way as the true complementary circuits previously discussed.

A final caution


After the repair of an output circuit of an audio amplifier, it is vitally important to make sure that the cause of failure is not external. Many times output circuits can be blown by shorted speaker wires, an excessive number of speakers being driven by the unit, or by something defective in one of the speakers themselves. Many servicers I know will not warranty an output circuit repair unless the customer brings in the speaker wire and sometimes even the speakers themselves. Doing anything less is taking a gamble.

It is also entirely possible that when the output stage failed, the speaker system was simultaneously damaged. Failure to check out this possibility leaves you open to all kinds of unpleasant possibilities.



Chassis – RCA CTC108
PHOTOFACT – 2030-2


1

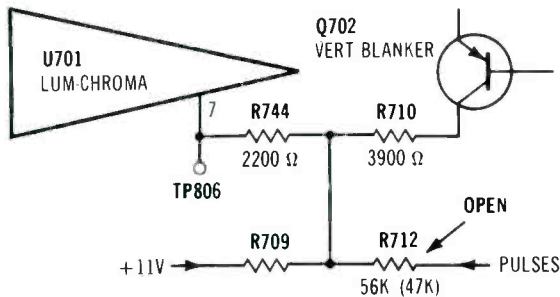

Symptom – Normal sound, but no raster
Cure – Check resistor R712, and replace it if open or increased in value

Chassis – RCA CTC53E
PHOTOFACT – 1201-1 or 1342-2


2

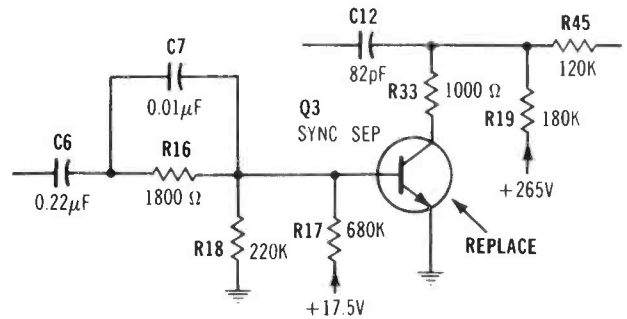

Symptom – Erratic horizontal pulling in picture
Cure – As a test, replace Q3 sync separator

Chassis – RCA CTC76
PHOTOFACT – 1468-2 or 1616-1


3

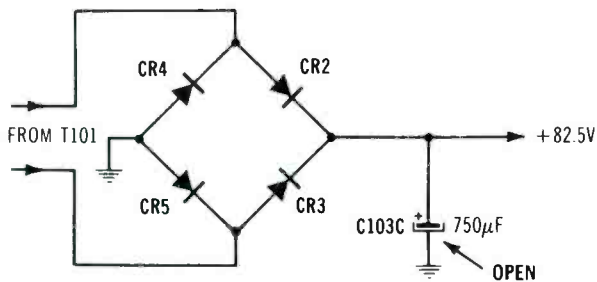

Symptom – Insufficient height at bottom and erratic vertical rolling
Cure – Check filter capacitor C103C, and replace can if any section is open

Chassis – RCA CTC97
PHOTOFACT – 1862-1 or 1931-2


4

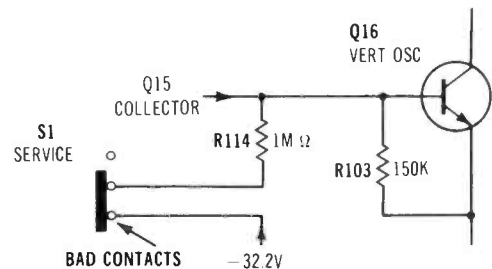

Symptom – Intermittent rolling or loss of height
Cure – Check the service/normal switch, and replace it if contacts are erratic or leaking to ground

Chassis – RCA CTC111
PHOTOFACT – 2038-1


5

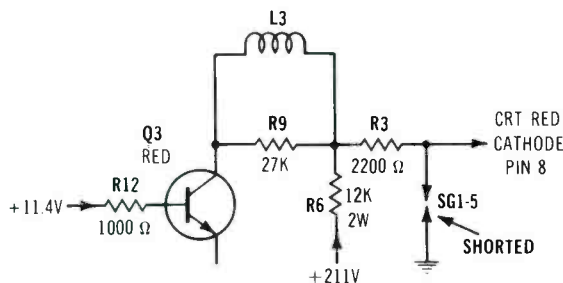

Symptom – Bright red screen with retrace; shut-down after a few seconds
Cure – Check spark-gap SG1-5 on the kine-drive board, and replace it if shorted

Chassis – RCA CTC109
PHOTOFACT – 1952-1


6

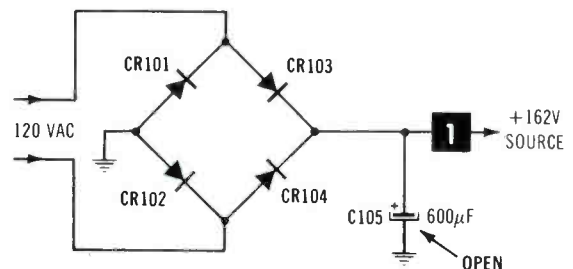

Symptom – Receiver began operating by itself and cannot be switched off, also the picture has an hour-glass shape with ac-hum instability
Cure – Check C105 filter capacitor, and replace it if open

Answers to quiz (from page 48)

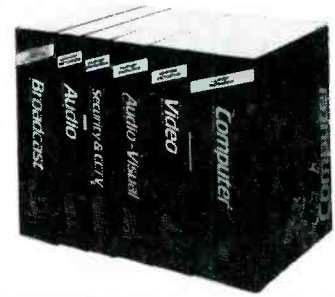1. *C* There is no assurance that the reverse resistances of diodes are equal even though they have the same type number. It is possible that a reverse voltage can be excessive across one of the diodes if its reverse resistance is high compared to the other two. The high-resistance resistors in Figure 1 have identical values and they equalize the reverse voltage drop.
2. *B* If one diode has a forward voltage of 0.7V and the other has a forward voltage of 0.8V, they cannot be connected directly in parallel. The reason is that if the 0.7V diode starts to conduct, the other one will never have enough voltage across it to start it into conduction. The resistors assure that when one diode starts to conduct, the voltage across that branch will be high enough to start the other diode.
3. *D*
4. *E* Discriminator and ratio detectors require tuned transformers.
5. *D* The purpose of this shield is to prevent electrostatic coupling between the primary and secondary.
6. *C* In a few cases this resistor has been used for two purposes. It protects the diode from the surge current that occurs when the capacitors are first charged. At the same time it may be used as a fuse to protect the supply from a constant overload.
7. *A* The output capacitor charges to the peak voltage of the input minus the drops across the filter, diode and surge limiter.
8. *A* Power amplifiers do not require a highly filtered dc voltage. By connecting the power amplifier to point a, it is not necessary to have a high current flowing through the filter resistor.
9. *E* With about 0.7V across each diode, the output voltage will be about 2.1V.
10. *A* The only limit to the secondary current on each half cycle is the forward voltage drops across the diodes.



Professionals, Here are your Black Books

- Over 1500 Manufacturers
- 25,000 Products
- 8½" x 11" Catalog Format
- Perfect Binding for Durability
- Pictures, Descriptions, Features, Options, Specifications, Prices
- Up-to-date as of August 1983

Telephone Orders Accepted With
Purchase Order or Credit Card

Call Toll Free (800) 255-6038

HIGH TECH MARKETING CO.
P.O. Box 2056
Shawnee Mission, KS 66201

Exclusive Distributors for BILL DANIELS CO., INC.

Circle (23) on Reply Card


TOLL FREE ORDERS • 1-800-826-5432
(IN CALIFORNIA: 1-800-258-6666)

AK, HI OR INFORMATION • (213) 380-8000

5 KEY ASSEMBLY
 \$1.00 EACH
CONTAINS 5 SINGLE-POLE NORMALLY OPEN SWITCHES
MEASURES 3 3/4" LONG

6 KEY ASSEMBLY
 \$1.25 EACH
CONTAINS 6 SINGLE-POLE NORMALLY OPEN SWITCHES
MEASURES 4 1/4" LONG

120V INDICATOR
 NEON INDICATOR. RATED 120 V 1/3 W. MOUNTS IN 5/16" HOLE. RED LENS.
75¢ EACH
10 FOR \$7.00
100 FOR \$65.00

MINIATURE 6 VDC RELAY
 SUPER SMALL SPOT RELAY. GOLD COBALT CONTACTS.
RATED 1 AMP AT 30 VDC. HIGHLY SENSITIVE. TTL DIRECT DRIVE POSSIBLE. OPERATES FROM 4.3 TO 6 V. COIL RES 220 OHM.
1 3/16" x 13/32" x 7/16"
AROMAT # RSD-6V
\$1.50 EACH
10 FOR \$13.50

13 VDC RELAY
 CONTACT: S.P.N.C. 10 AMP @ 120 VAC
ENERGIZE COIL TO OPEN CONTACT ...
COIL: 13 VDC 650 OHMS
SPECIAL PRICE \$1.00 EACH

FREE! SEND FOR NEW LARGER 48 PAGE CATALOG

MINIATURE TOGGLE SWITCHES

ALL ARE RATED 5 AMPS @ 125 VAC

S.P.D.T. (on-on) P.C. STYLE, NON-THREADED BUSHING 75¢ EACH 10 FOR \$7.00	S.P.D.T. (on-on) SOLDER LUG TERMINALS \$1.00 EACH 10 FOR \$9.00 100 FOR \$80.00	S.P.D.T. (on-off-on) SOLDER LUG TERMINALS \$1.00 EACH 10 FOR \$9.00 100 FOR \$80.00
S.P.D.T. (on-off-on) NON-THREADED BUSHING P.C. STYLE 75¢ EACH 10 FOR \$7.00	S.P.D.T. (on-on) P.C. LUGS, THREADED BUSHING \$1.00 EACH 10 FOR \$9.00 100 FOR \$80.00	D.P.D.T. (on-on) SOLDER LUG TERMINALS \$2.00 EACH 10 FOR \$19.00 100 FOR \$180.00

ALL ELECTRONICS CORP.
ALL ELECTRONICS CORP.

905 S. VERMONT • P.O. BOX 20406 • LOS ANGELES, CA 90006

• QUANTITIES LIMITED • FOREIGN ORDERS: INCLUDE SUFFICIENT SHIPPING
• USA: \$2.50 SHIPPING • CALIF. RES. ADD 6 1/2%
NO C.O.D.'s

Circle (25) on Reply Card

ARTICLE REPRINTS

Interested in reprints of an article out of this or another issue? Reprints of articles about your company or the industry can be valuable sales and marketing tools. For information, call or write Robyn Kahn, Intertec Publishing Corp., P.O. Box 12901, Overland Park, Kansas 66212; (913) 888-4664.

ATTENTION TECHNICIANS

- ★ JOB OPENINGS
- ★ MONTHLY TECHNICAL TRAINING PROGRAM
- ★ BUSINESS MANAGEMENT TRAINING
- ★ LOW COST INSURANCE
- ★ CERTIFICATION
- ★ TECHNICAL SEMINARS

All of this in a nonprofit international association for technicians

FIND OUT MORE:



R.R. 3 Box 564
Greencastle, IN 46135



SINCE 1950


- LEADING SPOKESMAN
- TRADE INFORMATION DISPENSER
- WATCHDOG
- NATESA SCOPE
- STANDARDS YARDSTICK
- CONSUMER RELATIONS
- PROBLEM SOLVER
- CONCISE PRACTICAL BUSINESS OPERATIONS MANUAL
- SERVICE CONTRACT MANUAL
- CUSTOMER PLEASING PROFIT PRODUCING ORDER FORMS
- PARTS PROCUREMENT EXPEDITOR
- SERVICE BUSINESS
- DIVERSIFICATION PLANS
- TECHNICIAN DEVELOPER

5930 So. Pulaski Rd. • Chicago, Illinois 60629

Products

Powered solder cleaner

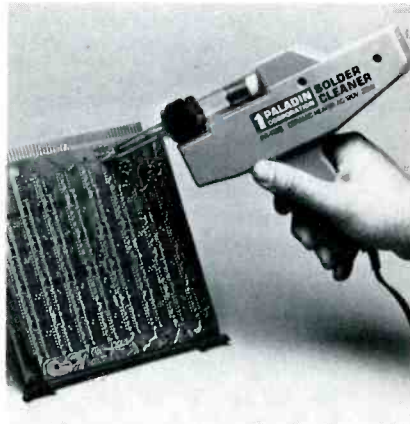The *Paladin* PA 1715 is the result of a technology that puts electric power desoldering within reach of small electronic assembly and service operations. Unique features include a virtually




maintenance-free ceramic substrate heating element, and iron and chrome-dipped tip that outlasts ordinary tips five to one. The straight-duct designed solder-collector cartridge prevents solder from clogging, sticking or interfering with the vacuum pump.

Circle (133) on Reply Card

Logic probe tester

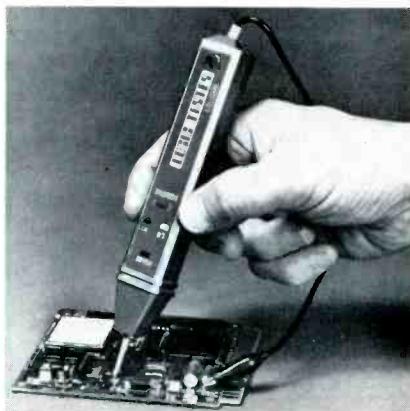Logic Probe Tester LG1000 by *Vaco Products* simplifies the task



of servicing logic circuits by instantly detecting faulty circuits so repairs can be initiated. It has a built-in power supply, making an external power cord unnecessary. A power-on-demand switching system permits power to be turned on automatically only while the probe is being used, for the ultimate in cost-effective operation. This tester is sensitive to minus voltage and features a negative voltage indicator.

Circle (85) on Reply Card

VCR battery packs

LCOMP, a distributor of electronic equipment, now offers sealed, rechargeable lead-acid battery packs for portable VCR equipment. Made by Gates Energy Products and assembled by LCOMP, the battery packs can be used for replacement or spares for original factory equipment.

The 12V, 2.5Ah, sealed batteries come in three configurations: 0810-0177 for Sony BP20, 0810-0178 for JVC PBP-1, and 0810-0179 for Sony BP60 systems. Other configurations are available for other portable videotape systems from LCOMP.

Circle (130) on Reply Card

Electronic grade coolant

An electronic circuit/component coolant to aid in servicing video games and vending machines has been introduced by *Chemtronics*. The coolant, named *Freez-It*, is designed to make thermal intermittent troubleshooting of circuit boards and electronic components easier. Applied as an aerosol spray, *Freez-It* will freeze to -65°F . Rapid chilling of suspected components allows individual components to be isolated for instrument testing.




Freez-It coolant also can be used to prevent transformer burnout. Other uses include low-temperature testing of circuits and equipment, preventing cold solder joints, soldering delicate, heat-sensitive components and aiding in shrink-fit assembly

Circle (79) on Reply Card

Microcircuit soldering kit

A kit including soldering iron, tips and holder, from *Ungar*, is designed for precision microelectronic soldering.

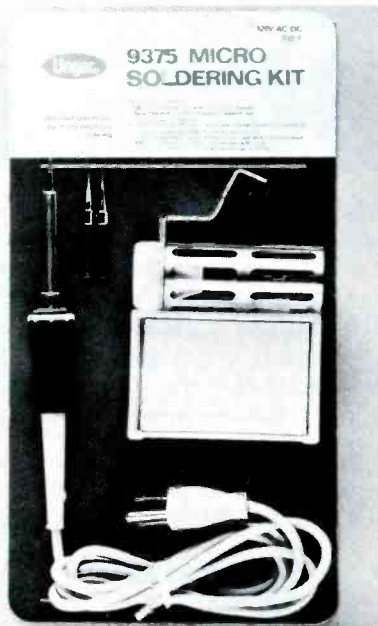The 9375 Micro-Soldering Kit includes a 3-wire handle that is slimmer than earlier models to facilitate close-tolerance soldering, a ThermoDuric heating element, tips of three different configurations and a holder assembly.



Thermo-Duric heating elements reach temperature and recover quickly, and eliminate electric leakage, which could ruin microcircuits. The three precision tips supplied in the kit are a needle point (0.005in. diameter at the point), a 0.03in-wide spade point and a 0.06in-wide screwdriver. Nine other tips are available.

Circle (87) on Reply Card

Aerosol flux remover

Developed for electronic production, re-work and repair, *Chemtronics'* new aerosol flux remover

speeds the removal of activated and non-activated rosin flux and ionic soils from electronic sub-assemblies, printed circuit boards, switches, connectors and semiconductors, silicone wafers and other electronic components.

Flux-Off, a highly concentrated CO₂ propelled solvent, removes tough deposits without harm to delicate components. It will also effectively remove other contaminants such as dirt, grease and molding compounds without leaving a white residue.

Circle (75) on Reply Card

Floppy disc drive maintenance

Dumont Magnetic Technology has announced third-party maintenance, repair and refurbishment service on floppy disc drives. Nearly every variety of floppy disc drive from companies such as Shugart, Tandon, MPI and Qume can be repaired and refurbished to the companies specifications. In addition to complete drive service, Dumont has a head repair facility and can repair most heads without additional cost.


Circle (76) on Reply Card

Capacitance meter

The 3002 autoranging capacitance meter, from *Global Specialties*, combines the precision, range and flexibility of bench-top models with the convenience and operating efficiency of a hand-held, portable unit. This meter provides direct readings of capacitance from 1pF to 19,990 μ F with eight automatically selected ranges providing accurate measurements of capacitance without manual switching.

The dual-threshold measurement technique eliminates reading errors due to dielectric absorption. By using dc charging characteris-

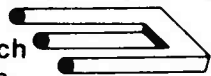It's no puzzle to order Oelrich Service Forms



For TV-radio and two-way radio service — legal forms for Calif., Florida and Utah. Now at parts jobbers or write for cat. B64.

OELRICH PUBLICATIONS

4040 N. Nashville Ave., Chicago, IL 60634
Now call toll-free! 800-621-0105

Circle (24) on Reply Card

PREVENT HI-TECH HEADACHES

Our Isolators eliminate equipment interaction.



clean up interference, curb damaging power line spikes and lightning bursts.

ISO-1 Isolator

3 isolated sockets; quality spike suppression; basic protection. . . \$76.95

ISO-3 Super-Isolator

3 dual isolated sockets; suppressor; commercial protection. 115.95

ISO-17 Magnum Isolator

4 quad isolated sockets; suppressor; laboratory grade protection. . . 200.95

ESP Electronic Specialists, Inc.

171 S. Main St., Box 389, Natick, MA 01760

Toll Free Order Desk 1-800-225-4876
MasterCard, VISA, American Express

Circle (26) on Reply Card

UNIVERSAL CRT ADAPTER

- Works with **All** color CRT testers
- Checks virtually **Every** color CRT
- Money-back guarantee
- Test/Restore/Rejuvenate
- Distributors inquiries welcome
- \$59.95 & \$2.00 shipping & handling

Master Card/Visa Accepted

CA28 3 Piece Adapter Kit

Set-up manual included

Dandy Manufacturing Co.


1313 N Main St,
Muskogee, OK 74401
918 682-4286

Call Toll Free
1-800-331-9658

Circle (27) on Reply Card

Marketplace

1983 I.C. MASTER 2-VOLUME EDITION

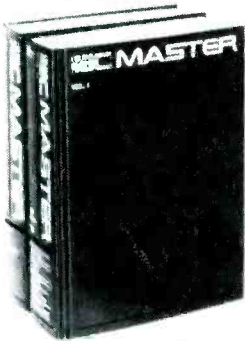

The only publication with the answers to your questions on integrated circuit and microcomputer board selection

55,000 entries in the world's most comprehensive function-for-function, pin-for-pin I.C. replacement guide.

3500 pages organized by function, type, and key parameters to make finding the device which best satisfies a need fast and easy.

For a FREE 6 page brochure about the I.C. Master, call, write or circle reply card.


Active Electronics

P.O. Box 8000
Westboro, Mass. 01581

Toll Free: 1-800-343-0874
Mass. Call: (617) 366-0500

Circle (28) on Reply Card

ATTENTION ELECTRONIC TECHNICIANS



Highly Effective Home Study BSEE Degree Program for Experienced Electronic Technicians. Our New Advanced Placement Program grants Credit for previous Schooling & Professional Experience. Advance Rapidly! Our 36th Year!

FREE DESCRIPTIVE LITERATURE!

Cook's Institute of Electronics Engineering
DESK 15, P.O. BOX 20345, JACKSON, MS 39209

Circle (29) on Reply Card

FREE CATALOG
HARD-TO-FIND PRECISION TOOLS



Lists more than 2000 items: pliers, tweezers, wire strippers, vacuum systems, relay tools, optical equipment, tool kits and cases. Send for your free copy today!

JENSEN TOOLS INC.
7815 S 46TH STREET PHOENIX AZ 85040

Circle (30) on Reply Card

FREE KIT Catalog

Test Equipment-Kit or Assembled FUNCTION GENERATOR Kit \$59.95
Auto-Ranging Cap-meter kit \$79.95

Phone 209-772-2076

Circle number or phone for catalog.

DAGE SCIENTIFIC INSTRUMENTS
BOX 144 VALLEY SPRINGS CA 95252

contains TEST & EXPERIMENTER'S EQUIP.

Circle (31) on Reply Card

SATELLITE TV VIEWERS
Get the most complete weekly listings.
Send \$1 for sample copy.

Satellite TV Week

P.O. Box 308, Fortuna, California 95540
800-358-9997 (U.S.) • 800-356-8787 (Calif.)
707-725-2476 (all others)


Circle (32) on Reply Card

tics to determine true capacitance, the 3002 can determine capacitance in cable, switches and other electronic components and hardware in addition to capacitors and capacitor networks.

Circle (84) on Reply Card

Digital storage oscilloscope

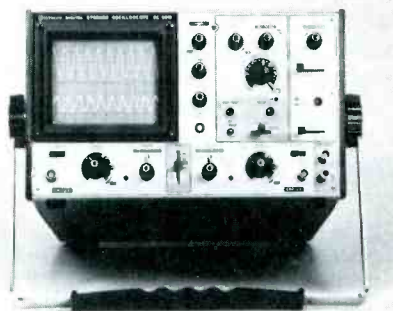Hitachi's VC-6015 digital storage scope features a memory capacity of 1000 words per channel with a writing speed of 1 μ s per word to 1ms per word. The VC-6015 has a pretrigger function that enables the capture of an event before the trigger pulse oc-




curs, a feat that up to now was impossible with conventional CRT-storage type scopes. The pretrigger position may be set at 0, 2, 5 or 8 divisions, and the trigger point is displayed on the CRT as an intensified point, allowing the user to determine its relationship to the captured waveform.

Circle (78) on Reply Card

Signal generators

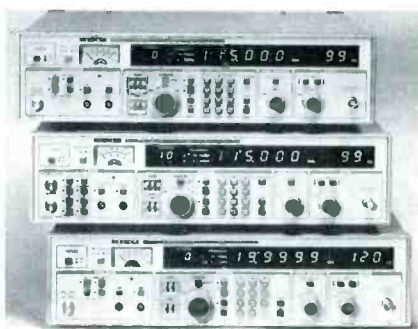Leader Instruments has introduced three new programmable synthesized AM/FM RF signal generators. The new series of generators features convenient keyboard control of frequency and output level. Semi-automatic



Circle (85) on Reply Card

operation is available by pre-programming up to 100 different test conditions.

The LSG-217 offers an output frequency range of 0 to 70MHz in two bands, 0.1 to 19.9999MHz in 100Hz steps and 20 to 70MHz in 1kHz steps. Output level range is 0 to 120dB μ V in 1dB steps.

Circle (81) on Reply Card

Portable light

Headlights, from *Brighteyes of California*, are a self-contained, portable light source for the repairman or inspector. They direct bright light where you look while leaving both hands free for tools, writing or adjusting. They light



when you put them on, and there are no switches, cords or battery packs to snag or break. Headlights are designed to be worn comfortably with or without glasses, and allow you to get as close to the work as you wish.

Circle (80) on Reply Card

Digital multimeter


A new, 3 $\frac{1}{2}$ -digit auto-manual ranging hand-held digital multimeter with 0.7% dc accuracy, overload and transient protection, high energy fuse, diode test and audible continuity check is available from the B&K-Precision Test Instrument Product Group of Dynascan Corporation.

Model 2806 features auto-ranging or step-through manual ranging for all voltage and ohm measurements, and manual ranging on amp measurements. The dc voltage ranges are 200mV, 2000mV, 20V, 200V and 1000V, and the ac voltage ranges are 200mV, 20V, 200V and 750V.

B&K

Literature

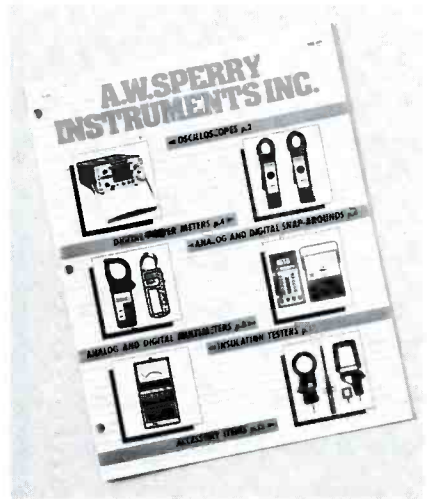A. W. Sperry Instruments has released a new full-line catalog, MC-499 Issue A. The catalog features the entire AWS line of test equipment including



oscilloscopes, analog and digital snap-arounds, analog and digital multimeters, power meters, insulation testers, indicating devices and accessory items.

Circle (100) on Reply Card


Etco Electronics has released a new 112-page catalog featuring thousands of items from the fields of electronics, communications, telephone, cable TV and video, in addition to a complete parts selection for the hobbyist or repair shop.

A 16-page section of the catalog has been devoted to telephone and related equipment for small systems applications as well as for the home user. Simple systems that can be user-installed are shown.

Circle (105) on Reply Card

The new 96-page Fall/Winter Catalog is now available from Misco. The catalog offers more

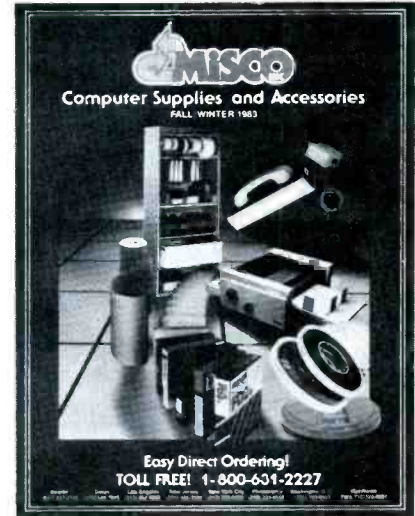than 200 new items and contains three new product section categories. All products are available for immediate shipment by phone or upon written order. The company offers supplies and accessories for computer and word processors, in-



cluding a complete line of Clean Room cleaning and decontamination products.

Circle (101) on Reply Card


FORDHAM DISCOUNTS DISCOUNT PRICES ON HITACHI SCOPES

SPECIAL OFFER!
For a limited time only

35 MHz DUAL TRACE SIGNAL DELAY LINE

Vertical sensitivity 5m V/div to 5V/div and 1m V/div to 1 V/div with 5X amplifier • Trigger modes Automatic, Normal, TV (+), TV(-)

REG \$895
OUR PRICE
\$599⁹⁵
WITH PROBES

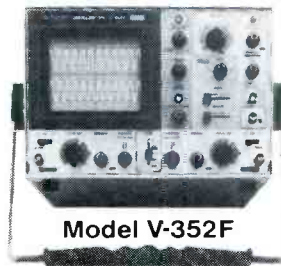

Model V-352F

60 MHz DUAL TRACE DELAYED SWEEP

High sensitivity • 1 mV/div (10 MHz) • 5 ns/div sweep rate
• 3rd channel display (trigger view) • Variable trigger hold-off
• Full TV triggering • Single sweep • Automatic focus correction.

OUR PRICE
\$995
WITH PROBES




Model 650F

100 MHz QUAD TRACE DELAYED SWEEP

Large, bright 8x10 cm screen
• Quad trace operation/Ch1, Ch2. A trigger and B trigger • High sensitivity 500 μ V/div (5 MHz)
• Full TV triggering.

OUR PRICE
\$1590
WITH PROBES

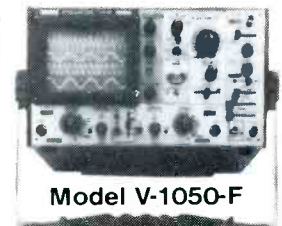

Model V-1050-F

TOLL FREE (800) 645-9518

FORDHAM



260 Motor Parkway, Hauppauge, N.Y. 11788

in N.Y. State 800-832-1446

■ VISA ■ COD ■ Master Charge
■ Money Order N.Y. State residents add appropriate sales tax.
■ Check
COD's extra (required 25% deposit)

ADD FOR SHIPPING AND INSURANCE

\$250.00	\$4.50
\$251.00 to 500.00	6.50
501.00 to 750.00	8.50
751.00 to 1000.00	12.50
over 1000.00	15.00


Circle (33) on Reply Card

Opportunity knocks.

The professional world of the Electronics Service Dealer is rough. That's why we're working so hard to make it easier for you to operate a cost effective business. NESDA offers substantial savings on bank-card and insurance rates, business contacts, technical and management certification, and that's just the beginning.

Our members are kept informed about industry developments, and are offered the most comprehensive managerial and technical training programs available. Opportunity knocks. Don't let it pass you by.

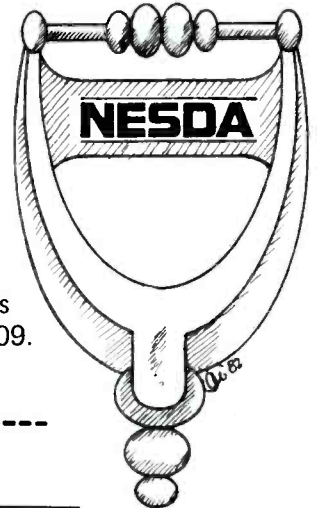For more information about the National Electronics Service Dealers Association, write to: NESDA, 2708 W. Berry St., Ft. Worth, TX 76109.




NAME _____

FIRM NAME _____

FIRM ADDRESS _____ Member of State Local Assn.

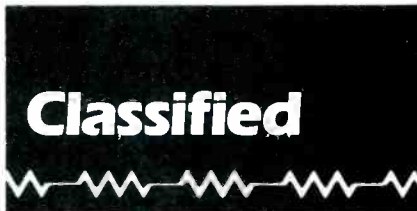CITY _____ STATE _____ ZIP _____ PHONE _____



Advertising rates in the Classified Section are 50 cents per word, each insertion, and must be accompanied by payment to insure publication.

Each initial or abbreviation counts a full word.

Minimum classified charge \$10.00.

For ads on which replies are sent to us for forwarding (blind ads), there is an additional charge of \$3.00 per insertion to cover department number, processing of replies, and mailing costs.

Classified columns are not open to advertising of any products regularly produced by manufacturers unless used and no longer owned by the manufacturer or distributor.

FOR SALE

SCRAMBLED TELEVISION, encoding/decoding. New book. Theory/circuits, \$9.95 plus \$1 shipping. Workshop, Box 393ES, Dept. E, Bethpage, NY 11714. 7-80-tfn

TUBES FOR TV AND RADIO—35c ea. Washington TV Service, 1330 E. Florence Ave., Los Angeles, CA 90001. 1-83-121

CABLE TV CONVERTER/DECODER. LOWEST PRICE ANYWHERE. Oak N-12 or Jerrold SB-3 replacement \$79.00, Combo with 35 channel converter \$139.00, Jerrold DRX-3DIC with remote \$179.00. Send \$2.00 with order or for catalog, refundable with your order to: CK Electronics, 397 Route 18 East, Suite 377, East Brunswick, NJ 08816, 201-739-2671. 10-83-21

COMPLETE JERROLD WIRELESS REMOTE/DE-SCRAMBLER—full warranty, \$159.00. Complete Oak descramblers, full warranty, \$169. Trap/filters in line type, \$49, 2 min. installation, SG613 transistors, only \$6.99. Original Toshiba 2SC1172B, only \$1.99 with hardware. 100/450, 80/480, 200/300, 40/450, 25 1st only \$1 each mixed or single lot. Super special while they last 800-860 41 each safety caps Zenith type, 10 lot only \$2.50. Bulk 2SC1172B only 50 lot, \$1.69. Redcoat Electronics, 104-20—68th Drive, Forest Hills, NY 11374, (212) 459-5088. 5-83-tfn

CABLE CONVERTERS, DECODERS. Free catalog! APS, POB 263, Newport, RI 02840. 6-83-121

SUBSCRIPTION TV MANUAL, covers all three major scrambling systems, only \$12.95. includes theory, circuits., waveforms and trouble shooting hints. Save your VIDEO GAME CARTRIDGES on EPROM with our EPROM duplicator. Plans \$9.95. Catalogue \$2.00, refundable. RANDOM ACCESS, Box 41770A, Phoenix, AZ 85080. 8-83-tfn

2SC1172B's, 50 LOTS—\$1.69; 2SC1308K's, original Sanyos, 50 lots—\$1.99; Cheater cords, 25 lots—35c; pol- and non-polarized. 1,000 ft. reels of RG 59 U. Coax Cable—\$39/roll. Minimum order \$75. Redcoat Electronics, 104-20 68th Drive, Forest Hills, NY 11375, 212-459-5088. 10-82-tfn

ELECTRONIC SURPLUS: CLOSEOUTS, LIQUIDATIONS! Parts, equipment stereo, industrial educational. Amazing values! Fascinating items unavailable in stores or catalogs anywhere. Unusual FREE catalog ETCO-011, Box 762, Plattsburgh, NY 12901. 6-78-tfn

SPRING SPECIALS on Popular Electrolytics—40/450V—75c; 80/450V—85c; 100/450V—95c 200/300V—\$1.05. Quantity 20 lot only. Minimum order of \$50. SUPER SPECIALS. Bulk Zenith safety capacitors 800-860, 12 lot only \$2.50 each. REDCOAT ELECTRONICS, 104-20 68th Drive, Forest Hills, NY 11375, 212-459-5088. 10-82-tfn

REPLACEMENT COLOR YOKES-DEALERS ONLY. Zenith 95-2501-2532-2887 etc. \$22.95. Magnavox 361380-1 etc. \$24.95. Sylvania \$24.95. American-made fuses in bulk-example 3AG 2 regular price .23 each our price .12 each. Factory packaged GE transistors at discounts. Example GE-20 regular price \$1.10 our price .65. Request circular on your letterhead. David Sims Enterprises, Inc., 665 East Jericho Tpke., Huntington Sta., NY 11746, 800-645-5030, NY State (516) 549-3925-1592. 10-82-tfn

TUBES—Receiving, Industrial and Semi-conductors, factory boxed. Free price list. Low; low prices. **TRANSELETRONIC INC.**, 1365-39th Street, Brooklyn, NY 11218E, 800-221-5802, 212-633-2800. 5-82-tfn

TV TROUBLE ANALYSIS TIPS. Over 300 symptoms/ remedies by circuit area; tough ones over the years. Save time and money. Send \$12.50 to CHAN TV, 8151 Grandview Rd., Chanhassen, MN 55317, 5-82-tfn

PRINTED CIRCUIT boards from your sketch or artwork. Affordable prices. Also fun kit projects. Free details. **DANOCINTHS INC.** Dept. ES, Box 261, Westland, MI 48185. 5-81-tfn

SONY-PANASONIC-RCA-ZENITH-EXACT REPLACEMENT PARTS-LARGE INVENTORIES-SEND PART OR MODEL NUMBERS-WILL UPS OR COD-GREEN TELE-RADIO DISTRIBUTORS, 172 SUNRISE HIGHWAY, ROCKVILLE CENTRE, NY 11570. 5-82-tfn

AUTOMOBILE RADIO and tape replacement parts: Delco, Chrysler, Philco-Ford, Motorola, Panasonic and many others. Large inventory. Laran Electronics, Inc., 3768 Boston Road, Bronx, NY 10469. (212) 881-9600, out of New York State (800) 223-8314. 5-79-tfn

COLOR PICTURE TUBES direct from manufacturer. Prices from \$55 to \$75 exchange. One year warranty. Send your old tube ups to ATOLL Color Tubes, 6425 West Irving Park, Chicago, Illinois 60634. Phone: 312-545-6667. We also sell equipment for rebuilding CRT's. 9-83-31

FOR SALE (CONT.)

ATTENTION TECH/SHOP OWNERS—Profits getting smaller with increasing cost of parts? Take advantage of our buying power and huge inventory on well known electronic c products and replacement parts. Prices below dealer cost. Write for information. United Services Assoc., Old Grand Union Shopping Ctr., Rt. 9W, Stony Point, N.Y. 10980, 914-942-2173. 7-83-tfn

CB RADIO BOOKS, kits, modifications. Catalog \$1.00 refundable. APS, POB 263, Newport, RI 02840. 6-83-12T

SOUTHERN CALIFORNIA SALES AND SERVICE OPERATION available; Over 2 million gross 1982; Thirteen years in area with excellent growth and high visibility. Audio/Video Sales and Servicenter, 26837 Bouquet Canyon Road, Saugus, California 91350, 805-255-5562. 9-83-3T

ADVENT VIDEO PARTS and service available from professional electronics. Call 504-467-1717 for further information. 9-83-3T

FOR SALE: SAMS 900 to 1695, total 300, price \$450. CEC P.O. BOX 383, Bellflower, CA 90706. 11-83-1T

RETIRED: Sell or Trade entire inventory TV parts, Modules, Test Equipment, Sams, RCA & Zenith prints. Cost over \$19,000, sell \$9,500. A. Hudson, 935 Center Ave., Red Bluff, CA 96080 (916) 529-0350. 11-83-1T

COMPLETE SERVICE SHOP. Parts, Sams, Test equipment, tools, fixtures for TV, stereo, CB and Radio Service. A turnkey operation, except for van and building. (704) 729-5983 after 6 pm. 11-83-1T

INDIVIDUAL PHOTOFACT FOLDERS (not sets) under #1200. First class postpaid \$3.00. Loeb, 414 Chestnut Lane, East Meadow, NY 11554. 11-83-3T

WANTED

WANTED FOR CASH: 50, 53, 6AF6, 6HU8, 304TL, 4CX1000A, 4-1000A, all transmitting, special purpose tubes of Eimac/Varian. DCO, Inc., 10 Schuyler Avenue, North Arlington, New Jersey 07032. Toll Free (800) 526-1270. 5-82-tfn

PHOTOFACTS WANTED. Numbers 900 to 1100. LB Television, 326 Kingston Avenue, Brooklyn, NY 11213. 11-83-1T

TELEVISION SERVICE SHOP in Florida or California. Call or write ATOLL TV, 6425 West Irving Park, Chicago, IL 60634; Ph. 312-545-6667. 11-83-3T

BUSINESS OPPORTUNITIES

NORWALK, CALIFORNIA ESTABLISHED TV AND STEREO SERVICE AND SALES very busy money maker, excellent location, low rent, very good lease, 2300 square feet, 10 minutes to beaches and Los Angeles. \$40,000 includes inventory, large enough for living quarters, owner retiring, phone 213-863-1919. 11-82-tfn

SPEAKER RECONING: Most makes, sizes, models. For prompt service send to Mercury Speaker Reconing, 2018 W. Division St., Chicago, Illinois, 60622; (312) 278-2211. 9-83-tfn

COLORADO'S WESTERN SLOPE BECKONS: Established R.V. Repair and Sales business. Good lease, good terms. Century 21-Old Homestead, John McDermott, 737 Horizon Drive, Grand Junction, Colo. 81501 or call (303) 243-5100. 10-83-2T

RESIDENTIAL SECURITY ALARM sales are exploding and the Rampart Associate Program offers you ENORMOUS PROFIT POTENTIAL PLUS EXCITING RESIDUAL INCOME. Rampart's success and reputation are a result of a total business format approach for the residential, small commercial market and its new low cost system, the Rampart REACTOR, with central station monitoring. We provide product, marketing and management training with complete backup. Start part time, full time. No experience necessary; just a strong desire to succeed and help your customers. Investment only \$2,850. With only 6% of the market penetrated, now's the time to get yourself started in what Time Magazine calls the "runaway growth industry." Call Mr. Roberts 1-800-823-8002 or write, Rampart Ind. Inc. One Oxford Valley, Langhorne, PA 19047. 11-83-tfn

BUSINESS OPPORTUNITIES

LEARN TO REPAIR HOME VIDEO GAMES IN YOUR OWN SHOP! Did you know that more than 9 million HOME VIDEO games have been sold? Now you can learn to repair! Atari, Coleco, Intellivision, or Atari 400/800 computers in your own shop. Our courses are taught on VIDEO TAPE (Beta or VHS) and come with a manual containing all the necessary technical information you will need to do repairs. For more information or to order, call: Electronic Institute (800) 221-0834 (outside N.Y.) or (212) 377-0369 (in N.Y.) Customized live in shop training courses are also available, call for more information and price schedules. 7-83-tfn

10 YEAR ESTABLISHED TV SALES and SERVICE BUSINESS (service equipment included) with TV rental business in same building. Excellent downtown location with 2000 sq. ft. floor space, side service entrance, new parking lot being built. Owner will help finance and assist initial operation of store. Call 207-696-4242. 11-83-1T

TV TUNER REBUILDING BUSINESS, LOS ANGELES, CALIFORNIA 23 years same location, other interests, requires sale very reasonable, (213) 342-4745. 7-83-tfn

TELEVISION SHOP LIQUIDATION: All parts, shop and office equipment for sale. Send "stamped envelope" for parts lists. Samar TV, 8 Dusk Dr., Centereach, NY 11720. 11-83-1T

HELP WANTED

SR. VIDEO TECHNICIAN

Pentax Corporation, headquartered in Denver, has an employment opportunity for a Sr. Video Technician. This senior position includes actual hands-on servicing of various video products and electronic survey instruments. Also will include control of service production, providing work direction and training technicians plus performing administrative duties.

This opportunity requires extensive electronics experience (3-6 yrs.) with previous video servicing experience desirable. Formal electronics training is required plus experience in administrative processes. The position also requires good communications skills for customer service.

If you are interested in this challenging opportunity, a competitive salary and benefit package, please call for additional information or send resume to:

PENTAX®

PENTAX CORPORATION
35 Inverness Drive East
Englewood, CO 80112
(303) 799-5212

Equal Opportunity Employer

Everyone benefits...
pricing by "The Book"
1-800-228-4338
MON.-THRU FRI 8-5 / C.S.T.

Circle (35) on Reply Card

Advertisers' Index

Reader Service Number		Page Number
28	Active Electronics	60
25	All Electronics Corp.	57
21	Automated Production Equipment	49
18	B&K Precision	45
15	Chemtronics, Inc.	39
16	Components Express, Inc.	41
34	Consolidated Electronics, Inc.	64
29	Cook's Institute of Electronics Engineering	60
7	The Cooper Group	9
31	Dage Scientific Instruments	60
27	Dandy Manufacturing Co.	59
19	Digitron Electronics Corp.	47
	ETA	58
26	Electronic Specialists, Inc.	59
5	John Fluke Mfg. Co., Inc.	5
33	Fordham Radio Supply	61
	General Electric Co. Television	37
23	High Tech Marketing Co.	57
30	Jensen Tools, Inc.	60
4	MCM Electronics	1
	NATESA	58
	NESDA	62
11	North American Philips	19
24	Oelrich Publications	59
12	Omnitron Electronics	21
20	Optima Electronics	47
36	ORA Electronics	43
1	PTS Corp.	IFC
	Philips ECG	17
22	Primefax	49
17	Projector-Recorder Belt Corp.	41
	RCA Distributor & Special Products Div.	7,27
9	Howard W. Sams & Co.	13
32	Satellite TV Week	60
2,3	Sencore	BC
37	Simpson Electric Co.	23
14	Soltec Corp.	28
10	Sony Corp. of America	15
13	A.W. Sperry Instruments, Inc.	25
35	Sperry Tech, Inc.	63
	TCC/New-Tone Electronics, Inc.	26
8	Winegard Co.	11
	Zenith Radio Corp.	IBC

CEI SPECIALS CEI

REPLACEMENT FOR
ADC QLM 30MK III
MAGNETIC CARTRIDGE

PART NO.
CE-487



\$4.95

CEI-123 AP
TRANSISTOR



9¢



FREE
SHIPPING
& HANDLING

*If order is 5 lbs. or less, good only in the continental U.S. with purchase of \$75 or more.

CALL
TOLL
FREE!

FREE
T-SHIRT

*With order of \$75 or more

2SD 712
 SIMILAR TO ECG® 152




39¢

2SC1172B
HORIZONTAL OUTPUT
TRANSISTOR
 SIMILAR TO
 ECG® 238



\$1.95

2SB 682
 SIMILAR TO ECG® 153

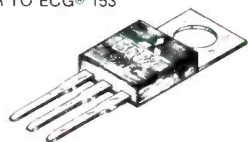

45¢

1-800-543-3568
 NATIONAL WATS

705 WATERVLIET AVE.,
 DAYTON, OHIO 45420
SORRY, NO MIXED QUANTITIES
 MINIMUM ORDER \$10



Consolidated Electronics,
Incorporated

Circle (34) on Reply Card


1-800-762-3412
 OHIO WATS

IN DAYTON, OHIO
 CALL 252-5662

* THESE ITEMS ARE FOR 10 OR MORE

Don't touch that connection!

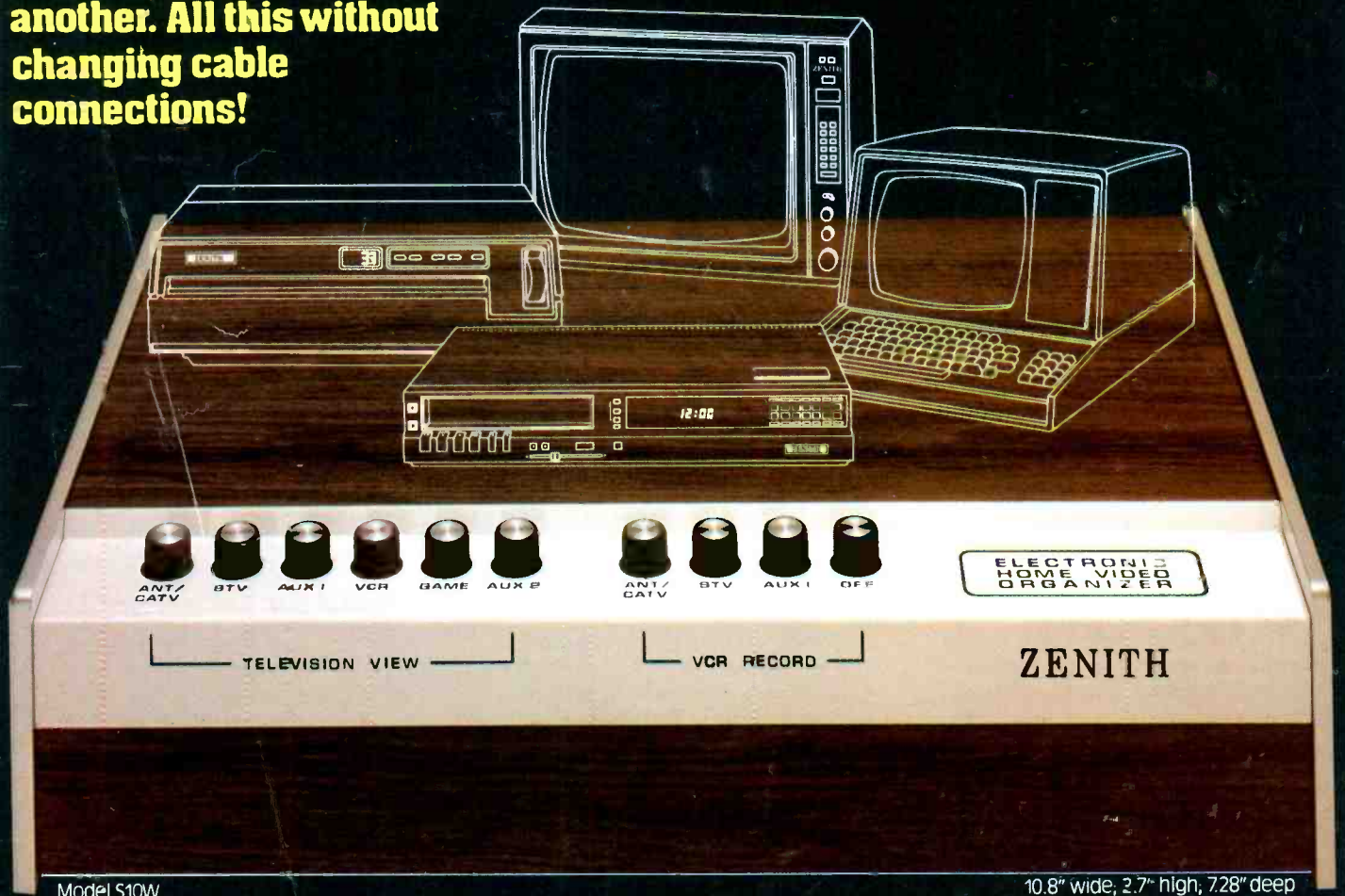New Zenith push-button VIDEO ORGANIZER permits switching from one program source to another without changing cable connectors. Permits selection of up to six different program sources for viewing. Up to three different sources for recording. Even lets viewer watch one program source while recording another. All this without changing cable connections!



At last the nuisance of changing cable connections by hand is a thing of the past!

With Zenith's new Video Organizer, separate input and output jacks facilitate a complete connection of TV and VHF/UHF antenna or cable TV antenna, subscription TV decoder, video disc player, video cassette recorder, video game and home computer or other auxiliary video equipment.

So videophiles switch from one program source to another with push-button ease — without changing connections.

Equally important, the Video Organizer's advanced engineering design by Zenith results in low insertion loss and high isolation. Eliminates electromagnetic interference for maximum picture quality. And permits greater flexibility in use and ease of operation for more hours of uninterrupted home video enjoyment.

Write now for more information and the name of your Zenith distributor so you can start cashing in on the fastest growing segment of the TV business!



The quality goes in before the name goes on.®

Zenith Radio Corporation/Service, Parts & Accessories Division/11000 Seymour Avenue/Franklin Park, Illinois 60131

Double Your Troubleshooting and Testing Productivity . . . Or Your Money Back!

Six-digit readout: Automatically tracks every CRT test. We call it digital autotracking. It's patent pending.

Bright dual-trace CRT: 60 MHz (-3 dB); 100 MHz (-12 dB).

Delta PPV, Time, Freq: Measure any part of a waveform for PPV, time or frequency using Delta measurements. Just dial in the waveform section you want to measure and push.

Simplify Freq ratio tests: Automatically compare input/output ratio of multiply/divide stages from 1:1 to 1:999,999 with the push of a button.



Autotracking DCV, PPV, Freq: Measure DCV to .5%, PPV to 2%; freq. to .001%. Just push a button for either Channel A or B.

One probe input: One probe input per channel for all measurements - digital and scope - with 5 mV to 2000 V measuring range. (2 lo-cap probes provided.)

Super sync: ECL provides rock-solid sync trigger circuits with only 4 controls; includes TV sync separators for video work.

U. S. Patent Pending
Financing Available

The first scope with push button digital readout. If you use general purpose oscilloscopes for troubleshooting or testing, we can double your present productivity with the SC61 Waveform Analyzer, the first instrument to turn every conventional scope measurement into an automatic digital readout.

No more graticule counting. Connect only one probe to view any waveform to 100 MHz. Then, just push a button to read DCV, PPV, frequency and time — automatically!

There are no graticules to count or calculations to make, which speeds every measurement.

The digital readout is from 10 to 10,000 times more accurate as well.

Plus you have everything you want to know about a test point, at the push of a button, which speeds troubleshooting tremendously.

A special Delta function even lets you intensify parts of a waveform and digitally measure the PPV, time or frequency for just that waveform section.

And it's neat. No more tangled leads, piles of probes or dangling cords. The SC61 is an entire test station in one unit.

The one and only. There are other scopes with digital readout, but none of them completely automate every conventional scope measurement so you can automatically analyze any waveform without counting one single graticule. Totally automatic waveform analyzing at the push of a button. It will make all the difference in your productivity.

Double your productivity. When we say the SC61 will double your productivity, we're being conservative. We've seen cases of

three, four, even ten time increases in productivity with this first-of-its-kind, automated oscilloscope. Every situation is different, however, so try the SC61 and judge for yourself. Here's our offer.

Money back guarantee. If the SC61 does not at least double your productivity during the first thirty days, you may return it for a full refund, including freight both ways.

Call today. Get the entire SC61 Waveform Analyzer story. Call toll-free today, and ask for our eight page color brochure. It could be the most productive call you make this year!

Phone Toll-Free
1-800-843-3338

Alaska, Hawaii, Canada and
South Dakota call collect
(605) 339-0100

SENCORE
3200 Sencore Drive, Sioux Falls, SD 57107

For Information Circle (2) on Reply Card
For Demonstration Circle (3) on Reply Card