

85 cents

*hp*

focus  
on  
communications  
technology . . .

# *ham radio*

*magazine*

FEBRUARY 1974

solid state  
TRANSMITTING  
CONVERTER  
for  
144-MHz ssb



## *this month*

- digital capacitance meter 20
- designing L-networks 26
- RTTY message generator 30
- universal frequency standard 40
- fm receiver 54

# Savoy

## BASSETT

High efficiency mobile and portable antennas for all amateur bands, CAP, MARS, CB, SECURITY, PUBLIC SERVICE, MARINE, AND GOVERNMENT USE.

- 2-6-10-15-20-40-75
- Identical size, cost, and appearance
- FULLY ADJUSTABLE TO FREQUENCY IN FIELD
- Low weight, low drag, high strength fiberglass
- Polished chrome brass standard 3/8-24 thread
- High gain collinear on 2 meters

MODEL DGA-2M  
\$29.50 postpaid  
in U.S.A.



\$3.75

Postpaid in U.S.A.

TYPE 900 A

TYPE 901



## HIGH ACCURACY CRYSTALS FOR OVER 30 YEARS

Either type for amateur VHF in Regency, Swan, Standard, Drake, Varitronics, Tempo, Yaesu, Galaxy, Trio, Sonar, Clegg, SBE, Genave.

Quotes on request for amateur or commercial crystals for use in all other equipments.

Specify crystal type, frequency, make of equipment and whether transmit or receive when ordering.



### BASSETT VACUUM TRAP ANTENNA SYSTEM

Complete packaged multi-band antenna systems employing the famous Bassett Sealed Resonators and Balun from which air has been removed and replaced with pure helium at one atmosphere. Operating bands are indicated by model designation.

MODEL DGA-4075 . . . .	\$59.50
MODEL DGA-204075 . . .	\$79.50
MODEL DGA-2040 . . . .	\$59.50
MODEL DGA-152040 . . .	\$79.50

## BASSETT VACUUM BALUN



The famous sealed helium filled Balun . . . employed with the DGA Series Antenna Systems. Solderless center insulator and easily handles more than full legal power while reducing unwanted coax radiation. Equipped with a special SO-239 type coax connector and available either 1:1 or 4:1.

MODEL DGA-2000-B . . . \$12.95  
Postpaid in U.S.A.

CONTACT YOUR DISTRIBUTOR OR WRITE FOR DATA


# Savoy Electronics, Inc.

P.O. Box 5727 - Fort Lauderdale, Florida - 33310

Tel: 305-563-1333 or 305-947-9925



# A NEW CONCEPT IN HIGH POWER . . .

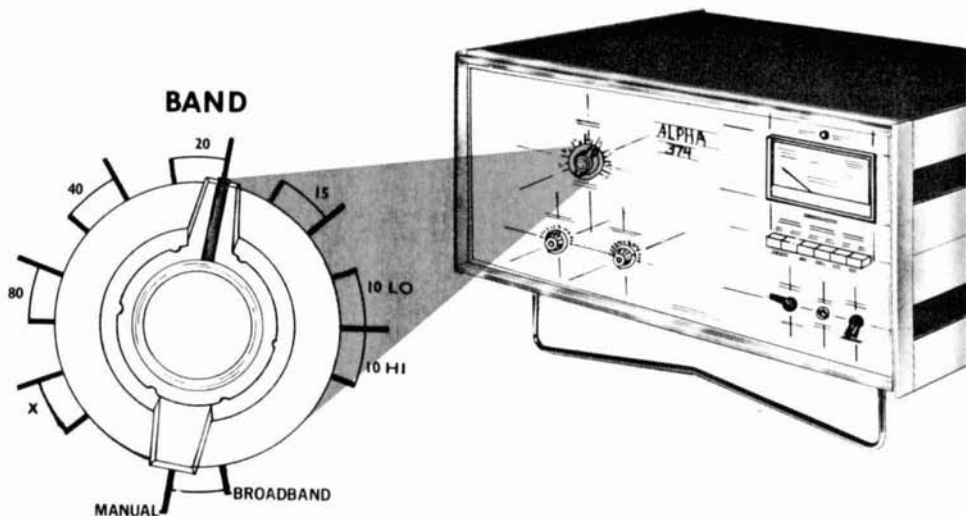

## THE "HANDS OFF" **ALPHA 374** ... BY ETO, OF COURSE!

WITH THE ALPHA 374 . . .

- YOU CHANGE BANDS INSTANTLY and without tune-up
- YOU RUN MAXIMUM LEGAL POWER, even continuous SSTV or RTTY, with a substantial margin of safety
- YOU NEVER TOUCH A TUNING OR LOADING CONTROL if your load SWR is reasonably low
- YOU OPERATE AT PEAK EFFICIENCY because substantial antenna mismatch can be fully compensated
- YOU GET TRADITIONAL *ALPHA* QUALITY you'd expect from the leader in fine linears, PLUS sleek new designer-styled desk-top cabinet, advanced new ALC and protective circuitry, direct metering of PEP input, and much more.

YOU CAN OWN THE ALPHA 374 for little more than the cost of an old-fashioned linear with none of the 374's big new features . . . Just \$995 during the initial introductory period. Call or write ETO now to insure earliest delivery.



**EHRHORN TECHNOLOGICAL OPERATIONS, INC.**  
BROOKSVILLE, FLORIDA 33512  
(904) 596-3711

Drake gear keeps getting better and better...

NOW, OUR FINEST...  
THE NEW  
**Drake C-Line**

**NEW FEATURES:**

- 1 kHz Dual Concentric Dial Readout
- Receiver and transmitter lock together in transceiver operation
- No side controls
- Iridited cadmium-plated chassis
- Compatible with all previous Drake lines



**R-4C Receiver**

The receiver hams have dreamed of...



**T-4XC Transmitter**

The one worthy of the R-4C

**NEW R-4C FEATURES:**

- 8-pole crystal filter combined with passband tuning, SSB filter supplied
- Provision for 15 additional accessory 500 kHz ranges
- Transistorized audio
- Optional high-performance noise blanker
- AVC with 3 selectable time constants
- Optional 8 pole filters available for CW, AM, RTTY
- \$499.95

**NEW T-4XC FEATURES:**

- Plug-in relay
- More flexible VOC operation; including separate delay controls for phone and CW
- Crystal control from front panel for amateur, Mars, commercial uses
- Provision for AFSK RTTY operation
- \$529.95

See for yourself—at your dealer's.

**R. L. DRAKE COMPANY**

540 Richard Street, Miamisburg, Ohio 45342 • Phone (513) 866-2421 • Telex 288-017



February 1974  
volume 7, number 2

**staff**

James R. Fisk, W1DTY  
editor-in-chief

Joseph Schroeder, W9JUV  
editor

Patricia A. Hawes, WN1QJN  
assistant editor

J. Jay O'Brien, W6GDO  
fm editor

Alfred Wilson, W6NIF  
James A. Harvey, WA6IAK  
associate editors

Wayne T. Pierce, K3SUK  
cover

T.H. Tenney, Jr. W1NLB  
publisher

Hilda M. Wetherbee  
assistant publisher  
advertising manager

**offices**

Greenville, New Hampshire 03048  
Telephone: 603-878-1441

**ham radio** magazine is  
published monthly by  
Communications Technology, Inc  
Greenville, New Hampshire 03048

Subscription rates, world wide  
one year, \$7.00, three years, \$14.00  
Second class postage  
paid at Greenville, N.H. 03048  
and at additional mailing offices

Foreign subscription agents  
United Kingdom  
Radio Society of Great Britain  
35 Doughty Street, London WC1, England

All European countries  
Eskil Persson, SM5CJP, Frotunagrand 1  
19400 Upplands Vasby, Sweden

African continent  
Holland Radio, 143 Greenway  
Greenside, Johannesburg  
Republic of South Africa

Copyright 1974 by  
Communications Technology, Inc  
Title registered at U.S. Patent Office  
Printed by Wellesey Press, Inc  
Framingham, Massachusetts 01701, USA

**ham radio** is available to the blind  
and physically handicapped on magnetic tape  
from Science for the Blind  
221 Rock Hill Road, Bala Cynwyd  
Pennsylvania 19440  
Microfilm copies of current  
and back issues are available  
from University Microfilms  
Ann Arbor, Michigan 48103



# contents

**6 two-meter transmitting converter**

Robert S. Stein, W6NBI

**20 digital capacitance meter**

John R. Megirian, K4DHC

**26 designing L-networks**

Robert E. Leo, W7LR

**30 RTTY message generator**

C. A. Ellsworth, W6OXP

W. G. Malloch, W8KCC

**40 universal frequency standard**

A. A. Kelley, K4EEU

**50 i-f alignment generator**

Courtney Hall, WA5SNZ

**54 multichannel fm receiver**

Stirling M. Olberg, W1SNN

**4 a second look**


**60 ham notebook**

**94 advertisers index**

**62 new products**

**83 flea market**

**94 reader service**

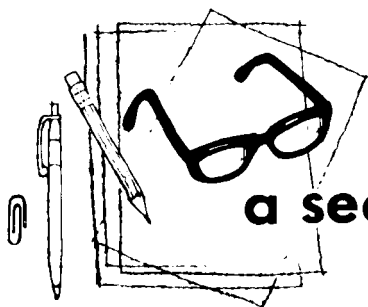

## a second look

by jim  
fisk

The first two issues of *HR Report* are now off the presses and in the hands of subscribers around the country. If you want to know what's happening behind the scenes in amateur radio, and rapidly, as the news breaks, *HR Report* is the only way to do it. For example, did you know that we will probably lose the upper 2 MHz of the 420-MHz band (448 to 450 MHz) to the Emergency Medical Service? Did you know that the ARRL's first ten-meter contest was a partial success, with openings to Africa and South Pacific? Did you know that more than 500 two-meter repeater licenses have been issued by the FCC, nearly clearing up the backlog? Did you know that a large variety of quality-made coils, chokes and terminal boards, packaged for the amateur, are now available from Cambridge Thermionics Corporation (CTC)? These are just some of the items covered in detail in recent issues of *HR Report*. For subscription details for this new bi-weekly amateur newsletter, look on page 72.

This month we will kick off the latest project of our *more for 74* program, an

Automatic License Renewal Service for all FCC-licensed amateurs (except Novices), subscribers to *ham radio* or not. The cost to you? Absolutely nothing, except for the effort to open an envelope. It will work like this: 60 to 90 days before your amateur license is due to expire you will receive in the mail a copy of FCC Form 610 plus a supplementary instruction sheet prepared by our staff which will include some info on such things as renewal fees, operating after your license expires if you filed a timely renewal application, etc. All you have to do is fill out the Form 610, enclose your check or money order, and mail it back to the FCC.

No last-minute scurrying around to find the proper form, or discovering that your license expired a month ago. However, for the Automatic License Renewal Service to operate successfully, your correct address must be on file with the FCC as required by the regulations. If you have moved since you last renewed your amateur license and the FCC does not have your current address you will not receive your License Renewal packet. It's as simple as that.

Early this month the first Automatic License Renewal packets will be in the mail to amateurs whose licenses expire in March and April, 1974. In early March License Renewal packets will be mailed to amateurs whose licenses expire in May. From then on mailings will be made the first of every month so you should receive yours at least 60 days before your license expires.

Jim Fisk, W1DTY  
editor-in-chief

---

**hr** Automatic  
License  
Renewal  
Service

IT'S A FACT:

# LESS THAN 82¢ PER WATT



## SWAN'S NEW 700CX CHAMPION TRANSCEIVER 700 WATTS P.E.P./SSB/AM/CW/5-BANDS

SWAN'S 700CX is a real inflation fighter. You can experience more powerful communications with this one rugged value-packed transceiver, for less cost, than any other ham rig in its class. Here is all the dynamic power you need to punch through QRM—without an expensive accessory amplifier.

Shop around and compare. There's just no competitive method that'll give you everything the CHAMPION has to offer for such a reasonable investment.

Here's some of the many standard features built into the 700CX:

- Automatic Level Control • Fast attack AGC, with controlled decay
- CW sidetone • Selectable sideband • Dual-ratio planetary tuning • S-meter
- 2.7 kHz bandwidth • 5.5 MHz I.F. • Wide-range "Pi" antenna coupler.

\$569.95 will put the CHAMPION in your ham shack. Simple arithmetic shows that at this price you get 700 watts for less than 82¢ per watt—a real value!

Order your new CHAMPION today. For direct delivery, use the coupon below and mail to:



**SWAN**  
ELECTRONICS

A subsidiary of Cubic Corporation

305 Airport Road  
Oceanside, CA 92054

H2

Gentlemen:

Please send me the following SWAN products:  700CX Transceiver @ \$569.95  117XC AC Power Supply & Speaker @ \$109.95  14-117 AC/DC Power Supply @ \$139.95  FP-1 Phone Patch @ \$48.95  
Total amount of order is \$\_\_\_\_\_.

(California residents please add 5% sales tax)

20% down payment enclosed, ship C.O.D.  Full payment enclosed.  10% down payment enclosed, charge remainder to my Swan Credit Account #\_\_\_\_\_. (All items shipped best way collect.)

Name: \_\_\_\_\_ Amateur Call: \_\_\_\_\_

Address: \_\_\_\_\_

City: \_\_\_\_\_ State: \_\_\_\_\_ Zip: \_\_\_\_\_

# solid-state transmitting converter for 144-MHz ssb

Complete  
construction details  
for a solid-state  
transmitting converter  
that provides  
more than  
30-watts output  
on two meters

In the past few years numerous articles have been published describing transistorized fm and CW transmitters and class-C power amplifiers for use in the 144- to 148-MHz band. However, there has been a noticeable lack of information covering single-sideband applications or *linear* transistor amplifiers, due primarily to the problem of generating reasonable amounts of power in linear amplifiers operating in the vhf region.

When my faithful but venerable tube-type two-meter ssb transmitter started to show its age, I began to investigate the possibilities of replacing it with a solid-state unit. A review of the published literature and manufacturers' data indicated that there should be no major obstacles up to the 1-watt level, but I found little encouragement to attempt the 30- to 35-watt output I was seeking. Fortunately, I had available a substantial quantity of vhf power transistors, designed for class-C service, with which to experiment. This article will show that it is entirely feasible to operate vhf power transistors as linear amplifiers, using techniques which are well within the capabilities of the serious vhf experimenter.

## prerequisites

My needs were to generate a minimum of 30 watts PEP between 144 and 146 MHz, using my high-frequency ssb transmitter as the basic exciter. This dictated using the 28- to 30-MHz output from the transmitter in order to cover a 2-MHz range without changing the local-oscillator frequency in the transmitting converter. However, a close examination of the mixing scheme revealed one dismaying problem—operation at 145 MHz requires the ssb input to be at 29 MHz, and the fifth harmonic of 29 MHz is also 145 MHz, which is most undesirable. Since most mixers are excellent harmonic generators, I had to find one that was not. Luckily, the double-balanced mixer

Bob Stein, W6NBI, 1849 Middleton Avenue, Los Altos, California 94022



has excellent characteristics in this respect, thus eliminating one stumbling block.

I also decided that if I were going to have major problems (more than just the expected ones), there was no point in constructing the entire unit, and that if a problem was to prove insurmountable, it would show up before the final stage. Therefore the logical approach would be to build up the circuit to the driver stage, and then cover the final amplifier as a separate subproject. As it turned out, this

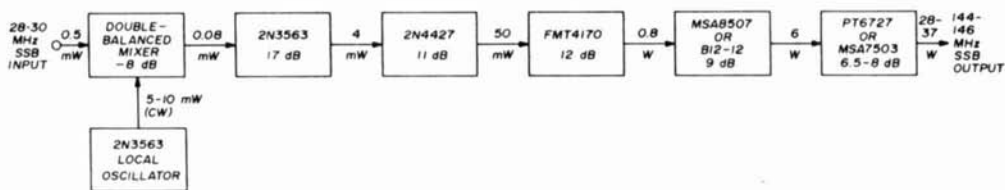


fig. 1. Block diagram showing approximate stage gains and peak-envelope-power levels throughout the converter. Output power and gain of the final stage depend on the type of transistor used and the collector supply voltage.

was a fortunate decision, since it allowed me considerable flexibility in designing the final stage.

### driver unit

A complete block diagram of the transmitting converter appears in fig. 1, showing the approximate stage gains and power levels throughout the circuit. The schematic of the driver unit is shown in fig. 2. The 28- to 30-MHz ssb input is applied to the RF (R) input port of double-balanced mixer Z1, and should not exceed -3 dBm (0.5 mW) to keep distortion products to a minimum. The 50-ohm pad formed by resistors R1 through R3 has been included to insure proper termination of the transmission line from the SSB exciter and to provide the mixer with a 50-ohm source. Values have not been specified for the pad resistors, since the required attenuation will depend on the output power of the exciter and the amount of attenuation present in your external power attenuator. The total loss in the two attenuators must be sufficient to limit the input to the mixer to the specified 0.5 mW. Design equations for calculating the resistance


values may be found in reference 1 or any standard reference text.

I used a double-balanced mixer board which had been given to me because of a broken wiring trace. Its characteristics are identical to several inexpensive mixers now available, such as the Anzac MD108, Mini-Circuits SRA1, and Vari-L DBM166. Any one of these will be suitable, as would be the more expensive Hewlett-Packard or Relcom models. I have recommended the Anzac mixer in the parts list for fig. 2, since it is the least costly

and is directly available from the manufacturer in single-lot orders.

In order to achieve minimum loss through the mixer, a local-oscillator signal of at least 7 dBm (5 mW) is required. This is easily obtained from a 2N3563 operating in a Miller oscillator circuit which uses a 116-MHz overtone crystal. The oscillator output is taken from a tap on the collector coil, chosen to provide maximum power transfer to the mixer.


The output of the mixer is obtained at

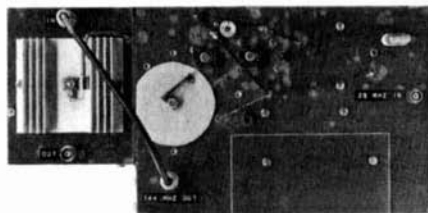

Top view of the driver unit and MSA7503 final amplifier. The metal disc is the heat sink for the driver transistor; top-hat heat sinks are used on the 2N4427 and FMT4170 transistors. The 1N4001 and 1N4719 diodes are inside the clamps on the driver and amplifier mounting studs, respectively.

the i-f (X) port and is applied to a double-tuned top-coupled filter, resonant at 145 MHz. The Q of each tuned circuit and the coupling coefficient have been selected for a bandwidth of approximately 4 MHz. The input and output taps on L1 and L2 provide impedance matching

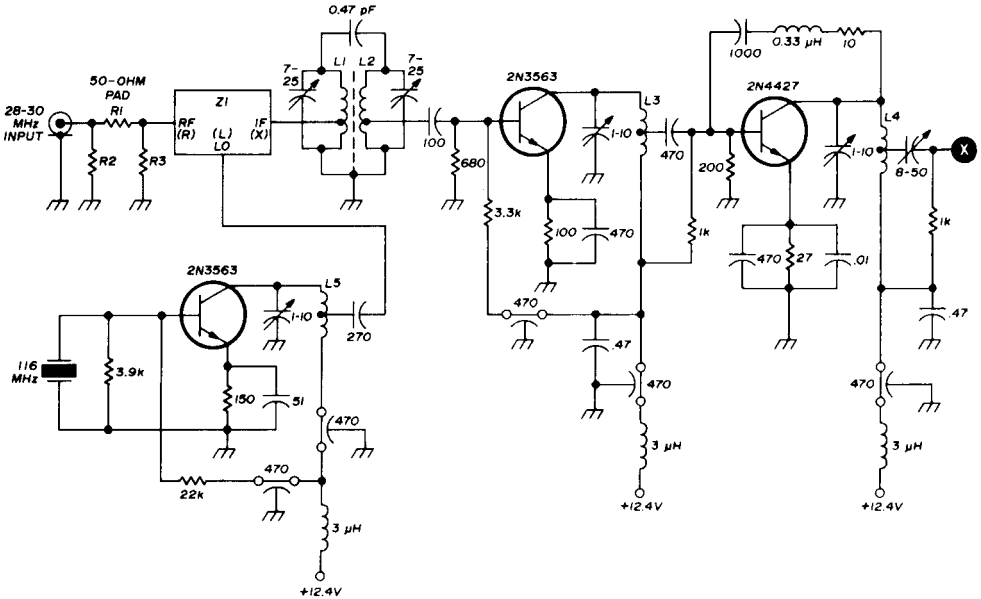additional .01- $\mu$ F emitter bypass capacitor were included to suppress a tendency of this stage to oscillate. The output of the 2N4427 is matched to the base of transistor Q1 by means of a trimmer capacitor tapped down on the collector coil.



- C1,C3 1.5-20 pF compression trimmer (Arco/EI Menco 402)
- C2,C4 7-100 pF compression trimmer (Arco/EI Menco 423)
- L1,L2 4 turns no. 20, 1/4" ID, 1/2" long, tapped 1/2 turn from ground end
- L3 5 turns no. 20, 1/4" ID, 3/8" long, tapped 1/2 turn from supply end
- L4 6 turns no. 20, 1/4" ID, 1/2" long, tapped 1 turn from supply end
- L5 6 turns no. 20, 1/4" ID, 1/2" long, tapped 1/2 turn from supply end

- L6 copper strap, 1/4" long x 3/16" wide
- L7 3 turns no. 16, 1/4" ID, 5/8" long
- L8 \*25 turns no. 26E wound on Micrometals T37-3 core
- Q1 \*Fairchild FMT4170, RCA 2N5913, or Motorola HEP-S3001
- Q2 \*Fairchild MSA8507 or CTC B12-12
- R1,R2,R3 see text
- Z1 \*double-balanced mixer (Anzac MD108 or equal)

fig. 2. Schematic diagram of the driver unit. Sources of asterisked items are listed in the appendix. All 1-10 pF capacitors are piston type.


into and out of the filter. Total loss through the mixer and filter is about 8 dB.

Another 2N3563 follows the mixer, configured as a conventional class-A amplifier. The output of the 2N3563 drives a 2N4427 amplifier, which also operates class A. The RLC network between the collector and base of the 2N4427 and the

Several types of transistors were tried at Q1, all with some degree of success. The best of these was found to be the Fairchild FMT4170, although the lower-priced 2N5913 or HEP-S3001 (in that order of preference) should also be satisfactory. This stage operates closer to class-AB than class-A to keep the transistor power dissipation within acceptable

limits. The RC network between the collector and base improves the linearity of the stage. Parasitic oscillations in the hf region are suppressed by the 10- $\mu\text{H}$  rf choke in parallel with a 10-ohm resistor, plus the large bypass capacitors in the collector supply circuit.

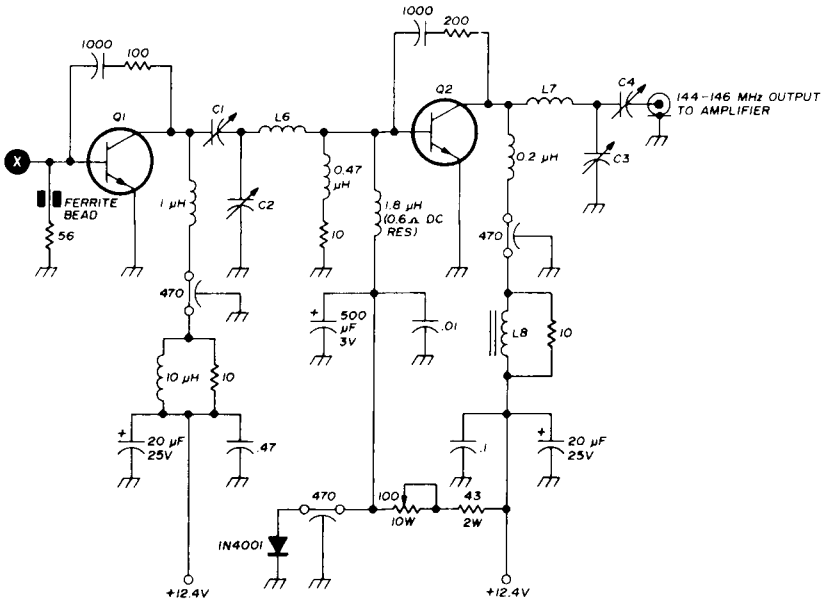To prevent thermal runaway of the transistor, the base current is controlled by a 1N4001 diode which is thermally coupled to the transistor case. This is physically accomplished by mounting the diode on the stud of the transistor so that it follows the temperature of the device.



The driver stage was designed around a Fairchild MSA8507 vhf power transistor which is characterized only for class-C operation. The transistor is forward biased into class AB operation by means of a bias circuit described by Roy Hejhall, K7QWR.<sup>2</sup> Quiescent collector current is set by adjusting the base bias by means of the 100-ohm adjustable resistor.

It is essential that there be approximately one-half ohm dc resistance between the base and bias source for the bias circuit to operate properly. I used a 1.8- $\mu\text{H}$  rf choke from my junk box because it had a resistance of 0.6 ohm. Any choke having an inductance between 0.47 and 2  $\mu\text{H}$  will be satisfactory, provided that it has the required resistance. Otherwise a resistor may be inserted between the rf choke and the bias source to make the total resistance about 0.5 ohm.


Therefore, as an increase in transistor temperature tends to increase the base and collector currents, the increase in diode temperature causes the base bias to decrease, thereby reducing the base and collector currents to the equilibrium values set by the bias-adjust resistor.

The collector-to-base RC linearizing network and the collector-supply hf table 1. Characteristics of the Fairchild MSA8507 transistor at 175 MHz with 12-volt collector supply.

$P_{out}$	12 watts minimum
$P_{in}$	3.5 watts maximum (at rated $P_{out}$ )
$Z_{in}$	$1.5 + j1.3$ ohms
$Z_{out}$	$3 - j2.7$ ohms
$C_{cb}$	35 pF (at 1 MHz)
$BV_{CES}$	36 volts
$V_{CEO}$	18 volts
$I_c$	2.0 amperes maximum
$P_D$	22 watts

parasitic-suppression network are both similar to those used in the preceding stage. Power is coupled into and out of the transistor by means of conventional T-networks, resulting in an output from this stage of approximately 6 watts PEP when fed into a 50-ohm load.

lizing resistors. The circuit is shown in **fig. 3**. The first obvious question is why a nominal 28-volt transistor was used when the rest of the converter uses 12-volt devices. The answer is equally obvious when you look at the typical characteristics of 12-volt, 50-watt transistors—they

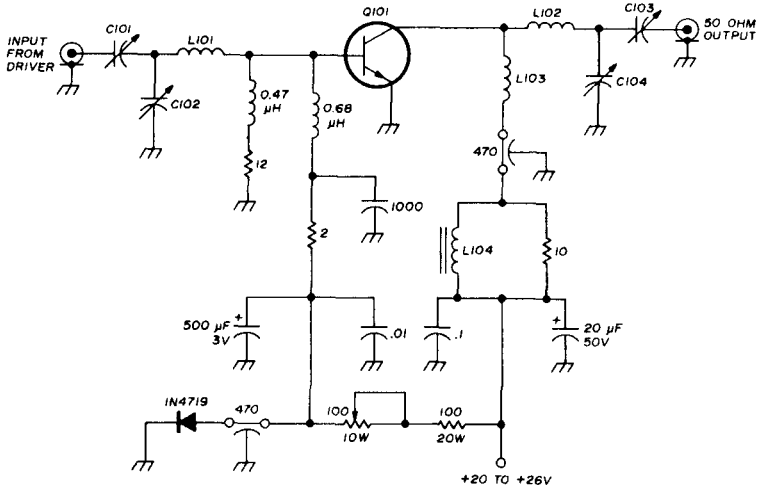

**fig. 3.** Schematic diagram of the final amplifier which uses a high-conductance diode to control base biasing. Details of the parts identified by reference designators appear in table 2.

Unfortunately, the Fairchild MSA8507 is no longer in production, although there may be some to be found as old stock or at surplus outlets. However the B12-12, manufactured by Communications Transistor Corporation, has similar characteristics and should be as good, if not better. For those interested in trying other transistors, the pertinent characteristics of the MSA8507 are listed in **table 1**. Reference 3 contains the design equations for the input and output networks, which must be redesigned if you use a transistor having input and output impedances substantially different from the MSA8507 or B12-12.

### final amplifier

Two different amplifiers were designed, built, and operated on the air. The first uses a transistor characterized for class-C service in the 100- to 175-MHz region and having internal emitter stabi-

do not have the necessary power gain. And as will be seen later, the dual voltage requirement is not a major problem.

The circuit configuration is similar to that used in the driver stage, and uses a Fairchild MSA7503 transistor. The input and output networks are designed to match a 50-ohm source and load, respectively. As with the MSA8507, the MSA7503 is also out of production. However, the technique of placing a 50-watt transistor in linear service, when it was designed for class-C operation, may be of interest. The bias circuit is the same as previously described for the driver stage, except for one minor difference. Because of the relatively large value of base current, an rf choke having less inductance but using larger wire was used in the base circuit. Therefore a 2-ohm resistor was added between the choke and bias source to provide an empirically determined optimum value of resistance.

The transistor operates as close to true class B as possible. That is, the base is just barely forward biased, so that the quiescent collector current is 2 or 3 mA. Considering that the peak dc collector current is about 2 amperes, that is truly class B. All attempts to increase the static collector current resulted in catastrophic failure of the device when excitation was applied, probably caused by secondary breakdown. (See reference 4 for a discussion of this phenomenon.) However, as long as the static collector current is limited to 3 mA or less, the amplifier is stable, reliable, and entirely satisfactory. The output powers obtained at collector voltages between 20 and 26 volts are shown in fig. 4.

A second amplifier was then designed and built, using a commercially available transistor and a different biasing scheme. A TRW PT6727 is used in the circuit shown in fig. 5. This transistor is emitter-ballasted and is designed not only for CW operation at 150 MHz, but for a-m service as well.

The heart of the bias network in this circuit is a device called a *byistor*, which is manufactured by Communications Transistor Corporation, and shown in fig. 5 as a Y-shaped symbol (originated by CTC) with its type designation BY1. The byistor acts as a low-impedance dc bias source and consists of a diode and silicon resistor; fig. 6 shows the internal arrangement. The device is packaged in a ceramic stripline configuration, identical to that

used for rf power transistors, and is meant to be mounted on the same heat sink as the transistor for temperature tracking. The diode is fabricated using the same material, geometry, and diffusion as an rf power transistor, so that it will thermally track the transistor. Tracking is

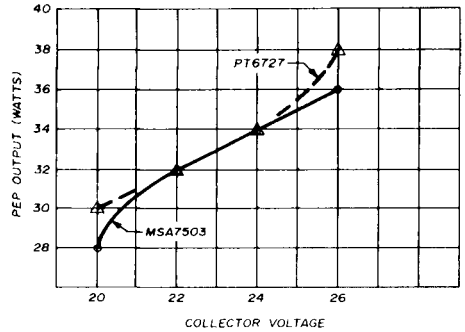


fig. 4. Outputs obtained from the Fairchild MSA7503 and TRW PT6727 transistors, plotted against collector supply voltage. These curves are not to be construed as indicating relative gains, since the drive power and tuning were optimized for each transistor at each value of collector voltage.

further improved by the temperature characteristics of the silicon resistor.

A constant current of approximately 350 mA is applied to injector terminal I, causing the diode to act as a voltage source having about 0.3 ohm impedance. The silicon resistor adds approximately 0.7 ohm and increases the apparent source impedance to approximately 1 ohm at supplier terminal S. The voltage at the supplier terminal will be between 0.45 and 0.85 volt, depending on the current being drawn from S and the temperature of the device. Thus, if a variable resistor is connected between the supplier (S) and reference (R) terminals, the supplier voltage can be adjusted. This is accomplished by the 4.7- and 100-ohm resistors shown in fig. 5; a single 5-ohm adjustable resistor could be used, but a 4.7-ohm, half-watt resistor in parallel with a printed-circuit type trimmer potentiometer provides finer control.

As the temperature of the byistor increases, the resistance of the silicon

table 2. Inductors and capacitors used in the amplifier circuits of figs. 3 and 5. Numbers in parentheses following the capacitance values are Arco/EI Menco part numbers.

Q101	MSA7503	PT6727
C101	1.5-20 pF (402)	7-100 pF (423)
C102	7-100 pF (423)	24-200 pF (425)
C103	same as C102	3-35 pF (403)
C104	same as C102	2-25 pF (421)
L101	1/2 turn no. 18, 3/8" ID, 1 1/4" lead length	copper strap, 1" long, 3/8" wide
L102	1 turn no. 14, 3/8" ID, 1 1/4" lead length	3 turns no. 14, 1/4" ID, 1/2" long
L103	7 turns no. 20, 3/16" ID, 3/8" long	7 turns no. 20, 3/16" ID, 3/8" long
L104	35 turns no. 20E wound on Micrometals T80-2 core	


resistor increases and the diode voltage decreases. This results in an increase in the apparent source impedance and lowers the bias voltage at the supplier terminal. Consequently, the base current of the associated transistor is reduced, preventing thermal runaway and providing improved dc stability of the amplifier. A more rigorous explanation of the byistor, with temperature-characteristic curves, appears in reference 5.

Aside from the biasing arrangement, the amplifier circuits of **figs. 3 and 5** are identical. Different values of inductance

appear in **fig. 4**, plotted against collector supply voltage.

## power supplies

The low-power stages require a 12- to 12.6-volt dc source which is capable of supplying approximately 1.5 amperes at peak power output. The MSA7503 final amplifier draws about 2 amperes, while the PT6727 requires a 2.5-ampere supply, both values being the peak current. Both of the supplies must be reasonably well regulated because of the varying load inherent in ssb operation.

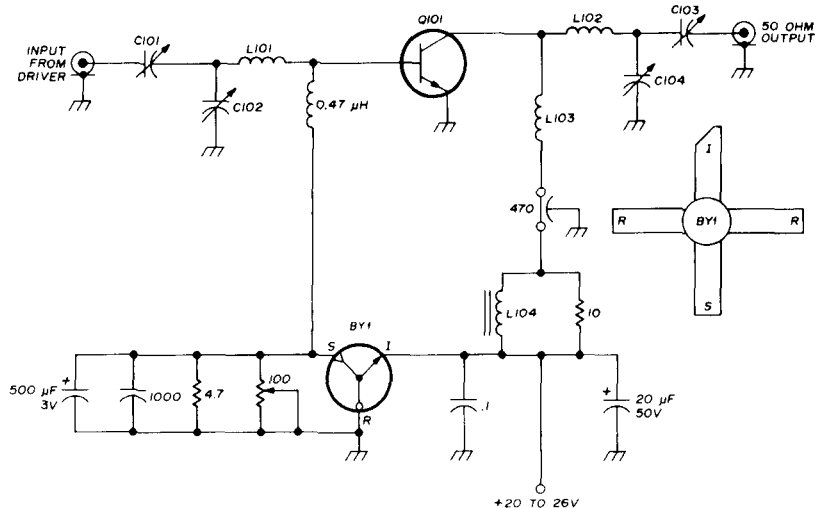

**fig. 5.** Schematic diagram of the final amplifier which has its base bias controlled by the CTC byistor. Details of parts identified by reference designators appear in **table 2**.

and capacitance in the input and output networks are required for each type of transistor, but either transistor can be used in either circuit. However, the improved construction of the PT6727 permits class-AB operation, which reduces the intermodulation distortion products to some extent. **Table 2** contains inductance and capacitance data applicable to either circuit, for each type of transistor.

The PT6727 appears to be somewhat better than the MSA7503 in terms of power gain, output, and distortion products, which is to be expected in view of its intended application. The power outputs obtained from the PT6727

A convenient way to obtain the two supply voltages is to use a 20- to 26-volt supply capable of providing the total load current, and incorporate a simple regulator circuit to drop the voltage to the nominal 12 volts required for the driver unit. Such a regulator is shown in **fig. 7**. The value of dropping resistor R will depend on the input supply voltage, and may be calculated from the equation shown on the diagram.

If the 20- to 26-volt supply is regulated with a circuit similar to or better than that shown in **fig. 7**, the 12-volt regulator is more than adequate for local-oscillator stability. Purists may want to add a 10- or 11-volt zener diode at the

local oscillator for additional regulation, but it was found to be unnecessary.

### construction

Construction of the driver unit and the final amplifiers is shown in the various photographs. I started out using a piece of single-sided copper-clad board approximately 6-1/2 by 9-1/4 inches, since the circuits were developed stage by stage. I ultimately ran out of board, so for that reason the driver stage runs at a right angle to the low-level circuits. This is no problem except for the fact that it leaves a large portion of the board unused. To run all of the stages in the driver unit in a conventional straight line, I suggest using a piece of board approximately 12-inches long by 4-inches wide.

The normal techniques used for vhf construction should be followed—short leads and small, high-quality components. The low-level stages are each enclosed within shielded partitions which are made of pieces of copper-clad board soldered to the main board. The partitions should be placed across the transistor sockets to isolate the input and output circuits, thus minimizing any tendency of the high-gain stages to oscillate on their own. Liberal use of feedthrough capacitors and rf chokes for the supply voltages, with the dc wiring run on the top side of the board, prevents stray coupling through the power leads.

L1 and L2 in the mixer output circuit are shielded from one another by placing L1 and its associated capacitor on the mixer side of a shield partition, and L2 and its capacitor on the other side. The 0.47-pF coupling capacitor is then con-

nected to the top end of each coil via a feedthrough terminal in the partition.

The MSA8507 (or B12-12) and PT6727 transistors are in stripline-opposed-emitter packages, which require some care in mounting. Virtually all of the published articles employ this pack-

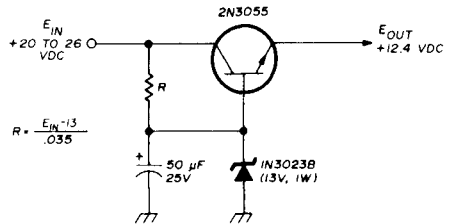


fig. 7. Regulator circuit for use in dropping the 20- to 26-volt dc supply to 12.4 volts.

age configuration in circuits which use printed-wiring inductances or transmission-line sections. Since my design uses only discrete components, the mounting and connection techniques are slightly different.

There are two major conditions which must be met when mounting stripline transistors: the emitter leads must be grounded as closely as possible to the case, in order to minimize emitter lead inductance, and the case must be mounted on a heatsink without putting undue strain on any of the transistor leads. Considering the latter condition first, it can be satisfied by mounting the transistor to the heatsink, through a hole in the copper-clad board, *before* soldering to any of the leads. A sparse application of silicone thermal compound should be used between the body of the transistor and the heatsink.

Reducing the emitter lead inductance, as accomplished by soldering the leads close to the case, creates the annoying problem of what to do with the collector and base leads. Fortunately, operation at 144 MHz is not so critical as to preclude using one of the arrangements shown in fig. 8. In fig. 8A, the base and collector leads are soldered to lands which are insulated from the ground plane. These lands may be formed in one of two ways.


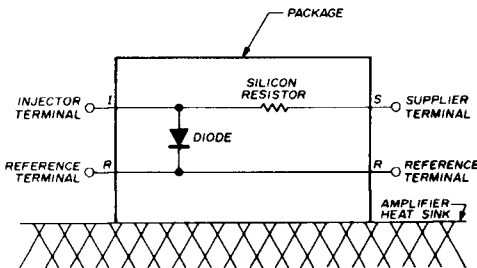


fig. 6. Schematic diagram of the bylster (courtesy CTC).

The copper can be routed out around the transistor leads, creating areas that are isolated from ground, and the leads then soldered to these lands. An alternate method is to cut small pieces of copper-clad board and cement them to the ground plane to form small insulated

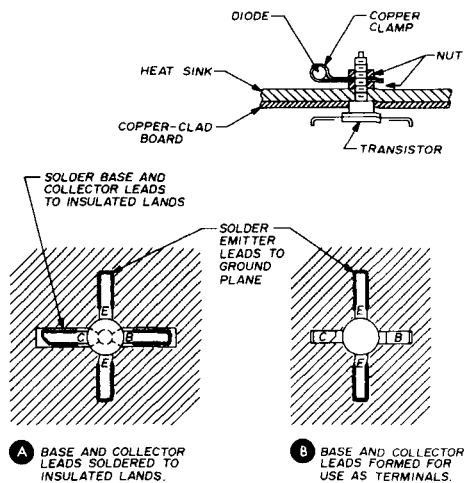

**fig. 8.** Methods of mounting stripline-opposed-emitter packaged transistors. Also shown is a base-bias control diode clamped to the transistor mounting stud for thermal tracking.

platforms to which the transistor base and collector leads can be soldered. In both cases, the heatsink must be spaced away from the main board so that the emitter leads are level with the ground plane or close enough to the ground plane so that they can be bent down slightly without too much strain.

**Fig. 8B** shows a third method which allows the heatsink to be mounted directly to the board without spacers. The base and collector leads are folded back on themselves, by means of long-nose pliers, and the folded ends carefully bent up away from the stud. This provides a relatively rigid terminal for connections to the transistor. The emitter leads are carefully bent down to the ground plane and soldered.

The heat sink for the driver transistor was made from a scrap piece of aluminum and has an area of about 6-1/2 square inches. This is enough radiating surface to

keep the transistor from getting any more than barely warm to the touch. Of course, any one of the many commercial heat sinks having equivalent radiating surface could be used.

The 1N4001 diode is thermally coupled to the driver transistor by means of a clamp mounted on the transistor stud, as shown in **fig. 8B**. The clamp is made of a small piece of sheet copper which is formed around the diode to fit snugly. The diode and clamp surfaces should be coated with a thin film of thermal compound before being secured to the transistor stud. The diode cathode is soldered to the clamp, which is grounded via the heatsink, while the anode lead is connected to the bias-adjust resistor through a feedthrough capacitor.

The final amplifier is built on another piece of single-sided copper-clad board which measures 4 by 5 inches. The heat sink, which has a radiation surface of 33.4 square inches, is an Archer 276-1360, available at Radio Shack stores. The PT6727 stripline-packaged transistor is mounted to the board and heat sink in one of the ways previously described.

The MSA7503 is packaged in a TO-60 stud-mount case, which poses an additional problem in securing a low-impedance emitter-to-ground path. The emitter is connected internally to both the case and a terminal pin on the body, but using the pin is not practical because of the high internal lead inductance. The scheme shown in **fig. 9** was finally reached, and should be a useful method for mounting any similar transistor. First mount the heatsink to the board and, using a number-9 drill, drill a 0.196-inch hole through the heat sink and board for the transistor mounting stud. Then disassemble the heat sink from the board and enlarge the hole in the board to a diameter of 1/2 inch. Remount the heat sink on the board.

Obtain a small piece of copper *foil* (the kind used for electrostatic shields between power-transformer windings) and cut out a disc 1 to 1-1/4 inch in diameter. Carefully cut a hole in the




center of the disc just large enough to clear the transistor stud. Apply thermal compound to that part of the heatsink which is accessible through the enlarged hole in the board. Place the copper foil on the stud and mount the transistor to the heatsink. (Note that thermal compound is not used between the copper foil and the transistor, in order to maintain a good rf path between emitter and ground.) Slit the edges of the copper foil, now protruding from the hole in the board, so that the foil can be pressed flat against the copper board, and solder it down. This results in a continuous ground plane from the board to the transistor emitter.

If a 1N4719 diode is to be used to control the bias, mount it to the transistor stud in the same manner as described for mounting the 1N4001 on the driver transistor. If you use the BY1 byistor, mount it in one of the ways described for stripline packages, except that there is no need for concern about lead inductance. I located the byistor stud 1 inch from the transistor stud, on a line with the base lead. This places it under the input inductor, which hides it in the photograph of the PT6727 amplifier.
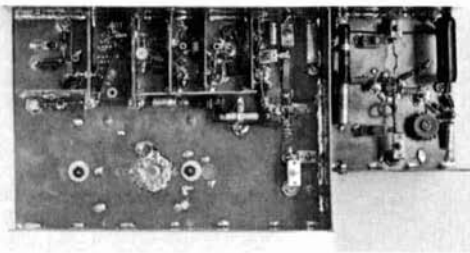
### adjusting and tuning the driver

One of the advantages of having the final amplifier separate from the driver



Bottom of the driver unit and MSA7503 amplifier. The local oscillator is at the left side, followed by the mixer and low-level stages to the right. The driver stage runs along the right side of the larger driver-unit board. The amplifier input circuit is at the top of the smaller board, and the collector circuit is at the bottom. Note the use of shield partitions to prevent feedback.

unit is being able to tune up the low-power stages independently of the final. And since two relatively high-power transistors are involved, having to worry about just one at a time makes the process much easier.

Before making any power connections,

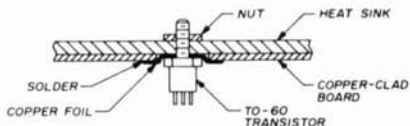



fig. 9. Method of mounting TO-60 stud-mount transistors to minimize emitter-to-ground lead inductance.

set the 100-ohm adjustable resistor in the driver bias network for maximum resistance. Then temporarily break the collector supply circuit in the driver stage and insert a 0-50 or 0-100 mA meter between L8 and the supply. Be sure the meter will indicate only the collector current and not the current drawn by the 1N4001 diode. Connect a good 50-ohm load and power meter to the driver output connector.

Connect the 12-volt supply and apply power. The meter should read zero or close to it. Adjust the 100-ohm resistor until the collector current is approximately 20 mA; this sets the operating bias on the driver transistor. Next check the operation of the 2N3563 oscillator, using an electronic voltmeter and rf probe at the output, or a sensitive detector coupled to the collector tank circuit. Tune the oscillator for maximum output. If the circuit fails to oscillate, it may be necessary to experiment with the value of the emitter bypass capacitor.

Turn off the power supply and replace the milliammeter with a 0-1 ammeter. Now connect the hf single-sideband transmitter, tuned to 29 MHz, to the input connector of the driver unit. Be sure that you have enough attenuation between the transmitter and converter to limit the power at the mixer input to 0.5 mW. Reapply power to the driver unit and slowly insert carrier at the transmitter while watching the driver-stage collector

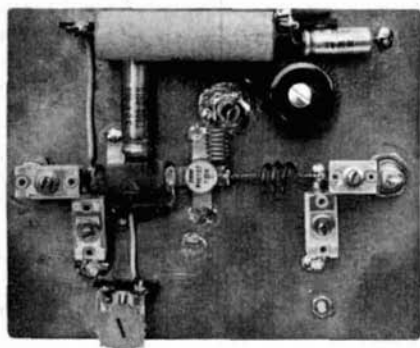current. If the collector current starts to increase, immediately adjust the tuning capacitors in the driver output network for maximum output power. Actually, there is little likelihood of this occurring before the low-level stages have been tuned, so reduce the 29-MHz excitation



Component side of the PT6727 final amplifier. The copper-strap inductor in the input circuits hides the byistor. The transistor and byistor are mounted on the same type of heat sink as shown in the photograph of the MSA7503 amplifier.

and tune up the converter by means of the following technique.

Tune each stage for maximum power output. An electronic voltmeter with an rf probe, connected at a point which follows the circuit or stage being adjusted, makes a good tuning indicator without loading down the circuit (e.g., connect the probe to the collector of the stage *following* the one being tuned). As each stage is tuned, gradually increase the 29-MHz carrier and monitor the driver collector current so that the driver output circuit can be tuned for maximum output as soon as the collector current starts to increase. As excitation to the driver stage is increased, the collector current will rise to a maximum of 0.75 to 1 ampere. Tune the driver output circuit for maximum output consistent with minimum collector current. Since the Q of the output circuit is low, tuning is relatively broad, making it easy to pick the point of best efficiency.

As the 29-MHz drive is increased and

as each stage is tuned, the output should gradually rise to at least 6 watts. However, if the output goes to 9 watts or so, it is an indication that one or more of the low-level stages are saturated. If this happens, reduce the excitation to the point where the output power drops sharply. This is the limit of linear operation, and all tuning adjustments should be repeaked at this level. Vary the frequency of the ssb transmitter from 28 to 30 MHz and retune it for constant output at several points within the frequency range, but do not retune the transmitting converter. The output from the converter should vary less than 10 percent.

Deenergize the power supply, remove the ammeter, and restore the driver collector circuit to its original state. You now have a 6-watt ssb signal, ready to put on the air or to drive the final stage. If you want to get it on two meters at this point, be sure to read the section headed *operation* before connecting the antenna.

## adjusting and tuning the final amplifier

If you are using the amplifier circuit shown in **fig. 3**, set the 100-ohm adjustable resistor for *maximum* resistance. If you are using the circuit of **fig. 5**, set the 100-ohm pot for *minimum* resistance between the byistor supplier terminal and ground. Temporarily open the collector circuit, as was done for the driver, and insert a milliammeter between L104 and the power supply so that it will measure only the collector current. A 0-50 or 0-100 mA meter can be used for the PT6727; a 0-10 mA meter is preferable if an MSA7503 or equivalent is used.

Using the lowest supply voltage which will provide you with the output power that you need, turn on the power supply and adjust the bias resistor on the amplifier for a collector current of 25 mA if the PT6727 is being used. If you are using an MSA7503 or an equivalent transistor, adjust the bias resistor to the point where the collector just starts to draw current—about 2 or 3 mA. Remove power and replace the milliammeter with an am-

meter having at least a 2.5 ampere range.

Connect the driver unit to the amplifier by means of a short length of 50-ohm coax cable, and terminate the amplifier with a power meter and good 50-ohm load. Energize the driver unit and amplifier power supplies, and *gradually* apply rf excitation. Tune the amplifier input and output capacitors for maximum output each time the drive is increased. The output should rise smoothly until it reaches the approximate value indicated in **fig. 4** for the supply voltage being used. As with the driver stage, the final tuning should provide maximum efficiency (maximum output consistent with minimum collector current). The collector efficiency of the PT6727, operating class AB, should be approximately 60 percent. The efficiency of the MSA7503 or any other transistor operating virtually at cut-off may be as high as 75 percent. Tuning the exciter over a 2-MHz range should not affect the output of the transmitting converter by more than 10 percent.


Driver-stage tuning may be refined during the amplifier tuning procedure by peaking the capacitors in the driver collector circuit for maximum amplifier output, but this must not be done until after the amplifier input tuning capacitors have been adjusted for maximum output. Then remove all power, disconnect the ammeter, and restore the final collector circuit to its original condition.

## operation

The transmitting converter is now ready to feed an antenna or to drive a high-power linear amplifier. In the latter case, connect the converter to the amplifier through a 50-ohm coax cable (assuming that the amplifier being driven has a 50-ohm input impedance) and retune the converter amplifier collector circuit for maximum drive. It is advantageous to monitor the transistor amplifier collector current to achieve maximum efficiency, which can be done simply by inserting an ammeter in the lead from the dc supply. Remember, however, that you will now be measuring the collector current plus

the current drawn by the bias-control diode or byistor, so that the total current through the meter will be 200 to 350 mA greater than the collector current alone.

If the transmitting converter is fed directly to an antenna, a lowpass filter must be inserted between the output

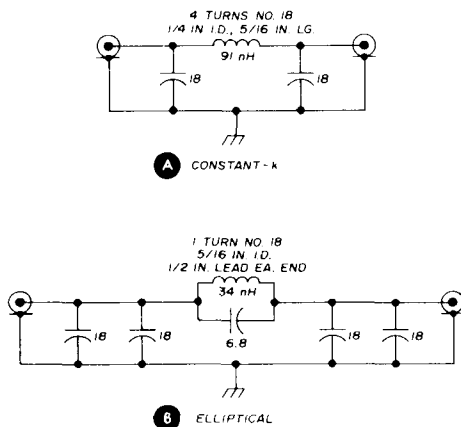

**fig. 10. Schematic diagrams of two lowpass filters for suppressing harmonic radiation. The coil in the elliptical filter (B) should be adjusted so that it resonates with the 6.8-pF capacitor at 327 MHz. Capacitors are silver mica, 5 percent or better.**

connector and the transmission line to attenuate harmonics which will be passed by the low-Q output network of the driver or amplifier. (The higher-Q tuned circuits in a vacuum-tube amplifier following the converter will provide sufficient filtering, and eliminate the need for a lowpass filter.) Two such filters are shown in **fig. 10**. The constant-k pi-section in **fig. 10A** is slightly simpler than the elliptical pi-section of **fig. 10B**, but the latter will provide at least 6-dB, and as much as 16-dB, more attenuation to the second harmonic than will the constant-k configuration.

After making the necessary connections and applying power, retune the output collector circuit for maximum output power. Again, it is wise to monitor the collector current, as described above. Once the preceding tuning procedures have been completed, it will not be necessary to retune any of the circuits

## appendix

Most of the parts used in the transmitting converter are available through regular distributors. The following list is provided for those items which must be ordered from other sources, and includes prices (as of July 1973) for those of major importance.

item	unit price	source
CTC B12-12 BY1	\$ 9.50 6.00	Communications Transistor Corporation, 301 Industrial Way, San Carlos, California 94070
Anzac MD108	7.00	Anzac Electronics, 39 Green Street, Waltham, Massachusetts 02154
TRW PT6727	35.00	Request name and address of closest distributor from Marketing Department, TRW Semiconductor Division, 14520 Aviation Boulevard, Lawndale, California 90260
Fairchild FMT4170	5.50	Request name and address of closest distributor from Marketing Department, Fairchild MOD, 4001 Miranda Avenue, Palo Alto, California 94304
Micrometals cores		Amidon Associates, 12033 Otsego Street, North Hollywood, California 91607

over long periods of time, provided that you do not change the load or supply voltages. The low-Q tuned circuits are relatively insensitive to other changes.

### conclusions

Operation on two meters during the past several months, using both amplifiers, has shown that the transmitting converter is stable and trouble-free. A spectrum analyzer was not available for distortion measurements, but rough measurements using a receiver and calibrated step attenuator indicate that the third-order products are down approximately 24 dB when using the MSA7503 amplifier, and approximately 27 dB for the PT6727. The limitation in the latter case is probably due to the distortion products generated in the MSA8507 driver stage.

### acknowledgements

I would like to acknowledge the technical and material assistance received from the following: Joe Reisert,

W6FZJ, of Fairchild Microwave and Optoelectronics Division; Jack Manon, W6FIG, of TRW Semiconductors; and Bob Artigo, W6GFS, Lee Max, and Mike Mallinger of Communications transistor Corporation. Thanks are also due to Alan Stein for the photography.

### references

1. F. Langford-Smith, "Radiotron Designer's Handbook," Radio Corporation of America, Harrison, New Jersey, Fourth Edition, 1952, page 795.
2. Roy C. Hejhall, K7QWR, "Broadband Solid-State Power Amplifiers for SSB Service," *QST*, March 1972, page 36.
3. Paul Franson, WA7KRE, "How to Use RF Power Transistors," *ham radio*, January, 1970, page 8.
4. Z. F. Chang and J. F. Locke, "Use of the RCA-2N6093 HF Power Transistor in Linear Applications," Application Note AN-4591, RCA Solid State Division, Somerville, New Jersey.
5. Lee B. Max, "Byistor—A New Device for Linear Amplifier Bias Networks," Application Note 2.0.8.1D, Communications Transistor Corporation, San Carlos, California, 1973.

ham radio



①



②



④



③



⑤

# We guarantee you'll be satisfied with the complete line of Robot Slow Scan TV equipment.

## ① MODEL 70 A SSTV MONITOR

Displays amateur standard pictures from any SSTV audio source: station receiver, tape, camera. Six inch (diagonal) display.

Front panel controls for easy station operation. Connectors for receiver, transmitter, microphone, tape, waveform monitor, tuning indicator, and auxiliary demodulated SSTV output for external monitoring.

All solid state except cathode ray tube.

\$295

## ② MODEL 80 A SSTV CAMERA

Generates amateur standard SSTV pictures and fast scan video for viewfinders. Controls for contrast, brightness, vidicon beam, SSTV signal level, black/white reversal, 1/4-1/2 full frame selection.

All solid state except vidicon. All station cabling included; requires suitable C-mount lens.

\$295

## ③ VIEWFINDERS

Choice of 4 inch diagonal (Model 60) or 6.5 inch diagonal (Model 61) display to fit your station.

Displays fast-scan video pictures to simplify setting camera focus and field of view. All solid state except cathode ray tube. Tripod mountable (Model 60 only).

Model 60: \$249

Model 61: \$239

## ⑤ VIEWING HOOD

Two piece detachable hood. Fits monitor bezel to block outside light.

\$25

## CALIBRATION TAPES

Three inch reel or cassette tape recording aids setting monitors and cameras to SSTV standards.

Cassette \$4

Reel \$3

## ④ LENSES

Lens	Focal Length m m.	Min. f stops (All 22 max)	Min. focus (in inches)	Price
A	12.5	1.9	10	\$ 49
B	25	1.9	24	\$ 25
E	25	1.4	6	\$ 54
F	50	1.9	42	\$ 43
G	150	3.2	96	\$ 79
H	18-90	2.0	60	\$220

All Robot equipment carries a one-year warranty. Four easy ways to purchase: cash, C. O. D., Master Charge, Bank-Americaid.

# ROBOT

ROBOT RESEARCH, INC.  
7591 Conroy Court  
San Diego, California 92111  
Phone 714-279-9430

Enclosed \$ \_\_\_\_\_ Please send the following equipment  
via AIR  or SURFACE

Name \_\_\_\_\_

Call \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

California residents add 5% sales tax. Prices do not include shipping.

"We have a limited supply of our Model 70's and Model 80's available at a 10% discount. Same full one year warranty as on all Robot equipment."



## digital capacitance meter

Construction details  
for a wide-range  
digital capacitance meter  
that doubles  
as a 20-MHz  
frequency counter

Depending on your point of view, this instrument may be called a capacitance meter which will also function as a frequency counter or it can be called a frequency counter which will also measure capacitance. To me it's a capacitance meter since that was my need at the time I designed it. However, to provide one function without the other would be foolish since circuitry for both is practically identical and requires only the switching of a few points in the control logic to implement either mode of operation.

### theory of operation

The capacitor to be tested is placed in a timing circuit whose output gates a

train of fixed-frequency pulses into a standard counter. The output pulse length from the timer circuit is proportional to the size of the capacitor, thus varying the gate time. The resultant count is indicated by the digital readouts. A large capacitor would result in a long gate time and a high pulse count.

If the resistance factor in the RC time constant is used as a calibrating device, it could be adjusted in conjunction with a known value of capacitance to give a known gate time and, therefore, a known count. For example, if R were adjusted to provide a 1.0-millisecond output pulse in conjunction with a 1000-pF capacitor and the pulse rate was 1.0 MHz, during the 1.0-ms opening of the gate 1000 pulses would get through to the counter and register on the readouts. A 900-pF capacitor would shorten the gate time sufficiently to allow only 900 pulses through. Larger capacitors permit proportionately longer count times with resulting higher counts.

In the capacitance meter frequency is fixed and gate time is variable, while in the counter gate time is fixed and frequency is variable.

### circuit details

About the time I first started thinking about this idea, Signetics introduced their NE555 IC timer. This little item requires only two external components, a resistor and a capacitor, and is just the thing for

Ray Megirian, K4DHC, Box 580, Deerfield Beach, Florida 33441

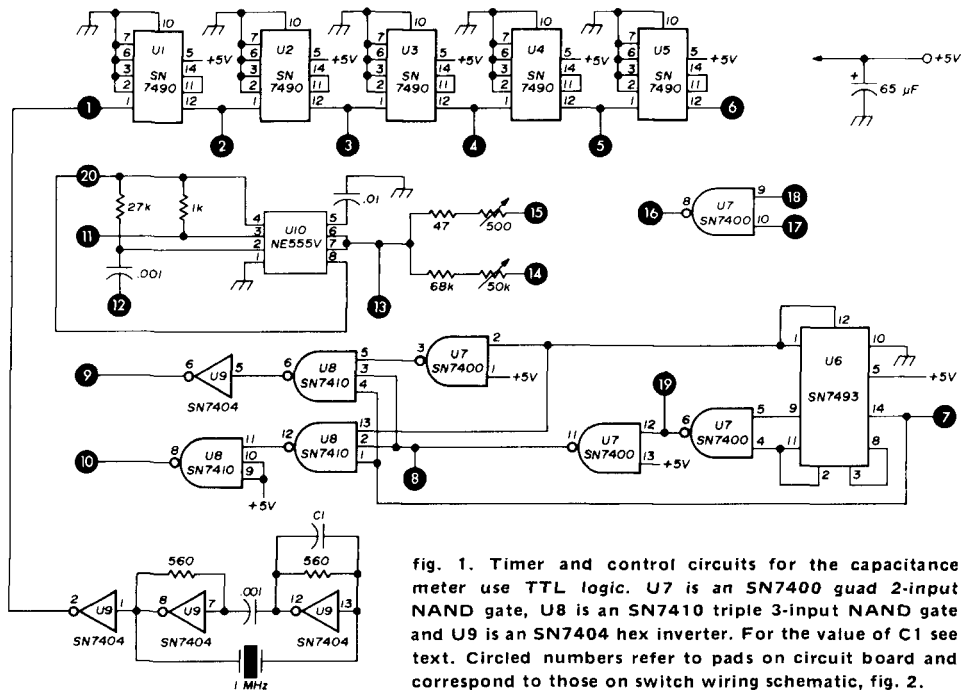


fig. 1. Timer and control circuits for the capacitance meter use TTL logic. U7 is an SN7400 quad 2-input NAND gate, U8 is an SN7410 triple 3-input NAND gate and U9 is an SN7404 hex inverter. For the value of C1 see text. Circled numbers refer to pads on circuit board and correspond to those on switch wiring schematic, fig. 2.

generating the timing pulses. In this case the resistor would be a calibrating pot and the capacitor would be the unit under test.

Inside the NE555 are two comparators, a flip-flop, an output stage and a discharge transistor. Initially, the capacitor is held discharged by the transistor connected across it. When a negative-going pulse is applied to pin 2 of the IC, the flip-flop is set, releasing the short across the capacitor and charging commences.

A circuit operating in this mode is the old familiar one-shot or monostable. The NE555 may also be wired as an astable if free-running operation is desired. For interested readers, the data sheets show many other interesting applications for this IC.

The control logic circuit used in this instrument was borrowed from an article by W1ED in *QST*.<sup>1</sup> A 1-MHz crystal oscillator and SN7404 hex inverter IC were added to provide the clock input (see fig. 1). Five SN7490 decade counters

table 1. Capacitance ranges used in the instrument built by the author.

range	calibration	clock frequency	readout format
1000 $\mu\text{F}$	1.0 $\mu\text{F}$ = 0.1 ms	100 kHz	1000.0
1.0 $\mu\text{F}$	.001 $\mu\text{F}$ = 0.1 ms	100 kHz	1.0000
0.1 $\mu\text{F}$	.001 $\mu\text{F}$ = 0.1 ms	1.0 MHz	0.1000

The reference voltage for the comparator is internally set at two-thirds of the operating voltage. When the voltage ramp across the capacitor reaches this level, the circuit fires, resetting the flip-flop and discharging the capacitor. Upon receipt of another trigger pulse, the cycle repeats.

divide the crystal frequency down to 10 Hz — this results in a string of pulses spaced exactly one-tenth second apart. An SN7493 is used as a divide-by-twelve counter to provide a period of 1.2 seconds or 12 clock pulses for a complete timing cycle.

The initial 1-second portion is the count period during which the count gate is open. During the 0.2-second interval between counting periods, a transfer pulse is generated which allows the in-

latter two pulses are formed by interconnecting various gates contained in an SN7400 and an SN7410 IC. The pulse appearing at pin 11 of U7 is negative-going at the start of the timing period and is used to trigger the NE555 for capacitance measuring.

When the instrument is operating as a capacitance meter, the control pulse for the count gate comes from the timer circuit and the pulse train to be counted is generated by the internal clock. When functioning as a straightforward counter, the count gate reverts to internal control and the signal to be counted comes from an external source. These and other points require switching and are combined into a single multi-pole switch. In my unit this switch provides three capacitance ranges and two for counter operation. Sections of the function switch are also used to apply power and trigger pulses to the timer when operating in the capacitance-measuring mode (see fig. 2).

Table 1 shows the relationships between the various parameters when applied to a 5-digit counter such as that used here. Obviously this scheme is not a mandatory one and can be altered to suit other situations. If you are planning to place decimal points at appropriate points in the display, don't forget to reserve a pole on the function switch for that purpose.

### construction

The heart of the capacitance meter is the control logic and timer circuitry. A two-sided PC board was laid out to accommodate all of the circuitry in an uncrowded area 2.5 by 4.6 inches. Since the TTL logic ICs come in dual-inline packages, a similar version of the Signetics NE555 timer was used. This is their 8-pin mini-DIP known as the V package (NE555V).

The 1-MHz crystal is in an HC6-U holder with wire leads. The calibrating trimmers are the common 1-inch type which have pin spacings of 0.2 and 0.3 inch with a 0.2-inch straddle. The decoupling filter capacitor is a 65- $\mu$ F dipped

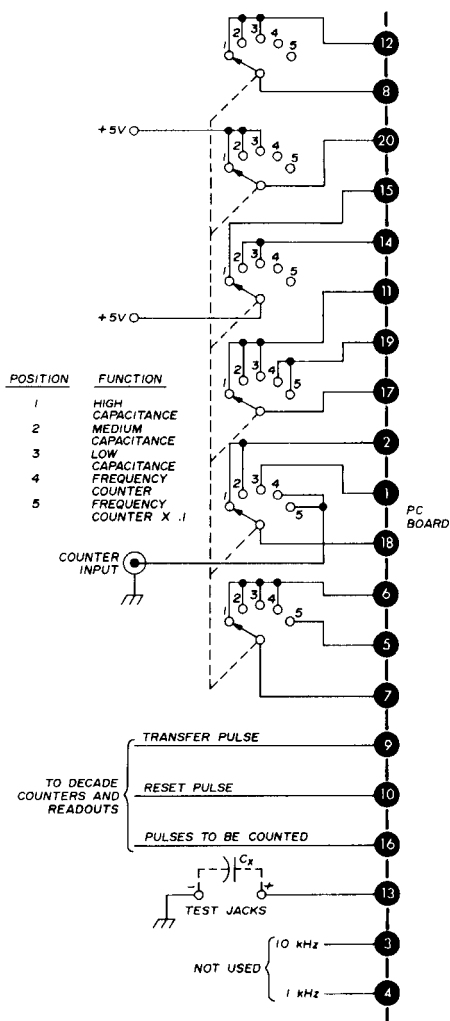


fig. 2. Wiring diagram for the function switch. Circled numbers refer to pads on the circuit board (see fig. 4).

formation stored in the latches (if used) to be shifted to the decoder/drivers for readout of the latest count.

A subsequent reset pulse is also generated during this interval which returns all counters to zero in preparation for the next 1-second counting period. These



tantalum but any substitute unit of 50- $\mu$ F or so may be used if it fits on the board.

Circuit pads are provided at all points being switched as well as at inputs and outputs. A pad is provided at the crystal

the blank board so that it just fits in the opening without moving around. Position one of the negatives over the opening with the proper side up and tape the edges to the cardboard frame. Turn the

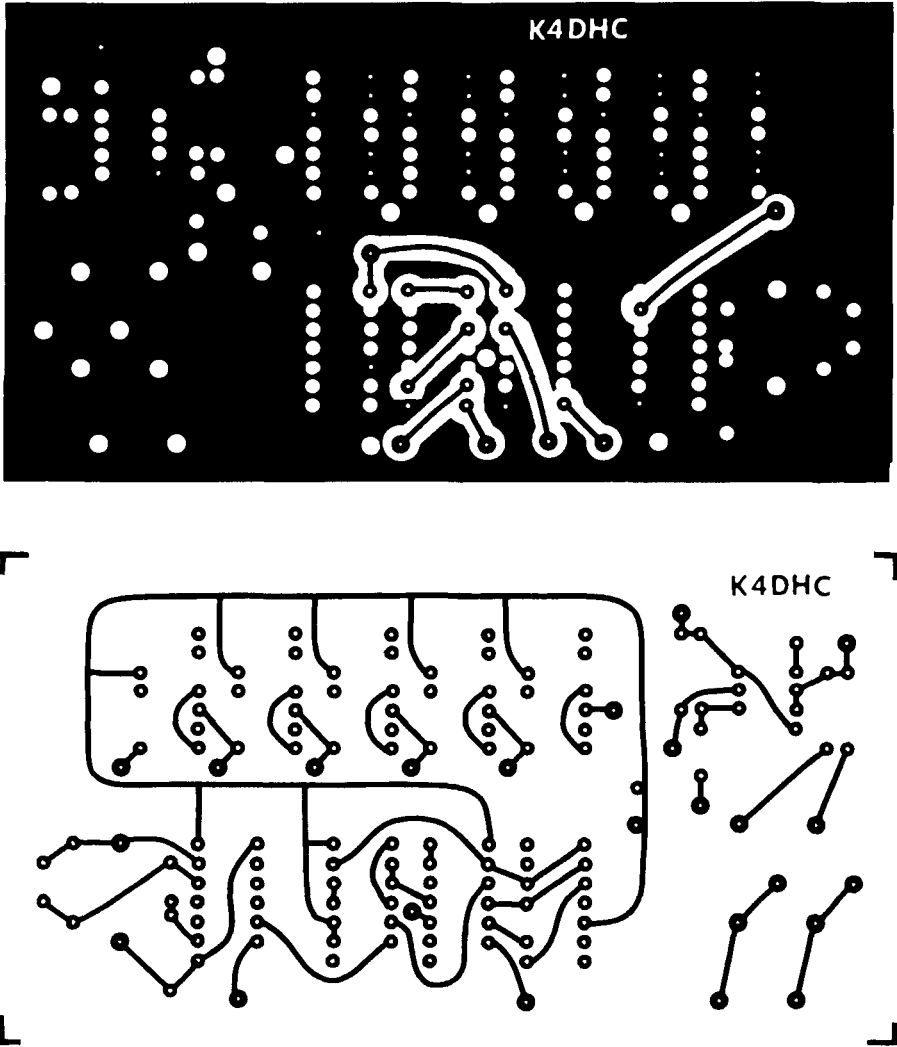


fig. 3. Full-size layout for both sides of the double-sided circuit board.


output as well as at each decade although not all frequencies will be used in this particular application.

The most practical scheme I've been able to devise for making double-sided PC boards is to cut out a cardboard frame for

frame over and place the second negative so that the two are back-to-back and in perfect registration. Tape this one along one edge so that it may be lifted to allow insertion of the blank PC board. After both sides have been exposed, develop

and etch in the normal manner. The board in the photograph was homemade in this way (see fig. 3 for the layout).

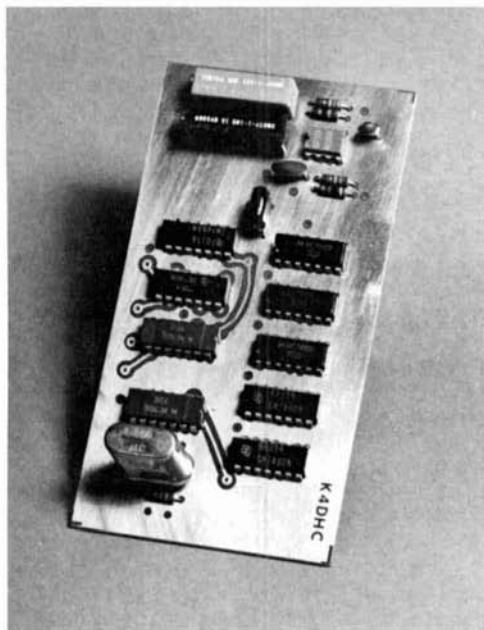If you are planning to build one of these instruments from scratch, you'll need several decades of counting and readout circuitry. Many of the advertisers in *ham radio* sell kits consisting of a



Component side of the printed-circuit board containing the timer and control circuits for the digital capacitance meter.

counter, a latch, a decoder/driver and a readout device, along with a PC board for easy assembly. Four decades would be the minimum required. Anything over that would be at the builder's discretion.

I used five stages because I happened to have five hybrid assemblies on hand which were suitable for this application. Each of these dual-inline packages contained a counter, a latch and a decoder/driver. I mated these with five homemade readouts and ended up with a neat 5-digit counter section.

I would have used one or two more stages if I'd had more of the hybrids since it would have made the frequency counter a little more useful. For capacitance

measurements, however, the five digits are adequate since the accuracy of the system doesn't really warrant any greater resolution.

If you already own a counter and don't mind tearing into it, you could do a little rearranging along the lines described here to add the capacitance measurement feature. In counters that provide for external gate control the output from the timer could be fed into this connection. In addition, a suitable trigger pulse must be brought out to fire the timer at the start of the cycle. Suitable clock pulses could also be brought out for the various operating ranges.

It is by no means mandatory that a PC board be used for assembly. The circuit described here was at one time made up on a piece of perforated board and wired from point-to-point. It worked just fine.

## calibration

All you need for calibration are a couple of fairly close tolerance capacitors of suitable values. With a capacitor connected to the test jacks and the instrument switched to the high range, adjust the 500-ohm trimmer for proper display of the value. Adjust the 50k trimmer for either of the two remaining ranges.

A capacitor of around 1.0  $\mu\text{F}$  could be used for setting both trimmers since there is an overlap between ranges. The more points you can check, of course, the more accurate the instrument. From my experience it seems reasonable to expect at least 10% accuracy across the operating range of 1000 pF to 1000  $\mu\text{F}$ .

Since this unit was intended primarily to measure large capacitors, readings should be close enough for most experimental work. They will also bear out the fact that most electrolytics have values a lot higher than marked.

It should be pointed out that the unit will read well over 1000  $\mu\text{F}$  but accuracy falls off rapidly above 1500  $\mu\text{F}$ . This is apparently due to shortening of the output pulse from the timer as the duty cycle increases. At the opposite end, reading values below 1000 pF seems to be

impractical due to bad jitter on the timer output pulse. The comparator input which the capacitor is connected across is a high impedance point and consequently picks up all kinds of noise and hum. Looking at the trailing edge of the output pulse on a scope will verify this. The end result is that the count gate sees a

decade divider. A calibrating trimmer capacitor could also be added in series with the crystal for precise adjustment of the clock. This would be primarily for improving frequency measuring accuracy.

Incidentally, you may find that some 1-MHz crystals won't oscillate at their

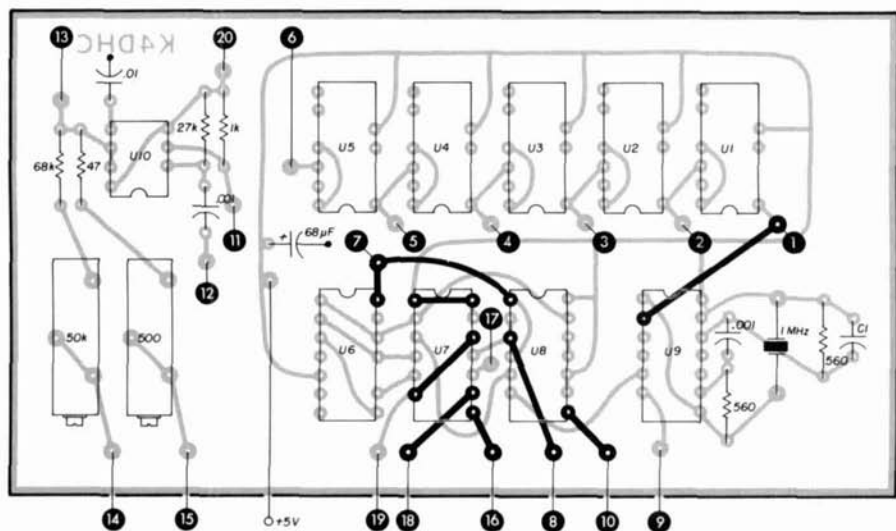


fig. 4. Component layout for the capacitance meter circuit board. Circled numbers correspond to connections on the function switch (see fig. 2). Bold traces are on component side of the printed-circuit board.

constantly varying count time which makes valid readings impossible.

All circuitry is powered from a single 5-volt supply capable of supplying the required current. In my instrument maximum current is about 1.5 amperes. Close regulation is not essential as voltage variations will not affect the timer output. When you are measuring electrolytic capacitors, remember that they should have a minimum rating of 6 volts just to be safe.

### summary

Parts of this circuit may be of interest to some readers even if not all of it. The control logic may be suitable for a counter you've been thinking of building or the timer circuitry may be extracted for use with an existing counter. The crystal oscillator could be modified for 10-MHz operation by adding another

fundamental frequency. A scope should be used to check this. Holes have been provided on the circuit board to install a capacitor across one of the feedback resistors if this problem is encountered. Try about 100 pF as a starting value and substitute values until you're sure the oscillator will start properly every time you fire up.

A preamplifier and conditioning circuit for the counter was not included on the board. There have been numerous examples of such circuits in all the amateur publications so finding what you want should not be too difficult.

### reference

1. Kenneth Macleish, W1EO, "A Frequency Counter for the Amateur Station," *QST*, October, 1970, page 15.

ham radio

# how to design L-networks

How to choose  
the proper L-network  
for your particular  
impedance-matching  
problem, and how to  
calculate the  
required component values

Robert E. Leo, W7LR, Electronics Research Laboratory, Montana State University

Graphical methods of designing L-networks have been presented several times in the past.<sup>1,2,3</sup> As shown in reference 1, there are eight possible L-networks for matching a pure resistance to *any* impedance. In most amateur cases the pure resistance is the 52-ohm coaxial transmission line, and the impedance is that at the base of a vertical antenna.

It is important to note that only certain networks can be used to match certain ranges of impedance. Also, because of possible mutual coupling, networks using two inductors are less desirable than the others. The lowpass filter network is the most desirable, but can be used only for some load conditions. One criteria which affects the choice of network is whether or not the antenna resistance is greater or less than 52 ohms. A more definite way of selecting the correct network is shown in the graphs that follow.

One of my former graduate students, John Lewis, studied the L-network situation and found that there are three different networks that will match any conceivable load impedance. He developed equations for these three networks and wrote a computer program that would, for a given problem, select the proper network and calculate the two necessary L-network element values. This article will give those equations, and describe them so that you can design your own L-networks, using simple equations and elementary arithmetic.


He developed the equations by writing the network equations for a given network, calling the input impedance  $R_i$  (50

ohms in our case). He then solved the equations for the network element values. For example, for the case of the network in fig. 1C

$$R_i = \frac{-jX_C (R + j(X_L + X))}{R + j(X + X_L - X_C)}$$

tions for  $X_L$  and  $X_C$ . John called these networks **A**, **B**, and **C** as shown in fig. 1.

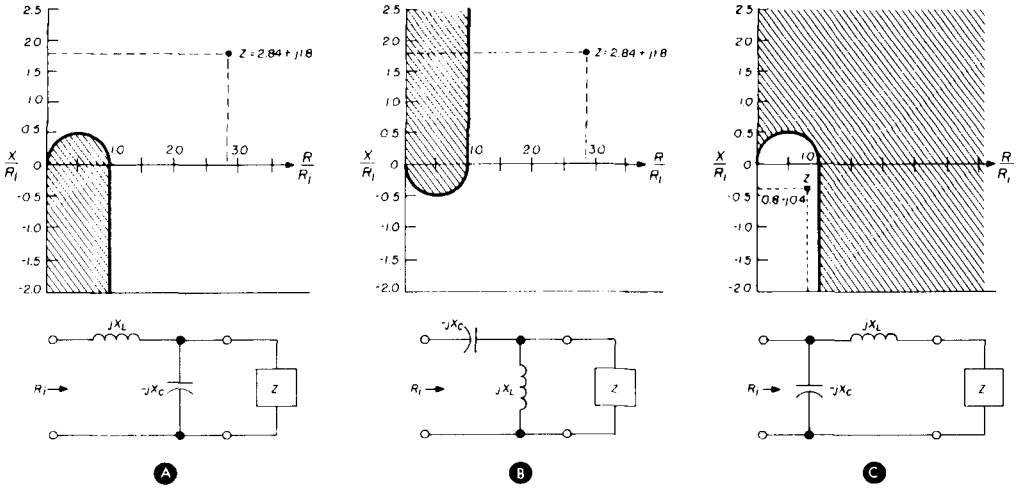The best way to show which load impedances each network can match is by means of a graph, first presented by Smith in *Electronics*.<sup>4</sup> The shaded part of each graph shows those load values which that



Network A  $X_C = \frac{-2 R_i X + k}{2(R - R_i)}$  (1)

$X_L = \frac{R_i X + X_C (R - R_i)}{R}$  (2)

Network B  $X_L = \frac{2 R_i X + k}{2(R - R_i)}$  (3)

$X_C = \frac{X_L (R - R_i) - R_i X}{R}$  (4)

Network C  $X_L = (\sqrt{R_i R - R^2}) - X$  (5)

$X_C = \frac{(X_L + X)^2 + R^2}{X_L + X}$  (6)

constant  $k = \sqrt{4 R_i^2 X^2 + 4 R_i (R - R_i) (X^2 + R^2)}$  (7)

fig. 1. Three types of L-networks which may be used for impedance matching. The accompanying graphs show the range of impedances which may be matched by each of the networks. Point Z in (A) and (B) is the normalized impedance used in the first example in the text. Point Z in (C) is the normalized load impedance used in the second example.

solving,  $X_L = (R_i R - R^2)^{1/2} - X$

$$X_C = \frac{(X_L + X)^2 + R^2}{X_L + X}$$

The steps in the solution are not shown here. To do that the first equation was expanded and the real and imaginary terms properly equated, resulting in solu-

particular network cannot match. The network can provide a match for any impedance in the non-shaded area. The graphs are normalized, which means that all graph values are divided by the impedance value of transmission line used (50 ohms). Thus, a load resistance of 50 ohms shows up on the graph as 1 unit horizontally.

When using the graphs and formulae presented in fig. 1, solve first for the net-

work element given in the left-hand column. For example, assume you have a vertical antenna with an input impedance of  $142 + j90$  ohms and want to feed it with 50-ohm coaxial cable. Therefore,  $R = 142$  ohms,  $X = 90$  ohms and  $R_i = 50$  ohms. Normalizing,  $R/R_i = 2.84$  and  $X/R_i = 1.8$ . In this case either network A or B must be used because the impedance ( $Z = 2.84 + j1.8$ ) falls into the forbidden region in the graph for network C.

To use network A, first calculate the constant,  $k$ , from eq. 7. Then find  $X_C$  and  $X_L$ , respectively, using eqs. 1 and 2.

$$k = \sqrt{(4 \cdot 50^2 \cdot 90^2) + (4 \cdot 50)(142 - 50)(90^2 + 142^2)} = 24516.48$$

$$X_C = \frac{-(2 \cdot 50 \cdot 90) + (24516.48)}{2(142 - 50)} = 84.33 \text{ ohms}$$

$$X_L = \frac{(50 \cdot 90) + 84.33(142 - 50)}{142} = 86.33 \text{ ohms}$$

To determine the component values for network B calculate  $X_L$  and  $X_C$  from eqs. 3 and 4, respectively. The constant,  $k$ , is the same as before.

$$X_L = \frac{(2 \cdot 50 \cdot 90) + 24516.48}{2(142 - 50)} = 182.15 \text{ ohms}$$

$$X_C = \frac{182.15(142 - 50) - (50 \cdot 90)}{142} = 86.32 \text{ ohms}$$

These values check with the graphical solutions shown in figs. 2 and 3 (see reference 3 for application with a 7-MHz vertical antenna).

As another example, assume that you want to match a 50-ohm transmission line to an antenna with an input impedance of  $40 - j20$  ohms. Therefore,  $R = 40$  ohms,  $X = -20$  ohms and  $R_i = 50$  ohms;  $R/R_i = 0.8$  and  $X/R_i = -0.4$ . The normalized input impedance is  $0.8 - j0.4$  ohms. This value can be matched by network C but

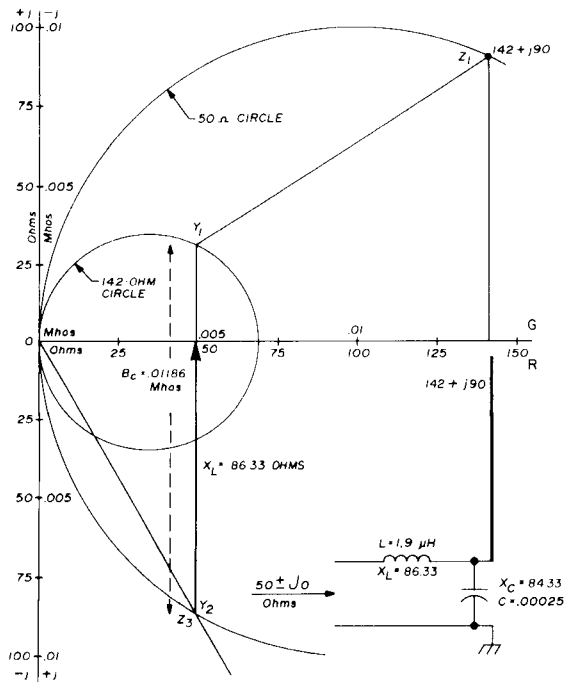


fig. 2. Graphical solution using the L-network of fig. 1A to match a load impedance of  $142 + j90$  ohms.

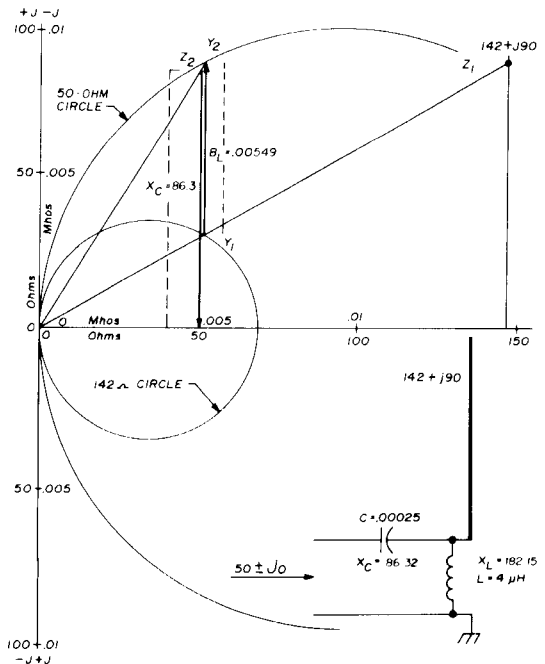


fig. 3. Graphical solution of the L-network of fig. 1B to match a load impedance of  $142 + j90$  ohms.

falls into the forbidden region in networks A and B.

To determine the proper values for network C first calculate  $X_L$ , using eq. 5. Then find  $X_C$  using eq. 6.

$$X_L = [(50 \cdot 40) - 1600]^{1/2} + 20 = 40 \text{ ohms}$$

$$X_C = \frac{(40 - 20)^2 + 1600}{40 - 20} = 100 \text{ ohms}$$

To check the correctness of these values it is necessary to calculate the impedance seen at the input terminals. From inspection, it can be seen that  $Z_C$  is in parallel with the series combination of  $Z_L$  and the complex load impedance  $Z$ . Using the formula for parallel impedances:

$$\begin{aligned} R_i &= \frac{(Z_C)(Z + Z_L)}{Z_C + (Z + Z_L)} \\ &= \frac{(-j100)(40 - j20 + j40)}{(-j100)(40 - j20 + j40)} \\ &= \frac{(-j100)(40 + j20)}{(-j100) + (40 + j20)} \\ &= \frac{-j4000 + 2000}{40 - j80} \end{aligned}$$

Multiplying by the conjugate:

$$\begin{aligned} &\left( \frac{-j4000 + 2000}{40 - j80} \right) \left( \frac{40 + j80}{40 + j80} \right) \\ &= \frac{400 \times 10^3}{8 \times 10^3} = 50 + j0 \end{aligned}$$

This network provides a perfect match to 50-ohm transmission line.

#### references

1. Robert Leo, W7LR, "An Impedance-Matching Method," *QST*, December, 1968, page 24.
2. I. L. McNally, W1NCK, Henry S. Keen, W3CTK, "Graphical Design of Matching Networks," *ham radio*, December, 1969, page 26.
3. Robert Baird, W7CSD, "Designing Impedance-Matching Systems," *ham radio*, July, 1973, page 58.
4. Phillip H. Smith, "L-Type Impedance Transforming Circuits," *Electronics*, March, 1942, page 48.

ham radio

# NEW RINGO RANGER

## for Amateur FM

Get extended range with this exciting new antenna. A one eighth wave phasing stub and three half waves in phase combine to concentrate your signal at the horizon where it can do you the most good.

6.3 dB Gain over 1/4 wave whip

4.5 dB Gain over 1/2 wave dipole

ARX-2 146-148 MHz  
\$22.50

ARX-450 435-450 MHz  
\$22.50

ARX-220 220-225 MHz  
\$22.50

Extend your present AR-2 Ringo with this RANGER KIT. Simple installation.

ARX-2K .....\$8.95

IN STOCK AT  
YOUR LOCAL DISTRIBUTOR

Cush  
Craft  
CORPORATION

621 HAYWARD STREET  
MANCHESTER, N. H. 03103

# RTTY message generator

Complete construction  
details for  
an RTTY  
message generator  
that uses  
TTL digital logic

For a number of years, the users of teletypewriter services have relied on an automatic response from an interrogated RTTY terminal unit to confirm completion of a desired traffic circuit. The interrogated terminal, upon command, generates a station identification code or message such as, DE KX6IT. This message is usually generated by an electro-mechanical device consisting of a number of coded bars on a rotating drum, momentarily closing electrical contacts.

With the advent of low-cost, multi-function integrated circuits, it is feasible

to generate the message using digital logic. This increases reliability and makes maintenance easier as well as lowering the cost. Moreover, some electro-mechanical message generators are mechanically peculiar to a specific type or family of teleprinters. The digital logic method is directly applicable to any machine or circuit of any family of teleprinters using compatible signaling codes.

## RTTY signaling code

The presently used Baudot (Murray) RTTY code is a binary code, a two-state condition, such as the presence or absence of current. As applied to most teletypewriter circuits, it is a condition of current flowing in a loop (*mark*) or no current flowing in the loop (*space*). Each printed character or machine function is determined by the sequence of mark and space pulses received by the machine.

The format of the signaling code depends on the maximum number of different characters to be printed or functions to be performed by the machine. The two most common arrangements used are the 5-level and 8-level formats. The term *level* refers to the number of unit intervals or pulses in the intelligence-determining portion of the code. Each unit interval is either a *mark* or *space* as determined by the code for the desired character. The 5-level code has  $2^5$  (32) character permutations available and the 8-level code has  $2^8$  (256) available permutations.

To keep the transmitting and receiving machines in synchronization a start pulse

C. A. Ellsworth, W6OXP, W. G. Malloch, W8KCO



is placed in front of the group of intelligence pulses. A stop pulse is placed at the end of the group of intelligence pulses to complete the synchronization function. The start pulse is always a *space* condition and has the same pulse width or unit interval as an intelligence pulse. The stop pulse is always a *mark* condition and its minimum duration may be up to two unit intervals.

The 5-level code may be divided into three subcode types, depending on the width of the stop pulse. For example, a 60 word-per-minute 5-level code character includes the start pulse and five intelligence pulses, each of which has a pulse width of 22 milliseconds. Each 22-ms pulse or bit may be referred to as a *unit*. If the stop pulse in this group is also 22-ms wide then the group is called a 7-unit code. If the stop pulse is 31-ms wide then it is a 7.42-unit code. The 7.42-unit code is the most common 5-level code.

Another code in use is the 7.5-unit code where the stop pulse is 33-ms wide. The intended effect of the longer stop pulse is to decrease the amount of message garble under marginal operating conditions. However, the longer stop pulse has the undesirable effect of slightly decreasing the circuit speed capability.

## functional description

The design objective was a simple, semi-programmable, all-electronic message generator using low-cost TTL IC logic packages and meeting the following requirements:

1. The required serial message format is: letters (LTRS), space, DE, space, K, X, figures (FIGS), 6, letters (LTRS), I, T, space, carriage return (CR), and line feed (LF).
2. The message generation cycle is initiated by an external momentary contact closure and/or a TTL compatible negative-going pulse.
3. The device must be self-stopping at the end of the message generation cycle.

4. The device keyer output must be compatible with any normal RTTY loop without regard to loop polarity or voltage level.
5. The device's message must be field programmable, either by means of plug-in boards or minor hardware changes, or both.


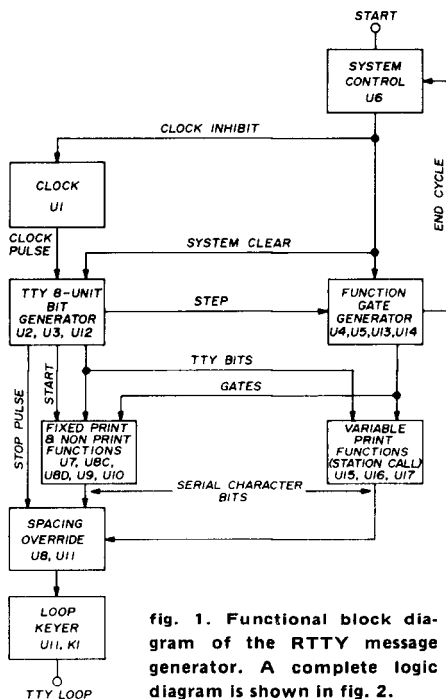


fig. 1. Functional block diagram of the RTTY message generator. A complete logic diagram is shown in fig. 2.

Fig. 1 illustrates the operation of the device at a basic functional block diagram level. A detailed logic diagram is shown in fig. 2.

**System control.** When the circuit is in an idle state, U6 generates a signal that inhibits 2 clock pulse generation (U1) and sets the 8-unit big generator and function gate generators to a cleared condition. On receipt of an external start signal, system control removes the clock inhibit and system clear signal. The device now begins the message generation cycle. At the end of the message, the function gate generator provides an end-of-cycle signal which returns system control to idle

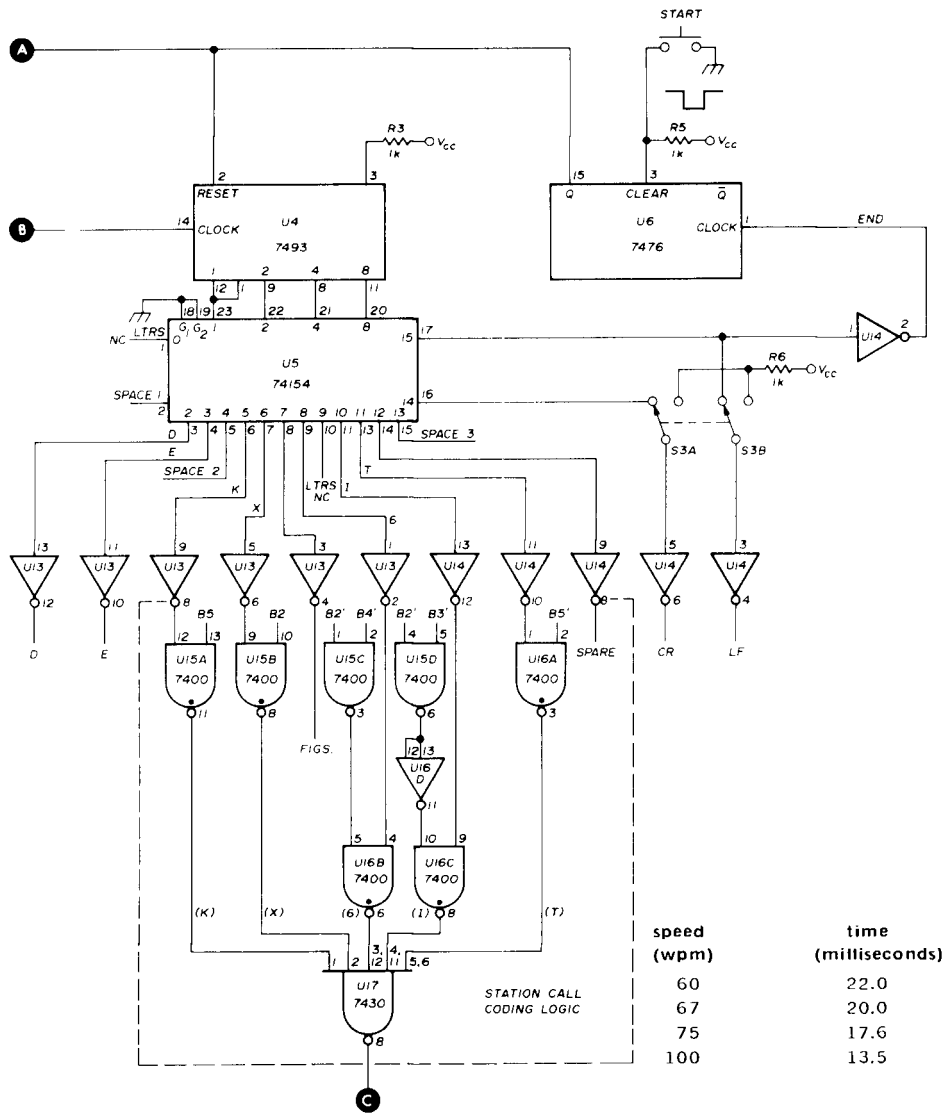



- K1 spst printed-circuit relay (Clare LA-005, 5-volts, 380 ohms, DIP package)
- K2 spst normally closed reed relay (Grisby-Barton GB821B-2)
- S1,S2 spdt toggle switch
- S3 dpdt toggle switch
- U1 dual NAND Schmitt trigger (SN7413)
- U2,U4 4-bit binary counter (SN7493)
- U3 BCD-to-decimal decoder (SN7442)
- U5 4-line to 16-line decoder/demultiplexer (SN74154)
- U6 dual J-K master-slave flip-flop (SN7476)
- U7 triple 3-input positive NAND gate (SN7410)
- U8,U9 quadruple 2-input positive NAND gate (SN7400)
- U10,U17 8-input positive NAND gate (SN7430)
- U11 quadruple 2-input positive NAND buffer (SN7437)
- U12,U13 hex inverter (SN7404)
- U14

status, thereby terminating the message cycle.

**Clock.** IC U1 is connected as a gate-controlled pulse generator. The time between the negative-going edges of two adjacent pulses is set to equal the desired unit or bit width, i.e., 22 ms for a 5-level, 60-wpm machine.

**RTTY 8-unit bit generator.** The clock pulse from U1 is fed to the 4-bit binary counter, U2. The output of the binary counter is decoded by 1-of-10 decoder U3. This decoder sequentially produces eight unit bits each character generation cycle. In order of generation they are start, five intelligence bits and stop, which is 2 units in length. At the end of the 7th unit bit (halfway through the stop pulse) a step pulse is applied to the function gate generator. Complements of the bits are available through hex inverter U12. An 8-unit code is used instead of the standard 7 or 7.42-unit codes in the interest of circuit simplicity and minimum package count.

**Function gate generator.** The function gate generator is functionally similar to the 8-unit bit generator described above. The decoder section is a 1-of-16 decoder. The active function gate is advanced to the next decoded line each character generation cycle of the 8-unit bit generator. The last (16th) function gate pulse is inverted and applied to system control, U6, to terminate the message generation cycle. ICs U13 and U14 invert all function gates to match the character coding logic.

**Fixed character.** The 2-input and 3-input gate ICs in this block combine the active function gate and selected intelligence bits from the 8-unit bit generator to form the desired fixed print and non-print RTTY functions.

**Variable character.** This block is functionally similar to the fixed character block, combining function gates and selected bits to form the desired printing functions. It is labeled variable as this is the area of the circuit that can be

programmed for different station call signs by use of plug-in circuit boards.

**Spacing override.** To realize gate and interconnection economy in the fixed and variable character circuits during the generation of certain characters, it was convenient to allow a spacing condition to exist at the outputs of these blocks during the stop-pulse generation period. The logic gates in the spacing override block ensure that the stop pulse is always fed to loop keyer, even if a spacing condition from the fixed or variable character blocks happens to be present simultaneously with the stop pulse.

**Loop keyer.** ICs U11C and U11D drive the loop keying relay, K1. Only one gate is used when driving a normally-open contact relay. The second gate is used as an inverter if a normally-closed contact relay is used. A high-voltage transistor could replace the relay if loop polarity is observed.

## character coding logic

The idle condition of a teleprinter is the marking (loop current flowing) state. Moreover, examination of a coding chart reveals a slight preponderance of *mark* over *space* in the code as a whole if you disregard the seldom used *blank* character. Thus, it is logical to set up a condition at the loop keyer where it is only necessary to create a spacing condition at the proper intervals to generate the desired message.

The first space pulse in any character or machine function is the start pulse. In the letters (LTRS) function, where all five information pulses are marking, the start pulse is the only spacing pulse in the entire code group. Therefore, to generate a LTRS function, it is only necessary to apply the start pulse to the loop keyer — and the machine performs the LTRS function.

Refer to the logic diagram in **fig. 2** to follow the formation of the LTRS function. Initially, the circuit is in the standby state. Clock U1 is inhibited. Binary counters U2 and U4 are set to zero count.

One-of-ten decoder U3 is low on output zero and is high on the remaining 7 outputs (outputs 8 and 9 are not used for 5-level codes).

Output zero of U3 (pin 1) is labeled stop 2. This is the last half of the 2-unit stop pulse and is applied to U8A as a low level. The remaining input to U8A is a

characters with only one or two information bits marking, it is convenient to set up the character coding logic so that a spacing condition (a high level at the output of U17) is applied to the remaining input of U11B during the last half of the stop pulse. Thus, a low on one input of U11B overrides the spacing condition, keeping the output of U11B high. This, in turn, keeps the loop in the marking state during the entire stop-pulse period.

To initiate generation of the message and the first character (LTRS), momentarily depress the start switch, S4. This sets the Q output of flip-flop U6 to low, removing the inhibit from the clock, U1, and removing reset from U2 and U4. The first negative-going edge of the clock pulse toggles binary counter U2, causing output zero (stop 2) of U3 to go high and output 1 (start) of U3 to go low.

At this time both inputs of U8A are high, its output is low, and the output of U8B is now high and applied to one input of both U11A and U11B. Simultaneously, output 1 (start) of U3 is low and is applied to one input of U10, causing the output of U10 to go high. This high is applied to the remaining input of U11A. Both inputs of U11A are now high, causing the output to go low, creating a spacing condition at the loop keyer.

Thus, it may be seen that the loop is in a spacing condition immediately following arrival of the first negative-going edge of the clock waveform. It remains in this condition until the next negative-going edge of the clock again toggles binary counter U2; then output 1 (start) of U3 goes high and output 2 (intelligence bit 1) goes low. As soon as output 1 goes high, the output of U10 goes low, and the resulting high output of U11A causes the loop keyer to return to the marking condition. This sequence completes the generation of the start pulse, which is always a spacing condition.

Successive clock pulses applied to binary counter U2 move the low output of U3 through outputs 2 through 6 (intelligence bits 1 through 5). Since the function gate generator, U4 and U5, is still set

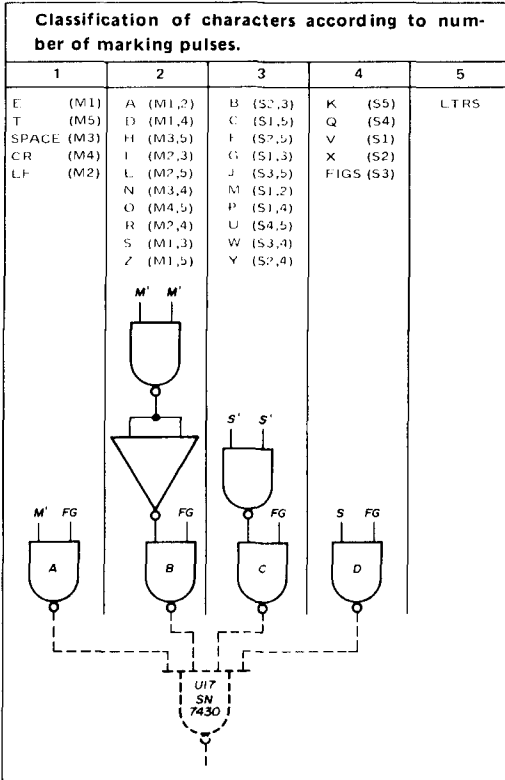


fig. 3. Callsign programming chart.

high level from output 7 (stop 1). The output of U8A is a high, inverted by U8B, and applied to both U11A and U11B as a low. Therefore, with one input of both U11A and U11B at a low level, the output of these AND gates will always be high, regardless of whether highs or lows appear at the remaining gate inputs.

For example, in the case of generating

to zero, and because output zero of U5 (labeled LTRS) is not connected, no space pulses are generated during the periods of the five intelligence bits and the loop keyer remains in the marking state. Clock pulses continue to move the counter and decoder through 7 (stop 1)

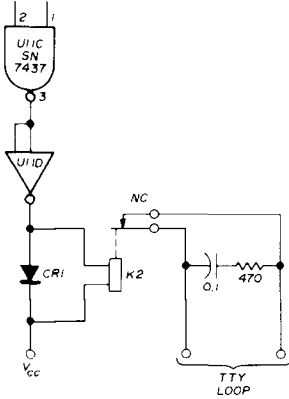


fig. 4. Alternate loop keyer circuit using a normally-closed relay. Relay K2 is a Grigsby-Barton 5-volt, 80-ohm spst relay in a DIP package. Diode CR1 is a silicon diode.

and returns it to output zero (stop 2). These two units of stop pulse complete the formation of the LTRS function.

### space function

The machine space function character code has only bit 3 of the five intelligence bits in the *mark* state. Examination of 1-of-16 decoder U5 in fig. 2 shows that output zero (pin 1, labeled LTRS) is low during the idle condition and during the first character generation cycle of U3. At the time output 7 (stop 1) goes high, a pulse is applied to the clock input to U4. This changes the count from zero to 1 and moves the active low from output zero to output 1 in U5.

Output 1 from U5 (labeled *space 1*) is connected to one input of U7A through switch S1. This input goes low (all three inputs were high), the output goes high and is applied to U9B. At this time the B3 input to U9B is still high so the output goes low, causing the U10 output applied to U11A to go high. However,

since the stop 2 bit applied to U8A is now low, the remaining input to IC-U11A, is also low, and, the loop keyer, U11C, continues to hold relay K1 in the marking state.

The next clock pulse applied to U2 moves the active low output of U3 to *start*. This low is applied to pin 12 of U10, but because of the low already on pin 3 of U10, the output and input to pin 9 of U11A remain high. At the same moment the active low in U3 moves from *stop 2* to *start*, the output of U8B goes high and the U11A output goes low, creating a spacing condition at K1 for the duration of the *start* pulse. Successive clock pulses continue to move the active low through the outputs of U3.

Because input to pin 3 of U10 remains in the high state, the loop keyer remains spacing throughout the periods of information bits 1 and 2. At the instant bit 3 goes low, the signal at pin 4 of U9B goes from high to low and U10 has all inputs high. This causes the loop keyer relay K1 to go to the marking condition for the duration of intelligence bit 3. Relay K1 returns to a spacing condition during the periods of bits 4 and 5 and then goes to marking during *stop 1* and *stop 2* periods. The *space* machine function character is now complete.

### message characters

Completion of the *space* machine function character described above has advanced the count in U4 to three. Decoder U5 is now low on pin 3, labeled D. This low is inverted by one section of U13 and applied as a high level to pin 9 of U9D. The character D has intelligence bits 1 and 4 marking. These two bits are applied to the inputs of U7B. Both inputs are high at all times except during the periods of bits 1 and 4. Thus, a spacing condition exists at the output of U9D during the formation of the letter D except during the periods of bits 1 and 4, which are marking.

It is now apparent that as each character is completed, the gate function generator, U4 and U5, is advanced one count, and the associated active output is

applied to a logic gate or group of logic gates, enabling the appropriate selection of marking or spacing intelligence bits from the bit generator, U2 and U3, to form the desired characters.

Character generation continues until the beginning of the 17th pulse input to U4 which sets output 15 (pin 17) of U5 from low to high, and applies a negative-going level to the clock input (pin 1) of flip-flop U6. This causes the U6 Q output to go low, resetting both binary counters to zero and inhibiting the clock, U1, returning the message generator to idle. Should the clear input (pin 3 of U6) be held low continuously, it will override the end-of-cycle signal on pin 1 and the message generator will repeat itself until the low on pin 3 is removed.

## programming

Switch S1 is provided to inhibit the *space 1* machine function if a space is not desired before the first printed character in the message. When *space 1* is inhibited, the message generator forms the non-printing machine function LTRS. Switch S2 inhibits a space after the last printed character in the message. Switch S3 inhibits the carriage return (CR) and line feed (LF) machine functions when a continuous line of print across the page is desired.

As many as four different character gating configurations are required for programming the generator. The gating configuration selected for a specific character is dependent upon the number of marking pulses in the character. **Fig. 3** tabulates characters according to their marking pulse content and illustrates the appropriate gating configuration. The notation FG at a gate input in **fig. 3** indicates connection to the inverted function gate originating at U5. The notation M' indicates connection to the appropriate marking bit from the bit generator. Note that marking bits are selected only when the character contains one or two marking pulses.

The notation S' indicates connection to the appropriate spacing bit from U3. Spacing bits are selected when the desired

character contains three or four marking pulses. The numerals to the right of each character in columns one and two refer to the location of marking pulses in the 5-bit pattern. The numerals in columns three and four refer to the location of spacing pulses in the bit pattern.

In gate D (**fig. 3**) note the absence of a prime mark after the S input reference. This means that the spacing bit for characters in column four must be inverted instead of coming directly from the outputs of U3. Refer to connections in U8C and U12, pin 8 in **fig. 2** for an example.

As previously covered in the text, no gating or connections are required for the LTRS function.

## construction

The physical configuration of the prototype message generator consists of two printed-circuit boards (main and station call) with edge connectors, a regulated power supply and a fully enclosed aluminum cabinet to provide radio frequency interference shielding as well as control mounting facilities. The main printed-circuit board is a universal dual in-line package (DIP) type breadboard with 15 sets of DIP IC pads for the 14 ICs and one DIP reed relay. Each IC pin pad has up to three solder pads for interconnection. The station call board is about half the size of the main circuit board and contains the three ICs indicated within the station call coding logic box in **fig. 2**.

Total cost of the IC packages for this unit is less than ten dollars. The cost of all components including ICs, power supply and transformer, but not including the printed-circuit boards, connectors and cabinet, amounts to less than \$35.00. These costs are based on single unit prices.

Although not indicated in the logic diagram or in the parts list, the prototype unit uses a 4-position, single-pole rotary switch to select one of four 1000-ohm trimpots (R1) in the clock circuit. Each trimpot is adjusted for one of the four operating speeds listed in the speed-time chart in **fig. 2**. Also not shown on the

logic diagram are  $V_{cc}$ -to-ground bypass capacitors for ICs U1 through U6. These are 0.1- $\mu$ F disc ceramic capacitors mounted as closely as possible to the  $V_{cc}$  and ground pins of each of the indicated ICs. These capacitors are required for suppressing noise generated by internal IC switching transients.

The spark suppression network (C2, R7) across the contacts of the keying relay is mandatory. Operation of the device without this network will result in premature failure of relay contacts, and in erratic operation of the circuit due to noise. Diode CR1 suppresses the voltage transient caused by back-emf generated in the coil of the relay at de-energization.

The normally open, spst reed relay, K1, is the type actually used in the prototype. It is less costly and easier to obtain from supply sources than the normally-closed, spdt reed relay, K2, shown in the alternate loop keyer configuration in fig. 2. Actually, the alternate configuration is preferred for most applications because loop continuity is maintained when power is removed from the unit.

The power supply consists of a 6.3 volt, one ampere power transformer and a rectifier-regulator circuit with 1% line-load regulation of the 5-volt dc  $V_{cc}$  output. The  $V_{cc}$  supply should be maintained within the limits of 5 volts,  $\pm$  5%.

## troubleshooting

Troubleshooting improper operation is simplified if a typing reperforator is available as this permits recording of all normally non-printing machine functions on paper tape. Should a character not be the same as programmed, correlation of the tape readout with the appropriate area of the logic diagram should assist in isolating the problem. Experience has shown that almost all initial checkout problems in a handwired prototype result from improper or missing connections.

Rf interference can cause problems, although the prototype has functioned without error in the immediate vicinity of gain radiators with power inputs of 100 watts rms at 14 MHz. Most rfi problems

can be cured with proper application of shielding and installation of bypass capacitors on all the input and output lines.

## summary

A simple, reliable, low-cost method of generating short RTTY messages has been described. An operational prototype message generator using state-of-the-art integrated circuits has been constructed and tested under field operation conditions. This unit was built with components costing less than thirty-five dollars at unit quantity prices.

## bibliography

1. *Principles of Telegraphy (Teletypewriter)*, NAVSHIPS 0967-255-0010, Department of the Navy, Electronic Systems Command, June, 1967.
2. *Designing with TTL Integrated Circuits*, Texas Instruments Electronics Series, McGraw Hill Book Co., New York, 1971.
3. *The Integrated Circuits Catalog for Design Engineers*, Texas Instruments Incorporated, 1972.

ham radio



"I've discovered how to keep it playing a little longer at a time. I put a time-lag fuse in the box."



# Before you buy... take time to compare

WHEN YOU'RE GOING 2 FM . . . AND YOU MATCH ANY MEMBER  
OF THE INOUE-ICOM TEAM . . . feature for feature . . .  
. . . spec for spec . . .

We think we know how you will come out.



For example, compare these features on the IC-22  
against anything else available in its price class . . .

1. 22 channel capacity . . . plenty of room for today's and tomorrow's use.
2. 10 xtals installed . . . (that's about \$45 worth of xtals included in the price of the rig!)
3. Solid state T-R relay . . . nothing to wear out.
4. Large speaker built in for high noise applications.
5. 1/10 watt switch power saving option.
6. Mosfet front end and 5 helical resonator cavities.
7. Noise canceling mike included.
8. Quick disconnect mobile mount . . . taking the rig in and out is a snap!
9. Trimmer caps on both trans. and rcv. on all 22 channels . . . with a discriminator output jack in the back to let you get on and stay on freq.
10. PLUS the '22 is one good lookin' compact rig that you will be proud to put in your car—(the XYL won't mind it either)—with soft green back lighting on the front panel and a light to silently let you know you are getting out . . . and a second light to let you know there is an incoming signal (even though you may have the volume down).

Feature for feature . . . \$ for \$ . . . at \$289  
. . . the Inoue IC-22 just can't be beat anywhere . . .

*See the unique Inoue IC-22 and the rest of the ICOM family  
at your nearby ICOM dealer . . . today . . . !*

Distributed by:



— Dealerships Available —

**ICOM WEST, INC.**  
Suite 232 — Bldg 11  
300 - 120th Ave. N.E.  
Bellevue, Wash. 98005  
(206) 454-2470

**ADIRONDACK  
RADIO SUPPLY**  
185 West Main Street  
Amsterdam, N.Y. 12010

**ICOM EAST**  
Div ACS, Inc.  
Box 331  
Richardson, Tex. 75080  
(214) 235-0479



## universal frequency standard

A precision  
frequency standard  
featuring a  
high-accuracy crystal,  
stable transistor  
oscillator and  
TTL logic

This frequency standard has been designed to supply precision frequencies for several purposes. Its main use is with my station receiver as a precise and reliable frequency calibrator. It may also be used as a digital counter time base, a scope calibrator or to drive a digital clock. With all integrated circuit packages installed on

the board there are no less than eighteen frequencies available extending from 2 MHz down to 1 Hz. Ten of these, of your choice, are connected to a rotary switch for calibrator use while the lower frequencies below 1 kHz that would not normally be used with the station receiver, are picked off terminals on the circuit board by a small clip lead when needed.

The design is flexible. If you do not need the versatility of the complete unit, the photo shows a frequency standard that will provide markers at 1 and 2 MHz, and at 500, 250, 100, 50, 25 and 12.5 kHz with the installation of only three digital IC packages. Provision is made on the circuit board for as many or as few output frequencies as are likely to be needed.

### circuit features

Features include excellent frequency stability, front panel calibration and a precise, self-contained, regulated power supply. An adjustable level control is included so the calibrator output can be matched to incoming signals such as WWV for really accurate zeroing or advanced full on for strong, clear markers.

Bert Kelley, K4EEU, 2307 South Clark Avenue, Tampa, Florida 33609

With proper temperature compensation, the frequency standard will stay within 1 Hz of WWV at 10 MHz over an extended period of time with no adjustment.

This precision is not needed if the unit is used only to find band edges or set the receiver graticule. However, for frequency measurement or use as a time base for a

move, capacitors change value. Solid-state circuitry has substantial advantages over vacuum-tube circuits; much heat is eliminated, components run cooler and the crystal is driven at the low levels recommended by the manufacturer. However, a substantial amount of drift can come from the semiconductor alone.

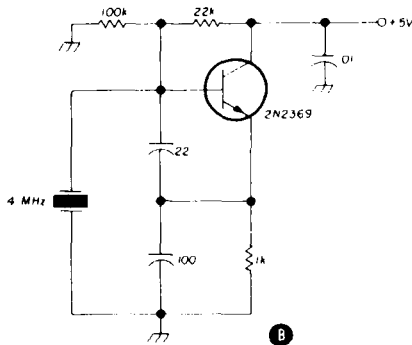
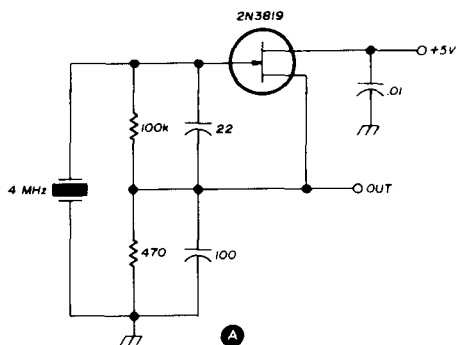


fig. 1. Solid-state crystal oscillator circuits. Fet circuit in (A) is considerably more stable than the bipolar circuit shown in (B). For a more stable bipolar oscillator circuit, see fig. 2.

counter or digital clock, you need all the accuracy you can get. The best reason for going first class is that it costs little more, and probably less, in this do-it-yourself project. The required stability can be obtained with inexpensive construction.

The oscillator circuit in this calibrator was first used as a stable time base for a digital clock and later in a receiver.<sup>1</sup> Several circuits evaluated in drift tests showed the Clapp-Colpitts to be most stable — not a new circuit, but seldom used in recent designs. While both the circuit used and the TTL logic is familiar, it is the combination of circuit, crystal and construction that makes this calibrator better. Stability comes when a few hertz drift is removed or greatly reduced from each of several sources. A 10-Hz drift caused by a trimmer might be tolerated, but when the drift from other sources is combined, the total becomes excessive.

Most oscillator circuits would cause even a perfect crystal to drift. Voltage and temperature changes cause changes in the semiconductor's internal impedance. Trimmers don't stay where set, wires

How much? Two circuits are shown. Fig. 1A shows a fet oscillator circuit using crystals in the 1- to 9-MHz range. The crystal load for 32-pF is sometimes brought on frequency with a small trimmer. If this circuit is built so the semiconductor is isolated, it can be heat cycled without affecting other components and the drift can be measured on a


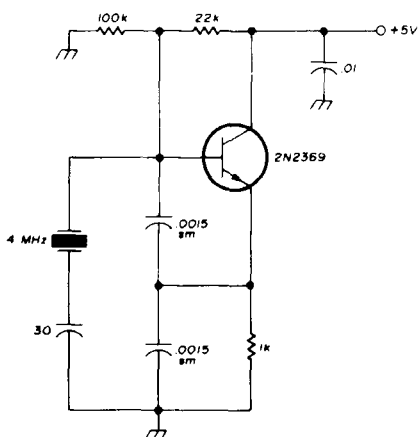


fig. 2. This transistor crystal oscillator circuit is stable because impedance changes are swamped out by the 1500-pF silver-mica capacitors.

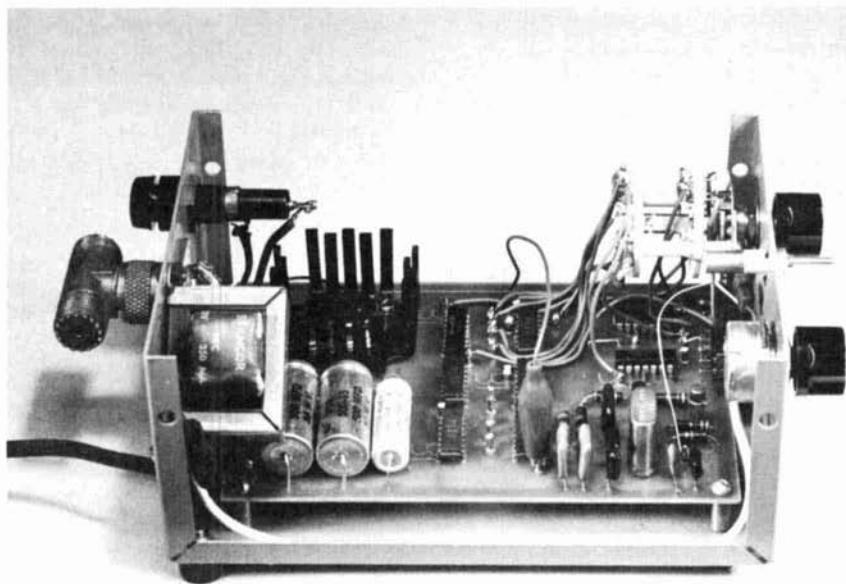

Frequency standard and power supply are installed in a 3x5x7-inch (7.6x12.7x17.8-cm) Minibox.

digital counter. The best of several fets caused a change of 12 Hz at 4 MHz with a 5-degree ambient temperature variation.


Fig. 1B shows a transistor in a similar oscillator circuit, not recommended, but sometimes used. Although not as sensitive as the fet to temperature, a change of only one volt caused a 70-Hz frequency shift. If this circuit is modified as shown in fig. 2, there is a substantial improvement. Changes of ten degrees and one volt did not cause a frequency change

readable on the counter. The transistor case could be heated with a soldering iron to the point where it burned the fingers with a 2 Hz change registered at 4 MHz.

These experiments show both the extent of drift that can be contributed by the semiconductor and indicates the solution. The more stable the capacitance used across the transistor, the better the stability. The 1500-pF capacitors have a very low reactance at 4 MHz, swamping out any other impedance changes in the circuit. This circuit will not oscillate with some transistors because there must be enough gain to sustain oscillation. This requirement is met by the Motorola HEP715, a pnp device with a typical beta of 120. Other transistors with similar current gain can be substituted.
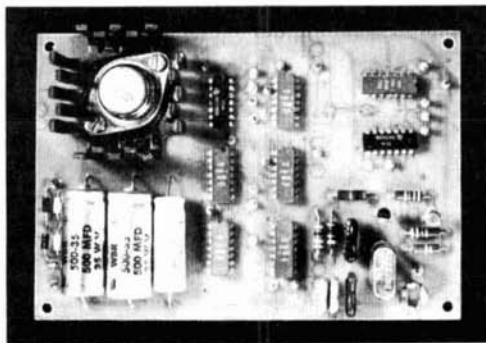
### the crystal

Some time ago while working with digital counter time bases<sup>2</sup> I noticed that the ordinary 100-kHz crystal was not as stable as it might be. A time base derived from the power line was nearly as accurate. Although used in amateur calibrators for many years, the 100-kHz rock is



Printed-circuit board with all logic packages installed, as would be required for driving a digital clock or a frequency counter. One jumper is used.

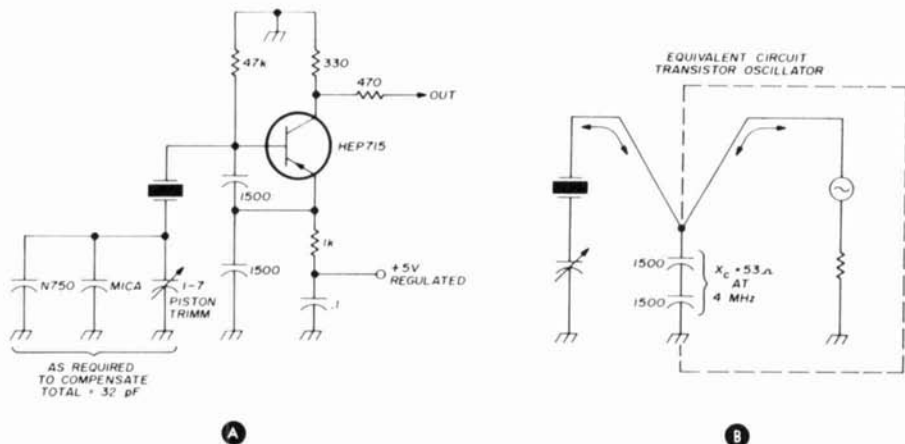



fig. 3. Stable transistor crystal oscillator circuit. Equivalent circuit in (B) shows how 1500-pF capacitors swamp out any internal impedance changes which would cause the output frequency to drift.

not a good choice as it must be stabilized by use of an oven; this adds bulk, expense and a heater supply.

A better crystal for a frequency standard is the high-accuracy 4-MHz crystal recommended by W6FFC.<sup>3</sup> High accuracy as used here means the crystal drifts less, and at a predictable rate. Although cheaper crystals in the 1- to 5-MHz range are better than those at 100 kHz, they are subject to random drift which is difficult to compensate. Therefore, it is important to obtain the better quality crystal. They are manufactured by both Sentry and International and cost less than \$10.\*


Note the drift characteristic curves for a typical AT-cut crystal in fig. 4. As the temperature increases, the crystal frequency decreases. Drift can be almost entirely eliminated at room-temperature operation which most amateurs are interested in by selecting the proper value of negative coefficient compensation capacitor. Curve A requires the most compensation while curve B requires little if any. A crystal cut for a 32-pF load allows about 30 pF for compensation with the piston trimmer adding the 2 or 3 pF needed to pull the crystal to the exact frequency.

A new crystal might require anything from a maximum of 30-pF (N1500) to a 30-pF silver mica (NPO), depending on its temperature vs frequency characteristic. Since there is no way to know what will be needed, it is advisable to have a supply of different values of N750 and N1500 coefficient capacitors on hand, with small silver micas to pad the total to 30 pF, before starting any temperature compensation work. A piston trimmer is recommended because of the smoother adjustment and lack of drift. It is also easier to determine if capacitance is being added or removed, useful information when temperature compensating the calibrator.

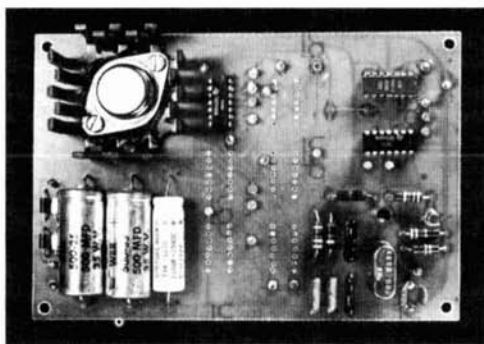

If you don't need the versatility of the complete unit, this photograph shows a frequency standard that will provide markers at 1 and 2 MHz, and at 500, 250, 100, 50, 25 and 12.5 kHz with the installation of only three logic packages.

\*Write for their catalogs. Sentry Manufacturing Company, Crystal Park, Chickasha, Oklahoma 73018; International Crystal Manufacturing Company, 10 North Lee, Oklahoma City, Oklahoma 73102.

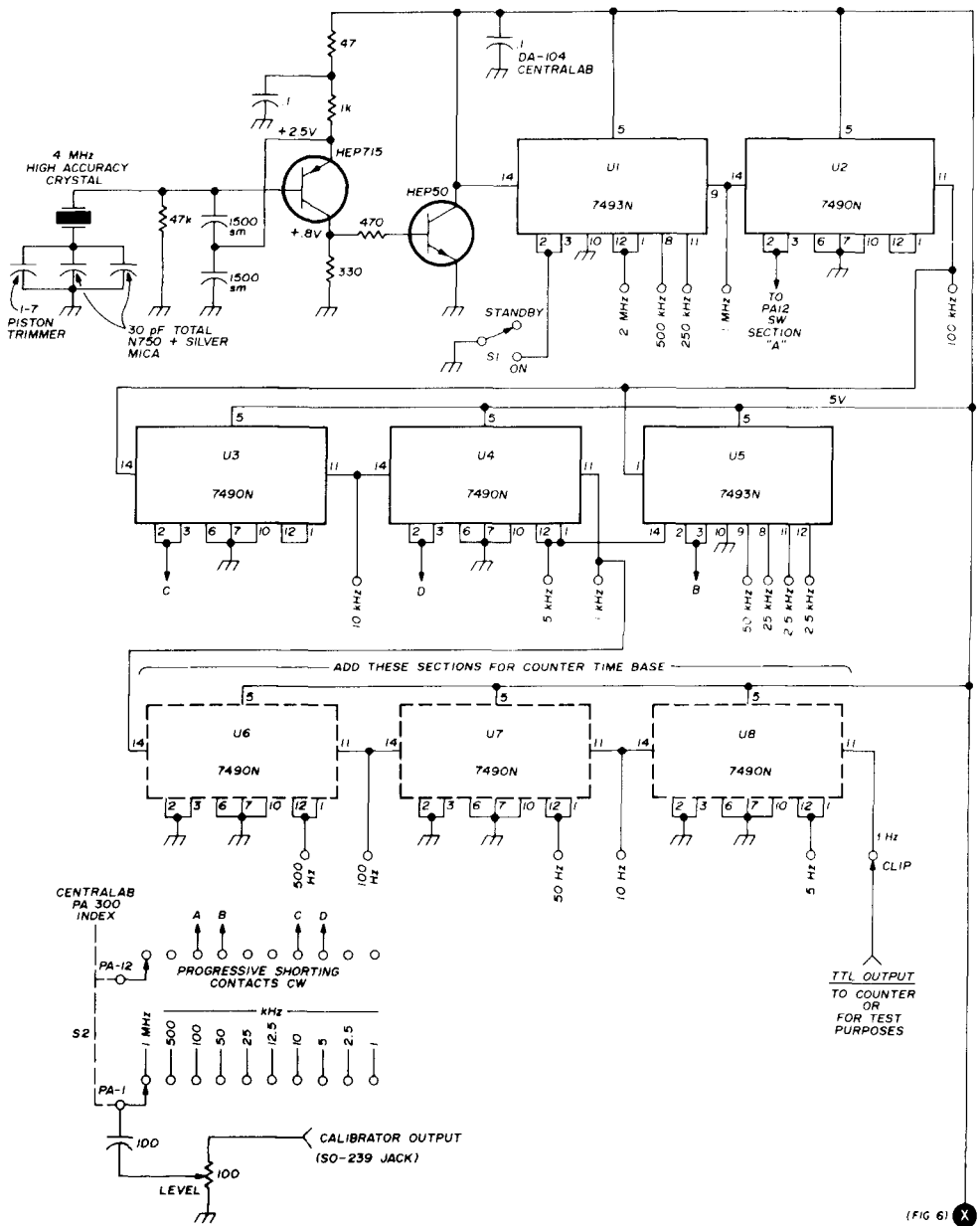

(FIG 6) X

fig. 5. Complete schematic diagram for the universal secondary frequency standard. Unit uses high performance TTL logic ICs. A printed-circuit layout is shown in fig. 6.

## the circuit

In fig. 5 the pnp oscillator transistor, Q1, is coupled to the TTL logic by transistor Q2. The 7493 binary dividers U1 and U5 are used to divide by factors of 2, with 7490 decade packages making

up the remainder of the logic. IC U5 has two inputs for 5 kHz and 100 kHz. Reset pins 2 and 3 control operation of the logic, either by switch S1, the standby switch, or by progressively shorting contacts on the rotary switch.

This way, the oscillator runs contin-

ously for best stability, and unused packages are disabled. It prevents some markers from leaking across the selector switch and being heard in the receiver. If this feature is not wanted, pins 2 and 3 should be jumpered to ground.

Board outputs and compensating ca-

easily supplied by a LM309K voltage regulator IC mounted on a heatsink (fig. 6). All power supply components except the power transformer are mounted on the circuit board. High temperature shut-down and overcurrent protection are provided by the regulator.

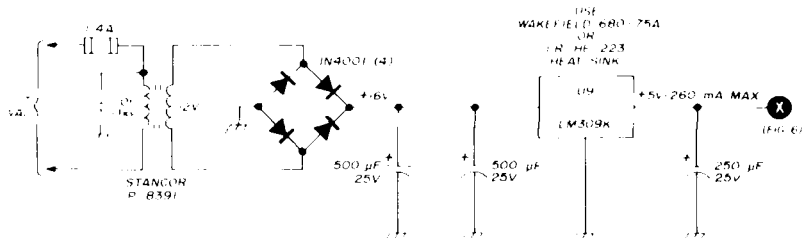


fig. 6. Power supply for the universal frequency standard.

pacitor terminals appear at convenient terminals at the top of the board made by forcing short lengths of bare number-12 wire into 5/64-inch holes. This facilitates exchange of compensating capacitors, or selection of a different logic output at some future time. After completion, it is difficult to work on the underside of the board without removing several wires.

The fast switching TTL logic has active transistor pull-up circuitry which is well suited to driving external loads. The 2900th harmonic of the 10-kHz marker is over S9 in the ten-meter band. In the unlikely event that a logic package fails, repair would be facilitated if Molex socket sockets are used.

The full current drain with all IC packages installed is 5 volts at 260 mA,

### construction

This frequency calibrator is simple to build. The circuit board may be hand duplicated following the layout given in fig. 7, or an etched, plated epoxy board is available which speeds construction and minimizes errors.\* Parts locations and identifications are screened on the board. It is only necessary to drill the IC holes with a number-60 drill, insert parts, and solder. The assembly is mounted in a compact 3x5x7-inch Minibox.

### temperature compensation

Crystals should be ordered for 0.0005% tolerance, F-700 or SP7-P holder (depending on manufacturer), 32-pF load, 4 MHz at room temperature. New crystals should be operated for a time before starting any compensation work. You will need the previously mentioned supply of N750 and N1500 capacitors, and a receiver with an S-meter that will tune WWV.

Start with 15 pF in parallel with a 15-pF N750, allow an hour for the unit to stabilize, and adjust to frequency using the S-meter on the receiver as an aid to exact zeroing. Select a time when WWV is


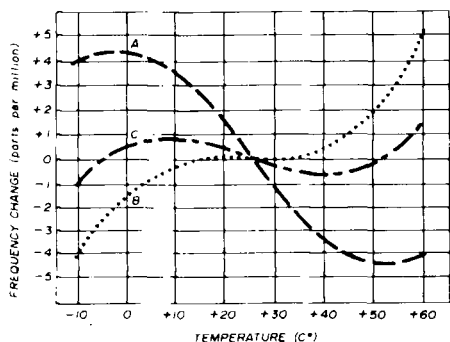


fig. 4. Frequency vs temperature chart for typical high-accuracy AT-cut crystals.

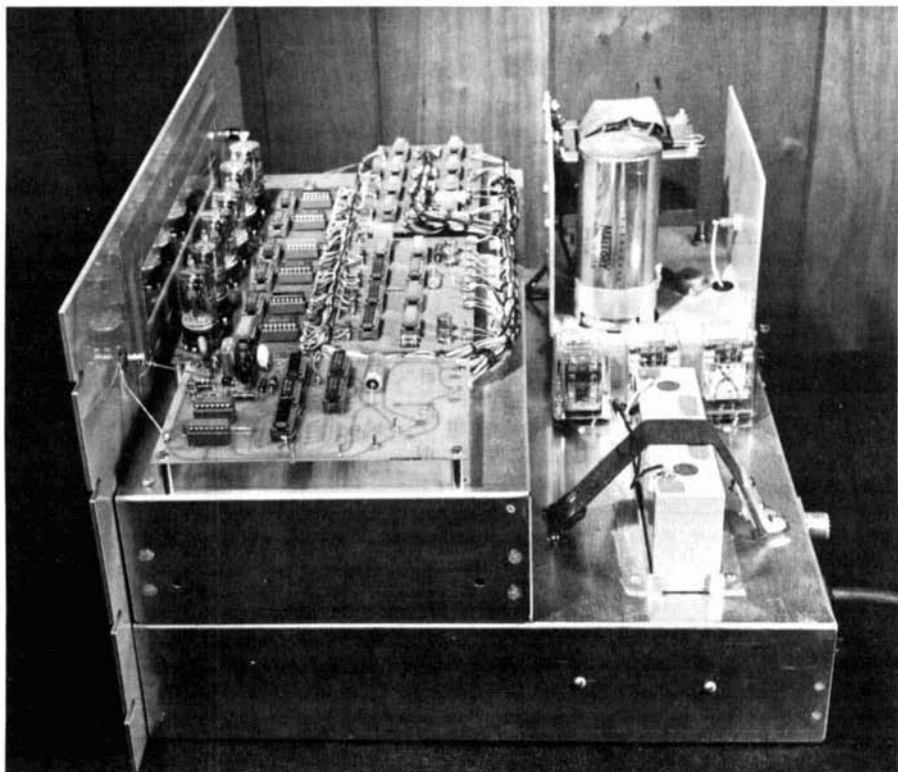\*An epoxy, plated 4x6-inch printed-circuit board for this frequency standard is available from the author. \$8.00, postpaid, in the United States.








Precision digital clock discussed in the text. The frequency standard board used to provide the 1-second driving pulses is located in the foreground on the upper deck. Nicad battery to the right is part of the failsafe power supply (see fig. 7).

second. But, since the crystal is compensated closer than this, and any minor drift is above and below the frequency, the average error is very small.

The secondary frequency standard would also make a good time base for a digital or Rec-Counter.<sup>5</sup> Readout kits

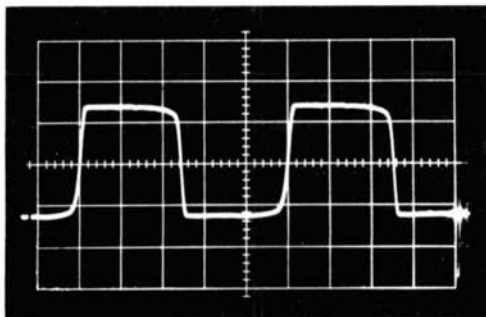with the tubes, storage latches and counter ICs are advertised in this magazine, so only the gating circuitry would have to be hand wired. Other applications for the standard include audio oscillator or signal generator calibration, or calibration of the sweep time base in oscilloscopes.



1-MHz output of the frequency standard as observed on a 10-MHz oscilloscope. Rounded waveform shows bandpass limitation of the scope. Horizontal scale is 0.2 microsecond per cm.

#### references

1. A.A. Kelley, K4EEU, "RTTY Monitoring Receiver," *ham radio*, December, 1972, page 27.
2. A.A. Kelley, K4EEU, "15-MHz Digital Frequency Counter," *ham radio*, December, 1968, page 8.
3. Irvin M. Hoff, W6FFC, "The Mainline FS-1 Secondary Frequency Standard," *QST*, November, 1968, page 34.
4. A.A. Kelley, K4EEU, "How to Make your Own Printed-Circuit Boards," *ham radio*, April, 1973, page 58.
5. Kenneth Macleish, W1EO, "A Frequency Counter for the Amateur Station," *QST*, October, 1970, page 15.

ham radio




# the REPEATER 2 Meter Fixed Station

Designed for the man who demands professional standards in 2 meter equipment. *REPEATER LINE* fixed station antennas are the 2 meter HAM's dream come true. With everything you need for top fixed station performance... toughness, efficiency and the gain to gain access to distant repeaters with ease. Work many stations, fixed or mobile, without access to a repeater.

The right antennas for the new FM transceivers... or any 2 meter fixed station.
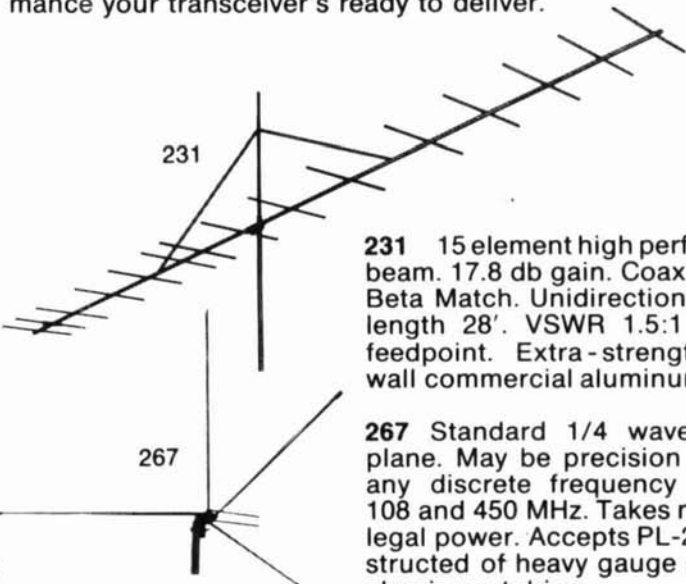
### *REPEATER LINE* Fixed Station Antennas

Tough, high efficiency antennas with a long, low radiation. For the top signal and reception you want... and the top performance your transceiver's ready to deliver.



**231** 15 element high performance beam. 17.8 db gain. Coaxial balun. Beta Match. Unidirectional. Boom length 28'. VSWR 1.5:1 52 ohm feedpoint. Extra-strength heavy wall commercial aluminum tubing.

**267** Standard 1/4 wave ground plane. May be precision tuned to any discrete frequency between 108 and 450 MHz. Takes maximum legal power. Accepts PL-259. Constructed of heavy gauge seamless aluminum tubing.

**268** For repeater use. Special stacked 4 dipole configuration. 9.5 db offset gain. 6.1 db omnidirectional gain. Heavy wall commercial type construction. 144 thru 174 MHz. 1.5:1 VSWR over 15 MHz bandwidth eliminates field tuning. Extreme bandwidth great for repeater use. Center fed for best low angle radiation. DC ground. Complete with plated steel mounting clamps.


# LINE from **Hy-gain** Antennas with real PUNCH!

**340** 3 element high performance beam. 9 db gain. Coaxial balun. Special VHF Beta Match configuration. Unidirectional pattern. VSWR 1.5:1. 52 ohm impedance. Heavy gauge aluminum tubing and tough aluminum rod construction.

**341** 8 element high performance beam. 14.5 db gain. Coaxial balun. VHF Beta Match. Unidirectional. Boom length 14'. VSWR 1.5:1. 52 ohm feedpoint. Heavy gauge commercial type aluminum construction.

**338** Colinear ground plane. 3.4 db gain omnidirectionally. Vertically polarized. 52 ohm match. Radiator of seamless aluminum tubing; radials of solid aluminum rod. VSWR less than 1.5:1. All steel parts iridite treated. Accepts PL-259.

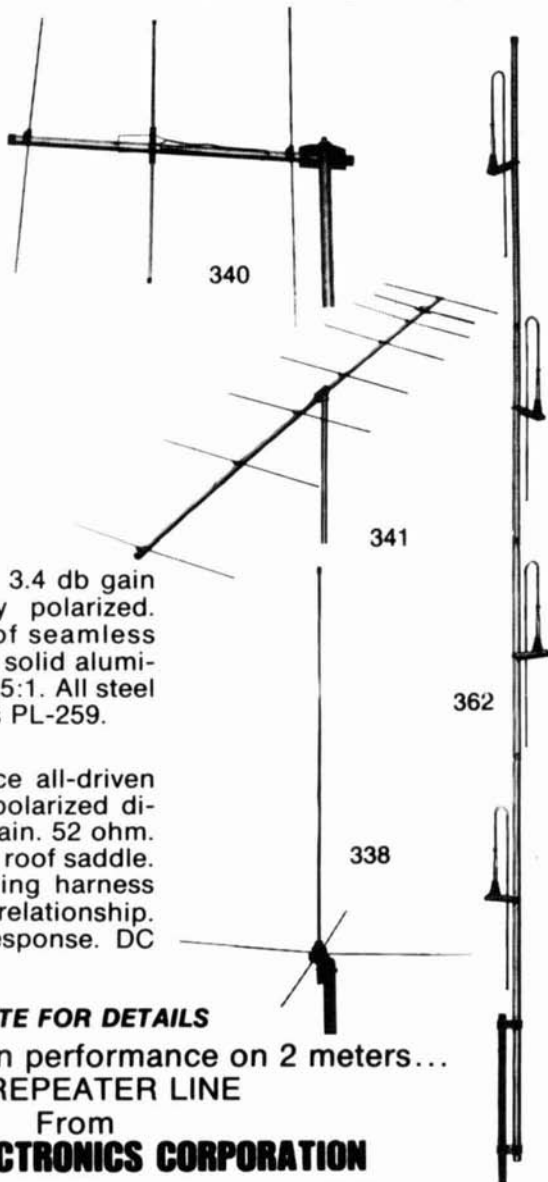**362** SJ2S4 high performance all-driven stacked array. 4 vertically polarized dipoles. 6.2 omnidirectional gain. 52 ohm. May be mounted on mast or roof saddle. Unique phasing and matching harness for perfect parallel phase relationship. Center fed. Broad band response. DC ground.



## WRITE FOR DETAILS

For top fixed station performance on 2 meters...

THE REPEATER LINE

From

**HY-GAIN ELECTRONICS CORPORATION**

Dept. BB, 8601 Northeast Highway Six, Lincoln, NE 68507  
402/464-9151

Telex 48-6424



## 455-kHz i-f alignment signal generator

Simple,  
crystal-controlled  
signal generator  
for aligning  
i-f strips —  
modulation  
is built in

I recently completed a homebrew receiver project which included a 455-kHz i-f strip, and I needed a signal source to align it. My home workshop doesn't boast a signal generator, and even if I had one, I would have no way of precisely setting its output frequency to 455 kHz. A little thought and investigation provided a fairly cheap and easy solution.

### circuit

A schematic of the resulting generator is shown in **fig. 1**. It consists of an fet crystal oscillator and an amplitude modulator. I decided on crystal frequency control because it would set the frequency accurately and because 455-kHz crystals are available from JAN Crystals for \$1.75 plus 10 cents postage.\* These crystals are supplied in an FT-241 holder;

\*JAN Crystals, 2400 Crystal Drive, Ft. Myers, Florida 33901.

the pins are 0.093 in diameter with 0.486 spacing. JAN sells the mating SSO-1 socket for 15 cents.

Transformer T1, the drain load for the fet oscillator, is a 455-kHz i-f transformer salvaged from a junked a-m transistor radio. This provides a simple way to tune

A Colpitts audio oscillator is used to provide amplitude modulation, and a switch allows the modulation to be turned on or off. A surplus 88-mH toroid is used in the audio oscillator. These can be found listed in surplus and classified ham ads for about 50 cents each or less.

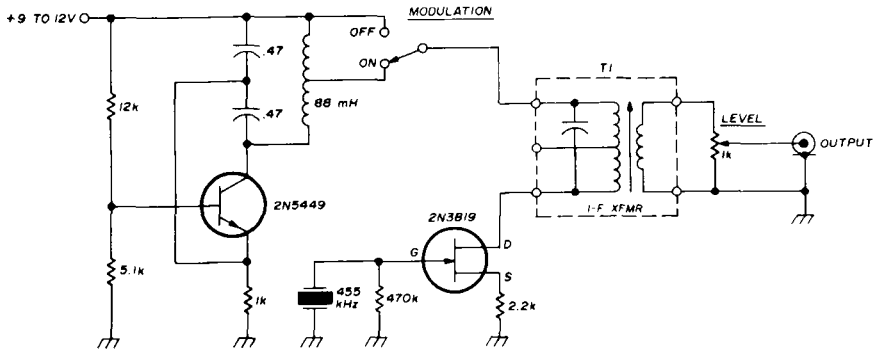


fig. 1. Schematic for the 455-kHz signal generator. Transformer T1 was salvaged from a junked transistor broadcast radio.

the drain circuit and obtain a low output impedance. Removing these transformers from the radio PC board is tricky because you have to simultaneously melt the solder at several different points. A large soldering iron is an advantage.

The junked radio had three i-f transformers, and I tried all three. I couldn't get the first one (mixer output) to oscillate at all, but it may have been damaged in removing it from the PC board. The last i-f transformer (which feeds the detector) had the highest output, but oscillations stopped if it was loaded with less than 200 ohms. I used the middle transformer because it would still oscillate when loaded with 50 ohms.

Another source of i-f transformers is Radio Shack. They sell a kit of four transformers for \$1.39 (catalog number 273-1383). I believe the one in this kit which would correspond to the one I used is color-coded white.

The one I used has four leads, and two adjacent leads must be tied together to provide the center-tap. The audio frequency is about 1-kHz, but this may be altered by changing the value of the 0.47- $\mu$ F tank capacitors.

I used a 2N3819 fet, but a Motorola MPF102 or Siliconix U183 should perform identically. The 2N5449 modulator should be available at local Radio Shack stores for 79 cents (catalog number 276-2014).

## construction

As shown in the photographs, the generator is housed in a 2 $\frac{1}{4}$ x2 $\frac{1}{4}$ x5-inch Minibox. A piece of perfboard holds most


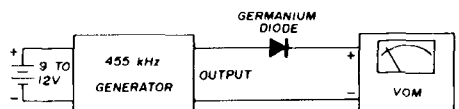


fig. 2. Arrangement used to adjust transformer T1 for maximum rf output.

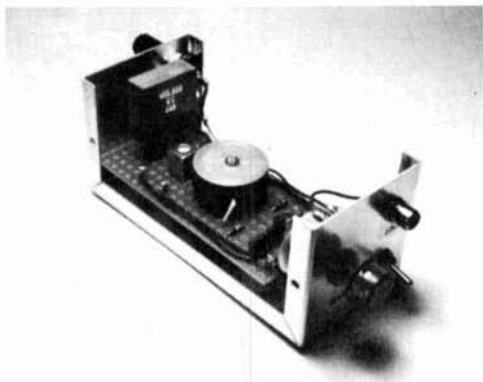

Layout of the 455-kHz i-f signal generator. All components are wired on a section of perfboard which is mounted in a small Minibox.

of the circuit components. It is mounted in the Minibox by two screws with 1/2-inch spacers. The 88-mH toroid is held to the perfboard by a screw and two discs (one metal, one plastic) which were furnished with the toroid. I detected nothing critical in the layout.

One end of the Minibox holds the modulation switch, output phono jack and level control. Two 5-way binding posts are mounted on the other end for connecting the generator to a dc power source.

### operation

The fet may not oscillate until T1 is adjusted. Connect a sensitive vom to the output through a germanium diode detector as shown in fig. 2. Set the level control at maximum and the vom to its most sensitive dc volts scale. Now adjust the tuning slug in T1 for a maximum reading on the vom. This will only be a fraction of a volt, but this is more than enough for i-f amplifier alignment. The level control pot will not set the output voltage low enough for sensitive i-f circuits, and I found it necessary to use the

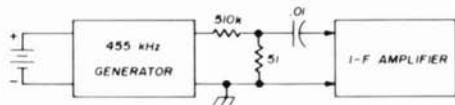


fig. 3. External attenuator which may be used to decrease generator output.

external attenuator shown in fig. 3 to prevent overdriving the i-f strip.

Although the circuit was originally designed to operate from a 12-volt dc supply, it appears to perform well using only a 9-volt transistor radio battery for a power source. Current drain is about 7 mA with a 12-volt supply and 5 mA using the 9-volt battery.

### conclusion

This little gadget is intended only for 455-kHz i-f alignment which is a rather limited use. However, it has a limited cost too — only a few dollars. A well stocked junk box can cut the dollar outlay to a very nominal amount. I haven't had an opportunity to check its frequency on a counter or observe its output waveform on an oscilloscope, but it performed its intended function to my satisfaction. If amplitude modulation is not required, the unit could be simplified to a single fet circuit. This would reduce battery drain substantially. A worthwhile addition would be a built-in step attenuator which would permit setting the output voltage to micro-volt levels.

ham radio



"The wife just gave me a hint of something I need to do!"

# for the EXPERIMENTER!

**INTERNATIONAL EX CRYSTAL & EX KITS**  
 OSCILLATOR • RF MIXER • RF AMPLIFIER • POWER AMPLIFIER



### 1. MXX-1 TRANSISTOR RF MIXER

A single tuned circuit intended for signal conversion in the 3 to 170 MHz range. Harmonics of the OX oscillator are used for injection in the 60 to 170 MHz range. Lo Kit 3 to 20 MHz, Hi Kit 20 to 170 MHz (Specify when ordering)..... **\$3.50**



### 2. SAX-1 TRANSISTOR RF AMP

A small signal amplifier to drive MXX-1 mixer. Single tuned input and link output. Lo Kit 3 to 20 MHz, Hi Kit 20 to 170 MHz (Specify when ordering)..... **\$3.50**




### 3. PAX-1 TRANSISTOR RF POWER AMP

A single tuned output amplifier designed to follow the OX oscillator. Outputs up to 200 mw, depending on the frequency and voltage. Amplifier can be amplitude modulated. Frequency 3,000 to 30,000 KHZ..... **\$3.75**


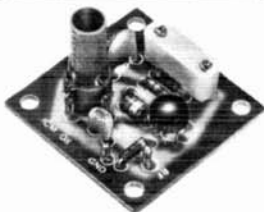
### 4. BAX-1 BROADBAND AMP

General purpose unit which may be used as a tuned or untuned amplifier in RF and audio applications 20 Hz to 150 MHz. Provides 6 to 30 db gain. Ideal for SWL, Experimenter or Amateur ..... **\$3.75**



### 5. OX OSCILLATOR

Crystal controlled transistor type. Lo Kit 3,000 to 19,999 KHz, Hi Kit 20,000 to 60,000 KHz. (Specify when ordering)..... **\$2.95**



### 6. TYPE EX CRYSTAL

Available from 3,000 to 60,000 KHz. Supplied only in HC 6/U holder. Calibration is  $\pm .02\%$  when operated in International OX circuit or its equivalent. (Specify frequency) ..... **\$3.95**

## for the COMMERCIAL user...

### INTERNATIONAL PRECISION RADIO CRYSTALS

International Crystals are available from 70 KHz to 160 MHz in a wide variety of holders. Crystals for use in military equipment can be supplied to meet specifications MIL-C-3098E.

**CRYSTAL TYPES:** (GP) for "General Purpose" applications  
 (CS) for "Commercial Standard"  
 (HA) for "High Accuracy" close temperature tolerance requirements.



write for  
**CATALOG**



**INTERNATIONAL**  
 CRYSTAL MFG. CO., INC.  
 10 NO. LEE • OKLA. CITY, OKLA. 73102

# multichannel fm receiver

## for six and two

How to use  
commercial fm  
receiver strips  
in a multichannel,  
two-band vhf  
fm receiver

Surplus public-service vhf-fm equipment, which is sold in *strip* form, can be used as the basis for a low-cost, multichannel, two-band fm receiver. This is accomplished simply by adding a two-meter converter and a logic crystal oscillator<sup>1</sup> to a single-channel 30-50 MHz Motorola Sensicon receiver strip as shown in block

form in fig. 1. If the output of the two-meter converter is fed into the strip receiver's first-conversion i-f input, and a logic oscillator is provided as the local oscillator (17.775 to 17.830 MHz) the strip will cover the fm channels for 146.34/94 MHz. By adding a multiple crystal oscillator operating at approximately 16 MHz and appropriate switching controls, two-band control and channel selection is possible.

These modifications are not limited to Motorola receivers, as there are a number of commercial fm receiver strips sold in the same way. Any of these strips can be adapted to perform the same task. However, before modifying one of these units it's a good idea to put it into operating condition before adding to the confusion. A circuit diagram and receiver tuneup data, if you can find them, are a great help in this respect. Information on many of these units is included in *The FM Schematic Digest*.<sup>2</sup>

### two-meter converter

If you already have a good two-meter converter, all you have to do is convert its output frequency to the same frequency as the receiver strip you are going to use (4.3 MHz in the Motorola Sensicon receiver strip). This may be as simple as

Stirling Olberg, W1SNN, 19 Loretta Road, Waltham, Massachusetts 02154



plugging in the two-meter logic oscillator and realigning the converter, or it may require more extensive circuit modifications. If considerable modification is required, it might be easier to build a two-meter converter specifically for use with the fm receiver strip.

My two-meter converter consists of a single mosfet rf stage using an RCA 40822 mosfet. Another mosfet, an RCA 40823, is used as the mixer (see fig. 2). Both of these devices were designed for vhf work and provide good performance on two meters. The rf amplifier has excellent gain as an unneutralized rf amplifier, a low noise figure, and wide dynamic range which results in low cross modulation. The dual-gate mosfet used in the mixer stage isolates the output and allows low-level local-oscillator injection.

The tuned input network to the rf amplifier is designed to match a 50-ohm antenna. The small trimmers, C1 and C2, the inductor, L1, and the rf amplifier transistor, Q1, are located in a shielded compartment made from 1-inch-wide strips of copper-clad PC material. The drain lead of Q1 passes through a small hole in the shield wall and is connected to inductor L2. Gate 2 and the source lead of the mosfet are connected directly to 1000-pF standoff capacitors. The 275-ohm source resistor is grounded next to the source bypass capacitor with as short leads as possible. A ferrite bead is installed on the drain lead.

Similar construction is used for the mixer stage. A small coaxial cable must be used to connect gate 2 of the mixer to the output of the multiplier chain. This is because the mixer requires only a small amount of local-oscillator signal — un-

wanted signals can leak in and appear in the 4.3-MHz output.

### local oscillator

Construction of the logic oscillator will not be discussed as that was covered in detail in the previous article.<sup>1</sup> Crystal

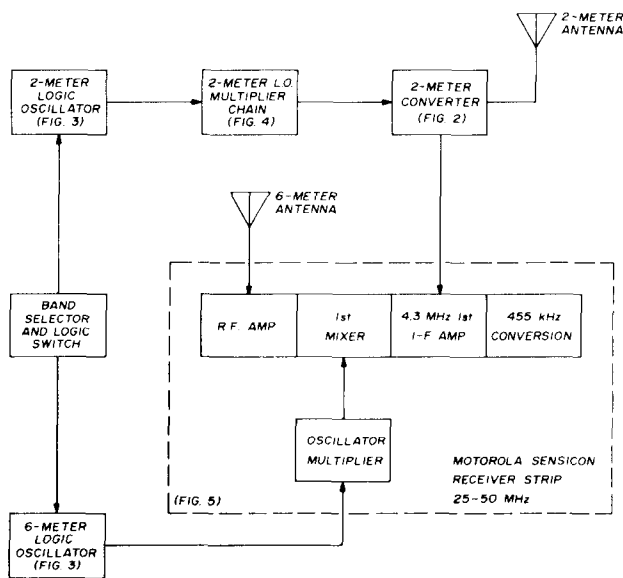


fig. 1. Block diagram of the multichannel six- and two-meter fm receiver using a Motorola Sensicon receiver strip.

frequencies for the logic oscillator may be determined from the following formula

$$f_{\text{xtal}} = \frac{f_o - f_{i-f}}{8} \quad (144 \text{ MHz})$$


$$f_{\text{xtal}} = \frac{f_o - f_{i-f}}{3} \quad (50 \text{ MHz})$$

where  $f_{\text{xtal}}$  is the crystal frequency,  $f_o$  is the desired operating frequency and  $f_{i-f}$  is the intermediate frequency of the receiver strip (often 4.3 MHz). For example, the crystal required for a two-meter input frequency of 145.500 MHz is

$$f_{\text{xtal}} = \frac{145.500 - 4.30}{8} = 17.650 \text{ MHz}$$

For a six-meter input at 52.525 MHz, the required crystal frequency is
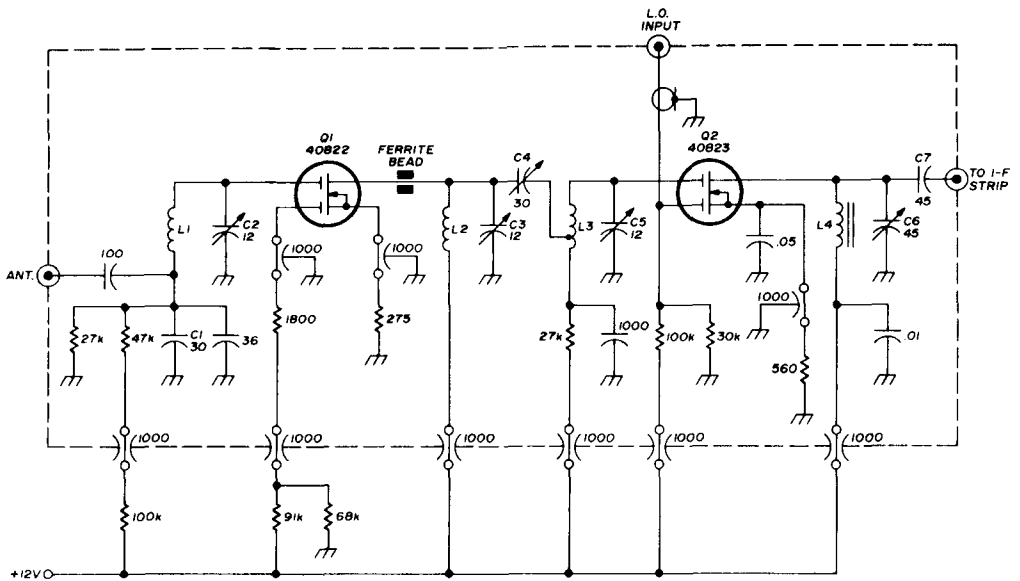
$$f_{\text{xtal}} = \frac{52.525 - 4.30}{3} = 16.075 \text{ MHz}$$




- L1, L2 6 turns number 22, air wound, 1/4" diameter
- L3 6 turns number 22, air wound, 1/4" diameter, center tapped
- L4 37 turns number 32 on Amidon T50-2 toroid core

fig. 2. Simple two-meter converter for the two-band fm receiver. The ferrite bead on the drain lead of Q1 is an Amidon 45-101.

The frequency-selector switch is a 2-pole, 6-position rotary wafer switch wired so that +12 volts is applied to the two-meter converter when the two-meter channel crystals are switched into the circuit. More crystal frequencies can be added simply by adding additional logic

oscillator stages — the only limiting factor to the number of logic-oscillator channels is the current handling ability of the voltage regulator.

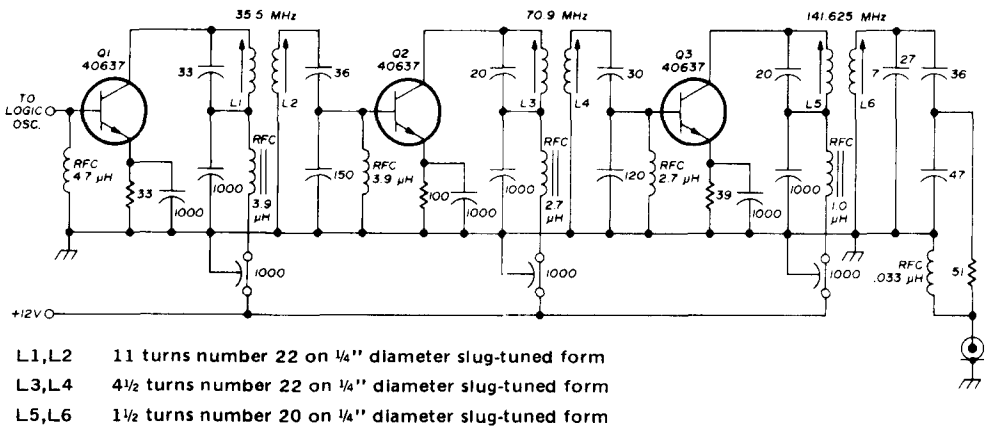The logic oscillator will operate properly with fundamental-mode crystals up to about 20 MHz. Above 20 MHz it is



- L1, L2 11 turns number 22 on 1/4" diameter slug-tuned form
- L3, L4 4 1/2 turns number 22 on 1/4" diameter slug-tuned form
- L5, L6 1 1/2 turns number 20 on 1/4" diameter slug-tuned form

fig. 4. Local oscillator multiplier chain. Stagger-tuned circuits provide relatively flat output across the two-meter fm band. L1, L3 and L5 are peaked for the lowest frequency crystal; L2, L4 and L6 are peaked for the highest.

necessary to use higher speed gates than the TTL ICs shown in fig. 3. Do not use overtone crystals in this circuit as they will not oscillate at the same frequency as that marked on the crystal can.

spaced by the diameter of one coil form (1/4 inch). The input coil of each pair is peaked for the lowest frequency crystal while the secondary coils are peaked for the highest frequency crystal. The fre-

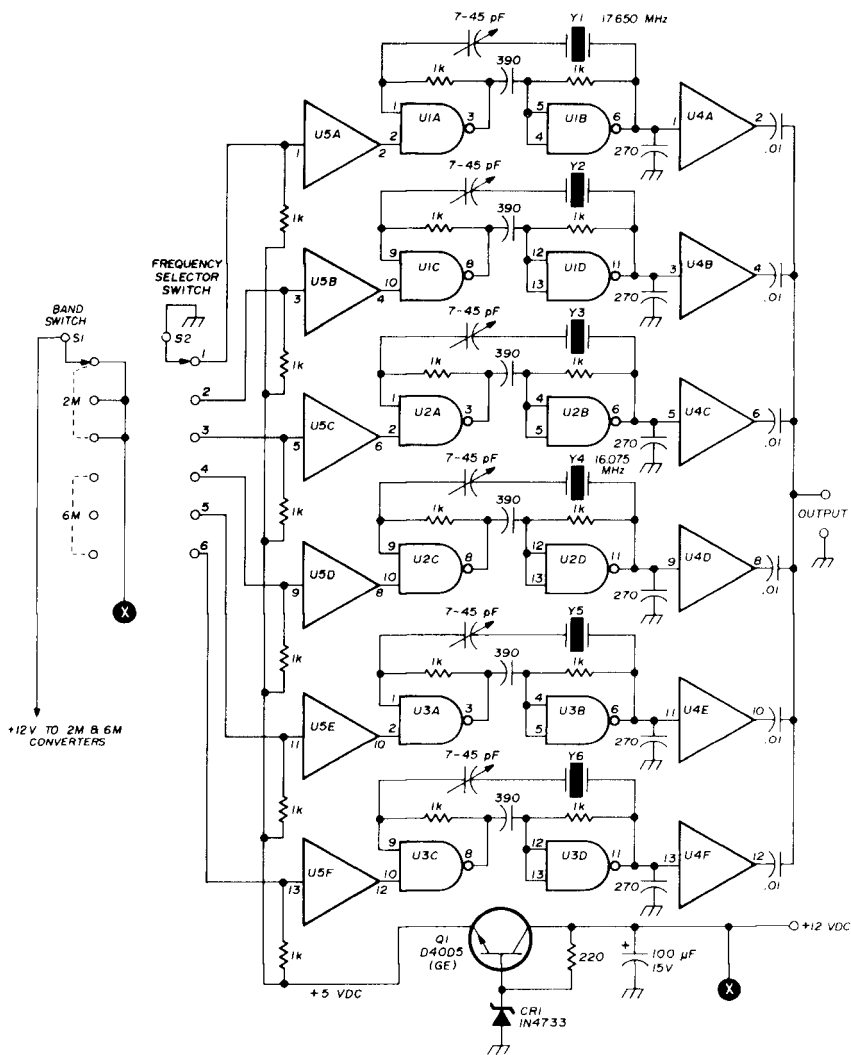


fig. 3. The logic oscillator circuit uses TTL ICs which are suitable for use with fundamental crystals up to approximately 20 MHz. Overtone crystals do not operate properly in this circuit.

Construction of the local-oscillator chain (fig. 4) is very straight forward and should cause no problems. The stagger-tuned stages provide the bandwidth necessary to cover the entire two-meter fm band. Each of the inductors is wound as described in fig. 4, and the coil pairs

frequencies indicated in the circuit diagram are the approximate center frequencies of the stagger-tuned stages.

The two-meter converter, logic oscillator and multiplier chain are built on a single piece of copper-clad board 3-inches wide by 8-inches long. The oscillator is

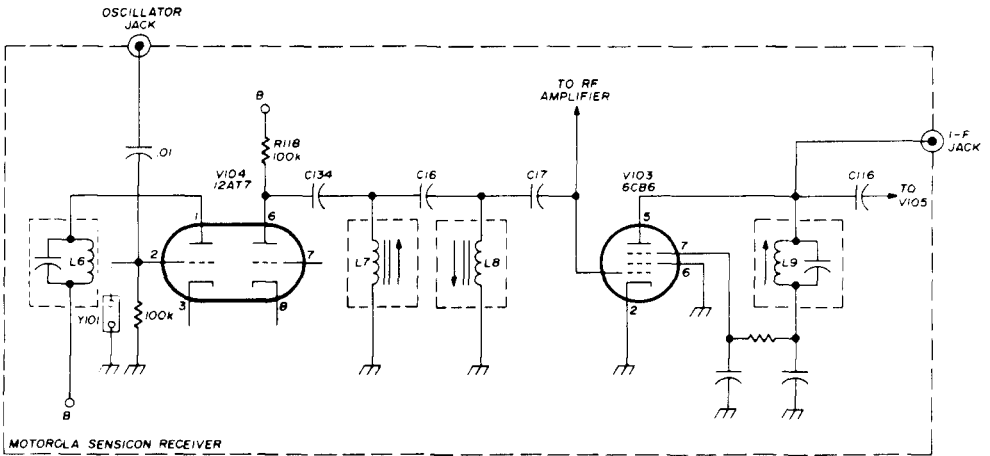


fig. 5. Partial diagram of the Motorola Sensicon receiver strip used in the two-band fm receiver built by W1SNN.

built into a separate shielded compartment as are the multiplier chain and the two-meter rf amplifier and mixer stages. Short lengths of coaxial cable are used to connect these units together and to the fm receiver strip.

### receiver strip

The low-band Motorola Sensicon receiver (model PA9244-12) I modified for use in the two-band receiver is easily moved into the six meter fm band by replacing the fixed tuning capacitors in the rf amplifier, mixer and local-oscillator stages. The values for these capacitors are given in the Motorola schematic and are prefixed with the letters L, M or H, depending on the desired operating frequency. The H values (for high-band) are the values that should be installed for six-meters.


To use the receiver strip in the two-band fm receiver it is necessary to add an i-f input jack and an access jack to the first local oscillator. The i-f jack is located close to V103 so that the lead to pin 5 of the 6CB6 is as short as possible (see fig. 5). Another jack is mounted on the opposite side of the chassis and connected to pin 2 of V104, the grid of the 12AT7 oscillator multiplier. This completes the modifications to the receiver strip.

The receiver is aligned by connecting a center-scale dc vtvm to the discriminator output and adjusting the frequency control trimmer of each channel crystal until the meter reads zero with an incoming signal.

### references

1. Stirling Olberg, W1SNN, "Logic Oscillator for Multi-Channel Crystal Control on VHF FM," *ham radio*, June, 1973, page 46.
2. Sherman M. Wolf, "FM Schematic Digest," P.O. Box 535, Lexington, Massachusetts 02173.

### ham radio

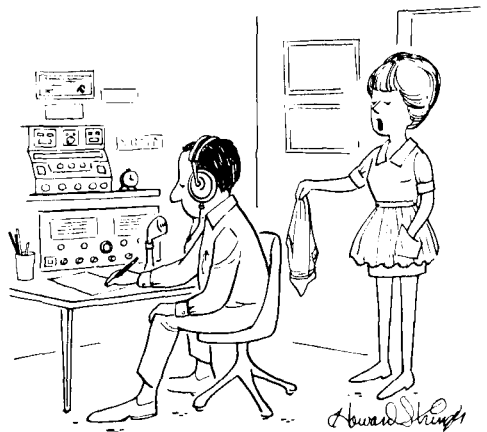

"Delta ... India ... Sierra ... Hotel ... Echo ... Sierra."

the most powerful antennas under the sun!



# The Best Vertical There IS!

## 80 through 10 meters

# ### *hy-gain* 18AVT/WB

**New, from the inventors of wideband verticals.**

Pack some punch! All the omnidirectional performance of Hy-Gain's famous 14AVQ/WB...plus 80 meter capability! Unrivaled performance, rugged extra heavy duty construction, and the price you want...all in one powerful package!

- Automatic switching on all five bands through the use of three beefed-up Hy-Q traps...featuring extra large diameter coils for exceptional L/C ratio and extremely high Q.
- Recessed coax connector furnished.
- Top loading coil and four element static hat.
- Constructed of extra heavy wall high tensile aluminum.
- Hot performance all the way across the band with just one setting (10 through 40).
- Hy-Q traps effectively isolate antenna sections for full 1/4 wave resonance on all bands.
- No dissimilar metals to cause noise.
- SWR 2:1 or less at band edges.
- Maximum legal power with low frequency drift.
- Exceedingly low radiation angle makes DX and long haul contacts a cinch...whether roof or ground mounted.
- Very low RF absorption from insulating materials.

The 18AVT/WB is constructed of extra heavy duty, taper swaged, seamless aircraft aluminum with full circumference, corrosion resistant compression clamps at all tubing joints. This antenna is so rigid, so rugged...that its full 25' height may be mounted using only a 12" double grip mast bracket...no guy wires, no extra support...the 18AVT/WB just stands up and dishes it out!

**Order No. 386**

**\$79.95**




Get the strength, the performance and the price you want...from the man who sells the complete line of quality Hy-Gain equipment.

## **HY-GAIN ELECTRONICS CORPORATION**

Dept. BB, 8601 Northeast Highway Six, Lincoln, NE 68507  
402/464-9151

Telex 48-6424

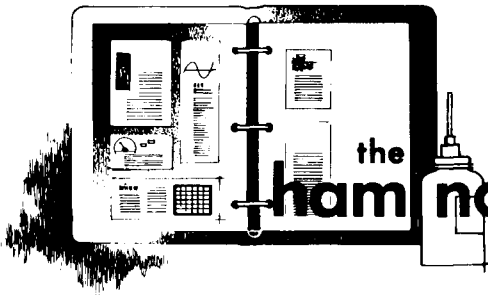

# the ham notebook

## vhf fm scanner modifications

Although solid-state equipment is fast becoming the ideal equipment, at the same time there is still quite a bit of tube-type equipment in use. At the time I saw the February, 1973, edition of *ham radio* I was in the process of trying to come up with a scanner to add to my base station receiver. After looking over K2ZLG's vhf fm receiver scanner, I decided it was worth a try. However, the basic design was not completely acceptable for use with tube-type equipment. The following modifications were developed and tried. So far the unit has worked flawlessly.

Since most vacuum-tube receivers produce a negative-going voltage when the squelch is open, the original input circuit will not work. The circuit shown in **fig. 1** was finally tried and seemed to work the best of any. One of the major problems with the bipolar input was to get the input impedance high enough to prevent loading of the receiver squelch circuitry; the dual-gate fet takes care of this problem nicely.

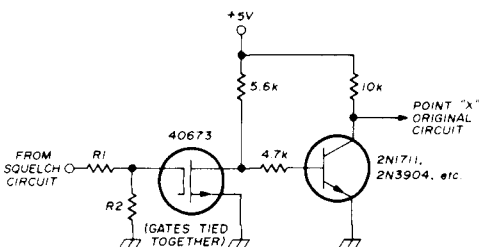


fig. 1. Input circuit for frequency scanner.

A negative-going voltage of more than -2 volts is required to stop the scanner. However, this voltage should not be more than -6 volts at the gate of the fet. For voltages in the range of -2 to -6 volts R2 can be eliminated. For voltages higher than -6 volts, R1 and R2 should limit the gate voltage to less than -6 volts. Typical values are between 1 and 10 megohms. The important thing is to try to keep the input impedance as high as possible since

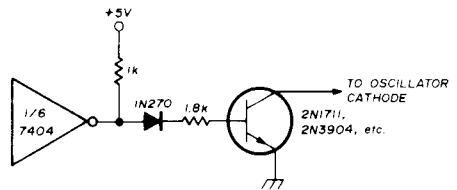


fig. 2. Output circuit. Repeat for each channel.

loading of less than about 1 megohm will interfere with normal squelch operation.

The next problem is that most tube-type receivers use separate oscillators for each frequency. Most circuits require that the cathode of the appropriate oscillator be grounded for operation of that particular oscillator. In addition, the ungrounded cathode produces about 30 volts. The simplest way around this seems to be to use an npn transistor to isolate the cathode from the scanner since TTL circuitry will not normally tolerate 30 volts. This is shown in **fig. 2**. The transistor used is non-critical as long as it will withstand the voltage present when the tube cathode is above ground.

In the unit at my station some MC4039 ICs were on hand instead of the 7446 decoder, so these were used. This IC happens to have an enable pin that was used with an inverting transistor off the

output of the input circuit. I didn't like seeing the numbers go by as the unit scanned, and this configuration turns the readout off while the unit is scanning. The same thing could be done by putting a switching transistor in the +5-volt line to the readout.

Mike Jones, WA5WOU

## 10 MHz coverage for the SB-303

The utility of 15-MHz WWV reception on Heath SB-303 receivers is somewhat dubious, considering present propagation conditions in this area. I've changed mine to tune WWV-10, finding virtual 24-hour coverage on 10 MHz. Modifications are relatively simple, but refer to the manual and schematic.

The 23.895 MHz crystal, Y104, used for 15 MHz, is replaced with an 18.895 MHz, HC6-U type, third overtone crystal intended for a 32 pF load. This change is made on the *crystal switch-board* (85-348), whose Xray pictorial with other PC boards is found at the back of the SB-303 manual.

To resonate the LC circuit marked "15 MHz" on the *heterodyne oscillator switch-board*, a 33-pF dipped mica or disc capacitor is added across C131. The slug in L117 must be moved in a few turns until oscillation occurs as noted by voltage appearing at TP on the PC board. An extra half-turn provides positive crystal starting when switching bands.

Modification of the *rf amplifier switch-board* (85-346) involves isolating foil pad areas around switch-points 5 and 6. Switch-point 5 will then be jumpered back to the foil lead coming from L111, the 14-MHz tuned circuit. A new resonant circuit for 10 MHz is required. I used 22 turns of number-24 enamel wire on an Amidon T-50-2 toroid, turns spaced evenly around the core. This is approximately 2.9  $\mu$ H which, with a 47-pF disc in parallel, will resonate — out of the circuit — at 14 MHz. The older vacuum tube type of grid dipper will dip this unit satisfactorily. One end of this

LC combination is soldered to switch-point 6 (on 85-346) and the other to ground foil near the *rf in* phone jack. Mount it close to the board, avoiding shorts.

Operation of the receiver on 10 MHz may be checked by attaching a short antenna through a few pF to *rf in* at C106 on the *amplifier switch-board*. The *preselector* should resonate broadly at about 30 to 40 percent of its range.

The *antenna switch-board* (85-345) is modified similarly to the previous PC board. Again, switch-point 5 and 6 pad areas are isolated, 5 being jumpered back to the foil lead running to the 14-MHz tuned circuit L103-C103. Also, between and clear of switch-points 6 and 7, drill about a number-58 hole. This board has a double-section rotary switch, the section nearest the board being the secondary, and the outer, the primary. Switch-points 5 and 6 on the primary are isolated by unsoldering the blue wire and jumper between 5 and 6. Resolder the blue wire directly to switch-point 5 (14 MHz).

Primary switch-point 6 is left blank for the moment. The LC antenna circuit also uses an Amidon T-50-2 toroid with 22 turns of number-24, with the addition of 6 turns of number-26 or -28 wire forming the primary. Use an adjacent winding rather than over-winding for the primary. The tuning capacitor is again a 47-pF disc paralleled with the 22-turn secondary. The combination mounts on the foil side of the board (85-345).

One end of the secondary goes to switch-point 6 and the other to any convenient ground-foil point. One side of the 6-turn primary also ties to this point, the other side being fed through the pre-drilled hole and soldered to outer switch-point 6. An adjustment of a turn on the secondary may be desirable for better tracking, but I found the *pre-selector tuning* to be adequately sharp.

This application can be used for other 500-kHz segments. The crystal frequency must be 8895 kHz above the lowest signal frequency.

Bill Fishback, W1JE

# new products

## fm signal generator



The Measurements Model 800A series of solid-state fm signal generators cover all mobile communication frequency bands allocated by the FCC. Any desired frequency can be quickly obtained by selecting one of the six frequency bands, tuning the coarse tuning control, and making narrowband adjustments with either the electronic fine tuning or incremental frequency controls.

The Model 800A signal generator provides accurate output voltages traceable to the National Bureau of Standards. The output is continuously variable from 0.1 microvolt to 0.1 volt by means of a

mutual inductance type attenuator. Output voltages are automatically maintained at all levels by a temperature-compensated bolometer circuit. Rf leakage is negligible, and microphonics are so low that accurate receiver sensitivity measurements can be made down to 0.1 microvolt.

Internal modulators provide frequency modulation at 1000 Hz sine wave or 20 Hz sawtooth. External modulation from dc to 30 kHz may be applied through front-panel binding posts. Sync out and sync phase are available for external modulation (up to  $\pm 32$  kHz peak deviation) so that dual-trace sweep alignment techniques may be used.

For complete technical data write to Edison Electronics, Division of McGraw-Edison Co., Grenier Field, Manchester, New Hampshire 03103, or use *check-off* on page 94.

## WWV data folder

Complete, up-to-date information on the many services provided by The National Bureau of Standards Radio Stations WWV, WWVH and WWVB is being offered at no charge by the True Time Instrument Company, manufacturers of receivers for all of the standard time and frequency broadcasts.

The NBS transmissions provide an invaluable service to radio amateurs, laboratories and engineers throughout the world. Extremely precise audio and radio frequency standards are broadcast, as well as accurate time signals, geophysical alerts, Atlantic and Pacific area storm warnings and radio frequency propagation forecasts. This information is at the disposal of anyone having a receiver capable of tuning to one or more of the transmitting frequencies. The proper use of NBS facilities can greatly supplement the instrumentation of any laboratory.

Maximum utilization of this valuable "natural resource" depends upon a complete knowledge of the current broadcasting schedules and transmitting frequencies. The folder supplies this data, as



well as information on suitable methods of comparison with local chronometers or instrumentation. Also included are the hourly broadcast schedules of National Bureau of Standards stations WWV, WWVH, WWVB, with supporting data.

Write to True Time Instrument Company, 225 Melbrook Way, Santa Rosa, California 95405, and request Bulletin 373-1, or use *check-off* on page 94.

## swr meter



Carvill International has announced its new in-line swr and power meter, the model ME-IIN. The ME-IIN is a direct-reading swr and power meter which measures the ratio of the forward and reflected wave on a coaxial transmission line. In this instrument a printed-circuit transmission line is used to eliminate unbalanced rf pickup which is often a problem in more simple swr meters. The swr meter is usable on all bands from 3.5 to 150 MHz.

For more information, write to Carvill International Corporation, 825 Constitution Drive, Foster City, California 94404, or use *check-off* on page 94.


## signal intensifier

The new SABA-5 (Symtek Automatic Broadband Amplifier) provides low-noise and high *useful* gain for amateur communications receivers. This new amplifier, which covers 80, 40, 20, 15 and 10 meters with no tuning has a typical noise figure of 2.5 dB and gain of 20 dB (minimum). Input and output impedance is 50 ohms.

The SABA-5 uses a dual-gate, diode-protected mosfet to take advantage of its low noise characteristics as well as its



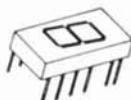Uses Standard 7447 Decoder-driver. Seven Segment Readouts. All tested and guaranteed. Specs included. Fit standard 14 pin DIP socket. Full .335 inch high. Color, RED.  
Less Decimal \$2.00 ppd.  
With Decimal \$2.25 ppd.  
With Colon \$2.50 ppd.



Same unit only contains numeral 1 and plus and minus sign. \$2.25 ppd.

### GI Printed Circuit type bridge rectifiers.

200 v PIV @ 1.5 A  
50¢ ea or 3 for \$1.25  
400 v PIV @ 1.5 A  
60¢ ea or 3 for \$1.75



LED Pilot Lites.  
Full 3/16 inch Dia.  
4 for \$1.00 ppd.



JUMBO Seven Segment Readouts. Full .770 inches high, RED. Uses 7447 Decoder-driver. Specs included.

With Decimal point. \$5.00 ppd.  
Same unit only numeral 1 and plus & minus sign. \$5.00 ppd.



### NEW NEW NEW

6 foot Koil-Cord with molded PL-55 plug. Very nice.  
75¢ Each, 3 for \$2.00 ppd.

General Purpose Germanium Diodes.  
Similar to 1N34a etc. 16 for \$1.00 ppd.  
All Cathode banded. 100 for \$5.00 ppd.  
Full leads. 1000 for \$40.00 ppd.

### NEW

Transformer — American Made — Fully shielded. 115 V Primary. Sec. — 24-0-24 @ 1 amp with tap at 6.3 volt for pilot light.  
Price — A low \$2.90 each ppd.

400 Volt PIV at 25 Amp. Bridge Rectifier.

\$4.00 ea. or 3 for \$10.00 ppd.



6.3 Volt 1 Amp Transformer. Fully Shielded  
\$1.60 Each ppd.

### NEW

JUST ARRIVED — Transformer, 115 VAC primary, 18 volt, 5 amp ccs or 7 amp intermittent duty secondary \$6.00 ea. ppd.

### NEW NEW

TRANSFORMER. 115 volt primary, 12 volt 1/2 amp secondary. \$1.50 ppd.



TOROIDS — YOUR CHOICE — 88 mhy or 44 mhy — 5 for \$2.50 ppd.

DIGITAL CLOCK on a single chip, national type 5314. Complete with specs and circuit \$12.00 ea. ppd.

SEND STAMP FOR BARGAIN LIST  
Pa. residents add 6% State sales tax  
ALL ITEMS PPD. USA

**m. weinschenker**  
K 3DPJ BOX 353 · IRWIN, PA. 15642

**NURMI ELECTRONIC SUPPLY**

Departments 17  
1727 Donna Road · West Palm Beach, Florida 33401  
PHONE — (305) 686-8553



**HEP 170's**



THE "DO EVERYTHING" 2% AMP, 1000 VOLT DIODE  
Motorola is catching up on the backlog and we've got thousands of them back in stock. 10/\$3.00 - 100/\$25.00

**RCM 40673's**

THE MOST POPULAR DUAL GATE PROTECTED MOS FET around. Good to over 400 MHZ. We got 'em and you get 'em for only . . . . . 5/\$6.00

**OTHER FET'S**

2N4220A	N - JFET	\$2.07
2N4221A	N - JFET	2.03
2N4222	N - JFET	1.70
2N4222A	N - JFET	2.03
2N5454	N - JFET	2.00
2N5592	N - JFET	2.00
2N5593	N - JFET	2.00
MFE3004	N - MOSFET	1.80

**RG - 174/U**

WE WENT THROUGH 20 MILES OF IT LAST TIME!  
We are authorized Belden Distributors and new shipments have come in from the factory. Split a 500' spool with a friend and save \$\$\$\$\$

BELDEN NO. 8216 100'/\$4.80 - 500'/\$17.85

**LED Readouts**



	SIZE	COLOR	DECIMAL	EACH	SPECIAL
OPCOA SLA-1	.33	Red	Yes	2.95	4/\$11
OPCOA SLA-11C	.33	Green	Yes	4.95	4/\$16
OPCOA SLA-3H	.70	Red	Yes	4.50	4/\$16

All use 7447 Drivers. Specs included.

**RF POWER TRANSISTORS**

We did it again - All brand new with standard markings and most were manufactured this year. A major manufacturer dropped his RF power line and we bought his inventory.


2N5589	3 Watts Out	\$ 3.50
2N5590	10 Watts Out	6.00
2N5591	25 Watts Out	12.00
2N6080	4 Watts Out	5.00
2N6082	25 Watts Out	10.00
2N6083	30 Watts Out	12.00
2N6084	40 Watts Out	15.00



All are Silicon NPN and power output ratings are good to 175 MHZ. Hurry some quantities are limited.

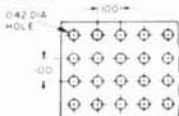**KEYSTONE PERF BOARD**

G 10 Glass Epoxy  
Perf Board 3/64" Thick



No.	UNCLAD	Size (in.)	Price
4229		2 x 4"	\$ 85
4230		2 x 6	1.09
4231		4" x 6	1.55
4232		17 x 6	5.75
COPPER CLAD ONE SIDE			
4238		2 x 4"	1.35
4239		2 x 6	1.85
4240		4" x 6	3.20
4241		17 x 6	6.70

WE GUARANTEE WHAT WE SELL!!!!

We ship UPS whenever possible. Give street address. Include enough for postage, excess refunded in cash. Florida residents include 4% Tax.

inherent protection against strong rf fields. The Qs of the tuned circuits are engineered for high gain and adequate bandwidth to cover the entire amateur bands with MARS overlap. Insertion loss, when the amplifier is turned off, is kept to a minimum through the use of a straight-through coaxial loop and low-loss ceramic switches.

Biasing of the amplifier is optimized for best gain, cross-modulation and noise-figure characteristics. Gain may be adjusted by varying the main supply voltage  $\pm 3$  volts. The amplifier is easily installed on any communications receiver in minutes by simply inserting it between the receiver and the antenna. Transceivers may be easily modified by breaking the antenna circuit from the T/R relay to the receive rf amplifier and bringing each end to an external phono jack.

The SABA-5 carries a 30-day money-back guarantee and 1-year warranty, and is priced at \$79.95. Models for 160 meters, 6 meters and 2 meters are also available. For more information, write to Symtek, Inc., Box 128, Clearwater, Florida 33517, or use *check-off* on page 94.

**three-pin voltage regulators**



Many times the need arises for a simple, low-cost voltage regulator which can provide a moderate amount of current without complex current-boosting circuitry. Applications include on-card regulation and power supply distribution in large systems.

A new Motorola device family composed of seven fixed-voltage regulators

housed in a popular plastic power transistor package fulfills these needs. The MC7805/24 series positive voltage regulators can supply in excess of 1 ampere at nominal voltages of 5, 6, 8, 12, 15, 18 or 24 volts (as designated by the last two digits of the device number). However, unlike most voltage-regulator ICs, these devices have only three terminals — input, output and ground — and they require no external components. The devices can be easily attached to a heatsink surface with a machine screw through the hole in the package to attain higher maximum power dissipation.

To insure a rugged device, internal current limiting, thermal shutdown, and output transistor safe operating area compensation techniques are employed. These features make the regulators essentially burn-out safe.

For further information contact the Technical Information Center, Motorola Inc., Semiconductor Products Division, Post Office Box 20912, Phoenix, Arizona 85036, or use *check-off* on page 94.

## spring-type fuse holder




Oneida Electronics has recently introduced a new coil-spring fuse holder that makes it easier than ever to replace fuses. The new holder eliminates the need for using more costly type pig-tail fuses and does away with cutting and re-soldering pig-tail leads.

Regular fuses can be snapped into the coil-spring holder in seconds. Service people will find them ideal for use in those hard-to-get at places. Replaces permanently installed pig-tail fuses by merely soldering the leads of the new

\*patents pending

new Slinky® dipole\* with helical loading

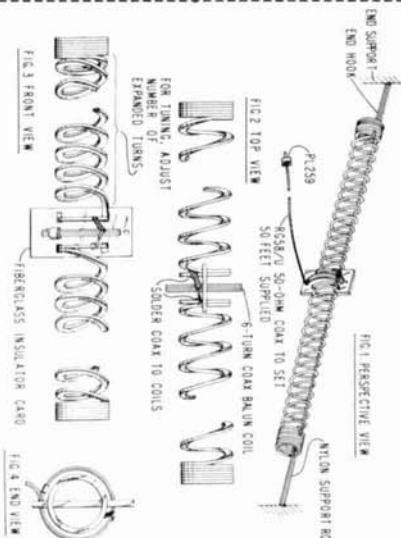radiates a good signal at 1/10 wavelength long!



• This electrically small 80/75, 40, & 20 meter antenna operates at any length from 24 to 70 feet • no extra balun or transmatch needed • portable — erects & stores in minutes • small enough to fit in attic or apartment • full legal power • low SWR over complete 80/75, 40, & 20 meter bands • much lower atmospheric noise pickup than a vertical • Kit includes special 4" coils, balun, 50 ft. RG58/U coax, PL259 connector, & nylon rope • this new antenna was developed for a government application, and really works •

Send for your antenna to: code HR

**TELETRON CORP.**, 2950 Veterans Hwy. Bohemia, L. I., N. Y. 11716

Kit #80-40-20 \$29.95 plus \$1 shipping

Coils only (pair of 4" dia. special coils) \$17.95 plus \$1 shipping

(N. Y. residents add 7% sales tax)

name \_\_\_\_\_

street \_\_\_\_\_

town \_\_\_\_\_ zip \_\_\_\_\_

enclose check with order - we ship UPS upon receipt of order

Export: 2200 Shames Dr., Westbury, N. Y. 11590

Cable: CHURCHIN, Westbury, N. Y.

**HERE IS A FIST FULL  
of 2 METER POWER**



**NEW**

American Made  
Quality at Import Price

## Model HRT-2 5 Channel, Narrow Band 2.2 watt FM Transceiver

This light weight, "take anywhere" transceiver has the "Regency-type" interior componentry to give you what others are looking for in portable communications. You get a heavyweight 2.2 watt signal . . . or if you want, flip the HI/LO switch to 1 watt and the receiver gives you 0.7 uv sensitivity and 0.5 watts audio. Both transmitter and receiver employ band-pass circuitry so that power and sensitivity are maintained across the entire band. Get one to go. . . . only


**\$179<sup>00</sup>**

Amateur Net

**Regency** ELECTRONICS, INC.

7707 Records Street  
Indianapolis, Indiana 46226

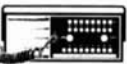
An FM Model For Every Purpose . . .  
Every Purse



HR-2MS  
8 Channel Transcan  
2 Meter FM Transceiver



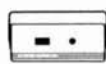HR-212  
12 Channel-20 Watt  
2 Meter FM Transceiver



AR-2  
2 Meter FM  
Power Amplifier

spring holder to stubs of removed pig-tail fuse. The spring holders have been designed to accommodate tv, radio, hi-fi and most other electronic device fuses.

The new spring-type holder is permanent — quality constructed of tempered spring steel with dip soldered leads. Available packaged 5 pair per pack on dealer cords and in bulk for OEM use. For detailed information write Oneida Electronic Manufacturing, Inc., Meadville, Pennsylvania 16335, or use *check-off* on page 94.

## new allied catalog



Allied Electronics (Division of Tandy Corporation) has published their new catalog number 740. Previous catalogs have served as the electronics industry's "answer book," and the new catalog is even better. In addition to the easy-to-use tab-index format and easy-to-use 9 x 11-inch size introduced in 1973, even more useful product information is included in the book. Prime feature of the Engineering Manual and Purchasing Guide catalog is the inclusion of *Engineering Drawings* of all electrical components. All physical dimensions are given to allow efficient design of electronic packages before components are purchased. Electrical characteristics of all items are also included.

Allied has also introduced a new policy for obtaining a copy of their

catalog: instead of the \$5.00 price, or \$10.00 order requirement, *anyone* can now obtain a copy for the cost of postage and handling—just \$1.00. All items shown are in stock at all Allied warehouses. With Allied enjoying the best order filling record in the industry, this, as always, is the one catalog you can't do without. For your copy, send \$1.00 for postage and handling to Allied Electronics, 2400 W. Washington Boulevard, Chicago, Illinois 60612.


## transistor substitution handbook

The *Transistor Substitution Handbook* is updated continuously, and a new edition is published annually. This 13th edition has been published in an easy-to-read 8-1/2x11-inch format, and contains over 100,000 transistor substitutions. To guarantee the most accurate possible substitutions, the electrical and physical parameters as described in the manufacturers' published specifications for each bipolar transistor were fed into a computer; then each transistor was compared with all others. Consequently, transistors which matched within prescribed limits are listed as substitutes.

Section 1 of the handbook contains substitutions for both American and foreign-made transistors which are arranged in numerical and alphabetical order. Types recommended by the manufacturers of general-purpose replacement transistors are included at the end of each list of substitutes. Additional data on these general-purpose replacement types — manufacturer, npn or pnp, germanium or silicon, and the recommended applications — are also reviewed.

The *Transistor Substitution Handbook* is a valuable source of information for amateurs concerned with transistor replacement in communications industrial, commercial or home-entertainment equipment. 144 pages, softbound. \$2.95 from Comtec Books, Greenville, New Hampshire 03048.

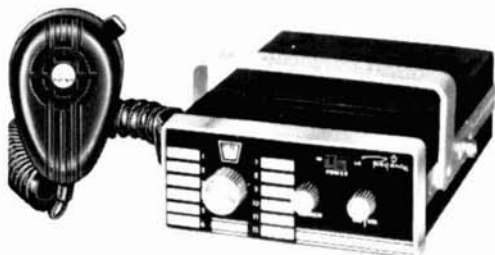*Regency* <sup>👑</sup> **HR-2B gives**  
a lot to talk over



American Made Quality at Import Price

## Full 12 Channel, 15 Watts with HI/LO power switch

Here is everything you need, at a price you like, for excellent 2 meter FM performance. The 12 transmit channels have individual trimmer capacitors for optimum workability in point-to-point repeater applications.

Operate on 15 watts (minimum) or switch to 1 watt. 0.35 uv sensitivity and 3 watts of audio output make for pleasant, reliable listening.

And the compact package is matched by its price.

**\$229<sup>00</sup>**

Amateur Net

*Regency* <sup>👑</sup> **ELECTRONICS, INC.**  
7707 Records Street  
Indianapolis, Indiana 46226

An FM Model For Every Purpose . . .  
Every Purse



HR-6  
12 Channel-25 Watt  
6 Meter FM Transceiver

HR-220  
12 Channels-10 Watts  
220 MHz FM Transceiver

ACT 10-H/L/U  
3 Band-10 Channel FM  
Scanner Receiver

# 10.7 MHz CRYSTAL FILTERS FOR FM

## SYNONYMOUS FOR QUALITY AND ADVANCED TECHNOLOGY



### MATCHING CRYSTAL DISCRIMINATORS


NBFM XD107-01  
 WBFM XD107-02  
 (1-9) \$22.10 each



SPECTRUM  
 INTERNATIONAL  
 BOX 1084 CONCORD  
 MASSACHUSETTS 01742

Filter Type	XF107-A	XF107-B	XF107-C	XF107-D	XF107-E	XF107-S04	XF107
Application	NBFM	NBFM	WBFM	WBFM	WBFM	NBFM	NBFM
Number of Filter Crystals	8	8	8	8	8	4	2
Bandwidth	12.0 kHz	15.0 kHz	30.0 kHz	36.0 kHz	40.0 kHz	14.0 kHz	14.0 kHz
Pass Band Ripple	← < 2 dB →					← 1 dB →	← 2 dB →
Insertion Loss	≤ 3.5 dB	≤ 3.5 dB	≤ 4.5 dB	≤ 4.5 dB	≤ 4.5 dB	≤ 3 dB	≤ 1.5 dB
Input-Output	820 Ω	910 Ω	2000 Ω	2700 Ω	3000 Ω	910 Ω	2500 Ω
Termination	25 pF	25 pF	25 pF	25 pF	25 pF	35 pF	-
Shape Factor	(70 dB) 2.4	(70 dB) 2.3	(70 dB) 2.2	(70 dB) 1.9	(70 dB) 2.0	(40 dB) 3.0	(20 dB) 3.6
	(90 dB) 2.8	(90 dB) 2.9	(90 dB) 2.7	(90 dB) 2.5	(90 dB) 2.5	-	(30 dB) 5.7
Ultimate Attenuation	← > 90 dB →					> 60 dB	> 30 dB
Size	← 1 27/64" x 1 3/64" x 3/4" High →					Hc 6/u	Hc 18/u
	← Mounting Hardware Included →					can	can
Price (1-9)	← \$40.60 →					\$18.95	\$7.95

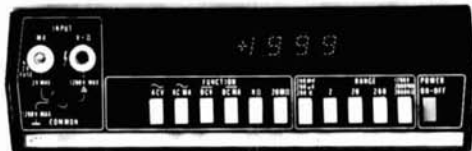In order to simplify matching, the input and output of all filters (except XF102) comprise tuned differential transformers with the "common" connections internally connected to the metal case.



### Think of it as the best tester in your bag. Only \$299

Now you can get a high performance Model 8000A Digital V.O.M. from Fluke, America's foremost maker of quality digital multimeters, especially designed for TV, radio, stereo and audio service. No other digital V.O.M. gives you the resistance range to check breakers and switches, the high resolution voltage to look at emitter base and other transistor voltages, excellent accuracy and full accuracy with a 30 second warm-up.

Measures in 26 ranges 100 μV to 1200 V, 0.1 μA to 2A, and 100 milliΩ to 20 megΩ with a basic dc accuracy of 0.1%. Full year guarantee. Low cost options include rechargeable battery pack, printer output, deluxe test leads, HV, RF & 600-amp ac current probes, carrying case, and rack mount. Unique self zero eliminates offset uncertainty. Electronics securely mounted in high-impact case. Service centers throughout U.S., Canada, Europe and Far East for 48-hour turnaround repair.



P. O. Box 7428,  
 Seattle, Washington 98133.

Get all the details from your nearest Fluke sales office. Dial toll-free 800-426-0361 for address of office nearest you.

### USED TEST EQUIPMENT

All checked and operating unless otherwise noted. FOB Monroe. Money back (less shipping) if not satisfied.

Boonton 190A Q-mtr 20-260 MHz	Q5-1200	375
Boonton 202B Sig Gen AM-FM	54-216 MHz	325
Boonton 202E - Later version of above		585
Boonton 260A Q-mtr .05-50 MHz	Q10-625	375
HP100D-Freq, stand, w/scope-Acc.	1ppm	85
HP185A Scope w/186B amp sampling	1GHz	335
HP330C Dist anal 20 Hz-20kHz	1%	225
HP524D-Freq Counter, Basic unit	10Hz-10MHz	185
HP540B Trans osc. for 524 to 12.4GHz		185
HP608D (TS510A/U) sig. gen.	10-420 MHz	450
Nems Clark 1671 FM rcvr	175-260MHz	125
Polarad MSG34-Sig. Gen	4.2-11GHz calib. attn.	
	AM-FM-Pulse mod.	495
Polarad R uwave rcvr	4.84GHz with plug-in	AM, FM, CW, Pulse — less plug-in
		225
Polarad TSA Spec. Anal	.01-44GHz with plug-in	
	— less plug-in	125
Republic VA260 Q-mtr (sim. Boonton 260A)		185
Soliton 200A SCR tester-checks anode, gate	voltage, current, leakage and holding	165
Stoddart NM10A (URM-6) RF intens mtr	10-250 kHz, complete with acc.	630
Stoddart NM20A (PRM-1) RF intens mtr	15-25MHz, complete with acc.	655
Stoddart NM52A-RFI mtr.	.375-1GHz, w/ acc.	985
Tek RM 15-DC-15MHz GP scope		265
Tek 181 Time mark generator		95
Tek 190A Const. Ampl. Sig. Gen.	.35-50MHz	125
Tek 531 DC-15MHz scope-takes letter plug-in		175
Tek 565 dual beam 10 MHz scope, less plug-ins		625
SG24/TRM3 Sweep Gen.	15-400 MHz, CW, AM, FM Xtal markers, scope-Dev. to 20%	245
TS-403A-Sig. Gen. (HP616)	1.8-4GHz	385
URM 7 RI-FI mtr (sim. NF-105)	20-400MHz	750

(Send SASE for complete list)

**GRAY** Electronics  
 P. O. Box 941, Monroe, MI 48161  
 Specializing in used test equipment

# LIKE FM OR CW ?



*Then you'll love  
Data Engineering's  
new catalog*

Write for your free copy today!

## TOUCH TONE PADS

More features than any other pad including built-in monitor speaker and latest Phase-Lock loop circuitry.

TTP-1 Standard pad for portable transceiver mounting.

TTP-2 Standard pad in attractive case for home or mobile use.

TTP-3 Mini-pad in attractive case for home or mobile use.

TTP-4 Mini-pad for portable transceiver mounting.

TTP-1, 2, 3 & 4, Sh. wt. 1 lb. .... \$44.50

TTP-1K, 2K, 3K & 4K, Sh. wt. 1 lb. .... \$34.50

## CRICKET 1

A popularly priced IC keyer with more features for your dollar. Cricket 1 is a small size, solid state keyer designed for the beginner as well as the most advanced operator. It provides the user with fatigue-free sending and its clean, crisp CW allows for easy copying at all speeds. Turned on its side, the Cricket can be used as a straight key for manual keying.

CRICKET 1 Sh. Wt. 3 lbs. \$49.95

## 2-METER PREAMP

Specially made for both OLD and NEW receivers. The smallest and most powerful preamp available. Provides 20dB gain at 2.5 N.F. to bring in the weakest signals.

Sh. wt. 4 oz. \$9.50 kit  
\$12.50 wired

Please include sufficient postage for shipping.



# DATA ENGINEERING INC.



Ravenswood Industrial Park, Springfield, Va. 22151

5554 Port Royal Road • 703-321-7171

QRM  
QRM  
QRM

QRM QRN QRM



## WHY FIGHT QRM & QRN?

Are your CW contacts lost because of QRM or QRN? The NEW DE-101 family of Signal Discriminators is designed to fight QRM and QRN for you without rig modifications. Each discriminator unit consists of two 3 pole operational amplifier filters stagger tuned for a flat 100 hertz bandpass at 1,000 Hz. A buffer amplifier is included for driving earphones, or a 3 watt power amplifier for driving an 8 ohm speaker. No adjustments, factory tuned, plug in installation, one year warranty, and 15 day return privilege.

**DE-101** For earphones only. 115 VAC \$29.95 + \$2 ship.  
**DE-101A** For spkr & phones. 115 VAC \$39.95 + \$2 ship.  
**DE-101B** For spkr & phones. 12 VDC \$29.95 + \$1 ship.  
**DE-101C** For earphones only. 12 VDC \$19.95 + \$1 ship.  
**CB-1** Wired & tested DE-101C circuit board \$14.95 ppd.  
**CB-2** 3 Watt Audio PWR AMP for 8 ohm spkr. 12 VDC Kit \$8.95 ppd. Wired & tested \$10.95 ppd.  
 Ala. residents add 5% sales tax.

**DYNAMIC ELECTRONICS INC.**  
 BOX 1131 DECATUR, AL. 35601

QRM QRN QRM

# STOP

TEN-TEC-TRITON II	\$606.00
TEN-TEC-TRITON I	\$519.00
MAGNUM 6 RF PROCESSORS	
MOR GAIN ANTENNAS	\$ 40.00
GENAVE-2	\$249.95
MOSLEY-CLASSIC 36	\$188.10
REGENCY HR-212	\$259.00
HYGAIN TH6DXX	\$179.95
GALAXY GT-550A	\$595.00
VENUS SSTV	\$349.00
GLADDING 25	\$249.95
STANDARD 146A	\$289.00

**LOU GOLDSTEIN, K4LAN**  
 P.O. BOX 3561, PENSACOLA, FLA. 32506  
 Drop me a line for those unadvertised extras

## MINIATURE SUB-AUDIBLE TONE ENCODER

\$14.95  
 Wired-Tested



- Compatible with all sub-audible tone systems such as Private Line, Channel Guard, Quiet Channel, etc.
- Glass Epoxy PCB, silicon transistors, and tantalum electrolytics used throughout
- Any miniature dual coil contactless reed may be used (Motorola TLN6824A, TLN6709-B — Bramco RF-20)
- Powered by 12vdc @ 3ma
- Use on any tone frequency 67Hz to 250Hz
- Miniature in size 2.5 x .75 x 1.5" high
- Complete with Reed \$28.45 (Specify Freq.)
- Output 3v RMS sinewave, low distortion

Postpaid — Calif. residents add sales tax  
**COMMUNICATIONS SPECIALISTS**  
 P. O. Box 153, Brea, CA 92621

## SUPER CRYSTAL THE NEW DELUXE DIGITAL SYNTHESIZER!! FROM RP



**MFA-22 DUAL VERSION**  
 Also Available MFA-2 SINGLE VERSION

- Transmit and Receive Operation: All units have both Simplex and Repeater Modes
- Accurate Frequency Control: .0005% accuracy
- Stable Low Drift Outputs: 20 Hz per degree C typical
- Full 2 Meter Band Coverage: 144.00 to 147.99 MHz. in 10KC steps
- Fast Acting Circuit: 0.15 second typical setting time
- Low Impedance (50 ohm) Outputs: Allow long cable runs for mobiles
- Low Spurious Output Level: similar to crystal output

SEND FOR FREE DETAILS **RP Electronics**  
 Prices MFA-2 \$210.00 BOX 1201H  
 MFA-22 \$275.00 CHAMPAIGN, ILL.  
 Shipping \$3.00 extra 61820

For **FREQ. STABILITY**  
 Depend on JAN Crystals. Our large stock of quartz crystal materials and components assures Fast Delivery from us.

## CRYSTAL SPECIALS

- 2-METER FM for most Transceivers ea. \$3.75  
 144-148 MHz — .0025 Tol.
  - Frequency Standards
    - 100 KHz (HC 13/U) 4.50
    - 1000 KHz (HC 6/U) 4.50
  - Almost all CB Sets, Tr. or Rec. 2.50  
 (CB Synthesizer Circuit on request)
  - Any Amateur Band in FT-243 1.50  
 (80-meter, \$3.00 - 160-meter not avail.) 4 for 5.00
- For 1st class mail, add 20¢ per crystal. For Airmail, add 25¢. Send check or money order. No dealers, please.



Division of Bob Whan & Son Electronics, Inc.  
 2400 Crystal Drive  
 Ft. Myers, Florida 33901  
 All Phones (813) 936-2397

Send 10¢ for new catalog with 12 oscillator circuits and lists of frequencies in stock.



CW or RTTY, whichever way you go,  
**HAL HAS TOP QUALITY  
 YOU CAN AFFORD!**



**TOP QUALITY RTTY... WITH THE HAL MAINLINE ST-6 TU.** Only 7 HAL circuit boards (drilled G10 glass) for all features, plug-in IC sockets, and custom Thordarson transformer for both supplies, 115/230 V, 50-60 Hz. Kit without cabinet, only \$135.00; screened, punched cabinet with pre-drilled connector rails, \$35.00; boards and complete manual, \$19.50; wired and tested units, only \$280.00 (with AK-1, \$320.00).\*



**TOP QUALITY... WITH THE HAL 1550 ELECTRONIC KEYSER.** Designed for easy operation; perfectly timed CW with optional automatic ID for sending call letters, great for DX and RTTY; TTL circuitry, transistor switching for grid block, cathode keying. Handsome rugged crackle cabinet with brushed aluminum panel. With ID, only \$90.00; without ID, \$65.00.\*

**OTHER HAL PRODUCTS INCLUDE:**

ID-1 Repeater Identifier (wired circuit board)	\$ 75.00*
ID-1 (completely assembled in 1 1/2" rack cabinet)	\$115.00*
HAL ARRL FM Transmitter Kit	\$ 50.00*
W3FFG SSTV Converter Kit	\$ 55.00*
Mainline ST-5 TU Kit	\$ 50.00*
Mainline AK-1 AFSK Kit	\$ 27.50*



**TOP QUALITY... WITH THE HAL MKB-1 MORSE KEYBOARD.**

As easy as typing a letter—you get automatic CW with variable speed and weight, internal audio oscillator with volume and tone controls, internal speaker, and audio output jack. Smooth operation; completely solid-state, TTL circuitry using G10 glass boards, regulated power supplies, and high voltage transistor switch. Optional automatic ID available. Assembled MKB-1, \$275.00. In kit form, \$175.00.\*



**NEW FROM HAL—TOP QUALITY RVD-1002 RTTY VIDEO DISPLAY UNIT.** Revolutionary approach to amateur RTTY... provides visual display of received RTTY signal from any TU, at four speeds (60, 66, 75, and 100 WPM), using a TV receiver modified for video monitoring. Panasonic solid-state TV receiver/monitor, or monitor only, available. RVD-1002, \$525.00; Panasonic TV receiver/monitor, \$160.00; monitor only, \$140.00.\*

**TOP QUALITY... WITH THE HAL RKB-1 TTY KEYBOARD.** Gives you typewriter-easy operation with automatic letter/number shift at four speeds (60, 66, 75, and 100 WPM). Use with RVD-1002 video display system, or insert in loop of any teleprinter, for fast and easy RTTY. Completely solid state, TTL circuitry using G10 glass boards, regulated power supplies, and transistor loop switch. RKB-1 assembled, only \$275.00.\*



HAL provides a complete line of components, semi-conductors, and IC's to fill practically any construction need. Send 24¢ to cover postage for catalog with info and photos on all HAL products. Above prices do not include shipping costs. Please add 75¢ on parts orders, \$2.00 on larger kits. Shipping via UPS whenever possible; therefore, street address required.

**HAL COMMUNICATIONS CORP.**

Box 365 L, Urbana, Ill. 61801 • 217-359-7373



# THE MOST COMPLETE 2 METER REPEATER AVAILABLE...

# DYCOMM ECHO III

- INCLUDES EVERYTHING NEEDED BUT THE ANTENNA AND DUPLEXER
- DESIGNED TO COMPLY WITH NEW FCC REQUIREMENTS
- ASK FOR FLYER SHEET

**DYNAMIC COMMUNICATIONS, INC.**  
948 Ave. "E" P.O. Box 10116  
Riviera Beach, Fla. 33404  
(305) 844-1323



**MODEL "A" Frequency Counter Price \$299.00**  
10Hz to 80 MHz ( $\pm$  1Hz) Direct Count guaranteed (1Hz to over 100MHz) typical)  
Read Out: 5 LED digits + LED Over Range  
Sensitivity: Less than 100 millivolts over entire range.  
Power Req.: Either 120 VAC or 12 VDC 15 watts approx.  
Small Size: 2.34" x 5.68" x 8.18"  
Overload protected input and DC power input.

**MODEL "AS" Frequency Counter Price \$375.00**  
Exactly as above plus an internal 250MHz Scaler ( $\pm$  10Hz to well over the guaranteed frequency of 250 MHz.) No external power is required.  
Shifting DECIMAL POINT gives a DIRECT READOUT of VHF Frequencies.  
One BNC INPUT for both ranges. No cable changing from HF to VHF.  
(CA residents add State Sales Tax)  
Dealer inquiries invited



**ELECTRONICS**  
P.O. BOX 1672  
VISTA, CA. 92083  
714-726-1313

## the latest ...

- FROM
- FCC
  - ARRL
  - INDUSTRY
  - PROPAGATION
  - CONTESTS
  - DX



ISSUE\*

AFTER ISSUE  
AFTER ISSUE!

\*24 issues  
per year  
(or more when things  
get busy)

A four page, instant  
newsletter in the mail  
when it happens, not  
weeks later

1 year \$12.00 US, Canada & Mexico — \$15.00 Worldwide

**hr REPORT**  
GREENVILLE, NH 03048

# Largest Selection TTL IC's

Lowest Prices • Buy 3 or more, 10% discount

Under six type numbers! See sheets on request ONLY

pe New	• DIP Packages	SN7437	.55	SN7472	.50	SN74112	.95	SN74163	1.95
SN7400	\$0.30	SN7438	.55	SN7473	.55	SN74113	.95	SN74164	1.95
SN7401	.30	SN7440	.30	SN7474	.45	SN74114	.95	SN74165	2.10
SN7402	.30	SN7441	1.40	SN7475	.65	SN74115	.60	SN74166	2.05
SN7403	.35	SN7442	1.50	SN7476	.95	SN74122	.95	SN74173	2.50
SN7404	.30	SN7443	1.50	SN7477	.95	SN74123	1.20	SN74174	3.20
SN7405	.35	SN7444	1.50	SN7478	.95	SN74124	1.20	SN74175	3.20
SN7406	.45	SN7445	1.50	SN7479	.95	SN74125	.71	SN74176	2.10
SN7407	.55	SN7446	1.65	SN7480	.65	SN74126	.71	SN74177	2.10
SN7408	.35	SN7447	1.45	SN7481	1.25	SN74127	1.25	SN74178	2.10
SN7410	.30	SN7448	1.50	SN7482	1.25	SN74128	1.25	SN74179	2.10
SN7411	.30	SN7450	.30	SN7483	1.25	SN74129	1.25	SN74180	2.10
SN7413	.95	SN7451	.30	SN7484	1.41	SN74130	1.61	SN74181	4.90
SN7415	.55	SN7453	.30	SN7485	1.41	SN74131	1.61	SN74182	2.20
SN7416	.55	SN7454	.30	SN7486	1.41	SN74132	1.61	SN74183	2.20
SN7417	.55	SN7455	.30	SN7487	1.41	SN74133	1.61	SN74184	2.20
SN7419	.30	SN7456	.50	SN7488	4.50	SN74134	1.61	SN74185	2.50
SN7420	.30	SN7457	.50	SN7489	4.50	SN74135	1.61	SN74186	2.50
SN7421	.35	SN7458	.50	SN7490	4.50	SN74136	1.61	SN74187	2.50
SN7422	.35	SN7459	.50	SN7491	1.35	SN74137	1.61	SN74188	2.50
SN7425	.50	SN7460	.30	SN7492	1.35	SN74138	1.61	SN74189	2.50
SN7426	.36	SN7461	.35	SN7493	1.35	SN74139	1.61	SN74190	1.95
SN7427	.30	SN7462	.35	SN7494	1.35	SN74140	1.61	SN74191	1.95
SN7432	.35	SN7463	.35	SN7495	1.35	SN74141	1.61	SN74192	1.95
SN7433	.35	SN7464	.30	SN7496	1.35	SN74142	1.61	SN74193	2.65
SN7434	.35	SN7465	.50	SN7497	1.35	SN74143	1.61	SN74194	2.65
SN7435	.35	SN7466	.50	SN7498	1.35	SN74144	1.61	SN74195	2.65
SN7436	.35	SN7467	.50	SN7499	1.35	SN74145	1.61	SN74196	2.65
SN7437	.35	SN7468	.50	SN7500	1.35	SN74146	1.61	SN74197	2.65
SN7438	.35	SN7469	.50	SN7501	1.35	SN74147	1.61	SN74198	2.65
SN7439	.35	SN7470	.50	SN7502	1.35	SN74148	1.61		
SN7440	.35	SN7471	.55	SN7503	1.35	SN74149	1.61		
SN7441	.35	SN7472	.55	SN7504	1.35	SN74150	1.61		
SN7442	.35	SN7473	.55	SN7505	1.35	SN74151	1.61		
SN7443	.35	SN7474	.55	SN7506	1.35	SN74152	1.61		
SN7444	.35	SN7475	.55	SN7507	1.35	SN74153	1.60		
SN7445	.35	SN7476	.55	SN7508	1.35	SN74154	2.10		
SN7446	.35	SN7477	.55	SN7509	1.35	SN74155	1.58		
SN7447	.35	SN7478	.55	SN7510	1.35	SN74156	1.55		
SN7448	.35	SN7479	.55	SN7511	1.35	SN74157	1.45		
SN7449	.35	SN7480	.55	SN7512	1.35	SN74158	1.55		
SN7450	.35	SN7481	.55	SN7513	1.35	SN74159	1.55		
SN7451	.35	SN7482	.55	SN7514	1.35	SN74160	1.95		
SN7452	.35	SN7483	.55	SN7515	1.35	SN74161	1.95		
SN7453	.35	SN7484	.55	SN7516	1.35	SN74162	1.95		
SN7530	.35	SN7561	.55	SN7593	1.35	SN74239	1.95		

VHF  
DX OPS



**MODEL 60 SPEECH PROCESSOR** — QRO the average-to-peak ratio of the speech waveform as much as 8 db using a logarithmic principle. Operates with FM, SSB and AM transmitters and transceivers. Low/High impedance Mic input Two 9Vdc batteries provide a self-contained unit.

**Model 60W** (Processor Assembled) \$26.50  
**Model 60K** (Processor Kit) \$21.90  
**200-15** (Processor Board Kit) \$12.95

**MARTEK**

BOX 185A • FRANKLIN, PA. 16323  
PHONE: 814/432-3647

DEALERS:

VE AMATEUR RADIO SALES, Downsview, Ontario, Canada •  
SST ELECTRONICS, Lawndale, CA. 90260 • GARY RADIO, INC.,  
San Diego, CA. 92111 • AN-TEK INDUSTRIES, Elkhart, IN. 46517 •  
SIGNAL SYSTEMS, Bedford, OH. 44146 • KASS ELECTRONICS  
DISTRIBUTORS, Drexel Hill, PA. 19026 • M. WEINSCHENKER  
K3DPJ, Irwin, PA. 15642 • HAMTRONICS, Treviso, PA. 19047

QRO  
?



**MODEL 20 DIGITAL DIAL** — Available for Collins and Drake gear. Optional four digit readout and crystal time base. QSY your fixed or mobile transmitter, receiver or transceiver with 100 Hz accuracy and no last digit jitter. Simple one wire connects dial to rig and you're ready to go. Specify your type of rig.

**Model 20** (5-5.5 Mhz VFO range) ... \$169.95  
**Model 20C** (Collins) ... \$169.95  
**Model 20D** (Drake) ... \$169.95  
**Options:** (4 Digit Readout) ... \$ 29.95  
(Crystal Time Base) ... \$ 29.95

CW  
OPS



**MODEL 11A PADDLE** — Designed with reliability in mind. No mechanical switches or bearings to fail. Paddle contact spacing adjusts easily.

**Model 11A** (Assembled) ... \$9.95

**MODEL 10A ELECTRONIC KEYS** — Has NEW features at no extra cost! Linear Speed Control and Operate/Tune Switch. Plus internal penlight cells and ready relay output provide a compact, portable, versatile unit.

**Model 10AWA** (Keyer & Sidetone Assembled) ... \$33.95  
**Model 10AW** (Keyer Assembled) ... \$26.50  
**Model 10AK** (Keyer Kit) ... \$21.95  
**200-2K** (Keyer Board Kit) ... \$12.95  
**200-3K** (Sidetone Board Kit) ... \$ 4.95

# FM Schematic Digest

A COLLECTION OF  
MOTOROLA SCHEMATICS

Alignment, Crystal, and Technical Notes  
covering 1947-1960

136 pages 11 1/2" x 17" ppd \$6.50

S. Wolf  
P. O. Box 535

Lexington, Massachusetts 02173

DIGITAL THEORY, DESIGN,  
CONSTRUCTION

# LOGIC NEWSLETTER


SAMPLE COPY \$ 1.00  
LOGIC NEWSLETTER  
POB 252  
WALDWICK, N.J. 07463
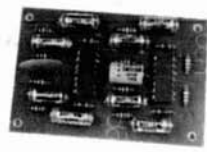
## CW FILTER



**New Model CWF-20X** — \$19.95.  
Ready to use. Please include  
\$1.00 postage.

- Get Razor Sharp selectivity from any receiver or transceiver.
- Extremely high skirt rejection.
- Drastically reduces all background noise.
- No audible ringing.
- No impedance matching.
- Ultra modern active filter design uses IC's for super high performance.



**Model CWF-2** — \$12.95. Kit.  
\$14.95 Wired, tested, guaranteed.  
Please include 55c postage.

We have what we think is the finest CW filter available anywhere. The 80 Hz selectivity with its steep sided skirts will allow you to pick out one signal and eliminate all other QRM and QRN. Simply plug it into the phone jack or connect it to the speaker terminals of any receiver or transceiver and use headphones, small speaker or speaker amplifier. Better yet, connect it between any audio stages to take advantage of the built in receiver audio amplifier.

Build the 2+3 CW-F-2 PC card into your receiver or get the self contained and ready to use CWF-20X and plug in!

### SPECIFICATIONS

**BANDWIDTH:** 80 Hz, 110 Hz, 180 Hz (Switch selectable)  
**SKIRT REJECTION:** At least 60 db down 1 octave from center frequency for 80 Hz bandwidth  
**CENTER FREQUENCY:** 750 Hz  
**INSERTION LOSS:** None. Typical gain 1.2 at 180 Hz BW. 1.5 at 110 Hz BW. 2.4 at 80 Hz BW  
**INDIVIDUAL STAGE Q:** 4 (minimizes ringing)  
**IMPEDANCE LEVELS:** No impedance matching required  
**POWER REQUIRED CWF-2:** 6 volts (2 ma) to 30 volts (8 ma). CWF-20X standard 9 volt transistor radio battery  
**DIMENSIONS:** CWF-2 2+3 PC board: CWF-20X 4+3 1/4 x 2 3/16" (black nickel steel top; white aluminum bottom; rubber feet)

TRY this fantastic CW filter. If you don't think it is the best you have ever used, ask for your money back. We will cheerfully refund it. These filters carry a full one year warranty.

Write for FREE brochures and magazine test reports. Other IC active filters available. CW mini filter (1 1/2" x 2 1/2"), low pass, high pass, and wide bandpass filters. Audio amplifiers: 1, 1.2 watts. Crystal calibrator.

MJF ENTERPRISES

P. O. Box 494-A, Mississippi State, MS 39762

## — PCB KITS —

RTTY SPEED CONVERTER Drilled PCB 5 & 11 VDC \$40.00  
DRILLED PCB ONLY \$ 6.00  
RTTY AFSK Gen. All Shifts & CW I.C. 9 VDC @ 2ma \$6.60  
100 KHZ XTAL CALIBRATOR Less Xtal 9 VDC @ 2ma \$4.75  
POWER SUPPLY — 28 VDC @ 650 ma output \$8.95  
PREAMP MICROPHONE, 26 DB Gain 9 VDC @ 1ma \$3.50  
LIMITER PREAMP For High Z Mike 9 VDC @ 1ma \$4.80  
PRODUCT DETECTOR For Your Receiver 9 VDC @ 1ma \$3.60  
15' METER KIT Less 1ma Meter 6.3VAC \$4.75  
SWR METER, Stripline, Less 200µa Meter \$2.95  
WWV CONVERTER 3.5-4.0 MHz Output 9 VDC @ 5ma \$5.25  
Requires 6-6.5MHz Crystal  
6 METER CONVERTER FET Front End 9 VDC @ 5ma \$5.95  
7-11 MHz Output, Less 43 MHz Xtal  
CW KEYING MONITOR, RF Keyed, Less Spkr. 9 VDC @ 9ma \$4.70  
POWER SUPPLY - 9 VDC @ 50ma Output 115VAC \$4.85  
6 METER CASCADE PREAMP 80 VDC @ 4.5ma \$4.95  
Wired & Tested Less 2 ea 6CW4 Nuvistors  
DRILLS, #54, 56, 58 or 60 (each) \$4.00  
Finest Quality for PCB'S, Made in USA Three For \$1.00

EXCEPT AS NOTED ABOVE, ALL KITS ARE NEW, 100% SOLID STATE, AND COME COMPLETE WITH AN UNDRILLED G-10 PCB (PRINTED CIRCUIT BOARD) AND ALL PCB MOUNTED COMPONENTS. KITS ARE LESS POWER SUPPLIES, CHASSIS, AND ENCLOSURE HARDWARE. SEND SELF-ADDRESSED, STAMPED ENVELOPE FOR COMPLETE DATA SHEET AND SCHEMATIC.

SATISFACTION GUARANTEED. RETURN IN 30 DAYS FOR REFUND. ALL KITS POSTPAID. INCLUDE 25¢ HANDLING CHARGE. WASHINGTON RESIDENTS ADD 5.3% SALES TAX.

**Martex Corporation**

519 S. AUSTIN, SEATTLE, WASH. 98108

Your assurance of Performance and Quality



# FTdx401-B

Transceiver



## More For Your Money

### FTdx401

Built-in AC Power Supply  
Built-in WWV 10 MHz Band  
Built-in Noise Blanker  
25 and 100 KHz Calibrators  
VOX  
Clarifier  
Break-in CW with Sidetone  
1 KHz Readout  
Selectable SSB  
6 Month Warranty by Dealer  
Cooling Fan  
AM Position

**\$599.00**

No charge  
No charge  
No charge  
No charge  
No charge  
No charge  
No charge  
No charge  
No charge  
No charge  
No charge

**Total only \$599.00**

Amateur Price Net  
Price Subject To Change

**Tomorrow's Transceiver Today:** 20 tubes plus 50 silicon semiconductors, passive crystal filter (6 pole), velvet smooth tuning, superb noise blanker, standard electrical parts. This is truly the best buy in the amateur field today. See your local dealer for brochure & demonstration.

Factory Service is available even after your warranty has expired for the cost of labor and parts.

### YAESU DEALERS:

ADIRONDACK RADIO SUPPLY 518-842-8350  
185 West Main Street, Amsterdam, New York 12010  
AMATEUR ELECTRONIC SUPPLY 414-442-4200  
4828 W. Fond du Lac Ave., Milwaukee, Wisc. 53216  
AMATEUR ELECTRONIC SUPPLY 305-894-3238  
621 Commonwealth Avenue, Orlando, Florida 32803  
ELECTRONIC EXCHANGE CO. 508-834-9000  
608 Papworth, Metairie, Louisiana 70005  
FRECK RADIO SUPPLY 704-254-9551  
38 Biltmore Avenue, Asheville, North Carolina 28807  
GRAHAM ELECTRONICS 317-634-8486  
133 S. Pennsylvania St., Indianapolis, Indiana 46204  
HAM RADIO CENTER 314-993-6060  
8342 Olive Blvd., St. Louis, Missouri 63132  
HAM RADIO OUTLET 415-342-5757  
999 Howard Avenue, Burlingame, California 94010

HAMTRONICS 215-357-1400  
4033 Brownsville Rd., Trevese, Pennsylvania 19047  
HARRISON RADIO 516-293-7990  
20 Smith Street, Farmingdale, LI, New York 11735  
HENRY RADIO 213-272-0861  
11240 W. Olympic Blvd., Los Angeles, Calif. 90064  
JUGE ELECTRONICS 817-926-5221  
3850 S. Freeway, Fort Worth, Texas 76110  
QUEEN CITY ELECTRONICS, INC. 513-931-1577  
1583 McMakin Ave., Cincinnati, Ohio 45231  
RACOM ELECTRONICS 206-255-6656  
15051 S.E. 128th St., Renton, Washington 99055  
WEBSTER RADIO 209-224-5111  
2602 Ashlan, Fresno, California 97326  
WILSON ELECTRONICS 702-451-6650  
P.O. BOX 116, Pittman, Nevada 89044



### YAESU MUSEN USA INC.

7625 E. Rosecrans Avenue, Unit #29

Paramount, California 90723

Phone 213-633-4007

# **SBE** "CRUNCHER"

turns mild mannered 2 meter mobile FM transceivers into 70-90 watt roaring tigers!



SEND FOR DETAILED BROCHURE

**SB-1PA**, Class C amplifier, connects between FM transceiver and antenna and to car battery — **boosts output power approximately 10 times** (i.e., 7W in, 70W out, etc.) And broad band — covers 143-149 MHz.

Small — less than 1/10 cu/ft. — rugged cast housing readily mounted in car. Built-in antenna relay operates from rectified RF. All solid state using highest commercial quality **CTC** transistors — not surplus culls. Long-life — minimum drain.



LINEAR SYSTEMS, INC. 220 Airport Boulevard, Watsonville, CA 95076

## A FASCINATING HOBBY!

VINTAGE RADIO brings you the pioneer days of wireless and radio in pictures. The collector's bible, it opens the doors to a new hobby. Great browsing, too. Over 1,000 pictures, 263 pages. 1887-1929.



AVOID DELAY; SEND TODAY

Mail check to Vintage Radio, Dep't H, Box 2045, Palos Verdes Peninsula, CA., 90274

Vintage Radio, hard cover \$6.95   
 Vintage Radio, handbook 4.95   
 Radio Collectors Guide 3.95

Postage Paid, California residents add 5% Tax.

Name \_\_\_\_\_

Street \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

**ENJOY THE OLD DAYS!**

## STAR-TRONICS

INDUSTRIAL AND GOVERNMENT ELECTRONIC SURPLUS

PARTS & PIECES FOR SCHOOLS, SHOPS, HAMS & HOBBYISTS  
 SEND FOR OUR LATEST ALL DIFFERENT MONTHLY PICTURE CATALOG. NOW!

Box 17127, Portland, Ore. 97217



## IT'S FREE — IT'S AUTOMATIC

A packet containing a renewal application and renewal instructions will be sent to every US licensed amateur (except novices) approximately 3 months before his license expires. This service will start with licenses expiring in March 1974.

Watch your mailbox for this important reminder.

A PUBLIC SERVICE

from

**ham radio** Greenville NH 03048

## COMPUTER KEYBOARD

\$7.00 (as is)



Several styles on hand in poor condition, broken key/keys, broken case or no case, etc. Still a good value at \$7.00 for parts, switches, and each has encoder board in base.

2N2152	45 volt	170 watt	PNP-G	\$1.00
*2N3713	80	150	NPN-S	1.00
*2N3789	60	150	PNP-S	.75
2N5301	40	200	NPN-S	1.25
*2N5301	40	200	NPN-S	1.00

\*Removed from used equipment

## TRANSFORMERS

BRAND NEW, 115 volt AC input. OP AMP XFMR, out puts: 16 VCT 1/2 amp, 17 VCT 1/2 amp. \$3.50

## FILAMENT or BTRY CHARGER XFMR

output of 18 volts at 4.5 amp \$3.50



## CALCULATOR KEYBOARD

Brand new keyboards for hand held calculators. Two styles available.

One for use with calculator chip CAL TEX 5001-5002-5012 or MOSTEK 5010-5012. Another for use with Gen. Inst. chip C500.

Priced at \$8.00 each or two for \$15.00.



## CT 5005 CALCULATOR CHIP

Single MOS chip with all logic required for 12 digit 4 function desk top calculator with extra storage register for memory or constant. Multiplexed 7 segment outputs for LED, Incandescent, Fluorescent, or Gas Discharge displays. Brand new, bargain priced, with specs. \$8.00 each, 2 for \$15.00



## HP LED DISPLAYS

Brand new 4-on-a-strip LED readouts. End-butt two strips and come up with 8 digit readout. An unheard of Super Value . . . \$8.00 per strip, 2 strips \$15.00

Another strip . . . this one a Clock Chip readout. 2 digits . . . a space . . . and 2 more digits. Just right for a clock reading hours and minutes. This one only \$8.00

JOHN MESHNA JR. ELECTRONICS

## 313,344 CORE MEMORY \$125.00

From SPECTRA computer, visually OK. 64 x 68 x 4 x 18 core stack. Figures out to 35K Byte.

## LED 7

### SEGMENT READOUT

Similar to MAN-1. Factory seconds but functionally OK. Fit 14 pin DIP socket.

7 segment w/left decimal	\$3.00
#LED-A-L	
7 segment w/right decimal	3.25
#LED-A-R	
7 segment no decimal	2.75
#LED-A	

Above LEDES 2 for the price of 1  
Socket for above, gold plated leads 3/1.00



## IC SALE YOUR CHOICE 3 for \$1.00

μl 900 BUFFER TO-5	
μl 914 DUAL 2 INPUT GATE TO-5	
μl 923 JK FLIP FLOP TO-5	
μl 926 Hi speed JK FLIP FLOP TO-5	
μl 931 JK/RS FLIP FLOP (DIP)	
10 pin socket for TO-5 IC	3/1.00

## GIANT NIXIE B7971

Used \$1.00 Brand New \$2.00  
With schematic for GIANT clock.

## COMPUTER TAPE DECK \$75.00

Takes 1/2 inch tape, made by Computer Entry Systems. Visually ok, with electronics, no data available.

LASER DIODES: 6 watt \$10, 12 watt \$15

## CMOS 4814 HEX INVERTER

CMOS HEX INVERTER, dual inline package. 3-18 volt range, dual diode protection against static charge. Dielectrically isolated complimentary MOS. \$1.00 each 12 for \$10.00

## DUAL 16 BIT MEMORY

Dual 16 bit memory, serial MOS by Philco TO-5 case, brand new with 2 page specs. #PLR 532 \$1.00 each \$10/12

## 2048 BIT MOS MEMORY

2048 bit MOS LSI random access memory NEC 6003. All inputs except clock are TTL compatible. 2048 word by 1 bit. 22 pin ceramic dual-in-line. With specs. \$9.00 each 2 for \$17.00

## ASCII KEYBOARDS LIKE NEW \$45.00

From Raytheon, with encoder board in base, output on blue ribbon connector. This is the same keyboard we sell at \$50 except this one has no case. 5 extra function buttons each side. Price includes shipping world wide.



Postage Extra on all Items

P. O. Box 62 E. Lynn, Mass. 01904

# A COMPLETELY PORTABLE FREQUENCY COUNTER WITH . . .

- \* 10 HZ to 65 MHZ range
- \* Full six digit readout (L.E.D.)
- \* Sensitive front end (LESS THAN 10 MV.)
- \* Only \$199

## FEATURES

- High capacity rechargeable Ni Cd batteries
- Crystal controlled time base (can be field calibrated)
- Convenient 3-position range select switch allows:
  1. Readout always in MHZ.
  2. Eight digit resolution by range selection
  3. Direct reading pre-scaler operation to 999.999 MHZ.
- "Battery save" switch for spot checks
- Less than 5 watts power consumption (5 volts @ 0.9 AMPS)
- Dimension 6" x 3.5" x 2.3"
- TTL input for use with pre scaler
- Can be operated on internal or external power, with trickle charge and full charge positions
- Sample control lets operator determine how often the readout is updated. Can "hold" present count without being updated



Mail orders directly to:  
Great American Miniatures,  
Inc.  
P. O. Box 10990  
Midwest City, Okla. 73110

Model C-65 Freq. counter \$199.<sup>00</sup>  
Battery charger 8.<sup>00</sup>  
Battery charger & eliminator 18.<sup>00</sup>



## EAST COAST SERVICE CENTER

We also service all other popular makes.

Complete professionally staffed laboratory fully equipped for all aspects of maintenance and service. Graduate Engineer on duty. Custom Design services available.

### PROFESSIONAL ELECTRONICS CO., INC.

1710 JOAN AVE. EUDWOOD BRANCH  
BALTIMORE, MD. 21204  
301-661-2123

## WORLD QSL BUREAU

THE ONLY QSL BUREAU to handle all of your QSLs to anywhere; next door, the next state, the next country, the whole world. Just bundle them up (please arrange alphabetically) and send them to us with payment of 5¢ each.

5200 Panama Ave., Richmond, CA USA 94804

## EXPERIMENTER'S LIBRARY

HAMS, HOBBYISTS. If you like experimenting (we do), you'll love the Library! The Library is a series of plans sold on a subscription basis, including: microwave transceivers, an automatic Morse Code sender, mini-computer projects, plus telephone and audio circuits. Presented in an understandable manner.

SEND FOR A FREE LISTING  
EXPERIMENTER'S LIBRARY  
BOX 1182, LAFAYETTE, IN 47901

**NOW**

EXCLUSIVE 66 FOOT



75 THRU 10 METER DIPOLE

NO TRAPS — NO COILS — NO STUBS — NO CAPACITORS

Fully Air Tested — Thousands Already in Use



**IS BACK**

#16 40% Copper Weld wire annealed so it handles like soft Copper wire—Rated for better than full legal power AM/CW or SSB-Coaxial or Balanced 50 to 75 ohm feed line—VSWR under 1.5 to 1 at most heights—Stainless Steel hardware—Drop Proof Insulators—Terrific Performance—No coils or traps to break down or change under weather conditions—Completely Assembled ready to put up—Guaranteed 1 year—ONE DESIGN DOES IT ALL; 75-10HD—ONLY \$12.00 A BAND!

Model 75-10HD . . . \$60.00	66 Ft. . . 75 Thru 10 Meters	Model 75-40HD . . . \$40.00	66 Ft. . . 75 Thru 40 Meters
Model 75-20HD . . . \$50.00	66 Ft. . . 75 Thru 20 Meters	Model 40-20HD . . . \$33.00	35 Ft. . . 40 Thru 20 Meters
	Model 80-40HD . . . \$42.00	69 Ft. . . 80-40-15 Meter (CW)	

ORDER DIRECT OR WRITE FOR  
FULL INFORMATION




300H Shawnee  
Leavenworth, Kansas 66048

OR THRU YOUR FAVORITE  
DISTRIBUTOR



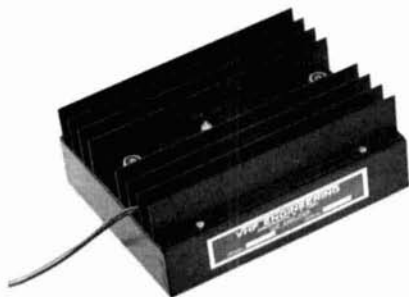
# 110 WATT POWER BOOSTER

- 110 watts PLUS with your Clegg 27
- 80 watts PLUS with your Regency



**PA 110/30**  
**\$149.95**

wired  
and  
tested

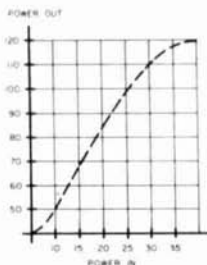

*Also Available*

**PA 110/10**

10 WATTS IN

**110 WATTS MINIMUM OUTPUT**

wired and tested — **\$179.95**

## BUILDING STUFF — ALL NEW FACTORY FRESH PARTS

### RF POWER TRANSISTORS

2N3553	2.5W	400 MHZ	\$2.10	2N6084	40W	175 MHZ	25.00
2N3866	1W	400 MHZ	1.40	CTC-B25-12	25W	175 MHZ	15.95
2N5589	3W	175 MHZ	5.75	CTC-B40-12	40W	175 MHZ	22.50
2N5590	10W	175 MHZ	9.50	CTC-C3-12	3W	470 MHZ	6.95
2N6080	3W	175 MHZ	5.95	CTC-C12-12	12W	470 MHZ	9.95
2N6081	15W	175 MHZ	12.50	CTC-C25-12	25W	470 MHZ	19.95
2N6082	25W	175 MHZ	16.50				

Underwood uncased micas 22 - 33 - 47 - 68 - 100 - 150 - 200 - 500 mmf \$1.00 each or 10 assorted your choice **\$7.50**

Mobile microphone - dynamic hi output PTT with 4 foot coiled 4 conductor cord (The same microphone used on our Marine Radio) **\$8.95**

Mica Trimmers - 403 - \$.50, 404 - \$.60, 406 - \$.75, 463 - \$.50

Ferrite Beads - \$.10 each or 12 for \$1.00 Ferrite Choke VK200.20/4B - \$.60

Molded Chokes - .15, .33, 10, 100, 82K uH **\$.70 each**

Miniature IF Transformers 455 kHz - **\$.50 each**, 10.7 MHz - **\$.65 each**.

LED — Motorola MLED 655 with plastic mounting assembly \$.60 each or 10 for \$5.00

Telephone COD orders accepted. Be sure to include enough postage.



# VHF ENGINEERING

— DIV. OF BROWNIAN ELECT. CORP. —

320 WATER ST. POB 1921 BINGHAMTON, N.Y. 13902 607-723-9574

# Mixed Doubles

Midland's all-new  
2-meter FM mobile  
transceiver has  
selective and  
simultaneous  
control of all TX  
and RX frequencies



**30 WATTS • 12 CHANNELS**

Double channel selectors for crystal controlled TX and RX frequencies in the 144-148 MHz range. Dual power transmitter delivers 30-watt or 5-watt RF output—and has automatic VSWR protection.

Double meters—Discriminator meter and S/RF/SWR meter.

Crystals are installed for 146.16, 146.34 and 146.94 TX plus 146.76 and 146.94 RX.

Built rugged in all-metal cabinet. And built to the rigid standards that have made Midland a leading name in communications. Suggested list price is \$299.95. Model 13-505

**MIDLAND**  
ELECTRONICS COMPANY

Write for FREE Midland Amateur Radio Catalog  
Dept. H, P.O. Box 19032, Kansas City, Mo. 64141

## RECEIVERS, OK GRD, WITH BOOKS:

SP-600-JX: AM, CW, 0.54-54 MHz continuous	275.00
R388/URR: AM, CW, 1/2-30 1/2 MHz linear dial, PTO	325.00
R390A/URR: 1/2-32 MHz by digits, PTO tuning	595.00
AN/FRR-59B (later version WRR-2): 2-32 MHz digital tune each 500 Hz or continuous. A1, 2, 3, 9, F1, 4. FSTTY, SSB, carrier suppressed, either band or both for 2 different intelligences. Stable and accurate enough to use as freq. meter! Net wt. 276 lbs. in 2 cabinet in rack cradle	750.00
WWVB 60 KHz rcvr/comparator	295.00
WWVB 1 KHz tones, use to calib. 100 KHz	175.00
38-1000 MHz by Band Switching, 4 bands: Separate antenna for each band. AN/ALR-5 modified for 117 v 50/60 cy line. AM/FM. The Tuner is a plug-in converter; the receiver is 30 MHz IF and all that follows IF. Choose selectivities 200 KHz or 2 MHz each side of center. Factory checkout sheet, typical for the original-pack tuner you get, says sensitivity ranges from 1.1µV at 28 MHz to 7 at 1 GHz. IF attenuator is calibrated in 6 dB steps to -74 dB. Diode current meter makes this rcvr useful for relative field strength measurements and harmonic finder. Rcvr unit is exc. used and checked out OK	375.00
30 MHz PANADAPTER may be useful with above	295.00
A.I.L. #132 30 MHz rcvr/amplifier/atten. calib.	99.50
EDDYSTONE AM/CW/FM/NBFM 19-165 MHz rcvr	295.00
CV-591A: SSB Converter either sideband	137.50
MOTOROLA 3 MHz OSCIL. 5 parts in 10 to 11th	199.50

### Attention!

**Buyers, Engineers, advanced Technicians:**

We have the best test-equipment & oscilloscope inventory in the country so ask for your needs . . . don't ask for an overall catalog . . . we also buy, so tell us what you have. Price it.

**R. E. GOODHEART CO. INC.**  
Box 1220-HR, Beverly Hills, Calif. 90213  
Phone: Area Code 213, Office 272-5707



Radio Amateurs  
Reference Library  
of Maps and Atlas

**WORLD PREFIX MAP** — Full color, 40" x 28", shows prefixes on each country . . . DX zones, time zones, cities, cross referenced tables **\$1.25**

**RADIO AMATEURS GREAT CIRCLE CHART OF THE WORLD** — from the center of the United States! Full color, 30" x 25", listing Great Circle bearings in degrees for six major U.S. cities: Boston, Washington, D. C., Miami, Seattle, San Francisco & Los Angeles. **\$1.25**

**RADIO AMATEURS MAP OF NORTH AMERICA!** Full color, 30" x 25" — includes Central America and the Caribbean to the equator, showing call areas, zone boundaries, prefixes and time zones, FCC frequency chart, plus useful information on each of the 50 United States and other Countries. **\$1.25**

**WORLD ATLAS** — Only atlas compiled for radio amateurs. Packed with world-wide information — includes 11 maps, in 4 colors with zone boundaries and country prefixes on each map. Also includes a polar projection map of the world plus a map of the Antarctica — a complete set of maps of the world. 20 pages, size 8 1/4" x 12" **\$2.50**

Complete reference library of maps — set of 4 as listed above **\$3.75**

See your favorite dealer or order direct.

Mail orders please include 50¢ per order for postage and handling.

**WRITE FOR FREE BROCHURE!** RADIO AMATEUR **callbook** INC.  
Dept. E 925 Sherwood Drive  
Lake Bluff, Ill. 60044

# POLICE CALL

## FREQUENCIES/CALL LETTERS/ AREAS OF OPERATION

- Police
- Ambulance
- Rescue Squad
- Fire
- Paramedic
- Government

1974 EDITION

- 9 Volumes now available
- Price... \$3.95 per volume plus 50 cents per volume for postage and handling. N. J. Residents please add 20 cents sales tax per volume. All mailings sent first class.
- VOLUME 1 ... Connecticut, Maine, Massachusetts, New Hampshire, New York, Rhode Island, Vermont
- VOLUME 2 ... Delaware, Maryland, New Jersey, Pennsylvania
- VOLUME 3 ... Ohio, Michigan
- VOLUME 4 ... Illinois, Indiana, Kentucky, Wisconsin
- VOLUME 5 ... Iowa, Kansas, Minnesota, Missouri, Nebraska, North Dakota, South Dakota
- VOLUME 6 ... District of Columbia, Florida, Georgia, North Carolina, South Carolina, Virginia, West Virginia
- VOLUME 7 ... Alabama, Arkansas, Louisiana, Mississippi, Oklahoma, Tennessee, Texas
- VOLUME 8 ... Arizona, Colorado, Idaho, Montana, New Mexico, Nevada, Utah, Wyoming
- VOLUME 9 ... California, Oregon, Washington

Send Money Order or Check to:  
**POLICE CALL MAGAZINE**  
LEBANON, NEW JERSEY 08833



## TRI-tek, Inc.

P.O. BOX 14206 DEPT H  
PHOENIX, ARIZONA 85063

### VOLTAGE REGULATORS

- MFC-6034... VARIABLE UP TO -20V, 200mA.....\$1.00
- MC7805, 7812, 7815, FIXED +VOLTAGE, 1A.....\$2.50
- MC7912, 7915..... FIXED -VOLTAGE, 1A.....\$2.50

### DTL INTEGRATED CIRCUITS

- 930... DUAL 4 INPUT NAND GATE.....\$ .30
- 946... QUAD 2 INPUT NAND GATE.....\$ .30
- 962... TRIPLE 3 INPUT NAND GATE.....\$ .30

### TTL ... BRAND NEW ... HOUSE NUMBERED ...

- 5N7400, 7402, 5N7410, 5N7430.....\$ .25

### TRANSISTORS

- 2N3905... HIGH SPEED PNP, HOUSE NUMBERED 5/S1
- MJE 1093... PNP DARLINGTON, 70W, 80V.....\$2.25
- JAN2222A... HIGH SPEED NPN SWITCH.....\$ .39
- MPF 120... DUAL GATE MOS FET.....\$ .75
- MFE 2000... VHF/UHF N CHANNEL JFET.....\$ .75
- MFE 2001... VHF/UHF N CHANNEL JFET.....\$ .80

### CAPACITORS

- GLASS SEAL TANTALUMS.....6V.....NEW
- .47uf, 12/51.00...4.7uf, 10/51.00, .6Buf, 8/51
- ELECTROLYTICS, COMPUTER GRADE, BRAND NEW
- 720uf/150V, \$1.25.....36,000uf/15V, \$2.25

- 12V, 1/2A TRANSFORMER.....\$1.50
- 1N3289.....200V/100A SILICON RECTIFIER.....\$10.00
- MM5314 CLOCK CHIP WITH SPECIFICATIONS.....\$9.50
- 7 SEGMENT LED READOUT, 7/10in CHARACTER...\$4.00
- RED WIDE ANGLE LED \*TOSL3.....\$ .25
- RED NARROW ANGLE HI-LUM LED \*TOSL6.....\$ .25
- GREEN HI-LUM CLEAR LENS LED \*TOSL16.....\$ .50
- SUBMINI CERAMIC TRIMMER, 3.5-13pf, PC MOUNT .70
- ALL ORDERS POSTPAID, MINIMUM \$3 U.S., \$15 FOREIGN
- LATEST LISTS, 10c STAMP.....PLEASE ADD INSURANCE

Oneida

OVER  
**150**  
APPLICATIONS  
IN EACH TUBE

**ONE DROP**

THE SPACE AGE  
MIRACLE ADHESIVE  
THAT BONDS ALMOST  
ANYTHING TO ANYTHING

INDUSTRIAL STRENGTH  
ALPHA CYANOACRYLATE

**ADHESIVE**

**JUST ONE DROP** (Tensile Strength up to 5,000lbs/in<sup>2</sup>) can take the place of bolts, nails, rivets, screws, clamps, locks, etc.

**VERSATILE** Bonds practically anything - it will help you put things together in a new, better fashion than ever before possible! glass-metal-ceramics-jewelry-rubber-plastics

## Seconds To Bond... Years To Undo!

Literally thousands of uses; Repair printed circuit boards, cabinets, install knobs, controls, all types of hardware... metal, ceramic, porcelain, glass, etc. One Drop should be in every workshop. It's ideal for repairing jewelry, appliances, sporting goods, tools and countless other items.

If unavailable in your area order direct with 30 Day Money-Back Guarantee

- 132 Drop Dispenser (2 grams) \$3.00 postpaid
- SAVE... Order two for only \$5.00
- Send check or money order - No C. O. D.'s.



Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

Note: This One-Drop formula is not recommended for use on porous materials unless it is properly filled. Request Instant-Weld 240 for use on porous materials. No. 240 sets in about 3 minutes on most materials.


Oneida

**ELECTRONIC  
MFG. INC.**

Meadville, Pa. 16335
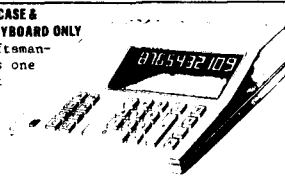
## TABLE TOP CALCULATOR CASE & KEYBOARD ONLY

Attractively designed! Excellent craftsmanship. Case and keyboard (designed as one unit). Cabinet is made of high-impact plastic beige color with black bezel and amber window. Keyboard consists of a 3-position slide switch and 25 keys, 5 of which are used for memory function. 20 keys gray, 5 keys orange. All keys mounted on one printed circuit board. This modular unit is well suited for our calculator chips. Ideal for the CT5005. Case and Keyboard Complete: ONLY \$29.95



### RECTIFIERS

VARO FULL-WAVE BRIDGES

V5447	2A	400V	\$ .90
V5647	2A	600V	1.10

MR180 Rect. 50V 1A .10

### Special 811: Hex Inverter

TTL DIP Hex Inverter; pin interchangeable with SN 7404. Parts are brand new and are branded Signetics and marked "811."

Data Sheet Supplied	EACH.....\$ .30	10 FOR..... 2.50	100 FOR..... 23.00	1000 FOR.... 220.00
---------------------	-----------------	------------------	--------------------	---------------------

### RCA NUMITRON

EACH.....\$ 5.00  
SPECIAL: 5 FOR \$20.00



### LED's

MV50 red emitting	\$ .25
10-4 ma @ 2V	5 FOR 1.00
MV5024 red TO-18	\$ .75
high dome	10 FOR 6.50
MV10B visible red	\$ .30
5-7 ma @ 2V	10 FOR 2.50

### 3-CHIP CALCULATOR

This calculator set provides all of the electronics for an 8-digit, floating point calculator with left-hand entry. Keyboard, display, clock generator, and display driver is all that need to be added to make a calculator that will add, subtract, multiply and divide. Overflow and negative signals are also provided. Complete instructions to build a calculator included.

CHIPS AND DATA.....\$8.95  
DATA ONLY (Refundable).... 1.00

### SPECIAL 874

256-BIT RANDOM ACCESS MEMORY  
TTL bi-polar fully-decoded 256 x 1 bit:

- Single 5V supply
- 80 NS access time
- Simple memory expansion thru 3-chip select lines

Data with chip. 16-Pin DIP.  
\$5.00 10 FOR \$39.95

### CT5005 CALCULATOR

This calculator chip has a full four-function memory, which is controlled by four keys, **M** (adds entry into memory), **-M** (subtracts entry from memory), **CM** (clear memory, without clearing rest of registers), **RM** (read memory or use as entry).

12-Digit display and calculate  
Fixed decimal at 0, 1, 2, 3, 4, or 5  
Leading zero suppression  
7-Segment multiplexed output  
True credit sign display  
Single 28-pin chip  
CHIP AND DATA.....ONLY \$9.95  
DATA ONLY (Refundable)..... 1.00

### 3-Amp Power Silicon Rectifiers

Marked Epoxy Axial Package

PRV	PRICE	PRV	PRICE
100.....\$ .10	800.....\$ .30		
200..... .15	1000..... .40		
400..... .18	1200..... .50		
600..... .23	1500..... .65		

### CMOS

CD4001 \$ .75	CD4023 \$ .75
CD4002 .75	74C00 .75
CD4010 1.00	74C20 .75
CD4011 .75	74C160 3.25
CD4012 .75	

### 7400 Series DIP

7400 \$ .25	74151 \$ .30
74H00 .35	74H51 .35
7401 .25	7453 .20
7402 .35	7454 .25
74H01 .35	74154 .35
7403 .30	74L55 .35
7404 .28	7460 .20
74H04 .35	74L71 .30
7405 .28	7472 .40
7406 .70	74L72 .50
74H05 .35	7473 .60
7408 .35	74L73 .75
74H08 .35	7474 .65
7410 .25	74L74 .80
74110 .35	74H74 .80
74H11 .35	7475 1.40
7413 1.25	7476 .60
7417 .40	74L78 .80
7420 .25	7480 .65
74120 .35	7483 1.00
74H20 .35	7489 4.00
74H22 .35	7490 1.20
7430 .25	7491 1.00
74H30 .35	7492 .90
74130 .40	7493 1.15
7440 .25	7494 1.15
74H40 .35	7495 1.15
7441 1.25	74L95 2.00
7442 1.20	74121 1.25
7446 1.20	74123 1.50
7447 1.20	74154 2.30
7448 1.00	74161 2.00
7450 .25	74163 2.00
74H50 .35	74193 1.50
7451 .25	74195 1.00

### 5001 CALCULATOR

40-Pin calculator chip will add, subtract, multiply, and divide. 12-Digit display and calculate. Chain calculations. True credit balance sign output. Automatic over-flow indication. Fixed decimal point at 1, 2, 3, or 4. Leading zero suppression. Complete data supplied with chip.  
CHIP AND DATA.....ONLY \$9.95  
DATA ONLY (Refundable).... 1.00

All ICs are new and fully-tested; leads are plated with gold or solder. Orders for \$5 or more will be shipped prepaid. Add 35c for handling and postage for smaller orders; residents of California add sales tax. IC orders are shipped within 2 workdays--kits are shipped within 10 days of receipt of order. \$10.00 minimum on C.O.D.s (phone in).

MAIL ORDERS:  
P. O. Box J 4811 Myrtle Ave.  
Carmichael, CA Sacramento, CA  
95608 (916) 334-2161  
MONEY BACK GUARANTEE ON ALL GOODS!  
SEND FOR FREE FLYER LISTING 100's OF MONEY-SAVING BARGAINS!



### LINEARS

NE540 70-watt power driver amp.....	\$2.00
NE555 precision timer.....	1.50
NE560 phase lock loop DIP.....	3.25
NE561 phase lock loop DIP.....	3.25
NE565 phase lock loop TO-5.....	3.25
NE566 function generator TO-5.....	4.00
NE567 tone decoder.....	4.00
NE555B dual 741 op amp MINI DIP.....	1.00
709 popular op amp DIP.....	.45
710 voltage comparator DIP.....	.75
711 dual comparator DIP.....	.40
723 precision voltage regulator DIP.....	1.00
741 op amp TO-5/MINI DIP.....	.55
747 dual 741 op amp DIP.....	1.00
748 op amp TO-5.....	1.00
CA3018 2 isolated transistors and a Darlington-connected transistor pair.....	1.00
CA3045 5 NPN transistor array.....	1.00
CA3026 dual differential amp.....	1.00
LM100 positive DC regulator TO-5.....	1.00
LM105 voltage regulator.....	1.25
LM302 op amp voltage follower TO-5.....	1.25
LM307 op amp.....	.50
LM308 op amp TO-5.....	2.00
LM311 comparator TO-5.....	1.75
LM370 AGC amplifier.....	2.00
LM701 RF-IF amp epoxy TO-5.....	.45
LM309K 5V-1A power supply module TO-3.....	2.00
LM3900 quad op amp.....	2.00
LM1595 4-quadrant multiplier.....	2.00
8038 sine square triangle function generator.....	4.95

# flea market



**WE BUY ELECTRON TUBES, diodes, transistors, integrated circuits, Semiconductors.** Astral Electronics, 150 Miller Street, Elizabeth, New Jersey 07207, (201) 354-2420.

**FINE DX LOCATION,** outstanding NW Chicago suburb (343 countries with 2-element yagi and honest kw). 4 bedrooms, 2½ baths, attached garage, modern kitchen, full basement with fireplace. City park with tennis, swimming, skating and picnic area at end of street; 2½ block walk to commuter train, shopping, library; ½ mile to grammar school and junior high. Contact W9JUV/1, Ham Radio Magazine, Greenville, NH 03048 (603) 878-1441.

**B.A.R.T.G. SPRING RTTY CONTEST:** 0200 GMT, March 23rd to 0200 GMT, March 25, 1974. Not more than 36 hours of operation is permitted. Listening counts as operating time. Off periods may not be less than 2 hours at a time. Times on and off the air must be summarized on the log and score sheets. Also open to short wave listeners. 3.5, 7.0, 14, 21 and 28 MHz Bands. Stations may only be contacted once on any band, but additional contacts may be made on other bands. Use ARRL countries list, except KL7, KH6 and VO are separate countries. Message exchange will consist of: Time GMT, message number and RST. All two-way RTTY contacts with one's country earn TWO points. All two-way RTTY contacts outside one's country earn TEN points. All stations receive a bonus of 200 points per country worked including their own. Any country may be counted again if worked on another band but continents are counted once. **SCORING:** Two way exchange points times total countries worked, plus total country points times number of continents worked. Use one log for each band and indicate any rest periods. Include date, time GMT, message and RST numbers sent and received and exchange points claimed. All logs must be received by May 31, 1974 to qualify. Send your contest logs to: Ted Double, G8CDW, 89 Linden Gardens, Enfield, Middlesex, England. EN1 4DX.

**USED MYLAR TAPES** — 1800 foot. Ten for \$8.50 postpaid. Fremerman, 4041 Central, Kansas City, Mo. 64111.

**VERY inter-est-ing!** Next 5 big issues \$1. "The Ham Trader," Sycamore IL 60178

**CALCULATOR OWNERS:** Use your +—X÷— calculator to compute square roots, cube roots, sin(X), cos(X), tan(X), arcsin(X), arccos(X), arctan(X), logarithms, exponentials, and more! Quickly, Accurately, Easily! Send today for the Improved and Expanded Edition of the first and best calculator manual — now in use throughout the world . . . only \$2.00 postpaid! Be sure to try this manual before buying a more expensive calculator — Absolutely Unconditional Money-back Guarantee — and Fast service! Mallman Optics and Electronics, Dept.-G, 836 South 113, West Allis, Wisconsin 53214.

**DAYTON HAMVENTION** expands to three days April 26, 27, 28, 1974 at HARA Arena and Exhibition Center. Brochures mailed March 15th. Write for information if you have not attended the last two years. P. O. Box 44, Dayton, Ohio 45401.

**TELETYPEWRITERS** — Kleinschmidt — portable, fixed, sets, punches, parts, reconditioned, reasonable. Mark/Space Systems, 3563 Conquista, Long Beach, Calif. 90808. 213-429-5821.

**FIGHT TVI** with the RSO Low Pass Filter. For brochure write: Taylor Communications Manufacturing Company, Box 126, Agincourt, Ontario, Canada. M1S 3B4.

**FAX PAPER:** For desk-fax, new (not surplus), precut (not rolls), \$15 per thousand sheets, postpaid worldwide. Bill Johnston, 1808 Pomona Drive, Las Cruces, New Mexico 88001.

**HOMEBREWERS:** Stamp brings list of high quality components. CPO Surplus, Box 189, Braintree, Mass. 02184.

**THE FIFTEENTH ANNUAL HAMFEST,** sponsored by the Southern Tier Amateur Radio Clubs, is scheduled for 2:00 p.m., March 30, 1974, at St. John's Ukrainian Hall, Johnson City, New York. Admission to lectures and flea market is free; awards and excellent dinner, \$6.00. For tickets or further information, write to STARC, P. O. Box 11, Endicott, N. Y. 13760. Advance ticket sales only by March 27, 1974.

■ **RATES** Commercial Ads 35¢ per word; non-commercial ads 10¢ per word payable in advance. No cash discounts or agency commissions allowed.

■ **COPY** No special layout or arrangements available. Material should be typewritten or clearly printed and must include full name and address. We reserve the right to reject unsuitable copy. **Ham Radio** can not check out each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue. Deadline is 15th of second preceding month.

■ **SEND MATERIAL TO:** Flea Market, Ham Radio, Greenville, N. H. 03048.

**1000 PIV AT 2.5 AMP DIODES.** New Motorola HEP-170. 10 for \$2.50, 100 and up 20¢ each, postpaid. K. E. Electronics, Box 1279, Tustin, California 92680.

**THE ANNUAL CUYAHOGA FALLS RADIO CLUB AUCTION** to be held Friday, February 22nd at the United Electronics Institute Building, 1225 Orlean Ave., Cuyahoga Falls, Ohio. Hours are 7 p.m. to 11 p.m. More details are available from WABZGL, Tom Carroll, Box 106, Cuyahoga Falls, Ohio 44222.

**RTTY BAUDOT LOOP TO ASCII CONVERTER** accepts loop signal at any RTTY speed and delivers corresponding 6 or 8 level parallel ASCII, all on one 4 x 6 inch circuit board for \$120. Petit Logic Systems, Box 51, Oak Harbor, Va. 98277

**THE CALGARY AMATEUR RADIO ASSOCIATION** will host an international meeting on Friday, Saturday, and Sunday, August 1, 2, and 3, 1975 — Calgary's Centennial Year. Canadian division ARRL meeting, a CLARA meeting, technical meetings, surprises, exhibits and banquet, several on-the-air contests, two days program for the ladies and for all children (3 age groups). Watch for additional information in this column, or write: 75CONVEN, Box 592, Calgary, Alberta.

**TRY US** for hard-to-get parts, transformers, devices, etc. for your project. Electronic Transformer Service, 825 Arquello Street, Redwood City, Calif. 94063.

**EMBROIDERED EMBLEMS AND PATCHES.** Custom made from your design. 10 to 1000's. Write Russell, 1109 Turner St., Auburn, Maine 04210.

**TRAVEL-PAK QSL KIT** Converts photos, post cards to QSLs! Send call and 25¢ for personal sample. Samco, Box 203H, Wynantskill, N. Y. 12198.

**BUY—SELL—TRADE.** Write for monthly mailer. Give name, address, call letters. Complete stock of major brands new and reconditioned equipment. Call us for best deals. We buy Collins, Drake, Swan, etc., SSB & FM. Associated Radio, 8012 Conser, Overland Park, Kansas 66204, 913-381-5901.

**30-140 WATTS** **NEW**

KLM Electronics  
SOLID STATE  
PA30-140B

VHF POWER AMPLIFIERS						
Frequency (MHz)	Model	Input Range (w)	Nominal P <sub>o</sub> (w)	Nominal Amps	Price	
144	PA2-12B	1 — 4	12	1.8	\$ 44.95	}
	PA10-40B	5 — 15	40	5.0	79.95	
	PA10-70B	5 — 15	70	7.0	129.95	
	PA2-70B	1 — 4	70	8.0	149.95	
	PA10-140B	5 — 15	140	18.0	179.95	
	PA30-140B	15 — 40	140	15.0	169.95	
220	PA2-140B	1 — 4	140	20.0	199.95	}
	PA10-60F	5 — 15	60	7.0	139.95	
440	PA5-25C	4 — 8	25	5.0	129.95	}
	PA2-30C	1 — 4	30	6.0	149.95	

\*Availability to be announced

Calif. residents add 5% sales tax, add \$2 per unit for p.p.d. USA prices subject to change without notice

SEND FOR FULL CATALOG ON VHF AMPLIFIERS AND HF-VHF-UHF ANTENNAS.

DEALER INQUIRIES INVITED

## LEARN RADIO CODE



### THE EASY WAY!

- No Books, To Read
- No Visual Gimmicks To Distract You
- Just Listen And Learn

Based on modern psychological techniques—This course will take you beyond 13 w.p.m. in LESS THAN HALF THE TIME! Available on magnetic tape \$9.95 — Cassette, \$10.95

**\$9.95**

Album contains three 12" LP's 2 1/2 hr. Instruction

## EPSILON [E] RECORDS

508 East Washington St., Arcola, Illinois 61910

## C F P ENTERPRISES

866 RIDGE ROAD

LANSING, N. Y. 14882

Central Upstate New York's  
Mail-Order Headquarters*Specializing in Two-Meter FM  
and Quality Used Gear*Office & Salesroom Hours by Appointment Only  
24-Hour Phone: 607-533-4297Send SASE for Bi-Monthly Listing of  
Used Equipment and Bargain Goodies

Trade-ins accepted on both new and used equipment. Cash deals get prepaid shipping in the Continental U.S.A. plus a 15% discount on used items on our regular listing!!!!



### YAESU FT-101

now with 160 meters

### SEE WILSON

for your Yaesu products

FTDX 401 Transceiver

FL2100 Linear Amplifier

FL2000B Linear Amplifier

Interested in trading Tempo One's  
and other Yaesu equipment.

## WILSON ELECTRONICS

BOX 794 HENDERSON, NEVADA, 89105  
702-451-5791

## LOW PRICES ON POPULAR COMPONENTS

### IF FILTERS

- Monolithic crystal filters at 10.7 and 16.9 MHz
- Ceramic filters at 455 kHz

### SEMICONDUCTORS

- VHF power transistors by CTC-Varian
- J and MOS FETS
- Linear ICs — AM/FM IF, Audio PA
- Bipolar — RF and AF popular types

### INDUCTORS

- Molded chokes
- Coil forms — with adjustable cores

### CAPACITORS

- Popular variable types

### QUALITY COMPONENTS

- No seconds or surplus
- Name brands — fully guaranteed
- Spec sheets on request

### GREAT PRICES

- Price breaks at low quantities
- Prices below large mail-order houses

## WRITE FOR CATALOG 173

## AMTECH

P. O. BOX 624, MARION, IOWA 52302  
(319) 377-7927 or (319) 377-2638

**CURTIS ELECTRODEVICES AND MADISON ELECTRONICS** present the finest in CW devices: EK420 CMOS deluxe keyer 139.95; KM420 CW message memory 299.95; KB4200 keyboard Morse generator 499.95; Write literature; Brown and Vibroplex paddles; postage collect. Madison Electronics, 1508 McKinney, Houston, Texas 77002. 713/224-2668; nite/weekend 713/497-5683.

**QST CQ 73** from 1923. 965 issues, \$50 plus shipping. SASE for list. W61DU, 3978 Blackwood, Newbury Park, CA 91320.

**RESISTORS:** Carbon composition brand new. All standard values stocked.  $\frac{1}{2}$ W 10% 40/\$1.00;  $\frac{1}{4}$ W 10% 30/\$1.00 — 10 resistors per value, please. Minimum order \$5.00. 15W RMS 1C Audio Amplifier — Panasonic. Frequency response 20Hz-100 kHz.  $\frac{1}{2}$ % distortion. Price \$6.95 Postpaid. Pace Electronic Products, Box 161-H, Ontario Center, New York 14520.

**HT37 \$125, SX111 \$115, w/manuals, both for \$225, plus shipping.** W61DU, 3978 Blackwood, Newbury Park, CA 91320.

**RECIPROCATING DETECTOR,** write Peter Meacham Associates, 19 Loretta Road, Waltham, Mass. 02154.

**TECH MANUALS** for govt. surplus gear, \$6.50 each: R-220/URR, R-274/FRR, R-390/URR, URM-250, URM-32, TT-63A/FGC, TS-382D/U, USM-16, BC-779B, TS-497B/URR, LM-21, TS-34A/AP, PRC-10, GRR-5, ALR-5, TS-413A/U, ARR-7, GRC-19, TS-175/U, TS-173/UR. Thousands more available. Send 50¢ (coin) for list. W31HD, 7218 Roanne Drive, Washington, D. C. 20021.

**TEFLON WIRE** #22 gauge stranded, silver plated. \$1.75/100 ft. Rich Shyer, 625-4 S. Palomares, Pomona, Ca. 91766.

**I HAVE SOME** regulated 12VDC 4 amp power supplies for \$24.95 plus postage. WA5UBQ, 119 Harmony, McComb, MS. 39648.

**QSL'S — BROWNIE W3CJI** — 3111B Lehigh, Allentown, Pa. 18103. Samples 10¢. Cut catalogue 25¢.

**KWM-2, 516F2, 312B5 NOISE BLANKER,** \$1,000.00; 75S3B, 32S3, 516F2, 312B4, 30LI, \$1,550.00; SB610, \$60.00; Clegg 22'er, \$110.00; HW 32A, \$45.00; Eico 710 GDO, \$20.00; Clegg interceptor rec., AM & SSB, 6 & 2 meter, \$175.00; Clegg Venus w/booster & A.C. supply, 6 meter SSB & AM, \$200.00; Heath SM105A 80 mc counter, \$185.00; Fairchild digital VOM, \$65.00. Certified check or money order include shipping. WB2PMF, G. J. McGranham, 808 Brook Ave., Union Beach, N. J. 07735.

**SURPLUS TEST EQUIPMENT,** VHF and microwave gear; write for bulletins. David Edsall, 2843 St. Paul, Baltimore, Md. 21218.

**OUTSTANDING RTTY MANUAL.** Teleprinter handbook. Covers everything. Beautiful hardbound volume. \$14.95 ppd from HR Books, Greenville, NH 03048.

**6939's, 6360's, Guaranteed good, \$2.50 each.** Jack W6TNR, 15718 Mayall, Sepulveda, Calif. 91340.

**DISCOUNT PRICES PLUS FULL WARRANTY,** Call or write for fast quote and delivery. All items new, guaranteed. 2M: Midland 13500 15W/12CH 219.95; SB144 199.95; SB450TRC converts 2M-3/AM 149.00; Standard 826MA 299.95; Ham-M 99.00; TR44 59.95; Belden 8-wire rotor cable 10¢/ft; AR22R 31.95; CDE parts 20%-plus off; Hygain TH6DX 143.00; TH3MK3 124.00; 204BA 129.00; 402BA 144.00; DB10/15A 96.00; Mosley Classic 33 124.00; CL36 149.00; MCQ3B quad 91.00; S402 143.00; Belden Consolidated RG8 foam coax 17¢/ft; guaranteed gear: 75S1 (clean) 345.00; SB303, filters 350.00; Tenteq 315 receiver 199.95; CushCraft A147-22 49.00; Johnson KW matchbox 219.95; Triex W51 437.00; MW50 283.00; MW65 374.00; Write: Swan, Tenteq, Drake, Kenwood, Electra Bearcat 2-band scanner 129.95; Prices FOB Houston. Free flyer. Madison Electronics, 1508 McKinney, Houston, Texas 77002. 713/224-2668; nite/weekend 713/497-5683.

**WORLD QSL** — See ad page 78.



**GREGORY ELECTRONICS**  
Reconditioned & Used  
**FM 2-WAY RADIO SAVINGS**  
Send for New Catalog

**now  
available  
New  
1974  
Catalog  
FREE...  
FM Used  
Equipment**

- GENERAL-ELECTRIC
- MOTOROLA • R.C.A.

High Band . . . Low Band  
. . . UHF Equipment  
Checked on Our Benches.  
**HEADQUARTERS FOR  
QUALITY-CERTIFIED  
USED 2-WAY MOBILE  
COMMUNICATIONS  
EQUIPMENT**



**GREGORY ELECTRONICS CORP.**  
239 Rt. 46, Saddle Brook, N. J. 07662  
Phone: (201) 489-9000



8MC. XTALS-8333-9000.  
Silk Screened Panel.  
18 Watts Output.

Price **49<sup>95</sup>**

Net to Amateurs  
Complete with Tubes  
Power Supply \$9.95

### SIX METER TRANSMITTER

for

- MOBILE
- FIXED STATION
- EMERGENCY
- AVIATION

**TUBE COMPLIMENT**  
6U8 Oscillator Multiplier  
12AX7 Speech Amplifier  
2E26 Final Amplifier  
6BQ5 Modulator



## EXCELTRONICS RESEARCH LABS

MANUFACTURERS OF ELECTRONIC DEVICES

224-15 Linden Blvd. Cambria Heights, N. Y. 11411

**LOWER PRICES**

AC1



Two models



**TIME TELLER**

DX Operating Aid

MC1

A turn of knob and 2-color drum dial shows time your QTH and corresponding local time in all zones ... also GMT. Both models feature 2-color map panel of enamel on aluminum 9" in length.

MODEL	AMATEUR NET
MC1 Unfinished mahogany cabinet	\$9.90
AC1 Polished acrylic cabinet	14.75
Add \$1.25 for mailing cost	

**U-J**

Industries

6605 Shoal Creek Blvd.  
Austin, Texas 78757

### LOOKING FOR A NEW CHALLENGE?

... then build a TV camera!



ONLY SOLIDSTATE CAMERA AVAILABLE IN KIT FORM OR FACTORY ASSEMBLED. COMPLETE KIT WITH VIDICON TUBE ONLY \$157.00. POSTPAID DELIVERY ANYWHERE IN USA, CANADA and MEXICO. OPTICAL AUDIO SUBCARRIER \$18.95. WRITE OR PHONE NOW FOR COMPLETE CATALOG OF KITS, PARTS and PLANS. DIAL 402-987-3771.

1301 BROADWAY, N.W. **ATV Research** DAKOTA CITY, NEBR. 68731



### RTTY VIDEO DISPLAY UNIT

300 CHARACTERS—ANY TV SET  
**VIDItype**  
**MODEL 872 \$550**

WRITE FOR BROCHURE

### LELAND ASSOCIATES

18704 GLASTONBURY RD.  
DETROIT, MI. 48219

### DUAL BAND ANTENNAS

These ready to mount antennas consist of full  $\frac{1}{2}$  wavelength elements of No. 12 copperweld wire and can be used as either dipoles or inverted vees. No traps, coils, gimmicks, etc. are used to shorten the elements, 2KW rating. Single coax feedline required. Individually mounted dipoles with common center insulator: 80/40, \$21.95; 40/20, \$16.25; 20/15, \$14.10. Other combinations available. Send for free catalog listing dual band, monoband, and folded-dipole antennas. Baluns available. Postpaid continental U. S. A.

### HOUSE OF DIPOLES

P. O. BOX 8484  
ORLANDO, FLORIDA 32806

WE PAY **HIGHEST**  
PRICES FOR ELECTRON  
TUBES AND SEMICONDUCTORS

## H & L ASSOCIATES

ELIZABETHPORT INDUSTRIAL PARK  
ELIZABETH, NEW JERSEY 07206  
(201) 351-4200

### THE ULTRA-BAL 2000

NOW ----- An extremely rugged, weather-proof BALUN!

- Full 2KW, 3-30 MHZ., 1:1 or 1:4 ratios.
- Special Teflon insulation. May be used with tuned lines and tuners.
- With dipole insulator and hang-up hook.



ONLY \$9.95ppd. (state ratio)

At your dealer or order direct

**K.E. Electronics** Box 1279, Tustin Calif. 92680

# QRP

A Challenge of Skill & Determination

# THE MILLIWATT

THE ONLY MAGAZINE DEVOTED ENTIRELY TO UNDER-FIVE WATT HAM RADIO

- Construction Projects
- Technical Articles
- Operating News
- QRPp WAS & DXCC Standings
- Awards: QRPp DXCC, MILLIWATT DXCC, FIELD DAY TROPHY

Subscriptions \$3.75 yearly Reprints Vol 1 \$4.00. II, III, IV - \$3.50 each (All four - \$13.40) SAMPLE 50¢ TO: ADE WEISS KREEG, 213 Forest, Vermillion, SD 57069.



**DO-IT-URSELF EXPEDITION** — Stay at ZFISB — Cayman Is. Vertical antenna and Caribbean at your doorstep. Diving/fishing if band folds. We arrange license. Write Spanish Bay Reef Resort, Box 800K, Grand Cayman, B. W. I.

**NEED PARTS?** We carry parts for R-388-390-390A-391-392-1051-51S1 - Nems Clark-Racal-Pack sets - PRC-25-41-47-62-70-71-73-74-77. If you need a part no matter what you have. If its U.S. government we have it or can get it. Also we want to buy or trade all aircraft communications. All ground radio communications. All plug-in modules control heads. No matter what cond. they are in - bent or busted ok. We will buy or trade. We have R-390-388-390A-392-1051-51S1 Nems Clark - Racal - and new ham gear for trade. D & R Electronics, R. D. #1, Box 56, Milton, Pa. 17847. Phone 1-717-742-4604 after 6:00 P.M.

**TELETYPEWRITER PARTS**, gears, manuals, supplies, tape, toroids, SASE list, Typetronics, Box 8873, Ft. Lauderdale, Fl. 33310. Buy parts, late machines.

**QSLs**. Second to none. Same day service. Samples 25¢. Ray, K7HLR, Box 331, Clearfield, Utah 84015.

**PRECISION HAND TOOLS**, special ham-experimenter discount. Letter brings mailings. Artisan Tool Company, Box 36, Glenmont, New York 12077.

**MAGNUM SIX** for Heath SB-401, \$100.00 postpaid. K9HJU, 312-349-9002.

**WANT OLD RADIO SHOW TRANSCRIPTION** discs. Any size or speed. Send details to, Larry Kiner, W7FIZ, 7554 132nd Ave. N.E., Kirkland, Wa. 98033.

**FOR SALE:** TA33 beam with TA40KR conversion — beam in very new condition with slightly bent director element, TA40KR is brand new, \$150; Boonton radio model 202B FM signal generator, \$145; general radio bolometer bridge mode 1651A, \$150; R. C. A. distortion and noise meter for 600Ω system, \$125; Spectrum analyzer TS-148/UP 8430-9600 MHz, \$35; Lambda power supply model 50, 0-500 VDC, adjustable @ 500 ma, 2-6.3 V @ 5A, 0-50 & 0-200 VDC adjustable bias, \$150; General Radio 720-A heterodyde frequency meter 10-3000 MHz with built in power supply, \$150; Western Electric frequency meter model 1-183-A, \$75; Zenith frequency meter BC-221T, \$40; 1500 Sprague difilm metallized capacitors .082 uF @ 200 VDC, #188P82392S4, \$2.90 list ea., my price \$5.00 ea. 1004 - 5 to 20pf Erie trimmer capacitors CVIIB200 temperature coef. N300, \$1.43 list price, my price \$.25 ea.; 150 Allen Bradley HB-2 watt 30k 5% resistors - make offer, 235 - 8 prong octal saddle socket (cinch) \$.80 ea. Richard Mayer, 3131 Decatur Ave., Bronx, N. Y. 10467.

**CANADIAN JUMBO SURPLUS** and Parts Catalogs. Bargains Galore. Send \$1. ETCO-HR, Box 741, Montreal "A" H3c 2V2.

**KLM AND MADISON ELECTRONICS** present the finest in VHF antennas. 144-148MHz, 7EL to 16EL; 9EL 31.95; 14EL 45.95; 16EL 49.95; 420-450 MHz, 14EL 19.95; 27EL 41.95; Write for literature. Freight collect. Madison Electronics, 1508 McKinney, Houston, Texas 77002. 713/224-2668, nite/weekend 713/497-5683.

**WANTED:** tubes, transistors, equipment, what have you? Bernard Goldstein, W2MNP, Box 257, Canal Station, New York, N. Y. 10013.

**FREE:** 18 crystals of your choice with the purchase of a new Genave GTX-200 at \$259.95. Send cashier's check or money order for same-day shipment. For equally good deals on Drake, Swan, Standard, Clegg, Regency, Hallicrafters, Tempo, Kenwood, Midland, Ten-Tec, Galaxy, Hy-Gain, CushCraft, Mosley, Sony, and Hustler, write to Hoosier Electronics, your ham headquarters in the heart of the Midwest. Become one of our many happy and satisfied customers. Write or call today for our low quote and try our individual, personal service. Hoosier Electronics, R. R. 25, Box 403, Terre Haute, Indiana 47802. (812)-894-2397.

**QSLs CATALOG SAMPLES** 35¢. Ritz Print Shop, 5810 Detroit Avenue, Cleveland, Ohio 44102.

**TELL YOUR FRIENDS** about Ham Radio Magazine.

## L. I. Electronic Supermart (Off the wall self service)

**New P.C. Boards** — G10, 1 oz. - 1 side copper-fiber glass  
6" x 6", 80¢ ea. — 6 x 12, \$1.50 ea. - 12 x 12, \$2.85 ea.

**New P.C. Boards** — G10, 1 oz. - 2 side copper-fiber glass  
6" x 6", \$1.10 ea. - 6 x 12, \$2.00 ea. - 12 x 12, \$3.75 ea.

**New P.C. Boards** — G10, Fiber glass punch:  
F Pattern 4.5 x 6.5, .062 holes, 5 per 1" \$1.30  
P Pattern 4.5 x 6.5, .042 holes, 10 per 1" \$1.35  
G Pattern, 4.5 x 6.5, .062 holes, \$1.30  
Pkg. 10 Bircher P.C. Board, metal 2" slides \$1.00  
Package of 50 flea clips for above punched Boards, .062 ..... 75¢  
30 ¼ or ½ W resistors, packaged 5 per value your choice of values ..... \$1.00  
25-1W resistors, packaged 5 per value, your choice of values ..... \$1.00  
15-2W resistors, packaged 5 per value, your choice of values ..... \$1.00  
5 ¼ or ½ W, 1% resistors, packaged 5 per value, your choice of values ..... .50  
5 ceramic disk caps, .001-01, packaged 5 per value, your choice of values ..... .50  
5 mica dip caps, 1 pf-150 pf, packaged 5 per value, your choice of values ..... .50  
5 mica dip caps, 180 pf-820 pf, packaged 5 per value, your choice of values ..... .75  
5 mica dip caps, 910 pf-1500 pf, packaged 5 per value, your choice of values ..... \$1.00  
Wire Kit #22 solid PVC, 6 spools, 6 colors, 50' ea. spool ..... \$3.50  
Wire Kit #22 stranded PVC, 6 spools, 6 colors, 50' ea. spool ..... \$3.50  
Wire Kit #24 Solid PVC, 6 spools, 6 colors, 50' ea. spool ..... \$3.50  
Wire Kit #24 stranded PVC, 6 spools, 6 colors, 50' ea. spool ..... \$3.50  
10' — Ten cond. ribbon wire, color coded, #22 or #24, stranded ..... \$1.50  
C & K #7101 mini switch, SPDT on-on ..... \$1.05  
C & K #7103 mini switch, SPDT on-off-on ..... \$1.20  
C & K #7201 mini switch, DPDT on-on ..... \$1.35  
C & K #7203 mini switch, DPDT on-off-on ..... \$1.55  
Alco 105D MST momentary on-off-momentary on ..... \$1.25

Central Lab DPDT push momentary. SPEC. 4/ \$1.00  
Connectors, PL259, \$.45; PL258, \$.70; 175U or 176U, \$.20 ea.; UG 88 cu., \$.50; UG 201 a/u (N to BNC adapter), \$.75; RCA to UHF, \$.90  
Encapsulated chokes 1uh to 5 Mh, choice 3/ \$1.00  
Varo type mini bridge rectifiers, approx. ½" sq. size: 2 amp. - 50 v., \$1.25; 4 amp. - 50 v., \$1.25; 6 amp. - 50 v., \$1.25; 2 amp. - 100 v., \$1.25; 4 amp. - 100 v., \$1.25; 6 amp. - 100 v., \$1.25; 2 amp. - 200 v., \$1.50; 4 amp. - 200 v., \$1.50; 6 amp. - 200 v., \$1.50; 2 amp. - 400 v., \$1.50; 4 amp. - 400 v., \$1.50; 6 amp. - 400 v., \$1.50  
Triacs — thermo tab package — 1 amp. - 400 v., \$.80 ea.; 3 amp. - 400 v., \$1.40 ea.; 4 amp. - 200 v., \$1.20 ea.; 6 amp. - 200 v., \$1.40 ea.; 6 amp. - 400 v., \$1.60 ea.; 6 amp. - 500 v., \$1.80 ea.; 8 amp. - 200 v., \$1.60 ea.; 8 amp. - 500 v., \$1.80 ea.  
To-5 case, 1 amp. - 200 v., \$.70 ea.; 1 amp. - 400 v., \$1.00 ea.  
SCR 200 v. - 8 amp. thermo tab ..... \$ .80 ea.

**SEND SELF ADDRESSED ENVELOPE FOR FREE MAILER. INCLUDES MANY HUNDREDS OF ITEMS NOT LISTED ABOVE.**

Send check or money order - include 60¢ to cover parcel post and handling. UPS shipping available. Minimum order \$4.50.

**FREE BONUS WITH EACH \$10.00 ORDER**  
50' SPOOL 600 V. #22 PVC WIRE

**KRP**  
**ELECTRONIC SUPERMART, INC.**  
219 WEST SUNRISE HIGHWAY  
FREEPORT, L. I., N. Y. 11520  
516-623-3346-9

# FREE CATALOG

CRAMMED WITH GOV'T SURPLUS  
ELECTRONIC GEAR **WRITE TODAY!**



## BC-348 RADIO RECEIVER

200-500 Kc & 1.5 18 Mc. 8-Tube  
6-Band Communications Receiver, Excellent  
Used, with tubes and Dynamotor  
Checked out..... **\$58.50**

## BRAND NEW BC-645 TRANSCIVER

EASILY CONVERTED FOR  
420MC OPERATION

This equipment originally  
cost over \$1000. You get  
all in original factory carton.



Dependable Two Way Communication more than 15 miles.

- FREQUENCY RANGE: About 435 to 500 Megacycles.
- TRANSMITTER has 4 tubes: 2E5, 2E6, 2E7, 2E8.
- RECEIVER has 11 tubes: 2-955, 4-7H7, 2-7E6, 3-7F7.
- RECEIVER I. F.: 40 Megacycles.
- SIZE: 10 1/2" x 13 1/2" x 4 1/2".

Makes wonderful mobile or fixed rig for 420 to 500 Mc.  
Easily converted for phone or CW operation

### "SPECIAL PACKAGE OFFER"

BC-645 Transceiver, Dynamotor and all accessories below, including conversion instructions for Citizens Band. **BRAND NEW, while stocks last. \$26.95**

F.O.B. NY City or Ogden, UT for Savings on Freight Charges.

Accessories for BC-645 transceiver  
PE-101C Dynamotor, 12-24 V (easily converted to 6 volts).  
Mounting for PE-101C Dynamotor.  
**TRANSCIVER ONLY..... \$15.95**

motor  
UHF Antenna assemblies (set of 2)  
Complete set of 11 connectors  
Control Box BC-645  
Mounting for BC-645 ctr. box.

## G&G RADIO ELECTRONICS COMPANY

45-47 Warren St. (Dept. H-F) New York, N.Y. 10007 212-267-4605

TERMS: F.O.B. NYC 25% deposit with order, balance COD or remittance in full. MINIMUM ORDER \$5.00. Subject to prior sale and price change.

## NEW - 440 MHz PREAMPS

**\$54.95**

POSTPAID  
432PA-1



Two stage preamps use KMC Bipolar and Mosfet Transistors. 20db gain, 20 MHz bandwidth. These are high quality preamps suitable for the most demanding applications. AC models have die cast case, others have metal enclosure.

432PA 3.5db NF 12VDC	\$29.95
432PA-1 3.5db NF 117VAC	\$54.95
432PC 1.5 to 2.0db NF 12VDC	\$69.95
432PC-1 1.5 to 2.0db NF 117VAC	\$94.95

**JANEL LABORATORIES**

P. O. BOX 112  
SUCCASUNNA, N. J. 07876  
201-584-6521

## SPACE SAVER TOWERS & MASTS

CZ series towers, cranks up, installs without guy wires. New lacing design creates greater strength.


Mini and Magna rotating masts . . . high strength galvanized tubing, self supporting crank-up.

For complete details and prices please check your local dealer or write

Certified Welders L.A. City License #634

**TRISTAO TOWER CO.**

P.O. Box 115, Hanford, California 93230

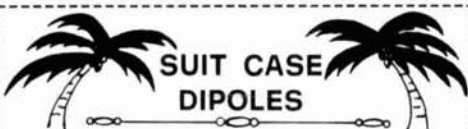

## SUIT CASE DIPOLES

- #16 stranded copper wire
- Insulated for cleaner, easy handling
- Pretuned and tested guaranteed resonance
- Available 80 thru 10 meters amateur radio bands
- Clips included for portable use allowing same coax to be used for different antennas (small coax only)

C110 - \$6.95 C115 - \$7.95 C120 - \$9.95  
C140 - \$12.95 C180 - \$17.95

RG-58/U & RG-59/U available at \$12.95 per 100 feet.  
Information available or order direct

## CATRONICS INTERNATIONAL

P. O. BOX 132 • MIAMI, FLORIDA 33156

## THE ULTIMATE MORSE KEYBOARD

- 64 character buffer
- Standard typewriter format with space
- Compatible with KM-420 memory

Available 1 November Model #KB-4200  
Write for specifications \$499.95

**GURTS ELECTRO DEVICES** BOX 4090 • MOUNTAIN VIEW, CALIF. 94040 • TEL. (415) 964-3136



KM-420 CW MESSAGE MEMORY 100 OR 200 CHARACTERS \$299.95 Write for brochures  
EK-420 CW MESSAGE MEMORY 100 OR 200 CHARACTERS \$199.95 Write for brochures

**GURTS ELECTRO DEVICES** TEL. (415) 964-3136 NEW FOR 1973  
INC. BOX 4090, MOUNTAIN VIEW, CA. 94040

## WANTS TO BUY

All types of military electronics equipment and parts. Call collect for cash offer.

### SPACE ELECTRONICS division of MILITARY ELECTRONICS CORP.

76 Brookside Drive, Upper Saddle River  
New Jersey 07458 • (201) 327-7640

AK-1 BOARD ONLY	\$ 3.25
AK-1 KIT OF ELECTRONIC PARTS	\$ 20.00
ST-5 BOARDS ONLY	\$ 5.25
ST-5 KIT OF ELECTRONIC PARTS	\$ 47.50
ST-5A BOARDS ONLY	\$ 5.25
ST-5A KIT OF ELECTRONIC PARTS	\$ 54.00
ST-6 BOARDS ONLY (These are the 8 original by W6FFC)	\$ 18.00
ST-6 KIT OF ELECTRONIC PARTS	\$128.50
MOD. KIT FOR UPDATING THE ST-5 TO THE ST5A	\$ 9.00
PEMCO 250 EIGHT DIGIT COUNTER WITH BUILT-IN PRE-SCALER AND POWER SUPPLY SEMI KIT	\$165.00
PEMCO MODEL 50A FREQUENCY COUNTER SEMI-KIT	\$125.00

These are fully assembled and tested boards only, you add your own cabinet, etc. Write for details.

You must supply the cabinet, A.C. cord, meter, switches, etc. on all kits except where noted otherwise. (All prices are postage paid (we pay shipping).)

We will do most any printed circuit board for individuals or prototypes. If required we will also do the layout of the boards. All our boards are G-10 glass-epoxy solder plated and come drilled only. At present time we can do only single sided. All component parts used in our kits are new manufacturers stock. We Do Not Use Any Used or Surplus Parts. All inquiries are answered promptly.

## PEMCO ELECTRONICS MANUFACTURING

422 18th St., N.E., Salem, Ore. 97301, (503) 585-1262

**PARTS BARGAIN:** Motorola HEP170 epoxy diode 2.5A/1000PIV 29¢; 25.00/100-lot; 6 x 9 copper clad board 69¢, 3/2.00; #15 copper antenna wire 1.95/C; 3/16" cable clamps 18¢; Belden, Consolidated RG8 foam coax 17¢/ft; CDE .001/10KV doorknob cap 1.95; Sigma 12VDC 4PDT/15A relay 3.95; Amidon ferrite cores in stock; RG63/U 15¢/ft; RG22B/U 15¢/ft; Motorola Semi-conductor Data Series 7.50; Monarch code module 1.50; Hammarlund variable cap 50PF 1.95; Sorensen ACR2000VA AC regulator 150.00. Madison Electronics, 1508 McKinney, Houston, Texas 77002. 713/224-2668; nite/weekend 713/497-5683.

**KW LINEAR** Johnson Viking Thunderbolt & manual. i250. SX101 Mk2A 100 kHz calb. \$90. PME 502P. i03P 2 & 6 preamps unused, each with two 6CW4 iuvistors, \$14. Vibro keyer, \$20. B & W 851 P;Net new \$14. Collins 4 kHz filter for R390, \$20. Galaxy 100 power supply, \$25. 3-touchtone pads, \$10 each. Model 19 complete, \$135. Model 28KSR excellent with 60 and 100 wpm gears, \$295. Model 28 or 35 live or eight level answer back, new, \$50. Moving. First M.O. YOU pay shipping. Send S.A.S.E. for list. Miranda "G" SLR Camera & Kako Strobe, \$100. (4AVQ/3, AL, 20 Lepore Drive Lancaster, Pa. 17602. Call after 4 p.m. EST, 1-717-392-4237.

**STANDARD 146-A** still in factory carton with warranty card. \$238.70. W40AQ, Box 17222, Nashville, Tenn. 37217, (615-834-8999).

**GALAXY R-530 RECEIVER.** Mint. Tunes 500KC thru 30 MC continuously. AM, CW, RTTY, SSB. Has .5, 2.1 and 6KC filters. Noise blanker. Picture in most current ham magazines. \$495 firm, you ship. Bryan Davidson, Box 119, Salem, Illinois 62881. (618) i48-2188.

**300 NEWS** — SRRC Hamfest June 2, 1974 at fabulous new site in Princeton Illinois Fairgrounds. SRRC-W9MKS, R.F.D. #1, Box 171, Oglesby, Illinois 61348.

**TS-382D/U AUDIO SIGNAL GENERATOR.** 20 Hz to 200 kHz in 4 bands. 0-10 volt calibrated output. Works good, \$50.00. W6LKV, Box 503, Burney, CA. 96013.

**MOBILE IGNITION SHIELDING** provides more range with no noise. Available most engines in assembled or kit forms, plus many other suppression accessories. Free literature. Estes Engineering, i43-H West 184th, Gardena, California 90248.

**COLLINS FOR SALE:** Complete S-Line purchased new Dec. 72. Very, very mint condx: 75S-3C, 32S-IA, 516F-2, 312B-4, 30L-1, SM-3 mic. Rec. includes i00 Hz filter & MARS xtals — Cost today over i4,000. Will sell complete package for \$2,950.00. R. O. Lions, K6ZGW/7, 326 Morris Ave. So., Reno, Wa. 98055.

**TREASURE COAST HAMFEST,** March 9-10 — sponsors, Vero Beach Amateur Radio Club, Inc. and i. Lucie Repeater Association, Community Center, iero Beach, Fla. 32960. Free continental breakfast — first prize 80-10 transceiver. Dozens of thers. Speaker. Swappers row. Tickets and information, write: Ike Roach, K4QM, Box 3088, Vero Beach, Fla. 32960.

**-1000A, 4X500A** with chimney, \$50 each. 6688, i922, \$2 each. All like new, postpaid. WA9SPA, i253 S. Luna, Chicago, IL. 60638.

**SIGNAL ONE OWNERS,** expert and prompt service by ex-Signal/One engineer. Also will purchase your unctioining or not functioning unit or spare parts. Write or call for details. Larry Pace, K2IXP/7, 1071 V. Roller Coaster, Tucson, AZ. 85704 (602-888-5234).

**WANTED FM 2M U43HHT, U53HHT, U63HHT, CM-2A30, CMCA60.** Send quote. WB4EGW, 600 East Concord Street, Morganton, N. C. 28655.

**C.'s Need a project for winter?** Send a SASE for list of available boards. Semtronics, Charles R. iempirek, Route #3, Box 1, Bellaire, Ohio 43906.

**VESTINGHOUSE IC's FOR SALE:** Many digital, some iinear; flat pack, DIP, TO-5 cases. 6F, 6G, WC series ind others. SASE for list. Chris Fadden, 526 Kaplock St., Bronx, N. Y. 10463. (212) 796-9514 eves.

## World's Most Advanced STATE-OF-THE-ART TRANSCEIVER



THE TRITON by TEN-TEC

## TOTAL SOLID STATE HF TRANSCEIVER



Available ANYWHERE IN THE WORLD directly from


**ELECTRONIC DISTRIBUTORS, INC.**

—Communication Specialists for over 35 years—

1960 Peck St., Muskegon, Michigan 49441

Tel. (616) 726-3196

Telex 228-411

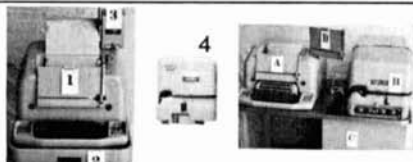

## BARGAINS!

KLEINSCHMIDT TELETYPE EQUIPMENT

- |   |         |
|---|---------|
| (1) TT-100 PAGE PRINTER AS IS 60 OR 100 WPM             | \$59.95 |
| (A) TT-117 PAGE PR OR (B) TT-179 REPERF. & TD, AS IS    | \$59.95 |
| ABOVE CHECKED OUT, OILED & ADJUSTED. EA                 | \$89.95 |
| (2) TABLE \$19.95 (C) TABLE \$34.95 (D) COPYHOLDER      | \$3.95  |
| (3) PAPERWINDER \$14.95 (4) TT-107 REPERF. ONLY         | \$49.95 |
| TH-5 CONVERTER TRANS/REC 100 CYCLES ADJUST TO 170 SHIFT | \$49.95 |

**Andy Electronics Co., Inc.**

6431 Springer Street / Houston, Texas 77017

ALL PRICES FOB HOUSTON, TEX.

## GROTH-Type

### COUNTS & DISPLAYS YOUR TURNS



- 99.99 Turns
- One Hole Panel Mount
- Handy Logging Area
- Spinner Handle Available

**PRICES** POST PAID  
TC 2 — \$7.00  
TC 3 — \$7.50  
Spinner (S) — \$1.00  
Add \$0.75 for Air or UPS

Case: 2x4"; shaft 1/4"x3"  
Model TC2: Skirt 2 1/8"; Knob 1 1/2"  
Model TC3: Skirt 3"; Knob 2 3/8"

**R. H. BAUMAN SALES**

P.O. Box 122, Itasca, Ill. 60143

# INTERNATIONAL ELECTRONICS UNLIMITED

## TTL

7400	\$ 25	7446	\$1 45	74121	\$ 85
7401	25	7447	1 45	74122	55
7402	25	7448	50	74123	1 15
7403	25	7449	29	74126	95
7404	29	7451	32	74145	1 25
7405	27	7453	32	74150	
7506	55	7454	45	74151	1 05
7407	53	7455	32	74153	1 45
7408	29	7460	30	74154	1 75
7409	29	7461	30	74155	1 35
7410	25	7464	45	74156	1 50
7411	35	7465	45	74157	1 50
7413	95	7470	50	74161	1 85
7415	50	7472	45	74165	2 00
7416	50	7473	55	74164	2 95
7417	50	7474	55	74165	2 95
7420	25	7475	95	74166	1 95
7421	32	7476	55	74173	1 95
7422	37	7478	85	74175	1 95
7423	37	7483	35	74176	95
7425	39	7485	20	74177	95
7426	35	7476	45	74180	1 95
7427	39	7489	25	74181	4 25
7430	25	7490	25	74182	1 10
7432	30	7491	40	74190	
7437	50	7492	1 05	74192	1 65
7438	55	7493	1 05	74193	1 65
7440	25	7494	1 10	74194	1 65
7441	25	7495	1 05	74195	1 15
7442	1 15	7496	1 05	74196	1 85
7443	1 25	74100	1 65	74197	1 15
7444	1 30	74106	55	74198	1 10
7445	1 25	74107	55	74199	2 50

Low Power TTL

74100	\$ 40	74142	\$1 75	74185	\$1 25
74102	40	74145	1 45	74186	95
74103	40	74151	40	74190	1 75
74104	40	74154	60	74191	1 75
74106	40	74172	60	74193	1 75
74110	40	74173	80	74194	1 75
74120	40	74174	80	74195	1 75
74130	40	74178	80		

8000 Series TTL

8054	\$ 45	8123	\$1 75	8570	\$2 95
8050	30	8122	1 15	8600	1 15
8091	69	8714	1 95	8610	95
8092	69	8720	2 95	8612	1 25
8093	69	8780	95	8622	2 95
8094	69	8788	1 05	8830	69
8122	1 05	8570	1 45	8831	2 95

### ALL DIP PKGS.

Specify spec. sheets required with order. Add \$ .50 per spec sheet for items less than \$1.00 ea.

## Linear

LM 300	Pc. V Reg (super 723)	TO 5	\$ .85 ea
LM 301	3 Voltage AMP/L	TO 5 or MINI DIP	46 ea
LM 302	Voltage Follower	TO 5	95 ea
LM 304	Negative Voltage Regulator	TO 5	1 25 ea
LM 305	Positive Voltage Regulator	TO 5	1 25 ea
LM 307	Op AMP (super 741)	TO 5 or MINI DIP	46 ea
LM 308	Macro Power Op Amp	TO 5 or MINI DIP	1 25 ea
LM 309H	5 V Regulator	TO 5	1 25 ea
LM 309E	5 V Regulator	TO 3	1 95 ea
LM 310	Voltage Follower Op Amp	TO 5	1 45 ea
LM 311	Hi perf. Voltage Comparator	TO 5 or MINI DIP	1 25 ea
LM 319	Hi Speed Dual Comparator	DIP	1 85 ea
LM 320	5.2 V Negative Regulator	TO 3	1 95 ea
LM 320	12 V Negative Regulator	TO 3	1 95 ea
LM 320	15 V Negative Regulator	TO 3	1 95 ea
LM 3401	Positive Voltage Regulator (BV, BV, 15V or 24V)	TO 220	2 25 ea
LM 370	ADC/Squarer	TO 5 or DIP	1 25 ea
LM 372	AT IF Strip-detector	DIP	85 ea
LM 373	AM/FM/SS Strip	DIP	3 60 ea
LM 376	Pos Volt Regulator	MINI DIP	65 ea
LM 380	2 Watt Audio Regulator	DIP	1 75 ea
LM 382	Low Noise Dual Pn-Amp	DIP	2 25 ea
LM 560	Precision Voltage Regulator	DIP	55 ea
LM 709	Operational AMP/L	TO 5 or DIP	39 ea
LM 711	Dual Differential Comparator	DIP	39 ea
LM 723	Voltage Regulator	DIP	75 ea
LM 739	Dual Hi Performance Op AMP	DIP	1 25 ea
LM 741	Comp. Op AMP	TO 5 or MINI DIP	46 ea
LM 747	Dual 741 Op AMP	TO 5 or DIP	50 ea
LM 7900	Quad Amplifier	DIP	50 ea
LM 7905	Precision Timer	MINI DIP	49 ea
LM 9001	Retrievable One Shot	DIP	75 ea
LM 75451	Dual Peripheral Driver	MINI DIP	49 ea
LM 75452	Dual Peripheral Driver (LM 7511 Dual Peripheral Driver)	MINI DIP	49 ea

Specify TO 5, DIP or MINI DIP Package. Specify Spec. Sheet Required with order. Add \$ .50 per spec sheet for items less than \$1.00 ea.

## Phase Locked Loops

NE 560	Phase Locked Loop	DIP	\$2 95 ea
NE 561	Phase Locked Loop	DIP	2 95 ea
NE 562	Phase Locked Loop	DIP	2 95 ea
NE 565	Phase Locked Loop	DIP	2 95 ea
NE 586	F Function Generator	MINI DIP OR TO 5	49 ea
NE 587	Tone Decoder	MINI DIP OR TO 5	2 95 ea

Specify TO 5, Dip or Mini Dip Package

## FEBRUARY SPECIALS

MM 7400	Quad two input NAND gate	\$ .80 ea
SN 74163	Up/down Binary Counter	1 29 ea
MM 1101	256 Bit static random access memory	2 00 ea
LM 385K	Similar to LM 309K except input voltage limited to 20 V - no current limiting - while they last!	1 35 ea
LM 730	Hi performance operational amplifier DIP	1 18 ea
LM 741	Hi performance operational amplifier	5 for 2 00
MV 100	Visible red led TO 18 Infra red (invisible) diff. dome TO 18	100 for \$15.86
MV5020	Amber clear dome visible red	100 for \$18.96

### MM5313 CLOCK CHIP WITH LED's

28 pin any readout 8 digit IPS BCD with 8 Match 2m LED's Complete with Drive ..... \$17.50/hat

### FLAT PACK GRAB BAG

7400 Series - Assorted generation 1cm. Spac. Full Out Efficiency good ..... 25 for \$1.85

## 4000 Series RCA Equivalent

CD 4001	\$ .88	CD 4012	\$ .88	CD 4033	\$ .85
CD 4002	88	CD 4013	1 90	CD 4038	85
CD 4008	1 00	CD 4016	1 50	CD 4027	1 35
CD 4010	88	CD 4017	2 96	CD 4030	88
CD 4011	88	CD 4019	1 28	CD 4036	2 98

## CMOS

74C00	\$ .88	74C76	\$1 70	74C182	\$3 38
74C02	88	74C107	1 50	74C183	3 28
74C04	95	74C165	2 90	74C186	2 80
74C10	85	74C154	3 50	74C173	2 80
74C20	88	74C187	2 28	74C187	3 30
74C42	2 18	74C180	3 30	74C188	3 00
74C73	1 70	74C181	3 28	80C87	1 90
74C74	1 80				

## Memories

1101	288 bit RAM MOS (2501)	\$2 50 ea.
1103	1024 bit RAM MOS	7 95 ea.
1488	84 bit RAM TTL Programmable ROM	3 25 ea.
8223		6 95 ea.

### \* NEW ITEM \*

MM 5280 1024 bit RAM Second generation version of 1103. Featuring 16 pin DIP rather than 18 pin. 30% less power consumption. Introductory Price ..... 9 95 ea.

## Digital clock ... on a Chip

MM 5311 (28 pin)	Any readout 6 digit BCD with spec sheet	\$11.95 ea
MM 5312 (24 pin)	Any readout 4 digit BCD with spec sheet	6 95 ea
MM 5313 (28 pin)	Any readout 6 digit BCD with spec sheet	10 95 ea
MM 5314 (24 pin)	LED readout readout 6 digit with spec sheet	10 95 ea
MM 5316 (40 pin)	Normal alarm, snooze alarm, sleep timer 12 or 24 hr operation with spec sheet	15 95 ea

## MOS

MM1404	1024 bit dynamic shift register	\$2 25 ea.
MM4513	1024 bit dynamic shift Register/Accumulator	2 25 ea
MM4520	2560 bit static character generator	4 95 ea
MM5241	3072 bit static read-only memory	7 95 ea

## Untested IC's

UNTESTED MOS

MM1403	1024 bit dynamic shift register	DIP	85 ea
MM1408	1024 bit dynamic shift register	DIP	85 ea
MM5013	1024 bit dynamic shift register/accumulator	DIP	TO 6 55 ea
MM5016	512 bit dynamic shift register	DIP	TO 6 25 ea
MM5019	Dual 256 bit mask prog. shift register	TO 5	25 ea
MM5054	Dual 32 bit static shift register	TO 5	35 ea
MM5054	Dual 64 bit static shift register	TO 5	35 ea

MOS Shift Registers 2500 Series  
2502 2506 2508 2510 2511 2518 2519 2521 2522  
Untested series  
Grab Bag Specials!  
15 Assorted TTL's (dip) ..... \$1.00/bag  
28 Assorted TTL's (dip) ..... \$1.00/bag

## Opto Isolators

MCA 2 30	Darlington Diodes	\$ .80 ea
MCT 2	Transistor	1 45 ea

## ON ORDERS OVER \$25.00 DEDUCT 10%

Satisfaction guaranteed. All items except as noted are fully tested. Minimum order \$5.00 prepaid in U.S. and Canada. Calif. residents add sales tax. Orders filled within three days from receipt.

INTERNATIONAL ELECTRONICS UNLIMITED  
P.O. BOX 1708R  
Monterey, Calif. 93940

QSL's, Sample catalog 20¢. N & S Print, P. O. Box 11184, Phoenix, Ariz. 85061.

LEDS, sample pack of 10, includes green and yellow, \$3.25 postpaid U.S.A. East Coast Electronics, 50 Scott St., Hamburg, N. Y. 14075.

432 MHz TRANSMITTER CONVERTER, 5 watts out, 6933 mixer, 6939 amplifier and solid state LO chain. 4½ x 7½ cast aluminum box. Send for more information. Carmichael Communications, P. O. Box 256, Carmichael, CA 95608.

MOTOROLA PORTABLES — Expert repairs, reasonable prices, fast turn-around time. More details and flat rate catalog FREE. Ideal Services, 6663 Industrial Loop, Greendale, WI. 53129.

MANUALS for most ham gear made 45/65, some earlier. Send SASE for specific quote. Hobby Industry, W0JJK, Box H-864, Council Bluffs, Iowa 51501.

THE LaPORTE INDIANA, Amateur Radio Club will hold its annual Swapfest-Auction on the 10th of February, 1974, inside the LaPorte Civic Auditorium, beginning at 10 a.m. Auction beginning at 1 p.m. Talk-in will be on .94 Simplex and 22-82 Repeater.

WANTED, April 1968 Ham Radio. S. E. Janes, G2FWA.

TOUCH-TONE PADS . . . twelve button . . . lighted \$15.00 . . . unlighted \$11.00 . . . postpaid/Insured . . . Swank Roberts, WA5GNT, 1130 Fuller Drive, Apartment 223, Dallas, Texas 75218 . . . (214) 328-9307.

PRINTED CIRCUIT DRILL BITS. Trumbull, 833 3alra Drive, El Cerrito, California 94530.

IV-FM ANTENNA, New Rollable (perfect color bandwidth). Just unroll and hang on wall, even a metal wall! Uses no poles, no rabbit ears, No Signal Splitters since the UHF-VHF-FM terminals are useable and available at the same time. (New 1971 slotted design with U.S. Patent S/N3577196). Antenna size is 18" x 48" when unrolled (long side hangs vertical). Made of decorative plastic such as colored Burlap, yet rugged enough for use in yacht or RV, and can work behind picture. The price is only \$10 or model with the following gains: VHF-FM, 6 dB; and UHF 12 dB. Order postpaid airmail from Antenna Design Co., Subcontract Division, 11621 Hughes Ave. N.E., Albuquerque, N. M. 87112.

0 POUNDS ELECTRONICS PARTS \$10. Tubes for sale too . . . Williams, P. O. 7057, Norfolk, Va. 23509.


WORLDWIDE VHF ACTIVITY: March 9 and 10, 1974, 1 p.m. local time Saturday to 10 p.m. local Sunday. "2 Way" contacts made on 6, 2, or 1¼ meters constitute QSOs. The exchange will be call letters, county, state and a short ragchew. Each band will be scored separately. A station may be worked once per band. Each county and state to be counted once as multipliers. A station operating from more than one county shall be considered to be a different station. Number of contacts x number of counties x number of states worked x total points per band. Do not add scores from two or more bands. Multiband operation is encouraged. Send logs by April 15th, 1974 to WA3NUL, P. O. Box 062, Hagerstown, Maryland 21740. For information contact Page Pyne, WA3EOP via WA3NUL.

HIGH-PERFORMANCE H.F. SYNTHESIZER replaces FO and delivers output 1-30 MHz continuous coverage with accuracy, stability, resolution, and alibration to one Hertz. Write for information, edit Logic Systems, Box 51, Oak Harbor, Wa. 98277

END PERFECT MORSE WITH YOUR RTTY and save over \$150 on price of a comparable Morse keyboard. TMC-1 RTTY to Morse converter connects right into your loop trouble-free and accepts input from keyboard or paper tape reader. Entire circuit including 64-letter buffer memory on one 6 x 6 inch board for \$310. Write for information, edit Logic Systems, Box 51, Oak Harbor, Wa. 98277

OUR AD belongs here too. Commercial ads 35¢ per word. Non-commercial ads 10¢ per word. Commercial advertisers write for special discounts or standing ads not changed each month.

## TOUCH—TONE DECODER

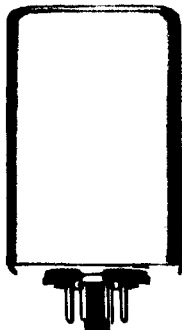

- Dual tone decoder decodes one Touch-Tone digit.

- Available for 1, 2, 3, 4, 5, 6, 7, 8, 9, 0, #, \* and other dual tones 700-3000 Hz.

- Latch and reset capability built-in.

- COR control built-in.
- Relay output SPST ½-amp.
- Octal plug-in case.
- Compact 1-¾" square, 3" high.
- Free descriptive brochure on request.

T-2 Touch-Tone Decoder ... \$39.95 PPD.

Specify digit or tone frequencies.  
(Include sales tax in Calif.)

## PALOMAR ENGINEERS

BOX 455, ESCONDIDO, CA 92025

## NEW DYCOMM SUPER BRICK KIT

1 watt in 30 watts min. out


5 WATTS MAXIMUM DRIVE  
ABSOLUTE MAXIMUM OUTPUT  
CAPABILITY 45 WATTS

See Page 63 December Ham Radio  
for full details

Only \$49.95 postpaid U.S.A.
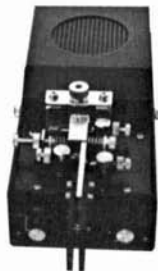
## DYCOMM

948 AVE E P. O. BOX 10116  
RIVIERA BEACH, FLA. 33404  
305-844-1323



## NEW! GLOBALMAN TRANSKEY

**EK-108D**  
with built in monitor  
**\$64.95 ppd.**

Jam-Proof IC Circuitry • 5-50 wpm  
self completing • Output heavy-duty  
TR switch 250v. 2 amps • Power: 2  
flashlight batteries or external 6VDC

1 year unconditional guarantee — 10 day return privilege

Write for specs & photos. Dealers Wanted

**W6PHA — GLOBAL IMPORT CO.**

714-533-4400 Telex 678496 Box 246, El Toro, Calif. 92630

## ECM-5 FM Modulation Meter

Only **\$75.00** less batteries  
and crystal

- Operates 30-500 MHz
- Crystal controlled for fast and easy operation
- Peak reading
- Battery powered with AA pencils
- All solid state
- Built-in antenna
- Quality constructed with G-10 p.c. boards



Phone or write "Skip" W9HAK  
for complete information.

Dial 812-476-2121

Available by direct mail only. ORDER INFO: Send check or money order  
for \$75.00 plus \$1.00 for handling. Indiana residents add 4% sales tax.  
Crystals for 146.94 MHz: \$3.95 ea. All other freqs: \$7.10

# ECM

ECM Corporation  
Dept. E  
412 N. Wernbach Ave.  
Evansville, Indiana 47711

# GATEWAY ELECTRONICS

8123 PAGE AVENUE  
ST. LOUIS, MISSOURI 63130  
314-427-6116

COLLINS MECHANICAL FILTER — Round case  
— from R-390A — 2kHz, 4 kHz, 8 kHz or 16  
kHz. 445 kHz center freq. \$15.00

VACUUM VAR. COND. — JENNINGS UXC 500  
— 500 mmf @ 15 KV \$35.00

TEKTRONIX 527 WAVEFORM MONITOR — Ex.  
Cond. — less case \$295.00

GEL-CELL RECHARGEABLE BATTERY — 6 volt-  
1 Amp 1 1/2" x 2 x 2 \$3.50

0.1" PUNCHED BOARD — Standard spacing  
for IC's

Phenolic — 4.5 x 5.125 - \$1.49, 4.5 x 17 - \$3.19,  
6 x 17 - \$4.19

Epoxy — 4.5 x 6.5 - \$1.69, 4.5 x 8.5 - \$2.10  
4.5 x 17 - \$3.83

Push in Terminals for above boards — Package  
of 100 terminals — \$1.80

8 x 8 7/8" SINGLE SIDED PHENOLIC PC BOARD  
50¢

TRANSISTORS — 2N2219 NPN Sil - 50¢, 2N2222  
NPN Sil - 50¢, 2N2905 PNP - 50¢, 2N2646 Uni-  
junct - 70¢, 2N3394 NPN Sil - 20¢, 2N3569 NPN  
Sil - 45¢, 2N3567 NPN Sil - 40¢, 2N3905 PNP  
Sil - 30¢, 2N4072 NPN Sil RF - 75¢, 2N4852  
Uni-junct - 70¢, MJE1093 Pwr Darlington - \$2.25

**\$5 Minimum Order.**

Visit us when in St. Louis.

Please include sufficient postage.

# CALL BOOK 74

*When you want  
an authoritative,  
up to date,  
complete reference  
It's the  
CALLBOOK*

Over 210,000 QTH's  
in the DX edition  
DX CALLBOOK for 1974  
**\$8.95**



Over 285,000 QTH's  
in the U.S. edition  
U.S. CALLBOOK for 1974  
**\$9.95**

See your favorite dealer or Send today to  
(Mail orders add 50¢ per CALLBOOK  
for postage and handling)


WRITE FOR  
FREE  
BROCHURE

RADIO AMATEUR  
**callbook** INC.  
Dept. E, 925 Sherwood Drive  
Lake Bluff, Ill. 60044

for the most advanced antennas under the sun!



# HY-GAIN 204BA MONOBANDER

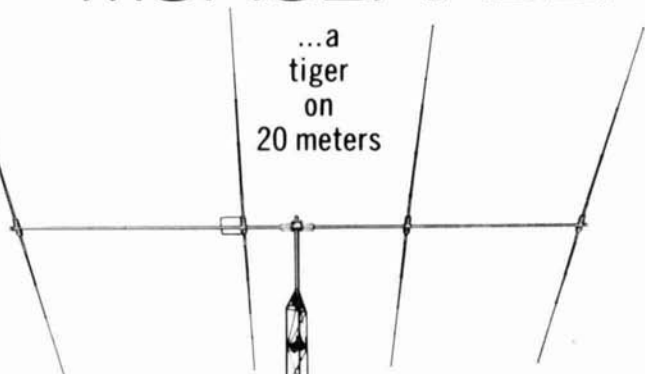

The best antenna of its type on the market. Four wide spaced elements (the longest 36'6") on a 26' boom along with Hy-Gain's exclusive Beta Match produce a high performance DX beam for phone or CW across the entire 20 meter band.

- 10 db forward gain
- 28 db F/B ratio
- Less than 1.05:1 SWR at resonance
- Feeds with 52 ohm coax
- Maximum power input 1 kw AM; 4 kw PEP
- Wind load 99.8 lbs. at 80 MPH
- Surface area 3.9 sq. ft.

The 204BA Monobander is ruggedly built to insure mechanical as well as electrical reliability, yet light enough to mount on a lightweight tower. (Recommended rotator: Hy-Gain's new Roto-Brake 400.) Construction features include taper swaged slotted tubing with full circumference clamps; tiltable cast aluminum boom-to-mast clamp; heavy gauge machine formed element-to-boom brackets; boom 2" OD; mast diameters from 1½" to 2½"; wind survival up to 100 MPH. Shipping weight 51 pounds.

See the best distributor under the sun...the one who handles the Hy-Gain 204BA Monobander.

<b>Model 204BA</b> (4-element, 20 meters).....	<b>\$159.95</b>
<b>Model 203BA</b> (3-element, 20 meters).....	<b>\$149.95</b>
<b>Model 153BA</b> (3-element, 15 meters).....	<b>\$ 79.95</b>
<b>Model 103BA</b> (3-element, 10 meters).....	<b>\$ 64.95</b>



## FERRITE BALUN MODEL BN-86

Improves transfer of energy to the antenna; eliminates stray RF; improves pattern and F/B ratio. **\$14.95**



## ELECTRONICS CORPORATION

Dept. BB, 8601 Northeast Highway Six, Lincoln, NE 68507  
402/464-9151

Telex 48-6424

# Advertisers check-off

... for literature, in a hurry — we'll rush your name to the companies whose names you "check-off"

Place your check mark in the space between name and number. Ex: Ham Radio  234

## INDEX

Allied	204	Janel	068
Amtech	006	K. E.	072
Andy	007	KLM	073
Babylon	014	KRP	074
Barry	016	Leland	193
Bauman	017	Linear	081
CFP	022	Logic	133
Carvill	135	MFJ	082
Catronics	189	Martex	197
Communications Specialists	030	Matric	084
Comtec	151	Meshna	085
Curtis	034	Midland	086
CushCraft	035	Milliwatt	198
Data	037	Mor-Gain	089
Drake	039	Motorola	160
Dycomm	040	Nurmi	090
Dynamic Elect.	041	Oneida	144
ECM	190	Palomar	093
Edison	202	Pemco	095
Ehrhorn	042	Police Call Mag.	199
Eimac	043	Poly Paks	096
Elect. Dist.	044	Prof. Elect.	140
Epsilon	046	RP	098
Exceltronics	139	Callbook	100
Exp. Library	200	Regency	102
Fluke	049	Robot	103
Gateway	052	Savoy	105
Global	053	Space-Military	107
Goldstein's	130	Spectrum	108
Gray	055	Star-Tronics	110
Great American Miniatures	132	Swan	111
Gregory	201	Symtek	203
H & L	056	Teleton	188
HAL	057	Tri-Tek	117
Ham Radio	150	Tristao	118
Henry	062	True Time	205
House Dipoles	036	U J	119
Hy-Gain	064	VHF Eng.	121
Icom	065	Vintage	131
International Crystal	066	Weinschenker	122
International Elect. Unltd	141	Wilson	123
Jan	067	Wolf	124
		World QSL	125
		Y & C	126
		Yaesu	127

Limit 15 inquiries per request.

## February 1974

Please use before March 31, 1974

Tear off and mail to  
**HAM RADIO MAGAZINE — "check off"**  
 Greenville, N. H. 03048

NAME.....

CALL.....

STREET.....

CITY.....

STATE..... ZIP.....

# Advertisers iNdex

ATV Research	86
Amtech	84
Andy Electronics	89
Babylon Electronics	82
Barry	95, 96
Bauman	89
CFP Enterprises	84
Catronics	88
Communications Specialists	70
Curtis Electro Devices	88
CushCraft	29
Data Engineering	69
Drake Co. R. L.	2
Dycomm	72, 91
Dynamic Electronics	70
ECM Corporation	92
Ehrhorn Technological Operations, Inc.	1
Eimac, Div. of Varian Assoc.	Cover IV
Electronic Distributors, Inc.	89
Epsilon Records	84
Exceltronics Research Labs	86
Experimenter's Library	78
Fluke	68
G & G Radio Supply Co.	88
Gateway Electronics	92
Global Import Co.	92
Goldstein's	70
Goodheart Co., Inc. R. E.	80
Gray Electronics	68
Great American Miniatures	78
Gregory Electronics	85
H & L Associates	86
HR Report	72
HAL Communications Corp.	71
Ham Radio	76
Henry Radio Stores	Cover III
House of Dipoles	86
Hy-Gain Electronics Corp.	48, 49, 59, 93
Icom	39
International Crystal Mfg. Co. Inc.	53
International Electronics Unlimited	90
Jan Crystals	70
Janel Labs	88
K. E. Electronics	86
KLM Electronics	84
KRP Electronic Supermart, Inc.	87
Leland Associates	86
Linear Systems, Inc.	76
Logic Newsletter	74
MFJ Enterprises	74
Martex Corporation	74
Matric	74
Meshna, John, Jr.	77
Midland Electronics Co.	80
Milliwatt	86
Mor-Gain, Inc.	78
Nurmi Electronic Supply	64
Oneida Electronic Mfg. Co., Inc.	81
Palomar Engineers	91
Pemco	88
Police Call Magazine	81
Poly Paks	73
Professional Electronics	78
RP Electronics	70
Radio Amateur Callbook, Inc.	80, 92
Regency Electronics, Inc.	66, 67
Robot Research	19
Savoy Electronics	Cover II
Space-Military Electronics	88
Spectrum International	68
Star-Tronics	76
Swan Electronics	5
Teleton Corp.	65
Tri-Tek, Inc.	81
Tristao Tower Co.	88
U J Industries	86
VHF Engineering, Div. of Brownian Elect. Corp.	79
Vintage Radio	76
Weinschenker, M.	63
Wilson Electronics	84
Wolf, S.	74
World QSL Bureau	78
Y & C Electronics	72
Yaesu Musen USA	75



# BARRY

presents

## CLEGG FM-27B



Total 146-148 MHz coverage without buying a crystal. 25w. out, fully synthesized.

**\$479.95**

Clegg FM-27B Regulated AC power supply  
**\$79.95**

### TEMPO

2 Meter Linear Amplifiers, 502, 5-12 watts input, 35-55 watts output ..... \$105.00  
Model 1002-3 5 to 15 watts input, 135 watts output: ..... \$225.00

### BIRD 43 WATTMETER

**\$100.00**

Bird 43 Slugs specify frequency and power

HF ..... \$35.00 each  
VHF ..... \$32.00 each

Also 4350 80-10M dual scale 200w/2kw HamMate — \$79.00

### DRAKE

R4B Receiver ..... xInt. Write  
W/xtr xtals ..... mint \$325.00  
AA-10 Amplifier for TR-22 ..... \$ 49.95  
AC-10 AC Supply for AA-10, TR-22, TR-72, 13.8 VDC @ 3 amps ..... \$ 39.95  
TR-22, in stock ..... \$189.00  
TR-72 2 meter FM transceiver, 23 channel, 1 & 10 watts, 13.8 VDC ..... \$320.00  
TR4/C new, \$599.95 T-4XC Trans. \$530.00  
R4C Rec. \$499.95 MS-4 Speaker \$22.00  
AC-4 Drake A.C. Power Supply ..... \$ 99.95

### DYCOMM

DYCOMM BRICK, 2w in 35w out ..... \$ 79.95  
DYCOMM BLOCK, 10 in 50w out ..... \$ 99.95

### HALLICRAFTERS

SR-160 Transceiver 80, 40, 20 meters ..... write  
FM-300 ..... new, \$625.00  
SX122 Mint condition amateur and general coverage receiver: ..... \$349.00



### GE INDUSTRIAL SILICON RECTIFIER

1400 PIV

250 amp., GE #41A281049-11. Quantities in stock. \$90.00 value, brand new ..... \$15.00

### MISC.

Rubicon precision potentiometer in hardwood case ..... \$ 75.00  
Eico Model 460, 5 MHz factory wired scope: re: \$179.00  
Like New Mint: \$135.00  
IBM 12 volt power supplies, not regulated \$35.00 and up Write or Call  
HP Model 400D VTVM ..... \$125.00

Pay us a visit when you are in New York  
Thousands of unadvertised specials.

Separate export department to expedite overseas orders.

### TEN TEC

TRITON II 5 Band Solid State Transceiver 200 W pep R.I.T. .... \$606.00  
AC Power Supply 252 ..... \$ 89.00  
315 RECEIVER 10-80 meters SSB, AM, CW ..... \$229.00  
CW FILTER FOR 315 ..... \$14.95  
AC4 SWR Bridge ..... KR2 ..... \$ 12.95  
\$ 14.95 ..... KR40 ..... \$ 89.95

### VIBROPLEX

Vibro Keyer ..... Standard \$ 24.95  
Deluxe \$ 32.95  
Original Standard Vibroplex Bug ..... \$ 29.95

### INSTRUMENTS

Millen 2kw matchbox: ..... Write  
Millen 90652 Solid State Dipper, New with 7 coils and carrying case, 1.6 - 300 MHz \$110.00  
PAN ADAPTER BC-1031A ± 100 kc unused with spare parts & book useful with any short wave receiver ..... \$ 55.00

SWR BRIDGE COUPLER, DC-800 MHz  
TNC Connectors  
(no indicator) full amateur power  
\$90.00 Value  
**\$10.95**

### E. F. JOHNSON

Matchbox complete with directional coupler and indicator, 10-80 meters.  
2KW PEP, 1 KW AM — new, Write  
151-1.4 Variable Capacitor, 250 pF, medium Xmitting type ..... \$5.95 ea.

### SWAN

SS-200 Solid State SSB Transceiver with power supply & 16 pole filter ..... Brand new, Write

### MARINE

Barry stocks and has fast availability Sonar, Pearce-Simpson, Andrea, SBE and Antenna Specialists VHF Transceivers, Antennas, Depth Finders and compasses by Andrea.

**BARRY** 512 Broadway NY, NY 10012  
DEPT. H-2  
212-WA-5-7000 **ELECTRONICS**  
TELEX 12-7670

## MISC.

Frequency Meter Counter Model FR114/U \$275.00  
 Heathkit FB-301 with matching SB600 Speaker  
 and Matching SB620 Panoramic adapter: Beau-  
 tiful condition: Write or Call  
 UTC/s-44 Plate Transformer, primary 115, sec-  
 ondary 1.150 VCT at 500 Ma. \$ 35.00  
 UTC Model S4P, primary 115, secondary 3,000  
 VCT at 500 Ma. \$ 49.00  
 Collins Radio, 152J-1 Phone Patch & Station  
 Control. Circuitry similar to 312B-4, xtint con-  
 dition, with schematic \$ 24.95  
 Scanmatic HighBand 8 channel scanner Write  
 TMC - 0-330 B/FR 2 to 6 MHz VFO Exciter, New  
 Condition, Deluxe Quality, Write  
 U.S. Callbooks \$ 9.95  
 DX Callbooks \$ 8.95  
 Radio Handbooks latest 19th edition \$ 14.95  
 Lafayette Telsat-SSB 25, Sideband CB Rig \$195.00  
 Model #104R NPC Power Supply, input 115  
 VAC — 12 VDC out at 4 amp REGULATED  
 at \$ 34.95  
 Model #102 NPC Power Supply, input 115 VAC  
 output at 4 amps. Not Regulated: \$ 24.95  
 LM freq. meters Brand new \$ 19.95  
 Millen magnetic shields for 3" C.R. scope tubes  
 with brackets Brand new \$ 6.95  
 115 Volt AC Power Supply for BC-221, slips into  
 battery compartment. Also can be used with  
 LM freq. meters \$ 29.50  
**ALUMINUM DIE CAST BOXES** in many different  
 sizes. Dossy boxes. Details in New Green Sheet  
 No. 23. Write for latest prices.  
 2 METER VHF DUMMY LOAD/WATTMETER  
 Good up to 15 watts — w/SO-239 CONNECTOR  
 and 3" METER \$ 15.95  
 Original J-38 Key new, \$ 12.50



Jackson G80 brass 50:1 anti-back-  
 lash dial drive 1/4" to 1/4" \$19.00  
 value \$ 5.50

## INOUE IC-230-4

SYNTHESIZED, NO CRYSTALS TO BUY.  
 2 METER TRANSCEIVER

### \$489.00

Inoue IC-22 2 Meter Transceiver.  
 10 watts output plus tremendous  
 receiver — 22 channels. Ready to  
 go with crystals for 5 frequencies  
 at no extra charge. \$289.00

MANY INOUE CRYSTALS IN STOCK  
 IC-3PA Power Supply, Deluxe Regulated  
 for IC-22 or IC-230 \$99.00

## BARKER & WILLIAMSON

Little Dipper, GDO \$ 94.50

DUMMY LOAD WATTMETER 334A DC-300  
 MHz, 1000 watts \$139.95

850A, 852 Inductors \$ 59.95

851 Inductor \$ 29.95

425 Low Pass Filter, 10-80 meters 1 kw \$ 24.95

210 Audio Osc., ideal for lab & broadcast \$329.95

410 Distortion Meter, ideal for lab & broadcast \$369.95

## INVERTER/CONVERTER:

INVERTER, 12 volt DC input, 115 volt AC out,  
 Model 12-115 solid state power supply, 200  
 watts continuous new, \$ 59.95

## BARRY HAS NEW VENUS SS2 SLOW SCAN MONITOR IN STOCK \$349.00 COME TAKE A LOOK OR WRITE

## SBE

NEW "CLOVERLEAF" SBE-450 TRC Transcon-  
 verter instant access to 450 from 144, use with  
 10 watt, 2 meter transceiver to operate on  
 450 MHz \$195.00

## BARRY HAS ANTENNAS

C.D. HAM "M" ROTATORS, new complete \$99.95  
 CD Ham-M for 220 VAC in stock \$175.00  
 C.D. TR-44 ROTATORS, new (complete) \$ 69.95  
 CABLE for Ham-M & TR-44 @ 14¢/ft.  
 CD AR-22R cmplt. rotator for small beams \$33.95  
 BN86 Balun by HyGain \$ 14.95  
 RG-8A/U 100 ft. rolls. VHF connector PL-259  
 one end Type "N" (UG-21E/U) other end \$ 12.50  
 RG8A/U — 65 feet with PL-259 connectors on  
 each end \$ 9.50  
 Times Wire & Cable, T-4-50 (FM-8) 50 ohm  
 lowest loss type RG8/U foam cable 20¢/ft.  
 Columbia Superflex, RG-8/U 50 ohm high qual-  
 ity foam 20¢/ft.  
 Coaxial adapter for VHF to RG-17 (Amphenol  
 83-86) RG-17 plug to VHF female connector \$6.95  
 BNC to RG-17 adapter UG-167C/U \$ 7.95  
 Authorized factory dealers for Antenna Special-  
 ists, CushCraft, Gam, Heights Towers, Hy Gain,  
 Nor-Gain Antenna, Mosley, Newtronics, Tri-Ex,  
 Rohn, E-Z Way, Times Wire, Telrex.  
 RINGO AR-2 3.75 dB gain, 135-175 MHz \$ 14.50  
 BBLT-144 Trunk Lip, 3.75 dB gain \$ 34.95  
 Newtronics CGT-144 mobile 5.2 dB gain \$37.95  
 Quick Disconnect by Newtronics for CGT, etc.  
 \$ 10.95  
 CG-1 Gutter Clip by Newtronics \$ 1.25  
 2M MAGNETIC MOUNT w/RG58 & PL259  
 with 10 ft. RG 58 ready to go \$ 9.95  
 14AVQ/WB VERTICAL \$ 55.00  
 Roofmounting Kit: \$ 15.95  
 18AVT/WB VERTICAL \$ 79.95  
 Newtronics BBLT-110 Trunk lid antenna for  
 car: \$ 36.95  
 Newtronics Hustler Antenna 44 MHz \$ 27.95  
 Antec unusual transmatch: \$ 99.00

## LITTLE LULU

6 Meter AM Transmitter with VFO  
 12 VDC/115 VAC Power Supply

Available factory wired or as parts  
 Write for details

## DX ENGINEERING

### SPEECH COMPRESSORS

DIRECT PLUG-IN FOR COLLINS 32S \$79.50 ppd. U.S.A.

DIRECT PLUG-IN FOR KWM-2 \$79.50 ppd. U.S.A.

DIRECT PLUG-IN FOR NEW DRAKE TR3 or  
 TR4C RECEIVER \$98.50 ppd. U.S.A.

**Tube Headquarters. Diversified Stock. Heavy  
 inventory of Eimac tubes, chimneys, sockets, etc.  
 572B \$ 17.50**  
 Barry Now Stocks Bogen, Electrovoice & Univer-  
 sity. Call or Write.

CASH PAID . . . FAST! For your unused TUBES,  
 Semiconductors, RECEIVERS, VAC. VARIABLES,  
 Test Equipment, ETC. Write or call Now! Barry,  
 W2LN1. We Buy! We ship all over the World.

Send for Green Sheet Supplement 23.  
 Send 50¢ postage & handling (refund 1st order).

**BARRY** 512 Broadway NY, NY 10012  
 DEPT. H-2  
 212-WA-5-7000 **ELECTRONICS**  
 TELEX 12-7670

# choose from the finest line of amplifiers ever offered



**2K-ULTRA**  
... THE "ULTIMATE"

There has never been an amateur linear amplifier like the new 2K-ULTRA. Small and lightweight, yet rugged and reliable... all that the name implies. The ULTRA loafs along at full legal power without even the sound of a blower. Its anode heat is silently and efficiently conducted to a heat sink through the use of a pair of Eimac 8873 tubes. In fact, all of its components are the very best obtainable.

#### **TEMPO/2001**

Small but powerful, reliable but inexpensive, this amplifier is another top value from Henry Radio. Using two 8874 grounded grid triodes from Eimac, the Tempo 2001 offers a full kilowatt of output for SSB operation in an unbelievably compact package (total volume is .8 cu. ft.). The 2001 has a built-in solid state power supply, a built-in antenna relay, and built-in quality to match much more expensive amplifiers. This equipment is totally compatible with the Tempo One as well as most other amateur transceivers. Completely wired and ready for operation, the 2001 includes an internal blower, a relative RF power indicator, and full amateur band coverage from 80-10 meters.


#### **TEMPO/6N2**

The Tempo 6N2 joins the Henry Family of fine HF amplifiers, bringing the same high standards of performance and reliability to the 6 meter and 2 meter bands. Using a pair of advanced design Eimac 8874 tubes, it provides 2,000 watts PEP input on SSB or 1,000 watts input on FM or CW. The 6N2 is complete in one compact cabinet with a self-contained solid state power supply, built-in blower and RF relative power indicator. Price... \$695.00

#### **3K-A COMMERCIAL/MILITARY AMPLIFIER**

A high quality linear amplifier designed for commercial and military uses. The 3K-A employs two rugged Eimac 3-500Z grounded grid triodes for superior linearity and provides a conservative three kilowatts PEP input on SSB with efficiencies in the range of 60%. This results in PEP output in excess of 2000 watts. In addition, the 3K-A provides a heavy duty power supply capable of furnishing 2000 watts of continuous duty input for either RTTY or CW with 1200 watts output.

Prices subject to change without notice.

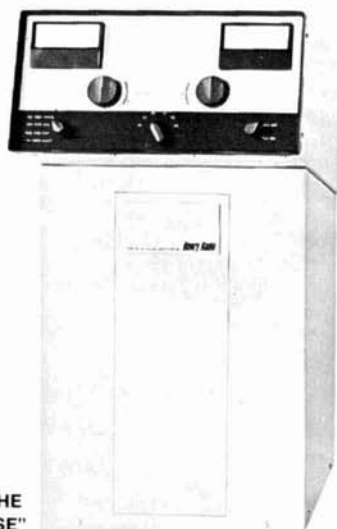


**2K-4... THE  
"WORKHORSE"**

The 2K-4 linear amplifier offers engineering, construction and features second to none, and at a price that makes it the best amplifier value ever offered to the amateur. Constructed with a ruggedness guaranteed to provide a long life of reliable service, its heavy duty components allow it to loaf along even at full legal power. If you want to put that strong clear signal on the air that you've probably heard from other 2K users, now is the time. Move up to the 2K-4. Floor console or desk model.

## *Henry Radio*

11240 W. Olympic Blvd., Los Angeles, Calif. 90064  
213/477-6701  
931 N. Euclid, Anaheim, Calif. 92801 714/772-9200  
Butler, Missouri 64730 816/679-3127
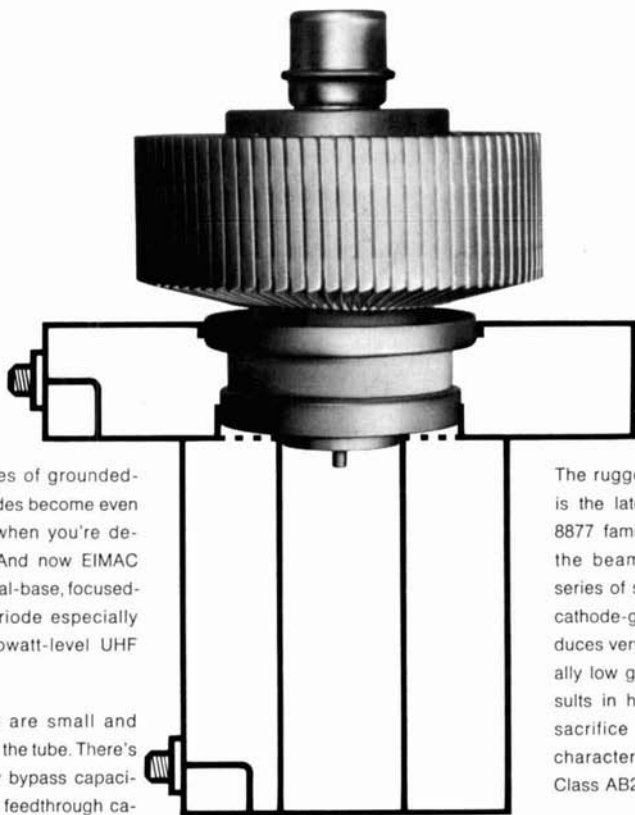
# Simplify UHF circuits with EIMAC's 8938 high mu triode.



All the advantages of grounded-grid, high-mu triodes become even more important when you're designing at UHF. And now EIMAC introduces a coaxial-base, focused-beam, high-mu triode especially designed for kilowatt-level UHF applications.

At UHF, cavities are small and closely coupled to the tube. There's no room for bulky bypass capacitors, rf chokes, or feedthrough capacitors. With the 8938 in cathode driven (grounded-grid) service, there's no need for the grid circuit bypass capacitor; and no need for screen capacitors, bias or screen power supplies and associated decoupling circuitry. The internal tube structure is simple and the surrounding circuitry is much less complicated.

The rugged, ceramic/metal 8938 is the latest addition to EIMAC's 8877 family of tubes. Because of the beam focusing action of a series of strip electron guns in the cathode-grid region, the 8938 produces very high mu with exceptionally low grid interception. This results in high power gain with no sacrifice of low intermodulation characteristics in cathode-driven Class AB2 amplifier service.

It's one more example of EIMAC's ability to provide tomorrow's tube today. For details, contact EIMAC Division of Varian, 301 Industrial Way, San Carlos, California 94070, (415) 592-1221. Or any of the more than 30 Varian/EIMAC Electron Tube and Device Group Sales Offices throughout the world.

