


85 cents

hcr

focus
on
communications
technology . . .

ham **radio** *magazine*

NOVEMBER 1974

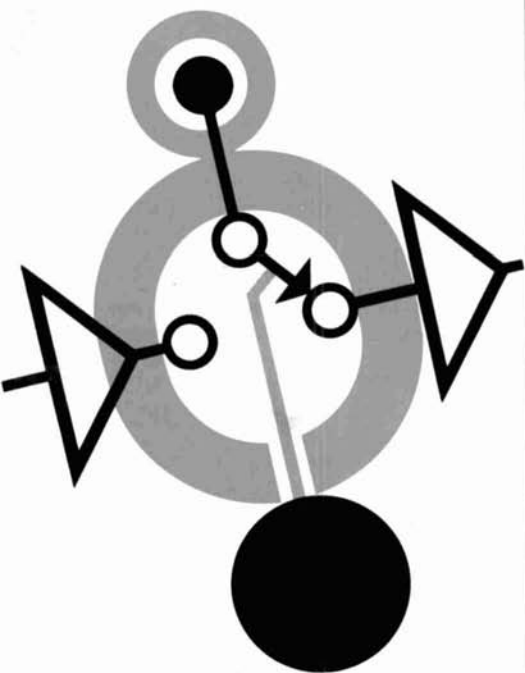

low-power
single-band CW
transceiver

this month

- artificial radio aurora 18
- vhf channel scanner 26
- predicting harmonics 34
- low-frequency converter 49
- solar power 52



Holiday Specials

ORDER EARLY FOR CHRISTMAS DELIVERY

This year, invest in an ALL American made Swan 300B Cygnet *de novo* transceiver. You'll never get a better deal for yourself or that special ham on your Christmas gift list.

- 300 watts P.E.P. input (SSB)
- Internal 110V AC power supply
- USB, LSB, AM and CW modes
- 5 Bands, 10 through 80 meters
- Natural sounding voice
- Convenient financing with NO MONTHLY PAYMENTS UNTIL 1975 on your Swan Revolving Credit Service Plan.

HOLIDAY PACKAGE BUY #1

Swan 300B transceiver PLUS TD-80/40 trap-dipole antenna for 80 and 40 meters. Regular list value of \$595.85, now just \$536.25 complete.

HOLIDAY PACKAGE BUY #2

Swan 300B transceiver PLUS 14-A 12V DC converter PLUS 404 microphone PLUS 45 mobile 5-band antenna. Regular list value of \$679.80 at only \$611.95.

HOLIDAY PACKAGE BUY #3

Swan 300B transceiver PLUS 444 microphone PLUS TB-3HA beam antenna for 10, 15 and 20 meters. Regular list value of \$715.85 reduced to \$679.95.

Sorry, no substitutions/deletions to special packages. Reduced prices shown are restricted to combinations stated through December 25, 1974, only. California residents, please include sales tax when ordering direct from the factory.

Order through any participating Swan dealer or, if you prefer, complete and mail the coupon with your down payment (certified check or money order) to:

SWAN ELECTRONICS, 305 Airport Road, Oceanside, CA 92054.



Swan 300B Cygnet *de novo* \$519.95

HOLIDAY PACKAGE BUY #4

Swan 300B transceiver PLUS 444 microphone PLUS TB-3HA beam antenna PLUS 1200X linear amplifier. A 1200 watt P.E.P. station. Regular list value of \$1015.80, now at \$964.95 complete.

MOBILER PACKAGE BUY #5

Swan MB-40A 160 watt P.E.P. 40-meter transceiver PLUS 404 microphone PLUS 35 mobile 40-meter antenna . . . OR . . . Swan MB-80A 160 watt P.E.P. 80-meter transceiver PLUS 404 microphone PLUS 35 mobile 80-meter antenna. Up to a \$407.75 list value — your choice — for \$385.95.

Gentlemen:

Please ship, best way — collect, the items checked to:

Name _____

Address _____

City _____

State _____ Zip _____

Amateur Call _____ Phone _____

PACKAGE BUY #1 — \$536.25

PACKAGE BUY #2 — \$611.95

PACKAGE BUY #3 — \$679.95

PACKAGE BUY #4 — \$964.95

PACKAGE BUY #5 — \$385.95

(MB-40A or MB-80A)

300B Cygnet *de novo* — \$519.95

TOTAL AMOUNT OF ORDER = \$ _____

TOTAL AMOUNT ENCLOSED = \$ _____

Full Payment Enclosed, 20% down payment

enclosed, ship C.O.D. 20% down payment enclosed,

charge remainder to BankAmericard # _____

expires _____ 20% down payment enclosed,

charge remainder to Mastercharge # _____

expires _____ 4-digit Interbank # _____

10% down payment enclosed, charge remainder to

Swan Account # _____

(Signature)

(Date)

The Inside Story on Amateur Slow Scan TV

PART 1



SEND FOR OUR 7 PC. 10,000 WORD SSTV

STORY. Everything from SSTV frequency allocations to reprints of ham magazine SSTV articles that you may have missed.

PART 3



TUNE TO 14.230 MHz AND SEE ALL THE SSTV ACTION

There is almost continuous SSTV activity on 14.230. A good way to get the inside SSTV story is to monitor this frequency.


PART 2



WE'LL SEND YOU OUR DIRECTORY OF SSTV OPERATORS!

Talk with them yourself and see how much they enjoy SSTV. You might find that old friend you used to work on 6 meters has gone to SSTV.

PART 4

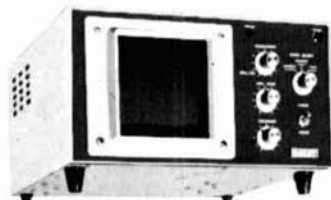

WE'LL SHIP YOU OUR MONITOR AND/OR CAMERA ON OUR 100% SATISFACTION OR MONEY BACK GUARANTEE

See for yourself why SSTV is the fastest growing amateur radio activity.

MODEL 70A SSTV MONITOR \$345

MODEL 80A SSTV CAMERA \$345

MODEL 61 VIEWFINDER \$265

Please send me the following:

- Free 7 pc SSTV literature Model 70A SSTV monitor
 Model 80A SSTV camera Model 61 Viewfinder

NAME _____ CALL _____

ADDRESS _____

CITY _____

STATE _____ ZIP _____

ORDER FACTORY
DIRECT
TODAY

ROBOT

ROBOT RESEARCH INC.

7591 Convoy Court
San Diego, CA 92111
Ph. (714) 279-9430

signal/one For those who demand the finest...



INTRODUCING THE MODEL CX-11... *Deluxe Integrated Station*

9 New Features

New solid state broadband linear power amplifier 10-160 meters. 175 Watts DC output — requires no tuning, operates into any VSWR — continuous duty at full rated output.

New concept front-end design — utilizing double active balanced mixers for unmatched sensitivity, blocking and cross-modulation rejection.

Solid-state modular construction utilizing gold-plated, pins and plug-in sockets for all transistors, IC's, and circuit board connectors.

Five Bandwidths of selectivity are standard — 2.4, 1.5, 1.0, .4, .1 kHz.

Peak notch filter with adjustable frequency notch depth and Bandwidth controls.

RTTY narrow and wide shift FSK-LSB. Built-in electronic Keyer with independent speed and weight control and partial or full dot memory.

Power supply completely self-protecting — both thermal and current overload, integrated circuit controlled.

New six-digit frequency counter utilizing new 1/2 inch amber or red LEDs optimized for a non-blinking, stable display.

ADDITIONAL FEATURES

- Dual VFO's for transceive, split operation, or dual receive.
- Adjustable IF shift.
- Receive or transmit offset tuning.
- Push Button spotting.
- Adjustable R.F. clipping.
- Instantaneous break-in CW.
- Built-in Wattmeter.
- Built-in noise blander.
- Adjustable R.F. power output.
- Pre-IF, adjustable noise blander.

Distributed by

PAYNE RADIO

BOX 525, SPRINGFIELD, TENNESSEE 37172
Phone (615) 384-5573 — Nights (615) 384-5643

In Europe contact:
SB COMMUNICATIONS

Palmtorpsvagen 3
S-640 20 BJORKVIK, Sweden

Due to our tremendous growth — openings now available for communications design engineer, engineering aids and technicians.

Up date your CX7, CX7A to the CX7B with the all new 4-digit LED freq. counter and the new IC self-protecting CX7B power supply.

Complete Parts & Service At



Box 127 Franklin Lakes, NJ 07417
Tel: (201) 891-0459

November, 1974
volume 7, number 11

staff

James R. Fisk, W1DTY
editor-in-chief

Joseph Schroeder, W9JUV
editor

Patricia A. Hawes, WN1QJN
assistant editor

J.Jay O'Brien, W6GDO
fm editor

Alfred Wilson, W6NIF
James A. Harvey, WA6IAK
associate editors

Wayne T. Pierce, K3SUK
cover

T.H. Tenney, Jr. W1NLB
publisher

Hilda M. Wetherbee
assistant publisher
advertising manager

offices

Greenville, New Hampshire 03048
Telephone: 603-878-1441

ham radio magazine is
published monthly by
Communications Technology, Inc
Greenville, New Hampshire 03048

Subscription rates, world wide
one year, \$7.00, three years, \$14.00
Second class postage
paid at Greenville, N.H. 03048
and at additional mailing offices

Foreign subscription agents
United Kingdom
Radio Society of Great Britain
35 Doughty Street
London WC1N 2AE, England

All European countries
Eskil Persson SM5CJP
Frotunagrand 1
19400 Upplands Vasby, Sweden

African continent
Holland Radio, 143 Greenway
Greenside, Johannesburg
Republic of South Africa


Copyright 1974 by
Communications Technology, Inc
Title registered at U.S. Patent Office
Printed by Wellesley Press, Inc
Framingham, Massachusetts 01701, USA

Microfilm copies of current
and back issues are available
from University Microfilms
Ann Arbor, Michigan 48103



contents

- 8 low-power cw transceiver**
Wesley H. Hayward, W7ZOI
- 18 scattering characteristics of artificial radio aurora**
Victor R. Frank, WB6KAP
- 26 vhf fm channel scanner**
Gerald F. Vogt, WA2GCF
- 32 measuring peak envelope power**
Carl C. Drumeller, W5JJ
- 34 harmonic prediction**
Fin K.L. Utne
- 38 the code mill**
H.E. Thomas, W6CAB
- 44 automatic phone controller for repeaters**
Robert C. Heptig, K0PHF
Robert D. Shriner, WA0UZO
- 49 tunable low-frequency converter**
Guenter Ruehr, OH2KT
- 52 solar power**
Edward M. Noll, W3FQJ
- 4 a second look** **60 ham notebook**
94 advertisers index **94 reader service**
58 comments **6 stop press**
83 flea market

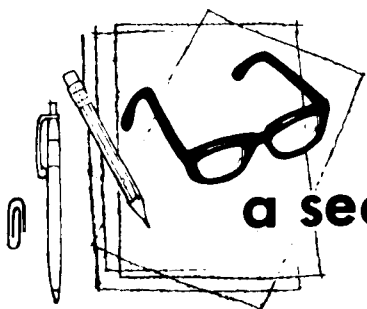

a second look

by jim
fisk

Here's a new technology that you're going to be hearing a lot more about in the not too distant future: *additive* printed circuit wiring. If you're wondering what's new, the process used to manufacture most of the PC boards used nowadays is called the *subtractive* process: you start with a copper-clad board and etch out the desired conductor pattern. In the additive process the copper is deposited on the board in the desired conductor pattern. The big advantage is that the process uses up to 75% less copper — obviously important to an industry that is facing a real squeeze by the world-wide copper shortage.

Additive printed-circuit wiring has been around for several years, but until recently users have been troubled by peeling and edge lifting, as well as warpage and cracking. Now, however, many of these problems have apparently been solved, and it appears that the additive technique is about to produce a substantial portion of the PC boards now manufactured by the conventional subtractive process. In fact, some industry spokesmen indicate that the additive process will account for up to 50% of the market by the end of 1975.

In addition to the conservation of copper, the additive printed-circuit process eliminates undercutting due to etching and offers improved circuit design capabilities such as closer line-width tolerances. For example, in standard etched printed-circuit boards with 1-ounce copper foil, the minimum line width is about 10 mils; with the additive process 5-mil line widths are routine. Closer manufacturing tolerances in the near future are expected to allow line widths down to 2 mils.

In addition, when used for high production quantities, the cost of boards produced by the additive technique are considerably less expensive. In mass applications such as television sets and stereo systems, the savings over subtractive PC boards can be as much as 35%. And high production is not the only promising area for additive circuits — because of the smaller line widths and spacings the technique is expected to find wide use in high-density interconnection applications such as computer peripherals.

The principal problem that had to be solved before the additive technique became a viable manufacturing process was finding a way to make the electroless-copper stick to the glass-epoxy laminate. This adhesion (typically 8- to 10-pounds pull) is provided by micropores on the laminate surface. This is no easy task, but one successful approach is to coat the bare laminate with a special adhesive which is activated by a chromic-acid etch. The etchant produces micropores in the adhesive surface and is similar to the treatment used in the plating of plastics.

I don't expect that this technique will replace the various subtractive systems that amateurs have developed to make their own printed circuit boards, not in the near future anyway. However, printed-circuit boards were being used by the manufacturers of television sets long before the process was even considered for one-off amateur projects, so nothing will surprise me. Perhaps one of the chemists among us will come up with a simple additive PC process that we can use in our own home workshops.

Jim Fisk, W1DTY
editor-in-chief

It speaks for itself



-
- FREQUENCY RANGE** 2 - 30 MHz *Continuous*
- STABILITY and SETABILITY** ± 1 Hz at constant ambient
- MODES** SSB/CW, AM, FM
- IF BANDWIDTHS SUPPLIED** 500 Hz CW
3.2 kHz USB/LSB/ISB
6 kHz
16 kHz
- SENSITIVITY (10dB S+N/N)** 0.6 μ V SSB
2.5 μ V AM
- CROSS MODULATION** Signals removed by $\pm 10\%$ from the displayed frequency may be 80 dB greater than the specified sensitivity without producing more than 10% modulation of the desired signal.
- INTERMODULATION DISTORTION** Two tones in the RF passband must be at least 65 dB above 1 μ V to produce a 3rd order product equal to a 1 μ V signal
-

For more information, send for our data sheet
MODEL 1230A RECEIVER — \$3930

RAYTHEON

RAYTHEON COMPANY
 MARKETING DEPT. (SP)
 P. O. BOX 1542
 GOLETA, CALIFORNIA 93017
 AREA CODE 805 967-5511



FCC AMATEUR RADIO ADVISORY COMMITTEE PROJECT, proposed in ARRL/FCC meeting May 10th beginning to warm up as Amateur and CB Division staff lay groundwork for a formal presentation to the Commissioners. A letter has been sent to quite a number of amateurs outlining the purposes and responsibilities of the ARAC.

Letter Was Definitely NOT An Invitation to membership in the ARAC, but instead was sent out as a means of determining whether there would be sufficient support from amateurs to insure ARAC success if the Commissioners were to approve it. Letter proposed basic 12-15 member "Steering Committee" to be chaired by FCC representative, a number of Ad Hoc subcommittees (each chaired by a Steering Committee member) to consider specific problem areas. Steering Committee membership would be by invitation of the Commission, with broad geographical as well as interest-area representation.

ARRL PREPARATIONS FOR 1979 World Telecommunications Conference should be aided by WIRU and KIZND having participated in a frequency management seminar in Geneva during September.

BLOCKBUSTER TRANSCEIVER FROM HEATHKIT announced this month (see centerfold). The new SB-104 is all solid state, totally broadbanded, digital readout and covers all ham bands from 3.5 to 29.7 MHz! Delivering 100 watts SSB or CW, the SB-104 operates from 13 Vdc, weighs only 20 pounds and measures about 6x14x14 inches; its 6-digit readout provides 100-Hz resolution, 200-Hz accuracy.

New Accessories Complement the SB-104 -- SB-230 linear with conduction-cooled output tube; SB-614 Station Monitor; SB-634 Station Console; SB-644 Remote VFO. Truly state-of-the-art!

GENAVE GOING TO DIRECT SALES IN THE AMATEUR MARKET, with change becoming official November 1st. Inflationary pressures, determination that 75-80% of Genave's ham gear has been selling by mail order anyway are cited as the reasons. High proportion of mail-order sales has meant most service has been factory responsibility, so change to factory selling is a logical one.

Genave's Pricing will reflect the change -- list on the popular GTX-200 will go from \$399.95 to \$299.95, and other models will show similar reductions.

HILDA WETHERBEE LEAVES HAM RADIO. Hilda, a key part of HR since its beginning and well known to many amateurs and the ham industry for her participation in many hamfests and highly effective ad selling, has joined a research firm in New Hampshire.


MOBILERS BEWARE: Minnesota has joined Florida and Virginia in forbidding the wearing of headphones while driving.

ANOTHER 10-METER BEACON PLANNED, this one proposed for San Diego by K6HME and WB6KNC. Request for Special Temporary Authority has been returned for justification of proposed 100-watt power and SSB ID, but as soon as questions are resolved it should be operative using K6HME call. Proposed frequency is 29.0 MHz, same as German DLØAR beacon.

"COMMERCIAL" USE OF HAM BANDS subject of concern in Washington, confusion among hams. Recent League Lines item (August, 1974 QST) caused most nets to scrub "swap shop" sessions, but one subsequent interpretation seems to permit such activities providing they are scrupulously "non-commercial" and any given individual limits himself to "infrequent" participation (whatever that means)...

JA STATIONS TO GET NEW 80 METER "WINDOW" within the next month or so. Present JA allocations are 3500-3525 CW, 3525-3575 for phone; the new band is a 10-kHz slice from 3793-3803 kHz, will help JA-Europe and JA-U.S.A. QSOs.

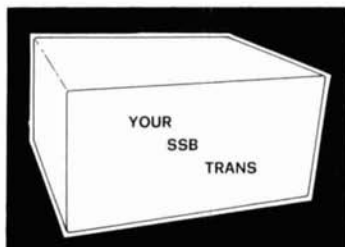Slow-Scan Enthusiasts can also look for a big increase in JA SSTV activity very shortly. Although over 100 stations have been licensed for slow-scan in Japan since April, 1973, reorganization of the Japanese Ministry of Post and Telecommunications has caused a big backlog to develop. Kinks are now being worked out, and a big influx of JA SSTVers is expected momentarily.



PLUS



EQUALS



AND---



*160-meters is fun,
and it's easy besides
when your equipment
comes from Dentron.*



Here's a REAL plus

You will add a real plus to your SSB station when you give it complete 160-meter receive and transmit capability with the exciting new Dentron 160 XV Transverter. Just two simple connections with no modifications and you're on the air.

- 5 watts drive gives 100 watts DC input
- 3.8 to 4.0 MHz input
- Matches 50 ohm antenna
- Built in 110/220 V 50/60 Hz supply

Dentron 160 XV Transverter

\$199.50 ppd. USA

plus even more!

Let the Dentron 160 AT antenna tuner solve your 160-meter antenna problems the easy uncomplicated way. This transmatch will load any random length antenna from a short whip to an extra-long wire. Use it with virtually any existing HF antenna you already have. Handles maximum legal power. Use with the 160-XV or any other 160 meter equipment requiring a 52 ohm antenna.

Dentron 160 AT Antenna Tuner

\$49.95 ppd. USA

Dentron

27587 Edgemark Dr.
North Olmsted, Ohio 44070
Telephone (216) 734-7388



low-power single-band cw transceiver

Design and
construction of a
deluxe 1.5-watt
QRP CW package
for 20 meters

There is little doubt that low-power (QRP) operation has become one of the more popular amateur radio activities in recent years. I got hooked on the QRP game a little over ten years ago when a need arose for light-weight portable gear for use on mountaineering trips. Although this goal was easily and quickly realized, my interest continues. Even today, after a few thousand QSOs with a

power of only a few watts, I still get a thrill when another QRP contact is completed.

While some manufacturers are now seriously aiming products at the QRP market, the area is still ripe for the home experimenter. To many QRP enthusiasts, the only equipment which is considered for construction is that which is as simple as possible. While simplicity certainly has its merits, especially for portable operation in a severe environment,^{1,2} home-station operation is greatly enhanced with equipment which is a bit more elaborate. This article describes a transceiver for 20-meter CW which is aimed at this improved performance.

One of the more significant deficiencies of many QRP stations is the lack of selectivity and dynamic range in the receiver. Although it is possible to obtain superb performance from a direct-conversion design, as demonstrated by the recent work of DeMaw,³ there is still no substitute for a cleanly operating superhet. Hence, this approach was taken in this design.

Wes Hayward, W7ZOI, 7700 SW Danielle Avenue, Beaverton, Oregon

Some of the simplicity of a direct-conversion design is retained by eliminating virtually all of the gain usually found at the intermediate frequency. The result is a receiver which is more than adequately sensitive and selective, but is still easy to duplicate. Provision is made for receiving both CW and ssb in the unit described, with sideband included mainly for use with vhf converters. Further simplification and reduced cost will result if one of the modes is deleted.

The transmitter portion of the package was designed with a number of objectives

built-in sidetone oscillator and a semi-break-in keying system. These features are not absolutely necessary, but are easily realized and add measurably to the operating enjoyment derived from the station.

Shown in fig. 1 is a block diagram of the transceiver. The usual 9-MHz i-f and 5-MHz vfo scheme is used, providing good performance in a single-conversion system. A total of seven individual circuit boards are used, most of them based upon a simplified double-sided PC board technique outlined earlier. The use of

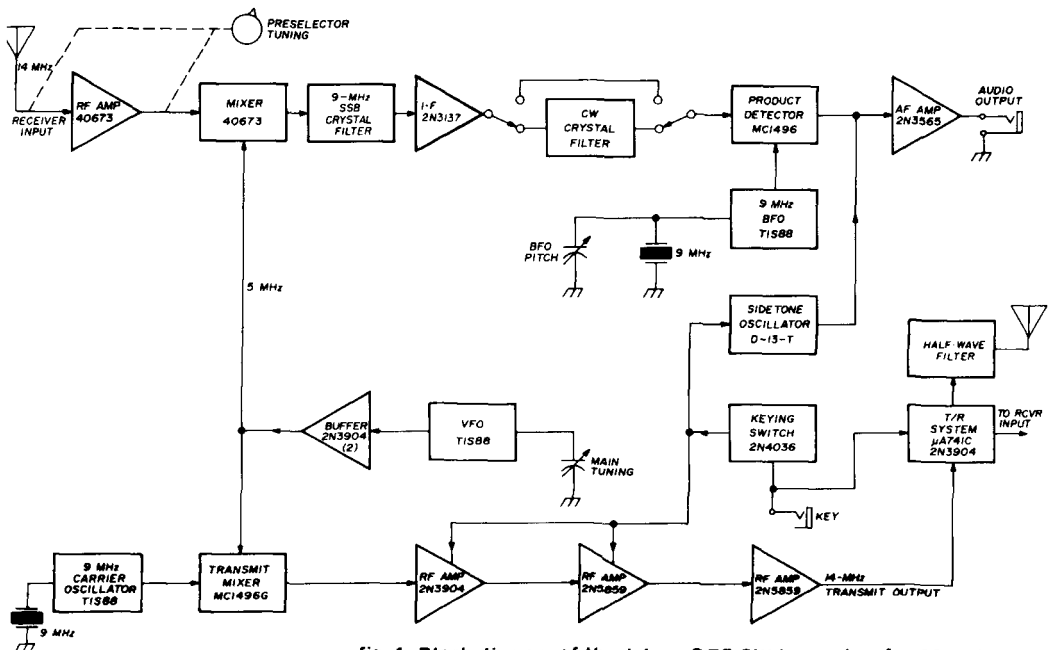


fig. 1. Block diagram of the deluxe QRP CW transceiver for 20 meters.

in mind. First, full transceive operation was desired. However, it was not acceptable to sacrifice the cleanliness of the system output. Experience with an earlier 40-meter transceiver demonstrated that this objective is not easily met with a casual design. The unit described in this article has been evaluated with lab quality test equipment, and all spurious outputs were more than 50-dB below the desired 1.5-watt output.

Additional design criterion for the transmitter included the desire for a

double-sided board is highly recommended since it provides the low-impedance ground paths required for clean, spur-free performance.


vfo design

Shown in fig. 2 is the variable-frequency oscillator which controls both the receiver and the transmitter. The design offered several years ago by Hanchett⁴ was used, although the original mosfet was replaced with a junction fet. I keep coming back to this design since it is

both stable and reliable. As with most oscillators, the selection of components is a large part of achieving stability. The inductor is wound on a ceramic form which was originally tuned with a powdered-iron slug. However, the slug was removed to enhance stability, and the number of turns on the coil was pruned to obtain the proper inductance. The vfo is tuned with the ever reliable and easy-

forms well in this circuit. The oscillator supply voltage is stabilized with a 6.8-volt zener diode. The voltage rating here is not critical.

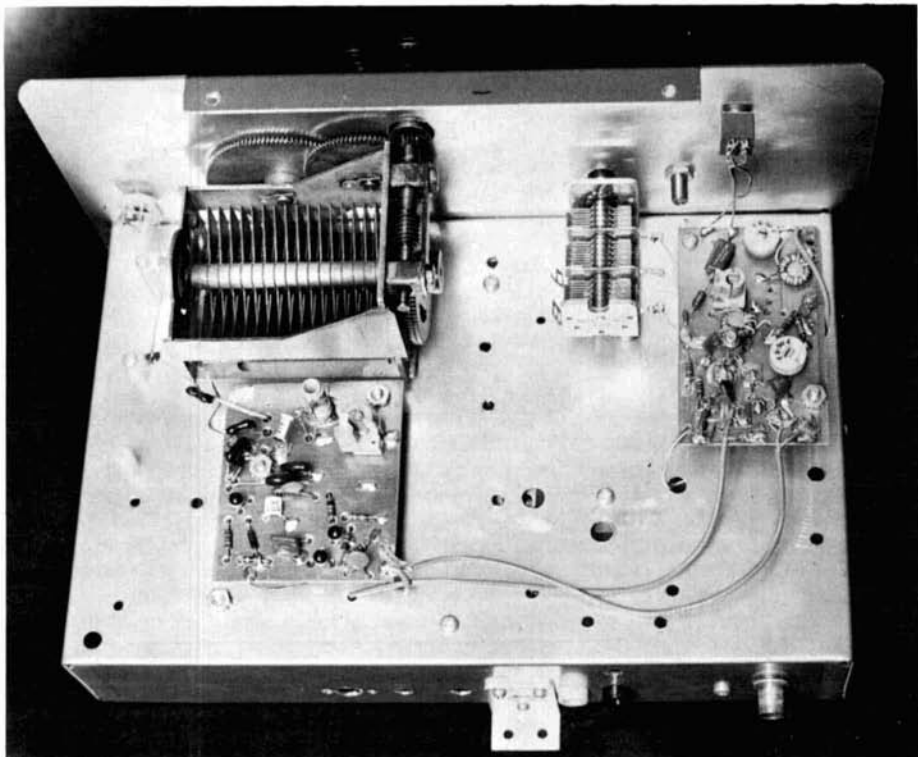The vfo is buffered with a single-stage feedback amplifier using a pair of 2N3904 transistors. Again, transistor type is not critical in this application, although devices with an f_T of at least 250 MHz should be used. The output of the buffer



Top view of the 20-meter CW transceiver, showing the vfo (left) and receiver rf amplifier (right).

to-use capacitor from a surplus ARC-5 Command transmitter. Although becoming scarce, these capacitors can still be found in junk boxes and at hamfest flea markets. With the components shown, the oscillator tunes from 5.0 to 5.55 MHz.

A number of commonly available field-effect transistors can be used in this oscillator. I used a TIS88 which is a plastic device very similar to the popular 2N4416. The Motorola MPF102 also per-

is 3 volts, peak-to-peak and sinusoidal. If it is suspected that significant harmonic energy might be present in the oscillator output, a lowpass filter could be included.⁵

receiver front-end and i-f filtering


Presented in **fig. 3** is the front-end and filter section of the receiver. For the most part, the design is quite standard and is easily duplicated. Both the rf amplifier

and the mixer circuits use RCA 40673 dual-gate mosfets. Since my transceiver tunes a 500-kHz range, a dual-section variable capacitor was included for front-panel preselector tuning. An earlier version of this transceiver tuned only the CW portion of the band, and front-panel tuning was not needed. The toroid cores used in the receiver and in the transmitter section described later are very similar in

on the respective coils. The minimal degradation in gain and noise figure should present no problem in typical applications. The dynamic range of this receiver has not yet been measured.

A coarse rf gain control is provided by a front-panel switch which decreases the gate-2 bias from the nominal 4-volt level to ground. This yields a gain reduction of about 15 dB. Since the application of

fig. 2. Vfo for the deluxe QRP transceiver tunes from 5.0 to 5.55 MHz. Inductor L1 is 3.5 μ H, wound on 1/4" (6 mm) ceramic form, no tuning slug.

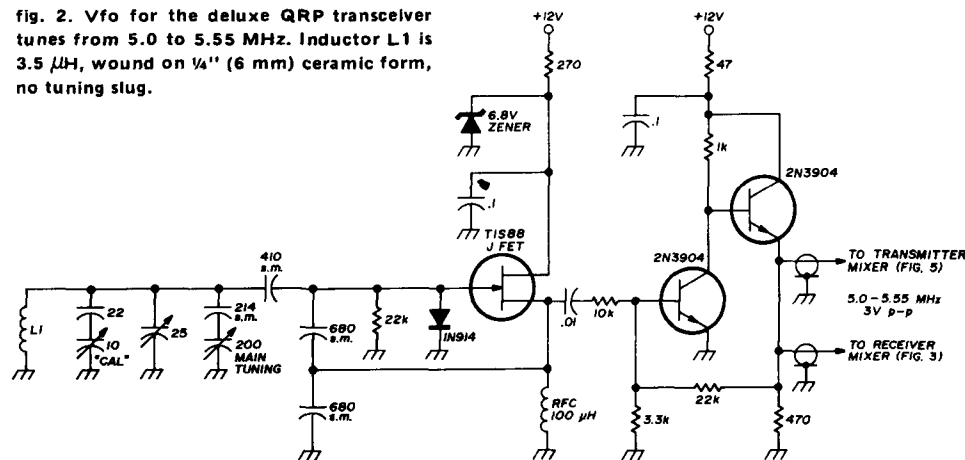

inductance and Q to the Amidon T-50-6.* Substitution of Amidon cores should be possible using the same number of turns shown.

Sensitivity measurements revealed a system noise figure of around 7 dB. Hence, the receiver is probably quite a bit hotter than can be used in normal locations. Much of the dynamic range possible with mosfets was retained by terminating the mixer output with a 330-ohm resistor. Since drain non-linearity is the usual mechanism for blocking in a fet mixer, a decrease in output load impedance results in relative freedom from this problem. Similarly, the load resistance presented to the drain of the rf amplifier is about 1000 ohms. If dynamic range problems are encountered, further improvement would result if the gate of each stage were driven from a tap

gain reduction can often decrease the immunity of an fet rf amplifier to cross-modulation and IMD, passive front-end signal attenuation would be a better means of gain control.

The output of the mixer is routed through a coax cable to the first crystal filter. This filter is always in the signal path and is used for ssb reception. The filter I chose was the WF-8 model manufactured by Wheatlands Electronics.† This eight-pole unit performs well in this application, and probably represents one of the better component buys around.

The output of the first filter is applied to a low-gain amplifier. A junk box 2N3137 was used, although this stage is not critical, and could probably be replaced with a 2N3904 or a 2N4124. Alternately, if some impedance matching is done at the input, a dual-gate mosfet

*Amidon Associates, 12033 Otsego Street, North Hollywood, California 91607.

†Wheatlands Electronics, P.O. Box 343, Arkansas City, Kansas 67005.

with a 510-ohm drain load resistor should perform well in this slot. The main function of this stage is to provide a proper driving impedance for the second filter with a minimum gain.

During CW operation, a KVG type XF-9M four-pole crystal filter is switched into the system.* The switching is done with a pair of inexpensive slide switches which are mounted on the circuit board.

input resistors have been chosen to properly terminate the KVG crystal filter. The bfo is a simple fet crystal oscillator which is trimmed from the front panel with an 80-pF variable capacitor.

The audio section consists of a pair of 2N3565 transistors and provides around 70-dB of gain to drive high-impedance headphones. This amplifier is built on the same board that contains the sidetone

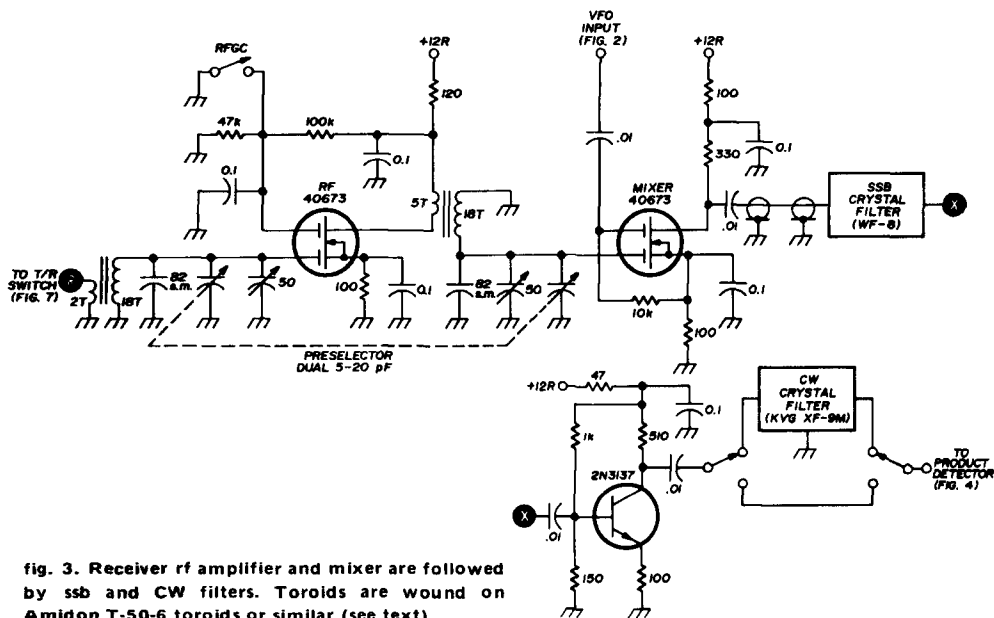


fig. 3. Receiver rf amplifier and mixer are followed by ssb and CW filters. Toroids are wound on Amidon T-50-6 toroids or similar (see text).

The switches are ganged together by drilling small holes in the plastic handles and attaching a strip of scrap PC board. A spade lug is also bolted to the connecting strap. A tapped, 1/4-inch (6-mm) spacer is then screwed onto the spade lug. This spacer extends through the front panel where a knob is mounted.

product detector and audio

Shown in fig. 4 is the product detector and bfo used in the receiver. The detector uses a Motorola MC1496G integrated circuit. The configuration is generally the same as that shown in the Motorola applications literature, except that the

*KVG crystal filters are available from Spectrum International, Box 1084, Concord, Massachusetts 01742.

oscillator and control circuitry and is shown in fig. 7.

Although the lack of gain at the intermediate frequency makes the possibility of adding agc a bit difficult, this simplified distribution does have its virtues. The main advantage is that product detection occurs at fairly low signal levels. This minimizes the noise modulation effects which often occur in product detectors. Another problem which is avoided is the effect of bfo leakage. Often, stray bfo energy finds its way into a high gain i-f amplifier, causing both intermodulation and noise modulation to occur. This is avoided in a system of this kind. The overall result is a receiver which sounds exceptionally crisp and clean, a virtue usually limited to direct-conversion

receivers and some well designed superhets.

transmitter mixer

Shown in fig. 5 is the transmitting mixer and carrier oscillator for the transceiver. Although it would be possible to replace the carrier oscillator with some energy from the bfo, this would necessitate the introduction of some offset of

Motorola chip is by far the more satisfactory and is easily applied.

Balance is maintained in the mixer by using a center-tapped tuned circuit in the output. This is realized by putting a bifilar winding of 15 turns on a toroid core and tuning the series combination. The required power-supply voltage is injected on the center tap and output is extracted from the tuned circuit with a

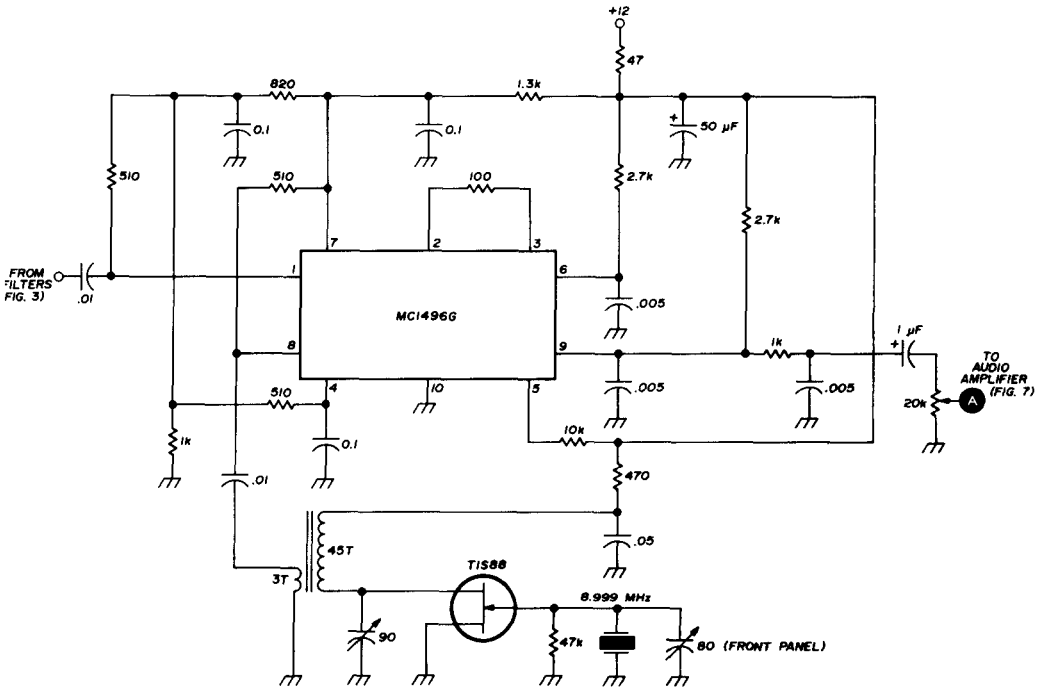


fig. 4. Product detector and bfo for the receiver used in the QRP transceiver. Transformer is wound on Amidon T-50-6 toroid or similar.

the main system vfo during transmit. The use of a separate crystal oscillator was considered to be the simpler solution.

The transmitting mixer itself uses another Motorola MC1496G doubly-balanced modulator IC. This chip is ideally suited for this application due to the excellent balance available. This significantly reduces the amplitudes of many of the spurious products in the output from those which would appear in the output of a single-ended mixer. I have also used the RCA CA3028A and diode rings in this application, although the

3-turn link. An alternate output network would be realized by shunt-feeding the MC1496G output collectors with rf chokes. Then, the high-impedance end of a tuned circuit could be lightly coupled to one of the output terminals. This method would have the advantage of being more easily bandswitched.

The input levels feeding the mixer IC are not extremely critical, although severe overdriving should be avoided since this will cause some deterioration in the rejection of spurious output products. In the mixer shown, the carrier port is driven

with a little over 0.5 volt, rms, and the signal port has about 200 millivolts of drive. During receive periods, the supply voltage is removed from the mixer/carrier-oscillator board.

transmitter power chain

The three-stage power amplifier which completes the transmitter is shown in fig. 7. The 2N3904 pre-driver and the

gain might be provided by a single stage. First, I have found that it is usually worthwhile to add an additional stage with a decreased gain-per-stage to insure stability. The cost increase is minimal, but the unconditional stability is quite assuring.

Class-A operation has the advantage of preserving linearity. This is somewhat important, even in a CW rig. In previous

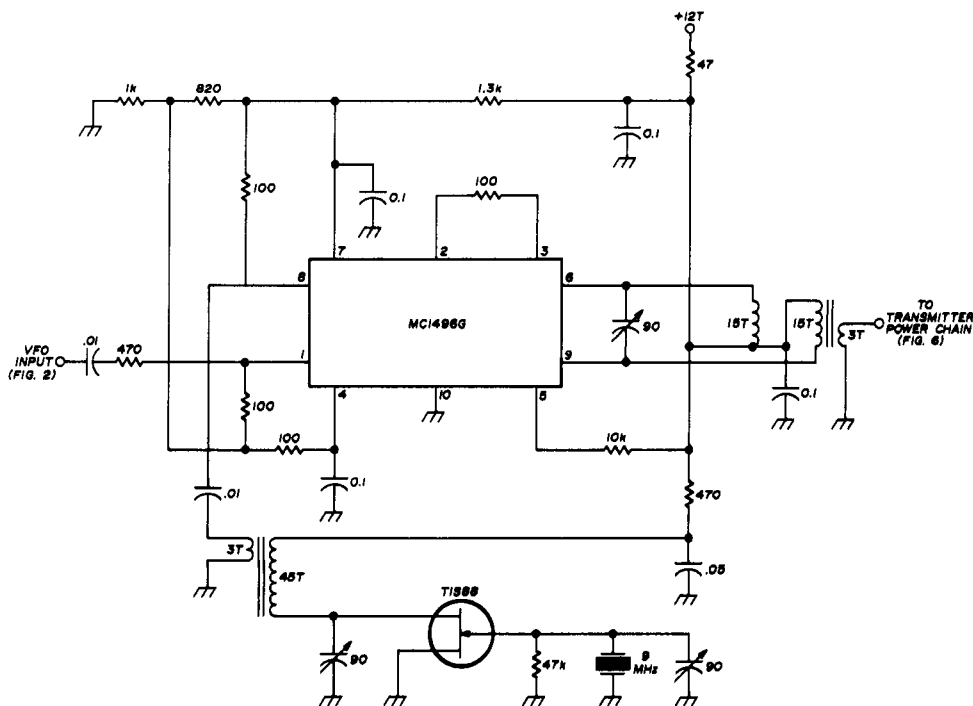


fig. 5. Transmit mixer and carrier-oscillator circuits. The frequency of the 9-MHz crystal oscillator is adjusted to the center of the 9-MHz I-f with the crystal filter (fig. 3) switched in. Transformers are wound on Amidon T-50-6 toroids or similar.

2N5859 driver are keyed. The final amplifier also uses a 2N5859. This Motorola TO-5 device is an excellent, general-purpose QRP device with a price tag of under one dollar. Since it has an f_T of around 250 MHz, it should be usable up as high as the six-meter band, with power output up to about two watts.

Both the pre-driver and the driver stages are operated as class-A amplifiers with emitter degeneration. There are a couple of reasons for this, even though sufficient

transmitters it was noted that the spurious components in the output would be increased if an amplifier was allowed to saturate. The reason is that saturation would occur for the primary driving frequency, but the amplifier would still behave in a fairly linear fashion for spurious products. The net effect was that much of the filtering prior to the amplifier was negated.

The bandwidth of the amplifier strip of fig. 6 is rather restricted. With the

system aligned at 14.065 MHz, the commonly used QRP frequency on 20 meters, the output was down by about 30 dB when the vfo was tuned to the middle of the phone band. Most of the output power could be obtained, however, by retuning the output of the pre-driver. If operation of the transmitter over the total 20-meter band is required, the builder should provide for front-panel

relaxation oscillator using a programmable unijunction transistor (PUT). The sawtooth output is attenuated and applied to the input of the audio amplifier. Transmitter keying is accomplished with a series switch using a 2N4036 silicon TO-5 transistor. Almost any silicon pnp device can be used in this slot.

In the circuits discussed above, the power supplies on the schematics have

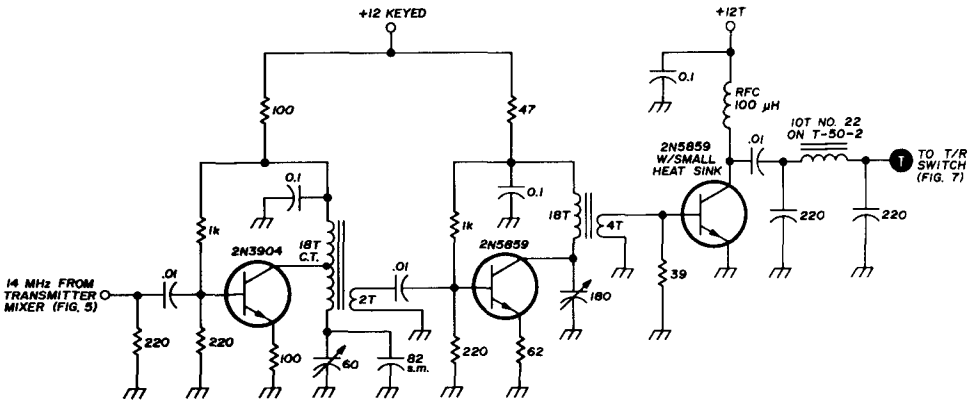


fig. 6. Transmitter power chain provides 1.5-watt output into a 50-ohm load.

adjustment of this tuned circuit. As shown, the system is flat over the CW portion of the band.

The output power of the transmitter was measured at 1.5 watt into a 50-ohm load. When the output of the transmitter board was investigated with a lab-quality spectrum analyzer, it was found that the second harmonic was down by only 27 dB. However, all other spurious outputs were over 60 dB down. Additional harmonic rejection is easily obtained with the half-wave filter at the transceiver antenna terminal. With two class-A stages being keyed, the backwave was more than 70 dB below the usual output.

control circuits

Shown in fig. 7 is the final board which completes the transceiver. This board contains not only the audio system mentioned earlier but the sidetone oscillator, a keying transistor and the T/R circuitry. The sidetone is obtained from a simple

been labeled as +12V, +12R or +12T. All circuits labeled with +12V have voltage applied at all times. However, those with the R or T suffix have power applied only during receive or transmit intervals, respectively. The two voltages are derived from the antenna relay, K1. I used a dpdt relay with an 800-ohm, 12-volt coil, with the second set of contacts switching the antenna.

You may have noted that the product detector has power applied at all times, even during transmit intervals. Initially, the detector was muted during transmit. However, an objectionable click appeared when the receiver came on again. This was the result of the large current surge in the 50- μ F decoupling capacitor used on the detector board.


The transmit-receiver logic is based upon a μ A741C operational amplifier IC used as a differential comparator. Under key-up conditions, the 2.2- μ F capacitor is fully charged. However, when the key is

closed, this capacitor is discharged. When this happens, the voltage on the inverting input of the op amp (pin 2) drops below half of the power supply potential. This causes the op amp output to switch to a high state, near the 12-volt supply, and saturates the 2N3904 relay driver. When the key is released again, the timing capacitor begins to charge toward the 12-volt supply through the 220-kilohm resistor. When the capacitor passes the

keyer. This keyer⁶ is based upon differential comparator logic similar to that used for the T/R control.

additional thoughts

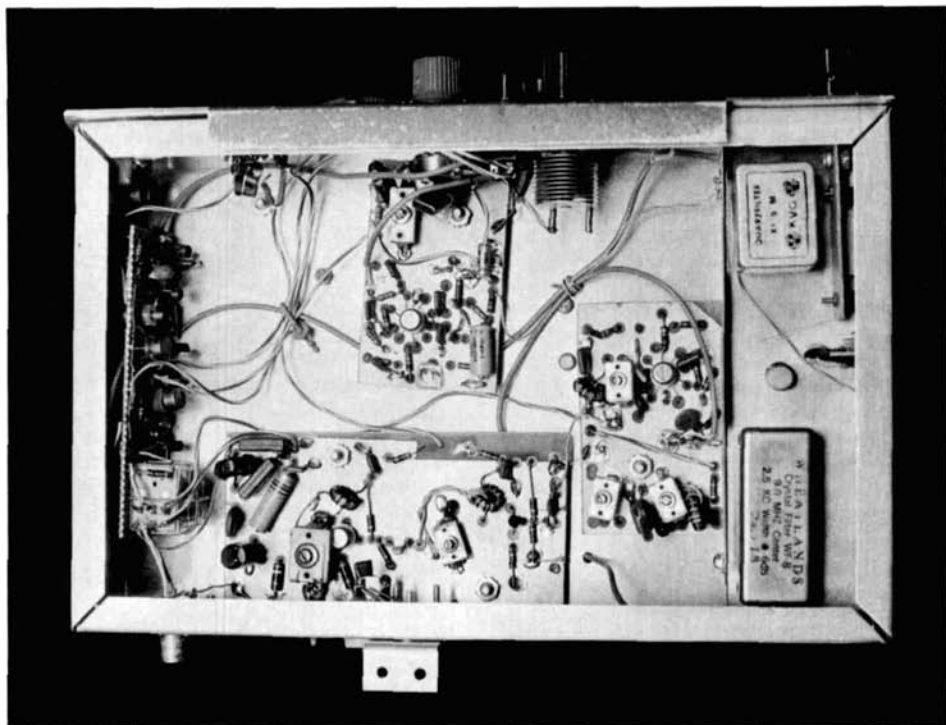The transceiver described and shown in the photographs was packaged in an LMB type CO-2 cabinet. The extra holes shown in the chassis are a reminder of an earlier receiver which resided in the same enclosure. Although there is an abundance



There's plenty of room under the chassis. Crystal filters are at right, next to transmit mixer and carrier oscillator. Transmit power chain is at bottom with control, keying and audio circuits to the left.

6-volt point, the op amp changes state again and the relay opens. The hold-in time can be varied from the 0.5 second I used by changing the 220-kilohm timing resistor.

There are two keying inputs shown. One is for the usual hand key. The other uses a *two-circuit* phone jack, with +12 volts available on the second pin to supply power to an external electronic

of extra room left, this will eventually be used for a variety of accessories, including equipment for at least one vhf band.

An obvious extension of this design would be the addition of other bands. Of the possible combinations, the easiest would be a 20- and 80-meter CW transceiver. The receiver can be made operative on 80 meters merely by switching the tuned circuits in the front end.

The transmitter mixer is moved to 80 meters by changing the output network in the transmitting mixer as described earlier. The output of the mixer should then be well filtered for the band in use. In this case, a lowpass filter would be suitable for 3.5 MHz with a bandpass filter being switched in for 14-MHz operation.

The transmitter power chain could be replaced with a broadband design with appropriate lowpass filters switched into

beyond the relatively simple systems considered in this article.

The performance of this transceiver has been more than satisfactory. Using only a ground-plane antenna, contacts have been made all over the United States and Canada as well as with VK, JA, UA0 and DM. While the unit does not represent the absolute ultimate in simplicity, the superior performance is well worth the minimal extra effort and expense.

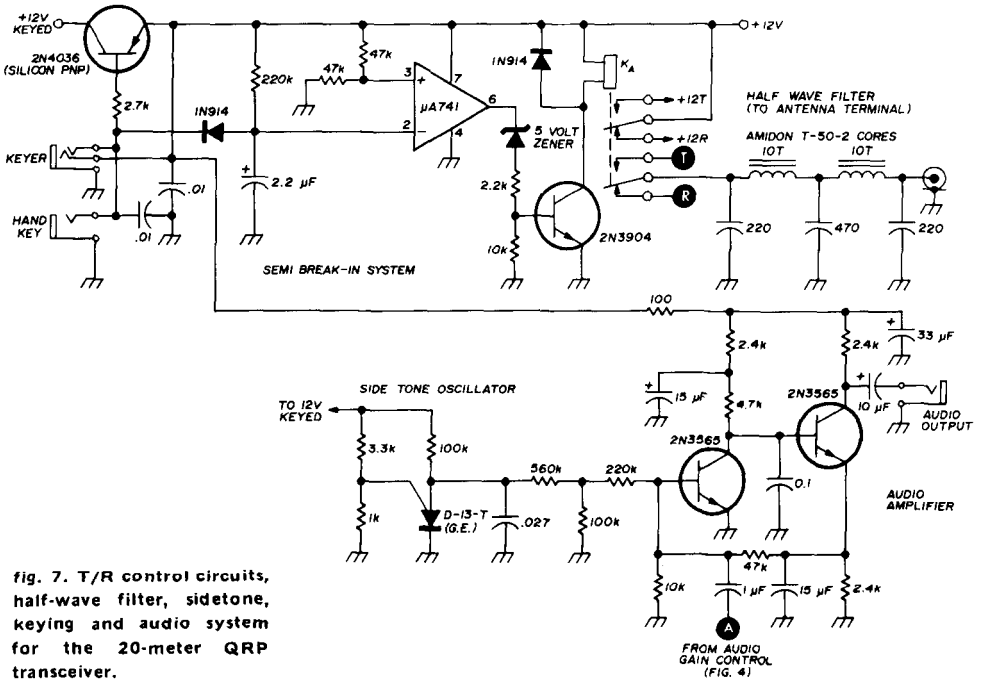


fig. 7. T/R control circuits, half-wave filter, sidetone, keying and audio system for the 20-meter QRP transceiver.

the output. If such an approach is taken, it is important that the filtering between the mixer and power amplifier be sufficient to provide an output free of spurious products. In most cases, a two- or three-section bandpass filter will do the job.

If bands other than 80 and 20 meters are considered, it will be necessary to derive other local-oscillator signals. This could be achieved either by band-switching the vfo or by premixing the existing 5-MHz signal. Other, more elaborate synthesis techniques would yield superb performance, but they go

references

1. Wes Hayward, W7ZOI, Terry White, K7TAU, "The Mountaineer," *QST*, August, 1973, page 23.
2. Wes Hayward, W7ZOI, "The Micromountaineer," *QST*, August, 1973, page 11.
3. Doug DeMaw, W1CER, "HW-7 QRP Transceiver Modifications," *QST*, January, 1974, page 35.
4. George Hanchett, W2YM, "The Field-Effect Transistor as a Stable VFO Element," *QST*, December, 1966, page 11.
5. Wes Hayward, W7ZOI, "A Second-Generation MOSFET Receiver," *QST*, December, 1970, page 11.
6. Wes Hayward, W7ZOI, "An Integrated-Circuit QRP Keyer," *QST*, November, 1971, page 38.

ham radio

scattering characteristics of artificial radio aurora

Artificial aurora,
created at will
by high-power,
high-frequency
transmitters,
may prove useful
for long-distance
vhf communications

The U.S. Department of Defense has recently disclosed that it is now possible for man to create his own artificial radio aurora (ARA) capable of scattering radio waves of frequencies up to 450 MHz. The ARA can be produced in either the ionospheric E- or F-regions over a source of very powerful high-frequency radio waves directed upwards. Don't, however, expect to see this "aurora." The optical effects of ionospheric modification are very weak, corresponding to less than a 30% change in the level of some characteristic lines in the night airglow spectrum.¹

Research has taken place at three sites. One,² near Platteville, Colorado, operated by the Institute for Telecommunications Sciences (ITS), uses a transmitting system with an effective radiated power of 40 megawatts. Two transmitting arrays are

used; one, for the frequency range 2.5 to 5 MHz is composed of five crossed dipoles, and the other, usable between 5 and 10 MHz, uses ten crossed dipoles. The crossed-dipole elements are fed in phase quadrature to produce circular polarization. It has been found that the ordinary magnetoionic component³ produced by right-hand circular polarization (in the northern hemisphere) produces the strongest ARA. The second ionospheric heating facility at Arecibo, Puerto Rico, operated by Cornell University, uses a transmitter with one tenth the power output and an antenna with 10 dB more gain (the 1000-foot dish). A third facility, located at Gorki, 400 km east of Moscow, USSR, uses a transmitter with 60-kW average power and 22-dB antenna gain.⁴

In the ionosphere, just below the reflection height, the high-frequency wave is retarded and energy is imparted to the electron gas, raising its temperature. It is forced to expand along the magnetic field lines, creating field-aligned ionization irregularities. Although the fractional change in ionization density through these irregularities may be only a percent or so, each irregularity scatters coherently. Many of these long, thin irregularities are capable of scattering high-frequency and vhf signals just as the natural aurora does. The primary differences as far as the radio amateur is concerned are that this is a very localized aurora, it may be turned on and off within seconds, and its height is determined by the frequency of the heating transmitter.

Since the scattering region is localized

Victor R. Frank, WB6KAP, Stanford Research Institute, Menlo Park, California 94025

and the Doppler spreading is not great, voice signals reflected by ARA are still intelligible although there is rapid and deep flutter fading.

A companion article appearing in *QST*⁵ this month describes ARA sounding and communications experiments and the directional properties of the scatterers. Since I will go into further detail here, it may be to the reader's advantage to read the *QST* article first.


F-region scatter observed

Soon after the announcement of the triggering of spread F by the Platteville facility,⁶ experimenters noted echoes on high-frequency sounding paths that were determined to be due to reflection from

that the scattered signal remained after turnoff of the heating transmitter varied with the frequency and with the scattering angle. The lower frequencies and the forward scatter paths had lower fading rates and were more persistent than higher frequencies and backscatter paths.

High-frequency soundings had indicated that even higher frequencies might be usable, so equipment for receiving TV video carriers was set up at another field site near Bakersfield, California. The receiving system used an array of eight commercial LPA antennas (fig. 2), crystal-controlled converters and narrow-band receivers with recording on chart and tape. Fig. 3 shows chart recordings of some of the signals observed while the

fig. 1. Field-strength recordings made in central California of the ITS ionospheric modification transmissions (A) and a transmission from Arkansas at a frequency above the direct path MOF (B).

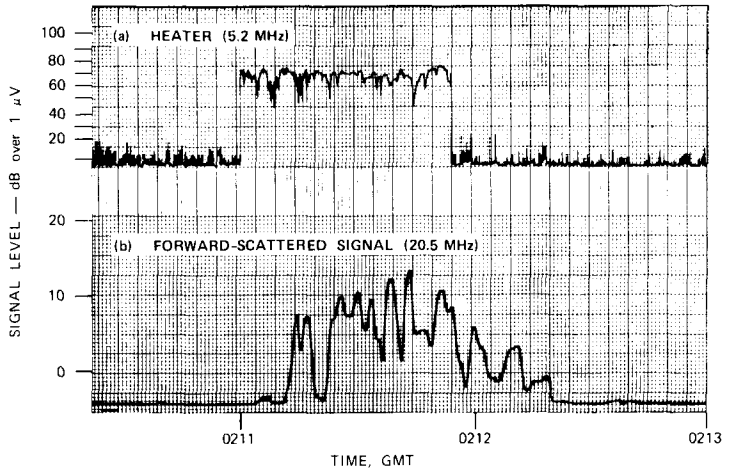

field-aligned irregularities from the F-region over Platteville. Fig. 1 shows a chart recording made in March, 1971, at an SRI field site in central California of experimental transmissions from a station in Arkansas. The frequency was chosen on the basis of oblique soundings to be a few MHz above the direct path MOF. A clear cause-and-effect relationship is shown, with the 20-MHz signal fading into the noise some 20 seconds after turnoff of the ionospheric modification transmitter. A-m voice modulation on this signal was quite readable.

The fading rate and the lengths of time

Platteville transmitter was being operated on a one-minute on, one-minute off cycle.

It is difficult to identify a television station solely on the basis of its video carrier frequency.* Signals were never strong enough to demodulate and, in addition, too much co-channel interference existed from stations in northern and southern California. Based on ray-

*In the United States, Canada and Mexico, vhf TV stations are assigned video carrier frequencies of either 1.24, 1.25 or 1.26 MHz above the lower edge of the channel. These are referred to as minus-, zero- or plus-offset, respectively.

tracing calculations, these TV signals are believed to have originated from stations in northern Mexico and southwest Texas.

E-region scatterer

One of the most recent developments in ionospheric modification has been the observation of artificial radio aurora in the E-region over Platteville, Colorado. This development was made possible by

110 km over Platteville, Colorado. (A similar picture for F-region reflectors is shown in the companion *QST* article.) Specular scattering may take place between stations located on intersections of supplementary cone angles (their sum equals 180°). These curves were derived for a single field-aligned scatterer. Actually, such scatterers are present in a scattering region of 100-km diameter and

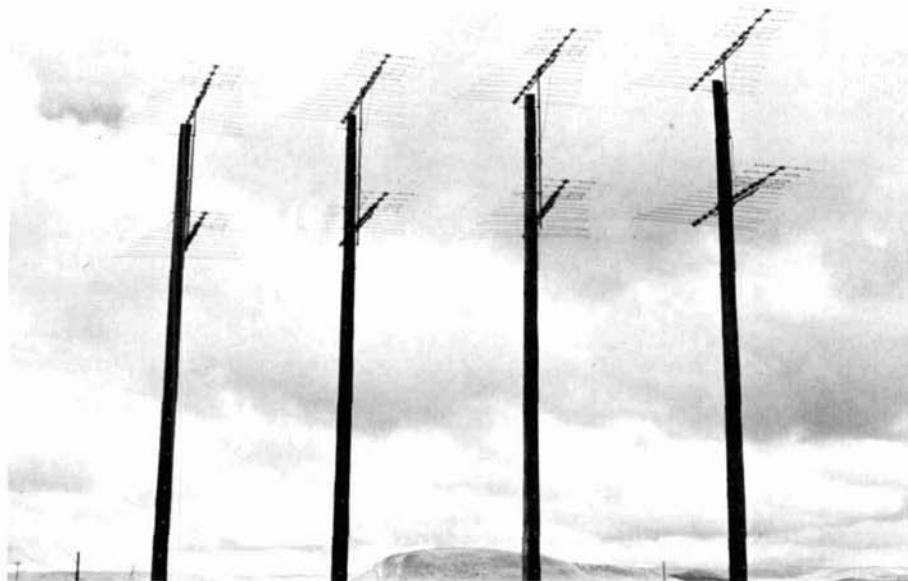


fig. 2. Array of log-periodic TV antennas used at site near Bakersfield, California, to monitor TV video carrier signals scattered by ARA.

the addition of five low-frequency crossed dipoles in an array at Platteville, which allowed operation at frequencies as low as 2.8 MHz. These frequencies are reflected from the E-layer during the daytime.

Actually, most amateur experience with natural field-aligned scattering is that from the E-region, since the aurora rarely penetrates far enough south for echoes to be obtained from the F-region. Fig. 4 shows the intersection with the earth of scattering cones of various angles to the magnetic field at a height of

10-km thickness. This distribution will spread the coverage by a similar distance. Soundings were made over a path from a transmitter site south of Albuquerque, New Mexico, to an ITS receiving site near Haswell, Colorado, where there is a 60-foot parabolic dish antenna (fig. 5). One of the sweep frequency soundings taken over this path, fig. 6, shows time delay, frequency coverage and radar cross section versus frequency. The sounding transmitter was turned off during those portions of the frequency sweep that fell within TV channels 4, 5 and 7.

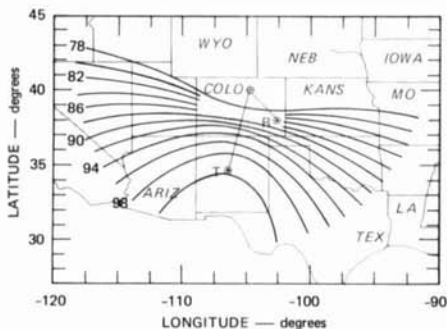


fig. 4. Contours of intersections with the earth of scattering cones from field-aligned scatterer at 110 km over Platteville, Colorado. Communication can be established between stations located on contours of supplementary aspect angles.

Radar cross section may be a new concept to some of you. It is here defined by the radar formula

$$\sigma = \frac{P_r (4\pi)^3 r_1^2 r_2^2}{P_t G_t G_r \lambda^2}$$

where P_t is the transmitted power output, P_r is the received power input, λ is the wavelength and r_1 and r_2 are the distances from transmitter and receiver to target, respectively, in meters, and G_t and G_r are the transmitting and receiving antenna power gains over an isotropic radiator. This value of received power, P_r ,

must compete with the noise power, P_n which is

$$P_n = FkTB$$

where F is the ratio of cosmic noise power to that produced by a termination (Johnson noise), k is Boltzmann's constant (1.38×10^{-23}), T is the absolute temperature in degrees Kelvin, and B is the receiver bandwidth in Hz. To spare the reader the exercise of going through the numbers, I have calculated the minimum detectable cross section for an amateur CW station in various amateur bands having the following characteristics:

P_t	=	500 watts
r_1	=	$r_2 = 10^6$ meters
B	=	100 Hz
P_r/P_n	=	1
G_t	=	$G_r = 10$ (10 dB) 28 MHz
		= 20 (13 dB) 50 MHz
		= 40 (16 dB) 144, 220 MHz
		= 60 (18 dB) 432 MHz

The minimum observable cross sections are about 10^3 to 10^4 square meters (30 dBsm to 40 dBsm). These are shown in fig. 7 along with the range of cross sections observed from the Platteville heated region under ideal conditions for both E- and F-region heating. You can see

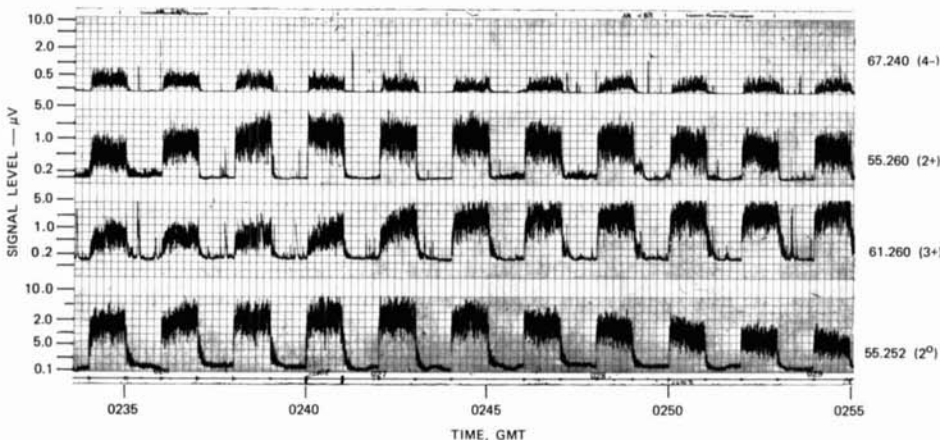


fig. 3. Field-strength recordings of TV signals received during 1-minute on, 1-minute off cycling of ionospheric modification transmitter.

that detection at 50 and 144 MHz is well within the capabilities of the advanced amateur station.

It is quite possible that some amateurs may have already communicated two-way via ARA without realizing they were doing so. During the last test series at Platteville, about 264 hours of heating

ionospheric modification at arecibo

Since the Arecibo heating antenna beam is narrower than that at Platteville, the expected cross sections are some 10 dB lower. Also, since Arecibo is not licensed at present for frequencies below 5 MHz, E-region heating is not possible

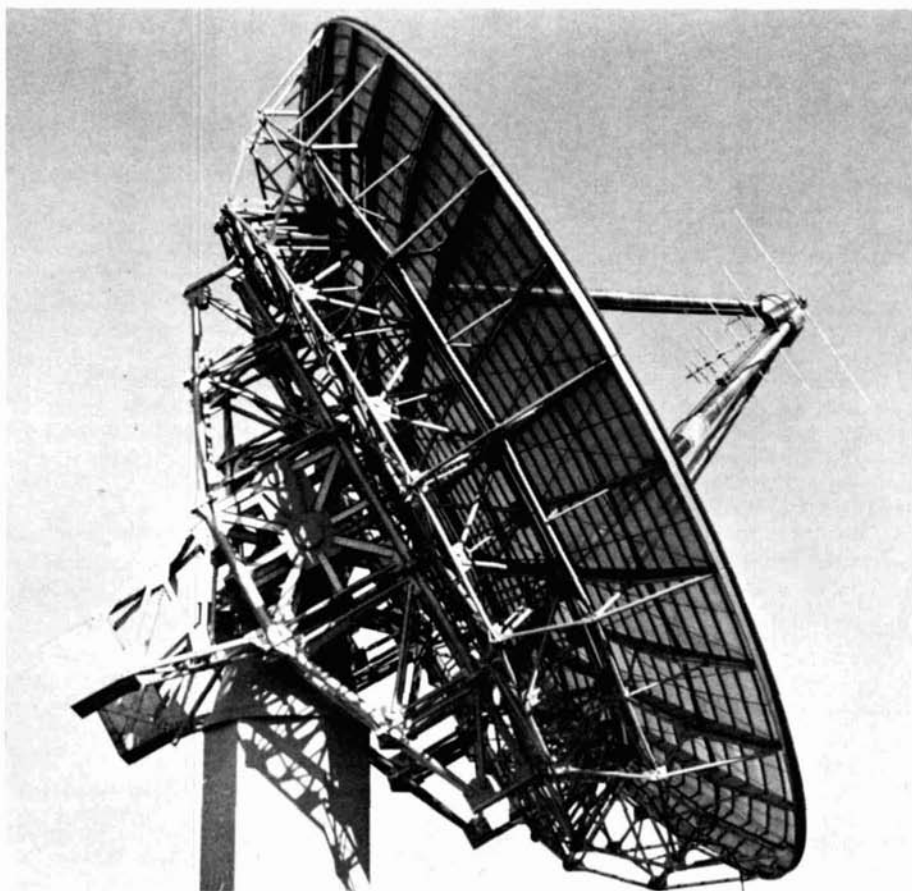


fig. 5. Sixty-foot dish and LPA feed at ITS field site near Haswell, Colorado.

experiments were conducted (between September 10 and November 2, 1973). Of these, 47 were in the prime evening time interval, 0000-0600 UT. It is hoped that radio amateurs will have a chance to participate in future tests presently scheduled for Platteville, Colorado, some time during the first half of 1975 and for Arecibo, Puerto Rico, during the first weeks of April, 1975.

and F-region heating is possible only during daylight and early evening hours. Fig. 8 shows a map of intersections with the earth of scattering cones from a field-aligned scatterer at 300-km height over Arecibo, Puerto Rico.

Most likely to benefit from Arecibo ARA are the Caribbean, Venezuela, Columbia and possibly Central America—areas with very little amateur vhf activity.

Perhaps some vhf DXpeditions would be in order. These are good areas, and April is a good time of year for transequatorial scatter.

other possibilities

If you are not fortunate enough to be in the ARA coverage areas of Platteville or Arecibo, do not despair. Much remains to be learned about what is really happening during ionospheric modification. There is another form of scattering caused by plasma and ion-acoustic waves^{7,8} which, though very weak, may be usable for stations within line-of-site of the ARA. Amateurs, being spread all over the country, are in a unique position to investigate paths not previously available to researchers.

In addition, much of what we have learned during these experiments will be of use to the radio amateur interested in scatter and auroral communication. Field-aligned ionization in nature? Yes, even at mid-latitudes, if you know how to look for it.⁹ Further information on coverage areas for scattering by the natural aurora may be found in an article by R.L. Leadbrand.¹⁰ I am convinced that the so-called *X-mode* (50-MHz signals back-scattered from sporadic E-patches) is due to field-aligned ionization in those patches.¹¹ And transequatorial propaga-

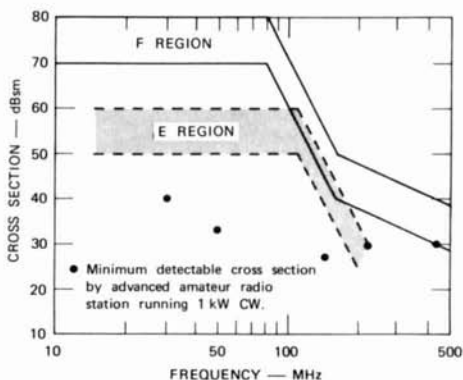


fig. 7. Radar cross-section of the Platteville ARA versus frequency for E- and F-layer echoes.

tion is also probably due to forward scattering from field-aligned irregularities in the equatorial F-region.¹² In addition, experimenters have found that meteor-trail debris becomes field-aligned.^{13,14}

Ranging capability, something lacking in most radio amateur stations, would prove invaluable in identifying these propagation modes. It is possible some may have been used for decades without proper identification. Ranging capability implies pulse or linear sweep-frequency CW operation, neither of which is in amateur use in the vhf bands. But here, perhaps, is an opportunity for the radio amateur to use some of those radar

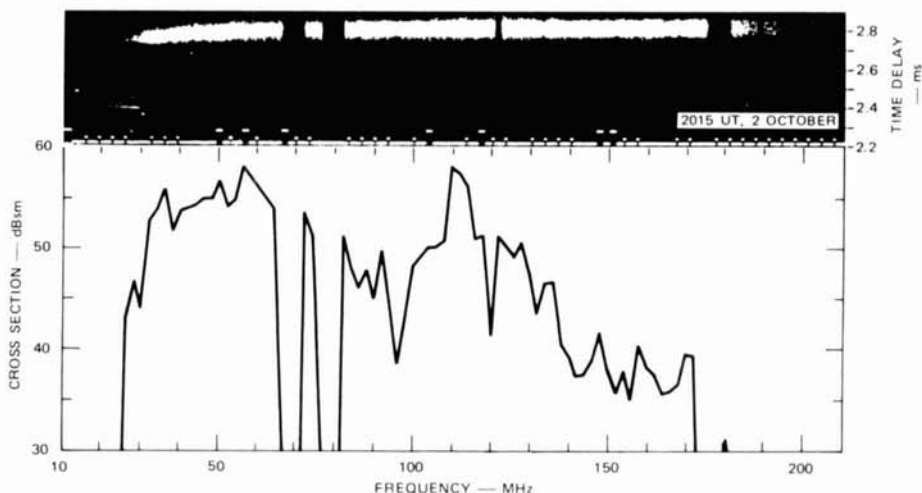


fig. 6. Sweep-frequency sounding received at Haswell, Colorado, showing echo from E-region ARA.

signals in the 220- and 420-MHz bands for scientific investigation.

acknowledgements

I wish to thank W.F. Utlaut and his associates at the Institute of Telecommunications Sciences, Boulder, Colorado, for their cooperation in the conduct of these experiments and for graciously allowing us to use their Haswell facility. Acknowledgment should also be made to the other organizations that were part of the team that explored the scattering properties of ARA. They are Raytheon Corporation, Sudbury, Massachusetts; Riverside Research Institute, New York City, New York; Barry Research, Palo Alto, California; and the Aeronomy Corporation, Champaign, Illinois. This research was sponsored by the Defense Advanced Research Projects Agency through the Office of Naval Research.

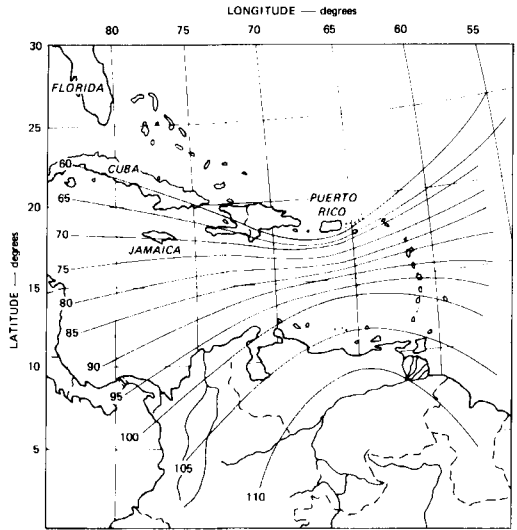


fig. 8. Contours of intersections with the earth of scattering cones from field-aligned scatterers at 300 km over Arecibo, Puerto Rico. The contour values are the angles between the cones and the geomagnetic field.

references

1. W.F. Utlaut and R. Cohen, "Modifying the Ionosphere with Intense Radio Waves," *Science*, 174, 15 October, 1971, page 245.
2. J. Fisk, "A Second Look," *ham radio*, December, 1971, page 4.
3. V.R. Frank, "Ionospheric Propagation," *ham radio*, August, 1969, page 58.
4. G.G. Getmantsev et al., "Some Results of Investigations of Nonlinear Phenomena in the F-Layer of the Ionosphere," *JETP Letters*, 18(10), 20 November, 1973, page 364 (Russian original: *ZhETF Pis'ma Red.*, Vol. 18, No. 10, 20 November, 1973, page 621).
5. V.R. Frank, R.B. Fenwick and O.G. Villard, Jr., "Communicating at VHF via 'Artificial Radio Aurora'," *QST*, November, 1974.
6. W.F. Utlaut, E.J. Violette and A.K. Paul, "Some Ionosonde Observations of Ionosphere Modification by Very High Power, High-Frequency Ground-Based Transmission," *Journal of Geophysical Research*, November, 1970, page 6429.
7. V.R. Frank, "Observations of Ion-Acoustic Wave Scattering over Long Oblique Paths," *Radio Science*, November, 1974.
8. H.C. Carlson, W.E. Gordon and R.L. Showen, "High-Frequency Induced Enhancements of the Incoherent Scatter Spectrum at Arecibo," *Journal of Geophysical Research*, March, 1972, page 1242.
9. A.M. Peterson, O.G. Villard, Jr., R.L. Leadbrand and P.B. Gallagher, "Regularly-Observable Aspect-Sensitive Radio Reflections from Ionization Aligned with the Earth's Magnetic Field and Located Within the Ionospheric Layers at Middle Latitudes," *Journal of Geophysical Research*, December, 1955, page 497.
10. R.L. Leadbrand and I. Yabroff, "The Geometry of Auroral Communications," *Trans. IRE on Antennas and Propagation*, AP-6, January, 1958, page 80.
11. S. Basu, R.L. Vesprini and J. Aarons, "Field-Aligned Ionospheric E-Region Irregularities and Sporadic E," *Radio Science*, March, 1973, page 235.
12. I. Kuriki, K. Tanohata, T. Sakamoto and M. Iguchi, "Propagational Mode Deducted from Signal Strengths in the VHF Band on the Trans-Equatorial Path," *Journal of the Radio Research Laboratories*, 19, 100, 1972, page 175.
13. J.L. Heritage, S. Weisbrod and W.J. Fay, "Evidence for a 200-Megacycles per Second Ionospheric Forward Scatter Mode Associated with the Earth's Magnetic Field," *Journal of Geophysical Research*, September, 1959, page 1235.
14. J.L. Heritage, S. Weisbrod and W.J. Fay, "Experimental Studies of Meteor Echoes at 200 Mc," *IRE Transactions on Antennas and Propagation*, AP-8, January, 1960, page 57.

ham radio

Savoy

BASSETT

High efficiency mobile and portable antennas for all amateur bands, 160M, 80M, 40M, 20M, 15M, 10M, 6M, 2M, CB, SECURITY, PUBLIC SERVICE, MARINE, AND GOVERNMENT USE.

2-6-10-15-20-40-75

Identical size, cost, and appearance

FULLY ADJUSTABLE TO FREQUENCY IN FIELD

Low weight, low drag, high strength fiberglass

Polished chrome brass standard 3/8-24 thread

High gain collinear on 2 meters

MODEL DGA-2M

\$29.50 postpaid

in U.S.A.



\$3.75
Postpaid in U.S.A.
TYPE 900 A TYPE 901



HIGH ACCURACY CRYSTALS FOR OVER 30 YEARS

Either type for amateur VHF in Regency, Swan, Standard, Drake, Varitronics, Tempo, Yaesu, Galaxy, Trio, Sonar, Clegg, SBE, Genave.

Quotes on request for amateur or commercial crystals for use in all other equipments.

Specify crystal type, frequency, make of equipment and whether transmit or receive when ordering.



BASSETT VACUUM TRAP ANTENNA SYSTEM
Complete packaged multi-band antenna systems employing the famous Bassett Sealed Resonators and Balun from which air has been removed and replaced with pure helium at one atmosphere. Operating bands are indicated by model designation.

MODEL DGA-4075 . . . \$59.50
MODEL DGA-204075 . . \$79.50
MODEL DGA-2040 . . . \$59.50
MODEL DGA-152040 . . \$79.50

BASSETT VACUUM BALUN



The famous sealed helium filled Balun . . . employed with the DGA Series Antenna Systems. Solderless center insulator and easily handles more than full legal power while reducing unwanted coax radiation. Equipped with a special SO-239 type coax connector and available either 1:1 or 4:1.
MODEL DGA-2000-B . . . \$12.95
Postpaid in U.S.A.


CONTACT YOUR DISTRIBUTOR OR WRITE FOR DATA

Savoy Electronics, Inc.

P.O. Box 5727 - Fort Lauderdale, Florida - 33310

Tel: 305-563-1333 or 305-947-9925



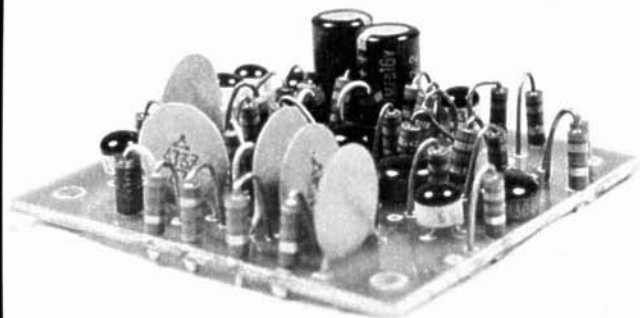

improved channel scanner

for vhf fm

A complete
four-channel
vhf fm scanner
that can be built
for ten dollars

If someone were to tell you that an integrated-circuit receiver scanner could be improved by redesigning it with discrete components, you'd say they were crazy! But, forced with difficulties in obtaining TTL logic elements for the K2LZG scanner kit,¹ and having previous experience in simplifying communications circuitry by eliminating ICs, I redesigned the scanner circuit with discrete components. This produced many unexpected side benefits.

The scanner built with discrete components (fig. 1) offers the following advantages, in addition to availability and cost of components.

1. Simpler type of readout.
2. Ease of maintenance — troubleshooting is easier with discrete components and spare parts are no problem (almost any silicon transistors provide proper operation).
3. Unit operates directly from a 10- to 15-volt power supply. IC version requires a 5-volt regulator.
4. Less current drain — about 8 times less than the IC version with regulator.
5. Smaller — PC board layout is one-quarter to one-third the size of the IC version. Actual size of board is 2x2-1/8 inches (51x54 mm). This is primarily due to the flexibility of discrete components in crossover-free, small area layout.
6. Flexibility of design — unit can be adapted easily for less than the full four channels without having to skip channels between the active ones. The unit is also adaptable to any desired scan rate with a simple component change.

Jerry Vogt, WA2GCF, 182 Belmont Road, Rochester, New York 14612

The new design also takes into account several variable factors which you may run into when applying the scanner to your particular receiver. The unit can be used with either positive or negative logic from your squelch circuit. That is, scanning can be stopped with either a positive or ground signal. The input circuit is very sensitive; therefore, almost any voltage,

theory of operation

Transistors Q3 and Q4 form an astable multivibrator, operating at a pulse repetition rate of approximately 10 pulses per second. Transistor Q2 turns *on* to stop the multivibrator when Q2's base is *high*. Q2 does this by shorting the base of Q4 to ground. Normally, squelch circuits have a *high* output available when closed

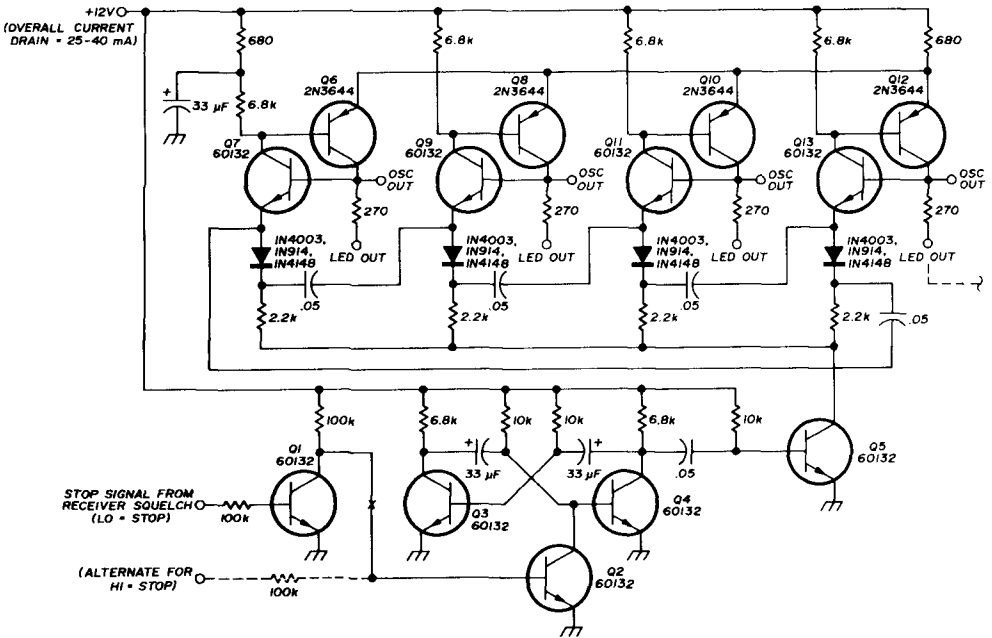


fig. 1. Schematic diagram of the improved fm receiver scanner. Additional channels may be added by connecting additional ring-counter stages, as discussed in the text.

typical test voltages, volts (ground reference)

Q1 collector	0.6/0
Q3/Q4 base	0/0.6
Q3/Q4 collector	0/12
Q5 base	0.6
Q5 collector	0.1
Q6/Q8/Q10/Q12 base	12/4
Q6/Q8/Q10/Q12 collector	0/5
Q7/Q9/Q11/Q13 emitter	0/3.8

from a few volts up, may be used to operate the scan-stop circuit. The unit normally puts out +5 volts to turn on (*enable*) the oscillator. However, simple additional inverter transistors used with the oscillator turn-on circuits allow the scanner to operate with oscillator circuits requiring a ground signal to *enable*.

and a *low* output when open. Therefore, inverter Q1 is used to provide the proper polarity signal to operate Q2. Transistor Q1 is tied to the collector of the squelch switch stage in the receiver through a 100k isolation resistor to turn on Q1 when the squelch is closed. When the squelch is open, Q1 is turned *off*, Q2 is turned *on*, and Q4 is locked *off*. This stops the sequencing action of the scanner. For those squelch circuits operating in the opposite sense, the alternate circuit connections shown on the schematic may be used. Transistor Q1 is deleted, and Q2's base is operated directly from the receiver.

Transistors Q6 to Q13 form a four-stage ring counter. Normally each stage is turned off by the base-emitter biasing on the pnp transistor. When power is first applied, the 33- μ F capacitor in the biasing circuit for the base of Q6 ensures that the first stage will turn on by momentarily upsetting the normal bias. Subsequent-

put of one ring counter stage *high* until the squelch circuit closes.

The collector of the pnp transistor in each stage provides a +5 volt output directly to the oscillator to be enabled and also through a 270-ohm current-limiting resistor to the LED readout corresponding to the enabled channel. It is important to note that the 270-ohm resistor in each stage must be connected to the LED for proper biasing to be maintained. If LEDs are not used, adjustments in the circuit or dummy resistor loads must be used to maintain the same current flow in other parts of each ring-counter stage.

The outputs of the scanner can be used to turn on oscillators in various ways, depending on the particular oscillator. Since this subject has been treated in several magazine articles,^{1,2} only a few examples will be given. Refer to fig. 2 for examples of two common types of oscillators which may be encountered. The examples illustrate, in general, how oscillators may be enabled by the scanner.

The first circuit (fig. 2A) shows a typical +5 volt turn-on type of oscillator. This circuit is used in a vhf fm receiver described in a previous article.³ The oscillator has no internal bias; therefore, it cannot oscillate by itself. The base of the transistor, connected through a coil to the crystal and to the *enable* line through a resistor and 0.01- μ F bypass capacitor, is biased on by +5 volts from an external source. The resistor and bypass capacitor block the flow of rf on the control line. Application of approximately +5 volts from a scanner circuit to the control line will turn the desired oscillator on.

The second circuit (fig. 2B) shows a conventional oscillator circuit adapted to multichannel operation by using diode switching. This circuit was commonly used a few years ago to modify older tube-type equipment for multichannel operation. In this circuit the crystal is essentially turned on at appropriate times by grounding the corresponding control line. In this case each leg is turned *on* when desired by a *ground* from an added

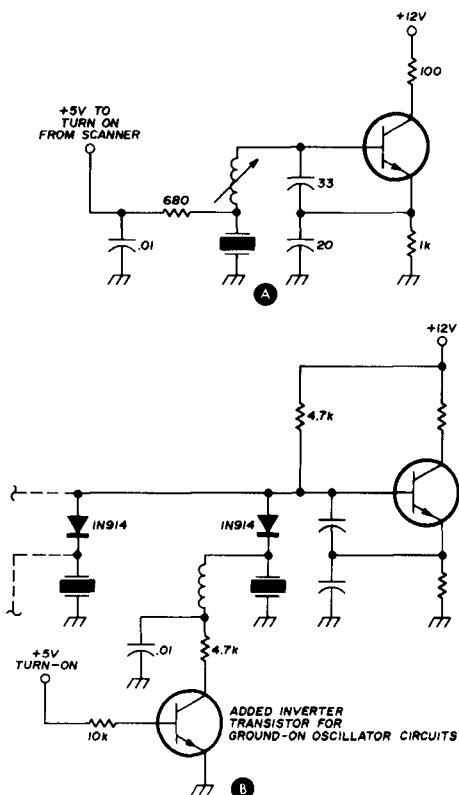


fig. 2. The receiver scanner shown in fig. 1 may be used with oscillators that require +5 volts for turn-on (A), or for oscillators requiring a ground for turn-on (B).

ly, due to the return for ring counter stages being pulsed by Q5, the *high* output is passed from one stage to the next in an endless ring pattern. Normally Q5 is turned *on* hard to ground, and it is pulsed to a *high* condition for a short pulse duration each time a negative-going pulse is received from the multivibrator. When the pulsating action ceases due to operation of the squelch circuit, the ring counter stops stepping, holding the out-

inverter transistor which turns *on* when +5 volts is applied to its base from the scanner through an isolation resistor.

It can be seen from these examples and the referenced articles that almost any fm transceiver or receiver can be modified to provide scanning operation. Application of one or more of the ideas

instead of the next stage. This effectively shortens the ring. The Q6/Q7 stage must always be used since the bias circuit for the base of Q6 includes a capacitor and resistor which ensure that the ring counter operates when power is first applied. On the PC board shown in fig. 3 this is best done by reconnecting the last

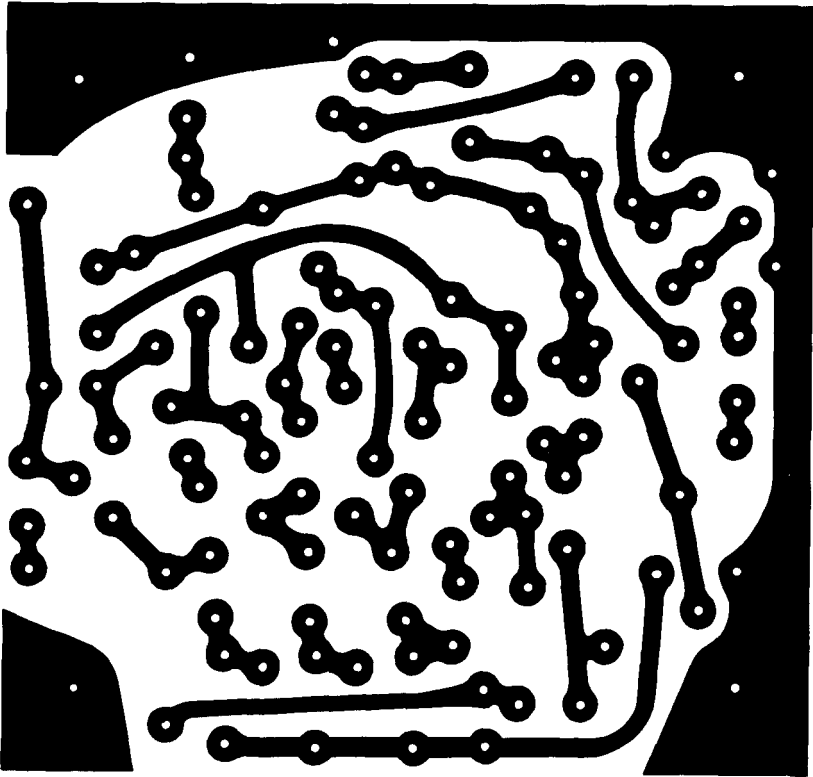


fig. 3. Printed-circuit layout for the improved fm receiver scanner. Component layout is shown in fig. 4.

illustrated can be used to convert almost any oscillator circuit.

scanner circuit modifications

There are at least four possible modifications which may be of interest to other system requirements, if necessary.

1. **Less than four-channel scan.** This may easily be accomplished by reconnecting the 0.05- μ F capacitor at the bottom of the last ring-counter stage to be used. It should be rewired to the first stage

0.05- μ F capacitor to the line along the bottom of the board running back to the first stage.

2. **Changing scan speed.** The speed was set up to be the optimum compromise between proper squelch triggering and ability to catch short transmissions. If the approximate 10 channel/second rate requires change for some reason, different values for the two 33- μ F capacitors in the multivibrator will change the oscillation rate of that stage.

3. Increasing number of channels. If you can stand the confusion of scanning more than four channels, more than one board may be used. Link the ring counter stages on the two (or more) boards, and use only the triggering and timing circuits of the first board.

4. Programming channels. Switching schemes can be used between the scanner

pads darkened in on the layout drawing, **fig. 4**, and the top leads are looped back down to the pads which are circled. Polarity should be observed on the diodes and electrolytic capacitors. Install the 2N3644 transistors first to avoid any mixup later with the 60132 (general purpose npn) transistors.

Pads which are circled and have an X in them are inputs and outputs and will

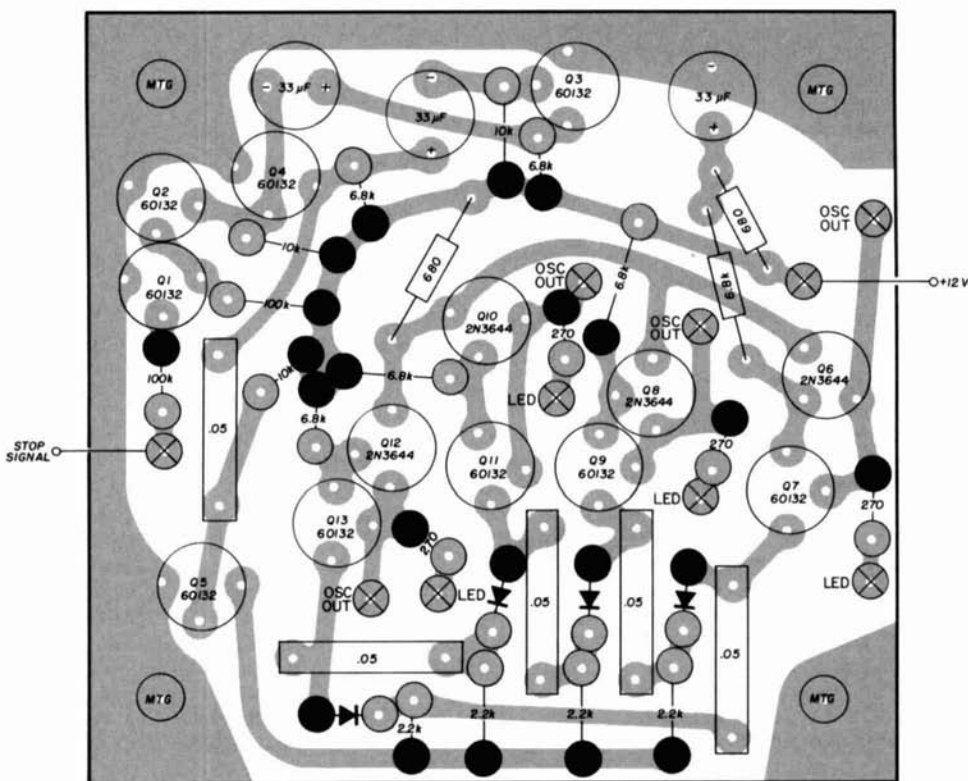


fig. 4. Component layout for the improved fm receiver scanner. Dark circles indicate bottom of resistors (or diodes) installed in vertical position; the other lead is looped over to the open circle.

outputs and the various oscillators to disable one or more channels at certain times or to select particular channels to be monitored out of a bank of the available channels.

construction

Assembly is straightforward. If the etched circuit board shown in **fig. 3** is used, most of the resistors and all of the diodes are installed standing up on the

accept wire such as number-22 hookup wire, for connections to the outside world. The +12-volt terminal should be connected to a source of filtered +10 to +15 Vdc. The input terminal should be connected to the collector of the receiver's squelch switch stage. If the alternate input is used, Q1 and the 100k resistor from +12 volts to the base of Q2 can be eliminated and the 100k resistor from the input terminal can be connected

directly to the base of Q2. The oscillator outputs should be connected to individual oscillator stages, and the LED outputs should be connected to the anodes of the LEDs.

The cathodes of the LEDs should be connected to ground. Using the type of LED supplied in the kit,* the orange dot on the base indicates the cathode terminal. Be sure you observe polarity or the LED won't illuminate. The LEDs supplied with the kit may be mounted by inserting them in 13/64-inch (5-mm) holes drilled in the front panel of the radio. A spot or two of epoxy cement on the base of each LED behind the panel should hold them in place. Alternate LEDs sometimes have one short lead to indicate the cathode. Likewise, alternate 1N4148 diodes used in ring counters have their cathodes identified by a shorter lead.

If you wish to use both the scanner and a regular channel switch, this may be done by first connecting the oscillators to operate with the scanner and then wiring up a rotary channel switch to supply +5 volts to select oscillators when the scanner is turned off. A five-position switch can be used for this purpose with the fifth position turning on the scanner. In positions 1 through 4, the scanner is turned off, and +5 volts is connected through the switch to the oscillators corresponding to the selected channel positions on the switch.

references

1. Bob Reifsteck, K2ZLG, "VHF Receiver Scanner," *ham radio*, February, 1973, page 22.
2. George Allen, W2FPP, "VHF FM Channel Scanner," *ham radio*, August, 1971, page 29.
3. Jerry Vogt, WA2GCF, "VHF FM Receiver," *ham radio*, November, 1972, page 6.

ham radio

*In conjunction with this article a kit is available, complete with undrilled G-10 PC board, all components, the LED indicators and an instruction manual. Price of the kit is \$10, including domestic parcel post. If desired, add 50¢ for a number-66 drill bit or 40¢ for air-mail delivery. To order, or to obtain information on other fm kits, write to Hamtronics, Inc., 182 Belmont Road, Rochester, New York 14612.

DATA SIGNAL

the latest in station accessories

AUDIO AUTOMATIC GAIN CONTROL AMPLIFIER

Is your tone decoder having problems due to input signal variations? If so, eliminate these and other problems caused by weak, strong or varying input signals. The AAGC-1 will take signal levels between 50 mV to 5 Volts and feed a clean rock stable signal to any decoder for perfect operation. Give your decoder a chance to decode properly with our AAGC-1 amplifier.

Shipping Weight 3 oz. **\$14.95 kit**
\$19.95 wired

DELUXE RECEIVER PREAMPS

Specially made for both OLD and NEW receivers. The smallest and most powerful single and dual stage preamps available. Bring in the weakest signals with a Data Preamp. Now with improved FET's for greater performance.

BAND	STAGES	GAIN	NOISE FIGURE	KIT PRICE	WIRED PRICE
10 meter	Single	25 dB	2 dB	\$15.50	\$18.50
6 meter	Single	25 dB	2 dB	\$15.50	\$18.50
2 meter	Single	20 dB	2.5 dB	\$15.50	\$18.50
2 meter	Double	40 dB	2.5 dB	\$30.50	\$36.50
220 MHz	Single	17 dB	2.5 dB	\$15.50	\$18.50
220 MHz	Double	35 dB	2.5 dB	\$30.50	\$36.50

CRICKET 1 ELECTRONIC KEYS

A popularly-priced IC keyer with more features for your dollar. Cricket 1 is small in size and designed for the beginner as well as the most advanced operator. It provides fatigue-free sending and its clean, crisp CW allows for easy copying at all speeds. Turned on its side, the Cricket can be used as a straight key for manual keying. Right or left hand operation. AC/DC.

Shipping Weight 3 lbs. **\$49.95**

OTHER EXCITING PRODUCTS INCLUDE

TOUCHTONE TO ROTARY CONVERTER
TOUCHTONE TO TOUCHTONE CONVERTER
TOUCHTONE PADS
AUTOMATIC DIALER
ANTI-FALSING TOUCHTONE DECODER
AGC AMPLIFIER

Write today for complete details

Data Signal, Inc.

Successor to Data Engineering, Inc.

2212 Palmyra Road

Albany, Ga. 31701

912-435-1764

how to measure peak envelope power

Don't depend
on your meters
for *accurate* measurement
of PEP input power —
use the technique
discussed here

It's unfortunate that the FCC requires amateur radio stations to compute power input for logging purposes. This is simple for fm or CW or even the almost-obsolete "conventional a-m" (6A3). For the user of single sideband (3A3J), however, the undertaking is far from simple. The purpose of this article is to identify those aspects that contribute to the difficulty of measurement and to present methods whereby the measurement may be made with a reasonable degree of accuracy.

Because the input power to an ssb transmitter continually varies when transmitting voice signals, custom and law stipulates that peak input power must be that which is measured. How do you catch that fleeting, almost ethereal peak of power induced by the upper excursion

of a complex waveform? No meter can follow it without unpredictable lag or overshoot. Even if it could, what eye could register a needle flick of less than a thousandth of a second? Being knowledgeable of the instantaneous plate current, assuming you're using a vacuum tube in the metered stage, is, by itself, a formidable undertaking. But power computation also requires knowledge of instantaneous plate voltage. Unless the transmitter's power supply has superb dynamic regulation, far better than you have any right to assume, you're faced with another (but not quite so formidable) task of super-quick information gathering.

We've coasted along for years with the possibly-right, probably-wrong assumption that the peak needle excursion of a plate current meter equals one-half of the actual peak current. The FCC gives a quasi blessing to this assumption by accepting it, but only if the meter is that supplied by the original equipment manufacturer. It's highly doubtful that any FCC engineer has illusions regarding the accuracy of this method of ascertaining peak plate current. It's accepted only because not accepting it would rule off nearly every ssb transmitter in the Amateur Radio Service.

Unless the input power is within 10% of the maximum permitted, the FCC will also accept the nominal *rated* voltage of the plate power supply.

Now, let's review what we have for making our educated guess as to the peak

Carl Drumeller, W5JJ, 5824 NW 58 Street, Warr Acres, Oklahoma 73122

input power of a voice-modulated ssb transmitter:

1. A plate meter indication that is dependent upon the dampening characteristics of the meter as well as upon the voice characteristics of the speaker. These voice characteristics vary not only from person to person, but also as to type of speech used by the individual. If you talk close to the microphone, with the gain turned up, using a monotone normal to confidential conversation, the meter will give one type of deflection. On the other hand, if you're back from the microphone, talking in a quick, excited tone, the deflection will be quite different for a given *peak* excursion.

2. The plate voltage may be measured, or it may be taken from the manufacturer's specifications. If measured, it may have been under *no load* condition. If under loaded conditions, the fall-off under syllabic current loads may possibly be gradual enough to be read on the voltmeter. Unless a huge filter capacitor is used, it's probable that voice-peaks markedly load down the voltage.

The probabilities of truly accurate measurement of peak input power are about the same as those of rolling a seven ten times running at a Las Vegas gambling table! How, then, can you make an accurate measurement?

Assuming, for a start, that you have a child-like trust in the utter trueness of the stated plate voltage, I'll delve into the matter of plate current measurement. Let's hope your transmitter permits an easy access to its negative high-voltage lead so that this lead may be broken for the insertion of a small resistor. Otherwise you'll need, in addition to the normal equipment, an isolation transformer (good for quite high voltage), a well-insulated oscilloscope cart and the type of constitution that permits playing Russian roulette!

But let's say your transmitter is metered in the negative lead, as are most modern designs. You break the lead at a point that does not present any uninten-

tional shunt paths, insert a resistor of a few ohms, connect an oscilloscope across this resistor, and then calibrate the scope in terms of current. It's best to use a scope with a long-persistence CRT. This lets you take a deliberate view of a trace that flicks across the face in less than a thousandth of a second. Now, as you speak into the microphone, you'll be able to see the maximum current drawn, reading it off the calibrated oscilloscope graticule.

For a better idea of your peak input power (if you can scrape up another scope), you can build a resistive voltage divider across the output of your power supply, tapping off a little potential for your scope input. Here, again, you have a simple calibration job to do. With two measuring devices which are not burdened by inertia and yet hold a reading (peak for current, dip for voltage) long enough to permit accurate observation, you're all set to read peak input power. (Provided that you're using a common-cathode triode operating in class A or class AB1.)

Have you noticed the way the FCC is currently grading its operator examinations? Power input to a vacuum tube no longer is measured by just its plate power input. You must also consider the power fed into the screen grid (if used), the suppressor grid (if used) and the control grid! That last is rf power. The others are dc, of course.

Most high-power rf amplifiers use common-grid triode vacuum tubes (also called grounded-grid). If yours does, coming up with the total power input is comparatively easy. All you need to do is to first measure the vswr on the line between the exciter and final. Make it unity. Then measure the instantaneous rf voltage on it with another calibrated oscilloscope. Compute the rf power by E^2/R , where R is the cable impedance. Add this power to the measured dc input power, and you should have fully satisfied all the requirements for ascertaining the peak input power of your ssb transmitter!

ham radio

how to predict harmonic output

Determining
drive points
for optimum
harmonic
generation

Why are certain oscillator circuits better suited for frequency doubling than others? Why are other circuits more suitable for frequency tripling? Questions like these have bothered many amateurs and experimenters. It is the aim of this article to shed some light on the subject of the harmonic content of some common non-sinusoidal waveforms.

A signal of pure sine waves contains only its fundamental frequency. Any departure from this sine-wave pattern, no matter how small, is due to the presence of additional frequencies that are multiples (harmonics) of the fundamental frequency. If this non-sinusoidal wave can be given an exact mathematical description, the amplitude and phase of each harmonic frequency it contains may be calculated.

analysis

For example, assume that we have a series of waves, all alike, each looking like that pictured in fig. 1. This is a sine wave

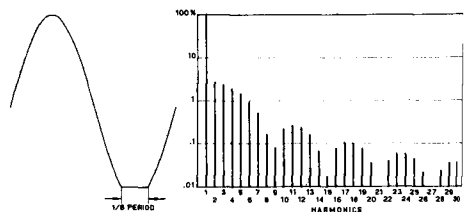


fig. 1. Sine wave with a small amount of negative peak clipping. Graph shows relative amplitudes of the resulting harmonic products.

Fin K. L. Utne, Fjellvn. 7, 1800 Askim, Norway

with the tip of the lower loop sliced off. Such a waveform might be produced when an amplifier is driven slightly beyond the cutoff point.

A Fourier analysis will show that this deformation of the sine wave gives rise to an endless number of harmonics, with amplitudes that tend to decrease with growing frequency. However, this tendency is not uniform.

The chart in fig. 1 illustrates the relative amplitude of each harmonic frequency up to the 30th. The scale is logarithmic, and the columns show the amplitudes of the harmonics as a percent of the original waveform's amplitude.

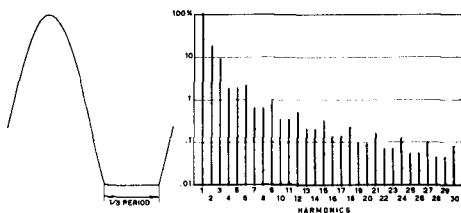


fig. 2. Harmonics generated when the lower portion of a sine wave is sliced off for one-third of the period. Maximum harmonic output occurs at harmonics which are third multiples (3, 6, 9, etc.) of the fundamental frequency.

As mentioned before, the general trend is for the amplitude to decrease with increasing harmonic number, but this tendency is not uniform. A curve joining the tops of the relative amplitude columns makes a kind of wave pattern of its own, with minimum values at the 9th, 15th, 21st, and 27th harmonics.

Fig. 2 shows the situation when a still larger portion of the lower half of a sine wave is sliced off. In this case it would seem that an amplifier is driven into cutoff for a third of the duration of a period. In this case harmonic content is maximum for every harmonic divisible by three. Peculiarly, the two intervening harmonics have amplitudes of equal magnitude.

Another point worth noting is that the fundamental frequency (or the first harmonic) has an amplitude about 7% larger

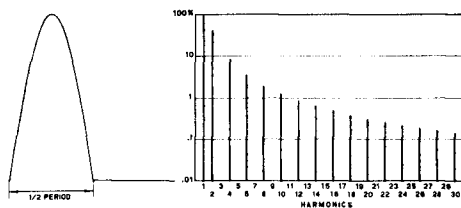


fig. 3. Sine wave with entire negative portion clipped off (rectified half-wave). Note that odd-order harmonics are eliminated entirely.

than the original deformed sine curve. What a temptation to drive an amplifier just a trifle over saturation, to get that little extra gain at the fundamental frequency! Actually, for this series of idealized waveforms the fundamental frequency increases to a maximum of 107.305% when the portion of the sliced-off sine wave represents 31.9% of the period.

half sine waves

Fig. 3 shows the case where the lower excursion of the sine wave has been clipped off entirely—a rectified half wave. Note that every harmonic with an uneven number has disappeared. The fundamental frequency has an amplitude equal to the actual amplitude of the half wave.

Fig. 4 shows a sine wave sliced off even more, so that only a third of the period is left. The envelope over the harmonic columns shows a pattern much like fig. 2, but the fundamental frequency has an amplitude of only 78% of the curve's amplitude. The higher harmonics, though, have larger amplitudes than those of fig. 2.

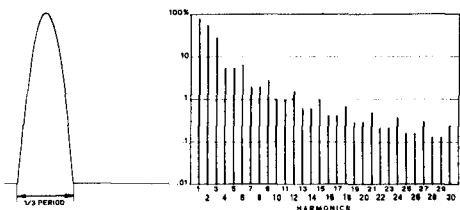


fig. 4. Raising the clipping point above the zero-crossing point sharply increases harmonic output. Note resemblance of this spectrum to that of fig. 2.

In fig. 5 the sine wave is sliced off so much that only one-sixth of the period remains. The fundamental frequency has an amplitude of only 43% of the curve but the harmonics are quite prominent. As in fig. 1, the envelope over the harmonic amplitude columns shows a wave pattern with minima at the 9th, 15th, 21st and 27th harmonic. For more precise harmonic amplitude values for fig. 1 through fig. 5, see table 1.

what this means

Now we can return to the questions asked at the beginning of this article. Why are certain circuits better suited for frequency doubling than others? Looking at table 1, you can see that the second harmonic in the column under 2/3 is larger than all the others. This means that slicing off two-thirds of the sine wave would give better second harmonic per-

table 2. Sine waveform clipping required to optimize different harmonics.

harmonic number	clipping required	conduction angle	amplitude (maximum)
1	31.9%	245.1°	107.305%
2	66.7%	119.9°	55.133%
3	77.9%	79.7°	36.908%
4	83.4%	59.8°	27.719%
5	86.7%	47.7°	22.190%
6	89.0%	39.8°	18.498%
7	90.5%	34.1°	15.859%
8	91.7%	29.9°	13.878%
9	92.6%	26.5°	12.337%
10	93.4%	23.9°	11.104%
11	94.0%	21.7°	10.095%
12	94.5%	19.9°	9.254%

formance than any of the other clipped waveforms pictured. Actually, for the highest second harmonic content, 66.68% of the sine wave must be clipped off. This represents a conduction angle of 119.9° and provides a second-harmonic amplitude of 55.133% of the basic curve's amplitude.

table 1. Harmonic amplitudes as a percentage of the basic sinusoidal waveform for various amounts of clipping.

harmonic number	portion clipped off bottom of sine waveform				
	1/6 (fig. 1)	1/3 (fig. 2)	1/2 (fig. 3)	2/3 (fig. 4)	5/6 (fig. 5)
1	104.089	107.267	100.000	78.200	43.045
2	2.843	18.378	42.441	55.133	39.598
3	2.462	9.189	0.000	27.566	34.293
4	1.990	1.838	8.488	5.513	34.293
5	1.477	1.838	0.000	5.513	27.719
6	0.975	2.100	3.638	6.301	20.576
7	0.528	0.656	0.000	1.969	13.577
8	0.169	0.656	2.021	1.969	7.349
9	0.082	0.919	0.000	2.757	2.357
10	0.224	0.334	1.286	1.002	1.143
11	0.269	0.334	0.000	1.002	3.120
12	0.239	0.514	0.890	1.542	3.741
13	0.162	0.202	0.000	0.606	3.323
14	0.069	0.202	0.653	0.606	2.261
15	0.018	0.328	0.000	0.985	0.957
16	0.079	0.135	0.499	0.405	0.245
17	0.109	0.135	0.000	0.405	1.106
18	0.106	0.228	0.394	0.683	1.513
19	0.078	0.097	0.000	0.290	1.471
20	0.036	0.097	0.319	0.290	0.506
21	0.006	0.167	0.000	0.501	0.089
22	0.040	0.073	0.264	0.218	0.559
23	0.058	0.073	0.000	0.218	0.813
24	0.059	0.128	0.221	0.384	0.826
25	0.045	0.057	0.000	0.170	0.633
26	0.022	0.057	0.189	0.170	0.311
27	0.003	0.101	0.000	0.303	0.042
28	0.024	0.045	0.163	0.136	0.336
29	0.036	0.045	0.000	0.136	0.507
30	0.038	0.082	0.142	0.245	0.529

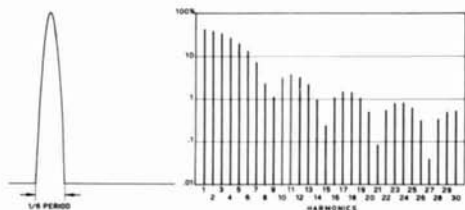


fig. 5. Severely clipping a sine wave so that only the positive peak remains results in lower-order harmonic output very nearly as strong as the fundamental.

In table 2, the optimum slice-fractions (conduction angles) are given for harmonics up to the 12th, with their corresponding highest possible amplitude for this set of non-sinusoidal curves.

summary

An oscillator producing an output curve in the form of a horizontally amputated sine wave will provide good second harmonic content if the horizontal part of the curve is approximately two-thirds of the total period. If frequency tripling is wished, the horizontal part of the curve (that is, the duration of the cutoff) should be in the neighborhood of three-quarters of the total period. Conversely, if a specific harmonic must be minimized the data of table 1 can be used to determine the best operating point.

APPENDIX

A Fourier-series of the form $f(X) = \frac{1}{2}a_0 + a_1 \cos X + a_2 \cos(2X) + \dots$ for a sine wave clipped off by a fraction $2V$ of the total period 2π will have the following coefficients:

$$a_0 = [2/(1 + \cos V)] [2/\pi] \int_0^\pi (\cos V - \cos X) dX$$

$$= [4/\pi(1 + \cos V)] [(\pi - V) \cos V + \sin V]$$

$$a_1 = [2/(1 + \cos V)] [2/\pi] \int_0^\pi (\cos V - \cos X) \cos X \cdot dX$$

$$= [2/\pi(1 + \cos V)] [V - \pi - \sin V \cdot \cos V]$$

$$a_n = [2/(1 + \cos V)] [2/\pi] \int_0^\pi (\cos V - \cos X) \cos(nX) \cdot dX$$

$$= [2/n(1 + \cos V)]$$

$$\left[\frac{\sin(n+1)V}{n+1} + \frac{\sin(n-1)V}{n-1} - \frac{2 \sin(nV) \cos V}{n} \right]$$

a_0 represents the value of the direct current present, and has no significance in this discussion. The absolute values of a_1 , a_2 , and so on, give the relative amplitudes of the corresponding harmonics.

ham radio

Regency brings you the best
in 220 MHz transceivers

MODEL HR-220



American Made Quality at Import Price

Full 12 Channels with 10 Watts Power Out

Compactly designed for dash mount, this little transceiver gives you big signal power on the go . . . at low current drain. 3 watts audio equipped with a noise operated squelch system provides clear reception and excellent sensitivity of 0.4 μ v. High-Low power switch. American Made and Regency reliable, the HR-220's solid state design brings you tough, top quality circuitry at the low price of only

\$239⁰⁰

Amateur Net

Regency **ELECTRONICS, INC.**

7707 RECORDS STREET
INDIANAPOLIS, INDIANA 46226

An FM Model For Every Purpose . . .
Every Purpose



HRT-2

5 Channel Hand-Held
2 Meter FM Transceiver



HR-2MS

8 Channel Transcan
2 Meter FM Transceiver



AR-2

2 Meter FM
Power Amplifier



the code mill

A Morse keyboard
that provides perfect
character generation
as well as
perfect letter and
word spacing,
regardless of the
operator's
keyboard skill

H.E. Thomas, W6CAB, 33020 Almond Street, Lake Elsinore, California 92530

Almost without exception, any person who uses Morse code can attain highest copying speed only when the code is sent perfectly. Because of this, and also in many cases as a matter of pride, most amateurs have tried to improve their sending technique. Many different kinds of equipment have been devised which can assist in this, but none of these, reasonably available to the average amateur, can produce perfect code, despite claims to the contrary.

Perfect International Morse code consists of five parts: the dot, which is one time unit or baud; the dash, which is three bauds; the space between each element of a Morse character, which is one baud; the space between letters, which is three bauds; and the space between words, which is seven bauds. Each and every one of these five parts of International Morse must be produced with machine-like precision — not a single one can be produced by human estimation if *perfect* code is to be the result.

The typical bug can make dots quite well but the other parts of the code are up to the operator. Some types of electronic keyers can produce dots, dashes and the spaces between them in proper form, but the operator is responsible for

the letter and the word spaces. The latest device, which goes a step beyond the electronic keyer, is what I call a *code mill*. In radio parlance a typewriter is a *mill*, so what better name for keyboard keyers?

These code mills create perfect dots, perfect dashes, perfect spacing between

elements of the characters and terminate each character with a perfect letter space. Whether this letter space remains perfect depends on the availability of the succeeding letter at precisely the right time. This in turn depends on whether the operator is successful in punching the key of the succeeding letter during what might be called its *launch window*. This launch window becomes quite narrow as the code speed increases and is almost intolerably narrow for any character which may follow the letter E (the launch window in this case is less than a tenth of a second at 30 wpm).

Some keyboard keys provide a one-character storage latch at the input of the circuitry but even this partial solution requires the operator to anticipate various letter combinations. The varying length of the different Morse characters is not compatible with the smooth rhythm of good typing, particularly at the higher speeds. And, of course, the usual code mill does nothing whatsoever about word spacing. Listening on the air will give ample evidence of the inability of such devices to produce perfect code.

the solution

The obvious answer to the problem is to design a code mill which will automatically produce all five parts of the Morse code. Since this includes word spaces, a space bar for the keyboard is required, as in teletype equipment. Furthermore, to maintain exact letter spacing, the availability of successive characters must also be automatic. This means that the operator and his sometimes erratic operation of the keyboard must be isolated from the code transmitting circuits.

The electronic equivalent of a vending machine can best meet this requirement. The keyboard operator dumps the merchandise in at the top in the proper sequence and at whatever rhythm suits, including the "hunt and peck" system. The code transmitting circuit puts the "coin in the slot" and extracts the merchandise in the same sequence but at precisely the correct instant.

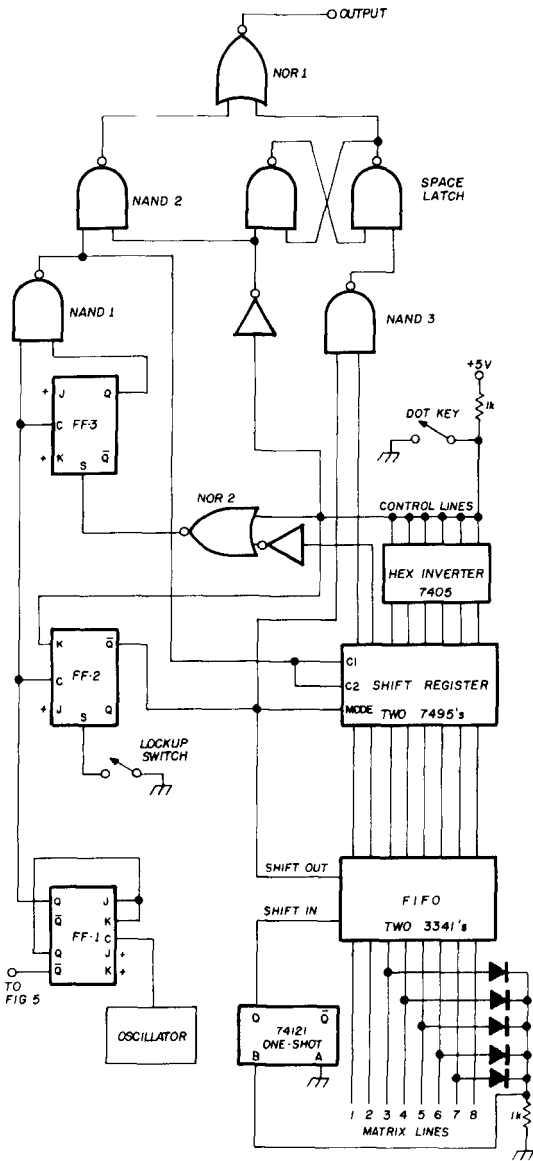


fig. 1 Block diagram of the code mill which uses first-in first-out (FIFO) serial memory to generate perfect Morse code characters and spacing, regardless of the operator's keyboard skill.

the circuit

This and the following paragraphs describe a code mill with an electronic vending machine having a storage capacity of 64 Morse characters. This code mill produces perfect code at any speed between 7 and 70 wpm as long as the operator keeps the storage partially filled and does not exceed its storage capacity at any time.

The block diagram of fig. 1 shows the basic arrangement which uses two Fairchild 3341 mos ICs for storage. Each 3341 is a 64 by 4-bit FIFO (first-in first-out) serial memory, and is available in a standard ceramic 16-pin dual-inline package. A detailed description of circuit operation will not be given here since the circuit, excluding the FIFOs, is a modernized version of a circuit which was described in fine detail in a previous article.¹ However, a brief description follows.

The oscillator is a variable-speed pulse generator which runs continuously. It triggers dual flip-flop 1 whose second Q output gives the required square wave. This square wave will produce transmitted dots through gates NAND 1, and NAND 2 and NOR 1 if none of these gates is inhibited. When no character is being processed through the shift register, the control line will be *high* and this inhibits NAND 2 via an inverter. Also, with the control line *high*, the K input of flip-flop 2 is *high* and this flip-flop is then triggered back and forth by the output of flip-flop 1. Whenever the \bar{Q} output of flip-flop 2 is *high*, the FIFOs and the shift registers are ready to process Morse characters for transmission.

At this point it should be mentioned

that the mos chips used in this circuit require a bit higher than normal *high* level. For this reason flip-flop 2 is one-half of a Signetics SP321A dual J-K flip-flop. Flip-flop 3 is the other half. Despite the fact that the Fairchild 3341 has internal pull-up circuits to make them compatible with TTL logic, the 3.8 volts minimum *high* of the SP321A looks a lot

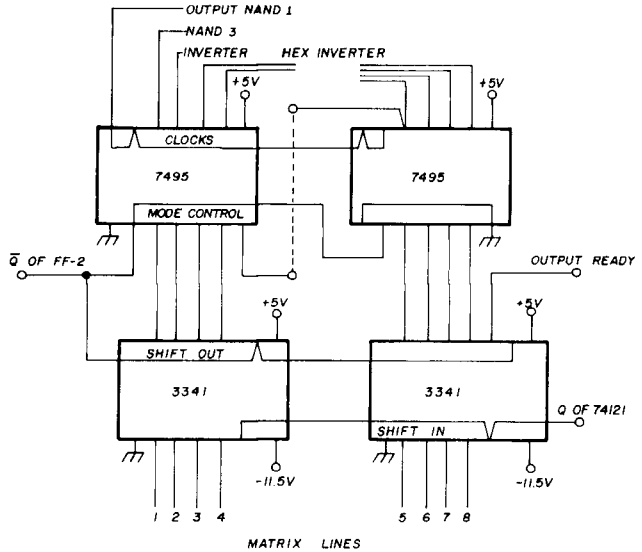


fig. 2. Bottom view, or foil side, of the ICs used in the first-in first-out serial memory and shift register.


better than the 2.4 volts minimum *high* for the TTL flip-flops. A 7473 TTL could probably be used to replace the SP321A, but it was not tried.

The *set* input of flip-flop 2 may be grounded with a switch near the keyboard. This blocks the output of the mill while the FIFOs are being filled. With the lockup switch blocking the mill, calls may be typed up while still listening to the transmission from the other station or stations in a two-way or round-table QSO. It is also nice to use when setting up for a repetitive transmission using the recirculating shift registers to be described later.

When any key on the keyboard other than the space bar is depressed, the inputs to the FIFOs are actuated by the 74121

one-shot multivibrator, the character enters the FIFOs and almost instantly appears at the outputs. By the action of flip-flop 2 and the output of NAND 1 on the FIFOs' *shift out* controls and the shift registers' mode controls and clocks, the character enters the shift registers and eventually appears at the inputs of the hex inverter. This drops the control line

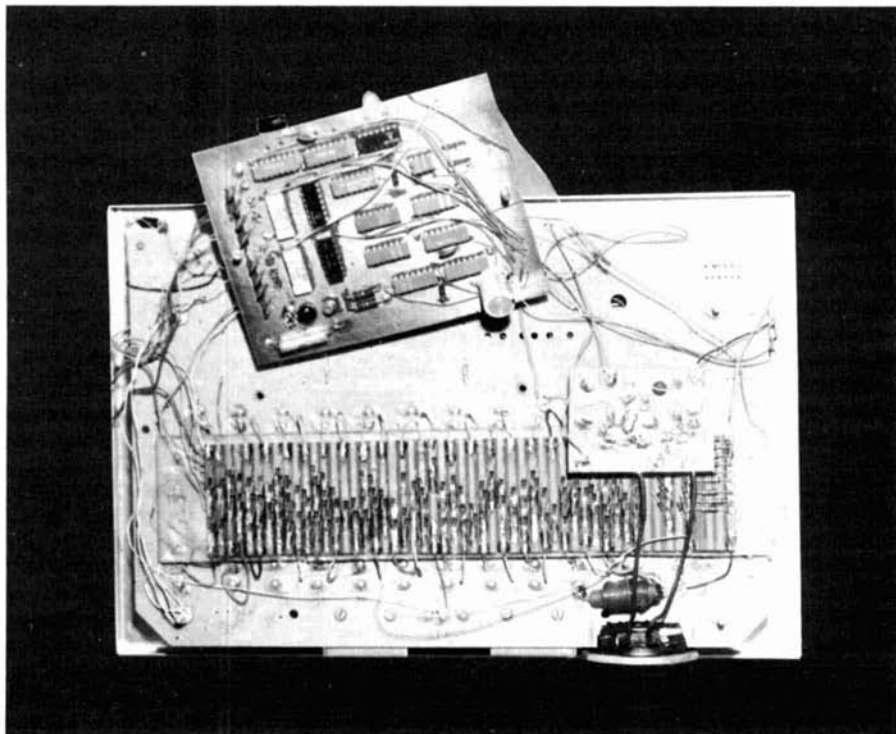output of the shift registers, the control line goes *low* because of the E, enabling NAND 2 and the left-hand gate of the space latch. The *high* on line 1, via NAND gate 3, sets the latch, which in turn inhibits NOR gate 1 and prevents transmission of the E. Note that NAND 3 is inhibited by the output of flip-flop 2 except during the loading of the shift



Construction of the code mill showing the matrix board mounted on the back of the keyboard switches. Oscillator is on small board to the right. Main circuit board, including memory, is at top.

to a *low* which enables NAND 2 (via the inverter) and the character is transmitted. NOR gate 2 and flip-flop 3 serve with NAND 1 to bridge the gap between two successive dots to produce a dash when required.

word space

When the space bar is depressed the letter E is formed and matrix line 1 is also activated (raised to a *high*). When the E and the *high* on line 1 appear at the

registers. This prevents line 1 from setting the space latch when it goes *high* due to the shifting of *highs* along the shift registers. At the completion of every character the control line goes *high*, resetting the space latch through an inverter.

The letter E is used for the space character because it's one-baud length plus the three-baud automatic letter space adds to the previous three-baud letter space to become a seven-baud word

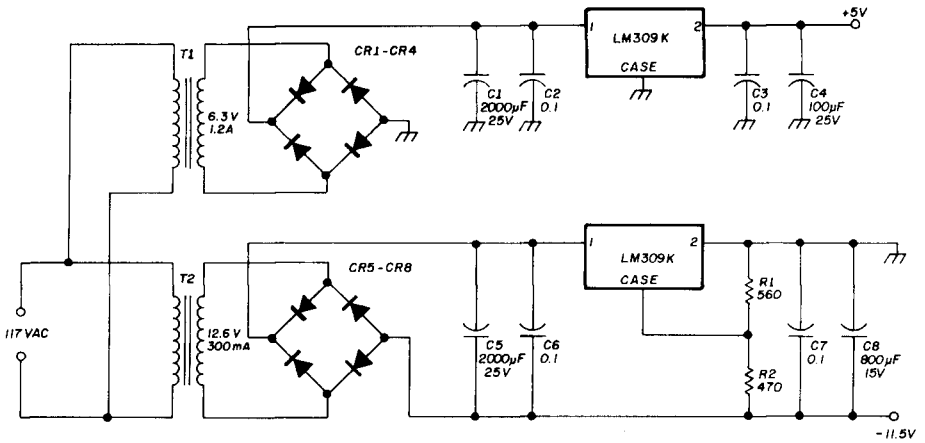


fig. 3. Regulated power supply for the code mill uses LM309K voltage-regulator ICs.

space. The letters I, S, H or the numeral 5 may be used if wider word spaces are desired. A switch is provided for this purpose, although it has seldom been used except while teaching code to beginners.

Fig. 2 shows the bottom view, or foil side, of the ICs comprising the FIFO and the register. Fig. 3 shows the circuit for the power supply. Both the +5 volt and the -12 volt supplies are regulated by LM309K voltage regulators. The values of the resistors in the -12 volt supply were chosen to give an output of -11.5 volts.

last-character elimination

Fig. 4 shows a circuit which was added some time after the code mill was built. Without touching the keyboard, this circuit will trigger the FIFO inputs at the conclusion of a character (control line goes high) and when the output ready terminal of one of the 3341s indicates that the FIFO is empty. Unfortunately, the 3341 will never completely empty itself. The last character will remain at the output of the FIFO until another character enters and "falls through" to the output. This causes continuous repetition of the last character. The operator must either learn to punch the space bar as a last character or a circuit must be designed to prevent this repetition. By

triggering the input without punching a key, a complete blank is entered and passes through, and in turn takes the place of the offending character.

Since the Fairchild 3341 memories require +5 volts and a -12 volts in addition to the usual ground connection, it was a simple matter to add the recirculating shift registers shown in fig. 5. The reason flip-flop 1 is a dual unit is now apparent: it permits triggering the recircu-

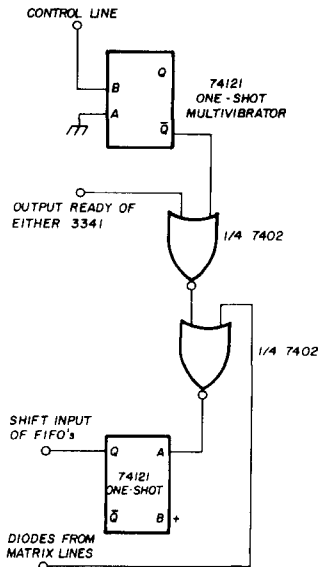


fig. 4. Circuit for last-character elimination.

lating shift registers with the output from the first \bar{Q} which is equivalent to a trigger for every baud in the mill output.

The inverters at the input and output of the 2522 chips are used as buffers. The two 2522 chips will store every transmission from the code mill up to a limit of 528 bauds. When the spd switch is thrown, the information stored in the 2522s will repeat over and over, and at any speed. Although not a necessary part of the code mill, this circuit is handy for preliminary callups prior to broadcasts, directional CQs or whatever, while you sip your coffee.

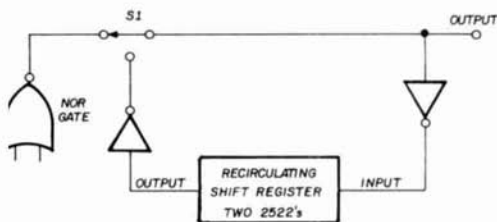


fig. 5. Recirculating shift register, shown here, is useful for transmitting repetitive material or calling CQ.

The code mill described in this article was built for just over one hundred dollars, and all chips were purchased at full list price. My keyboard itself is a surplus unit and similar types are available at several outlets. The price was not too high considering the very great pleasure and satisfaction derived from building the unit and operating it on the air. Without mentioning the code mill, almost every QSO elicits favorable comments on the keying. The code mill is just great for code practice, of course, but probably the best feature of all is the ability to send absolutely perfect code at fairly high speeds, hour after hour if need be, and with no great effort.

reference

1. J.A. Bryant, W4UX, "Touchcoder II," *QST*, July, 1969, page 12.

ham radio

You HEAR the Difference...

when it's a Larsen Külrod Mobile Antenna



Larsen Külrod Antennas are "solid" on all scores. They have a low, low silhouette for best appearance and minimum wind drag. Hi-impact epoxy base construction assures rugged long life. The Larsen mount gives you metal to metal contact, has only 3 simple parts and goes on fast and easily.

And performance! Larsen Antennas for the 144-148 MHz range deliver a full 3 db gain over a 1/4 wave whip. V.S.W.R. is less than 1.3 to 1. The exclusive Larsen Külrod assures you no loss of RF through heat. Handles full 150 watts.

It adds up to superior performance . . . and a difference you can HEAR! Available as antenna only or complete with mounting hardware coax and plug. Write today for fact sheet and prices.

**Sold with a full money back guarantee.
You hear better or it costs you nothing!**

Need a BETTER 450 MHz Antenna?

Get the Larsen 5 db gain Phased Collinear. Same rugged construction and reliability as the 2 meter Larsen Antennas including exclusive Külrod. Write for full fact sheet.



©Külrod
a trademark of Larsen Electronics

Larsen Antennas

11611 N.E. 50th Ave. P.O. Box 1686
Vancouver, WA 98663
Phone: 206/573-2722

automatic telephone controller for your repeater

A simple, reliable
and foolproof
control system
for remote control
of your repeater

The problem of building a practical, positive remote-control system has plagued amateurs for years. Some of the suggested schemes used have been very complex while others have been simple, but not foolproof. The technique applied in the design described here uses the telephone line. Positive and automatic control in the event of line failure are the

basic assets of this unique system. Don't be alarmed at the apparent complexity of the schematic, **fig. 1**, as all the IC gates are contained in five, inexpensive SN7400 IC packages. Total cost of the circuit for ICs is less than \$5.00 and a well stocked junk box will supply the balance. Although the circuit can be built on peg board, a custom made printed-circuit board is available and is recommended for simplicity.* See **fig. 3** for a suggested parts layout.

construction

A small chassis was made from sheet aluminum and bent in a vise to form the chassis shown in **fig. 2**. The power supply and relays are mounted on the chassis for convenience. A small equipment box could have been used but one was not available at the time I built the system. It is suggested when you choose your chassis that you keep the top and bottom open to aid in troubleshooting. A coat of white paint on the front panel and instant press-on lettering may be used to dress it up.

The model illustrated is set up for a

*Printed-circuit boards and nonlatching relays are available from Circuit Board Specialists, 3011 Norwich Avenue, Pueblo, Colorado 81008. Circuit boards are \$5.50 each; nonlatching relays, \$2.00 each.

Robert C. Heptig, KØPHF, Robert D. Shriner, WAØUZO

latching function—it turns our repeater off. If you happen to have a stepping relay, this is fine, but I didn't, so another SN7473 was mounted in a socket off to the side and wired in as shown in the alternate circuit, fig. 4.

operation

An operating function, such as shut-down or turn-on of a remote station, requires a specific number of rings on the telephone, hang up, wait a specific length of time, then another specific number of rings and the function will be carried out.

In this discussion I will use 3 rings, hang up, wait 20 seconds, another 3 rings and hang up. Any combination of number of rings may be used so long as the total is less than nine. By examining the decoder (U2) you can see that it can be very easily programmed by the moving of only two jumper wires to the various outputs of U2.

Depending upon the type of relay used at relay K2, a momentary, latching or stepping function can be obtained. Relay K1 is used for validating the phone line. The remote station keying voltage can be taken through the contacts of this relay. If the phone line is interrupted, the transmitter cannot be activated.

circuit description

The phone line must be connected with the polarity as shown in the schematic. To assure the phone line being operational, the negative voltage is passed by CR1 and R1, charging C1, which will store the voltage during brief interruptions such as when the phone is ringing. The negative voltage applied to the gate of Q1 causes it to cease conducting. A high plus voltage will appear on the drain of Q1. This voltage is passed to the Q3 base by R4, causing Q3 to conduct and close relay K1. For repeater control K1 is connected in the push-to-talk or transmitter keying line so that it must be closed in order for the repeater to operate.

Although an explanation of the ring-counting circuit is a bit complicated,

operation is actually very simple. In the ring circuit you are only interested in the ac signal. Capacitor C2 is used to block the dc and pass the ac signal to the rectifiers. The negative dc voltage is smoothed by C3 and C4 and applied to the gate of Q1, causing a rise in voltage on the drain of Q1. As soon as the ring signal disappears, R7 pulls the gate of Q1 to ground, resulting in full conduction of Q1, causing pin 14 of U1 low. Each shift from high to low on pin 14 will cause U1 to toggle once.

Therefore, the first ring will step the decade counter (U1) one count. The decoder-driver (U2) has now moved off zero position to its first count. When U2 leaves zero, pin 16 goes to +5 volts. This high is fed to pins 1 and 2 of gate 17 (U8A), and pin 3 goes low, causing the ready light to go out. Also, pins 4 and 5 of gate 18 are low, causing pin 6 to go high, turning on the start light indicating that a function has started. The high from gate 18 pin 6, is also fed to U7, pin 14, providing a set signal for flip-flop 1 (U7A), as well as providing the clear voltage to both flip-flops at pins 2 and 6.

To back up a little, to U2 pin 16, +5 volts is also fed to the emitter of Q4. This is the timing circuit of the telephone controller which provides the 20-second timing necessary for all phases of the function. The time is controlled by the RC network R11 and C5.

This all happens on the first ring of the telephone. The second ring simply advances the counter to count two. The third ring, the one that does the business, advances the decoder driver, U2, to count 3 position. The resultant low on pin 9 (count 3) of U2 is seen at pins 1 and 2 of gate 3. Gate 3, pin 3, will provide a high enabling voltage to pin 12, gate 1. Now, assuming that the telephone quit ringing on the third time, pin 12, gate 1 will remain high. After 20 seconds the uni-junction transistor, Q4, will have charged up and fired a voltage spike out B1. This spike is fed to pin 13, gate 1. The output of this gate goes low, clocking FF1 (U7A) at pin 1. The Q output of FF1 goes high,

applying a set voltage to FF2. At the same time the phase 1 lamp comes on indicating that the first requirement of a function has been accomplished. Pin 11, gate 1, is also fed to gate 16, pin 2, which

is used to reset the whole system if the telephone fails to ring again within the next twenty seconds.

When phase 1 has been successfully completed, the telephone must ring three

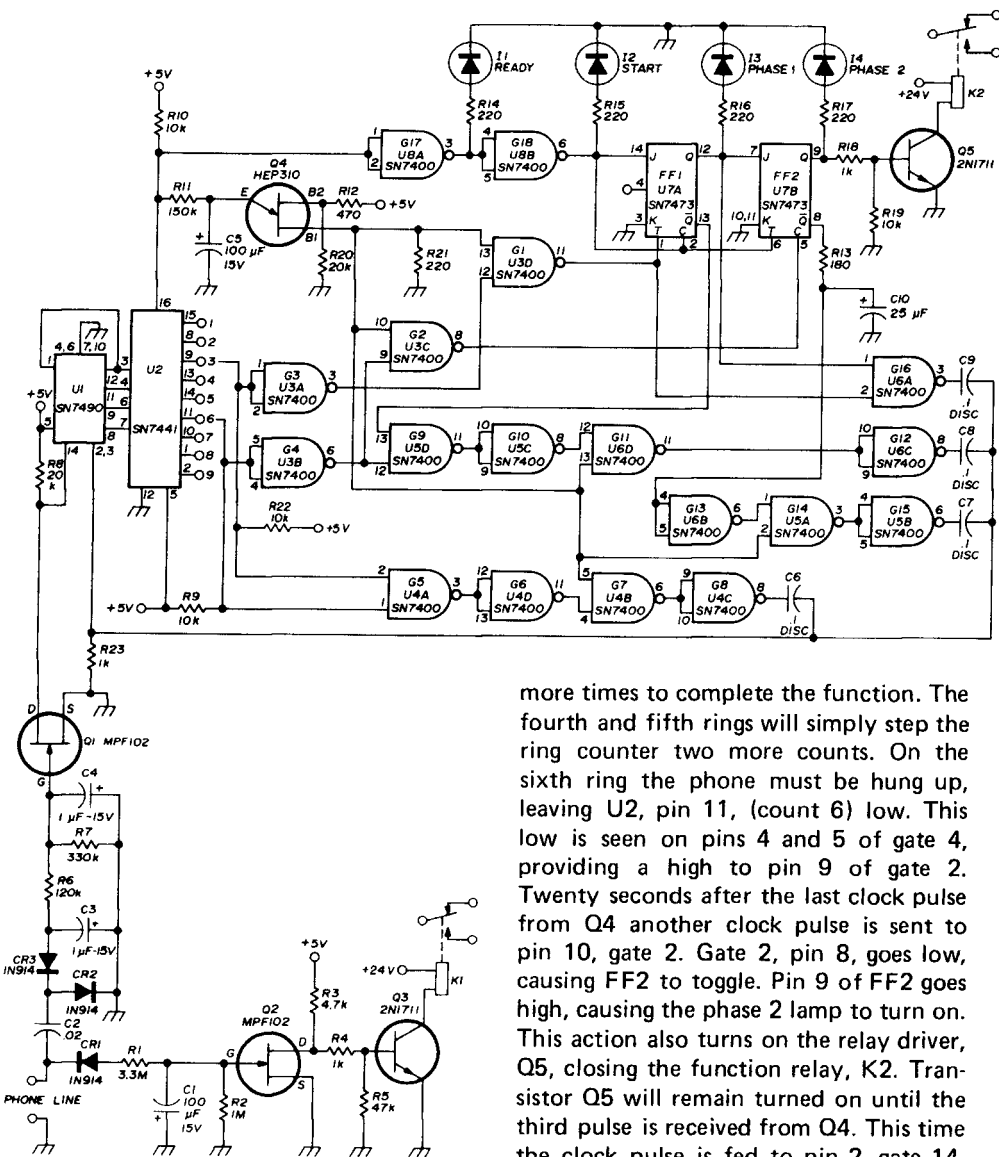


fig. 1. Schematic diagram of the automatic phone controller. All gates are SN7400 or equivalent. Relays K1 and K2 are sensitive dpdt relays with 8000-ohm coils. Resistor R11 is selected for the desired time setting. Resistors R14, R15, R16 and R17, in series with the LEDs, are adjusted for proper light output.

more times to complete the function. The fourth and fifth rings will simply step the ring counter two more counts. On the sixth ring the phone must be hung up, leaving U2, pin 11, (count 6) low. This low is seen on pins 4 and 5 of gate 4, providing a high to pin 9 of gate 2. Twenty seconds after the last clock pulse from Q4 another clock pulse is sent to pin 10, gate 2. Gate 2, pin 8, goes low, causing FF2 to toggle. Pin 9 of FF2 goes high, causing the phase 2 lamp to turn on. This action also turns on the relay driver, Q5, closing the function relay, K2. Transistor Q5 will remain turned on until the third pulse is received from Q4. This time the clock pulse is fed to pin 2, gate 14. Pin 1 is now high since it is controlled by the \bar{Q} output of FF2. The pulse is fed through gate 14 and 15 to reset U1. This restores U2 to zero, clearing FF1, FF2 and turning on the ready light. Thus, one complete function has been performed.

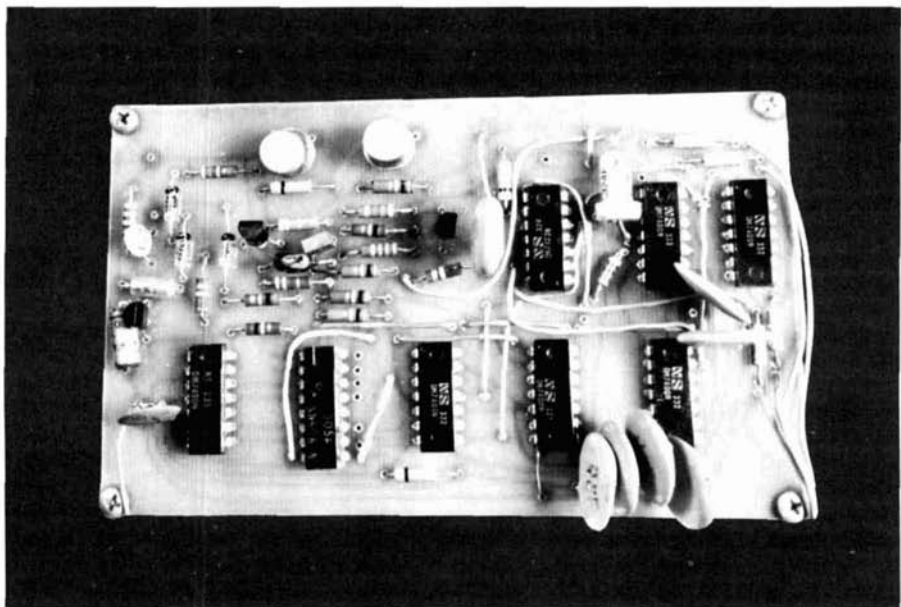


fig. 3. Component layout. The two transistors at the top are Q3 and Q4. The input and output connections are on the bottom; wires run to the light-emitting diodes located on the front panel. (Photo by Russell McGee, WBØGSU.)

troubleshooting

A high-impedance scope or a vacuum-tube voltmeter will be required in the event of trouble. However, the light-emitting diodes connected to each stage will generally suffice for troubleshooting.

After construction is completed and voltage is applied to the circuit check for the following: the ready light, I1, should be on and all others off. Pin 16, U2, should be low, pins 9 and 12, U7, should be low and pins 8 and 13, U7, should be high. Connect the positive terminal of a small 9-volt battery to ground and the negative side to the input. Relay K1 should close and remain closed for about

30 seconds after removing the 9-volt battery.

Next, apply the 9-volt battery lead momentarily to the junction of CR3 and R6. Approximately 2 seconds after removing the battery lead I2 should light, indicating a function has started. Make and break this connection, allowing about 2 seconds between pulses for the correct number that corresponds to the first number of rings that you have programmed for. About 15 seconds later I3 should light, indicating that the first phase of the system has been satisfied. Now make and break the battery connection in the same manner for the second combination of rings; in approximately 5 seconds I4 will light, indicating that the sequence has been completed and the function has been carried out.

In the event of difficulty check base 1 of the unijunction transistor with a scope for the pulse that controls the system. If the pulse is being generated, then trace the pulse through the system to determine which gate or flip-flop is not responding.


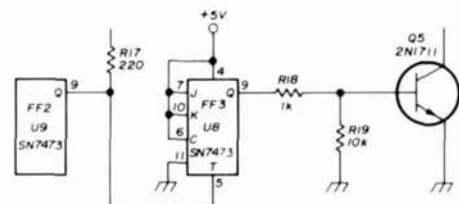


fig. 4. Alternate circuit for use when a latching function is required.

ham radio

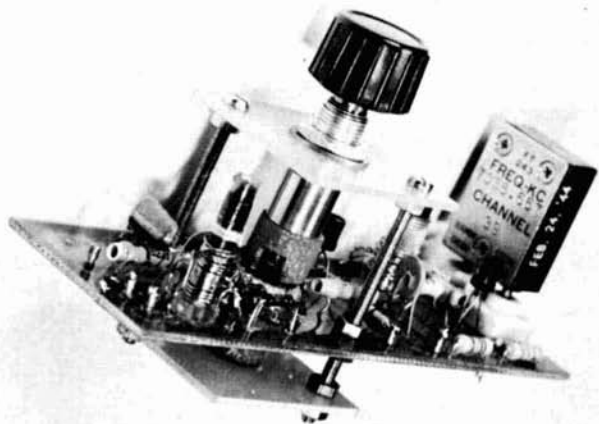

tuned very low-frequency converter

Novel tunable inductance
provides basis
for tuned
VLF converter
that covers
wide frequency range
without bandswitching

There is considerable interest in the very-low frequencies, particularly for the WWV transmissions on 20 and 60 kHz, and for operation on the no-license band around 1750 meters.¹ One of the big problems in building receivers or converters for this part of the spectrum is in constructing a variable tuned circuit

which will cover a substantial portion of the desired frequency range. Assuming that the desired band extends from 10 to 150 kHz, with a ratio of the corner frequencies of $150:10 = 15$, the tunable component must have a variation of $15^2 = 225$. Since this cannot be accomplished with conventional variable capacitors or inductors, the frequency range has to be divided into a number of sub-bands or the tuned circuit is eliminated altogether. The latter is done in most VLF converters — they are untuned.

tuned circuit

There is, however, a novel method of inductive tuning which will cover the required range.² This method makes use of a toroidal ferrite core which is magnetically biased by a pair of small permanent magnets as shown in fig. 2. By rotating one of the magnets with respect to the other, the amount of flux penetrating the toroid is varied, changing the ferrite's permeability and thus, the inductance. It is interesting to note that maximum flux penetration and minimum inductance occur when like poles are opposite one another.

Guenter Ruehr, OH2KT, Porintie 1 C 35, SF - 00350 Helsinki 35, Finland

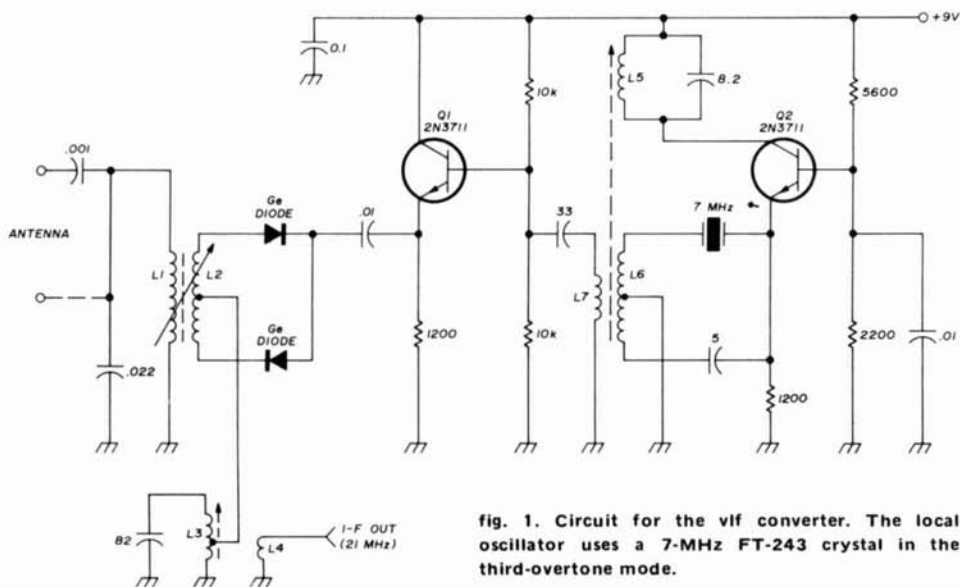



fig. 1. Circuit for the vlf converter. The local oscillator uses a 7-MHz FT-243 crystal in the third-overtone mode.

- L1,L2 magnetically tuned inductor (see text)
 L3 10 turns no. 20 on 1/4" (6-mm) slug-tuned form, tapped 5 turns from cold end
 L4 2 turns no. 20 around cold end of L3

- L5 15 turns no. 20 on 1/4" (6-mm) slug-tuned form
 L6 4 turns no. 20, center tapped, around cold end of L5
 L7 2 turns no. 20 around cold end of L5

The two magnets used to bias the toroid inductor are of the *button* type with a half-inch (13-mm) outside diameter. The outside diameter of the toroid is

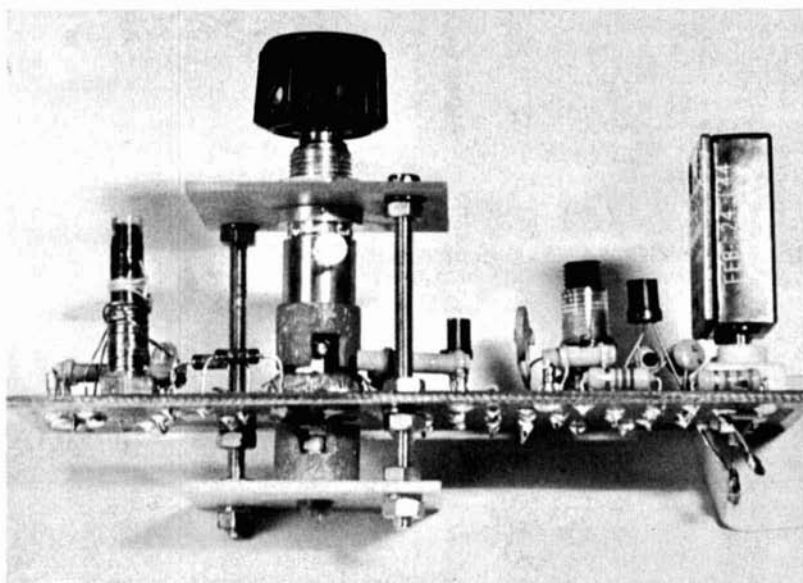also 1/2-inch. The whole tuning assembly is built around the bushing and shaft of a discarded potentiometer. The particular toroid core I used required 100 turns of



Closeup of the tunable vlf converter showing magnetically-biased tuning inductor.

stranded wire for an inductance variation of 100 μH to 12 mH (a 120:1 range). However, ferrite cores with higher permeability would require fewer turns. Measured Q values for my inductor were around 50 for frequencies between 10 and 150 kHz.

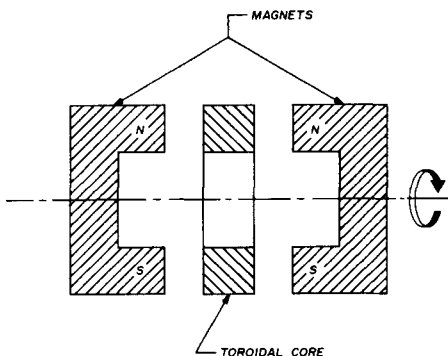


fig. 2. Method for magnetically biasing a toroidal ferrite core with two small button magnets. This technique provides an extremely wide inductance tuning range.

converter circuit

The circuit for my VLF converter, which has an output on 15 meters for use with a communications receiver, is fairly conventional as shown in fig. 1. The antenna is coupled directly to the hot end of the tuned circuit (or through a capacitor to provide a degree of matching to long antennas). The mixer uses a matched pair of germanium diodes and the local oscillator uses a FT-243-variety crystal in the third-overtone mode. To obtain third-overtone oscillation at 21,000 MHz, choose a crystal with a fundamental frequency a few kHz above 7 MHz. By simply changing the crystal frequency and the oscillator and i-f output coils, output can be changed to any desired frequency band.

references

1. J.V. Hagan, WA4GHK, "A Crystal-Controlled Converter and Simple Transmitter for 1750-Meter Operation," *QST*, January, 1974, page 19.
2. N.H. Brown, "Miniature Wide-Range VLF Tuner," *Electronics World*, July, 1971.

ham radio

electronics center, inc.

hy-gain
Antennas!

TH6DXX

6-Element Super Thunderbird DX Superior Performance TriBand! Impressive coverage 10-15-20 meters.

TH3Mk3

3-Element Super Thunderbird Popular Tri-Band Beam Improved!

Outstanding performance 10-15-20 meters at reasonable cost.

18AVT/WB

The Great Wide Band Vertical Super Performer 80 through 10 meters! Superb omnidirectional capabilities.

18 HT

Incomparable Hy-Tower Finest Multiband on the Market! Automatic band selection 80 through 10 meters.


Also a complete selection of Hy-Gain accessories including: rotators, baluns, mounts, springs, switches, phone patches and lightning arrestors!

Electronics Center carries complete lines of Ham equipment, accessories and antennas. Write or call WA1, WSZYA, or AL WSPXIH for your HAM needs

electronics center, inc.

2929 N Haskell - Dallas, TX 75204 - 214/528-2823

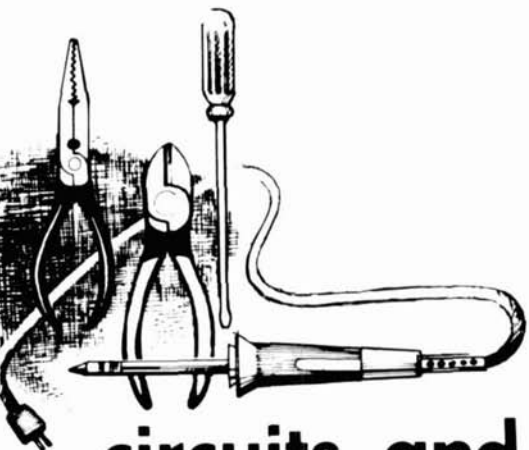Home of the world's largest Electronic Flea Market It's free! First Saturday of each month



circuits and techniques

ed noll, W3FQJ

W3FQJ goes solar power

On April 15, 1974, the solar-powered QRP station at W3FQJ made an initial radio contact with Hank Brazeal, WB4ZXJ, in Birmingham, Alabama on 15 meters. The transceiver was the five-watt PEP Ten-Tec Argonaut. The same evening W3FQJ checked into the RF Hill Amateur Radio Club's 10-meter net.

The essential units of the solar-powered station are the Argonaut transceiver, charging panel and 5.5-ampere-hour motorcycle battery (fig. 1) and a roof-mounted light-energy converter, (fig. 2). The 5x2½x5½-inch (12.7x6.6x14-cm) battery is positioned behind the charging panel for normal operation. Such batteries can be purchased at local motorcycle shops or by mail from one of the auto accessory houses or from Sears. The Sears batteries are shipped with a dry electrolyte which must be added to the battery along with water according to the instructions. In most shops the electrolyte is added when the battery is purchased.

The Spectrolab light-energy converter has a rating of 12-volts at 0.3 amperes.

When the solar panel is so operating it is supplying 3.6 watts. This is an average figure. At dawn and dusk and during dark, overcast days the power level is significantly lower. When the rays of the sun are striking the panel directly, the delivered power is slightly more. Nevertheless, it will make available more than enough electrical energy for a very busy five-watt QRP station.

The solar panel can be operated as a continuous float-voltage charger or it can be operated whenever you wish to recharge the battery. As I am writing this column in the early morning hours of a high-overcast day the float-voltage connection is supplying 50 milliamperes.



fig. 1. Solar power converter used by W3FQJ is mounted on the roof. Details of the mount are discussed in the text.

Yesterday in bright sunlight a series resistor was inserted to keep the trickle charge current below the 100 mA level. As set up now the station plan is very conservative and would provide continuous operation for normal back-and-forth amateur chatter. Over a period of time I will learn the limits of the system, pressing high-powered transmitters into operation.

Such is not conducive to the furthering of corporate empires.

charging panel

Several components are needed for the charging panel. Refer to the schematic diagram and parts list shown in **fig. 3**. About 50-feet (15-meters) of two-conductor cable (number-12 or -14 con-



fig. 2. Basic solar-powered QRP station used by W3FQJ uses Ten-Tec Argonaut transceiver, solar power converter (**fig. 1**), solar control panel (**fig. 4**) and 12-volt motorcycle battery.

Reports will appear in this column from time to time.

solar power cost


Today solar electric power is expensive. The small 3x39-inch (7.6x99.1-cm) unit I am using lists for more than 150 dollars. Much about it is handcrafted and as yet systems have not been adapted to mass production. Unfortunately, it must be the American citizen that is obliged to set up a widespread clamor for solar power. One cannot anticipate that the oil institute, the electric power industry or the atomic energy bureaucracy will do too much to further the cause of this non-polluting method of power generation. Such power would offer a degree of independence for many homes, small businesses and small industrial plants.

ductors) connects the solar polar converter to the charging panel. The panel itself supports a dc milliammeter, a 1-ampere diode, CR1, and a number of binding posts that permit ease in monitoring and experimentation.

The two binding posts at the top right of the front panel, **fig. 4**, can be used for monitoring the voltage delivered by the solar panel. The meter to the left reads the actual current being delivered by the solar cells. The two binding posts underneath the meter permit the insertion of a jumper if you want to take the meter out of the circuit for those experiments where you want to draw maximum current under the condition of bright sunlight directly striking the cell surface.

The battery terminals are at the lower right. In a continuous service application

fig. 3. Schematic diagram of the charging panel shown in fig. 4.

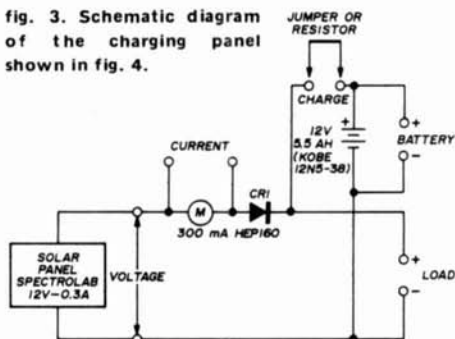

the 12-volt device being powered is connected across these two terminals. When the battery is to be charged, a jumper is connected between the two terminals labeled *charge*. If you wish to limit the charge to a specified current level under bright conditions, a resistor can be connected between these two terminals. Often, under very bright conditions, I shunt a 100-ohm, 5-watt resistor between the terminals.

The two load terminals at the bottom center of the panel permit you to supply energy directly from the solar panel to a 12-volt device. In this application the battery is disconnected completely by making certain there is no jumper or resistor connected across the two charge terminals.

Diode CR1 is an important part of the charging system. The actual charging current declines as the battery reaches full charge. This is to be anticipated because the charging battery attains a voltage ever closer to the voltage of the charging source. However, it is possible, especially when the battery climbs to full charge voltage, that the impinging light will not be great enough to maintain the charging source voltage above the level of the battery voltage. Without the diode in the circuit, the battery would then discharge into the solar source. This is avoided because under the condition of high battery voltage and low charging source voltage the diode is reverse biased (cath-

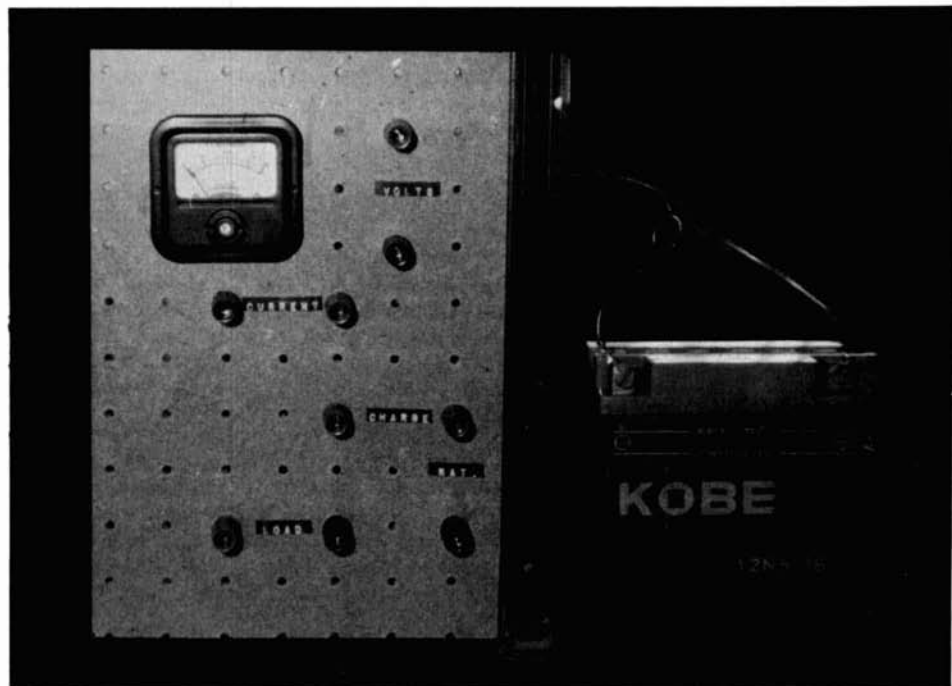


fig. 4. Solar control panel and 12-volt battery used by W3FQJ. Control panel is mounted on 8x11-inch (20.3x27.9-cm) piece of Masonite peg-board. Circuit is shown in fig. 3.

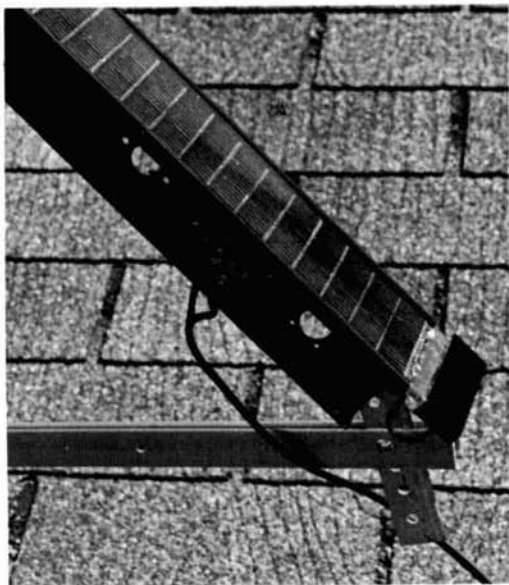


fig. 5. Closeup, showing tilt angle adjusting mechanism for the solar energy panel.

ode connected to positive side of battery and anode connected to the positive side of the charging voltage).

roof mount

The basic physical support for the solar panel is the vent pipe on the roof of my house, fig. 1. At one time the two standoff brackets supported an antenna mast. A shortened 5-foot mast section and a homemade bracket arrangement supports the solar panel. It was arranged to permit ease in experimenting with the tilt of the panel. A U-bolt permits the top of the panel to be moved up and down the mast. At the bottom of the panel a flat piece of aluminum with a series of holes permits easy accommodation of various tilt angles.

The recommended tilt for the panel corresponds to the latitude of your station (degrees north [or south] from the equator). My station is reasonably near the 40° north latitude line. This figure refers to the angle of tilt away from the horizontal as shown in fig. 6. The nearer you approach the equator, the

nearer the optimum mounting angle approaches a horizontal position.

In setting up the mounting arrangement the solar panel becomes the hypotenuse of a right triangle, fig. 7. Sine and cosine functions can then be used to determine the vertical and horizontal sides. The overall panel length is 39 inches (99.1 cm); this becomes the length of the hypotenuse. Therefore, the horizontal and vertical side dimensions become:

$$\begin{array}{ll}
 b = h \sin a & a = h \cos A \\
 b = 39 \text{ inches (99.1 cm)} & a = 39 \text{ inches (99.1 cm)} \\
 \quad \times \sin 50^\circ & \quad \times \cos 50^\circ \\
 b = 30 \text{ inches (76.2 cm)} & a = 25 \text{ inches (63.5 cm)}
 \end{array}$$

The vertical side is an appropriate section of the 1¼-inch (32-mm) mast section. The horizontal support is two 1¼-inch (32-mm) aluminum strips bolted together but separated where they wrap around the mast section and where they connect to the short length of aluminum strip that permits the adjustment of tilt angle.

battery data

A 5.5-ampere-hour capacity battery provides a conservative and well-regulated source for the 5-watt Argonaut transceiver. Transceiver specifications suggest a 12-volt, 1-ampere source although peak current demand by the transceiver is less than this value. At any rate, such a battery would supply the unit for continuous overnight operation. In fact, the battery could supply almost a continuous demand of 1 ampere for 4 to 5 hours.

Based on a 20-hour, 5.5-ampere-hour rating, the continuous current demand for this period of time would be:

$$I = \frac{5.5}{20} = 275 \text{ milliamperes}$$

A charging current of the same value would recharge the battery in the same amount of time plus additional time, depending upon the charging efficiency of the battery.

In normal amateur applications deep discharge of the battery and continuous high-current charging are not necessary. Once the battery is fully charged a float

charge arrangement is quite adequate. If you assume a charge rate of 1/4 to 1/6 of the rated current value, you are considering a minimum charge current in the 45- to 70-mA range. In the set-up described this level of current and higher is readily available for hazy-bright days. A generous, up to 300-mA, current is available during bright sunny days. Even on a high overcast day the solar panel supplies current at the low end of the range. Charging current is limited for dark days but the battery capacity is adequate, even for the very active QRP operator.

solar power QSO record

Correspondence from Edgar Janes, G2FWA, disclosed two solar-powered CW contacts made on October 27, 1954. Initial contact was made between G3HMO (solar-powered station) Buckingham, England and G5RZ, Leighton Buzzard, England. Here is an account from the December, 1954, issue of *Short Wave Magazine*:

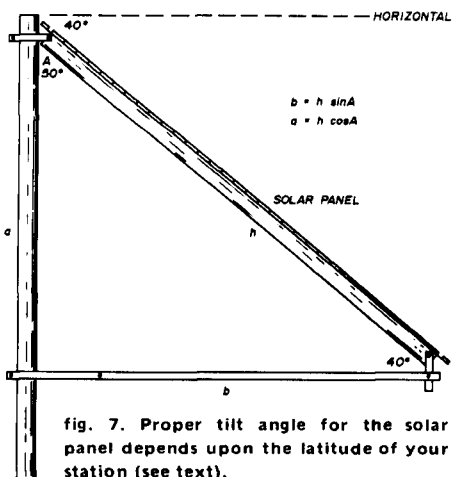


fig. 7. Proper tilt angle for the solar panel depends upon the latitude of your station (see text).

"Fortunately, the sun was shining fairly strongly, and the photo-electric cell battery was giving ample output — about 2 mA at 4 volts — to energize the transmitter... Two-way CW contacts (were made) with G5RZ (Leighton Buzzard, 15 miles) at 1505 gmt and with

G3IYX (Bradwell, Bucks, 7½ miles) at 1515 gmt. The daylight powered transmitter signals on 1820 kHz were reported as RST 559 in Leighton Buzzard and RST 569 in Bradwell.

These contacts, though pre-arranged, were initiated on the transistor trans-

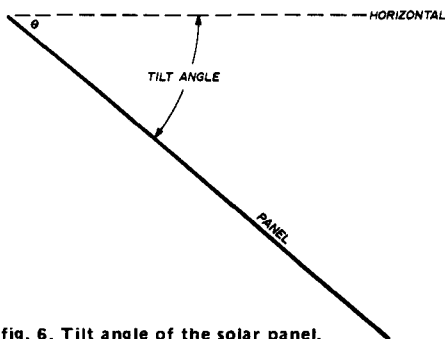


fig. 6. Tilt angle of the solar panel.

mitter running on the photo-cell battery alone and were carried through under normal band conditions, with quite troublesome interference on the frequency."

Thank you, Edgar, and Austin Forsyth, G6FO, Managing Editor of *Short Wave Magazine*.

My contact with WB4ZXJ on April 15, 1974, is degraded to the first solar-powered ssb contact, not arranged. Maybe? The paramount question, however, is why we have waited so long (except for satellite communications) to take advantage of this limitless source of energy.

new applications

More small companies are now producing small solar energy converters. Zurn Industries* sells two models with peak ratings of 1.5 and 6 watts. These two 12-volt models are covered with a transparent waterproof and detergent-proof coating. A major application of the Zurn models is for marine batteries. Under the condition of a week of normal daylight, sufficient charging power is available that

*Zurn Industries Incorporated, 5533 Perry Highway, Erie, Pennsylvania 16509.

a bilge pump can pump 600 gallons of water with the small energizer and 3000 gallons with the larger model. Such a device is particularly useful for maintaining battery charge during long idle periods, as during winter storage of a small boat.

Another active organization, Solar Energy Company,[†] sells solar power converters as well as wind-powered electrical sources. Their devices find application in vhf/uhf repeaters, microwave relays, wire and wireless telephone systems, TV translators, monitors, offshore platforms, data buoys, railroad signals and controls, plus traffic and security systems. They also make a unit that maintains the charge on batteries used to power farm electric fences.

Why haven't such devices been used to supply a portion of the power needed in the average household? Needed is a solar heater for the home with its electrical blowers, fans and circulators powered by a solar energy converter. At least there should be a home furnace capable of using a variety of fuels with its electrical accessories powered completely by battery and solar power converters.

experimental approaches

There are several avenues of experimentation. What are the operating limits using direct drive to 12-volt devices and no battery? Some voltage-regulator device would be required. How bright would it have to be to provide operation of a 12-volt zener diode? How much longer a period of operation would be feasible using the solar source for 9-volt regulated operation? What are the limits of a particular solar panel in terms of higher power demand and keeping a higher capacity battery fully charged relative to your normal operating schedule?

Connecting solar panels in parallel increases current capability. How many panels would be required to provide adequate charging current for a high

capacity battery system? How many panels and what battery capacity would provide enough power to match normal operating time for your 200-watt side-band transceiver? What advantages are to be obtained from series-parallel groupings of solar panels?


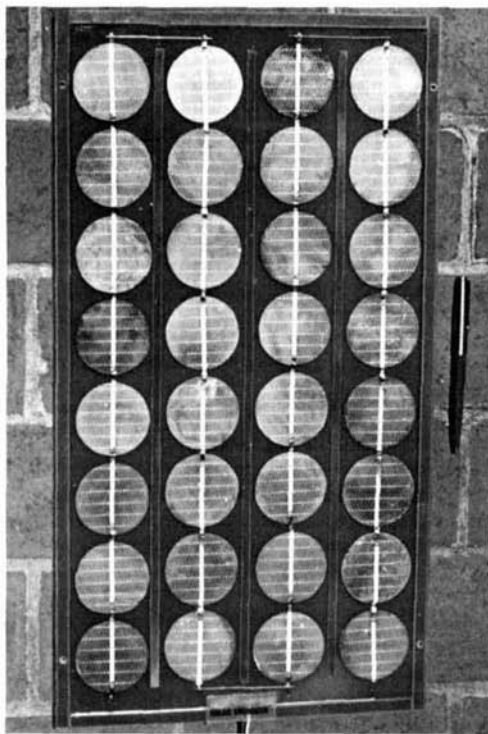


fig. 8. 12-volt, 500-mA solar panel (courtesy Solar Energy Company).

What additional capacity can be gained by using a mechanical mount that would permit you to chase the sun across the sky? Would an equatorial mount and clock-drive be practical? How would you hold the weight of the assembly down? What percentage of the derived power would be needed to power the drive system? Perhaps drive power could be conserved by changing positions only once each hour, or half-hour. I will be discussing these and similar subjects in the months ahead.

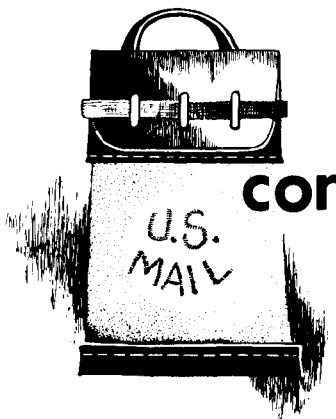[†]Solar Energy Company, 810 18th Street, NW, Washington, D.C. 20006.



comments

coherent fsk RTTY

Dear HR:

I would first like to commend Steve Maas, K3WJQ, for his article bringing modern communication theory into the area of amateur RTTY in the June, 1974, issue of *ham radio*. However, I feel that a few areas need comment. First, the numbers in **table 1** (page 32) for coherent FSK probability of error are slightly in error. The published data is based on a shift between the mark and space frequencies of $f_s \approx 0.7/T$, where T is a baud time.¹ For 60 wpm RTTY, $T = 0.022$ second, resulting in an f_s of only 32 Hz. It can be shown that this shift results in the lowest probability of error for coherent demodulation of FSK. However, for many practical reasons, this is too narrow a shift, so for standard 170- or 850-Hz shifts, that column should be amended to

input snr	probability of error coherent FSK
0 dB	0.16
2 dB	0.10
3 dB	0.08
6 dB	0.02
9 dB	0.002

The probability of error, as well as the Rayleigh and Rician probability density functions, are derived assuming no fading, with white noise having a Gaussian density function at the inputs of the mark and space filters. This is sometimes a good assumption, but primarily at vhf

and above. Since most RTTY activity is in the high-frequency spectrum, this white Gaussian noise assumption needs examination.

The National Bureau of Standards has attempted to model atmospheric noise.² They have found that the performance of an FSK demodulator can be several orders of magnitude worse than calculated by the white Gaussian noise assumptions, and this study didn't include QRM, which seems to be the most prevalent type of "noise" in our crowded bands.

The high-frequency spectrum is time varying with frequency-selective fading (QSB). This fading results in a tremendous degradation in the probability of error performance. Fading is thought to be due to constructive and destructive combining of various received signals that have been reflected from different layers of the ionosphere, resulting in a received signal with varying amplitude and with a random phase angle. So, while the transmitted phase may be constant, because of the varying time delays through the propagation path, the received signal can have any phase. It appears that demodulation schemes which require phase information, such as coherent FSK, are degraded *more* than noncoherent schemes.³

By requiring that a PLL (**fig. 4** in K3WJQ's article) remain close to the previously transmitted phase while the

1. Schilling and Taub, *Principles of Communications Systems*, McGraw-Hill, New York, 1970.

2. Alyce M. Conda, "The Effect of Atmospheric Noise on the Probability of Error for an NCFSK System," *IEEE Trans. on Communications Techniques*, September, 1965, page 280.

3. G.L. Turin, "Error Probabilities for Binary Symmetric Ideal Reception Through Non-selective Slow Fading and Noise," *Proceedings of IRE*, September, 1958, page 1603.

other channel is being transmitted would result in a very long time constant in the lowpass filter. This would also have the effect of increasing the time it takes for the PLL to lock up. PLLs in amateur demodulators have usually had the additional problem of locking on to a strong nearby interfering signal. Finally, there is evidence that the use of two oscillators at the transmitter end, which results in discontinuities in the phase of the transmitted signal, will have poorer performance than shifting the frequency of a single oscillator.⁴

Most mathematical analysis of systems like the one described in K3WJQ's article ignore the effect of one bit on the next. This problem is called intersymbol interference, and is found in any receiver having narrow bandpass filters. The degrading effects of intersymbol interference are extremely difficult to analyze, but they are of concern, as evidenced by the multitude of articles on attenuation and delay equalizers in the technical journals.⁵

The major causes of errors in an amateur's RTTY system thus seem to be those caused by fading, high atmospheric noise levels, interfering stations and intersymbol interference introduced by the propagation medium and receiver. Table 1, while slightly in error in practice, does point up the fact that a small increase in antenna gain can tremendously improve the performance. Also, for those fortunate hams with forty acres and unlimited resources, space diversity antenna systems reduce the effects of fading. Other known techniques for removing the effects of interference or fading, such as frequency diversity, error correcting codes and spectrum spreading methods, aren't looked upon favorably by the FCC.

4. P.A. Belle and B.D. Nelin, "The Effect of Frequency-Selective Fading on the Binary Error Probability of Incoherent and Differentially Coherent Matched Filter Receivers," *IEEE Trans. on Communications Systems*, June, 1963, page 170.

5. A. Gersho, "Adaptive Equalization of Highly Dispersive Channels for Data Transmission," *Bell System Technical Journal*, January, 1969, page 55.

I hope that the above comments will stimulate thinking on the design of FSK demodulators. The articles, such as the ones referenced, should provide indications as to the directions a design should take. I hope that I have shown that while I am enthusiastically for more theoretical articles in the amateur magazines, they should be tempered with the idea that mathematical analysis of various systems can be, at best, extremely difficult. The only way that a majority of amateurs, including myself, will be convinced of a new method's effectiveness is by seeing a working model perform as well or better than existing models.

John Fehlauer, WAZWTL
Gibbstown, New Jersey

bequests amateur gear

Dear HR:

Your March editorial was interesting and to the point regarding the disposition of a deceased ham's equipment. Specifically, it takes into account the fact that there is a big difference between *good* junk and *junk*. Too many of today's hams consider homebuilt equipment to be in the latter category, but I think I have the solution.

My will specifies that all of my equipment which can be categorized as amateur radio equipment and support parts shall be made available to the County Board of Education, with specific instructions that such items be sent to the local high school (which happens to have an amateur station). Further, I have specified that any taxes, fees and/or delivery costs be paid from my estate because I wanted to prevent any failure of delivery because of some cost or expense that the Board of Education might elect not to pay.

There are no strings attached, the high school will receive some valuable equipment and—hopefully—some youngster will learn something from the bequest.

Dean Young, W3FZ
Adelphi, Maryland




the ham notebook

identification timer

Lengthy QSOs and time-consuming phone patches can lead to problems with the FCC if you do not identify your station every ten minutes. After becoming an Official Observer I became aware of times between ID—especially those of ragchewing stations and stations running phone patches. Operators in these two categories tend to let time ramble by without the proper 10-minute identification. To alleviate this problem at my station I set out to build a timer that would accurately reproduce a 10-minute time out, have a minimum number of parts, and could be assembled in one evening. The circuit is shown in **fig. 1**.

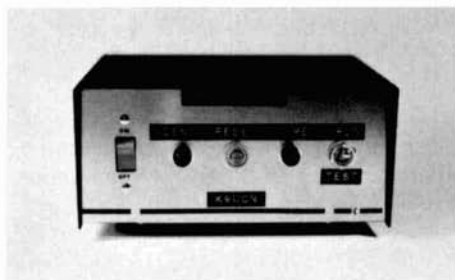This timer was designed around the Signetics NE555 integrated circuit. Any 9- to 12-volt dc supply can be used to run the timer. Once the power supply is turned on, the red lamp (*ident*) will light. The *run-test* switch is placed in the *test* position and the *reset* button should be



depressed and released. A ground at pin 2 will cause the green lamp to light and the red lamp to extinguish—indicating that the unit is *timing*. With the values shown the *test* position will allow a time cycle of 2 to 3 seconds after which the lamps will change from green to red (*ident*). Now

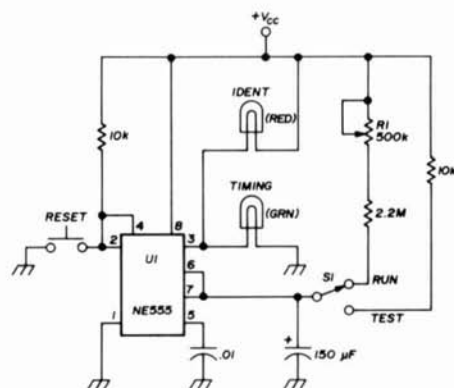


fig. 1. Simple ten-minute ID timer uses low-cost NE555 timer IC. Timing period, adjustable from 7 to 11 minutes, is set by R1.

place switch S1 in the *run* position. Again depress and release the *reset* button. The unit will time out between 7 and 11 minutes, depending on the setting of R1. I have R1 (500k pot) on my unit set to time out at 9 minutes. This allows a one-minute time frame in which to identify.

Even with $\pm 10\%$ variation from nominal supply voltage of 12-volt dc the timer retains a 9 minute, ± 1 second, accuracy. If during a timing cycle you

wish to identify your station and return to zero time it is only necessary to depress and release the *reset* switch. It is recommended that the indicator lamps draw no more than 100 mA each so as not to strain the current-sinking ability of the NE555 (200 mA max).

The total cost to build this timer is under five dollars. Circuit layout is not critical and component minimization makes the unit very reliable. With a timer like this one next to your phone patch you don't have to worry about being cited for lack of a correct 10-minute ID.

Don Backys, K9UQN

spurious signals

The October, 1973, issue of *ham radio* (page 67) carried details of Yaesu FTdx560/570 vfo frequency ranges, and the incorporation of the 6.358.6-kHz suck-out crystal in recent production. This was summarized in the December, 1972, issue (page 69), based on JA1MP's letter earlier in the year. This modification eliminated a 28-MHz spurious, but does not appear to affect the clean lower-sideband phone signals appearing in the 14-MHz DX band in a manner similar to those reported from the Yaesu FTdx400.

W6PKK added the crystal to his FTdx560, then retrimmed traps L18 and L19 (but not L23). His 14270-kHz upper-sideband transmissions caused lower-sideband spurious on 14080 kHz. Trimming eliminated the spurious completely at my location. In the case of a W7 who installed the suck-out crystal (\$5 plus COD postage), the 14197 lower-sideband spurious caused by the 14212 kHz upper-sideband transmission was not reduced; it presumably requires adjustment of the two traps as accomplished by W6PKK.

It appears that all Yaesu amateur equipment may have one or more traps which must be properly adjusted and the performance confirmed by listening tests.

A number of CW signals heard in the phone band may have been spurious from

the CW band on 14 MHz, but were not all investigated when heard. One was on about 14345 kHz. Several RTTY signals around 14085/14090 kHz have also been heard in the vicinity of 14220 kHz, these being from HW100, SB101, SB400 and SB401 equipment, according to information received. Some of these sets appear to depend upon a "bandpass coupler" out of the first mixer to suppress any undesired second harmonics of the input frequencies, or of the resulting output frequency. If the bandpass coupler is not sufficient, suitable traps might be applied to the first mixer output or the second mixer input (if two mixers are incorporated) to suppress the undesired products.

Information should be accumulated on the spurious performance of all types of amateur equipment, and the necessary cure for any spurious emissions or responses, to eliminate unnecessary receiver interference.


Bill Conklin, K6KA

full-quieting meter for Clegg 27B

Many amateurs who use the Clegg 27B as a base rig have wanted a visual indication of incoming signal strength for peaking up mobile signals and for keying up repeaters. This can be simply accomplished as follows: Connect one end of a piece of miniature RG-74/U coaxial cable, center conductor to the orange wire on the squelch control and braid to the yellow wire of the squelch control. Run the RG-174/U coax back to the hole near the antenna connector and connect it to a miniature 1/8-inch female connector. For the meter, which is connected to the coax with a matching 1/8-inch male connector, I used a 0-500 microampere meter. A 0.01- μ F capacitor across the meter will smooth out any needle movement. Make sure the cable braid is not grounded at any point as this will bypass the squelch circuit and make it inoperative.

Tom Clerk, WA2YUD

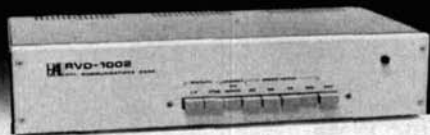Explore the world of RTTY... with sophisticated equipment from HAL.



The RVD-1002. The silent, reliable RTTY video display unit from HAL.

The revolutionary HAL RVD-1002 RTTY video display unit "prints" an RTTY signal from any TU at the four standard data rates (60, 66, 75 and 100 WPM), using a TV receiver with slight modification. Or it will directly feed a TV monitor. Power consumption is low, thanks to the RVD-1002's solid-state construction. So turn on to silent, trouble-free RTTY — with the RVD-1002.

Price: \$575 ppd, USA. Air shipment \$10.



The silent RTTY keyboard — that's the HAL RKB-1.

The RKB-1 TTY keyboard is loaded with features to make sending RTTY easy and fun. You get automatic letter/number shift at all four speeds, typewriter keyboard layout, and no clatter! The loop keying transistor is isolated from other keyboard circuits — wire it into any convenient point in your loop. Plus TTL logic, glass epoxy PC board, commercial grade keyswitches and more.

Price: \$250 Assembled, ppd USA. Air shipment \$5.



RTTY — and CW on one keyboard! The HAL DKB-2010.

All solid-state. Transmit at data rates of 60, 66, 75 or 100 WPM at the flick of a switch. Complete alphanumeric keys, 15 punctuation marks, 3 carriage control keys, 2 shift keys, break key, 2 character function keys, a "DE-call sign" key, even a "Quick brown fox..." test key.

The DKB-2010 is equally versatile in the CW mode, with complete alphanumeric and punctuation keys, speeds from 8-60 WPM, and a "DE-call sign" key. The DKB-2010 includes a three-character buffer operational in either the RTTY or CW mode. Optional 64 or 128 key buffer also available.

Price: \$425 Assembled, \$325 Kit, ppd USA.
64 key buffer \$100, 128 key buffer \$150.
Air shipment \$10.



Commercial quality on an amateur's budget — the HAL ST-6 TU

Every amateur who knows his RTTY respects the ST-6 terminal as being the best. Autostart operation, an antispaces feature and switch selection of 850 and 170 Hz shifts are standard. Circuitry is state-of-the-art, including DIP IC's on plug-in PC cards. Filters and discriminators are designed for standard RTTY tones. A 425 Hz shift discriminator is an option which allows superior reception when copying commercial press transmissions. Another option is the AK-1 audio frequency shift keyer for input to an SSB transmitter. The ST-6 and its options are available in assembled or kit form. Cabinet not included in kit.

Price: ST-6 \$310 Assembled, \$147.50 Kit, ppd USA.
425 Hz Discriminator \$40 Assembled, \$29 Kit, ppd USA.
AK-1 AFSK \$40 Assembled, \$29 Kit, ppd USA.
Air shipment: Assembled ST-6 with any or all options \$10, ST-6 Kit \$4, 425 Hz Kit \$1, AK-1 Kit \$1.



HAL Communications Corp.
Box 365, Urbana, Illinois 61801
Telephone: (217) 359-7373

Enclosed is \$_____ for: RVD-1002 RKB-1 DKB-2010 ST-6
Please specify Assembled Kit Options _____
Please send me more information on the following HAL products
 RVD-1002 RKB-1 DKB-2010 ST-6
 Complete HAL catalog

Name _____ Address _____ Call Sign _____

City/State/Zip _____ Illinois residents add 5% sales tax.

How to win the fist fight... with CW equipment from HAL.



The economical HAL 1550 keyer.

The easy-to-use 1550 keyer is your answer if you're looking for an electronic keyer that lets you send accurate CW effortlessly. Send from 8 to 60 WPM with conventional, iambic, and dot memory operation. Operates with dual or single lever keys. The optional 1550/ID automatically sends "DE" followed by your station call. For fast, accurate CW, order the HAL 1550/ID or 1550 today.

Price: 1550/ID, \$95; 1550, \$75; ppd USA. Air shipment, add \$3.



ID-1A repeater identifier. Commercial quality, low price.

The HAL ID-1A brings the radio amateur a commercial-quality repeater identifier that complies with FCC ID requirements. It has a unique read-only-memory that you can easily reprogram yourself. Capacity of the ROM is 39 dots, dashes and spaces. TTL IC's assure immunity from noise and temperature. ID intervals available: 3, 6, 12 or 24 min. Specify call.

Price: \$115, ppd USA. Air shipment, \$3.



Send perfect CW every time with the MKB-1.

A complete Morse keyboard. Code speed variable from 10-60 WPM with variable dot-to-space ratio (weight). All solid-state, featuring computer-grade components. Complete alphanumeric and punctuation keys, plus an optional "DE-call sign" key factory programmed for you. Includes built-in speaker/oscillator monitor.

Price: \$290 Assembled, \$199 Kit, ppd USA. Without ID, \$250 Assembled, \$170 Kit. Air shipment, \$5.



CW — and RTTY on one keyboard! The HAL DKB-2010.

All solid-state. Type out CW at 8-60 WPM. Adjustable dot-to-space ratio (weight). Complete alphanumeric keys, plus 11 punctuation marks. Five standard two-character keys, 2 shift keys, break-for-tuning key, 2 three-character function keys, and a "DE-call sign" key. We'll program your call right into the DKB-2010. Plus complete RTTY capabilities. Built-in three-character buffer. Optional 64 or 128 key buffer also available.

Price: \$425 Assembled, \$325 Kit, ppd USA. 64 key buffer \$100, 128 key buffer \$150. Air shipment, \$10.



HAL Communications Corp.
Box 365, Urbana, Illinois 61801
Telephone: (217) 359-7373

Enclosed is \$_____ for: DKB-2010 MKB-1 1550 ID-1A
Please specify Assembled Kit Options _____
Please send me more information on the following HAL products . . .
 DKB-2010 MKB-1 1550/1550 ID ID-1A
 Complete HAL catalog

Name _____ Address _____ Call Sign _____

City/State/Zip _____

Illinois residents add 5% sales tax.

The "STANDARD" by Heights

Light,
permanently
beautiful
ALUMINUM
towers

**THE MOST
IMPORTANT
FEATURE OF
YOUR ANTENNA
IS PUTTING
IT UP WHERE
IT CAN DO
WHAT YOU
EXPECT.
RELIABLE DX —
SIGNALS EARLIEST IN
AND LAST OUT.**

ALUMINUM

Self-Supporting
Easy to Assemble
and Erect

All towers mounted
on hinged bases

Complete Telescoping
and Fold-Over
Series available


And now, with motorized options, you can crank it up or down, or fold it over, from the operating position in the house.

Write for 12 page brochure giving dozens of combinations of height, weight and wind load.

HEIGHTS MANUFACTURING CO.

In Almont Heights Industrial Park
Almont, Michigan 48003

PORTA-PAK

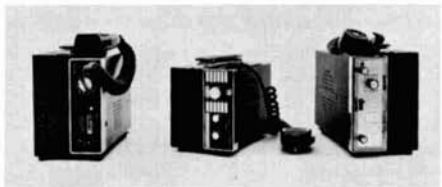

The accessory that makes your mobile radio really portable. Models available to fit most transistor transceivers. No holes to drill, it fastens with and thru the mounting holes provided for the mobile bracket.

PORTA-PAKS are attractively finished in textured vinyl or black wrinkle and are baked for durability and lasting good looks. The **DELUXE PORTA-PAK** features a battery with no free electrolyte to spill. A charger and plug-in for it are provided.

Models in stock include: Regency HR6, HR2B, BTL, BTH, MT25, MT15; Genave, all models; Heathkit HW202; Icom 230; Midland; Standard.

DELUXE PORTA-PAK **\$59.95**
ups prepaid

REGULAR PORTA-PAK **\$39.95**
ups prepaid

PORTA-PAK

P. O. BOX 67
SOMERS, WISCONSIN 53171

USED TEST EQUIPMENT

All checked and operating unless otherwise noted. FOB Monroe. Money back (less shipping) if not satisfied.

Boonton 190A Q-mtr 20-260 MHz Q5-1200	375
Boonton 202B Sig Gen AM-FM 54-216 MHz	325
Boonton 202D (sim. to above) 175-250 MHz	225
HP100D-Freq. stand. w/scope-Acc. 1ppm	85
HP185A Scope w/186B amp sampling 1gHz	335
HP202A Function Gen. .008-1200Hz	95
HP205AG Audio Gen. .02-20kHz-metered	195
HP330B Dist anal 20 Hz-20kHz .1%	205
HP524D-Freq Counter. Basic unit 10Hz-10MHz	185
HP540B Trans osc. for 524 to 12.4gHz	185
HP608D (TS510A/U) sig. gen. 10-420MHz	450
HP610B Sig Gen .45-1.2gHz calib attn	365
HP803A Imp Bridge 50-500MHz, 2-200 ohm	195
Panoramic SPA-4 Spec. Anal. Bandswitching. 10MHz-44gHz, 5 or 70MHz sweep width	985
Polarad MSG34-Sig. Gen 4.2-11gHz calib attn. AM-FM-Pulse mod.	495
Polarad R uwave rcvr .4-84gHz with plug-in AM, FM, CW, Pulse - less plug-in	225
Polarad TSA Spec. Anal .01-44gHz with plug-in less plug-in	125
Soliton 200A SCR tester-checks anode, gate volts, current, leakage and holding	165
Stoddart NM10A (URM-6) RF intens mtr 10- 250 kHz, complete with acc.	630
Stoddart NM20A (PRM-1) RF intens mtr .15- 25MHz, complete with acc.	155
Stoddart NM52A-RFI mtr .375-1gHz, w/acc.	655
Tek RM 15-DC-15MHz GP scope	265
Tek 181 Time mark generator	95
Tek 190A Const. Ampl. Sig. Gen. 35-50MHz	125
Tek 565 dual beam 10MHz scope, less plug-ins	625
TS-403A-Sig. Gen. (HP616) 1.8-4gHz	385
URM 7 RI-FI mtr. (sim. NF-105) 20-400MHz	750

GRAY Electronics
P. O. Box 941, Monroe, MI 48161
(Send SASE for complete list)
Specializing in used test equipment

SAROC

JANUARY 2-5, 1975

Tenth National Convention

Hotel Sahara Space Center, Las Vegas, NV

DEL WEBB'S HOTEL
SAHARA
LAS VEGAS, NEVADA

Advance Registration, \$11.00 per person, includes:

1. Advance Registration ticket.
2. Regular Registration ticket.
3. Admission ticket to Social Hour, hosted by T. P. L. Communications and TRI-EX Tower Corp. with SAROC on Friday.
4. Admission to Exhibit Area and Technical Sessions.
5. Ladies will receive an additional ticket.
6. Admission ticket to Social Hour, hosted by Ham Radio Magazine with SAROC on Saturday.
7. Hotel Sahara Safari Brunch ticket for Sunday.
8. Tax and Gratuity on all items listed.

Advance Registration, with midnight show, \$21.00 per person:

Includes all items 1 thru 8, plus Hotel Sahara's midnight show with two drinks in the Congo Room starring Totie Fields.

Advance Registration, with dinner show, \$27.42 per person:

All items 1 thru 8, plus Hotel Sahara's Dinner Show, no drinks, in the Congo Room starring Totie Fields.

Mail your SAROC Advance Registration check now to SAROC, P. O. Box 945, Boulder City, Nevada 89005, must be received before 15 December 1974.

Full refund on advance registration if written request is received in SAROC, P. O. Box 945, Boulder City, Nevada before 2 January 1975.

Special airfares via United Airlines round trip to Las Vegas, Nevada from selected cities, includes three nights accommodations, SAROC Advance Registration, Dinner Show, Tax and Gratuity. Request complete details from SAROC, P. O. Box 945, Boulder City, Nevada 89005.

Call toll free 800-634-6666 for Del Webb's Hotel Sahara accommodations, for SAROC special room rate of \$15.00 per night, plus room tax, single or double occupancy, effective January 2-6, 1975.

hy-gain 2-meter antenna for hand-held transceivers

144-148 MHz

This rubber duckie
is one
tough antenna!


When the going gets tough, Hy-Gain's flexible 2-meter antenna is the one to have. So short, it goes where whips can't. Continuously loaded for optimum performance and completely insulated with a special vinyl coating, it won't crack or break, no matter how you bend it. Cannot be shorted out accidentally! Designed with the same care and excellence in engineering that produces our superb commercial and mobile antennas. Whether your 2-meter hand-held is one of the fine commercially available units or a beauty you built yourself, this is the antenna that can go where you go!

Available with three connector types and tuned for optimum performance:

Order No. 274 BNC or 'snap' fitting, fits Tempo, Wilson, Ken Product, Klegg and other popular hand-held 2-meter transceivers.

Order No. 275 Accepts SO-239 connector, fits Drake and Motorola.

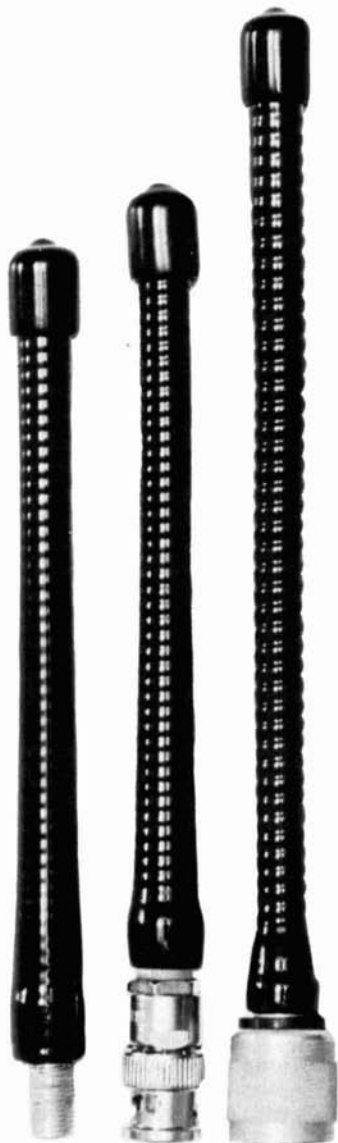Order No. 269 Male screw 5/6 x 32, fits Motorola, GE, Johnson, RCA and CommCo.



For information on the complete line of fine Hy-Gain Amateur products, see your Hy-Gain distributor or write:

hy-gain

Hy-Gain Electronics Corporation; 8601 Northeast Highway Six; Lincoln, NE 68507; 402/464-9151; Telex 48-6424
Branch Office and Warehouse; 6100 Sepulveda Blvd., #322; Van Nuys, CA 91401; 213/785-4532; Telex 65-1359.
Distributed in Canada by Lectron Radio Sales, Ltd.; 211 Hunter Street West; Peterborough, Ontario.

ODDS & ENDS

HERE IS A PILE OF GOODIES THAT WE THOUGHT YOU WOULD LIKE TO KNOW ABOUT . . . SOME ARE ONE OF A KIND, SO DON'T DELAY IF YOU SEE SOMETHING YOU LIKE.

RADIOS

- GENERAL ELECTRIC, VOICE COMMANDER IIIs.** Hi band tech specials that need some work, with nicad **\$49.00**
- PT 300s** . . . Lo band, 5 watt, 30-42 MHz units. "Tech Specials". Less nicad & mic. **\$70.00**
- 250 WATT Lo Band Base** . . . FSTR520BR, 30-40 MHz. Ideal for conversion to 10 meters **\$170.00**

TEST EQUIPMENT

- HEWLETT PACKARD, 400C AC VTVM.** Calibrated **\$80.00**
- BECKMAN/BERKELEY 7570** amplifier with 7571 & 7573 converters to 220 MHz. Unchecked. **\$75.00**
- BECKMAN 5580** Reference Generator. Unchecked **\$75.00**

ODDS & ENDS

- HO3BNC NICADS** . . . good condx out of code surplus **6/\$10.00**
- HT220 NICADS** . . . good used omni rapid charge units **\$10.00**
- MULTIPLE PL HEADS** for Motracs, less reeds **\$10-\$20.00**
- BLOWER MOTORS** for T44 series bases & repeaters. Original cost \$80.00+. Get a spare NOW only **\$5.00**
- PTT HANDSETS** . . . mint condx, turquoise only **\$7.00**
- H23BAM AC SUPPLIES**, model NPN6012A, mint condx **\$35.00**
- 12VDC SUPPLY**, ideal for use with T33BAT mobiles with minor mod. With print model NPN6034 **\$18.00**
- PERMAKAY FILTERS** . . . good supply of wide band for Tracs **\$3.00**
- TR RELAYS** . . . from 80D series radios. 12 VDC prox 60W rating at 150 MHz **\$4.00**
- P8270 REMOTE** . . . Desk top 2 wire control unit **\$45.00**
Same as above but for parts only **\$19.00**

TERMS OF SALE: Sales to licensed Radio Amateurs for use on Amateur freqs only. All prices FOB Oak Park, IL. Check with order, COD or you can charge to your BankAmericard or Master Charge.

STORE HOURS: Mon.-Thurs. 9:30-6:00, Fri. 9:30-8:00, Sat. 9:30-3:00. Closed Sun. & Holidays
INQUIRIES WITHOUT ZIP CODE OR CALL . . . NO ANSWER

WANTED: Good used FM & test equipment. No quantity too large or small. Finders fees too.



SPECTRONICS INC.

1009 GARFIELD STREET
OAK PARK, ILL. 60304
(312) 848-6778

AMATEUR SALES ONLY / SPECTRONICS / The FM people





CRYSTAL FILTERS and DISCRIMINATORS

1 27/64" x 1 3/64" x 3/4"



by
K.V.G.

10.7 MHz FILTERS

XF107-A	14kHz	NBFM	\$40.60
XF107-B	16kHz	NBFM	\$40.60
XF107-C	32kHz	WBFM	\$40.60
XF107-D	38kHz	WBFM	\$40.60
XF107-E	42kHz	WBFM	\$40.60

10.7 MHz DISCRIMINATORS

XD107-01	30kHz	NBFM	\$22.10
XD107-02	50kHz	WBFM	\$22.10
XM107-SO4	14kHz	NBFM	\$18.95
XF102	14kHz	NBFM	\$7.95

(Export inquiries invited)

CRYSTAL SOCKET (for XM107-SO4) type DG1 \$1.50

UHF VARACTOR MULTIPLIERS

Model	MMv432	MMv1296	MMv432H	MMv1296H
Frequency Range				
Output MHz	420-459	1260-1377		
Input MHz	140-153	420-459		
Input Power max.	20 W.	20 W.	70 W.	35 W.
Output Power at Max. i/p.	12 W.	10 W.	35 W.	20 W.
Typical	14 W.	12 W.		
PRICE	\$75.20	\$85.95		

High Power units to special order.

No Power Supply Required.
All specifications apply to 50 ohm input/output system.
Construction Die cast aluminum box.
Size 4.5 x 2.5 x 1.25 ins. + connectors.
Broad band design, NO tuning required.
Shipping: Filters 50c; Varactor Multipliers \$1.00.



**SPECTRUM
INTERNATIONAL**
BOX 1084 CONCORD
MASSACHUSETTS 01742
U. S. A.

R-X NOISE BRIDGE



- Learn the truth about your antenna.
- Find its resonant frequency.
- Find R and X off-resonance.
- Independent R & X dials greatly simplify tuning beams, arrays.
- Compact, lightweight, battery operated.
- Simple to use. Self contained.
- Broadband 1-100 MHz.
- Free brochure on request.
- Order direct. \$39.95 PPD U.S. & Canada (add sales tax in Calif.)

**PALOMAR
ENGINEERS**

BOX 455, ESCONDIDO, CA 92025

- PCB KITS -

RTTY SPEED CONVERTER/Drilled PCB 5 & 11 VDC	\$42.00
DRILLED PCB ONLY	\$ 6.50
RTTY AFSK Gen. All Shifts & CW I.C. 9 VDC @ 2ma	\$7.25
100 kHz XTAL CALIBRATOR Less Xtal 9 VDC @ 2ma	\$5.25
POWER SUPPLY — 28 VDC @ 650 ma output	\$9.85
PREAMP MICROPHONE 26 dB Gain 9 VDC @ 1ma	\$3.85
LIMITER PREAMP For High Z Mike 9 VDC @ 1ma	\$5.30
PRODUCT DETECTOR For Your Receiver 9 VDC @ 1ma	\$3.95
"S" METER KIT Less 1ma Meter	6.3VAC \$5.25
SWR METER, Stripline, Less 200 μ a Meter	\$3.25
WWV CONVERTER 3.5-4.0 MHz Output 9 VDC @ 5ma	\$5.75
Requires 6-6.5MHz Crystal	
6 METER CONVERTER FET Front End 9 VDC @ 5ma	\$6.50
7-11 MHz Output, Less 43 MHz Xtal	
CW KEYING MONITOR, RF Keyed, Less Spkr. 9 VDC @ 9ma	\$5.20
POWER SUPPLY - 9 VDC @ 50ma Output 115VAC	\$5.35
6 METER CASCODE PREAMP 80 VDC @ 4.5ma	\$5.45
Wired & Tested Less 2 ea 6CW4 Nuvistors	
DRILLS, #54, 56, 58 or 60	(each) \$.50
Finest Quality for PCB's, Made in USA	Three For \$1.25

EXCEPT AS NOTED ABOVE, ALL KITS ARE NEW, 100% SOLID STATE, AND COME COMPLETE WITH AN UNDRILLED G-10 PCB (PRINTED CIRCUIT BOARD) AND ALL PCB MOUNTED COMPONENTS. KITS ARE LESS POWER SUPPLIES, CHASSIS, AND ENCLOSURE HARDWARE. SEND SELF-ADDRESSED, STAMPED ENVELOPE FOR COMPLETE DATA SHEET AND SCHEMATIC.

SATISFACTION GUARANTEED. RETURN IN 30 DAYS FOR REFUND. ALL KITS POSTPAID. INCLUDE 50¢ HANDLING CHARGE. WASHINGTON RESIDENTS ADD 5.3% SALES TAX.

Martex Corporation

519 S. AUSTIN, SEATTLE, WASH. 98108

Come Face to Face with the facts...

IC-21A . . . 24 channel capability, with 7 channels supplied. It's MOSFET front end provides better than 0.4uv sensitivity at 20 db quieting. 5 HELICAL FILTERS virtually eliminate intermodulation. Built in AC and DC power supplies. Modular construction, of course. Many other features make the IC-21 a great two meter transceiver. The IC-21A is capable of using our new digital VFO.



...and choose ICOM

IC-22 . . . 22 channel capacity, with 5 supplied. Solid state T-R switching, and an extra large speaker. All the great quality features that label it as one of the truly fine ICOM transceivers. 10/1 watt power saving option. Trimmer caps on all 22 channels for both transmit and receive, plus a built in discriminator jack to let you get on and stay on frequency.

The **IC-3PA** is a regulated DC power supply for all the INOUE mobile transceivers. Use it with your IC-230 for base operation. It's completely regulated and gives you an indication of it's operating condition: normal, excessive current, or if the protection circuit is working. These are shown through the use of eye catching indicator lamps. There is also a built in speaker in the cabinet.



Distributed by: **ICOM WEST, INC.**, Suite 232 - Bldg. II, 300 - 120th Ave. N.E., Bellevue, Wash. 98005 (206) 454-2470
Dealerships Available: **ICOM EAST Div. ACS Inc.**, Suite 501, 13777 N. Central Expwy., Dallas, Texas, 75231 (214) 235-0479

300 MHz PRESCALER MODEL PD-301

Model PD 301 is a 300 MHz. prescaler designed to extend the range of your counter 10 times. This prescaler has a built-in preamp with a sensitivity of better than 50 mv at 150 MHz, 100 mv at 260 MHz, and 175 mv at 300 MHz. The 95H90 scaler is rated at typical 320 MHz. To insure enough drive for all counters, a post amp. was built-in.

The prescaler has a self contained regulated power supply. The PD 301 is supplied without power supply if desired (input 50 Ohms) (output Hi Z). The PD 301 has been tested on the following counters: Heath Kit 1B101 - Heath Scientific 105 - Monsanto 105A - Miida - Regency - Beckman - Hewlett - Packard 524B - and many home built. In short to this date we do not know of any counter that the PD 301 has failed to work well with. All prescalers are shipped in a 4" x 4" x 1 1/2" cabinet all wired and tested.



- PD 301 Kit With Power Supply \$43.50
 PD 301 With Power Supply \$55.50
 PD 301 Without Power Supply \$50.50

Include \$1.50 to cover postage and insurance.

Shipped Same Day Order Received

K-ENTERPRISES

1401 N. Tucker Shawnee, Okla. 74801

RIGHT ON FREQUENCY!



**±100Hz
ACCURACY
ASSURED!**

DIGITAL DIAL MODEL 22

Interchangeable input module to match your present or next rig.


AVAILABLE FOR VFO'S IN:
**Swan • Kenwood • Collins
 Heathkit • Hallicrafter
 Galaxy • Drake — others.**

MODEL 22K (KIT) \$135.95
 MODEL 22W (WIRED) \$169.95

ORDER DIRECT OR WRITE FOR BROCHURE AND NAME OF NEAREST DEALER.



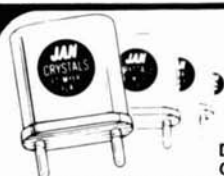PHONE: (814) 432-3647
 BOX 185-A • FRANKLIN, PA. 16323



For FREQ. STABILITY

Depend on JAN Crystals. Our large stock of quartz crystal materials and components assures Fast Delivery from us.

CRYSTAL SPECIALS

- 2-METER FM for most Transceivers ea. \$3.75
 144-148 MHz — .0025 Tol.
- | | |
|---|------|
| Frequency Standards | |
| 100 KHz (HC 13/U) | 4.50 |
| 1000 KHz (HC 6/U) | 4.50 |
| Almost all CB Sets, Tr. or Rec. | 2.50 |
| (CB Synthesizer Crystal on request) | |
| Any Amateur Band in FT-243 | 1.50 |
| (80-meter, \$3.00 - 160-meter not avail.) 4 for 5.00 | |
| For 1st class mail, add 20¢ per crystal. For Airmail, add 25¢. Send check or money order. No dealers, please. | |




Division of Bob Whan & Son Electronics, Inc.
 2400 Crystal Drive
 Ft. Myers, Florida
 33901

All Phones
 (813) 936-2397

Send 10¢ for new catalog with 12 oscillator circuits and lists of frequencies in stock.

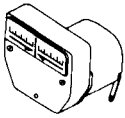COOL 30-0-30 V - 2.5 AMP SHIELDED TRANSFORMER — NEW — AMERICAN MADE YES
— 3 pound with 1 3/4" deep core vertical end bell mount. 2 1/4" w. x 3" h. x 3 1/4" deep, with 6.3 V - 1A winding. \$4.85 ppd.




NEW — IMPORTED

MINI-METERS —
50-0-50 μ A, 1" square, 3/4" deep. Center zero plastic body fits 3/4" dia. or 3/4" x 5/8" opening. White scale can be rear lighted. Ideal for tuning null. \$1.25 ppd.

NEW — UNUSED

ORGAN MFR. OVERRUN

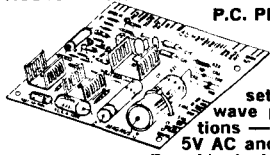AUDIO AMPLIFIER — Med. Power 4 3/4" x 6" P.C. PLUG-IN ASSEMBLY



Uses 4 amp-70V Complimentary pair output transistors with 2nd set as drivers. 2 full wave power supply sections — need only 26 and 5V AC and signal. Complete Board/untested \$4.80 ppd.

63 Components Tested \$5.75 ppd.

INTEGRATED CIRCUITS

7400	33¢ ea.	741 c Op Amp	55¢ ea.
7473	60¢ ea.	747 Dual Op Amp	\$1.25 ea.
7475	90¢ ea.	723 Regulator	\$1.00 ea.

UNPOTTED TOROIDS — All toroids are center tapped, 88MHY
Price is a low 5 for \$2.75 ppd.

METER PROTECTOR

Protect that expensive meter. Our proven, tested, guaranteed meter protector will protect your meter movement against 100% overload when installed according to instructions. Price: 75¢ each or 4 for \$2.50 ppd.

PRINTED CIRCUIT BOARD MATERIAL — ALL G10 — Direct from the factory mfg. by Westinghouse. All board is 1/16" with 2 oz. copper.

3" x 3"	45¢
3" x 6"	85¢
6" x 9"	\$2.75
12" x 12"	\$6.00

All ppd. U.S.A.

VERTICAL MOUNT PC BOARD POTENTIOMETERS


American made (CRL) high quality pots. Available in the following sizes: 25,000 ohms, 50,000 ohms, 100,000 ohms. Price is 5 for \$1.00 ppd.



3 inch 4 ohm VC Square frame with 4 mounting holes. \$1.20 each ppd.

PL-55 TYPE PHONE JACKS

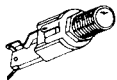High quality American made jacks. 3/8 inch mounting with hex nut. Extends 1 1/8" behind the panel. Price: 50¢ each or 3 for \$1.25 ppd.




ILLUMINATED ROCKER SWITCH

American made UL approved. Rating: 125 Volt AC 3 Amp 125 Volt DC .5 Amp DPDT with a 6 volt illuminating bulb. Your choice of color. Red or White. Price is 80¢ each or buy 3 for \$2.25 ppd. USA




9 PIN SOCKET — SNAP-IN MINIATURE for P.C. Board Mtg. 6 for \$1.00 ppd.

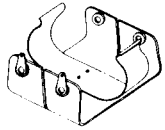ALUMINUM BATTERY BOX
American made, high quality. Holds two type 'C' cells. All terminals insulated.



55¢ each ppd.

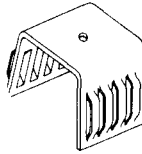


ALUMINUM HEAT SINK
Very nice American made heat sink. 1/16 inch thick and approx. dimensions are 1" x 1" x 1" high with an 1/8 inch hole in the center. Price is a low 35¢ each or 3 for \$1.00 ppd.



RED NYLON CABLE TIES BALL-BEAD TYPE — 4 1/4" LONG
Price is 70 for \$1.00 ppd.

HIGHEST QUALITY, AMERICAN MADE POWER CORD

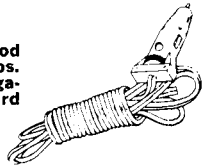6 Foot Gray Cord. Good For At Least 7 Amps. Plugs Into Auto Cigarette Lighter. A Hard To Find Item. 75¢ Each or 3 For \$2.00 ppd.



NEW NEW NEW

3/16 inch Dia. LED Lites
Red \$.25 ea. ppd.
Green \$.40 ea. ppd.
Yellow \$.40 ea. ppd.
Super BI-LED — Lites red with polarity one way and green when you reverse the polarity. Neat for many things. Price is a low \$.75 ea. ppd.



Transformer — 115 Volt Primary — 12 Volt 1.2 Amp Secondary \$2.45 ppd.

JUST ARRIVED — Transformer, 115 VAC primary, 18 volt, 5 amp ccs or 7 amp intermittent duty secondary \$6.00 ea. ppd.

General Purpose Germanium Diodes
Similar to 1N34a etc. 15 for \$1.00 ppd.
All Cathode banded. 100 for \$5.00 ppd.
Full leads. 1000 for \$40.00 ppd.

Transformer — American Made — Fully shielded. 115 V Primary Sec. — 24-0-24 @ 1 amp with tap at 6.3 volt for pilot light. Price — A low \$2.90 each ppd.

Power Transformer, 115 Volt AC Primary. Secondary #1: 32-0-32 Volt @ 1 Amp. Secondary #2: 6.3 Volts. Low Current For Pilot Lights. Size 2 1/2" x 2 1/2" x 3". Price: \$2.50 Each ppd.

6.3 Volt 1 Amp Transformer, Fully Shielded. \$1.60 Each ppd.

SEND STAMP FOR BARGAIN LIST

Pa. residents add 6% State sales tax
ALL ITEMS PPD. USA

Canadian orders for less than \$5.00 add \$1.00 to cover additional postage costs.

m. weinschenker
K 3DPJ BOX 353 · IRWIN, PA. 15642

NOW! BUY DIRECT

WHAT DOES THIS MEAN?

It means that GENAVE'S outstanding line of Amateur radios is now available to you at new, inflation-beating prices. A glance at the new prices confirms that the dealer's discount has been entirely eliminated, to your benefit. The same fine radios that you've seen in his shop may now be ordered on a Factory-Direct basis. **You** pocket the savings. Warranty policies remain the same: if your new GTX fails within three months of purchase, send it back. We'll fix it or replace it, **fast**.

Order TODAY—Orders will be processed as they are received!

Standard crystal frequencies in stock @ \$3.75 each:

1 1/4 Meter		2 Meter		6 Meter	
TX	RX	TX	RX	TX	RX
222.30	223.50	146.01	146.34	52.25	52.38
222.34	223.90	146.10	146.52	52.525	52.525
222.38	223.94	146.12	146.61	52.70	52.60
223.14	223.98	146.16	146.70	52.76	52.64
223.26	224.74	146.19	146.72	52.82	52.68
223.30	224.86	146.22	146.76	52.88	52.72
223.34	224.90	146.25	146.79	52.92	52.79
223.50	224.94	146.28	146.82	52.96	52.80
		146.34	146.85	53.15	53.05
		146.52	146.88	53.25	53.08
		146.94	146.94	53.68	53.16

Contact factory for prices on other crystal frequencies.

Made In U.S.A.



**USE THIS HANDY ORDER FORM
TO HELP YOURSELF
TO GIANT SAVINGS!**



General Aviation Electronics, Inc., 4141 Kingman Drive, Indianapolis, Indiana 46226—Area 317-546-1111

for GIANT SAVINGS!



GTX-600 6-Meter FM
100 channels, 35 watts

WAS \$309.95

NOW
\$219⁹⁵

(Incl. 52.525 MHz)



GTX-100 1 1/4-Meter FM
100 channels, 12 watts

WAS \$309.95

NOW
\$219⁹⁵

(Incl. 223.5 MHz)



GTX-2 2-Meter FM
10 channels, 30 watts

WAS \$299.95

NOW
\$189⁹⁵

(Incl. 146.94 MHz)



GTX-200 2-Meter FM
100 channels, 30 watts

WAS \$299.95

NOW
\$199⁹⁵

(Incl. 146.94 MHz)



GTX-10 2-Meter FM
10 channels, 10 watts

WAS \$239.95

NOW
\$169⁹⁵

(Incl. 146.94 MHz)

CLIP OUT AND ORDER NOW!



GENAVE, 4141 Kingman Dr., Indianapolis, IN 46226

HR

HEY, GENAVE! Thanks for the nice prices! Please send me:

- | | |
|--|--|
| <input type="checkbox"/> GTX-600 @ \$219.95 \$ _____ | <input type="checkbox"/> Lambda/30 2-M Base Antenna @ \$59.95 \$ _____ |
| <input type="checkbox"/> GTX-200 @ \$199.95 \$ _____ | <input type="checkbox"/> Lambda/6 2-M Trunk Antenna @ \$29.95 \$ _____ |
| <input type="checkbox"/> GTX-100 @ \$219.95 \$ _____ | <input type="checkbox"/> TE-1 Tone Encoder Pad @ \$59.95 \$ _____ |
| <input type="checkbox"/> GTX-2 @ \$189.95 \$ _____ | <input type="checkbox"/> PSI-9 Port. Power Package @ \$29.95 \$ _____ |
| <input type="checkbox"/> GTX-10 @ \$169.95 \$ _____ | <input type="checkbox"/> PS-1 AC Power Supply @ \$49.95 \$ _____ |

and the following **standard** crystals @ \$3.75 each: _____ \$ _____

Sub-Total \$ _____ Ind. residents add 4% sales tax: _____ Cal. residents add 6% sales tax: _____ **TOTAL: \$ _____**

All orders shipped post-paid within continental U.S. For C.O.D., Include 20% Down.

NAME _____ AMATEUR CALL _____

ADDRESS _____ CITY _____ STATE & ZIP _____

Payment by: Certified Check/Money Order Personal Check C.O.D.

Note: Orders accompanied by personal checks will require about two weeks to process.

20% Down Payment Enclosed. Charge Balance To:

BankAmericard # _____ Expires _____

Master Charge # _____ Expires _____ Interbank # _____

Prices and specifications subject to change without notice.

First in its class!



Introducing the Galaxy R-1530. A receiver of remarkable performance, the first in its class to combine true professional features and moderate cost. It adds a new dimension of performance to general coverage, monitoring, shortwave listening, commercial and military communications.


Frequency range: 0.1 to 30 MHz continuous (.01 to .1 with reduced sensitivity) • Sensitivity: 0.25 microvolts for 10 db signal plus noise to noise ratio SSB • Intermodulation Distortion: 3rd order suppressed more than 70 db • Front-End Overload: .1 volt for 10% distortion (On Signal)

For prices and information, contact your local Hy-Gain distributor or write Hy-Gain.

hy-gain

Hy-Gain Electronics Corporation; 8601 Northeast Highway Six; Lincoln, NE 68507; 402/464-9151; Telex 48-6424.
Branch Office and Warehouse; 6100 Sepulveda Blvd., #322; Van Nuys, CA 91401; 213/785-4532; Telex 65-1359.
Distributed in Canada by Lectron Radio Sales, Ltd.; 211 Hunter Street West; Peterborough, Ontario.

There Is a Difference In Quartz Crystals

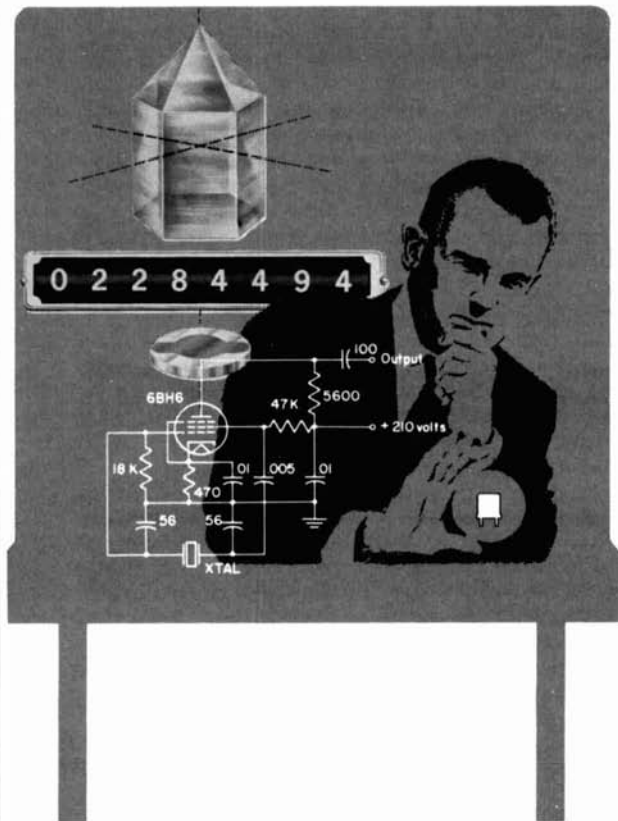

Space age communication equipment demands a crystal that meets all standards of technical advancement. Crystals that were acceptable some years ago do not meet present day specifications. As a general rule, your crystal must be selected from the best quartz . . . (no throw off cuts). Tight tolerances demand selected angles of cut. The x-ray is important in making this selection. The crystal should be preaged with stress cycling. It should be checked for frequency change vs temperature change. It must be checked for optimum spurious response. It should be calibrated to frequency with the correct oscillator. International Crystals are manufactured to meet today's high accuracy requirements. That's why **we guarantee all** International crystals against defective materials and workmanship for an unlimited time when used in equipment for which they were specifically made.

WRITE FOR CATALOG



CRYSTAL MFG. CO., INC.
10 NORTH LEE
OKLAHOMA CITY, OKLA. 73102

2 METER FM

NEW! Hours Location at ERICKSON . . .

SRC-146A SPECIAL WITH

- Charger
 - "Stubby" antenna
 - Leather case
 - Ni-Cads
 - 94/94, 34/94 and one channel of your choice
- \$369 List
—50 Package Discount
\$319 Prepaid — Cashier's Check or M.O.



SYNTHESIZED!


Inoue's
New



IC-230

- 162+ channels, simplex or offset (600 kHz) for repeaters
- All modular construction
- Super hot MOSFET/helical coil .4μV receiver
- AVAILABLE NOW! . . . only \$489.00

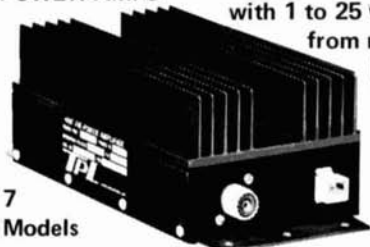TEMPO **TALK POWER!**
POWER AMPS up to 135 W OUT with 1 to 25 w drive from mobile, base or HT . . .



7 Models

MODEL	POWER (in/out)	PRICE
1202	10W/120-W	\$228.00
1202B	1W/120-W	\$239.00
802	10W/85-W	\$190.00
802B	1W/85-W	\$198.00
502	10W/50W	\$110.00
502B	1W/50W	\$130.00
302	1W/30W	\$ 93.00
152	1W/15W	\$ 59.00

Solid State Micro-Strip Circuit
Ready-to-go, Cables supplied
All U. S. made

In stock. Shipped same day UPS ppd. for Cashier's Check or M.O.

ERICKSON COMMUNICATIONS

4135 Main Street (New Location)
Skokie, IL 60076 (312) 677-2161
Hours: 9-4:30 M-S; 6:30-9 M, Th, F

LOW PRICES ON POPULAR COMPONENTS

IF FILTERS

- Monolithic crystal filters at 10.7 and 16.9 MHz
- Ceramic filters at 455 kHz

SEMICONDUCTORS

- VHF power transistors by CTC-Varian
- J and MOS FETS
- Linear ICs — AM/FM IF, Audio PA
- Bipolar — RF and AF power transistors

INDUCTORS

- Molded chokes
- Coil forms — with adjustable cores

CAPACITORS

- Popular variable types

QUALITY COMPONENTS

- No seconds or surplus
- Name brands — fully guaranteed
- Spec sheets on request

GREAT PRICES

- Price breaks at low quantities
- Prices below large mail-order houses

WRITE FOR CATALOG 173

AMTECH, INC.

P. O. BOX 624, MARION, IOWA 52302
(319) 377-7927 or (319) 377-2638

YOU ASKED FOR IT!

ECM-5B FM Modulation Meter
Only \$99.95 less batteries and crystals

- 0-7.5 kHz deviation peak reading
- Meets commercial requirements
- Operates 30-500 MHz
- Crystal controlled for easy operation
- Telescopic antenna

- NEW OPTIONS
- NICAD power pak \$20.46
 - Charger \$28.95
 - Audio/scope output with earphone \$12.95



Write or call for complete info

Send check or money order for \$99.95 plus \$1.50 for shipping. Indiana residents add 4% sales tax. Crystals for 146.94 MHz \$3.95. All other freq. \$7.10.

ECM

ECM Corporation
412 North Weinbach Ave.
Evansville, Indiana 47711
812-476-2121

VHF/UHF

CONVERTERS PREAMPS

Ten meters through 432 MHz. A post card will bring our full 1974 Catalog.



JANEL laboratories

BOX 112, SUCCASUNNA, NJ 07876

Telephone: 201 584 6521

ALL-BAND ANTENNA CONNECTOR



HYE-QUE 1 molded connector has eyelets for securing antenna elements, heavy copper leads, coax PL-250 connector for feedline, and tie-point for antenna support. Drip-cap protects connector. Reinforced. At your dealer's, or \$3.95 postpd. Companion insulators, 2 for 99¢ ppd. Instructions included.

BUDWIG MFG. CO., P. O. Box 97H, Ramona, Calif. 92065

APOLLO PRODUCTS by "Village Twig"



"L"


package enclosure "Shadow Box" machined with: 2-SO239, 1-Pilot Light, 3-Rocker Switches, and 2-Knobs pkg. \$33.00



700X-4 KW Wattmeter

Dummy Load Wattmeter for 52 Ohm Input. Measures RF in 4 ranges to 1000 watts. Front panel frequency counter jack-attenuated per range for frequency counter take-off. Portable

\$139.95

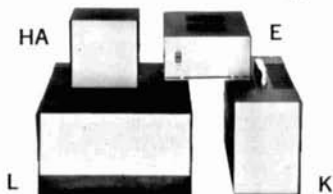

2500X-2 Trans-Antenna Systems Matcher

KW plus 52 ohm and random wire.
\$149.50

MODEL	WIDTH-HEIGHT-DEPTH	RESALE NET
A	5-3/8 x 2-1/2 x 3	4.25
AA*	4 x 3-7/16 x 3-1/8	5.50
B	5-11/16 x 3-3/8 x 3-3/4	5.55
BB*	9 x 2-1/2 x 3-1/8	5.90
C	7-1/4 x 3-3/8 x 5	7.80
D	8 x 2-1/2 x 8**	9.85
E	6-1/2 x 3-15/32 x 7-1/16	9.25
F	7-1/2 x 4-1/2 x 10	11.15
G	10-1/16 x 3-5/16 x 9	11.15
HA	5-1/8 x 5-1/2 x 4	7.85
D1	Mtg. bracket set for D	.40
J	5 x 3-1/2 x 5-3/4	8.35
K	4-3/4 x 7-3/8 x 11	15.00
L	11-1/8 x 6-1/8 x 12-3/4	22.95
M	11-1/8 x 6-1/8 x 16-3/4	24.40
NA	12-1/8 x 5-7/8 x 12-1/16	23.80

*.050 aluminum cover & chassis w/grained panel
**Mobil mounting available.



2100X-2
SWR
Bridge
Large
Meter

Sloping Panel Cabinet - Rubber Feet - Keep in Antenna Line up to 1 Kilowatt

\$33.95



900X-2
Wattmeter
Measures RF in 2 ranges 25 and 500 watts. 52 Ohm input.

\$33.95

2200X-2

SWR Bridge and Antenna Tuner

Both mounted in slope front cabinet

\$62.50

2300X-2

SWR Bridge with 900X Wattmeter

Handles 500 watts, mounted in slope front cabinet

\$66.95

APOLLO "SHADOW BOX ENCLOSURES"

are fabricated of heavy, cold rolled steel. The front panels are of 20-gauge brushed chrome steel; some models are line screened and have a red Rocker DPDT switch installed with gold plated contacts and terminals. Covers are baked on Wrinkle enamel.

All cabinets are completely assembled and supplied with four rubber feet riveted in. Individually packed in a heavy-duty, corrugated mailer carton.

Chassis C thru M are CRS, nickel-plated over copper for excellent RF conductivity.

PRODUCTION CABINETS TO YOUR SPECIFICATIONS ON SPECIAL QUOTATION; 250 PIECE MINIMUM. WRITE FOR QUOTATION.

APOLLO PRODUCTS

BOX 245 · VAUGHNSVILLE, OHIO 45893 · Phone (419) 646-3495 · Evening Phone (419) 646-3495

a NEW antenna principle

PROVEN IN EXACTING TESTS AND MANY YEARS ON THE AIR AT W0MBH — K0AST — K8VRM

THE *Little* GIANT BEAM ANTENNA

only 27 inches high
by 22 inches wide

A COMPLETELY NEW ANTENNA

Here is an ultra compact beam antenna which can be tuned to any frequency between 7.0 and 14.5 MHz. Weighing only 18 lbs. this antenna may not outperform a full sized beam but it sure will give you your share of DX and state-side contacts. Will handle 1 KW over a 100 kHz bandwidth.

- Fully weather proof
- Hi-Q, attenuates harmonics
- Mounts easily on TV masting
- Comes assembled & tested
- Figure 8 pattern

KITS 10-40 \$74.50

LITTLE GIANT MODEL 100X1000-40

\$149.50

Other models available for 10, 15 & 20 meters

Add \$3 trans.

Little Giant Antenna Labs, Box 245, Vaughnsville, Ohio 45893

Subsidiary "Apollo Products" Village-Twig Co.


419-646-3495





-TXX-

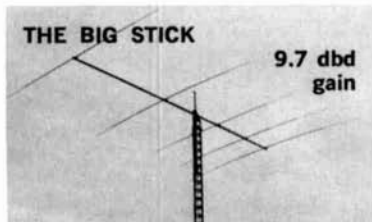
**THE SMART HAMS
ARE CATCHING ON
KLM PRODUCTS DO
GIVE YOU THE EDGE**



THE BIG STICK

9.7 dbd
gain


5EL 20 mtr. mono bander
KLM 13.9-14.4-5

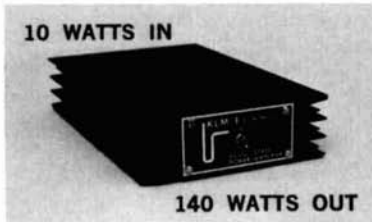

10 WATTS IN


140 WATTS OUT

2 mtr Amplifier
PA 10-140B

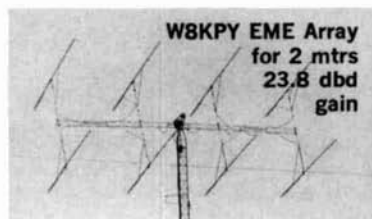

**W8KPY EME Array
for 2 mtrs
23.8 dbd
gain**

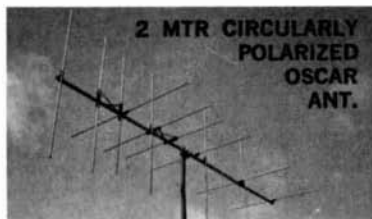8 KLM 16EL 2 MTR
ANTENNAS (KLM144-148-16)



**2 MTR CIRCULARLY
POLARIZED
OSCAR
ANT.**

KLM 140-150-12C

**WRITE FOR COMPLETE CATALOG
OR
CHECK WITH KLM's GROWING LIST OF
DISTINGUISHED DEALERS**

GEORGIA

STEREO CITY INC.
Augusta, GA 30904

LOUISIANA

PRESTON ELECTRONICS
Houma, LA 70360

MICHIGAN

RAY LIBY
Kalamazoo, MI 49001

NEW JERSEY

MULTITONE ELECTRONICS INC.
Springfield, NJ 07081

NEW YORK

BRATTY COMMUNICATIONS
Tonawanda, NY 14150

INDENTICORPORATION
New York City, NY 10022

J. H. ELECTRONICS
Babylon, NY 11704

D. B. GRIFFIN and ASSOC. LTD.
Hamburg, NY 14075

PENNSYLVANIA

HAMTRONICS
Trevose, PA 19047

OHIO

COMMUNICATIONS WORLD
Cleveland, OH 44109

CHALLENGER ELECTRONICS
Middletown, OH 45042

QUEEN CITY ELECTRONICS
Cincinnati, OH 45231

KELLY SCHEIMBERG
Dayton, OH 45424

OKLAHOMA

CALS RADIO
Tipton, OK 73570

LARRY M. DILLARD, WB5CWB
Oklahoma City, OK

OREGON

JUNIPER PHOTO ELECTRONICS
Redmond, OR 97756

TEXAS

KENNEDY ASSOCIATES
San Antonio, TX 78222

TRIMBLE ELECTRONICS
Pampa, TX 79065

J. P. ASHCRAFT
Dallas, TX 75206

FOREIGN COUNTRIES

WEST INDIES SALES CO.
San Juan, PR 00907

ELECTRONICA FERNANDEZ
Hato Rey, PR 00918

INQ. HANS SCHULTZ LTDA.
San Jose, Costa Rica


OMNICOM
Switzerland

GEMINI ELECTRONICS LTD.
Auckland, New Zealand

SEE SEPT. 1974, PAGE 106 FOR OTHER KLM DEALERS

KLM ELECTRONICS 408-683-4240
1600 DECKER AVENUE SAN MARTIN, CA 95046

NEW

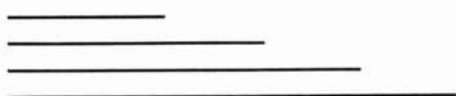

HT-144B

TWO METER FM PORTABLE

- CRYSTAL SOCKETS INCLUDED!
- IMPROVED TRANSMIT AUDIO!
- UP TO 6 KC DEVIATION!
- .35 μ V SENSITIVITY OR BETTER!
- .25 SQUELCH SENSITIVITY!
- IMPROVED INSTRUCTION MANUAL!
- F.C.C. TYPE APPROVAL PENDING!

KIT ONLY \$129.95 COMPLETE less batteries

AND for a limited time only we will furnish

ONE SET OF CRYSTALS FREE!

Your choice of 94-94; 52-52; or 34-94.

IT'S AN EVEN BETTER BUY NOW!!!!!!!

ACCESSORIES: "Rubber Duckie" Antenna (BNC Connectors)	\$12.95
Nicad Battery Charger	\$ 4.95
Sealed 12v Nicad Battery Pack	\$29.95

Please include \$1.00 for Shipping and Handling - N.Y.S. residents add sales tax



VHF ENGINEERING

— DIV. OF BROWNIAN ELECT. CORP. —

320 WATER ST. POB 1921 BINGHAMTON, N.Y. 13902 607-723-9574

Now select from the SGC Avenger One, The SG 711, or the brand new globe-spanning SGC InterContinental One.

Whether you are piloting a tanker, cruising to Tahiti, bringing back a load of fish, or towing a barge to Alaska, one of these reliable Pierre Goral-Don Stoner designed single sideband radio telephones will meet your communications needs.

Top: The Avenger One. Designed for foreign markets, the Avenger One can be installed and channelized by the purchaser. Specifications: all solid state, 12 channels between 2 and 9 MHz, 30 watts PEP, range about 600 miles.

Middle: The SG 711. The work horse and leader in the SSB communications field, the SG 711 is

designed for the middle range market. Specifications: all solid state, 11 channels between 1.6 and 9.0 MHz, 100 watts PEP, range about 1000 miles.

Bottom: The InterContinental One sets new standards for clarity of transmission and reception. A digital readout is an exclusive option. The InterContinental One is backed by a 5 year warranty. Specifications: all solid state, 36 channels between 1.6 and 18 MHz, 150 watts PEP, world-spanning range when atmospheric circuits are open.

The SGC SSB family is backed by authorized SGC Service Centers throughout the world. Even if you are on your way to Sydney, we've been there ahead of you. Authorized Service Centers in Honolulu, Papeete, Suva and Noumea, to name a few, are waiting to serve you.

Pierre Goral and Don Stoner have over 25 years combined experience in supplying communications requirements throughout the world. They and their factory representatives travel extensively, exploring new markets and meeting the present needs in existing markets.

Find out why SGC is the leading supplier of single sideband equipment. Ask for a demonstration today. Join the growing family of satisfied SGC customers.

SGC

Inc.

13737 S.E. 26th Street
Bellevue, Wash. 98005, U.S.A.
(206) 746-6310/CABLE: SGCINC


World's finest SSB family.



hy-gain TH3Mk 3

10-15-20 Meter Tri-Band Antenna

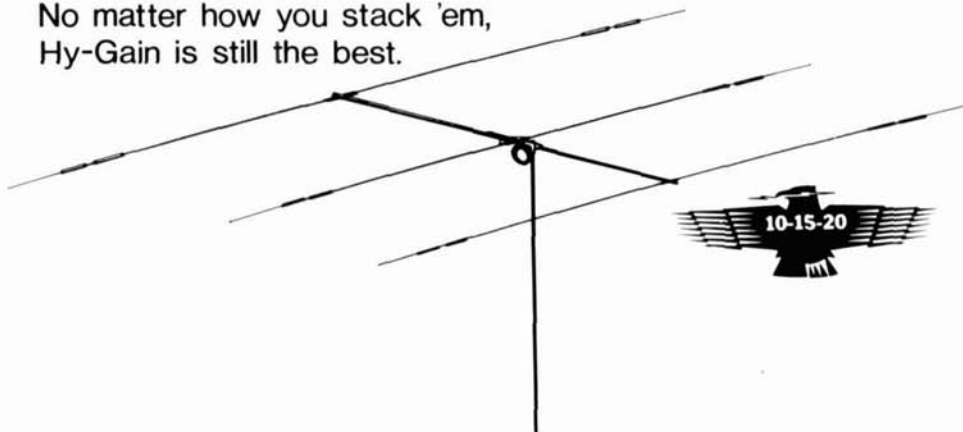No matter how you stack 'em,
Hy-Gain is still the best.



Outstanding performance makes the difference in Hy-Gain's popular 3 element TH3Mk3 tri-band beam. Superior construction makes it the best. The Hy-Gain TH3Mk3 superior construction includes a cast aluminum, tilt head, universal boom-to-mast bracket that accommodates masts from 1 1/4" to 2 1/2". Allows easy tilting for installation, maintenance and tuning, and provides mast feedthru for beam stacking.

Taper swaged slotted tubing on all elements. Taper swaged for larger diameter tubing at the element root where it counts, and less wind loading at the element tip. Slotted for easy adjustment and readjustment.

Full circumference compression clamps at all joints are mechanically and electrically superior to self-tapping metal screws.

Extra heavy gauge machine-formed, element-to-boom brackets with plastic sleeves used only for insulation. Bracket design allows full support.

"Hy-Q" traps for each band are tuned at the factory. You can tune the antenna, using charts supplied in the manual, for optimum performance on your preferred mode, phone or CW.

Hy-Gain's exclusive Beta Match for optimum matching, balanced input on all 3 bands and DC ground to eliminate precipitation static.

For best results, use with Hy-Gain BN-86 balun is recommended.

- Up to 8 db gain.
- 20-25 db front-to-back.
- VSWR less than 1.5:1 at resonance.
- 1 KW AM, 2 KW PEP power capability.
- Turning radius...15.7'.
- Net weight...36 lbs.
- Boom length...14'.
- Longest element...27'.
- Surface area...5.1 sq. ft.
- Nominal 50 ohm input.

Other great Hy-Gain Tri-Band beams...

TH6DXX	6-element Super Thunderbird	Order No. 389
TH3JR	3-element Thunderbird Jr.	Order No. 221
TH2Mk3	Inexpensive 2-element	Order No. 390

For prices and information, contact your local
Hy-Gain distributor or write Hy-Gain.

Hy-Gain Electronics Corporation, 8601 Northeast Highway Six, Lincoln, NE 68507; 402/464-9151; Telex 48-6424.
Branch Office and Warehouse, 6100 Sepulveda Blvd., #322, Van Nuys, CA 91401; 213/785-4532; Telex 65-1359.
Distributed in Canada by Lectron Radio Sales, Ltd.; 211 Hunter Street West; Peterborough, Ontario.



hy-gain

THREE QUARTER INCH DIGITS BY OPCOA

3 for \$13.

- 0.7 character
- 0 to 9

Any color \$4.95

RED — GREEN — YELLOW

Type
SLA-3H
SLA-4H*
SLA-13
SLA-14*
SLA-23
SLA-24

Color
RED
RED
GREEN
GREEN
YELLOW
YELLOW

*Plus or Minus one

Order by type number

OPCOA SLA-1 REFLECTIVE LED READOUT

"Red" \$1.95

3 for \$5

7-segment. Character 0.33"

Calculator Basics

Year Choice \$16.95

BASIC KIT #1 — includes case, all-function Flex Key keyboard, Cal Tech CT5002 calculator chip, 9-digit Antex LED display with built-in individual magnifiers, plus sheets.

BASIC KIT #2 — same as Basic #1 except calculator chip is National 8-digit MM5725.

BASIC KIT #3 — same as Basic #1 except calculator chip is National 6-digit MM5736 and 75492.

"ULTRA BRITE" XCI TRON LEDS

\$2.50 9-pc. kit

One of Poly Paks exclusive ultra-brite offers at "dirt" prices. Kit includes: 3 REDS, 3 GREENS, 3 YELLOWS, each including JUMBO, MEDIUM and MICROS.

8 WATT STEREO AUDIO AMP

The factory "snipped" most of the cables to this compact 8 watt stereo unit with aluminum escutcheon plate. It's easy to use because we have all the cables marked ready to use. With power supply, 115vac, 3 controls, LEFT and RIGHT VOLUME controls for two speakers for balancing and center TONE control. With knobs. 7 x 3 1/2 x 3 1/2. Hookup spec sheets.

5.95

12 DIGIT BASIC #4

Key parts include: CT6001 chip, 4-3 digit readouts, factory etched PC board, case, carrying case, 2-resistor networks, decimal switch, Wild Rover Keyboard with ON-OFF switch diagrams. Sale \$24.95

12* DIGIT BASIC "MEMORY" KIT #5 — Key parts for 4-memory calculator. Case with "slight touch keyboard", CT5005 memory chip, 6 MAN 3's, ON-OFF switch, book. (*extend key allows 12 digits, pc boards). \$19.95

EPOXY FULL WAVE SILICON BRIDGE RECTIFIERS

PIV 100	2 Amp	6 Amp
50	\$ 5.88	\$ 9.99
100	7.99	11.99
200	9.95	14.25
400	11.99	15.50
600	13.99	17.25
800	15.95	19.95
1000	17.99	22.25

Code: 2 amp 1000 1.79 2.25
10-6 case 6 Amp 1 2 x 1 2 x 4/16 80

PROFESSIONAL 8-TRACK TAPE TRANSPORT

Same type unit found in the most expensive home tape players. It's a complete 8-track player system with BUILT-IN PREAMP — just plug into any stereo amplifier (see some of our low-priced units). Excellent replacement unit, or you can design your own high-quality stereo tape system. It's the type you use as a cartridge to turn-on, deck, then enjoy up to 80 minutes of non-stop, non-repeat stereo. Remove cartridge and player "shuts off" automatically. Built-in output controls in preamp. Features: 4 PROGRAM INDICATOR LIGHTS, automatic or manual program change, plays your car tapes at home. WOW-FREE precision fan-cooled motor, which operates off 115Vac. Requires external 12Vdc supply, for the electronics. With diagrams.

15.95

CLOCK CHIPS ON A "DIP"

as Low as \$4.95

MM5311 6-digit 28-Pin	\$7.77
MM5312 4-digit 28-Pin	7.77
MM5313 6-digit 28-Pin	7.77
MM5314 6-digit 24-Pin	7.77
MM5316 4-digit 40-Pin Alarm	9.95
MM5316 4-digit Alarm	9.95

Buy Any 3 TO-5, 8 or 10-Pins 1.00
8-Pins (Mini DIP) .69
14-Pin, Wire Wrap .69
16-Pin, Wire Wrap .89c

WITH DATA SHEETS

8-Watt Stereo Amplifier. Only 8-Track Tape Transport and hook-ups both. \$19.95

INTEGRATED CIRCUIT SOCKETS

Mfr's Type Watts Sale

SI-1010Y	10	\$ 8.88
SI-1025E	25	18.88
SI-1050E	50	28.95

Used extensively in hi-fi systems, tape decks, FM tuners, record players, stereo components, musical instruments, P.A., etc. All amplifiers, flat within 1/2 db from hz to 100,000. Each unit properly heat-sinked, with heavy-duty connecting tie-clip connections. Single-ended push-out output. Power supply required 2VDC. Output to 8 ohms. Order by Stock No.

6 DIGIT KRONOS CLOCK

Using MAN-3'S Complete \$29.95

Money-Back GUARANTEE on all items

PRECISION CRYSTAL Only \$1.95

Excellent time base and other uses. 5,000 MHz. Type H6U case.

SANKEN HYBRID AUDIO POWER AMPS

3 for \$3 \$1.49

Removed from new equipment! Includes popular 2N174 doorknob transistor TO-18, germanium.

Mfr's Type Watts Sale

SI-1010Y	10	\$ 8.88
SI-1025E	25	18.88
SI-1050E	50	28.95

Used extensively in hi-fi systems, tape decks, FM tuners, record players, stereo components, musical instruments, P.A., etc. All amplifiers, flat within 1/2 db from hz to 100,000. Each unit properly heat-sinked, with heavy-duty connecting tie-clip connections. Single-ended push-out output. Power supply required 2VDC. Output to 8 ohms. Order by Stock No.

PRECISION CRYSTAL

Excellent time base and other uses. 5,000 MHz. Type H6U case.

Money-Back GUARANTEE on all items

Inflation-Fighting ECONOMY IC PRICES

Buy 100 — Take 25%
Buy 1000 — Take 25%

Type	Sale	Type	Sale	Type	Sale	Type	Sale
SN7400	.19	SN7430	.24	SN7472	.42	SN74107	.49
SN7401	.22	SN7432	.28	SN7473	.39	SN74108	.95
SN7402	.24	SN7437	.45	SN7474	.39	SN74112	.95
SN7403	.27	SN7438	.49	SN7475	.91	SN74113	.95
SN7405	.28	SN7440	.22	SN7476	.52	SN74114	.95
SN7407	.79	SN7441	1.19	SN7477	7.79	SN74121	.49
SN7407	.79	SN7442	1.02	SN7478	.52	SN74122	.55
SN7408	.27	SN7443	1.02	SN7479	7.79	SN74123	1.09
SN7409	.27	SN7444	1.02	SN7482	.99	SN74125	.65
SN7410	.22	SN7445	1.09	SN7483	1.19	SN74126	.89
SN7411	.31	SN7446	1.19	SN7485	2.50	SN74139	1.25
SN7412	.85	SN7447	1.19	SN7486	4.49	SN74140	2.50
SN7413	.89	SN7448	1.19	SN7489	3.19	SN74141	1.19
SN7414	2.25	SN7450	.26	SN7490	1.19	SN74145	1.19
SN7415	.45	SN7451	.26	SN7491	1.35	SN74148	2.95
SN7416	.45	SN7453	.28	SN7492	.99	SN74150	1.19
SN7417	.50	SN7454	.39	SN7493	.99	SN74151	.99
SN7420	.22	SN7455	.28	SN7494	1.05	SN74153	1.39
SN7421	.50	SN7456	.28	SN7495	1.05	SN74154	1.69
SN7422	.32	SN7457	.26	SN7496	1.59	SN74155	1.29
SN7423	.39	SN7458	.39	SN74100	1.25	SN74156	1.45
SN7425	.35	SN7459	.48	SN74105	.95	SN74157	1.45
SN7426	.31	SN7470	.49	SN74106	.95	SN74158	1.45
SN7427	.35	SN7471	.55			SN74160	1.85

Order by type number! Spec sheets on request ONLY! * Factory Marked

JUMBO 0.6" MITY DIGIT DCM

NEVER BEFORE OFFERED! Digital counting module kit using the big "M" Monsanto MAN-6 "ALL LED" readout. Same electrical specs as the MAN-1. Measures 1 x 7/8 x 1/8" encapsulated in red epoxy lens. Outperforms all reflective bar types. MFR BRILLIANT! Made for distance and wide-angle viewing. Fits into standard 14 pin DIP socket. Kit includes MAN-6, right angle IC socket, edge connector, pc board, assorted resistors and capacitors, SN7475, SN7447, SN7490, Molex sockets and booklet.

Same as above except uses MAN-64, 0.4 ALL LED readout. MAN-1 characteristics Only \$8.88

"C" THRU S METER \$2.50

Indicates: 0 to 1.5 Plastic case. 1 1/2 x 1 1/2 x 1 1/2.

SCR'S! TRIACS! QUADRACS! SAME PRICE SALE!

10-Amp Power Tab Plastic Units

PRV	Sale
50	\$.75
100	.95
200	1.25
300	1.50
400	1.90
600	2.25
800	2.50

Rare buy of these popular precision modules that are used by ham radio enthusiasts, hobbyists. By Monitor. Type 850. Freq: 4,000 MHz. Accuracy: ±.01. Requires 5VDC. Generates a square wave on output. Size: 1 1/4 x 1 x 1/2.

Terms: add postage. Rated: net 30

Phone Orders: Wakefield, Mass. (617) 245-3829
Retail: 16-18 Del Carmine St., Wakefield, Mass. (off Water Street). C.O.D.'S MAY BE PHONED

20c CATALOG Fiber Optics, IC's, Semi's, Parts MINIMUM ORDER — \$4.00

POLY PAKS

P.O. BOX 642H LYNNFIELD, MASS. 01940

flea market



EQUIPMENT FOR SALE: DX-60 with HG-10 VFO, \$50; HX-20 with AC-supply, \$50; SX-111, \$50; ARC-5 rcvr, 80M, with AC-supply, \$15; ARC-5 xmtr, 40M, \$10; Redline keyer, similar to TO-5, \$20; SR-160 with AC & mobile supplies, \$150. Larry Osolkowski, 87 Park Ave., Hamburg, N. Y. 14075.

PC's, Send large S.A.S.E. for list. Semtronics, Rt. #3, Box 1, Bellaire, Ohio 43006.

HALLICRAFTERS HT-46 SSB/CW xmtr, \$149. Radiophone mod. 44 band scanner (CRT also mod. mon.) \$50. All good condx — orig. owner. FOB K4MI, 2401 E. 4th St., Greenville, N. C. 27834.

LEARN DESIGN TECHNIQUES. Electronics Monthly Newsletter. Digital, linear construction projects, design theory and procedures. Sample copy \$1.00. Valley West, Box 2119-C, Sunnyvale, Calif. 94087.

NEW PARTS BARGAINS: Calrad KW SWR-relative power dualmeter bridge 24.95; HyGain TH6DXX — see this months ad; CDE Ham-2 109.00; CD44 79.95; Belden 8-wire rotor cable #8448 12¢/ft; many new Sprague capacitors, write needs; door-knobs: Sprague 500PF/20KV 1.95; CDE .001/10KV 1.95; Erie padder caps 3-12PF & 8-50PF, 49¢ both; coax: RG62B/U 8¢/ft; RG71/U 8¢/ft; RG13B/U 15¢/ft; Belden, Consolidated RGH foam 8214 18¢/ft; Amphenol PL259 59¢; Motorola semiconductor data series books 7.50; Rider, Tab, Radio Publications, ARRL AMECO, Callbooks; many old tubes — write needs; New panel meters — write; H-P series 5082 LED's 99¢; new Raytheon, GE 811A 7.95; 15.00/pr; Sorensen ACR2000VA AC regulator 150.00; GE covering tubes 50% off list; KY65 code keyer 5.95; free flyers. All items new, guaranteed, prices FOB Houston. Madison Electronics, 1508 McKinney, Houston, Texas 77002. 713/244-2668. Nite: 713/497-5683.

NEED PARTS? We carry parts for R-388-390-390A-391-392-1051-51S1 - Nems Clark-Racal-Pack sets - PRC-25-41-47-62-70-71-73-74-77. If you need a part no matter what you have. If its U.S. government we have it or can get it. Also we want to buy or trade all aircraft communications. All ground radio communications. All plug-in modules control heads. No matter what cond. they are in - bent or busted ok. We will buy or trade. We have R-390-388-390A-392-1051-51S1 Nems Clark - Racal - and new ham gear for trade. D & R Electronics, R. D. #1, Box 56, Milton, Pa. 17847. Phone 1-717-742-4604 after 6:00 P.M.

DRAKE TR-6, the Cadillac of 6 meters, with NB, AM filter, AC4, MS4, mint, \$615. Russell, 19680 Mountville Dr., Maple Heights, Ohio 44137.

SIGNAL ONE OWNERS, expert and prompt service by ex-Signal/One engineer. Also will purchase your functioning or not functioning unit or spare parts. Write or call for details. Larry Pace, K2IXP/7, 5717 Genematas, Tucson, AZ. 85704 (602-888-5234).

FOR SALE; Yaesu FLDX 400 tran., 6 months old. Going transceiver. \$200.00, you ship. James Stafford, 2125 Chandler Ave., Fort Myers, Fla. 33901.

WANTED - USED FM 2-way radio communications equipment and test equipment. Mot., GE and RCA etc. No doggies please. CAL-COM Systems, Inc., 701-51A Kings Row, San Jose, Calif. 95112, Tel. 408/998-4444.

RADIO LICENSE — Exact reproduction, including signature. Engraved in solid brass. Send GOOD Xerox copy with \$5.00 to Metal Art Graphics, 1136 Potomac Ave., Hagerstown, Md. 21740. Md. residents please include state sales tax.

YAESU TRANSCEIVER OWNERS — Present and Prospective. Join the International Fox-Tango Club. Send business-size SASE or two IRCs for complete information and sample of monthly FT newsletter. Milton Lowens WA2AOQ, 3977-F Sedgwick Ave., Bronx, N. Y. 10463.

SWAP-N-SELL ADS FREE in TRADIO. Box 4391, Wichita Falls, Texas 76308.

MASSILLON ARC Annual Flea Market and Auction. November 22, 1974. Send card for map and details. MARC, Box 8711, Canton, OH 44711.

TELL YOUR FRIENDS about Ham Radio Magazine.

■ **RATES** Commercial Ads 35¢ per word; non-commercial ads 10¢ per word payable in advance. No cash discounts or agency commissions allowed.

■ **COPY** No special layout or arrangements available. Material should be typewritten or clearly printed and must include full name and address. We reserve the right to reject unsuitable copy. **Ham Radio** can not check out each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue. Deadline is 15th of second preceding month.

■ **SEND MATERIAL TO:** Flea Market, Ham Radio, Greenville, N. H. 03048.

SURPLUS TEST EQUIPMENT, VHF and microwave gear; write for bulletins. David Edsall, 2843 St. Paul, Baltimore, Md. 21218.

TELETYPEWRITER PARTS, gears, manuals, supplies, tape, toroids. SASE list. Typetronics, Box 8873, Ft. Lauderdale, Fl. 33310. Buy parts, late machines.

QSL's, Sample catalog 20¢. N & S Print, P. O. Box 11184, Phoenix, Ariz. 85061.

STOLEN Motorola Motran VHF Transceiver, Model #U43MSN-1100A, 12 volt. Serial #DG153W, Frisco ID #H-616, Frequency 161.130. Contact H. E. Johnson, 7059 Marquette Avenue, St. Louis, Mo. 63139.

MANUALS for most ham gear made 1940/65, some earlier. Send SASE for specific quote. Hobby Industry, WØJJK, Box H-864, Council Bluffs, Iowa 51501.

FOR SALE: KWM-2 Plus; NCL2000; Model 19; BGP Converter; Johnson KW matchbox with SWR; R388; magazines, etc. S.A.S.E. Glenn Milner, W5DLO, 911 Enfield, Bryan, Texas 77801.

WANTED: GENERAL CLASS (or higher) hams to join 4,500 member Morse Telegraph Club. Hundreds of hams already belong. Send modest \$3 annual dues (includes subscription to great slick paper newspaper "Dots and Dashes") to GST A. J. Long, 520 West Schwartz Street, Salem, Ill. 62881 for membership card and assignment to nearest chapter.

DRAKE 2-B RECEIVER with matching Q multiplier. Excel. condx. \$155.00. WA2SJV/7, 650 N.W. Overlook, Gresham, Ore. 97030, (503) 666-1056.

EXCLUSIVELY HAM TELETYPE 21st year, RTTY Journal, articles, news, DX, VHF, classified ads. Sample 30¢. \$3.00 per year. Box 837, Royal Oak, Michigan 48068.

FREE IC

With Every \$10 Order*

- REDUCE YOUR PROJECT COSTS
- MONEY-BACK GUARANTEE
- 24-HOUR SHIPMENT
- ALL TESTED AND GUARANTEED

• TRANSISTORS:

NPN:		
2N3563 TYPE RF Amp & OSC to 1GHz (pl. 2N918)	6/\$1.00	
2N3565 TYPE Gen. Purpose High Gain (TO-106)	6/\$1.00	
2N3691 TYPE GP Amp to 25 mA and 50 MHz	6/\$1.00	
2N3866 TYPE RF Pwr Amp 1-2 W @ 100-600 MHz	\$1.50	
2N3903 TYPE GP Amp & Sw to 100 mA and 30 MHz	6/\$1.00	
2N3904 TYPE GP Amp & Sw to 100mA (TO-92)	5/\$1.00	
2N3919 TYPE RF Pwr Amp 3-5 W @ 3-30 MHz	\$3.00	
Assort. NPN GP TYPES, 2N3565, 2N3641, etc. (15)	\$2.00	

PNP:

2N3638 TYPE Gen. Purpose Amp & Sw	4/\$1.00
2N4249 TYPE Low-Noise Audio Amp 1 μ A to 50mA	4/\$1.00

• FET's:

N CHANNEL (LOW NOISE):

2N4416 TYPE RF Amplifier to 450 MHz (TO-72)	2/\$1.00
2N5486 TYPE RF Amp to 450 MHz (plastic 2N4416)	3/\$1.00
2N5163 TYPE Gen. Purpose Amp & Sw (TO-106)	3/\$1.00
2N4091 TYPE RF Amp & Switch (TO-106)	3/\$1.00
ITE4868 TYPE Ultra-Low Noise Audio Amp.	2/\$1.00
Assort. RF & GP FET's, 2N5163, 2N5486, etc. (8)	\$2.00

P CHANNEL

2N4360 TYPE Gen. Purpose Amp & Sw (TO-106)	3/\$1.00
M104 TYPE MOS FET (Diode protected) 0.3 pF	\$3.00

• LINEAR IC's:

555X Timer 1 μ s-1 hr, Dif. pinout from 555 (DIP)	\$.90
709 Popular OP AMP (DIP/TO-5)	\$.39
723 Voltage Regulator 3.30 V @ 1.250mA (DIP/TO-5)	\$.75
739 Dual Low-Noise Audio Preamp/OP AMP (DIP)	\$1.00
741 Freq. Compensated OP AMP (DIP/TO-5/MINIDIP)	\$.45
2556 Dual 555 Timer 1 μ sec to 1 hour (DIP)	\$1.55
LM305 Positive Voltage Regulator (TO-5)	\$1.25
MC1458 Dual 741 OP AMP (MINI-DIP)	\$.95
Assorted Linears-741/709/723, etc. (4)	\$2.00

• DIODES:

1N914 TYPE Gen. Purpose 100V/10mA	10/\$1.00
1N3600 TYPE Hi Speed SW 75V/200mA	6/\$1.00
1N4608 TYPE GP & SW 80V/400mA	6/\$1.00
1N3893 TYPE RECTIFIER Stud Mount 400 V/12 A	2/\$1.00
1N749 ZENER 4.3 Volt 400mW	3/\$1.00
1N753 ZENER 6.2 Volt 400mW	4/\$1.00
1N755 ZENER 7.5 Volt 400mW	4/\$1.00
1N757 ZENER 9.1 Volt 400mW	4/\$1.00
1N758 ZENER 10 Volt 400mW	4/\$1.00
1N965 ZENER 15 Volt 400mW	4/\$1.00
1N968 ZENER 20 Volt 400mW	4/\$1.00
D5 VARACTOR 5-50 W Output @ 30-250 MHz, 7.70 pF	\$5.00
F7 VARACTOR 1-3 W Output @ 100-500 MHz, 5.30 pF	\$1.00

*MAIL NOW! With every order of \$10 or more, postmarked prior to 12/31/74, FREE 739 or 749 Low-Noise Dual OP AMP included—\$1 VALUE.

ORDER TODAY—All items subject to prior sale and prices subject to change without notice. DATA SHEETS included with all items.

WRITE FOR FREE CATALOG offering hundreds of semi-conductors not listed here. Send 10¢ stamp.

TERMS: All orders prepaid. We pay postage. \$1.00 handling charge on orders under \$10. Calif. residents add 6% sales tax.

ADVA

ELECTRONICS

BOX 4181-L, WOODSIDE, CA 94062
Tel. (415) 851-0455

WORLD QSL BUREAU

THE ONLY QSL BUREAU to handle all of your QSLs to anywhere; next door, the next state, the next country, the whole world. Just bundle them up (please arrange alphabetically) and send them to us with payment of 6¢ each.

5200 Panama Ave., Richmond, CA USA 94804

"THE ELECTRONICS STORE"

RMS CORPORATION

675A GREAT ROAD (ROUTE 119)
LITTLETON, MASS. 01460

7400 SERIES I.C.'s MATRIC-KEYERS
HUSTLER ANT. GOTHAM ANTENNAS
VHF ENG. KITS — VHF-HT-144 — VENUS SSTV
LARGE INVENTORY OF COMPONENTS
I-495 to Rte. 119, Groton Exit 19
2 Miles On The Right

COMPLETE ANTENNA SYSTEMS

A complete ready-to-use antenna system designed for your favorite frequency. Includes No. 12 copperweld wire element dipole, 100 ft. of coax with connector, and 100 ft. of 1/4 inch diameter dacron halyard at each end of dipole. No "diddling" or trimming required. You furnish the supports, plug the feedline into your xmttr and start operating. Power rating — 2KW, VSWR 1.5:1 or less.

75/80M Monoband	130 Ft.	\$ 74.75
40M Monoband	65 Ft.	69.75
80/40M Dualband	130 Ft.	99.95
80/40/20M Triband	130 Ft.	133.00

Descriptive literature available. State desired frequency. Postpaid contiguous USA.

HOUSE OF DIPOLES

Box 8484 Orlando, Fla. 32806



Radio Amateurs
Reference Library
of Maps and Atlas

WORLD PREFIX MAP — Full color, 40" x 28", shows prefixes on each country . . . DX zones, time zones, cities, cross referenced tables **\$1.25**

RADIO AMATEURS GREAT CIRCLE CHART OF THE WORLD — from the center of the United States! Full color, 30" x 25", listing Great Circle bearings in degrees for six major U.S. cities; Boston, Washington, D. C., Miami, Seattle, San Francisco & Los Angeles. **\$1.25**

RADIO AMATEURS MAP OF NORTH AMERICA! Full color, 30" x 25" — includes Central America and the Caribbean to the equator, showing call areas, zone boundaries, prefixes and time zones, FCC frequency chart, plus useful information on each of the 50 United States and other Countries **\$1.25**

WORLD ATLAS — Only atlas compiled for radio amateurs. Packed with world-wide information — includes 11 maps, in 4 colors with zone boundaries and country prefixes on each map. Also includes a polar projection map of the world plus a map of the Antarctica — a complete set of maps of the world. 20 pages, size 8 3/4" x 12" **\$2.50**

Complete reference library of maps — set of 4 as listed above **\$3.75**

See your favorite dealer or order direct.

Mail orders please include 50¢ per order for postage and handling.

WRITE FOR
FREE
BROCHURE!

RADIO AMATEUR
callbook INC.



Dept. E 925 Sherwood Drive
Lake Bluff, Ill. 60044

TECH MANUALS for Govt. surplus gear, \$6.50 each: R-220/URR, R-274/FRR, R-390/URR, URM-25D, URM-32, USM-16, TT-63A/FGC, TS-382D/U, BC-779B, TS-497B/URR, LM-21, TS-34A/AP, ALR-5, GRR-5, ARR-7, TS-323/UR, PRC-10. Thousands more available. Send 50¢ (coin) for list. W31HD, 7218 Roanoke Drive, Washington, D. C. 20021.

WANTED: tubes, transistors, equipment, what have you? Bernard Goldstein, W2MNP, Box 257, Canal Station, New York, N. Y. 10013.

FREE: 12 Extra crystals of your choice with the purchase of a new Regency HR-2B at \$229. Send cashier's check or money order for same-day shipment. For equally good deals on Collins, Drake, Atlas, Kenwood, Standard, Clegg, Swan, Icom, Genave, Hallcrafters, Tempo, Ten-Tec, Venus, Hy-Gain, Cushcraft, Mosley, and Hustler, write to Hoosier Electronics, your ham headquarters in the heart of the Midwest. Become one or our many happy and satisfied customers. Write or call today for our low quote and try our individual, personal service. Hoosier Electronics, R.R. 25, Box 403, Terre Haute, Indiana 47802. (812) 894-2397.

CANADIAN JUMBO SURPLUS and Parts Catalogs. Bargains Galore. Send \$1. ETCO-HR, Box 741, Montreal "A" H3C 2V2.

INSTRUCTION MANUALS — Thousands available for test equipment, military electronics. Send \$1.00 (refundable first order) for listing. A service of Tucker Electronics, Box 1050, Garland, Texas 75040.

RECIPROCATING DETECTOR, write Peter Meacham Associates, 19 Loretta Road, Waltham, Mass. 02154.

SELL: ROBOT SSTV Models 80 Camera and 70 Monitor. Original cartons and instruction books. Excellent condition. \$500.00. Gordon Buckner, WØVZK, Box 721, Marshall, Missouri 65340.

TRAVEL-PAK QSL KIT Converts photos, post cards to QSLs! Send call and 25¢ for personal sample. Samco, Box 203H, Wynantskill, N. Y. 12198.

FOR SALE: TR4 - \$375, AC4 - \$75, DC4 - \$100, SB102 - \$350, Linear Systems 400-12 - \$100, HP23 - \$40. Consider station deal. Walt Hagen, WA2ALV, 19 Aviation Road, Glens Falls, New York 12801. Phone: H 518-792-5162, B 518-793-4491 X60.

INDIANA — The Fort Wayne Hamfest is January 19, 1975 at Shiloh Hall (1/2 mile west of Ind. 3 on Carroll Rd.). Flea market, food. Tickets are \$1.50 at the door. XYL's and children under 12 years free. Tables available at \$1.00 for 4 ft. Talk in on 28-88 and 16-76.

ROCHESTER, N. Y. — Hamfest date of 1975 — May 31st. Marriott Inn is new headquarters. Information? Write WNY Hamfest, Box 1388, Rochester, N. Y. 14603.

BEAUTIFUL CLEAN GEAR: Central Electronics 100V HQ 170A. D104 mike & stand, Vibroplex bug, Hallcrafters SR-42 2 meter transceiver. All for \$450.00. Make offer. Joseph Strolin, K1REC, 21 Ellen St., Norwalk, Conn. 06851.

WANTED: ARC-51, 618T-1, ARC-102, FM-633, ARC-131, 807A Wilcox, Transceivers. Pay Cash. Bob Sanett, 616 S. Holmby Ave., Los Angeles, CA. (213) 279-1275.

TELETYPEWRITERS — Kleinschmidt — portable, fixed, sets, punches, parts, reconditioned, reasonable. Mark/Space Systems, 3563 Conquista, Long Beach, Calif. 90808. 213-429-5821.

CANADIANS — We carry a broad line of electronic parts, including most solid-state devices, LED's, ICs. Send for free flyer to: Ken, VE1AOJ, Dartek Electronics, Dept. H, Box 2460, Dartmouth, Nova Scotia B2W 4A5.

FIGHT TVI with the RSO Low Pass Filter. For brochure write: Taylor Communications Manufacturing Company, Box 126, Agincourt, Ontario, Canada. MIS 3B4.

QRP TRANSMATCH for HW7, Ten-Tec and others. Send stamp for details to Peter Meacham Associates, 19 Loretta Road, Waltham, Mass. 02154.

World's Most Advanced STATE-OF-THE-ART TRANSCEIVER



THE TRITON by TEN-TEC

TOTAL SOLID STATE
HF TRANSCEIVER



Available ANYWHERE IN THE WORLD directly from
ELECTRONIC DISTRIBUTORS, INC.
—Communication Specialists for over 35 years—

1960 Peck St., Muskegon, Michigan 49441
Tel. (616) 726-3196 Telex 22-8411

MORSE MUSIC by CURTIS

KB-4200 Morse Keyboard \$499.95
EK-420A CMOS Deluxe Keyer \$139.95
KM-420 CW Message Memory \$299.95

See Oct. '73
QST Review

Write for
brochures.

CURTIS ELECTRO
DEVICES

MASTERCHARGE
TEL: (415) 964-3136
INC., BOX 4090, MOUNTAIN VIEW, CA. 94040

RADIO COMMUNICATION

Many thousands of you have become familiar with the various Radio Society of Great Britain books and handbooks, but very few of you are familiar with their excellent magazine, Radio Communication.

We can now offer this fine magazine to you along with the other advantages of membership in the RSGB (such as use of their outgoing QSL Bureau) for \$12.95 a year.

ham
radio Greenville
NH 03048

MADISON Electronics Supply, Inc.



Hy-Gain TH6DXX

6-Element Super Thunderbird DX
Superior Performance TriBander

Impressive coverage 10-15-20 meters

List \$224.95

CALL OR WRITE FOR QUOTE

Belden Coax, Ham-II, Tri-Ex Tower

FREE FLYER


Madison Electronics Supply, Inc.

1508 MCKINNEY AVENUE
HOUSTON, TX 77002

Phone: 713-224-2668

Nite/Weekend: 713-497-5683

NEW HOT SUGGESTED GIFT ITEM

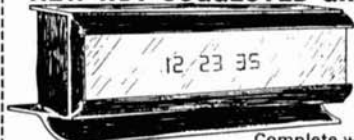

DIGITAL
CLOCK
KIT
\$34.95

Full 6 digit LED display Complete with anodized alum. case. All parts and P.C. board. With complete assembly drawings. Ship wt. 1 1/2 lbs.

SLA-1 7 SEG READOUT\$1.75 EA. 6/\$9.50
12 ASST'D LEDS MOSTLY JUMBO\$2.00
15 1N4007 1000V PIV 1 AMP\$2.00

Orders over \$10.00 ppd. Others add 50¢ handling & mailing.

HAL-TRONIX

P. O. BOX 1101 SOUTHGATE, MICH. 48195
(313) 285-1782

DIGITAL:THEORY,DESIGN,
CONSTRUCTION

LOGIC NEWSLETTER[®]

SAMPLE COPY \$ 1.00
LOGIC NEWSLETTER
POB 252
WALDWICK,N.J. 07463

DYCOMM for RF POWER




ECHO III REPEATER



MODEL 34 WATTMETER



A4950

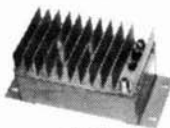

A8949

A COMPLETE LINE OF FM AMPLIFIERS

model — power output — gain — price

6 METER FM

A4950 - 50W - 10db - \$183.
A4960 - 50W - 8db - \$192.
A8949 - 100W - 10db - \$270.
450 - UHF

2 METER FM

MODEL C - 25W - 4db - \$69.
MODEL D - 50W - 7db - \$99.
SUPER D KIT - 80W - 3.5db - \$60
MODEL DS - 80W - 3.5db - \$139
MODEL E - 25W - 10db - \$80.
SUPER E KIT - 40W - 11db - \$60.
MODEL ES - 40W - 11db - \$115.
10-0 - 100W - 7db - \$209.
1-10-0 - 100W - 14db - \$226.
35-0 - 100W - 4db - \$185.

MODEL 25 - 30W - 7db - \$167.
MODEL 30 - 30W - 9db - \$194.
MODEL 70 - 70W - 6db - \$255.

OTHER PRODUCTS

ECHO III FM REPEATER - \$949.
MODEL 34 WATTMETER - \$60.

SUPER CRYSTAL THE NEW DELUXE DIGITAL SYNTHESIZER!! FROM R_P



MFA-22 DUAL VERSION

Also Available MFA-2 SINGLE VERSION

- **Transmit and Receive Operation:** All units have both Simplex and Repeater Modes
- **Accurate Frequency Control:** .0005% accuracy
- **Stable Low Drift Outputs:** 20 Hz per degree C typical
- **Full 2 Meter Band Coverage:** 144.00 to 147.99 MHz. in 10K steps
- **Fast Acting Circuit:** 0.15 second typical settling time
- **Low Impedance (50 ohm) Outputs:** Allow long cable runs for mobiles
- **Low Spurious Output Level:** similar to crystal output

SEND FOR
FREE DETAILS

R_P Electronics

Prices MFA-22 \$325.00 810 DENNISON DR.
MFA-2 \$260.00 BOX 1201H
Shipping \$3.00 extra CHAMPAIGN, IL 61820



DYNAMIC

COMMUNICATIONS

948 AVE. "E" P.O. BOX 10116
RIVIERA BEACH, FLA. 33404
(305) 844-1323



HOMEBREWERS: Stamp brings list of high quality components. CPO Surplus, Box 189, Braintree, Mass. 02184.

HAM-M ROTOR FOR SALE. Complete, used 4 months, \$90. K. Teague, WB5FMJ, Box 65, Alma, AR 72921.

QSL'S — BROWNIE W3CJI — 3035B Lehigh, Allentown, Pa. 18103. Samples with cut catalog 35¢.

FOR SALE: Hallicrafters FPM-300, 1 yr. old, \$300. Kravat, 103C Wellington, West Palm Beach, Fla. 33401. (689-0394).

VERY in-ter-est-ing! Next 5 big issues \$1. "The Ham Trader," Sycamore IL 60178

NOW PAYING \$2000.00 and up for ARC-94/618T ARC-102/618T. \$1200.00 and up for ARC-51BX, \$1500.00 and up for 490T-1 antenna couplers. We also need these control boxes — C-6287/ARC-51BX, C-6476/ARC-51BX, C-714E-2. We also need R-1501 receivers, RT-662/GRC-106 transceivers. We buy all late aircraft and ground radio equipment. Also pack radios. We are buyers not talkers. Bring your equipment in, you are paid on the spot. Ship it in, you are paid within 24 hours. We pay all shipping charges. If you want the best price for your equipment, call us. Call collect if you have, and want to sell or trade. We also sell. What do you need? D & R Electronics, R.D. #1, Box 56, Milton, Pa. 17847. Phone — 717-742-4604 - 9:00 a.m.-9:00 p.m.

USED MYLAR TAPES — 1800 foot. Ten for \$8.50 postpaid. Fremerman, 4041 Central, Kansas City, Mo. 64111.

TELETYPE EQUIPMENT FOR SALE for beginners and experienced operators. RTTY machines, parts, gears. Send us a list of your teletype needs. Atlantic Surplus Sales Co., 1902 Mermaid Ave., Brooklyn, New York 11224. Call us first (212) 266-2629.

PRINTED CIRCUIT TECHNIQUES for the hobbyist. Booklet: \$2.00. H. S. steel and carbide drill bits and PC artwork. Send SASE for flyer. Trumbull, 833 Balra Dr., El Cerrito, Ca. 94530.

7400's 40¢. No minimum order. Fastcode, Box 55, Hernando, MS 38632.

MOBILE IGNITION SHIELDING provides more range with no noise. Available most engines in assembled or kit forms, plus many other suppression accessories. Free literature. Estes Engineering, 543-H West 184th, Gardena, California 90248.

WORLD QSL — See ad on page 84.

BATTERY*CHECK — Mobile Operators — Continuous, precision monitor of battery condition can prevent brown-outs, sulphation, dead batteries. BATTERY*CHECK, Box 122-HR, Natick, Massachusetts 01760.

FOR SALE — Tempo "One" SSB, CW, AM transceiver and AC/One power supply. Mint condition. Original manuals and boxes. Must sell. I ship. \$300 total. Dale Bernelle, 406 Richmond Rd., Monroe, Louisiana 71201.

FOR SALE. LAFAYETTE HA460 six meter transceiver, complete, mint condition. Write W8FQM, 23012 Virginia Ave., North Olmsted, Ohio 44070.

PERSONAL ATTENTION plus the best cash deal anywhere is what you receive at Queen City Electronics in the heart of the midwest. Queen City carries all major brands including Drake, Tempo, Kenwood, Yaesu, Swan, Regency, Clegg, Standard, Icom, Genave . . . Write or phone us for your equipment needs. Queen City Electronics, Inc., 7404 Hamilton Avenue, Cincinnati, Ohio 45231. (513) 931-1577.

BUY — SELL — TRADE. Write for monthly mailer, give name, address, call letters. Complete stock of major brands new and reconditioned equipment. Call us for best deals. We buy Collins, Drake, Swan, etc. SSB & FM. Associated Radio, 8012 Conser, Overland Park, Kansas 66204. 913-381-5901.

YOUR AD belongs here too. Commercial ads 35¢ per word. Non-commercial ads 10¢ per word. Commercial advertisers write for special discounts for standing ads not changed each month.

It's Still Summer At CFP



We are happy to extend
STANDARD COMMUNICATIONS
Special Summer Sale in November

ALL 12 CHANNELS CRYSTALLED, FREE
in every Standard 826MA sold this month
(A \$104 Saving)

Write for our special cash price!

CFP ENTERPRISES

866 RIDGE ROAD, LANSING, N. Y. 14882
24 HOUR PHONE 607-533-4297

Send SASE for monthly listing of used equipment and bargain goodies.

QUALITY • THE SIZE • THE FEATURES • CHECK

CTCSS — MINI ENCODER
G-10 Glass epoxy circuit board. Precision grade American components. 3/4" x 1-1/4" (single freq.). Fits with ease into handheld units. Multi-freq. units avail. Low power consumption (less than 2mA). Single Freq. Unit Only \$14.95. Each Additional Freq. Only \$2.00.

• COMMUNICATION PRODUCTS & ENGINEERING •
P. O. Box 261 • Milford, Michigan 48042

RECEIVER-TRANSMITTER



R-392/URR RECEIVER:

High performance, rugged, 32 bands; 500 kHz thru 32 MHz continuous. Mechanical counter type digital readout to 300 Hz. Separate Megacycles and Kilocycles tuning. Triple conversion lower eight bands, double conversion all others. Built in crystal calibrator, squelch, RF gain, audio gain, antenna tuning, BFO, variable selectivity 8, 4, 2 kHz. Requires 22-30 VDC 3 Amps. Size: 11 1/2 x 14 1/4 x 11". Wt.: 52 lbs.; Shpg. Wt.: 65 lbs.

USED, REPAIRABLE \$125.00 USED, CHECKED \$195.00

T-195/GRC-19 TRANSMITTER: 1.5-20 MHz, 10 Bands. Freq. stability 0.03% plus 1000Hz. Manual or automatic tuning. CW, voice, or FSK operation. Power output: 50 Ohm antenna; 1.5-12 MHz 100 watts, 12-16 MHz 90 watts, 16-20 MHz 80 watts. Input voltage required: 22-30 VDC 42 Amps maximum, standby 9 amps. Size: 11 1/2 x 14 1/4 x 22". Wt.: 122 lbs.; Shpg. Wt.: 150 lbs. Price: Used - Complete Repairable: \$89.50

MT-851 MOUNTING BASE for R-392 & T-195. Shpg. Wt.: 60 lbs. \$10.00

CX-1599 CABLE, connects R-392 to T-195 — 10' length: \$6.95. **BATTERY CABLE** for T-195 w/Plug: \$4.95. AN/GRC-19 MANUAL: \$8.50. T-195 Maint. MANUAL: \$7.50.

COMBINATION OFFER: Repairable R-392, T-195, MT-851, CX-1599, T-195 Bat. Cable: Spec. Price, compl. \$200.00
All Prices FOB, Lima, Oh. Send for Free Catalog. Dept. HR

FAIR RADIO SALES

1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

NEW AND DIFFERENT!!



The all new T_{doc} manual for electronics experimenters and hobbyists ---

More than two years in the making, T_{doc} has gathered the most practical and usable data from industry, the U. S. Patent Office, DOD, NASA, NTIS (National Technical Information Service) and others. Jam-packed with all the data needed by the hobby experimenter at the bench. From theory refresher to applications diagrams, device characteristics, tables and formulas, charts and graphs -- hundreds upon hundreds of illustrations.

A High-Density Modular Document

No wasted space or words. Separate sections are removable in loose-leaf fashion -- books within a book -- mounted in a rugged binder, big enough to hold other T_{doc} publications -- or your own notes.

Just by way of example, the section on hand soldering was boiled-down from the practices of the American Welding Society -- Committee on Soldering and Brazing; NASA, USN, solder manufacturers, the Bell Telephone System and others. The section contains everything you need to know about solder, fluxes, soldering tools and techniques.

There are over 100,000 words covering theory and application of semiconductor devices -- diodes, transistors, the SCR/TRIAC, digital and linear integrated circuits, operational amplifiers, voltage regulators, counters and decoders, and much, much more.

Sections also treat the vacuum tube and CRT, capacitors and electrostatic devices, relays and switches, electromechanical devices and mechanical movements, energy sources, cable and wire, +++++

Update Without Annual Replacement

No need to buy a whole new book every year to keep abreast of information in the field; the "book within a book" style permits you to update only as needed.

There has never been another manual like it. That's why we undertook to put it together!! Once you have had a chance to put the manual to use, you'll start enjoying electronics as a hobby, with fewer unfinished projects that could have been completed had there not been an information gap!

Electronics Bench Manual

Introductory Price: \$17⁹⁵ Postpaid
In U.S.A.

Send check or money order marked "EBM" with your name and address to:

TECHNICAL DOCUMENTATION
BOX 340
CENTREVILLE, VA 22020

703-830-2535

Virginia residents please add 4% sales tax.

FREE CATALOG

CRAMMED WITH GOV'T SURPLUS ELECTRONIC GEAR **WRITE TODAY!**

TG-34A CODE KEYS self-contained, automatic, reproduces code practice signals from paper tape. 5 to 12 WPM built-in speaker. Brand new with tech manual. AC line cord \$24.50
Code practice tapes. Price upon request.



HEADSET Low impedance. W/large chamois ear cushions. 4' cord & plug. Reg. \$12.50. Our Special Price \$2.95
Less ear cushions \$1.95
High impedance adaptor for above 69



BC-1206-C RECEIVER Aircraft Beacon Receiver 200 to 400 Kc. Operates from 24V DC 1.5A. Continuous tuning, vol. control, on-off switch and phone jack. Very sensitive. Compact. Complete with tubes. NEW \$12.50



HANDMIKE Rugged, heavy-duty carbon hand-mike with press-to-talk switch. Equipped with 4-ft. cord & phone plug.
New, boxed Each \$1.88
2 for \$3.25



ARC-5 VHF RECEIVER, TRANSMITTER MODULATOR 100-156 MC
R-28/ARC5 VHF RECEIVER — Tunes 100 to 156 Mc AM. Easy to convert for 2 meter Operation! Ideal for installation in vehicles. Excellent Used With Tubes \$19.50



T-23 TRANSMITTER with tubes and crystals. Brand New in original carton \$21.50
MD-7 MODULATOR with tubes, exc. used \$10.50

G & G RADIO ELECTRONICS COMPANY

45-47 Warren St. (Dept. H-N) New York, N.Y. 10007 212-267-4605

TERMS: F.O.B. NYC 25% deposit with order, balance COD or remittance in full. MINIMUM ORDER \$5.00. Subject to prior sale and price change.

UHF COUNTER PREAMP 500 MHz

A super-wideband preamp with approx. 20dB gain from 1 MHz to 500 MHz. Output level is 200 to 300 millivolts. Probe is for measuring oscillators or transmitters without direct connection. Saves counters from overload damage when measuring high level RF. A self contained battery powered (3 pencils) hand-held unit with BNC connectors for 50 ohm systems, it is very useful for shop or lab. Write for details or order direct.
UHF Counter Preamp, w/probe, less batt. \$49.00 p.pd.



PAGES ELECTRONICS
ELECTRONIC COUNTERS

6742-C TAMPA AVENUE / RESEDA, CALIFORNIA / 91335

(213) 342-2714 (213) 345-1833

SPECIAL \$7.00 post-paid

COIL KIT FOR . . .

PART NUMBERS

L1
L2, 3
L4
RFC1
RFC2
L5, 6, 7



AS DESCRIBED
IN JULY
ham radio
PAGE 16

miniature
7-MHz transceiver

Coil Winding
Send Specs or Sample

Quick Quotes

Stock Coils
Coil & Choke Forms



CADELL COIL CORP.



THE ULTRA-BAL 2000

NOW -----An extremely rugged, weather-proof BALUN!

- Full 2KW, 3-30 MHz., 1:1 or 1:4 ratios.
- Special Teflon insulation. May be used with tuned lines and tuners.
- With dipole insulator and hang-up hook.

ONLY \$9.95ppd. (state ratio)

At your dealer or order direct

K.E. Electronics Box 1279, Tustin Calif. 92680



RTTY VIDEO DISPLAY UNIT

1000 CHARACTERS—ANY TV SET
VIDITYPE
MODEL 872 \$550
WRITE FOR BROCHURE

LELAND ASSOCIATES
 18704 GLASTONBURY RD.
 DETROIT, MI. 48219

YOUR BEST BET FOR FM!

- PREAMP KITS \$6, WIRED \$10 — FREQ. FROM 20 TO 230 MHz
- LED SCANNER KITS \$10
- FM RCVR KITS FOR 6 & 2M AND COMMERCIAL FREQ. \$49.95
- COMPONENTS FOR VHF PROJECTS

— SEND SASE FOR LITERATURE —

HAMTRONICS, INC.

182 BELMONT RD. ROCHESTER, N. Y. 14612

-VALU-PAK-

VOLTAGE REGULATORS TO-3

1 AMP NEGATIVE ea. 10 pak	1 AMP POSITIVE ea. 10 pak
LM 520 5V \$1.95 17.50	LM 309k 5V \$1.25 10.00
LM 320 5.2V 1.95 17.50	7806 6V 1.50 13.00
LM 320 12V 1.95 17.50	7812 12V 1.95 17.50
LM 320 15V 1.95 17.50	7815 15V 1.95 17.50
	7824 24V 2.25 20.00

CALCULATOR CHIP A1030

North American Rockwell A1030 4 function & percent; on-chip clock; 8 digit floating or fixed DP; full memory and constant 42 pin staggered lead DIP (unbent). ea. \$4.95 w/data



74S206 SCHOTTKY BIPOLAR

74S206 Schottky Bipolar 256x1 Random Access Memory. ea. \$3.49 10 pak \$29.00

10 AMP FULL WAVE BRIDGE RECTIFIER

10 AMP Full Wave Bridge Rectifier 100 PRV Motorola MDA 762-2. ea. \$2.25 10 pak \$20.00



OPTO ISOLATOR

ea. \$1.75 10 pak \$6.95
 Monsanto MCT 26 6 pin Dip

2N3055 NPN TRANSISTOR

2N3055 Transistor (power); PD-115W; VCE-60V; HFE-50; FT-30K; Case-TO-3. ea. \$1.15 10 for \$6.95

DIP RC NETWORKS

14 and 16 pin IC packages containing precision resistors and capacitors. NO SCHEMATICS AVAILABLE. Sample indicates most contain 10 to 15R and 1 or 2C. Assortment of 8, \$1.00

All Merchandise is new unused surplus and is sold on a money back guarantee.

Five dollar minimum order. Free first class postage on all orders. California Residents please add sales tax.

Send stamp for free catalog. Write to:

VALU-PAK

box AF Carmichael, Ca. 95608

DEALER INQUIRY INVITED



B-104 ANTENNA BUMPER MOUNT

NON-MARRING, adjustable to most bumper angles w/no damage to car, holds antenna secure w/no spring required, E-Z installation, tested to 100 mph\$9.00



TM-3 TRUCK & CAMPER ANTENNA MOUNT

E-Z installation under hood or on top of camper, available in black or chrome finish.

Chrome\$9.00 Black\$7.50



LITE-BOARD

A 5 in. x 6 in. unbreakable writing surface that plugs into 12 volt cigarette lighter socket providing indirect illumination at night, ideal for mini-logs and notes\$6.00

LARGER SIZES MADE TO ORDER

All CHM products are guaranteed 100% for workmanship and materials. If it works, tell others! If it doesn't, send it back and we'll fix or replace.

Send check or M.O. to.

CHM products

p.o. box 6193
 san bernardino, california 92412

Calif. res. add 6% sales tax

ANNOUNCING

THE NEW MODEL HCV-70FSVFK SLOW SCAN TO FAST SCAN VIEWFINDER MODIFICATION KIT FOR ROBOT*70 & 70A SLOW SCAN TELEVISION MONITORS

Also available for HCV-2A monitors. Covered by U.S. Patent #DD-033468.

NOW HERE AT LAST — From the Designer of the TEEC HCV-1B SSTV Camera and the HCV-2A SSTV Monitor and other Slow Scan TV Equipment (WB4HCV) comes another quality SSTV product...

This kit, when properly installed in the ROBOT* Model 70 & 70A SSTV Monitor, will allow Fast Scan (Sampling rate of Model 80 & 80A or the HCV-1B Camera) viewing on the same CRT display you now watch slow scan on, by a simple flip of a front panel switch. Viewing the scene in real time allows for quick, easy set-up of scene. Allows for razor sharp focus. Displays movement and a picture brighter than the normal p-7 slow scan picture. Allows slow scan to be transmitted while viewing the picture on fast scan.

Easy to assemble kit of parts and full step by step instructions. Nothing else to buy. Save \$195 by ordering your HCV-70FSVFK Fast Scan Viewfinder Kit today, instead of a separate monitor to take up more space. You will not only save \$195 but you will have the advantage of having both monitoring features in a single cabinet. Picture quality similar to model 60 & 61 viewfinders.

Note: Should be attempted by experienced kit builders only. Can be supplied factory installed for \$30.00 additional plus shipping. Turn around time about 3 days after receipt of monitor at factory. Write for details.

ALLOW 2-3 WEEK DELIVERY ON ORDERS WITH PERSONAL CHECKS. 3-4 DAYS ON CERTIFIED CHECKS, MONEY ORDERS, ETC.

PRICE COMPLETE POSTPAID IN U.S.A.

SORRY NO C.O.D. ORDERS

\$69.95

LATE BULLETIN — The Famous HCV-1B Camera and the HCV-2A Monitor is now scheduled to again be available by December 15, 1974. The HCV-3KB SSTV Keyboard by late January 1975. HCV-2B to have built-in fast scan viewfinder and HCV-1C to have auto/manual ALC (automatic light control); grey scale generator and more. Write James Thomas, WB4HCV, for full information at:

Sumner Electronics & Eng. Co. inc.

P.O. BOX 572
HENDERSONVILLE, TENNESSEE 37075
TELEPHONE 615 824 3235

Craig radio



IC-230 Icom
\$489.00

P. O. Box 615
Portsmouth, N.H. 03801

Phone (207) 439-0474
(603) 436-9062

Cash for any Collins military or commercial equipment or parts, especially 618T Tranceivers, 400T antenna couplers, AN/ARC-102, AN/ARC-94.

CASH

AN/MRC-95, SPACE ELECTRONICS CO.,
76 Brookside Drive, Upper Saddle River, N.J. 07458
(201) 327-7640

LEARN RADIO CODE



\$9.95

Album contains three 12" LP's 2 1/2 hr. instruction

THE EASY WAY!

- No Books To Read
- No Visual Gimmicks To Distract You
- Just Listen And Learn

Based on modern psychological techniques—This course will take you beyond 13 w.p.m. in LESS THAN HALF THE TIME! Available on magnetic tape \$9.95 — Cassette, \$10.95

EPSILON [E] RECORDS

508 East Washington St., Arcola, Illinois 61910



tri-tek, inc.

P. O. Box 14206, Dept. H
Phoenix, AZ 85063

8038C VCO WAVEFORM GENERATOR new factory parts, full specs. 14 pin DIP \$5.75, 2/\$10.50

LM566CH VCO FUNCTION GENERATOR new, TO-5, specs. \$4.00

MC1455 (555) PRECISION TIMER. new, mini-DIP \$1.65

MM5314 CLOCK CHIP. New, full specs. \$9.50

8220 MEMORY. 8 bit (4x2) content addressable memory. TTL and DTL compatible. For use in data-to-memory comparison, pattern recognition, cache memory, auto correlation, virtual memory, learning memory. New, house numbered. 16 pin DIP, specs. \$6.00; 10/\$45.00

VOLTAGE REGULATORS

MFC 6034. Variable to +20V, 200 MA. \$1.00

MC7805, 7806, 7812, 7815, 7824, positive voltage, 1A \$2.50

MC7912, 7915, Negative voltage, 1A \$2.50

723G variable 2 to 37V, 150 ma. House numbered. \$7.00

DTL SALE. 930, 946, 962, \$25, \$10/\$1.75; 100/\$15.00 Any Mix

TTL SALE. New, house numbered. SN7400, SN-7402, SN7410, SN7430, SN7450, SN7453, SN-7460. \$.25 ea, 10/\$2.00, 100/\$17.50 Any Mix

All orders postpaid. Minimum \$5 U.S., \$15 foreign. Latest lists, 10¢ stamp. Please ADD INSURANCE.

Improve performance with

hy-gain

AMATEUR ACCESSORIES!



Get the best from your beam!

BN-86 Broad Band Ferrite Balun Couples any 52 ohm unbalanced transmission line to any 3 to 30 MHz 52 ohm balanced antenna system. Improves energy transfer to antenna and eliminates stray RF from feedline and tower. Stops coax shield currents that upset front-to-back ratios and disrupt patterns. Helps stop TVI from line radiation. Has negligible insertion feed-through loss. The frequency independent BN-86 comes complete with all hardware required for beam or doublet installation. Gives you optimum performance over all Ham bands! **Order No. 242**

• VSWR 1:1 when terminated with balanced 52 ohm load • Rated at 1 kw CW • Impedance ratio 1:1 at 52 ohms • SO-239 input connector



Lightweight Center Insulator for Multi-Band Doublets

Model CI Strong, lightweight, water and weather-proof insulator molded from high impact cycolac. All hardware iridited to MIL specs. Accepts 1/4" or 3/8" coax. **Order No. 155**



Rugged End Insulators for Multi-Band Doublets

Model EI Hefty, 7-inch insulators molded from high impact cycolac. Leakage path increased to 12 inches by heavily serrated body. Available in pairs only. **Order No. 156**

For prices and information, contact your local Hy-Gain distributor or write:

hy-gain

Hy-Gain Electronics Corporation; 8601 Northeast Highway Six; Lincoln, NE 68507; 402/464-9151; Telex 48-6424.
Branch Office and Warehouse; 6100 Sepulveda Blvd., #322; Van Nuys, CA 91401; 213/785-4532; Telex 65-1359.
Distributed in Canada by Lectron Radio Sales, Ltd.; 211 Hunter Street West; Peterborough, Ontario.



GREGORY ELECTRONICS

The FM Used
Equipment People.

Send for New 1975 Catalog



MOTOROLA

T51G or T51GGV, 40-50 MHz.,
6 or 12 volt, 50 watts, vibrator
power supply, fully narrow
band, less accessories **\$58**

T53GGD, 150-170 MHz., 6/12
volt, 50 watts, dynamotor power
supply, transmit narrow band,
receive wide band, less acces-
sories **\$36**

D43GGV-3100, 150-170 MHz.,
6/12 volt, 30 watts, vibrator
power supply, front mount with
"private line" (less reeds), fully
narrow band, with accessories **\$88**

FMTRU41V, 150-170 MHz., 6/
12 volt, 10 watts, vibrator power
supply, front mount, transmit
narrow band, receive wide
band, with accessories **\$48**



R.C.A.

CMFT50, 25-54 MHz., 12 volt,
50 watts, transistorized power
supply, partially transistorized
receiver, fully narrow band with
accessories **\$128**

CMCT30, 150-170 MHz., 12 volt,
30 watts, transistorized power
supply, fully narrow band, com-
plete with accessories **\$98**

Now! Full line of
G.E./T.P.L. Solid State
2-way radios.



GREGORY ELECTRONICS CORP.

239 Rt. 46, Saddle Brook, N. J. 07662
Phone: (201) 489-9000

**YOU WOULDN'T
START A LOG
IN MARCH**



RIGHT NOW

is the time to order your


75

callbook


Don't wait until 1975 is half over. Get your new **Callbooks** now and have a full year of the most up-to-date QSL information available anywhere.

The new 1975 U. S. **Callbook** will have over 300,000 W & K listings. It will have calls, license classes, names and addresses plus the many valuable back-up charts and references you have come to expect from the **Callbook**.

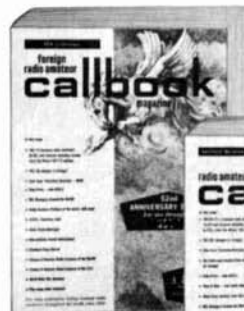Specialize in DX? Then you're looking for the new, larger than ever 1975 **Foreign Callbook** with over 225,000 calls, names and addresses of amateurs outside of the USA.



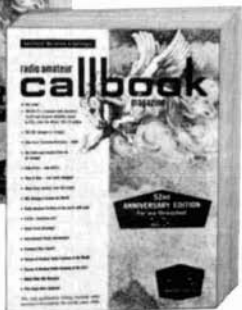**United States
Callbook**
All W & K Listings
\$12.95



**Foreign Radio
Amateur Callbook
DX Listings**
\$11.95

Order from your favorite electronics dealer or direct from the publisher. All direct orders add 75¢ shipping and handling per **Callbook**.

WRITE FOR **RADIO AMATEUR**
FREE
BROCHURE  **callbook** INC.
Dept. E 925 Sherwood Drive
Lake Bluff, Ill. 60044

Webster radio

2602h E. Ashlan
Fresno, Calif. 93726

Phone (209) 224-5111



FT101B Yaesu
\$649.00



DYNAMIC Electronics Inc.
P. O. Box 1131
Decatur, AL 35601

Signal Discriminators for Superior CW reception through QRM & QRN. Plug in installation, one year warranty, & 15 day return privilege.

DE-101 for phones only 115 VAC	\$32.95
DE-101A for SPKR & phones 115 VAC	\$43.95
DE-101B for SPKR & phones 12-18 VDC	\$32.95
DE-101C for phones only 12-18 VDC	\$21.95
CB-1 Tested DE-101C Circuit Board	\$15.95 ppd
CB-2 Tested Audio PWR amplifier BD	\$11.95 ppd
CB-3 Tested DE-101B Circuit Board	\$21.95 ppd

Add \$2 ship. for AC models, \$1 for DC models

LOOKING FOR A NEW CHALLENGE?

... then build a TV camera!



ONLY SOLID STATE CAMERA AVAILABLE IN KIT FORM OR FACTORY ASSEMBLED. COMPLETE KIT WITH VIDEO TUBE ONLY \$16.00. POSTPAID DELIVERY ANYWHERE IN USA, CANADA and MEXICO. OPTIONAL AUDIO SUBCARRIER \$16.95. WRITE or PHONE NOW FOR COMPLETE CATALOG OF KITS, PARTS and PLANS. DIAL 302-967-3771.

1301 BROADWAY N.W. ATV Research DAKOTA CITY, NEBR. 68731

SPACE SAVER TOWERS & MASTS

CZ series towers, cranks up, installs without guy wires. New lacing design creates greater strength.

Mini and Magna rotating masts . . . high strength galvanized tubing, self supporting crank-up.

For complete details and prices please check your local dealer or write Certified Welders L.A. City License #634

TRISTAO TOWER CO.
P. O. Box 115, Hanford, California 93230

YOUR GEAR WANTED!

WE PAY TOP DOLLAR OR TRADE!

Tell us what YOU have. Here's a partial list of what we want.

RT-742/ARC-51BX and control boxes . . . RT-743/ARC-51A . . . RT-662/GRC-106 . . . RT-698/ARC-102 . . . RT-823/ARC-131 or Magnavox FM-622 . . . RT-857/ARC-134 . . . RT-859/APX-72 . . . RT-524/VRC . . . RT-246/VRC . . . R-442/VRC . . . R-390A/URR . . . RT-648/ARC-94 . . . AN/TRC-68 . . . AN/VRC-24 . . . AN/URC-9 . . . CU-1669/AR . . . 490T-1 . . . 618T-1, -2, -3 . . . C-6287/ARC 51BX, Wilcox 807 . . . AN/PRC-25-74-77 . . . AN/ARC-114, -115, -116 . . . We buy all types of military test equipment . . . radios, etc. Do you have a TS-683/TSM Crystal Impedance Meter, H-P, or TEKTRONIX equipment?

If you hate money, we'll trade for NEW ham gear! But if you love that green stuff, or even like it a little bit — LET'S TRADE YOUR EQUIPMENT FOR OUR DOUGH!

COLUMBIA ELECTRONICS SALES, INC.

Box 9266-C, No. Hollywood, CA. 91609

Phone: (213) 764-9030



Like everything else in these mixed-up times, the price of Ham Radio, whether by subscription or newsstand, is going to be raised.

You can SAVE by subscribing or extending your existing subscription at today's low rates, but you must do it before the end of the year when our new rates take effect.

Remember, you can save even more with our low priced three year subscriptions where you get three years for the price of two.

going up

Please enter my

- new extension subscription
- 1 YEAR _____ \$ 7.00 These rates
- 3 YEARS _____ \$14.00 expire
- LIFE _____ \$99.00 Dec. 31, 1974

Name _____ Call _____

Address _____

City _____ Zip _____

ham radio

 magazine

GREENVILLE, NH 03048

Advertisers check-off

... for literature, in a hurry — we'll rush your name to the companies whose names you "check-off"

Place your check mark in the space between name and number. Ex: Ham Radio 234

INDEX

ATV *	International
Adva ___ 265	Crystal ___ 066
Amtech ___ 006	Jan ___ 067
Apollo ___ 011	Janel ___ 068
Barry *	K. E. ___ 072
Budwig ___ 233	K-Enterprises ___ 071
CHM ___ 273	KLM ___ 073
CFP ___ 022	Larsen ___ 078
Caddell ___ 247	Leland ___ 193
Columbia ___ 212	Logic ___ 133
Comm. Prod.	Madison ___ 083
& Eng. ___ 268	Martex ___ 197
Craig ___ 177	Matric ___ 084
Curtis ___ 034	Pagel ___ 092
Cush Craft ___ 035	Palomar ___ 093
Data Signal ___ 270	Poly Paks ___ 096
Dentron ___ 259	Porta-Pak ___ 274
Dycomm ___ 040	RMS ___ 239
Dynamic Elect. ___ 041	RP ___ 098
ECM ___ 190	Callbook ___ 100
Eimac ___ 043	Raytheon ___ 101
Electronics	Regency ___ 102
Center ___ 236	Robot ___ 103
Electronic Dist. ___ 044	SGC ___ 275
Epsilon ___ 046	Saroc ___ 146
Erickson ___ 047	Savoy ___ 105
Fair ___ 048	Signal/One ___ 262
G & G Radio *	Space-Military ___ 107
General Aviation ___ 168	Spectronics FM ___ 191
Gray ___ 055	Spectrum ___ 108
Gregory *	Summer Elect.
Hal ___ 057	& Eng. ___ 276
Hal-Tronix ___ 254	Swan ___ 111
Hamtronics ___ 246	Technical Doc. ___ 226
Ham Radio ___ 150	Tri-Tek ___ 117
Heath ___ 060	Tristao ___ 118
Heights ___ 061	VHF Engineering ___ 121
Henry ___ 062	Valu-Pak ___ 264
House of Dipoles ___ 036	Webster ___ 255
Hy-Gain ___ 064	Weinschenker ___ 122
Icom ___ 065	World QSL ___ 125

*Please contact this advertiser directly

Limit 15 inquiries per request.

November 1974

Please use before December 31, 1974

Tear off and mail to
HAM RADIO MAGAZINE — "check off"
 Greenville, N. H. 03048

NAME.....

CALL.....

STREET.....

CITY.....

STATE..... ZIP.....

Advertisers iNdex

ATV Research	93
Adva Electronics	84
Amtech	76
Apollo Products	77
Barry	96
Budwig Manufacturing Co.	76
CHM Products	89
CFP Enterprises	87
Caddell Coil Corp.	88
Columbia Electronics	93
Communication Products & Engineering	87
Craig Radio	90
Curtis Electro Devices	85
Cush Craft	95
Data Signal, Inc.	31
Dentron Radio Co.	7
Dycomm	86
Dynamic Electronics, Inc.	93
ECM Corporation	76
Eimac, Div. of Varian Assoc.	Cover IV
Electronics Center, Inc.	51
Electronic Distributors	85
Epsilon Records	90
Erickson Communications	76
Fair Radio Sales	87
G & G Radio Supply Co.	88
General Aviation	72, 73
Gray Electronics	64
Gregory Electronics	92
Hal Communications Corp.	62, 63
Hal-Tronix	86
Hamtronics, Inc.	89
Ham Radio	85, 93
Heath Company	48A-F
Heights Manufacturing Co.	64
Henry Radio Stores	Cover III
House of Dipoles	84
Hy-Gain Electronics Corp.	66, 74, 81, 91
Icom	69
International Crystal Mfg. Co. Inc.	75
Jan Crystals	70
Janel Labs	76
K. E. Electronics	89
K-Enterprises	70
KLM Electronics	78
Larsen Electronics	43
Leland Associates	89
Logic Newsletter	86
Madison Electronic Supply	86
Martex Corporation	68
Matric	70
Pagel Electronics	88
Palomar Engineers	68
Poly Paks	82
Porta-Pak	64
RMS Corporation	84
RP Electronics	86
Radio Amateur Callbook, Inc.	84, 92
Raytheon Company	5
Regency Electronics, Inc.	37
Robot Research, Inc.	1
SGC, Inc.	80
Saroc	65
Savoy Electronics	25
Signal/One	2
Space-Military Electronics	90
Spectronics FM	67
Spectrum International	68
Summer Electronics & Engineering	90
Swan Electronics	Cover II
Technical Documentation	88
Tri-Tek, Inc.	90
Tristao Tower Co.	93
VHF Engineering, Div. of Brownian Elect. Corp.	79
Valu-Pak	89
Webster Radio	93
Weinschenker, M.	71
World QSL Bureau	84

BUY OUR ANTENNA...TAKE IT OUT OF BOX...ASSEMBLE IT EASILY

IT WORKS

No Professional Help Required!
If I (an ad man) can put one together in minutes, anyone can!
And then...

IT WORKS BEAUTIFULLY!

FM 2 METER ANTENNAS

FROM THE WORLD'S LEADING MANUFACTURER
OF VHF/UHF COMMUNICATIONS ANTENNAS

NEW FM GAIN RINGO RANGER — Get extended range with this exciting new antenna. A one eighth wave phasing stub and three half waves in phase combine to concentrate your signal at the horizon where it can do you the most good. Your present AR-2 can be extended with a simply installed RANGER KIT.

ARX-2	100 watts	146-148 MHz
ARX-220	100 watts	220-225 MHz
ARX-450	100 watts	435-450 MHz
ARX-2K	RANGER KIT	

NEW FM MOBILE — Fiberglass 5/8 wave professional mobile antenna for roof or trunk mount. Superior strength, power handling and performance.
AM-147T 146-175 MHz mobile

NEW 4 POLE — A four dipole gain array with mounting booms and coax harness 52 ohm feed, 360° or 180° pattern.

AFM-4D	1000 watts	146-148 MHz
AFM-24D	1000 watts	220-225 MHz
AFM-44D	1000 watts	435-450 MHz

IN STOCK WITH YOUR LOCAL DISTRIBUTOR



cushcraft
CORPORATION

621 HAYWARD ST., MANCHESTER, N.H. 03103

Bird

We are official distributors for all Bird products
 Bird Model 43 Wattmeters \$100.00
 2 to 30 MHz Slugs \$35.00 Most VHF Slugs \$32.00

C.D. Ham II Rotator New Improved \$149.95

write or call for introductory offer
 8 conductor cable for HAM II or TR-44 Rotators 15¢/ft.

From Drake

Drake T-4XC \$580.00
 TR-22C Transceiver \$229.95
 Drake TR-72, 2-meter FM transceiver, 23 channels, 1 or 10 watts output, 13.8 volts \$320.00
 Drake TR-4C Transceiver new, \$599.95
 Drake AC-4 Power Supply \$120.00
 Drake 2NT Transmitter New cond. \$125.00
 Drake Operational Station Console Model C-4 \$395.00

IC-230 by Inoue

Completely synthesized with phase locked loop, Single Knob Control, Smart compact styling.

\$489.00

Latest Inoue Power Supply: IC3PA \$89.00

VENUS

SS-2, SLOW SCAN MONITOR - \$349.00
 SS-2K, SLOW SCAN MONITOR KIT
 \$269.00
 C1, FAST SCAN/SLOW SCAN
 CAMERA & CONVERTER - \$469.00

BARRY has Antennas

CushCraft A-147-4 \$13.50
 CushCraft A-147-11 \$21.95
 CushCraft New Ringo 8RX-2 6dB \$26.50
 Hustler 4 BTV Vertical Antenna \$56.95
 HyGain 18V 10-80 m. vertical \$33.00
 HyGain BN86 Deluxe Balun \$15.95
 HyGain 18 AVT/WB 10-80 meters vertical \$97.00
 Newtonics CGT-144 5.2 dB gain. Trunk lid mount \$39.95
 Gold Line Single Pole, 5 position coaxial switch, wall bracket or panel mount, 1 KW AM \$17.95

CONSTANT VOLTAGE TRANSFORMER. Input 115 VAC @ 60 Hz output, 24 Volts @ 15 amps regulated (plus or minus 1%) requires 6 mfd. 660 VAC capacitor add \$4.95 \$60 value \$14.95 ea. Mallory UHF Inductuner, covers 50-250Mc

\$9.95 ea.
 SWR Bridge less meter by Automatic Electric.
 To 800 Mcs, see July '74 CQ pg. 43 TNC connectors, \$90 value \$10.95
 Same with N connectors \$14.95

From VHF Engineering

HT Kit 2 watts out, 4 channel 2 meter transceiver kit HT-144 \$99.95
 RX 144C 2 meter receiver kit, .3µv sens. 2 watt audio \$69.95
 TX 144 or 220 Transmitter kit \$29.95

NPC POWER SUPPLIES

115 VAC Input - 12 VDC 4 amps out \$29.95
 Same as above but regulated \$47.95
 Model 108R — 115 VAC/13.6 VDC 8 amps continuous 12 amps surge. REGULATED \$69.95

From Barry

Deluxe Headsets, excellent for ham radio or audio visual labs: 600 ohms, vinyl cushioned: \$9.99
 With volume control \$11.99
 Collins 152-J1 Phone Patch, good, removed from equip. with detailed schematic \$24.95
 DYCOMM Block Booster "D" Kit, 10-15 watts in 45-55 watts out continuous Sale \$59.95
 DYCOMM Brick Booster "E" Kit, 1-3.5 watts in 12-30 watts out \$59.95

The Bassett DGA-2M high gain 2-meter collinear featuring fiberglass construction and polished chrome brass 3/8-24 thread mounting, 6 dB gain \$29.95

HF Gear from Barry

Famous Triton-II by Ten-Tec. Fully solid-state, 200 watt transceiver. 5 bands - full break in on CW \$669.00
 Ten-Tec 262 AC Power Supply with VOX \$129.00
 R-392/URR. 500 kc to 31.99 Mc, digital readout similar to R-390. 24 volts dc at 3 amps.
 As is \$150.00
 Checked Operational \$195.00
 Lab aligned, Lab tested OK \$240.00
 R-389/URR 15 to 1500 kc. Manual or motor tuned with digital readout. Very good \$495.00
 Servo Corp. R-5200 Receiver 50 to 250 Mc continuous CW, FM, AM, adjustable selectivity, 115 volt AC \$150.00
 Hunter Bandit Linear Amplifier, w/3-400Z's \$495.00
 HQ-170 - Hammarlund 170 6-160 meter with/clock: \$175.00
 Millen, Solid State Dipper 1.7-300 MHz Model 90652 \$125.00
 Kenwood R-599a. With accessories Write
 Nye (Johnson) 52 ohm low pass filter \$19.50
 Nye Heavy Duty transmitting Key \$9.95
 Nye Kilowatt Matchbox with relay \$239.50
 Nye 275 Watts Matchbox with relay \$139.50

Clegg FM-27B, 146-148 Mc coverage without buying a crystal. Fully synthesized 25 w. out \$479.95
 Shipping prepaid on all FM-27B's
 031 Power Supply for FM-27B \$89.95

Tube Headquarters. Diversified Stock. Heavy Inventory of Eimac tubes, chimneys, sockets, etc. 3-500Z or 3-400Z Specify \$42.50
 572-B \$19.95

BARRY 512 Broadway NY, NY 10012
 DEPT. H-11
 212-WA-5-7000 **ELECTRONICS**
 TELEX 12-7670

top quality... top value... fm by tempo

Tempo's VHF transceivers offer commercial performance at amateur prices. Compare these transceivers with any other available. Compare their performance, their quality of construction, their ease of maintenance, and then compare prices. Your choice will have to be Tempo.



TEMPO/CL 146

The CL-146 offers operation on the 146 MHz amateur band. The price includes a microphone power cord, mounting bracket and one pair of crystals. A full line of accessories is also available.

- 12 channel capability • 13 watts or a power savings 3 watts
- All solid state, 12 VDC • 144 to 148 MHz (any two MHz without retuning)
- Supplied with one pair of crystals • RF output meter, S-meter, receiver detector meter
- Provisions for external oscillator • Monitor feature • Audio output at front panel
- Internal speaker • The Price: \$299.00

TEMPO/CL 220



As new as tomorrow! The superb CL-220 embodies the same general specifications as the CL-146, but operates in the frequency range of 220-225 MHz (any two MHz without retuning). At \$299.00 it is undoubtedly the best value available today.



FMH-MC for Marine & Commercial service also available.

TEMPO/fmh

So much for so little! 2 watt VHF/FM hand held. 6 Channel capability, solid state, 12 VDC, 144-148 MHz (any two MHz), includes 1 pair of crystals, built-in charging terminals for ni-cad cells, S-meter, battery level meter, telescoping whip antenna, internal speaker & microphone. \$199.00



TEMPO VHF/UHF Power Amplifiers

Solid state power amplifiers for use in most land mobile applications. Increase the range, clarity, reliability and speed of two-way communications.

VHF (135 to 175 MHz)

Drive Power	Output	Model No.	Price
2W	130W	130A02	\$199
10W	130W	130A10	\$179
30W	130W	130A30	\$189
2W	80W	80A02	\$169
10W	80W	80A10	\$149
30W	80W	80A30	\$159

UHF (400 to 512 MHz)

2W	70W	70D02	\$270
10W	70W	70D10	\$250
30W	70W	70D30	\$210
2W	40W	40D02	\$180
10W	40W	40D10	\$145
2W	10W	10D02	\$125


FCC Type accepted models also available. Please write.

Henry Radio

11240 W. Olympic Blvd., Los Angeles, Calif. 90064 213/477-6701
931 N. Euclid, Anaheim, Calif. 92801 714/772-9200
Butler, Missouri 64730 816/679-3127

AVAILABLE AT SELECT DEALERS THROUGHOUT THE U.S.

Prices subject to change without notice.

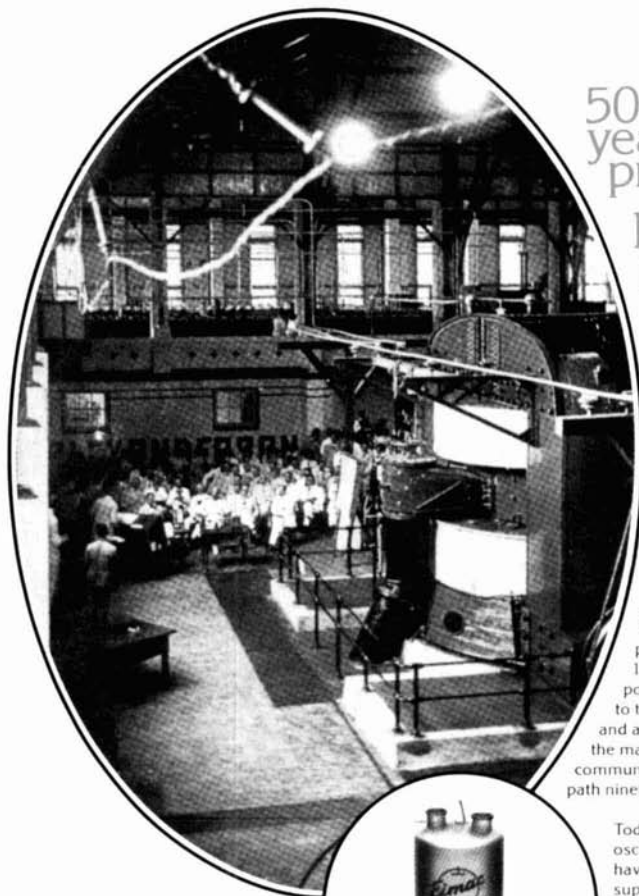

50
years of
progress

Now EIMAC leads in super power

1924 was an eventful year. Appleton and Barrett measured the Heaviside layer. George Gershwin wrote *Rhapsody in Blue*. The Olympic games were held in Paris.

And on the far side of the world, the Director of Radio for the Dutch East Indies announced the opening of commercial wireless service from Java to Holland. The new super power station, PKX, was on the air with 1.6 megawatts on 15,600 meters. With a power input of slightly over 3.2 megawatts to the 236,080 kg (260 ton) oscillating arc and an antenna strung between mountains, the mammoth Malabar facility provided communication over a 12,000 km (7,500 mile) path nineteen hours out of the twenty four.

Today, fifty years later, the huge generators, oscillating arc and mountain-size antennas have returned to the jungle. Now, EIMAC super power tetrodes dominate the communication world, a single EIMAC X-2159 replacing the 260 ton arc transmitter of yesterday. Dependability, reliability and cost-effectiveness are dominant as EIMAC leads the field in super power communication. EIMAC has the answer **today** for your communication needs tomorrow.

Today,
the EIMAC
X-2159
super power
tetrode.



For further information contact EIMAC, Division of Varian, 301 Industrial Way, San Carlos, California 94070. Or any of the more than 30 Varian/EIMAC Electron Device Group Sales Offices throughout the world.


Eimac
division
varian

**MORE THAN THREE YEARS AGO,
HEATH ENGINEERS ACCEPTED
THE CHALLENGE TO DEVELOP
A COMPLETELY NEW
APPROACH TO AMATEUR
RADIO DESIGN.**

**THE RESULTS SOON WILL BE
HEARD WORLD-WIDE.**



THE NEW HEATHKIT SOLID-STATE TRANSCEIVER

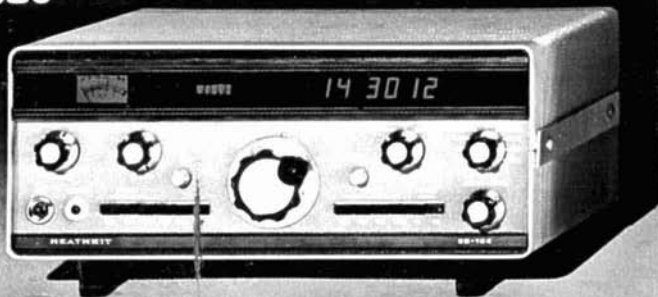

SB-104...the most advanced design in amateur radio

All the modern circuitry, built-in features, high performance, and honest operating convenience you have wanted for years...here today.

Completely solid-state...from front end to RF output, with over 275 advanced solid-state devices, including 31 ICs, 75 transistors and 171 diodes. The result is a design that runs cooler, quieter, better, longer. The four finals are totally protected.

Totally broadbanded. The new 104 means instant QSY. You can go from CW on the low end of 80 to USB on the high end of 10 in seconds...with perfect tune. Gone are the bothersome Preselector, Load and Tune controls. Just choose the band, dial in the operating frequency, select your mode...and go!

True digital readout. The new SB-104 provides 6 digits of large, bright, easily read frequency information...with resolution down to 100 Hz on all bands. And unlike other so-called digital readout systems that interpret just the VFO frequency, the SB-104 incorporates true digital frequency measurement circuitry that takes into account all three frequencies: VFO, HFO and BFO. What you see is where you are...always.

Total operating convenience. The front panel is clean, well-labeled and easy to use. The large spinner knob on the VFO delivers about 30 kHz per revolution. To the right of the VFO knob are controls for Drive Level, Bandswitch and the switched (Off-fast-slow) AGC to suit various operating conditions. Pushbuttons select mode (USB/LSB/CW), a Tune button for loading linear amplifiers, a Hi-Lo power switch, and Power on-off switch. On the left of the VFO knob are controls for audio and RF gain, jacks for a PTT mike and phones, and pushbuttons to monitor input DC voltage, ALC action and relative power on the front panel meter. The built-in VOX can be switched in and out with another pushbutton...and we've put the VOX gain and delay controls on the front panel, too. And, if you've installed the optional Noise Blanker, a front panel pushbutton switches it on or off.

Performance-plus! The SB-104 is more than convenient to use...it's a pleasure. The transmitter delivers a solid 100 watts *output* in the high power position; for QRPers the output can be switched to one watt instantly with the front panel pushbutton.

The broadband receiver performance is spectacular...carefully designed to minimize cross-modulation and intermodulation; active devices are kept to a minimum ahead of the highly selective crystal filter. Adjacent signal overload is negligible, yet sensitivity is better than 1 μ V. And there is a 15 MHz WWV receive position on the band switch.

Easy assembly and alignment. We believe the new SB-104 is the most sophisticated amateur radio transceiver on the market. It has over 2800 parts, consequently it won't go together in just an evening or two, (we have averaged about 50 hours in pre-production assembly). But it does go together easily, easier than any we've ever offered. All but a handful of the components mount on one of the 15 glass epoxy boards, and two wiring harnesses eliminate most of the point-to-point wiring. Eleven of the boards plug-in for easier assembly, and 7 of them can be extended out of the chassis.

And still more features! The SB-104 will operate directly from a 12V automobile electrical system. For fixed station use, just hook-up the new HP-1144 supply. Complete back panel inputs and outputs...see feature photo on right page. And, we've even designed-in a place on the readout panel where you can light up your call sign when you build the SB-104...we give you all the letters and numbers you need to do it.

This is the transceiver you'll be hearing worldwide. Years ahead of every other...at any price. The SB-104...it belongs at your operating position.

Kit SB-104, 31 lbs. 669.95

**Kit SBA-104-1, Noise Blanker, 1 lb.,
mailable 24.95**

**Kit SBA-104-2, Mobile mount with hinged rear,
telescoping front support, 11' cable, power relay,
and circuit breaker, 6 lbs., mailable. \$34.95**

**Kit SBA-104-3, 400 Hz CW crystal filter,
1 lb., mailable 34.95**

Available December

SPECIFICATIONS

SB-104 SPECIFICATIONS — TRANSCIVER SECTION — GENERAL OPERATION: Frequency Coverage: 3.5 MHz through 29.7 MHz amateur bands, 15 MHz WWV receive only. **Frequency Stability:** Less than 100 Hz/hr drift after 30-min. warmup; less than 100 Hz drift for $\pm 10\%$ change in primary voltage. **Modes of Operation:** Selectable upper or lower sideband (suppressed carrier) and CW. **Readout Accuracy:** Within ± 200 Hz ± 1 count. **Audio Frequency Response:** 350 to 2450 Hz ± 75 Hz (6 dB bandwidth). **Dial Backlash:** 50 Hz max. **Phone Patch Impedance:** 4 ohm output to speaker; high impedance output to transmitter. **Power Requirements:** 13.8 VDC nominal (max. 16 VDC) at: Receiver: 2 amp. Transmitter: low power: 3 amps; high power: 20 amps. **TRANSMITTER:** **RF Power Output:** High Power (50 ohm non-reactive load): SSB: 100 watts PEP ± 1 dB; CW: 100 watts ± 1 dB. **Low Power SSB:** 1 watt PEP (minimum); CW: 1 watt (minimum). **Output Impedance:** 50 ohms, less than 2:1 SWR. **Carrier Suppression and Unwanted Sideband Suppression:** 55 dB down from 100 watt single-tone output at 1000 Hz reference. **Harmonic Radiation:** 45 dB below 100 watt output. **Spurious Radiation:** -50 dB within ± 3 MHz of carrier; -60 dB farther than ± 3 MHz from carrier, except -40 dB at 3.39 MHz on 80 meter band. **Third Order Distortion:** 30 dB down from two-tone output, reference at 100 watts PEP. **Transmit/Receive Operation:** SSB: PTT or VOX; CW: Keyed-tone VOX or manual. **CW Side-Tone:** Internally switched to speaker or headphones in CW mode. Approximately 700 Hz tone. **Microphone Input:** High impedance with a rating of -45 to -55 dB; approx. 25K ohms to match Heath desk-type microphone. **RECEIVER — Sensitivity:** Less than 1.0 microvolt for 10 dB signal-plus-noise-to-noise ratio for SSB operation. **Selectivity:** 2.1 kHz minimum at 6 dB down, 5 kHz maximum at 60 dB down. (2:1 nominal shape factor). **CW Selectivity:** (with accessory CW filter) 400 Hz at 6 dB down, 2 kHz max. at 60 dB down. **Overall Gain:** Less than 1 microvolt for 0.5 watt audio output. **Audio Output:** 2.5 watts into 4 ohms, 1.25 watts into 8 ohms, at less than 10% THD. Low impedance headphones (4-8 ohm). **AGC:** Less than 1 millisecond attack time; switch selectable 100 μ sec. and 1 msec. release, and OFF. **Intermodulation Distortion:** -65 dB min. **Image Rejection:** -60 dB min. **IF Rejection:** -60 dB min. **Internally Generated Spurious:** Below 2 microvolt equivalent antenna input, except at 3.65, 3.74, and 21.2 MHz. **MECHANICAL — Front Panel Controls/Switches:** AGC — Off, Slow, Fast; AF Gain; Microphone Jack; Headphone Jack; Main Tuning; Mic/CW Level; Vox Gain; Vox Delay; Band Switch. **Pushbuttons:** ALC (Meter); 13.8V (Meter); Relative Power (Meter); 100 Hz (Disable); Noise Blanker (On/Off); LSB (Mode); USB (Mode); CW (Mode); Tune; Hi/Lo (Power Select); VOX (On/Off); PWR (On/Off). **Rear Panel Controls/Sockets:** Anti-Trip; Sidetone Level; Linear Amplifier ALC Input; Phone Patch Input; Phone Patch Output; Key (CW) Input; Speaker (4 ohm) Output; Spare (2); Receiver Audio Input; VFO Input; VFO Output; IF Output; Driver Output; Ground Post; Power Plug; Accessory Socket (includes relay output); Antenna Input; Receiver Antenna Input; Common/Separate Antenna Switch. **Dimensions:** 5 1/2" H x 14 1/2" W x 13 1/4" D. (Less knobs, feet and connectors). **Weight:** 20 lbs.

The SB-104 output board and final transistors are warranted for one full year.

HP-1144 SPECIFICATIONS — Output Voltage: 13.8 VDC regulated (Adjustable from approximately 11 to 16 VDC). **Maximum Output Current:** 20 amperes, Intermittent. 8 amps continuous. **Transistor Integrated Circuit and Diode Complement:** 2N3643 transistor; 2N3055 transistor; 40411 pass transistor (2); MF6030 regulator IC; 1N4002 silicon diode; MDA990-2 bridge rectifier. **Power Requirements:** 110 to 130 VAC @ 6A or 220 to 260 VAC @ 3A, 50/60 Hz maximum. **Dimensions:** 5 1/2" H x 9 1/4" W x 10 1/4" D. **Regulation:** Less than 2% output voltage variation from no load to 20 amperes. **Ripple:** Less than 1% at 20 amperes. **Fuses:** 7-amp, 3AG, slow-blow primary. 20-amp, 3AG, output. **Net Weight:** 23 lbs.

SB-604 SPECIFICATIONS — Speaker Size: 5" x 7" oval. **Voice Coil Impedance:** 3.2 ohms. **Frequency Response:** 300 to 3000 Hz. **Magnet Weight:** 3.16 oz. **Cabinet:** Aluminum with gray wrinkle finish. **Dimensions:** 7 1/4" H x 10 1/4" W x 14" D.

SB-644 SPECIFICATIONS — Frequency Coverage: 5.0 — 5.5 MHz allowing 80, 40, 20, 15, 10 meter operation in the SB-104. **Frequency Stability:** Less than 100 Hz drift per hour

after thirty minute warmup. **Modes of Operation:** Remote VFO; Main VFO; Receive Remote/Transmit Main; Receive Main/Transmit Remote; Crystal frequencies (2) (crystals not supplied). **Dial Backlash:** 100 cycles max. **Power Requirements:** 11V and 13.8V at 500 mA from the SB-104. **RF Output:** 0.34 to 0.4V RMS over 5 to 5.5 MHz into a 50 ohm load.

SB-634 SPECIFICATIONS — CLOCK — Display: Six full digits. **Time Base:** 24 hours. **Accuracy:** Determined by accuracy of power line frequency. **TIMER — Display:** Three full digits. **Time Interval:** 10 minutes with automatic reset. Manual reset at any portion of 10-minute period. **Accuracy:** Determined by accuracy of power line frequency. **Signal:** Visual only or both visual and aural; switch selected. **RF POWER/SWR METER — Frequency Range:** 1.8 to 30 MHz. **Wattmeter Accuracy:** $\pm 10\%$ of full-scale reading. **Power Handling Capability:** 2000 watts (maximum). **SWR Sensitivity:** Less than 10 watts. **Impedance:** 50 ohm nominal. **SWR Bridge:** Continuous to 2000 watts P.P. **Connectors:** UHF type SO-239. **PHONE PATCH — Circuit:** Telephone hybrid circuit. Allows voice control or manual operation. **TELEPHONE LINES — Input Impedance:** Approximately 600 ohm. **Null Depth:** At least 30 dB isolation between transmit and receive circuits. **Receiver Impedance:** Effective match from 3 to 16 ohm. **Transmitter Impedance:** 600 ohm or higher impedance output. **GENERAL — Meter:** 100 μ A movement. VU readings for phone patch monitoring. Null depth indication. RF power output, relative power, and SWR readings. **FRONT PANEL CONTROLS — Timer:** Off, Visual, Aural Visual. **Reset:** Push-button switch. **Patch Gain:** Transmitter, Receiver. **SWR:** Sensitivity. **Mode:** SWR, Forward and Reflected. 2000 W and 200 W. **Phone Patch. Rear Panel Controls — Clock:** Time hold, minutes set, seconds set. Null Adjust control; Null-Monitor switch; C adjust control; R adjust control. **Power Requirements:** 120/240 VAC, 50/60 Hz, 15 watts.

SB-614 SPECIFICATIONS — RF SAMPLING SECTION: Frequency Coverage: 80 through 6 meters (3.5 — 54 MHz). **RF Power Limits:** Exciter input (50 — 75 ohm) 10 to 300 watts; Antenna input (50 — 75 ohm) 10 to 1000 watts (up to 1500W PEP). **Insertion Loss:** Negligible. **VERTICAL AMPLIFIER:** Input Impedance: 1 Megohm shunted by 75 pf. Sensitivity: 60 mV rms/1/4" vertical deflection. **Attenuator:** 2 position; x1, 2 volts rms max. input; x10, 20 volts rms max. input. **Frequency Response:** 10 Hz to 50 kHz ± 3 db. **HORIZONTAL AMPLIFIER:** Input Impedance: 1 Megohm shunted by 50 pf. Sensitivity: 50 mV rms/1/4" horizontal deflection. **Frequency Response:** 10 Hz to 3 MHz ± 3 db. **SWEEP GENERATION:** Type: Recurrent; automatic sync. **Frequency Range:** 10 Hz to 10 kHz in three ranges. **GENERAL:** CRT: 3RP1-A flat face, green, medium persistence phosphor. **Graticule:** 250 inch squares 6 x 8 (1.5 x 2.0 inches total viewing area). **Power Supplies:** All solid-state rectifiers. All amplifier supplies regulated. **Power Requirements:** 110-130 or 220-260 VAC, 50/60 Hz, 35 watts. **Front Panel Controls:** Intensity — Off-on; Mode — SSB, TRAP, CROSS; Focus; Vertical Gain; Vertical Position; Horizontal Gain; Horizontal Position; Sweep — variable; Range — 100 Hz, 1 kHz, 10 kHz. **Rear Panel Controls:** Astigmatism; Vertical attenuator — X1, X10. **Rear Panel Connectors:** Antenna: SO-239; Exciter: Phono; Vertical Input: Phono; Horizontal Input: Phono. **DIMENSIONS:** 7 1/4" H x 10 1/4" W x 15 1/4" D. **Net Weight:** 12 lbs.


SB-230 SPECIFICATIONS: Band Coverage: 80, 40, 20, 15 and 10 meter amateur bands. **Maximum Power Input:** 1200 W PEP SSB; 1000 W CW; 400 watts RTTY/SSTV. **Duty Cycle:** SSB: continuous voice modulation; CW: continuous (max. key-down time 30 seconds); RTTY/SSTV: 50% (max. transmit time 10 minutes at 400 watts). **Driving Power Required:** less than 100 W. **Third Order Distortion:** -30 dB or better. **Output Impedance:** 50 ohms at 2:1 SWR max. **Input Impedance:** 52 ohms at 1.5:1 SWR max. **Meter Switch:** Exciter only; Relative Power; Plate Current; Grid Current; High Voltage. **Front Panel:** Load; Tune; Band; Relative Power sensitivity; Power switch; Meter switch. **Rear Panel:** ALC output; Exciter relay; RF input; RF output; Ground lug; Fuse; Line cord. **Tube:** Type 8873. **Zero signal plate current:** 25 mA. **Power Requirements:** 120 VAC, 50/60 Hz, 14 A max. 240 VAC, 50/60 Hz, 7 A max. **Dimensions:** 14 3/4" W x 16" D x 7" H. **Net Weight:** 33 1/2 lbs.

HEATH

Schlumberger

HEATH COMPANY
BENTON HARBOR,
MICHIGAN 49022

NEW SYSTEM-ENGINEERED

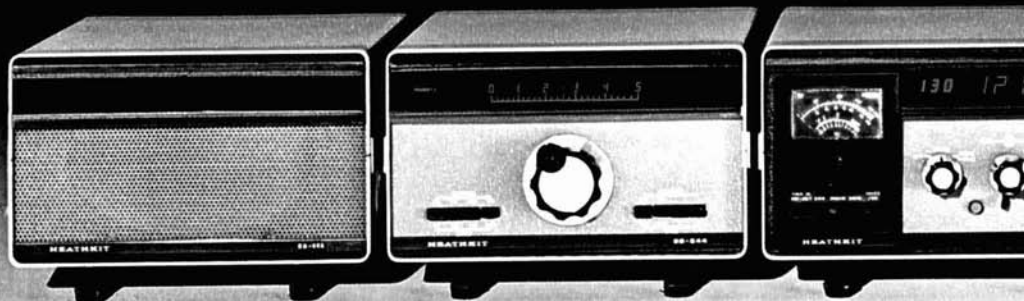

SB-604 Station Speaker

Designed and styled to match the new SB-104 Transceiver, the cabinet is large enough to house the HP-1144 AC Power Supply. The 5" x 7", 3.2 ohm speaker is response-tailored for SSB. Connector cable & plug are included.

Kit SB-604, Speaker & cabinet,
8 lbs., mailable **29.95**

HP-1144

Fixed-Station AC Power Supply



This new 120 V/240 VAC operated supply provides the 13.8 VDC required by the new SB-104 Transceiver. The full-wave bridge circuit has triple Darlington regulation with an integrated circuit which samples, compares, and automatically adjusts transistor bias to maintain a fixed output level. Output is remotely sampled at the load end of the power cable, thereby compensating for voltage drop across fuse and cable, to provide almost no change in voltage from no load to full load conditions. A cable and socket provide output power and a series connection to the SB-104 remote on-off switch. The generous heat sink fits on the back of the supply, and the entire unit may be mounted within the SB-604 speaker cabinet.

Kit HP-1144, fixed-station supply,
28 lbs., mailable **89.95**

SB-634 Station Console

Five station accessories in one!

24-hour digital clock: six half-inch gas discharge digits indicate hours, minutes and seconds. The clock runs continuously, as long as the console is plugged in.

Ten-minute ID timer: Three gas discharge digits indicate minutes and seconds up to 9:59. At ten minutes the timer recycles and provides either a visual alarm or both visual and audible alarms. Pushbutton zero reset.

RF wattmeter: The big meter delivers measuring capability of either 200 watts or 2000 watts full scale. 160 through 10 meters.

SWR bridge: Push a button to measure SWR. Separate front panel SWR sensitivity control.

Phone patch: The hybrid patch can be used either manually or with VOX control without switching connections. VU capability on the meter and separate front panel controls to adjust transmitter and receiver gain independently. Line isolation can be adjusted with a rear panel control.

Kit SB-634, 14 lbs. **179.95**

SB-644 Remote VFO

Designed exclusively for the new SB-104. The new SB-644 provides serious DXers with really useful split transmit/receive capability. With the "104/644" combination, you aren't frequency limited in any way—the transceiver can be at one end of the band, the remote VFO at the other end.

Multi-mode capability. The "644" allows transceive operation on either itself or the "104"... transmit on the "104" and receive on the "644"... receive on the "104" and transmit on the "644". And you can use either of the two crystal positions in the "644" for fixed-frequency control.

Easy pushbutton operation. Front panel pushbuttons on the "644" control all transceive, transmit and receive modes on both the "104" and the remote VFO. No switching on the "104" is necessary. Status lamps behind the window indicate frequency-control mode.

Digital readout in the SB-104. Although the SB-644 includes a linear dial on its front panel to get you into the right frequency area, actual frequency readout takes place in the "104". The display automatically changes to the correct frequency as you go from transmit to receive.

Kit-built VFO. The "644" uses the same kit VFO as the new SB-104. And thanks to the true digital frequency readout in the "104", concern about dial VFO linearity problems is a thing of the past. If you work serious DX with your new SB-104, you'll want the new "644".

Kit SB-644, 10 lbs. **119.95**

SOLID-STATE ACCESSORIES



SB-614 Station Monitor

How clean is your signal? With the SB-614, you'll know. It monitors transmitted SSB, CW, and AM signals up to 1 kW from 80 - 6 meters. The highly visible 1½ x 2" CRT, with push-pull drive for a keystone-free, sharp, clean trace, indicates a wide variety of common operating problems: non-linearity, insufficient or excessive drive, poor carrier or sideband suppression, regeneration, parasitics and CW key clicks. The manual includes 40 CRT display illustrations and explanations.

Complete controls. All standard scope control functions are available in the "614"...Vertical Gain & Position, Horizontal Gain & Position, Focus, Mode (SSB, Trapezoid & Cross for RTTY Mark/Space adjustments). The improved recurrent, automatic sync-type sweep generator is adjustable in three ranges from 10 Hz to 10 kHz. Front panel control gives 11 steps of attenuation. For limited test applications the "614" can be used as a normal scope, and provides 10 Hz to 50 kHz bandwidth, good sync and high input sensitivity. A rear panel 10:1 vertical attenuator provides extra convenience.

Additional features include all solid-state design; rear panel Astigmatism control; standard horizontal and vertical inputs for use as a scope; exciter and linear inputs/outputs. Circuit board/wiring harness design makes assembly fast and easy. What kind of signal do you have? Order your new SB-614 today and know.

Kit SB-614, 17 lbs. 139.95

SB-230 Conduction-Cooled 1 KW Linear

Strong and silent. The new "230" uses a husky Eimac 8873 triode in proven, stable, grounded grid circuitry to deliver up to 1200 watts PEP SSB, 1000 watts CW input from less than 100 watts drive. And the "230" is also rated at 400 watts input for slow-scan TV and RTTY. A massive heat sink eliminates the need for a fan.

Complete operating convenience. On the front panel of the new SB-series low profile cabinet you'll find all controls at your fingertips for easy operating. Bandswitching is done with a

single knob...Load and Tune controls are clearly marked. Full metering facilities.

A full complement of built-in safety features. The cabinet features microswitch interlocks on both the top and bottom to shut down the primary power when the cabinet shells are removed. Front panel status lights indicate Hi Temp, Exciter and Delay. The heat sink for the 8873 is temperature monitored; if the temperature rises too high, a thermal circuit breaker opens, the linear shuts down and the Hi Temp light goes on. The Exciter light indicates that the linear is running straight through, without amplification. To allow the tube sufficient time to warm up, a delay circuit is built-in. When warm-up is completed, the Delay light goes out. The On-Off switch also includes a built-in circuit breaker for the primary side of the power transformer. And the cathode of the tube is fused for additional protection.

Easy assembly. The new SB-230 goes together in 15 to 20 hours. No alignment is necessary.

The new SB-230, styled to match the SB-104 transceiver, delivers all the features and performance you've come to expect from Heath. We think you will agree it's the greatest value in modern linears.

Kit SB-230, 40 lbs. 319.95

GET FULL DETAILS
Send for the new FREE
1975 Heathkit Catalog.



HEATH COMPANY, Dept. 122-11
Benton Harbor, Michigan 49022

HEATH
Schlumberger

Please rush my FREE Heathkit Catalog.

Name _____


Address _____

City _____ State _____ Zip _____


*Mail order prices; F.O.B. factory
Prices & specifications subject to change without notice.

SS-103


CHECK THESE ADVANCE DESIGN FEATURES:

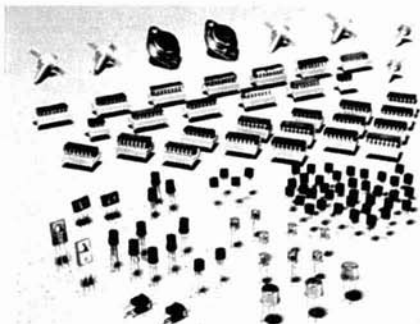

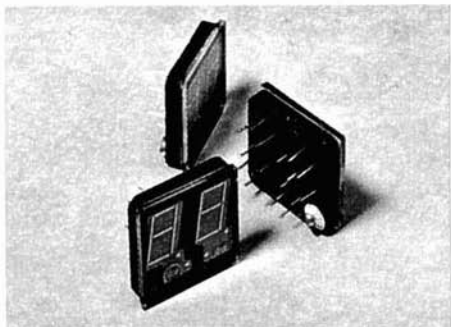
Completely solid-state design...including the finals. Over 275 solid-state devices, including 31 integrated circuits. *The SB-104 output board and final transistors are warranted for one full year.*



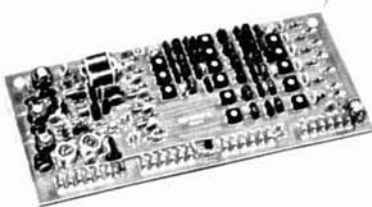True digital readout. Six 1/2" gas-discharge displays deliver resolution down to 100 Hz with across-the-room visibility.



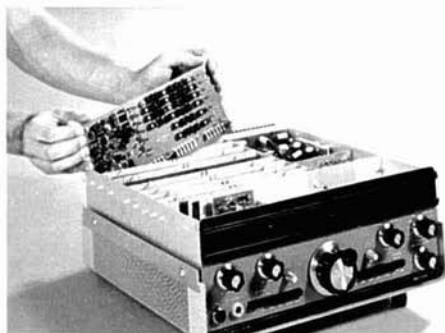
Completely broadbanded. Neither the transmitter nor receiver sections require tuning from 3 to 30 MHz...instant QSY from 80 to 10 meters is a reality.



Circuit board construction. Most components mount on 15 circuit boards for easy assembly. The seven major boards can be extended out of the chassis for adjustment or troubleshooting while rig is operating.



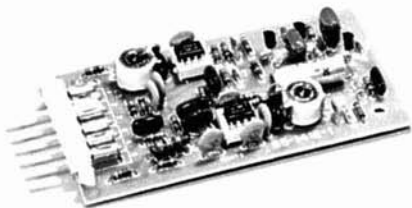Complete back-panel connections: Phone patch in & out; auxiliary audio input; speaker; key; ALC; VFO in & out; driver out; IF out; accessory plug; power plug; two spare jacks; separate transmit & receive antenna jacks.



New noise blanker plugs into SB-104 & solves the ignition noise problem. Provides up to 50 dB of effective blanking. Rep rate 10 to 2000 pulses/sec.; pulse widths 1 to 250 μ sec.