

\$2.00

ham radio


magazine

hr 

MARCH 1979

- voltage-tuned oscillator 26
- digital display 40
- grounded-grid matching 48
- phase-shift networks 70
- cabinet construction 76

small beams
with big
performance

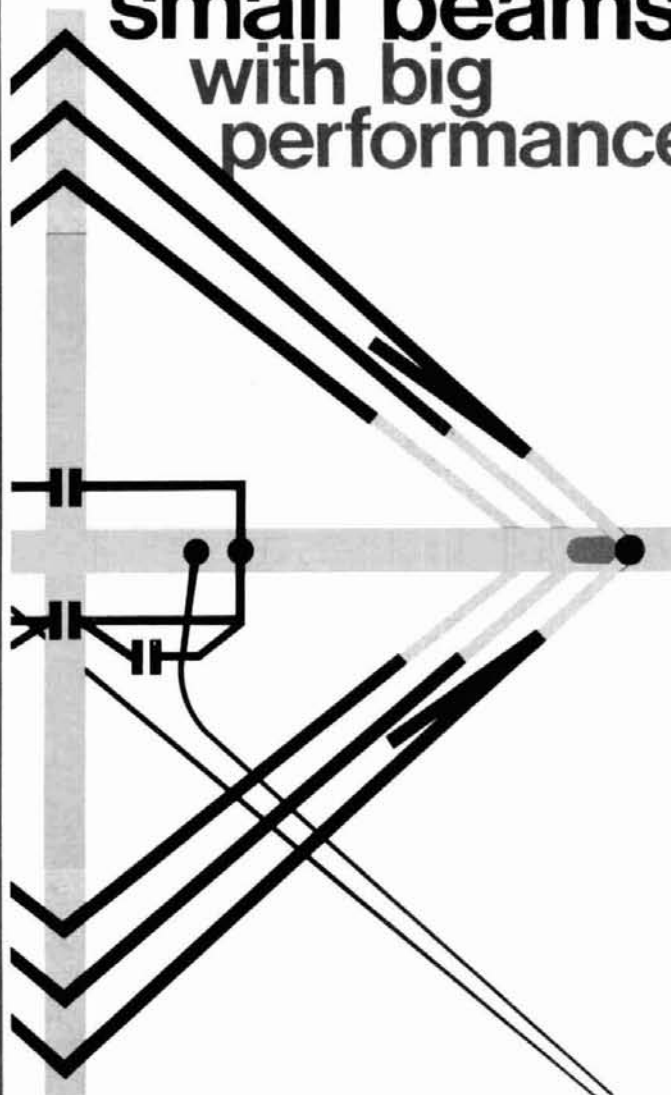

PORTABLE... MOBILE... BASE STATION



the TEMPO SYNCOM S1 DOES IT ALL AND GIVES YOU 800 CHANNELS



Top view showing controls

*Shown with accessory touch tone pad

TEMPO PRESENTS THE WORLD'S FIRST SYNTHESIZED 800 CHANNEL HAND HELD TRANSCEIVER

This amazing pocket sized radio represents the year's biggest breakthrough in 2-meter communications.

Other units that are larger, heavier and are similarly priced can offer only 6 channels. The SYNCOM'S price includes the battery pack, charger, and a telescoping antenna. But, far more important is the 800 channels offered by the S1.

The optional touch tone pad adds greatly to its convenience and the addition of a Tempo solid state amplifier adds tremendously to its power.

SPECIFICATIONS

Frequency Coverage: 144 to 148 MHz
Channel Spacing: Receive every 5 kHz, transmit Simplex or +600 kHz

Power Requirements: 9.6 VDC
Current Drain: 17 ma-standby, 500 ma-transmit

Batteries: 8 pieces ni-cad battery included

Antenna Impedance: 50 ohms
Dimensions: 40 mm x 62 mm x 165 mm (1.6" x 2.5" x 6.5")

RF Output: Better than 1.5 watts
Sensitivity: Better than .5 microvolts

Price... \$349.00 With touch tone pad... \$399.00

SUPPLIED ACCESSORIES

Telescoping whip antenna, ni-cad battery pack, charger.

OPTIONAL ACCESSORIES

Touch tone pad: \$55 • Tone burst generator: \$29.95 • CTCSS sub-audible tone control: \$29.95 • Rubber flex antenna: \$8 • Leather holster: \$16 • Cigarette lighter plug mobile charging unit: \$6 • Matching 30 watt output 13.8 VDC power amplifier (S30): \$89 • Matching 80 watt output power amplifier (S80): \$129

The Tempo line also features a fine line of extremely compact UHF and VHF pocket receivers. They're low priced, dependable, and available with CTCSS and 2-tone decoders. The Tempo FMT-2 & FMT-42 (UHF) provides excellent mobile communications and features a remote control head for hide-away mounting.

The Tempo FMH-2, FMH-5 & FMH-42 (UHF) hand held transceivers provide 6 channel capability, dependability and many worthwhile features at a low price. FCC type accepted models also available.

Please call or write for complete information. Also available from Tempo dealers throughout the U.S. and abroad.

TEMPO VHF & UHF SOLID STATE POWER AMPLIFIERS

Boost your signal... give it the range and clarity of a high powered base station. VHF (135 to 175 MHz)

Drive Power	Output	Model No.	Price
2W	130W	130A02	\$209
10W	130W	130A10	\$189
30W	130W	130A30	\$199
2W	80W	80A02	\$169
10W	80W	80A10	\$149
30W	80W	80A30	\$159
2W	50W	50A02	\$129
2W	30W	30A02	\$ 89

UHF (400 to 512 MHz) models, lower power and FCC type accepted models also available.

NEW TOLL FREE ORDER NUMBER: (800) 421-6631
For all states except California
Calif. residents please call collect on our regular numbers

11240 W. Olympic Blvd., Los Angeles, Calif. 90064 213/477-6701
931 N. Euclid, Anaheim, Calif. 92801 714/772-9200
Butler, Missouri 64730 816/679-3127

Henry Radio

Prices subject to change without notice

FROM THE COMPANY WITH A LONG LINE OF RTTY FIRSTS

RVD-1002
1st RTTY
Video Generator



1971

1972



DKB2010
1st RTTY & MORSE
Keyboard

1973

RVD-1005
Improved RTTY
Video Generator



1974



1975

ST6000
High-performance
RTTY Demodulator

DS3000 KSR Version 2
1st Microprocessor
Controlled Amateur Equipment
with Editing for Baudot & ASCII



1976

1977

1978



DS3000 KSR Version 3
1st 3-mode Amateur Send-Receive Terminal
for Baudot, ASCII, and MORSE

1979



ST5000
Low-cost, Big-performance
RTTY Demodulator

AND NOW ... DS3100 ASR

The FIRST Automatic Send-Receive Electronic Terminal for Baudot, ASCII, and MORSE

- Type and edit your message **while** receiving
- 200 line storage
- Non-volatile and programmable HERE-IS
- Internal real-time clock
- WRU answer-back
- 24 line screen
- RTTY and CW ID
- Upper and lower case ASCII



\$1995.00
Call or write
for complete
new catalog



HAL COMMUNICATIONS CORP.
Box 365
Urbana, Illinois 61801
217-367-7373

In Europe contact:
Richter & Co.; Hannover
I.E.C. Interelco; Bissone

NEW! MFJ INTRODUCES THE GRANDMASTER MEMORY KEYERS

At \$139.95 this MFJ-484 GRANDMASTER memory keyer gives you more features per dollar than any other memory keyer available — and Here's Why . . .

WEIGHT CONTROL TO PENETRATE QRM. **PULL** TO COMBINE MEMORIES A AND B FOR 1, 2, OR 3 FIFTY CHARACTER MESSAGES.

MESSAGE BUTTONS SELECT DESIRED 25 CHARACTER MESSAGES.

RESETS MEMORY IN USE TO BEGINNING.

SPEED CONTROL, 8 TO 50 WPM. **PULL** TO RECORD.



LEDs (4) SHOW WHICH MEMORY IS IN USE AND WHEN IT ENDS.

TONE CONTROL. **PULL** TO TUNE.

VOLUME CONTROL. **POWER ON-OFF**.

DELAY REPEAT CONTROL (0 TO 2 MINUTES). **PULL** FOR AUTO REPEAT.

LED INDICATES DELAY REPEAT MODE.

MEMORY SELECT: POSITIONS 1, 2, 3 ARE EACH SPLIT INTO MEMORY SECTIONS A, B, C, D (UP TO TWELVE 25 CHARACTER MESSAGES). SWITCH COMBINES A AND B. **POSITION K** GIVES YOU 100, 75, 50, OR 25 CHARACTERS BY PRESSING BUTTONS A, B, C, OR D.

NOW YOU CAN CALL CQ, SEND YOUR QTH, NAME, ETC., ALL AUTOMATICALLY.

And only MFJ offers you the MFJ-484 Grandmaster memory keyer with this much flexibility at this price.

Up to twelve 25 character messages plus a 100, 75, 50, or 25 character message (4096 bits total).

A switch combines 25 character messages for up to three 50 character messages.

To record, pull out the speed control, touch a message button and send. To playback, push in the speed control, select your message and touch the button. That's all there is to it!

You can repeat any message continuously and even leave a pause between repeats (up to 2 minutes). Example: Call CQ. Pause. Listen. If no answer, it repeats CQ again. To answer simply start sending. LED indicates Delay Repeat Mode.

Instantly insert or make changes in any playing message by simply sending. Continue by touching another button.

Memory resets to beginning with button, or by tapping paddle when playing. Touching message button restarts message.

LEDs show which 25 character memory is in use and when it ends.

Built-in memory saver. Uses 9 volt battery, no drain when power is on. Saves messages in memory when power loss occurs or when transporting keyer. Ultra compact, 8x2x6 inches.

PLUS A MFJ DELUXE FULL FEATURE KEYS. Iambic operation with squeeze key. Dot-dash insertion.

Dot-dash memories, self-completing dots and dashes, jamproof spacing, instant start (except when recording).

All controls are on front panel: speed, weight, tone, volume. Smooth linear speed

control. 8 to 50 WPM.

Weight control lets you adjust dot-dash-space ratio; makes your signal distinctive to penetrate QRM.

Tone control. Room filling volume. Built-in speaker.

Tune function keys transmitter for tuning. Ultra reliable solid state keying; grid block, cathode, solid state transmitters (-300 V, 10 ma. max., +300 V, 100 ma. max.), CMOS ICs, MOS memories. Use 110 VAC or 12 to 15 VDC. Automatically switches to external batteries when AC power is lost.

OPTIONAL SQUEEZE KEY for all memory keyers. Dot and dash paddles have fully adjustable tension and spacing for the exact "feel" you like. Heavy base with non-slip rubber feet eliminates "walking". \$29.95 plus \$2.00 for shipping and handling.



THIS MFJ-482 FEATURES FOUR 25 OR A 50 AND TWO 25 CHARACTER MESSAGES.

- Speed, volume, weight, tone controls
- Combine memory switch
- Repeat, tune functions
- Built-in memory saver

\$99⁹⁵



Similar to MFJ-484 but with 1024 bits of memory, less delay repeat, single memory operating LED. Weight and tone controls adjustable from rear panel. 6x2x6 inches. 110 VAC or 12 to 15 VDC.

THIS MFJ-481 GIVES YOU TWO 50 CHARACTER MESSAGES.

- Repeat function
- Tune function
- Built-in memory saver

\$79⁹⁵



Similar to MFJ-482 but with two 50 character messages, less weight controls. Internal tone control. Volume control is adjustable from rear panel. 5x2x6 inches. 110 VAC or 12 to 15 VDC.

For Orders Call toll-free **800-647-1800**

Order any product from MFJ and try it. If not delighted, return within 30 days for a prompt refund (less shipping). Order today. Money back if not delighted. One year unconditional guarantee. Add \$2.00 shipping/handling. For technical information, order/repair status, in Mississippi, outside continental USA, call 601-323-5869.

Order By Mail or Call TOLL FREE 800-647-1800 and Charge It On



MFJ ENTERPRISES, INC. P. O. BOX 494 MISSISSIPPI STATE, MISSISSIPPI 39762

ham radio

magazine

MARCH 1979

volume 12, number 3

T. H. Tenney, Jr., W1NLB
publisher

James R. Fisk, W1HR
editor-in-chief

editorial staff

Martin Hanft, WB1CHO
administrative editor

Charles J. Carroll, K1XX
Patricia A. Hawes, WA1WPM
Alfred Wilson, W6NIF
assistant editors

Thomas F. McMullen, Jr., W1SL
Joseph J. Schroeder, W9JUV
associate editors

Wayne T. Pierce, K3SUK
cover

publishing staff

C. Edward Buffington, WB1AMU
assistant publisher

Fred D. Moller, Jr., WA1USO
advertising manager

James H. Gray, W1XU
assistant advertising manager

James R. Wales
art director

Susan Shorrock
circulation manager

ham radio magazine
is published monthly by
Communications Technology, Inc
Greenville, New Hampshire 03048
Telephone: 603 878-1441
Address all editorial and
advertising correspondence to
Greenville, New Hampshire 03048

subscription rates

United States: one year, \$15.00
two years, \$26.00; three years, \$35.00

Canada and other countries (via Surface Mail)
one year, \$18.00; two years, \$32.00
three years, \$44.00

Europe, Japan, Africa (via Air
Forwarding Service) one year, \$25.00

All subscription orders payable in
United States funds, please

foreign subscription agents

Foreign subscription agents are
listed on page 105

Microfilm copies
are available from
University Microfilms, International
Ann Arbor, Michigan 48106
Order publication number 3076

Cassette tapes of selected articles
from ham radio are available to the
blind and physically handicapped
from Recorded Periodicals
919 Walnut Street, 8th Floor
Philadelphia, Pennsylvania 19107

Copyright 1979 by
Communications Technology, Inc
Title registered at U. S. Patent Office

Second-class postage
paid at Greenville, N.H. 03048
and at additional mailing offices
ISSN 0148-5989

Subscription inquiries and changes of
address should be directed to ham radio
magazine, Greenville, New Hampshire 03048
Please include address label from most
recent issue if possible

Postmaster send Form 3579 to ham radio
Greenville, New Hampshire 03048



contents

12 small beams

Leslie A. Moxon, G6XN

26 voltage-tuned oscillator

Norman J. Foot, WA9HUV

**32 operation characteristics
of the 555 timer**

Robert J. Marshall, WB6FOC

40 receiver digital display

Frank C. Getz, N3FG

46 1-MHz oscillator

Thomas V. Cefalo, WA1SPI

48 matching grounded-grid tubes

Ulrich L. Rohde, DJ2LR

50 the key-toggle

Donald E. Hildreth, W6NRW

56 i-f transformers

Joseph J. Carr, K4IPV

62 updating the HW-2036

Michael J. Miller, WB6TMH
Edmund B. Fitzgerald, WA6ODR

68 the dasher

Joseph H. Fenn, KH6JF

70 passive phase-shift networks

Robert B. Wilds, K6ZV

76 cabinet construction

Robert A. Thompson, W7KDM

**82 digital circuits:
propagation delay
and flip-flops**

Leonard H. Anderson

4 a second look

118 advertisers index

105 flea market

112 ham mart

88 ham notebook


6 letters

92 new products

8 presstop

118 reader service

56 weekender

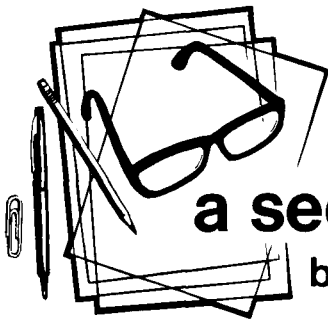

a second look

by Jim Fisk

This is the time of year when many high-school seniors are scurrying around, planning their future education, sending applications off to the college of their choice, and taking entrance exams. Seniors who are also Radio Amateurs are probably considering a career in electronics. If they're lucky, they will have a knowledgeable guidance counselor who can steer them in the right direction; if not, they'll probably pick a school with a good reputation and work from there. Sometimes this works out, and sometimes it doesn't — it depends entirely on what the student is looking for.

Electrical and electronics engineers who graduated more than ten years ago would probably not recognize the engineering curriculum now offered by their old alma mater because, in the past few years, there have been significant changes in engineering education. During the 1960s the classical engineering educational programs tended to become more and more theoretical oriented, with less emphasis on applied engineering. The backgrounds of some electrical engineering staffs changed from being primarily applied electronics to applied mathematics, and attempts to develop practical engineering programs were not all that successful. In recent years, however, some engineering colleges have restructured their curriculums for a better balance between the theoretical and the practical. On the other hand, some colleges have continued to stress the theoretical aspects of engineering science, so the prospective student is faced with a very important, but difficult, choice.

Not too long ago, the prestige of an engineering school was almost always gauged by the theoretical emphasis of its courses; each school tried to outdo the others in the theoretical sophistication of its curriculum. Unfortunately, the majority of jobs within the sphere of electronics engineering does not require such an advanced mathematical sophistication as they do a "gut" understanding of electronics. If you talk to students at a *theoretical* school, you'll find that many of them don't know how to solve a simple steady-state ac problem, although they can invert a matrix and use state-variable techniques.

The difficulty with this type of engineering education is that graduates are not adequately prepared to solve the day-to-day engineering problems they will be presented with in industry. Employers are faced with the prospect of several months of on-the-job training before the newly hired engineer becomes a fully contributing member of the staff. Obviously, a new engineer who can solve problems quickly and practically in the real world is a valuable asset.

In the 1970s several colleges introduced four-year electronic technology programs in an attempt to get back to the old practical engineering concept; the courses at these colleges emphasize electronic hardware and laboratory techniques as well as electrical theory. Although graduates of these Bachelor of Science Technology programs have been pictured as fitting into the occupational spectrum somewhere between the technician and the engineer, many professors see technology graduates as having much wider employment opportunities. In fact, technology graduates now have opportunities in many areas of electronic applications and design traditionally occupied by engineering graduates, jobs vacated because of the change in emphasis in engineering education programs.

Students who are interested in this type of engineering program should be aware that there is a wide difference in B.S. programs parading under the "Technology" banner. Some curriculums are managerially oriented, others are slanted toward applications and design, while still others are little more than two-year electronic technician training programs with added courses in the arts and humanities to fill out four years. Students who wish to enter this area should obviously choose a school carefully to be sure they get exactly what they want.

Jim Fisk, W1HR
editor-in-chief



IC-701, Your Synthesized Passport

Enter the exciting world of HF DX with ICOM's outstanding, fully synthesized **IC-701**. Globe-spanning QSO's are as easy as hook-up and tune-in. Complete installation requires only a good 50 Ohm antenna and an AC power plug-in. Your **IC-701** comes with everything else you need for beginning DX transmissions, including the matching **IC-701PS** external speaker and power supply, the fine **SM-2** base microphone, and even two built-in VFO's.

Turn on the power, and the world's at your single fingertip. The **IC-701** lets you scan all the Amateur HF bands from 160M to 10M (plus some MARS coverage above and below some of the Ham bands) with one finger. No more fooling around with two or more tuning knobs, and no complicated retuning when you QSY.

When talking on your **IC-701**, you get a 200 watt PEP input signal whose punch is significantly increased by the high quality

built-in RF speech processor. This makes your 200 watts sound like so much more that we recommend you leave the speech processor on all the time.

For adding on frequency memory and remote frequency control, the **IC-701's** synthesizer is completely compatible with ICOM's **RM2** remote computer controller: and with ICOM's optional **EX1** extension, you can operate with the **RM2** and a linear amplifier at the same time.

Nothing else matches the value and ease of the **IC-701**. Plunge into the excitement of HF DX now, and get the whole HF world with ICOM's **IC-701** LSI system.



IC-701: DXterity

HF/VHF/UHF AMATEUR AND MARINE COMMUNICATION EQUIPMENT

DISTRIBUTED BY:




ICOM

ICOM WEST, INC.
Suite 3
13256 Northrup Way
Bellevue, Wash. 98005
(206) 747-9020

ICOM EAST, INC.
Suite 307
3331 Towerwood Drive
Dallas, Texas 75234
(214) 620-2780

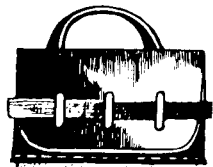ICOM CANADA
7087 Victoria Drive
Vancouver B.C. V5P 3Y9
Canada
(604) 321-1833



comments

metric dimensions

Dear HR:

The meter is a widely used unit of length abroad. It is convenient only in that fractions and multiples are decimal. As a specific unit of length it is as arbitrary as the foot; for reference, see the NBS history book *Measures for Progress*. Navigators use the international unit of distance, the nautical mile (based on the earth's equator), rather than the result of two French surveyors' efforts in measuring the distance from Paris to Marseilles.

There are times when metric measurements are useful, other times when other standards are better. Having used so many different standards for so long, I am not really partial to all-metric or all-other. For construction and items used therein it would seem advisable to state the local measurement (depending on the author's location and supply) first, then the conversion. For example, the W7DI antenna in the November issue used tubing from a U.S. supplier. It comes in standard diameters in inches. The same for plumbing pipe. One is hard pressed to make a supplier understand millimeters or centimeters. It would seem reasonable to state such dimensions in inches first with cm or mm in parentheses. If DK1AG had written the article it would seem reasonable to expect the local German dimensions first, then inches. I am referring mainly to those dimensions where specific material is widely available.

A sheet of plywood in the United States is going to be 4 by 8 feet for a long while to come. Three-quarter-inch plumbing is going to remain $\frac{3}{4}$ " for a long time — in fact, any material used in the building trades can be expected to remain in established dimensions for the next ten years — perhaps longer. Many electronic items also remain in the "English" standard. Most numerous are the ICs. They remain rooted on the 0.05-inch (1.27-mm) grid for a simple reason: The United States started it and uses millions of them every year. And many are fabricated in metric countries.

There are a host of other standards. Why the $1\frac{3}{4}$ " increment on the height of rack panels? Think of how long those have persisted. Some rack panel heights have varied, but the 19-inch (42.3-cm) width is still here. Quarter-inch (6.4-mm) shafts are common. Fasteners are described in threads per inch with roughly arbitrary diameters; both U.S. and foreign types should be differentiated. Consideration should also be given to the enormous number of United States types in use and made each year.

The scientific community remains in both camps and is not certain on a few items. There is increasing use in optics of the nanometer instead of the Angstrom, for example. Seimens has yet to replace mhos. Parsecs, kilometers (why not megameters?), and light-years seem to be interchangeable in astronomical distances. At least to NASA.

We have made the transition from tubes to transistors but tubes are still here. I believe that a double standard can continue, and should do so if certain material is in common supply in the author's country; contemporary literature should reflect that fact.

It is difficult for all to go completely metric, both for editor and author. We will continue to write on 21.6 by 27.9 cm paper using 3.94 pitch, double-spaced. I am awaiting delivery of a new IBM typewriter with a 38.1-cm carriage and dual pitch (4.72 for correspondence). If it bothers me, I'll just pour a glass of milk from the 1.89-liter carton.

Leonard H. Anderson
Sun Valley, California

Mr. Anderson's view of metrification is reasonable and well stated. The response we received to our boxed "metrics only" editorial which appeared with W7DI's article in the November issue was both immediate and loud. Based on the letters which have crossed my desk during recent weeks, ham radio will be using both metric and English dimensions in our magazine articles for the foreseeable future.

W1HR

zip-cord feedlines

Dear HR:

The article on zip-cord feedlines in the April, 1978, issue and the follow-up comments in October brought back some old memories. I first heard of lamp-cord around 1930 (twisted-pair in those days) from the Globe Wireless operators who used it for transmission line to their "noise reducing" receiving antennas. Later there were a number of articles in the Amateur magazines on how to use lamp-cord transmission lines for both receiving and transmitting dipoles; it provided a reasonable match to the feedpoint impedance. Lamp-cord may have been a little lossy, but the early forms of coax which came into use a few years later was not all that good either!

Wayne W. Cooper, AG4R
Miami Shores, Florida

Instant recall. (and with 10 or 25 watts of power)



Kenwood offers you a choice. The TR-7600 (10-watt) or TR-7625 (25-watt) with optional RM-76 Microprocessor Control Unit.

TR-7600 and TR-7625...one of them is sure to fit the needs of today's Amateur Operator who's looking for optimum versatility in a 2-meter FM transceiver. And, when either rig is combined with the RM-76, a whole new dimension unfolds in channel memory and scanning capability. Here's what you get:

TR-7600 AND TR-7625 (ONLY)

- Memory channel...with simplex or repeater (± 600 kHz transmitter offset) operation.
- Mode switch for operating simplex or for switching the transmit frequency up or down...or for switching the transmitter to the frequency you have stored in the TR-7600 or TR-7625's memory (while the receiver remains on the frequency you've selected).
- Digital frequency display (large, bright, orange LEDs).

- Dual concentric knobs for fast, easy selection of any 2-meter frequency, in 100-kHz and 10-kHz steps.
- Full 4-MHz coverage (144.000-147.995) on 2-meters; 800 channels; 5-kHz offset switch, and MHz selector switch...for desired band (144, 145, 146, or 147 MHz).
- UNLOCK indicator...an LED that indicates transceiver protection when the frequency selector switches are improperly positioned or the PLL is not locked.

TR-7600 AND TR-7625 WITH RM-76

- Store frequencies in six memories (simplex/repeater).
- Scan all memory channels.
- Automatically scan up the band in 5-kHz steps.
- Manually scan up or down in 5-kHz steps (or fast tune).
- Set lower and upper scan frequency limits.
- Clear scan (for transmitting)

- Stop scan (with HOLD button).
- Scan for busy or open channel.
- Select repeater mode (simplex, transmit frequency offset (± 600 kHz or ± 1 MHz), or one memory transmit frequency).
- Operates on 143.95 MHz simplex (MARS)
- Adaptable to all MARS frequencies.
- Display indicates frequency (even while scanning) and functions (such as auto-scan, lower scan frequency limit, upper scan limit, and error, i.e. transmitting out of band).

See the exciting TR-7600, TR-7625 and RM-76 now at any Authorized KENWOOD Dealer!



KENWOOD
...pacesetter in amateur radio

TRIO-KENWOOD COMMUNICATIONS INC.
1111 WEST WALNUT/COMPTON, CA 90220

presstop

JIM FISK, W1HR and Editor-in-Chief of ham radio and Ham Radio Horizons magazines, suffered a heart attack in late January. The following week Jim was out of intensive care, with vital signs stabilized and all indications good. He will, however, be in the hospital for two to three weeks and resting at home for another six to eight weeks after that.

NOVICE USE OF 220-225 MHz was proposed by the ARRL in a Petition for Rule Making submitted to the FCC. In its petition, the League suggests that Novices be authorized A1, A2, and F3 privileges across 220-225 MHz, with a maximum input power of 50 watts. A Novice would not be able to set up and operate a repeater or auxiliary station, although he would be able to use one.

In The Petition, the ARRL noted that the Commission had recently changed the character of the Novice license from a short-term, nonrenewable "learner's permit" to a full-term renewable license. This, they noted, reduced one of the most serious former objections to Novice phone privileges, the tendency of some Novices to operate mostly or entirely on phone until their license expires, putting them off the air — often for good.

FM In The 52.0-52.5 MHz segment of six meters was proposed in mid January by another ARRL Petition for Rule Making. This recommendation stems from a resolution to promote better use of the six-meter repeater sub-band. The resolution was passed unanimously at the board of directors July meeting.

Responding In An unusually short time, the FCC assigned RM-3314 to the 220-MHz Novice proposal and RM-3313 to the six-meter FM petition. Comments on both RMs must reach the FCC before March 1.

BROADCAST INTERESTS MAY THREATEN the U.S. Amateur Radio WARC position far more than the question of sharing 220 MHz with Maritime services. U.S. international broadcasters, not satisfied with the 865 kHz of new hf spectrum proposed for them in the Commission's carefully worked out WARC Report and Order, are now waging a behind-the-scenes battle to double that amount at the expense of other hf users. If they succeed, it will mean cuts for the other services, whose hf expansion was proposed in the U.S. position, and, in the process, it will destroy much of the carefully worked out agreement achieved by various government agencies and industry advisory groups during the past several years.

The Broadcasters Position is supported in a joint separate statement of Commissioners Washburn and Quello that's included in the WARC Report and Order. In it, the two commissioners note that the international broadcasters — specifically the International Communications Agency (Voice of America) and the Board for International Broadcasting (Radio Free Europe and Radio Liberty) — want international broadcasting to have another 800 kHz over and above the new 865 kHz already proposed for it. They also point out that the Executive Branch of the government has yet to make its final decision on the potentially explosive issue.

WILSON ELECTRONICS HAS BEEN bought by Regency. The move puts Regency back into the Amateur Radio business it left early last year, though Regency itself plans to remain in scanners and marine radio while Wilson, operating under its present management, will continue in Amateur and CB products.

FCC'S PERSONAL RADIO DIVISION was abolished as part of a sweeping reorganization of the Safety and Special Services Bureau. In the reorganization, Safety and Special Services has been arranged functionally, rather than by service, into four divisions: Policy Development, Rules, Licensing, and Compliance.

Safety And Special Services previously had three "service" divisions, Personal Radio, Aviation, and Marine; Industrial Safety; and Public Service, all of which went out of existence in the reorganization. In addition, there had also been an Industrial and Public Safety Rules Division, plus a Legal, Advisory, and Enforcement Division.

The Result Of The Change is expected to be an improvement in Safety and Special Services' overall efficiency, with much more flexibility in shifting workloads. What it will mean for the FCC licensees such as Amateurs is less clear. Improvement in such routine matters as license processing seems certain, but getting a question answered or discussing a problem might be more confusing than under the old setup.

THE CHICAGO FM CLUB has just announced its First Annual "Call for Technical Papers Competition." The winning entry will receive \$500 plus expenses (less transportation) for the best Amateur Radio oriented paper. To receive the prize, the winner must be present at Radio Expo '79 to present his paper and for the prize presentation ceremony. In addition, ham radio will consider buying and publishing the winning paper. The names of the winner and runner ups will be published in the September issue of ham radio. All entries must be received by June 1, 1979. A detailed set of rules and instructions and application forms are available from Radio Expo '79, Post Office Box 305, Maywood, Illinois 60153, or phone (312) 345-5252.

OMNI HAS IT ALL. All the advantages and capabilities, all the new conveniences and new levels of performance you need, whatever your HF operating specialty. All built-in, ready to use.

ALL SOLID-STATE. All the advantages of total solid-state from the pioneer of HF solid-state technology. Reliable, cool, stable — from receiver front-end to transmitter final.

ALL HF BANDS. From 160 through 10 meters (and all the crystals) plus convertible 10 MHz and "AUX" band positions for possible future needs.

ALL BROADBAND. Band changing without tuneup — without danger to the final amp.

ALL READOUTS. Choose OMNI-A for analog dial (1 kHz markings) or OMNI-D for six 0.43" LED digits (100 Hz readability.)

ALL VOX AND PTT FACILITIES built-in; 3 VOX controls plus PTT control at front and rear jacks for external PTT switch.

ALL SQUELCH NEEDS for tuning and monitoring are built-in.

ALL FILTERS INCLUDED: 4-position CW/SSB filter (150 Hz bandwidth with 3 selectable skirt contours) plus 8-pole Crystal filter (2.4 kHz bandwidth, 1.8 shape factor.)

ALL MODE SWITCH puts all filters to work in any mode.

ALL BREAK-IN: Instant or delayed receiver muting to fit any band condition or mobile operation.

ALL-VERSATILE OFFSET TUNING; dual ranges, ± 5 kHz range for off-frequency DX or ± 0.5 kHz range for fine tuning.

ALL-SENSITIVE RECEIVER; from $2 \mu\text{V}$ on 160 m to $0.3 \mu\text{V}$ on 10 m (10 dB S+N/N) for ideal balance between dynamic range and sensitivity.

ALL OVERLOADS HANDLED; dynamic range typically exceeds 90 dB and PIN diode switched 18 dB attenuator also included for extra overload protection.

ALL LINEAR/ANTENNA BANDSWITCHING FROM FRONT PANEL; auxiliary bandswitch terminals on back panel for external relays or circuits are controlled simultaneously by the OMNI bandswitch.

ALL INTERFACE JACKS FOR PHONE PATCH; access to speaker and microphone signals.

ALL-LEVEL ADJUSTABLE ALC; set output from low power to full, retain low distortion at desired drive to power amp.

ALL SIDETONE ADJUSTMENTS; pitch and volume.

ALL-POWERFUL, ALL-WARRANTED FINAL AMPLIFIER. 200 watts input to final. Proven design with full warranty for first year and pro-rata warranty for additional 5 years.

ALL 100% DUTY CYCLE. For RTTY, SSTV or sustained hard usage.

ALL-MODE POWER: basic 12 VDC for easy mobile use, external supplies for 117/220 VAC operation.

ALL FRONT PANEL MICROPHONE AND PHONE JACKS. Convenient.

PLUS ALL THE OTHER HANDY BUILT-INS: "Timed" 25 kHz crystal calibrator in OMNI-A with automatic 5-10 sec. "on" time for easy 2-hand dial skirt adjustment... Zero-Beat switch for placing your signal exactly on CW listening frequencies... SWR bridge switches "S" meter to read SWR each time you transmit for continuous antenna monitoring... Separate receive antenna capability... Dual speakers for greater sound at lower distortion... Plug-in circuit boards for fast, easy field service.

ALL-FUNCTIONAL STYLING. "Clamshell" aluminum case clad in textured black vinyl with complementary nonreflective warm dark metal front panel and extruded aluminum bezel and bail. Convenient controls. Complete shielding. And easier-to-use size: $5\frac{3}{4}$ "h x $4\frac{3}{4}$ "w x 14"d.

AND ALL THE OPTIONS: Model 645 Keyer, Model 243 Remote VFO, Model 248 Noise Blanker, Model 252MO AC Power Supply.

Model 545 OMNI-A \$899 Model 546 OMNI-D \$1069

Experience the all-encompassing HF world of OMNI. See your TEN-TEC dealer or write for all the details.

arma

TEN-TEC, INC.
SEVIERVILLE, TENNESSEE 37862
EXPORT: 5715 LINCOLN AVE., CHICAGO, ILL. 60648

TEN-TEC's "OMNI" FILLS ALL YOUR HF NEEDS



April 27, 28, 29, 1979

HARA ARENA AND EXHIBITION CENTER DAYTON, OHIO

- Technical Forums
 - ARRL and FCC Forums
 - GIANT Flea Market
 - New Products and Exhibits
 - Grand Banquet
 - FCC Exams
- Special Group Meetings
 - Fabulous Prizes
 - CW Proficiency Tests
 - Amateur of Year Award
 - Special Achievement Awards
 - Expanded Parking

Information Brochure Available in March.

FOR MOTEL RATES AND RESERVATIONS WRITE BOX 44, DAYTON, OH 45401
OR CALL (513) 228-0016 9 A.M.-5 P.M. EST WEEKDAYS

FOR OTHER INFORMATION CALL (513) 293-0459 — 5-10 P.M. EST

Bring Your Family and Enjoy A Great Weekend in Dayton

Sponsored by The Dayton Amateur Radio Assn., Inc., Box 44, Dayton, OH 45401

TPL 1/4 KILOWATT LINEAR AMPLIFIER

TPL proudly presents the first true power 1/4KW
SSB/AM, FM or CW solid state
2 meter linear amplifier
A remote control plug allows
you to operate with the ampli-
fier ON or OFF, or in
SSB/AM, FM or CW
from the dashboard.



The 2002 utilizes the latest state of the art engineering including micro-strip circuitry and modular construction. The three final transistors combine to produce 250W when driven by 15W or more at 13.8VDC.

POWER INPUT:

5-20W Carrier FM or CW
20W PEP maximum SSB or AM

POWER OUTPUT:

200-250W carrier FM or CW
300W PEP SSB or AM

FREQUENCY RANGE:

144 to 148 MHz*
* will operate with slight
degradation at 142 150 MHz.

HARMONIC ATTENUATION:

All Harmonics Attenuated
60 dB or Greater

CURRENT DRAIN:

FM-40 Amps @ 250W
SSB-30 Amps @ 300W PEP

DUTY CYCLE:

FM 50% @ 150W 33% @ 250W
SSB 60% @ 150W 50% @ 250W

Model 2002 \$499.00

can be ordered for repeater application
for additional information contact

TPL COMMUNICATIONS INC.

1324 W. 135TH ST., GARDENA, CA 90247 (213) 538-9814

Canada: Lenbrook Industries, Ltd., 1145 Bellamy Rd., Scarborough, Ontario M1H 1H5
Export: EMEC Inc., 2350 South 30th Avenue, Hallandale, Florida 33009

NEW VISUAL CODE READER AND ELECTRONIC KEYS



Works with any
keyer, including
squeeze keyer in
speeds from 7
WPM to 40
WPM. Both in a
single unit.
Model CR101E
\$249

from **ATRONICS**

- Display letters, numbers, and commonly used punctuation visually as Morse Code signal is received.
- Operating speed 5 to 50 WPM at selected speeds.
- All Solid State.
- Makes code learning faster and easier.
- A single connection to your receiver or transceiver speaker puts it into operation.
- Hard copy read-out of CW available with TU-102 TTY interface Module accessory.

Our popular, lowest priced CODE READER KIT

Model KCR101 \$149

Ready made CODE READER...Model CR101... \$225

BUY FACTORY DIRECT & SAVE! SEND FOR FREE LITERATURE.
USE YOUR BANKAMERICARD OR MASTER CHARGE


BOX 2946

LAGUNA HILLS, CA 92653


(714) 830-6428

Atronic

The Drake MN-2700 2kW Matching Network

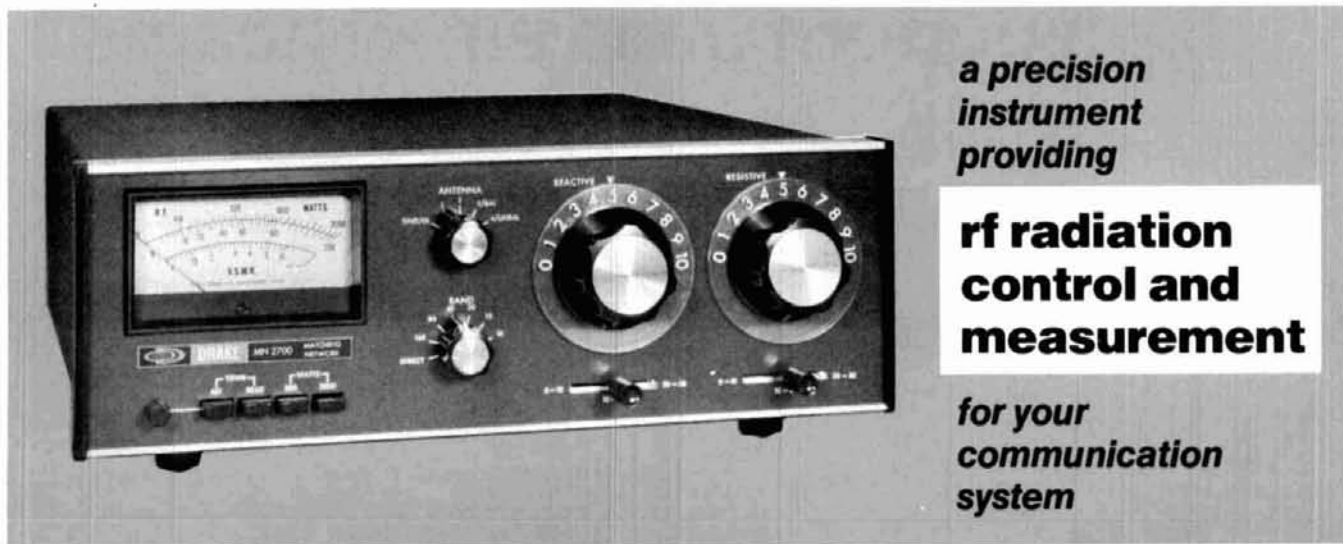

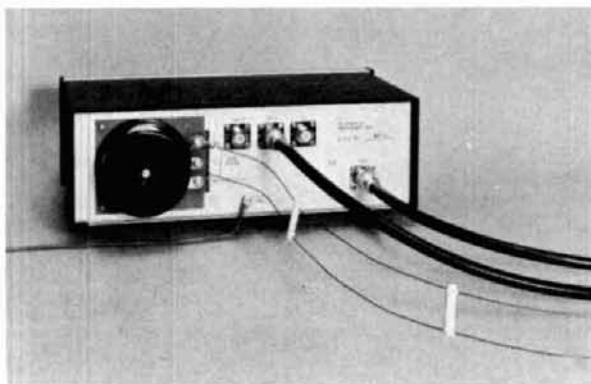The Drake MN-2700 manages rf radiation in the areas of impedance match to the antenna, rf power measurement, VSWR measurement, reduction of harmonic radiation, and antenna selection.



Drake B-1000 Balun installed on Matching Network.



The Drake MN-7. Same features as the Drake MN-2700, but rated at 250 watts. Same width and height, but only 8½" (21.6 cm) in depth, and weighs 10 lbs. (4.55 kg).

160 thru 10 Meters Frequency Coverage—With out-of-band coverage for MARS, future band expansions and other applications.

Antenna Choice—Matches antennas fed with coax, balanced line, or random wire. (For balanced line use optional Drake B-1000 Balun, which mounts on rear panel of MN-2700.)

Antenna By-pass Switching—Unique design allows unit to be switch-by-passed regardless of which antenna is in use, whether coax or wire type. No need to manually disconnect feedlines. Switch also selects various antennas.

Extra Harmonic Reduction to help fight TVI—Drake Matching Networks employ special "pi-network" low-pass filter type circuitry for maximum harmonic rejection. This feature alone makes the MN-2700 a worthwhile investment; it is a Drake exclusive.

Built-in Metering—Accurate rf wattmeter/VSWR bridge is pushbutton controlled from front panel.

Power Capability—2000 watts PEP, 1000 watts average. Continuous Duty.

Dimensions—13¾"W x 4¼"H x 13" D (33.26 x 11.5 x 33 cm), weight 11 lbs. (5 kg).

PRICES

Model 1539 Drake MN-2700	\$279.00
Model 1538 Drake MN-7	\$165.00
Model 1510 Drake B-1000	\$ 24.95

Prices and specifications subject to change without notice or obligation.

For a FREE Drake Full Line Catalog contact your favorite Drake Dealer.

R. L. DRAKE COMPANY



540 Richard St., Miamisburg, Ohio 45342
Phone: (513) 866-2421 • Telex: 288-017

high performance small beams

For antenna sizes
up to that of the
quad or three-element Yagi,
there is no
direct connection
between size and gain.
This article shows
how to design
small beams
without sacrificing gain.

In view of the urgent need for small beams, the number of them in use is remarkably small. In a recent sample of 14-MHz contacts with Australian amateurs, I found that eighty per cent of the stations worked were using quads or three-element yagis; the remainder, the ones with the biggest signals, had even larger beams, beyond the resources of most of us. There are, nevertheless, some smaller beams, such as the VK2ABQ and the capacitively loaded quad,^{1,2} which usually give a good account of themselves. Of particular importance, in the present context, is the fact that some of the most outstanding signals observed during my 50 years as a licensed amateur have originated from stations using driven arrays with only two elements!

The significance of this lies in the ease with which the performance of such beams can be calculated,³ and the fact that size comes into the calculations *only when estimating the efficiency, which remains high for element sizes and spacings down to approximately 3 meters (10 feet)*. Translating this fact into practice has brought to light some interesting prob-

lems, in particular the problem of overcoupling. That is so basic a problem that the absence of references to overcoupling in the literature suggests that no serious attempt has, until this time, been made to make beams as small as possible.

To achieve this reduction in size, elements *must* be capacitively end-loaded, without resorting to lossy inductances. This involves large concentrations of metal, which, besides tuning the elements, also couple them very tightly together. Following the normal behavior of coupled circuits, a large secondary (parasitic element) current and a small primary (driven element) current are generated, and there is virtually no beam action. Fortunately, I have found it quite easy to overcome this problem by neutralization similar to that used in push-pull amplifiers.

Another inevitable consequence, when small size is combined with high efficiency, is narrow bandwidth; this makes it essential to use separate feeders for each element so that fine tuning can be carried out in the shack. Also, this arrangement brings with it other important advantages. Since the beam is instantly reversible, less time is wasted in beam rotation, and, because less than 180 degree rotation is required, you can use low-loss, open-wire feed lines as well as simpler and cheaper methods of beam rotation. The direct relationship between the size and performance of large beams is well known, and some readers may find it difficult to accept that a small beam can be as good as a big one, particularly if those readers have experience with typical small beams using large loading inductances. The claim is, on the face of it, improbable, and one might think that it could be dismissed by invoking some general scientific principle, as in the case of *perpetual motion*. Looking for such a principle we come instead to the surprising discovery that, although the gain of *big* beams is limited, there is absolutely no limit to the *theoretical* gain from an antenna, *provided it is small enough!* You would be justified in some skepticism at this point, since it turns out that gains much in excess of 6 dB are impracticable unless the boom length is increased to half a wavelength or more. It is

By Leslie A. Moxon, G6XN, 1 Stoner Hill House, Froxfield, Petersfield, Hants, England

possible, though, to go down in size to about 3 meters square (10 feet square) without dropping below about 4.5 dB gain.

If such statements are found puzzling, it is probably because of the failure in most of the literature to distinguish between two completely different methods of beam formation, additive and subtractive. The subtractive method is typified by the W8JK array, and, as I have shown elsewhere,^{3,4} most amateur high-frequency beams can be regarded as derived from or related to this array. The radiation patterns are calculable without using any variable other than the direction. Therefore, the gain is independent of size, provided the efficiency remains high enough to ensure that most of the power is radiated. It is this constraint, allied with the need for adequate bandwidth, which in practice limits the gain of subtractive beams to about 6 dB.

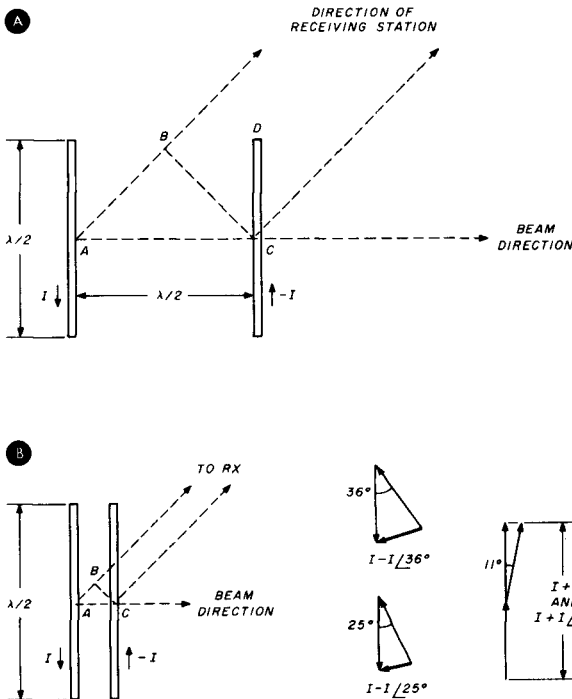


fig. 1. In (A), the elements are fed 180 degrees out of phase so that the fields add in phase along the line at right angles to the elements. A receiver located 45 degrees off the main beam sees a phase difference corresponding to AC-AB, i.e., 54 degrees, causing a drop of 4 dB in signal level in addition to the 3 dB which would be expected for a single element. Thus, the use of two elements has produced a narrower beam by virtue of the wide spacing. For subtractive gain, as shown in (B), the elements are closely spaced. Radiation would be cancelled except for a small phase shift of which the maximum value corresponds to the distance AC, or 36 degrees for a spacing of $\lambda/10$. At 45 degrees to the beam, the phase shift is reduced by the ratio of AB to AC (11 degrees), which translates into a 3-dB drop in signal level. If the fields are additive in the wanted direction, the 11-degree shift is of no consequence and the radiation pattern becomes that of a single dipole.

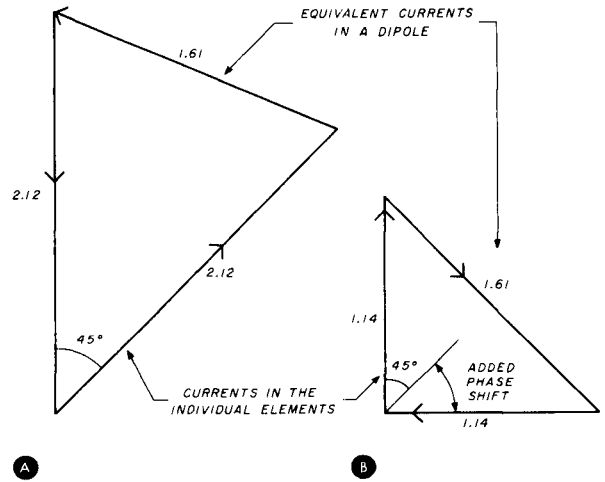


fig. 2. Method for estimating gain from the radiation resistance. Diagram (A), which is drawn to scale, shows how the W8JK element currents of 2.12 amps "add" to give the equivalent of 1.61 amps in a single element. The currents are correct for a radiated power of 72 watts. This would produce a current of 1 amp in a dipole, so that the voltage gain is 1.61, i.e. 4.2 dB. (B) shows how if one element is given a phase lead equal to the spacing, only about half as much current is needed to produce the same field strength. In each case, the current is obtained from $I = \sqrt{P/R}$.

The following discussion is intended to provide further insight into the problems of designing small beams, so that you can make your own choice from the available options and then design the "best-possible" beams for the space and facilities you have available. Practical details and some performance data are given for a number of designs, but these are intended as guidelines and not as blueprints. Although the feasibility of the 3 meter square (ten foot square) design has been proved, my own preference, given the space, is a 5.2 meter square (17 foot square) 3-element design, which, besides providing slightly more gain and greater bandwidth, lends itself to a particularly light form of construction and easier methods of achieving multiband operation.

It is a strange paradox that the main advantages of increased size relate to operation at the higher frequencies, to the extent that considerable extra gain can be obtained at 28 MHz by using full-size, 14-MHz elements. For no reason that I can discover, this advantage is usually thrown away by using traps or nesting to "cut the elements down to size" at the higher frequencies.

gain variation vs antenna size

Gain results from concentrating the radiation in one particular direction at the expense of other directions. This can be achieved by arranging more-effective addition or, as with the W8JK, less-

effective cancellation of radiation for the wanted direction. Addition requires wide spacing, as in **fig. 1A**, where the elements are arranged so that their fields add in phase for the wanted direction. Viewed at an angle of 45 degrees to the line of fire, the elements are closer together by 0.29 wavelength, which translates into a phase shift of 104 degrees and a corresponding drop of 4 dB in signal level. This drop of course, is in addition to the $\cos \theta$, or "angle to the wire" effect, which applies equally to beams and dipoles and amounts to -3 dB at 45 degrees. But for the wide separation of the elements, there would be no phase shift, no narrowing of the radiation pattern, and hence no gain.

On the other hand, given an array of n elements sufficiently far apart for mutual interaction to be ignored, we can provide each $1/n$ of the power. Since the voltages at the receiver add in phase, there is a power gain equal to the number of elements. Because the antennas have to be separated by at least $\lambda/2$, it turns out, not surprisingly, that gain is proportional to size. During reception, such an antenna collects most of the energy contained in the volume of space which it occupies, thus giving rise to the concept of aperture, for which it is sometimes claimed "there is no substitute." It is perhaps difficult to conceive that a tiny beam can collect as much energy as a big one, but the explanation lies in the high Q of the smaller antenna. Just as tuned circuits couple together more tightly when their Q is increased, so reduction in the radiation resistance is accompanied by "tighter coupling" of the antenna into the surrounding space.

To understand the mechanism of small beams, the W&JK system shown in **fig. 1B** is the easiest starting point. Radiation would be completely cancelled in all directions except for that caused by the phase shift, which results from the elements not being exactly the same distance from the receiver. Field strength is proportional to the apparent separation AB , which, like the radiation from a single element, varies as $\cos \theta$. In simpler language, the field strength, at a given distance and direction, is proportional to the apparent length multiplied by the apparent separation of the elements. The separation factor applies equally in a plane at right angles to the diagram, so that the radiation pattern of a horizontal W&JK array is given by $\cos^2 \theta$ in the horizontal and $\cos \theta$ in the vertical plane. For a single horizontal wire, the pattern is $\cos \theta$ in the horizontal plane and an omni-directional pattern in the vertical plane. The important point to note is that none of these patterns contain any reference to the dimensions, though we are of course assuming them to be small. In fact, the conclusion that gain is independent of size turns out to be accurate within about 0.5 dB for spacing up to $\lambda/4$ and element

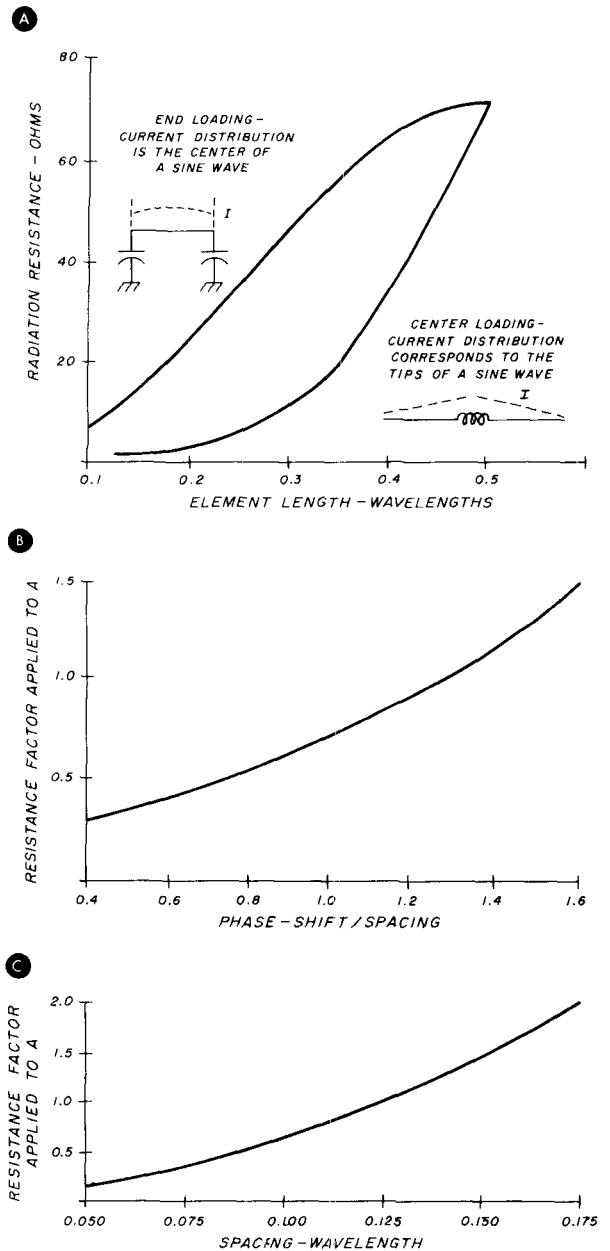


fig. 3. Graphs for determining the radiation resistance of short elements. (A) shows the variation of radiation resistance with both end and center loading. The multiplying factor [see (B)] is used to give the sum of the radiation resistance for a pair of elements with $\lambda/8$ spacing. For miniature beams, such as those shown in **figs. 9** and **11**, this approximates to the impedance seen by the feeder going to the front element. The value for spacing is converted to the same angular units as the phase shift, which is relative to the condition 180 degrees out of phase. The third chart, (C), is an additional factor which is used if the spacing is other than $\lambda/8$.

lengths up to just over $\lambda/2$. Up to these sizes, each element behaves in the same way, *i.e.*, as a "point source" of energy. It is only when an element is very large that appreciable extra gain, or directivity, can

be expected, as for example when a 14-MHz element is used as two half-waves in phase on 28 MHz. It should be obvious from inspection that quad loops, even full-sized ones, do not meet this condition.

To prove the point, there is no harm in treating the loops as a pair of stacked dipoles. Various handbooks provide data indicating that the stacking gain for $\lambda/4$ spacing is only 1 dB. However, some of the 1 dB is lost by bending over the ends, since a half-wave dipole has only a small gain (up to 0.4 dB) when compared with shorter dipoles; a further small amount is lost due to radiation off the ends. Even more is lost when parasitic elements are added, since the stacked dipoles then become stacked yagis, and, according to the usual rules, the higher the gain of individual antennas the further apart they have to be placed in order to achieve an appreciable stacking gain.

It is unfortunate that many wild claims have been made for the quad, some of them involving professional journals and computer studies. It needs to be stressed that measurements are very difficult and computers need to be asked the right questions. The habit of accepting figures without checking them against ordinary common sense is not confined to the Novice! In fact, as I have found, better low-angle gain is obtained by omitting the lower halves of quad loops and using the upper halves as inverted V or U elements. This increases the mean height by 2.4 meters (8 feet) at 14 MHz; low-angle gain for a flat, unobstructed site being proportional to antenna height, this more than offsets any slight loss of free-space gain for heights up to about 21 meters (70 feet)!

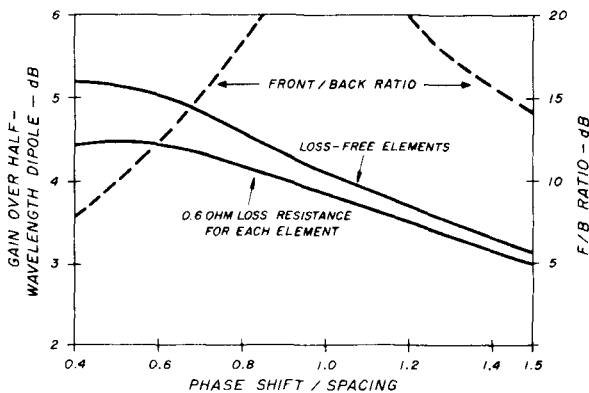


fig. 4. Gain and front-to-back ratio for the two elements, with and without losses. Loss resistance per unit of conductor length is inversely proportional to diameter and directly proportional to the square root of the frequency. The figure of 0.6 ohm is based on a half-wavelength of no. 12 AWG (2.1-mm) wire having a sinusoidal current distribution at 14 MHz. The element currents are assumed to be equal. The upper gain curve is for loss-free elements, while the lower is for 3.7-meter (12-foot) elements spaced at 2.4 meters (8 feet).

The real advantage of the quad is the large amount of extra gain (3-4 dB) obtainable by using the 14-MHz elements at 28 MHz with suitable resonators so that they become a "Bi-Square," but this is rarely exploited. Another frequently made claim, that the quad provides better DX signals by "lowering the angle of radiation," is also without foundation; the lobes of practical antennas are too broad to discriminate between direct and ground reflected waves which must always interact in the same way, resulting in a loss at low angles unless the antenna is very high or the ground sloping. To obtain the effective gain at a low angle of radiation, the free-space gain is multiplied by the ground reflection factor, which, for horizontal antennas, depends only on antenna heights and radiation angle, being the same for a quad, yagi, dipole, small rhombic, or even a minibeam!

The 4-dB gain of the W8JK can be estimated very roughly from the 3-dB widths of the radiation patterns discussed earlier, or, more accurately, from mutual-impedance data. For $\lambda/2$ dipoles spaced at $\lambda/8$, mutual impedance is 64 ohms, which has to be subtracted from the self-resistance of 72 ohms so that for each element the radiation resistance is 8 ohms. If the power available is 72 watts, you would have a current of 1 ampere in an ordinary dipole, or 2.12 amps in each of the W8JK dipoles. The phase difference due to spacing is 45 degrees, and, by "completing the triangle" as in fig. 2, you'll see that the distant field is the same as that which would result from 1.61 amps in the dipole, *i.e.*, there is a voltage gain of 1.61/1 or 4.2 dB.

Now, if the phase of the current in one element is advanced by an amount corresponding to the spacing, the total phase shift becomes zero for one direction and is doubled for the other direction. The resultant unidirectional (cardioid) pattern would require only about half the current to produce a given field strength. It happens (by coincidence) that the gain is unchanged, so that the effective radiation resistance has been multiplied by about four, proving that the beam can be made a lot smaller with the same results. Fig. 3, adapted from references 3-6, shows how radiation resistance varies with element length, spacing, and phase angle, from which it can be seen that *provided you shorten the dipoles by sacrificing the ends and not the middle*, the length can be reduced to 37 per cent of a half-wavelength before the radiation resistance drops to its W8JK value, giving a length of only 37 meters (12 feet) at 14 MHz. This reduction in size could be carried out by taking the W8JK beam and folding its ends to fit the available space. Whether or not the example can be improved upon, it does demonstrate that *if the W8JK beam works properly you could expect to be*

equally successful at 14 MHz with a 3.7×2.4 meter (12×8 foot) miniature beam which has been adjusted to give a large front/back ratio.


Thus, changing the size does not alter the gain, but, obviously, if the length or spacing is halved, the current must be doubled to maintain a constant signal, so that the radiation resistance has been divided by four. In the same way, you could alter the shape to just under 3 meters square (10 foot square) without affecting matters in any way, save that the diameter of turning circle is slightly decreased and it becomes easier to handle the ends.

Whatever shape is selected, radiation resistance may be obtained by multiplying the resistances plotted in **fig. 3A** by the factors obtained from **figs. 3B** and **3C**. This is not quite the full story, since, as demonstrated by **fig. 3** and **4**, an extra dB of gain results from using an intermediate value of phase shift. However, this halves the radiation resistance and doubles any power loss. From the lower gain curves in **fig. 4**, it can be deduced that for a 3-meter-square (10-foot-square) 14-MHz beam, using no. 12 AWG (2.1-mm) wire elements with bent ends, a net gain of 4.5 dB should be obtained after allowing for resistance losses. There may be a slight additional loss due to the "short dipole" effect mentioned, but this is caused by a small difference in the amount of endwise radiation and is much less in the case of a beam.

To put this into perspective, the maximum gain theoretically possible for a three-element parasitic array on a quarter-wavelength boom is 7.5 dB, but in this case, the radiation resistance is only 4 ohms (even less than that of the small beam), and the maximum gain normally found in practice⁷ is less than 6 dB. Theory goes on to predict a possible gain equal to the square of the number of elements,³ but before getting far along this road you're faced with huge currents and voltages, infinitesimal radiation resistances, and microscopic tolerances to the extent that the 6-dB figure is unlikely to be exceeded in practical rotary beams for 14 MHz without increasing the boom length to at least $\lambda/2$, which is sufficient to provide some "additive" gain. Reducing the size below 3 meters square (10 feet square) leads to a similar rapid increase of practical difficulties. And, as I shall point out later, there are substantial advantages, particularly for multiband operation, in an increase to about 5.2 meters square (17 feet square).

Limitations on the reductions possible in antenna size result from the following:

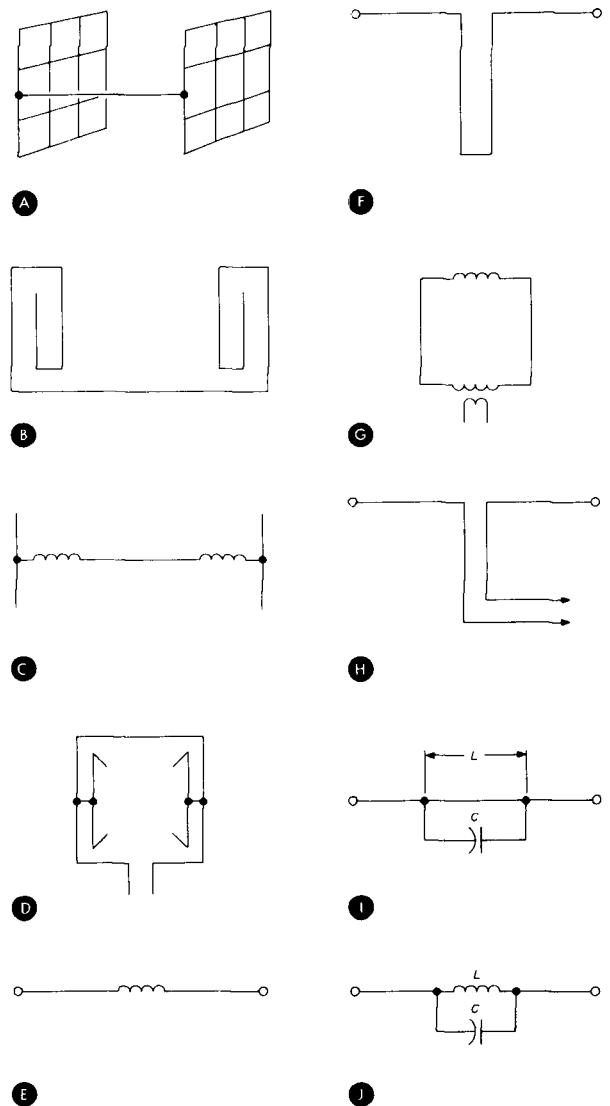1. Drop in efficiency, *i.e.*, the radiation resistance becomes comparable with the losses. This is basic and imposes a well-defined, practical limit.



- A Capacitance plates consisting of wire grids
- B Half-wavelength elements with folded ends. The length must be increased slightly to maintain resonance.
- C Small capacitance hats — the effective capacitance is enhanced by near resonance with the inductors
- D A loop with capacitance hats. This is equivalent to a stacked pair of B-type elements with their ends in contact.
- E Center loading with an inductor
- F A half-wavelength element with a folded center. This is similar to E with a stub instead of the coil. However, the R values from **fig. 3A** are transformed by the stub to give an even lower value at the closed end of the stub.
- G Loop equivalent to E
- H Resonant feeders
- I Version of a two-band element as used by DL1FK. The capacitor tunes the inductance of the center of the radiator to increase its effective value at the lower frequency. Series resonance of the capacitor with its connections shortens the electrical length for the higher frequency.
- J Lumped circuit equivalent of I as used in one form of the G4ZU minibeam.

fig. 5. This figure shows ten different methods for loading short elements. The merits of each type are discussed in the text.

2. Narrow bandwidth — the acceptable lower limit depends on the skill of the designer and the skill plus patience of the operator.

Short elements have to be loaded to bring them to resonance. The aim must be to keep the radiation resistance high, which requires end loading, and the loss resistance low, which rules out the use of lossy devices such as coils or long resonant feeders. Fig. 5 shows ten methods that have been used, with only 5A through 5D meeting the radiation resistance requirement. The others tend to be more convenient, but use the triangular tips instead of the center of a sine-wave current distribution, thus halving the average current and dividing the radiation resistance by four, besides requiring an inductive and therefore relatively lossy loading device in the center. Of these methods, 5F is open to least objection, since stubs have less resistance than coils; 5H is particularly bad, since it multiplies the losses of 5F by the total number of half-wavelength in the resonant system. Methods 5I and 5J are used for multibanding,⁸ which necessarily adds to the losses because of circulating currents in the resonators. Methods 5E to 5H are therefore applicable only for very modest reductions in antenna size.

Of the remainder, 5C makes use of small end-loading capacitances which have their effective values greatly inflated by near resonance with the inductors. In one typical design, the total inductance is

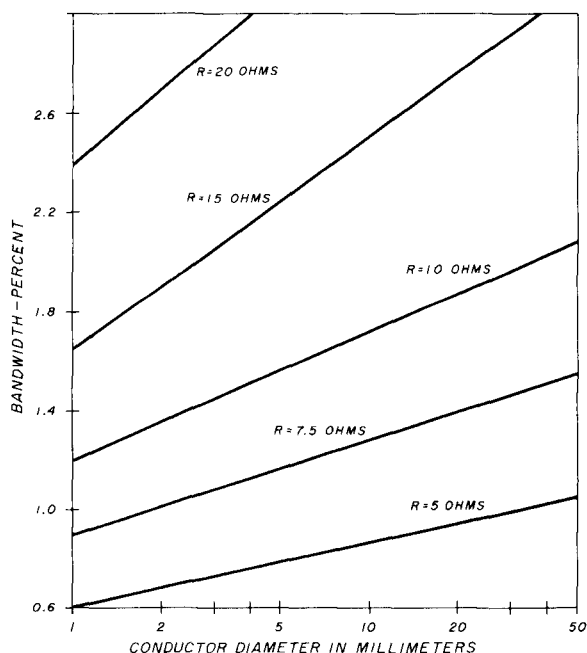


fig. 6. Bandwidth of folded $\lambda/2$ wires at 14 MHz for different values of radiation resistance, plus loss resistance. The curves are calculated for an SWR of 2:1 at the band edges, neglecting any change in Z_a caused by folding. For a coupled pair of elements, the bandwidth for a given R is increased slightly.

about $14 \mu\text{H}$, so that for a Q of 200 the loss resistance would be 6 ohms and more or less comparable with the radiation resistance, the element lengths being 3.7 to 4.3 meters (12 to 14 feet). Fig. 5A is ideal insofar as there is negligible loss in the capacitance, but it is difficult to achieve enough loading, so that some inductance on the lines of 5C is likely to be required; in this case, however, it could take the form of short stubs and the losses would be minimal. Arrangement 5B, consisting of a half-wavelength dipole with its ends bent over, is very similar, but simpler and equally efficient. The bent ends are not, of course, pure capacitances and there are losses, but, as has been seen, this method allows high efficiency to be maintained down to very small beam sizes. Efficiency can be estimated with the help of fig. 4.

Another efficient type of small element is the capacitively loaded loop shown in fig. 5D. Loops with 3.2-meter (10.5-foot) sides have been used by G3YDX for a 14-MHz, two-element beam,² and a design patented by G3IMX achieves two-band operation by using traps to remove the loading at the higher frequencies. For a single 3.7-meter (12 foot) loop, the radiation resistance is 75 ohms. About 20 ohms could be expected for a 1.8-meter (6-foot) loop, the loss resistance (referred to the feedpoint) probably being about 2 ohms. My own attempt to compress a 14-MHz quad into a 1.8-meter (6-foot) cube was unsuccessful, but I still think it might be achieved with rigid, all-metal construction and inductive loading stubs, plus sufficient ingenuity. The problem is to dispose of enough loading in the space available. In this case, neutralization will certainly be required as the lower physical limit is approached. Neutralization will not be required with 3-meter (10-foot) loops, as sufficient loading can be achieved within the plane of the loops without bringing ends into proximity.

It is important in all cases to arrange the loading so that wires carrying appreciable current are not doubled back in a direction parallel to the driven element, in which case they subtract from the wanted radiation, bringing the radiation resistance "down with a bump!" This constitutes one of the main problems of construction.

bandwidth

The bandwidth of a dipole may be roughly estimated from the radiation resistance (R) and the characteristic impedance (Z), which depends on the ratio of length to diameter. Each per cent of detuning produces a reactance of $0.015 \cdot Z$ ohms; and the 3-dB bandwidth points (corresponding to an SWR of 2:1) may be found by equating this to R . Bandwidths are plotted in fig. 6 for 14-MHz dipoles of various wire diameters. The figures should be valid, as an approxi-

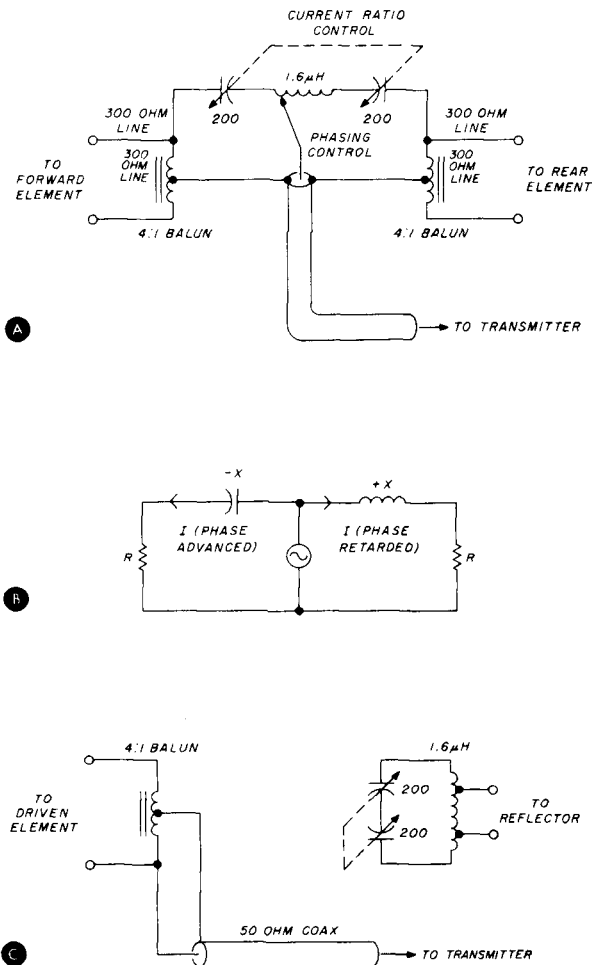


fig. 7. The top illustration shows a practical arrangement for a 14-MHz phasing control. The beam reversing switch, though not shown, interchanges the feeders. This circuit may be usable to 28 MHz, but the inductance should be reduced to about 0.8 μH ; some experimentation with values may be needed. The principle of operation is demonstrated by (B); as shown the load currents are equal and the ratio of X/R determines the phase shift. If, as is more usual, the loads are unequal, current equality may be achieved by adjustment of the reactances provided in (A). The components of (A) can also be rearranged as a tuner for a parasitic type of beam [see (C)].

mation, even when the dipoles are folded as in figs. 5B or 5F. When two elements are assembled to form a beam, the bandwidth is reduced because of the drop in R , though, for a given value of R it is increased and could be almost doubled by virtue of the "coupled circuit effect."

It is important to distinguish between three kinds of bandwidth:

1. The pattern bandwidth — the bandwidth over which the radiation pattern and gain are satisfactory
2. The bandwidth for satisfactory SWR
3. The bandwidth over which the antenna is usable

subject to adjustments that can be carried out without leaving the shack.

To illustrate, one element of the first version of my small beam had an intrinsic bandwidth (as calculated) of about 450 kHz. The completed minibeam, using a parasitic reflector, had a useful bandwidth of only about 200 kHz; at one edge the front/back ratio had dropped below 8 dB and at the other edge the gain had dropped by 1 dB. In wet weather, due to an inadequately treated bamboo spider, the tuning shifted 200 kHz low, outside the desired range. In contrast, with the second version the useful bandwidth was only 130 kHz. However, it was desirable to keep within about 20 kHz of the tune-up frequency. But, by using separate feeders to each element, the beam was tunable to any frequency in the 14-MHz band either as a driven array or a driven element plus reflector. So, for practical purposes, despite the smaller intrinsic bandwidth, the useful bandwidth was greater.

With the parasitic reflector, the phase-shift is related to the ratio of reactance to the total resistance, R , of the reflector, and, in addition, must meet the requirement for reasonable gain in accordance with fig. 4. Although the actual relationship is much more complex, a rough idea of the bandwidth for useful performance can be obtained as follows. Referring to fig. 4, we might decide that performance is acceptable for values of phase shift from one half up to one and one half times the spacing, which means from 25 to 75 degrees in the case of a spacing of 3 meters (10 feet). At 25 degrees, the front-to-back ratio is down to 10 dB and the radiation resistance (fig. 3) is getting very low, while at 75 degrees the gain is down to 3 dB. Phase shift is partly due to X , and partly to the mutual reactance between the elements, which, in this case, takes care (more or less) of the required mean value of 50 degrees. The maximum allowable shift of ± 25 degrees occurs when X/R is roughly equal to this angle (measured in radians), i.e., $X = R/2$. From fig. 3, $R = 15$ ohms and for $Z = 1000$ ohms (a typical value) a reactance $R/2$ results from ± 0.5 per cent detuning, i.e., the bandwidth is 1 per cent or 140 kHz, in good agreement with the observed figure of 175 kHz (i.e., 14.300-14.125) from fig. 10.

The first version of the small beam was 3.7 meters square (12 feet square), which would be expected to double the radiation resistance and bandwidth; in this case, too, the calculations are in line with the observed performance and there was good agreement in regard to the observed bandwidth for a 20-dB front-to-back ratio. From fig. 4, the theoretical 20 dB points correspond to a change of ± 18 per cent in phase angle, or 36 per cent in reactance, i.e., 6 ohms, which translates into a bandwidth of 0.4 per

cent, or 56 kHz in comparison with a measured figure of 55 kHz; however, this must be regarded as coincidental, since both figures are very rough.

phasing

It is essential for the currents in the elements to be equal (or nearly so), as well as correctly phased. With parasitic arrays there is usually no independent control of these quantities, though equality tends to be achieved in the case of quad reflectors. With $\lambda/2$ dipole elements the inequality, though it degrades the front/back ratio, does not upset gain to a serious extent. In contrast, the small-beam elements behave as overcoupled circuits resulting in large ratios of reflector to driven element currents.

Neutralization allows the coupling to be reduced to any desired extent, so that it can be adjusted in conjunction with the tuning of the reflector to obtain equal currents with any required value of phase shift. In this way, very deep nulls can be obtained in one or more back directions without resorting to driving both elements. This is subject to a number of assumptions: For example, the neutralization, which has to be adjusted at ground level, must remain "right" when the antenna is raised to its full height, at all frequencies, and in all types of weather.

A driven arrangement with provision for adjustment of phases and amplitudes is obviously more versatile and allows compensation for considerable errors in tuning or neutralization, but the methods usually employed for driven arrays are based on false assumptions that are particularly disastrous in the case of small beams with reactively coupled elements. It is usually assumed, for example, that $\lambda/8$ of line provides a 45 degree phase shift — which is true if the lines are perfectly matched. But often there is little attempt at matching, which will, in any case, be upset if the phasing is adjusted. A further difficulty is that for the elements to have equal impedances the mutual coupling between them must be a pure resistance, a condition that applies in practice only for straight $\lambda/2$ elements spaced just over $\lambda/8$. This, incidentally, is an important special case since it is then easy to calculate gain and radiation resistance.^{3,5} Having established that gain is independent of size, the numbers obtained can be applied to other sizes on the basis of **fig. 3**.

If there is capacitive reactance coupling, as happens with wider spacing or miniature elements, the radiation resistance of the reflector may be zero or even negative, in which case its feeder returns more power to the transmitter than it receives! Matching is clearly impossible under these conditions. The method I use, which can take various forms,^{6,9} is based on resonance; in **fig. 7**, the two feeders are connected through a series-resonant circuit and the complete system, minus the connection to the

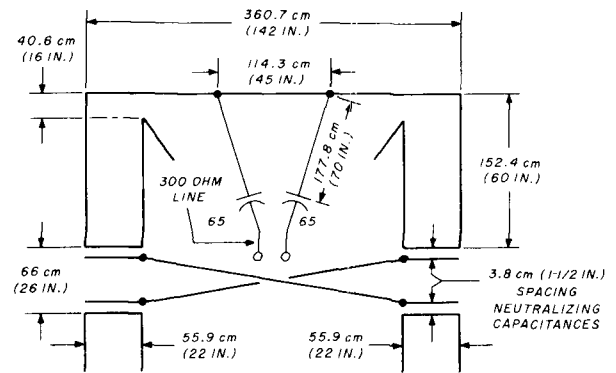


fig. 8. Original version of the small beam showing one element plus the neutralizing wires. The elements are identical, with a wire length of 11.4 meters (37.3 feet). For initial adjustment, one element without the feeder may be tuned as a parasitic reflector, in which case the length is about 10.9 meters (35 feet, 10 inches). The elements and neutralizing capacitors are made from no. 14 AWG (1.6-mm) wire, but the delta match and neutralizing cross connections can be made of a lighter gauge wire. The spider projects beyond the elements, which are suspended by lengths of polyethylene cord.

transmitter, is made resonant. Phase-shift is obtained by off-center connection of the feedline from the transmitter. If necessary, element currents can be made the same by detuning the series circuit so that one element or the other is brought closer to resonance. Matching should be carried out to reduce the SWR in the line to the forward element, a high SWR in the reflector line being of no importance as there is very little power transferred along it. Cross-over of the elements as with the W8JK, though normally essential with full-sized elements, is sometimes not required when coupling to highly reactive elements. Using this arrangement, it has been possible to work with different or even unequal lengths of feedline, and to compensate for quite large errors of adjustment, though never to the extent of being able to use it as a substitute for neutralizing. The beam can be reversed either by interchange of feeders or moving the coil tap. It is possible, in principle, to null out from any given direction "off the back." A curious feature of reactive coupling is that, despite the remarkable effect it has on relative impedances, the *sum* of the two radiation resistances is not affected; for **fig. 3** to have universal application, it was therefore necessary to plot the sum and not the individual resistances. The sum is in any case a more useful figure for the present purpose since it is into this value that the feeder for the front element has to be matched (so that the antenna impedance is "repeated" in the shack). It is often possible, particularly if the feeder length is a whole number of half wavelengths, to use the phasing circuit with very little modification as a remote tuner for driven element and reflector operation (see **fig. 7**); this reduces the

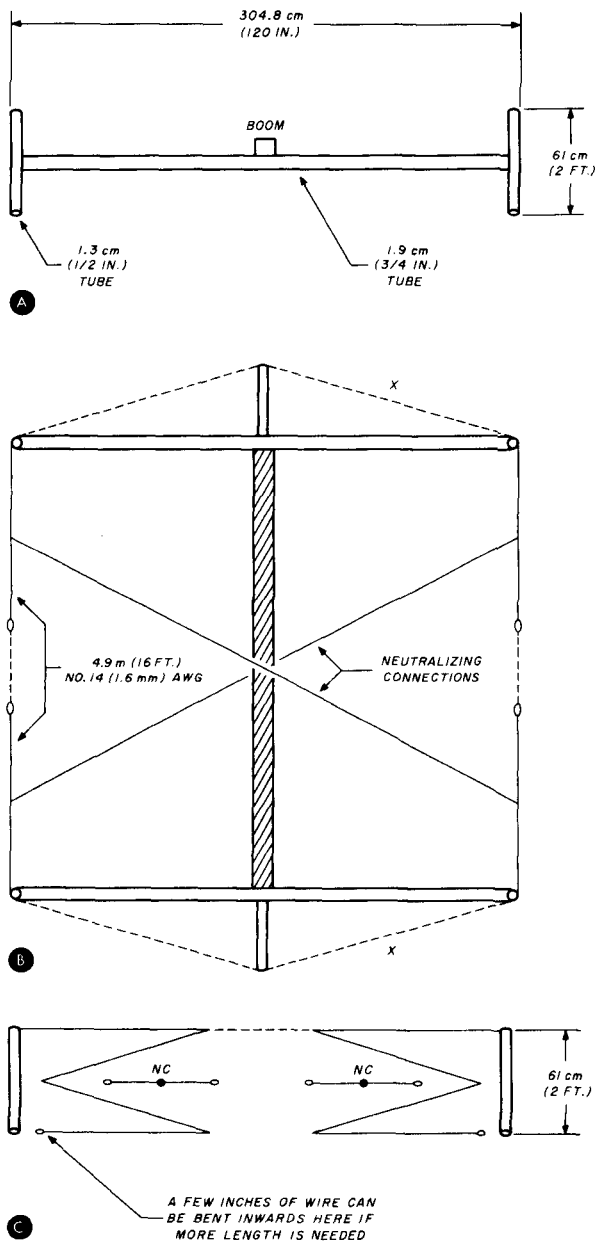


fig. 9. Construction details for a 3-meter-square (10-foot-square) beam for 14 MHz. The front, plan, and side views are shown in (A), (B), and (C), respectively. In (B), the bow-string-type arrangement is used to counter the pull of the loading wires and to allow the use of lightweight elements. Each neutralizing capacitor, as shown in (C), is approximately 0.6 meter (1.9 feet) long. If greater wire length is needed, additional wire can be added as indicated in (C).

number of knobs and has proved more convenient in practice, provided the neutralization is reasonably accurate. It has been found that, although small differences can be compensated, care in making the elements identical pays big dividends in convenience of operation, since it allows beam reversal with no change of tuning or matching. One can tune for a minimum on either the wanted station or an interfer-

ing signal from the back direction, using the reversing switch as required.

practical designs

Several construction methods have been used.¹⁰ Fig. 8 gives the dimensions of my first small beam, the elements being suspended by thin polyethylene cords from a six-armed spider made from bamboo garden canes which extended just beyond the wire. The two central arms were required to counter the inward pull of the folded sections. One element was driven using 300-ohm line with a delta match having series capacitors to tune out the reactance. I tried to tune the other for a null in the back direction, but this was barely perceptible. Current in the reflector was found to be higher than that in the driven element, so the neutralizing capacitance (formed by parallel wires) was increased by reducing the spacing, retuning the reflector, and adjusting the driven element for lowest SWR at each step. Eventually current equality and a good front-to-back ratio was achieved. At a height of 16.8 meters (55 feet) the antenna was compared with a two-element quad at 13.7 meters (45 feet) and appeared to be at least as good.

Mention has already been made of bandwidth and wet weather problems. It quickly became obvious that two feeders would have to be used. To save cost, I used the transparent, plastic-type of 300-ohm line; lacking previous experience with it, I was unprepared for the rapid deterioration, which caused a lot of confusion. Later, good results were briefly obtained using a pair of 600-lines.

However, mechanical problems arose and the next step was a new design using metal construction with 3-meter (10-foot) elements made from 19-mm (0.75-inch) tubing. Short vertical rods at the ends of the elements (see fig. 9) act mainly as brackets for supporting wire zigzags. I found that, because of limited space, almost as much wire was needed as in the original design so that the use of tubing provided no electrical advantage apart from getting rid of "wet weather" effects caused by the bamboo. To avoid the need for heavy-gauge elements, their ends were guyed back with polyethylene cord to the boom extensions, thus countering the inward pull of the loading wires. Two open-wire feedlines were used.

Some typical measured performance figures are shown in fig. 10. On-the-air performance was down compared with earlier results, on average about 2 dB; this might be due to the smaller size (radiation resistance being halved) in addition to closer proximity to tree branches, the mast being slightly shorter due to breakage and splicing! Another uncertainty arose from loss of the quad as a standard of reference; the 3-element beam, though equal to the quad

in performance, was so placed that it tended to screen the smaller beam. I could not be certain that rotation to an end-on position was removing all this effect. From this, I felt that the best test for the small beam would be as a direct replacement for the larger one. Now, however, I used a new multiband version, the disposition and loading of the elements for 14 MHz being as shown in **fig. 11**.

For such tests my yardstick for many years has been another station using a TH6 at 11.6 meters (38 feet) and with a slightly better location for VK (long path) over which most of the tests were made. With the small beam at 14.6 meters (48 feet), I was able, for the first time on record, to equal the signals of the other station on three consecutive days. Normally with a quad at 12.1 meters (40 feet) I should be down in most cases by 1/2 to 1 S-unit. Added to the initial results of the first small beams, this would provide substance for a claim that small beams, given a few feet of extra height, are actually better than big ones! Unfortunately, such a claim could not be supported by theory or common sense, but I was confirmed in my belief that the small beam can be made fully competitive.

Any type of feeder can be used, but, because of its lightness, good-quality 300-ohm line can be recommended as an alternative to open-wire line. I have also used 50- and 75-ohm coax with 4:1 baluns and delta matches identical to the one shown in **fig. 8**.

three-element beam

A starting point for this development was the original VK2ABQ design¹ in which a quad loop lying on its side is converted into a two-element beam by insulators in the sides. The rather wide spacing ($\lambda/4$) unfortunately means that performance is slight-

ly worse than the best that can be achieved with two elements, and it seemed logical to me to put a third element in the middle. No increase in the diameter of the turning circle dictated a maximum element length of 7.3 meters (24 feet). With some end loading by vertical rods and the use of linear resonators, I was able to design a triband element (see **fig. 12**) having almost as much radiation resistance as a full half-wavelength at 14 MHz, higher radiation resistance than a normal element at 21 and 28 MHz, a small amount of extra gain at 28 MHz, and no trap losses.

Tubing was used for this element, but retention of bent wire elements for directors and reflectors made engineering sense, since these elements have less current flowing in them and a lot of cost and weight could be saved. The next step was to eliminate the quad spider by using the driven element as one diagonal of a square and making it support the ends of the parasitic elements which were now V shaped instead of U shaped and filled in the sides of the square as shown in **fig. 12C**. The other diagonal became the "boom" and consisted of two 2.4-meter (8-foot) bamboo garden canes joined by a length of aluminum, supporting the apex of the Vs.

V-shaped elements are not suitable for multibanding by the methods used for the driven element, and ordinary traps would be unsuitable for suspension in wires supported by such a light framework, as well as being too lossy. I therefore used separate elements for each band with their ends strung out to different points on the vertical loading rods of the driven elements in the hope that this way they might not get entangled! Though somewhat haywire, this arrangement has unexpectedly survived two severe storms and, although it needs a lot of tidying up mechanically, comes fairly close to the ultimate in lightness combined with high performance. Details in **fig. 12** should assist any reader wishing to experiment on similar lines. Despite the larger size, the overcoupling problem was not completely avoided and there was some slight difficulty in adjusting the 14-MHz reflector, but this was overcome by increasing the spacing slightly as indicated in **fig. 12C**.

The linear resonators work as follows.^{9,11} The inductance L_{AB} of the central portion (AB) of the element is tuned to resonance by C1 so that it acts as insulator for 28 MHz, making the element two half-waves in phase. At 21 MHz, about half of C2 serves to eliminate the inductance by tuning it to parallel resonance, with the remainder used to series resonate the inductance (L_O) of the outer portions of the element, L_{AB} and L_O chosen to be roughly equal. At 14 MHz, the capacitors are virtually "not there," their values at 21 and 28 MHz having been inflated by series resonance with their connections, and consequently AB no longer acts as a tuning inductance

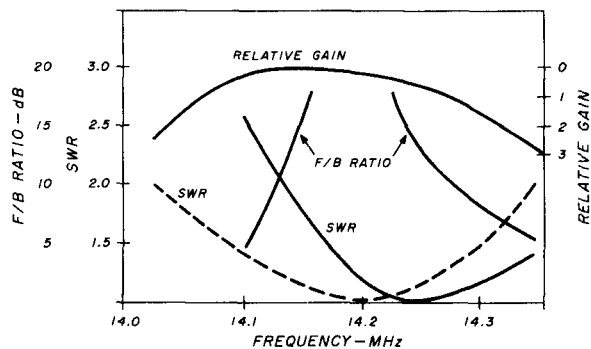


fig. 10. Typical performance of the 1-meter-square (10-foot-square) beam. All parameters were measured with the beam at a height of 2.1 meters (7 feet) and the reflector tuned for 14.2 MHz. The dotted curve shows the improvement in SWR after adding 10 cm (4 inches) to each end of both elements and retuning the reflector for best front-to-back ratio at each frequency. Note: The gain curve is listed as dB down from the maximum.

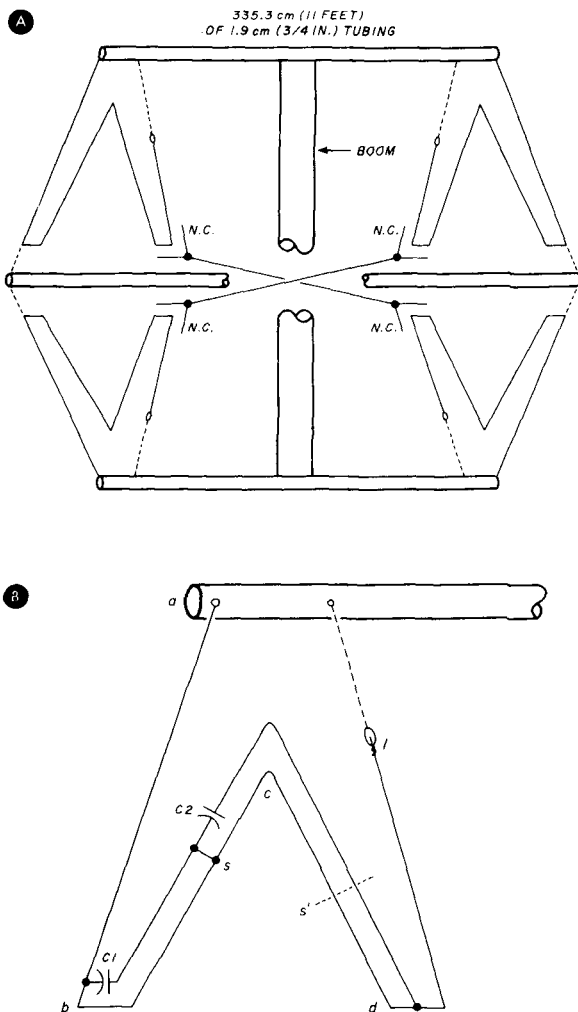


fig. 11. This is an alternative form of the beam shown in fig. 9. In this case (A), the elements have been folded in a horizontal plane to avoid any vertical projections. The metal supporting strut in the center of the boom also serves as a 21/28-MHz driven element in the multiband version. The detail shown in (B) illustrates the arrangement for multibanding with linear traps. Moving the shorting bar from *S* to *S'* results in an improved trap for 28 MHz, but separate parasitic elements must then be used for 21 MHz. For monoband 14-MHz operation, the capacitors are omitted, but extra wire may be needed to obtain sufficient loading. The wire lengths, *a*, *b*, *c*, *d*, and *e*, are all equal and approximately 35.6 cm (14 inches). *C1* and *C2* use the wire segments *bs* and *sd* to form the linear traps for 28 and 21 MHz respectively.

but reverts to its normal role as the "middle portion of a dipole." This process is accelerated by mutual coupling between the capacitive and inductive branches of the resonators. Values for *C1* and *C2* are critical and I used selected capacitors slightly lower than the required values (about 10 pF and 20 pF respectively) making up the difference with short, open-wire, adjustable stubs.

Although linear resonators have little effect at




lower frequencies, the 21-MHz resonator in its simplest form has disastrous consequences at 28 MHz, where it looks like a rapidly varying inductance that results in a very narrow bandwidth. This problem is overcome by the capacitors (*C3*) which form additional linear resonators tuned somewhat above 28 MHz so that the effective inductance at 28 MHz is greatly increased without affecting 21 MHz. *C3* is not critical. Using a grid-dip oscillator, the driven element should be tuned by adjustment of *C1*, *C2*, and the length of the loading wires to provide the required resonant frequencies, taking care to avoid spurious resonances. Using a pick-up loop with a rectifier and meter as a simple rf current indicator, currents in *L* and *C1* at 28 MHz will be roughly equal and some four times greater than the loop current observed at point *D*, (see fig. 12C). At 21 MHz, currents in *C2*, *L*, and just outside *AB* can be expected to be roughly in the ratio 3:2:1. This is not critical, but any major departure could indicate a spurious resonance. It is important to ensure symmetry and this requires a balanced feed, not a gamma match.

When tuning three-element antennas, there are many performance combinations, but I tended to aim for maximum gain in the 14.1-14.2 MHz region. This yielded the following typical performance figures:

Bandwidth for greater than 9 dB front/back ratio	200 kHz
Maximum front/back ratio	12-15 dB
Bandwidth for less than 1 dB drop in gain	230 kHz
SWR at band edges	2.0:1

Better front/back ratios and bandwidths were obtainable at the expense of gain, thus emphasizing the desirability of remote tuning; in this way it should be possible to achieve effective gains between 6 and 7 dB. I tried to achieve this by using a single pair of additional feeders, attached to coupling loops placed near the centers of each set of parasitic elements, but achieved only limited success. A practical, but rather cumbersome alternative is to use separate feeders to all elements.

At 21 MHz, the SWR was 1.5-1.6 over the whole band; front/back ratio increased with frequency from 13 to 16 dB, but was accompanied by an apparent 2-dB drop in gain. At 28 MHz, bandwidth for an SWR better than 2:1 was 350-400 kHz. Tuning for maximum gain at 28.5 MHz, there was a drop of 2 dB at 28.25 and 29 MHz. The front/back ratio rose from 11 dB at 28.5 to 15 dB at 28.9, but was down to 6 dB at 28.25 MHz. These figures have been selected as fairly typical from a wide assortment and the variations illustrate the degree of improvement to be expected from remote tuning. The linear resonator

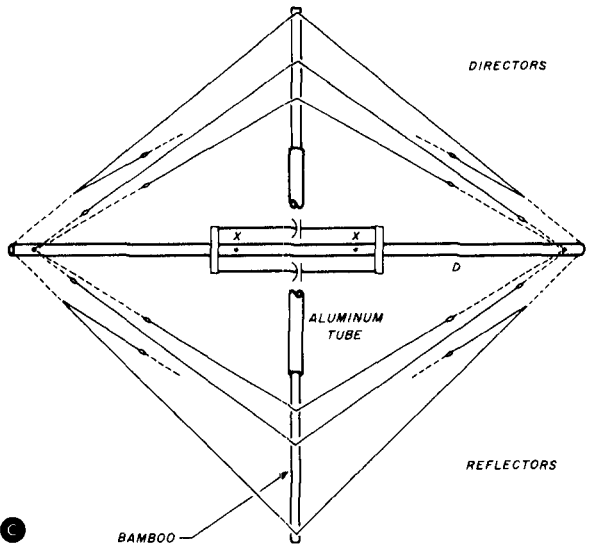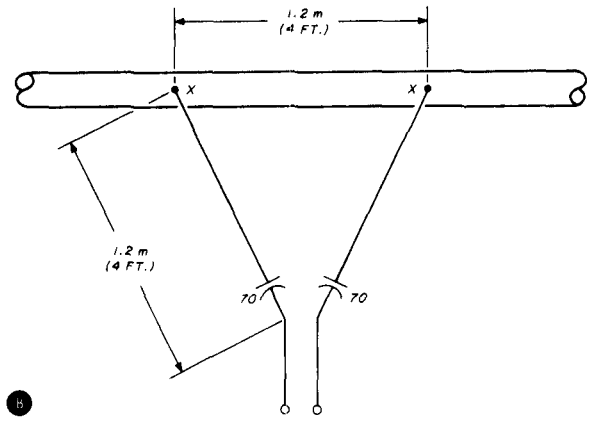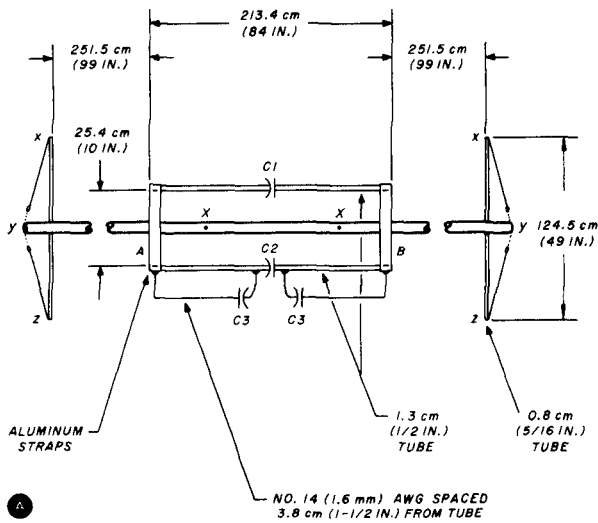

frequency	element lengths	
	reflector	director
14 MHz	11.2 meters (440 inches)	10.8 meters (426 inches)
21 MHz	6.9 meters (272 inches)	6.3 meters (259 inches)
28 MHz	5.1 meters (202 inches)	4.8 meters (188 inches)

frequency	boom length from center of driven element to apex of Vs	
	reflector	director
14 MHz	4 meters (156 inches)	3.2 meters (126 inches)
21 MHz	2.6 meters (101 inches)	2.6 meters (101 inches)
28 MHz	2.2 meters (86 inches)	2.2 meters (86 inches)

fig. 12. (A) shows the plan view of the driven element made from aluminum tubing, starting with 32 mm (1¼ inch), tapering down to 12.5 mm (0.5 inch) diameter. The feeder is connected to points x,x using the delta match shown in (B). Close examination of the end of the element may be necessary to fully understand the loading. Each vertical rod (x,z) is not only a help in providing the end loading, but is also used as an attachment point for the ends of the parasitic elements. Also attached to the vertical rods is the other portion of the end loading, short lengths [40.6 cm (16 inches)] of no. 14 AWG (1.6-mm) copper wire. These lengths are run from x and z to point y, i.e., in the same line as the center element. The delta match detail is shown in (B). For open-wire line, the capacitors are omitted and the spacing is increased slightly. A plan view showing the parasitic elements is shown in (C). The elements are made from no. 14 AWG (1.6-mm) copper wire.

details shown in fig. 12 are applicable also to "full-size" elements, a reduction in length of about four per cent being required due to the presence of C2.

Earlier I criticized trapped beams, but the situation is quite different with small elements, including the V-shaped parasitic elements of the beam just described. If the folded ends are left in place, at the higher frequencies they degrade performance because of an inefficient current distribution and by radiation from the ends. The only practical way to remove the excess capacitance is by means of traps, but ordinary traps result in appreciable losses even with full-size elements. And, as the radiation resistance drops, the power loss increases in the same proportion so that large losses can be expected. This

problem can be resolved with the help of the linear resonator, which, instead of degrading the performance at 14 MHz, actually has a very slight beneficial effect by increasing the total capacitance.

Another problem is caused by excessive spacing between elements at the higher frequencies. This can be avoided by using a separate, centrally placed, driven element for 21 and 28 MHz, a coax feeder with 4:1 balun, and a delta match into a linear resonator, providing two-band operation. To keep within an area 3 meters square (10 feet square), long, vertical, loading rods would have been required, but I thought it was better to increase the element lengths to 3.4 meters (11 feet) and make full use of the 4.7-meter (15.5-foot) turning circle.

Multiband operation, with good front-to-back ratios, was obtained using traps as shown in **fig. 11B**, but on 21 MHz the bandwidth was too narrow to be acceptable. The structure was braced with a lot of cord ties and I was able to use them to support separate (wire) parasitic elements for 21 MHz.

Capacitive coupling from these into the driven element was excessive, however, and the reflector had to be neutralized. Bandwidth was still rather narrow and devious means were needed to achieve even enough remote tuning for band coverage (without beam reversal) on 21 MHz. Despite satisfactory performance, the design became too complicated to be recommended in its present form. It has nevertheless proved that the problem is solvable, and guidelines have been established for further experiments. In particular, I found that proximity between the 14 and 21 MHz parasitic elements (average separation less than 0.3 meter [1 foot]) had no effect on 14-MHz performance. One obvious solution would be the use of separate parasitic elements for the higher bands, stacked about 0.6 meter (2 feet) above and below the 14-MHz elements. Linear traps remain the neatest method, and from inspection of **fig. 11B**, it is obviously possible to increase the trap length (and hence the bandwidth) by using the entire available length for 21 MHz, in which case the 28 MHz traps would have to be accommodated within the 21 MHz traps. Experiments along these lines can be recommended to anyone who feels he has the necessary skill and patience.

Unfortunately, narrow bandwidth at 21 and 28 MHz, *in comparison with a monoband antenna of the same size*, appears to be a price that has to be paid for the multibanding of a "smallest-possible" beam. (It is also part of the price usually, but mistakenly, paid for the multibanding of full-size elements which, when used without traps, have very much higher radiation resistances at the higher frequencies.)

One practical point that must be stressed is the need for accurately maintaining the shape of the linear resonators. With separate feeders to each element, small changes in resonant frequency can, of course, be corrected from the shack, but any asymmetry causes the current maximum to shift toward one end of the radiator. Probably worse, a voltage will exist in the center causing current to flow in a metal boom or dielectric losses in a wooden boom if wet! Insulating a metal element from a metal boom is not a complete cure, because there is bound to be some capacitance, but it has been found preferable to bonding.

future trends

I have tried to cover the subject in all its aspects

and find it difficult to envisage a future for small beams outside the guidelines presented here, but perhaps someone will take this as a challenge and come up with something really new! There is room for plenty of ingenuity in finding ways of folding elements to fit them into small spaces, and it should be possible to improve bandwidth by the somewhat mind-boggling process of folding a folded dipole! The mini-quad also has interesting possibilities and appears to lend itself to a number of options for multibanding, of which I favor use of 20-meter loops for 10 meters, and separate, stacked elements for 15 meters.

Better construction methods are needed to improve reliability and achieve closer tolerances. A completely foolproof tune-up procedure, which can be used in all situations, has yet to be evolved. More data is needed on the range over which remote tuning from the shack can be achieved without penalties; further development is needed to find the best methods for remote tuning and reversal of small three-element beams. Perhaps someone may then get around to applying these features to the big beams — which will otherwise find themselves at a disadvantage! For multibanding of beams such as those described here, I believe the future lies in improved versions of the linear resonator trap, which would ease the problem of remote fine tuning and avoid the complications of stacking.

As an alternative to neutralizing, I have tried using the 21/28-MHz element as an electrostatic screen between the 14-MHz elements, but I failed to achieve a viable system. There are difficulties, for example, in specifying exactly what is "earth," and I have found it advisable, even with neutralizing, to insulate elements from the boom and preferably to use a wooden boom.

references

1. Fred Caton, VK2ABQ/G3ONC, *Electronics Australia*, October, 1973.
2. R. G. D. Stone, G3YDX, "Practical Design for a Capacity Hat Loaded 14-MHz Mini-Quad," *Radio Communications*, October, 1976.
3. L. A. Moxon, G6XN, "Supergain Aerials," *Radio Communications*, September, 1972.
4. L. A. Moxon, G6XN, "Evaluating Aerial Performance," *Wireless World*, February and March, 1959.
5. L. A. Moxon, G6XN, "Gains and Losses in HF Aerials," *Radio Communications*, January, 1974.
6. L. A. Moxon, G6XN, "Two-Element Driven Arrays," *QST*, July, 1952.
7. H. P. Williams, *Antenna Theory and Design*, Second Edition, Volume II, Pitman, London.
8. Karl Rothamel, *Antennenbuch*, Telekosmos-Verlag, Berlin, 1968, page 210.
9. L. A. Moxon, G6XN, "The Disappearing Inductance — A New Trick and Some Better Beams," *Radio Communications*, April and May, 1977.
10. Pat Hawker, *Radio Communications*, (Technical Topics), June, 1977 and 1978.
11. L. A. Moxon, "High Frequency Antennae and Propagation Modes in Relation to the Amateur Service," IEE Conference on Aerials and Propagation, 1978.

ham radio

YOU ASKED FOR IT YOU GOT IT DSI QUIK-KIT®

50 HZ TO 550 MHZ COUNTER KIT

95% ASSEMBLED 100% TESTED
Performance You Can Count On

FREQUENCY COUNTER APPLICATION:

- Ham Radio — Two Way Radio — CB
- Audio Amplifier & Receiver Repair
- Computer Maintenance & Construction
- A Must for TV & PLL Repair

\$99.95
MODEL 3550K

includes built-in
Pre-Amp & Prescaler



DSI OFFERS THE BEST OF TWO WORLDS . . .

An unprecedented DSI VALUE . . . in a high quality, LSI Design, 50 HZ to 550 MHZ frequency counter kit. And, because it's a DSI innovation, you know it obsoletes all competitive makes, both in price & performance.

With 95% of the assembly completed by DSI, you are only one hour away from solving all of those difficult bench problems, from adjusting 60 HZ clock-time bases to setting the frequency of a 468 MHZ Mobile Radio.

FACT: Every 3550 QUIK-KIT® PC board is factory assembled and tested before shipment. **FACT:** The problems of bad LED's, IC's, and Capacitors are a thing of the past. **FACT:** No manufacturer except DSI offers a 550MHZ frequency counter with . . . 8 digits, .5 in. LED's, TCXO, 1HZ resolution and a one year warranty on parts for under \$100.00. **FACT:** We do not know how long we can hold this low, low price. **GO WITH THE LEADER . . . BUY A DSI FREQUENCY COUNTER KIT TODAY. SAVE TIME & MONEY AND BE ASSURED IT WILL WORK THE FIRST TIME.**

DSI — GUARANTEED SPECIFICATIONS

Time Base TCXO 1PPM 65° to 85°F
Freq. Range 50HZ to 550MHZ incl. two SO239 inputs
Resolution 1HZ to 55MHZ, 10HZ to 550MHZ
Gate Time 1 sec & 1/10 sec with Auto Decimal Point
Display 8 digits, ½ inch LED with Leading Zero Blanking
Sensitivity 25MV @ 25MHZ, 150MHZ, 250MHZ;
 75MV @ 450MHZ
Power Batt., 12VDC @ 300Ma, 110VAC (with AC-9)

3550K Kit \$99.95
 T-101 Ant. 3.95
 AC-9 AC Adp. 7.95
 Shipping, Handling, Ins. . . . 10.00

3550W Wired 149.95
 T-101 (incl.) NC
 AC-9 (incl.) NC
 Shipping (incl.) NC



CALL TODAY TOLL FREE: (800-854-2049) Cal. Res. CALL (800-542-6253) TO ORDER OR RECEIVE MORE INFORMATION ON DSI'S FULL PRODUCT LINE OF FREQUENCY COUNTERS RANGING FROM 10HZ TO 1.3GHZ

TERMS: MC - VISA - AE - Check - M.O. - GOD in U.S. Funds. Orders outside of USA & Canada, please add \$20.00 additional to cover air shipment; California residents add 6% Sales Tax.

DSI INSTRUMENTS, INC.

7924 Ronson Road, Dept. G, San Diego, CA 92111

high-performance voltage-tuned mosfet oscillator

One comment often heard on the amateur bands is that the art of homebrewing is a thing of the past. Nothing could be further from the truth. The amateur fraternity has acquired new vigor and growth, and more hams now than ever before, are "rolling their own." This is happening in spite of the fact that, again as a result of recent amateur growth, commercial manufacturers of ham gear are able to offer greater bargains in terms of performance per dollar. Yet there is a growing number of do-it-yourself amateurs who are dedicated to building all or some of their own equipment. The VTO described here is only one example of this trend. I am admittedly a homebrew addict.

concept

The constantly changing state of the art has provided a diversity of methods and circuits applicable to today's requirements. The VTO described in this article is more than just another of the garden variety. It was deliberately designed to perform well under the most demanding conditions. You may be interested in duplicating the design, or in using the basic concept to build one to suit your own particular needs.

This article is intended to provide sufficient specific information so that the design can be easily duplicated. If you need a VTO possessing superior performance characteristics, scrutinize the following checklist and decide if this construction project is for you.

1. Adjustable tuning range
2. Exceptionally clean spectrum — like that of a VCXO
3. Frequency essentially independent of load
4. A temperature compensation adjustment to cancel drift
5. Power output + 10 dBm in a 50-ohm load
6. Remote tuning capability
7. Frequency independent of line voltage
8. Excellent short-term frequency stability
9. Excellent long-term frequency stability
10. Fast warm-up

After reading this article, you may wish to modify

the design to fit your own needs. If so, there are certain things you should not do or need not do:

Don't use powdered-iron tuning slugs in the oscillator coil. It is particularly important to stay away from pot cores, bobbins, sleeves, toroids, and other ferromagnetic materials. Not only do these devices generally have relatively high temperature coefficients, but they possess a characteristic called hysteresis, which may cause the VTO frequency to wander from time to time for what appears to be no good reason. The permeability of powdered iron and ferrite materials is relatively sensitive to even weak magnetic fields.

Don't use a clamping diode on the MOSFET oscillator gate. It isn't necessary and only adds to the complexity. Note that the gate is grounded through the coil winding and therefore bias shift on gate 1 cannot occur.

The VTO described here should be operated at the fundamental, not a subharmonic. With the source bias used, the waveform on gate 1 is very nearly a pure sine wave, as is the waveform at the output. The circuit does not work well as a multiplier.

Don't operate the varicaps with too little bias. If the peak rf voltage exceeds the bias, rf rectification may occur which will generally disrupt performance. In the present design, varicap bias varies between 7 and 10 volts, although bias as low as 4 volts may be used if a wider band is to be covered.

Don't use a zener to provide voltage regulation for gate 2 or the drain of the MOSFET oscillator. (See fig. 1.) Use an integrated circuit regulator such as the μ A723. Gate 2 voltage should be provided from a resistor divider network fed from the 723 output.

Don't mount the oscillator on a printed circuit board, since flexing or warping can cause serious stability problems. It is much better to assemble the entire oscillator on a brass or copper plate that can be mounted firmly to a shield box. Copper is preferred

By Norm Foot, WA9HUV, 293 East Madison Avenue, Elmhurst, Illinois 60126

because it has higher heat conductivity, which helps to keep all circuit components at the same temperature. Use a small plate not less than 0.8 mm (0.032 inch) thick.

Don't use plastic, phenolic, or fiber coil forms. The coil forms used in this VTO are Cambion part number 1536-3-1. Only the amplifier circuit coil uses the tuning slug, which is carbonyl J (green).

Do not use ceramic trimmers in the oscillator circuit. The glass-piston trimmers specified possess a low temperature coefficient and are mechanically rugged.

Do not locate the VTO circuit near heat-generating components such as power supply regulators or transformers. Remember, since the oscillator is voltage-tuned, it can be located at any convenient location because it does not require mechanical linkage with the front panel. You may want to take advantage of this feature and locate it next to the mixer where it belongs.

application

This particular VTO was designed as the local oscillator for the second mixer in a communications receiver. The design requirements were very exact-

ing. It had to operate above 30 MHz and also drive a counter to provide a digital readout. The readout constantly monitors the frequency, which means that any drift exceeding 50 Hz would be particularly annoying, not to mention the problem associated with copying sideband signals. Furthermore, the tuning range was to be adjusted to cover exactly 100 kHz plus 100 Hz overlap at each end. The drift after warmup turned out to be considerably less than originally expected, in spite of the higher-than-normal operating frequency and the use of varicaps for tuning.

tuning mechanism

Although the circuit values can be modified so that the VTO covers other frequency ranges, this particular unit tunes 30,250 to 30,350 kHz. A five-turn, linear-taper, Bourns precision potentiometer (part number 35205-417-453) is used for frequency tuning. A 6.4-mm (2.5-inch) diameter Millen fluted knob provides approximately 20-kHz per revolution, permitting ssb signals to be tuned in with relative ease. This amounts to 18 degrees per kHz. A ten-turn potentiometer can be substituted if greater tuning resolution is desired. In any event, avoid the use of a gear train to increase resolution if backlash is to be avoided.

Originally, there was considerable concern regarding the ability of the potentiometer to stand up

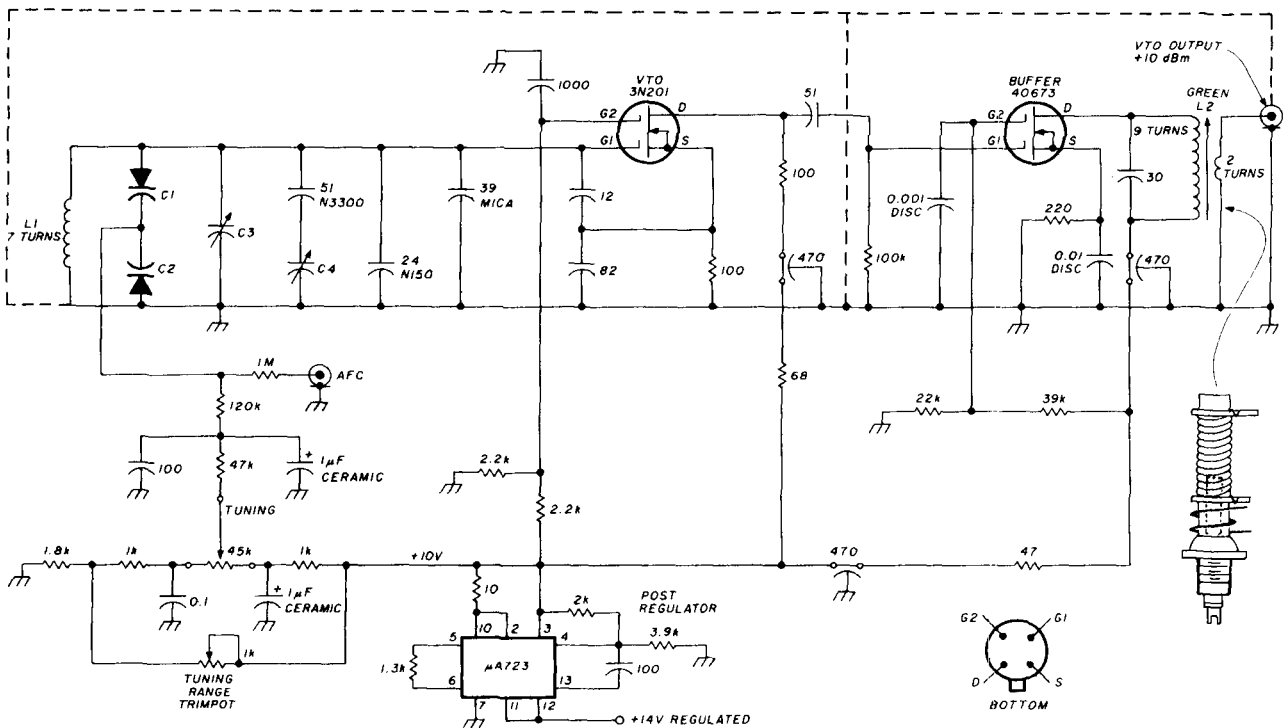


fig. 1. Schematic diagram of the voltage-tuned oscillator. All fixed resistors are 1/4-watt composition, and all capacitors are dipped silver mica unless otherwise indicated. The 470-pF feedthrough capacitors are from Spectrum Control (part number 54-794-002-741M). The varactors are TRW 4808s. Capacitor C3 is an Erie 0.7-12 pF piston trimmer, while C4 is a 1-18 pF Erie piston trimmer. L1 is wound on the Cambion 1536-3-1 coil form; L2 uses the same form with the carbonyl J tuning slug inserted as shown in the diagram.

to abuse day after day. However, the original unit showed no indication of wear after two years of almost daily and often grueling use.

circuit details

The VTO includes a 3N201 dual-gate MOSFET oscillator driving a low-cost 40673 MOSFET buffer ampli-

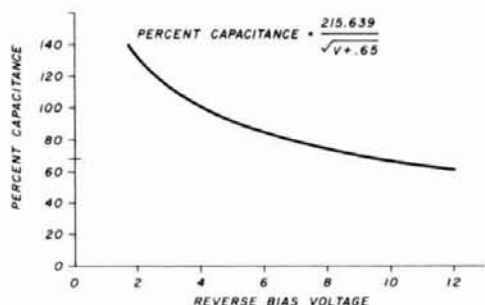


fig. 2. Manufacturer's specifications for the TRW 4808 varactor.

fier. A high degree of isolation is achieved by use of the 100-ohm resistor in the oscillator drain circuit. As a result, pulling of the oscillator as the buffer coil is tuned through the oscillator frequency is less than 200 Hz. Since the buffer circuit is broadband and therefore fixed tuned, this effect has insignificant effect on drift. If the load terminals are opened or short-circuited, the change in the oscillator frequency is less than 100 Hz. Power output over the 100-kHz range is essentially constant at 10 milliwatts under load.

The coils are wound on ceramic forms with no. 26 (0.4-mm) AWG enameled copper wire and heavily doped with polystyrene Q dope. The 50-ohm output winding on the amplifier coil consists of two turns of no. 26 (0.4-mm) AWG enameled copper wire, pushed up tight against the bottom (cold) end of the tuned circuit coil. It is important that the tuning slug be positioned at the 50-ohm output end of the coil, partly overlapping both the tuned circuit and the output winding.

power supply considerations

Both the oscillator and its buffer are powered from a μ A723 integrated circuit regulator which accepts current from a regulated 14-volt supply. The 723 reduces the 14 volts to 10 volts. The importance of this additional regulator cannot be overemphasized. Not only does it provide the required tight voltage regulation, but by its nature the output voltage is extremely well filtered. For example, when the spectral purity of the VTO was compared while using a battery supply and then the 723 post regulator, there was no noticeable difference. By contrast, without the post regulator, there was considerable hum mod-

ulation. Small changes in supply voltage cannot be tolerated because the same supply is applied to the tuning varactors.

A pair of TRW 4808 voltage-variable, varactor diodes (varicaps) are used to control the VTO frequency. These 27-pF tuning varactors are connected in the conventional back-to-back manner with the tuning voltage fed to their junction through an RC filter. The 1000-ohm tuning range trimpot is set near its midpoint so that the voltage across the 45k-ohm tuning potentiometer is approximately 3 volts. Under these conditions, the tuning potentiometer provides the varicaps with between 7 and 10 volts. Long life and reliability is assured since the potentiometer carries only 64 microamperes while the current carried by the moving arm is essentially zero. Data on the varicap is shown in fig. 2.

The varicap tuning sensitivity is 30 μ V/Hz. If the spectral purity of the oscillator is to be high enough for the intended application, power supply noise and ripple must be extremely low. The μ A723 is specified at 20 μ V rms noise typical. This could cause a random peak-to-peak fm of 1.89 Hz. Most of this noise is eliminated by means of the lowpass filter consisting of the 47k-ohm resistor and the 1.0 μ F capacitor. What little noise actually remains should consist of very low-frequency components, since the RC filter has a 20 Hz cut-off frequency. In the author's application, there is no detectable reduction in receiver output noise when a battery is substituted for the μ A723 regulator.

Ripple from the 723 is specified as typically 74 dB below the input ripple. Even if the input ripple were 100 mV peak-to-peak, the output ripple would only be 2.0 μ V, including the filtering action of the varicap RC filter. This translates to less than a tenth of a cycle fm.

The varactor capacity as seen by the oscillator coil varies from 3.8 to 4.4 pF. Since the total circuit capa-



Since the VTO is dc tuned, it does not have to be located near the front panel. In this case, it has been incorporated into the same module as the HFO buffer.

city is approximately 90 pF, the ratio of high to low end frequencies is as follows:

$$\frac{F_H}{F_L} = \sqrt{\frac{C + \Delta C}{C}} = \sqrt{\frac{90.6}{90}} = 1.0033$$

where

- F_H = high-end frequency
- F_L = low-end frequency
- C = total circuit capacitance

Therefore, if

$$\begin{aligned} F_L &= 30,250 \text{ kHz,} \\ F_H &= 1.0033 \times 30,250 \\ &= 30,350 \text{ kHz.} \end{aligned}$$

Of course, the tuning range tripot can be adjusted to provide overlap at each end of the tuning range if that is desired.

The frequency ratio formula can also be used for different frequencies and tuning ranges. I suggest that the circuit capacity be scaled in proportion to wavelength. A VTO operating between 5.0 and 5.1 MHz, for example, could use a circuit capacity of about 500 pF. The varicaps would each be 150 pF, while C would be approximately 20.2 pF, which requires a tuning voltage range of about 6.4 to 10 volts.

tuning linearity

While the tuning potentiometer is linear, the varicap tuning characteristic is not. As a consequence, the frequency tunes slightly faster at the low end of the range than at the high (see fig. 3). However, the departure from linearity is small. Based on the manufacturer's data, and by measurement, the number of kilohertz per revolution at the low end is 22.4 compared with 18.2 at the high end. This nonlinearity might be objectionable if it were necessary to employ a mechanical frequency indicator, such as a planetary mechanism. In my application, the VTO drives a programmable digital counter in which case the small nonlinearity is of no consequence.

temperature compensation

Considerable effort went into developing a variable temperature compensating circuit for this VTO. While the idea is not new, it lends itself well to this particular application. The compensation circuit is simple and easy to adjust.

A piston trimmer is connected in series with a negative temperature coefficient ceramic capacitor. The coefficient was intentionally made larger than needed. The effective circuit coefficient is adjusted by tuning the piston trimmer, C4. The change in frequency which resulted is compensated for by adjusting C3. There is a particular setting of these two

capacitors which will provide zero temperature coefficient, therefore zero oscillator drift after warm-up.

Based on manufacturer's data, the voltage-tuned varactors have a temperature coefficient of 250 to 300 ppm/degrees C. Of course, most of the other circuit elements exhibit positive coefficients as well, but their coefficient is generally less — in the order of 50

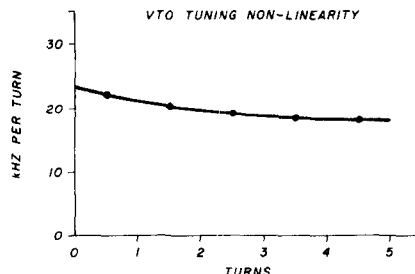


fig. 3. Chart of the voltage-tuned oscillator's linearity as the oscillator tunes from one end of its range to the other.

to 100 ppm/degrees C. Dipped silver-mica capacitors were found to be entirely satisfactory for use in the oscillator and amplifier tuned circuits.

A series of tests was performed using NTC capacitors with various temperature coefficient values. Finally, a 51-pF, N330 capacitor was selected. An additional 24-pF, NTC 150 capacitor was added in parallel to bring the circuit temperature coefficient within range of C4. C4 is a key circuit element because it allows the effective temperature coefficient to be adjusted, and therefore the amount and direction of oscillator drift. The proper setting was found after a number of drift tests were performed over a period of a few hours using different settings of C3 and C4. The results of these tests are shown in fig. 4.

After a period of about three months, and again a year later, the drift was checked. It was found that no change in compensation had taken place. The circuit gives you a real good opportunity to check the other fellow's frequency stability!

After two years of drift-free use, and strictly out of curiosity, the original 3N201 oscillator MOSFET was replaced with another made by a different manufacturer. It was found that the frequency was slightly higher and needed trimming. Subsequent drift tests showed the circuit to be over-compensated. A new set of drift tests were run and the overall temperature coefficient quickly brought back to zero.

If the drift that occurs after turn-on from a cold start is annoying, or if the application requires absolutely zero warmup drift, I recommend that the drift correction circuit described by PAØKSB¹ be used. This circuit was built and applied to the AFC terminal shown in fig. 1. The performance was excellent.

There was absolutely no warmup drift. It was necessary, however, to include the up-down tuning push buttons recommended to periodically correct for calibration errors inherent in the design. Since this requirement was more of a nuisance than the warmup drift, the circuit was not permanently installed. From a practical standpoint, about the time the 6146s are warmed up and ready to go, the VTO has stabilized! It was also interesting to note that if the VTO design described here were to be modified for operation at 5.0 MHz, the warmup drift would be only about 100 Hz.

dryer will probably prove only that the temperature compensating circuit has a thermal lag.

Short-term drift and low-frequency shot noise effects can be determined by tuning in WWV (assuming the VTO is used as the local oscillator of the receiver). Using the BFO, set the tuning for a convenient heterodyne (500 Hz for example), and then acoustically zero beat an audio oscillator and speaker combination with the receiver output. Listen for any warbling and jumping. If you use a low-beat note, you should be able to hear and detect frequency variations as small as ± 2 Hz by reading frequency

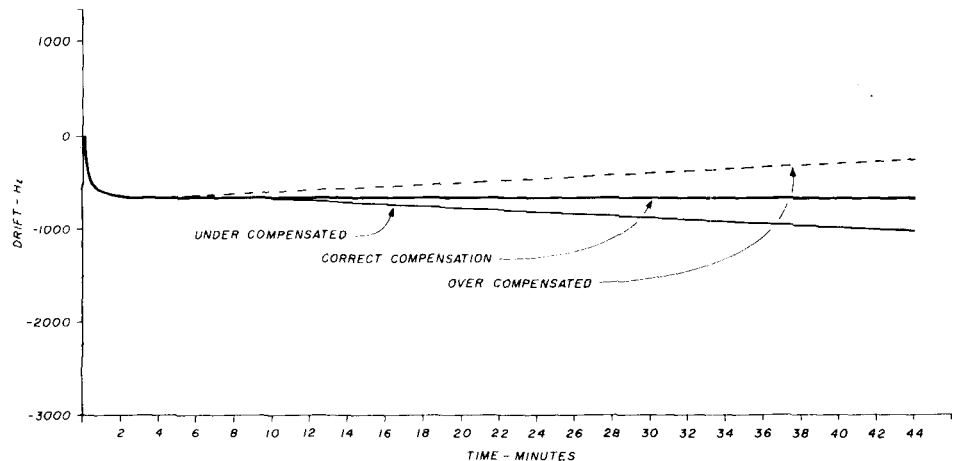


fig. 4. Typical results of the oscillator drift tests. Incorporating the drift correction circuit described by PA0KSB will reduce the frequency change to zero.

Excellent short-time stability was achieved by enclosing the VTO circuit in a metal box. Also, a brass cup heatsinked to the chassis was mounted over the 3N201 transistor and its socket. This protects the transistor from drafts to which it is particularly susceptible, and forces the ambient temperature in the vicinity of the transistor to track that of the entire circuit. This combination was found to be very effective.

One of the most frustrating problems associated with checking out a new oscillator is being able to separate out the various causes of drift. They include the effective temperature coefficient of the overall electrical circuit, the effects of voltage variations, and mechanical effects. If the oscillator varies or jumps when the oscillator chassis is tapped sharply with a screwdriver, you have mechanical problems. Don't try to temperature stabilize the circuit until it is mechanically sound. It is a good idea to run the temperature of the circuit up and down several times using a hair dryer to reduce mechanical strains before checking drift.

If you use the regulator circuit suggested here, you should be able to set the line voltage as low as 100 volts before detecting any oscillator drift. Long-term drift tests should be performed by running the circuit as it would normally be operated. The use of a hair

changes from the audio oscillator dial. If the oscillator is working properly, random variations should not exceed ± 5 Hz at 30 MHz, or ± 1 Hz at 5 MHz, and there should not be any jumping. It is interesting that the technique described here allows you to detect variations as small as one part in 10^7 or better.

references

1. Klaas Spaargaren, PA0KSB, "Drift Correction Circuit for Free-Running Oscillators," *ham radio*, December, 1977, page 45.

bibliography

- Cromartie, Edmund S., "Synthesis of a Varicap," *QST*, September, 1972, page 44.
- DeMaw, Doug, W1CER, "Building a Simple Two-Band VFO," *QST*, June, 1970, page 21.
- DeMaw, Doug, W1CER, "VFO Design Techniques for Improved Stabilities," *ham radio*, June 1976, page 10.
- Foot, Norman J., WA9HUV, "A Digitally Programmable HF Communications Receiver," *ham radio*, October, 1978, page 10.
- Lee, Di Ming, "A VTO for 80 Through 10 Meters," *QST*, November, 1970, page 21.
- McDowell, Warren, W2A00, "Varicap Tune Your VFO," *QST*, April 1975, page 27.
- McGraw, Robert W., W2LYN, "A 3- to 4-MHz Franklin VFO," *QST*, August 1971, page 29.
- Mather, A.S., VK2JZ, "An External VFO For The SB-100 Transceiver," *QST*, October 1970, page 42.
- Schrick, Gerd H., WB81FM, "Digital Readout Variable Frequency Oscillator," *ham radio*, January 1973, page 14.

ham radio

NOW
THERE ARE

3

SWAN RF LINEAR AMPLIFIERS



1500Z

Swan linear amplifiers give you all the power you need for low power transmitters in a choice of compact models engineered for maximum efficiency and performance. All three units operate on 80, 40, 20, and 15 meters with AC input of 110V-220VAC, 50-60 Hz.

THE 1500Z. The self-contained 1500Z with tuned input makes it an ideal companion for the Swan 100MX! A high quality, conservatively rated, 110/220 VAC power supply provides 2200 volts DC to two 572B tubes. Rated at 1500 watts PEP input, nominal output is 750 watts into the antenna. Metering is selectable for "relative output," "Ip,"

and "Ep," and instant operation with the "Operate" and "Bypass" switch.

THE 1200Z completely self-contained amplifier and power supply gives you 1000 watts PEP input on SSB and 750 watts DC input on CW. With most of the features of the 1500Z, this unit is lightweight and portable.



1200Z

THE MARK II 2000 watt Linear Amplifier delivers maximum legal PEP power on SSB and 1000 watts DC on CW, including 10 meter band. Included is a matching power supply. Both units are independently cooled with low noise blowers.

Available only through authorized dealers.

MARK II



Please send full details
on Swan Linear Amplifiers to:

 **SWAN**
ELECTRONICS

305 Airport Road, Oceanside, CA 92054 |
(714) 757-7525

NAME _____

ADDRESS _____

CITY _____

STATE _____ ZIP _____

operational characteristics

of the 555 timer

Care and feeding of the multi-purpose 555 timer — a closer look at some of the reasons behind the designs

The 555 timer has become one of the most popular ICs used by both industry and hobbyists alike. Since its introduction by Signetics Corporation in 1972 (as the NE555), every major IC manufacturer has produced a 555 equivalent. Variations have been developed by Signetics and others, primarily for specific applications (NE556, NE558 quad, XR2250 programmable).

Circuits using the 555 show up in virtually every electronics-oriented magazine. The popularity of the 555 is partly due to its versatility and partly because of its cost (generally less than 50 cents). These published circuits use the timer to generate ramps and time delays, detect missing pulses, act as oscillators, and a host of other applications. The list of specifics can become quite extensive. Most of these applications now appear as "cookbook" circuits with little detail on how the design was accomplished and what variations a builder of that circuit can expect.

This article was written to help you get a better understanding of the 555 and how its eight pins react to external components. With this information, you can get a feel for how most 555 applications work. For the more creative, I'll outline the basic design rules for using the 555. (Information on the 555 also applies to the 556 dual timer.)

Fig. 1 shows the block diagram of the 555 timer. The basic components consist of an output driver, a control flip-flop, and two voltage comparators. The flip-flop drives the discharge transistor and output driver. The state of the flip-flop is controlled by the reset pin (pin 4) or one of two comparators. One comparator is controlled by the voltage on the trigger pin (pin 2) and the other controlled by the voltage on the threshold pin (pin 6).

These comparators have separate reference points which are controlled by the three-resistor divider from V_{CC} to ground. The resistors are all of equal value (5-k ohms). The reference voltage for the threshold comparator is thus $2/3$ of V_{CC} , and is also available on pin 5, the control voltage pin. The reference voltage into the trigger comparator is set at $1/3$ V_{CC} by the divider network (Note: it is also one half of the voltage on the control voltage pin).

The output (pin 3) has the capability of providing 200 mA. Because of the totem-pole structure, this

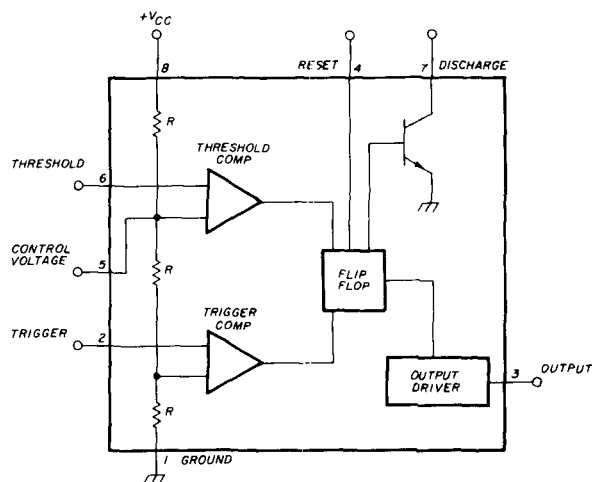


fig. 1. Block diagram of the 555 timer. The three-resistor divider network causes the voltage comparators to work on a ratio, rather than an absolute voltage level. This makes any timing functions relatively insensitive to supply voltage.

By Bob Marshall, WB6FOC, Signetics Corporation, Post Office Box 9052, 811 East Arques Avenue, Sunnyvale, California 94066

current supply is available whether the output is high or low. Additionally, when the output is high, the discharge transistor is turned off.

monostable operation

To help understand the action of the comparators it is best to show the operation of the 555 in one of the basic timing modes. The monostable configuration of the timer requires only two external components. It is shown in **fig. 2A** (the capacitor on pin 5 is optional).

A resistor (R_A) is connected from V_{CC} to the discharge pin (pin 7) and threshold pin (pin 6). A capacitor is then connected from pins 6 and 7 to ground. The values of R_A and C will determine for how long the output remains high.

Initially, the output is low and the discharge transistor is turned on. This essentially shorts the timing capacitor C . Therefore, the threshold comparator input is at zero volts. When the trigger comparator

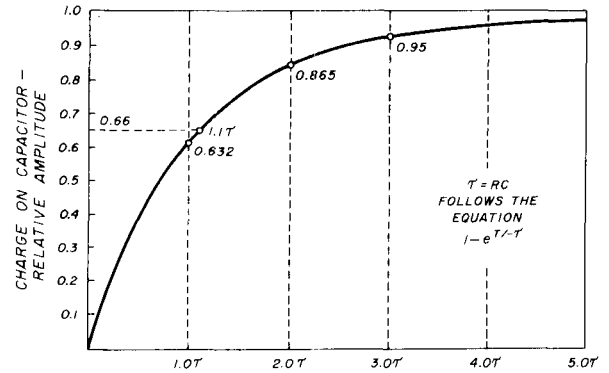


fig. 3. Diagram of the normal RC time-constant curve. When connected as a monostable, the output pulse width from the timer is determined by the time it takes the capacitor to charge between zero and 66 per cent of the full charge.

receives a trigger that is less than $1/3 V_{CC}$, it causes the flip-flop to switch. The output goes high and the discharge transistor turns off. When this happens, the timing capacitor starts charging to V_{CC} via R_A . As soon as the charge on the capacitor reaches the threshold voltage level ($2/3 V_{CC}$), the threshold comparator triggers the flip-flop. This drives the output stage low and turns on the discharge transistor, which discharges the timing capacitor, and the timer is back to its initial condition. **Fig. 2B** shows the waveforms on the timer during this time.

triggering

Due to the nature of the trigger circuitry, the trigger comparator will trigger the flip-flop whenever the trigger voltage drops below $1/3 V_{CC}$. For proper timing, the trigger level must return to a voltage level greater than $1/3 V_{CC}$. This is because the trigger comparator has overriding control of the flip-flop. Should the trigger input be held low for a period longer than the timing cycle, the output will remain high, without regard to the voltage on the threshold comparator.

reset function

The 555 has a reset pin for applications that require an abort signal. That is, it may be necessary to interrupt a timing period or to inhibit a trigger. The reset control (pin 4) is normally high. If the reset is held greater than 1.0 volt, the 555 will function normally. However, if pin 4 is held below 0.4 volt the output will be held low. When the timer output is high and the reset goes low, the output will turn off immediately. If the reset pin is between 0.4 and 1.0 volt, the timer is in no man's land; some devices may reset, some may not. When using the reset function, it is important to have the reset less than 0.4 volt. This level is guaranteed to cause the timer to reset. To prevent possible noise spikes from causing an unwanted reset, pin 4 is normally connected to the V_{CC} pin when not being used.

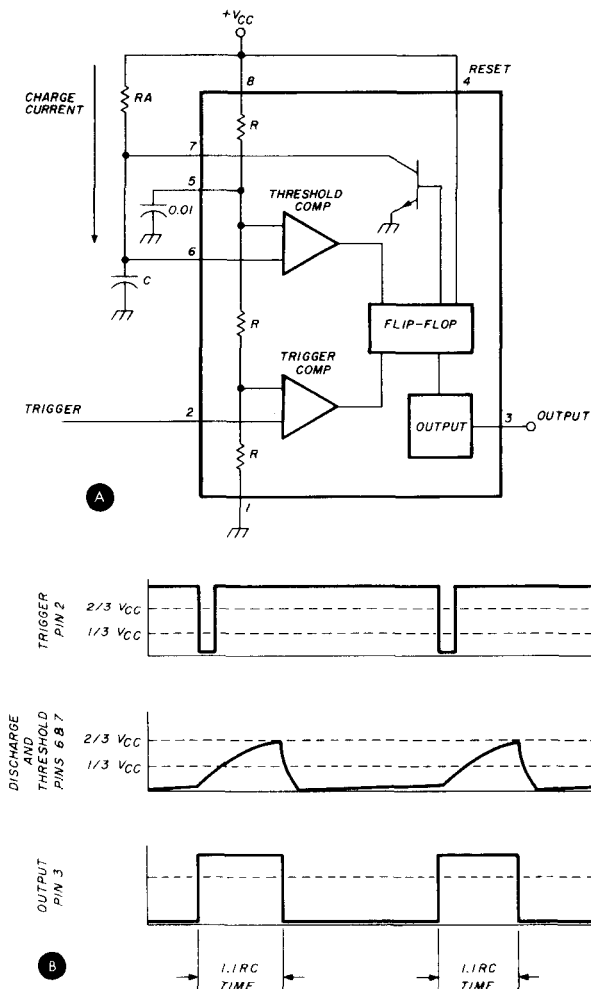


fig. 2. Configuration of the 555 timer for use as a monostable multivibrator and the associated waveforms (B). The negative-going pulse applied to the trigger input causes the internal flip-flop to change states, generating the output pulse.

calculating pulse width

When describing the operation of the 555 timer in the monostable operation, I mentioned that the values of R_A and C determined the time the output stayed high. The voltage on C must charge to $2/3 V_{CC}$. Fig. 3 shows the normal RC charge curve. As shown, the voltage rises from 0 to 100 per cent in five RC time constants (τ). The 66.6 per cent ($2/3$) point occurs at 1.1τ , or

$$T = 1.1 RC \quad (1)$$

where

T is in seconds,
 R is in ohms
 C is in farads

changing the pulse width in the monostable mode

The threshold control voltage on pin 5 is an important feature of the NE555 timer. By imposing a voltage on pin 5, the internal comparator reference levels, the timing can be varied. For example, if one-half the supply voltage were placed on pin 5 (normally held at $2/3 V_{CC}$), the timing capacitor would charge only to one-half V_{CC} before the threshold trip level is reached. The time required to charge the capacitor can be found by observing how many time constants it takes for the capacitor to charge to 50 per cent using the equation $T = \ln(1 - \frac{V_5}{V_{CC}}) RC$ or by using fig. 3. With the voltage on pin 5 equal to $0.5 V_{CC}$, the new timing equation is $T = (\ln 0.5) RC = 0.693 RC$.

You must remember that the trigger threshold is also affected by changes on the voltage level at pin 5. In the example above, the trigger threshold is now lowered to one-quarter V_{CC} (halfway below the voltage on pin 5). In order to trigger, the trigger pulse must now go below one-quarter V_{CC} . This feature of the timer opens a multitude of application possibilities such as pulse width modulators, voltage-controlled oscillators, and so forth.

As can be seen, any variations on pin 5 will cause a change in timing. For that reason it is recommended that a small bypass capacitor (about $0.01 \mu F$) be used on pin 5. This will increase noise immunity of the timer to high frequency trash that could cause timing errors by modulating the threshold trip levels.

astable operation

To configure the 555 timer in the astable or oscillatory mode requires only a slight modification to the monostable configuration. Fig. 4A is the schematic of a 555 timer in the basic astable mode. It requires two resistors and a timing capacitor. Assume that the charge on the timing capacitor is charging toward V_{CC} through R_A and R_B . The output is high

and the discharge transistor is off. When the capacitor charges to the threshold trip level ($2/3 V_{CC}$) the output goes low and the discharge transistor turns on, shorting pin 7 to ground. The capacitor now begins to discharge through R_B toward ground. But as soon as the capacitor discharges to $1/3 V_{CC}$ (the trip level of the trigger comparator), the output again goes high, the discharge transistor turns off, and the

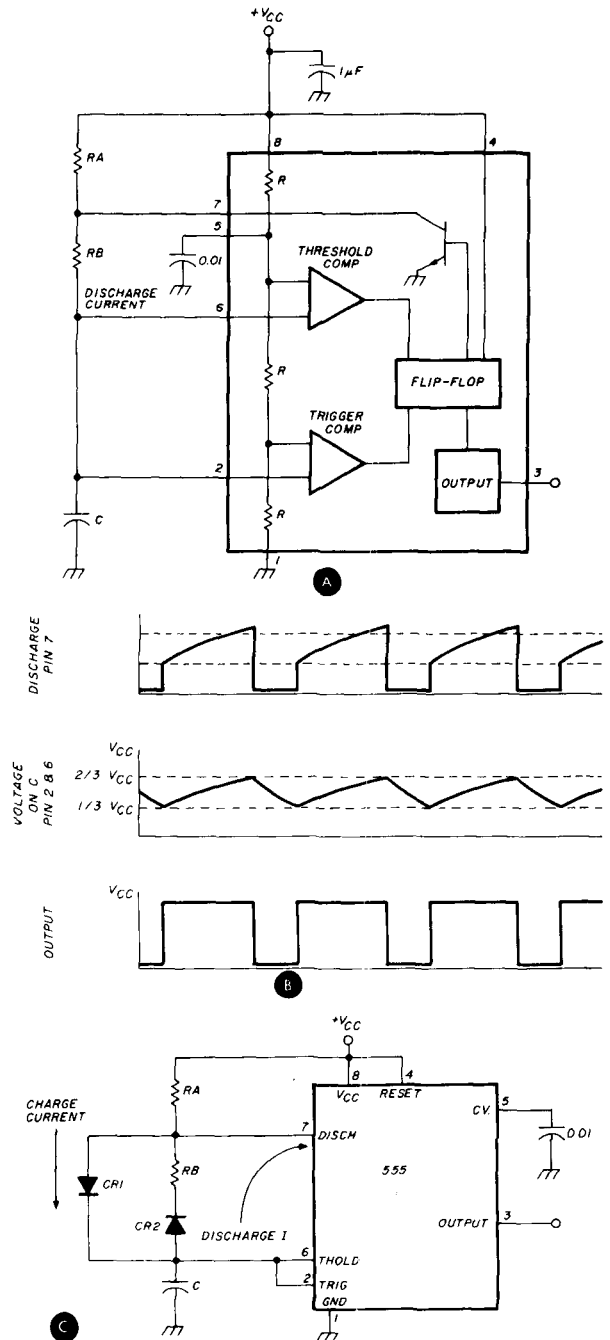


fig. 4. Schematic diagram of the 555 connected as an astable multivibrator and the waveforms at different points in the circuit (B). In applications where a 50 per cent duty cycle is required, the circuit shown in (C) can be used. In this case, CR1 effectively shorts out R_B during the capacitor charge time.

capacitor starts charging through R_A and R_B again, creating an oscillator. **Fig. 4B** shows the waveform in the astable mode.

calculating frequency

The time required to charge from $1/3$ to $2/3 V_{CC}$ is $0.671 RC$. The charge path is through $R_A + R_B$. This is the period of time that the output is high, or

$$T_1(\text{High}) = (R_A + R_B) C \quad (2)$$

During the discharge time the output is low. The time required to discharge from $2/3$ to $1/3 V_{CC}$ is also $0.671 RC$. But the discharge path is through R_B only, so

$$T_2(\text{Low}) = 0.671 (R_B) C \quad (3)$$

The total period of oscillation is then:

$$T_{TOT} = T_1 + T_2 = 0.671 (R_A + 2R_B) C \quad (4)$$

and the frequency

$$F = \frac{1}{T_{TOT}} = \frac{1}{.671 (R_A + 2 R_B) C} \\ = \frac{1.49}{(R_A + 2 R_B) C} \quad (5)$$

The duty cycle is given by:

$$D = \frac{R_A}{R_A + 2 R_B} \quad (6)$$

Since the charge and discharge paths are different, the duty cycle cannot be less than 50 percent. In some applications, this may cause a problem. With a slight modification to the basic circuit, the 555 output can be made a square wave. **Fig. 4C** details the circuit configuration for a 50 per cent duty cycle when $R_A = R_B$.

In this circuit, CR1 shorts R_B and the charge time is $0.671 R_A C$. The discharge path is still through R_B and does not change. The series diode, CR2 is optional to match the charge and discharge paths. With the diodes in the circuit the formulas for frequency and duty cycle become:

$$F = \frac{1.49}{(R_A + R_B) C} \quad (7)$$

$$\text{Duty Cycle} = \frac{R_B}{R_A + R_B} \quad (8)$$

With this configuration, the timer is capable of generating duty cycles from 5 to 95 per cent.

supply voltages

In selecting supply voltages, note that the 555 timer is guaranteed to operate from 4.5 volts to 16 volts. Because the threshold levels work on a ratio, the supply voltage will not change the timing calculations. The timer has a "totem pole" output structure

capable of switching high levels of load current. As a result, large current spikes can develop on the supply line. This momentary loading effect can cause a degree of timing error because of changes in charging current. It can also cause noise glitches and false triggering in TTL circuits. To eliminate this phenomenon, it is necessary to bypass the supply line to ground with a capacitor. The size of the bypass required generally depends on the load to the timer. Values range from 0.1 to $10 \mu F$, or more. The bypass capacitor should be as close to the device as possible.

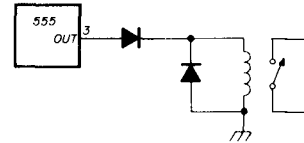


fig. 5. When driving an inductive load, a protective diode is required to prevent the inductive kick from latching up the output of the timer.

Bypassing the control voltage pin (pin 5) is generally considered good design practice. As mentioned earlier, the value is not critical, but the capacitor should be as close to the device as possible. Typically, the bypass capacitor is $0.01 \mu F$.

capacitors

The timing capacitor size is virtually unlimited; but, the type of capacitor is important. Ceramic disk capacitors are usually unsuitable. They generally are not stable enough to operate in an RC timing circuit. Electrolytics usually have very high leakage rates and would cause drastic timing errors. The Signetics data sheet lists several acceptable types of capacitors, including silver mica, mylar, polystyrene, and tantalum. The smaller the timing capacitor used, the more

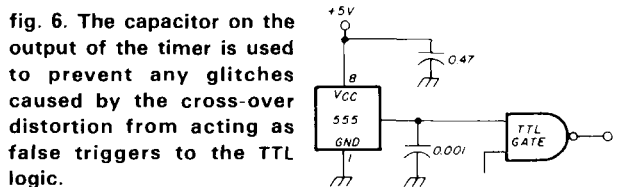



fig. 6. The capacitor on the output of the timer is used to prevent any glitches caused by the cross-over distortion from acting as false triggers to the TTL logic.

apparent effect stray capacitance can have on the timing. The larger the capacitor, the more expensive the capacitor is. This is particularly true of the low-leakage types. For long delays, the capacitor has to be very large, but there are ways of getting long delays without using big capacitors.

resistors

There are certain maximum and minimum values

fig. 7. In this example of ac triggering, the trigger pulse must be less than the duration of the output pulse from the timer. The duration of the trigger depends upon the RC time constant of the components.

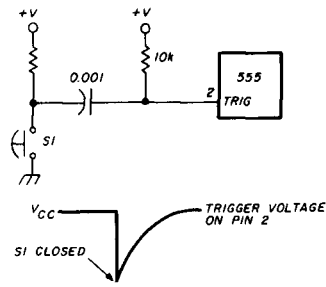

for the resistors. The threshold comparator requires $0.25 \mu\text{A}$ of current to trip the output. Considering worst case, the resistor must be able to supply $0.25 \mu\text{A}$ of current for the comparator and still charge the capacitor to $2/3 V_{CC}$. To calculate the maximum resistance, the IR drop must not exceed $1/3 V_{CC}$ with $0.25 \mu\text{A}$ current flow, or

$$\begin{aligned} IR \text{ drop} &= V_{CC} - V_{CAP} \\ &= V_{CC} - 2/3 V_{CC} \\ &= 1/3 V_{CC} \end{aligned}$$

The maximum resistance between V_{CC} and pin 6 is defined as

$$R_{MAX} = \frac{V_{CC} - V_{CAP}}{\text{threshold current}} \quad (9)$$

With a 15-volt supply

$$\begin{aligned} R_{MAX} &= \frac{15V - 10V (2/3 V_{CC})}{0.25 \times 10^{-6}} \\ R_{MAX} &= \frac{5}{0.25 \times 10^{-6}} \\ &= 20 \text{ megohms} \end{aligned}$$

With a 5-volt supply


$$\begin{aligned} R_{MAX} &= \frac{5V - 3.33V}{0.25 \times 10^{-6}} \\ &= \frac{1.67}{0.25 \times 10^{-6}} \\ &= 6.6 \text{ megohms} \end{aligned}$$

When using large resistors, capacitor leakage can cause larger timing errors because it represents a larger percentage of the total charge current available. Excessive capacitor leakage current will also cause an IR drop and not allow the threshold comparator to reach $2/3 V_{CC}$.

The minimum value of resistance is determined by the current that the discharge transistor can supply. The discharge transistor is internally current limited to about 35 mA. The discharge transistor must supply two loads. The first is the current through R_A . This should be reduced so that the second path into the capacitor (or through R_B) carries most of the load. As a general rule, R_A should not be less than 5k ohms. R_B should not be less than 3k ohms.

control voltage changes

As mentioned earlier, the control voltage pin (pin 5) is normally bypassed to ground by a $0.01\text{-}\mu\text{F}$ capacitor. By imposing a voltage on this pin, it was shown that the timing can be changed since the threshold level is changed. The voltage level on pin 5 can be lowered to about 45 per cent of V_{CC} when operating the timer in the monostable mode. The trigger level is also changed because it will equal one half the voltage on pin 5, and a certain minimum volt-

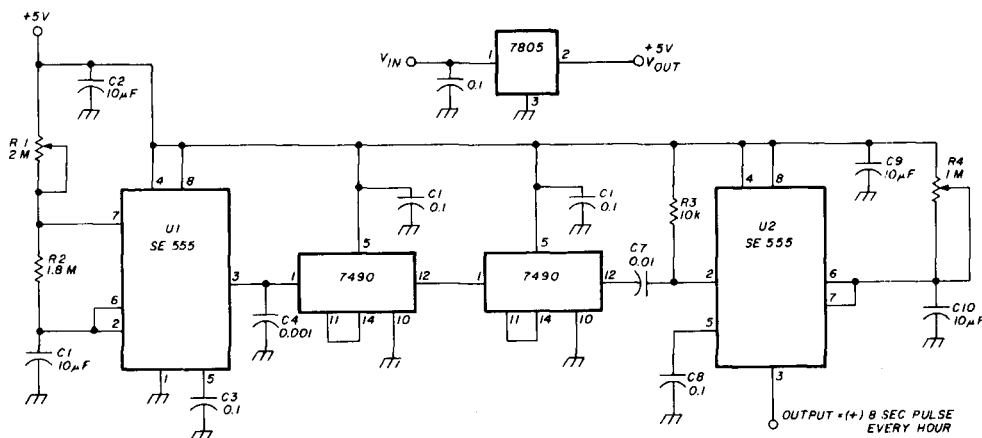

U1 — frequency = $1/36 \text{ Hz}$
 $R1 = R2$, let $C = 10 \mu\text{F}$
 with $F = \frac{1.49}{(R1 + 2R2)C}$

Since $R1 = R2$, $F = \frac{1.49}{3R \cdot C}$

therefore $R = \frac{1.49 \cdot 36}{10 \cdot 10^{-6}} = 1.8 \text{ megohms}$

U2 — 8-second output pulse
 let $C = 10 \mu\text{F}$

therefore $R = \frac{T}{1.1C} = 0.727 \text{ megohms}$

fig. 8. Long time delays can be generated by cascading timers with other count-down devices. In this example, the basic timer, U1, runs at about 0.028 Hz, is divided down by 100, and then used to trigger another timer configured as a monostable. The output is an eight-second pulse, once every hour.

age level must be maintained on the trigger comparator reference. If the voltage drops below 45 per cent on pin 5, the timer becomes more sensitive to noise because the trigger voltage nears ground. At the other extreme, the control voltage on pin 5 should not exceed about 90 per cent of V_{CC} since the timing capacitor must charge to V_{CC} . Exceeding this voltage range in the monostable mode may cause timing error, false triggering, or other problems.

In the astable mode, the voltage level changes on the control voltage pin can be used to change the oscillating frequency about ± 25 per cent and still remain linear. Changes greater than this will still cause the frequency to change, but linearity decreases due to the RC timing circuit.

Before examining some specific circuits, there are several idiosyncracies of the timers that can cause problems unless you are aware of them.

Temperature. The timer exhibits a small negative temperature coefficient (50 ppm/C°). This can cause small timing changes in the monostable mode and frequency drift in the oscillator mode. In critical applications, R/C values can be selected which have positive coefficients, with the net result a lower drift. Since the astable mode relies on both trigger and threshold levels, the drift from temperature is usually higher than when in the monostable mode. An

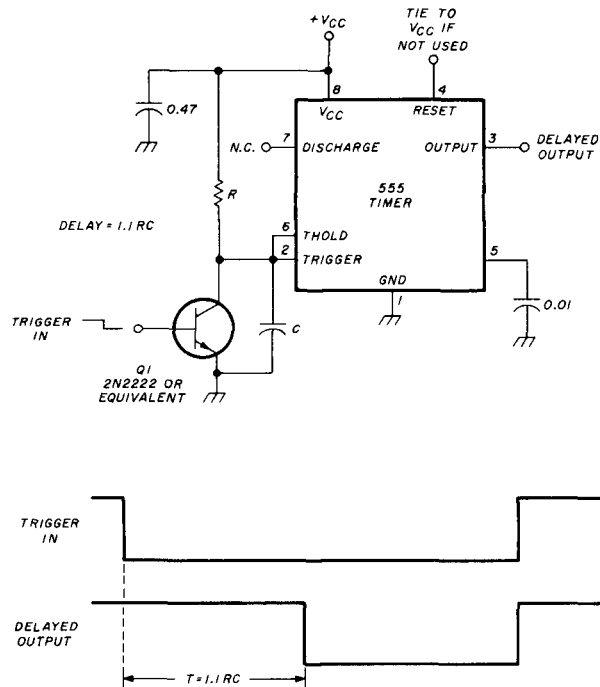


fig. 9. In this time delay circuit, the timing capacitor is effectively short circuited by the normally conducting transistor. A negative-going trigger cuts off the transistor, allowing the timer to operate and provide a pulse after the delay time.

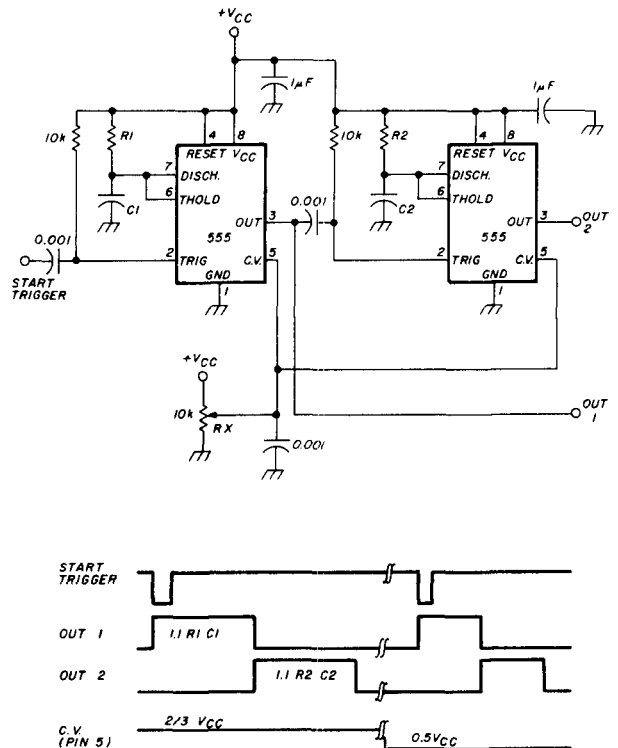


fig. 10. This version of a sequential timer uses the control voltage input to change the pulse width of the output pulses, though they do remain in the same ratio.

important point to remember when working with the timer (for that matter any IC) is that power dissipation of the device should never be exceeded. Power causes heat, and excessive heat will destroy the device. The 555 can handle about one-half watt of power at room temperature. This power rating is lower when the device is operated at higher temperature.

Output. If a negative voltage (with respect to pin 1) is applied to the output of the timer, the 555 could latch up. This can happen when the 555 is used to drive an inductive load, such as a relay. To prevent this inductive kick back from latching the timer, a diode in series with the output should be used. Fig. 5 shows a schematic of a timer being used to drive an inductive load.

The output drive capability of the timer is 200 mA. Because of the output structure's high current capabilities, and fast rise and fall times, the timer exhibits crossover distortion. This glitch can cause false triggering of TTL circuits. By providing a capacitive load, the timer output is slowed to a point that the glitch does not occur. A capacitor of about 1000 pF from the output to ground will eliminate any false triggering of the TTL circuit (see fig. 6).

Triggering. I've stated that in the basic monostable mode the trigger must go below $1/3 V_{CC}$ (or one half

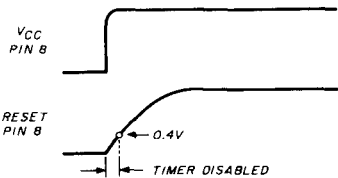
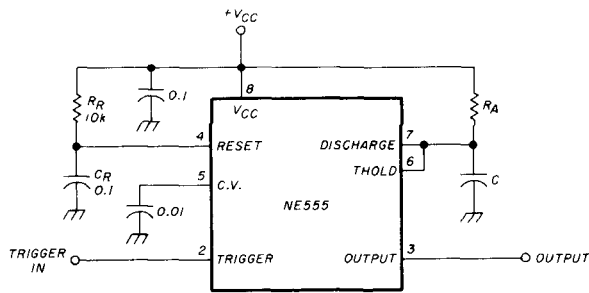


fig. 11. With the capacitor attached to the reset input, the timer cannot produce an output when power is initially applied. After C_R has charged, a trigger will produce the desired output pulse.

the voltage on pin 5) and return high before the end of the timing cycle. One way to generate such a trigger is to ac-couple the trigger. Fig. 7 shows such a circuit. The duration of the trigger pulse depends on how long the RC time constant is. The switch must return high again before the timer can be retriggered.

example circuit

The following circuits illustrate the use of the 555 timer (or 556 where two timers are used).

Long time delays. Because of the limitations of resistor size, long time delays (times greater than one hour) can be difficult to achieve using the basic circuit. One method of getting long delay times is shown in fig. 8. This particular circuit provides a positive 8-second pulse once each hour. U2 receives a trigger once each hour. The output of U2 is set for the desired pulse output by R_4 and C10. R3 and C7 provide the ac-coupled trigger. The 7490 counters are set to divide by 100. To provide one cycle per hour, the input must be clocked at a frequency of 1/36 Hz; U2 is then set to oscillate at 0.028 Hz. Note that C4 provides a deglitch filter on the output of U2. Because the timer must interface with TTL counters, the timers and counters use 5-volt supplies. The entire circuit can also be built by using a single 556 dual timer and one 74390 dual-decade counter. By changing the divider network or frequency of U1, it is possible to get an almost infinite combination of pulse outputs.

Simple time delay. Fig. 9 shows a simple circuit

that is a modification of the monostable operation. This circuit provides an output after some predetermined time. Initially, the trigger input to the base of Q_1 is high, causing Q_1 to conduct. Pin 2 of the timer is low and the output (pin 3) is high. When the input goes low Q_1 turns off, allowing the timing capacitor to charge. When C charges to $2/3 V_{CC}$, the output of the timer goes low. The output will stay low for as long as Q_1 is turned off. The reset pin can be used to keep the output low if required; otherwise it should be tied high.

Sequential timing. Fig. 10 shows another type of delay circuit. This is a sequential timer. The output of the first timer is used to trigger the second. The control-voltage pin is used to vary the sequence time, but the ratios remain the same. The timing diagram shows how the pulse width is reduced as the control voltage pins are lowered.

Delayed triggering. When power is first applied to the circuit shown in fig. 2 there is a chance that the trigger voltage on pin 2 will be lower than $1/3 V_{CC}$ and the timer will trigger. This may not be desirable. To prevent this initial trigger when power is turned on, the reset circuit can be modified as shown in fig. 11.

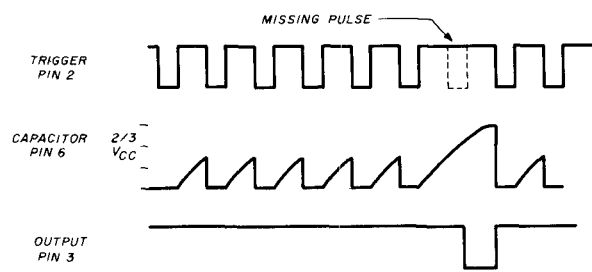
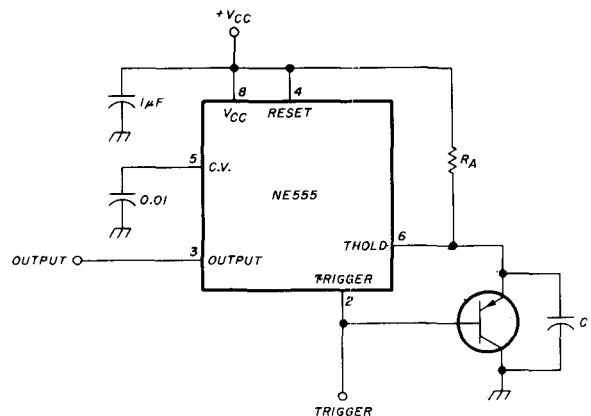


fig. 12. In the missing pulse detector, each trigger shorts the charging capacitor, preventing the output pulse from appearing. If a pulse is missing, the capacitor will charge to the required level, producing the output pulse which indicates the missing pulse.

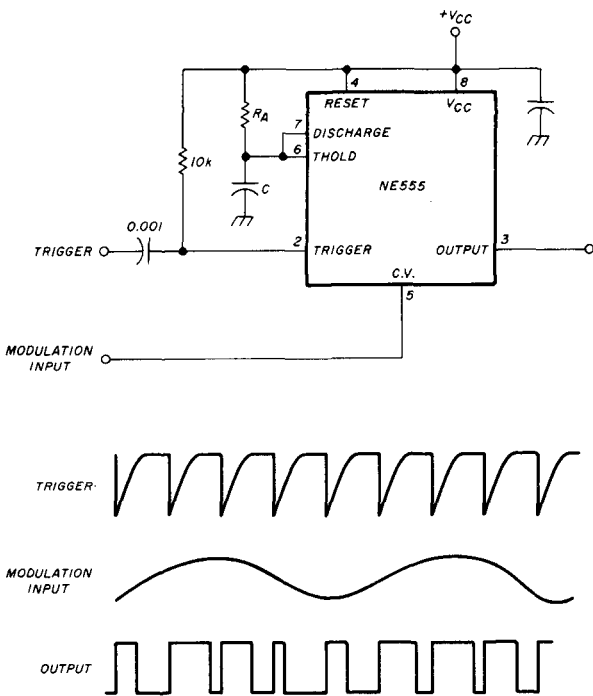


fig. 13. The modulation input is applied to the control voltage input, with the width of the output pulse varying as the amplitude of the modulation.

Pin 4 is held below 0.4 volt since C_R is fully discharged. When power is applied, the timer is held reset until C_R charges to above 0.4 volt.

Missing pulse detector. Fig. 12 shows an NE555 timer hooked up as a missing pulse detector. The trigger input also drives the base of a transistor. When a trigger occurs, the transistor conducts and shorts the timing capacitor before the timer can time out. If an input trigger is missing, the timer will time out and pin 3 will go low indicating a missing pulse. The values of R_A and C are set to be slightly longer than the period of incoming pulses.

Pulse width modulator. Fig. 13 shows a circuit which uses the control voltage pin to modulate the pulse width of an incoming clock signal. As the voltage on pin 5 varies, it changes the threshold level of the internal comparator and the pulse width of the output changes.

The examples covered were used to illustrate some of the possibilities of the 555 timer. The uses for this handy little IC could well take a whole book to illustrate. With an understanding of the basic operation, you can analyze timer circuits and design a circuit for your particular need. Who knows, you may come up with an original application and add your name to an evergrowing list of 555 timer circuit designers.

ham radio

SF

S-F Amateur Radio Services

(213) 837-4870

4384 KEYSTONE AVE., CULVER CITY, CA. 90230

the W6TOG* RECEIVER MODIFICATION KITS

INCREASE SELECTIVITY • IMPROVE SENSITIVITY
LOWER INTERNAL NOISE
IMPROVE NOISE BLANKER OPERATION
COMBAT BLOCKING FROM LOCAL SIGNALS

TS-520 KIT	\$27.50	FT-101 SERIES KIT ...	\$32.50
TS-520S KIT	32.50	FR-101 SERIES KIT ...	34.50
TS-820 & 820S KIT ...	34.50	FT-301 SERIES KIT ...	34.50
R-599 A/D KIT	27.50	FT-901 SERIES KIT ...	34.50

EXPLICIT INSTRUCTIONS MAKE MODIFICATION A CINCH

* IT'S MAGIC... IT'S "MAGICOM" PROCESSOR MODIFICATION KIT IMPROVES AUDIO PUNCH

IMPROVES PROCESSED SPEECH QUALITY

Converts TS-820 / 820S speech processor from RF compressor to RF clipper \$27.50
RF speech processor for TS-520 / 520S \$42.50
The "MAGICOM" RF processor module provides up to 6dB increase in output with smooth, clean, non-distorted audio and more penetration for those pile-ups.

ENDORSED BY W6TOG AND BIG GUN DXers WORLD WIDE

- ### * the W6TOG* INTERNAL ELECTRONIC KEYS
- FOR ALL AMATEUR TRANSMITTERS OR TRANSCEIVERS USING GRID BLOCK KEYING
- No holes mounting with TS-820 Series
 - Mounting options for TS-520, TS-520S, FT-101 Series, TR4 Series, T4X Series, T-599 Series and 32S Series.
 - C-MOS DESIGN — Dot and dash memory — full iambic or manual operation.
 - Simple installation \$49.50

THE S-F REJEKTOR FILTER


AN INTEGRATED CIRCUIT
ACTIVE BANDPASS FILTER
FOR PROCESSED RECEIVER AUDIO

- Separate active filter elements for CW and SSB audio output stage
- 8 ohm input and output impedance
- Headphone jack for convenience
- ON CW: from 500 hz to 100 hz, variable
- ON SSB: 2 KHz fixed bandwidth
- Rejects unwanted signal better than 60 dB
- Designed for today's transceivers or yesterday's older equipment \$49.50

*WELL KNOWN DXer WITH OVER 300 COUNTRIES CONFIRMED.

All prices postpaid - in Calif. add 6% sales tax - Mastercharge & Visa accepted

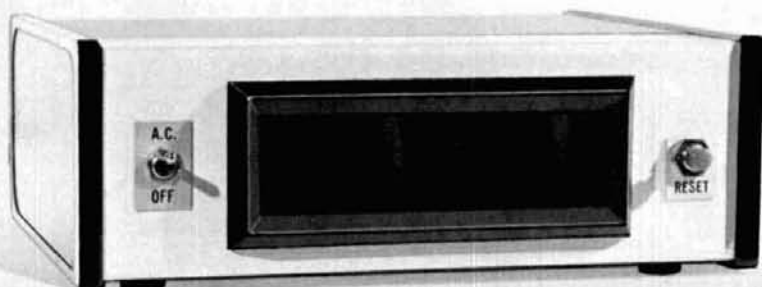SATISFACTION GUARANTEED OR MONEY REFUNDED



receiver digital display

A digital display
for your receiver
featuring 100-hertz readout,
single frequency input,
and provisions for
forward or
reverse tuning VFOs

The addition of a digital frequency display to a receiver goes a long way in enhancing operator convenience. It eliminates squinting at the fine markings found on the usual mechanical dial; and, at the same time, it provides an accurate frequency readout across an entire band without any need for recalibration between band ends. A bright digital display is not only easy to read, it also adds a touch of class to a perhaps otherwise ordinary station.

The circuit described in this article provides a stable, four-digit readout that includes the 100-kHz digit through the 100-Hz digit and will accommodate forward or reverse tuning VFOs at the flick of a switch. The resolution is greater than is usually provided by the typical receiver dial and is handy for returning to a particular frequency in a crowded band. In the interest of economy and simplicity, I did not in-

clude the MHz digits; they are easily read from the receiver band switch.

The technique used here¹ requires only a single connection to the receiver's VFO, which, in many modern receivers, is usually available at a connector on the rear panel, making it unnecessary to tamper with the receiver in any way.

theory of operation

In the case of a backward-tuning VFO, the frequency to be displayed is equal to a fixed frequency minus the VFO frequency. All that needs to be done is store the fixed frequency, subtract the VFO frequency, and display the result. In the case of a forward-tuning VFO, store the complement of the fixed frequency (subtract the fixed frequency from zero), add the VFO frequency, and display the result. These additions and subtractions are easily accomplished by using up/down counters and sequentially gating the frequency to be added to the up input and the frequency to be subtracted to the down input, each for the same fixed interval. The fixed frequency is usually crystal controlled and changes very little with time. Thus, measuring and storing it once during an initial calibration is usually adequate.

The price paid for the single interconnection and the simpler circuit is the need to perform a single calibration step each time a new band is used. The operator, using the receiver's internal calibrator, tunes to the bottom edge of the band and presses the calibrate (RESET) button on the display. No further adjustments are necessary. Depressing the


By Frank C. Getz, N3FG, 685 Farnum Road, Media, Pennsylvania 19063

CALIBRATE button stores the VFO frequency and displays all zeros. The operator may now tune up the band in the normal manner and read the display as the frequency above the bottom edge of the band. On the twenty-meter band, for example, 14.0253 MHz would be displayed as 025.3, with the 14 read from the receiver bandswitch. This calibration requires only a few seconds and is something that should normally be done anyway.

The circuit will handle either forward- or reverse-tuning VFOs, but, for the purpose of this explanation, assume a reverse-tuning VFO. Pressing the CALIBRATE button will clear the 74192 up/down counters and cause them to count the VFO frequency in the up direction for 100 milliseconds. The result is then stored in the 7475 latches. All subsequent count cycles will start at the number stored in the latches and count down for 100 milliseconds. Suppose the calibrate button were pressed when the receiver was tuned to exactly 14.0000 MHz. As a result, 5000 would be stored in the latches because the VFO was at 5.5000 MHz. Tuning the receiver to 14.0253 MHz would cause the receiver VFO to be 25.3 kHz lower, or 5.4747 MHz. The display counter would now start at 5000 and count down for a period of 100 milliseconds. The resulting count would be 5000 minus 4747, or 0253. By permanently enabling the decimal point to the left of the least significant digit (LSD), the display would show 025.3. Notice that by counting for 100 milliseconds, 54747 cycles are fed to the counters, but, since it has only four displays, the figure 5 is lost.

For a forward-tuning VFO, the sequence switch is placed in the reverse position. Pressing the calibrate button will then cause the first count cycle to be a down count with all subsequent cycles up counts.

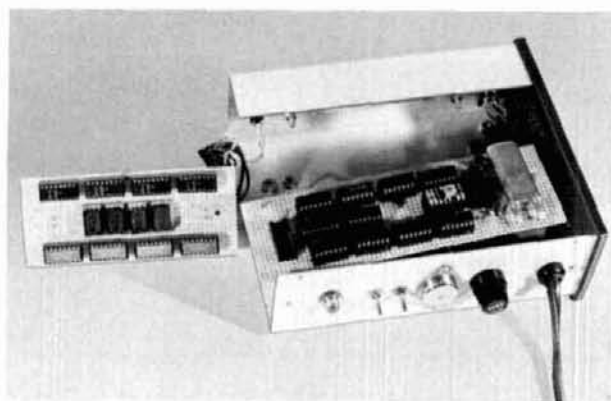Inside view of the assembled digital display. The smaller perf board is mounted right behind the bezel.



Inside view of the receiver digital display. The displays, up-down counters, and latches are mounted on the small board at the left. All other circuitry is mounted on the board inside the enclosure.

circuit description

One section of U1 serves as a 100-kHz crystal-controlled oscillator (see fig. 1). A divider chain, consisting of U2, U3, U4, and U5, drives a 7490 decade counter, U6 with one clock pulse every 100 milliseconds. The output of U6 is decoded by U7, with output pins 1, 3, and 4 each sequentially going low for 100 milliseconds of each measurement cycle. A jumper between pins 2 and 8 of U6 causes it to have only four output states rather than ten.

Assume the sequence switch is in the normal position. Pressing the CALIBRATE button causes the sequence of the next cycle to be *clear, count up, update*. This clears the counters to zero, counts for 100 milliseconds, and stores the final count in the 7475 latches. All succeeding cycles follow the sequence *load, count down, latch*. This loads the number stored in the latches into the counters, counts down for 100 milliseconds, and latches the final count into the displays.

U11 synchronizes the beginning and end of the calibrate cycle with the state of U7. Pressing S1 causes pin 5 of U11 to go high. As a result pin 9 goes high at the end of the current cycle and causes the next cycle to follow the calibrate sequence, in addition to resetting the first half of U11. At the end of the calibrate sequence, pin 4 of U7 goes high, resetting the second half of U11. U10 is the equivalent of a double-pole, double-throw switch and determines the count sequence, either up/down or down/up.

The remaining sections of U11 amplify and square-up the VFO signal. Three 4049 CMOS inverters are used. The first is biased to serve as an amplifier and functions well to above 6 MHz. This is fine for the large number of receivers with 5 to 5.5 MHz VFOs; but if your VFO operates at frequencies above this, a


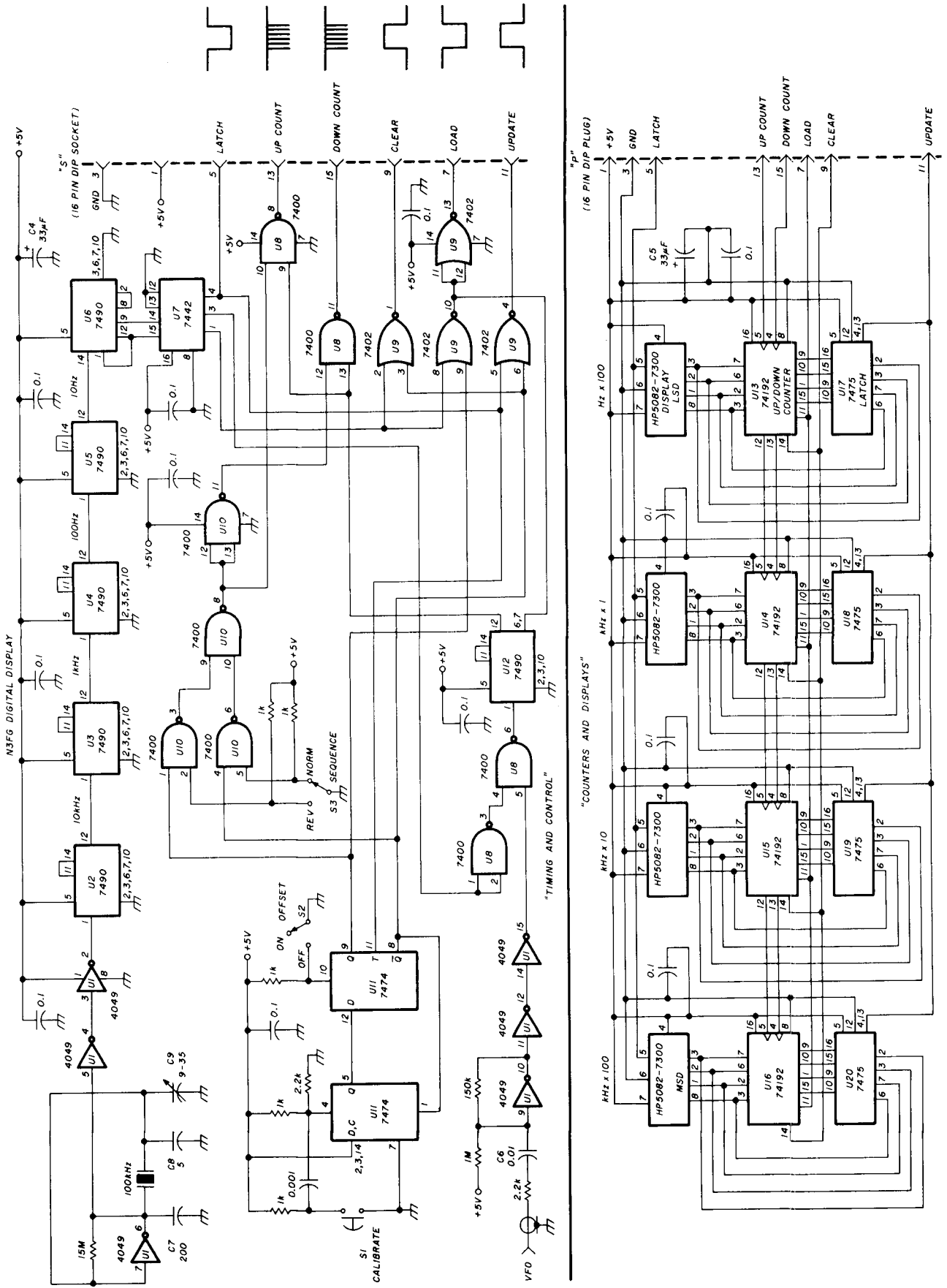


fig. 1. Schematic diagram of the complete digital display. C7 and C8 are silver-dipped micas; C9 is a small ceramic trimmer. Substitution of the LS-series ICs for the 7490s and 74192s will greatly reduce the power supply current permitting the use of a small regulator and transformer.

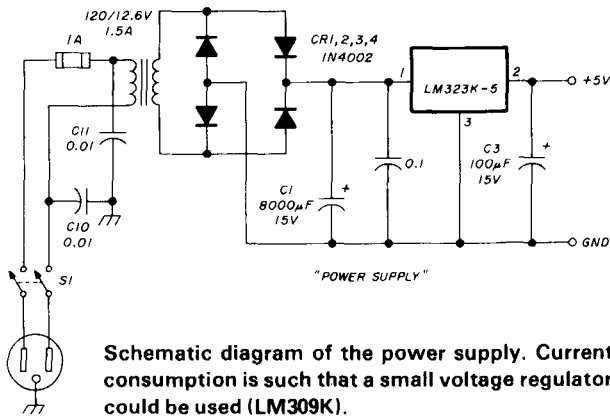

NEW — NEW — NEW from DATA SIGNAL

TOUCH TONE® MICROPHONE DataCoder 5



\$39⁰⁰

JUST LOOK AT THESE FEATURES:

- Tough "Mobile Environment" Microphone
- Positive-Action Tactile Keys
- High-Impedance Ceramic or 500-ohm Dynamic Cartridge
- Adjustable Tone Balance and Output Level
- "Positive Hold - Easy Lift" Hanger
- For Vehicle or Hand-held Portable Use
- Complete . . . Not a Kit . . . \$39.00

*Touch-Tone is a registered trade name of AT&T

MINIATURE ENCODERS DTM



MODEL DTM — Completely self-contained miniature encoder for hand-held portables. Only 5/16" thick. Three wire connection. Automatic PTT keying optional. With your choice of 12- or 16-digit Digitran keyboard.
Price DTM - \$39.00, DTM-PTT - \$49.00

SUB-MINIATURE ENCODERS



MODEL SME-1: Smallest available crystal-controlled Touch-Tone encoder, only 0.2" h x 0.5" w x 1.8" d. Complete with all connecting wires, mounts inside portable. **MODEL SME-2:** Only 1" square, mounts directly to pins on 12- or 16-digit Digitran keyboards. Price of either unit \$29.00 with choice of keyboards. SME-1 or SME-2 encoder only (less keyboard) \$24.00.

DATA SIGNAL, INC.

2403 COMMERCE LANE
ALBANY, GEORGIA 31707, 912-883-4703



Be sure to ask about
our new keyers and CW
memory for CW buffs.

JAN CRYSTALS

JAN CRYSTALS KEEP YOU ON THE AIR

- CB
- CB standard
- 2 meter
- Scanners
- Amateur Bands
- General Communication
- Industry
- Marine VHF
- Micro processor crystals

Send 10" for our latest catalog
Write or phone for more details

Jan Crystals
2400 Crystal Drive
Ft. Myers, Florida 33907
all phones (813) 936-2397

easy to charge

432 Yagis by K2RIW

IF YOU'RE SERIOUS ABOUT 432 . . .

... MEET RIW's 432-19

- 1st PLACE - EAST COAST VHF SOCIETY'S 1978 ANTENNA GAIN CONTEST
- 19 ELEMENTS, TANDEM-REFLECTOR*
- 12-MHz BANDWIDTH, 432-MHz CF
- INTEGRAL BALUN, 50 Ω TYPE N
- ALL ELEMENTS INSULATED FROM BOOM - NO GAIN LOSS FROM WEATHERING!
- 13-FT SELF-SUPPORTING BOOM
- WEIGHS ONLY 2-3/4 POUNDS!

*PATENT PENDING

MODEL 432-19 . . . \$59.95
441 MHz CF ATV MODEL 441-19 . . . \$59.95

New POWER DIVIDERS New

FOR FEEDING MULTIPLE ANTENNAS
420 - 450 MHz - RUGGED - WEATHERPROOF

- 2-WAY SPLIT, MODEL 4PD2 . . . \$24.95
- 4-WAY SPLIT, MODEL 4PD4 . . . \$29.95
- 8-WAY SPLIT, MODEL 4PD8 . . . \$49.95

PLEASE ADD \$2.00 PER ITEM SHIPPING/HANDLING. N.Y.C. RESIDENTS: ADD SALES TAX.

riw PRODUCTS

BOX 191, BABYLON, N.Y. 11702

YOU'VE SEEN THE MAGAZINE ARTICLES

Here's what you can expect from the **DX ENGINEERING RF Speech Processor**

- 6 db INCREASE IN AVERAGE POWER
- MAINTAINS VOICE QUALITY
- IMPROVES INTELLIGIBILITY
- NO CABLES OR BENCH SPACE REQUIRED
- EXCELLENT FOR PHONE PATCH
- NO ADDITIONAL ADJUSTMENTS — MIKE GAIN ADJUSTS CLIPPING LEVEL
- UNIQUE PLUG-IN UNIT — NO MODIFICATIONS REQUIRED

This is RF Envelope Clipping—the feature being used in new transmitter designs for amateur and military use.

Models Now Available
Collins 32S, KWM-2 . . . \$ 98.50 ea.
Drake TR-3, TR-4, TR-6, TR-4C,
T-4, T-4X, T-4XB, T-4XC \$128.50 ea.
Postpaid — Calif. Residents
add 6% Tax

Watch for other models later!

DX Engineering

1050 East Walnut, Pasadena, Calif. 91106

Introducing Kantronics' Field Day TRADEMARK

Morse Code/teletype reader and code speed display:

Kantronics' Field Day Morse Code/teletype reader and code-speed display reads code signals right off the air. Its powerful microcomputer system picks out signals, computes their speed, and reads even sloppy copy up to 80 words per minute!

1. Flies through the air with the greatest of ease.

Field Day is simple to use. You plug it into your station receiver just as you would a set of headphones.

Code and teletype conversations are converted from dots and dashes to standard alphanumeric text. The text advances across 10 big half-inch displays, and lab tests show that even the fastest CW is easily readable.

Field Day displays incoming or outgoing code speeds for you at the touch of a button. An accurate code speed-sampling program shows the speed right on the front panel. Everything is enclosed in a single, lightweight package that's small enough to fit in with the rest of your station.

2. Pay a little, get a lot.

In addition to a highly superior code-reading program and unique "on-board" speed display, **Field**

Day has the specifications that make it a truly great code reader.

Modes: CW, RTTY and speed display. **Speed Range:** 3-80 WPM. **RTTY Speeds:** 60, 67, 75 and 100 baudot. **Code Display:** 10 alphanumeric displays. **Special Characters:** AS, AR, SK, BT, /, ?, (,), ", , comma, period, colon, semicolon, "understood," "attention," and "error." **Filtering:** Active, 750 Hz center, 200 Hz bandwidth. **Input Impedance:** 1,000 ohms. **Power Requirements:** 117 Vac, 20 watts. **Dimensions:** HWD 3.44" by 8.50" by 9.25". **Warranty:** Limited, one year parts and labor. **Price:** \$449.95 Shipments after 3/1/79.

3. C'mon, take a test drive.

Check with these Authorized **Kantronics** dealers for more information on the **Field Day** Morse Code/teletype reader and code-speed display:

Associated Radio / Kansas City, **Barry** / New York, **Bill's** / Carbondale, IL, **Brodie** / Moore, OK, **Burghardt** / Watertown, SD, **Burstein-Applebee** / Kansas City, **Cohoon** / Trenton, KY and Austintown, OH, **Fontana Electronics** / Fontana, CA, **H-E-P** / Aurora, CO, **Hirsch** / Williamsville, NY, **Long's** / Birmingham, **Madison** / Houston, **MidCom** / St. Louis, **Omar** / Durand, MI, **Omaha Radio Center** / Omaha, **Queen City** / Cincinnati, **Radio World** / Oriskany, NY, **Spectronics** / Oak Park, IL, **Tracy** / Fort Worth.

KANTRONICS
The Lightweight Champs.

(913) 842-7745
1202 East 23rd Street
Lawrence, Kansas 66044


Our Smart Machine TRADEMARK reads sloppy copy.

COMPACT ENCLOSURE.
In inches, FIELD DAY is only
3.44 high by 8.50 wide by 9.25 deep!

SPEED DISPLAY.
Special program computes
received and transmitted
code speeds.

RTTY COPY.
Control functions in back
for copying at
the standard baudot speeds.

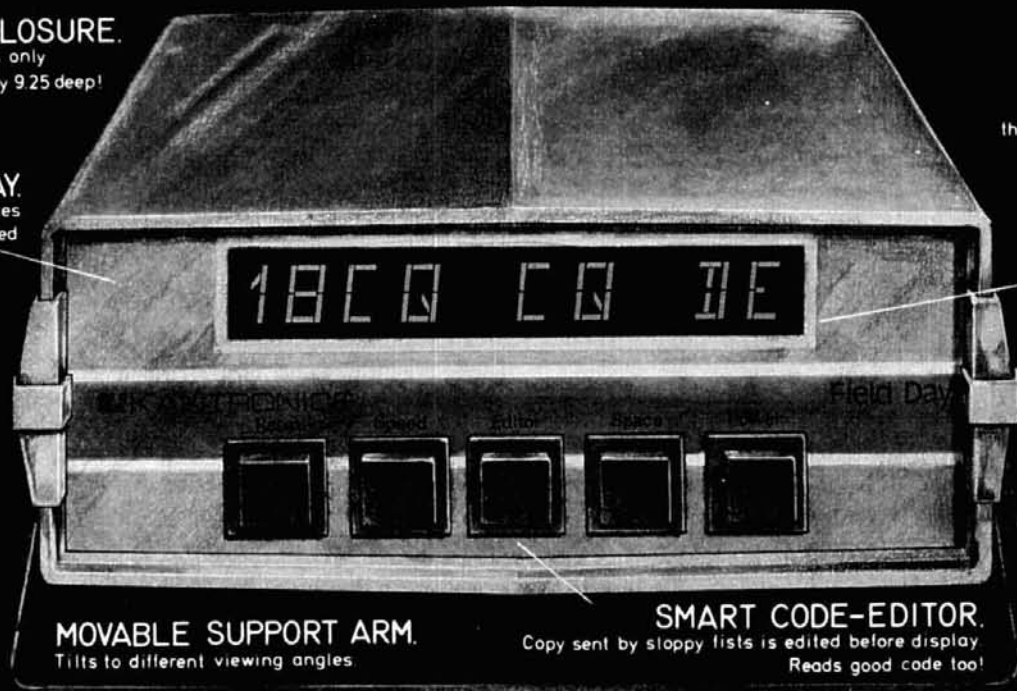**ON-BOARD
CODE DISPLAY.**
No need to tote around
a TV set to copy code.



MOVABLE SUPPORT ARM.
Tilts to different viewing angles

SMART CODE-EDITOR.
Copy sent by sloppy lists is edited before display
Reads good code too!

new approach for a 1-MHz oscillator

A reversion to
basic oscillator concepts,
this oscillator
was built
with optimized circuitry
for each stage

Most of the oscillators built by Amateurs use a single transistor to perform several functions. However, the basic principles of operation are somewhat a mystery. The original analysis of the oscillator, done in the 1920s, showed that it could be divided into separate stages (see fig. 1). By actually building separate stages, you can obtain a better understanding of oscillator operation. This article presents an oscillator built using those basic concepts.

circuit description

The RCA CA3028 differential amplifier, shown in fig. 2, is used as an amplifier and limiter. Feedback, for the actual oscillator, is the limited sinewave from the pin 6 output. Note that this is a noninverting configuration. The amount of feedback is controlled

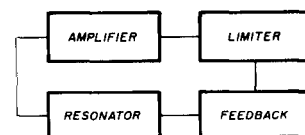


fig. 1. Diagram of the basic stages needed for an oscillator.

by the 5-kilohm pot connected to pin 6. Feedback is injected into the quartz-crystal resonator. Because the crystal acts as a bandpass filter, the output will be a sinewave, in this case at 1 MHz. However, the crystal cannot be connected to the limiter without a penalty. The input impedance of a limiting differential pair is nonlinear. To overcome this problem, the crystal must be isolated from the limiter. This is done by connecting a common-base amplifier between the resonator output and the amplifier input. The com-

By Thomas V. Cefalo, WA1SPI, 29 Oak Street, Winchester, Massachusetts 01890

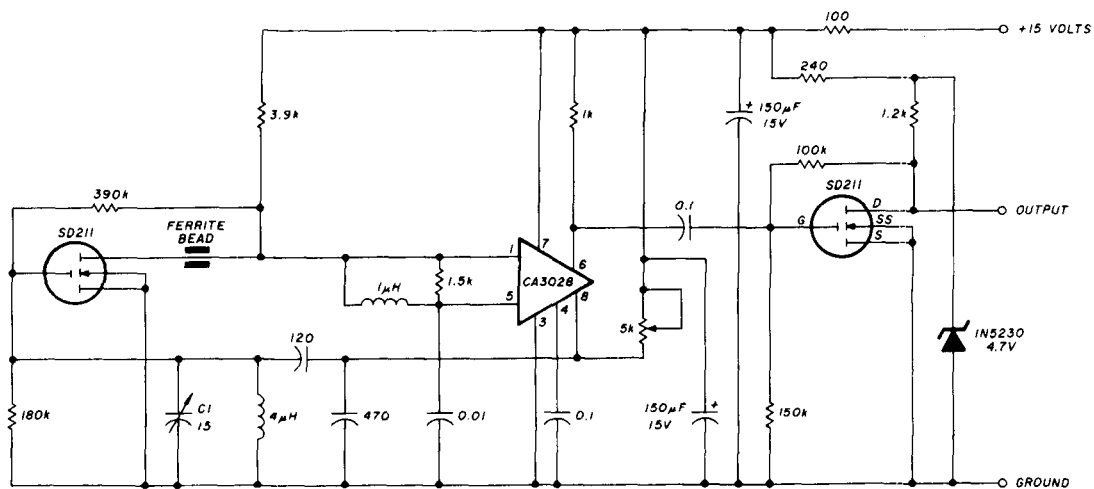


fig. 2. Schematic of the 1-MHz oscillator built using separate stages for each function rather than combining functions into a single device. All resistors, except R1, can be 1/8 watt; R1 is a 1/4-watt resistor. The power requirement is 36 mA at 15 volts.

mon-base amplifier provides a constant impedance load for the crystal. Because the output of the limiter is fixed, regardless of its input, and because the resonator also sees a constant impedance, the sine-wave at the collector of the common-base stage has

should oscillate. If it does not, increase the feedback until oscillation occurs at 8 volts. After the feedback is correctly adjusted, connect the output to a counter and adjust the crystal frequency with the small trimmer.

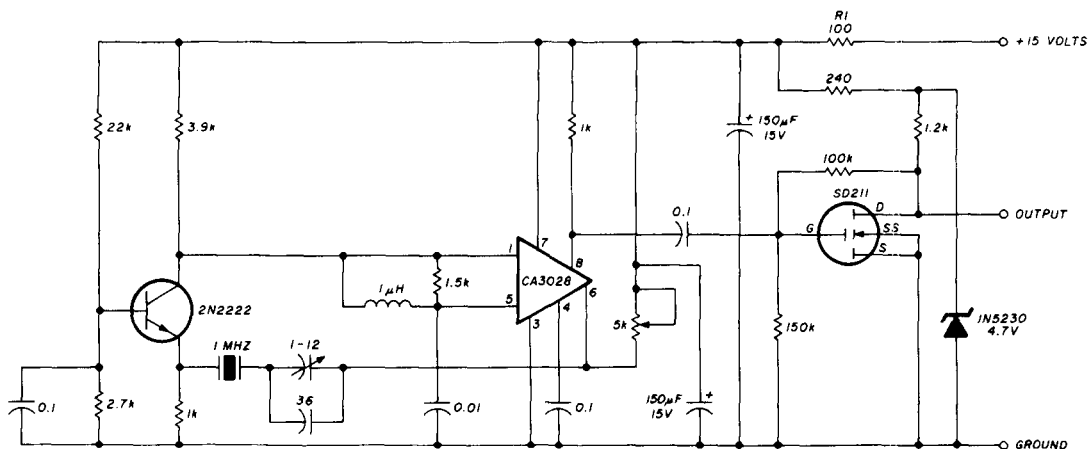


fig. 3. Diagram of a 40-meter LC-tuned VFO built using the same guidelines as the crystal oscillator.

a constant amplitude. This signal completes the loop by driving the limiter. The output is taken from pin 8, the unused inverting output. The output from the CA3028 is a limited sinewave. To make the output a clean square wave, an SD211 DMOS FET was used. The FET is driven into saturation, squaring the signal.

construction and adjustment

The oscillator was built on a piece of perforated board and housed in a 10 × 5.4 × 4.3 cm (4 × 2-1/8 × 1-5/8 inch) mini-box. Adjust the 5-kilohm variable resistor until the circuit goes into oscillation. Next, reduce the power supply voltage to zero and slowly increase the voltage. At 8 volts, the circuit

The output is a 4-volt peak signal with a rise time of 100 ns. The variation in frequency, at 1 MHz, is 0.5 Hz over a 1-second interval. This is due to the quality of the crystal and thermal effects. This variation can be reduced if a higher-quality crystal is used. Also, the environment can be temperature controlled with an oven or the use of insulation. The final frequency error was adjusted to 0.05 Hz. My present application for the oscillator is a time base in a frequency counter. However, you could modify the circuit to act as an LC-tuned VFO (see fig. 3). Since the SD211 FET amplifier is inverting, feedback is taken from pin 6, the inverting output.

ham radio

novel method for matching input impedance of grounded-grid power-amplifier tubes

When I was thinking about driving a tube power amplifier with my 20-watt transistorized ssb general-coverage transceiver, I noticed that uniform matching from the 50-ohm output of the transceiver into the amplifier between 1.8 and 30 MHz might present some problems. A circuit with a grounded cathode tube wasn't too attractive, because of the required neutralization and the various voltages needed for a tetrode or pentode. So I decided to use one of the modern grounded-grid tubes of the 8873-8875 series. Their input impedance is in the vicinity of 100 ohms, but since it's a dynamic input, impedance varies as drive level changes.

It's therefore highly recommended to use at least one tuned circuit between the exciter and the cathode connection of the tube to store energy and stabilize the dynamic input impedance. Since this tuned circuit requires retuning when the frequency is changed more than 10 per cent, such an arrangement would be highly impractical.

Note that this energy-storing circuit, although sometimes used in a pi configuration, does not really suppress exciter harmonics. Standard practice is to have enough harmonic suppression already in the exciter, and a 50-ohm output is provided from the exciter.

matching network

With these things in mind, and using a calculator to determine elliptical filters, I constructed a matching network that provides perfect matching and ideal energy storage between 1.8 and 30 MHz (fig. 1). This is a bandpass filter, which has Chebyshev response in both bandpass and stop-band areas. It provides a constant impedance match over the fre-

quency range of between 1 MHz and 60 MHz. This is important, because even high-order harmonics must be properly terminated, otherwise high transient voltages can be developed in the driver stages.

If you consider the fact that the frequency range between 1.8 and 30 MHz, on the basis of individual filters, must be split into at least seven segments

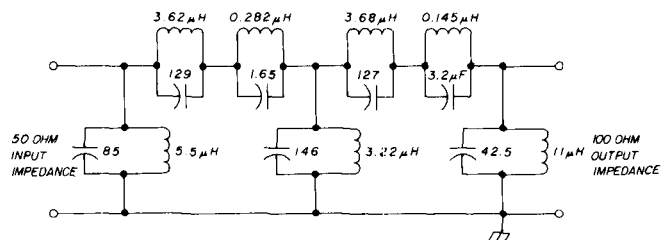


fig. 1. Simple network for constant impedance matching and ideal energy storage between a low-level driver and power amplifier using tubes in the grounded-grid configuration. System is a bandpass filter with Chebyshev response in both bandpass and stop-band regions. Frequency range is 1-60 MHz. See text for recommended components.

(and assuming three components per segment), the total number of segments would be twenty-one, while here only fourteen are required.

components

All component values are included in the schematic. You must use 500-volt mica capacitors together with either air-wound coils or coils with suitable ferrite materials, such as toroids. The recommended material for the latter is either Q1 or Q2 (Indiana General), Part no. F625/9 (dimensions in inches: D1 equals 0.375, D2 equals 0.187, and H equals 0.125).

A filter of this design has been successfully used, and no contribution to intermodulation distortion has been measured at a 25-watt drive level.

ham radio

By Ulrich L. Rohde, DJ2LR, 52 Hillcrest Drive, Upper Saddle River, New Jersey 07458

SSB TRANSMITTING CONVERTERS



FEATURES:


- Linear Converter for 5SB, CW, FM, etc.
- A fraction of the price of other units
- 2W p.e.p. output with 1 MW of drive
- Use low power tap on exciter or attenuator pad
- Easy to align with built-in test points

Frequency Schemes Available:

MODEL	INPUT(MHz)	OUTPUT(MHz)
XV-2-1	28-30	50-52
XV-2-2	28-30	220-222
XV-2-3	28-30	222-224
XV-2-4	28-30	144-146
XV-2-5	28-29	145-146
XV-2-6	26-28	144-146

ONLY \$59.95!

VHF Linear PAs

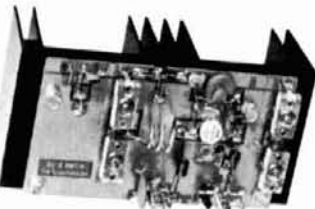

- Use as Linear or Class C PAs • For XV-2 Xmtg Converters, 150 Exciters, or any 2W Exciter
- LPA 2-15 Kit: \$59.95
- 15W out (linear) or 20W (class C) • Solid State T/R Switching • Models for 6M, 2M, or 220 MHz



- LPA 2-45 Kit: \$109.95
- 45W out (linear) or 50W (class C)
- Models for 6M or 2M
- LPA 8-45 Kit: \$89.95
- For 2M, 8-10W in, 45W out

T80 UHF POWER AMP



- Broadband PA • No Tuning Required • Class C PA
- 430-470 MHz
- 13-15W Out
- 200 mW Drive
- Model T80-450
- \$99.95
- Wired & Tested

VHF RECEIVING CONVERTERS

LET YOU RECEIVE OSCAR AND OTHER EXCITING SIGNALS ON YOUR PRESENT HF RECEIVER!



MODEL	RF RANGE	I-F RANGE
C28	28-32MHz	144-148MHz
C50	50-52	28-30
C144	144-146	28-30
C145	145-147	28-30
C146	146-148	28-30
C110	26-30	26-30
C220	220-222	28-30
C222	222-224	28-30

ONLY \$34.95

UHF RECEIVING CONVERTERS



MODEL	RF RANGE	I-F RANGE
C432-2	432-434	28-30MHz
C432-4	432-436	144-146
C432-5	435-437	28-30
C432-7	427.25	61.25
C432-9	439.25	61.25

ONLY \$34.95

A9 Extruded Alum Case with BNC's for above Converters (Optional) ... \$12.95

VHF & UHF FM RECEIVERS

- NEW GENERATION RECEIVERS
- MORE SENSITIVE • MORE SELECTIVE (70 or 100 DB)
- COMMERCIAL GRADE DESIGN
- EASY TO ALIGN WITH BUILT-IN TEST CRTS
- LOWER OVERALL COST THAN EVER BEFORE



R70 6-channel VHF Receiver Kit for 2M, 6M, 10M, 220 MHz, or com'l bands..... \$69.95
Optional xtal filter for 100 db adj chan 10.00



R90 UHF Receiver Kit for any 2 MHz segment of 380-520 MHz band..... \$89.95

FAMOUS HAMTRONICS PREAMPS


let you hear the weak ones!

Great for OSCAR, 55B, FM, ATV. Over 10,000 in use throughout the world on all types of receivers.



P9 Kit \$12.95
P14 Wired \$24.95

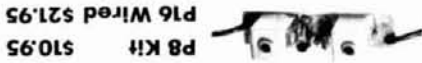- Deluxe vhf model for applications where space permits • 1-1/2 x 3" • Models avail to cover any 4 MHz band in the 26-230 MHz range • 12 Vdc
- 2 stages • Ideal for OSCAR • 20 db gain
- Diode transient protection • Easily tunable



P8 Kit \$10.95
P16 Wired \$21.95

- Miniature vhf model for tight spaces - size only
- 1/2x2-3/8 • Models avail to cover any 4 MHz band in the range 20-230 MHz • 20 db gain • 12V



P35 Wired \$34.95
P15 Kit \$18.95

- Covers any 6 MHz band in UHF range of 380-520 MHz
- 20 db gain • 2 stages • Low noise

NEW FM/CW EXCITER KITS

- BUILD UP YOUR OWN GEAR FOR MODULAR STATIONS, REPEATERS, & CONTROL LINKS
- Rated for Continuous Duty • Professional Sounding Audio • Built-in Testing Aids



T50 Six Channel, 2W Exciter for 2M, 6M, or 220 MHz (Specify band)..... \$49.95
T50U Six Channel, 1W Exciter for 430-450 MHz vhf operation \$49.95

Ask For Free Catalog

IT'S EASY TO ORDER! CALL OR WRITE NOW FOR FREE CATALOG OR TO PLACE ORDER!

PHONE 716-392-9430. (Electronic answering service eves & weekends)

Use credit card, c.o.d., check, m.o. Add \$2.00 shipping & handling.

IN CANADA, order from Communications Plus, 3680 Cole Verdy St-Laurent, Quebec or phone 514-337-7255. Add 38% to cover duty, tax, and exchange.

Note New Address and Phone No.

hamtronics, inc.
65c MOUL RD • HILTON, NY 14468

--Dealer Inquiries Invited--



the key-toggle

Key-toggle, another form of fast break-in, featuring simple but effective hand-key control of the transmitter

I wonder whether some psychologist won't someday discover that ham radio owes much of its appeal to the fact that you can say your piece in silence and the other guy can't interrupt until you're through. Even in most VOX systems, the other person cannot force interruption. Perhaps this is one of several reasons why "full break-in" CW operation has not yet become prevalent. It is not difficult technically, but there are still those of us who choose not to use it.

For handling commercial traffic on a clear channel, full break-in is perhaps best; but for most other activities, coupled with reasonable and unselfish operating practices, I prefer my key-toggle mode. To come on the air, you just start keying. To switch to receive, you simply hold a dash a little longer than

normal (time adjustable). Key-toggle can be just about as fast as full break-in, but the other guy can't break you. For example, when you are winding up a transmission, the last letter normally sent is dah-di-dah. With key-toggle, it's dah-di-dahah, click, click. The first click switches your transmitter's plate supply off and the second click, milliseconds later, switches the antenna relay and opens the receiver (optional). You are now in receive mode until you start keying again. When you hit the key, once again: click, click. But this time the antenna relay is switched and the receiver muted first; then, milliseconds later, the transmitter's plate supply comes on and you are ON again. No combination of letters or long pauses will change the relays, switching you back to the receive mode. Only a long dash will toggle your station back to receive.

circuit description

Major components, as seen in **fig. 1**, include a 741 operational amplifier configured as a dual time constant integrator, a 711 comparator, a 7474 TTL flip-flop, a few transistors, and three relays. The KEY UP output of U1 is a nominal +2 volts. Q1 is conducting, which effectively limits the voltage across the 1- μ F timing capacitor to near zero volts. With the +1 volt on pin 2, and 3 volts on pin 3, the output of U3 is also low. This places K2 and K3 in the de-energized (receive) state.

When the key is pressed, Q1 is cut off, which lets

By Don E. Hildreth, W6NRW, Post Office Box 60003, Sunnyvale, California 94088

the op-amp circuit start ramping positive because of the +2 volts and the timing components connected to pin 2 of U1. When the level at pin 2 of U2 just exceeds the voltage at its negative input, the comparator snaps high (with the help of some positive feedback). This toggles the U3, making Q high (pin 9) and \bar{Q} low. With pin 9 of U3 high, a turn-on volt-

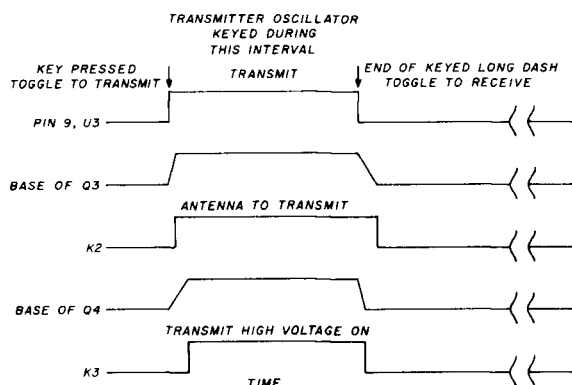


fig. 2. Relay keying sequence when switching from receive to transmit.

age is fed to Q3 and Q4 through timing control networks. The base network for Q3 comes on first and causes it to turn on very fast and turn off slowly. Q3 operates K2 for antenna control and receiver muting. The RC network connection through K3 to the base of Q4 causes this transistor to turn on after Q3. After K3 is activated, the RC network is removed, allowing Q4 to turn off before Q3. Fig. 2 shows the timing sequence for K2 and K3. K2 is the basic keying relay and must be able to follow keying speeds. For some keying circuits, K1 may be replaced with a 1-kilohm resistor for direct keying.

By using the \bar{Q} output of U3 and Q2 as a switch, the system provides a short time constant for switching from receiver to transmit and the longer, variable-time constant when switching from transmit to receive.

why key-toggle

Back in May, 1950, Hiele showed a system¹ which, with variations, has been much used. In Hiele's system, the switch-over from receive to transmit is done quickly, just as in key-toggle, but the transmit mode switches to receive after your key is up a selectable time, sort of a "dead man's switch." This system is used in many modern transceivers through an application of the VOX system to CW operation. The relay timing system is simpler with this method because your key must be up in order to switch, but it has its own drawbacks in operation. If you adjust the

time delay to allow for reasonable pauses when sending, the time seems like forever when switching over. And, if you adjust the timing for a quick turnover, your receiver blasts you when you pause. With key-toggle, you are in command. In fairness, however, it is recognized that key-toggle is not applicable to any automatic type of keyer.

power supply and construction

I used an inexpensive wall transformer supply system, although the 12-volt units usually supply 14 volts when lightly loaded, this poses no problem to the relays or op-amp. A zener diode is used to obtain +5 volts for the comparator and flip-flop. Maximum current is approximately 150 mA. Since this device is always used where strong rf fields are generated, a metal enclosure is probably mandatory.

connections

Outputs from *Key-Toggle* are contact closures intended to operate existing antenna and transmitter relays. Capacitors have been chosen to prevent switching transients from burning contacts and from false-triggering U3. For low voltage operation, as is the case in solid state equipment, the closures may be applied directly to the equipment.

operating with key-toggle

Assuming you are in receive status, you switch to transmit at the initial touch of your key (the switching process will shave a small piece off of your first dot or dash). Your transmitter will remain active until you hold a dash slightly longer than normal, the exact time determined by the TIME DELAY setting, which may be set between approximately 0.2 and 2.0 seconds. Adjust the time delay pot such that the time required to toggle your system is slightly longer than the time length of the dashes at the rate you intend to send.

One note, however: If you simply press your key and hold it when switching from receive to transmit, your transmitter will remain ON as long as the key is held down. After switching from receive to transmit, your key must be released at least once before a dash can toggle the relays.

This system takes a little time to get used to, but once you get the hang of it you can actually toggle for a quick listen between words, even between letters when you are not sending too fast. And switching will only occur when *you* choose.

reference

1. M. E. Hiele, W2SO, "An Automatic Transmitter Turner-Onner," *QST*, May, 1950, page 56.

ham radio

Introducing the first price breakthrough in amateur radio equipment in a decade!



\$388

ATLAS 110 TRANSCEIVER

- Self-contained power supply and speaker
- All solid state
- Covers 10-80 meters
- 20 watt input power
(250 watt model available)
- SSB and semi-break-in CW with sidetone

True, it doesn't have all the bells and whistles, but it does two things extremely well:

It does an excellent job of receiving.

It does an excellent job of transmitting.

On both SSB and CW.

Compare the performance of the Atlas 110 with any other equipment on the market, and see for yourself: it is truly a high performance transceiver in every respect.

And it costs only \$388.

Also available is the Model 110 Special, which includes RIT, CW Filter, and RF Gain Control.

Both the 110 Standard and the 110 Special transceivers are available with either 20 watt or 250 watt power

input rating. (250 watt model requires a separate AC power supply.)

The receive portion of the 110 transceiver is also available separately, as the Atlas RX-110 receiver. The TX-110 transmit module may be added later.

20 W MODEL 110 STANDARD TRANSCEIVER... **\$388**

20 W MODEL 110 SPECIAL* TRANSCEIVER... **\$428**
(Illustrated above)

250 W MODEL 110 STANDARD TRANSCEIVER... **\$478**

250 W MODEL 110 SPECIAL* TRANSCEIVER... **\$518**

PS-110H AC POWER SUPPLY... **\$ 89**
(required with 250 watt transceiver)

*Includes RIT, CW filter, RF Gain Control.

For complete details see your Atlas dealer or drop us a card and we'll mail you a brochure with dealer list.



**ATLAS
RADIO INC.**

417 Via Del Monte, Oceanside, CA 92054
Phone (714) 433-1983




TS-1



TS-1JR



PE-2

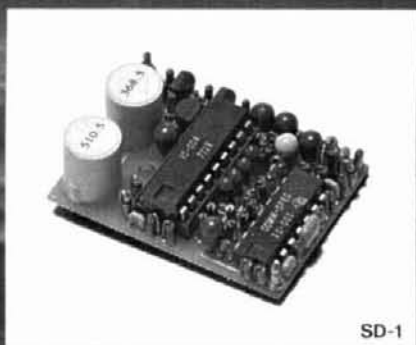


SD-1

THE DAWNING

The age of tone control has come to Amateur Radio. What better way to utilize our ever diminishing resource of frequency spectrum? Sub-audible tone control allows several repeaters to share the same channel with minimal geographic separation. It allows protection from intermod and interference for repeaters, remote base stations, and autopatches. It even allows silent monitoring of our crowded simplex channels.


We make the most reliable and complete line of tone products available. All are totally immune to RF, use plug-in, field replaceable, frequency determining elements for low cost and the most accurate and stable frequency control possible. Our impeccable 1 day delivery is unmatched in the industry and you are protected by a full 1 year warranty when our products are returned to the factory for repair. Isn't it time for you to get into the New Age of tone control?

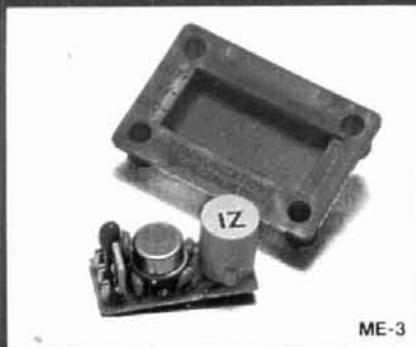

ME-3



TE-8

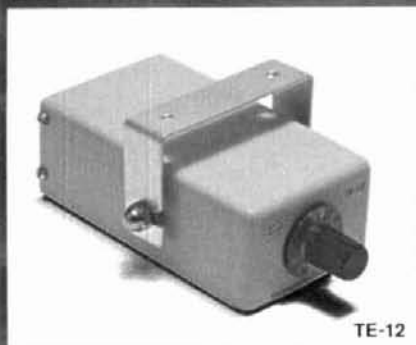

TE-12



ST-1

OF A NEW AGE.

TS-1 Sub-Audible Encoder-Decoder • Microminiature in size, 1.25" x 2.0" x .65" • Encodes and decodes simultaneously • **\$59.95** complete with K-1 element.

TS-1JR Sub-Audible Encoder-Decoder • Microminiature version of the TS-1 measuring just 1.0" x 1.25" x .65", for hand-held units • **\$79.95** complete with K-1 element.

ME-3 Sub-Audible Encoder • Microminiature in size, measures .45" x 1.1" x .6" • Instant start-up • **\$29.95** complete with K-1 element.

TE-8 Eight-Tone Sub-Audible Encoder • Measures 2.6" x 2.0" x .7" • Frequency selection made by either a pull to ground or to supply • **\$69.95** with 8 K-1 elements.

PE-2 Two-Tone Sequential Encoder for paging • Two call unit • Measures 1.25" x 2.0" x .65" • **\$49.95** with 2K-2 elements.

SD-1 Two-Tone Sequential Decoder • Frequency range is 268.5 - 2109.4 Hz • Measures 1.2" x 1.67" x .65" • Momentary output for horn relay, latched output for call light and receiver muting built-in • **\$59.95** with 2 K-2 elements.

TE-12 Twelve-Tone Sub-Audible or Burst-Tone Encoder • Frequency range is 67.0 - 263.0 Hz sub-audible or 1650 - 4200 Hz burst-tone • Measures 4.25" x 2.5" x 1.5" • **\$79.95** with 12 K-1 elements.

ST-1 Burst-Tone Encoder • Measures .95" x .5" x .5" plus K-1 measurements • Frequency range is 1650 - 4200 Hz • **\$29.95** with K-1 element.



COMMUNICATIONS SPECIALISTS

426 West Taft Avenue, Orange, CA 92667

(800) 854-0547, California residents use: (714) 998-3021



the **weekender**



i-f transformers — problems and cures

All serious communications receivers, transceivers, and most transmitters use the heterodyne principle for frequency generation. For receivers, various frequencies are converted to a single frequency called the *intermediate frequency* (i-f), while

primary and secondary coils are resonated by a capacitor) in a shielded can.


Fig. 1A shows two i-f transformers. Both of these are in the now-standard 1.9-cm (0.75-inch) shielded can. One of the transformers uses a threaded rod attached to the inductor core for tuning, while the other uses just an access hole to admit a tuning tool. In some cases, the inductor core will have a screwdriver slot to permit adjustment, while in others a hexagonal hole is cut through the center of each core. In the latter case, a special insulated hex alignment tool is used. The hex type offers the advantage of permitting adjustment of both primary and secondary tank circuits from the same side of the chassis.

Fig. 1B shows the pins at the bottom of the transformer. For an i-f transformer, at least four pins are required and some may have five or six pins. Some older models used wire leads instead of pins, and, of course, transformers intended for printed-circuit mounting will have solder tails instead of pins.

Fig. 2 shows several of the literally dozens of i-f



A

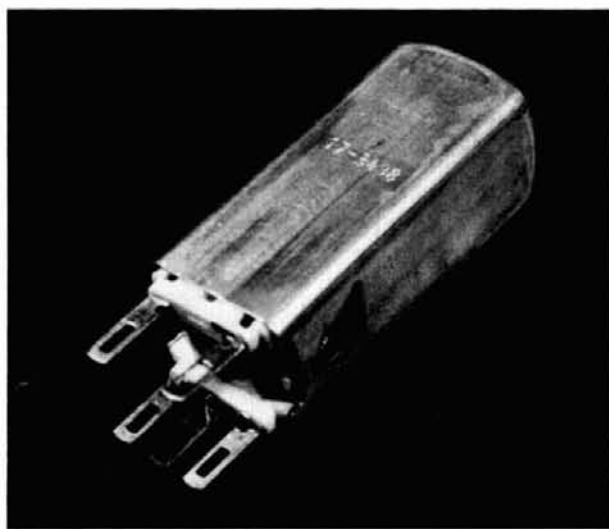

B

fig. 1. Two versions of the standard 1.9-cm (0.75-inch) i-f transformer, showing the different methods of tuning the inductor. (B) shows the connection pins at the base of the transformer.

transmitters, on the other hand, will create the ssb signal at an i-f and then heterodyne it to the ham bands.

An i-f amplifier is a tuned radio-frequency amplifier that operates on a single frequency (e.g., 455 kHz, 3350 kHz, or 9 MHz). In most cases, the tuned circuits in the i-f amplifier are tuned transformers (the

By Joe Carr, K4IPV, 5440 South Eighth Road, Arlington, Virginia 22204

transformers used in Amateur Radio gear. The transformer in fig. 2A uses two tuned coils. In a few early receivers, the tuning of the tanks was accomplished by the adjusting capacitors, the adjustment screws being accessible through holes cut into the shielded can. Most modern transformers, however, use a slug-tuned coil to tune the tank. The version shown in fig. 2A is commonly found in vacuum-tube equipment. Figs. 2B and 2C show transformers designed for use in solid-state equipment. The version in fig.

2B uses taps on the primary and secondary windings to match the low impedances normally found in transistor circuits. In fig. 2C the secondary is an untuned link. The transformer in fig. 2D is very similar to the one in Fig. 2A, except that a built-in bypass capacitor is provided to decouple the cold side of the secondary. These i-f transformer circuits are not unusual; they represent those most commonly found in receivers.

Fig. 2E shows a pinout configuration used by many manufacturers; note the odd sequence for numbering the pins. A color dot, usually green, identifies pin number one, with pins two through four occupying the four corners. These pins are usually connected to the tank circuit in the manner shown in fig. 2A. Pins 5 and 6 are reserved for such things as taps (fig. 2B) or bypass capacitors (fig. 2D).

Older units, using wire leads instead of pins often follow the specific color code:

- blue — plate
- red — B+
- green — grid or detector diode
- black — grid or diode return

transformer failures

Fortunately, i-f transformers are relatively simple devices, with failures limited to a few problems, such as open windings, shorted or open capacitors, windings shorted together, and the inability to resonate.

Open windings rarely occur anyplace except right at the transformer pins. Fig. 3 shows a close-up view of the wire from one winding that has broken at the pin. Once the signal tracing gets you to the



fig. 3. Example of a broken transformer wire at the connection pin.

driver to pry open the metal shield. Most of the transformers in use have a coil form mounted on a plastic base, with the entire assembly slid into the shielded can. Tabs on the can are then bent over to form retainers which keep the coil form and base in place. It is a simple matter to pry these tabs loose and then gently pull the base from the metal shell.

Use small long-nose pliers when working on the transformer. In fact, it is best if you use tweezers instead of pliers. Avoid pulling on the wire; it will break, and right at the coil form! It is then almost impossible to repair the coil without rewinding it.

The wire should be resoldered to the pin using a small, pencil-type soldering iron, not a gun. There will usually be enough pretinned wire left to allow re-

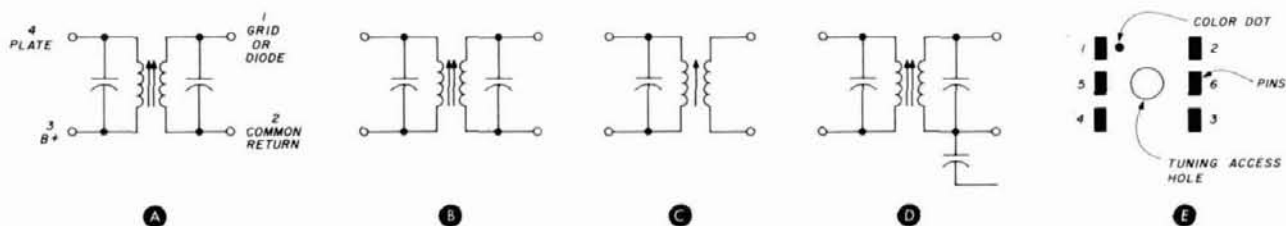


fig. 2. Versions (A) through (D) show different configurations for the i-f transformers. The pin numbering system is shown in (E) (bottom view).

correct stage, this type of problem can be diagnosed with an ohmmeter.

The open winding is also the usual cause of the intermittent i-f. Interestingly enough, I have seen many cases over the years where the wire had never been soldered. The transformer worked nicely for many years, until either corrosion built up or a mechanical jarring knocked the wire loose.

Repairing the open-winding problem is easy in many cases — if you are gentle. Use a small screw-

soldering to the pin. But, if not, do not try stripping the wire or you will break it. Insulation may be removed by gently scraping the wire with a razor blade or sharp knife. Keep in mind that even this is at the risk of breaking the wire. The best method is to melt the insulation with the tip of the pencil iron.

Ordinarily, there will be enough slack to make the new connection without stretching the wire. If not, bend the pin toward the wire — do not try to stretch the wire. If this is not possible, then solder a short

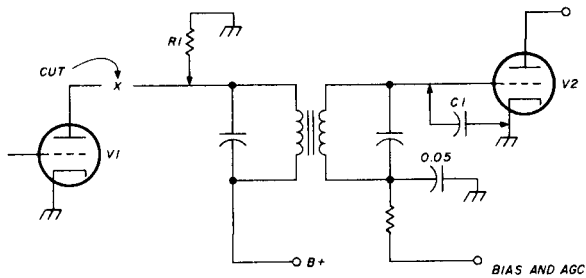


fig. 4. Technique for isolating a noisy i-f transformer. R should be equal to the plate resistance of the tube, with C being 0.01 to 0.1 μ F.

piece of wire to the pin for use as a jumper. A single wire removed from a piece of stranded hookup seems about right.

Because of the low coil resistance, it is often impossible to tell if an i-f transformer capacitor is bad. Signal tracing will usually isolate the problem at the correct stage, and then dc measurements and a tube or transistor check will leave you with the fact that there is nothing left except the transformer.

Only one type of problem, the noisy i-f transformer, is easily identified as a bad transformer. This problem produces a crashing, crackling, static-type noise. To isolate the problem, remove the tube from its socket or break the plate lead between the transformer and the plate pin on the tube socket. Temporarily solder a resistor (see fig. 4) between the plate and cathode pins (or ground). The value of the resistor should be approximately the plate resistance of the tube. If noise persists, then suspect the transformer. As a quick extra confirmation, shunt a 0.01- to 0.1- μ F capacitor across the grid and cathode of the following stage. If the noise disappears, then the i-f transformer is bad.

The i-f transformer is bad if the noise persists when the tube is removed and the resistor is connected to the circuit, or if the noise disappears or is reduced significantly when the shunt capacitor is connected. In a multi-stage, cascade i-f amplifier, each stage may have to be checked separately in succession, beginning with the stage that is closest to the detector.

In many cases, the noise is caused by a bad tuning capacitor inside the transformer can. Some transformers use individual ceramic or silver mica capacitors (which rarely go bad), but in most cases the two capacitors will be as shown in fig. 5. In fig. 5A, the capacitor is formed from a piece of mica dielectric with the silver plates deposited on both sides. A pair of contact springs connect each plate to its respective pin. This arrangement can cause noise by dc breakdown of the mica or by noisy contacts. In the latter case, cleaning and retensioning often cures the problem. The second arrangement, shown in fig. 5B, buries the fixed mica compression capacitors inside of a molded plastic base.

A study by the service department of a major automobile radio manufacturer revealed that, in humid regions of the country, there are roughly two to three times as many trimmer capacitor and i-f transformer problems than in dry areas. The best remedy for this is to replace the transformer. But, if that is impossible or would take too long, try replacing the bad capacitor with a disc ceramic or silver mica capacitor.

If the original capacitor is like the one in fig. 5A, it is a simple matter to use side cutters to clip off the top spring clip contact. Then solder a capacitor of the proper value across the terminals (see fig. 6A). The proper value can be determined experimentally (check first to see if the manufacturer gives the value in the schematic) using a GDO or signal generator to locate a standard value that will allow the coil to resonate at the correct frequency.

If the bad capacitor is not easily removed or disconnected, there is still a possible cure. Disconnect the coil wire going to one end of the capacitor, and then connect it and one end of the replacement capacitor to an unused pin. Or add a pin in one of the blank pin slots (fig. 6B) by forcing a piece of hook-up wire through the slot.

The problem of primary to secondary short circuits comes about because the wires from the upper coil pass by, and may touch, the winding of the lower coil. The problem almost always results in B+ leaking through to the grid of the next stage or the plate of the detector diode.

The cure here may be as simple as moving the wires apart and then patching up the damaged spot using Q-dope, high voltage corona dope, or just glue. Replacement of the transformer, however, may be required.

You'll sometimes find a transformer that is not causing static, passes all dc checks, but signals will



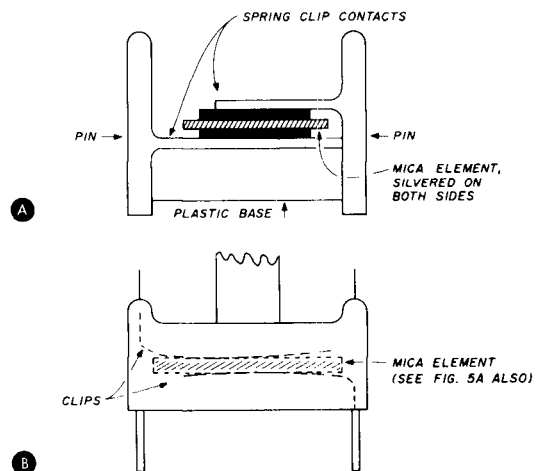


fig. 5. The compression trimmer can be one of two types, either open or enclosed in the plastic base. Cleaning and retensioning the version shown in (A) can cure the problem, though replacement is required for the molded version (B).

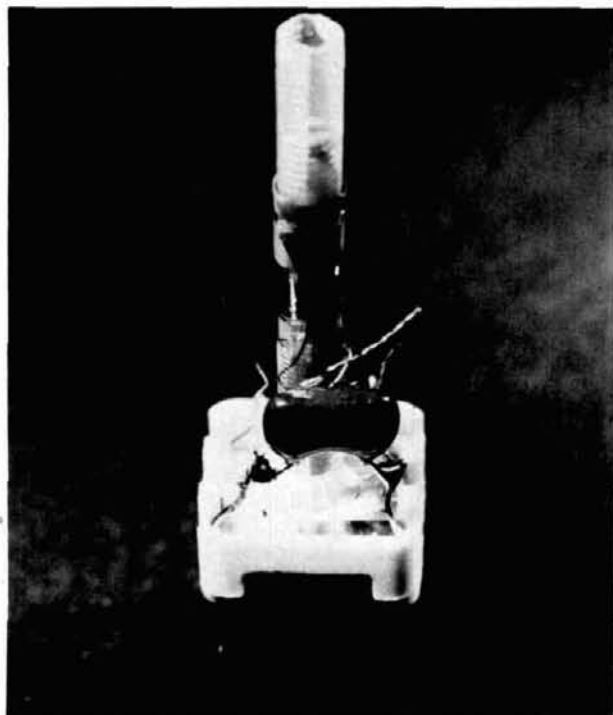

A

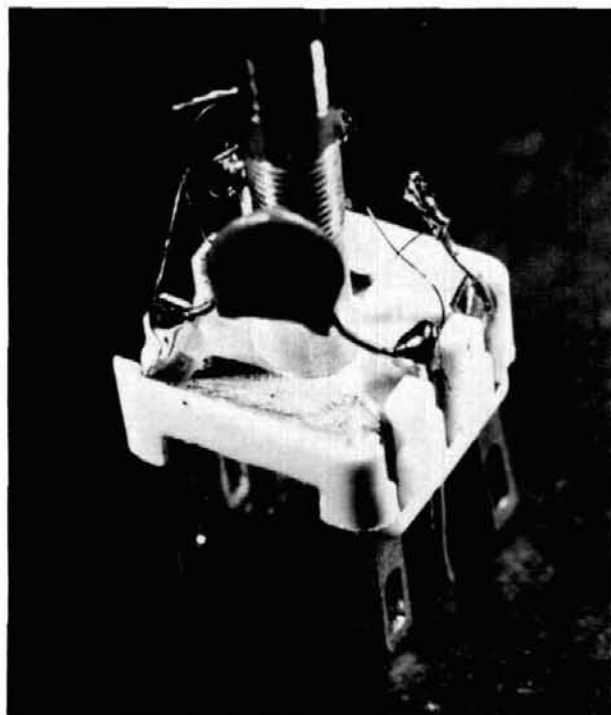

B

fig. 6. (A) shows a replacement capacitor soldered directly across the pins at the base. To replace a molded capacitor, a new pin is inserted in the base of the transformer (see photograph B).

not go through or are severely reduced in strength. Barring such rare problems as shorted windings and open capacitors, it is often the case that one of the tanks is off resonance due to a cracked or broken ferrite tuning slug. To replace the slug, break it into smaller pieces (it rarely will come out by its threads!) and then remove them by shaking. A replacement slug can then be installed. Find an i-f transformer of the same frequency range and with the same type of slug. Salvage the slug and install it in the bad transformer. Some electronic parts suppliers stock small assortments of tuning slugs for just this purpose. Note that 9-MHz ssb transceiver slugs can often be

replaced with a slug from a 10.7-MHz fm broadcast receiver.

Regardless of the problem, except perhaps the open coil repair, the best solution is to replace the bad i-f transformer with a new part purchased from the equipment manufacturer. However, this is not always possible, especially in older gear. Even if the company is still in business, the set may be so old that they no longer support the product. A few years after a model is discontinued, support usually vanishes.

It is possible to buy new i-f transformers. Companies such as J.W. Miller and others still manufacture both direct replacements for many types, and so-called "universal" i-f transformers. Their catalogues should reveal at least one or two currently made models which are good candidates for replacement of the bad unit in your rig. It's unlikely that a cross-reference listing for a piece of ham gear is available, but a careful reading of the specifications and inspection of the circuit diagram will lead to a replacement.

Older 2.5-cm (1-inch) or larger i-f transformers are especially difficult to replace. However, if you are willing to make a few mechanical modifications, the standard 1.9-cm (0.75-inch) transformers can be pressed into service using the adapter plates and mounting clips (fig. 7) provided with replacement transformer.

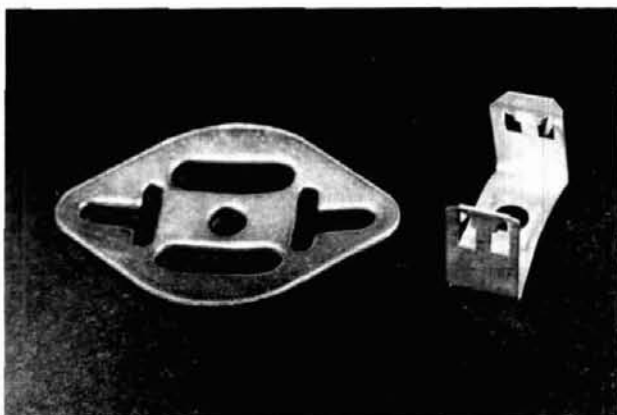


fig. 7. Mounting hardware for i-f transformers, which can be used to replace older 2.5-cm (1-inch) transformers.

ham radio

The DXer's Choice.



Kenwood's TS-820S has everything the Amateur Operator could want in a quality rig.

Time proven over thousands of hours of operating time, the Kenwood TS-820S has become the preferred rig for those individuals interested in high reliability. And, the TS-820S has every feature any Amateur could want for operating enjoyment, on any band, from 160 through all of 10 meters...plus an RF speech processor in the transmitter, IF shift and sharp filters in the receiver. All combine to give optimum performance under all conditions.

You can always tell who's running a TS-820S. Its superb quality stands out from all the other rigs on the band...and when the QRM gets heavy the TS-820S's adjustable RF speech processor,

utilizing a 455-kHz circuit to provide quick-time-constant compression, will get the message through. RF negative feedback is applied from the final to the driver to improve linearity, and third-order products are at least -35 dB. Harmonic spurious emissions are less than -40 dB and other spurs are less than -60 dB.

RF input power is 200 W PEP on SSB, 160 W DC on CW, and 100 W DC on FSK. Receiver sensitivity is better than 0.25 μ V for 10 dB S/N.

The TS-820S from Kenwood! See it today at your nearest Authorized Kenwood Dealer.

By popular demand.



TS-520S and DG-5 DIGITAL FREQUENCY DISPLAY

It's an ideal choice for anyone looking towards owning a highly reliable, highly efficient amateur radio transceiver.

FEATURES:

Full coverage, 160 through 10 meters...digital readout with optional DG-5...effective noise blanker and audio processor...RF input power: 200 watts PEP on SSB, 160 watts DC on CW. The TS-520S transceiver provides full transmit and receive coverage of all Amateur bands from 160 through 10 meters. It also receives 15.0 (WWV) to 15.5 MHz and another

500-kHz range of your choice in the auxiliary band position. With the optional DG-5, you have a large digital frequency readout when transmitting and receiving, and the DG-5 also doubles as a 40-MHz frequency counter. The TS-520S includes a built-in AC power supply, and, with the addition of the optional DS-1A DC-DC converter, it can function as a mobile rig. It features a very effective noise blanker, RIT, eight-pole crystal filter, 25-kHz calibrator, front-panel carrier level control, semi-break-in CW with side-tone, built-in speaker, heater

switch, 20-dB RF attenuator and easy phone-patch connection. RF input power is 200 W PEP on SSB and 160 W DC on CW. Carrier suppression is better than -40 dB and side-band suppression is better than -50 dB. Spurious radiation is less than -40 dB. Receiver sensitivity is 0.25 μ V for 10 dB (S+N)/N. Selectivity is 2.4 kHz at -6 dB/4.4 kHz at -60 dB and, with the optional CW-520 CW filter, is 0.5 kHz at -6 dB/1.5 kHz at -60 dB. See your Authorized Kenwood Dealer now for complete information!



KENWOOD
...pacesetter in amateur radio

TRIO-KENWOOD COMMUNICATIONS, INC.
1111 WEST WALNUT / COMPTON, CA 90220

updating the Heath HW-2036 to the HW-2036A

Modifications to the
Heath HW-2036
to provide complete coverage
of the new
two-meter repeater subband

Now that the two-meter band has repeater allocations in the lower half, people with HW-2036 transceivers are feeling left out in the cold. No longer! With a small parts kit available from Heath, a few additional parts obtained (through Heath or purchased on your own), and these simple instructions, you can update your HW-2036 to cover the entire band. In fact, the transceiver will operate over a six-MHz range, from 143 MHz to beyond 149 MHz, although with reduced output at the extreme edges.

updating early HW-2036s:

Before actually beginning conversion of the HW-2036, check to see that your HW-2036 has all the updates that Heath has added since this model was introduced. There were addendum sheets included with the manual, in addition to several changes in the manual itself to reflect parts values different from those printed on the circuit boards. On the receiver board, R206 and R209 should be 10 kilohms, and C214, C215, and C216 should be 4.7-pF NPO disc ceramics. Also, Q204 was changed from a MPF-105 to an EL-131. If you have to replace these six parts, you will need to realign the receiver i-f. Wait, however, until the rest of the changes have been made.

On the synthesizer board, R419 should be 10-kilohms, C442 a 20-pF NPO disc ceramic, C403 a 100-pF NPO disc ceramic, and R445 220 ohms. These parts changes reduce drive to the synthesizer loop mixer. And finally, on the transmitter board, R141 should be 180 kilohms, ½ watt, which increases the

zener bias in the 11-volt regulator. Only very early HW-2036s might need any of these changes. Your HW-2036 is now up to date. **Table 1** lists all the parts needed to convert the HW-2036.

conversion to the HW-2036A

There are changes to be made on each board, and we found it easier to do one board at a time and then do the alignment board-by-board when everything was bolted back together. It is necessary to have some method of removing solder from the double-sided boards before attempting to remove the parts.

Power Amplifier Board. Remove the transceiver top and bottom covers and begin with the power amp board by removing the heatsinks from the back panel. Unsolder and disconnect the ground wires connected to the corners of the transmitter and receiver boards. Carefully pull the molex connector apart, remove the two nuts that hold the power amplifier assembly to the back of the chassis, and swing the board down on its leads. A 12-pF dipped-mica capacitor (C235 in the HW-2036A manual) is added to the output connector on the inside of the board.

Prepare this capacitor by cutting the leads 22 mm (7/8 inch) long and slipping 19 mm (3/4 inch) of spaghetti or insulation over each lead. Bend the exposed 2-mm (1/8-inch) lead at right angles away from the body of the capacitor. Lay the capacitor on the foil of the board and solder one lead to the antenna jack center pin and the other to the foil where the ground wire pokes through the board. This forms a filter across the output. The lead length is the inductance part of the filter. Reassemble the board to the rear apron, but leave the ground wires to the transmitter and receiver boards loose for now. Replace the molex connector.

VCO Board. Heath now supplies a parts kit for modifying the VCO; it consists of two mica capaci-


By Mike Miller, WB6TMH and Ed Fitzgerald, WA6ODR. Mr. Miller's address is 173 Leveroni Road, Sonoma, California 95476. Mr. Fitzgerald can be reached at Post Office Box 75, Cotati, California 94928.

tors, a coil, and a new varicap diode (parts kit number 830-29, \$3.95). Begin by removing the VCO cover screws and unsoldering the two lugs on the side (a soldering gun may be necessary for this step). Break loose the epoxy bead between the coil and the cover. Remove the nuts and washers and pull the board up on its leads to gain access to the bottom. Cut the epoxy bond between C503 and L501. If C503 is broken it will be necessary to replace it (Heath 21-192 \$1.35).

Unsolder and remove L501, C513, C509, and VD502. Replace each component with the parts supplied in the Heath package. Reglue L501 to the board, C503 to the side of L501, and C513 and C509 to each other. Now, replace the board on its bolts and turn on the power. Set the frequency switches to 146.000 MHz and run the slug of the new coil up and down, checking that the synthesizer lock light on the front panel goes out at some point, indicating the VCO is operational. Install the cover, gluing the coil to the top and soldering the lugs on the side. These changes increase the tuning range of the VCO by increasing the oscillator L/C ratio and making the varicap diode a larger part of the total capacitance. A full alignment of the VCO will be completed later.

Synthesizer Board. First, remove the black wire attached to point C on the power amp board to allow room for the synthesizer board to swing up. Remove the thirteen wires that attach the thumbwheel switches to the front end of the board and the four nuts and washers. Now, swing the board up on its remaining leads and remove R427 and R428, changing the values so that R427 becomes 5.6 kilohms and R428 10 kilohms. Page 61 of the manual can be used to locate these two resistors.

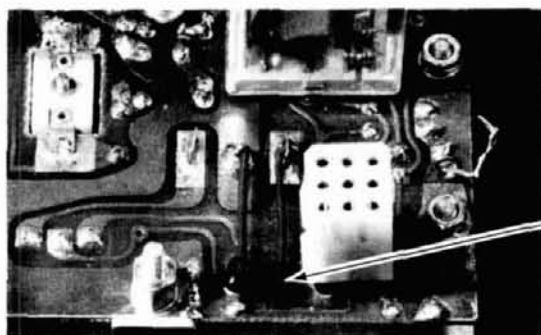Replace the board on its bolts, attach the black wire to point C on the power amp board, and refer to pictorials 4-10 and 4-11 for color code and wire placement when attaching the thirteen wires to the frequency switches. Again turn on the power and check to see that the synthesizer lock light goes out.



Location of C235 which, in conjunction with its lead length, forms a filter on the output of the transmitter.

table 1. Parts list of components needed to update the HW-2036 to an HW-2036A. Unless otherwise noted, all resistors are 1/4 watt, 5 per cent tolerance.

update parts		Heath number	Heath price
Designation	value/description		
C214, C215, C216	4.7-pF NPO disc ceramic	21-168	\$0.29
C442	20-pF NPO disc ceramic	21-51	0.25
Q204	EL-131 (replaces MPF-105)	417-241	2.10
R141	180 ohms, 1/2 watt	1-112	0.22
R206, R209	10 kilohms 10 per cent	1-9-12	0.24
R419	10 kilohms	6-103-12	0.25
R445	2.2 kilohms	1-4-12	0.24
C403*	100-pF disc ceramic	21-75	0.25
conversion parts			
C503	0.1- μ F monolithic ceramic	21-192	\$1.35
C509*	22-pF 5 per cent dipped mica	20-99	0.40
C513*	125-pF 5 per cent dipped mica	20-117	0.50
C201*	5-pF NPO dipped ceramic	21-78	0.25
C235*	12-pF 5 per cent dipped mica	21-130	0.45
L501*	0.25 μ H	40-1855	0.95
VD502*	Motorola MV2110	56-640	1.65
R103*	100 ohms	6-101-12	0.25
R233*	15 kilohms	6-153-12	0.25
R427*	5.6 kilohms	6-562-12	0.25
R428*	10 kilohms	6-103-12	0.25

*Note These parts can be obtained as a kit with instructions (Heath part number 830-29) for \$3.95

Receiver Board. Remove the four nuts and washers, remove the coax from points A and B, and tilt the board up on its remaining leads. Referring to pages 45-52 in the manual, change the value of R233 to 15 kilohms. This increases the drive to the receiver doubler.


Next, remove C201 and the shield alongside of L201 and L202. Remove 3 mm (1/8 inch) of the paper insulation from the vertical edge nearest L213. Cut a piece of 0.2-mm (0.01-inch) brass shim stock or copper flashing to 22 x 16 mm (7/8 x 5/8 inch), bending 3 mm (1/8 inch) of the long side at right angles to form a tab. Clean the shim stock and shield with steel wool and solder the tab to the existing shield where the insulation was removed. Alligator clips will hold the pieces together during the soldering.

Remove L202 and install the modified shield on its original pins. Solder the shield pin nearest L204 to hold it in place and run a bead of solder along the shield extension, joining it to the board foil behind C203 and L202. Also, run a bead of solder along the back of the shield next to C201. Replace L202, noting the polarity, and change C201 to a 5-pF NPO disc ceramic; solder both components in place, as well as the second shield pin.

Bolt the board down again and resolder the ground lead from the power amplifier board to the corner of

the receiver board. Connect the power, turn on the transceiver, and tune in a local repeater to see that everything works properly. Full alignment will be done last.

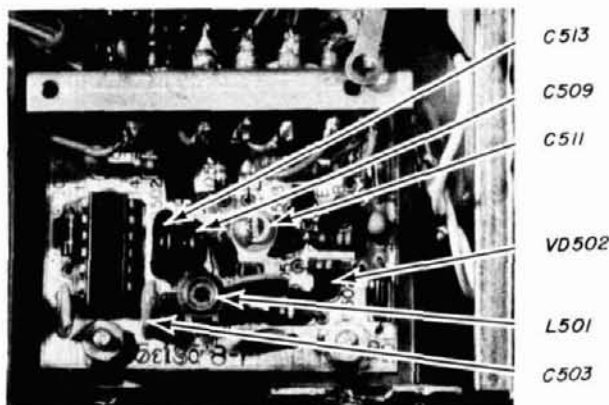Transmitter Board. Remove the phono plugs from J101 and J102, and remove the five nuts and washers holding down the board. Disconnect the molex connector to the power amplifier board and also the



This photograph shows the locations of components that were changed on the VCO board.

four large power connections labeled G, P, R, and V. Pull off the three-pin connector on regulator IC1 and unsolder the lead of the 0.001- μ F capacitor from ground lug DA (refer to page 106). Carefully tilt up the board on its remaining leads.

Referring to page 74, remove R103 and replace it with a 100-ohm resistor. Remove the connectors on pins B, L, and N and solder the base of these pins to the board foil. These pins are the shield connections for interconnecting coax leads and should be rigidly grounded to both sides of the circuit-board ground plane!

Pull the red wire from pin S. Clip off and discard the 0.001- μ F capacitor from the end and remove the two ferrite beads. Strip 3 mm (1/8 inch) of insulation from the end of the red wire and add approximately 7.5 mm (3/4 inch) of wire of a similar size, covering the soldered splice with heat shrink tubing or spaghetti. Now strip 16 mm (5/8 inch) of insulation from the extended wire and slip on the two ferrite beads just removed. There should be about 3 mm (1/8 inch) of wire sticking out. Solder this end to pin OUT, alongside the yellow wire from regulator IC1. Next, take a 2.5-cm (1-inch) piece of solid wire, bend a 3-mm (1/8-inch) tab on one end, and solder this tab to the circuit board foil next to pin N.

Install the board on its bolts again. Be sure to position the long coaxial cable along the top of the front of the board, as shown on page 106 of the manual. Replace all board connectors, phone plugs, and the connector on IC1. Don't forget the shield connec-

tor to pin B, hidden under the wiring harness. Now, solder the other end of the 2.5-cm (1-inch) wire from the board foil near pin N to solder lug DA on the rear apron. Make this lead as short as possible and trim off the excess. Reconnect the ground wires from the receiver and transmitter boards to the power amplifier board.

Install two ground lugs at stud X on the power amplifier board. Solder one lug directly to the chassis. Remove the coax shield from point B on the power amplifier board and solder it to the second lug on stud X.


alignment

VCO Board. Set C511 on the VCO board to mid capacity. Attach the dc probe of a VTVM to TP401 on the synthesizer board; set the frequency switches to 146.000 MHz; and set the mode switch on the front panel to SIMPLEX. Turn the slug of coil L501 up until it shows at the top of the coil. Key the transmitter with the dummy load attached and rotate the slug down until the VTVM reads 2.2 volts. The SYNTHESIZER LOCK light should be out at this point.

With the transceiver *not* keyed, adjust C501 until the VTVM again reads 2.2 volts. This completes the VCO adjustments.

Transmitter Board. Since the transmitter strip is already aligned to a center frequency of 147.000 MHz, an abbreviated procedure is used to center the transmitter at 146.000 MHz, providing full output over the entire frequency range. First, install the dummy load. Set the thumbwheel switches to 146.000 MHz and connect the rf probe to TP101. The kit-supplied probe is fine and can be used with the dc scale of a standard VTVM for better sensitivity. Adjust L101 and L102 for maximum output with the transmitter keyed. Several adjustments may be necessary.

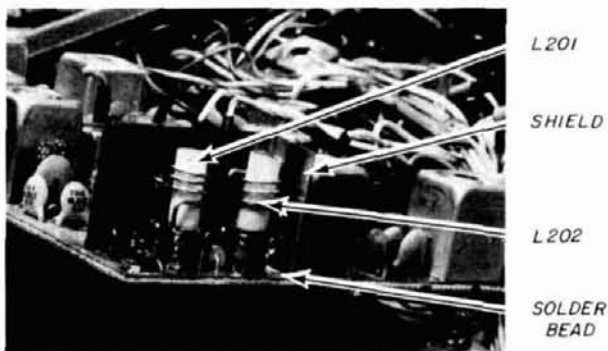Move the rf probe to TP 102, key the transmitter,



The addition to the shield can be seen in this photograph of the receiver board. Part of the paper insulation was removed to allow the addition to be soldered to the original shield. When it's installed, the bottom of the new piece is soldered to the circuit board.


and adjust L103 and L104 for maximum. Remove the probe, and, with the transmitter keyed, adjust L105, L106, and L107 for maximum output as indicated on the front panel's relative power meter. The peak on L106 will be very broad.

Now, set the frequency switches to 144.500 MHz and adjust L101 for maximum output at this lower band edge. Then, with the frequency set to 147.500 MHz, adjust L102 for maximum. Repeat these two steps, which are designed to stagger the tuning over the full band. Finally, set the frequency to 144.000 MHz, key the transmitter, and check the relative power meter to be sure the transmitter has full output at the extreme band edge. Repeat this step at 147.990 MHz. There may be a slight difference at each end, but not much.

Power Amplifier Board. Set the frequency switches to 145.000 MHz, and, with the transmitter keyed into the dummy load, adjust the power amplifier trimmers in this order: A, B, C, D, E, D, C, A, B. Do not adjust trimmer capacitor A any further clockwise than is necessary for maximum output. This single adjustment series should provide nearly equal output across the entire band. Remember to replace the heatsinks!


Receiver Board. Set the frequency to 146.000 MHz, connect the rf probe to gate 2 of Q202 on the receiver board, and adjust L402 and L403 on the synthesizer board and L212 and L213 on the receiver board for maximum level. Perform these adjustments in the order listed and repeat at least once. This provides maximum local-oscillator injection to the first mixer.

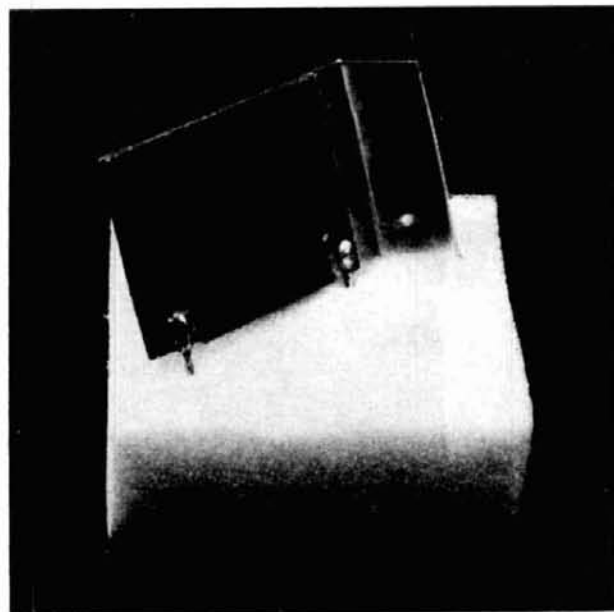Next, remove the antenna coax from points A and B on the receiver board and connect the kit-supplied



Close-up of the receiver shield with the addition soldered to the right edge.

jumper from points A and B to points TP106 and TP107 on the transmitter board. Now, adjust L201, L202, L203, and L204 for maximum S-meter reading with the frequency set to 146.000 MHz. It may be necessary to adjust the frequency up or down slightly to pick up the harmonics of the reference oscillator being used as the alignment signal source. Also, since there is a high signal level, C147 on the transmitter board may be adjusted to maintain the meter

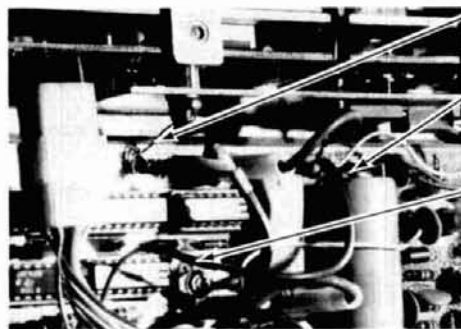

GROUND WIRE NEXT TO PIN N.

FERRITE BEAD ON WIRE CONNECTED TO PIN OUT.

SPLICED CONNECTION TO RED WIRE.

Changes to the transmitter board can be seen in this photograph. Note that the wire extension is now soldered to pin OUT instead of pin S.

reading at half scale or less. If this does not provide enough signal reduction, slightly detune i-f coil L207 on the receiver board. Once L201 through L204 are adjusted properly, L207 can be repeaked by removing the jumper from point A and holding it a small distance from the pin. This will provide enough signal to peak L207 without overloading the i-f strip.

At this point, if you replaced the parts in the i-f strip, refer now to the manual instructions for aligning the i-f stages. Few will need this however, and, if not disturbed, the rest of the i-f will not need attention. This completes the conversion.

remarks and notes

We found that the birdies on 146.000 MHz and 146.520 MHz were slightly decreased in signal strength but not eliminated. The reference oscillator and offset oscillator should not need attention if care was taken not to disturb their trimmers during the modification.

Reducing power consumption. Several ICs can successfully be replaced with low-power Schottky versions (LS series). IC104, IC105, and IC106 (7490s) may be replaced with 74LS90s. IC107 (7492) may be changed to a 74LS92. IC405 (7400) may be changed to a 74LS00, and IC404 (7473) may be changed to 74LS73. IC103 (7400) may *not* be replaced! These changes will reduce current drain about 20 per cent. It may be possible to change these devices to the CMOS series for further power reduction, but we haven't yet tried that substitution.

ham radio

TROUBLE FREE TOUCH-TONE® ENCODER

Patented




POSITIVE TOUCH (KEYS DEPRESS) • MOBILE • HANDHELD
 POSITIVE MOUNT • NO POTTED PARTS (SERVICEABLE)
 MIL. SPEC. COMPONENTS • NO RFI • SELF CONTAINED
 XTAL CONTROLLED • LEVEL ADJUSTMENT FROM FRONT
 • 4.5 - 60 V.D.C. • WILL OPERATE ANY SYSTEM

Supplied with: Instructions, schematic, template, hardware. PP-1A designed for Standard Communications Handhelds. (California orders add 6% sales tax)

PP-1=\$55.00, PP-2=\$58.00, PP-1A=\$58.00
 PP-1K=\$66.00, PP-2K=\$69.00

K-Series = Self Contained Delay Relay
 M-Series = Detached Frame for irregular installations
SEND FOR CATALOG

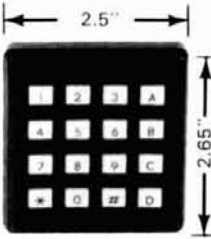Available at: Ham Radio Center (800) 325-3636
 Denver Colo., CW Electronics (303) 893-5525
 Los Angeles, Henry Radio (213) 272-0861
 New York City, Harrison (800) 645-9187
 Canada - Winnipeg, Prairie Comm. (204) 786-6986



PP-2 & PP-2K

PP-1 & PP-1K
 LETTERING
 OPTIONAL

Mail Order To


Pipo Communications

Emphasis is on Quality & Reliability

P.O. Box 3435 DEPT. B
 Hollywood, California 90028
 213/852-1515

NOW AVAILABLE FROM M & M

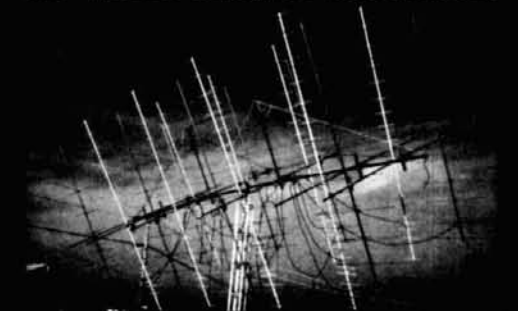The first West Coast dealership
 for these unique antennae.



Array of 8 K2RIW 19s used by WB6NMT on 432 MHz EME Louis QSOed W1JR 21 October 78 with this array to become the first amateur on FOUR BANDS EME (50, 144, 220 also) and all 4 bands were made only with home-to-home QSOs. The 8 RIW array did the job in just under two months of work for the entire system. Much faster than had hoped for. (This configuration also included 8-10 element Yagis for 144 MHz EME.)

K2RIW 19 EL YAGI

With Tandem-reflector*

(pat. pend.)

HEY HFers!

How's your 10 meter receiver working? Signals a little weak? Having trouble pulling out those weak ones? Lunar has a new preamp just for you.

Their model PAI 28E-s is a mini-inline 10 mtr. preamp that will perk up your transceiver.

Small enough to fit inside most any HF rig, a flick of the switch bypasses the preamp, and the transceiver is back to normal operation for other bands. On 10 meter, another flick of the switch, and new life is added to that tired receiver. Stop missing those weak rare ones. Call for immediate delivery of this preamp, and all Lunar products, too.



- Outperforms all others
- 24 degree beamwidth
- Handles legal power
- Low VSWR, under 1.2:1 at 432 MHz
- Handles 434 MHz ATV also
- Complete with all hardware and balun
- Easily arrayed for increased gain
- Lightweight at 1.3 Kg

Call us for immediate delivery of these antennae. RIW Power Dividers, too.

M & M RF DISTRIBUTORS

P.O. BOX 82183 • SAN DIEGO, CA 92138 • (714) 299-9741.

ALUMA TOWERS

60 Ft. Ham Crank-Up Model T-60-H

40 Ft. Crank-Up Ham Model T-140

HIGHEST QUALITY

MADE IN ALUMINUM

- ★ TELESCOPING (CRANK UP)
- ★ GUYED
- ★ TILT OVER MODELS

QUALITY MADE

Excellent for

HAM COMMUNICATIONS

MANY MODELS MFG.

Towers to 100 feet. Specials designed & made. See dealer or send for free catalog.

ALUMA TOWER CO.
 BOX 2806HR
 VERO BEACH, FLA. 32960
 PHONE (305) 567-3423

TOP QUALITY MOBILE ANTENNAS

FROM G & C Communications

- Stainless Steel Radiator
- Heavy Nickel-Chrome Plated Brass Base and Fittings
- Mounts Come with 17' RG-58AU and PL-259 Connectors.
- Compatible with Motorola TAD and TAE Mounts.

When ordering, suffix "T" indicates complete antenna assembly with trunk lid mount. Suffix "M" indicates for hole mounting.

BM-2700T — 27-31 MHz ¼ wave base-loaded, 200 watt rating. Covers 10 meters or CB. Great mobile antenna for converted CB rigs. 49" at lowest frequency and is approximately 42" when cut for ten meters. Complete with trunk lid mount assembly. \$29.95

BM-MATH — Extra whip (Cut one for 10 and one for CB) ... \$5.00

BM-4700T — Same assembly except for 47-54 MHz ... \$29.95

BM-5800T — 144-174 MHz ¼ wave gain antenna, 200 watt rating. Complete ... \$29.95

BM-MAT 58 or **BM-MAT 22** — ¼ matching coils (these coils with whips allow same mounting assembly to be used on different bands) ... \$14.95

BM-5822 — 220-225 MHz ¼ wave gain antenna ... \$29.95

Note: Deduct \$4.00 from "T" price for "M" assemblies

Additional Information On Other Antenna Models Available

G & C Communications
 Dept. HH, 730 Coltonwood
 Lincoln, NE 68510



for the experimenter

INTERNATIONAL CRYSTALS & KITS / OSCILLATORS • RF MIXERS • RF AMPLIFIER • POWER AMPLIFIER

OX OSCILLATOR



Crystal controlled transistor type. 3 to 20 MHz, OX-Lo, Cat. No. 035100. 20 to 60 MHz, OX-Hi, Cat. No. 035101.

Specify when ordering
\$5.22 ea.

MXX-1 TRANSISTOR RF MIXER



A single tuned circuit intended for signal conversion in the 30 to 170 MHz range. Harmonics of the OX or OF-1 oscillator are used for injection in the 60 to 179 MHz range. 3 to 20 MHz, Lo Kit, Cat. No. 035105. 20 to 170 MHz, Hi Kit, Cat. No. 035106.

Specify when ordering.
\$5.80 ea.

OF-1 OSCILLATOR



Resistor/capacitor circuit provides osc over a range of freq with the desired crystal. 2 to 22 MHz, OF-1 LO, Cat. No. 035108. 18 to 60 MHz, OF-1 H, Cat. No. 035109.

Specify when ordering.
\$4.48 ea.


PAX-1 TRANSISTOR RF POWER AMP



A single tuned output amplifier designed to follow the OX or OF-1 oscillator. Outputs up to 200 mw, depending on frequency and voltage. Amplifier can be amplitude modulated 3 to 30 MHz, Cat. No. 035104.

Specify when ordering.
\$6.06 ea.


SAX-1 TRANSISTOR RF AMP

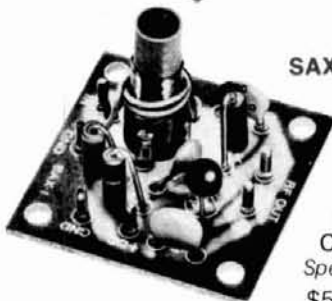

A small signal amplifier to drive the MXX-1 Mixer. Single tuned input and link output. 3 to 20 MHz, Lo Kit, Cat. No. 03512. 20 to 170 MHz, Hi Kit, Cat. No. 035103.

Specify when ordering.
\$5.80 ea.

BAX-1 BROADBAND AMP

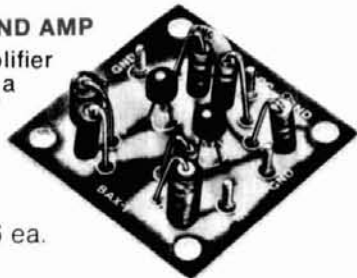


General purpose amplifier which may be used as a tuned or untuned unit in RF and audio applications. 20 Hz to 150 MHz with 6 to 30 db gain. Cat. No. 035107.

Specify when ordering.
\$6.06 ea.

.02% Calibration Tolerance

EXPERIMENTER CRYSTALS

(HC 6/U Holder)

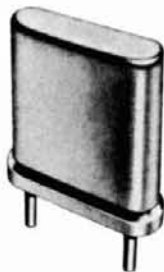

Cat. No.	Specifications	
031080	3 to 20 MHz — for use in OX OSC Lo	\$6.25 ea.
	<i>Specify when ordering</i>	
031081	20 to 60 MHz — For use in OX OSC Hi	\$6.25 ea.
	<i>Specify when ordering</i>	
031300	3 to 20 MHz — For use in OF-1L OSC	\$5.22 ea.
	<i>Specify when ordering</i>	
031310	20 to 60 MHz — For use in OF-1H OSC	\$5.22 ea.
	<i>Specify when ordering</i>	

Shipping and postage (inside U.S., Canada and Mexico only) will be prepaid by International. Prices quoted for U.S., Canada and Mexico orders only. Orders for shipment to other countries will be quoted on request. Address orders to:

M/S Dept., P.O. Box 32497,
Oklahoma City, Oklahoma 73132



INTERNATIONAL CRYSTAL MFG. CO., INC.
10 North Lee / Oklahoma City, Okla 73102

the dasher

Update your Vibroplex bug
by using the Dasher —
a simple circuit
that provides a continuous
series of dashes

Back about 1946, during my days as a commercial CW operator, I used to spend an eight-hour shift sending traffic in strings of 40 or more messages. Many of them were weather messages which had groups of five digits and many, many groups per message. I was getting a glass arm doing this at 40 words per minute or better every working day.

I saw a circuit in an Amateur magazine which used two tubes in a multi-vibrator circuit that could be mounted on top of a regular Vibroplex bug and would automatically make the dashes while you still get the dots from the mechanical side of your bug. I built and used one for years, saving my arm a thousand times over. It had the advantage that you could make the dashes much longer than the traditional 3 to 1 ratio. Therefore, you could retain your original sending style, yet send perfect code without fatigue.

Since then I haven't been too active — until recently when I got back into both MARS and CW work. That's when I remembered that silly thing I once built into a cake pan and mounted on top of my old Vibroplex.

Today, however, with all solid-state devices and small parts, one can be built in a small box, using a 9-volt battery for power. I used the 555 IC as a timer and a small 6-volt, dc-sensitive relay.

circuit description

Fig. 1 shows the circuit I used for the *Dasher*. In some circuits, pin 7 on the 555 was keyed. I tried this configuration but it caused a slight "hangover" on

By Joseph H. Fenn, KH6JF, 3612 Puuku Makai Drive, Honolulu, Hawaii 96818

the last dash of a train, making it very difficult to handle. I decided to try keying the 9-volt supply to the entire circuit, but this caused the first dash of a series to be stretched. Then, I tried leaving the 9 Vdc connected to all parts of the circuit and keying the lead to pin 8. This got rid of the problems, resulting in perfect dashes.

The two pots permit adjustment of both speed and weight. The only change needed on a Vibroplex bug is to disconnect the lead under the base from the dash contact post. Then, use a two-wire, shielded mike cable to provide three connections from the bug to the input of the *Dasher*. The shield forms one lead from the frame post of the bug, and the other two leads connect to the dot and dash contacts. Inside the *Dasher*, the lead from the dot contact is connected to the output lead, with the dash contact used to control the 555.

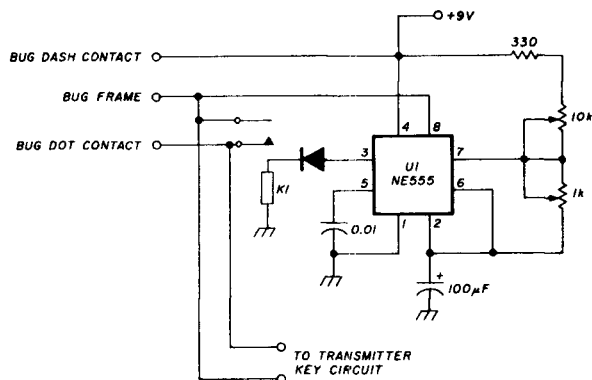


fig. 1. Circuit diagram of the *Dasher*. The relay is a small 6-volt unit available from Radio Shack. The diode can be any small signal switching diode.

Two things I might add for information. I used one of the rechargeable, 9-volt, ni-cad batteries and brought leads from the battery to screw terminals on the side of the box. This way I can connect a charger without opening the box. Also, a note of caution. Do not ground any of the 9-volt points to a ground that is common to the relay output or the bug common lead. When I tried the *Dasher* with my Collins KWM2A barefoot, no problems were encountered. However, when I ran the linear with a full kilowatt, rf was induced into the leads, causing erratic dash length. Putting ferrite beads on the input and output leads cured the problem. So have fun and don't end up with a glass arm; use the *Dasher*.

ham radio

FREQUENCY COUNTER KIT

Outstanding Performance

Incredible Price

\$89⁹⁵



CT-50

The CT-50 is a versatile and precision frequency counter which will measure frequencies to 60 mHz and up to 600 mHz with the CT-600 option. Large Scale Integration, CMOS circuitry and solid state display technology have enabled this counter to match performance found in units selling for over three times as much. Low power consumption (typically 300-400 ma) makes the CT-50 ideal for portable battery operation. Features of the CT-50 include large 8 digit LED display, RF shielded all metal case, easy pushbutton operation, automatic decimal point, fully socketed IC chips and input protection to 50 volts to insure against accidental burnout or overload. And, the best feature of all is the easy assembly. Clear, step by step instructions guide you to a finished unit you can rely on.

Order your today!

CT-50 60 mHz counter kit

CT-50WT 60 mHz counter, wired and tested

CT-600 600 mHz scaler option, add

\$89.95

\$159.95

29.95

CB-1 Color TV calibrator-stabilizer

DP-1 DC probe, general purpose probe

HP-1 High impedance probe, non-load

\$14.95

12.95

15.95

SPECIFICATIONS:

Frequency range: 6 Hz to 65 mHz, 600 mHz with CT-600

Resolution: 10 Hz @ 0.1 sec gate, 1 Hz @ 1 sec gate

Readout: 8 digit 0.4" high LED, direct readout in mHz

Accuracy: adjustable to 0.5 ppm

Stability: 2.0 ppm over 10 to 40 °C temperature compensated

Input: BNC, 1 megohm, 20 pF direct, 50 ohm with CT-600

Overload: 50VAC maximum, all modes

Sensitivity: less than 25 mV to 65 mHz, 50-150 mV to 600 mHz

Power: 110 VAC 5 Watts or 12 VDC @ 400 ma

Size: 6" x 4" x 2" high quality aluminum case, 2 lbs.

ICS: 13 units, all socketed

CAR CLOCK

The UN-KIT, only 5 solder connections

Here's a super looking, rugged and accurate auto clock, which is a snap to build and install. Clock movement is completely assembled—you only solder 3 wires and 2 switches, takes about 15 minutes! Display is bright green with automatic brightness control photocell—assures you of a highly readable display, day or night. Comes in a satin finish anodized aluminum case which can be attached 5 different ways using 2 sided tape. Choice of silver, black or gold case (specify)

DC-3 kit, 12 hour format

\$22.95

DC-3 wired and tested

\$29.95

110V AC adapter

\$5.95

Under dash car clock

12/24 hour clock in a beautiful plastic case features: 6 jumbo RED LEDs, high accuracy (1min/mo), easy 3 wire hookup, display blanks with ignition, and super instructions. Optional dimmer automatically adjusts display to ambient light level

DC-11 clock with mtg. bracket

\$27.95

DM-1 dimmer adapter

2.50

PRESCALER

Extend the range of your counter to 600 mHz Works with any counter. Includes 2 transistor pre-amp to give super sens, typically 20 mV at 150 mHz. Specify +10 or +100 ratio

PS-1B, 600 mHz prescaler

\$59.95

PS-1BK, 600 mHz prescaler kit

49.95

OP-AMP SPECIAL

741 mini dip

12/\$2.00

B1-FET, mini dip, 741 type

10/\$2.00

VIDEO TERMINAL

A completely self-contained, stand alone video terminal card. Requires only an ASCII keyboard and TV set to become a complete terminal unit. Two units available, common features are: single 5V supply, XTAL controlled sync and baud rates (to 9600), complete computer and keyboard control of cursor, Parity error control and display. Accepts and generates serial ASCII plus parallel keyboard input. The 3216 is 32 char. by 16 lines, 2 pages with memory dump feature. The 6416 is 64 char. by 16 lines, with scrolling, upper and lower case (optional) and has RS-232 and 20ma loop interfaces on board. Kits include sockets and complete documentation.

RE 3216, terminal card

\$149.95

RE 6416, terminal card

189.95

Lower Case option, 6416 only

13.95

Power Supply Kit

14.95

Video/RF Modulator, VD-1

6.95

Assembled, tested units, add

60.00

CALENDAR ALARM CLOCK

The clock that's got it all: 6-5" LEDs, 12/24 hour, snooze, 24 hour alarm, 4 year calendar, battery backup, and lots more. The super 7001 chip is used. Size: 5x4x2 inches

Complete kit, less case (not available)

\$34.95

DC-9

30 Watt 2 mtr PWR AMP

Simple Class C power amp features 8 times power gain: 1 W in for 8 out, 2 in for 15 out, 4 W in for 30 out. Max. output of 35 W incredible value, complete with all parts, less case and T-R relay.

PA-1, 30 W pwr amp kit

\$22.95

TR-1, RF sensed T-R relay kit

6.95

FM MINI MIKE KIT

A super high performance FM wireless mike kit! Transmits a stable signal up to 300 yards with exceptional audio quality by means of its built in electret mike. Kit includes case, mike, on-off switch, antenna, battery and super instructions. This is the finest unit available

FM-3 kit

\$12.95

FM-3 wired and tested

16.95

CLOCK KITS

our Best Seller
your Best Deal



Try your hand at building the finest looking clock on the market. Its satin finish anodized aluminum case looks great anywhere, while six 4" LED digits provide a highly readable display. This is a complete kit, no extras needed, and it only takes 1-2 hours to assemble. Your choice of case colors: silver, gold, bronze, black, blue (specify)

Clock kit, 12/24 hour, DC-5

\$22.95

Clock with 10 min. ID timer, 12/24 hour,

DC-10

27.95

Alarm clock, 12 hour only, DC-8

24.95

12V DC car clock, DC-7

27.95

For wired and tested clocks add \$10.00 to kit price.

Hard to find PARTS

LINEAR ICs		REGULATORS	
301	\$ 35	78MG	\$1.25
324	1.50	723	.50
380	1.25	309K	.85
380-8	.75	7805	.85
555	.45	78L05	.25
556	.85	7905	1.25
566	1.15	7812	.85
567	1.25	7912	1.25
1458	.50	7815	.85
3900	.50	TTL ICs	
4011	.20	74500	.35
4013	.35	7447	.65
4046	1.85	7475	.50
4049	.40	7490	.50
4518	1.25	74196TI	1.35
5369	1.75	SPECIAL ICs	
CMOS ICs		11C90	13.50
2N3904 type	10 1.00	10116	1.25
2N3906 type	10 1.00	4511	2.00
NPN 30W Pwr	3 1.00	5314	2.95
PNP 30W Pwr	3 1.00	5375AB	2.95
2N3055	.60	7001	6.50
UJT 2N2646 type	3 2.00	4059-N	9.00
FET MPF102 type	3 2.00	7208	17.95
UMF 2N5179 type	3 2.00	LEDs	
MRF-238 RF	11.95	Jumbo red	8 1.00
SOCKETS		Jumbo green	6 1.00
8 pin	10 2.00	Jumbo yellow	6 1.00
14 pin	10 2.00	Mini red	8 1.00
16 pin	10 2.00	Micro red	8 1.00
24 pin	4 2.00	BiPolar	.75
28 pin	4 2.00	FERRITE BEADS	
40 pin	3 2.00	With info. specs	15 1.00
		6 hole balun	5 1.00

Ramsey's famous MINI-KITS

FM WIRELESS MIKE KIT

Transmits up to 300' to any FM broadcast radio, uses any type of mike. Runs on 3 to 9V. Type FM-2 has added sensitive mike preamp stage

FM-1 kit **\$2.95**

FM-2 kit **\$4.95**

VIDEO MODULATOR KIT

Converts any TV to video monitor. Super stable, tunable over ch. 4-6. Runs on 5-15V, accepts std. video signal. Best unit on the market!

Complete kit, VD-1 **\$6.95**

tone decoder

A complete tone decoder on a single PC board. Features: 400-5000 Hz adjustable range via 20 turn pot, voltage regulation, 567 IC. Useful for touch-tone decoding, tone burst detection, FSK, etc. Can also be used as a stable tone encoder. Runs on 5 to 12 volts

Complete kit, TD-1 **\$5.95**

SUPER SLEUTH

A super sensitive amplifier which will pick up a pin drop at 15 feet! Great for monitoring baby's room or as general purpose amplifier. Full 2 W rms output, runs on 6 to 15 volts, uses 8-45 ohm speaker

Complete kit, BN-9 **\$5.95**

POWER SUPPLY KIT

Complete triple regulated power supply provides variable 6 to 18 volts at 200 ma and +5V at 1 Amp. Excellent load regulation, good filtering and small size. Less transformers, requires 6.3V @ 1 A and 24 VCT

Complete kit, PS-3LT **\$6.95**

COLOR ORGAN/MUSIC LIGHTS

See music come alive! 3 different lights flicker with music. One light for lows, one for the mid-range and one for the highs. Each channel individually adjustable, and drives up to 300W. Great for parties, band music, nite clubs and more

Complete kit, ML-1 **\$7.95**

LED Blinky KIT

A great attention getter which alternately flashes 2 jumbo LEDs. Use for name badges, buttons, warning panel lights, anything! Runs on 3 to 15 volts

Complete kit, BL-1 **\$2.95**

WHISPER LIGHT KIT

An interesting kit, small mike picks up sounds and converts them to light. The louder the sound, the brighter the light. Completely self-contained, includes mike, runs on 110VAC, controls up to 300 watts

Complete kit, WL-1 **\$6.95**

SIREN KIT

Produces upward and downward wail characteristic of a police siren. 5 W peak audio output, runs on 3-15 volts, uses 3-45 ohm speaker

Complete kit, SM-3 **\$2.95**

ramsey electronics

BOX 4072, ROCHESTER, N.Y. 14610

PHONE ORDERS CALL

(716) 271-6487



TERMS: Satisfaction guaranteed or money refunded. COD, add \$1.50. Minimum order \$6.00. Orders under \$10.00, add \$ 75. Add 5% for postage, insurance, handling. Overseas add 15%. NY residents add 7% tax.

formation of passive lumped constant 90-degree phase-difference networks

Construction details for designing equal amplitude, 90-degree, phase-difference networks

A variety of networks, both active and passive, have been used over the years for splitting a signal into two equal amplitude signals while maintaining a quadrature phase relationship between the two components. Roger Harrison's article¹ presented a number of such circuits and rekindled my interest in these devices. I first became interested in these circuits while designing image outphasing systems for sweeping microwave receivers about 20 years ago.^{2,3} At UHF and microwave frequencies, 90-degree phasing networks are readily achieved with coaxial or stripline hybrids which can be designed for bandwidths of several octaves. These distributed element hybrids become large and difficult to build for the lower frequencies. Sometimes, it is also desirable to have circuits capable of greater bandwidth.

I have prepared a table (see **table 1**) of prototype values from which passive, lumped-constant, first-order lattice networks (**fig. 1**) may be designed. This table is an adaptation of early work by Darlington² and later work by Bedrosian. Darlington's work is basic and requires background in network theory plus a comprehensive table of elliptic functions to arrive at a practical design. Bedrosian's³ paper included a number of tables of prototype values which can be used to calculate inductances, but you are stuck with the arbitrary bandwidths he chose unless you have access to a table of elliptic functions. Even then, there are several calculations to be done before arriving at a design. I have chosen a number of bandwidths which I believe would be

most useful for Amateur Radio users, 2 to 1 through 20 to 1.

network description

The phase-splitting networks consist of two separate lattice networks, a P-network and a Q-network. For a given bandwidth, the amount of phase ripple (deviation from 90-degree phase difference) depends upon the number of lattice sections, the more networks the smaller the deviations. N is the total number of lattice sections in both branches.

Although the first-order networks are simple, they may not be the most practical. This sometimes becomes apparent when you try to produce a pair of networks operating over a relatively broad range.

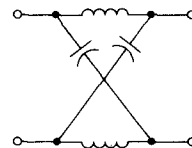


fig. 1. Diagram of a first-order lattice network.

You may discover that the networks, which are operating over the low-frequency end of the band as "all pass" networks, are also behaving at the higher frequencies like lowpass filters with a cut-off frequency within the design bandwidth. The reason for this is the self-capacitance of the inductors, which makes it difficult to place the self-resonance of the coils in the low-frequency lattices outside the design band.

Orchard⁴ presented a transformation whereby two first-order networks may be combined in a single second-order network as shown in **fig. 2**.

description and use of the table

Once you have determined the bandwidth required (ratio of upper to lower frequency) and the phase ripple that can be tolerated, you are ready to select the appropriate prototype design from the table. Assume a 3 to 30 MHz 90-degree network is needed, requiring

By R. B. Wilds, K6ZV, 14633 Ambric Knolls Road, Saratoga, California 95070

A True "State of the Art" System **INFO-TECH** **M-100E TRI-MODE CONVERTER**



**Converts
MORSE,
BAUDOT
& ASCII
to video**

CHECK THESE FEATURES:

- **Morse Reception**
6-60 wpm with automatic speed & workspace
- **RTTY Reception**
4 speeds, unshift on space select, auto. speed readout
- **ASCII Reception**
110 Baud only
(For RTTY and ASCII operation, requires
- demodulator for "off the air" reception. Interfaces directly with Dovetron or any demodulator with digital output.)
- **Video Outputs**
32 character line x 16 line video with scrolling
72 character line x 16 line video with scrolling

M-100E (32 character video) \$355.00

M-100E (72 character video) 375.00

For 230v 50-60hz add **10.00**

Order direct or from these dealers:

Advanced Electronics
1349 W. King Street
Cocoa, Florida 32922
305-631-1190

Cohoon Amateur Supply
Highway 475
Trenton, Kentucky 42286

Dialta Amateur Radio Supply
212 48th Street
Rapid City, S. Dakota 57701

Emona Electronics
661 George Street
Sidney N.S.W. Australia

Germantown Amateur Supply
3202 Summer Avenue
Memphis, Tennessee 38112
800-238-6168

Ham Radio Center
8342 Olive Blvd.
St. Louis, Missouri 63132
800-325-3636

N & G Distributors
7285 N.W. 12th St.
Miami, Florida 33126
305-592-9685

Rickles Electronics
2800 W. Meighan Blvd.
Gadsden, Alabama 35904
205-547-2534

Universal Amateur Radio
1280 Aida Drive
Reynoldsburg, Ohio 43068
614-866-4267

PANACOM
P.O. Box 76093
Caracas 107 Venezuela

Marcucci-SPA
via F. LLI-Bronzetti
Milan, Italy

INFO-TECH **INCORPORATED**
Specializing in Digital
Electronic Systems



2349 Weldon Parkway • St. Louis, Missouri 63141 • (314) 576-5489

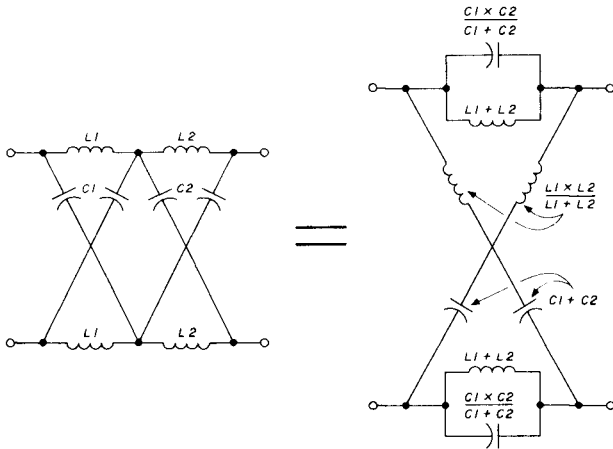


fig. 2. Transformation of a second-order to a first-order lattice network.

a phase deviation of less than two degrees. **Table 1** shows that a network with four lattice sections will yield a 10 to 1 bandwidth with a phase ripple of 1.08 degrees. **Table 1** also has normalized prototype values which are used to arrive at the actual designs.

denormalization and design

The lattice networks are denormalized for the geometric center frequency, in this case $\sqrt{3 \times 30} = 9.487 \text{ MHz}$. The inductances for the P network are calculated by:

$$L = \frac{P \text{ value } (Z_o)}{2\pi f_o} \quad (1)$$

where P = value from **table 1**

Z_o = characteristic impedance of network

f_o = geometric center frequency

table 1. Prototype values used for prototype designs.

BW ratio	N	phase tolerance	P1	P2	P3	Q1	Q2	Q3
2	2	1.687	0.405616			2.4654		
3	2	4.12254	0.3933			2.543		
3	4	0.0742	0.1859	1.539		0.65	5.38	
4	4	0.178	0.179	1.564		0.64	5.6	
4	5	0.03	0.142	1	7.04	0.476	2.1	
5	4	0.308	0.173	1.586		0.63	5.787	
5	5	0.06	0.137	1	7.3	0.466	2.15	
6	4	0.455	0.167	1.61		0.622	5.97	
6	5	0.1	0.133	1	7.54	0.456	2.19	
6	6	0.02	0.11	0.731	2.75	0.363	1.37	9.1
8	4	0.77	0.1585	1.64		0.6084	6.31	
8	5	0.184	0.1254	1	7.97	0.441	2.267	
8	6	0.044	0.1038	0.72	2.87	0.348	1.388	9.63
10	4	1.08	0.151	1.675		0.597	6.61	
10	5	0.28	0.1196	1	8.36	0.428	2.33	
10	6	0.07	0.0989	0.711	2.97	0.336	1.41	10.1
15	4	1.91	0.137	1.74		0.573	7.28	
15	5	0.577	0.108	1	9.25	0.403	2.48	
20	4	2.55	0.1285	1.79		0.559	7.78	
20	5	0.829	0.101	1	9.9	0.387	2.59	

You are now ready to complete the design using the P and Q values from **table 1**. For the P network assume $Z_o = 50$.

$$L_1 = \frac{P_1 \cdot Z_o}{2\pi f_o} = \frac{0.151 \times 50}{2\pi \times 9.487 \times 10^6} = 0.1267 \mu\text{H}$$

$$L_2 = \frac{1.675 \times 50}{59.6 \times 10^6} = 1.405 \mu\text{H}$$

$$C_1 = \frac{P_1}{Z_o \cdot 2\pi f_o} = \frac{0.151}{50 \times 59.6 \times 10^6} = 50.7 \text{ pF}$$

$$C_2 = \frac{1.675}{50 \times 59.6 \times 10^6} = 562 \text{ pF}$$

For the Q network:

$$L_1 = \frac{Q_1 \cdot Z_o}{2\pi f_o} = \frac{0.597 \times 50}{2\pi \times 9.487 \times 10^6} = 0.5 \mu\text{H}$$

$$L_2 = \frac{6.61 \times 50}{59.6 \times 10^6} = 5.54 \mu\text{H}$$

$$C_1 = \frac{Q_1}{Z_o \times 2\pi f_o} = \frac{0.597}{50 \times 59.6 \times 10^6} = 200 \text{ pF}$$

$$C_2 = \frac{6.61}{50 \times 59.6 \times 10^6} = 2218 \text{ pF}$$

Now the complete circuit can be sketched (see **fig. 3**). An example of an $N = 5$ network for the same bandwidth is shown in **fig. 4**.

The first-order lattice is a balanced circuit whose unbalanced equivalent requires the use of a transformer. Several types of balanced-to-unbalanced transformers, which are suitable for adapting the lattice to an unbalanced circuit, are described in reference handbooks. You have the option of choosing the impedance level of the lattices to effect the desired impedance match at the common junction of the networks.

theoretical and experimental results

The values for **table 1** were obtained from a BASIC computer program (PHASE90) which is capable of designing a wide range of first-order networks with bandwidths up to 100 to 1. Several designs from this program were analyzed using a BASIC (GNET) network analysis program and were found to perform as predicted.

Finally, to prove the usefulness of the theoretical design, a four-section ($N = 4$) network consisting of first-order lattices was built for the 20 to 150 MHz range. The phase deviations from 90 degrees were about 5 degrees, which is greater than the theoretical tolerance of 0.7 degree, but adequate for most requirements. This experimental data shows that the first-order lattices can be used for an 8 to 1 band-

FREQUENCY COUNTERS



COMPLETE KITS: CONSISTING OF EVERY ESSENTIAL PART NEEDED TO MAKE YOUR COUNTER COMPLETE. **HAL-600A** 7-DIGIT COUNTER WITH FREQUENCY RANGE OF ZERO TO 600 MHz. FEATURES TWO INPUTS: ONE FOR LOW FREQUENCY AND ONE FOR HIGH FREQUENCY; AUTOMATIC ZERO SUPPRESSION. TIME BASE IS 1.0 SEC OR .1 SEC GATE WITH OPTIONAL 10 SEC GATE AVAILABLE. ACCURACY $\pm .001\%$. UTILIZES 10-MHz CRYSTAL 5 PPM.

COMPLETE KIT \$129

HAL-300A 7-DIGIT COUNTER WITH FREQUENCY RANGE OF ZERO TO 300 MHz. FEATURES TWO INPUTS: ONE FOR LOW FREQUENCY AND ONE FOR HIGH FREQUENCY; AUTOMATIC ZERO SUPPRESSION. TIME BASE IS 1.0 SEC OR .1 SEC GATE WITH OPTIONAL 10 SEC GATE AVAILABLE. ACCURACY $\pm .001\%$. UTILIZES 10-MHz CRYSTAL 5 PPM.

COMPLETE KIT \$109

HAL-50A 8-DIGIT COUNTER WITH FREQUENCY RANGE OF ZERO TO 50 MHz OR BETTER. AUTOMATIC DECIMAL POINT, ZERO SUPPRESSION UPON DEMAND. FEATURES TWO INPUTS: ONE FOR LOW FREQUENCY INPUT, AND ONE ON PANEL FOR USE WITH ANY INTERNALLY MOUNTED HALTRONIX PRE-SCALER FOR WHICH PROVISIONS HAVE ALREADY BEEN MADE. 1.0 SEC AND .1 SEC TIME GATES. ACCURACY $\pm .001\%$. UTILIZES 10-MHz CRYSTAL 5 PPM.

COMPLETE KIT \$109

PRE-SCALER KITS

HAL 300 PRE \$19.95

(Pre-drilled G-10 board and all components)

HAL 300 A/PRE \$24.95

(Same as above but with preamp)

HAL 600 PRE \$34.95

(Pre-drilled G-10 board and all components)

HAL 600 A/PRE \$39.95

(Same as above but with preamp)

TOUCH TONE DECODER KIT

HIGHLY STABLE DECODER KIT. COMES WITH 2 SIDED, PLATED THRU AND SOLDER FLOWED G-10 PC BOARD. 7-567's, 2-7402, AND ALL ELECTRONIC COMPONENTS. BOARD MEASURES 3-1/2 x 5-1/2 INCHES. HAS 12 LINES OUT. ONLY \$39.95

DELUXE 12-BUTTON TOUCHTONE ENCODER KIT utilizing the new ICM 7206 chip. Provides both VISUAL AND AUDIO indications! Comes with its own two-tone anodized aluminum cabinet. Measures only 2-3/4" x 3-3/4". Complete with Touch-Tone pad, board, crystal, chip and all necessary components to finish the kit.

PRICED AT \$29.95

For those who wish to mount the encoder in a hand-held unit, the PC board measures only 9/16" x 1-3/4". This partial kit with PC board, crystal, chip and components.

PRICED AT \$14.95

ACCUKEYER (KIT) THIS ACCUKEYER IS A REVISED VERSION OF THE VERY POPULAR WB4VVF ACCUKEYER ORIGINALLY DESCRIBED BY JAMES GARRETT, IN QST MAGAZINE AND THE 1975 RADIO AMATEUR'S HANDBOOK.

PRICED AT \$16.95

ACCUKEYER — MEMORY OPTION KIT THIS ACCUKEYER MEMORY KIT PROVIDES A SIMPLE, LOW COST METHOD OF ADDING MEMORY CAPABILITY TO THE WB4VVF ACCUKEYER. WHILE DESIGNED FOR DIRECT ATTACHMENT TO THE ABOVE ACCUKEYER, IT CAN ALSO BE ATTACHED TO ANY STANDARD ACCUKEYER BOARD WITH LITTLE DIFFICULTY.

PRICED AT \$16.95

6-DIGIT CLOCK • 12/24 HOUR

COMPLETE KIT CONSISTING OF 2 PC G-10 PRE-DRILLED PC BOARDS, 1 CLOCK CHIP, 6 FND 359 READOUTS, 13 TRANSISTORS, 3 CAPS, 9 RESISTORS, 5 DIODES, 3 PUSH-BUTTON SWITCHES, POWER TRANSFORMER AND INSTRUCTIONS.

DON'T BE FOOLED BY PARTIAL KITS WHERE YOU HAVE TO BUY EVERYTHING EXTRA.

PRICED AT \$12.95

CLOCK CASE Available and will fit any one of the above clocks. Regular Price ... \$6.50 But Only \$4.50 when bought with clock.

SIX-DIGIT ALARM CLOCK KIT for home, camper, RV, or field-day use. Operates on 12-volt AC or DC, and has its own 60-Hz time base on the board. Complete with all electronic components and two-piece, pre-drilled PC boards. Board size 4" x 3". Complete with speaker and switches. If operated on DC, there is nothing more to buy.

PRICED AT \$16.95

Twelve-volt AC line cord for those who wish to operate the clock from 110-volt AC. \$2.50

SHIPPING INFORMATION

ORDERS OVER \$15.00 WILL BE SHIPPED POSTPAID EXCEPT ON ITEMS WHERE ADDITIONAL CHARGES ARE REQUESTED. ON ORDERS LESS THAN \$15.00 PLEASE INCLUDE ADDITIONAL \$1.00 FOR HANDLING AND MAILING CHARGES. SEND SASE FOR FREE FLYER.



"HAL"

HAROLD C. NOWLAND
W8ZXH

HAL-TRONIX

P. O. BOX 1101
SOUTHGATE, MICH. 48195
PHONE (313) 285-1782

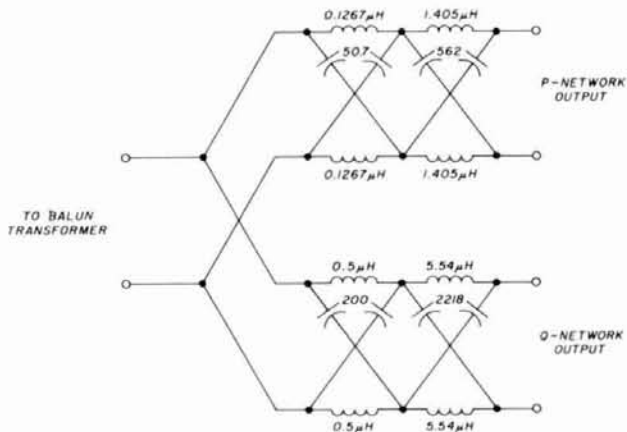


fig. 3. Component values for the 3 to 30 MHz, four-section network.

width. For greater bandwidths you may have to resort to the second-order lattice configuration.

acknowledgments

I am indebted to R. E. Booth, WB6SXV, who wrote the GNET network analysis program, and

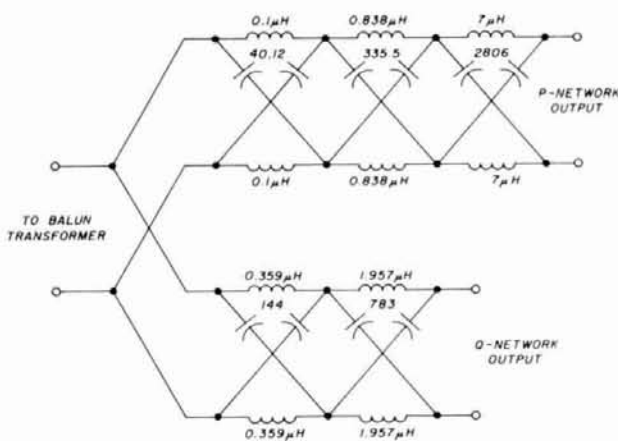


fig. 4. A five-section equivalent of the network shown in fig. 3.

whose assistance in writing the PHASE90 program is gratefully acknowledged.

references

1. Roger Harrison, VK2ZTB, "A Review of SSB Phasing Techniques," *ham radio*, January 1978, page 52.
2. R. B. Wilds, "An S-Band Two-Phase Demodulator," *1958 IRE WESCON Convention Record*, Part I, page 48.
3. R. B. Wilds, "Microwave Two-Phase Converters for Imageless Receivers," *Microwave Journal*, September 1961, page 84.
4. Sidney Darlington, "Realization of a Constant Phase Difference," *Bell System Technical Journal*, January 1950, page 94.
5. S. D. Bedrosian, "Normalized Design of 90-degree Phase Difference Networks," *IRE Transactions on Circuit Theory*, June 1960, page 128.
6. H. J. Orchard, "Synthesis of Wideband Two-Phase Networks," *Wireless Engineer*, March 1950, page 72.

ham radio

BULLET ELECTRONICS

P.O. Box 19442
Dallas, TX. 75219
(214)823-3240

UNIVERSAL SOUND EFFECTS BOARD

The SE-01 is a kit that contains all the parts needed to build a programmable sound effects generator. Designed around the new Texas Instruments 76447 Sound Chip, the board provides banks of Mini DIP switches and pots to program the various combinations of the SLF Oscillator, VCO, Noise, One Shot and Envelope Controls. Another IC is used to implement an Adjustable Pulse Generator, Level Comparator and Multiplex Oscillator for even more versatility. The 3 1/4" by 5" plated PC Board features a prototype area to allow for user added circuitry. Easily programmed to duplicate Explosions, Phasor Guns, Steam Trains, or an almost infinite number of other sounds, the unit has a multitude of applications. The \$16.95 price includes Assembly Manual, Programming Charts, and 76477 Chip specifications (speaker not included). Available from stock.

POWER SUPPLY KIT PS-14

- Better than 200mV load and line regulation
 - Foldback Current Limiting
 - Short Circuit Protected
 - Thermal Shutdown
 - Adjustable Current Limiting
 - Less than 1% ripple
 - 15 amps 11.5 to 14.5V
 - All parts supplied including heavy duty transformer
 - Quality plated fiberglass PC board.
- Less Case meters & jacks
UPS SHIPPING PAID!

REVIEWED IN 7/78 73 MAG.
15A CONT. 20A INT. 42.95

OVERVOLTAGE PROTECTION KIT 6.95

Provides cheap insurance for your expensive equipment. Trip voltage is adjustable from 3 to 30 volts. Overvoltage instantly fires a 25A SCR and shorts the output to protect equipment. Should be used on units that are fused. Directly compatible with the PS-12 and PS-14. All electron kits supplied. Drilled and plated PC board. (Color SVR 1)

NEVER A SWEETER METER!

Beautiful American made panel meters are a snap to install. Huge 3 1/2" wide dials are easy to read. You would expect to pay more for each than we get for the pair! MATCHED SET 0-15VDC, 0-30ADC.

12.95 *Set*

FANTASTIC SOUND EFFECTS CHIP

THIS 28 PIN CHIP CONTAINS A LOW FREQUENCY OSCILLATOR, VCO, NOISE OSCILLATOR, ONE SHOT MIMER AND ENVELOPE CONTROL. WITH 8 PAGE MANUAL. 3.95

LM3900 QUAD NORTON AMP

WE BOUGHT A LARGE QUANTITY OF THESE HOUSE NUMBERED PARTS AT A BARGAIN PRICE THAT ALLOWS US TO SELL THEM AT A LOW LOW.

3.95

EMITTER RESISTORS

HARD TO FIND

VALUES!

1 ohm @ 5W

25 ohm @ 5W

YOUR CHOICE

7/1.00

6 DIGIT ZULU CLOCK KIT

At last a clock for HAMS. Designed with large bright LED digits to enhance your shack. The unit is a pleasure to assemble and so easy on the budget! You get top quality parts and plated PC Boards. The unique design of the board set eliminates the headaches of running wires between clock and readout board. As a bonus the unit has a switchable timer that can be reset to zero without disturbing real time. Elapsed time in minutes and seconds up to 25 minutes. Six full sized FNDS10 readouts and coils making viewing easy from across the room. Does NOT use the old style 5314 chip. DUE TO A SPECIAL PURCHASE WE HAVE A LIMITED QUANTITY.

COMPLETE ZULU CLOCK KIT

Includes: All components, plated, drilled PC Boards, large easy to read instructions, and AC transformer. Clock board: 2 1/2" x 4 1/4". Readout Board: 1 1/2" x 4 1/4".

Hand made solid hardwood case for the Zulu Clock. Includes ruby front filter and back panel.

6.95

NO COD'S
SEND CHECK OR MONEY
ORDER OR CHARGE CARD NO.
ADD 5% FOR SHIPPING

TEX RESIDENTS ADD 5% TAX
FOREIGN ORDERS ADD 10%
ORDERS UNDER \$10
ADD 75¢ FOR HANDLING

PHONE ORDERS ACCEPTED ON VISA & MC

RTTY for ALL Systems



MODEL 400

ELECTROCOM® "SERIES 400" FREQUENCY SHIFT CONVERTERS

Professionally engineered for outstanding performance, stability, and reliability, the Electrocom® Models 400 and 402 add new dimensions of compatibility between radio and teletypewriter systems. Manufactured to highest quality standards—an Electrocom tradition for nearly two decades—these units are ideal for military, government, commercial, civil defense and amateur applications. The Model 400 front panel digital knob accurately selects shifts up to 1000 Hz., while two such knobs on the Model 402 independently set the mark and space frequencies. Both models may also be preset with any tone pair between 1000 and 3200 Hz.

Optimum performance with FSK or AFSK

systems is assured by matched filters, precision linear detectors, baud rate selector, bias compensation, and semi-diversity circuitry. Operation is enhanced by a CRT monitor, autostart with solid-state motor switching, antispacer, markhold, EIA/MIL output voltages, and a constant current loop supply. In addition, various options are available including rack mounting and polar current output.

Write or call us for complete product details and specifications. Learn why Electrocom® "400" Converters are designed not only for today's communication environment, but ultimately to fulfill RTTY requirements for years to come.

Electrocom® INDUSTRIES
1105 N. IRONWOOD DRIVE, SOUTH BEND, INDIANA 46615
Telephone: (219) 232-2743

THIS IS IT BIRD



MODEL 4431 THRULINE®

RF DIRECTIONAL WATTMETER
with VARIABLE RF
SIGNAL SAMPLER - BUILT IN
IN STOCK FOR PROMPT DELIVERY

AUTHORIZED DISTRIBUTOR

Webster
associates

115 BELLARMINE
ROCHESTER, MI 48063

CALL TOLL FREE

800 - 521-2333

IN MICHIGAN 313 - 375-0420

BUILD-IT-YOURSELF AVIONICS FOR HAM PILOTS

Free catalogue describes high technology, low cost avionics and test equipment offered in kit form. Product line includes audio panel, aircraft band two-channel transceiver, digital chronometer, navigation and communications test equipment, bench power supply, and more. Shoot us the coupon for details.

Name _____
Address _____
City _____ State _____ Zip _____

(916) 272-2203
**Radio Systems
Technology, Inc.**
RR 5, GRASS VALLEY, CA 95945

SUB-AUDIBLE GENERATOR for FM

THE CUBE



5 x 6 x 8 in.

- Inexpensive multi tone encoder
- Compatible with PL-CG-QC
- Low distortion sinewave
- Input 8-18 VDC unregulated
- Rugged, plastic encased with leads
- Adjustable frequency (98-250 Hz), Lower available
- Excellent stability

Price \$19.95

Freq. set at
factory
\$5.00 extra

Calif. res. add 6%

Send for more info

yle
Products

Dept. hr P.O. Box 2083 Santa Clara, CA. 95051



Puts the World at Your Fingertips

Get your antenna high enough with a TRI-EX tower and bring the world to you.

Receive signals which you have never heard before.

Send your call to other HAMS who have never heard you.

A TRI-EX tower will give you listening power ...calling power ...and stay-up power that means durability.

Durability comes from TRI-EX's 25 years of building quality towers. These years of experience combined with the latest engineering knowledge and materials are used to design and build towers which stay up under the antenna loads and wind speeds specified. After manufacture our steel towers are hot dipped in molten zinc (galvanizing). All exposed steel is covered inside and out — including the inside of tubing.

Our aluminum towers are self-resistant to corrosion. TRI-EX TOWERS makes them all: GUYED TOWERS, CRANK-UP TOWERS, FREE STANDING TOWERS, STACKED TOWERS.

And we will install a tower on your site, upon request.

Call, or write TRI-EX now for information on the right TRI-EX tower for you. We will send you our complete list of prices, delivery dates, installation information and the name of your nearest dealer. **Call TOLL FREE.**

Call our New Number
1-800-528-6050, Extension 1025

In Arizona, dial:
1-800-352-0458, Extension 1025



7182 Rasmussen Avenue, Visalia, California 93277

cabinet construction techniques

A new construction technique which allows the builder to build a cabinet to fit his equipment — rather than fitting his equipment into the cabinet

All builders of electronic devices eventually come up against a continuing problem — what type of cabinet to put their creation in. The magnitude of the problem increases in direct proportion to the dimensions desired. Commercially manufactured answers to the problem are few. If a cabinet is inexpensive, it is usually too small or flimsy; if it is rugged enough it will usually be too expensive. Trying to find a cabinet with the desired size and configuration often seems next to impossible. It has been my experience that few local dealers ever carry a large percentage of a cabinet manufacturer's total line. Therefore, mail order must be resorted to, which takes time.

Many times, the builder must choose "the best of the worst" from stock on hand and then tailor construction of the device to fit the cabinet. This practice usually results in unnecessary work and design trade-offs. Another problem that occasionally occurs is the need to increase or decrease the depth of a cabinet, something not easily accomplished. All of this adds up to what I call the "cabinet frustration syndrome."

What follows is an idea that evolved from attempts to solve these problems. The result is a rugged, inexpensive cabinet which is easy to construct in any needed size. Fabrication materials are universal in that they can be used for most any size cabinet. Most of the pieces from scrapped cabinets can be used again. With this method, the depth of the cabinet can be easily extended or reduced.


fabrication

The basic cabinet is made of only two items, the end plates and the end-plate support brackets. The end plates can be the front and rear panels of your unit or they can be subpanels, using a method to be described later. The two end plates are simply cut from aluminum sheet stock to the desired front-panel dimensions. A mounting hole for each bracket is drilled in each corner. The end-plate support brackets are the key to this whole method of construction. Bolted between the end plates, they provide cabinet rigidity, while at the same time allowing construction flexibility.

The brackets are made of aluminum U-channel, cut to the desired depth. Aluminum U-channel was chosen because it is light, relatively inexpensive, and readily available at most hardware stores. My first attempt, for which I used 12.5-mm (1/2 inch) U-channel, was acceptable but resulted in a more rugged (and heavier) cabinet than was necessary for that application. Cabinets built of 9.5-mm (3/8-inch) channel proved to be best for most of my uses.

Once the U-channel size is decided upon, the next step is to locate or fabricate something to lay in the channel that will accept the end-plate mounting screws. My junk box yielded some threaded metal standoffs about 5 cm (2 inches) in length. These fit snugly in the channel. The standoffs had a 10-32

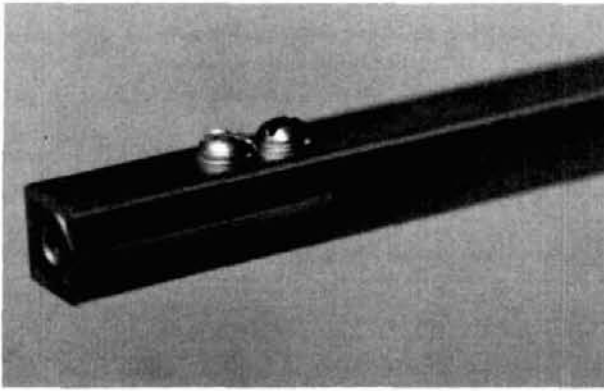By Bob Thompson, W7KDM, 12213 South Oneida, Phoenix, Arizona 85044




As seen in this photograph, the standoff was drilled and tapped for two additional holes, providing a means of securing the standoff in the channel stock.

(M5) threaded hole through their length. Two other mounting holes were drilled perpendicular to the length and tapped for a 10-32 (M5) thread. These holes are for bolting the standoffs to the U-channel.

If you don't have any standoffs, square aluminum stock is usually sold along with the U-channel. This can be cut to length, drilled, and tapped as necessary. Of course, the square stock can be cut to a length equal to the cabinet depth and used as the entire mounting bracket. In that case, only one hole must be drilled and tapped in each end. However, a solid bracket will have a few disadvantages when compared with the U-channel approach; it will be heavier, and it will offer less flexibility in the mounting of parts to the brackets.

Once each bracket has a standoff mounted at each end, the four brackets are bolted to the end plates, and the basic cabinet is finished! Component mounting plates can be above or below the brackets. If a center mounting plate is needed, this can easily be accomplished with L-brackets. Incidentally, a good source of L-brackets for any project is L-shaped

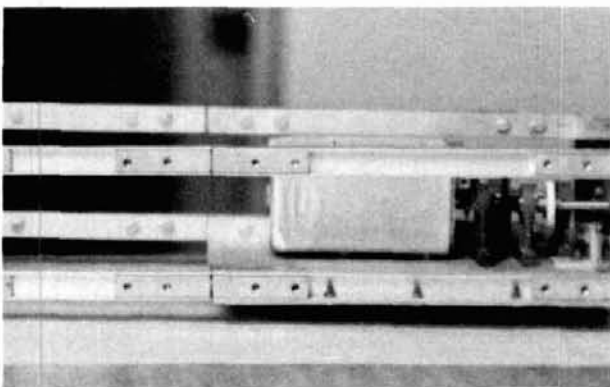
Example of a chassis that has been lengthened by using additional side bracket pieces.



aluminum stock, usually sold in the same place as the other materials. Merely cut the stock to the width of L-bracket desired. The L-bracket will be much stronger than one made by bending a piece of flat stock.

The basic cabinet is essentially a frame that can be covered by cutting and bending lightweight sheet aluminum. The design is such that the cover is not needed to provide the basic structural integrity and strength. This is a big problem with all but the most expensive commercial cabinets. Here again, the lightweight aluminum cover material is usually sold where all the other materials are.

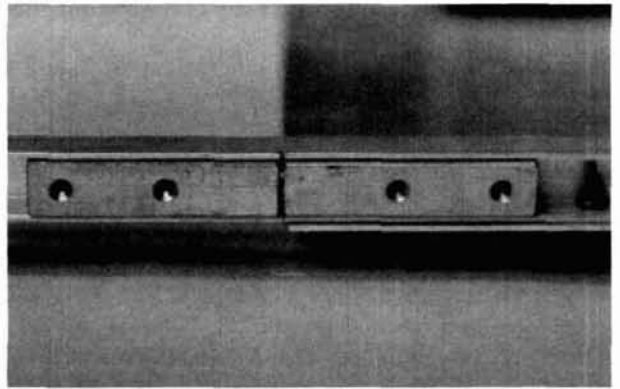Rather than making a cover by bending, cutting individual pieces of stock and attaching them to their respective sides with small screws is also a possibility. Where a heavier gauge metal will be used for the cover, it is possible to entirely eliminate the brackets.



Close-up of the connection between the two sections of a side bracket.

In this case, a central chassis plate is fastened to the end plates with L-brackets. Unless the cabinet is very small, the aluminum sheeting used for the end plates and chassis plate should be heavy enough to provide sufficient rigidity. Most of the aluminum that I use for chassis and end plates is 3 mm (1/8 inch) thick, although I've also used material 1.5 mm (1/16 inch) thick with success.

Aluminum sheeting is used because of its widespread availability and low cost. In the past, I have used some magnesium alloy sheet which provided excellent rigidity and light weight. The problem is, of course, that it is both expensive and difficult to come by.

As mentioned earlier, cabinets made with the U-channel technique can be easily lengthened or shortened. To shorten a cabinet, merely remove the standoffs from one end of each bracket, cut the brackets to the desired length, and remount the standoffs in the ends.

Clegg and



What a Combination!



Whether you're looking for a complete "TR-7 System," a TVI Filter, an Antenna Tuner or the famous Drake C-Line — If Drake makes it — Clegg has it!


Call us today for all of your Drake needs. CLEGG and DRAKE guarantee you'll be satisfied!

Clegg

Communications Corp.
1911 Old Homestead Lane
Lancaster, PA 17601
(717) 299-7221

The process of lengthening a cabinet is just a little more involved. If materials are available, just make longer brackets. However, if you don't have a piece of U-channel long enough to make four new brackets you can use four small pieces and add to the length of the existing bracket. This approach will require more work, but could be the most expedient and most economical under certain circumstances.

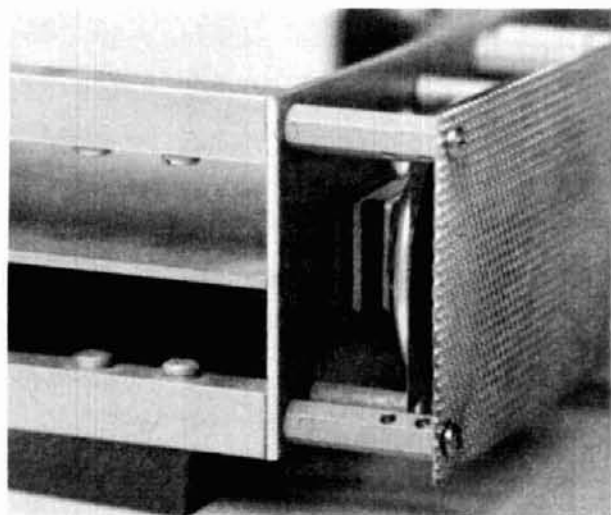First, cut and fashion four extension brackets for the desired added depth. Remove one of the end



This photograph illustrates a false panel speaker grille using standoffs mounted on an end plate.

plates. Insert adequate lengths of threaded screw stock (I favor 10-32 [M5]), into the ends of the brackets to be lengthened. Leave about 12.5 mm (1/2 inch) protruding. Screw the extension brackets onto the exposed screw stock. Now comes the only tricky part: when the two brackets are snugged up tight against each other, they should be aligned. If they do not align, insert a piece of metal shim stock or a thin washer between the two pieces and try again until alignment is achieved. Mount the other end plate on the extended brackets. If desired, one end plate can be used as a subpanel for false front panels or speaker grilles. This is accomplished with metal standoffs.

The only item which might prove difficult to procure is the aluminum sheet used for the chassis and end plates. Sheet metal dealers will usually sell remnants at scrap value. Scrap metal dealers sometimes have acceptable pieces. Your best bet is to get out and browse around to see what is available.

It's my hope that this article has provided you with a basic method (plus some variations) for relieving "cabinet frustration syndrome."

ham radio

Vhf engineering

DIVISION OF BROWNIAN ELECTRONICS CORP.

EFFECTIVE
JANUARY 1979

THE WORLD'S MOST COMPLETE LINE OF VHF-FM KITS AND EQUIPMENT

RX28C	28-35 MHz FM receiver with 2 pole 10.7 MHz crystal filter	\$ 64.95
RX28C W/T	same as above—wired & tested	129.95
RX50C Kit	30-60 MHz rcvr w/2 pole 10.7 MHz crystal filter	64.95
RX50C W/T	same as above—wired & tested	129.95
RX144C Kit	140-170 MHz rcvr w/2 pole 10.7 MHz crystal filter	74.95
RX144C W/T	same as above—wired & tested	131.95
RX220C Kit	210-240 MHz rcvr w/2 pole 10.7 MHz crystal filter	74.95
RX220C W/T	same as above—wired & tested	131.95
RX432C Kit	432 MHz rcvr w/2 pole 10.7 MHz crystal filter	84.95
RX432C W/T	same as above—wired & tested	142.95

RECEIVERS



RXCX	accessory filter for above receiver kits gives 70 dB adjacent channel rejection	9.95
RF28 Kit	10 mtr RF front end 10.7 MHz out	13.50
RF50 Kit	6 mtr RF front end 10.7 MHz out	13.50
RF144D Kit	2 mtr RF front end 10.7 MHz out	18.50
RF220D Kit	220 MHz RF front end 10.7 MHz out	18.50
RF432 Kit	432 MHz RF front end 10.7 MHz out	29.50
IF 10.7F Kit	10.7 MHz IF module includes 2 pole crystal filter	29.50
FM455 Kit	455 KHz IF stage plus FM detector	18.50
AS2 Kit	audio and squelch board	16.00

TX50 Kit	transmitter exciter, 1 watt, 6 mtr.	44.95
TX50 W/T	same as above—wired & tested	71.95
TX144B Kit	transmitter exciter—1 watt—2 mtrs	34.95
TX144B W/T	same as above—wired & tested	65.95
TX220B Kit	transmitter exciter—1 watt—220 MHz	34.95

TRANSMITTERS



TX220B W/T	same as above—wired & tested	65.95
TX432B Kit	transmitter exciter 432 MHz	49.95
TX432B W/T	same as above—wired & tested	87.95
TX150 Kit	300 milliwatt, 2 mtr transmitter	24.95
TX150 W/T	same as above—wired & tested	43.95

POWER AMPLIFIERS

PA2501H Kit	2 mtr power amp—kit 1w in—25w out with solid state switching, case, connectors	69.95
PA4010H Kit	2 mtr power amp—10w in—40w out—relay switching	69.95
PA50/25 Kit	6 mtr power amp, 1w in, 25w out, less case, connectors & switching	59.95
PA144/15 Kit	2 mtr power amp—1w in—15w out—less case, connectors and switching	49.95
PA144/25 Kit	same as PA144/15 kit but 25w	59.95
PA220/15 Kit	similar to PA144/15 for 220 MHz	49.95
PA432/10 Kit	power amp—similar to PA144/15 except 10w and 432 MHz	59.95



Blue Line	RF power amp, wired & tested, emission—CW-FM-SSB/AM			
	Model	Band	Power Input	Power Output
	BLC 10/70	144 MHz	10W	70W 149.95
	BLC 2/70	144 MHz	2W	70W 174.95
	BLC 10/150	144 MHz	10W	150W 269.95
	BLC 30/150	144 MHz	30W	150W 249.95
	BLD 2/60	220 MHz	2W	60W 164.95
	BLD 10/60	220 MHz	10W	60W 169.95
	BLD 10/120	220 MHz	10W	120W 269.95
	BLE 10/40	420 MHz	10W	40W 159.95
	BLE 2/40	420 MHz	2W	40W 189.95
	BLE 10/80	420 MHz	10W	80W 289.95

POWER SUPPLIES

PS15C Kit	15 amp—12 volt regulated power supply w/case, w/fold-back current limiting and overvoltage protection	99.95
PS15C W/T	same as above—wired & tested	134.95
PS25C Kit	25 amp—12 volt regulated power supply w/case, w/fold-back current limiting and overvoltage protection	139.95
PS25C W/T	same as above—wired and tested	169.95
PS25M Kit	same as PS25C with meters	159.95
PS25M W/T	same as above—wired and tested	189.95



O.V.P.	adds over voltage protection to your power supplies, 15 VDC max.	14.95
PS3A Kit	12 volt—power supply regulator card with fold-back current limiting	11.95
PS3012 W/T	new commercial duty 30 amp 12 VD regulated power supply w/case, w/fold-back current limiting and overvoltage protection	274.95

REPEATERS

RPT50 Kit	repeater—6 meter (less crystals)	599.95
RPT50 W/T	repeater—6 meter, wired & tested	899.95
RPT144 Kit	repeater—2 mtr—15w—complete (less crystals)	599.95
RPT220 Kit	repeater—220 MHz—15w—complete (less crystals)	599.95
RPT432 Kit	repeater—10 watt—432 MHz (less crystals)	649.95
RPT144 W/T	repeater—15 watt—2 mtr	899.95
RPT220 W/T	repeater—15 watt—220 MHz	899.95
RPT432 W/T	repeater—10 watt—432 MHz	949.95



DPLA50	6 mtr close spaced duplexer	680.00
DPLA144	2 mtr, 600 KHz spaced duplexer, wired and tuned to frequency	409.95
DPLA220	220 MHz duplexer, wired and tuned to frequency	409.95
DPLA432	rack mount duplexer	379.95
DSC-U	double shielded duplexer cables with PL259 connectors (pr.)	29.95
DSC-N	same as above with type N connectors (pr.)	34.95

TRANSCIEVERS

TRX50 Kit	Complete 6 mtr FM transceiver kit, 20w out, 10 channel scan with case (less mike and crystals)	259.95
TRX144 Kit	same as above, but 2 mtr & 15w out	259.95
TRX220 Kit	same as above except for 220 MHz	259.95
TRX432 Kit	same as above except 10 watt and 432MHz	284.95
TRC-1	transceiver case only	34.95
TRC-2	transceiver case and accessories	54.95



OTHER PRODUCTS BY VHF ENGINEERING

CD1 Kit	10 channel receive xtal deck w/diode switching	\$ 8.95
CD2 Kit	10 channel xmit deck w/switch and trimmers	16.95
CD3 Kit	UHF version of CD1 deck, needed for 432 multi-channel operation	14.95
COR2 Kit	carrier operated relay	23.95
SC3 Kit	10 channel auto-scan adapter for RX with priority	21.95
Crystals	we stock most amateur grade pairs from 146.0—147.0 (each)	5.00
CWID Kit	159 bit, field programmable, code identifier with built-in squelch tail and ID timers	42.95
CWID	wired and tested, not programmed	59.95
CWID	wired and tested, programmed	64.95
MIC1	2,000 ohm dynamic mike with P.T.T. and coil cord	13.95
TS1 W/T	tone squelch decoder	59.95
TS1 W/T	installed in repeater, including interface accessories	94.95
TD3 Kit	2 tone decoder	39.95
TD3 W/T	same as above—wired & tested	64.95
HL144 W/T	4 pole helical resonator, wired & tested, swept tuned to 144 MHz ban	34.95
HL220 W/T	same as above tuned to 220 MHz ban	34.95
HL432 W/T	same as above tuned to 432 MHz ban	34.95

SYNTHESIZERS

SYN II Kit	2 mtr synthesizer, transmit offsets programmable from 100 KHz—10MHz, (Mars offsets with optional adapters)	169.95
SYN II W/T	same as above—wired & tested	239.95
SYN 220 Kit	same as SYN II Kit except 220-225 MHz	169.95
SYN 220 W/T	same as above—wired & tested	239.95



Vhf engineering

DIVISION OF BROWNIAN ELECTRONICS

Prices and specifications subject to change without notice.

ERICKSON'S MOVED!

Come in and see our new,
bigger, and better store.
Just a few blocks south of
our old location.

YOU'LL FIND the best from

- AEA • Ameco • ASP • Atlas
- Belden • Bencher • Bird
- CDE • CIR • CES • Cushcraft
- DenTron • Drake • Hy-Gain
- Icom • KLM • Kenwood
- Larsen • MFJ • Midland
- Mosley • NPC • Newtronics
- Nye • Palomar • Regency
- Shure • Swan • Standard
- Tempo • Ten-Tec • Tonna
- Transcom • Wilson • Yaesu

NEAR CHICAGO?

COME IN AND SEE US!



Tim WB8SBL and Mike WN9ANF
serving you!



CALL TOLL FREE
FOR THE ERICKSON PRICE!

ILLINOIS, OUTSIDE 312: (800) 972-5841
OUTSIDE ILLINOIS: (800) 621-5802



Hours:

9:30-5:30 Mon., Tues., Wed. & Fri.

9:30-9:00 Thursday

9:00-3:00 Saturday




ERICKSON

COMMUNICATIONS, INC.

5456 N. MILWAUKEE AVE

CHICAGO, IL 60630 (312) 631-5181

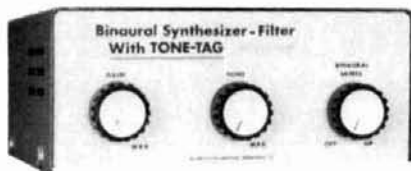

NEW - IMPROVED*

Model 1500 - Binaural Synthesizer-Filter with Tone-Tag
Uses 8 "D" Cells - Less Batteries \$86.00 ppd, U.S.

Model 1501 - Requires your 12 to 15 volt DC input, 100 ma.
nom. (internal regulation) \$89.00 ppd, U.S.

Wall Transformer 115V AC supply rated at 12 volts, 350 ma.
for use with Model 1501 or . . . \$4.95

*A new balanced bipolar Tone-Tag modulator system replaces diode modulators of Models 1100 and 700

GET BETTER THAN 100 HZ EFFECTIVE SELECTIVITY ON CW, A SELECTABLE NOISE BANDWIDTH OF LESS THAN 150 HZ PLUS PERIPHERAL HEARING IN BINAURAL SOUND . . . ALL WITHOUT LISTENING THROUGH THE TINKLING ROAR OF A NARROW-BAND FILTER OR FUSSING WITH SELECTIVE SQUELCH SYSTEMS. . . EXPERIENCE THE BINAURAL FUNCTION ON SIDE BAND VOICE . . . Just connect to your receiver's headphone or speaker jack and plug in two 8 Ohm speakers arranged stereo fashion . . . additional jack provided at lower power to protect your stereo headset.

See HR magazine articles on Nov. '75 and Nov. '76 . . . Ask for our note on listening with binaural and Tone-Tag systems

HILDRETH ENGINEERING BOX 60003 SUNNYVALE CA 94088

CURTIS LSI's help you



speak MORSE

- ★ 8044; Keyer-On-A-Chip* (Replaces 8043). \$14.95
Apr '75 HR, Feb '76 QST, Radio Hdbk '75, Apr Hdbk '77-78
- ★ 8044-3; IC, PCB, Socket, Manual 24.95
- ★ 8044-4; Semi-Kit 54.95
- ★ 8045; Morse Keyboard-On-A-Chip IC . . . 59.95
- ★ 8045-1; IC, PCB, FIFO, Sockets, Manual . . 89.95
- ★ 8045-2; Semi-Kit 159.95
- ★ 8046; Instructokeyer-On-A-Chip IC 49.95
- ★ 8046-1; Semi-Kit 79.95
- ★ 8047; Message Memory-On-A-Chip IC . . . 39.95
- ★ 8047-1; IC, PCB, RAM, Sockets, Manual . . 69.95

(add \$1.75 on above for postage and handling)
EK-430; CMOS Keyer* (Feb '76 QST) 124.95
IK-440A; Instructokeyer* (Mar '76 QST) . . . 224.95
*now with dash memory as standard
System 4000 Ham Computer (see Jan '78 QST) (write)

Curtis Electro Devices, Inc.
Dept. H (415) 964-3136
Box 4090, Mountain View, CA 94040



HI-Q BALUN

- For dipoles, yagis, inverted vees, doublets & quads
- For full legal power & more
- Puts power in antenna
- Broadbanded 3-40Mhz.
- Small, light, weather-proof
- 1:1 Impedance ratio
- Replaces center insulator
- Helps eliminate TVI
- Fully Guaranteed



\$9.95
PPD
U.S.A.
Van Gorden Engineering
BOX 21305, S. EUCLID, OHIO 44121

Govt. SURPLUS ELECTRONIC EQUIPMENT CATALOG

New ITEMS . . . New BARGAINS!
FREE UPON REQUEST!
Send today for FREE copy of
NEW CATALOG WS-79. Address Dept. HR

FAIR RADIO SALES
1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802



*our little boxes
replace a lot of cable!*

- select any of five antennas at the turn of a knob, with just one feedline and a control cable to the remote switching unit •
- saves coax, simplifies station layout •
- handles 4 kw p.e.p. •
- other models to nine positions •
- full one-year warranty •

model sw-5 heavy duty -
REMOTE CONTROLLED ANTENNA SWITCH - \$135.00 plus \$3 shipping
• order direct or write for brochure •

ANTENNA MART 515-292-7114
box 1010, i.s.u. station, ames, iowa 50010



MICROWAVE MODULES LTD.

432 MHz Linear Transverter

UP YOUR FREQUENCY!



Put your 28Mhz Transceiver to work at 432MHz!!

- EXTRA RANGE (434-436 Mhz) for Satellite operation.
- 10 Watts RMS output power.
- Simple Frequency Range Selection Using Toggle Switches.
- Highly Stable Regulator Controlled Crystal Oscillator Stages.
- 30 dB Receive Gain.
- Better than 3.0dB Noise Figure.
- Antenna Changeover Achieved by Low Loss Pin Diode Switch.
- 50 Mhz and 144 Mhz IF's Available.

MMT432/28-S — PRICE: \$329.95 INCLUDING SHIPPING

144 MHz Linear Transverter

Join the Fun on 2 Meter Sideband — using your 28MHz Transceiver.

- 10 WATTS RMS OUTPUT POWER
- 30dB RECEIVER GAIN
- BETTER THAN 2.5dB NOISE FIGURE
- 50 Mhz IF's AVAILABLE



MMT 144/28 — Price 259.95 INCLUDING SHIPPING

432 MHz LINEAR AMPLIFIER 100 WATTS OUTPUT

ALL MODE



RF VOX

10dB Minimum Gain

- 100% Duty Cycle Rated
- FULLY PROTECTED VSWR OVERHEATING, REVERSE POLARITY

MML 432/100 — PRICE **449.95** INCLUDING SHIPPING

432-436 Dual Range Receiving Converter



MMC 432/28S
Price 95.95

INCLUDING SHIPPING

- OSCAR, MODE J RECEPTION
- 30dB GAIN
- BETTER THAN 3.0dB NOISE FIGURE
- IF's AVAILABLE 28-30Mhz, 144-146Mhz

GUARANTEE

ALL MICROWAVE MODULES PRODUCTS ARE GUARANTEED FOR 1 YEAR. IN ADDITION, THEY MAY BE RETURNED WITHIN 10 DAYS FOR A FULL REFUND IF YOU ARE NOT SATISFIED FOR ANY REASON.

TEXAS RF DISTRIBUTORS IS THE EXCLUSIVE IMPORTER OF MICROWAVE MODULES PRODUCTS, AND WE SUPPLY A COAST-TO-COAST DEALER NETWORK. WRITE OR PHONE FOR DETAILS OF THESE PRODUCTS AND THE OTHER VHF AND UHF MICROWAVE MODULES PRODUCTS WHICH WE STOCK.

TEXAS RF DISTRIBUTORS, INC.


CARL — WSUPR

JOE — WA5HNK



Exclusive U.S.A. Distributors of Microwave Modules Products

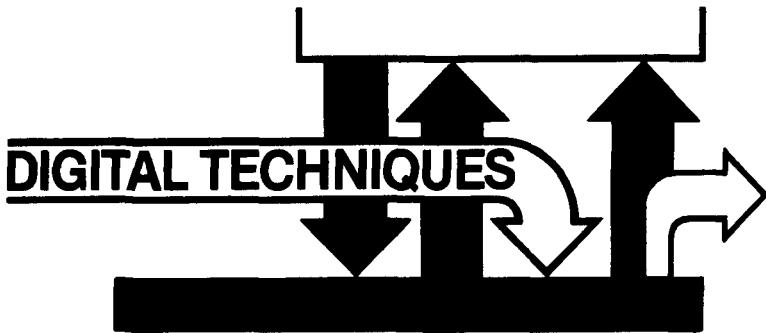4800 WEST 34TH STREET • SUITE D12A
HOUSTON, TEXAS 77092
PHONE 713/680-9797 • TELEX 791 322



digital circuits — propagation delay and flip-flops

So far, the basic gate has been examined under dc or static conditions. This part will discuss dynamic conditions of switching, propagation delay, and the most simple flip-flop, the latch.

All digital devices have delay from internal charge storage. Input and output may switch rapidly, but the delay between input transition and output transition is usually longer than the transition itself. Fig. 1 is an example of dynamic conditions in a simple inverter.

The term t_p or t_d is associated with propagation delay and will have a number of different subscript letters to distinguish different types of delay. A table in the front of the Texas Instruments *TTL Data Book* lists most of them. The term *propagation* is used, since the input-to-output path within a device may go through several stages.

The inverter shows only two delays. t_{pLH} is the input transition-to-low delay to output transition-to-high state; t_{pHL} is the opposite. They may occur at different times. Measurement is made at half amplitude between maximum low-level voltage and minimum high-level voltage.

Output-state transition time is also listed, almost always at a specified load of maximum capacity. Load capacity affects output transition delay strongly but has only a slight effect on propagation delay.

Multi-function devices have a number of different delays. Data sheets must be carefully studied to understand the effect of delays on the overall circuit. Lack of understanding of delays can waste a lot of debugging time (most times are too short to measure on inexpensive scopes) and also can cause a circuit to fail entirely. Delay time can't be underestimated!

By Leonard H. Anderson, 10048 Lanark Street, Sun Valley, California 91352

the RS latch flip-flop

Fig. 2 shows the block symbol, waveforms, and an equivalent circuit constructed of NAND gates. The *RS* term comes from reset/set. A flip-flop is a bi-stable circuit (stable in two conditions) and is either set or reset by an external input. Because it's bi-stable, it's said to be latched in one state or the other.

The circuit of fig. 2 has active low set and reset inputs, indicated by inversion bubbles on the symbols. Outputs are not shown with bubbles, since the flip-flop is a bistable device.

Flip-flop terminology sometimes refers to the Q output as true, \bar{Q} as false, or NOT. Output-to-input cross-connection would appear to create an oscillator. This would be true with linear devices, but it's the key to holding a bistable condition with digital devices.

Assume initial conditions of both inputs and Q high, \bar{Q} low. NAND gate G1 is held high by the low from G2. G2 is held low since both inputs are high (the *NAND RULE*). The initial state is stable. Either output could have been high at power turn-on, depending on which gate was the fastest.

The first \bar{S} low input does nothing; G1 is already held high. The first \bar{R} low will force G2 high. G1 then

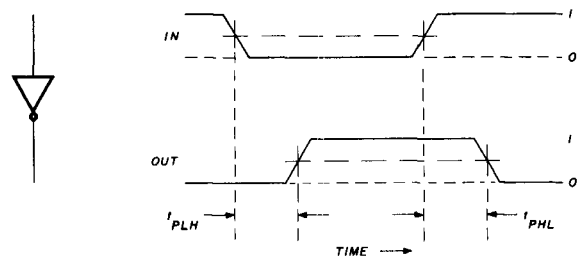


fig. 1. Propagation delay of an inverter.

goes low, since all inputs are high and the latch has flipped to a reset condition (Q low). This is the other stable condition.

Note the exaggerated time delays and sequence of changes. Each input must hold at a low state long enough for both gates to change state. Flip-flop spec sheets will give this parameter of time as t_{hold} .

A following \bar{R} low will do nothing; the latch is already reset. A second \bar{S} low will force G1 high. G2 will go low since all inputs are high; the latch has flopped into a set condition.

What happens if both inputs are low? Both outputs will be forced high as long as that condition persists. The unknown condition occurs when both inputs return high. Either stable condition could occur and, as in power-on, it depends on which gate is the fastest. This is the indeterminate state and should be avoided.

a switch debouncer

All switches and relays, except for mercury wetted types, have contact bounce. Contact bounce is the opening and closing of contacts because of mechanical vibration. It lasts between 0.2 and 50 milliseconds, depending on construction, and can raise havoc with certain digital circuit inputs; a cure is found in fig. 3.

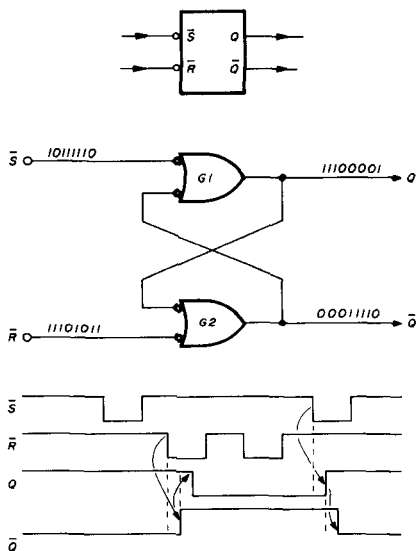


fig. 2. Simple RS flip-flop latch symbol, circuit, and waveform.

The RS latch is an interface between the switch and controlled circuit. The grounded switch arm provides the active low latch input signal. Pull-up resistors provide a high state for open contacts. The 4.7k pull-up is for TTL; CMOS values can range from 56k to 270k.

Contact bounce still exists, but the controlled circuit does not see it. The first contact closure will flip the latch. Subsequent bounce will not affect the latch as long as the switch is break-before-make. Compare this circuit with that of fig. 2 for full understanding.

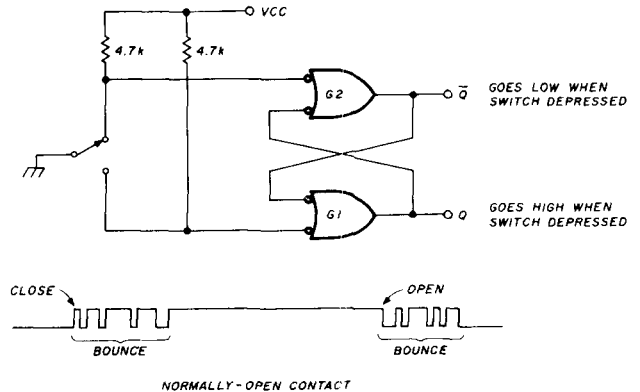


fig. 3. Switch debouncer.

Fig. 3 could be made with CMOS NOR gates, switch arm to V_{CC} and pull-down resistors. Try this on scratch paper. A hint: Use the gate truth tables in Part 1.1 The same thing won't work well with TTL. Why?

The difference lies in the high-TTL logic-0 current. Pull-down resistors would have to be 180 ohms or less for 0.4 volt maximum at 1.6 mA. It's fine if you can afford to waste 28 mA when the pull-down is connected to V_{CC} . A 4.7k pull-up resistor wastes only 1.1 mA.

Can a single-throw switch be substituted? The thought comes to mind that an inverter could be used for the other latch input. Sorry, this won't work; the same bounce is repeated in the latch. A single-throw switch can be applied only to static switching inputs or those unaffected by bounce.

clocked flip-flops

The term *clock* refers to a timing signal and came from early computer work, when the clock synchronized all functions. Applied to flip-flops, the clock input is really a trigger to initiate a change of state.

Fig. 4 shows the most common clocked flip-flops, the JK and D, in symbolic form with truth tables. Two things should be noted here: These truth tables are time-dependent, and the clock input may or may not have an inversion bubble. The clock edge is the trigger. A positive-going (low-to-high) edge is shown direct as in the D flip-flop. A negative-going (high-to-low) edge is shown with the bubble.

J, K, or D inputs are control or data inputs. Each truth table shows the effect of these inputs on the Q

**BUILD
YOUR DREAM
ANTENNA:**

**YOUR
WISH IS OUR
COMMAND!**

JUST TELL US WHAT YOU
NEED — WE SUPPLY ALL THE
MATERIALS, AND YOU HAVE ALL
THE FUN! ASK ABOUT OUR CUSTOM
ANTENNA PACKAGES.

- 6061-T6 DRAWN ALUMINUM TUBING
- AIRCRAFT-GRADE PLATED HARDWARE
- HIGH-STRENGTH FIBERGLASS SPREADERS
- STAINLESS-STEEL ELEMENT CLAMPS

Call or write for FREE information
(414) 583-4001



ROUTE 1, BOX 10G
BROWNSVILLE, WI
53006



LUMITIME



CC-24 Digital Alarm Clock
U.L. APPROVED

24 hour numerals and 24 hour alarm. The illuminated orange bar numerals are 1-5/8" high. Also featured are new slim line styling, catnap control and an illuminated constantly changing kaleidoscopic pattern to indicate continuous operation. Available in Beige or Charcoal-Brown case colors. Size: 2-1/4" x 4-1/8" x 8-3/4" **\$27.95**



MADISON
ELECTRONICS SUPPLY, INC.
1508-D MCKINNEY • HOUSTON, TEXAS 77002
713/658-0268



output after receipt of a clock edge. If both J and K are held low, Q of the JK does not change. This is indicated by Q_n . Holding one low and one high will force the 0 and 1 condition. With both high, Q will flip to the state opposite what it was before the clock edge arrived. This is what \bar{Q}_n means.

The D flip-flop is easier to understand. Its Q state takes the D input state after receiving a clock edge.

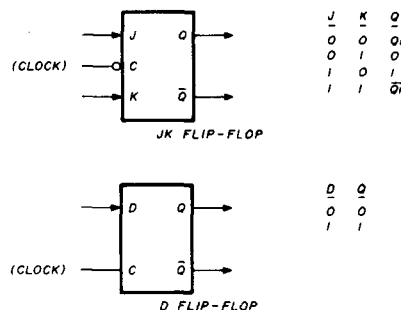


fig. 4. Symbols and truth tables for the basic clocked flip-flops.

Both flip-flops will change Q based on the control input state before a clock edge occurs. Control inputs do not directly affect output.*

Clocked flip-flops require an additional time parameter: setup. J, K, and D states must exist a specific minimum number of nanoseconds before a desired clock edge occurs. Too short a setup time will result in skipping a clock period for a Q state change.

An output state change is sometimes called toggling. A JK with both inputs high will toggle on each clock. Output period will be twice clock period, and the flip-flop becomes a divide-by-two device. Connecting \bar{Q} to D in a D flip-flop will accomplish the same function.

Both flip-flops may have direct set and reset inputs. These override any clock input and may occur at any time. As such they're sometimes called asynchronous. Terms vary and set is sometimes *preset*; reset is sometimes called *clear*.

The next part of this series will look inside clocked flip-flops, present NAND gate circuits, and discuss timing.

*Some old JK types did flip when both J and K changed together with the same state.

reference

1. Leonard H. Anderson, "Digital Techniques, Basic Rules and Gates," *ham radio*, January, 1979, page 76.

ham radio

Call Toll Free 1-800-243-7765

FREE

• Retail Price Catalog • Monthly
Computerized Used Equipment List



KENWOOD TS-820S



YAESU FT-901



ICOM IC-701




KDK 2015R



IC-701



TEN TEC OMNI-D

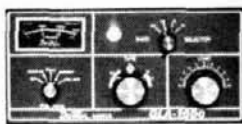

GLA-1000



CPU 2500 R-K

OVER 50 BRANDS IN STOCK

- KENWOOD • SWAN • KDK • DENTRON •
- MOSLEY • WILSON • YAESU • DRAKE •
- LARSEN • BENCHER • PIPO • BEARCAT •
- B & W • DATONG • ICOM • PANASONIC •
- ARRL PUBLICATIONS • ALLIANCE • MFJ •
- CUSHCRAFT • TRAC • MICROLOG • CDE •
- FINCO • DSI • DAYBURN INSULATORS •
- BIRD • ASTATIC • HAM KEY • REGENCY •
- HUSTLER • SAXTON • TEN TEC • AMECO •
- AMCOMM • CALL BOOK • KLM • TEMPO •
- ROHN • BUTTERNUT • Plus Many More!

- ★ NEW AND USED EQUIPMENT
"Get on our used equipment mailing list"
- ★ TRADES WELCOME
"The best allowances anywhere"
"We buy good used SSB gear"
- ★ FREE CATALOG
"Prices of all major manufacturers"
- ★ SAME DAY U.P.S. SHIPPING
"Just a phone call away"
- ★ COMPLETE RADIO SERVICE SHOP
"Mail Order Repair Service"

- Fast Efficient Service • We Repair All Brands
- All Work Guaranteed • Amateur Extra/First Class Licenses • Send Us Your Defective Equipment U.P.S. Collect • Free Shipping Both Ways If Work Is Done
- Most Repairs Done and Shipped Within 7 Days

OUR FINE REPUTATION SPEAKS FOR ITSELF

"YOU SHIP IT
WE FIX IT"

THOMAS COMMUNICATIONS

Call
or Write
for your
super quote
today!

95 Kitts Lane, Newington, Conn. 06111

"Near ARRL Headquarters"

Connecticut Residents Call:
(203) 667-0811



OPEN MON.-FRI. 10-6 • THURS. 10-8 P.M. • SAT. 10-4

EASY DIRECTIONS: Rt. 15 South — 2 blocks past McDonald's
(Berlin Turnpike)

multi-filter


ALL MODE ACTIVE FILTER AND SIGNAL PROCESSOR

- OPTIMUM 2100 Hz BANDWIDTH NEW STANDARD FOR SSB INTELLIGIBILITY
- ALL FEATURES NEEDED FOR THE MOST DISCRIMINATING CW OPERATOR
- Contest proven reliability, features and ease of use
- Slim package, 7" x 7" x 3/4", fits under, on top of or along side of any rig.
- Heavy, anodized aluminum case is RF tight
- Logic output (CMOS) of processed CW drives digital Morse Code reader or microprocessor.
- Professional quality design, components and construction.

- 3 FILTER MODES—Up to 12 poles of active filtering
- ATTENUATION: 45 dB @ 2400Hz—70 dB @ 3600Hz
- 1—SSB MODE) 2100Hz cut off for optimum intelligibility
- 2—VARIABLE MODE) Proprietary circuit adds independently adjustable filter for bandpass or notch within the selected passband.

Frequency adjustable 300—1800Hz
Bandwidth adjustable 25—450Hz
3—CW MODE) Allows super CW reception. Peak or null with as low as 25Hz bandwidth
• CW processing and regeneration with tone and volume controls gives perfect copy conditions.

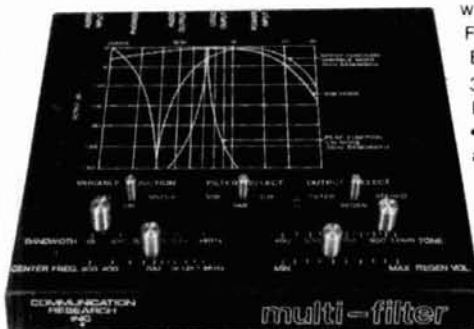• Unique stereo function produces the regenerated CW in one channel and the filtered audio in the other channel yielding a dynamic spectrum of signal perception.



COMMUNICATION RESEARCH INC. • \$149.95 including power supply, cable and shipping

3 GREAT PASTURE ROAD
W. REDDING, CT 06896
(203) 938-2273



Regency Scanner

BRINGS YOU THE NEWS WHILE ITS HAPPENING



10 channels covering all 5 bands. AC/DC operation.

SAVE \$40 **\$89.95**
LIST-\$129.95



1,000's OF CRYSTALS

- H25C Case Scanner Monitor
- 10.7 Amateur Ham
- 2 Meter, CB, Standard

1 to 9 **\$3.70** 10 to 49 **\$3.00** 50 and UP **\$2.50**

CRYSTAL BANKING SERVICE
P.O. BOX 683
LYNNFIELD, MASS. 01940

THE BIG SIGNAL UNADILLA W2AU Baluns

DEMANDED BY PROFESSIONALS WORLD-WIDE OVER 12 YEARS

- The Original Lightning Arrest
- 650" Strength
- Stainless Hardware
- Sealed
- GUARANTEED



FULL-POWER, QUALITY HAM ANTENNA PARTS

AT YOUR DEALER

- BALUNS - TRAPS - INSULATORS
- QUAD PARTS - ANTENNA KITS
- BOOM/MAST MOUNTS - WIRE
- CABLE - CONNECTORS

WRITE FOR FULL CATALOG [Enclose 30c Stamps]

UNADILLA/REYCO DIVISION [Dept. HR]
375 KINNE STREET EAST SYRACUSE, NEW YORK 13207

DEALERS WANTED - OVER 300 WORLD-WIDE

TEST EQUIPMENT

All equipment listed is operational and unconditionally guaranteed. Money back if not satisfied. Prices listed are FOB Monroe.

- Boonton 190A Q mtr 20 260MHz Q 5 1200 395
 - GR1001A Stand sig gen 5kHz -50MHz calib atfn 255
 - HP170A (USM140) 30MHz scope with reg horiz, dual trace vert plugs 475
 - Tek565 Dual beam 10MHz scope less plug-ins (3 series) 625
 - URM25 Stand Sig Gen 10kHz-50MHz calib atfn 225
 - Weinschel 70 Prec RF atfn DC 1ghz 0 60db, 1db steps 4w 395
- Lists outdated. Write specifying test equipment needs. Quick response assured.

GRAY Electronics
P.O. Box 941, Monroe, Mich. 48161
Specializing in used test equipment.

Barry Electronics . . .

Your One Source for Amateur Radio Gear

Yes — In Stock!

ATLAS 210X / 215X & 350XL — SSB/CW transceivers for hf bands mobile or fixed
TEMPO S-1 SYNCOM — synthesized 2-m FM hand held

We also have

- ANTENNAS FOR HF & UHF
- ROTORS
- TOWERS
- REPEATERS
- MICROPHONES
- KEYS & KEYERS
- TUBES and much, much more

JUST CALL OR WRITE FOR THE BARRY PRICE; BETTER STILL... STOP IN!!

Yes, we have EIMAC Tubes & Chimneys, and YAESU Replacement Tubes in stock! Repair lab on premises.


WE STOCK THESE FAMOUS NAME BRANDS

- | | | |
|---------------------|------------|-------------|
| AEA | DRAKE | ROBOT |
| ALDA | EIMAC | ROHN |
| ANTENNA SPECIALISTS | E-Z WAY | STANDARD |
| ATLAS | HY-GAIN | SWAN |
| B & W | ICOM | TEMPO |
| BIRD | KDK | TEN-TEC |
| COLLINS | KLM | TRI-EX |
| CUSHCRAFT | MFJ | VHF |
| DSI | MIRAGE | ENGINEERING |
| DENTRON | MOSLEY | WILSON |
| | NEWTRONICS | YAESU |

BARRY ELECTRONICS

512 BROADWAY
NEW YORK, N. Y. 10012

(212) 925-7000

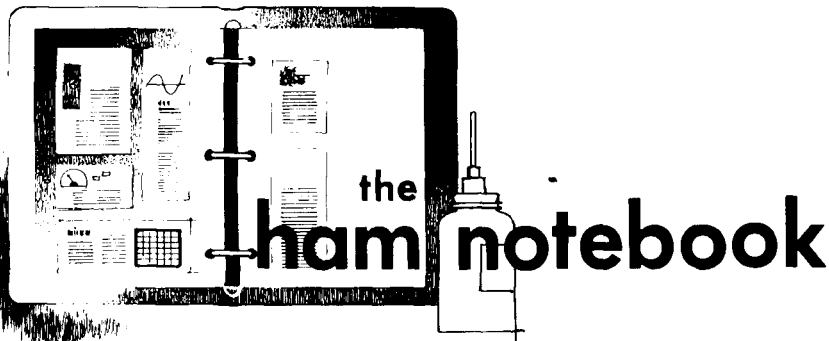

the ham notebook

integrated circuit tone generator

The MK5085/86 as shown in the February, 1977, issue of *ham radio*, can be used to make a very simple, inexpensive, and reliable tone encoder. In fact, with the exception of the addition of the transmitter keying relay and driver transistor, the circuits shown have been taken directly from the Mostek data sheet.

A couple of additional comments are in order, however. First, it is usually inadvisable to feed the encoder's output into the microphone line as indicated in the article. The pre-emphasis in the audio amplification circuits will distort the level differential between the high and low group tones, which should be on the order of 3 dB. Thus, the levels actually transmitted, *i.e.*, presented to the decoders at the receiver, will not be correct and decoding difficulty may result. In order to use the microphone input, some kind of rolloff circuitry is necessary, and this adds to the complexity of the overall encoder.


A second problem with using the microphone input is that of background noise; the tones receive as much amplification as the ambient noise. Since the output of the MK5085/86 is on the order of 700 millivolts for the low group and 1100 millivolts for the high group, these high-level signals do not need high amplification.

The chip was primarily designed for telephone application, and to feed a load of approximately 600 ohms. In

the telephone application, a convenient output load is the telephone line itself. However, the line is also the power source. With this background, it is easy to see that the chip really prefers to deliver its output right into the power line. Using an independent power source, this characteristic can

power where the 12-volt line enters the rig, and not directly from the rig's power supply. The temptation to do the latter may be great in view of the less-than-10 volts allowed by the MK5085/86. The diode in **fig. 1** is not really necessary if power is taken directly from the car battery, but it

fig. 1. Diagram of the method used to eliminate tones from the power line.

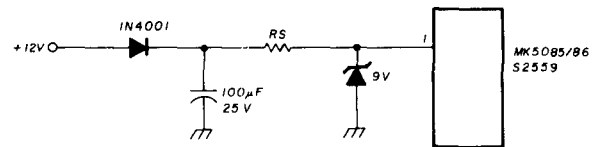


be ignored. Powered from the radio, however, the effect will be to modulate the entire primary power. In short, the tones will wind up in all kinds of places where you don't want them.

A simple solution is shown in **fig. 1**. A large capacitor will swamp the tones, provided the power source impedance is low enough; take

should be noted that the MK5085/86 is (mostly) CMOS and can generate appreciable spikes.

I prefer the AMI S2559 over the Mostek 5085/86 primarily because of its ability to stand power of up to 15 volts, eliminating the need for the zener and dropping resistor shown in **fig. 1**. The S2559 is pin-compatible with the Mostek chips and can direct-

fig. 2. Schematic of a more satisfactory method for generating a variable dropout time. CR1 through CR3 are all 1N914 diodes. R3 is an appropriate current limiting resistor for the LED used. The maximum operating current permissible for the relay is 150 mA. Varying the 1-megohm resistor will change the dropout time from approximately 0.1 to 1 second.

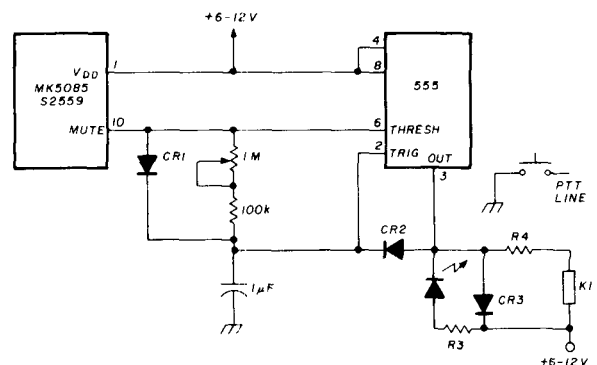

ly replace them. It is also driven from the standard 3.58-MHz color-burst crystal. Aside from the wider power tolerance (down to 3 volts or so), there is yet another advantage: The S2559 can be used with either a Class A or 2-of-8 (or 2-of-7) DTMF keyboard. The choice of which Mostek chip to use is dictated by the keyboard key configuration.

A final observation concerns the transmitter keying arrangement shown in the article. It will work, and is simple and inexpensive, but it does have a potential drawback. The two-second time delay is too long (easily changed by choice of capacitance), but it is not very constant or reliable. This could cause problems when the circuit is used with an autodialer or repertory dialer.

In my opinion, a better (and only slightly more expensive) arrange-

is low, holding the threshold voltage at pin 6 of the 555 low. The trigger voltage at pin 2 of the 555 is also low, the capacitor having discharged through the timing resistors. The 555 output, pin 3, is high (because trigger went low), charging the capacitor through CR2. This does not change the timer state, even though trigger is now high, because threshold stays low. The 555 is stable in this state: threshold low, trigger high, output high, and capacitor charged. K1 is not energized.

When a key is pressed, the MUTE output from the encoder goes high, tripping the threshold of the 555 and driving the output low. This energizes K1. Full charge is maintained on the capacitor through CR1. When the key is released, the capacitor begins to discharge through the timing resistors. If no key is pressed before the

CR3 is transient suppression for K1. I found it useful to use a relatively low-voltage relay with series resistance because (a) I got a real buy on 5-volt reed relays and (b) by adjusting the resistor the timing circuit will operate down to the lower functional limit of the 555 and the S2559. The LED and its associated series resistor are optional.

If this timing circuit is used with the MK5085/86, an 82k resistor should be used in series with CR1. The MUTE output current is capable of providing 10 μ A. (The S2559 will provide a couple of mils.) However, since the capacitor never discharges below 1.3 Vcc and because the majority of charging current comes from the 555, the 82k resistor suggested isn't really required. However, it is cheap insurance to protect an \$8.20 IC.

It is preferable to use a pot in series with the encoder output (see fig. 3). This provides both level adjustment and isolation concurrently. Taking the output from a pot in the output emitter line (as shown in the article) is not recommended, as it more greatly affects the impedance the chip is working into. I have found a 25K pot to be about the right value, using it in place of the 20k isolation resistor previously mentioned.

One final thought: A useful addition would be to short out the microphone (or open the microphone audio line) when the encoder is active, eliminating background noise. This can be done in a variety of ways, the most obvious being to use another pole on the keying relay connected to the 555 timer.

Concerning the relay, the 10 mA operating current does *not* include the relay current. Care must be taken if a 9-volt battery is used; they're not made to drive current-hungry devices like relays. Also, the 10 mA figure is with Vdd equal to 6 volts, but the circuit shows a 9-volt source. Under these conditions the current will be around 20-25 mA.

Frank Bates, W6IPB

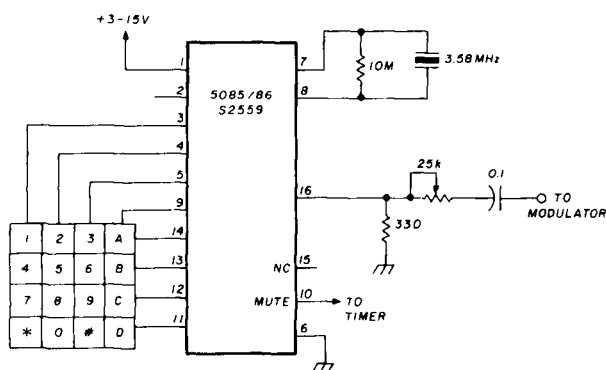


fig. 3. Circuit for a complete tone decoder. The AMI S2559 is a pin-for-pin replacement, featuring the capability of a higher input voltage, 15 vs 10 volts. Pin 15 is grounded for dual tones only. When left open, a single tone is generated when two keys in the same row or column are generated. For all practical purposes, the 330-ohm load resistor on pin 16 can remain the same value when Vdd is changed, though the optimum value is 270 ohms for a 12-volt supply and 628 ohms for a 5-volt supply. If an audible side tone is desired, a 4- to 8-ohm speaker can be inserted in the supply line.

ment can be made using the work-horse 555 timer. The circuit, as shown in fig. 2, gives an easily adjustable hang time of from 0.1 second, to about 1.1 seconds, by adjusting the 1 megohm pot in series with the 100k fixed resistor. Once set, the hang time is extremely consistent.

The circuit works as follows. With no key pressed, the MUTE output at pin 10 of the MK5085/86/AMIS2559

capacitor discharges to 1/3 Vcc (approximately one time constant) the 555 triggers, returning the 555 to its previously stable state. The capacitor recharges virtually instantaneously through CR2. If another key is pressed before the capacitor discharges to 1/3 of Vcc, it immediately recharges to full voltage through CR1 and remains there until the key is released.

RADIO AMATEUR CALLBOOKS



Respected worldwide as
the only complete authority
for radio amateur
QSL and QTH information.

The U. S. Callbook has nearly 350,000 W & K listings. It lists calls, license classes, names and addresses plus the many valuable back-up charts and references you come to expect from the Callbook.

Specialize in DX? Then you're looking for the Foreign Callbook with almost 285,000 calls, names and addresses of amateurs outside of the USA.

U.S. Callbook \$15.95

Foreign Callbook \$14.95

(Plus Shipping)

Order from your favorite electronics dealer or direct from the publisher. All direct orders add \$1.75 for shipping. Illinois residents add 5% Sales Tax.

RADIO AMATEUR
callbook INC
Dept. E 925 Sherwood Drive
Lake Bluff, Ill. 60044

TR-7400A "KENWOOD" OWNERS: SCANNER KIT

- Installs completely inside rig. No obtrusive external connections.
- Scans the complete band or only the portion you select on the MHz switch of your rig (e.g. 144-148 or 146-148 MHz).
- Scan frequency is displayed on digital readout.
- Two miniature toggle switches supplied with kit (scanner: on-off, scan-lock may be mounted externally or on the top or bottom cover of the rig).
- In the scanner off mode the TR-7400A behaves normally. In the scanner ON mode the scanner locks up on an occupied frequency, pauses for a preset time (3-30 seconds) and then resumes scanning. This means you can eavesdrop all over the band without lifting a finger. When you hear something interesting you flip the switch to the lock mode and the rig is ready to transmit.
- Scans at the rate of 50 kHz per second.
- Complete with detailed instructions (even for the beginner).

Kit **\$39.95** Preassembled **\$59.95**
add \$1.50 postage and handling



AED ELECTRONICS

750 LUCERNE RD., SUITE 120, MONTREAL, QUEBEC, CANADA H3R 2H6
TEL. 514-737-7293



FT-227 "MEMORIZER" OWNERS: SCANNER KIT

- Selectable sweep width (up to full band).
- Scans **only** the portion of band you select.
- Scans at the rate of 200 kHz per second.
- Switch modification on mike allows you to scan past, or lock on, any occupied frequency.
- Complete kit with detailed instructions.
- Installs **inside** rig; no obtrusive external connections.
- Rig can easily be returned to original condition whenever desired.
- Scans to preset limits and reverses.
- Automatic bypass of locked frequency in 3-1/2 seconds unless you press lock-on switch.
- You can eavesdrop all over the band without lifting a finger.

Kit **\$34.95** preassembled and tested **\$54.00**
add \$1.50 postage and handling

IC-22S Scanner Kits also available
Kit **\$34.95; \$54.00** assembled.
add \$1.50 postage and handling

dealer inquiries invited

GERMAN DEALER

I'm looking for a wholesaler or manufacturer of transceivers and of all other accessories for Amateur Radio and CB. If you are interested in direct export to Germany, please send us your proposal.

I am also interested in taking charge of an outlet, for example a dealership carrying your items, if possible with your participation.

Amateur- und CB-Funk
Ortenberger Str. 58, P.O.B. 2226
D 7600 Offenburg, West Germany
Karl Rauchalles, DF 9 UK

"RUBBER DUCKIES"

FROM

g & c Communications

A MUST FOR 2-METER HAND HELDS

Model	Description	Price
GC-1	5/16" Knurled Stud: Fits Icom, Motorola and many others	\$ 6.50
GC-2	BNC Connector	\$ 9.98
GC-3	TNC — Connector for Wilson 1405	\$13.98
GC-4	PL-259 Connector	\$ 6.50
GC-5	Type F Connector fits Wilson 1402 and Tempo	\$ 9.50

Equipment made in USA by OEM MFRS
Send to
GC-2 **G & C COMMUNICATIONS**
730 Cottonwood, Lincoln, NE 68510
Add \$1.00 for handling and shipping
(Dealer and OEM RFQ's Welcome)

Iron Powder and Ferrite TOROIDAL CORES

Wide selection — Large stock
Fast, one-day service
Technical data with each order
Write for free Tech-Data Flyer

AMIDON
Associates

12033 Otsego Street, North Hollywood, Calif. 91607

In Germany: Elektronikladen, Wilhelm — Mellies Str. 88, 4930 Detmold 18, West Germany
In Japan: Toyomura Electronics Company, Ltd., 7-9, 2-Chome Sota-Kanda, Chiyoda-Ku, Tokyo, Japan



NEW!**NEW!****NEW!**

FM2016A

All Solid State-CMOS PL digital synthesized - No Crystals to Buy! 5KHz steps - 144-149 MHz-HUGE 3/8" LED digital readout PLUS MARS-CAP and MULTIPLE OFFSET BUILT IN.

- 5 MHz Band Coverage - 1000 Channels (instead of the usual 2 MHz to 4 MHz-400 to 800 Channels)
- 4 CHANNEL RAM IC MEMORY WITH SCANNING AND AUTO TRANSMIT
- MULTIPLE FREQUENCY OFFSETS
- ELECTRONIC AUTO TUNING - TRANSMIT AND RECEIVE
- INTERNAL MULTIPURPOSE TONE OSCILLATOR
- RIT
- RF ATT
- DISCRIMINATOR METER - 16 Watts Output-Unequaled Receiver Sensitivity and Selectivity - 15 POLE FILTER, MONOLITHIC CRYSTAL FILTER AND AUTOMATIC TUNED RECEIVER FRONT END, COMPARE!
- Superb Engineering and Superior Commercial Avionics Grade Quality and Construction Second to None at ANY PRICE.

**INTRODUCTORY
PRICE**
\$359⁰⁰

Regulated AC/PS
Model FMPS-4R . . . \$39.95



FMMS-1* Micro-
phone with Built-in
Touch Tone Pad.

WHY BUY LESS?

**THE FMMS-1
HAS IT ALL!**

- New! Auto key up
- Snap-Action Keyboard
- Adj. level and tone balance
- Use with any transceiver
- Only 3 1/2" x 2" \$39.95

SHOWN WITH OPTIONAL μ P-800 MICRO-PROGRAMMER*

- **FREQUENCY RANGE:** Receive and Transmit: 144.00 to 148.995 MHz, 5 KHz steps (1000 channels) + MARS-CAP and MULTIPLE OFFSET BUILT IN.
- **HUGE 3/8" LED DIGITAL READOUT.**
- **4 CHANNEL RAM SCANNER WITH IC MEMORY AND AUTO TRANSMIT:** Program any 4 frequencies and reprogram at any time using the front panel controls—search for occupied (closed) channel or vacant (open) channels. Internal Ni-Cad included to retain memory (no diode matrix to wire or change).
- **MULTIPLE FREQUENCY OFFSETS: NO CRYSTALS TO BUY - EVER -** Any offset any split! "Odd Ball" splits accomplished by digital programming. Never any need for crystals!
- **INTERNAL MULTIPURPOSE TONE OSCILLATOR BUILT IN:** Sine Wave 1750 Hz tone burst for "whistle on operation" and sub-audible tone operation. Internal 2 position switch for automatic and manual operation, tone burst or sub-audible tone PL - adjustable 60-203 Hz (100 Hz Pre-Set).
- **AIRCRAFT TYPE FREQUENCY SELECTOR:** Large and small coaxially mounted knobs select 100KHz and 10KHz steps respectively. Switches click-stopped with a home position facilitate frequency changing without need to view LED's while driving and provides the sightless amateur with full Frequency Selection as standard equipment.
- **FULL AUTOMATIC TUNING OF RECEIVER FRONT END AND TRANSMITTER CIRCUITS:** DC output of PLL fed to varactor diodes in all front end RF tuned circuits provides full sensitivity and optimum intermodulation rejection over the entire band. APC(AUTO POWER CONTROL) - Keeps RF output constant from band edge to band edge. NO OTHER AMATEUR UNIT AT ANY PRICE has these features which are found in only the most sophisticated and expensive aircraft and commercial transceivers.

- **TRUE FM:** Not phase modulation - for superb emphasized hi-fi audio quality second to none.
- **RIT CONTROL:** Used to improve clarity when contacting stations with off frequency carrier.
- **MONITOR LAMPS:** 2 LED's on front panel indicate (1) incoming signal-channel busy, and (2) Transmit.
- **FULLY REGULATED INTEGRAL POWER SUPPLY:** Operating voltage for all 9v circuits independently regulated. Massive Commercial Hash Filter.
- **MODULAR COMMERCIAL GRADE CONSTRUCTION:** 3 Unitized modules eliminate stray coupling and facilitate ease of maintenance.
- **ACCESSORY SOCKET:** Fully wired for touch tone, phone patch, and other accessories. Internal switch connects receiver output to internal speaker when connector is not in use.
- **MULTI-PURPOSE METER:** Triple Function Meter Provides Discriminator Meter, "S" Reading on receive and Power Out on Transmit.
- **RECEIVE:** Better than .25uv sensitivity, 15 POLE FILTER as well as monolithic crystal filter and AUTOMATIC TUNED LC circuits provide superior skirt selectivity - COMPARE!
- **HIGH/LOW POWER OUTPUT:** 16 watts and 1 watt, switch selected. Low power may be adjusted anywhere between 1 and 16 watts. Fully protected - short or open SWR.
- **RF ATT:** Live right next to King Kong Repeater and can't operate? With the 2016A You Can - Just flick the RF ATT switch. Only the 2016A has this feature.
- **OTHER FEATURES:** Dynamic Microphone, built in speaker, mobile mounting bracket, external 5 pin accessory jack, speaker jack, and much, much more. Size 2 1/2 x 7 x 7 1/2. All cords, plugs, fuses, microphone hanger, etc. included. Weight 5 lbs.

Regional Sales & Service Centers
East: Sanford Communications, Inc.
Colonia, N.J.
(201) 574-3003
Northeast: Buzzards Bay Electronics
Buzzards Bay, Mass.
(617) 759-3376
West: The Radio Shop
Riverton, Utah
(801) 254-0991
Northwest: Action Supply, Inc.
Boise, Idaho
(208) 344-5084
Midwest: Universal Service
Columbus, Ohio
(614) 866-4267
South: Electronic Communications
Highland Springs, Virginia
(804) 737-5100

Manufactured by one of the world's most distinguished Avionics manufacturers, Kyokuto Denshi Kaisha, Ltd.
First in the world with an all solid state 2 meter FM transceiver.

AMATEUR-WHOLESALE ELECTRONICS

8817 S.W. 129th Terrace, Miami, Florida 33176
Telephone (305) 233-3631 • Telex: 51-5628
U.S. DISTRIBUTOR

DEALER INQUIRIES INVITED



NEW products

For literature on any of the new products, use our *Check-Off* service on page 118.

NDI 800-channel 2-meter transceiver



NDI, Incorporated, of Torrance, California, has announced the HC-1400, a new, high-performance 2-meter fm mobile transceiver of advanced design. This microprocessor-controlled, digitally synthesized unit has 800-channel capability within the Amateur 144-148 MHz band, and offers 5- or 10-kHz channel spacing. A fast-acting, single-knob selector shifts LED digital frequency readout in 10-kHz steps; the HC-1400 also has a 100-kHz "speedup" button.

Transmit frequency offsets are pre-programmed, and are switchable to plus or minus 600 kHz. Simplex operation is also available. The HC-1400 can be programmed to hold three transmit-receive frequency pairs in memory, with the capability of instant recall. The transmitter delivers 25 watts output, and requires 13.8 Vdc for operation.

The receiver is sensitive, selective, and uses an FET front-end with three coaxial resonators. The dual i-f has a crystal lattice filter and multiple tuned circuits.

For more information write to NDI, Inc., 22125 1/2 South Vermont, Torrance, California 90502.

350-watt solid-state amplifier

R.F. Power Labs, Inc., of Kirkland, Washington, is proud to announce their newest amplifier, Model V350. This solid-state vhf amplifier is designed for the Amateur Radio 2-meter band, but can be used (on special orders) over a 5-MHz bandwidth from 135 to 170 MHz. It is capable of producing more than 350 watts of rf output power into 50 ohms when driven with 10 to 15 watts. The amplifier weighs only 23.5 kg (52 pounds), including the built-in ac power supply.

The V350 is priced at \$895.00; delivery is one to three weeks. For con-



tinuous-duty operation the F135 (115 Vac) or F235 (230 Vac) fan kit should be used, priced at \$59.00 each.

For more information, contact R.F. Power Labs, Inc., 11013 - 118th Place N.E., Kirkland, Washington 98033.

Cushcraft vertical antennas


Many hams are convinced that to work a lot of DX they need a couple of thousand watts and a monster antenna array. While that undoubtedly helps, where is it written that the ham suffering from a money or space cramp can't compete for his day in the DXCC sun?

The three new Cushcraft verticals, the ATV-3, ATV-4, and ATV-5, provide a common-sense solution to a commonplace problem. Specifically designed for the DXer, these antennas provide the low angle of radiation necessary for long-haul DX communications, along with the performance and quality long associated with the Cushcraft name. The ATV-3, ATV-4, and ATV-5 operate over the 10, 15, and 20 meter Amateur bands. The ATV-4 has built-in 40-meter coverage, and the ATV-5 is all set for complete five-band operation.

All antennas feature a built-in PL-259 coax connector and stainless-steel hardware for all electrical connections; all are matched to 50 ohms and rated for a full 2000 watts PEP. Factory-marked tubing and plain English instructions make assembly a snap.

Built to withstand the severest weather, the ATVs feature specially designed, high-Q traps employing large diameter enameled copper wire and solid aluminum, air-dielectric capacitors. The trap forms are manufactured from fiberglass for minimum dielectric loss and high strength.

Available from dealers worldwide,

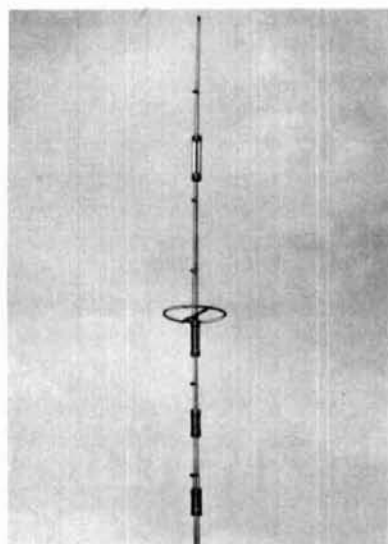

Q.S.L.

the ATV-3, ATV-4, and ATV-5 retail for \$49.95, \$89.95, and \$109.95 respectively. For more information and a full-color catalog highlighting the entire Cushcraft antenna line, write to Cushcraft, P.O. Box 4680, Manchester, New Hampshire 03108.

B&K model 820 digital capacitance meter




Dynascan Corporation has just announced the introduction of the B&K-Precision Model 820 portable digital capacitance meter. The 820 is a compact instrument capable of measurement over the wide capacitance range of 0.1 pF to 1 farad. Accuracy will greatly exceed the tolerance of most capacitors. The unit features a bright, four-digit LED display for easy reading in laboratories, product lines, or field applications.

The capacitance of virtually any capacitor can be measured quickly and accurately with the 820. Because the accuracy of this unit greatly exceeds the tolerance requirements of most users, required values can be "hand selected." Matched capacitors can also be singled out for use in bridge circuits and other critical applications. Ten ranges cover from 0.1 pF to 1 farad with resolution up to 0.1 pF.

The 820 allows quick measurement of unmarked capacitors or verification that a capacitor is within tolerance. Virtually any type of capacitor can be measured, from miniature

Something New from . . .

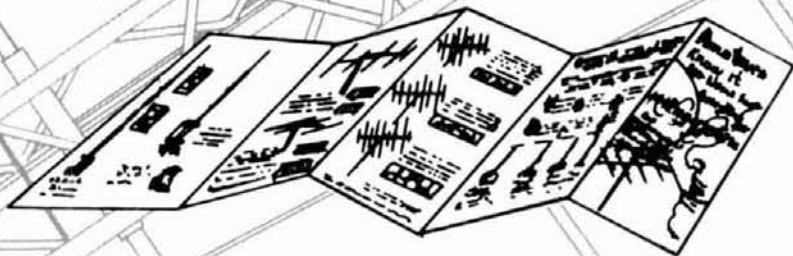

Call or write for a FREE product brochure.

Over 150 amateur antennas, accessories and Telex headsets and microphones. Complete with illustrations, descriptions and prices.



Please send me your Amateur Product Brochure

Name

Address

City State Zip

• • • **hy-gain** electronics
DIVISION OF TELEX COMMUNICATIONS, INC.

8801 Northeast Highway 6 • Lincoln, Nebraska 68505 U.S.A.
Telephone: (402) 467-5321 telex: Hygain Leo a 48-4324

**ERC PROMISES UP TO THE MINUTE STATE-OF-THE-ART DESIGN AND PERFORMANCE
WE'VE DONE IT FOR 1979**

**FOUR SIMULTANEOUS FILTERS IN ONE FOR UNPARALLELED QRM FREE RECEPTION (SSB & CW)
*PLUS A SPECIAL PATENTED CW PROCESSOR***



**SL-56
AUDIO ACTIVE FILTER
(3.5 x 5.5 x 7.5 INCHES)**

200-1600 Hz RANGE. THIS 3 FILTER COMBINATION IS UNBEATABLE FOR THE ULTIMATE IN QRM FREE SSB RECEPTION. ADJACENT CHANNEL QRM IS ELIMINATED ON THE HIGH AND LOW SIDES AT THE SAME TIME AND DOES NOT INTRODUCE ANY HOLLOWNESS TO THE DESIRED SIGNAL. ON CW THE SL-56 IS A DREAM. THE LOWPASS, HIGHPASS AND NOTCH FILTERS ARE ENGAGED ALONG WITH THE TUNABLE BANDPASS FILTER (400-1600 Hz) PROVIDING THE NEEDED ACTION OF 4 SIMULTANEOUS FILTER TYPES. THE BANDPASS MAY BE MADE AS NARROW AS 14 Hz (3dB). ADDITIONALLY, A SPECIAL PATENTED CIRCUIT FOLLOWS THE FILTER SECTIONS WHICH ALLOWS ONLY THE PEAKED SIGNAL TO "GATE ITSELF" THROUGH TO THE SPEAKER OR HEADPHONES (4-2000 OHMS). RECEIVER NOISE, RING AND OTHER SIGNALS ARE REJECTED. THIS IS NOT A REGENERATOR, BUT A MODERN NEW CONCEPT IN CW RECEPTION. THE SL-56 CONNECTS IN SERIES WITH THE RECEIVER SPEAKER OUTPUT AND DRIVES ANY SPEAKER OR HEADPHONES WITH ONE WATT OF AUDIO POWER. REQUIRES 115 VAC. EASILY CONVERTED TO 12 VDC OPERATION. COLLINS GRAY CABINET AND WRINKLE GRAY PANEL.

THE BRAND NEW SL-56 AUDIO ACTIVE FILTER SUPERCEDES OUR SL-55 IN BOTH CONCEPT AND PERFORMANCE. CONSOLIDATION OF MANY COMPONENTS HAS ALLOWED US TO MAKE 16 OPERATIONAL AMPLIFIERS (COMPARED TO 6 IN THE SL-55) INTO A FILTER GUARANTEED TO OUT PERFORM ANY OTHER AT A COST ONLY SLIGHTLY HIGHER THAN THE SL-55. THE FEATURES OF THE SL-56 ARE SO ADVANCED FROM ITS PREDECESSOR THAT CALLING IT THE SL-55A IS NOT JUSTIFIED. UNLIKE OTHER FILTERS THAT SIMPLY OFFER A CHOICE OF ONE OR TWO FILTER TYPES AT A TIME (NOTCH, BANDPASS, ETC.) SL-56 PROVIDES WHAT IS REALLY NEEDED --- THE SIMULTANEOUS ACTION OF A 6 POLE 200 Hz FIXED HIGH-PASS FILTER AND A 6 POLE 1600 Hz FIXED LOWPASS FILTER WITH A 60 dB NOTCH WHICH IS TUNABLE OVER THE

**WARRANTED ONE YEAR FULLY RFI PROOF FULLY WIRED AND TESTED AVAILABLE NOW
\$75.00 POSTPAID IN THE USA AND CANADA. VIRGINIA RESIDENTS ADD 4% SALES TAX.**

**ATTN SL-55 OWNERS: THE CIRCUIT BOARD OF THE SL-56 IS COMPLETELY COMPATIBLE
WITH THE SL-55 CHASSIS. OUR RETROFIT KIT IS AVAILABLE AT \$35.00 POSTPAID.**



**ERC INTRODUCES A BRAND NEW CONCEPT IN THE MEASUREMENT
OF VSWR AND POWER ACCEPTED BY THE LOAD**

REQUIRES 115 VAC AT LESS THAN 1/16 AMP.

COLLINS GRAY CABINET.
WRINKLE PANEL - BRIGHT
RED LED DIGITS (.33").
DECIMAL POINT IS THE
PILOT LIGHT.



1.8-30 MHz

TWO SO-239 COAX CONNECTORS ARE AT THE REAR PANEL.

DIMENSIONS 3.5 x 5.5 x 7.5 INCHES.

WEIGHT IS 2 POUNDS.

THE MODEL SL-65* (20-2000 WATTS) AND THE QRP MODEL SL-65A* (0.2-20 WATTS) DIGITALLY INDICATE ANTENNA VSWR UNDER ANY TRANSMISSION MODE -- SSB, CW, RTTY, AM ETC. THERE IS NO CALIBRATION REQUIRED AND NO CROSSING METER NEEDLES TO INTERPRET. SIMPLY LOOK AT THE READOUT AND THAT IS THE VSWR. SPEAKING NORMALLY INTO A SSB TRANSMITTER MIC. INSTANTLY CAUSES THE VSWR TO BE DISPLAYED THROUGHOUT YOUR ENTIRE TRANSMISSION. REVERSING THE POSITION OF A FRONT PANEL TOGGLE SWITCH AND THE DISPLAY INDICATES THE NET POWER (FORWARD LESS REFLECTED) THAT IS ACCEPTED BY THE ANTENNA. THE PEAK OF THE NET PEP IS DETECTED AND DISPLAYED WITHOUT FLICKER FOR ANY MODULATION TYPE. DISPLAY UPDATE IS CONSTANT YET FLICKER FREE AS YOU MAY CHANGE THE POWER ACCORDING TO YOUR VOICE. THERE IS NOTHING LIKE THIS QUALITY INSTRUMENT AVAILABLE ANYWHERE ELSE. IT IS THE ONLY VSWR-NET POWER INDICATOR THAT LETS YOU KNOW THE STATE OF YOUR ANTENNAS AND TRANSMITTED POWER AT ALL TIMES WHILE TRANSMITTING. EITHER MODEL IS A SOPHISTICATED DEVICE CONTAINING FOUR CIRCUIT BOARDS AND THIRTEEN INTEGRATED CIRCUITS.

**SL-65
VSWR INDICATOR**

- TWO DIGIT DISPLAY SHOWS VSWR TO AN ACCURACY OF .1 FOR VALUES FROM 1.0 AND 2.2. ACCURACY IS TO .2 FOR VALUES FROM 2.3 TO 3.4 AND TO .3 FROM 3.4 TO 4.0. FROM 4.1 TO 6.2 THE INDICATION MEANS THAT VSWR IS VERY HIGH.

- FOR VSWR VALUES NEAR 1.0, THE POWER RANGE FOR A VALID READING IS 20 - 2000 WATTS OUTPUT. FOR HIGHER VALUES THE UPPER POWER LIMIT FOR A FLICKER FREE VALID READING IS SOMEWHAT LESS (35 - 1000 WATTS FOR VSWR AT 2.0).

- DIVIDE THE ABOVE POWER LEVELS BY 100 TO OBTAIN THE PERFORMANCE OF THE SL-65A QRP MODEL.

WARRANTY ONE YEAR

**SL-65
NET POWER INDICATOR**

- THE POWER DISPLAYED IS THE DETECTED PEAK OF THE PEP FOR ANY MODULATION. THIS IS THE POWER THAT THE TRANSMITTER IS "TALKED" UP TO. DISPLAY DECAY TIME IS ABOUT ONE SECOND.

- THE POWER DISPLAYED IS THAT WHICH IS ACCEPTED BY THE ANTENNA (FORWARD LESS REFLECTED).

- POWER IS DISPLAYED ON THE SAME TWO DIGITS AS VSWR IN TWO AUTORANGED SCALES. 20 TO 500 WATTS AND 500 TO 2000 WATTS. TRIPOVER AT THE 500 WATT LEVEL IS AUTOMATIC EX: A READING OF 1.2 COULD MEAN 120 OR 1200 WATTS. YOU MUST KNOW WHICH RANGE YOU ARE IN.

- ACCURACY IS TO 10 WATTS IN THE LOWER RANGE AND 100 WATTS IN THE UPPER RANGE. DIVIDE POWER SPECS BY 100 FOR SL-65A.

SPECIAL AUDIO VERSION AVAILABLE FOR THE SIGHTLESS
• WRITE FOR DETAILS •

PRICE: \$189.50 POSTPAID IN USA & CANADA. VA. RESIDENTS ADD 4% SALES TAX.

BOOKLET AVAILABLE AT \$2.00 REDEEMABLE TO-
WARD PURCHASE.
* PATENT PENDING.

**ELECTRONIC RESEARCH CORP. OF VIRGINIA
P. O. BOX 2394
VIRGINIA BEACH, VIRGINIA 23452
TELEPHONE (804) 463-2669**

discs to pole-mounted power types. Even the small amounts of capacitance encountered in cable or switches can be measured.

For production-line applications, the 820 is an excellent means of pre-testing critical capacitors or accurately adjusting trimmer capacitors. The simplicity of operation allows even untrained workers to be quickly instructed in proper operation. To facilitate fast incoming component sorting and selection, slot-type front panel lead-insertion jacks are used. The slot jacks eliminate the time-wasting step of guiding a capacitor lead into the type of small lead insertion holes commonly found on other instruments.

In classroom applications, the 820 can be used to verify capacitor network calculations by measuring the actual value of a network. The operation of a variable capacitor can also be demonstrated, as can the temperature effects on a capacitor.

The B&K-Precision Model 820 comes with a 26-page detailed manual. Optional accessories include the BP-28 rechargeable battery pack, BC-28 charger, and LC-28 carrying case. The 820 is now available for immediate delivery at local B&K-Precision distributors at a price of \$130.00. For additional information, contact B&K-Precision, Sales Department, 6460 West Cortland Street, Chicago, Illinois 60635.

Yaesu two-meter transceiver

A new state-of-the-art, two-meter, all-mode transceiver, the FT-225RD, has been added to Yaesu's quality line of Amateur Radio equipment.

The new transceiver covers the entire 4 MHz and provides for USB, LSB, CW, fm and a-m. Power output is variable, 1-25 watts. Squelch, VOX, PTT, semi break-in CW with side tone, and tone burst are standard features of the FT-225RD. A superb noise blanker permits mobile ssb operation, and a discriminator zero-center meter allows precise tuning of

fm signals. Repeater splits are the standard 600 kHz; however, any split up to 1 MHz is possible with optional crystal. Provision has been made for up to eleven fixed channels using optional crystals.

The transceiver uses high-quality, plug-in circuit boards throughout, and an optional memory unit enables the storage and recall of any frequency within the range of the unit. This allows instant programmable QSY to a favorite repeater or calling frequency with just a flick of the switch. The digital frequency is accurate to 0.1 kHz or to 1 kHz with the FT-225R, which offers the analog dial readout only and at slightly less cost.

A built-in power supply provides taps for operation on 100/110/117/200/220 and 234 volts 50/60 Hz; dc operation covers 11.5 to 16 volts, negative ground at 6.5 amps on transmit, 1.2 amps on receive.

An attractive, four-color brochure is available at your nearby authorized Yaesu dealer or from Yaesu Electronics Corporation, 15954 Downey Avenue, P.O. Box 498, Paramount, California 90723.

second generation VMOS



Siliconix has introduced the first of a new family of high-current and high-voltage VMOS power fets, serving both analog and digital applications. The VN84GA has a rated output of 12.5 amperes, 80 volts, and 0.4 ohms — about sixfold current increase over previously available units.

The VN84GA, with input power in the microwatt range, produces up to 80 watts output at lower frequencies, or as much as 50 watts at 30 MHz.

R-X Noise Bridge

All Palomar Engineers products are made in U.S.A. Since 1965, manufacturers of Amateur Radio equipment only.



- Learn the truth about your antenna.
- Find its resonant frequency.
- Adjust it to your operating frequency quickly and easily.

If there is one place in your station where you cannot risk uncertain results it is in your antenna.

The Palomar Engineers R-X Noise Bridge tells you if your antenna is resonant or not and, if it is not, whether it is too long or too short. All this in one measurement reading. And it works just as well with ham-band-only receivers as with general coverage equipment because it gives perfect null readings even when the antenna is not resonant. It gives resistance and reactance readings on dipoles, inverted Vees, quads, beams multiband trap dipoles and verticals. No station is complete without this up-to-date instrument.

Why work in the dark? Your SWR meter or your resistance noise bridge tells you only half the story. Get the instrument that really works, the Palomar Engineers R-X Noise Bridge. Use it to check your antennas from 1 to 100 MHz. And use it in your shack to adjust resonant frequencies of both series and parallel tuned circuits. Works better than a dip meter and costs a lot less. Send for our free brochure.

The price is \$49.95 in the U.S. and Canada. Add \$2.00 shipping/handling. California residents add sales tax.

Fully guaranteed by the originator of the R-X Noise Bridge. ORDER YOURS NOW!

Palomar Engineers

Box 455, Escondido, CA. 92025 • Phone: [714] 747-3343

Heavy Duty Power Supplies

from **ASTRON**
High Quality • Rugged • Reliable

SPECIAL FEATURES

- SOLID STATE ELECTRONICALLY REGULATED
- FOLD-BACK CURRENT LIMITING Protects Power Supply from excessive current & continuous shorted output.
- CROWBAR OVER VOLTAGE PROTECTION on Models RS-7A, RS-12A, RS-20A, & RS-35A.
- MAINTAIN REGULATION & LOW RIPPLE at low line input Voltage.
- HEAVY DUTY HEAT SINK • CHASSIS MOUNT FUSE
- THREE CONDUCTOR POWER CORD
- ONE YEAR WARRANTY • MADE IN U. S. A.

PERFORMANCE SPECIFICATIONS

- INPUT VOLTAGE: 105 - 125 VAC
- OUTPUT VOLTAGE: 13.8 VDC ± 0.05 volts (Internally Adjustable: 11-15 VDC)
- RIPPLE: Less than 5mv peak to peak (full load & low line)
- REGULATION: $\pm .05$ volts no load to full load & low line to high line



ASTRON 12 AMP REGULATED POWER SUPPLY Model RS-12A


9 Amps continuous
12 Amps ICS*
4" (H) x 8" (W) x 9" (D)
Shipping Weight 13 lbs.

Price..... \$72.95

Other popular POWER SUPPLIES also available: (Same features and specifications as above)

Model	Continuous Duty (amps)	ICS* (amps)	Size (in.) H x W x D	Shipping Wt. (lbs.)	Price
RS-35A	25	35	5 x 11 x 11	29	\$136.95
RS-20A	16	20	5 x 9 x 10½	20	\$94.95
RS-7A	5	7	3¼ x 6 x 7½	7½	\$49.95
RS-4A	3	4	3¼ x 6 x 7½	5	\$39.95

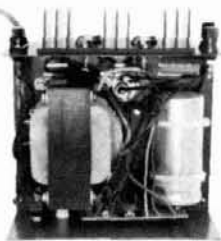*ICS — Intermittent Communication Service (50% Duty Cycle)
If not available at your local dealer, please contact us directly.



Inside View — RS-12A

ASTRON CORPORATION

1971 SOUTH RITCHEY ST., SANTA ANA, CA 92705 (714) 835-0682

If you expect to invest in a new ham antenna in the next 90 days, invest 15¢ postage to get Antenna Specialists' brand new, complete ham catalog today.



Bind'em and find'em!

HAM RADIO BINDERS

Don't let your valuable issues of HAM RADIO get dog-eared or scattered who knows where! Get a handsome, durable buckram binder from HRB complete with date labels.

HR-BDL Each \$6.95
3 for \$17.95

To order, just send check, money order or credit card information to:
(include \$1.00 shipping)

Ham Radio's Bookstore
Greenville, NH 03048

Newnes Radio and Electronics Engineer's Pocket Book

In this, the latest edition of this handy pocket book first published in 1940, author H. W. Moorshead has succeeded in keeping this standard reference book up to date. Obsolete material has been eliminated to make room for the most current information. The section on ICs, in particular, has been expanded to cover the many recent advances in the field. Among the other topics contained in the book are transistor and diode data and basing diagrams, transistor circuits, transformer data, and many tables of information useful to the working technician and engineer. Pocket-notebook size (5 inches long and 3 inches wide), hard cover, 191 pages. \$5.95, plus \$1.00 per order for shipping, from Ham Radio's Communications Bookstore, Greenville, New Hampshire 03048; order NR-PB.

Antenna Radio Spoken Here!

FREE decal just for fun!

Name _____
Address _____
City _____ State _____ Zip _____



the antenna specialists co.

a member of The Allen Group Inc.
12435 Euclid Ave. Cleveland, Ohio 44106
Export, 2200 Sharners Drive, Westbury, L.I., New York, 11590
Canada: A. C. Simmonds & Sons, Ltd.

soldering-tool holder and mini-soldering station



EDSYN, Incorporated, of Van Nuys, California, announces a low-cost soldering tool holder which also serves as a compact soldering station. Designated the Idle-Rest TL194 General Purpose Holder, the unit holds most available soldering tools due to its specially designed tool cradle. The exterior of the holder remains within safe skin-touch temperature limits because of the low heat transfer characteristics of the molded Bakelite housing. Also, an efficient heat shield and ventilating-grill system helps keep heat concentrated to the soldering tip area.

The holder sits securely on the bench top without tipping. If desired, the integral fastener nut may be used for permanent installation to the bench top.

In addition, the holder contains a supply of desoldering wick and solder (included with purchase), parts or tip-storage tray, and a large tip-cleaning sponge which self-wets at the touch of a finger. The sponge may be removed if desired to obtain an additional storage tray for components or soldering supplies.

For more information, contact an authorized Edsyn distributor; for the name of the one nearest you, write Edsyn, Incorporated, 15958 Arminta St., Van Nuys, California 91406.

Mirage MP1, peak- reading wattmeter

Mirage Communications is now offering the MP1 high-frequency (1.8-30 MHz) peak-reading wattmeter. It is designed to provide the

SC — SCR 1000 — **SC**

Repeater of Your Dreams!

**2M &
220 MHz
450 MHz
Soon!**



**Available
With Features
You've Only
Dreamed About!**

*Now FCC Type Accepted
for Commercial Services!
Parts 21, 89, 91 & 93.*

Like —

- Full Autopatch, with or without Reverse patch and "Landline" or Radio Remote Control of the Repeater.
- Radio and/or Landline Touch-Tone* Remote Control of such repeater functions as HI/LO Power; Patch Inhibit/Reset; Switch ID Tracks; Repeater ON/OFF; PL ON/OFF, etc.
- 65Wt. Transmitter!
- "PL"-CTCSS; HI/LO Pwr.; Multi-Freq.; Up to 4 different IDs; Automatic switching to "Emergency Power ID" when on battery pwr.
- Ultra-sharp 10 Pole Xtal Filter; Xmt. Xtal oven — for the "ultimate" in stability.
- Timeout-Timer Reset Tone Annunciator.
- And many other "custom-designed" options per your request — such as auxiliary receivers, radio links, etc. Please Inquire.
- Along with a complete line of Repeater System Accessories . . . such as — The Finest Duplexers, Cavities, Cabinets from 7" to 7', Antennas, "Hardline", Cables, etc.

The SCR1000 — simply the finest repeater available on the market — absolutely Top Quality throughout . . . and often compared to (lesser featured) units selling for 2-3 times the price! This is a 30Wt. unit, with a very sensitive & selective receiver. Included is a built-in AC Supply, NEW Expanded Memory CW IDer, full metering and lighted status indicators/control push-buttons, crystals, local mic, etc. . . .

- Join the thousands of very pleased Spec Comm customers world-wide — knowledgeable Amateur Radio groups, Commercial 2X Radio users, Military & Government Agencies, Red Cross, Universities, etc.
- So, make your dream a reality . . . Call or write Spec Comm today! Give us all of your repeater system requirements — whether modest . . . or "Super Deluxe", and let us send you a quote.

*Registered Trade Mark of A.T.&T.

A Full Line of SCR1000 Repeater Boards & Complete Sub-Assemblies Are Also Available: Inquire.

Export Orders — Contact our International Department

SPECTRUM COMMUNICATIONS

Dept. HM — 1055 W. Germantown Pk.
Norristown, PA 19401 (215) 631-1710

NOT TOOTING OUR OWN HORN BUT- WE TRY HARD TO PLEASE YOU, THE CUSTOMER!!

FOR FAST RELIABLE DELIVERY AND SERVICE
LET US SHOW YOU OUR STUFF!!

"creative electronics"

P.O. BOX 7054
MARIETTA, GEORGIA 30065
PHONE (404) 971-2122 OR OUTSIDE GA. (800) 241-4547


ASK FOR NEIL OR JUDI
DEALERS & DISTRIBUTORS FOR:

- VHF ENGINEERING
- HAMTRONICS
- PHELPS DODGE
- WACOM

we accept



*"or
inflated
U.S.
dollars!"*

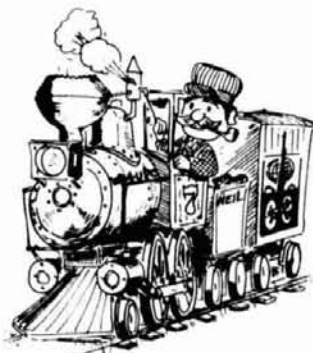

Electronic Research, Development & Consulting



Amateur Radio operator with a versatile fixed or portable wattmeter, without having to use cumbersome plug-in or add-on accessories.

Three power ranges are available (25, 200, and 2000 watts), providing reading convenience whether you use it for low-power operation or with the biggest DX setup. The wattmeter will read both forward and reverse power at the flip of a switch. The *MP1*, like its vhf predecessor, the *MP2*, has the ability to display either average or peak power reading. The peak-reading feature is a must for ssb transmitters. The *MP1* also will display swr, which is measured directly, without having to use extra charts or graphs. For ease of installation, the *MP1* has a removable r-f coupling unit that may be placed up to 1.2 meters (4 feet) from the indicator.

The *MP1* is portable, containing the latest in low-power ICs and powered by a 9-volt battery. For long-term, fixed-station operation, an optional ac adaptor is available. A low-battery-voltage indicator has been built into the wattmeter to indicate when the battery needs changing.

For more information please contact your local dealer or Mirage Communications, P.O. Box 1393, Gilroy, California 95020.

J. W. Miller catalog

A new 100-page catalog with specifications for more than 5,000 coils, filters, and communications

RECITAL

THEATRE

CONSOLETTA II

SPINET



You can assemble any of these Schober Organs

—and save 50% off store prices.

This coupon will bring you the fascinating Schober color catalog which describes the organs and shows you how easy it is to assemble them from Schober's complete kits. Include \$1 if you want a 12-inch demo record.

The *Schober* Organ Corp., Dept. HA-1
43 West 61st Street, New York, N.Y. 10023

- Please send me the Schober Organ Kit Catalog.
 Enclosed is my \$1 for the 12-inch demo record.

Name _____

Address _____

City _____ State _____ Zip _____

essentials is now available from the J. W. Miller Division of Bell Industries, Compton, California.

Newest additions to their catalog include direct reading SWR/power meters, an rf speech-processor, and coaxial switches. Included also is the broad line of high pass, lowpass, audio, and ac power-line filters.

Catalog 79 gives detailed specifications for rf coils, chokes, filters, and related communication components. To assist in selection, coils are categorized by frequency from 0 through 500 MHz in the table of contents. Schematic diagrams for all shielded and unshielded coils, showing adjustment accessibility, are given.

For additional information, contact Jerry Hall, Operations Manager, Bell Industries, J. W. Miller Division, 19070 Reyes Avenue, P.O. Box 5825, Compton, California 90224.

Astatic amplifying microphone




A microphone designed for repeater-control and phone-patch operations has been introduced by the Astatic Corporation, Conneaut, Ohio. It's the new *Astatic T²M* amplified microphone with touch-pad encoder.

For fingertip convenience, the touch pad encoder is an integral part of the microphone itself. It has a tactile twelve-key keyboard and provides visual feedback through a front-mounted LED.

Priced comparably to a conventional microphone, the T²M is of an

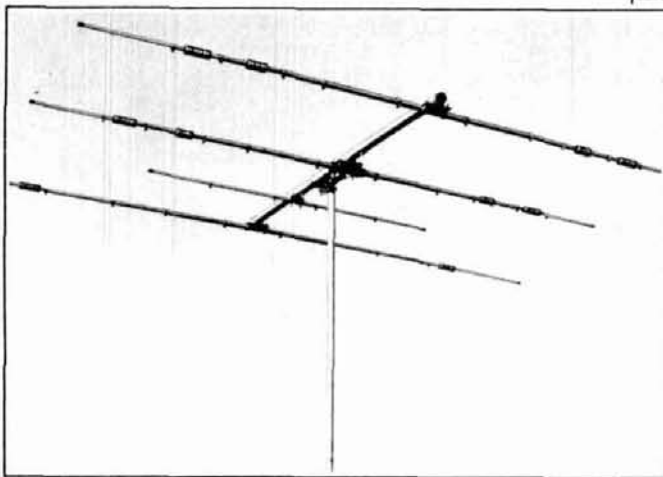CUSHCRAFT IS THE HF MULTIBAND ANTENNA COMPANY.




ATB-34, Three Band

Cushcraft manufactures a full range of high-frequency antennas which are performance engineered for the most discriminating amateur. For the amateur who demands top performance in a multiband Yagi beam there's the incomparable ATB-34 three-band beam for broadband, high-gain coverage on 10, 15 and 20 meters.

And for the Amateur with limited antenna space and budget who wants reliable, multiband radio communications there are three Cushcraft multiband verticals to choose from: the three-band ATV-3 for 10, 15 and 20; the four-band ATV-4 for 10, 15, 20 and 40 meters; and the ATV-5 for low VSWR five-band performance from 80 through 10 meters.

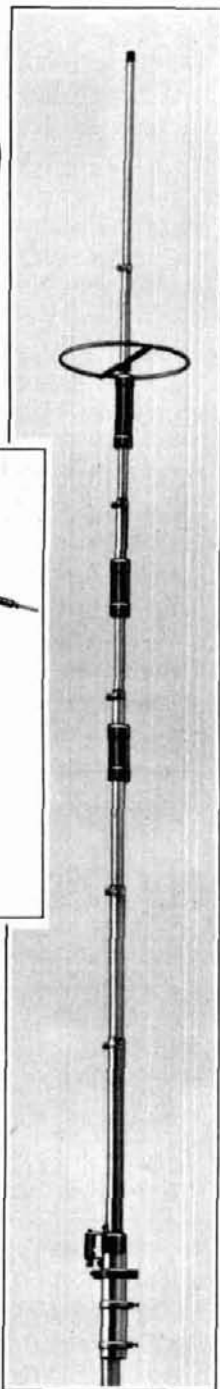Cushcraft high-frequency antennas are quality engineered for top performance; they are often imitated, but never duplicated.



ATV-4, Four Band



cushcraft
CORPORATION


UPS SHIPPABLE

In Stock With Dealers World Wide P.O. Box 4680, Manchester, N. H. 03108

NEW CoaxProbe* NEW

Coaxial RF Probe for Frequency Counters and Oscilloscopes That Lets You Monitor Your Transmitted Signal Directly From the Coax Line.

Only **\$12.95**
plus .50 postage

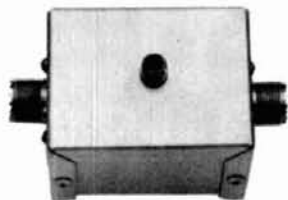

FINALLY! A RF PROBE that lets you connect into your coax cable for frequency measurements and modulation waveform checks directly from the transmitter.

JUST CONNECT THE CoaxProbe* into your transmission line and plug the output into the frequency counter or oscilloscope. Insertion loss is less than .2db so you can leave it in while you operate.

A NECESSITY IN ANY WELL-ORGANIZED HAM SHACK, the CoaxProbe* eliminates "jerry-rigging" and hassles when tapping into the coax line is desired.

A SPECIAL METHOD OF SAMPLING keeps output relatively constant with a wide variation of power. Power output of 8 watts gives .31v out, while 800 watts will give 1.8v out. (rms 3-30 mhz.) 2000 watts PEP rating too!

*Trademark of CoaxProbe Co. for rf sampling device.
© 1978 by CoaxProbe Co.

USE IT ON 2 METER RIGS TO ADJUST FREQUENCY. The CoaxProbe* has a range of 1.8 to 150 mhz.

MONITOR YOUR MODULATION WAVEFORM. With an oscilloscope of proper bandwidth, you can check your modulation for flat-topping, etc. Ideal for adjusting the speech processor.

NOW YOU CAN MONITOR SIGNALS when connected to the dummy load, eliminating unnecessary on-the-air radiation.

AVAILABLE FOR THE FIRST TIME TO AMATEURS. Try it for 10 days. If not satisfied, send it back for refund (minus shipping charges).

Order today from:

CoaxProbe Co.
P.O. Box 426, Portage, MI 49081
Michigan Res. Add 4% Sales Tax

advanced design that has such high-quality features as a preamplified electret element with tailored response and integral modulation control; a digital, integrated tone-generator circuit with 3.5795 MHz crystal for stable frequency control; and a mixer amplifier with up to 15 dB gain for impedance matching and audio and tone mixing.

The attractive Cyclac housing resists abusive treatment. It also features shielding to reduce external interference and rf feedback. The T2M operates from filtered 6 to 16 volt dc sources. Included is an eight-foot, three-conductor (one shield) cable and coiled cord.

For additional information on the new Astatic T2M amplified microphone with touch pad encoder, write The Astatic Corporation, Conneaut, Ohio 44030.

communications equipment catalog

Harrison Radio is pleased to announce the availability of the all-new 1979 Harrison Radio Communications catalog. The catalog has 120 pages of illustrations, descriptions, specifications, and prices covering several hundred transceivers, antennas, and accessories for Amateur Radio, marine radio, business-band radio, public-service-frequency equipment, and CB.

The catalog is free and available by writing to Harrison Catalog, 22 Smith Street, Farmingdale, New York 11735.

receiver preamplifier

Telco Products Corporation announces two new mobile in-line receiver preamplifiers. Known as Models VHF 144 and UHF 450, they are specifically designed for amateur, police, emergency, business-band, and Class A CB transceivers.

These new computer-designed preamplifiers boost receiver sensitivity. A unique rf-sniffer circuit allows the preamplifier to sense when the transceiver is keyed, and switches the preamplifier off during the trans-

NEW FROM GLB

A complete line of **QUALITY 50** thru 450 MHz **TRANSMITTER AND RECEIVER KITS**. Only two boards for a complete receiver. 4 pole crystal filter is standard. Use with our **CHANNELIZER** or your crystals. Priced from \$69.95. Matching transmitter strips. Easy construction, clean spectrum, **TWO WATTS** output, unsurpassed audio quality and built in **TONE PAD INTERFACE**. Priced from \$29.95.

SYNTHESIZER KITS from 50 to 450 MHz. Prices start at \$119.95.

Now available in **KIT FORM** — GLB Model 200 **MINI-SIZER**.

Fits any HT. Only 3.5 mA current drain. Kit price \$159.95 Wired and tested. \$239.95

Send for **FREE 16 page catalog**.

We welcome Mastercharge or VISA

GLB ELECTRONICS
1952 Clinton St., Buffalo, N. Y. 14206

MILITARY SURPLUS WANTED

Space buys more and pays more. Highest prices ever on U.S. Military surplus, especially on Collins equipment or parts. We pay freight. Call collect now for our high offer. 201 440-8787.

SPACE ELECTRONICS CO.
div. of Military Electronics Corp.
35 Ruta Court, S. Hackensack, N. J. 07606

DIPLOLE ANTENNA CONNECTOR



HYE-QUE (HQ-1) dipole connector has coax SO-239 socket molded into glass filled plastic body to accept coax PL-259 plug on feedline. Drip cap keeps coax fittings dry. Instructions included. Guaranteed. At your dealer, or \$4.95 postpaid. Companion insulators 2/\$9.99.

BUDWIG MFG. Co. PO Box 97H, Ramona, CA 92065

TRS 80-II

Antenna Polar Plot Modeling Program **PPM**. Experiment with multiple driven element antenna design on your computer.

See Field Effects due to changing:

- Polarization
- Number of elements
- Elements spacing
- Elements position
- Transmission lines delay
- Drive phasing

#PPM — Program Tape & Instructions ... \$35.00
714-461-3927

L. D. MAY & CO.

4607 30th STREET
SAN DIEGO, CA 92116



mit cycle. This feature allows the pre-amplifier to be connected directly into the coax line with no modification to the existing mobile system.

The VHF 144 has 20 dB gain over a 5-MHz band in the frequency range of 140-180 MHz. Model UHF 450 features 10-12 dB gain over any 1-MHz band in the frequency range of 400-512 MHz. The VHF 144 will safely handle transmitter output of 40 watts, and UHF 450 will work with 100-watt transmitters.

Suggested retail price for the VHF 144 is \$49.95; and for the UHF 450 is \$59.95. For additional information, contact Telco Products Corporation, 44 Sea Cliff Avenue, Glen Cove, New York 11542.

solderless breadboards


Continental Specialties Corporation is probably best known for their popular line of versatile and easy-to-use solderless breadboards. One of the best is their Proto-Board model 203A, which is actually more than a solderless breadboard. In addition to offering a very large socket-type solderless breadboard array to work on, Proto-Board 203A has three separate, regulated, power supplies built into the box. They offer 5 Vdc at 1 per cent regulation and up to 1 amp of output current, and ± 15 Vdc (nominal) supplies, each good for 0.5 amp and each independently internally adjustable over a 9-18 Vdc range.

The statistics on the Proto-Board 203A are impressive. The whole package measures only 25 x 17 x 8 cm (9.8 x 6.6 x 3.3 inches). It features 2250 tie points for a 24-DIP (14-pin package) capacity. The +5, ± 15 Vdc and ground connections are available at four five-way binding posts. The power switch and a power pilot are adjacent to the power supply terminals.


The PB-203A is designed for 117 Vac, 60-Hz operation and carries a suggested amateur net price of \$129.95. For further information, contact Continental Specialties Corporation, 70 Fulton Terrace, New Haven, Connecticut 06509; or phone (203) 624-3103.

CUSHCRAFT IS THE VHF-UHF ANTENNA COMPANY.

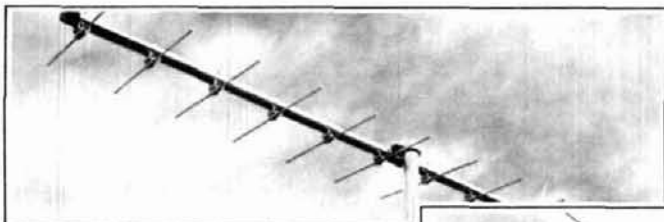Cushcraft precision engineered VHF/UHF Yagi beams have become the standard of comparison the world over for SSB and CW operation on 6 meters through 432 MHz. Built by skilled craftsmen from the best available materials, these beams represent that rare combination of high electrical performance, rugged construction, and durability.




1 1/2-2 Meter Yagi

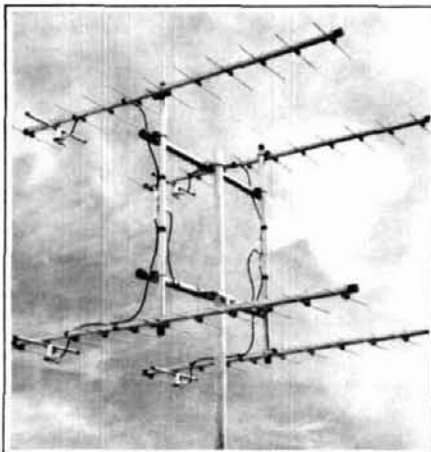

Quad Array

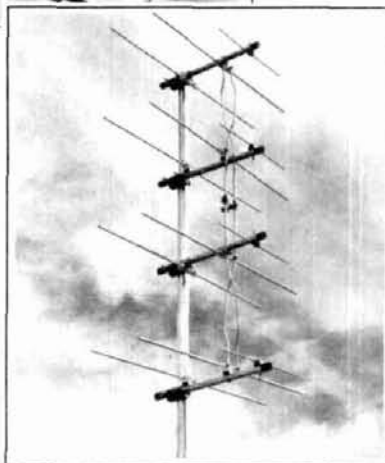Cushcraft's Quad Arrays for 144, 220, and 432 MHz use four matched 11-element Cushcraft Yagis and are the ultimate in a high-performance Yagi array. These arrays have been carefully engineered for maximum forward gain, high front-to-back ratio, and broad frequency response. All antennas provide a low VSWR match to 50-ohm coaxial feedline.



20 Element DX Array

Cushcraft's wide variety of VHF/UHF Beams includes an antenna for every amateur activity above 50 MHz, whether local ragchewing or long haul over-the-horizon DX. All models have been carefully optimized for maximum forward gain with high front-to-back ratio. The heavy wall bright hard drawn aluminum booms and elements are combined with heavy formed aluminum brackets and plated mounting hardware for long operating life and survival in severe weather.

 **cushcraft**
CORPORATION

UPS SHIPPABLE

In Stock With Dealers World Wide P.O. Box 4680, Manchester, N. H. 03108

Repeater Jammers Running You Ragged?

Here's a portable direction finder that REALLY works—on AM, FM, pulsed signals and random noise! Unique left-right DF allows you to take accurate (up to 2°) and fast bearings, even on short bursts. Its 3dB antenna gain and .06µV typical DF sensitivity allow this crystal-controlled unit to hear and positively track a weak signal at very long ranges—while the built-in RF gain control with 120 dB range permits positive DF to within a few feet of the transmitter. It has no 180° ambiguity and the antenna can be rotated for horizontal polarization.



The DF is battery-powered, can be used with accessory antennas, and is 12/24V for use in vehicles or aircraft. It is available in the 140-150 MHz VHF band and/or 220-230 MHz UHF band. This DF has been successful in locating malicious interference sources, as well as hidden transmitters in "T-hunts", ELTs, and noise sources in RFI situations.

Price for the single band unit is \$195, for the VHF/UHF dual band unit is \$235, plus crystals. Write or call for information and free brochure.

W6GUX

L-TRONICS
5546 Cathedral Oaks Road
(Attention Ham Dept.)
Santa Barbara, CA 93111

WD6ESW

QUARTZ CRYSTALS



"IN A HURRY"
SINCE 1970

CRYSTALS AVAILABLE FOR:

- CB - Synthesizers
- Amateur - HF, VHF, UHF
- Industrial
- Scanner
- Marine - LB & VHF
- Conversion Crystals
- Special Attention to R & D.
- Micro-processor Types.

DISCOUNTS AVAILABLE TO
DEALERS & MANUFACTURERS

CALL "BONNIE" FOR
PRICES & DELIVERY

VISA & MASTER CHARGE

credit cards accepted.



CAL CRYSTAL LAB, INC.

1142 N. Gilbert Street
Anaheim, CA 92801
(714) 991-1580

GILFER'S "BEST SELLER" SHORTWAVE BOOKS



Just Released 1979 Edition
CONFIDENTIAL FREQUENCY LIST
Identifies those thousands of HF stations (SSB, CW, FAX) between 4 and 26 MHz. \$6.95 ppd.

Just Released 33rd Edition
WORLD RADIO TV HANDBOOK
The "bible" of the shortwave listener — most comprehensive directory of stations plus last-minute info on skeds, new band allocations, best bands due to sunspots. \$14.95 ppd.


SPECIAL COMBO OFFER:
Both books only \$20 ppd.

**NEW FREE GILFER
SHORTWAVE CATALOG**

• Receivers • Antennas • Preselectors
• Tuners • Headphones • Clocks • Callibrators • AM, FM & TV Directories • Logs and QSL Albums • Report Forms

GILFER SHORTWAVE
Dept. HR3, Box 239, Park Ridge, NJ 07656

16-POLE R-4C SSB!

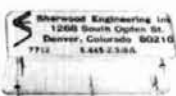

Improve the early-stage selectivity of your Drake R-4C while adding 8 additional poles (total 16) with an internally-mounted, switchable set of first-IF crystal filters. Reduce QRM, leakage, overload. Ideal for DX and contest work. Overall shape factor better than 1.4. Maximum skirt selectivity with maximum intelligibility. Total bandwidth with CF-2.1K/8: 2100 Hz at -6dB, 2900 Hz at 60 dB. Modest variable bandwidth. Other bandwidths available. Filter set can be mounted in receiver and relay switched with our kits which start at \$33.00. 3 and 4 filter switching options can include our CF-600/6 and/or existing 8-kHz first-IF filter, all internally mounted, controlled from rear or front panel. USB and LSB CF-2.1K/8 pair is \$120.00 per set. Money back if not satisfied. Add \$3 shipping per order; \$6 overseas air. Dealer inquiries welcome.

Sherwood Engineering Inc.

1268 South Ogden St.
Denver, Colo. 80210
(303) 722-2257



COMPUTERIZED GREAT CIRCLE BEARINGS

\$1⁰⁰ Postpaid Worldwide (\$2.00 for Air Mail) \$1⁰⁰
★ Centered on your QTH ★ Gives return bearings also
★ 660 Locations listed ★ Distances in miles & km

Bill Johnston, N5KR

1808 Pomona Dr., Las Cruces, New Mexico 88001

FACSIMILE

**COPY SATELLITE, PHOTOS,
WEATHER MAPS, PRESS!**

The Fax Are Clear — on our full size (18-1/2" wide) recorders. These commercial-military units now available at surplus prices. Learn how to copy with our FREE Fax Guide Tel: (212) 372-0349

ATLANTIC SURPLUS SALES

3730 NAUTILUS BROOKLYN, N.Y. 11224

ALL BAND TRAP ANTENNAS!



PRETUNED - COMPLETELY ASSEMBLED - ONLY ONE NEAT SMALL ANTENNA FOR UP TO 6 BANDS! EXCELLENT FOR CONGESTED HOUSING AREAS - APARTMENTS LIGHT - STRONG - ALMOST INVISIBLE!

FOR ALL MAKES & MODELS OF AMATEUR TRANSCEIVERS - TRANSMITTERS - GUARANTEED FOR 2000 WATTS SSB 1000 WATTS CW. FOR NOVICE AND ALL CLASS AMATEURS!

COMPLETE AS SHOWN with 90 ft. RG58U-52 ohm feedline, and PL259 connector, insulators, 30 ft. 300 lb. test dacron end supports, center connector with built in lightning arrester and static discharge - molded, sealed, weatherproof, resonant traps 1"X6"-you just switch to band desired for excellent worldwide operation - transmitting and receiving! **WT. LESS THAN 5 LBS.**

160-80-40-20-15-10 bands 2 trap--149 ft. with 90 ft. RG58U - connector - Model 777BU ... \$54.95
80-40-20-15-10 bands 2 trap --- 102 ft. with 90 ft. RG58U - connector - Model 998BU ... \$49.95
40-20-15 -10 bands 2 trap --- 54 ft. with 90 ft. RG58U coax - connector - Model 1001BU ... \$48.95
20-15-10 bands 2 trap --- 26 ft. with 90 ft. RG58U coax - connector - Model 1007BU ... \$47.95

SEND FULL PRICE FOR POST PAID INSURED DEL. IN USA. (Canada is \$5.00 extra for postage - clerical - customs - etc.) or order using VISA Bank Americard - MASTER CHARGE - AMER. EX-PRESS. Give number and ex. date. Ph 1-308-236-5333 9AM - 6PM week days. We ship in 2-3 days. **PRICES MAY INCREASE SO - ORDER NOW AND SAVE!** All antennas guaranteed for 1 year. Money back trial! Made in USA. **FREE INFO. AVAILABLE ONLY FROM.**

WESTERN ELECTRONICS

Dept. AR- 3

Kearney, Nebraska, 68847

CALL TOLL FREE



1-800-228-4097
Communications Center

443 N 48th Street
 Lincoln, Nebraska 68504
 In Nebraska Call (402)466-8402

1-800-634-6227
Communications Center
West

1072 N. Rancho Drive
 Las Vegas, Nevada 89106
 In Nevada Call (702)647-3114

Antenna Sale!

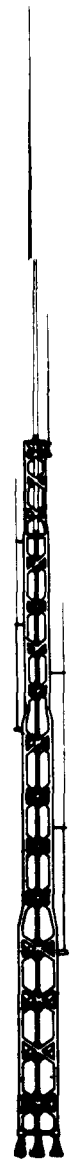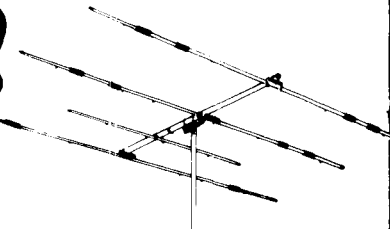

18HT

	HY-GAIN	Regular	Special
TH6-DXX	Super Thunderbird	\$296.95	\$ 209.95
TH3-MK3	3 ele. 10, 15, 20 Mtr. beam	219.95	179.95
Hy-Quad	2 ele. Quad 10, 15, 20 Mtr.	229.95	199.95
TH3-Jr.	3 ele. 10, 15, 20 Mtr. beam	144.50	129.95
18 HT	Hy-Tower 10-80 Mtr. Vertical	299.95	259.95
14AVQ/WB	10-40 Mtr. Trap Vertical	67.00	57.00
18AVT/WB	10-80 Mtr. Trap Vertical	97.00	84.95
205 BA	5 ele. "Long John" 20 mtr.beam	289.95	249.95
203	3 ele. 2 Mtr. beam	14.95	
205	5 ele. 2 Mtr. beam	16.95	
208	8 ele. 2 Mtr. beam	24.95	
214	14 ele. 2 Mtr. beam	31.95	

MOSLEY

Classic 33	3 ele. 10, 15, 20 Mtr. beam	304.75	219.95
Classic 36	6 ele. 10, 15, 20 Mtr. beam	392.75	289.95
TA-33	3 ele. 10, 15, 20 Mtr. beam	264.00	199.95
TA-36	6 ele. 10, 15, 20 Mtr. beam	392.75	289.95
TA-33 Jr.	3 ele. 10, 15, 20 Mtr. beam	197.00	149.95
TA-40KR	40 Mtr. add on	119.50	89.95

CUSHCRAFT

ATB-34	4 ele. 10, 15, 20 Mtr. beam	259.95	209.95
ARX-2	2 Mtr. Ringo Ranger	36.95	32.95
A147-20T	2 Mtr. Twist	59.95	52.95
A144-10T	10 ele. Twist 2 Mtr.	39.95	32.95
A144-20T	20 ele. Twist 2 Mtr.	59.95	52.95
A147-11	11ele. 146-148 MH2	34.95	30.95
A147-22	Power Pack 22 ele.146-148 MH2	99.95	88.95
A432-20T	430-436 MH2 20 ele. TWIST	54.95	49.95
ATV-4	10,15,20,40 MTR Vertical	89.95	79.95
ATV-5	10,15,20,40 MTR Vertical	109.95	94.95

HUSTLER

4BTV	10-40 Mtr. Trap Vertical	99.95	82.95
RM-75	75 Meter Resonator	16.95	14.50
RM-75s	75 Meter Super Resonator	31.95	27.50
G6-144-A	6 db. 2 Mtr. Base Colinear	79.95	64.95
G6-144B	7 db. 2 Mtr. Base Colinear	119.95	99.95


WILSON

System One	5 ele. 10, 15, 20 Mtr. beam	274.95	239.95
System Two	4 ele. 10, 15, 20 Mtr. beam	219.95	189.95
System Three	3 ele. 10,15,20 MTR beam	179.95	159.95
WV-1 Vertical	10-40 MTR Vertical	79.95	69.95

CDE ROTORS

Ham III \$125.00 T2X Tail Twister \$225.00

CUSHCRAFT
ATB-34

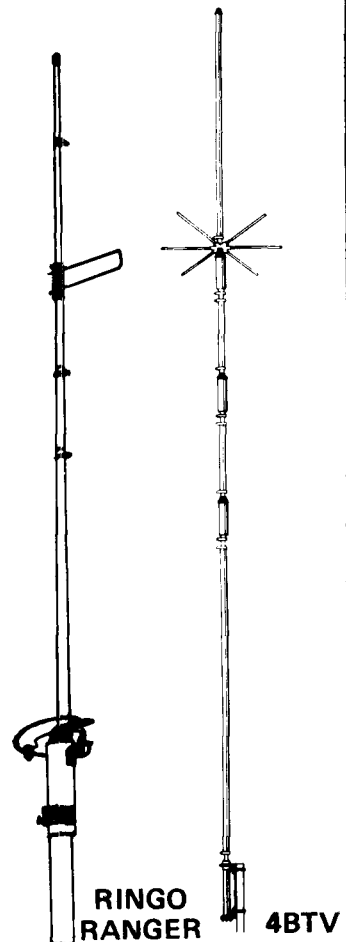

RINGO
RANGER

4BTV

We carry all major brands of ham radios
AT DISCOUNT PRICES

Yaesu — Kenwood — Drake — ICOM — Dentron —
 Ten-Tec — Swan — Tempo — Midland — E.T.O. — Wilson



State
of the art



by
K.V.G.

CRYSTAL FILTERS and DISCRIMINATORS

10.7 MHz FILTERS, 8 POLE			
XF107-A	14kHz	NBFM	\$51.55
XF107-B	16kHz	NBFM	\$51.55
XF107-C	32kHz	WBFM	\$51.55
XF107-D	38kHz	WBFM	\$51.55
XF107-E	42kHz	WBFM	\$51.55

10.7 MHz FILTERS, 4 POLE			
XM107-S04	14kHz	NBFM	\$23.05

OSCILLATOR CRYSTALS, 1 kHz to 200 MHz available. Write for Data Sheet and prices.

SOCKET (for XM107-S04) type DG1 \$1.50

10.7 MHz DISCRIMINATORS			
XD107-01	30kHz	NBFM	\$27.80
XD107-02	50kHz	WBFM	\$27.80

Export Inquiries Invited

Shipping \$1.50 per filter

432 MHz SSB TRANSVERTERS

Use your HF Transceiver on the 432 MHz band with the addition of the MMt432 linear Transverter. The MMt432 operates on all modes; SSB, CW, AM, FM. It contains BOTH the linear transmit up-converter and the receive down-converter. An internal PIN diode T/R connects to your Transceiver T/R line. The MMt432 is FT101 and similar HF rig compatible. Add the 70/MBM48 MULTIBEAM and operate direct into OSCARS 7 & 8. Write for application note.

Specifications:

Output Power 10 W PEP
Drive, 10 Meters 1/2 W max
Receiver N.F. 3.0 dB typ
Receiver gain 30 dB typ
Prime Power 12 V D.C.

Shipping: \$3.50



MMt432-28S	\$290.00	MMt144-28	\$230.00
MMt432-50	\$299.00	Also Available:	
MMt438-ATV	\$310.00	FMt440-146	\$175.00
MMt432-144	\$340.00	QMt432-144	\$175.00

OSCAR-J FILTERS

NEW!

Suppress 2m Tx Third Harmonics. Low 2m loss (0.5 dB typ.). High loss at 435 MHz (30/40dB).

MMf200-5	30 dB min. atten.	\$29.95
MMf200-7	40 dB min. atten.	\$39.95

RECEIVE CONVERTERS



MODELS FOR ALL BANDS 50 MHz THRU 1296 MHz. LOW NOISE OPTIONS AT 432 MHz.

STANDARD I.F. 10M. I.F. OPTIONS 6M & 2M AVAILABLE
POWER 12V D.C. Shipping \$2.50

MMc50	N. F. 2.5 dB typ.	\$59.95
MMc144	N. F. 2.8 dB typ.	\$59.95
MMc220	N. F. 3.0 dB typ.	\$69.95
MMc432	N. F. 3.8 dB typ.	\$69.95
MMc432-S	N. F. 3.0 dB typ.	\$84.95
MMc438/ATV	Ch2 or Ch3 IF	\$94.95
MMc1296	N. F. 8.5 dB typ.	\$89.95

Send 30¢ (2 stamps) for full details of KVG crystal products and all your VHF & UHF equipment requirements.


Pre-Selector Filters Amplifiers SSB Transverters
Varactor Triplers Crystal Filters FM Transverters
Decade Pre-Scalers Frequency Meters VHF Converters
Antennas Oscillator Crystals UHF Converters



**Spectrum
International, Inc.**
Post Office Box 1084
Concord, Mass. 01742, USA



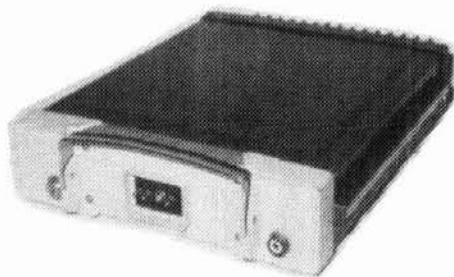GREGORY ELECTRONICS
The FM Used
Equipment People.



Save
\$20

Motorola Motrac

U43HHT-1100E, 12 volts, 150-170 MHz, 40 watts, Single Frequency, Fully Narrow Band, with accessories.

NOW

~~\$278~~
\$258.



GREGORY ELECTRONICS CORP.

245 Rt. 46, Saddle Brook, N.J. 07662
Phone: (201) 489-9000



WHERE ELSE
BUT DAVIS ?

600 MHz Mini Counter at \$149⁹⁵!

All Davis Frequency Counters deliver highest quality at low cost. But Series 7200 plug-in or battery-powered Mini Counters are truly minimal cost, general purpose instruments that sacrifice no basic performance characteristics. No other counter offers such superior features at Mini Counters' prices. One year warranty on assembled units, 90-day on kit components.

- 2 MODELS:** Kit \$149.95 Assembled \$199.95
- All Metal Cabinet
 - 8 Digit .4" LED Display
 - 115 V or 12 V operation
 - Selectable Gate Times: .1 & 1 sec.
 - Crystal Time Base (1 ppm after cal.)

- OPTIONS:** Portable w/Ni-Cad Battery (Built-in Charger) \$39.95
Crystal Oven (1 ppm 10 to 50°C) \$39.95 Handle \$5.00

Order direct from factory. Add \$3.00 for shipping, \$1.00 extra for C.O.D., and 7% sales tax in N.Y. State. Payment by certified check, money order, Master Charge, VISA, Credit-rated company P.O. accepted. Money back guarantee if returned in good condition in 10 days. Kits returnable only unassembled.

For more information, request FREE DESCRIPTIVE LITERATURE, or for in-depth preview, send \$3.00 for 32-page INSTRUCTION MANUAL. Detailed, illustrated. Credited against purchase of either unit.



DISTRIBUTOR INQUIRIES INVITED
Affordable quality is the Davis difference.

DAVIS ELECTRONICS
636 Sheridan Drive, Tonawanda, N.Y. 14150 • 716/874-5848

flea market



RATES Non-commercial ads 10¢ per word; commercial ads 60¢ per word both payable in advance. No cash discounts or agency commissions allowed.

HAMFESTS Sponsored by non-profit organizations receive one free Flea Market ad (subject to our editing). Repeat insertions of hamfest ads pay the non-commercial rate.

COPY No special layout or arrangements available. Material should be typewritten or clearly printed (not all capitals) and must include full name and address. We reserve the right to reject unsuitable copy. **Ham Radio** cannot check each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue

DEADLINE 15th of second preceding month.

SEND MATERIAL TO: Flea Market, Ham Radio, Greenville, N.H. 03048.

VERY in-ter-est-ing! Next 3 issues \$1. "The Ham Trader", Scyamore, IL 60178.

2FM — HR-212: 24 watts. 12 sets crystals. Microphone. Factory Service Manual. Excellent condition. \$125, delivered. TR-2200A: Batteries, Charger. Microphone. Case. 11 sets crystals. Manual. Mint condition. \$150, delivered. 2.5/20 watt M-Tech Amplifier, \$27.50, delivered. W8QX, 467 Park, Birmingham, Michigan 48009.

CANADIANS: 1,000,000 surplus electronic parts. Hundreds of fantastic bargains! Good deals on Yaesu & Icom. Free catalog, ETCO-HR, 183G Hymus Blvd., Pointe Claire, Quebec H9R 1E9.

FOR SALE Excellent Clegg FM-28 synthesized 2 meter FM transceiver 25 watts output and Clegg 12 amp regulated power supply \$300. Excellent Ameco preamplifier Model PT-2 for 1.8 to 54 MHz \$45. Shipping paid; offers considered. George Konnick Apt. C-5, 1750 West Main Street, Riverhead, New York 11901. (516) 727-6294.

MOBILE IGNITION SHIELDING provides more range with no noise. Available most engines. Many other suppression accessories. Literature, Estes Engineering, 930 Marine Dr., Port Angeles, WA 93862.

Foreign Subscription Agents for Ham Radio Magazine

Ham Radio Austria
Karin Ueber
Postfach 2454
D-7850 Loerrach
West Germany

Ham Radio Belgium
Stereohouse
Brusselsesteenweg 416
B-9218 Gent
Belgium

Ham Radio Canada
Box 114, Goderich
Ontario, Canada N7A 3Y5

Ham Radio Europe
Box 444
S-194 04 Upplands Vasby
Sweden

Ham Radio France
Christiane Michel
F-89117 Parly
France

Ham Radio Germany
Karin Ueber
Postfach 2454
D-7850 Loerrach
West Germany

Ham Radio Holland
MRL Electronics
Postbus 88
NL-2204 Delft
Holland

Ham Radio Italy
STE. Via Maniago 15
I-20134 Milano
Italy

Ham Radio Switzerland
Karin Ueber
Postfach 2454
D-7850 Loerrach
West Germany

Ham Radio UK
P.O. Box 63, Harrow
Middlesex HA3 6HS,
England

Holland Radio
143 Greenway
Greenside, Johannesburg
Republic of South Africa

SOLAR CELLS 4 inches diameter 2 amps. 4 volts \$6.75 each or 10 for \$65.00 plus shipping. W80DFS, 1742 Dowd Drive, St. Louis, Missouri 63136, (314) 522-6667.

CARTRIVISION Video recorders, parts, accessories and service (408) 224-0606.

FREE CATALOGS: P.C. Boards from artwork or magazine. 30¢ a sq. in. Also artwork, drills, parts and kits. Hauck Electronics, 1928 Fairacres Avenue, Pittsburgh, PA 15216.

WANTED: Any of the following items of military surplus communications equipment: AN/ARC-518X, R-761/ARC-58, T-730/ARC-58, or Wilcox 807 A/B. Will consider non-working units in repairable condition. Geoffrey W. Jones PSC 3, Box 6, APO NY 09692.

RECONDITIONED TEST EQUIPMENT for sale. Catalog \$.50. Walter, 2697 Nickel, San Pablo, Ca. 94806.

WANTED: Chassis for 'Broadcast Quality Television Camera' (Ham Radio, January 1978) with same specifications as shown in mechanical drawings for article. Will pay for professional-type job. SSGT Larry L. Garrison, PSC Box 2713, APO New York 09123.

HAM STATION EQUIPMENT plus test equipment. Send SASE to Len, W1ZTL, 22 Abbott Rd., Waltham, MA 02154.

SST ANTENNA TUNERS — your best buy. SST Electronics, Box 1, Lawndale, CA 90260.

ROHN TOWERS — Buy wholesale from World Wide distributor 25G sections \$35.97 each — 45G sections \$54.89 each. 100 foot tower kit \$628.22. 48 foot fold over tower \$515.50, freight paid — 40 foot free standing BX \$171.97 — Hill Radio, 2503 G.E. Road, Bloomington, IL 61701, (309) 663-2141.

SOLAR PANELS. Amateur group has limited number of very high quality panels for sale or trade for 220 rptr or rigs. Perfect for solar rptr. For info send SASE to Don, 110 Amigo Rd., Danville, CA 94526.

QSL CARDS 500/\$10. 400 illustrations, sample. Bowman Printing, Dept. HR, 743 Harvard, St. Louis, MO 63130.

EMC/RFI. Quick-Look analysis, low cost, military and commercial specifications. EMC Comp-U-Scan, Box 861-A, Valley Forge, PA 19481.

ELECTRONIC BARGAINS, CLOSEOUTS, SURPLUS! Parts, equipment, stereo, industrial, educational. Amazing values! Fascinating items unavailable in stores or catalogs anywhere. Unusual FREE catalog. ETCO-012, Box 762, Plattsburgh, N.Y. 12901. SURPLUS WANTED.

FOR SALE: One G.E. Master Pro in outdoor cabinet with duplexer. B. M. Ellison, III, 222 Bramblewood, Summerville, SC 29483.

EZ deals are the best! Try me and see for Yaesu, Drake, KLM, Swan, Cushcraft, DenTron, VHF Eng., ICOM, CDE, Hustler, Wilson and more. Call, see or write W0EZ, Bob Smith Electronics, RFD 3, Hwy 169 & 7, Fort Dodge, IA 50501. (515) 576-3886.

RTTY PARTS AND MACHINES: Model 28RO's, KSR's, ASR's, typing reperfs, TD's. Gears — all machines. Undermore reperf for 28ASR, single-speed, \$285.00 PP. Auto CR-LF non-overline kit for M28, \$12.75 PP. M28 stand-alone TD, single-speed, \$170.00 PP. Model 15 covers, gears, etc. 14TD, \$50.00 PP. M14 keyboard typing reperf, \$95.00 PP. Much more. Send SASE for complete list machines and parts. Lawrence R. Pflieger, K9WJB, 1715 E. McPherson St., Kirksville, MO 63501.


RM-300 RTTY Modem, the complete TU and AFSK generator on one board. This modem featured Sept '78 Ham Radio. Complete documentation \$2.00. RM-300 Modem or RP-400 Power Supply board just \$21.25. Complete RM-300 or RP-400 kit less PROM \$71.25. PROM programmed with your call \$7.00. WA6DNR Eclipse Communications, 5 Westwood Drive, San Rafael, CA 94901.


FREQUENCY ALLOCATION CHART. See how the entire radio spectrum is used. 2 kHz to 200 GHz. Send \$3.00. Collins Chart Co., Box 935, Coronado, CA 92118.


MANUALS for most ham gear made 1937/1970. Send only 25¢ coin for list of manuals, postpaid. HI, Inc., Box H864, Council Bluffs, Iowa 51501.


FERRITE BEADS: w/specification and application sheet - 12/\$1.00. Assorted PC pots - 10/\$1.00. Miniature mica trimmers, 3-40 pF. - 5/\$1.00. Postpaid. Includes latest catalog. Stamp for catalog alone. CPO Surplus, Box 189, Braintree, MA 02184.

MOBILE HF ANTENNA, 3.5 - 30 MHz inclusive, 750 watts PEP, center loaded coil, tuned from the base, eliminating coil changing or removing from mount. Less than 1.5 to 1 VSWR on all ham bands. \$119.95 each — contact your local dealer or order from Antec, Inc., Box 543, Jerome, Idaho 83338. (208) 324-3400. Master Charge and VISA cards accepted. Dealer inquiries invited.

14 Pin DIP extender cable. 36" long with MOLDED plug each end. Highest quality \$2.00 ea.  6 for \$10.00

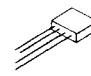
Molded bridge rectifier. 100 volt PIV @ 2 amps. 45¢ ea. or 5 for \$2.00 ppd. 


Photocell — first quality plastic encapsulated. Dark resistance 100 megohm; Lite resistance 150 ohms. 20¢ ea. 6 for \$1.00 ppd. 


Single RCA type jack. High quality factory new. 15¢ ea. 8 for \$1.00 


7 segment display FND type. Cosmetic rejects. Common anode .5 high. Real nice. 75¢ each 

Jumbo LEDs. .2 inch diameter. Color-Red. Prime factory units. Not seconds or retests. 20¢ ea. ppd.

4PDT Relay, 12 VDC coil, Potter Brumfield, 5 amp contacts, factory new of course, a beauty. Also available with 24 VDC coil. \$1.90 ea. ppd. 

Vertical Mount Trimmer Pots — All highest quality. No junk. 100 - 1000 - 2000 - 5000 - 10K - 20K - 25K - 50K - 250K - 500K Ohms. All have thumbscrew adjust. Your choice 5 for \$1.00 ppd. 

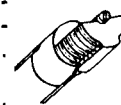Highest Quality E. F. Johnson Trimmer Caps. Hard-to-find P.C. board mount. .5-11 mmfd. No junk. 90¢ each; 10 for \$7.50 ppd. 

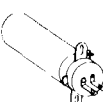SUPER-BUY — 5000 mfd. @ 40 volt electrolytic cap. factory new and complete w/all hardware. \$1.35 ea. ppd. 

1000 volt PIV 2 amp diodes .10 ea.


88 mHy unpotted toroids 5 for \$3.50

S0239 Coax Fittings 50¢ ea.
PL259 Coax Fittings 50¢ ea.

Transformer: 115V AC Primary, Secondary 17-0-17V @ 7 Amps. We tested and find good for 10 Amps intermittent duty. Ideal for 2M rigs! \$8.00 ea. ppd.

ALL ITEMS PPD USA
SEND STAMP FOR LIST OF BARGAINS
PA RESIDENTS ADD 6% SALES TAX
FONE 412-863-7006

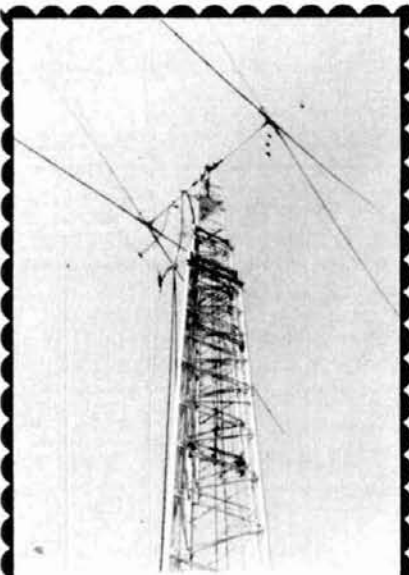 **Full Electronics**
12690 ROUTE 30
NORTH HUNTINGDON, PA. 15642



The Popular CUA 64-12 by Heights

Light,
permanently
beautiful
ALUMINUM
towers

**THE MOST IMPORTANT
FEATURE OF
YOUR ANTENNA
IS PUTTING
IT UP WHERE
IT CAN DO
WHAT YOU EXPECT.
RELIABLE DX —
SIGNALS EARLIEST IN
AND LAST OUT.**

ALUMINUM
Complete Telescoping
and Fold-Over
Series Available
Self-Supporting
Easy to Assemble
and Erect
All towers mounted
on hinged bases

And now, with motorized options, you can crank it up or down, or fold it over, from the operating position in the house.

Write for 12 page brochure giving dozens of combinations of height, weight and wind load.

Please include 30¢ (stamps or coins) for postage and handling when requesting our free literature.

ALSO TOWERS FOR WINDMILLS

HEIGHTS MANUFACTURING CO.

In Almont Heights Industrial Park
Almont, Michigan 48003

MICROWAVE TECHNICIANS: Donrey Media Group in Las Vegas and Reno seeks qualified microwave service technicians for Lenkurt 7576 systems on 7 kmc. Send resume & salary requirements or call: E. Doren, Director/Engineering, Donrey Media Group, P.O. Box 70, Las Vegas, Nevada 89101, Phone (702) 385-4241, Ext. 258. Equal Opportunity Employer.

TELETYPE EQUIPMENT for beginners and experienced operators. RTTY machines, parts, supplies. Beginner's special: Model 15 Printer and demodulator \$139.00. Dozen black ribbons \$6.50; case 40 rolls 11/16 perf. tape \$17.50 FOB. Atlantic Surplus Sales, 3730 Nautilus Ave., Brooklyn, N. Y. 11224. Tel: (212) 372-0349.

RTTY — Bandpass active filter 2125/2295 Hz. Kit \$11.95, W/T \$16.95 ppd. SASE for info. Nat Stinnette Electronics, Tavares, FL 32778.

440-MHz — Regency HR-440 like new \$220.00, SBE-450 very clean \$140.00. trade/sell listing 70 items test equipment, FM, Ham misc, write K6KZT, 2255 Alexander, Los Osos, CA 93402.

MOTOROLA low band Mocom 70 29.6 MHz, no accessories \$275. Motorola low band PT300 5W portable 52.525 MHz with charger \$300, Motorola SSR-2 solid state 30W repeater 146.28/146.88 MHz \$600. Homebrew "ACCUMEMORY" keyer with paddle \$125. Basket Case HT200 VHF \$50. Eric Meth, VE2AS, 6716 Sherbrooke W., Apt. 201, Montreal, Que. H4B 1P2, (514) 482-6608.

TEKTRONIX 310A oscilloscope, mint condition, calibrated, \$175.00 or trade for test equipment, commercial FM VHF, Ham gear. H. Beene, W5ZSL, P.O. Box 5702, Santa Fe, NM 87502, (505) 471-5458.

THE MEASUREMENT SHOP has used/reconditioned test equipment at sensible prices; catalog. 2 West 22nd St., Baltimore, MD 21218.

HAMS requesting our famous "SHOOT THE BULL" QSL Card, send yours & SASE K4BNB, Box 23413, Jacksonville, FL 32217.

CLUB CALL PINS 3 lines 1 1/4 x 3 1/4 \$1.55 each. Call, first name and club. Colors — black, blue or red with white letters. (Catalog) Arnold Linzner, 2041 Linden Street, Ridgewood, N. Y. 11227.

SELL — Boonton 202D Signal Generator, Reconditioned, \$50 plus transp. W6LGO, 34 Laurel Ave., Petaluma, CA 94952.

AUTHORIZED DISTRIBUTOR F9FT Antennas, Microwave Modules, RIW Products' new tandem reflector, 19 element, 432 MHz Yagi — Radio Clinic — N2MB (formerly WA2BIT) 212-327-4952.

FOR SALE 75S-3B, 32-S3, 516F-2, Manuals & Cables. Excellent condition, \$1375. Extra 75S-3B \$550. S. J. Huber W7NOI, 318 Steven Ct., Benicia, CA 94510. (707) 745-8089.

TUNGSTEN CARBIDE CIRCUIT BOARD DRILLS. 12 assorted sizes for \$3.95 ppd. L. R. Design, Box 41, McMinnville, OR 97128.

SWAN 250, TV-2, 14-117 power supply, bandswitching, manuals, mike, 250 Watts input on both 6 and 2 meters. \$375.00. Fred Clinger, 640 Grove Avenue, Galion, Ohio 44833, WABKJJ.

PORTA PAK — Make your FM mobile a self-contained portable. Models in stock for most popular makes. 4.5 amp hr model \$67.50. 9 amp hr \$88.00. Charger included, shipping extra. P.O. Box 67, Somers, WI 53171.

TEST EQUIPMENT CATALOG listing used Tektronix, HP and GR equipment at bargain prices. PTI, Box 8699, White Bear Lake, MN 55110. Price \$1.00 refundable with first order.

WANTED: 150 MC HT RCA, Comco, Repco type with plug-in modules, 7735 TV camera tube, 2 meter cavities, K6KZT, 2255 Alexander, Los Osos, CA 93402.

WANTED — Radio transcription discs. Any size or speed. Larry, W7FIZ, Box 724, Redmond, Washington 98052.

DESK TOP CONSOLES, ultimate operating convenience. Free brochure. Thompson Electronics, P.O. Box 363, Westfield, IN 46074.

BUY-SELL-TRADE: Send \$1.00 for catalog. Give name, address and call letters. Complete stock of major brands new and reconditioned amateur radio equipment. Call for best deals. We buy Collins, Drake, Swan, etc. Associated Radio, 8012 Conser, Overland Park, KS 66204 (913) 381-5900.

TECH MANUALS for Govt. surplus gear — \$6.50 each: SP-600JX, URM-25D, OS-8A-U, TS-17/UR. Thousands more available. Send 50¢ (coin) for 22-page list. W3IHD, 7218 Roanne Drive, Washington, DC 20021.

MILO ASSOCIATES

BOX 2323 • INDIANAPOLIS, INDIANA 46206

EQUIPMENT
SUBSTITUTES
COMPONENTS
MATERIALS

PHONE 318-5350

YEAR	HAMS SERVING HAMS
	COAXIAL CONNECTORS
PL259's	10/\$5 \$40/C
SO239's	10/\$5 \$40/C
UGB3's	(*N'/UHF) \$4.50
UG146U (UHF/N)	\$4.50
PL258	Barrel \$1.25
PL259PO	Push-on \$1.50
UG1094	BNC F \$1.00
UG88	BNC M \$1.25

WE STOCK ALL TYPES!!!

CERAMIC TRIMMERS	76477 SOUND EFFECT IC
3-9pf	5-5-18pf
3-10pf	10-60pf
4.5-20pf	30-90pf
MIX/MATCH	10/\$5

BRIDGES	FERRITE!
IR #30DB4P-NEW!	RODS — 1/2" x 5"
400V @ 3AMP	\$1 ea. 6/\$5
Stock up NOW!	*****
\$1 ea. 6/\$5	BEADS 12/\$1
	Limited supply

ELECTROLYTIC'S	H-P TEST EQUIPMENT
FACTORY FRESH RADIALS!	200CD Osc. \$75
1mfd @ 25v 8/\$1.00	211B - NEW! \$375
100 @ 25v 6/\$1.00	400H \$110
2200 @ 16v 3/\$1.00	415B - NEW! \$175
	425A \$125
	34701A \$75

ITS EASY TO ORDER!

Use Visa; Master Charge; Check, M.O.; C.O.D.
Telephone orders welcome
Allow for shipping - excess quickly refunded
Minimum order of \$5.00 please!
Indiana residents add 4% tax
Prices good through cover month

BIRD WATCHERS

Don't be absurd, buy a BIRD!
... from your Bird distributor

MODEL 43 \$125

**ALL ITEMS AND ELEMENTS
ORDINARILY IN STOCK**
Prepaid Shipment in Continental USA Only

MADISON ELECTRONICS SUPPLY, INC.

1508 MCKINNEY HOUSTON, TEXAS 77002
713/658-0268 Nites 713/497-5683

Presenting
THE A.R.O. UNITY RING

Instant Identity

The time has come for all amateurs to unite on sight. We must know each other as do other fraternal organizations. The ability to recognize each other on any occasion is a true mark of fraternal brotherhood. Group III, (WB2LCK, KB2DX and KB2DZ) designed this 10 karat gold ring to portray our great and proud fraternity. This exquisite ring is made exclusively for you by Josten's (world famous for their quality achievement rings) with your call letters prominently displayed. For detailed information and reusable ring size... Write: Group III Sales Co. Dept. 35 P.O. Box 259 Little Neck, N.Y. 11362

No Obligation

DIODES/ZENERS			
QTY.			
1N914	100v	10mA	.05
1N4005	600v	1A	.08
1N4007	1000v	1A	.15
1N4148	75v	10mA	.05
1N4733	5.1v	1 W Zener	.25
1N753A	6.2v	500 mW Zener	.25
1N758A	10v	"	.25
1N759A	12v	"	.25
1N5243	13v	"	.25
1N5244B	14v	"	.25
1N5245B	15v	"	.25

SOCKETS/BRIDGES			
QTY.			
8-pin	pcb	.20 ww	.35
14-pin	pcb	.20 ww	.40
16-pin	pcb	.20 ww	.40
18-pin	pcb	.25 ww	.95
20-pin	pcb	.35 ww	.95
22-pin	pcb	.35 ww	.95
24-pin	pcb	.35 ww	.95
28-pin	pcb	.45 ww	1.25
40-pin	pcb	.50 ww	1.25
Molex pins	.01	To-3 Sockets	.25
2 Amp Bridge		100-prv	.95
25 Amp Bridge		200-prv	1.50

TRANSISTORS, LEDES, etc.			
QTY.			
2N2222	(2N2222 Plastic .10)		.15
2N2222A			.19
2N2907A	PNP		.19
2N3906	PNP (Plastic Unmarked)		.10
2N3904	NPN (Plastic Unmarked)		.10
2N3054	NPN		.45
2N3055	NPN 15A 60v		.60
T1P125	PNP Darlington		1.95
LED Green,	Red, Clear, Yellow		.15
D.L.747	7 seg 5/8" High com-anode		1.95
MAN72	7 seg com-anode (Red)		1.25
MAN3610	7 seg com-anode (Orange)		1.25
MAN82A	7 seg com-anode (Yellow)		1.25
MAN74	7 seg com-cathode (Red)		1.50
FND359	7 seg com-cathode (Red)		1.25

9000 SERIES			
QTY.		QTY.	
9301	.85	9322	.65
9309	.35	9601	.20
9316	1.10	9602	.45

MICRO'S, RAMS, CPU'S, E-PROMS			
QTY.		QTY.	
8T13	1.50	2107B-4	4.95
8T23	1.50	2114	9.50
8T24	2.00	2513	6.25
8T97	1.00	2708	10.50
74S188	3.00	2716 D.S.	34.00
1488	1.25	2716 (5v)	59.00
1489	1.25	2758 (5v)	23.95
1702A	4.50	3242	10.50
AM 9050	4.00	4116	11.50
		6800	13.95
MM 5314	3.00	6850	7.95
MM 5316	3.50	8080	7.50
MM 5387	3.50	8212	2.75
MM 5369	2.95	8214	4.95
TR 1602B	3.95	8216	3.50
UPD 414	4.95	8224	3.25
Z 80 A	22.50	8228	6.00
Z 80	17.50	8251	7.50
Z 80 PIO	10.50	8253	18.50
2102	1.45	8255	8.50
2102L	1.75	TMS 4044	9.95

C MOS	
QTY.	
4000	.15
4001	.15
4002	.20
4004	3.95
4006	.95
4007	.20
4008	.75
4009	.35
4010	.35
4011	.20
4012	.20
4013	.40
4014	.75
4015	.75
4016	.35
4017	.75
4018	.75
4019	.35
4020	.85
4021	.75
4022	.75
4023	.20
4024	.75
4025	.20
4026	1.95
4027	.35
4028	.75
4029	1.15
4030	.30
4033	1.50
4034	2.45
4035	.75
4037	1.80
4040	.75
4041	.69
4042	.65
4043	.50
4044	.65
4046	1.25
4048	.95
4049	.45
4050	.45
4052	.75
4053	.75
4066	.55
4069/74C04	.35
4071	.25
4081	.30
4082	.30
4507	.95
4511	.95
4512	1.10
4515	2.95
4519	.85
4522	1.10
4526	.95
4528	1.10
4529	.95
MC 14409	14.50
MC 14419	4.85
74C151	1.50

LINEARS, REGULATORS, etc.			
QTY.		QTY.	
MCT2	.95	LM323K	5.95
8038	3.95	LM324	1.25
LM201	.75	LM339	.75
LM301	.45	7805 (340T5)	.95
LM308	.65	LM340T12	.95
LM309H	.65	LM340T15	.95
LM309K (340K-5)	1.50	LM340T18	.95
LM310	.85	LM340T24	.95
LM311D	.75	LM340K12	1.25
LM318	1.75	LM340K15	1.25
LM320H6	.79	LM340K18	1.25
LM320H15	.79	LM340K24	1.25
LM320H24	.79	LM373	2.95
7905 (LM320K5)	1.65	LM377	3.95
LM320K12	1.65	78L05	.75
LM320K24	1.65	78L12	.75
LM320T5	1.65	78L15	.75
LM320T12	1.65	78M05	.75
LM320T15	1.65		
		LM380 (8-14 Pin)	1.19
		LM709 (8-14 Pin)	.35
		LM711	.45
		LM723	.40
		LM725	2.50
		LM739	1.50
		LM741 (8-14)	.35
		LM747	1.10
		LM1307	1.25
		LM1458	.65
		LM3900	.50
		LM75451	.65
		NE555	.45
		NE556	.85
		NE565	.95
		NE566	1.25
		NE567	.95

- T T L -			
QTY.		QTY.	
7400	.10	7482	.75
7401	.15	7483	.75
7402	.15	7485	.55
7403	.15	7486	.25
7404	.10	7489	1.05
7405	.25	7490	.45
7406	.25	7491	.70
7407	.55	7492	.45
7408	.15	7493	.35
7409	.15	7494	.75
7410	.15	7495	.60
7411	.25	7496	.80
7412	.25	74100	1.15
7413	.25	74107	.25
7414	.75	74121	.35
7416	.25	74122	.55
7417	.40	74123	.35
7420	.15	74125	.45
7426	.25	74126	.35
7427	.25	74132	.75
7430	.15	74141	.90
7432	.20	74150	.85
7437	.20	74151	.65
7438	.20	74153	.75
7440	.20	74154	.95
7441	1.15	74156	.70
7442	.45	74157	.65
7443	.45	74161	.55
7444	.45	74163	.85
7445	.65	74164	.60
7446	.70	74165	1.10
7447	.70	74166	1.25
7448	.50	74175	.80
7450	.25	74176	.85
7451	.25	74180	.55
7453	.20	74181	2.25
7454	.25	74182	.75
7460	.40	74190	1.25
7470	.45	74191	1.25
7472	.40	74192	.75
7473	.25	74193	.85
7474	.30	74194	.95
7475	.35	74195	.95
7476	.40	74196	.95
7480	.55	74197	.95
7481	.75	74198	1.45
		74221	1.00
		74367	.95
		75108A	.35
		75491	.50
		75492	.50
		74H00	.15
		74H01	.20
		74H04	.20
		74H05	.20
		74H08	.35
		74H10	.35
		74H11	.25
		74H15	.45
		74H20	.25
		74H21	.25
		74H22	.40
		74H30	.20
		74H40	.25
		74H50	.25
		74H51	.25
		74H52	.15
		74H53	.25
		74H55	.20
		74H72	.35
		74H74	.35
		74H101	.75
		74H103	.55
		74H106	.95
		74L00	.25
		74L02	.20
		74L03	.25
		74L04	.30
		74L10	.20
		74L20	.35
		74L30	.45
		74L47	1.95
		74L51	.45
		74L55	.65
		74L72	.45
		74L73	.40
		74L74	.45
		74L75	.85
		74L93	.55
		74L123	.85
		74LS00	.30
		74LS01	.30
		74LS02	.30
		74LS04	.30
		74LS05	.35
		74LS08	.35
		74LS10	.35
		74LS11	.35
		74LS12	.35
		74LS13	.35
		74LS15	.35
		74LS16	.35
		74LS17	.35
		74LS100	.35

INTEGRATED CIRCUITS UNLIMITED
 7889 Clairemont Mesa Blvd., San Diego, California 92111
 24 Hour Toll Free Phone 1-800-854-2211
 (714) 278-4394 California Residents 1-800-542-6239
 CABLE ADDRESS ICUSD

CUSTOMER NAME _____
 STREET ADDRESS _____
 CITY _____ STATE _____ ZIP _____
 PHONE _____ CHARGE CARD # _____ AE Visa BA MC _____ EXP. DATE _____

SPECIAL DISCOUNTS

Total Order	Deduct
\$35-\$99	10%
\$100-\$300	15%
\$301-\$1000	20%

C.O.D. _____ WILL CALL _____ UPS _____ POST _____ NET 10th OF THE MONTH _____ PO # _____
 ALL ORDERS SHIPPED PREPAID - NO MINIMUM - COD ORDERS ACCEPTED - ALL ORDERS SHIPPED SAME DAY
 OPEN ACCOUNTS INVITED - California

Antenna Designers

Is your career on the beam? At Cushcraft it could be. We are looking for good engineers who would like to use their expertise to create the best communications antennas in the world.

We are involved in the full spectrum of antennas from 3 to 1000 MHz. From multiband to single frequency we manufacture antennas for commercial, government and amateur applications.

We have engineering openings for EE's with experience in antenna design and production engineering. Cushcraft needs productive self-starters who can carry a design from concept through production, who can supervise their assistants, and who can separate their hobby from their professional activities.

We have advanced design lab and test facilities, challenging and interesting assignments, and an excellent working atmosphere.

We are located in southern New Hampshire which offers suburban conveniences and close proximity to the rural White Mountains and Metropolitan Boston. Sound interesting? Send your resume along with salary requirements to:

Glen Whitehouse



The Antenna Company

P.O. Box 4680, 48 Perimeter Road
Manchester, N. H. 03108

603-627-7877

An Equal Opportunity Employer

BE GOOD TO YOURSELF through R-UN. Reward yourself with a new accessory or antenna or a new band or a second rig or new first-string replacement rig. Here's R-UN's partial reward-yourself list. Accessory: keyer (), tuner (), amp (), other (), Antenna: mobile (), fixed vertical (), tower (), other (), A second rig: mobile (), GRP (), hernia special (), A new band: 2 meters (), higher (), to duh moon (), Solid state HF for your ARS (). We can help you select from top amateur equipment brands. And will even mail along a "Thank You" card from U to U. (Or anyone else.) Don't just leave to North Pole Nick (or the Bunny) again. R-UN in or jingle the telephone bells now to Radios Unlimited, 1760 Easton Avenue, P.O. Box 347, Somerset, New Jersey 08873. (201) 469-4599.

STAR-TRONICS monthly picture flyer is full of parts and pieces for the builder. Cheap. Quality. U.S. only. Star-Tronics, Box 683, McMinnville, OR 97128.

MICROWAVE low-noise TWT preamplifiers for satellite/amateur bands; 2.0-4.0 GHz passband; 25-30 dB gain; 100 volt 60 Hz power; TNC connectors; used units tested okay but sold as-is; \$200 plus \$4 shipping. M. Mursec, 5511 West Jerelyn, Milwaukee WI 53219.

STOP LOOKING for a good deal on amateur radio equipment — you've found it here — at your amateur radio headquarters in the heart of the Midwest. We may not have a toll free number but we'll save you more in the long run! We are factory-authorized dealers for Kenwood, Drake, Yaesu, Collins, Wilson, Ten-Tec, Atlas, ICOM, DenTron, MFJ, Tempo, Regency, Hy-Gain, Mosley, Alpha, Cushcraft, Swan, and many more. Write or call us today for low quote and try our personal and friendly Hoosier service. HOOSIER ELECTRONICS, P.O. Box 2001, Terre Haute, Indiana 47802. (812) 238-1456.

Coming Events

RADIO EXPO '79 September 15th and 16th, 1979, Lake County Fair Grounds, Routes 120 and 45, Grays Lake, Illinois. Manufacturers' displays, flea market, seminars, ladies programs. Advance tickets \$2.00. Write EXPO, P.O. Box 305, Maywood, IL 60153. Exhibitors inquiries: EXPO Hotline (312) 345-2525.

MASSACHUSETTS: University of Lowell Wireless Society 5th annual ham radio auction, Friday, March 16. Doors open 5 pm, auction starts 6 pm, talk-in on 52, coffee, donuts. Directions: from Route 495 take exit 26 (Route 38) north two miles to route 110 west two miles right on University Avenue.

ROCHESTER Hamfest & NY State ARRL Convention, May 25-27. Add your name to mailing list. Send QSL to Rochester Hamfest, Box 1388, Rochester, NY 14603. Phone (716) 424-1100.

MINNESOTA: Rochester ARC and the Rochester Repeater Society's Hamfest, Saturday, April 7, St. John's School Gymnasium, 490 W. Center St., Rochester. Doors open 8:30 AM. Large indoor flea market, prize raffles, free parking. Talk in on 146.22/82. For info: RARC, c/o K0TS, 2514 N.W. 4th Ave., Rochester, MN 55901.

MICHIGAN: ARRL Great Lakes Division Convention and Hamfest, Muskegon Community College, Muskegon, March 30-31. Exhibits, technical forums, large swap/shop, dining facilities. Friday evening — "Ham Hospitality" at Muskegon Ramada Inn courtesy of MAARC; and a Wouf Hong initiation. For info: MAARC, P.O. Box 691, Muskegon, MI 49443 or WABGVK (616) 722-1378/9.

OHIO: First Annual Lake County ARA Hamfest, April 1, 8:00 AM to 4:00 PM, Lake County Armory, N. E. corner Painesville Fairgrounds, Rt. 20, Painesville, (35 miles east of Cleveland). All indoors for exhibitors and flea market, 1:00 PM auction. Reserved tables — full \$2.00, half \$1.00. Admission: \$2.00. Under 12 free. Talk in on 52/52 and 147.8121. For info: LCARA, P.O. Box 868, Painesville, OH 44077 or call (216) 257-4486.

WASHINGTON: Pacific Northwest Hamfest, July 14 & 15, HAM Inc., Box 78442, Seattle, WA 98178.

OHIO: Teays Amateur Radio Club Ham Fiesta, March 4, Pickaway County Fairgrounds colosseum, Circleville. All indoors. For info: Leonard Campbell, 8951 State Rt. 188, Circleville, OH 43113, phone (614) 474-6687.

OKLAHOMA: Lawton — Ft. Sill Amateur Radio Club's 33rd annual Hamfest. March 23, 24, 25, Montego Bay Motel, Lawton. Flea market, ARRL officials, technical meetings, QCWA breakfast. Activities for ladies. For info: Lawton-Ft. Sill ARC, P.O. Box 892, Lawton, OK 73502.

NORTH CAROLINA: Mecklenburg Amateur Radio Society's Metrolina Hamfest, March 24-25. NC State convention site, Charlotte. For info: Ken Winston, Jr., WA4OBO, Mecklenburg ARS, 2425 Park Rd., Rm. 023, Charlotte, NC 28203.

MILITARY SURPLUS WANTED

WE NEED: ARC-51BX, ARC-94, ARC-102, ARC-109, ARC-115, ARC-116, ARC-131, ARC-134, ARC-164, ARN-82, ARN-83, ARN-84, APN-59, APN-153, APN-141, APN-147, APN-171, APX-72, 618T, CU-1669A, 490T-1, CU-1658A, 51Y-4, 51R-8, 51RV-1, FM-620, 807A, URC-9, TOP DOLLAR PAID OR TRADE FOR NEW AMATEUR GEAR. WRITE OR PHONE BILL SLEP (704) 524-7519, SLEP ELECTRONICS COMPANY, HIGHWAY 441, OTTO, NORTH CAROLINA 28763.

SYNTHESIZERS

We have the worlds largest selection of synthesizers for receivers, transmitters and transceivers. For complete details see our 1/3 page ad in the April 1976 issue of this magazine or call or write for additional information. Phone orders accepted between 9 AM and 4 PM EDT. (212) 468-2720

VANGUARD LABS

196-23 JAMAICA AVENUE
HOLLIS, N. Y. 11423



July 28 thru August 10, 1979

Have trouble finding time to study for Upgrading?

Do it on your vacation at the
**OAK HILL ACADEMY
AMATEUR RADIO SESSION**

20 years of successful teaching

Two weeks of intensive code and theory starting at your level.

Classes from Novice thru Amateur Extra

- Expert instructors
- Friendly surroundings
- Excellent Accommodations

C. L. PETERS, K4DNJ, Director
Oak Hill Academy Amateur Radio Session
Mouth of Wilson, Virginia 24363

Name _____ Call _____
Address _____
City/State/Zip _____

MADISON ELECTRONICS SUPPLY, INC.

1508-D MCKINNEY • HOUSTON, TEXAS 77002

713/658-0268

Master Charge — VISA

NEW! EXCITING! BREAKTHROUGH! YAESU FT7B Transceiver



FT7B **\$675.00**
100W Input, CW Filter

CALL FOR QUOTES ON:

YAESU	KENWOOD
FT901 DM	TS820S
FT625	TS520S
FT225	TR7400A
ALDA, AMCOMM, ETO ALPHA TEMPO VHF ONE PLUS	

Q 5-QRM Enterprises

SPRING, TEXAS 77373

The broad-band characteristics enable you to cover the entire phone band with less than 2:1 VSWR.

A distinctive advantage is the low-noise characteristics of the antenna, especially effective in reducing static noises since the antenna is D.C. Ground design.

This antenna is constructed of "high-quality" materials and many hours of pleasurable operation can be expected.

73's Mike WB5UZZ

- 75 BBD — \$59.95
- 40 BBD \$49.95



CALL FOR FAST QUOTES SPECIAL ORDERS WELCOME

TERMS: All prices FOB Houston. Prices subject to change without notice. All items Guaranteed. Some items subject to prior sale. Send letterhead for Amateur dealers price list. Texas residents add 6% tax. Please add postage estimate.

W5GJ, W5MBS, K5AAD, N5JJ, W5IMJ, AG5K, W5VVM, WD5EDE, K5ZD, WD5ABR, WA5TGU, WD5BDX, WB5AYF, K5RC, K5BGB, WB5USV

Have A Nice Day!

Buy our radios and you will never get static!

MARCH SPECIALS

OMNI-J & heavy duty magnet mount complete	\$49.95
TRIEX W-51 FT Self Support Tower (Reg. \$825.00)	
Your Cost (F.O.B. California)	\$725.00
Tonna F9FT Antennas 144/16el	\$79.95
RIW 432/19el	\$59.95
KLITZING VHF-UHF Amplifiers	
2M 10W In — 100W Out	\$198.00
432 10W In — 50 W Out	\$198.00
BIRD 43 & Slugs, UPS Paid	Stock
Microwave Modules 432-28S, UPS Paid	\$329.00
Telrex TB5EM, In Stock	\$415.00
NEW Palomar Engr. Transceiver Preamp	\$89.50
Bencher Paddles \$39.95; Chrome	\$49.95
ETO 76 Amplifiers	Stock
Lunar 6M-2M-220 In Line Preamps	\$49.95
Lunar 2M Amp 10-80 with Preamp, UPS Paid	\$198.00
Janel QSA-5	\$41.95
CDE HAM-3 \$129.00; HAM-X	\$249.00
VHF Engrs. blue line amps	Stock
Cetron 572B	\$29.50
Amperex 6146B	\$7.95
Motorola HEP-170	\$0.29 ea.
Mallory 2.5A/1000 PIV Epoxy Diode	\$0.19 ea.
Aerovox 1000PF/500V Feed thru	\$1.95
GE 6146B or 8950	\$7.95
Technical books: AMECO, ARRL, Sams, TAB, Rider, Radio Pub., Callbook, Cowan, many others	Call
NEW BELDEN 9405 (2#16) (6#18) 8 wire Rotor Cable	
heavy duty for long runs	\$0.26/ft.
8448, Std. 8-wire Rotor	\$0.16/ft.
9888, double shield RG8 Foam	\$0.39/ft.
8214, RG8 Foam	\$0.25/ft.
8237, RG-8	\$0.21/ft.
8267, RG-213	\$0.25/ft.
Amphonor Silver Plate PL259	\$0.59
TIMES 1/2" Foam Hardline \$0.65/ft	Connectors \$15.00 ea.
BERKTEK RG-8X, 52 ohm, KW	\$0.16/ft.
Consolidated HD-18 Ga. Galv. Tower, 10' Sec	\$29.95
Robot "Slow Scan" Now In Stock	Call
Alliance HD73 Rotor	\$109.95
Teletower - self support - 55 ft/w breaker	\$499.00

THIS MONTH'S SPECIAL

ICOM IC280 — \$385.00
BELDEN 8000 #14 Ga. Stranded 6¢/Ft.
We cut any length up to 1000 ft.



The 'Tonna' You've
been
hearing about

144/146 MHz	SWR 1.2:1
50 ohms	Horiz./Vert.
length 6.4 m.	Wt. 4.4 kg.
Side lobe attenuation — Superb	
Horizontal aperture	2 x 16° (-3 dB)
Vertical aperture	2 x 17° (-3 dB)

\$79.95

9 Element 144-146	\$39.95
4 Element 144-146	\$32.95

MADISON ELECTRONICS SUPPLY, INC.

1508-D MCKINNEY • HOUSTON, TEXAS 77002

713/658-0268

Master Charge — VISA

CONNECTORS  BNC M/UHF-F UG-253U \$3.00  BNC F/UHF-M UG-273U \$2.50  BNC F/BNC-F UG-914U \$2.00  UHF F/UHF-F PL-258 \$1.50  'M' F/BNC-M UG-149U \$3.75  'N' M/UHF-F UG-146U \$4.75  'N' F/UHF-M UG-83BU \$4.75  RCB Adapter UG-175 \$.25  BNC M-CABLE UG-88 \$1.35  BNC F-PANEL UG-1094 \$1.00  "N" M CABLE UG-210 \$2.95  "N" F PANEL UG-58 \$2.25		5 V. DIP RELAY  \$1.50						
 DIODES HIGH VOLTAGE 3000PIV 250MA \$1.55 8000PIV 350MA \$1.25 6000PIV 750MA \$2.75		 16 PIN IC ADAPTER. MFG. BY AUGAT. HAS ROUND GOLD PINS WITH SOLDER CONNECTIONS. 65¢ each SURPLUS POWER SUPPLY 5V. 6A. Regulated 115VAC \$14.95						
LED JUMBOS 1. 10M \$1.00 100 FOR \$7.95		 Solder Tail 8 pin \$1.20 14 pin \$1.18 16 pin \$1.18 22 pin \$1.36 24 pin \$1.35 28 pin \$1.40 40 pin \$1.85 WIRE WRAP 14 pin \$1.35 16 pin \$1.38 24 pin \$1.75 40 pin \$1.95						
25¢ 1N4007 10¢		50 ohm COAX RG 174 U 50 FT. \$2.75						
.1 OHM 5 WATT RESISTORS 5 FOR \$1.00 50 OHM 200 WATT \$2.50 EA.		POWER SUPPLY MODULE RATED AT 12V @ 2.5A. CAN BE MODIFIED BY CHANGING THE ZENER. PARTS: 4-3A DIODES, 1-2.5A FUSE, 1-2200MF @ 35V CAP., 1-12V ZENER, 1-PASS TRANS., WITH HEAT SINK. \$4.95						
 USED FANS 100 CFM 115VAC 4.5" x 1.5" GUARANTEED \$6.95		Computer Grade capacitors 10,000uf 50v \$2.95 23,200uf 50v 1.50 100,000uf 10v 1.75						
 Touch-Tone Housing. BLACK only...\$3.25		 5V NICA 4 AA SIZE CELLS. THEY GIVE 5V @ 500MA \$3.95						
 NYLON CABLE TIES 4 INCH 100EA \$1.50 6 INCH 100EA \$2.50		 50-239 65¢ PL-259 65¢ 10/\$6.00 MIX & MATCH						
 2N5589 CASE 107-73 \$2.95		 2N5590 CASE 10-117 \$4.95						
 200PIV 25A \$1.75		7812 V. REG. 12V. 1AMP. HOUSE MARKED 75¢						
<table border="1"> <tr> <td>M</td> <td>P</td> <td rowspan="2"> MARLIN P JONES & ASSOC. PO BOX 9023 RIVIERA BEACH, FLORIDA 33404 (305) 848-8236 </td> </tr> <tr> <td>J</td> <td>A</td> </tr> </table>				M	P	MARLIN P JONES & ASSOC. PO BOX 9023 RIVIERA BEACH, FLORIDA 33404 (305) 848-8236	J	A
M	P	MARLIN P JONES & ASSOC. PO BOX 9023 RIVIERA BEACH, FLORIDA 33404 (305) 848-8236						
J	A							

*Fla. residents add 4% sales tax.
 *MC & VISA accepted, please include expiration date and signature as on card.
 *Add \$1.00 for order under \$10.00.
 *Canada & Foreign orders please add sufficient postage.
 **USA orders please add 5% postage.

MARYLAND: Greater Baltimore Hamboore, Sunday, April 1, 8:00 AM, Calvert Hall College, Goucher Blvd. and LaSalle Rd., Towson. (1 mile south of Exit 28, Beltway Interstate 695) Food, prizes, giant flea market. Admission: \$3.00. 250 tables inside. For info and reservations: Bro. Gerald Maiseed, W3WVC, Calvert Hall College, 8102 LaSalle Rd., Towson, MD 21204 or (301) 825-4266.

ILLINOIS: Libertyville & Mundelein Amateur Radio Society's annual Hamfest, March 25, J. M. Club, 708 Greenwood Avenue, Waukegan. Open 7 AM. Tickets: \$2.00 gate, Advance: \$1.50. Under 10 free. Tables \$4.00 each. Large indoor flea market, Dozens of prizes including Wilson Mark IV Handie-Talkie. Hot Lunch, free parking. Talk in 146.94 simplex. For info: LAMARS, 1226 Deer Trail Lane, Libertyville, IL 60048. (312) 367-1599. (Include SASE).

NEBRASKA: Midway Spring Ham Convention, Saturday, Sunday, March 31, April 1. Holiday Inn — Holidome, Kearney. Over \$3,000 in prizes, FCC testing, Ladies Day, QCWA meeting, Flying Hams breakfast. Code contest, flea market, auction, banquet. For free brochure: Midway Spring Ham Convention, 3606 Third Avenue, Kearney, NE 68847.

TEXAS: Midland Amateur Radio Club's annual Swapfest, March 18, Midland County Exhibit Building. Door prizes. Talk in on 146.16/146.76. Preregistration: \$4.50 to Midland ARC, Box 4401, Midland, TX 79701 or \$5.00 at door.

WISCONSIN: Trj County ARC Hamfest, March 18, Jefferson County Fairgrounds, Jefferson. (Formerly at Whitewater). Advance tickets \$1.50. Reserve 6-ft tables \$2.00 advance. 6-ft space \$1.00. Send SASE to Glenn Eisenbrandt, WA9VYL, 711 East St., Fort Atkinson, WI 53538.

WISCONSIN: Madison Area Repeater Association's 7th annual Swapfest, Sunday, April 8, Dane County Exposition Center Forum Building, Madison. Open 7:00 AM for exhibitors and sellers, 8:00 AM public. Admission: \$1.50 advance, \$2.00 door. Twelve and under free. Tables \$3.00 advance, \$3.50 door. Flea market, plenty of parking, overnight camping and hotels within walking distance. Door prizes. All-you-can-eat pancake breakfast and Bar B-Q lunch. Free movies throughout the day. Talk in on WR9ABT — 146.16/76. For reservations and info: MARA, P.O. Box 3403, Madison, WI 53704.

FLORIDA: Ninth Annual North Florida Swapfest, Ft. Walton Beach Fairgrounds, March 24 and 25. 8:00 AM to 4:00 PM. QCWA, MARS, ARES meetings. Talk in 52 and 19/79. For info: PARC, Box 873, Ft. Walton Beach, FL 32548.

QSO PARTY — NEW ZEALAND: ZL3 Canterbury Chapter of the International 10/10 net. From 0000 GMT Saturday, March 31, 1979 to 1200 GMT Sunday, April 1, 1979 (36 hours). Contact each station only once, on the ten meter band only; exchange call sign, name, QTH, 10X number, if any, Canterbury Chapter number (if held) and your own local Chapter name and number, if any. Awards include trophy to highest scorer overall, and a pennant to the highest scorer in each U.S., Canadian, Australian, Japanese and New Zealand call area, to each Central and South American country; to each European, Asian, and African country; and in three Pacific Ocean zones. Logs must be received no later than May 15, 1979. Please write clearly, show name, call, address and 10X number. Send logs to ZL3ME — C.J. Bramley, 198 Greers Road, Christchurch 5, New Zealand.

TEXAS: "Luckenbach DXpedition", 0800 CDT May 12, 1979 to 1200 CDT May 13, 1979, continuous. Call W5TEX. CW: 7.110 MHz and 21.110 MHz (+/- 5 kHz); FM: 52.525 MHz, 29.6 MHz, and 146.52 MHz; SSB: 3.9, 7.235, 14.285, 21.360, 28.625, 50.110 and 144.200 MHz; (+/- 5 kHz). Luckenbach sits nestled between two small rivers in the heart of the Texas hill country. Virtually untouched by modern civilization, this 1870's cowtown got its first pay telephone only last year. Luckenbach's general store/saloon/postoffice combination serves as a community center and gathering place for citizens to watch for the annual return of the mud dauber — a red hornet. Don't miss the fun of our "DXpedition": Send all logs and inquiries to Bob Schneider, AI5Q, 7206 Gumtree, San Antonio, Texas 78238.

Stolen Equipment

ICOM IC-701, serial number 8000-2786; ICOM matching power supply serial number E7802674; Yaesu FT-101, serial number 7K291710, plus matching accessories. Equipment packed in two bags and checked in at Braniff International, Inc., at Miami International Airport on January 6, 1979. It is believed that the equipment never reached the airplane, and probably will be sold locally. Any information, please advise Miami Police Department and/or Thomas Roesler, PY2DFR, Caixa Postal 6742, 01.000 Sao Paulo, SP, Brasil; telephone 288-7232.

DAMES COMMUNICATION SYSTEMS

Ham Gear

Collins 51J4, general coverage receiver	\$595
Collins 516 F2 power supply, new, in box	\$275
Collins KWM2A transceiver, exc. rnd.	\$1375
Collins 75A4 ham receiver, vy good	\$425
Collins 312B4, Sta Cntl, rd, exc	\$250
Collins 312B5, Vfo Console, exc	\$550
Collins 75S3C, rnd, exc	\$1250
Collins 180S1, antenna tuner	\$295
Collins 30L1, vy gd	\$595
Collins 516F2, power supply	\$175
Collins R-390A rcvrs, overhauled exc cond	call for quote
Collins 51S1, 2-30 MHz rcvr	Special
Hammarlund SP-600JX, rcvr	\$395
Collins CP-1 Crystal Pack	\$195
Racal 6217E, 5-30 MHz receiver	\$1350
Collins 32S3 ham transmitter, vy gd	\$650
Harrison 0-20 volt/1.5 amp lab pw supplies, ea.	\$45
Johnson 2kw Matchbox w/swr meter	\$195

Test Gear

HP-302A wave analyzer	\$375
Boonton Radio 225A sig. gen., 10-500 MHz	\$495
HP-200CD wide-range oscilloscope	\$150
Measurements Model 80, 2-400 MHz	\$295
Measurements Model 65B signal generator	\$295
HP-202H 54-216 MHz AM/FM sig gen	\$695
HP-608D 10-420 MHz sig gen	\$550
Tek 564 storage scope, w/plug ins	\$695
Tek 545 30-MHz scope	\$395
Tek 531A scope, exc	\$350
Tek 851 digital tester new, w/access	call for quote

We stock Amateur and Professional equipment from manufacturers such as Collins, Hewlett-Packard, etc.

All equipment sold checked and realigned
 Write for free catalog.

201-998-4256
 10 SCHUYLER AVENUE
 NORTH ARLINGTON, N. J. 07032

MOVING?

KEEP HAM RADIO COMING ...

If possible let us know four to six weeks before you move and we will make sure your HAM RADIO Magazine arrives on schedule. Just remove the mailing label from this magazine and affix below. Then complete your new address (or any other corrections) in the space provided and we'll take care of the rest.

ham
radio
 Magazine

Allow 4-6 weeks for correction.

Greenville, NH 03048

Thanks for helping us to serve you better.

Here's my new address:

Call _____
 Name _____
 Address _____
 City _____ State _____ Zip _____

AFFIX
 LABEL
 HERE

Duns #01-048-6066

Cash plus shipping paid for clean late model Motorola GE, RCA mobiles. Base Stations, Accessories. We also sell used and reconditioned equipment. For further information contact:

Jesse La Fleur
The Communications Center
1629 Wyoming
El Paso, Texas 79902
(915) 545-1133

Call for cash quotation 16 years of fair dealing

DX OPERATORS
CUSTOM CALCULATED, PERSONALIZED BEAM HEADING AND DISTANCE CHART TO OVER 330 FOREIGN CALL AREAS AND COUNTRIES BASED ON YOUR EXACT QTH. UP TO DATE FOR 1979. SEND CALL SIGN AND \$5.95 TO WILLCOMP, INC., P.O. BOX 86, SOUTH SALEM, N. Y. 10590. N. Y. RESIDENTS ADD 5% SALES TAX.

UNPOTTED TOROIDS — Center tapped.
88 MHY - 5 oz. 5/\$2.95; 9 oz. - 5/\$3.49
44 MHY - 5/\$3.95 ALL PPD.

m. weinschenker
electronic specialties-BOX 353, IRWIN, PA 15642

D & V RADIO PARTS
VARIABLE & TRIMMER CAPACITORS-RF CHOKES-
AIR WOUND COILS-TOROIDS-FEED THRU'S-
TUBULAR TRIMMERS-KNOBS-WIRE-COUPPLINGS-
TRANSMATCH COMPONENTS.
No minimum order-low cost shipping.
First class stamp for complete flyer.
12804 W. SARLE, FREELAND, MICHIGAN 48623

BROADCAST EQUIPMENT DESIGN ENGINEERS

Join our engineering team doing creative work in the areas of: small signal RF, video, audio console, audio processing, cartridge tape equipment, filter synthesis, digital, and microprocessor design.

We are a small well established company with products distributed world wide. We have openings for experienced or entry level engineers with a BSEE and/or MSEE degree or equivalent experience. We are also looking for technicians and engineering assistants with an associate degree or equivalent training to work in the areas mentioned above.

"Hands on" experience with broadcast studio or transmitting equipment and amateur radio experience are helpful for any of these positions.

Broadcast Electronics, Inc. is a subsidiary of Filmways, Inc. and offers excellent career opportunities within a small progressive company. We offer a friendly, individual oriented working environment with excellent facilities, competitive salaries, and comprehensive benefits.

Please direct your inquiry to:
A. H. BOTT, Vice President of Engineering - K9HB, or

G. N. MENDENHALL, Manager of Small Signal RF Engineering - W9NEZ



a FILMWAYS company

BROADCAST ELECTRONICS INC.

4100 NORTH 24th STREET • P.O. BOX 3606
QUINCY, IL 62301 • PHONE (217) 224-9600


(Equal Opportunity Employer)

STEP UP TO TELREX

Professionally Engineered Antenna Systems

Single transmission line "TRI-BAND" ARRAY

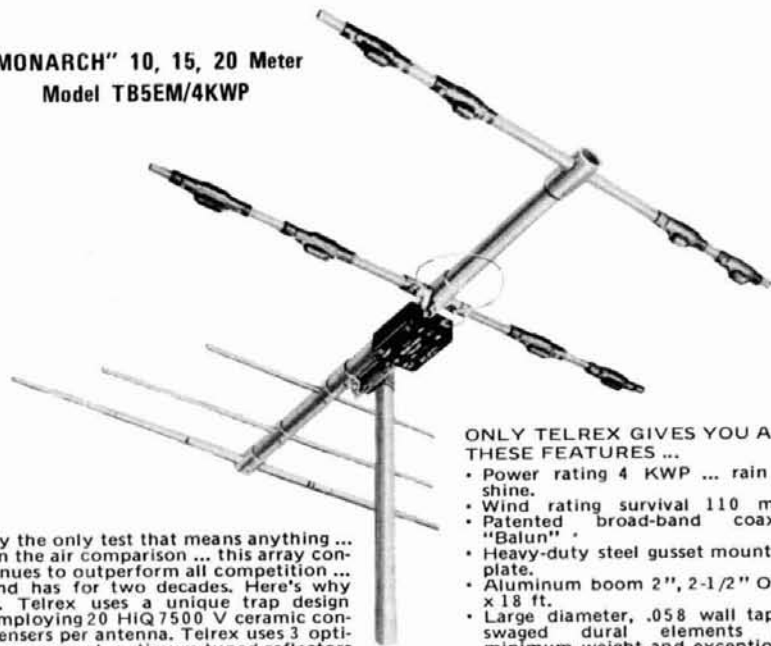"MONARCH" 10, 15, 20 Meter
Model TB5EM/4KWP




ONLY TELREX GIVES YOU ALL THESE FEATURES ...

- Power rating 4 KWP ... rain or shine.
- Wind rating survival 110 mph
- Patented broad-band coaxial "Balun"
- Heavy-duty steel gusset mounting plate.
- Aluminum boom 2", 2-1/2" O.D. x 18 ft.
- Large diameter, .058 wall tapered swaged dural elements for minimum weight and exceptional strength to weight ratio.
- Stainless steel electrical hardware.

By the only test that means anything ... on the air comparison ... this array continues to outperform all competition ... and has for two decades. Here's why ... Telrex uses a unique trap design employing 20 HIQ 7500 V ceramic condensers per antenna. Telrex uses 3 optimum-spaced, optimum-tuned reflectors to provide maximum gain and true F/B Tri-Band performance.

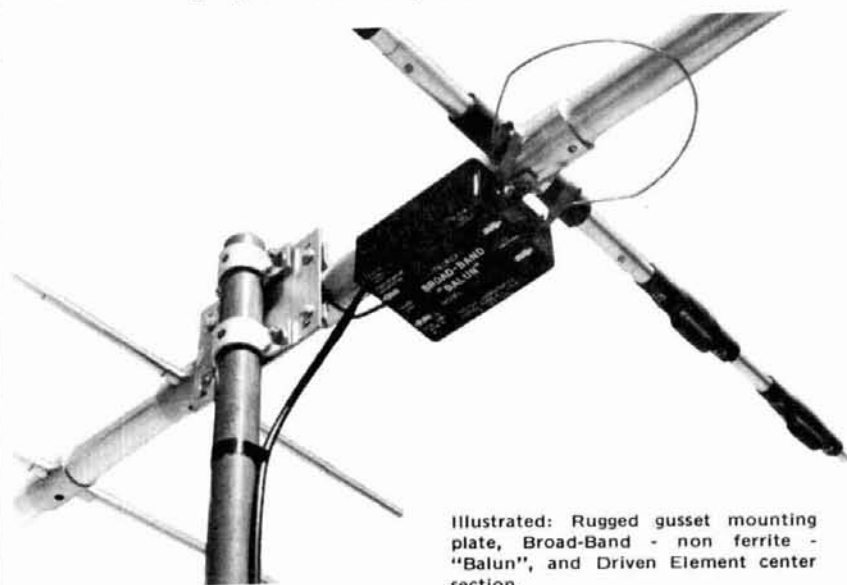At 50 ft. or more (above ground) a rugged Telrex "Tri-Band" is the only answer to longevity ... a true money saver.



Illustrated: Rugged gusset mounting plate, Broad-Band - non ferrite - "Balun", and Driven Element center section.

For technical data and prices on complete Telrex line, write for Catalog PL-7.

TV and Communications Antennas Since 1921

telrex LABORATORIES

P.O. Box 879 - Asbury Park, New Jersey 07712

Phone 201-775-7252



Ham Radio's guide to help you find your local

Alaska

RELIABLE ELECTRONICS

3306 COPE STREET
ANCHORAGE, AK 99503
907-279-5100
Kenwood, Yaesu, DenTron, Wilson,
Atlas, ICOM, Rohn, Tri-Ex.

Arizona

HAM SHACK

4506-A NORTH 16TH STREET
PHOENIX, AZ 85016
602-279-HAMS
Serving all amateurs from beginner
to expert. Classes, sales & service.

KRYDER ELECTRONICS

5520 NORTH 7TH AVENUE
NORTH 7TH AVE. SHOPPING CTR.
PHOENIX, AZ 85013
602-249-3739
Your Complete Amateur Radio Store.

POWER COMMUNICATIONS

6012 NORTH 27th AVE.
PHOENIX, AZ 85017
602-242-6030
Arizona's #1 Ham Store.
Kenwood, Drake, ICOM & more.

California

C & A ELECTRONIC ENTERPRISES

22010 S. WILMINGTON AVE.
SUITE 105
P. O. BOX 5232
CARSON, CA 90745
800-421-2258
213-834-5868 - Calif. Res.
Not The Biggest, But The Best —
Since 1962.

HAM RADIO OUTLET

999 HOWARD AVENUE
BURLINGAME, CA 94010
415-342-5757
Visit our stores in Van Nuys
and Anaheim.

JUN'S ELECTRONICS

11656 W. PICO BLVD.
LOS ANGELES, CA 90064
213-477-1824 Trades
714-282-8682 San Diego
The Home of the One Year
Warranty — Full Service.

QUEMENT ELECTRONICS

1000 SO. BASCOM AVENUE
SAN JOSE, CA 95128
408-998-5900
Serving the world's Radio Amateurs
since 1933.

SHAVER RADIO

3550 LOCHINVAR AVE.
SANTA CLARA, CA 95051
408-247-4220
Atlas, Kenwood, Yaesu, KDK,
Icom, Tempo, Wilson, Ten-Tec.

Connecticut

THOMAS COMMUNICATIONS

95 KITTS LANE
NEWINGTON, CT 06111
800-243-7765
203-667-0811
Call us toll free - See our full
page ad in this issue.

Delaware

DELAWARE AMATEUR SUPPLY

71 MEADOW ROAD
NEW CASTLE, DE 19720
302-328-7728
Delaware's largest stock of amateur
radio equipment & accessories.

Florida

AGL ELECTRONICS, INC.

1800-B DREW ST.
CLEARWATER, FL 33515
813-461-HAMS
West Coast's only full service
Amateur Radio Store.

AMATEUR RADIO CENTER, INC.

2805 N.E. 2ND AVENUE
MIAMI, FL 33137
305-573-8383
The place for great dependable
names in Ham Radio.

MARC'S

CENTRAL EQUIPMENT CO., INC.
18451 W. DIXIE HIGHWAY
NORTH MIAMI BEACH, FL 33160
305-932-1818
See Marc, WD4AAS, for complete
Amateur Sales & Service.

RAY'S AMATEUR RADIO

1590 US HIGHWAY 19 SO.
CLEARWATER, FL 33516
813-535-1416
West coast's only dealer:
Drake, Icom, Cushcraft, Hustler.

Illinois

AUREUS ELECTRONICS, INC.

1415 N. EAGLE STREET
NAPERVILLE, IL 60540
312-420-8629
"Amateur Excellence"

ERICKSON COMMUNICATIONS, INC.

5456 N. MILWAUKEE AVE.
CHICAGO, IL 60630
Chicago - 312-631-5181
Illinois - 800-972-5841
Outside Illinois - 800-621-5802
Hours: 9:30-5:30 Mon, Tu, Wed &
Fri.; 9:30-9:00 Thurs; 9:00-3:00 Sat.

SPECTRONICS, INC.

1009 GARFIELD STREET
OAK PARK, IL 60304
312-848-6777
One of America's Largest
Amateur & SWL Stores.

Indiana

KRYDER ELECTRONICS

GEORGETOWN NORTH
SHOPPING CENTER
2810 MAPLECREST RD.
FORT WAYNE, IN 46815
219-484-4946
Your Complete Amateur Radio Store.
10-9 T, TH, F; 10-5 W, SAT.

Kansas

REVCOM ELECTRONICS

6247 N. HYDRAULIC
WICHITA, KS 67219
316-744-1083
New - Used HF, VHF, & Microwave
Gear. Manufacturing & Sales.

Massachusetts

TEL-COM, INC.

675 GREAT RD. RT. 119
LITTLETON, MA 01460
617-486-3040
The Ham Store of New England
you can rely on.

Dealers: *YOU SHOULD BE HERE TOO!*
Contact Ham Radio now for complete details.

Amateur Radio Dealer

TUFTS RADIO ELECTRONICS
209 MYSTIC AVENUE
MEDFORD, MA 02155
617-395-8280
New England's friendliest
ham store.

Michigan

ELECTRONIC DISTRIBUTORS
1960 PECK STREET
MUSKEGON, MI 49441
616-726-3196
Dealer for all major amateur
radio product lines.

Minnesota

PAL ELECTRONICS INC.
3452 FREMONT AVE. NO.
MINNEAPOLIS, MN 55412
612-521-4662
Midwest's Fastest Growing Ham
Store, Where Service Counts.

Missouri

HAM RADIO CENTER, INC.
8340-42 OLIVE BLVD.
ST. LOUIS, MO 63132
800-325-3636
For Best Price and Fast Delivery
Call toll free 1-800-325-3636

Nebraska

COMMUNICATIONS CENTER, INC.
443 NORTH 48 ST.
LINCOLN, NE 68504
800-228-4097
Kenwood, Yaesu, Drake and more
at discount prices.

Nevada

COMMUNICATIONS CENTER WEST
1072 RANCHO DRIVE
LAS VEGAS, NV 89106
800-634-6227
Kenwood, Yaesu, Drake and more
at discount prices.

New Hampshire

EVANS RADIO, INC.
BOX 893, RT. 3A BOW JUNCTION
CONCORD, NH 03301
603-224-9961
Icom, DenTron & Yaesu dealer.
We service what we sell.

New Jersey

ATKINSON & SMITH, INC.
17 LEWIS ST.
EATONTOWN, NJ 07724
201-542-2447
Ham supplies since "55".

METUCHEN RADIO
216 MAIN STREET
METUCHEN, NJ 08840
201-494-8350
New and Used Ham Equipment
WA2AET "T" Bruno

RADIOS UNLIMITED
1760 EASTON AVENUE
SOMERSET, NJ 08873
201-469-4599
New Jersey's Fastest Growing
Amateur Radio Center.

THE BARGAIN BROTHERS
216 SCOTCH ROAD
GLEN ROC SHOPPING CTR.
WEST TRENTON, NJ 06828
609-883-2050
A million parts - lowest prices
anywhere. Call us!

New York

AM-COM ELECTRONICS INC.
RT. 5
NORTH UTICA SHOPPING CTR.
UTICA, NY 13502
315-732-3656
The Mohawk Valley's Newest &
Largest Electronics Supermarket.

GRAND CENTRAL RADIO
124 EAST 44 STREET
NEW YORK, NY 10017
212-682-3869
Drake, Atlas, Ten-Tec, Midland,
Hy-Gain, Mosley in stock

HAM-BONE RADIO
3206 ERIE BLVD. EAST
SYRACUSE, NY 13214
315-446-2266
We deal, we trade, all major brands!

RADIO WORLD
ONEIDA COUNTY AIRPORT
TERMINAL BLDG.
ORISKANY, NY 13424
Toll Free 800-448-7914
NY { 315-337-2622
Res. { 315-337-0203
New & Used Ham Equipment.
See Warren K2IXN or Bob WA2MSH.

Ohio

**AMATEUR RADIO
SALES & SERVICE INC.**
2187 E. LIVINGSTON AVE.
COLUMBUS, OH 43209
614-236-1625
Antennas and Towers for
All Services.

Oklahoma

KRYDER ELECTRONICS
5826 N.W. 50TH
MACARTHUR SQ. SHOPPING CTR.
OKLAHOMA CITY, OK 73122
405-789-1951
Your Complete Amateur Radio Store

RADIO STORE, INC.
2102 SOUTHWEST 59th ST.
(AT 59th & S. PENNSYLVANIA)
OKLAHOMA CITY, OK 73119
405-682-2929
New and used equipment —
parts and supply.

Pennsylvania

ELECTRONIC EXCHANGE
136 N. MAIN STREET
SOUDERTON, PA 18964
215-723-1200
Demonstrations, Sales, Service
New/Used Amateur Radio Equip.

"HAM" BUERGER, INC.
68 N. YORK ROAD
WILLOW GROVE, PA 19090
215-659-5900
Delaware Valley's Fastest Growing
Amateur Radio Store

**HAMTRONICS, DIV. OF
TREVISE ELECTRONICS**
4033 BROWNSVILLE ROAD
TREVISE, PA 19047
215-357-1400
Same Location for 30 Years.
Call Toll Free 800-523-8998.

HAM MART

LaRUE ELECTRONICS
1112 GRANDVIEW STREET
SCRANTON, PENNSYLVANIA 18509
717-343-2124
ICOM, Bird, Cushcraft, CDE,
Ham-Keys, VHF Engineering,
Antenna Specialists.

Tennessee

GERMANTOWN AMATEUR SUPPLY
3203 SUMMER AVE.
MEMPHIS, TN 38112
800-238-6168
No monkey business. Call
Toll Free.

Texas

AGL ELECTRONICS
3068 FOREST LANE, SUITE 309
DALLAS, TX 75234
214-241-6414 (within Texas)
Out-of-State, Call our toll-free
number 800-527-7418.

HARDIN ELECTRONICS
5635 E. ROSEDALE
FT. WORTH, TX 76112
817-461-9761
Your Full Line Authorized
Yaesu Dealer.

TRACY'S ELECTRONIC MODULE
5691 WEST CREEK DRIVE
FORT WORTH, TX 76133
817-292-3371
We Handle and Service
All Major Lines.

SEE
HAM
MART
THIS ISSUE FOR
YOUR LOCAL
DEALER!



Radio World

CENTRAL NEW YORK'S FASTEST GROWING HAM DEALER



Featuring Yaesu, Icom, Drake, Atlas, Ten-Tec, Swan, DenTron, Pace, Palomar, Alda, Midland, Wilson, KDK, MFJ, Microwave Module, Standard, Tempo, Astron, KLM, Hy-Gain, Mosley, Larsen, Cushcraft, Hustler, Mini Products, Universal and Tristao Towers. *We service everything we sell!* Write or call for quote. **You Won't be Disappointed.**
We are just a few minutes off the NYS Thruway (I-90) Exit 32

Warren K2IXN **ONEIDA COUNTY AIRPORT TERMINAL BUILDING** **Bob WA2MSH**
ORISKANY, NEW YORK 13424
Call Toll Free: 1-800-448-7914 New York State Residents Call: 315-337-2622 or 315-337-0203

SST T-4 ULTRA TUNER



ULTRA TUNER DELUXE

The new SST T-4 Ultra Tuner Deluxe matches any antenna---coax fed or random wire on all bands (160-10 meters). Use it with your dipole, vertical, beam, etc. It works with any transceiver.

Tune out the SWR on your antenna for more efficient operation of your rig. One antenna can even be used for all bands. The SWR on mobile whips can be tuned out from inside your car.

An easy-to-read two color meter scale provides convenient indication of SWR for easy tuning. A back panel antenna switch allows you to select between two coax fed antennas, a random wire, or tuner bypass.

The SST T-4 Ultra Tuner Deluxe is compatible with any rig---solid state or tube. It's compact size (9" x 2-1/2" x 5") makes it ideal for mobile, portable, or home operation. Features an attractive bronze finished enclosure and exclusive SST styling.

Compare features, quality, and price---SST antenna tuners are your best value. This is our seventh year of manufacturing compact antenna tuners.

Features:

- Matches any antenna - coax fed or random wire. 1.8-30 MHz.
- 300 watt **output** power capability.
- SWR meter.
- Antenna switch on back panel.
- Efficient tapped inductor.
- 208 pf. 1000v. capacitors for flexible, reliable operation.
- Johnson binding posts. Four SO-239 connectors.
- *Balun* included for balanced lines.
- Made in USA.

only \$69.95

New model T-4A covers 80-10 meters. Limited range on 80 meters (fine for use with any antenna resonant in the 80 meter band).
only \$59.95

Available now at your SST dealer or order direct---information on following page.

WE ACCEPT




ELECTRONICS
P.O. BOX 1 LAWDALE, CALIF
90260 (213) 376-5887

WANTED FOR CASH



490-T Ant. Tuning Unit
(Also known as CU1658
and CU1669)

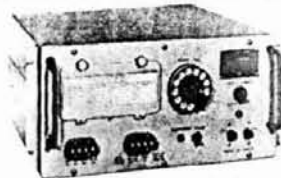
Highest price paid for these units. Parts purchased.
Phone Ted, W2KJW collect. We will trade for new
amateur gear. GRC106, ARC105 and some aircraft
units also required.



RADIO SET CONTROL
C-3866/SRC

We stand on our long term offer to pay 5% more
than any other bonafide offer.

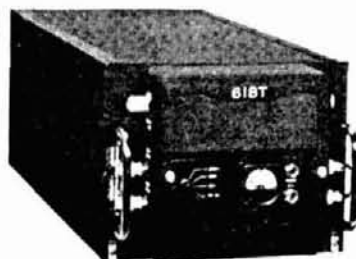See last month's ad for other items available.



618-T Transceiver
(Also known as MRC95,
ARC94, ARC102, or VC102)

DCO, INC.

10 Schuyler Avenue
(201) 998-4246

No. Arlington, N.J. 07032
Evenings (201) 998-6475

SST HA-2

2 METER SSB MOBILE ANTENNA

The SST HA-2 is a full half wave, horizontally polarized omnidirectional 2 meter antenna. With the horizontal polarization standard, the HA-2 is a must for 2 meter SSB mobile. With the vertical/horizontal adapter option, use it with your FM rig too!

Although the SST HA-2 was designed for mobile operation it will work well as a fixed or portable antenna—its small size provides the traveling ham with an antenna that can easily be packed in a briefcase.

Features:

- Mobile, portable, or fixed operation.
- Horizontal or vertical polarization with operational adapter.
- Greater than 3.5 MHz bandwidth.
- Less than 1.5:1 VSWR.
- High performance—additional data available on request.
- Solid construction—built to last.




HORIZONTALLY POLARIZED ANTENNA

Impedance matching is accomplished by means of a pre-adjusted gamma match and a variable capacitor. The HA-2 comes complete with RG-58, which is neatly fed through the center of the mast section, PL-259 coax connector, and 3/8" 24 stud mount. The HA-2 fits standard mounts. Our recommended ram gutter mount is available as an option. Also optional is a vertical/horizontal adapter, which allows changeover to be made in minutes with a screw driver.

only \$39.95

GM-1 gutter mount \$5.95 VH-1 vertical/horizontal adapter \$5.95

SST T-1 RANDOM WIRE ANTENNA TUNER

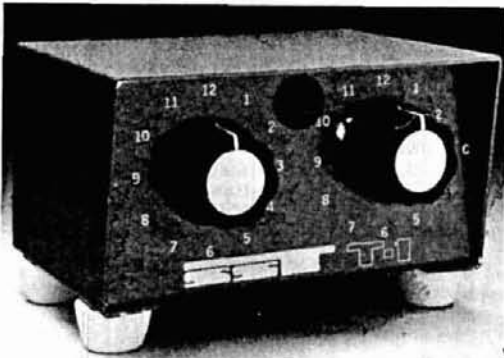

All band operation (160-10 meters) with any random length of wire. 200 watt output power capability—will work with virtually any transceiver. Ideal for portable or home operation. Great for apartments and hotel rooms—simply run a wire inside, out a window, or anyplace available. Efficient toroid inductor for small size: 4-3/4" x 2-3/8" x 3", and negligible loss. Built-in neon tune-up indicator. SO-239 connector. Attractive bronze finished enclosure.

only \$29.95

The Original Random Wire Antenna Tuner
in use by amateurs for 7 years.

SST T-2 ULTRA TUNER

Tunes out SWR on any coax fed antenna as well as random wires. Works great on all bands (80-10 meters) with any transceiver running up to 200 watts power output. Includes balun for balanced lines.

Increases usable bandwidth of any antenna. Tunes out SWR on mobile whips from inside your car.

Uses efficient tapped inductor and specially made capacitors for small size: 5-1/4" x 2-1/4" x 2-1/2". Rugged, yet compact. Negligible line loss. Attractive bronze finished enclosure. SO-239 coax connectors are used for transmitter input and coax fed antennas. Convenient binding posts are provided for random wire and ground connections.



only \$39.95

SST T-3 Mobile Impedance Transformer



Matches 52 ohm coax to the lower impedance of a mobile whip or vertical. 12-position switch with taps between 3 and 50 ohms. 2-30 MHz. 300 watt output. 2-1/4" x 2" x 2-1/4".

\$19.95

SST DL-1 K4RLJ DUMMY LOAD

The DL-1 is a unique chemical dummy load. Unlike messy oil-filled dummy loads, it will not leak. Sealed, ready to use. Max. 1000 watts PEP for 15 sec. SWR less than 1.5:1 1.225 MHz. Portable—only 3-1/4" x 4-1/2".

only \$17.95

TO ORDER:

Send a check or money order—or use your Master Charge or VISA card. COD and credit card orders are also accepted by phone. Simply give us your card number and expiration date. Our phone order desk is open at most hours for your convenience and so that you can take advantage of the very low before/after hour phone rates.

GUARANTEE:

All SST products are unconditionally guaranteed for 1 year. In addition, they may be returned within 10 days for a full refund (less shipping) if you are not satisfied for any reason.

Call (213) 376-5887 or 379-9572 to order
C.O.D., VISA or Master Charge

or send to: SST Electronics,
P.O. Box 1, Lawndale, Calif. 90260

Please add \$3 for shipping and handling (\$6 Air-mail Worldwide). California residents, please add sales tax. \$1 charge for COD.

Name _____
Street _____
City _____ State _____ Zip _____
Models Desired: Total Enclosed _____
\$ _____
or charge to: VISA M.C. C.O.D.
Card # _____ Exp. Date _____

SST ELECTRONICS
P.O. BOX 1 LAWDALE, CALIF.
90260 (213) 376-5887

MARCH TOP



NEW!

Brand New 4th Edition CONFIDENTIAL FREQUENCY LIST

Here's a necessary companion to any general coverage receiver. This completely new edition of the very popular CFL is the most recent listing of station frequencies, call signs, locations, emission modes and power for just about any non-ham signal you can pick up from 4 to 26 MHz. Stations are listed by frequency for easy identification and location. From foreign military to weather broadcasts, the CFL is 96 pages of the most up-to-date short-wave listening information available. 96 pages.

©1979.

GL-CF

Softbound \$6.95

Available March 1979

NEW!

HAM RADIO MAGAZINE FILES

Your collection of HAM RADIO Magazines is a valuable resource. Here's a brand new, inexpensive way to store them. These sturdy cardboard magazine files keep them clean, neat and up front where you can use them for quick and easy reference.

HR-HRMF

\$1.95 each, 3/\$4.95

**IN A HURRY?
ORDER
TOLL FREE
1-800-258-5353**

VISA



or use handy
order card

**MARCH
FEATURE**



OPERATOR'S PACKAGE

Here is a collection of books which no ham should be without. Whether you're a beginner or old-timer, DXer or Ragchewer, you'll find much valuable information in this package. Included is:

1) **The 1979 U. S. Callbook** with the listings of 374,487 U.S. Hams, including 41,245 new listings and over 100,000 listing changes. To keep up with all the new hams and new calls, you need the latest edition of the Callbook. 2) **The ARRL Operating Guide**. Separate chapters cover basic operating skills needed for handling emergency and message traffic, using repeaters, DXing, contesting, QRPing, and other subjects. 3) **Band Aids** compiled by James Dersh, W0BAJE, a collection of 60 different operating aids, charts, and tables including the National Traffic System listing, a decibel ratio chart, Ohm's Law table of formulas, WWV and W1AW operating schedules, and much more, all in one handy spiral book. 4) **Two Ham Radio Log Books** — each has space for over 2,000 entries, or a total of over 4,000 QSOs! You also get Q signals, international prefixes, and the amateur frequency spectrum chart — all spiralbound for easy use.

The Operator's Package — an incredible amount of information for \$27.95.

HR-OPER

**SPECIAL
JUST \$27.95**

U.S. Callbook	\$15.95
ARRL OP Guide	4.00
Band Aids	7.95
2 HR Logs	3.50

**\$31.40
Value**

Already BEST SELLERS from the ARRL

FM and REPEATERS FOR THE RADIO AMATEUR by the ARRL Staff

This is a completely new and updated version of the mobile operator's favorite. This new edition features the latest in FM technology and design theory, highlighted by microprocessor control circuitry and a phase-lock loop 2-meter transceiver. More on FM — receivers, transmitters, antennas and repeater operation. If you are into FM, get this book today! 176 pages. ©1978.

AR-FM


Softbound \$5.00

THE ARRL ANTENNA ANTHOLOGY by the ARRL Staff

This brand new book pulls together a wide selection of antenna articles from QST. Written for Amateurs of all levels and interests. Included are phased arrays, verticals, Yagi's . . . even the VHF Quagi! Detailed instructions and full illustrations make this a really useful book for any antenna buff. 152 pages. ©1979.

AR-AA

Softbound \$4.00

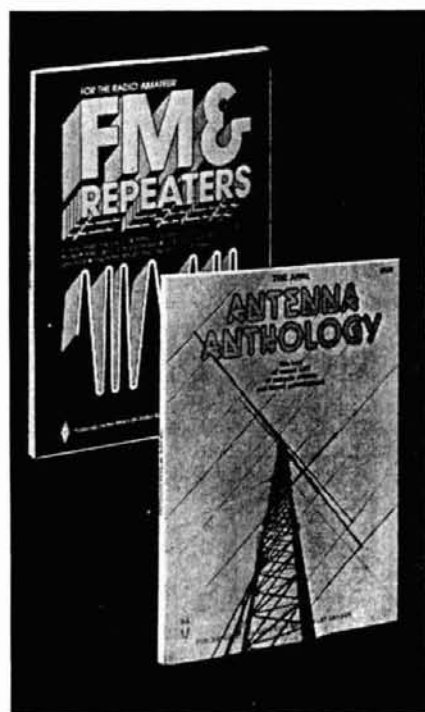

SELECTIONS

Member
AMERICAN BOOKSELLERS ASSOCIATION

Spring has **SPRUNG!!!**

Tune Up for Antennas

ery Popular!

THE RADIO AMATEUR ANTENNA HANDBOOK

by William I. Orr, W6SAI and Stuart D. Cowan, W2LX

RP-AH One of Amateur Radio's most notable authors Bill Orr, W6SAI has combined with W2LX to provide you with a clearly written, understandable book on antennas. All types of beam, quad, horizontal and sloping wire antenna information is included in this useful volume. Location decisions, height, ground loss, towers, rotors, SWR meter reading — it's all here in one great book. 148 illustrations, charts and diagrams. An antenna book you have just got to read! 190 pages. ©1978.

Softbound \$6.95

HOME-BREW HF/VHF ANTENNA HANDBOOK

by William Hood, W2FEZ

T-963 A do-it-yourself antenna book primarily designed for someone with a working knowledge of antennas, although the first chapter offers excellent basic reference information. Transmission lines, couplers, filters, mobile antennas, compact antennas, directive antennas and many more. A practical, usable book sure to get lots of use. 210 pages. ©1977.

Softbound \$5.95

THE ANTENNA CONSTRUCTION HANDBOOK FOR HAM, CB & SWL

by Rufus P. Turner

T-1054 One of the most complete antenna-building books available. There's design data, diagrams and how-to-build-it instructions to customize and install your own antenna. Elementary theory, tests and measurements and construction notes plus over 50 antenna ideas! 237 pages. ©1973.

Softbound \$5.95

SIMPLE, LOW-COST WIRE ANTENNAS

by William I. Orr, W6SAI

RP-WA This 192-page book describes over 40 horizontal, vertical, and multiband trap antennas. Invisible antennas for apartment houses, high-gain beam antennas, novice antennas, tuners and ground systems. It's all here in this exciting, revised edition by the "antenna expert". 192 pages. ©1972.

Softbound \$4.95

ALL ABOUT CUBICAL QUAD ANTENNAS

by William I. Orr, W6SAI

RP-CQ Long considered "THE BOOK" on Quads, this edition has more information on these antennas than you will find anywhere else. Everything you need to design, build and adjust your Quad for top performance. 112 pages. ©1977.

Softbound \$4.75


BEAM ANTENNA HANDBOOK

by William I. Orr, W6SAI

RP-BA For many years this book has been the best-seller on beam antennas. It covers all areas of the subject, both theory and practice. Recommended by such famous DXers as W4BPD, W2AB, W4KFC and 5Z4ERR. 198 pages. ©1977.

Softbound \$4.95

All 3 Orr Books Just \$12.95

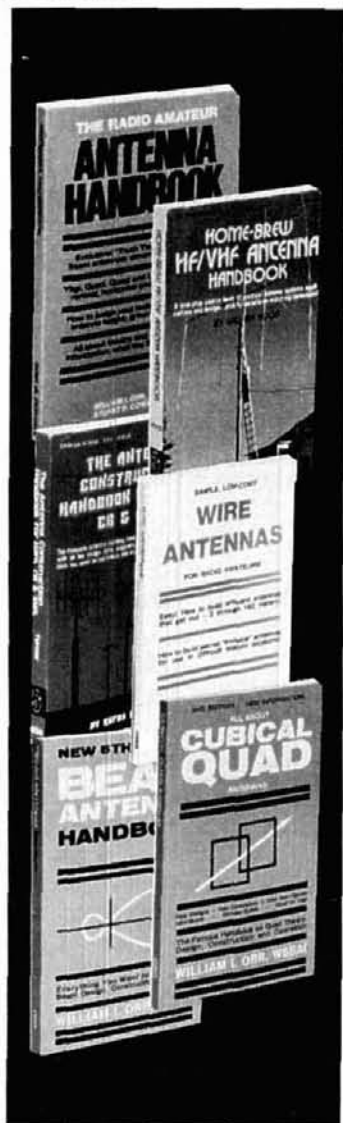

NOVICE INSPIRATION
Great Licensing Aids

SAVE
OVER
10%



TUNE IN THE WORLD WITH HAM RADIO

by ARRL Staff

Learn what Amateur Radio is, how to pass your Novice exam and how to talk to other hams in the U.S. and around the world. **Tune in the World With Ham Radio** gives an exciting overview of ham radio highlighting various facets of this great hobby. In addition, it has everything you need to pass the novice exam — from a plain talk, basic radio electronics manual and study guide to a Morse Code cassette instruction course — here in one package. Tens of thousands of hams have started with this package.

AR-HR Complete package \$7.00
Includes booklet, study guide, and cassette tape.

COMMUNICATE WITH THE WORLD THROUGH HAM RADIO

from Ameco

Here's a complete, simple novice license course not requiring any technical background. One of the very best available. If you know enough about ham radio to want to get started immediately, then this package is for you. It contains Ameco's popular Novice Theory Course as well as a Morse Code training package featuring a cassette tape and 32 page instruction booklet. Radio theory, Morse Code training, FCC type practice code and theory exams. It's all here in this complete and economical package. A great way to get your ticket to worldwide communication.

NP-1 Complete package \$6.95



Amateur Radio's highly popular Logbook.

Order yours and see why!

LOG BOOK

from The Ham Radio Publishing Group

Ham Radio's new Log Book is a tool you just can't do without. With room for over twice as many entries as other popular log books, this log covers more than 2,000 contacts. There's sharp ruling too for all FCC-required information — plus extra space for the name and address of each station you contact. For contesters, there is a consistent 30 entries per page for easy scoring. In addition there is a handy frequency spectrum chart showing the exact privileges for each Amateur license band, privileges from novice to extra, plus a listing of all worldwide Amateur prefixes currently in use. And, it's all spiralbound to lie flat on your operating table. This is unquestionably the best log book value anywhere. 8 1/2" x 11" 80 pages. ©1978.

HR-LB2 Spiralbound \$1.75



FREE!

HAM RADIO'S BOOKSTORE CATALOG

Amateur Radio's most complete source for license study guides, code practice tapes and operating aids from every major electronics publisher. Send postcard with your name and address or check off box on order card.

Advertisers check-off

... for literature, in a hurry — we'll rush your name to the companies whose names you "check-off"

Place your check mark in the space between name and number. Ex: Ham Radio 234

INDEX

AED _____ 710	Icom _____ 065
Aluma _____ 589	Info-Tech _____ 351
Amateur Und CB Funk * _____	Integ. Circuits _____ 518
Am. Wholesale Elec. _____ 003	Int. Crystal _____ 066
Amidon _____ 005	Jameco _____ 333
Antenna Mart _____ 009	Jan _____ 067
Antenna Spec. _____ 010	Johnston * _____
Astac _____ 484	Jones _____ 626
Astron _____ 734	Kantronics * _____
Atlantic Surplus _____ 644	Kerwood _____ 576
Atlas _____ 198	L Tronics _____ 576
Atronic _____ 382	Long's _____ 468
B&K Precision _____ 516	Lyle _____ 373
Barry _____	MFJ _____ 082
Broadcast Elec. * _____	M&M RF Distr. _____ 577
Budwig _____ 233	Madison * _____
Bullet _____ 328	May * _____
Cal Crystal _____ 709	Microwave Filter _____ 637
Clegg _____ 027	J. W. Miller _____ 745
CoaxProbe _____ 726	Milo _____ 736
Communications Center _____ 534	Mirage _____ 760
Comm. Research _____ 753	NDI _____ 761
Comm. Spec. _____ 330	Oak Hill Acad. A.R.S. * _____
Cont. Spec. _____ 348	Paloamar Eng. * _____
Creative Elec. _____ 751	Pipo _____ 481
Crystal Banking _____ 573	RF Power Labs _____ 602
Curtis Electro _____ 034	RIW * _____
Cushcraft * _____	Callbook _____ 100
D&V Radio * _____	Radio Sys. Tech. _____ 422
DCO _____ 324	Radio World * _____
DSI _____ 656	Ramsey _____ 442
DX Eng _____ 222	S-F A. R. S. _____ 640
Dames Comm. _____ 551	SST _____ 375
Data Signal _____ 270	Schober Organ _____ 762
Davis Elec. _____ 332	Sherwood _____ 435
Dayton Hamvention * _____	Siliconix _____ 582
Drake * _____ 759	Slep _____ 232
E.T.O. _____	Space _____ 107
Electrocom _____ 663	Spec. Comm. _____ 366
Elec. Research Virginia * _____	Spec. Int. _____ 108
Erickson * _____	Swan _____ 111
Fair Radio _____ 048	TPL _____ 240
G & C Comm. _____ 754	Telco _____ 708
GLB _____ 552	Telrex _____ 377
GL Enterprises * _____	Ten-Tec * _____
Gilfer _____ 207	Texas RF Distr. _____ 763
Gray _____ 055	The Communication Center * _____
Gregory * _____	Thomas Comm. _____ 730
Group III _____ 701	Tri-Ex _____ 116
Gull _____ 635	VHF Eng. _____ 121
Hal _____	Van Gorden Eng. _____ 737
Hal-Tronix _____ 254	Vanguard Labs _____ 716
H. R. B. _____ 150	Varian _____ 043
Hamtronics, NY _____ 246	Webster _____
Harrison _____ 575	Assoc. _____ 423
Heights * _____	Weinschenker _____ 122
Henry _____ 062	Western * _____
Hildreth _____ 283	Willcomp _____ 764
Hy-Gain _____ 064	Yaesu _____ 127

*Please contact this advertiser directly.
Limit 15 inquiries per request.

March, 1979

Please use before April 30, 1979

Tear off and mail to
HAM RADIO MAGAZINE — "check off"
Greenville, N. H. 03048

NAME _____

CALL _____

STREET _____

CITY _____

STATE _____ ZIP _____

MADISON SUPER BOWL BUYS



% WRITE IN
YOUR
BEST QUOTE
FROM THE
"800 GANG."

NOW, LIST THE EQUIPMENT YOU WANT IN THE SPACES PROVIDED BELOW, CUT OUT THIS AD, AND SEND IT TO US WITH YOUR NAME, ADDRESS AND TELEPHONE NUMBER. WE WILL WRITE OR CALL (CHECK ONE) YOU BACK AS SOON AS POSSIBLE WITH THE **MADISON** QUOTE.

(HINT: DON'T GO BELOW OUR COST).

WE HAVE AN IN-DEPTH STOCK AND LARGE INVENTORY OF MAJOR LINES AND ACCESSORIES.

PLEASE QUOTE ON:

1. _____

2. _____

3. _____

4. _____

NAME _____

ADDRESS _____

TELEPHONE _____

ZIP _____

TERMS: ALL PRICES FOB HOUSTON. PRICES SUBJECT TO CHANGE WITHOUT NOTICE. ALL ITEMS GUARANTEED. SOME ITEMS SUBJECT TO PRIOR SALE. SEND LETTERHEAD FOR AMATEUR DEALER'S PRICE LIST. TEXAS RESIDENTS ADD 6% TAX. PLEASE ADD POSTAGE ESTIMATE.

MADISON ELECTRONICS SUPPLY, INC.

1508-D MCKINNEY HOUSTON, TEXAS 77002
713/658-0268 NITES 713/497-5683

Advertisers index

AED Electronics	90
Aluma Tower Co.	66
Amateur Und CB Funk	90
Amateur Wholesale Electronics	91
Amidon Associates	90
Antenna Mart	80
Antenna Specialists	96
Astron Corporation	96
Atlantic Surplus Sales	102
Atlas Radio	53
Atronic	10
Barry Electronics	86
Broadcast Electronics	111
Budwig Mfg. Co.	100
Bullet	74
Cal Crystal Lab, Inc.	102
Clegg	78
CoaxProbe Co.	100
Communications Center	103
Communications Research, Inc.	86
Communications Specialists	54, 55
Creative Electronics	98
Crystal Banking Service	86
Curtis Electro Devices	80
Cushcraft	99, 101, 108
D & V Radio Parts	111
DCO, Inc.	115
DSI Instruments	25
DX Engineering	44
Dames Communications Systems	110
Data Signal, Inc.	44
Davis Electronics	104
Dayton Hamvention	10
Drake Co., R. L.	11
Ehrhorn Technological Operations	119
Electrocom Industries	74
Electronic Research Corp. of Virginia	94
Erickson Communications	80
Fair Radio Sales	80
G & C Communications	66, 90
GLB	100
GL Enterprises	84
Gilfer Associates	102
Gray Electronics	86
Gregory Electronics	104
Group III Sales Company	106
Gull Electronics	105
Hal Communications Corp.	7
Hal Tronix	1
Ham Radio's Bookstore	96, 116, 117
Ham Radio Magazine	110
Hamtronics, Inc., Rochester, NY	49
Heights Mfg. Co.	105
Henry Radio Stores	Cover II
Hildreth Engineering	80
Hy-Gain Electronics	93
Icom	5
Info-Tech	71
Integrated Circuits Unlimited	107
International Crystal	67
Jameco Electronics	87
Jan Crystals	44
Johnston	102
Jones, Marlin P. & Assoc.	110
Kantronics	45
Kerwood Communications Inc.	7, 60, 61
L Tronics	102
Long's Electronics	120
Lyle Products	74
MFJ Enterprises	2
M&M RF Distributors	66
Madison Electronic Supply	84, 106, 109, 118
May, L. D. & Co.	100
Microwave Filter, Inc.	86
Milo Associates	106
Oak Hill Academy Amateur Radio Session	108
Palomar Engineers	95
Pipo Communications	66
RIW Products	44
Radio Amateur Callbook	90
Radio Systems Technology, Inc.	74
Radio World	114
Ramsey Electronics	69
S-F Amateur Radio Service	39
SST Electronics	114, 115
Schober Organ Corp.	98
Sherwood Engineering	102
Slep Electronics	108
Space Electronics	100
Spectrum Communications	97
Spectrum International	104
Swan Electronics	31
TPL Communications	10
Telrex Laboratories	111
Ten-Tec	9
Texas RF Distributors	81
The Communication Center	111
Thomas Communications	85
Tri-Ex Tower Corporation	75
VHF Engineering, Div. of Brownian	79
Van Gorden Engineering	80
Vanguard Labs	108
Varian, Eimac Division	Cover IV
Webster Associates	74
Weinschenker	111
Western Electronics	102
Willcomp, Inc.	111
Yaesu Electronics Corp.	Cover III

Maroon Bells Peaks, Colorado — In ETO's "back yard."



ALPHA

Sure you can buy a cheaper linear . . . But is that really what you want?

You can buy a so-called "maximum legal power" linear for quite a bit less than the price of an ALPHA. What makes the ALPHA worth more . . . or the other model less?

TALK TO AN ALPHA OWNER — Notice how scarce used ALPHA's are? Owners are rarely willing to part with them, and will be delighted to tell you why.

CHECK ETO's TWO-YEAR (limited) WARRANTY — Others give you 90 days. But EIGHT TIMES as much protection is only part of the ALPHA warranty story; there's also a clear message about durability.

NO ALPHA 76/374/77D OWNER HAS EVER BURNED UP A POWER TRANSFORMER, despite our No Time Limit (NTL), full power key down rating. Maybe it's because our '76A transformer is nearly TWICE the size

of those in competitive desk-top amplifiers and is cooled by ETO's full-cabinet, ducted-air system to boot.

LOOK INSIDE AN ALPHA — the difference in quality and ruggedness is conspicuous. *Big* coils . . . axial-flow ceramic triodes thoroughly cooled by a centrifugal blower . . . yet ETO's new acoustic-isolation blower system makes the ALPHA 76A series now even quieter than ever before.

EFFICIENCY, versatility, ease of operation, resale value — the story of ALPHA superiority goes on. Before you decide on a new linear, get all the details from your dealer or ETO direct. And ask for our free guide, "Everything You Always Wanted to Know About (Comparing) Linears . . . But Didn't Know Whom to Ask." Finally, do talk to an ALPHA owner . . . look for him on top of the nearest pile-up.



ALPHA/VOMAX can boost the "talk power" of any rig up to ten times or more. The new SBP-4 split band speech processor uses the only system *more effective than r/ clipping* — AND distortion is extremely low so your voice sounds natural. Under tough conditions VOMAX can help as much as most linears. Combine VOMAX with a good linear and WOW! It's simple to install and operate with any rig.


Ehrhorn Technological Operations, Inc.

P. O. Box 708 • Cañon City, Colorado 81212 • (303) 275-1613

ANTENNA VALUES FROM LONG'S




1-800-633-3410

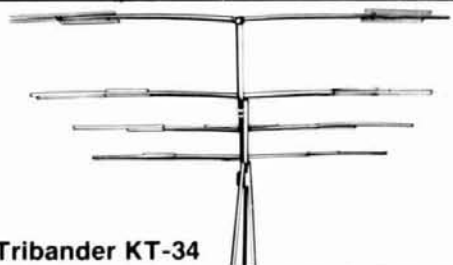

KLM Tribander KT-34

Covers 20m, 15m, 10m, gain: 7dB over a dipole. VSWR: better than 1.5:1, 4 elements on each band, 4 KW PEP, wind area: 6 sq. ft., boom: 16 ft. x 3", turning radius: 15 ft., max. element length: 24 ft., 2" o.d. mast or larger recommended, F/B: 20 dB or better.

349.95 Call for quote.

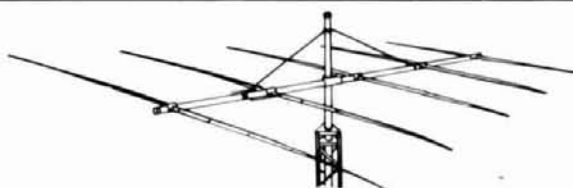

HY-GAIN 5-element monoband 20m beam antenna

5 elements up to 36 1/2" long spaced on a 34' by 2" diameter boom, bandwidth: 400 KHz, average gain: 11.6 boom length: 34 ft., longest element: 36.5 turning radius: 25 ft., wind load: 230, surface area: 9 ft., F/B: 20 dB input impedance: 50 ohms.


289.95 Call for quote.



MOSELEY TA-33 Jr.

Covers 10, 15, 20 meters, 3 element beam features: Gain 10.1 dB (over isotropic source), F/B: 20 dB, 1KW PEP SSB input, VSWR at resonance 1.5/1 or better, longest element: 26 ft. 8 in., wind surface: 4.0 sq. ft.

197.00 Call for quote.

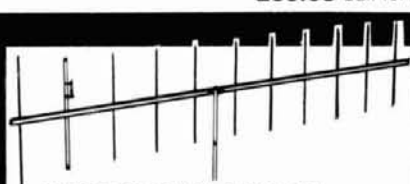

CUSHCRAFT A147-11 2m antenna

The 11-element antenna is rated at 1000 watts with direct 52 ohm feed and PL-259 connectors. Boom length 144 ins. Longest element 40 ins. Gain/F/B ratio dB: 13.2. Freq. 146-148 MHz. Wind area 1.21 sq. ft.

36.95 Call for yours today.



KLM 144-148 13LB 2 meter antenna

Has 13 elements, covers 144-148 MHz, gain: 15.5 dBd VSWR less than 1.2:1, feed impedance: 200 ohm balanced, boom length: 215 ft., center mounting, max mast size: 2 ins., 4:1 balun for 50 ohm coax feed supplied with the antenna.

69.95 Call for yours today



HY-GAIN TH6DX The Ultimate tribander

Gain 8.7 dB • Front-to-back ratio 25 dB • SWR (at resonance) less than 1.5:1 • Number of elements 6 • Frequency 10, 15, and 20 meters • Longest element 31.1' • Boom length 24' • Wind load at 80 m.p.h., 207 lbs. • Surface area 8.09 sq. ft. Balun BN-86 recommended 15.95.


296.95 Call for quote.



CUSHCRAFT ARX-2 2m antenna

Three 1/2 waves in phase and a 1/2 wave matching stub. Extremely low angle of radiation for better signal coverage. Tuneable over a broad freq. range. Matched to 52 ohm coax.

39.95 Call for yours today

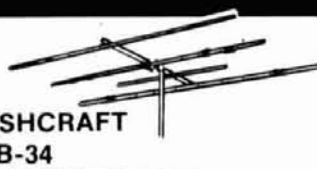

CUSHCRAFT ATB-34 HF 4-element beam

Catch DX instead of chasing DX with the ATB-34! • Covers 10, 15, and 20 meters • High-Q coax traps rated for 2 Kw power • Direct 52 ohm feed thru 1-1 balun • Forward gain: 7.5 dB, all bands • Front-to-back ratio: 30 dB • Turn radius: 18'9" • Wind survival: 90 MPH.

259.95 Call for quote.



Long's Electronics



MAIL ORDERS: P.O. BOX 11347 BIRMINGHAM, AL 35202 • STREET ADDRESS: 2808 7TH AVENUE SOUTH BIRMINGHAM, ALABAMA 35233


Remember, you can Call Toll Free: **1-800-633-3410** in the U.S.A. or call **1-800-292-8668** in Alabama for our low price quote. Store hours: 9:00 AM til 5:30 PM, Monday thru Friday.

ALL NEW

FT-101ZD

HIGH-PERFORMANCE HF TRANSCEIVER

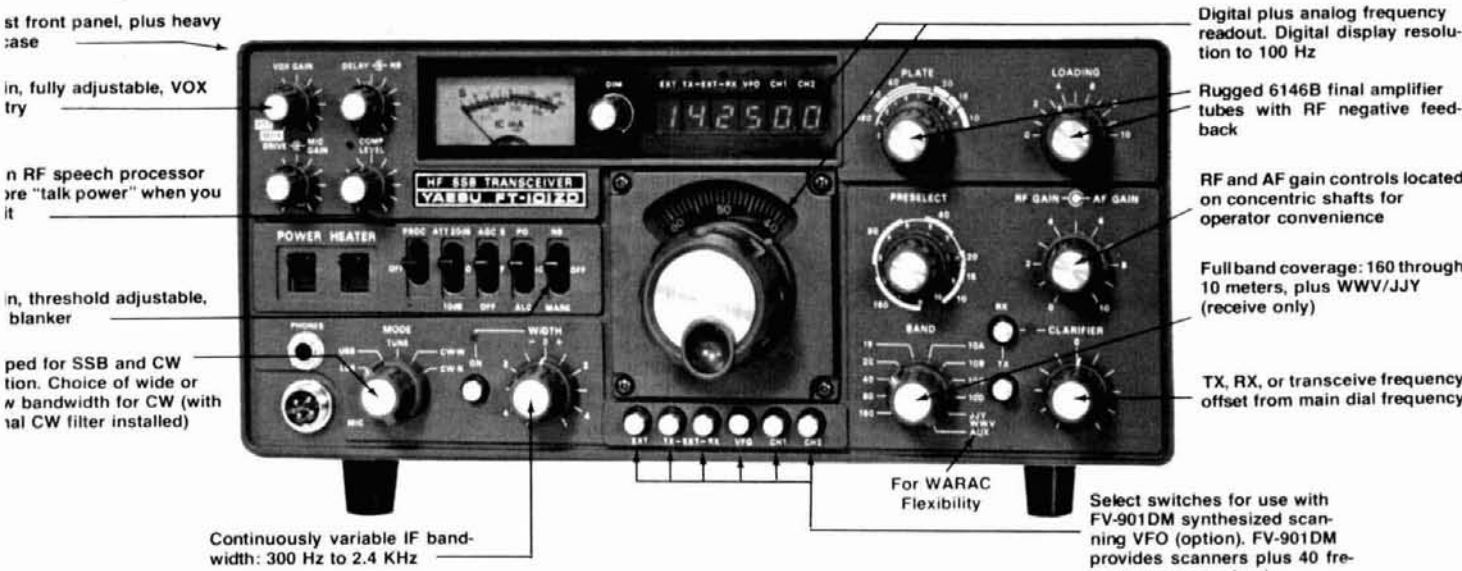Today's technology, backed by a proud tradition, is yours to enjoy in the all-new FT-101ZD transceiver from YAESU. A host of new features are teamed with the FT-101 heritage to bring you a top-dollar value. See your dealer today for a "hands on" demonstration of the performance-packed FT-101ZD.



SPECIFICATIONS

TRANSMITTER

- PA Input Power:** 180 watts DC
- Carrier Suppression:** Better than 40 dB
- Unwanted Sideband Suppression:** Better than 40 dB @ 1000 Hz, 14 MHz
- Spurious Radiation:** Better than 40 dB below rated output
- Third Order Distortion Products:** Better than -31 dB
- Transmitter Frequency Response:** 300-2700 Hz (-6 dB)
- Stability:** Less than 300 Hz in first 30 minutes after 10 min. warmup; less than 100 Hz after 30 minutes over any 30 min. period
- Negative Feedback:** 6 dB @ 14 MHz
- Antenna Output Impedance:** 50-75 ohms, unbalanced

GENERAL

- Frequency Coverage:** Amateur bands from 1.8-29.9 MHz, plus WWV/JJY (receive only)
- Operating Modes:** LSB, USB, CW
- Power Requirements:** 100/110/117/200/220/234 volts AC, 50/60 Hz; 13.5 volts DC (with optional DC-DC converter)
- Power Consumption:** AC 117V: 75 VA receive (65 VA HEATER OFF) 285 VA transmit; DC 13.5V: 5.5 amps receive (1.1 amps HEATER OFF), 21 amps transmit
- Size:** 345 (W) x 157 (H) x 326 (D) mm
- Weight:** Approximately 15 kg.

COMPATIBLE WITH FT-901DM ACCESSORIES

RECEIVER

- Sensitivity:** 0.25 uV for S/N 10 dB
- Selectivity:** 2.4 KHz at 6 dB down, 4.0 KHz at 60 dB down (1.66 shape factor); Continuously variable between 300 and 2400 Hz (-6 dB); CW (with optional CW filter installed): 600 Hz at 6 dB down, 1.2 KHz at 60 dB down (2:1 shape factor)
- Image Rejection:** Better than 60 dB (160-15 meters); Better than 50 dB (10 meters)
- IF Rejection:** Better than 70 dB (160, 80, 20-10 m); Better than 60 dB (40 m)
- Audio Output Impedance:** 4-16 ohms
- Audio Output Power:** 3 watts @10% THD (into 4 ohms)



Price And Specifications Subject To Change Without Notice Or Obligation

YAESU The radio.



379X

YAESU ELECTRONICS CORP., 15954 Downey Ave., Paramount, CA 90723 • (213) 633-4007
YAESU ELECTRONICS Eastern Service Ctr., 9812 Princeton-Glendale Rd., Cincinnati, OH 45246

Two EIMAC 3-500Zs provide the punch in Kenwood's new amplifier.


Kenwood chooses EIMAC for trouble-free service.

The new heavy-duty Kenwood TL-922A linear amplifier provides 2 kW PEP input for SSB service and 1 kW input for CW, RTTY, and SSTV operation.

Kenwood chose two EIMAC 3-500Z high-mu triodes to do the job. With a total of 1000 watts anode dissipation, the two 3-500Zs coast along to provide trouble-free, long-life service.

For more information

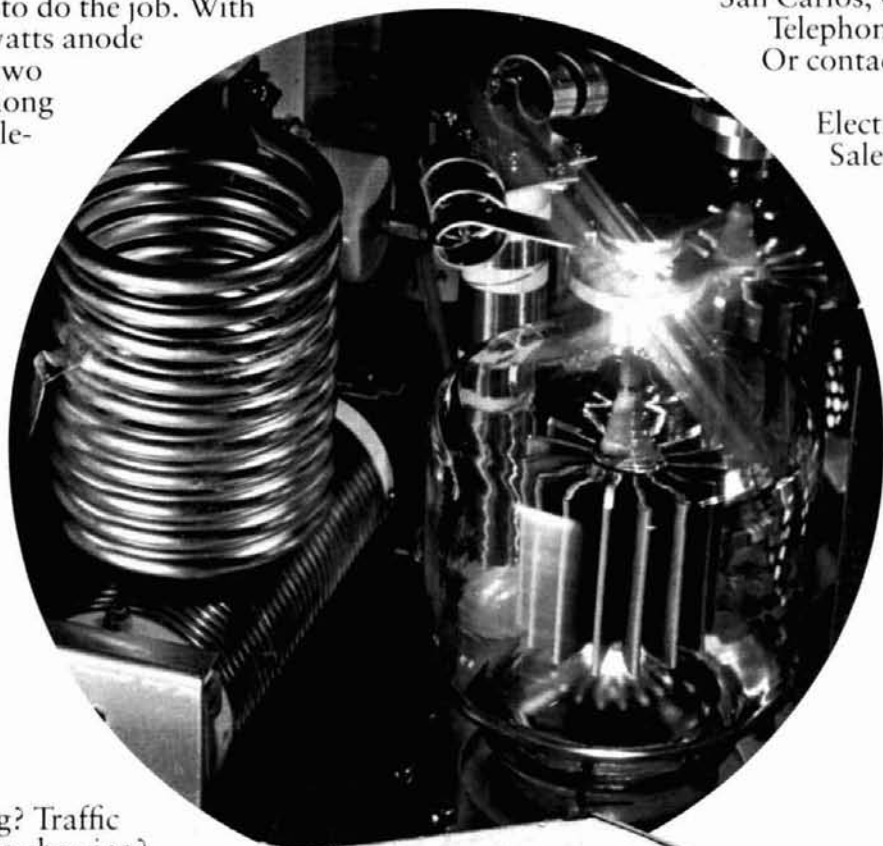Send for the EIMAC Quick Reference catalog covering the complete line of EIMAC products and for the 3-500Z Data Sheet. Learn why the important manufacturers of communication equipment choose EIMAC. Varian, EIMAC Division, 301 Industrial Way, San Carlos, California 94070. Telephone (415) 592-1221. Or contact any of the more than 30 Varian Electron Device Group Sales Offices throughout the world.



What's your pleasure?

DX chasing? Traffic nets? RTTY? Rag chewing? SSTV? The EIMAC 3-500Z provides the power when you need it, with ample safety margin. Value wise amateurs always look for the EIMAC power tube for reliability. And equipment manufacturers, such as Kenwood, choose EIMAC for leadership in power tube technology.



varian