

AN ELECTRONIC REPETITIVE TIMER

PRACTICAL ^{1/6} WIRELESS

APRIL
1960

CONTENTS

TRANSISTORISED
SUPER-REGENERATOR

RECORD PLAYER WITH
CABINET

FREQUENCY METER BC 221

TRANSISTORISED MORSE
PRACTICE OSCILLATOR

MODEL CONTROL CIRCUITS

ETC. ETC. ETC.



RADIO & TV TABLES

"**NEWSTEAD**" (as illustrated). This contemporary "Slimline" TV Table is finished in highly polished walnut veneer. Measures 19" x 13" x 20" high.

Price £3.7.6 (inc. P.T.)

"**CHATSWORTH**." Finished in highly polished walnut veneer. Measures 19" x 14" x 21" high.

Price £4.0.0 (inc. P.T.)

"**WELBECK**" (as illustrated) measures 20" x 20" x 20" and is fitted with self-adjusting gliders.

Price £3.15.0 (inc. P.T.)

"**SHERWOOD**" will accommodate the largest television receivers: measures 23" high x 25" wide x 22" deep.

Price £5.5.0 (inc. P.T.)


"**SENIOR**," of ample dimensions (18" x 24" x 25" high).

Price £4.18.9 (inc. P.T.)

All are supplied packed flat ready for instant assembly and with the exception of the Welbeck and the Chatsworth have easy running 2" castors.



*The symbol
of extra
High Quality*

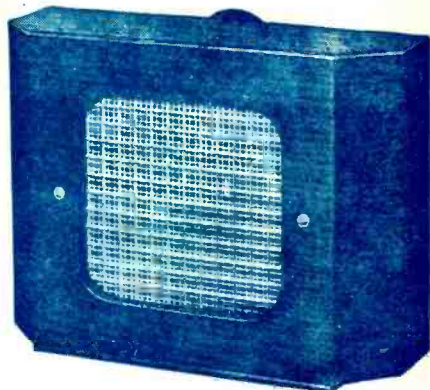

Stentorian EXTENSION SPEAKERS

These well designed speakers demonstrate the traditional Whiteley quality at really competitive prices. This range of extension speakers has finger-tip volume control, is superbly finished in polished walnut veneer and provides excellent reproduction.

WHITELEY ELECTRICAL RADIO CO. LTD.
MANSFIELD . NOTTS

**WITH THE
EXCLUSIVE
FINGER-TIP
VOLUME
CONTROLS**

'BUDE' 60/-
'BEDFORD' 72/-
'BRISTOL' 86/6

Prices include P.T.

For Safety's Sake use AVO Prodclips



... with Trigger-Action Spring-Loaded Clips

PRESS TRIGGER TO OPEN

RELEASE TO GRIP

Safety first every time with these patented spring-loaded AVO Prodclips.

Cleverly designed for use as insulated prods, they are invaluable for reaching and holding test points which are difficult of access.

Suitable for use with AvoMeter, Multiminor and Avo Electronic Test Meter Leads.

Post Free
15/-
per pair.

AVO LTD · AVOCET HOUSE,
92-96 VAUXHALL BRIDGE ROAD, LONDON, S.W.1.
VICTORIA 3404 (12 lines)

A MEMBER OF THE METAL INDUSTRIES GROUP OF COMPANIES

ADCOLA

(Regd. Trade Mark)

SOLDERING EQUIPMENT

THE INSTRUMENTS CREATED
FOR THE DISCRIMINATING
USER.

British & Foreign Pats., Regd.
Designs, etc.

ILLUSTRATED
Protective Shield
(Cat. No. 68)
Instrument $\frac{1}{8}$ " Bit
(Cat. No. 70)


The ideal combination for transistor and other intricate work.

Apply direct for catalogues:—

ADCOLA PRODUCTS LTD.,

**GAUDEN RD.,
CLAPHAM HIGH ST.,
LONDON, S.W.4.**

Telephones
MACaulay 4272 and 3101

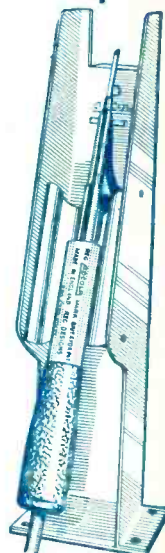

Tel: Mitcham 6201
Open Daily to Callers

R S T

All Valves Brand New
and Fully Guaranteed

211 STREATHAM ROAD, MITCHAM, SURREY

Special 24 Hour Express Mail Order Service.

| | | | | | | | | | | | | | | | | |
|-------|------|--------|------|------------|-------|---------|------|---------|------|---------|------|------------|--------|------|--------|-------|
| OZ4 | 5/9 | 6CH6 | 12/- | 10C2 | 27/10 | 32 | 13/6 | CCH35 | 14/6 | ECL83 | 12/6 | HL23DD | PCL82 | 11/6 | U251 | 17/6 |
| 1A5 | 6/- | 6E5GT | 10/- | 10F1 | 26/2 | 35A5 | 10/6 | CL4 | 12/6 | ECH82 | 12/6 | HL23DD | PCL83 | 12/6 | U281 | 20/- |
| 1A7 | 14/6 | 6F1 | 15/6 | 10F9 | 17/6 | 35L6GT | 15/- | CL33 | 18/6 | E79 | 21/- | HL41 | PEN4A | 17/6 | U282 | 22/- |
| 1D5 | 14/- | 6F6 | 6/9 | 10F9 | 12/6 | 35W4 | 8/- | CY1 | 15/9 | EF22 | 17/6 | HL41DD | PEN4A | 17/6 | U301 | 22/6 |
| 1D6 | 10/6 | 6F7 | 15/9 | 10LD3 | 12/6 | 35Z3 | 10/- | CY31 | 15/9 | EF36 | 7/6 | HL42DD | PEN4D | 22/6 | U329 | 17/6 |
| 1H5 | 10/6 | 6F12 | 4/9 | 10LD11 | 15/- | 35Z4 | 7/6 | D41 | 12/6 | EF37 | 8/6 | HL42DD | PL33 | 18/6 | U339 | 19/- |
| 1L4 | 6/- | 6F13 | 17/6 | 10P13 | 21/- | 35Z5 | 9/6 | D42 | 12/6 | EF37A | 8/6 | HL42DD | PL38 | 23/9 | U403 | 11/6 |
| 1LN5 | 4/6 | 6F14 | 17/6 | 10P14 | 20/- | 40SUA | 15/- | D63 | 3/6 | EF39 | 5/- | HY90 | PL81 | 14/9 | U404 | 10/- |
| 1N5 | 10/6 | 6F15 | 14/9 | 11D3 | 17/6 | 41STH | 23/6 | D77 | 5/6 | EF40 | 15/- | IVW4/350 | PL82 | 8/- | U401 | 29/- |
| 1R5 | 9/- | 6F17 | 12/- | 11D5 | 17/6 | 42 | 15/- | D152 | 6/- | EF41 | 9/3 | IVW4/500 | PL83 | 10/6 | U4020 | 15/6 |
| 1S4 | 8/6 | 6F33 | 5/6 | 12A6 | 6/6 | 43 | 15/- | DAC32 | 10/6 | AF42 | 10/6 | KBC32 | PL820 | 21/- | UABCB8 | 8/- |
| 1S5 | 9/- | 6H6 | 2/6 | 12AH8 | 10/- | 50C5 | 15/- | DAF91 | 7/6 | EF50(E) | 3/6 | KF35 | PL820 | 21/- | UAF42 | 9/6 |
| 1T4 | 5/6 | 6J5GT | 4/6 | 12AT6 | 9/- | 50CD6G | | DF33 | 10/6 | EF50(A) | 4/- | KL32 | PL83 | 10/6 | UB41 | 9/6 |
| 1U5 | 10/6 | 6J6 | 7/6 | 12AT7 | 8/- | | | DF91 | 5/- | EF80 | 7/- | KL32 | PM22A | 13/6 | UBC41 | 9/6 |
| 2D21 | 8/6 | 6J7GT | 9/6 | 12AU7 | 9/- | 50L6GT | 9/- | DF92 | 7/- | EF85 | 6/6 | KL35 | PM24M | 21/6 | UBF80 | 9/6 |
| 2X2 | 5/- | 6K7G | 3/- | 12AX7 | 9/6 | 61BT | 17/6 | DF96 | 9/6 | EF86 | 11/- | KT2 | PM24M | 21/6 | UBF89 | 8/6 |
| 3A5 | 12/6 | 6K8GT | 10/6 | 12BA6 | 9/- | 61SPT | 17/6 | DF97 | 9/6 | EF89 | 10/- | KT32 | PM202 | 16/- | UCC85 | 10/- |
| 3D6 | 14/6 | 6K8GT | 12/6 | 12BE6 | 9/6 | 62BT | 17/6 | DH63 | 10/- | EF91 | 4/9 | KT33C | PY31 | 16/6 | UCL82 | 12/6 |
| 3Q4 | 8/- | 6K25 | 19/6 | 12EJ | 17/6 | 75 | 12/6 | DH76 | 7/6 | EF92 | 5/- | KT36 | PY32 | 15/6 | UCL83 | 13/6 |
| 3Q5 | 10/6 | 6L1 | 15/6 | 12J7GT | 9/6 | 77 | 12/6 | DH77 | 8/3 | EF93 | 7/6 | KT41 | PY80 | 8/- | UF41 | 9/- |
| 354 | 8/- | 6L6 | 7/6 | 12K7GT | 8/6 | 78 | 12/6 | DH107 | 13/6 | EF95 | 15/- | KT44 | PY81 | 7/6 | UF42 | 11/6 |
| 3V4 | 9/- | 6L18 | 12/6 | 12K8GT | 12/6 | 80 | 10/- | DH719 | 7/6 | EL31 | 12/6 | KT55 | PY82 | 8/- | UF80 | 9/- |
| SR4GT | 9/- | 6L19 | 21/- | 12Q7GT | 8/6 | 85A2 | 12/6 | DK91 | 9/- | EL32 | 5/- | KT61 | PZ30 | 18/6 | UF85 | 9/- |
| 5U4G | 7/- | 6L34 | 10/- | 12SA7 | 8/- | 150B2 | 12/6 | DK92 | 9/6 | EL33 | 18/6 | KT63 | QP25 | 14/6 | UF89 | 8/- |
| 5V4 | 9/6 | 6/30L2 | 10/- | 12SC7 | 8/- | 150B3 | 12/6 | DK96 | 10/6 | EL35 | 12/6 | KT66 | QP231 | 17/6 | UL41 | 9/- |
| 5Y3GT | 8/6 | 6LD3 | 9/6 | 12SG7 | 8/6 | 185BT | 32/- | DL33 | 9/- | EL37 | 18/6 | KT71 | QP231 | 17/6 | UL44 | 24/6 |
| 5Z3 | 10/6 | 6LD20 | 15/6 | 12SH7 | 8/- | 303 | 7/6 | DL38 | 12/6 | EL38 | 23/9 | KT74 | R10 | 21/- | UL46 | 21/6 |
| 5Z4G | 10/6 | 6N7GT | 7/6 | 12SJ7 | 8/- | 304 | 7/6 | DL92 | 0/6 | EL41 | 10/6 | KT76 | R19 | 19/6 | UL84 | 9/6 |
| 6A7 | 18/6 | 6M1 | 10/6 | 12SK7 | 8/- | 305 | 7/6 | DL94 | 9/- | EL42 | 10/6 | KT101 | SD6 | 8/6 | UJ6 | 20/11 |
| 6A8 | 10/6 | 6M2 | 10/6 | 12SQ7 | 11/6 | 328 | 7/6 | DL96 | 9/6 | EL81 | 14/9 | KTW61 | SP4 | 14/6 | UJ7 | 15/- |
| 6AB8 | 12/6 | 6P1 | 17/6 | 12SN7 | 17/6 | 329 | 7/6 | EA50 | 2/- | EL84 | 7/- | KTW62 | SP4 | 3/6 | UJ8 | 26/- |
| 6AJ8 | 9/6 | 6P25 | 19/6 | 12Z3 | 15/- | 807 | 7/6 | EABCB80 | 7/6 | EL85 | 10/6 | KTW63 | SP4 | 12/6 | UY21 | 15/6 |
| 6AK5 | 8/- | 6P28 | 26/6 | 13D3 | 12/6 | 955 | 4/- | EAC91 | 7/6 | EL90 | 8/6 | KTZ41 | SP61 | 3/6 | UY41 | 7/6 |
| 6AK8 | 7/6 | 6Q7GT | 10/6 | 14H7 | 12/6 | 9002 | 7/6 | EAF42 | 10/- | EL91 | 5/- | KTZ63 | T41 | 22/6 | UY85 | 7/6 |
| 6AM | 4/9 | 6SG7 | 7/6 | 14F7 | 12/6 | 9003 | 7/6 | EB41 | 7/6 | EM80 | 10/- | L63 | TDD4 | 17/6 | VP28 | 17/6 |
| 6AM5 | 5/- | 6SH7 | 6/6 | 15A2 | 17/6 | AC4/PEN | | EB91 | 5/- | EM81 | 10/- | LN309 | TDD13C | 17/6 | VP48 | 17/6 |
| 6AM6 | 5/6 | 6SJ7 | 5/6 | 15D2 | 23/9 | AC5/PEN | | EBC33 | 5/- | EY81 | 10/6 | LZ319 | TH41 | 23/9 | W17 | 8/6 |
| 6AN5 | 7/6 | 6SK7 | 7/6 | 19AQ5 | 10/6 | AC6 | 21/- | EBC41 | 9/6 | EY84 | 10/6 | MH4 | TP22 | 17/6 | W76 | 7/6 |
| 6AQ5 | 8/3 | 6SL7GT | 6/6 | 19BG6G24/4 | | AC7 | 22/6 | EBF80 | 9/6 | EY86 | 9/6 | MHD4 | TP25 | 17/6 | W77 | 5/- |
| 6AQ8 | 9/3 | 6SN7GT | 5/6 | 20D1 | 12/6 | AC8 | 21/- | EBF89 | 9/6 | EY91 | 9/6 | MHL4 | TP25 | 17/6 | W81 | 6/- |
| 6AT6 | 8/3 | 6U4GT | 11/6 | 20D2 | 23/- | AC9 | 21/- | EBL31 | 21/6 | EZ35 | 7/- | MKT4 (5/7) | U14 | 15/9 | W19 | 7/6 |
| 6AU6 | 10/- | 6U5 | 7/6 | 20F2 | 26/6 | ACHL | 12/6 | EC90 | 9/6 | EZ40 | 7/6 | MS4B | U16 | 10/- | W727 | 7/6 |
| 6B7 | 10/6 | 6U7 | 7/6 | 20L1 | 26/6 | AC/PEN | | EC91 | 9/6 | EZ40 | 7/6 | MS4B | U18/20 | 10/- | X18 | 11/6 |
| 6B8 | 4/- | 6V6G | 5/- | 20P1 | 26/- | | | ECC31 | 10/- | EZ80 | 7/6 | MU14 | U22 | 10/- | X61M | 21/- |
| 6BA6 | 7/6 | 6V6GT | 8/- | 20P3 | 23/- | ACTH1 | 34/9 | ECC32 | 10/- | EZ81 | 7/6 | MX40 | U24 | 29/6 | X65 | 23/9 |
| 6BE6 | 7/6 | 6X4 | 5/- | 20P4 | 16/- | ACVPI | 17/6 | ECC33 | 5/- | EZ90 | 7/6 | N18 | U25 | 16/6 | X66 | 21/- |
| 6BG6G | 21/- | 6X5GT | 5/- | 20P5 | 22/6 | ACVPI | 17/6 | ECC34 | 15/- | FC2 | 21/- | N19 | U26 | 12/6 | X78 | 21/- |
| 6BJ6 | 7/6 | 7B7 | 8/- | 25L6GT | 9/6 | AC2/PEN | | ECC35 | 8/6 | FC13 | 17/6 | N37 | U31 | 9/6 | X79 | 21/- |
| 6BR7 | 10/6 | 7C5 | 8/- | 25Y5 | 10/- | AC2/PEN | | ECC40 | 21/- | FC13C | 21/- | N78 | U33 | 21/- | Y61 | 10/6 |
| 6BV6 | 8/6 | 7C6 | 8/- | 25Z4 | 9/6 | AC2/PEN | | ECC81 | 8/- | FW4,500 | 10/- | N108 | U35 | 21/- | Y63 | 9/- |
| 6BV7 | 6/6 | 7D5 | 15/- | 25Z5 | 9/6 | AC2/PEN | | ECC82 | 9/6 | FW4,800 | 10/- | N142 | U47 | 21/- | Z21 | 12/6 |
| 6BX6 | 7/- | 7D6 | 15/- | 25Z6 | 10/6 | AC2/PEN | | ECC83 | 9/6 | | | N147 | U50 | 8/6 | Z66 | 19/6 |
| 6BY7 | 7/6 | 7D8 | 15/- | 25Z7 | 17/6 | AC2/PEN | | ECC84 | 9/6 | | | N150 | U52 | 7/6 | Z77 | 4/9 |
| 6C4 | 6/6 | 7H7 | 8/- | 30 | 13/6 | AC2/PEN | | ECC85 | 9/6 | | | N153 | U76 | 7/6 | Z152 | 8/6 |
| 6CSGT | 8/- | 7K7 | 10/6 | 30C1 | 12/6 | AC2/PEN | | ECC91 | 5/6 | | | N309 | U78 | 7/6 | Z719 | 7/6 |
| 6C9 | 6/6 | 7Q7 | 11/6 | 30F5 | 11/6 | AC2/PEN | | ECCF80 | 12/6 | | | N329 | U142 | 8/- | ZD152 | 9/6 |
| 6C9 | 12/6 | 7R7 | 12/- | 30FL1 | 10/6 | AC2/PEN | | ECCF82 | 12/6 | | | H63 | U145 | 15/- | | |
| 6C10 | 12/6 | 7S7 | 10/6 | 30L1 | 11/6 | AC2/PEN | | ECH42 | 10/- | | | HBC90 | P2 | 10/6 | | |
| 6CD6G | 27/6 | 7Y4 | 5/6 | 30P4 | 22/- | AC2/PEN | | ECH81 | 9/- | | | HL133DD | PCC84 | 9/6 | | |
| 6D1 | 8/- | 8D3 | 5/6 | 30P12 | 11/6 | AC2/PEN | | ECH81 | 9/- | | | HL133DD | PCF80 | 10/6 | | |
| 6D2 | 5/- | 9BW6 | 14/9 | 30P16 | 10/- | AC2/PEN | | ECH35 | 9/- | | | HL133DD | PCF82 | 11/6 | | |
| 6D3 | 15/- | 10C1 | 18/- | 30P11 | 15/- | AC2/PEN | | ECL80 | 9/- | | | HL23 | | | | |

METAL RECTIFIERS

| | | | | | |
|-----|------|---------------|------|--------------|------|
| RM1 | 6/- | 1BRA 1-1-8-1 | 4/6 | 16RE 2-1-8-1 | 8/6 |
| RM2 | 8/- | 1BRA 1-1-16-1 | 6/6 | 16RA 1-2-8-1 | 11/- |
| RM3 | 9/- | 16RC 1-1-16-1 | 8/6 | 14A86 | 17/- |
| RM4 | 16/6 | 14RA 1-2-8-2 | 18/- | 14A97 | 23/6 |
| RM5 | 22/- | 14RA 1-2-8-3 | 21/- | 14A100 | 24/- |

CATHODE RAY TUBES

Type 43/69 £10.0.0

Type 36/44 £8.10.0

TERMS OF BUSINESS C.W.O. or C.O.D.
2/9 PACKING CHARGE ON ALL C.O.D.
ORDERS. POSTAGE 3d. PER VALVE.

OBsolete VALVES A SPECIALITY.
QUOTATIONS GIVEN ON ANY TYPE
NOT LISTED.

W.D. Circuit Details

Diagrams and other information extracted from official manuals. All 1/6 per copy, 12 for 15/-.


A.134
BC.348
BC.312
R.103A
BC.342
R.A.1B
R-203
R-1155
R-1124A
R-1132A/R-1481
R-1147
R-1124A
R-1082
R-1355
B.C.1206-A/B
B-455-A (or-B)
B-454-A (or-B)
B-456-M-A (or-B)
Transmitter TT154
Fifty-eight walkie talkie
Frequency meter
B.C. 221

R.109
HRO Receiver
R28/ARC5
R1116/A
R.A.1B
AR88D
AN/APA-1
78
76
R.T.13
CAY-46-AAM-
RADAR
A.S.B.-3
Indicator 62A
Indicator A.S.B.3
Indicator 62
Indicator 6K
R.F. unit 24
R.F. unit 25
R.F. unit 26
R.F. unit 27
Wireless set No. 19
Demobbed valves

Avo Proclips

The advantage of these test prods is that by pressing the trigger at the side they become crocodile clips and can be left in circuit. This is a great time saver when servicing. Price 15/- Pair.

Now reduced to 19/6

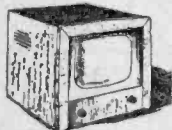

9/6 each. Carriage and extra. Masks 10/- extra.

Band III Converters



fine tuner, contrast control, condensers and resistors. (Metal case available as an extra.) Price only 19/6, plus 2/6 post and insurance. Data free with parts or available separately, 1/6.

Please send two more kits, the one you sent last week is performing magnificently. We receive this sort of letter every day of the week, so if you have hesitated because you thought our kits too cheap you need hesitate no longer.

Waterproof Heater Cable 14 n per foot, 10d. per yard.


Radio Stethoscope

This can be slipped into the pocket rather like a fountain pen. With it in most districts a receiver can be checked from the grid of the first valve right through to the output without a signal generator, the stethoscope will operate in both L.F. and R.F. circuits without alteration. It is a complete fault-finder. All the necessary parts to make this tracer 6/6, post 1/-.



Circular Fluorescent Lighting

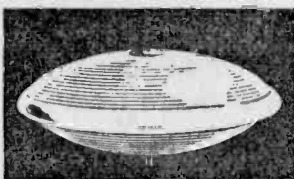
Introducing the "Saturn" is our newest circular fluorescent lighting unit. It really is a wonderful unit which will enrich your room not only by its elegance but the bright warm light from the fluorescent tube will light up every corner of the room and bring out the richness and colour of your furnishings and decorations.



The top and bottom spheres are available in red, yellow, blue, opal and green so you may choose the colour or pair of colours to suit your taste and furnishings. The "Saturn" is made in two models, 40 watt and 80 watt, both approx. 16in. in diameter. The price of the 40 watt is £5.19.6 and the 80 watt is £6.19.6. These prices include a warm white tube and suspending chain. In fact you have nothing else to buy. Nor is extra wiring required, you simply take down the existing fitting. The wires that went to this, join to the wires of the "Saturn" and that is all. Running cost of the "Saturn" is approx. 25 hours per unit for the 40 watt and 12 hours for the 80 watt. Light output of the 40 w. is equivalent to the average 150w. lamp and the 80w. equivalent to two 150w. lamps. We manufacture Fluorescent lighting units from 6 inches to 8 feet; a stamped envelope will bring our illustrated list. Trade inquiries welcome.

Component Storage Drawers

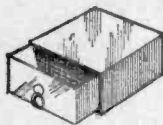Stout board construction these drawers are ideal for small parts. Supplied complete with simple erection instructions—1/6 each or 12 drawers each 6 x 2 1/2 x 6 1/2 in. 13/6, post 2/-.



RI155 for Spares

These are less valves but otherwise reasonably complete—ideal for spares—prices £2 to £4 depending on condition—carriage 7/6.



THIS MONTH'S SNIP Super Transistor Set



Makes ideal bedroom radio, uses one transistor and one crystal diode, complete with case 19/6, post and insurance 2/6.


Motor Snip

Miniature motor 2 1/2 in. long x 1 1/2 in. diameter, laminated stator and armature, separate winding for reversing. Operates off 20-30 v. D.C. or off A.C. mains through stepdown transformer. Original cost at least £3 each. Snip price for one month only 8/6, plus 1/6 postage and insurance.




10 Valve 1 1/2 Metre Superhet

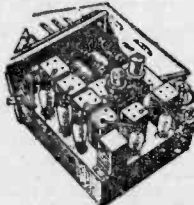Ideal for Commercial TV. These contain 6 valves type SF61, and one each RI.7, RI.16 and EA50. Six I.F. transformers, 12 Mc/s band, and hundreds of other useful components. Price 29/6, plus carriage and packing 7/6. These receivers are unused.



FOR ADDRESS SEE OPPOSITE PAGE

Charging Switchboard

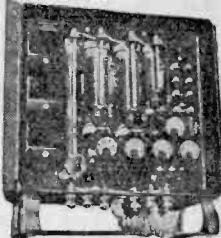


Offered at about one-twentieth of original cost. This is an ex-Government switchboard. It contains three separate current relays, one voltmeter, one main ammeter, two secondary ammeters and three variable resistors for controlling circuits. These are original cases. Price £2/15/0, carr. 10/-.

Novelty Radio

Completely wired tunable medium and long wave, originally intended for ETG valves and external batteries but could easily be converted for transistors with internal batteries. Less valves and speaker, otherwise complete. 15/-, plus 1/6 postage.



Thermostats

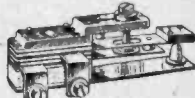

Useful for the control of appliances such as convectors, gluepots, vulcanisers, hot plates, etc. Adjustable to operate over temperature range 50-550 deg. fitted with heavy silver contacts. 8/6. Other types: 11 amp., 3/6; 5 amp., 8/6; 2 amp. QMB, 5/6; 15 amp. QMB, 15/-, plus 1/6 postage.

A.C./D.C. Multimeter Kit

Ranges: D.C. volts 0-5, 0-50, 0-100, 0-500, 0-1,000. A.C. volts 0-5, 0-50, 0-100, 0-500. D.C. milliamps 0-5, 0-100, 0-500. Ohms 0-50,000 with internal batteries. Measures A.C./D.C. volts, D.C. current and ohms. All the essential parts including metal case, 2in. moving coil meter, selected resistors, wire for shunts, range selector, switches, calibrated scale and full instructions price 19/6, plus 2/6 post and insurance.



Cabinet Snip



This fine cabinet as illustrated but less control knobs is available this month at a special snip price of 12/6, plus 3/6 post and insurance. Size is 13 1/2 x 9 x 4 1/2 in. and it is nicely covered in two tone I.C.I. fabric.

Special This Month

Moving Coil Meters:
 0-500 microamp, 2in. flush ... 17/6
 250-0-250 microamp, 2in. surface ... 27/6
 750 microamp, 2in. surface ... 17/6
 5-0-5 milliamp, 2in. flush ... 17/6
 0-30 milliamp, 2in. flush ... 17/6
 0-100 milliamp, 2in. flush ... 15/-
 0-300 milliamp, 2in. flush ... 15/-
 0-500 milliamp, 2in. flush ... 15/-

Luminous Switch. Double pole designed for electric blankets, neon indicators glow when appliance is switched on. 10/-.

Unbreakable Mains Lead. Type of lead fitted to electric razors makes fine lead for test meters and any other devices where subject to continuous bending. Twin figure eight construction, soft cream p.v.c. covered. Normally costs 2/- per yard. Three 8ft. leads for 2/-.

Metal Rectifier. Equivalent RM5, 12/6.

Metal Rectifier. 60/80 mA 250/300 v., 4/6.

Output Transformer. Standard Pentode, 4/6. Multi ratio, 6/6.

Bi-metal Strip. with heavy duty contact, ideal for thermostat, fire, lamp, etc., etc., 2/6.

Neon Lamp. Midget wire ended, ideal mains tester, etc., 2/-, ex. gov. 1/8.

Phillips Trimmers. 0-300F, 1/- each, 9/- doz.

Set of 8 Allen Keys, 3/6.

Install those extra Points, 3,029 twin flat T.R.S. cable. Big purchase enables us to sell this at 45/- per 100 yds., carriage 3/6.

Low Resistance Head Phones. Ideal crystal sets, etc., 7/6, plus 2/6.

Goodmans Multi Ratio Output Transformer, 6 watt, 8 ratios, from 12-1 to 72-1. Centre tapped for push/pull, 7/6 plus 1/-.

Ditto unbranded, 6/6, post 1/-.

Cold Cathode Valve CV413. Voltage regulator or trigger switch—unused but ex-equipment. 2/- each.

Tag Panels. Ideal for constructors, experimental circuits, etc., 3 of each of 12 different types, 5/-, post 1/6.

Slydlok Panel Mounting Fuses with carrier, 5 amp, 2/- each, 15 amp, 2/6 each.

Belling Lee 2BA fully insulated terminals for mounting through metal panels 2/- each.

Terminal Heads, insulated 4BA, 2/- doz.

0.1 mFd 350 v. Small tubular metal cased condensers made by Dubilier. 2/6 doz.

50 Assorted Resistors. Well mixed and useful values 1 and 1 watt, 5/- for 50.

Ditto, but 1 watt, 6/6 for 50.

Mains Transformer, Standard 230 v., input 250-0-250 at 80 mA, 6.3 v. at 5 A, 12/6.

Toggle Switch. Standard metal body type with round dolly, fixing ring and on/off indicating plate, 1/3 each or 12/- doz.


Screened Cable. Rubber covered, flexible with metal braiding, ideal for microphone or gramophone extensions, 4d. per yd., 30/- per 100 yds.

Miniature Microphone

American made. Dynamic type, real bargain at 2/6, plus 6d. postage.



B.29 Receiver

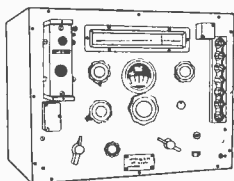

A fine receiver made by the famous Marconi Company. Covers the shipping bands 15 k/c to 500 k/c in four switch stages. Has Vernier tuning and all refinements. Works off A.C. mains with internal power pack. A few only, in good working order £15 each. Also some needing servicing £12.10.0 each.


Making a Solder Gun



A 7-second solder gun of the type costing £3-14 was described in "Practical Mechanics". Only two essential parts are required—(a) the transformer and (b) the push switch. These we can supply at 11/6, plus 2/- post. The rest of the parts you will have in your own "junk" box. Copy of the article concerned given free with the kit.

Another Car Battery Charger Bargain

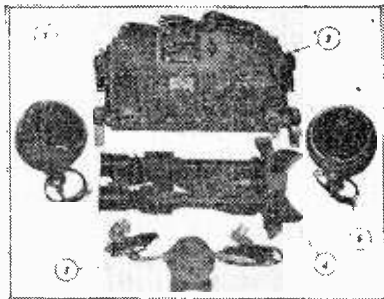Car Battery Charger—ready-made high output battery charger in stove enamelled sheet steel louvered case. New, complete and ready to work. Rated at 12 v. 5 amps. and variable rate selector for trickle charging, also a meter to show charging rate. Suitable for 230-250 A.C. mains. Special snip price of 65/-, plus 3/6 post and ins.



TABBY EQUIPMENT COMPLETE

Complete equipment for seeing in the dark, as fitted to Army vehicles for night driving, etc. Complete working equipment comprises: 2 Infra Red Radiators, adjustable binoculars, powerpack for 6 or 12 volts, control units and inter-connection cables. Original cost probably around £100. Unused and in perfect order—£2-19.6 or 10/- deposit and 15 fortnightly payments of 10/-.

Fluorescent Light Bargain

Kit of Parts comprising: choke, two lamp holder, starter holder and starter. 40 watt, 19/6, 80 watt, 23/6. Plus 2/- Post and insurance.


Transistor Set Parcel



Cabinet as illustrated—with handle and knobs—2 gang tuning condenser—printed circuit—tuning scale—full circuit necessary

diagram showing other parts—separate value £3—will all be sent for 29/6, plus 2/6 post and insurance.

Rectifier Bargains

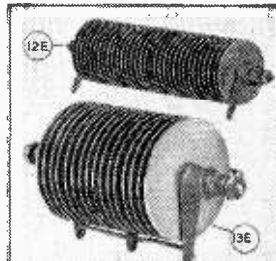

Selenium rectifier type 12, 500 v. ± A. half-wave, easily rebuilt into full wave or multiple type, contains 30 35 mm. discs. Price 8/6, plus 1/6 post. **Type 13, 36 volt 9 amp.** easily rebuilt into six full wave charger rectifiers suitable for 6 or 12 volt batteries at 3 amps, contains 24 84 mm. discs. Real bargain at 19/6, plus 1/6 post.

Speaker Bargain



12in. Hi-fidelity loudspeaker. High flux. Permanent magnet type with standard 3 ohm speech coil. Will handle up to 12 watts. Brand new by famous maker. Price 32/6, plus 3/6 post and insurance.

1960 All Mains Amplifier



Undoubtedly finest value obtainable in amplifiers—powerful three valve circuit ideal for dances, parties, etc. Complete with valves, mains transformers, volume and tone controls, but less chassis, speaker and cabinet. Price only 29/6, plus 2/6 post and ins. Data free with parts or available separately 1/6.

ELECTRONIC PRECISION EQUIPMENT LTD.

66, GROVE ROAD, EASTBOURNE, SUSSEX.

This is the correct address for post orders and for prompt attention please mark your envelope Dept. 7, also enough for postage.

Electronics (Manor Park) Ltd., 320 High Street North, Manor Park, E.12

Electronics (Ruislip) Ltd., 42-46 Windmill Hill, Ruislip, Middx. Phone: RUISLIP 5780 Half day Wednesday

Electronics (Croydon) Ltd., 288 London Road, Croydon. Phone: CRO 6558 Half day Wednesday

Electronics (Finsbury Park) Ltd., 29 Stroud Green Rd., Finsbury Park, N.4. Phone: ARCHWAY 1049 Half day Thursday.

BENTLEY ACOUSTIC CORPORATION LTD.

THE VALVE SPECIALISTS. 38 CHALCOT ROAD, LONDON, N.W.1.

Telephone: PRIMROSE 9092

EXPRESS POSTAL SERVICE! ALL ORDERS DESPATCHED SAME DAY AS RECEIVED. FOR ONLY 2/6 EXTRA TELEPHONE FOR THAT URGENT ORDER TO BE DESPATCHED IMMEDIATELY BY OUR SPECIAL C.O.D. SERVICE.

ANY ORDER INSURED AGAINST DAMAGE IN TRANSIT FOR ONLY 6/6 EXTRA.

| | | | | | | | | | | | | | | | | | |
|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
| ACROSS THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF THE BOARD - 100% OF | | | | | | | | | | | | | | | | | |
|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

FULL RANGE OF TRANSISTORS AND GERMANIUM DIODES IN STOCK. TECHNICAL DATA AND PRICES FREE ON RECEIPT OF SELF-ADDRESSED ENVELOPE.

NEW METAL RECTIFIERS—FULLY GUARANTEED

Technical leaflet on Metal Rectifiers free on receipt of S.A.E.

| | | | | | | | | | | | |
|--------|------|------|------|-------|------|--------|------|---------------|------|---------------|------|
| DRM-1B | 15/4 | RM-1 | 7/- | WX3 | 3/6 | 14A100 | 27/- | 14RA 1-2-8-2 | 17/6 | 16RE 2-1-8-1 | 8/6 |
| DRM-2B | 16/2 | RM-2 | 9/- | WX4 | 3/6 | 14A124 | 28/- | 14RA 1-2-8-3 | 21/- | 18RA 1-1-8-1 | 4/6 |
| DRM-3B | 23/3 | RM-3 | 9/6 | WX | 3/6 | 14A163 | 38/- | 14RA 2-1-16-1 | 21/- | 18RA 1-1-16-1 | 6/6 |
| LW7 | 21/- | RM-4 | 16/- | 14A8 | 17/6 | 14B130 | 35/- | 16RC 1-1-16-1 | 8/6 | 18RA 1-2-8-1 | 11/- |
| RM-0 | 7/11 | RM-5 | 19/6 | 14A97 | 25/- | 14B261 | 11/6 | 16RD 2-2-8-1 | 12/- | 18RD 2-2-8-1 | 15/- |

Training in Radio and Television Servicing

The Pembridge College of Electronics provides a full-time One Year course in the basic principles of Radio and Television for prospective servicing engineers. It is also suitable for those wishing to become proficient in the maintenance of all types of industrial electronic equipment.

The next course commences on 26th April, 1960 and enrolments are now being accepted. The following course will commence on 6th September, 1960.

HOME-STUDY COURSES AND KITS-OF-PARTS

We are the only organisation with a full-time technical staff, backed by laboratories, offering these courses and kits.

Kits-of-Parts

1. 20000 ohms/volt Multimeter for Kit Assembly.

These kits provide a unique opportunity to construct a first-class instrument at a reasonable price. Our instructions place success well within the capabilities of the average constructor.

Simple tools only required, no calibration necessary.

£7.10.0d. cash with order. Postage and packing 3/- (U.K. only).

2. Transistor Receiver.

A six-transistor superhet radio receiver of high sensitivity and excellent reproduction is available with full constructional details. This receiver is a current model from a well-known manufacturer.

Other kits available in the near future.

All our kits are provided by manufacturers who are leaders in their field. The parts are drawn directly from their stocks for their current models.

Home-Study Courses

Available now—

a. Course for Intermediate examinations of the new City and Guilds' Telecommunication Technicians' Course. (New Scheme)

b. "Transistors for the Radio Servicing Engineer", including assembly and testing of a six-transistor receiver.

c. "Basic Electricity and Magnetism", including Multimeter assembly kit-of-parts and basic experiments and measurements.

d. "Basic Mathematics and Mechanics for Radio".

In preparation—

a. Course leading to City and Guilds' Final Certificate.

b. "Elements of Radio Servicing" with constructional kit.

c. Advanced Radio Servicing.

d. Basic Television.

Our courses are prepared by lecturers whose daily work is to teach Radio, Television and Telecommunications at all levels to full-time and part-time students. They have an intimate knowledge of student problems and requirements beyond that found in ordinary correspondence course work.

For our Prospectus on the One Year course, admission forms and details of our activities, write to:

The Principal, P.10,

THE PEMBRIDGE COLLEGE OF ELECTRONICS

34A, Hereford Road, London, W.2.

BAYswater 9117



FOR VALVES - TUBES AND COMPONENTS - BY RETURN POST SERVICE

| | | | | | | | | | | | | | | | | | |
|---------|-------|------------|-------|------------|-------|-------------|-------|--------|-------|--------|---------|------------|-------|----------|--------|------|------|
| ACHLDD | EF80 | 7/6 | PCL82 | 12/- | U06 | 19/11 | 6C5 | 5/- | 10L1 | 15/11 | 12SK7 | 6/- | 30L15 | 23/3 | 210VPT | 3/6 | |
| AC/P | 7/6 | EF85 | 7/6 | PL38 | 26/6 | UYIN | 12/6 | 6C9 | 17/3 | 10LD11 | 12/- | 12SL7 | 8/- | 30P4 | 15/- | 82 | 10/6 |
| ACSPEND | EF89 | 8/9 | PCL84 | 16/7 | UY41 | 7/6 | 6CD31 | 7/6 | 10M2 | 23/3 | 12SN7GT | | 30P12 | 12/6 | 301 | 10/6 | |
| | 26/6 | EF91 | 5/9 | PL36 | 15/- | UY85 | 7/- | | 10P13 | 15/- | | | 30P16 | 9/6 | 302 | 10/6 | |
| AC6PEN | 6/6 | EF91 (BVA) | 7/6 | PL82 | 8/6 | VP133 | 15/- | 6D6 | 5/- | 10P14 | 19/3 | 12SQ7 | 8/6 | 30PL1 | 12/6 | 304 | 10/6 |
| ATP4 | 3/6 | | | PL83 | 11/6 | VR22(PM) | 2A) | 6F6G | 7/6 | 12A6 | 6/6 | 1457 | 17/- | 30PL1321 | 11/1 | 305 | 10/6 |
| AZ1 | 10/- | EF97 | 13/3 | PL84 | 12/7 | 2A) | 3/- | 6F6M | 7/6 | 12AT6 | 10/6 | 15D2 | 7/9 | 35L6GT | 10/- | 306 | 10/6 |
| AZ31 | 10/- | EF98 | 13/3 | PL820 | 18/7 | VP23 | 6/6 | 6F1 | 14/- | 12AT7 | 7/6 | 19AQ5 | 9/9 | 25Y5 | 9/9 | 607 | 6/6 |
| AZ41 | 13/11 | EL32 | 5/6 | PX25 | 12/6 | VP41 | 8/6 | 6F13 | 14/- | 12AU6 | 8/- | 19BG6G23/3 | | 35W4 | 7/6 | 954 | 2/- |
| B36 | 10/- | EL33 | 14/- | PY31 | 16/7 | VR105/30-8 | | 6F14 | 26/6 | 12AU7 | 8/- | 20D1 | 15/3 | 35Z4GT | 8/- | 955 | 4/- |
| CB11 | 26/6 | EL34 | 19/11 | PY32 | 17/11 | VR116 | 4/- | 6F15 | 14/- | 12AX7 | 8/- | 20F2 | 26/6 | 42 | 8/- | 956 | 3/6 |
| CB131 | 23/3 | EL36 | 19/11 | PY80 | 7/6 | VR150/307/6 | | 6F18 | 15/3 | 12BA6 | 9/- | 20L1 | 26/6 | 35Z23 | 16/7 | 957 | 3/6 |
| CCH35 | 23/3 | EL38 | 26/6 | PY81 | 8/6 | VI120A | 3/6 | 6F23 | 18/7 | 12BE6 | 9/- | 20P1 | 26/6 | 35Z5GT | 9/- | 5763 | 9/- |
| CL4 | 12/6 | EL41 | 10/6 | PY82 | 7/6 | VU39(MU) | | 6F33 | 7/6 | 12C8 | 9/- | 25A6G | 10/6 | 50C5 | 11/6 | 9002 | 5/6 |
| CL33 | 19/3 | EL42 | 10/6 | PY83 | 8/6 | 12/14 | 9/- | 6H6 | 2/6 | 12H6 | 3/6 | 25L6GT | 10/- | 50CD6G | | 9004 | 5/6 |
| CY31 | 16/7 | EL43 | 16/7 | PZ30 | 19/11 | VU111 | 2/6 | 6H6GT | 2/6 | 12J5GT | 3/- | 25Z4 | 9/6 | | 29/10 | 9006 | 5/6 |
| CY1 | 18/7 | EL43 | 19/11 | PEN4DD | 26/6 | W75 | 7/6 | 6J5GT | 5/- | | | | | | | | |
| CV73 | 4/- | EL84 | 9/- | | | W77 | 8/6 | 6J5M | 6/6 | | | | | | | | |
| C36A | 6/6 | EL821 | 26/6 | PEN45 | 12/6 | W79 | 10/6 | 6J6 | 6/6 | | | | | | | | |
| DAF96 | 8/9 | EM34 | 9/6 | PEN46 | 7/6 | X78 | 21/3 | 6J6GT | 9/- | | | | | | | | |
| DF96 | 8/9 | EM80 | 10/6 | PEN47 | 6/6 | Y63 | 9/- | 6J7M | 9/- | | | | | | | | |
| DH63 | 7/6 | EM81 | 10/6 | PEN46 | 7/6 | Z309 | 7/6 | 6K7G | 4/- | | | | | | | | |
| DK96 | 8/9 | EY51 | 10/6 | PEN383 | 23/3 | Z359 | 7/6 | 6K7M | 6/9 | | | | | | | | |
| DL96 | 8/9 | EY81 | 13/3 | PEN220A | 4/- | IA3 | 3/6 | 6K8G | 7/6 | | | | | | | | |
| DM70 | 7/6 | EY86 | 10/6 | PEN45DD | | IA7GT | 12/6 | 6K6GT | 7/- | | | | | | | | |
| E150 | 1/6 | EZ35 | 16/7 | | | IC2 | 11/6 | 6K8GT | 5/9 | | | | | | | | |
| EABCB80 | 9/- | EZ40 | 7/6 | PENA4 | 26/6 | IC5GT | 12/6 | 6K8GT | 10/- | | | | | | | | |
| EAF42 | 10/6 | EZ41 | 7/6 | PM12M | 8/- | ID5 | 12/6 | 6K25 | 19/11 | | | | | | | | |
| EB34 | 2/- | EZ80 | 7/6 | QP21 | 5/- | ID6 | 12/6 | 6L6G | 8/6 | | | | | | | | |
| EB41 | 8/6 | EZ81 | 7/6 | R16 | 26/6 | IHSGT | 10/6 | 6L6M | 9/6 | | | | | | | | |
| EB91 | 5/- | EZ90 | 7/6 | SP41 | 3/6 | IL4 | 6/6 | 6L7G | 7/6 | | | | | | | | |
| EB33 | 6/9 | E1148 | 2/6 | SP61 | 3/6 | ILDS | 3/6 | 6L1 | 23/3 | | | | | | | | |
| EB41 | 9/6 | FC4 | 26/6 | SP45 | 10/6 | INS | 10/6 | 6L18 | 11/6 | | | | | | | | |
| EB8C1 | 11/4 | FC13 | 6/6 | SP47 | 10/6 | IRS | 7/6 | 6L19 | 23/3 | | | | | | | | |
| EB8C90 | 12/7 | FW4/500 | | T41 | 23/3 | ISA | 10/6 | 6LD20 | 15/11 | | | | | | | | |
| EB8C91 | 12/7 | | | TH233 | 10/6 | ISS | 6/6 | 6M1 | 17/3 | | | | | | | | |
| EBF80 | 9/6 | | | TP25 | 10/- | IT4 | 6/- | 6N7GT | 7/6 | | | | | | | | |
| EBF89 | 9/6 | GTIC | 27/6 | U10 | 10/6 | 2C26 | 1/6 | 6P1 | 19/3 | | | | | | | | |
| EBL21 | 23/3 | GZ32 | 12/- | U10 | 10/6 | 2P5 | 26/6 | 6P28 | 19/11 | | | | | | | | |
| EBL31 | 23/3 | H30 | 4/6 | U16 | 12/6 | 2X2 | 4/6 | 6P28 | 26/6 | | | | | | | | |
| EC31 | 7/6 | H133DD | 8/6 | U22 | 8/- | 3A4 | 7/- | 6Q7G | 7/6 | | | | | | | | |
| EC40 | 23/3 | HL22 | 6/6 | U25 | 14/- | 3A5 | 12/6 | 6Q7GT | 8/6 | | | | | | | | |
| EC81 | 8/- | HN309 | 24/7 | U26 | 12/6 | 3A8GT | 6/- | 6SA7GT | 8/6 | | | | | | | | |
| EC82 | 7/6 | K40N | 9/7 | U37 | 26/6 | 3D6 | 5/- | 6SG7 | 7/6 | | | | | | | | |
| EC83 | 9/- | KF35 | 8/6 | U45 | 15/- | 3Q4 | 8/- | 6SH7 | 8/6 | | | | | | | | |
| EC84 | 10/- | KK32 | 21/11 | U50 | 8/- | 3Q5GT | 9/6 | 6S17 | 8/6 | | | | | | | | |
| EC85 | 9/6 | KL132 | 24/7 | U76 | 8/- | 354 | 7/6 | 6SK7 | 6/- | | | | | | | | |
| ECF80 | 12/- | KT2 | 5/- | U191 | 11/6 | 3V4 | 8/6 | 6SL7GT | 8/6 | | | | | | | | |
| ECF82 | 13/- | KT24 | 5/- | U339 | 12/- | 4D1 | 3/6 | 6SN7GT | 7/6 | | | | | | | | |
| EC83 | 26/6 | KT32 | 14/- | U403 | 16/7 | 5R4GY | 9/6 | 6SQ7 | 9/3 | | | | | | | | |
| EC831 | 23/3 | KT33C | 8/6 | U404 | 11/4 | 5U4G | 6/6 | 6U4GT | 12/- | | | | | | | | |
| EC835 | 23/3 | KT36 | 29/10 | U801 | 29/10 | 5V4 | 11/6 | 6U5G | 8/6 | | | | | | | | |
| EC842 | 9/6 | KT61 | 13/6 | UACB8010/- | | 5Y3G | 8/- | 6U7G | 8/6 | | | | | | | | |
| EC881 | 9/- | KG3 | 7/6 | UAF42 | 9/6 | 5Y3GT | 8/- | 6V6G | 6/- | | | | | | | | |
| EC883 | 9/- | KG6 | 17/6 | UBC41 | 9/- | 5Z4G | 9/- | 6V6GT | 7/6 | | | | | | | | |
| | 13/11 | KT88 | 22/6 | UBC81 | 11/4 | 5Z4M | 10/- | 6X4 | 7/6 | | | | | | | | |
| ECL80 | 10/- | KT101 | 10/6 | UBF80 | 9/6 | 6A7 | 10/- | 6X5G | 7/- | | | | | | | | |
| ECL82 | 12/6 | KTW61 | 6/6 | UBF89 | 13/11 | 6A8G | 9/- | 6X5GT | 7/- | | | | | | | | |
| ECL83 | 19/3 | KTW63 | 7/6 | UBL21 | 23/3 | 6AC7 | 5/- | 6/30L2 | 12/6 | | | | | | | | |
| EF9 | 23/3 | KTZ41 | 3/6 | UC92 | 13/3 | 6AG5 | 5/- | 786 | 10/6 | | | | | | | | |
| EF22 | 8/6 | MH41 | 7/6 | UCC8410/11 | | 6AK5 | 6/6 | 787 | 8/6 | | | | | | | | |
| EF36 | 5/- | M4 | 8/6 | UCB05 | 10/6 | 6AL5 | 4/6 | 788 | 6/6 | | | | | | | | |
| EF37A | 15/- | MSP45 | 7/6 | UCF80 | 16/7 | 6AM5 | 7/6 | 7C5 | 8/- | | | | | | | | |
| EF39 | 5/9 | MSP47 | 7/6 | UC82 | 13/3 | 6AM6 | 4/6 | 7C6 | 8/- | | | | | | | | |
| EF40 | 14/6 | N37 | 19/11 | UC82 | 10/6 | 6AQ5 | 7/6 | 7D7 | 13/6 | | | | | | | | |
| EF41 | 9/9 | N78 | 19/11 | UC831 | 10/6 | 6AT6 | 8/6 | 7H7 | 9/- | | | | | | | | |
| EF42 | 11/- | N339 | 17/6 | UCL82 | 16/7 | 6AU6 | 10/6 | 7Q6 | 9/6 | | | | | | | | |
| EF50 | 4/- | OZ4 | 5/6 | UCL83 | 13/6 | 6BBG | 4/- | 757 | 9/6 | | | | | | | | |
| EF50SYL | 7/- | P61 | 3/6 | UF41 | 9/- | 6BA6 | 7/6 | 7Y4 | 8/6 | | | | | | | | |
| EF54 | 6/- | PABC80 | | UF42 | 17/3 | 6BE6 | 8/- | 8D2 | 2/9 | | | | | | | | |
| EF55 | 10/- | | 13/11 | UF80 | 13/11 | 6BG6G | 23/3 | 9D2 | 3/6 | | | | | | | | |

| | | | | | | | | | |
|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|--|--|--|--|--|--|--|--|--|
| ACOS MICROPHONES | | | | | | | | | |
| Acos Mic 39/1. Crystal Stick Microphones for use as hand, desk or floor stand units for high quality recording, broadcast and public address work. List Price £5.50. OUR PRICE 3/6. With stand 47/6. With floor stand adaptor 52/6. Postage 1/6. | | | | | | | | | |
| BATTERY BUZZERS | | | | | | | | | |
| 3/9 each. | | | | | | | | | |
| MORSE KEYS | | | | | | | | | |
| 3/- each. | | | | | | | | | |
| DUBILIER TYPE "C" | | | | | | | | | |
| controls 500 K. 6/6 each. | | | | | | | | | |
| CO-AXIAL CABLE | | | | | | | | | |
| semi-airspaced 75 ohms. 6d. yard. 15/6. | | | | | | | | | |
| CRYSTAL CARTRIDGES | | | | | | | | | |
| Complete with styli. Acos HEP3Y/1, HGP59/5C, BSR, TC8. Collard Studio. All 15/6 each. | | | | | | | | | |
| CHARGER TRANSFORMERS | | | | | | | | | |
| Tapped primary 200/240 v., secondary 3.5 v., 9 v. and 17 v. 1 amp. type 13/6; 2 amp. type 15/6; 4 amp. type 21/-; 6 amp. type 32/6. Postage 2/-. | | | | | | | | | |
| HEATER TRANSFORMERS | | | | | | | | | |
| All 24v. input. 4v. 3 amp. 10/-; 6.3v. 1amp. 6/9; 6.3v. 3 amp. 12/-; 12.6v. 3/6; 5 amp. 5/9; 5v. 2 amp. 10/-; 2v. 3 amp. 8/3. | | | | | | | | | |
| METERS. PANEL MOUNTING (Round) MOVING COIL. | | | | | | | | | |
| Make F.S.D. Res. Scale Size Price | | | | | | | | | |
| Weston (U.S.A.) 1mA 150 ohms 0-100 3 1/2in. 27/6 | | | | | | | | | |
| Weston (U.K.) 1mA 75 ohms 0-100 3 1/2in. 22/6 | | | | | | | | | |
| W.D. (U.K.) 5mA 0-0037 ohms 0-20 2in. 9/6 | | | | | | | | | |
| W.D. (U.S.A.) 500mA 0-600 2 1/2in. 15/6 | | | | | | | | | |
| PUBLICATIONS | | | | | | | | | |
| Wireless World Valve Data Book, 5/-, post 4d. Data TV Fault Finding Book, 5/-, post 4d. Mullard Circuits for Audio Amplifiers, 8/6, post 6d. Short Wave Receivers for the Beginner, 6/-. | | | | | | | | | |
| TERMS: Cash with order or | | | | | | | | | |

| | | | | | | | | | |
|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------|--|--|--|--|--|--|--|--|--|
| MICRO SWITCHES | | | | | | | | | |
| 3/9 each. | | | | | | | | | |
| REGUNNED | | | | | | | | | |
| Television Tubes, 12-month guarantee, 12 to 14in. £5.10. 15 to 17in. £6. Carriage and Insurance 10/- extra. | | | | | | | | | |
| OUTPUT TRANSFORMERS | | | | | | | | | |
| Elstone OT/3 for Mullard 3 watt Amplifier, 25/-; Elstone OT6 Low Load, OT8 Normal Load, OT/M Dist. Load, all 45/- and all for Mullard 5/10 amp. | | | | | | | | | |
| Single ended 5000/3 ohms, 40mA, 4/6; 5000/3 ohms, 60mA, 5/9; 10000/3 ohms, 30mA, 4/6. Universal 18 Ratio Type 40mA, 5/9 each. | | | | | | | | | |
| ACOS CRYSTAL PICK-UPS | | | | | | | | | |
| Turnover Heat (2 sapphire styli), 29/11. P.P. 2/6. | | | | | | | | | |
| SCOTCH RECORDING TAPE | | | | | | | | | |
| 1200ft Reels Standard 23/-; 1800ft Reels Extra Play 37/6 | | | | | | | | | |
| RECTIFIERS | | | | | | | | | |
| RM1 5/3, RM2 6/9, RM3 7/6, RM4 13/6, RM5 19/6, 14A 100 19/6, 14A 97 19/6, 14A 100 19/6, LW7 17/6, 18RA 1-1-16-1 6/-, FC31 (14RA 1-2-8-3) 22/6, FC101 (14RA 1-2-8-2) 16/6. | | | | | | | | | |
| CATALOGUE | | | | | | | | | |
| Our 1960 catalogue is now available, please send 1/- in stamps for your copy. | | | | | | | | | |

ACOS MICROPHONES

Acos Mic 39/1. Crystal Stick Microphones for use as hand, desk or floor stand units for high quality recording, broadcasting and public address work. List Price £5.5.0. OUR PRICE 39/6. With floor stand adaptor 52/6. Postage 1/6.

BATTERY BUZZERS

3/9 each.

MORSE KEYS

3/- each.

DUBILIER TYPE "C"

controls 500 K. 6/6 each.

CO-AXIAL CABLE, semi-

airspaced 75 ohms. 6d. yard.

CRYSTAL CARTRIDGES.

Complete with stylus. Acos HE37/1, HGP59/5C, BSR, TC8. Collard Studio. All 15/6 each.

CHARGER

TRANSFORMERS

Tapped primary 200/240 v., secondary 3.5 v., 9 v. and 17 v. 1 amp. type 13/6; 2 amp. type 15/6; 4 amp. type 21/-; 6 amp. type 32/6. Postage 2/-.

HEATER

TRANSFORMERS

All 24v. input. 4v. 3 amp. 10/-; 6.3v. 1 amp. 6/9; 6.3v. 3 amp. 19/-; 12.6v. 2 amp. 5/9; 5v. 2 amp. 10/-; 2v. 3 amp. 8/3.

METERS. PANEL MOUNTING (Round) MOVING COIL.

Make F.S.D. Res. Scale Size Price
Weston (U.S.A.) 1mA 150 ohms 0-100 3 1/2in. 27/6
Weston (U.K.) 1mA 75 ohms 0-100 3 1/2in. 22/6
W.D. (U.K.) 5mA 0-0037 ohms 0-20 2in. 9/6
W.D. (U.S.A.) 500mA — 0-600 2 1/2in. 15/6

PUBLICATIONS

Wireless World Valve Data Book, 5/-, post 4d. Data TV Fault Finding Book, 5/-, post 4d. Mullard Circuits for Audio Amplifiers, 8/6, post 6d. Short Wave Receivers for the Beginner, 6/-, post 5d.

MICRO SWITCHES

3/9 each.

REGUNDED

Television Tubes, 12-month guarantee, 12 to 14in. £5.10.0. 15 to 17in. £6. Carriage and Insurance 10/- extra.

OUTPUT

TRANSFORMERS

Elston OT3 for Mullard 3-watt Amplifier. 25/-
Elstone OT6 Low Load, OT8 Normal Load, OT/ML Dist. Load, all 45/- and all for Mullard 5/10 amp.
Single ended 5000/3 ohms, 40mA, 4/6; 5000/3 ohms, 60mA, 5/9; 10000/3 ohms, 30mA, 4/6. Universal 18 Ratio Type 40mA, 5/9 each.

ACOS CRYSTAL

PICK-UPS

Turnover Head (2 sapphire stylus), 29/11. P.P. 2/6.

SCOTCH RECORDING

TAPE

1200ft Reels Standard 23/-
1800ft Reels Extra Play 37/6

RECTIFIERS

RM1 5/3, RM2 6/9, RM3 7/6, RM4 13/6, RM5 19/6, 14A 86 19/6, 14A 97 19/6, 14A 100 19/6, LW17 17/6, 18RA 1-1-16-1 6/-, FC31 (14RA 1-2-8-3) 22/6, FC101 (14RA 1-2-8-2) 16/6.

TERMS: Cash with order or

C.O.D. Postage and Packing charges extra; as follows: Orders value 10/- add 1/-, 20/- add 1/6; 40/- add 2/-; £5 add 3/- unless otherwise stated. Minimum C.O.D. fee and postage 3/-. For full terms of business see inside cover of our catalogue. Personal Shoppers 9 a.m. to 5 p.m. Mon. to Friday; Saturday 10 a.m. to 1 p.m.

ALPHA
- RADIO SUPPLY CO.



103 LEEDS TERRACE
WINTOUN STREET
LEEDS 7

Stern's "fidelity" TAPE EQUIPMENT

A SELECTION OF HIGH FIDELITY PORTABLE TAPE PREAMPLIFIERS

Adds "Hi-Fi" TAPE RECORDING
TO YOUR EXISTING AUDIO
INSTALLATION

IN ALL MODELS WE INCORPORATE THE TYPE "C" PREAMPLIFIER

AND OFFER IT COMPLETE IN CASE WITH

- (a) The new COLLARO "STUDIO" 3 Speed Deck **\$36.10.0**
H.P. Deposit £7.6.0, 12 months £213.6.
- (b) The COLLARO Mk. IV "Transcriptor" 3 Speed Deck **\$41.10.0**
H.P. Deposit £8.6.0, 12 months £30.11.
- (c) The new TRUVOX Mk. VI Tape Deck **\$43.10.0**
H.P. Deposit £8.14.0, 12 months £33.10.
- (d) The BRENNELL Mk. V 3 Speed Deck **\$51.10.0**
H.P. Deposit £10.8.0, 12 months £315.7.
- (e) The WEARITE MODEL 4A Tape Deck **\$61.0.0**
Deposit, £12.4.0, 12 months £49.5.

STERN'S MULLARD TYPE "C" TAPE PREAMPLIFIER-ERASE UNIT

INCORPORATING THE NEW FERROXCUBE POT CORE PUSH-PULL OSCILLATOR AND 3 SPEED TREBLE EQUALISATION by means of the latest FERROXCUBE POT CORE INDUCTOR. PRICES INCLUDING SEPARATE SMALL POWER SUPPLY COMPLETE KIT OF PARTS **\$14 0 0**
ASSEMBLED AND TESTED **\$17 0 0**

Dep. £3.8.0 and 12 of £14.11.

ALSO AVAILABLE EXCLUDING POWER SUPPLY UNIT FOR £11.15.0 and £14.10.0, respectively. WHEN ORDERING PLEASE STATE MAKE OF TAPE DECK TO BE USED. We present this "Hi-Fi" Preamplifier strictly to Mullard's specification incorporating ONLY NEW HIGH-GRADE COMPONENTS and the SPECIFIED NEW MULLARD VALVES. It comprises a COMPLETELY SELF-CONTAINED UNIT, neatly finished in Hammered Gold with a very attractively engraved PERSPEX FRONT PANEL.

FOR PERMANENT HIGH QUALITY INSTALLATIONS WE ALSO OFFER (excluding case)

- (a) The COLLARO "STUDIO" TAPE DECK and our Mullard Type "C" PREAMPLIFIER and Power Unit Assembled and Tested. **\$32.10.0**
H.P. Deposit £6.10.0, and 12 months £27.8.
- (b) As above but TYPE "C" PREAMPLIFIER supplied as complete KIT OF PARTS. **\$29.0.0**
- (c) The COLLARO Mk. IV TAPE DECK and the MULLARD TYPE "C" PREAMPLIFIER & Power Unit assembled, tested. **\$35.0.0**
H.P. Deposit £7, and 12 months £211.4.
- (d) As (c) but Type "C" as COMPLETE KIT OF PARTS. **\$32.0.0**
- (e) The TRUVOX Mk. VI DECK and the assembled Type "C" Preamplifier and Power Unit. **\$40.0.0**
H.P. Deposit £8.0.0, and 12 months £218.3.
- (f) As above but Type "C" as complete KIT OF PARTS. **\$36.10.0**
- (g) The BRENNELL Mk. V DECK and the assembled Type "C" PREAMPLIFIER and POWER UNIT. **\$46.0.0**
H.P. Deposit £9.4.0, and 12 months £37.6.
- (h) As (g) but Type "C" as complete KIT OF PARTS. **\$43.0.0**
- (i) The WEARITE 4A DECK with TYPE "C" assembled and tested. **\$56.0.0**
H.P. Deposit, £11.4.0 and 12 months £42.1.

(Carriage and Insurance on above quotes 10/- extra.)

PLEASE ENCLOSE S.A.E. WITH ALL CORRESPONDENCE.

YOU CAN BUILD A COMPLETE TAPE RECORDER

for **£36.0.0**

H.P. TERMS Deposit £7.4.0
12 months £212.10.

FOR THIS WE SUPPLY:

- * COMPLETE KIT OF PARTS TO BUILD THE HF/TR3 TAPE AMPLIFIER.
- * THE NEW COLLARO "STUDIO" TAPE DECK.
- * PORTABLE CARRYING CASE (as illustrated).
- * ROLA CELESTION 10in. x 6in. P.M. LOUDSPEAKER.
- * ACOS CRYSTAL MICROPHONE. 1.200ft. SPOOL E.M.I. TAPE.

For those who prefer another type of TAPE DECK we will supply precisely as above—but IN PLACE OF THE COLLARO "STUDIO" DECK—WE INCLUDE:

- (a) The Mk. IV COLLARO "TRANSCRIPTOR" DECK **\$39.15.0**
H.P. Deposit £8.0.0 and 12 months £218.2.
(£1 extra to wire up the Transcriptor Switch Banks.)
- (b) The New TRUVOX Mk. VI DECK **\$45.0.0**
H.P. Deposit £9.0.0, and 12 months £36.0.
(Carriage and Insurance on all above is 12/6 extra.)

For Constructors with their own Cabinet WE OFFER

- (a) COMPLETE KIT to build the HF/TR3 Amplifier, together with the COLLARO "STUDIO" DECK. **\$28.0.0**
- (b) As above but with HF/TR3 supplied ASSEMBLED and TESTED. **\$31.10.0**
H.P. Deposit £26.6.0, and 12 months £26.0.
- (c) COMPLETE KIT to build the HF/TR3, together with the Mk. IV COLLARO "TRANSCRIPTOR" TAPE DECK. **\$30.15.0**
(£1 extra if we are to wire up Deck Switch Banks.)
- (d) As above but HF/TR3 supplied ASSEMBLED and TESTED. **\$34.10.0**
- (e) COMPLETE KIT to build the HF/TR3, together with the NEW TRUVOX Mk. VI TAPE DECK. **\$36.0.0**
- (f) As above but HF/TR3 supplied ASSEMBLED and TESTED. **\$39.10.0**
H.P. Deposit £7.18.0, and 12 months £217.11.
- (g) COMPLETE KIT to build the HF/TR3 AMPLIFIER with the BRENNELL Mk. V TAPE DECK. **\$41.10.0**
- (h) As above but HF/TR3 supplied ASSEMBLED and TESTED. **\$45.0.0**
H.P. Deposit £9.0.0, and 12 months £36.0.

Carriage and Insurance on each above is 10/- extra. The Attractive PORTABLE CASE is available to accommodate the TRUVOX or COLLARO TAPE DECKS and we offer it, together with ROLA CELESTION 10 x 6in. LOUDSPEAKER—ACOS CRYSTAL MICROPHONE—and 1.200ft. SPOOL E.M.I. TAPE—ALL FOR £9.0.0. Carriage and Insurance 5/- extra.

WE HAVE THE NEW 2 SPEED TWIN TRACK TRUVOX Mk VI TAPE DECK IN STOCK £26.5.0

DEPOSIT: £5.5.0 and 12 MONTHS £118.6.


THE MODEL HF/TR3 TAPE AMPLIFIER

INCORPORATING 3-SPEED TREBLE EQUALISATION by means of the latest FERROXCUBE POT CORE INDUCTOR.

PRICE for COMPLETE KIT OF PARTS **\$12.15.0**

PRICE FULLY ASSEMBLED & TESTED **\$16.10.0**

HIRE PURCHASE. Deposit £3.6.6 and 12 monthly payments of £14.2. A very high-quality Amplifier based on the very successful TYPE "A" design completed in the MULLARD LABORATORIES. ONLY NEW HIGH-GRADE COMPONENTS are incorporated including MULLARD VALVES and a GILSON OUTPUT TRANSFORMER. Other features are—Magic Eye Recording hand indicator—Effective Tone Control—Monitoring and Extension Speaker Sockets—has own Power Supply and can be used as independent Amplifier for direct reproduction of Gram Records or from Radio Tuner. Overall size 11 x 8 x 6in. Can be supplied for use with Truvox—Collaro—Lane—Brennell or Motok Decks. Please specify which. Send S.A.E. for leaflet or 2/6 for complete Assembly Manual.

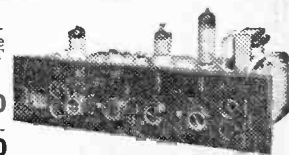

STERN RADIO LTD.

109 & 115 FLEET ST., LONDON, E.C.4

Telephone: FLEET STREET 1812/3/4

STERN S. MULLARD DESIGNS

Designed by MULLARD—presented by STERN strictly to specification

COMPLETE KIT OF PARTS—

MULLARD "5-10" MAIN AMPLIFIER

For use with the MULLARD 2-stage pre-amplifier with which an undistorted power output of up to 10 watts is obtained. We supply SPECIFIED COMPONENTS and NEW MULLARD VALVES, including PARMEKO MAINS TRANSFORMER and choice of the latest Ultra-Linear PARMEKO or the Partridge Output Transformer. PRICE COMPLETE KIT (PARMEKO Output Trans) **£10.00**

Alternatively we supply ASSEMBLED **£11.10.0** and TESTED.

ABOVE INCORPORATING PARTRIDGE OUTPUT TRANSFORMER, £1.6.0 EXTRA

MULLARD'S PRE-AMPLIFIER

ONE CONTROL UNIT

Employing two EF80 valves, and designed to operate with the MULLARD MAIN AMPLIFIERS, but also perfectly suitable for other makes.

PRICE, COMPLETE **£6.6.0** Alternatively we supply ASSEMBLED AND TESTED **£8.0.0**

Supplied strictly to MULLARD'S SPECIFICATION and incorporating

- Equalisation for the latest R.I.A.A. characteristic.
- Input for Crystal Pick-ups, and variable reluctance magnetic types.
- Input, (a) Direct from High Imp. Tape Head, (b) From a Tape Amplifier or Pre-amplifier
- Sensitive Microphone Channel. ● Wide range BASS and TREBLE Controls.

COMPLETE MULLARD "5-10"

The popular and very successful complete "5-10" incorporating Control Unit providing up to 10 watts high quality reproduction. Only Specified Components and new MULLARD VALVES are supplied including PARMEKO MAINS TRANSFORMERS and choice of the latest PARMEKO or PARTRIDGE ULTRA-Linear Output Transformers.

KIT OF PARTS **£11.10.0** OR ASSEMBLED **£13.10.0**

Alternatively we supply ASSEMBLED AND TESTED **£14.0.0**

DEPOSIT **£2.14.0**, 12 months at **£9.10.0**

ABOVE INCORPORATING PARTRIDGE OUTPUT TRANS. £1.6.0 extra

COMPLETE MULLARD "3-3"

THE IDEAL AMPLIFIER FOR A SMALL HIGH QUALITY INSTALLATION PROVIDING EXCELLENT REPRODUCTION OF UP TO 3 WATTS OUTPUT
COMPLETE KIT **£7.10.0** OR ASSEMBLED **£8.19.6**
OF PARTS and TESTED
(plus 6/6 coverage and insurance) H.P. Terms: Deposit **£2.0.0** and 8 months at **£1.0.0**. Complete to MULLARD'S SPECIFICATION including Mullard valves and a PARMEKO OUTPUT TRANSFORMER

STEREO "3-3"

MAIN AMPLIFIER

Comprises two "3-3" MULLARD MAIN AMPLIFIERS on one chassis and is designed to operate with our DUAL CHANNEL PRE-AMPLIFIER for both STEREO or MONAURAL operation. Its output power is 6 watts (3 watts per channel).

PRICE: COMPLETE KIT **£10.0.0**

Alternatively ASSEMBLED AND TESTED **£11.15.0**

H.P. Terms: Deposit **£2.7.0** and 12 months at **£17.4.**

!! RECORD PLAYERS !!

THE LATEST MODELS ARE IN STOCK MANY AT REDUCED PRICES

SEND S.A.E. FOR ILLUSTRATED LEAFLET

B.S.R. MONARCH UA8 4-speed mixer Autochanger with Crystal Pick-up.

£6.19.6

The NEW COLLARO MODEL RP594 4-speed Single Record Player. Studio Cartridge.

£9.18.9

The COLLARO "CONQUEST" 4-speed Autochanger. Studio Pick-up.

£7.10.0

The COLLARO 4-speed Single Record Player. Studio Pick-up.

THE NEW B.S.R. Model UA12 in Stock. A4 "SPEED" MIXER AUTOCHANGER. **£6.15.0**

UA12 also available incorporating the B.S.R. STEREO UA12 plays L.P. and 78 Records. **£8.7.6**

GARRARD MODEL TA/MK.11 4-Speed Player fitted high output Crystal Pick-up. **£10.10.0**

GARRARD MODEL RC/12/4. Autochanger 4-Speeds. **£8.10.0**

High output. Crystal Pick-up. **£10.0.0**

Carriage and Insurance on each above, 5/- extra.

SPECIAL PRICE REDUCTIONS

(c) The KIT OF PARTS to build both the "5-10" Main Amplifier and the 2-valve PRE-AMP CONTROL UNIT **£15.15.0**

(d) The "5-10" and the 2-stage PRE-AMP both ASSEMBLED and TESTED H.P. Dep. **£316.0** and 12 months of **£17.8.** **£18.18.0**

(e) The KIT OF PARTS to build the DUAL-CHANNEL "3-3" AMPLIFIER and the DUAL-CHANNEL PRE-AMPLIFIER CONTROL UNIT **£21.10.0**

(f) The DUAL-CHANNEL "3-3" AMPLIFIER and the DUAL-CHANNEL PRE-AMPLIFIER CONTROL UNIT BOTH ASSEMBLED and TESTED **£25.0.0**

H.P. Terms: Deposit **£5** and 12 months of **£1.16.8**

(g) The KIT OF PARTS to build one "5-10" MAIN CHANNEL and the DUAL-CHANNEL PRE-AMP CONTROL UNIT **£21.10.0**

(h) ONE "5-10" AMPLIFIER and the DUAL-CHANNEL PRE-AMPLIFIER both ASSEMBLED and TESTED **£25.0.0**

H.P. Terms: Deposit **£5**, 12 months of **£1.16.8**

(i) KIT OF PARTS to build Two "5-10" MAIN AMPLIFIERS (incorporating Parmeko Output Transformers) and the DUAL-CHANNEL PRE-AMPLIFIER CONTROL UNIT **£31.0.0**

(j) TWO "5-10" AMPLIFIERS and the DUAL-CHANNEL PRE-AMPLIFIER CONTROL UNIT BOTH ASSEMBLED & TESTED **£36.0.0**

H.P. Terms: Deposit **£7.4.0**, 12 months **£2.12.0**

Carriage and Insurance 7/6 extra.

Prices quoted are subject to **£1.6.0** extra for Partridge Transformer.

STEREO DUAL CHANNEL PRE-AMPLIFIER

This model incorporates two Mullard 2-valve Pre-Amplifiers combined into a Single Unit enabling it to be used for both STEREO or MONAURAL operation. It is designed primarily to operate with our range of MULLARD MAIN AMPLIFIERS but will also operate equally well with any make of Amplifiers requiring an input of 250 mvolts.

COMPLETE KIT **£12.10.0** ASSEMBLED **£15.0.0**

OF PARTS and TESTED

Operates equally well for MONAURAL only operation with one "5-10" Main Amplifier to which the second Main Amplifier can at any time be added, thus very easily providing for both STEREO or MONAURAL reproduction.

THE ASSEMBLY MANUAL is available for 3/-.

COMPLETE STEREO AMPLIFIER

A thoroughly recommended

Mullard design that very effectively

meets the many requests for a

low-priced but good quality

DUAL CHANNEL STEREO

AMPLIFIER. Output power is 4 watts

from STEREO or MONAURAL

gram inputs. PRICE: COMPLETE

KIT OF PARTS **£8.10.0**

ALTERNATIVELY ASSEMBLED AND TESTED **£10.10.0**

EMBEDDING

! RADIOGRAM CHASSIS !

and V.H.F. RADIO TUNING UNITS

WE HAVE THE COMPLETE RANGE OF ARMSTRONG and

DULCI high quality replacement Chassis IN STOCK.

Descriptive leaflets are available—enclose S.A.E.

Please enclose S.A.E. for DESCRIPTIVE LEAFLETS

COMPLETE ASSEMBLY MANUALS are available

at 1/6 each.

STERN RADIO LTD.



Stern's "fidelity" TAPE RECORDERS

**BEFORE YOU BUY
—YOU SHOULD
HEAR THESE**

**RECORDERS. THEY ARE COMPARABLE
TO THE MUCH HIGHER-PRICED MODELS**

There are no better value for money Tape Recorders on the market—if you can't call and hear them, send S.A.E. for fully descriptive leaflets.


MODEL CR3/S Incorporates the New COLLARO "STUDIO" TWIN TRACK 3-Speed Deck **£41.0.0**
H.P. Terms: Deposit **£8.4.0** and 12 months of **£3.0.2**.

MODEL CR3/T Incorporates the very popular 3-Speed COLLARO Mk. IV "TRANSCRIPTOR" Deck which has both upper and lower tape tracks. **£49.10.0**
H.P. Terms: Deposit **£9.18.0** and 12 months of **£3.12.7**.

MODEL TR3/Mk. VI. Incorporates the New TRUVOX Mk. VI TWIN TRACK 2-speed Tape Deck **£49.10.0**
H.P. Terms: Deposit **£9.18.0** and 12 months of **£3.12.7**.

All prices quoted provide for the COMPLETE RECORDER including CRYSTAL MICROPHONE and 1,200 ft. Spool of Tape.

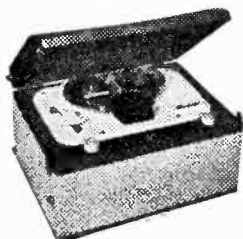Each Model incorporates the highly successful HF/TR3 Amplifier (described opposite) thus ensuring truly "Hi-Fi" record and playback facilities.



and NOW WE INTRODUCE

● The MODEL HF/G2P TAPE PREAMPLIFIER

The Ideal "Link" to add High Quality Tape Recording facilities to existing Audio Installations and the

● The MODEL HF/G2A TAPE AMPLIFIER

Designed to our usual High Technical Standard. Being based on the very successful Mullard Tape Designs. They incorporate MULLARD VALVES and only HIGH GRADE COMPONENTS

... AS A RESULT WE PRESENT...

**TWO UNITS METICULOUSLY MATCHED TO CORRECTLY OPERATE
The NEW GARRARD "MAGAZINE" TAPE DECK**

Both Units form an entirely new "Easy to handle" presentation, each is completely self contained with Power Supply (Loudspeaker Amplifier HF/G2A only), and all INPUT and OUTPUT sockets incorporated on the chassis, which itself is constructed to allow for direct attachment to the tape deck. Thus the tape deck with the Amplifier (or Preamplifier fixed to it) form ONE COMPLETELY SELF-CONTAINED WORKING UNIT which requires only screwing into a Cabinet and Connecting to the Mains supply. As is usual with GARRARD products this Tape Deck is a Precision Engineered Unit of Excellent Quality operating two tracks at 3 in./sec. speed. It is the "Easiest to Handle" Tape Deck, having only two controls and incorporates the new Instantaneous Tape Loading Magazine which makes tape loading as simple as putting on a Record.

WE OFFER THEM AS FOLLOWS:

- Complete Portable TAPE RECORDER (as illustrated).
- Complete Portable TAPE PREAMPLIFIER (similar to illustration).
- HF/G2A AMPLIFIER incorporated on TAPE DECK. Both ASSEMBLED and TESTED. READY FOR USE.
- HF/G2P PREAMPLIFIER incorporated on TAPE DECK. BOTH ASSEMBLED and TESTED. READY FOR USE.
- THE ASSEMBLED and TESTED HF/G2A AMPLIFIER only.
- THE ASSEMBLED and TESTED HF/G2P PREAMPLIFIER only.

OVERALL PERFORMANCE IS REALLY EXCELLENT BUT OUR PRICES ARE GOING TO BE REMARKABLY LOW FOR SUCH HIGH QUALITY EQUIPMENT.

A SPECIAL CASH ONLY OFFER !!

This very attractive PORTABLE AMPLIFIER CASE together with a good quality GRAM AMPLIFIER and a matched F.M. SPEAKER.

ALL for ONLY **£8.7.6** (Plus 7/6 Carr. & Ins.)

The Amplifier consists of a 2-stage design incorporating 3 modern B.V.A. valves and has separate BASS and TREBLE CONTROLS. The Portable Case will also accommodate almost any make of Autochanger and is attractively finished in Mushroom Grey Relexine. WE ALSO SUPPLY SEPARATELY—

(a) The 2-stage (plus Rectifier) AMPLIFIER **£4.2.6**

(b) THE PORTABLE CARRYING CASE **£3.17.6**

(c) F.M. SPEAKER **18/9** Carriage and Insurance 4/- extra.



STERN'S MK. II "fidelity" F.M. TUNING UNIT

PRICE **£14.5.0** (Plus 5/- Carr. and Ins.)

HIRE PURCHASE. Deposit **£2.17.0** and 12 Monthly Payments of **£1.0.11**

Incorporates the latest MULLARD PERMEABILITY TUNING HEART and the corresponding MULLARD VALVE LINE-UP. A really first-class Tuner, very attractively presented and comparable to many offered at much higher prices. Power consumption is only 1.5 amps at 6.3 volts and 25 m.w. at 250 volts.


HOME CONSTRUCTORS! YOU CAN BUILD THIS TUNING UNIT FOR ONLY **£10.10.0** (Plus 5/- Carr. & Ins.) Please send S.A.E. for fully descriptive leaflet, or the Assembly Manual is available for 1/6.



THE "ADD-A-DECK" incorporating the W.B. "MONARDECK" and Matched Preamplifier

Carriage and Insurance, 10/-
Deposit **£3.12.0** **£17.17.0**
12 mths. **£1.6.2**

Designed to operate through the Pick-up Sockets of the standard RADIO RECEIVER through which first-class results are obtained. It consists of a Twin Track Tape Deck, incorporating matched Preamplifier, and operates at 3 in./sec. speed. Supplied fully tested and completely assembled on an attractive wood plinth, and only requires connections to the mains supply and the Pick-up Sockets, for which purposes "floating" leads are incorporated.

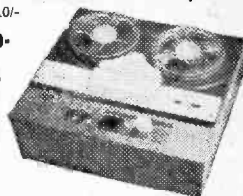

"Hi-Fi" LOUDSPEAKERS WE HAVE IN STOCK A COMPLETE RANGE BY GOODMANS—WHARFEDALE—W.B. Illustrated and Priced Leaflets on request.

HOME CONSTRUCTOR

A RANGE OF "EASY TO ASSEMBLE" PREFABRICATED CABINETS. Designed by the W.B. "STENTORIAN" COMPANY for "Hi-Fi" Loudspeaker systems or to accommodate high-quality equipment. The acoustically designed Bass Reflex Cabinets containing the very successful "Stentorian" Speakers give really first-class reproduction and are well recommended. Models are also available to accommodate high-quality Amplifiers, Preamplifiers, Tuning Units, Record Players, etc. All models are very easily assembled, in fact, only a screwdriver is required. Fully illustrated leaflets are available, including specifications of the STENTORIAN LOUDSPEAKERS.

109 & 115 FLEET ST., LONDON, E.C.4


Telephone: **FLEET STREET 5812/3/4**

PLEASE ENCLOSE S.A.E. WITH ALL ENQUIRIES.

EASY AS A.B.C. TO BUILD

The new, exciting De Luxe "Gold Star" Pocket Radio in beautiful moulded plastic case—
This model is a highly sensitive, self-contained set covering all medium waves. Uses modern miniature "button-base" valve and specially designed high efficiency coil. Exceptionally easy to build from our step-by-step plans—the case is supplied ready drilled! Size of radio only 4 1/4 in. x 2 1/4 in. x 1 1/4 in. —and batteries fit inside. We can supply all parts including case, detachable aerial, instruction book, wire, screws, etc., for only 37/6, plus 2/- Post and Packing. C.O.D. 2/- extra. (Parts sold separately, priced parts list 1/6.)

37/6

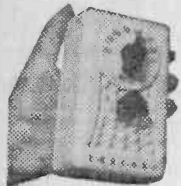


2/- extra. (Parts sold separately, priced parts list 1/6.)



29/6

Our engineers have designed a novel Wrist-Watch Radio using latest Transistor Techniques. Size only 1 1/4 in. x 1 1/4 in. x 1 1/4 in. "Feather-weight"—yet gives clear, crisp, personal-phone reception over all medium waves. Tiny battery inside lasts months at costs 5d. No Snags, anyone can build it in an hour or two using our pictorial step-by-step simple plans. All parts supplied (including case and strap) for only 29/6 (add 2/6 Post, etc.). C.O.D. 2/- extra. (All parts sold separately, priced parts list 1/6.) Send Now!

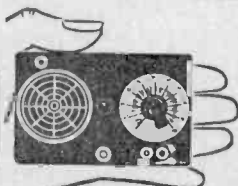

29/6

Can Be Built for 47/6. Build this exceptionally sensitive high efficiency personal phone radio. Uses unique assembly system and can be built by anyone without any radio knowledge whatever in 45 minutes. Handsome black-crackle steel case with specially made black and gold dial with stations printed. Size of radio only 6 1/4 in. x 5 1/4 in. x 3 1/4 in. Covers all medium and long waves. H.T. consumption only 1 to 1.5 mA. Ideal for Bedroom, Garden, Holiday, etc. BUILD THE "SKY-ROMA" NOW! Total building cost—everything down to the last nut and bolt. 47/6 (Postage, etc., 2/-)—with full set of clear, easy-to-follow plans. (Parts sold separately. Priced parts list and plans 1/6.) C.O.D. 2/- extra.



47/6



29/6

The sensational "Silvertone" model! A highly compact self-contained miniature "button-base" valve pocket radio at absolute "rockbottom" building cost! Covers all the medium waves with the very latest circuitry bringing in stations from all over Europe—without fuss. Easy as A.B.C. to assemble, using our step-by-step instruction manual. Size only 4 1/4 in. x 2 1/4 in. x 1 1/4 in.—a fascinating little pocket radio. We can supply all the parts including beautiful two-tone case, detachable aerial, instruction book, screws, wire, etc., for only 29/6 (plus 2/- post and packing). C.O.D. 2/- extra. (Parts sold separately, priced parts list 1/6.)

THIS TRANSISTOR SET Can Be Built For Only 29/6. The "Sky-Scout" Pocket two-stage transistor set, size only 1 1/4 in. x 3 1/4 in. x 4 1/4 in. Covers all medium waves and works entirely off tiny penlight battery which costs 6d. and fits inside case. All parts tested before despatch. Can be built for 29/6, plus 2/- Post and Packing. INCLUDING CASE, TRANSISTOR, STEP-BY-STEP PLANS FOR ABSOLUTE BEGINNERS, nuts, bolts, etc. (C.O.D. 2/- extra.) Parts sold separately, priced parts list and plans 1/6. VERY SIMPLE TO BUILD.




17/6

This amazing "Tiny-Tim" model—no larger than a matchbox—costs nothing to run—ever! No batteries! No Valves! No complete electricity! Will never run down or burn out. Uses the latest TRANSISTOR TYPE GERMANIUM DIODE, receives local stations anywhere—without extra aerial. Clear, Crisp Tone. No snags, anyone can build it within an hour using our step-by-step instruction book, etc., for only 17/6, plus 2/- Post and Packing (C.O.D. 2/- extra). (Parts sold separately, priced parts list 1/6.)


Choice of beautiful veneered walnut cabinet or ivory bakelite. This is the

107/6

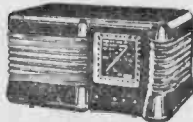

lowest possible price consistent with high quality. No radio knowledge whatever needed can be

built by anyone in 2-3 hours, using our very simple, easy-to-follow diagrams. The terrific new circuit of the "Ocean-Hopper" covers all medium and long waves, has razor-edge selectivity and exceptionally good tone. Price also includes ready drilled and punched chassis, set of simple-to-follow plans—before despatch! Uses standard octal-base valves. (Low running costs—approximately 18 watts.) Size 12 in. x 8 in. x 5 in. Build this long-range powerful midget NOW. TOTAL BUILDING COST INCLUDING PLANS, ETC., 25/7.3. (Post and Packing 3/6.) Parts sold separately. Priced parts list and plans 1/9. C.O.D. 2/- extra.

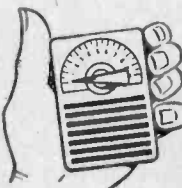

45/-

TWO-TRANSISTOR POCKET SET. Can Be Built for 45/-. BUILD THE "SKY-ROMA" NOW! VEST-POCKET TWO TRANSISTOR RADIO which gives a superb performance and is highly sensitive. Weight under 7 ozs.—yet it is a THREE-STAGE receiver covering all medium waves, working entirely off a "penlight" battery. Every part tested before despatch! SPECIAL STEP-BY-STEP PLANS FOR ABSOLUTE BEGINNERS. Total building cost including case, transistors, etc.—everything down to the last nut and bolt—ONLY 45/- with plans. Postage, etc., 2/-. (C.O.D. 2/- extra.) (Parts sold separately. Priced parts list and plans 1/6.) RUSH YOUR ORDER TODAY!



39/6

Anyone can build this beautiful precision Pocket Radio in an hour or two. No knowledge whatever needed. Our simple pictorial plans take you step-by-step! Remarkably sensitive—covers all medium waves, inc. Luxembourg, Home, Light. Size only 2 1/4 in. x 3 1/4 in. x 5 1/4 in.—Not a Tow! But a Real, Personal-phone, Valve Radio With Detachable Aerial! IDEAL FOR BEDROOM, GARDEN, etc. We supply ALL parts necessary, together with plans, etc., for the special price of 39/6, plus 2/6 post and packing. (C.O.D. 2/- extra.) BUILD YOURS NOW! (All parts sold separately, priced parts list 1/9.) Send Today! Money refunded if parts returned intact within 7 days



CONCORD ELECTRONICS
210, Church Road, Hove, Sussex

Dept. PW17

Orders receive prompt attention. Cheques accepted. Cash on delivery 2/- extra. Please print name and address in block letters. Suppliers to Schools, Universities, Government and Research Establishments. Complete range of components and valves stocked. Regret no C.O.D. abroad. DEMONSTRATIONS DAILY AT WORKS.

TUBES

DIRECT FROM OUR FACTORY New low prices
New top quality guns. ALL GUARANTEED

Carriage and Insurance 12/6
CRM92, MW22-7, MW22-14, MW22-14C,
MW22-17, MW22-18
12KPA, 121K, C12B, CRM121, CRM121A,
CRM121B, CRM122, CRM123, MW31-14C,
MW31-16, MW31-18, MW31-74
141K, 7201A, C14FM, CRM141, CRM142,
CRM143, MW36-34, MW36-44
17ASP4, 171K, AW36/21, C17FM, CRM171,
CRM172, MW43-64, MW43-69
7401A, AW43-80, C14BM, C17BM, CRM151,
CRM152A, CRM152B, CRM153, CRM173,
MW43-80, MW41-1
AW58-80, CRM212, MW53-20, MW53-80

| 8 MONTHS REVAUCUED | 12 MONTHS REGUNNED | 12 MONTHS NEW TYPES |
|-----------------------|-----------------------|---------------------------|
| \$2-10 | \$4-10 | |
| \$2-15 | \$4-10 | MW31/74 \$4-15 |
| \$3-5 | \$5-5 | MW36/34 \$7-19 |
| \$3-15 | \$5-15 | MW43/64 \$8-10 |
| \$4-5 | \$6-5 | |
| \$5-10 | \$8 | |

NEW 108K (Equiv. 3/16) TUBES SPECIAL OFFER: 49/-
PLEASE NOTE: Many other types not listed available. S.A.E. enquiries.

13 CHANNEL TV's

TABLE MODELS, FAMOUS MAKES. Complete with all valves and tubes. These sets are unequalled in value due to huge purchase direct from source. They are untested and are not guaranteed to be in working order. Carr. Free.

12" — £3.19.

14" — £7.10.

17" — £12.10.

12" 5 CHANNEL TV's 55/-

Complete Table Models as Above. Carr. Free.

B.S.R. MONARDECK TAPE DECKS \$9.10.0.
12in. TV's 5 channel table models including speaker, line transformer, cabinet. Top makes requiring only valves and tube to complete, your choice if available (carr. 4/-). (Or 28 per dozen, carr. free.) **15/-**
14in. TV's 5 channel as above (carr. 4/-). **35/-**

100 CONDENSERS 10/-
A must for your spare box. A well-balanced assortment of miniature silver mica and ceramic condensers. 3-10,000 P.F. List value over £3.
CO-AX standard and low loss, 25 yds, 12/6. 50 yds, 22/6. 100 yds, 42/6.
Co-ax. Plugs 1/3. Wall outlet boxes, 3/6.

100 RESISTORS assortment 7/6
standard and low loss, 25 yds, 12/6. 50 yds, 22/6. 100 yds, 42/6.
Co-ax. Plugs 1/3. Wall outlet boxes, 3/6.

SINGLE RECORD PLAYERS
COLLARO 4-speed 4548 ... £6 19 0
GARRARD 4-speed 48P ... £7 7 6
GARRARD 4-speed TA MKII ... £8 19 0
GARRARD 4-speed 48P ... £17 15 0
10 RECORD AUTOCHANGERS
GARRARD RC75A Senior ... £7 19 0
GARRARD RC120D MKII ... £9 7 6
GARRARD RC121A MKII ... £9 19 0
Carr. and Pack. 4/-.

INFRA RED HEATERS

Under Half Price. Super finish. Choice of
800 w. 1,200w. 2,000w. 59/- each

PICK-UP CARTRIDGES
ACOS 22/6 POWER POINT 18/6
STEIG AND REUTER 15/- SONOTONE 17/6

PORTABLE RECORD PLAYERS
Collaro 4-speed auto-changer, 24 watt high gain amplifier. Super-two-13 Gns.
Or case only 59/-. 21-watt Amplifier complete on battle with Speaker, £310/-.

STEREO SINGLE PLAYERS
4-speed. Famous make. **£6-19-0**
Stereo head. Unreplaceable.

VALVES ALL GUARANTEED 3 MONTHS
PL81 SOILED AMAZING 5/-
VALUE AT ONLY

EY51 SHORT 5/- U25 SHORT 7/-
ENDS

DIODES General purpose, famous make, 9d. 8/- doz. GEX44 type, 3/6.

B.S.R. AUS AUTOCHANGERS, £6.15.0. **RED TRANSISTORS 4/6**

I.P.F. L.F. and Output up to 800 kc/s. (48/- dozen). WHITE SPOT. R.F. and I.F. 2.5 Me/s, 6/8 (60/- per dozen). XA103, XA104, 17/6; XB104, 10/-; GET15, 25/-.

RECTIFIERS For Chargers, selenium, full wave bridge, 12 volt 3-4 amps, 9/6. (Carr. 1/-) 25 per doz. 250 v. 80 ma. 5/- RM1, 6/8; RM2, 8/-; RM3, 9/-; RM4, 15/6; RM5, 21/-; 14A85, 17/-; 14A97, 23/-; 14A100, 25/-; 16RC1-16-1, 7/9; 18RA1-1-6-1, 7/9; 18RD2-2-6-1, 14/-; 14RA1-2-8-2, 17/-; 14RA1-2-8-3, 20/-.

COLLARD CONQUEST CHANGERS £7.10.0
PM SPEAKERS 3 ohms, top makes, performance guaranteed.
8in. 8/- 5in. 11/- 10in. 13/-
6in. 7/4 7/4 10/6

CONNECTING WIRE
25 FT. P.V.C. Insul., excellent (5 coils, diff. colours, 4/8)
CRTs ECR30 (VCR139A), 15/-; 5FP3, 19/-; ECR35 (VCR138), 9/-; VCR97, 12/6

TRANSCRIPTION TAPE DECKS £13-15-0

VALVES BY RETURN OF POST

10% DISCOUNT SPECIAL OFFER
on any SIX VALVES marked in black type (15% in dozen). Post: 1 valve, 6d.; 2-11, 1/-.

| | | | | | | | | | | | | | | | | | | | | | | | |
|-------|------|-------|------|--------|------|------|------|--------|------|--------|------|-------|------|------|------|------|------|-----------|------|-------|------|-------|------|
| 024 | 5/8 | 6AT6 | 7/- | 6J7GT | 7/6 | 6XG5 | 5/6 | 12E1 | 12/6 | 42 | 7/6 | DAF96 | 8/3 | EC81 | 6/- | EL91 | 4/8 | N108 | 18/- | T41 | 7/6 | VC181 | 9/- |
| 1A6GT | 5/8 | 6AU6 | 5/6 | 6K6GT | 6/6 | 6XG7 | 6/6 | 12J5GT | 3/6 | 43 | 7/6 | DF33 | 9/9 | EC82 | 6/6 | EM34 | 8/6 | N152 | 10/6 | TH30C | 12/6 | VC182 | 11/8 |
| 1A7GT | 12/6 | 6B7 | 6/6 | 6K7 | 5/9 | 6Z4 | 9/- | 12K7GT | 6/6 | 50C5 | 9/9 | DF91 | 8/9 | EC83 | 7/6 | EM80 | 9/6 | U1 | 4/8 | U14 | 8/6 | VC183 | 13/6 |
| 1C5GT | 11/8 | 6B8G | 3/6 | 6K7G | 2/3 | 7A7 | 10/6 | 12K8GT | 12/6 | 50L6GT | 9/3 | DF96 | 8/3 | EC84 | 8/9 | EM81 | 9/3 | U18 | 8/6 | U18 | 8/6 | VC184 | 14/6 |
| 1D5 | 9/6 | 6B8A | 6/6 | 6K7GT | 5/- | 7B5 | 12/6 | 12K9GT | 8/6 | 53KU | 10/6 | DH83 | 6/6 | EC85 | 9/3 | EM84 | 9/3 | FAB8011/- | U22 | 6/8 | U22 | 7/9 | |
| 1D6 | 9/6 | 6B8B | 6/6 | 6K8 | 6/- | 7B6 | 9/6 | 12K9GT | 8/6 | 54KU | 8/9 | DH76 | 6/6 | EC86 | 10/3 | EM85 | 10/6 | PC84 | 7/9 | U24 | 7/8 | U24 | 7/9 |
| 1H8GT | 9/6 | 6B8G6 | 12/6 | 6K8GT | 11/- | 7B7 | 7/3 | 12K9GT | 5/6 | 61SP1 | 11/- | DH77 | 7/7 | EC87 | 9/9 | EN31 | 16/- | PC85 | 9/3 | U25 | 12/6 | U25 | 12/6 |
| 114 | 3/6 | 6B8H | 6/6 | 6K85 | 7/6 | 7C5 | 7/6 | 12K9GT | 5/6 | 615 | 8/- | DK32 | 12/6 | EC88 | 14/- | EY61 | 6/6 | PC88 | 19/- | U26 | 12/6 | U26 | 14/6 |
| 1LD5 | 3/6 | 6B8J | 6/6 | 6L1 | 12/6 | 7C6 | 7/3 | 12K9GT | 5/6 | 617 | 8/6 | DK91 | 8/6 | EC89 | 14/- | EY61 | 6/6 | PC88 | 19/- | U26 | 12/6 | U26 | 14/6 |
| 1LN6 | 4/6 | 6B8W | 10/6 | 6L6 | 9/6 | 7C7 | 7/6 | 12K9GT | 5/6 | 618 | 7/6 | DK92 | 8/6 | EC90 | 14/- | EY61 | 6/6 | PC88 | 19/- | U26 | 12/6 | U26 | 14/6 |
| 1N6GT | 9/6 | 6B8W | 8/6 | 6L6G | 7/6 | 7C7 | 7/6 | 12K9GT | 5/6 | 619 | 8/6 | DK96 | 8/6 | EC91 | 14/- | EY61 | 6/6 | PC88 | 19/- | U26 | 12/6 | U26 | 14/6 |
| 1R5 | 8/6 | 6B8W | 8/6 | 6L7 | 9/- | 7K7 | 6/6 | 12K9GT | 5/6 | 619A | 5/6 | DK96 | 8/6 | EC91 | 14/- | EY61 | 6/6 | PC88 | 19/- | U26 | 12/6 | U26 | 14/6 |
| 184 | 8/6 | 6B8X | 9/6 | 6L8 | 9/- | 7K7 | 10/6 | 12K9GT | 5/6 | 619AV | 5/6 | DK96 | 8/6 | EC91 | 14/- | EY61 | 6/6 | PC88 | 19/- | U26 | 12/6 | U26 | 14/6 |
| 1T5 | 6/- | 6C4 | 3/6 | 6L19 | 11/6 | 7T7 | 9/6 | 12K9GT | 5/6 | 619B | 5/6 | DK96 | 8/6 | EC91 | 14/- | EY61 | 6/6 | PC88 | 19/- | U26 | 12/6 | U26 | 14/6 |
| 1T5 | 4/6 | 6C5 | 3/6 | 6L19 | 11/6 | 7T7 | 9/6 | 12K9GT | 5/6 | 619B | 5/6 | DK96 | 8/6 | EC91 | 14/- | EY61 | 6/6 | PC88 | 19/- | U26 | 12/6 | U26 | 14/6 |
| 2D81 | 4/6 | 6C8 | 3/6 | 6L19 | 11/6 | 7T7 | 9/6 | 12K9GT | 5/6 | 619B | 5/6 | DK96 | 8/6 | EC91 | 14/- | EY61 | 6/6 | PC88 | 19/- | U26 | 12/6 | U26 | 14/6 |
| 3A4 | 5/6 | 6C9 | 3/6 | 6L19 | 11/6 | 7T7 | 9/6 | 12K9GT | 5/6 | 619B | 5/6 | DK96 | 8/6 | EC91 | 14/- | EY61 | 6/6 | PC88 | 19/- | U26 | 12/6 | U26 | 14/6 |
| 3Q4 | 7/6 | 6C8G | 15/6 | 6N7 | 6/6 | SD3 | 3/6 | 20P1 | 11/6 | 807A | 5/- | DL94 | 7/6 | EC92 | 12/6 | GTIC | 7/6 | PC85 | 4/6 | U26 | 5/6 | U26 | 12/6 |
| 3Q6GT | 8/6 | 6C8H | 9/6 | 6P1 | 14/- | 10C1 | 11/- | 20P2 | 14/- | 807A | 5/- | DL96 | 8/6 | EC93 | 12/6 | GTIC | 7/6 | PC85 | 4/6 | U26 | 5/6 | U26 | 12/6 |
| 3S4 | 8/6 | 6D1 | 9/6 | 6P25 | 9/- | 10C2 | 13/6 | 20P2 | 14/- | 807B | 5/- | DL96 | 8/6 | EC93 | 12/6 | GTIC | 7/6 | PC85 | 4/6 | U26 | 5/6 | U26 | 12/6 |
| 3V4 | 7/6 | 6D2 | 9/6 | 6P25 | 9/- | 10C2 | 13/6 | 20P2 | 14/- | 807B | 5/- | DL96 | 8/6 | EC93 | 12/6 | GTIC | 7/6 | PC85 | 4/6 | U26 | 5/6 | U26 | 12/6 |
| 1BR40 | 11/- | 6D3 | 9/6 | 6P25 | 9/- | 10C2 | 13/6 | 20P2 | 14/- | 807B | 5/- | DL96 | 8/6 | EC93 | 12/6 | GTIC | 7/6 | PC85 | 4/6 | U26 | 5/6 | U26 | 12/6 |
| 5V4G | 5/6 | 6D6 | 4/6 | 6P25GT | 9/3 | 10P9 | 10/3 | 25L6GT | 9/4 | 5763 | 10/3 | EA42 | 3/6 | EC94 | 12/6 | GTIC | 7/6 | PC85 | 4/6 | U26 | 5/6 | U26 | 12/6 |
| 5V4G | 9/6 | 6P1 | 9/6 | 6P25GT | 9/3 | 10P9 | 10/3 | 25L6GT | 9/4 | 5763 | 10/3 | EA42 | 3/6 | EC94 | 12/6 | GTIC | 7/6 | PC85 | 4/6 | U26 | 5/6 | U26 | 12/6 |
| 5Y3G | 6/- | 6P8G | 6/6 | 6P25GT | 9/3 | 10P9 | 10/3 | 25L6GT | 9/4 | 5763 | 10/3 | EA42 | 3/6 | EC94 | 12/6 | GTIC | 7/6 | PC85 | 4/6 | U26 | 5/6 | U26 | 12/6 |
| 5Y3GT | 6/6 | 6P8G | 6/6 | 6P25GT | 9/3 | 10P9 | 10/3 | 25L6GT | 9/4 | 5763 | 10/3 | EA42 | 3/6 | EC94 | 12/6 | GTIC | 7/6 | PC85 | 4/6 | U26 | 5/6 | U26 | 12/6 |
| 5Z4G | 9/6 | 6P8G | 6/6 | 6P25GT | 9/3 | 10P9 | 10/3 | 25L6GT | 9/4 | 5763 | 10/3 | EA42 | 3/6 | EC94 | 12/6 | GTIC | 7/6 | PC85 | 4/6 | U26 | 5/6 | U26 | 12/6 |
| 5Z4GT | 11/- | 6P13 | 6/6 | 6P25GT | 9/3 | 10P9 | 10/3 | 25L6GT | 9/4 | 5763 | 10/3 | EA42 | 3/6 | EC94 | 12/6 | GTIC | 7/6 | PC85 | 4/6 | U26 | 5/6 | U26 | 12/6 |
| 6A7 | 11/- | 6P14 | 9/6 | 6P25GT | 9/3 | 10P9 | 10/3 | 25L6GT | 9/4 | 5763 | 10/3 | EA42 | 3/6 | EC94 | 12/6 | GTIC | 7/6 | PC85 | 4/6 | U26 | 5/6 | U26 | 12/6 |
| 6A8G | 9/6 | 6P15 | 9/6 | 6P25GT | 9/3 | 10P9 | 10/3 | 25L6GT | 9/4 | 5763 | 10/3 | EA42 | 3/6 | EC94 | 12/6 | GTIC | 7/6 | PC85 | 4/6 | U26 | 5/6 | U26 | 12/6 |
| 6A8GT | 13/6 | 6P16 | 9/6 | 6P25GT | 9/3 | 10P9 | 10/3 | 25L6GT | 9/4 | 5763 | 10/3 | EA42 | 3/6 | EC94 | 12/6 | GTIC | 7/6 | PC85 | 4/6 | U26 | 5/6 | U26 | 12/6 |
| 6A8B | 8/6 | 6P17 | 9/6 | 6P25GT | 9/3 | 10P9 | 10/3 | 25L6GT | 9/4 | 5763 | 10/3 | EA42 | 3/6 | EC94 | 12/6 | GTIC | 7/6 | PC85 | 4/6 | U26 | 5/6 | U26 | 12/6 |
| 6A7 | 4/6 | 6P18 | 9/6 | 6P25GT | 9/3 | 10P9 | 10/3 | 25L6GT | 9/4 | 5763 | 10/3 | EA42 | 3/6 | EC94 | 12/6 | GTIC | 7/6 | PC85 | 4/6 | U26 | 5/6 | U26 | 12/6 |
| 6A8G | 4/6 | 6P19 | 9/6 | 6P25GT | 9/3 | 10P9 | 10/3 | 25L6GT | 9/4 | 5763 | 10/3 | EA42 | 3/6 | EC94 | 12/6 | GTIC | 7/6 | PC85 | 4/6 | U26 | 5/6 | U26 | 12/6 |
| 6A8G | 4/6 | 6P20 | 9/6 | 6P25GT | 9/3 | 10P9 | 10/3 | 25L6GT | 9/4 | 5763 | 10/3 | EA42 | 3/6 | EC94 | 12/6 | GTIC | 7/6 | PC85 | 4/6 | U26 | 5/6 | U26 | 12/6 |
| 6A8G | 4/6 | 6P21 | 9/6 | 6P25GT | 9/3 | 10P9 | 10/3 | 25L6GT | 9/4 | 5763 | 10/3 | EA42 | 3/6 | EC94 | 12/6 | GTIC | 7/6 | PC85 | 4/6 | U26 | 5/6 | U26 | 12/6 |
| 6A8G | 4/6 | 6P22 | 9/6 | 6P25GT | 9/3 | 10P9 | 10/3 | 25L6GT | 9/4 | 5763 | 10/3 | EA42 | 3/6 | EC94 | 12/6 | GTIC | 7/6 | PC85 | 4/6 | U26 | 5/6 | U26 | 12/6 |
| 6A8G | 4/6 | 6P23 | 9/6 | 6P25GT | 9/3 | 10P9 | 10/3 | 25L6GT | 9/4 | 5763 | 10/3 | EA42 | 3/6 | EC94 | 12/6 | GTIC | 7/6 | PC85 | 4/6 | U26 | 5/6 | U26 | 12/6 |
| 6A8G | 4/6 | 6P24 | 9/6 | 6P25GT | 9/3 | 10P9 | 10/3 | 25L6GT | | | | | | | | | | | | | | | |

R.S.C. HI-FI TAPE RECORDER KIT

REALISM AT INCREDIBLY LOW COST. CAN BE ASSEMBLED IN 1 HOUR
The Recorder incorporates the Latest Coliario Studio Tape Transcriber. The Linear LT45 High Quality Tape Amplifier listed £12.120 High Flux P.M. Speaker listed 30/-, empty Tape Spool, a Reel of Best Quality Tape listed 2/6, and a Hand-some Portable carrying Cabinet finished in veneered walnut or Two-tone Rexine size 18 x 13 x 9 in. high, listed £4.10.0, and circuit. Total cost if purchased individually approx. £40. Performance equal to units in the £60-£80 class. Send S.A.E. for leaflet.


251 GNS. I.P. TERMS. Deposit
2 Carr. payments 45/9. Cash
17/6 price if settled in 3 mths.

R.S.C. A8 HIGH FIDELITY 12 WATT AMPLIFIER

Ultra Linear Push-Pull Amplifier with "Built-in" Tone Control. Pre-amp stages, high sensitivity. Includes 5 valves (807 outputs). High Quality sectionally wound output transformer, specially designed for Ultra Linear operation, and reliable small condensers of current manufacture. INDIVIDUAL CONTROLS FOR BASS AND TREBLE "Lift" and "Cut." Frequency response 3-30 db. 30-30,000 c/s. Six negative feedback loops. Hum level 71 db. down. ONLY 70 Millivolts INPUT required for FULL OUTPUT. Suitable for use with all makes and types of pick-ups and practically all microphones. Comparable with the very best designs.

For STANDING or LONG PLAYING RECORDS. For MUSICAL INSTRUMENTS such as STRING BASS, GUITARS etc. OUTPUT SOCKET
with plug provides 300 v. 30 mA and 6.3 v. 1.5A. For supply of a RADIO FEEDER UNIT. Size approx. 12.9-7in. For A.C. mains 200-250 v. 50 c/s. Outputs for 3 and 15 ohm speakers. Kit is complete to last nut. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. Unapproachable value at £7.15.0 or factory built 45/- extra. Carriage 10/-
If required louvered metal cover with 2

£7-15-0

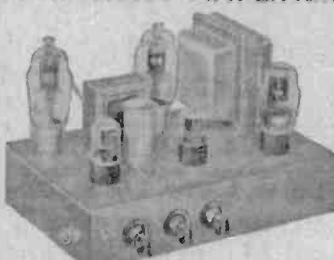

carrying handles can be supplied for 18/9. Additional input sockets, with associate Vol. control so that two different inputs such as Gram and "Mike" or Tape and Radio can be mixed, can be provided for 13/- extra. Guaranteed 12 months.

TERMS on assembled two input model: DEPOSIT 18/9 and 12 monthly payments 18/9.

HIGH FIDELITY MICROPHONES and SPEAKERS in stock. Keep cash prices or credit terms if supplied with amplifier.

HI-FI 10 WATT AMPLIFIERS

Slightly store soiled but guaranteed unused and in perfect order. Fitted Mullard valves. Dual inputs for "mike" and gram, etc. Bass and Treble Controls. High sensitivity and quality. For 200-250 v. A.C. mains.

£5-19-9

Carr. 7/6

STAAR GALAXY 4-SPEED MIXER AUTO-CHANGERS

Brand new, cartoned. Turnover sapphire styl. Many exclusive features. Unique design motor virtually free from rumble. For 200-250 v. A.C. mains. Only £5.19.6.

PORTABLE CABINETS

Full range of attractive designs from

15/9

SPECIAL OFFER. Two tone Portable cabinet. Gram amplifier. Staar. Changer and 7 x 4in. P.M. Speaker. 10 gns. Carr. 10/- or with B.S.R. UAS. 12 gns.

THE SKYFOUR T.R.F. RECEIVER.
A design of a 3-valve Long and Medium wave 200-250 v. A.C. Mains receiver with selenium rectifier. High gain H.F. stage and low distortion detector. Power pentode output. Valve line-up 6K7, 6P6, 6V6. Selectivity and quality are well up to standard, and simplicity of construction is a special feature. Point-to-Point wiring diagrams, instructions and parts list, 1/9, maximum building costs £4.19.6. Inc. attractive Walnut veneered wood cabinet 12 x 6 x 5 1/2 in.

R.S.C. PORTABLE TAPE RECORDER

A completely assembled unit in attractive two-tone rexine covered carrying case. Excellent frequency response. Auto-erase. Fast rewind. Takes up to 6in. tape, spools. High Flux Radio/Gram and "Mike." For 200/250 v. 50 c.p.s. A.C. mains. Sensational value! Price, including "Mike" Reel of best quality tape and empty spool. Usual 12 months' guarantee. H.P. Terms: Deposit 44/- and 12 monthly payments of 33/4.

19 GNS.

PICK-UP ARMS complete with HI-FI turnover crystal head. Acos GP54. Limited number brand new, perfect, at approx. half price. Only 29/11.

ACOS CRYSTAL MICROPHONES.
M10 40 hand or desk. Listed 45/- Only 25/9. Type 33-1, hand or desk. List price 50/- Brand new, cartoned. 35/9. 39-1 stick types. List price 5 gns. Brand new. 39/6.

EXTENSION SPEAKERS

Ready for use in walnut veneered cabinet.

6in. 2-3 ohms. 29/11.

8in. 2-3 ohms. 35/9.

10in. 2-3 ohms. 56/9.

Very limited number.



RECORDING TAPE AT BARGAIN PRICES. Leading makes. Brand new. P.V.C. based. 3in., 150ft., 5/11; 225ft., 7/9; 5in., 600ft., 15/11; 650ft., 22/6; 7in., 1700ft., 35/-

EMPTY SPOOLS. (Plastic.) 3in., 2/9; 5in., 2/11; 7in. 3/9.

R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interwound and impregnated. Primaries 200-250 v. 50 c/s. Screened. **TOP SHROUDED DROP THROUGH**
250-0-250 v. 70 mA, 6.3 v. 2a, 5 v. 2a, 17/9
350-0-350 v. 80 mA, 6.3 v. 2a, 5 v. 2a, 18/9
250-0-250 v. 100 mA, 6.3 v. 4a, 5 v. 3a, 25/9
300-0-300 v. 100 mA, 6.3 v. 4a, 5 v. 3a, 25/9
350-0-350 v. 100 mA, 6.3 v. 4a, 5 v. 3a, 25/9
350-0-350 v. 100 mA, 6.3 v. 4a, 4a, C.T., 0-4-5 v. 3a, 25/9
350-0-350 v. 150 mA, 6.3 v. 4a, 5 v. 3a, 29/9

FULLY SHROUDED UPRIGHT

250-0-250 v. 60 mA, 6.3 v. 2a, 5 v. 2a, 17/9
Midret type 21-3-3in., 25/9
250-0-250 v. 100 mA, 6.3 v. 4a, 5 v. 3a, 28/9
300-0-300 v. 100 mA, 6.3 v. 4a, 5 v. 3a, 28/9
350-0-350 v. 100 mA, 6.3 v. 4a, 5 v. 3a, 28/9
300-0-300 v. 130 mA, 6.3 v. 4a, 5 v. 1a, for Mullard 610 Amplifier, 35/9
425-0-425 v. 200 mA, 6.3 v. 4a, C.T., 35/9
6.3 v. 4a, C.T., 5 v. 3a. Suitable Williamson Amplifier, etc. 49/9

COSSOR VHF/FM RADIO RECEIVER KITS

Including 6 valves, Printed Circuit and Goodmans 10 x 4in. Elliptical Speaker. Pre-aligned I.F.T.S. Made to retail at 15 GNS. £8-19-6 limited number at

R.S.C. BATTERY TO MAINS CONVERSION UNITS

Type BM1. An all-dry Battery eliminator. Size 5 1/2 x 4 1/2 in. approx. Completely replaces battery supplying 1.4 v. and 90 v. where A.C. mains 200-250 v. 50 c/s is available. Suitable for all battery portable receivers requiring 1.4 v. and 90 v. This includes latest low consumption types.

Complete kit with diagrams, 39/9, or ready to use 46/9.



Type BM2. Size 8 x 5 1/2 x 2 1/2 in. Supplies 120v. 90 v. and 60 v., 40 mA, and 2 v. 0.4 a. to lamp. fully smoothed. Thereby completely replacing both B.T. batteries and L.T. 2 v. accumulators when connected to A.C. mains supply 200-250 v. 50 c/s. **SUITABLE FOR ALL BATTERY RECEIVERS**

normally using 2 v. accumulator. Complete kit of parts with diagrams and instructions, 49/9, or ready for use, 59/6.

ELIMINATOR TRANSFORMERS

Primaries 200-250 v. 50 c/s.
120 v. 40 mA, 5-0-5 v. 1a. 15/9
90 v. 15 mA, 4-0-4 v. 500 mA. 9/9

SMOOTHING CHOKES

150 mA, 7-10 H250 ohms 11/9
100 mA, 10 H 200 ohms 8/9
80 mA, 10 H 350 ohms 5/9
50 mA, 10 H 400 ohms 4/11

CHARGER TRANSFORMERS

All with 200-250 v. 50 c/s Primaries:
0-9-15 v. 11 a. 12/9; 0-9-15 v. 3 a. 16/9;
0-9-15 v. 5 a. 19/9; 0-9-15 v. 6 a. 23/9.

AUTO TRANSFORMERS, 50 watt
0-110/115-230/250 v. 8/11 each.

COLLARO CONQUEST 4-SPEED AUTO-CHANGER with high fidelity Studio pick-up. Latest model. Brand new. Cartoned. For 200-250 v. 50 c.p.s. A.C. mains. Our price £7.19.6. Carr. 5/6.

COLLARO 4-SPEED SINGLE FLAYER UNITS. Type AC/4564 with turnover crystal head. £6.12.6. Carr. 4/6.

R.S.C. A12 STEREOPHONIC AMPLIFIER KIT

A complete set of parts to construct a Stereo amplifier with an undistorted output total 8 watts. For A.C. mains input of 200-250 v. Outputs for matched 2-3 ohm speakers. Sensitivity 130 m.v. Ganged Vol. and Tone Controls. Preset balance control. Full instructions and point-to-point wiring diagrams supplied. Only good quality Carr. and pkg. components and latest high grade valves used. Exceptionally realistic reproduction can be obtained at ample volume for the home, as can be demonstrated in typical surroundings at our County Arcade premises. A really sensational offer.

STEREO EQUIPMENT OFFER.
Comprising A12 Kit, 2 matched 8in. L/ Speakers, and Acco 'TVO Stereo head with diamond stylus suitable most pick-ups.

£6-19-6

Carr. 7/6

BUILD A TRANSISTORISED RECORD PLAYER to operate from 6 v. Dry Batteries. Total cost of parts Only

£7-19-6

Unit is housed in attractive portable cabinet and will play standard 7in. 45 r.p.m. records at ample output level. All parts available separately. 1. Garrard Player Unit with pick-up. £3.19.6. Portable Cabinet 29/6.

R.S.C. 30 WATT ULTRA LINEAR HIGH FIDELITY AMPLIFIER A10

A highly sensitive Push-Pull high output unit with self-contained Pre-amp. Tone Control Stares. Certified performance figures compare equally with most expensive amplifiers available. Hum level 70 db. down. Frequency response 23 db. 20-20,000 c/c. A specially designed sectionally wound ultra linear output transformer is used with 807 output valves. All components are chosen for reliability. Six valves are used. E796, E796, ECC83, 6X4, 6X5, 6X6, 6X7, 6X8, 6X9, 6X10, 6X11, 6X12, 6X13, 6X14, 6X15, 6X16, 6X17, 6X18, 6X19, 6X20, 6X21, 6X22, 6X23, 6X24, 6X25, 6X26, 6X27, 6X28, 6X29, 6X30, 6X31, 6X32, 6X33, 6X34, 6X35, 6X36, 6X37, 6X38, 6X39, 6X40, 6X41, 6X42, 6X43, 6X44, 6X45, 6X46, 6X47, 6X48, 6X49, 6X50, 6X51, 6X52, 6X53, 6X54, 6X55, 6X56, 6X57, 6X58, 6X59, 6X60, 6X61, 6X62, 6X63, 6X64, 6X65, 6X66, 6X67, 6X68, 6X69, 6X70, 6X71, 6X72, 6X73, 6X74, 6X75, 6X76, 6X77, 6X78, 6X79, 6X80, 6X81, 6X82, 6X83, 6X84, 6X85, 6X86, 6X87, 6X88, 6X89, 6X90, 6X91, 6X92, 6X93, 6X94, 6X95, 6X96, 6X97, 6X98, 6X99, 6X100.

SUITABLE CLUBS, SCHOOLS, THEATRES, DANCE HALLS or OUTDOOR FUNCTIONS, etc. For use with Electronic ORGAN, GUITAR, STRING BASS, etc. For standard or long-playing records. **OUTPUT SOCKET PROVIDES L.T. and H.T. for a RADIO FEEDER UNIT.**

An extra input with associated vol. control is provided so that two separate inputs such as Gram and 'Mike' can be mixed. Amplifier operates on 200-250 v. 50 c/s. A.C. Mains and has output for 3 and 15 ohm speakers. Complete kit of parts with fully punched chassis and point-to-point wiring diagrams and instructions. If required cover as for A8 can be supplied for 35/9.

11 GNS.
Carr. 10/-
Amplifier can be supplied, factory built with 12 months' guarantee, for £13.19.6. **TERMS: DEPOSIT 24/9 and 12 monthly payments of 24/9.**

LINEAR 'DIATONIC' 10-14 WATT HIGH FIDELITY PUSH-PULL ULTRA LINEAR AMPLIFIER. For 200-250 v. A.C. mains. Valves ECC83, ECL84, EL84, EZ81. Self-contained Pre-amp Tone Control stage. Separate Bass and Treble Controls. Independent 'Mike' and Gram input sockets. Outputs for 3 and 15 ohm speakers. Only 12 GNS.; or Deposit 22/3 plus 10/- carr. and 12 monthly payments of 22/3. Send S.A.E. for leaflet.

LINEAR L50 50 WATT P.A. AMPLIFIER. High quality and sensitivity. 19 GNS. Send S.A.E. for leaflet.

GARRARD 4-SPEED AUTO-CHANGERS. Type RC120H. Very limited number at only £10.19.6. Carr. 5/6.

R.S.C. 3-4 WATT A7 HIGH-GAIN AMPLIFIER

For 200-250 v. 50 c/s. Mains input. Appearance and Specification, with exception of output wattage, as A5. amplifier. Complete Kit with diagrams. £3.15.0. Carr. 3/6.

R.S.C. BRADFORD, MANCHESTER and LEEDS
(Leeds) Ltd.

£3-19-6

LINEAR L45 MINIATURE 4/5 WATT QUALITY AMPLIFIER. Suitable for use with any record playing unit, and most microphones. Negative feed-back 12 db. Separate Bass and Treble Controls. For A.C. mains input of 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Three miniature Mullard valves used. Size of unit only 6-5-6in. high. Guaranteed for 12 months. Only £5.19.6. Send S.A.E. for illustrated leaflet. Terms: Deposit 22/6 and 5 monthly payments of 22/6.

R.S.C. 4-5 WATT A5 HIGH-GAIN AMPLIFIER



A highly-sensitive 4-valve quality amplifier for the home, small club, etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest high fidelity pick-up heads. In addition to all other types of pick-ups and practically all 'mikes.' Separate Bass and Treble Controls are provided. These give full long-playing record equalisation. Hum level is negligible being 71db. down, 15 db. of negative feedback is used. H.T. of 300 v. 25 mA. and L.T. of 6.3 v. 1.5 A. is available for the supply of a Radio Feeder Unit, or Tape-Deck pre-amplifier. For A.C. mains input of 200-230-250 v. 50 c/s. Output for 2-3 ohm speaker. Chassis is not alive. Kit is complete in every detail and includes fully punched chassis (with baseplate) with Blue Hammer finish and point-to-point wiring diagrams and instructions. Exceptional value at only £4.15/-, or assembled ready for use £25/- extra, plus 3/6 carr. or Deposit 22/6 and 5 monthly payments of 22/6 for assembled unit.

R.S.C. PORTABLE GUITAR AMPLIFIERS

Junior 5 watts High Quality output. Separate Bass and Treble 'Cut' and 'Boost' controls. Sensitivity 15 m.v. Twin inputs. High Flux 8in. Loudspeaker 'built-in'. Handsome, strongly made Cabinet (size approx. 14 x 14 x 7in.) finished in satin walnut, and fitted with a carrying handle. H.P. Terms. Deposit £1 and 9 monthly payments of £1.

Senior 10 watts High Fidelity output. Separate Bass and Treble 'Cut' and 'Boost' controls. Twin separately controlled high gain inputs so that two instruments such as Guitar and String Bass can be used at the same time. Two loudspeakers are incorporated, a high Flux 12 in. for Bass notes and a 7 x 4 m. elliptical for Treble. Cabinet is well made and finished satin walnut. Size approx. 19 x 18 x 9 in. H.P. Terms. Deposit 26/9 and 12 monthly payments of 26/9. Both models for 200-250 v. A.C. mains.


£8-19-6

Carr. 7/6

15 GNS.

Carr. 10/-

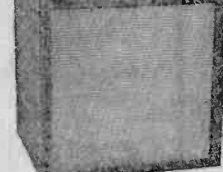19in. 10 WATT HIGH QUALITY LOUD-SPEAKERS IN POLISHED WALNUT FINISHED CABINET



Gauss 12,000 lines. Speech coil 3 ohms or 15 ohms. Only £4.19.6 Carr. 5/- Terms: Deposit 11/- and 8 monthly payments of 11/-.

12 in. 20 WATT HI-FI LOUD-SPEAKERS IN CABINETS. Size 18 x 18 x 8 in. Finish as above. Terms: Deposit 19/10 and 12 monthly payments of 19/10. Only £7.19.6. Carr. 8/6.

PHILIPS CONCENTRIC (Dual Cone) 10in. P.M. SPEAKERS. 3-5 ohms. Limited number at only 20/9.

TERMS: C.W.O. or C.O.D. No C.O.D. under £1. Open 9 to 6: Weds. until 1 p.m. Trade supplied. S.A.E. with all enquiries.

AM/FM RADIOGRAM CHASSIS HIGH QUALITY 6-8 WATT PUSH-PULL OUTPUT

For 200-250 v. Mains. Long Wave, Medium, F.M. and Gram. Complete with 8 B.V. valves. Guaranteed 12 months. Only 22 GNS. Or Deposit £2.12.0 and 9 monthly payments of £2.12.0.



PLESSEY DUAL CONCENTRIC 12in. 15 ohms HIGH FIDELITY SPEAKER

(12,000 lines) with built-in tweeter (completely separate elliptical speaker with choke, condensers, etc.), providing extraordinarily realistic reproduction when used with our A8 or similar amplifier. Rated 10 watts. Price only £5/17/6.

HI-FI CRYSTAL PICK-UP HEADS.

Turnover type with sapphire stylus. HGP59. Standard replacement for Garrard and B.S.R. B.S.R. Ful-0. Garrard GC2. 10/9.

POWER PACK KIT.

Output 250 v. 50 mA, fully smoothed and 6.3 v. 1.5 A. Consisting of Mains Trans., Selenium Rectifier, Smoothing Choke, Double Electrolytic Condensers. Chassis 6in. x 3 1/2 in. and Circuit. Only 18/6.

P.M. SPEAKERS. 2-3 ohm, 2 1/2 in. Perdio 21/9. 5in. 17/9. 8in. 16/9. 10in. 19/9. 12in. 22/9. 15in. 25/9. 18in. 28/9. 20in. 31/9. 22in. 34/9. 1126in. 1690/9. 1128in. 169

PHILIPS Continental F.M. UNIT

The smallest and cheapest F.M. Unit of its kind on the market. Simplicity itself to install. Consists of a two-valve chassis-mounted tuner fitted with one EF41 and one EF42 valve (which are under 12 months' guarantee).

Actual dimensions: $4\frac{1}{2} \times 3\frac{1}{2} \times 1\frac{1}{2}$ in.
Permeability tuned and detected output.

Including Valves and Postage.

59/11

USA THROAT MIKES 7/6

BVI Painting is Easy! Electric PAINT SPRAYER

only **79/-** complete with built-in motor Fully Guaranteed

Completely self-contained. Needs no Extras. Just plug in and Spray. Easy and Fast. Sprays All Paints, Distemper, Varnish, Enamel, Shellac, Lacquer, Insecticide, etc., Only 5/- down and 16 fortnightly at 5/- or 79/-. Post 2/6.



RADIO BULLS VALVES

246, HIGH ST. HARLESDEM HAVEN

DEMOSOLD VALVES 2/6 MANUAL

Giving equivalents of British and American Service and Cross Reference of Commercial Types with an Appendix of B.V.A. Equivalents and Comprehensive Price List. We have still some Valves left at very old Budget Rates (33 1/3%) which are actually sold at the old price (1951). Also ready our **NEW COMPREHENSIVE VALVE LIST**

9/6 REDUCED FROM 21/- 9/6

Pre-heated Electric Soldering Irons, 24 v. 36 watts. Press-button switch fitted. Corrosion-free bit. Specially designed for fine work. Limited quantity. Unrepeatable bargain.

Unique Opportunity to build Fine Transistor Set

Constructor's parcel: to build Pocket Transistor Set as currently being sold at £17.17.0. Parcel comprises Modified two-tone cabinet as illustrated, tuning dial, two gang tuning condenser combined bakelite chassis/printed circuit and easy to follow circuit. Costing value 57/6—offered while supplies last at only 29/6 plus 2/6 post. Suitable for your own circuit or to build original circuit. All parts available at highly competitive prices. Do not miss the tremendous bargain.



Chassis Cutters with key



All prices are with keys.

The operation is quite simple. Prices incl. key: 1in. 12/9; 1 1/2in. 13/8; 1 3/4in. 14/-; 1 1/2in. 14/6; 1 1/2in. 15/-; 1 1/2in. square, 30/-; 1 1/2in. 15/6; 1 1/2in. 15/6; 1 1/2in. 17/8; 1 1/2in. 18/6; 1 1/2in. 21in. 31/9; 2 1/2in. 34/9; 2 1/2in. 39/9. Post 1/-



The easiest and quick est. way of cutting holes in sheet metal. The cutter consists of three parts: a die, a punch and an Allen screw.

All-in-one Radiometer A.C./D.C.

★ CIRCUIT TEST.

★ L.T. and H.T. TESTS.

★ mA TEST.

★ VALVE TEST.

Continuity and Resistance Tests. Complete with Test Leads.

Post 1/-.

Guaranteed **32/6**



SERVICE 10/6 SHEETS



The one you require enclosed if available in a dozen assorted of our best choice.

FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy? ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

We definitely Guarantee "NO PASS — NO FEE"

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £20 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Incorporating E.M.I. Institutes) (Dept. SE/21), 29 Wright's Lane, London, W.8

WHICH IS YOUR PET SUBJECT?

Mechanical Eng.,
Electrical Eng.,
Civil Engineering,
Radio Engineering,
Automobile Eng.,
Aeronautical Eng.,
Production Eng.,
Building, Plastics,
Draftsmanship,
Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

A.M.I. Mech. E.
A.M.I. C.E.
A.M.I. Prod. E.
A.M.I. M.I.
I.O.B.
A.F.R. Ac. S.
B.Sc.
A.M. Brit. I.R.E.
City & Guilds
Gen. Cert. of Education
Etc., etc.

PRACTICAL EQUIPMENT

Basic Practical and Theoretical Courses for beginners in Radio, T.V. Electronics, Etc., A.M. Brit. I.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. (Incorporating E.M.I. Institutes) NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T. SCHOOL OF ELECTRONICS

POST COUPON NOW!

Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES" (Write if you prefer not to cut page)


NAME

ADDRESS

SUBJECT OR EXAM THAT INTERESTS ME



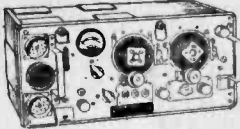THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD



WIRELESS SET No. 19 Mk. II

AS DESCRIBED IN "PRACTICAL WIRELESS" MARCH ISSUE, PAGE 961 AND CONTINUED IN THIS ISSUE.


Special Offer—Order Now!
Limited number only.

This most famous Army Trans/Receiver covers 2-8 Mc/s. (150-37 metres) in two bands and 230-240 Mc/s. V.H.F. Has an intercom. amplifier. Designed for 12 and 24 volt operation. Uses a 6-valve superhet receiver, I.F. being 465 kc/s., and a 6-valve transmitter designed for voice and C.W. operation. Incorporates test and tuning meter for voltages, aerial loading and current tests. Panel Controls: Frequency tuning, P.A. tuning, Gain control, M.C.W., C.W., R.T. switch, Het-tone, netting, off-on, Quench, aerial—A.V.C.—L.T.—H.T.—Drive tests. Supplied complete with 15 valves and instruction book.


SET ONLY

65/-

Carr. 10/-

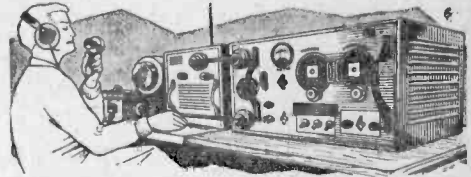

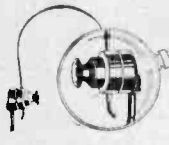Complete station (as illus.) comprising: 19 Set, Supply Unit, Control Box, Headphones, Microphone, Morse Key, Variometer, Short Wave and V.H.F. Aerials and Bases and full set of leads. All for only £9. Carr. 25/-.



LIGHT-WEIGHT HEAD SET.
These H.S. 30 phones are the smallest used by the U.S. Air Force. 2500 Imp.

using soft rubber miniature ear moulds for maximum music and voice reproduction of the finest quality. Only 15/-, p. & p. 2/6.

CRYSTAL DIODES 6/- per doz. P. & P. 1/-.

MICROPHONES — BRAND NEW. Throat magneto 4/6; Throat carbon 3/6; No. 8 carbon with switch 6/6; No. 7 moving coil 6/6. Tannoy power mikes only 5/-.

U.S.A. WHIP AERIALS. 12ft. 12/6. P. & P. 2/6.

V.H.F. MOBILE AERIAL and base, as used by Taxicabs, Police, etc. 7/6. P. & P. 2/6.

CONCOR DOUBLE BEAM OSCILLOSCOPE 339. 10-position time base; 6 c.p.s. to 250,000 c.p.s. Amplifier 10 o.p.s. to 2 mill. c.p.s. Used condition but in working order. £22-10-0. Carr. £1.

CONVERT TO V.H.F.



Within minutes you can extend the frequency of your receiver to cover V.H.F. by using our brand new V.H.F. Converter. R.F. 28 covers 50-65 Mc/s. vernier calibrated tuning. 20/-; R.F. 25 covers 40-50 Mc/s. Switched tuning. 8/6. Circuits supplied. P. & P. 3/6 on each.




aerial posts, M.O. or crystal frequency switch, speaker jack, card holder to log 30 stations, hand vernier tuning knob turning a large etched calibrated plate behind hand lined window, anti-backlash gears used. Used condition. £8-10-0. Carr. 15/-.

POCKET MULTIMETER BRAND NEW

2,500 o.p.v. Multi range 6/30/120/300/1,200 v. A.C., ditto D.C. 0-1 K., 0-1 megohm; 2 Micro-A., 12 mA, 300 mA —00 to +64 db 5 ranges; 3in. x 4in. x 1 1/4in. Large clear dial. Leads supplied. List Price £6.19.6. OUR PRICE £4.7.6. Saving you £2.12.0. P. & P. 2/6.

T.C.S. RECEIVER. 15 to 12 Mc/s. 7-valve superhet, built like a dream. 12SK7-RF, 12SA7 Mixer, 12A6 Oscillator, 12Q7 Detector, A.V.C-BFO-1st AF, 12SK7-I.F.'s The 12A6 final puts 1.4 watts into 500 ohms with an input modulated only 30%. Panel controls: R.F. Gain, A.F. Gain, C.W. Pitch, band-switch, mod-C.W. switch, power switch, ground and tuning knob turning a large etched calibrated plate behind hand lined window, anti-backlash gears used. Used condition. £8-10-0. Carr. 15/-.

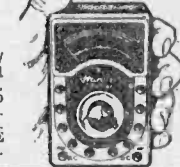

POLICE—AIRCRAFT—HAM RECEIVER P. 104

Frequency range 80-150 Mc/s. I.F. freq. 5 Mc/s. Complete with tuning meter, 14 valves: 2-R.F., 3-I.F., B.F.O., A.G.C., Audio. Crystal controlled with separate R.F. and oscillator tuning. R.F. and Audio controls, B.F.O. tone control, Oscillator and Audio signal fully metered. Power requirements 250 v. H.T., 6.3 v. L.T.

Brand NEW Only £5 Carr. 15/- Mains power pack only 60/- Carr. 7/6.

HI-FI CO-AX SPEAKERS, BRAND NEW—U.S.A. MADE. 12in. Co-axial Speaker. The woofer uses 6.8oz. Alnico 5 magnet. Has 3in. tweeter and an electronic crossover network to separate the speaker functions. Frequency response: 40-17,000 cycles. Output 12 watts. Impedance 8 ohms. ONLY 150/- 3in. 2in. tweeter, 10 watts, etc. 90/- P. & P. 4/- on each.



PRINTED CIRCUIT KIT


Easily and quickly you can make miniature professional printed circuits. Complete with illustrated manual. 19/6. P. & P. 1/6.



INSTANT VALVE FILAMENT TESTER, MODEL VT-41

Pocket-size, battery operated. GIVES INSTANT CHECK OF:

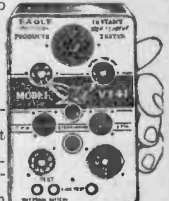- All Radio Valves.
- All TV Valves.
- All TV & Radio Fuses.
- Circuit Continuity.
- All Pilot Lamps.
- Has built-in miniature 7 and 9-pin valve sockets.



straightens and battery test. * International Octal, B.8, B.9, B.7 Battery and Mains types. Beautifully styled — precision made. Supplied complete. Fully guaranteed. ONLY 30/- P. & P. 2/6

BRAND NEW VARIABLE TRANSFORMERS

Input 250volts. Output 0-260 volts. 5 amps. Brand new only £9. Carr. 12/6.



PORTABLE TRANSMITTER RECEIVER No. 18

Entirely self-contained 6-valve Transmitter Receiver for voice and C.W. Frequency: 6-8 Mc/s (50-33 metres). The Transmitter signal is generated by a master oscillator circuit followed by a power amplifier. The aerial is auto-coupled to the power amplifier by aerial taps to a parallel tuned output circuit. The Receiver is a 4-valve superhet, comprising signal frequency amplifier, frequency changer, I.F. amplifier, 2nd det. —A.V.C.—A.F. Stage. Selectivity: The resonance curve of the I.F. amplifier has a width of 7 kc/s. with

an average cut-off of 5 db/kc/s. Full netting facilities. circuit set for full modulation, operated by standard dry batteries, range approximately 10 miles. Incorporates Test Meter for aerial loading, H.T. & L.T. readings. Supplied Brand New complete with Power Microphone, Headphones, Morse Key, Aerials, Webbing and full instruction book all for only 80/- Carriage 10/-, 18 Set as above less attachments. 60/- Carriage 10/-.

80/-

Carr. 10/-



Callers: 87 Tottenham Court Road, London W.1.
Mail Orders: (Dept. P), 32a Coptic Street, London W.C.1
Telephone: MUSEum 9607

FULLY ILLUSTRATED CATALOGUE 1/3 Post Free.

Brand new, individually
checked and guaranteed

VALVES

| | | |
|---------------------|------------|--------------|
| AC/DD 2/6 | DF70 9/- | EL84 8/3 |
| AC/P 4/6 | DH76 4/9 | EL91 7/6 |
| AC/PI 2/6 | DL72 7/6 | EM4 4/- |
| AC/SPEND 1/323 25/- | ESU208 8/- | |
| 4/- | EA50 1/6 | EY91 3/6 |
| AC6/PEN 5/- | EAC91 4/6 | EZ40 7/- |
| AC/SP3 4/6 | EB34 1/6 | EZ80 7/6 |
| AL60 2/6 | EBC33 6/- | FW4/500 6/6 |
| AR6 2/6 | EC52 3/6 | H30 5/- |
| AR8 5/6 | EC54 3/6 | H63 3/6 |
| ARDD5 2/- | ECC32 4/- | HPA101 6/- |
| ARP3 3/- | ECC81 6/6 | KBC32 5/- |
| ARP4 3/6 | ECC82 6/9 | KF35 5/- |
| ARP12 2/9 | ECC83 7/- | KT2 4/- |
| ARP24 3/6 | ECC84 7/9 | KT31 8/- |
| ARP31 5/6 | ECC91 4/- | KT33C 7/- |
| AV4 5/- | ECL80 9/6 | KT44 7/- |
| SRP34 4/6 | EF22 7/3 | KT41 9/- |
| STP4 2/9 | EF32 5/- | KTW63 6/6 |
| ATP7 5/6 | EF36 3/6 | L30 4/- |
| AUI 5/- | EF39 4/6 | MH4 3/6 |
| AW3 4/- | EF50 2/6 | ML4 4/- |
| BL63 6/- | EF52 5/- | ML6 6/- |
| BT45 40/- | EF54 3/6 | MC/PEN 6/- |
| BT9D 40/- | EF55 6/- | MC/PENB6/- |
| D41 3/3 | EF70 4/- | N34 8/- |
| D42 4/- | EF80 6/9 | NR15A 3/6 |
| D77 4/3 | EF85 6/10 | MT37 5/- |
| DA30 12/6 | EF89 8/9 | (4033A) 10/- |
| DD41 4/6 | EF91 4/10 | OD3 5/- |
| DET5 15/- | EF92 5/- | OZ4 5/- |
| DET18 30/- | EL32 3/9 | OZ4A 5/- |
| DET19 2/6 | EL35 9/- | P61 4/6 |
| DET20 2/6 | EL41 8/3 | PCC84 8/3 |

AND MANY OTHERS IN STOCK, INCLUDING CATHODE RAY TUBES AND SPECIAL VALVES. All U.K. Orders below 10/-. P. & P. 1/-; over 10/-, 1/6;

Brand new original spare parts for AR88 Receivers.

Please write your requirements.

Low Resistance Headphones, brand new, type CLR, 5/-, Balanced Armature, 7/6, P. & P. 1/-.

Microphone Transformers, Balanced input 30 or 250 ohms. U.S.A. manufacture 7/6, P. & P. 1/6.

813 Ceramic Valveholders, 3/- each, P. & P. 1/6.

Vacuum Condenser 32,000 V. 50 pF, 15/-, Post free.

Modulation Transformers (U.S.A. Collins), primary imp. 6,000 Ω , C.T., secondary 6,000 Ω 20 W., 9/6 ea. Post free.

Carbon Inset Microphone, G.P.O. Type 2/6, P. & P. 1/-.

Telescopic Aerial Masts, 7 sections, total 11 yards. Immediate erection. £4.10.0 each or £8 per pair. Post free.

Light Headgear Assembly, Ideal for mobile use. Headphones 600 ohms carbon microphone, 18/-, P. & P. 3/-.

Rotary Transformer, 171 W 12 v input, 1,600 v. 100 mA output, 30/-, P. & P. 7/6.

R109 Receiver, Covering 2-8 Mc/s 6 v. D.C. New and Tested, £45.0.0. C. Pd.

R109A Receiver, Covering 2-12 Mc/s 6 v. D.C. New and Tested, £55.0.0.

Variometers for W/S No. 19. Fully tested and working, 12/6, P. & P. 2/6.

Complete V.F.O. Unit from TX53. Freq. range in 4 switched bands from 1.2-17.5 Mc/s. Two V.T. 501s as oscillator and buffer, 807 as driver, two 1310s as voltage stabilizers. Output sufficient to drive two 813s in parallel. Slow motion drive directly calibrated in Mc/s. Provision for crystal control, metering of buffer and driver stage. Power requirements 400 v. and 6.3 v. D.C. Can also be used as low power transmitter. In excellent condition with valves and circuit diagram, £5. P. & P. 15/-.

R.C.A. Master Oscillator (V.F.O.) with

| | | |
|---------------|--------------|-----------|
| PCC85 8/- | U18 6/6 | 4D1 2/6 |
| PEN25 4/6 | U27 8/- | 5U4G 5/- |
| PEN46 5/6 | UL84 8/6 | 5V4 7/- |
| PEN65 6/6 | UY85 7/- | 5Y3GT 6/9 |
| PEN220A 3/- | V248A 4/- | 5Z3 8/6 |
| PENDDD 1/6 | V2D33B 8/- | 5Z4G 8/6 |
| 1360 9/6 | VP23 3/6 | 6A6 5/- |
| PL81 1/6 | VR78 4/- | 6AB7 5/- |
| PL82 8/- | VR99 8/- | 6AC7 4/3 |
| PL83 9/- | VR105/307/6 | 6AG5 4/6 |
| PM4DX 3/- | VR150/304/3 | 6AG7 8/6 |
| PT25H 7/6 | VR150/30 6/- | 6AK6 7/6 |
| PY82 8/- | VS110 4/- | 6AK7 8/- |
| QP21 6/- | VT25 8/6 | 6AM5 5/- |
| QP25 5/3 | VU111 3/6 | 6AM6 6/3 |
| QS75/20 6/9 | VU120 3/3 | 6BG4 4/6 |
| QS95/10 6/9 | VU133A 3/- | 6B8 5/6 |
| QSC108/45 6/9 | W31 7/- | 6BBG 2/6 |
| QSI50/15 6/9 | Y63 5/- | 6C4 4/- |
| | Y66 8/- | 6C5 6/- |
| | Z31 6/- | 6C6G 4/6 |
| | 1A3 3/6 | 6CBG 5/6 |
| R10 12/6 | 1A5GT 5/- | 6F6 7/- |
| REL21 25/- | 1C5GT 7/6 | 6F8H 6/6 |
| RG1-240 17/6 | 1D8GT 6/- | 6F12 4/6 |
| RG3-250 17/6 | 1E7GT 7/6 | 6G6G 3/6 |
| RG4-1250 9/- | 1L4 3/9 | 6HM6 2/3 |
| | 1LD5 3/6 | 6HG6T 1/9 |
| | 1R5 6/9 | 6HA7 4/3 |
| | 1S5 6/- | 6J5 3/6 |
| RK34 2/6 | 1T4 4/- | 6J6 4/6 |
| RL37 3/6 | 2A3 8/- | 6K6GT 6/6 |
| SP2 4/- | 2A6 7/- | 6K7G 2/3 |
| SP4B 7/6 | 2C34 2/6 | 6K7GT 5/3 |
| SP13C 4/6 | 2DA4 4/- | 6K8G 6/6 |
| SP21 2/6 | 2X2 4/- | 6LSG 6/6 |
| SP41 2/6 | 3A4 6/- | 6L6 9/- |
| SP61 2/6 | 3B34 3/- | 6L6G 6/6 |
| SU2150A 4/9 | 3E29 60/- | 6L6GA 6/6 |
| T41 1/9 | (829B) 60/- | 6L34 4/6 |
| TP25 15/- | 3Q5GT 9/- | 6N7GT 7/3 |
| TT11 3/- | 4A1 4/6 | 6Q7G 6/3 |

stability of 0.0007%. Frequency range 2-20 Mc/s with built-in constant frequency tone generator. Regulated A.C. power supply 115/230 v. and fitted with plate and volt meters. Valves line-up: Electronic coupled oscillation 3Q5(2). Buffer amplifier—807, tone generator—6AB7(1), 6F6(1), regulated power supply—5U4(2), 6Y6(5), 1852(1), VR150/30(2). Brand new, complete in grey crackle steel cabinet size 67in. x 22in. x 17in. Fitted with full-length door at rear with standard 19in. panels. Can be used as complete TX with existing 807 output. The bottom half of the cabinet with 3 blank panels being empty ready for installation of complete R.F. modulator and power unit, thus making a complete totally enclosed compact TX. Circuit diagrams and working instructions supplied. Price complete with valves, £71.0.0 each. Supplies: strictly limited.

Filament Transformers, Primary 0-190-210-230-250 v. 50 C.T. 1.25 v. C.T. at 10 amps.; 2.25 v. C.T. at 10 amps.; 3.105 v. C.T. at 11 amps.; 4,000 v. insulation. Price £21.0.0. P. & P. 5/-.

Primary 0-190-210-230-250 v. 50 C.T. 1.10 v. C.T. at 4.5 amps.; 2.10 v. C.T. at 4.5 amps., 4,000 v. insulation. £11.6.0. P. & P. 5/-.

Primary 230 v. 50/60 c. 67 v.amps. Sec. 1 6.3 v. 1-6 amps.; 2 6.3 v. C.T. 3 amps.; 3 6.3 v. C.T. 3 amps.; 3 6.3 v. C.T. 3 amps.; 4 6.3 v. C.T. 3 amps. £11.2.0. P. & P. 5/-.

Driver Transformers, Primary 500 ohms imp. Sec. to match two 805 in push pull. £17.6. P. & P. 5/-.

| | | |
|------------|-------------|-------------|
| 6R7G 7/6 | 35Z3GT 7/- | 1626 3/6 |
| 6SC7G 5/6 | 39/44 6/- | 1629 4/6 |
| 6SC7GT 6/- | 53A 3/- | 4242A 6/- |
| 6SG7 5/- | 58 6/- | 7193 1/9 |
| 6SH7 5/- | 59 6/- | 7475 5/- |
| 6S17 6/9 | 71A 4/6 | 8010AR 22/6 |
| 6S17G 6/6 | 77 6/- | 8013A 10/- |
| 6SK7 5/6 | 80 6/3 | 8020 6/- |
| 6SL7GT 6/9 | 82 8/- | 9001 5/- |
| 6SN7GT 4/6 | 83V 12/- | 9003 5/6 |
| 6SQ7 6/6 | 84 12/6 | 9004 4/- |
| 6SR7 6/6 | 85A1 12/- | 9006 4/- |
| 6SS7 5/- | 89 6/- | |
| 6V6G 5/6 | 210LF 3/- | |
| 6V6GT 6/- | 210VPT 3/- | |
| 6X5G 5/6 | 7 pin 2/6 | |
| 6X5GT 6/6 | 217C 17/6 | |
| 7SAZ 6/9 | 220VSG 3/- | |
| 8D2 2/6 | 446A 14/- | |
| 8B08 5/6 | 446B 14/- | |
| 9D2 3/- | 705A 17/6 | |
| 12A6 5/- | 715B 97/6 | |
| 12AH7 6/6 | 717A 8/6 | |
| 12AT7 6/9 | 801 6/6 | |
| 12AU7 6/9 | 803 22/6 | |
| 12AX7 7/- | 805 30/- | |
| 12CB 7/6 | 807AMER 5/3 | |
| 12E1 22/6 | | |
| 12H6 2/6 | 807BR 3/9 | |
| 12J5GT 3/6 | 813 70/- | |
| 12SC7 4/6 | 815 80/- | |
| 12SG7 6/6 | 816 30/- | |
| 12SH7 4/9 | 829A 30/- | |
| 12SJ7 6/- | 833A 614 | |
| 12SK7 5/- | 843 7/6 | |
| 12SL7 7/- | 866A 10/- | |
| 12SR7 6/- | 827A 35/- | |
| 15D2 6/- | 930 8/- | |
| 15E 8/- | 956 2/- | |
| 15R 7/6 | 1619 5/- | |
| 30 5/- | 954 2/- | |
| 35T 30/- | 1625 6/- | |

Cathode Ray Tubes

3BP1 25/-

5CP1 42/6

5P7 45/-

SGF/5 15/-

VCRX258

(with scanning coil) 45/-

5BP1 35/-

Photo Tubes

GS16 12/6

GMG25 12/6

Special Valves

231 45/-

3A/1481 45/-

3J/170E £35

3J/192E £14

£37.10

723AB 52/6

726B 27/6

ACT25 40/-

CV691 60/-

KR3 45/-

VX7110 15/-

WL147A15/-

Transformers. Relay supply. Primary 230 v. Sec. 0-27-28-31 v. at 0.5 amps. 15/-, P. & P. 5/-.

I.F. TRANSFORMERS 4.5 Mc/s, American. Made in black crackle finish housing, 6/-, P. & P. 1/-.

SCR.522 Receivers (BC624), 100-156 Mc/s including all valves, 25/-, P. & P. 5/-.

SCR.522 Transmitter (BC624) including all valves, 22/6, P. & P. 5/-.

Vibrator Unit, 12 v./160 v. 35 mA. Exceedingly well filtered and smoothed, excellent for car radios. New, including 6X5G valve and vibrator, 17/6, P. & P. 5/-.

Moving Coil Round Hand Microphone No. 13, 2 1/2 in. dia. with press switch, 12/6, P. & P. 1/-.

Plate Transformer, Input 190-210-230-250 v., output 2,250-0-2,250 c.t., 400 mA. 19 x 9 x 6 1/2 in., weight 75 lb. Price £6.10.0, carr. 10/-.

Complete Set of Strong Aerial Rods (American). Screw-in type MP49, 50, 41, 52, 53, total length 15ft. 10in., top diameter 0.615in., bottom diameter 0.185in., together with matched aerial base. MP37 with ceramic insulator, ideal for car or roof installation, £2.10.0, post free.

AR88D and L.F. Receivers, completely overhauled and tuned, £60 and £57.10.0 respectively. Completely rebuilt with P.V.C. wiring, £85.

HRO Mains power pack, input 115/250 v. A.C.; output 250 v. 0.75 mA and 6.3 v. 3.5 amps. £3, inc. carr.

Non Inductive Carbon Resistance, 800 Ω about 30 watt lin. dia. 10in. long, 7/6, P. & P. 1/6.

Avominors, Leather case. With leads, fully tested and guaranteed. With batteries. A.C./D.C. volt range to 500 v. £4.19.6.

As above but to 1,000 volt, D.C. only. £39.6. P. & P. 2/6 on either.

Personal Callers Welcome

P. C. RADIO LTD.

170 GOLDHAWK RD., W.12

SHepherds Bush 4946


A REVOLUTIONARY NEW BRITISH INVENTION!

- ★ Uses standard tapes
- ★ Plays at $7\frac{1}{2}$ " per. sec. or 3 other speeds
- ★ Records direct from radio or microphone
- ★ Erase and fast rewind

£13.12s

Special moving-coil microphone and tape extra.

EASY TERMS

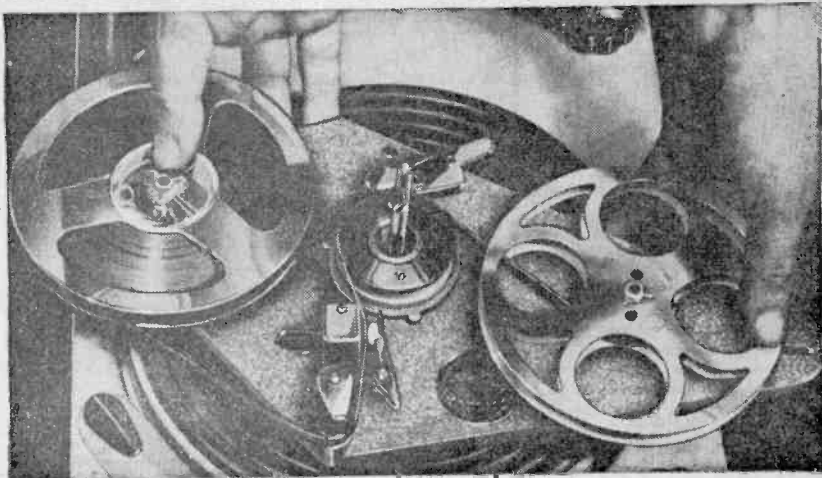

Instantly turns any gramophone into a first-class Tape-Recorder and back into a record-player in a moment!

Gramdeck is completely new . . . a revolutionary and ingenious invention that instantly turns your gramophone into a tape-recorder and back into a gramophone at will! Slip the Gramdeck on to your turntable and you have the finest tape-recorder you've ever heard! Lift it off . . . your gramophone is ready to play records again. There are no motors or valves to go wrong—and you get a quality that has to be heard to be believed! Everyone is praising the Gramdeck.

"The quality is at least equal to that obtained from a good microgroove disc," says a leading professional journal.

"Ingenious—simple . . . why on earth did no one think of it before!"—THE TAPE RECORDER.
 "Ingenious and robust"—BRITISH SOUND RECORDING ASSOCIATION JOURNAL.
 "Quality of reproduction excellent . . . real hi-fi results . . . potential is tremendous . . . both designer and manufacturer should be congratulated."
 —BRITISH RADIO & T/V RETAILERS REVIEW.

"Better than many so-called hi-fi recorders . . . robust . . . carefully designed . . . excellent value."—AMATEUR CINE WORLD.

Gramdeck

GRAMOPHONE TAPE RECORDER
HIGH QUALITY TAPE-RECORDING FOR EVERY HOME

WORKS FROM ANY RECORD-PLAYER OR RADIOGRAM

Gramdeck records and reproduces with a wonderful depth and breadth of tone. Because it uses equipment that is already in your gramophone it only costs a fraction of the high-quality tape-recorder you would normally require. Full details, specifications, photographs, easy terms, etc., are given in the Gramdeck Book. Send for your FREE copy, today.

MADE BY THE FIRM THAT MAKES RADAR EQUIPMENT FOR VISCOUNTS & BRITANNIAS

FREE BOOK—POST NOW.

I would like to know how to turn my gramophone into a first-class tape-recorder . . . please send me the Gramdeck Book—FREE and without obligation.

(Write if you prefer not to cut page)

NAME

ADDRESS

Gramdeck (Dept. PA/807) 29 Wright's Lane
Kensington, London, W.8

GRAMDECK TURNS A TURNTABLE INTO A TAPE-RECORDER

NO DEPOSIT - INTEREST FREE - 20 or 36 WEEKS TO PAY!

4/1
DEPOSIT



RP2

Balance at 2/11 per week for 19 weeks. A beautifully styled cabinet. Made by a famous manufacturer. In polka dot cloth with clipped lid and carrying handle. Size 16 x 14½ x 8½ in. deep. Will take B.S.R. Monarch 4-speed Autochanger and 7 x 4 in. elliptical speaker and most of the modern portable amplifiers. Carr. & Ins. 4/6.

Cash price **59/6**

PL10 CABINET

Size 14½ x 12½ x 6 in. Takes a B.S.R. T.U.9 4-speed record player unit. 8 x 3 in. elliptical speaker. Single control amplifier. Carr. & Ins. 4/6.




39/6

Stereo Record Player Cabinet

with extension speaker cabinet.

Portable 1960 show model in two tone colours. Extension speaker cabinet secured in lid. (Arrow indicates position when fixed.) Size 18 x 14 x 8½ in. high. This stereophonic player retails at 35 gns. in the shops today. A must for teenagers, and an essential for the enthusiast. Carr. & Ins. 5/6 with order.

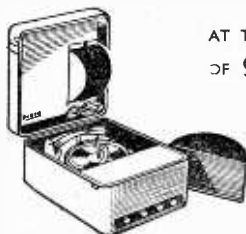
OR 6/11 initial payment and balance at 4/11 for 19 weeks.



AT THE AMAZING OFFER
OF **99/6**

Model S.T.1 (including extra speaker cabinet)
99/6 plus insurance and carriage 6/6

4/7
DEPOSIT

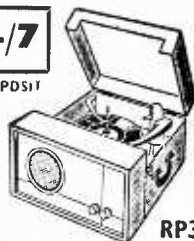


RP3

Balance at 3/5 per week for 19 weeks. A delightful looking cabinet. Size 14½ x 17½ x 8½ in. in 2-tone leatherette. Will take a B.S.R. Monarch 4-speed autochanger and 6 in. round speaker. Carr. & Ins. 4/6.

Cash Price **69/9**

TAPE RECORDER CABINET

19/6

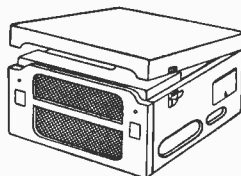

A must if you are building your own tape. Suitable for the Truvox Tape Recording Desk. Less front cast speaker panel. Size 13½ x 15 x 8½ in. deep. Detachable lid with compartment for spare tape. Covered in green washable plastic material. P. & P. 4/6.

EXTENSION SPEAKERS 19/9



Polished oak cabinet of attractive appearance. Fitted with 8 in. P.M. speaker V.W.B. or Goodmans of the highest quality. Standard matching to any receiver (2-5 ohms). Switch and flex included. Ins. & Carr. 3/9.

8 in. P.M. Speaker 8/9

Std.; 2-5 ohms. With O.P. Trans., 10/-, P. & P. 2/6.

Elliptical Speaker 19/6

7 x 4 in. Elliptical Speaker 22/6

7 x 4 in. B.S.R. FUL-FI Crystal Turn-over cartridges 19/6

Brand new, including sapphire needles for L.P. and Standard, giving fullest range and finest tone obtainable for any player, can be fitted to all standard pick-up arms. P. & P. 9d.

De-Luxe Tape Recorder Cabinet

ONLY
29/9



Beautifully made Tape Recording Cabinet. Size 14 x 11 x 8½ in. Covered in 2-tone coloured rexine cloth. Stylish design. Carrying handle and detachable lid with lock and key. Easily adapted to Record Player Cabinet. Exceptional value at this very low price.

P. & P. 4/6

B.S.R. MONARCH U.A.8. 4-SPEED AUTO CHANGER

£6/19/6

4-speed auto changer. Incorporating auto and manual control complete with turn-over crystal P.U.

and Sapphire stylus. A.C. Post. & Ins. 5/6 or Initial Payment 8/11 plus Post. & Ins. and 19 weekly payments of 6/11.

T.U.9. B.S.R. 4-speed single player **£4.9.6**

Collaro Conquest 4-speed Autochanger **£6.19.6**

Collaro Conquest Stereo Autochanger **11 gns.**

P. & P. on all above 5/6.



DUKE & CO. (DEPT. D.4)

621/3 ROMFORD ROAD

MANOR PARK, E.12


Tel. 1LF 6001/3

SEND FOR A FREE CATALOGUE

CONTEMPORARY EXTENSION SPEAKERS

ONLY
19/9

Ideal for that extra stereophonic speaker. Covered in smart two-tone leatherette colour scheme. Takes 8 in. P.M. Speaker. P. & P. 3/9.

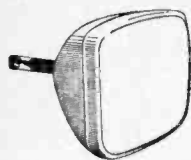NO DEPOSIT - INTEREST FREE - 20 or 36 WEEKS TO PAY!**REPLACEMENT
REBUILT
TV TUBES**Yours for initial
payment of **8/6**Balance at 8/6 for 19 weeks.
12 months full guarantee.

All sizes except 10in. Completely rebuilt gun assembly, new cathode, heaters, etc., giving the high standard required for long picture life, quality and value. Carr. & Ins. 15/6.

EXPRESS DESPATCH SERVICE

Please 'phone to confirm Tube in stock. Telegraph Money Order. Tube despatched Passenger Train same day. This service is only available with remittance by a telegraph Money Order and cash sales, not terms.

**A CHASSIS FOR SPARES. ALL THIS
FOR ONLY **9/6****


56 Resist. incl. 7 variable Controls Condensers, incl. electrolytics, Coils, 71.F. and R.F. Trans. 14 valve holders. 9 B7G, 5 B5G. 3 octal, 4 trans. Mains—O.P.P.—Line—Frame. Chokes 250 mA. Metal rec. 300 volt 250 mA. Fuse panel—scanning coils—focus magnet. Plugs—sockets—switch—chassis screws—tag strips etc. I.F. strip is separate. Power pack can be used without dismantling. Chassis have been used but were working—when stored. Seven pages of circuits and instructions showing position of each component. Carriage 10/6.

BAKELITE CABINETS


only 5/9

Brand new. Colour brown. Attractive design. Size 12 x 7 x 5 1/2 in. Ideal for small receivers, converters, etc.

P. & P. 3/9.

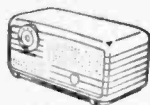**SOLO SOLDERING TOOL 12/6**

110 v., 6 v., 12 v. (special adaptor for 200/250 v., 10/- extra). Automatic solder feed including a 20ft. reel of Ersin 60/40 solder and spare parts. It is a tool for electronic soldering or car wiring. Revolutionary in design. Instantly ready for use and cannot burn. In light metal case with full instructions for use. Post 3/6.

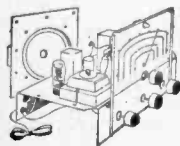
**SUPER CHASSIS****3/11 per week**

On the initial payment of 5/1 plus carriage of 5/6, this chassis will be despatched. Balance at 3/11 for 19 weeks. Cash price 79/6. 5-valve Superhet chassis including Bin. P.M. speaker and valves. Four control knobs (tone, volume, tuning, w/change switch). Four wavebands with position for gram p.u. and extension speaker. A.C. Ins. & Carr. 5/6

DUKE & CO. (DEPT. D.4)
621 3 ROMFORD ROAD
MANOR PARK, E.12

Tel.: ILF 6001/3

SEND FOR A FREE CATALOGUE

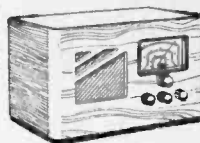**HOME RADIO
A.C. or UNIVERSAL****79/6**

A.C./D.C. Universal mains 5-wave octal superhet. 3-waveband receiver can be adapted to gram p.u. In attractive wooden cabinet. Size 9 1/2 x 18 1/2 x 1 1/2 in. Ins. & Carr. 1/6. Terms available.

FOCUS MAGNETS 9/9
Brand new. 30 mm. incorporating picture shift control. P. & P. 1/3**FOCUS MAGNETS 12/6**
38 mm. Brand new. P. & P. 1/3.**SCANNING COILS 10/6**
Low impedance. 38 mm. Brand new. P. & P. 1/3.**SCANNING COILS 15/9**
Wide angle 90 deg. 38 mm. Low impedance. P. & P. 1/3.**TV MASKS 2/9**
Gold plastic for 15in. tubes. Post. 1/3.**CHASSIS 1/-**
6 or 8 valve latest type midgelet valve design for A.M. or F.M. Brand new. Cadmium plated. Size 12 1/2 x 7 1/2 x 2 1/2 in. P. & P. 1/9.**MAINS TRANSFORMERS 7/9**
Primary 200-250. Secondary 300-0-300. 6 v. at 3.3 amps. P. & P. 2/9.**MAINS AUTO 8/9**
0-205-225-245 Volts at 300 m.A.
Isolated windings of 6.3 v. at 2-6 amp. 6.3 v. at 3-6 amp. 2 v. at 1-4 amp. P. & P. 3/9.**O.P. TRANSFORMERS 1/3**
Standard size. 2-5 ohms. P. & P. 1/-. 20 for £1. P. & P. 5/6.**MODERN****17" TV****CHASSIS****COMPLETE****AND WORKING****22 Gns.**

A chassis including 17in. tube, permanent magnet speaker, 13 channel Turret Tuner (any two selected channels fitted). Other Channels supplied on request at 7/6 each. 13 valves. Chassis and valves guaranteed for three months. CRT 2 months' full guarantee. Sound I.F. 19.5 Mc/s. Vision 16 Mc/s. A.C. only. Ready and working to fit into your own cabinet. Carr. & Ins 25/-. As above with 14in. tube, complete and working, £19.19.0.

TV AERIALS 23/6
For all I.T.A. channels. Outdoor or loft. 3 elements. P. & P. 2/6.**AERIALS 15/6**
BBC indoor type. Folded dipole with 12ft. co-ax cable fitted. P. 1/9.**TV AERIALS 35/-**
Combined I.T.A. or B.B.C. New. L/SD. P. & P. 2/6.**CAR AERIALS 6/9**
Plates. Whip antennae. 50in. long collapsing to 11in. One hole fixing. P. & P. 1/-. (Not telescopic).**SOUND/VISION & I.F. STRIP 7/9**
Plessey I.F.s. 11.5 Mc/s sound. 14 Mc/s vision. 8 valve holders. Less valves. Size 8 1/2 x 5 x 4 1/2 in. Circuit incl. The tuner unit plugs directly into this chassis. P. & P. 2/6.**SOUND/VISION & I.F. STRIP 2/9**
Salvaged. Complete sound and vision strip. 8 valve holders. Less valves. I.F.s 16-19.5 Mc/s. Size 8 1/2 x 4 1/2 x 4 1/2 in. Drawings free with order. P. & P. 2/6.**TIMEBASE 2/9**
Containing scanning coils, line transformers, etc., less valves. Drawings free with order. P. & P. 2/6.**CO-AX CABLE 6d. YARD**
Good quality. Cut to any length, 1/6 postage on 20 yards.**INSULATING TAPE 1/6**
75ft x 1/2 in. In sealed tins. Post 9d.

Easy-to-build kit-sets of**Heathkit****highest quality at lower cost****HI-FI F.M. TUNER**

Tuning range 88-108 Mc/s. For your convenience this is available in two units sold separately as follows: Tuner Unit (FMT-4U) with 10.7 Mc/s I.F. output (£32.0, inc. P.T.). I.F. Amplifier (FMA-4U) complete with cabinet and valves (£10.10.6).
Total £13.12.6

HI-FI 16W. STEREO AMPLIFIER Model S-88

10 mV. basic sensitivity (2 mV. available, 30/- extra). Ganged controls. Stereo/Monaural gram., radio and tape recorder inputs. Push-button selection. Two-tone grey metal cabinet. £25.5.6

6-TRANSISTOR PORTABLE Model UXR-1

Pre-aligned I.F. transformers, printed circuit, 7 x 4 in. high-flux speaker. Real hide case. £15.18.6

DUAL-WAVE TRANSISTOR RADIO UJR-1

This sensitive headphone set is a fine introduction to electronics for any youngster. £2.16.6

RES.-CAP. BRIDGE Model C-3U

Measures capacity 10pF to 1,000µF., resistance 10Ω to 5 MΩ and power factor. 5-450 v. test voltages. With safety switch. £7.19.6

AUDIO SIGNAL GENERATOR Model AG-9U

10 c/s to 100 kc/s., switch selected. Distortion less than 0.1%. 10 v. sine wave output metered in volts and dB's. £19.3.0

VALVE VOLTMETER Model V-7A

Measures volts to 1,500 (D.C. and R.M.S.) and 4,000 pk. to pk. Res. 0.1Ω to 1,000 MΩ. D.C. input Imped. 11 MΩ. Complete with test prods, leads and standardising battery. £13.0.0

R.F. PROBE Model 309-CU

Extends the frequency range of our V-7A to 100 Mc/s. and enables useful voltage indication to be obtained up to 300 Mc/s. £15.5.6

5 in. OSCILLOSCOPE Model O-12U

Has wide-band amplifiers, essential for TV servicing, F.M. alignment, etc. Vertical freq. response 3 c/s. to over 5 Mc/s. without extra switching. T/B covers 10 c/s. to 500 kc/s. in 5 ranges. £34.15.0

ELECTRONIC SWITCH S-3U

(Oscilloscope Trace Doubler)

Enables a single beam oscilloscope to give simultaneous traces of two separate and independent signals. Switching rates approx. 150, 500, 1,500, 5,000 and 15,000 c/s. £9.18.6

CAPACITANCE METER CM-1U

Direct-reading 4½ in. scale. Full-scale ranges 0-100µF. 0-1,000 µF 0-0.01µF and 0-0.1µF £14.10.0



CM-1U



S-33



USP-1



S-88



F.M. TUNER



S-3U



DX-100U

6-W STEREO AMPLIFIER Model S-33

3 watts per channel, 0.3% distortion at 2.5 w/chnl., 20dB N.F.B. Inputs for Radio (or Tape) and Gram., Stereo or Monaural, ganged controls. £11.8.0
Sensitivity 100 mV.

TRANSCRIPTION RECORD PLAYER RP-1U

4-speed A.C. motor. Ronette Stereo/ Mono pick-up. Complete with plinth £12.10.0

HI-FI SPEAKER SYSTEM Model SSU-1

Ducted-port bass reflex cabinet "in the white". Twin speakers. With legs £11.12.6. £10.5.6

"HAM" TRANSMITTER Model DX-40U

From 80-10 m. Power input 75 w. C.W., 60 w. peak C.C. phone. Output 40 w. to aerial. Compact and self-contained. Prov. for V.F.O. £29.10.0

AMATEUR TRANSMITTER Model DX-100U

Covers all amateur bands from 160-10 metres. Self-contained including Power Supply. £78.10.0
Modulator and V.F.O.

"GLOUCESTER" EQUIPMENT CABINET

46½ x 30 x 21 in. deep. Mk. I houses Record Player, Stereo Amplifier, F.M. Tuner, records, etc. Mk. II will house a Tape Deck in addition. Left in the white for finish to personal taste.

Mk. I ... £15.18.6 Mk. II ... £17.8.6

"COTSWOLD" HI-FI SPEAKER SYSTEM KIT

Acoustically designed enclosure "in the white" 26 x 23 x 15½ in., housing a 12 in. bass speaker with 2 in. speech coil, elliptical middle speaker and pressure unit to cover the full frequency range of 30-20,000 c/s. Compete with speakers, cross-over unit, level control, etc. £19.18.6

COMPLETE MATCHED STEREO OUTFIT

Includes record player, amplifier and twin speaker systems (pedestal speaker legs optional, £42.10.0 extra). £42.10.0

AUDIO VALVE MILLIVOLTMETER AV-3U

1 mV. to 300 v. A.C. 10 c/s to 400 kc/s. £13.18.6

AUDIO WATTMETER Model AW-1U

Up to 25 w. continuous, 50 w. intermittent. £13.18.6

STEREO-HEAD BOOSTER USP-1

Input 2 mV. to 20 mV. Output adjustable from 20 mV. to 2 v. 40-20,000 c/s. Also suitable as high-gain monaural amplifier. £5.19.6

VAR. FREQ. OSCILLATOR VF-1U

From 160-10 m. Ideal for our DX-40U and similar transmitters. £10.12.0
Price inc. valves £8.19.6

Prices include free delivery UK
Deferred Terms
available on orders over £10

THE "GLOUCESTER"
EQUIPMENT CABINET

Please send me FREE CATALOGUE (Yes/No) _____

Full details of model(s) _____

Deferred Payments (Yes/No) _____

NAME _____

ADDRESS _____

PW4

DAYSTROM LTD.**DEPT. P.W.4, GLOUCESTER, ENGLAND**

A member of the Daystrom Group, manufacturers of the
WORLD'S LARGEST-SELLING ELECTRONIC KITS

Practical Wireless

VOL. XXXV, No. 638 APRIL 1960

Editorial and Advertisement
Offices:

PRACTICAL WIRELESS

George Newnes, Ltd., Tower House,
Southampton Street, Strand, W.C.2.

© George Newnes Ltd., 1960.

Phone: Temple Bar 4363.

Telegrams: Newnes, Rand, London.

Registered at the G.P.O. for trans-

mission by Canadian Magazine Post.

SUBSCRIPTION RATES

including postage for one year

Inland - - - - £1.3.0 per annum

Abroad - - - - £1.1.6 per annum

Canada - - - - 19s. per annum

Contents

| | Page |
|------------------------------------|------|
| Editorial | 1021 |
| Round the World of Wireless | 1022 |
| A Comprehensive Pre-amp | 1024 |
| Improving the 19 Set | 1027 |
| A Quality Octet | 1029 |
| On Your Wavelength | 1035 |
| Model Control Circuits | 1036 |
| Transistorised Super-regener- | |
| ator | 1039 |
| Miniature Add-in I.F. Stage | 1043 |
| Frequency Meter BC 221 | 1045 |
| Record Player and Cabinet | 1048 |
| Choosing Detector Circuits | 1051 |
| Simple Morse Oscillator | 1054 |
| Repairing "Staar" Motors | 1057 |
| Rectification and Smoothing | 1061 |
| A Repetitive Timer | 1062 |
| Becoming an Amateur | 1069 |
| Club News | 1073 |
| News from the Trade | 1077 |
| Open to Discussion | 1081 |

The Editor will be pleased to consider articles of a practical nature. Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor PRACTICAL WIRELESS, George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Owing to the rapid progress in the designs of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in PRACTICAL WIRELESS is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. PRACTICAL WIRELESS incorporates "Amateur Wireless."

IMPORT CONTROLS

WITH effect from Monday, November 9th, 1959, many controls on imports from the Dollar area, Western Europe and a number of other countries, were removed. Electrical equipment and apparatus was included in the list of freed goods although, as we stated in our Editorial in the January issue, the heading "Electrical equipment and apparatus" included valves but not transistors. We pointed out that relaxation of import control of transistors would be of benefit both to industry and to the home constructor. However, in reply to a Parliamentary Question, the President of the Board of Trade, Mr. Reginald Maudling, announced that, with effect from February 1st, control has been removed from a further number of Dollar imports. Transistors are no longer subject to import restrictions from the Dollar and Relaxation Areas although imports of Japanese transistors and transistorised radio sets will remain subject to control.

STEREOPHONIC BROADCASTING

SEVERAL systems have been proposed for the broadcasting of two-channel programmes but most have been over-complicated or expensive. The proposals have varied from the straightforward use of separate transmitters for each channel to methods of modulating the same carrier with two sets of information. For instance, experiments have been carried out using VHF with frequency modulation for one channel and amplitude modulation for the second channel. However, all of the techniques which have been given trials have been found to have several disadvantages. The system of stereophonic broadcasting which will eventually be used must be economical in the use of transmitted bandwidth and also compatible; listeners who do not wish to receive the programmes in stereophonic form must be able to receive them using their existing receivers without modification and the results to be expected from such receivers should be equivalent to those obtained from normal monophonic transmissions. A new system of stereophonic broadcasting has recently been proposed by Mullard Ltd. and seems to fulfil most of the requirements for such transmissions. The system utilises time multiple × communication techniques, is applicable to normal F.M. (Band II) transmissions and is also suitable for bilingual or other twin signal purposes. The system is summarised, in a report from the Mullard Research Laboratories, as follows: "The system is a twin-channel application of the principles of pulse amplitude time multiplexing under conditions in which the bandwidth, after multiplexing but before modulation of the transmitter, is restricted to a logical minimum. The system is essentially symmetrical in character . . . and leads, in particular, to simplicity and therefore economy in receiver design and construction. Its implementation would also require only minor modifications to normal F.M. broadcast transmitting equipment".

In view of the interest which will be aroused in this system we propose to deal with it in an article in our next issue and give some details of the circuitry employed although such information will naturally be tentative.

Our next issue, dated May, will be published on April 7th.

Round the World of Wireless

POTENTIAL AND CURRENT NEWS

Broadcast Receiving Licences

THE following statement shows the approximate number of Broadcast Receiving Licences in force at the end of December, 1959, in respect of wireless receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland. The numbers include Licences issued* to blind persons with without payment.

| Region | | Total |
|---------------------------|-------|-----------|
| London Postal | | 835,634 |
| Home Counties | | 799,813 |
| Midland | | 588,728 |
| North Eastern | | 656,252 |
| North Western | | 546,532 |
| South Western | | 473,047 |
| Wales and Border Counties | | 291,492 |
| <hr/> | | |
| Total England Wales | | 4,191,498 |
| Scotland | | 494,608 |
| Northern Ireland | | 145,087 |
| <hr/> | | |
| Grand Total | | 4,831,193 |

New NATO Headquarters

THE new NATO headquarters in Paris, inaugurated this month, has what is claimed to be the most up-to-date electro-acoustical installation of any public building in Europe, possibly the world. The equipment has been supplied by the Philips Organisation with the co-operation of its companies in Holland, Germany and Belgium. It will now be possible to feed transmissions from the NATO building directly into the Eurovision network. The camera set-up is such that it permits direct connection between crucial points in the building to broadcasting vans parked outside. Reporters, watching monitor screens, will be able to describe the scene. A simultaneous interpretation equipment for a thousand delegates has also been provided. This has been installed in the main council chamber, the Press theatre and in six smaller conference halls in the building. It involves hundreds of microphones and more than a thousand headsets and languages selectors as well as small personal loudspeakers for



Mr. A. T. Collins, Editor of PRACTICAL WIRELESS and Practical Television opens our film show held at Caxton Hall, Westminster, on January 22nd last in collaboration with Mullard Ltd. On Mr. Collins' left are Mr. C. H. Gardner and Mr. P. I. Nicholson of Mullard Ltd.

use in some of the more important conference rooms.

International Instrument Show

FOR the last five years B & K Laboratories Ltd. have organised the annual International Instrument Show, but there will be no I.I.S. this year, and, to appreciate the reason, it is necessary to recap on its origin. The idea was conceived in 1955 when all of the then existing "big shows" were national rather than international. However, this year there is certainly no reason why any British engineer should not compare products from overseas in at least one British show. B & K Laboratories Limited are not exhibition organisers and hope that specialists in this field will continue the trend towards larger and better international exhibitions.

New Depot at London Airport

A NEW service depot at London Airport has been opened by Marconi's Wireless Telegraph Co. Ltd. to replace the temporary one previously in use.

The new depot, which is in the No. 1 Maintenance Area and therefore conveniently situated,

is considerably larger than its predecessor and can handle a much wider range of work with greater speed and efficiency. All post-war Marconi airborne equipment can be serviced and kept up to its full specification and to the standards demanded by the Air Registration Board. The telephone number is Skyport 1039.

Suez Contract

A CONTRACT worth many thousands of pounds has been placed with Pye Telecommunications Limited by the Suez Canal Authority for the supply of VHF radio equipment for the control of the Authority's vessels in the Canal. The system will be used to direct tugboats, dredgers and other official craft in the Suez Canal from points on shore.

International Award

THE establishment of an annual award in memory of Guglielmo Marconi, the world-famed radio pioneer, is announced by Permindex, the World Trade Centre in Rome. This award will be made to the individual making the greatest contribution to the development

of Marconi's discoveries. Recipients will be chosen by a Committee composed of important international personalities, a member of the Marconi family and representatives of Permindex. This announcement followed the dedication of the Marconi obelisk, to be known as the Marconi Antenna, in the Piazza Italia around which are grouped the four majestic buildings shortly to be occupied by Permindex. To celebrate the occasion the Square itself was renamed Piazza Guglielmo Marconi. The prize consists of a small reproduction in gold of the obelisk to be executed by Commendator Ventrella, Italy's leading jeweller, under the supervision of Arturo Dazzi, the sculptor of the obelisk.

BBC Appointments

THE BBC announces the appointment of Mr. C. J. Dolan, A.M.I.E.E., as Engineer-in-Charge, Television, Belfast. This is a new post and it reflects the increase in BBC Television Service activities in Northern Ireland.

Mr. Dolan joined the Corporation in 1932 as an Assistant Maintenance Engineer in the London Control Room. Towards the end of the same year he was appointed to Glasgow, where he became Maintenance Engineer in 1936 and Senior Maintenance Engineer in 1941.

In 1952 Mr. Dolan transferred to the Scottish Television Unit in Glasgow and became a Senior Television Engineer later that year, which post he has held until taking up his new duties on 1st February, 1960.

The Hon. R. T. B. Wynn, C.B.E., will on April 19th retire from the position of Chief Engineer of the BBC after thirty-four years' service with the Corporation. He will be succeeded by Mr. F. C. McLean, C.B.E., Deputy Chief Engineer, who will have the title of Deputy Director of Engineering. The post of Deputy Chief Engineer will be abolished.

Mr. Wynn, who was born in North Wales, served with the Experimental Section, Designs Department, of the Marconi Wireless Telegraph Company at Writtle from 1922 to 1926. He was concerned with the first regular broadcasting transmissions in this country. His first post with the BBC was as Head

of the Technical Correspondence Department. He became Senior Superintendent Engineer in 1934 and was appointed Chief Engineer in 1952.


Obituary

THE Dubilier Condenser Co. (1925) Ltd. announce with regret the death on January 3rd of their technical director, Philip R. Coursey, B.Sc.(Eng.), M.I.E.E., F.Inst.P., F.Phys.Soc., M.R.I. He was 68 and was a well-known figure in the industry. He was with the Admiralty and the technical Press before joining Dubilier in 1923, and was the author of several books.

vision receivers in order to reduce (a) interference caused by them and (b) their susceptibility to interference other than that picked up by the aerial/earth installation. It deals also with anti-interference and communal aerial systems.

Methods of test for determining compliance with the various requirements of the standard are specified in detail.

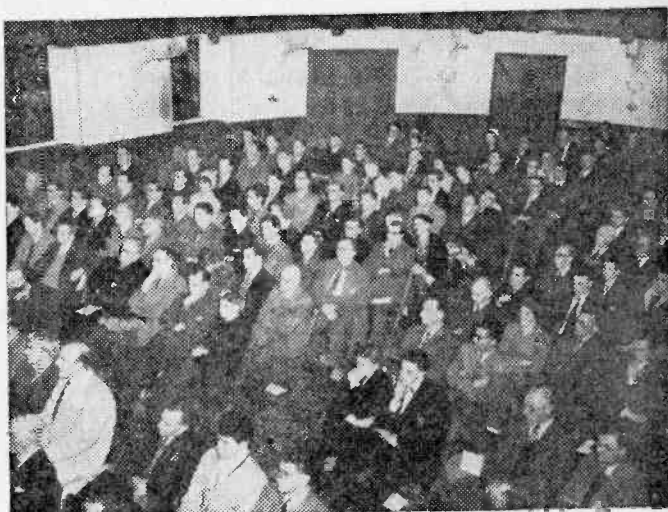The Foreword to the standard carries a recommendation on the choice of intermediate frequencies for television receivers, frequency-modulation sound broadcast receivers and combined television and frequency-modulation sound broadcast receivers.



A section of the large audience which was present at our recent film show.

New British Standard

Interference characteristics and performance of radio receiving equipment for aural and visual reproduction
(B.S. 905 : 1959)

THE work of one of B.I.S.'s many committees of experts, this revised publication brings up-to-date the first (1940) edition of B.S. 905, *Interference characteristics and performance of radio receiving equipment for aural and visual reproduction (excluding receivers for motor cycles and marine equipment)*. It specifies requirements which should be complied with in the design of sound radio and tele-

The new publication concludes with four appendices: they deal separately with: 'Recommendations for protection against atmospheric electricity', 'The standard reference aerial for long and medium wave bands', 'Measuring equipment' and 'Measurement of oscillator voltage appearing at the aerial terminals of television and F.M. sound broadcast receivers'.


Copies of this Standard may be obtained from the British Standards Institution, Sales Branch, 2 Park Street, London W.1. Price 12s. 6d. (Postage will be charged extra to non-subscribers).

Comprehensive Pre-Amp

(Continued from page 954 of the March issue)

FURTHER CONSTRUCTIONAL DETAILS

By R. Taylor

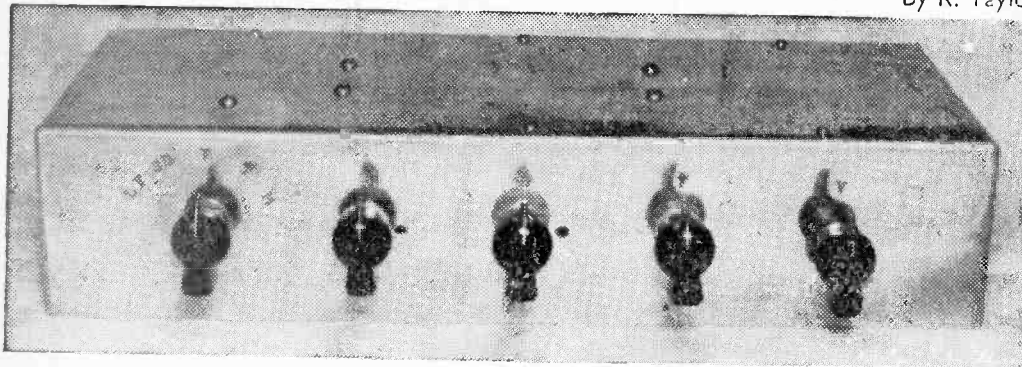

Front view of the completed amplifier.

IN the previous article, details of the circuit and a complete list of components were given. The chassis drilling details were also given and having drilled the holes in the chassis for mounting switches, potentiometers and coaxial sockets, this should be set on one side. The components for group board (1) should be placed in position on the appropriate tags (Fig. 4a), soldered, and the excess wire removed. As will

On the opposite side of the board a 470k resistor links tag (4) to (6). Further down the group board two resistors are mounted diagonally across tags; from tag (8) a 100k resistor terminates at tag (9) on the opposite of the group board. Similarly a 270k resistor from tag (9) terminates on the opposite side at tag (10). Note also the shorting links in insulated wire from tags (1) to (9), (2) to (8) and (7) to (10).

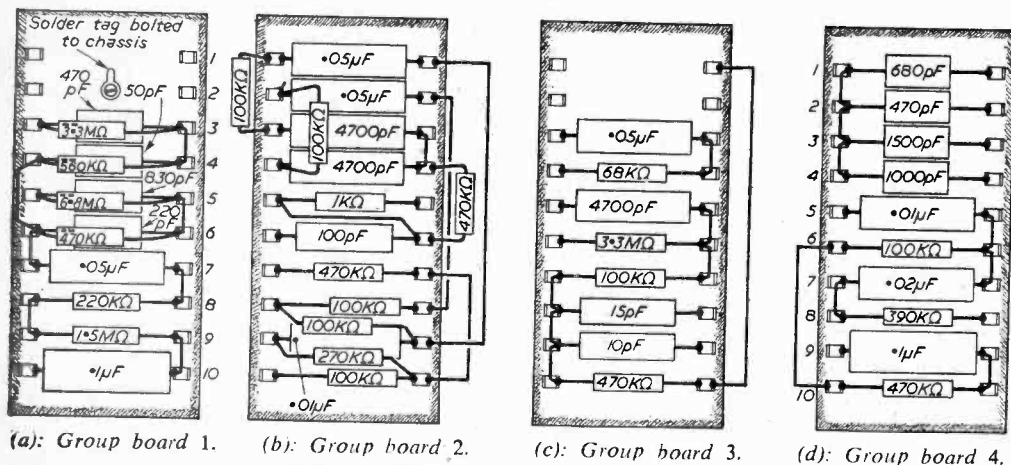


Fig. 4.—Wiring of the four group boards.

be seen, some of the components are joined in series across the tags, e.g. (3), (4), (5) and (6), and some are linked by means of connecting wire, which may be bare wire when going from tag (3) to (4), etc., but must be insulated if bypassing a tag, e.g., a link from tag (4) to tag (6).

Assembly

The assembly of components on group board (2) (Fig. 4b) should be completed in a similar manner. It will be noted that a 100k resistor links tag (1) to (3), and another 100k resistor links tag (2) to (4).

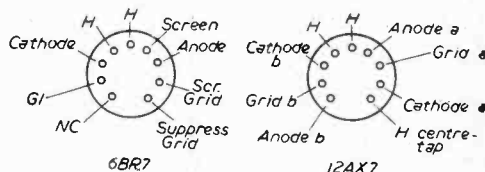


Fig. 4a.—Valve base wiring details.

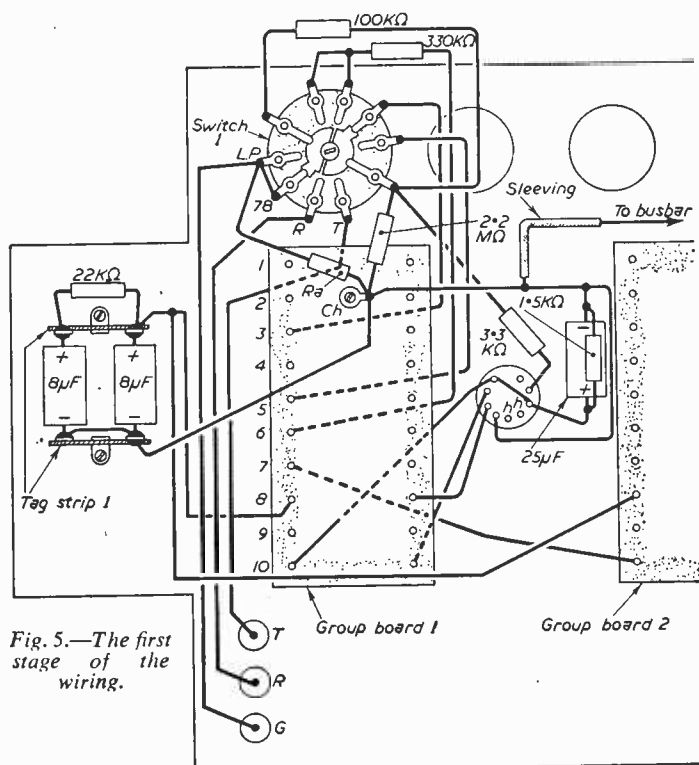


Fig. 5.—The first stage of the wiring.

Group boards (3) and (4) (Figs. 4c and 4d) are similarly assembled, and then all four group boards may be bolted to chassis, with a spacer nut between paxolin and chassis to allow for the passage of connecting wires.

Group board (1), is secured at one end by the passage of a bolt (head outside the chassis) through the normal eyelet hole, and secured by a nut, but at the end nearest to the controls, a hole is drilled midway between tags (2) and (2), for the securing bolt and nut. A soldering tag is located underneath the nut, and this is the only earth connection to chassis. A length of heavy gauge copper wire (at least 18s.w.g.) should be run from this tag, which is terminated across tags (1) and (1) of group board (3). The position of the wire relative to other components can be seen from the main wiring diagrams, and must be insulated by sleeving where it is liable to contact other components, or the chassis, other than those to be directly

joined to it. If switch 2 (three-pole, three-way) is liable to foul this earth bus-bar, the termination should be made to tags (2) and (2) on the group board (3). The shorting link from tags (1) to (10) on this group board must be correspondingly altered, i.e., tags (2) to (10).

Other Components

The switches, potentiometers and coaxial sockets may now be attached to the chassis, and then the brackets holding the valve sockets. For the next stage of construction reference should be made to Fig. 5. It should be noted that the valve bases shown in Fig. 5 and Fig. 7 are depicted as if mounted in a vertical position, in order that the wiring may be more easily identified.

Screening leads are run from the coaxial input sockets to switch 1 (two-pole, four-way), the ends of the screens being connected together and soldered to a wire which is then joined to the earth bus-bar. Care must be taken to avoid shorting between the screens and other components. It should be noted that the Gram. input is linked to ways 1 and 2 of the switch,

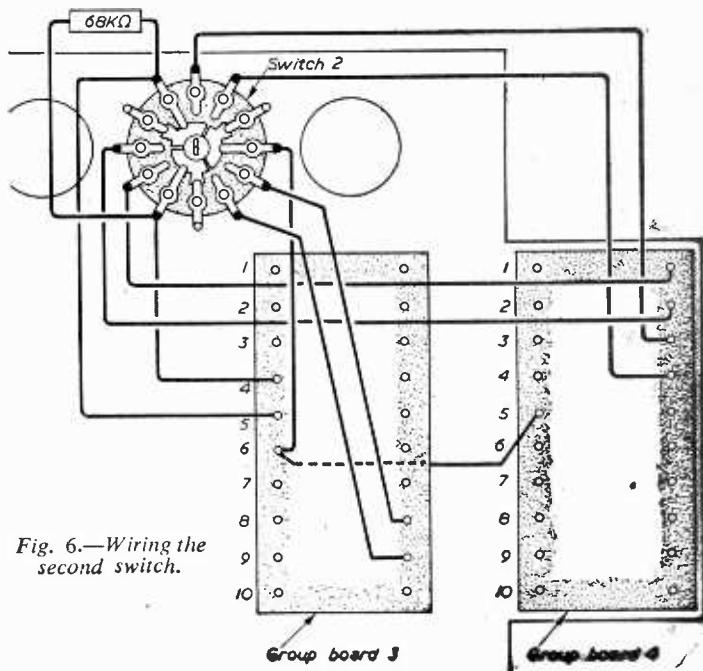


Fig. 6.—Wiring the second switch.

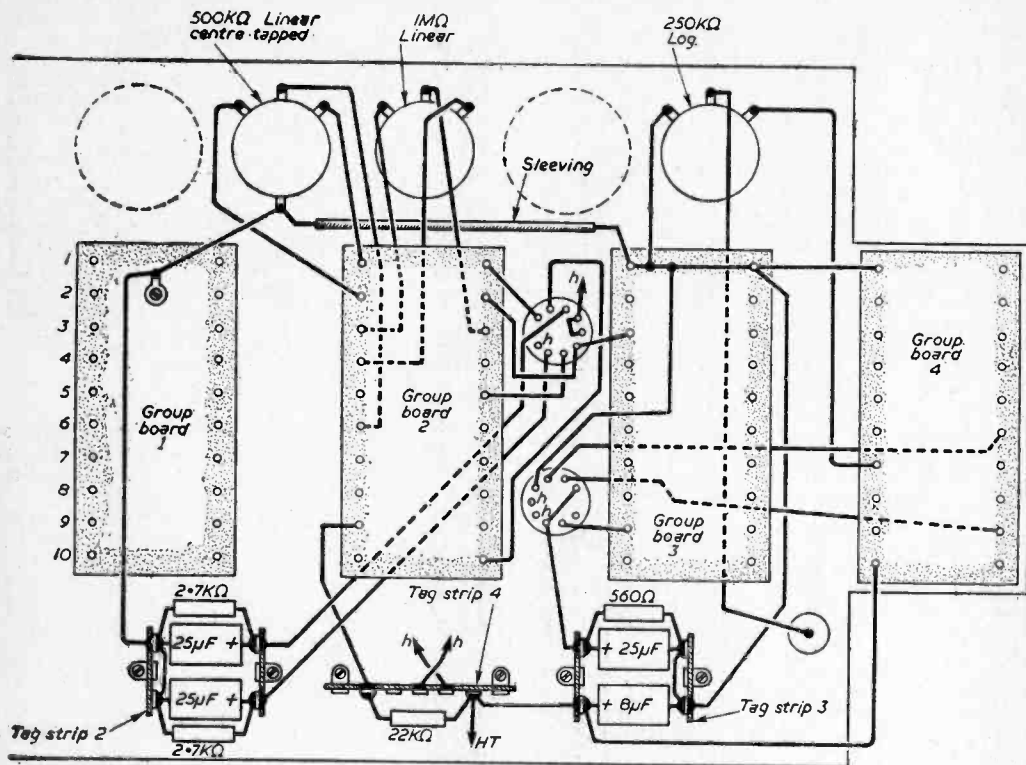
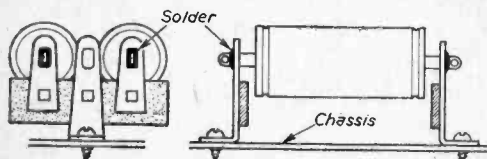


Fig. 7.—Completing the wiring.

The other wiring is straightforward, and dotted wiring signifies passage beneath the group board. The bias resistor and capacitor for this stage are sandwiched between the valve bracket and group board (3). The $8\mu\text{F}$ electrolytics are mounted on tag strips soldered as shown

Fig. 8.—The 8 and $25\mu\text{F}$ condensers are soldered to tag strips for mounting on the chassis.

in Fig. 8, and bolted to chassis, with a 22k resistor linking the positive ends. It should be remembered that resistor R_a may have to be changed if the output of the pick-up is greater than 59mV . The modified circuits for other pick-ups were shown in Fig. 2 (last month).

Final Wiring

This stage having been completed, the wiring to the other switch (three-pole, three way), as shown in Fig. 6, may now be undertaken. No difficulty should be found in this stage, and then the final section can be started (Fig. 7).

The mounting of the electrolytic capacitors on tag strips (2) and (3) is identical to that used for

tag strip (1) (Fig. 8); tag strip (5) (Bulgin T 24) is used only as an anchoring strip.

The electric power supply from the main amplifier or power pack is taken to a junction block on the rear of the chassis. Wires are then fed through a hole in the chassis, protected by a rubber grommet, from the junction block to the anchoring tag strip (5), but only the tags insulated from the chassis are used. The heater wiring consists of an insulated pair of tightly twisted wires run from tag strip to V3 (6BR7), and then on to V2 (12AX7), and a separate pair from the tag strip to V1 (6BR7).

The power requirements are 250-300V H.T., and 6.3V at 0.6A, centre tapped to earth.

JOIN THE PRACTICAL GROUP

PRACTICAL TELEVISION ... 1/6

Every Month.

PRACTICAL MECHANICS ... 1/3

Every Month.

Devoted to Mechanics, Science and Invention.

PRACTICAL MOTORIST ... 1/6

Every Month.

PRACTICAL HOUSEHOLDER ... 1/3


Every Month.

The "No. 19" Set

FURTHER IMPROVEMENTS

By D. W. Dillon

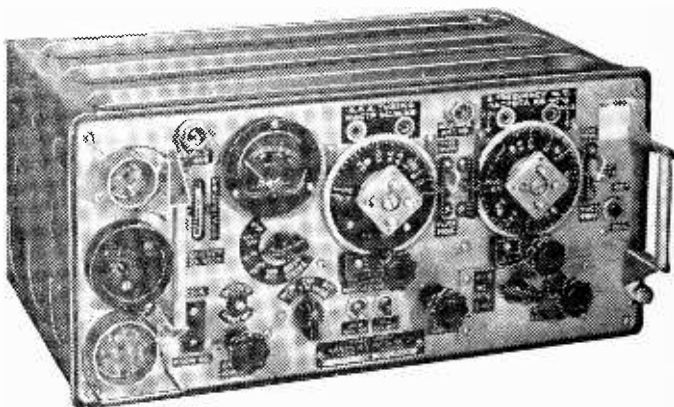(Continued from page 962 of the March issue)



AFTER the modifications for 6V operation and to the tank coil, etc., have been carried out as described last month, the set is ready for trial.

Intermediate Testing

For testing, a suitable power unit supplying 250-300V and 6.3V is necessary. If only the receiver portion is required, a power unit similar to that shown in Fig. 4 should be constructed or purchased. If, however, the transmitter portion is also required, the circuit of Fig. 5, which includes a relay supply, should be constructed. The smaller power unit could also contain a small speaker, the connections to it being through the chassis and the unused 500V pin on the power socket. The circuit for an output stage will be given later.

The power unit is connected to the set, switched on, and a pair of low impedance headphones plugged into the new jack. The P.A. tuning should be set to approximately the same frequency as the main tuning. A long wire aerial is attached to the feed-through insulator. Rotation of the aerial tuning condenser should show a point where a great increase of signal level, or noise, results. The R.F. gain control is turned down, the AVC off, and the receiver tuned into a signal. No movement of the AVC meter should result. If all works correctly, the next stage of alteration may be commenced.

Selectivity

The most important part of the receiver modifications is the improvement of the selectivity. Although the replacement of the fixed condensers in the I.F.T. cans, removal of damping resistors, and complete realignment does help greatly, and has, in fact, been carried out on the author's set, the need was felt for even more selectivity. In the circuit to be described, this modification need not be carried out, although it is advisable to do so. Until a few years ago, the only solution to this problem would have been in the use of a crystal filter, involving the

entire rebuilding of the second I.F. stage, but recently the idea of the Q-multiplier circuit has been imported from the U.S.A. A circuit suitable for use in the "19" set is shown in Fig. 6.

The 6K7 valveholder beside the aerial tuning unit (Fig. 3, February issue) is removed by filing the tops of the aluminium rivets, and a B9A valveholder mounted on small aluminium strips. Holes are drilled in the chassis to hold an I.F.T. can over the valve, with the valve in one corner of it. A coaxial lead is connected to pin 3 (anode) of the 6K8 frequency changer (V2A). The outer sheath is not connected at this end. Coil L1 is mounted at the bottom of the can in such a position that the core can be adjusted from the side of the set. The coil L2 is mounted directly above L1, and the coil-shaped trimmer at the top of the can. The condensers C3 and C4 should be high stability 2 per cent or 5 per cent types. The 5k wirewound potentiometer is used to vary the sensitivity, and can be substituted for the B set gain control; but if the transmitter modifications are to be carried out, it can be wired in temporarily

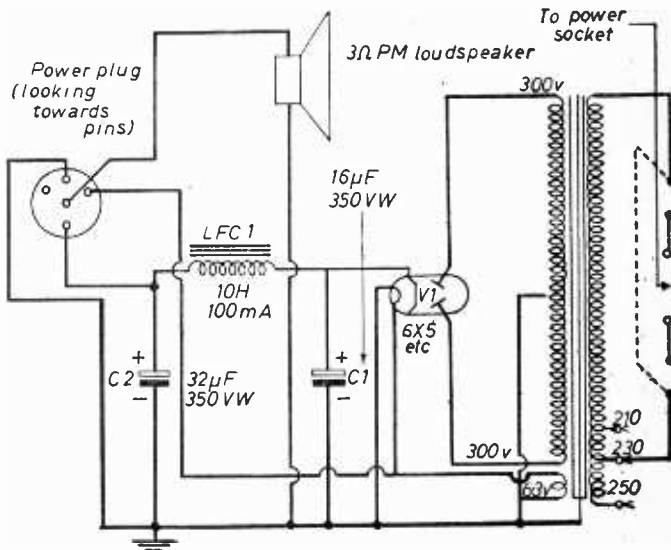


Fig. 4.—Circuit of a power unit.

≡ A Quality Octet ≡

A SENSITIVE VHF/FM RECEIVER

By A. Sydenham

THIS receiver was built around the well-known RF27 unit, a chassis which has proved its worth, being virtually a ready made VHF front end. The hazards of F.M. front-end construction—the length and position of practically every wire; the orientation of each component, etc.—is therefore successfully bypassed and a complete self-powered—and surprisingly efficient—receiver results, the cost of which is less than that of most unpowered front ends. The inductors contained in the unit do not need rewinding as by removing all trimmers but one the operating frequency rises in excess of 100Mc/s. Where an RF26 unit is available it might be possible to use this instead of the RF27, but the mixer and oscillator inductors will need to be rewound to $4\frac{1}{2}$ and $3\frac{1}{2}$ turns respectively; however, as the author has no practical knowledge of the RF26 no further reference to it will be made.

Circuit

The complete receiver, the circuit of which is illustrated in Figs. 1 and 2, brings in the desired transmissions at full loudspeaker strength in a fringe area, the aerial used being a thin wire dipole, attic mounted.

The diagrams are largely self-explanatory and it will be seen that the I.F./Discriminator strip is

mounted on an inverted "L" of tinfoil secured to the side runner of the RF27 unit (see Fig. 3) so that all valves are operated upright.

The audio and power sections are contained on a separate chassis the same size as the R.F. unit, and spaced one inch from it so that the I.F. transformer cores are accessible. The layout used gives thorough inter-section screening. Front and rear panels $\frac{1}{2}$ in. thick retain both chassis simultaneously.

Note that in Figs. 1 and 2, components are numbered separately. In Fig. 1 those items with only the value specified beside them are already *in situ* and are only mentioned for reference; the remainder (with reference and value) must be added. The circuit diagram of an unmodified RF27 unit has appeared in previous issues and will not be repeated here.

Modifying the R.F. Unit

Remove all trimmers above and below chassis except the one adjacent to the oscillator inductor at the rear and also any resistors connected across them. Remove the aerial socket, front panel trimmer, both inductors in the front compartment and also the one in the third compartment together with its parallel-connected 10k resistor. Remove the short length of coaxial cable connected to the

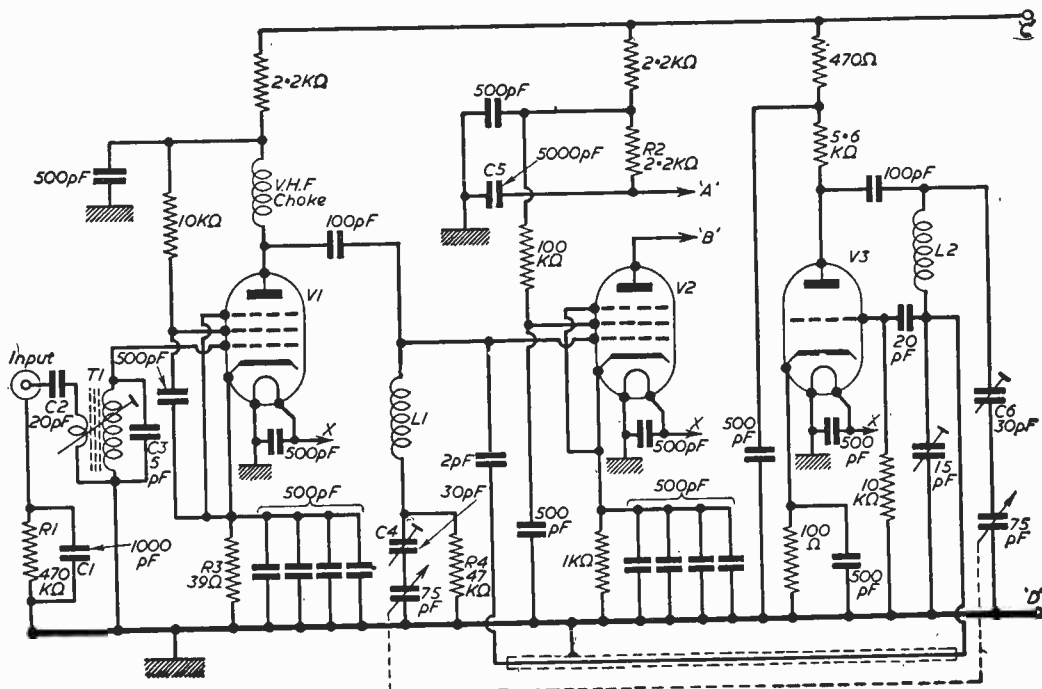


Fig. 1.—Circuit diagram of the modified RF27.

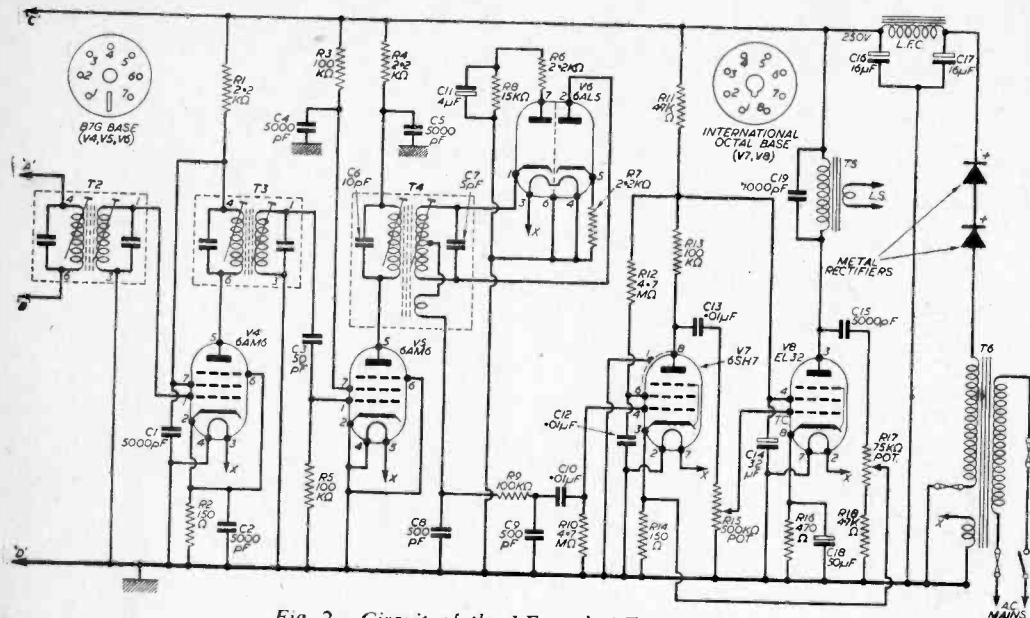


Fig. 2.—Circuit of the I.F. and A.F. amplifiers.

Jones plug and put aside, for use later, the stand-off insulator associated with it. Prise off both lugs at the rear of chassis and re-position the stand-off insulator (the one adjacent to the oscillator inductor which carries the L.T. wiring) in one of the vacated holes. Remove the dial bulb holder and locate the dial fixing bolt and loosen it, together with another at the bottom right-hand side of the dial. Take off the dial after disconnecting the live lead of the dial bulb. Remove the panel and the handle so that the chassis stands level. Either remove or disconnect the front section of the 3-gang tuning capacitor.

Disconnect the wire which runs through a rubber grommet in the chassis connecting the mixer inductor to one section of the fixed vanes of the tuning capacitor. Take a 30pF beehive trimmer

(C4) and solder a length of wire to its long terminal, and pass it through the grommet, soldering the free end of the wire to the fixed vanes and the free trimmer terminal to the inductor terminal at its base. Connect a 47k resistor (R4) from chassis to the junction of the trimmer and inductor. Insert a 30pF beehive trimmer (C6) similarly in the oscillator section, but no resistor is required here. For both of these operations a pencil bit is necessary on the soldering iron. Screw both trimmers fully home then unscrew one half a turn, leaving both available to assist trimming later.

Aerial Coil

Remove the 10k resistor feeding the anode of V1 and insert the VHF choke in its place. Replace,

COMPONENTS LIST

For R.F. unit.

Capacitors—

C1—1,000pF.
C2—20pF.
C3—5pF.
C4, 6—30pF trimmers.
C5—5,000pF.

T1—QAFM (Osmor).

Choke—VHF type (Osmor).

Aerial socket—Belling Lee.

Resistors—

R1—470k.
R2—2.2k.
R3—39Ω.
R4—47k.

For I.F. Strip and Audio Sections.

Capacitors—

C1, 2, 4, 5, 15—5,000pF.
C3—50pF.
C6—10pF.
C7—5pF.
C8, 9—500pF.

Resistors—

R1, 4, 6, 7—2.2k.
R2, 14—150Ω.
R3, 5, 9, 13—100k.
R8—15k.
R10, 12—4.7M.
R11, 18—4.7k.

C10, 12, 13—0.01μF.
C11—4μF. elec.
C14—32μF. elec.
C16, 17—16μF. elec.
C18—50μF. elec.
C19—1,000pF.

Valves—V4, 5—6AM6
V6—6AL5.
V7—6SH7.
V8—EL32.

Rectifiers—RM3 (2).

LFC—midget 10H.

Chassis—16s.w.g. aluminium four sided type, size 8½ x 4½ x 1½in.

Transformers—T2, 3—QIFM (2) (Osmor).
T4—(see text).

T5—Output transformer.

T6—Mains isolating transformer (see text).

Valve bases—Three B7G, Two I.O.

also, the bias resistor of this valve by one of 39Ω (R3). Prise out the rubber grommet in the first compartment and into the vacated hole plug the aerial transformer, T1, upside down and with its can removed; a perfect fit will result.

After removing the S-shaped spring retainer on the rear flange of the chassis, bolt the aerial input socket to a piece of Paxolin and fix the assembly in position, using the existing holes in the chassis.

secondary. The completed windings are covered with cellulose cement, capacitors C6, C7, inserted and the can replaced after making a note of the terminations.

The bracket is retained by means of the bolts securing the tuning capacitor and the necessary holes should be drilled before wiring up is commenced. When correctly mounted the I.F. transformer cans should be level with the top of the RF27 side flange. The stand-off insulator retrieved earlier is positioned centrally on the underside of the bracket and forms the H.T. feed point for this section.

Wiring up may now be commenced, it being essential to use modern, miniature V.H.F. capacitors to maintain efficiency and prevent the strip from becoming unduly congested. Normal short wave wiring techniques (not shown in the diagrams) should be employed and care taken to ensure that the I.F. transformer cores remain accessible. Cans for

V4 and V5 can be made by bending lengths of thin tinplate around a suitable size tubular capacitor so that they fit comfortably over the valves. These cans should be connected to chassis.

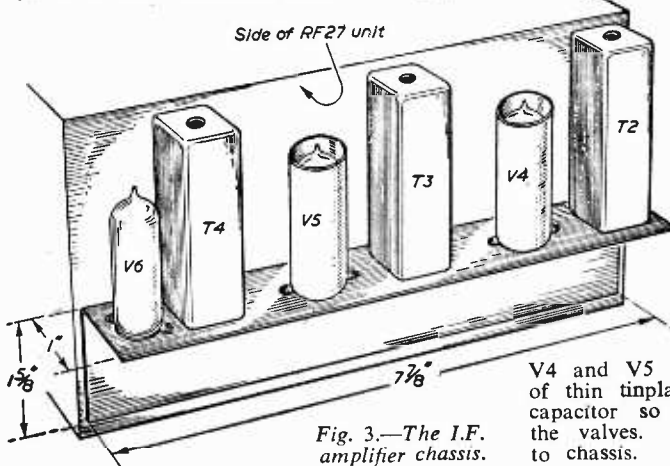


Fig. 3.—The I.F. amplifier chassis.

Connect up C1, C2, R1, and run a length of coaxial cable along the chassis and through to T1.

Removal of the Jones plug is optional as the rear panel can be shaped to cover the points.

The I.F. Strip

The inverted "L" of tinplate is now prepared and main components mounted as illustrated in Fig. 3. The figures in Fig. 2, incidentally, refer to the correct connecting terminals of the I.F. transformers and appear on the bases. For convenience they should be copied off on to the cans prior to mounting as the originals become obscured.

A commercially-made ratio discriminator transformer can be used if desired, but that used in the prototype was home-made as experience shows that this can be done successfully (and more cheaply). A dual-core former and can, type Aladdin PP5937-TV1, is required and is wound as follows: Primary, 28 turns 28s.w.g. enamelled copper wire closewound; Secondary, 15 + 15 turns 28s.w.g. enamelled copper wire, bifilar wound and spaced 3/16in. from primary; Tertiary, 10 turns 36s.w.g. D.S.C. wire wound over a paper interlay over primary at the end farthest from the

Audio and Power Section

The layout is shown in Fig. 4 and no difficulty should be experienced here. Loudspeaker trans-

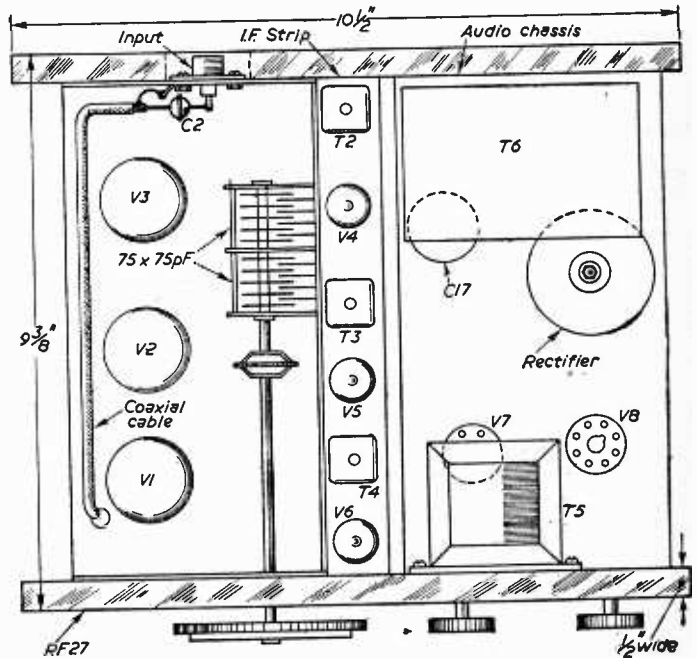


Fig. 4.—Above-chassis layout.

former T5 is mounted on the inside of the front panel and C18 forms part of a triple electrolytic type, though adequate space is available for a separate component. In the prototype, half-wave rectification supplies 250V at 80mA for the H.T. line with negligible hum level. Other arrangements are possible and full-wave rectification in conjunction with a valve rectifier might make possible the use of one less smoothing capacitor. The EL32 output pentode was chosen for its moderate current demands. The volume control is placed in its grid circuit, this position being found superior to the more usual one of associating it with V7 grid. The L.T. requirements are 6.3V at 3A.

Miscellaneous

When both chassis are complete, front and rear panels may be prepared and bolted in position, care being taken when refixing the dial to ensure that no fouling occurs. If the first section of the

(Continued on page 1058)

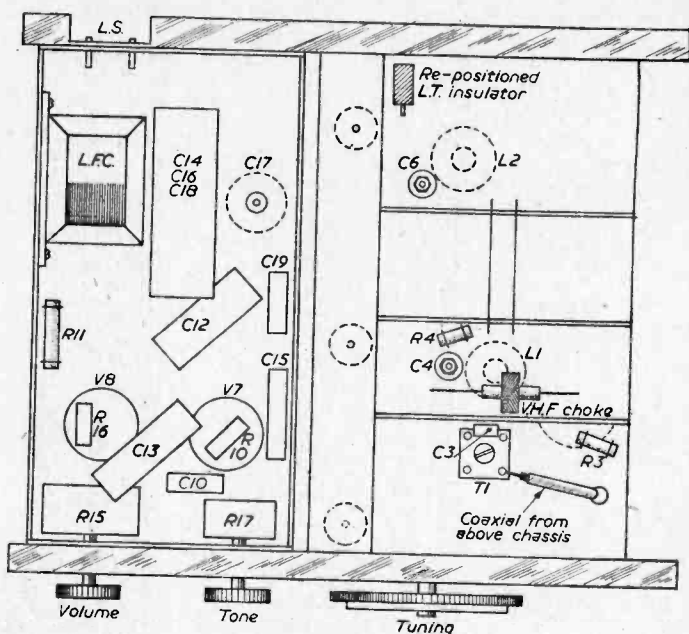


Fig. 5.—Under-chassis layout.

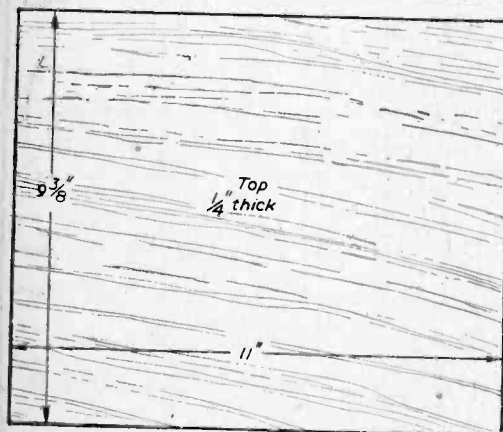
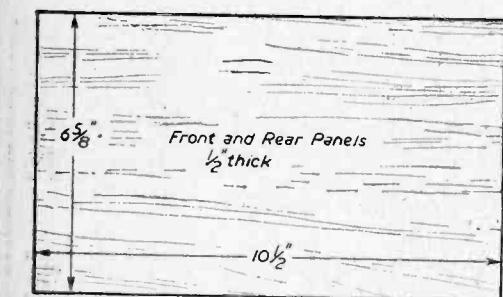


Fig. 6.—Dimensions of the front and rear panels.


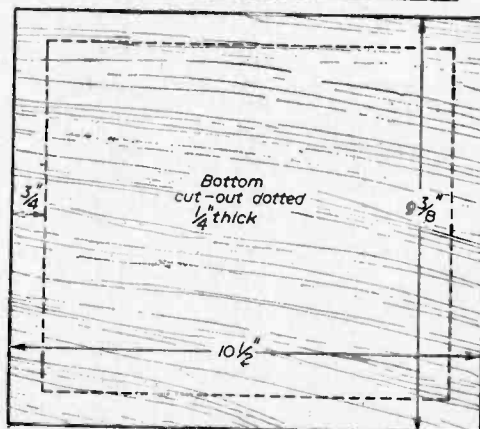
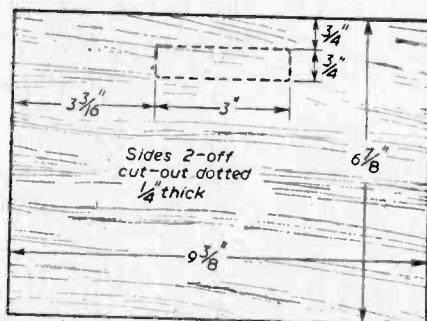


Fig. 7.—Dimensions of the sides and bottom.

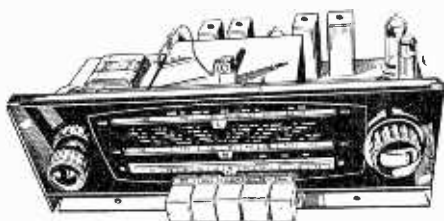BRAND NEW AM/FM (V.H.F.) RADIOGRAM CHASSIS AT £13.6.8. (P. & P. 10/-)



Why buy a F.M. Tuner at the same price?

Tapped input 220-225 v. and 226-250 v. A.C. ONLY. Chassis size 15 x 6 1/2 x 5 1/2 in. high. New manufacture. Dial 1 1/2 x 4 in. in gold and black.

Pick-up, Extension Speaker, Ae., E., and Dipole sockets. Five "piano" push buttons—OFF, L.W., M.W., F.M. and Gram. Aligned and tested. With all valves & O.P. Transformer. Tone Control Fitted.

Covers 1,000-1,900 M.: 200-500 M.: 88-89 Mc/s.

Valves EZ80 rect., ECH81, EF89, EABC80, EL84, ECC85.

Speaker & Cabinet to fit chassis, (table model), 47/6. 10 x 6 in. ELLIPTICAL SPEAKER, 20/-, to purchasers of this chassis.

TERMS:—(Chassis) £4.16.8 down + 10/- carr. and 6 Monthly Payments of 30/-, or with Cabinet & Speaker £5.9.2 down and 7 Monthly Payments of 32/-.



COMPLETE RADIO FOR ONLY £10.10.0 carr. pd.

Size 19 x 13 x 7 1/2 in. or Chassis and dial for £8 (carr. paid.). Chassis Size 15 x 6 1/2 x 5 1/2 in.; 1,000-2,000 M.: 200-550 and 16-54 M. Mains (200-250 v. A.C.) and O.P. Trans. (3 ohm); Gram., Aer., E., Ext. L.S. Sockets; New Mullard Valves ECH42, EF41, EBC41, EL41, EZ40 and Magic Eye EM41. Dial 15 x 3 in. Fully aligned. Fantastic value for money.

6 1/2 in. or 6 x 4 in. speaker fitted to cabinet. New Manufacture.

BATTERY ELIMINATOR. Converts your Battery Set to Mains. For 4 Low Consumption Valves (DK range). 90 v. 15 ma. and 1.4 v. 125 ma., 42/6 (26 post). 200-250 v. A.C. Size 5 1/2 x 3 1/2 x 2 in. Also for 250 ma. 1.4 v. and 90 v. 15 ma. at same price. Specify which, or give Valve line-up.


TELERECTION AERIAL. "Twenty-20" adjustable set top or table for Bands 1, 2 and 3. "Gold" finished rods and mounting. List Price 42/-. Our price 30/- (carr. paid).

50 SILVERED MICA AND CERAMIC CONDENSERS, 10/-, 50 RESISTORS, 5/-, ALL DIFFERENT VALUES.



COMPLETE TAPE RECORDER FOR ONLY £19.10.0

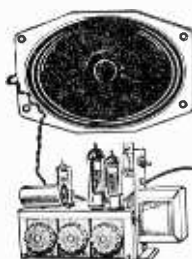B.S.R. deck. Two-tone leatherette case, Acos crystal mike, 850ft. tape extra spool. On/Off Tone and Vol. 7 x 4 in. Speaker. 1 1/2 hrs. playing time. Single speed 3 1/2 in./sec., fast forward and reverse, mike and radio inputs, ext. speaker socket; cannot be accidentally erased. 13 1/2 x 12 x 8 in. Weight 20 lbs. 12 months guarantee. Carr. 7/6 extra. Terms: £8 down and 6 monthly payments of 50/-.



3-VALVE AMPLIFIER (INC. RECT.). Capable of giving 6 watts. Mains and output transformers. Valves ECC81, EL84 and Rect. 3 Controls, volume, bass and treble. On/Off switch. Fully guaranteed. Chassis size 6 1/2 x 3 x 2 1/2 in. 6 1/2 in. round or 7 x 4 in. elliptical speaker, state which. Not suitable for microphone input.

67/- (3/- p. & p.).



LISTEN WITHOUT INTERFERENCE

Fully built V.H.F./F.M. Tuner for £5.10.0 (3/- post). Covers 88-98 Mc/sec. Wired, aligned and tested. 4 Mullard valves; for use up to 40 miles from transmitter. FRINGE MODEL for above this (5 valves), £6 (p. & p. 3/-). External H.T. and L.T. supplies reqd. for both of foregoing. BUT a complete V.H.F. set, four valves, with mains transformer, (with above frequency coverage) can be supplied for ONLY £8.8.0 (4/- carr.). Cheap room dipole 10/-, 300 ohm twin feeder, 6d. yd. All with 12 months' guarantee.



GRAMOPHONE AMPLIFIER with 5 in. SPEAKER. On Fabric-covered Baffle 12 1/2 x 5 in. Mains and Output Transformers, Metal Rectifier, ECL82 Valve. Tone and

Volume Controls. On/Off switch. Plenty of Volume. Fully Guaranteed. Two Knobs supplied. Ready to play. Useful for Stereo.

ONLY 57/-, post 3/-

BEEC "PIONEER" RADIO IN MAKER'S CARTON. Valves DK96, DF96, DAF96, DL96. Beec Ever-Ready Battery




BK93, 15/6 extra. Two Short Wavebands 2.5 to 7 Mc/s and 6.5 to 17 Mc/s. Cabinet, 12 x 7 1/2 x 6 in. ONLY £4.10.0 (2/6 p. & p.) (MW and SW £4.15.0 plus 2/6 p. & p.). In kit form with instructions and fully wired coil pack. Two Short Wavebands £4. One M.W. and S.W. £4.5.0. Plus 2/6 p. & p. Separate items supplied. Send for List.

TAKE A CHANCE. We have surplus to present manufacturing requirements tens of thousands of resistors, silvered mica, tubulars, volume controls, electrolytics, valve holders, etc. SEND US 20/- for a bargain parcel of new goods. Our good name is your guarantee. Money back if not satisfied. State preference of types of goods.

SIX TRANSISTOR SUPERHET KIT

£8.19.6

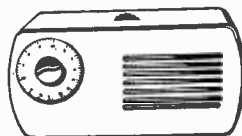Med. and L.W.: Printed Circuit; Instruction Book. Internal aerial. All items supplied separately. Write for price list. Battery, 9 v., PP4 2/6.



Send 6d. (stamps will do) for our illustrated catalogue of the above items and others. All New Goods. Delivery by return. Terms:—One-third down and balance plus 7/6 in four equal monthly payments. Postage with down payment. (C.O.D. 2/- extra.)

SEE SPECIAL TERMS FOR A.M./F.M. CHASSIS AND TAPE RECORDER.

Posted Orders to Camberley Please.

See additional advertisement on page 1068

GLADSTONE RADIO—58A HIGH STREET, CAMBERLEY, SURREY. Tel. 22791

Also at 3 Church Road, Lawrence Hill, Bristol 5.
Camberley, closed Saturdays. Bristol, closed Wed., afternoons

CIRCUITS FOR AUDIO AMPLIFIERS

-a book every enthusiast will want!

This new Mullard publication is a practical manual for every audio enthusiast. In addition to describing twelve of the most popular Mullard circuits, it has introductory chapters on many of the theoretical and practical aspects of high quality sound reproduction.

Whether you are interested in disc or tape, monaural or stereo, you will find that "Circuits for Audio Amplifiers" gives just the sort of information you need.

This informative book costs only 8/6. The demand for it is high, so get your copy now from your local radio dealer.

Mullard



MULLARD LIMITED • MULLARD HOUSE • TORRINGTON PLACE

LONDON W.C.1
MVM423A


KINGSMERE SUPPLIES LIMITED

Insured Post 1/-, over £2 Free. (Export extra.)
Single valves, post 6d.

MAIL ORDER HOUSE

TERMS: Remit with Order or C.O.D.

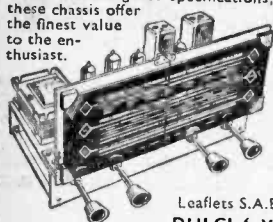Built to the highest specifications, these chassis offer the finest value to the enthusiast.



Leaflets S.A.E.

ALL BRITISH RADIOGRAM CHASSIS. 3 WAVEBANDS 5 MULLARD VALVES
ECH81, EF89, E8C81, EL84, EZ80

Brand new and guar. A.C. 200/250 v. Short-Medium-Long-Gram. P.U. High Q dust core coils. Latest circuit technique. AVC and neg. feedback. 4 watts. Chassis size 13½ x 6 x 7in. high. Aligned and calibrated ready for use. Quality at Low Cost. Chassis isolated. H.P. Dep. £5 and five monthly of £1.

OUR PRICE £9.9.0

DULCI 6 VALVE AM-FM MODEL £18.18.0

Matched Speakers, 5in., 6½in., 8in. 17/6 ea. 10in. 25/-



The Brilliantly Successful

Monarch

BRAND NEW AND BOXED

OUR PRICE

£6.19.6

GARRARD 4-SPEED HIGH FIDELITY UNITS

Autochanger 121 Mk.11 10 gns. { Price inc. plug-in normal
Single Player TA Mk.11 8 gns. { heads. Stereo hds. £2 ex.

BRAND NEW

| | | | |
|------|-----|-------|-----|
| OZ4 | 6/- | 6BA6 | 7/6 |
| IR5 | 7/6 | 6BE6 | 7/6 |
| IS5 | 7/- | 6C4 | 5/- |
| IT4 | 6/- | 6D6 | 6/- |
| 2X2 | 3/6 | 6F6G | 7/6 |
| 3Q5 | 9/- | 6G6 | 5/6 |
| 3S4 | 7/6 | 6H6 | 3/6 |
| 3V4 | 7/6 | 6J5 | 5/6 |
| 5U4 | 7/6 | 6J6 | 5/6 |
| 5Y3G | 7/6 | 6J7G | 6/6 |
| 5Z4G | 9/6 | 6K6GT | 6/6 |
| 6AC7 | 5/- | 6K7G | 5/- |
| 6AC5 | 5/- | 6K7M | 7/6 |
| 6AL5 | 5/6 | 6K8G | 7/6 |
| 6AM6 | 5/- | 6N7M | 6/6 |
| 6AT6 | 7/6 | 6Q7G | 7/6 |
| 6BBG | 5/- | 6SA7M | 6/- |

VALVES

| | | | |
|--------|-----|---------|------|
| 6S17M | 6/6 | DF96 | 8/6 |
| 6SN7GT | 7/6 | DK96 | 8/6 |
| 6U5G | 5/- | DL96 | 8/6 |
| 6V6G | 6/- | EABCB80 | 8/6 |
| 6X5G | 6/6 | EB91 | 5/6 |
| 12AT7 | 8/- | EB41 | 8/6 |
| 12AU7 | 7/6 | EBF80 | 10/- |
| 12AX7 | 7/6 | ECC84 | 9/6 |
| 25Y5G | 9/6 | ECH42 | 10/6 |
| 12K7GT | 6/6 | ECL80 | 10/6 |
| 12Q7GT | 6/6 | ECL82 | 10/6 |
| 35L6 | 9/6 | EF39 | 5/6 |
| 35Z4 | 7/6 | EF41 | 9/6 |
| 807 | 5/6 | EF80 | 7/6 |
| 954 | 1/6 | EF91 | 5/6 |
| 956 | 2/6 | EF92 | 5/6 |
| DAF96 | 8/6 | EL32 | 5/- |

ALL GUARANTEED

| | | | |
|---------|------|----------|------|
| EL41 | 9/- | PCL82 | 11/6 |
| EL84 | 8/6 | PY80 | 7/6 |
| EM81 | 9/6 | PY81 | 9/6 |
| EY86 | 9/6 | PY82 | 7/6 |
| EZ40 | 10/- | PY83 | 9/6 |
| EZ80 | 7/6 | QP25 | 7/6 |
| E1143 | 1/6 | R3 | 9/- |
| HABCB80 | 10/6 | SP61 | 3/6 |
| 12/6 | | UF41 | 9/- |
| HVR2A | 6/- | UY41 | 7/6 |
| KT33C | 10/- | U22 | 8/- |
| MU14 | 9/- | VP23 | 6/6 |
| P61 | 3/6 | U76 | 6/6 |
| PCC84 | 8/- | VR105/30 | 9/- |
| PCF80 | 8/- | | |

FAMOUS MAKE

PLASTIC RECORDING TAPE

| | |
|------------------------------|------|
| Long Play 7in. reel, 1,700ft | 35/- |
| 5½in. reel, 1,200ft | 18/- |
| 5in. reel, 850ft | 21/- |
| 3in. reel, 225 ft. | 7/6 |
| Standard 7in. reel, 1,200ft | 22/6 |
| 5in. reel, 600ft | 15/- |
| Spare Plastic reels | 3/- |


"Instant" Bulk Tape Eraser and Head Defluxer, 200/250 v. A.C., 27/6. Leaflet, S.A.E.

ALFA MULTIMETER

300 microamp. 3in. Scale. 17 Ranges.
A.C. volts, 0-1,200 v. D.C. volts, 0-1,200 v.
D.C. Current, 0-300 mA.
Resistance, 0-20K and 0-20 meg.
Decibels, -20 to +37 db.

5 gns.

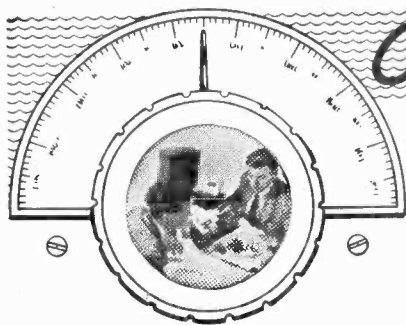25 FOAMCOURT WAY, FERRING, WORTHING, SUSSEX




On Your Wavelength

BY THERMION

for his amateur band transmitter, the driver and P.A. stages not yet having been built. To the left of the modulator is a self-contained direct measurement resistance/capacity bridge (built to a PRACTICAL WIRELESS circuit). In the window is an aerial tuning unit, 350V stabilised power pack and

FOLLOWING my article in the December 1959 issue on the lack of a real spirit of home construction in the world of amateur radio today. Mr. T. Sutton has written to me with reminiscences of his youth and says he remembers abstracting a piece from his mother's broomstick to make a former for a coil. The illustration opposite shows one of his early constructional efforts and the receiver is a 0-V-1 using two Hivac D210's which cost about 3s. 9d. each in those days. This set was built in 1934 when Mr. Sutton was fifteen. One of the Telsen coils with the aerial capacitor on the top can be seen in the picture. The headphones were bought for 2s. 6d. from a junk shop and were of German manufacture bearing the trade name of "Dr. Nesper". They had adjustable magnets and were very sensitive and also had a marked resonance in the middle of the audio band which was most useful for CW DX reception.

The illustration below is of Mr. D. W. Dillon in his den. All the gear shown (with the exception of the 19 set) is home-built and includes an 11-valve double conversion superhet covering 100kc/s to 30Mc/s. It has I.F.s of 1.6Mc/s and 50kc/s and contains a Q-multiplier (giving selectivity down to 50c/s), reflex I.F. stages and a 10W modulator. The large unit on the floor on the left is a 60W modulator and 750V power pack and on top of this is an 80m VFO with a measured accuracy of 0.0005 per cent. Both these units are

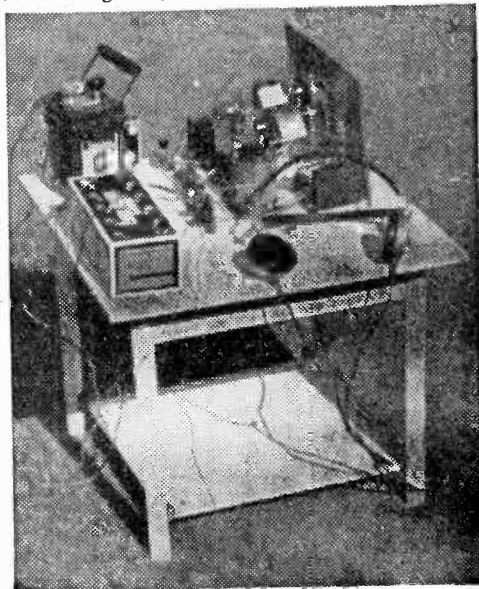


An early receiver built by Mr. T. Sutton.

a 4W 10m walkie-talkie. The 19 set shown has been considerably modified and is completely self-contained except for the aerial and microphone. Miniature valves have been used in the I.F. stages and a Q-multiplier installed. A link coupled aerial tuning unit is built in and enables loading into almost any aerial.

Our Film Show

ONCE again our film show at Caxton Hall was attended by several hundred of our readers and once again I was able to meet many old friends and we had a most enjoyable evening chatting about old times and the recent advances made in the world of radio. Three very interesting films were shown at the meeting which were presented by Mr. C. H. Gardner of Mullard Ltd., who introduced Mr. A. T. Collins, Editor of this, and our companion journal, *Practical Television*. A tribute was paid to our late Editor Mr. F. J. Camm by Mr. C. Clark Ramsay of Newnes Book Sales Department.

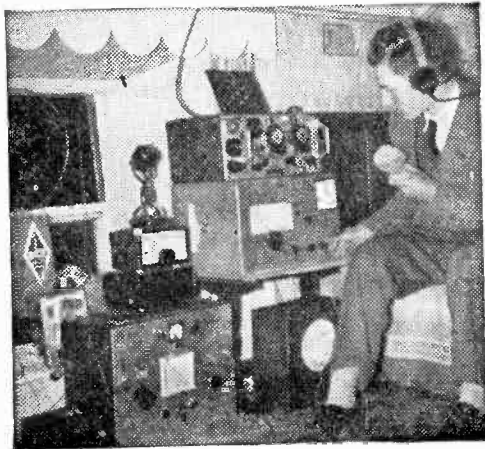All in all, with the help of the free refreshments provided to all in the interval, a very enjoyable evening was had, and all of those to whom I spoke expressed the wish that the film show would become an annual occurrence.



D. W. Dillon in his den.

Model-Control Circuits

SIMPLE RECEIVERS FOR OPERATING RELAYS

By C. Stone

MOST model control receivers employ simple circuits which can be made up in compact form. The best type of circuit depends on the purpose in view. For example, short range working with a powerful transmitter would require a much less sensitive receiver than would long range control, possibly with a low power transmitter only.

Valves

The gas-filled triode type of receiver is quite often used, and is fairly easy to adjust, and can be controlled at considerable range. A circuit of this kind is shown in Fig. 1, and may be used with the Hivac XFG1 valve, with 45V H.T. supply and 1½V for filament. The valve acts as a super-regenerative detector, and the anode current is

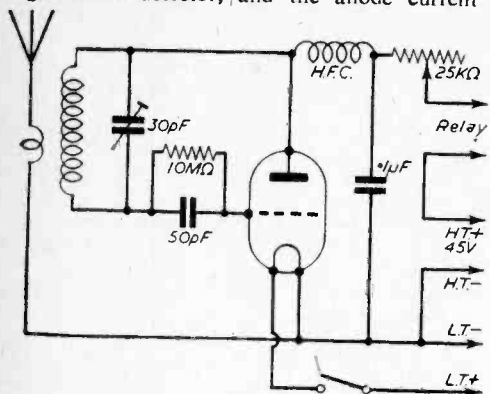


Fig. 1.—Circuit using a gas-filled triode.

normally up to 2mA or so, dropping to ½mA or so when the transmitter is keyed. Component values are not very critical, but a high value grid leak is necessary. The H.F. choke may be omitted if the H.T. circuit is taken to a centre tap on the coil.

The working life of the valve will be much increased if the anode current is kept low by setting the 25k potentiometer to a fairly high value. A good model control relay can be adjusted to operate with a current change of 0.1mA, so when only moderate range is needed, maximum anode current may be about 1mA, falling to perhaps ½mA when the transmitter is keyed. Valve life may also be extended by taking the 10MΩ grid leak to H.T. negative. In use, the 30pF trimmer is rotated until a reduction in anode current, as shown by a meter wired in the H.T. circuit, shows that the signal has been picked up. The aerial can be coupled to the set by a 2-turn loop near the tuning coil. Or if a short aerial is used, this can be taken



directly to the tuning coil, the best tapping point being found by trial.

Diode and Valve Amplifier

The circuit shown in Fig. 2 uses a "hard" valve, which will have a normal, long life. A high-slope pentode for battery running is most satisfactory, and suitable types will be found in the "all dry" portable range, such as the 1S5, 1S4, 3S4, etc. The H.T. voltage can be according to the anode current required, provided the maximum rating of the valve is not exceeded.

Adjustment is extremely simple, the 30pF trimmer being tuned for maximum current change. When the transmitter radiates, the signal is rectified by the crystal diode, and provides bias for the valve and its anode current thus changes. An increase or fall in anode current can be obtained according to the polarity with which the diode is wired. Grid bias must be adjusted so that the valve is operating on the best part of its characteristic curve, so that a small change in bias produces a fairly large change in anode current.

The aerial may be taken directly to the coil, since the question of damping preventing oscillation does not arise as with Fig. 1. The range achieved is very much less than with the circuit in Fig. 1, but is sufficient for boats on a small pond, and

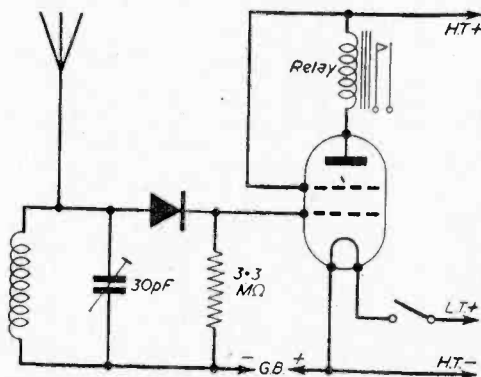


Fig. 2.—Hard-valve circuit.

similar purposes, with a powerful transmitter. The main advantage of the circuit lies in its ease of adjustment, and the fact that a gas-filled valve having a relatively short life is not required.

Single Transistor Circuit

A transistor may be used to amplify the voltage obtained from a diode, instead of a valve and a circuit of this type can be constructed upon a small piece of paxolin as shown in Fig. 3. In this case

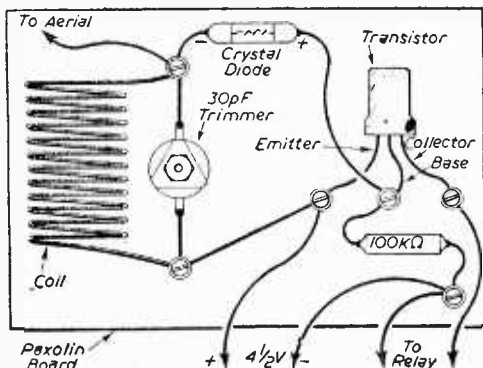


Fig. 3.—Wiring of a transistor circuit.

the output from the diode serves to bias the transistor, resulting in a collector current change which is sufficient to work the relay.

The tuning coil can be self-supporting. If a length of 18s.w.g. or other fairly stout wire is wound tightly round an object about $\frac{1}{2}$ in. in diameter, this will provide a self-supporting coil with an outside diameter of nearly 1in., when the temporary former is removed. This coil is then pulled out until eleven turns form a winding about 1 $\frac{1}{2}$ in. long. The ends can be cut off and loops formed to fit small 8B.A. bolts, as in Fig. 3. The trimmer is wired directly across the coil, and is best of the 30pF air-spaced or beehive type.

A coil made in the same way can be used with any of the other circuits described. The gauge of wire, diameter, and number of turns are not very important provided the coil can be tuned to the transmitter signal without the trimmer being closed down very far.

A piece of ebonite rod or small diameter tube, shaped to engage the trimmer, should be used for tuning. Re-tuning is necessary if any change is made to the aerial, or layout of the receiver etc. A meter wired in series with the relay forms the best tuning device because it will show when rotation of the trimmer has brought the receiver into resonance with the transmitter.

As with the circuit in Fig. 2, control cannot be maintained at anything like the range achieved with a gas-filled triode. But it is sufficient for small ponds, etc., with a transmitter providing a good output.

Twin Diode Circuit

In few cases very short range is sufficient, and a powerful transmitter may be used. A sensitive

relay can then be worked directly by the rectified radio frequency picked up by the receiver. A circuit for this purpose is shown in Fig. 4. The 1 $\frac{1}{2}$ V to 4 $\frac{1}{2}$ V battery, with 5k potentiometer, provides a standing current through the relay, which is adjusted in conjunction with the 5k control, for maximum sensitivity. When the transmitter is keyed, and the receiver tuned in, the change in current operates the relay.

A Three-valve Circuit

A receiver for use with a modulated transmitter is shown in Fig. 5. The valve types are not in any way critical. The first valve acts as detector, and the second as audio amplifier. The third valve is just sufficiently biased to prevent anode current passing. When modulation is applied to the transmitter carrier, this is picked up and amplified, and applied to the grid of the third valve, which passes anode current on positive peaks of the audio signal. These pulses are smoothed by the 0.1 μ F condenser, and provide anode current to operate the relay.

Such a circuit is best adjusted by wiring phones or speaker in place of the relay, and applying normal bias to this stage. The 50k potentiometer and tuning coil tapping should then be adjusted for maximum possible volume, at range. Cut-off bias may then be applied, and the relay connected.

It is important that the super-regenerative oscillation of the detector does not provide an audio signal which causes the third valve to conduct. This can most easily be arranged by keeping the quench above audibility, in the phones or speaker, and by

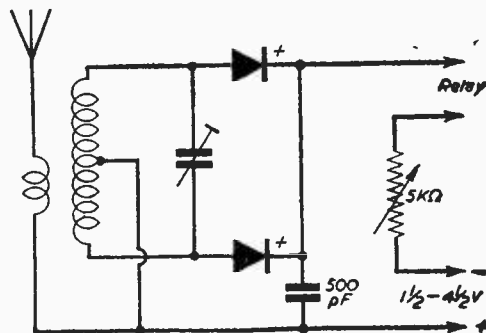


Fig. 4.—Circuit using two diodes.

shunting the coupling transformer, and choke, if necessary, with a fairly large condenser (say, 0.005 μ F.) A modulation tone of some 1,000c/s or so will then be strongly heard at the output valve anode, while the quench frequency, usually in the neighbourhood of 10kc/s or so, will not.

Direct Coupled Amplifier

If a circuit like that in Fig. 1 is made up with a "hard" valve it will be difficult to obtain a reliable anode current change of more than perhaps 0.1 or 0.2mA even at short range. It is for this reason that a gas-filled valve is substituted.

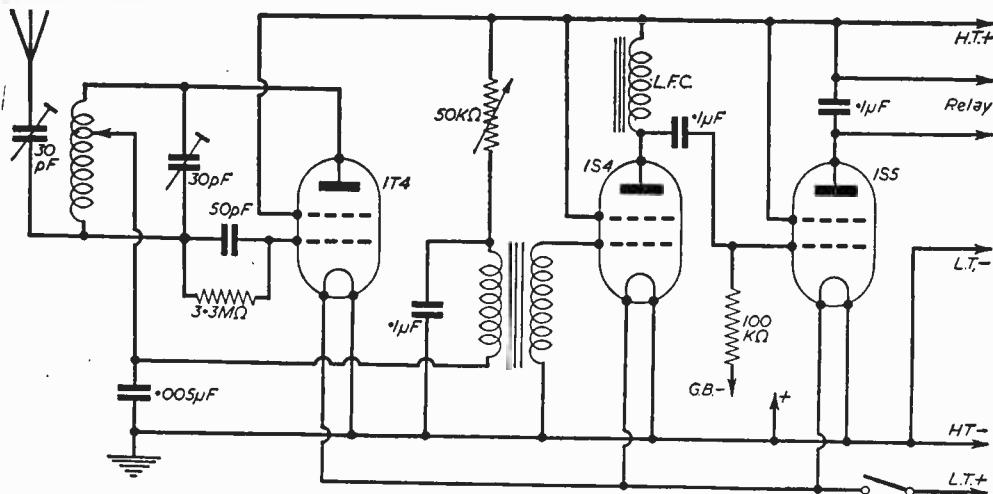


Fig. 5.—Receiver for use with a modulated transmitter.

Another method is to use a directly coupled stage, as shown in Fig. 6. Various circuits may be employed, that shown being perhaps the simplest.

In use, bias is adjusted by means of the 50k potentiometer until the valve is in the condition explained for the circuit in Fig. 2. The triode receiver may be wired as in Fig. 1. When the signal is received, the slight change in anode current causes a change in the voltage drop arising in the 30k potentiometer. This change in voltage is applied as bias to the second valve, causing a much increased change in anode current, so that the relay operates.

Batteries

Correctly adjusted, such a circuit has a range approaching that of the gas filled valve. Unfortunately it requires separate L.T. batteries for the two valves, and either separate H.T. batteries, or a tapped H.T. battery of fairly high voltage. It is thus only suitable for large models.

With any receiver, a fairly good change of current is obtained when the transmitter is near the receiver. As the model, and receiver, move to greater range, the change in current falls, until control is eventually lost. This is the maximum range for the equipment, and depends to quite a large extent on the careful adjustment of the relay.

When a model control relay is first obtained, a little time spent experimenting with its adjustment will be well worthwhile. This is most easily done by wiring a dry battery, variable resistor, and meter in series with the relay. Current can then be varied at will, and the relay adjusted as necessary.

For sensitive operation, a very small armature movement is necessary. For example, if poorly adjusted, the relay may rise at perhaps 0.5mA, but not draw down until the current reaches 1mA or more. With gap reduced, and tension adjusted if necessary, it may easily be drawn down at

0.6mA, while still rising reliably at 0.5mA. This would represent a considerable increase in range for the model.

It is also necessary to adjust the relay in accordance with the change which will be experienced

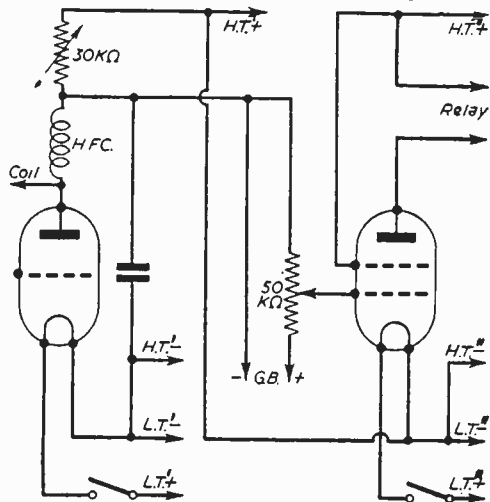


Fig. 6.—Using direct coupling.

at range. For example, with the circuit in Fig. 1, the change in current might be from 2mA to $\frac{1}{2}$ mA at short range, but only 2mA to $\frac{1}{2}$ mA at considerable range. If the relay were set to rise at currents just under 2mA, control would still be achieved at range. But if it were set to draw down when the current exceeds $\frac{1}{2}$ mA, control would be lost as soon as the model moved away. This must, therefore, be kept in mind, and the relay adjusted accordingly, or the model must be adjusted at the maximum range at which control will be wanted, before releasing it. The latter method is preferable.

Transistorised Super-Regenerator

A TWO-TRANSISTOR CIRCUIT FOR HEADPHONE RECEPTION

By L. Baker

SUPER-REGENERATIVE receivers have been well known to amateurs and radio experimenters since the very early days of radio. This type of detector has a very high sensitivity and gain but suffers from one drawback, however, and that is a loud hissing noise. In the two transistor super-regenerative receiver to be described, this drawback, whilst not eliminated entirely, is reduced to negligible proportions and when the set is tuned to a station the hissing noise is scarcely audible. The circuit is suitable for all frequencies but, with this type of detector, operation is most efficient on the higher frequencies. With this in mind, the set was designed to operate on the 10m amateur band and frequencies adjacent to this band. The set uses two transistors, a type SB344 acting as the detector and a type OC72 as audio amplifier. It is constructed around the front panel

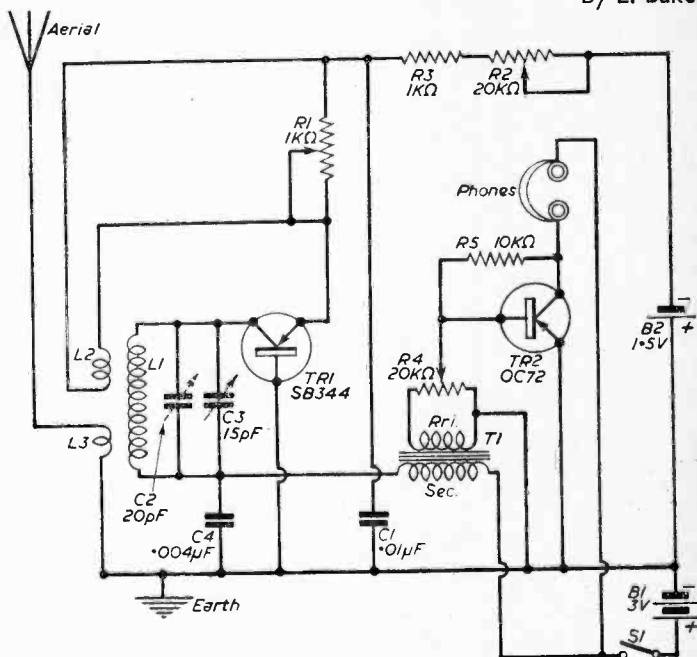


Fig. 1.—The circuit diagram.

of the cabinet and no "chassis" is necessary. All controls are mounted on the front panel, and the tuning condenser C3 is rotated by means of a slow motion dial. The bandset condenser C2 in the original model is of the semi-variable type.

Bandsetting

If required C2 can be of the fully variable type and a further control could be put on the front panel for this condenser which would give greater coverage. In the original set however, interest was mainly in the 10m amateur band and therefore C2 was made of the semi-variable type. It was adjusted until the 10m band was heard with C3 approximately half open. This made the amateur band "spread" over the full travel of C3. The coils L1, L2 and L3 are wound on a ceramic former.

The coil is constructed first. The former should be of ceramic or similar material. The tuned coil, L1, consists of $7\frac{1}{2}$ turns of 20 gauge enamelled wire evenly spaced out over a length of 1in. Coil L2 is three turns of the same wire at the

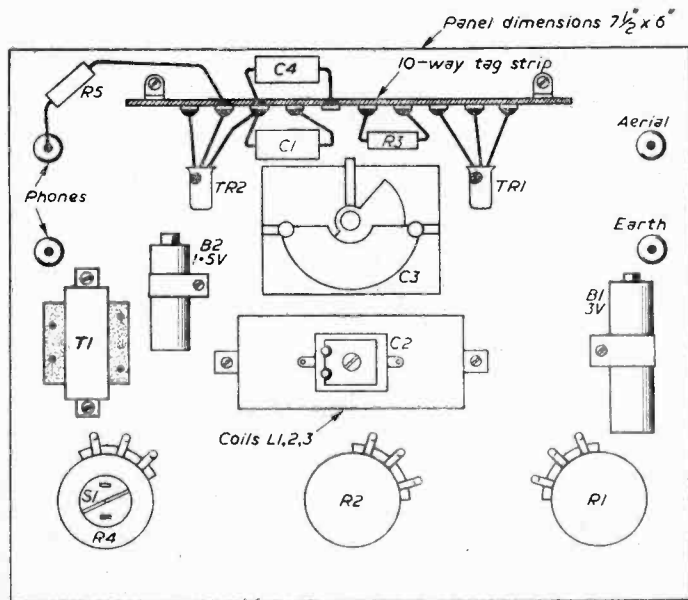


Fig. 2.—Layout of the parts.

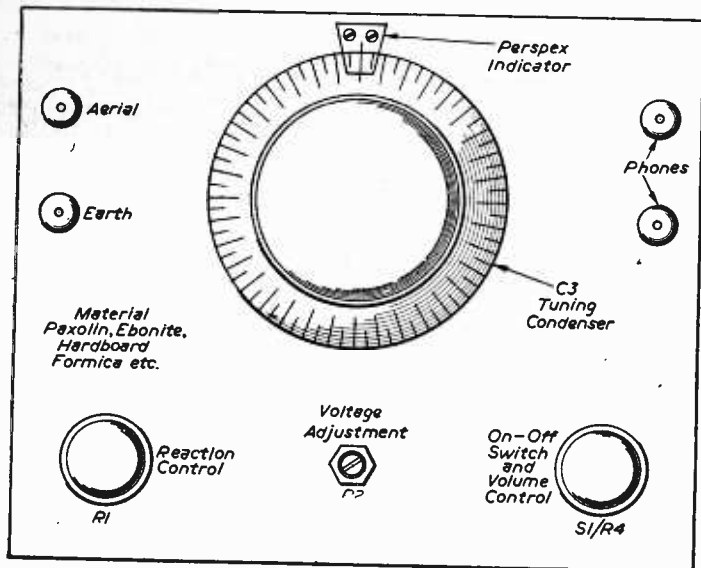


Fig. 3.—Front panel.

"hot" end of L1. The aerial winding, L3, is two turns of the same gauge wire wound at the remote or "cold" end of L1 (see Fig. 4). All the coils should be given a coating of cement after trial to ensure that the turns do not slip. The wire for these coils should be free from kinks. The coil should be provided with mounting brackets as shown and the entire assembly should be quite rigid. If the intending constructor desires to have C2 of the semi-variable type (as in the original) then, C2 can be made part of the coil assembly as shown.

Coupling Transformer

The interstage transformer T1 is of the ordinary intervalve type connected so that its primary (low resistance winding) is feeding into the base circuit of the OC72. This arrangement gives approximately correct impedance matching. The audio gain potentiometer, R4, is of the midget type and is ganged with the on/off switch S1. R2 is a midget potentiometer of value 20k, and since this will only need very occasional adjustment it is of the preset type.

The sensitivity control is R1, and since it has to be adjusted for practically every station it is best to use a component of the wire-wound type which will give much better wear and service than a carbon type. Condenser C1, which controls the quench frequency, should be of known good quality with high insulation. The value of C1 is given as 0.01μF. This may have to be altered to suit different sets. For the rest of the components, use should be made of good quality parts, and dubious items should be avoided. In the original model, C3 was made by stripping down a "surplus" air-spaced trimming condenser until only two stators and one rotor remained. The batteries are held in place by spring clips made from pieces of scrap brass sheet.

Panel

The front panel of the receiver should be of insulating material. If plywood is used, it should be perfectly dry. The panel should be cut to the dimensions shown and drilled to take the mounting bushes of the various controls as shown. The mounting lugs of the coil and transformer T1 should be carefully marked out and drilled on the panel. Clips for the batteries should be mounted likewise. The tag strip for the smaller components should be positioned and holes drilled to hold it to the front panel. When drilling for the mounting bush of C3 (tuning), the assembly holes for the dial and pointer should also be drilled.

Wiring

Having mounted all the components on the rear of the front panel, wiring may be commenced. The wiring for the coil and inter-connections for the detector stage should be of the heavy, stout type. Loose or wandering connections should be avoided. Each joint should be carefully soldered using a clean, hot iron in conjunction with a resin-coated solder. Normal hook-up wire may be used

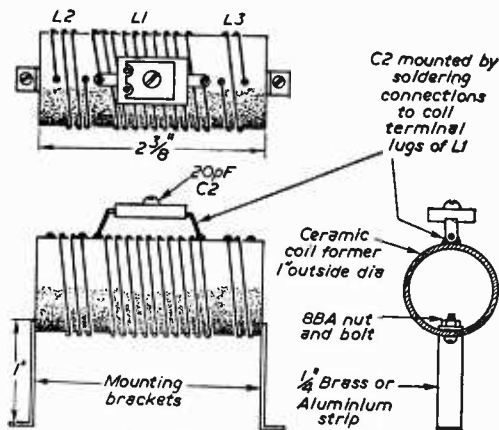


Fig. 4.—Coil winding details.

for the audio amplifier section. The transistors should be wired in last of all, using a heat shunt on each connecting wire when the soldering iron is applied. This will avoid damage to the transistors. The batteries should not be connected until all connections and interwiring has been very carefully checked to avoid the possibility of mistakes. Having made sure that all is in order, the earphones should be connected to the set and the batteries connected with the set switched off.

(Continued on page 1058)

LEARN

Train at home in your spare time

RADIO & TV. SERVICING
this new, easy, practical way!**YOUR OWN... BUSINESS...
CAREER... OR
FASCINATING HOBBY**

Electronics is rapidly becoming a great new industry with far reaching applications into every field of modern activity.

You can learn all the essentials of this new science at home in your spare time and turn your knowledge to good purpose!

Now is your chance to set up your own business and be your own boss!

**RADIOSTRUCTOR EQUIPMENT COURSES
MAKE LEARNING SO SIMPLE**

You learn by building actual equipment with the big kits of components and parts which we send you. You advance by simple steps using high quality equipment and performing a whole series of interesting and instructive experiments—there are no complicated mathematics! Instruction manuals and our teaching staff employ the latest techniques for showing clearly how radio works in a practical and interesting manner; in fact, you really have fun whilst learning! And you end by possessing a first-rate piece of home equipment with the full knowledge of how it operates, and how to maintain it afterwards. In fact, for those wanting help with their radio career training, to set up their own full or part-time servicing business, or the hobbyist, this new and instructional system is exactly what is needed, and it can be provided at very moderate cost with payments available. Post the coupon now, for full details. There is no obligation of any kind.

POST TODAY FOR FREE brochure

To **RADIOSTRUCTOR** (Dept. G82)
46 MARKET PLACE, READING, BERKS.

Please send Brochure without obligation to:

Name _____

Address _____

**BLOCK
CAPS
PLEASE**

(827)

We do not employ representatives

4-60

- NO MATHEMATICS
- EASY TERMS AVAILABLE
- ALL TEST EQUIPMENT SUPPLIED
- PERSONAL TUITION
- FINEST EQUIPMENT

RADIOSTRUCTOR


BRITAIN'S LEADING RADIO TRAINING ORGANISATION

CONSTRUCTORS CORNER

Construction price includes valve and one coil covering 40-100 m.
 ● Can be converted to 2v. or 3v.
 ● Receives speech and music clearly from all over the world.
 Send 2/- for diagram and price list.

Explore the world on short-wave radio (10-100 m)


FOR ONLY **35/-**

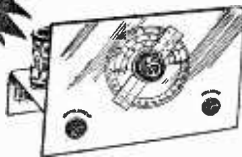

TRANSISTOR POCKET RADIO

Two-stage circuit using variloopstick coil.

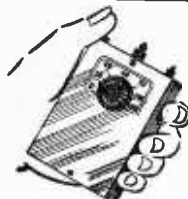- Ideal for the beginner.
- Can be built in 30 minutes.
- Works for months off 7d. battery.
- Fits into palm of your hand.



The ideal low-cost transistor pocket radio for the beginner.
 Send 2/- for data and list of components.

ONLY

30/-

CRYSTAL RECEIVER

Covers M/W Band

All components including case for

10/6

Ideal for the beginner.

Post and packing: Under 10/- add 9d.; under 40/- add 1/6; over POST FREE

ENSURE SUCCESS WITH R.C.S.

SENSATIONAL RESULTS WITH 2 TRANSISTORS

- ★ No aerial or earth.
 - ★ Dial tuning with mini .0005.
 - ★ Drilled chassis, colour coded, components, simple layout for beginners.
 - ★ Special small case fits shirt pocket.
 - ★ Soldering iron and pliers are only tools needed.
- Finest results ever obtained with 2 transistors and diode layout. The ideal radio to carry with you everywhere. PARTS PRICE LIST & EASY LAYOUT PLANS, 2/-. Total building cost, including transistors, wire, etc.



62/6

BUILD THIS AMAZING RADIO

POWERFUL! PERSONAL! PORTABLE!

- ★ Sturdy metal case.
 - ★ No holes to drill.
 - ★ Detachable rod aerial.
 - ★ All batteries self contained.
 - ★ Can be built in 1 hour.
 - ★ Covers medium waves.
 - ★ Loud clear tone.
 - ★ Selective tuning.
 - ★ All parts are sold separately.
- This delightful set is designed to give you a completely personal portable radio. Bronze-finished case. Ideal for the beach, the bedroom, the office—in fact, anywhere. Send 2/- for wiring diagram and component price list.

FOR ONLY **35/-**



Trade Enquiries
 Welcomed

R.C.S. PRODUCTS (RADIO) LTD. 11 OLIVER RD., LONDON, E.17.

Mail Order
 Only

EXPRESS ELECTRONICS

ROSEDENE LABORATORIES
 KINGSWOOD WAY, SELSDON, SURREY
VALVES NEW, TESTED AND GUARANTEED
 REDUCED PRICES

| | | | | | | | | | |
|-----|-----|-------|------|--------|------|------|------|-------|------|
| 10L | 7/6 | 6B87 | 10/6 | 19Q7GT | 7/6 | 8B91 | 5/6 | N17 | 7/6 |
| 10C | 8/- | 6B87 | 7/6 | 16A5 | 9/6 | 8B91 | 10/6 | N18 | 8/- |
| 10F | 8/- | 6B87 | 7/6 | 26A6G | 10/6 | 8B91 | 8/6 | N19 | 7/6 |
| 10G | 7/6 | 6C10 | 9/- | 26L8GT | 9/- | 8C08 | 7/6 | PC084 | 9/- |
| 10H | 7/6 | 6D2 | 5/6 | 26Z4G | 9/- | 8C08 | 7/6 | PCP80 | 9/- |
| 10I | 7/6 | 6F12 | 4/6 | 80C1 | 8/- | 8C08 | 7/6 | PCP82 | 10/6 |
| 10J | 6/6 | 6H8GT | 2/- | 80L1 | 8/- | 8C08 | 9/6 | PCP82 | 9/- |
| 10K | 8/- | 6J7GT | 8/6 | 85L8GT | 9/- | 8C08 | 10/6 | PL81 | 12/- |
| 10L | 7/6 | 6K7G | 5/6 | 85W4 | 8/6 | 8C08 | 10/6 | PL82 | 9/- |
| 10M | 7/6 | 6KAG | 7/6 | 85Z4GT | 8/6 | 8C08 | 10/6 | PL82 | 9/- |
| 10N | 7/6 | 6Q7G | 7/6 | 85K1 | 11/6 | 8C08 | 10/6 | PL82 | 9/- |
| 10O | 7/6 | 6Q7G | 7/6 | 85K1 | 11/6 | 8C08 | 10/6 | PL82 | 9/- |
| 10P | 7/6 | 6Q7G | 7/6 | 85K1 | 11/6 | 8C08 | 10/6 | PL82 | 9/- |
| 10Q | 7/6 | 6Q7G | 7/6 | 85K1 | 11/6 | 8C08 | 10/6 | PL82 | 9/- |
| 10R | 7/6 | 6Q7G | 7/6 | 85K1 | 11/6 | 8C08 | 10/6 | PL82 | 9/- |
| 10S | 7/6 | 6Q7G | 7/6 | 85K1 | 11/6 | 8C08 | 10/6 | PL82 | 9/- |
| 10T | 7/6 | 6Q7G | 7/6 | 85K1 | 11/6 | 8C08 | 10/6 | PL82 | 9/- |
| 10U | 7/6 | 6Q7G | 7/6 | 85K1 | 11/6 | 8C08 | 10/6 | PL82 | 9/- |
| 10V | 7/6 | 6Q7G | 7/6 | 85K1 | 11/6 | 8C08 | 10/6 | PL82 | 9/- |
| 10W | 7/6 | 6Q7G | 7/6 | 85K1 | 11/6 | 8C08 | 10/6 | PL82 | 9/- |
| 10X | 7/6 | 6Q7G | 7/6 | 85K1 | 11/6 | 8C08 | 10/6 | PL82 | 9/- |
| 10Y | 7/6 | 6Q7G | 7/6 | 85K1 | 11/6 | 8C08 | 10/6 | PL82 | 9/- |
| 10Z | 7/6 | 6Q7G | 7/6 | 85K1 | 11/6 | 8C08 | 10/6 | PL82 | 9/- |

VOLUME CONTROLS MIDGET SIZE LONG SPINDLES D.P. switch.
 3/9; S.P. 3/3; Less switch, 2/6. Values 10K to 2M. Pre set 2/3.

MATCHED PAIRS

EL84 21/-, 6V6 17/-, KT66 27/6, 6B87 18/- per pair. Push Pull O.P.
 Transformers for above 3-15 1/4, 12" P.M. Speakers 3 1/2 24/6.

SETS OF VALVES

| | |
|----------------------------------|------|
| DK91, DP91, DA91, DL92 or DL44 | 23/6 |
| DK96, DP96, DA96, DL96 | 23/6 |
| 1C3, 1F1, 1F1, 1F1 | 23/6 |
| 1R3, 1T4, 1S5, 3A4, or 3V4 | 23/6 |
| 6K3, 6K7, 6Q7, 6V6, 5Z4G or 6X5G | 27/6 |

Postage and packing 6d. Over £1 post free. C.O.D. 2/6.

SOUTHERN RADIO'S WIRELESS BARGAINS

ATTACHMENTS for "18" Transreceivers. ALL BRAND NEW. HEADPHONES, 15/6; HAND MICROPHONE, 12/6; AERIALS, 5/-; SET OF 6 VALVES, 30/-.

CONDENSERS. 100 Assorted. Mica, Tubular, etc. NEW 15/-.

CONTACTOR TIME SWITCHES. 2 impulses per sec. in case 11/6.

REMOTE CONTACTOR. For use with above 7/6.

LUFBA HOLE CUTTERS. Adjustable 1/2" to 3/4". For Metal, Plastic, etc. 7/6.

MAGNETS. Strong Bar Type. 2" x 1/2". 1/6 each.

MORSE PRACTICE SET. TAPPER with BUZZER on Base. Complete with Battery. BRAND NEW 12/6.

MORSE TAPPERS. Midget Type, 2/9. Standard, 3/6. Heavy Type of Base, 5/6. ALL BRAND NEW.

PACKARD-BELL AMPLIFIERS. Complete BRAND NEW with Valves: Relay, etc. 17/6 each.

QUARTZ CRYSTALS. Types F.T.241 and F.T.243, 2-pin, 1/2 Spacing. Frequencies between 5.675 Kc/s. and 8.650 Kc/s. (F.T. 243) 20 Mc/s. and 38.8 Mc/s. (F.T.241), 54th Harmonic, 4/- each. ALL BRAND NEW. TWELVE ASSORTED CRYSTALS, 45/-. Holders for both types, 1/- each. Customers ordering 12 crystals can be supplied with lists of frequencies available for their choice.

RECORDING BLANKS. New "Emidisc" ready for use. 13" 6/- each. Quantity of 15 in metal case £4.

RESISTANCES. 100 Assorted useful values. New wire end, 12/6.

SPECIAL OFFER. 12 ASSORTED METERS. Slightly damaged. Mainly broken cases (perfect movements). Including 3 Brand New Aircraft Instruments. 12 for 45/-.

STAR IDENTIFIERS. Type 1 A-N Covers both Hemispheres, 5/6.

T1154 TRANSMITTERS. Complete, NEW condition, in Transit case. £25.0

TRANSPARENT MAP CASES, Plastic. 14" x 10 1/2". Ideal for Maps, Display, etc. 5/6

TRANSCEIVERS. Type "38" complete with 5 valves, etc. New condition, untested by us, but serviceable, no guarantee. 22/6 each.

ATTACHMENTS for Type "38" Transreceivers. ALL BRAND NEW. HEADPHONES, 15/6; THROAT MICROPHONES, 4/6;

INTERCOM BOXES, 2/6; AERIALS, No. 1, 2/6; No. 2, 5/-;

WEBBING, 4/-; HAVERSACKS, 5/-; VALVES, A.R.P.12, 4/6; A.T.P.4, 3/6. Set of FIVE VALVES, 19/- the set.

POST OR CARRIAGE EXTRA. FULL LIST OF RADIO BOOKS, ETC., 3d.

SOUTHERN RADIO SUPPLY LTD.

11, LITTLE NEWPORT ST., LONDON, W.C.2. GER. 6653

Miniature Add-in I.F. Stage

IMPROVE SELECTIVITY AND SENSITIVITY

VERY many receivers have one I.F. stage only, and it is usually possible to add an extra I.F. amplifier to these. Such a stage will give a quite considerable increase in sensitivity. There will also be an improvement in selectivity, and in the ability of the automatic volume control circuit to control fading. The addition is a relatively simple matter because the I.F. circuits are fixed tuned.

Heater Wiring

The I.F. stage shown here is of small size and space could often be found for it even in compact table receivers. The 6BA6 requires a 6.3V, 0.3A heater supply and if the receiver is of the AC/DC type, with 0.3A heaters in series, the 6BA6 heater is wired between the present I.F. stage and frequency changer, and the resistance of the line cord or mains dropper reduced by approximately 21ohms. In the case of receivers with heaters fed from a 6.3V transformer, the extra 0.3A can usually be drawn without overloading. If the heater transformer is fully loaded already, and of small size, an economy may be made elsewhere, so that current for the extra valve is available.


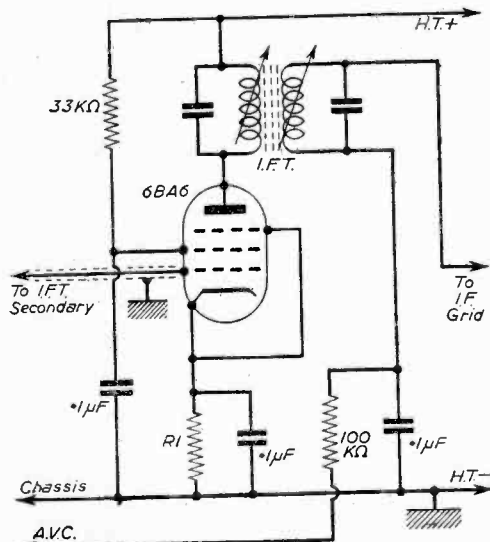


Fig. 1.—The circuit diagram.

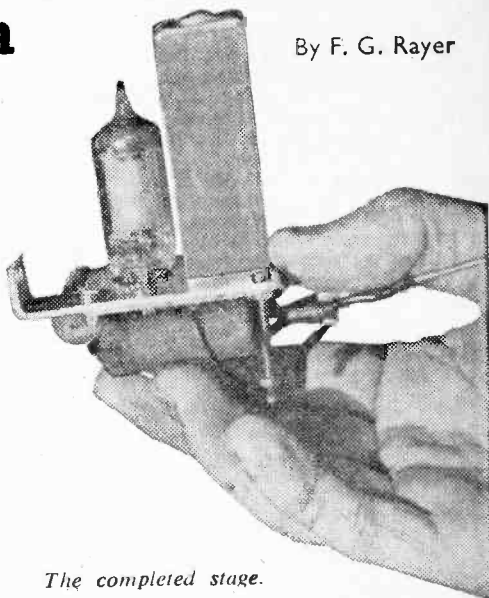This may be done by replacing a pair of 0.3A dial lights with 0.15A bulbs. If there is only one bulb, of 6.3V 0.3A rating, this can be replaced by a 6V, 0.04A bulb with a resistor of about 25ohms in series. But in most receivers the extra current may be taken without difficulty.



The completed stage.

The H.T. consumption is up to about 15mA, depending on the voltage. Good results can be obtained with less current, and the cathode bias resistor R1 can be increased in value if necessary. It should, however, be possible to obtain the small extra H.T. current needed.

The extra stage is particularly intended for receivers having one I.F. stage only. Care is needed if two I.F. stages are already present, or instability will be caused. If layout and screening cannot be improved, R1 may be increased from its usual value of approximately 68ohms (for the 6BA6 type) up to 250 or 500ohms. This will reduce gain, and help to restore stability.

Circuit and Layout

The circuit is shown in Fig. 1. The existing connection from the I.F. transformer to the present I.F. valve control grid is removed, the transformer being wired to the 6BA6 grid by means of a screened lead. The grid lead of the transformer in the new stage is then taken to the existing I.F. valve control grid. The new stage should be so positioned in the receiver as to allow short leads from it to the I.F. transformer and valve.

The stage is completely wired as shown in Fig. 2, leads being left for AVC, H.T., and other connections. Transformer wiring must be correct, so the positions of leads or tags should be checked on the maker's leaflet.

Size

If very small size is not important, a little extra space can be allowed for the stage. An enclosed chassis would, however, make wiring up rather difficult, unless it is considerably larger.

The stage is fixed securely in the receiver in the position chosen. This can be done with brackets, long bolts with lock nuts, or any other means, according to circumstances.

Frequency Meter BC 221

ITS PRACTICAL APPLICATIONS
AND USES

By H. J. Long, B.E.M. (G5LO)

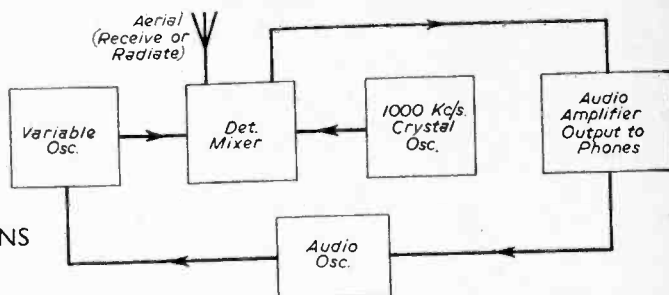


Fig. 1.—Block diagram of frequency meter BC221.

THE frequency meter or wavemeter as it is sometimes called is a useful piece of apparatus that should be found in most amateur stations. Amateur transmitting stations must be operated strictly within the allotted frequency bands; there must be no excuse for off-band operation, at least as far as the authorities are concerned. The importance of this is reflected by questions usually posed in the City and Guilds Radio Amateur's Examination, when the would-be amateurs knowledge of the use and application of a frequency meter will no doubt occur. The following notes are intended as a description and guide for the beginner in the practical use of the frequency meter, with particular reference to the popular American BC 221.

A frequency meter is an apparatus capable of measuring frequencies in any pre-determined band to which it has been calibrated. They can be as simple as the absorption type, which consists of a variable condenser and an inductance (coil), calibrated to cover the required range, or they can be complicated items costing thousands of pounds. As far as the radio amateur is concerned, the frequency meter must be fairly inexpensive, but must be capable of reasonable accuracy. Fortunately, large numbers of frequency meters were produced for use by the forces during the war, and became available on the "surplus" market afterwards.

Perhaps the most popular and sought-after frequency meter is the American BC 221. This is a portable instrument, battery operated, but can be adapted to mains operation by the addition of a small power pack. This requires about 150V H.T. at about 20mA, and 6.3V at 1A for the heaters.

Frequency Meter BC 221 contains:

- (1) A crystal controlled oscillator used as a reference standard;
- (2) A heterodyne oscillator with two fundamental tuning ranges which, with their useful harmonics, are calibrated to provide continuous coverage from 125 to 20,000kc/s;
- (3) A high gain detector provided with means of coupling to each of three sources of excitation;
- (4) An audio frequency amplifier;
- (5) An audio frequency oscillator, provided with means for modulating the heterodyne oscillator.

The block diagram (Fig. 1) shows how these five principal parts are lined up. Three valves are employed in the frequency meter: a 6K8, triode-hexode, and two 6SJ7s, pentodes.

Crystal Circuit

The crystal circuit uses the triode section of the 6K8 valve. The fundamental frequency of the crystal oscillator is approximately 1,000kc/s. A variable condenser is connected across the crystal for the purpose of adjusting the frequency of the crystal to a closer tolerance if required. The crystal is mounted inside an airtight enclosure to protect it from dust and moisture.

The crystal controls a valve oscillator, and the latter emits a virtually constant frequency of 1,000kc/s with additional harmonically related frequencies. These additional frequencies are exact integral multiples of the fundamental frequency; i.e., these added harmonics are 2, 3, 4, etc., times the fundamental frequency and are therefore 2,000kc/s, 3,000kc/s, 4,000kc/s, etc., and each has the same percentage of accuracy as the fundamental. They may be used as reference frequencies throughout the range of the meter. The highest harmonic used as a "crystal check point" is the 15th, or 15,000kc/s, but harmonics of much higher order are present although they become progressively weaker as the frequency increases.

The crystal circuit has two functions: It furnishes constant, exactly measured, frequencies by which to check and correct the calibration of the variable frequency oscillator. It radiates exactly known marker frequencies by which other equipment, such as a receiver, may be calibrated.

Variable Frequency Oscillator

The variable frequency section of the frequency meter consists of three essential elements, the tuning condenser, the coil assembly and the valve. The valve used is a 6SJ7 and is a pentode. Its function is to produce a signal the frequency of which may be adjusted as desired, and which is rich in harmonics to extend the useful frequency coverage without a large number of frequency bands. This signal may be radiated from the frequency meter into an adjacent receiver thereby acting as a frequency standard against which to set the receiver. The output of the variable oscillator may be mixed in the converter valve with signals picked up from a transmitter to produce zero beat and thereby obtain a measure of the frequency of the transmitter. This variable oscillator may also be modulated by the internal audio oscillator for use with receivers without a beat oscillator.

Detector Valve Circuit

The pentode portion of the 6K8 valve is the detector in the frequency meter. When making measurements on transmitters, energy from the transmitter is fed into the control grid of this valve through the aerial connection on the meter, while energy from the variable oscillator is also fed into the same grid. When the frequencies differ by only a few hundred cycles, a distinct audio beat note, equal in frequency to the difference between the two impressed frequencies, is

The calibration book contains a list of closely spaced frequencies together with their corresponding readings (dial). The scope of this list can be shown best in tabular form (Table 1).

Reading the Dial

The drum behind the small window on the front panel of the frequency meter indicates the reading of the dial setting in hundreds. The large dial shows the units; the vernier scale above and

Table 1. Scope of a typical calibration book.

| LOW BAND | | | |
|----------------|-----------------|-------------------------------------|----------------------|
| Harmonic Order | Frequency Range | Interval Between Listed Frequencies | No. of Listed Points |
| Fundamental | 125—250kc/s | 100c/s (0.1kc/s) | 1251 |
| Second | 250—500kc/s | 200c/s (0.2kc/s) | 1251 |
| Fourth | 500—1000kc/s | 400c/s (0.4kc/s) | 1251 |
| Eighth | 1000—2000kc/s | 800c/s (0.8kc/s) | 1251 |
| HIGH BAND | | | |
| Fundamental | 2000—4000kc/s | 1000c/s (1kc/s) | 2001 |
| Second | 4000—8000kc/s | 2000c/s (2kc/s) | 2001 |
| Fourth | 8000—16000kc/s | 4000c/s (4kc/s) | 2001 |
| Fifth | 16000—20000kc/s | 5000c/s (5kc/s) | 801 |

produced in the anode circuit of the detector and passed on to the audio amplifier.

For this, the operation switch is set at HET Osc.

When the switch is turned to XTAL CHECK, the signal from the variable oscillator is impressed on the control grid of the 6K8 valve, while the voltage from the crystal oscillator (triode portion of the 6K8 valve) is impressed on the injector grid of the pentode portion producing detection in the fashion of the familiar pentagrid converter.

The output (anode) circuit of the mixer is made responsive to low audio frequencies by using a choke of high inductance in the anode circuit, and has its high frequency response reduced by a condenser connected across the inductance.

Audio Amplifying Circuit and Audio Modulator

The audio amplifier is a conventional self-biased circuit except that the 6SJ7 pentode valve used is connected as a triode. The audio signal transmitted to the headphones can be adjusted manually by the gain control to suit the operator's requirements.

The audio oscillator is a simple oscillating circuit generating a tone of approximately 400c/s. Some of the earlier models of the BC 221 do not have this audio oscillator.

Calibration Book

Each BC 221 frequency meter should have a calibration book in the front cover of the meter case. Without it, the frequency meter is useless. Each book is different and bears the serial number of the meter to which it belongs. In the event of loss or damage, a new book must be calibrated. The book from another instrument can never be substituted.

adjacent to the large dial shows the tenths place of the setting. To read the vernier, find the line of the vernier scale which coincides most closely with a line of the large dial. The number of this vernier line (counting the arrow as zero) gives the tenths place of the complete dial setting. Fig. 2 shows the dial set for a reading of 0961.7. Before using the frequency meter for actual measurements, it is advisable to practice on the dial until settings can be read off quickly and accurately. It should be noted that these dial readings are not actual frequencies, but must be referred to the calibration book to find the frequency to which they refer.

Determining Frequency When Dial Reading is Given

Very often the desired frequency (when the frequency meter is being used to calibrate a radio transmitter) or the observed dial setting (when the frequency meter is being used to measure an unknown frequency) may fall between the values listed in the calibration book. To aid in calculating the proper dial setting or measured frequency corresponding to these intermediate values, the following method can be used. If, for example, the observed dial setting is 2428.8 and lies between two successive book values of 2430.2 and 2428.1, and their corresponding frequencies are 2936 and 2935kc/s (fundamental), the frequency (f) corresponding to the 2428.8 dial setting is determined as follows:

| Dial Readings | Frequency |
|---------------|-----------|
| 2430.2 | 2436kc/s |
| 2428.8 | f kc/s |
| 2428.1 | 2935kc/s |

Therefore, when the frequency generated increases by 1kc/s, the dial reading increases from 2428.1 to 2430.2, that is, by 2.1 divisions.

Therefore, no. of kc/s per dial division = $[1/2.1]$.
When the frequency increases from 2935kc/s to f kc/s, the dial reading increases by 0.7 divisions.

$$\text{Therefore, } f = \left\{ \frac{1 \times 0.7}{2.1} + 2935.0 \right\} \text{ kc/s} \\ = 2935.333 \text{ kc/s}$$

Further Explanation

The difference between the two book values of frequency is 1kc/s and corresponds to 2.1 dial divisions. The frequency in kilocycles or dial divisions is then found by dividing the 1kc/s by the 2.1 dial divisions (and is 0.4762). The difference between the observed dial setting and the book value dial setting for the lesser book frequency is 0.7 of a division. The frequency which this difference represents is then the product of the difference and the number of kilocycles per division, 0.4762×0.7 or 0.333kc/s. This is then added to the lesser book frequency, $2935 + 0.333$, or 2935.333kc/s, the frequency corresponding to the 2428.8 dial setting.

Determining Dial Reading When Frequency is Given

Conversely, to adjust the frequency meter to a given frequency which falls between the book values, it will be necessary again to make an interpolation to determine the exact dial setting to be

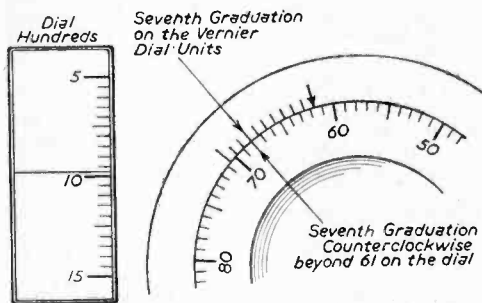


Fig. 2.—Reading the vernier scale; the dial is set at 0961.7.

used. For example, it is desired that the frequency meter be adjusted to 2935.333kc/s. The necessary calculations follow:

| Dial Readings | Frequency |
|---------------|--------------|
| 2430.2 | 2436.0kc/s |
| D | 2935.333kc/s |
| 2428.1 | 2935.0kc/s |

Therefore for an increase in dial reading of 2.1 divisions the frequency increases by 1kc/s.

Therefore no. of dial divisions per kc/s = 2.1.

When the dial reading increases from 2428.1 to D, the frequency increases by 0.333kc/s.

$$\text{Therefore } D = \left\{ (2.1 \times 0.333) + 2428.1 \right\} \text{ kc/s} \\ = 2428.8 \text{ kc/s}$$

This method is accurate for all frequency columns (harmonics) in the calibration book. For practical purposes, the nearest book value would suffice.

The Frequency Meter in Use

In use, the frequency meter should be switched on and allowed to warm-up for at least 15 minutes to allow for any drift that might take place. Also, whenever a frequency is to be checked, the variable oscillator should be adjusted to "zero beat" at the nearest "check-point" in the calibration book. Furthermore, when a transmitter frequency is being checked, this type of heterodyne frequency meter should always be used in conjunction with a simple type of absorption frequency meter. The heterodyne frequency meter gives an indication at the fundamental frequency and also its harmonics, whereas the absorption type, although not so accurate (it need only be roughly calibrated to the required band) will only respond to the fundamental frequency to which it is tuned, and is a valuable safeguard.

BBC YEARBOOK 1960

THE BBC Yearbook for 1960 was published on January 27. The following are some points from the book:—

Television

The Television Service maintained its two-fold aim, first to present programmes which have a general appeal and which attract very large audiences, secondly to provide programmes which stimulate thought, widen people's horizons and enhance their artistic appreciation. Something approaching half of the BBC's total output during the year consisted of material of this kind.

Alternative Television Service

The Corporation reaffirms its belief in the need for a planned alternative television service, in the interests of the viewing public.

The BBC Regions

The development of television facilities and resources in the BBC regional centres meant that regions were able to play an increasingly responsible and representative part in the service of programmes broadcast to the country as a whole. In sound radio, the coming into service of more V.H.F. transmitters allowed further extensions of area broadcasting and the broadening of existing area services with new programme material catering for local interests.

Jamming

The penetration of jamming by broadcasts to the Communist-dominated countries of Europe was confirmed by evidence of wide-spread listening in the U.S.S.R. and the satellite countries.

Coverage

During the year the substantially interference-free V.H.F. service was extended to make BBC programmes available on this system to 96.4 per cent of the population. This is in addition to the existing long and medium wave systems which cover the whole of the British Isles.

By the first quarter of 1959 BBC television programmes could be received by 98.5 per cent of the population, and the planned building of fourteen satellite stations would increase coverage by 200,000 people and an improved service become available to a further 940,000 people.

The Yearbook is published by the BBC and the price is 6s. 0d. exclusive of postage and is obtainable from booksellers and BBC Publications, 35 Marylebone High Street, London, W.1.

Record Player and Cabinet

By R. S. Higgs

A HIGH quality record player that looks really professional with a low, modern cabinet can be constructed by any handyman who can use the simplest carpentry tools and a soldering iron. The record player described will give really high quality reproduction of modern high fidelity records that will satisfy the most critical music lover.

Panels

The cabinet is designed to avoid anything that is tricky or difficult in carpentry and to this end, use has been made of the ready prepared, fully

The amplifier can then be constructed and all components fixed in place on the front panel. Countersunk screws should be used for speaker and chassis fixing in order to leave a flat surface for the speaker cloth panel which will later cover all screw heads. It should be noted that the Cossor chassis brackets should be fixed by the nuts and bolts provided only in the case of the top holes. The lower fixing holes should be used for a $\frac{1}{2}$ in. wood screw driven in from the back otherwise the front panel will be spoilt by two unsightly bolt heads which would show below the speaker cloth panel.

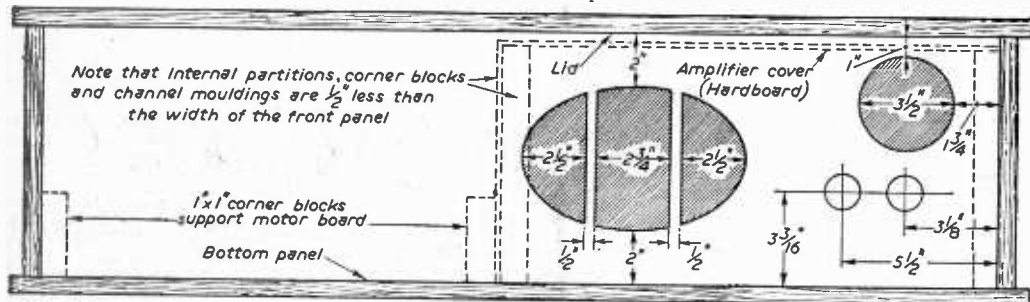


Fig. 1.—The front panel showing the cut-outs required for the loudspeakers and control knobs.

veneered chipboard panels now obtainable in standard sizes. These panels are veneered on all sides and edges and are simply glued and panel-pinned together with corner blocks inside for strengthening where possible.


The gramophone unit and amplifier are readily obtainable from many radio component dealers. The units used in the record player described were the B.S.R. Monarch U.A.8., 4 speed, 10 record autochanger obtainable for about £6 12s. 6d. and the amplifier was the Cossor 3W audio amplifier obtainable in kit form from many radio dealers for about £5 19s. 6d. This kit has the advantage of having twin loudspeakers included and is easily constructed with printed circuit and most of the components already mounted and connected.

Procedure


A start is made by taking the best of the 9in. wide boards for the front panel. The necessary cut-outs for the speakers and holes for the control knobs are cut after reducing the length of the panel from 3ft to 2ft 9 $\frac{1}{2}$ in. The shape of the cut-outs and holes will of course, vary according to the components used, but in the case of the Cossor equipment, the pattern will be as shown in Fig. 1. A paper pattern is included in the Cossor kit which would need to be re-arranged to suit the "long low" cabinet.

The cabinet can then be assembled as follows:—

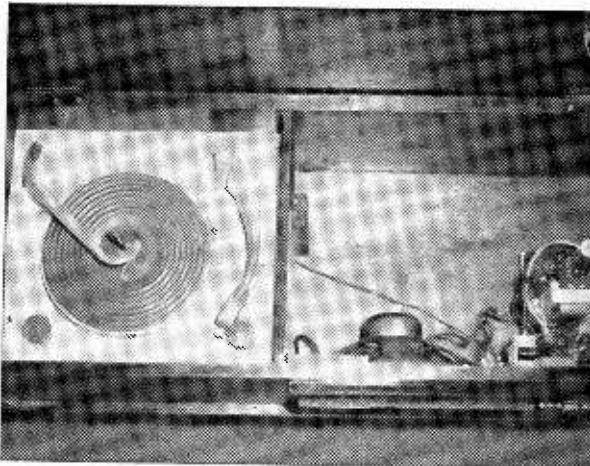Cut one 3ft. x 9in. panel 2ft 9 $\frac{1}{2}$ in. long to form the back. The remaining 3ft x 9in. panel is used for the two ends. This is done by cutting a 15in. length from each end of the panel, leaving the 6in.



The record player from above.

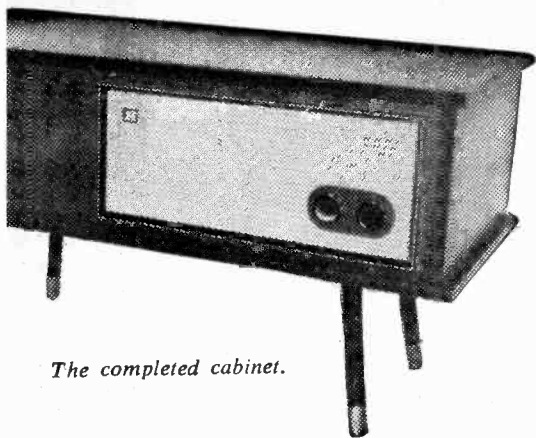

The completed cabinet.

of waste in the middle. Thus each end piece will have a veneered edge to face the front. Glue and panel-pin the parts together as in Fig. 2. Note that the front panel is set back $\frac{1}{4}$ in.

The whole of the cabinet so far assembled should then be sanded with fine sandpaper. Note that the only cut edges now showing are the two rear edges of the side panels.

The bottom panel should then be fixed in place using glue and $1\frac{1}{2}$ in. countersunk screws all the way round. This panel will overlap the sides by $\frac{1}{4}$ in. each end and of course will continue the recessing of the front panel also by $\frac{1}{4}$ in.

Motor Board

The next stage should be to prepare the motor board. This board consists of a piece of plywood not less than $\frac{1}{4}$ in. thick and about 13 in. by 14 in. A cutting pattern will be included with the record turntable unit, and this rather complicated shape can be easily managed with a keyhole saw or padsaw. Do ensure, however, that when mounted on the board there is at least $6\frac{1}{2}$ in. clear in each direction from the spindle centre, otherwise there will be difficulty in playing 12 in. records.

The internal partition can then be fitted to form the separation between the motor compartment and the amplifier. This can be a piece of veneered plywood about $\frac{1}{4}$ in. thick and is kept in place by pieces of 1 in. square timber glued in place on the base of the cabinet and also in the corners to form the supports for the motor board. These supports should be $3\frac{1}{2}$ in. long and should be repeated below the opposite end of the motor board as in Fig. 2.

Record Compartment

The remaining partitions to protect the amplifier and to form a compartment for storage of 7 in. records can be constructed easily by using some hardboard channel moulding into which a piece of


hardboard can be slotted with a similar piece forming a cover over the amplifier.

Wiring

Wiring up the unit is carried out as in Fig. 3 by providing a twin flexible lead from the mains through a 2A fuse to the porcelain connector. The mains supply cables of the amplifier and motor can then be connected to the porcelain block. When connecting the pick-up lead from the amplifier to the pick-up connector tags below the motor unit, you must use coaxial cable, connecting the centre core to the red lead of the pick-up and the outer sheath to the earthed lead. It will probably be found advisable to earth the metal panel carrying the motor independently to the outer sheath of the coaxial cable in order to reduce hum to a minimum. The unit may now be tested and if all is well—and there is no good reason why it should not be—the finishing touches can be added.

The lid is fitted with two 3 in. cabinet hinges and is supported with a cabinet lid stay.

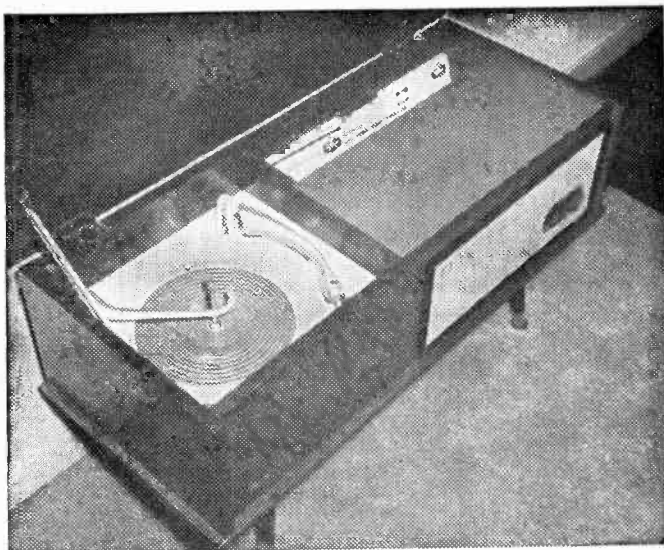The speaker cover panel is made up by using a piece of stiff cardboard of the necessary size to cover the speaker apertures, i.e. approximately $7\frac{1}{2}$ in x 18 in., cutting out suitable openings in front of the speakers and a shaped section to coincide



The finished cabinet has a professional appearance.

with the control knob panel. The cardboard is then covered with speaker cloth. An impact adhesive will be most useful for this in order to obtain a really neat finish. If the Cossor amplifier is used the clear plastic panel provided can be mounted behind the knobs before the speaker cloth panel is fixed, but in order to make the plastic panel with its gold transfer lettering show up better, give the panel a couple of coats of enamel (black or brown is suitable) over the gold lettering on the wrong side. When this is dry, the gold transfer stands out well against its enamelled

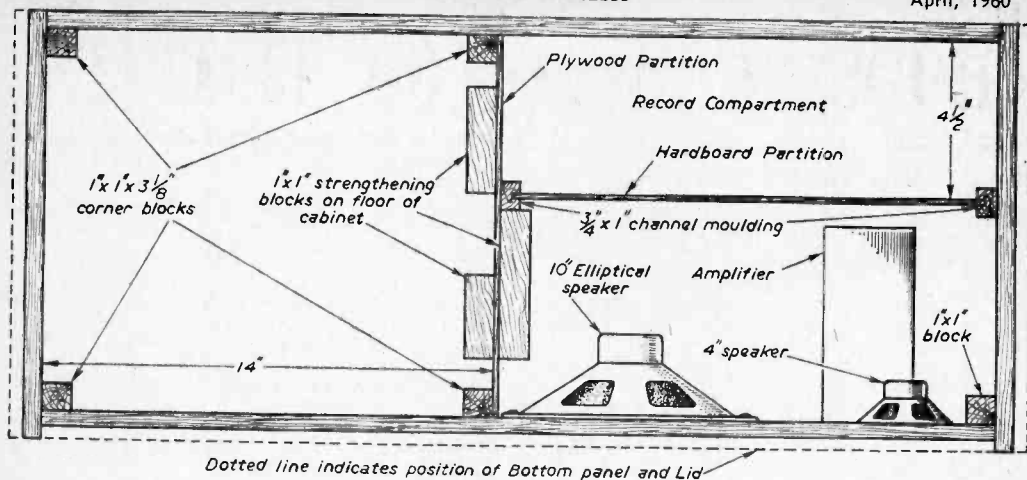


Fig. 2.— Plan view of the cabinet.

background. The speaker cloth panel can then be mounted in place using impact adhesive. A finishing touch can be given by framing the panel. This is ordinary modern picture frame moulding mitred and glued and then enamelled black. Before fixing in place, the front edge only is carefully sandpapered to expose the bare wood, this is then polished with wax polish and the frame glued into place.

The legs can be purchased already polished black and fitted with brass ferrules, and the fixing plates are quickly screwed into place. As the brass ferrules may dig rather unpleasantly into the carpet, a set of lin. rubber heels of the ordinary revolving kind can be screwed on to the base of the ferrules.

Finishing the cabinet consists of filling all pin holes and joint cracks with wood filler, carefully sandpapering down to a good finish and then

applying stain and a coat of wood sealer. Further sanding using the finest grade obtainable and a good coating of wax polish will produce a finish that will bear comparison with the far more expensive items in the local radio shops.

The Interior

To give a smart appearance inside the unit, the motor board, and the walls of the motor compartment to a height of about 4in. can be covered with

PARTS REQUIRED

- 1 4 speed autochanger record player unit.
- 1 Audio amplifier (about 3-4W output).
- 1 Set 9in. legs with metal fixing plates.
- 2 Veneered chipboard panels 36in. x 15in.
- 3 Veneered chipboard panels 36in. x 9in.
- 1 Cabinet stay.
- Tygan speaker cloth 19in. x 9in.
- Picture moulding (6ft).
- Adhesive plastic sheet— $\frac{1}{2}$ yd.
- 1 Porcelain junction block.
- 1 2A fuse and holder.
- 2ft coaxial cable.

Screws, panel pins, glue, solder, mains connecting lead, odd blocks of wood and plywood or hardboard for internal divisions, wood stain, filler and wax polish, hinges, etc.

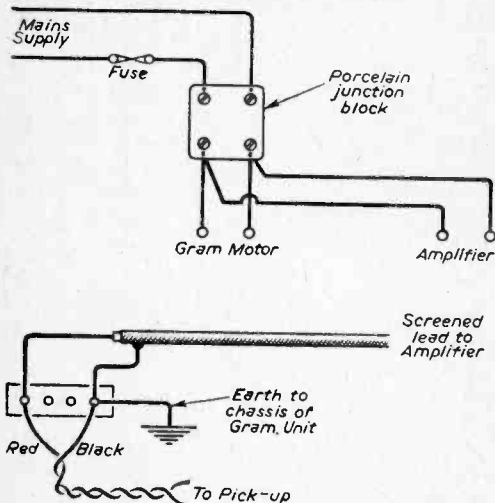


Fig. 3.— Mains and amplifier wiring.

a white plastic sheeting. This is also used to cover the hardboard cover of the amplifier. The remainder of the interior can be polished to match the outside.

Criticism

In conclusion, it may be stated that the pleasing appearance of the cabinet will put an end to the oft-voiced criticism of home-constructed apparatus—that it is only fit for the workshop or laboratory. The final touch to the author's record player was given by using some adhesive metal foil letters bought in a large store, to decorate the front with his initials.

CHOOSING DETECTOR CIRCUITS

CIRCUITS AND CHARACTERISTICS OF DIFFERENT TYPES

By J. B. Dance

EVERY radio and television receiver employs some form of detector (also known as a demodulator) which converts the incoming radio frequency signal into an audio frequency signal. The various types of detector circuits each have their own particular advantages and disadvantages.

Diode Detectors

The simplest form of detector circuit uses a diode. A form of diode was used in the crystal sets which were made in the early days of radio but nowadays a germanium diode would be used for a crystal set in order to achieve reasonable mechanical stability.

A simple diode detector circuit is shown in Fig. 1 with the filter circuit which removes the carrier frequency from the audio output. The filter consists of a resistor (R_1) and two condensers (C_2 and C_3); the condensers are chosen so that they present a low impedance to the carrier frequency and a high impedance to the audio frequency. If the carrier were not removed it might cause instability or overloading of the amplifier which follows the detector. The condenser C_4 prevents the D.C. output from the

supply and to keep the size of the circuit to a minimum.

The diode detector will handle large signals and the linearity is very good providing that the signal input amplitude is not less than about ten volts peak. It is, therefore, suitable for use in high fidelity circuits providing care is taken to avoid A.C. shunting of the detector output circuit which consumes power from the previous tuned circuit

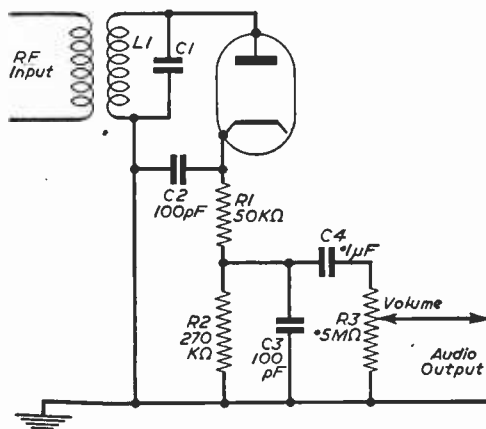


Fig. 1.—A practical diode detector circuit.

and, therefore, reduces the effective Q and the selectivity. The diode gives no gain and therefore the sensitivity of the diode detector circuit is low. This disadvantage is overcome in most simple broadcast and superhet receivers by the use of a double diode triode valve as shown in the circuit of Fig. 2. In this circuit the upper diode is the audio detector. The output from the detector is applied to the triode grid for amplification and the other diode is used to provide delayed AGC.

Leaky Grid Detectors

Leaky grid (or cumulative grid) detectors give a greater gain than any other type of single valve detector except the super-regenerative circuits. They are therefore very useful in battery receivers where the number of valves must be kept to a minimum in order to keep the power consumption low and are also usually used in simple one or two valve receivers. This type of detector circuit is not usually used in super-heterodyne receivers because it is so easily overloaded.

A typical circuit of a leaky grid detector is shown in Fig. 3 (neglecting, for the moment, the components shown dotted). The grid of the valve acts in the same way as the anode of the

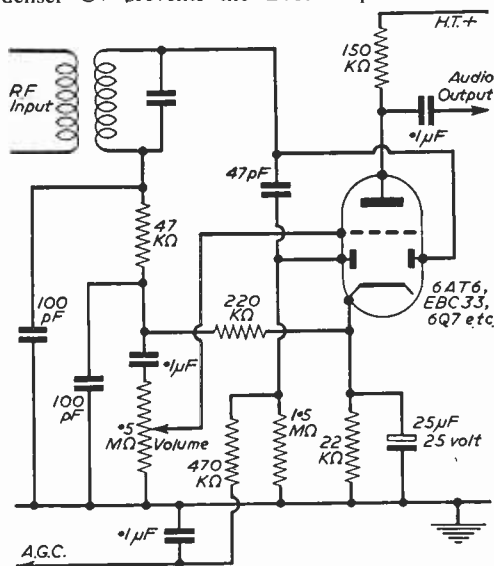


Fig. 2.—A double-diode-triode used as a detector, audio amplifier and AGC rectifier.

diode from passing into the volume control and the audio amplifier. The flow of D.C. through a high resistance gain control may cause "scratchy" noises. A suitable germanium diode (e.g. OA73) may be used instead of the valve diode in order to avoid the need for a heater

diode detector; the detection takes place in the grid circuit. The grid is biased by the rectified signal, no other bias being required. The condenser C2 and the grid leak resistor R1 are chosen so that the biasing voltage changes at the

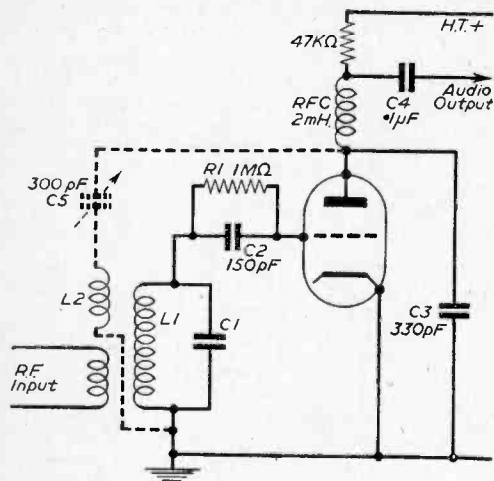


Fig. 3.—A leaky grid detector. The components shown may be used to make the stage regenerative.

audio frequency but not at the radio frequency. The audio biasing voltage is amplified by the valve in the ordinary way. C3 and RFC remove the carrier from the output of the detector. This type of detector is really equivalent to a diode detector followed by an audio amplifier.

Alternative Values

The amplification of the circuit can be increased by raising the value of R1 to about 3M but this will also reduce the signal handling capability of the circuit. Alternatively R1 may be reduced to about 100k and C1 to about 50pF in order to increase the signal handling capacity and the high audio frequency response at the sole expense of sensitivity; a leaky grid detector operated under these conditions is often called a power grid detector.

The gain of the circuit may be increased by the use of a pentode valve as shown in Fig. 4. Alternatively if a triode is used, the resistor R2 of Fig. 3 may be replaced by the primary of an audio transformer in order to obtain more gain. The output would then be taken from the transformer secondary and C4 of Fig. 3 would not be required. If a pentode is used it is not practical to use a transformer because pentodes have a very high anode resistance. The same performance will be obtained from the circuit if the grid leak resistor R1 is connected between the grid and cathode of the valve instead of in the position shown in Fig. 3. A valve having a low mutual conductance and a low amplification factor will operate satisfactorily at higher input voltages than modern valves, but the gain is lower.

Although the high gain of a leaky grid detector is often useful, the circuit has a number of disadvantages and is not often used in modern receivers. The tuned circuit feeding the detector is loaded by R1 and its selectivity is therefore reduced. The linearity is poor and the signal handling capability is very limited so that the circuit is not used when good quality reproduction is desired. The circuit is not very efficient at small input voltages.

Regeneration

The sensitivity and selectivity of the leaky grid circuits can be improved considerably by the use of some positive feedback (reaction or regeneration). This is not possible with diode detectors because they do not amplify. The only components required to make a leaky grid detector circuit regenerative are shown dotted in Fig. 3. As the condenser C5 is increased in value, the amplification of the detector circuit increases until it eventually oscillates. The sensitivity and selectivity are greatest just before oscillation commences. It is important to connect L2 (the feedback or reaction) the correct way round or the feedback will be negative and the sensitivity will be reduced. If no regeneration can be obtained the connections to the reaction coil should be reversed. It should be at the earthed end of the grid coil and the number of turns used should be the minimum which will allow the circuit to oscillate on all the input frequencies. Generally the number of turns should not be more than about one sixth of the number of turns on the grid coil, L1. For a certain setting of C5 the amount of regeneration depends on the input frequency.

Anode Bend Detectors

In anode bend or plate detectors rectification takes place in the anode circuit of the valve. Negative bias is applied to the grid (or positive

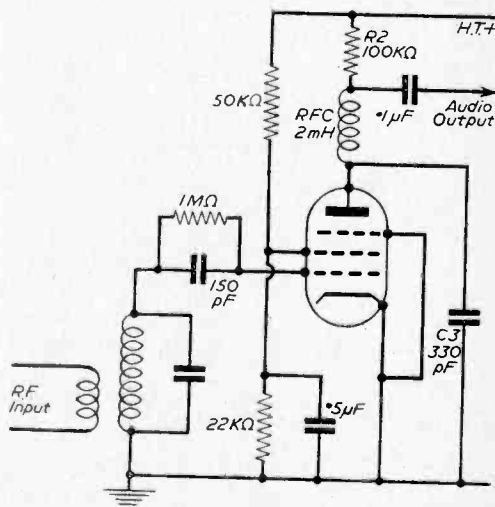


Fig. 4.—A leaky grid detector circuit using a small pentode.

voltage to the cathode) so that the valve is almost cut off; i.e., the anode current is very small. When a signal is applied to the grid, the anode current increases. A triode may be used as shown in Fig. 5, but more gain can be obtained from a pentode. Both audio and R.F. frequencies are by-passed by C4. The RFC and C3 remove R.F. frequencies from the audio out-

put at audio frequencies (but not at radio frequencies) and audio distortion is much reduced. The loss of gain is also very considerable. The results obtained from an anode bend detector with negative audio feedback are intermediate between those which can be obtained without feedback and those obtained from a cathode follower detector circuit.

Cathode Follower Detector

This type of detector imposes a smaller load on the tuned circuit feeding it than any of the circuits described above. It is, therefore, sometimes known as an infinite impedance detector. A circuit is shown in Fig. 7 (page 1066). The condenser C3 is of such a value that it bypasses R.F. signals but not audio signals. If C3 is much too small the detector can become unstable. C4 prevents the D.C. voltage from being applied to the following audio amplifier and C5 in conjunction with R3 filters out the carrier.

The cathode follower detector is very similar to the anode bend detector except that the signal is taken from the cathode; negative feedback therefore occurs at audio frequencies. The output voltage is always slightly lower than the input voltage. The signal handling capabilities of the

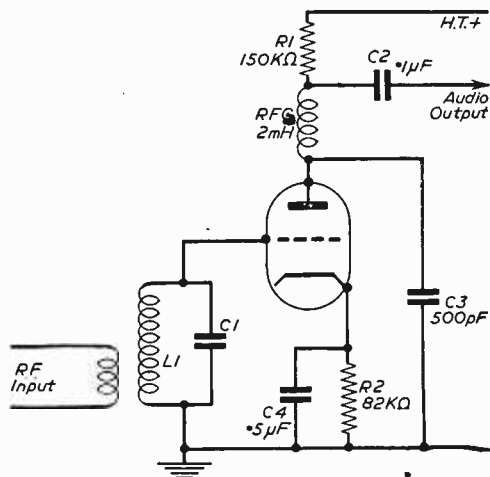


Fig. 5.—An anode bend detector using a triode.

put. The output from an anode bend detector cannot normally be transformer coupled to the next stage because the anode resistance of the valve when biased nearly to cut-off is very high.

The value of the bias voltage required for an anode bend detector is too critical for it to be obtained from a grid bias battery and a resistor should be used in the cathode lead as in Fig. 5. If the characteristics of the valve change during life or if the valve is replaced at any time, the self compensating action of the circuit will provide the correct bias under all conditions.

The anode bend detector has the advantage that it does not impose an appreciable load on the tuned circuit (providing the detector is not overloaded) and therefore maximum selectivity is obtained. Although the amplification obtained from an anode bend detector is less than that obtained from the leaky grid circuit, it is nevertheless much more sensitive than the diode circuit. The anode bend detector will handle larger signals than the leaky grid circuit but it is much inferior to the diode in this respect. The linearity for small inputs is very poor.

Anode Current

When a signal is tuned in, the anode current of an anode bend detector increases but that of a leaky grid detector decreases owing to the extra negative bias. It is therefore possible to ascertain which of these two types of detector circuit is being used in a receiver by placing a milliammeter in the detector anode circuit and noting the reading with and without a signal.

Much less distortion at the expense of sensitivity can be obtained from an anode bend detector if the value of C4 in the circuit of Fig. 5 is reduced to about 200pF. Feedback then occurs

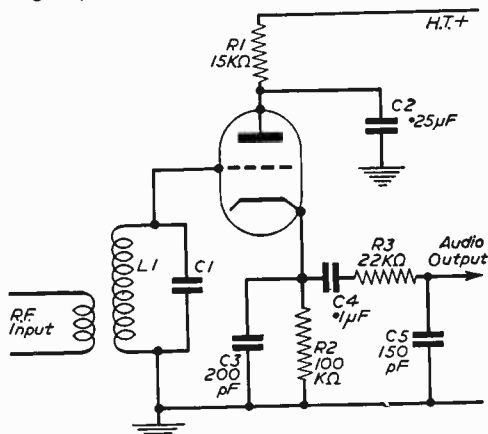


Fig. 6.—A cathode follower detector circuit.

cathode follower detector are good. The linearity of the anode bend detector is only fair, but this is vastly improved in the cathode follower circuit by the negative feedback. The cathode follower detector can, therefore, be used in high fidelity circuits and is especially useful for TRF tuner units for local station reception when it is desired not to load the previous tuned circuit in order to obtain maximum selectivity. The distortion and sensitivity of the cathode follower detector are about equal to that of the diode circuit. The cathode follower detector gives its best performance at fairly high input voltages (about ten).

Obtaining AGC

One of the greatest disadvantages quoted against the cathode follower circuit is that AGC cannot easily be obtained. This is probably the major reason why it is not used to a greater extent
(Continued on page 1066)

Simple Morse Oscillator

A TRANSISTORISED CIRCUIT

By J. H. Talbot

IF, as is hoped, the would-be amateur transmitter has followed the instructions given in the February issue of *PRACTICAL WIRELESS*, in memorising the morse code, he should be in a position to think about having some practice in sending on a morse key, for it is only by constant practice that one is able to master the art of sending and receiving morse code.

Suitable Key

The first requirement is a suitable morse key. There should be no difficulty in obtaining, at moderate cost, a well balanced, adjustable morse key from one of the many dealers in ex-government equipment.

The function of the morse key is to make and break the transmitted carrier wave (CW), into a

"spares" box. Power requirements are also very low: a single $1\frac{1}{2}$ V battery will give a good signal in the headphones. Also, on being keyed, the oscillator is free from key clicks, thump or chirp, which can be rather distracting to the beginner.

Circuit Details

The circuit, which uses an OC70 transistor, is shown in Fig. 1. Oscillation is produced at audio frequency by feedback from collector to base of the transistor by means of a small intervalve transformer. The type of transformer does not appear to be at all critical, provided it has two separate windings, with a fair amount of turns on each. It will have some bearing on the frequency of the tone produced, but if the value of condenser C2 is varied, it should be possible to produce a tone of approximately 400c/s frequency, which is about right for a morse practice set. Resistor R1, which is 270k, provides the bias and limits the current drawn by the collector. With the values shown in the circuit and with $1\frac{1}{2}$ V applied, the total collector current as measured was just on $300\mu\text{A}$ (0.3mA). If, on testing, no signal is heard in the headphones, the leads on one of the transformer windings should be reversed.

Construction

Apart from the usual care needed when soldering transistor leads (by the heat-shunt method) the actual constructional details are left to individual requirements. If the transformer used has a tag-board, the few components could be grouped on this, and the whole unit, including the battery, housed in a small box, with a couple of jack sockets on the lid for plugging in the headphones and morse key.

One other point, be sure that the battery is connected so that negative voltage (—) is applied to the collector of the transistor. If positive voltage (+) is applied, if only for an instant, the transistor will be destroyed.

Other Uses

In conclusion, it might be mentioned that this handy little unit might well have other uses. In the writers case, so well did it perform, that it was promptly installed into a resistance/capacity bridge, in place of an existing mains-driven audio oscillator, where it is giving excellent service.

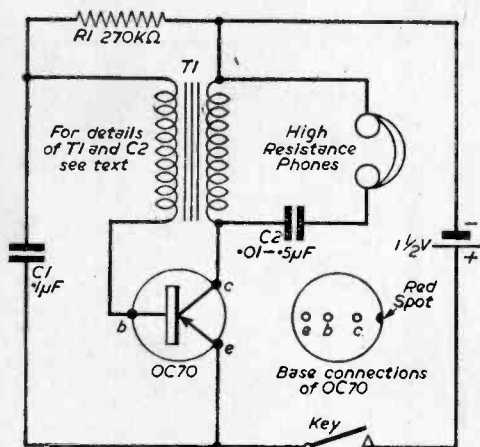


Fig. 1.—The circuit diagram.

timed sequence, so that the intelligence of the morse symbol is conveyed to the receiver. Remember that a dash is equal to three dots in time, while the interval between the dots and dashes in a sequence equals a dot in time, between two letters in a word the interval equals three dots and between two words five dots.

Oscillator

For practice purposes, some form of audio frequency oscillator will be required. A signal generator could be used, provided it has a modulated tone and can be keyed. However, it is strongly recommended that the transistor audio frequency oscillator, of which details are given, should be constructed. It has several advantages over the usual type of audio oscillator.

The cost is very modest, as apart from the purchase of the transistor, most of the few components required will no doubt be found in the

PRACTICAL WIRELESS CIRCUITS

17th Edition

By F. J. CAMM

17/6, by post 18/7

from

GEORGE NEWNES, LTD.,

Tower House, Southampton Street, Strand, W.C.2.

**FULLY
UP-TO-DATE
EDITION**

**FOR
READERS OF
"PRACTICAL
WIRELESS"
AT REMARKABLY
LOW COST!**

RADIO, TELEVISION & ELECTRICAL REPAIRS

SAVES YOU POUNDS!

Here is just the practical, at-a-glance guidance YOU need, whether you wish to know how to service radio and TV sets, install an extra lighting point, or repair any domestic electrical appliance—from a bell or an iron to a vacuum cleaner or washing machine. Explains, in simple language, basic principles and working of modern radio and TV sets and electrical appliances. Shows how to test for faults and carry out maintenance and repair work by the most modern methods. Special section on the operation and servicing of frequency modulated receivers. 480 pages. Over 400 illustrations. Amazing value—De Luxe Edition only, superb leathercloth, 20/-. Price includes post, packing, etc.



**480
PAGES
OVER
400
ILLUSTRATIONS**

**ALL THIS—AND
MORE—IN ONE
GREAT VOLUME**


Comprehensive Contents Include

Current, Voltage, and Resistance. Coils, Capacitors and Valves. Basic Radio-receiver Circuits. Preliminary Tests. Instruments for Set Testing. Locating Faults. Dynamic Testing. Tuned Circuit Alignment. Noises, Interference, Distortion and Instability. Components. Loudspeakers. Pick-ups. Gramophone Motors. Frequency Modulation. Television Circuits and Test Gear. Television Faults, Symptoms and Cures. Aerials and Pre-amplifiers. Maintenance of Domestic Electric Wiring. Small Appliances. Fires and Space Heaters. Vacuum Cleaners and Polishers. Rewinding Small Motors. Cookers and Boiling Plates. Washing Machines. Refrigerators. Electric Water Heaters. Battery Charging, Testing and Repair, etc.


**ESSENTIAL TO EVERY SERVICE ENGINEER,
ENTHUSIAST AND HANDYMAN!**

GETTING THE BEST FROM RADIO AND TV SETS

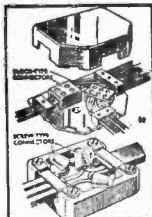Here is expert advice that will enable you to make the necessary adjustments or repairs in order to get the best possible performance from any radio or TV set. **All you need to know about DOMESTIC WIRING**



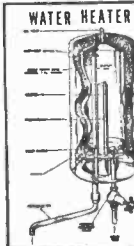Learn from these helpful pages how to carry out all kinds of installations and extensions—with efficiency and safety! Complete guidance on conductors, insulation, safety regulations, conduits, cables, earthing, practical work, fuses, flexible cords, etc.



FIRES & SPACE HEATERS


Full, easy-to-follow instructions for servicing small domestic fires—whether of the radiant, reflector or convector type.

WATER HEATING

All you should know about the various types of electric water-heaters and how to install them and keep them in perfect working order. Advice that will save you POUNDS!

TRACKING DOWN TROUBLE

This grand book is invaluable for tracing faults in radio and TV sets. Tells you all you want to know—from how to carry out Preliminary Tests to how to align R.F. and I.F. circuits. Shows how to carry out Dynamic Testing. Also shows how to trace the cause of Noises, Distortion and Instability and deal with the trouble. Gives detailed information on Components and Loud-speakers and how to deal with any faults that may develop.

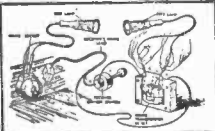

DO THIS NOW!

Simply fill in form and post in 2d. stamped, unsealed envelope to Dept. E.B.35, People's Home Library, Basted, Sevenoaks, Kent. Offer applies in U.K. and Eire only, closes April 30. **FULL SATISFACTION or No Charge GUARANTEE**

BASIC RADIO CIRCUITS

All you want to know about circuits, so that you can find your way around modern sets without hesitation. How components form various types of set; gives circuits for 1-valve receiver, 3-valve receiver, battery TRF receiver, 4-valve superhet, Universal sets, etc.



Disconnecting Boiling Plate on Cooker

See how to maintain **Vacuum Cleaners and Floor Polishers, Refrigerators, Cookers and Boiling Plates, Washing Machines, etc.**

Do your own BATTERY CHARGING
Here are clear, complete instructions.

The book that cuts out guess work! **TV FAULTS—** their SYMPTOMS AND CURES

POST FORM NOW!

Dept. E.B.35, People's Home Library
Basted, Sevenoaks, Kent.

WITHOUT OBLIGATION reserve me "Radio, Television and Electrical Repairs" and send invoice with "100% Satisfaction or No Charge" Guarantee.

BLOCK LETTERS

NAME _____

Full Postal ADDRESS _____

Firmly affix
2d. stamp
in margin

E.B.35/Apl. '60

Premier RADIO

23, TOTTENHAM COURT ROAD, LONDON, W.1.

TEL.: MUSEUM 3451/2



The "Petite" PORTABLE

MAY BE BUILT FOR

£7.7.0

Plus p. & p. 3/-.

BATTERIES EXTRA.
H.T. 10/- (Type B126) or
equivalent L.T. 1/6 (Type
AD35) or equivalent.

★Size only 8in. x 8in. x
4 1/2in.

★Instruction book 1/6.

THE BERIC

The 'Beric' Battery Receiver for only
£4.19.6, plus 5/- p. & p., or £1.0.0
dep. and 5 mthly pymts of 19/-. Suitable
for use in the home or where normal
electricity supply is not available, re-
markable reception on med. and short
wavebands, using DK92, DF92, DAF96,
DL96, latest type min. Battery Valves : operates on an external
B.103 Battery or equiv. Housed in an attractive, two-tone metal
case. Size 11 1/2 x 7 1/2 x 5 1/2 in. BATTERY EXTRA 18/6



VISIT OUR NEW BRANCH AT 309 EDGWARE ROAD, W.2.

Telephone PAD 6963



The Famous Cossor 3 watt
AUDIO AMPLIFIER KIT 562K
Original Price £9.15.0.

OUR PRICE **£5.19.6**, p. & p. 2/6

This Kit assembled will provide a compact versatile Amplifier which incorporates the most up-to-date pre-assembled printed circuit and is suitable for operation from Radio, Microphone or Gramophone. The circuit design includes negative feedback, valve line-up 6V4, 6BQ5, EF86. Two Loudspeakers are used, i.e., 10in. x 6in. Elliptical and 4in. Treble, ensuring high quality output, suitable for use on 200/250 v. A.C. mains. All items are supplied, including Loudspeakers, Knobs and Escutcheon, with full assembly instructions and in maker's original cartons.

POCKET TEST METER

Truly efficient Meters for the enthusiast:-

CABY MULTI-METER A-10

Ranges: DC/V 10-50-250-500-1kΩ (2kΩ/V)
AC/V " " " " " "
DC/mA 0.5-25-250 (250mV) " "
OHM 0-10kΩ-1MΩ

Complete with Test Leads

£4.17.6 p. & p. 2/6

ERSIN MULTICORE SOLDERS

for a first class joint every time

Ersin Multicore contains 5
cores of extra-active, non-corro-
sive Ersin Flux. Prevents oxida-
tion and cleans surface oxides.

SIZE 1 CARTON

5/-

HANDYMAN'S CARTON

Suitable for 200
average joints.



6d.

HOME CONSTRUCTORS 2/6 PACK

In addition to the well-known
Home Constructors Pack (con-
taining 19ft. of 18 s.w.g.
60/40 alloys) a similar
pack is now avail-
able containing
40ft. of 22 s.w.g.
60/40 alloy
especially suitable
for printed circuits.



Wherever precision soldering
is essential, manufacturers,
engineers and handymen rely
on MULTICORE. There's a
MULTICORE SOLDER just made
for the job you have in hand.
Here are some of them.

SAVBIT TYPE 1 ALLOY

A specially formula-
ted alloy to reduce
the wear of soldering
iron bits. Contains 5
cores of non-corro-
sive Ersin Flux and
is ideal for all sol-
dering purposes.



SIZE 1 CARTON 5/-

Available in three specifications.

BIB WIRE STRIPPER AND CUTTER

Strips insulation
without nicking wire,
cuts wire cleanly,
splits extruding
flex. 3/6 each



MULTICORE SOLDERS LTD.,

MULTICORE WORKS, HEMEL HEMPSTEAD, HERTS. (BOXMOOR 3656)

Build your own HI-FI!

At last! A specially
selected and
designed HI-FI
Sound installa-
tion for your home
at really reason-
able cost!

You save because you
assemble everything
yourself following
our step by step in-
structions. You gain
because you learn
about the equipment
as you build and are
able to service and
maintain it after-
wards. Best of all—
you'll have fun building it and be thrilled with the finished in-
strument which will bring you an entirely new experience in the enjoy-
ment of sound. No previous skill or experience is needed. Post coupon
now for full details, without any obligation. Easy terms available.

Equipment includes: Luxury Cabinet - Top Quality Amplifier
suitable for stereo or non-stereo reproduction. VHF/FM Radio
Units - Record Player - Tape Recorder - HI-FI Speaker system.

FREE BROCHURE - POST TODAY

Radiostructor (Dept. H34), 46 Market Place, Reading, Berks.

Please send Brochure without obligation to:

Name _____ BLOCK
Address _____ CAPS
PLEASE

309

We do not employ representatives

RADIOSTRUCTOR

BRITAIN'S LEADING RADIO TRAINING ORGANISATION

Repairing "Staar Motors"

WINDING NEW COILS FOR "GALAXY" RECORD CHANGERS

By D. Brammer

THE motor fitted to Staar Galaxy record changers is very compact, and quiet in operation. No cooling-fan is fitted, and as a result it overheats with prolonged use, the insulation suffers and one or both of the two coils shorts to the frame, which is earthed, and it burns out. Repairing the motor is not a difficult task, providing care and patience are exercised.

Dismantling

Before the motor can be removed, the grub-screw securing the motor pulley to the shaft of the motor must be removed, or else difficulty will be found in withdrawing the motor later on. First remove the top cover by undoing the Phillips screw next to the speed selection lever, and by lifting the record-steady arm and swinging it sideways, after the tone arm has been lifted from its rest, it will be easy to lift the cover clear. A small Allen key will be required to loosen the grub-screw. If one is not available, a simple substitute can be made by bending over the end of a piece of 20s.w.g. piano wire, and this should just fit in the grub-screw. When the motor pulley has been removed, it should be put aside in a small box, and as work progresses, other small pieces should be added, for they are easily lost. As the unit will be upside down whilst the next stages are in progress, it is a good idea to remove the turntable, because of its weight. This is done quite simply by removing the spring-clip which holds it in place, and lifting it out. Before the unit is inverted, the clip anchoring the wires which lead from the motor to the voltage selector and to the micro-switch (if fitted) should be unscrewed. Note down carefully where the motor wires are connected, and disconnect them. On some models the connections are made under the "chassis"

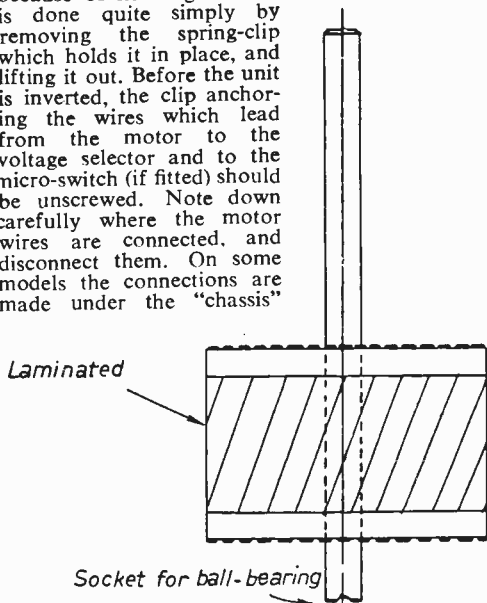


Fig. 2.—The rotor of the unit.

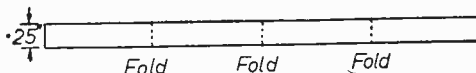
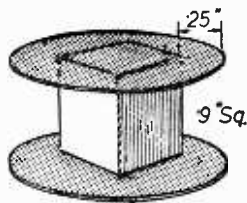


Fig. 1.—The coil former.

and cannot therefore be reached yet. Now the unit must be inverted. If it is mounted on a plastic base, leave it on for the time being; it makes it easier to handle.

Raise the record-steady arm and swing it inwards (towards the speed selector) as far as it will go. Holding it in that position, invert the unit and place it on the bench so that it rests on the centre-spindle and the record-steady arm. Lift the plastic base, and put it away. Having made sure that the motor is disconnected, remove it. This is done by removing the spring clips from the three supporting pillars, and lifting it clear. It will be evident on examination that before any work can be done on the motor, the mounting plate must be removed. It is riveted on to the frame of the motor at two diagonally opposite corners, and the rivets can be drilled out easily.

Bearings

The next step is to remove the two black steel spring clips which secure the bearing cages. In the bottom bearing is a small ball. It must not be lost. When the rotating part of the motor is removed it will be seen that there are four pieces of metal which can be withdrawn (see Fig. 3) from the frame of the motor by sliding them out, either upwards or downwards. A metal strip (see Fig. 3) is bent around each coil, holding it against the frame. When these have been removed, the coils can be eased out. Assuming that only one coil has burnt out, and that the other one is still usable, it is a good idea to improve the insulation of this coil by packing thin pieces of Paxolin, transformer paper, or some other insulator around it, so that the coil does not touch the frame anywhere.

Cardboard Former

A former should be made up, of thin cardboard, as in Fig. 1, and the parts fixed together with self-adhesive tape. Fix the former on a coil winder, and wind on 40s.w.g. enamelled wire until the former is nearly full. Test its resistance, which should be about 500Ω. Adjust the number of turns until this figure is obtained. Cut the wire, remove the coil, and cut the tape away carefully with a sharp modelling knife or razor blade. When the former has fallen away from the coil wind on the insulating tape, tightly. The ideal tape width is ½ in., and as this may not be available, normal ¾ in. tape may be cut in half down the centre to produce this. When two or three layers have been wound on, solder on the connecting wires, and add another two layers to secure these wires.

Testing

When the motor has been re-assembled, it should be tested before replacing it in the player. The

coils should be connected in series for operation on 210-240V A.C. mains, and it should run noiselessly. If it is noisy, the motor is probably off centre. To cure this, just loosen the two block clips and move one of the cages slightly. Replace the clips and test the motor again. If the fault persists it is possible that one or more of the "pole pieces" inside the motor are slightly out of position. This can be checked by removing the bottom cage and sliding the motor out. When the motor is running satisfactorily, the top mounting plate may be soldered on, after first scraping off the varnish.

Should the motor run too slowly, one of the coils is out of place, and its connections should be reversed.

Final Assembly

The motor may now be replaced in the player. Check all the winding very carefully before connecting to the mains. The only other point to watch is that the motor pulley is at the correct height for the speed change to operate and that its grub-screw is well tightened. The rest should be plain sailing!

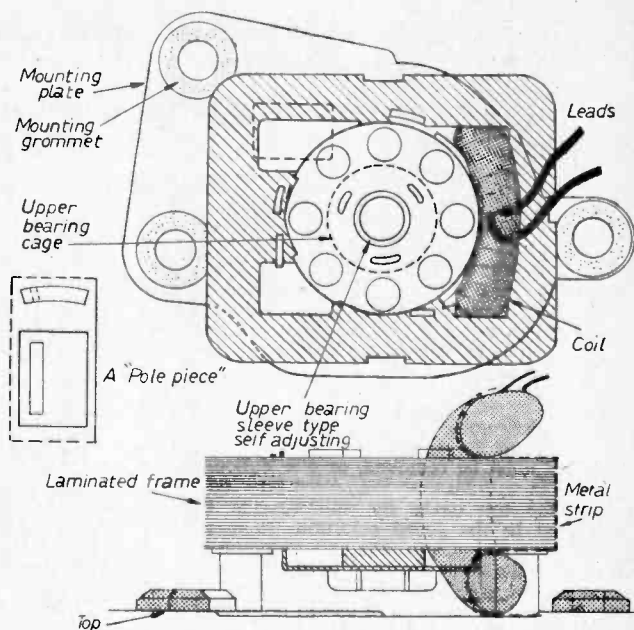


Fig. 3.—Diagram of the motor.

A QUALITY OCTET

(Continued from page 1032)

3-gang capacitor has been removed a length of $\frac{1}{4}$ in. spindling will be required. Final interconnecting leads can then be soldered in position. Note that in the original the dial has been countersunk in the front panel, but some patience is required for this operation.

A small speaker is inadequate for F.M. quality reception and the prototype feeds a 10 in. baffle-mounted unit leaving little to be desired.

Alignment of the I.F. strip—which operates at 10.7 Mc/s—should be carried out with a signal generator, etc., but alignment of the R.F. stages may be carried out on signals when a dual tuning wand will be found useful.

Cabinet

The author professes no skill in carpentry and the simple plans detailed in Fig. 5 could doubtless be improved. However, the final result looks pleasing and, except for the front and rear panels is made entirely from 5-ply wood. The top, sides and bottom are secured by $\frac{1}{4}$ in. wood screws projected into the front and rear panels, the resultant edges being obscured at the front by a frame of $\frac{1}{4}$ in. beading glued securely, after covering the panel with a suitable shade of wallpaper. When the glue is dry, the protruding edges of the paper are trimmed away and that remaining treated with clear nail varnish, etc., to strengthen it. The greater part of the bottom plate is cut away to assist ventilation and to make components accessible. Ventilation is further assisted by rectangular cut-outs made in the sides of the cabinet so that air is convected from below. These cut-outs also act as carrying handles.

TRANSISTORISED SUPER-REGENERATOR

(Continued from page 1040)

The set can now be switched on, whereupon a hissing sound will be heard in the phones indicating that the detector is operating properly. A short vertical aerial of approximately 15 ft, together with a good earth, should be connected to the set. Signals should now be heard. Potentiometer R2 may now be adjusted for maximum gain consistent with good selectivity and low background noise with a station tuned in. Thereafter, R2 will need little, if any, adjustment. It will be found that R1 also has an effect on signals, and this control should be used and adjusted in conjunction with the tuning control C3, adjusting R1 as each station is tuned to suit personal requirements. The gain control, R4, may be adjusted to give a comfortable level of volume. In the event of no oscillation, or spasmodic operation over the range of C3, the coil L2 may be adjusted closer to L1 and the condenser C1 altered in value up to a maximum of 0.1 μ F.

The coil, L3, may also be adjusted for best sensitivity in a similar manner.

Results

It is, of course, important that one should listen when the 10 m band is "open". There are times when no signals at all are heard on this band.

A few hours later signals may be heard very strongly.

A cabinet to suit the taste of the individual constructor can be made to fit the front panel. Plywood covered with one of the self-adhesive plastic materials gives a very pleasing effect for very little expense and trouble.

be TRANSISTOR-WISE! be POCKET-WISE!



"RECO" MIDDY ONE

(Medium and Long Waves.) Size $4\frac{1}{2} \times 3\frac{1}{2} \times \frac{1}{2}$ in. Variable sensitivity control. High gain Vari Q Ferrite Rod Aerial. "Sonotone" Dynamic Earpiece. Months of listening pleasure from $1\frac{1}{2}$ volt pencil. Complete Kit with EDISWAN TRANSISTOR and easy build plans, 39/6, post free.


AMAZON THREE TRANSISTOR POCKET RADIO

Covers 100 to 500 metres and Short Waves. New improved, super sensitive 5-stage reflexed circuit. EDISWAN transistors. Pocket sized case $4\frac{1}{2} \times 3 \times 1\frac{1}{2}$ in. Ferrite rod aerial. Case body in black polystyrene with contrasting grille in red. Complete kit with easy build diagrams and "Sonotone" dynamic miniature earpiece with moulded insert. 72/6, p.p. 2/6. Fitted (in PPS case) with high grade 3in. moving coil speaker (for local station use), less earpiece, £4.7.6, p.p. 2/6. "The tonal quality and bass response is surprisingly good."

—Midlands customer

"RECO" PUSH - PULL FOUR TRANSISTOR KIT

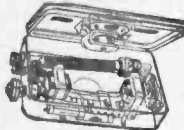(Medium and Long Waves with two S/W Coils FREE upon request.) Case size as PP5. New improved circuit. 3in. High Grade Moving Coil Speaker. Bias sensitivity volume control. Ferrite Rod Aerial. Gleaming Pale Blue Polystyrene Case with Contrasting Speaker Grille in Red. Complete Kit with 4 1st grade EDISWAN TRANSISTORS and 3 volt battery, £5.3.6; p.p. 2/6.



"RECO" PUSH-PULL FIVE TRANSISTOR KIT

(Size $6\frac{1}{2} \times 4\frac{1}{2} \times 1\frac{1}{2}$ in.) Medium, Long Waves and Trawler Band. Indoors or outdoors this brilliant radio brings Home and Continental Stations to your fingertips. High Grade 3in. Moving Coil Speaker. Regenerative receiver with EDISWAN TRANSISTORS. Push-Pull Output Stage. High Gain Ferrite Rod Aerial. Gleaming Pale Blue Polystyrene Case with Contrasting Speaker Grille in Red. Complete Kit with Pencil battery and easy build diagrams, etc., £6.9.6; p.p. 2/6. A customer in Dorset writes—"Makes fine car radio."

"RECO" TRANSIGEN THREE TRANSISTOR KIT

(Case as PP5.) (Medium, Long Waves and Trawler Band.) Entirely self-contained no external aerial required. Fitted Super High Gain Ferrite Rod Aerial. R.F. Stage, EDISWAN TRANSISTORS. On test: tuned in Home, Light, Third, Radio Luxembourg, A.F.N. and many others at good listening level. The Prototype was tested at approximately 50 miles from nearest transmitter. Complete Kit with Super B.A. Reproducer and battery, 75/-, p.p. 2/6. Or with "Sonotone" super dynamic miniature earpiece, 79/6.



"RECO" INJECTOBOOST

Add an R.F. stage to your receiver; bring in those weak stations, improve selectivity. Complete kit with XB102 (list 26/-) regeneration control, switches, Plastic case, wiring diagram, etc. Simple—effective. 29/6, p.p. 1/6. (Not suitable for valve, super-het or regenerative receivers). Plans with kit only.

AFTER SALES SERVICE.


Circuits and price list for 4 above kits, 2/6.

RADIO EXCHANGE CO.

27 HARPUR ST., BEDFORD.

Telephone 2367

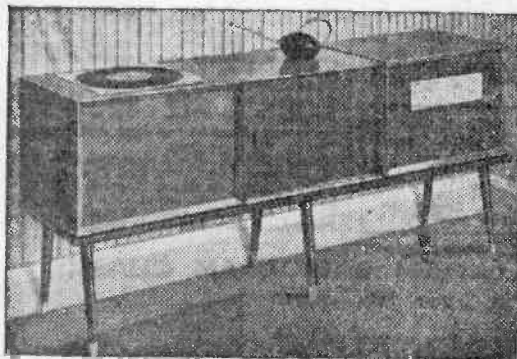Name, address BLOCK letters please. Closed 1 p.m. Saturdays.



NORDYK HI-FI UNITS

suit every kind of home; you build up the wall in small rooms, along the wall in large ones.

Dimensions: 19 $\frac{1}{2}$ in. wide x 15 $\frac{1}{2}$ in. deep x 13 $\frac{1}{2}$ in. high. The Speaker Enclosures (left) designed for us by Goodman's for their 8 in. Axiatic, costs £5.17.6. The Record Unit (centre) holds 150 records. Price £4.17.6. The Gram Unit (right) will house all turntables, amplifiers, and maybe a radio tuner too. Price £5.19.6. As illustrated they stand on the Continental Bench, which costs £5.7.6.

If you tell us your nearest main shopping centres we will gladly advise you of your nearest dealer. Write for illustrated catalogue to Dept. P.W.460.

RECORD HOUSING

Brook Rd. London N22
BOWes Park 7487.


Multi-Purpose VALVE FILAMENT TESTER

Model VT41

- Pocket size
- Battery operated

GIVES INSTANT CHECK OF:

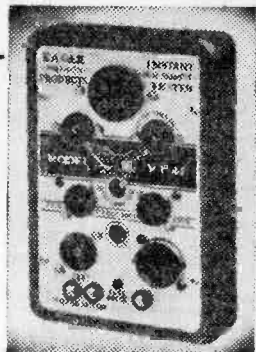- ★ All TV and Radio Valves and Fuses.
- ★ All pilot lamps.
- ★ Circuit Continuity.
- ★ Built-in 7 and 9 pin valve straighteners.
- ★ Built-in Battery Test.



Finished in black hammer case with gold front panel.

30/- Complete with internal batteries and ready for use.

P. & P. 2/6.

With this revolutionary instrument you can test all current Valves, Fuses, Continuity and other radio parts. All components tested are shown "good" or "faulty" on panel indicator.

From your local dealer or if in difficulty order direct:

EAGLE PRODUCTS (Dept. P.W.1.)
EAGLE WORKS, COPTIC ST., LONDON, W.G.1.

Rectification and Smoothing

VARIOUS FILTER CIRCUITS

By J. Ball

ONE of the main decisions which must be made when constructing a power pack is whether a mains transformer will be used. Mains transformers are fairly expensive and cannot be used in equipment designed for A.C./D.C. operation. The advantages of using a mains transformer are that any desired voltage can be obtained, full-wave rectification can easily be used and the chassis can be isolated from the mains and earthed. In A.C./D.C. receivers and other equipment without a

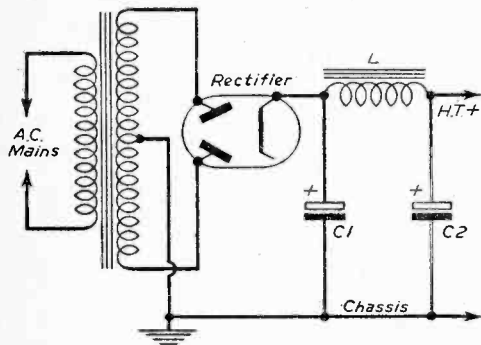


Fig. 2.—A typical full-wave rectifier circuit.

mains transformer, the chassis is connected to one side of the mains; as this may be the "live" side, the chassis should not be touched when the receiver is connected to the mains. Constructors who enjoy experimenting are therefore strongly advised to use a mains transformer.

Metal rectifiers are especially useful in A.C./D.C. equipment, as they do not require a heater supply. A typical half-wave rectifier circuit for use without a mains transformer is shown in Fig. 1.

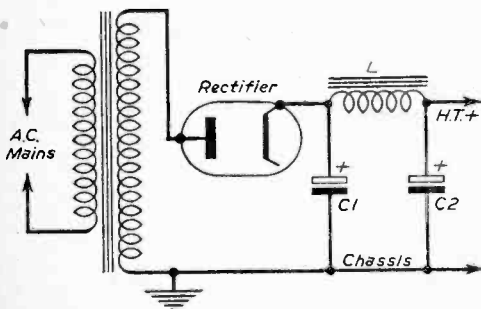


Fig. 3.—Simple half-wave rectifier circuit.

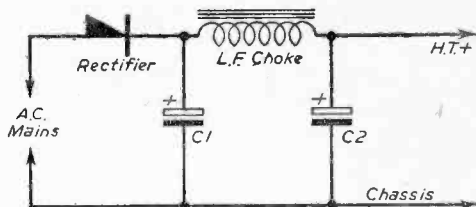


Fig. 1.—An H.T. supply which does not employ a mains transformer. Half-wave rectification is used and the chassis is "live".

Common Circuit

The circuit of Fig. 2 is perhaps the most commonly used circuit for providing H.T. in broadcast receivers. Full wave rectification is used and therefore smaller values of smoothing components can be employed than in the similar half-wave circuit shown in Fig. 3. The transformer used in the circuit of Fig. 2 must have a centre-tapped H.T. secondary winding such that the total voltage (r.m.s.) across this winding is nearly double the H.T. output required. The H.T. secondary winding of mains transformers for use in normal broadcast receivers is usually rated at about 300-0-300V at 80 to 120mA.

Where possible an indirectly heated rectifier should be chosen so that, after switching on, the H.T. voltage is not applied to the valves in the equipment until they have warmed up. This prolongs valve life and prevents condensers from having to withstand a much higher voltage than normal just after switching on. For similar reasons, the use of metal rectifiers is not always advisable.

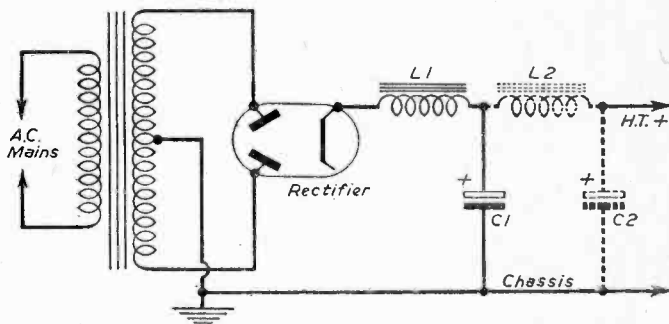


Fig. 4.—A full-wave rectifier circuit employing a choke input filter. The components shown dotted will give a further reduction in hum.

Smoothing

The output from any rectifier contains a considerable amount of 50c/s hum voltage or "ripple." Most of this must be eradicated or hum will be present in the output of the receiver. A trace of hum always remains in the output from a power pack after smoothing, but this hum voltage is further reduced by the decoupling components used in certain stages.

The two condensers and choke used for smoothing in Figs. 1, 2 and 3 form the commonly used simple smoothing circuit known as a π -filter

(Continued on page 1074)

Repetitive Timer

A VERSATILE CIRCUIT

By E. Leatherland

THE writer was asked to construct a repetitive timer to be used in lightning chess; the requirements being that a bell should ring automatically every 15 seconds when the players were required to make their next move.

This is, of course, only one of the many uses to which a device of this nature could be put. For instance, in photography it could be most useful as a timer for developing and printing purposes.

Circuit

It was decided to make the "time on" and "time off" periods variable; from 1 to 30 seconds "time off" and from 1 to 5 seconds "time on".

The circuit used is based on multivibrator principles (see Fig. 1). Its action is as follows:—

Valve V2 conducts and a negative voltage is applied to the control grid of V1 cutting it off. As C1 charges through VR1 the control grid of V1 becomes less negative, until after a given time, depending on the time constant of C1 and VR1, V1 conducts.


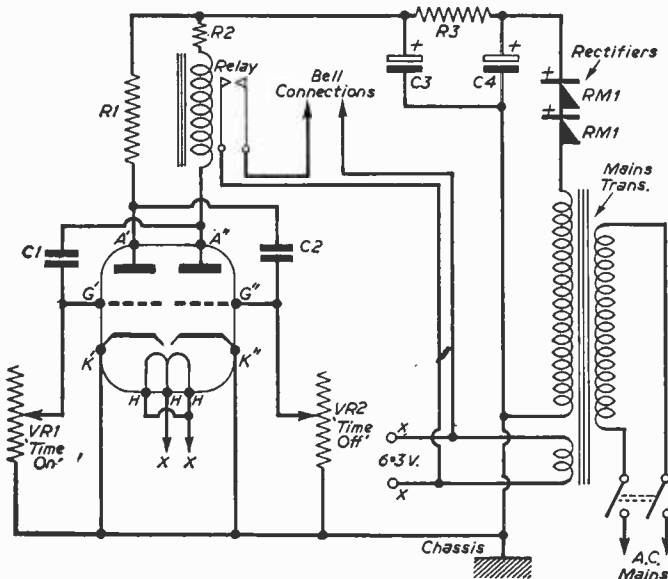
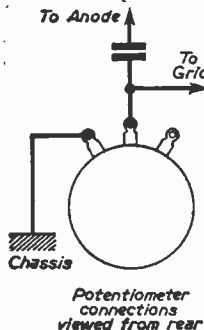


Fig. 1.—Circuit diagram and potentiometer connections.

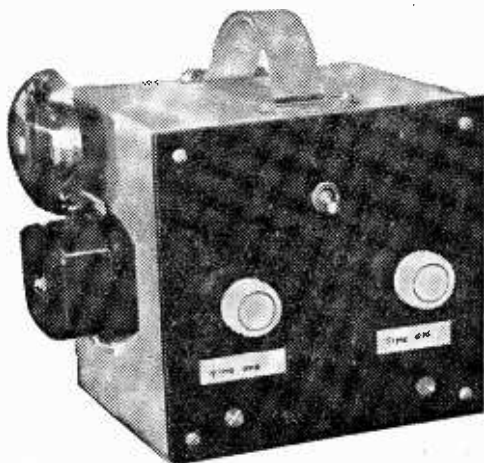

The completed timer.

This action now cuts off V2 because its grid has now a negative voltage applied to it and it will remain in this state until C2 has charged up through VR2 when V2 will conduct once again and the whole operation is repeated.

As will be seen, here an unbalanced arrangement is being used inasmuch as C1 and VR1 are $2\mu\text{F}$ and 100k and C2 and VR2 are $2\mu\text{F}$ and 5M respectively. This is due to the fact that it is unlikely that the "time on" period would ever be required to exceed three or four seconds. Should a long "time on" period be required, the constructor should increase the value of VR1.

Construction

The unit is extremely simple to construct and no special layout of components is necessary. The illustration shows the prototype both in and out of the case, giving the constructor a good idea of the lines to follow. The dimensions of the unit are approximately $5\frac{1}{2}\text{in.} \times 5\frac{1}{2}\text{in.} \times 5\frac{1}{2}\text{in.}$, making it very compact. The only controls are on the front panel and consist of the mains "on-off" switch, and the "time on" and "time off" regulating potentiometers. Calibration scales and pointer knobs should be used and calibration carried out with the aid of a stop-clock. It should be appreciated that if the potentiometer marked "time on" is turned to absolute minimum, then the bell will ring continuously, and likewise if the "time off" potentiometer is turned to absolute minimum, the unit will not operate.


The valve used in the unit is an ECC81 double triode which has a B9A base. The connections are shown in Fig. 2. The relay used in the prototype has a resistance of $1,000\Omega$. The rest of the anode load for V2 is made up to $10\text{k}\Omega$ by

HOME RADIO OF MITCHAM

(Dept. P), 187 LONDON ROAD, MITCHAM, SURREY. MIT 3282

Shop Hours : 9 a.m.—6.30 p.m. Wednesday 9 a.m.—1 p.m.


NEW ARMSTRONG CHASSIS AF208

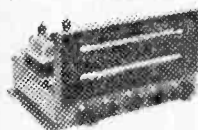

Medium wave plus full FM/VHF. 7 valves and 5 watts output. Separate treble boost and bass boost controls. There is no similar chassis on the market today to equal the AF208. Full instructions, circuit, etc., supplied with each set. PRICE 22 gns., carriage 2/6. S.A.E. for leaflet.

equal the AF208. Full instructions, circuit, etc., supplied with each set. PRICE 22 gns., carriage 2/6. S.A.E. for leaflet.

"GLOBE KING" SHORTWAVE KITS

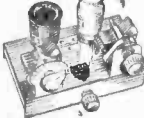

Reception from every country in the world on this wonderful little one-valve short-wave set. Easy to assemble and amazing results. High grade quality components. Start


this instructive and fascinating hobby today and explore the world on short waves. Kit of parts including three matched coils £3.19.6, post 1/-. S.A.E. for leaflet.

NEW GOODMAN'S LOUDSPEAKERS



Model AXIOM 110, £5.0.0.
Model AXIOM 112, £8.10.0.
Send S.A.E. for leaflet.

JASON FM/VHF TUNER

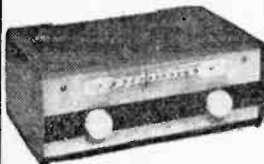

Enjoy crystal clear Hi-Fi radio reception with an F.M. tuner and the best one is without doubt the JASON FMT2. Full constructional data with detailed price list 2/9, post paid. Easy to assemble with punched chassis and pre-aligned coils. Set of parts costs £8 (power pack parts, 28/- extra).

HAVE YOU HAD OUR CATALOGUE?

This is essential to all home constructors, engineers, etc. 128 pages listing over 4000 items and lavishly illustrated. This is EXCLUSIVE to Home Radio and cannot be bought elsewhere. PRICE 2/-, plus 9d. post.

"DESIGNS FOR AUDIO AMPLIFIERS"

This latest Mullard book from stock, price 8/6, post 1/-. We also carry all parts in stock for these designs including punched chassis, ganged controls, switches, etc.

"INSTANT" TAPE ERASER


Enables a complete reel of tape to be erased in a few seconds. Eliminates background noise and leaves tape as new. Will also deflux heads. S.A.E. for leaflet. PRICE £1.7.6, post 1/-

AG2009


PHILIPS RECORD PLAYER UNIT

Transcription

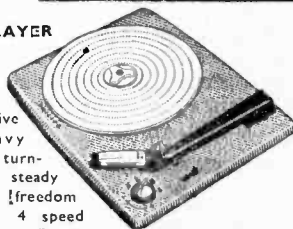quality at a very competitive price. Heavy machined turntable ensures steady running and freedom from wow. 4 speed with variation. Hi-Fi crystal pick-up. PRICE £10.10.0, plus 2/- post. Stereo plug-in head, 30/- extra.



LINEAR L3/3 STEREO

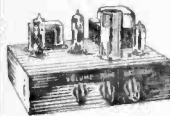


Full two channel STEREO amplifier. 3 watts each channel. Response 50 to 15,000 cycles. Matched for 3 ohms. 200/250 volts A.C. Illustrated leaflet on request with S.A.E. PRICE 7 gns., plus 2/6 post.

HI-FI EQUIPMENT

We have a range of sensible Hi-Fi equipment on demonstration in our showroom. Both ready built systems and in kit form. Amplifiers, tuners, gram units, speakers, etc. Send s.a.e. for our list of Hi-Fi systems.

MULLARD '3-3' and '510' AMPLIFIERS

The famous MULLARD '3-3' and '510' amplifiers are still the most popular home constructor Hi-Fi designs available. We can offer both these superb equipments in kit form with printed circuit ensuring guaranteed results every time. Easily adapted for stereo. Price list of parts free on receipt of S.A.E. Constructional data and drawings 1/6 for each amplifier. Call and inspect and hear these two excellent amplifiers.

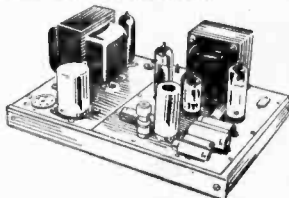

"PERSONAL TWO" PORTABLE




2 valve dry battery personal portable. With rod aerial and ideal for bedroom, holidays, etc. Smart metal case and easy to build from data sheets price 2/-, post paid. Parts for set cost 41/-. Price list on request with s.a.e.

ELECTROVOICE TRANSFORMERS

We stock most of these quality mains and output transformers. All fully shrouded, conservatively rated, and tested to highest standards. A few examples:

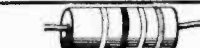104F 250-0-250 at 65mA 6.3v at 1A 6.3v at 1A 28/-
105A 350-0-350 at 150mA 6.3v at 5A 6.3v at 5A 46/-
195 300-0-300 at 120mA 6.3v at 4A 6.3v at 2A 45/-
117/8 for EL84 or 6V6. 3, 7, and 15 ohms. 21/-
117A EL84 or 6V6 push-pull. 21/6
D68 as specified for Five-Ten. 37/6
Please Add 2/- part post.



Miniature high grade insulated resistors 10% tolerance in all preferred values from 10 ohms to 10 megohms. Type R5, 1/2 watt (1/2 watt max.), 4d. each. Type R6, 1/2 watt (1 watt max.), 6d. each. Type R7, 1 watt (2 watt max.), 9d. each.

LINEAR BATTERY CHARGERS




For A.C. mains and all fitted with ammeter. Strongly-made and guaranteed for 12 months. Send s.a.e. for illustrated leaflet. MODEL CL1, 6 volt at 1 Amp, 35/9. MODEL CL2, 6 or 12-volt at 1 1/2 Amps, 49/11. MODEL CL3, 6- or 12-volt at 3 Amps, 75/-. MODEL CL5, 6- or 12-volt at 5 Amps, 99/6. Add 2/- packing and postage.

SOLDERING IRONS



ES41. Tyana medium instrument iron. 16/9. ES22. Remploy instrument iron (illus.), £1.2.6. ES30. Solon 25-watt instrument iron, £1.4.0. ES7. Adcola 25-watt instrument iron, £1.13.6. ES16. Litesold for very fine work. 10 watts. £1.1.6. Please state voltage and add 9d. post.

SW TUNING CONDENSERS

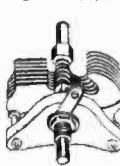

Wavemaster High Grade tuning condensers with brass vanes and ceramic insulation. Single hole fixing and individually boxed. 15pf, 4/3. 25pf, 4/6. 40 pf, 4/9. 50 pf, 5/- 60pf 5/3. 75pf, 5/6-. 100pf, 5/9. 160pf, 6/- 200 pf, 7/6. Add 9d, packing and post.

TAPE DECKS

We now have reasonable stocks of all the popular tape decks, including B.S.R. Monardeck, Collaro Studio deck, Collaro Mk. IV transcriber, Truvox Mk. IV, Brenell Mk. V etc., etc.

RECORDING TAPES

STANDARD. 5in., 15/6. 5 1/2in., 19/6. 7in., 25/-. LONG PLAY. 3in., 6/6. 5in., 19/6. 5 1/2in., 25/-. 7in., 32/6. All brand new and guaranteed. Send for list. Add 1/- postage to order.

SHORT WAVE RECEIVERS

WE ARE MAIN STOCKISTS FOR EDDYSTONE COMMUNICATIONS RECEIVERS AND SHORT WAVE COMPONENTS. SHIPPING ARRANGED TO ANY PART OF THE WORLD.



**Solve
that
Circuit
trouble!**

PIFCO
Radiometer


Not only circuit tests but everything electrical can be tested with this handy compact meter. Tests H.T. & L.T., Valves, components, electrical appliances and car lighting systems, etc. May be used on A.C. & D.C. mains.

See the Radiometer at your dealer or write for illustrated leaflet to —

PIFCO LTD.
WATLING STREET · MANCHESTER · 4.

only
32/6
complete

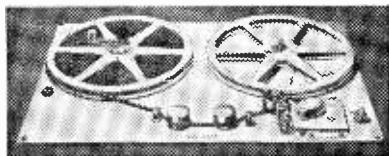START TAPE RECORDING WITH “ASPDEN” Tape Deck and Amplifier Kits



TAPE DECKS. 2-speed, twin track, easy to assemble kits with finest motor. Ferroxcube heads and full instructions.
Reduced Prices:—

Model 582 for 5in. spools, kit £7.10.0.

Model 782 for 7in. spools, kit £8.10.0.

Either model assembled and tested, 30/- extra.

AMPLIFIER kit, 2½ watt, record/replay, 2 recording positions, neon indicator, etc., £5.18.0. Power Pack kit for above, £2.18.6 (both without valves). Carr. and packing extra.


Mr. D. B. A., of Sheffield, writes:
“I have been very pleased with the performance obtained, several of my friends being agreeably surprised by the quality of the reproduction from equipment at such a low price.”

Send STAMP for full particulars to:—

W. S. ASPDEN Stanley Works, Clevedon Road,
Blackpool, Lancs.

Modernise Your Radiogram with an

Armstrong Chassis

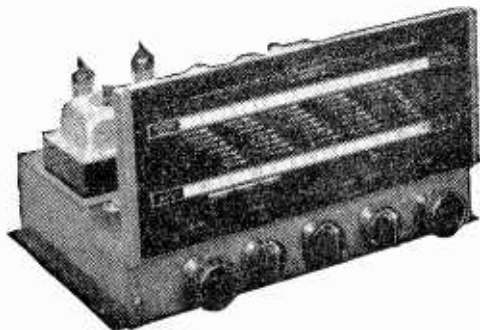

AF 208 (illustrated)

22 GNS.

5 watts output ● Full VHF band (87-108 mc/s) and medium wave ● Switched inputs for different crystal pick-ups ● Inputs for tape record and playback ● Separate bass and treble controls ● Dimensions (as for Stereo 44) 12in. x 8in. x 7in. high.

STEREO 44

27 GNS.

8 watts output, 4 each channel ● Full VHF band and medium wave ● Stereo and monaural inputs for all crystal pick-ups, tape record and playback ● Separate bass and treble controls ● Mullard EL84 output valves ● Dual volume control for stereo balance.

It is not at all difficult to fit a new chassis into an old radiogram or even to build a completely new radiogram into the cabinet of your choice. Why bother? Well, it's less expensive than all but the cheapest commercial radiograms and you get incomparably better quality into the bargain. Aren't those two splendid reasons? It's cheaper AND it's better.

The name **ARMSTRONG** is the registered trade mark of **ARMSTRONG WIRELESS & TELEVISION Co. Ltd.** WALTERS ROAD, LONDON, N.7 Tel.: NOR 3213

Post this coupon or write for descriptive literature or call at our Holloway Showroom for full, unhurried demonstration and professional advice on your installation. Open 9-6 weekdays and 9-5 Saturdays.

NAME

ADDRESS

PAC

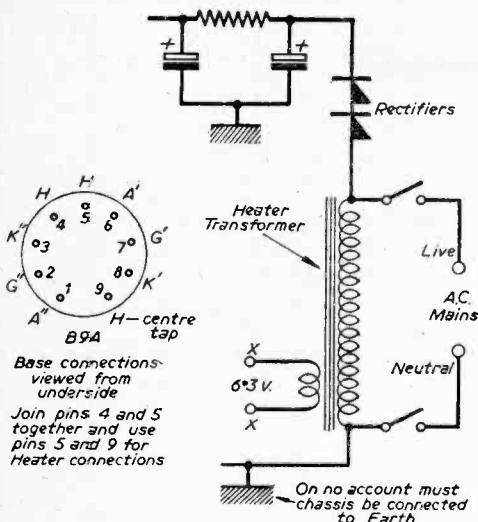


Fig. 2 (Left).—Valve base wiring.

Fig. 3 (Right).—Power pack circuit using the mains connected to the chassis.

suitable resistors. However, a 10k relay operating on a current of up to 10mA will be suitable. These are readily obtainable at most "surplus" shops, and are very cheap. The bell was obtained from a well-known store for a few shillings. This is

driven from the power pack transformer using the 6.3V heater winding. Rectification is by means of two RM1 metal rectifiers in series. These can be obtained cheaply, though any metal rectifier rated 240V at 20mA upwards would be suitable. The circuit diagram shows the mains transformer used as having a separate H.T. winding. This is desirable, as it isolates the mains from the chassis. However, if the constructor happens to have only a heater transformer available, and decides to use this, he must make sure that the fixing screws for the chassis which will be inserted through the front panel are suitably isolated by applying a sealing compound over the screw heads.

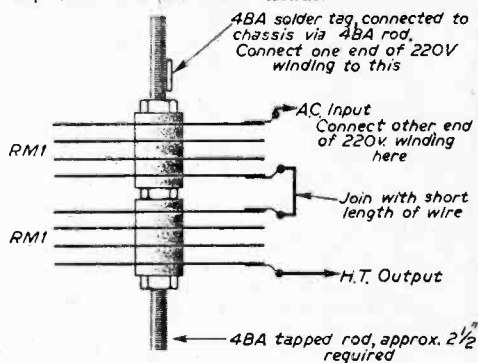


Fig. 5.—Mounting the two metal rectifiers.

Fig. 3 shows the method of connection when using a mains transformer with a heater winding only.

The box should be made of wood, and the front panel of Paxolin or similar insulating material.

Layout

As stated earlier no special layout of components is necessary, but it is felt that the less experienced constructor may prefer to work from a definite layout. Fig. 4 shows the one used in the prototype; comprehensive drilling details are not given because the components used by the constructor may be of a different mounting style from those used by the writer. If two RM1s are used for rectification, they should be mounted vertically, bolted together and fixed to chassis with a length of 4BA rod, as shown in Fig. 5. If an ex-government relay is used, they usually have two mounting studs at their base. Suitable brackets can be attached to these which are then bolted to the chassis. The smoothing capacitor (16-16 μ F) and smoothing resistor R3 along with R1 and R2 (if used) are mounted below the chassis. The wiring for the bell passes through a small hole

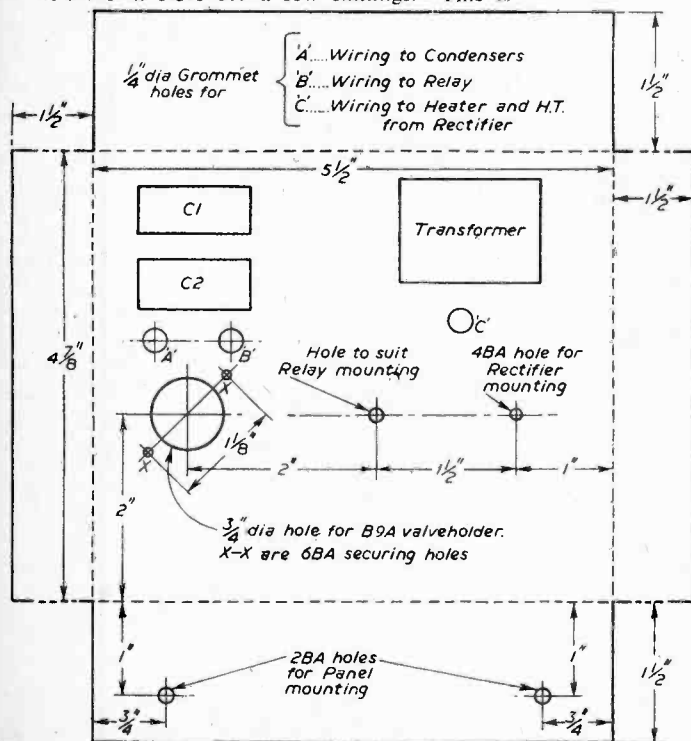


Fig. 4.—Chassis drilling details.

COMPONENTS LIST

C1, C2— $2\mu\text{F}$ 350VW.
 C3, C4— $16 + 16\mu\text{F}$ 350VW, electrolytic.
 R1—10k, 1W.
 R2—Dependent on the relay resistance. See text.
 R3—2.2k, 1W.
 VR1—100k linear potentiometer.
 VR2—5M linear potentiometer.
 Valve: ECC81 or equivalent.
 Valve base B9A.
 Metal rectifiers (RM1) (2).
 Mains transformer, Primary to suit mains voltage.
 220V at 20mA. } Secondaries.
 6.3V at 1A.
 Electric bell 6-8V.
 Relay up to 10k coil resistance.
 Mains switch toggle type, double pole, on/off.

drilled in the side of the case just underneath the bell. This should be of sufficient length to allow withdrawal of the chassis from the case. Panel dimensions and drilling details are shown in Fig. 6.

The case should be constructed of five pieces of $\frac{1}{4}$ in. board, the dimensions as follows:—

Top and bottom $6\frac{1}{2}$ in. \times 5in.
 Sides $5\frac{1}{2}$ in. \times 5in.
 Back $6\frac{1}{2}$ in. \times $6\frac{1}{2}$ in.

These should be panel-pinned and glued. Brackets for the front panel fixing should be made out of $\frac{1}{4}$ in. \times $\frac{1}{4}$ in. brass or steel, 1in. long, with a $\frac{1}{4}$ in. right-angle bend. Centre holes should be drilled and tapped 4B.A. and fixed in the four corners of

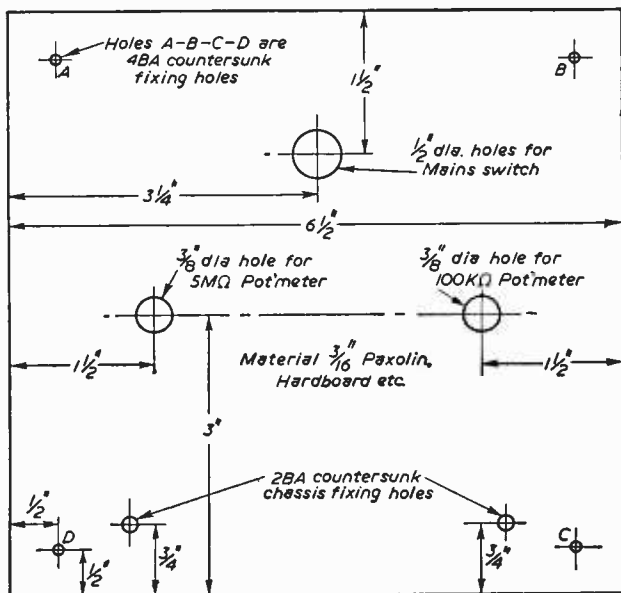


Fig. 6.—Panel drilling details.

the case, using countersunk screws. The screws fixing the brackets to the case should be as short as possible, otherwise they will foul the front panel screws. Three $\frac{1}{4}$ in. holes should run across the centre line of the back to allow for ventilation, not forgetting a further hole near the transformer for the mains lead.

The case can then be suitably polished, and a handle attached, to give a professional looking finish to the job.

CHOOSING DETECTOR CIRCUITS

(Continued from page 1053)

in broadcast receivers. Although a D.C. voltage is present at the cathode of the detector, it is positive and becomes more positive with increase of signal strength; it is therefore of the wrong polarity for AGC purposes. If however, an additional resistor is placed in the anode circuit as shown in Fig. 7, it is possible to obtain an R.F. voltage from the detector anode with the advantage that it is slightly amplified. This amplified R.F. voltage is then detected by the diode V2 so that a negative voltage is obtained for AGC purposes. Whilst it would be possible to place the diode (V2) circuit across the tuned input to the detector, the previous circuit would then be loaded and no AGC amplification would be obtained. If no delay is required the diode cathode may be earthed, but R8 and R9 may be included to give the desired delay. The value of R8 is usually several megohms.

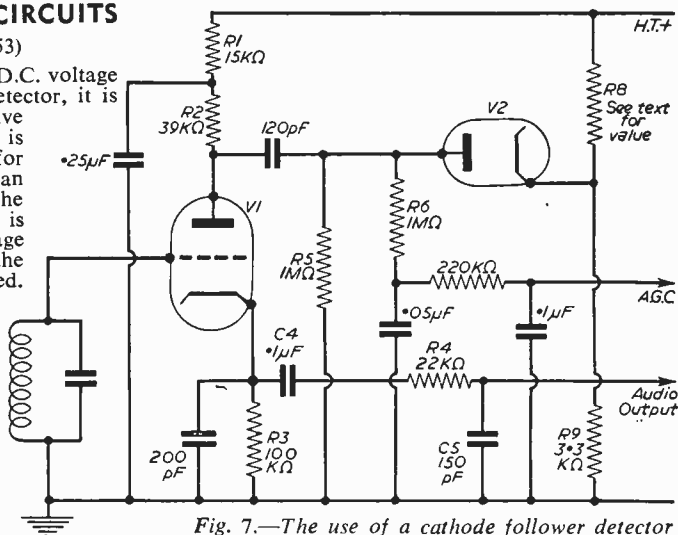


Fig. 7.—The use of a cathode follower detector to amplify AGC. An EAC91 diode-triode is convenient for V1 and V2.

TO BUILD YOURSELF

ALL PARTS AVAILABLE SEPARATELY

**WE ARE THE EXPERTS IN THIS FIELD
AND CARRY THE MOST COMPREHENSIVE
STOCKS IN THE COUNTRY**







| | All required components at special inclusive price | P. & P. | Instruction Book and itemised price list available separately |
|-------------------------------------------------------------------------|-------------------------------------------------------------------|---------------|------------------------------------------------------------------------------|
| (1) New Look "RAMBLER" all dry superhet portable | £7 7 0 | 2/6 | 1/6 |
| (2) "RAMBLER" Mains Unit (suitable for most portables) | £2 7 6 | 1/6 | 9d. |
| (3) "ECONOMY FOUR" T.R.F. Mains Receiver | £5 10 0 | 2/6 | 1/6 |
| (4) "FAMILY FOUR" (our new T.R.F. Receiver) | £3 19 6 | 2/6 | 1/6 |
| (5) "SUPERIOR FOUR" (four valve Mains Receiver) | £5 15 0 | 2/6 | 1/6 |
| (6) Standard JASON F.M. Tuner | £6 15 0 | 2/6 | 2/- |
| (7) Fringe area JASON F.M. Tuner | £7 15 0 | 2/6 | 2/- |
| (8) JASON "MERCURY" Switch tuned F.M. feeder | £9 19 6 | 2/6 | 2/- |
| (9) OSRAM 912 Printed circuit F.M. Tuner | £8 8 0 | 2/6 | 2/6 |
| (10) JASON "ARGONAUT" A.M./F.M. Chassis | £15 5 0 | 2/6 | 2/- |
| (11) JASON "ARGONAUT" A.M./F.M. Tuner | £13 19 6 | 3/6 | 2/- |
| (12) F.M. Power Pack (suitable for most Tuners) | £1 17 6 | 1/6 | 1/- |
| (13) R.C. 3/4 watt amplifier (with Bass, Middle and Treble controls) | £4 5 0 | 2/6 | 1/- |
| (14) 2-amp. Battery Charger | £1 16 6 | 2/6 | 3d. |
| (15) R.C. Transistor/Crystal Receiver (phone extra) | £1 1 0 | 1/3 | 3d. |
| (16) R.C. Super Transistor/Crystal Receiver (Ferrite Rod) (phone extra) | £1 7 6 | 1/3 | 3d. |
| (17) R.E.P. 1-valve Battery Receiver | £2 2 0 | 2/- | 9d. |
| (18) "CRY-BABY" ALARM (Baby Alarm) | £3 12 6 | 2/6 | 1/- |
| (19) MULLARD 510 Amplifier (printed circuit) Ultra Linear version | £9 9 0 | 3/6 | 1/6 |
| (20) TELETRON "TRANSIDYNE" Transistor Portable | £11 19 6 | 2/6 | 1/- |
| (21) "DE-LUXE" Printed Circuit Superhet | £7 19 6 | 3/6 | 1/6 |
| (22) JASON J.T.V.2 Tuner | £13 19 6 | 3/6 | 2/6 |
| (23) RADIO JACK | 19 6 | 1/6 | 6d. |
| (24) MULLARD TYPE "C" Tape pre-amp | £12 9 6 | 3/6 | 2/6 |
| (25) JASON J.3-3 Stereo pre-amp | £15 17 0 | 2/6 | 2/6 |
| (26) JASON J.4-4 Stereo pre-amp | £22 14 0 | 2/6 | 3/- |
| (27) NEW JASON F.M. TUNER with built-in power supplies and cabinet | £8 19 6 | 3/6 | 2/6 |
| (28) NEW JASON FRINGE AREA F.M. TUNER as above | £10 19 6 | 3/6 | 2/6 |
| (29) PULLIN Series 90 TEST METER | £5 19 6 | 2/6 | 1/6 |
| (30) R.C. Super Personal Portable, 1 valve (phone extra) | £1 15 0 | 2/6 | 2/- |
| (31) R.C. Super Personal Portable, 2 valve (phone extra) | £2 1 0 | 2/6 | 2/- |
| (32) R.C. Transette two Transistor Personal Portable | £3 9 6 | 2/- | 2/- |
| (33) JASON EVEREST 6 Transistor 2-wave Portable | £13 19 9 | 3/6 | 3/6 |
| (34) JASON EVEREST 7 Transistor 2-wave Portable | £15 18 9 | 3/6 | 3/6 |
| (35) CLYNE Cathode Ray Oscilloscope | £12 19 6 | 5/- | 10/- |
| (36) Compact Multi-range Test Meter | £2 19 6 | 1/6 | 1/6 |
| (37) Car Radio. Printed Circuit. 5-valve Superhet | £12 19 6 | 3/6 | 3/6 |
| (38) JASON Audio Generator AG10 | £14 5 0 | 3/6 | 2/- |
| (39) JASON Oscilloscope OG10 | £22 10 0 | 5/- | 3/6 |
| (40) Super SHORTWAVE RADIO one valve | £1 15 0 | 2/- | 2/- |
| (41) "WAVEMASTER" 7 Transistor Luxury Portable | £10 19 6 | 3/6 | 2/6 |

Instruction Books which contain full description, easy-to-follow practical wiring diagrams, theoretical diagrams, itemised price lists, etc., are free of charge with all parcels but may be purchased as shown above.

The following are also available, assembled and tested:—

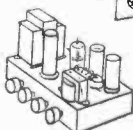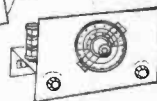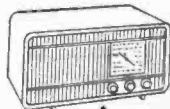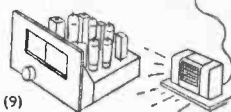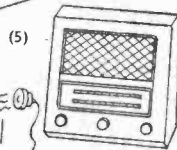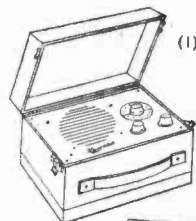(2) "RAMBLER" Mains Unit, £3/5/0, (12) F.M. Power Pack, 52/6; (13) R.C. 3/4 watt Amplifier £5/5/0; (14) 2-amp Battery charger, 45/-; (18) "CRY-BABY" Alarm, 89/6; (19) Mullard 510, £12/12/0.

NOTE: (2) The "RAMBLER" Mains Unit is suitable for use with MOST all-dry portables.



NEW BRANCH !!

CITY BRANCH NOW OPEN AT **99 CHEAPSIDE, E.C.2**

Telephone: MONarch 6860

Situated midway between Bank and St. Paul's Stations and no more than one minute from either. Open: Monday to Friday 9 a.m.—6 p.m. Saturday 1 p.m.

STILL LEADING THE FIELD!

CLYNE RADIO LTD.

THE COMPONENT SPECIALISTS



162 HOLLOWAY ROAD, LONDON, N.7
18 TOTTENHAM COURT ROAD, W.1
99 CHEAPSIDE, LONDON E.C.2

NORTH 6295/6/7
MUSEum 5929/0095
MONarch 6860


All post orders and correspondence to 162 HOLLOWAY ROAD, LONDON, N7.

OPEN: Tottenham Court Rd., and Cheapside: 9 a.m. to 6 p.m. Mon. to Fri., Sat. 1 p.m. Holloway Rd.: 9 a.m. to 6 p.m. daily. Thurs. 1 p.m., Sat. 5.30 p.m. Our Advantageous H.P. and Credit Sale Terms are available on any single item over £5. Your enquiries invited. Please print your name and address !!

Gladstone Radio

PUSH-PULL AMPLIFIER £5.10.0 (3/6 P. & P.)

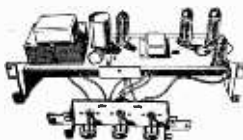Brand new by famous manufacturer. 200-240 A.C. mains. Bass, treble and vol. controls flying panel. With valves EZ80, ECC83 and 2-EL84 giving full 8 w. Chassis 12 x 3 1/2 x 3 1/2 in. With o.p. trans. for 2-3 ohm speaker.



COSSOR AMPLIFIER KIT TYPE 562K £5.2.6 (3/- P. & P.)

With valves EZ80, EF86 and EL84. 2 speakers (10 x 6 x 4 in. h.f.). Full instructions; printed circuit; A.C. mains; original carton.

BUILD THIS BATTERY OPERATED TRANSISTOR RECORD PLAYER FOR £6.10.0 (3/6 P. & P.)

Plus cost of speaker 17/- extra.

Built and tested Cossor printed circuit 4-transistor amplifier. Cabinet; baffle; motor board, cut for motor; Garrard 45 r.p.m. battery player type BA1; speed control; knob; plugs, wiring instructions. Speaker extra. Cabinet size 11 x 9 1/2 in.; less than 8 1/2 in. batteries. Requires two Ever Ready AD28 batts. State colour—red/cream or blue/cream.



BUILDING THE 6K7 SUPERHET?

(Page 885 February Issue.)

Send for price list, e.g., Two-gang 500 pF with reduction drive incorporated in spindle 5/-; five valves 6K7 for 12/6.



THE NEW TAYLOR MULTI-METER MODEL 127A £10 (Carriage Paid.)

20,000 ohms per volt. Pocket size. Two colour scale with 3 1/2 in. arc. Only 5 1/2 x 3 1/2 x 1 1/2 in. Write for free leaflet. 12 voltage ranges and 6 resistance ranges. Batteries included.

Small extension speaker cabinet, 12 x 6 in. high x 1 1/2 in. Ideal for mantelpiece. Med. oak finish. New. Will also take clock movement. ONLY 5/- (post 1/6).



For the last 50 I.T.A. Converters of this type (Brand New and Fully Guaranteed) we will accept the "Below Cost" figure of ONLY 60/- (3/- P. & P.) Reduced from 24/6.

Two valves ECC81—grey hammer finish—Switch positions OFF, I.T.A., BBC. Own Power supply. BUY IT NOW.



60/- (3/- P. & P.)

FOR ADDRESSES SEE THE OTHER ADVERTISEMENT
FOR GLADSTONE RADIO ON PAGE 1063

UNIVERSAL AVOMETER MODEL D

Just released by the Air Ministry, these famous AC/DC Test Meters are a "ship" for anyone requiring a First Grade General Purpose Instrument. Normal Avometer size, 7 1/2 in. x 6 1/2 in. x 3 1/2 in., with carrying strap, indication being given on a 5 in. Mirror Scale. Thoroughly overhauled and complete with batteries and instructions. Provides 34 ranges of current, voltage and resistance, as follows:

| D.C. Voltage | A.C. Voltage | D.C. Current | A.C. Current |
|--------------|--------------|--------------|--------------|
| 150 mv. | 7.5 v. | 15 ma. | 75 ma. |
| 300 mv. | 15 v. | 30 ma. | 150 ma. |
| 1.5 v. | 75 v. | 150 ma. | 750 ma. |
| 3 v. | 150 v. | 300 ma. | 1.5 amp. |
| 15 v. | 300 v. | 1.5 amp. | 7.5 amps. |
| 30 v. | 600 v. | 3 amps. | 15 amps. |
| 150 v. | 750 v. | 15 amps. | |
| 300 v. | 1,500 v. | 30 amps. | |
| 750 v. | | | Resistance |
| 1,500 v. | | | 1,000 ohms |
| | | | 10,000 ohms. |

ONLY £9.19.6 (carriage 3/6d).

25,000 OHMS PER VOLT TEST METER. Made by TRIP-LITT, the famous American meter manufacturers. Full bench size 7 1/2 in. x 6 1/2 in. x 6 1/2 in., and incorporates a unique tilting bakelite container size 5 1/2 in. x 3 1/2 in., which has 2 meters, a 25,000 ohms per volt moving coil for D.C. Measurements, and a First Grade moving iron for A.C. Reads Resistances up to 40 MΩ ohms, A.C. and D.C. volts to 1,000 V. Current to 250 mA., and also has 0-50 Microamps range. Facilities for measuring Condenser Capacity and Audio Output. Completely portable, with protective face cover. Complete with Test Leads, Instruction Book, and Batteries. Ex-Ministry of Supply, New Condition and thoroughly checked and overhauled. ONLY £10.10.0 (post, etc., 3/6).

CARRYING CASES. Solid leather. Brand New. Internal measurements 8 1/2 in. x 8 1/2 in. x 4 1/2 in. Fitted lock and key, and shoulder strap. Ideal for Test Instruments, Camera and Accessories, etc. ONLY 35/- (postage 2/-).

POWER UNITS TYPE 234. Designed for R.A.F. R1132 Receiver. Primary 200/250 v. 50 cycles. Outputs of 250 v. 100 mA., and 6.3 v. 4 amps. Fitted double smoothing. For normal rack mounting (or bench use) having grey front panel size 19 in. x 7 in. BRAND NEW. ONLY 59/6 (carriage 7/6).

POWER PACK FOR R1155 RECEIVERS. Fitted with Output Stage and 8 in. P.M. Speaker. Operates receiver immediately without any alteration. In black crackle case size 11 in. x 10 in. x 6 in. ONLY £8.10.0 (carriage 5/-).

CANADIAN MOVING COIL PHONES. Low resistance, fitted noise excluding chamolais ear muffs, and leather covered head band. Lead terminates to jack plug. Supremely comfortable. BRAND NEW. ONLY 19/6 (post 1/6).

INTERCOM. TELEPHONE SET. Two pairs of Brand New Headphones connected to Breast Microphones, with leads, etc., in fitted carrying cases. Supplied with 4 volt battery, 10 yards twin wire, and full instructions for connecting to make super intercom. ONLY 27/6 (post 3/6). Extra Wire 3d. per yard.

RCA 8 in. P.M. SPEAKER, in heavy black crackle metal case. Can be used as normal 3 ohms extension. Size 11 in. x 10 1/2 in. x 6 in. NEW IN MAKER'S CARTONS. ONLY 45/- (post 3/6).

"Q FIVER" COMMAND RECEIVER. The famous American BC453, covering 190-550 kc/s, I.F.s being 85 kc/s. Complete with all 6 valves and circuit. NEW IN MAKER'S CARTONS. ONLY 89/6 (post 3/6).

R1155 SUPER SLOW-MOTION TUNING ASSEMBLY. As used on all late model 1155s. Easily fitted to "A" sets, etc. BRAND NEW. ONLY 12/6.

EHT TRANSFORMERS. 5.5 kV (Rect.) with 2 v. 1 a., 79/6. 7 kV. (Rect.) with 2 v. 1 a., 89/6. 2.5 kV. (Rect.) with 2-2 v. 1.1 a., 2-0-2 v. 2 a. (for VCR97 tube, etc.). 47/6 (postage 2/- per trans.).

POCKET VOLTMETERS. Read 0-15 volts and 0-300 volts A.C. or D.C. BRAND NEW and UNUSED. ONLY 18/6.

10/- CONSTRUCTORS PARCEL. 10 yards each of 6 colours wiring wire, solder, 24 each assorted Resistors and Condensers.

RESISTORS. 100 assorted values. NEW, 10/-.

CONDENSERS. 100 assorted mica and silver mica. NEW, 12/6.

SPRAGUE CONDENSERS. Metal cased, wire ends. New .01 mfd. 1,000 volt, and .1 mfd. 500 volt, 7/6 per dozen. Special quotes for quantities.

HARRIS ELECTRONICS

(LONDON) LTD.

138 Gray's Inn Road, London, W.C.1.

(Phone TERMINUS 7937)

Please include carriage costs on All items.
(Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross.)

Becoming an Amateur

No. 7—ADDITIONS TO THE ONE-VALVER

(Continued from page 866 of the February issue)

By J. D. Pearson, G3KOC

WHEN the beginner has built and operated the simple single-valve receiver described in previous issues he will, eventually, require some means of increasing output, thereby making the weaker stations more readable. This can be done in two ways: (a) by the addition of an R.F. stage, preceding the detector valve; or (b) by the addition of an L.F. stage after the detector. In the present context the word "stage" refers to a single valve together with its associated circuitry and components. One could, of course, add both stages at the same time thus converting the one-valver into a three-valve T.R.F. set of the type so common before the war. The beginner is advised, however, to deal with additional stages separately, and to understand fully the design and operation of each before progressing further.

L.F. Amplification

The detector stage is the "heart" of any receiver. For the moment, it will be sufficient if the reader visualises the function of this stage to be the separation of the "intelligence", or modulation, which is "impressed" upon the carrier wave at the transmitter from the carrier wave. The carrier wave, of course, owing to its very high frequency, is inaudible.

In the superhet receiver, which normally uses a simple diode detector, the above process is performed by a separate valve and tuned circuit, the complete unit being known as a Beat Frequency Oscillator, or BFO.

The main point the student should impress upon his memory is that, technically speaking, an unmodulated radio frequency wave is inaudible unless one of the two systems briefly described above is used in the receiver. The "note" he hears when taking down CW (not to be confused with Modulated CW) is supplied by his own receiver. The R.A.E. paper may include a question on the purpose and operation of the BFO.

Coupling Transformers

To return to the simple detector. Assuming we have separated the audio content from the now useless carrier we can amplify the audio to whatever level we wish. For headphone reception a single stage is usually sufficient. Probably the simplest way is transformer coupling using an L.F., or intervalve, transformer. This usually has a turns ratio of 3 : 1 or 5 : 1. The primary is connected in series with the H.T. supply to the detector, whilst the secondary is in series with the bias supply to the grid of the L.F. stage.

Mutual inductance, on which the action of the transformer depends, has not yet been discussed. This is deliberate. The writer firmly believes

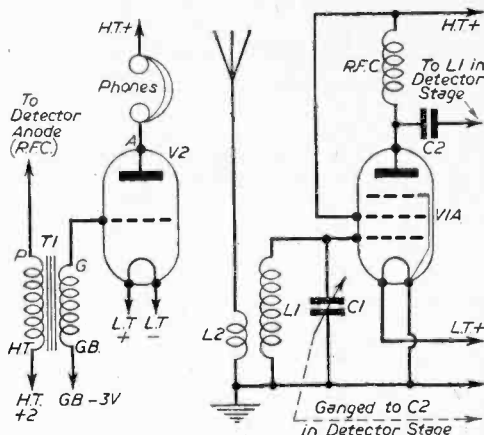


Fig. 1 (Left).—A simple L.F. stage.

Fig. 2 (Right).—Simple R.F. stage.

that the student's mind is much more receptive as to what happens, and why, in the equipment he builds, *after* he has built it than it is before.

The circuit of a suitable L.F. stage for adding on to the simple detector circuit given previously is shown in Fig. 1.

R.F. Amplifier

Sometimes known as "high frequency" amplification, the beginner will find this stage not quite so simple to adjust and operate as an L.F. stage. As the name implies, the method involves amplification of the signal as received on the aerial, and the amplified signal is then passed to the detector for rectification, or demodulation.

An efficient R.F. stage will often bring in stations which previously were inaudible; an L.F. stage cannot do this—it will only amplify that which is already there.

Tuning

The beginner should study as many T.R.F. circuits as possible, noting the difference in inter-stage coupling between detector and L.F. and R.F. and detector. Whilst the former is usually accomplished by the use of high inductance iron-cored transformers or resistance-capacity networks, the latter requires very efficient high-"Q" tuned circuits, which are tuned "in step" with the detector tuned circuits, by way of ganged condensers. The R.F. and detector stages can, of course, be tuned individually using separate controls; this procedure would overcome any tracking errors caused by differences in inductance values when using home-wound coils in both stages. However this also entails sacrificing the facility of "single knob" tuning. The interested beginner may care to try both methods; the only effort entailed is to release grub-screws on the flexible coupler and move the R.F. stage tuning condenser to a more convenient position.

When building and operating experimental circuits of the simple type described, it is advisable to begin with a fairly large chassis; one then has space for subsequent additions and modifications.

The circuit of the R.F. stage is given in Fig. 2 and a suggested layout is shown in Fig. 3.

Circuit Description

When describing straight receivers, on SWL reports, etc., certain abbreviations are used. The letter "V" is used to denote the detector stage; the figures before and after the "V" represent the number of stages of R.F. and L.F. amplification respectively. In the case of receivers not

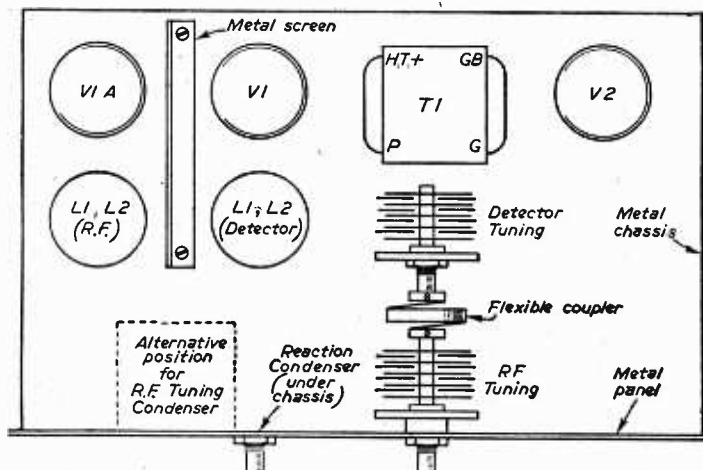


Fig. 3.—A suggested layout.

fitted with any particular stage an "0" is substituted in the group. The simple one-valve receiver for instance, would be written as 0-V-0; whilst the three-stage receiver is covered by the term 1-V-1.

Soldering

Newcomers to the hobby of radio-construction may have doubts about their ability with a soldering-iron. Properly soldered, oxide-free joints are essential in radio work, and are very easy to achieve if the process is understood and the job tackled properly at the outset.

The golden rule is to have the surfaces to be joined, and the iron (electric or otherwise), scrupulously clean. A 25W lightweight soldering iron will handle almost any radio job the constructor may undertake. Resin-cored wire solder only should be used; corrosive fluxes must not be employed.

It is often recommended that a sound mechanical joint be made before soldering is attempted, using long-nosed pliers to secure component wire ends to valvholder tags, etc., but this is a matter for choice after experience has been gained. Remember that wiping a speck of dust from a component tag with the finger can do more harm than good by depositing an invisible layer of moisture or grease.

Tinning the Iron

The copper bit of the iron should be rubbed smooth with a fine file. When the iron has reached working temperature, solder should be applied to various points on the working surface of the bit

and quickly smoothed out with a clean, soft, cotton rag. The iron is now "tinned".

Most components and valvholder wires and tags when purchased new are already tinned, and unless dirt has accumulated or oxidation occurred during storage, soldering will "take" satisfactorily. Assuming that a good mechanical joint has been made, apply the iron to both the wire and the tag together where possible, and allow a second or two for the surfaces to reach iron temperature, or thereabouts. Then apply the solder. If the joint is hot enough, the solder will "run" immediately. Use only enough solder to make a good electrical joint. Remove both iron and solder from the joint, and it should set with a smooth bright surface.

Never carry solder to the joint on the iron, and never place the solder on a cold joint with the iron on top. The resultant joint may look all right but will eventually give trouble owing to a minute layer of cold air having been trapped beneath the hot solder and iron, causing a high resistance, or "dry" joint.

Difficulties

At this stage the student should be devoting his time equally between Short Wave Listening, building a receiver for that purpose and studying theory. He should by this time be fully conversant with the licencing rules and regulations governing the issue of an Amateur Sound Licence (this knowledge can earn up to thirty marks out of a possible hundred, when taking the R.A.E.).

He will also by this time have reached a point in his textbooks at which he finds himself "out of his depth", and it is not always easy to determine just where this occurred. If the student can say precisely at what point he parted company with the author of his textbook, then the problem is halfway to solution. The writer will be pleased to assist readers with problems of this nature, but queries must be addressed to the Editor, and be accompanied by the query coupon from the current issue.

(To be continued)

ADDITIONAL COMPONENTS

T1: L.F. transformer (Ratio 3 or 5:1).

V2: Triode valve (LP2 etc.).

L1, L2, C1: values as for detector stage given in the February issue.

C2: 100pF.

RFC: Radio frequency choke.

V1A: IN5, DF33, SG15 etc.

C.R.T. ISOLATION TRANSFORMERS
TYPE A. V. OR 0.3 V. OR 10.8 V. OR
13.3 V. 12/8. MAINS INPUT.
OUR LATEST SUPERIOR PRODUCT
TYPE A2. HIGH QUALITY. LOW CAPACITANCE.
1015 pF. OPTIONAL BOOST 25%, 50%, 75%, 10/8 EACH. MAINS INPUT.
TYPE B. MAINS INPUT. MULTI OUTPUT 2, 4, 6.3, 7.3, 10 AND 13 VOLTS. BOOST 25% AND 50%. LOW CAPACITANCE 21/-.

TRIMMERS, Ceramic. 30, 50, 70 p.f., 9d.; 100 p.f., 1/3d.; 1/3, 250 p.f., 1/8. 500 p.f., 75d. 1/9.
 RESISTORS, Preferred values, 10 ohms to 10 meg., 1/4 w., 4d.; 1/2 w., 4d.; 1 w., 6d.; 1 1/2 w., 8d.; 2 w., 1/1-
HIGH STABILITY. 1/2 w., 1/2-. Preferred values, 100 ohm to 10 meg. Ditto, 5%, 100 ohm to 5 meg. 1/4, 9d.
 5 watt WIRE-WOUND RESISTORS 1/3
 10 watt 25 ohms-10,000 ohms 2/-
 15 watt 15,000 ohms-50,000 ohms, 5 w., 1/8; 10 w., 2/3.

PLASTIC RECORDING TAPE

Long Play 7in. reel, 1,700ft. ... 35/-
 15in. reel, 1,300ft. ... 28/-
 4in. reel, 850ft. ... 21/-
 3in. reel, 225ft. ... 7/8

Standard 7in. Reel, 1,200ft. ... 24/-
 5in. reel, 600ft. ... 15/-


"Instant" Bulk Tape Eraser and Head De-buzzer. 200/250 v. A.C. 27/6. Leaflet, S.A.E.

O.P. TRANSFORMERS. Heavy Duty 50 mA, 4/6 Multiratio push-pull, 7/8. Miniature, 384, etc., 4/6.
L.F. CHOKES 15/10 1H. 500/50 mA, 5/-; 10 1H. 85 mA, 10/8. 10 H. 150 mA, 14/-.

MAINS TRANSFORMERS 200/250 v. A.C. STANDARD. 250-0-250, 80 mA, 6.3 v. 3.5 a. Tapped 4 v. 4 a. Rectifier 6.3 v. 1 a. 5 v. 2 a. or 4 v. 2 a. ditto, 350-0-350 ... 22/6
 100 mA, 6.3 v. 3.5 a. 1 a. 5 v. 2 a. or 4 v. 2 a. ditto, 350-0-350 ... 10/6
MINIATURE. 200 v. 20 mA, 6.3 v. 1 a. ... 15/6
MIDGET. 220 v. 45 mA, 6.3 v. 2 a. ... 15/6
SMALL. 250-0-250, 100 mA, 6.3 v. 3.5 a. ... 17/6
STD. 250-0-250, 65 mA, 6.3 v. 3.5 a. ... 17/6
HEATER TRANS. 6.3 v. 1 1/2 amp. ... 7/8
 Ditto, tapped sec. 2, 4, 6.3 v., 1 1/2 amp. ... 8/6
 Ditto, sec. 6.3 v. 3 amp. ... 10/6

ALADDIN FORMERS and core, 1in., 8d.; 1in., 10d. 3in. FORMERS 5937/8 and Cans TV1/2. 1in. sq. x 2 1/2in. and 1in. sq. x 1 1/2in., 2/- ea., with cores.
TYANA. Midget soldering iron, 230 v. 25 w., 10/8.
REMPLOY Instrument Iron. 230 v. 25 w., 17/8.
MAINS DROPPERS. 3in. x 1 1/2in. Adj. Sliders. 0.3 amp., 750 ohms, 4/3. 0.2 amp., 1,000 ohms, 4/3.
LINE CORD. 0.3 amp., 90 ohms per ft., 0.2 amp., 100 ohms per ft., 2-way, 6d. per ft. 3-way, 7d. per ft.
LOUDSPEAKER P.M. 3 OHM. 5in. Rola, 17/8. 5in. Pleasy, 19/8. 6in. x 4in. Rola, 8/-; 6in. Rola, 18/8. 8 x 6in. 21/-, 10 x 6in. 27/8. 10in. Rola, 30/-.
 12in. Tweeter, 25/-; 12in. P.A. 30/-, 8 x 14in. 45/-
STENTORIAN HP1012. 10in. 3 to 15 ohms 10w., 95/-.
 12in. Baker 15 watt 3 ohms or 15 ohms 105/-
12IN BAKER FOAM SUSPENSION. 15 ohms, 28/-
CRYSTAL DIODE. G.P.C. 2/-, GEX34, 4/-
HIGH RESISTANCE PHONES. 4,000 ohms, 16/8 per pair.
MIKE TRANS. 50:1, 3/8 ea.; 100:1, Potted, 10/8.
SWITCH CLEANER. Fluid squirt applicator, 4/3 tin.
TWIN GANG TUNING CONDENSERS. 365 p.p.f. miniature 1in. x 1 1/2in. x 1 1/2in., 10/-, 0.0005 standard with trimmers, 9/-; less trimmers, 8/-; midget, 7/8.
SINGLE. 50 p.p.f. 2/8; 80 p.p.f. 100 p.p.f. 160 p.p.f. 7/-; Solid dielectric 100, 300, 500 p.p.f. 3/8.
SPEAKER FRET. GOLD CLOTH. 17in. x 25in., 5/-; 25in. x 30in., 10/-; Typan 4in. 6 in. wide, 10/-; 10 in. wide, 5/-; 16 in. wide, S.A.E.
 New and Bored Valves 80-day Guarantee.

| | | | | | | | |
|-------|------|-------|------|--------|------|--------|------|
| 145 | 7/8 | 6K90 | 7/8 | 6ABG30 | 8/8 | 6ABG30 | 8/8 |
| 154 | 7/8 | 6L60 | 10/8 | 6B91 | 8/8 | 10/8 | 10/8 |
| 176 | 6/8 | 6N7G | 6/8 | 6BC33 | 8/8 | 6HVR2A | 6/8 |
| 2X2 | 3/8 | 6Q7G | 7/8 | 6HC41 | 8/8 | 6MU14 | 9/8 |
| 384 | 7/8 | 6SA7 | 6/8 | 6BF80 | 10/8 | 6P61 | 3/8 |
| 3V3 | 7/8 | 6SJ7 | 6/8 | 6CC84 | 9/8 | 6PC384 | 8/8 |
| 814 | 7/8 | 6SN7 | 6/8 | 6CF80 | 9/8 | 6PCF80 | 9/8 |
| 574 | 7/8 | 6V6G | 7/8 | 6CI42 | 10/8 | 6POL82 | 11/8 |
| 524 | 9/8 | 6A4 | 7/8 | 6CL82 | 10/8 | 6PEN25 | 6/8 |
| 6AM6 | 5/- | 6X5 | 6/8 | 6EP39 | 5/8 | 6PL82 | 10/8 |
| 618 | 5/8 | 12A7 | 8/- | 6F41 | 8/8 | 6P780 | 7/8 |
| 618B | 7/8 | 12A7 | 8/- | 6F41 | 8/8 | 6P781 | 8/8 |
| 61H6 | 10/8 | 12AX7 | 8/- | 6F80 | 7/8 | 6P782 | 7/8 |
| 6BW6 | 10/8 | 12BH6 | 10/8 | 6F91 | 5/8 | 6SF61 | 3/8 |
| 6D6 | 6/- | 12K7 | 6/8 | 6F92 | 5/8 | 6UB4C1 | 10/8 |
| 6F6G | 7/8 | 12Q7 | 6/8 | 6L33 | 5/8 | 6UB4Z | 10/8 |
| 6G5 | 8/8 | 13A7 | 9/8 | 6L84 | 8/8 | 6UF41 | 9/8 |
| 6J3 | 5/8 | 6Z624 | 7/8 | 6M18 | 9/8 | 6U141 | 9/8 |
| 6J6 | 5/8 | 80 | 10/8 | 6E740 | 7/8 | 6U41 | 8/8 |
| 6J7G | 5/8 | 807 | 5/8 | 6E750 | 7/8 | 6U22 | 8/6 |
| 6K6GT | 6/8 | 854 | 1/8 | 6E751 | 7/8 | 6R105 | 8/6 |
| 6K7G | 6/8 | 8A00 | 1/8 | 6E1148 | 1/8 | 6V1150 | 8/6 |

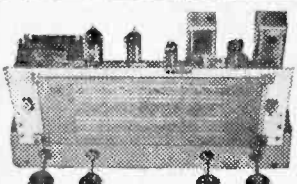

1560 RADIOGRAM CHASSIS
THREE WAVEBANDS FIVE VALVES
 S.W. 16 m.-50 m. LATEST MULTIAID
 M.W. 200 m.-550 m. EC181, EF89, EIC81,
 L.W. 800 m.-2,000 m. EL84, EK80,
 12-month guarantee.
 A.C. 200/250 v. 4-way Switch; Short-Medium-Long-Gang. A.V.C. and Negative feedback
 4.2 watts. Chassis 131 x 2 1/2 x 2 1/2in. Glass clad,
 horizontal or vertical, size 10in. x 4 1/2in.
 Aligned and calibrated. Isolated Chassis.

£9.10.0 Carr & Ins. 4/6.
 TERMS: Dep. £5.5.0 and five monthly of £1.
MATCHED SPEAKERS FOR ABOVE CHASSIS.
 8in., 17/8; 10in., 25/-; 12in., 30/-.

DULCI AM-FM MODEL H3
 6 Valves **£19.17.6** Leaflet, S.A.E.



£6.19.6 Maranch
 World's finest hi-pot auto-charger

TERMS: Dep. £2.10.0 and four monthly of £1.
 Stereo Model UA8 £7.19.6 UAL2 £10.10.0.

BUILD THESE REPRODUCER BARGAINS SINGLE PLAYER KIT
 Ready for immediate assembly

4-speed Collaro "Junior" Unit ... £4 12 6
 Hand-crank case 17 1/2 x 13 1/2 x 7 1/2 in.
 with room to play 12in. records. ... £2 5 0
 Ready-built 3-watt amplifier with
 two valves and loudspeaker ... £2 12 6
 or **£9.15.0** complete kit post free.

COLLARO AUTO-PLAYER KIT
HIGH-FIDELITY AUTOCHARGER
 4-SPEEDS-10 RECORDS
 Studio "Q" pick-up

OUR PRICE £7.19.6 post free.
 Or with cabinet, speaker, and amplifier.
£11.19.6 Carr. 5/6.

STEREO E.M.I. 4-SPEED SINGLE RECORD PLAYER. Acos 73 hi-fi stereo and normal xtal pick-up. Silent motor, heavy turntable. Special Offer **£8.19.6**. Post 3/6.

ALUMINIUM CHASSIS. 18 s.w.g. undrilled. With 4 sides, riveted corners and lattice fixing holes. 2 1/2in. slides, 7 1/2in. 4in.; 6 x 7in. 5/8; 1 1/2 x 7in. 6/8; 1 3/8 x 9in. 8/6; 1 1/2 x 1 1/2in. 5/8; 1 1/2 x 1 1/2in. 12/8; 1 1/2 x 1 1/2 x 3in. 16/6.

TRANSISTORS. GENUINE EDISWAN
 R.F. 4 Mola, 18/-; 2 Mc/s, 15/-; Audio, 10/-.
 Complete data sheets supplied.

CRYSTAL MIKE INSERT by Acos, precision engineered. Size only 1in. x 3/16in. 6/8

HI-GAIN BAND 3 I.T.A. PRE-AMP KIT. Cascade circuit with valve EOC84, Price 29/6. With Power Pack, 49/6. Plans only 6d.

Band 1 BB2 version same prices.

BBC TRANSISTOR RADIO. M. L. wave. Complete kit 32/6, phones 7/8 extra. Dent Aid Earpiece 12/6. Special Lead 2/6. Details 6d.

GARRARD SINGLE PLAYERS
AUDIO PERFORMANCE

Designed to play 16, 33, 45, 78 r.p.m. Records 7in., 10in., 12in. Lightweight Xtal pick-up. GGS plug-in head. Stereo Wired.

MODEL TA MK II £8-10.
MODEL 4 HF £18.
 (Stereo heads £2 extra). Leaflets, S.A.E.

Volume Controls 80 ohm CABLE COAX
 Long spindles. Guaranteed 1 year. Midget. 5K ohms to 2 Meg. 0K Sw. D.P.S.W. 3/-
 Linear or Log Tracks. 4/8
 Air Spaced. 1/- yd.

COAX PLUGS 1/- **LEAD SOCKET** 2/-
PANEL SOCKETS 1/- **OUTLET BOXES** 4/6
BALANCED TWIN FEEDER rd. 6d. 80 or 300 ohms.
DITTO SCREENED per yd. 1/8. 90 ohms only.
WIRE-WOUND POTS. 3 WATT. Pre-set Min. T.V. Type. All values 25 ohms to 25 K., 3/- ea. 30 K., 50 K., 8/-; (Carbon 30 K., to 9 meg. 8/-).
WIRE-WOUND 4 WATT Pots. Long Spindles. Values, 100 ohms to 50 K., 9/6; 100 K., 7/8.
CONDENSERS. New Stock. 0.001 mfd. 7 kV. T.C.C. 5/6 Ditto, 0.001 kV., 9/6 0.1 mfd. 7 kV. 9/6
 27ulgar 60 v. 0.001 to 0.05 mfd., 9d. 0.1 1/-
 0.25 1/8; 0.5/350 v. 1/8; 0.1/350 v. 9d.; 0.1/1000 v. 1/8; 0.01/2,000 v. 1/8; 0.1 mfd., 2,000 volts. 5/-
CERAMIC COND. 500 v. 0.3 pF. to 0.01 mfd. 9d.
SILVER MICA CONDENSERS. 100 v. 5 pF. to 500 pF. 1/-; 600 pF. to 3,000 pF., 1/3. Close tolerance (± 1 pF.) 1.5 pF. to 47 pF., 1/8. Ditto 1/50 pF. to 815 pF., 1/8; 1,000 pF. to 5,000 pF., 2/-.

I.F. TRANSFORMERS 7/6 pair.
 465 Kcs/Sig Tuning Miniature Can. 2 1/2in. x 1 1/2in. High Q and good bandwidth.
 By Pye Radio. Data sheet supplied.
 Wearite M800 I.F. 465 Kcs. 12/8 per pair.
 Wearite 500 I.F. 465 Kcs. 12/8 per pair.

NEW ELECTROLYTICS. FAMOUS MAKES.
TUBULAR TUBULAR CAN TYPES

| | | | | | | |
|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----|-------------|-----|-------------------|------|------|
| 1/350v. | 2/- | 64/350v. | 5/6 | 8/500v. | 1/- | 3/- |
| 2/450v. | 2/3 | 100/25v. | 3/- | 16/500v. | 4/- | 4/- |
| 4/450v. | 2/3 | 250/25v. | 3/- | 32/350v. | 4/- | 5/8 |
| 8/450v. | 2/3 | 500/25v. | 3/- | 100/275v. | 4/- | 5/8 |
| 8/500v. | 2/3 | 8/450v. | 4/6 | 2,000/35v. | 4/- | 4/- |
| 16/450v. | 3/8 | 8/450v. | 5/- | 32/32/350v. | 4/8 | 4/8 |
| 16/500v. | 4/- | 8/16/450v. | 5/- | 32/32/450v. | 6/8 | 6/8 |
| 32/450v. | 5/8 | 8/16/500v. | 5/8 | 50/50/350v. | 5/- | 5/- |
| 25/25v. | 1/9 | 16/16/450v. | 6/8 | 64/4/120/375v. | 7/8 | 7/8 |
| 50/25v. | 2/- | 32/32/350v. | 6/8 | 64/100/120/375v. | 11/8 | 11/8 |
| 50/50v. | 2/- | 32/32/350v. | 4/8 | 100/100/200/375v. | 12/8 | 12/8 |
| SELENIUM RECTIFIER. 300 v. 85 mA, 7/8. CONTACT COOLED 250 v. 50 mA, 7/8. 50 mA. 9/8; 200 mA. 21/-; 300 mA. 27/6. COILS WOUND "P" type. 3/- each. Osmor Midget "Q" type adj. dust core from 4/-; All ranges. TELETRON. L. & M. T.R.F. with reaction, 3/8. FERRITE ROD AERIALS. M.W. 8/8; L. & L. 12/6. T.F. COILS A.H.F. 7/- pair. H.F. CHOKES 2/6. FERRITE ROD. 7in. x 1 1/2in. 2/8. | | | | | | |

JASON F.M. TUNER COIL SET. 26/- H.F. coil, aerial coil. Oscillator coil, two I.F. trans. 10.7 Mc/s. Ratio Detector and heater choke. (Circuit book using four 6AM6, 2/8).
COMPLETE JASON F.M. KIT WITH VALVES. £6.15.0. Fringe area kit, 22/8 extra.

FULL WAVE BRIDGE SELENIUM RECTIFIERS. 2, 6 or 12 v. 1 1/2 amp., 8/8; 2 a., 11/3; 4 a., 17/6.
CHARGER TRANSFORMERS. Tapped input 200/250 v. for charging at 2, 6 or 12 v., 1 amp., 15/6. 2 amps., 17/6; 4 amps., 22/6. Circuit included.

VALVE and TV Tube equivalent books. 5/-
TOGGLE SWITCHES. 2 P. pair, D.P. 3/8. D.P.D.T. 4/6.

WAVECHANGING SWITCHES
 5 p. 4-wave 2 wafers long spindle ... 6/8
 2 p. 2-way, or 3 p. 2-way short spindle ... 2/6
 2 p. 6-way, or 3 p. 2-way, 4 p. 3-way long spindle ... 3/6
 3 p. 4-way, or 3 p. 1 d. 12-way long spindle ... 2/6
VALVE HOLDERS. 1ax. Int. Oct. 4d. EF50, EA50, 6d. B12A, C1T, 1/3. Eng. and Amer. 4, 5, 6, and 7 pin, 1/-; MOULDED MAZDA and Int. Oct., 1d. B7G, B8A, B8B, B9A, 9d. B7G with can., 6d. B9A with can., 1/8. CERAMIC EF70, B7G, B9A. Int. Oct. 1/-; 5Cana. B7G, B9A, 1/-.

COSSOR MAINS-BATTERY POWER PACK 60 v. H.T. 1 1/2 v. L.T. Same size as BATTERY B126 and RD 35. List 63/-, our price 59/6.

RADIO COMPONENT SPECIALISTS


Postal service 1/4, over £2 free. (Export Extra.) C.O.D. 1/6. (Wed. 1 p.m.)

OUR ONLY ADDRESS
337 WHITEHORSE RD.,
WEST GROYDON
 THO 1665. Buses 133 or 68

MOTEK

Patents Pending.
Details of K10 (as
illustrated) on Request.

THREE SPEED TAPE-DECK

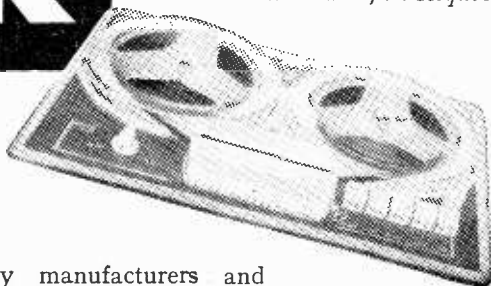

The Motek tape deck is both the heart and backbone of a multitude of recording machines. Confidence in Motek, felt by manufacturers and enthusiasts alike, grows with the technical excellence of Motek equipment.


Three speeds, pause control, push button operation, accidental erasure prevention, positioning counter . . . these are a few of the outward signs of internal quality.

List 21 gns.

MODERN TECHNIQUES

Wedmore Street, London, N.19.

Tel.: Archway 3114.

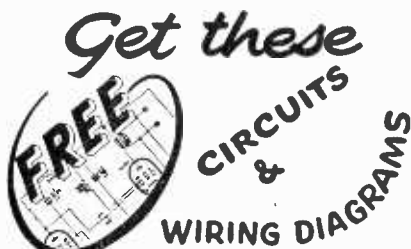

T.R.F. Circuits
Battery Circuits
Portable Circuits
S'het Circuits
Mains Circuits
Filter Circuits
F.M. Tuner

Single Valve F.M. Tuner.
2 Valve F.M. Complete Set.
Same on Printed Circuit, etc., etc.
Send Postage 1/- (stamps)

OSMOR COILS are regularly used and recommended by designers writing in "Practical Wireless," "Wireless World" and "Radio Constructor." Why not follow the experts?

"Q Coils" All ranges
Potted Coils
F.M. COILS
TAPE COILS
ROD AERIALS
Speaker Cross-over Coils
Coils and I.F.s for Transistor Circuits
SUB-MINIATURE COILS
Midget I.F. Trans. With ferrite cores

OSMOR

418 Brighton Road,
South Croydon.
Telephone: CRO 5148/9

GENUINE GUARANTEED BRITISH TRANSISTORS

FAMOUS MAKES . . . LOWEST PRICES EVER

FLASH! Perfect Mullard OC70 9/-

TS1 (BRIMAR).—L.F./I.F./General purpose 800 kc/s. 4/6.
RED SPOT.—L.F./I.F. General Purpose 900 kc/s. 5/-.
WHITE SPOT.—R.F. Osc./I.F. 3-4 Mc/s. 6/6.
Green/Yellow.—Audio/Output 125 mW. 7/6.
TS3.—Special Offer, a few only. 12/6.
EDISWAN.—XA104, 18/-; XB102, 10/-; XB104, 10/-; XA103, 15/-.
EDISWAN.—Set of Seven Transistors. XA102, two XA101, XB102, XB103, two XC101. ONLY 60/6 per set.
MULLARD.—OC18, 54/-; OC44, 28/-; OC45, 23/-; OC85, 22/6; OC68, 25/-; OC70, 14/-; OC71, 14/-; OC72, 17/-; 2/OC72 (Matched Pair), 34/-; OC170 (70 Mc/s), 50/-; OCPT1, 50/-.
ANY TYPE OF TRANSISTOR CAN BE SUPPLIED.

TRANSISTOR HOLDERS, 1/3. ARDENTE sub-miniature, 1/9.
CRYSTAL DIODES, 1/-, GEX34, 4/-; Mullard OA81, 4/-; OA70, 4/-.
FERRITE ROD.—5 x 1/4 in., 2/6; 6 x 1/4 in., 2/9; 3 x 5/16 in., 1/6.
COILS.—Repanco DRR2, 4/-; DRX1, 2/6; Teletron HAX, 3/-, All complete with circuits.
TUNING CONDENSERS.—Solid, dielectric, 500 pF (0.0005 mfd.). 4/-; 300 pF, 3/9; 100 pF, 3/-, MINIATURE 500 pF, 5/-.
TRANSISTOR CIRCUITS.—MINI 3, 1/3; Mini 7, 1/6; Major 7, 1/6; MAXI "Q" 6, 8d.; Teletron Transdyna, 11d. (Full Kit, £11/17/6); Three Dee, 11d. (Full Kit, 67/6). The NEW 300-500 mW Amplifier and Feeder Units (6 circuits and plans), 1/6.
BEGINNERS' 1 VALVE.—Circuit and plans, 11d. Kit, 37/6.
RESISTORS.—All values 10% ± w. 6d.; 1 watt, 9d. 1% ± w. 2/-.
CONDENSERS.—Miniature, 0.01/100 v., 10d.; 0.1 mfd./100 v., 1/2; 0.005/200 v., 10d.; standard size 0.01/1,000 v., 8d.; 0.1/250 v., 9d.; 0.1/500 v., 10d.; 0.5/550 v., 1/10.
ELECTROLYTICS.—(Can Type) 32-32/450 v., 6/6; 100-200/275 v., 8/9; 60-250/275 v., 8/9; 64-120/350 v., 9/6; 60-100/275 v., 7/-; 24-24/350 v., 4/6; 100-100/200/275 v., 13/-; 60-50-50/350 v., 9/10; Wire ended, 16 mfd./450 v., 2/4; 16-16/450 v., 4/-; 8-8/450 v., 2/9; 8-16/450 v., 2/9; 50 mfd./50 v., 1/6; 25 mfd./25 v., 1/8; 100 mfd./6 v., 2/3.
Miniature, 25 mfd., 2/8; 50 mfd., 2/3; 3 mfd., 2/3; 2 mfd., 2/6.
SUB-MINIATURE, 32 mfd., 25 mfd., 16 mfd., 8 mfd., 4 mfd., 2 mfd. All 3/6; 100 mfd., 2/9; 0.1 mfd., TCC, 4/-.
CONNECTING WIRE. Six assorted colours. 1 yard of each colour 1/8; 2 yards of each colour 2/9; 10 yards each colour 10/6.
TERMS: Cash with Order (or C.O.D. on orders over £2).
ALL OUR PRICES ARE POST PAID.

OAKFIELD RADIO

THE TRANSISTOR PEOPLE

Mail Order Only

44 Oakfield Road, Stockport, Cheshire

.....Club News.....

REPORTS OF CURRENT ACTIVITIES

BARNET AND DISTRICT RADIO CLUB

Red Lion Hotel, High Barnet, Herts.

Hon. Sec.: K. Robinson, 3 Castle Road, North Finchley, N.12.

Meetings are held on the last Tuesday of each month. The club has a transmitting licence—G3FFA—and puts out a slow Morse practice on about 1930kc/s every Monday evening at 8.

Future events:

March 29th.—Talk on Radio in Antarctica illustrated with coloured slides and films by Major G. Watson.

April 26th.—Lecture on the Collins range of equipment.

May 31st.—Special meeting to make final arrangements for National Field Day.

June 28th.—Lecture on Metal Rectifiers by Rectifier Division of S.T.C.

July 26th.—A talk on receivers.

August 30th.—To be announced.

September 27th.—Annual General Meeting.

BRADFORD AMATEUR RADIO SOCIETY

Cambridge House, 66 Little Horton Lane, Bradford 5.

Hon. Sec.: David M. Pratt (G3KEP).

Two very interesting lectures were held recently: on January 12th, "Colour Photography" by A. R. Bailey, M.Sc., and on February 9th, "Inexpensive Sound Fidelity" by Secretary D. M. Pratt.

Future events:

March 8th.—Talk on radio and television interference by Mr. J. G. Belcher, A.M.Brit., I.R.E. (G5FCS).

March 22nd.—Annual General Meeting.

April 5th.—Field Day Arrangements.

April 26th.—Lecture by D. G. Enoch on the "Development of Television".

THE BRITISH INSTITUTION OF RADIO ENGINEERS

9 Bedford Square, London, W.C.1.

Meetings for March.

London Section.—Meetings are held at the London School of Hygiene and Tropical Medicine, Keppel Street, Gower Street, W.C.1.

March 14th at 6.30 p.m.—Radar Group. Discussion on "Short Range Navigational Aids".

March 24th at 6.30 p.m.—Medical Electronics Group. "The Continuous Recording of Heart Activity" by Dr. I. Boyd and W. R. Eadio.

March 30th at 6.30 p.m.—"Silicon Photo-Voltaic Cells for Instrumentation and Control Applications" by V. Magee, Ph.D., and A. A. Shepherd, Ph.D.

Birmingham—West Midlands Section.—Meetings are held at Matthew Boulton Technica College.

March 8th at 7.15 p.m.—"Transistor Power Amplifiers" by F. Butler, O.B.E., B.Sc.

Bristol—South Western Section.—Meetings are held at the School of Management Studies, Unity Street.

March 30th at 7 p.m.—"Training for Operating and Maintaining Television Studio Broadcasting Equipment" by K. R. Sturley, Ph.D., and A. E. Robertson, B.Sc.

Cardiff—South Wales Section.—Meetings are held at the Welsh College of Advanced Technology.

March 16th at 6.30 p.m.—"Recent Development in Printed and Potted Circuits" by H. G. Manfield.

Edinburgh—Scottish Section.—Meetings are held at the Department of Natural Philosophy, The University, Drummond Street.

March 25th at 7 p.m.—"Radio Guidance in the Automatic Landing of Aircraft" by J. Shaylor, B.Sc.Tech.

Glasgow—Scottish Section.—Meetings are held at the Institution of Engineers and Shipbuilders, 39 Elmbank Crescent.

March 24th at 7 p.m.—"Radio Guidance in the Automatic Landing of Aircraft" by J. Shaylor, B.Sc.Tech.

Liverpool—Merseyside Section.—Meetings are held at the University Club.

March 7th at 7 p.m.—Short informal papers by members.

Malvern—South Midlands Section.—Meetings are held at the Winter Gardens.

March 29th at 7 p.m.—"Microwave Propagation—Some Characteristics and Curiosities" by M. W. Gough, M.A.

Newcastle-upon-Tyne—North Eastern Section.—Meetings are held at the Institution of Mining and Mechanical Engineers, Neville Hall, Westgate Road.

March 9th at 6 p.m.—"Silicon Photo-Voltaic Cells in Instrumentation and Control" by A. A. Shepherd, Ph.D.

BRITISH SOUND RECORDING ASSOCIATION

The B.S.R.A. is holding a Convention on Saturday, 23rd April, at the London School of Hygiene and Tropical Medicine, Keppel Street, London, W.C.1, in conjunction with the

London Audio Fair. Morning, afternoon and evening sessions will be held and the papers to be presented will survey post-war development in tape and disc recordings, pick-up design and cinema sound systems. Registration will cost 5s. for B.S.R.A. members and 10s. for non-members. Full details can be obtained from S. W. Stevens-Stratten, Greenways, 40 Fairfield Way, Ewell, Surrey.

DERBY AND DISTRICT AMATEUR RADIO SOCIETY

Sub-base, Derby College of Art, Green Lane, Derby.

Hon. Sec.: F. C. Ward (G20VV), 5 Uplands Avenue, Littleover, Derby.

The Annual General Meeting was held on February 3rd and the transmitting and receiving contest for the President's and the G4YY Trophies on February 7th.

Future events:

March 9th.—Open Evening in the club rooms.

March 16th.—"A Top Band converter for use by the SWL in conjunction with a Broadcast Receiver"—Room No. 4, 119 Green Lane, at 7.30 p.m.

March 18th at 7.15 p.m.—Annual Dinner and Social Evening at the Irongates Grill.

March 23rd.—Open Evening.

August 14th.—Third Annual Mobile Rally at Rykneld School.

GRIMSBY AMATEUR RADIO SOCIETY

R.A.F.A., Abbey Drive West.

Hon. Sec.: Mr. Owen Gilliat, 24 Station Road, Healing, Lincs.

Meetings are held on the first and third Thursdays in each month at 8 p.m.

Future event:

March 31st.—Talk and demonstration by G3ELZ on his new six band TX.

HALIFAX AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: A. Robinson, Candy Cabin, Ogden, Halifax.

On January 5th the members met for a lecture dealing with TVI by G3ADG, and on January 8th the Annual Dinner was held. A Ragweek was held on February 16th and a Film Show on March 1st.

Future events:

March 15th.—National Field Day arrangements.

March 29th.—Informal Evening.

LIVERPOOL AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: H. James, 448 East Prescott Road, Knotty Ash.

Liverpool 14.

Future events:

March 8th.—"Stereo Amplifiers".

March 15th.—Swap Night.

March 22nd.—The Panadapter.

March 29th.—Film Show.

April 5th.—Junk Sale.

MIDLAND AMATEUR RADIO SOCIETY

The Birmingham Midland Institute, Paradise Street, Birmingham.

Hon. Sec.: C. Haycock (G3JJD).

Future events:

March 15th.—"Frequency measurements and VHF demonstrations by R. Rew.

April 7th.—"The New Trunk Dialling Scheme" by Brig. F. Jones.

April 19th.—"Radio Pictures" by Mr. K. Stevens.

April 24th.—Mobile Rally at Trentham Gardens, Stoke-on-Trent.

May 5th.—"Complete Construction of 70cm Transmitter" by R. Rew and T. F. Douglas.

THE OXFORD UNIVERSITY RADIO SOCIETY

President: C. E. Chatwin, Jesus College, Oxford.

On February 9th a talk was given by B. Marsden of Associated Television on "The Operation of Commercial Television".

and on February 17th, Mr. W. J. Morcum of Marconi Ltd. gave a talk on "High Power Transmitters".

Future event:

March 8th.—"Single Sideband Radio Communication" by N. Elson of Racal Engineering Ltd.

RADIO SOCIETY OF GREAT BRITAIN

Region 14, Glasgow

Hon. Sec.: Richard Craig (GM3NIF), 272 Bellrock Street, Glasgow, E.3.

Meetings are held on the last Friday of each month in the Christian Institute, 70 Bothwell Street, Glasgow, C.2, commencing at 7.30 p.m.

THE READING AMATEUR RADIO CLUB

Palmer's Hall, West Street, Reading.

Hon. Sec.: R. J. Nash (G3EJA), "Peacehaven", 9 Holybrook Road, Reading.

At the January meeting G5HZ was again voted Chairman for the coming year, G3KH as Treasurer and G3EJA as

Secretary. The meeting was well attended and G3GKH continued morse instruction with the largest class he has had to date. A discussion was held on RSGB matters, field days and a Scout Jamboree. A junk sale in aid of funds followed. All meetings are held on the last Saturday in each month at 7 p.m.

Future event:
March 26th.—Films and lecture on the practical application of transistors to receivers and transmitters.

REIGATE AMATEUR TRANSMITTING SOCIETY

Hon. Sec.: F. D. Thom, 12 Willow Road, Redhill, Surrey.

The first annual general meeting was held on January 16th and was very well attended.

Future events:

March 19th.—Talk on TVI by G4ZU at The Tower, Redhill.

April 9th.—Talk by G8KW.

SPEN VALLEY AMATEUR RADIO SOCIETY

Hon. Sec.: N. Pridc, 100 Raikes Lane, Birstall, Leeds.

The annual dinner was held on January 23rd and was attended by 61 members. The silver cup for outstanding services to the Society was awarded to Mr. F. Varley, G2FCF.

Future events:

March 16th.—Visit to Mains Radiograms Ltd., Bradford.

March 30th.—"Electronics in Industrial Research" by Dr. N. H. Chamberlain.

April 13th.—Post Office Mechanisation at Leeds G.P.O.
April 27th.—Open Meeting.

SOUTH YORKSHIRE AMATEUR RADIO SOCIETY

Stag Inn, Dockin Hill Road, Doncaster.

Hon. Sec.: W. Farrar, 2-A Highbury Avenue, Bessacarr, Doncaster.

At the meeting on January 14th it was decided to hold meetings on the second Tuesday and fourth Thursday of each calendar month. These meetings will be held at 7.30 p.m.

WEST KENT AMATEUR RADIO SOCIETY

Culverden House, Tunbridge Wells.

Hon. Sec.: H. F. Richards, 17 Reynolds Lane, Tunbridge Wells, Kent.

Meetings are held at 7.30 p.m. on alternate Fridays.

Future events:

March 14th.—A practical demonstration of wiring, layout, and testing, principally for the benefit of younger members.

April 1st.—Informal evening.

April 29th.—Annual General Meeting.

THE WANSTEAD AND WOODFORD RADIO SOCIETY

Wanstead House, The Green, Wanstead, E.11.

Hon. Sec.: P. J. Seaman, 39 Kensington Drive, Woodford Green, Essex.

The club continues to meet every Wednesday at 8 p.m.

RECTIFICATION AND SMOOTHING

(Continued from page 1061)

because of the resemblance between the circuit diagram and the Greek letter π . In this type of filter there is a condenser, C1, across the output from the rectifier; it is therefore one type of condenser input filter. The condenser, C1, which stores the electrical energy supplied by the rectifier is known as the reservoir condenser. The working voltage of this condenser should not be less than $\sqrt{2}$ (i.e. about $1\frac{1}{2}$) times the mains voltage in the circuit of Fig. 1, $\sqrt{2}$ times the voltage from either end of the transformer winding to the centre tap in the circuit of Fig. 2, or $\sqrt{2}$ times the voltage of the transformer winding in the circuit of Fig. 3. The working voltage of the smoothing condenser, C2, need only be a little above the H.T. voltage. If a valve rectifier is used, the value of the reservoir condenser, C1, must not exceed the maximum value recommended by the valve manufacturers or the peak cathode current of the rectifier may be exceeded momentarily during each cycle.

The smoothing circuit shown in Fig. 4 is known as a choke input filter because a choke is the first filter component. The components shown dotted may be used for extra smoothing.

Outputs

The D.C. output voltage obtained with condenser input is higher than that obtained with choke input assuming that other conditions (including the output current and mains transformer voltage) are identical. The output voltage from a condenser input filter drops steadily as the output current increases; in other words the regulation is poor. The D.C. output from a choke input filter drops very suddenly when a small current is taken from the unit, but, after this initial drop, the voltage falls only slightly with further increase in output current. The regulation over this region is therefore good. Actual measured output voltages of the circuit of Fig. 2 when $C1 = C2 = 16\mu\text{F}$ and $L = 20\text{H}$ are shown in Fig. 5 for various output currents together with the output voltage from the choke input filter of Fig. 4 when $C1 = C2 = 16\mu\text{F}$ and $L1 = L2 = 10\text{H}$. In each case, the transformer winding was rated at 350-0-350V at 80mA.

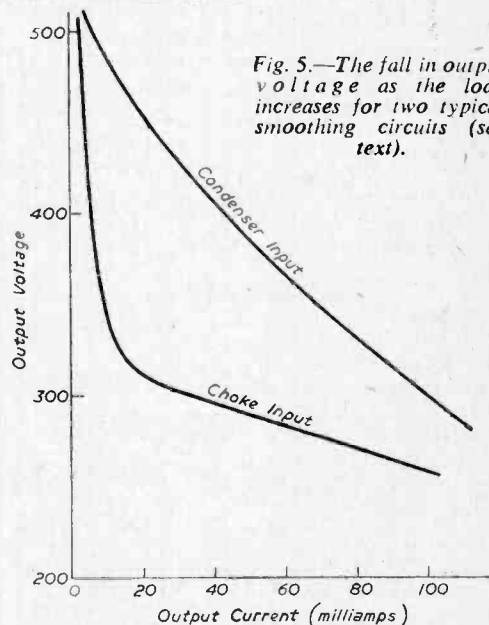


Fig. 5.—The fall in output voltage as the load increases for two typical smoothing circuits (see text).

When the output current required from a power pack is not more than a few milliamps, the smoothing chokes in any of the circuits shown can be replaced by resistors of a few thousand ohms. In addition to lowering costs, this also saves space, but the output voltage is reduced and the regulation is poor. It is important that the resistors should have an adequate power rating.

Generally the values of smoothing components are not very critical and any remaining hum voltage can often be reduced by placing extra smoothing condensers in parallel with those already in the power pack. Electrolytic smoothing capacitors should be placed well away from hot objects such as valve rectifiers. If one of the circuits shown is used to operate an ordinary radio receiver, satisfactory results will normally be obtained if a 10H choke and 16 μF electrolytic condensers are used.

RETURN-OF-POST SERVICE

NEW ILLUSTRATED LISTS

New illustrated lists are available on all the following. Any will be sent free upon request.
TEST GEAR. Test meters, Signal Generators, etc., by AVO, Jason, Pullin and Taylor.

CATHODE-RAY TUBES

BRAND NEW STOCK. NOT REBUILDS.
12 MONTHS' GUARANTEE

We can supply all BVA branded tubes at the new reduced prices. This includes Brimar, Cossor, Emiscope, Emitron, Ferranti, G.E.C., Mazda and Mullard. Full list of all available types sent on request.

MULLARD. 12in. and 14in. types, £10-10.0. H.P. Deposit £22.0 and 12 monthly payments of 15/8. 17in. Types (except MW43/43), £12.0.0. H.P. Deposit £22.8.0 and 12 payments of 17/8. 17in. MW43/43 £14.0.0. H.P. Deposit £22.16.0 and 12 payments of £1.0.6. 21in. Types £16.0.0. H.P. Deposit £34.0 and 12 payments of £1.3.6.

All tubes sent carriage free and safe delivery guaranteed.

GRAMOPHONE EQUIPMENT

ALL LATEST MODELS Hire Purchase
 Cash Price Deposit Mthly. Pmts.
RECORD CHANGERS

| | | | |
|----------------------------------------------------------|-----------|----------|--------------|
| COLLARO Conquest (Studio O PU) | £7.19. 6 | £1.12. 0 | 6 of £1.4.7 |
| GARRARD RC121 (GC8 PU) | £29.19. 6 | £1.19. 6 | 12 of 15/- |
| GARRARD RC88 (GC8 PU) | £18. 9. 0 | £3. 6. 0 | 12 of £1.4.0 |
| GARRARD RC98 (GC8 PU) | £18.12. 8 | £3.15. 8 | 12 of £1.7.3 |
| BSR UA8 Monarch (TC8 PU) | £7. 5. 0 | £1. 9. 0 | 6 of £1.2.8 |
| BSR UA12 Monarch (TC8 PU) | £9.19. 6 | £1.19. 6 | 12 of 15/- |
| BSR UA12 Monarch (TC8S Stereo PU) | £10.17. 6 | £2. 3. 6 | 12 of 16/2 |
| GARRARD TA (GC8 PU) SING. RECORD PLAYERS | £3.10. 0 | £1.14. 0 | 12 of 13/- |
| BSR TU8 (TC8 PU) | £4.10. 0 | £1. 5. 0 | 3 of £1.5.0 |
| COLLARO RP384 (O, P or T PU) | £8.18.11 | £1.15.11 | 12 of 13/7 |
| COLLARO RP394 (O, P or T PU) | £9.18. 9 | £1.18. 9 | 12 of 15/- |
| E.M.I. (Acos Stereo PU) | £6.15. 0 | £1. 7. 0 | 12 of 10/8 |

TRANSCRIPTION UNITS

| | | | |
|--------------------------------------------|-----------|----------|--------------|
| COLLARO 4T/200 (TX88 PU) | £18.13. 0 | £3.15. 0 | 12 of £1.7.4 |
| COLLARO 4TR/200 Motor only | £13.18. 3 | £2.15. 3 | 12 of £1.0.5 |
| GARRARD 4HF (GC8 PU) | £18. 9. 9 | £3.15. 9 | 12 of £1.7.0 |

Many of the above can be supplied for stereo working. See our Gramophone Equipment List for details.

MULLARD TAPE PRE-AMPLIFIER

This unit is intended for use with an existing amplifier and provides all the circuits necessary for tape recording and playback. Instruction manual, giving full constructional information is available price, 2/10, post free.
COMPLETE KIT containing every item required down to the last nut and bolt. First-class items only included, £14.7.0. H.P. Deposit £2.17.0 and six monthly payments of £2.2.6. Kit less valves, £10.19.6. H.P. Deposit, £1.19.6 and six payments of £1.13.4. Power Unit kit, £3.19.6.

LATEST CABY TEST METERS

Now in stock. CABY SUPREME MULTI-RANGE METERS. Made abroad. We can confidently recommend these meters as being accurate, well made and very good value for money.

MODEL A-10. Sensitivity 2,000 ohms per volt A.C. and D.C. Five voltage ranges 10-1,000 volts A.C. and D.C. Three D.C. current ranges 0.5-250 mA. Two resistance ranges. Size 5 1/2 x 3 1/2 in. Price, £4.17.6. H.P. Deposit £1.7.6 and three monthly payments of £1.6.8.

MODEL B-20. Sensitivity 4,000 ohms per volt A.C. and D.C. Voltage ranges—Five D.C. 10-1,000 volts. Four A.C. 10-1,000 volts. Four D.C. current ranges. 0.5-250 mA. Four resistance ranges. Price £6.10.0. H.P. Deposit £2 and three monthly payments of £1.13.4.

Illustrated leaflet giving full details of both models free upon request.



LOUDSPEAKERS. Full details of Goodmans, Whiteley, Wharfedale and Elac types.

TAPE DECKS. All popular makes with a special offer.

RECORDING TAPES. A very wide range of all tapes and accessories.

GRAMOPHONE EQUIPMENT. Details of many types of Auto Changers, Single Record Players and Transcription Units including all the latest models. Many at special prices.

RECORDING TAPE

DOUBLE PLAY

BASF. 300ft. (3in.), 14/-; 600ft. (4in.), 25/-; 1,200ft. (5in.), 42/-; 1,600ft. (5 1/2in.), 52/6; 2,400ft. (7in.), 77/6.
SCOTCH BOY. 300, 600ft. (3in.), 17/-; 1,200ft. (5in.), 45/-; 2,400ft. (7in.), 80/-.
TELEFUNKEN. 1,200ft. (5in.). In plastic container, 40/-; 1,800ft. (5 1/2in.), in plastic container, 50/-; 2,400ft. (7in.), 75/-.
SPECIAL OFFER. 1,200ft. Standard Tape. Brand new. Famous maker. Fully guaranteed, 25/-; Four for 95/-; Full range of standard and L.P. tape and accessories also stocked. Send for list. All tape post free.

LATEST AVO TEST METERS


AVO METER MODEL 8. The finest multi-range meter available. 20,000 ohms per volt on D.C. ranges. Eight D.C. Voltage ranges 2.5 v. to 2,500 v. Seven D.C. current ranges 50 microamps to 10 amps. Seven A.C. Voltage ranges 2.5 v. to 2,500 v. Four current ranges 100 mA to 10 amps. Three resistance ranges. Fully detailed leaflet available. Price £23.10.0. H.P. Deposit £4.14.0 and 12 monthly payments of £1.14.6. Price with leather carrying case, £27.8.0. H.P. Deposit £5.8.0 and 12 payments of £2/4.
 Other AVO Meters available include the Model 7, £19.10.0. H.P. Deposit £3.18.0 and 12 payments of £1.8.8 and the Multiminor price £29.10.0. H.P. Deposit £1.18.0 and 12 monthly payments of 14/4.

JASON FM TUNER

There are no less than four different Jason FM Tuner Kits now available to the Home Constructor. Brief details are given here and individual lists on any are available free.

MOST IMPORTANT. We take great pains to see that the kits we supply are *absolutely complete* in every detail and also that all components supplied are entirely suitable in every way. This accounts for differences in price you may notice between our prices and those of some of our competitors. **THIS SHOULD BE BORNE IN MIND WHEN COMPARING PRICES.**

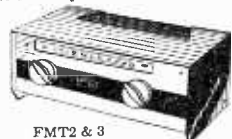Hire Purchase Terms available. **FMT2 & 3**



STANDARD TUNERS

STANDARD TUNER, FMT1. The very popular tuner which is supplied with a chassis assembly fitted with a gold hammer finish front panel and glass dial. Employs four EF81 valves. External power supply is required. Complete kit £8.19.6. Power pack kit 39/-.

STANDARD TUNER IN SHELF MOUNTING CASE, FMT2. This is a new version of the above tuner. The circuit has been brought up to date and is built into the very attractive shelf mounting case of the new Fringe Tuner mentioned below. The circuit uses four EF80 valves and the power supply can be built into the case if desired. Complete Kit £7.17.6 without power supply components, £9.16.0 with power supply.
MERCURY SWITCHED TUNER. This is a tuner in chassis form which has a three position switch for the three BBC programmes. Uses one ECF80 and four EF80 valves. External power supply is required. Complete Kit £9.19.0. Power Pack Kit 39/-.

FRINGE TUNERS

NEW FRINGE TUNER IN SHELF MOUNTING CASE, FMT3. This is an entirely new Fringe Tuner and is supplied complete with a very attractive green shelf mounting case with Perspex dial. The tuner is fitted with variable AFC. Internal power supply if desired. Valves used are one ECC81 and five EF80. Complete Kit £21.8.6 without power supply components, £11.18.0 with power supply.

INSTRUCTION MANUALS

All our kits include the appropriate instruction manual. All available separately as follows:
 Manual covering both Standard Tuners and the new Fringe Area model, 2/10; "Mercury," 2/3. All post free.

Hire Purchase Terms are available on any item. Repayments may be spread over 3, 6 or 12 months. Details as follows: Three months: Deposit 9/- in the £. Service charge 5% but minimum charge 10/-. Six and Twelve months: Deposit 4/- in the £. Service charge 10% but minimum charge 20/-.

Terms of Business.—Cash with order or C.O.D. Postage extra under £3. We charge C.O.D. orders as follows. Up to £3, postage and C.O.D. fee minimum 2/8. Over £3 and under 25, C.O.D. fee only 1/6. Over £25 no charge.

WATTS RADIO
 (MAIL ORDER) LTD.

54 CHURCH STREET, WEYBRIDGE, SURREY
 Telephone: Weybridge 4556

Please note: Postal business only from this address.

WEYRAD

COILS AND TRANSFORMERS FOR A 2-WAVE TRANSISTOR SUPERHET WITH PRINTED CIRCUIT AND FERRITE ROD AERIAL

LONG AND MEDIUM WAVE AERIAL—RA2W
On 6 in. rod, 7/16 in. diameter, flying lead
connections, 208 pF tuning

OSCILLATOR COIL P50/1AC

Medium wave in screening can. For 176 pF
tuning condenser

1st AND 2nd I.F. TRANSFORMERS—P50/2CC
470 Kc/s operation with 250 pF tuning in cans.

11/16 in. diameter by 3/4 in. high

3rd I.F. TRANSFORMER—P50/3CC

Last stage transformer to feed diode detector.

Size as P50/2

DRIVER TRANSFORMER—LFD2T

Upright mounting with six connecting tags—
1 5/8 in. x 7/8 in. x 1 3/4 in.


12/6

5/4

5/7

6/-

9/6

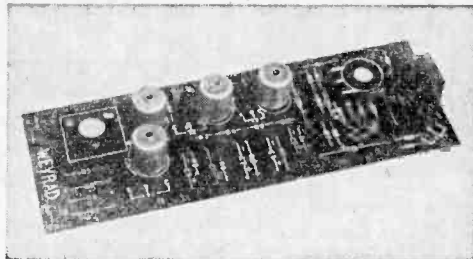

PRINTED CIRCUIT—PCAI

Size 2 3/4 in. x 8 1/4 in. Ready drilled and printed with component positions

9/6

THESE COMPONENTS ARE APPROVED BY TRANSISTOR MAKERS
AND PERFORMANCE IS GUARANTEED.

Constructor's Booklet with full details, 2/-.

WEYMOUTH RADIO MANUFACTURING CO., LTD.

CRESCENT STREET, WEYMOUTH, DORSET

VALVES

SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS

1R5, 1S6, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DK92, DL92, DL94, any 4 for 23/6
DAF96, DF96, DK96, DL96
6K7G, 6A8G, 6Q7G, 6V6G, 6X5G, or 5Y3G

4 for 30/-

5 for 27/-


| | | | | | |
|------------|-------------|-------------|------------|------------|------------|
| 1A7GT 12/- | 6L1 15/- | 25Z4G 8/- | EBG41 8/- | EY86 8/3 | PZ30 17/- |
| 1D5 9/- | 6L18 12/3 | 25Z6GT 9/6 | EBF80 8/- | EZ40 6/9 | SP61 3/6 |
| 1H5GT 10/- | 6P25 9/- | 30C1 8/- | EBF89 8/9 | EZ41 7/6 | T41 15/6 |
| 1N5GT 10/- | 6Q7G 6/9 | 30L1 8/- | EBL21 20/6 | EZ80 6/3 | U25 12/- |
| 1R5 6/9 | 6Q7GT 9/6 | 35L8GT 10/- | EC92 11/- | EZ81 8/- | U26 12/- |
| 1S4 9/- | 6SL7GT 6/3 | 35Z4GT 8/- | ECC81 3/9 | FW4500 8/- | U50 7/6 |
| 1S5 5/9 | 6SN7GT 4/9 | 35Z5GT 8/6 | ECC82 6/6 | GZ32 9/- | U76 6/- |
| 1T4 4/9 | 6U4GT 11/- | 43 8/- | ECC83 7/- | KT33C 7/- | U78 6/- |
| 3U5 6/6 | 6V6G 5/- | 50CD6G 26/9 | ECC84 8/9 | KT41 14/6 | UABC80 7/9 |
| 3A5 10/6 | 6V6GT 6/6 | 50L6GT 8/9 | ECC85 8/3 | KT61 10/- | UAF42 9/6 |
| 3Q4 8/6 | 6X4 5/- | AZ31 9/6 | ECF80 10/- | KT83 6/6 | UBC41 7/9 |
| 3S4 6/9 | 6X5GT 5/6 | B36 8/9 | ECF82 10/- | KT71 8/6 | UBF80 9/6 |
| 5V4 7/6 | 7B7 7/6 | CL33 13/- | ECH21 20/6 | MH4 6/- | UBF89 8/6 |
| 5U4G 5/3 | 7C5 7/6 | DAC32 10/- | ECH35 6/6 | MU14 8/- | UBL21 20/6 |
| 5V4G 9/6 | 7C8 7/6 | DAF91 5/9 | ECH41 8/8 | MX40 12/6 | UCC84 12/9 |
| 2Y3GT 6/9 | 7H7 7/6 | DAF96 8/3 | ECH81 8/6 | N15 9/6 | UCC85 8/- |
| 6Z4G 9/6 | 7S7 9/9 | DCC90 10/6 | ECL80 8/- | PCC84 8/- | UCF80 14/- |
| 6AL5 3/9 | 7Y4 7/- | DF33 10/- | ECL82 10/- | PCC89 14/- | UCH21 20/6 |
| 6AM5 5/- | 10C1 14/6 | DF91 4/9 | EF39 4/6 | PCF80 8/- | UCH42 9/- |
| 6AM5 3/6 | 10M2 17/6 | DF96 8/3 | EF41 8/9 | PCF82 9/3 | UCH81 8/6 |
| 6AQ5 6/- | 10F1 15/6 | HW6 6/6 | EF42 11/6 | PCL82 9/2 | UCL82 11/6 |
| 6AT5 7/3 | 12AH8 10/6 | DH77 7/3 | EF80 6/6 | PCL83 11/- | UCL33 13/- |
| 6BA5 6/- | 12AT7 5/9 | DK32 12/- | EF85 6/9 | PCL84 8/- | UF41 8/9 |
| 6BE5 9/- | 12AU6 7/6 | DK40 14/- | EF86 10/6 | PEN44 11/- | UF42 8/6 |
| 6BH5 5/9 | 12A17 6/- | DK51 8/9 | EF89 8/- | PEN36C 8/6 | UF89 7/6 |
| 6BJ5 5/9 | 12AX7 7/- | DK92 8/9 | EF91 3/6 | PEN45 8/- | UL41 8/- |
| 6BR7 10/- | 12BA6 8/- | DK96 8/3 | EF92 4/6 | PEN46 5/6 | UL42 8/- |
| 6BW6 10/- | 12K7GT 5/6 | DL33 9/- | EL33 10/- | PL36 11/9 | URIC 8/- |
| 6BW7 6/6 | 12K9GT 11/6 | DL35 10/6 | EL38 21/6 | PL38 14/6 | UY21 14/- |
| 6CD6G 28/9 | 12Q7GT 5/6 | DL32 6/9 | EL41 9/- | PL81 10/- | UY41 6/6 |
| 6F1 14/6 | 12Z3 7/6 | DL94 7/6 | EL42 10/6 | PL82 7/6 | UY85 6/9 |
| 6FG6 6/6 | 14S7 16/9 | DL96 8/3 | EL84 7/6 | PL83 8/- | VP4B 8/6 |
| 6FI3 12/6 | 19AQ5 7/- | EABC80 7/- | EM34 8/6 | PY32 12/- | VP41 6/- |
| 6FI4 17/6 | 20F2 17/6 | EAC91 4/6 | EM80 9/- | PY80 7/6 | W76 6/6 |
| 6KT5 3/9 | 20L1 17/6 | EAF42 8/6 | EM81 9/- | PY81 6/9 | W77 4/6 |
| 6K7GT 6/- | 25AG6 11/- | EB31 3/9 | FM84 9/- | PY82 7/- | X76M 11/6 |
| 6K8G 6/9 | 25L6GT 9/- | EB33 5/- | EY51 9/- | PY83 7/9 | Z77 3/6 |

BARGAIN OFFER

DE-LUXE 4 WATT
GRAM AMPLIFIERS

LIST PRICE £9-7-6

OFFERED AT

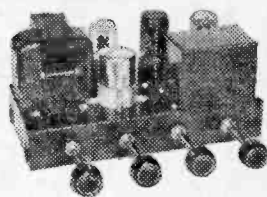

£4-0-0

Guaranteed for 12 months

This Amplifier is a high quality unit by a well known manufacturer. It has independent boost and cut on treble, middle, and bass. The response curve can be varied to compensate for non-linearity in pick-up or speaker. The hum level is virtually non-existent and voltage negative feedback gives a very low distortion level. The Amplifier is finished in stove enamel, with fully shrouded transformers and modern knobs with gold rings. Valves 6SN7, 6V6, 6X5. Size 9 x 4 1/2 x 4 1/2 in. Mains 200-250 volts A.C. fully isolated.

C.W.O. or C.O.D. P. & P. 3/6

A.G. SUPPLIES

241A THE BROADWAY, S.W. 19

READERS RADIO

24, COLBERG PLACE, STAMFORD HILL,
LONDON, N.16. STA. 4587


Post 6d. per valve
extra.
Any Parcel Insured
Against Damage in
Transit 6d. extra.
Any C.O.D. Parcel 2/6
extra.

NEWS FROM THE TRADE

LATEST DEVELOPMENTS IN RECEIVERS AND COMPONENTS

MULTIMUSIC TAPE DECK

A NEW tape deck has been introduced by Multimusic Ltd. There are no belts or interwheels and in operation there are only five moving parts. Three of these are the motors, all specifically designed for the purpose, one being the main drive motor, synchronous or alternatively hysteresis synchronous, and two side motors. The only other moving parts are the pinch-wheel and a gear-driven clock type tape position indicator. The main motor, which gives direct drive, can be

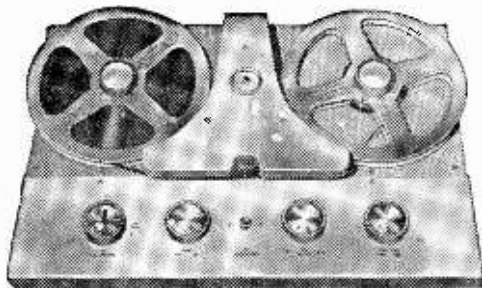


The Multimusic tape deck.

reversible and provision is made in the head assembly unit for three heads to be accommodated each side of the capstan. It is therefore possible to produce for stereo quarter track recording a model which will record one way, stop, reverse and record the other way and then switch off. The deck is supplied for use with reels up to 8½ in. diameter, and is standard rack size—19 in. wide. It will be used with a new range of Reflectograph tape recorders. This tape deck will soon be available from manufacturers of high fidelity equipment and is made by *Multimusic Ltd., Maylands Avenue, Hemel Hempstead, Herts.*

NEW "RAI-TEL-ADE"


AFTER four years consumer research with the original "Rai-Tel-Ade" Electric Ades have now produced the improved "Rai-Tel-Ade" Mark 2, which provides remote control over TV, Radio and Radiograms, and assistance to the deaf and hard of hearing to enable them to enjoy sound programmes fully. By use of switches and control knobs the unit provides complete armchair control for the listener or viewer and improves tone quality for both the hard of hearing and the

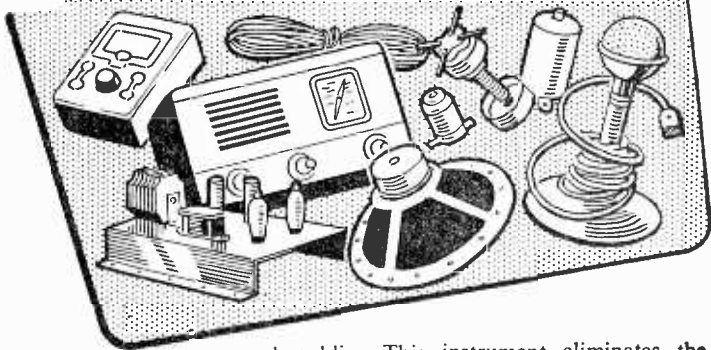

general public. This instrument eliminates the distortions picked up by the usual practice of dangling the deaf aid microphone in front of the source of sound. The "Rai-Tel-Ade" costs £5 5s. and is made by *Electric Ades Ltd., 4, Eastbourne Road, Hanworth, Middlesex.*

MINIATURE POTENTIOMETER

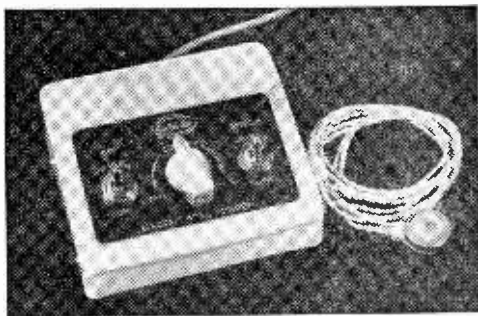IN response to growing demand for miniaturised equipment the Plessey Co. have introduced the Type L potentiometer, the smallest of the spindle-operated type in production. Housed in an aluminium case, it is only 0.5 in. in diameter. The L series incorporates a brush assembly of unique design. Two tracks are included in the moulding; a carbon, resistive outer and a silver-




The "Rai-Tel-Ade" Mark 2.

loaded, conductive inner. They are bridged by a single tension-located brush housed in an insulated carrier. By reducing the number of pressure contacts, greater reliability is achieved. The L potentiometer operates within the temperature range —55 deg C to 58 deg C and has a voltage limitation of 350. It is made by the *Plessey Company Ltd., Ilford, Essex.*

PUSH-BUTTON SWITCH

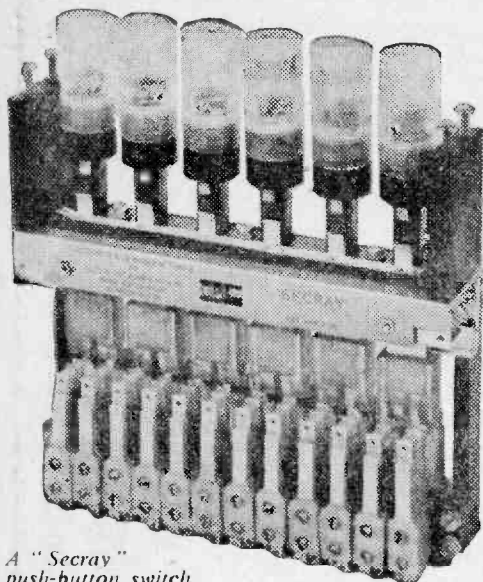A BRITISH company has now produced the prototype of a precision push-button switch for mass production. It is especially suited to high-frequency applications and is designed to



A "Secray" push-button switch.

reduce maintenance and the likelihood of mechanical breakdown. The switch can be made with any number of buttons up to 16. Each button has a standard contact arrangement of two double-pole changeovers. Only one push-button can be operated at one time and the contacts of the operated button are cleared before a new contact is made. The manufacturers are *Seton Creaghe Engineering Ltd., G.W. Trading Estate, Park Royal Road, N.W.10.*

A.E.I. EDUCATIONAL AIDS

PRACTICAL aids to the teaching of basic electronics theory are now available from the Special Products Department of A.E.I. Radio and Electronic Components Division. They have been designed to form the basis of an extensive range of laboratory experiments to be carried out in conjunction with courses in radio and electronic theory. Eleven chassis are available, to teach the basic connections of International Octal, B7G and B9A valves, and the operation of an R/C coupled amplifier, R/C coupled and tuned-anode oscillators, low-pass and high-pass networks and a power output stage. The units have been designed to operate in the audio frequency range. The circuit diagram of each major unit is printed on top of the chassis and where a terminal or switch occurs in the


theoretical circuit, there the actual component is mounted. Each unit is supplied with instruction sheets covering a number of experiments and the underlying theory. Further information can be obtained from *Associated Electrical Industries (Woolwich) Ltd., 155, Charing Cross Road, London, W.C.2.*

NEW SCREWDRIVER

THE Steadfast Ratchet Screwdriver has a handle shaped in a pistol grip fashion making it easy to use and comfortable to handle. The blades are chromium plated, six inches in length, and the handle is made from translucent amber plastic which is virtually unbreakable. The ratchet action is robust and positive. This tool should prove very useful to handymen and constructors, and it may be purchased from most tool dealers and ironmongers and the retail price is 10s. 6d. The makers are *J. Stead and Co. Ltd., Manor Works, Cricket Inn Road, Sheffield 2.*

A.M.G. STANDARD

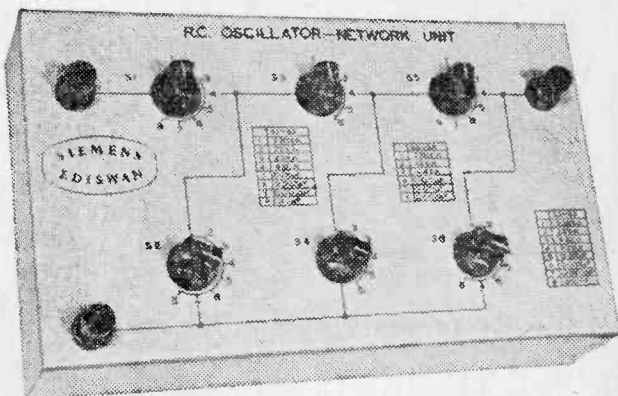A NEW standard has been published by the Technical Committee of the Audio Manufacturers' Group on inter-unit connectors. The aim of the standard has been to facilitate the interconnection of units of different manufacture, provided that their electrical characteristics are matched.




One of the A.E.I. educational aids.

When considering the various forms of connectors, priority has been given to performance and safety requirements. This standard applies to equipment which has its chassis isolated from the mains by a double wound transformer. This standard, "Recommended Practice for Plugs, Sockets and Connectors for use with Audio Amplifying Equipment" is free of charge and is available from *The Secretary, Audio Manufacturers' Group, 49, Russell Square, London W.C.1.*

C.W.S. RADIO SET

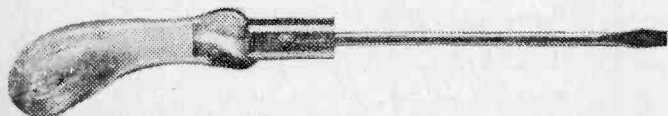A C.W.S. Defiant radio set has been chosen by the Council of Industrial Design for a special exhibition which the Council is staging in Liverpool in May. The set, Model AF21, is a six valve receiver in a modern cabinet and retails at 21 guineas.



The Steadfast ratchet screwdriver.

COMPLETE V.H.F./A.M. RADIO FOR £12.12.0


Brand new set, in superb walnut cabinet (size 19 x 8½ x 14 in. high). Covering 80-100 Mc/s. 16-49 M. 200-500 M. and 1,200-2,000 M. Mains trans. 200-250 v. with 3 tapings. Ferrite rod aerial for A.N. Controls: volume on/off tone, tuning, w/change, Gram. and ext. speaker position provided. Fully guaranteed. Post and packing 5/- extra.




AMPLIFIER AND CABINET

3-watt Amplifier, using an ECL82 Valve and Metal Rectifier, housed in a modern attractive styled walnut cabinet with 5" P/M Speaker and on/off and tone controls. Can be sold for

£4.12.6

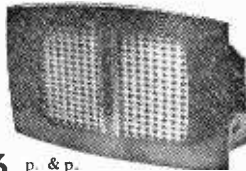

p. & p.
3/6.

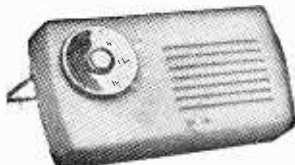

TRANSISTOR KIT

A six Transistor pocket radio, can be built for

£9.19.6

plus 3/6 post. Full medium and long wave superhet. Printed circuit construction, using latest miniature components, 2½" moving coil speaker, Ferrite Aerial. Choice of an attractive plastic cabinet in Cream, Blue or Red. Complete easy-to-build instruction book included. All Parts Sold Separately.

OUR LATEST OFFER: THE FAMOUS COSSOR (Traveller's Friend) TRANSISTORISED POCKET RECEIVER

This set can be built for £7.19.6. Size 6 x 3½ x 1½ in.

£7.19.6



Weight 17 ozs. This set covers medium waveband 190/500 metres intermediate frequency. 470 kc/s using 4 transistors (Ediswan) and 2 diodes on a printed circuit board, plus a 2½" moving coil speaker. Instruction book with point to point wiring diagram, 2/6 each. Batteries, PP4 (Ever Ready) 2/- each. P. & P. 2/-.

ALL PARTS CAN BE SOLD SEPARATELY



Convert your Battery Set to Mains with a COSSOR BATTERY ELIMINATOR

MU2. For operation on 200/250 v. 50 c/s A.C. mains. Output: L.T., 1.5 v 125 mA.; H.T., 90 v. 10 mA.

OUR PRICE **37/6** p. & p.



AMPLIFIER KIT

This is the famous Cossor 562K, 3-watt Audio Amplifier Kit, using 1 EF86, 6BQ5 and 5V4 valves, a 10" x 6" elliptical speaker and a 4" round speaker. This kit can be easily assembled to provide a compact and versatile printed circuit amplifier suitable for operation from radio microphone gramophone inputs. The circuit design includes negative feed-back and high performance loudspeakers, an easy-to-build instruction pamphlet. Original list price £9.15.0.

OUR PRICE **£5.19.6** P. & P. 2/6.

AUTO-CHANGERS BRAND NEW OFFER

COLLARO 4-SPEED AUTO-CHANGER

Incorporating auto and manual control. Complete with Studio crystal p.u. and sapphire stylus. Plus 3/6 p. & p.

OUR PRICE

£7.19.6



MAINS TRANSFORMERS

M.T.1 250/250 80 mA, 19/6.
M.T.2 350/350 80 mA, 19/6.
M.T.3. 0/30 volts tapped, 19/6.
M.T.4 150 watt Auto Transformer, 19/6.
M.T.5. Battery Charger 4 amp., 19/6.
M.T.5a Battery Charger 1½ amp., 16/6

STANDARD ELECTROLYTICS

8 µF x 450 volt .. 1/8
8 x 8 x 450 volt .. 2/4
16 mf. x 450 volt .. 2/3
16 x 16 x 450 volt .. 3/6
32 µF x 450 volt .. 3/6
32 x 32 x 450 volt .. 5/6

SUB-MINIATURE CONDENSERS

All at 2/3 each

8 µF x 6 volt.
10 µF x 6 volt.
30 µF x 6 volt.
50 µF x 6 volt.
100 µF x 25 volt.

BARGAIN OFFER

90° 17" Tube by well-known manufacturer, Type CME/1702 (Substandard). Price **£5.19.6** (Callers only.)

WIRECOMP ELECTRONICS

378 HARROW ROAD, LONDON, W.9. TEL.: CUNNINGHAM 9530

Hours of business: 9 a.m.-6 p.m. Open all day Saturday.

THE LINEAR LI/10

A 10-WATT HIGH FIDELITY ULTRA LINEAR AMPLIFIER WITH INTEGRAL PRE-AMP

Full advantage has been taken of latest component miniaturisation developments to produce a 10-watt Hi-Fi push-pull amplifier incorporating tone control pre-amplifier stages within the measurements of 9 x 7 x 5 ins. In addition two high impedance input sockets are provided for microphone and gram., etc. With selector switch and vol. control, five B.V.A. valves are employed ECC83, ECC83, EL84, EL84, EZ81. H.T. and L.T. power supply point is included for a radio tuner.

FREQUENCY RESPONSE

± 1 db., 20-20,000 c.p.s.

MAXIMUM POWER OUTPUT

In excess of 14 watts.

SENSITIVITY

L.P. 220 m.v. for 10 watts, 78 r.p.m. 220 m.v. for 10 watts, Radio/Microphone 40 m.v. for 10 watts.

TREBLE LIFT CONTROL

+ 10 db. to -22 db. at 12,000 c.p.s.

BASS CONTROL

+14 db. to -10 db. at 50 c.p.s.

HUM LEVEL

Referred to maximum output and including integral pre-amp.—70 db.

NEGATIVE FEEDBACK

21 db. in main loop.



HARMONIC DISTORTION Less than 0.1% measured at 8 watts at 1000 c.p.s. Weight 10 lbs. Power consumption 90 watts. For 200-230-250 v. 50 c.p.s. A.C. mains. Outputs for 3- and 15-ohm speakers. Chassis finish stoved Gold hammer.

HIGHEST QUALITY ! Retail Price

MAXIMUM RELIABILITY !
AT A PRICE YOU CAN AFFORD.

13
GNS.

Send S.A.E. for descriptive literature.

TRADE ENQUIRIES to

Also Available—THE L.45. A compact High Quality 4.5 watt amplifier. Size approx. 7-5-5 1/2 in. high. Sensitivity is 28 millivolts so that the input socket can be used for either microphone or gram., tape, radio tuner, etc. B.V.A. valves used are ECC83 EL84, EZ80. Controls are: Vol. Treble and Bass with mains switch. The Tone controls provide full compensation for long playing records. Output matching for 3 ohm loudspeaker. Retail price £5/19/6.

THE LT45 TAPE DECK AMPLIFIER.

A complete unit (power pack and oscillator incorporated) ready for connection to A.C. mains. 3 ohm loudspeaker and practically any make of deck. Negative feedback equalization adjustment by multi-position switch for 3 1/2, 7 1/2 and 15in. per set. Retail price 12 gns.

DIATONIC 10-14 WATT. High Fidelity amplifier with integral pre-amplifier. Retail 12 gns.

CONCHORD 30 WATT. Hi-Fi amplifier with two separately controlled inputs. Retail 16 gns.

L3/3 STEREOPHONIC AMPLIFIER. Sensitivity 150 m.v. Output 3 watts on each channel. Retail 7 gns.

L5/5 STEREO AMPLIFIER. 5 + 5 watt. 12 gns.

LINEAR PRODUCTS LTD. ELECTRON WORKS, ARMLEY, LEEDS.

A television course for you to study at home

*Entirely new! Practical!
Bang up to date!*

THE FAMOUS BENNETT COLLEGE OFFERS YOU THIS

An entirely new course of study based upon up-to-date techniques has now been prepared by The Bennett College.

The course is non-mathematical, and contains clear diagrams, starting from the very beginning (even including the basic principles of sound radio receivers, if desired) and covering all that you need to know!

This is what you've been looking for! A home-study course includes: production

of the signal, scanning and reproduction of picture from signal. Aerials, types and purpose. The cathode-ray tube. Time-base oscillators, and output circuits. Synchronisation. Video frequency amplifiers. The TV tuner, turret, incremental, etc. Television test gear. Television faults.

For more details, fill in the coupon below. Your studies cost little, the book you need is included in the cost.

TO THE BENNETT COLLEGE (Dept. D104TV Sheffield)

*Please send me details of the new
TELEVISION SERVICING COURSE*

NAME

ADDRESS

AGE

REPANCO TWINETTE

A NEW REMARKABLE TWO TRANSISTOR PORTABLE RADIO FOR THE HOME CONSTRUCTOR

- ★ LOUDSPEAKER. 7 x 4in. ELLIPTICAL
- ★ TWIN FERRITE SLAB AERIALS
- ★ LONG AND MEDIUM WAVES
- ★ PROVISION FOR EXTERNAL AERIAL
- ★ SIZE 7 x 5 x 3in.
- ★ LOW BATTERY CONSUMPTION

Send now for Easy Wiring Plans and Component Price List. 1/6 (post free).

OTHER REPANCO EASY-TO-BUILD RECEIVERS

| | Envelope |
|-------------------------------------------------|----------|
| The R.E.P. One-valve Radio | 9d. |
| The Hiwayman. A 4-valve Portable Radio | 1/6 |
| F.M. Tuner Unit. 5 Valves plus Tuning Indicator | 1/6 |
| Three Dee. 3-transistor Radio | 9d. |
| Mini-3, 3-transistor Pocket Radio | 1/3 |
| Mini-7, Mk. II. 7-transistor Pocket Receiver | 1/6 |
| Transeven. 7-transistor Portable Receiver | 1/6 |
| Major-7, 7-transistor Portable Receiver | 1/6 |
| Transistor Car Radio Receiver | 2/- |
| Transistor Amplifier and Feeder Unit Circuits | 1/6 |


Please add towards postage.

For details of our Components send 6d. in stamps for our 1960 Catalogue.

Mail Order and Trade:
**RADIO EXPERIMENTAL
PRODUCTS, LTD.**
33 Much Park St.
COVENTRY
Tel.: 27114

Wholesale Inquiries and Export:
REPANCO, LTD.
O'Brien's Buildings,
203-269 Foleshill Rd.,
COVENTRY
Tel.: 24224

Open to Discussion

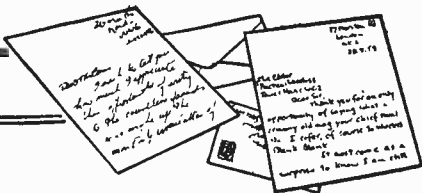

The Editor does not necessarily agree with opinions expressed by his correspondents.

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying commercial or surplus equipment. We cannot supply alternative details for receivers described in these pages. **WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE.** If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of cover.

Naval Amateur Radio Society

SIR,—It has been proposed by several serving, and ex Royal Navy amateur radio enthusiasts that a Society be formed to enable all those interested to keep in touch with old friends and to foster the Amateur Radio movement within the Royal Navy as a whole. Already a sizeable list of those eligible for membership has been compiled, but it is known that there are far more amateurs eligible who have not yet forwarded their names. Any serving, or ex member of the Royal Navy is eligible, who holds, has held, or hopes to hold an amateur radio licence. SWL's are also welcome. Anyone who is interested should contact either G8IX, 11 Dotteslow Street, Manley, Stoke-on-Trent, Staffs., or G3JFF, PO's Mess, H.M.S. Ganges, Shotley, Suffolk. Members of the Commonwealth Navies are also invited to forward their names and relevant details. If you know the names or call-signs of any other eligible hams please let us know, so that we can contact them. Please forward name, call-signs, home address, serving QTM (if any), rank/rate and official number along with brief details of rig, operating times and special interests.—M. T. MATTHEWS (G3JFF).

An Inexpensive T.R.F.

SIR,—After constructing "An Inexpensive T.R.F." (January 1960 issue) I found that the gain control was inadequate to control the overall gain of my receiver. This was attributed to the high gain of the 6K7 stage. I carried out a modification to the circuit as follows. I disconnected R3 both from the cathode and the "top" end of the potentiometer and connected it between the chassis and the bottom end of the potentiometer. The slider of the potentiometer I connected to the cathode of the valve (and C8 of course) and wired a 22k $\frac{1}{2}$ W resistor between the "top" of the gain control and the H.T. line. This 22k resistor is the only additional component required.—W. R. B. SPEAKE (Southbourne, Bournemouth).

Wow and Flutter

SIR,—My sympathies go out to G. Brian James (January issue) as I too abhor that most unpleasant rise and fall of a long sustained note

heard on some long playing records, a fault known technically as "wow". It can be due to many causes such as oversize record holes, eccentric or warped records, undersize or eccentric turntable pins, uneven turntable speeds or even poor recordings—fortunately rare occurrences these days. My experience however tends to suggest that it is almost always a problem of the record grooves not being cut concentrically with the centre hole, the pick-up therefore making its path across the record in a series of side swings to the aural distress of the discerning or musically minded listener. The simple remedy is very carefully to draw over the centre hole in the direction of maximum pick-up swing, using a fine round file, and taking repeated checks with the pick-up until little perceptible sideways movement is left. An arrow inked on the record label then indicates which end of the elongated centre to butt up against for future playing. This operation often has to be performed for both sides of the record as the pressing of one side never seems quite the same as the other.—J. C. WILLIAMS (Crawley, Sussex).

SIR,—I was interested to read of G. Brian James' experience with inconstant performance from a classical LP record. There are, of course, very many mechanical faults which can be associated with record players these days but I am assuming that since he refers to a Hi-Fi gramophone he must be using "transcription" equipment. On this assumption, he might transfer his attention to other physical properties of the disc itself. Is it really flat? Despite the fact that there is a British Standard Specification which defines within reasonable limits the tolerable distortion that a record may have when it leaves the factory. I have been obliged to return 12in. hi-fi records of a certain manufacture to the makers for replacement. In each case the disc was badly dished and in some cases warped. A warped record could, if torque were of a low order, cause inconstant performance. To a lesser extent, a dished record could produce similar effects since the stylus is tracking "on the side of a hill".—W. J. HUNTINGFORD (Guildford, Surrey).

27Mc/s Transmitter

SIR,—With reference to Mr. C. Goddard's letter concerning the 27Mc/s transmitter, the effect noticed may be due to one of two things happening.

If the receiver used for monitoring is a superhet, the 27Mc/s signal is probably overpowering the local oscillator in the superhet. If the I.F. of the receiver is 465kc/s, stations on 27 ± 0.465 Mc/s

will be heard. Only strong signals will break through, as the receiver's R.F. stages will be 465kc/s off the frequency of the station.

However, if the receiver is a T.R.F., one of the R.F. stages or detector is acting as a mixer, and signals will be heard on $27\text{Mc/s} \pm$ the frequency to which the receiver is tuned. Stations heard in this case will probably be in the long wave band.

There are probably more, similar, explorations but I have often noticed the effect in the first case myself. When monitoring signals from a top band transmitter, Radio Luxembourg can often be heard, no matter what frequency the receiver is tuned to, i.e. $1.86\text{Mc/s} - 0.465\text{Mc/s}$ (I.F.) = 1.4Mc/s .—J. BEDDOWS (Walsall).

Correspondents Wanted

SIR,—I would like to communicate with other readers interested in short wave radio and also tape recording. My recorder is a Grundig TK20. All letters and tapes will be answered.—D. B. HORGSON (21 Carline Road, Lincoln).

SIR,—I am 14 years old and would like to correspond by tape with other aspiring amateurs of my own age.—D. WILSON (Deepdene, 48, Godstone Road, Purley, Surrey).

SIR,—I am $13\frac{1}{2}$ years old and I have been interested in radio construction for about 5 years now. I would like to correspond with someone about my age.—R. PATON (183, Brampton Road, Carlisle, Cumberland).

Information Required

SIR,—Does any reader know where I could obtain some 6S7 valves. These are metal valves and used as R.F. and I.F. amplifiers in the Hammarlund H.Q. 120X? Also has any reader done any modifications of any sort on this receiver? I should be pleased to hear from anyone with information on this receiver.—SYDNEY BROWN (9, Roland Avenue, Nuthall).

SIR,—May I ask if your readers have any information on circuits, etc., for building a communications receiver with transistors using OC170 for R.F. and OC35 in class B?

I look forward to your magazine and have taken it for years. My interest now lies with transistors. It is a pleasure not having to carry heavy power packs, etc.—JACK BROOKES (1, Dean Street, Blackpool, S.S., Lancs.).

Aerial Tuning Unit

SIR,—Regarding the circuit of my Aerial Tuning Unit which was published in the previous issue, I would like to point out two things. Firstly, the unit is intended to match a high-impedance to a low-impedance aerial input, and if it is used with a receiver which has a high-impedance input, a mis-match will be the result. Those using ex-Government receivers may find the signals go up a great deal owing to the fact that many surplus sets have a low-impedance aerial input. Secondly, I have found that the circuit may be improved by not having the link winding joined to the rest of the circuit.—M. REYNOLDS (Nailsea, Somerset).

Satisfaction

SIR,—I wish to thank you for your very prompt reply to my inquiry about a hum when connecting an amplifier and a record changer. Your observation on the point of earthing both chassis was the one thing I had overlooked: when applied, the hum ceased. Thank you once again from a recent convert to hi-fi and also a new reader of PRACTICAL WIRELESS.—R. B. AVIS (Tonbridge).

Variometers

SIR,—In February, PRACTICAL WIRELESS Open to Discussion. Variometers were mentioned. Variometers in the early days of Wireless were the thing, one of the best tuners you could have. The coverage of the wavelength was small, compared with a variable condenser. To obtain the wavelength coverage many sets had a variometer together with a loading coil. The Dutch valve was a soft valve and rectified, without the use of a grid leak. It had a low vacuum. The soft type of valve was at that time gradually going out of use and the all-purpose hard valve came into use. The hard valve was as good for rectification as the soft, in conjunction with a grid leak. The Dutch valve had an H.T. in the neighbourhood of 22V. At that time, I bought one for the sum of 3s. 6d. and very good it was. Soft valves were generally very sensitive to filament control and it was frequently possible in those days to tune out an interfering station by judicious use of the filament resistance. Valves of this type are useless as low-frequency amplifiers.—B. J. LEE (Wimborne).

The "Old Days"

SIR,—I was somewhat amused by the majority of the statements made by Mr. A. Trowbridge in the March issue. Of course, amateur radio is not what it used to be—that goes for most things—and a good thing too! The situation would be odd if all of Mr. Trowbridge's wishes were current practice. We need modern components of the "solder-in" type, and as for the statement that every amateur does not own a soldering iron, anyone that has not taken the trouble to buy even a cheap, simple, "gas" iron should go back to bricklaying. Mr. Trowbridge is very much behind the times with knowledge of components—he quotes a capacitor as being "a plain roll covered in wax with wires sticking out of each end". Perhaps he should know that capacitor manufacturers today produce so many different types that they require large catalogues to illustrate them. As for requiring a pretty box to buy them in, whoever heard of such packing improving the performance of the component? I know too of the old metal-cored resistors—inefficient, noisy and have as much use today as an early car would be on the M1. The same goes for the old transformers—what monstrosities they were—the tuning capacitors "Delimiters"—inefficient then, and no use now.

No, Mr. Trowbridge, if you work on the old lines using modern components, your product would look like a bird's nest! Would it work? My guess is that whatever it was supposed to be, it would either oscillate or destroy itself in despair!—H. N. KIRK (Rotherham).

D.C. OSCILLOSCOPE

A.C. MAINS 200-250 VOLTS

SIMPLIFIED SERVICING
PROBLEMS WHEN USING
THE

'TESTGEAR' SCOPE


3in. D.C. OSCILLOSCOPE

Engineered to precision standards, this high-grade instrument is made available at the lowest possible price, incorporating the essential features usually associated with luxury instruments.

This "SCOPE" will appeal particularly to Service Engineers and Amateurs. A high gain, extremely stable differential

Y-amplifier (30 mV/C.M.). Provides ample sensitivity with A.C. or D.C. inputs. Especially suitable for measurement of transistor operating conditions where maintenance of D.C. levels is of paramount importance. Push-pull X amplifier; Fly-back; external use; pulse output available for checking TV Line O/P Transformers, etc.; Provision for external X I/P and CRT. Brightness Modulation. Size 10in. high, 6in. wide, 9in. deep. Wgt. 11½ lbs. £15.15.0. plus P. & P. 7/6, or 30/- deposit, plus P. & P. 7/6 and 12 monthly payments of 25/6.

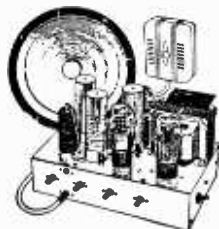FULL 12 MONTHS' GUARANTEE INCLUDING VALVES AND TUBE.



± 2 db; 4 db down to 20 K/c. Output 8 watts at 5% total distortion. Noise level 40 db down all hum. Output transformer tapped for 3 and 15 ohm speech coils. For use with Std. or L.P. records, musical instruments such as £4.19.6 p. & P. 7/6. Or 20/- deposit Plus P. & P. 7/6, and 4 monthly payments of 23/-.

8-WATT PUSH-PULL AMPLIFIER

COMPLETE WITH CRYSTAL MIKE AND 8in. LOUDSPEAKER

A.C. mains 200-250 v. Size 10in. x 6in. x 2in. Incorporating 6 valves. H.F. pen., 2 triodes, 2 output pens and rectifier. For use with all makes and type of pick-up and mike. Negative feedback. Two inputs mike and gram, and controls for same. Separate controls for Bass and Treble lift. Response flat from 40 cycles to 15 K/c..

± 2 db; 4 db down to 20 K/c. Output 8 watts at 5% total distortion. Noise level 40 db down all hum. Output transformer tapped for 3 and 15 ohm speech coils. For use with Std. or L.P. records, musical instruments such as £4.19.6 p. & P. 7/6. Or 20/- deposit Plus P. & P. 7/6, and 4 monthly payments of 23/-.

B.S.R. MONARCH UA8 WITH FUL-FI HEAD



4-speed plays 10 records 12in., 10in or 7in. at 16, 33, 45 or 78 r.p.m. Intermixes 7in., 10in and 12in. records of the same speed. Has manual play position; colour brown. Dimensions: 12in. x 10in. Space required above baseboard 4in. below baseboard 2in. Fitted with Ful-Fi turnover crystal head.

£6.19.6 Plus 5/- Postage & Packing.

With Stereo Head, £7.19.6, plus 5/- P. & P.


CHANNEL TUNER

Will tune to all Band I and Band III stations. BRAND NEW by famous manufacturer. Complete with PCCB4 and PCFB9 valves (in series) I.F. 16-19 or 33-38. Also can be modified as an aerial converter (instructions supplied).

Complete with knobs.

22/6 Plus 3/6 P. & P.

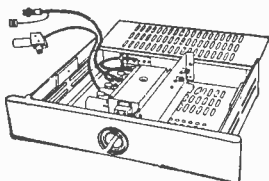
HEATER TRANSFORMER to suit the above. 200-250 v., 6/-, Plus 1/6 P. & P.



RADIO CHASSIS

A.C. MAINS 200/250 v. Medium & Long Wave Superhet-4 valve and rectifier. Complete with 8in. P.M. speaker Valve line-up 6K8, 6K7, 6G7, EL32 and rectifier. These have been used but fully serviced with new Electrolytics and valves. **FULLY GUARANTEED.** **42/6** Plus 7/6 P. & P.

SIGNAL GENERATORS

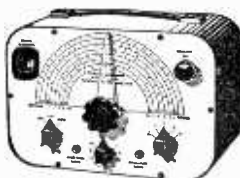


Cash £6.19.6 or 25/- deposit and 6 monthly payments of 21/6. Post and Packing 5/- extra.

Coverage 100 Kc/s-100 Mc/s on fundamentals and 100Mc/s to 200 Mc/s on harmonics. Metal case 10in. x 6in. x 5in., grey hammer finish. Incorporating three miniature valves and Metal Rectifier. A.C. Mains 200/250 v. Internal Modulation of 400 c.p.s. to a depth of 30%; Modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch, variable A.F. output. Incorporating magic eye as output indicator. Accuracy plus or minus 2%.

Cash £4.19.6 or 25/- deposit and 4 monthly payments of 21/6. Plus Postage and Packing 5/-.

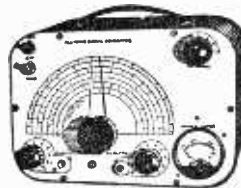Coverage 120 Kc/s-84 Mc/s. Metal case 10in. x 6in. x 4in. Size of scale, 6in. x 3in. 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30%; modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch variable A.D. output and moving coil output meter. Grey hammer finished case and white panel. Accuracy plus or minus 2%.




2-TRANSISTOR POCKET RADIO

Plus Germanium diode, fully tuneable over medium and long waves. Size 3in. x 4in. x 1in. Complete, set of components including case, 2 transistors and earpiece (less batteries).

19/6 Plus P. & P. 1/6.

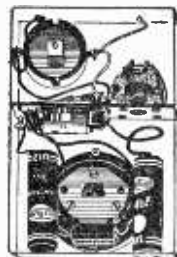Point to point wiring diagram 1/6, free with kit.



PUSH-PULL OUTPUT STAGE




Inclusive of transistors with input and output transformers to match 3 ohms speech coil, suitable for use with the above kit. Complete kit of parts including transistors.

19/6 Plus Post and Packing 1.6.

Point to point wiring diagram 1/6 free with kit

A.C./D.C. POCKET MULTI-METER KIT

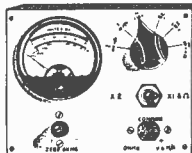

Comprising 2in. moving coil meter, scale calibrated in A.C./D.C. volts, ohms and milliamperes. Voltage range A.C./D.C. 0-50, 0-100, 0-250, 0-500. Milliamps 0-10, 0-100. Ohms range 0-10,000. Front panel, range switch, wire-wound pot (for ohms zero setting), toggle switch, resistor and rectifier. In grey hammer finish case.

19/6 Plus Built and tested P. & P. 1/6 7/8 extra.

Point to point wiring diagram 1/-, free with kit.

F.M. TUNER UNIT

By famous German Manufacturer. Coverage 88-100 Mc/s. Complete with ECC85. **25/-** Plus Size 4in. x 2in. x 2in. Circuit diagram 1/-, free with unit. 10.7 Mc/s I.F. and Discriminator Coil, 4/- pair.

RADIO & T.V. COMPONENTS (Acton) LTD.

23 HIGH STREET, ACTON, LONDON, W.3.

All enquiries S.A.E. Goods not dispatched outside U.K.

HOLIDAYS

PRACTICAL WIRELESS enthusiasts (and others) will enjoy a holiday at **RECVLER LODGE (PW)**, Bellinge, Kent.

RECEIVERS & COMPONENTS

TRANSISTORS—OC44. XA102, 12/6 each; OC71, 6/6; Brand new PL81, 10/6; PCL80, 9/6; EY86, 9/6; EY51, 9/6; post 6d. each. D. B. CARTER, 347, Ladypool Road, Birmingham 11.

TRANSISTORS. Free circuits given with each order. Example: 10 metre Rx Radio Contr. 1 Rx, TV Sig. Gen., for the amazing surface barrier types, SB305, 15/-, SB231 22/6, SB231 30/-, Also available with Circuits Normal Transistors, Sub-Minature Components, etc. A. R. TAYLOR, 24 Emore Road, London S.W.15.

WEYMOUTH and Wearite coils, all at half list prices, cannot be repeated. Valves used but guaranteed at 5/- each. B. JACKSON ELECTRICALS, Terminus Place, Eastbourne.

POWER IN PACKETS. Special Scoop! Brand new 426A(6) Control Units complete with 9 valves 6 xtals. Slow motion drives, dust cores, etc., packed in transit case and delivered, 33/6 each. Similar Unit 426A(1)—same as above but only 1 xtal, 24/6 delivered. You must not miss these two scoops—stamp for special leaflet. First come first served—delivery by R.R.S. 18 Set H.T.S. 10/9, most other types in stock—stamp for list. P.S. We guarantee you will purchase one of these Control Units when you have seen the leaflet—and you will be glad to purchase one by return, and what's more, even more pleased on examination of Unit. R. J. DIGGINS, 129/133 Radnor Street, Hulme, Manchester 15.

SPEAKER REPAIRS. Cones/Fields fitted. Clock Coils Wound. L.S. REPAIRS, Pluckley, Ashford, Kent.

ANNAKIN

PAMPHONIC HI-FI AMPLIFIERS, £15/15/- post free. **FANE SPEAKERS**, 3in. £3/15/-, 12in. £9, 15in. £18. New. Boxed. Post free. **PLESSEY SPEAKERS** 7in. x 4in. elliptical, 3 ohm. New, special price 17/6 ea. post 1/6. **AMPLIFIERS** No. 7787 (net audio) Has 3-IT4, 1—1L4, 1—CV2742, 2-diodes. Lots of other parts. Only 17/6 ea. post 1/9. **TRANSMITTER UNIT No.105A**. Has 2—CV63, 1—CV73 valves. Selector Drive Unit. Lecher lines, etc., etc. New. Boxed. A real bargain at 7/6 ea. post 3/3. **RECEIVER R4A-ARR2**. Has 7—9001, 3—6AK5, 1—12A6A. Dial is numbered 34-58. Less dynamotor. Used, outer case solid. Only £1 ea. post 3/3. **MAINS TRANSFORMERS**, 220-250V. In 220V, 25mA, 6.3V, 6.6A, 12/9 ea. post 1/6. **HEADSET HS-38**. Two earpieces (200 ohms). Cord Plug. No headband, 7/-, post 1/6. **MUIRHEAD EPICVCLIP DRIVE** and Knob. Cursor. No numbered dial. New, 4/- ea. post 11d. **RELAYS**, small U.S.A. 700 ohm. 2—CO, 3/6. Thermal Delay, vacuum type, 2-54V. New, 4/6. Sealed types, 670 ohm, 4-M, 4/6. Many other types. Post extra. **FROST WARNING THERMOSTATS**, low voltage, 1/6, post 7d. Mainland only. No Export. C.W.O. only. Send stamped addressed envelope for lists. — 25 ASHFIELD PLACE, OTLEY, YORKS.

RATES: 5/6 per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., Strand, London, W.C.2.

RECEIVERS & COMPONENTS

(continued)

"WEYRAD" TRANSISTOR RECEIVER

COMPLETE KIT—LONG & MEDIUM-WAVE PUSH-PULL O.P. £9/12/6
CONSTRUCTORS BOOKLET 2/-
Send S.A.E. for Shopping List.

WESTHAM RADIO SUPPLIES
Rear of 176, Abbotbury Road
WEYMOUTH, DORSET

CALLING 9IN. TELEVISION OWNERS—Brand new factory fresh 9in. Ferranti Tubes, originally £14/10/-, will replace Mazda, Brimar, G.E.C., etc., £4/10/- each; 6 months' guarantee. TOMLINS 127, Brockley Rise, Forest Hill, S.E.23.

MULLARD TUBES, reclaimed, 6 months guarantee. 9in. 30/-, 12-14in. 59/6, 17in. 79/6. All pictures tested. **FITTED FREE**. Picture shown to callers. Other makes types, cheap. Salvaged spares for modern and obsolete sets. Prices from: LOT 17/6. POT 7/6. Osc. Tr. 6/-, Mains tr. 10/-, Valves, 1,000 types in stock. EP91, EB91, 6J5, 2/6. EP80, 10F1, UF42, 3/6. Save money. Send a S.A.E. with enquiries or for free list. "ST. JOHN'S RADIO" 156 John's Hill, S.W. 11. (BAT9838).

5in. ELAC SPEAKERS, 9/6. 3ohm round, p.p. 1/6. 6in. 10/6, p.p. 2/-, 8in. 11/6, p.p. 2/3. £5 per doz. 7 day refund guar. If not satisfied. B. & E. SUPPLIES, 47 Middlehill Gate, Stockport, Cheshire.

50-WATT POWER AMPLIFIERS, rack mounting, input 200/250 v. A.C.: only 35/- (15/-), less valves, requires —MH4, 2—PX25, 1—5U4, 2in. **MILLIAMMETERS**, 2in. 0/1, 20/- (2/6). **TYPE 3 POWER UNITS**, de luxe model with 2 meters. 55/- (17/6 includes 10-returnable case). **MONITOR 56** (Indicator 248 and Power Unit 675), 28 (20/-). **VIRRA-PAKS** 6 v. D.C. to 250 v. 100 ma., smoothed. In case, 15/- (3/6). **MOTOROLA POLICE CAR TRANSMITTERS**, 30/40 mcs., F.M. 6 v. input, 10 valves, 30 watts, £12/10/- (12/6). **HC-859J TRANSMITTER RECEIVERS**, 6 1/2, or 24 v. input, with separate Power Unit, £12/10/- (15/-). **PLESSEY 6 TR. TRANSMITTER CABINETS**, open front for standard 19in. panels, full length rear door with latch, ventilated top and sides. £4/10/- (23/-). **R-201 BRIDGE UNITS** give C.O. output from Radio Receiver for teleprinters, undulators, etc., 230 v. input, £12/10/- (15/-). **DA-30 OUTPUT VALVES**, 20/- (1/-). **40IN. MOBILE WHIP AERIALS**, one piece, with loading coil in base effectively increasing length to 12ft..

SEND FOR 40-PAGE LIST OF OVER 1,000 DIFFERENT ITEMS.

American super finish. 35/- (5/-). **AMPLIFIERS AMERICAN**, 40/250 ohms input, 300 and 2,000 ohm output with 2-12J5 and 2-12A6: 28 v. input, with dynamotor, 9in. x 5in. x 5in., 20/- (5/-). Amounts in brackets are carriage England and Wales.

We have large quantities of "bits and pieces" and can probably help your needs. Please enquire—everyone answered.

P. HARRIS, Organford, Dorset

RECEIVERS & COMPONENTS

(continued)

DUD TRANSISTOR? Know for sure. Simple pocket tester 18/-, s.a.e. details: R. & E. LAMB, 17 Queens Road, London E.11.

RESISTORS—100 new, wire ended, assorted, all types, 7/6 box, post free. **COOK'S OF BEDFORD**, 29, St. Mary's St., Bedford.

COMPONENTS. Valves. Tubes, etc. Write or phone for free list. **ARION TELEVISION**, 4, Maxied Rd., Peckham. S.E.15. (New X 7152.)

FM-AM STEREO

Radiogram chassis—CB8

Paired output 6 watts Plain or Stereo Records. A hand-built quality unit with two speakers

ONLY £20.

BEL SOUND PRODUCTS CO., Marlborough Yard, London, N.19. ARC. 5078.

H.M.V. 15IN., English Electric 15in., Ultra, etc., Televisions, not working, originally £175 each, £5/10. **TOMLINS**, 127, Brockley Rise, Forest Hill, S.E.23.

VALVES FROM 1/6; all guaranteed. Radio. T/V Components. Lists 3d. **HAMILTON RADIO (W)**, 237, Sedlescombe Rd. N., Hastings.

RECLAIMED VALVES, tested and perfect; huge stocks; all one price. 5/-, plus 6d. postage each. Delivery by return. **LEWIS**, 57, Chalford Walk, Woodford Green, Essex.

TRANSISTORS 3/6. Test Prods w/ leads 1/6 pr. Small .01mf Micacs 6d. List 4d. **CARTER'S**, 578 Washwood Heath Road, Birmingham 8.

VALVES FOR OLD SETS, 1/- and 2/6 (tested, working). List stamp. 55, Charnminster Ave., Bournemouth. (Continued on next page)

KINGSLAND ELECTRONIC COMPONENTS

Stupendous Offers

HURRY—A Must—while stocks last: Set of 4 Files with Handles. Set of 13 Drills from 1/16-1/4. Set of 4-Piece, 2-way Screwdrivers in Plastic Cases, one Neon Mainstester, 6-piece Saw Set consisting of Hand, Tenon, Keyhole, etc., one Bench Vice. Barxian Price 21/-, P.P. 2/6.

FREE! Small Bench Vice OR Ratchet Screwdriver, with bargain pack consisting of: pair throat microphones, 50 assorted resistors, approx. 150 assorted screws, dial pointer, 20c. 2in. screened lead with sockets, one 5 Henry 250 mA. choke, two electrolytic condensers, knobs, toggle switches, Octal valve bases, vibrators, headphones, waveband switch, four Co-Ax. plugs, assorted coils, cartridge fuses, three potentiometers, WV multiplier, 24 assorted condensers, Festoon lamp and holder, coil PVC wiring-up wire.

All this for 35/-, p.p. 4/6.

100 ASSORTED CONDENSERS OR RESISTANCES OR 50-50, 10/-, p.p. 1/9. **HEADPHONES, LOW IMPEDANCE**, Ideal for Crystal Sets, etc., NEW, 4/6, p.p. 1/6.

SIX ASSORTED POTENTIOMETERS, 5/-, p.p. 1/6.

Open Saturday until one o'clock. Personal callers welcome.
182 KINGSLAND RD., SHOREDITCH
E.2. Tel. SHO 6572. Sorry, U.K. only.

RECEIVERS & COMPONENTS

(continued)

BENDIX RECEIVERS RA-10. 4-band superhet. 150ks/s-10Mc/s. 8 valves; 6SK7-R.F.; 6K8-Mixer; 2-6SK7-I.F.; 6BT-sec. det.; 6C5-BFO; 6K6-OP. 6H6-diode. Built-in P.U. 24V. Clean. Size 6 1/2 in. x 15 1/2 in. Easily converted to mains as described on p. 453 Sept. 1957 "P.W." £4, p.p. 10/-.

AMERICAN RT-37/PPN-2 lightweight portable Tx-Rx 214-238Mc/s, brand new composed of Tx-Rx (9 valves: 5-3A5; 3-1S5; 1-1R5); built-in 2V. Vibrator Pack: square vibrator; head-set; connector leads; 10ft collapsible aerial; instr book. £3/15/-, p.p. 7/6.

CRYSTAL FILTER UNITS, HRO 455kc/s with crystal set and phasing controls, new, boxed. £1, p.p. 2/-.

E.W.S. CO., 69 Church Road, Moseley, Birmingham 13.

RECOVERED SPEAKER bargains. 5in., 6in., 8in., 7in. x 4in. 5/-, p.p. 2/6. All guaranteed. **J. R. CALVERLEY & CO. LTD.,** 130 Water Street Radcliffe, Lancs.

TRANSISTORS: OC71/72, 12/6 each; OC44, 15/- each; OC72, matched pairs, 24/-; return of post service. **A. W. WARD,** 142, Railton Rd., London, S.E.24.

MISCELLANEOUS

SMALL QUANTITY engraving on Taffylete for Radio Nameplates, etc. Quotations by return. **C. D. BRANDON,** White Ho, Hr. Denham.

YOU READ MUSIC?

Then how about making yourself an electronic organ? Constructional data available—full circuits, drawings and notes. It has 5 octaves, 2 manuals and pedals with 24 stops—uses 4 valves. With its variable attack you can play Classics and Swing.

Write NOW for free booklet and further details to **C. & S., 20, Maude Street, Darlington, Durham.**

MAKING YOUR OWN TELESCOPES.

Enlargers. Projectors. Viewers. Microscopes. Episcopes, etc., then our booklets "How to Use ExGov. Lenses and Prisms." Nos. 1 and 2 at 2/6 ea. will show you easily and quickly how to achieve the finest possible results at lowest possible cost. The most comprehensive lists of optical and scientific equipment in the British Isles is free for s.a.e. **H. W. ENGLISH, Rayleigh Rd., Hutton, Brentwood, Essex.**

PROTECT YOUR CAR AT NIGHT

"LITON"

PHOTOELECTRIC
PARKING LIGHT
SWITCH

will switch your lights on at dusk—off at dawn, automatically, while you are at work, in bed, or away from home. Controlled by light. Transistorised. Avoid accidents, fines. Save your battery.

**KIT OF PARTS, 52/6
BUILT AND TESTED, 57/6**
Pat. Pending. Send 6d. stamp for pamphlet.
"St. John's Radio," 156 St. John's Hill, S.W.11. **BATersea 9838**

FOR SALE

SATISFACTION ASSURED. — 12in. Televisions £9/10/-, 14in. £16, 17in. £19/10/-. Write for quotation, stating requirements. We guarantee satisfaction. **TOMLINS,** 127, Brockley Rise, Forest Hill, S.E.23.

BLANK CHASSIS
MADE TO ORDER
SAME DAY SERVICE

Metalwork Dept.

H. L. SMITH & CO. LTD.

287-289 Edgware Road, London, W.2.

PAD. 5891-7595.

100 BAYS of brand new adjustable steel Shelving, 72in. high x 34in. wide x 12in. deep; stove enamelled, dark green; sent unassembled; 6-shelf Bay, £3/15/-; sample delivered free; quantity discounts. **N. C. BROWN, LTD.,** Eagle Steelworks, Heywood, Lancs. (Tel.: 69018.)

SUB-MINIATURE SOLDERING
INSTRUMENTS

Ultra-lightweight—only 1/2 oz.! The most efficient tool for all Transistor and other delicate soldering. 6 volt 9 watt. 10/6 post free, or with isolating transformer for A.C. Mains, 14/6 plus 1/9 p. & p.

KENNETT & COMPANY

Doe Park, Denholme, Yorks.

Trade enquiries invited.

ASTOUNDING VALUE.—9in. Televisions 45/-, 12in. Televisions 70/-, 14in. £9/10/-, 15in. £15/10/-. Complete but not guaranteed working, as received in part exchange. **TOMLINS,** 127, Brockley Rise, Forest Hill, London, S.E.23. All famous makes available, carriage 7/6.

NEW
DESIGNS IN
STEREO
GRAM
CABINETS

Write for new list 'S'

A. L. STAMFORD

LTD., Dept. N.29,

84 Weymouth Terrace,

London, E.2.



GP59 16 Gns.

WANTED

A PROMPT CASH OFFER for your surplus Brand New Valves, Speakers, Components, Test Instruments, etc. **R.H.S.,** 155, Swan Arcade, Bradford, 1.

URGENTLY REQUIRED, new Radio, Television or Industrial Valves. Also old and obsolete types. Cash prices offered for any quantity. Write, call or phone: **MIT 6202, 201, Streatham Rd., Mitcham, Surrey.**

ALL TYPES of Valves wanted, PL81, ECL80, EY51, U25, PCF80, P230, U801, etc., etc., best cash price by return. **STAN WILLETT'S,** 43, Spon Lane, West Bromwich, Staffs. (Tel.: WEST 3392.)

WANTED. Service Sheets and Manuals. No quantity too large, or too small. Highest prices paid. **SULTAN RADIO,** 2 Stanley Road, Tunbridge Wells, Kent.

WANTED

(continued)

WANTED VALVES

All types for prompt cash. Must be new. State quantity.

WILLIAM CARVIS LTD.

103, North Street, Leeds, 7.

SERVICE SHEETS

SERVICE SHEETS.—Huge stock at 4/- ea. List 1/-. Immediate delivery. **GLOBE SUPPLIES,** 33 Fairfield Close, Sidcup, Kent.

FAULTFINDER FILES (TV), showing common faults that each receiver is prone to, and other useful servicing information. 2/- ea. List 9d., plus postage. **S. P. DISTRIBUTORS,** 11, Old Bond St., London, W.1.

SERVICE SHEETS (trade type).—TV 4/-, Radio 3/-. List 1/-. All orders dispatched on day received. C.O.D. if desired. Also Manuals for sale and hire. **SULTAN RADIO,** 2 Stanley Road, Tunbridge Wells, Kent.

38 SET WALKIE TALKIE

CIRCUIT INFORMATION

Alignment Procedure. Typical faults in Ex W.D. Sets. Component location diagrams. Circuit diagram. Complete Circuit description. Instructions for use, etc. P.O. 5/-. Address in block capitals, please.

CAMPBELL

Laundry Lane, Hungerford, Berks.

SERVICE SHEETS. — We have the largest stock of Radio and TV Service Sheets in the country for sale at 4/- ea. Why tolerate delay in obtaining your supplies when we will dispatch by return? Also Manuals for sale and hire. Service sheet list 1/-. Manuals list 9d. S.A.E. please. Mail orders only. **S.P. DISTRIBUTORS,** 11 Old Bond Street, London, W.1.

SERVICE SHEETS, Radio, T.V., 5,000 models. Lists 1/-. S.A.E. enquiries. **TELRAY,** 11, Maudland Bk., Preston.

SERVICE SHEETS

RADIO and Television

Over 100,000. S.A.E. for List. Large stock of obsolete Radio and Television Valves.

JOHN GILBERT RADIO

20, Extension

Shepherd's Bush Market, London, W.12
SHE 3052

SERVICE SHEETS for sale, all types, from 1/-. Free fault-finding guide with all service sheets. 100 T/V Service Sheets covering 330 popular models, 18/6. Radio, T/V, Electronic. Books; s.a.e. lists/enquiries. **HAMILTON RADIO (W),** 237, Sedlescombe Rd., N., Hastings.

(Continued on next page)

SOUND RECORDINGS

TAPE/DISC/TAPE transfer, 1,800ft. new L.P. Tape, 32/6. Unimixer Mixing Units for quality. **SOUND NEWS**, 10 Cliford St., London, W.1.

SITUATIONS VACANT

STUDY RADIO, TELEVISION AND ELECTRONICS with the world's largest home study organisation—**I.C.S.** Courses for the enthusiast and for those seeking examination qualification. **Brit.I.R.E.**, City and Guilds, **R.T.E.B.**, etc. Build your own equipment with **Practical Radio Course**. Write today for Free book: **INTERNATIONAL CORRESPONDENCE SCHOOLS**, Intertext House, Parkgate Rd. (Dept. 541A), London, S.W.11.

T/V AND RADIO, **A.M.Brit.I.R.E.**, City and Guilds, **R.T.E.B.**, Cert., etc., on "No pass—no fee" terms. Over 95% successes. For details of Exams and Courses (including practical apparatus) in all branches of Radio, T/V and Electronics, write for 148-page handbook, free. **B.I.E.T.** (Dept. 242G), 29, Wright's Lane, London, W.8.

SITUATIONS VACANT

(continued)

OVERSEAS Oil Exploration Company with world-wide seismic parties, offers permanent career to Electronic Technicians. Work consists in maintaining and operating electronic recording equipment under field conditions. Live generally in camp. Qualification: **H.N.C.** or equivalent essential, with practical experience in electronics. Home leave every 2 years. Box No. 24.

A.M.I.Mech.E., **A.M.Brit.I.R.E.**, City and Guilds, **G.C.E.**, etc., bring high pay and security. "No pass—no fee" terms. Over 95% successes. For details of exams and courses in all branches of Engineering, Building, Electronics, etc., write for 148-page handbook, free. **B.I.E.T.** (Dept. 242B), London, W.8.

CITY AND GUILDS (Electrical, etc.), on "No pass—no fee" terms. Over 95% successes. For details of Electrical Engineering, Applied Electronics, Automation, etc., send for our 148-page handbook, free and post free. **B.I.E.T.** (Dept. 242A), 29, Wright's Lane, London, W.8.

EDUCATIONAL

INCORPORATED Practical Radio Engineers home study courses of radio and TV engineering are recognised by the trade as outstanding and authoritative. Moderate fees to a limited number of students only. Syllabus of Instructional Text is free. The "Practical Radio Engineer" journal, sample copy 2/-, 6,000 Alignment Peaks for Superhets, 5/9. Membership and Entry Conditions booklet, 1/-, all post free from the **SECRETARY, I.P.R.E.**, 20, Fairfield Road, London, N.8.

WIRELESS. See the world as a Radio Officer in the Merchant Navy; short training period; low fees; scholarships, etc., available. Boarding and Day students. Stamp for prospectus. **WIRELESS COLLEGE**, Colwyn Bay.

LEARN RADIO AND ELECTRONICS the new practical way! Hosts of absorbing experiments carried out at home under expert guidance to teach you Radio in a new, enjoyable and interesting way. Construction, servicing and fault finding on equipment made easy for the first time! No previous experience needed. No mathematics used. Free brochure from: Dept. 11 **P.W. RADIO-STRUCTUR**, 40, Russell St., Reading, Berks.

LEARN-AS-YOU-BUILD Course in basic radio, electronic and electrical theory with practical training building a 4-valve TRF and 5-valve superhet radio receiver; Signal Generator and High-quality Multi-tester. Write for free book: **INTERNATIONAL CORRESPONDENCE SCHOOLS**, Intertext House, Parkgate Road (Dept. 541), London, S.W.11.

★ LEARN ★ RADIO & T/V SERVICING for your OWN BUSINESS/HOBBY

● by a new exciting no-maths system, using practical equipment, recently introduced to this country.

FREE Brochure from:—

RADIOSTRUCTOR

DEPT. G77, 46, MARKET PLACE,
READING, BERKS. 4/60

BOOKS & PUBLICATIONS

BOOKS for C. and G. exams: Tels. Principles, A and B, 9/6; Tels. (Principles), 1 and 2, 10/6; Maths for Tels., 1, 7/-; Maths for Tels., 2, 5/-; all post free. **RIDDIFORD**, 384, Tilehurst Rd., Reading.

ASTRAL RADIO PRODUCTS

'HOME RADIO,' 32-page illustrated booklet. Simple wiring instructions for Crystal Set, 1, 2, 3 Valves, 2/-, post 3d. **TRF COILS**, 7/-, pr., post 6d. **DUAL WAVE HF** Coil with **REACTION**. Specified for 'Summer All Dry Portable', 'A.C. Double Triode 1' etc., 4/6, post 3d. **IFT's** Miniature, 1" x 1 1/2" x 2 1/2" in cans. Extra high 'Q'. Special offer, 9/-, pr., post 6d. **Crystal Set Coils**, L. & M.W. 2/3, post 3d. **82 Centurion Road, Brighton**

APPOINTMENTS

WANTED 677 Trainee Engineers

The Electricity Supply Industry has vacancies this year for 677 recruits to its engineering training schemes. They are required both by the Central Electricity Generating Board and by the 12 Area Electricity Boards.

83 university graduates are needed as graduate trainees. They should possess a degree in electrical or mechanical engineering of a British university.

73 technical college graduates are required as engineering trainees. They should possess a Diploma in Technology, a College Diploma, a Higher National Diploma or a Higher National Certificate in electrical or mechanical engineering.

521 school-leavers are needed as student apprentices. There are two levels of entry: for those who possess a good Ordinary level **G.C.E.**, including passes in maths and science, and for those who have taken **G.C.E.** at "O" level and have also obtained passes in maths and physics at Advanced level.

Training for university and technical college graduates is by means of a planned two-year course of practical experience,

satisfying the requirements of the professional institutions.

Training for school-leavers is by means of a five-year apprenticeship, including day-release or a Sandwich Course, leading to a professional engineering qualification.

On satisfactory completion of training, all trainees are guaranteed employment in this essential, expanding industry. A wide range of careers is available in many types of engineering—generation, transmission, distribution, commercial and research. Because the demand for electricity doubles every ten years, the prospects of promotion are good.

For further information write to:

**The Education and Training Officer,
The Electricity Council,
155 Winsley Street,
London, W.1**

LASKY'S RADIO

CONSTRUCTOR PARCELS

Circuit Diagram and building instructions,
1/6 each, post free.

New 7-Transistor Pocket S/Het.

Complete Parcel £7.19.6, post 3/6.

4-Valve S/Het. Portable

All-dry Battery, complete parcel,
7 gns. Mains/Battery £8.19.6, post 3/6.

Midget T.R.F. (A.C. mains)

Complete Parcel, 99/6, post 5/-.

SEND FOR OUR 100-PAGE Components Catalogue

Price 2/-, Post 6d.

With latest 12-page Bargain Bulletin
free.

LASKY'S LATEST! TAPE RECORDER KITS!

Look at these star features:

- ★ Very latest Printed Circuit.
- ★ T.C.C. Condensers.
- ★ Amplifier can be supplied fully assembled and connected to Deck.
- ★ New Mullard Valves, EF86, ECC83, EL84, EM34 magic eye, EZ80 rect.
- ★ Choice of Speaker, 7 x 4in., 8 x 5in., 9 x 4in., 6in., 8in., etc.
- ★ Collaro Studio or B.S.R. Monardeck Tape Deck.
- ★ Complete with Acos 39/1 Mike, Tape and Spool.
- ★ Choice of Carrying Cases.

20 Gns.

☐ (B.S.R. Deck)

Prices from

25 Gns.

(Collaro Deck)

All components available separately.

Full details and shopping list post free on request.



LASKY'S CAR RADIO

CAN BE BUILT FOR
£12.19.6

using all brand new components and complete with 7 x 4in. elliptical speaker.

- ★ 12 v. operation.
- ★ New hybrid circuit.
- ★ 5-valve Superhet with Transistor.
- ★ New Brimar Valves.
- ★ Low consumption, 1.5 amp
- ★ No vibrator. 12 volt H.T. and L.T.
- ★ T.C.C. Printed Circuit and condensers.
- ★ Tuned R.F. stage.
- ★ Med. and long waves.
- ★ Permeability tuning.
- ★ Small size, 7 x 2in. Fits any car.

Instruction booklet giving full details, circuit diagram, etc. 2/6, post free (returned if you order.)

207 EDGWARE ROAD, W.2

Five yards from Praed Street.

PAD 3271/2 and CUN 1979.

42 TOTTENHAM COURT RD., W.1

Nearest Station: Goodge Street.

MUSEUM 2605.

Both addresses open all day Saturday.

Close 1 p.m. Thursday.

All Mail Orders to: Lasky's (Harrow Rd.) Ltd., Dept. PW, 207 Edgware Rd., London, W.2.

Convert to STEREO REALISM!

... for only £4.19.6 plus cost of second loudspeaker

The "Symphony" STEROPHONER has caused a bigger stir! in the Press and the Trade than even we anticipated. Many are wholeheartedly enthusiastic. Some remain unconvinced. And some hold grimly to the opinion that it is impossible!

But in audio matters, hearing is believing, and the facts are that while argument rages, more and more people every day are hearing the STEROPHONER for the first time, believing the evidence of their own ears, and even writing, uninvited, to tell us how pleased, delighted and astonished they are with results!

The "Symphony"

STEROPHONER

... gives a new realism and presence FROM ANY MONAURAL SOURCE HI-FI AMPLIFIER TAPE RECORDER, RADIO, RADIOGRAM. Satisfaction guaranteed. No maintenance required—last indefinitely.

Price only £4.19.6 plus postage 2/6
(C.O.D. 2/- extra, U.K. only)

Overseas £5.10.0 or \$16.00 post paid.

For illustrated literature, reviews, reports, etc., send us a postcard mentioning this magazine.

Accredited dealers required for closed territories throughout Gt. Britain.

NORTHERN RADIO SERVICES (LONDON) LTD.

11 KING'S COLLEGE ROAD, SWISS COTTAGE, N.W.3

Telephone: PRImrose 3314

SOLDERING EQUIPMENT

BY



PRECISION SOLDERING INSTRUMENTS for the ELECTRONICS INDUSTRY

- Comprehensive range
- Robust & Reliable
- Light weight
- Rapid heating
- Bit sizes 3/32in. to 7/16in
- 'Permagit' or Copper bit/c
- All voltage ranges 27v to 30/240v
- Prices from 19/6

Illustrated is the 25w. 3/16in. replaceable bit model with safety shield.

British and Foreign Patents. Registered designs. Suppliers to H.M. and Foreign Governments. Agents throughout the world.

Brochure No. S.10 sent free on request. Sole proprietors and manufacturers:

LIGHT SOLDERING DEVELOPMENTS
LIMITED

28, Sydenham Road, Croydon, Surrey.

Phone: CROydon 8589 Grams: Litesold Croydon



Let I.C.S. train YOU!

COURSES ON:—

- RADIO and TELEVISION
- SERVICING • ELECTRONICS


EXAMINATION COURSES FOR:—

- **C. & G. Radio Servicing Certificate** (R.T.E.B.)
 - **C. & G. Radio Amateurs' Exam.** (Amateurs' Transmitting Licence)
 - **British Institution of Radio Engrs., etc. C. & G. Telecom Technicians.**
- Whether you plan to have your own business, to become an electronics engineer or to take up a career in industry, an I.C.S. Course will help you to succeed. You learn at home in your own time, under expert tuition. Moderate fees include all books.


LEARN-AS-YOU-BUILD

Practical Radio Course

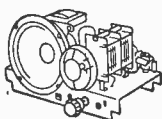- A basic course in radio, electronic and electrical theory backed by thorough practical training. You build a 4-valve T.R.F. and a 5-valve superhet radio receiver, signal generator and multi-tester.
- Other Learn-as-you-Build radio courses are available



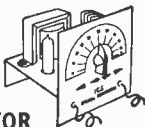MULTI-TESTER
(Sensitivity 1,000 ohms per volt)



5-VALVE SUPERHET RECEIVER

RF/AF SIGNAL GENERATOR

Post this Coupon TODAY! for FREE book on careers in Radio, etc., and full details of I.C.S. Courses.

INTERNATIONAL CORRESPONDENCE SCHOOLS

(Dept. 171J), Intertext House, Parkgate Road, London, S.W.11.

Name (Block Letters please) Age

Address

Occupation 4-60

INTERNATIONAL CORRESPONDENCE SCHOOLS

Special Bargain Offers

AVOMETER MODEL 'D' 34 range testmeter. D.C. volts to 1,500 v. (10 ranges). A.C. volts to 1,500 v. (8 ranges). D.C. current to 30 A (8 ranges). A.C. current to 15 A (6 ranges). Ohms 0-1 k, 0-10 k. A robust instrument with 5in. mirror scale and cut out. With battery and leads. Guar. £8.19.6. Post 3/6.

FERRANTI TESTMETER TYPE Q. An extremely compact self-contained multimeter. Volts 0 to 30, 150, 600 AC/DC, with additional 0.3 v. DC and 0-15 v. AC. ranges: milliamperes 0 to 7.5, 30, 150 and 750 DC; ohms 0-25 K Ω . Accuracy BSS first grade. Knife-edge pointer and clear calibrated 2 1/2 in. scale. 500 Ω /volt. With leads, prods, battery and instructions. In fitted velvet-lined 4 x 7 x 3 in. case. Brand new condition, tested. 52/6, post 2/6.

ADVANCE SIGNAL GENERATORS. Type 20. Ex-Govt. These fine instruments cover 100 Kc/s to 30 Mc/s in 6 bands. Mod. R.F. C.W. and 400 cps audio outputs are provided. Individual charts are missing but guidance charts will be provided. A.C. Mains. Not new but in good cond. & wkg. order. As only a limited no are available CALLERS ONLY. £5.10.0.

Q5'er. (BC-453 Command Receiver). Covers 190-550 Kc/s (IF 85 Kc/s). Ideal for double superhet conversion, etc. Supplied BRAND NEW in original cartons, with all 6 valves and CIRCUIT, 89/6. Post 3/6. **R-1155-B.** with latest drive, first-class condition. £7.19.6. **R-1155-L.** £12.19.6. Power Packs. £6.10.0. S.A.E. details. **CR100 COMMUNICATION RECEIVERS.** Covers 80 Kc/s—30 Mc/s in 6 bands. 11 valves. 2 R.F. and 3 I.F. stages. Variable BFO, etc. Ready for 200-250 v. A.C. mains 21 watts output for 3 ohms speaker. **SUPERB CONDITION and OUTSTANDING PERFORMANCE for ONLY £21.** S.A.E. for illustrated details. **HRO COMMUNICATION RECEIVERS,** complete with 9 coils. From 18 kns. S.A.E. for full particulars.

RCA AR-88 SPEAKERS. 30 8in. P.M. speaker in heavy gauge black cracked steel cabinet 11 x 10 x 6 in. with rubber feet. A **SUPER QUALITY** unit. BRAND NEW, for ONLY 45/- Post 3/6.

MINIATURE 373 I.F. STRIPS.—For F.M. tuner described in P.W., With 3 of EP91, 2 of EP92 and EB91. A fresh release enables us to offer these once again. BRAND NEW with circuit and full P.W. Reprint. 35/- OR less valves. 12/6. Post either 2/6. **MOVING COIL PHONES.**—Finest quality Canadian, with Chamois ear-muffs and leather-covered headband. With lead and jack plug. Noise excluding, supremely comfortable, 19/6. Post 1/6. **R.F. UNITS.** R.F.26, 17/6; R.F.27, 22/6. Good condition. Post each 3/6.

PLEASE ADD POSTAGE OR CARRIAGE ON ALL ITEMS

CHARLES BRITAIN (RADIO) LTD.

11 Upper Saint Martin's Lane, London, W.C.2

TEMPLE Bar 0545

Shop Hours 9-6 p.m. (9-1 p.m. Thursday). Open All Day Saturday.

RADIOGRAM CHASSIS

by famous manufacturer

Chassis 16 1/2 x 6 1/2 x 7 in. high. Dial in red, gold and brown. 18 x 4 in. 1000-2000M; 200-550M and 6-18Mc/s. 4 knobs in front. Ferrite rod aerial; Tone control; Ext. L.S.; P.U.; Ae and E sockets. Gram. mains socket 200-225 v. and 226-250 v. A.C. Valves ECH81, EBF80, ECC83, two EL84 in push-pull. GZ30 rect. Fine value for money at £7.10.0 (7/6 carr.).

A cheaper Radiogram Chassis for £6.10.9 (7/6 carr.). Chassis 16 1/2 x 5 1/2 x 6 in. high. Dial in gold and brown 15 1/2 x 4 1/2 in. 4 knobs, two at each end. Tone; ext. L.S.; P.U.; Ae; Earth. Valves E240, ECH42, EF41, EL41, EBC41. Also by the manufacturer of above chassis.

Cossor Battery Eliminator for 35/- (2/6 post). 90 v. at 12mA and 1.4 v. at 125mA. In two units to take the place of existing batteries.

COMPLETE V.H.F./A.M. RADIO FOR £12.12.



Brand new set, in superb walnut cabinet (size 19 x 8 1/2 x 14 1/2 in. high). Covering 80-100 Mc/s, 16-49 M., 200-500 M. and 1,200-2,000 M. Mains trans. 200-250 v. with 3 tappings. Ferrite rod aerial for A.M. Controls: volume on/off, tone, tuning, w/change. Gram. and ext. speaker position provided. Fully guaranteed. Post and packing 10/- extra. Terms: £3.12.0 down (inc. carr.) and 5 monthly payments of £2. Indoor V.H.F. aerial 10/- extra, cash.

UNIC SHAVERS LTD.,

25 Wordsworth Road, Worthing, Sussex

MAXI-Q

HOME CONSTRUCTOR CHASSIS SERVICE

Our chassis are made with new 16 s.w.g. heavy duty bright aluminium. Front Panels in 19 s.w.g. Steel with attractive Hammered Gold finish and clearly marked with neat control positions; all finishes and construction are made to enable constructors to match one unit with another.

MULLARD CHASSIS

| | |
|----------------------------------------------------------------------------------------------------|------|
| "5-10" Amplifier Chassis, Base, Screen and Screws | 19 6 |
| "5-10" Slim Line Chassis, without control positions, complete with Base and Screws | 19 6 |
| Complete Metalwork for the "5-10" T.C.C. Printed Circuit | 15 0 |
| Type "A" Pre-amplifier Chassis and Front Panel (unprinted) | 8 6 |
| Type "B" Pre-amplifier Chassis and Front Panel (unprinted) | 12 6 |
| 2 Valve Pre-amplifier Chassis complete with printed Hammered Gold finished Front Panel and Screws | 16 6 |
| 3 Valve Pre-amplifier Chassis, complete with printed Hammered Gold finished Front Panel and Screws | 19 6 |
| 3 Valve "3 Watt" Hi-Fi Amplifier Chassis | 10 6 |
| "20 Watt" Amplifier Chassis, Base, Transformer Covers, Transformer Adaption Plate and Screws | 68 6 |
| "20 Watt" Pre-amplifier Chassis | 25 0 |
| Mullard Tape Recorder Type "A" Amplifier Chassis | 31 6 |
| Mullard Tape Recorder Type "B" Amplifier Chassis | 31 6 |

| | |
|---------------------------------------------------------------------------------|------|
| Mullard Tape Recorder Type "C" and New Type "C" Amplifier Chassis | 32 6 |
| Mullard Tape Recorder Power Pack Chassis | 11 6 |
| "7 Watt" Stereophonic Amplifier Chassis, Printed Front Panel and Screws | 24 6 |
| 3 Valve Stereophonic Amplifier Chassis and Printed Front Panel | 22 0 |
| Stereophonic Pre-amplifier Chassis, Printed Front Panel and Screws | 24 6 |
| Mullard "7 Watt" D.C./A.C. Amplifier Chassis with Paxolin and Bracket | 20 0 |
| Four-Channel Input-Mixing Pre-Amplifier Chassis, Printed Front Panel and Screws | 18 6 |

NOTE.—Transformer holes are not drilled in the above Chassis excepting for the "20 Watt" Amplifier.

MULLARD FRONT PANELS

| | |
|-------------------------------------------------------------------------------------------------------|------|
| Type "C" Tape Pre-amplifier with EM81 Escutcheon Cut-out, 11½ x 4½in. | 8 0 |
| "5-10" Amplifier, 15 x 5in. | 7 6 |
| Type "A" Pre-amplifier, 4½ x 2½in. | 2 6 |
| Type "B" Pre-amplifier, 10½ x 2½in. | 3 6 |
| WF1388 Push-pull Bias and Erase Tape Deck Oscillator Coil for the Mullard Type "C" Tape Pre-amplifier | 29 6 |
| Treble Lift Inductor for the Mullard Type "C" Tape Pre-amplifier | 22 6 |

GENERAL CATALOGUE covering full range of components; send 1/4 in stamps or P.O. PLEASE SEND S.A.E. WITH ALL OTHER INQUIRIES.

DENGO (CLACTON) LTD. (Dept. P.W.), 357/9 Old Road, Clacton-on-Sea, Essex

FIRST-CLASS RADIO COURSES . . .

GET A CERTIFICATE!

QUALIFY AT HOME—IN SPARE TIME

After brief, extremely interesting study—undertaken at home in your spare time—**YOU** can secure your professional qualification. Prepare for **YOUR** share in the post-war boom in Radio. Let us show you how!

—FREE GUIDE—

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success-compelling qualifications as **A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs, Exams., Gen. Cert. of Educ., London B.Sc. (Eng.), A. M. I. P. E., A. M. I. Mech. E., Draughtsmanship** (all branches) etc., together with particulars of our remarkable Guarantee of

SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER 150,000 SUCCESSES.

NATIONAL INSTITUTE OF ENGINEERING
(Dept. 461), 148, HOLBORN, LONDON, E.C.1.

S. Africa: P.O. Box 8417, Jo'burg.
Australia: P.O. Box 4570, Melbourne

PADGETTS RADIO STORE

40, MEADOW LANE, LEEDS, 11
Tel.: Cleckheaton 2886

Special Valve Offer. NEAV EB91, EF91, EL91. All at 3/- each. Post free.

Twelve-inch TV Sets for all BBC Stations. Less tube, but otherwise complete, 45/- carr. 7/6. Good tubes, 30/- carr. 7/6. Bush, Pye, Ekco, Ultra, etc. only the best.

Speakers from TV Sets. Best makes only. 7 x 4in., 10/-; 8in., 6/6; 8in., 6/6. Post 2/6. Remember a good second-hand one is a better buy than a cheap new one.

1154 Transmitter. Model M. four wave-band. Good condition. Complete with Valves and Meters. 16/- carr. 12/6.

Tube Unit BC929A. Complete with a good tube 3BP1 (guaranteed). Less Valves. Switch, Motor and 500 cycle transformer. Store soiled, 15/- carr. 8/-.

Ultra 14in. TV. Models 815 and 915. BBC-TV. Perfect results, and sold with a money back guarantee, £12 only, carr. 17/- Tube in separate carton.

Indicator Units. Type 116. Complete with VCR97 tube and seven EF50 valves. Good condition, 25/- carr. 7/6.

Remote Control Units for No. 19 Set. New boxed, two for 20/- Less Phones and Mike. Carr. 7/6.


Brand New in crates 12in. tubes. Type CV429, 8/- each, carr. 7/6. Also brand new 6-inch tubes, type CU1397, 4/- each, carr. 7/6. Brand new crated VCR97 tubes, 10/- carr. 7/6. Free insurance on tube.

New Co-axial Cable. Best make, 6d. per Yard. Post free. 50 yds. for 20/- 100 yds. for 37/-.

Send 3d. for list of valves and small parts

CABINETS & HI-FI EQUIPMENT

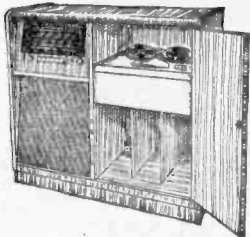We can supply any Cabinet to your own specification



'The Serenade' £13.19.6

This is only one example taken from our extensive range of stock cabinets. Write for our NEW 24 page fully illustrated catalogue on:

THE LARGEST RANGE OF CABINETS IN THE COUNTRY.


Equipment is also our speciality and we now offer in a novel book form: **A NEW EQUIPMENT COMPARATOR** illustrating our range of radio chassis, speakers, tape decks, single players and autochangers.

SEND TODAY for a copy of these two books, which are absolutely FREE.

LEWIS radio

120 (PW460) Green Lanes, Palmers Green
London, N.13. BOWs Park 1155/6
(Nr. The Cock Tavern)

TELETRON TAPEJAK

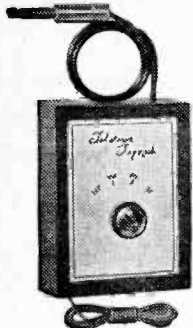

The first Transistorized Radio Tuner, specially designed for use with Tape Recorders. Converts your Recorder to a high quality Radio receiver. Direct Recording on Tape.

5 x 3½ x 1½ in.

- ★ High sensitivity.
- ★ Twin Tuned Circuits.
- ★ Pre-setting for M.V. Programmes.
- ★ Fixed Tuned for 1,500 M.
- ★ Switched programme selector.
- ★ Self powered.

Tested and ready for use.

£5.9.0. BATTERY EXTRA.

**THE
TELETRON CO. LTD.,**
112B Station Rd., London, E.4

*Phone: SIL. 0836.

BENSON'S BETTER ARGAINS

POWER UNITS. Input A.C. 110/250 v. Outputs: D.C. 330 v., 120 mA. and 6.3 v. A.C. (twice). Potted trans. and L.F. choke, new (post 3/6).

30/- MONITOR 56, comprising Indicator 248 and Power Unit 676. Valves VCR138A, 3/EF50, 2/EC033, 5/EF55, EF37A. 6V6, 3/EA50 and 2/5U4G, VU120A. Two units each 12 x 9 x 18in., black finish. 230 v. A.C. input, with 18-way Cable and mains cable. Cathode probe unit extra, 17/6. £8.10.0 (Rail 20/-).

RELAYS (Con- tactor), two heavy-make contacts: 12 v. or 24 v. either 3/8. **INDICATORS,** type 277, with 1in. C.R.T., 4/VR31, 2/VR92, 37/6 (p.p. 3/6). Type 101 with VCR330 (6in. Blue, magnetic. Octal base), and 2/EB01, 2/EF91, 2/R10, new cond., 30/- (Post 7/-). Type 1, with VCR263, 2/EF52, 5/6J6, 1/6V6, 1/EY61, 2/EB91, 3/EF91, RF EHT Generator and 28 kc/s. xtal. 45/- (Rail 7/6). Type 97 with VCR517, 10 valves, 30/- (Rail 7/6). **HEADPHONES,** CLR, 7/6. CR109 Noise Limiter assemblies, with valves, 3/6.

NEW M.C. METERS, 3pin. round finish, 50(A.A. 70/- 100(A.A. 65/- 1 mA, 55/- 2 mA (rectified), 45/- 24in. 1 mA, 22/8 2in. 20 mA 300 mA, each 8/6. 2pin. 30. A.C. 8/6 2in. 40 v. 8/6 200 v. A.C. 24in. 15/- **VIBRATORS,** Mallory G634C 12 v. 4-pin. 7/6 6 v. 5-pin reversible, 7/6. R1155B, good condition, tested with handbox £7.10.0 (Rail 10/-).

SCR522 Modulation or Driver Trans., either 7/8. **DRIVES,** Slow-motion Admiralty 200 : 1 ratio, scaled 0-100, 5/6. R1155 S.M., "N" type, new, 10/8. **VIBRAPAK,** 6 v. D.C. to 250 v. 60 mA. smoothed case, 12 v. to 250 v. 60 mA. 2/- (p.p. 3/6). **DYNAMOTORS** (post 3/6): 12 v. to 250 v. 60 mA and 6.3 v. 2.5 A. 11/6 6 v. to 250 v. 60 mA, 11/6. Potentiometers, miniature wire-wound, 6Q, 100Q, 600Q, 1k and 2k, each 1/4. **CHOKES,** LF 10 H 200 mA, 8/6 3H 100 mA, 5/6 Potted 10H 100 mA, 7/6 "C" 5H 400 mA, 10/8. **SWITCHES,** toggle U.S.A., DPDT, 1/8. R.P.27, good cond., 18/- (p.p. 3/6). **METAL RECTIFIERS,** 240 v. 100 mA, 4/- 240 v. 30 mA, 3/8 600 v. 30 mA, 6/6.

LIST AND INQUIRIES S.A.E. please. Ternus, G.W.O., Postage extra. Immediate dispatch. **Callers and Post:** W. A. BENSON (PW), 138 Rathbone Road, Liverpool 15. S.F.F.853 **Callers:** SUPERADIO (Whitechapel) LTD., 116 Whitechapel, Liverpool 2. ROY 1130

WIRING ACCESSORIES

Return of Post Service. Lowest Possible prices consistent with high quality. Money back guarantee.

PVC Cable Flat Twin with E. 3 Core

| | | | |
|-------|----------|----------|----------|
| 1.044 | £2. 1. 8 | £2.15. 1 | £2.19. 4 |
| 3.029 | £2.14. 2 | £3. 8.11 | £3.19. 0 |
| 3.036 | £3.16. 5 | £4.10. 9 | £5.10.10 |
| 7.029 | £4.19.11 | £6. 1.11 | £6.18. 3 |

TRS CABLE

| | | | |
|-------|----------|----------|----------|
| 1.044 | £2. 3. 5 | £2.13.11 | £3. 0.10 |
| 3.029 | £2.15. 9 | £3. 6.10 | £4. 5. 4 |
| 3.036 | £3.15. 2 | £4. 6. 5 | £5. 8. 7 |
| 7.029 | £4.13.10 | £5.18. 2 | £6.16. 7 |

Prices per 100 yds. All sizes stocked. Supplied in 25, 50, 75 or 100 yd. lengths. 7.029 and above cut to length—no cutting charge. Carriage paid on all orders over £2. Full range of accessories available. Send for complete lists.

ELECTROSURE

118 FORE STREET, EXETER

Phone: Exeter 56687.

Quality Components For Constructors

capacitors, resistors, coils, valves, diodes, controls, chassis, transformers, speakers, pickups, cartridges, styli and all types of components in stock.

52 Page Catalogue Available on Request

J. T. FILMER 82 Dartford Road, Dartford, Kent

Tel. Dartford 24057

NEW VALVES !

Guaranteed Set Tested
24 HOUR SERVICE

1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DK92, DL62, DL34, SET of 4, 21/6.
DAF96, DF96, DL64, DL66, SET of 4, 29/6.

| | | | | | |
|--------|------|-------|------|--------|------|
| 1D5 | 8/- | DL33 | 8/6 | PCL82 | 8/8 |
| 1R5 | 6/3 | DL36 | 8/6 | PCL83 | 11/6 |
| 1S5 | 5/6 | DL92 | 6/3 | PEN44 | 11/- |
| 1T4 | 4/6 | DL94 | 7/3 | PEN36C | 8/6 |
| 3S4 | 6/3 | DL96 | 7/11 | PL36 | 11/6 |
| 3V4 | 7/3 | EB041 | 7/11 | PL38 | 14/6 |
| 5U4G | 5/3 | EBF30 | 8/- | PL61 | 9/3 |
| 5Y3GT | 6/- | ECB81 | 5/6 | PL82 | 9/6 |
| 5Z4G | 9/6 | ECB82 | 6/- | PL83 | 7/6 |
| 6K7G | 2/- | ECB83 | 6/6 | PY32 | 11/- |
| 6K8G | 5/6 | ECB84 | 8/3 | PY80 | 7/- |
| 6AT6 | 6/3 | ECB85 | 8/- | PY81 | 6/3 |
| 6SL7GT | 8/- | ECF30 | 9/- | PY82 | 8/9 |
| 6SN7GT | 4/6 | ECH35 | 8/9 | PY83 | 7/3 |
| 6V6G | 5/- | ECH42 | 8/6 | U25 | 11/- |
| 6V8GT | 6/3 | ECH40 | 7/9 | U26 | 11/8 |
| 6X5GT | 5/- | EF41 | 8/6 | U27 | 5/6 |
| 12K7GT | 5/6 | EF30 | 5/6 | UAC80 | 7/6 |
| 12K8GT | 11/6 | EF85 | 6/6 | UAF42 | 9/- |
| 12Q7GT | 5/6 | EF86 | 10/3 | UB041 | 7/8 |
| 3SL6GT | 9/- | EF89 | 7/6 | UBF80 | 8/6 |
| 35Z4GT | 5/6 | EL41 | 8/6 | UC084 | 12/9 |
| A231 | 8/6 | EL94 | 8/6 | UC085 | 7/- |
| B36 | 8/6 | EY51 | 8/9 | UCF80 | 14/- |
| CL33 | 12/6 | EY86 | 8/9 | UCH42 | 7/9 |
| DAC32 | 9/9 | EZ40 | 6/9 | UCH81 | 8/- |
| DAF91 | 5/6 | EZ41 | 7/6 | UCL32 | 11/6 |
| DAF96 | 7/11 | EZ60 | 8/3 | UCL83 | 12/6 |
| DF33 | 9/9 | EZ81 | 7/- | UP41 | 8/3 |
| DF91 | 4/6 | GZ32 | 9/- | UP42 | 7/6 |
| DF96 | 7/11 | KT63 | 8/6 | UF89 | 7/- |
| DH7 | 6/6 | ML14 | 7/9 | UL41 | 7/6 |
| DK32 | 12/- | MX40 | 12/6 | UL84 | 7/6 |
| DK91 | 6/3 | PCC84 | 7/6 | UY21 | 13/6 |
| DK92 | 8/- | PCF80 | 7/6 | UY85 | 6/9 |
| PK96 | 7/11 | PCF82 | 8/6 | VP4B | 9/6 |

Postage 6d. per valve extra. Any Parcel Insured Against Damage in Transit 6d. extra. Any C.O.D. Parcel 2/6 extra.

Office address, no callers.

GERALD BERNARD
10 CARR MANOR AVENUE,
LEEDS 17

Morse Code operating . . .

. . . as a PROFESSION

45 years of teaching Morse Code is proof of the efficiency of the Candler system.

Send 3d. stamp for Payment Plans and full details of all Courses.

CANDLER SYSTEM CO. Dept. 5L0
52b Abingdon Road, London, W.8.
Candler System Co., Denver, Colorado, U.S.A.

TRANSISTORS

Red Spots, 4/-; White Spots, 5/-; Yell/GR, 5/-; Ediswan XB104, 8/6; XA103 (4 Mc/s), 10/-; XA104 (6.8 Mc/s), 12/-; Mullard OC70, 14/-; OC71, 14/-; OC72, 17/-; OC44, 26/-; OC45, 23/-; OC170 (70 Mc/s), 35/-; Newmarket V15/10P (10 watt power), 17/6; Diodes, 1/- and 2/6; Mullard Diode, 4/-; Transistor Holders, 1/-; Electrolytics (sub. min. 15 v.) 2, 4, 8, 50, 100 uf, 3/- ea.; Inductive Trans. D239, 8/6; D240, 8/6; D131, 12/6; D132, 12/6; T107, 12/-; D167, 12/-; Headphones L.R., 8/6; H.R., 17/-; Resistors 10% tol. 6d; 5% tol., 1/-; Tannoy Mike, 5/-; Desk Mike, 31/6; Balance Inserts (use as earpiece or speaker), 2/6; M.C. Earpiece (use Min. Speaker), 5/-; Westalite Contact Rectifier 250 v., 60 mA, 7/6; Trans 200/250 v. in. out 250-0-250, 6.3 v., 5 v., 15/-; Phillips Trimmers 30 pf., 1/-; Jack P. and Socket, 2/6; 365 pf. Air Var. (suit TXS), 3/-; 6 v. Vibrator Supply 120 v. 60 mA out, 12/6.

TERMS.—Cash with order. Post extra. excess refunded. Morco Reflex Rx, best 2-transistor Receiver. Send 8d. stamps for notes.

MORCO EXPERIMENTAL SUPPLIES
8 & 10 Granville Street, Sheffield 2
Tel.: 27461

12in. SPEAKER AND 5in. TWEETER by leading manufacturer, 75/- This is less than half list price.

CUT PRICE TOOLS. 5in. side cutters, 5/-; 5in. plated round nose tapered pliers, 5/-; 7in. flat-nosed tapered pliers, 8/6. Pocket neon testers with retractable screwdriver, 5/-; 7in. combination pliers, 8/-; 8in. Steel Block Planes 1in. blade, 10/8.

FULL SIZE H/S CHRYVAN TWIST DRILLS, Sets 7—1/16 to 1in. in. Walled, 6/-; Smaller size sets, 4/-.

NEW BOXED BSR UA8 4-SPEED AUTO-CHANGERS, 200/250 v. A.C. £8.19.6. Carriage 5/-.

OUR FAMOUS TRANSFORMERS. Input 200/250. Output tapped 3 to 30 v. 2 a. or 5, 11, 17 v. 5 a. Each 24/6.

F.W. METAL RECTIFIERS 12/6 volt, 1 a.; 7/8; 3 a.; 13/- 4 a.; 17/8; 6 a.; 27/6.

TOGGLE SWITCHES DPDT. 3/6.

MICRO SWITCHES. Make & Break. 5/6.

MAINS TRANSFORM. & RECTIFIER. Output 12 v. 1 a. D.C. 19/6.

NICKEL NIFE BATTERIES. 1.2 v. 2.5 a. Size 3 x 21 x 1in. 8/-, or 3 for 16/-, 4 for 21/-.

ARMY MORSE KEYS. 3/-.

RELAYS. We hold large stocks. Any contact combination and operating coil voltage supplied from 3/-.

KEY SWITCHES from 3/-.

6 OR 12 v. RELAYS. With 4 make contacts. 6/-, 2 for 11/6. 3 for 16/-, 4 for 21/-.

VERY POWERFUL GEARED SMALL 12 v. D.C. MOTORS, instant stop, 3 x 1in. 18/6.


All items new, guaranteed and post free except where stated.

Lists sent on request. Post orders only to THE RADIO & ELECTRICAL MART

29 STATION APPROACH, SUDBURY TOWN, WEMBLEY, MIDDXX.

More

for less...

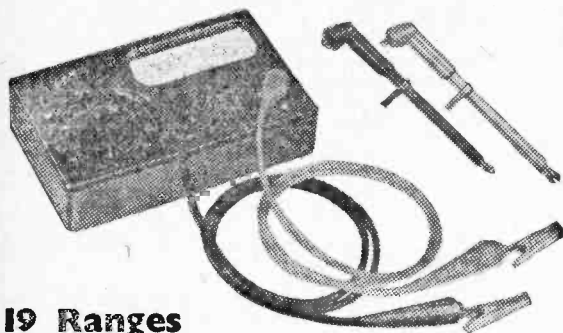

19 Ranges

| | |
|---------------------|---------------------|
| D.C. Voltage | A.C. Voltage |
| 0—100mV. | 0—10 V |
| 0—2.5 V. | 0—25 V. |
| 0—10 V. | 0—100 V. |
| 0—25 V. | 0—250 V. |
| 0—100 V. | 0—1000 V. |
| 0—250 V. | |
| 0—1000 V. | |
| D.C. Current | |
| 0—100μA | |
| 0—1mA | |
| 0—10mA | |
| 0—100mA | |
| 0—1A | |
| Resistance | |
| 0—20,000Ω | |
| 0—2MΩ | |

List Price: **£9: 10s.**

complete with Test Leads
and Crocodile Clips.

Leather Case if required 39/-

Size: $5\frac{1}{2} \times 3\frac{1}{2} \times 1\frac{1}{2}$ in.
Weight: 1 lb. approx.

Designed to offer the widest possible range of accurate and reliable measurements at the lowest possible price, the versatility and usefulness of the Multiminor are now further extended by specially designed leads. These new leads, available at no extra cost, will accept crocodile clips or **PRODCLIPS**.

The Multiminor takes full advantage of the possibilities of printed circuit techniques to achieve outstanding compactness and economy of weight. The scale is clear and open. The fine red colour pointer and effectively damped movement facilitate easy and rapid reading.

For use in Radio, TV, Electronics, Motor Vehicles, domestic appliances, workshop equipment, you'll find the Multiminor a great little meter!

Use **PRODCLIPS** with the **MULTIMINOR** (Pat. No. 748811)

These cleverly designed spring-loaded insulated prods are the complete answer to a long-standing problem. Press the trigger to open, release to grip. Keep your hands free no matter how difficult of access your test points may be.

15/- per pair.

...with the

MULTIMINOR®

Write now for illustrated literature to:—

AYO LTD

**AYOCET HOUSE - 92-96 VAUXHALL BRIDGE ROAD
LONDON - S.W.1**

VICtoria 3404 (12 lines)

A MEMBER OF THE METAL INDUSTRIES GROUP OF COMPANIES

GUIDE TO BROADCASTING STATIONS

3/6 12th Edition Postage 6d.

USING AN OSCILLOSCOPE. By D. W. Easterling. 6/6. Postage 6d.

TRANSISTOR CIRCUITS FOR THE CONSTRUCTOR. No. 3. By E. N. Bradley. 3/6. Postage 4d.

SHORT WAVE RECEIVERS FOR THE BEGINNER. A Data Pubn. 6/-. Postage 6d.

MODEL RADIO-CONTROL. E. L. Safford. 21/-. Postage 1/-.

WORLD RADIO HANDBOOK for Listeners. Broadcasting, Television, 1960. 15/6. Postage 1/-.

R.S.G.B. AMATEUR RADIO CALL BOOK. 1960 ed. 3/6. Postage 6d.

HI-FI MADE EASY. By N. H. Crowhurst. 23/-. Postage 1/-.

RADIO VALVE DATA. Compiled by "WVW". 6th ed. 5/-. Postage 9d.

A BEGINNER'S GUIDE TO RADIO. By F. J. Camm. 7/6. Postage 8d.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS
of British and American Technical Books

**19-23 PRAED STREET,
LONDON, W.2.**

Phone: PADdington 4185.

Open 6 days 9-6 p.m.

HIGH GAIN TRANSISTORS

BRAND NEW AND GUARANTEED

Red/Yell. (6 Mc/s), 8/6. White Spt. (4 Mc/s), 7/6. Yell./Grn., 6/6 (Matched pr. 250 mW), 13/6. Red Spt., 6/6.

MINIATURE AMPLIFIER

3-stage 4 TRANSISTORS, p.p. output, 250 mW, for 2-3 ohm speaker. Ideal for Gram, Radio, etc. High gain. Excellent quality. Easy assembly. Full kit, matched Transistors, complete instructions. New Components, 59/6, p.p 1/6. Circuit etc., 2/6.

SUB-MIN. P/P TRANSISTOR TRANSFORMERS. Driver, 11/3. Output, 10/-.

SUB-MIN. ELECTROLYTICS, 2, 4, 8, 25, 50, 100 mfd., 15 v.w., 2/9.

SMALL ELECTROLYTICS, 5, 10, 25, 100 mfd., 50 v, 1/6.

MIDGET RESISTORS, $\frac{1}{2}$ wt. Approved values, 3½d.

MIDGET VOL. CONTROLS. Standard values, 2/10. With S.P. switch, 4/-.

MIDGET ACCUMULATORS. 2 v. 0.27 amp./hrs., 3/-.

PLASTIC BOXES. Hinged lids: $4\frac{1}{2} \times 3 \times 1\frac{1}{2}$ in., 2/6, $5\frac{1}{2} \times 3\frac{1}{2} \times 1\frac{1}{2}$ in., 3/3, $7\frac{1}{2} \times 3\frac{1}{2} \times 1\frac{1}{2}$ in., 4/9, p.p. 1/3.

PERSPEX. 6 x 3 x $\frac{1}{8}$ in. Ivory. 1/-, p.p. 6d.

Please include sufficient postage when ordering. Send 3d. stamp for list of New Components.

BURLAND RADIO ACCESSORIES

Est 1947

G3JZ

ANN'S PLACE, SOUTHWICK, SUSSEX

H.A.C. SHORT-WAVE EQUIPMENT

AND

SHORT WAVE KITS

Famous for over 25 years for S.W. Receivers and Kits of Quality.

H.A.C. were the original suppliers of SHORT-WAVE RECEIVER KITS for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, Hams, etc.

Improved designs with Denco coils: One-valve Kit, Model "C." Price 25/-.

Two-valve Kit, Model "E." Price 50/-.

New Addition: Model "K." Receiver. Super sensitive "All Dry" Receiver. Special incl. price, Complete Kit, 77/-.

All kits complete with all components, accessories and full instructions. Before ordering call and inspect a demonstration receiver, or send for descriptive catalogue and order form.

POST THIS COUPON NOW!

"H.A.C." SHORT-WAVE PRODUCTS

(Dept. TH), 11, Old Bond Street, London, W.1.

Please send me FREE and without obligation your 1960 literature.

NAME

ADDRESS

Visit the City's popular acoustically designed

HI-FI Centre

Electronics FLEET ST Ltd

Dept. B

152/3 Fleet St., London, E.C.4. Tel. FLE 2833
Business Hours: Weekdays, 9-6. Saturdays, 9-1.

Stockists for

AMPLIFIERS, V.H.F. TUNERS, HI-FI SPEAKERS BY ALL
THE LEADING MANUFACTURERS

ANOTHER OF OUR AMAZING SCOOPS

A Snip for the Constructor

Build this Cossor Pocket 4 Transistor Superhet Receiver

Circuit Description: 4 transistors (OC44/OC45, OC45 OC72), two OA70 diodes, two AGC systems, coverage 190-550 metres. Power output 30 M/VV, ferrite slab aerial, 2½ in. moving coil speaker, printed circuit, attractive tuning control knob, leatherette case 6 x 3½ x 1½ in. All components including theoretical and point to point diagrams for easy construction. **ONLY £7.19.6**, post and packing 2/6.

All parts available separately

9 v. PP4 battery 2/-. Makers' original price nearly £20.

SOMETHING NEW !!

THE POCKET VALVE FILAMENT TESTER

Battery operated, it gives instant check on radio and TV valves, pilot lamps, fuses, continuity of circuit; also built-in 7 and 9 pin valve straightener. The ideal precision instrument for service engineer or amateur constructor. Finished in grey hammer case with gold panel. Fully guaranteed and ready for use. **OUR PRICE 30/-**. Post and packing 2/-.

BARGAINS IN PICK-UP CARTRIDGES

Brand new and complete with sapphire stylus. **BSR TC8** less bracket 15/- each. **BSR Hi-G 37/1** with bracket 17/6. **Acos Hi-G** with bracket 17/6. **Acos Hi-G 59** with bracket 17/6.

MAKE YOUR OWN PRINTED CIRCUITS

Printed circuits made to any wiring diagram. This kit contains all instructions, laminated board and the necessary chemicals for making numerous printed circuits. Additional laminated boards available. All materials of high quality, safe and easy to handle. Complete in perspex case. Our price 19/6. P. & P. 1/6.

BRAND NEW AND GUARANTEED

| | |
|------------------------|----------------------------------------------|
| 7in. reels of 1,200ft. | P.V.C. base tape 21/- plus 1/6 post and pkg. |
| 5in. " " 600ft. | " " " 14/6 " 1/6 " " " |
| 4in. " " 300ft. | " " " 9/6 " 1/- " " " |
| 7in. " " 1,800ft. LP | " " " 32/6 " 1/6 " " " |
| 5 1/2in. " " 1,200ft. | " " " 25/- " 1/6 " " " |

THE NEW INSTANT BULK TAPE ERASER

Can erase a spool of magnetic tape in a few seconds. Demagnetises oxide deposits on tape heads. **Only 27/5** post free.

SNIPS IN TAPE ACCESSORIES

Brand new E.M.I. 7in. take-up spools in polythene bag, 3/9 each post free. 6 for 20/-. Brand new 5in. Scotch Boy take-up spools 3/3 post free. 6 for 18/-.
KLENZATAPE, the new method for cleaning record and erase heads, 12/6. P. & P. 1/6.

METROTABS for identifying recorded passages on tape, 3/11 plus postage.

THE NEW AMERICAN AUDIO TAPE WITH PLASTIC BASE

Also supplied in green or blue at no extra cost. 3in. reel 150ft., 6/-; 4in. reel 300ft., 10/6; 5in. reel 600ft., 18/-; 7in. reel 1200ft., 30/-; 7in. reel L.P. 1800ft., 35/-. Post and Packing 1/- per spool.

STOP PRESS

Limited number R.C.A. Diamond L.P. stylus. Will fit any studio cartridge. Our price 25/-. Post 6d.

GZAK: This Month's Bargains

VARIABLE CONDENSERS

All Brass with Ceramic End Plates and Ball Race Bearings. 50 pf., 5/9; 100 pf., 6/6; 160 pf., 7/6; 250 pf., 8/6 and 300 pf., 9/6. P. & P. 1/6. Designed for the S.V.V. constructor.

RIBBED GLASS 3" AERIAL INSULATORS

or 6 for 7/6. P. & P. 1/6.

TRANSMITTER/RECEIVER AN/PPN-2. Frequency 214/234 Mc/s. Complete in carrying pack, with 9 valves (5-3A5, 3-155, 1-1R5). **WITH DUAL VIBRATOR PACKS** (2 v.), H5 30 'PHONES and ANTENNA, full instruction book, £3.19.6, carr. 7/6.

HEADPHONES H.R. TYPE. 4,000 ohms, very sensitive. **ONLY 12/6** pr. P. & P. 1/6. C.L.R. Type (low res.), 8/6. P. & P. 1/6.

Absorption Wavemeters. 3.0 to 35 Mc/s in 3 switched bands, marked on scale. Complete with indicator bulb. **A MUST** for any Ham shack. **ONLY 19/6**, post free.

2 METER 5 ELEMENT BEAM, W.S. Yagi. complete in box with 1"-2½" masthead bracket. **PRICE 49/-**. P. & P. 3/6.

SUPER LOW LOSS AERIAL CABLE, 1/8 yd. P. & P. 1/6.

ROTARY CONVERTERS. 6 v. input, 250 v., 125 mA output. **ONLY 17/6**. P. & P. 3/6. Also 12 v. D.C. MINIATURE, output, 360 v., 30 mA cont. or 310 v. 70 mA intermittent rating. 12/6 each or 22/- for 2. P. & P. 2/-.

CHAS. H. YOUNG LTD.

THE COMPONENT SPECIALISTS

Dept. "P". 110 Dale End, Birmingham, 4 (CEN. 1635)

(No C.O.D. under £1 please.)

(By return Service.)

GOVERNMENT SURPLUS AND MANUFACTURERS CLEARANCE

METERS. 500-0-500 Microamp. 3 1/4 in. dia. 37/6 ea. Dual Range 0-5 v. 0-100 v. FSD 1 mA. 20/- ea.; 50-0-50 Microamp. 2 1/4 in. 30/-; **TV AERIALS.** Combined BBC/ITV, 3 element. 32/6, 5 element 37/6. ITV 3 element. 22/6, 5 element. 27/3.

COAXIAL CABLE 64 yd. AIR SPACED 3d. DIPLEXERS, 12/-; GERMANIUM DIODES 1/-; 10/- doz. TRANSISTORS from 6/-; VOLUME CONTROLS. Long Spindle Midget. 10K-2 meg. Less Switch, 3/-; D.P. switch, 4/6.

CONDENSERS. Twin Gair 0.0005 Standard, 5/6. Midget, 6/6. **VHF CHASSIS,** contains over 50 components, 5/6 ea.

FERRITE ROD AERIALS, M. and L. wave, mfrs. surplus, 6/ea. METAL BOXES. Well vent., ideal p. packs, etc. 11 x 11 x 7 in. H. 8/6 ea.

SEL. RECS. 12 v. 1 amp., 5/-; 2 amp., 11/6; 4 amp., 15/-; 500 v. 1 amp. containing 30/35 mm. discs, 10/- ea.

ELECTROLYTICS. Canned. 20 ± 20 mfd. 450 v., 2/8 ea.; 25/- doz.

V.A.R. SLIDERS. 10 ohm 30 w. for chargers, trains. 3/- ea.

CONNECTING WIRE. P.V.C. 100ft., 2/8; various colours.

RELAYS. Large stocks, assorted sizes, from 2/6 ea.

PICK-UP ARM with turn-over cartridge, 19/6.

SLEEVING 2, 3, 4, 5. M/m. 3d. yard, 2/6 dozen.

VENNER SILVER-ZINC ACCUMULATORS. H.105. New, 15/-; 12 v. D.C. MOTORS, 3 x 1 1/4 in. D.E. Spindle, very powerful, 12/6 ea.

VALVES TESTED ON MULLARDS ELECTRONIC TESTER

| | | | | | | | | | |
|------|-----|------|-----|--------|------|-------|-----|----------|------|
| 11A | 5/- | 6F1 | 7/6 | 8D2 | 4/8 | EB41 | 7/6 | P61 | 4/4 |
| 11A | 6/6 | 6F6 | 7/6 | 8D2 | 5/- | EB91 | 5/6 | PEN45 | 7/6 |
| 10A | 6/- | 6F1C | 7/6 | 10F1 | 7/6 | ECH42 | 8/- | PEN46 | 7/- |
| 3A4 | 6/- | 6J5 | 6/- | 12A5 | 7/6 | ECH50 | 5/- | PL81 | 12/6 |
| 3Z4 | 6/- | 6J6 | 6/- | 12A18 | 8/- | EF36 | 8/- | PL83 | 8/- |
| 4D1 | 4/- | 6J7 | 6/- | 12AT7 | 6/- | EF37 | 9/- | SP41 | 4/- |
| 6AQ5 | 5/- | 6K7 | 4/6 | 12AU7 | 7/- | EF39 | 5/6 | SP61 | 4/- |
| 6AL5 | 5/- | 6L6 | 6/6 | 12AX7 | 7/- | EF50 | 3/6 | VR150/30 | |
| 6AM5 | 5/- | 6SA7 | 8/- | 12BH7 | 10/- | EF50 | 5/- | | |
| 6AM6 | 8/- | 6SC7 | 6/6 | 12SK7 | 6/- | EF80 | 8/- | | |
| 6AQ5 | 6/- | 6S37 | 5/- | 12ST7 | 6/6 | EF91 | 6/- | UL84 | 5/- |
| 6AU6 | 7/- | 6SK7 | 5/- | 12SK7 | 5/- | EF92 | 7/- | VCR97 | 15/- |
| 6BA6 | 8/- | 6SL7 | 6/- | 15D2 | 8/- | EL32 | 5/- | VCR138A | 8/- |
| 6BE6 | 5/8 | 6SN7 | 7/- | 50C5 | 10/- | EL81 | 5/6 | VCR138A | 2/- |
| 6BE6 | 5/- | 6U5 | 6/6 | 60T | 5/- | EY51 | 5/- | VCR138A | 2/- |
| 6BW6 | 6/8 | 6V6 | 6/6 | E450 | 1/6 | EY51 | 8/- | | |
| 6C4 | 5/- | 6X4 | 7/- | E4BC80 | 8/- | EY86 | 9/6 | | |
| 6D2 | 6/- | 6X5 | 7/- | | | | | | |

SECONDHAND VALVES, YOUR CHOICE, £1.00 for EIGHT. ECH80, 6C4, 6AM6, 6AQ5, 6J6, EF50, 6BE6, 3A4, EF80, SP61, P61, 315, PY30, PY92, 277, 6AL5, 6K7, 6S37, EL32, EF42, 6D2, 20P1, 6F13, SP41, EY51, EB91, EF91, EF39, PCL83, EF36, PEN45, PEN46.

INQUIRIES - S.A.E. PLEASE

HUGGETT'S LIMITED



2-4 PAWSONS ROAD, WEST CROYDON

NEW! UNIQUE!**MINIATURE TRANSISTORIZED
SIGNAL GENERATOR TYPE 40**

- ★ Up to 20 Mc/s on fundamentals.
- ★ R.F. and Audio Output, Attenuated.
- ★ Accuracy better than 2%.
- ★ Miniature size only $4\frac{1}{2}$ in. x $3\frac{1}{2}$ in.

PRICE NET **£5.15.0.** Battery 2/6 extra

Post (C.O.D. or C.W.O.), 2/6.

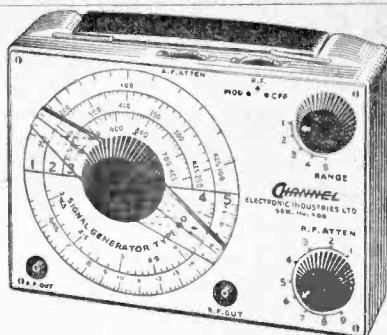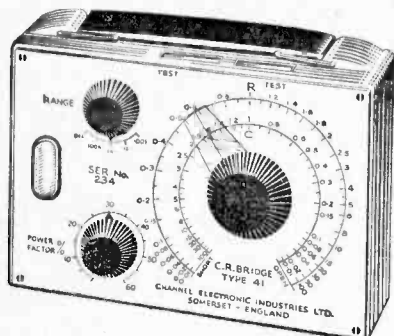**MINIATURE TRANSISTORIZED
R.C. BRIDGE TYPE 41**

- ★ Capacitance $5\mu\text{F}$ to $20\mu\text{F}$.
- ★ Resistance 5Ω to $20\text{M}\Omega$.
- ★ Magic Eye Balance Indicator.
- ★ Calibrated Power Factor Check.
- ★ Miniature Size—Light Weight.

PRICE NET **£5.10.0.** Battery 3/3 extra.

Post (C.O.D. or C.W.O.), 2/6.

SEND S.A.E. FOR LEAFLETS, OR ORDER TODAY, FROM—

CHANNEL ELECTRONIC INDUSTRIES LTD. DEPT. P., DUNSTAN RD.
BURNHAM-ON-SEA, SOM.

RADIO SERVICING. G. N. Patchett.
Vols. 1, 2, 3, 4. 5/4d. each.

RADIO CONTROL OF MODELS.
G. Sommerhoff. 5/4d.

**ELECTRONIC NOVELTIES FOR
THE CONSTRUCTOR.** E. N. Bradley.
5/4d.

**ELECTRONIC GADGETS FOR THE
CONSTRUCTOR.** E. N. Bradley. 3/10d.

**TRANSISTOR CIRCUITS FOR THE
CONSTRUCTOR.** Nos. 1, 2, 3.
E. N. Bradley. 3/10d. each.

USING AN OSCILLOSCOPE.
D. W. Easterling. 6/10d.

Postage included in above prices.

**STOCKIST OF INEXPENSIVE BOOKS
FOR THE CONSTRUCTOR.**

THE SELRAY BOOK CO.

60 Hayes Hill, Hayes, Bromley, Kent.

Factory Rebuilt . . . Super TELEVISION TUBES

All types fitted with New Gun
Assembly. Fully guaranteed
12 months.

Mullard, Mazda, etc.:

12 inch **£5.0.0**

14/15 inch **£5.10.0**

17 inch **£6.0.0**

Carriage and Insurance 12/6

ALLOWANCE ON OLD TUBE

C.W.O.

C.O.D. or Credit terms available.

S.A.E. for all inquiries.

K.V.A. ELECTRONICS Dept. (P/I)
3b Godstone Rd, Kenley, Surrey

JUST RELEASED

REPANCO TRANSISTOR AMPLIFIER AND FEEDER UNIT CIRCUITS

Envelope of theoretical and practical
layout diagrams or:

350/500 milliwatt Transistor Amplifier.

Simple T.R.F. Band Pass Feeder Unit.

Medium wave T.R.F. Feeder Unit with
R.F. Stage.

Medium and Long wave Unit with
R.F. Stage.

Medium and Long wave Superhet
Feeder Unit.

Microphone Preamplifier.

Send now 2/- (post free)
for envelope.

RADIO EXPERIMENTAL PRODUCTS LTD.

33 MUCH PARK STREET
COVENTRY

TRANSFORMERS

Suppliers to B.B.C., I.T.A., and leading radio
manufacturers. Single or long runs. Prompt
delivery. Home and export. Rewinds to
all makes.

FORREST TRANSFORMERS LTD.,
SHIRLEY, SOLIHULL, WARWICKS

Tel: SHI 2483

LYONS RADIO LTD.

Dept. M.P., 3, GOLDHAWK ROAD,
SHEPHERD'S BUSH, LONDON, W.12

Telephone: SHEpherd's Bush 1729

HIGH-GAIN AMPLIFIERS. Constructed
on chassis only $7\frac{1}{2}$ x $2\frac{1}{2}$ x 11in. Utilises latest
printed circuit technique, employing double-
wound mains isolating transformer, con-
tact cooled rectifier, EL84 triode pentode
O/P valve giving 2/3 watts output. With tone
control and combined on/off switch and
volume control. Suitable for either mag-
netic or crystal pick-ups, operate from
220/240v. A.C. mains. PRICE ONLY 5/6.
Knobs 2/6 extra. Post 3/6.

1 VALVE RECEIVER KITS. (Medium and
Long wave Band). All components supplied
right down to the last nut and bolt, in-
cluding valve, punched chassis, point to point
wiring diagram, full instructions, etc.
Ideal for the beginner. PRICE ONLY 38/-,
post 2/- All parts can be supplied separately.
Optional extras: High resistance head-
phones, 13/6; single H/R earpiece, 3/6;
combined HT/LT battery, 8/-. Instructions
only with price list 1/-.

UNIVERSAL MEASURING BRIDGES.
Ex/Govt. by Mullards, measure 0.1 ohms to
10 megohms and 10 pF to 10 mfd. Can also
be used to calculate power factor, for the
measurement of inductance with the use
of external standards and for percentage
tolerance measurement. Operate from 100
to 250v. A.C. mains. PRICE ONLY 21/0, post and in-
surance 4/-. S.A.E. for illustrated leaflet.

MULTI-RANGE METERS. 20,000 ohms/
volt, by Taylors. Measure A.C. and D.C.
volts and current and resistance up to 20
megohms without the use of external
batteries. PRICE ONLY 21/0, post and in-
surance 4/-. S.A.E. for illustrated leaflet.

EXTENSION SPEAKERS. Smart white
bakelite case fitted with 5 in. m.c. speaker.
Overall size 6 $\frac{1}{2}$ x 6 $\frac{1}{2}$ x 3 $\frac{1}{2}$ ins. Ideal for kitchen,
etc. PRICE ONLY 32/6, post 3/-.

EDDY'S (Nottm.) LTD.

172 ALFRETON ROAD, NOTTINGHAM

| | | | | | |
|-------|------|--------|-------|-------|------|
| 1A7GT | 12/6 | 6K7G | 2/3 | AZ1 | 12/6 |
| 1C5GT | 10/6 | 6K8G | 6/6 | DAF96 | 8/3 |
| 1D5 | 9/6 | 6Q7G | 7/6 | DF96 | 8/3 |
| 1H5GT | 9/9 | 6SA7M | 6/- | DK96 | 8/6 |
| 1L4 | 3/9 | 6SG7M | 5/- | DL96 | 8/3 |
| 1N5GT | 9/9 | 6SN7GT | 4/9 | DM70 | 7/6 |
| 1R5 | 7/- | 6V6G | 5/9 | EB41 | 7/- |
| 1S5 | 6/6 | 6V6GT | 6/6 | EB91 | 4/- |
| 1T4 | 4/9 | 6X5GT | 6/- | ECC81 | 6/- |
| 2D21 | 4/6 | 10F9 | 7/6 | ECC82 | 7/- |
| 3Q5GT | 8/9 | 12A6 | 5/6 | ECC83 | 7/6 |
| 5U4G | 5/9 | 12AT6 | 8/6 | ECC84 | 8/9 |
| 5Z4G | 9/- | 20D1 | 9/6 | ECC85 | 8/6 |
| 6AM6 | 4/- | 25A6G | 8/- | ECL80 | 9/6 |
| 6B8G | 2/11 | 25L6GT | 9/- | ECL82 | 10/6 |
| 6BA6 | 6/6 | 25Z4G | 7/6 | EF42 | 7/6 |
| 6BE6 | 6/6 | 35L6GT | 9/6 | EF50 | 1/9 |
| 6BJ6 | 6/6 | 35V4 | 6/9 | EF80 | 6/6 |
| 6C4 | 3/6 | 35Z4 | 12/11 | EF86 | 11/- |
| 6C6 | 4/3 | 807(B) | 3/9 | EL84 | 8/3 |
| 6CH6 | 9/3 | 954 | 1/6 | EZ80 | 6/9 |
| 6F1 | 6/6 | 955 | 3/11 | GT1C | 7/6 |
| 6J5G | 2/6 | 958 | 2/11 | UCH42 | 8/- |
| 6J5GT | 3/6 | 9001 | 4/6 | UF42 | 8/6 |
| 6J5M | 4/3 | 9004 | 4/- | UY41 | 6/6 |

Surplus New and Guaranteed Valves

Huge Purchase

TRANSISTORS

Red Spot, 4/9 ea. Doz. lots, 4/3 ea.
White Spot, 7/- ea. Doz. Lots, 6/6 ea.
Postage and Packing 6d.

LUXEMBOURG EXPANDING AERIALS. Compact and easy to fit. No technical knowledge required. Greatly improves reception. 3/11, post 6d.

DIMMER SWITCHES. Ideal for train speed regulators, 1/11, post 9d.

THROAT MIKES, 1/-, post 6d. Could be used for electrifying musical instruments.

SPECIAL OFFER—CAR RADIO KITS. Seven Transistor. Long and Medium Waves. 2 watts output. R.F. stage and automatic gain control. Complete kit with cabinet, 10½ gns. Speaker extra, 17/11, post and packing 5/-. (Please state voltage.)

GERMANIUM DIODES, 1/- each, 9/6 dozen, post 4d.

HEADPHONE CORDS. High quality 6ft. lengths, 1/11 pair, post 6d.

VIBRATORS, 12 v. 4 pin, 4/11, post 1/-.

SPEAKER GOLD GRILLE, 6½ x 4in., 1/- each, post 6d.

JACK PLUGS, Standard, 1/11, post 6d.

ACOS MIKES, 40, 25/-, post and packing 1/6.

2000mfd CONDENSERS, 6 v., working, 1/6, post 6d.

NIFE ACCUMULATORS, Size 3 x 2½ x ¾in., 7 amp. hrs. 1.25 v. Weight 13 ozs., 1/11 ea., post and packing 1/6 one, only add 9d. per cell.

CO-AXIAL CABLE, Air spaced, suitable for TV fringe area, V.H.F., etc., 7½d. per yd. Cut to any size. Post 1/3 per doz. yds.

CONDENSERS, Tubular Wire End, Midget 25 x 25, 1/3, post 6d.

All Above are New and Guaranteed

Any parcel insured against damage in transit for only 6d. extra per order. All uninsured parcels at customer's risk. Postage and Packing 6d. per valve extra. Over £3 free. C.O.D. or C.V.O. only. C.O.D. charge 3/- extra. S.A.E. with inquiries.

LEARN MORE - EARN MORE THIS EASY WAY

These practical books have been selected because they feature:

- ★ Top technical writers.
- ★ Explain every detail clearly.
- ★ Represent good value.

No. 76. SERVICING TRANSISTOR RADIOS by D'Airo. How to handle the specialized servicing problems encountered in repairing transistor and miniature equipment. 224 pages, 23/-, postage 10d.

No. 78. RAPID RADIO REPAIR by Reath. Learn to fix radios fast! Time saved will soon pay for this popular book! 220 pages, 23/-, postage 10d.

No. 80. STEREO, HOW IT WORKS by Burstein. A complete course with latest techniques. 224 pages, 23/-, postage 10d.

No. 81. SERVICING PRINTED CIRCUITS. Printed circuits are here to stay so now is your opportunity to learn all you can about them! 23/-, postage 10d.

No. 75. TRANSISTORS, THEORY AND PRACTICE by Turner. One of the best books you can buy on transistors. It's an all-time best seller—do you have your copy? 23/-, postage 9d.

No. 47. RADIO AND TV HINTS. Hundreds of short cuts, practical hints to save you time and energy. 8/-, postage 6d.

No. 44. BASIC RADIO COURSE by Frye. If you are just starting into radio this is your best buy. 176 pages, 18/-, postage 1/-.

No. 49. RADIO AND TV TEST INSTRUMENTS. Build 22 instruments, picture tube analyzer, picture tube tester, three-inch scope, marker generator. 12/-, postage 8d.

For the Short Wave Radio Amateur

No. 10. ALL ABOUT CUBICAL QUAD ANTENNAS by Wm. Orr. W.8 S.A.L. The complete story of the Cubical Quad antenna—history, theory, design, construction and adjustment of single, multi-band, and multi-element Quad antennas. 22/9, postage 10d.

No. 11. BETTER SHORT WAVE RECEPTION by Wm. Orr. How to hunt DX! How to get verification cards! "Do-it-yourself" radio projects, DX tuning hints. Jam packed with data. Order yours now. 22/9, postage 10d.

No. 12. V.H.F. HANDBOOK by Wm. Orr. Covers in detail the generation, propagation, and reception of V.H.F. signals, plus the construction and design of equipment and antennas. A most complete handbook on V.H.F. 23/-, postage 10d.

No. 13. NOVICE AND TECHNICIAN HANDBOOK by William Orr and Stoner? Covers transmitters, receivers, antennas in step-by-step, easy to follow instructions. Written so you can understand it! Get your copy! 22/9, postage 10d.

TRY ANY BOOK 7 DAYS WITH MONEY-BACK GUARANTEE

To: **SIM-TECH BOOK CO.,**

HURST CLOSE, TOTTEN
SOUTHAMPTON, HANTS.

Please send the books circled below for 7 days' free examination. If not satisfied I will return books in good condition within 7 days, post-paid, and you agree to refund my money.

PLEASE CIRCLE

| | | | | | |
|----|----|----|----|----|----|
| 76 | 78 | 80 | 81 | 75 | 47 |
| 44 | 49 | 10 | 11 | 12 | 13 |

Name.....
Address.....

Enclosed please find £..... s. d.

payment, including postage (free if order exceeds £3 in value).
Please write for complete list of additional books?

METERS GUARANTEED PERFECT Charging Types

| | |
|------------------------------------------|------|
| 2½ amp. D.C. M.I. 2in. fl. rnd. | 7/6 |
| 5 amp. D.C. M.I. 2½in. fl. rnd. | 11/6 |
| 7½ amp. D.C. M.I. 3½in. proj. rnd. | 12/6 |
| 9 amp. D.C. Hot Wire W.R. 2½in. fl. rnd. | 6/6 |

Voltmeters

| | |
|----------------------------------|------|
| 12 v. D.C. M.C. 2½in. proj. rnd. | 8/6 |
| 20 v. D.C. M.C. 2in. fl. sq. | 9/6 |
| 25 v. D.C. M.C. 2in. fl. rnd. | 7/6 |
| 30 v. M.I. 3in. proj. rnd. | 10/6 |
| 150 v. M.C. 2in. fl. sq. | 9/6 |
| 150 v. D.C. M.C. fl. rnd. 2½in. | 10/6 |

250 v. A.C. rectified moving coil linear scale 3½in. fl. rnd. 35/-

300 v. A.C. M.I. 2½in. fl. rnd. 22/-

400 v. A.C. M.I. 4½in. fl. rnd. 35/-

Milliammeters

| | |
|-----------------------------|------|
| 1 mA. M.C. 2½in. fl. rnd. | 25/- |
| 2 mA. M.C. 2½in. fl. rnd. | 14/6 |
| 5 mA. M.C. 2in. round. | 12/6 |
| 10 mA. M.C. 3½in. fl. rnd. | 30/- |
| 30 mA. M.C. 2½in. fl. rnd. | 9/6 |
| 500 mA. M.C. 2½in. fl. rnd. | 9/6 |

Microamp

50 microamp, scaled 0-100, M.C. 2½in. rnd. fl. 42/6

200 microA, M.C. 2½in. rnd. fl. (calibrated 0-50) 29/6

50 microA 2½in. square, sidefitting 3 scales. 35/-

500 microA, M.C. 2in. rnd. 16/6

Postage on all meters 1/- each.

MAINS POWER SUPPLY UNITS,

potted and sealed transformer and choke by famous maker. Mounted on metal chassis 6½ x 7½in., complete with 5Z4 rectifier valve and full smoothing. Input tapped 220-230-240 volts.

Output: 300 v. D.C. at 100 mA.

6.3 v. A.C. at 4.5 amp.

6.3 v. A.C. at 2 amp.

Rectifier supply 5 v. A.C. at 3 amp. Very conservatively rated. Price 42/6 plus P. & P. 6/6.

NEW UNCHARGED UNFILLED 12 VOLT ACCUMULATOR

9 ampere in unspillable plastic case. Comprises 6 x 2 v. separate cells connected by terminal strips. 6 x 5½ x 4½in. over terminals. Price 19/-, plus P. & P. 2/9. Wooden carrying case for same with lid and strap, price 3/6.

VENNER 8-DAY CLOCKWORK TIME SWITCH.

Contacts 1 amp. 230 volt. 24-hour phase, 1-hour divisions, allows setting for one make and one break to be made every 24 hours, complete with key. Used but guaranteed perfect. Price 27/6 each. P. & P. 1/6.

SIEMENS H.S. RELAY. Very latest type, sealed. H96E. 1,700 ohms plus 1,700 ohms, single C.O. contacts. Brand new with fixing clip. In maker's cartons. Price 16/6 each, plus 1/- P. & P.

A VERY SUPERIOR BRAND NEW RELAY IDEAL FOR MODEL WORK.

7,000 ohms coil. Will pull in at 750 microamp and out at 450 microamp. Change-over, platinum contacts. Vacuum sealed, will therefore not be affected by oil, moisture or water and never needs adjusting. Weight 2½ oz. Price 18/6. P. & P. 1/6.

BRAND NEW SOUND POWER OPERATED EX ADMIRALTY HEAD AND BREST SETS.

Two such sets connected up will provide perfect intercomm., no batteries required. Will operate up to ½ mile. Original manufacturer's boxes. Price 17/6 each, plus P. & P. 2/-; or 32/6 per pair. P. & P. 3/-.

SERVICE TRADING CO.

Personal callers:

9 LITTLE NEWPORT STREET,
LONDON, W.C.2

All mail orders:

Dept. P, 47 HIGH STREET,
KINGSTON-ON-THAMES.

R.S.C. MANCHESTER BRADFORD & LEEDS

(Leeds) LTD.

Terms C.W.O. or C.O.D. No C.O.D. under £1.

EX. GOVT. MAINS TRANSFORMERS

| | |
|--------------------------------------------------|-------|
| Primaries 200-250 v. 50 c.p.s. A.C. | |
| 250 v. 80 m.a., 6.3 v. 2 a..... | 10/11 |
| 275-0-275 v. 100 m.a. 6.3 v. 7 a. 5 v. 3 a..... | 21/9 |
| 300-0-300 v. 60 m.a. 6.3 v. 2 a..... | 11/9 |
| 300-0-300 v. 100 m.a. 6.3 v. 2 a. 5 v. 2 a..... | 18/9 |
| 350-0-350 v. 180 m.a. 6.3 v. 5 a., 5 v. 3 a..... | 27/9 |

SELENIUM RECTIFIERS

| F. W. BRIDGE | H.T. Types | H.W. |
|-------------------|------------|----------------------|
| 6/12 v. 1 a..... | 3/11 | 150 v. 40 m.a..... |
| 6/12 v. 2 a..... | 6/11 | 250 v. 50 m.a..... |
| 6/12 v. 3 a..... | 9/9 | 250 v. 80 m.a..... |
| 6/12 v. 4 a..... | 12/3 | 250 v. 90 m.a..... |
| 6/12 v. 6 a..... | 15/3 | 250 v. 250 m.a. 12/9 |
| 6/12 v. 10 a..... | 25/9 | CONTACT COOLED |
| 6/12 v. 15 a..... | 35/9 | 250 v. 30 m.a. H.W. |
| 25 v. 2 a..... | 14/9 | 6/11, 250 v. 75 m.a. |
| | | F.W. (Bridges) 8/11 |

Mail Orders to 29-31 Moorfield Rd., Leeds, 12.
Callers to 5 and 7 County (Mecca) Arcade, Briggate, Leeds 1,
8-10 Brown St. (Market St.), Manchester 2, or 56, Morley
Street (Next Majestic Ballroom), Bradford.

SENSATIONAL TRANSISTOR OFFER. 3 for 10/9. A huge purchase enables us to offer Brand New. Guaranteed Brimar TSI Audio Transistors at a small fraction of list price.

TELEVISION RECTIFIERS. 250 v. 200 m.a. small size. Only 6/9 ea.
RE-ENTRANT SPEAKERS. Tannoy. 8 watt, 7.5 ohms. Only 19/6 each. Or 35/- per pair.

ARDENTE DEAF AID EAR-PIECES. Brand new, complete with ear insert and lead. Only 15/6 each.

R.S.C. BATTERY CHARGING EQUIPMENT

ASSEMBLED CHARGERS

| | |
|-----------------------------------------|------|
| 6 v. 1 amp..... | 19/9 |
| 6 v. or 12 v. 1 amp..... | 29/9 |
| 6 v. 2 amps..... | 29/9 |
| 6 v. or 12 v. 2 amps..... | 39/9 |
| 6 v. or 12 v. 3 amps. with ammeter..... | 59/9 |

Above ready for use. With mains and output leads. Carr. 3/6.

HEAVY DUTY CHARGER KIT.

6/12 v. 6 amps. variable output. Consisting of Mains Transformer 0-200-230-250 v.; F.W. (Bridge) Selenium Rectifier; Ammeter. Multi Position Switch with Knob; Panels. Plugs, Fuses, Fuseholder, and circuit 59/9. Carr. 4/6.



Assembled 6 v. or 12 v. 4 amps.

Fitted Ammeter and variable charge rate selector. Also selector plug for 6 v. or 12 v. charging. Louvred steel case with splayed blue hammer finish. Fused 69/9 and ready for use with Carr. 5/- mains and output leads. Terms: Deposit 13/3 and 5 monthly payments 13/3.

ASSEMBLED CHARGER

6 v. or 12 v. 2 amps.

Fitted Ammeter and selector plug for 6 v. or 12 v. Louvred metal case. Finished attractive hammer blue. Ready for use. With mains and output leads. Double Fused. Only Carr. 3/9. 49/9

All for A.C. Mains 200-250 v., 50 ccs. Guaranteed 12 months.

BATTERY CHARGER KITS

Consisting of Mains Transformer, F.W. Bridge, Metal Rectifier, well ventilated steel case. Fuses, Fuseholders, Grommets, panels and circuit. Carr. 3/6 extra.
6 v. or 12 v. 1 amp..... 24/9
As above, with Ammeter... 32/9
6 v. 2 amps..... 25/9
6 v. or 12 v. 2 amps..... 31/6
6 v. or 12 v. 2 amps. inclusive of Ammeter..... 42/9
6 v. or 12 v. 4 amps..... 53/9
6 v. or 12 v. 4 amps. with Ammeter and variable charge rate selector. 59/9.
CHARGER AMMETERS. 0-1.5 a., 0-3 a., 0-4 a., 0-7 a., 0-25 a. 0-50 a. 9/9.

EX-GOVT. CASES. Size 14-10-9 1/4 in. high. Well ventilated, black crackle finished, undrilled cover. IDEAL FOR BATTERY CHARGER OR INSTRUMENT CASE, OR COVER COULD BE USED FOR AMPLIFIER. Only 9/9. plus 2/9 postage.
2 v. 16 a.h. EX-GOVT. ACCUMULATORS. New, boxed. Only 5/6 each. 3 for 15/-, post 5/6. 6 for 27/6. carr. 3/6.

D.C. SUPPLY KIT. 12 v. 1 a. consisting of partially drilled metal case, mains trans., F.W. Bridge Rectifier. 2 fuseholders and fuses. Change Direction switch, variable Speed regulator and circuit. For 200-250 v. A.C. mains. Suitable for Electric Trains, etc. Limited number available at 33/6.

STANDARD JACK PLUGS. With 4ft. screened lead, 1/11 ea.
5 CORED P.E.N. Rubber insulated. 1/30, 1/3 yd., 50/- 50 yds.
TRANSISTORS. Audio Type, 6/8. R.F. 12/6. Power type, 2 watts. V15/10P, 17/9. Mullard OC71, 10/-; OC72, 16/9; XB102, XB104, 10/-. Most types at bargain prices. Diodes 0A81, GD3, 3/9.
REPAIRO CONSTRUCTIONAL ENVELOPES AND PARTS
SWITCH STOCK. Parts for 3 Decade Transistor Radio. £3-6-6.
Mini-Seven 7 Transistor Pocket Portable 10 Gram
TURNOVER STEREO/MONORAL PICK-UP HEADS, by Acos. Suitable for normal 78, 45, or 33 1/3 r.p.m. records or for stereo type. Sapphire Stylus. Will fit Garrard B.S.R. Collaro and Staar Galaxy Record Changers. Only 49/9.

4/6 TRANSISTORS 4/6

Red Spot, 4/6; White Spot, 5/6; Yellow/Green, 5/6; Red/Yellow, 10/6; Crystal Diodes, 1/-; GEX34, 4/-; Mullard OA70 or OA81, 4/-; Slab Aerials Repanco F53 Med. Wave, 7/6; F54 Long Wave, 7/6; F52 M & L, 13/6; Ferrite Rod Aerials Rep. F.R.I. M & L, 12/6; Teletron FX25 M & L, 15/-; FM 2 MW, 10/-; Coils Repanco D70 M & L Crystal Set Coil, 2/6; DRR2 Dual Wave with Reaction, 4/-; Teletron HAX MW Crystal Set Coil, 3/-; HAXL LW, 3/6; HMX MW Transistor Coil, 3/-; HLX LW, 3/6; Circuit with above coils. Reaction Condensers 0.0001, 3/-. 0.0003, 3/9. 0.0005, 4/-. Miniature 0.0005, 4/-.

All sent post free in the U.K. by:

PETHERICK'S

Radio Supplies

22 HIGH ST., BIDEFORD, N. DEVON


A.R.R.L. RADIO AMATEURS HANDBOOK 1960

New edition 32/6. Postage 1/9.
World Radio Handbook, 1960, by Hans Johansen, 15/6. Postage 1/-.
Mullard Circuits for Audio Amplifiers, 8/6. Postage 10d.
Using an Oscilloscope, by Easterling, 6/6. Postage 6d.
Transistor Circuits Book 3, by Bradley, 3/6. Postage 6d.
Guide to Broadcasting Stations, by W/World, 3/6. Postage 6d.
Radio Valve Data, by Wireless World, 5/-, Postage 8d.
Model Radio Control, by Safford, 21/-, Postage 1/-.
TV Servicing, by Patchett, Vol. 4, 7/6. Postage 6d.
Amateur Radio Call Book, by R.S.G.B., 1960, 3/6. Postage 6d.

UNIVERSAL BOOK CO.

12 Little Newport Street, London, W.C.2 (adjoining Lisle Street)

BBC - ITV - F.M. AERIALS

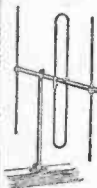

RBC (R&ND 1). Telescopic loft, 19/6. External, S/D, 28/3.

ITV (R&ND 3). 3 Element loft array, 24/-, 5 Element, 32/6. Wall mounting, 3 Element, 33/9. 5 Element, 41/3.

COMBINED BBC + ITV. Loft 1-3 Element, 41/3. 1-5 Element, 48/9. Wall mounting, 1-3 Element, 56/3. 1-5 Element 63/9. Chimney and mast mounting units also available.

F.M. (R&ND 2). Loft "H", 28/-, 3 Element, 52/6. S/D loft, 12/6. External S/D 26/3. State channel when ordering. C.W.O. or C.O.D. P.P. 2/6. Coaxial cable, 8ft. yd. Coaxial plugs, 1/3. Send 6d. stamps for illustrated lists.

K.A.A. ELECTRONICS (Dept. P.W.)
3, Godstone Road, Kenley, Surrey

DO IT YOURSELF

Build your own electronic keyboard and play everything! Send for free leaflet. Guitar, cello, flute and trumpet are all easy. Write now...

C. & S., 20 Maude Street, Darlington, Co. Durham.

"GLOBE-KING"

WORLD-FAMOUS KITS AND RECEIVERS for the Radio Amateur and S.W. Listener. Catalogue Free, enclose stamp for Postage. Kits from 79/6 at your dealers, or direct from **JOHNSONS (RADIO)** ST. MARTINS GATE, WORCESTER

TRANSISTOR TEST SET

Measures Gain directly in three ranges 0-50, 125, and 250. Also measures Base current, 0-100uA, and Collector current 0-5mA. Works from 9 v. GB Battery, not supplied. Complete, ready to use, with instructions, 37/6. P. & P. 1/6.

Transistors. Red Spot, 4/6; White, 5/-; Yellow/Green, 7/6; Red/Yellow, 14/-; STC TSI, 4/3.

15 Range A.C./D.C. Multimeter Kit. 1,800 o.p.v. Ranges 15, 60, 150, 300 600 v. C. and A.C.; 3 v. D.C.; 6, 60, 600 mA D.C.; Ohms to 2M. Kit comprises 3,000uA meter, scaled 0-15 and 0-600, resistors 8 at 1 per cent, 2 at 10 per cent; Shunts ready adjusted, 3 at 1 per cent; switches 1p 11 w., and 3p 4 w.; wirewound pot; Salford Instrument Rectifier. With Instructions 45/-, Post free. **Bridge Type Instrument Rectifiers.** Salford 1mA, 5mA, 7/6; Westinghouse 250uA, 1mA, 5mA, 14/6, 100uA, 17/4.

PLANET INSTRUMENT CO.,

25 DOMINION AVENUE, LEEDS 7

IS YOUR T.V. TUBE DIMMING? YOU CAN EXTEND THE LIFE OF THAT TUBE AND IMPROVE THE PICTURE



PRICE 30/-

P.P. & Ins. 2/6
C.W.O. C.O.D.
Satisfaction or money refunded within 7 days.

NO SOLDERING
NO WIRING **JUST PLUG IN** **IT'S AUTOMATIC** **IT'S GUARANTEED!**
We can offer these units for any make of set. **IMPORTANT.** State name, address, & make and model no. of set, & tube in block caps.
SINCLAIR ELECTRONICS,
Dept. P.W., 33, BERWICK ST., W.I.
Callers Welcome — REGent 5520

FREE LISTS

BY RETURN

LARGE RANGE OF VALVES, TUBES, MAINS TRANSFORMERS, QUARTZ CRYSTALS, METERS, TEST UNITS, TRANSISTORS, MINIATURE COMPONENTS, RECTIFIERS, ETC.

TELESCOPIC CHROME AERIALS

7-Sections, 3ft. 6ins. open: 6ins. closed. Ideal for Portable Receivers, Walkie-talkies, Radio Control, etc. 12/6, P.P. 1/-.

SUB-MIN. TRANSISTOR CONDENSERS

2mfd 1½VW: 4mfd 6VW: 30mfd 6VW, 2/- ea. 8mfd: 10mfd: 6mfd: 50mfd, 2/3 ea. 500mfd 6VW, 1/6; 2mfd 9VW, 2/3.

VALVE REDUCTIONS

(WHEN PURCHASED IN SETS)

| | |
|-------------------------------------------------------|------|
| TP25, VP23, HL23/DD, PEN25 (or QP25) | 25/- |
| 1A7GT, 1N5GT, 1C5GT, 1Q5GT (or 3Q5GT) | 35/- |
| X66, KTW61, DH63, KT63, U50 | 30/- |
| 6K8G, 6K7G, 6Q7G, 5Z4G, 6V6G | 32/6 |
| IR5, IS5, IT4, IS4 (or 3S4 or 3V4) | 25/- |
| DK96, DF96, DAF96, DL96 | 35/- |
| 6K8G, 6K7G, 6Q7G, 25L6GT, 25Z5 (or 25Z6G) | 35/- |
| 12K8GT, 12K7GT, 12Q7GT, 35Z4GT, 35L6GT (or 50LGT) | 40/- |
| 12SA7GT, 12SK7GT, 12SQ7GT, 35Z4GT, 35L6GT (or 50L6GT) | 32/6 |

P.P. 1/- per set of Valves.

Free complete list on request.

CAR RADIO VIBRATOR UNITS

| | |
|---------------------------|------|
| 2 volts 7-pin Synchronous | 7/6 |
| 12 " 6 " " " | 12/6 |
| 12 " 7 " " " | 12/6 |
| 6 " 7 " " " | 12/6 |
| 6 " 4 " non-synchronous | 7/6 |
| 12 " 4 " " " | 5/- |

PACKARD BELL PRE-AMPLIFIER

Low Impedance Mic. Pre-Amp. 6SL7GT and 28D7. Complete in screened box with leads, jack-plugs and handbook. BRAND NEW IN CARTONS, 12/6, P.P. 2/-.

8-IN. HIGH-FLUX SPEAKER

Complete in Black Crackle Case. 3 ohms Speaker. 45/- P.P. 2/6.

CATHODE-RAY TUBES


(Ideal for 'Scopes and Indicators.)

| | | |
|-------------------|-------|------|
| 2AP1 | 2in. | 25/- |
| VCR139A | 2½in. | 35/- |
| 3BP1 | 3in. | 30/- |
| 3FP7 | 3in. | 12/6 |
| 3AP1 | 2½in. | 30/- |
| Mullard DG7/5 | 2½in. | 45/- |
| 5FP7 | 5in. | 20/- |
| VCR517C | 6in. | 30/- |
| VCR97 | 6in. | 40/- |
| Screens for VCR97 | | 7/6 |

P.P. 2/- any type Fully Guaranteed.

FREE LIST and Data on request.

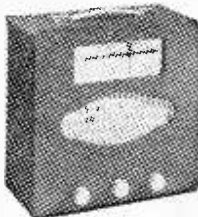TRADE INQUIRIES INVITED ON ALL ITEMS AND DO-IT-YOURSELF UNITS



Chassis Size 10 x 10 x 4in.

SHORT-WAVE RADIO

- ★ 3 Wavebands (10 to 550 metres)— 650 kc/s to
- ★ 2 Mc/s, 3 to 11 Mc/s to 30 Mc/s.
- ★ 5-valve Marconi Superhet.
- ★ A.C./D.C. 200 to 250 v. mains.
- ★ 7 x 4in. Speaker; Gram. Input.
- ★ Slow-motion Drive. ★ Frame Aerial.


NOW £6.15.6 P.P. 3/6.

OR COMPLETE IN PORTABLE CABINET, £7.12.6, P.P. 4/-.

- ★ ALTERNATIVE MODEL: MEDIUM, LONG AND SHORT

— THE WORLD IN YOUR HOME —

POCKET MULTI-TESTERS BRAND NEW

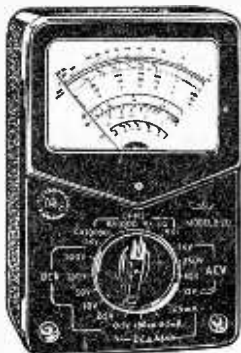

MODEL A-10 (500 Micro-amp Movement). D.C. (2k per volt) 0/10/50/250/500/1000 v. A.C. (2k per volt) 0/10/50/250/500/1000 v. D.C. current 0/0.5/25/250 mA. Resistance: 0/10K/1 Meg. Size: 5½ x 3½ x 1½in. Weight: 17 ozs. Price £4.17.6, P.P. 1/6 inclusive of Test Prods, Instruction Book and Batteries

MODEL B-20 (100 Micro-amp Movement). D.C. (10,000 ohms per volt) 0/0.5/2.5 volts. D.C. (4000 ohms per volt) 0/10/50/250/500/1000 v. A.C. (4000 ohms per volt) 0/10/50/250/500/1000 v. D.C. Current, 0/0.1/2.5/25/250mA. Size: 5½ x 3½ x 2½in. Weight 24 ozs. Price £6.10.0, P.P. 1/6, inclusive of Test Prods. Instruction Booklet and Batteries.

FREE ILLUSTRATED LEAFLET ON REQUEST

A.C., D.C. and R.F. METERS

| | |
|-----------------------------------|------|
| 0-15 v. 2½" M.I. (A.C.) F.R. | 8/6 |
| 0-1 mA 2½" M.C. (D.C.) F.R. | 22/6 |
| 0-500µA 3½" M.C. (D.C.) F.R. | 59/6 |
| 2½-20 mA 2½" M.C. (D.C.) F.R. | 12/6 |
| 5-0-5 amp 2½" M.C. (D.C.) P. | 10/- |
| 20-0-20 amp 2" M.C. (D.C.) F.S. | 12/6 |
| 0-1 amp 2" T.C. (R.F.) P. | 6/- |
| 0-3 amp 2" T.C. (R.F.) F.S. | 6/- |
| 0-12 amp 2½" T.C. (R.F.) P. | 10/- |
| 0-6/60 volts 2½" M.C. (D.C.) P. | 10/- |
| 0/12/120 volts 2½" M.C. (D.C.) P. | 10/- |
| 0-400µA 3½" M.C. (D.C.) F.R. | 59/6 |

CRYSTAL MICROPHONES AND INSERTS

ACOS AND OTHER WELL-KNOWN MAKES. BRAND NEW.

| | |
|------------------------|------|
| 1in. Square | 7/6 |
| 1½in. Square | 7/6 |
| 1½in. Round | 7/6 |
| 1½in. Round | 8/6 |
| 1½in. Round | 14/- |
| 2in. | 12/6 |
| 2½in. Square, ex-units | 3/6 |

All guaranteed. P.P. 6d. any type.

Acos 39-1 Stick Mic. 32/6, P.P. 1/6

Acos 40 Desk Mic. 25/-, P.P. 1/6

TRANSMITTER/RECEIVER

Army Type 17 Mk. II. Complete with Valves. High Resistance Headphones, Hand Mike, Instruction Book and Circuit. Frequency Range 44.0 to 61 Mc/s. Range approximately 3 to 8 miles. Power requirements: Standard 120v. H.T. and 2 v. L.T. Ideal for Civil Defence and communications.

BRAND NEW 45/- P.P. 5/-.

44-61 Mc/s calibrated wavemeter for same, 10/- extra.

TYPE 38 TRANSMITTER/RECEIVER

Complete with 5 valves. In new condition. These sets are sold without guarantee, but are serviceable.

7 to 9 Mc/s 22/6 P.P. 2/6.

Headphones 7/6 pair. Junction Box 2/6. Throat Mike 4/6. Canvas Bag 4/- Aerial Rod 2/6.

AVO MINOR TESTMETER



A.C./D.C. 0-500 volts. (in 5 Ranges) D.C. 0-500 mA (in 5 Ranges). RESISTANCE 0-20 K.

COMPLETE WITH LEADS AND LEATHER CASE 79/6 P.P. 2/- FULL GUARANTEE.

HENRY'S (RADIO) LTD.

Opposite Edgware Road Tube Station, PADDINGTON 1008/9.

5 HARROW ROAD, EDGWARE ROAD, PADDINGTON, LONDON, W.2
OPEN MONDAY to SAT. 9-6. THURS. 1 o'clock.

SEE
BACK
PAGE

Practical Wireless

BLUEPRINT

SERVICE

ALL OF these blueprints are drawn full-size and although the issues containing descriptions of these sets are now out of print, an asterisk in the list below denotes that constructional details are available free with the blueprint.

The index letters which precede the Blueprint Number indicate the periodical in which the description appeared. Thus PW refers to PRACTICAL WIRELESS; AW to *Amateur Wireless* and WM to *Wireless Magazine*.

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to

PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

SPECIAL NOTE

THE following blueprints include some pre-war designs and are kept in circulation for those constructors who wish to make use of old components which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.

| Title | Number | Price |
|--------------------------------|--------|-------|
| CRYSTAL SETS | | |
| Junior Crystal Set | PW94* | 2/- |
| Dual-wave Crystal Diode | PW95* | 2/6 |

| | | |
|--------------------------|-------|-----|
| STRAIGHT SETS | | |
| Battery Operated | | |
| Modern One-valver | PW96* | 2/6 |
| All-dry Three | PW97* | 3/6 |
| Modern Two-valver | PW98* | 3/6 |

| | | |
|-----------------------------|--------|-----|
| SUPERHETS | | |
| Mains Operated | | |
| A.C. Band-pass Three | PW99* | 4/- |
| A.C. Coronet-4 | PW100* | 4/- |
| A.C./D.C. Coronet | PW101* | 4/- |

| | | |
|-------------------------------------------|----|-----|
| MISCELLANEOUS | | |
| The PW 3-speed Autogram | —* | 8/- |
| The PW Monophonic Electronic Organ | — | 8/- |

| | | |
|----------------------------------|----|-----|
| TELEVISION | | |
| The PT Band III Converter | —* | 1/6 |

| Title | Number | Price |
|------------------------------------|--------|-------|
| A.C. Fury Four | PW20* | 2/6 |
| Experimenter's Short Wave | PW30a* | 2/6 |
| Midget Short Wave Two | PW38a* | 2/6 |
| Band-Spread Three (Battery) | PW68* | 2/6 |
| Crystal Receiver | PW71* | 2/- |
| Signet Two (Battery) | PW76* | 2/6 |
| Simple S.W. One-valver | PW88* | 2/6 |
| Pyramid One-valver | PW93* | 2/6 |
| BBC Special One-valver | AW387* | 2/6 |
| Short-Wave Two | AW429* | 2/6 |
| Short-Wave World Beater | AW436* | 3/6 |

| | | |
|-------------------------------------|--------|-----|
| Standard Four Valve S.W. | WM383* | 3/6 |
| Enthusiast's Power Amplifier | WM387* | 3/6 |
| Standard Four Valve | WM391* | 3/6 |
| Listener's 5-Watt Amplifier | WM392* | 3/6 |

TELEVISION

| | | |
|------------------------------------|----|-----|
| Argus Television Receiver | —* | 3/- |
| Simplex Television Receiver | —* | 3/6 |

QUERY COUPON

This coupon is available until 8th April, 1960 and must accompany all queries in accordance with the notice on our "Open to Discussion" page.

PRACTICAL WIRELESS, APRIL, 1960

Entirely New Design in Transistor Portable Radios !

"CONTINENTAL-6" Combined Portable/Car Radio.

"For Style, Quality Performance and Value for Money."

Medium and Long Wave Full Tuning.


- ★ Plessey Printed Circuit
- ★ 6 Ediswan Transistors
- ★ 5" High Fidelity Speaker
- ★ 400mW Push-Pull Output
- ★ Internal Ferrite Aerial
- ★ Slow Motion Tuning
- ★ Full Instructions
- ★ Printed Circuit marked with Component Numbers
- ★ Trimming Tool Supplied
- ★ Double Tuned I.F.s

All components available separately. Send for descriptive leaflet and prices. **CALL FOR DEMONSTRATION**

Total Cost of all Components

£11.10.0 p.p. 3/6

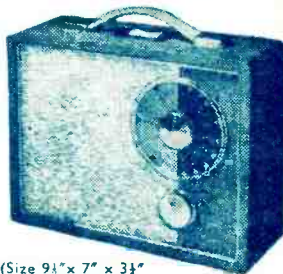including Cabinet, Battery, Transistors, Car Radio, AVC and all necessary items.



A highly sensitive and selective portable fully tunable on medium and long waves. Performs equally well as a car radio. Low running costs, good looks and care of construction combine to produce a radio equal to commercial receivers in the 20 gns. class.

(Size 9½" x 7" x 3½"
Weight 4 lbs.)

All Components for the Popular **"TRANSISTOR 8"** £10.19.6 .P. 2/6 FREE BOOKLET

MAJOR-2

(Two-transistor Pocket Radio)



69/6 TOTAL COST
P.P. 1/6.

- ★ 4-stage reflex !
- ★ Medium wave : tunable !
- ★ Very sensitive !
- ★ No aerial or earth !
- ★ Complete layout !
- ★ Over 6 months on one battery.
- ★ 4½ x 3 x 1½ in.
- ★ Weight only 4 ozs.
- ★ Personal phone.

RED-SPOT TRANSISTORS

5/- EACH

WHITE-SPOT

7/6

NEW FREE LIST ON REQUEST (See below)

MAJOR-3

(THREE TRANSISTOR POCKET RADIO)



(As Described in "R.C." Sept. 9)

- ★ 5-stage Reflex Circuit.
- ★ No Aerial or Earth.
- ★ Min. Volume Control.
- ★ 3 Ediswan Transistors.
- ★ Medium Wave Tuning.
- ★ Size 4½ x 3 x 1½ in.
- ★ Personal phone.

NEW BOOKLET FREE : All components sold separately. (Beware of Imitations.)

GOOD RECEPTION ANYWHERE !

TOTAL COST **87/6** P.P. 1/6 NEW BOOKLET FREE
FANTASTIC OUTPUT, TERRIFIC RECEPTION, GUARANTEED ANYWHERE

2-Watt Output AMPLIFIER

For connection to any Battery Portable to give up to 2 watt. Work from 12-volt battery.

Ideal for car radio use, size 4½ x 3 x 2½ in.; uses V15/10P transistor; all components (less speaker)

52/6 P. & P. 2/-

Built up and tested (less speaker) 65/- P. & P. 2/-.

Ideal for use with "Continental-6" etc.

Special offer of MERCURY Batteries

1.3 volts, 3000mA/H

Size ¾ in. diam. x ¾ in. length.

ONLY 1/3 ea. or 12/- a doz.

IDEAL FOR ALL TRANSISTOR WORK

250mW Push-Pull OUTPUT AMPLIFIER

For use with any 2, 3 or 4 transistor radio, having earpiece or headphone output. 2-transistor with speaker, battery, input socket, cabinet, etc.

59/6

P. & P. 1/6

"PRACTICAL TRANSISTOR CIRCUITS" 2/- Post Free

TRANSISTOR UNITS DESCRIBED FOR EASY CONSTRUCTION

| | Total Cost | P.P. |
|-------------------------------------------------|------------|------|
| 1 RADIO CONTROL RECEIVER (27 Mc/s) ... | 50/- | 1/- |
| 2 R.F., I.F. GENERATOR (450 kc/s to 3 Mc/s) ... | 25/- | 1/- |
| 3 LIGHT OPERATED SWITCH ... | 27/6 | 1/- |
| 4 SQUARE WAVE GENERATOR (Audio) ... | 20/- | 1/- |
| 5 SIGNAL TRACER (Audio I.F. R.F.) ... | 37/6 | 1/6 |
| 6 HEARING AID AMPLIFIER ... | 95/- | 1/- |
| 7 3-CHANNEL AUDIO MIXER ... | 42/6 | 1/- |
| 8 AUDIO GENERATOR (Amplifier Testing) ... | 25/- | 1/- |
| 9 ADDON AMPLIFIER (250mW powerstage) ... | 59/6 | 1/6 |
| 10 2 WATT POWER STAGE (for Continental) ... | 52/6 | 2/- |
| 11 BABY ALARM—100% SAFE ... | 99/6 | 2/- |
| 12 TOP BAND TRANSMITTER (1.8 to 2 Mc/s) ... | 57/6 | 1/6 |
| 13 TO 12 MC/S XTAL OSC. ... | 22/6 | 1/- |
| 14 METRE C.W. TRANSMITTER ... | 27/6 | 1/- |

ALSO TRANSISTOR DATA, EQUIVALENTS AND INFORMATION

TRANSISTORS—PRICES DOWN AGAIN ! !

Full List and Data Free on Request

MULLARD: OC44, 19/6; OC45, 18/6; OC71, 10/-; OC72, 17/-; OC72 (pairs) 32/- pr.; OC16, 54/-; OC170 (70 Mc/s), 35/-.

EDISWAN: XA102, 26/-; XA101, 23/-; XB103, 14/-; XC101, 16/-; XC101 (pairs), 32/- pr.; XC121, 17/-; XC131 (pairs), 34/-.

SEMI-CONDUCTORS: SB078 20 Mc/s, 10/-; SB305 25 Mc/s, 15/-; SB231 30 Mc/s, 22/6; SB231R 50 Mc/s, 30/-.

NEWMARKET: V15/10P 10 watts, 15/-; V15/20IP 2 watts, 25/-; V30/30P 57/-.

SURPLUS: Red Spot, 5/-; White Spot, 7/6; Photo-transistor, 10/-; OC44, 15/-; OC45, 12/6; OC72, 12/6.

WE ARE ABLE TO SUPPLY MOST OF THE COMPONENTS USED ON CIRCUITS PUBLISHED IN THIS AND OTHER MAGAZINES AND BOOKLETS. WHERE THE EXACT ITEM IS NOT STOCKED WE ARE ABLE TO RECOMMEND A SUITABLE SUBSTITUTE.

SEE OTHER ADVT. INSIDE

HENRY'S (RADIO) LTD.

Opposite Edgware Road Tube Station, PADDINGTON 1008/9

5, HARROW ROAD, EDGWARE ROAD, PADDINGTON, LONDON, W.2.
OPEN MONDAY to SAT. 9-6, THURS. 1 o'clock.