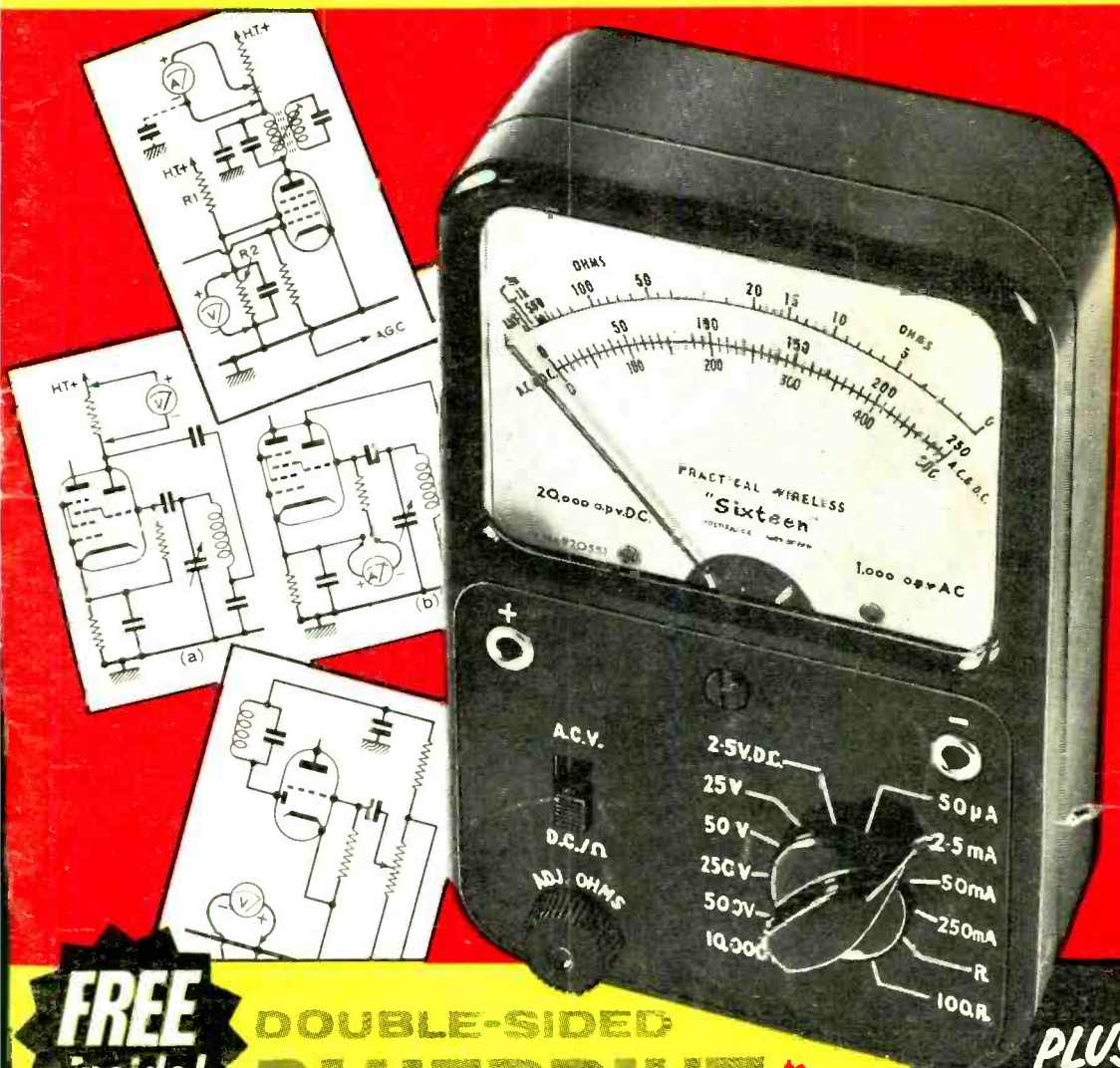


# PRACTICAL WIRELESS

JANUARY 1964

2'



**FREE**  
inside!

DOUBLE-SIDED

**BLUEPRINT**

to  
build  
this

## MULTIRANGE TEST METER

• 16 SWITCHED RANGES

• 20,000 OHMS RESISTANCE

**PLUS**

COMPLETE  
GUIDE TO  
TEST METER  
PROCEDURE




## SOLDERING INSTRUMENTS

### EQUIPMENT FOR THE RADIO AMATEUR

#### ILLUSTRATED

List 64.  
 $\frac{3}{16}$ " DETACHABLE BIT  
IN  
PROTECTIVE SHIELD  
List 700

BRIT. & FOR. PATS.

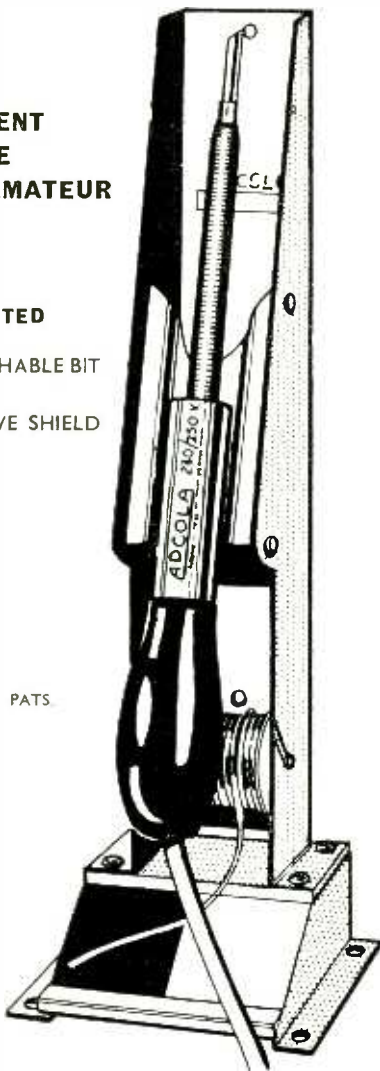

#### Sales & Service

APPLY DIRECT FOR CATALOGUE  
TO

**ADCOLA PRODUCTS LTD**  
**ADCOLA HOUSE**  
**GAUDEN ROAD, LONDON, S.W.4**

Telephones  
MACaulay 4272 & 3101

Telegrams  
SOLJOINT LONDON SW4

# Model 8 Universal AVOMETER



### Designed for Dependability

The Model 8 Universal Avo Meter is a high sensitivity multi-range a.c./d.c. electrical testing instrument providing thirty ranges of readings on a 5-inch hand calibrated scale. Range selection is effected by two rotary switches for a.c. and d.c. respectively.

The instrument has a sensitivity of 20,000 ohms per volt on d.c. voltage ranges and 1,000 ohms per volt on a.c. from the 100-volt range upwards, and meets the accuracy requirements of B.S.S.89/1954 for 5-inch scale length portable industrial instruments. It is robust, compact, and simple to operate, and is protected by an automatic cut-out against damage through inadvertent electrical overload.

VOLTAGE		CURRENT		RESISTANCE
D.C.	A.C.	D.C.	A.C.	First indication 0.5Ω Maximum indication 20MΩ
2.5V	2.5V	50μA	100mA	0—2,000Ω
10V	10V	250μA	1A	0—200,000Ω
25V	25V	1mA	2.5A	0—20MΩ
100V	100V	10mA	10A	0—200MΩ
250V	250V	100mA	—	—
500V	—	1A	—	—
1,000V	1,000V	10A	—	—
2,500V	2,500V	—	—	—
				<b>DECIBELS</b> —15dB to +15dB

Various external accessories are available for extending the above ranges of measurement. Leather carrying cases are also available if required.

Dimensions: 8½" x 7¼" x 4½". Weight: 6½ lb.

Write for fully descriptive Folder or for complete Catalogue of AVO Instruments.



**AVO LTD**

AVOCET HOUSE, 92-96 YAUXHALL BRIDGE ROAD,  
LONDON, S.W.1

Tel: VICtoria 3404 (12 lines)



## TRANSISTORS & DIODES

**GUARANTEED TOP QUALITY**  
Huge reductions. Red Spot  
standard L.F. type now  
only **1/6**  
White Spot R.F. **2/-**

Mullard Matched Output Kits  
(OC81D and 2-OC81's) **12/6**

R.F. Kits (OC44, OC45  
(2), 3 transistors) **12/6**  
AF114 8/- OC44 5/8  
AF115 7/8 OC45 5/8  
AF116 7/8 OC72 5/8  
AF117 7/- OC81 5/8  
AF127 9/8 OC81D 5/8  
OC28 12/8 OC82 6/-  
OC38 14/8 OC170 8/8  
OC171 8/8

## GERMANIUM DIODES

General Purpose miniature de-  
tector A.V.C. etc. or 6/8 doz. **8d.**

Gold Bonded highest quality.  
Individually tested. **1/-**  
9/8 doz.

## SILICON POWER RECTIFIERS

Guaranteed performance. Top  
Make. Tested 250 V working.  
**100mA 3/9 350mA 7/6**  
(3 for 9/8) (3 for 19/8)

## 3 VALVE AMPLIFIERS

Kit of new parts, consisting chassis,  
main and output transformers, valves  
(P61, 6X5G, 6X5G) and all components.  
With full instructions for making high  
gain amplifier with separate bass and  
treble controls, negative feedback,  
etc. Truly unequalled value **29/-**

**LINE TRANS.** s.a.e. enquiries.  
Huge quantity, most  
makes at only **29/-**

**TURRET TUNERS**  
Most makes, your choice if avail-  
able, with valves 18/-, less valves  
10/-, S.A.E. enquiries.

CO-AX, low loss, 6d. yd., 25 yds.  
11/6, 50 yds., 22/-, 100 yds., 42/6.  
Co-ax Plugs, 1/3. Wall outlet boxes 3/6.

**SPECIAL C.R.T. OFFER**  
Due to huge Bulk Special Purchase  
are offering MW 31-74 Tubes at the  
unrepeatable price of 29/-, MW  
30/24 ditto, 39/-, P.P. 12/5. The  
above are guaranteed for 6 months.

**LOUDSPEAKERS.** 3 Ω Top Makes.  
6in. **7/6** 5in. **5in.**  
8in. **7 x 4in. 8/6**

## Tubes

Carr. & Ins. 12/6.

		HIGHEST QUALITY— COMPARE OUR PRICES		
		6 Months	12 Months	NEW TYPES
MOST MULLARD.				
MAZDA, COSCOR.	12in.	£2. 0. 0	£3. 0. 0	MW 31/74 £3.15.0
EMITRON, EMIS- SCOPE, BRIMAR.	14in.	£2.10.0	£3.10.0	MW 39/24 £4.15.0
FERRANTI TYPES, PROCESSED IN OUR OWN FACTORY	15-17in.	£3. 5. 0	£4. 5. 0	CRM 172 MW 43/64 £6.0.0
	21in.	£3.15.0	£5.15.0	

## BULK BARGAINS

12 POTS. Popular values. 5K to  
2 Meg. Unused, mixed, pre-  
set, long sp., switched, etc. **4/6**  
CONDENSERS. 25 Mixed. Electrolytic.  
Many popular sizes. List  
Value £5. Our Price **10/-**

**100 RESISTORS 6/6**  
Excellent. Sizes 1/2 watt.

**100 CONDENSERS 9/6**  
Miniature Ceramic and Silver Mica  
Condensers. 3 pF to 5,000 pF. LIST  
VALUE OVER £5.

**25 TAG STRIPS 4/-**  
2, 4, 6, 8 way etc. Unused.

**100 HI STABS 9/6**  
1% to 5% 100 Ω to 5M Ω.

TELEPHONE C.O.D. ORDERS  
DISPATCHED THE SAME DAY.

## MAINS TRANSFORMERS

Excellent Quality. Guaranteed.  
Upright mounting 250-0-250 V  
80 mA, 6.3 V 3 A. **9/6**  
Ditto semi-shrouded 9/6. Ditto up-  
right 80 mA 12/6.

## TWEETERS

Famous German electrostatic LSH75  
easily fitted without extra transformer  
into existing radios. Loud-  
speakers, etc. **4/6**

## AM/FM TUNING CONDENSERS

400 + 400 pF and 15 + 15 pF. Top  
Quality. Ideal for communications  
receivers to give bandspread on am-  
ateur bands. Built-in slow  
motion. **5/6**

## CONNECTING WIRE

P.V.C. Bright colours. Five  
25ft. coils only **4/-**

## MIDGET TRIMMERS

3-30 pF. ceramic base standard  
receiver type. (6 for 2/8) **6d.**

## KEENER PRICES VALUES

by return of post  
THE MOST ATTRACTIVE COMPETITIVE VALVE  
LIST IN THE COUNTRY

All valves are new and unused unless otherwise advised

POST	3 MONTHS GUARANTEE	FREE TRANSIT IN- SURANCE.	Satisfaction or Money back Guarantee on Goods if returned within 14 days.
1 Valve 6d., 2-11, 1/-. FREE for 12 or more valves.	1n writing with every valve.		

02A	4/9	6K7	7/3	20D1	8/8	DL82	8/9	EZ40	5/6	U18	7/6
1A7GT	3/1	8K7G	1/9	20P2	9/8	DL92	4/8	EZ41	6/-	U22	5/9
1C5GT	7/-	8K7GT	4/3	20L1	11/6	DL94	5/8	EZ80	4/8	U24	12/6
1D5	6/8	6K8G	4/9	20P1	9/8	DL96	6/8	EZ81	4/8	U25	8/8
1D6	9/8	6K8GT	8/3	20P3	9/8	EA50	1/3	FW4500	7/9	U26	7/8
1H5GT	8/-	8K25	9/8	20P4	13/6	EA50	6/8	GT1C	9/9	U31	6/8
1L4	3/8	6L1	8/9	20P5	12/6	EA91	3/9	GZ32	7/3	U33	14/-
1LD5	4/-	6L6	7/8	25A6G	7/9	EA92	7/6	GZ34	10/6	U35	12/6
1LN5	4/8	6L6G	6/8	25L6GT	6/-	EB34	1/3	HABC80	9/8	U37	23/3
1N5GT	8/-	6L18	7/3	25V5G	7/9	EB41	4/8	HL41DD	8/8	U39	4/9
1R5	4/8	6L19	12/6	25Z4G	6/8	EB81	2/8	HVR2	5/6	U52	4/9
1S4	7/8	6L20	5/9	25Z6	7/9	EB83	3/8	KT31	6/8	U76	5/6
1S5	3/8	6N7	5/-	25Z6G	6/-	EB84	7/8	KT33C	4/-	U78	4/8
1T4	2/8	6P1	12/6	27S4	17/6	EB81	6/8	KT36	14/-	U107	12/6
1U5	5/3	6P25	7/-	30C1	5/9	EBF80	6/8	KT44	5/6	U191	9/8
2D21	5/3	6P28	9/8	30C15	9/8	EBF83	7/8	KT55	17/6	U281	9/8
3A4	4/-	6A7G	5/6	30F5	6/-	EBF89	7/8	KT57	7/8	U282	12/6
3A5	8/8	6A7GT	7/9	30P11	9/8	EBL21	9/8	KT63	4/8	U301	11/6
3D6	4/-	6R7G	6/-	30L1	5/6	EC52	4/3	K.96	12/6	U309	5/8
3Q4	6/8	6SA7	5/9	30L15	9/8	EC91	3/-	KT77	7/9	U329	9/8
3S4	4/8	6SC7	4/8	30P4	9/8	EC92	7/8	KT88	19/8	U339	9/8
3V4	5/8	6SG7	4/8	30C12	7/3	EC93	5/8	KT91	5/6	U403	9/8
5T4	7/9	6S7	3/-	30P19	9/8	EC93C	3/8	KTW62	5/6	U404	5/9
5U4G	4/9	6SK7	4/8	30P13	8/8	EC93	4/8	KTW63	5/6	U408	16/6
5V4G	7/3	6SL7GT	5/9	35C5	8/8	EC93C	5/9	L63	3/-	U432	7/8
5Y3G	4/9	6S8GT	4/8	35L6GT	7/3	EC94	7/8	ML52	5/6	U441	6/8
5Y3GT	4/9	6S8GT	4/8	35W4	5/6	EC94	3/8	MU14	5/6	U4C41	6/8
5Y4G	8/9	6S8T	3/6	35Z4GT	4/8	EC92	4/8	N37	10/6	U4C81	6/8
5Z4	9/-	6U4GT	9/8	35Z5GT	6/8	EC93	5/6	N78	11/6	U4F80	9/8
5Z4G	7/-	6V8G	4/3	41	6/8	EC94	6/8	N108	13/6	U4F81	9/8
5Z4GT	9/8	6V8GT	4/8	42	5/9	EC95	6/8	N122	10/6	U4L21	10/6
6A0L	3/8	6X4	4/6	50B5	6/8	EC95	10/6	P41	3/6	U4C92	7/8
6A6	3/9	6X5G	4/9	50C5	6/8	ECF90	6/8	P61	2/6	U4C84	9/8
6A7	9/-	6X5GT	6/-	50L6GT	7/-	ECF82	7/3	PACB80	7/8	U4C85	6/8
6A8G	6/8	7B6	8/9	53K1	10/8	ECF81	10/8	PC80	10/3	U4C86	11/6
6A8GT	12/6	7B7	7/8	53L1	17/6	ECF83	7/8	PC97	8/-	U4C91	9/8
6A97	7/8	7C5	7/3	62BT	13/6	ECF82	7/8	PC98	5/6	U4C92	6/8
6AG5	2/6	7C6	7/-	75	7/8	ECF81	6/8	PC95	7/8	U4C91	6/8
6AG7	5/9	7H7	5/9	78	4/8	ECF83	7/8	PC98	11/6	U4C82	8/8
6AK5	4/9	7R7	14/-	80	5/3	ECL80	5/9	PC98	9/8	U4C83	7/8
6AL5	2/3	7Y4	5/-	81	9/8	ECL82	5/9	PCF89	10/6	U4F41	7/8
6AM6	2/9	7A	4/8	185BT	10/6	ECL83	9/8	PCF80	5/9	U4F42	5/3
6AQ5	5/9	8D3	2/9	185BT10/6	ECL86	9/-	PCF82	6/8	PCF84	9/2	
6AT6	5/-	10C1	9/8	807(A)	8/-	EF22	6/6	PCF84	9/2	U4F85	7/8
6AU6	8/-	10C2	12/6	807E	5/9	EF22	3/3	PCF86	8/9	U4F89	6/8
6AV8	5/6	10C3	9/8	813	4/8	EF24	6/8	PCF88	8/9	U4L41	6/8
6B7	8/-	10F9	10/-	832	14/-	EF24	4/8	PCF83	8/8	U4L44	14/-
6BBG	3/-	10F18	9/8	866A	11/6	EF40	9/9	PCF84	9/8	U4L46	8/9
6BA8	5/6	10LD11	12/6	954	3/6	EF41	6/8	PCF85	8/8	U4L48	8/9
6BE8	5/-	10P13	8/8	955	2/3	EF42	5/9	PCF86	5/6	U4L49	8/9
6BG6G	13/-	12H7	9/8	956	2/-	EF43	7/8	PCF87	5/6	U4L50	8/9
6B16	5/6	10P18	6/9	1825	5/6	EF50(A)	2/6	PCF84	7/9	U4U6	9/9
6B16	5/6	12A8	2/3	5763	7/6	EF54	3/3	PCF84	4/8	U4U7	8/8
6BR7	8/-	12A8H	9/-	9001	3/-	EF80	3/8	PL33	9/8	U4U8	11/6
6BR8	5/-	12A76	6/8	9002	4/8	EF85	5/6	PL38	8/3	U4Y1N	10/6
6BW6	6/8	12A77	3/9	9003	5/9	EF86	6/8	PL38	15/-	U4Y21	8/6
6BW7	5/-	12A86	7/6	ATP4	2/-	EF89	5/9	PL51	7/9	U4Y41	6/9
6C4	2/3	12A77	4/3	ATP1	6/8	EF91	2/9	PL52	5/8	U4Y85	4/9
6C5	5/6	12A86	6/8	AZ41	6/8	EF92	2/6	PL83	5/3	U4Y86	2/3
6C8	3/-	12AX7	5/6	B36	6/8	EF93	8/8	PL84	5/3	U4Y87	5/3
6C9	10/6	12BA6	6/8	C10	8/-	EF84	9/6	PL89	7/9	U4Y88	5/3
6CDB6	18/6	12BA8	6/8	CH35	12/6	EC32	5/9	PM54	9/8	U4Y89	5/6
6CH6	5/-	12BH7	7/-	CL33	3/6	EX4	9/8	PM54	9/8	U4Y90	5/6
6D2	2/3	12C8	3/8	CY31	6/8	EL33	7/-	PX25	8/9	U4Y91	5/9
6D3	8/6	12E1	16/-	D77	2/3	EL34	9/8	PX31	6/8	U4Y92	11/6
6D6	3/-	12H8	9/8	D80	11/6	EL35	9/8	PX39	9/8	U4Y93	11/6
6E1	6/6	12H9T	2/9	DA32	8/-	EL38	11/6	PY33	9/8	U4Y94	5/6
6E6	6/9	12I7GT	7/9	DAF91	4/6	EL41	7/6	PY80	5/6	U4Y95	5/6
6E6G	4/8	12K7GT	4/8	DAF96	6/8	EL42	7/9	PY81	5/3	U4Y96	5/6
6F13	4/8	12K8G	9/8	DEF3	8/-	EL81	8/8	PY82	5/3	U4Y97	11/6
6F14	4/8	12K9G	9/8	DF91	2/9	EL84	9/8	PY83	5/3	U4Y98	11/6
6F15	6/8	12K7GT	4/8	DF96	6/8	EL85	7/9	PY88	8/-	U4Y99	21/6
6F19	5/6	12SA7	6/8	DF97	7/6	EL91	2/3	PY800	7/3	Y63	5/6
6F32	4/-	12SG7	3/8	DH63	5/6	EL95	6/-	PZ30	9/8	Y66	5/6
6F33	4/-	12SH7	3/8	DH78	4/8	EM34	6/8	PZ30	9/8	Y68	5/6
6H6	4/8	12D7	5/8	DK32	8/-	EM80	6/8	RL18	9/8	Z66	7/8
6J5	4/9	12SK7	4/8	DK91	4/9	EM81	7/8	SP41	2/-	U4Y99	5/6
6J5G	3/-	12SN7GT	6/8	DK92	6/8	EM84	8/-	SP61	2/-	U4Y99	5/6
6J5GT	4/8	12SQ7	8/-	DK96	7/3	EM85	9/-	SU25	16/-	U4Y99	5/6
6J8	3/-	12SR7	4/8	DL33	7/3	EN31	6/8	SU2150	16/-	U4Y99	5/6
6J7GT	7/8	12A95	6/8	DL35	7/-	EY51	6/8	TD4	8/8	U4Y99	5/6
6K6GT	7/8	12A95	6/8	DL35	6/8	EY98	5/9	TD4	8/8	U4Y99	5/6
6K6GT	14/-	12L75	6/8	DL75	6/8	EY98	5/9	U14	7/8	U4Y99	5/6

100%  
TYPES  
NOT  
LISTED  
S.A.E.

Post: 2 lbs. 2/-, 4 lbs. 2/6, 7 lbs. 3/6, 15 lbs. 4/-, etc. (C.O.D. 2/- extra). ALL ITEMS LESS 5% AND POST FREE IN

# Make Your Ability PAY

**UNLIMITED OPPORTUNITIES** exist today for "getting on" . . . but only for the fully trained man. Let I.C.S. tuition develop your talents and help you to success.

**STUDY IS EASY** with I.C.S. guidance. The courses are thorough. Printed manuals, fully illustrated, make study simple and progress sure.

**YOUR ROAD TO SUCCESS** can start from here—today. Complete this coupon and post it to us, for full particulars of the course which interests you. **MODERATE FEES INCLUDE ALL BOOKS.**

## Take the right course now . . .

### ADVERTISING & ART

Copywriting  
Layout & Typography  
Commercial Illustrating  
Oil & Water Colour

### BUILDING & CIVIL ENGINEERING

Architecture, Bricklaying  
Building Construction  
Builders Draughtsman  
Interior Decoration  
Quantity Surveying  
Heating & Ventilation  
Carpentry & Joinery

### COMMERCE

Book-keeping  
Accountancy & Costing  
Business Training  
Office Training  
Purchasing, Storekeeping  
Secretariats  
Shortland & Typing  
Computer Programming  
Small Business Owners

### DRAUGHTSMANSHIP

Architectural, Mechanical  
Drawing Office Practice

### ELECTRONICS

Computer & Maintenance  
Electronic Technicians  
Industrial Electronics

### FARMING

Arable & Livestock  
Pig & Poultry Keeping  
Rabbits & Chinchillas

### GENERAL EDUCATION

G.C.E. subjects at Ordinary &  
Advanced Level  
Good English  
Foreign Languages

### INTENSIVE COACHING for all principal examinations

—G.C.E., Secretaryship, Accountancy, Engineering,  
Work Study, Management, Radio, Architecture and  
Surveying.

Member of the Association of British Correspondence Colleges

*Start today the I.C.S. way!*

### INTERNATIONAL CORRESPONDENCE SCHOOLS

(Dept. 172)

Intertext House, Parkgate Rd., London, S.W.11.

Send FREE book on \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_


Occupation \_\_\_\_\_

1.64

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

## NEW YEAR STOCKROOMS MUST BE

### MINIATURE SPY CAMERA

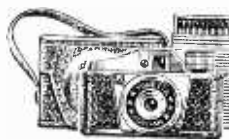

FREE Leather Carrying Case  
and 6 Rolls of film.

**ONLY 20/-**

**NO MORE TO PAY**

World Shattering Purchase By Our FOREIGN AGENTS Makes this exciting  
scoop yours for Only 20/-. This exciting little camera is not a toy but a  
precision made photographic instrument in chrome steel and leather with  
minute multi-magnifying lens—each 14 mm. film takes 10 pictures—  
size 1 1/4 x 1 1/4 x 2 1/4 in.—ONLY 20/- P. & P. 2/6 extra. (C.O.D. extra.)

Stock No. 144—BRAND NEW 2 1/2 in. MOVING COIL LOUD-  
SPEAKERS. SPECIAL PRICE 9/6, plus 1/6 P. & P. 30 ohms.

Stock No. 145—BRAND NEW ASSORTED RESISTORS in packets of  
100, 5/-, plus 5d. P. & P.  
Stock No. 146—4 PIN BATTERY PLUGS (Pits Ever Ready Batteries  
B114 etc.) 3 for 1/-, plus 3d. P. & P.  
Stock No. 147—4 PIN SOCKET PANELS to fit above, 3 for 1/-, plus  
3d. P. & P.  
Stock No. 148—2 PIN BATTERY PLUGS, 6 for 1/-, plus 3d. P. & P.  
Stock No. 149—FERRITE RODS 6 1/2 in. long by 3/4 in. diameter. Price 1/6,  
plus 1/- P. & P.  
Stock No. 150—4 WAY SOCKET STRIPS. Takes Standard Wander  
Plugs, 3 for 1/-, plus 3d. P. & P.

Stock No. 151—BRAND NEW "PLESSEY" MOVING COIL  
SPEAKERS, 2 1/2 in. 80 ohms. Matches Transistor Direct—No O.P.T.  
needed. Special prices 12/6, plus 1/6 P. & P.

Stock No. 152—BRAND NEW H.F. TRANSISTORS. (Equivalent  
to 0071). OUR PRICE 2/6, plus 3d. P. & P.

Stock No. 153—BRAND NEW "EDISWAN" L.F. TRANSISTORS,  
TESTED, 1/6, plus 3d. P. & P.

### NO EARTH OR AERIAL REQUIRED

### ALL TRANSISTOR RADIO



**ONLY 35/-**

THE COSTA BRAVA

Revolutionary INTERNAL  
FERRITE AERIAL makes  
this sensational pocket-size  
radio the best money-  
saving bargain of all time.  
Powerful, superb tone and  
clarity, ensures perfect  
reception for all your  
favourite programmes.

Completely portable, only 5 1/2 x 3 x 1 1/4 in. Two-tone

case. Anyone can assemble with our simple  
PRINTED CIRCUIT PLAN. Send 35/-, plus 2/6 P. & P. (C.O.D. 2/-  
extra). Satisfaction guaranteed. (All parts available separately).  
**FREE** HIGH SENSITIVITY HIDE-AWAY EAR-PIECE GIVEN  
WITH EACH SET.

### "OUR NEW 4-STAGE MINUETTE"

Build this newly-designed "MINUETTE" 4-STAGE transistor  
set in very strong ready drilled ULTRA-MODERN CASE, size  
only 6 x 3 1/4 x 1 1/4 in. Uses three transistors and diode and SELF-  
CONTAINED LOUDSPEAKER. Very  
sensitive, ideal for office, bedroom,  
holidays, etc. Months and months  
of listening on an 8d. battery. Can  
be built FOR ONLY 30/- including  
PROPER CASE, miniature speaker,  
etc. SIMPLE AS A.B.C. PICTORIAL  
STEP-BY-STEP PLANS etc., plus  
post and packing 1/6 (C.O.D. 2/-  
extra). Parts sold separately, priced  
parts list 1/-.

**30/-**



D.D. of Huddersfield  
writes:—"I have fitted all  
the parts and it is working  
wonderfully."

M.B. of Wellingborough  
writes:—"I would like to  
say how pleased my son is  
with the radio. He has it  
working already."

L. E. Crumlin writes:—"Thank you for the 'SAN  
REMO' radio parts which is far  
superior than expected."

### TERMS OF BUSINESS

C.O.D. 2/6 extra, regret no  
C.O.D. under £1. Add extra  
postage for overseas. Special  
prices for quantity and the  
Trade. All goods guaranteed.  
Components, technical books  
Hi-Fi by Leak, Jason, Lorenz,  
Quad, etc., etc. Send S.A.E.  
for quotation or with any  
enquiry.

### CONCORD ELECTRONICS

PERSONAL CALLERS WELCOME



# CLEARANCE SALE—PRICES SLASHED CLEARED TO MAKE WAY FOR 1964 STOCKS

Stock No. 101—Few Only MAINS BURG-  
LAR ALARMS. With complete set of door  
and window microswitches and connecting  
wires etc. Advertised at 75 p.p. OUR PRICE  
to clear 3/6, plus 3/- P. & P.

Stock No. 102—BRASS RIGHT ANGLE BRAC-  
KETS, drilled with 2 holes. Approximately 1in.  
square. Only 9d. a pair.

Stock No. 103—9 ONLY ELECTRIC SHOE  
BRUSHES. To clear 8/6, plus 1/6 P. & P.

Stock No. 104—MINIATURE MEDIUM WAVE  
TUNING COILS with reaction winding. Clearance  
price 2/- each, plus 6d. P. & P.

Stock No. 105—39 ONLY PRECISION CAMERAS.  
Taken 127 film. To clear 8/6 each, plus 1/6 P. & P.  
Stock No. 106—193 ONLY MINIATURE PLAS-  
TIC RADIO CABINETS, complete with Chrome  
carrying handles. Dial and tuning knob. Size  
5 1/2 x 3 1/2 x 1 1/2 in. Clearance price only 5/6, plus 1/-  
P. & P.

Stock No. 107—PRINTED CIRCUITS of 3  
Transistor Reflex Radio made to fit above radio,  
2/6, plus 1/6 P. & P.

Stock No. 108—MINIATURE PRINTED RADIO  
CABINETS, 5 x 3 1/2 x 1 1/2 in. 3/6 each to clear, plus  
6d. P. & P.

Stock No. 109—BEAUTIFUL MINIATURE  
SIZE PLASTIC RADIO CABINETS. Size  
5 x 3 x 1 1/2 in. Printed and ready drilled. OUR  
PRICE 3/6, plus 1/- P. & P.

Stock No. 110—MINIATURE PLASTIC RADIO  
CABINETS unprinted. Size 3 x 2 1/2 x 1 1/2 in., 2/6  
each to clear, plus 6d. P. & P.

Stock No. 111—BEAUTIFULLY MOULDED  
MINIATURE PLASTIC RADIO CABINETS,  
complete with tiny carrying handle and tuning  
knob. Size 4 x 2 1/2 x 1 1/2 in. Price to clear 3/6, plus  
1/- P. & P.

Stock No. 112—Specially Printed Circuits for  
above cabinet of two transistor reflex radio, 2/6,  
plus 6d. P. & P.

Stock No. 112—EXCEPTIONALLY GOOD  
LOOKING PLASTIC RADIO CABINETS  
"SLIM LINE". Size 6 x 3 1/2 x 1 1/2 in. Clearance  
price 5/6, plus 9d. P. & P.

## AMAZING CIGARETTE RADIO only 18/6



Complete set of parts.

Amaze your friends!

—this highly sensitive

TRANSISTOR "CI-

GARADIO" receives

all medium wave

stations clear and

crisp—holds ten cigar-

ettes—weighs less than

3 ozs. with cigarette

tinny battery inside

—parts sold separately,

priced parts list 1/-.

costs 3d. and lasts over three months. This brilliant  
little novelty personal phone radio is ideal for  
Bedside, News, Sports, Office. Can be built by  
anyone from our simple pictorial diagrams in an  
hour or two. All parts supplied for 18/6 (add 1/6  
P. & P.). C.O.D. 2/- extra. (Parts sold separately,  
priced parts list 1/-).

Stock No. 113a—BEAUTIFUL BLACK & GOLD  
READY DRILLED FRONT RADIO PANELS  
TO GO WITH THESE, 5/-, plus 1/- P. & P.

Stock No. 114—MINIATURE RADIO CAB-  
INETS IN GOLD not drilled. Size 4 1/2 x 3 x 1 1/2 in.  
Give away price 2/6, plus 6d. P. & P. Special  
carrying cases for above at 1/6, plus 6d. P. & P.

Stock No. 115—RADIO CABINETS same as  
as specified as above, but upright design, 2/6 each,  
plus 6d. P. & P.

Stock No. 115a—Special carrying case for above  
at 1/6, plus 6d. P. & P.

Stock No. 116—ANOTHER TYPE RADIO  
CABINET, horizontal, 2/6 each, plus 6d. P. & P.

Stock No. 125—BRAND NEW MAGNETIC  
DEAF AID TYPE EARPIECES, complete  
with Plug and Socket. 300 ohms. OUR  
SPECIAL PRICE 5/-, plus 6d. P. & P.

Stock No. 126—BRAND NEW CRYSTAL  
DEAF AID TYPE EARPIECES. Our  
price 4/-, plus 6d. P. & P.

Stock No. 128—3in. PLASTIC CARRYING  
HANDLES with fixing screws, 6d. each, plus 6d.  
P. & P.

Stock No. 129—BRAND NEW ASSORTED  
RADIO KNOBS including pointer types, 6/- a doz  
plus 9d. P. & P.

Stock  
No. 130.



**SELL SAFETY TO THE  
MOTORIST**  
**AUTOMATIC  
CIGARETTE LIGHTER**  
Instantly provides ready  
lit cigarette, without the  
driver taking his eyes from the road.  
Heavily chromium plated case holds 10.  
Easily and simply fitted to any car's dash-  
board. Works off 6 or 12 volts. Retail Price  
44/9. Special Clearance offer only  
sold in minimum lots of 6, **10/6** ea.  
Carriage free.

Stock No. 117—477 SUB-MINIATURE TRANS-  
ISTOR RADIO CASES (Plastic, unprinted).  
Size only 1 1/2 x 1 1/2 x 1/2 in. To clear 1/- each, plus  
6d. P. & P.

Stock No. 118—SPRING TERRY CLIPS for  
holding Miniature Valves. Price for 3, 1/-, plus  
6d. P. & P.

Stock No. 119—72 ONLY MINIATURE 6 TAG  
COILS covering Medium Wave and Long Wave  
with reaction winding. Price to clear 3/- each,  
plus 6d. P. & P.

Stock No. 120—SIMILAR TO ABOVE but  
Medium Wave only 2/- each, plus 6d. P. & P.

Stock No. 169.

## "VOLKSRADIO" POCKET RADIO ONLY 15/-

Take - Over Bid  
makes this Fan-  
tastic Offer possible  
—the beautifully  
compact "5 Star  
Volkstaradio" meas-  
uring 4 1/2 x 2 1/2 x  
1 1/2 in. receives per-  
fectly—in the bed-  
room, office, garden—over all medium waves  
(incl. Luxembourg). Under 1d. hour running  
cost. Anyone can assemble it in 1 or 2 hours.  
Use our simple A B C plan. Complete set of  
parts. Only 15/-, plus 1/6 P. & P. C.O.D. extra.  
(Parts can be bought separately).



Stock No. 137—BRAND NEW TRIMMER  
"CYLON", 250 pF. To clear 1/- each, plus 4d.  
P. & P.

Stock No. 138—MINIATURE ACORN VALVES.  
Type 954, 9d. each, plus 6d. P. & P.

Stock No. 139—6K7G BRAND NEW VALVES,  
2/9, plus 9d. P. & P.

Stock No. 140—5V6G VALVES, 4/6, plus 9d.  
P. & P.

Stock No. 141—11A BRAND NEW VALVES.  
1/9, plus 6d. P. & P.

Stock No. 142—BRAND NEW B7G VALVE  
HOLDERS, 6d., plus 4d. P. & P.



## THE MINUTE TRANSISTOR RADIO

## MIAMI

## ONLY 17/6

Unbelievably small—out-  
standingly cheap. You  
will be amazed at the fine quality of tone and  
volume of this great little radio. Only a fantastic  
3 1/2 x 2 1/2 x 1 1/2 in. the MIAMI will bring you great  
entertainment for months on an 8d. battery.  
Simple assembly plan with each set. ONLY 17/6.  
FREE 17/6. Plus 2/6 P. & P. C.O.D. 2/- extra.  
Satisfaction guaranteed. Demonstrations given  
daily. Parts available separately if required.

### TERMS OF BUSINESS

C.O.D. 2/- extra, regret No C.O.D. under £1.  
Add extra postage for overseas. Special prices  
for quantity and the Trade. All goods guaranteed.  
Components, technical books, Hi-Fi by Leak,  
Jasen, Lorenz, Quad, etc. Send S.A.E. for  
quotation or with any enquiry.

Stock No. 121—MEDIUM WAVE LOOPSTICK  
COILS with Variable Tuning Core, 73 only.  
To clear 2/9 each, plus 6d. P. & P.  
Stock No. 122—FEW ONLY VARIABLE TUN-  
ING CONDENSER (Mica Dielectric)—0005 mfd.  
3/6, plus 6d. P. & P.  
Stock No. 123—173 RADIO DIALS, Printed  
Medium and Long Wave, Squat Shape, Size  
4 1/2 x 3 1/2 in. with central hole. Price 1/8, plus  
3d. P. & P.  
Stock No. 124—SUB-MINIATURE DIODES,  
all brand new and tested. Clearance price 3 for 1/-  
plus 3d. P. & P.

## Stock No. 170 TRANSISTOR PKT RADIOS

**BULK PURCHASE  
ENABLES US TO  
MAKE THIS FAN-  
TASTIC OFFER  
—AND WITH  
MONEY BACK  
GUARANTEE!!!**  
The "SAN REMO"  
... so tuned that it  
brings the voices of  
star entertainers  
and vocalists dramati-  
cally to life—in  
your home, office,  
etc. Only 4 1/2 x 2 1/2  
x 1 1/2 in. Fits easily  
into your pocket  
or handbag. Works  
for months off 1/2  
battery. Should last a lifetime, anyone  
can assemble it in an hour or two with our  
easy plan. Complete set of parts including  
miniature speaker, carrying case—everything  
only 28/6. P. & P. 2/6. C.O.D. 2/6 extra.  
(Parts can be bought separately). Limited  
period—so rush your order before it too  
late. DEMONSTRATIONS DAILY.

## ONLY 28/6

No More To Pay.  
Complete set of parts  
into your pocket  
or handbag. Works  
for months off 1/2  
battery. Should last a lifetime, anyone  
can assemble it in an hour or two with our  
easy plan. Complete set of parts including  
miniature speaker, carrying case—everything  
only 28/6. P. & P. 2/6. C.O.D. 2/6 extra.  
(Parts can be bought separately). Limited  
period—so rush your order before it too  
late. DEMONSTRATIONS DAILY.

Stock No. 154—BRAND NEW MINIATURE  
ELECTROLYTIC CONDENSERS 100 mfd.  
12V. Our price 1/6 each, plus 6d. P. & P.

Stock No. 155—30 mfd. 12V. condensers, 1/8 each,  
plus 6d. P. & P.

Stock No. 156—24 mfd. 25V. condensers, 1/8 each,  
plus 6d. P. & P.

Stock No. 157—16 mfd. 30V. condensers, 1/6 each,  
plus 6d. P. & P.

Stock No. 158—12 mfd. 50V. condensers, 1/6 each,  
plus 6d. P. & P.

Stock No. 159—10 mfd. 12V. condensers, 1/- each,  
plus 6d. P. & P.

Stock No. 160—5 mfd. 50V. condensers, 1/3 each,  
plus 6d. P. & P.

Stock No. 161—4 mfd. 100V. condensers, 1/- each,  
plus 6d. P. & P.

Stock No. 162—BRAND NEW SUB-  
MINIATURE ELECTROLYTIC CON-  
DENSERS, 100 mfd. 12V., 2/- each, plus  
6d. P. & P.

Stock No. 163—BRAND NEW ASSORTED  
CONDENSERS 50 pF to .01 mfd., 25 for 7/6,  
plus 1/- P. & P.

Stock No. 164—SPECIAL OFFER OF HOME  
CONSTRUCTED RADIOS NEEDING ATTEN-  
TION. Filled with components in good condition  
Stock No. 164a—TYPE (A) 3 Transistor printed  
circuit radios in Beautiful Miniature Cases.  
Size 3 1/2 x 3 1/2 x 1 1/2 in. Price 15/-, plus 2/- P. & P.

Stock No. 164b—TYPE (B) 2/3 Transistor. Size  
4 1/2 x 3 x 1 1/2 in. Price 5/- each, plus 1/- P. & P.

Stock No. 164c—TYPE (C) Miniature Coil Speakers, worth  
1d., given free with every order for five.

Stock No. 164d—TYPE (D) 2 Transistor Printed  
Circuit reflex Radios in beautifully Moulded Case.  
Size 4 x 2 1/2 x 1 1/2 in. Price 10/-, plus 1/6 P. & P.

Stock No. 164e—TYPE (E) Miniature Valves in  
plastic case. Size approximately  
5 x 3 x 1 1/2 in. Price 5/-, plus 1/6 P. & P.

Stock No. 164f—TYPE (F) 20 only Valve Radios  
in small Fibre attaché cases. Size 7 x 5 x 2 1/2 in.  
Price 22/6, plus 2/6 P. & P.

Stock No. 165—SURPRISE PARCEL TYPE (a).  
Assorted components. Price 5/-, plus 1/6 P. & P.

Stock No. 166—SURPRISE PARCEL TYPE (b).  
Containing 3 times the above components. Price  
12/6, plus 1/6 P. & P.

Stock No. 167—GIANT SURPRISE PARCEL  
TYPE (c). Price 15/-, plus 2/- P. & P.

Stock No. 132—WANDER PLUGS. New and  
unused. 2/- doz., plus 6d. P. & P.

Stock No. 134—5in. MOVING COIL LOUD-  
SPEAKERS. Brand new, 3 ohms, 10/-, plus  
2/6 P. & P.

**CONCORD ELECTRONICS (Dept. P.W.3) 210 Church Road, Hove, Sussex**

PERSONAL CALLERS WELCOME:—

Open 8.30 a.m. until 1 p.m. and 2 p.m. until 5.30 p.m.

Saturdays: 8.30 a.m. to 1 p.m.

★ Demonstrations Daily.

EQUIPMENT FOR HOME,  
AMATEURS, COMMUNICATIONSINSTRUMENTS FOR TEST  
SERVICE AND LABORATORY

*You can Build the world's best kit-sets; save money and enjoy yourself the Heathkit way*

*The clearly written instruction manuals, issued with each kit, show you how.*

DEFERRED TERMS ON ORDERS ABOVE £10. ALL MODELS ALSO AVAILABLE ASSEMBLED

## TEST INSTRUMENTS



5in. OSCILLOSCOPE. Model 0-12U. Laboratory quality at utility oscilloscope price. Wide band amplifiers essential for T.V. servicing, F.M. alignment, etc. T/B covers 10 c/s-500 kc/s in 5 ranges.

£43.10.0 assembled. **£35.10.0** Kit

PORTABLE 'SCOPE. Model OS-1. A compact portable oscilloscope, ideal for servicing and general work. Printed circuit board. Case: 7½ x 4½ x 12½in. long. Wt. only 10½ lbs.

£29.8.0 assembled **£21.18.0** Kit

ELECTRONIC SWITCH. Model S-3U. Converts a single beam oscilloscope into double beam operation.

£18.10.0 assembled **£12.18.0** Kit



V-7A

VALVE VOLTMETER. Model V-7A. The world's best selling VTVM. Measures up to 1,500 volts (D.C. and R.M.S.) and 4,000 pk. to pk. Res. 0.1 Ω 1,000 MΩ. Centre zero dB scale, D.C. input. Resistance 11 MΩ, 4½in. meter. Complete with test prods, leads and standardising battery.

£19.18.6 assembled **£13.18.6** Kit

RF PROBE. 309-CU extends range to 100 Mc/s. Indication to 300 Mc/s

**£1.13.6** Kit

HV PROBE, HV-336 measures up to 30,000V DC

**£2.19.6** Kit

RF SIGNAL GENERATOR. Model RF-1U. Up to 100 Mc/s fundamental, 200 Mc/s harmonics. Up to 100 mV output on all bands

£19.18.0 **£13.8.0** Kit

MULTIMETER. Model MM-1U. Ranges: 0-1.5 v. to 1,500 v. A.C. and D.C.; 150µA to 15A D.C.; 0.02Ω to 20M.Ω 4½in. 50µA meter.

£18.11.6 assembled **£12.18.0** Kit

A wide range of other test instruments available including: R/C Bridge C-3U £10.10.0. AF V/Voltmeter AV-3U, £16.10.0. Wattmeter AW-1U, £17.5.0. Capacitance meter CM-1U, £15.15.0. Power supplies. Decade boxes etc. Many other instruments available under American Mail order scheme. Why not send for full details.

## SSU-I SPEAKER SYSTEM



SSU-I

A practical solution to the problem of a moderately-priced speaker suitable for Stereo/Mono amplifiers, where the equipment has to be compact. Two speakers, balance control, ducted port reflex cabinet.

Horizontal or vertical (without legs)

Incl. P.T. **£10.17.6** Kit

Horizontal or vertical (with matching legs)

Incl. P.T. **£11.12.0** Kit

## TRANSISTOR RECEIVERS

### "OXFORD" LUXURY TRANSISTOR DUAL WAVEBAND RECEIVER.

The ideal domestic, car or personal portable receiver. 10 Semi-conductors. Solid leather case. Send for full details.

Incl. P.T.

**£14.18.0** Kit



UXR-1

6 TRANSISTOR PORTABLE. Model UXR-1. Prealigned I.F. transformers. Printed circuit, 7in. x 4in. high flux speaker. Real hide case. Very easy to build.

Incl. P.T.

**£12.11.0** Kit

7 TRANSISTOR PORTABLE. Model RSW-1. Two short, trawler and medium wave bands.

Incl. P.T.

**£19.17.6** Kit

"MOHICAN" GENERAL COVERAGE RECEIVER. Model GC-1U. Excellent portable or general purpose receiver for amateur or short wave listening. See full spec. leaflet.

Assembled £48.17.6

**£39.17.6** Kit



GC-1U

## "AMATEUR" EQUIPMENT

### AMATEUR BANDS RECEIVER

Model RA-1. Covers all amateur bands from 160-10 m. Half lattice crystal filter, 8 valves, "S" meter, tuned R.F. amplifier stage.

**£39.6.6** Kit


Assembled £52.10.0



RA-1

AMATEUR TRANSMITTER. Model DX-100U. Covers all amateur bands 160-10M. 150 w. D.C. input, self contained with power supply. Modulator, VFO

Assembled £104.15.0 **£79.10.0** Kit

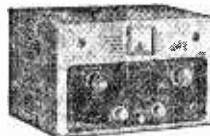

DX-40U

### AMATEUR TRANSMITTER

Model DX-40U. Covers 80-10 m. Power input 75 w. C.W., 60 w. peak C.C. phone. Output 40 w. to aerial. Prov. for V.F.O.

**£33.19.0** Kit

Assembled £45.8.0

Other kits in the amateur range include: SSB Adapter SB-10U, £39.5.0. Variable Freq. Oscillator VF-1U, £12.10.0. Balun Coil Unit B-1U, £4.15.6. Grid-Dip Meter GD-1U, £10.19.6. Q Multiplier QPM-1, £8.10.0. Wide range of models under American Mail Order Scheme.

SEND FOR FREE BRITISH CATALOGUE  
OVER 50 MODELS TO CHOOSE FROM

# DAYSTROM LTD.

Dept. PW-1.

GLOUCESTER,  
ENGLAND.

A member of the Daystrom Group, manufacturers of the WORLD'S LARGEST-SELLING ELECTRONIC KITS

THE WORLDS BEST  
KIT-SETS OF THE




HIGHEST QUALITY  
AT LOWER COST

Millions of Heathkit models are in use throughout the world because :—

- ★ They are so easy to build even for an absolute beginner.
- ★ The manual of instructions is foolproof because all manuals are written by the world's experts in kit-set design.
- ★ You get professional appearance and performance with every model.

## HI-FI AMPLIFIERS

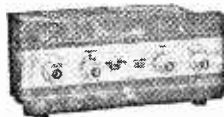

S-33

**6W STEREO AMPLIFIER.** Model S-33. 3 w/chl. Inputs for radio, tape and gram. Stereo/Mono ganged controls. Sensitivity 200 mV.

£18.18.0 Assembled **£13.7.6 Kit.**

**6W DE-LUXE STEREO AMPLIFIER.** Model S-33H. An inexpensive stereo/mono amplifier with high sensitivity. Suitable for use with Decca Deraam cartridge.

£21.7.6 assembled **£15.17.6 Kit.**

**TAPE RECORD/REPLAY AMPLIFIER KITS.** Will operate with most tape decks. Send for details.

**TA-1M (Mono), £19.18.0. TA-1S (Stereo), £25.10.0**

**18W STEREO AMPLIFIER.** Model S-99. Ganged controls. Stereo/Mono gram, radio and tape recorder inputs. P/B selection.

£37.19.0 Assembled. **£27.19.6 Kit.**



S-99

**5W HI-FI MONO AMPLIFIER.** Model MA-5. A low priced amplifier based on the S-33. Printed circuit construction makes it easy to build. £14.19.6 assembled.

**£10.19.6 Kit.**

**HI-FI SINGLE CHANNEL AMPLIFIER.** Model MA-12. Ideal for use with Models USC-1 and UMC-1, 0.1 THD at 10 W. Wide freq. range.

**£11.18.0 Kit.**

£15.18.0 Assembled.

## NEW MODELS



**PUBLIC ADDRESS AMPLIFIER,** PA-1. For vocal and instrumental groups, guitars, etc. 50 W rms, 100 W pk output. 4 inputs, 2 loudspeakers. Send for full details.


£74.0.0 Assembled **£54.15.0 Kit.**

Set of 4 Legs 17/6 extra.

**COMMUNICATIONS TYPE RECEIVER RG-1.** A high performance low cost receiver for the discriminating listener. Freq. cov. 600 kc/s-1.5 Mc/s and 1.7 Mc/s to 32 Mc/s. Send for details.

£53.0.0 Assembled.

**£39.16.0 Kit.**

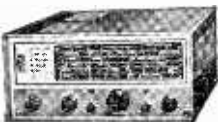

**SELF SUPPORTING AERIAL TOWER KIT, Model HT-1.** Ideal for Amateur Radio or TV reception, etc. Strong steel construction, height 32 ft. tapered square section 3ft. x 3ft. at base.

Kit **£29.15.0** Oxide Painted. **£35.15.0** Galvanised.

Accessories available. Send for details.

### MONEY BACK GUARANTEE

Daystrom Ltd. unconditionally guarantee that each Heathkit product assembled in accordance with our easy to understand instruction manual must meet our published specifications for performance or the purchase price will be cheerfully refunded.

## 'COTSWOLD' SPEAKER SYSTEMS

### STANDARD MODEL

Acoustically designed enclosure in the white 26 x 23 x 15½ in. 12 in. bass speaker, elliptical middle speaker, 2 in. pressure unit. Covers 30-20,000 c/s.

Complete kit with all controls



### MFS SYSTEM

A minimum floor space model for the smaller room. 36 in. high x 16½ in. x 14 in. deep. Almost identical performance to standard model.

Price either model **£23.4.0 Kit.**

## HI-FI TUNERS

**Model FM-4U.** Tuning range 88-108 Mc/s. Tuning unit (FMT-4U) with 10.7 Mc/s I.F. (£215.0 inc. P.T.). I.F. Amp (FMA-4U) complete with cabinet and valves

Total **£15.18.0 Kit.**

**FM-4U**

**AM/FM TUNER.** Covers FM 88-108 Mc/s. AM, 16-50, 200-550, 900-2,000 m. Tuning heart (£413.6 inc. P.T.). and I.F. Amp.

Total **£26.10.0 Kit.**



## EQUIPMENT CABINETS

A large range, in kit form or assembled and finished, available to meet most needs. Illustrated details on request.

Prices from **£6.19.6**

to **£29.8.0**



250

## AMERICAN HEATHKIT MODELS

Full details of Direct Mail Order Scheme and fully illustrated catalogue of range can be obtained from us for only 1/- post paid. (FREE to Service Depts.)

Please send me **FREE BRITISH CATALOGUE (Yes/No)**

Full details of model(s) \_\_\_\_\_

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

PW1

# DAYSTROM LTD.

Dept. P.W.1, GLOUCESTER, ENGLAND

A member of the Daystrom Group, manufacturers of the  
WORLD'S LARGEST-SELLING ELECTRONIC KITS

# SURBITON PARK RADIO LTD.

## FOR POST HASTE—POST FREE SERVICE

### MARTIN RECORDAKITS

#### HALF TRACK

B.S.R. TD2 Monardeck, Latest model, 5in. spool	£9.90
Deposit £1.00 and 9 monthly	£1.10
Tape Amplifier for B.S.R. Deck, printed circuit ready wired with EC83, EC182, EM85 and EZ40. Complete with all plugs, sockets, panels, knobs etc. The whole amplifier mounts on to the deck making a self-contained unit.	£8.80
Deposit £1.00 and 8 monthly	£1.10
Case with 7 x 4in. speaker, two-tone grey	£4.40
Complete Kit as above, with Tape and Microphone	£22.00
Deposit £2.40 and 12 monthly	£1.16.8
Collaro Studio Deck, Very latest model, 3 speeds 7in. spools	£10.19.8
Deposit £1.20 and 8 monthly	£1.7.3
Tape Amplifier for Studio Deck, with ready wired printed circuit, control and input panels, mains and output transformers, knobs, plugs, screws etc. EF80, EC83, EM84, EZ81 and 2 EL84, 3 watts output. Magic eye, Radio and Mic. Inputs, Ex 1/8 socket. Tone and Monitor controls. Can be used as amplifier	£11.11.0
Deposit £1.40 and 12 monthly	19/-
Case for above, with 8 x 6in. speaker, two-tone grey	£5.50
Complete Kit, with Tape and Microphone	£29.0.0
Deposit £2.10 and 12 monthly	£2.8.2
Building instructions available at 2/6 each kit (refunded if kit bought)	

#### JASON F.M. TUNERS

FMT1, complete with 4 EF81 valves	£8.8.8
Deposit £1.00 and 8 monthly	£1.0.9
FMT2, less power, complete with 4 EF80 valves	£10.12.8
Deposit £1.3.6 and 12 monthly	17/6
FMT2, with power, complete with 4 EF80 and 1 EZ80	£12.18.8
Deposit £1.8.6 and 12 monthly	£1.1.1
FMT3, Fringe complete with valves, less power	£12.10.0
Deposit £1.5.0 and 12 monthly	£1.0.8
FMT3, with power, complete with all valves	£14.15.0
Deposit £1.9.6 and 12 monthly	£1.4.5
JTV3, switched F.M. and TV sound, self-powered, all valves	£17.0.0
Deposit £1.14.0 and 12 monthly	£1.5.2
Mercury II, as JTV3 but less power, all valves	£11.12.8
Deposit £1.5.6 and 8 monthly	19/-
Instruction book is included in all kits, but otherwise 2/6 and 3/6.	
JTV3, ready built (as Mercury II)	£22.5.0
Deposit £2.4.6 and 12 monthly	£1.10.11
Monitor, ready built (as Mercury II)	£16.10.0
Deposit £1.13.0 and 12 monthly	£1.7.4

#### AMPLIFIERS (MONO)

Linear L45, 3 watt, 3 valve	£5.19.6
Linear Dantonio, 12 watt, suitable Mic. or Guitar	£12.12.0
Deposit £1.7.0 and 12 monthly	£1.0.8
Linear Concord, 30 watt, ideal guitar amp., with case	£18.9.0
Deposit £1.8.0 and 12 monthly	£1.9.10
Dulci GA6, integrated amp. and P.A., 5 watt, EC182 valve	£18.2.6
Deposit £1.8.6 and 12 monthly	£1.1.6
Dulci DPA16, 15 watt with 2 valve pre-amp	£25.4.0
Deposit £2.10.6 and 12 monthly	£2.1.11
Tripletone Hi-Fi Master with pre-amp, Guitar or Mic.	£15.18.9
Deposit £1.15.3 and 12 monthly	£1.6.1
Leak TL12, 10 watt Main amp. only	£18.18.0
Deposit £2.0.6 and 12 monthly	£1.11.1
Leak Variotone III pre-amplifier	£15.15.0
Deposit £1.11.6 and 12 monthly	£1.6.1
Quad, 15 watt Main amplifier only	£22.10.0
Deposit £2.5.0 and 12 monthly	£1.17.4
Quad pre-amplifier, Mono	£19.10.0
Deposit £1.19.0 and 12 monthly	£1.12.4

#### AMPLIFIERS (STEREO)

Dulci AC802, integrated	£12.12.0
Deposit £1.7.0 and 12 monthly	£1.0.8
Dulci GA606, integrated	£18.18.0
Deposit £2.0.6 and 12 monthly	£1.11.1
Rogers Cadet Mk. 2 with pre-amplifier, 4 EF186 valves	£26.15.6
Deposit £2.18.6 and 12 monthly	£2.4.5
Leak Stereo 30, Main amplifier	£30.9.0
Deposit £2.4.6 and 12 monthly	£2.10.3
Leak Variotone III, stereo pre-amplifier	£26.0.0
Deposit £2.10.0 and 12 monthly	£2.1.6
Quad 22 Stereo Control Unit	£25.0.0
Deposit £2.10.0 and 12 monthly	£2.1.6
For Quad Main Amplifiers see Mono section above.	

#### QUARTER TRACK

B.S.R. TD2, Marriot heads, L-series	£11.11.0
Deposit £1.4.0 and 12 monthly	19/-
Tape Amplifier, as over, but quarter-track	£9.9.0
Deposit £1.00 and 9 monthly	£1.1.0
Case, two-tone grey, with speaker	£4.4.0
Complete Kit, with tape and microphone	£25.0.0
Deposit £2.10.0 and 12 monthly	£2.1.6
Collaro Studio Deck, Marriot X series heads	£17.17.0
Deposit £1.7.0 and 12 monthly	£1.9.5
Tape Amplifier, as over but quarter track	£12.12.0
Deposit £1.17.0 and 12 monthly	£1.0.8
Case, with speaker, two-tone grey	£5.5.0
Complete Kit, with tape and microphone	£35.0.0
Deposit £3.10.0 and 12 monthly	£2.18.2
Tape Pre-amplifier for Collaro Studio Deck, with power supplies, EC83, EC182, EZ80 and EM85. Radio and Mic. sockets, gives an equalised output of 400mV.	
Half Track	£8.8.0
Deposit £1.00 and 8 monthly	£1.1.0
Quarter Track	£9.9.0
Deposit £1.00 and 9 monthly	£1.1.0

#### TAPE HEADS

M.S.S. Quarter track, Record/Replay and Erase Set	£3.3.0
Bradmatic Half track Record/Replay head only	£1.12.6
Bradmatic Half track Record/Replay and Erase as Studio Set	£1.19.6
Collaro pressure pad for third head position	4/-
Brenell Mk. 5 Series 2 speed deck half track	£32.11.0
Deposit £3.5.0 and 12 monthly	£2.14.0
Brenell Mk. 5 Tape Amplifier with power pack	£26.0.0
Deposit £2.12.0 and 12 monthly	£2.3.2

#### NEW ARMSTRONG TUNER-AMPLIFIERS

Armstrong (Mono) T4C V.H.F. Tuner, self-powered	£17.19.0
Deposit £1.19.6 and 12 monthly	£1.9.5
Armstrong (Mono) AF208 A.M./F.M. Radio chassis, base and treble controls, I.F. inputs, etc.	£21.4.0
Deposit £2.6.0 and 12 monthly	£1.14.10
Armstrong (Mono) ST3 Mk. 2 A.M./F.M. Self powered tuner	£25.12.0
Deposit £2.13.0 and 12 monthly	£2.2.4
Armstrong (Mono) 227M A.M./F.M. Radio chassis, 10 watts	£33.8.10
Deposit £3.10.6 and 12 monthly	£2.16.1
Armstrong (Stereo) Stereo 55 A.M./F.M. Radio chassis, with Stereo gram	£29.18.0
Deposit £3.2.6 and 12 monthly	£2.9.5
Armstrong (Stereo) 227 A.M./F.M. Radio chassis, Stereo gram, 10 watts each channel	£48.15.0
Deposit £4.17.6 and 12 monthly	£4.1.1
Armstrong (Stereo) 228 A.M./F.M. Radio chassis, Stereo gram, 10 watts each channel, Filters etc.	£56.0.0
Deposit £5.12.0 and 12 monthly	£4.12.2
Rogers Switched F.M. Tuner, self-powered	£14.12.8
Deposit £1.11.6 and 12 monthly	£1.4.0
Tripletone F.M. Tuner, less power	£13.19.6
Deposit £1.8.0 and 12 monthly	£1.3.2
Tripletone F.M. Tuner, self-powered	£15.14.6
Deposit £1.11.6 and 12 monthly	£1.6.1

#### GRAMOPHONE UNITS

Garrard SRP10 with 10in. cartridge, Mono, single player	£5.9.11
B.S.R. UA14 with 7in.8 cartridge, Mono, 4 speed changer	£6.19.6
Deposit £1.00 and 6 monthly	£1.3.3
Garrard Autolism, Mono GCS cartridge, 4 speed changer	£7.17.0
Deposit £1.00 and 7 monthly	£1.2.6
Garrard AT8 Autolism de Luxe, GCS Mono cartridge	£11.9.0
Deposit £1.8.6 and 9 monthly	£1.4.9
Philips AG1018, Stereo cartridge, with change 7in. records	£12.12.0
Deposit £1.7.0 and 12 monthly	£1.0.6
Decca Deram Arm and Plug-in Shell	£5.5.0
Decca Deram Transcription Cartridge	£4.14.6
Decca Deram Auto Cartridge	£3.13.8
Goldring GL58 with arm, less cartridge	£15.19.8
Deposit £1.12.0 and 12 monthly	£1.6.8
Goldring '98' Transcription, no arm	£17.14.0
Deposit £1.19.0 and 12 monthly	£1.9.0
Goldring GL55X, as GL58 but less pick-up arm	£13.1.7
Deposit £1.9.0 and 12 monthly	£1.1.6
Garrard 4H/F with 10in. GCS cartridge	£17.0.0
Deposit £1.14.0 and 12 monthly	£1.8.2
Garrard Lab Type "A" Transcription auto-changer, Mono GCS	£19.14.9
Deposit £1.19.8 and 12 monthly	£1.12.9
Garrard 30	£20.12.2
Deposit £2.3.2 and 12 monthly	£1.14.0
Garrard 301 Strobe	£22.0.0
Deposit £2.4.0 and 12 monthly	£1.16.8

#### LOUDSPEAKERS

Goodmans Axiotele 3	£5.5.7
Goodmans Axiom 10	£6.5.11
Goodmans 5K/50/XL	£7.0.0
Wharfedale Super 8/RS/DD	£6.14.2
W.B. HF1012 10in.	£4.7.8
R.T.C. 12in. Unit, 15 watt	£5.5.0
R.T.C. Hi-Fi Master	£8.8.0
Goodmans XO 5000 cross-over	£1.19.0
Goodmans Axiom 201 12in. Unit	£10.7.0
Deposit £1.1.0 and 8 monthly	£1.5.9
Goodmans Axiom 301 12in. Unit	£14.10.0
Deposit £1.9.0 and 12 monthly	£1.4.0
Wharfedale W12/EO 12in. 15 watt Guitar speaker	£10.10.0
Deposit £1.1.0 and 12 monthly	17/6
Wharfedale Super 10/RS/DD 10in. high quality unit	£10.18.0
Deposit £1.3.8 and 12 monthly	17/11
Wharfedale RS12/DD 12in. 15 watt Hi-Fi speaker	£11.10.0
Deposit £1.7.6 and 9 monthly	£1.4.9

48 SURBITON ROAD, KINGSTON UPON THAMES, SURREY

Established over 30 years

Telephone KIN 5549

We pay all postage and insurance. All orders despatched same day. Money refund guarantee. Hours: 9 a.m.-6 p.m. (1 p.m. Wednesday). We do not close for lunch. Open all day Saturday.



TOP QUALITY—LOW COST




AMATEUR RADIO EQUIPMENT
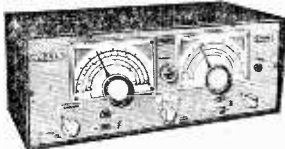
## BUILD YOUR SHORT WAVE LISTENING STATION WITH CODAR-KITS. CR 66 COMMUNICATIONS RECEIVER

★  
THE FINEST  
SUPERHET  
KIT EVER  
OFFERED

OUTSTANDING SUCCESS AT THE  
RADIO COMMUNICATIONS EXHIBITION



Frequency Range  
540 Kc/s to 30 Mc/s  
in four Band-  
switched ranges.

Electrical Bandsread. Coil Unit wired ready and I.F. Transformers factory aligned, no test equipment required. Temperature compensated trimmers. Regenerative I.F. stage for maximum gain and B.F.O. Panel aerial trimmer, separate speaker switch, 3 watts output for external 2-3 ohm speaker. Separate cathode follower for tape recording etc. Valve line-up—ECH81, EBF89, ECC81, EL84, EZ80, EM84 (Optional extra). For 200-250 volt A.C. Cabinet size 16 x 6½ x 8½ in.

Complete Kit with 17-page Instruction Manual Carriage 6/- **£18.5.0**

Tuning indicator parts with EM84, 17/6.

H.P. TERMS AVAILABLE ON REQUEST.

## ★ P.R. 30 R.F. PRESELECTOR ★


Frequency range 1.5-30 Mc/s. Substantially improves the performance of any superhet receiver.

G4HZ writes . . . I am delighted with it, it improves my Eddystone 640 in all respects. The difference with the Pre-selector is fantastic, a weak signal on 15 metres about S2 changed to S8. On the L.F. Bands, unwanted noise and mush is cut out.

G3RIA writes . . . The results in conjunction with my Eddystone 888 are amazing. Signals are twice as strong with much higher signal/noise ratio. A first-class product well worth the money. The P.R.30 uses EF183 Frame Grid R.F. Amplifier and provides up to 20 dB gain. Features include vernier tuning, gain control, selector switch for either dipole or end fed antenna. External power supplies (obtainable from Rx). Smart styling in grey and black. Complete, ready for use, with all plugs, cables. Now available in two models.

P.R.30 for external power supplies 180-250 volts H.T., 6.3 volts 3 amp. L.T. (obtainable from receiver). **£4.17.6**

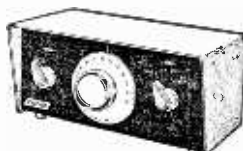
P.R.30X self powered with internal power supply for 200-250 volt A.C. Will provide 200 volts up to 25 M/a. and 6.3 volts 1 amp. for other accessories. **£7.2.0**



Carr. 3/6.  
Carr. 3/6.
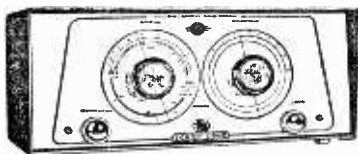
## THE NEW CR 45 MAINS T.R.F. SHORT WAVE RECEIVER

World-wide short wave reception, North-South America, India, Russia, Far East, Australia, amateurs, shipping, etc.



- ★ Separate electrical bandsread.
- ★ Three slow motion vernier drives.
- ★ Low loss polystyrene plug-in coils, factory aligned.
- ★ Dials calibrated in frequencies and degrees.
- ★ Power output 3 watts for 2/3 ohm speaker.
- ★ Valve line-up: ECC81/EL84/EZ80.
- ★ Front Panel Silver and Black, control knobs Grey.
- ★ Provision for panel phone jack.

Superb modern styling and Top quality components throughout. Complete CR 45 CODAR-KIT, with valves and 3 Coils, 10-28, 25-75, 60-176 metres. Instruction Manual 11 pages, less Cabinet

CR 45 Cabinet Silver Grey 12 x 5½ x 7 in. with sliding door for easy coil changing and detachable louvred rear panel **£7.5.0** Carr. 4/6.

Instruction Manual only 4/- post free. Extra coils 4/9 each.

## ★ THE MINI-CLIPPER ★

- ★ Miniature 1 valve short wave receiver.
- ★ Low loss polystyrene plug-in coils, factory aligned.
- ★ Air spaced ball bearing condensers.
- ★ Provision to add two-transistor amplifier.
- ★ Battery lasts months.



Can be built in one evening, ready to switch on, to bring the fascination of Short Wave listening at very low cost. Complete MINI-CLIPPER CODAR-KIT, valve, and one coil 25-75 metres, Instruction Manual 4 pages, 37/6, carr. 2/6. Extra Coils 4/9 each. Electrical Bandsread available. Instruction Manual only 2/-, post free.

**36/6**

## ★ THE SUPER CLIPPER ★

- ★ Peak Performance short wave battery receiver.
- ★ Large precision dial, dual slow motion drives.
- ★ Bandsread on all Bands.
- ★ High gain valve/transistor hybrid circuit.
- ★ 2 Mullard transistor amplifiers pre-assembled and tested.
- ★ Low loss polystyrene plug-in coils, factory aligned.
- ★ Batteries last months.

**88/6**



Easy to assemble, this famous Short Wave Receiver brings a new world of listening pleasure to your finger tips. Complete SUPER-CLIPPER CODAR-KIT, valve, transistors, 2 Coils 20-60, 55-180 metres. Instruction Manual 7 pages, 88/6, carr. 2/6. Front Panel Silver Grey, 10 x 7½ in. 6/9 extra if required. Extra Coils 4/9 each.

CODAR-KITS are famous for PEAK PERFORMANCE, EASY TO FOLLOW INSTRUCTIONS, CLEAR PICTORIAL DIAGRAMS. Some of the Top Quality names who supply material for CODAR-KITS . . . MULLARD, BRIMAR, JACKSON, DENCO, ELECTRONIQUES, THORN, A.E.I. etc. etc. . . only the best is good enough for the high CODAR standards which make complete success certain. 6d. in stamps brings illustrated leaflets.

# CODAR RADIO COMPANY

BANK HOUSE, SOUTHWICK SQUARE, SOUTHWICK, SUSSEX

G3IRE

Canadian Distributors: CODAR RADIO OF CANADA, TWEED, ONT.

G3HGG

# BENTLEY ACOUSTIC CORPORATION LTD.

Suppliers to H.M. Government. 38 CHALCOT ROAD, LONDON, N.W.1 Telephone: PRIMROSE 9090  
NEAREST UNDERGROUND: CHALK FARM. ALL GOODS LISTED BELOW ACTUALLY IN STOCK

ALL GOODS ARE NEW, BEST QUALITY BRANDS ONLY, AND SUBJECT TO MAKERS' FULL GUARANTEE. PLEASE NOTE THAT WE DO NOT SELL ITEMS FROM DISMANTLED EQUIPMENT NOR MANUFACTURERS' SECONDS & REJECTS, WHICH ARE OFTEN DESCRIBED AS "NEW AND TESTED," BUT HAVE A SHORT AND UNRELIABLE LIFE

0A2	4/8	68B7	25/-	6V6GT	5/8	30P4	13/8	ACSPEN	5/-	EB34	1/-	EL81	8/8	LN152	6/-	R18	10/8	U78	4/-	AF126	10/-
0B2	6/-	68W6	7/6	6X4	4/-	30P5	13/8	ACSPEN	5/-	EB34	4/8	EL83	7/8	LN309	8/3	R19	7/-	U84	4/7	AF127	9/6
0Z4GT	4/8	68W7	5/-	6X6	4/-	25A6G	7/6	(5)	17/6	EB34	2/3	EL84	5/-	LN319	9/-	K52	9/-	U101	10/8	BY123	11/8
1A3	2/6	68X6	4/-	6Y6G	6/-	25L6GT	6/-	AC/CPEN	5/-	EB43	20/6	EL85	7/-	LP2	9/-	RQ1/240A	5/-	U107	17/6	GD3	5/6
1A5	5/-	6C4	2/3	7B5	12/6	25V4GT1812	(7)	17/-	AC/CPEN	5/-	EB43	8/6	EL86	7/8	ME41	15/2	54/-	U191	10/8	GD6	5/6
1A7GT	8/-	6C6	4/-	7B7	7/6	25V6	5/-	AC/8G	22/8	EB41	6/8	EL91	2/8	ME91	12/6	RK34	7/6	U251	9/6	GD14	10/-
1C1	4/6	6C5	3/-	7C5	10/-	25Y5G	8/-	AC/8G/VM	EB41	6/-	EL95	8/3	MH4	3/6	S139	22/8	U251	9/6	GET102	8/6	
1C2	6/8	6C8	3/-	7C6	7/-	25Z4G	8/-	AC/8G/VM	EB41	6/-	EL96	27/-	MH4	8/6	S149	19/6	U251	13/-	GET103	3/6	
1C3	6/8	6C9	11/-	7D3	21/-	25Z5	7/8	ACTH1	15/-	EB41	6/8	EL97	20/8	MH4	12/8	S149	19/6	U251	13/-	GET104	3/6
1C5	6/8	6C10	7/9	7D5	15/-	25Z6GT	7/8	ACT/PT	19/-	EB43	7/8	EL98	18/8	MH4	12/8	S149	19/6	U251	13/-	GET105	3/6
1C6	10/6	6C12	6/-	7D8	15/-	27A4	22/8	AC/VP112	EB43	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET106	3/6	
1D5	6/6	6C17	12/8	7D8	15/-	28D7	7/-	AC/VP2	20/5	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET107	3/6
1D6	9/6	6C18G	12/8	7H7	5/-	30C1	5/8	ATP4	8/6	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET108	3/6
1P1	5/8	6C18G	5/-	7K7	12/8	30C15	9/8	AZ1	8/6	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET109	3/6
1P2	6/8	6C18G	24/-	7K7	12/8	30C15	9/8	AZ1	8/6	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET110	3/6
1P3	2/3	6D1	1/6	7Y4	5/-	30F11	9/8	AZ1	8/6	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET111	3/6
1P7	15/-	6D3	9/6	8D2	2/6	30F112	11/-	B36	5/-	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET112	3/6
1P9	3/8	6D6	3/-	8D3	3/-	30L1	5/8	BL63	10/6	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET113	3/6
1G6	5/-	6D8	15/-	9B8W	6/8	30L15	10/8	C1	12/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET114	3/6
1H5GT	6/8	6E5	9/6	9D2	3/-	30P4	12/3	C1C	12/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET115	3/6
1L4	2/6	6F1	9/6	9D7	12/3	30P12	7/8	CH35	13/6	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET116	3/6
1L4E	16/10	6F5	5/3	10C1	9/6	30P16	6/-	CK506	6/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET117	3/6
1L5	4/8	6F6G	4/-	10C2	13/-	30P19	12/3	CL4	23/10	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET118	3/6
1L5E	4/8	6F6GT	7/6	10D1	7/-	30P19	12/3	CL4	23/10	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET119	3/6
1L5GT	4/8	6F6GT	7/6	10D1	7/-	30P19	12/3	CL4	23/10	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET120	3/6
1P1	5/8	6F11	12/8	10P1	10/-	30P13	9/8	CV3	2/6	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET121	3/6
1P10	4/8	6F12	3/-	10P9	10/-	35A5	20/9	CV3	10/6	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET122	3/6
1P11	5/8	6F13	5/-	10F18	10/-	35L6GT	7/8	CV3	10/6	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET123	3/6
1L5	4/8	6F14	23/8	10L13	6/8	35W4	5/8	CV3	10/6	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET124	3/6
1L4	5/-	6F15	6/8	10L11	9/-	35Z3	18/4	CV3	10/6	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET125	3/6
1L5	3/8	6F16	6/8	10P13	8/6	35Z4GT	18/4	C1	12/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET126	3/6
1L7	4/11	6F17	12/8	10P14	11/8	35Z5GT	6/-	D15	13/6	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET127	3/6
1L7	2/8	6F18	13/8	11D3	7/8	40H4U	6/8	D42	10/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET128	3/6
1L4	6/-	6F19	4/8	11D5	17/8	41H18	15/-	D63	5/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET129	3/6
1L5	10/8	6F20	4/8	11E1	2/8	42H1	15/-	D63	5/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET130	3/6
2A7	10/8	6F24	9/6	12C3	7/8	43	10/8	DAC32	3/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET131	3/6
2C28	3/-	6F26	5/-	12A8	8/8	50A5	21/10	DAF91	3/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET132	3/6
2D130	7/-	6F32	4/-	12A8	18/8	50B5	7/8	DAF96	5/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET133	3/6
2D21	6/8	6F33	3/8	12A8	8/8	50C5	6/8	DC090	6/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET134	3/6
2P	2/8	6F34	3/8	12A8	8/8	50D6GT	6/8	DC090	6/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET135	3/6
2X2	3/-	6H6	1/8	12A8	8/8	50E1	6/8	DD41	12/3	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET136	3/6
3A4	4/-	6J5G	3/-	12A7	7/8	52K1	14/8	DDT4	8/6	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET137	3/6
3A5	6/8	6J5GT	4/3	12A8	9/8	52K1	14/8	DDT26	7/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET138	3/6
3B7	3/-	6J6	3/-	12A7	6/8	52K1	14/8	DDT26	7/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET139	3/6
3D6	4/-	6J7	4/8	12A7	6/8	52K1	14/8	DDT26	7/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET140	3/6
3Q4	5/8	6J7GT	7/-	12A6	6/8	52K1	14/8	DDT26	7/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET141	3/6
3Q5	7/3	6J8	12/8	12A7	6/8	52K1	14/8	DDT26	7/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET142	3/6
3B4	4/8	6K6GT	6/8	12A6	6/8	52K1	14/8	DDT26	7/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET143	3/6
3V4	6/8	6K7	1/8	12A7	6/8	52K1	14/8	DDT26	7/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET144	3/6
4D1	4/-	6K7GT	4/8	12A5	6/8	52K1	14/8	DDT26	7/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET145	3/6
4H4GY	9/8	6K8	3/8	12B6	5/-	53V	8/8	DDH3	6/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET146	3/6
5T4	8/-	6K8GT	7/8	12B7	7/8	55A1	22/8	DDH7	3/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET147	3/6
5U4G	4/8	6K25	12/8	12P1	17/8	55A2	8/8	DDH7	3/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET148	3/6
5V4G	7/8	6L6	9/8	13H1GT	1/8	90A3	8/8	DDH1	23/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET149	3/6
5Z3GT	4/8	6L6G	4/8	13H1GT	1/8	90A3	8/8	DDH1071811	11	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET150	3/6
5Y4	6/8	6L6M	9/-	12J7GT	7/8	90C3	42/-	DK32	3/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET151	3/6
5Z3	6/-	6L7GT	4/8	12K5	10/8	90CV	42/-	DK40	18/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET152	3/6
5Z4G	7/-	6L17	12/8	12K7GT	3/8	90C1	16/-	DK40	18/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET153	3/6
5P0L2	8/8	6L18	7/8	12K8GT	3/8	130B2	16/8	DK91	4/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET154	3/6
6A7	9/-	6L19	9/8	12K7GT	3/8	130C2	7/8	DK92	6/8	EB41	6/8	EL99	18/8	MH4	12/8	S149	19/6	U251	13/-	GET155	3/6
6A8G	7/-	6L19	9/8	12K7GT	3/8	130C2	7/8	DK92	6/8	EB41	6/8	EL9									

# STERN-CLYNE

Incorporating STERN RADIO LTD., PREMIER RADIO, CLYNE RADIO LTD.

Three well-known names with a reputation for quality and service.



Combined resources, technical knowledge and over 50 years' experience gives you an organisation offering a fully comprehensive specialist service in the rapidly expanding world of electronics.



## MULLARD 3-VALVE PRE-AMPLIFIER TONE CONTROL UNIT

Designed mainly for Mullard Range of Amplifiers, also suitable for any Amplifiers requiring input up to 250mV. Incorporates 5 input channels, including for Tape and Magnetic Pickups. Separate Bass and Treble controls. High pass filter 20 to 100 c/s. low pass filter 5-9 Kc/s. Totally enclosed in case size 11" x 4" x 4". **£10.00** (Carr. & Ins. 5/-) **ASSEMBLED & TESTED £13.13.0** (Carr. & Ins. 5/-)

Instruction book and detailed price list (free with kit) available separately at 3/6 Post Free.

## MULLARD "5-10" MAIN AMPLIFIER

For use with MULLARD 2 or 3 valve pre-amplifiers with which an undistorted power output of up to 10 watts is obtained. SPECIFIED COMPONENTS and MULLARD VALVES including PARTRIDGE MAINS TRANSFORMER and choice of PARMEKO or PARTRIDGE Output Transformer **COMPLETE KIT (Parmeko Output Trans.) £10.00** **ASSEMBLED AND TESTED £13.10.0** (Carr. & Ins. 6/6).

ABOVE incorporating PARTRIDGE OUTPUT TRANS. £1.6.0 extra. Instruction book and detailed price list (free with kit) available separately at 2/- Post Free.

## THE MULLARD 5-10RC AMPLIFIER

The popular complete "5-10" incorporating Passive Control Unit providing up to 10 watts high quality reproduction with input of 600 mV. Specified components and new MULLARD VALVES. Includes PARTRIDGE MAINS TRANSFORMERS and choice of PARMEKO or PARTRIDGE Output Transformers. Surplus Power available for Tuner. **COMPLETE KIT £12.0.0** **ASSEMBLED AND TESTED £16.0.0** (Carr. & Ins. 7/6). With PARTRIDGE OUTPUT TRANS. £1.6.0 extra.

Instruction book and detailed price list (free with kit) available separately at 2/- Post Free.

## THE MULLARD 3-3RC

A HIGH QUALITY AMPLIFIER DEVELOPED FROM THE VERY POPULAR 3-WATT MULLARD "3-3" DESIGN. **KIT OF PARTS £8.8.0** **ASSEMBLED AND TESTED £11.10.0**

Complete to the MULLARD specification including PARMEKO OUTPUT TRANSFORMER. 4-tapped inputs for 78 and 50KHz. L.P. records plus a Radio position. Extra power to drive a Radio Tuning Unit is also available. (Carr. & Ins. 6/6). Please state L.S. impedance. Instruction book and detailed price list (free with kit) available separately at 2/6 Post Free.

## THE "MONO-GRAM"

A small Amplifier of genuine high quality performance. Incorporates MULLARD ECL86 Valve, separate BASS and TREBLE controls. PARTRIDGE output Transformer producing up to 3 watts undistorted output. (Carr. & Ins. 3/6).

Kit of **£4.10.0** Assembled and Tested **£6.0.0** Parts **£4.10.0**

Instruction book and detailed price list (free with kit) available separately at 2/6 Post Free.

## The NEW CHASSIS PUNCH SET

Five of the most used Hole Punches made of the finest hardened steel will save hours of tedious hand labour, suitable for Aluminium, Sheet Metal, Plastic, etc. Punch Sizes 1"-4"-11" complete with Tommy Bar, Tapered Reamer, and Zip Fastening Carrying **49/6 P.&P.** Case. **PRICE 3/6**

SEND FOR CURRENT PRICE LIST OF ALL LEADING RECORDING TAPES AND ACCESSORIES

## PRICE REDUCTIONS

- (a) THE KIT OF PARTS to build both the "5-10" Amplifier and the 2-Valve Pre-Amplifier. .... **£15.15.0** (Carr. & Ins. 8/6).
- (a) Assembled and Tested. .... **£21.10.0**
- (b) THE KIT OF PARTS to build both the "5-10" Amplifier and the 3-Valve Pre-Amplifier. .... **£19.10.0** (Carr. & Ins. 10/-).
- (b) Assembled and Tested. .... **£25.10.0**
- With PARTRIDGE OUTPUT TRANSFORMER **£1.6.0 extra.**

## MULLARD 2-VALVE PRE-AMPLIFIER TONE CONTROL UNIT

Employing two EF86 valves and designed to operate with the Mullard AMPLIFIERS but also perfectly suitable for other makes with input up to 250 mV. ★ Equalisation for the latest R.I.A.A. characteristics.

- ★ Inputs for Crystal Pick-ups and variable reluctance magnetic types.
- ★ Input (a) Direct from High Imp. Tape Head. (b) From a Tape Amplifier or Pre-Amplifier.
- ★ Sensitive Microphone Channel. ★ Wide range BASS and TREBLE Controls.

KIT OF **£6.6.0** **ASSEMBLED AND TESTED £9.10.0** (Carr. & Ins. 5/-). Instruction book and detailed price list (free with kit) available separately at 2/- Post Free.

## THE "TUDOR" STEREO AMPLIFIER

PRICE **£15.0.0**

(Pkg. & Carr. 7/6)

A self-contained Shelf-mounting Amplifier designed to provide high quality stereophonic and monophonic reproduction. Each channel provides a rated output of 6 watts and for monophonic operation approx. 12 watts is produced. Separate BASS and TREBLE CONTROLS. The Cabinet is finished in Black Crackle. Size 14 x 8 x 4in. Send for full specification.

## HI-FI STEREO HEADPHONES

For the connoisseur who requires perfection. Each Earphone consists of a 2 1/2" Dynamic Loudspeaker with a full frequency range, fitted with foam rubber Ear Pads for added comfort to keep out noise and to maintain an excellent bass response. The resistance Junction box with change-over switch provides simple transfer from Phones to Speaker. Specifications: Frequency Range - 25-15,000 c/s. Input Impedance - 16 ohms. Power rating - 1 watt. Weight - 13 ozs.

PRICE **5 Gns.** P. & P. 2/6. (Junction box 15/- ex.)

## STEREO STETHOSCOPE HEADSETS

Enjoy personal listening in absolute comfort with the new lightweight Stethoscope Headsets suitable for stereo or monaural. Available in either magnet low impedance or high impedance crystal complete with 6ft. of Cable P. & P. and Stereo Jack Plug. PRICE **25/-** 1/6

## MONAURAL STETHOSCOPE HEADSETS

Suitable for Radio, Tape Recorders, or monitoring tape recordings, magnetic low impedance or Crystal High impedance. Complete with 4ft. of lead and mini-ature Jack Plug. PRICE **10/6** 1/6

**SPECIAL PURCHASE! THE SHURE MODEL M3D** Professional Dynamic Stereo Cartridge with diamond Stylus, the Shure Dynetic Moving Magnet System combines the most faithful and distortion-free reproduction with complete reliability. Specifications: Diamond Stylus 0.7 thou. Load Imp. 470K ohms. Output 5mV. Range 20-15,000 c/s. ± 3 dB. Stylus pressure 3-4 grammes. PRICE **12 Gns.**

SEE FOLLOWING PAGES FOR ADDRESSES AND DETAILS OF OTHER STERN-CLYNE PRODUCTS

# Great Britain's Greatest Electronic Hobbies Organisation

# STERN-CLYNE

## NEW LOW PRICES — NOW YOU CAN AFFORD A CAR RADIO



### THE 'HIGHWAYMAN'


OUR QUALITY CAR RADIO  
TO BUILD YOURSELF AT  
A NEW LOW PRICE

Look at these features:

★ Attractive styling. ★ Push-pull output. ★ Three latest Mullard transistors plus valves types 6BF83 and 6CH83. ★ No fuzz, high output and sensitivity. ★ Printed circuit (latest type). 7 x 4in. high flux p.m. speaker and baffle. ★ Medium and Long Waves. ★ Push button for frequency control. ★ Extremely low battery consumption (less than 1 amp). ★ Easy to fit any make car. (Positive earth only). ★ 12-volt operation. ★ Compact size, measures only 7 x 7 x 2in. deep. ★ Easy assembly, supplied with dial and drive already mounted.

Special inclusive price of ONLY **£7.19.6** Plus 5/- P. & P.

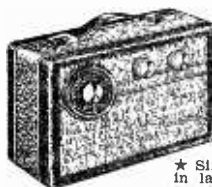All parts available separately. Individually priced parts list and comprehensive instruction booklet 2/6 post free. (Deducted from cost if complete parcel purchased later.)



### THE 'AIR KING'

Our highly successful six-transistor luxury portable with the "SLIM LINE" look. To build yourself, with printed circuit chassis for reliability and simplicity in construction. May be used as Car Radio, with full MEDIUM wave and LONG wave coverage.

Look at these features:

★ 500 milliwatt output to high flux 3 1/2in. high fidelity loudspeaker. ★ Six selected MULLARD TRANSISTORS in latest supersensitive circuit plus germanium diode. ★ Compact size only 8 1/2 x 3 1/2 x 6 1/2in. high. ★ Attractive three-tone cabinet, black, dark grey and silver grey with gilt control knobs and all gilt fittings. ★ Coax. socket for car aerial. ★ Brand new guaranteed components. ★ Push-pull output. ★ Automatic volume control. ★ Long-life battery. ★ Super-sensitive internal Ferrite rod aerial. Special inclusive price for all required components. ONLY **£7.19.6** (Plus P. & P. 4/-). Alignment service available. Full assembly details and individually priced parts list, all of which are available separately, price 1/6 post free.

### TRANSISTORISED SOUND MIXER



Mixing 4 channels from high impedance source, giving professional results. Inputs for high impedance Microphone, Tuner, Gram and/or Tape Recorder. 9 volt battery operation. Compact and beautifully styled, size 6" x 2 1/2" x 2 1/2". Standard Jack socket input.

PRICE **59/6** P.P. Complete with PP3 9v 2/6 battery circuit, diagram and instructions.

### THE HE30 4-BAND COMMUNICATION RECEIVER



One of the finest general coverage bandspread Receivers available at this price. Covering 550Kc/s—1600Kc/s, 4.8Mc/s—14.5Mc/s, 16Mc/s—48Mc/s, 10.5Mc/s—30Mc/s. Illuminated slide rule dial, calibrated every 5Kc/s on 80 and 40 metres. Edgewise 5-meter, 0.100 logging scale. Coverage from 0.55—30Mc/s. 8 valve plus Rectifier superhet circuit. RF Stage with an Aerial Trimmer, 2 IF Stages, B.F.O. control Q-multiplier. Controls: Function Switch, Audio Gain, Selectivity (Q-multiplier) Frequency (BFO), Band Selector, IF Gain, Trimmer, AVC-MVC Switch, Ant Switch, Main Tuning, Bandspread Tuning and Headphone Jack. Selectivity—90dB at 10Kc/s, 0.8Kc/s at 6dB (with Q-multiplier). I.F. 455Kc/s. External PM Speaker reqd., 4 or 8 ohms impedance. Output 1.5 watts. 8 modern Miniature 37G Base Valves and 5Y3 Rectifier. Size 15 x 10 x 7 1/2in. Grey crackle finish. 220/240 volt A.C. mains, 50-60 cycle operation. Full instructions and circuit diagram supplied. Send S.A.E. PRICE **40 Gns.** Carr. & Pkg. 15/- for leaflet.

SEND STAMP FOR COPY OF OUR INTERESTING LITTLE BOOKLET "What is High Fidelity?" and Suggestion List of Budget Hi-Fi Systems.

SEE PRECEDING PAGE FOR  
OTHER STERN-CLYNE PRODUCTS

### THE 'TRAVLER' MkII

Introducing our new ready-built transistorised car radio for ONLY **9 1/2 Gns.** P. & P. 5/-

including 7 x 4" speaker fitted to baffle, fixing brackets, filter unit, all nuts and bolts with fitting instructions **£2.19.6** H.P. Terms: Dep. (Plus 5/- P. & P.)



and 7 monthly Payments of £1.26. Star Features: ★ Handsomely Styled. ★ Mullard Valves and Transistors. ★ Push Buttons. ★ 14 watts Output. ★ Long and Medium Wavebands. ★ Quality Speaker (E.M.I.). ★ Easily Fitted. ★ Radio Luxembourg (and many other foreign stations) 12 volt Positive Earth Only (applies to 99.8% of the cars on the road). ★ Dimensions 7 x 2 x 7 1/2" depth. ★ Optional extras. 3 section chromium plated weatherproof telescopic aerials type 1 17/44, 19/6; type 2, 27/43, 29/6, both plus P. & P. 2/6 if purchased separately.

### POCKETCORDER TRANSISTORISED RECORDER

Why be bothered with a notepad? Take Pocketcorder with you on those business trips, the mighty Midget is ideal. Simply to operate, a unique 4-way push-button Switch for record/playback, etc., and remote control switch built into microphone ensures complete ease of handling. Fully adjustable speed through the life of Batteries and the volume and tone from the 2 1/2" internal speaker is outstanding. All accessories included such as Leather Case, Accessory Case, Crystal Earpiece, Tape, Batteries and Microphone, no other extras required. Up to 34 mins. recording time, operates on 1.9 volt PP3 and 2 1/4 volt U12 Pen Batteries. Size 5 1/2 x 4 x 2 1/2in. Weight 12 Gns. P. & P. 4/-. PRICE **12 Gns.** Spare 2 1/2" empty spools, 1/-; Spare 2 1/2" 200ft. L.P. Tape, 5/-.



### STEREO TAPE DECK WITH BUILT IN PRE-AMPLIFIER

A professional addition to your Hi-Fi Stereo System consisting of two basic Units, the Tape Deck and Pre-amplifier, which employs 4 Transistors and 4 Valves. The Unit with record and playback 1 track stereo or 1 track mono at either 7 1/2 i.p.s. or 3 1/2 i.p.s. both speeds being fully equalised.

Features: Track System: 1 track 2 channel stereo or monaural record and playback. Independent single channel recording on either channel while playback on other single channel record on either channel while playback on other single channel. Head Type: 1 track 2 channel inline stereo and associated erase heads. Low loss laminated pole pieces. Level indicators: 2 Meters, 1 per channel. Digital Counter: 3 digit tape position indicator. Automatic Stop: When tape runs out or breaks. Inputs: Microphone 1mV (50K ohms impedance) Gram/Tuner 50mV (high impedance). Output: (cathode follower). Monitor Sockets: 2 x 5K ohms impedance. Audio Output: 500mV. Oscillator: Pushpull 80 Kc/s, S/N Ratio: —45dB or better at 7 1/2" tape speed. Separation: 45dB or more between stereo channels. Frequency Response: 40 to 15,000 cycles per sec. at 7 1/2 i.p.s. 40 to 15,000 cycles per sec. at 3 1/2 i.p.s. Single Motor: 4 pole heavy duty induction type. Power Supply: 240v A.C. 50 cycles. Size: 6 1/2 x 10 1/2 x 15". Tape Size: Up to 7 Line Up: 4-2SB173 Transistors, 2-12AT7, 1-12AU7, 1-12BH7 Valves.



**42 GNS.** Carr. & Pkg. 15/-

### THE HE-40 4-BAND COMMUNICATION RECEIVER

Completely built and ready to go. High sensitivity Superhet receiver covering 550Kc/s—1.600Kc/s, 4.8Mc/s—14.5Mc/s, 16Mc/s—48Mc/s, 10.5Mc/s—30Mc/s. Illuminated slide rule dial, calibrated every 5Kc/s on 80 and 40 metres. Edgewise 5-meter, 0.100 logging scale. Coverage from 0.55—30Mc/s. 8 valve plus Rectifier superhet circuit. RF Stage with an Aerial Trimmer, 2 IF Stages, B.F.O. control Q-multiplier. Controls: Function Switch, Audio Gain, Selectivity (Q-multiplier) Frequency (BFO), Band Selector, IF Gain, Trimmer, AVC-MVC Switch, Ant Switch, Main Tuning, Bandspread Tuning and Headphone Jack. Selectivity—90dB at 10Kc/s, 0.8Kc/s at 6dB (with Q-multiplier). I.F. 455Kc/s. External PM Speaker reqd., 4 or 8 ohms impedance. Output 1.5 watts. 8 modern Miniature 37G Base Valves and 5Y3 Rectifier. Size 15 x 10 x 7 1/2in. Grey crackle finish. 220/240 volt A.C. mains, 50-60 cycle operation. Full instructions and circuit diagram supplied. Send S.A.E. PRICE **40 Gns.** Carr. & Pkg. 15/- for leaflet.



Sockets for optional outdoor aerial. Internal high flux monitor loudspeaker. Latest modern miniature 37G base valves. Headphone socket (may also be used for external loudspeaker). Ant. BFO, built-in "S" meter. 220/240 volt A.C. mains, 50-60 cycle operation. Handsomely styled cabinet with grey crackle finish and handsome front panel, with chrome and satin chrome fittings. Measures 13 1/2in. x 8 1/2in. x 5 1/2in. (high) and weighs only 11 lbs. A comprehensive instruction manual is supplied. An ideal receiver for the radio amateur and short wave listeners of all ages. Send S.A.E. for leaflet. PRICE **£24.15.0** Carr. & Pkg. 12/6

## INTRODUCTION OFFER!! Available Shortly



FOR  
ONLY  
**48 gns**

Plus 15/-  
Pkg. & Carr.

THE TUDOR STEREO HI-FI SYSTEM, comprising a Self Powered AM/FM Tuner, Stereo Pre-amplifier, 12 watt per channel Stereo Power Amplifier. The Tuner and Pre-amplifier are housed in matching black crackle finish metal cabinets for shelf mounting, with silver metal dials and matching knobs. Specifications: Tuner—Outstanding quality providing full VHF/FM long and medium waveband coverage. Frequency range FM 87.5-108.5 Mc/s, AM/MW 522-1630 Kc/s, LW 145-270 Kc/s 100mV output mains supply 105/240 A.C. Valve line-up: ECC85, ECH81, EBF89, EF80, EB91, EM84, ECC83. Multiplex outlet provided. Pre-amplifier—Designed for use with the Tudor Stereo Power Amplifier with inputs for most types of Pickups, direct play from Tape-Heads and ample sensitivity for either Crystal or Moving Coil Microphone. Distortion 0.1%. Tape outputs 100mV from 90K ohm



source. Inputs—Microphone 5 mV, Tape 5.3 mV, R.I.A.A. 4.3 mV flat 250 mV, Tuner 100 mV. Valve line-up: 2—EF86, 4—ECC83. Power Amplifier—14 watts per Channel, sensitivity 1 volt r.m.s. for 14 watts output, frequency response  $\pm 0.5dB$  20 c/s.—20 Kc/s. Speaker Impedance 4, 8 or 16 ohms, surplus power available for Tape Pre-Amp, mains supply 105/240 v. A.C. Valve line-up: 2—ECC83, 4—EL84, 1—GZ34.

## GREAT NEWS!

### We have pleasure in giving advance details of the NEW STERN DOUBLE FEATURE PRE-AMPLIFIER AND JLI0 POWER AMPLIFIER

A new conception in the field of audio engineering by  
Stern-Clyne development engineers.

The most up-to-date circuitry is used in the Double Feature Pre-amplifier. It has matched inputs for microphone, crystal or magnetic pick-ups and radio tuner and in addition offers full facilities for tape recording and high fidelity replay. This unique feature means that should you wish to include tape in your hi-fi system at a later date all that is required is a suitable tape deck. Offers superb reproduction from all sources at low cost. Available shortly. Brief Specifications:

#### JLI0 POWER AMPLIFIER

Incorporates the latest triode/pentode ECL86 valves in push-pull. PARTRIDGE ultra linear output transformer. PARTRIDGE mains transformer and smoothing choke. 10 watts power output, surplus power available for tuner output impedance 3-7.5-15 ohms.

PRICE: KIT OF PARTS **11 Gns.** Carriage and Insurance 7/6.

READY BUILT **14 Gns.**

#### DOUBLE FEATURE PRE-AMPLIFIER

Inputs for microphone, crystal or magnetic pick-ups, tuner unit. Push-button switching for 3 tape speeds equalised. Tape erase Bias Oscillator circuit incorporating ferroxcube transformer. Function switch, separate base, treble and volume controls, level control and latest EM87 magic eye level indicator. The pre-amplifier is totally enclosed in a steel case, finish in silver hammer and an attractive per-plex front panel carefully designed to blend in with modern wood finishes complete the presentation.

PRICE: KIT OF PARTS **21** Carriage and Insurance 5/-.

READY BUILT **21 Gns.**

PRICES: If both above units purchased together.

KIT OF PARTS **£27.10.0** Carriage and Insurance 10/-.

READY BUILT **32 Gns.**



### MODEL CR3/S TAPE RECORDER

MODEL CR3/S incorporates the HF/TR3 Mk. II Tape Amplifier (described below) and the Collaro "Studio" Twin Track 3-speed Deck operating at 14in., 3in., and 7in. speeds. Complete with microphone and 1200ft. tape.

KIT OF PARTS **£33.8.0**  
ASSEMBLED AND TESTED **£43.0.0**

(Carr. & Ins. 15/- extra).

Instruction book and detailed price list (free with kit) available separately at 3/- Post Free.

#### STEREO TAPE PRE-AMPLIFIER

MODEL STP-1. For use with current TRUVOX BRENNELL or COLLARO "STUDIO" 1 and 1 track Stereo Decks. Incorporates Ferroxcube Oscillator, 4-speed Equalisation Signal Level Meter and separate Gain Control. Includes separate Power Unit kit of **£22.0.0** (Carr. & Ins. 8/6) ASSEMBLED **£28.0.0**

Instruction book and detailed price list (free with kit) available separately at 3/- Post Free.

#### TAPE PRE-AMPLIFIER MULLARD Type "C"

Suitable for most 1 track, Mono Tape Decks. Incorporates Ferroxcube Push-Full Oscillator, Treble Inductor and 3-sp. Equalisation. Includes separate Power Unit.

KIT OF PARTS **£14.0.0** (Carr. & Ins. 7/6) ASSEMBLED **£19.10.0**

Instruction book and detailed price list (free with kit) available separately at 3/5 Post Free.

#### MULLARD TAPE AMPLIFIER

MODEL HF/TR3/MK.II Based on Mullard's Type "A" design and suitable for most 1 track Mono Tape Decks. Incorporates Ferroxcube Treble Inductor, Gilson Output Transformer, and 3-speed Equalisation. Includes separate Power Unit, using PARTRIDGE Mains Transformer.

KIT OF PARTS **£13.13.0** (Carr. & Ins. 7/6) ASSEMBLED **£19.0.0**

Instruction book and detailed price list (free with kit) available separately at 3/- Post Free.

## COMBINED PRICE OFFERS!!!

Includes small charge for special testing and PRECISE MATCHING OF THE ASSEMBLED PRE-AMPLIFIER (or Amplifier) to TAPE DECK

STP-1 (Kit) and "STUDIO" Deck	£39.0.0	Assembled	£46.0.0
STP-1 (Kit) and Brenell Deck	£26.0.0	Assembled	£27.0.0
STP-1 (Kit) and Truvox Deck	£51.0.0	Assembled	£58.0.0
TYPE "C" (Kit) and "STUDIO" Deck	£26.10.0	Assembled	£33.0.0
TYPE "C" (Kit) and BRENNELL Deck	£43.0.0	Assembled	£50.0.0
TYPE "C" Assembled and Wearite Deck	£70.0.0	Inc. Head Lift Trans.	
HF/TR3 (Kit) and "STUDIO" Deck	£28.0.0	Assembled	£33.0.0
HF/TR3 (Kit) and BRENNELL Deck	£43.0.0	Assembled	£50.0.0
HF/TR3 Assembled and Wearite Deck	£70.0.0	Inc. Head Lift Trans.	

## VISIT YOUR NEAREST STERN-CLYNE BRANCH

#### WEST END:

18 Tottenham Court Road, W.1.  
23 Tottenham Court Road, W.1.  
309 Edgware Road, W.2.

#### CITY:

109 Fleet Street, E.C.4.  
162 Holloway Road, N.7.

#### NORTH LONDON:

9 Camberwell Church Street, S.E.5.

#### SOUTH LONDON:

12 Suffolk House, George Street.

#### CROYDON:

26 Merchant Street, Bristol 1.

#### BRISTOL:

10 Withy Grove, Manchester 4.

#### MANCHESTER:

Mail Orders and enquiries to Dept. P.W.

162 Holloway Road, London, N.7. NORTH 8161/5


MUSEum 5929/0095 Half-day Sat  
MUSEum 3451/2 Half-day Thurs  
PADddington 6963 Half-day Thurs  
FLEet St. 5812/3 Half-day Sat  
NORth 8161/5 Half-day Thurs  
RODney 2875 Half-day Thurs  
MUNicipal 3250 Half-day Wed  
Bristol 20261 Half-day Wed  
BLACK Friars 5379 Now open 6  
days a week

Great Britain's Greatest Electronic Hobbies Organisation


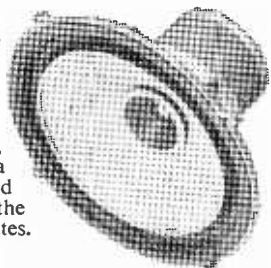
# Praise for the WHARFEDALE SUPER 10/RS/DD

The following letter is typical of many received praising the performance of the new Wharfedale Super 10/RS/DD, both of which have a remarkably wide and smooth response as the response curve indicates.



16 Grant House,  
Albion Avenue,  
LONDON, S.W.8.

Dear Mr. Briggs,

I feel I must write to you to say how pleased I am with my converted W10 Speaker (now a Super 10/RS/DD) which I received safely on Saturday.


The treble response is a delight to hear and even my poor quality records sound better, no doubt due to the absence of peaks in the middle and upper register. My pressure unit tweeter has now been dispensed with as it certainly cannot compete with the treble in your unit.

Being lucky enough to live within good range of Wrotham, I was able to put it through tests with various transmissions including the Proms, and we all have been most impressed—the bass improvement is also exceptionally good.

Yours sincerely,

Geo. H. Hunter.

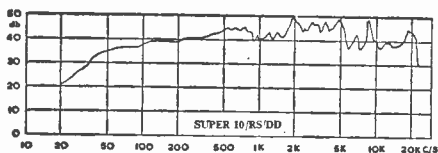Impedance 10/15 ohms only. 1in. dia. centre pole. Flux density 16,000 oersteds. Max. input 10 watts rms or 20 watts peak. Frequency range 30–20,000 c/s. Aluminium voice coil. Roll surround and double diaphragm. Axial response curve. Mic. distance 12in. Input 4 v. at 1,000 c/s.



PRICES: SUPER 10/RS/DD £10.18.8 including P.T.  
GOLDEN 10/RS/DD £7.17.5 including P.T.  
Descriptive Leaflet on request




WHARFEDALE WIRELESS WORKS  
IDLE BRADFORD YORKSHIRE

Grams: 'Wharfedel' Idle Bradford  
Phone: Idle 1235/6

## HARVERSON SURPLUS CO. LTD.

For address see  
opposite page

### OUR LATEST BULK PURCHASE!

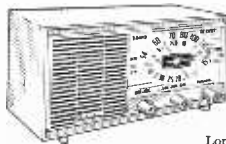


#### BRAND NEW A.C. MAINS 5 VALVE SUPERHET RADIO RECEIVERS

Housed in beautifully styled cabinets offering terrific performance and very high quality reproduction. Built-in ferrite rod aerial for reception of all your favourite programmes. Fully guaranteed.

MODEL 55 (as illus.). Covers Medium, Long and Short waves. Size 8 1/2 in. w. x 3 1/2 in. d. x 4 1/2 in. h. PRICE ONLY £7.17.6. P. & P. 5/6.

MODEL 38. Similar circuitry to above but covers Medium wave only. Size 7 1/2 in. w. x 3 1/2 in. d. x 4 1/2 in. h. PRICE ONLY £4.14.8. P. & P. 5/6. Either of the above can be easily adapted for use with AM Feeder unit.

### 3-VALVE AUDIO AMPLIFIER. MODEL HA34

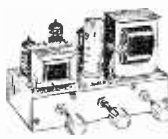

Designed for Hi-Fi reproduction of records A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2 in. w. x 4 in. d. x 4 1/2 in. h. Incorporates EUC83, EL84, EZ80. valves, heavy duty double wound mains transformer and output transformer matched for 3 ohm speaker, separate Bass, Treble and volume controls. Negative feedback line. Output 41 watts. Front panel can be detached and leads extended for remote mounting of controls.

The HA34 has been specially designed for us and our quantity order enables us to offer them complete with knobs valves, etc., wired and tested for only **£45.0** P. & P. 4/-

TWO VALVE AMPLIFIER similar to above but using EUL82 and EZ80. with tone and volume controls. Output 3 watts. PRICE 75/- P. & P. 4/-.

### SPECIAL OFFER! MARCONI QUARTZ CRYSTAL TYPES ZHB

Glass encapsulated, 2 wire lead out. Size 1 1/2 in. high x 1/2 in. dia. Following frequencies (Kc/s) only available  
13521, 13583, 13646, 13708  
13771, 13833, 13895, 13958  
14021, 14083, 14146, 14208  
14271, 14333, 14396, 14459  
6/- each. P. & P. 1/- per crystal,  
3 or more Post Free.

### 4-SPEED PLAYER UNIT BARGAINS

TU/12 SINGLE PLAYERS Carr. 3/6  
AUTO CHANGERS  
B.S.R. UA14 ..... £6.2.6  
Latest B.S.R. UA16 ..... £7.2.6  
LATEST GARRARD AUTO-SLIM  
with heavy-duty 4-pole motor.  
FEW ONLY £7.7.0. (Standard  
Auto-Slim £8.17.8). Carr. 5/- on each.


### SPECIAL TRANSISTOR BARGAINS ALL BRAND NEW

GET 15 Matched Pair 15/-  
OC71 5/- PXA101 6/6  
OC72 6/- XA103 6/6  
OC78 6/- V15/10p 12/6  
Set of Mullard 6 transistors, OC44,  
2-OC45, OC81D matched pair  
OC81, 25/-

#### EDISMAN MAZDA

R.F.1 Pack: 1-PXA102 Mixer;  
2-PXA101 L.F. Amp. (Equiv.  
OC44 and OC45) ..... 10/6  
R.F.2 Pack: 2-PXA101 L.F.  
PXA102 Osc.; 1-PXA102  
Mixer ..... 12/6  
L.F.6 Pack: Consisting of PXB113  
Driver. Matched pair PXG171,  
mounted complete with heat sinks  
(Equiv. OC81D and OC81) ..... 12/6  
ALL TRANSISTORS POST FREE

FEW  
ONLY

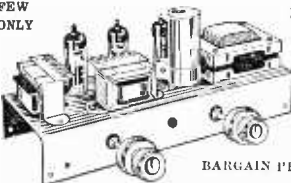

### STEREO AMPLIFIER

Incorporating 2 ECL82s and 1 EZ80, heavy duty, double wound mains transformer. Output 4 watts per channel. Full tone and volume controls. Absolutely complete.

BARGAIN PRICE **89/6** P. & P. 5/-

### BRAND NEW CAR RADIO AERIAL BARGAINS!

BY WELL KNOWN MAKER

Following types available for wing mounting: simple one hole fixing, all heavily chromed, telescopic and complete with coax plug and lead.

TYPE HS1. 3 section, open 43 1/2 in., closed 17 in. (list 32/6), OUR PRICE 22/-

TYPE HS2. 4 section, open 44 1/2 in., closed 21 in., length below wing 12 in., adjustable angle 0-25° (list 47/6) OUR PRICE 40/-

TYPE HS3. 5 section, open 41 in., closed 1 1/2 in., length below wing 9 1/2 in., adjustable angle 0-25°. Features a tamper-proof locking device, aerial cannot be extended without using special key provided. (list 57/6). OUR PRICE 60/-

All aerials plus 2/6 P. & P.




### TELEFUNKEN HI-FI STEREO AMPLIFIER

Model 882 with BALANCE CONTROL 110/250 v. A.C. input 5 watt undistorted output (10 watts nominal). Size 12 x 9 x 2 in. Weight 9 lb. (complete with spec. and instructions STILL ONLY £5.19.6. Carr. 7/-

### SPECIAL PURCHASE! TURRET TUNERS

by famous maker Brand new and unused. Complete with PC084 and PCF80 valves, 34-38 Mc/s I.F. Biscuits for Channels 1 to 3 and 8 and 9. Circuit diagram supplied. **ONLY 25/- each. P.P. 2/6.**

### F.M. TUNER HEAD

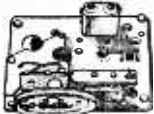

A permeability tuned tuner head by a famous maker, supplied without valve (ECC85) and drum and spindle, 15/8, plus 1/9 P. & P. Valve 3/6 extra. Drum and spindle 3/6 extra.

### GÖRLER F.M. TUNER HEADS

10.7 Mc/s I.F. 15/-, plus 1/9 P. & P. (ECC85 valve, 8/6 extra)

### E.M.I. 4-speed Player and P.U. FURTHER RUGE

PURCHASE enables us to offer these **67/6** P. & P. at 4/6.



Heavy 8 1/2 in. metal turntable. Low flutter performance 200/250v. shaded motor with tap at 45v. for amplifier valve filament if required. Turnover LF78 band.

### RECORD PLAYER AMPLIFIER


2 valve (E280 ECL82), A.C. mains, 3 watts output. ready built, tested and complete with valves and output transformer. Size 7 1/2 in. w. x 2 1/2 in. d. x 5 1/2 in. h. 55/- P. & P. 3/-. Suitable speakers: 8 in. 15/- P. & P. 1/6. 10 x 6 in. 25/- P. & P. 1/6.

### SPEAKER & CABINET FABRICS

Oatmeal, Red and Gold fabrics and various patterns in Vinyl and Tygan for speaker and cabinet covering. Also Red Rexine for cabinet covering only. All 5 1/4 in. wide and usually sold at 35/- yard. O.C.R. **PRICE 13/6** per yard plus P. & P. 1/6. (Minimum order 1 yard). Send S.A.R. for samples.
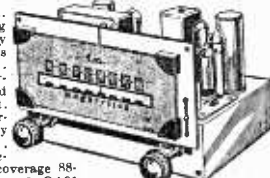
### HARVERSON'S F.M. TUNER Mk.1

● F.M. tuning head by famous maker. ● Guaranteed non-drift. ● Permeability tuning. ● Frequency coverage 88-100 Mc/s. ● OA81 balanced diode output. ● Two I.F. stages and discriminator. ● Attractive maroon and gold dial (7 x 3 in. glass). ● Self powered, using a good quality mains transformer and valve rectifier (rectifier). ● Fully drilled chassis. ● Size of completed tuner 8 x 6 x 5 1/2 in. ● All parts sold separately. Set of parts if purchased at one time **£5.19.8**, plus 8/6 P.P. and ins. Circuit diagram and instructions 1/6 post free. Mark II Version as above but complete with magic eye, front panel and brackets. **£5.12.8** P. & P. 8/6. Mark III Version as Mark I but with output stage (ECL82) and tone control. **£7.7.0** P. & P. 3/6. Handsome Metal Cabinets. Choice of Grey, Black or Green. To fit Mark I, 25/- P. & P. 2/6. To fit Mark II, 17/6. P. & P. 2/6.



### 6 TRANSISTOR AND DIODE SUPERHET

A first-class 2 waveband transistor superhet. ● Printed circuit panel (size 8 1/2 x 2 1/2 in.) ● 3 pre-aligned I.F. transformers. ● High-gain Ferrite rod aerial. ● All First-grade transistors. ● Car aerial windings. ● Push-pull output. ● All parts supplied with simple instructions. All parts sold separately. Set of parts if purchased at one time. **ONLY £4.5.0** P. & P. 2/6



### 35 OHM SPEAKERS

Suitable for use with above 2 in. Goodmans. Ideal replacement for most pocket portables 8/6; 2 1/2 in. 10/6; 3 1/2 in. 12/6; 5 in. 17/6; 7 x 4 in. 21/- P. & P. 1/6 per speaker.

### Portable CABINET

Size approx. 9 1/2 x 6 1/2 x 3 1/2 in. Suitable for above using 3 1/2 in. speaker. 26/- P. & P. 2/-.

### COIL AND TRANSFORMER SET FOR TRANSISTOR SUPERHET

3 I.F. transformers, one oscillator coil, one driver transformer and wound Ferrite aerial (med., long and aerial coupling). 28/6 complete, post 1/- 6 transistor printed circuit board to match. 8/6, post 5d. Circuit diagram 1/6 extra.

### QUALITY RECORD PLAYER AMPLIFIER

A top-quality record player amplifier. This amplifier (which is used in a 29 gn. record player) employs ECC83, EL84, E280 valves. Bass, treble and volume controls. Complete with output transformer matched for 3 ohm speaker.

**PRICE 69/6 P. & P. 3/6**

DITTO. Mounted on board with output transformer and 8 in. speaker.

**Complete at 89/6 P. & P. 4/6.**


### QUALITY PORTABLE RECORD PLAYER CABINET

Unseen motor board. Will take above amplifier and B.S.R. or CARBARD. Autochanger or Single Record Player Unit. Size 18 x 14 x 8 1/2 in. **PRICE £39.6** Carr. 5/-

### HIGH GAIN 4-TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT
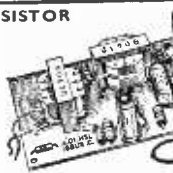
#### Type TAI

● Peak output in excess of 1 1/2 watts. ● All standard British components. ● Built on printed circuit panel, size 6 x 3 in. ● Generous size Driver and Output Transformers. ● Output transformer tapped for 3 ohm and 15 ohm speakers. ● Transistors (GET14 or 81 Mullard OC81D matched pair of OC81 op.) ● 9 volt operation. ● Everything supplied, wire, battery clips solder etc. ● Comprehensive easy to follow instructions and circuit diagram 1/6 (Free with Kit). All parts sold separately. Also ready built and tested, 62/6. P. & P. 2/6. A pair of TAI's are ideal for stereo.




#### SPECIAL PRICE

45/-

P. & P. 2/6.
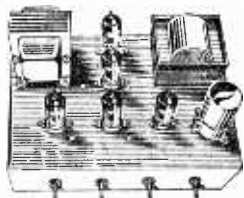
### 10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84 in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 ohm speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 1/6 (Free with parts). All parts sold separately. **ONLY £6.19.6** P. & P. 4/6. Also available ready built and tested complete with input jack plugs. **£8.15.0** P. & P. 5/6.



### BRAND NEW 3 OHM LOUDSPEAKERS

2 1/2 in. 12/6; 5 in. 12/6; 6 1/2 in. 15/-; 8 in. 21/-; 10 in. 25/-; 12 in. 27/6. K.M.I. 2 1/2 in. tweeter ... 10/6. 8 in. x 5 in. Ry famous maker ... 10/6. E.M.I. Ceramic 'Magnet' 1 1/2 in. x 8 1/2 in. high flux ... 36/-. Rola (selection approx. 9 in. x 6 in. midrange register speaker) 10/6. 10 in. x 6 in. ... 26/-. Also 16 ohm 12 inch, 30/- P. & P. up to 6 in. 1/8; over 6 in. 2/6 per speaker.

### AMPLIFIER CARRYING CASES

#### BRAND NEW

Strongly made wooden construction, tough vinyl covered, complete with carrying handles. Overall size 13 1/2 in. wide x 9 in. deep x 8 in. high with sloping front panel. Weight only 4 1/2 lbs. Ideal for our 10/14 watt amplifier and many others.

**BARGAIN PRICE 28/6** P. & P. 4/-

### AMPLIFIER ON PRINTED CIRCUIT BOARD

Two valve. UV85, U1A4. O.D. trans. use with 80 volt tap off motor, 39/6. P.P. 2/6 on above. Dropper res. for filaments if required 2/6.

### B.S.R. AUTO UNITS

150 v. suitable for use with above (slightly soiled.) **£4.4.0**

**Superior CABINET** To take 8 x 5 in. speaker, with motor board will accommodate BSR UA14 or UA16. **£3.8.8** Carr. 5/6. Speaker 15/- extra. P. & P. 1/6 extra.

**LARGE CABINET** Similar to above with 3 ohm speaker. **£9.9.9** Carr. 5/-.

### BARGAIN CORNER!!

**ACOS CRYSTAL MIKES.** High Imp. For desk or hand use. High sensitivity. 18/6. P. & P. 1/6.

**TSL CRYSTAL STICK MIKE.** Listed at 45/-. Our price 18/6. P. & P. 1/6.

**CARBON MIKE INSERTS.** Brand new, 2 1/2 in. dia. 3/6. P. & P. 9d.

**MIDGOT 2-GANG CONDENSERS.** Capacity 195 and 100 pF Polystyrene case with built-in trimmers. Size 1 x 1 x 1/2 in. Not used but removed from P/C boards. Two for 9/-, plus 1/- P. & P.

**TRANSISTOR DRIVER AND O/P TRANSFORMERS.** (Tapped 3 ohms and 15 ohms output), plus 4 suitable Transformers giving approx. 1 watt output. 30/- P.P. 2/6.

**3 PUSHBUTTON TRANSISTOR SWITCH.** D.P. - D.T. Each switch 5/6 and 1/- P. & P.

### MAINS TRANSFORMER

Drop thru' type. Tapped primary 110v., 200v., 220v., 240v. 320-0-320v. at 80ma and 6.3v. at 3 amps. Generous core. Stock size 3 1/2 x 2 1/2 x 1 1/2 in. Weight 4 lbs. **ONLY 15/- P. & P. 3/6.**

### 4-WAY NON-TANGLE TELEPHONE CABLE

Latest spring back coil type, extends 12 in. to 5 ft. Complete with rubber bushes. 3/6 each. P. & P. 1/-.

### COLLARO HI-FI STEREO T/O CARTRIDGE

Type 'T'. Complete with universal bracket and stylus for Stereo LP and 78. Original list price 59/8. **OUR PRICE 25/- P. & P. 1/-.**

**ACOS GP85/1 T/O MONO CRYSTAL CARTRIDGE.** Comp. with sapphire stylus and mounting bracket. Limited offer only at 12/6. P.P. 1/-.

### TAPE DECKS

**COLLARO STUDIO DECK** £10.10.0 plus 5/6 carr. and ins. **B.S.R. MONARDECK** (Single speed) 3 1/2 in. per sec., simple control, use 8 1/2 in. spools. **£8.16.0** plus 5/6 carr. and ins. (Tapes extra on both).

◀ LOOK OPPOSITE FOR MORE BARGAINS

## HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, S.W.19. CHerrywood 3985/6

Open all day Saturday Early closing Wed., 1 p.m.

A few minutes from South Wimbledon Tube Station. (Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY P. & P. ON OVERSEAS

ORDERS CHARGED EXTRA.


SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

# Brand new individually checked and guaranteed VALVES

AC/HL 4/6	Y1295 50/-	EP95 5/-
ACP4 6/8	E1145 30/-	EF183 8/-
ACPFEN 5/6	E1524 12/6	EF184 8/-
AR8 5/-	E2134 16/-	EL32 3/8
ARF3 3/6	E450 1/6	EL34 8/6
ARF4 3/6	E476 7/-	EL35 5/-
ARF12 2/6	E480 1/6	EL38 17/6
ARF21 7/6	EAC91 3/6	EL41 7/3
ARF24 3/6	EAF42 8/-	EL42 8/-
ARF34 4/6	EB34 1/6	EL50 9/-
ARTP1 6/8	EB91 3/6	EL81 8/6
ATP7 2/3	EB93 6/-	EL84 5/-
AU7 50/-	EB94 6/8	EL85 8/-
BS4 10/-	EB90 6/8	EL01 4/6
BS84 47/6	EBF50 6/8	EL55 6/8
BT19 25/-	EBF83 7/6	EM50 6/8
BT35 25/-	EBF89 6/8	EM81 7/6
BT45 15/-	EC53 12/6	EM84 8/-
BT63 35/-	EC70 8/-	EM85 9/-
CSL 2/6	EC90 20/-	EN31 10/-
CIC 6/6	EC91 3/6	EN208 9/-
CL33 9/-	ECX81 4/-	EY51 7/-
CV71 3/6	ECX82 5/-	EY56 5/6
CV77 6/6	ECX83 6/-	EY91 3/-
CV102 1/-	ECX84 6/8	EZ40 5/6
CV103 4/6	ECX85 6/8	EZ41 6/8
CV4014 7/-	ECX91 4/-	EZ50 5/6
CV4015 7/-	ECX90 7/6	EZ81 4/6
CV4025 10/-	ECX92 7/-	F0657 3/-
CV4046 40/-	ECX93 8/-	F0691 3/-
CV51 6/6	ECX94 8/-	F0693 3/-
D1 1/6	ECX95 8/-	F0694 3/-
D41 3/6	ECX96 8/-	F0695 3/-
D77 4/6	ECX97 8/-	F0696 3/-
DA30 12/6	ECX98 8/-	F0697 3/-
DAF96 6/6	ECX99 8/-	F0698 3/-
DD41 4/6	ECX100 8/-	F0699 3/-
DE75 4/6	ECX101 8/-	F0700 3/-
DE75 4/6	ECX102 8/-	F0701 3/-
DE75 4/6	ECX103 8/-	F0702 3/-
DE75 4/6	ECX347 8/-	F0946 3/-
DE75 4/6	ECX348 8/-	
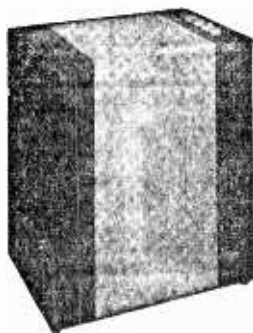
# THE R.S.C. BASS-MAJOR 30 WATT GUITAR AMPLIFIER

A MULTI-PURPOSE HIGH FIDELITY, HIGH OUTPUT UNIT  
FOR VOCAL AND INSTRUMENTALIST GROUPS



Eminently suitable for bass, lead or rhythm guitar and all other musical instruments

- \* Incorporating two 12in. heavy duty 25-watt high flux (17,000 lines) loudspeakers with 2in. diameter speech coils. Designed for efficiently handling full output of amplifier at frequencies down to 25 c.p.s.
- \* Dual Cone in second speaker reproduces frequencies up to 17,000 c.p.s.
- \* Heavily made cabinet of convenient size 24 x 21 x 14in. has an exceptionally attractive covering in two contrasting tones of Vynair.
- \* For 200-250 v. to 50 c.p.s. A.C. mains operation.
- \* Four jack socket inputs and two independent vol. controls for simultaneous connection of up to four instrument pick-ups or microphones.
- \* Separate bass and treble controls providing more than adequate "Boost" or "Cut"
- \* LEVEL frequency response throughout the audible range.
- \* SUPERIOR TO UNITS AT TWICE THE COST.

**39½ Gns.**

Send S.A.E. for leaflet.  
OR DEPOSIT OF £4.3.0 and 12 monthly  
payments of £3.9.11. Carr. 17/6.

**R.S.C. JUNIOR GUITAR AMPLIFIER**  
5-watt high quality output. Separate bass and treble "cut" and "boost" controls. Sensitivity 15 m.v. Two high impedance inputs. 10in. loudspeaker. Handsome, strongly made cabinet (size 14 x 14 x 7in. approx.) finished in attractive and durable polychrome. 200-250 A.C. mains operation. **£8.19.6** Or DEPOSIT £1 and 9 monthly payments of £1. Carr. 7/6.

**LINEAR TREMOLO/PREAMP. UNIT**  
Designed for introducing the Tremolo effect to any amplifier which is fitted with a reserve power supply point for smoothed H.T. and 6.3 v. A.C. L.T. This applies to practically all amplifiers of our manufacture, and to those of several other manufacturers. The unit plugs into power supply point and any input socket (frequency of interruptions). Depth (for heavy or light effect). Volume and Switch. Three sockets are for two inputs and Foot Switch. **4 Gns.** ONLY

**R.S.C. SENIOR 15 watt Guitar Amplifier**

For lead or rhythm guitar. High-fidelity push-pull output. Separate bass and treble "cut" and "boost" controls. Twin separately controlled inputs for two instruments or "mike" and pick-up can be used at the same time. Loudspeaker is a heavy duty high flux 12in. 20 watt model with cast chassis. Cabinet is well made and finished as Junior Model. Size approx. 18 x 18 x 8in.

Only **18 Gns.** Carr. 10/-

Send S.A.E. for leaflet.  
Or DEPOSIT 35/- and twelve monthly payments of 35/-.

## R.S.C. B20 BASS GUITAR AMPLIFIER



A highly efficient unit incorporating a massive 15in. high flux loudspeaker specially constructed to withstand heaviest load conditions. Rating 25 watts. Individual bass and treble controls give ample "boost" and "cut". Two inputs are separately controlled. All controls are conveniently positioned in a recess on top of the cabinet. Cabinet is of substantial construction and attractively finished in two contrasting tones of Rexine and Vynair. Size approx. 24 x 21 x 13in. Operation from 200-250 v. 50 c.p.s. A.C. mains.

**29½ Gns.** Send S.A.E. for leaflet.  
Or Deposit £23.2.0 and 12 monthly payments of 56/10. Carr. 17/6.

## DERBY NOW OPEN AT 26 Osmaston Road THE SPOT

**TRANSISTOR SALE.** Mullard OC71 3/9, OC45 4/11, OC44 4/11, OC72 4/8, OC81 4/11, OC11 8/9, Ediswan XA101 3/9, XB102 3/9, XA112 3/9, XB113 3/9, XB104 3/9, XC101A 3/9. Postage 6d. for up to 3 Transistors.

**D.C. SUPPLY KIT.** 12 v. 1 a. consisting of a partially drilled metal case, mains trans., F.W. Bridge Rectifier, 2 fuseholders and fuses. Change Direction switch, variable Speed regulator and circuit. For 200-250 v. A.C. mains. Suitable for Electric Trains. Limited number available at 29/11.

### SELENIUM RECTIFIERS

F.W. BRIDGE		24 v. 2 amp. . .	14/9
6/12 v. 1 a. . .	3/11	24 v. 20 amp. . .	89/9
6/12 v. 2 a. . .	6/11	H.T. TYPES H.W.	
6/12 v. 3 a. . .	9/9	150 v. 40 mA . .	3/8
6/12 v. 4 a. . .	12/3	250 v. 50 mA . .	3/11
6/12 v. 6 a. . .	15/3	250 v. 60 mA . .	4/11
6/12 v. 10 a. .	26/9	250 v. 80 mA . .	5/11
6/12 v. 15 a. .	35/9	250 v. 250 mA . .	11/9
CONTACT COOLED. 250 v. 75 mA. F.W.			
(Bridge). 10/11. 250 v. 50 mA. F.W. (Bridge).			
8/11. H.W. 250 v. 60 mA. 5/11.			

**CONTACT COOLED.** 250 v. 75 mA. F.W. (Bridge). 10/11. 250 v. 50 mA. F.W. (Bridge). 8/11. H.W. 250 v. 60 mA. 5/11.

### HI-FI 10-WATT AMPLIFIERS

Brand New Complete **£7.19.9** Carr. 5/6  
Manufacturers' discontinued Model. Push-Pull output. Latest high efficiency valves. Dual separately controlled inputs for "Mike". Separate Bass and Treble Controls. High sensitivity. Output for 3 or 15 ohm speaker. Guaranteed tested and in perfect working order.

**HUGE PURCHASE OF BRAND NEW 24 v. 20 amp. F.W. (BRIDGE) SELENIUM RECTIFIERS.** each **49/9**

**HEAVY DUTY LOUDSPEAKERS IN SUBSTANTIAL REXINE COVERED CABINETS.** Type BGL Suitable for Bass Guitar. Speaker Unit 15in. High Flux. 15 ohms. 30 watts. Cabinet size approx. 24 x 21 x 13in. Only 19½ gns. Or Deposit 37/6 and 12 monthly payments of 37/6.

Type BG2 Suitable for Bass Guitar. Super Sensitive. 15in. 15 ohms high flux speaker. Cabinet size approx. 30 x 21 x 14in. Attractive covering of two contrasting tones of Rexine and Vynair. Rating 50 watts. Only 29 gns. Or Deposit £3.7.6 and 12 monthly payments of 50/-.

Type BG3/2 Suitable Bass and Lead Guitar. Two 12in. high flux 15 ohms 25 watt speakers, one with aluminum speech coil and dual cone to provide smooth frequency response from 25 to 17,000 c.p.s. Cabinet size approx. 30 x 21 x 14in. Covered in two contrasting tones of grey Vynair and Rexine. Rating 50 watts. Only 29 gns. Or Deposit £3.7.6 and 12 monthly payments of 50/-.

**LARGE REXINE COVERED SPEAKER CABINETS.** Heavy blockboard construction. Very attractive two tone covering of Rexine and Vynair. Size 30 x 21 x 16in. cut for 15in. or 18in. speaker or for two cut for 15in. or 18in. speaker 25/9 and 9 monthly payments 25/9. Size 30 x 30 x 16in. cut for 15in. or 18in. speaker 13 gns. or Deposit 30/4 and 9 monthly payments 30/4. Suitable speakers available.

**FANE EXTRA HEAVY DUTY LOUDSPEAKER 15in. TYPE 153.** 40 watts. Total flux 375,000 lines. Extremely high sensitivity. 15 ohm voice coil. Only 18 gns. or Deposit 35/- and 12 monthly payments 35/-.


**FANE EXTRA HEAVY LOUSPEAKER** 183 18in. 15 ohms 60 watts, 3in. diam. Speech coil. Total Flux 375,000 lines. High sensitivity. ONLY 25 gns. or Deposit 52/9 and 12 monthly payments of 43/- Send S.A.E. for leaflet on 153 and 183.

**EX. GOVT. SMOOTHING CHOKES.** 200 mA. 3-5 H. 50 ohms. Parmeko 8/9; 150 mA. 10 H. 50 ohms 9/9; 80 mA. 20 H. 900 ohms 5/9; 120 mA. 12 H. 100 ohms 8/9; 50 mA. 50 H. 1,000 ohms 6/9; 100 mA. 10 H. 100 ohms 8/9; 60 mA. 5-10 H. 250 ohms 2/11.

**COMPLETE POWER PACK KIT 19/11** Consisting of Mains Trans., Metal Rectifier, Double electrolytic, smoothing choke chassis and circuit. For 200-250 v. A.C. mains. Output 250 v., 60 mA. 6.3 v. 2 a.

**R.S.C. POWER PACK, 39/9.** Louvered metal case only 8 x 5 x 2 1/2 in. Store enamelled. For 200-250 v. A.C. mains. Output at 4 pin plug and socket 250 v. 60 mA, fully smoothed and 6.3 v. 2 a. Suitable for power requirements of almost any Pre-amp. or Radio Tuner.

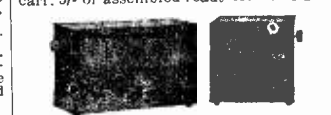**R.S.C. BABY ALARM or INTERCOMM. KIT.** Complete set of parts with diagrams, etc. Housed in two polished walnut finished cabinets of pleasing design. High sensitivity. For 200-250 v. A.C. mains. Fully isolated. Controllable at both units. An intercomm. of this class would normally cost £20-£30. Only 89/6, carr. 5/- or assembled ready for use 6 gns.



**EX. GOVT. SELENIUM RECTIFIERS 12v. 15 AMP (BRIDGE) F.W. ONLY 19/9**

## R.S.C.

(Manchester) Ltd.

LEICESTER  
32 High St.

Half-day  
Thursday

BIRMINGHAM  
6 Gt. Western  
Arcade

(Opp Snow Hill  
Sta) No half-day

SHEFFIELD  
13 Exchange St.

Half-day Thursday

HULL  
51 Savile  
St., Hull

Half-day Thursday

LIVERPOOL  
73 Dale St.

Half-day Wednesday

BRADFORD  
56 Morley St.  
(Above Alhambra  
Theatre) Bradford

Half-day Wednesday

MANCHESTER  
8-13 Brown St.  
(Market St.)

Manchester 2  
No half-day

LEEDS  
5-7 County  
(Mecca) Arcade

Briggate, Leeds  
Half-day Wed.

MAIL ORDERS to 5 County Arcade, Leeds 1. Terms: C.W.O. or C.O.D. No C.O.D. under £1. Postage 2/9 extra under £2. 4/6 extra under £5. Trade Supplied. S.A.E. with all enquiries please.

**R.S.C.**(Manchester)  
Ltd.MAIL ORDERS to 5 County Arcade, Leeds 1. Terms: C.W.O. or C.O.D. No C.O.D. under £1  
Postage 2/9 extra under £2. 4/6 extra under £5. Trade Supplied. S.A.E. with all enquiries please.

LEICESTER

BIRMINGHAM

SHEFFIELD

HULL

LIVERPOOL

BRADFORD

MANCHESTER

LEEDS

32 High St.

6 Gt. Western

13 Exchange St.

51 Savile

73 Dale St.

56 Korfey St.

8-10 Brown St.

5-7 County

Half-day

Arcade

Castle Market

St., Hull

Liverpool 2

(above Ambra

(Market St.)

Briggate, Leeds

Thursday

(Opp Snow Hill

Bldgs. Sheffield

Half-day Thursday

Half-day Wednesday

Theatre) Bradford

No half-day

Half-day Wed.

**FANE HEAVY DUTY HI-FI SPEAKERS**

12in. 15 ohms. Cast chassis. Exceptionally robust 2in. diam. Voice Coil Assemblies.  
 122/12 20w., 5 gns. 122/10A 20w., 6 gns.  
 122/12 20w., 6 gns. 122/12A 20w., £7.19.6  
 122/14 22w., 8 gns. 122/14A 22w., 10 gns.  
 122/17 25w., 11 gns. 122/17A 25w., 12 gns.  
 15in. 15 ohms. Cast chassis. Exceptionally robust 2in. diam. Voice Coil Assemblies.  
 152/12 20w., 12 gns. 152/12A 20w., 13 gns.  
 152/14 27w., 14 gns. 152/14A 27w., 15 gns.  
 152/17 35w., 16 gns. 152/17A 35w., 17 gns.  
 "A" indicates dual cone type, 30-17,000 c.p.s. Send S.A.E. for leaflets. Terms available.

**R.S.C. 30-WATT ULTRA LINEAR**

**HIGH FIDELITY AMPLIFIER A10**  
 A highly sensitive Push-Pull high output unit with self-contained Pre-amp. Tone Control Stages. Certified performance figures compare equally with most expensive amplifiers available. Hum level 70 db down. Frequency response -4.3 db, 30-30,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 807 output valves. All components are chosen for reliability, six valves are used EF86, EF86, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls are provided. Minimum input required for full output is only 12 millivolts so that **ANY KIND OF MICROPHONE, OR PICK-UP IS SUITABLE.** The unit is designed for CLUBS, SCHOOLS, THEATRES, DANCE HALLS or OUT-DOOR FUNCTIONS, etc. For use with Electronic ORGAN, GUITAR, STRING BASS, etc. For standard or long-playing records. **OUTPUT SOCKET PROVIDES L.T. and H.T. for a RADIO FEEDER UNIT.** An extra input with associated vol. control is provided so that two separate inputs such as Gram and "Mike" can be mixed. Amplifier operates on 200-250 v. 50 c/s. A.C. Mains and has output for 3 and 15 ohm speakers. Complete Kit of parts with fully punched chassis and point-to-point wiring diagrams and instructions. If required perforated cover with carry handles can be supplied, £1.25 extra. **TERMS: DEPOSIT 33/9** and 9 monthly payments of 33/9. Suitable microphones and speakers available at competitive prices.

**11 Gns.**

Carr. 10/-


for 19/9. The amplifier can be supplied, £1.25 extra, with carry handles and 12 months guarantee, for 14 Gns. Send S.A.E. for leaflet.

**WE STOCK ARMSTRONG, DULCI, LINEAR, ROGERS, LEAK and JASON EQUIPMENT. GOODMAN'S, W.B. AND FANE SPEAKERS. GARRARD AND GOLDRING T/ABLES CASH or H.P.**

**SUPERHET FEEDER UNIT.** Design of a high quality Radio Tuner (specially suitable for use with our Amplifiers). Delayed A.V.C. Controls are tuning W.Ch. and Vol. Only 250 v. 15 mA. H.T. and L.T. of 6.3 v. 1 amp. required from amplifier. Size approx. 9 x 6 x 7in. High. Simple alignment procedure. Point-to-Point wiring diagrams, instructions and priced parts list with illustrations, 2/6. Total building cost £4.15.0. S.A.E. for leaflet.

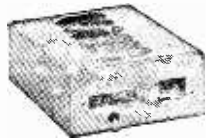**R.S.C. BATTERY TO MAINS CONVERSION UNITS**

Type BM1. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 in. approx. Completely replaces battery supplying 1.4 v. and 90 v. where A.C. mains 200-250 v. 50 c/s is available. Suitable for all battery portable receivers, requiring 1.4 and 90 v. This includes low consumption types. Complete kit with diagrams, 39/9, or ready to use, 46/6.



kit of parts with diagrams and instructions, 49/9, or ready for use, 59/6.

**P.M. SPEAKERS.** 10in. W.B. "Stentorian" 3 or 15 ohms type HF 1012 10 watts, hi-fidelity type. Recommended for use with our A11 Amplifier, £4.7.6. 12in. R.A. 3 ohms 10 watts (12,000 lines), 59/6.

**TWEETERS.** R.A. 3 ohm, 19/9; 15 ohm, 25/9

**R.A. 12in. DUAL CONE 3 ohm 8 watt Speakers.** Ideal for Stereo. Only 39/9 ea.

**Jason FMTI V.H.F./F.M. Radio Tuner design.** Total cost of parts including valves, Tuning dial, Escutcheon, etc., £7.19.6.

**LINEAR L45 MINATURE 45 WATT QUALITY AMPLIFIER.** Suitable for record playing unit, and most microphones. Negative feedback 12 db. Separate Bass and Treble Controls. For mains 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Mullard valves E280, ECC83, EL81. Size only 7 1/2 x 5 1/2 in. high. Guaranteed 12 months. Only £5.19.6. Send S.A.E. for leaflet. Terms: Deposit 22/6 and 5 monthly payments of 22/6.



220-250 v. 50 c/s. Output for 2-3 ohm speaker. In every detail and includes fully punched chassis (with baseplate) with Blue Hammer finish and point-to-point wiring diagrams and instructions. Exceptional value at only £4.15.0, or assembled ready for use 25/- extra. Plus 3/6 carr., or deposit 22/6 and 5 monthly payments of 22/6 for assembled unit.

**NOW OPEN AT 26 Osmaston Road THE SPOT**

**DERBY**

**R.S.C. GRAM AMPLIFIER KIT.** 3 watts output. Negative feedback. Controls Vol. Tone and Switch. Mains operation 200-250 v. A.C. Fully isolated chassis. Circuit, etc., supplied. Only 39/9. Carr. 3/9.

**THE SKYFOUR T.R.F. RECEIVER.** A design for a valve long and medium wave 200-250 v. A.C. Mains receiver with selenium rectifier. High gain H.F. stage and low distortion detector. Valve line-up 6K7, 5P61, 6V6G. Selectivity and quality excellent. Simple construction. Point-to-point wiring diagrams, instructions and parts list 1/9. maximum building costs £4.19.6. inc. attractive walnut veneered wood cabinet 12 x 6 1/2 x 5 1/2 in.

**MULTI-METERS.** CARY M1. Sensitivity 2,000 ohms per volt. A.C. and D.C., 54/- A.10. Basic Meter sensitivity 155 microamps A.C. and D.C. ranges £4.17.6. B.20. Sensitivity up to 10,000 ohms per volt A.C. and D.C., £6.10.0. 30,000 ohms per volt, with overload buzzer, £9.19.6.

**R.S.C. JUNIOR HI-FI REPRODUCER.** The very latest Goodman Axiote 8 High Fidelity loudspeaker (retailing at approx. 5 gns.) fitted in a specially designed Bass Reflex cabinet size 12 x 18 x 10in. Acoustically lined and ported and finished in polished walnut veneer. Thereby completely replacing both H.T. batteries and L.T. 2 v. accumulators when connected to A.C. mains supply 200/250 v. 50 c/s. **STUTABLE FOR ALL BATTERY RECEIVERS** normally using 2 v. accumulators. Complete kit of parts with diagrams and instructions, 49/9, or ready for use, 59/6.

**8 Gns.**

Carr. 4/6.

**12in. 10 WATT HIGH QUALITY LOUSPEAKER**

18 x 18 x 10in. Finish as above. Terms: Deposit 17/9 and 9 monthly payments of 17/9. Only £7.19.6. Carr. 3/6. For larger types see preceding page.

**LINEAR LG34 GRAM AMPLIFIER.** High quality. Separate Bass and Treble controls. Handsome appearance. Completely enclosed. Black/Gold Frontplate 5 gns.

**R.S.C. 45 WATT A5 HIGH-GAIN AMPLIFIER**

A highly-sensitive 4-valve quality amplifier for the home, small club, etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest hi-fi fidelity pick-up heads, in addition to all other types of pick-ups and practically all "mikes". Separate Bass and Treble Controls are provided. These give full long-playing record equalisation. Hum level is negligible being 71 db. down, 15 db. of Negative feedback is used. H.T. of 300 v. 25 mA. and L.T. of 6.3 v. 1.5 A. is available for the supply of a Radio Feeder Unit, or Tape-Deck pre-amplifier. For A.C. mains input of 200-250 v. 50 c/s. Chassis is not alive. Kit is complete Hammer finish and point-to-point wiring diagrams and instructions. Exceptional value at only £4.15.0, or assembled ready for use 25/- extra. Plus 3/6 carr., or deposit 22/6 and 5 monthly payments of 22/6 for assembled unit.

**R.S.C. BASS REFLEX CABINETS, JUNIOR MODEL.** Specially designed for W.B. HF1012 Speaker, but suitable for any good quality 10in. speaker. Acoustically lined and ported. Polished walnut veneer finish. Size 18 x 12 x 10in. Handsome appearance. Ensure superb reproduction for only £3.19.6.

**STANDARD MODEL.** As above but for 12in. speakers. Size 20 x 15 x 13in. For vertical or horizontal use, £5.19.6. Suitable legs with brass ferrules, 19/6 per set of 4.

**R.S.C. CORNER CONSOLE CABINETS**

Polished walnut veneer finish. Please refer to JUNIOR MODEL. Size 20 x 11 x 8in. for 8 x 5in. or 10 x 6in. speakers, £2.9.9.

**STANDARD MODEL.** Size 27 x 18 x 12in. for 8 or 10in. speakers, £4.11.9.

**SENIOR MODEL.** Size 30 x 20 x 15in. for 12in. Speaker. Suitable Speaker systems below. Only 7 gns.

**AUDIOTRINE HI-FI SPEAKER SYSTEMS.** Consisting of matched 12in. 12,000 line, 15 ohm high quality speaker; cross-over unit (consisting of choke, condenser, etc.) and Tweeter. The smooth response and extended frequency range ensure surprisingly realistic reproduction. Standard 10 watt rating £4.19.9. Carr. 5/-. Or Senior 15 watt, £6.19.8. Carr. 7/6.

**AUDIOTRINE EQUIPMENT CABINETS.** Size 36 x 15 x 18in. Beautiful walnut veneered finish. Elegant contemporary design. Robust construction. Uncut, removable baseboard. Depth above baseboard 5 1/2".

Only 12 gns. Carr. 15/-. Terms: Dep. 29/9, and 9 mthly. pymts. 29/9.



# AUDIOTRON HI-FI TAPE RECORDER KIT 25 1/2

**REALISM AT INCREDIBLY LOW COST, CAN BE ASSEMBLED IN AN HOUR**  
Incorporating the latest Collaro Studio Tape Transcriber. The Audiophone High Quality Tape Amplifier with negative feedback equalisation for each of 3 speeds. High Flux P.M. Speaker, empty Tape Spool, a Reel of Best Quality Tape and a Handsome Portable carrying Cabinet with latest attractive two-tone polychrome inner, size 14 1/2 x 15 x 8 1/2 in. high and circuit. Total cost if purchased individually approximately £40. Performance equal to units in the £60-£80 class. S.A.E. for leaflets. **TERMS:** Deposit £2.13.9 and 12 monthly payments of 44/- Cash price if settled in 3 months.

## HIGH FIDELITY 12-14 WATT AMPLIFIER TYPE A11


**PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP STAGES**

Two input sockets with associated controls allow mixing of "mike" and gram, as in A10. High sensitivity. Includes 5 valves, ECC83, ECC83, EL84, E281. High quality sectionally wound output transformer specially designed for Ultra Linear operation and reliable small condensers of current manufacture. **INDIVIDUAL CONTROLS FOR BASS AND TREBLE "Lift" and "Cut".** Frequency response  $\pm 3$  db 30-30,000 c/s. Six negative feedback loops. Hum level 60 db down. **ONLY 23 millivolts INPUT** required for **PULL OUTPUT**. Suitable for use with all makes and types of pick-ups and microphones. Comparable with the very best designs for **STANDARD or LONG PLAYING RECORDS**. For **MUSICAL INSTRUMENTS** such as **STRING BASS, LEAD OR RHYTHM GUITARS, etc.** **OUTPUT SOCKET** with plug provides 300 v. 30 mA. and 6.3 v. 1.5 A. For supply of a **RADIO FEEDER UNIT**, size approx. 12 x 9 x 7 in. For A.C. mains 200-250 v. 50 c/s. Output for 3 and 15 ohms speakers. Kit is complete to last in chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. **Only 8 Gns.** (factory built 51/- extra.)

If required loured metal cover with 2 carrying handles can be supplied for 18/9. **TERMS ON ASSEMBLED UNITS.** DEPOSIT 24/9 and 9 monthly payments of 24/9. Send S.A.E. for illustrated leaflet detailing Cabinets, Speakers, Microphones, etc., with cash and credit terms.

**LINEAR TAPE PRE-AMPLIFIER.** Type LPH. Switched Negative feedback equalisation. Position for Record (lin. 3 in. 3 in. and Playback. E281 Recording level indicated primarily as the link between a Collaro Tape Transcriber and a high fidelity amplifier, but suitable for almost any Tape Deck. **only 9 gns.** S.A.E. for leaflet.
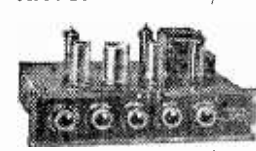
## R.S.C. STEREO/TEN HIGH QUALITY AMPLIFIER



A complete set of parts for the construction of a stereo-phonograph amplifier giving 5 watts high quality output on each channel (total 10 watts). Sensitivity is 50 millivolts. Suitable for all crystal stereo heads. Ganged Bass and Treble Control give equal variation of "lift" and "cut". Provision is made for use as straight (monaural) 10-watt amplifier. Valve line-up ECC83, ECC83, EL84, EL84, E281. Outputs for 2-ohm speakers. Point-to-point wiring diagrams and instructions supplied. Send S.A.E. for leaflet. **8 Gns.** Full constructional details and price list 2/6. Carr. 10/-.

Kit can be supplied assembled ready to use for 59/6 extra.

## SENSATIONAL STEREO OFFER

A complete set of parts to construct a good quality Stereo amplifier with an undistorted output total 20 watts. For A.C. mains input of 200-250 v. Sensitivity 130 m.v. Ganged Vol. and Tone Controls. Preset balance control. Full instructions and wiring diagrams supplied. Stereo Pick-up Head 19/9 extra with above only.

**HEAVY DUTY CHARGER KIT.** F/12 v. 6 amps., variable output. Consisting of Mains Transformer 0-200-250 v. F.W. (Bridge) Selenium Rectifier; Ammeter; Variable Charge Rate Selector Panels; Plugs; Fuses; Fuseholder and circuit. 59/0. Carr. 4/6.

## R.S.C. BATTERY CHARGING EQUIPMENT

Guaranteed 12 months

**ASSEMBLED 4.5 amps 6/12 v.**  
Fitted Ammeter and variable charge rate selector. Also selector plug for 6 v. or 12 v. charging. Loured blue hammer finish. Fused and ready for use **69/9** with mains and 5/- output leads. Carr. 5/-. **Terms:** Deposit 13/3 and 5 monthly payments 13/3 6/12 v. 3a. all facilities as above. Only 59/9, carr. 3/9.

**CHARGER KIT, 12V. 4 AMP. or 24V. 2 AMP.** Consisting of mains trans., 200-250 v. F.W. (Bridge) selenium Rectifier, Ammeter, Fuses, Variable Selector and circuit. **6 gns.** Carr. 15/-. Please state if 12 v. or 24 v. kit required.

**BATTERY CHARGER KITS** Consisting of Mains Transformer, Bridge, Metal Rectifier, well ventilated steel case. Fuses. Fuseholders. Grommets, panels, Heavy Duty Clip, circuit. Carr. 3/6 extra.  
6 v. or 12 v. 1 amp. **22/9**  
As above, with Ammeter 28/9  
6 v. 2 amps. **19/9**  
6 v. or 12 v. 2 amps. **25/9**  
6 v. or 12 v. 2 amps. inclusive of Ammeter. **35/9**  
6 v. or 12 v. 4 amps. **45/9**  
6 v. or 12 v. 4 amps. with Ammeter and variable charge rate selector. **52/9**

**CHARGER AMMETER.** 1.5 A. 0-4 A. 8/9 ea.  
**CHARGER KIT, 12V. 10 AMP** with variable charge rate adjustment and ammeter. **£4.19.6.** Carr. 10/-.

## R.S.C. MAINS TRANSFORMERS (GUARANTEED)

Interleaved and Impregnated. **Primarys 250-250-250 v. 50 c/s.**  
**TOP SHROUDED DROP THROUGH**  
250-0-250v. 70mA. 6.3v. 2a. 0.5-6.3v. 2a. **17/9**  
350-0-350v. 80mA. 6.3v. 2a. 0.5-6.3v. 2a. **18/9**  
250-0-250v. 100mA. 6.3v. 2a. 0.5-6.3v. 1a. **21/9**  
250-0-250v. 100mA. 6.3v. 3.5a. C.T. **25/9**  
250-0-250v. 100mA. 6.3v. 4a. 0.5-6.3v. 3a. **25/9**  
300-0-300v. 130mA. 6.3v. 4a. 6.3v. 1a. for Mullard 51A Amplifier **29/9**  
300-0-300v. 100mA. 6.3v. 4a. 0.5-6.3v. 3a. **26/9**  
350-0-350v. 100mA. 6.3v. 4a. 0.5-6.3v. 3a. **26/9**  
350-0-350v. 150mA. 6.3v. 4a. 0.5-6.3v. 3a. **29/9**  
425-0-425v. 200mA. 6.3v. 4a. 5v. 3a. **49/9**  
**FULLY SHROUDED UPRIGHT**  
250-0-250v. 60mA. 6.3v. 2a. 0.5-6.3v. 2a. **17/11**  
Midnight type 2 x 2 in. **21/9**  
250-0-250v. 100mA. 6.3v. 4a. 0.5-6.3v. 3a. **27/9**  
300-0-300v. 100mA. 6.3v. 1a. 0.5-6.3v. 3a. **27/11**  
300-0-300v. 130mA. 6.3v. 4a. C.T. 6.3v. **33/9**  
1a. for Mullard Amplifier **27/11**  
350-0-350v. 100mA. 6.3v. 4a. 0.5-6.3v. 3a. **27/11**  
350-0-350v. 150mA. 6.3v. 1a. 0.5-6.3v. 3a. **35/9**

**FULLY SHROUDED (continued)**  
425-0-425v. 200mA. 6.3v. 4a. C.T. 5v. 3a. **55/-**  
425-0-425v. 200mA. 6.3v. 4a. C.T. 6.3v. 4a. C.T. 5v. 3a. **59/9**  
450-0-450v. 250mA. 6.3v. 4a. C.T. 5v. 3a. **69/9**  
**OUTPUT TRANSFORMERS**  
Midget Batter Pentode 66:1 for 3S4. **4/6**  
etc. **4/6**  
Small Pentode 5,000 $\Omega$  to 3 $\Omega$ . **4/6**  
Small Pentode 778:300 $\Omega$  to 3 $\Omega$ . **4/6**  
Standard Pentode 5,000 $\Omega$  to 3 $\Omega$ . **4/6**  
Standard Pentode 7,000 $\Omega$  to 3 $\Omega$ . **5/9**  
10,000 $\Omega$  to 3 $\Omega$ . **5/9**  
Push-Pull 8watts, EL84, or 6V6 to 3 $\Omega$  or matched to 15 $\Omega$ . **9/9**  
Push-Pull 10-12 watts to match 8V6 or EL84 to 3.5-8 to 15 $\Omega$ . **19/9**  
Following types for 1 and 15 $\Omega$  speakers:  
Push-Pull 10-12 watts 6V6 or EL84. **18/9**  
Push-Pull 15-18 watts 6V6 or EL84. **22/9**  
Push-Pull Mullard 51A Ultra Linear. **29/9**  
Push-Pull 20 watts, sectionally wound, 6L6, KT66, EL84, etc. **49/9**

**MIDGET MAINS Primarys 200-250 v. 50 c/s.** 250v. 60mA. 6.3v. 2a. **11/9**  
0-250-0-250v. 60mA. 6.3v. 2a. **12/11**  
Both above size 2 1/2 x 2 1/2 in.


**FILAMENT TRANSFORMERS**  
All with 200-250v. 50 c/s primarys 6.3v. 1.5a. 5/9; 6.3v. 2a. 7/8; 0.4-6.3v. 2a. 7/8; 1.2a. 1.11; 6.3v. 3a. 8/11; 6.3v. 6a. 17/6; 12v. 1.5a. twice, 17/6.

**SMOOTHING CHOKES**  
150mA. 7-10 H. 250 ohms. **11/9**  
100mA. 10H. 250 ohms. **8/9**  
80mA. 10H. 350 ohms. **5/9**  
60mA. 10 H. 400 ohms. **4/11**







**CHARGER TRANSFORMERS**  
All with 200-250v. 50 c/s Primarys:  
0.9-15v. 11a. 12/9; 0.9-15v. 2a. 14/9; 0.9-15v. 3a. 16/9; 0.9-15v. 5a. 19/9; 0.9-15v. 6a. 23/9; 0.9-15v. 8a. 28/9.  
**ATO (step up/Step down) TRANS.**  
0.110-120-230-250v. 50-80 watts. 13/9;  
250 watts. 39/9; 150 watts. 27/9.

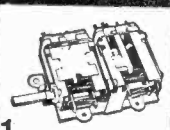**MICROPHONE TRANSFORMERS**  
120-1. high grade, clamped. 8/9.





# Just a few of our **BARGAINS**

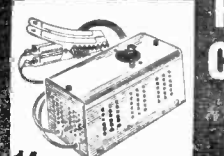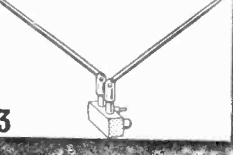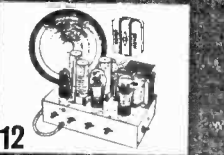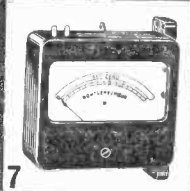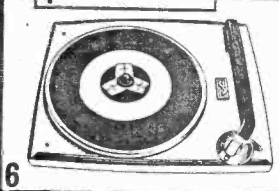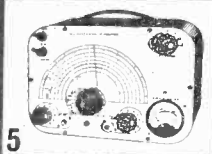

**RADIO & T.V.  
COMPONENTS  
[ACTON]  
LIMITED**

- 1. A.M. F.M. PERMEABILITY TUNER FOR ALL TRANSISTOR OPERATION.** Size 2½ x 2½ in. approx. By famous manufacturer. A.M.-I.F. 470Kc/s. P.M.-I.F. 10.7 Mc/s. A.M. coverage from 1620 Kc/s-525 Kc/s. P.M. coverage 108Mc/s-55Mc/s. Circuit diagram 2/6. FREE with Tuner. 25/-, 1st, 2nd, 3rd A.M. I.F.'s, 12/6 set, 1st, 2nd, 3rd and 4th F.M. I.F.'s, 12/6 set. V.H.F. Osc. choke. 1/- A.M. I.F. trap. 1/6. A.F. 114 and A.P. 115. 5/- each. All the above are the R.P. end of an AM/F.M. receiver car radio, etc. The above six items purchased together £2.10.0.
- 2. TRANSISTORISED POCKET RADIO** with printed circuit, mini-circuit, high gain ferrox slab aerial. No aerial or earth required. To build yourself for completely personal listening. 4½ x 3½ x 1½ in. Luxembourg in favourable areas. Only 21/-, P. & P. 2/6. All parts available separately.
- 3. A.C./D.C. POCKET MULTI-METER KIT.** 2in. moving coil meter scale, calibrated in A.C./D.C. volts, ohms and milliamperes. Voltage range A.C./D.C. 0-50, 0-100, 0-250, 0-500. Milliamperes 0-10, 0-100 Ohms ranges 0-10,000, 0-100,000, 10/6. P. & P. 2/6. Wiring diagram 1/- free with parts.
- 4. SIGNAL GENERATORS:** Cash £7.5.0, or 30/- deposit and 6 monthly payments of 21/6. P. & P. 6/6. Coverage 100 kc/s to 100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Case 10 x 6½ x 5½ in. Three miniature valves and Metal Rectifier. A.C. mains 200/250v. Internal modulation of 400 c.p.s. to a depth of 30 per cent. Modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch. variable A.F. output. Magic eye as output indicator. Accuracy 2 per cent.
- 5. SIGNAL GENERATORS.** Cash £5.5.0. P. & P. 6/6. Coverage 120 kc/s to 54 Mc/s. Case 10 x 6½ x 4½ in. Size of scale 6½ x 3½ in. 2 valves and rectifier. A.C. mains 230-250v. Internal modulation of 400 c.p.s. to a depth of 30 per cent. modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch variable A.F. output and moving coil output meter. Accuracy ± 2 per cent.
- 6. STAAR 45, 9 v. BATTERY RECORD PLAYER** complete with pick-up and deck. A completely portable player. Head protected by plastic dome with a brush which cleans the stylus as it rises into playing position. 45 r.p.m. Auto on-off switch governed motor, attractive two-tone grey finish, £2.9.6. P. & P. 2/6.
- 7. 50 MICRO-AMP METER** movement by world famous manufacturer. Size 3 x 2½ in. 25/- plus 1/-, P. & P.
- 8. ALTITUDE METER,** 180 degree scale. 3in. diameter. Would make ideal car rev. counter. £1 plus 2/6 postage and packing.
- 9. CHANNEL TUNER I.F. 16-15 Mc/s.** Continuously tunable from 174-216 Mc/s. Valves required—PC980 and PC984 (in series). Cover RBC and ITA ranges. Also Police, Fire and Taxis, etc. Brand new by famous maker, 10/-. P. & P. 3/6.
- 10. B.S.R. MONARCH UA14 WITH FUL-FI HEAD.** 4-speed, plays 10 records, 12in., 10in. or 7in. at 16, 33, 45 or 78 r.p.m. Internizes 7in., 10in. and 12in. records of the same speed. Has manual play positions: colour brown. Dimensions: 12½ x 10½ in. Space required above baseboard 4½ in., below baseboard 2½ in. Fitted with Full-Fi turnover crystal head, £5.19.6. P. & P. 6/6.
- 11. POCKET MULTI-METER.** Size 3½ x 2½ x 1½ in. Meter size 2½ x 1½ in. Sensitivity 1,000 O.P.V. on both A.C. and D.C. A.C. and D.C. volt. 0-15, 0-150, 0-1,000. D.C. current 0-150 mA. Resistance 0-100K Ω. Complete with test prods, battery and full instructions, 35/-. Plus 1/- P. & P.
- 12. 8-watt PUSH-PULL 4 VALVE AMPLIFIER** plus METAL RECTIFIER. A.C. mains 200-250 v. Size 10½ x 6½ x 2½ in. 4 valves. For use with all makes and types of pick-up and mike. Negative feed back. Two input, mike and gram, and controls for same. Separate controls for Bass and Treble lift. Response flat from 40 cycles to 15 kc/s. Noise level 40 dB down all hum. Output transformer tapped for 3 and 15 ohms speech coils. For use with Std. or L.P. records, musical instruments such as guitars etc. Suitable for small halls, £3.19.6. P. & P. 6/6. Crystal mike to suit 15/-, P. & P. 2/6. 8in. P.M. Speaker to suit, 12/6. P. & P. 3/6.
- 13. INDOOR AERIAL** for ITV/BBC/FM. Complete with standard co-axial plug. Heavy chrome extending dipoles—7ft. fully extended. Plug straight into T.V. or V.H.F. Tuner. Fully directional, 10/6. P. & P. 1/6.
- 14. NO MORE FLAT BATTERIES.** Charge your own battery overnight with this wonderful little charger. Output 6 and 12 volts, 2 amps. Input 200-250 v. A.C. mains. Mains fuse incorporated. Attractive silver hammer finished case. 6 x 3 x 3ins. Complete with leads and battery clips only 21/-. P. & P. 3/6.

**21b HIGH STREET  
ACTON, LONDON, W.3.**

ALL ENQUIRIES S.A.E.  
GOODS NOT DESPATCHED OUTSIDE U.K.  
Shop hours 9 a.m.—6 p.m. Early closing Wednesday

# INCREASE YOUR KNOWLEDGE



## CHOOSE THE RIGHT COURSE FROM:

RADIO AND TELEVISION ENGINEERING, INDUSTRIAL TELEVISION, RADIO AND TELEVISION SERVICING, ELECTRONICS, COMPUTERS AND PROGRAMMING, ELECTRONIC TECHNICIANS, SERVOMECHANISMS, TELEMETRY, COLOUR TV, INSTRUMENTATION, AND PRINCIPLES OF AUTOMATION.

## ALSO EXAMINATION COURSES FOR:

A.M.Brit.I.R.E.; City and Guilds Telecom. Technicians, C. & G. Radio and T.V. Servicing (R.T.E.B.), and P.M.G.'s Certificates. C. & G. Radio Amateurs' Certificates.

## LEARN AS YOU BUILD

Practical Radio Courses: Gain a sound knowledge of Radio as you build YOUR OWN 5-valve superhet Receiver, and Portable Transistor, Signal Generator and High-quality Multitester. At the end of the course you have invaluable practical equipment and a fund of personal knowledge and skill. ICS Practical Radio Course opens a new world to the keen Radio amateur.

**YOUR  
CAREER  
IN**

**ELECTRONIC ENGINEERING  
RADIO AND TELEVISION  
ENGINEERING  
ELECTRICAL ENGINEERING**

INTERNATIONAL CORRESPONDENCE SCHOOLS - LONDON

# RADIO TELEVISION ELECTRONIC ENGINEERING

MEMBER OF THE ASSOCIATION  
OF BRITISH CORRESPONDENCE COLLEGES

## THERE IS AN **ICS** COURSE FOR YOU

Whether you need a basic grounding, tuition to complete your technical qualifications, or further specialised knowledge, ICS can help you with a course individually adapted to your requirements.

There is a place for you among the fully-trained men. They are the highly paid men—the men of the future. If you want to get to the top, or to succeed in your own business, put your technical training in our experienced hands.

ICS Courses are written in clear, simple and direct language, fully illustrated and specially edited to facilitate individual home study. You will learn in the comfort of your own home—at your own speed. The unique ICS teaching method embodies the teacher in the text; it combines expert practical experience with clearly explained theoretical training. Let ICS help you to develop your ambitions and ensure a successful future. Invest in your own capabilities.

## FILL IN AND POST THIS COUPON TODAY

You will receive the FREE ICS Prospectus listing the examinations and ICS technical course in radio, television and electronics. PLUS details of over 150 specialised subjects.

PLEASE SEND FREE BOOK ON \_\_\_\_\_

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

OCCUPATION \_\_\_\_\_ AGE \_\_\_\_\_

INTERNATIONAL CORRESPONDENCE SCHOOLS  
Dept. 170, INTERTEX HOUSE, PARKGATE RD, London SW11



# GO TRANSISTOR WITH SINCLAIR

## BRITAIN'S LEADING TRANSISTOR SPECIALISTS

### 3 VITAL BOOKS FOR THE TRANSISTOR USER

Here are three books to keep you in step with the latest development in transistor design and practice. Each is crammed with invaluable information, tested circuits and layout diagrams. All are expertly prepared and based on Sinclair Transistors. These three books cover an exciting range of transistor applications. You can save 2/6 by buying all three together for



**15/-**  
POST FREE

#### GENERAL

22 Tested Circuits Using Micro Alloy Transistors. *Post free* **5/6**

#### SHORT WAVES

Tested Short Wave Receivers Using MATs. *Post free* **5/6**

#### S.W. & COMMUNICATIONS

Tested Superhet Circuits for Shortwave and Communication Receivers, using MATs. *Post free* **6/6**

### THE WONDERFUL SINCLAIR RANGE OF TRANSISTORS

#### M.A.T.'s

##### (MICRO-ALLOY TRANSISTORS)

Give extremely high power gains at all levels of collector current and voltages and from A.F. to 100 Mc/s. Greatly improve performance of any circuit.

MAT 100 High gain low level. .... 7/9  
MAT 101 Extra high gain, low level. .... 8/6  
MAT 120 High gain, medium and high level. .... 7/9  
MAT 121 Extra high gain, medium and high level. .... 8/6

#### ADT.140 FOR V.H.F. and U.H.F.

Only 1/8 in. high x 1/8 in. dia. Made by the unique alloy-diffused process, and specially suitable for F.M., T.V., V.H.F. and U.H.F. frequencies. Has typical alpha cut-off of 400 Mc/s with power gains of 15dB at 100 Mc/s and 9dB at 200 Mc/s. **15/-**

## TWO OUTSTANDING AF AMPLIFIERS

### SINCLAIR TR5

#### COMBINED PRE-AMP AND HALF-WATT POWER AMPLIFIER



#### READY BUILT AND TESTED

"I have tried the TR.5 amplifier with a gram P.U. feed and find it a remarkable 'mighty atom' with astonishing volume and quality."  
-D.A.B., Welwyn Garden City.

Will produce a perfectly clean half watt of audio power even from very low output sources such as low-impedance tape heads, pick-ups and microphones. Ready built with instructions and unconditionally guaranteed.  
CIRCUIT—5 matched transistors and temperature compensating diode in a transformerless complementary-symmetry configuration.  
POWER OUTPUT—500 mW undistorted into 15 ohms.  
SENSITIVITY—0.5 mV.  
POWER GAIN—80 dB (100 million times).  
FREQUENCY RESPONSE—50 c/s to 20 kc/s  $\pm$  3dB.  
SIZE—2 1/2 x 1 1/2 x 1 in.  
POWER REQUIREMENTS—9V. battery or power supply. **59/6**

### SINCLAIR MICRO AMPLIFIER



#### 40dB GAIN at 1Mc-s OUTPERFORMS AMPLIFIERS 20 TIMES LARGER

This fantastically powerful amplifier is smaller than a 3d. piece. With a frequency response from 30 to 50,000 c/s  $\pm$  1 dB, and power gain of 60dB (1,000,000 times) it can be used as a sub-miniature hi-fi amplifier with an output suitable for any earpiece or even a loudspeaker.

With MAT Transistors, brand new micro-miniature quality components and micro-printed circuit, inc. instructions for building and many uses.


**28/6**

## THE SMALLEST AND MOST EFFICIENT YET SINCLAIR MICRO-INJECTOR
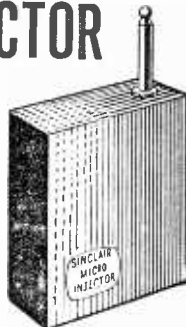
### FOR FAULT FINDING AND SERVICING

Using two MICRO-ALLOY TRANSISTORS, the Sinclair Micro-Injector is a precision sub-miniature instrument which generates and injects a test signal into any part of a receiver or amplifier at any frequency from 1 Kc/s to 30 Mc/s. By this means, the position of any fault can be rapidly found.

This Micro-Injector is powered by a standard Gd. battery which will last for about 6 months. Size is 1 1/4" x 1 1/2" x 1" excluding the 3/16" probe. Assembly is extremely simple and will take even a beginner only half an hour. With illustrated building and operating instructions.



Total cost including all parts, MAT Transistors, printed circuit board, plated probe, and case in royal blue with gold trim. **27/6**

ALL EQUIPMENT  
UNCONDITIONALLY GUARANTEED

READY BUILT AND TESTED **32/6**

**SINCLAIR radionics LTD. 69 HISTON RD. CAMBRIDGE**

# SINCLAIR 'SLIMLINE'

THE SET YOU  
WILL NEVER WANT  
TO BE WITHOUT

BUILD ONE  
FOR YOURSELF

*Give one for Xmas!*


THE MOST FANTASTIC TRANSISTOR PERFORMANCE YET  
—GIVES YOU EUROPE IN THE PALM OF YOUR HAND

## UNIQUE CIRCUITRY!

The secret of the Slimline's performance is in its unique circuit. This circuit, specially developed by Sinclair Radionics Ltd., makes full use of our incredible Micro-Alloy Transistors (MAT's), and because of its ingenious design the quality of reproduction is outstandingly good with selectivity and sensitivity of an amazingly high order.
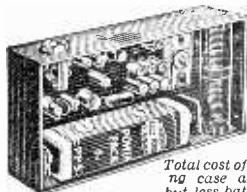
## BUILD IT IN A COUPLE OF HOURS

The parts necessary to build this wonderful set comprise printed circuit board, sub-miniature components including MAT Transistors, case in royal blue and gold, featherweight high quality ear-piece etc. Full instructions with every order.



$2\frac{1}{8}'' \times 1\frac{1}{8}'' \times \frac{3}{4}''$

Total cost of parts including case and earpiece, but less battery

**49/6**

IDEAL AS A RADIO JACK

No matter what your experience with radio, the Sinclair Slimline is unique in its ability to give you reception in a way that no other set can. Its power and selectivity are truly phenomenal when you remember that this completely self-contained receiver is smaller than a packet of twenty cigarettes. It can be your companion everywhere, even letting you listen in car or train. Building is fascinatingly easy even if you have never built a set before in your life. If you are going to build and give one for Christmas, you had better order two—for once you have experienced making and listening to the Slimline, you won't want to be without one either.

## "BEATS MY SEVEN-TRANSISTOR SET"

Thousands of Slimline Sets have been built and countless users have written expressing their enthusiasm. They have been used hundreds of miles out to sea, in the air, and in remote parts of Europe. Used as we are to receiving such letters even we were surprised by the following:—

"A friend of mine bought a Slimline and has used it from here to Aden with great success, equalling the performance and at times beating my seven transistor set.

I am going on draft in another week and I would like very much to take a Slimline with me so could you rush the order through as soon as possible.

Yours sincerely,

K.H.R., H.M.S. Dryad, Southwick."

- TRUE HIGH FIDELITY PERFORMANCE
- INCREDIBLE VOLUME AND SENSITIVITY
- TUNES OVER THE ENTIRE MEDIUM WAVEBAND
- FULL SERVICE FACILITIES ALWAYS AVAILABLE

**POST  
TO-DAY**

To SINCLAIR RADIONICS LTD., 69 HISTON RD., CAMBRIDGE  
PLEASE RUSH.....

FOR WHICH I ENCLOSE £.....s.....

NAME.....

ADDRESS .....

Block letters please .....

PW.1



# ARMSTRONG AF208AM/FM RADIOGRAM CHASSIS



**20 gns.**  
(carriage free)

- FULL VHF BAND (87-108 Mc/s). MEDIUM BAND 187-570 m.
- 5 WATTS OUTPUT.
- 15 dB NEGATIVE FEEDBACK. 7 VALVES.
- SEPARATE WIDE-RANGE BASS AND TREBLE CONTROLS.
- 2 COMPENSATED PICK-UP INPUTS.
- FREQUENCY RESPONSE 50-22,000 c.p.s. ±2 db.
- TAPE RECORD AND PLAYBACK FACILITIES.
- CONTINENTAL RECEPTION OF GOOD PROGRAMME VALUE.

FOR 3, 7½ and 15 ohm SPEAKERS.

Write for free literature.

## New Boxed VALVES 30-day Guarantee

024	6/-	6K7G	5/-	EB91	4/-	PCL82	10/-
185	6/-	6K9G	5/-	EB41	8/-	PCL84	10/-
185	6/-	6L6G	8/-	EB81	8/-	PL81	10/-
174	6/-	6N7M	6/-	EBF80	9/-	PL83	8/-
2X3	2/-	6Q7G	6/-	ECH42	9/-	PY3	15/-
384	7/-	6N7M	5/-	ECH81	9/-	PY80	7/-
3V4	7/-	6V6G	5/-	ECL80	9/-	PY81	8/-
3Q4	7/-	6X4	5/-	ECL82	10/-	PY83	7/-
5U4	6/-	6X5	6/-	EF85	8/-	PQ22	8/-
6V3	6/-	6Z4T	6/-	EF89	8/-	SP41	3/-
6Z4	9/-	12A07	6/-	EL32	6/-	SP61	3/-
6AC7	4/-	12AX7	7/-	EL94	7/-	U22	7/-
6AM6	6/-	12BH7	7/-	LY61	9/-	UBC41	8/-
6AT6	6/-	12K7	6/-	RY36	7/-	UBC81	9/-
6BA6	7/-	12K8	14/-	U240	7/-	UBF89	6/-
6BE6	6/-	12Q7	5/-	KZ80	7/-	UCL82	10/-
6BW6	7/-	25Y6G	9/-	EZ81	7/-	UCL83	12/-
9C4	6/-	35L6	8/-	HAB80101	10/-	UCL83	12/-
6BD6	6/-	35Z4	5/-	LYR54	5/-	UP8	8/-
606	4/-	954	2/-	KT380	8/-	UL41	8/-
6H6	3/-	DAP96	8/-	KT76	8/-	UY41	7/-
6J5	6/-	DF96	8/-	MU14	7/-	UY85	7/-
6J6	6/-	DK96	8/-	PCU84	8/-	UY9	7/-
6J7	6/-	DL66	8/-	PCF80	8/-	VX190	7/-
6K6	5/-	EACB80	8/-	PCF82	8/-	W31	6/-

## NEW ELECTROLYTICS FAMOUS MAKES

NEW ELECTROLYTICS				FAMOUS MAKES	
TUBULAR	TUBULAR	CAN TYPES			
1/350V	2/-	50/350V	5/8	8/600V	9/-
2/350V	2/3	100/25V	5/-	18/450V	5/-
4/450V	2/3	250/25V	5/-	18/600V	12/-
8/450V	2/3	500/12V	5/-	18+16/500V	7/8
18/450V	3/-	1,000/12V	5/-	50/450V	6/8
32/450V	3/9	5,000/8V	5/-	32+32/350V	6/8
25/25V	1/9	8+8/450V	5/8	32+32/450V	6/-
25/50V	2/-	8+8/450V	5/8	32+32+32/350V/7/8	
50/25V	2/-	16+16/450V	4/8	50+50/350V	7/-
50/50V	2/-	32+32/350V	4/8	64+120/350V	11/8
				100+200/275V	12/8

**TELESCOPIC CHROME AERIALS.** 11m. extending to 43m. 8/6 ea. 6in. to 32in. 7/8 ea.

**TRIPLEXERS** Bands I, II, III, 12/6. **COAX PLUG.** 1/-.

**LEAD SOCKET.** 2/1-. **PANEL SOCKETS.** 1/-.

**OUTLET BOXES** (surface or flush). 4/- ea.

**BALANCED TWIN FEEDER** yd. 6d. 80 or 300 ohms.

**DITTO SCREENED** per yd. 1/6. 80 ohms only.

**Wire-wound Ext. Speaker Control.** 10Ω 3/1-, 25Ω 6/3.

**WIRE-WOUND POTS.** 3 WATT. Pre-set Min. TYP. All values to 10 ohms to 25 K. 3/- ea. 30 K. 50 K. 4/- (Carbon 30 K. to 2 meg. 8/-).

**WIRE-WOUND 4 WATTS POTS.** Long. speaker. Value. 50 ohms to 50 K. 6/8; 100 K. 7/8.

**PHILIPS TRIMMERS.** 0-10 pF. 3-30 pF. 1/-.

**TRIMMERS.** Ceramic. 30, 50, 70 pF. 9d.; 100 pF. 120 pF. 1/3; 250 pF. 1/6; 500 pF. 750 pF. 1/9. TYP. etc. **TRIMMER.** 1000 pF. with knob. 2/1-.

**RESISTORS.** Preferred values. 10 ohms to 10 meg. 1 w. 4d.; 1 w. 4d.; 1 w. 8d.; 1 w. 8d.; 2 w. 1/-.

**High Stability.** 1/2, 1/3, 2/3, 2/3. Preferred values 10Ω to 10 meg. Ditto 5% 10Ω to 22 meg. 9d.

**BRIMSTONS.** CZ1, 3/8; CZ2, 2/8; CZ3, 1/8.

5 watt	WIRE-WOUND RESISTORS	1/3
10 watt	10 ohms—10,000 ohms	2/-
15 watt		3/-
12.5K to 47K 10 w.		3/-

**Volume Controls**

Linear of Log Tracks

Long spindles. Midget

5 K ohms to 2 Meg.

L.S. 8/-; D.P. 4/6;

Stereo L/S 10/6; D.P. 14/6

**80 ohm COAX**

Semi-air spaced 1in.

Stranded core 6d. yd.

40 yds. 17/6

60 yds. 25/-

Frings Quality 1/- yd.

Air spaced

Ideal 600 lines.

## MAINS TRANSFORMERS 200/250 v. A.C.

Voltage 2/- each transformer.

STANDARD 250-0-250, 80 m.A., 6.3 v. 3.5 a. tapped 4 v. 2 a. Rectifier, 6.3 v. 1 a. 5 v. 2 a. or 4 v. 2 a. 22/6, ditto, 350-0-350. 29/6

MINIATURE 200 v. 20 m.A., 6.3 v. 1 a. 10/6

MIDGET, 220 v. 45 m.A., 6.3 v. 2 a. 15/6

SMALL, 250-0-250, 40 m.A., 6.3 v. 2 a. 17/6

STD. 250-0-250, 65 m.A., 6.3 v. 3 a. 17/6

HEATER TRANS. 6.3 v. 1 amp. 7/6

Ditto, tapped 1.4, 2, 3, 4, 5, 6.3 v. 8/6

Ditto, sec. 6.3 v. 4 amp. 10/6

GENERAL PURPOSE LOW VOLTAGE, 2 amp 2, 4, 5, 8, 9, 10, 15, 18, 24, 30 v. 22/6

AUTO TRANSFORMER, 150 v. 22/6

0, 115, 200, 230, 250 v., 500 w. 82/6

MULLARD "S10" Mains Transformer 88/6

FARMER MAINS TRANSFORMER. Made for special contract, the ratings can safely be doubled. Guaranteed 2 years. Primary 0-110-210-250 v. H.T. 300-0-300 v. 60 m.A., L.T. 6.3 v. 1.8 amp. Size 4 x 3 1/4 x 3 in. 17/6

## INTERVAL TRANSFORMERS. 3:1 or 5:1 8/-

O.P. TRANSFORMERS. Heavy Duty 50 m.A. 4/6. Multitap, 7/6. Multitap heavy duty push-pull 10 w., 15/6. Miniature, 384, etc., 5/6.

10 w. O.P. matching transformer, 3, 7, 15Ω, 12/6.

2.2 CHOKES 15/10H, 50/65 m.A., 5/-; 10H, 85 m.A., 10/6; 10 H, 150 m.A., 14/6.

TINNED COPPER WIRE 16 to 22 awg., 4lb., 3/-.

ENAMEL COPPER WIRE 16-22, 2/8; 24-30, 3/6; 32-40, 4/6; D.C.C. 28, 34, 36 swg. 2oz. 3/6.

## I.P. TRANSFORMERS 7/6 pair

485 K/Ω Slug Tuning Miniature Can, 2 x 1 x 1 1/2 in. High K and good bandwidth. Data sheets. Standard size Weyrad, 10/6 pair.

## FULL WAVE BRIDGE SELENIUM RECTIFIER:

2, 6 or 12 v. 11 amp. 8/8; 2 a., 11/3; 3 a., 17/6.

CHARGER TRANSFORMERS. Tapped input 200/250 v. for charging at 2, 6 or 12 v. 1 1/2 amps., 15/6; 2 amps., 17/6; 4 amps., 22/6. Circuit included.

4 AMP. CAR. BATTERY CHARGER with ammeter Leads, Fuse case, etc., for 6 v. or 12 v., 89/6.

AMMETER to 5 amp., 9/6.

## BOOKS list S.A.E.

Boys' Book of Crystal Sets. 2/6

"V.W." Radio Valve Data. 8/-

High Fidelity Speaker Enclosure 5/-

Valve and TV Tube Equivalents 9/6

TV Fault Finding 5/-

Mullard Amplifier Manual. 8/6

Radio Valve Guide, Books 1, 2, 3. 15/-

4 or 5

Transistor Superhet Receivers 7/6

Practical Radio Inside Out 3/6

Master Colour Code Chart 1/6

Transistor Colour Coding Models 7/6

Principles of Colour TV 15/-

International Radio Stations 2/6

## 4 TRANSISTOR PUSH-PULL AUDIO

Size 3 x 1 1/2 x 1 1/2 in. AMPLIFIER

A ready built miniature push-pull amplifier with Driver and output transformers. 4 transistors. Ideal for use with record players, intercoms, BABY ALARMS, etc. Complete with (full 4/6) instructions and circuit.

Price. 47/6

9v. Batt. 2/3 2 1/2 in. Speaker 15/-.

## 1963 RADIOGRAM CHASSIS



**THREE WAVEBANDS**

S.W. 16 m.—50 m. LATEST MULLARD

M.W. 200 m.—550 m. ECH81, EF89, EBC81, L.W. 800 m.—2,000 m. EL84, E280

A.C. 200/250 v. 4-wire 2-wire Short-Medium, Long/Gram. Ferrite Aerial A.V.C. and Negative feedback, 3 ohm output, 5 watts. Glass dial, horizontal wording, size 13in. x 4in. Aligned and calibrated. Isolated Chassis, size 13 1/2 in. x 9 in. high x 5 1/2 in. deep.

**£8.19.6** Carr. & Ins. 4/6.

## BAKER SELHORST LOUDSPEAKERS

12in. Baker 15w. Stalwart 3 or 15 ohms, 45-13,000 c.p.s. 90/-

12in. Stereo, Foam Suspension, 12w., 36-18,000 c.p.s. 28/17.6

12in. Standard H.D. 20w. 40-14,500 c.p.s. 28.0

12in. De Luxe 15w., 25-17,000 c.p.s. 28/6

12in. Bass 25w. 20-18,000 c.p.s. 312.12.0

15in. Auditorium, 35w., Bass, 20 c.p.s. to 12 kc/s. Ideal Bass Guitar. 818.

Portable enclosures for 12in. "Stalwart", 23 each.

## LOUDSPEAKERS P.M. 3 OHM. 3 1/2, 3, 4, 5in;

7 x 4in., 15/6; 6 1/2 in., 10/6; 8in. Pleceay, 17/6; 10 x 6in., 22/6; 10in. Kola, 30/-; 12in. K.A., 30/-; 12 1/2 x 6in. Double Cone, E.M.I., 35/-.

STENTORIAN HP1012, 10in. 8 to 15 ohms, 10w. 87/6; 8in. HP812, 72/-; Tweeter T369, 30/-; Cross-over EX3000, 30/-.

## EXTENSION SPEAKER CABINETS. 5in. 15/6,

6 1/2 in., 18/6, 8in. 19/6, 10in. 29/6.

## C.R.T. BOOSTER TRANSFORMERS

for heater cathode short circuit, or tubes with failing emission. Full instructions supplied, mains input. Type A optional 25% and 50% boost 2v. or 4v. or 6v. or 10v. 12.6v. State voltage required. PRICE 10/6.

## TWIN GANG TUNING CONDENSERS. 365 pF,

miniature 1in. x 1 1/4 in. x 1 1/4 in., 10/-; 300 pF standard 6 1/2 in. trimmers, 9/-; midset, 7/6; with trimmers, 9/-; 500 pF slow motion tuning potentiometer or midset, 8/-.

Transistor gang 208 + 176 pF with trimmers, 10/6.

SMALL 3 gang 500 pF, 17/-; SINGLE 365 pF, 7/6.

SINGLE 10 pF, 25 pF, 50 pF, 75 pF, 100 pF, 160 pF, 360 pF. Solid dielectric 100, 200, 500 pF, 3/6.

CONDENSERS. New stock. 0.001 mid. 7 kv. T.C.C., 5/6; Ditto, 20 kv., 9/6; 0.1 mid., 7 kv. 9/6. Tubular 500 v. 0.001 to 0.05 mid., 9d.; 0.1, 1/-; 0.25, 1/6; 0.5/350 v., 1/8; 0.1/350 v., 9d.; 0.1/2,000 v.; 0.1/1,000 v., 1/8; 0.1 mid., 2,000 volts, 3/6.

CERAMIC CONDS. 500 v. 0.3 pF to 0.01 mid., 9p.

SILVER MICA CONDENSERS, 10% 5 pF to 500 pF. 9d.; 600 pF to 3,000 pF, 1/-.

(Close tolerance (+1 pF) 2.2 pF to 47 pF, 1/-; ditto 1/2 to 50pF, to 816 pF, 1/-; 1,000 pF to 5,000 pF, 1/8.

## 465 kc/s SIGNAL GENERATOR

Price 15/-, Uses B.F.O. Unit, 2A 30038 ready made with valve 155. P.O.C.K. 14 SIZE 2 1/2 x 4 1/2 in. One resistor to change, full instructions supplied. Battery 3/6 extra. 69V11V. Details S.A.E.

## WAVECHANGE SWITCHES

6 p. 4-way 2 water long spindle 8/6

2 p. 2-way or 2 p. 6-way long spindle 8/6

4 p. 2-way or 4 p. 3-way long spindle 3/6

3 p. 4-way or 1 p. 12-way long spindle 8/6

Wavechange "MAKITS" Valves available: 1 p. 12 way, 2 p. 6 way, 3 p. 4 way, 4 p. 3 way, 6 p. 2 way, 1 water switch, 8/6.

2 water switch, 12/6; 1 water switch, 16/-; additional wafers up to 12. 36 each extra; Toggle Switches, s.p., 2/-; d.p., 3/-; d.p.d.t., 4/-; Min. Slide d.p.d.t., 3/6.

## CRYSTAL MIKE INSERTS, 6/8

High output. Size 1 1/4 in. dia. x 1 in. ACOS MIC. 14, Insert 1 1/4 in. dia. x 1 in. 8/6

ACOS 39-1 DE LUXE STICK MIKE 35/-

TSL QUALITY STICK MIKE 25/-

## Valveholders. EA50, 6D, B12A, CRT. 1/3,

Enkl. and Amer. 4, 5, and 7 pin. 1/-.

ALCO BDC Mazda and Int. oct. 8d.; B7G, B8A, B9A, 9d.; ETC with can. 1/8. B9A with can. 1/8. Ceramic EF50, B7C, B7A, Int. oct. 1/-; B7G, B8A cans. 1/- each. Valve plugs B7G, B9A, 2/8.

## HIGH GAIN TV PRE-AMPLIFIERS

BAND I B.B.C.

Tunable channels 1 to 5. Gain 18dB. ECC84 valve. Kit price 29/6 or 49/6 with power pack. Details 6/1, (PC84 valves if preferred.) Cols only 9/6.

BAND III I.T.A.—Same prices.

Tunable channels 8 to 13. Gain 17dB. Circuit and cols only 9/6.

**A HAPPY CHRISTMAS TO ALL READERS OF**


**RADIO COMPONENT**

Our written guarantee with every purchase.

New COMPONENT LIST 1/-.

Bus 133 or 68 pass door S.R. Station Selhurst
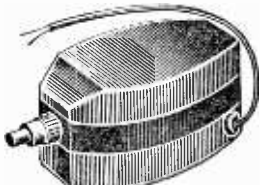
# THE "INSTANT" BULK TAPE ERASER AND RECORDING HEAD DEMAGNETIZER



200/250 v. A.C. **35/-** Leaflet S.A.E.

## PLASTIC RECORDING TAPE

Double Play	7in. reel, 2,400ft.	42/-	Spare Plastic Reels
	5in. reel, 1,200ft.	25/-	
Long Play	7in. reel, 1,800ft.	22/8	3in. 1/6
	5in. reel, 900ft.	17/6	4in. 2/-
	5in. reel, 900ft.	15/6	5in. 2/-
Standard	7in. reel, 1,200ft.	17/8	5in. 2/-
	5in. reel, 600ft.	11/6	7in. 2/6

"EASISPLICE" Tape Splicer 5/-

CRYSTAL SET BOOKLET, 1/-.  
CRYSTAL DIODE G.E.C., 2/-, GEX34, 4/-, OA81, 3/-.  
HIGH RESISTANCE PHONES, 4,000 ohms, 15/- per pair.  
MOVING COIL PHONES, 100 ohms, 10/-.  
SWITCH CLEANER, Fluid squirt sprout, 4/6 tin.

## "6+1" TRANSISTOR RADIO MEDIUM AND LONG WAVE KIT

First class components to make a 6 transistor 2 waveband superhet chassis. Ideal for portable or table radio. All parts including BVA transistors, ferrite aerial, with car aerial coil, printed circuit, 8in. x 2in., but EXCLUDING Speaker and cabinet. Speakers, 35 ohms, 7 x 4in. 21/- 5in., 17/6, 3in., 15/6. **£45.0**

BULGIN PLUGS AND SOCKETS. Non-reversible P74, 3pin, 4/3; P73, 3pin, 4/3; P194, 6pin, 6/6. "DOMINA" plugs; 8/6; sockets, 2/6.

JACKS. English open circuit, 2/6. Closed circuit, 4/3. Grindly type, 3pin, 1/3. Grindly lead jack, 3/6. JACK PLUGS. English, 3/-; Screwed, 4/-; Grindly, 3pin, 3/6; Phone Plugs, 1/-; Sockets, 8d.

ALADIN FORMERS and cores, 4in., 8d.; 1in., 10d. 0.3in. Formers 9937 or 8 cans TVI or 2, 2in. sq. x 2in., or 4in. sq. x 1 1/2in., 2/- with cores.

SLOW MOTION DRIVES. 8.1, 4/3.

SOLOIN IRON, 25W, 200V or 230V, 24/-.

ANTEX SUB-MIN. IRON, 15W, 200 or 240V, 29/6.

BENCO Start for above, 12/6. Spares in Stock.

1/16in. Paxolin Panels, 10 x 6in., 2/-.

Miniature Contact Cooled Rectifiers, 250V 30mA, 7/6; 250V 60mA, 8/6; 250V 85mA, 9/6; Selenium Rect., 300V 85mA, 5/-.

TV etc., Silicon Sub. Min. Rectifier, 250V 450mA, 10/-; K3/25, 60V, 5mA, 5/-.

R.M.3, 14A100, 14A11610/- each, FC31, 20/-.

Coils Wearite "P" Type, 3/- each.

Osmor Midgel "Q" type, adj. dust core, from 4/- each. All ranges. List S.A.E.

Teletron D.V.R. L. and Med. T.R.F. with reaction, 4/-.

Med. wave D.R., 3/6.

Ferrite Aerials, M., 8/8; M. and L., 12/6.

Osmor Ferrite Rod Aerials, L. and M. for transistor circuits, 10/- each.

Ferrite Rods, 3 x 1in., 6 x 1in., 8 x 1 1/2in., 3/-.

H.P. Chokes, 2/6; Osmer 0C1, 6/9.

T.R.F. Coils, A.H.F., 7/- pair; HAX, 3/-.

Repenco DRR2, 4/6; DRX1, 2/6.

Radio Screwdriver, 3in., 6d. Test Prods, 2/8.

Nosoid Trimming Tool, 1/8.

Neon Mains Tester Screwdriver, 5/-.

Multicore Solder, 4d. yd., Dispenser, 2/6.

Aluminium Chassis, 18 s.w.g. Plain, undrilled, 4 sides, riveted corners, lattice fixing holes, 2 1/2in. sides, 7 x 4in., 4/6; 9 x 7in., 5/9; 11 x 7in., 6/9; 13 x 9in., 8/6; 14 x 11in., 10/6; 15 x 14in., 12/6.

Aluminium Panels, 18 s.w.g., 12 x 12in., 4/6; 14 x 9in., 4/-; 12 x 8in., 3/-; 10 x 7in., 2/8; 8 x 6in., 2/-.

JASON FM TUNER COIL SET 29/-.  
H.F. coil, aerial coil, oscillator coil, two i.i. transformers 10.7 Mc/s. detector transformer, heater choke. Circuit book using four 6AM6, 2/6.  
Complete Jason FMT Kit. Jason chassis with calibrated dial, components and 4 valves, £65.0.  
Model FMT2 with new shelf cabinet, 5 valves, components and powerpack, £10.

MAINS DROPPERS. Midget adjustable sliders 0.3A, 1,000 ohms, 5/-; 0.2A, 1,200 ohms, 5/-; 0.15A, 1,500 ohms, 5/-; 0.1A, 2,000 ohms, 5/-.

MIKE TRANSFORMERS, 50-1, 3/9.  
P.V.C. Covered Wire, single or stranded, 2d. yd. Slewing, 1 or 2 mm., 2d.; 3 mm., 3d.; 6 mm., 5d. yd. SPEAKER-FRET, Gold, Maroon or Green Cloth, 17 x 25in., 5/-; 25 x 35in., 10/-; Tygan, various colours 52in. wide from 10/- ft.; 26in. wide from 5/- ft. Samples S.A.E. Expanded Metal, Gold, 12 x 12in., 6/- Panel mounting fuse holders, 2/-; Fuses 1 1/2in. 60mA 5A, 6d. Insulated side cutters, 8/6. Bib Stripper, 3/6.

## RADIO AND TELEVISION SPARES

All leading makes, volume controls, etc., home output transformers, etc., B. V. A. valves (current and obsolete types). Send S.A.E. for quotation.

## WEYRAD

COILS AND TRANSFORMERS FOR 2-WAVE TRANSISTOR SUPERHETS WITH PRINTED CIRCUIT AND FERRITE ROD AERIAL.

Long and Medium Wave Aerial—RA2W On 6in. rod, 208pF tuning, with car aerial coupling coil, 12/6.

Osc. Coil P50/1AC, 176 pF tuning, 5/4.

1st and 2nd I.F. Trans.—P50/2CC, 470k/s 1/16in. dia. by 1in., 5/7 each.

3rd I.F. Trans.—P50/3CC, 6/- each.

Spare Cores 6/- each.

Driver Transformer—LFT4, 9/6.

Wavechange Slide Switch d.p.d.t., 3/6.

Printed Circuit—PCAT, Size 2 1/2 x 8in., 9/6.

Ready drilled, and printed, 9/6.

Volume Control, 5K-DP, 4/6.

35 ohm Speakers, 3 1/2in., 15/6; 5in., 17/6; 7 x 4in., 21/-.

Tuning Gangs with trimmers, 10/6.

6 Mullard Transistors and diode, 42/6.

Constructor's Booklet, 2/-.

3 ohm O.P. Trans. O.P.T.1, 10/6.

## NEW MULLARD TRANSISTORS

OC71 6/-, OC72 7/6, OC81D 7/6, OC81 7/6.

OC43 9/6, OC45 8/6, OC171 10/6, AF117 9/6.


Sub Miniature Condensers, 0.1 mfd, 30v., 1/3, 1, 2, 4, 5, 8, 16, 25, 30, 50, 100 mfd, 15 volt 2/6 each. Transistor Holders 1/3.

R.R.C. Pocket 2 Transistor, Plus Diode M.W. and L.W. Radio Kit, 22/6.

Miniature earpiece, 7/6. Batt. 2/3.

Circuit details, etc., S.A.E.
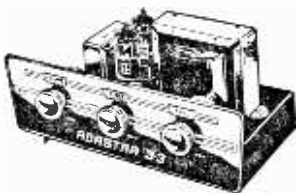
## ADASTRA 3-3 AMPLIFIER 3 WATTS HIGH FIDELITY AT LOW COST



READY BUILT, WIRED AND TESTED A.C. only, 200-250 v. Valves ECL86 and EZ80, 3 ohms quality output. Mullard tone circuits. Controls: boost, treble and volume. Separate engraved front panel with de luxe finish. Quality mains transformer. Stove enamelled chassis size 6in. x 3in. x 3in. Bargain Price £4.19.6 Details S.A.E.

"Performs agreeably well" (The Gramophone)

## BUILD YOUR OWN RECORD PLAYER

AND  
SAVE  
POUNDS!!



4 Speed Autochange or Single Player units supplied with brand new 2-tone Portable Cabinets 17 x 15 x 8in. deluxe strong carrying handle, gilt finish clips and hinges. As used by Famous Make for 20ans. models. Ready cut-out motor board 14 x 13in. Front baffle with 7 x 4in. high flux UY85-speaker and 3 watt 2 valve UY85, UCL82 2-stage amplifier ready built on metal chassis 12 x 3 x 2 1/2in. Quality 3 ohm output transformer, low hum level circuit. Volume and Tone controls. 3-core safety mains lead. All items fit together perfectly. Special instructions enable assembly in 30 minutes, only 5 wires to joint! 12-month written guarantee. Available separately or package deals as below.

### AUTOCHANGER KITS COMPLETE (as above)

B.S.R. Monarch .. .. £11.10.0 P.P. 5/6  
Collaro .. .. £11.15.0 P.P. 5/6  
Garrard .. .. £12.15.0 P.P. 5/6

### SINGLE PLAYER KITS Complete (as above)

E.M.I. Junior .. .. £9.19.6 P.P. 5/6  
E.M.I. auto stop/start .. £11.5.0 P.P. 5/6

### OR SEPARATELY

Cabinet with cut out board to your choice £3.9.6 P.P. 3/6

Amplifier with 7 x 4in. speaker £3.17.6 P.P. 2/6

### AUTOCHANGERS

B.S.R. UA14 .. .. £16.18.6 P.P. 4/6  
B.S.R. UA18 .. .. £6.17.6 P.P. 4/6

### SINGLE PLAYERS

E.M.I. auto stop/start .. £5.10.0 P.P. 4/6  
E.M.I. Junior .. .. £5.7.6 P.P. 3/6

### TRANSFORMATION UNITS

Garrard 4HF .. .. £16.10.0 P.P. 5/6  
Philips AG1016 .. .. £12.5.0 P.P. 5/6  
Garrard AT6 .. .. £11.0.0 P.P. 5/6

### BARGAIN

B.S.R. Autochange UA12 stereo/Mono .. .. £7.10.0 P.P. 4/6

Replacement sapphire styli available from 5/8.

Replacement Xtals from 15/-; Stereo from 18/6.

### BARGAIN SINGLE PLAYER KIT 200/250 v. A.C. (less cabinet)

**£5.15.0**

Post 5/-.

With 2-stage Amplifier; 3-watt; 2 valves, UCL82.

UY85: High-flux 5in. speaker; 4-speed E.M.I. Turntable, 18, 33, 45, 78 r.p.m.; Crystal Pick-up for LP/ST. Records, 7in. 10in., 12in.; Cut out Mounting board 12 1/2 x 9 1/2in.

### ARDENTE TRANSISTOR TRANSFORMERS

D3055, 7.3 CT.1 Push-Pull to 3 ohms for OC72, 11/-

D3054, 1.74:1 C.T. Push-Pull Driver for OC72, 11/-

D3058, 11.5:1 Output to 3 ohms for OC72, etc., 12/-

D167, 18.2:1 Output to 3 ohms for OC72, etc., 12/-

D238, 4.5:1 Driver, 4in. x 4in. x 4in., 11/6

D240, 8.5:1 Driver, 4in. x 4in. x 4in., 11/6

### ARDENTE TRANSISTOR VOLUME CONTROLS

VC1545, 5K or 1 meg. with switch dia., 9in., 6/3

DEAF AIR EARPIECE, Xtal or magnetic, 7/6

SUB-MIN. JACK and PLUG, 3/6 pair

## MINIATURE PANEL METERS

Size 1 1/2in. sq. Precision jewelled bearings, 2% accuracy, silvered dials, black numerals and fine pointers, zero adjustment screw on front of meter.

0-1 mA .. 27/6 0-50uA .. 39/6

0-5 mA .. 27/6 0-500uA .. 32/6

0-300 V .. 27/6 "S" Meter .. 35/-

## "PRACTICAL WIRELESS" SPECIALISTS

P.P. charge 1/-.


C.O.D. 2/- extra.

337 WHITEHORSE ROAD  
WEST CROYDON

Telephone: THO 1665

(Export welcome. Send remittance, and extra postage, no C.O.D.)

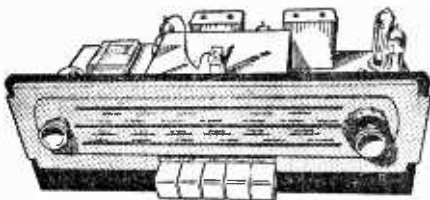
## BRAND NEW AM/FM (V.H.F.) RADIOGRAM CHASSIS AT £13.13.0 (Carriage Paid)



Chassis size 15 x 6½ x 5½ in. high. New manufacture. Dia: 14½ x 4 in. in 2 colours, predominantly gold. 200-250 v. A.C. only. Pick-up, Ext. Speaker, Ac., E., and Dipole Sockets. Five push buttons—OFF, L.W., M.W., P.M. and Gram. Aligned and tested. O.P. Transformer. Tone Control. 1000-1900 M.: 200-550 M.: 88-98 Mc/s. Valves E280 rect.; ECH81, E289, EAB380, EL84, ECH35. Speaker 5 x 5 in. and Cabinet to fit chassis (table model). 47/6 (post 5/-).


10 x 6 in. ELLIPTICAL SPEAKER 25/- to purchasers of this chassis. TERMS: (Chassis) £8.10.0 down and 6 monthly payments of £2.4.0. (Cheap Room Dipole for V.H.F., 12/6. Feeder 6d. per yard. Circuit diagram 2/6. ALTERNATIVE DESIGN. L.W. 1000-2000 M.: 8-8½. 17-50 M. (6-17 Mc/s). M.W. 200-550 M.: V.H.F. 87-100 Mc/s. Gram. position. Otherwise similar to above chassis. Price £15.15.0 (carr. paid). TERMS: £3.10.0 down and 6 monthly payments of £2.4.0.
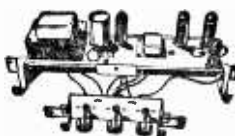
### PUSH-PULL AMPLIFIER £55.0 (6/- Carr.)



Brand new 200/240 A.C. mains. Bass, treble and vol. controls, with valves E280, ECH35 and 2-EL84 giving full 8 w. Chassis 12 x 3½ x 3½ in. With o.p. trans. for 2-3 ohm speaker. Front panel (normally screwed to chassis) may be removed and used as "flying panel". Stereo version 2 x 4 w., same price. Fixed panel. Tone & Vol. Controls.

### TAPE RECORDER AMPLIFIER

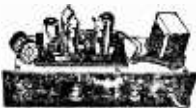

Type TE3. Fully built, high gain, low noise, printed circuit. Attractive grey and gold front panel 13 x 1½ in. Height 5½ in. overall. Front to back 5½ in. Vol. and on/off tone. Mike. radio and ext. speaker jacks. Valves, magic eye, ECH35, ECH22, E27-90. Mains trans. Ready to bolt to B.S.R. Deck. Complete with switch water wired. Our Price ONLY £6.15.0 (6/- Packing and Carr.). Also available for Collaro Deck at 5/- extra.

### THE "REGENT" 6-TRANSISTOR AND DIODE PORTABLE COMPLETE KIT FOR ONLY

£5.17.6 (post 5/-)



500mW push-pull output. Ferrite rod aeral. Car aeral socket and coil. M.W. and L.W. full coverage. Operates on two 4.5v. cells. Printed circuit board 8½ x 2½ in. All holes drilled and component positions marked. Instructions 2/6 for 16p. (refunded on purchase of kit). Size 9 x 3½ x 7 in. 8 x 2½ in. P.M. high quality speaker. Attractive Vynair covered cabinet. Two-tone. Two batteries 5/6 the pair (Ever Ready 126). Mullard transistors OC44, 2 x OC45, OC51D and 2 x OC81. Top grade Weymouth Radio coils and transformers. Alignment service required 17/6 (inc. post). Write for list of prices. All parts supplied separately. Built in two hours.



### 6-TRANSISTOR PORTABLE—Fully Built

The "SCALA" for only £7.10.6, carr. paid. 8½ x 2 x 5½ in. high. Choice of colours. Rexine. M.W. and L.W. Ferrite aeral. Battery 2/6 extra. Printed circuit. Nicely styled. A professional job. 3½ in. speaker. Fully tunable M.W. and L.W. Superhet circuit.

100 mF. + 200 mF. ELECTROLYTIC. New 275 v. (350 v. sugel. 4in. x 1½ in. dia., 5/- each. (Post 1/-).

ALL ITEMS ARE NEW AND FULLY BUILT UNLESS OTHERWISE STATED. TESTED BEFORE DESPATCH. Terms Available on Items over £5. Send 6d. (stamps will do) for 20 page illustrated catalogue. Delivery by return. C.O.D. 2/- extra.

ALL ITEMS GUARANTEED 12 MONTHS VALVES 3 MONTHS

## GLADSTONE RADIO

"SCALA", CAMP RD., FARNBOROUGH, Hants. Farnborough 8371

CLOSED SATS.

## "REALISTIC" 'SEVEN'

7 Transistor Superhet. 350 Milliwatt output, 4-inch speaker. All components mounted on a single printed circuit board size 5½ x 5½ in. in one complete assembly. Plastic cabinet, with carrying handle, size 7 x 10 x 3½ in. External socket for car aeral. Ferrite rod aeral. Price for the complete parcel including Transistors, Cabinet, Speaker, etc., and Full Construction Data: £5.19.6 P. & P. 4/-



FP9 Battery 3/8. Data and instructions separately 2/6. Refunded if you purchase the parcel.

Any parts supplied separately.




### 4 TRANSISTOR MINATURE PUSH-PULL AUDIO AMPLIFIER

PRINTED CIRCUIT. 5in. x 2½ in. x 1½ in. over transformers. Output for 3-ohm speaker. Suitable for microphone, record player, guitar and radio input. 4-12 volt battery required. Frequency range 100 cps. to 25 Kcps. Push/pull output single ended. Instruction sheet provided. Fully wired ready for use. Two types available. 1 watt output, 35/-, 1½ watts 41/- P. & P. 2/6.
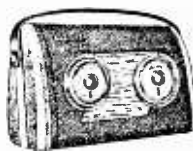
### THIS SUPERB SET for £9 (Carr. pd.)

6-transistor radio covered in sponge clean Duracour fabric, in latest two tone shades. M.W. and L.W. ferrite rod, provision for car aeral, 2-colour scale. With PP9 Battery giving 300 hours use. Weighs under 4 lbs. With carrying handle, 12 x 7 in. high x 4 in. at base tapering to 2 in. at top. Brand new fully guaranteed. 3 push buttons. Superhet circuit. 3 in. L.S.



### 5 WATT AMPLIFIER

Our price ONLY 58/- (post 5/-); a new hundred only; valves EF91 and EL84 with metal rectifier; 6 x 1 x 1½ in. high (5 in. over EL84). Mains trans. and o.p. with vol. and tone controls; on-off; co-ax input.

### SPECIAL REDUCTIONS ON GRAMOPHONE AMPLIFIERS

1½ watt type. Save 4/6. With 5in. speaker. Raffle 12½ x 6 in. 200-240 v. A.C. EL84 and Rectifier. Tone and Volume. On/off switch. Two knobs. Ready to play. Useful for Stereo. 45/-, post 5/-

4 watt type. Save 20/-. Valves UV35, UP30 and EL84. 200-240 v. A.C. Covered Raffle 13½ x 7½ in. (5 in. speaker). 3 front controls: bass, treble, on-off/vol. 34/-, post 5/-. Double wound metal transformer.

2½ watt type. Save 20/-. 2½ watts. ECH35, ECH22 and E2750. Controls volume, bass and treble. On/off switch. 200-240 v. A.C. O.P. trans. Size 12 x 3½ x 5 in. over valves. Suitable for microphone input and for Guitar. 55/-, post 5/-.

### STEREO CONVERTER UNIT



Converts existing Radiogram to play stereo records. Chassis 6½ x 2½ x 4 in. overall height. Mains and O.P. trans., Metal Rect., ECH22 valve and all screws, panels, etc. Moulded front enclosure, fully built, brand new only extra needed, speaker and stereo cartridge. Full instruction leaflet. Limited quantity at 39/6. (6/6 P. & P.). Lonette Stereo Cartridge, 25/-.

### TOP QUALITY RECORDING TAPE (Guaranteed)

(1/- per tape, six or more post free).					
4in.	600ft.	12/6	57in.	1200ft.	17/6
5in.	600ft.	11/3	57in.	1800ft.	35/-
5in.	900ft.	17/-	7in.	1200ft.	15/-
5in.	1200ft.	30/-	7in.	1800ft.	19/6
5½in.	850ft.	11/8	7in.	2400ft.	32/6

### BATTERY ELIMINATOR

For 4 Low Consumption Valves (96 range) 90v. 15mA and 1.4v. 125mA. 45/- (4/- post). 200-250v. A.C. Also for 250mA 1.4v. and 90v. 15mA at same price. Two separate units to replace existing batteries. 4 x 2½ x 2½ in. and 3 x 2½ x 1½ in.

AMPLION "Activette" for charging dry batteries. Mains operated 200-250v. A.C. Size 4½ x 2½ x 1½ in. with output socket and plug for 45v., 60v. and 90v. H.T. with 1.5v. L.T. Price ONLY 27/6.

### HEATER TRANSFORMER

Mains input giving 6.3v. 2 amp. Size 3½ x 2½ x 1 in. (2½ in. over winding) 5/6 ea. Less 10% for 12, or 20% for 50. P. & P. 2/- for 1 to 5, post free more than six.

# Practical Wireless

Vol. XXXIX No. 683 JANUARY, 1964

Editorial and Advertisement  
Offices:

**PRACTICAL WIRELESS**

George Newnes Ltd., Tower House,  
Southampton Street, W.C.2.

© George Newnes Ltd., 1964

Phone: Temple Bar 4363

Telegrams: Newnes, Rand, London,  
Registered at the G.P.O. for trans-  
mission by Canadian Magazine Post.

## SUBSCRIPTION RATES

including postage for one year

To any part of the world £1.9.0

## Contents

	Page
Editorial ... ..	809
Round the World of Wireless ...	810
The P.W. "Sixteen" ... ..	812
A Wide Range L.F. Oscillator ...	814
Crystal Controlled V.H.F./F.M. Tuner ... ..	816
Variable Capacitance Diodes... ..	819
A Quality Transistor Amplifier ...	824
A Variable Power Supply for Transistors ... ..	827
Domestic Straight Three ... ..	836
Simple Impedance and Re- actance Calculations... ..	842
Beat the 'Beam' ... ..	849
The Progressive Portable ... ..	853
Alternative Tape Decks for the Malvern ... ..	858
Trade News ... ..	866
On Your Wavelength ... ..	869
Home Inter-com Unit Mark II ...	870
Books Reviewed... ..	873
Club News ... ..	874
Letters to the Editor ... ..	877

The Editor will be pleased to consider articles of a practical nature. Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, PRACTICAL WIRELESS, George Newnes, Ltd., Tower House, Southampton Street, London, W.C.2. Owing to the rapid progress in the designs of wireless apparatus and to our efforts to keep readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in PRACTICAL WIRELESS is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. PRACTICAL WIRELESS incorporates "Amateur Wireless."

## Measure of Success

ONE sometimes hears of enthusiasts who consistently build equipment without the aid of test gear. This is possible, of course, but what happens when a completed job fails to function satisfactorily or does not work at all? One can only poke about haphazardly hoping to stumble on a mechanical fault or abandon the project.

At all events, time and energy are wasted, often fruitlessly. Not only that, but this approach is to say the least a very untechnical one in a technical hobby!

Test gear is not only helpful in tracing breakdowns. Even assuming that all home-built equipment works, how much of it functions at optimum? How many receivers and amplifiers are there at this moment working at less than full efficiency?

All components, whether from the spares box or new from dealers, are subject to tolerances and variations in quality. The permutations possible in even simple equipment are considerable. Again, a "4-7k" resistor, for example, may be actually 47k or 470Ω due to wrong colour coding and components may be o/c or s/c or changed in value. These things do happen and if there is no means of checking when in doubt, the constructor may spend many frustrating hours looking for a constructional fault that does not exist. Without test gear he is working blind.

The acquisition of test gear need not be prohibitive, because for the average enthusiast a few basic items should suffice. And of these, an accurate multirange test meter is the obvious starting point. For those regularly building equipment it is an indispensable item and will provide facilities for overcoming many everyday snags and for solving mysteries of sub-standard performance.


It is, however, inadvisable to buy an inferior meter, for this type of false economy may only aggravate certain problems. Bearing in mind the need for an inexpensive yet accurate and sensitive test meter we felt it would be a popular conclusion to our present series of blueprints to present an instrument of the calibre of the P.W. "Sixteen".

It will stand comparison with a good quality commercial product. A special plastics case is available, with the switch ranges and other lettering already printed on the front panel. The scale arcs are specially calibrated and printed ready for use. All the special components are available through usual sources.

We have thus overcome all the snags in building your own test meter—no tricky work in making up special shunts and multipliers, no calibration to work out and mark up on the scale. In other words we are making available to the home constructor a multirange test meter which not only performs to commercial standards but looks professional, too!

With its sixteen a.c. and d.c., voltage, current, and resistance ranges, the P.W. "Sixteen" is a fine opportunity for those not having a test meter or wishing to replace an old one.

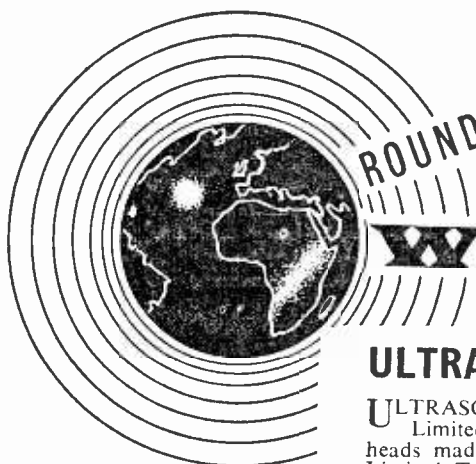Our next issue dated February will be published on January 7th



ROUND THE WORLD

# of WIRELESS

## NEWS AT HOME AND ABROAD

### Commonwealth Telephone Link Complete

ON October 10th, the final part of the Commonwealth Telephone cable was layed off Hawaii and for the first time the Pacific Ocean was spanned by telephone cable. This occasion also marked the completion of the 14,000 mile Commonwealth link between Britain and Australia. With the trans-Atlantic cable between Britain and Canada—which has been in service since December 1961—and the new 3,000 mile microwave network which crosses Canada, London and Sydney operators will be able to dial right through to subscribers at each end of the link.

For telephone users in Australia and Britain, this link means a reliable method of communication over more than half the world's circumference. A total of 80 two-way speech channels thus become available which, unlike previous radio links, will be free from fading and atmospheric conditions. As well as telephone conversations, the new cable will be used for teleprinter traffic; each speech channel being capable of carrying 22 such circuits. Circuits will also be made available to commercial concerns, such as airlines and shipping companies.

In itself, the Pacific section of the link is the longest submarine telephone cable in the world; as a whole, the Commonwealth link is by far the biggest project of its kind ever attempted.

All of the cable used in the project—and there were 11,000 miles of it—was manufactured in Britain by Submarine Cables Limited, and Standard Telephone and Cables Limited. This cable, which at one point in the Pacific section of the lay reaches a depth of over three miles, is little more than an inch in diameter.

The Atlantic and Pacific cable-laying operations have taken two and a half years to complete by the three British ships which had the task of making the lays. Terminal points of the Atlantic link are Oban in Scotland and Hampden, Newfoundland. The Pacific cable joins Sydney, Australia with Vancouver, Canada, via Auckland (New Zealand) and Suva (Fiji).

### ULTRASONIC CLEANING FOR GEARS

ULTRASONIC cleaning equipment made by Mullard Equipment Limited, has replaced conventional methods of cleaning gearheads made at the Egham factory of O.T.M. Servo Mechanisms Limited. To ensure the efficient operation of these gearheads—which are used in servo systems of aircraft and guided missiles—it is essential for the gears and pinions to be thoroughly cleaned before they are assembled into the head.

Originally hand-washing in a solution of carbon tetrachloride was the cleaning process used, but this was found to take too long and the standard of cleanliness achieved was not satisfactory. The Mullard Ultrasonic equipment, however, successfully removed all particles of dirt bigger than two microns in diameter after a two minute cleaning period. This not only saves time but also increases considerably the life-expectancy of the gearheads because of the large percentage of dirt that can be removed by this process.

The Mullard equipment consists of an ultrasonic generator and a 1½ gallon stainless-steel tank, which holds the cleaning solution (a chlorinated hydrocarbon) into which the gears are placed for the cleaning operation.

### New Communication Equipment for Police

POLICE forces throughout the U.K. are to be supplied with new radio communication equipment manufactured by Ultra Electronics Limited under a contract from the Home Office Communications Branch. Three separate types of equipments come under the contract and these are, a hand-held transceiver, a mobile transmitter/receiver for motor-cycles and a similar unit for other motor vehicles used by the police.

In the design of the motorcycle and car units, the manufacturers have employed circuit techniques which have resulted in economies in space and weight. The new pocket-sized transceiver is fully transistorised and takes its power from a nickel cadmium rechargeable battery which gives it an operating life of several hours.



## HI-FI IN THE ARABIAN GULF

**E**QUIPMENT made and tested by the British manufacturers prior to its delivery, has been installed in the club recently built for the staff of the Bahrain Petroleum Company Limited in the Arabian Gulf. The equipment, which has been supplied by A.E.I. Limited, provides a high-fidelity amplification system covering every part of the several acres of ground which the club occupies.

Six A.E.I. 30W power amplifiers provide amplification for microphone, tape recorder, radio broadcast or record player inputs.

## Laboratory Extension

**T**HE Research and Development department of Garrard Engineering Limited at Swindon, has recently undergone a major extension programme which has resulted in an enlarged laboratory with the number of engineers and scientists employed there increased to 70. By the end of the year at least 80 technicians will be engaged on the research, development and testing of Garrard-made products.

## Power Amplifiers Clear Birds from Runways

**A** COMMON hazard faced by pilots of aircraft is the presence of large numbers of birds on and around runways. At several of the major airports in Britain steps have been taken by the authorities to remove this hazard and thus make take-offs and landings safer.

The device which is used in dispersing the birds consists of loud-speakers and amplifying equipment installed in a van. These mobile units operate close to the airport runways and broadcast bird cries which are effective in removing certain species from the area.

The Sappho audio equipment employed in these vehicles, is made by Trix Electronics Limited. The latest order for such equipment received by Trix is for a unit for Speke airport, Liverpool.



*A mobile bird-dispersal unit, fitted with Sappho audio equipment, in position near an airport runway.*

## British Simulator Trains Canadian Mariners

**A** FULLY transistorised marine radar simulator manufactured in England by the Solartron Electronic Group, Limited, has been installed in the Navigation Department of the College for Trade and Technical Training, St. John's, Newfoundland,

Canada. Here it will be used to train some of Canada's future mariners in the methods of handling all kinds of ships in congested coastal seas.

The simulator confronts the student mariner with situations typically met with in the more

crowded shipping areas as displayed on a radar screen. He has all the controls and navigation aids that would be found on the bridge of a ship and his handling of the "ship" under varied simulated conditions is reproduced on the screen. Other simulated ships can be brought into the field of his radar and the movements of these are constantly fed to a computer where they are compared with the movement of the student's "ship".

The instructor who decides how to deploy these simulated ships can also simulate coastlines and typical radar effects which are often present with sea-borne equipment.

## Laser Drills Holes in wire

**I**N a technical paper presented at the National Electronics Conference held recently in Chicago, U.S.A., Dr. Danilo V. Missio of the Raytheon Company of Massachusetts, revealed that he and his fellow research workers had successfully used accurately controlled flashes of laser light to bore holes through tin wire only two-thousandths of an inch in diameter. The holes themselves were

less than five microns (two ten-thousandths of an inch) in diameter, and this was the first report of holes of such small magnitude being drilled using a beam of laser light, although previous work had indicated that it was possible.

## RADIO EQUIPMENT FOR AIRLINERS

**E**VER since 1949, Central African Airways have specified Marconi aeronautical radio equipment for their aircraft. Now the Marconi Company Limited have received an order from C.A.A. to equip their new B.A.C. One-Eleven aircraft with the Sixty Series of airborne radio units.

Under this order, each aircraft will have dual v.h.f. communications systems, a single v.h.f. navigation system and dual automatic direction finding systems.

## THE PRACTICAL WIRELESS

# "Sixteen" Multirange METER

The Blueprint given away free with this issue provides all the circuit and wiring diagrams for this instrument

16 switched ranges; nine for voltage measurements, four current ranges, and three resistance ranges.

Voltage	Current	Resistance
0-2.5V d.c.	0-50 $\mu$ A	0-2,000 $\Omega$
0-25V	0-2.5mA	0-200k $\Omega$
0-50V	0-50mA	0-20M $\Omega$
0-250V	0-250mA	
0-500V		

a.c. and d.c.


**Meter sensitivity:** 20,000 $\Omega$ /V on d.c. ranges; 1,000 $\Omega$ /V on a.c. ranges.

**Basic movement:** 40 $\mu$ A f.s.d. moving coil. With universal shunt full scale deflection current is 50 $\mu$ A.

**Physical details:** Black plastic case, 3 $\frac{1}{2}$ in. x 5 $\frac{1}{2}$ in. x 1 $\frac{1}{2}$ in. 3in. scale window; two scales printed black on white.

**Controls:** 12-position range switch; slide action a.c. volts—d.c./ohm switch; ohms zero adjustment potentiometer; meter zero.

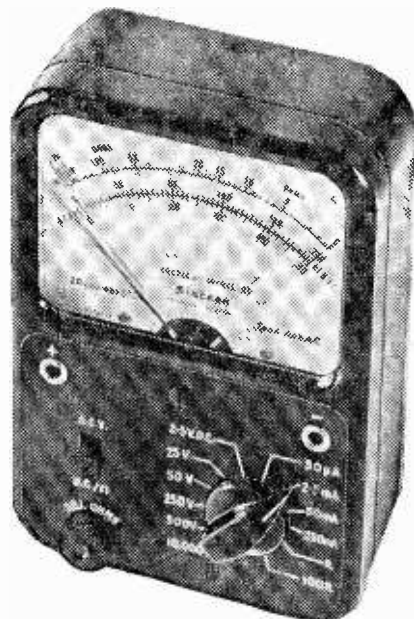**External Connections:** Two sockets to suit 4mm test lead plugs.



WHEN properly assembled, with the specified components used throughout, the P.W. Sixteen will meet most of the requirements of the average radio constructor for voltage, current and resistance measurement. The special arrangements that have been made with various manufacturers ensure that not only will the finished multimeter have an excellent electrical performance but that it will also have a neat, professional external appearance.

The multimeter is built around a highly accurate and sensitive moving coil movement. The universal shunt used in conjunction with this movement brings the overall d.c. sensitivity to 20,000 ohms per volt. Two clearly printed scales are provided on the meter face. Uppermost is the ohms scale which is calibrated (right to left) from zero to 2k $\Omega$ . The second scale is used for the d.c. and a.c. ranges and is in fact a double scale.

This scale is divided linearly into 50 small divisions, with main calibration points at every tenth division. These points are marked 50, 100, 150, 200 and 250 on the upper edge, and 100, 200, 300, 400 and 500 on the lower edge of the scale. A quick glance at the setting of the range switch is all that is necessary to establish which particular calibration is to be read.

## THE COMPONENTS

It is emphasised straight away that with an instrument of this nature, no liberties can be taken as far as the components are concerned. Close

adherence to the details given in the components list on the blueprint is essential if the calibration accuracy and general performance of the final instrument is to be up to standard.

The following notes amplify the information in the components list and should be read with particular care before arranging to purchase the various parts. In this connection it should also be made clear that all components are obtainable through usual retail sources and that the manufacturers named here do not, as a general rule, supply direct to individuals.

The instrument case is supplied with the meter movement built in. With the meter case is supplied a specially selected swamp resistor (R17); note that meter movements and swamp resistors are not interchangeable. This point also applies to the meter rectifier (MR1), which comes complete with its own associated shunt resistor (R19). All these components are supplied as a kit by Taylor Electrical Instruments Ltd.

The slide type changeover switch (S2) has been listed as an Arco-electric type T225; however, mention should also be made of an alternative Aerial pressings type RA 2133/PVC. This particular switch has p.v.c. insulation which is impervious to moisture.

The range switch (S1) is an N.S.F. type, and can be obtained by quoting its reference "PW16".

The various multiplier and shunt resistors are generally of non-standard values and it will

certainly prove convenient to obtain these as a complete kit: as manufactured and supplied by The Radio Resistor Co.

### BUILDING THE METER

Having obtained all necessary parts and materials, it is good policy to examine carefully Fig. 2 and Fig. 3 on the blueprint and so familiarise oneself with the arrangement to be adopted. The task of construction is not unduly complicated but the restricted space necessitates a methodical approach. The wiring-up should not be rushed, but a high standard of workmanship aimed at as befits a piece of test equipment.

A small instrument type iron is essential. Good soldered connections are vital. A badly-made, high-resistance joint may have a serious effect upon the accuracy of the meter. Overheating of components must be guarded against.

Remove the two 4BA screws from back of instrument case and lift off the top panel. Inside will be found the meter rectifier, two resistors (R17, R19) and two sockets, with solder tags, locking nuts and plastic pillars.

Do not remove the protective cap fitted to the rear of the meter movement, as particles of dirt or dust could easily fall into the movement while assembly work is in progress.

Fit the two input sockets to the front panel; place a solder tag beneath each locking nut and then screw on the plastic pillar.

Mount the a.c./d.c. switch (S2) and secure to the front panel by means of two screws.

Remove the knob from the potentiometer (VR1) and place this component in position securing with the ring nut supplied (a pair of fine nosed pliers can be used for this purpose). Fit the knob by pressing lightly into the hole, rotate until the slot engages and then press right down to lock it.

Screw the solder tags "A" and "B" in position (Fig. 2). If a double tag is not available, use two single tags for tag "B".

Solder R19 across uppermost pair of tags on S2, then solder the meter rectifier to these same tags. The centre lead on the rectifier is soldered to tag "A".

Special care is required during this soldering operation, because excessive heat will (1) affect the calibration of the rectifier and (2) melt the p.v.c. switch plate and cause intermittent contact.

The range switch S1 should next be dealt with. All the wiring shown in Fig. 3 must be performed before the switch is installed. It is suggested that each switch tag be dealt with in turn, proceeding

in a clockwise direction and starting with tag 1. See Fig. 3. The high stability resistors must be handled with care. If the thin protective coating suffers damage, the resistance value can be seriously affected. Grip by the wire leads only.

Ensure that all resistors have at least  $\frac{1}{4}$ in. of wire at each end, this is to avoid overheating when soldering—which might result in damage or change of value. Space all resistors at least  $\frac{1}{4}$ in. away from each other, and also from any other switch tags. Careful positioning of R1 and R6 is particularly important as these resistors carry 500V.

It may be an advantage to fit a plastic protective sleeve to the following resistors in order to prevent them coming into contact with other components of a different potential: R3, R7 and R18.

See that all flying leads are of adequate length, check by referring to Fig. 2. Use 7/36 p.v.c. covered wire for the battery leads; these should be suitably colour coded, and should extend 6in. from the edge of the switch wafer.

All other wiring can be in 22 or 24s.w.g. tinned copper, p.v.c. covered.

Carefully check over the wiring of S1, then fit this switch in position, ensuring that the orientation and the rotor setting agrees with that shown in Fig. 2 and Fig. 3. Secure the switch with the nut, then fit knob, aligning the pointer with the 2.5V position engraved on the front panel.

The remaining wiring should now be completed as per Fig. 2. Handle the wirewound meter swamp resistor R17 with care to avoid open-circuiting the winding. R5 and R16 should preferably be sleeved.

Thread a  $2\frac{1}{2}$ in. length of 6mm plastic sleeving over the four battery leads and push this down as far as possible into the centre of the switch. This sleeving will prevent chaffing of the leads by the switch spindle or rotors.

Place the instrument case body close against the left hand side of the panel, and solder the four battery leads to the connection points on the back of the battery compartment. The uppermost pair of connection points are for B2 (15V), the lower pair for B1 (1.5V). The right hand connection points are positive (+).

Close the two sections of the case, carefully dressing the battery leads so that they do not foul anywhere, and secure by replacing the two 4BA screws.

To install the batteries, remove the small panel at the rear of the instrument case. Looking into the battery compartment, the positive contacts are those to the left hand side. ■

## Christmas 1963

The editor, staff and contributors join in wishing all readers  
a Happy Xmas and a successful New Year

# a wide range l.f. OSCILLATOR

by P. CAIRNS

*A good-quality instrument  
for the amateur experimenter*

**T**HIS article describes a simple and cheaply made sine wave oscillator covering audio and ultrasonic frequencies. This unit, when correctly built and calibrated, can be extremely useful, having many practical and experimental applications, and should prove of use to both the amateur and professional engineer. The frequency stability is extremely good, being better than  $\pm 2\%$  for changes in h.t. of  $\pm 20\%$ , and changes in heater voltage of  $\pm 5\%$ . The wave shape is also of good sine waveform, though very slight distortion was noticeable at the extreme h.f. end of the tuning ranges.

## Circuit Description

The complete oscillator circuit is shown in Fig. 1. This covers the frequency range 35c/s to 70kc/s in six overlapping ranges. The oscillator is the double triode V1 with the necessary resistance-capacitance phase shift network required to maintain oscillation. The output stage, V2, gives both high and low impedance outputs.

The frequency of oscillation is determined by the resistance-capacitance network R1-R6, R7-R12,

and VC1. Feedback is fed from V1b anode to V1a via C6, the amount of feedback being controlled by VR1. This pre-set control also has a marked effect on waveform. The frequency range with the variable capacitor shown and a given set of resistors is less than 4:1. Thus six resistor ranges were necessary to cover the required band of frequencies, S1 being the range selector switch.

The oscillator output is taken from the cathode of V1b via C8 and VR2 to the triode amplifier V2. This has two outputs which are selected by S2, position 1 being the high impedance output, V2 working as an amplifier. Position 2 gives the low impedance output with V2 working as a cathode follower. In either position the output not in use is bypassed to earth via C10 or C11, these being the output coupling capacitors in the alternative position. Position 3 is "off", with the output point earthed. The amplitude of the output waveform is controlled in both cases by VR2. With VR2 at maximum, the output voltage in the high impedance position is approximately 25 peak, and in the low impedance position, approximately 2.5 peak.

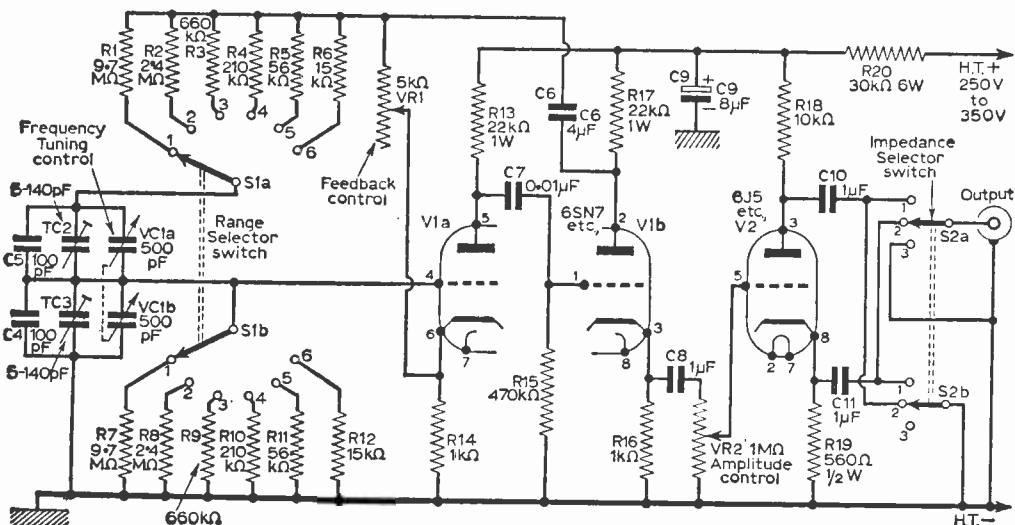


Fig. 1: The circuit of the oscillator.

### Construction

The layout of the majority of the circuit components is not critical, and a suggested scheme is shown in Fig. 2. Care should be taken with the resistors R1 to R12 on S1, these being mounted directly on to S1, the resistor end wires being cut as short as is practicable. S1 should also

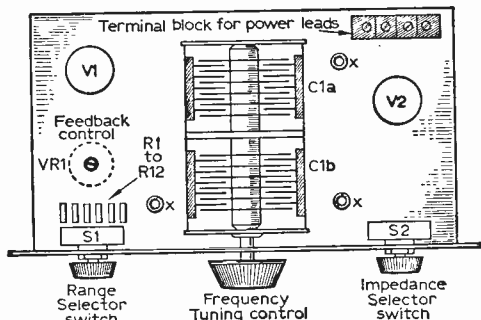


Fig. 2. An above-chassis view of the instrument.

be a good quality switch, ceramic if possible. This is to avoid leakage on the l.f. ranges as the 10M resistors (range 1) may approach the insulation value of a poor quality switch.

Good insulation is also preferable on the twin gang capacitor VC1 for similar reasons, this being mounted away from, and insulated from, the chassis. The V1a section of the circuit should be kept to its own part of the chassis and wired with reasonably heavy gauge wire.

To reduce any possibility of mains hum, the heaters can be wired with screened wire. Screened wire may also be used on the VR2 output lead. An important point regarding the resistors R1 to R12 should be made. As these resistors are of non-standard values, the correct values may be obtained by measuring the nearest preferred value for a high or low component as suggested in the components list. These resistors should be within 5% and preferably 2% of the stated values and of each other. This latter point is most important as any great discrepancy between resistor pairs on the same range can result in poor tracking, variations in amplitude, and possibly dead spots in the tuning range.

### Values

Should difficulty be met with in obtaining the correct value, two resistors may be used in series; e.g., R2, R8, are 2.42M each, and these could be made up from a 2.2M and a 220k in series. The resistor pairs, R1-R7, R2-R8, etc., should be matched on an ohmmeter if possible before connecting them into circuit.

No power unit has been incorporated as the oscillator will work from any 250-350V power pack without affecting the frequency calibration, the h.t. current drain being only 6mA.

For those wishing to keep the size of the unit to a minimum, miniature all-glass type valves may be used without any change in circuit values.

### COMPONENTS LIST

#### Resistors

R1, R7	9.7M $\frac{1}{2}$ W (low 10M)
R2, R8	2.4 $\frac{1}{2}$ W (high 22M)
R3, R9	660k $\frac{1}{2}$ W (low 680k)
R4, R10	210k $\frac{1}{2}$ W (low 220k)
R5, R11	56k $\frac{1}{2}$ W
R6, R12	15k $\frac{1}{2}$ W
R13, R17	22k 1W
R14, R16	1k $\frac{1}{2}$ W
R15	470k $\frac{1}{2}$ W
R18	10k 1W
R19	560 $\Omega$ $\frac{1}{2}$ W
R20	30k 6W (two 15k in series)
VR1	5k w.w.
VR2	1M

see text

#### Switches:

S1	2-pole, 6-way
S2	2-pole, 3-way

#### Valves

V1	6SN7 or ECC82, 12AU7
V2	6J5, 6B5 or EC90, L77

#### Capacitors:

VC1	Twin gang capacitor, 500pF per section
TC2, TC3	5 to 140pF trimmers
C4, C5	100pF (silver mica)
C6	4 $\mu$ F 350V (electrolytic)
C7	0.01 $\mu$ F 350V
C8, C11	1 $\mu$ F 25V
C9	8 $\mu$ F 350V (electrolytic)
C10	1 $\mu$ F 350V

### Alignment and Use


Switch on and allow the unit to warm up, set both trimming condensers TC2, TC3 to maximum, S1 to position 3, S2 to position 1, and VR2 to minimum. A pair of headphones are connected to the output. An audio note should then be heard when VR2 is increased; if not, adjust the feedback control VR1 until the circuit just goes into oscillation. If the circuit is already oscillating, adjust VR1 in the opposite direction until oscillation is just occurring, as at this point the best waveform is obtained. Too much feedback gives a distorted waveform. With the circuit just oscillating, swing VC1 through its entire tuning range. Should oscillation stop at this point, adjust the trimmers TC2, TC3, for better capacitance balance. With correct adjustment of TC2, TC3, the oscillator should work correctly over the entire range of VC1.

The other frequency ranges are then checked in a similar manner. Should any range not oscillate over the complete sweep of VC1, the resistor pairs on that particular range are not closely enough matched. This should not occur, however, if the tolerances quoted are used. Should difficulty be met with in maintaining oscillation over all ranges, the feedback may be increased by a very slight adjustment of VR1. It should be stressed, however, that the purest sine wave is obtained with VR1 at the lowest setting which maintains oscillation over the entire frequency range.

—continued on page 870

# CRYSTAL CONTROLLED V.H.F. - F.M. TUNER

By E. M. BERNEY

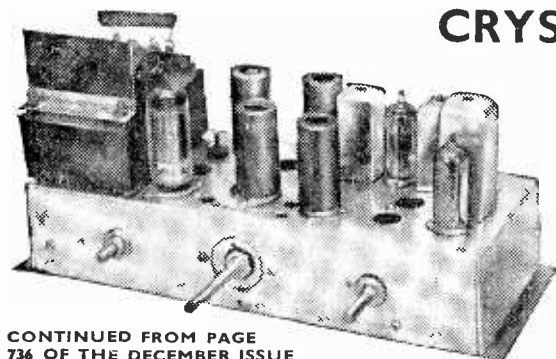

CONTINUED FROM PAGE  
736 OF THE DECEMBER ISSUE

**I**N last month's article the author referred to the coils and crystals used in this tuner. There are several other components which warrant special attention.

## OTHER COMPONENTS

Resistors generally should be of 10% tolerance, and R16 and R17 should be matched as accurately as possible. If the ratio detector is used, R22 and R23 should be similarly matched, and R20 and R21 should be 5% or better. Wattage ratings are given in the list of components.

The i.f. transformer should ideally have an acceptance band width of 250-300kc/s. This is usually achieved by over-coupling, and if critically coupled transformers are used it may be necessary to fit damping resistors across their primaries. The manufacturer's instructions should be followed here.

The choke, L4, is made by close winding 50 or 60 turns of 30 gauge enamelled copper wire onto a 100kΩ resistor of about 5/32in. diameter. The value of the resistor is not critical.

## WIRING

It is essential to observe v.h.f. technique here, reducing all connections to minimum length. Do not make any attempt at orderly layout; the short direct connection is the primary requirement and must take precedence.

If the specified types of components are used, it will be found possible to reduce connections to decoupling components to less than 3in. in length and this should be the aim.

A small iron of the instrument type is essential. Tinned copper wire of 20s.w.g. covered with sleeving can be used for the heaters, but 22 gauge is a more suitable size for the remainder of the wiring.

Decoupling resistors are conveniently fitted in a vertical position so that the h.t. line can be taken around to each stage in turn in the final stages of construction, well away from other components. It will not then be liable to carry r.f. currents from one stage to another.

The main smoothing resistor, R24, must be mounted in a position where its heat is easily dissipated. The top of the mains transformer is a good place but the choice is one of convenience provided it is above the chassis.

Complete wiring diagrams, showing all the connections, are given in Figs. 7 and 8. It should be noted that as the wiring has been opened out for clarity the positions of the components are only

approximate, and many of the connections appear much longer than is permissible in construction.

The circuit diagram (Fig. 1) shows the grid of V2 connected to the cathode, this is, of course, incorrect and pins 1 and 6 should be taken directly to chassis, as indicated in Fig. 7.

It should also be mentioned here that V2 is an EC91—not an EF91 as stated in the components lists.

## TESTING

When the wiring has been completed and checked against the circuit diagram, test with a meter between C30 and chassis to see that there are no shorts in the h.t. circuits. Power can then be applied and a further check made with the meter that the proper voltages are present at the valve electrodes. The h.t. line voltage should be between 220 and 250, and if it is not the value of R24 must be altered as necessary.

## ALIGNMENT OF I.F. AMPLIFIER

If a signal generator is available, it is advisable first to align the i.f. amplifier to 10.2Mc/s. as follows.

Remove V2 and connect a high resistance d.c. voltmeter positive to chassis and negative to test point A. Inject an unmodulated 10.7Mc/s. signal at the grid of V5 and adjust both cores of IFT2 for maximum reading on the meter, reducing the output from the generator as the circuits come into line.

Transfer the generator to the grid of V4 and adjust IFT1 in the same way.

To align the discriminator, connect the voltmeter between test point B and chassis and detune the transformer secondary by withdrawing the bottom core so that it projects about 1/16in. from the can. Inject an amplitude modulated signal at the grid of V5 and adjust the primary core for maximum response; then adjust the bottom core for extinction of the response. Finally, set the secondary core to produce a very small negative reading and peak this reading by adjusting the primary core. Return the secondary core to zero.

## RATIO DETECTOR

If the ratio detector has been used, connect the meter to test points D and E, observing polarity, and inject an unmodulated signal at the grid of V5. Adjust the top core of the transformer for maximum response. Connect the meter next between chassis and test point C and adjust the bottom core for zero output. This will affect the



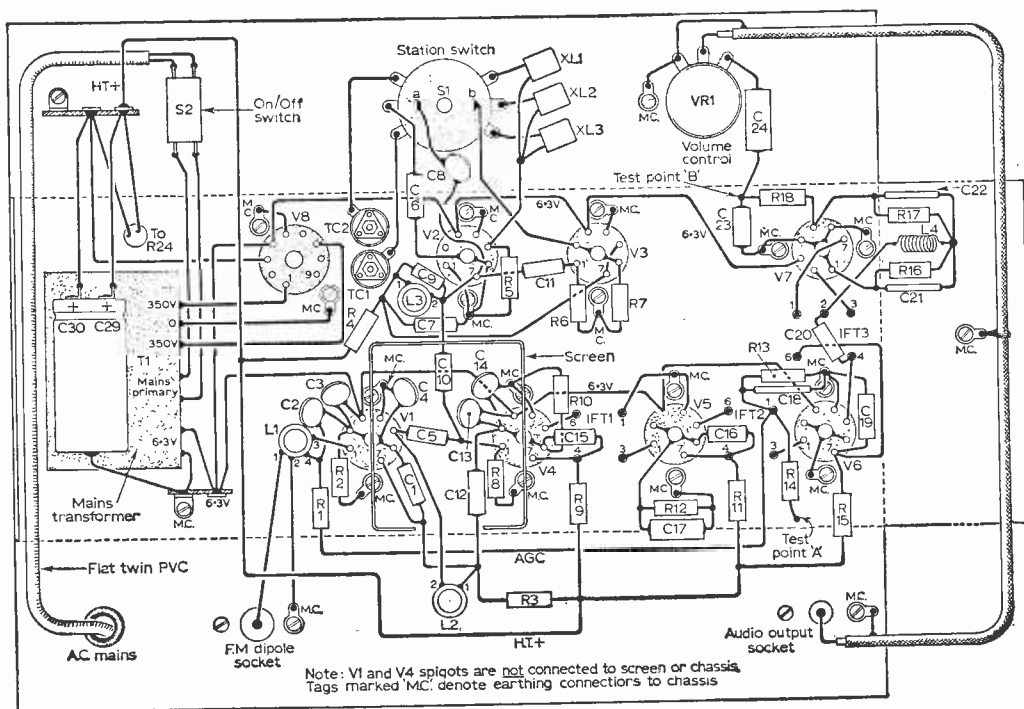


Fig. 7: The main underchassis wiring diagram.

top core which should be re-adjusted for maximum as already described.

The foregoing adjustments need not be made with the greatest accuracy since the final alignment must be done on a BBC transmission. With both types of detector transformer, it will be found that as the bottom core is traversed through the former, the meter reading will rise to a maximum, fall through zero to a reverse maximum, and then return to zero, after which further movement has no effect. The correct position for the core is at the zero between the two maxima.

### OSCILLATOR CIRCUIT

To align the oscillator, replace V2 and connect an audio amplifier. Set the tuning switch to the highest frequency to be received. Commencing with the core of L3 almost fully withdrawn, enter it slowly into the former until the programme is heard. It will be found that as the inductance of L3 is increased, the programme strength will rise slowly and then fall suddenly to zero as the crystal relinquishes control. The proper position for the core is just before the point at which control is lost.

If the programme cannot be found, reduce the inductance of L2 and try again. If there is still difficulty it should be checked that the oscillator circuit is in order and covers the required range. Remove the highest frequency crystal and fit in its place a mica or ceramic capacitor of about 47pF. With the switch in the appropriate position it will then be possible, if the circuit is in order, to tune

all three transmissions by manipulating the core of L3.

The i.f. amplifier and the detector transformer must now be aligned accurately to the crystal controlled signal in the manner described for alignment with a signal generator.

The tuning switch can next be set to each of the other two positions in turn and the programmes tuned in with the trimmers TC1 and TC2. Commence at minimum capacity and set the trimmers to a position just before that at which control is lost.

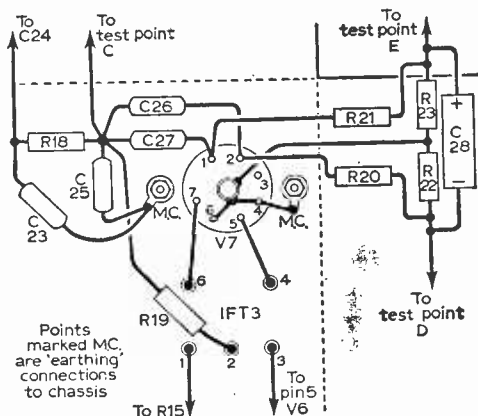


Fig. 8: The ratio detector wiring diagram.

### H.F. PROBE

A more accurate method of adjustment, and one that may be found essential in poor reception areas, is to use a high frequency probe connected to a high resistance voltmeter, or a low range milliammeter to detect resonance of the crystals.

A suitable circuit for such a probe is given in Fig. 9, while Fig. 10 shows how it may be constructed on a strip of paxolin or other similar material. It may be applied to the grid of the mixer valve or to the cathode of V2. As the inductance or capacitance of the oscillator circuit is increased, the meter reading will rise slowly, falling abruptly to zero as control is lost. The diode used in the probe is not critical; a GEX34 or similar will serve.

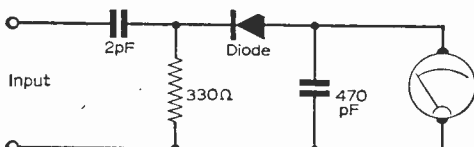


Fig. 9: A suitable circuit for an h.f. probe.

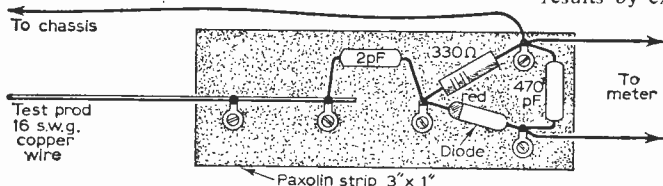


Fig. 10: A suggested form of construction of the probe.

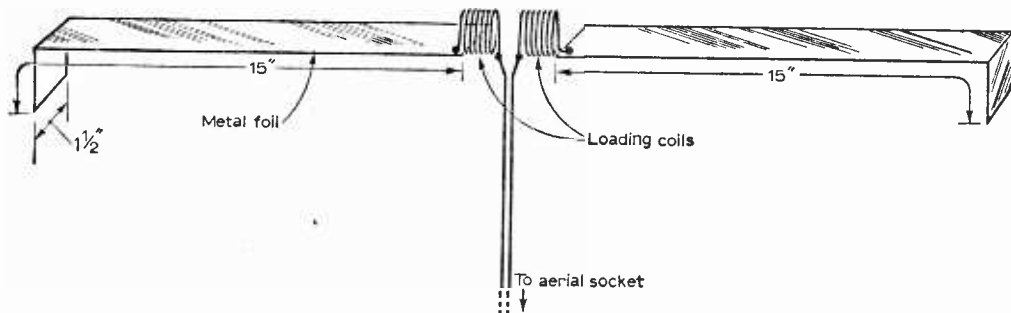


Fig. 11: Internal aerial for high field strength areas.

### R.F. CIRCUITS

Connect the meter negative to test point A and positive to chassis. Adjust L1 for maximum on the lowest frequency transmission and the L2 similarly on the highest.

### ALIGNMENT WITHOUT A GENERATOR

If the signal generator is not available, it is best to use pre-tuned i.f. and detector transformers. If this is not done, then one of the crystals must first be brought to resonance by the probe method when, provided a reasonable signal is available, it should be possible to align the i.f. and r.f. circuits as described.

### OPERATION

The aerial required will depend on local reception conditions.

A loft-mounted or outside dipole with reflector and low loss 75Ω coaxial down lead is recommended for fringe conditions; while in areas of good field strength satisfactory results may be had from an internal cabinet aerial. This may be made from a length of flat twin p.v.c. covered flex by parting the conductors at one end over a length of 30in. and extending them along the top of the cabinet to form a rudimentary dipole. The arms can be turned downwards 90 deg. if their whole length cannot be accommodated horizontally.

If something smaller is required, the arms of the dipole can be shortened and the deficiency made up with loading coils as shown in Fig. 11. No large scale experiments have been done on this by the author but promising results were obtained with metal foil glued to the inside of the cabinet, each arm being 1 1/2in. wide and 15in. long. The loading coils can be self supporting, consisting of 18 gauge tinned copper wire, four or five turns each and about half an inch in diameter. The inductance can be adjusted for optimum results by extending or compressing the coils.

In all cases, the aerial should be mounted perpendicular to the direction of transmission, and it is worth remembering that with a normal dipole the strength of the received signal varies almost directly with the height of the dipole above the ground. If the Foster-Seely discriminator has been used, do

not forget that a fairly large signal is required at V5 grid for efficient limiting.

### VENTILATION

The cabinet in which the tuner is housed should permit free ventilation above and below the chassis.

### PRACTICAL WIRELESS CIRCUITS

17th Edition

By F. J. CAMM

17/6 by post 18/7

from

**GEORGE NEWNES, LTD.,**

Tower House, Southampton Street, London W.C.2.

A. GLOVER discusses

# Variable Capacitance Diodes

Theory and applications of this new semiconductor device

VARIABLE capacitance diodes have a wide variety of uses both industrially and commercially, one of the more popular uses being that of remotely controlling the tuning of radio receivers. These devices are now becoming more readily available to the home constructor and experimenter, and this article provides a brief summary of their operation and shows the practical aspects of their use.

## P-N JUNCTIONS

The normal junction diode consists of two pieces of germanium (or silicon) sandwiched together, one

of which is 'n' type, the other 'p' type, Fig. 1(a) shows this diagrammatically. It will be noticed that the electrons in one side and the "holes", or absence of electrons, in the other side collect near the junction. This region, known as the "depletion layer", has a relatively high resistance compared with the rest of the diode, and in fact forms the dielectric of our capacitor; the two outer pieces forming the plates.

Fig. 1(b) shows the same diode with a reverse voltage applied across it. The "depletion layer" (the dielectric of our capacitor) has now increased in width, so the capacitance has been reduced.

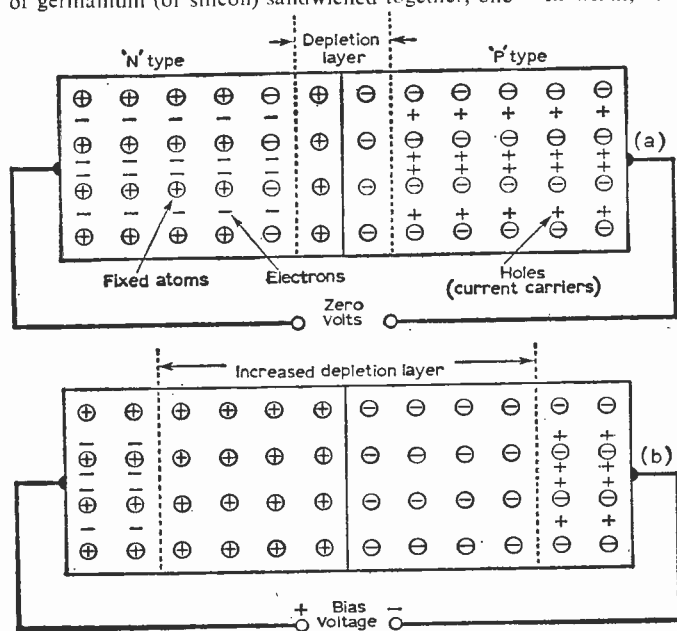


Fig. 1a: A p-n junction, without bias.

Fig. 1b: A p-n junction, with reverse bias.

The fact that capacitance decreases with an increase in voltage should be born in mind when using these devices, and a typical curve showing capacitance/voltage relationships is given in Fig. 2. The lower part of this curve is definitely not straight and is due to what is termed the "built in voltage". This can be overcome, if required, by biasing the diode on to a straighter part of its characteristic.

## CHANGE OF CAPACITANCE

This change of capacitance with applied voltage is common to all types of germanium silicon diodes, and this, of course, includes point contact diodes and transistors. Before attempting to use these devices, it is wise to check the capacitance to ensure they have the capacitance range for the particular application. The test circuit shown in Fig. 3 is useful here. Two similar devices should be used to ensure that the bridge voltage does not produce

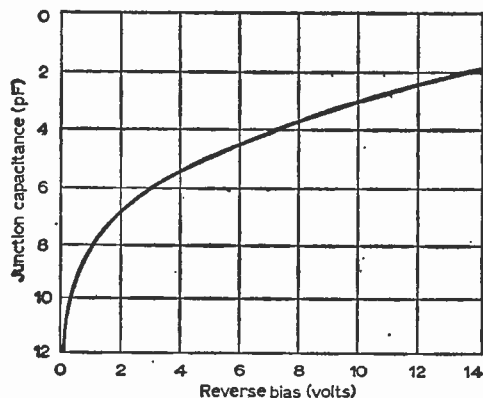


Fig. 2: A typical curve for a low capacitance variable capacitance diode.

an error, the bridge voltage should be kept as low as possible, and the peak inverse voltage of the diodes, obtainable from manufacturers data, should never be exceeded. The capacity reading on the bridge should be doubled for a single diode, as here we have two capacities in series.

In practice it will usually be found that the larger the junction the greater the capacitance, point contact diodes normally do not exceed about 10pF, on the other hand there are variable capacitance diodes which change from approximately 50pF to 250pF for a 25V change in applied voltage.

## REMOTE CONTROL OF RECEIVERS

The circuit shown in Fig. 4 is for the remote operation of a radio receiver, with both the oscillator and r.f. stages remotely tuned. In the

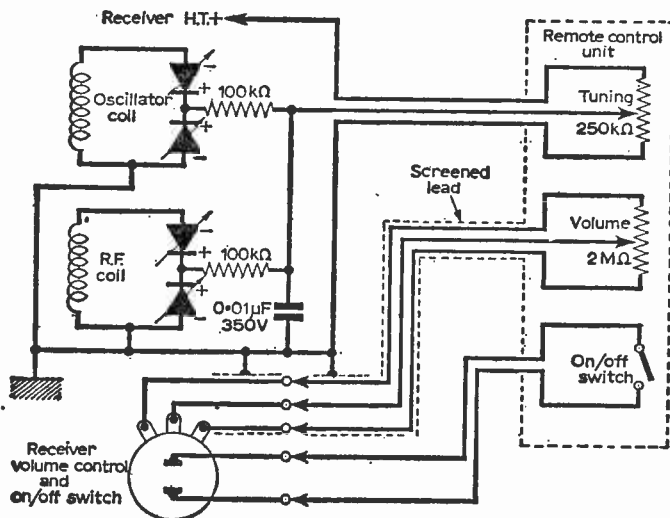


Fig. 4: Circuit for remote control of a radio set, using a variable capacitance diode.


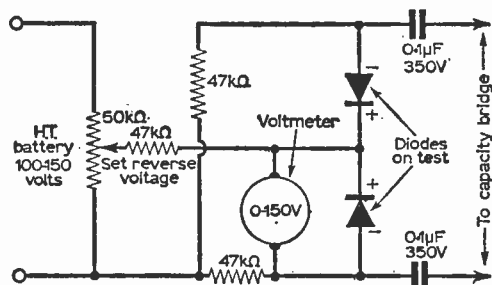


Fig. 3 (above): Suggested test circuit for checking the capacitance of diodes.

Fig. 5 (below): Replacing a reactance valve by a v.c.d.

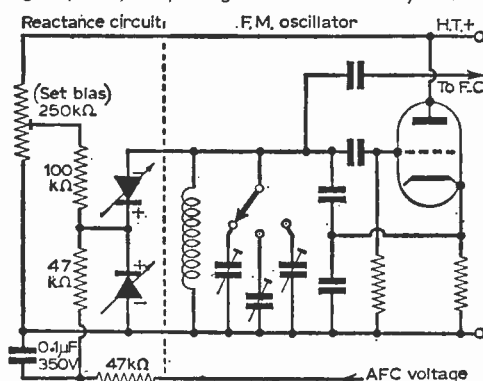

case of f.m. receivers it is usually unnecessary to tune the r.f. circuit, so one pair of diodes may be replaced by a trimming capacitor.

The volume control may be used remotely as shown together with the receiver on/off switch. All these interconnecting leads, and the control unit itself, should be adequately insulated, particularly so in the case of a.c./d.c. equipment.

In Fig. 5 we have a circuit which shows how the reactance valve in a switched tuned receiver may be replaced by capacitance diodes. The preset resistor which is used to bias the diode to the centre portion of its characteristic could at a later stage be replaced by two fixed resistors.

A similar circuit may be used for frequency modulating an oscillator, in this case, however, we replace the a.f.c. voltage input by a modulating signal; this method is shown in Fig. 6. The audio oscillator is in most instances already built into the signal generator. The maximum frequency deviation will depend

TRADE ENQUIRIES  
INVITED**RADIO CLEARANCE LTD.**Telephone: MUSeum 9188  
EST. 35 YRS.THE OLDEST COMPONENT SPECIALISTS IN THE TRADE  
27 TOTTENHAM COURT ROAD, LONDON W.1**ANOTHER SCOOP—  
LIMITED QUANTITY ONLY**

Don't miss a chance like this!

**The "Minigram" Transistorised Record Player**

## FEATURES:

- Ready-built amplifier with four first-grade Mullard transistors.
- Plays 45 R.P.M. pop records.
- Built-in automatic stop.
- Lightweight and portable.
- Instruction leaflet supplied.
- Crystal pickup with expendable stylus.
- Operates from a 9V battery (3/9 ext.).
- Available in two colours—cream/red or cream/blue.
- The Perfect Xmas Gift.
- Motor and pickup deck.....(2/8 P. & P.)
- A real "FAMILY FAVOURITE".
- Ideal for Teenagers.
- For use ANYWHERE.
- Hours of amusement for the younger members of the family.
- Assemble one of these amazing Players in less than 30 minutes; supplied in 3 complete units with only 10 connections to make.
- Approximate dimensions 9x8x4in.

**A**

Ready-built 4-transistor amplifier, complete with volume control and L'speaker (2/- P. &amp; P.)

**B**

Portable two-tone case with handle. (1/- P. &amp; P.)

**C**

ONLY

**79/6**

the complete pkgs. (plus 5/- P. &amp; P.) or any unit sold separately.

**Loudspeaker Bargains Still Available**

Enormous purchases of Brand New and Guaranteed Plessey loudspeakers enable us to offer these units at THE LOWEST PRICES EVER! Don't miss this golden opportunity to obtain a first-grade permanent-magnet LOUDSPEAKER of the production line at LESS THAN THE MANUFACTURER'S COST! Read carefully the prepared list below and choose just the right speaker for the job—COMPARE THE PRICES ANYWHERE! SELLING FAST—STOCKS CHANGING RAPIDLY.

## SCHEDULE OF LOUDSPEAKERS AVAILABLE

Diameter in inches	Gauss in lines	Imped. in ohms	Price	Diameter in inches	Gauss in lines	Imped. in ohms	Price	Diameter in inches	Gauss in lines	Imped. in ohms	Price	Diameter in inches	Gauss in lines	Imped. in ohms	Price
2	7000	80	8/-	4	6000	3	8/-	5	6000	3	8/-	5	9500	5	10/6
2½	7000	35	8/8	4	7000	3	8/8	5	6000	5	8/-	5	1000	3	11/6
2½	7000	50	8/3	4	8500	5	9/8	5	7000	3	8/8	5	6000	25	10/6
2½	7000	80	8/1	4	8000	25	10/8	5	7000	5	8/8	5	9500	25	11/6
2½	8500 E.M.L.3	8/6		4	7000	25	11/8	5	7500	3	9/-	6½	7000	3	11/-
3½	7000	35	8/8	4	6000	35	10/8	5	8500	3	9/8	6½	7000	5	11/-
3½	9500	50	10/8	4	7000	35	11/-	5	8500	5	9/8	6½	8500	3	11/6
4	8000	3	7/8	4	9500	35	11/6	5	9500	3	10/8				

Elliptical Size	Gauss in lines	Imped. in ohms	Price	Elliptical Size	Gauss in lines	Imped. in ohms	Price	Elliptical Size	Gauss in lines	Imped. in ohms	Price	Elliptical Size	Gauss in lines	Imped. in ohms	Price
5 x 3	6000	3	7/8	5 x 3	9000	35	11/-	7 x 4	9500	3	11/-	8 x 2½	9500	5	10/-
5 x 3	7000	3	8/-	6 x 4	6000	3	8/8	7 x 4	9500	30	11/8	8 x 5	6000	3	8/8
5 x 3	9000	3	8/8	6 x 4	7000	3	9/-	8 x 2½	6000	3	8/8	8 x 5	7000	3	9/-
5 x 3	9000	4	8/8	6 x 4	8500	3	9/8	8 x 2½	7000	5	9/-	8 x 5	8500	3	9/8
5 x 3	9000	5	8/8	6 x 4	9500	3	10/-	8 x 2½	6000	30	9/8	8 x 5	9500	3	10/-
5 x 3	6090	25	9/8	7 x 3½	9500	3	10/8	8 x 2½	8500	5	9/8	8 x 5	9500	15	13/6
5 x 3	7000	25	10/-	7 x 4	7000	3	10/8	8 x 2½	9500	3	10/-	10 x 6	10000	3	19/6
5 x 3	9000	25	11/-	7 x 4	8500	3	10/8	8 x 2½	9500	4	10/-				

ALLOW 2/- each Speaker for postage and packing, and please specify the exact requirements—the nearest available will be sent.

**OVER 50,000 SOLD AND STILL THE DEMAND CONTINUES FOR OUR "HEAVENLY TWINS"**

Ask for a demonstration in the shop.


**"CAPRI"**Sensitive!  
Super-selective!  
Superb Speaker!New Price  
NOW ONLY  
**79/6**(2/- P. & Pkg.)  
Pocket Super-  
net MW and  
Droitwich LWSize 4½ x 2½ x 1½ in.  
Constructional data 1/9 Post free.The best and  
easiest transistor  
build-yourself  
sets available.Send S.A.E.  
for FREE  
PARTS LIST6 First Grade  
MULLARD  
Transistors  
Diode(s) and  
all components  
BRAND NEW  
and  
GUARANTEEDChoice of a dozen stations  
in daylight...**"CONTESSA Mk. III"****"QUEEN OF THEM ALL"**ONLY **£9.19.6**

(3/6 p. &amp; pkg.)

PORTABLE CAR RADIO

2 WAVEBAND SUPERHET

Construction manual 2/10 Post Free.

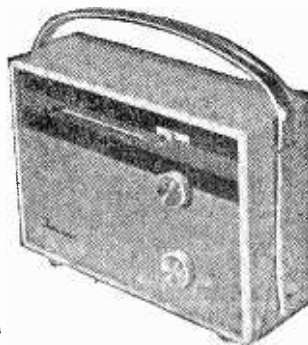Inclusive price for all associated components, case, battery  
and instruction Book complete in every detail.  
ANY PARTS SOLD SEPARATELY ON THE  
BUILD-AS-YOU-BUY SCHEME**CONTESSA III £9.19.6** (plus  
3/6)  
**CAPRI** Battery 2/6 extra **79/6** (plus  
2/-)

## SELECTED GUARANTEED BARGAINS

Beautifully geared AM/FM 2 Gang Condensers, 4/6: AM/FM IFT's 465 kc/s and 10.7 Mc/s, 4/6 pair; Magnavox Crystal Tape Recorder  
Mikes, 12/6; Double-tuned Transistor (terox) IFT's Q120, 470 kc/s, 5/6 pr; 3 matched IFT's and oscillator coil for Mullard transistor  
circuits, 10/6 the set; Plessey-Brayhead turret tuners 34/38 Mc/s, valves 8/6 each; 3 watt Stereo Amplifiers, complete, ready to switch  
on 79/6; Sentercell rectifiers R3/2D-D3-2-1Y, 2/6 each. DIODES—OA70, OA79, OA81, OA90, CG46H, GD10 2/- each.  
TRANSISTORS: Set of 6 (RF and LF) including 1 watt matched pair, heat sink and diode, 13/6 the set; OC44 (or equiv.), 6/9, OC45  
4/6, OC81 5/6; matched pair 12/-, PXC 101A 4/6, matched pair 9/6, PXA 101 8/9, AP 115 4/6, Submin. Germanium diode 1/3.  
Please send STAMPED and ADDRESSED envelope with any enquiry. We regret no catalogues—our stocks move too quickly! Kindly  
make provision for additional postage and packing charges to avoid delay. Terms: Cash With Order or C.O.D. on Orders Over 10/-



A NEW range of Tuner-Amplifiers with all the performance capabilities of separate tuners and amplifiers, superseding the Stereo 12 and Jubilee models.



## 227 AM-FM STEREO TUNER-AMPLIFIER

20 watt power output. Covering the full FM and medium wavebands. Inputs for any ceramic or crystal pick-up and tape play-back, also outputs for tape recording. Exceptional sensitivity and stability on FM. The Foster Seeley Discriminator being preceded by two IF Stages and a limiter stage. Medium waveband featuring automatic variable selectivity and heterodyne rejection filter provides Continental reception of good programme value.

PRICE £48.15.0

## 227 M. AM-FM TUNER-AMPLIFIER

This is the mono version of the 227 above and is identical in performance and specification except that a single channel control unit is incorporated with only one amplifier. Styling is also similar to the 227.

PRICE £33.18.0



## STEREO 55 TUNER-AMPLIFIER CHASSIS

One compact chassis combines AM and FM tuners. Stereo Control Unit and two power amplifiers. For mono reproduction the two amplifiers are used together so that up to 10 watts output is available. Provision for tape recording and play-back is made with a choice of inputs for crystal or ceramic pick-ups including the Decca Deram.

PRICE: £29.18.0

## AF 208 AM-FM CHASSIS

A high-quality tuner-amplifier chassis which can be used for the conversion of an existing radiogram or as the basis for building a new radiogram or reproducing system.

PRICE: £21.4.0

Full descriptive literature available from Dept. No. PJA

**ARMSTRONG AUDIO LTD.**

WARLTERS RD., LONDON, N.7. Tel: North 3213

# ADAMIN- by LITESOLD



These new ADAMIN micro soldering instruments supplement the well-known LITESOLD models for special applications and still further extend our very comprehensive range of specialised soldering equipment.

Bit sizes now 1/32in. to 1/16in.

## A POPULAR ADAMIN MAINS MODEL

The C10L (shown on bench stand) is probably the smallest mains model in the world. Bit dia. 3/32in., length 7in., weight 1oz. (less flex). Heats in 30 secs.

Brochure No. S10 sent free on request.

Sole proprietors and manufacturers:

**LIGHT SOLDERING DEVELOPMENTS LTD**

28 Sydenham Road, Croydon, Surrey

Phone: CR0Ydon 8589

Grams: Litesold Croydon

# EXPRESS ELECTRONICS

32 SOUTH END CROYDON SURREY

TEL. CR0 9186

**VALVES** NEW TESTED AND GUARANTEED FOR THREE MONTHS

101	4/9-6RE6	7/-12A07	6/9-DH142	8/6-EF91	4/-3PL83	7/-
102	7/6-6BR16	5/9-12AN7	6/9-DH150	10/-EF92	5/6-PY33	10/6
103	6/6-6BR16	5/9-12BR6	8/6-DK91	4/6-EL41	9/6-PY81	8/9
104	6/6-6BR17	8/9-12BH7	10/6-DK96	6/6-EL44	7/-PY82	7/6
105	2/9-6W6	6/6-12KSGT11/-	DL92	5/6-EM85	10/-PY83	7/6
106	6/6-6W7	7/-12Q7GT	7/6-DL94	6/-EX51	7/6-R19	6/6
107	4/-6P12	4/-12SN7	6/-DL96	6/6-RY81	10/-SSA1	9/6
108	6/6-6P12	4/-16A5	9/-EF91	4/-EZ40	5/6-152	7/6
109	5/6-6L16GT	2/-19A05	9/6-ER41	7/6-EZ90	6/-175	7/6
110	6/-6L7GT	7/6-25L6GT	7/6-EF90	8/6-EZ81	6/6-178	5/-
111	4/9-6K7G	5/6-30L1	7/6-ECC81	4/-HYR2	9/6-1142	7/6
112	4/-6K80	6/6-30L1	7/6-ECC82	6/6-KT3C	8/-1BR41	8/6
113	2/9-6Q7G	6/6-35L6GT	7/6-ECC83	6/6-KT96	13/6-1142	9/6
114	5/6-6L16GT	6/-35W4	8/6-ECC84	6/6-N17	5/6-1L41	8/6
115	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
116	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
117	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
118	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
119	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
120	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
121	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
122	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
123	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
124	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
125	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
126	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
127	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
128	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
129	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
130	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
131	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
132	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
133	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
134	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
135	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
136	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
137	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
138	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
139	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
140	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
141	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
142	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
143	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
144	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
145	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
146	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
147	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
148	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
149	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6
150	5/6-6L16GT	7/6-35Z4GT	8/-ECC85	7/6-N18	5/6-1L41	8/6

**ASK FOR RESISTOR AND CAPACITOR COLOUR CODE FREE WITH EVERY PURCHASE**

High Stability Resistors 1W 5% 50Ω to 1M, 8d. Midset Ceramics 500 v., 9d. Coax. Super Quality 1in. 6d. yd. Plugs 9d. Sockets 9d. Silicon H.T. Rects. 250 v. 300 mA 1in. x 1in. 8/6. Contact Cooled 250 v. 50 mA 8/6. 85 mA 8/6. NEW TRANSISTORS BY MULLARD. OC19, OC28, OC66, 25/-; OC44, OC45, 5/-; OC70, 9/-; OC71, 5/-; OC72, 6/-; OC73 Matched pair, 12/-; OC74, OC75, OC78, 7/6; OC81, 6/-; OC81 Matched pair, 12/-; OC870, OC871, 7/6.

## VALVES MATCHED IN PAIRS

EL34 27/6, EL84 15/-, 6N09 15/-, 6V6G 15/-, 6BR6 14/- per pair. Push-Pull O.P. Transformer for above 315Ω 14/6. P. & P. 1/6. 12in. P.M. Speakers 3Ω 24/6. Baker's "Selhurst" 12in. 15Ω 15W Stalwart 80/-, 12in. Stereo Model £8.15.0.

## SETS OF VALVES

DK91, DP91, DAP91, DL92 or DL94...16/6 ECH42, EF41, ERC41, DK96, DE96, DAP96, DL96...28/- EL41, EZ40...37/6 6K5, 6K7, 6Q7, 6V6, 5Z4 or 6X5G...19/6 EF42, EF41, ERC41, 1R5, 1T4, 18V, 384 or 33L...16/6 EL41, CY41...35/-

Postage and packing 6d. Over £1 post free. C.O.D. 4/-



on the type of diode used and the modulation voltage available. The resistor R1 is used to limit the peak inverse voltage, and the preset resistor to bias the diode to the centre of the operating characteristic.

## PARAMETRIC AMPLIFIER

Another device which uses the variable capacitance effect of diodes is the "parametric amplifier". This is a very low noise type of amplifier and is now used fairly extensively for increasing the range of sensitive radio receivers, such as those used in radio telescopes.

Fig. 7 shows a simplified circuit and the device functions as follows. If we charge up a capacitor then pull the plates apart, the voltage across the capacitor will increase as shown by the familiar expression  $Q = C \times V$ , i.e. "Q" is the quantity of electricity stored by the capacitor. So when we halve C (the capacity) the voltage across the capacitor must double. What we do in this circuit is to arrange that the capacity is reduced when the input signal reaches its positive or negative peak, and we do this by increasing the voltage across the diode at the right moment. This driving voltage is supplied by an oscillator running at twice the signal frequency in order that the peaks of the signal are "pumped" every half cycle.

There are many other applications for these diodes, such as voltage controlled oscillators, and filters, pocket-sized transistors, f.m. transmitters and d.c. to a.c. converters, in fact more and more uses are being continually found for them. In the

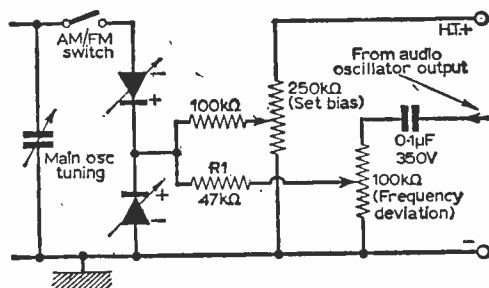


Fig. 6: Circuit for frequency modulating an oscillator.

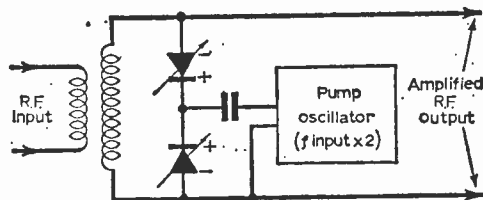


Fig. 7: Simplified circuit of a parametric amplifier.

future we can expect to see more sensitive devices with a greater capacitance range, and it is also to be hoped that the home constructor and experimenter will have a wider range from which to choose.

## THE "PRACTICAL WIRELESS" FILM SHOW

The "Practical Wireless" Film Show which is held annually and to which readers of P.W. are invited, is to be held, as before, at Caxton Hall, Westminster. The date of the Show, which is arranged in collaboration with Mullard Limited, is the 31st January, 1964.

The programme will appeal to all readers of "Practical Wireless" and of especial interest will be the illustrated talk on colour, 625-line and u.h.f. television, which will form the first part of the programme. After a break for refreshments, the programme will continue with a film entitled "Ultrasonics".

Tickets may be obtained free on request from these offices. A stamped addressed envelope must be enclosed with all applications for tickets.

## INTERESTED IN TV?

Then you cannot afford to miss PRACTICAL TELEVISION!

- ★ Regular articles on servicing and fault finding
  - ★ Monthly commentary and hints on TV DX reception
  - ★ Articles on amateur TV transmitting
  - ★ Colour TV explained
- plus other informative articles

## SPECIAL IN JANUARY!

### Building a Flying Spot Scanner

Also, there is still time to build the P.T. Closed Circuit


Television System now being described.

MAKE SURE OF YOUR COPY-JANUARY ISSUE OUT ON DECEMBER 19th-2/-

# A Quality Transistor Amplifier

BY A. J. SHORT

*A Compact,  
Three-Transistor  
Design*

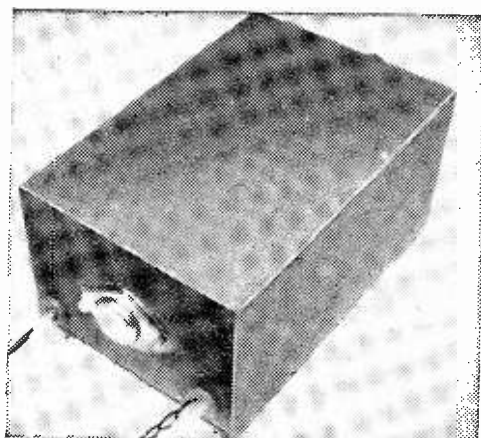

**T**HIS little amplifier is suitable for use with domestic tape recording equipment or with hi-fi record playing equipment. It is preferable to conventional class B transistor amplifiers as it is so simple to make and gives a higher quality of sound reproduction.

Another feature of this amplifier is the extremely wide audio-frequency response, limited only by the characteristics of the output transformer. By using transistors having good high-frequency characteristics the response of the amplifier itself is virtually linear right up to the lower part of the radio-frequency spectrum. This results not only in absence of frequency distortion but also in extremely good transient response. The lack of coupling capacitors eliminates phase distortion. The automatic mismatching between stages resulting from the direct coupling gives a high degree of linearity of transistor characteristic.

## Technical Description

This unusual circuit employs three directly-coupled transistors in the grounded emitter configuration. To achieve satisfactory d.c. levels the first and third transistors are of the usual pnp type, while the middle one is an npn transistor.

Suitable working currents for the first and second transistors in the amplifier are determined by the judicious choice of collector resistors. The overall working currents in the amplifiers are set by adjustments of the base-bias resistor VR2 of the first stage, which is then stabilised from the average collector voltage of the output (or third) transistor.

Overall negative feedback compensates for the characteristics of the output transformer T1.

A thermistor in the base circuit of the first transistor overcompensates for temperature variations and, although this effect is partially offset by the d.c. feedback loop, the overall effect is to prevent use of the amplifier at unsuitable temperatures.

## The Circuit Stage by Stage

The first stage is a high-gain, directly-coupled, grounded emitter a.f. amplifier. The base circuit of this stage is provided with separate a.c. and d.c. negative feedback circuits. The a.c. feedback consists of a fraction of the amplifier output signal developed across R2, via R3, from the loudspeaker speech coil. This voltage is then fed, via the volume control VR1 and C1, to the base of the first transistor Tr1. It will be seen that the feedback voltage appears effectively in series with the input signal, thereby increasing the impedance of the input circuit and reducing the effect of the curvature of the voltage/current characteristic of the first transistor. This, in turn, permits use of a lower value of R1 when the amplifier is used with "voltage" sources such as crystal pick-ups, allowing some reclamation of the loss of gain inherent with negative feedback.

The d.c. feedback circuit R6, C2, VR2 is a supplementary stabilising circuit to the overall temperature control of the thermistor R4. Having a relatively short time constant, about 2sec., it exerts prompt partial control of standing-current variations. The d.c. feedback voltage is developed due to the voltage drop produced by the output stage collector current through the resistance of the primary winding of the output transformer and the a.c. component is removed by the filter circuit R6, C2. The resultant voltage is used to provide the base bias of the first transistor. Increased output stage collector current, causing increased voltage drop across the transformer primary therefore reduces the bias to the first stage, resulting in amplified bias reduction to the output stage and overall stabilisation. Long-term overall amplifier dissipation is controlled by the thermistor R4, which takes into account not only local heating due to amplifier dissipation but also the effect of ambient temperature.



by long-nosed pliers while flying leads are quickly soldered to their ends.

### Setting-up

When construction is complete and all wiring checked the amplifier is ready for setting-up for use. For this purpose a 0-500mA meter will be required, together with a 12V low-consumption lamp.

Before connecting to the power supply ensure that the variable resistor VR2 is set to maximum resistance. If this is not done, damage to the transistors may result when the power supply is connected.

Check the polarity of the power supply and connect the amplifier to the power supply via a

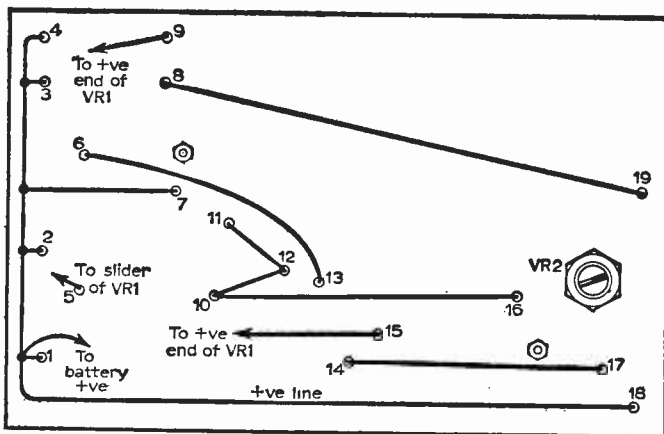


Fig. 3: The wiring on the reverse of the mounting panel.

### COMPONENTS LIST

#### Resistors:

R1 100kΩ (or to suit pick-up)	R5 22kΩ
R2 10Ω	R6 47kΩ
R3 1-5kΩ	R7 1kΩ
R4 Thermistor CZ1 (Brimar)	R8 1kΩ
All ½W carbon, except where otherwise stated	
VR1 500kΩ carbon potentiometer, log	
VR2 1MΩ carbon preset potentiometer, linear	

#### Capacitors:

C1 10μF electrolytic 6V
C2 100μF electrolytic 12V

#### Miscellaneous:

Tr1 OC170, XA123, GET692, MAT121
Tr2 OC139, OC140, 2N647, 2N649
Tr3 OC22
T1 Output transformer (Repenco TT12)
LS Loudspeaker 3Ω
FS1 Fuse 500mA
Steel instrument case 6in. x 4in. x 3in. (Tele-Radio Ltd.)

A signal may now be applied to the amplifier and a trial run made, checking the current drawn from time to time and adjusting VR2 if necessary. It will be necessary to adjust VR2 further only if a change of supply voltage occurs or the amplifier is operated at a greatly different ambient temperature. As the amplifier is intended for domestic use, however, this is not likely to arise. Should it be desired to operate the amplifier over a wide ambient temperature range a permanent 0-500mA meter should be fitted. Should the amplifier be unstable when switched on it will be found to be due to the feedback connections to the loudspeaker speech coil being the wrong way round. Reversal of these connections should clear the fault.

Note that if the output transistor is bolted directly to the steel case the metal of the case will be "live" to the power supply negative. If this should not be desired the power transistor should be insulated from the steel case by use of the mica and plastic washers provided. A small dab of silicone grease between washers, case and transistor will improve thermal conductivity.

12V low-consumption bicycle headlamp bulb and the milliammeter. The bulb will protect the meter and the amplifier should a mistake have been made in wiring the amplifier. When connected and switched on, at this stage, the bulb should not light. If it does light there has been either a mistake in construction or the variable resistor VR2 has not been turned to maximum resistance. If the lamp does not light, short-circuit it or remove it completely from the circuit, reconnecting the supply, and commence gradually to decrease the resistance of VR2. Up to this point the amplifier has not been drawing any appreciable current from the supply and the milliammeter will have been reading "0". As VR2 is gradually decreased in value, however, a point will be reached where the amplifier suddenly begins to draw current. The transition will be quite abrupt and must be watched for. Carefully adjust VR2 until the milliammeter reads 350mA, allowing time after each adjustment for the d.c. stabilising circuit to settle down and take effect.

### HELP FOR HOME BUYERS

When you are buying or selling property it is vitally important to know where you stand as far as the law is concerned. Ignorance or carelessness might cost you hundreds of pounds. There's sure to be a big welcome, then, for the new FREE LEGAL ADVICE SERVICE just announced by Newnes *Property Advertiser and Holiday Guide*. Every week, from now on, this paper will carry questions and answers on such topics as mortgages, insurance, surveying and general legal points. In addition any reader may have his own particular questions answered by a panel of experts simply by filling in a Query Coupon on the Legal Advice Page. Newnes *Property Advertiser and Holiday Guide*, which contains details of thousands of houses, flats, shops, business and holiday addresses, is on sale every Friday, price 4d.

# A Variable POWER SUPPLY for Transistors

*This unit provides a d.c. output adjustable from 0 to 26.7V in steps of 0.15V. Its maximum continuous current rating is 1.2A.*

By R. Leyland

WHEN powered from self-contained batteries, transistorised apparatus is fully portable but, on the other hand, a supply derived from the mains has very low running costs despite the higher initial expenditure on the power unit.

Dry batteries cannot supply large currents for long periods and are therefore inadequate when power output stages are to be worked, especially the class A type required for quality reproduction. For these it is necessary to employ either a car battery or a directly derived mains supply. The mains voltage is usually dependable and does not fall with the passage of time as in the case of batteries.

The power unit to be described (the circuit is shown in Fig. 1) provides up to 24V, which is probably as high a voltage as could be required with transistors—at least with types so far available. It has a maximum continuous current rating of 1.2A (at 14V). The rectifiers can deliver up to 1.5A but cannot do so for more than half an hour without reaching ambient temperatures too high for such a current rating, whereas at 1.2A the power unit can work continuously, reaching a

maximum temperature of about 50 deg. C in three hours.

## Silicon Rectifiers

The silicon rectifiers, Ediswan type XU612, have ratings similar to S.T.C. type RS210AF and to G.E.C. type SX631. However, type SX631 have provision for 6B.A. stud mounting, while the XU612 and the RS210AF are wire-ended only and cannot be fitted to heat sinks.

In a compact power unit the proximity of the transformer and choke raises the ambient temperature and this limits the current that can be drawn continuously without exceeding the rating of the rectifiers. Although silicon rectifiers can be used at 100 deg. C their current rating is reduced considerably as compared with that at lower temperatures and, of course, the temperature has to be kept much lower if an electrolytic capacitor is to be included.

The time lag of three hours in warming up to the maximum temperature is accounted for by the large thermal capacity of the transformer and choke.

## The Transformer

A less elaborate transformer than the one here proposed would usually suffice but a series of secondary windings offers a more convenient and efficient method of controlling the output voltage than dropper resistors and raises the temperature less.

The provision of both coarse and fine windings enables close adjustment of the output voltage to be made. The windings are brought out to connector strips which extend along both sides of the power unit: 12-way for the principal windings and 15-way for the fine windings. This allows the r.m.s. input to the rectifiers to be adjusted from zero up to 26.7V in steps of 0.15V.

The use of switches for selecting the windings was not considered advisable. These would require to be of a break-before-make type to avoid short-circuiting sections of the winding but, even so, sparking would probably cause rapid deterioration of the contacts. As the output voltages are low there is no objection to the use of connector strips along the sides of the box with flying leads for voltage selection. The connector strips are adequately insulated for much higher voltages than those encountered here.

Laminations with a window large enough to ensure ample winding space are required because a large number of windings to take up more room than straightforward calculation would suggest (see Fig. 2). The size of stack is chosen to give a cross-section large enough to keep the turns per volt to a reasonable number.

## Primary Turns

The primary was wound with 1,560 turns of 35s.w.g. double silk covered wire for a nominal

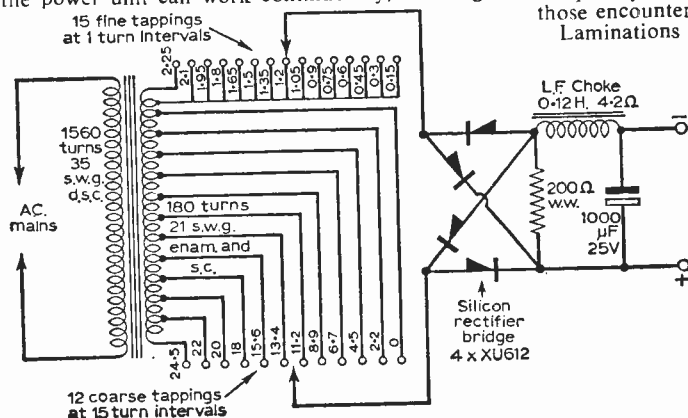


Fig. 1: The circuit of the unit.

mains voltage of 240.

At first the actual mains voltage appeared less, but this was because allowance had not been made for the current (about 0.3A) taken by a large a.c. voltmeter used in measuring the secondary voltages. The unloaded a.c. voltages of the secondary windings are therefore about 3% higher than the values that have been marked on them. This is not a large difference but it brings a close agreement between the voltage ratios and turns ratios.

As the maximum open-circuit output voltage (measured by a d.c. voltmeter) has been adjusted in this circuit by means of a resistance to be approximately the maximum working voltage of the electrolytic capacitor, to obtain the same results on a different mains voltage would simply require proportionate change in the number of primary turns. The number of turns per volt is 6.5. Thus to obtain the same results on 250V would require 1.625 turns.

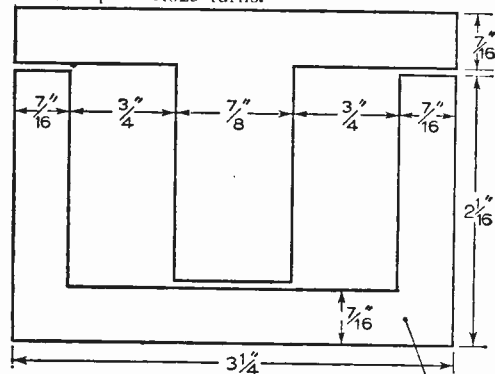


Fig. 2: Details of the laminations of the mains transformer.

It is necessary to check that the highest direct voltage obtained across the electrolytic capacitor does not exceed 25V with the 200Ω resistor in circuit. Should higher voltages be obtained, the secondary windings giving these voltages would have to be disconnected, insulated and left unused.

### Winding the Transformer

The transformer bobbin, made of 1/16 in. insulating material and provided with rows of holes in the cheeks to bring out the 2.2V windings, was wound by fitting into it a wooden block drilled in the centre for a 1/4 in. shaft. This was retained between collars on the shaft. A screw inserted in the block and tied to a screw on one of the collars prevented the bobbin from slipping on the shaft.

The 1/4 in. shaft was fitted into bearings mounted on two supports on a base-board. A handle was fixed on one end and a short flexible drive at the other connected to a turns counter through a universal joint to give the maximum freedom from alignment difficulties.

With this arrangement the transformer bobbin could be wound quite rapidly. Flexible plastic-covered wire leads were used to the mains primary winding with the soldered joints well insulated by a double thickness of Empire cloth. Plastic

insulating tape should not be used for such applications as it is easily pierced by any irregularity in the solder.

Three thicknesses of Empire cloth separated the primary and the secondary. The secondary consisted of 180 turns of 21s.w.g. enamelled and single cotton covered wire, wax-dipped before winding to prevent fraying of the cotton. Double cotton covered wire takes up less than 10% more space and could possibly have been used instead. Double silk covered wire of the same gauge could certainly have been used as it takes up less room than E. and S.C. It, too, would preferably be waxed before winding to ensure undamaged insulation at bends in the wire. Enamelled wire without additional protection would require interleaving and special care in insulating the windings. The 180-turn secondary has a resistance of 1.4Ω.

### Secondary Tappings

Tappings extending 6 in. outside the transformer were made at half-layer intervals (15 turns) by doubling the wire. The second and third windings were taken out at the opposite side from the start of the winding, then the next two at the other (first) side and so on. Pieces of Empire cloth were applied as insulation above and below each loop where it traversed the winding and at the bends in the wire. The resulting bulge occurs on one of the exposed sides of the winding and does not affect the winding space set by the size of the window of the transformer laminations.

The outermost 15 turns were tapped at every turn, the loops being twisted to keep them from coming apart and insulated with small pieces of insulating tape, doubled and pressed around the place at which the tapping is made. When the secondary had been completed it was bound with insulation tape to secure it firmly. The laminations were then inserted from alternate sides and the entire transformer was wax-dipped to improve the insulation and exclude moisture. This seemed worth while, although under continuous working at maximum loading the transformer heats enough for some of the wax to run out.

Sleeving was used outside the transformer where necessary to separate the windings. This requires to be of at least 2mm to allow the double wire to pass through it and a limp type of sleeving was found suitable.

In arranging the leads to the connector strips most of them required to be shortened slightly. The waxed cotton covering was pushed back and the enamel scraped off. The ends were then twisted together and soldered before insertion into the connector and screwing down the grub screw. As the windings are loops the current of the winding has to pass through a succession of soldered joints, so it was necessary to ensure a low-resistance junction between the wires at each connector position.

### A.C. Ripple Reduction

A power supply delivering a large current at low voltage has a tendency to give too much a.c. ripple, comparing very unfavourably with batteries as regards the background hum produced. Filtering poses a problem because the resistance of any series smoothing component has to be small to avoid a large voltage drop with correspondingly



# LASKY'S RADIO

## THE FINEST RANGE OF TRANSISTOR RECEIVERS

we consider our construction parcels to be the finest value on the home constructor market. If on receipt you feel not competent to build the set, you may return it as received within 7 days, when the sum paid will be refunded less postage.



### The SKYROVER

Controls: Waveband Selector, Volume Control with on/off switch, Tuning Control. In plastic cabinet, size 10 x 6 1/2 x 3 1/2 in. with metal trim and carrying handle.

Can be built for

**£10.19.6**

Post & Pkg. 5/- extra.

Data for each receiver 2/6 extra. Refunded if you purchase the parcel. Four U2 batteries, 2/8 extra. Four Leak-Proof batteries, 3/4 extra. All Components Available Separately.

## LASKY'S FIRST AGAIN!

Now offer to the Home Constructor - full short wave coverage

## The SKYROVER and the SKYROVER DE LUXE



### The SKYROVER de luxe

Tone Control Circuit is incorporated, with separate Tone Control in addition to Volume Control, Tuning Control and Waveband Selector. In a wood cabinet, size 11 1/2 x 6 1/2 x 3 1/2 in. covered with a washable material, with plastic trim and carrying handle. Also car aerial socket fitted.

Can be built for **£12.19.6** P. & P. 5/- extra

### "SPRITE"

Can be built for

**79/6**

P. & P. 3/6 extra.

★ Six-Transistor Superhet Miniature Personal Pocket Radio. ★ Long and Medium wavebands. ★ Ferrite Rod aerial. ★ I.F. Frequency 470 Kc/s. ★ 3in. Speaker. ★ Printed circuit 2 1/2 x 2 1/2 in. ★ Slow Motion Drive. ★ In Plastic Case. Size 4 x 2 1/2 x 1 1/2 in. In order to ensure perfect results, the SPRITE is supplied to you with R.F. and I.F. stages. Driver and Output stages ready built with all components mounted on the printed circuit. The SPRITE pre-assembled, plus cabinet, speaker and all components for final construction, can be built for **79/6** P. & P. 3/6 extra. Data and instructions separately 2/6. Refunded if parcel is purchased. *Real calf leather case, wrist strap, personal earpiece and case for earphone and battery 12/6 the lot extra. Make no mistake this is a SUPERHET receiver of genuine commercial quality. It is not a regenerative circuit.*



### IDEAL PRESENTS BOY'S TRANSISTOR RADIO

Ready built, 2 transistor pocket radio, in attractive plastic case, size only 4 x 2 1/2 x 1 1/2 in. Fitted with 24in. loudspeaker. Socket for personal earpiece & telescopic aerial. Works from single PP3 type battery. Fully tunable over full medium waveband. Supplied complete with earpiece, telescopic aerial, carrying purse and 9 volt battery. Ideal Birthday or Christmas Present.

LASKY'S PRICE **45/-** with all accessories P. & P. 2/6.



6 TRANSISTOR POCKET RADIO fully built, 4 x 2 1/2 x 1 1/2 in. with 24in. speaker. Uses single PP3 type battery. Supplied complete with personal earpiece and leather case. Tunable over full medium waveband.

LASKY'S PRICE **79/6** P. & P. 2/6. Complete with all accessories.

### "REALISTIC" Seven

★ 7-transistor Superhet. ★ 350 milliwatt output into 4in. high flux speaker. ★ All components mounted on a single printed circuit board, size 5 1/2 x 5 1/2 in. In one complete assembly. ★ Plastic cabinet with carrying handle, size 7 x 10 x 3 1/2 in. in Red/Grey, Blue/Grey or all Grey. ★ Easy to read Dial. ★ External socket for car aerial. ★ I.F. frequency 470 Kc/s. ★ Ferrite rod internal aerial. Operates from PP9 or similar battery. ★ Full comprehensive data supplied with each receiver. ★ A coils and I.F.'s etc. fully wound ready for immediate assembly.



An Outstanding Receiver. LASKY'S PRICE for the complete parcel including Transistors, Cabinet, Speaker, etc., and Full Construction Data. Can be built for **£5.19.6** P. & P. 4/6. PP9 Batt. 3/6. Data and instructions separately 2/6. Refunded if you purchase the parcel.

### PRIVILEGE PARCELS

A "Privilege Parcel" allows you to purchase the Audio System of your choice at a worth while cash saving. Some examples are listed below, but we shall be pleased to quote our "Privilege Parcel" Prices for any selection of equipment of your own choice. Send us details of your requirements.

Tudor Stereo Amplifier	£15.0.0	Collaro Studio Tape Deck, 1-track model	£10.10.0	Collaro Studio Tape Deck, 1-track model	£13.19.6
Tudor Stereo Amp	£15.0.0	Lasky's Tape Amplifier	£3.19.6	Martin Tape Amplifier, 1-track model	£12.12.0
Connoisseur Craftsman, 2-speed transcription player	£18.6.6	Ptable Case	£3.15.0	Portable Case with Speaker	£5.5.0
Decca FFSS Stereo Pick-up	£18.18.0	2 x Sharon Loudspeaker systems	£19.19.0		
<b>Total £50.4.6</b>		<b>Total £47.8.6</b>		<b>Total £24.0.0</b>	

"Privilege Parcel" Price: £47.10.0.

"Privilege Parcel" Price: £45.0.0.

"Privilege Parcel" Price: £22.10.0.

"Privilege Parcel" Price: £30.0.0.

Carriage and Packing on all the above parcels, 10/6 extra.

### REALISTIC Seven DELUXE

By popular request a De Luxe version of the well-proven Realistic "Seven" now available. With the same electrical specification as standard model—PLUS A SUPERIOR WOOD CABINET IN CONTEMPORARY STYLING, covered in attractive washable material, with super-chrome trim and carrying handle. Also a full vision circular dial, externally mounted to further enhance the pleasant styling. ALL FOR ONLY **£1 EXTRA.** P. & P. as for Std. model

207 EDGWARE ROAD, LONDON, W.2. 33 TOTTENHAM COURT ROAD, W.1.  
Near Praed St. PADDINGTON 3271/2 Near Stn., Goudge St. MUSEUM 2605  
BOTH OPEN ALL DAY SAT. Early Closing Thurs. Mail Orders to Dept. P.W., Edgware Rd.

152/3 FLEET STREET, LONDON, E.C.4.  
Telephone: Fleet Street 2833.  
Open all day Thursday. Early closing Sat.



A sustained demand for the Mullard "Reference Manual of Transistor Circuits" has led to a further printing of the second edition. Over 35,000 copies of this important reference work have been sold to technicians, service engineers, junior designers and electronics students. Whatever your interest in transistor circuitry you will find this Manual a proved and valuable source of reference—comprising 300 pages, with 241 diagrams, and describing more than 60 circuits.


Get a copy of the Mullard "Reference Manual of Transistor Circuits" from your local Radio Dealer or direct from Mullard Ltd. (Postage and packing, 1s. extra.) Overseas readers should enquire at their local Mullard Agents.

Published by—

UK Price 12/6



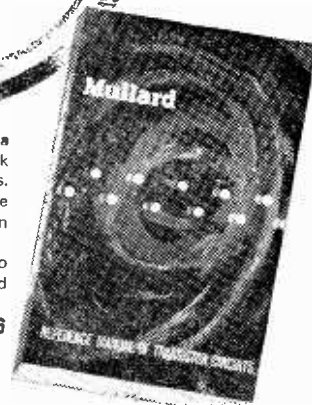MULLARD LIMITED · DEPT. B  
MULLARD HOUSE · TORRINGTON PLACE · LONDON · W.C.1.



MVM/1574

#### MULTI-RANGE TESTMETERS

Caby M1 .. .. .	£2 14 0
Caby B20 .. .. .	£6 10 0
Eagle EP10K .. .. .	£4 12 6
Model 200H .. .. .	£5 5 0
Eagle EP50K .. .. .	£9 19 6
Caby A10 .. .. .	£4 17 6
Taylor 127A .. .. .	£10 0 0
Eagle TK20A .. .. .	£2 9 6
Eagle EP30K .. .. .	£6 19 6

**Portable Tape Recorder**, fully transistorised, battery operated, dual track, complete with all accessories. Of the finest quality construction. A 4-transistor plus diode, push-pull amplifier, built-in loud-speaker, £9.19.6.

**Stereo Amplifier**, beautifully styled, ultra compact, 4 watts per channel, wide range tone and volume controls. £9.10.0.

**Stereo Amplifier**, 7.5 watts per channel, accommodates stereo magnetic cartridges as well as crystal ceramic cartridges, tuner, tape mic and auxiliary inputs, bass and treble controls. £16.10.0.

**Radio Tuner**, suitable for use with amplifiers and tape recorders, complete with standard Jack plug, covers medium wave-band, with instructions, 29/- each.

**Transistor Intercom.**, suitable as a baby alarm or for communications in home, offices, shops, etc., transistorised, a 2-way buzzer-call system, beautifully styled in moulded plastic cases, complete with battery, connecting wire, instructions, etc., £4.4.0.

**American Recording Tape**, standard play 5in. spool, 600ft., 9/6; 5in. spool, 850ft., 11/9; 7in. spool, 1200ft., 14/9; long play 5in. spool, 200ft., 12/6; 5in. spool, 1200ft., 15/-; 7in. spool, 1800ft., 19/6.

#### ADASTRA 3-3 AMPLIFIER

Specification: Controls—Volume, Treble, Bass with on/off. Valves—E230 rectifier, ECL86 amplifier and output. Output power—3 watts at 3.5 ohms impedance. Input sensitivity—200 millivolts. Frequency response—75-20,000 c/s. Hum and noise—70 dB. Feedback—10 dB. For 200-250 volts A.C. 50 c/s. Well finished in blue with a smart panel with gold markings. Soundedly made of good components and performs exceptionally well for the price, £4.19.6.

#### MICROPHONES

Acos Mic 39/1 .. .. .	£1 12 6
Floor Stand Adaptor .. .. .	12 6
Acos Mic 45 .. .. .	19 6
Table Stand .. .. .	12 6
Mic 100C .. .. .	£1 19 6
Table Stand .. .. .	7 6
Acos Mic 40 .. .. .	19 6
BM3 Microphone .. .. .	£2 5 0
Floor Stands MS4—3 sections .. .. .	£2 19 6
Table Top Stand .. .. .	8 0

#### GRAMOPHONE UNITS

BSR TU12 unit, with Mono TC8H cartridge, £5.19.6.	
BSR GU7 unit, with TC8M or TC8H Cartridge, Mono, £4.15.0.	
BSR GU7 unit, with TC8S cartridge, Stereo, £5.5.0.	
Garrard Autoslim, automatic, with GC8 Mono cartridge, £7.15.0.	
Garrard Autoslim, automatic, with EV26 Stereo cartridge, £8.10.0.	
Garrard Autoslim, de luxe, with GC8 Mono Cartridge, £11.5.0.	
Garrard Autoslim de luxe, with EV26 Stereo Cartridge, £12.0.0.	
BSR Monarch UA14, with TC8 Mono Cartridge, £6.6.0.	
BSR Monarch UA14, with TC8S Stereo Cartridge, £7.7.0.	
BSR Monarch UA16, with TC8 Mono Cartridge, £6.19.6.	
BSR Monarch UA16, with TC8S Stereo Cartridge, £7.19.6.	

#### TRANSISTORS AND DIODES

AC107 14/6	OC16W 35/-	2 x OC72 18/-
AD140 25/-	OC19 25/-	OC74 8/-
AF102 27/6	OC26 25/-	OC75 8/-
AF114 11/-	OC35 15/6	OC78 8/-
AF115 10/6	OC42 8/6	OC81 5/9
AF116 10/-	OC44 5/9	OC81M 5/9
AF117 9/6	OC44M 5/-	OC82 10/-
AF118 20/-	OC45 5/9	OC83 6/-
AF119 10/-	OC45M 5/-	OC139 9/-
AF125 10/6	OC70 6/6	OC170 9/6
AF126 10/-	OC71 4/3	OC171 10/6
AF127 9/6	OC72 6/-	OAZ207 8/-

New Mazda AC154 equivalent to OC81 5/-

#### SETS OF TRANSISTORS

Set No. 1, comprising OCC44, 2 x OC45, OC81 Driver, matched pair OC81, Miniatures .. .. 20/- per set

Set No. 2, comprising OC81 Driver, matched pair OC81 .. 12/6 per set

#### VALVES

DK96 7/9	PCC84 7/6	PCL82 9/-
DAP6 6/9	PL82 7/6	6V6G 4/-
DF96 6/9	PY83 7/6	6K7G 2/-
DL96 6/9	UABC80 7/6	6AM6 3/6
ECC81 5/-	UAF42 7/6	EB91 3/-
ECC82 5/6	UBF80 7/6	1R5 5/3
ECC83 6/-	UCH42 7/6	1T4 3/6
ECC84 7/6	UL41 7/6	1S5 4/6
ECC85 7/6	EY61 8/-	354 5/6
ECH81 7/6	PL81 8/6	6X8G 4/9
EB41 7/6	PL36 9/6	6L6G 7/6
ECL80 7/6	PCL83 9/6	6Q7G 5/6
PCF80 7/6	PCF82 9/6	6X5G 5/-



**ALPHA**

RADIO SUPPLY CO.

103 LEEDS TERRACE

WINTOUN STREET

LEEDS 7

TERMS: Cash with Order or C.O.D. Postage and Packing charges extra. Single valves 9d. Minimum Parcel Post charges 2/-. Please include sufficient postage with your order. Minimum C.O.D. fees and postage 3/6. These Postal Rates apply to U.K. only. For full terms of business see inside cover of catalogue. Personal shoppers 9 a.m. to 5 p.m. Mon. to Friday, Saturday 10 a.m. to 1 p.m.

high power loss (which also adds to the temperature of the power unit).

Apart from decoupling individual transistor stages that do not require large currents, the only satisfactory method of reducing ripple is to include a low-resistance choke.

In this power unit the choke has an inductance of 0.12H with 1A flowing and a d.c. resistance of 4.2Ω. Although the inductance seems small its reactance is 75Ω at 100c/s—the ripple frequency from the full-wave rectifier bridge.

Connected between the output terminals is a 1mF capacitor (usually marked 1,000μF) which has a reactance of 1.6Ω at 100c/s, so the ripple will be attenuated about 46 times to a level which, although not totally imperceptible in a loud-speaker, should serve for working an output stage.

Earlier stages will, however, require additional decoupling, which may not be present in the simpler types of battery receiver where its only function would be to prevent feedback via the battery impedance and not to stop ripple—which does not occur with a battery supply.

Ripple will be greatest when the maximum a.c. input is applied to the rectifiers and it also varies with the load current due to variation in the choke inductance, which is about twice as high at small output currents.

With the entire secondary in circuit the ripple at the output terminals when drawing 1.2A at 14V is 210mV r.m.s. When the load is disconnected the output voltage rises to 24V but the r.m.s. ripple decreases to 90mV.

A reservoir capacitor of about 1,000μF, if added to the circuit, gives little improvement except at small output currents. The ripple voltage at full load is reduced only slightly, so a large ripple current flows through the capacitor. A surge resistor is necessary in series and this becomes quite hot, requiring to be of substantial wattage.

When a large direct current is flowing the reservoir capacitor is unable to charge sufficiently to raise the voltage and so to decrease the ripple (with a reduction in the conducting period of the rectifiers). To do this would apparently require at least 10mF (at 25V working), which is ruled out on the grounds of bulk and because of the large current pulses that would pass in the rectifiers. At least as much ripple reduction would be obtained by connecting such a capacitance across the output terminals.

There is also little improvement to be obtained by tuning the choke with electrolytic capacitors. For example, a 16μF capacitor halved the ripple at full load but slightly increased it at no load. It also distorted the ripple waveform by increasing the higher harmonics. Capacitors of 8μF and 25μF across the choke were even less beneficial.

### Details of the Choke

The choke winding contains 400 turns of double silk covered wire of 25s.w.g.

The laminations, of the E and I pattern, are of the type shown in Fig. 3. The gap between the E and I laminations (which occurs as a double gap in the magnetic circuit) was adjusted, using slips of paper. These were cut from a page of a spiral-bound notebook and six pieces gave the optimum gap of 0.02in. As the graph in Fig. 4 shows, any size of gap is better than none. Complete removal

of the I laminations gave an inductance of about 0.05H as compared with 0.12H at the optimum gap.

When completed the choke also was wax-dipped. The effect of this on the gapping paper was assumed negligible and the values of output ripple that have already been stated were measured subsequent to this wax impregnation.

The resistance of the choke, 4.2Ω, is not entirely a disadvantage, for it gives the rectifiers some protection against accidental short-circuits of the output, provided that these are only momentary. For this reason it was not considered necessary to add a fuse in the output circuit.

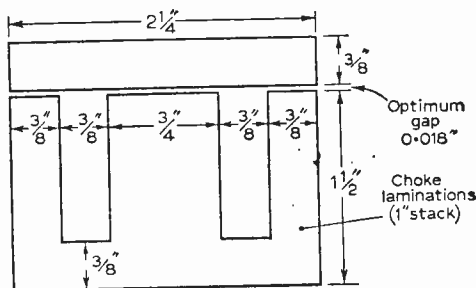


Fig. 3: The choke lamination dimensions.

The 1,000μF, 25V working capacitor connected between the output terminals and positioned over the choke is a miniature type measuring 1 1/2 in. x 1 in. diameter. It is unnecessary to shorten its leads, but sleeving should be used on these.

### Rectifier Assembly

The silicon junction rectifiers can be seen to have one axial lead in electrical connection with the metal case at the end with the circular flange. This lead is of + polarity, corresponding to the cathode of a thermionic diode.

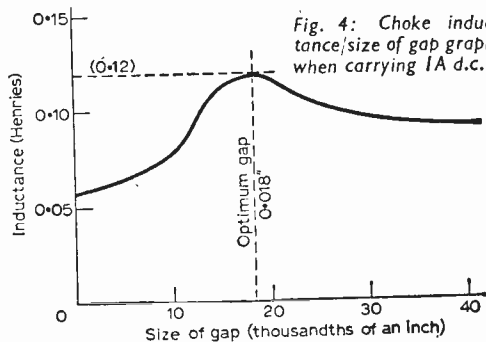


Fig. 4: Choke inductance/size of gap graph, when carrying 1A d.c.

The separation between the rectifiers must be sufficient to ensure that contact cannot occur between them. A suitable tag-board of the usual type was not at hand, so an eyeletted panel was made with 20s.w.g. tinned copper wire linking pairs of eyelets (see Fig. 5) and providing short projections on to which the leads of the rectifiers were hooked and soldered. The lead wires should not be bent close to the seal and are held with pliers during the soldering to keep the heat from reaching the rectifier.

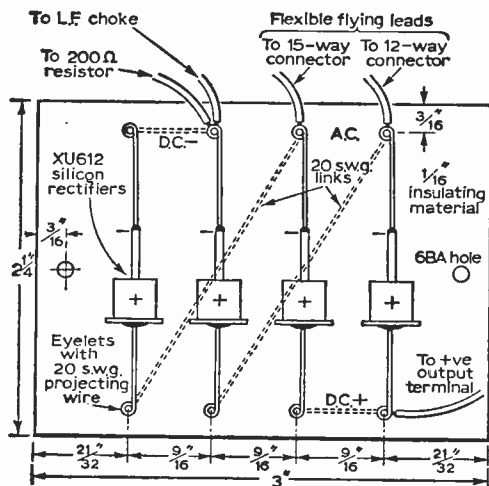


Fig. 5: The rectifier bridge assembly.

The 200Ω resistor is connected on the input side of the choke because in this position it helps to safeguard the rectifiers against any voltage surges, and comes in parallel with the reverse resistances of the rectifiers during their non-conducting half-cycles, thus protecting them against surges via the mains. This resistor should therefore be considered an essential rather than an auxiliary component.

It is anticipated that the power unit will normally be supplying voltages well below the maximum. Where only a 9V supply is needed the much higher voltages available could represent a source of risk to the apparatus being supplied, but the tappings have been marked clearly and external meters would normally be used in adjusting the voltage to circuits under test, beginning at a lower voltage and gradually adjusting upwards until the correct output voltage was obtained on load.

Silicon rectifiers produce less heat as they are much more efficient than selenium rectifiers and drop far less voltage. Losses in the other components, however, make the overall efficiency

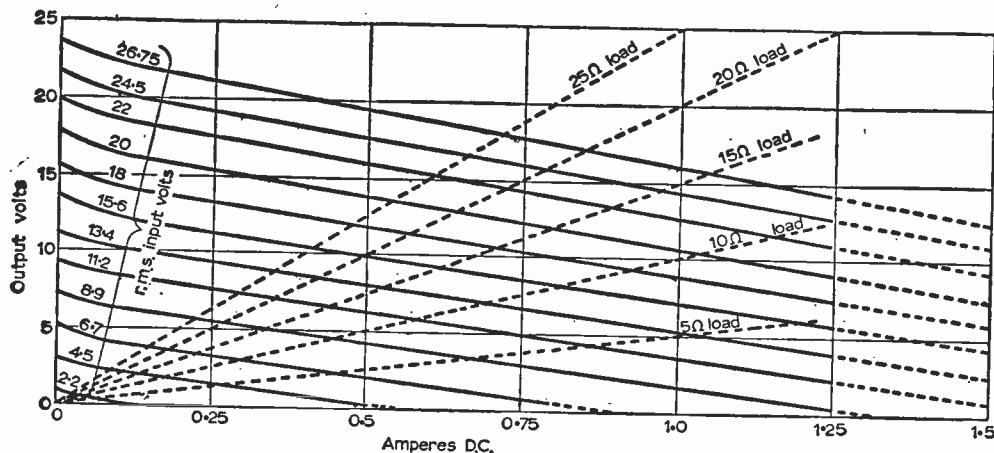


Fig. 6: Regulation curves of external d.c. output at different a.c. input voltages. (There is also an internal resistance of 200Ω taking an additional current.)

All four rectifiers were mounted vertically with the + end downwards, and the tag-board with backing piece is bolted on the inside of the box under the 15-way connector.

#### The Wire-wound Resistor

A 200Ω wire-wound resistor is connected across the output of the rectifiers. The purpose of this resistor is to prevent the output voltage from rising to an excessive value on no load. It ensures that the open-circuit output voltage is not too high for the electrolytic capacitor, which has a working voltage of 25V. There is a steep rise in the regulation curve at small direct currents and in the absence of this resistor over 30V would appear across the output (using the entire secondary) at zero direct current as against a maximum of 24V with the resistor included. It dissipates up to 3W and is positioned at the transformer end of the power unit.

of the supply much lower. The power unit consumes 35W when supplying an output of 14V at 1.1A, which implies an overall efficiency of 44%. The power losses consist of 5.1W in the choke and 1.7W in the 200Ω resistor. There are also those of the transformer and rectifiers whose combined efficiency at this output is 63%.

#### Output Characteristics

Except for currents of below 100mA, the source resistance of the supply is constant with loading and has a value of 5 to 7Ω according to the a.c. input voltage. The source resistance rises slightly with a higher a.c. input as more of the secondary is brought into circuit, corresponding to a slight increase in the slope of the upper regulation curves of Fig. 6, which are not quite parallel.

The a.c. input voltage from the transformer secondary falls slightly with increased loading due to the resistance of the transformer windings.

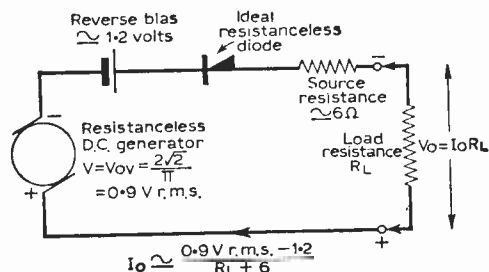


Fig. 7: Equivalent circuit of d.c. output of power supply.

With the entire secondary in circuit the input drops about 2V r.m.s. for an ampere of direct current in the external load.

The d.c. source resistance determines the fall in direct voltage for a given increase of direct current. Thus an increase of half an ampere in the current drawn will cause the output voltage to drop by about 3V. Although not exactly equal to the a.c. source resistance of the supply the d.c. value probably will not differ appreciably from it up to about 25c/s, where the 1,000 $\mu$ F capacitor begins to take over, making the output impedance capacitive with a reactance of only 1.6 $\Omega$  at 100c/s.

A set of load lines have also been drawn on the regulation curves of Fig. 6. It is thus easy to determine the approximate output voltage and current for a given value of load resistance and input tapping.

The spacing of the regulation curves shows that each additional 2.2V step of a.c. input voltage gives just under 2V increase of direct volts output

(for the same current), but there is the usual non-linearity with inputs of about 1V or less which has an effect somewhat like a small reverse bias voltage on an ideal resistanceless diode.

It is possible to draw an approximate equivalent circuit for the d.c. output as in Fig. 7. This is based upon the regulation curves.

### Dimensions

The dimensions of the power unit (6 $\frac{1}{2}$ in. x 3 $\frac{1}{2}$ in. x 3 $\frac{1}{2}$ in.) are the minimum that will accommodate the transformer and choke and it was necessary to check that the components to be used would in fact fit into this limited space, especially as the bunching of the tappings tended to increase the room taken by the transformer. The arrangement of components and wiring is shown in Fig. 8.

A ready-made pressed-steel box of the required size for the power unit was not available, so a box was specially constructed from 18s.w.g. aluminium. Aluminium of this thickness is easily fretsawed and the narrow flanges required can be accurately formed by stages in a vice. Hammering should be avoided in this process to avoid distorting the metal, but if some proves necessary to flatten a bulge a piece of wood can be interposed to avoid damage. The line of the flange is set just at the top of the vice (with the flange gripped in the vice). The flange then turns out a little deeper while the dimension of the main part is kept close to the original measurement.

### Details of the Construction

The top panel, which bridges the gap between the connector strips, is a piece of hardboard as this is less likely to damage the tappings on removal and replacement, Fig. 9(J).

—continued on page 835

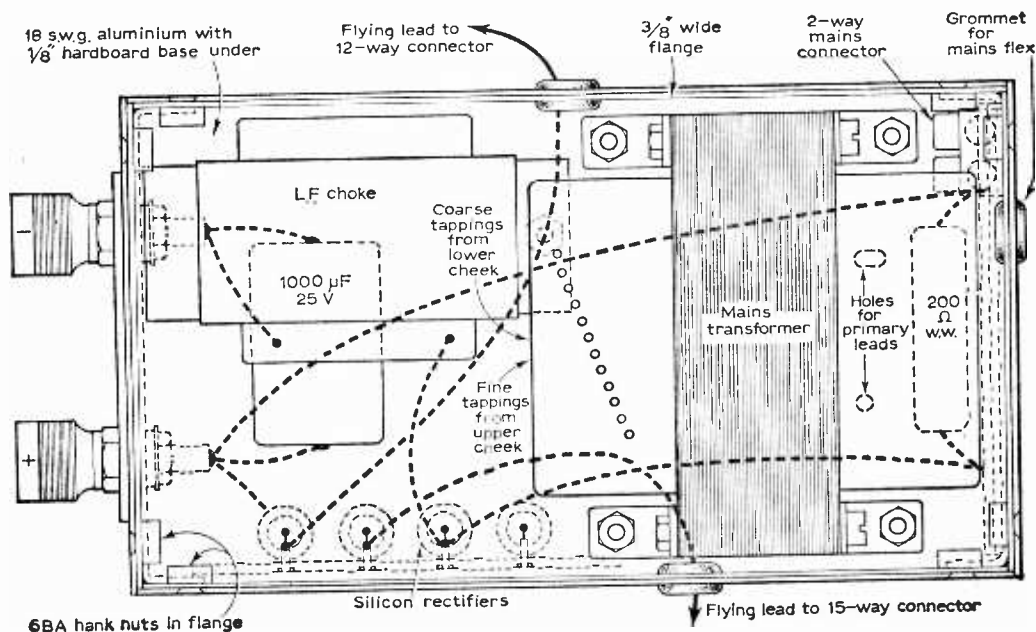


Fig. 8: The arrangement of the power unit.

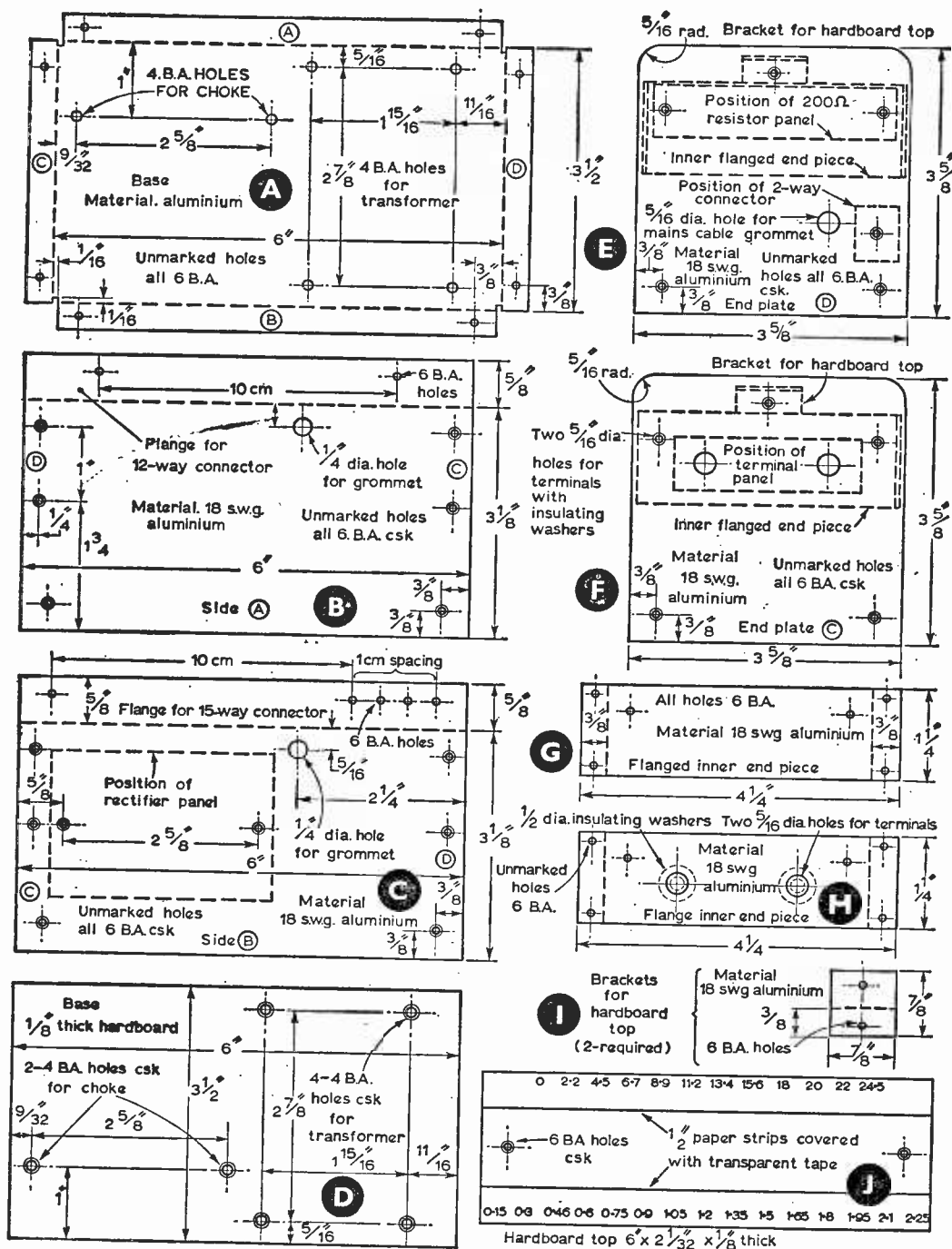


Fig. 9: Details and dimensions of the component parts of the power supply case.



—continued from page 833

Another piece of hardboard, Fig. 9(D), is used under the 18s.w.g. bottom of the box as the latter is too thin to take the 4B.A. countersunk screws which secure the transformer and choke. The rough side of the hardboard base is downwards to provide a non-slip surface which, with the 5½lb weight of the power unit upon it, makes it less likely to be pushed out of position.

The bottom of the box is a flanged tray of 18s.w.g. aluminium measuring 6in. x 3½in. and with ½in. flanges as shown in Fig. 9(A).

The sides of the box measure 6in. x 3½in. and have ½in. flanges which form ledges supporting the connector strips. Refer to Fig. 9(B) and (C).

Flanging is carried out before drilling. Holes for 6B.A. screws are drilled first in the sides, which are then used as templates for the 6B.A. holes in the flanges. After temporarily fitting the sides, holes are drilled in the ends and similarly transferred to the flanges and inner end pieces, Fig. 9(G) and (H). The end plates are shown in Fig. 9(E) and (F). These plates are without flanges to give the box neater corners and are secured by the flanged end pieces which fit inside.

The top, of ½in. hardboard, rests on the edges of the connector strips on each side and fastens at each end by a 6B.A. countersunk screw to a small bracket on the end plate. See Fig. 9(I). The use of countersunk screws throughout, although not essential except in the hardboard base, gives the box a much better appearance, but 18s.w.g. is rather thin and in countersinking the 6B.A. holes it is advisable not to go too deeply as the screw sinks in further than intended when it is tightened. A 60 deg. countersink drill appears to be best for countersinking holes for the 6B.A. screws but a 90 deg. countersink drill is more suitable for the 4B.A. holes in the base.

Final assembly of the power unit is greatly facilitated if 6B.A. hank nuts are fitted to all the flanges. Most of the interior of the box becomes inaccessible when the sides and ends are in position and the usual type of nut would be very awkward to get into position. Where a hank nut is to be fixed the 6B.A. hole previously made in the flange is drilled through with a ⅜in. drill and then lightly countersunk. The hank nut, which is really a sort of combined nut and rivet, is easily riveted into this hole by hammering.

The box was painted with grey plastic enamel, which it is thought should give better cooling than the polished aluminium left unpainted, although probably less efficient than a coating of black crackle paint.

### Connector Strips

The connector strips are of the more compact type with 1cm spacing. The 12-way strip on one side does not extend the full length of the box and leaves a small aperture at each end for ventilation.

The 15-way connector strip that fully occupies the other side consists of a 12-way strip with a three-way portion added at one end. The connectors are retained in position by 6B.A. bolts ½in. long, inserted from the top into hank nuts in the flanges, with a washer between the head of each nut and the connector strip. Countersunk bolts should not be used here as they would break the connector strips when tightened.

It is necessary to arrange the tappings in sequence to give an ascending series of voltages. The r.m.s. values are marked with Indian ink at 1cm intervals on ¼in. strips of paper which are then covered with Sellotape for protection and glued along the edges of the top panel beside the multi-way connectors.

The ends of the flying leads are doubled and soldered to avoid breaking of the strands.

To guard against interchange of the red and black tops of the output terminals a small disc of paper with a + sign in red was stuck on beside the positive terminal.

### Mains Connection

The lack of a switch in the primary circuit might be felt to be a disadvantage. A small snap-action switch could be fitted at the transformer end on the opposite side from the two-way connector. It is advisable to wrap insulating tape around the switch tags to ensure that if the switch should loosen no contact can be made with the metal box.

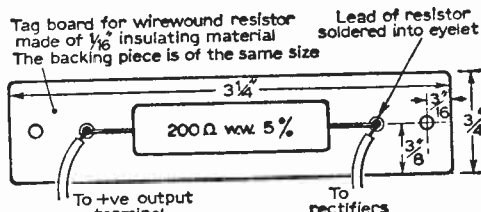


Fig. 10: The tag board mount for the wire-wound resistor.

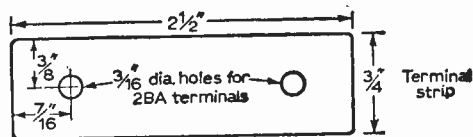


Fig. 11: The terminal strip.

The plastic insulation of the wires entering the connector block must be carried right into the connector. No bare conductors should show in the primary circuit. With a three-pin plug and three-wire flex (red for live, black neutral and green to the large earthing pin) the green wire would be connected to a soldering tag under one of the nuts securing the transformer. In a two-wire system additional insulation is recommended, e.g. insulating tape over the plastic covering and adjacent strips of plastic insulating tape covering adjacent metal surfaces.

Before use, an ohmmeter check is made to ensure that the insulation between the metal case and internal circuits is satisfactory. The wiring of the power unit is insulated from the metal box on both the primary and secondary sides. It is also important to check the wiring before connection to the mains. The fault most likely to damage the rectifiers would be connection of one of the flying leads to a wrong part of the rectifier bridge.

If, as a test, the flying leads are first connected to a 9V battery, a voltmeter across the output terminals should read over 7V with the battery connected either way round.

# DOMESTIC STRAIGHT

*This simple yet reliable design can be recommended to the newcomer to*

*by J. B. WILLMOT*

**T**HERE is a constant stream of "new entrants" to the hobby of radio receiver construction, many of whom are in search of a design for a receiver which, whilst simple to construct, will be reliable in operation and ensure really worthwhile reception of a selection of home and Continental programmes; at the same time the receiver must be inexpensive to construct and comprise only standard, easily obtainable components. With these criteria in view the author constructed the receiver described in the following paragraphs, and it is thoroughly recommended to the novice who has mastered the art of soldering and who, having possibly built one or two simple crystal and transistor receivers, is now desirous of tackling a mains operated valve receiver.

Reference to the theoretical circuit diagram, Fig. 1, will no doubt bring back to the older readers memories of their early efforts at mains receiver construction. Basically the design employed is that which was regarded as "standard" in the early days of mains operated receivers, namely a three-stage t.r.f. ("straight") line-up comprising a vari-mu pentode r.f. amplifier stage, followed by a triode grid leak detector and a.f. amplifier and a pentode power output stage, the whole being fed with the necessary power supplies from a fully isolated mains transformer and full-wave rectifier with choke and capacity smoothing.

Many t.r.f. receiver designs, particularly those of the "midget" type, employ a.c.-d.c. power supply technique or a heater transformer in conjunction with a half-wave rectifier. Admittedly this gives a considerable saving in cost, but in the writer's view the greater safety factor given by the avoidance of a "live" chassis (unavoidable in the a.c.-d.c. type of receiver), when a full-wave power supply with double-wound mains transformer is employed, is particularly desirable in the case of all home-constructed receivers and especially so for those assembled by beginners. A further advantage is that performance of the completed receiver is enhanced by virtue of the fact that an h.t. positive line of a full 250V is available, allowing adequate voltage to be fed to the valve anodes and screen grids even after the "drop" due to load and decoupling resistors and at the same time smoothing is more efficient and the resultant hum level kept to a low order.

Octal-based valves are used throughout, as these are efficient and robust and very cheaply obtainable from numerous advertisers in this magazine, also their comparatively large base connections

greatly facilitate wiring up for the novice. In spite of the fact that the basic principles of the circuit date back some 30 years, good results are assured in all but the very poorest reception locations, the inclusion of pre-set reaction in the detector stage greatly enhancing the sensitivity and selectivity of the receiver. Long and medium waveband coverage is provided, but listeners residing in areas where the B.B.C. Light Programme is satisfactorily received on 247 metres (such as the London area, for example) may omit the long waveband if desired, with resultant simplification and saving in cost.

## CIRCUIT DESCRIPTION

Signals are fed to the control grid of V1, which is a 6K7, by way of the aerial input coil L1 or L2 (as selected by the wavechange switch S1) and tuned by the section of the two-gang tuning capacitor VC1.

Wearite "P"-type coils are used throughout the receiver. They are easily obtainable, simple to mount and match up to the station markings of the standard type of tuning dial, and the necessary adjustable trimming capacitors can be soldered directly across the tuned windings of the coils themselves (see Fig. 3).

R.F. amplification takes place in V1, the gain of which is made variable by VR1 in the cathode circuit, which thus acts as a volume control. In some locations it would not be possible to reduce the volume sufficiently on strong local stations by variation of bias on V1 alone, so the "cold" end of VR1 is connected to the aerial input, with the result that as the volume control is turned "down" a progressively lower resistance is shunted across the primary of the aerial tuning coils until, at minimum volume setting, the aerial is virtually short-circuited to earth (chassis of the receiver). Conversely, at maximum volume setting, the shunting effect of the full 10k $\Omega$  resistance of VR1 is negligible.

The amplified r.f. signal at the anode of V1 is developed across the r.f. choke L3. A choke is used here in preference to a resistor as, being of comparatively low d.c. resistance, practically the full h.t. voltage is thus applied to the anode of V1, giving maximum efficiency.

C4 acts as a d.c. blocking capacitor to prevent flow of h.t. through the detector coils L4 or L5 to chassis but allows the r.f. signal to pass unimpeded, via the wavechange switch S1c, to the appropriate detector coil (tuned by VC2, the second section of

# T THREE

radio construction

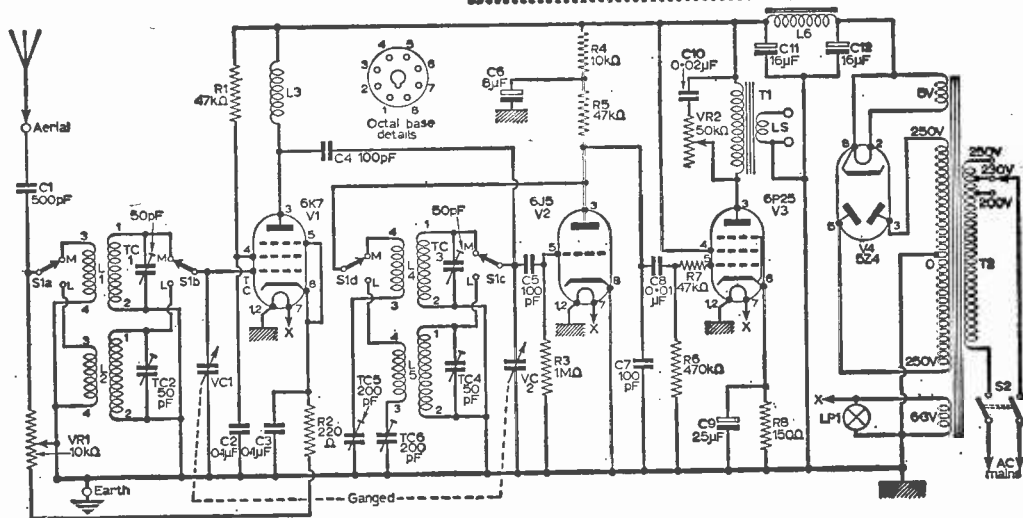
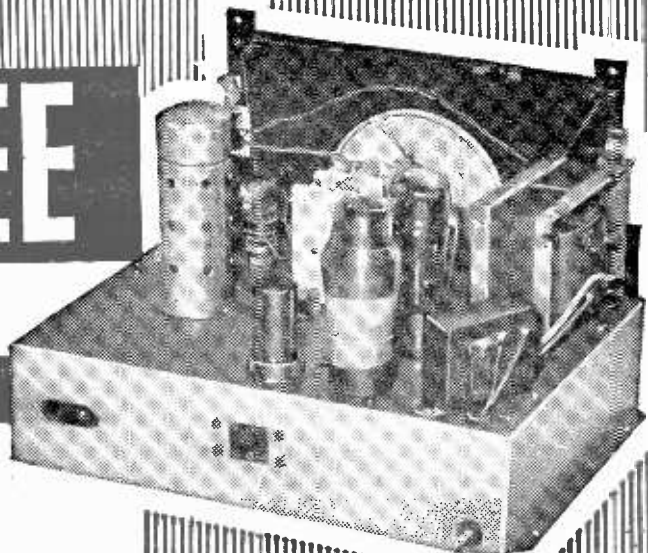


Fig. 1: The complete circuit diagram.

the gang capacitor) and via the grid leak capacitor C5 to the control grid of V2, R3 being the grid leak resistor.

V2 is a 6J5 triode and the cathode of this valve is connected directly to earth and thus the valve combines the functions of demodulation (detection) and a.f. amplification. The values of C5 and R3 have considerable influence on overall performance and those finally chosen and specified in the parts list seemed to give the best compromise between "selectivity" and "quality".

The a.f. voltage appearing at the anode of V2 is developed across the load resistor R5; R4 and C6 provide decoupling from the h.t. line and serve both to prevent unwanted leakage of residual r.f. signals into the h.t. line (with risk of feedback to V1 and instability) and to provide additional smoothing for the h.t. supply to V2.

Grid leak detectors are very prone to "hum" pick-up unless adequately smoothed power supply is provided and neat, short wiring, particularly of the grid input circuit, is a must.

## THE OUTPUT STAGE

The a.f. signal is fed via C8 to the control grid of V3, which is a high-slope pentode output valve of the 6P25 type. R7 is a grid stopper resistor inserted as close as possible to the control grid of V3 to prevent any r.f. voltages from reaching this valve, which could cause parasitic oscillation (sometimes at supersonic frequencies) to be set up, with resultant poor reproduction of speech and music.

R8 and C9 provide for correct biasing conditions of V3 and the output is developed across the primary winding of the output transformer T1.

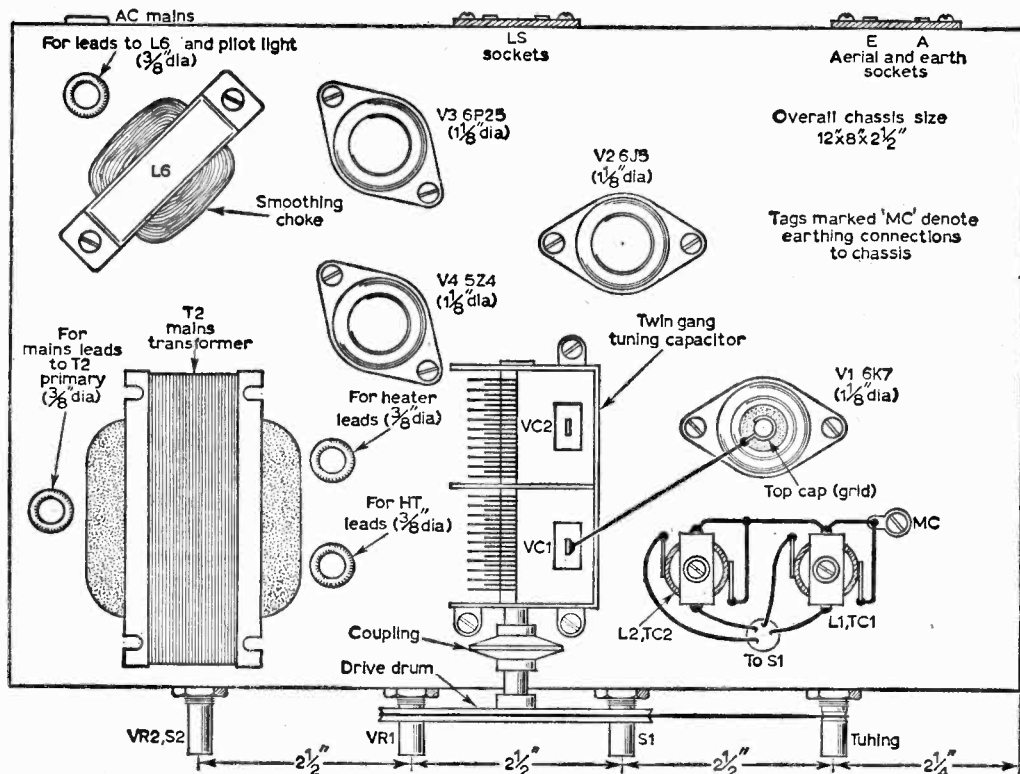


Fig. 2: A suggested layout for major components.

whose secondary winding is "matched" to the loudspeaker speech coil.

A simple type of tone control, comprising C10 and VR2, is connected across the primary of T1 and this gives the necessary control over frequency response. As pentode valves tend to accentuate the higher frequencies, including such unwanted noises as heterodyne whistles caused by transmitting stations radiating on frequencies near to the one being received, the inclusion of a means of "top cut" is very desirable. VR2 is thus useful in reducing background "noise", especially when listening to the more distant stations.

#### FEEDBACK ARRANGEMENTS

Returning now to the anode circuit of V2, the purpose of the other components connected thereto will now be explained. In addition to the a.f. signal there will be signals at r.f. present at this electrode; a portion of these is bypassed to earth via C7 but the remainder is deliberately fed back through the coupling coils of L4 or L5 (according to setting of the wavechange switch S1d), via the preset trimmer capacitor TC5 or TC6, to earth. Variation of the setting of these trimmers allows the amount of feedback ("reaction") to be controlled and in practice, when the receiver is completed, they are set to give the maximum amount of feedback which can be tolerated without the receiver bursting into self-oscillation, and an enormous increase in both sensitivity and selectivity results from this arrangement. It

should be noted that the windings of the feedback coils must be connected in the correct "sense", otherwise a diminution in signal strength, instead of an increase, will take place. The correct method of connecting the specified coils is indicated by reference to Figs. 1 and 3.

#### POWER SUPPLY

The power supply section comprises a double-wound mains transformer T2, provided with primary tappings to suit the various standard

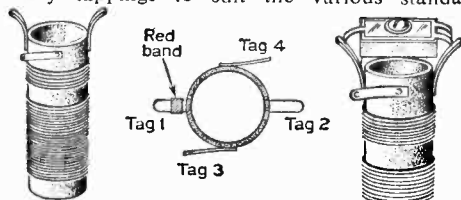


Fig. 3: The Wearite coils with the additional trimmers.

mains supply voltages. An on/off switch S2 (actually combined with VR2) is inserted in one of the primary leads. Two separate secondary windings provide 5V at 2A to feed the heater of the rectifier valve V4 (which is a 5Z4) and 6.3V at 3A to feed the heaters of all the other valves, plus any pilot bulb(s) provided for illumination of the tuning dial. The centre tapped 250—0—250V h.t. secondary winding of T2 should be rated at not less than 60mA.

Full-wave rectification takes place in V4 and the resultant d.c. is smoothed by the reservoir capacitor C12, l.f. choke L6 and smoothing capacitor C11. The choke should be rated at about 10H for a current of 60mA. C11 and C12 can conveniently be a "double" electrolytic capacitor of 8+16 or 16+16 $\mu$ F of not less than 350V working. These values will be found to give adequate smoothing and the resultant h.t. voltage available at C11 should be approximately 250V "on load".

Provided that the stated values and voltage ratings of the components given in the parts list are adhered to they can be of any make; only the tuning coils (Wearite "P" type) are specified by name, and as these were used in the original and connection data for these is given the beginner in particular is advised to adhere to the specification.

If alternative makes of coils are used the manufacturer's data as to connections must, of course, be adopted. It is not recommended that dual-range types (i.e., those having both long and medium waveband coils on one former) be employed, as these normally have only one coupling or feedback winding common to both wavebands. This would render the separate preset

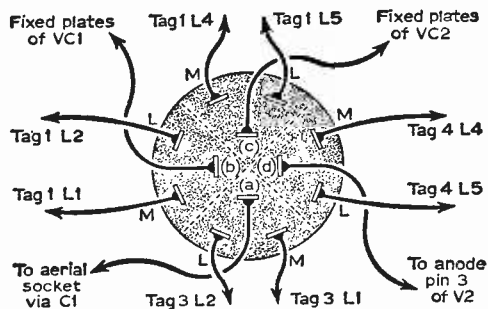


Fig. 4: The wavechange switch details.

adjustment of reaction in the detector stage no longer possible on the two wavebands, with the result that whilst it might be found possible to advance the reaction to a certain level on medium waves, the same setting would not hold good on long waves and a compromise setting would have to be accepted, with consequent loss of performance. The slight extra expense and complication of separate coils is fully justified.

The r.f. choke should be of the standard "all wave" type; the one used in the original was taken from an old receiver but a Denco RFC Type 7A or an Osmor Type QC1 should perform satisfactorily in this position.

In the case of valves the specified octal types are very easily obtainable; a "metal" type is recommended for V2 and if a "metal" type is used for V1 the screening can shown in the illustration and parts list can be omitted. If desired an EF39 can be substituted for V1 and either a KT61 or an EL33 substituted for V3 without any circuit changes. It would also be possible to use a directly heated rectifier such as a 5Y3 in the V4 position, but in the writer's opinion the use of the indirectly heated 5Z4 is to be preferred as it prevents the rise of the h.t. voltage to too high a

## COMPONENTS LIST

### Resistors:

R1	47k $\Omega$	R5	47k $\Omega$
R2	220 $\Omega$	R6	470k $\Omega$
R3	1M $\Omega$	R7	47k $\Omega$
R4	10k $\Omega$	R8	150 $\Omega$
All 20%, $\frac{1}{2}$ W carbon			
VR1	10k $\Omega$ wire-wound potentiometer		
VR2	50k $\Omega$ carbon potentiometer, with switch (S2)		

### Capacitors:

C1	503pF mica or ceramic
C2	0.1 $\mu$ F paper 350V
C3	0.1 $\mu$ F paper 350V
C4	103pF silver mica or ceramic
C5	103pF silver mica or ceramic
C6	8 $\mu$ F electrolytic 350V
C7	103pF silver mica or ceramic
C8	0.01 $\mu$ F paper 100V
C9	25 $\mu$ F electrolytic 25V
C10	0.02 $\mu$ F paper 100V
C11	16 $\mu$ F electrolytic 350V
C12	16 $\mu$ F electrolytic 350V
VC1	500pF
VC2	503pF
} twin-gang variable	
TC1	50pF compression type trimmer
TC2	50pF compression type trimmer
TC3	50pF compression type trimmer
TC4	50pF compression type trimmer
TC5	200pF
TC6	200pF
} double compression-type trimmer	

### Inductors:

L1	M.W. aerial coil (Wearite PA2)
L2	L.W. aerial coil (Wearite PA1)
L3	All-wave r.f. choke (Denco RFC7)
L4	M.W. h.f. coil (Wearite PHF2)
L5	L.W. h.f. coil (Wearite PHF1)
L6	Smoothing choke 10H 60mA

### Transformers:

T1	Output transformer 5,000 $\Omega$ primary, 3 $\Omega$ secondary
T2	Mains transformer. Tapped primary. Secondaries: 250-0-250V 60mA; 5V 2A; 6.3V 3A

### Other Circuit Components:

S1	4-pole 2-way wafer switch
----	---------------------------

### Valves:

V1	6K7	V2	6P25
V3	6J5	V4	5Z4

### Miscellaneous:

Chassis 12 x 8 x 2 $\frac{1}{2}$ in. Dial and drive assembly (Jackson SL8). Four I.O. valveholders. One grid clip. One loudspeaker socket strip. One aerial and earth socket strip. Pilot lamps 6.3V, and bulbholders.

level while the other valves in the receiver are warming up.

Considerable latitude of layout is permissible in a receiver of this sort, provided that short and direct wiring of the r.f. circuits is adopted. In actual fact the prototype was constructed on the chassis of a former 5-valve superhet receiver which had been stripped of all components except the two-gang tuning capacitor, drive mechanism and tuning dial; and it may well be that the novice constructor will have such a chassis in his possession—discarded as "junk" at some time in the past! If this is the case and provided the existing

valveholder mounting holes are large enough to accommodate octal valveholders (or are capable of enlargement to enable this to be done), and that the gang capacitor is undamaged by rough storage or mishandling, much tedious metalwork can be avoided.

The use of a top-mounting type of mains transformer will obviate any need to cut out a large rectangular hole in the chassis such as would be needed to accommodate a component of the drop-through type. However, to suit the constructor who has not a suitable chassis already available, or who wishes to make a neater and more workmanlike job, a suggested layout plan, with the major dimensions indicated, is given in Fig. 2.

It is suggested that the components be mounted in the following order: Firstly the four international octal valveholders, which should be fixed with their locating spigots orientated as near as possible to that shown in Fig. 2 to facilitate short and direct wiring. This can be followed by bolting into position the mains transformer, output transformer, smoothing choke and the dual electrolytic capacitor C11/C12 (using a fixing clip for the purpose).

Next mount the controls, namely the volume control VR1, wavechange switch S1, tone control (with switch) VR2 and tuning drive spindle if this latter is not already fitted in the case of those utilising a "second-hand" chassis.

Aerial and earth and loudspeaker socket connecting strips can then be added and, lastly, the tuning coils.

The aerial coils (L1 and L2) should be mounted above chassis and the detector coils below chassis; any attempt to mount both sets of coils below chassis is almost certain to lead to uncontrollable feedback between the r.f. and detector stages, rendering the receiver completely unworkable.

Naturally a number of holes will be required in the chassis to permit the passage of leads from above-chassis components to those below; in the case of leads carrying supplies to and from the mains transformer the holes should be fitted with insulating rubber grommets; in all other cases the insulation of the wires themselves may be relied upon to give sufficient protection.

#### WIRING UP THE RECEIVER

Wiring up can now be carried out and reference to Fig. 5 and Fig. 1 should make this clear even to the beginner; even so it is recommended that a logical sequence be followed to obviate errors.

It is a good plan to start by carrying out all the wiring associated with the mains transformer, e.g. starting from the mains supply lead, connect these to the appropriate voltage tapping on the primary winding, including the on/off switch in one lead. Next connect the rectifier heater winding (5V) to the appropriate tags on V4 valveholder, noting that in the case of a 5Z4 valve this is pins 2 and 8; follow up by wiring the high-voltage secondary windings to the rectifier anodes (pins 3 and 5), not forgetting the connection from centre tap to earth. This leaves only the 6.3V heater supply to wire in and this is done by connecting one side of the

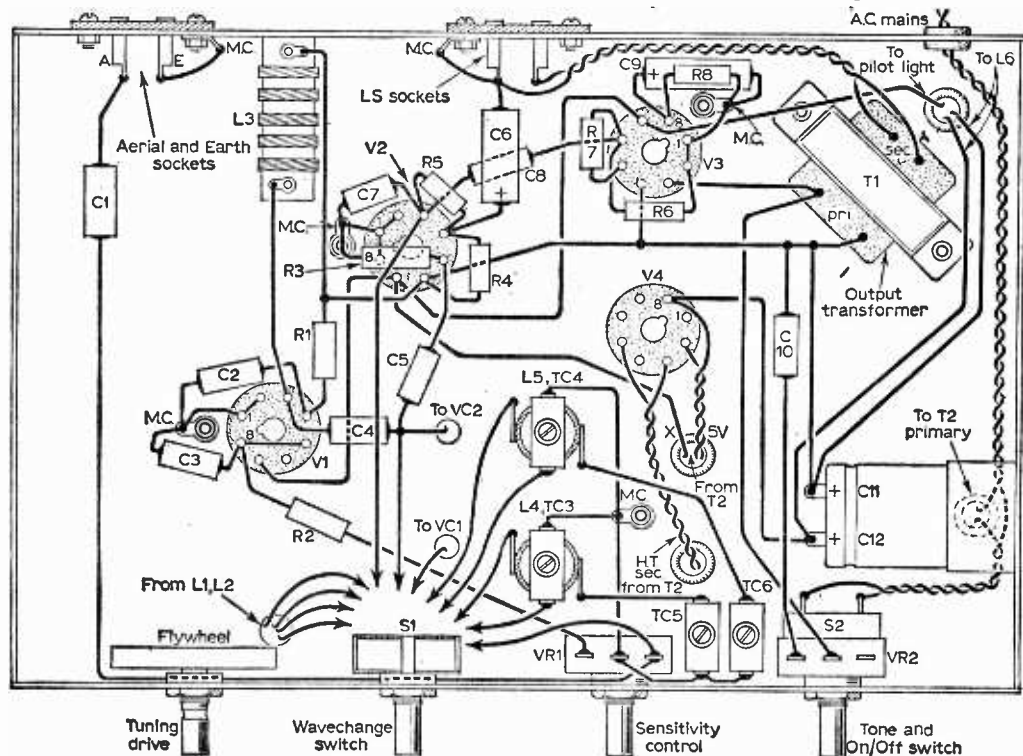


Fig. 5: The underchassis wiring diagram.

6.3V winding to earth and taking an insulated wire from the other end of this winding to pin 7 on the valveholders V1, V2 and V3, also to any pilot bulbholder(s), by the shortest convenient route. This wire should be pressed as close down to the chassis as possible. The return path for the heater supply is via the metal chassis itself and to provide for this pins 1 and 2 of V1, V2 and V3 are wired to earth (solder tags mounted on valveholder fixing bolts). Note that in the case of V2 pin 8 (cathode) is also earthed in this way.

Complete the power supply circuits by wiring in the smoothing choke L6 and the electrolytic capacitors C11/C12. Make sure that C12 does in fact form the reservoir capacitor, i.e. that which is connected to the cathode of V4; normally this section of the capacitor will be distinguished by a red-marked tag. The wiring of the h.t. supply can now be proceeded with, noting the use of pin 6 on V2 and V1 as anchoring points (these are "spare" pins with no internal valve connections); pin 4 of V2 is also used as an anchor point for the junction of R4, R5 and C6.

Interstage wiring is best carried out with bare tinned copper wire of about 22s.w.g. This wire is covered with systoflex sleeving. Resistors and capacitors are, of course, wired into place with their own lead-out wires, shortening where necessary and insulating with systoflex wherever there is any danger of accidental contact between wires or wiring and chassis.

The connections between the h.t. line and various valve electrodes, together with their associated decoupling capacitors, should now be completed; note the polarity of C6. Components associated with the cathode circuits of V1 and V3 can now be added, referring to Fig. 5 for correct method of wiring VR1 in order to ensure that the volume control works in the correct "sense" (clockwise rotation giving increased volume).

Last of all the "signal path" must be wired in. Starting from the aerial socket and including the various coils and capacitors as shown on the circuit diagram right through to the anode of V3.

Fig. 3 clearly shows the tag connections to the Wearite coils and these numbers are repeated on the theoretical diagram (Fig. 1), while Fig. 4 clearly shows the method of wiring up the wavechange switch. It is this latter that is most likely to puzzle the beginner, but if it is tackled methodically, working steadily round the tags of the switch in order, no trouble should be experienced.

As was mentioned earlier, the trimmer capacitors TC1, 2, 3 and 4 are sweated directly to the coil tags, while the large value reaction trimmers TC5 and TC6 are mounted on a small fixing bracket cut from scrap aluminium and mounted on the front chassis runner as close to the coils as possible.

## TESTING AND ALIGNMENT

Unscrew all trimmer capacitors approximately three full turns from their "fully screwed up" position. If a meter or continuity checker is available test for any possible shorts between the h.t. line and chassis and verify that there is continuity between the main h.t. supply (pin 8 of 5Z4), through the smoothing circuits, to the anode and screen grid pins on V1, V2 and V3.

If no meter is available it will be as well carefully to check overall wiring once again. Insert

all valves except V4, connect up to mains supply point and switch on. The pilot bulb(s) should light up immediately and the valve heaters glow in a few seconds. Naturally, if "metal" valves are used in V1 and V2 positions, the heater glow cannot be seen, but after a couple of minutes or so the outer envelope of these valves should feel warm to the touch.

If all is well switch off, insert V4 and again switch on. Watch carefully for any signs of stress in V4; if there is a "tizzing" sound, or signs of flashing as V4 warms up, switch off immediately as you have a short-circuit between the h.t. line and chassis at some point which must be put right before proceeding.

If the above test proves satisfactory turn up the volume control VR1 to maximum and insert an aerial in the aerial socket when, on swinging the tuning capacitor across the dial, some stations will almost certainly be heard. If no sign of life, gently tap the metal blade of a screwdriver on to pin 5 (the control grid) of V3, when a steady hum should be audible from the loudspeaker. Now transfer the screwdriver to pin 5 of V2, when a much louder hum should result. Finally, tapping the screwdriver on the aerial socket should produce a loud click in the speaker. Try this test with the wavechange switch in both positions.

If at any of the above test points the expected response is not obtained, investigate the wiring to that particular valve stage for possible errors or faulty components. Naturally, if a test meter is available, voltage readings taken at the valve electrodes will quickly reveal any faults. However, it is more than probable that in the case of a simple receiver of this sort first-time results will be achieved.

Set the wavechange switch to medium waves (clockwise) and endeavour to tune in a station near the low wavelength end of the dial such as Radio Luxembourg (or even the BBC Light Programme) and adjust the trimmers TC1 and TC3 for maximum volume consistent with reasonably accurate indication on the tuning dial. Reduce the volume with VR1 so that the effect of small changes in volume are more easily noticeable.

Having done this, swing the ganged capacitor across the full range of the medium waveband, when a number of stations should be receivable at their correct dial indications. Now select any weak transmission and gradually screw up the medium wave reaction trimmer TC3; there should be a noticeable increase in signal strength until a point is reached where the set bursts into self-oscillation. Slacken the trimmer sufficiently to stop the oscillation and then swing the tuning back and forth across the dial. If at any setting the set tends to go into oscillation, slacken TC3 a little further. Now switch over to long waves and locate the BBC Light Programme on 1,500 metres. Adjust TC2 and TC4 for maximum volume at correct dial setting and screw up reaction trimmer TC6 until just below point of oscillation. Ensure that the receiver is stable at all settings of the tuning capacitor and alignment is then complete.

## AERIAL AND EARTH

The type and position of aerial used will have a marked effect on the ability of the receiver to

—continued on page 865



# Simple Impedance and Reactance Calculations

BY G. A. W. PARTRIDGE

CONTINUED FROM PAGE 745 OF THE DECEMBER ISSUE.

**C**CHECKING the impedance of a coil or the reactance of a capacitor may prove necessary from time to time. The impedance is the total resistance an inductive or capacitive circuit offers to alternating current. The resistance that a capacitor offers to d.c. can be regarded as infinite, so only its reactance is considered here.

## Inductor Measurements

There are instruments such as impedance meters for this purpose, but they are rather expensive, so for reasonable accuracy the simple ammeter and voltmeter method when applied to coils is most suitable. Fig. 6 illustrates the basic circuit. The impedance ( $Z$ ) is equal to the voltage divided by the current in amperes.

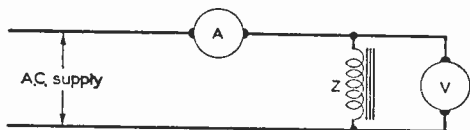


Fig. 6: The basic circuit for inductor measurements.

It is obvious that such a circuit needs considerable modification. First, the voltmeter will have to be extremely sensitive. In other words it will have to have a very high internal resistance. For this reason an electronic voltmeter or a calibrated oscilloscope will have to be used. Second, a low reading milliammeter or in some cases a microammeter will be necessary to measure the small current.

Failing this a non-inductive resistor may have to be connected in series with the impedance and the current found by dividing the voltage across it by its resistance. Fig. 7 shows the modified circuit.

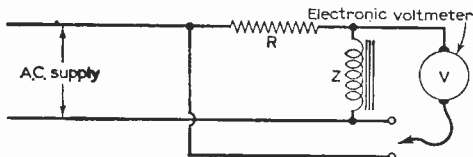


Fig. 7: The modified circuit of Fig. 6.

cuit. The value of  $R$  depends upon the safe current consumption of the impedance. For example, if the current is 1mA, it will need a 10,000Ω resistor to give a deflection of 10V. The most suitable resistance is most usually found by experiment.

The voltage across  $R$  is first measured and then the voltage across  $Z$ . The current consumption in amperes is:

$$I = \frac{\text{Voltage across } R}{\text{Resistance of } R}$$

The impedance of  $Z$  is:

$$Z = \frac{\text{Voltage across } Z}{\text{The current consumption in amperes}}$$

Milliamperes or microamperes have to be converted to fractions of an ampere for the impedance formula. Remember that the supply must be also at the frequency which the impedance will be operating on. Impedance varies with frequency.

This method is suitable for low frequencies only. Anything above 5kc/s would usually require more elaborate apparatus. However, there are other ways of calculating impedances provided a few facts are known. Take the formula:

$$Z = \sqrt{(L2\pi f)^2 + R^2}$$

where  $Z$ =Impedance in ohms

$L$ =Inductance in henries

$\pi$ =3.142

$f$ =Frequency in cycles per second

$R$ =D.C. resistance in ohms.

The inductance may have to be measured if it is not marked on the coil. The d.c. resistance can be checked with an ohmmeter, Wheatstone bridge, or d.c. milliammeter and voltmeter method.

For example, a coil has an inductance of 300 henries and the d.c. resistance is 250 ohms. What is its impedance at 1,000 cycles per second?

$$\begin{aligned} Z &= \sqrt{(L2\pi f)^2 + R^2} \\ &= \sqrt{(300 \times 2 \times 3.142 \times 1,000)^2 + (250)^2} \\ &= \sqrt{1885200 + 62500} \\ &= \sqrt{1947700} \end{aligned}$$

Therefore  $Z=1,396\Omega$  approximately.

## Capacitor Measurements

Much the same idea can be applied to a capacitor. The formula in this case is:

$$X_c = \frac{1}{2\pi fC}$$

$X_c$ =Capacitive reactance in ohms

where  $\pi$ =3.142

$f$ =Frequency in cycles per second

$C$ =Capacitance in Farads.

An 0.2μF capacitor is connected to a 100c/s supply. What is its reactance?

$$\begin{aligned} X_c &= \frac{1}{2\pi fC} \\ &= \frac{1}{2 \times 3.142 \times 100 \times 0.2} \\ &= \frac{1}{1,000,000} \end{aligned}$$

# RETURN-OF-POST SERVICE

We offer a really efficient Mail Order Service on all items stocked. All cash orders are dealt with on the day of receipt. ★ Hire purchase orders are subject to slight delay but this is kept to the absolute minimum.

## ● ILLUSTRATED LISTS

Illustrated lists are available on LOUDSPEAKERS, TAPE DECKS, TEST GEAR, GRAMOPHONE EQUIPMENT, AMPLIFIERS. Any will be sent free upon request.

## ● AMPLIFIER KITS

We have full stocks of all components for the Mullard 510, Mullard 3-3, Mullard 2 and 3 Valve Pre-amp, Mullard Stereo, Mullard Mixer, GEC912 Plus. Fully detailed list on any of these sent upon request.  
Instruction Manuals: All Mullard Audio Circuits in "Circuits for Audio Amplifiers". 9/5, GEC912, 4/6, All post free.

## ● TRANSISTORISE YOUR CRYSTAL SET

We have two new designed for Transistor amplifiers which can be used to greatly improve the signal from any crystal set. RLD4 Kit, one stage 10/6; RLD5 Kit, two stage 17/6, both post free. The kits are easy to build and very detailed instructions are supplied. Leaflet available.

## ● ARMSTRONG EQUIPMENT

### TUNER AMPLIFIERS

	Cash Price	Deposit	Hire Purchase
Model 227 Stereo ..	£48.15.0	£9.15.0	12 of £2.11.6
Model 227M Mono ..	£38.18.0	£6.18.0	12 of £2. 9.6
Model 226 De Luxe Stereo ..	£56. 0.0	£11. 0.0	12 of £4. 2.6
Stereo 55 Stereo ..	£29.18.0	£5.18.0	12 of £2. 4.0

### RADIOGRAM PHONES

Model AF20s AM/FM ..	£21. 4.0	£4. 0.0	12 of £1.11.2
----------------------	----------	---------	---------------

### TUNERS

Model T4R FM ..	£20. 8.0	£4. 2.0	12 of £1. 9.11
Model ST3 Mk 2 AM/FM ..	£25.12.0	£5. 2.0	12 of £1.17.11

Makers' literature available on any item.

## ● NEW MULLARD CONDENSERS

Mullard Miniature Foil and Polyester condensers as used in the latest TV and Transistor sets.

Miniature Foil. 30 volt working for Transistor sets. .01mfd, 74d.; .022mfd, 9d.; .047mfd, 9d.; .1mfd, 11d.  
Polyester Tubular Capacitors. Moulded outer case designed to withstand accidental contact with the soldering iron. Tolerance 10%. 125v. range: .01mfd, .022mfd, .047mfd, all 9d. each. 1mfd, 1/2; .22mfd, 1/3; .47mfd, 1/6; 1mfd, 3/-.  
400v. range: .001mfd, .002mfd, .0047mfd, .01mfd, .022mfd, all 9d. each. .047mfd, 1/2; .1mfd, 1/3; .22mfd, 1/6; .47mfd, 2/5. Postage extra.

## ● MINIATURE ELECTROLYTIC CONDENSERS

Latest miniature types by Mullard and Radio spares.  
RADIO SPARES. All 15 volt, 2mfd, 4mfd, 5mfd, 8mfd, 10mfd, 16mfd, 32mfd, 50mfd, 100mfd, all 2/3 each. Postage extra.  
MULLARD. 2mfd, 10v, 1/9; 4mfd, 4v, 1/9; 10mfd, 16v, 1/8; 16mfd, 10v, 1/8; 32mfd, 4v, 1/8; 32mfd, 25v, 1/8; 32mfd, 2.5v, 1/8; 32mfd, 40v, 1/8.

## ● "SYNCHROTAPE" RECORDING TAPE

Low priced British tape, all reels fitted with leaders.  
Standard Play: 600ft, (5") 13/6; 850ft, (5 1/2") 17/-; 1,200ft, (7") 21/-; Long Play: 900ft, (5 1/2") 17/-; 1,200ft, (5 1/2") 20/-; 1,800ft, (7") 30/-; All Post Free.

## ● TAPE RECORDING EQUIPMENT

	Cash Price	Deposit	Hire Purchase
ALL CARRIAGE FREE			
COLLARO STUDIO, latest model, Two track, Bradmatic Heads	£10.19.6	£2. 3.6	12 of 16/4
Four Track, Marriott Heads	£17.17.0	£3.12.0	12 of 26/2

### MARTIN TAPE AMPLIFIER KITS

Tape Amplifiers  
For Collaro 8311-V 2-Track £11.11.0 8311-V 4-Track £12.12.0  
Tape Pre-Amplifiers  
For Collaro 8312-CP 2-Track £8.8.0 8312-CP 4-Track £9.9.0  
Drop through assembly for mounting 8312 Pre-Amp under Collaro Deck, £11.11.6  
Carrying Cases with speaker. For Collaro Deck and 8311 Amplifier 25.5.0.

H.P. TERMS available on decks, amp, and cases. Ask for quote.  
MULLARD TAPE PRE-AMPLIFIER KIT  
We stock complete kits and all separate components for the Mullard Tape Pre-Amplifier. Fully detailed list available.

## ● LOUDSPEAKERS

GOODMANS: Axiote 8in., £5.5.7; Axiom 10in., £6.5.11; 12in. Axiom 301, £10.7.0; 12in. Axiom 301, £14.10.0; 12in. Audiom 51 Bass, £8.14.0; 12in. Audiom 61 Bass, £13.14.0; Treble Tweeter, £6.0.0; N50000 Crossover unit, £1.19.0  
WHITELEY: HF1016 10in., £7.0.0; HF1012 10in., £4.7.6; HF16 8in., £6.0.0; T16 8in., £5.13.6; T10 Tweeter, £4.8.3; T459 Tweeter, £1.10.6; CX3000 Crossover unit, £1.11.6; CX1500 Crossover unit, £2.0.0. H.P. Terms available on all speakers.

## ● STEREO COMPONENTS

Morganite ganged potentiometers as specified for the Mullard, circuits. ★ Log/Antra Log 500k, 1 meg., 2 meg. ★ Log/Log, 50k, 250k, 1 meg., 2 meg. ★ Lin/Lin 500k, 500k, 1 meg., 2 meg. All 10/6 each. Postage extra.

## ● TRANSISTORS

MULLARD. Current production types, not rejects. All in makers' boxes. Postage 3d. on each.  
AF114, 11/-; AF115, 10/6; AF116, 10/-; AF117, 9/8; OC44, 8/3; OC45 8/-; OC70 and OC71, 6/6; OC72, 8/-; OC72 Matched Pairs, 18/-; OC78, 5/-; OC81, 8/-; OC170, 8/6; OC171, 9/-; Any other Mullard type obtained promptly. Ask for quotation.

## ● JASON F.M. TUNERS

We stock all parts needed for the construction of these excellent tuners. All parts can be supplied separately but we can offer attractive reductions in price if all items are purchased at same time as follows.

FMT1, £6.12.6; FMT2 (less power), £7.15.0.
FMT3 (with power), £9.12.6; FMT3 (less power), £9.9.6.
FMT3 (with power), £11.7.6; Mercury 2, £10.14.6.

JTV/2, £14.12.6.

Hire Purchase Terms available. Ask for list.

## ● P.W. STRAND, MAYFAIR & SAVOY UNITS

We stock parts for the P.W. Strand Amplifier, Mayfair Pre-Amp and Savoy FM Tuner. Detailed price lists are available.

## ● LATEST TEST METERS

	Cash Price	Deposit	Hire Purchase
AVO Model 8 Mark II	£24. 0.0	£4.16.0	12 of £1.15.2
AVO Model 7 Mark II	£21. 0.0	£4. 4.0	12 of £1.10.10
AVO Multimeter Mark 4	£9.10.0	£1.18.0	12 of 14/4
T.M.K. TP10	£3.19.6	£1. 3.6	3 of £12.0
T.M.K. TP55	£5.19.6	£1.15.6	3 of £11.4.4
T.M.S. Model 500	£5.19.6	£1.15.6	12 of 13/6
TAULOR MODEL 127A	£10.10.0	£2. 2.0	12 of 15/8
CABY A10 ..	(Post 1/6)	£4.17.6	£1. 7.6 3 of £13.8
CABY B-20 ..	(Post 1/6)	£6.10.0	£2. 6.0 3 of £13.4
CABY M-1 ..	(Post 1/3)	£2.14.0	—

Full details of any of the above supplied free on request.  
The AVO models 7 and 8 are both latest models from current production—not to be confused with Government Surplus.

## ● OUTPUT TRANSFORMERS

GILSON: W096A, W096B, 50/6, post 2/6. W0710, 55/6, post 2/6. W0892, 62/3, post 2/9. W0767, 27/-, post 1/6. W0176A, 57/6, post 2/6. W01932, 84/-, post 3/-  
PARTIDGE: P2667, 75/-, post 2/9. P4131, 75/-, post 2/9.  
PARMEK: P2629, 47/6; P2642, 45/-; P2643, 47/6. All plus post 2/9; P2641, 29/6, post 2/-; P2628, 17/-, post 2/-; P2632, 41/-, post 2/6.  
ELSTONE: OT/ML, 49/6, post 2/9; OT/3, 27/6, post 2/6.

## ● MAINS TRANSFORMERS

GILSON: W0741A, 63/-, post 4/-; W0839, 48/9, post 2/9; W01328, 58/6, post 3/6; W01268, 58/-, post 3/6; W01566, 80/-, post 4/6; W01341, Choke, 36/-, post 2/-  
PARMEK: P2651, 35/-, post 2/9; P2630, 54/9, post 3/3; P2644, 76/6, post 4/-; P2630, 41/-, post 3/-; P231, 56/-, post 3/3.  
ELSTONE: MT/ML, 49/6, post 3/3; MT/3M, 38/6, post 3/-; MT/510, 46/3, post 3/3.

## ● GRAMOPHONE EQUIPMENT

	Cash Price	Deposit	Hire Purchase
ALL LATEST MODELS			
ALL POST FREE			

	Cash Price	Deposit	Hire Purchase
GARRARD AUTOSLIM (Mono PU)	£7. 2.6	£1. 5.6	12 of 11/2
GARRARD AUTOSLIM De-luxe AT6 (Mono PU)	£11. 9.0	£2. 6.0	12 of 16/11
GARRARD AUTOSLIM AT6 (Stereo/Mono PU)	£12. 5.4	£2. 8.4	12 of 19/-
B.S.R. UA14 (TC8 Mono PU)	£6.19.6	£1. 7.6	12 of 11/-
B.S.R. UA14 Monarch (TC8 Stereo/LEP/78)	£7.19.6	£1.11.6	12 of 12/4
B.S.R. UA16 (TC8 Mono PU)	£7.19.6	£1.11.6	12 of 12/4
B.S.R. UA16 (TC8 Stereo/LEP/78)	£8.19.6	£1.15.6	12 of 13/8
B.S.R. TU12 (TC8 Mono PU)	£3.17.6	£1. 4.6	3 of £1.10
B.S.R. GU7 (TC8 Mono PU)	£4.18.8	£1. 8.8	3 of £1.8.8
GARRARD SRP10 (Mono PU)	£5. 9.11	£1.12.11	3 of £1.8.0

## ● TRANSCRIPTION UNITS

GARRARD 4HF (GC8 PU) £16.12.6 £3. 6.6 12 of £14.5  
PHILIPS AG10H (S/M PU) £12.12.0 £2.10.0 12 of 18/6  
Many of the above can be supplied for stereo working. See our Gramophone Equipment List for details.

## ★ TERMS OF BUSINESS

Cash with order or C.O.D. We charge C.O.D. orders as follows: Up to £5, minimum of 4/2. Over £5 and under £10, 2/8. Over £10, no charge. Postage extra on CASH orders under £5 except where stated. Postage extra on overseas orders irrespective of price.

# WATTS RADIO

(MAIL ORDER) LTD.

54 CHURCH ST., WEYBRIDGE, SURREY

Telephone: Weybridge 47556

Please note: Postal business only from this address  
Callers welcome by appointment

## ★ HIRE PURCHASE TERMS


Available on any item. Repayments over 3, 6 or 12 months as below. Three months: Deposit 6/- in the £. Service charge 5%. minimum charge 10/-. Six months: Deposit 5/- in the £. Service charge 7 1/2%, minimum charge 15/-. Twelve months: Deposit 4/- in the £. Service charge 10%. minimum charge 20/-.

# Easy-to-make cabinets to house your hi-fi

- 1 Tape deck/record storage
- 2 & 5 Loudspeaker
- 3 Record storage
- 4 Radio/record player

These easy-to-make sectional units are part of an outstanding new range of designer-styled cabinets for high fidelity sound equipment. They are the direct result of a close collaboration between well-known industrial designer Frank Guille Des RCA FSIA and Percy Wilson MA, technical editor of "The Gramophone" and prominent authority on acoustical engineering.

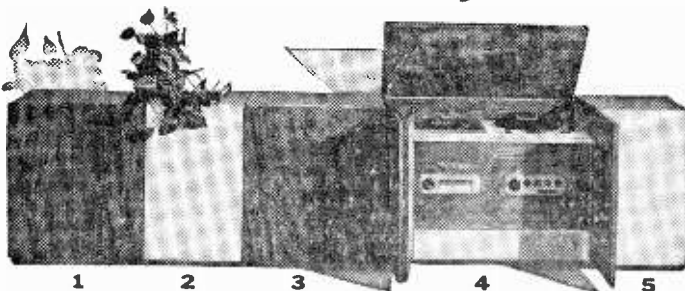The cabinets which will house almost any combination of Hi-Fi equipment have been especially designed for making in Vipboard. Vipboard



is a fine quality board with superior screw-holding qualities; specifically made for easy and economical furniture-making within the home. It comes in 20 standard sizes, fully veneered on all surfaces and ready

to polish. No special skills are required, and you need only basic household tools. Total cost of Vipboard for the cabinets shown above is £24.4.3. The individual cabinets cost from £3.1.9 (units 2 and 5).

## Vipboard fully veneered chipboard with the natural wood finish

Find out how you can choose and build the units best suited to your Hi-Fi requirements—at a fraction of their "shop price". Ask for Free Instruction Leaflets and the Vipboard Furniture Brochure at your local Vipboard stockist, or write to: Vipboard Division, G.W.E. Boards Limited, 6 John Street, London WC1. Holborn 8421

**VALVES FOR RADIO, TV AND AUDIO APPLICATIONS**  
All valves sold by us are first quality, unused and guaranteed for three months.

When ordering by mail, please add 2/6 in the £ for handling.  
MINIMUM CLEARANCE 1/6.

0A2	6/-	6AH6	11/-	6SL7GT	5/-	85A2	8/6	8BF89	6/9
0A3	11/-	6AK5	5/-	6SN7GT	4/8	807	9/-	E81	11/-
0B2	6/-	6AK6	7/-	68Q7GT	5/-	814	20/-	E8131	11/-
0B3	6/-	6AL5	3/-	6U4GT	9/8	832	20/-	E8C40	9/-
0C3	5/6	6AM6	4/-	6V6	8/-	866A	14/-	E8C84	8/6
0D3	5/-	6AQ5	6/-	6V6GT	4/-	884	10/-	E8C85	6/8
1A7GT	8/-	6AR6	6/-	6V6GT	5/8	985	8/-	E8C88	10/-
1C6GT	7/-	6A86	5/-	6V6GT	5/8	985	8/-	E8C90	7/8
1D5	7/8	6A87G	22/6	6X5G	4/8	957	5/-	E8C92	7/-
1Q6GT	7/-	6AT6	4/-	6X5GT	5/8	958A	4/8	E8C91	10/-
1H6GT	7/-	6AU8	7/-	6Y6G	6/-	959	8/-	E8C93	10/-
1L6	17/-	6AV6	8/-	6Z4	5/-	9670	10/-	E8C94	8/-
1N5GT	8/-	6B7	5/-	10D1	19/-	9763	10/-	E8C95	6/-
1R5	5/-	6B8	5/-	10P14	15/-	9763	10/-	E8C96	7/8
1B4	5/-	6BA5	4/8	12A8H	11/-	9902	5/-	E8C97	4/8
1B5	4/8	6B55	5/-	12AT6	5/-	9903	7/-	E8C98	7/8
1T4	7/-	6B18	7/-	12AT7	4/-	AZ1	9/-	E8C99	10/-
1U4	6/-	6B16	8/-	12AT7	5/-	AZ31	8/-	E8C100	10/-
1U5	6/-	6BQ7A	8/-	12A7	5/-	AZ41	8/6	E8C101	10/-
1X2A	7/-	6BR7	11/6	12A77	10/-	C1C	5/-	E8C102	10/-
1X2B	7/-	6BR8	5/-	12B4A	9/-	CL33	3/-	E8C103	10/-
1Y4	14/-	6B93	11/6	12B4A	6/-	CV31	6/6	E8C104	10/-
2D21	6/-	6B97	9/-	12B8A	5/-	DAC32	8/-	E8C105	10/-
2X3	3/-	6C5GT	6/-	12B8A	5/-	DAC32	8/-	E8C106	10/-
3A4	4/-	6C6	4/-	12B8T	5/-	DAF91	4/8	E8C107	10/-
3A5	7/-	6C8G	7/-	12G7GT	5/-	DAF92	6/-	E8C108	10/-
3B7	6/-	6C86	6/-	12G7GT	5/-	DAF96	6/-	E8C109	10/-
3B28	15/-	6C86GA	6/-	12G7GT	5/-	DAF96	6/-	E8C110	10/-
3D6	4/-	18J	18/-	12J87	5/-	DF96	6/-	E8C111	10/-
3E29	50/-	60L6	10/-	12J87GT	10/-	DK32	8/-	E8C112	10/-
3Q4	6/8	6C88	7/8	12B4G615	10/-	DK91	5/6	E8C113	10/-
3Q5GT	7/8	6C94	14/-	20L4	14/-	DK96	6/6	E8C114	10/-
3R4	5/-	6D4	15/-	90P1	14/-	DK96	6/6	E8C115	10/-
3V4	5/8	6D84	15/-	95L6GT	8/-	DL33	9/-	E8C116	10/-
6A8GY	9/-	6F13	6/8	95Z4G	6/8	EL34	10/-	E8C117	10/-
6U46	6/-	6F17	6/-	95Z6	7/8	EL34	10/-	E8C118	10/-
6U46B	6/8	6G4	9/-	95Z6GT	7/8	EL34	10/-	E8C119	10/-
6V4G	6/-	6G5	5/8	95Z8T	7/8	EL34	10/-	E8C120	10/-
6Y3G	4/-	6J7G	5/-	90P5	8/8	EL41	7/3	E8C121	10/-
6Y3GT	5/8	6K6GT	8/-	90P19	14/-	EL42	8/8	E8C122	10/-
6Z3	6/-	6K7	5/-	95P14	10/8	EL43	8/8	E8C123	10/-
6Z4	6/-	6K8G	4/-	95P14	10/8	EL43	8/8	E8C124	10/-
6Z4G	7/8	6L4	9/-	95W4	7/-	EAF42	8/6	E8C125	10/-
6A6	6/-	6L6G	6/-	95Z4GT	6/-	EBC41	8/8	E8C126	10/-
6A8G	6/-	6L18	8/-	95Z4GT	6/-	EBC81	8/8	E8C127	10/-
6A8A	6/8	6N7	6/-	95Z4GT	6/-	EBC90	4/8	E8C128	10/-
6A8B	4/-	6Q7G	6/-	95Z4GT	6/-	EBC91	6/8	E8C129	10/-
6A7C	3/-	6R7	6/-	95Z4GT	6/-	EBC91	6/8	E8C130	10/-
6A8G	6/-	6BGT	5/-	95Z4GT	6/-	EBC91	6/8	E8C131	10/-

## Z & I AERO SERVICES LTD.,

Retail Shop: 85, TOTTENHAM COURT ROAD, W.1

Tel. LANGham 8403

Head Office and Warehouse now in new premises at: 44A WESTBOURNE GROVE, W.1  
Tel. PARK 5641/2/3.

Please send ALL correspondence and Mail Orders to the Head Office.

SELENIUM RECTIFIERS			
CONTACT COOLED, 230VAC 300mA Half Wave ..	2/6		
Ditto Centre Tapped ..	4/-		
CARTRIDGE, MINIATURE WIRE ENDED, D1601, 230VAC (resistive) 15mA ..	2/-		
CENTRE TAP S.T.C. 30-mA RECTIFIER STACKS: 27V AC, 3/8, 180V AC, 6/8, 220V AC, 7/-	35/-		
GERMANIUM JUNCTION STUD MOUNTED RECTIFIERS			
GJ5M, 300 p.p.v., 1A max. ..	3/6		
GJ7M, 80 p.p.v., 1A max. ..	3/6		
SILICON JUNCTION MAINS RECTIFIERS			
MULLARD BY100, 700 p.p.v., 450 mA, DC LUCAS DD058, 900 p.p.v., 500mA DC subminiature (less than pin. dia.) ..	8/-		
2.25 WATT ZENNER DIODES	12/6		
VR 425 (3.9 to 4.8V); VR 475 (4.4 to 5.1V); VR 525 (4.9 to 5.6V); VR 575 (5.4 to 6.1V); VR 625 (5.9 to 6.8V); VR 76 (6.4 to 7.6V); VR 9B (8.4 to 9.6V) all at 6/6 each. VR 10B (9.4 to 10.6V); VR 11B (10.4 to 11.6 V) all at 7/- each			
TRANSISTORS			
OC28 .. 17/8	OC71 .. 5/-	OC78D .. 7/-	
OC35 .. 15/-	OUT2 .. 8/-	OC81 .. 7/-	
OC44 .. 6/-	OC75 .. 6/-	OC81D .. 12/-	
OC45 .. 6/-	OC78 .. 6/-	OC139 .. 12/-	
OC70 .. 5/-	OC78 .. 7/-	OC170 .. 8/-	
R.C.A. 2N410 (I.F. 465 kc/s) ..			4/8
2N412 (540-1600 kc/s mixer) ..			4/3
MICRO ALLOY V.H.F. TRANSISTORS			
MAT101 (90 mc/s) 8/8	MAT121 (120 mc/s) 8/6		
SUBSTANDARD TRANSISTORS: These are perfectly suitable for most application where maximum gain is not required.			
OC44 .. 2/3	OC45 .. 2/3		
CATHODE RAY TUBES			
2AP1 .. 25/-	SCP1 .. 80/-	VCR97 .. 40/-	
3AP1 .. 22/8	3FP7 .. 10/8*	VCR138 .. 50/-	
310P1A .. 15/-	56P7 .. 60/-	VCR17 B or C 40/-	
3FP7 .. 12/-	7BP7 .. 15/-*	ACR10 .. 20/-	

\* Electromagnetic

$$\begin{aligned}
 &= \frac{1,000,000}{2 \times 3.142 \times 100 \times 0.2} \\
 &= \frac{1,000,000}{125.68}
 \end{aligned}$$

Therefore  $X_c = 7,956\Omega$  approximately.

These formulae are suitable for a.f. and r.f. circuits, but the results must be regarded as approximate, especially on the higher frequencies due to stray capacitances and inductances.

## IMPEDANCE TRIANGLES AND L.F. COILS

Testing low frequency coils can be very interesting as well as instructive. Such work is also necessary when the efficiency of a coil is in question. The impedance triangle can be used to find out all sorts of information without using expensive apparatus. Fig. 8 shows how it adds up the three great resistive quantities.

Fig. 8: The impedance triangle.

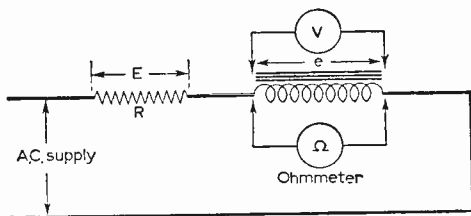
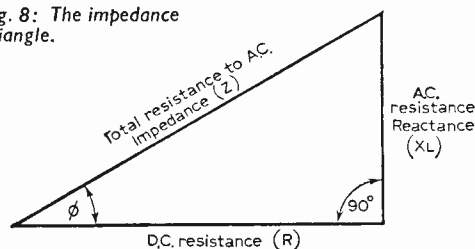


Fig. 9: The circuit required to provide the measurements used in the impedance triangle.

$R$  represents the resistance the coil offers to d.c. only. This is due to the length and cross sectional area of the wire that makes up the coil.  $X_L$  known as the inductive reactance is the resistance to a.c. due to magnetism. Both these quantities make up the impedance ( $Z$ ).

The angle  $\theta$  is also important. It tells us about the efficiency of the coil. The greater the angle the less efficient it is.

Fig. 9 illustrates the circuit required to determine these measurements. The coil to be tested is connected to a suitable voltage at the required frequency through a resistor ( $R$ ) of known value. The voltage ( $e$ ) across the coil is checked and the current found by measuring the voltage ( $E$ ) across the resistor ( $R$ ).

$$I = \frac{E}{R}$$

Now the impedance is calculated from:

$$Z = \frac{e}{I}$$

The d.c. resistance of the coil can be checked with an ohmmeter after disconnecting it from the a.c. supply.

We now know two sides of the triangle. The reactance can be found from:

$$X_L = \sqrt{Z^2 - r^2}$$

All sides of the triangle are now known.

The power factor which is the cosine of the angle  $\theta$  is found by:

$$\cos \theta = \frac{r}{Z}$$

The nearer the power factor comes to one the greater is the efficiency of the coil.

Finally, the inductance in henries is:

$$L = \frac{X_L}{2\pi f}$$

where  $\pi = 3.142$

$f$  = frequency in cycles per second.

Here is an example:

A coil is tested at a frequency of 50c/s. The resistor  $R$  is  $100\Omega$  and the voltage ( $E$ ) developed across it is 30. The voltage ( $e$ ) across the coil is 150, while its d.c. resistance ( $r$ ) is  $450\Omega$ .

The current ( $I$ ) flowing through the coil and resistor is:

$$\begin{aligned}
 I &= \frac{E}{R} \\
 &= \frac{30}{100} \\
 &= \frac{3}{10} \text{ or } 0.3 \text{ A}
 \end{aligned}$$

The impedance is:

$$\begin{aligned}
 Z &= \frac{e}{I} \\
 &= \frac{150}{0.3} \\
 &= 500\Omega.
 \end{aligned}$$

The reactance is:

$$\begin{aligned}
 X_L &= \sqrt{Z^2 - r^2} \\
 &= \sqrt{(500)^2 - (450)^2} \\
 &= \sqrt{250,000 - 202,500} \\
 &= \sqrt{47,500} \\
 &= 218\Omega \text{ approx. (by logs).}
 \end{aligned}$$

The power factor is:

$$\begin{aligned}
 \cos \theta &= \frac{r}{Z} \\
 &= \frac{450}{500} \\
 &= \frac{9}{10} \\
 &= 0.9 \text{ power factor.}
 \end{aligned}$$

This is a very efficient coil.

The inductance is:


$$L = \frac{X_L}{2\pi f}$$

$$\begin{aligned}
 &= \frac{217.9}{2 \times 3.142 \times 50} \\
 &= \frac{217.9}{314.2} \\
 &= 0.69\text{H.}
 \end{aligned}$$

We have now completed the impedance triangle which gives us useful information about the coil we have tested.
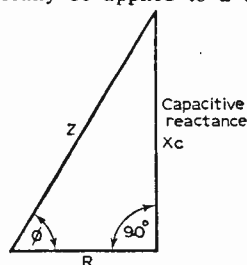
#### IMPEDANCE TRIANGLES and CAPACITORS

It is obvious that the impedance triangle cannot really be applied to a capacitor alone. First of



all a good capacitor would have almost infinite resistance to d.c., so the base of the triangle (Fig. 10) would be undecided. The power factor would be at almost zero lead, so the angle  $\theta$  would be about 90 deg.

Fig. 10: The impedance triangle as applied to capacitors.

A capacitor can, however, be tested with a known non-inductive resistor connected in series with it, as shown in Fig. 11. The capacity is measured on a capacity bridge and the capacitive reactance ( $X_c$ ) calculated from

$$X_c = \frac{1}{2\pi fC}$$

where  $f$  = frequency in cycles per second.

$C$  = capacity in farads.

Two sides of the triangle,  $X_c$  and  $R$  are now known. The third side  $Z$  is calculated from:

$$Z = \sqrt{R^2 + X_c^2}$$

This gives the correct impedance of the circuit. Now this impedance is checked directly. The correct impedance ( $Z$ ) has only so far been calculated. It remains to be seen if the circuit really has this value.

The voltages  $E_s$  and  $E$  are carefully measured with a valve voltmeter.

$$Z = \frac{E_s}{I} \times \frac{R}{E}$$

A good capacitor should have  $\frac{E_s}{I} \times \frac{R}{E}$  equal to  $\sqrt{R^2 + X_c^2}$  or very close to it.

The correct power factor of the circuit can be calculated from:

$$\text{Correct power factor} = \frac{R}{\sqrt{R^2 + X_c^2}}$$

The actual power factor will be:

$$\text{Actual power factor} = \frac{R}{\frac{E_s}{I} \times \frac{R}{E}}$$

Here again both calculations should be much the same.

For example:

A capacitor is found to have a value of  $0.01\mu\text{F}$  and it is connected to a non-inductive resistance of  $1,000\Omega$ . The circuit is connected to a  $100\text{V}$   $50\text{kc/s}$  supply (Fig. 11).

Before starting the test calculate the correct capacitive reactance:

$$\begin{aligned}
 X_c &= \frac{1}{2\pi fC} \\
 &= \frac{1}{2 \times 3.142 \times 50 \times 1,000 \times 0.01} \\
 &= \frac{1}{3142} \\
 &= \frac{1}{1,000,000} \\
 &= \frac{1}{0.003} \\
 &= 333\Omega.
 \end{aligned}$$

Now calculate the impedance

$$\begin{aligned}
 Z &= \sqrt{R^2 + X_c^2} \\
 &= \sqrt{(1,000)^2 + (333)^2} \\
 &= \sqrt{1,000,000 + 110,889} \\
 &= \sqrt{1,110,889} \\
 &= 1053 \text{ (by logs).}
 \end{aligned}$$

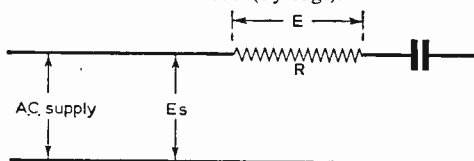


Fig. 11: The test circuit for a capacitor.

The circuit is checked with the valve voltmeter.  $E_s$  is found to be 100 and  $E$  90V. The actual impedance is:

$$\begin{aligned}
 Z &= \frac{E_s}{I} \times \frac{R}{E} \\
 &= \frac{100}{1} \times \frac{1,000}{90} \\
 &= 1,111\Omega.
 \end{aligned}$$

There is a difference of  $58\Omega$ , which is probably due to leakage in the capacitor.

The correct power factor of the circuit will be:

$$\begin{aligned}
 \text{Correct power factor} &= \frac{R}{\sqrt{R^2 + X_c^2}} \\
 &= \frac{1,000}{1,053} \\
 &= 0.95 \text{ lead.}
 \end{aligned}$$

The actual power factor of the circuit is:

$$\begin{aligned}
 \text{Actual power factor} &= \frac{R}{Z} \\
 &= \frac{1,000}{1,111} \\
 &= 0.90 \text{ lead.}
 \end{aligned}$$


The difference in the correct and actual power factors is very close, which is quite good. A large difference would indicate a faulty capacitor. ■

## HAWAIIAN PORTABLE RECORD PLAYER

Uses a unique pick-up unit, turntable and speaker to give amazing volume and reproduction without the use of valves or transistors. Battery operated, plays up to 12 in. records at 33 $\frac{1}{3}$  or 45 r.p.m. Separate fine speed and volume controls. 45 r.p.m. adaptor. Plastic cabinet. Fully waterproof with carrying handle and record storage compartment. Size 9 in. dia. x 3 $\frac{1}{2}$  in. deep. Weight 2 lb. 9 ozs. PRICE **£5.19.6**



## TRANS. RADIO TUBULAR SPEAKER

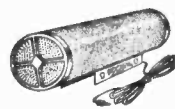

that will amaze you, size Approx. 9 x 2 $\frac{1}{2}$  in. PRICE **25/- 1/9**


## HI-FI GT.50 RADIO JACK

Full medium coverage. Ideal for all tape recorders, amplifiers, etc. No batteries required—just plug in. Amazing reception from your equipment. ONLY **29/-**


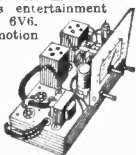
## SUPERHET RADIO CHASSIS

These well-made chassis were made for the Government for Forces entertainment with 6KA, 6K7, 6Q7, 6V6. Choke smoothing slow-motion tuning, printed scale, 200-550 metres. BRAND NEW, ONLY **57/6**



Post 5/-, Cabinet with 8 in. speaker **27/6** P.&P. to fit, 3/-

## 12 to 250v. CONVERTER UNIT

100mA output, double choke smoothed, bridge rectified. Spare vibrator, fuse wire, battery clips, indicator bulbs. Absolutely **30/-** P.&P. Brand New in Makers' cartons. 5/-

## HOOVER ROTARY TRANSFORMERS

12v. input, 500v. output at 65mA or 6v. input, 250v. output at 75mA. A. P.&P. PRICE **9/11** 3/-



## PORTABLE MAINS SOLDERING IRON

30 watts. Features removable handle that covers tip and barrel. Complete **14/6** P.&P. with lead and plug. 6d

## CHRISTMAS OFFER


Crystal Set (all components supplied) and PORTABLE MAINS SOLDERING IRON. BOTH **17/11** P.&P. for 9d.

TRADE SUPPLIED



## This month's bargain

### No. 19 TRANSMITTER RECEIVER

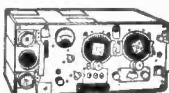

Trans/Receiver covers 2-8Mc/s. (150-37 metres in two bands). Has an intercom. amplifier. Designed for 12 and 24 volt operation. Uses 6-volts superhet receiver, I.F. being 465Kc/s, and a 6-volt transmitter driven for voice and C.W. operation. Incorporates test and tuning meter for voltages, aerial loading and current tests. Panel controls: frequency tuning, P.A. tuning, gain control, MCW, CW, S/T switch. Hel-tone netting. On-on quench aerial, AVO LT-HT drives test. **52/6** no P.&P.

ONLY **52/6** no P.&P. INSTRUCTION HANDBOOK 3/6. Whip Aerial (U.S.A.) 10ft 7/6 P.&P. 2/6, 6ft 4/- P.&P. 1/3.

## SONA SINCLAIR SLIMLINE

Gives choice of British and European programmes with staggeringly good quality and selectivity. Building is easy and interesting, and as well as providing superb listening through the earpiece, the "Slimline" makes a wonderful radio jack. FULL coverage of medium waveband. Extremely robust **49/6** construction



## RADIO HEADPHONES

Balance armature type. P.&P. 2/6. **15/11**

## DOUBLE THROAT MICROPHONE

Can be adapted for use with musical instruments. P.&P. 6d. **4/11**

## TRANSISTOR SALE

Mullard OC 44 ..... 3/11 P.&P. 3d.  
Mullard OC 45 ..... 3/11 P.&P. 3d.  
Mullard OC 71 ..... 2/11 P.&P. 3d.  
Mullard OA 81 ..... 1/11 P.&P. 3d.  
Ediswan X920 Germanium diodes, ..... 1/11 P.&P. 3d.  
Transistor Holder, 3 Pin, 11d, each, P.&P. 3d.

## MICRO ALLOY TRANSISTORS

Mat 100 ..... 7/9  
Mat 101 ..... 8/8  
Mat 120 ..... 8/8  
Mat 121 ..... 8/8  
Above MATs Postage Paid.  
Ferrite Slab Aerials, suitable for Transistor Sets, ..... 3/- P.&P. 6d.

## HIGH IMPEDANCE PERSONAL LISTENING EARPIECES

Suitable for all types of crystal sets and transistor sets. Complete with plug. **5/11** P.&P. 6d.

## LEAD ACID ACCUMULATORS

(Unspillable)  
2 volts 16 A.H. Brand new. Size 4 x 7 x 5 in. 4/11 each, 3 for 12/6. P.P. 3/-


PERSONAL CALLERS WELCOME AT OUR NEW BRANCH BELOW:



SONA ELECTRONIC CO (DEPT PWI)  
BRIGGATE HOUSE, 13 ALBION PLACE, LEEDS. TEL: 34703
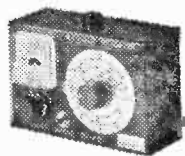
## RF FIELD INDICATORS

Designed for checking the radiation from a transmitting antenna. The sensitivity can be controlled by adjustment of panel control, the antenna length, or by increasing distance from the radiator. Frequency range 1-250Mc/s. 200uA D.C. **69/6**




## HEAVY DUTY RF CHOKES on STAND

Suitable for transmitting circuits. P.&P. 1/6. **4/11**

MOVING COIL HEADPHONES AND MICROPHONE ATTACHED. Suitable for 19 set. Not new. P.&P. 2/3. **5/11**
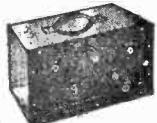
## OSCILLATOR TEST SET No. 10

Enabling the equipment to be used from a telephone line, etc., 230 volts A.C. input having an internal P.W. HT supply testing unit. **37/11** EACH. P.&P. 7/6.



## COMPONENTS

SMOOTHING CHOKES. 100mA, 10-20H resistance 450 ohms. Sturdy metal case. 4/11 P.&P. 2/6.

SMOOTHING CONDENSERS. TCC metal enclosed block condensers, 4 x 2 $\frac{1}{2}$  x 1 $\frac{1}{2}$  in. with terminals. 8mFd, 250v. working. Suitable for cross-over units. 3/11, P.&P. 1/6.

MAINS TRANSFORMER. Mains standard primary 250, 0.250v, 80mA, 6.3v. volts at 4 amps, 5 volts at 2 amps. Both tapped at 4v. 18/11 each. P.&P. 2/6.

As above 350.0.350v sec. 19/11. P.&P. 2/6.

FILAMENT TRANSFORMERS. 250-250v, 50c/p primaries, 6.3v. at 2 amps. 6/11, P.&P. 1/3.

OPERATORS' UNITS. A host of valuable components (Block condenser. Jack plug, socket, etc.). ONLY 1/11 each. P.&P. 1/3.

PAXOLIN TAG STRIPS. (14 tags). Double way. 1/3 each. P.&P. 6d.

PANEL MOUNTING FUSE HOLDERS. Beautifully made, plastic, sturdy construction. 2/11 each. P.&P. 6d.

ELECTROLYTIC CONDENSERS. 0.5mFd. TCC. 500v. working. 1/5 each. P.&P. 3d.

MORSE KEYS. Morse key assembly No. 8. Key with base, cover and terminals. Complete with lead, jack plug, and connector. BRAND NEW. 6/11, P.&P. 2/3.

OCTAL MOULDED VALVE HOLDERS, 6d., 3 for 1/3. 807 valve holders, 9d., 3 for 2/-.

B7G valve holder, ceramic moulded with screening skirt, 9d., 3 for 2/-.

P. &P. on each 3d. CONDENSERS. Variable condenser solid dielectric. 0.005mFd. 3/3. P.&P. 9d.

TRIMMERS. 0.750pF max. 9d. P.&P. 3d.

CONDENSERS. 60mFd electrolytic reversible 12v. working. 1/8. P.&P. 3d.

1 mFd CONDENSERS. 130v. working. Suitable as suppressors. 1/11. P.P. 8d. 470pF. 10% tolerance, 750v. working. 7d. P.&P. 3d.

## VERNIER DIALS

Precision vernier dials with approx. 5 to 15 ratio. Surface mounting. Accurately centred metal insert for 1/8 in. shaft. Reads counter clockwise 0-100 in 180°.



Model T.501 1 1/2 in. dia. **12/6**


Model T.502 2 in. dia. **14/-**

Model T.503 3 in. dia. **16/-**
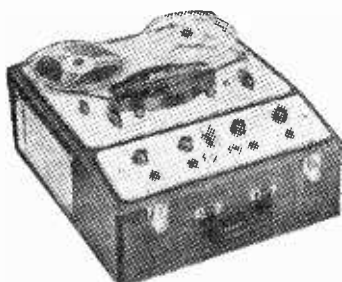
## FREE FREE

WITH ALL ORDERS OVER £3.00 YOU WILL RECEIVE A PORTABLE MAINS SOLDERING IRON.

Terms: Cash with orders. No C.O.D. under £1.10.0.




69 gns.
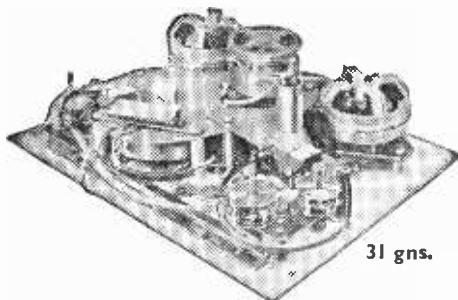
## The new Mark 5 Series 2 TAPE RECORDER


... with this specification:

4 speeds  $1\frac{7}{8}$ ,  $3\frac{3}{4}$ ,  $7\frac{1}{2}$  and 15 ips—frequency correction at all 4 speeds—3 independent motors—exceptionally low 'wow and flutter' content—double-gapped ferrite erase head to minimise erase noise—narrow-gapped record/playback head to give extended frequency response—pause control—superimpose control—recording level indicator (meter extra)—takes in  $8\frac{1}{2}$  in. dia. reels—fast rewind (1200ft. in 45 seconds)—digital rev. counter.



31 gns.

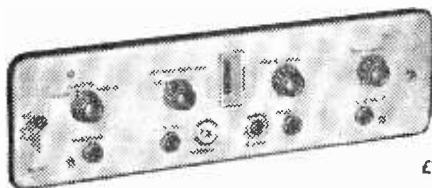... and the MARK 5 Series 2 deck for  $8\frac{1}{2}$  in. reels.  
(and the MARK 510 Series 2 deck for 10 $\frac{1}{2}$  in. reels.)



£26

... and matching amplifiers  
are all available from:—

**BRENELL ENGINEERING CO. LTD.**  
1a Doughty St., London, W.C.1. HOLborn 7356/8

**Brenell**

Write or phone for  
full details and  
price list.

CD 590

# SPECIAL OFFER!

## FROM R. & T.V. LTD.

*Elegant Seven*

## COMBINED PORTABLE & CAR RADIO

The Radio with  
the Star features

★ 7-transistor superhet. Output 350mW. ★ Two-tone grey wooden cabinet, fitted handle with silver coloured fittings. Size 12 $\frac{1}{2}$  x 8 $\frac{1}{2}$  x 3 $\frac{1}{2}$  in. ★ Horizontal tuning scale, size 11 $\frac{1}{2}$  x 2 $\frac{1}{2}$  in., in silver with black lettering. ★ All stations clearly marked. ★ Ferrite-rod internal aerial. ★ IF 470 Kc/s. ★ Operated from PP9 battery. ★ Full comprehensive instructions and point-to-point wiring diagram. ★ Printed circuit board, back printed with all component values. ★ Fully tunable over medium and long waveband. ★ Car aerial socket. ★ Full after sale service. Goods not despatched outside U.K.



ONLY  
**£5.9.6**

Plus 5/6 Postage & Pkg.  
PARTS LIST & CIRCUIT  
DIAGRAM 216. FREE  
with parts. Terms C.W.O.  
All enquiries S.A.E.

## RADIO & T.V. COMPONENTS LTD.


21c HIGH STREET, ACTON, LONDON, W.3.

Shop hours 9 a.m. to 6 p.m. Early closing Wednesday
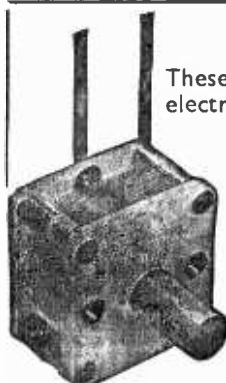
# JACKSON

the big name in **PRECISION** components

Precision built radio components are an important contribution to the radio and communications industry. Be sure of the best and buy Jackson Precision Built Components.



## "DILEMIN" CONDENSERS

These miniature solid dielectric condensers are only  $\frac{7}{8}$ " square. The  $\frac{1}{4}$ " dia. spindle projects  $\frac{1}{2}$ " from the Front Plate. Low loss construction provides Power Factor better than .001.

It's reliable if it's  
made by Jacksons!

Write for literature

## JACKSON BROS. (LONDON) LTD.

(Dept. P.W.) KINGSWAY-WADDON, SURREY

Phone: Croydon 2754-5 Grams: Walfico, Souphone, London



# Challenge your friends to BEAT the 'BEAM'

## A Novel Device to keep your Christmas Guests Amused

By G. A. MELLOR

SOME kind of electronic game was required to provide an amusing distraction at a recent party. The unit had to be fairly inexpensive to build and automatic in operation. With these points in mind the following unit was devised, which may be constructed in two forms, beatable and non-beatable.

The finished product is a square box with perspex windows, internally illuminated by a 100W lamp. In the front is a hole 6in. square through which the competitor must put his hand to reach a prize placed on a shelf at the rear of the box. A beam of light is projected across the inside of the hole, the light falling on a photo-sensitive device. Immediately a hand is put through the hole, the beam of light is interrupted, causing a relay to become energised. This relay performs two operations. (a) switches off the interior light, (b) brings a "cheat" alarm to the ready.

The idea of the game is to reach in the box and remove the prize before the interior light goes out; if the prize is lifted from the shelf when the light is out, the "cheat" alarm rings.

### Light Sensitive Unit and Amplifier

Various methods were tried to sense the cutting of the beam of light. The method finally adopted uses a glass encased transistor with the protective paint removed.

This transistor TR1 is mounted in the reflector from a disused torch, the reflector then being pushed into a 35mm film tin, see Fig. 1. The transistor leads are brought through a hole in the base of the tin and fastened to a three-way terminal strip. Connections to the transistor should be made with twin core screened cable. A number of transistors were tried in the prototype and all worked very well, even one which had been slightly damaged by heat gave good results as a detecting device.

TR2 acts as a d.c. coupled amplifier. When light reaches the junction of TR1, its collector current increases, this increase is accompanied by an even greater rise in TR2. When TR2 collector current reaches 750 $\mu$ A the relay RLA energises. If the light beam to TR1 is interrupted RLA de-energises.

RLA is a Carpenters type polarised relay in which the contact screws have been adjusted to make it a monostable type, this is a simple adjustment. Any other type of relay would work in RLA position, the only requirements being a low resistance coil and a low energising current.

### Light Source

The light beam to the transistor is provided by a 6.3V 3W bulb. This bulb LPI is also contained in a film tin, connections being made to a two-way terminal strip bolted to the bottom of the tin. A reflector was used in the prototype, but was found to be unnecessary if the tin be polished on the inside to give a good reflecting surface. Lamp brilliance is adjusted by RV1.

### Switching Circuits

Fig. 2 shows the relay switching circuits, and the sequence of operation is as follows. When the light beam to TR1 is interrupted, RLA de-energises, its contacts RLA1 make, feeding 50V

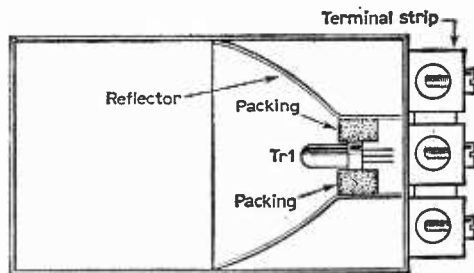


Fig. 1: The method of mounting Tr1.

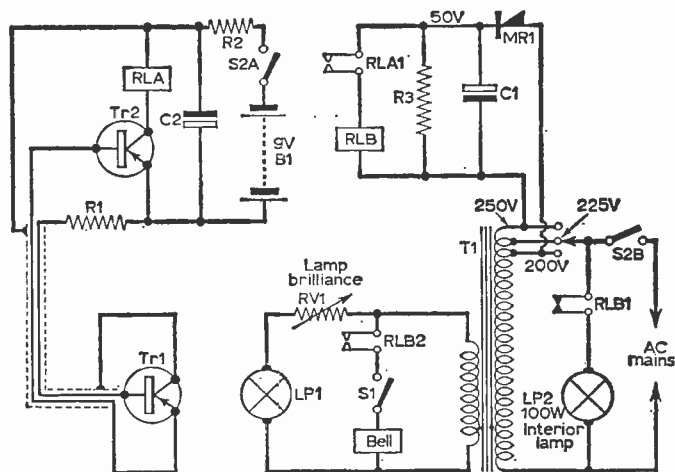


Fig. 2: The relay switching circuits.

to RLB. This second relay RLB energises, contacts RLB1 open so switching off the 100W lamp LP2; contacts RLB2 close, feeding 6.3V to S1.

If now the prize is lifted from the shelf, S1 closes putting 6.3V across the alarm bell, the bell will commence to ring and will not stop until the hand is replaced or the hand is withdrawn from the unit.

The microswitch S1 is mounted as shown in Fig. 3. The button should be sufficiently proud of the shelf to ensure reliable operation. In the prototype a 4lb box of chocolates operated the switch reliably.

### Power Supplies

As the maximum consumption of the amplifier was only 1mA it was considered unnecessary to build a mains power unit, so instead two 4.5V flat batteries were used, one half of S2 being

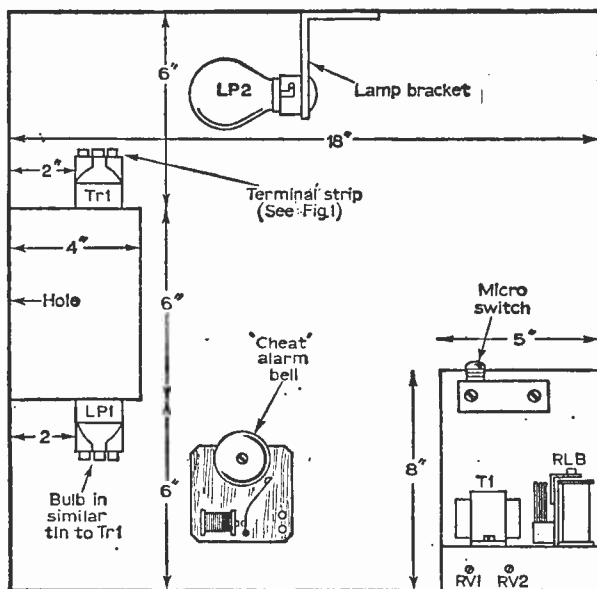


Fig. 3: The mounting for S1.

### Construction

The box is 18in. square with perspex windows as shown in Fig. 3.

The amplifier, bell and transformer are all mounted on a small sub-chassis beneath the shelf. It is advisable to conceal the main on/off switch or the constructor may find himself buying a large number of prizes!

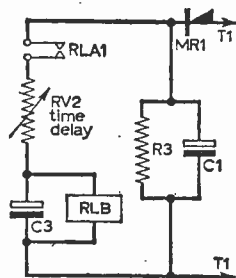


Fig. 4: The C-R network necessary to provide a time delay.

One important point to note in the construction is the position of the interior lamp. This must have no effect on TR1, for this reason it has been mounted above and behind TR1 as shown.

### Setting Up

When the unit is finished, turn RV1 to maximum resistance and switch on, relay RLA should not hold in. Increase the lamp brilliance until RLA becomes energised. Cutting the light beam should now operate the unit.

If RLB is fed directly from the 50V supply it will energise as soon as RLA1 contacts make, and the competitor therefore has no chance of reaching the prize before the light goes out. To give the competitor a chance to win a prize it is possible to insert a long C-R network into the supply of RLB as shown in Fig. 4. The time delay may be varied by adjusting RV2. The component values shown gave a delay from almost zero to four seconds in the original model.

### COMPONENTS LIST

R1	180kΩ ½W
R2	100Ω ½W
R3	10kΩ ½W
RV1	50Ω wire-wound potentiometer
RV2	50kΩ wire-wound potentiometer
C1	16μF electrolytic 100V
C2	12μF electrolytic 12V
C3	500μF electrolytic 100V
TR1	See text
TR2	OC71 or any audio type
LPI	6.3V 3W
LP2	240V 100W
RLA	Carpenters type polarised relay. Low resistance coil
RLB	Relay with double c/o contacts, 3,000Ω coil
MR1	115V 30mA half wave rectifier
S1	Microswitch
S2	D.P.S.T. toggle switch
T1	Heater transformer. Primary 200/230/250V. Secondary 6.3V 5A
Bell	6V a.c. type

utilised to switch off this supply with the rest of the equipment.

The lamp LP2 is powered from the mains, while LP1 and the alarm bell are fed from a 6.3V heater transformer, T1. The 50V for RLB is also taken from this transformer, a tap being made between the 200V and the 250V windings. This a.c. supply is rectified by MR1 and smoothed by C1, the value of C1 need only be sufficient to prevent relay chatter. It should be noted at this point that the coil and contacts of RLB and the contacts of RLA are all at mains potential, these contacts should therefore be well out of reach of the hand in the box!

# PORTABLE TRANSISTOR RADIOS

BACKED BY SUPER AFTER SALES SERVICE

## ROAMER SEVEN Mk III

● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves, Trawler Band and two Short Waves to approx. 17 metres. Push-pull output for room filling volume from rich toned heavy duty 5in. speaker. Ferrite rod aerial for M & L waves and telescopic aerial for S Waves. Air spaced ganged tuning condenser ensures wonderful station selection. Simulated hide case with gilt trim and shoulder and hand straps. Size 9 x 7 x 4in. approx. The perfect portable and the ideal car radio. (Uses PP9 battery available anywhere.)

## 5 WAVEBAND PORTABLE OR CAR RADIO

Amazing performance and specification

Total cost of parts now only

**£5.19.6** P. & P. 5/6


Parts Price List and easy build plans 3/-.



## TRANSONA FIVE

'Home, Light, A.P.N. Lux. all at good volume' G.P., Durham.

● 7 stages—5 transistors and 2 diodes.

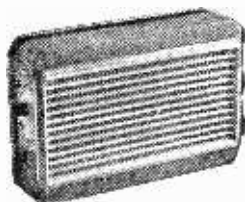

Parts Price List and easy build plans 2/-

Total cost of all parts now only **42/6**

P. & P. 3/6.

## TRANSONA SIX NEW!

● 8 stages—6 transistors and 2 diodes.

This is a top performance receiver covering full Medium and Long Waves and Trawler Band. High-grade powerful magnet, 3in. speaker makes listening a pleasure. Push-pull transformers for ample power. Ferrite rod aerial. Many stations listed in one evening including Luxembourg loud and clear. Attractive case in grey with red grille. Size 6 1/2 x 4 1/2 x 1 1/2 in. (Uses PP4 battery available anywhere.) (Carrying strap 2/- ex.)




Total cost of all parts now only **59/6** P. & P. 3/6

Parts Price List and easy build plans 1/6
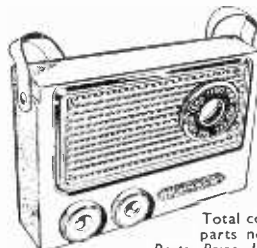
## SUPER SEVEN

● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves and Trawler band. The ideal radio for home, car or can be fitted with carrying strap for outdoor use. Completely portable—has built in aerial for wonderful reception. Special circuit incorporating 2 R.P. stages, push-pull output, 3in. speaker (will drive larger speaker). Size 7 1/2 x 5 1/2 x 1 1/2 in. (Uses PP8 battery available anywhere.)



Total cost of all parts now only **£3.19.6** P. & P. 3/6


Parts Price List and easy build plans 2/-

## ROAMER SIX

**FREE!** Miniature Earpiece, plug and socket (value 9/6) and details of conversion to private listening.

● 8 stages—6 transistors and 2 diodes.

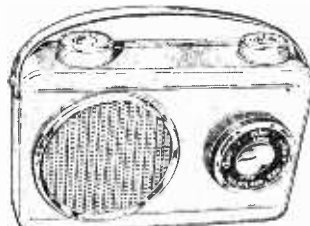Listen to stations half a world away with this 5 waveband portable. Tunable on Medium and Long waves. Trawler Band and two Short waves. Sensitive ferrite rod aerial and telescopic aerial for short waves. Top grade transistors, 3-inch speaker, handsome case with gilt fittings. Size 6 1/2 x 4 1/2 x 1 1/2 in.



Total cost of all parts now only **£4.19.6** P. & P. 3/6.

Parts Price List and easy build plans 3/-.


## MELODY SIX

**FREE!** Miniature Earpiece, plug and socket (value 9/6) and details of conversion to private listening.

"... amazed at volume and performance... has really come up to my expectations." S.G., Stockton-on-Tees.

● 8 stages—6 transistors and 2 diodes.

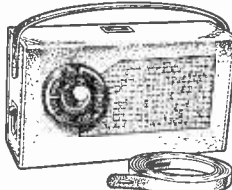Our latest completely portable transistor radio covering medium and long waves. Incorporates pre-tagged circuit board, 3in. heavy duty speaker, top grade transistors, volume control, tuning condenser, wave change slide switch, sensitive 6in. ferrite rod aerial. Push-pull output. Wonderful reception of B.B.C. Home and Light, 208 and many Continental stations. Handsome leather-look pocket



size case, only 6 1/2 x 3 1/2 x 1 1/2 in. approx., with gilt speaker grille and supplied with hand and shoulder straps.


Total cost of all parts only **£4.9.6** P. & P. 3/6.

Parts Price List and easy build plans 2/-
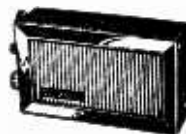
## POCKET FIVE

● 7 stages—5 transistors and 2 diodes.

Covers Medium and Long Waves and Trawler Band, a feature usually found in only the most expensive radios. On test Home, Light, Luxembourg and many Continental stations were received loud and clear. Designed round supersensitive Ferrite Rod Aerial and fine tone 2 1/2 in. moving coil speaker, built into attractive black case with red speaker grille. Size 5 1/2 x 1 1/2 x 3 1/2 in. (Uses 1289 battery available anywhere.)



Total cost of all parts now only **42/6** P. & P. 3/6.

Parts Price List and easy build plans 1/6

All components used in our receivers may be purchased separately if desired. Parts price lists and easy build plans supplied free with sets of parts or available separately at prices stated.

## Radio Exchange Co.


27 HARPUR STREET, BEDFORD  
Phone 2367 ● Opposite Co-op. ● 10-1 p.m. Sats

# TAPE RECORDER SCOOP!
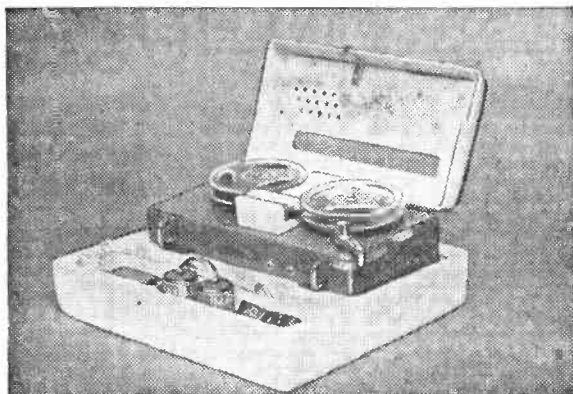
# £4.19.6

Post  
Paid

- ★ FOUR TRANSISTORS
- ★ MICROPHONE
- ★ EARPHONE
- ★ REEL OF TAPE
- ★ SPARE SPOOL
- ★ BATTERIES
- ★ CARRYING HANDLE
- ALL INCLUDED!



## IDEAL CHRISTMAS PRESENT!

### ALSO—

Resistors:  $\frac{1}{2}$  watt, 10/- per 100; 1 watt, 15/- per 100; 2 watt, 20/- per 100.


Miniature Paper Condensers: .0001 to .04, 7/6 per 100.

Transistor Electrolytics: 1 $\mu$ f, 2 $\mu$ f, 4 $\mu$ f, 8 $\mu$ f, 10 $\mu$ f, 16 $\mu$ f, 25 $\mu$ f, 32 $\mu$ f—15V, 64 $\mu$ f—10V. All 1/6 each.

Four-Transistor Printed Circuit Amplifiers, complete 39/6.  
Kit Radios, table size, with full step-by-step instructions, 75/-.  
Acos MIC40, 19/6. Telephone Tape Pick-up, 9/-.  
Tubular Speakers with two plugs, 17/6.  
Multimeters, A.C. and D.C. volts, current, ohms, 39/6.  
Earphones, Midget for Transistor Sets, 2/6 each.

**MILWARD 17 PEEL CLOSE, DRAYTON BASSETT, STAFFS.**
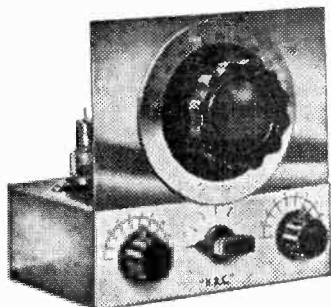
## FAMOUS FOR THIRTY YEARS for SHORT-WAVE EQUIPMENT of QUALITY H.A.C. SHORT-WAVE KITS



H.A.C. were the original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, Hams, etc.

### NEW 1964 RANGE NOW READY ONE-VALVE MODEL "CX"— COMPLETE KIT PRICE 34/6

Customers say: "Definitely the best one-valve S.W. kit available at any price." This kit contains all genuine Short-Wave components, a drilled chassis, accessories and full instructions. Ready to assemble and of course, as all our products, fully guaranteed. FULL RANGE of other kits still available including the famous model "K", price 77/-.

Before ordering call and inspect a demonstration receiver or send for a descriptive catalogue and order form to:—

"H.A.C." SHORT-WAVE PRODUCTS  
(Dept. T.H.), 44 Old Bond St., London W.1

## ERSIN Multicore SOLDER

The world-famous copper loaded alloy containing 5 cores of non-corrosive flux, that saves the soldering iron bit. Ersin Multicore Solder is also available in high tin quality alloys. 60/40 in 22 s.w.g. for printed circuits, transistors, etc.

### THE HANDY DISPENSER



Easy to find in the tool box—simple to use. Virtually a third hand for tricky soldering jobs. 15 feet 5-core 18 s.w.g. ERSIN MULTICORE SAVBIT alloy in a continuous coil used direct from free-standing dispenser.

2/6 each

**SAVBIT ALLOY**  
saves wear on  
soldering iron bits

### SAVBIT SIZE 1 CARTON

Contains approximately 45 feet of 18 s.w.g. SAVBIT. It is also supplied in 14 s.w.g. and 16 s.w.g. Obtainable from radio and electrical stores.

5/- each



### BIB WIRE STRIPPER AND CUTTER

Strips insulation without nicking wire, cuts wire cleanly, adjustable to most thicknesses. Splits extruded plastic twin flex.

3/6 each



## MULTICORE SOLDERS LTD.

MULTICORE WORKS · HEMEL HEMPSTEAD · HERTS. (BOXMOOR 3636)

# The Progressive PORTABLE

By R. F. Graham

WITH the Class B output stage, the output transistors are so operated that they pass very little current when no signal is present. Current rises in proportion to volume, and the Class B output stage will provide very much more power with greater economy of current, than was available from the single transistor.

Both driver and push-pull output stages are shown in Fig. 7, but the OC71 driver stage (Tr3) will already be present, and will have been tested. Converting to the push-pull stage is thus quite an easy modification.

The output transformer T1 is already fitted, and the driver transformer T2 is located as in Fig. 10, taking care to position it so that the coloured leads emerge as in Fig. 11. The 2.7k $\Omega$  resistor R10 wired to the collector of the OC71 is removed, and the driver transformer primary is wired in its place.

Other components and wiring, as in Fig. 7 can then be added. The physical arrangement should agree with Figs. 10 and 11.

Take care that the centre taps of both transformers are correctly connected. In addition, it is only necessary to connect the 6.8k $\Omega$  (R22) and 220 $\Omega$  (R23) resistors, and the additional OC72 (Tr6). The 100 $\mu$ F capacitor C16 is also added. The 50 $\mu$ F capacitor C10 originally used with the Class A OC72, now decouples the negative battery line to all earlier stages, and becomes C15 of Fig. 7 subsequent diagrams.

When the stage is finished, a meter in one battery lead should show approximately 10mA to 12mA or so, with no station tuned in. As a station is

*This receiver is built in successive stages, each new stage adding to the performance of the set and culminating in a six-transistor, two waveband portable.*

CONTINUED FROM PAGE 745 OF THE DECEMBER ISSUE

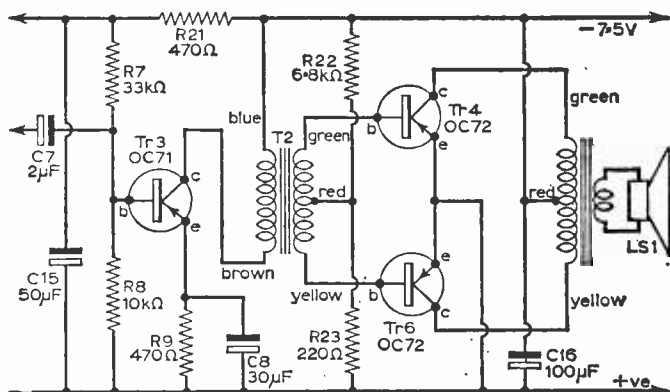


Fig. 7: The driver and Class B push-pull output stage.

tuned in, and volume is increased, the current will rise. On peaks, with average volume, it will jump up to 20mA to 25mA or so. If maximum volume is obtained from a powerful local station, peaks of current may be considerably higher than 25mA. For many purposes indoors, sufficient volume will give peaks of only 15mA or so.

Reproduction should be of good quality. If the no signal current is very low, and results are distorted, reduce the 6.8k $\Omega$  (R22) resistor slightly in value. Should the no signal current be high, the 220 $\Omega$  (R23) resistor is probably too high in value, or the 6.8k $\Omega$  resistor too low. Normally, no adjustment to these values should be wanted.

When the set is found to work correctly, negative feedback may be added to driver and out-

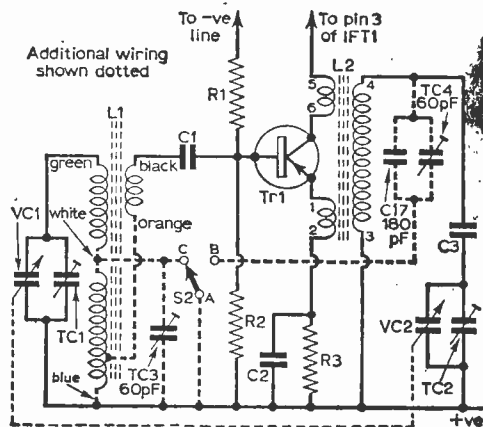


Fig. 8: The circuit for dual-wave coverage.

## SUMMARY OF REQUIREMENTS FOR FOURTH, FIFTH AND SIXTH STAGES

### Driver and Class B Push-Pull Output (Fig. 7)

Resistors: R20-22  
Capacitors: C15-C16  
Transistor: Tr6  
Transformer: T2

### Long Wave Coverage (Fig. 8)

Capacitors: C17, TC3, TC4  
Inductor: l.w. winding for L1  
Switch: S2

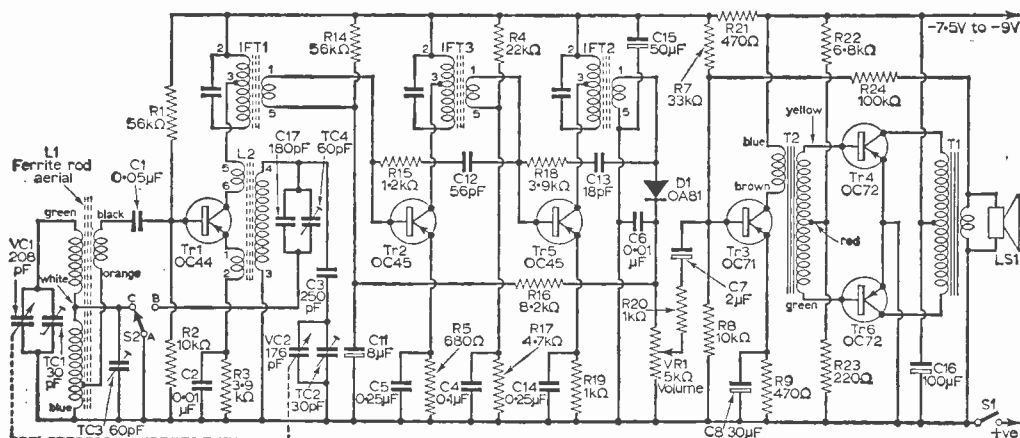


Fig. 9: The complete 6-transistor, dual-wave receiver circuit.

put stages. This is obtained by means of the 100kΩ resistor R24 in Figs. 9, 10 and 11.

One loudspeaker tag is returned to the "earth" line, as in Fig. 10. The 100kΩ resistor is taken from the other loudspeaker tag, to the OC71 base

(Fig. 11). There should be a slight drop in volume, as the resistor is connected. If oscillation results instead, switch off and reverse the two wires which go from the output transformer secondary to the loudspeaker.

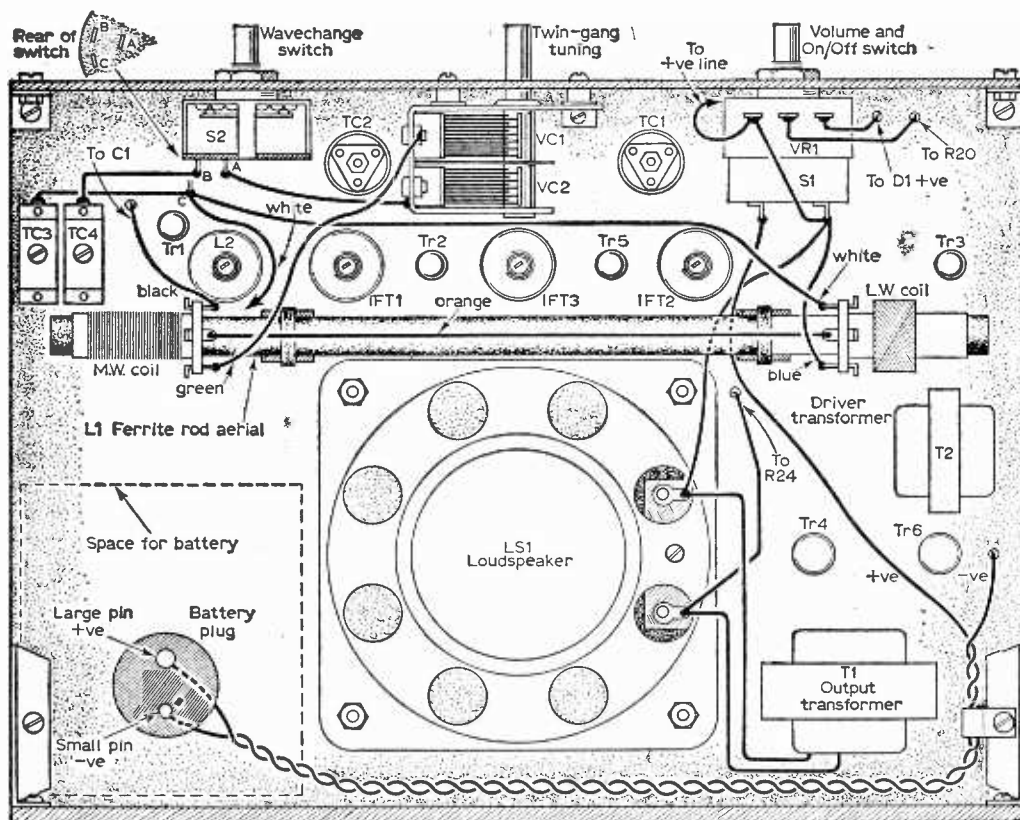


Fig. 10: Layout of major components on the rear of the panel.

## PCR COMMUNICATION RECEIVERS

Manufactured by Pye and Philips. One of the Army's most versatile and sensitive sets. RF stage and 2 of IF using 6 British I.O. type valves. Large 180 degrees illuminated and Calibrated Dial. Flywheel tuning with locking device. Aerial trimmer. Tone and volume controls. Band switch from panel jacks for speaker or phones. In black metal case, size 17" L x 8" H x 10" D. Model PCR2 covers 6-22 Mc/s, 200-550 metres and 850-2,000 metres. £5.19.6. Model PCR3. As PCR2 but has 2 Short Wave Bands. 2.0-7.0 Mc/s and 7.0-21.0 Mc/s and Medium Wave Band 190-550 metres. ONLY £5.5.0. Every receiver aerial tested before despatch. Add 10/6 carr. Both types used, but excellent condition. Designed to operate from bulky external power supply, but any set can be fitted with BRAND NEW COMPONENTS INTERNAL PACK for 200/250 v. A.C. at extra cost of £2. S.A.E. for illustrated leaflet.



**2,000 O.P.V. MODEL TP-10**  
Reads A.C. & D.C. Volts up to 1,000; D.C. Current to 500 mA; Resistance to 1 Meg; Capacitance to 1  $\mu$ F; Decibels from -20 to +36; Output Jack for Audio Measurements. Size 9  $\frac{1}{2}$  x 5  $\frac{1}{2}$  x 1  $\frac{1}{2}$  in.  
£3.19.6



**20,000 O.P.V. MODEL TP-5S.**  
Reads voltage up to 1,000 D.C. at 20,000 ohms per volt and A.C. at 10,000 O.P.V.; D.C. Current to 500mA; Resistance to 10 Mers.; Capacitance to 0.1  $\mu$ F; Decibels from -20 to +36. Size 3  $\frac{1}{2}$  in. x 5  $\frac{1}{2}$  in. x 1  $\frac{1}{2}$  in. £5.19.6



**30,000 O.P.V. MODEL 500.** Volts up to 1,000; D.C. at 30,000 O.P.V. A.C. at 20,000; 12 Amps D.C. Current; 60 Megs Resistance; -20 to +36 dBs; Internal buzzer short circuit warning; Size 3  $\frac{1}{2}$  in. x 6  $\frac{1}{2}$  in. x 2  $\frac{1}{2}$  in. £8.19.6

All New Stock, with leads, probes and internal batteries. 6 months' guarantee backed by full service facilities. Details S.A.E.

**DOUBLE BEAM OSCILLOSCOPE TUBES, TYPE CV-1596.** Equivalent to Cossor 09D (as used in Oscilloscopes by Cossor 339 series) and Hartley & Erskine (13 series). Listed £12. BRAND NEW IN MAKER'S CRATES. ONLY 25/- (carriage 5/-).

**LAVOIE CUF WAVEMETER MODEL 165.** Coverage 375/725 Mc/s. Complete with correct Calibration Chart. First-class condition. Battery operated and portable. Size 11 x 8 x 7  $\frac{1}{2}$  ins. ONLY £3.19.6 (carriage 7/6).

**AMERICAN DISK TELEPHONE,** complete with handset. Non-dial type but has internal bell. Ideal for extension or intercom. BRAND NEW. ONLY 30/- (post 4/-).

**ACOS 39/1 STICK MIKE** with screened lead and table stand. ONLY 32/6 (post 1/6).

**CRYSTAL DESK MIKE** with screened lead and built-in stand. ONLY 15/- (post 1/6).

**BC221 FREQUENCY METERS.** The famous American crystal controlled frequency measuring standard. Coverage 125 K/s - 20 Mc/s. With original Calibration Book. Perfect order. ONLY £16.

**MINIATURE MOTORS.** Ideal for models. Operates on 3-6 volts D.C. Size 1  $\frac{1}{2}$  x 1 x 1  $\frac{1}{2}$  in. plus  $\frac{1}{2}$  in. spindle. BRAND NEW. 5/- or 6 for 25/-.

**SPRAGUE CONDENSERS.** Metal cased, wire end. New 0.01 mfd. 1,000 volt, and 0.1 mfd. 500 volt. 7/6 per dozen. Special quotes for quantities.

**12 VOLTS AMERICAN DYNAMOTORS.** Deliver 220 volts at 100 mA. Size 5  $\frac{1}{2}$  in. x 3  $\frac{1}{2}$  in. diameter. Ideal for running Electric Shaver etc. for Car battery. ONLY 32/6 (post 2/6).

**20/- CONSTRUCTOR'S PARCEL.** Assorted colours wiring wire, solder, resistors, condensers, volume controls, tag panel. ALL NEW (post 2/6).

**RESISTORS.** 100 assorted values our choice. NEW, 7/6.

**CONDENSERS.** 100 assorted mica and silvermica. NEW, 10/-.

## TRANSISTORISED INSULATION TESTERS




Size 7 in. x 4  $\frac{1}{2}$  in. x 4 in.  
batteries and test leads.  
S.A.E. for illustrated details.

The latest technique for checking insulation of electrical circuits, appliances and components. One handed operation (no turning of generator), a Transistor DC-DC converter being employed to supply the high potentials. Three Testine voltages, 100, 250 and 500, to measure up to 500 megohms. Complete with leather carrying case. Internal ONLY £17.10.0

## TEST METERS FOR EVERY PURPOSE & POCKET


### P.W. "CELESTE 7" RECEIVER

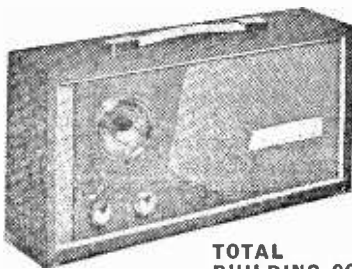

Build this latest P.W. seven transistor portable, as described in June and July issues. Medium and Long waves, with output of 1 watt from large 7 x 4 in. loud-speaker. Internal high gain aerial with car aerial socket. All components sold separately—parts list S.A.E.

**TOTAL BUILDING COST £9.19.6**

### "POCKET 4" TRANSISTOR RECEIVER

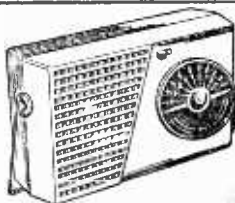

Uses miniature speaker, proper tuning condenser, and volume control. Built-in aerial makes unit efficient and portable. Ideal for the beginner. Full medium wave coverage. All components and case for only 42/6 (P. & P. 2/6). Ten-page constructional book free with parts or separately 1/6. S.A.E. for parts price list.

### BATTERY CHARGER

6 v. or 12 v. at 3/4 amps. Fused and fitted with Ammeter and Voltage Selector. Lustrous metal case finished attractive handpainted blue. Ready for use with mains and output leads. ONLY 55/- (Post 3/6).

### PORTABLE A.C. VOLTMETER

First Grade Moving Iron with 6 in. Mirror Scale. Reads up to 150 volts A.C. 400 and 1200-2400 cycles. In substantial oak case with removable lid. Overall size 8  $\frac{1}{2}$  x 8  $\frac{1}{2}$  x 5  $\frac{1}{2}$  ins. BRAND NEW. ONLY 25.

**COSSOR TYPE 1035 DOUBLE BEAM OSCILLOSCOPES.** A few only of these modern scopes, overhauled and in perfect order. ONLY £45. Further details on request.

**PANEL METERS.** 25 microamps D.C. 2  $\frac{1}{2}$  in. Proj.-circular 59/6. 50 microamps D.C. 2  $\frac{1}{2}$  in. Flush circular, 59/6. 100 microamps D.C. 2  $\frac{1}{2}$  in. Flush circular, 59/6. 40 amps D.C. 2 in. Proj. circular, 7/6. 300 volts A.C. 2  $\frac{1}{2}$  in. Flush circular, 25/-.

**RECORD INSULATION TESTERS.** Read up to 20 meg. at 500 volts pressure. Overhauled and in perfect order. ONLY £8.10.0

**TELESCOPIC AERIAL.** 8 sections 30 in. open, 5 in. closed, with 3 in. projection. Chromium plated and ideal for a variety of uses. ONLY 10/6.

**HARRIS ELECTRONICS**  
(LONDON) LTD

138 Gray's Inn Road, London, W.C.1  
Phone TERminus 7937

Please include carriage costs on all items.  
(Open until 1 p.m. Saturdays). We are 2 mins. from High Holborn  
(Chancery Lane Station) and 5 mins. by Bus from King's Cross.



# HOME RADIO

(MITCHAM) LTD.

Our cartoon is prompted by a recent request for our catalogue from a Persian Gentleman. It ran as follows:


Dear Sir, Mrs.,

Please send pure your general catalogues, addresses to ...

and then followed eleven addresses. No money was enclosed so we thought it might be a case of barter.

We tried to conjure up the list of items we might receive. We thought of Hookabs, Fezes, Yashmaks ... and then we thought he might send us a small Harem, roof garden size. My fellow directors and I had almost finished washing a dozen catalogues in rose water to make sure they were pure, when our wives got to hear about it. Well, fellow sufferers, you know wimmen ... no sense of humour! However, we can still dream. In the meantime a Happy New Year, and if it's not too late, a Merry Christmas!

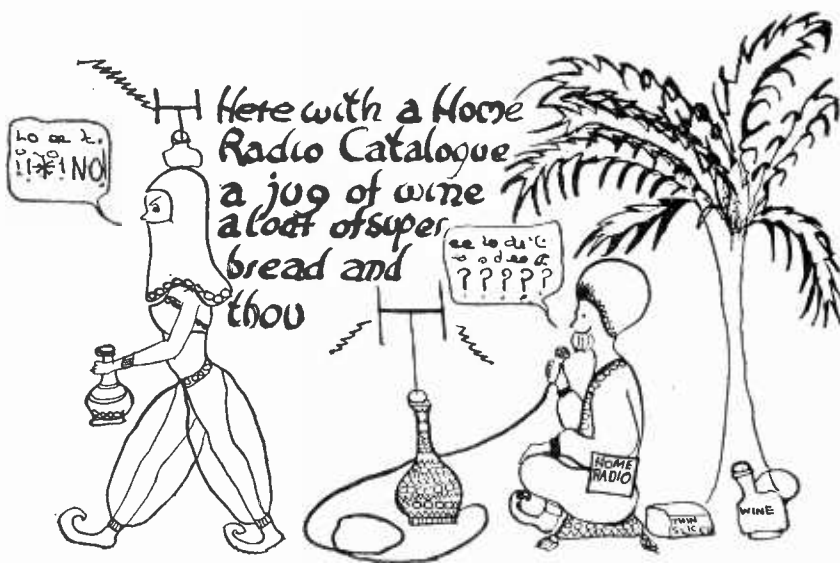And don't forget we still have some excellent catalogues (unwashed) at 3/6 post paid



**HOME RADIO LTD.**

Dept. PW, 187 London Rd.,  
Mitcham, Surrey

## WEYRAD

### 6-TRANSISTOR 2-WAVE SUPERHET RECEIVER MODIFICATIONS NOW AVAILABLE FOR 500 mW OUTPUT

#### ROD AERIAL—RA2W

6 in. long, 3/8 in. diameter, connections to tags on Coils. For 208pF tuning capacity. Complete with Car Aerial Coil ... 12/6

#### OSCILLATOR COIL—P50/1AC

M.W. covered with 176pF tuning capacity, L.W. by extra padder ... 5/4

#### I.F. TRANSFORMERS


1st and 2nd Stage—P50/2CC ... 5/7  
(2 required)

3rd Stage—P50/3CC ... 6/-

DRIVER TRANSFORMER—LFDT4 ... 9/6

OUTPUT TRANSFORMER—OPT1 ... 10/6

PRINTED CIRCUIT—PCA1 ... 9/6

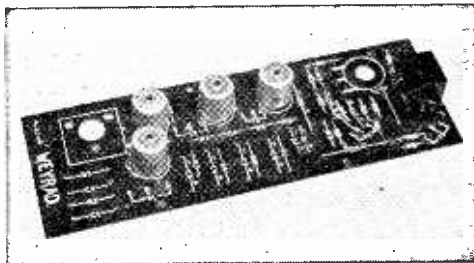

In response to many requests we have redesigned the output stages to give 500 mW and to enable a standard 3 ohm Speaker to be used. Full details of the simple changes are given on a separate leaflet available on receipt of stamp.

CONSTRUCTOR'S BOOKLET WITH FULL DETAILS ... 2/-

TRANSISTOR A.F. AMPLIFIER TYPE A.F.1—LOW IMPEDANCE INPUT, 3-TRANSISTOR, 500 mW OUTPUT, FULLY ASSEMBLED WITH VOLUME CONTROL ... 63/6

**WEYMOUTH RADIO MANUFACTURING CO., LTD.**

REGENT FACTORY, SCHOOL STREET,

WEYMOUTH, DORSET

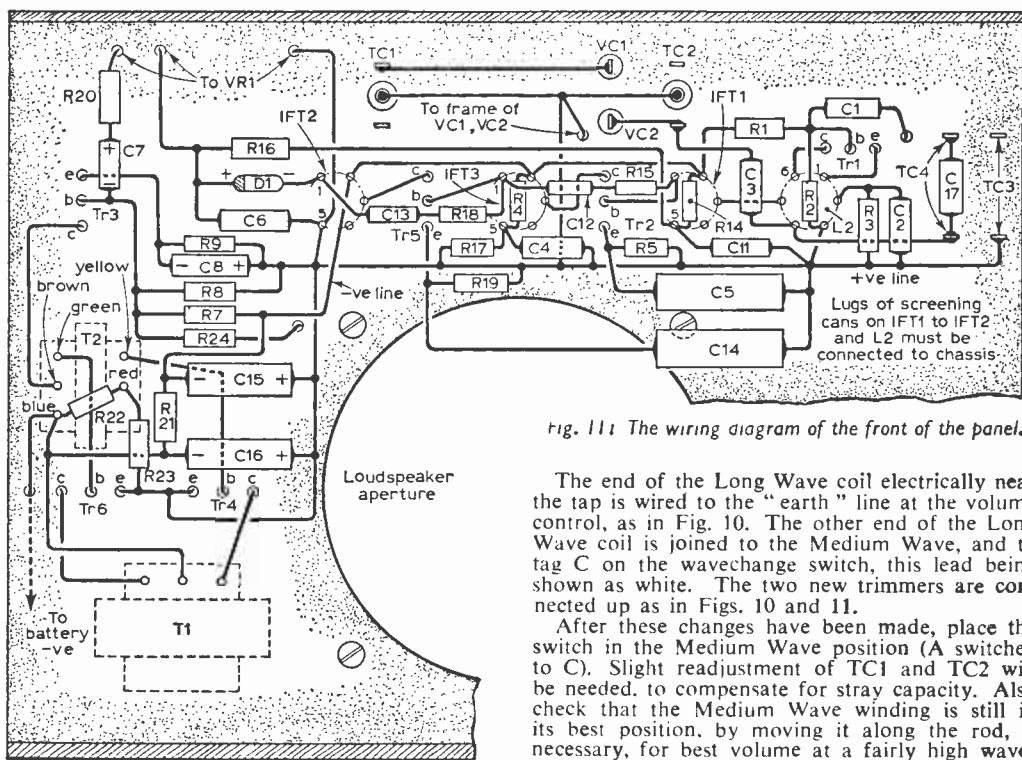


Fig. 11: The wiring diagram of the front of the panel.

The end of the Long Wave coil electrically near the tap is wired to the "earth" line at the volume control, as in Fig. 10. The other end of the Long Wave coil is joined to the Medium Wave, and to tag C on the wavechange switch, this lead being shown as white. The two new trimmers are connected up as in Figs. 10 and 11.

After these changes have been made, place the switch in the Medium Wave position (A switched to C). Slight readjustment of TC1 and TC2 will be needed, to compensate for stray capacity. Also check that the Medium Wave winding is still in its best position, by moving it along the rod, if necessary, for best volume at a fairly high wavelength on the Medium Wave band (tuning capacitor fairly well closed).

Turn the switch for long waves (A switched to

—continued on page 865

### Adding Long Waves

The required additions for dual-wave tuning can be made at any time, irrespective of the number of stages so far provided in the receiver. When adding long waves, no changes have to be made to the other parts of the receiver. In the same way, if long wave tuning has already been fitted at an earlier stage, this has no effect on the other constructional details.

The extra items required, to permit dual-wave coverage, are shown in Fig. 8. A Long Wave winding section is added to the ferrite rod. There is a 180pF fixed capacitor C17, and two 60pF compression trimmers TC3, TC4, in addition to the single pole two-way wavechange switch S2.

The two trimmers, TC3 and TC4, are positioned as in Fig. 10. Holes are drilled to clear the projecting tags, and also the adjusting screws. Bending the tags slightly will hold the trimmers in place.

The actual wiring will be clear from Figs. 10 and 11. Green is used for the beginning of the Medium Wave winding, which already goes to VC1, and is unchanged. Black is used for the coupling winding, and already goes to C1, this being unchanged.

The free end of the coupling winding no longer goes to the "earth" line, but is wired to the tapping on the Long Wave coil; this lead is shown as orange in Figs. 8, 9 and 10.

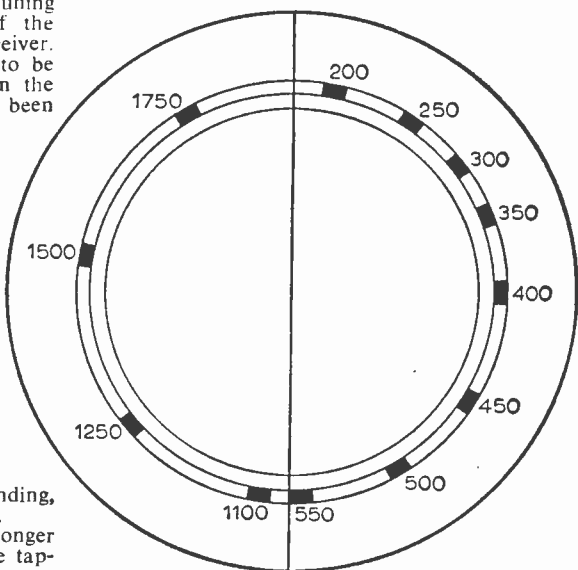


Fig. 12: The tuning scale of the receiver, drawn actual size.

# Alternative Tape Decks for the Malvern

By T. Snowball

Many readers have written to the author of the series of articles which described the construction of this tape recorder, requesting modification details for using different tape decks. For their benefit and for any other readers contemplating building the Malvern, this present article has been prepared, showing how two very popular decks are used with the original design.

THE recorder circuitry, as described in July, August and September issues of P.W. is suitable for all decks with medium to high impedance record play heads and low impedance erase heads. However it only gives correct frequency response for  $3\frac{1}{2}$  in/sec; so below will be found information on how to convert the Malvern tape recorder for use with a very popular deck.

## THE COLLARO STUDIO DECK

The inductance of heads fitted on the Collaro studio deck is similar to those on the B.S.R. deck, thus no change is required to the output stage or input circuit. The bias and erasure circuits will also stay unchanged.

Compensation to the frequency response of the amplifier is necessary for the three speeds. Frequency responses which should be easily

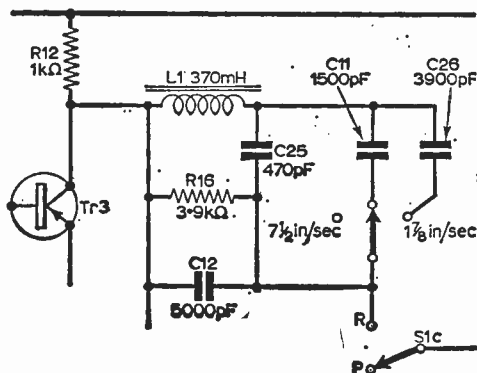


Fig. 1: This shows the circuit changes necessary to obtain the frequency responses given in the text.

obtainable are given below:

$1\frac{1}{2}$ in/sec	80c/s to	4kc/s	} At a recording current of 100μA and bias of 0.9mA
$3\frac{1}{2}$ in/sec	60c/s to	6kc/s	
$7\frac{1}{2}$ in/sec	50c/s to	12kc/s	

The circuit changes to obtain these responses are indicated below: and in Fig. 1.

## On Record

The treble boost inductor L1 has to be tuned to 4, 6 and 12kc/s with a boost of 10dB, involving the addition of two capacitors, C25 and C26, and also changing the value of C11, C12 and R16.

## On Playback

The time constant of the integrator has to be changed from 100μS at  $7\frac{1}{2}$  in/sec to 200μS and 300μS at  $3\frac{1}{2}$  in/sec and 1 1/2 in/sec respectively.

This is achieved by adding C27 and C28, also changing the values of C5 and C4 and R8. See Fig. 2.

This corrects the low frequency end of the characteristic, but some top boost is best applied by varying the value of C13 as shown in Fig. 3.

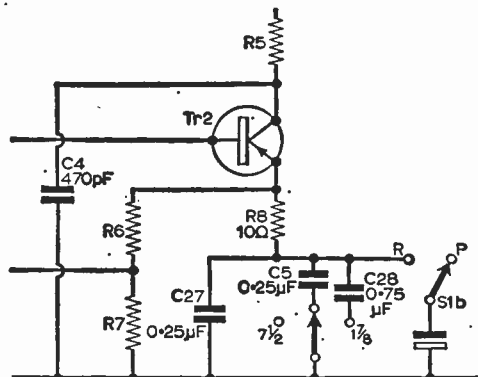


Fig. 2: Changes necessary to alter the time constant of the integrator.

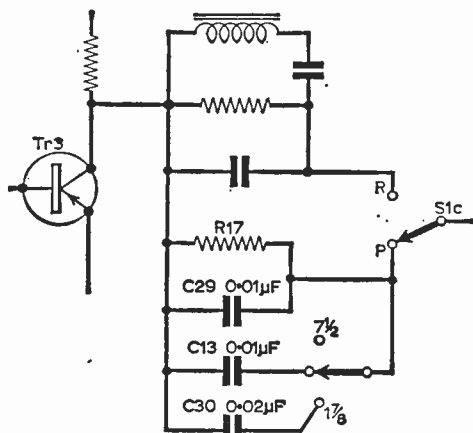


Fig. 3: Varying the value of C13 gives some top boost to the characteristic.

## UNIVERSAL AVOMETERS



Guaranteed perfect working order. Supplied complete with leads, batteries and instructions. Model "1" 34 range £8.19.6 Model "7" 30 range £11.0.0 Registered Post 5/- extra.

**COSSOR 1035 DOUBLE BEAM OSCILLOSCOPES**  
Available in excellent condition, fully checked, £40 each. Carr. 30/-.

## MICROAMMETERS

0-500 microamps. 2in. circular flush panel mounting. Dials engraved 0-15, 0-500 volts. BRAND NEW. BOXED. 15/- P. & P. 1/6.  
**230/250 VOLT A.C. MOTORS**  
4 1/2 x 3in. dia. 90 watts, 5,000 r.p.m. 1/4in. spindle. Brand New. 22/6 each. P. & P. 2/-.

## FIELD STRENGTH METERS

Frequency coverage 1 to 250 Mc/s. Fitted with 200 micro-amp meter. Supplied with telescopic aerial, ear-piece and instructions. 69/6 post paid.

**FIELD TELEPHONES TYPE "P"**  
Suitable for many applications. Generator bell ringing. 2 line connection. With batteries and wooden carrying case. Fully tested. £4.19.6 per pair. Carr. 5/-.

**HEAVY DUTY AUTO TRANSFORMERS**  
0/115/230 volt step up or step down. Brand New, boxed. Ex. U.S.A. 3,000 watt. £7.10.0, carr. 10/-, 7,500 watt. £15, carr. £1.

**FIELD TELEPHONES TYPE "L"**  
Generator bell ringing. 2 line connection. Supplied complete with batteries, ready for use, 69/6 per pair. Carriage 5/-.

## PANEL METERS

100µA	2 1/2" F.M. D.C.	42/6
1 mA	2 1/2" F.M. D.C.	25/-
30/10/30 mA	2 1/2" F.M. D.C.	9/6
350 mA	2 1/2" F.M. D.C.	10/6
15 amp.	3 1/2" F.M. D.C.	39/6
5/0/5 amp.	3 1/2" F.M. D.C.	25/-
300 v.	2 1/2" F.M. A.C.	19/6
300 v.	2 1/2" F.M. A.C.	25/-
500 v.	2 1/2" F.M. A.C.	25/-
120 v.	3 1/2" F.M. D.C.	32/6

Postage extra.

## SILICON RECTIFIERS

400V. p.i.v. 4.7 amp	7/6
200V. p.i.v. 6 amp	5/6
800V. p.i.v. 500 mA	5/6
400V. p.i.v. 500 mA	3/6
7W. p.i.v. 1 amp	1/6

CA 202 miniature silicon rectifiers 1/- each. Discount for quantities. Please add postage.

## JR-101 AMATEUR COMMUNICATION RECEIVER

4 bands covering 550 Kcs to 30 Mc/s continuous. Operation 200/240 volt. A.C. Special features include: Easy to read illuminated slide rule dial—Built in Q multiplier—Aerial trimmer—Calibrated electrical bands—spread on amateur bands 0-100 logging scale—Noise limiter—AVC—MVC selector—stable oscillator and BFO for clear CW and SSB reception—built in edgewise "S" meter. Output for phones or Std. speaker. Brand new guaranteed with operational manual £42, carriage paid. Trade ins welcome.


## P.C.R.2 COMMUNICATION RECEIVERS

Excellent performance for modest outlay. Frequency coverage on three bands 800-2,000 metres, 190-550 metres, 8-22 Mc/s. Output for phone or speaker. Supplied in perfect condition £5.19.6 each. Carr. 10/- The receiver can be supplied with an internal power supply to operate on 200/250 volt A.C. at 39/6 extra or plug in external power supplies are 35/- extra. Full circuit supplied.

## AVO WIDE RANGE SIGNAL GENERATORS

Frequency coverage 50 Kcs to 80 Mc/s in six turret operated ranges. For use on standard A.C. mains. Packed in original transit cases with accessories. Supplied in as new condition, fully checked before despatch, £15. Carriage 10/-.

## NATIONAL H.R.O. RECEIVERS

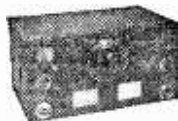

**SENIOR MODEL.** Supplied complete with full set of 9 coils covering 50 Kcs. to 30 Mc/s. Each receiver thoroughly checked and available as follows:—  
**TABLE MODEL.** As new condition £25.  
**TABLE MODEL.** Good used condition £19.10.0

**RACK MODEL.** As new condition £22.10.0

**RACK MODEL.** Good used condition £18.15.0

NB—Rack model is identical to table model with extended front panel to fit a 19in. rack. Carriage £1 extra.

200/250 volt A.C. power supplies for all above receivers, also sold separately. 59/6, carr. 5/-.

## HALLICRAFTER S-36 V.H.F. RECEIVERS

F.M./A.M. 27-143 Mc/s 110 volt A.C. transformer supplied for 230 v. A.C.). Improved version of S-27. Tested before despatch. Brand new boxed with instructional manual. **£40** each. Carr. £2

## LAFAYETTE BRAND TAPES



First grade quality American tapes. Brand new, guaranteed. Discounts for quantities.

5in. 600ft. Std. Plastic	8/8
5in. 900ft. L.P. Acetate	10/-
5in. 1200ft. D.P. Mylar	15/-
5 1/2in. 1200ft. L.P. Acetate	14/6
5 1/2in. 1800ft. D.P. Mylar	21/-
7in. 1200ft. Std. Mylar	12/6
7in. 1800ft. L.P. Acetate	15/-
7in. 1800ft. L.P. Mylar	20/-
7in. 2400ft. D.P. Mylar	25/-

Post 2/- over £3 post paid.

## MULTIMETERS BRAND NEW—FULLY GUARANTEED LOWEST EVER PRICES

Supplied with Leads, Batteries and Instructions.

1,000 Ω/VOLT	20,000 Ω/VOLT
0/15/150/1,000 v. A.C. and D.C.	0/15/50/250/500/1,000 v. A.C. and D.C.
0/100 KΩ etc.	0/500 µA/0/25/500 mA, D.C.
39/6, P. & P. 1/6.	0/50K/500K/5 meg., etc. 97/6, P. & P. 2/6.



30,000 Ω/VOLT	50,000 Ω/VOLT
0/1/10/50/250/500/1,000 v. D.C.	0/10/50/250/500 v. A.C.
0/500 µA/0/10/250 mA, D.C.	0/10K/1 meg./10 meg., etc. £5-10.0. P.P. 2/6.
30,000 Ω/VOLT	0/1/10/50/250/500/1,000 v. D.C. and A.C.
0/500 µA/0/50/500 mA/0/12 amp. D.C.	0/60K/6 meg./60 meg., etc. £8.17.6. Post paid
50,000 Ω/VOLT	0/10/50/250/500/1,000 v. D.C. and A.C.
0/25 mA/2.5/25/250 mA, D.C.	0/10K/10K/1 meg./10 meg., etc. £7.10.0. P.P. 2/6.
100,000 Ω/VOLT	5/2.5/10/50/250/500/1,000 v. D.C.
2.5/10/50/250/1,000 v. A.C.	10/250 µA/2.5/25/250 mA/10 amp. D.C.
20K/200K/2 meg./20 meg. ohm etc.	£8.19.6. Post paid.

Hours of Business: 3 LISLE STREET, 9 a.m.—6 p.m. Half Day Saturday  
34 LISLE STREET, 9 a.m.—6 p.m. Half Day Thursday

## MODEL RX60 AMATEUR COMMUNICATION RECEIVER

Four bands, 550 Kcs-30 Mc/s. Special features, 8 meter-analogue-electrical band spread—internal 5in. speaker—head set socket—tone control—standby switch—3 aerials, loop wire, telescopic—200-250 volt A.C./D.C. Brand new guaranteed with manual £24.15.0 each. Post paid.

## COLLARO/MAGNAVOX STUDIO TAPE DECKS

Latest 1963 model. Fitted with latest bradmatic heads and interlock button. Brand new, guaranteed, with instructions and mings. £10.10.0. Carr. paid.

## MINE DETECTOR No. 4A

Will detect all types of metals. Fully portable. Complete with instructions, 39/6 each. Carr. 10/- Battery 8/6 extra.

## L.T. METAL RECTIFIERS

All full wave, bridge connected. Brand new.

12/18v. 1.5A.	3/9	24/36v. 1A.	7/3
12/18v. 2.5A.	6/3	24/36v. 2A.	13/6
12/18v. 4A.	8/6	24/36v. 1.5A.	45/6
12/18v. 10A.	22/6	36/48v. 6A.	32/6

Please add postage.

## L.T. TRANSFORMERS

All primaries tapped 200/250 volts.

1 Battery Charging.	3.5, 9 or 17 volt. 1 amp.	9/9.
14/3.	Ditto 4 amp.	16/6.
9 or 17 volt. 6 amp.	26/-	

2 Model Type M. 4, 5, 6, 8, 10, 12, 15, 18, 20, 24 or 30 volt. 2 amp. 18/6. Ditto 4 amp. 30/-, Ditto 5 amp. 37/6. Add Postage.

## MINIFLUX TAPE HEADS

Set of three, record, playback, erase. Only 29/6 set. P. & P. 9d.

## MINIATURE PANEL METERS

For 1 1/2in. dia. panel hole.

0/500 µA	39/6	0-1 mA	27/6
0-500 µA	32/6	0-5 mA	27/6

0-300 v. D.C. 27/6  
"S" meter 35/-

## TWIN MOTOR BARGAIN



200/250 volt A.C. Twin concentric spindles operated independently. Either motor reversible. 1440 r.p.m. Brand New. Boxed. Only 12/6 each. P. & P. 2/6.

## CR.100 RECEIVERS

80 Kcs to 30 Mc/s on 8 bands. 200/250 v. A.C. operation. Supplied in perfect working order. £21, carr. 30/-.

## AUTO TRANSFORMERS

Step up—step down. Tapped 0/115/200/250 v. 15W. 9/-, 60W. 12/6; 75W. 15/6, 150W. 18/6, 200W. 27/6, 300W. 42/6, 500W. 67/6, 1,000W. 90/-, Postage extra.

## ERSKINE 13A DOUBLE BEAM OSCILLOSCOPES

Guaranteed perfect working order. £27.10.0, carr. £1.

**G.W. SMITH & CO (RADIO) LIMITED**  
Phone: GERRARD 8204/9135  
Cables: SMITHEX LESQUARE  
3-34 LISLE STREET, LONDON, W.C2



Wide-range Transistorised  
**SIGNAL GENERATOR—Model 27**  
Range 150 Kc/s to 350 Mc/s.

- ★ Accuracy better than 2%
- ★ Directly calibrated
- ★ Battery operated
- ★ Compact and light

**£7.18.6**

with test lead and battery.  
Post and Packing 3/6 extra.

Trade and Export Enquiries Invited


**NOMBREX LTD.** Instruments  
Division 69

## NOMBREX INSTRUMENTATION

Wide-range Transistorised  
**AUDIO GENERATOR—Model 63**  
Range 10—100,000 c/s.

- ★ Laboratory Standard Specification
- ★ Sine and Square Wave
- ★ Direct Frequency Calibration
- ★ Accuracy and Low Distortion
- ★ Calibrated Output Voltage
- ★ Battery Operated and Compact

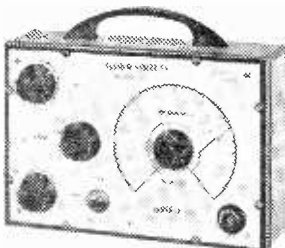**£15.0.0** complete with  
test lead  
Battery 2/3. Post and Packing 3/6.



Wide-range Transistorised  
**C.R. BRIDGE—Model 62**  
6 Ranges: 1Ω to 100MΩ  
1pF to 100μF

- ★ Visual null indicator
- ★ Power factor check
- ★ Electrolytic leakage test
- ★ Battery operated

**£7.2.3**


including battery.  
Post and Packing 3/6 extra.

S.A.E. for full technical leaflets

ESTUARY HOUSE, CAMPERDOWN TERRACE  
EXMOUTH, DEVON. Phone: 3515.
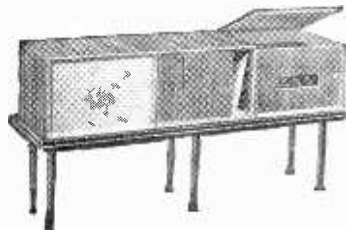
## HOUSING HI-FI?

Nordyk units are part of the wide range of cabinets for every hi-fi purpose. The Speaker cabinet (left) costs £6.15.0, Record cabinet (centre) £5.7.6, and the Equipment cabinet right £6.19.6. Soundly designed, superbly finished, sensibly priced. Send for illustrated catalogue and name of local stockist.



**RECORD HOUSING**

(Dept. P.W.I.), Brook Road, London N22.  
Telephone: BOWes Park 7487/8

Why not give tapes this Christmas?



**LOWEST  
EVER  
PRICES**

**SPECIAL!!  
"LAFAYETTE"**  
7in. Std. 1,200ft., 12/6  
7in. L.P. 1,800ft., 15/-  
7in. D.P. 2,400ft., 25/-

**EXCLUSIVE TO  
GEE'S  
AMERICAN  
"SHAMROCK"**  
Professional quality  
7in. L.P. 1,800ft., 15/6

**SPARE SPOOLS, 4in.,  
5in., 5½in., 2/- each;  
7in. 2/6; 8½in. 5/-.**

Obtainable only from—

**GEE BROS. (RADIO) LTD., Dept. P.W.  
15 LITTLE NEWPORT ST., LONDON W.C.2  
(Adjoining Leicester Sq. Tube) GER 6794/1453**



5in. Std.	600ft.	...	8/6
7in. Std.	1,200ft.	...	12/6
5in. L.P.	900ft.	...	10/-
5½in. L.P.	1,200ft.	...	12/6
7in. L.P.	1,800ft.	...	15/-
4in. D.P.	600ft.	...	9/-
5in. D.P.	1,200ft.	...	15/-
5½in. D.P.	1,800ft.	...	22/6
7in. D.P.	2,400ft.	...	25/-

**"GEE'S" ACCESSORY KIT, 1 "BIF"**  
Splicer, 1 Splicing Tape, 3 Leader Tapes (3 colours), 10 Retaining Clips. Packed in plastic container. PRICE 32/6. While stocks last.

**COLLARO "STUDIO" TAPE TRANSCRIBERS.** Brand new in original cartons. 3 speeds. 1½, 3½, 7½ i.p.s. 3 motors, digital counter, etc. Complete with instructions and fittings. A.C. 200/250 v. operation. **SPECIAL PRICE 10 GNS.** Carr. paid.

P. & P. 2/- per order (over £3 post free). Other types available. S.A.E. for Bumper Tape and Accessories list.

Special discounts for quantities.

Fig. 4: The re-designed transformer in circuit.

This completes the modifications for use with the Collaro deck, but since the article was originally published, a considerable number of constructors have requested details on how to make the recorder completely portable.

Obviously a battery driven tape deck is the main requirement here, and the Garrard Battery Tape Deck, which runs at  $1\frac{1}{2}$  in/sec and  $3\frac{1}{2}$  in/sec and is powered from a 9V battery, supplies this need.

### THE GARRARD BATTERY TAPE DECK

The modifications required when this deck is used are similar to those just given for the Collaro deck. However, only two speeds are involved, and because of the lower inductance heads the output stage can be advantageously changed.


In the output stage there are at least three possibilities, each one having its own particular merit.

- Leave the output circuit as designed.
- Leave the output circuit unchanged but change the head transformer.
- Change the output circuit and head transformer.

Method (a) is perfectly correct, but it uses expensive output transistors, which are not needed unless high power (0.35 to 2W) is required. It also demands large batteries, PPI or "Lantern" type cells as a minimum.

Considering (b), there is a case for redesign of the output transformer, because of the different head inductance.

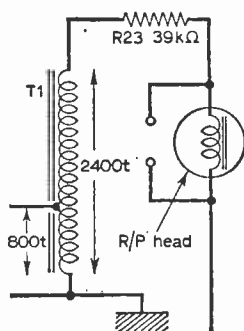This head inductance is given as 0.11H with a recording current of 60-200  $\mu$ A r.m.s. If the 10dB of top boost is used then, as the amplifier will give out 3.8V r.m.s. in this condition; a normal output is 10dB down on 3.8V r.m.s., or 1.25V, which should give a recording current of approximately 100  $\mu$ A.



The impedance of the head at 5kc/s is  $3.5k\Omega$  from  $XL=2\pi fL$ . So in order to get a constant recording current the series resistor is made ten times larger, i.e.  $39k\Omega$ . The transformer output of 3.9V r.m.s. will give a recording current of 100  $\mu$ A. Therefore the output transformer ratio should be

$$\frac{3.9}{1.25} = 1/3.$$

Winding the transformer on the same core L.A1. now means that a higher primary inductance can be used, thus demanding less amplifier current and reduced risk of core saturation at low frequencies.

The redesigned transformer should therefore have 2,400 turns of 44 s.w.g. enamelled wire, tapped at 800 turns. This gives a primary

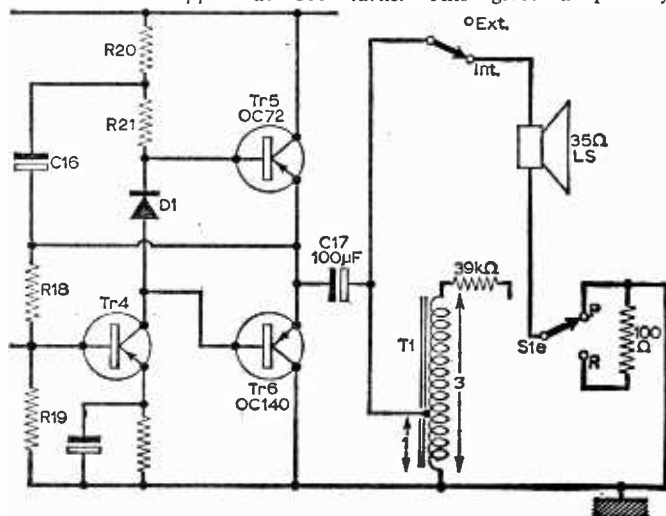


Fig. 5: The output stage for a 35Ω speaker.

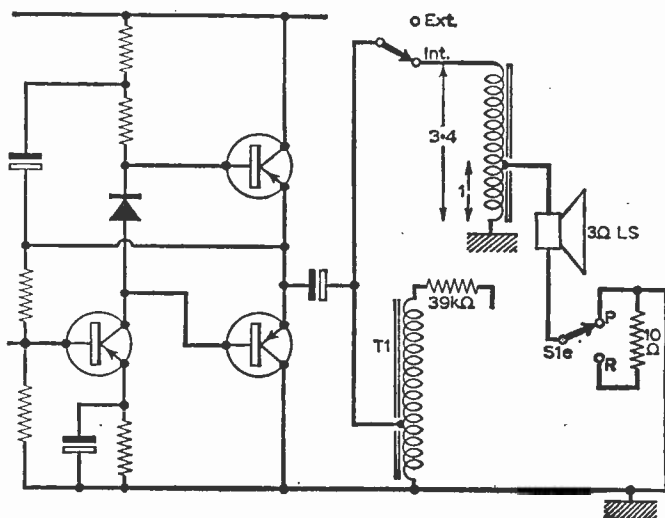


Fig. 6: The output stage for a 3Ω speaker.

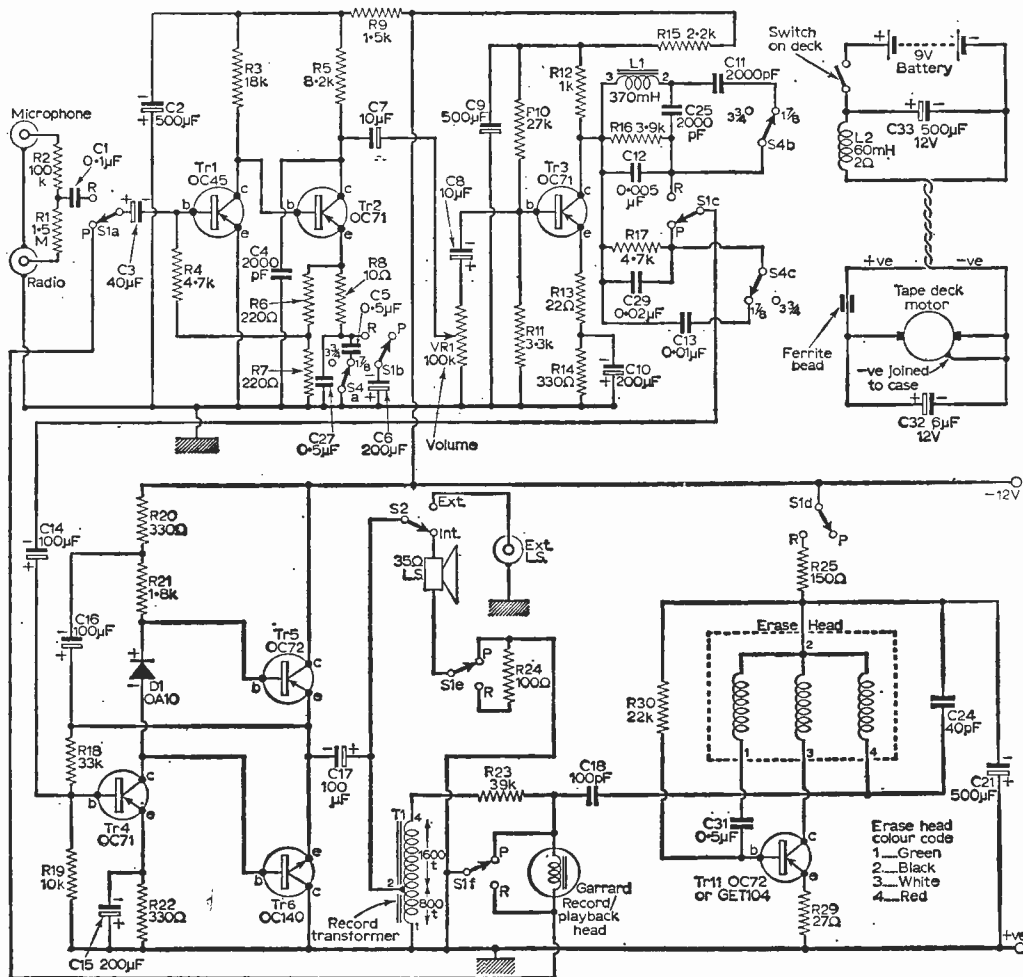


Fig. 7: The modified circuit for the Garrard deck.

inductance of 220mH, and presents a load of 60Ω at 50c/s, whereas the original transformer only presented 12Ω.

Now for method (c). The last fact mentioned above means that with the rewind transformer the circuit can be simplified for less battery drain.

The modification limits the audio output on playback to 350mW which is, of course, eminently suitable for a small portable tape recorder. In this modification the two power output transistors are omitted and the head transformer is driven directly from the OC140 and OC72 as shown in Fig. 5.

The loudspeaker can still monitor on record, but the loading must be matched by means of an output transformer or a 35Ω loudspeaker must be used. If a 3Ω loudspeaker is used, the transformer

ratio needs to be  $\sqrt{\frac{35}{3}} = 3.4/1$ , with a primary

inductance of at least 50mH. See Fig. 6. This can be easily made by the constructor because, as the inductance required is low, so are the number of

turns. And on a normal loudspeaker transformer core, which is about  $\frac{1}{2}$ in. x  $\frac{1}{2}$ in., the required inductance is given by 250 turns, tapped at 70 turns. The gauge of wire is chosen so as to fairly well fill the bobbin, 30 s.w.g. is a good guide. C17 can be reduced to 100μF because of the higher output impedance.

So to review these three types of output stages:

- Is suitable if large batteries and output power is needed, and requires no extra work.
- Is the best theoretical answer and is recommended.
- Is suitable if reduced battery and audio power satisfies the constructor's requirement.

Now to finish the circuit modifications.

#### On Record

The treble boost circuit should be similar to the Collaro circuit, keeping only C25 and C11.

C25=200pF, C11=200pF, C26=not used.

Also on record, which of course includes the function of erasure and bias, the circuit needs to



### Infra-Red Heaters

Make up one of these latest type heaters. Ideal for bathroom, etc. They are simple to make from our easy-to-follow instructions—uses silica enameled elements designed for the correct infra-red wave-length (3 microns). Price for 750 watt element and metal casing as illustrated 19/6, plus 2/6 post and insurance.

### Limited Quantity Only

Waterproof heater wire, 16 yds. length, 70 watts. Self-regulating temperature control, 10/-, post free.

### Microphone Inserts


American made, Dynamic type. Real bargain at 3/6, plus 6d. postage

Crystal type 5/6.


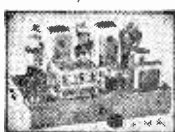
### Beginner's Superhet

As supplied to many schools and colleges. A simple basic superhet—easy to understand and which can be progressively extended—Ideal for students—components include—valves—metal rectifier tuning condenser—I.F. transformers, etc. In fact complete superhet except speaker. Price £3 plus 3/- post and insurance. Data included free or sep., 1/6.



### TV CAMERA LENSES

18 mm. lens in mount, f/5.5 and triple anastigmatic suitable for vidicon tube, £3.10.0.

This fine cabinet as illustrated but less control knobs is available this month at a special snip price of 15/6, plus 4/6 post and insurance. Size is 13 1/2" x 9 1/2" x 4 1/2" and it is nicely covered in two tone fabric.



### Cabinet Snip

### Yaxley Switches

1 pole, 2 way	2/-	1 pole, 3 way	2/-
1 pole, 4 way	2/3	1 pole, 5 way	2/6
1 pole, 7 way	3/-	1 pole, 9 way	3/-
1 pole 11 way	3/-	1 pole, 12 way	3/3
2 pole, 2 way	2/3	2 pole, 4 way	2/6
2 pole, 5 way	4/-	2 pole, 6 way	3/6
2 pole, 12 way	5/6	3 pole, 3 way	2/-
3 pole, 6 way	4/-	3 pole, 12 way	5/6
4 pole, 2 way	2/-	4 pole, 3 way	3/6
4 pole, 4 way	3/6	4 pole, 5 way	5/6
4 pole, 6 way	6/6	4 pole, 11 way	10/6
4 pole, 12 way	11/6	5 pole, 3 way	4/6
5 pole, 6 way	8/-	5 pole, 12 way	14/6
6 pole, 2 way	3/6	6 pole, 3 way	4/6
6 pole, 6 way	9/6	6 pole, 11 way	16/6
6 pole, 12 way	17/6	8 pole, 2 way	4/6
8 pole, 4 way	8/6	8 pole, 6 way	11/6
8 pole, 12 way	23/6	12 pole, 2 way	8/6
12 pole, 5 way	16/6	12 way fader	3/6
1 pole, 6 way incremental	shorting, 3/6		

### Meter Bargains

2in. Moving Coil 500 micro-amp. f.s.d. Brand new, 17/6, plus 1/- Packing and Insurance.

### Bargains For Callers

We always have plenty, e.g., T.V. Cabinets, ideal for shelves etc., 2/6 each.

### CABINET & PICK-UP

Made for a famous company intending to make a Battery Record Player but changing their minds. This is an extremely fine looking cabinet, must have cost at least £2 to make. It is complete with handle and fasteners as illustrated. Also included in the parcel is a Cosmocon pick-up with crystal cartridge and supreme stylus. Both items new and perfect. Only 19/6, plus 4/6 post and insurance.



### TV CABINETS for callers only

#### FOR 17in. MODEL

Really well made and finished with polyester lacquer. Originally intended for Philco sets.

Price 5/-

SHELLS available for 21in. models, beautifully polished and finished, but would need a moulded front and back to complete.

Price 7/6

for callers only

### THIS MONTH'S SNIP




1 1/2 volt tape motor with pulleys and drive mechanism, volume control, record—erase—playback—off lever action switch. Every item listed above is warranted in good working order and if not so, will be replaced free of charge.

The whole offered at less than the value of the amplifier 55/-, plus 2/6 carriage. Plastic case with carrying handle as illustrated, 12/6 extra.
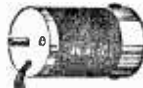
### MAINS MOTOR

Suitable to drive fan, small model drilling machine etc. A.C. only, and starting. Size 2in. diameter by 2in. long (plus spindle). Only 9/6, plus 2/6.

Tape recorder type motor synchronous working 230 volts, 12/6, plus 2/6 post. Ditto but more powerful 20/-, plus 2/6.



### "CORONET" Mk. III

An excellent pocket set using 3 MAT transistors for the oscillator and I.F. stages and 3 function types including a matched pair for the output stage. It fully covers the medium-wave band and that part of the long-wave band to bring in R.B.C. Light. The circuit includes a highly efficient slab aerial and Pleesey tuning condenser incorporating wave change switch. Overall size approximately 4 1/2 x 2 1/2 x 1 1/2. Supplied complete with carrying case, this two-way pocket set is available whilst stocks last at the very low price of £3.12.6.



### MULTI-METER BARGAIN

Model number EP10K. Extra wide scale fitted corner wise for compactness, extra accurate as it uses 1% components. Sensitivity 10,000 ohms per volt A.C. and D.C. ranges 11 C. voltage up to 1.2KV in 5 ranges. A.C. voltage up to 1.2KV in 5 ranges. D.C. current up to 300mA in 3 ranges. Resistance up to 2 meg. Capacities .005 to .15 mfd and decibels. Complete with full instructions and test plugs and battery for ohms range. A real bargain not repeatable once stocks cleared. Price £3.19.6. Carriage and insurance 5/-.

### BUILDING A DOUBLE BEAM 'SCOPE'

We can supply VCR517 brand new, 9/6, plus 6/6 carriage and packaging, also 1750 v. mains transformer, 22/6, plus 8/6 carriage and packaging. Other parts in stock, send for list.

### Electric Blanket Spares

We carry a good stock of elements, thermostats and switches etc. for Electric Blankets. Send S.A.E. for list.

### Timer Kit

Special offer of all components except metal box to make mains operated interval timer for photography etc., 12/6 plus 2/6 post.


### 5000 mfd Condensers

12 V., working—Pleesey—perfect, 2/- each, 18/- doz.
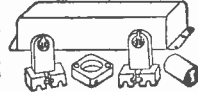
### Fluorescent Light Bargain

For pelmet or window lighting, etc. Kit of parts comprising: choke, two lamp holders, starter holder and starter.

40 watt, 19/6; 80 watt, 27/6. Plus 2/6 post and insurance.



### Building A 'Scope,



3in. oscilloscope tube, American made type No. 3FP7, 6.3 v. 0.6 amp. heater, electrostatic deflection. Brand new and guaranteed with circuit diagram of scope, 15/- each, plus 2/6 post and insurance.

### Adjustable Thermostat



Suitable for Industrial or domestic purposes, such as controlling furnace oven, immersion heater, etc. Can also be used as a thermostat or fire alarm. Made by Sunvic these are approximately 17in. long and adjustable over a range 0 to 550 F. The contacts are rated at 15 amps., 230 volts, and the adjustment spindle, which comes to the top, can be fitted with a flexible drive for remote control or just a pointer knob for local control. Listed at £3 or £4 each, these are offered at only 9/6, plus 2/6 postage and insurance.

### Ice-Stat

This is a small thermostat which cuts on and off at around freezing point. Has many uses, one of which could be an ice warning device to be fitted under your motor car. Price 7/6, post 1/-.

### Refrigerator Thermostat

Standard type with adjustment for all normal refrigerator temperatures, 7/6, plus 1/- post.

### Simmerstat Heater Regulator

Suitable to control elements, heater, soldering irons and boiling rings up to 2,500 watts. Complete adjustable, normal price 55/- each, special snip price 12/6, plus 1/6 postage and insurance.

### 15 amp. Thermostat

Adjustable over a fairly wide range of temperatures but set for 70 F., suitable for wall mounting to control room heaters. Exceptional bargain at 9/6, plus 1/- post and insurance.


### B29 Receivers

A fine receiver made by the famous Marconi Company. Covers the shipping bands 15 K/c to 560 K/c in four switch stages. Has vernier tuning and all refinements. Works off A.C. mains with internal power pack. These sets need servicing, but we are selling at less than spare parts value i.e., £5.0.0, plus 30/- carr.

**ELECTRONICS (CROYDON) LTD**  
266 LONDON ROAD, WEST CROYDON, SURREY  
(Opposite SAVOY CINEMA)

LATEST HIGH QUALITY COMPONENTS FROM THE MAXI-Q RANGE . . . . .

TESTED AND TRIED OVER 5 FREQUENCY RANGES

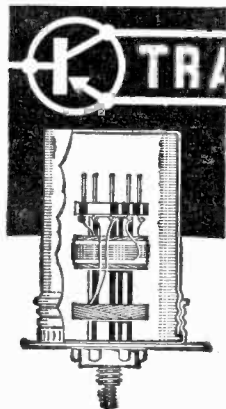

## TRANSISTOR DUAL PURPOSE COILS

Coils for transistor superhets or converters, with or without an R.F. stage and using 465 Kc/s or 1.6 Mc/s I.F.

- ★ Noval B9A Based for Plug-in application—Screw threaded for Chassis application.
- ★ Formers moulded in low-loss polystyrene for best results.
- ★ Each coil is packed in an aluminium container which may be used as a screening can.
- ★ Brass threaded adjustable iron-dust cores.

The following colour code identifies the coils:

- BLUE — Aerial coil with base input windings.
- YELLOW — Interstage R.F. coil with couplings.
- RED — Oscillator coil for 465 Kc/s I.F.
- WHITE — Oscillator coil for 1.6 Mc/s I.F.

PRICE 4/9d. each

Coverages: Range 1T—15/4 Mc/s; 2T—515/1,545 Mc/s; 3T—1.67/5.3 Mc/s; 4T—5/15 Mc/s; 5T—10.5/31.5 Mc/s.

Full technical details now included in Technical Bulletin DTB.4—1/6d.

- IFT.13 Miniature 465 Kc/s. I.F. Transformer.... 7/6d. each
- IFT.14 Miniature 465 Kc/s. Last I.F. Transformer 7/6d. each
- IFT.16 Miniature 1.6 Mc/s. I.F. Transformer.... 6/6d. each
- IFT.17 Miniature 1.6 Mc/s. Last I.F. Transformer 6/6d. each

GENERAL CATALOGUE covering full range of components, send 1/6d. in stamps. PLEASE SEND S.A.E. WITH ALL OTHER ENQUIRIES.

DENCO (CLACTON) LTD. (DEPT. P.W.), 357/9 Old Road, Clacton-on-Sea, Essex

## It's so easy to build TAPE EQUIPMENT with a MARTIN RECORDAKIT and Audiokits for Hi-Fi, too!

With a Martin Recordakit you can either build a complete tape recorder (in which case you can have it with deck and portable type case if desired) or assemble a pre-amp to connect the deck to existing amplifier system. There are Recordakits for two or four track Collaro, Magnavox and B.S.R. decks. When finished, you will enjoy performance and quality of wonderfully high standards more usually associated with far costlier equipment and with Audiokits you can build Hi-Fi to your personal requirements.

- Printed circuit board sections supplied complete tested and with valves in position on Recordakits.
- Kits well packed in fitted cartons and complete down to last screw and measured length of wire.
- Full assembling and operating instructions.



THE KITS YOU BUY WITH SUCCESS BUILT IN

- AMPLIFIERS FOR COMPLETE INSTRUMENTS
- PRE-AMPS TO ADD TO HI-FI
- 2 TRACK AND 4 TRACK
- AND NOW MARTIN AUDIOKITS

The newest thing in Hi-Fi construction systems

### MARTIN AUDIOKITS

A brilliant new technique enabling you to combine, interchange and add stereo by means of cleverly designed transistorized units to produce equipment just as you want. The range of kits so far includes:

- 5-STAGE SELECTOR SWITCH WITH MATCHING INPUTS.
- PRE-AMP & TONE CONTROL UNIT
- 3 WAY MIXER WITH NEW MATCHING SYSTEM
- AMPLIFIERS
- POWER PACKS

### AMP. & PRE-AMP. KITS

- 8311-V—2 Tr. for Collaro 3 sp. deck with valves, transformers, knobs, etc.
- 8311-4-V as above, for 4 Tr.
- 8312-CP for Collaro 2 Tr.
- 8312-4 CP for Collaro 4 Tr.

11 gns.  
12 gns.  
8 gns.  
9 gns.

### COMPLETE KITS

- Kit 'C' with 8311-V amp., case, 9" x 5" speaker and Collaro Deck.
- Kit 'D' with 8311-4-V amp., case, Collaro Deck and 9" x 5" speaker.

28½ gns.  
34 gns.

MARTIN ELECTRONICS, LTD., 154—155 High Street Brentford, Middlesex.

Full details of Martin Recordakits ☐

Full details of Martin Audiokits ☐

NAME

ADDRESS

(Block letters)

PW14

MARTIN ELECTRONICS LTD., 154/155 HIGH ST., BRENTFORD, M'SEX

Phone: ISLeworth 5885/1161

## COMPONENTS LIST

## Additional Components:

C27	0.5 $\mu$ F paper
C25	2,000pF mica
C29	0.02 $\mu$ F paper
C31	0.5 $\mu$ F paper
C32	6 $\mu$ F electrolytic 12V
C33	500 $\mu$ F electrolytic 12V
R29	27 $\Omega$ 1W 10%
R30	22k $\Omega$ 1W 10%
S4	Equalisation switch, 3-pole 2-way
L2	60mH 2 $\Omega$ filter choke
LS	35 $\Omega$ transistor type
TR11	OC72, GET104 or NKT243

## Change in Value:

C4	470pF ceramic
C5	0.5 $\mu$ F paper
C11	2,000pF mica
C12	0.005 $\mu$ F paper
C13	0.01 $\mu$ F paper
C24	40pF ceramic or mica
C18	100pF ceramic or mica
C17	100 $\mu$ F electrolytic 12V
R8	10 $\Omega$ 1W
R16	3.9k $\Omega$ 1W
R23	39k $\Omega$ 1W
R24	100 $\Omega$ 1W
R25	150 $\Omega$ 1W
T1	2,400 turns of 44 s.w.g. e.w. tapped at 800 turns on LA1

be changed considerably. Here because of the high efficiency of the Garrard heads a great saving of battery current is possible.

The erase oscillator employs only one transistor—an OC72, GET104, or NKT243. The erase head is also the oscillator coil and the consumption is very small; 20mA at 9V is quoted.

Bias is supplied from an overwind on the oscillator coil, this develops 65V which is applied to the recording head via a 100 $\mu$ F capacitor.

## On Replay

Once again as the Collaro modifications with:  
C27=0.5 $\mu$ F C5=0.5 $\mu$ F C28=not used.  
C29=0.02 $\mu$ F C13=0.01 $\mu$ F C30=not used.

When using the Garrard deck a separate 9V battery is recommended for the motor. Because the motor is governor-controlled, some interference may enter the amplifier unless some supply filtering is done.

## Progressive Portable

—continued from page 857

B) and adjust TC4 and the position of the Long Wave coil on the rod, for best sensitivity, at a high wavelength. Then tune to a low wavelength on this band (tuning capacitor fairly well open) and adjust TC3 for best results. In reasonable circumstances, some Long Wave stations other than the Light Programme on 1500m should be received, and these can be used for adjustments.

For maximum possible performance, it is usual to repeat all adjustments on both Medium Wave and Long Wave bands, until no further improvement can be obtained.

Figs. 9, 10 and 11 show the complete receiver, using six transistors, and covering both wavebands. The type of connector illustrated in Fig. 10 is for a 7 $\frac{1}{2}$ V battery, which has a very long working life indeed.

## Tuning Dial

The tuning dial is shown in Fig. 12, and is marked in wavelengths, for Medium and Long Waves. This dial is fitted on the panel under the tuning knob, and held with adhesive. A piece of thin Perspex or other transparent material will protect the dial.

To obtain best agreement with the wavelengths marked, adjust the trimmers at a low wavelength, and the oscillator coil and aerial windings at a high wavelength, on each band, in the previously described manner.

A circuit which has proved satisfactory is included in the redrawn diagram (Fig. 7). The choke may consist of about 300 turns of 28 s.w.g. enamelled, wound in an old small speaker transformer core. The resistance of the choke should not exceed 2 $\Omega$ . A battery switch for the deck motor is mounted on the deck and operated by the wind and play controls.

The recording switch is carried below as in the B.S.R. deck and the wafers for S1 can be fitted. Suitable size wafers are the Plessey type GA1 size 2.

The approximate consumption of the modified amplifier will be as follows:

	Record	Play
(a)	35—330mA	12—300mA
(b)	35—330mA	12—300mA
(c)	30—80mA	8—60mA

Tape deck consumption is 100mA at  $\frac{3}{4}$ in/sec. and up to 200mA for fast wind.

## DOMESTIC STRAIGHT THREE

—continued from page 841

pick up the weaker transmissions, but in almost every case a picture-rail aerial, comprising some 12 to 20ft of insulated wire, will suffice. The use of a good earth connection will also be found beneficial in the poorer reception areas.

Volume obtainable from the local BBC transmissions should be more than adequate for all domestic requirements and the quality of reproduction will be found to be remarkably good, particularly in view of the simple nature of the circuit and few components employed.

## FADING

It is only in especially adverse situations, such as the East Coast of England, where after dark there is trouble from fading of BBC stations and interference from the more powerful Continentals, that results may disappoint; there is no easy remedy for this, as even quite elaborate superhet receivers are frequently incapable of giving a satisfactory performance in these areas. Sometimes the use of a short indoor aerial is beneficial, but this, of course, renders it impossible to receive more distant stations when these are required. But in the vast majority of cases this receiver will prove a fitting reward to the effort of building it, particularly in the case of the novice building his first mains operated set and will, it is hoped, provide the spur to go ahead with more ambitious designs in due course.

# T rade N ews


## General-coverage Receiver Kit

THE model RG-1 general-coverage receiver is available from Heathkit either in kit form or ready-assembled. It tunes over the medium wave band and short wave bands from 1.7Mc/s to 32Mc/s in five ranges.

The sensitivity of the receiver on short waves is  $3\mu\text{V}$  for 10dB signal/noise ratio or better. The eight valve circuit incorporates a variable noise limiter and a half-lattice crystal filter. When built, the set has an i.f. of 1621kc/s and an audio output of 2W.

The kit includes an attractive, robust steel cabinet measuring  $13\frac{1}{2}\text{in.} \times 11\frac{1}{2}\text{in.} \times 6\frac{1}{2}\text{in.}$ , and a tuning meter is a feature of the front panel.

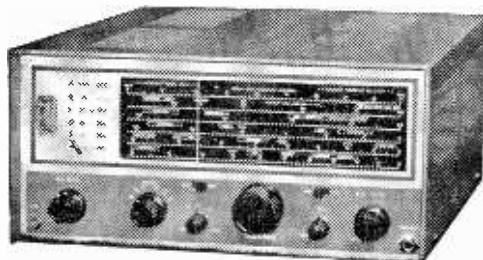The Heathkit RG-1 is made by *Daystrom Limited, Gloucester.*



*Heathkit's new general coverage receiver.*

## Dual-trace Oscilloscope

THE new dual trace oscilloscope, type CD.1183, designed by the Solartron Electronic Group, Ltd., has made use of the principle of modular construction so that the "X" and "Y" self-contained modules may be interchanged speedily and easily when required.

The main unit contains a high resolution c.r.t., a multi-range 1kc/s calibrator, two main vertical deflection amplifiers, one main horizontal deflection amplifier, and all power supplies.

The type CD.1183 oscilloscope is manufactured by the *Solartron Electronic Group, Ltd., Farnborough, Hampshire.*

## New Range of Hi-Fi Equipment

A NEW range of high fidelity tuners and amplifiers has recently been introduced by Armstrong Audio Limited. Included in this range is an integrated stereo amplifier, model 222, which delivers 20W output. It has been designed to accommodate the high quality ceramic pick-ups which are now coming on to the market. The controls include wide range bass, treble and balance controls and the circuit incorporates a rumble filter. The price of this amplifier is £27 10s.

Also in the new Armstrong range are two tuners; the type 224, which is an f.m. tuner costing £22 10s., and the type 223, which is an a.m./f.m. model and costs £28 15s. The manufacturers of this new range of equipment are *Armstrong Audio Limited, Warlters Road, Holloway, London, N.7.*



*The Armstrong type 223 a.m./f.m. tuner.*

## Sound Effects Records

A NEW series of sound effects records has recently been introduced by Recorded Tuition Ltd. On the Contrast label, MFX1 has a general selection of 14 sound effects, including train, car, ship and aircraft sounds, storm effects, etc. MFX2 augments this with a further selection of 12 assorted effects with the emphasis on footsteps, American police cars, but includes other effects such as applause, car crash, etc. Between them, these two records present a good general purpose library of 26 different sound effects.

More specialised is Contrast TFX1, which is devoted entirely to train sounds and the 11 tracks provide a comprehensive selection ranging from a tank loco to a diesel express. Contrast AFX1 is also specialised, this time the subject being wild animals—there are 15 tracks.

Electronic sounds are dealt with on Castle EFX1. Side 1 is taken up with electronic music intended for dramatic introduction and background in plays, documentaries, etc. Side 2 has several tracks devoted to "space ship" effects, the remainder being a selection of miscellaneous electronic sounds suitable for a variety of applications.

All these records are 7in. e.p.'s (45r.p.m.) and all the sounds were recorded by F. C. Judd, A.Inst.E. The quality of reproduction justifies the "hi-fi" claim, the realism is first rate. There are two practical points to note: the length of every individual item is given in seconds on the record sleeves and, secondly, all the tracks are free of copyright to all *amateur* users.

The standard price for any of these records is 8s. 0d., including tax, postage and packing. They may be obtained from *Recorded Tuition Ltd., 174 Maybank Road, Woodford, London, E.17.*

# HOME CONSTRUCTORS LOOK!

## AT THESE OUTSTANDING CHRISTMAS GIFT BARGAINS



**THE SKYROVER**  
7 TRANSISTOR  
PORTABLE  
RECEIVER

**THE SKYROVER**  
De Luxe  
7 TRANSISTOR PORTABLE



### GENERAL SPECIFICATION FOR BOTH MODELS

7 transistor and 2 diode superhet—6 waveband portable receiver, covering the full Medium Waveband (180-576 M) and Short Waveband (31-94 M) and in addition 4 separate switched Band Spread Ranges on 13M, 16M, 19M, and 25M/bands—with manual Band Spread Tuning for accurate Station selection. I.F. frequency 470 Kc/s. Output 500 MW. 5in. Ceramic Magnet P.M. Speaker. Telescopic and internal Ferrite Rod Aerial. All Mullard Transistors and Diodes. The coil pack and tuning heart is completely factory assembled, wired and tested. The remaining assembly can be completed in under three hours from our detailed and easy to follow instructions. Operates on four 1.5V torch batts. (U2 or equivalent).

**THE SKYROVER** Individual Details—controls: Waveband Selector. Volume Control with on/off switch. Tuning Control with easy to read Dial Scale. In attractive plastic cabinet, size: 10 x 6½ x 3¼in. with metal trim and carrying handle.

**MAY BE BUILT FOR £10.19.6**  
All Parts Sold Separately.

Circuit diagram and data for each set 2/6 extra, free if all parts bought. Four U2 batteries 2/8 extra. Four Leak-Proof Batteries 3/4 extra. Add 5/- P. & P. on each set.


**THE SKYROVER De Luxe.** Tone Control Circuit is incorporated with separate Tone Control in addition to Volume and Tuning Controls and Waveband Selector. In sturdy wood cabinet, size: 11½ x 6½ x 3¼in. covered in washable material with plastic trim and carrying handle. Also Car Aerial socket.

**MAY BE BUILT FOR £12.19.6**  
All Parts Sold Separately.
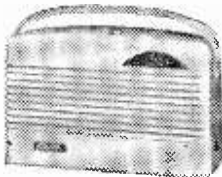
### THE 'REALISTIC 7'

A fully transistorised Portable Receiver made to the highest professional standards—is now available to the home constructor. Comprises 7 Mullard Trans. OC41, 2 OC45's, OC71, OC81D, and 2 OC81's plus OA70 Crystal Diode. Delivers 350 milliwatt output to 4in. high flux speaker—I.F. frequency 470 Kc/s.—fully tunable over medium and long wavebands. All components mounted on single printed circuit board, size 5½ x 5¼in. Attractive two-tone plastic cabinet with carrying handle—size 7 x 10 x 3¼in. with easy to read dial and socket for car aerial, choice of Red/Grey, Blue/Grey or all Grey. Complete with full instructions.

**MAY BE BUILT FOR £5.19.6** All parts sold separately. Battery 3/8 extra. P. & P. 4/6 extra. (Circuit diagram 2/6, free if all parts bought.)




### AND REALISTIC 7 De-Luxe

A "De Luxe" version of the well proven "Realistic 7" is now available, with the same specification as the standard model PLUS a restyled superior wood cabinet covered in attractive washable material, with chrome trim and carrying handle, AND ALSO a full vision circular tuning dial (externally mounted) to further improve this wonderful set.

**Only £1.0.0 extra**

P. & P. etc. as Standard Model.

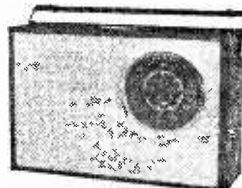

## SPECIAL XMAS OFFERS

### IDEAL GIFTS FOR ALL FROM 8 TO 80 !!

#### 2 TRANSISTOR POCKET RADIO—COMPLETELY BUILT

Ready made as illustrated—complete with personal ear-piece, telescopic aerial, battery and carrying case! Wonderful value and performance—full medium waveband coverage—built in 2½in. speaker gives full tone reproduction. Works on single PP3 9v. battery. In attractive plastic case—size only 4 x 2½ x 1½in. All accessories included in the price.

**WIRECOMP'S 42/-** P. & P. 2/6  
PRICE COMPLETE  
**ALSO 6 TRANSISTOR POCKET RADIO—FULLY BUILT**

Wonderful performance. Tunable over full medium waveband. Built-in 2½in. speaker. In attractive plastic carrying case—size 4 x 2½ x 1½in. Operates on single PP3 9v. battery. Supplied complete with personal earpiece, leather carrying case and battery.

**WIRECOMP'S 79/6** P. & P. 2/6  
PRICE COMPLETE



## WIRECOMP ELECTRONICS

378 HARROW ROAD, LONDON, W9.

TEL: CUNNINGHAM 9530

Hours of business: 9 a.m. to 6 p.m. Open all day Saturday, Opposite Paddington General Hospital. Buses 118 and 36 pass the door.

### THE 'SPRITE'



A unique Wirecomp offer. The Sprite is a Six transistor superhet Miniature Pocket Radio of Commercial Quality—offered to you in three main pre-assembled units—which together with simple wiring—enable you to build it in only one hour! Fully tunable over Long and Medium wavebands. Uses printed circuit and High sensitivity internal ferrite rod aerial. I.F. frequency 470 Kc/s. Transistors: 3 Philips 267's, 2 Mullard OC81M, OC81DM and OA90 diode. 3 inch speaker. Works on complete PP3 battery. Supplied with the complete R.F. and I.F. stages. Driver and Output stages, ready built and mounted on the printed circuit; for final assembly you only have to fit the wave-change switch, tuning condenser and drive, volume control, earphone socket and aerial rod. In very attractive plastic case, size 4 x 2½ x 1½in.

**MAY BE BUILT FOR 79/6** All parts sold separately. Real Calf Leather Case, wrist strap and Personal Earphone with case and battery. 12/6 extra. P. & P. 3/6 extra. (Data and instructions 2/6 free if all parts bought.)


### SPECIAL WIRECOMP OFFERS TO THE READERS OF "PRACTICAL WIRELESS"

**SPEAKERS** 6 x 4in. 3 Ω 8/9. 5in. Round 3 Ω 8/9  
**B.S.R. UA 14 Autochangers** .. .. £5.19.6  
**COLLARO Studio Tape Decks** .. .. £10.12.6  
Post FREE

# THE NEW NORCOL "GNOME"!
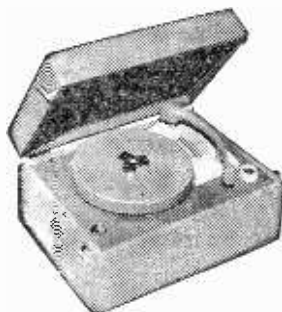
## 2-SPEED PORTABLE RECORD PLAYER KIT

We proudly present this fine new unit as the best value for money available. The volume and quality are superb and the finish of the cabinet so good that we are able to offer an **IMMEDIATE CASH REFUND** if not delighted. Ideal for the new  $33\frac{1}{3}$  rpm 7-inch American records.



Long Life on One 9v battery (3/9 ex.)  
All parts available separately.

### A PERFECT XMAS GIFT

- ★ Beautifully made two-tone blue and grey cabinet with gilt handle and trim. Only  $9\frac{1}{2} \times 7 \times 5$  in.
- ★ Hi-Flux  $8 \times 3$  in. Speaker with Ceramic Magnet.
- ★ 4-Transistor Amplifier on a clearly marked printed circuit.
- ★ Latest "STAAR" KT/4 2-speed turntable unit with automatic speed control.

*This unit is a winner and we confidently predict that when customers see the quality and finish they will agree that it is equal to or better than units costing nearly double the price.*

**COMPLETE KIT** £7.19.6 P.P.  
(with plans) ONLY 3/9

(Amplifier assembled and tested, 5/- extra).

**NORCOL LTD.** 147 LONDON ROAD, YORKTOWN,  
ELECTRONIC COMPONENTS CAMBERLEY, SURREY  
Phone: CAMBERLEY 3743

# YOURS FREE FOR 7 DAYS

## The New 'Picture-Book' way of learning

# BASIC ELECTRICITY (5 vols.) BASIC ELECTRONICS (6 vols.)

You'll find it easy to learn with this outstandingly successful new pictorial method—the essential facts are explained in the simplest language, one at a time; and each is illustrated by an accurate, cartoon-type drawing.

The books are based on the latest research into simplified learning techniques. This has proved that the Pictorial Approach to learning is the quickest and soundest way of gaining mastery over these subjects.

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

**WHAT READERS SAY**

"Learned more in part 1 than the previous 2 years." L.M.J., Durham. "I am convinced that I am on to something really worth while." J.L.P., Fife. "Without doubt they are the easiest to follow books I have ever studied." W.J., Aylesbury. "Congratulations on a well planned easy to learn series." M.K., Horsham. "First class, I cannot praise them too highly." J.J., Taunton.

**To Selray Book Co.**

**60 Hayes Hill, Hayes, Bromley, Kent**

Please send me Without Obligation to Purchase, Basic Electricity/Basic Electronics on 7 Days Free Trial. I will either return set, carriage paid, in good condition within 8 days or send down payment of 10/- (Basic Electricity) followed by 6 fortnightly payments of 10/-. Down payment of 12/- (Basic Electronics) followed by 6 fortnightly payments of 12/-. Alternatively, I will send 63/- (Basic Electricity—5 parts), 75/- (Basic Electronics—6 parts) post free. This offer applies to United Kingdom only.

Tick against set required (only one set allowed on free trial).

**BASIC ELECTRICITY** ☐ **BASIC ELECTRONICS** ☐

Signature \_\_\_\_\_  
(If under 21, signature of parent or guardian)

A TECHNICAL PRESS PUBLICATION


**POST NOW FOR THIS OFFER!!**

**BLOCK LETTERS BELOW**

**Name** \_\_\_\_\_

**FULL POSTAL**

**Address** \_\_\_\_\_

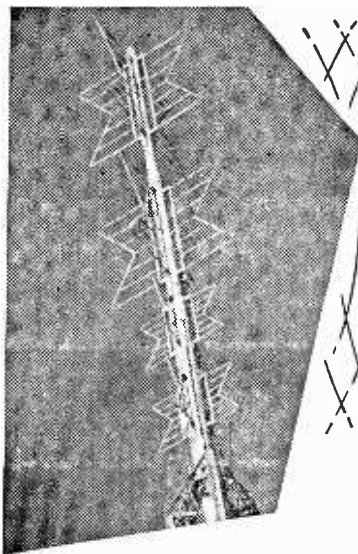

# On Your Wavelength

By THERMION

**J**UDGING by our correspondence it seems that large numbers of beginners are unable (or unwilling) to make the effort and do their own shopping for radio parts, but seek a complete kit even for some of the most basic receiver designs. Is this a lack of enterprise by the beginners of today or is it just another manifestation of the affluent age? At any rate it set me thinking of those far-off days when I embarked upon the construction of my first one-valver.

## Private Enterprise

First, the piecemeal collection of components—a few purchased but most obtained through divers other methods not involving the transfer of currency, such as exchange or the badgering of elders to donate parts. The preparation of the bread-board and front panel, the winding of the coil, the assembly of components and the wiring up. All ready now except for that one vital but expensive article—the valve.

Weeks of careful hoarding of pocket money would culminate in a Saturday morning expedition to the local radio shop and the dissipation of this accumulated wealth in one glorious fling. The brand new HL210 would be carried home in triumph, where trembling fingers would insert it in the long-vacant socket. The receiver was complete! Dare we connect up the accumulator and battery? Eagerness to try out the receiver would be tempered by fear of irrevocably damaging the valve, and so yet once more the wiring would be checked. Finally, the excitement and thrill as the phones became alive and emitted growls and squeals which were eventually coaxed away, leaving the broadcast signal in the clear.

## The Way to Learn

Prepared kits of components are unquestionably a boon in many respects, on the other hand I do feel that the youngsters taking up radio construction as a hobby will obtain far more satisfaction from a piece of apparatus which has been built

up from a host of individually selected parts. The many ensuing visits to radio shops in the process will provide valuable experience and a sense of judgment and discrimination over the disadvantages and advantages of various types and makes of component will, in this manner, soon be developed.

Finally, a word of advice. Even the rawest beginners should appreciate the need to present an orderly shopping list at the counter. This is particularly important when a large number of resistors or capacitors are to be purchased. Tot up the quantity of each value required and tick these off on the published components list as a check before setting out.

## R.S.G.B. Exhibition

Upon visiting the Seymour Hall in London last month my first impressions of the ponderously (and, perhaps, misleadingly) named "International Radio Communication Exhibition" were that I had entered a commercial equipment-cum-Forces' recruiting show. Wandering past the proud and magnificent factory-made receivers and transmitters, I was suitably humbled as thoughts of the chaste appearance of the homespun equipment in my garden shack flashed across my mind. Still, I mentally cheered myself, a highly garnished fascia panel does not help when trying to pull in that much-desired VR or HP.

I did regret the blatant professionalism everywhere and the abundance of shamateur operating stations, but on the credit side both the BATC exhibit, which included a demonstration of the reception of an actual ham TV transmission (from Harrow), and the teleprinter demonstration provided a touch of real amateur enterprise. It was interesting also to gaze upon the by-gones of wireless in a display of components and equipment ranging from the 1920's to the middle 1930's.

But the most heartening sight as far as your scribe was concerned was not even in the main hall. In the far end of a small backstage room, beyond a surplus components shop, I found the Roding Boys' Society stand. Here were examples of radio equipment built entirely by the young members of this organisation, each item a happy reminder that the spirit of amateur radio is very much alive among the lads of today, emphasising once again that enthusiasm and ability to use one's hands are the most important assets for success in this hobby.

On departing, I thought that the R.S.G.B. had done a great injustice in placing this boys' club exhibit in a remote corner apart from the main show, then upon reflection it occurred to me that perhaps this arrangement will (albiet unintentionally) bring home to the visitor the gulf, not merely in space but in mind, that exists between the genuine and the pseudo amateur.

## Home Inter-com Unit Mk II

A RECENTLY published circuit for a home intercom unit contained a fundamental error and this has not escaped the attention of many of our hawk-eyed readers! (See page 442, Sept. issue.)

A number of different re-arrangements have been proposed and we are publishing here (Fig. 1) one revised version which will perform satisfactorily while not requiring too drastic changes to the original design.

It will be seen that the telephone rest switch now has two contacts 'A' and 'B', and when one makes, the other is open.

Since the two poles of this switch must be completely isolated from each other, a different form of construction is needed for the handset rest. A suitable design is given in Fig. 2, where the rest is shown in the unloaded position, i.e. handset removed.

The main portion of the rest consists of a strip of Paxolin or other insulating material. The

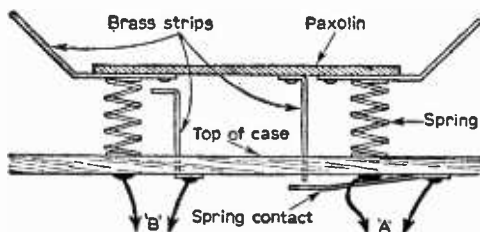


Fig. 2: The construction of the handset rest.

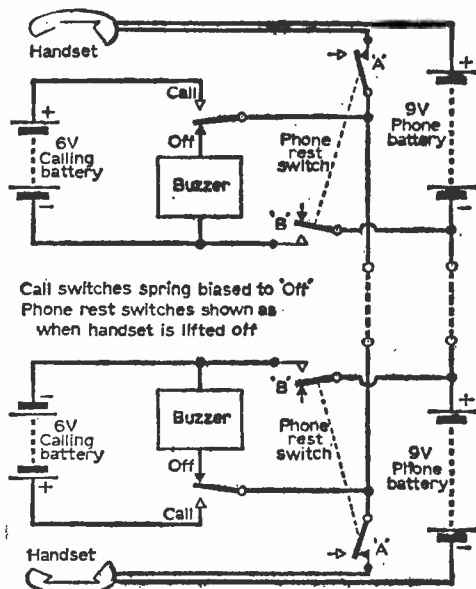


Fig. 1: The revised circuit.

springs are soldered to the brass wing pieces, and the latter are screwed or rivetted to the Paxolin. Brass strip is used for the two switch contact arms; 'B' is made a fixture to the top of the wooden housing, while 'A' is fixed to the insulated part of the rest. Contact arm 'A' operates a spring contact—this should be made from a piece of phosphor bronze.

## Wide Range L.F. Oscillator

—continued from page 815

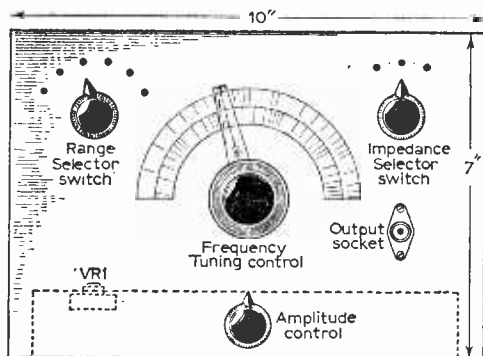


Fig. 3: The front panel of the unit.

### Checking with an Oscilloscope

It will not be possible to check range 6 and the h.f. end of range 5 by the method described,

these frequencies being above the normal audible hearing range. These can be checked on an oscilloscope, if available. An oscilloscope would also be an advantage when setting up the other ranges as any distortion would be at once evident.

If possible the oscillator should be calibrated against a commercially built instrument by the use of Lissajous figures on an oscilloscope, this giving extremely high accuracy. Another simple frequency check is to compare the audio tones heard in the headphones with the notes of a piano scale, this giving an approximate calibration over the audio range.

The calibration points may be marked on a large radio type dial with transparent cursor, or a simple pointer knob used with a 100° or 180° scale, a graph or table being drawn for each range, degrees against frequency.

Finally, the impedance of the low impedance output is of the order of 1000Ω and any external load much below this value may cause distortion. If the unit is to work into a lower impedance load, a series resistance should be used (in series with the output lead), to increase the total impedance to about 1000Ω level. Another method is to use a step-down transformer of the correct ratio.



## NOW! ANOTHER PURCHASE of the year's keenest TAPE RECORDER BARGAIN!



A 24 gns. Tape Recorder offered at the bargain price of only 15 gns. plus 10/- carr. Supplied in 3 Units already wired and tested. A Modern Circuit or quality recording from Mike, Gram or Radio, using latest B.S.R. Twin Track Monardeck Type TD2. Magic Eye recording Indicator, Ext. spkr., switch, super-impose and straight-through amplifier facilities, etc.

Valve line up: EF86, ECL82, EM84, EZ80 and Silicon Diode.

2 tone Cabinet and 8" x 5" Speaker Size 14" x 10" x 7"	<b>£3.10.0</b>	+ 5/- Carr.
Wired Amplifier complete with 4-Valves, front Panel, Knobs	<b>£5.12.6</b>	+ 3/6 Carr.
B.S.R. Monardeck Type T.D.2 Accessories—Mike, Tape, Screened Lead Plugs, etc.	<b>£7.7.0</b>	+ 4/6 Carr.
COMPLETE KIT comprising items above	<b>£1.0.0</b>	+ 2/- Carr.
	<b>15 gns.</b>	+ 10/- Carr.

Leaflet, circuits, instructions, 2/- post free.

## NEW BRITISH RECORDING TAPE

Famous Manufacturer. Bulk purchase, genuine recommended Tape Bargain. Unconditional (Guarantee). Filled Leader & Stop Foils (except 3in.).

Standard (PVC base)	Long Play (P.V.C. base)	Double Play (Mylar base)
3in. 150ft. 3/9	225ft. 4/9	300ft. 6/6
5in. 600ft. 11/6	900ft. 15/-	1200ft. 25/-
5 1/2in. 850ft. 13/6	1200ft. 17/6	1800ft. 32/6
7in. 1200ft. 17/6	1800ft. 22/6	2400ft. 42/6

Post and Packing—3in. Reels, 4d. Each additional Reel, 3d.  
4in. to 7in. Reels 1/- Each additional Reel, 6d.

EMPTY TAPE REELS (Plastic): 3in. 1/3, 4in. 2/- 5in. 2/-, 5 1/2in. 2/-, 7in. 2/3.  
PLASTIC REEL CONTAINERS (Cassettes): 5in. 1/9, 5 1/2in. 2/-, 7in. 2/3.

Condensers—Silver Mica. All values  
2pF to 1,000pF 6d. each. Ditto,  
Ceramics 8d. Tub. 450V T.C.C. etc.  
0.001 mF to 0.01 and 0.1/350V.,  
9d. 0.02-0.1/500V., 1/- 0.25 Hkts  
1/8, 0.5 T.C.C. 1/9, etc. etc. Close  
Tol. 8/Micas—10% 5pF-500pF, 8d.  
600-5,000pF, 1/-, 1% 2pF-100pF,  
9d. 100pF-500pF, 11d. 675pF,  
5,000pF, 1/8. Resistors—Pull  
Range 10 ohms-10 meg. ohms 20%,  
1 and 1W, 3d., 1W, 5d. (Midiget  
type modern ratings) 1W, 6d., 2W,  
9d. Hi-Stab. 5% 1W, 1W, 6d. (100  
ohms-1 meg). Other values 9d.  
1% 1W, 1/6, etc., etc.

### TUB-ELECTROLYTICS-CAN

25/25v. 50/12v. 1/9; 8+8/450v. 4/6  
50/50v. 100/125v. 2/-; 32+32/275v. 4/6  
8/450v. 4/350v. 2/3; 50/50/350v. 6/6  
16+16/450v. 5/6; 60/250/275v. 12/6  
32+32/450v. 6/6; 100+20/275v. 12/6

Volume Controls—5K-2 Meg. ohms,  
3in. Spindles. Morganite Midiget  
Type 1 1/2in. diam. Guar. 1 year.  
LONG or L/N Ratio less Sw. 3/-  
O/P. sw. 4/6. Twin Stereo less Sw.  
6/6. B/W. Sw. 8/-, Specials to order.

### JASON FM TUNER UNITS.

Designer-approved kits of parts.  
FMTL 5 gns. 4 valves. 20/-  
FMT2, 27, 5 valves, 35/- JTV  
MERCURY 10 gns. JTV2 £13.19.6.  
4 valves, 28/8. NEW JASON FM  
HANDBOOK, 2/6. 48 hr. Align-  
ment Services, 7/6. P. & P. 2/6.

TRIMMERS, Ceramic (compression  
Type)—30pF, 50pF, 70pF, 9d; 100pF,  
150pF, 1/3; 250pF, 1/6; 600pF, 1/9.  
PHILIPS. Bee Hive Type (conc. air  
space)—2-8pF, 1/-; 3-30pF, 1/-.  
KNOB5—Modern Continental types.  
Brown or Ivory with Gold Ring;  
1" dia., 9d. each; 1 1/4", 1/- each;  
Brown or Ivory with Gold Centre,  
1" dia., 10d. each; 1 1/4", 1/3 each.  
LARGE SELECTION AVAILABLE.  
METAL RECTIFIERS, STC Types—  
RM1, 4/9; RM2, 5/8; RM3, 7/6;  
RM4, 10/-; RM5, 21/-; RM4B, 17/6.

### BARGAIN CORNER

Brand New, Mfrs. lat. grade.  
1 OC44 & 2 OC45, 15/6, 1 OC81 &  
2 OC81, 15/6. All above and  
OAL, 32/6. Post Free.  
1 Meg. VOL. Controls D/B. Sw.  
1" flatted spindle. Famous Mfrs.  
4 for 10/-, post free.

## RECORD PLAYER

CABINETS 59/6 Carr. & Ins. 5/-

Contemporary style, rexine covered cabinet  
in two-tone maroon and cream. Size 14 1/2"  
x 14 1/2" x 5 1/2", fitted with all accessories including  
baffle board and Vnair fret. Space available  
for all modern amplifiers and auto-changers  
etc. Uncut record player mounting  
board 14 1/2" x 12 1/2" supplied.  
2-VALVE 2 WATT AMPLIFIER.  
EZ80 and Twin stage ECL82 with  
vol. and neg. feedback tone control.  
A.C. 200/250V with knobs, etc., ready  
wired to fit above cabinet. £2.17.6.  
P. & P. 1/6. 7" x 4" speaker and trans.,  
22/-, P. & P. 2/-.  
COMPLETE R/PLAYER KIT. As ill.  
inc. BSR UA14 Unit. New Bargain  
Price Now Only £11.10.0. 7/6 carr.  
Double wound mains Tr. no live chassis!




TYGAN FRET (Contem. pat.), 12 x  
12in. 2/-; 12 x 18in. 3/-; 12 x 24in.  
4/-, etc.

EXPANDED ANODISED METAL.  
Attractive gift finish 1 in. x 1 in.  
diamond mesh 4/8 sq.ft. Multiples of  
6in. cut. Max. size 4ft. x 3ft. 47/6,  
plus carr.

ENAMELLED COPPER WIRE—  
1lb. reels 14g-20g, 2/6; 22g-28g, 3/-;  
30g-34g, 3/9; 36g-38g, 4/3; 39g-40g,  
4/6, etc.



Est.  
1949

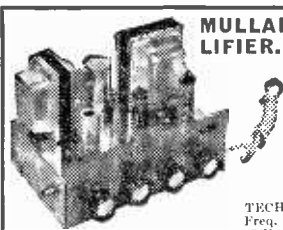

## MULLARD "3-3" HI-FI AMP- LIFIER. 3 VALVES 3 WATT

3 ohm and 15 ohm Output.  
A really first-class Amplifier  
giving Hi-Fi quality at a  
reasonable cost. Mullard's  
latest circuit. Valve line up:  
EF86, EL84, EZ81, Extra HT  
and LT available for Tuner  
Unit addition. This is the  
ideal companion Amplifier for  
FM tuner units.

TECHNICAL SPECIFICATION—  
Freq. Response: + or — 1 dB 40 c/s-  
25 Kc/s. Tone controls: Max. Treble cut  
14 dB at 80 c/s. Sensitivity: 100 Mv  
at least 70 dB below 3 w.

12 dB at 10 Kc/s. Max. Bass Boost 14 dB at 80 c/s. (distortion). Hum and Noise Level: COMPLETE KIT (incl. valves, all components wiring diagram and special quality sectional Output Trans.). Ben. Price £8.19.6. Carr. 4/6. Complete wired and tested, 8 gns. Wired power O/P socket and additional smoothing for Tuner Unit. 10/6 extra.

Bronze Escutcheon, Printed Vol. Treble, Bass, On-Off, supplied with each kit.  
Recommended Speakers—WB. HF 1012, 4.7in. Goodman's AX10M 10, £6.5.0. 8in. AX1ETTE £5.5.0 or AUDIOM 51 £8.10.0.

## DE-LUXE RECORD PLAYER KIT



Incorporating  
4 Sp. Garrard  
Auto-Stop unit and Mullard latest  
3 watt amplifier (ECL 86 and EZ 80),  
vol., bass and treble controls, with  
8" x 5" 10,000 line speaker.  
Amplifier Kit, price inc. speaker £4.19.6  
(carr. 4/6). The front panel unit contain-  
ing amplifier and speaker is detachable  
from the cabinet and can be purchased  
separately for stereo reproduction.  
Contemporary styled 2-tone cabinet,  
charcoal-grey and off-white with  
matching blue relief. Size 17 1/2" x 16"  
x 8".

COMPLETE KIT **£13.19.6**  
Carr. and ins. 10s.  
Cat. & Const. details 2/6 (free with kit).

## TRANSISTOR COMPONENTS

Midiget I.F.s—465 Kc/s 9/16in.  
diam. 5/3  
Osc. Coil M. & L.W. 5/3  
Midiget Driver Trans. 3.5/1 6/9  
Midiget Output Trans. Push-  
Pull—3 ohms 6/9  
Elect. Condensers—Midiget Type  
1 mfd.-50 mfd. ca. 1/9, 100 mfd.  
2/-, 15V.  
Condensers 150 v. working:  
.01 mfd., .02 mfd., .03 mfd.,  
.04 mfd. 9d.; .05 mfd., 1 d mfd., 1/-,  
.25 mfd., 1/3; 3 mfd., 1/8, etc.  
Midiget Tuning Condensers, J.B.  
"DOO" 208 pF and 176 pF, 8/8,  
ditto with trimmers, 9/8. J.B.  
220pF and 105pF conc. slow  
motion 10/6. 355pF single 7/8.  
Sub. Min. 1in. Dia. 100 pF,  
300pF, 500pF, 7/- each.  
FERRITE AERIALS. M. & L.W.  
car aerial coil 9/8.  
Midiget Vol. Control with edge  
control knob, 5 K/ohms, with  
switch 4/9; Ditto less switch 3/9.  
Speakers: P.M.: 2in. Plessey 75  
ohms 15/6, 2 1/2in. Continental 8  
ohms 13/6, 7 x 4in. Plessey 35  
ohms 23/6.  
Ear Plug Phones—Min. Con-  
tinental type 3ft. lead, jack plug  
and socket. High Imp. 8/-, Low  
Imp. 7/6.  
Tinned Copper Wire, 16-22g.,  
2/6 1lb.

## 7 VALVE AM/FM RADIOGRAM CHASSIS

Valve line-up: EOC85, ECH81, EF89,  
EABCO8, EL84, EM81, EZ80.

Three Waveband and Switched Gram  
positioning. Med. 200-550 m. Long  
1,000-2,000 m. VHF/FM 88-95 Mc/s.  
Phillips Continental Tuning insert with  
permeability tuning on FM and com-  
bined AM/FM IF transformers. 460  
Kc/s. and 10.7 Mc/s. Dust core tuning  
all coils. Latest circuitry including  
AVC and Neg. Feedback. Three watt  
output. Sensitivity and reproduction  
of a very high standard. Chassis size  
13 1/2 x 6 1/2in. Height 7 1/2in. Edge illu-  
minated glass dial 11 1/2 x 5 1/2in.

Vertical pointer. Horizontal station names. Gold on brown background.  
A.C. 200/250v. operation. Magic-eye tuning. Cct. diagram now available.

Aligned and tested ready for use **£13.10.0** Carr. & Ins. 7/6

Complete with 4 Knobs—walnut or ivory to choice. Indoor FM aerial 3/6 extra.  
3 ohm P.M. Speaker only required. Recommended Quality Speakers 10in.  
Riac H/D, 30/-; 13 1/2 x 8in. E.M.I. "Fidelity", 25/-; 12in. R.A. with conc.  
Tweeter, 42/6. Carr. 2/6.

Send for detailed bargain lists. 3d. stamp.

We manufacture all types Radio Mains Transf., Chokes, Quality O/P Trans., etc.  
Enquiries invited for Specials, Prototypes for small production runs. Quotation  
by return.

## RADIO COMPONENT SPECIALISTS

70 Brigstock Rd., Thornton Heath, Surrey.

Hours: 9 a.m.-6 p.m., 1 p.m. Wed.

THO 2188. Terms C.W.O. or C.O.D. Post and Packing up to 1 lb. 2d.; 1lb. 1/3; 3lb.  
2/3; 5lb. 2/9; 8lb. 3/6.


# CRYSTALS & COMPONENTS LTD

TEL: TEM 1189 2-4 EARLAM STREET, LONDON W.C.2.

Near Cambridge Circus. A few minutes' walk from Leicester Square or Tottenham Court Road Underground Stations  
**HOURS OF BUSINESS:** 9 to 6. Saturdays 9 to 1. **OPEN ALL DAY THURSDAY**
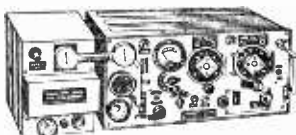
## WIRELESS SET NO. 19

Complete with original power supply unit for 12 volts input. Transmitter/Receiver covering 2-8 Mc/s and V.H.F. and 240 Mc/s. 6 valve superhet receiver and 6 valves in Transmitter. Using I.F. of 465 Kc/s. For voice and C.W. In good condition not tested. £4.17.8. Plus £1 packing and carriage. Microphone and headset for this set 17/6 plus 2/6 post and packing. 19 Set Variometers, 17/6 plus 2/6 post and packing. Booklet with circuits and instructions free with set or separately 2/9 post paid.



Control box for 19 set, 10/- plus 2/- post and packing.

## VIBRATORS

6V. 4 pin .. .. 3/8 plus 1/6 P. & P.  
 6V. 7 pin .. .. 3/8 plus 1/6 P. & P.  
 12V. 7 pin .. .. 4/6 plus 1/6 P. & P.

## TYPE 38 TRANS/RECEIVERS

Brand new. Operating on 7.4 to 9 Mc/s. Trans/Receivers. Complete with headphones, throat microphone, junction box and aerial rods. Operate on 150 volts HT & 3 volts LT dry batteries. Complete less batteries and not tested. 42/6 per set plus 6/6 post. Or £4 per pair plus 10/- post and packing.



## U.H.F. AERIAL

On 10 feet collapsible mast. Spring loaded in 1 foot tubular sections. Complete with 12 feet co-ax lead and rubber covered plug. 3 steel pins and nylon guys. Can be easily lashed to existing TV aerials for modification to new frequency. 12/6 plus 2/6 P. & P.



**TERMS OF BUSINESS**  
**CASH WITH ORDER**

## BARGAIN PACKS

Resistors assorted packets of 100 brand new including miniature and high stab. 12/6 POST PAID. All useful values. Condensers, 100 assorted, including mica, ceramic, metal tubular, etc., 15/- post free. 12 Assorted Pots. All new and useful sizes 12/6, post paid. Components Package containing 3 useful size pots, 3 wafer switches, 50 assorted resistors and condensers including electrolytic and ceramics. ALL NEW 15/- plus 2/- P. & P.

## SILICON RECTIFIERS

Westinghouse 1,000 P.I.V. 500mA. 9/- each. P. & P. 1/6. 800 P.I.V. 500 mA. 7/6 each. P. & P. 1/6.

**NOW AVAILABLE!**  
**OUR NEW**  
**CRYSTALS LIST**  
 SEND S.A.E.

# YOUR CAREER in RADIO?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the **CITY & GUILDS EXAMS**, (Technicians' Certificates); the Grad. Brit. I.R.E. Exam.; the **RADIO AMATEUR'S LICENCE**; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servomechanisms; Mathematics and Practical Transistor Radio course with equipment. We have **OVER 20 YEARS'** experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronic subjects only. Full details will be gladly sent without any obligation.


To: **BRITISH NATIONAL RADIO SCHOOL, Dept. 3**  
**RADIO HOUSE, READING, Berks.**

Please send **FREE BROCHURE** to:

NAME..... Block  
 ADDRESS .....Caps.  
 ..... Please  
 1.64

## BRITISH NATIONAL RADIO SCHOOL
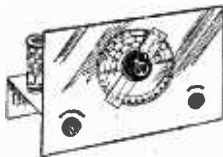
## LISTEN TO THE WORLD on TELSTAR our I-VALVE SHORT WAVE RADIO



Receives speech and music from all over the world. Price includes valve and one coil covering 40-100 metres. Can be extended to cover 10-100 metres. Can be converted to 2 or 3 valve and all-mains speaker use. Total Building Costs **35/-** P. & P. 2/-.

## R.C.S. TRANSISTORISED TAPE TUNER

Wonderful reproduction of all your favourite programmes. Covers full medium wave band. Special circuit incorporating ferrite rod aerial and tuning condenser gives **COMPLETE STATION SEPARATION**. Attractive case size 3 1/2 x 2 1/2 x 1 1/2 in. deep. **NO EXTERNAL AERIAL OR EARTH REQUIRED**. Chassis and components colour coded for easy construction. All parts supplied with step by step instructions.



**ONLY 25/-** P. & P. 2/-.  
 (VT3 battery 2/6 extra.)

## THE R.C.S. PERSONAL SET For Private Listening

An amazing little set, with built-in ferrite rod aerial bringing in medium wave at wonderful volume. Sturdy case. Size only 2 1/2 x 3 1/2 x 1 1/2 in. Fits into the palm of the hand. Drilled chassis colour coded for easy assembly. Total Building Costs (including earpiece) **30/-** P. & P. 2/-.



## R.C.S. CRYSTAL RECEIVER

Covering medium wave band. Ideal for the beginner! All components in- **8/6** P. & P. cluding case. 1/6.  
 (Suitable headphones 9/8.) Easily converted to 1-transistor or 2-stage transistor receiver



All parts available separately. Send S.A.E. for free layout plans and parts lists of any of the above sets.

## R.C.S. PRODUCTS (RADIO) LTD.

11 Oliver Rd., London, E.17. (Mail Order only)  
 Export Trade enquiries invited

# BOOKS REVIEWED

## MODERN TAPE RECORDING AND HI-FI

By Ken Peters; published by Faber and Faber, 24 Russell Square, London, W.C.1.  
248 pages, 6½ in. x 5½ in. Price 30s.

**M**ORE than 2,000 tape recorders are sold each week. Yet, the author points out, they are prone to a strange hibernating instinct that afflicts them three or four months after their purchase, driving them into cupboards, under beds and into attics where they lie inactive.

It is this phenomena that the author seeks to remedy, by the simple process of exploring, and explaining, some of the myriad uses to which a tape recorder may be put. And although dyed-in-the-wool radio enthusiasts are less likely to neglect their tape recorders than non-technical members of the public who often buy a machine on impulse for its novelty value which soon evaporates, they too will find a great deal of interest in this book.

It is essentially a practical book, its aim being to investigate a possibility, explain the principles, give an example. Apart from advice and information provided, it also leaves room for individual experiment by virtue of the ideas it propounds. The treatment is non-mathematical and essentially non-technical. But although it is aimed at the non-technical reader, this need not deter those with technical knowledge, for it incorporates subjects on which information is not too readily available.

There are two introductory chapters which are designed to assist prospective owners to choose a tape recorder and there is a lot of good practical advice here. This is followed by chapters on conventional usage of tape recorders, with some interesting ideas on things such as sound effects and continuous loops (marred only by a curiously incorrect drawing on page 56).

From here the author delves into such subjects as interviewing techniques, "audible colour" (tape-slide, tape and cine combinations), and "music on tape" utilising the potentialities of the tape recorder as a musical instrument itself.

This takes up to little under half the book. Chapters follow on indexing systems for sound libraries, "tapesponding" and tape clubs, home plays, party ideas. There is a chapter on hi-fi, again containing some good advice for the less well informed, followed by some notes on stereo.

The book rounds off with some general observations on audio maintenance, with a trouble-shooting chart, and a section listing the various accessories which the keen enthusiast might require. In this, as in other chapters dealing with products, prices are given as a guide.

All in all, despite the rather high price, the book should prove most informative to those with limited technical knowledge about to buy a tape recorder and to those who already have one lying inactive in some dark hideaway in the house. It certainly shows that the tape recorder has many facets for the enthusiast, some of them largely unexplored.—*W.N.S.*

## FREQUENCY DIVIDER ORGANS FOR THE CONSTRUCTOR

By Alan Douglas, I.E.E.E.; published by Sir Isaac Pitman & Sons Ltd.  
72 pages, 67 diagrams, 5½ in. x 8½ in. Price 25s.

**T**HIS book concentrates on the practical aspects of electronic organ building and the theory of the circuitry involved is not explained, although a general descriptive treatment is given.

There are two main chapters and these describe (1) a resistance-capacitance valve frequency-divider organ and (2) a gas-tube frequency-divider organ.

Both of these chapters contain full design details for the essential electronic components such as oscillator coils as well as chassis layout diagrams and circuit diagrams of all the units, e.g. tone-forming circuits, keying arrangements and oscillator and divider chains, etc. The construction of the electro-mechanical devices such as stop keys and pedal controls is also well covered in diagram and text.

Another chapter gives details of an instrument described as a simple melodic transistorised keyboard. This instrument operates from dry batteries and will provide sufficient audio output for an average-sized room.

The final chapter contains information concerning frequency-divider circuits at present used in commercial electronic organs and so may well give the amateur constructor further ideas to develop for his own purpose.—*D.D.R.*

## RADIO AND TELEVISION REFERENCE DATA

Compiled by J. P. Hawker; published by George & Lewis Ltd., Tower House, Southampton Street, London, W.C.2.  
96 pages, 9 in. x 6 in. Price 10s. 6d.

**T**HIS is a handy reference book containing, as the title implies, data of interest to radio and TV service engineers, amateur constructors and enthusiasts. Contents include a section on formulae in frequent use, details of colour codes, formulae and dimensions relating to aerials (including a frequency-wavelength conversion table) and a section on symbols and abbreviations.

Also featured is a list of broadcasting allocations and station frequencies, including a list of the major European broadcasting stations, together with details of television broadcasting standards. A short section on amateur radio gives a summary of facilities available, amateur radio abbreviations and prefixes, and a list of i.f.'s used in a wide range of commercial communications receivers.

Other information deals with mathematical data, including log tables, wire and cable data and battery equivalents. There is also a listing of valve, transistor and cathode ray tube pin connections, ratings, bases and equivalents, including selected CV types.—*D.C.*



#### BURSELM AMATEUR RADIO CLUB

Hon. Sec.: W. Luscott, 36 Rothsay Avenue, Sneyd Green, Stoke-on-Trent, Staffordshire.

Any local radio enthusiasts who are interested in joining the Club are invited to contact the Secretary. A full programme of film shows, lectures, etc., has been arranged for Club meetings, which are held on the third Wednesday of each month.

#### CLIFTON AMATEUR RADIO SOCIETY

Hon. Sec.: G30GE, 63 Broomfield Road, Beckenham, Kent. On 16th November, members of this Society made a visit to the headquarters of the Crystal Palace Amateur Radio Club for a "hi-fi" demonstration. Later in the month, on the 22nd, members took part in a quiz organised by the Secretary.

#### DERBY AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: F. C. Ward, G2CVV, 5 Uplands Avenue, Littleover, Derby. A social evening—which included a supper—was organised by T. Darn on 13th November. 20th November was declared an open evening and Juniors' Night.

A week later a demonstration on providing the finishing touch to home-built equipment was given by A. Hitchcock. December began, as usual, with a surplus sale on the 4th.

#### MELTON MOWBRAY AMATEUR RADIO SOCIETY

Hon. Sec.: D. W. Lilley, G3FDF, 23 Melton Road, Asfordby Hill, Melton Mowbray, Leicestershire.

On 21st November the Secretary was "at home" to members when the Society made a visit to his shack.

#### NORTHERN HEIGHTS AMATEUR RADIO SOCIETY

Hon. Sec.: A. Robinson, G3MDW, Candy Cabin, Ogden, Halifax. This Society reports increasing membership and attendance figures, with a growing proportion of licensed amateurs among its members.

"Antenna Problems" was the title of the lecture given by A. Bailey (G3IBN) on 4th December.

#### PETERBOROUGH AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: D. Byrne, G3KPO, Jersey House, Eye, Peterborough. At the recent meeting which officially opened the Society's winter session, Frank Crabtree (G3BK) demonstrated the KW77 communications receiver.

#### PLYMOUTH RADIO CLUB

Hon. Sec.: B. J. Curnow, 112 Mount Gold Road, Plymouth, Devon. On 9th November, members of this Club faced members of Torbay A.R.S. in a friendly battle of wits, organised by the two societies.

#### READING AMATEUR RADIO CLUB

Hon. Sec.: R. G. Nash, G3EJA, "Peacehaven", 9 Holybrook Road, Reading, Berkshire. For members who attended the meeting of 30th November, G3HGE gave a demonstration of some equipment about which members were invited to discuss any points that arose.

#### RODING BOYS' SOCIETY: RADIO SECTION

R. Marchant, 154 Essex Road, London, E.10. Recently much of the Society's activity has been directed towards a Club stand at a local exhibition.

#### SCARBOROUGH AMATEUR RADIO SOCIETY

Hon. Sec.: P. B. Briscoe, G8KU, "Roseacre", Irton, Scarborough, Yorkshire. November began with a surplus sale on the 7th. At the second meeting of the month, however, members enjoyed a film show.

The first meeting of December—which was on the 5th—was also a sale of surplus gear.

#### SPEN VALLEY AMATEUR RADIO SOCIETY

Hon. Sec.: N. Pride, 100 Raikes Lane, Birstall, Leeds. "The Electronic Marshalling Yard" was the title of the lecture given by Mr. S. Jones at the meeting on 14th November. On 12th November, the Society travelled to Bradford to see a film show at St. George's Hall.

On 28th November, J. Spivey (G2HHV) talked about "Office Electronics" and on 5th December, a party of members visited the Basinghall Street telephone exchange in Leeds.

#### STRATFORD-ON-AVON AND DISTRICT AMATEUR RADIO CLUB

Hon. Sec.: N. Smith, 54 Clopton Road, Stratford-on-Avon, Warwickshire.

The meeting for 8th November was an open evening, but a week later, on the 15th, G30MP gave a lecture on "Transistors". This was followed on the 22nd by a film show and the month ended with another open evening on the 29th.

#### THAMES VALLEY AMATEUR RADIO TRANSMITTERS SOCIETY

Hon. Sec.: K. Rogers, G3LIU, 21 Links Road, Epsom, Surrey.

November began with a constructional contest at the meeting on the 6th. One of the Society's foremost events of the year was held on 9th November, when members attended the 30th Annual Dinner.

On 4th December, A. Taylor gave a lecture entitled "Nuclear Power".

#### WESSEX AMATEUR RADIO GROUP

Hon. Sec.: G. J. Fowle, 138 Surrey Road, Branksome, Poole, Dorset.

On 14th November a group of members visited the headquarters of the Bournemouth Police, when the radio equipment installed in the police cars came in for some close scrutiny. The home of the President of the Group became the meeting place for members on 25th November.

A film show, which included a record of the Group's activities for the year, was given on 2nd December.

#### WEST KENT AMATEUR RADIO SOCIETY

R. Trevitt, 28 Dales Avenue, Tunbridge Wells, Kent.

At the meeting on 8th November, Ben Pooley gave an interesting talk on his experiences of VE-, VR2- and VK-lands. The only other meeting for November was on the 22nd when L. King gave a talk and demonstration called "SSB and the Linear Amplifier".

#### WIRRAL AMATEUR RADIO SOCIETY

Hon. Sec.: A. Seed, G3F00, 31 Withert Avenue, Bebington, Wirral, Cheshire.

"On First Working Single Side Band" was the title of the lecture given by Mr. J. Wyld on 6th November. The Society's Annual Dinner was held on 9th November, and on the 20th the Secretary gave a lecture on "Electronics in Industry".

The first meeting in December was devoted to a surplus sale.

#### ★ ★ ★ ★ ★ LAST-MINUTE CHRISTMAS GIFTS ★ ★ ★

★ No need to rush out to the shops. Here's ★  
★ one you can arrange now... in a few ★  
★ moments... in the comfort of your own ★  
★ armchair. A year's subscription for ★  
★ PRACTICAL WIRELESS is the ideal gift for ★  
★ friends who are radio enthusiasts.

★ But hurry! You must send now to make ★  
★ sure that first copies arrive in time for ★  
★ Christmas. Simply send your friends' ★  
★ names and addresses, together with your ★  
★ own and remittance \* to cover each ★  
★ subscription to The Subscription Manager ★  
★ (G.3), PRACTICAL WIRELESS, Tower ★  
★ House, Southampton Street, London, ★  
★ W.C.2. An attractive Christmas Greetings ★  
★ Card will be sent in your name to announce ★  
★ each gift.

★ \* RATES (INCLUDING POSTAGE) FOR ★  
★ ONE YEAR (12 ISSUES):—U.K. AND ★  
★ OVERSEAS £1.9.0, U.S.A. \$4.25.

★ To make sure of your own copy why not ★  
★ place a regular order with your newsagent.

★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★

# A MINIATURE TAPE RECORDER IN KIT FORM ONLY

**£3.19.6**



Exclusively offered complete with all accessories. No extras to buy. Consisting of three transistor amplifier, record-play, volume control, miniature speaker, forward-stop-rewind switch, reel of tape and spare reel, motor, attractive coloured case, Mic. and earphone sockets, pick-up coil, mike, earphone and carrying handle supplied. Standard battery operated. Simple to put together in less than an hour. Brand new and guaranteed.

**ALSO AVAILABLE  
READY-BUILT AT**

**£4.19.6**

## PICK-UP ARM COMPLETE



**NOW  
ONLY  
49/6**

Transcription type. Wired for stereo and complete with I.P. 78 Stereo Mono turn-over cartridge. (Originally 69/-). Save 19/6 at this low price.)

## 12in. THREE-WAY SPEAKER Model CR.30AE.



Designed and engineered to satisfy the most discriminating listener. The CR.30AE achieves full 3 speaker performance through its advanced triaxial design. The woofer, midrange radiator and tweeter are all axially mounted within a single speaker system. Rigid low silhouette die cast frame ensures perfect alignment and minimum space.

Brief Specification: Freq. Response: 30-16,000 c.p.s. Capacity: 10 watt, Peak 20 watt. Impedance: 16 ohm. Crossover Frequency: 18,000 c.p.s., 5,000 c.p.s. PRICE 10 gns.

## SE. 1. STEREO HEADPHONES



For use across the speaker output terminals of any amplifier and supplied complete with control box enabling permanent connection and immediate switching from headphone to loudspeaker reproduction. The SE.1. Stereo Headphones give you an exciting new experience in Stereo listening. Supplied complete with leads, control box and instructions. PRICE 6j gns. S.A.E. for leaflets.

## SUBSTITUTION BOXES

Fully calibrated complete with insulated leads. Model O.M.G. RESISTANCE BOX. Provides 24 standard values at 1 watt, 15 ohms to 10 meg. Price 37/6. Model O.M.B. CAPACITANCE BOX. Provides 9 standard values from 0.001 to 0.22 mfd. at 600 volt working. Price 29/6.

# SPECIAL XMAS OFFER! PORTABLE HIGH-FIDELITY RADIOGRAM Model RP200

Now you can have the best of both worlds: a super sensitive and highly selective radio combined with a high fidelity record player housed in a luxury two-tone washable case. Plays any records up to 12in. at 16, 33 $\frac{1}{3}$ , 45 or 78 r.p.m. Has turntable adaptor for 45 r.p.m. records as well as rubber turntable mat to protect your records. Lightweight pick-up arm has turnover cartridge with individual sapphire stylus for LP's or 78's. Expertly designed amplifier and high-fidelity speaker provide faithful sound reproduction from radio or records. On/off Volume Control: 200/250 v.; Size 8 $\frac{1}{2}$  x 15 x 4 $\frac{1}{2}$ in. Choice of two-tone grey or two-tone beige. S.A.E. for leaflet.



Originally  
£18.6.0

**NOW ONLY £14**

## REDA EXCLUSIVE!!! 100,000 O.P.V. MULTI-TESTER

MODEL EP.100K. A handy, high sensitivity multi-tester with a shock-proof meter of 9.5A. Incorporates three germanium diodes and simplified meter scale for easy reading. RANGE D.C. VOLTS: 2.5V, 10V, 30V, 250V, 1,000V (30,000 ohm V), 500V, 1,000V (30,000 ohm V) A.C. VOLTS: 2.5V, 10V, 30V, 250V, 1,000V (12,500 ohm V). D.C. Amps: 100A, 250A, 2.5mA, 25mA, 250mA. Ohms: 0-20K ohm, 0-200K ohm, 0-2M ohm, 0-20M ohm. Centre-100 ohm, 10K ohm, 16K ohm, 100K ohm. L.L.: 10A, 100A, 1.5mA, 18mA. L.V. 5V.

Decibels: minus 20db—plus 62db. Size: 5 $\frac{1}{2}$ in. x 3 $\frac{1}{2}$ in. x 2 $\frac{1}{2}$ in.


ORIGINALLY £14.10.0.

OUR PRICE **£6.19.6** COMPLETE

## NEW H402 ULTRA-SUB-MINIATURE TRANSISTOR COIL SET

Smallest 2 gang variable condenser  $\frac{1}{16}$ in. square x  $\frac{1}{16}$ in. deep. 3 L.F.'s and Oec. Coil  $\frac{1}{16}$ in. square x  $\frac{1}{16}$ in. deep. Ferrite rod with medium wave coil ready wound. All supplied with suggested 6 transistor set circuit and parts list. Matched coils shielded and impregnated high Q 455 Kc/s. all slug tuned. Tuning dial and knob fits securely on shaft. ONLY 24/6 complete.

## R.F. FIELD INDICATOR

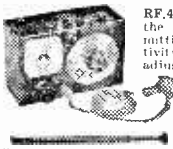

RF.40. Designed for checking the radiation from a transmitting antenna. The sensitivity can be controlled by adjustment of panel control the antenna length or by increasing distance from the radiator. Freq. range 1-250 Mc/s. 200A D.C. Meter. Complete as illustration with instructions. Price 89/6.




**NOW  
ONLY  
24/6**

Designed for use with transistor radios, valve radios, car radios, amplifiers, where quality reproduction of sound is required. Plug-in output socket of nearly all miniature sets. The cabinet is finished in beige leather with contemporary gold baffles at each end. Complete with 12ft. extension cord fitted with miniature plugs, individually cartoned and guaranteed. size: 9 $\frac{1}{2}$ in. x 3 $\frac{1}{2}$ in. diameter.
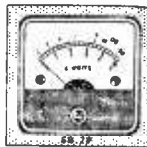
## "KEW" PANEL METERS

"8" Meter, 35/- D.C. Microammeters, 5 n/a, 27/6; 300 v. 27/6; 0-50A, 39/6; 0-500A, 32/6; D.C. Milliammeter, 0-1mA, 27/6. Available in Clear Plastic or Black Bakelite. Will cut 1in. dia. cut out. State choice when ordering. All models individually boxed and fully guaranteed.




## NEW! 1 mA PANEL METER— CLEAR PLASTIC WITH PANEL LIGHT 35/-

## EDGEWISE PANEL METERS

Size 3 $\frac{1}{2}$ in. w. x 1in. h. x 3 $\frac{1}{2}$ in. d. 0-200 A, 69/6; 0-1 A, 59/6. All boxed and fully guaranteed.



## No. 19. 2-8 Mc/s TRANSMITTER RECEIVER

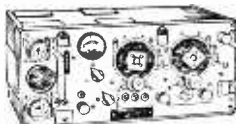

This most famous Army Trans. Receiver covers 2-8 Mc/s (150-37 metres in two bands). Has an intercom, amplifier, designed for 12 and 24 volt operation but supplied with "P.W." Mains conversion details. Uses a 6 valve superhet receiver, I.F. being 465 Kc/s, and a 6 valve transmitter designed for voice and C.W. operations, aerial loading and current sets. Panel Controls: Frequency tuning, P.A. tuning, gain control, MCW C.W. R/T switch. Het-tone netting. Off-on Quench aerial, AVC LT-HT—Drives tests.

plifier. Designed for 12 and 24 volt operation but supplied with "P.W." Mains conversion details. Uses a 6 valve superhet receiver, I.F. being 465 Kc/s, and a 6 valve transmitter designed for voice and C.W. operations, aerial loading and current sets. Panel Controls: Frequency tuning, P.A. tuning, gain control, MCW C.W. R/T switch. Het-tone netting. Off-on Quench aerial, AVC LT-HT—Drives tests.

**NOW ONLY 55/-**

Carr. paid.

12ft. WHIP AERIAL (U.S.A.), 10/-.

## AUTOMATIC SOLDERING IRON SF.1.



30 watt. First in the country that feels solder automatically. Easy one hand action, lightweight and extremely robust, gives you a third hand. Tip and solder are placed at the exact spot needed, any required amount of solder can be automatically fed to the tip by adjustable feed roller. Standard A.C. mains. Fully guaranteed.

**ONLY 52/6**

MAIL ORDERS TO  
(DEPT. P), 32a COPTIC STREET,  
LONDON W.C.1.

**Relda Radio**

CALLERS WELCOME AT  
87 TOTTENHAM COURT ROAD,  
LONDON W.1. MUS 9606

THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD



# LETTERS TO THE EDITOR

## AS YOU WERE

SIR,—I agree entirely with the opinion expressed by Mr. P. A. Roe in the November issue, that considerable confusion exists as to the correct meaning of the words 'vibrato' and 'tremolo', but I feel that Mr. Roe has done little to clear the air. In fact, by setting himself up as an authority, he will have, no doubt, made matters worse.

If Mr. Roe consults the available literature on orchestral and electronic musical instruments, he will find that the universally accepted definition of the terms vibrato and tremolo are exactly opposite to those given in his letter.—A. G. BRIDGE (Dagenham, Essex).

SIR,—I would refer to the comments of Mr. P. A. Roe in the November P.W. relating to tremolo and vibrato. While I agree that these terms are sometimes incorrectly used, Mr. Roe now wishes to place on record a statement which I cannot accept.

After reading books and articles on the subject for over twenty years, it would now appear that writers like R. H. Dorf, Robert Eby, Emeron Anderson, to mention but a few, have been using the incorrect terms all along the line. Without going into too much detail, I quote from a glossary of these terms which will be confirmed by any book of reference: Tremolo—the variation in volume of a tone; Vibrato—the periodic variation in frequency of a tone.

If you accept these definitions, this completely contradicts Mr. Roe's statements.—S. J. LEWIS (Narberth, Pembrokeshire)

## DECLINING MORSE STANDARDS

SIR,—As a S.W.L. of the tender age of fifty-six,

I find myself in absolute agreement with those of your correspondents who observe that amateur operators should be well technically qualified. When I listen to some of the amateur transmissions, I sometimes wonder if the G.P.O. should not stiffen the examination.

I am however, in disagreement with the present morse code qualification. This is said to be necessary, firstly by the G.P.O., because any amateur must be able to receive any traffic directed to him, and secondly by already licensed amateurs, mainly on the basis that because they had to undergo the test, so should everyone else.

Yet after a certain amount of listening to stations from all over the U.K., no one can help but be astonished by the number of amateurs who openly admit that their morse is not up to the required standard, either because they have never indulged in it since taking the test, or because they have been off the air for as long as eight, ten and thirteen years.

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying commercial or surplus equipment. We cannot supply alternative details for receivers described in these pages. **WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE.** If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of the cover.

The Editor does not necessarily agree with the opinions expressed by his correspondents

How can such people as these be in a position to satisfy the G.P.O.'s requirements? It is my contention that the G.P.O. should re-test each licence holder at least every two years, or end what appears to be a farcical situation.—J. W. KENNETH (Manchester, 21).

## BLUEPRINT APPRECIATION

SIR,—After buying the November issue of P.W. which contained the blueprint for the Beginner's Short Wave Two, I decided to build this set. This has now turned out to be a remarkable little receiver, far superior to the commercially produced kit that I had previously built. I have achieved good reception on several bands with only the simplest aerials.

I did not have a 954 valve as specified and so I used an EF80 which was to hand. Thank you for an exceptionally easy but effective circuit to build and use.—TONY SKAIFE (York).

Sir—I would be grateful if any reader could sell or loan me . . .

. . . information and equivalents for the following valves: VT62, VT26A, AT20, AT570, CV125, PT15 and 8013.—P. LAYTON, 26 Grattan Hill, Cork, Ireland.

. . . the circuit or any details of the H.M.V. model 1423 transistor receiver.—R. PETTAS, 66 Beethoven Street, Paddington, London, W.10.

. . . the circuit and/or manual of the Eddystone 358 type B receiver.—H. MULLIGAN, 103 Beresford Road, Longsight, Manchester.

. . . the August 1961 issue of P.W.—M. C. Green, 6 The College, Malvern, Worcestershire.

. . . any information concerning the R1155 receiver.—I. P. GREEN, 171 Easterly Road, Leeds 8.

. . . the circuit or any information on the American receiver R-3/ARR -2X.—L. E. NICHOLLS, 5 Centre Drive, Newmarket, Suffolk.

. . . circuit information on the set 22 and set 62 MkII and the W2113A transmitter.—V. G. W. EGGLETON, 30 Mincinglake Road, Stoke Hill, Exeter, Devon.

. . . the circuit for a transistorised process timer with a range of 0 to 120 seconds.—W. DEIGHAM, 2 Browning Road, Manor Park, London, E.12.

. . . information on the plug-in crystals originally fitted to a Collins receiver, type COL 46159. Also I would like any circuit information and details of power supply requirements.—N. T. FRANCIS, 71 Oxford Grove, Bolton, Lancashire.

## NOTES TO MEDIUM-WAVE DX FANS

Now that the medium wave DX season is with us again, "Medium Wave News" is again being issued. This is an extremely informative news letter publication which is issued through the winter months. Edited by Ken Brownless and published by Bernard Brown, it contains news of DX stations logged, notes on how to hear m.w. DX and competitive features. For those interested in this sideline of DX listening it is highly recommended. Details are available from Bernard Brown, 60 White Street, Derby. Please enclose a S.A.E.



## SERVICE SHEETS

**SERVICE SHEETS**, also Current and Obsolete Valves for sale. **JOHN GILBERT TELEVISION**, 1b Shepherd's Bush Road, London, W12. Phone: SHE 8441.

**SERVICE SHEETS: Radio, TV, 5,000 models.** List 1/- S.A.E. inquiries, **TELRAY**, 11 Maudland Bank, Preston.

**SERVICE SHEETS**, Radio and TV, 4/- each. 1963 List now available at 2/-. All orders dispatched on day received. Also Manuals for sale and hire. List 1/- S.A.E. please. **SULTAN RADIO**, 29 Church Road, Tunbridge Wells, Kent.

**S.P. DISTRIBUTORS** is now under New Management. Try our streamlined service. We supply **SERVICE SHEETS** for Radios, Televisions, Tape Recorders, Amplifiers, etc., etc., by RETURN OF POST at 4/- each, plus postage. Send S.A.E. with inquiries. New 1963 List now available at 1/6, plus postage. Mail orders only please to **S.P. DISTRIBUTORS**, 44 Old Bond Street, London W1.

**TRADE SERVICE SHEETS** offered by retired engineer. If I haven't got it you won't get it. All 4/- each by return. Please include large S.A.E. Mail orders only. **ETZIONI**, 80 Merrion Avenue, Slanmore, Middx.

**S.E.S. SERVICE SHEETS** for all TV, Radio, including Transistors, Tape Recorders, Echo Units, Amplifiers, Record Players and Autochangers, etc., also various domestic appliances. List 1/- S.A.E. Mail orders only. **SUN ELECTRICAL SERVICES**, 38 St. George's Road, Hastings.

**SERVICE SHEETS** for all makes of Radio and TV, 1925-1963. Prices from 1/- with free fault-finding guide. S.A.E. inquiries. Catalogue of 6,000 models, 1/6. 125 Radio/TV Sheets covering many popular models, 21/- Valves, modern and obsolete. Radio/TV Books. S.A.E. lists. **HAMILTON RADIO**, Western Road, St. Leonards, Sussex.

**SERVICE SHEETS**, Radio and Television, 3/6, post paid. **VEST AND EMERY**, 17 Hallgarth Street, Durham.

## BOOKS &amp; PUBLICATIONS

**FIND TV SET TROUBLES IN MINUTES** from the great book *The Principles of TV Receiver Servicing*, 10/6 all book houses and radio wholesalers. If not in stock from Dept. B Secretary, 32 Kidmore Road, Caversham, Reading, Berks.

**AUDIO**, America's foremost journal. Year's subscription 43/-, specimen copy 4/-. All American radio journals supplied—list free. **WILLIEN** (Dept. 40), 61a Broadway, London, E16.

## MISCELLANEOUS

## ELECTRONIC MUSIC?

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 6 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing.

Write NOW for free leaflet and further details to **C. & S.**, 20 Maude Street, Darlington, Durham. Send 2d. stamp.

**RATES: 7/3 per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., London W.C.2.**

## RECEIVERS &amp; COMPONENTS

**A.1 POST FREE BARGAINS**, Guaranteed set tested valves. EP80, EB91, 10F1, 9d. each, 3 for 1/6, L63, ECL80, 2/- each. PZ30, EL38, PL33, PY31, 2/6 each. PY81, 3/-, KT36, B36, 20P1 27SU, 4/-, N37, U281, U282, 4/3. ECC82, 4/6, EB41, EBC41, ECC81, EL42, U146, UB41, UF41, UF42, UL41, UL44, UL46, UF41, 6C13, 10C2, 6LD4, 20L1, EL33, 1/- each. 30P4, 30KU, PL36, 6/6, PL82, PL83, PY80, PY82, PCF80, 3/9, OC70, 5/9. Enquire for large or small quantity discounts. Examples: EP80, EB91, 10F1 20/- per 50, 35/- per 100. ECL80 43/- per 25, 75/- per 50. **A1 RADIO COMPONENTS**, 14, The Borough, Canterbury, Kent.

## NEW VALVES GUARANTEED!

1D5	5/-	6X5G	4/6	PEN36C	5/-
1T4	1/1	7C5	5/6	PCL82	7/6
1T4	2/6	2SL6GT	4/6	PCL83	7/6
1R5	4/11	C1C	5/-	PCL84	5/-
1S5	3/11	CY31	5/-	PEN4A	5/-
6K7G	1/3	ECC85	5/-	R19	9/6
6BW7	4/6				
6X4	3/6	PEN46	2/6	TY86F	6/-

Cash with order only. Postage 6d. per valve. Any parcel insured against damage in transit 6d. extra.

**A.D.A. MANUFACTURING Co.,**  
116 Alfreton Road, NOTTINGHAM.

**WANTED: VALVES, TRANSISTORS, Etc.**  
Bought for Cash.

**"HEATHKITS"** can now be seen in London and purchased on easy terms. Free brochure. **DIRECT TV REPLACEMENTS LTD.**, Dept. PW7/9, 126 Hamilton Road, West Norwood, SE27. GIPSY Hill 6166.

**EXCEPTIONAL VALUE:** Picture Tubes, brand new, Mazda 19in. CME1901, Mullard 19in. AW47-90/91, £4 10/-; Mullard 23in. AW50/90, £6 10/-; carriage (insured) paid. 12 months' guarantee. Note: All brand new. We also supply most other sizes completely reguaranteed at £4 17 6, guaranteed 12 months. **TOMLINS**, 156 Lewisham Way, New Cross, SE14. TID 3857.



**Receivers.** American 48 set. Compact 6-valve, 6 to 9 Mc/s Superhet. Requires 3V L.T. and 150V H.T. Clean condition with handbook, 30/-. Post free. Send S.A.E. for leaflet.

**Meters.** 2 1/2in. round, 0-200 microamps, 15/-; 2in. square, centre zero, 100-0-100mA, 7/6; 3in. square 0-250mA, 15/-; Post 1/6 each. Morse Keys with Jack, new, 3/6, post 1/6. Toggle switches, equipment, 9d. post 3d., any number. Relays 1000 ohm high speed, single pole changeover, suitable for keying a transmitter, 7/6, post 1/-. Relays 12 volt coil 50 amp contacts, 3/6, post 1/-. **Receivers:** Marconi CR100, 60 Kc/s to 30 Mc/s in good condition and working order, £18.10.0. Carriage £1.




## RECEIVERS &amp; COMPONENTS

(continued)

## MARCONI CANADIAN RECEIVER

No. 52 (Brand New)

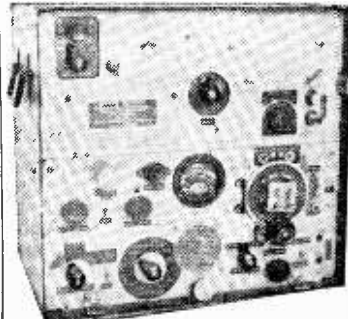

## AMATEUR SHIPPING BROADCAST

**MAGNIFICENT 10 VALVE RECEIVER.** 3 waveband 1.75-16 Mc/s 19-170 metres. with 3 valve xtal calibrator, speaker and phone outputs, complete for 230/240 AC mains and 12V DC. **BRAND NEW**, £14. Carriage £1.

**USED** Complete for 230/240 AC mains. £8.10.0. Carriage £1.

**USED (less Case)** Receiver only, £6.10.0. Carriage 10/-.

All fully tested before dispatch with circuits.

**WS 5015 MK III. TXRC.** 2-8Mc/s with economy power pack 12/24V DC. Excellent condition 80/-, Carriage 25/-, set only 55/-, Carriage 15/- all parts available.

**TXRC. 12 valve superhet 12V DC operation.** freq. 60-95 Mc/s ideal 2 or 4 metre mobile rig, easily converted, suggested mods. and circuit supplied, internal speaker and phone outputs. Size approx. 14 x 13 x 7in. **UNUSED**, £8.10.0. Carriage 10/-.

**TRANSMITTER.** 1.75-16 Mc/s 3 waveband tuneable, grid modulation using 813. Used complete with all valves, circuit £7.10.0. Carriage 10/-.

**COMMAND RECEIVERS.** BC454-B 3-6 Mc/s, BC455-B 6-9.1 Mc/s each at 90/-, Post 5/-, **BRAND NEW**.

**ROTARY TRANSFORMERS.** 12V DC input, 300V DC, 120mA output, note size only 4 1/2 x 2in. 15/-, Post 2/6.

**CONVERTER** 12 to 230V 100mA vibrator type, complete spare vibrator, battery clips, fuse, etc. **UNUSED** 25/-, Carriage 3/-.

**MOVING COIL HEADPHONES.** **BRAND NEW.** Chamois padded, complete with jack plug 15/6, Post 2/-.

**SET OF VALVES** (for 52 Receiver, 13 in all with vibrator 12/6, Post 2/6.

**110 POWER PACKS.** 115/250 AC 25/- **NEW**, 35/-, Post 5/-.

**MICROAMMETERS.** 2 1/2in. FSD 0-100 moving coil mounted in case 5 x 5 x 3in. with shock mounts, max/min sensitivity switch, 30/-, Post 5/-, Many other bargains. List 6d. S.A.E. inquiries.

**RECEIVER 308.** 19-145 Mc/s, 5 wavebands, 100/250 AC and 12V DC operation. AM/FM internal speaker, phone outputs, as **NEW**, £28.10.0. Carriage 30/-.

**TXRC. 1986.** 124-156 Mc/s. Complete 21 valves. Excellent condition. £6.10.0. Carr. 10/-.

A. J. THOMPSON

"EILING LODGE"

CODICOTE, RITCHIN, HERTS.

Phone: Codicote 242



## RECEIVERS & COMPONENTS

(continued)

### E. R. NICHOLLS

#### No. 1 BUMPER PARCEL

- 100 Assorted Resistors.  
50 Assorted Condensers.  
1 5in. 3 ohm Elac Speaker.  
1 Isolating Transformer.  
4 Terminal Blocks.  
2 Rotary Toggle Switches.  
1 Small Chassis containing 60 components.  
2 Westectors.  
2 Thermistors.  
100 Cartridge Fuses.

#### No. 2 BUMPER PARCEL

- 1 Pair Test Prods. retractable with leads and spurs.  
17 x 4in. 3 ohm Speaker.  
6 Assorted Valves.  
8 Assorted Potentiometers.  
6 Assorted Valve Bases.  
2 5-way Plugs and Sockets with leads.  
4 Mixed Plugs or Sockets.  
100 Cartridge Fuses.  
1 Inductance Variometer.

One for 20/- Post Free, or any two parcels 35/- Post Free.

20ft. Steel Telescopic Mast. 50/-.  
High Stab Resistors 6d. each.

List now ready for Paper Block Condensers, Valves, Oscillators, Test Sets. S.A.E. Please.

AR88 Jack Sockets with Isolating Switching. 4/-.

Crystal Adaptors. 1/6.  
1 amp Cartridge Fuses. 5/- per 100.  
D.P. D.T. Toggle Switches. 3 amp, 2/6; 5 amp, 3/6.

Multhead 500 pF fixed condenser at 5 kV working. 2/6.

Red Bezels for Panel Lamps. 1/- doz.  
Clydon 500 + 5000P Tuners. 2/-

Assorted Instrument Knobs. 5/- doz.  
3 assorted Thermistors. 7/6.

Plessey 25-way Plug and Socket ex new unit. 5/- pr.

Low Loss E.C. Locking Coax Plug and Socket. 3/- pr.

#### EX TV VALVES

#### MONEY BACK GUARANTEE

ECL80, EY86, PCC84, PCF80, PL81, PY81, all at 5/- each.

Paper Block Condenser, 4 mFds at 800 volts. 4/6.

Mixed New Resistors, 1 watt, 1 watt, 5/- per 100.

Transistors OC201 A.I.D. Tested, 100%. 15/- each.

Tantalum Constantin Sub Min. Disc Capacitor. 50 mF at 70 volts working. 8/- each.

Copper Laminate Board. single or double sided, 5/- per sq. ft. cut to your size.

Electro methods printed circuit connectors. 31-way. 4/6. Gold-plated contacts. Other sizes in stock.

19 Set Variometer. 5/-.

Special 0.5 ohm w.w. Resistor Sub Min. 6d. each.

Contract clearance of Speakers. 3 ohm P.M. 5in. 5/-, 6in. 6/-, 7 x 4in. 7/-, 8in. 8/-, 10in. 14/6.

TRADE ENQUIRIES WELCOME FOR ANY ITEMS ABOVE.

Mail Orders and Retail Shop:  
46 LOWFIELD ROAD,  
off SHAW HEATH  
STOCKPORT, CHESHIRE

## RECEIVERS & COMPONENTS

(continued)

**STOCK CLEARANCE:** Valves, Condensers, Resistors, Transformers. Mail only. Bargain lists. 98 Greenway Avenue, E17.

#### 100% TUBES

Rescreened, rebuilt, £4/15/-. Guaranteed year. 70°, 90°, 110°. Carriage 12/6. Mullard, Mazda, etc. NEW Boxed Valves, 12 months' guarantee! PCC84, PCF80, PCL82, EF183, EF184, BY100, BY101, etc., 7/6 each. PL81, U25, EF85, etc., 9/- each. Plus postage. Buy British Valves.

#### PHILIP BEARMAN

43 Leicester Road, New Barnet.  
Tel.: BAR 1934.

**TRANSISTORS** now half-price unmarked but tested packets of 16; unmarked untested packets of 40, duds suitable as diodes, packets of 80, all packets 10/- each, postage 1/-, Four packets post free. C.W.O. K. R. WHISTON (Dept. PWT), New Mills, Stockport.

**DIRECT TV REPLACEMENTS LTD.**, largest stockists of TV Components in the U.K. Line Output Transformers, Frame Output Transformers, Deflector Coils for most makes. Official sole suppliers for many set makers. Same Day Dispatch Service. Terms C.O.D. or C.W.O. Send S.A.E. for quotes. Day and Night Telephone GIPSY Hill 6166, 126 Hamilton Road, West Norwood, SE27.

**CRYSTAL CALIBRATOR No. 7 Mk. I** using 6 valves, a 1 Mc/s crystal osc. is used to synchronise 2 multi-vibrator osc. operating at 10 Kc/s and 100 Kc/s respectively. Harmonics of 10-100 and 1,000 Kc/s are available up to 20 Mc/s, far beyond this on any sensitive set, modulator also incorporated for receiving. In small Bakelite case with carrying handle, power 2 v. L.T., 80-120 v. H.T. Circuit and instructions supplied. BRAND NEW, 70/- Post 5/-.



**WAVE-METER INDICATOR Type 230.** Using plug-in wave-meter boxes. Into a 7-valve sensitive amplifier and indicator unit, mains operated 100-250 volts. Power unit at rear on a small separate chassis supplying 350V. D.C. at 100mA full wave rectified and 6.3 volts 4 amps L.T. Each supplied new or as new with a V.H.F. or U.H.F. wave-meter box and all connectors in wooden transit case. Wave-meter boxes easily made to all frequencies. Containing coil tuned by variable condenser, output in series with diode to input socket on indicator unit. Price for this essential piece of equipment, only 50/-, carr. 7/6.



**J. T. SUPPLY (Dept. H)**  
150 MEADOW LANE, LEEDS 11  
CALLERS WELCOME

## RECEIVERS & COMPONENTS

(continued)

**Signal Generator Type 106.** Made by Salford Electric. 5.5 to 55 Mc/s. With charts, leads, plugs, in original case. BRAND NEW. Free delivery. £7.10.0.

**ON STOCK NOW 600,000 High Stab Resistors.** ERIE, 10 ohms to 1 meg insulated 1w, 1/2, 5%. Welwyn 1w, 1/2, 5%, 10 ohms to meg. Example 1 or 1w Welwyn 5% 6d., 2% 8d., 1% 1/- Every order of 6 resistors packed in a linen finish component storage box with 7 compartments. 12 resistors 2 boxes, etc.

**SPECIAL OFFER Sub Min. Coax Plug and Socket.** made by M.E.C. 4/6 pair, also other items include Adaptors, Connectors, Junctions, Elbow Plugs, all by M.E.C.  
Complete list on application.

**Type 55 Power Pack.** Stabilised Mains Input. Outputs below:  
+200 volts at 120 mA, stabilised, DC H.T.  
-120 volts at 15 mA, stabilised, DC Bias.  
4.25 volts at 3 amp, 5 volts at 2 amp.  
6.54 volts at 18 amp, 115 volts + 115 volts.  
90/- SEND FOR FURTHER DETAILS.

**BREAKDOWN UNITS**  
**Transmitter Receiver Control Box** containing 7 instrument knobs, 4 toggle switches, 3 rotary switches, 20 small potentiometers, 2 Plessey Sockets, cases rough but components O.K. 6/- each, post paid or 2 for 10/-.

**19" RACK FITTING CABINET.** 34" high by 16" deep with telescopic drawer slides. Louvered sides, back and top. Brand new Swedish make. 24.0.0 only, plus B.R.S. delivery.

**Control Box for Photo Flash, Mk. 1,** containing 4 Toggle Switches, 2 Panel Lamps, 1 11-way 5-bank Wafer Switch, 2 Digital Counters, Electro magnetic 0 to 99 with 100 ohm coil, 4 Press-button Switches, etc. 18/-, post paid.

**Filter Unit, Type 504.** New, boxed in smart alloy case. Setable from 34 Mc/s to 86 Mc/s, with 6 Digit Counter. Complete Unit, 11/6, post paid.

#### MISCELLANEOUS

**Diamond H Sealed Relay.** 150 ohms. 4 pole double throw, 5/6, 115 volt AC Relay. P.O. Type H.D. 4 make 7 break, 7/6. Chrome handles 6in., 4/- pr; 4 1/2in., 3/- pr; 1 1/2in. 10/- pr.

**Mixed Valve Bases.** 5/- for 24. Includes latest PTFE types, Perspex 360 degree scale 10in. dia. x 1/2in., 4/6. Perspex Disc. 10 1/2in. dia. x 1/2in. 2/6.

**Government Valves.** KT33C 3/-, EB34 1/6, 5U4 4/-, EF39 2/-, ECH35 5/-, L83 3/-, 8V6 4/-, 6J5 3/-, 6J7 4/-, 6SN7 4/-, 6X5 5/-, 807 6/-, G233 3/-, 12Z1 6/-, 5Z4G 5/-, 6AC7 4/-, 6GT1 4/-, 6AM6 1/6. All Post Free.

**Capacitors.** Plesmin. .2 mF, .25 mF, 100 volts, 2/- each. Plessey Tantalum. 5 mF at 6 volt, 1/6; 10 mF at 150 volt, 2/- each. Min. Paper Dielectric .01 mF 150 9d., .01 mF at 400 1/- each. Lead through capacitor, 1000 pF 750 volts, 1/6.

**Latest Type Panel Lamps.** MES red bezel 1/6  
Arco Electric Panel Indicator Lamps, red, clear, amber, 4/6.

### E. R. NICHOLLS

Mail Order and Retail Shop:  
46 LOWFIELD ROAD  
off SHAW HEATH, STOCKPORT  
CHESHIRE

→ (continued overleaf)

## RECEIVERS & COMPONENTS


(continued)

**SPEAKER REPAIRS.** Cones fitted. Satisfaction guaranteed. L. S. REPAIRS, Pluckley, Ashford, Kent.

## DATA TRANSISTOR POCKET KITS

**NO SOLDERING OR DRILLING, COMPLETELY SELF-CONTAINED**

**NO AERIAL REQUIRED - MEDIUM & LONG WAVE - ASSEMBLY TOOL PROVIDED - CAN BE BUILT BY ANYONE**

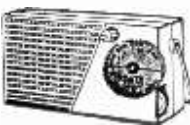

**DATA 55**  
5 SEMI-  
CONDUCTORS  
5 STAGES  
MOVING COIL  
SPEAKER  
**50/-** P.P. 2/9  
extra.  
Battery 2/3 extra.

5 1/2" x 3 1/4" in.

**DATA 427.** 4 TRANSISTORS, 2 DIODES, 7 STAGES, MOVING COIL SPEAKER **65/-**

Battery 2/3 extra. P.P. 2/9 extra.

All Parts Supplied Separately



**SPECIAL OFFER**  
**£4.19.6.**  
Post Free.

"DATROLA" transistor ELECTRONIC ORGAN. 3 octave. Complete and ready to play, with instructions and music. Size 14 1/2 x 5 in.


## DATA ELECTRONICS LTD.

6 HILLSIDE GDNS., EDGWARE, Middlesex.

## FOR SALE

**EXCEPTIONAL** Transistor Portable Tape Recorder, value £5/19/6, complete with crystal microphone, earphone, spools, tape, batteries, instructions, presentation box (extra tapes 100ft 4/6). Ideal gift. £5/19/6. Satisfaction guaranteed. Postage, packing 2/6. TOMLINS, 156 Lewisham Way, New Cross, SE14.

## SPECIAL OFFERS — NO INTEREST TERMS

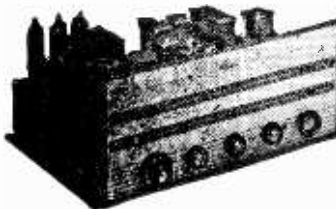

**ARMSTRONG Stereo 55 Chassis** Cash £29.18.0  
or 59/- dpt. and 12 pymts. of 44/11 monthly.  
**ARMSTRONG AF208 Chassis** Cash £21.4.0  
or 49/- dpt. and 12 pymts. of 31/10 monthly.  
**GARRARD Autoshim Changer** Cash £7.17.0  
or 16/- dpt. and 12 pymts. of 11/9 monthly.  
**GARRARD AT6/RV26A** Cash £12.5.5  
or 26/5 dpt. and 12 pymts. of 18/4 monthly.  
**A. L. STAMFORD Ltd.** (Dept. H30)  
Phone: 8HO 5003  
88 WYTHMOUTH TERRACE, LONDON E.2.

## FOR SALE

(continued)

**UNDERPILLOW SPEAKERS:** Listen without disturbing others, 15 ohms, £2/11/6; timer unit, designed for whisper teaching, famous make, 3 on/off periods in 24 hours, 13A, 200-240V, £6/13/3.—S.P. Ltd., York House, Huddersfield.

## YOU COULD READ MORSE BY JANUARY

**G** By using the RHYTHM METHOD of Morse tuition a student, starting from scratch, has passed his Morse Test in just 13 DAYS by faithfully following the instructions given in this fantastic course. You could pass the test NEXT MONTH. For explanatory booklet please send 6d. in stamps to: **GCHS, 45 GREEN LANE, PURLEY, SURREY**

**PICK OF THE WORLD'S FINEST RADIOS,** 150 models available; send s.a.e. for catalogues; part-exchanges welcome. **JOHN MUNRO,** International Radio Specialist, Library House, Lossiemouth, Morayshire, Scotland.

From **GORDON J. KING LIMITED**  
6 NEW ROAD, BRIKHAM, DEVON.  
Tel: Brixham 2304

**NOW! The "KING FM-BOOSTER"**  
(Latest VHF Transistor Printed Cct.)

★ For Better Fringe FM Reception.  
★ For FM DX Reception, etc.  
★ 6 Times Signal Gain (16dB).  
**ONLY £3.18.0 (inc. Battery, P. & P.).**

**SURPLUS SPEAKERS:** 3 ohms, 7in. x 4in. elliptical, 64in. round, 8/6 each, post free. **THE HOUSE OF WAX,** 181-183 Lake Road, Portsmouth.

## GUARANTEED TRANSISTORS

2/- each, XA101, XA102, XB103, XB104, XA112, OC430.

3/6 each, GET16, GET20, GET 884, GET873, 250mW ZENER DIODES 4 volt to 22 volt, OC44, OC45, OC71, OC81D, OC81.

4/- each, OC170, OC171, AF117, XU611, GET671, GET672, GET 673, GET691, GET692, GET693, GET694, GET884.

5/- each, OC309, OC320, OC703, OC800, OC46, OC47, ORP60, and many more.

**LARGE STOCKS of Mullard, Mazda, Bush, G.E.C., Impex, A.E.I.**

Send 3d. stamp for full list.

## B.W. CURSONS

78 BROAD STREET,  
CANTERBURY, KENT

## FOR SALE

(continued)

## GET PLASTERED!! FREE


**POINTING TROWEL WITH EACH ORDER OVER 45/-**

**RESISTORS,** Carbon 1Ω-4 meg, 1-5 watt 2/- doz. **DROPPERS,** 10Ω-20K 1/6. **POTENTIOMETERS,** 10Ω-2 meg 1/6. **CONDENSERS,** Ceramic (2-1000p), 3/Mica (5-250,000p), M/Mica (1,000,000-0.1 mfd, 3/- doz., Ppr Tube (0.001-5 mfd), 4/- doz., Block Ppr (0.001-8 mfd), 3/6, Metalpack (0.05-4 mfd), 6d. **ELECTROLYTICS** (2-8 mfd), 1/6; (8-200 mfd), 2/3; 201-14,000 mfd, 3/6. **TRIMMERS,** 1-6 gang, 5/- doz. **SWITCHES,** Water 1-3 gang, 2/3. **Biencils,** 9d. **Sliders,** 2/3. **Add-one D/P,** 1/3. **VALVE HOLDERS,** B7G, B9G, B9A, B4, B5, 6d. for 3/6 ast. doz., inc. PC Types). **TAG STRIPS,** 1, 2, 3, 7 way, 1/6 doz., 3 10, 11 way, 5/- doz. **TENSION SPRINGS,** 1-1 1/4 inch, 3/- doz., 3 inch 4d., 5 inch 5d. **SOCKETS,** 2, 3, 4, 5, 6, 8-pin, 2/- 1/2 doz. **COILS,** Aladdin, 1/-; Wierite 1/6; Others 4/9 1/2 doz. **Formers,** 2d. **BULBS,** 6-110V ast., 4/6 1/2 doz. **COND. CLIPS,** 1-1 1/4 inch, 1/6 1/2 doz. **VHRT,** 1-1 1/4 inch, 2/- doz. 2 inch 6d. **KNOBBS,** brown, 2/-, or astid., 3/6 doz. **INSULATION BOARD,** 248 sq. in. for 4/6. **GROMMETS & SLEEVES,** 1/- per 100. **FELT WASHERS,** 25 for 1/- 25 astid. **CLAMPS & BRACKETS,** 3/6. **RECTIFIERS,** 3/6. **POCKET VOLTMETERS,** 9/6. **FULSE GENERATOR** £18. **VALVE VOLTMETERS** (less Mr. Myvunt), 7/6. **BC-1094-A CONTROL UNITS,** 75/- 4-Valve **MODULATOR UNIT,** 11/6. **AC/DC P.U.,** 11/- 5-WATT **AMPLIFIER KIT,** 65/6. **S/W RADIO KIT** 57/6. **EF50A, 1/6. CONTROL UNIT No. 3 Mk. 1, 5/- 30 SELF TAP SCREWS, 2/3. SLEEVING,** 1d. yd. **TEST SET MICROPHONE & RECEIVER No. 4** £27. 2 amp. 2 pin sw. Skts, 1/- 1-**LARGE SELECTION OF ABOVE COMPONENTS** (No. 240) **GUARANTEED BARGAIN, 10/- 7 TV POTS on Strip, 7/6. Dimmer Switches, 7/6. ALL COMPONENTS ARE NEW.** Please add small amount for P. & P. S.A.E. for List. 1/- for Catalogue

**ALBATROSS ENGINEERING COMPANY**  
Dept. PW11, 78-80 HIGH STREET, GOSBERTON, SPALDING, Lincs. (Dov. 456)

**250 "12 DRAWER UNITS."** New, ex-works, £41/15/-, carriage paid (mainland). Each drawer 5 1/2 in. wide, 3 1/2 in. high, 10 1/2 in. long. Stove enamelled green, heavy gauge perfect steel. 12 dividers free. Catalogue free (Dept. Z4), N. C. BROWN LTD., Eagle Steelworks, Heywood, Lancs.

## GUITAR AMPLIFIERS WITH TREMOLO

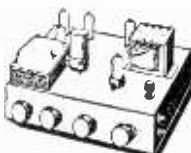

Hi Fi 15 watts. Valves ECC83, ECC83, ECC83, EL84, EL84, EZ81. Four jack inputs. Six controls: two volume, bass, treble, tremolo speed, depth. Remote plug. 3 and 15 ohm outputs. Real value. Kit £8, ready built £11. Similar 30 watt. Valves ECC83, ECC83, ECC83, EL34, EL34, GZ32. Kit £11, ready built £14. Similar twin input less tremolo 15 watt (illus.). Kit £6.10.0, ready built £9. 30 watt, Kit £9.10.0, ready built £12. Add carr. 7/6 any amplifier. Send for free leaflet.

**STROUD AUDIO**  
Bath Road, Stroud, Glos.


**A COMPLETE PORTABLE RADIO** (Peto-Scott Model B.P.4) for less than the cost of the 4 valves included—DK91, DF91, DAF91, DL92. Uses 90 V. and 14 V. batteries. A SNIP AT 39/6 (P. 7/6). ACT FAST—THEY WON'T LAST LONG.

**E.S.G.**

25 Christleton Road, Chester, Ches.

## FOR SALE (continued)

### 2 for price of ONE

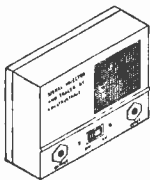

The first combined transistorised signal injector plus signal tracer in same case. Injector covers 2 K/c to 2 Mc. Tracer has R.F. detector. Separate flexible probes. Small battery lasts months. Easy to assemble with all diagrams provided.

ONLY 47/6 In Kit Form } P.P.P.  
OR 60/- Built and Tested } 1/-

Send now while stocks last to—

### CONSTRUCTAKIT

61 CEMETERY ROAD, GATESHEAD 8  
Co. Durham.

## WANTED

### WANTED VALVES ONLY

Must be new and boxed.  
Payment by return.

**WILLIAM CARVIS LTD.**

103 North Street, Leeds 7

**A PROMPT CASH OFFER** for your surplus brand new Valves and Transistors. R.H.S., Beverley House, Mannville Terrace, Bradford 7.

**BC312 RECEIVERS**, good condition unmodified. Giffilan, 98 Dominion Road, Worthing. Tel: 8719.

### NEW VALVES WANTED

Any type, any quantity

### CASH PAID

**R.S.T. Valve Mail Order Co.**

211A Streatham Road

Mitcham, Surrey

Telephone: MITCHAM 6202

**WANTED: TEST GEAR**, Meters, Valves, Components, Communication Sets, Amplifiers. Letters only. HUGGETT'S LTD., 2-4 Pawson's Road, West Croydon, Surrey.

### SOUND RECORDINGS

**A UNIQUE BUY!** Recording Tape, top brand, 5 1/2 in., 1,200ft. 19/6; 7 in., 2,400ft. D.P., 28/6. P. and P. 1/6 per spool. Bargains in all sizes. S.A.E. for list. E. C. KINGSLEY AND CO., 132 Tottenham Court Road, London, W1. EUSTON 6500.

## SITUATIONS VACANT

**A.M.I. Mech.E., A.M.Brit.I.R.E.,** City and Guilds, G.O.E., etc., brings high pay and security. 'No pass—no pay' terms. Over 95% successes. For details of exams and courses in all branches of Engineering, Building, Electronics, etc., write for 148-page handbook—free. B.I.E.T. (Dept. 242B), 29 Wright's Lane, London, W8.

**RADIO AND TV Exams and Courses** by Britain's finest Home-study School. Coaching for Brit.I.R.E., City and Guilds, Amateur's Licence, R.T.E.B., P.M.G. Cert., etc. FREE brochure from **BRITISH NATIONAL RADIO SCHOOL**, Russell Street, Reading.

**CITY AND GUILDS** (Electrical, etc.) on 'no pass—no fee' terms. Over 95% successes. For details of Electrical, Engineering, Applied Electronics, Automation, etc., send for our 148-page handbook, free and post free. B.I.E.T. (Dept. 242A), 29 Wright's Lane, London, W8.

**TV AND RADIO**, A.M.Brit.I.R.E., City and Guilds, R.T.E.B. Cert., etc., on 'no pass—no fee' terms. Over 95% successes. For details of exams and courses including practical apparatus, in all branches of Radio, TV and Electronics write for 148-page handbook—free. B.I.E.T. (Dept. 242C), 29 Wright's Lane, London, W8.

### METAL WORK

**METAL WORK.** All types cabinets, chassis, racks, etc., to your specifications. **PHILPOTTS METAL WORKS LTD.**, Chapman St., Loughborough.

**Cases, Chassis, Frames, etc.,** anything in metal. Send your drawings for quotation. 'One-offs' with pleasure. Trade enquiries welcomed.

Stove enamelled any professional finish.

*Moss Watson*

40 MOUNT PLEASANT STREET  
OLDHAM, LANCs. MAIN 9400

### EDUCATIONAL

**BECOME "TECHNICALLY QUALIFIED"** in your spare time. Guaranteed Diploma and Exam., Home-study Courses in Radio, TV Servicing and Maintenance, R.T.E.B., City and Guilds, etc. Highly informative 120-page Guide-FREE! **CHAMBERS COLLEGE** (Dept. 363), 148 Holborn, London, EC1.

**RADIO OFFICERS** see the world. Sea-going and shore appointments. Our many recent successes provide additional trainee vacancies during 1964. Day and Boarding students. Grants and Scholarships available. Stamp for Prospectus. **WIRELESS COLLEGE**, Colwyn Bay.

**THE INCORPORATED PRACTITIONERS** in Radio & Electronics (I.P.R.E.) Ltd., Membership Condition booklet 1/-, Sample copy of I.P.R.E. official Journal 2/- post free. Dept. B Secretary, 32 Kidmore Road, Caversham, Reading, Berks.

## EDUCATIONAL (continued)

### Radio Television & Electronics

Learn at home with the world's largest home study organisation, Brit.I.R.E.; City & Guilds; P.M.G.'s certs., etc. Also Practical Courses with equipment.

All books supplied.

Write for **FREE prospectus** stating subjects to

### I.C.S.

(Dept. 541), Intertext House,  
Parkgate Road, London, S.W.11

### THE AMATEUR RADIO HANDBOOK

by R.S.G.B., 3rd edition, 34/-, postage 2/6. Tested Superhet Circuits for Shortwave and Comm. Receivers using M.A.T.s, 6/-, Postage 6d.

T.V. Engineer's Pocket Book, by Hawker, 12/6, Postage 1/-.

Amateur Radio Call Book by R.S.G.B., 4/6, Postage 6d.

Electronics Pocket Book by Hawker, 21/-, Postage 1/-.

How to Listen to The World, 1963-64 ed. by Johansen, 14/6, Postage 1/-.

Wireless Servicing Manual, new ed. by Cocking, 25/-, Postage 1/-.

Understanding Amateur Radio, new ed. by A.R.R.L., 19/-, Postage 1/-.

Special offer of Micro Alloy Transistors etc. send for list.

**UNIVERSAL BOOK CO.**  
12 Little Newport Street, London, W.C.2  
(adjoining Lisle Street)

### NEW VALVES!

Guaranteed Set: Tested  
24-HOUR SERVICE

1R5, 1S5, 1T4, 354, 3V4, DAF91, DF91,  
DK91, DL92, DL94, SET of 4, 15/-,  
DAF96, DF96, DK96, DL96, SET of 4, 23/-

0A2 4/8 DK96 6/3 1CF80 5/6

1D5 4/8 DL33 7/- PCF82 6/8

1R5 4/8 DL35 6/3 PCL82 6/8

1S5 3/8 DL92 4/0 PCL83 8/8

1T4 2/3 DL94 5/6 PCL84 4/6

354 4/8 DL96 5/8 PL36 8/8

3V4 5/6 EB91 2/- PL81 7/-

5U4G 4/3 FBC41 7/- PL82 5/8

5Y3GT 4/3 EBF30 7/- PL83 5/8

6Z4G 7/- EBL21 8/- PL84 6/-

6K7G 1/3 ECC40 7/- PY31 6/-

6K8Q 3/6 ECC81 3/6 PY32 8/6

6Q7G 4/3 ECC82 4/6 PY80 5/-

6U7G 7/8 ECC83 5/6 PY81 5/6

6V8Q 3/6 ECC84 5/6 PY82 5/3

6X5GT 5/6 ECC85 7/- PY83 6/8

12K7GT 3/8 ECF80 6/- U25 8/9

12K8GT 8/8 ECF82 6/6 U26 7/8

12Q7GT 3/8 ECH42 7/9 UABC90 5/6

12SN7GT 6/8 ECL80 6/6 UAF42 7/8

35L8GT 7/3 EF41 6/6 UBC41 7/8

35Z4GT 4/8 EF80 4/- UB30 7/-

85A2 6/8 EF85 4/- UCC85 6/6

AC/TP 18/6 EF86 6/- UCH42 7/3

AZ3 8/6 EF89 3/9 UCH81 7/3

CL33 8/6 EF91 2/9 UCL82 7/9

DAC32 8/- EL41 7/3 UCL83 8/8

DAF91 3/8 EL84 5/3 UF41 6/9

DF96 5/9 EY51 5/9 UF89 6/3

DF33 5/6 EY86 5/9 UF91 6/11

DF91 2/3 EZ40 5/3 UL41 6/13

DF96 5/9 EZ90 4/6 UL84 6/3

DH77 4/3 EB81 3/9 UJ8 11/6

DK92 6/6 MU14 4/6 UY21 8/3

DK91 4/6 PCC84 5/9 UY41 4/6

DK92 6/8 PCC89 7/3 UY85 4/-

Postage 6d. per valve extra. Any Parcel

Insured Against Damage in Transit 6d. extra

Any C.O.D. Parcel 4/6 extra.

Office address, no callers.

**GERALD BERNARD**

83 OSBALDESTON ROAD,  
STOKE NEWINGTON,  
LONDON, N.16

**SPARES!**

Condensers, 100, 10 $\frac{1}{2}$ . New Assorted electrolytics & P.F.s. Resistances. 100—5 $\frac{1}{2}$ . Assorted sizes, watts, grades. VALVES 9d. each. 40—£1. Thousands of Valves available. P.P. on 1 - 4 6d., 12 1/6.

**SPEAKERS 7/9 EACH**

6in. 8in. 7in. x 4in. Money back guaranteed. Enquire for other sizes. Ex. mid. salvage. P.P. 1/3.

**TELEVISION TUBES**

REGUNDED. Guaranteed 1 Year.

21in. 17in. 15, 14 and 12in. 99/6 79/6 59/6

Ins. and Carr. 10/6. Add 10/- refundable on OLD TUBE. 110" Tubes in stock.

**TV EXTRAS**

TV AERIALS 25/- Indoor combined. Complete with 12ft. co-ax and plug. P. & P. 2/6.

**AERIALS**

Loft Combined 35/6. BBC with 3 element I.T.A. Universal fitting. P. & P. 3/6.

Co-ax Cable 6d. per yd. Plugs 1/3 ea. LEGS, complete with fittings, for any set, 35/6.

**TELEPHONE HANDSETS 15/6 pair.**

G.P.O. standard pattern, House to Workshop, garage, inter-office, etc. Works off any small battery. P. & P. 4/6.

**TELEPHONES 25/-.**

Complete instrument with dialing and bell. P.P. 5/-.

**TRANSISTOR EARPIECES 9/6.**

Complete with plug and lead. P.P. 6d.

ILford 6001/3

**DUKE & CO (LONDON) Ltd**

621/3 ROMFORD RD.

MANOR PARK E12

Stamp for latest Free List.

**Ex. Maintenance Tested Tubes.**

15/- 36/24, 14KP4 141, 121, 31/74

Satisfaction G't'nd. Carr. 5/-.

17"—£11.10.0

14"— £7.10.0

12 months' Full Written Guarantee.

Channels for all areas.

Demonstrations daily in our Shop. Personal collection advised.

Carr 14in. 20/- 17in. 30/-

**BARGAIN OFFER!**

**AMPLIFIER.** 3 watts, 2 valves, 6X4, ECL82. AC Mains. Mounted on board with 6in. speaker. Pilot light and Tone Control. £3.10.0 complete, post 4/6.

**SPEAKER** suitable for above cabinet. R.T.C. 15 ohm 15 watts. Heavy duty 12in., £5, post 4/-.

**CONNECTING WIRE.** Stranded or Single. Various colours, our selection, 100ft., 4/-.

**ELECTROSTATIC** Tweeter LSH75 with diagram, only 2/6 each.

**SPEAKER CABINET.** The HAYDON (17 x 15 x 8in.). Designed to take a 12in. heavy duty speaker. Made of 3in. wood. Ideal for bass guitar. Covered with Vynide and Vynair in contrasting colours. With strong carrying handle, 60/-, post 7/6 extra.

**STEREO** Ronette S106, 25/-.

**CARTRIDGES**, Monaural. Acos GP59-5 high output, 15/- . Acos GP65-1G medium output, 15/-, to fit most Garrard, Collaro or B.S.R. pick-ups.

**EARPIECES** with cord and 3.5 mm plug. Crystal, 4/-; 180 ohms magnetic, 6/6; 80 ohm 2.5 plug, 4/-.

**HIGH RESISTANCE PHONES:** 4,000 ohms. Chinese, 11/6 pair. **TRANSISTOR ELECTROLYTICS:** 1 $\mu$ F, 2 $\mu$ F, 4 $\mu$ F, 5 $\mu$ F, 8 $\mu$ F, 16 $\mu$ F, 32 $\mu$ F, 50 $\mu$ F, 100 $\mu$ F, all 15 volt, 1/3 each.

**BARGAINS IN TRANSISTORS.** The latest Mullard M Series. OC44M, two OC45M, OC81DM. Two OC81M matched pair; OA90 diode. Complete Set, 22/6. OC44, 3/6; OC45, 3/-; OC71, 2/6; OC72, 3/-; OA81, 2/3; GEC S6 Good AF General Purposes, 2/- . GET873 RF, 2/3.


TERMS: C.W.O.

**BROADWAY ELECTRONICS**  
92 MITCHAM ROAD, TOOTING, S.W.17.  
(four minutes from Tooting Broadway Underground Station)


**IDEAL XMAS GIFTS!**

The "PORTO-BELLO"

TRANSISTOR,  
POCKET  
RADIO

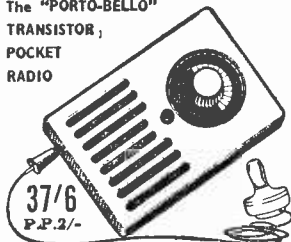

Designed exclusively for personal use. Works anywhere, any time—wonderful reception over the full medium wave band. B.B.C. Home, Light, Luxembourg, etc. Completely portable, compact size, only 2 1/2 x 3 1/2 x 1 1/2 in. slips into pocket. NO EXTERNAL AERIAL OR EARTH REQUIRED. Complete station separation, ideal for use as Tape Jack for recording or tuner unit for amplifier. Earpiece 5/- ex. Battery 2/6 ex.

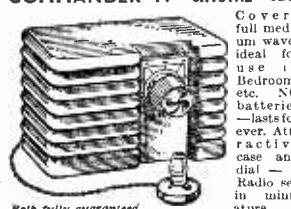**COMMANDER IV CRYSTAL SET**

Covers full medium wave, ideal for use in Bedroom, etc. NO batteries—lasts for ever. Attractive case and dial—a Radio set in miniature.

Both fully guaranteed  
PRICE 10/- P & P. 2/-. Earpiece 5/- ex.  
TRANSRADIO (Dept. P.W.12)  
11 OLIVER ROAD, LONDON E.17

**FIRST-CLASS RADIO AND T.V. COURSES... GET A CERTIFICATE!**

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure a recognised qualification or extend your knowledge of Radio and T.V. Let us show you how.

**FREE GUIDE**

The New Free Guide contains 120 pages of information of the greatest importance to both the amateur and the man employed in the radio industry. Chambers College provides first-rate postal courses for Radio Amateurs' Exam., R.T.E.B. Servicing Cert., C. & C. Telecoms., Grad. Brit. I.R.E. Guide also gives details of range of diploma courses in Radio/T.V. Servicing, Electronics and other branches of engineering, together with particulars of our remarkable Guarantee of

**SUCCESS OR NO FEE**

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER  
150,000 SUCCESSES

**CHAMBERS COLLEGE**  
(Incorp. National Inst. of Engineering)  
(Dept. 461), 148 HOLBORN  
LONDON, E.C.1



*The PUNCH  
you need!*

**HOLE PUNCHES**

Instant Type	...	...	...	6/10 ea.
3/8" diameter				
1/2" diameter Toggle switch				8/6 "
1/2" diameter				8/6 "
" B7G				9/- "
" B8A, B9A...				9/6 "
" ...				10/2 "
" ...				10/8 "
" ...				11/8 "
1 1/2" diameter Int. Octal...				13/4 "
1 1/2" " ...				16/2 "
1 1/2" " ...				18/10 "
1 1/2" " B9G				21/8 "
1 1/2" " ...				24/4 "
2 1/2" " Meter				33/2 "

Complete Set £9.3.6.

No extra charge for postage and packing in the U.K.

**Oliver & Randall Ltd**

Dept. 7  
7 KELSEY PARK ROAD  
BECKENHAM, KENT  
Tel.: Beckenham 8262

**SPEAKERS BY GOODMAN'S  
ELAC, PLESSEY, etc.**

	P. & P.
4in. square .....	12/- 1/6
5in. round .....	12/- 1/6
7 x 4in. elliptical..	13/6 1/6
8 x 5in. elliptical..	16/6 2/-
10 x 6in. elliptical..	23/6 2/-

**18G STEEL CASES**

Finished in superior quality hammer grey with aluminium removable panel on face.

**Sloping Front:**

4 x 4 x 4 .. .. .	10/6
8 x 5 x 5 .. .. .	16/-
12 x 6 x 6 .. .. .	25/6

**Rectangular Small:**

4 x 4 x 2 1/2 .. .. .	8/6
6 x 4 x 3 .. .. .	10/-
8 x 6 x 3 .. .. .	12/6

**Rectangular Standard:**

10 x 7 x 7 .. .. .	27/6
12 x 7 x 7 .. .. .	34/-
14 x 7 x 7 .. .. .	37/6
14 x 8 x 9 .. .. .	47/6
16 x 8 x 9 .. .. .	52/6
16 x 8 x 11 .. .. .	57/6
19 x 8 x 11 .. .. .	64/-
19 x 10 x 11 .. .. .	66/-

P.P. extra.

**OUR FAMOUS READIPACKS!**

- No. 1 100 resistors 1w to 5w 10 ohm to 5 meg.  
No. 2 25 condensers 1pF to 1000pF 5% to 20%.  
No. 3 20 condensers 1000pF to 0.01mfd.  
No. 4 12 condensers 0.01mfd to 0.1mfd.  
No. 5 25 Hi-stab resistors 1, 2 and 5% 10ohm-25meg.  
No. 6 10 w/w Resistors 60ohm-82K ohm.  
No. 7 4 Carbon controls, volume, tone, etc.  
All at 8/6 each. POST FREE.

**SWITCHES for MULLARD  
circuits to specification  
and "Mullard approved"**

TR2 2V Pre-Amp. ....	12/9
TR3 3V Pre-Amp. ....	12/9
TR4 3V Pre-Amp. Hi/Pass	10/9
TR5 3V Pre-Amp. Hi/Pass	8/4
TR6 3V Tape Amp. Rec/Play	16/6
TR7 3V Tape Amp. Rec/Play	16/6
TR8 Tape Pre-Amp. Rec/Play	7/4
TR9 Tape Pre-Amp. Rec/Play	18/6
TR10 Stereo Pre-Amp. Selector	9/6
TR11 Stereo Pre-Amp. Ch/E	9/6
TR12 Stereo Pre-Amp. Stereo-Mono	9/6

P. &amp; P. 1/- per switch.

**TELE-RADIO (1943) LTD**

189 EDGWARE ROAD, LONDON W2  
PADDINGTON 4455

OSMOR

## PRICE LISTS & INFORMATION ON Various Designs in

Practical | Radio | Wireless | R.S.G.B.  
Wireless | Constructor | World | Bulletin

SEND 6d. POSTAGE FOR

**CIRCUITS****OSMOR LTD**

418 BRIGHTON ROAD  
S. CROYDON SURREY  
Telephone CRO 5148

## FREQUENCY DIVIDER ORGANS FOR THE CONSTRUCTOR

This new book for amateur constructors describes the constructional details of two frequency divider organs. Both organs described are well tried designs but a number of other circuits are included for experimenters.

By A. Douglas.

25/- Postage 9d.

**ABC'S OF TRANSISTORS**, by G. B. Mann. 5/- Postage 6d.

**A BEGINNER'S GUIDE TO RADIO**, by F. J. Camm. 7/6. Postage 6d.

**RADIO SERVICING PROBLEMS**, by W. A. L. Smith. 5/- Postage 6d.

**ELECTRONICS POCKET BOOK**, by J. P. Hawker & J. A. Reddihough. 21/- Postage 9d.

**MODERN TAPE RECORDING & HI-FI**, by K. Peters. 30/- Postage 1/3.

**RADIO & TELEVISION TEST INSTRUMENTS**, by G. J. King. 25/- Postage 1/6.

**RADIO VALVE DATA**, Compiled by "VW" 7th Ed. 6/- Postage 10d.

**COMPLETE CATALOGUE** 1/-.

**THE MODERN BOOK CO.**

BRITAIN'S LARGEST STOCKIST  
of British and American Technical Books

19-21 PRAED STREET  
LONDON, W.2

Phone: PADDINGTON 4185  
Open 6 days 9-6 p.m.

## VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

**SETS** 1RS, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94 .. Set of 4 for 15/-  
DAF96, DF96, DK96, DL96 .. .. . 4 for 23/6

1A7GT 9/-	6V6GT 3/6	CY31 5/9	ECH81 6/6	PCC85 7/8	U52 4/3
1D5 6/6	6V6GT 6/6	EAC32 8/3	ECL80 8/3	PCC89 8/-	U78 3/9
1HSGT 8/3	6X4 3/9	LA91 3/9	ECL82 7/6	PCF80 5/9	U191 11/-
1NGST 8/-	6X5GT 6/9	LA96 6/9	ECL86 9/-	PCF82 6/9	U281 9/8
1K5 4/9	7B7 8/-	DCC90 6/9	EF37A 5/6	PCF84 11/9	U282 14/6
1T4 3/6	7C6 7/9	DF91 2/6	EF38 3/9	PCF86 8/-	U291 8/-
3A5 6/9	7H7 5/9	LF96 6/-	EF42 5/-	PCL82 7/3	U301 12/6
3Q4 5/6	7N7 9/9	DH76 3/9	EF80 4/3	PCL83 9/-	U801 18/-
3S4 4/9	7Y4 5/-	DH77 4/9	EF85 5/-	PCL84 5/-	UABC80 5/9
3V4 5/6	10C1 9/-	DK32 9/-	EF86 6/3	PCL85 8/6	UAF42 3/-
5U4G 4/6	10C2 13/-	DK91 4/9	EF89 4/-	PEN4DD	UBC41 6/11
5Y3GT 5/-	10F9 10/-	DK92 6/9	EF91 3/3		UBC81 7/3
5Z4G 8/9	12A76 4/9	DK96 6/6	EF92 2/6	PEN4A 7/3	UBF80 7/8
6AB9 6/9	12A77 3/9	DL33 7/3	EF184 2/9	PEN39C 9/-	UBF89 7/3
6AL5 2/-	12AU7 4/9	DL35 6/9	EL33 7/6	PL38 8/9	UBL21 10/-
6AQ5 6/-	12AX7 4/9	DL82 4/9	EL41 7/9	PL31 18/6	UCB4 9/-
6AT6 4/9	12K7GT 8/9	DL94 5/6	EL42 7/9	PL41 7/6	UCC85 6/9
6BA8 6/-	12K8GT 8/9	DL96 8/-	EL44 5/6	PL42 5/6	UCF80 10/3
6BE9 5/3	12Q7GT 4/3	EABCB0 5/3	EM34 7/3	PL43 5/6	UCH42 7/6
6BG6G 12/6	12Z3 8/6	EAF42 8/-	EN80 6/9	PL44 6/9	UCL82 8/-
6BH6 5/-	19BG6G 13/6	FB91 2/-	EM81 8/-	PL45 6/9	UCL83 9/-
6CB6 5/6	20F2 11/9	EB33 5/-	EM84 8/3	PN35 7/9	UF41 7/3
6CD6G 26/6	20P4 14/9	EB41 7/3	EM87 8/9	PY32 9/-	UF42 5/-
6F1 5/6	20P5 14/9	EB43 6/9	EM88 8/9	PY33 10/-	UF43 6/3
6F13 4/9	25L6GT 5/9	EBF80 7/3	EY86 6/-	PY80 5/3	UL41 6/9
6F14 9/-	25U4GT 10/6	EBF83 7/9	EZ40 5/6	PY81 5/9	UL44 10/6
6F21 9/6	30PL1 9/6	EBF89 6/9	EZ41 7/6	PY82 5/6	UL46 8/9
6K7G 1/6	30PL15 10/-	EBL21 8/9	EZ80 4/6	PY83 6/6	UL84 6/3
6K8GT 4/-	30PL17 9/-	EBL31 19/6	EY81 6/-	PY88 8/-	UY8 7/7
8K8G 4/3	30PL13 9/6	ECC40 7/6	KT32 5/-	TH21C 10/6	UY21 8/9
8K8CT 7/9	35A5 14/-	ECC81 3/9	KT36 14/-	TH233 15/6	UY41 4/6
8LBG 5/9	35L6GT 7/9	ECC82 4/9	KT61 7/6	TY86F 11/3	UY85 4/3
8LD20 5/3	35Z4GT 4/11	ECC83 7/-	KT63 3/9	U22 15/-	VP4B 8/9
8P25 7/9	A231 6/11	ECC84 6/3	MU14 5/-	U24 15/-	VP4B 8/9
8P28 9/6	B36 4/9	ECC85 7/3	MX40 5/6	U25 9/-	VP1321 15/-
8Q7G 4/9	CBL31 17/9	ECP80 8/3	N18 8/-	U26 8/-	W78 7/6
8Q7GT 7/9	COH35 12/9	ECP82 8/6	PC85 8/-	U37 17/-	W77 2/6
6SL7GT 5/9	CL33 9/6	ECH42 8/3	PC87 8/-	U38 9/9	W79 14/-
6SN7GT 4/-	CY1 12/6		PCC84 6/6	U50 4/6	W83 6/6

Post 6d. per valve extra.  
Any Parcel Insured  
Against Damage in  
Transit 6d. extra.  
Any C.O.D. Parcel 4/3 extra.

**READERS RADIO**  
24 COLBERG PLACE, STAMFORD HILL  
LONDON N.16 STA. 4587

## HERE'S A LOW COST WAY TO GET INTO REALLY PROFITABLE T.V. SERVICING FAST!

Maybe you enjoy fixing electrical gadgets or the odd radio or two. Maybe you wish you could. In either case you are probably just the man who could benefit from a new revolutionary type of television training programme now being introduced for the first time.

Knowing that early success will usually spur a man on to greater achievement, we have made a point of teaching first how to make the easiest T.V. repairs. Since the easiest T.V. repairs are the ones most often found on service calls, you are ready to make money right after the first lesson. Then as you progress you will learn how to handle every kind of trouble found in all makes of T.V. sets.

Here for example are some of the items covered in the course:

1. Simple adjustments to correct poor pictures.
2. Circuit faults indicated by a poor pattern.
3. Finding bad valves by observing picture faults.
4. Antenna principles and practices.
5. Facts about the T.V. signal to help you in repair work.
6. All about Cathode Ray tubes.
7. How to tell what is at fault.
8. Explanation of television circuits.
9. U.H.F. converters and tuners.
10. Television test equipment and alignment.
11. Advanced trouble shooting by picture analysis.

This is a real home study course that has been bound into one giant 8 x 11 in., 192 page manual to reduce cost.

Compares favourably with some courses costing very much more! By creating a mass market, through large volume sales and eliminating individual letter writing we are able to pass on these savings directly to you!

The course features over 325 different line drawings, circuits, servicing charts and illustrations to simplify the text and make your study more enjoyable. Soon you will be well on your way to becoming a first-class television repair technician!

### YOU TAKE NO CHANCES WHEN YOU DEAL WITH SIM-TECH

You must be convinced that this is the best value you have ever seen in television training, otherwise you can return the course (or have your money refunded if sent with order) after you have examined it in your own home for a period of seven full days.

The price? Only 36/- per course, plus postage and packing, 1/6.

### FREE TRIAL OFFER

Terms only 5/- per week if you wish.

To SIM-TECH BOOK COMPANY Dept. BT2, West End, Southampton, Hants.

☐ Please send your Television Course for a full seven days' free trial. If not delighted I will return the course post-paid without further obligation on my part. Otherwise I will pay cash or 5/- weekly until 37/6 plus 2/6 service charge, total 40/-, is paid.

☐ Tick here if enclosing full price of 37/6. (Same 7-day money back guarantee). NOTE: Customers who send cash with order get in addition a 71-page book on TELEVISION FAULTS. (This offer closes March 31st, 1964).

Overseas customers please send full amount (including Ireland).

Name .....

Address .....

City..... County.....

### ULTRA VIOLET BULBS

Easy to use source of UV for dozens of practical and experimental uses.

12 volt 36 watt AC/DC SBC 8/6. P. & P. 1/-.  
12 volt 60 watt AC/DC SBC 8/6. P. & P. 1/-.  
Transformer to suit the above. Input 200-240 A.C. Output 12 Volt A.C. 36 watt, 16/6. P. & P. 2/6. Input 200-240 A.C. 12 volt A.C. 60 watt, 22/6. P. & P. 3/6.

Set of 4 colours FLUORESCENT Paint. Red, Orange, Green and Blue in 1 oz. tins. Ideal for use with the above Ultra Violet Bulbs, 9/6. P. & P. 1/6.

### BUILD AN EFFICIENT STROBE UNIT FOR ONLY 37/6.

The ideal instrument for workshop, lab. or factory. This wonderful device enables you to "freeze" motion and examine moving parts as stationary. We supply a simple circuit diagram and all electrical parts including the NSP Strobe tube which will enable you to easily and quickly construct a unit for infinite variety of speeds, from 1 flash in several seconds to several thousands per minute. New modified circuits brings price down to 37/6 plus 3/- P. & P.

NSP 4V256 STROBOTRON FLASH-TUBE made by Ferranti, brand new. I.O. base. Price 15/-, P. & P. 1/-.

### MAGNETIC COUNTERS 10 MAGNETIC SECONDS

Very latest High Speed type ex P.O. guaranteed perfect. Type No. 100B. coil 2,300 ohms. for 48 volt D.C. operation (will work on 35 volt). overall size 4 x 1 x 1 in. Also available type 101A which can be used as an interesting accessory with our Strobe unit. Either type price 15/-, P. & P. 1/6.



### VARIABLE VOLTAGE TRANSFORMER £4.10.0

Post Paid. Input 230 v. A.C. Output 0-250 v. at 1 amp. fully shrouded, new. Also available 2.5, 5, 8, 10, 12 and 20 amp. Write for details.

4,000 Ohm Headphones, brand new (imported). 12/6 each pair. P. & P. 1/6.

SIEMENS H.S. RELAY. Very latest type, sealed. H86E. 1,700 ohms plus 1,700 ohms single C/O contacts. Price 18/6 each, plus 1/-, P. & P.

6 VOLT 40 A.H. ACCUMULATOR, in metal case with leather carrying handle. New. Price 27/6, carriage 8/-.

9 P.D. GEARED MOTOR 24 v. D.C. will operate from 12 v.). Double gear box. Consumption 200 mA. Size 3 1/2 x 2 1/2 x 2 1/2 ins. Weight 15 oz. Small. Powerful. Fully suppressed. 32/6. P. & P. 3/6.

230 VOLT A.C. GEARED MOTORS Type D18G 80 r.p.m. 2 1/2 lb. inch. £11.9.6. P.P. 2/-. Type D16G 5 r.p.m., 1.7 lb. inch. £2.9.6.. P.P. 2/6. Type D16G, 13 r.p.m., 1.45 lb. inch. £2.12.6. P.P. 2/6.

### LIGHT SENSITIVE SWITCH

Kit of parts, including ORP .12 Cadmium Sulphide Photocell, Relay, Transistor and Circuit, etc., price 25/- plus 2/6 P. & P. ORP 12, including circuit, 10/6 each plus 1/- P. & P.

### MINIATURE UNISELECTOR SWITCH

3 banks of 11 position plus homing bank 40 ohm coil. 24-240 v. operation. Ex-equipment. Individually tested. 22/6, plus 2/6 P. & P.

MINIATURE LEAD ACID ACCUMULATORS. (Brand new) 2V. 1.5 A.H. Size 1 1/2 x 1 1/2 in. Wt. approx. 1 lb. 16/6 for 3. P. & P. 1/6. 12V. 0.75 A.H. Size 4 x 3 x 1 1/2 in. Wt. approx. 2 lb. (can be used as double 6V.). 15/6 each. P. & P. 1/6.

### TRANSISTORS

OC30	10/-	OC78	7/-	Get 573	12/6
OC41	7/-	OC78	6/-	Get 573	25/-
OC45	5/-	OC77	9/-	M/Pair	
OC45	9/-	OC139	12/-	2N458	20/-
		OC140	19/-	SB345	7/6
OC71	5/-	OC140	19/-	AF114	11/-
OC72	5/-	OC200	10/6	AF115	10/6
OC72	14/-	OC201	21/-	AF116	10/6
		Get 104	6/-	AF117	9/6
OC73	6/-	Get 105	10/-		

### SERVICE TRADING CO.

All Mail Orders also callers.  
47-49 High Street, Kingston on Thames  
Tel: KINGSTON 9450

Personal callers only  
9 Little Newport Street, London W.C.2  
(off Leicester Square) Tel: GARRARD 0576

## Lewis have the Cabinet for you

We can supply any cabinet to your own specification

This is only one example of—  
THE LARGEST RANGE  
OF CABINETS IN THE  
COUNTRY

Equipment is also our  
speciality.



The Grosvenor  
Price 18 gns.



The Lowboy  
Price 24 gns.

### LEWIS radio

100(P14) Chase Side, Southgate  
London, N.14. Tel 3733/9666

Send today for the two new  
Lewis Catalogues

Designed to assist your choice of  
cabinet and equipment.

THE New Lewis Radio Cabinet Catalogue—the most comprehensive ever prepared. THE unique 60 page equipment catalogue.

Please send your two new catalogues! enclosed is P.O. for 3/6 which will be credited against any purchase I make.

Name.....

Address.....

BLOCK CAPITALS PLEASE

# STOP-LOOK!

## TRANSISTORS from 1/3

GREEN SPOT A.F. 3 volt. 1/3.  
RED SPOTS. Now only 1/9.  
WHITE SPOTS. Down to 2/3.  
MICRO-ALLOY MAT100 7/9, MAT101 8/6, MAT120 7/9, MAT121 8/6.

BOOKS 22 Tested Circuits  
Using MATs, 5/-.  
SHORT WAVE CIRCUITS using  
MATs 5/-.  
SHORT WAVE SUPERHETS using  
MATs 6/-.  
WIRELESS WORLD VALVE DATA 6/-.

## COMPONENTS by REPANCO

DRX1 Dual Range CRYSTAL Set Coil  
with Circuit, 3/-.  
DRR2 Dual Range Coil with REACTION  
with Valve and Transistor Circuits, 4/6.  
FR2 FERRITE ROD AERIAL with  
Circuit, 12/6.  
CHI R.F. Chokes, 2/6.  
TT46 Output Transformers, 5/-.  
TT49 4.5 to 1 Interstage Transformer,  
5/-.  
TT23 Driver for 10 Watt Amplifier, 22/6.  
TT24 Output Transformer 10 W, 22/6.  
XT50 Min. Double Tuned I.F.T., 6/9.

ALL REPANCO COMPONENTS  
AVAILABLE  
TRANSISTOR HOLDERS 3 or 5 pin, 1/-  
ALL SENT POST FREE IN U.K. by

## PETHERICK'S RADIO SUPPLIES

22 High Street, Bideford, N. Devon.  
Tel.: Bideford 1217

## RES/CAP. BRIDGE 39/6

Checks all types of resistors, condensers  
6 RANGES

Built in 1 hour. Direct reading  
READY CALIBRATED

Stamp for details of this and other kits.  
Please write to:

RADIO MAIL (Dept. PT)  
Raleigh Mews, Raleigh Street, Nottingham

## RADIO BOOKS

BASIC ELECTRICITY  
ELECTRONICS

HOW to Receive Foreign T.V. Pro-  
grammes With Simple Modifications 5/6  
TESTED SHORT WAVE RECEIVER  
CIRCUITS USING M.A.T.s 5/6  
TESTED SHORT WAVE SUPERHET  
RECEIVER CIRCUITS USING M.A.T.s 5/6

22 TESTED Circuits using M.A.T.s  
AT A GLANCE Valve and T.V.  
TUBE equivalents 4/-

BRITISH Transistor Directory 4/-  
OSCILLOSCOPE Book 5/6  
USING an Oscilloscope 7/-

OSCILLOSCOPE Equipment 5/6  
MULLARD Transistor Radios 5/6  
MULLARD Ref. Transistor Circuits 13/6

EXTRA Equipment Tape Recorder 6/6  
COIL Design and Construction 5/6  
TRANSISTOR Audio Amplifiers 6/6

TRANSISTOR Circuits for Radio  
Control of Models 8/-

RADIO Servicing Instruments 5/6  
BOYS Book of Crystal Sets 3/-

SERVICING Transistor Receivers 8/-  
ELECTRONIC Novelties 5/6  
ELECTRONIC Gadgets 5/-

RADIO Valve Data "Wireless World" 7/-  
BEGINNER'S Guide to Radio 8/6  
MODERN Transistor Circuits for Beginners 8/-

TRANSISTOR Test Equipment 4/-  
TRANSISTOR Circuits for the Con-  
structor (Bradley) Nos. 1, 2, 3 and 44/- each

All books include postage. List S.A.E.

## SELRAY BOOK CO.

60 HAYES HILL, HAYES, BROMLEY  
KENT. Tel. HURSTWAY 1818

## Lyons Radio Ltd.

3 Goldhawk Road, London W.12

SIGNAL INJECTOR (Model IT-1). Ideal  
instrument for rapid fault-finding in trans-  
istor, valve and TV receivers, etc. Consists  
of a transistor oscillator functioning as a  
modulated wide band signal generator.  
Simple to use. Powered by 4-pen-lite cells  
(Life—several hundred hours). Approx.  
5 x 2 ins. with plug-in probe. Complete with  
batteries and instructions. PRICE ONLY  
39/6, post free.

AIR CUSHION PHONE. Listen in com-  
fort and privacy to your transistor radio  
with our inflatable air cushion fitted with  
miniature loudspeaker. 3 1/2 x 4 ins. folded.  
15 x 12 ins. inflated with 4ft. connecting flex  
and twin plug to fit all types of transistor  
radios. With free plastic pouch. PRICE  
ONLY 23/-, post paid.

GRANDEX 45 WATT HIGH QUALITY  
AMPLIFIER. For 220/240V. A.C. mains or  
6V. car battery. Valve line-up 6SL7 6SK7.  
6V6 6X5. Separate gram and mike inputs.  
Heavy duty output transformer for 3, 4 and  
15 ohm impedance. Fully enclosed in metal  
case 9 x 8 x 6 ins. (slightly storage soiled).  
New and tested less vibrator (only required  
for 6V. input). Greatly reduced price, ONLY  
23/7.6, post 5/-. Vibrator II req'd. 7/6 extra.  
AUTO TRANSFORMERS. Input 200V.  
Output 230V. 275 Watts. Fully shrouded  
with fixing feet, overall size 4 x 3 1/2 x 3 ins.  
Manufacturers' surplus, brand new condi-  
tion. SNIP PRICE, ONLY 7/6, post 3/-.

## \* GIFT SUGGESTIONS \*

JUNIOR TAPE RECORDER with all  
accessories, ONLY £12.6, post 3/6.  
SENIOR TAPE RECORDER with all  
accessories, ONLY £12.6, post 3/6.  
TELEPHONE AMPLIFIER enables you  
to speak and listen without holding instru-  
ment, ONLY 63/-, post 2/-.  
PORTABLE ORGAN, battery operated  
24-note genuine musical instrument. Ideal  
for children and their elders. ONLY 69/6.  
Batteries 2/8, post 3/6.  
Illustrated leaflets available. S.A.E. please.

## Football Pool Computer

A Novel Circuit which is cheap to build.  
Forecasting made easy!

ANALOGUE COMPUTER  
Multiplies and Divides by electrical ana-  
logue methods. Exceedingly simple circuit.  
Fascinating demonstration of computer  
principles.

Both above circuits for 3/6, post free.  
Noughts and Crosses Machine  
Full circuit of our unbeaten machine. 3/6  
Post free.

PRICE GIFT to 10% of value of every multi-  
meter and multimeter kit bought in Decem-  
ber. Circuit of 18,000 o.p.v. kit at 85/-, and  
details of other multimeters from 35/- on  
request.

1% High Stab. Resistors. Brand new 1W 2%.  
Many special multimeter values. 100Ω, 1K,  
10K, 100K, 1% 1W. 1/6 each.

Precision Wirewound Resistors 1W.  
1Ω to 5K, 1%, 3/4% to 20K, 1%, 4/3, 1% add 3d.  
Your value wound to order.

## PLANET INSTRUMENT CO.,

25 DOMINION AVENUE, LEEDS 7

## 2 METRES 4

The thrills of VHF Amateur Radio  
can now be yours for as low as 39/6,  
complete kit, by post 2/6 extra.  
Tunable range 70-150 Mc/s. Write  
today for interesting literature, s.a.e.  
please. If a newcomer to Short Wave  
Radio, ask for free copy of world-  
famous "Globe-King" Short Wave  
Kits and other receivers. Stamp for  
post please, not s.a.e.

## JOHNSONS (Radio)

St. Martins Gate, Worcester

## JAG ELECTRONIC CABINET MAKERS LTD

No. 9 Workshop, Grayes Place,  
Slough, Bucks.

## CABINETS

We make a complete range  
of cabinets or will make to  
your own specification.

### GRAM CABINETS

For single player ..... 12  
For autochanger ..... 13  
P. & P. 5/- per cabinet

### SPEAKER CABINETS

With sloping fronts, all col-  
ours. 5in. 9/-, 6in. 10/6,  
8in. 15/-, 10in. 18/-, 12in. 25/-  
P. & P. up to 8in. 2/6, 10in. 3/-,  
12in. 3/6.

Trade enquiries invited for  
cabinets.

## LINE OUTPUT TRANSFORMERS AND SCAN COILS

FERGUSON: 204, 206, 306..... 17/6 ea.  
PYE: V4, V14, VT17..... 17/6 ea.  
EKCO: 221, 231..... 35/- ea.  
P. & P. 3/6 on each of above L.O.P.T.S.

## FIREBALL TURRET TUNERS

All ex-equipment .. 17/6 ea. P. & P. 3/-

AMPLIFIERS. Complete with output  
transformer and 6in. 3Ω speaker, mounted  
on board.

Type A using PCL82 & PY82, 39/6 c'plete.  
Type B using PL83, 12AU7, & PY82,  
45/6 c'plete.

Post 2/6 extra either type.

SPEAKERS, ex-equipment, 5in. 5/-,  
7 x 4in. 7/6, 8in. 7/6. P. & P. 2/- ea.

## CONTEMPORARY TABLES

With formica wood grain or patterned top  
and black legs with adjustable tennies.  
Size 24in. long and 12in. wide. Ideal for  
TV or coffee table 30/- ea. P. & P. 3/6

## VALVES

### SURPLUS or EX-EQUIPMENT

EB91	2/-	PCL82	4/6	6F1	3/-
EBF80	4/6	PCL83	5/-	6F12	2/-
EBF89	5/6	PCL84	6/6	6F13	5/-
ECH35	6/-	PL33	7/-	6F14	5/-
EC881	3/6	PL36	7/-	6F15	6/-
EC882	3/6	PL38	10/-	6L1	7/-
EC883	4/6	PL81	6/-	6L18	6/-
ECF80	4/6	PL82	4/6	6P25	5/-
ECF82	5/-	PL83	5/-	6P28	8/-
EC884	5/-	PY31	6/6	10F1	3/-
ECL80	4/6	PY32	7/6	10P13	6/6
ECL82	6/-	PY33	7/6	10P14	6/3
EF80	2/-	PY80	3/6	20D1	4/-
EF85	4/6	PY81	3/6	20F2	6/-
EF91	1/6	PY82	3/6	20L1	8/-
EL33	5/-	PY83	6/-	20P1	7/-
EL84	4/6	PT30	7/-	20P3	7/6
EY51	3/-	U24	6/-	20P4	12/-
EY86	4/6	U25	6/-	20P5	7/6
EZ80	4/6	U26	6/-	30P4	7/-
EZ81	4/6	U301	7/-	6C9	10/-
GZ32	5/-	U101	9/-	10C2	10/-
KT33C	4/-	U801	14/-	10C1	10/-
KT36	7/-	UB41	5/-	ECH42	6/-
PCC84	4/6	UCC84	7/6	UF42	2/6
PCF80	4/6	UCF80	7/6	UAF42	5/-

Many other types available Post 6d per valve.  
All enquiries S.A.E. please.

TERMS: C.W.O.

# NOW THREE LOW COST COURSES TO HELP YOU BECOME AN EXPERT IN RADIO, ELECTRONICS, OR TELEVISION

Our now famous Electronic Course won instant acclaim when offered just over one year ago.

NOW WE ARE PROUD TO BE ABLE TO OFFER TWO NEW COMPANION COURSES IN RADIO AND T.V. FOR THE SAME REASONABLE COST.

The lessons are crystal clear, practical, easy to master and use. Early lessons make fundamentals clear even to the beginner, while other lessons will give you the practical "know-how" of an expert.

These are real home-study courses that have been printed in large volume and bound into one giant 8 x 11 in. manual to reduce cost. Compare favourably with some courses costing ten times as much. By receiving all lessons at one time you save letter writing, additional postage, and other expenses.

Everyone can benefit from these practical courses. No old fashioned ideas used here. Just straightforward easy to understand explanations to help you get ahead in radio, electronics or television.

Modern wireless and t.v. sets use complex circuits, but their function is based on surprisingly few principles. These principles can easily be mastered when explained clearly. That is the object of these courses. Soon you will be well on your way to becoming a first-class radio, electronics, or t.v. technician.

More and more people are needed every day to repair wireless sets, amplifiers, VHF/FM radios, televisions and electronic equipment. Are YOU prepared to get your share of the money to be earned?

Just clip the coupon indicating the course required. You must be convinced that this is the best value you have ever seen in electronic, radio and t.v. training otherwise you can return the manual (or have your money refunded if sent with order) after you have examined it in your own home for a period of seven full days.

The price? Only 36/- per course, plus postage. YOU CAN QUALIFY FOR A CERTIFICATE. Details sent with each course ordered.

FREE DATA HANDBOOK WITH EVERY ORDER

## FREETRIALOFFER

TERMS ONLY 5/- PER WEEK!

To SIM-TECH TECHNICAL BOOKS, Dept. WA5, West End, Southampton, Hants.

Send ☐ ELECTRONICS COURSE

☐ RADIO COURSE

☐ TELEVISION COURSE

For a full seven days' free trial. If not delighted I may return the course post paid without further obligation on my part. Otherwise I will pay cash or 5/- weekly until 37/6, plus 2/6 service charge, total 40/- is paid.

☐ Tick here if enclosing full price (we pay postage). Same 7 day money-back guarantee. Postage charges 1/6 per course. Overseas customers please send full amount (including Ireland).

Name .....

Address .....

City .....

County .....

### STAR DXER S.R.-40 £24.15.0

General purpose superhet communications receiver for A.C. mains. 220-240 volts, covering 550 Kc/s to 30 Mc/s in four switching bands. Slide rule tuning dial, electrical bandspread, internal speaker, panel "S" meter, noise limiter, B.F.O., phone jack, Ferrite and whip aerials. Handsome grey crackle cabinet 13 1/2 x 8 1/2 x 5 1/2 in. Wt. 12 lbs. Full instruction manual. BRAND NEW CURRENT MODEL. 100% GUARANTEE. S.A.E. for full details. **100% SENIOR RECEIVERS.** Complete with 9 coils. £17.10.0, S.A.E. for full details. **POR-3 RECEIVERS.** 3-wave bands, medium wave and 2 short wave, from 120-13 metres. Good condition, tested, 8 gus. Carr. 10/- . A.C. mains internal power supply £2 extra.

**SILICON RECTIFIERS.** Type 1EA2 (4 x 1 in.) will handle 250 volts at up to 500 mA. Replaces any TV metal rectifier. 7/6. **AK-88 VIBRATOR PACKS.** For 6 v. operation. Complete with vibrator and OZ4 rectifier. BRAND NEW in original cartons. 17/6. P. & P. 6/-.

**MOVING COIL PHONES.** Finest quality Canadian with Chamols ear muffs and leather covered headband. With lead and jack plug. Noise excluding, supremely comfortable. BRAND NEW ..... £2/6 post 1/6.

**AVO WIDE RANGE SIGNAL GENERATORS.** Six turret operated ranges covering 50 Kc/s to 30 Mc/s. For use on standard A.C. mains. Packed in original transit cases with accessories. Post-war type in new condition. £15. Carriage 10/- . REAL BARGAIN.

**RECEPTION SETS R220/R230.** Consists of TWO identical receivers in one cabinet. Each receiver is complete with 14 modern miniature valves (3 x 6AK5, EF91, 3 x EF92, 2 x EB91, 2 x 12AT7, QST07/20, EL91 and 5U4G) its own stabilised AC mains power supply and speaker. Intended for reception of one fixed frequency between 90-100 Mc/s according to crystal used, but ideal for modification to 72 Mc/s or 144 Mc/s. Complete £17.10.0 (Carr. £1) or individual receivers (less cabinet) £3.19.6 (Carr. 7/6). Circuit supplied.

**MULLARD CRYSTAL CALIBRATOR.** In neat grey metal case 9 x 7 x 6 1/2 in. Gives 1 Mc/s, 100 Kc/s, and 10 Kc/s, marker pips and harmonics as selected. Optional 400 c/s modulation. Complete 6 valves (174 (5), IR5 (1), and 1 Mc/s H7G glass crystal. Requires 60 v. h.t. and 1.5 v. l.t. In original transit case. BRAND NEW. £4.19.6, carr. 7/6.

**MICRO-AMMETER.** 0-500 uA. Made by R.C.A., Weston Westinghouse, and other famous American manufacturers. Circular 2 1/2 in. flush panel mounting. Dials are engraved 0-15, 0-600 volts. As used in the American version of the "19 SET". TESTED AND GUARANTEED 15/-.

**CHARLES BRITAIN (RADIO) LTD, 11 UPPER SAINT MARTINS LANE, LONDON W.C.2**  
TEMPLE Bar 0545 Shop hours 9-6 p.m. (9-1 p.m. Thursdays). Open all day Saturday

## PADGETTS RADIO STORES OLD TOWN HALL, KNOWLER HILL, LIVERSEDGE, YORKS.

Telephone: Cleckheaton 2866

**ARMY SET TYPE 19MK. III.** Complete with one 6K8, four 6K7, one 6BG and one 6V6 valves. The Receiver side of the set is complete in every way, including the 500 micro-amp meter. The valves and a few parts have been removed from the "B" set. Clean inside, soiled outer case. We are offering a first class receiver at the special price of 32/-, carriage 10/- . Grade II, 20/-, carriage 10/-.

**Remote Control Unit for 19 Set.** complete with Bell Morse Key, etc., 12/6, carriage 7/6; two for 20/-, carriage 10/-.

**Valves Removed from TV Sets.** Tested on a Mullard valve Tester, and are 100% as new. "Three months' unconditional guarantee. POST FREE.

ECL80	2/-	10C2	5/-	PL82	5/-
ECC82	3/-	10F1	1/-	PY80	5/-
EY51	2/6	10P13	5/-	PY81	4/-
EBF80	4/6	10P14	5/-	PY82	5/-
EB91	9/4	20D1	3/-	PZ80	4/-
EF91	9/4	20L1	5/-	PCF80	4/6
6SN7	2/6	20P4	8/6	PCC84	4/6
6F1	1/-	185BT	8/6	EZ50	1/6
6F13	2/-	U281	5/-	PL83	5/-
6F14	5/-	U282	5/-	PL33	4/-
6F15	5/-	U329	5/-	PL38	8/-
6LD220	5/-	KT36	5/-	B36	4/-
PCL82	5/-	PL81	5/-	N37	5/-

EF80 1/6 or 10/- per doz. Grade II, EF80 for test purposes, 4/- doz.

**New Valves Ex. Units. POST FREE.**  
6K7 1/6, doz. 12/-, 6K8 2/6, doz. 22/-, 6V6 2/6, doz. 22/-, 807 U.S.A. 6/-, P3250 (PX4) 5/-, AC2PEN (PEN A4) 2/6, 5U4 3/-, 6SN7 3/-, 6V6GT 4/6, EF91 1/9, EL91 1/9, 6P6 2/-, 5Z4 5/6, 5Y3 4/6, 6X5 4/6, EF50 1/-, 6/- doz. ARP12 1/6, 6 for 5/6, box of 50 19/-, 174. ARTP2 2/-, ART4 2/-, APP87 2/-, AR8 2/-.

**P.M. Speaker All Perfect. EX. TV Sets. POST FREE BARGAINS.** All 3 ohms. Rola 6 x 4 in., 5/-; Goodmans 7 x 4 in., 7/-; R. and A. 7 x 4 in., 6/-; Philips 5 in. round, 6/8; R. and A. 6 in. round, 5/-; 10 in. round, 12/6; 12 in. round with Tweeter, new, 28/6. Special price for more than one speaker.

**New Boxed 12 volt Vibrator Packs.** with spare vibrator. Type P.C.R.. 250 volts at 150 mA. 18/-, Carriage 7/6.

**13 Channel 14 in. TV Sets.** Untested, 30/-, Carr. 10/- . 13 Channel 17 in. sets, untested, 50/-, Carr. 10/- . Well packed sent at owners' risk.

**TV Tubes.** completely rebuilt and refaced. 12 months' guarantee. Sizes up to 17 inch. Special trade price of 75/- . Carriage and Insurance 7/6.

**Reclaimed Tubes.** 14 in., 30/- . Carr. 7/6. 6 months' guarantee.

## BBC · ITV · F.M. AERIALS



**B.B.C. (BAND 1).** Telescopic loft, 21/- . External S/D 30/-.

**ITV. (BAND 3).** 3 Element loft array, 25/- . 5 Element, 35/- . Wall mounting, 3 Element, 35/- . 5 Element, 45/-.

**COMBINED B.B.C./ITV.** Loft 1+3, 41/3; 1+5, 48/9; Wall mounting 1+3, 56/3; 1+5, 63/9; Chimney 1+3, 63/8; 1+5, 71/3.

**F.M. (BAND 2).** Loft S/D, 12/6; "H", 30/- . 3 Element, 52/6. External units available. Coax. cable 8d. yd. Coax. plugs 1/3. C.W.O. or C.O.D. P.P. 3/- . Send 6d. stamps for illustrated lists.

Band IV 625 line Aerials also available.

**K.V.A. ELECTRONICS Dept. (P.W.)**  
3B Godstone Road, Kenley, Surrey. CR0 2527

An essential fact book...

## "Practical Wireless" Radio and Television Reference Data

Contains full details of colour codes; everyday formulae, for calculating the value of biasing components, potential divider, resonance, gain, etc.; aerial dimensions; a quick frequency-wavelength conversion table; stations and frequencies; common symbols and abbreviations; notes on amateur radio and a list of call-sign prefixes; communication receiver I.F.s; mathematical data including logarithm tables; wire and cable data; battery equivalents; valve, transistor and picture tube pin connections, bases, ratings and equivalents, including selected CV types. 96 pages, illustrated, over 62 pages of tables.

**10s. 6d. FROM ALL BOOKSELLERS**  
... or, in case of difficulty 11s. 6d. by post from  
**GEORGE NEWNES LTD., Tower House,  
Southampton Street, London, W.C.2.**

NEWNES



# R.S.T. VALVE MAIL ORDER CO.

Tel: MITcham 6202  
Open Daily to Callers  
Mon.—Sat. 9 a.m.—5.45 p.m.  
Wednesday 1 p.m.

211a STREATHAM ROAD, MITCHAM, SURREY.

All Valves Brand New and Fully Guaranteed — Obsolete valves a speciality.  
Quotations given on any type not listed. Send S.A.E.

## Special 24 Hour Express Mail Order Service

AC2/PEN 19/6	ECC85 7/6	EY83 12/6	PCC84 8/-	T41 15/-	UM80 10/6	6A8GT 13/6	6N7GT 9/6	12Q7GT 6/6
AC2/PEN DD 19/6	ECC88 12/6	EY86 7/-	PCC85 9/6	TDD4 12/6	URIC 15/-	6AC7 6/-	6P25 10/6	12SA7 8/6
AC/TP 29/-	ECC91 3/-	EY91 3/-	PCC88 12/6	TDD13C 17/6	UJ6 17/6	6AK5 5/-	6P28 12/6	12SJ7 8/-
AC/VPI-5-7	ECC82 8/6	EZ40 7/-	PCC89 8/6	TH41 20/-	UJ8 15/-	6AL5 5/-	6Q7 9/6	12SK7 6/-
AZ1 15/-	ECH35 10/-	EZ41 7/-	PCF80 9/-	TY86F 12/6	UJ9 7/6	6AM5 4/-	6Q7G 6/6	12SL7 8/-
AZ31 13/6	ECH21 21/-	EZ80 6/-	PCF84 12/6	U10 9/-	UY21 15/6	6AM6 4/-	6Q7GT 8/6	12SN7 10/-
B36 9/-	ECH42 9/6	EZ81 6/-	PCF86 12/6	U12 9/-	UY41 7/6	6AQ5 6/6	6SA7 7/6	12SQ7 12/-
CIC 10/-	ECH81 7/6	EZ90 4/6	PCL82 9/-	U14 9/-	UY85 6/6	6AT6 6/-	6SC7 8/6	14H7 10/-
CCH35 20/-	ECC80 7/6	E1148 2/6	PCL83 10/-	U22 8/-	VP4 15/-	6AU6 9/-	6SF5 10/-	14R7 10/-
CL33 12/6	ECC83 10/-	FC2 15/-	PCL84 7/-	U24 21/-	VP4A 15/-	6B8G 3/-	6SG7 7/6	19AQ5 8/-
CY1 15/-	ECL82 9/6	FW4/500 9/-	PCL85 9/-	U25 11/-	VP4B 15/-	6BA6 6/-	6SH7 6/-	19BG6 15/-
CY31 12/6	ECL83 10/6	FW4/800 9/-	PCL86 12/6	U26 10/-	VR105/307/1 9/-	6BE6 6/-	6S17 6/6	20D1 10/-
D77 4/-	ECL86 9/6	GZ30 10/6	PEN4A 19/6	U31 9/-	VR150/311/1 11/-	6BG6G 15/-	6SK7 5/6	20D2 21/-
DAC32 9/6	EF6 21/-	GZ32 10/6	PEN4D 22/6	U35 17/6	W61 11/-	6B8 6/-	6SL7GT 6/-	20F2 17/6
DAF91 5/6	EF9 21/-	GZ33 19/3	PEN4VA 17/6	U47 11/-	W6 5/-	6BQ7A 12/6	6SN7GT 5/6	20L1 22/6
DAF96 7/6	EF22 14/-	GZ34 13/6	PEN36C 20/-	U50 7/-	W7 5/-	6BR7 10/6	6SQ7 8/6	20P1 15/-
DCC90 12/6	EF36 4/-	GZ37 19/3	PEN45 10/-	U52 4/-	W81 6/-	6BS7 12/6	6U4GT 10/-	20P3 24/-
DF33 9/6	EF37 8/-	HABCB80107/-	PEN45DD 25/-	U76 7/6	W81M 6/-	6BVW 6/-	6U5G 7/6	20P4 20/-
DF91 4/-	EF37A 8/-	HL41 8/-	PEN46 5/-	U78 4/6	X41 22/6	6BW7 8/-	6V6G 4/6	20P5 20/-
DF92 7/-	EF39 4/-	HL41DD 8/6	PEN43DD 20/-	U81 10/6	X61M 10/-	6C4 3/6	6V6GT 8/-	25A6 8/-
DF96 7/6	EF40 15/-	HL92 8/6	PENDD4020 20/-	U91 13/6	X65 12/6	6C5GT 8/-	6X4 4/6	25L6 8/-
DH63 6/-	EF41 8/-	HL133DD 9/6	PL33 15/-	U251 15/-	X76 12/6	6C6 6/6	6X5G 6/-	25S5 8/-
DH77 7/-	EF42 10/-	HN309 25/-	PL36 12/6	U281 15/-	X76M 12/6	6C9 12/6	6X5GT 8/6	25Y5G 8/-
DK32 11/-	EF50A 3/6	IW4/350 10/-	PL38 21/-	U282 19/6	X78 26/-	6CD6G 27/6	6/30L2 10/-	25Z4 7/6
DK91 6/-	EF50E 3/-	IW4/500 10/-	PL38 21/-	U301 18/6	X79 26/-	6CH6 10/-	7B5 12/6	25Z5 8/-
DK92 7/6	EF80 5/-	KT33C 8/-	PL38 21/-	U329 15/-	Y61 10/-	6CW4 16/-	7B7 8/6	25Z6 8/6
DK96 7/6	EF85 5/-	KT33C 8/-	PL38 21/-	U339 13/6	Y63 10/-	6D2 4/-	7C5 8/-	27SU 19/6
DL33 10/-	EF86 8/-	KT36 17/6	PL38 21/-	U403 10/-	Z66 10/-	6D6 5/6	7C6 8/6	30C1 9/-
DL91 8/-	EF91 4/-	KT61 9/6	PL38 21/-	U404 10/-	Z77 4/-	6E5 10/-	7D5 15/-	30C15 12/6
DL92 6/-	EF92 4/-	KT66 15/-	PL38 21/-	U404 10/-	Z77 4/-	6F1 10/6	7D6 15/-	30F5 10/-
DL93 7/-	EF95 5/-	KT76 10/-	PL38 21/-	U404 10/-	Z77 4/-	6F6 6/9	7D8 15/-	30FL1 10/6
DL94 7/6	EF98 10/-	KT81 8/-	PL38 21/-	U404 10/-	Z77 4/-	6F12 4/-	7H7 6/-	30L1 6/6
DL96 7/6	EF183 10/6	KTW61 8/-	PL38 21/-	U404 10/-	Z77 4/-	6F13 10/-	7H7 6/-	30L15 11/-
EAS0 2/-	EF184 10/6	L63 5/-	PL38 21/-	U404 10/-	Z77 4/-	6F14 10/-	7Y4 6/6	30P4 18/-
EAB80 5/6	EK32 8/6	LN152 8/-	PL38 21/-	U404 10/-	Z77 4/-	6F15 12/6	8D3 4/-	30P12 10/-
EAC91 4/-	EL3 21/6	LN309 11/6	PL38 21/-	U404 10/-	Z77 4/-	6F19 12/6	9BVW 12/6	30P16 9/-
EAF42 9/6	EL32 4/6	LM219 12/6	PL38 21/-	U404 10/-	Z77 4/-	6F23 10/6	10C1 12/6	30P19 17/6
EB44 2/6	EL33 10/-	MKT4 17/6	PL38 21/-	U404 10/-	Z77 4/-	6F25 16/6	10C2 12/6	30PL1 15/-
EB41 6/-	EL34 14/-	MS4B 17/6	PL38 21/-	U404 10/-	Z77 4/-	6F26 13/6	10F1 10/-	30PL13 12/6
EB91 4/-	EL35 10/-	MVS/PEN 17/6	PL38 21/-	U404 10/-	Z77 4/-	6F33 5/6	10F9 12/6	30PL14 16/6
EB93 21/-	EL37 17/6	MVS/PEN 17/6	PL38 21/-	U404 10/-	Z77 4/-	6H6 2/-	10LD11 15/-	35A5 15/-
EB93 4/6	EL38 17/6	MVS/PEN 17/6	PL38 21/-	U404 10/-	Z77 4/-	6H6 2/-	10P13 15/-	35L6GT 8/6
EB94 8/6	EL41 9/6	MU14 9/-	PL38 21/-	U404 10/-	Z77 4/-	6H6 2/-	10P14 19/-	35V4 7/6
EB98 10/-	EL42 9/6	MX40 15/-	PL38 21/-	U404 10/-	Z77 4/-	6H6 2/-	11D5 23/6	35Z3 15/-
EBF80 8/-	EL81 12/6	N18 8/-	PL38 21/-	U404 10/-	Z77 4/-	6H6 2/-	12A6 6/6	35Z4 7/6
EBF83 8/-	EL84 6/9	N37 14/-	PL38 21/-	U404 10/-	Z77 4/-	6H6 2/-	12AH8 9/-	35Z5 8/6
EBF89 8/-	EL85 10/6	N78 22/6	PL38 21/-	U404 10/-	Z77 4/-	6H6 2/-	12AT6 7/6	41STH 22/6
EBL1 21/-	EL90 8/6	N108 15/-	PL38 21/-	U404 10/-	Z77 4/-	6H6 2/-	12AT7 5/-	42 12/6
EBL21 21/-	EL91 4/-	N308 18/-	PL38 21/-	U404 10/-	Z77 4/-	6H6 2/-	12AU6 17/6	50C5 10/-
ECC35 8/-	EL95 10/6	N339 30/6	PL38 21/-	U404 10/-	Z77 4/-	6H6 2/-	12AX7 5/-	50CD6G 30/-
ECC40 15/-	EM80 8/6	N369 10/6	PL38 21/-	U404 10/-	Z77 4/-	6H6 2/-	12BA6 7/6	50L6 8/6
ECC81 5/-	EM81 8/6	OD3 5/-	PL38 21/-	U404 10/-	Z77 4/-	6H6 2/-	12BE6 7/6	75 8/6
ECC82 5/-	EM85 10/6	OZ4 5/-	PL38 21/-	U404 10/-	Z77 4/-	6H6 2/-	12BH7 10/-	78 7/6
ECC83 5/-	EY51 7/6	P2 10/-	PL38 21/-	U404 10/-	Z77 4/-	6H6 2/-	12IG7 8/6	85A2 12/6
ECC84 8/6	EY81 8/6	PABC80 13/-	PL38 21/-	U404 10/-	Z77 4/-	6H6 2/-	12K7GT 5/-	85BT 30/-
			PL38 21/-	U404 10/-	Z77 4/-	6H6 2/-	12K8GT 10/-	807A 7/6
			PL38 21/-	U404 10/-	Z77 4/-	6H6 2/-		807B 7/-

## COMPLETE VALVE LIST FREE WITH ORDER

### METAL RECTIFIERS

RM1 7/6	14A86	23/-	16RD 2-2-8-1	12/- (FC142)
RM2 8/-	14A97	26/-	16RE 2-1-8-1	10/- (FC150)
RM3 10/-	14A100	28/-	18RA 1-1-8-1	5/- (FC118)
RM4 17/6	14RA 1-2-8-2 21/-	(FC301)	18RA 1-1-16-1	7/- (FC116)
RM5 19/6	14RA 1-2-8-3 25/-	(FC31)	18RA 2N-1-8-1	12/-
	16RC 1-1-16-1	10/-	18RD 2-2-8-1	16/- (FC124)

TERMS OF BUSINESS C.W.O. or C.O.D.  
4/2 PACKING CHARGE ON ALL C.O.D.  
ORDERS. POSTAGE 6d. per VALVE

### BRAND NEW TRANSISTORS

OC44 5/-	OC74 6/-	OC81D 6/-
OC45 5/-	OC75 6/-	OC81m/pr. 16/-
OC71 5/-	OC77 6/-	OC82 8/-
OC72 6/-	OC81 6/-	OC82D 8/-

### SILICON RECTIFIERS

400 volts 350 mA ... 7/6 each

### SETS OF VALVES

IRS, IS5, IT4, 354, 3V4	...	Set of 4, 19/-
DAF91, DF91, DK91, DL92, DL94	...	Set of 4, 19/-
DAF96, DF96, DK96, DL96	...	Set of 4, 26/6

# NEW MINIATURE 'SCOPE

Features 2½ in. DG7/5 Tube. Level 2dB, 50 c/s to 2 Mc/s. 3½ Sec. to 80m Sec. Sweep. High sensitivity. Fully portable scopes. Ideal for all transistor and valve design or servicing. 24 volt operated.

MODEL  
CT84

£16-10-0

CARRIAGE 7/6

We can supply from stock most of the components and items specified on circuits published in this and other magazines and radio books. Let us quote for your circuit, first grade components at realistic prices.

## DEAC RECHARGEABLE BATTERIES

- (a) 18 volt 100mA/H 4 x 1 in. diameter. Brand new sleeved, 30%.
  - (b) As above but 150mA/H, 35%.
  - (c) 3.9 volt 450mA/H, 12%.
- All types easily split into any multiple of 1.2 volt. Brand new.



## MULTI-METERS

Multi-range test meters featuring easy to read scales and provided with full operating instructions, lead and batteries. Suitable for amateur, designers, repair shops, all domestic uses. Full details and specifications in our catalogue.

- ★ PT34 1 Kohm/volt ..... £2 5 0
- ★ M1 2 " " ..... £2 9 6
- ★ TH133 2 " " (illus.) ..... £3 15 0
- ★ EP10K 10 " " ..... £4 9 6
- ★ IT1-2 20 " " ..... £5 5 0
- ★ TP55 20 " " ..... £5 19 6
- ★ EP30K 20 " " ..... £6 19 6
- ★ 500 30 " " ..... £8 19 6
- ★ EP50K 50 " " ..... £9 19 6

## SUBSTITUTION BOXES

- Capacitor Box. Provides 9 standard values from 0.001 to 0.22 mfd at 600 volt working, 29/6.
- Resistor Box. Provides 24 standard values at 1 watt. 15 ohms to 10 meg., 37/6.

Each box fully calibrated with insulated leads. Invaluable for service and design.

## NOMBREX TEST EQUIPMENT



All transistor portable units supplied with full instructions.

LEAFLETS  
ON  
REQUEST

- ★ 150 Kc/s to 350 Mc/s generator. RF, Mod., AF. 8 ranges. Leads, batt., instructions. £7.18.6, P.P. 2/6.
- ★ Resistance/Capacitance Bridge. 1 pF to 100mF and 1 ohm to 100meg. leakage. PF Tests, with batt. and instructions, £7.2.3. P.P. 2/6.
- ★ Power Supply. Gives any voltage 1 to 15 D.C. up to 0.1 amp. From Mains. £5.17.6. P.P. 2/6.
- ★ Audio Generator, 10 c/s to 100,000 c/s. Sine and square wave. With batt. and instructions. £15.2.3. P.P. 2/6.

## 4-WAVEBAND COMMUNICATIONS RECEIVER

- 550 kc/s to 30 Mc/s—BFO—AVC—Noise Limiter—Bandspread—"S" Meter—Telescopic Aerial—Full World Wide Coverage. 4 valve. PRICE £24.15.0. P.P. 10/-.
  - 9 valve version of above, 40 gns., P.P. 15/-.
- Details on request.

## 100 Kc/s QUARTZ CRYSTALS

- 2 Pin: Octal or 3 Pin.....15/- ea.
  - 500 Kc/s (AR88).....12/6
  - 455 Kc/s (AR88).....12/6
  - 456 Kc/s HRO.....15/-
  - 5000 Kc/s 2 Pin.....10/-
  - 10 Mc/s 2 Pin.....15/-
  - 27 Mc/s Radio Control.....15/-
- (Over 600 Frequencies in Stock for all purposes).

## MAINS AND BATTERY RECORD AND TAPE DECKS

- ★ BSR UA14 4-speed ..... £5 19 6
- ★ Garrard Autoslim ..... £6 10 0
- ★ Unpluggable Head Version ..... £7 10 0
- ★ SRP10 4-speed or GU786R ..... £5 7 6
- ★ Garrard AT6 with Stereo Cartridge ..... £10 19 6
- ★ Collaro, 2-track Deck Studio ..... £10 10 0
- ★ 4-track Deck ..... £13 19 6
- ★ P. & P. 5/- any type above.
- ★ 9 volt Star, 45 r.p.m. ....39/6
- ★ 45 or 33 r.p.m. Star, 9V.....92/6
- ★ 45 r.p.m. Garrard, 6V.....35/-
- ★ 4-speed B.S.R., 9V.....5 gns.
- ★ Garrard 9V. 2-speed, 2-track Tape Deck ..... £12 15 0
- ★ P. & P. 3/6 any of above.

## STEREO AMPLIFIERS



- Complete with full function pre-amplifiers and controls.
- ★ SA80 4 x 4 watts ..... £9 10 0
  - ★ SA150 7 x 7 watts ..... £16 10 0
  - ★ SA300 15 x 15 watts ..... £32 10 0
- Each amplifier completely self contained and designed for Mono and Stereo output. Supplied complete with full manual. Leaflets on any type on request. (Full range of Speakers, Tweeters and Decks in stock, see catalogue).

## CRYSTAL MICROPHONES

P. & P. 1/6. Any type.

- Acos 39-1 Stick Microphone ..... 32/6
- Acos 40 Desk Microphone ..... 15/-
- Acos 45 Hand Microphone ..... 25/-
- Lapel/Hand Microphone ..... 12/6
- MC24 Stick Microphone ..... 25/-
- 100C Stick with Stand ..... 39/6
- BM3 Stick with Stand ..... 52/6
- Lapel/Hand Magnetic ..... 12/6

## MINIATURE PANEL METERS

- \*0.50uA (D.C.) 39/6 \*0.5mA (D.C.) 27/6
- \*0.500uA (D.C.) 32/6 \*0.300V (D.C.) 27/6
- \*0.1mA (D.C.) 27/6 "S" Meter 35/-
- All Brand New Boxed. \*Available Clear Plastic Front or Black Moulded.
- 200uA D.C. Edge meter ..... 69/6
- 1mA D.C. Edge meter..... 59/6
- 3½ x 1 inch Front Panel.

## HI-FI SPEAKERS

- CX300 12 inch 25 watt ... 12 Gns.
  - CR12AE 12 inch 20 watt ... 8 Gns.
  - CR30AE 12 inch 20 watt ... 10 Gns.
  - triple range ... 79/6
  - BA7 8 inch 6 watt ... 29/6
  - 10 watt Horn Tweeter ... 29/6
- P.P. 1/6.

**POCKET SOLDERING IRON.** 30 watts. 220/250 volts A.C. Complete with pointed bit, mains plug, carry pouch. 14/6. P.P. 1/6.

## BUILD A QUALITY TAPE RECORDER.

- ★ Printed circuit. Record/playback 2 Track, 11 gns.
  - Amplifier Kits. 4 Track, 12 gns.
  - ★ Studio Deck. 2 Track, £10.19.6
  - 3 speed. 4 Track, £13.19.6
  - ★ Cabinet with Speaker 5 gns.
- Leaflet on Request.

Crystal Contact Microphone 12/6 P.P. 9d.  
2K, ½-track Tape Head.....15/-, P.P. 9d.  
Telephone Recording Attachment .....12/6 P.P. 9d.  
4-channel Transistor Mixer Unit.....59/6 P.P. 1/6  
Tape Jack Radio Tuner .....29/-, P.P. 1/-

**TEST LEAD KIT** supplied in Pocket Pouch. Contains probes, leads, clips, etc. 8/6. P.P. 9d.

## BOAC VHF POCKET RECEIVERS

● Complete units with CS 5A VHF Detector, S-V6/8R (OC44) Transistors, 3.9V. 450mA rechargeable Deac battery 2—OA91, OA 10 rectifiers, 1K ohm stethoscope headset, moulded casing, etc.

- Complete Unit 35/- P.P. 2/-
- with Full Circuit OR DEAC BATTERY OR HEADSET 12/6, P.P. 1/6. 15/- P.P. 1/-.
- Unit less DEAC & HEADSET 12/6, P.P. 1/6.

## FIELD STRENGTH METER

Five channels cover 1 Mc/s to 200 Mc/s. Fitted 200 microamp meter for CW or R.F. Indication and Earphone for A.F. Monitoring. Designed for checking all types of transmitters. Size 4 x 2½ in. Complete. Ready to Use, with instruction and telescopic aerial, 69/6. Post Free.

## RUN YOUR RADIO OR AMPLIFIER FROM MAINS BATTERY ELIMINATORS AND CHARGERS

1. For PP3 or equivalent 9 volt Pocket Radio Battery, 18/6. P.P. 1/-.
2. For PP4, PP7, PP9, 9 volt Portable Radio and Equipment. Supplies up to 300mA, 49/6. P.P. 2/-.
3. De Luxe version of No.1 also charges PP3 type batteries. 24/-, P.P. 1/-.

## TYPE 38, TRANSMITTER RECEIVER

Complete with 5 valves. In new condition. These sets are sold without guarantee but are serviceable. 22/6 P.P. 7.4 to 9 Mc/s. 2/6

Headphones 7/6 pair. Junction Box 2/6  
Throat Mike 4/6. Aerial Rod 2/6

**Henry's Radio Ltd**

PAddington 1008/9

303 EDGWARE RD., LONDON W.2

Open Monday to Sat. 9-6. Thurs. 1 o'clock.

PLEASE TURN TO BACK PAGE

# Practical Wireless

## BLUEPRINT SERVICE

ALL of these blueprints are drawn full-size and although the issues containing descriptions of these sets are now out of print, constructional details are available free with each blueprint except for those marked thus (\*).

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, London W.C.2.

### DOUBLE-SIDED BLUEPRINTS

Each blueprint in this series contains details of two separate instruments or items of equipment.

The Strand Amplifier ...	...	...	*	5/-
The PW Signal Generator ...	...	...		
The Savoy VHF Tuner ...	...	...	*	5/-
The Mayfair Pre-amplifier ...	...	...		
The Berkeley Loudspeaker Enclosure ...	...	...	*	5/-
The Luxembourg Tuner ...	...	...		
The PW Troubadour ...	...	...		7/6
The PW Everest Tuner ...	...	...		
The PW Britannic Two ...	...	...	*	6/-
The PW Mercury Six ...	...	...		
The PW Regency ...	...	...	*	5/-
The PW International Short Wave Two ...	...	...		

### RECEIVERS

The Tutor *	...	...	...	3/-
The Citizen *	...	...	...	5/-
Junior Crystal Set	...	...	PW94	2/-
Dual-wave Crystal Diode	...	...	PW95	2/6
Modern One-valver	...	...	PW96	2/6
All-dry Three	...	...	PW97	3/6
Modern Two-valver	...	...	PW98	3/6
A.C. Band-pass Three	...	...	PW99	4/-
A.C. Coronet-4	...	...	PW100	4/-
A.C. D.C. Coronet	...	...	PW101	4/-
The PW Pocket Superhet	...	...	...	5/-

### MISCELLANEOUS

The PW 3-speed Autogram ...	...	8/-
The PW Monophonic Electric Organ ...	...	8/-
The PW Roadfarer * ...	...	5/-
The PT Band III TV converter ...	...	1/6
The Mini-amp * ...	...	5/-
The PT Olympic * ...	...	7/6
The PT Multimeter * ...	...	5/-

### SOME EARLIER DESIGNS

THE following blueprints include some pre-war designs and are kept in circulation for those constructors who wish to make use of old components which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.

Experimenter's Short Wave ...	PW30a	2/6
Midget Short Wave Two ...	PW38a	2/6
Simple S.W. One-valver ...	PW88	2/6
Pyramid One-valver ...	PW93	2/6
BBC Special One-valver ...	AW387	2/6
A One-valver for America ...	AW429	2/6
Short-Wave World Beater ...	AW436	3/6
Standard Four Valve S.W. ...	WM383	3/6
Enthusiast's Power Amplifier ...	WM387	3/6
Standard Four Valve ...	WM391	3/6
Listener's 5-Watt Amplifier ...	WM392	3/6

### QUERY COUPON

This coupon is available until 7th January, 1964, and must accompany all queries in accordance with the notice on our "Letters to the Editor" page.

PRACTICAL WIRELESS, JANUARY, 1964.

## COMPONENTS EQUIPMENT HI-FI

SEE OUR LATEST 10 x 7½ in. FULLY DETAILED AND ILLUSTRATED CATALOGUE, TRANSISTORS, COMPONENTS, VALVES, CRYSTALS AND HI-FI EQUIPMENT. NOW INCLUDES 8 PAGE SUPPLEMENT

# 2/-

POST FREE

## MINIGRAM TRANSISTOR PORTABLE RECORD PLAYER



### "THE CONESSA"


★ **COMBINED PORTABLE AND CAR RADIO** ★  
★ **AMAZING SENSITIVITY AND SELECTIVITY ON MEDIUM AND LONG WAVEBANDS** ★  
★ The easiest Superhet Radio to build on the market. Features clearly-marked printed circuit and packaged components with full illustrated building instructions. Full tuning of medium and long wave bands with unbeatable sensitivity and selectivity. Excellent tone and volume with over 600mV push-pull output.

★ Clearly marked horizontal station dial with slow motion tuning. Two colour Blue or Beige cabinets with Gold handles, grilles and fittings. Size 10½ x 7½ x 3½ in., includes car aerial sockets, recording sockets.

★ 6 Mullard Transistors and 2 Diodes.

**UNBEATABLE FOR QUALITY AND VALUE**
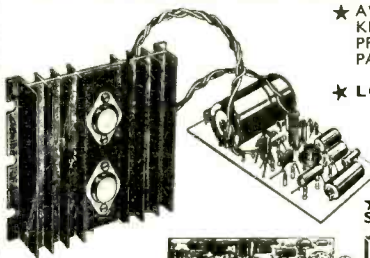
### 10 WATT TRANSISTOR HI-FI AMPLIFIER AND PREAMPLIFIER



★ **AVAILABLE IN KIT FORM OR PREBUILT PANELS**

★ **LOW NOISE**


★ **LOW POWER REQUIREMENTS**

★ **MONO OR STEREO**

Circuits and details **FREE** on Request

★ **CALL FOR DEMONSTRATION—ANY TIME** ★
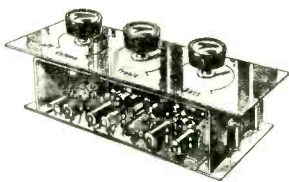
### 7-TRANSISTOR RECORD PLAYER/RADIOGRAM AMPLIFIER



- 4 watt peak output.
- Full Treble and Bass boost and cut.
- 40 c/s to 20 kc/s  $\pm 3$ dB.
- Inputs for Pick-ups, Radio Tuners, Microphones, mixers.

**BOOKLET FREE ON REQUEST**

### TWO VERSIONS AVAILABLE

- 12 18 volt for 15 ohm speakers. (mains unit 80/- extra).
- 9/12 volt for 3 ohm speakers (mains unit 49/6 extra).
- Size only 6 x 2½ x 2in.
- Ideal for mains or battery, portable or domestic record player, grams, etc. Or car.

Built Ready To Use **£5.19.6** P.P. 2/-.

### CHRISTMAS BARGAINS

Ready to use Radios complete with battery, leather case, Earphone.


- 6-Transistor MW, 79/6, P.P. 2/-.
- 7-Transistor version, 89/6, P.P. 2/-.
- 6-Transistor De-Luxe version, 85/-, P.P. 2/-.
- 6-Transistor MW and LW version, £5.19.6, P.P. 2/-.
- 7-Transistor MW/LW/SW, £13.19.6, P.P. 5/-.
- Two track "Minty" tape recorder (see Dec. advert), £7.15.0, P.P. 3/6.

**ALL FULLY GUARANTEED**

**TO BUILD YOURSELF**

- Mini Ranger Personal Radio, 49/6, P.P. 1/6
- Ranger-3, Personal Radio, 49/6, P.P. 1/6
- Sinclair Slimline, Personal Radio, 49/6, P.P. 1/6
- Quintet M/LW-5 ... 79/6, P.P. 2/-
- PW-6 Superhet ... £7 19 6
- PW Celeste ... £9 19 6
- PW Spinette ... £10 19 6
- PW Shortwave 2 ... 99/6 P.P. 2/6

Leaflet and details on request.

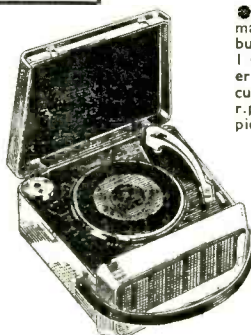

● Made by well known British manufacturer. Features ready built 4-transistor printed circuit 1 watt amplifier, elliptical speaker and volume control. Low current Star, constant speed 45 r.p.m. turntable with crystal pick-up. Strong moulded two colour cabinet with handle. Plays anywhere on long life 9 volt battery. Requires less than half an hour's work to connect up using ready built units and easy instructions.

**TOTAL 79/6** P.P. 5/-.  
**COST (BATTERY 3/9 EXTRA)**  
**ALL UNITS SOLD SEPARATELY**

★ **READY BUILT AMPLIFIER WITH SPEAKER AND VOLUME CONTROL 35/-** P.P. 2/-.

★ **TURNTABLE WITH PICKUP. 39/6** P.P. 2/6.

★ **2 TONE CASE WITH HANDLE. 5/-** P.P. 1/-.

● **EXCELLENT QUALITY AND VALUE** ●

PERFORMANCE EQUIVALENT TO VALVE AMPLIFIERS OF FOUR TIMES THE PRICE AND MANY TIMES THE SIZE.

★ Power output 10 watts at 400 c/s. Second harmonic distortion 0.1%. Total harmonic distortion 0.25% at 10 watts. Signal to noise ratio at 10 watts 70 dB. Overall response within 3 dB 40 c/s to 20 kc/s.


★ 6-Transistor 10 watt power amplifier. 0.25 ohm output impedance for 3 ohms. 24 volt supply, 300mA average for 10 watts. 100mV into 33 k.ohm sensitivity. 1 dB, 40 c/s to 20 kc/s.

Built £5.19.6 P.P. 2/6 or Kit £5.15.6 P.P. 2/6. (Mains Unit £3.9.6 P.P. 2/6).

★ As above but 10 watts for 15 ohms speakers. 40 volt supply, 150mA average for 10 watts. 1 dB, 40 c/s to 20 kc/s. Built £6.5.0 P.P. 2/6. Or Kit £6.6 P.P. 2/6. (Mains Unit £3.9.6 P.P. 2/6).

★ Full function pre-amplifier and control unit on printed circuit. Size 9 x 2½ in. Features 6 position input selector for microphones, tuners, tape, pick-ups—treble and bass controls + 12dB at 50 c/s and 12 kc/s—14dB at 50 c/s and 12 kc/s. Four-position filter and volume controls. 1.5mV input sensitivity. Front panel 8/6 extra. Built £5.10.0 P.P. 2/- Or Kit 99/6 P.P. 2/-.
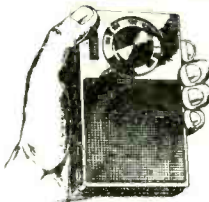
### "CAPRI" POCKET RADIO 6-TRANSISTOR SUPERHET



The most compact 6-transistor and diode radio with speaker available to the home constructor. Features the latest in miniature components and circuitry. Supplied with Mullard transistors and two-tone moulded cabinets in red-white or blue-white with gold fittings. All components are supplied in packets and clearly identified. A printed circuit is used with

Size only 4½ x 2½ x 1½ in.  
**REALLY POCKET SIZE!**

fully illustrated building instructions. Push-pull output coupled with a sensitive and selective circuit make the "CAPRI" hard to beat. Fitted Earphone/Record Socket. Full tuning on medium waves with long wave Light. All parts sold separately.

**TOTAL COST 79/6** P.P. 2/-.  
**OF ALL PARTS**  
(Battery 2/6 extra. Earphone 6/6 extra).  
Illustrated leaflet on request.

### Henry's Radio Ltd.

303 EDGWARE ROAD, LONDON, W.2

PADDINGTON 1009/9

Open Monday to Sat. 9-6. Thurs. 1 o'clock.