

PRACTICAL WIRELESS

APRIL
1967

216

FREE INSIDE

33 $\frac{1}{3}$ R.P.M.

RECORD


10

OF
FAULT
FINDING
EFFECTS

START OF NEW SERVICING SERIES




MULTIBAND TRANSISTOR SUPERHET

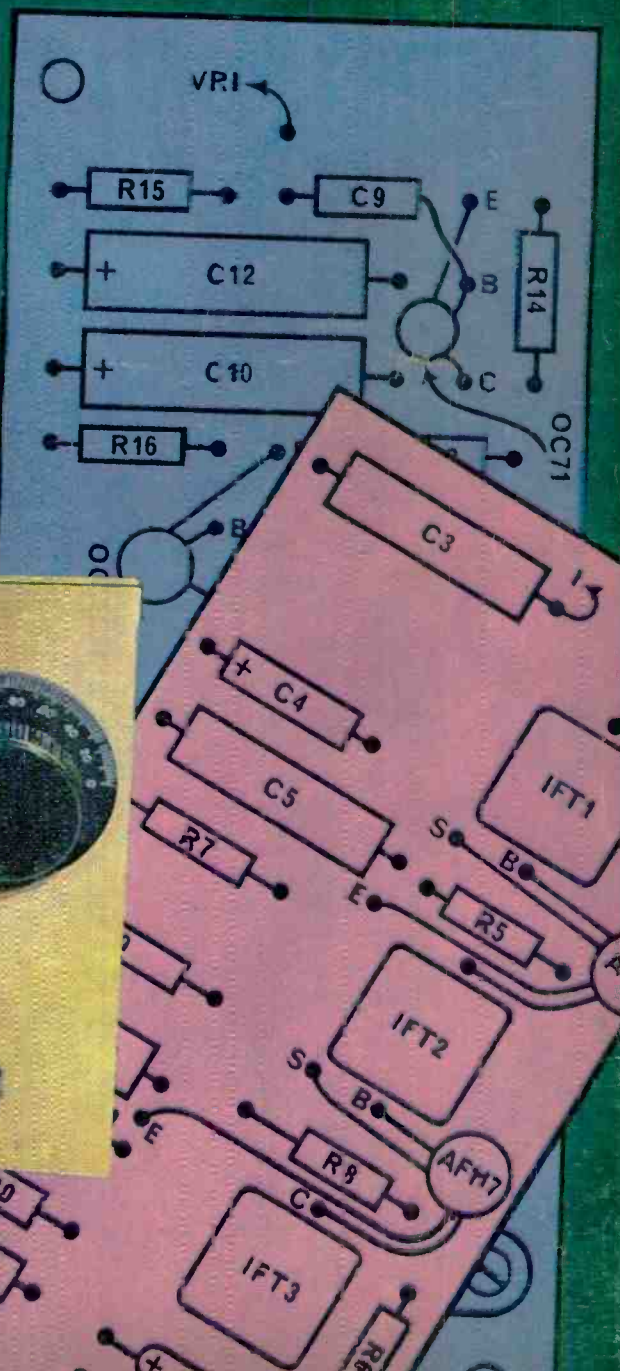



SOLDERING INSTRUMENTS AND EQUIPMENT

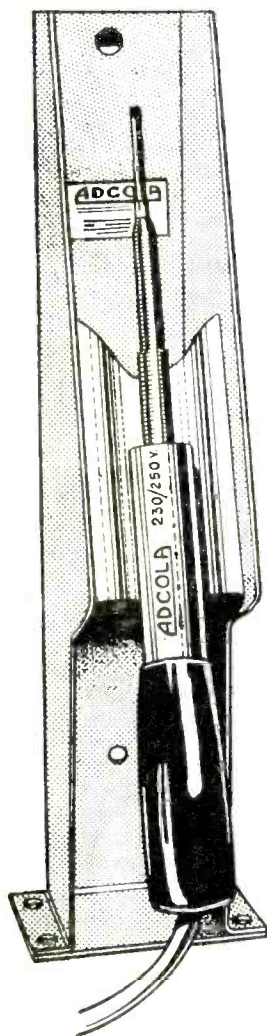

DESIGNED FOR
THE AMATEUR'S
RADIO STATION

ILLUSTRATED
List No. 70 $\frac{1}{8}$ " BIT
IN
PROTECTIVE
SHIELD
List No. 68

for catalogue apply direct to:—
Sales and Service Dept.
ADCOLA PRODUCTS LTD.,
ADCOLA HOUSE,
GAUDEN ROAD,
LONDON, S.W.4


Telephones Telegrams
MACaulay 0291/3 SOLJOINT LONDON SW4

JACKSON

the big name in PRECISION components
MINIATURE TUNING CAPACITORS

The Jackson 'O' range contains six basic types of different air-dielectric tuning capacitors with a wide variation of capacities available in each type. In addition, there are optional extras such as concentric-spindle slow-motion drives, built-in trimmers and plastic covers. The maximum capacitance per section ranges from 12, 18 or 24 pF for FM types to 420 pF for AM types.

TYPE "OO"

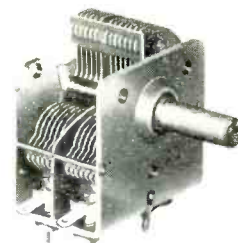

- ★ Type OO miniature twin capacitor at 12/6 each
- ★ Type OFM two-gang for FM at 12/9 each
- ★ Type O two-gang for AM at 12/9 each

Write for literature

JACKSON BROS. (LONDON) LTD. (Dept. P.W.)
KINGSWAY-WADDON, CROYDON, CR9 4DG
Phone Croydon 2754-5 (01-688) Grams: Walfilco, Croydon

NOMBREX INSTRUMENTATION

WIDE RANGE TRANSISTORISED SIGNAL GENERATOR MODEL 27



- ★ Range 150Kc/s-350Mc/s
- ★ Direct Calibration
- ★ Mod. or Unmod. output
- ★ Accuracy better than 2%
£10.16.9.

ALSO AVAILABLE

C. R. Bridge 62	..	£9.6.9
Inductance Bridge 66	..	£18.6.9
Power Supply Unit 61	..	£6.14.6

WIDE RANGE TRANSISTORISED AUDIO GENERATOR 63

- ★ Range 10c/s-100Kc/s
- ★ Sine or Square Wave
- ★ Accuracy & Low Dist.
- ★ Calibrated Output
£17.1.9



All prices include battery, post and packing

S.A.E. for Leaflet	Trade & Export Enquiries Invited	Prompt Delivery
-----------------------	-------------------------------------	--------------------

NOMBREX LTD INSTRUMENTS
DIVISION

Estuary House, Camperdown Ter., Exmouth, Devon

JASON

★ TAPE ★

We offer you fully tensilised polyester/mylar and P.V.O. tapes of identical quality hi-fi wide range recording characteristics as top grade tapes. Quality control manufacture. They are truly worth a few more coppers than acetate, sub-standard, jointed or cheap imports. TRY ONE AND PROVE IT YOURSELF.

Standard Play	Long Play
3in. 150ft. 2/3	3in. 225ft. 2/9
4in. 300ft. 4/8	4in. 450ft. 5/6
5in. 600ft. 7/8	5in. 900ft. 10/6
5 1/2in. 900ft. 10/8	6 1/2in. 1,200ft. 13/-
7in. 1,200ft. 12/6	7in. 1,800ft. 18/6
Double Play	Triple Play
3in. 300ft. 4/-	4in. 900ft. 13/-
4in. 600ft. 8/-	5in. 1,800ft. 25/-
5in. 1,200ft. 15/-	5 1/2in. 2,400ft. 34/-
5 1/2in. 1,800ft. 19/8	7in. 3,600ft. 44/-
7in. 2,400ft. 27/-	Quadruple Play
	8in. 600ft. 8/6

Postage 1/- reel.
Post Free less 5% on three reels.

Quantity and Trade enquiries invited.

NOTE. Large tape stocks at all branches.

BARGAIN PARCELS

Including variable condensers, i.f. coils, loud-speaker plugs/sockets, knobs, pots, condensers, resistors, nuts, bolts, cabinet fittings, switches, transformer choke, rectifier, transistors at a small fraction of list value. Due to heavy demand we are now packing them in several sizes—TRY ONE.

3 lbs. (post 3/-)	9/-
7 lbs. (post 5/-)	17/6
14 lbs. (post 6/-)	29/-

AVOID AMPLITUDE DISTORTION WITH YOUR HI-FI AMP.

STABILISED TRANSISTOR POWER SUPPLY

- VARIABLE 0—15V. AT 0—1 AMP.
- STABILISED FOR MAINS VAR. 210 - 250V.
- RIPPLE CORRECTED
- SHORT CIRCUIT PROTECTION
- HANDSOME STYLED CABINET

★ PRICE ONLY 6GNS.

10 WATT TRANSISTOR AMP

Consisting above stabilised power pack (can be used separately), with built-in pre-amp and controls driving two x OC26 main amp. in styled cabinet. New concept in value and design. 10 transistors, selection, vol. and tone controls equalisation.


PRICE 12GNS.

ELPICO MONO PREAMPS

DPA15. Latest black/satin chrome finish multiple input channels selector bass and treble controls. Matches all pick-ups and mikes. Provision tape recording. 4 Gns. Normally 10 gns. our price

Transistorised FM Tuner

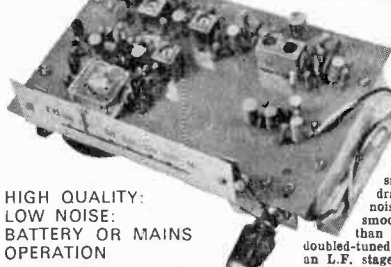CALLERS WELCOME Demonstration without obligation at all branches



HIGH QUALITY: LOW NOISE: BATTERY OR MAINS OPERATION

avoid disappointment

ORDER NOW £8-10

TRANSISTORS GUARANTEED TOP QUALITY

Mullard Matched Output Kits OC81D and 2-OC81 9/6
R.F. Kits OC44, OC45 (2) 3 transistors 9/6

GERMANIUM DIODES

General Purpose miniature detector A.V.C. etc. 6/6 doz. 8d.
Gold Bonded highest quality. Individually tested 9/6 doz. 1/-

SILICON H.T. RECTIFIERS

Guaranteed performance. Top makes. Tested 250v. working. 120 mA 2/9
(3 for 6/8) 7/6
500 mA
(3 for 19/6)

This beautifully compact 6 transistor machine (size 6 x 4 x 2 1/2 in.) will give quiet, more interference free reception. Months of use from a standard 9 volt battery or its small power requirements can be drawn from any amplifier. Low noise frequency changer with smooth 2 gang tuning feeding no less than three I.F. stages coupled to a double-tuned discriminator terminating in an L.F. stage giving ample output for all quality amplifiers.

LATEST GARRARD

All Factory Fresh. All with cartridge. EV26 Ceramic Stereo cartridge fitted to any deck for 15/- extra.

SRP12	£47.8
SP25	£89.10
AUTOSLIM	£56.10
Model 1,000	£56.50
Model 2,000	£56.10
Model 3,000	£56.10
AT60	£19.10
A70	£18.10
LAB80	£24.10
401	£28.10

B.S.R. BARGAINS

TU14	59/-
GU7	85/-
UA14	89/-
UA16	99/-
UA26 SUPERSLIM	£5.10

CARTRIDGES

G.C.E. Garrard Mono	16/-
EV26 Garrard Stereo Ceramic	24/-
EUPHONIC SUPER Ceramic Stereo Diamond 100mV Output	29/-

STEREO PORTABLE CABINETS

Latest black and silver metal finish. Consisting of centre cabinet size 16 1/2 in. x 13 in. x 8 in. deep with lift up lid together with two 10 x 6 speaker cabinets which clip on ends of main cabinet size 4 1/2 in. x 13 in. x 8 in. making overall size of 25 1/2 in. x 13 in. x 8 in. High quality chrome fittings. Will take almost any autochanger or tape deck. Approx. £3.19.0

Half price at

Ditto, but less chrome. £2.19.9

takes 7 x 4 speaker

MONO PORTABLE CABINETS.

B.S.R. tape deck or single record player, new, attractive 19/6

hush, half price.

AUTOCLEAN PORTABLE CABINETS.

As used on 18 gns. record player. Due to fortunate purchase we offer complete with motor 49/-

board and all fittings at only

PLEASE NOTE. A wide range of cabinets to callers at all branches.

100 HI-STABS 9/6

1% to 5% 100Ω to 5 MΩ.

CO-AX. low loss. 8d. yd. 25 yds. 11/6;

50 yds. 22/-; 100 yds. 42/6. Plugs 1/3.

100 RESISTORS 6/6

SIZES 1-3 watt.

MICROPHONE CABLE Highest quality. black, grey, white 9d. per yard.

100 CONDENSERS 9/6

Miniature Ceramic, Silver, Mica etc. 3p to 5p. LIST VALUE OVER £4.

25 ELECTROLYTICS

Assorted 2 to 500 mfd 6 to 400 volt. LIST VALUE OVER £5. 9/6

50 TAG STRIPS 7/6

Mixed sizes 2 to 15 way.

25 POTENTIOMETERS

Including with switch, long and short spindle, pre-set, log and lin. unused. 1k-2mΩ. LIST VALUE APPROX. £4. 9/6

CONNECTING WIRE

P.V.C. Bright Colours. Five 4/-

25ft. coils only.

CALLERS. A very wide range of electronic components available at all branches. Your enquiries welcomed.

Value in VALVES GUARANTEED 3 MONTHS BY RETURN OF POST

Satisfaction or Money Back Guarantee on goods if returned unused within 14 days.

ALL VALVES ARE NEW UNLESS OTHERWISE INFORMED FREE

TRANSIT INSURANCE. POSTAGE 1 valve 9d. 2-11 6d. per valve. Free over 12.

L14	2/3	6K8GT	9/6	20P4	17/9	ECC88	9/6	GZ34	10/6	SP61	2/9
1R5	4/9	6L1	9/6	25L6GT	7/-	ECC89	7/9	KT61	12/-	TTD4	7/-
1S4	4/9	6L6GT	9/6	25Z4G	7/-	ECC87	7/6	KT63	5/9	U14/18	7/6
1S5	4/6	6L8	7/9	30F5	9/-	ECC82	10/-	KT68	19/6	U25	9/6
1T4	3/-	6L20	8/6	30PL1	9/9	ECC85	11/-	KT88	27/6	U26	9/6
2D21	5/6	6P25	12/-	30L15	11/6	ECH42	10/6	KTW61	5/9	U35	12/6
3A5	6/-	6P28	9/6	30P4	11/6	ECH51	9/9	KTW63	5/-	U37	11/-
3Q4	5/3	6Q7G	7/-	30P12	9/-	ECH83	7/9	KTZ63	7/-	U107	12/6
5U4G	6/-	6Q7GT	8/9	30PL1	11/-	ECL80	5/9	MU14	7/-	U191	12/6
5Y3GT	8/6	6SL7GT	8/9	35A5	9/6	ECL82	7/6	N37	9/6	U281	9/6
5Z45	9/6	6SN7GT	8/9	35L6GT	8/6	ECL83	10/6	N78	13/-	U282	15/-
5Z4GT	9/6	6U6GT	9/6	35W4	6/6	ECL86	9/6	N108	13/-	U329	8/6
6/30L2	6/6	6V6G	4/9	35Z4GT	5/9	EP38	4/9	PC86	9/6	U801	19/-
6A8G	2/8	6V6GT	6/9	36L6GT	8/6	EP39	7/-	PC97	7/6	UABC80	6/6
6A55	4/9	6X4	4/6	80	7/6	EP40	10/-	PC84	8/6	UAF42	7/6
6AC5	3/-	6X5G	5/-	185BTA19/8	EP41	9/-	PC85	7/6	UB41	6/6	
6AT6	5/-	6X5GT	6/9	307	9/6	EP50	3/3	PC88	11/9	UB41	8/9
6BA6	5/6	7B8	11/6	955	3/6	EP80	4/3	PC89	11/-	UBC81	6/6
6BE6	5/6	7B7	7/6	956	3/-	EP85	6/3	PC189	9/6	UBF80	7/6
6BE6	6/6	7C5	9/6	AZ31	8/6	EP86	7/6	PCF80	6/9	UBF89	7/6
6B8	7/-	7C6	9/6	CB131	19/6	EP89	6/6	PCF82	8/9	UBL21	10/9
6BE7	9/6	7H7	7/6	DAF96	7/3	EP91	3/6	PCF86	8/3	UC92	6/6
6BW6	7/6	7S7	14/6	DF96	7/3	EP183	8/-	PC182	7/9	UCF85	7/3
6BW7	5/-	7Y4	7/-	DK92	8/6	EP184	8/-	PC183	9/6	UCF80	8/6
6C4	3/-	10C1	11/-	DL96	7/3	EL32	5/-	PC184	9/-	UCH21	10/9
6C5	5/6	10C2	12/6	DL92	6/-	EL33	12/-	PC185	9/6	UCH42	8/6
6C8	4/-	10F1	7/6	DL94	6/6	EL34	11/6	PC186	9/6	UCH81	7/6
6C9	11/-	10L11	14/6	DL96	7/3	EL35	8/-	PL13	8/6	UCL82	8/-
6CD6G	12/-	10P13	9/6	EAC830	6/9	EL38	15/-	PL36	11/-	UCL83	10/6
6D6	4/-	10P14	9/6	EAF42	8/-	EL41	9/6	PL38	12/6	UF41	9/-
6F1	8/6	12AT7	4/9	EB41	4/6	EL42	8/9	PL31	7/9	UF42	6/9
6F6G	5/-	12AU7	5/6	EB92	2/9	EL84	6/6	PL82	5/9	UF85	7/6
6F13	1/6	12AX7	6/-	EB93	7/6	EM80	7/-	PL83	6/-	UF89	6/9
6F14	7/6	12T6GT	9/-	EB941	9/6	EM81	7/6	PL84	7/-	UL11	10/-
6F15	9/6	12K7GT	5/-	EB991	6/9	EM84	7/9	PY31	7/6	UL14	14/-
6F23	8/-	12K8GT	6/6	EBF80	7/9	EY51	7/6	PY32	9/6	UL16	10/6
6F3G	4/-	12G7GT	6/6	EBP89	7/-	EY86	7/6	PY33	7/6	UL84	8/6
6F3GT	3/6	1457	14/6	EBL21	11/-	EY88	8/6	PY80	5/9	UM90	9/6
6H6	3/3	19A5	5/6	ECC40	9/6	EZ40	7/6	PY81	5/9	UY21	8/9
6H7G	3/6	20D1	8/9	ECC81	4/9	EZ41	8/6	PY82	5/6	UY41	7/-
6J7GT	9/6	20P2	9/6	ECC82	5/6	EZ50	5/6	PY83	5/9	UY85	5/6
6K7G	2/8	29L1	18/-	ECC83	6/-	EZ81	6/-	PY88	8/6	VR105	5/-
6K7GT	5/6	29L1	9/6	ECC84	7/-	GZ31	9/6	PY800	7/-	VR150	5/-
6K3G	5/9	20P3	9/6	ECC85	5/9	GZ32	9/6	PZ30	9/6	X86	7/9

Stockists of Leak, Quad, Chapman, Goodman, Armstrong, Tripletone Linear Rogers, Truvox, Ferrograph, Wharfedale, etc.
Post: 1 lb. 1/5, 1 1/2 lb. 2/6, 2 lb. 2/9, 4 lb. 3/3, 6 lb. 4/-, 14 lb. 5/6,
All Mail Orders to Brighton please

TECHNICAL TRADING

LONDON 10 Tottenham Court Road, W.1. Tel. MUSeum 2689
BRIGHTON Park Crescent Place Tel. 680782
PORTSMOUTH 350-352 Fratton Road Tel. 22034
SOUTHAMPTON 72 East Street Tel. 25851
WORTHING 132 Montague Street Tel. 2555

HI-FI AMPLIFIERS — TUNERS — RECORD PLAYERS

20+20
STEREO
AMP.
AA22U



GARRARD
PLAYER
AT-60



TRANSISTOR MIXER. Model TM-1. A must for the tape enthusiast. Four channels. Battery operated. Similar styling to Model AA-22U Amplifier. Kit £11.16.6. Assembled £16.17.6

20+20W TRANSISTOR STEREO AMPLIFIER. Model AA-22U. Outstanding performance and appearance. 5 stereo inputs each channel, 20 transistor, 10 diode circuit. Kit £39.10.0 Assembled £57.10.0 (Cabinet £2.5.0 extra)

GARRARD AUTO/RECORD PLAYER. Model AT-60. less cartridge £13.1.7 With Decca Deram pick-up £17.16.1 incl. P.T. Many other Garrard models available, ask for Lists.

HI-FI MONO AMPLIFIER. Model MA-5. A general purpose 5W Amplifier with inputs for Gram., Radio. Modern functional appearance. Kit £11.9.6 Assembled £15.15.0

10W
POWER
AMP.
MA-12



9+9W
STEREO
AMP.
S-99



HI-FI MONO AMPLIFIER. Model MA-12. 10W output, wide freq. range, low distortion. Use with control units. Models UMC-1 (Mono) or USC-1 (Stereo). Kit £12.18.0 Assembled £16.18.0

3+3W STEREO AMPLIFIER. Model S-33. An easy-to-build, low cost unit. 2 inputs per channel. Kit £13.7.6 Assembled £18.18.0

DE LUXE STEREO AMPLIFIER. Model S-33H. De luxe version of the S-33 with two-tone grey perspex panel, and high sensitivity necessary to accept the Decca Deram pick-up. Kit £15.17.6 Assembled £21.7.6

HI-FI STEREO AMPLIFIER. Model S-99. 9+9W output. Ganged controls. Stereo/Mono, gram, radio and tape inputs. Push-button selection. Printed circuit construction. Kit £28.9.6 Assembled £38.9.6

POWER SUPPLY UNIT. Model MGP-1. Input 100/120V, 200/250V, 40-60 c/s. Output 6-3V 2-5A A.C. 200, 250, 270V, 120mA max. D.C. Kit £5.12.6 Assembled £7.2.6



SEE HEATHKIT at the

EXHIBITION, DEMONSTRATIONS OF HI-FI (Admission Free)

NEW!



HIGH PERFORMANCE CAR RADIO, CR-1. Superb LW/MW entertainment, wherever you drive. For 12V pos. or neg. earth systems. Tastefully styled to match any car colour scheme. Many special features. Send for details. Can be built for a total price Kit (less spkr) £12.17.0 incl. P.T. (6 x 4 LS £1.4.5 extra)

RADIOS



Oxford



UXR-1

"OXFORD" LUXURY PORTABLE Model UXR-2. Specially designed for use as a domestic or personal portable receiver. Many features, including solid leather case. Kit £14.18.0 incl. P.T.

TRANSISTOR PORTABLE. Model UXR-1. Pre-aligned I.F. transformers, printed circuit. Covers L.W. and M.W. Has 7" x 4" loudspeaker. Real hide case. Kit £12.11.0 incl. P.T.

JUNIOR EXPERIMENTAL WORKSHOP Model EW-1. More than a toy! Will make over 20 exciting electronic devices, incl.: Radios, Burglar Alarms, etc. 72 page Manual. The ideal present! Kit £7.13.6 incl. P.T.

TRANSISTOR STEREO FM TUNER. Elegantly designed to match the Stereo Amplifier, model AA-22U seen above. Many special features include built-in power supply. Available in two units sold separately, can be built for a TOTAL PRICE KIT (STEREO) £24.18.0 incl. P.T. Cabinet £7.5.0 extra. (MONO) version £20.19.0 Kit.

WELCOME TO OUR LONDON HEATHKIT CENTRE

233 Tottenham Court Road, W.1
We open MONDAY-SATURDAY 9 a.m.-5.30 p.m.
THURSDAY 11 a.m.-2.30 p.m.
Telephone No: MUSEUM 7349

WHEN YOU ARE IN TOWN, WE HOPE YOU WILL VISIT US THERE

TEST INSTRUMENTS

Our wide range includes:

3" LOW-PRICED SERVICE OSCILLOSCOPE. Model OS-2. Compact size 5" x 7½" x 12" deep. Wt. only 9½lb. "Y" bandwidth 2 c/s-3 Mc/s ±3dB Sensitivity 100mV/cm. T/B 20 c/s-200 kc/s in four ranges, fitted mu-metal CRT Shield. Modern functional styling. Kit £23.18.0 Assembled £31.18.0

5" GEN. PURPOSE OSCILLOSCOPE. Model 10-12U. An outstanding model with professional specification and styling. "Y" band width 3c/s-4.5 Mc/s ± 3dB. T/B 10 c/s-500 kc/s. Kit £35.17.6. Assembled £45.15.0

DE LUXE LARGE-SCALE VALVE VOLT-METER. Model 1M-13U. Circuit and specification based on the well-known model V-7A but with many worth-while refinements, 6" Ernest Turner meter. Unique gimbal bracket allows operation of instrument in many positions. Modern styling. Kit £18.18.0 Assembled £26.18.0

AUDIO SIGNAL GENERATOR. Model AG-9U. 10 c/s to 100 kc/s, switch selected. Distortion less than 0.1%, 10V sine wave output metered in volts and dBs. Kit £23.15.0 Assembled £31.15.0

VALVE VOLTMETER. Model V-7A. 7 voltage ranges d.c. volts to 1,500 A.C. to 1,500 r.m.s. and 4,000 peak to peak. Resistance 0-1Ω to 1,000MΩ with internal battery. D.C. input resistance 11MΩ. dB measurement, has centre-zero scale. Complete with test prods, leads and standardising battery. Kit £13.18.6 Assembled £19.18.6


MULTIMETER. Model MM-1U. Ranges 0-1.5V to 1,500V a.c. and d.c.; 150μA to 15A d.c.; 0.2Ω to 20MΩ 4½" 50μA meter. Kit £12.18.0 Assembled £18.11.6

R.F. SIGNAL GENERATOR. Model RF-1U. Up to 100 Mc/s fundamental and 200 Mc/s on harmonics. Up to 100mV output. Kit £13.18.0 Assembled £20.8.0

SINE/SQUARE GENERATOR. Model 1G-82U. Freq. range 20 c/s-1 Mc/s in 5 bands less than 0.5% sine wave dist. less than 0.15μ sec. sq. wave rise time. Kit £25.15.0 Assembled £37.15.0

TRANSISTOR POWER SUPPLY. Model IP-20U. Up to 50V, 1.5A output Ideal for Laboratory use. Compact size. Kit £35.8.0 Assembled £47.8.9

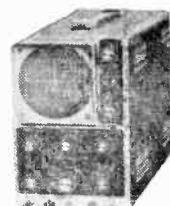Prices and specifications subject to change without notice



OS-2




VVM, 1M-13U



V-7A



RF-1U

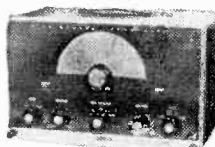

1G-82U

TUNERS — CONTROL UNITS



TUNERS
FM
AM/FM

HI-FI FM TUNER. Model FM-4U. Available in two units. R.F. tuning unit (£2.15.0 incl. P.T.) with I.F. output of 10.7 Mc/s and I.F. amplifier unit, with power supply and valves (£13.13.0). For free standing or cabinet mounting. Total Kit **£16.8.0** (Multiplex decoder available as extra).

HI-FI AM/FM TUNER. Model AFM-1. Available in two units which, for your convenience, are sold separately. Tuning heart (AFM-T1—£4.13.6 incl. P.T.) and I.F. amplifier (AFM-A1—£22.11.6). Printed circuit board, 8 valves. Covers L.W., M.W., S.W., and F.M. Built-in power supply. Total Kit **£27.5.0** (Multiplex decoder available as extra).


CONTROL UNITS (VALVE HI-FI)

MONO Designed to work with model MA-12 amplifier. 5 inputs. Baxandall type controls. Model UMC-1. Kit **£9.2.6**
STEREO 6 inputs. Push button selection. Ganged controls. Rumble and low pass filters. Model USC-J. Kit **£19.19.0**

LATEST MODELS



AMPLIFIER

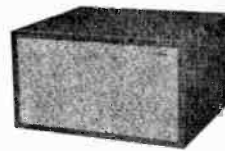

SPEAKER

Low-priced 3 + 3 watt TRANSISTOR AMPLIFIER. TS-23

Breaks the price barrier in quality stereo amplifier cost. Incorporates all the essential features for good quality reproduction from gram, radio and other sources. 3W rms (15W) each channel. Good frequency response. Modern, compact, slim-line styling. Ganged controls. 6 position selector switch. 16 transistor, 4 diode circuit. Walnut veneered cabinet, optional extra. Kit (Amplifier) **£17.15.0** Cabinet **£2.0.0** extra.

Good performance from a Mini speaker with the 'AVON' BOOKSHELF SPEAKER SYSTEM. Occupies the minimum space consistent with first class reproduction. Only 7½" x 13½" x 8½" deep. Two special speakers 6½" BASS, 3½" HF unit and crossover network. Kit **£4.18.0** incl. P.T. Walnut veneered, Fully finished cabinet, kit **£8.18.0**. TOTAL PRICE KIT **£13.16.0** incl. P.T.

GRAND HOTEL, LONDON



Concurrent with the Audio Fair. MARCH 30th — APRIL 2nd. 11 a.m.—9 p.m.

MULTIPLEX DECODER SD-1

For receiving Stereo FM. Convert your existing FM Mono receiver to stereo with this low cost, self powered unit. Fully transistorised. Kit **£8.10.0** Assembled **£12.5.0**
Styled to match British Heathkit models.



SD-1

SPEAKER SYSTEMS



SSU-1

HI-FI SPEAKER SYSTEM. Model SSU-1. Ducted-port bass reflex cabinet "in the white". Two speakers. Vertical horizontal models with legs, Kit **£12.12.0** without legs, Kit **£11.17.6** incl. P.T.

The **BERKELEY SLIM-LINE SPEAKER SYSTEM.** fully finished walnut veneered cabinet for faster construction. Special 12" bass unit and 4" mid/high frequency unit. Range 30-17,000 c/s. Size 26" x 17" only 7½" deep. Modern attractive styling. Excellent value. Kit **£19.10.0** Assembled **£24.0.0**

COTSWOLD SPEAKER SYSTEMS. Outstanding performance for price. MFS: Size 36" x 16½" x 14" deep. Kit **£25.12.0** Assembled **£33.17.0**
STANDARD: Size 26" x 23" x 14½" deep. Kit **£25.12.0** Assembled **£33.17.0**



Berkeley

**SEND FOR THE LATEST
FREE CATALOGUE**

Deferred terms available in UK over £10
Prices quoted are Mail Order prices,
retail prices in general 5/- extra.

DAYSTROM LTD. Dept. P.W.—4
GLOUCESTER

"AMATEUR" EQUIPMENT

80-10m TRANSMITTER. DX-40U. Power inputs 75W. C.W., 60W peak CC phone. Output 40W to aerial. Provision for VFO. Kit **£29.19.0** Assembled **£41.8.0**

AMATEUR BANDS RECEIVER Model RA-1. To cover all the Amateur Bands from 160-10 metres. Many special features, including: half-lattice crystal filter; 8 valves; signal strength "S" meter; tuned R.F. Amp. stage. Kit **£39.6.6** Assembled **£52.10.0**

160-10M TRANSMITTER. Model DX-100U. Careful design has achieved high performance and stability. Completely self-contained. Kit **£81.10.0** Assembled **£106.15.0**

COMMUNICATIONS TYPE RECEIVER. Model RG-1. A high performance, low cost receiver for the discriminating listener. Frequency coverage: 600 kc/s—1.5 Mc/s and 1.7 Mc/s—32 Mc/s. Kit **£39.16.0** Assembled **£53.0.0**

REFLECTED POWER METER and SWR BRIDGE. Model HM-11U. Indicates reliably but inexpensively whether the RF power output of your TX is being transferred efficiently to radiating antenna. Kit **£8.10.0** Assembled **£10.15.0**

OUTSTANDING "AMATEUR" EQUIPMENT
A wide range of American Amateur SSB equipment is now available in the U.K. Why not send for full details of range, for example:

FILTER TYPE SSB TRANSCEIVERS
Models for 80, 40 or 20 metre bands.
Model HW-12 (80M) **£62.10.0** Kit.
Model HW-22 (40M) **£61.0.0** each kit.
Model HW-32 (20M) price inc. duty, etc.



DX-40U



RA-1



HM-11U



80M Transceiver
HW-12

To DAYSTROM LTD. Gloucester. Tel. Glos. 20217.

☐ Please send me models for which I enclose £ s d post paid.
☐ Please send me FREE HEATHKIT CATALOGUE.

NAME

ADDRESS

DEPT. P.W.4

ABSORBING and EXCITING!

Unique and brilliantly simple. Hundreds of educational establishments—Universities, Technical Colleges, Schools, the Armed Forces—are already using Radionic for electronic instruction. Enthusiastic owners range from 9 to 82 years of age. Selected by the Council of Industrial Design for all British Design Centres. Featured in Sound and Television broadcasts.

The system is beautifully engineered from top quality British components. No soldering. No mains. No prior knowledge needed. Simply arrange components on perforated transparent panel, position brass connecting strip underneath fix with 6BA nuts and circuit works with full efficiency. You can then dismantle and build another circuit. Your results are guaranteed by our Technical Department and News Letter Service. All parts available separately for conversion or expansion of sets.

UNIQUE! Our "No soldering" printed circuit board for superhet portable. Simply insert components and tighten nuts.

No. 1 Set £5.18.6 14 Circuits (Earphone)
No. 2 Set £6.19.6 20 Circuits (Earphone)
No. 3 Set £10.19.6 22 Circuits (7 x 4in. Loudspeaker output)
No. 4 Set £14.19.6 26 Circuits (include 6 Transistor and reflex superhets)
Prices (Post Free)

(Plus P.T. increases of 1/8; 1/11; 3/1; 4/2d respectively.)

Full details from:


RADIONIC PRODUCTS LIMITED
STEPHENSON WAY, THREE BRIDGES
CRAWLEY, SUSSEX

Tel. CRAWLEY 27028


(Trade Enquiries invited)



A No. 4 SET and 6-TRANSISTOR SUPERHET

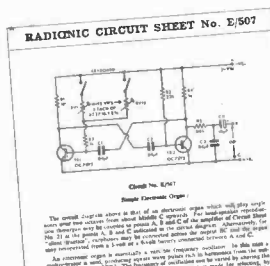

Theoretical Circuit

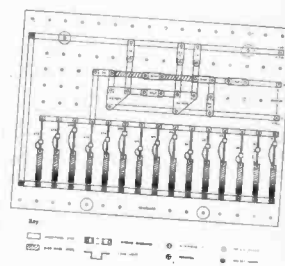

Practical Layout

Our 'E' Series of basic electronic circuits is available separately. Send for details of E/508 our do-it-yourself computer


surprise

surprise



Eddystone

HIGH PERFORMANCE RECEIVERS

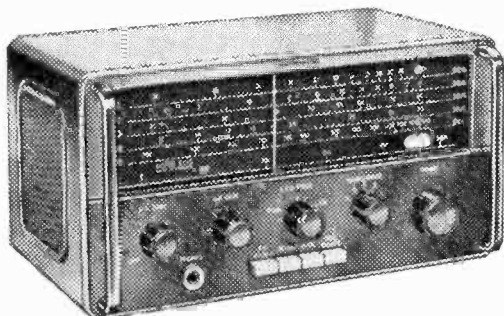

EC 10 ALL TRANSISTOR COMMUNICATIONS RECEIVER

Excellent reception on medium and shortwaves (545-10 metres) including marine coastal and six amateur bands. The Eddystone tuning mechanism, free from backlash, includes an accurate logging scale. Powered by U2 batteries. **£48.0.0**



EB 35 ALL TRANSISTOR BROADCAST RECEIVER

A versatile all-band receiver covering long, medium and shortwaves and interference-free VHF programmes. Can be used as a radio tuner with a hi-fi system, as a record player amplifier or with a tape recorder. Powered by U2 batteries. **£60.6.3**

An internally fitted AC mains unit can be supplied for these receivers

Eddystone Radio Limited

Eddystone Works, Alvechurch Road, Birmingham 31 • Telephone: Priory 2231 • Cables: Eddystone Birmingham • Telex: 33708

LTD/ED18

Perhaps you will be as surprised as the pundits when you hear the facts* about the BSR C1 ceramic cartridge "... another milestone on the public right-of-way to high fidelity"—said

The Gramophone.

You could even be surprised to know that the BSR UA70 manual/automatic turntable unit is fitted with such a splendid cartridge and that its all round performance is equal to such high standards.

But maybe not ... you could be one of those sensible people who knew all along that BSR don't just make a lot of autochangers but a lot of *very good* autochangers.

**If you'd like to read the independent test reports write to Arthur Nicholls at:*

BSR Limited, Monarch Works, Old Hill, Staffordshire.



for better
sound reproduction

BSR UA70 SPECIFICATION

Turntable

Wow Less than .2%

Flutter Less than .06%

Long term speed variation

Less than .5%

(mains voltage $\pm 10\%$)

Rumble (ref. 1kHz) — 29 dB

Pick-up arm

Counterbalanced lightweight arm with calibrated tracking pressure control, integral cueing device and automatic lock.

Tracking pressure (depending on cartridge)
2 grams. min.

Cartridge

The now famous C1 ceramic

Compliance 5.2×10^{-6} cm/dynes

Frequency response 20-15,000 Hz

± 2 dB

Standard UA70 player £12.18.3*


C1 Ceramic Cartridge

sapphire stylus £2. 7.0*

diamond stylus £3. 1.9*

*Inc. P.T. surcharge

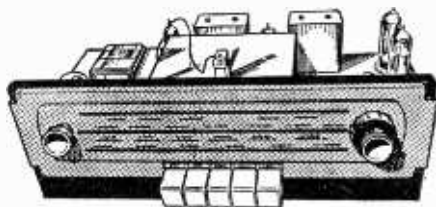BRAND NEW AM/FM (V.H.F.) RADIOGRAM CHASSIS AT £15.15.0 (Carriage Paid)



Chassis size 15 x 6 1/2 x 5 1/2 in. high. New manufacture. Dial 1 1/2 x 4 in. in 2 colours; predominantly cream. 200-250V. A.C. only. Pick-up Ext. Speaker. Ae., E. and Dipole Sockets. Five push-buttons—LW, MW, SW, FM and Gram. Aligned and tested. O.P. Transformer Tone control 1000-1900M; 200-550M; 88-98 Mc/s. 6-17 Mc/s. EZ80 rect.; ECH81, EF89, EABC80, EL84, EOC85, 3-ohm speaker required.

9 x 6 in. ELLIPTICAL SPEAKER, 80/- to purchasers of this chassis. TERMS: (Chassis), £5.5.0 down and 5 monthly payments of £2.5.0. Total H.P. price, £16.10.0. Cheap Room Dipole for V.H.F., 12/6. Feeder 6d. per yard. Circuit diagram 2/6. Carriage to N. Ireland, 20/- extra.

NEW 6 PUSH-BUTTON STEREOGRAM CHASSIS. M.W.; S.W.1; S.W.2: V.H.F., Gram; Stereo Gram. Two separate channels for Stereogram with balance control. Also operates with two speakers on Radio. Chassis size: 15 x 7 x 6 1/2 in. high. Dial cream and red. 16 x 3 in. 190-550M; 18-61M; 50-17M; V.H.F. 88-100 Mc/s. Valves: EOC85, ECH81, EF89, 2 x ECI86, EM84 and Rect. Price £19.18.0, carr. paid or £26.13.0 deposit and 5 monthly payments of 56/6. Total H.P. price £20.15.6. Cream moulded escutcheon included.

TAPE AMPLIFIER FOR MAGNAVOX TAPE DECKS — 2 or 4 TRACK (4 TRACK 25/- EXTRA)

Chassis 12 1/2 x 5 1/2 x 4 1/2 in. high. Plastic front panel "gold" finish—12 1/2 x 4 1/2 in. 200-250 A.C. Record/Playback amp. switch; Off/On-Tone; Vol/Mic; Vol/Gram; Mic. Input; Gram. Input; Monitor; Speaker Sockets. Valves 6BR7; 12AX7; EM84; EL84; 6X4 Separate power pack. Complete amp. and power pack, £8.17.6. (6/- P. & P.). Rexine covered cabinet (tan) 16 1/2 x 17 x 9 1/2 in. high with sloping front for amp. complete with two tweeter speakers, and special adapting brackets for Magnavox Deck—85/- (8/- carr.) 3 speed Magnavox 2 track tape deck £10.17.6; 4-track £12.15.0. Complete Recorders (with speed compensation) 2-track £29; 4-track £32 (carr. 25/-). Worth £10 more on normal retail prices.

The SUPER 6 LONG & MEDIUM WAVE TRANSISTOR RADIO



A quality radio available as a kit or ready-built. The sparkling performance and superb finish of the completed receiver give you value equivalent to a £21.12.0 commercial model.

★ All new parts. ★ 6 transistors and diode. ★ 350mW output. ★ Superhet circuit ★ Ferrite rod aerial. ★ Weymouth Radio printed circuit board. ★ Component positions and references printed on back of board. ★ Nicely styled wooden cabinet 11 x 7 1/2 x 3 1/2 in. ★ Vinyl covered in various colours. ★ 6 x 4 in. speaker giving good bass and treble response. ★ Full instruction booklet, 2/-. Free with kit. ★ I.f. frequency 470 kc/s. ★ Lining up service if required. ★ All parts supplied separately. Write for list, S.A.E. COMPLETE KIT ONLY £4.0.0 P. & P. 5/- OR FULLY BUILT £6.7.6. Tax and Carr. Paid.

TRANSISTORS AND DIODES

OC26, 7/6; OC44, 3/6; OC45, 3/6; OC71, 3/-; OC72, 4/-; OC81, 3/6; OC81D, 3/6; OC82, 6/-; OC83, 3/6; OC169, 8/-; OC170, 7/-; OC171, 8/-; OC172, 8/6; AC127, 7/6; AF115, 8/6; AF116, 8/-; AF117, 5/-; AF118, 7/6; AF119, 7/6; WG4B, 9d.; OA81, 2/6; OA79, 2/6; OA85, 2/6; BY100, 4/-, Post 4d. any quantity.

STEREO-AMPLIFIER 2 x 4 WATT

Valves EOC83, 2 x EL84, on printed circuit approx. 4 x 4 in. Neg. feed back. Controls (vol. or tone) on separate panel, 6 1/2 x 2 in. Separate power pack with rect., double wound mains trans., connection socket, etc. Supplied fully wired and tested with two O.P. transformers for 3-ohm speakers, only £5.10.0 (7/6 P. & P.). Two speakers, 8 in., 3-ohm for 20/- each, post paid, if ordered with above Amp.

BATTERY ELIMINATOR. 5 1/2 x 4 1/2 x 2 1/2 in. for 90 v. H.T. at 20mA and 1.5 v. at up to 250mA. Fully built, 55/- carriage paid.

GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants.

(2 mins. from Station and Buses)

CLOSED WEDNESDAY AFTERNOON CATALOGUE 6d.

Bulk enquiries invited for Export.

Aldershot 22240

For quick, easy faultless soldering



Easy to use and economical. Containing 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required. Ersin Multicore Savbit Alloy reduces wear of copper soldering iron bits.



SIZE 5 HANDY SOLDER DISPENSER
Contains 12 ft. of coil 18 s.w.g. Ersin Multicore Savbit Alloy. Quick and easy to use.
2/6 each



NEW SIZE 15
21 ft coil of 60/40 Alloy, 22 s.w.g. in a dispenser. Ideal for small components, transistors, diodes, etc.
3/- each



SIZE 12
Ideal for home constructors. Contains 102 ft. of 18 s.w.g. Ersin Multicore Savbit Alloy on a plastic reel. 15/- each (Also available in other sizes)



BIB MODEL 8 WIRE STRIPPER AND CUTTER
Strips insulation without nicking the wire, cuts wire and splits plastic twin flex. Plastic cushioned handles. 3/6 each

From Electrical or Hardware shops. If unobtainable write to:

MULTICORE SOLDERS LTD., Hemel Hempstead, Herts. M29 C

VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

SETS 1R5, 185, 1T4, 354, 3V4, DAF91, DF91, DK91, DL92, DL94. Set of 4 for 16/9. DAF96, DF96, DK96, DL96, 4 for 24/6

1A7GT 7/6	10C2 11/6	DH81 12/6	EF97 7/6	PEN383 9/6	UCH81 6/-
1R5GT 7/3	10F1 8/6	DK32 7/6	EF183 6/6	PFL200 14/-	UCL22 7/-
1N5GT 7/9	10P13 8/6	DK91 6/6	EF184 6/-	PL36 9/3	UCL83 8/6
1R5 5/6	12AT7 3/6	DK92 8/-	EL33 6/6	PL81 6/6	UF41 8/-
184 4/9	12AU6 4/6	DK96 6/6	EL41 6/6	PL82 6/6	UF80 7/6
185 3/6	12AU7 4/6	DL33 6/6	EL42 7/6	PL83 6/-	UF89 5/6
1T4 2/6	12AX7 4/6	DL35 3/-	EL44 4/6	PL84 6/6	UL41 8/9
3A5 7/-	12K7GT 3/6	DL92 4/6	EL95 5/-	PL500 12/6	UL44 20/-
3Q4 5/6	12K8GT 7/6	DL94 5/6	EM80 5/6	PL801 7/6	UL84 5/6
384 4/9	20F2 10/6	DL96 6/-	EM81 7/3	PX25 7/6	UY21 8/9
3V4 5/6	20L1 14/-	DY86 6/6	EM84 5/6	PY31 6/6	UY41 4/9
5U4G 4/6	20P1 9/-	DY87 6/6	EM87 6/6	PY32 8/6	UY85 4/9
6V4G 7/9	20P3 9/-	RAB380 6/-	EY51 6/3	PY33 8/6	VP4B 11/-
5Y3GT 5/-	20P4 13/6	EAF42 7/6	EY86 6/-	PY90 5/3	VP1321 21/-
5Z4G 7/-	25U4GT11/6	EB41 4/-	EZ40 8/3	PY81 5/3	W76 3/6
6/30L2 9/6	30C15 10/6	RB91 2/3	EZ41 6/6	PY82 5/-	W77 3/6
6AL5 2/3	30C17 11/6	EB33 7/-	EZ80 4/6	PY83 5/6	Z77 3/6
6AM6 3/6	30F5 9/6	EB341 7/9	EZ81 4/6	PY88 7/3	Transistors
6AQ5 5/6	30FL1 10/6	EBF50 6/-	GZ32 9/-	PY800 6/6	AC107 10/-
6A6T 4/-	30L15 11/-	EBF59 5/6	KT61 6/6	PY801 6/-	AC127 7/6
6BA6 4/6	30L17 12/-	ECC81 3/9	N18 5/6	R19 7/6	AD140 12/6
6BE6 4/3	30P4 11/6	ECC82 4/6	N78 14/9	R20 12/9	AF102 18/-
6BJ6 6/6	30P12 9/6	ECC83 7/-	PC86 9/-	U25 9/-	AF115 6/6
6BW6 7/6	30P19 11/6	ECC84 6/3	PC88 9/-	U36 8/9	AF116 6/9
6F1 7/9	30PL1 12/6	ECC85 5/6	PC87 5/9	U47 8/6	AF117 5/-
6F13 3/6	30PL3 11/9	ECP80 7/6	PC900 8/9	U49 9/6	AF118 13/6
6F14 9/-	35L6GT 6/3	ECP82 6/6	PC84 5/6	U82 4/6	AF124 9/-
6F23 9/9	35P1 4/6	ECP86 9/-	PC89 8/9	U78 8/6	AF125 8/6
6E7G 1/6	35Z4GT 4/6	ECH35 6/-	PC189 8/6	U191 10/6	AF126 8/-
6K8G 4/3	5A2 5/6	ECH42 9/-	PCF80 8/6	U301 11/9	AF127 8/-
6K8GT 7/6	185BT 20/-	ECH81 5/6	PCF82 6/-	U801 16/3	OC22 17/6
6L18 7/6	6063 12/6	ECH84 8/6	PCF86 8/3	UABC80 5/3	OC25 9/6
6Q7G 5/6	A231 9/-	ECL80 6/-	PCF800 10/6	UAF42 7/9	OC26 6/6
6V8G 3/6	B36 4/6	ECL82 6/3	PCF801 8/9	UBC41 6/6	OC44 4/3
6V8GT 6/6	BT29 10/-	ECL86 7/6	PCF802 8/6	UBF80 6/-	OC45 3/3
6X4 3/6	DAC32 7/3	EF39 3/9	PCF805 9/9	UBF89 5/9	OC71 3/6
6X5GT 5/9	DAF91 3/9	EF41 6/3	PCL82 6/9	UBL21 9/-	OC72 4/9
7B6 10/9	DAF96 6/-	EF80 4/9	PCL83 8/6	UC92 5/6	OC75 5/9
7B7 7/-	DC90 7/-	EF85 5/-	PCL84 7/6	UC84 7/9	OC81 3/6
7C5 9/6	DF31 7/9	EF86 6/3	PCL85 8/3	UC85 6/6	OC81D 3/6
7C6 9/6	DF91 2/9	EF99 5/6	PCF86 8/6	UCF80 8/6	OC82 5/9
7H7 5/6	DF96 6/-	EF91 3/6	PEN44 3/9	UCH21 9/3	OC82D 5/6
7X4 6/6	DF77 4/-	EF92 2/9	PEN36C15/-	UCH42 8/9	OC170 5/6

READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. CRE 7441

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra.

JOYSTICK VFA turns PRO!

History repeats itself!

Throughout the development of radio communication the keen private experimenter has contributed largely to the advance of our science. The amateurs of the thirties pioneered reliable shortwave transmission and reception. Basic theories and their practical application are to this day hatched in the fertile minds of ingenious men who are the leading amateurs of our time.

The Joystick Aerial System can now be regarded as the perfect example of a purely amateur development "turning professional". Thousands of Joystick variable frequency aerial systems have been sold. The enormous number of enthusiastic testimonials that have accumulated at the Joystick factory are now in themselves calling for a separate filing room! The continuing success of the VFA has not only spread right round the world but has finally penetrated the barrier of professional and official circles. Professional bodies in the USA, Europe, Africa and the Far East have ordered VFA systems for operational use and for experimental work. Security forbids the whispering of names but clearance has been given to mention the Nigerian Police and an Australian fire control organisation.

In the Scottish fishing boats which have installed the system, communication with other ships and shore stations has become considerably more reliable over difficult paths.

This VFA system is a remarkable invention and its unique quality of high performance at any selected frequency from 1 M/c to 30 M/cs—particularly from difficult locations—has radically changed the attitude of both the licensed amateur and the shortwave listener towards their aerial problems.

Each Joystick VFA system is complete with a Joymatch matching unit suitable for each type of operation.


Hundreds and Hundreds of terrific testimonials may be seen at the Joystick Office—the selection shown here will prove the point.

PAUL B. AUFENUST G10513—"Very satisfied—very FB antenna, the first call I heard on it was LA9MI/P Jan Mayen Islands!! R5S9."


C. W. BLAY, HULL—"Excellent results on all bands, when using A.T.U. Thank you for your prompt attention to my order."

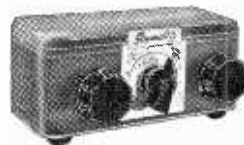F. G. MARSHALL, NEWCASTLE-ON-TYNE—"Satisfied—JOYSTICK is propped against wall in corner of room."

R. CHALMERS, G3SXO/A—"I am satisfied with the performance of my JOYSTICK. ALL TRANSMITTER I.O.W. TOP BAND STATION."



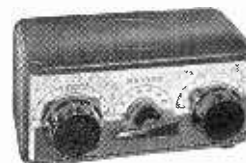Joymatch Type 2A—General medium wave coverage extending over short wave spectrum.



Joymatch Type 3A—General short wave coverage for SWL. Bandswitched for amateur bands. **Joymatch Type 4**—(similar to Type 3A). For transmission and reception. Bandswitched on 160—10 metres.



Joymatch Type 4RF—For transmission and reception on 160—10 metres. Includes RF meter for peak efficiency.



Joymatch Type 3—General short-wave coverage SWL (Junior model).

You cannot afford to ignore the potential of the Joystick VFA. The system is simple to use—the Joystick VFA will clip to a chimney, tree or mast, can be laid upon a pelmet, stood in the corner of a room, will even give a good account of itself in a basement.

Mobile Joystick systems are available and a new marine model has been introduced for the nautical types!

You are strongly recommended to contact the Joystick factory immediately (or one of our agents) for a brochure with full details.

U.K. Agents: G. W. Smith & Co. (Radio) Ltd., 3 Lisle Street, London, W.C.2. Stephens-James Ltd., 70 Priory Road, Liverpool, 4. Chas. H. Young, 170/172 Corporation Street, Birmingham, 4. R.S.C. (Manchester) Ltd., 326 Argyle Street, Glasgow, C.1 (and all branches) or ask your local dealer.

Overseas: France: Vareduc-Cominex, 2 Rue Joseph-Riviere, Paris, Courbevoie, France.

Scandinavia: Permo, Nygaardsgaten 42, Fredrikstad, Norway.

West Germany: Ing. Hannes Bauer, 86, Bamberg, Hornthalstrasse, 8, Stolz & Goessl, 8 Munchen 15, Bayerstrasse 3, and World Wide Agencies.

U.S. Patent No. 3074600. S. Africa Patent No. 63/4399. U.K. and World Patents applied for.

Post this coupon in the morning—without fail!

PARTRIDGE ELECTRONICS LTD.

Caister House, Prospect Road, Broadstairs, Kent

NAME.....Call Sign.....

ADDRESS

.....PWC

Litesold

SOLDERING INSTRUMENTS

With re-styled nylon moulded handles

- SEVEN SIZES from 10 WATTS to 55 WATTS
- REPLACEABLE BITS, COPPER & PERMATIP
- EXCELLENT TEMPERATURE REGULATION
- COOL, UNBREAKABLE HANDLE
- RAPID HEATING
- SIMPLE SERVICING
- ALL VOLTAGES
- LOW COST



LITESOLD

instruments

are compact and

nicely balanced. Bits

are spring-collet moun-

ted for firmness and easy

removal. Copper bits are stand-

ard; in sizes from $\frac{3}{32}$ " to $\frac{1}{2}$ " dia.

PERMATIP bits are slightly slower,

but eliminate bit face wear. LITESOLD

elements are encased in specially pre-oxidised

wire for constant temperature regulation from

new—less glamour but honest design, also apparent

in the simple, unbreakable handle, with the element unit

secured by two self-tapping screws (servicing couldn't be

easier) and firm, spring-on clip. LITESOLD hollow-spindle

construction prevents heat loss into the handle (which DOES

stay cool) and improves performance. Useful LITESOLD accessories

include HEAT GUARDS for elements, and BENCH STANDS.

BITLOOS anti-seize compound really does prevent bits sticking.

Available in 2-oz. tubes.


Free details of the whole wide range of LITESOLD and ADAMIN soldering equipment in brochure SP10.

LIGHT SOLDERING DEVELOPMENTS LTD.

28, Sydenham Road, Croydon, Surrey

Telephone: CROYDON 8589 and 4559

LATEST RADIOGRAM CABINETS £9.10.0

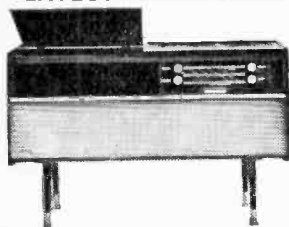

Superbly made and styled
in Veneered English
Walnut

Lift-up lid to changer and
record storage compartment

Position 8 x 5in. twin Speakers

Dimensions: 40 x 16½ x 15½ in.

Legs 1 gn. Carr. 30/-

Other Models—Send for list

RECORD PLAYER CABINETS, 49/6. Latest
designed covered cabinets. Takes any modern Auto-
changer. P. & P. 7/6.

TRANSISTOR CASES 19/6 9½ x 6½ x 3½ in. P. &
P. 2/6.

TV TURRET TUNERS, 2/6. New, less valves.
Slim models 5/-. Press button models 19/6. P. & P.
2/6.



17in.—£11.10.0

TWO-YEAR GUARANTEE EX-RENTAL TELEVISIONS

- 3 Star Guarantee
- ★ Tube ★ Valves
- ★ Components Carr. 30/-

FREE ILLUSTRATED LIST OF TELEVISIONS


17"—19"—21"—23"
WIDE RANGE OF MODELS
SIZES AND PRICES
DEMONSTRATIONS DAILY

TWO-YEAR GUARANTEED TUBES 100% REGUNNED

14in.—69/6 17in.—89/6
21in. and ALL SLIMLINE TUBES 99/6
Carr. 10/6

EX MAINTENANCE TESTED TUBES

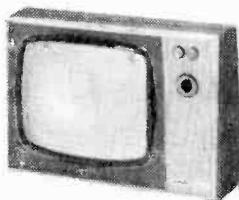17in.—35/- 14in.—15/-
Carr. 5/- (not slimline)



DUKE & CO. (LONDON) LTD.

621/3 Romford Road, E.12

ILF 6001-2-3

TRANSISTORS

OC23	10/-	OC82	3/6
OC25	9/6	OC82D	3/6
OC26	9/6	OC84	5/6
OC28	11/-	OC169	4/6
OC35	12/6	OC170	4/6
OC36	12/6	OC171	6/-
OC38	12/6	OC200	7/6
OC44	3/6	AC126	3/6
OC45	3/6	AC127	3/6
OC46	4/-	AC128	3/6
OC70	3/6	AD170	15/-
OC71	3/6	AF114	5/3
OC72	3/6	AF115	5/-
OC75	3/6	AF116	5/-
OC76	4/-	AF117	4/6
OC78	4/-	AF118	4/6
OC78D	4/-	AF119	4/6
OC81	3/6	AF119	4/6
OC81D	3/6	OA81	2/6

C.W.O., P.P. 2/- In £. Min. 1/-.

RECORDING TAPES

3in. Standard	150ft.	3/11
3in. Standard	225ft.	4/11
3½in. Triple Play	600ft.	42/6
5in. Standard	600ft.	10/-
5in. Long Play	900ft.	14/6
5in. Double Play	1200ft.	15/6

5½in. Long Play	1200ft.	16/-
5½in. Double Play	1800ft.	22/6

7in. Standard	1200ft.	17/6
7in. Long Play	1800ft.	22/6
7in. Double Play	2400ft.	25/-

Four of the tapes or more are post free
otherwise Postage 1/6.

SPOOLS

3in. spool	1/-	5½in. spool	2/-
3½in. spool	2/3	4in. spool	2/3
5in. spool	2/6	7in. spool	1/6

Postage and packing 6d. All items
listed are cash with order.

INTERCOM/BABY ALARM

Modernise your home or busi-
ness with this new all transistor
Intercom consisting of one
master and one sub. Complete
with all leads, battery and full
instructions. Usually 5 gns.

Our Price 49/6. P.P. 2/-.

TEST METERS

Pocket Test Meter D14
Specifications: DC voltage 0-15
-150-1,000 volts (1,000 R/V).
AC voltage 0-15-150-1,000
volts (1,000 R/V)
DC current 0-150 milliamperes.
Resistance 0-100 KΩ. Size:
57 x 93 x 30mm. Net weight
108 g. Only 39/- Carr. 2/-.

Send 3d. stamp for catalogue containing

Hi-Fi, Transistor Radios, Microphones, Autochangers, etc.

to: MOORDOWN RADIO LTD., 941 WIMBOURNE RD.,

MOORDOWN, BOURNEMOUTH. Tel 59866

CODAR — QUALITY

ANOTHER CODAR TRIUMPH!

THE CR.70A COMMUNICATION RECEIVER.

This completely new receiver sets a new high standard for performance and finish unequalled at the price, and is a worthy addition to the outstanding range of CODAR quality communication equipment. Frequency range: 580 Kc/s-30 Mc/s (540-10 metres) in four ranges: 580 Kc/s-1.5 Mc/s; 1.5 Mc/s-4.2 Mc/s; 4.2 Mc/s-11.5 Mc/s; 11.5 Mc/s-30 Mc/s. Slide rule scales for each band calibrated in frequencies plus an additional logging scale in degrees. Two speed vernier tuning control with reverse slow tune action. Unique aerial input stage exclusive to the CR.70A employing High 'Q' Air-spaced CODAR-COIL inductor giving extremely high gain with low noise level. Panel aerial trimmer for peaking weak signals. Double tuned I.F. Iron cored transformers. 470 Kc/s with EF183 frame grid valve for maximum gain and selectivity. 5 valves (including two twin triodes) giving 7 valve line-up. Separate H.F.O. stage for CW and SSB reception. Calibrated signal strength 'S' meter, illuminated. Automatic Volume control. Panel phone jack for 'private' listening. 2-3 ohm output for external speaker. (Matching unit optional extra.) Superb styling, metal cabinet in the new Organasol Satin lustre finish. Size: 13" x 5 1/4" x 7 1/4". For A.C. 200-250v. Ready built. Not a Kit at the fantastic low price of £19.10.0. Carr. 7/6.

CODAR R.F. PRE-SELECTOR MODEL P.R.30. Considerably improves the performance of any superhet receiver over 1.5-30 Mc/s. Uses EF183 Frame Grid Valve, and provides up to 20dB gain plus substantial image rejection, improved signal/noise ratio and selectivity. Selector switch for either dipole or single wire antenna. Power requirements 180-250 volts 12mA H.T. 6.3 volts, 3 amp L.T. Size 9 1/2 x 5 x 4 1/2 in. Ready built, complete with cables, plugs and instructions, £5.10.0. Carr. 4/6. **MODEL P.R.30X.** Self powered model for 200-250v. A.C. Also provides 25mA at 200v. H.T. and 6.3v. 1 amp L.T. for other accessories £7.4.0. Carr. 4/6.

CODAR "Q" MULTIPLIER MODEL R.Q.10. For use with any superhet receiver with an I.F. between 450 and 470 Kc/s. Provides considerable increase in selectivity for either peaking or rejecting a signal on AM, CW, or SSB, BFO. Size 9 1/2 x 5 x 4 1/2 in. Power requirements 180-250v. H.T. at 5mA 6.3v. 3 amp L.T. Ready built complete with cables, plugs and instructions, £6.15.0. Carr. 4/6. **MODEL R.Q.10X.** Self powered version for 200-250v. A.C. and also provides 25mA at 200v. H.T. and 6.3v. 1 amp L.T. for other accessories £8.8.0. Carriage 4/6.

CODAR A.T.5, 12 WATT 2 BAND TRANSMITTER. The newest most compact transmitter for fixed or mobile use on 160-80 metres. "The tiny TX with the BIG voice". Size only 8 1/2 x 5 x 4 1/2 in. (Base area is less than two-thirds of this page!) High stability new type calibrated VFO. 1.8-20 Mc/s and 3.5-3.8 Mc/s (up to 4 Mc/s export). Air-spaced CODAR COIL Pi-net output. P.A. Plate current meter plus neon indicator. Plate-Screen modulator. AM/CW switch and Panel key jack. Plug change over for 6 or 12 volts heater supply. Ready built £16.10.0. Carr. 4/6. **A.T.5 POWER SUPPLY UNITS.** For 200-250v. A.C. and 12v. Solid state for Mobile use, complete with all Transmit/Receive changeover switching available.


CODAR-KIT CR.45K MAINS T.R.F. SHORT-WAVE RECEIVER. World wide reception—North and South America, Russia, India, Australia, Far East, Amateurs, Shipping, etc. ★ Separate electrical bandspread. ★ 3 slow motion vernier drives. ★ Low loss polystyrene plug-in coils, factory aligned ★ Dials calibrated in frequencies and degrees. ★ Power output 3 watts for 2/3 ohm speaker. ★ Valve line-up: ECC81, EL84, EZ280. Size 12 x 5 1/4 x 7 1/4 in. **CODAR-KIT CR.45K** complete with valves, 3 coils (10-28, 25-75, 60-176 metres) and 11 page instruction manual, £9.10.0. Carr. 6/-. Extra coils 5/- each. Instruction manual only 4/- (credited on order). (Can also be supplied ready built—price on request).

CODAR-KIT MINI-CLIPPER—OUR FAMOUS SHORT-WAVE RECEIVER. ★ Can be built in one evening ready to switch on and bring the World to your fingertips at very low cost. ★ Supplied complete with valve, one coil 25-75 metres and 4-page instruction manual. PRICE 39/6. Carr. 3/-. Extra coils 5/- each. Instruction manual only 2/- (credited on order). Electrical bandspread available. Provision to add 2 transistor amplifier.

Send 6d. in stamps for illustrated leaflets of the Codar range

H.P. terms available

World-Wide Mail Order Service

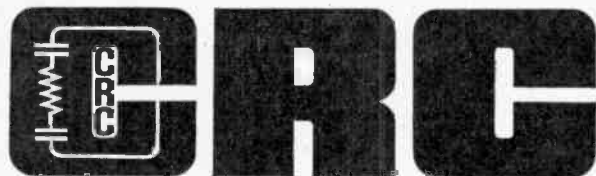

CODAR RADIO COMPANY

BANK HOUSE, SOUTHWICK SQUARE

SOUTHWICK, SUSSEX. Tel. 3149

G3IRE

G3HQQ


Canada: Codar Radio of Canada, Tweed, Ontario

VIKING TRANSISTOR

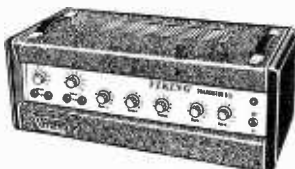40-50 WATT AMPLIFIER

OPERATING INSTRUCTIONS

GENERAL. An extremely reliable lightweight amplifier capable of giving 40-50 watts of undistorted sound, made possible by the use of the latest semi-conductors (transistors) and techniques which ensure space-age reliability under the most rugged conditions. It is



designed as a general purpose amplifier particularly suitable for use with musical instruments that require exceptionally high treble response (not recommended for Bass Guitar). Tremolo facilities are available on Channel 1 only. **INPUTS—CONTROLS—CHANNEL 1 (Tremolo):** this contains two high gain input jack sockets controlled by Volume Control 1 which is mounted directly above the two sockets marked tremolo. **BASS 1:** gives a controlled boost to the lower frequencies on Channel 1 only. **TREBLE 1:** gives a controlled boost to the high frequencies on Channel 1 only. **TREMOLO:** this operates on Channel 1 only and the variations of intensity and speed of the Tremolo beat is adjusted by the controls **DEPTH** and **SPEED**. A socket is provided in the rear of the amplifier so that the Tremolo may be switched on and off by the use of a footswitch plugged into the socket. If you wish the Tremolo to be used without the foot-switch, this is possible as the footswitch is only used to short out the effect. **INPUTS AND CONTROLS—CHANNEL 2 (Normal):** this contains two high gain input jack sockets controlled by Volume Control 2 which is mounted directly above the sockets marked Normal. **TREBLE 2:** gives a controlled boost to the treble frequencies on Channel 2 only. **MAINS VOLTAGE:** fully adjustable, 200-250 volts, A.C. 50 cycles. **POWER OUTPUT:** 40-50 watts sine wave British rating. Very little distortion. **OUTPUT IMPEDANCE:** 3 ohms. Price 21 gns. plus 1/6 postage and packing.

WOLSEY U.H.F. AERIAL AMPLIFIER, two stage, gain 23 dB, noise factor 8 dB, power consumption 6 mA at 14 volts. Two AF186 transistors, complete with built-in power supply in metal case, list price 9 gns., our price 4½ gns. plus 2/6 postage and packing.

MAINS TRANSFORMER, primary 200/250 volt, secondary 425/425 volt, 250 mA, 6.3 volt 4 amp, 5 volt 3 amp; fully shrouded, chassis mounting. Price £2.50 plus 7/6 postage and packing. Auto transformer step-up-step-down, 240/110 volt 400 watt. Price £1.50 plus 7/6 postage and packing.

MAINS TRANSFORMER 200/250 volt, secondary 250/250 volt, 70 mA, 6.3 volt, 3 amp drop through. Price 12/6 plus 4/6 postage and packing. Elac 10 inch, 10,000 lines ceramic magnet, 3 or 15 ohms, 7 watt, £1.9.6 plus 4/6 postage and packing.



POCKET MULTI-METER

Size 3½ x 2½ x 1½ in. Meter size 2½ x 1½ in. Sensitivity 1000 O.P.V. on both A.C. and D.C. volts. 0.15, 0.150 0.1000. D.C. current 0.150mA. Resistance 0.100kΩ. Complete with test leads, battery and full instructions, 42/6. P. & P. 3/6. **FREE GIFT** for limited period only. 30 watt Electric Soldering Iron value 15/- to every purchaser of the Pocket Multi-Meter.

40W FLUORESCENT LIGHT KIT




Incorporating GEC Choke size 8½ in. x 1½ in. x 1½ in., 2 bi-pin holders, starter and starter-holder. P. & P. 5/6. **11/6**
Similar to above: 80W. Fluorescent Light Kit incorporating GEC choke size 11½ in. x 1½ in. x 1½ in. 2 bi-pin holders start and starter holder. **17/6**
P. & P. 6/6.

Twin 40W Choke instant start for 2 x 2ft. tubes 17/6. P. & P. 5/6.


3 to 4 Watt AMPLIFIER

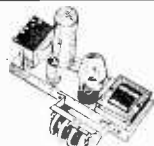3-4 watt Amplifier built and tested. Chassis size 7 x 3½ x 1½ in. Separate bass, treble and volume control. Double wound mains transformer, metal rectifier and output transformer for 3 ohms speaker. Valves ECC81 and 6V6. £2.5.0 plus 5/6 p. & p.
The above in Kit Form, £1.14.6 plus 5/6 p. & p.



"MUSETTE" 6-Transistor Superhet Portable Radio

★ 2½" Speaker. ★ 6 Transistor Superhet Output 200mW. ★ Plastic Cabinet in red, size 4½ x 3 x 1½" and gold speaker grille. ★ Horizontal Tuning Scale. ★ Ferrite Rod Internal Aerial. ★ IF 460 kc/s. ★ All components Ferrite Rod and Tuning Assembly mount on printed board. ★ Operated from PP3 Battery. ★ Fully comprehensive instructions and point-to-point wiring diagram. ★ Printed Circuit Board. ★ Tunable over medium and long waveband. ★ Car aerial and earpiece socket.

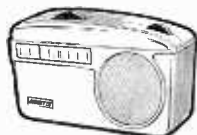

Price 39/6d. inc. carrying strap. Circuit Diagram 2/6 free with parts. P. & P. 3/6.

RADIO & TV COMPONENTS (Acton) LTD

21c High Street, Acton, London, W3


Shop Hours 9 a.m.—6 p.m. Early Closing Wednesday

Goods not despatched outside U.K. Terms C.W.O.
All enquiries Stamped Addressed Envelope

MULTIPLEX DECODER

For receiving Stereo FM

Now is your chance to benefit in full from the new B.B.C. stereo transmissions with our Multiplex Decoder. Design features: Highly efficient Mullard vinkor pot cores. Two semiconductor diodes. Double purpose valve. Printed circuit type construction high input impedance. Specification: Cross talk minus 26 dB at 1 kc/s. Input requirements 0.5-1.5 RMS. Stability plus or minus 0.1%. Voltage requirements H.T. 190-250 volts, D.C. at 5 mA, heaters 6.3 volts, A.C. at 300 mA. Self powered unit shortly available, price to be announced. Size 5½ x 3½ x 1½. Fully built and tested.

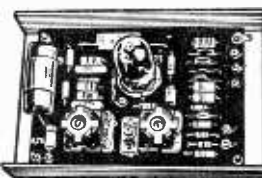

Price £4.4.0 P. & P. 3/-



Type E MOTOR


Small A.C. mains motor 230/250 volts complete with gearbox, 6 r.p.m. Price 15/- plus 4/- P. & P. Similar to above motor but without gearbox. Price 9/6 plus 3/- P. & P.

Silicon Rectifiers

250 v. P.I.V. 750 milliamperes. Six for 7/6, Post paid.

TRANSISTORISED 1½ WATT AMPLIFIER

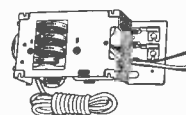comprising 2AC 128, 20C 75 and 2 AA129 separate bass and treble volume controls. Complete with Power Supply AC mains 240 v. Size 7½ x 3½ x 2". Price 50/- plus 2/6 P. & P.



POWER SUPPLY KIT

A.C. MAINS 200-250 V

Incorporating "C" core type mains transformer, full wave metal rectification and smoothing condenser. Smooth output 250 v. 250mA and 6.3v. 4 amp. for Heaters. 25/- P. & P. 9/6.




FIRST QUALITY P.V.C. TAPE

5½" Std. 850ft.	9/-	5" L.P. 850ft.	10/6
7" Std. 1200ft.	11/6	3" T.P. 600ft.	10/6
3" L.P. 240ft.	4/-	5" T.P. 1800ft.	25/6
5½" L.P. 1200ft.	11/6	5½" T.P. 2400ft.	32/6
7" L.P. 1800ft.	18/6	7" T.P. 3600ft.	42/6
5½" D.P. 1800ft.	18/6	4" T.P. 900ft.	15/-

P. & P. on each 1/6, 4 or more post free

EXTRACTOR FAN

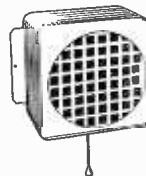

AC Mains 230/250 v. complete with pull switch. Size 6" x 6" x 4". Price 27/6 plus 5/- P. & P.

GEC DOORBELL

Complete with mains transformer 240 v. AC & illuminated bell push plus 5/6 P. & P.



8-watt 4-valve PUSH-PULL AMPLIFIER & METAL RECTIFIER

Size: 9" x 6" x 1½". A.C. Mains, 200-250V 4 valves. For use with Std. or L.P. records, musical instruments, all makes of pick-ups and mikes. Output 8 watts at 5 per cent of total distortion. Separate bass and treble lift control. Two inputs, with controls for gram. and mike. Output transformer tapped for 3 and 15 ohm speech coils. Built and tested, £4.4.0. P. & P. 11/-, 8" x 5" speaker to suit price 14/6 plus 1/6 P. & P. Crystal mike to suit 12/6 plus 1/6 P. & P.



GEC KETTLE ELEMENT

3,000W WITH AUTOMATIC EJECTION 200/240 v. Size of hole required 1½". List Price 32/-. Our PRICE 15/- P. & P. 1/6.



NEW TRANSISTORISED SIGNAL GENERATOR

Size 5½ x 3½ x 1½". For IF and RF alignment and AF output 700 c/s frequency coverage 460 kc/s to 2 mc/s in switched frequencies. Ideal for alignment to our Elegant Seven and Musette. Built and tested. 39/6 P. & P. 3/6

CYLDON U.H.F. TUNER

Complete with PC88 and PC86 Valves. Full variable tuning. New and unused. Size 4½ x 5½ x 1½ in. Complete with circuit diagram. 35/- plus 3/6 P. & P.



Our new branch at 323 EDGWARE ROAD, LONDON, W.2 is now open Personal shoppers only. Early Closing Thursday. All orders by post to our Acton address.

Elegant Seven Mk II A

SPECIAL OFFER

7" x 4" P.M. Speaker at no extra charge

Buy yourself an easy to build 7 transistor radio and save at least £10.0.0. Now you can build this superb 7 transistor superhet radio for under £4.10.0. No one else can offer such a fantastic radio with so many de luxe star features.

- ★ De luxe grey wooden size 12½" x 8½" x 3½".
- ★ Horizontal easy to read tuning scale printed grey with black letters, size 11½" x 2".
- ★ High 'Q' ferrite rod aerial.
- ★ I.F. neutralization on each separate stage.
- ★ D.C. coupled push pull output stage with separate A.C. negative feedback.
- ★ Room filling output 350 mW.
- ★ Ready etched and drilled printed circuit board back printed for fool proof construction.
- ★ Fully comprehensive instructions and point-to-point wiring diagrams.
- ★ Car aerial socket.
- ★ Fully tunable over medium and long wave. 168-535 metres and 1250-2000 metres.
- ★ All components ferrite rod and tuning assembly mount on printed boards.
- ★ Full after sales service.
- ★ Parts list and circuit diagram 2s, 6d., free with parts.


ONLY **£4.4.0**

Plus 7/6 P. & P. Parts List and circuit diagram 2/6 FREE with parts.

POWER SUPPLY KIT

To purchasers of 'Elegant Seven' parts, incorporating mains transformer, rectifier and smoothing condenser, A.C. mains 200/250 volts. Output 9v 100mA. 7s. 6d. extra.

COMBINED PORTABLE and CAR RADIO

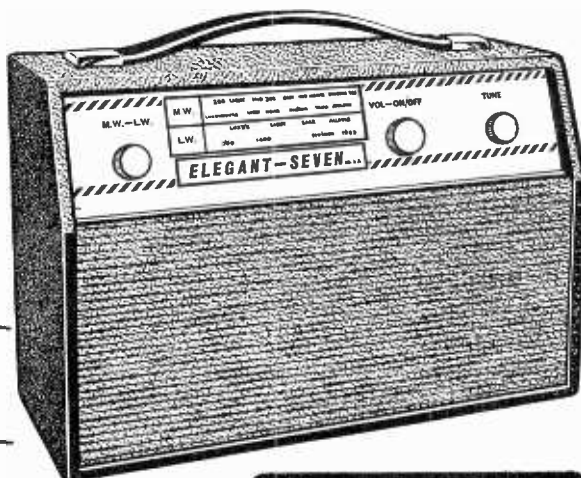

Our new branch at
323 EDGWARE ROAD, LONDON, W.2.
IS NOW OPEN
PERSONAL SHOPPERS ONLY

Edgware Road branch: early closing Thursday

All orders by post must be sent to our Acton address.

ALL ENQUIRIES STAMPED ADDRESSED ENVELOPE
OPEN 9 a.m.—6 p.m., INCLUDING SATS. EARLY CLOSING WED.
GOODS NOT DESPATCHED OUTSIDE U.K. TERMS C.W.O.

RADIO & TV COMPONENTS (ACTON) LTD
21C HIGH STREET • ACTON • LONDON • W.3



YOURS FREE FOR 7 DAYS

The New 'Picture - Book' way of learning

BASIC

ELECTRICITY (5 Vols)
ELECTRONICS (6 Vols)
ELECTRONIC CIRCUITS (2 Vols)
INDUSTRIAL ELECTRICITY (2 Vols)
SYNCHROS & SERVOMECHANISMS (2 Vols)

You'll find it easy to learn with this outstandingly successful new pictorial method—the essential facts are explained in the simplest language, one at a time; and each is illustrated by an accurate cartoon-type drawing.

The books are based on the latest research into simplified learning techniques. This has proved that the Pictorial Approach to learning is the quickest and soundest way of gaining mastery over these subjects.

The series will be of exceptional value in training mechanics and technicians in electricity, Radio and Electronics.

WHAT THIS MONTH'S ENTHUSIASTIC READERS SAY

... I was very pleased with the set of Basic Electronics. Please send Basic Electricity ... D.W., MARGATE

... I find them easy to follow because of their lucid and clear descriptive format ... M.V., EAST GRINSTEAD

TO SELRAY BOOK CO. 60 HAYES HILL, HAYES, BROMLEY, KENT

Please send me Without Obligation to Purchase, one of the above sets on 7 Days Free Trial. I will either return set, carriage paid, in good condition within 7 days or send the following amounts. Basic Electricity 70/-, Cash Price or Down Payment of 15/- followed by 4 fortnightly payments of 15/- each. Basic Electronics 82/-, Cash Price or Down Payment of 15/- followed by 5 fortnightly payments of 15/- each. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order.

Tick set required (only ONE set allowed on free trial).

BASIC ELECTRICITY 70/- ☐ BASIC ELECTRONICS 82/- ☐
BASIC ELECTRONIC CIRCUITS 40/- ☐
BASIC INDUSTRIAL ELECTRICITY 40/- ☐
BASIC SYNCHROS & SERVOMECHANISMS 38/- ☐
ALL PRICES INCLUDE POSTAGE

Signature
(If under 21, signature of parent or guardian)

NAME

FULL POSTAL ADDRESS
BLOCK LETTERS BELOW

POST NOW FOR THIS OFFER!

BRADFORD Tel. 25349
10 North Parade. (Half-day Wed.)
BRISTOL 14 Lower Castle
St. (Half-day Wed.) Tel. 22904
BIRMINGHAM 30/31 Gt.
Western Arcade, opp. Snow Hill
Station. CENTRAL 1279. No half-day
DERBY 26 Osmaston Rd.,
The Spot (Half-day Wed.)
Tel. 41361

DARLINGTON 13 Post
House Wynd (Half-day Wednes-
day) Tel.: 68043
EDINBURGH 133 Leith
Street (Half-day Wed.)
Tel.: Waverley 5766
GLASGOW 326 Argyle St.
(No half-day) Tel.: City 4158
HULL 91 Paragon Street
(Half-day Thursday) Tel.: 20505


R.S.C.

HI-FI CENTRES LTD.

MAIL ORDERS TO: 102
Hendon Lane, Bram-
ley, Leeds 13. No C.O.D.
under £1. Terms C.W.O.
or C.O.D. Postage 4/6
extra under £2, 5/9 extra
under £5. Trade supplied.
S.A.E. with enquiries

LEICESTER 32 High Street
(Half-day Thurs.) Tel.: 56420
LEEDS 5-7 County (Mecca)
Arcade, Briggate (No half-day)
Tel.: 28252
LIVERPOOL 73 Dale St.
(No half-day) Tel.: CENTRAL 3573
LONDON 238 Edgware Road,
W2 (Half-day Thurs.) Tel.: PAD
1629. 96 High Holborn, WC1
Tel.: HOL 9874 (Half-day Sat.)

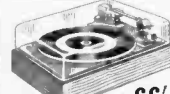MANCHESTER (No half-
day) 60A Oldham St.
Tel.: CENTRAL 2778
MIDDLESBROUGH
106 Newport Road (Half-day
Wednesday) Tel.: 47096
NEWCASTLE UPON TYNE
41 Blackett Street Opp Fenwicks
Store (Half-day Wed.) Tel.: 21469
SHEFFIELD 13 Exchange
Street, Castle Market Bldgs.
(Half-day Thursday) Tel.: 20716



66-

RECORD PLAYING UNITS

Ready for plugging in to Amplifier or Tape Recorder.
RP2 Consisting of Garrard SP25 fitted Goldring
CS90 high compliance ceramic Stereo/Mono
crtge with dmnst stylus, above Only 19½ Gns.
plinth & cover. Normally £25. Carr. 15/-
RP3 As above but with Goldring Lenco GL68 Trans-
cription unit and CS90 Cartridge. Normally
over £33. Terms avail- 26½ Gns.
able both units. Carr. 15/-

SPRING CLEARANCE SALE

Send S.A.E. for list of brand new lines which
must be cleared. Includes Record Playing
Units, Amplifiers, Tape Decks, Cabinets etc.

AUDIOTRINE HI-FI SPEAKER SYSTEMS


Consisting of matched 12in. 12,000 lne.
15 ohm high quality speaker; cross-over
unit and Tweeter. Smooth response
and extended frequency range ensure
surprisingly realistic reproduction.
Standard 10 watt rating. Or 5 Gns.
Senior 20 watt inc. Fane 5 Gns.
122/10 speaker 7 Gns. Carr. 8/9. Carr. 6/9



Tweeters R.A. 3 ohm or 15 ohm 25/9

15 watt HI-FI TRANSISTORISED AMPLIFIER TYPE A15

with integral pre-
amp tone control
stages. Output for 3,
7.5 and 15 ohm spkrs.
Kit includes Printed
Circuit and all parts
type semi-conductors.
Heat sink and full wir-
ing instructions or with printed circuit
fully wired and tested 21/- extra. Frequency
Response: ±1dB 20-20,000 c.p.s. Harmonic
Distortion: 0.1%. Hum and Noise:
-80dB. Sensitivity: 2mV. Bass Control:
-9dB to -14dB at 40 c.p.s. Treble Con-
trol: -8dB to -13dB at 10 Kc/s. Will
operate from batteries giving 34v. Suit-
able Power Pack Kit/47/9 or ready built 68/9

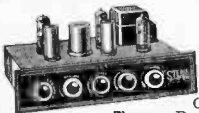

R.S.C. STEREO/TEN HIGH QUALITY AMPLIFIER
A complete set of parts for the construction of a unit giving 5 watts high quality
output on each channel (total 10 watts). Sensitivity is 50 millivolts. Suitable
all crystal or ceramic stereo heads. Ganged Bass and Treble Controls. Provision
is made for use as straight (monaural) 10 watt amplifier. Valve line-up ECC83,
ECC83, EL84, EL84, EZ81. Outputs for 2-ohm speakers. Point to point wiring
diagrams and instructions supplied. Send S.A.E. for leaflet.
Or supplied factory assembled with 12 months' guarantee for 11 Gns. £8.15.0
Terms: Dep. 36/- and 9 monthly payments 25/5 (Total £13.4.9). Carr. 11/6


R.S.C. STEREO 20/HIGH FIDELITY AMPLIFIER

PROVIDING 10/4 WATT ULTRA LINEAR PUSH-PULL OUTPUT ON
EACH CHANNEL. SUITABLE FOR "MIKE", GRAM, RADIO OR TAPE.
Employing valves ECC83, ECC83, ECL86, ECL86, ECL86, EZ81. Frequency
Response: ±2dB 20-20,000 c.p.s. Hum Level: 65dB down. Sensitivity: 5 millivolts
maximum. Harmonic Distortion: (each channel): 0.2%. ★Four-position tone
compensation and Input Selector Switch. ★Stereo/Mono switch.
★Will amplify direct from Tape Heads. ★Neon panel indicator. ★Handsome Perspex Frontplate.
★Separate Bass "Lift" and "Cut" and treble "Lift" and "Cut" controls. Output transformers are high-
quality sectionally wound to required specification. Output matching for 3 and 15 ohm spkrs. on 14 Gns.
each channel. Complete set of parts, point-to-point wiring diagrams and instructions. Carr. 12/6
Or factory assembled, tested and supplied with our usual 12 months guarantee for 19 Gns.
Or Deposit £3 and 9 monthly payments 43/2 (Total £22.4.6). Send S.A.E. for leaflet. Carr. 12/6



R.S.C. TFM1 TRANSISTORISED VHF/FM RADIO TUNER

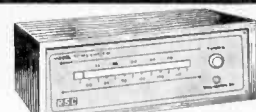Total cost of parts
with detailed wiring
diagrams and instructions.
Carr. 10/- 12½ Gns.
Or factory built
15½ Gns. Or in Teak
finished cabinet as
illustrated 19½ Gns.
Terms: Deposit £5
and 9 monthly pay-
ments 39/-.
Total £22.11.0.



★ High-sensitivity ★ 200-250v. A.C. Mains
operation. ★ Sharp A.M. Rejection.
★ Drift-free reception. ★ Output ample
for any amplifier (approx. 500 m.v.).
★ Simple alignment instructions. ★ Output
available for feeding tuning meter.
★ Output for feeding Stereo Multiplexer.
★ Tuner head using Silicon Planar Tran-
sistors. ★ Designed for standard 80 ohm co-axial input.
Made to visually match our Super 15 and 30 amplifiers and of the same high
standard of performance and reliability. The pre-wired tuning head facili-
tates speed and simplicity of construction. Printed circuitry. Only first grade
transistors and components used. Our latest product giving you the best at
half the cost of comparable units. Stereo Multiplexer available.

AUDIOTRINE HIGH FIDELITY LOUDSPEAKERS


Heavy cast
construction.
Latest high efficiency ceramic magnets.
Dual Cone for extended frequency range.
Plastic treated surround giving
low fundamental resonance. Response
35-20,000 c.p.s. Impedance
3 or 15 ohms. Carr. 5/6.



HF811D 8in. 10 WATT 4 Gns.
HF101D 10in. 12 WATT 5 Gns.
HF100D 10in. 15 WATT 25.15.0
HF121D 12in. 20 WATT 28.15.0
HF157D 12in. 30 WATT 9 Gns.

R.S.C. SUPER 15 HI-FI AMPLIFIER

FULLY TRANSISTORISED 200/250v. A.C. Mains.
OUTPUT 10 WATTS R.M.S. cont. into 15 ohms.
15 WATTS R.M.S. cont. into 3-4 ohms.
Maximum instantaneous Peak power output 28 watts.
PRINTED CIRCUIT CONSTRUCTION.
LATEST MULLARD TRANSISTORS. AD149, AD149,
OC127Z, OC81Z, OC44, OC44, OC81Z, OC44, AC107.
5 POSITION INPUT SELECTOR SWITCH
EQUALISATION to Standard R.I.A.A. and C.C.I.R.
Characteristics for Gram and Tape Heads.
FULL TAPE MONITORING FACILITIES.
SENSITIVITIES: Magnetic P.U. 4 mV. Crystal or
Ceramic P.U. 400 mV. Microphone 4.5 mV. Tape Head
2.5 mV. Radio/Aux or Ceramic P.U. 110 mV.
FREQUENCY RESPONSE: ±2dB 20-20,000 c.p.s.
TREBLE CONTROL: +15dB to -14dB at 10 Kc/s.
BASS CONTROL: +12dB to -15dB at 30 c/s.
HARMONIC DISTORTION at 10 Watts R.M.S. 1,000 c.p.s. 0.25%.
NEGATIVE FEEDBACK: 52dB.
Complete Kit of parts with full constructional details and
point to point wiring diagrams. Carr. 11/-
Supplied factory built 15 Gns. Carr. 12/6. Terms: Deposit 49/- and 9
monthly payments 33/9 (Total £17.12.9). Or fitted in beautiful Walnut or
Teak veneered cabinet as illustrated. 4 Gns. extra.
ALL COMPONENTS ETC. ARE OF A HIGH STANDARD AND
SUPPLIED BY LEADING BRITISH MANUFACTURERS.

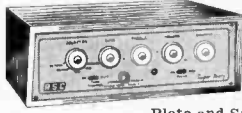


11 Gns.

R.S.C. SUPER 30 STEREO AMPLIFIER

A DUAL CHANNEL VERSION OF THE SUPER
15. Employing Twin Printed Circuits. Close tolerance
Ganged Pots. Matched Components.
CROSS TALK: -52dB at 1,000 c.p.s.
CONTROLS: 5 position Input Selector, Bass Control,
Treble Control, Volume Control, Balance Control, Stereo/
Mono Switch, Tape Monitor Switch, Mains Switch.
INPUT SOCKETS (Matched Pairs). (1) Magnetic P.U.
(2) Ceramic or Crystal P.U. (3) Radio/Aux. (4) Tape Head/
Microphone. Operation of the Input Selector Switch
assures appropriate equalisation.
Rigid 18 s.w.g. Chassis. Size approx. 12in. Wide, 8in. High
and 8in. Deep. Neon Panel Indicator. Attractive Facia
and Spun Silver Matching Knobs. Above facilities, etc., except for
Ganging and Balance Control, apply also to Super 15.
THESE UNITS ARE EMINENTLY SUITABLE FOR USE WITH
ANY MAKE OF PICK-UP OR MICROPHONE (Crystal, Ceramic,
Magnetic, Moving Coil, Ribbon). CURRENTLY AVAILABLE
SPEAKER SOUND QUALITY CAN BE OBTAINED BY
USING WITH FIRST RATE ANCILLARY EQUIPMENT. All
required parts, point to point wiring diagrams and detailed 18½ Gns.
instructions. Carr. 13/9
Unit factory built 25½ Gns. or deposit 83/9 and 9 monthly payments 56/9
(Total £29.14.6). Fitted cabinet as Super 15 29½ Gns. Carr. 15/- or Deposit
£4.14.9 and 9 mthly paymts 65/10 (Total £34.7.3). Send S.A.E. for leaflet.

AUDIOTRINE HI-FI TAPE RECORDER KIT

REALISM AT INCREDIBLY LOW COST: S.A.E. for leaflet.
CAN BE ASSEMBLED IN AN HOUR.
ONLY 4 PAIRS OF SOLDERED JOINTS PLUS MAINS.
Incorporating the latest Magnavox Tape Deck, The Audiotrine High Quality Tape Amplifier with switched equalisation for each of 3 speeds, High Flux P.M. Speaker, empty Tape Spool, a Reel of Best Quality Tape and a handsome Portable Cabinet of latest styling finished dark grey leathercloth. Size 14 1/2 x 8 1/2 in. and circuit. Purchased separately would total approx. £34. Performance equal to units in the £50-£60 class. Deposit **26 1/2 Gns.** 4 kns. and 9 monthly payments 59/6 (Total 291 kns.)
4 Track Model 3 kns. extra. Carr. 19/6

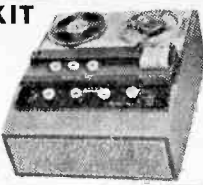

LINEAR TAPE PRE-AMPLIFIER. Type LP1 Switched Equalisation. Positions for Recording at 11in., 3 1/2in., 7 1/2in. per sec., and Playback. EM54 Recording Level Indicator. Designed primarily as the link between a Magnavox Tape Deck and Hi-Fi amplifier suitable most Tape Decks. Terms available. **10 1/2 Gns.**



R.S.C. 4/5 watt A5 HIGH GAIN AMPLIFIER

A highly-sensitive 4-valve quality amplifier for the home, small club, etc. Suitable for all crystal or ceramic P.U. heads and practically all "mikes". Separate Bass and Treble controls giving "lift" and "cut". Hum level 70dB down. Negative Feedback 15dB. Reserve power supply 300v 25 m.a., 6.3v 1.5 a. for Radio Tuner or Tape Pre-amp. For A.C. mains 200-250v. Speaker output 3 ohms. Complete in every detail with fully punched enameled chassis, point-to-point wiring diagrams and instructions. Or assembled ready for use 6 kns. plus 5/9 carr. **£4.17.9**

R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Pull high output, with Pre-amp./Tone Control Stages. Performance figures equal to most expensive amplifiers available. Hum level -70dB. Frequency response +3dB 30-20,000 c/s. Specially designed sectionally wound ultra linear output transformer with 807 output valves. All first grade components. Valves EF86, EF86, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls. Sensitivity 12 millivolts so that any kind of Microphone or Pick-up is suitable. Designed for Clubs, Schools, Theatres, Dance Halls or Outdoor Functions, etc. For use with Electric Organ, Guitar, String Bass, etc. Gram. Radio or Tape. Reserve L.T. and H.T. for Radio Tuner. Two inputs with associated volume controls so that two separate inputs such as Gram and "Mike" can be mixed. 200-250v. 50c/s A.C. mains. For 3 and 15 ohm speakers. Complete kit of parts **12 Gns.** Carr. Fully punched chassis, point to point wiring diagrams and instructions. Fully assembled factory built with EL34 output valves. 12 months guarantee for 15 kns. If required perforated cover with carrying handles can be supplied for 21/-, Send s.a.e. for leaflet. **TERMS:** Deposit 48/- and 9 monthly payments of 33/7 (Total £17.10.3).

JASON VHF/FM TUNER Complete kit with valves. **£6.19.11**
MINIATURE TRANSISTORISED VHF/FM TUNER Battery operated. In plastic case complete with Telescopic Aerial. **£6.19.11**

R.S.C. A11 HIGH FIDELITY 12-14 WATT AMPLIFIER

PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP Two input sockets with associated controls allow mixing of "mike" and gram, etc. etc. High sensitivity. Valves ECC83, ECC83, EL84, EL84, GZ34. High quality sectionally wound output transformer specially designed for Ultra Linear operation and reliable small condensers of current manufacture. **INDIVIDUAL CONTROLS FOR BASS AND TREBLE.** Frequency response +3dB 30-20,000 c/s. Six negative feedback loops. Hum level -80dB. SENSITIVITY 23 millivolts. Suitable for Crystal or Ceramic P.U.s. all types "mikes" and pick-ups, with the very best designs. For Musical Instruments such as String Bass, Electronic Guitars, etc. Reserve Power provides 300v. 30mA. and 6.3v. 1.5a. for Radio Tuner or Tape Pre-amp. Size approx. 12 x 9 x 7 1/2 in. For A.C. mains 200-250v. 50 c.p.s. Output for 4 and 15 ohm speakers. Kit complete to last nut. Chassis **£8.15.0** fully punched. Full instructions and point-to-point wiring diagrams for factory built **£11.15.0**. Metal cover with 2 handles available for 21/-. **TERMS ON CARR. 11/6** ASSEMBLED UNITS. Deposit 36/6 and 9 monthly payments of 25/9 (Total £13.8.3). Send S.A.E. for illustrated leaflet of Cabinets, Speakers, Mikes, etc.

R.S.C. BASS-REGENT 50 WATT AMPLIFIER

AN EXCEPTIONALLY POWERFUL HIGH QUALITY ALL-PURPOSE UNIT For lead, rhythm, bass guitar and all other musical instruments. For vocalists, gram, radio, tape, and general public address.

★ **UNUSUALLY POWERFUL LOUSPEAKER COMBINATION** consisting of a FANE HIGH FLUX 15in. 30 watt unit PLUS a FANE 12in. 20 watt unit with extended frequency response. ★ 4 Jack Inputs and two Volume Controls for simultaneous use of up to 4 pick-ups or "mikes". ★ Cabinets covered in two-tone Rexine/Vynair with gold trimming. Fitted carrying handles. ★ Separate Bass and Treble Controls giving "lift" and "cut". Send S.A.E. for leaflet. Or call at one of our many branches and compare the Bass-Regent with units at three times the cost. Carr. 30/- Or deposit £7.17.6 and 9 monthly payments of £5.10.10. (Total 55 gns.)

B20 MULTI-PURPOSE AMPLIFIER especially suitable for Bass Guitar

Incorporating massive 15in. high flux loudspeaker. Rating 25 watts. Individual bass and treble controls. Two jack inputs separately controlled. Substantial cabinet attractively finished in Rexine and Vynair. Size approx. 24 x 21 x 11in. Send S.A.E. for leaflet. **29 1/2 Gns.** Or Deposit £4.14.6 and 9 monthly payments of 66/- (Total £24.6.6). Carr. 17/6

LINEAR TREMOLO PRE-AMP UNIT

Suitable for use with any of our Amplifiers. Controls are Speed (frequency of interruptions). Depth (for heavy or light effect). Volume and Switch. **4 Gns.**

R.S.C. BATTERY/MAINS CONVERSION UNITS

Type BM1. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2 1/2 in. approx. Completely replaces batteries supplying 1.5v. and 90v. where A.C. mains 200-250v. 50 c/s is available. Complete kit with diagram 47/9 or ready for use 59/11.

SELENIUM RECTIFIERS F.W. (Bridged)

All 6/12 v. D.C. output. Max A.C. input 18 v. 1 a. 3/11. 2 a. 6/11. 3 a. 9/9. 4 a. 12/9. 6 a. 15/9.

HEAVY DUTY SELENIUM RECTIFIERS

12v. 15 amps. F.W. (Bridged). **19/9** Only

G15 15 WATT AMPLIFIER for Lead or Rhythm Guitar, Vocal Groups, etc.

High-fidelity output. Separate bass and treble controls. Twin separately controlled inputs so that two instruments giving "mike" and pick-ups can be used at the same time. Heavy Duty 12in. 20 watt Speaker. Cabinet covered in attractive Rexine/Vynair. Size 18 x 18 x 8 1/2 in. Deposit 3 kns. **19 1/2 Gns.** Carr. and 9 monthly payments of 43/7 (Total £23.15.3). S.A.E. for leaflet.

CLEARANCE SALE!

WATKINS COPYCAT ECHO UNITS 19 1/2 Carr. 17/6
Listed £38.10.0. Brand new
VON and LINEAR GUITAR AMPLIFIERS. Various models at half list price.

POWER PACK KIT

Consisting of Mains transformer. Metal Rectifier. Electrolytics. smoothing choke, chassis and enclosure. 200/250v. A.C. **22/11** mains. Output 250v. 60mA 6.3v. 2a Supplied with case in lieu of chassis 26/11. Or assembled 39/11.

HEAVY DUTY BATTERY CHARGER KITS 6/12 v.

Consisting of Mains Trans. 200-250 v. Rectifier. Ammeter. Variable Charge Rate Selector. Panels. Plugs. Fuses and Holders. Fully punched, etc. in case and circuit. **4a 49/11 6a 69/11**
Or assembled ready for use 10/- extra.

LONDON-NEWCASTLE

New branches now open - see addresses

R.S.C. COLUMN SPEAKERS

Covered in two-tone Rexine/Vynair. Ideal for vocalists and Public Address. 15 ohm matchline. Type C58. 15-20 watts. Fitted five 8in. high flux speakers. Overall size approx. 42 x 10 x 5 1/2 in. Or Deposit 44/- and 9 monthly pmts 31/5 (Total £16.6.9) **14 Gns.** Carr. 10/-

Type C412. 40 watts. Fitted four 12in. 12,000 line 10 watt speakers. Overall size 56 x 14 x 9 in. approx. Carr. 15/- Or Deposit £3.11.0 and 9 monthly payments of 46/7 (Total £24.10.3). **21 Gns.**

30 WATT HI-FI AMPLIFIER

for Guitar, Vocal or Instrumental Group
A 4 Input. 2 volume control Hi-Fi unit with Separate Bass and Treble controls. Latest valves. Strong Rexine covered cabinet with carrying handles. Attractive black/gold perspex fascia. For 200-250v. A.C. mains. For 3 or 15 ohm speaker- **17 Gns.** Carr. 12/6 for leaflet. Deposit £3 and 9 monthly payments of 37/5 (Total £19.16.9).

12in. HIGH QUALITY L'SPEAKERS

In teak veneered cabinets. 16 Watt Model. Gauss 12,000 lines. 3 or 15 ohms. Carr. 7/6 **£4.19.11**
20 Watt Model. 15 ohm. Size 18x18x10in. Gauss 12,000 lines. Carr. 10/6 **£7.19.11**
Terms available on both.

FANE HEAVY DUTY HI-FI SPEAKERS 5 Gns.

12in. 20 watt. Type 122/10. Carr. 5/9

LOUDSPEAKERS

Limited number at fraction of list price 15 ohms. impedance. Brand new, guaranteed. **12in. HEAVY DUTY 30 watts 7 Gns.** Carr. 12/6 Normally £12 approx.
15in. EXTRA HEAVY DUTY 40-50 watts 11 Gns. Carr. 17/6

Massive units with 3in. Diam. Pole Pieces. Terms available. (Normally appr. £19)

R.S.C. GRAM AMPLIFIER KIT. 3-4 watts output.

Negative feedback. Controls: Vol., Tone and Switch. Mains operation 200-250v. A.C. Fully isolated chassis. Circuit, etc. supplied. **10 49/11.**

HIGH FIDELITY 12in. 10 WATT SPEAKERS 59/11

Flux Density 12,000 lines. Impedance 3 or 15 ohms.

TRANSISTOR SALE

Mullard OC71, OC72, OC81, 2/11, OC48, OC45, 3/11, OC75, 7/9, AF17 6/9. Post 6d. for 3.

R.S.C. MAINS TRANSFORMERS

FULLY GUARANTEED. Interleaved and Impregnated. Primaries 200-250v. 50 c/s. Screened. **MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 in.**
250v. 60mA. 6.3v. 2a. **14/11**
250-0-250v. 60mA. 6.3v. 2a. **15/11**
FULLY SHROUDED UPRIGHT MOUNTING
250-0-250v. 60mA. 6.3v. 2a. 0-5-6.3v. 2a. **19/9**
250-0-250v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. **33/9**
300-0-300v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. **33/9**
300-0-300v. 130mA. 6.3v. 4a c.t., 6.3v. 1a. **41/9**
For Mullard 510 Amplifier
350-0-350v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. **33/9**
350-0-350v. 150mA. 6.3v. 4a. 0-5-6.3v. 3a. **42/9**
425-0-425v. 200mA. 6.3v. 4a. c.t., 5v. 3a. **37/9**
425-0-425v. 200mA. 6.3v. 4a. 6.3v. 4a. 5v. 3a. **69/9**
450-0-450v. 250mA. 6.3v. 4a. c.t., 5v. 3a. **79/9**

TOP SHROUDED DROP-THROUGH TYPE

200-0-250v. 70mA. 6.3v. 2a. 0-5-6.3v. 2a. **19/9**
250-0-250v. 100mA. 6.3v. 3.5a. **21/9**
250-0-250v. 100mA. 6.3v. 2a. 6.3v. 1a. **22/9**
350-0-350v. 80mA. 6.3v. 2a. 0-5-6.3v. 2a. **23/9**
250-0-250v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. **32/9**
300-0-300v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. **32/9**
300-0-300v. 130mA. 6.3v. 4a. 0-5-6.3v. 1a. **39/9**
Suitable for Mullard 510 Amplifier
350-0-350v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. **32/9**
350-0-350v. 150mA. 6.3v. 4a. 0-5-6.3v. 3a. **32/11**

FILAMENT or TRANSISTOR POWER PACK Types

6.3v. 1.5a 6/9, 6.3v. 2a 7/9, 6.3v. 3a 9/9, 6.3v. 6a 19/9, 12v. 1a 8/9, 12v. 3a or 24v. 1.5a 19/9, 0-9-18v. 1a. 15/9, 0-25-35-42v. 2a 27/9.

CHARGER TRANSFORMERS 0.9-15v. 1a. 13/11

21a, 16/11, 3a, 18/11, 6a, 21/11, 6a, 25/11, 8a, 31/11

AUTO (Step Up) Step Down TRANSFORMERS

0.9-10-20v. 200-250-225v. 100mA. 10-12 watts. 14/9
150 watts. 29/11. 250 watts. 49/9. 500 watts. 99/9

OUTPUT TRANSFORMERS

Standard Pentode 3,000 Ω or 7,000 Ω to 3 Ω **7/9**
Push-Pull 8 watts EL84 to 3 Ω or 15 Ω **11/9**
Push-pull 10 watts 6V8 ECL86 to 3, 5, 8 or 15 Ω **21/9**
Push-pull EL84 to 3 or 15 Ω 10-12 watts **37/9**
Push-pull Ultra Linear for Mullard 510. **35/9**
Push-pull 15-18 watts, sectionally wound 6L6, KT66, etc., for 3 or 15 Ω **29/9**
Push-pull 20 watt high quality sectionally wound, EL34, 6L6, KT66, etc., to 3 or 15 Ω fully shrouded **55/9**

SMOOTHING CHOKE

150 mA, 7-10 Ω , 250 Ω 12/9.
100 mA, 10 Ω , 200 Ω 9/11.
80 mA, 10 Ω , 350 Ω 7/9.
60 mA, 10 Ω , 400 Ω 4/11.



Why

NOT BUILD ONE OF OUR PORTABLE TRANSISTOR RADIOS...

FIRST FOR PERFORMANCE, QUALITY & PRICE!

BACKED BY OUR SUPER AFTER SALES SERVICE

"A wonderful range of transistor radios using first grade components guaranteed results."

NEW ROAMER SEVEN Mk IV

7 WAVEBAND PORTABLE OR CAR RADIO

Amazing performance and specification • Now with **PHILCO MICRO-ALLOY R.F. TRANSISTORS**

FULLY TUNABLE ON ALL WAVEBANDS

• 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves. Trawler Band and three Short Waves to approx. 15 metres. Push-pull output for room filling volume from rich toned 7 x 4 in. speaker. Air spaced ganged tuning condenser. Ferrite rod aerial for M. & L. Waves and telescopic aerial for S. Waves. Real leather-look case with gill trim and shoulder and hand straps. Size 9 x 7 x 4 in. approx.


The perfect portable and the ideal car radio. (Uses PP7 batteries, available anywhere.)

• **EXTRA BAND FOR EASIER TUNING OF LUXEMBOURG, etc.**

Total cost of parts now only


£5.19.6

P. & P. 5/6

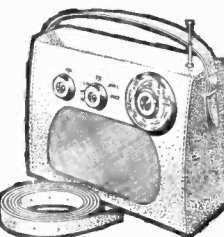

Parts Price List and easy build plans 3/- (Free with kit)

NEW MELODY MAKER SIX

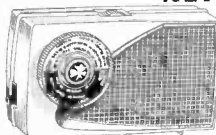


★8 stages. Six transistors and two diodes. Covers Medium and Long Waves and Extra Band for **EASIER** tuning of LUXEMBOURG etc. Top grade 3 in. Loudspeaker for quality output. Two R.F. stages for extra boost. High 'Q' 6 in. Ferrite Rod Aerial. Approx. 350 Milliwatts push pull output. Handsome pocket size case with gill fittings. Size 6 1/2 x 3 1/2 x 1 1/2. (Uses long-life PP6 battery). Carrying strap 1/6 extra.

This amazing receiver may be built for only **£3.9.6**

P. & P. 3/6. Parts price list and easy build plans 2/- (Free with kit).

QUICK CHECK TRANSISTOR TESTER.

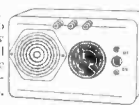Checks gain of R.F. and Audio Transistors. Also checks for noise level and studs. All parts ready to be assembled in attractive grey case with red grille, complete with Dial, Knobs, and Dynamic speaker. Simple assembly instructions free with set of parts. 29/6. P. & P. 2/6.



THE SIG-GEN. A versatile Signal Injector. Something no constructor should be without. The ingenious device generates an audible signal through the Audio and R.F. ranges. With variable output. Telescope Probe. Pocket size slim line case measures 4 1/2 x 3 1/2 x 3/4 in. Complete set of parts with full instructions. 19/6. P. & P. 2/-.

NEW TRANSONA FIVE

Now with 3 in. Speaker!

"Home, Light, A.F.N., Lux. all at good volume." G.P., Durham.

• 7 stages—5 transistors and 2 diodes

Fully tunable over Medium and Long Waves and Trawler Band. Incorporates Ferrite rod aerial, tuning condenser volume control, new type fine tone super dynamic 3 in. speaker, etc. Attractive case. Size 6 1/2 x 4 1/2 x 1 1/2 in. with red speaker grille. (Uses 1289 battery, available anywhere.)

Total cost of all parts now only

42/6

P. & P. 3/6. Parts Price List and easy build plans 2/- (Free with kit)



POCKET FIVE Now with 3 in. Speaker!

• 7 stages—5 transistors & 2 diodes

Covers Medium and Long Waves and Trawler Band, a feature usually found in only the most expensive radios. On test Home, Light, Luxembourg and many Continental stations were received loud and clear. Designed round supersensitive Ferrite Rod Aerial and fine tone 3 in. moving coil speaker. Built into attractive black and gold case. Size 5 1/2 x 1 1/2 x 3/4 in. (Uses 1289 battery available anywhere.)

Total cost of all parts now only

42/6

P. & P. 3/-

Parts Price List and easy build plans 1/6 (Free with kit)



STOP PRESS!

Pocket 5 med. and long wave version, with miniature speaker.

29/6

P. & P. 3/-

NEW ROAMER SIX

NOW, WITH **PHILCO MICRO-ALLOY R.F. TRANSISTORS**

• 6 WAVEBAND ! !

• 8 stages—6 transistors and 2 diodes

Listen to stations half a world away with this 6 waveband portable. Tunable on Medium and Long Waves. Trawler Band and two Short Waves. Sensitive Ferrite rod aerial and telescopic aerial for short waves. Top grade transistors, 3 in. speaker, handsome case with gill fittings. Size 7 1/4 x 5 1/4 x 1 1/2 in. (Carrying strap 1/6 extra.)

★ **EXTRA BAND FOR EASIER TUNING OF LUXEMBOURG, ETC.**

Total cost of all parts now only **£3.19.6**

P. & P. 3/6

Parts Price List and easy build plans 2/- (Free with kit)



TRANSONA SIX

• 8 stages—6 transistors and 2 diodes


This is a top performance receiver covering full Medium and Long Waves and Trawler Band. High-grade 3 in. speaker makes listening a pleasure. Push-pull output. Ferrite rod aerial. Many stations listed in one evening including Luxembourg loud and clear. Attractive case in grey with red grille. Size 6 1/2 x 4 1/2 x 1 1/2 in. (Uses PP4 battery available anywhere). Carrying strap 1/- extra.

Total cost of all parts now only

59/6

P. & P. 3/6

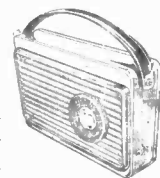Parts Price List and easy build plans 1/6 (Free with kit)



MELODY SIX


• 8 stages—6 transistors and 2 diodes

Our latest completely portable transistor radio covering Medium and Long Waves. Incorporates pre-tagged circuit board, 3 in. heavy duty speaker, top grade transistors, volume control, tuning condenser, wave change slide switch, sensitive 6 in. Ferrite rod aerial. Push-pull output. Wonderful reception of BBC, Home and Light, 208 and many Continental stations. Handmade leather-look pocket size case, only 6 1/2 x 3 1/2 x 1 1/2 in. approx. with gill speaker grille and supplied with hand and shoulder straps.

Total cost of all parts now only **£3.9.6**

P. & P. 3/6

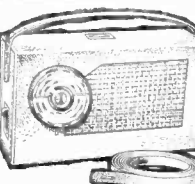Parts Price List and easy build plans 2/- (Free with kit)



SUPER SEVEN

• 9 stages—7 transistors and 2 diodes


Covers Medium and Long Waves and Trawler Band. The ideal radio for home, car, or boat can be fitted with carrying strap for outdoor use. Completely portable—has built-in Ferrite rod aerial for wonderful reception. Special circuit incorporating 2 R.F. Stages, push-pull output, 3 in. speaker (will drive large speaker). Size 7 1/2 x 5 1/2 x 1 1/2 in. (Uses 9V battery, available anywhere.)

Total cost of all parts now only

£3.19.6

P. & P. 3/6

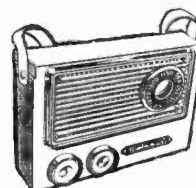Parts Price List and easy build plans 2/- (Free with kit)



Callers side entrance
Barratts Shoe Shop.

RADIO EXCHANGE CO.

Open 9—5 p.m.
Saturday 9—12-30 p.m.

61 HIGH STREET, BEDFORD Telephone: Bedford 52367

NEW MART

Dept: PW4
33 WITHY GROVE, MANCHESTER 4.
Telephone: DEAnsgate 7710

FREE GIFT OFFER

OF A BRAND NEW WORLD FAMOUS EMI FISK SOLARISCOPE VALUE £22.00, WITH EVERY ORDER VALUE 25 AND OVER. THIS UNIQUE INSTRUMENT WHICH IS A BOON TO SHORT WAVE LISTENERS CLEARLY SHOWS THE AREAS OF DAYLIGHT AND DARKNESS ALL OVER THE EARTH AT ANY GIVEN HOUR.

MINI-MOTORS 3v to 4.5v operation. Ideal for mini-racing cars, models and toys. "Large" (1 1/2 x 7/16 x 1 1/2 in.) 3/11d. Medium (1 x 7/8 x 1 1/4 in.) 3/6d. Small (7/16 x 1 x 1 in.) 3/3. P. & P. 9d. each.

BRAND NEW! Why use Sapphire Stylus in your record player when at very little extra cost you can have a first grade

GENUINE DIAMOND STYLUS

Price: 7/11d. plus 6d. P. & P. Available as replacements for the following popular types only at present: BSR/TCS L.P.; BSR/TCS Stereo; BSR/TCS L.P. Stereo; Colibro Studio "C"; L.P. Stylus; Garrard GC8 L.P.; Aeos GP 65/67 L.P.; Ronette RF40 L.P.; Garrard GC21 P. All fully guaranteed.

SPEAKERS. A few items from our range: 12in. Round high quality British fitted tweeter cone. 6 watts—available in 3Ω or 15Ω. Wonderful value at 29/6d., P. & P. 3/6d. 12in. Round R & A. 3Ω. 25/6d., P. & P. 3/6d. 13 x 8in. Guitar Special E.M.I., 15Ω, 20 watt. 28.5.0d., Carr. paid. 3in. Round, best British make, 8Ω, 8/6d., P. & P. 1/6d.

TWEETER. 2 1/2in. Black plastic cone, round on Square Frame, E.M.I. 3Ω. 12/6d. plus 1/6d. P. & P. P.A. HORN speaker, 8 1/2, 15 watt, 9 x 9in. Swivel mounting brackets, 85.5.0. Carr. Paid. Many other sizes and types available from 2in.

REMOTE CONTROL TWO-IN-ONE EXTENSION SPEAKER. In addition to providing an extension speaker, two independent knobs control volume in extension speaker and also in your radio, T.V., Hi-Fi, gram, etc. Stereo effect if desired. Complete with 25ft. multistrut cable and full instructions. Easily connected. Handsome cream finish—3 1/2 x 3 x 1 1/2in. Complete 27/6d. P. & P. 2/6d.

MICROPHONES. LAPEL/HAND MIKE—1 1/2in. dia. Lapel Clip, ideal for tape recording. With lead. Very sensitive. 7/6. P. & P. 1/2.

CRYSTAL HAND MIKE—Robust and sensitive. Cream Plastic Case. Just the thing for tape recorders. 8/6. P. & P. 1/6.

ACOS MIC 40—World famous Desk Mike. 13/9 + P. & P. 1/3

ACOS MIC 45—Splendid Curved Hand Grip Crystal Mike. 14/6 + P. & P. 1/6

ACOS MIC 60—"Stick" Type Crystal Mike. 18/6 + P. & P. 1/6

ACOS Round Crystal Inserts. 1in. dia. 0/6; 1 1/2in. dia. 7/6. P. & P. on either. 6d.

DYNAMIC HAND/DESK TYPE. 50KΩ with cable and plug to suit most recorders, etc. 18/6. P. & P. 1/3.

DYNAMIC HEAD. 50KΩ for use with stand. Most attractive, used by many professionals and groups. 48/- P. & P. 2/6.

TELESCOPIC FLOOR STAND. HEAVY BASE. Standard thread. Suits above or any other mike. 48/6. Carr. & Pkg. 2/6.

TELEPHONE PICK-UP COIL. For recording or amplifying both sides of telephone conversation. Ruction cup fitting to telephone. With lead. 7/6. P. & P. 1/2.

INTER-COMM. DE-LUXE 2 WAY. Ideal for offices, work-shops, theatres, etc. Highly efficient, safe BABY ALARM. No mains—works off PP3 battery, which lasts for months, obtainable everywhere. Buzzer call system, complete with lead, plugs, battery, in handsome carton. 63/- P. & P. 2/6d.

PICK-UP ARM. Lightweight, with T/O crystal cartridge and stylus for L.P. and 78 R.P.M. records on base with rest 27/6d. P. & P. 2/6d.

4 TRANSISTOR 3W AMPLIFIER. Size 2 1/2 x 2 1/2 x 1 1/2, 3, 8 or 15Ω output, 9 volt battery operated. Highly sensitive. Price (less battery) 52/6d. P. & P. 1/6d.

VERNIER DIALS—At standard 1in. spindle—approx. 8:1 ratio. Marked 0/100 through 180°. Small round 2in. dia. 10/6d. Large 3in. dia. 12/- Post on either 1/2.

MAINS TRANSFORMERS: 230/0/230 500mA, 6v and 6.3v at 2A Chassis MTG. 230v or 110V in Size 1 1/2 x 3 1/2 x 2 1/2in. 21/- ea. P. & P. 2/-

VOLTAGE DROPPING TRANSFORMER 230V/0/11N, 3.5v, 9v and 17v out at 4 amps. Many uses. Ideal for Battery Chargers etc. 3 x 2 1/2 x 2 1/2in. 22/6d. each. P. & P. 2/6d.

RECORD PLAYER DECKS. GARRARD. All latest models. All fitted Mono Cartridge.

SRP12 3 speed single-player ... 24.5.0

SP25 De Luxe 4 speed single-player 29. 9.6 Stereo 10/- extra. Carr. Paid.

MODEL 1000 Speed Auto-Change ... 18.19.6 P. & Pkg. all models 7/6d.

AT8 MKIIA 4 speed De Luxe Auto-change 28.19.6 (Except SRP12, 5/-)

MODEL 3000 4 speed Auto-Change ... 28.10.0 but price inc. free gift.

PICK-UP CARTRIDGE REPLACEMENTS

STANDARD FIXING FOR MOST RECORD-PLAYER ARMS. ALL TURN-OVER TYPES WITH STYLUS FOR L.P. & 78 RPM.

ACOS GP/67-2 Mono ... 12/6 each

ACOS GP/91-1 Mono de luxe ... 17/6 each

ACOS GP/73-2 Stereo ... 25/- each

Postage & Packing 9d. each

Finest Quality British made MYLAR Recording Tape. Fully Guaranteed.

3in. 225 Message ... 5/- 5 1/2in. 1200ft. Long Play ... 12/6

5in. 600 Standard Play ... 8/6 7in. 1800ft. Long Play ... 19/6

5 1/2in. 850 Standard Play ... 11/6 5in. 1200ft. Double Play ... 15/-

7in. 1200 Standard Play ... 14/6 5 1/2in. 1800ft. Double Play ... 22/6

5in. 900ft. Long Play ... 11/6 7in. 2400ft. Double Play ... 25/-

P. & P. 1/- per reel. Four reels and over post paid. N.B.—MYLAR based recording tape is of infinitely superior quality and far stronger than Acetate base tape.

MULTI-TEST METER. Pocket size—4 1/2 x 3 1/2 x 1 1/2in. 20,000Ω p.volt.

D.C. Volts (20,000 Ω P.V.) 0.5/25/250/500/2500 D.C. Current 0-50 microamp. 2.5mA/250mA.

A.C. Volts (10,000 Ω P.V.) 0.5/10/50/100/500/1000 Resistance 0.6kΩ-0.6 megohms Capacity 10pF-0.001μF/0.001μF to 1μF. Decibel: -20 to +22dB.

COMPLETE with batteries, instructions, leads 72/6d. P. & P. 1/6d.

Other types available from 37/6d. Details on request.

TRANSISTORS: Some popular types from our range:

OC44 & OC45 8/6d. ea. OC71 2/6d. OC72 3/6d. OC81 & OC81D 3/- ea. OC169 3/6d. OC170 3/6d. AF117 4/- OC26 7/6d. GET 8 5/8. General purpose (Approx. OC71) 1/- ea. Postage 6d. up to 3. Over 12 sent P. & P. paid.

R.F. FIELD INDICATOR. Ideal for use with radio controlled models. Checks radiation from existing antennas. Tunes 1 to 250 Mc in 5 bands. Sensitive 200mA meter movement, 5 section plug-in aerial. Phone jack and crystal earpiece for monitoring. No battery required. Powerful magnet for attaching to metal surfaces. Complete with instructions. 47/6d. P. & P. 2/6d.

TERMS. Cash with order—No C.O.D. Orders totalling £5 and over sent carriage paid (excepting Record player decks and Transceivers where carriage is shown). Guaranteed money refunded if goods returned perfect within 7 days of despatch.

REMEMBER THE NOVEL FREE GIFT EXCLUSIVE TO US!

Callers welcome—Very many more lines to choose from. Open 9.30 a.m.-6 p.m. Mon.-Sat.

TECHNICAL TRAINING

in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- Institution of Electronics & Radio Engineers (Brit.I.R.E.)
- C. & G. Telecommunication Techns' Certs.
- C. & G. Supplementary Studies
- R.T.E.B. Radio/T.V. Servicing Certificate
- Radio Amateurs' Examination
- P.M.G. Certs in Radiotelegraphy
- General Certificate of Education, etc.

Examination Students coached until successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, signal generator and multimeter—all under expert tuition. Transistor Portable available as separate course.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 171, Intertext House, Parkgate Road, London, S.W.11

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam.)

NAME

ADDRESS


4.67

INTERNATIONAL CORRESPONDENCE SCHOOLS

LASKY'S RADIO

FOR THE FINEST VALUE AND TO HOME CONSTRUCTORS

TRANSISTOR PORTABLES

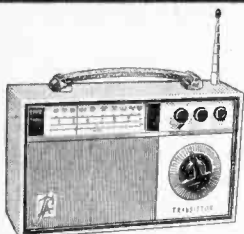

THE SKYROVER De Luxe

7 transistor plus 2 diode superhet, 6 wave-band portable receiver covering the full Medium Waveband and Short Waveband 31-94M and also 4 separate switched band-spreading ranges, 13M., 16M., 19M. and 25M., with Band Spread Tuning for accurate Station Selection. The coil pack and tuning heart is completely factory assembled, wired and tested. The remaining assembly can be completed in under three hours from our easy to follow, stage by stage instructions. Superbet, 470 Kc/s. All Mullard Transistors and Diodes. Uses 4 U2 batteries. 5in. Ceramic Magnet P.M. Speaker. Easy to read Dial Scale, 500 MW Output. Telescopic Aerial and Ferrite Rod Aerial. Tone Circuit is incorporated, with separate Tone Control in addition to Volume Control. Tuning Control and Waveband Selector. In a wood cabinet, size 11½ x 6½ x 3in. covered with a washable material, with plastic trim and carrying handle. Car aerial socket fitted.

Can now be built for **£8.19.6** Post 6/- extra
H.P. Terms: 60/- deposit and 11 monthly payments of 12/9. Total H.P.P. £10.0.8.
Four U2 batteries 3/4 extra.

LONG WAVEBAND COVERAGE IS NOW AVAILABLE FOR THE SKYROVER

A simple additional circuit provides coverage of the 1100/1950M. band (including 1500M. Light programme). This is in addition to all existing Medium and Short wavebands. All necessary components with construction data.

Only **10/-** extra Post Free.
This conversion is suitable for receivers that have already been constructed.
Data 2/8 extra; refunded if you purchase the parcel.
All components available separately.

SINCLAIR SUPER MINIATURE KITS

	Write for details of Package Deals
THE MICRO-6 miniature radio only 1½" x 1½" x 1½"	£2 19 6
THE MICRO-FM (tuner/receiver)	£5 19 6
THE X-20 20 watt P.W.M. amplifier	£7 19 6
Available ready built, tested and guaranteed	£9 19 6
THE Z-12 12 watt amp. and pre-amp., fully built	£4 9 6
PZ-3 power pack for Z-12	£3 19 6
STEREO 25 Pre-amplifier control unit, fully built	£3 19 6


TAPE RECORDERS

MAGNAVOX 363 TAPE DECKS

The very latest 3 speed model—1½, 3½, 7½ ips, available with either 1 track or 2 track head. Features include: pause control; digital counter; fast forward and rewind; new 4 pole fully screened induction motor, interlocking keys. Size of top plate 13½ x 11in. x 5½in. deep below unit plate. For 200/250v A.C. mains, 50 cps operation. New, unused and fully guaranteed.

Lasky's Price 1 track model **£10.10.0**
Lasky's Price 2 track model **£13.9.6**

Carriage and Packing 7/6 extra.

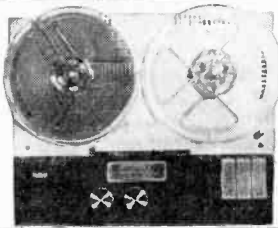

NEW MARTIN TAPE RECORD/REPLAY AMPS.

Now available from stock—for use with the Magnavox 363 Tape Deck.
1 track model..... LASKY'S PRICE **£14.19.6** Carriage and
2 track model..... LASKY'S PRICE **£15.19.6** Packing 4/6 extra.
Optional extra: Control panel escutcheon to take deck and amplifier controls.
LASKY'S PRICE 12/6 Post & Packing 2/6.

INTERNATIONAL TAPE

Famous American Brand—Fully Guaranteed

3in. Message tape, 150ft.	2 6	5½in. Long play, 1200ft. Acetate	12 6
3in. Message tape, 225ft.	3 9	5½in. Standard play, 850ft. PVC	11 6
3in. Message tape, 300ft.	7 6	5½in. Long play, 1200ft. Mylar	15 0
3½in. Triple play, 600ft. Mylar	10 0	5½in. Triple play, 2400ft. Mylar	45 0
4in. Triple play, 900ft. Mylar	17 6	7in. Standard play, 1200ft. Acet.	12 6
5in. Double play, 1200ft. Mylar	15 0	7in. Standard play, 1200ft. Mylar	12 6
5in. Long play, 900ft. Acetate	10 0	7in. Long play, 1800ft. Mylar	19 6
5in. Standard play, 600ft. PVC	8 6	7in. Double play, 2400ft. Mylar	25 0
5in. Triple play, 1800ft. Mylar	35 0	7in. Long play, 1800ft. Acetate	15 0
5½in. Double play, 1800ft. Mylar	22 6	7in. Triple play, 3600ft. Mylar	50 0

P. & P. 1/- extra per reel. 4 reels and over Post Free

MICROPHONES

EXPORT FM WIRELESS MICROPHONES THE TTC MODEL B4002

Highly sensitive—suitable for either static or mobile use. Signals can be picked up by any FM radio or tuner which receives frequencies between 96-104 Mc/s over several hundred yards. Size only 3 x 2½ x 1in. (in leather case). Operates on one P3 type battery. Complete with neck cord, clip on dynamic extension mike (½ x 2 x 5/16in.) and battery. LASKY'S PRICE 10 Gns. Post Free anywhere in world.

THE TTC MODEL 13/500. More powerful version of above—size 7½ x 1½ x 1in. Operates on one P3 type battery. LASKY'S PRICE 12 Gns. Post Free anywhere in world. These cannot be operated in the U.K. owing to G.P.O. regulations.



CONSTRUCTORS BARGAINS

SPECIAL PURCHASE—UHF/VHF TV TUNERS

Well known British makers surplus stocks. Now available for the first time to the Home Constructor. Add 2/6 Post and Packing on each.

TRANSISTORISED UHF MINIATURE MODEL 1
Shielded metal case only 3½ x 1½ x 3in. Fully tunable—complete with two AF130 transistors. LASKY'S PRICE 39/6

TRANSISTORISED UHF MODEL 2
Metal case size 3½ (plus spindle) x 2½ x 1½in. Fully tunable with slow motion drive. Complete with two AF130 transistors. LASKY'S PRICE 25/6

VALVE UHF MODEL (illustrated)
In metal case size 4 x 6 x 1½in. Fully tunable—complete with PC86 and PC88 valves. LASKY'S PRICE 29/6 Without valves 12/6


TRANSISTORISED VHF TUNER
Sui-Miniature turret type fitted with 12 sets of coils and 3 Mullard AF102 transistors. In metal case size 3 x 1½ x 2½in. LASKY'S PRICE 37/6



TREMENDOUS BARGAIN!

TV UHF TUNER AND IF AMPLIFIER PANEL

Model No. 89384 made by famous manufacturer as standard conversion unit to 625 line reception (BBC 2) for 19" and 23" 405 line (convertible model) Cosworth, Philips, Scott and Stella television receivers. The units are boxed, brand new and fully guaranteed, complete with detailed conversion and operating instructions. To effect conversion on the sets mentioned above you need only a pair of pliers and a screwdriver! The units are fitted with 7 Mullard valves—PCF80 x 2, EF185, EF184, ECC82, PC86, PC88. Size of unit: tuner 7½ x 4 x 8in. IF panel on 9 x 4½in. printed circuit board x 2½in. deep. Complete with all leads, screws, washers etc. Original Price £10.10.0.

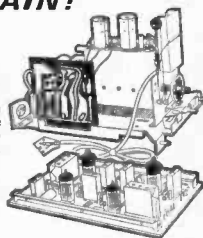

LASKY'S PRICE 49/6 Post 5/-

TREMENDOUS VALUE IF BOUGHT ONLY FOR THE VALVES AND COMPONENTS

NEW—LASKY'S MINIATURE TRANSISTOR AMPLIFIER MODULES

Incorporating the very latest circuitry to provide high sensitivity and good quality in conjunction with extreme small size and compactness. High quality Newmarket transistors used throughout. All designed to operate on 9v. miniature battery.

Add 1/- on each for Post and Packing.

TYPE LRPC 1. 3 transistor. Input sens. 50mV. output 150mW. output imp. 40Ω. Size 2 x 1 x 1½in. PRICE 27/6

TYPE LRPC 2. 5 transistor. Input sens. 1mV. output 330mW. output imp. 15Ω. Size 2½ x 1½ x 1½in. PRICE 22/6

TYPE LRPC 4. 5 transistor. Input sens. 150mV. output 330mW. output imp. 15Ω. Size 2½ x 1½ x 1½in. PRICE 22/6

TYPE LRPC 5. 6 transistor. Input sens. 8mV. output 3W. output imp. 3Ω. Size 5½ x 1½ x 1½in. PRICE 59/6

TYPE LRPC 6. Tape record/playback amp. (for use with self oscillating erase head). Output 750mW. output imp. 8Ω. Size 4½ x 2 x 1½in. PRICE 39/6

FULLY ENCAPSULATED MODULES


Special function modules—all one size 1½ x 1 x 1½in. Complete with detailed function and installation instructions. Send S.A.E. for specification sheets.

TYPE PA-1. Public address amp. for use with carbon, crystal or Dynamic microphones, 3Ω output imp. PRICE 30/-

TYPE GR-1. Gramophone amp.—provides sufficient power to fill average room. 3Ω output imp. PRICE 30/-

TYPE CO-1. Morse code practice oscillator—for use with morse key and 3Ω speaker. PRICE 20/-

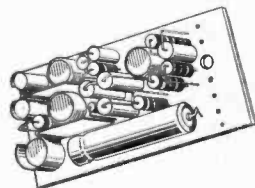TYPE MT-1. Metronome module—provides audible and visual beat from 30 to 240 beat per minute (for use with 3Ω speaker or indicator lamp). PRICE 22/6



GORLER UT 340 FM/VHF TUNING HEART

Permeability tuned—covering 87 to 108 Mc/s. For use with one ECC85 valve. In metal case, size 3 x 2½ x 1½in. Circuit supplied.
LASKY'S PRICE 15/11 Post 2/- ECC85 valve 9/- extra.

TRANSISTORS

ALL BRAND NEW AND GUARANTEED

GET 81, GET 85, GET 86 2/8; 873A, 874P 3/6; OC45, OC71, OC81D 4/6; OC44, OC70, OC76, OC81 5/6; (match pair 10/6); AF117, OC200 8/6; OC42, OC43, OC73, OC82D 7/6; OC201, OC204 15/8; OC205, PC206 18/6; OC28 24/6; OC75 8/-.

TRANSFILTERS

by BRUSH CRYSTAL CO., Available from stock.

TO—01B 465 kc/s. ± 2 kc/s.	TO—02D 470 kc/s. ± 1 kc/s.	9/6 each
TO—01D 470 kc/s. ± 2 kc/s.	TF—01B 465 kc/s. ± 2 kc/s.	Post 6d.
TO—02B 465 kc/s. ± 1 kc/s.	TF—01D 470 kc/s. ± 2 kc/s.	


NOW AVAILABLE—OUR NEW BARGAIN BULLETIN. 24 foolscap pages packed with hundreds of bargains for the "ham" and service man—exclusive to Lasky's—plus full list of regular stock items. PRICE 6d. POST FREE.

LASKY'S RADIO FOR FINEST VALUE and COURTEOUS SERVICE

SERVICE IN GREAT BRITAIN AND HI-FI ENTHUSIASTS

LASKY'S RADIO

RECORD PLAYERS

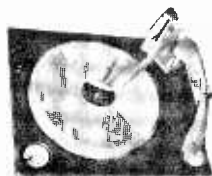

B.S.R. AUTOCHANGERS

AT LOWEST EVER PRICES

Fully guaranteed with cartridge and stylus.
UA16 9v. battery model..... £5 19 6
UA20 4 speed mains model..... £5 19 6

NEW! — B.S.R. UA70 4 speed mains autochanger,
superb modern styling at amazingly low price.

LASKY'S PRICE £9.19.6 (ex cartridge).
Add 5/- carriage and packing on each.

GARRARD AUTOCHANGERS

			SINGLE PLAYERS	
AT6 Mk. II	£10 19 6		SP25 Light turntable	£9 19 6
3000LM with stereo cartridge	£8 19 6		SP25 Heavy turntable	£10 19 6
AT60	£10 19 6		SRP12 with cartridge	£4 7 6
A70	£19 9 0		SRP10 Mains, with cartridge	£4 19 9
A50	£7 7 0		SRP10 Battery with cartridge	£4 19 6
A1000	£6 6 0		GARRARD BASES	
A2000	£6 16 6		WB1 £3 16 3 Clearview cover	£3 18 0
			WB2 £5 5 0 Clearview cover	£5 7 11

Postage and Packing on all above 5/-.

GREENCOAT RECORD PLAYER

33 1/3 and 45 r.p.m. 6v. Battery operated Comp. with pick-up and crystal cartridge.
LASKY'S PRICE 49/6 Post 2/6 Size 7 1/2 x 9in.

207 EDGWARE ROAD, LONDON, W.2 Tel. PAD 3271
118 EDGWARE ROAD, LONDON, W.2 Tel. PAD 9789
33 TOTTENHAM CT. RD., LONDON, W.1 Tel. MUS 2605
All the above branches open all day Saturday. Early closing Thursday.

Mail Orders and correspondence to 3-15 Cavell Street, Tower Hamlets, London, E.1. Tel.: STEPney Green 4821/2

SPECIAL INTEREST ITEMS

NEW! LASKY'S CLEAR PLASTIC PANEL METERS

Precision made in Japan by HIOKI. Each meter boxed and
fully guaranteed with all fixing nuts and washers. Sizes are
of front panel. Add. 1/6 Post on each.

Type KR-52 3 x 2 1/2 in. (illustrated)
1 mA DC 32/6 300 V DC..... 32/6
5 mA DC 32/6 500 μA 37/6
1 mA 8 Meter..... 39/6



Type MK-38A 2 1/2 in. square	22/6	Type KR-65 3 1/2 x 3 in.	36/-
1 mA DC.....	22/6	1 mA DC.....	35/-
5 mA DC.....	22/6	5 mA DC.....	35/-
300 V DC.....	22/6	300 V DC.....	42/6
500 μA.....	29/6	500 μA.....	39/6
1 mA 8 Meter.....	29/6	1 mA 8 Meter.....	37/6

Type MK-45A 1 1/2 in. square	25/-	Type MK-65A 3 in. square	36/-
1 mA DC.....	25/-	1 mA DC.....	35/-
5 mA DC.....	25/-	5 mA DC.....	35/-
300 V DC.....	25/-	300 V DC.....	39/6
500 μA.....	35/-	500 μA.....	37/6
1 mA 8 Meter.....	35/-	1 mA 8 Meter.....	37/6

THE HARROW POWER PACK

Battery eliminator for portable radios, etc. Converts your Battery radio to A.C. mains.
Replaces 4 1/2, 6v. and 9v. batts. Size only 3 x 2 1/2 in. State voltage required when
ordering.

LASKY'S PRICE 29/6 Post 2/-.

42 TOTTENHAM CT. RD., LONDON, W.1 Tel. LAN 2573
152/3 FLEET STREET, LONDON, E.C.4 Tel. FLE 2833

Both open all day Thursday. Early closing Saturday.

LASKY'S FOR SPEEDY MAIL ORDER SERVICE

THE PEMBRIDGE COLLEGE OF ELECTRONICS FOR TRAINING IN RADIO AND TELEVISION

FULL-TIME COLLEGE COURSE IN RADIO AND TELEVISION

Our Course, of sixteen months' duration, provides a fundamental
training for radio and television engineers. It includes theoretical
and practical instruction on transistor television receivers, U.H.F.
television receivers and colour television.

Exactly half the time is spent on practical work and the course
provides excellent practical experience on valve and transistor
radio receivers and high-fidelity equipment and all well known
makes of television receivers.

The Course is recognised by the Radio Trades Examination Board
(R.T.E.B.) for the Radio and Television Servicing Certificate
examinations.

Next Course commences 4th April, 1967.

To: The Pembridge College of Electronics (Dept. P11)

34a Hereford Road, London, W.2.

Please send, without obligation, details of the
Full-time Course in Radio and Television.

Name

Address

CMP 5

stern-clyne ELECTRONIC CENTRES

MEMBER OF THE PANTIYA GROUP OF COMPANIES

MAIL ORDER AND ALL ENQUIRIES TO STERN-CLYNE DEPT. PW., 3-5 EDEN GROVE, HOLLOWAY, LONDON N.7. Tel. 01 607 8161

LONDON:
18 Tottenham Court Rd., W.1.
23 Tottenham Court Rd., W.1.
309 Edgware Road, W.2.
109 Fleet Street, E.C.4.
162 Holloway Road, N.7.

MUSEUM 0095
MUSEUM 3451
PADDINGTON 6963
FLAET STREET 5812
NORTH 7841

9 Camberwell Church St., S.E.5.
220 Edgware Road, W.2.
CROYDON:
12 Suffolk House, George Street.
BRISTOL:
26 Merchant Street, Bristol 1.

RODNEY 2875
PADDINGTON 5607
MUNICIPAL 3250
BRISTOL 20261

LIVERPOOL: 52 Lord Street.
MANCHESTER:
20/22 Withy Grove, Manchester 4.
SHEFFIELD: 123 The Moor.
NOTTINGHAM:
Eastown House, Lincoln Street.

Royal 7450
Blackfriars 5579/5246
Sheffield 29993
Nottingham 45889

the versatile VERITONE 30 high power amplifier

- ★ For discriminating Hi-Fi.
- ★ Brilliant guitar reproduction
- ★ Crystal clear P.A. for meetings, fetes all outdoor activities



A magnificent professional instrument with a performance to satisfy the Hi-Fi enthusiast, plus superbly engineered construction and facilities that fulfil every amplifier need. Veritone 30 is packed with clean distortion-free power and a host of features found in amplifiers costing 3 times as much. It combines main amplifier giving a true 30 watts output, preamplifier with two separately controlled mixer inputs. Volume, Bass and Treble controls, speaker impedance selection (8 or 15 ohms), and extra power supply outputs of 300 volts at 40 mA, and 6.3 volts at 2A to drive auxiliary equipment. Veritone 30 is both an excellent rugged service P.A. amplifier, and the heart of a superlative Hi-Fi system. It makes an ideal basis for a guitar amplifier with inputs for two guitars.

£16.10.0 Carriage & Insurance 10/-
Optional top cover £1.15.0 extra.
Terms: Dep. £5.10.0. 12 monthly at £1.2.6. Total credit price £19.

DESCRIPTIVE LEAFLET ON REQUEST

A selection of our famous low cost, high quality speakers

Special Offer All-British 12in. Unit built-in tweeter cone, and a high flux magnet for wide range reproduction. Handles 6 watts. Available for 15 or 3 ohms impedance **39/6** P. & P. 3/6

Miniature 8 ohm Impedance Units suitable for most transistor sets. Extra powerful permanent magnets. Sizes available (circular only): 2, 2½, 3, 3½, 4 and 6in. dia. Any size **12/6** P. & P. 2/6


Standard 3 ohm Moving Coil Units, suitable for extension speakers, radio set replacements, car radios etc., up to 3 watts output.
6½in. circular 18/6 P. & P. 3/6
8in. circular 21 P. & P. 3/6
7 x 4in. elliptical 14/6 P. & P. 3/6
8 x 5in. elliptical 21 P. & P. 3/6
10 x 6in. elliptical 30/- P. & P. 3/6

Elac Extra Quality Units fitted high-flux Feroba II ceramic magnets. All sizes 3 ohm impedance.
8in. circular 30/- P. & P. 2/6
8 x 5in. elliptical 30/- P. & P. 2/6
9 x 5in. elliptical 32/6 P. & P. 2/6
10 x 6in. elliptical 33/6 P. & P. 2/6

BAKER "GROUP 25" 12in. bass model fitted with heavy cone giving full output down to E-string of bass guitar at 41 c/s. Impedance 15 ohms. Handling capacity 25 watts. **£5.5.0** P. & P. 5/-

UNIPEX TRUMPET SPEAKER

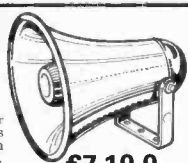- ★ Waterproof outdoor construction
- ★ Full 10 watts input
- ★ Adjustable mounting bracket




Superb, professional quality, re-entrant horn speaker for all outdoor P.A. work. 10in. diameter aluminium horn has rubber protected edge and diecast mounting fitted with universal bracket. Rated at 10 watts. Impedance 16 ohms. Frequency range 350 to 5000 cycles. Cut-off 280 cycles. Heavily enamelled two-tone grey finish. Length overall 10in.

£7.10.0 Carriage & Insurance 5/-

VERITONE 300 AMPLIFIER

A small versatile Gram. Amplifier with an output of 3-4 watts suitable for Crystal Pickup or Radio Tuner. Ideally suited for a small domestic installation requiring good quality low output, output impedance 3 ohms, volume control, treble control, bass control and middle control. Valve line-up EL84, EF86, E280. Smooth grey finished chassis, size 8½ x 4 x 1½in. with brushed aluminium front panel contrasting letters and knobs, front panel size 8½ x 2½in. Fully assembled and tested.

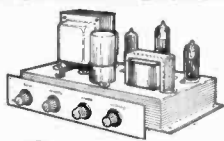

6 GNS.

The superb VERITONE VEGA STEREO AMPLIFIER



WITH CASE **£44.2.0**

Terms: Deposit £14.14.0, 12 monthly payments of £2.14.0. Total credit price £47.2.0. Carriage and Insurance, 10/-.

Veritone Vega means sound from the solid state. Great purity of sound comparable with that obtainable from the best valve amplifiers—plus all the advantages accruing from semi-conductor design employing the latest techniques. Important advantages such as improved reliability, absence of high-working temperatures, lack of valve noise, elimination of the output transformers, and design freedom that permits spacious layout within an optimum overall size to suit modern installation requirements. And the Vega is styled and finished in impeccable taste—totally enclosed in a handsome teak case with comprehensive controls functionally arranged on a clear silver grey and black panel.

LESS CASE **£40.19.0**

Terms: Deposit £13.13.0, 12 monthly payments of £2.10.1. Total credit price £43.14.0.

*stern-clyne's TREMENDOUS PRICE BREAKTHROUGH in NEW UNIVERSAL RECORDING TAPES

STERN-CLYNE make huge bulk purchases of recording tapes from the world's biggest manufacturers—and hand on the enormous price advantage to their customers. The quality is unequalled: Tensitized to ensure the most permanent type of base. Highly resistant to breakage, moisture, heat, cold or humidity. Highly polished, splice-free finish. Smooth output throughout entire audio range. Ideal for your most treasured recordings, cheap enough to use all the time. Double-wrapped—distinctively boxed. Available in both P.V.C. and Polyester qualities.

TENSITIZED P.V.C.		TENSITIZED POLYESTER	
3in. 250ft. Long Play	5 6	3in. 600ft. Double Play	11 0
5in. 600ft. Standard	8 6	5in. 1,200ft. Double Play	15 0
5in. 900ft. Long Play	10 0	5in. 1,800ft. Double Play	22 6
5in. 1,200ft. Long Play	12 6	5in. 2,400ft. Triple Play	37 6
7in. 1,200ft. Standard	12 6	7in. 2,400ft. Double Play	25 0
7in. 1,800ft. Long Play	15 0	7in. 3,600ft. Triple Play	50 0

TRIPLE BARGAIN OFFER 3-Reel packs of 3in. Professional quality (apex) self-mailing boxes with fill-in address label on reverse. Works on all tape recorders. 250ft. per reel. Famous Audio Magnetic brand. P. & P. 1/3d.

13/6

DIVIDAL CROSSOVER NETWORKS


Superb construction using selected high-grade components, each hand-somely finished and constructed in metal case with integral mounting feet. Inputs and speaker outputs are made to standard screw terminals. Full instructions supplied.



CV-1 Variable Crossover—Standard 2-way unit with low to medium power woofer and tweeter arrangement. Variable control permits adjustment of bass and treble output levels. In bronze finished case with black plastic panel size 4 x 2½ x 1½in. high. **12/6** Add 2/- P. & P.

CN-2 Crossover Network—Hi-Fi 2-way iron-cored choke and filter system offering high frequency crossover at 2,500 or 3,500 cycles/sec. Totally enclosed in bronze finished case size 3½ x 2½ x 1½in. high. **25/-** Add 3/- P. & P.

WHITEWOOD SPEAKER ENCLOSURES

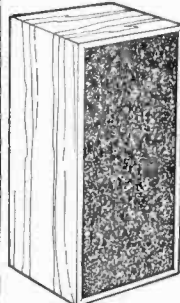

Specially designed and constructed for Stern-Clyne. Construction is of high density, non-resonant ½-inch chip-board, including rear panel. Front panels already cut for speaker sizes, rear panels are slotted to obtain correct acoustical loading. Ready for finishing, complete with attractive Vynal front panel speaker cloth and moulding.


- R1** 8in. speakers 11 x 24 x 9in. deep **£4.15.6**
- R2** 10in. speaker 15½ x 28 x 10in. deep **£6.10.0**
- R3** 12in. speakers 19 x 28½ x 12in. deep **£7.15.0**

Models R1 and R2 can also be supplied finished and polished in handsome walnut veneers. Quote reference:

RV1 8in. speakers **£9.9.0** **RV2** 10in. speakers **£11.11.0**

Add 10/- Carriage and Insurance when ordering any model

Exceptional offer of RADIOGRAM CHASSIS

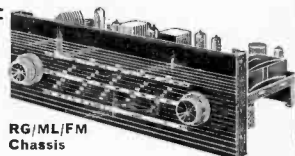

RG/ML/FM Chassis

MODEL RG/MLS

Modern 5-valve unit covers M/W (200-250 m.), L/W (1900-2000 m.) and S/W (15-50 m.). Superb sensitivity, built-in ferrite aerial external aerial unnecessary in most areas. Power output 3¼ watts. 8 ohms speaker. Attractive glass fascia, concentric control knobs. Size 13 x 6 x 6in. deep. For 200/250 AC. **£10.19.6** Carriage & Ins. 7/6

Model RG/ML/FM. Covers AM and FM Bands.

Superb, new 6-valve unit covering long and medium waves on AM and B.B.C. V.H.F. transmissions on FM. Highly sensitive AM circuit receives most stations through internal aerial; separate FM input with famous Gortler tuning heart. Uncluttered fascia to whole front area simplified adaptation to existing cabinets or building into contemporary bookshelf units. Extra large illuminated dial, dual concentric controls for volume, tone, and tuning. Powerful 4-watt output matches standard 3 ohm speaker. Inputs for external AM and FM aerials, gram. pick-up. 200/250 volts AC. Size 15 x 6½ x 7½in. deep. **£16.16.0** Carriage & Ins. 7/6

TERMS: Deposit £5.12.0, 12 monthly payments of £1.2.10. Total Credit price £18.6.0.

SEND FOR CATALOGUE

A 1/- P.O. brings new 100-page Bound and Science Catalogue packed with unique items; profusely illustrated.

PRACTICAL WIRELESS

VOL 42 No 12

issue 722

APRIL 1967

TOPIC OF THE MONTH

Repairers All

IT is probably true to say that inside most radio enthusiasts is a service engineer trying to break out. Overlooking the whimsicality and remembering that some folk would prefer the terms "technician", "repair mechanic", "troubleshooter" or "bodger" to "engineer", there is no doubt that we all derive satisfaction from restoring a dead set or stimulating a sickly one to vigorous health.

Although relatively few readers are professional repairers, there can be even fewer who do not find themselves involved at some time or another in handling faulty equipment. Indeed, it is clear that many in our ranks obtained their introduction to the hobby purely in order to obtain sufficient grasp of the subject to be able to repair and look after their radio sets.

Once embarked on the hobby you cannot hope to escape. Apart from looking after faults which develop in equipment you have built, there is the occupational hazard we all know so well. Once having been seen with a copy of P.W. or caught with a soldering iron in his hand, the enthusiast, no matter how elementary his knowledge, immediately achieves the local reputation of being "a radio expert". He then becomes prey to all his neighbours, friends and relatives who produce a regular supply of broken-down radios, defunct tape recorders, ancient amplifiers and (probably) a miscellany of inoperative electric irons, heaters and other hardware. These pieces of equipment always have a common feature: there's nothing much wrong with them, probably just a loose wire!

To many people, however, repair work is the main interest in the hobby. There is a peculiar (some would say horrible) fascination in fault finding. A large proportion of jobs fall into general routine, but there sometimes occurs a "dog" which seems like a combination of a Chinese puzzle, *The Times* crossword and a Sherlock Holmes case. To the real service man these are the spice of life and success is sweet.

What we have been saying is that to some degree we are all repair men—some are born service engineers, some achieve skill in servicing and others have servicing thrust upon them! Although reading is no substitute for practical experience, we hope that in the months ahead our new series of articles will be of interest and help to anyone engaged in Repairing Radio Sets.

W. N. STEVENS—*Editor*

NEWS AND COMMENT

Leader	899
News and Comment	900, 928
On the Short Waves <i>by John Guttridge and David Gibson, G3JDG</i>	908
Practically Wireless <i>by Henry</i>	917
New Books	938
The MW Column <i>by Alistair Woodland</i>	945
Club Spot—Silverthorn Radio Club G3SRA	946

CONSTRUCTIONAL

Multiband Transistor Superhet <i>by F. G. Rayer, G3OGR</i>	902
A Novel Transistor Preamp <i>by K. T. Wilson</i>	906
Dual Control Intercom <i>by Mike Fisher</i>	918
Crystal Calibration Marker <i>by A. S. Carpenter, G3TYJ</i>	921
Top Band Transceiver—Part 2 <i>by T. Simon</i>	933

GENERAL ARTICLES

Idea for an Infinite Baffle <i>by G. R. Fletcher</i>	910
Improving Cheap Tape Recorders <i>by W. S. Fowler, M.A.</i>	913
Repairing Radio Sets <i>by H. W. Hellyer and Gordon J. King</i>	924
Modulated Light Transmission <i>by H. L. Mason</i>	941

MAY ISSUE WILL BE PUBLISHED ON
APRIL 7th

All correspondence intended for the Editor should be addressed to: The Editor, "Practical Wireless", George Newnes Ltd., Tower House, Southampton Street, London, W.C.2. Phone: TEMple Bar 4363. Telegrams: Newnes Rand London. Subscription rates, including postage: 36s. per year to any part of the world. © George Newnes Ltd., 1967. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

Frequency Allocation

Having read the March 1967 issue of *Practical Wireless*, I wish to comment on some of the future broadcasting plans. On the subject of local sound radio, the White Paper says "The only possibility for such a service lies in v.h.f. . . .". We are all aware of the crowding that is prevalent in the medium wave band: could not this band be internationally stretched in frequency and this extension used solely for low power local broadcasting? The extension of the m.w. band to 1655kc/s would allow 6 extra channels (8kc/s spacing). These 6 extra outlets should be sufficient for any local radio plans if low power transmitters are used to give short range coverage of about 15 miles. Surely with the coastal and maritime services moving to the v.h.f. bands, it should be possible to extend the m.w. band for much needed local radio.

With reference to the "Pse QSL" article, I think an S-Meter calibration of 100µV in reads S9 would be correct. 1µV signals would hardly be readable on most Rx's never mind moving an S-Meter.

Desmond Walsh. Co. Tipperary,
Republic of Ireland.

You have a point regarding the allocation of frequencies for broadcasting. We would go further and say there is an urgent need for revisions, and probably rethinking, in other parts of the radio spectrum. You missed the point, however, about the S-meter readings—the specimen report (as stated) was hypothetical and merely intended to give a general pattern, the call signs, names and other details also existing only in imagination.—Editor.

Ready-made v Kits

I have been a reader of P.W. and P.T.V. for many years and I have recently made up some kits offered by your advertisers. Compared to the manufactured and tested units, these kits supplied are a flop and certainly do not prove economical. Advertised goods from Japan and Russia seem to be the best buys. Any comments from other readers?

S. Lenner. Leytonstone,
London, E.11.

Transistor Terminology

I too used to use valves but on account of the modest price and efficiency of transistors, have changed over. Many designs printed in this, and other journals employ Newmarket, Texas and Mullard transistors, to say nothing of Hitachi, Mazda, Sinclair, all of which use different notations. Also there does not seem to be any reliable equivalents data available.

Edwin King. Cookham Rise,
Berkshire.

NEWS AND..

NEW VENUE FOR RSGB EXHIBITION

The Radio Communications Exhibition is now renamed the International Radio Engineering & Communications Exhibition and will be at a new venue, The Royal Horticultural New Hall.

VERSATILE DIE-CAST BOXES FOR THE CONSTRUCTOR

Electronic Services—STC, introduce a range of aluminium die-cast boxes in five sizes from $4\frac{3}{4} \times 3\frac{1}{2} \times 1\frac{5}{8}$ in. to $10\frac{3}{4} \times 6\frac{3}{4} \times 2\frac{5}{8}$ in. They feature internal slots for sliding screens and printed circuit boards. Ranges of Veroboard are available to provide a wide variation of component layout and interconnection arrangements.

ROBERTS INTRODUCE THE R303



Roberts' Radio Company Ltd., Molesey Avenue, West Molesey, Surrey recently released model R303 which employs a transformerless audio amplifier which has been designed to give extra clarity and good reproduction of the lower frequencies.

Model R303 incorporates 8 transistors and three diodes: an AF115 self oscillating mixer, two AF117 i.f. amplifiers, one BC108 audio preamplifier, one AC127 audio amplifier, one AC128 driver, one AC127 and one AC128 as complementary output pair and OA90, AA119, BA114 diodes. Medium and long waves are covered and the operating voltage is 9V. The speaker is a $7 \times 3\frac{1}{2}$ in. elliptical having a 10Ω impedance. A ball-bearing turntable is fitted to the receiver base and sockets are provided for a car aerial and earphones. Housed in a wooden case covered with Rexine leathercloth in a choice of scarlet, warrior blue and silver green, the complete receiver measures $10 \times 5\frac{1}{8} \times 3\frac{3}{8}$ in. An alternative case has a black rexine covering with oiled natural teak end panels. Price is 15 gns. inc. battery and PT.

FROM COMMUNICATIONS Rx TO PEA BULBS

dca Electronics announce the publication of their new catalogue of equipment and components. Items listed range from communications receivers to dial bulbs. The price of this catalogue is 1s. 6d. and copies may be obtained from dca Electronics Limited, 28 Uxbridge Road, Ealing, W.5.


TREASURE TROVE

Remember all those old radar sets which flooded the surplus market after the war. There are still a few about and one begins to wonder if they might prove an investment. Some of these units were literally crammed with EF50 valves and many excellent circuits were designed and built around them. The latest price list from Mullards shows that the price for these valves new is £1 15s. 0d. each. Quick—up into the loft and search the junk box, you may be harbouring a fortune!

(A spokesman for Mullards commented that these valves were now produced specially on short run production, hence the high manufacturing cost and in turn the high purchase price.)

...COMMENT

SONIC STYLING FROM VAN DER MOLEN

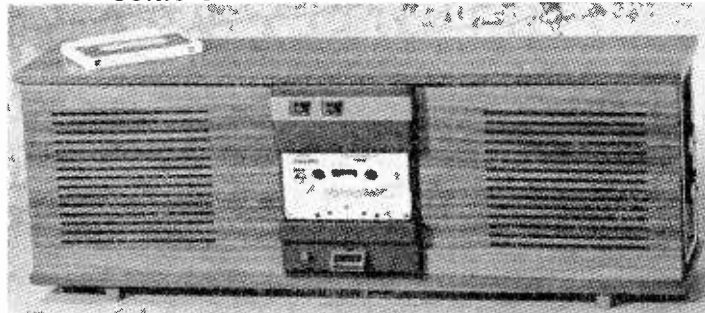

Designed around the Philips compact cassette system, Van Der Molen have produced three units—the Sonic Range—housed in polished wood cabinets suitable for placing on a bookcase or room divider.

The *Sonic Eight* is claimed to be the first stereophonic tape recorder based on a cassette system to be designed and produced in England. Associated units are the *Sonic Six* (mono record/play) and the *Sonic Seven* (stereo play) both at 39 guineas. All these transistorised units may be used in conjunction with external pickup and turntable or an f.m. tuner. Sockets and amplifier controls are in a recessed side panel.

The *Sonic Eight* (shown above) is a 4-track machine and tapes will give either 2 x 30 mins. or 2 x 45 mins. playing time. Fast forward and rewind is 70 seconds. Playback frequency response is 60–10,000c/s ± 3 dB and record frequency response is 100–10,000c/s ± 3 dB. Amplifier output is 4W per channel and two meters indicate the recording level. The speakers are high flux 5in. round types, one of which is detachable so that a full stereo effect may be obtained. It operates from 110–205–225–245V a.c. 50/60c/s or 20–25V d.c. Power consumption is 15W. Dimensions are 21 x 7½ x 5in., weight is approximately 15lb. and the recommended list price is 49 guineas, complete with cassette, dynamic microphone and recording lead. *Van Der Molen Ltd.*, 42 Mawney Road, Romford, Essex.

TECHNICAL WRITING COURSE

International Correspondence Schools now have a home-study course on technical writing which covers the syllabus of the City and Guilds of London Institute certificate examination (329). This course is geared to the special needs of technicians, technologists, engineers, scientists, technical journalists and others. It is designed to give practice in obtaining, sorting and using the information required for technical articles and report writing and as a part of the syllabus, the student is asked to complete five selected technical writing assignments.

Full details of the course are available from the Principal, ICS Ltd., Intertext House, Parkgate Road, London, S.W.11.

MAINS TESTER SCREWDRIVER



From Vitrex (Sales) Ltd., 457/463 Caledonian Road, London, N.7, comes the "Testmaster" mains tester embodying a cartridge fuse testing socket which also carries a spare fuse.

This instrument is moulded throughout in tough nylon, has a high intensity neon, high voltage insulation and a chrome vanadium blade. Suggested retail price is 7s. 6d.

It Still Hertz!

Your leader (December, 1966) declaring the intention of PRACTICAL WIRELESS to continue use of the term "c/s" for cycles per second instead of following the recently-devised "Hz" was like a breath of fresh air to the mental asphyxia being caused in recent years in electronics by the rising generations, who might sometimes do better to pay a little regard for the simple wisdom left them by their forefathers.

The object of electronic abbreviations and symbols is to provide a shorthand that enables a circuit or data to be more readily understood than otherwise. In recent years, however, much time and thought have rather misguidedly been devoted towards devising obscure abbreviations and sub-dividing the originally sensible and moderate number of symbols into such a forest that the wood cannot now be seen for the trees. In fact, the prior equipping of oneself with a tome of symbols, of so appreciable a size that reference for a particular symbol may itself require some minutes, is becoming the accepted thing.

No one, without first having been specially taught, could possibly appreciate that "Hz" meant cycles per second. The abbreviations "c.p.s." or "c/s", are capable of ready comprehension, which is as it should be; this feature, surely, far outweighs the use of "Hz" because it may be used by foreigners, or is said to honour Hertz, or may be quicker to say?

With every respect for Hertz (1857–1894), to whom I am sure there must be better ways of paying due honour, I fully applaud and endorse the independent decision to continue "c.p.s.", or "c/s", in PRACTICAL WIRELESS and hope this outlook receives wider recognition.

Peter W. Feeseey,

M.R.S.G.B., Dip.C.A.Eng.,

A.R.Ae.S.

London, S.W.20.

Correction:

The Explorer VHF Receiver


It has been brought to our attention, by the author, that four of the component values given in the circuit diagram and one of the items in the components list for The Explorer (January 1967 issue) are incorrect. To put matters right, the circuit diagram (page 646) should be amended as follows: R4 should read 100Ω, C4—2.2pf, TC2—3 to 8pf, and R9 should read 4.7kΩ. To correct the components list (page 649), the value of R9 should read 4.7kΩ.

More News and Comment on Page 928

MULTIBAND TRANSISTOR SUPERHET

F.G. RAYER G3OGR

COVER
SUBJECT

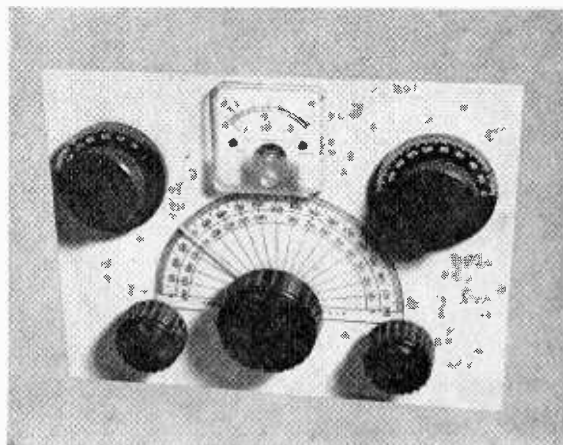

THIS receiver is constructed in three sections — mixer, intermediate frequency amplifier, and audio amplifier, and covers approximately 10-550 metres. It is built in a 3in. deep chassis, which encloses all items except the plug-in coils, so a cabinet is not required. This also allows the coils to be reached easily.

Denco (Clacton) Ltd. "Blue" coils are used for aerial tuning, and VC1 is a panel mounted trimmer. This circuit can thus be easily trimmed for best results, with any aerial, and there is no need for the fixed trimmers which often have to be provided and adjusted. The "Red" oscillator coils have a fixed trimmer TC1, which is left at about half capacity. VC2/VC3 is the ganged tuning capacitor. Cp1, Cp2 and Cp3 are padder capacitors, wired to tags 2, 3 and 4 of the oscillator coil holder. The coils are so made that the correct padder is in circuit when a coil is inserted. There is no padder for the highest frequency range.

The mixer section is constructed on the chassis. Coils for any of the following bands may be inserted: Range 2, 580-194m., Range 3, 180-57m., Range 4, 60-20m., Range 5, 28-9.5m. For general s.w. listening, Range 4 is recommended. Range 3 includes Amateur 80m. and 160m. bands and many other transmissions of interest. Range 5 gives very good results on those bands under 20m.

The intermediate frequency amplifier uses AF117 transistors, which give high gain and require no neutralising, and first and second i.f. transformers are double tuned. This allows five tuned i.f. circuits in all, with very good selectivity. Automatic volume control bias is obtained from the diode, and is applied to the first AF117 via R6. This operates the tuning meter, if required.

The audio amplifier has an OC71 and OC81D, directly coupled in a stabilised circuit, and driving two OC81's by means of T1. This is a very straightforward arrangement, with high gain and ample power output. Construction and testing are simplified by building i.f. and a.f. amplifiers as separate units. If necessary, the sections can be tested individually. Later, an aerial loading capacitor can be added, and helps secure best possible results on all bands, especially with a long aerial.

Audio amplifier

If this is built first, it can be tested with a pick-up, audio generator, or any other source of audio signals. It is assembled on 1/16th in. paxolin 5½ x 2½ in. Fig. 2 shows the top of the panel. Drill ¼ in. holes for the mounting bolts, and for T2. A 1/16th in. drill is suitable for the other holes.

T1 is secured by its wire ends, and a green dot

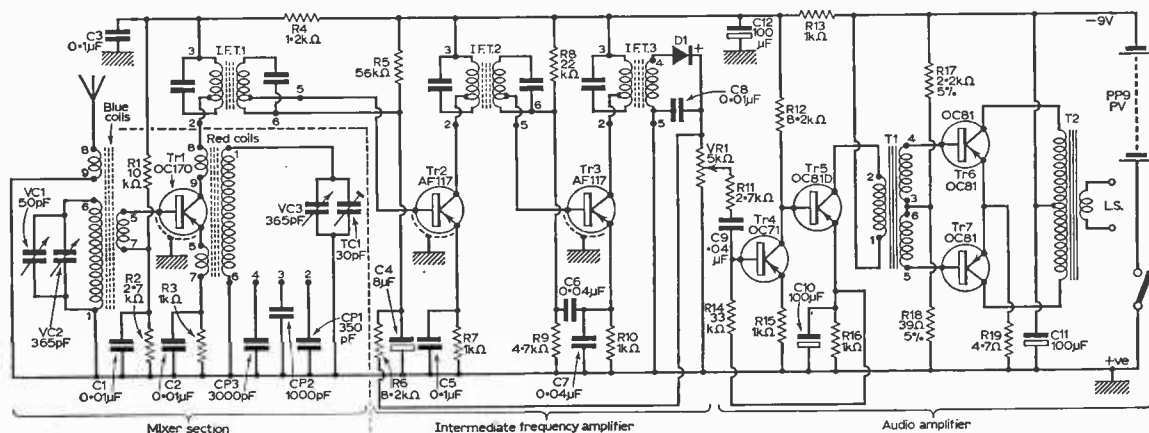


Fig. 1: Circuit diagram of the receiver showing the different sections.

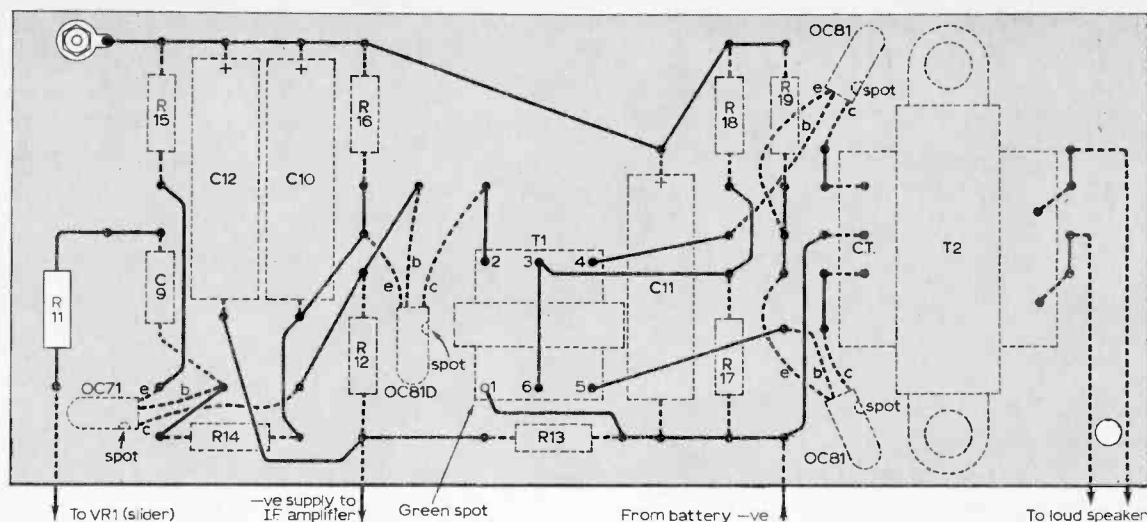


Fig. 2: Wiring diagram of the audio panel. Components shown dotted are on the other side.

marks tag 1. T2 is bolted in place.

The working of the output pair depends very much on the exact values of R17 and R18. Five per cent tolerance resistors should normally be satisfactory although ten per cent resistors do equally well if chosen for proper results. If the current drawn by the a.f. amplifier section exceeds 12mA, with no signal, R17 needs to be a trifle higher in value, or R18 a trifle lower. Should battery drain be low, and reproduction distorted, reduce the value of R17, or increase that of R18. Do not switch on with R18 disconnected. With an audio signal taken to R11, the a.f. amplifier should draw roughly 10mA with no output, rising to 40mA peaks at high volume. For normal volume, current will be in the 10-20mA range.

One of the quite large 9V batteries is recommended. Be sure polarity is correct—positive to chassis (via on/off switch).

I.F. amplifier

This is built on paxolin 4 x 2½ in. and the layout is shown in Fig. 3. Drilling positions for the i.f.t. pins can be found by pressing paper on the pins, then marking through this on to the paxolin. Each i.f.t. must go in its correct circuit position, and must be placed so that the pins come as in Fig. 3. Note that the screening can tags are connected to the earth (chassis) line. This section is assembled and wired as shown in Fig. 3. A soldering tag near C8 provides a connection with the chassis, when the amplifier is placed in position.

The leads of the transistors can be of such a length that the tops of the transistors are about

level with the top of the i.f. transformer i.f.t.3, which is shorter than the other i.f.t.s. The completed amplifier occupies the position shown in Fig. 4, and is mounted in the same way as the a.f. amplifier. It may be tested first. The top i.f.t. cores can be reached with a small trimming tool when the amplifier is in place. Lower cores are reached through holes in the chassis side.

If a signal generator is available, provide a modulated output at 465kc/s. Inject this at pin 5 of i.f.t.2

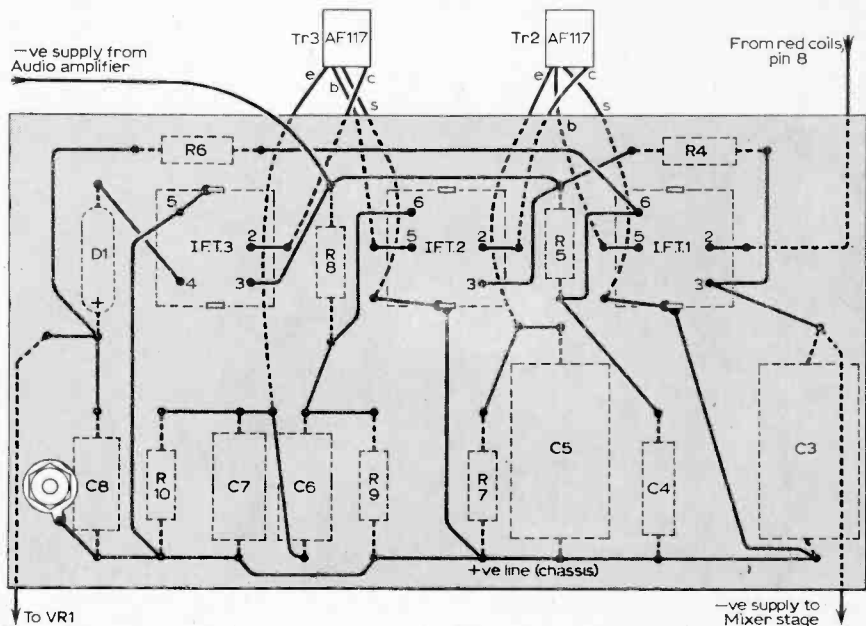


Fig. 3: Details of the i.f. panel. Frequency changer wiring shown in Figure 4.

and adjust the core of i.f.t.3 for best output. Move the generator input to pin 5 of i.f.t.1 and adjust both cores of i.f.t.2 for best results. Then inject at pin 2 on i.f.t.1, and adjust the cores of i.f.t.1. These adjustments are touched up after the amplifier is in position.

If no generator is available, leave alignment

until the mixer is completed. Then tune in a local transmission, preferably on medium waves. Rotate each i.f.t. core for best results. If the signal strength meter is included, this will correspond to maximum meter reading. Otherwise make adjustments by ear, or by observing readings on a meter placed in one battery lead. The programme should carry speech at uniform volume when aligning for

spindle passes through a clearance hole, and it is fixed to the front runner of the chassis by 4BA bolts. Washers or other spacers about $\frac{1}{8}$ in. thick are required between the chassis and capacitor. The bolts must be short so as not to touch fixed or moving plates. The panel is held by the nuts on VR1 and VC1. The tuning scale was a protractor with 2 in. radius. A pointer can be bought, or made

from perspex, or a stout straight wire. The wire may be soldered to a piece (with grub screw hole) sawn from a shaft coupler.

VC1 is best left off until the aerial coil holder is wired. VC1 is then connected to the chassis and VC2. Trimmer TC1 is supported by short, stiff connections. All leads can be 20s.w.g. with sleeving where necessary, and should be short and direct. The OC170 is placed as in Fig. 4. In this circuit, padders Cp1, Cp2 and Cp3 are not very critical. Provided VC1 can be peaked for maximum volume, there is no loss of efficiency, so the padders need not have very close tolerance.

When wiring is completed, take the black lead from the i.f. strip along near the front of the chassis to R1.

The coils, as supplied, generally seem to have the cores screwed fully in, for packing purposes and they should be unscrewed to allow the slug to be positioned half way. Band coverage depends on the position of the oscillator core, so this should be locked with a 6BA nut, after any adjustment necessary. For best reception of weak signals an earth is required, and it can be attached to one of the chassis bolts. A long, high aerial will also improve signal strength and range.

Normally, VC1 should peak for maximum signal strength or maximum background noise. On the higher frequencies, in particular, some signals may be heard which cannot be peaked by means of VC1. This is due to "image frequency" reception, which arises with any ordinary superhet, and which would probably not be identified as such if VC1

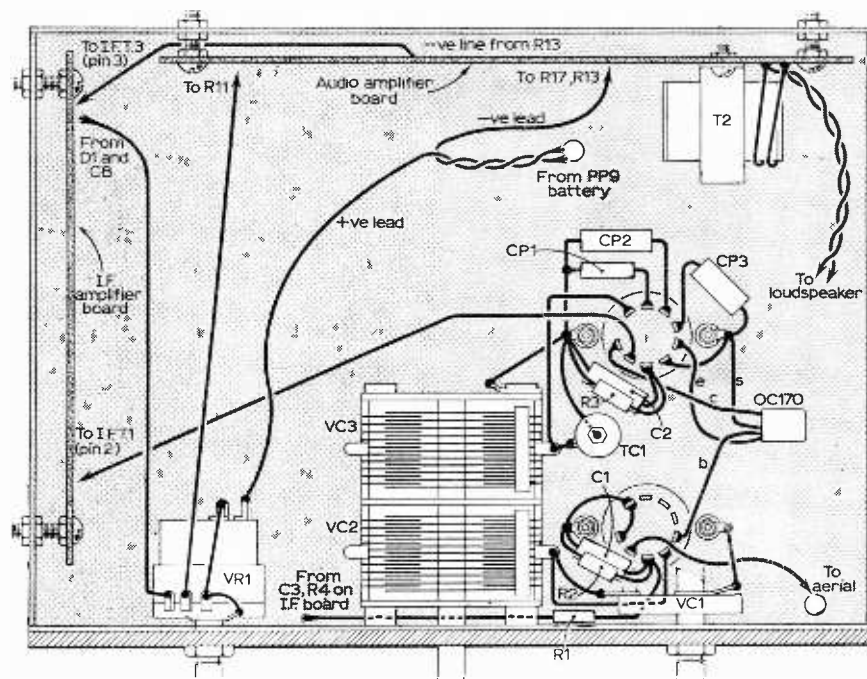


Fig. 4: Layout of first stage components. Note position of audio and i.f. panels.

maximum battery current to the output stages. At the same time VR1 should be turned back as necessary to keep speech peaks down to 30-40mA or so. Later, either provide a small input from a signal generator, or repeat adjustments on a weak, stable signal. The latter can be a local m.w. station, received with no aerial, or with a very short wire.

Mixer section

This is assembled under the chassis as in Fig. 4. Holes should be drilled before mounting i.f. and a.f. sections. A $\frac{1}{8}$ in. dia. chassis punch is most suitable for the coil holder holes. Put tags under the securing nuts for chassis connections MC. VC2/3 has an internal 6:1 ratio slow motion drive. Its

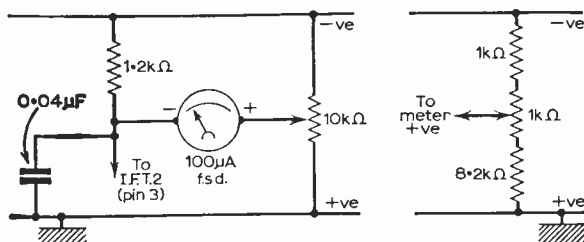


Fig. 5: Details for wiring in an "S" meter. The diagram on the right shows an alternative to the 10kΩ pot.

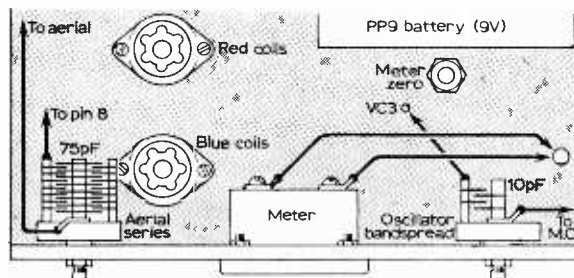


Fig. 6: Top-chassis view showing positioning of the coils and front panel components.

were not variable. It is caused by strong signals, not tuned in by VC2, nevertheless reaching the mixer. Placing a small capacitor between tag 8 of the aerial coil holder and the aerial lead will somewhat reduce this effect. A panel operated capacitor may be used, fitted above the chassis near the aerial coils. For general purposes, a 75pF or 100pF capacitor is suitable. Opening it reduces signal input, and also somewhat increases the selectivity of the aerial coil circuit. On some frequencies it will be found quite useful. The corner of one moving plate can be bent so that the capacitor shorts out when closed.

If listening is confined to a narrow band of frequencies, the addition of a bandspreading capacitor will be found useful. This can be about 10pF. It is mounted above the chassis, and is wired to the chassis and rear section of the ganged capacitor. This allows fine tuning over a narrow band of frequencies. With very weak signals, VC1 is adjusted slightly, to maintain alignment. Should a low value 2-gang capacitor be to hand, its sections could be wired in parallel with VC2 and VC3, to remove the need for adjusting VC1 when using bandspread tuning.

Tuning Meter

The collector current of the first AF117 depends on a.v.c. bias and is around 400μA with no signal, falling to about 200μA with strong signals. This can be arranged to operate a signal strength or tuning meter. Fig. 5 shows a bridge circuit in which the meter reads zero for low signal levels, rising with signal strength. Disconnect pin 3 of the 2nd i.f.t. from the negative line, and connect a 0.04μF capacitor from pin 3 to earth line. Add the 1.2kΩ resistor and 10kΩ or similar potentiometer as shown. The latter is best on the chassis, and the spindle can be slotted or fitted with a knob. Initially place the slider near the negative end of the element. Careless adjustment will cause a quite heavy current in the meter. If preferred, this can be avoided by using a fixed resistor in series with the potentiometer, Fig. 5. A miniature type square meter can be accommodated above the tuning dial.

With the aerial disconnected, carefully adjust the potentiometer for zero reading. The reading should approach full-scale for a very strong signal. Adjusting VC1, improving alignment, or increasing the efficiency of the aerial or earth, will cause higher meter readings. There is no reading on weak signals which provide no a.v.c. voltage.

★ components list

Resistors $\frac{1}{4}$ w 10% unless stated.

Resistors:

R1 10kΩ
R2 2.7kΩ
R3 1kΩ
R4 1.2kΩ
R5 56kΩ
R6 8.2kΩ
R7 1kΩ
R8 22kΩ
R9 4.7kΩ
R10 1kΩ
R11 2.7kΩ
R12 8.2kΩ
R13 1kΩ
R14 33kΩ
R15 1kΩ
R16 1kΩ
R17 2.2kΩ 5%
R18 39Ω 5%
R19 4.7Ω
VR1 5kΩ pot. with switch.

Capacitors:

C1 0.01μF 150V
C2 0.01μF 150V
C3 0.1μF 150V
C4 8μF 6V
C5 0.1μF 150V
C6 0.04μF 150V
C7 0.04μF 150V
C8 0.01μF 150V
C8 100μF 12V
C9 0.04μF 150V
C10 100μF 6V or 12V
C11 100μF 12V
C12 100μF 12V
CP1 350pF 5%
CP2 1000pF 5%
CP3 3000pF 5%
VC1 50pF air spaced variable.
VC2/3 Jackson 02 (2 x 365pF) slow motion variable.
TC1 30pF air spaced trimmer.

Semiconductors:

Tr1 OC170
Tr2 AF117
Tr3 AF117
Tr4 OC71
Tr5 OC81D
Tr6 OC81
Tr7 OC81
D1 OA81

Inductors:

T1 Weyrad (Electronics) Ltd. LFDT4 OPT1
T2 ditto
IFT1 IFT18/465
IFT2 IFT18/465 } Denco
IFT3 IFT14/465 } (Clacton) Ltd.
Coils, Blue and Red, ranges 2, 3, 4 and 5.

Miscellaneous:

4-sided chassis 7 x 5 x 3in. deep. Two B9A non-skirted holders. Panel 7 x 5½in. Paxolin 4 x 2½in. and 5½ x 2½in. 9V battery (PP9), etc. Pointer and scale. Knobs.

A plug-in medium wave ferrite aerial can be used instead of the Blue m.w. coil. An aerial intended for 208pF tuning capacitor can be adjusted so that alignment over the band falls within the range of VC1. The aerial is supported a few inches clear of the metal chassis, and connected to a plug-in base to fit the B9A holder. Take the tuned winding to pins 1 and 6, and the base coupling coil to pins 5 and 7. ■


Dear Reader,

This is to invite you to join us at the Practical Wireless Film Show to be held at Caxton Hall, Caxton Street, London, S.W.1., on Friday, April 14th, at 7-30 p.m. sharp.

In conjunction with Mullard Ltd., we will be showing the Film "Electrons in Harness" followed by a topical talk "Transistors and Television". Refreshments will be provided in the interval.

Tickets are free and applications should be made to - Film Show, Practical Wireless, Tower House, Southampton Street, London, W.C.2. A stamped addressed envelope of adequate size must be included.

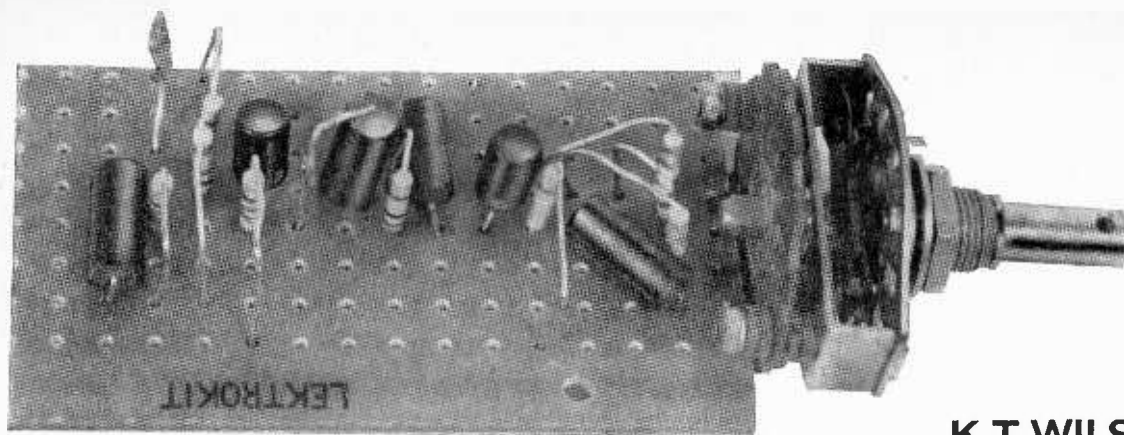The Editor and Staff, Practical Wireless and Practical Television.



K.T. WILSON

A NOVEL TRANSISTOR PREAMP

THE amplifier described here was built to be used as a universal preamp, capable of handling audio or video signals when the gain of the a.f. amplifier, the oscilloscope or the video amplifier of the TV set was insufficient. For such a purpose the preamp had to have very good frequency response, several switched gain settings, and had to be easy to build.

The answer was found in a new theory of transistor amplifiers developed by an Australian authority. Normally, the design of wide-band transistor amplifiers is an extremely difficult business, as anyone who has applied the formula for the gain of a single transistor stage to predict the gain of a complete amplifier will know. The whole trouble is that the gain and the input and output impedances of any stage of a transistor amplifier depends on what has gone before and on what follows. For example, if we make up a simple single-stage transistor amplifier and set up equipment to measure its gain and output impedance, we will find that the results we get from a 75 Ω source are quite different from those obtained using a 50k Ω source. This effect is not found to any noticeable extent in valves and is due to the internal feedback in the common types of transistor. One method of getting round all this is to use the most modern types of silicon planar transistor, where the internal feedback has been reduced to negligible proportions. Alas, these transistors are still very expensive in this country, and the manufacturers seem reluctant


to release details of circuits using such devices.

Those of us who do not have rich aunts in the USA are therefore forced to use cheap and readily available germanium transistors, and to find circuits which will enable us to construct amplifiers of good performance.

New Approach

This new approach is, like all good things, basically very simple. If the trouble with transistor amplifiers is interaction, we shall minimise the interaction by mis-matching between stages of the amplifier. Figure 1 illustrates the principle involved. In Fig. 1a, R1 represents the output impedance of one stage, and R2 and R3 represent the input and feedback impedances of the next stage. Suppose that all these impedances are equal. If now a voltage V appears at A, the voltage at B is V/2 since R1 is equal to R2; and this is the voltage "gain" of the coupling stage. The same argument applies in the opposite direction, though, and the feedback "gain" must also be 1/2. Since the forward gain is equal to the feedback gain, feedback theory tells us that the overall stage gain of the transistor to which this network is coupled must be one. Therefore a pair of transistors coupled in this way would have the same gain as a single transistor. This is a vivid example of the difficulty of predicting the effect of cascading transistor stages.

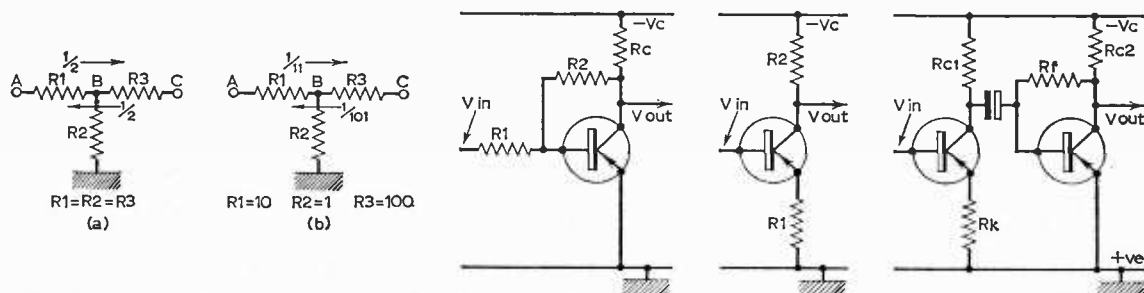Now consider the values given in Fig. 1b. Here the forward voltage gain is 1/11 and the feedback



Left to right. Fig. 1a, 1b: Principle involved in mismatching. Fig. 2: Shunt Feedback. Fig. 3: Series feedback. Fig. 4: A series feedback stage coupled to a stage with shunt feedback.

gain is 1/101. The ratio is a little more favourable this time, but the overall gain of the stage is still set by the feedback impedance, R_3 , whose precise value cannot be calculated, as it depends on the operating conditions of the transistor. The obvious method of stabilising the transistor impedances is by the use of feedback on each stage, and this indeed is the method used. There are two ways of applying local feedback to a transistor amplifier stage, shunt, illustrated in Fig. 2 and series, illustrated in Fig. 3. In either case the gain is very nearly equal to R_2/R_1 . It is a remarkable thing about the design of transistor amplifiers that an approximation is usually better for practical purposes than the most carefully worked "exact" solution. I use the word exact in quotation marks here because such solutions are usually worked with little or no regard to the large spread of transistor parameters and to the effects of coupling stages referred to earlier.

We know from feedback theory that the series feedback amplifier has high input and output impedances and the shunt feedback amplifier has low input and output impedances. If, then, we make the stages of a transistor amplifier of alternate series and shunt stages, we should be able to predict the gain of the amplifier accurately.

This turns out to be correct, and a further simplification can be made. In the circuit of Fig. 4, where biasing arrangements have been omitted in

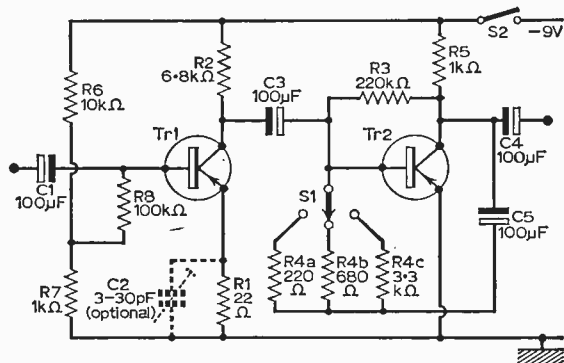


Fig. 5 (above): Circuit diagram of the preamp.

Fig. 6 (right): Veroboard layout and wiring.

order to show the feedback components more clearly, a series feedback stage has been coupled to a shunt stage. If the feedback resistor for the shunt stage is very much less than the load resistor for the first stage then the feedback resistor will in fact be the a.c. load for the first stage. The overall gain of the two stages is therefore R_f/R_k .

The following are therefore the conditions for being able accurately to predict the gain of a transistor feedback amplifier:

1. Use of alternate series and shunt stages.
2. Shunt feedback resistor must be small compared with the natural feedback of the transistor—the method may be inaccurate with some old types of power transistor.
3. Series feedback resistor (in the emitter lead) must be large compared with the emitter impedance of the transistor, which is usually about 6 ohms.

It is also necessary that for cascaded stages, the


shunt feedback resistor should be much smaller than the d.c. load resistor of the series stage.

To illustrate the use of these rules, the design of the wide-band amplifier will be outlined. The basic circuit is shown in Fig. 5. We shall aim for switched gain positions of $\times 10$, $\times 30$ and $\times 100$, and a bandwidth of about 20Mc/s in the $\times 10$ gain position; this implies a bandwidth of around 2Mc/s in the $\times 100$ gain position.

The first limitation is the emitter resistance of the series transistor because the series feedback resistor must be greater. We can reduce the emitter resistance of the transistor by using a large standing current, but this in turn will make it difficult to use a high value of d.c. load resistor, unless a fairly high voltage line is used.

Practical Values

For the series feedback resistor, 22Ω is a good compromise. This at once fixes the shunt feedback resistors as 220Ω, 680Ω and 2.2kΩ. For the d.c. load to be large compared to this last feedback resistor would require a load of at least 22kΩ, which in turn would need a battery voltage of at least 22V to bias the transistor to 1mA. We could, of course, use a 24V line; but with such a small handy amplifier it would seem a pity not to use a small 9V battery. We shall therefore bend the rules a bit;

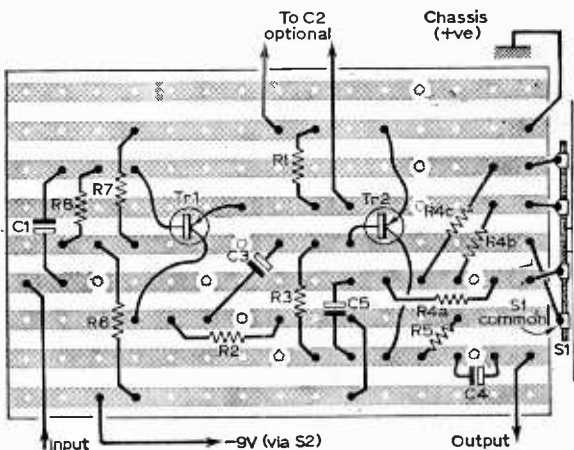

we shall make the load large compared to the intermediate gain feedback resistor, of 680Ω. This settles the load at 6.8kΩ, and we now have to find a feedback resistor which gives us a value of 2.2kΩ when in parallel with 6.8kΩ. Using the usual formula for shunt resistors, this works out at just over 3kΩ, and we can use the nearest value of 3.3kΩ.

The d.c. shunt feedback resistor, R_3 can now be specified, it must be much larger than the largest of the switched feedback resistors, and we can use 220kΩ here. The collector load of the second transistor will not be too critical due to the use of d.c. feedback through R_3 ; we can make it 1kΩ. It only remains now to specify the coupling capacitors and the bias network for the first stage to complete.

Have we forgotten something? We have not so far specified the transistors, and this is the most

—continued on page 950

ON THE SHORT WAVES

MONTHLY NEWS FOR DX LISTENERS

Times in GMT
Frequencies in kc/s

THE BROADCAST BANDS

by JOHN GUTTRIDGE

SOME readers have been confused recently between kilohertz and kilocycles. The difference is purely in name, the two terms being synonymous. The actual frequency is the same e.g. 15,000kc/s=15,000khz.

ASIA

China (Taiwan): *Broadcasting Corporation of China* (53 Sec, Jen Ai Road, Taipei, Taiwan) has English at 0250—0350 on 7,130/11,825/15,125/15,345/17,720/17,780/17,890 and 1800—1900 on 9,685/9,765/11,725/11,825/15,125/17,890.

India: *All India Radio* (P.O. Box 500, New Delhi) now using 15,165/17,705 in English from 1000—1100 to Australia. To Europe 7,215 is used 1715—2200, 9,915 1915—2200, 11,905 1715—2000. The 1845—1930 French transmission is on 7,290.

Pakistan: *Radio Pakistan* (Broadcasting House, Bunder House, Karachi) now using 17,770 during its 1335—1350 English Tx.

EUROPE

Albania: *Radio Tirana* (Rue Ismail Quemal, Tirana) using the new frequencies of 6,155/1,214. English noted 0630—0700 6,155, 1200—1230 7,265 and 1500—1530 or 1,214. The 1,214 outlet blots out the BBC Light Programme in East Anglia during the 1500 Tx.

Denmark: *Radio Denmark* (Radio House, Copenhagen V) will from March 3 air its South American transmissions on 15,165 at new times. There are Danish 2000—2045 and Spanish 2045—2115.

Finland: *Radio Finland* Unioninkatu 16, Helsinki) now gives its Finlandia Mixture English programme at 1600—1630 Saturday and 1215—1245 Sunday over 9,555/11,805/15,185.

Germany: *Deutsche Welle* (Bruederstrasse 1, Postfach 344, Cologne) to have four 250kW transmitters by the summer of 1968.

Great Britain: *BBC* (C.E.X.B., Bush House, London, W.C.2) has stopped its 1730—1800 Albanian transmission and is to cut the Arabic service by two hours. The General Overseas service has been noted during the morning on 25,650/25,670. From 1415—1445 the BBC relays the Canadian Broadcasting Corporation's Russian service over 7,260.

Holland: *Radio Nederland* (P.O. Box 222, Hilversum) has free leaflets on the following: Aerials; a 13,16, 19 m.b. Converter; Selectivity improvement; a B.F.O. circuit; crystal calibrator; product detector for SSB; "This is Dxing"; and an English/Spanish DX vocabulary. Enrolment is now open for the station's propagation course to be aired from April—September.

Hungary: *Radio Budapest* (Brody-Sandor-S.O. 5-7, Budapest VIII) now uses 21,685/17,890/9,833/7,100/5,902/3,995 at 1930—2000 and 9,833/7,220/7,100 6,234/5,902/3,995 at 2200—2230 for English to Europe.

Monaco: *Radio Monte Carlo* (16 Boulevard Princesse Charlotte, Monte Carlo) has moved its 41 m.b. outlet 3AM4 to 7,140. The station is on the air from 0500—0100.

Portugal: *Radio Lisbon* (Rua do Quelhas 2, Lisbon) now transmits to Europe on 6,025/7,130/9,740 with English 2045—2130, French 1830—1915; Italian 1915—2000; German 2000—2045. The station is now understood to have two 250kW transmitters in service.

AUSTRALASIA

Australia: *Radio Australia* (Box 428G, Melbourne) reported in 11 m.b. on 25,750 in the morning. The 1214—1315 English transmission has moved to 11,710. Dxers calling programme for Europe is now being heard at 0845. Frequencies remain 11,710/9,560.

NORTH AMERICA

Canada: *Canadian Broadcasting Corporation* (P.O. Box 6000, Montreal) is to have eight 250kW transmitters by 1970.

U.S.A.: *Radio New York Worldwide* (WNYW) (485 Madison Avenue, N.Y. 10022) now transmits in English 1145—1355 17,845/15,265/15,440, 1355—1900 21,530/15,440/17,845; 1900—2115 21,530/9,740/11,970/15,440; 2115—2315 15,440/9,740/6,145; 2315—0015 11,790/6,145/15,440; 0015—0045 11,790/15,440. There are slight differences on Sundays. Dxing Worldwide is now aired on Saturdays at 2307 and Sundays at 1607. *Voice of America* (U.S. Information Agency, 330 Independence Avenue, SW, Washington 25047, DC). Greenville has been heard in English at 1200 and 1500 on 26,040 and in Urdu at 1500 on 25,950.

CENTRAL AMERICA

Netherlands Antilles: *Trans World Radio* (5C Zoutpannenweg, Bonaire) now on 11,775 to Europe with Roumanian 2000, French 2015, German 2030 and English 2130—2200.

SOUTH AMERICA

Brazil: *Radio Dragao do Mar* (Rua P. Pereira 383, Fortaleza, Ceara) reported with a fair signal at 2230 on ZYH29 4,775.

Ecuador: *La Voz de los Andes* (HCJB) (Casilla 691, Quito) now using 15,325/17,880 for English from 1845—2000. Then moves to 15,115/11,770.

Clandestine: *Radio Revistanoted* in Spanish at 2300 on 9,955. This station is thought to possibly be an outlet of Radio Pekin.

Contributors this month were Radio Nederland, E. Ashburner, Pathfinder Radio Group, A. E. Roxburgh, J. W. Smith, International Short Wave Club, Radio New York Worldwide, D. C. Oates, D. S. Abbot, Swiss Broadcasting Corporation, T. E. Rogers, M. C. Donnelly, B. Burling, S. J. Wisher.

WHATEVER your poison it looks as though you're in luck if conditions continue the way they have this past few weeks. Whichever band you favour there's bound to be a lovely drop of genuine vintage DX to tickle your palate—if conditions continue. Twenty metres has come back into its own again and quite a large number of reports arrived which quoted a good assortment of stations liberally sprinkled between 14000 and 14350kc/s. Quite high activity on all bands although some seem to hear quite a batch of signals and others miss the boat completely. This is particularly true of 7Mc/s and sometimes 28Mc/s. In the case of 10 metres, this band is still a bit patchy so if it seems like an r.f. cemetery when you listen, try a different time.

The comments written by some s.w.l.'s are very interesting. One such report tells of a GW station who lives in a lighthouse with the antenna up the side. (Probably keys the lamp for local working!)

Alex Liggins (Fife), listened on eighty with the Beginners 5 Band t.r.f. as per Dec. '66 "P.W.". He speaks very highly of both the band and the receiver. His log includes most of Europe raised on 100ft. of garden wire. From further afield Alex logged—CT3AV, K1NPA, K2RBT, VS9ARV, WINQN, 3A2CP, 4U1TU. While on 20 the best was VK3AD. How about it you superhet types? Chris Claydon advises that the time to listen on fearful forty is around 0130. All owls please note!

TWENTY METRES

Very active now and certainly not dying out as some of us thought earlier in the year.

Peter Elliott (East London, South Africa) has just finished the P.W. Progressive S.W. Superhet. Using an 89ft. piece of wire he logged this lot on phone CE6EQ, CR8AG, DU-1FH, 1HR, 9FB, EP-2AX, 2BQ, 3AM, HI8EFO, HL9KX, HR1KAS, HS1CB, HS4AK, JA-1KG, 4OK, 8ADQ, 8BNK, 91L, KG6-AQG, FAE, KP4BB, KR6-IQ, KS, LL, MU, UD, KW6EJ, KX6BQ, MP4TBO, OD5EF, VE-4AF, 5LM, 7AON, 7CE, VK-2AFU, 3MA, 4JZ, 5NY, 6XX, 9X1, VP2-AA, AQ, VP9SU, VQ9AA, VS6CJ, WA6EFB, numerous W6's and W7's, XW8-AX, BJ, BQ, BS, CA, YA1FV, YK1AA, YS-1HO, 2BB, ZL-1AH, 3AY, ZP5CF, 3W8D, 6O1AU, 9M2-NF, OV, 9M6JP, 9V1ND. If you don't hear the DX on twenty, then get yourself 89ft. of garden wire and the Feb. '66 issue of "P.W."

David Douglas usually keeps an ear on top band but lately the dial on the receiver has been tuned to 20. Best for the session—CX5AAM, K6RFW (a.m.), LA1OK/MM, HV3SJ, TF2WHI, UF6KPA, VK7CK, ZB2A, 4S7NE (Ceylon), 9M2DQ. David says that new call signs are rampant again, 3B3=VO1, and 3C3=VE3. Wait till all G's become AX27's! Israel is now 4X and 4Z too.

Henry Law (Belfast) "Sky Champion", 70ft. l.w. plus a.t.u. heard mostly EU's on phone but also managed—CT1KT, K16LJK, SVØWL, SVØUF, TF2WJK, TF2WHI, VE-1AJO, 2BAZ, 3DFU, 3UR, 4OX, VO11B, VK-2AVA, 3AUP, 5XK, 9FR, 9JV, ØOV, VR2DI, VU-2KX, 4OG, XE1CCW, XF4RY.

Martin Davies (Northumberland) writes: "The

VK signals were extremely strong, the S-meter reading for the VK3 station was 40dB over S9!"

40 AND DOWN

Down to 7Mc/s and lower once more, but don't worry, we're not alone. Those who do listen seriously on 40 swear by it for producing DX. The two virtues necessary are patience and persistence (course—a receiver helps too!).

N. Henbry (Rye) EA12, 20 metre dipole at 25ft. captured these goodies on phone and that takes some doing on 40—EP2BU, HI8XNO, K5OSH, PY7VON, PY8QQ, PZ1CF, UB5QG, VP6EW, VP6KL, W2SJH, WØ1PB, WA1DBM, YV1PW. On eighty the same set-up raised—CN8AW, HI8XAL, K3UZE, K8YWG, MP4TBO, OD5EJ, UQ2KFT, VO1FX, W1FZJ/KP4, W2GO, W3BMS, W5KFD, 3B1FX (VO1FX) all s.s.b. Norman queries SV2HB heard on 80 at 2125 on 12.12.66.

C. Claydon (Fife), 84OC plus PR30, 12ft. vertical, tuned across 40 and heard—ET3RT, HI8XAL, HZ1AB, PY2-OTV, NE, PY6GN, PY7VON, PZ1CM, TF2WJX, TI2PZ, UL7IT, VE2TZ, VS9AJH, W8ZCK, WA9MJD, WB4CFN, XE1C, YV4NS, YV5BZH/6, 3C3BLU, 4Z4NAB, 7X2ED, 9Y4-AR.LE.

M. Smith (Shetland), PCR3, 35ft. vertical, claims he was heartbroken to read in February "P.W." "No DX on 20 and 15". His log for 21 reads—CT2AC, K1RPQ, LU1DAI, ST5SA, VE1GD, VK5KF (running 25 watts), VK6QL, VK6NA, W-1RF, 2PQG, 3LPN, 4POH, 8TUS, 9QHR, WA4UGB, WB2KWW, WØRWC, XE2SZ, ZC4DX, ZL2AQA, ZS4NL.

10 METRES

W. Nutt (Notts), says 28Mc/s is active in the early afternoons. His log reads—UA3VGN, UA3MOG, UT5KHT, VE3BVV, VP7NX, VQ8BJ, W1RFM, W2WQO, W9KAH, W9VUB.

David Douglas (see 20 metres), tuned in to ten metres and hooked—CR7CZ, CR7CI, CR7FM, FH8CD, VS9APW, ZC4MO, ZL1OD, 3C3AXF, 3C3BSM, 3C3DSL, 9J2MM.


N. Henbrey (see 80 metres) heard these on s.s.b.—K1LWI, W8HRS, WB2BEE, VK6CF, ZC4CI, ZE1JE. Norman writes to say that the VKØAA in his log printed in the Feb. issue should be DKØAA, sri OM.

NEWS AND CONTESTS

Contests and gatherings for this month include March 4-5th. 2 metre contest; 4-5th ARRL DX phone contest (should be a lively one to listen to, see if you can hear all States!); 11-12th BERU contest; 18-19th ARRL DX c.w. contest.

If you'd really like a challenge and you'd like to do something really useful then listen on April 2nd on eighty metres. It's the 3-5Mc/s QRP (low power) contest and all reports will be welcome.

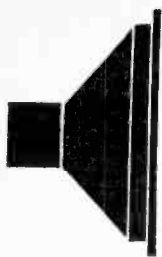Donald Wood writes from Nicosia and says that the "First Cyprus Amateur Radio Club will be on 160 and 80 by the end of March". He would like to hear from clubs or amateurs, his address is 9 Aetoles St., Nicosia.



G.R.FLETCHER

**idea for...*

INFINITE BAFFLE

WITH the increasing installation of central heating systems in the older type of house, fireplaces and chimneys are becoming useless items. The unused fireplace is usually filled in and the space wasted.

This very nearly happened to the writer, but being a hi-fi enthusiast in the throes of rearrangement and in particular seeking a new location for the loudspeaker my thoughts drifted towards the type of "infinite baffle" in which the loudspeaker is built into a wall thereby taking advantage of the large effective baffle area.

It then registered that a good enclosure of this type was available—the now disused chimney and fireplace. There would be no need to knock holes in the wall and the chimney would have enough volume to load the small loudspeaker available.

This was all theorising, since I could find no account of anyone having tried it out. So it was decided to find out the hard way. As it turned out the practical work was easy and only a few tools and a little time necessary.

The first step was to ensure that the open tops of the chimney were covered, or as the builders term it "capped". Next, to prepare the fireplace by filling in with brickwork except for a hole just large enough to take the loudspeaker (Fig. 1).

A square-shaped recess was made on the face of the brickwork around the hole, to take the small wooden board on which the loudspeaker was

mounted. This square-shaped recess was arranged by facing the brickwork with cement and leaving the recess the depth of the wooden board thickness. Possibly an expert mason could have prepared the hole so that the loudspeaker could be fixed directly on the wall.

The next step was to prepare the small wooden board from a hard wood, for mounting the loudspeaker, as in Fig. 2. This was made as small as possible, but stiff enough to secure the loudspeaker solidly to the wall. A small terminal block was fixed in a convenient position on the front of the board to take the loudspeaker connection.

Two small holes were drilled in the board for the wires from the loudspeaker to the terminals. These holes were just large enough to allow the wires to be drawn through under slight strain leaving no air gap in the hole.


When the loudspeaker had been fitted to the board and connections made to the terminals, it was only a matter of minutes to fix the board in position, with a screw in each corner (Fig. 2).

Before finally fixing the loudspeaker and board, I rolled up the pages of several newspapers into large wads and packed these up inside the chimney as far as I could reach. I wedged enough wads in position to ensure that soot and dust would not fall down the chimney. I found that this precaution did not affect the reproduction of the system.

A simulated log fire is normally placed on the fireplace surround, and this was most effective in screening the loudspeaker from view. This also reduced to the barest minimum the slight high frequency background hiss which is just perceptible on live radio transmissions, particularly when one is directly facing the loudspeaker cone. I did not place gauze or screening material over the board in front of the cone.

On testing, I did not quite expect such a revelation in sound. I had fitted a spare loudspeaker about 6 inches in diameter. Over the whole frequency range of a large orchestra, from the deepest bass to the highest scale of the violin, each instrument could be heard clear and distinct—the piano was certainly right in the room! The percussion instruments were clean and crisp even with the volume at a high level; no boom and the sound seemed to roll out—it was not forced out. Speech was excellent and such difficult sounds as clapping hands were heard just as they really are. Most people who have listened have been most impressed.

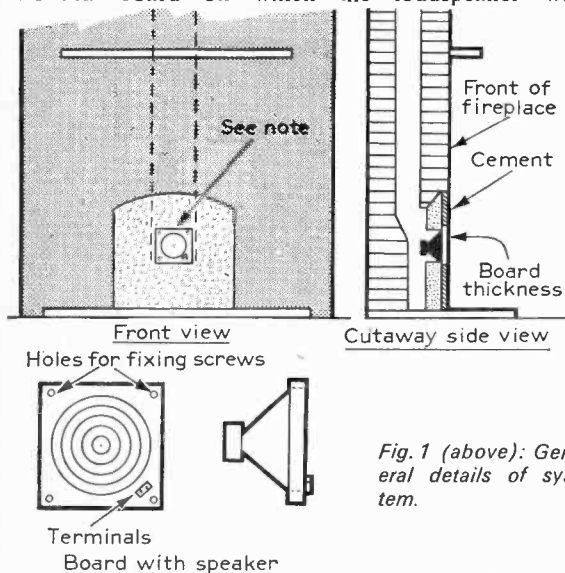Of course, I did check with the neighbour who shares the chimney stack if with the volume well up the sound level was noticeable. It was hardly perceptible in their room. This could have been the objectionable point to this system! ■





...High Fidelity Amplifier by Wharfedale

Yes, designed by Wharfedale in their own laboratory to extremely high standards, to take its place in the professional studio yet handsomely styled to be equally at home in domestic surroundings.

Wharfedale Amplifier TYPE No. WHF-20 incorporates every refinement to ensure that the programmes fed into it from your tuner, pick up or tape recorder are amplified with precise accuracy at all volume levels.

Every necessary control is incorporated but there are no gimmicks. Whilst the

technical expert will favour the flexibility of the controls and the reserves of power available, the layman will be delighted to find that here is a professional instrument that is easily controlled and handled.

To whet your appetite here is a brief specification:
Stereophonic high fidelity integrated control unit and power amplifier using silicon transistors throughout.

20 watts (continuous) per channel into 8 ohm load with total distortion of less than 0.2%.
Power response -3 db at 10 Hz and 50 kHz (Ref 0 db = 20 watts)
Tone control range ± 17 db at

40 Hz and ± 12 db at 10 kHz.
Filter slope variable from 0 db to 20 db per octave above 7 kHz.
Switched loudness control gives up to 10 db of bass lift at low volume control settings.
Disc input sensitivities of 3.5 mV or 50 mV (by switch) to match magnetic or ceramic cartridges.
Switched rumble filter -3 db at 40 Hz, -18 db at 20 Hz.
Tape input and output levels of 100 mV switched to allow tape monitoring.
Tuner and auxiliary inputs with 100 mV sensitivity.



For full details of this amplifier post this coupon now to:

**RANK WHARFEDALE
LIMITED
IDLE BRADFORD
YORKSHIRE**

NAME

ADDRESS

TOWN

COUNTY

PW.4

RANK WHARFEDALE LTD IDLE BRADFORD YORKSHIRE


LAFAYETTE HA-63 COMMUNICATION RECEIVER



Outstanding value. High-class 4 band receiver covering 550kc/s-31 Mc/s. Seven valves plus rectifier. RF stage, illuminated "S" meter, 1.5μV sensitivity. Electrical bandspread on 80/40/20/15 and 10 metre bands. Slide rule dial, aerial trimmer. B.F.O., A.N.L. Output for phones or speaker. 115/220/240V. A.C. Brand new, guaranteed, with manual. 24 Gns. Carr. 10/-

LAFAYETTE KT-340 COMMUNICATION RECEIVER SEMI-KIT

Build this wonderful receiver and save pounds. Supplied semi completed, main components ready mounted, R.F. section already wired and aligned. Full and precise instructions supplied. Specifications:—3 valves + rectifier, 4 bands covering 550kc/s-30 Mc/s. Incorporates 1 R.F. and 2 I.P. stages. 'Q' multiplier. R.F.O., A.N.L., 'S' meter, bandspread aerial trimmer etc. Operation 115/230V. A.C. Price 25 Gns. Carr. 10/-.

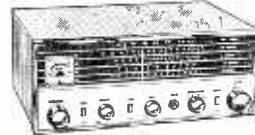

HAM-1, 4 BAND COMMUNICATION RECEIVER

4 wavebands covering 535 kc/s. to 30 Mc/s. 5 valve superhet circuit. Incorporates 8 meter B.F.O., BANDSPREAD TUNING, BUILT-IN 4in. SPEAKER, FERRITE AERIAL AND EXTERNAL TELESCOPIC AERIAL. Operation 220/240 v. A.C. Supplied brand new with handbook. £16.10. Carr. 10/-.

GARRARD RECORD PLAYERS

SRP12 Player mono £4.40; 1000 changer mono or stereo £5.19.6; 2000 changer mono or stereo £6.19.6; A50 Changer mono or stereo £7.10.0; 3000 Changer stereo £8.19.6; AT6 Mk II £9.19.6; SP25 Player mono or stereo £9.19.6; AT60 Changer mono or stereo £10.19.6; A70 less cartidge £19.19.6; LAB 80 Stereo £25.0.0; 401 Transcription 26 gns. Brand new and guaranteed. All plus post and packing 5/-.

MAIN LONDON AGENTS FOR CODAR EQUIPMENT

All items available as advertised.

SINCLAIR TRANSISTOR AMPLIFIERS

Z1P Amplifier 89/6; Z12 Power Pack 79/6; Stereo 25 Pre-Amplifier £9.19.6; Micro FM Radio Kits £5.19.6; Micro 4 Radio Kit 59/6; Micro Amp. Kit £8/6 Post Paid.



2-WAY RADIOS

Super quality. Brand new and guaranteed.

3 transistor £6.15.0 pr.
4 transistor £7.19.6 pr.
5 transistor £8.4.0 pr.
6 transistor £19.9.6 pr.

10 transistor £17.10.0 pr.
13 transistor £22.10.0 pr.

13 Trans. 1W £25.0.0 pr. Post extra.
These radios are operated in U.K.



TRANSISTORISED TWO-WAY TELEPHONE INTERCOM.

Operative over amazingly long distances. Separate call and press to talk buttons. 2-wire connection. 1000's of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. £8.10.0 pair. P. & P. 3/6.

ZQM TRANSISTOR CHECKER

It has the full capacity for checking on A, B and C.A. Equally adaptable for checking diodes, etc. Spec.: A: 0-7.0-9967. B: 5-200. 1cc: 0-50 microamps. 0-5 mA. Resistance for diode 200Ω-1 MEG. Supplied complete with instructions, battery and leads. £6.19.6. P. & P. 2/6.



P.C.R.1. RECEIVERS

Brand New Condition—Fully Tested and Checked before despatch. 3 Waveband with RF Stage—Wonderful value. 860-2080 metres 190-570 metres 5.6-18 Mc/s. with internal speaker £8.19.6. Carr. 10/6 with circuit. Plug in external power units. 230V A.C. 35/-, or 12V D.C. 19/6.

MAGNAVOX 363 TAPE DECKS

New 3 speed tape deck, superseded old Collaro studio deck. 2-track £10.10.0. 4-track £13.10.0. Carr. Paid.

AMERICAN TAPE

First grade quality American tapes. Brand new. Discounts for quantities.
3in., 225ft. L.P. acetate 4/-
3in., 600ft. T.P. mylar 10/-
5in., 600ft. std. plastic 9/6
5in., 600ft. L.P. acetate 10/-
5in., 1,200ft. D.P. mylar 15/-
5in., 1,800ft. T.P. mylar 35/-
5in., 1,200ft. L.P. acetate 12/6
5in., 1,800ft. D.P. mylar 22/6
5in., 2,400ft. T.P. mylar 45/-
7in., 1,200ft. std. mylar 12/6
7in., 1,800ft. L.P. acetate 15/-
7in., 1,800ft. L.P. mylar 20/-
7in., 2,400ft. D.P. mylar 25/-
7in., 3,600ft. T.P. mylar 58/6
Postage 2/- Over £3 post paid.

VARIABLE VOLTAGE TRANSFORMERS

Brand New—fully Shrouded. Input 230V. 50/60 c/s. Output 0-260 Volts.

1 Amp £4.10.0
2.5 Amp £5.17.6
5 Amp £9.0.0
8 Amp £13.10.0
10 Amp £17.0.0
12 Amp £19.10.0
20 Amp £32.10.0
2.5 Amp Portable—Metal Case with Meter. Fuses, etc. £9.17.6.

SILICON RECTIFIERS

200v. PIV. 200mA 2/6
200v. PIV. 6 amp 5/6
400v. PIV. 3 amp (SCR) 10/-
400v. PIV. 3 amp 7/6
1,000v. PIV. 50mA 6/6
800v. PIV. 500mA 5/6
800v. PIV. 5 amp 7/6
400v. PIV. 500mA 3/6
70v. PIV. 1 amp 3/6
150v. PIV. 165mA 1/-
150v. PIV. 25 amp 19/9
700v. PIV. 100 amp 49/6
Discounts for quantities. Post extra

PORTABLE OSCILLOSCOPE CT-52

A compact (9in. x 5in. x 16 1/2in.) general purpose 'scope T/B 10c/s-40 kc/s. Band width 1 Mc/s. Mullard DG 7/5 2 1/2in. CRT. For operation on 200/250v. A.C. Supplied complete with metal transit case, strap, test leads, and visor hood. Brand new. £22.10.0. Carr. 10/- Supplied complete with instructions.



F.M. WIRELESS MICROPHONE

94-104 Mc/s. Transistorised. Operates from 9v. battery. Complete with additional secret tie clip microphone. List £12.10.0. ONLY £7.10.0. P. & P. 2/6. These cannot be operated in U.K.

ERSKINE TYPE 13 DOUBLE BEAM OSCILLOSCOPE

Time base 2 c/s-750 kc/s. Calibrators at 100 kc/s and 1 Mc/s. Separate Y1 and Y2 amplifiers up to 5.5 Mc/s. Operation 110/230 volt A.C. Supplied in perfect working order. £22.10.0. Carriage 20/-.



LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYSER

2 PF—2,000 MFD, 2 ohms—2 Megohms. Also checks impedance, turns ratio insulation 200-250 v. A.C. Brand New £15. Carr. 7/6.



TE-20 RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 kc/s-250 Mc/s on 6 bands. Directly calibrated. Variable attenuator. Operation 200/240v. A.C. Brand new with instructions. £12.10.0. P. & P. 7/6. S.A.E. for details.

TE-900 20,000Ω/VOLT GIANT MULTIMETER

6in. full view meter. 2 colour scale. 0.25/10/250/1,000/5,000V A.C. 1/25/12.5/10/50/250/1,000/5,000 V. D.C. 0/50μA/110/100/500 mA/10 amp D.C. 0.2K/200K 20 Meg. Ohm. £12.19.6 P.P. 5/-.



TE22 SINE SQUARE WAVE AUDIO GENERATORS

Sine: 20 cps to 20k kc/s. on 4 bands. Square: 20 cps to 30 kc/s. Output impedance 5,000 ohms. 200/250v. A.C. operation. Supplied Brand New and Guaranteed with instruction manual and leads. £15 Carr. 7/6.



TRANSISTORISED F.M. TUNER



6 transistor, high quality, size only 6 x 4 x 2 1/2in. 3 I.F. stages. double tuned discriminator. Ample output to feed most amplifiers. Operates on 9v. battery. Covers 88-108Mc/s. Ready built, ready to use. Fantastic value for money. £6.19.6. P. & P. 2/6.

CLEAR PLASTIC PANEL METERS

First grade quality. Moving Coil panel meters, available ex-stock. S.A.E. for illustrated leaflet. Discounts for quantity. Available as follows: Type MR. 38P, 1 21/32in. square fronts.

100-0-100μA	27/6	200mA	22/6	100V D.C.	22/6
500-0-500μA	22/6	300mA	22/6	150V D.C.	22/6
1-0-1mA	22/6	500mA	22/6	300V D.C.	22/6
1mA	22/6	750mA	22/6	500V D.C.	22/6
2mA	22/6	1A D.C.	22/6	750V D.C.	22/6
5mA	22/6	2A D.C.	22/6	15V A.C.	22/6
10mA	22/6	5A D.C.	22/6	50V A.C.	22/6
20mA	22/6	10V D.C.	22/6	150V A.C.	22/6
50μA	32/6	22/6	22/6	300V A.C.	22/6
100μA	29/6	22/6	22/6	500V A.C.	22/6
200μA	27/6	22/6	22/6	50V D.C.	22/6
500μA	25/-	22/6	22/6	8" Meter 1mA	29/6
50-0-50μA	29/6				

POST EXTRA. Larger sizes available—send for list.

TE-51 NEW 20,000Ω/VOLT MULTIMETER

0 / 6 / 60 / 120* / 1,200V. A.C.
0 / 3 / 30 / 60 / 300 / 600/5,000V. D.C.
0 / 60μA / 12 / 300 MA. D.C.
0 / 60K / 6 Meg.Ω
85/- P. & P. 2/6.



MODEL TE-12

20,000 Ω.P.V. 0/100/500/120/600/1,200/3,000/5,000V. D.C. 0/60/120/600/1,200 v. A.C. 0/60μA/60/600 mA. 0/6K/600K/5 Meg.Ω Meg.Ω. P.P. £5.19.6. P. & P. 3/6.

MODEL 500

30,000 Ω.P.V. 0/12.5/10/25/100/250/500/1,000 v. D.C. 0/12.5/10/25/100/250/500/1,000 v. A.C. 0/50μA/5/50/1,000 v. D.C. 12 amp. D.C. 0/60K/6 Meg.Ω/60 Meg.Ω. £8.17.6. Post paid.

CALLERS WELCOME!

Open 9 a.m. to 6 p.m. every day Monday to Saturday. Trade supplied.

G.W. SMITH & CO

(RADIO) LIMITED

Phone: GERRARD 8204/9155
Cables: SMITHEX LESQUARE
3-34 LILE STREET, LONDON, W.C.2

IMPROVING CHEAP TAPE RECORDERS

W. S. FOWLER M.A.

SEVERAL types of inexpensive transistor tape recorder are at present on the market, at a price of four to five pounds. The general usefulness of these machines can be improved in a variety of ways.

Figure 1 shows the typical layout of such recorders. A simple single motor is almost invariably used to transport the tape past the record/playback head and on to the take-up spool. This motor is centrally pivoted and mechanically swung into contact with the rim drive mounting of the take-up spool. On rewind, the "rear" drive spindle of the motor is similarly swung to contact the rewind spool mounting.

In both operations, an electrical connection is made, at the same time, to a 3 volt or 6 volt cell unit which powers the motor. In the centre or rest position, when the recorder is "off", the two spindles of the motor provide slight pressure, thus acting as brakes and preventing tape spillage.

Conventional tape recorders employ a "capstan" system which regulates the speed of transport of the tape past the record/playback head (usually the speed is $1\frac{1}{2}$ in. per sec., or $3\frac{1}{2}$ and $7\frac{1}{2}$ in. per sec. for music). The simple spool drive system under consideration does not employ a capstan, and the speed of the tape therefore varies, becoming faster as the spool gathers more tape, thus increasing its own working diameter.

PAUSE CONTROL

The single motor drive, however, renders it a simple matter to provide an electrical "pause" system for the machine. The advantages of an electrically operated pause are:

1. It can be remotely operated, using a length of flex with a press button at the end.
2. It saves valuable battery power.
3. It saves tape (an important feature with the standard small 3in. spool).
4. It prevents awkward silences during pauses in speech when the tape normally continues to run.
5. It permits the machine to be used for dictation, and, on playback, allows the typist to keep in step with the dictation.

To fit the remote electric pause control, the positive battery connection to the motor should be broken at a convenient point. A miniature jack socket should then be fitted to the tape recorder. It is preferable to choose a non-metal part of the

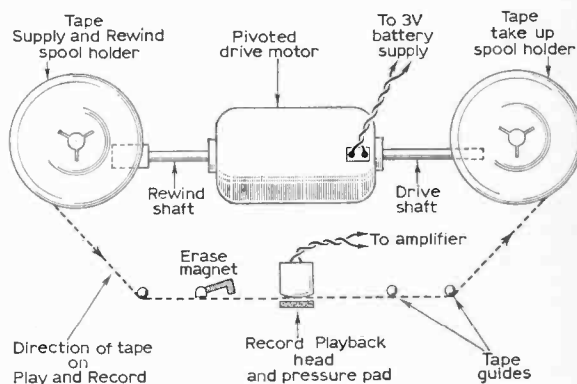


Fig. 1: Basic arrangement of tape transport system.

recorder as a fitting point, in order to avoid any accidental short-circuit through the metal chassis.

The broken lead should be connected with the battery side of the lead to one of the "make-break" contacts, and the motor side of the lead to the other contact. The battery lead is also joined to the "body" contact of the jack socket (the contact which is normally earth). To complete the pause control, a length of flex should be connected to a miniature jack plug. A small bell push, or similar press switch, is fitted to the other end of the flex.


When the jack plug is not inserted, the tape recorder functions normally. Inserting the jack disconnects the power supply from the drive motor, thus stopping the recorder. The reduction gearing effect of the drive system is such that stoppage is practically instantaneous. Pressing the push switch reconnects the power supply and the recorder resumes normal function, either on the record or the playback position.

SPEED CONTROL

A typical 3in. spool on a spool drive recorder results in a speed variation of from below $3\frac{1}{4}$ in. per second, at the start of the recording, to above 7in. per second at the end of the spool. Furthermore, the speed varies according to the initial centre diameter of the spool, which differs according to the make of spool. Further differences will result from the type of tape used, e.g., standard or long play tape. Different makes of machine also have different "basic" motor/drive speeds, which makes interchange of tapes impossible.

It is therefore desirable to have some means of

Fig. 2: Typical circuit of the type of tape recorder discussed in the text.

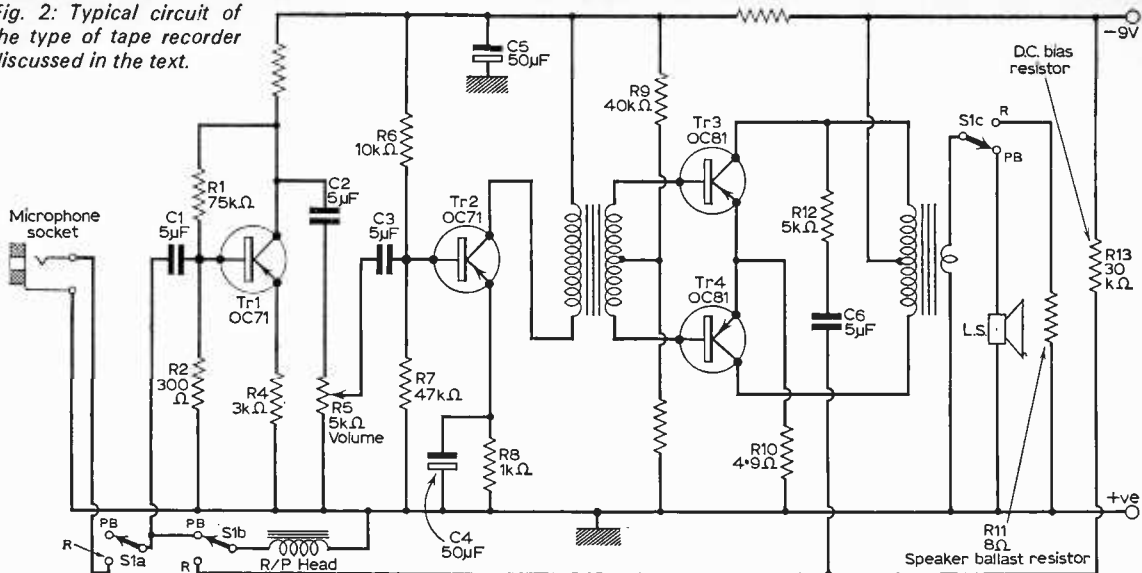

varying the tape speed on a spool driven recorder. This can be simply achieved by preparing a second jack plug for use in the "pause" jack socket. This second jack should have a small wirewound 10Ω variable resistor attached across it. Inserting the jack brings the resistance into the motor circuit and allows for control of speed for matching to a second recorder, or saving tape towards the end of a speech recording.

If desired the control resistance can be fitted permanently on to the tape recorder control panel. In this case, it is connected in series with the motor/battery positive lead. Some commercial spool driven recorders are now fitted with a speed control of this type.

SUPPRESSION

When considering the motor circuit, it is worth checking to see if a suppressor capacitor is fitted across the motor leads. Absence of this component tends to result in interference in the amplifier circuit, especially at the higher volume levels. A small paper capacitor of 0.05µF should be fitted if necessary.

A separate battery is usually employed to power the transistor amplifier (generally a 9 volt battery of the PP3 type). When the pause jack is inserted the motor drive batteries are disconnected, but the transistor amplifier circuit remains "on", and constitutes a useful 350mW amplifier in its own right.

AMPLIFIER CIRCUIT

The circuit of a typical transistor tape recorder (of this type) is shown in Fig. 2. The circuit is fairly conventional in all aspects. In the "record" position, the amplifier acts as a straight through circuit feeding from the microphone input. Loud-speaker output is disconnected and switched across a ballast resistor R11 to avoid feedback and consequent "howling".

The amplified signal is tapped from the primary of the push-pull output transformer and fed via an R-C network (C6/R12) to the record head. Some signal bias is necessary in all tape recording and

this is normally provided by a valve oscillator circuit. Portable transistor recorders often employ d.c. bias as a substitute and this is provided from the battery negative supply via R13. Some experimenting with the value of this resistor may improve the quality of the recording, and the signal-to-noise ratio.

A valve oscillator is also normally used to provide an a.c. voltage to the erasing head which cleans off previous recordings. In portable transistor recorders, a small permanent magnet usually fulfils the erase function (see Fig. 1). The position of this permanent magnet should be checked to ensure that it is brought up to the tape surface when the recorder is in the "record" position. It is important to check that the magnet is only operating against one half of the track, otherwise both tracks of recording will be erased simultaneously.

Permanent magnet erasure is less efficient and more "noisy" than a.c. erase systems, and it is a good idea to transfer the tapes to a "mains" type recorder occasionally, to clean-up used tapes more thoroughly.

USE OF THE AMPLIFIER SYSTEM

As has already been mentioned, the four-transistor circuit of the average portable transistor tape recorder constitutes a very useful small power amplifier in its own right. The inclusion of a miniature jack socket in series with the record/playback head enables this amplifier to be used independently of the recording function of the unit. This can then form the basis of a small radio receiver, by the use of a diode jack.


Alternatively a one-transistor r.f. reflex circuit, deriving its power requirements from the tape recorder itself, works well from a ferrite slab to form an acceptable portable radio. Programmes can of course be recorded while the machine is also being used as a receiver.

The portable transistor tape recorder also contains all the essential elements of a 45 r.p.m. transistor record player, and details of these adaptations may be given in a subsequent article. ■



SR.550. Professional Communications Receiver

**the
complete
range of**

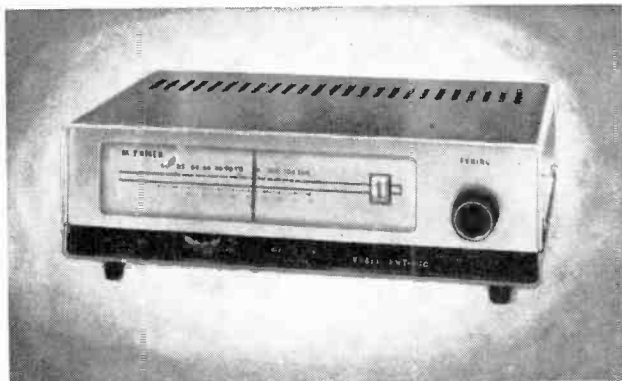


FMT.640. High Fidelity F.M. Tuner

When the "Eagle" Brand was launched 10 years ago it was impossible to foresee that in such a short time the range would grow to cover over 500 items, all carrying the "Eagle" name. Whether you are interested in Hi-Fi, Amateur Radio, Do-it-Yourself projects or any field of Electronics, "Eagle" offer you the widest choice of sensibly priced products and by the end of the year we plan to increase our range to cover the formidable total of 700 items.

If you would like to study our entire range in the leisure of your home we will be delighted to send you our catalogue free of charge or why not ask your local dealer (there are over 6,000 "Eagle" stockists) to show you the latest "Eagle" Products today!

**have
you
seen...**

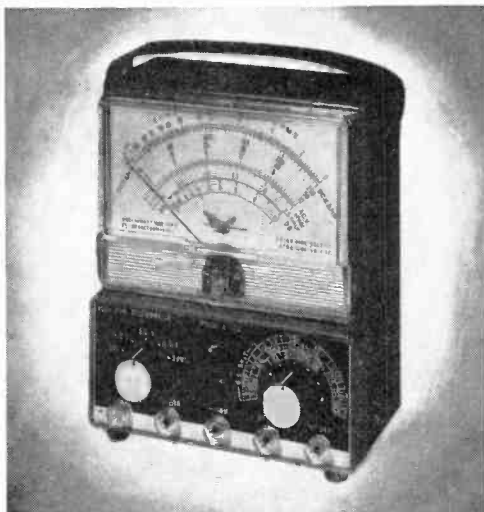

K.140. Professional Volt-Ohm-Milliammeter



**EAGLE
products**

To: EAGLE PRODUCTS, Dept. PW.4,
Coptic Street, London, W.C.1.

Please send me catalogue of the entire "Eagle"
range.

Name

Address

The Mountain climber needs a . . .



The Explorer needs a . . .

Without the guidance of a Home Radio Catalogue, the radio constructor might as well give up before he begins! The publication lists clearly some 6,000 components with over 1,000 of them illustrated; and as each catalogue contains 5 vouchers, each worth one shilling if used as directed, and is sold at the modest price of 7/6 (plus 1/6 P. & P.) it is almost a gift!



Gracer from Tooting (wishing he'd studied radio a bit more)

*Impenetrable Jungle**

* Don't ask us, . . . we don't know how he penetrated the impenetrable!

and the
Radio Constructor
needs the
Home Radio
Catalogue



Please write your Name and Address in block capitals

NAME

ADDRESS

HOME RADIO LTD, Dept. PW, 187 London Rd, Mitcham, Surrey, CR4 2YQ

Send the coupon
with your cheque
or P.O. for 9/-

This Martin Recordakit

is designed specially for the MAGNAVOX 363


3 WATTS OUTPUT

3 SPEEDS: 7" REELS
OUTLET FOR HI-FI AMP


SOLDERING NOT
NECESSARY

SEPARATE RECORDING
LEVEL AND VOLUME
CONTROLS

You need a MARTIN RECORDAKIT to do full justice to this excellent deck. With it, you will have a 2 or 4 track instrument of outstanding quality and dependability. MARTIN RECORDAKITS consist of basic Martin units assembled and tested, making it necessary for you simply to fit and connect in accordance with the detailed instructions book supplied. When built, your 3 speed Martin Recorder appears as shown here. The lid is detachable. Case with speaker, and deck also available. Details on request. MARTIN RECORDAKITS have long been famous for their high performance standards, quality of materials, simplicity and dependability. The latest is the best yet.

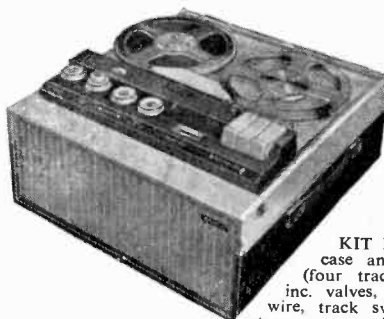

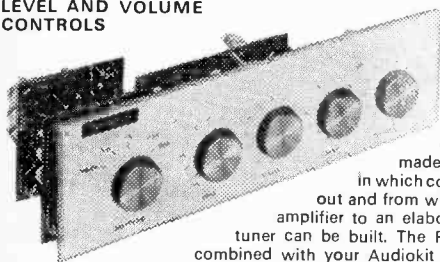KIT M4 less case and deck (four track) but inc. valves, screws, wire, track switching etc. £15.19.6
KIT M2 less case and deck (two track) but incl. valves, wire, screws, etc. £14.19.6



THE UNITS THAT ENABLE YOU TO BUILD BY STAGES FROM PRE-AMP TO A HI-FI STEREO/FM ASSEMBLY

Martin Recordakits and Audiokits are obtainable from good stockists everywhere. In cases of difficulty please write direct. Trade enquiries invited.

MARTIN ELECTRONICS LTD 154/155 HIGH ST., BRENTFORD M'SEX Phone: ISLeworth 1161/2

Martin Audiokits for Hi-Fi

The uniquely reliable kits with "Add-on-ability"

No other system allows you to enlarge your installation stage by stage as Audiokits do. They comprise a wide range of very well made prefabricated transistorised units in which connections are standardised throughout and from which anything from a simple straight amplifier to an elaborate hi-fi stereo amplifier with FM tuner can be built. The Recordakit described above can be combined with your Audiokit assembly if you wish.

- 5-Stage input Selector £2.7.6
- Pre-amp/vol. control £1.17.6
- Pre-amp/tone controls £3.2.6
- 10 watt amp. (3 ohms) £5.12.6
- 10 watt amp. (15 ohms) £6.12.6
- Mains power supply £2.15.0
- FM Tuner £12.17.6

MARTIN ELECTRONICS LTD

154 High St., Brentford, Middlesex

Full details of ☐ Recordakits ☐ Audiokits please

NAME

ADDRESS

(Block letters)

P.W.47

practically wireless

commentary by HENRY

No. 32

Cybernetic
Serendipity

COLLECTORS of electronic snippets will have been well rewarded during the past few months. This column has picked out the curious and the exotic from the swelling heap of scientific announcements and suffered for its pains by accusations that Henry occasionally stretches the pure white elastic of truth.

But truth is stranger than science-fiction in these days, when even a humble doorbell is re-christened an "electronic indicator". There is no need for literary invention when so much of the real stuff proliferates.

Our title, for instance. That is no pleasant fancy dreamed up in a Scrabble session. The Institute of Contemporary Arts is trying to raise thirty thousand quid to put on an exhibition of computer art. This dream-child was spawned when an Atlas computer went wrong and programmers found they could draw pretty pictures with the read-out symbols.

Now they compete for the honour of the most way-out design. We have had kinetic art and psychedelic art, so why not put some of our ageing electronic oddments to use in the furtherance of culture?

This would have been better than scrapping poor Humphrey, who, you may remember, was

sold to a Liverpool scrap merchant for fifty pounds because he couldn't do his sums rapidly enough. Humphrey was a cool £47,000 only five years ago when the U.S. Navy handed him over to Belfast University. But a computer that takes a week to do sums (even though those sums would take the traditional ten men ten years with ten pens etc . . .) is sadly unwanted and Belfast handed him back. The Navy, in the best traditions of the senior service, passed Humphrey on to the Air Force, and they say they made 200 enquiries in Britain before shuffling him off to a willing "Steptoe".

We wonder if he couldn't have been better employed choosing the Rag Queen for Dudley College of Education last December. The Rag Committee tried to take the element of "bitchiness" from their search for an ideal woman. Old hands at the electronic game could have warned them that they would probably come up with a female gorilla, like the other students who used a computer for a matchmaking experiment.

No wonder the two computer matchmaking companies have been wrestling matters out in a court of law to decide who had the right to a trade mark. Serendipity indeed!

At the other end of the scale, the minuscule electronic oddment is claiming its share of the news. Little pumps that stimulate and regulate the heartbeat, transceivers that work their way around the body while "Dr. Kildare" and his cronies study screens in a control room instead of creeping around those other screens in the ward.

We heard the tale of the elderly gents in a south-western hospital who made a concerted beeline for the loo at odd times and puzzled the boffins. It was



Man the ——— boats!

worked out that the electronic stimulators inserted to assist their bladders were being triggered off by the v.h.f. signals from the local lifeboat station.

As I write, there is a chappie waffling about "the Nirvana of Science" on the BBC Home Service. Soon, he says, when man thinks of God at all, he will think of him as a computer. Man, after all, is a biped whose activities are regulated by a computer that sits above his shoulders. He had better tell that to Dr. Taylor of University College, who has been slogging away at an analogue model of the electro-chemical processes of learning and has come up with a "brain" of 4,000 electronic neurons which is just able—after all their hard work, to differentiate between the sexes.

For the scoffers who imagine that Henry is trying to do a Fred Hoyle, another item of news from that prosaic body, the Electronic Engineering Association. They have drawn up a Code of Practice for laser systems. The day of the death ray is not only on us, it is passing us by. They warn against leaving the covers off equipment, citing an example of laser beams from quite modest apparatus that invisibly cuts a block of wood at forty feet. They advise, with deadpan humour, that ". . . great care should be taken to ensure that members of the public cannot stray into the beam".



Makes a change, doesn't it!



A DUAL

DUAL CONTROL INTERCOM

MIKE FISHER

ONE of the advantages of this solid-state intercom system is that the amplifier is switched on only when communication takes place. This makes it possible to operate the unit from a small battery and does away with the need of a mains power supply. A block schematic diagram of the intercom is shown in Fig. 1. As you can see, the two relays (RLA and RLB) are used to switch the amplifier on and to determine the direction of communication. The speakers are, of course, also used as microphones to save space and keep the cost down. Each relay has three functions: 1 to supply nine volts to the amplifier; 2 to select which speaker unit

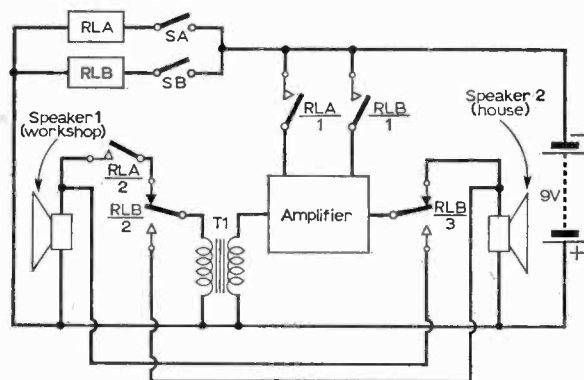


Fig. 1: Block schematic diagram of the complete intercom. Note how the relays are used to switch the speakers so that either one can be used as a microphone.

is to be used as the microphone; and 3 to connect the appropriate speaker to the input and output of the amplifier.

A circuit diagram of the amplifier is given in Fig. 2. For the purposes of explanation consider call button switch SA has been depressed. This energises relay RLA, which in turn causes the relay contacts RLA 1 and RLA 2 to change position. The first contact connects nine volts to the amplifier and the second connects the "workshop" speaker to the input transformer. As the other relay RLB is not in circuit (until call button SB is depressed), the "house" speaker is connected to the output of the amplifier, thus completing the communication path from the "workshop" to "house".

Should the "house" call button SB be depressed at the same time, relay RLB energises, and provides a secondary path for the nine volts to the amplifier. Also, contacts RLB 2 and RLB 3 change the speakers over so that the "home" speaker becomes a microphone and the "workshop" speaker is connected to the output of the amplifier.

With only the "house" call button depressed, the "house" speaker is connected (as a microphone) to the input transformer via RLB 2, the "workshop" speaker is connected to the output of the amplifier

★ components list

Resistors: (All $\frac{1}{2}$ watt, 10% carbon)

R1 82k Ω	R5 22k Ω	R9 8.2k Ω
R2 10k Ω	R6 10k Ω	R10 180 Ω
R3 5.6k Ω	R7 220 Ω	R11 22k Ω
R4 1k Ω	R8 1.2k Ω	
RV1 10k Ω pre-set skeleton miniature		

Capacitors: (All 15VW sub-min electrolytics)

C1, C3, C4 16 μ F	C2, C5, C6 50 μ F
-----------------------	-----------------------

Transistors:

Tr1, Tr2 OC75 (Mullard)
Tr3, Tr4 OC72 (Mullard)

Transformers:

T1 Step-up transformer, matching 3 Ω to approx 1,000 Ω . This transformer <i>must</i> be fully screened
T2 Radio Spares type TT1, ratio 1:1
T3 Radio Spares type TT2, ratio 6:1

Relays:

RLA 2 pole change-over, 6 to 9 volt coil, any coil resistance (prototype 680 Ω)
RLB 3 pole change-over, 6 to 9 volt coil, any coil resistance (prototype 680 Ω)

Miscellaneous:

Two moving coil 3 Ω speakers; two single-pole, two-way switches; a 9-volt battery; wire, insulated sleeving, Veroboard, etc.

via RLB 3, and power is applied to the amplifier via RLB 1. Operating the "workshop" call button with the "house" button depressed, has no effect on the path of communication.

Strict privacy is achieved with this system, since a call button has to be operated before communication can take place.

THE CIRCUIT

As loudspeakers are low impedance devices, it is necessary to step-up the impedance when they are used as microphones. This is done with T1, a microphone transformer having a primary of about 3 Ω and a secondary of around 1000 Ω . The ratio is not critical, but the transformer must be of the screened type. The wiper arm of the volume control, which is across the secondary of the microphone transformer, is coupled by C2 to the base of the first transistor Tr1. The output of this stage is also capacitively coupled to another common emitter amplifier Tr2, which functions as a driver.

Transformer T2 is used to split the audio signal so that Tr3 and Tr4 can operate as a push-pull

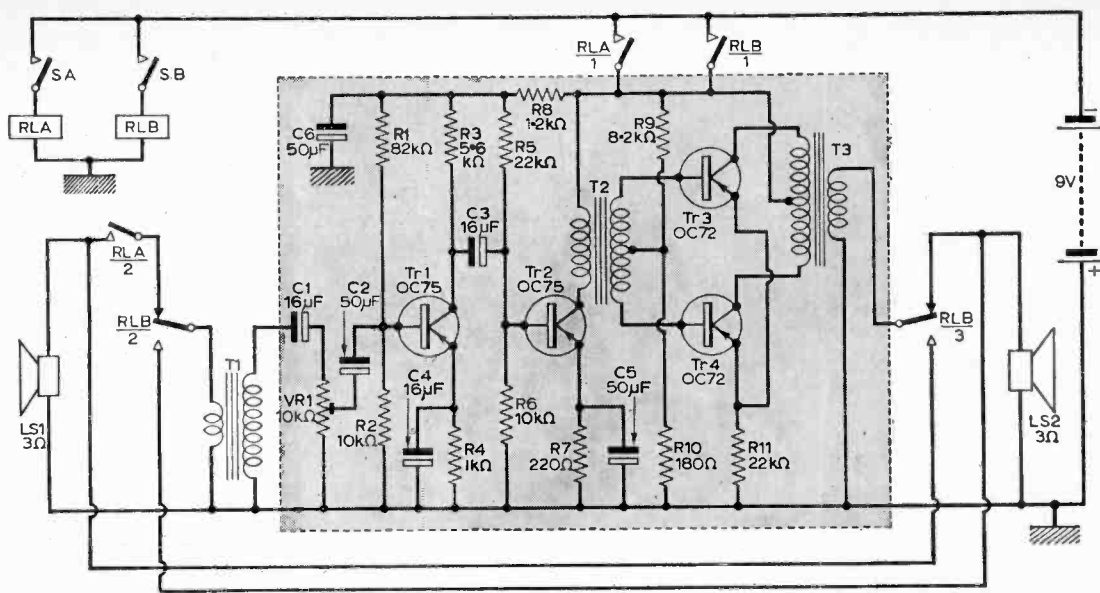


Fig. 2: Circuit diagram: the items within the dotted box are mounted on the Veroboard.

pair into the output transformer T3. This has the opposite function to the microphone transformer in as much as it has to step-down the impedance to match the 3Ω speakers. Most of the other components in the circuit are self-evident. For example, the potential dividers R1 and R2, R5 and R6, and R9 and R10 are incorporated to bias the transistors; R8 and C6 have been included to prevent instability.

This amplifier has been built for speech only and if one wishes to put music through it, a negative feedback loop should be fitted to improve the frequency response. Connections should be made from the secondary of T3 to the base of Tr2.

CONSTRUCTION

All the amplifier components are vertically mounted on a piece of Veroboard. Start construction by cutting the panel to size and breaking the copper strips as shown in Fig. 3. Now make the holes for mounting T2 and T3, using a fret-saw with a small

metal-cutting blade. These blades are quite cheap and are small enough in diameter to go through the holes in the Veroboard.

Start assembly by mounting T2 and T3 on the blank side of the Veroboard and soldering their mounting lugs to the copper strips on the other side, taking care to mount the two transformers the right way round. Next, wire up the transformer leads as shown in Fig. 3. Then take the 'skeleton' pre-set variable resistor, RV1, and carefully file down the mounting lugs, reducing their width until they will fit in the holes in the Veroboard. Again, mount RV1 on the blank side of the panel and solder the lugs to the copper strips on the other side.

Now, wire up the rest of the circuit as shown, remembering that all components are mounted vertically. Take care to mount the electrolytic capacitors with the polarities as shown, and make sure that you use heat shunts when soldering in the transistors; it is good practice to make sure that the transistor leads are tinned before any attempt is made to solder them to the Veroboard.


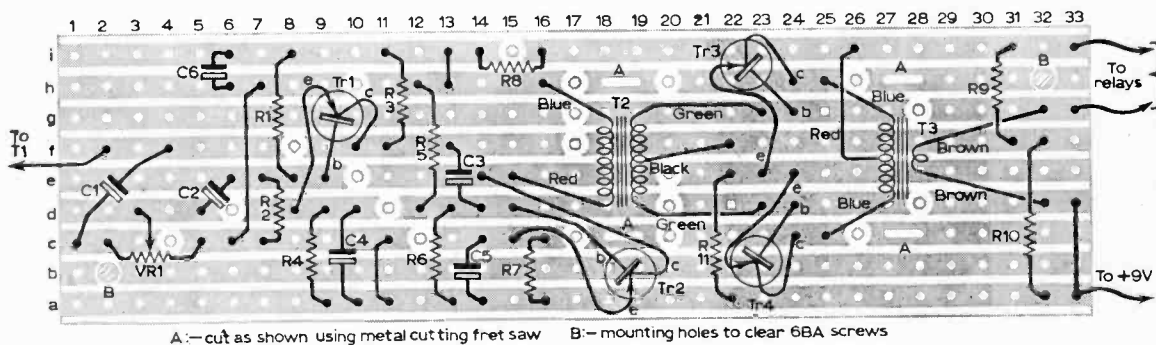


Fig. 3: Component layout diagram, showing theoretical components upon the Veroboard. In fact, all components are vertically mounted on the board to save space. One must be careful about the colour coding of the transformers T2 and T3, since the coding may only hold true for the types specified in the components list.

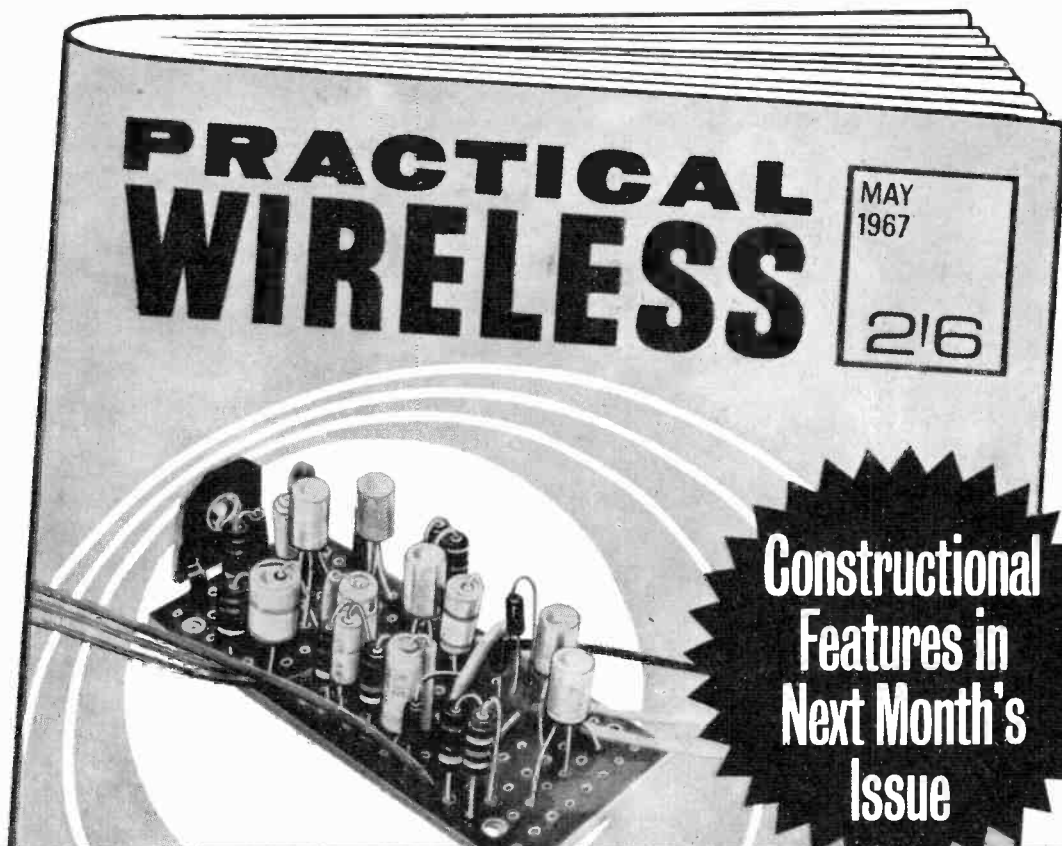Two mounting holes can be drilled in the Veroboard so that the panel can then be screwed to a chassis, using small rubber grommets as insulators. The rest of the unit, i.e., the relays, switches, speakers and T1, can be wired up to suit individual needs.



MULTI-PURPOSE AUDIO SWITCH

Extremely sensitive 5-transistor unit assembled on Veroboard and designed so that normal voices operate the "switch" at a range of up to 30ft. May be used for (either to switch on or off) radio, TV, lighting, heating equipment, tape recorders, dictation machines, etc.

BEGINNER'S 3-BAND MAINS RECEIVER
2-valve reflex receiver for headphone reception, using plug-in coils. Instructions included for winding coils for medium and short-wave bands. Optional wave-change switch.

CONVERTER FOR 70cm BAND
3-valve design for "hams", using an E88CC in the front end and two 6060 valves for mixer and crystal-controlled oscillator; i.f. output 12-14Mc/s. "Open type" construction on sheet copper simplifies assembly.

SIMPLE ANALOGUE COMPUTER
This inexpensive unit, using a minimum of components, can be quickly and simply assembled and calibration of main controls easily carried out. A centre zero meter is used as indicator.

**MAY ISSUE
ON SALE APRIL 7th**


**ORDER NOW! Hand this
Form to your Newsagent**

TO
(Name of Newsagent)

Please reserve/deliver the May issue of PRACTICAL WIRELESS (2/6) on sale April 7th, and continue until further notice.

NAME

ADDRESS

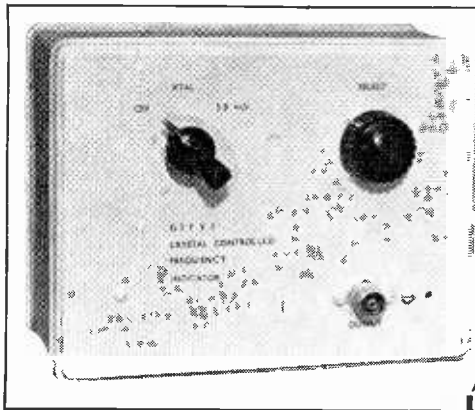

CRYSTAL CALIBRATION MARKER

A. S. CARPENTER G3TYJ



BUILT to provide accurate "marker pips" over the various amateur bands this compact and completely self-contained unit has proved invaluable for locating band edges and intermediate points. The output from the unit when fed to the aerial socket of a radio receiver may be tuned in, amplified and detected in exactly the same way as any normal radio frequency signal. Lack of modulation is unimportant and may even be beneficial since, if the receiver used is of the "communications" type fitted with a signal strength meter, there will be visual indication of the presence of the marker signal, whilst the beat frequency oscillator may be used to facilitate aural recognition.

Although the frequency of operation chosen for the marker signal may be any that lies within the

say 1,500kc/s (3f), a marker "pip" will be heard as it will be again at 2,000kc/s. The marker signal becomes progressively weaker as the receiver is tuned higher in frequency but may still be found at 20Mc/s or so depending on the sensitivity of the receiver used. Tests made using the prototype marker in conjunction with a RA-1 Amateur bands receiver enabled easy recognition of the signal to over 30Mc/s and this may be considered adequate for most amateur purposes.

Dividing the main markers

Marker pips at 500kc/s intervals although useful do tend to leave rather large uncalibrated frequency gaps on a receiver scale. The popular 80-metre band for example extends from 3,500 kc/s to 3,800 kc/s and although a marker signal pip would permit location of one end of this band (3,500kc/s) no further indication would result until the receiver was tuned to 4,000kc/s, and similar conditions exist on other bands available to amateurs: because of this it is beneficial to have optional perhaps, available. The intermediate marker pips at 50kc/s points would make possible location of both 80-metre band edges for pips would be heard at 3,500, 3,550, 3,600kc/s, and so on every 50kc/s, with the band edge at 3,800kc/s identifiable. A complete frequency marker may thus conveniently comprise two complementary sections, an oscillator providing main marker points with the other section sub-dividing them.

Generating the fundamental marker frequency with any degree of accuracy requires use of a crystal-controlled oscillator but it is beneficial to have a limited manual control over the frequency of the dividing oscillator.

The complete circuit of the prototype crystal-controlled frequency marker is shown in Fig 1, the section around Tr1 functioning as the main crystal oscillator operative at a frequency of 500kc/s. No tuned circuit is employed and this is desirable for it is not uncommon for some such oscillators to "take off" at as spurious frequency; some in fact will oscillate freely with no crystal in circuit. In this particular section output is made available at socket Sk1 when S1 is rotated to position 2.

When S1 is further rotated to position 3 the circuitry associated with Tr2 commences to function, this being the dividing oscillator. Here, Tr2 is arranged conventionally as a feedback oscillator,

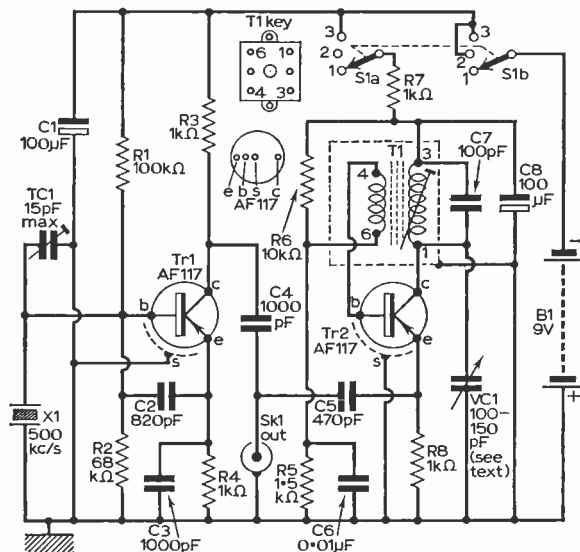


Fig. 1: Complete circuit of the marker.

tuneable range of the receiver it is generally convenient to generate it at a comparatively low frequency and use harmonics present to calibrate higher frequency points. For example, if the chosen fundamental operating frequency for the marker is $f = 500\text{kc/s}$, harmonics will occur at $2f$ (1,000kc/s) $3f$ (1,500 kc/s) and so on, therefore when the associated receiver is tuned to,

collector/base positive feedback occurring when the windings of T1 are connected as shown. Unlike the 500kc/s oscillator this stage is tuneable over a restricted frequency band, panel-controlled VC1 being included for the purpose. Variable tuning is desirable since in practice Tr2 (which is not allowed to function unless Tr1 is operative) may be made to fall in step with the crystal oscillator at a division frequency and although capacitors C4 and C5 are the respective output "blockers" the two in series connection, do enable the repetition frequency of the Tr2 circuit to be suitably "locked". Various "locks" depending mainly on the setting chosen for VC1 are possible in practice, hence the need for variability of tuning; this point will be mentioned later.

An alternative type of crystal oscillator circuit is given in Fig 2, and this may be substituted for the circuitry around Tr1 if preferred. Feedback is secured via transformer T1 which is a sub-miniature item of the type used as the final i.f. transformer in a conventional transistor superhet receiver; capacitor Cx is prefitted. In practice the onset of oscillation is sudden when the transformer dust core is rotated to the correct operating point, but excessive core rotation results in oscillation ceasing equally abruptly. Transistor types other than that specified may be used in this circuit and the OC44 and OC45 will function, however the original circuitry is preferred.

In the prototype, work is simplified by making use of a miniature 18-way tag board and this carries the bulk of the assembly. The tag board is eventually secured to the front panel—the inside of the lid of a metal box. When the lid is placed on the box itself all items including the battery, are suitably protected with the mass of the metal container assisting in maintaining a constant temperature to aid stability. Any small metal box approximately $6\frac{1}{2} \times 5 \times 2\frac{1}{4}$ in. is suitable but if it is of tin the lid should be reinforced internally with a rectangle of aluminium.

Wiring of the tag board is shown in Fig. 3 with panel details indicated in Fig. 4. It is beneficial when fitting T1 to bend the lugs of the screening can

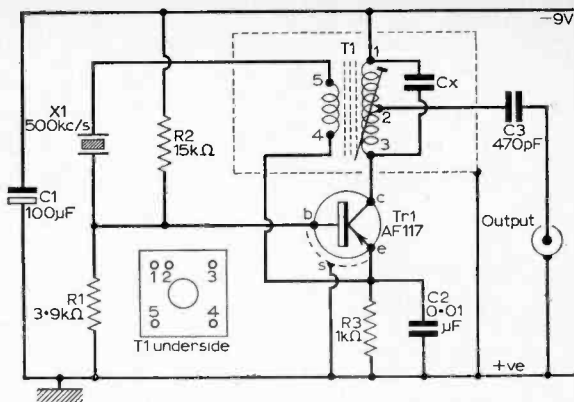


Fig. 2: Alternative circuit for the Crystal Oscillator.

outwards to coincide with holes and tags Nos. 2 and 35 on the board. Self-tapping screws hold the can securely yet permit its removal at any time without having to disturb the transformer wiring.

The on/off/function switch S1, together with VC1 (which may be any small variable capacitor of 100-150pF) and Sk1 are mounted on the lid of the box and the wiring for these items is given in Fig. 5. In the prototype a miniature 4-pole 3-way rotary switch is used for S1, the unrequired tags being left unconnected. Two stiff 'Stay' wires of 16s.w.g. copper wire are connected to the board as shown, bent to a convenient angle and soldered to the inside of the box lid to hold the whole assembly rigid; this is quite satisfactory since negligible weight is involved.

Testing

Test each oscillator separately to make sure functioning is correct. If an oscilloscope is available this is easily carried out by examining the outputs at capacitors C4 and C5. In other cases a receiver may be used when signals from the crystal oscillator should be tuneable at any multiple of 500kc/s. In cases of non-oscillation and assuming

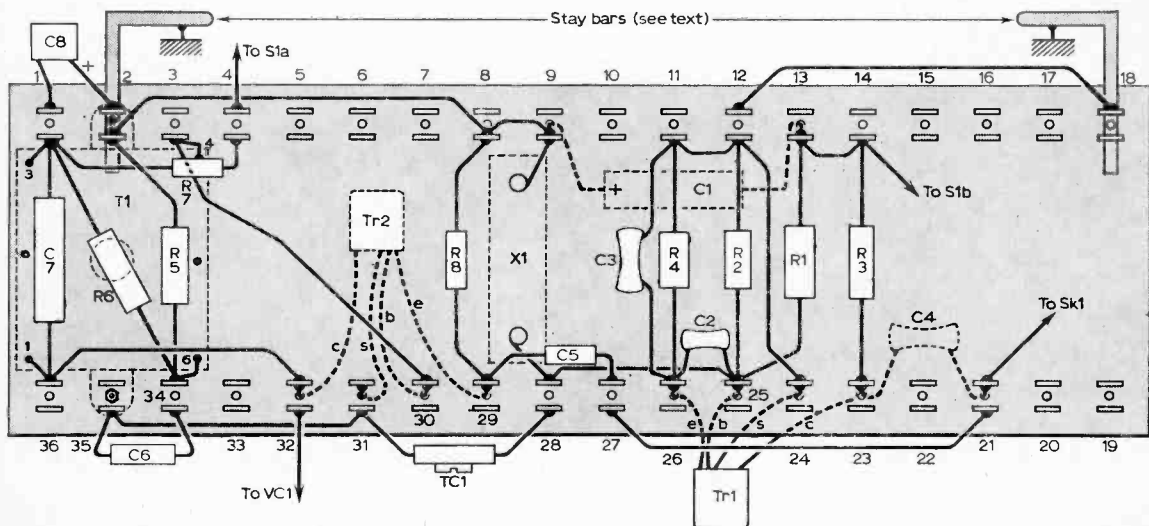


Fig. 3: Layout and wiring of the tag board. Components shown dotted are on the reserve side.

the crystal itself to be above suspicion, slight changes to component values in the section may be required—or trimmer TC1 may be excessively engaged. If the alternative crystal oscillator circuit of Fig. 2, is in use non-oscillation may well be due to the core of T1 being incorrectly set. During these tests the current drain should be monitored

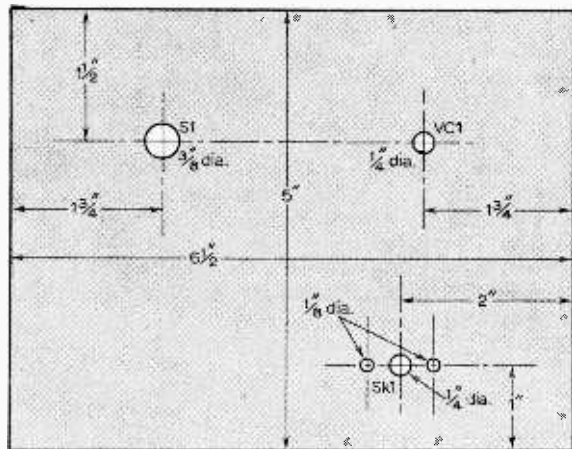


Fig. 4: Essential panel details.

and should be approximately 4mA when both oscillator and divider are functioning simultaneously.

The accuracy of the crystal oscillator should be checked against a receiver tuned accurately to either MSF transmissions on 2.5 or 5.0Mc/s, or the Light programme on 200kc/s may be used, preferably when no modulation is present. The marker signal should be made to beat with the selected frequency standard precisely and trimmer TC1 may prove useful in this respect.

Adjusting the divider

With S1 set to position 2 the marker signal is tuned in accurately on a receiver switched to a comparatively low frequency band—say 80 metres. A marker pip should be heard at 3500kc/s and another at 4000kc/s. The 3500kc/s point is chosen and the b.f.o. switched in, and allowed to stabilize after which S1 is rotated to position 3. The signal may now suddenly sound “dirty” or unstable, indicating that Tr2 is not functioning at an exact division frequency relative to 500kc/s. By carefully adjusting VC1 control knob however the note heard will suddenly seem to ‘purify’ or ‘sweeten’ itself as a lock is obtained. If the receiver is now tuned slowly towards the 4000kc/s marker point a number of additional equally spaced pips should be heard and these should be counted. Ignoring the original pips at 3500 and 4000kc/s a total of *nine* intermediate pips should be heard for correct functioning. At the first attempt however a different number may be heard—say four, or eight. When this occurs the original 3500kc/s marker should be re-sought and a fresh lock found by means of VC1 as already described. It may be found that a lock holds on over several degrees of tuner knob rotation before the signal becomes unstable again and before the next lock point is found; the correct position for the control in such cases is midway between “ends of lock” rotation.

Should eight intermediate marker pips be obtainable with the control knob of VC1 at either end of its travel, the core of T1 may be slightly adjusted or a different value chosen for C7. If possible the nine locks required should be obtainable when VC1 is at mid-travel.

With the construction, setting up and housing com-

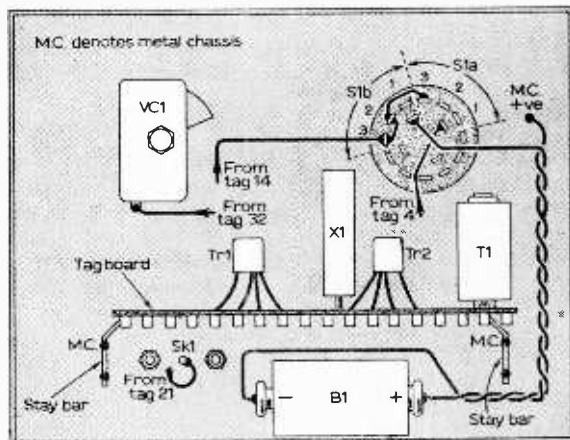


Fig. 5: Rear of panel layout and wiring.

pleted an accurate source of band edge marking is available provided care is taken thereafter with the instrument. A coat of lacquer, some neat lettering by means of Letteraset symbols, transfers, or freehand, and an attractive addition to the station is made available at but small overall cost.

★ components list

Resistors:

R1	100kΩ
R2	68kΩ
R3	1kΩ
R4	1kΩ
R5	1.5kΩ
R6	10kΩ
R7	1kΩ
R8	1kΩ
10% 1/8W	

Capacitors:

C1	100μF 15V electrolytic
C2	820pF silver mica
C3	1000pF silver mica
C4	1000pF silver mica
C5	470pF ceramic
C6	0.01μF paper
C7	100pF silver mica
C8	100μF 15V electrolytic
VC1	150pF variable (see text)
TC1	15pF Beehive trimmer

Miscellaneous:

500kc/s crystal two-pin 10X based (Henry's Radio).
T1—Denco type BF02-85. Miniature 4-pole, 3-way rotary switch (see text). Metal box approximately 6 1/2 x 5 x 2 1/2 in. Coaxial socket. Knobs (2). Miniature 18-way tag board (Radiospares). Battery, type PP4. Pair battery stud connectors.

Alternative items when circuitry of Fig. 2 is used

Resistors

R1	3.9Ω
R2	15kΩ
R3	1kΩ

Capacitors:

C1	100μF 15V electrolytic
C2	0.01μF ceramic
C3	470pF silver mica

Transformer:

T1 Denco sub-miniature transistor-type i.f. transformer, type IFT14.

Transistors (both circuits):

AF117, OC44, OC45

repairing radio

★ The idea behind this new series of articles is to divide the receiver into sections and then deal with each section separately in terms of fault symptoms and diagnosis. The series will comprise six articles dealing with valved equipment and six articles covering transistor counterparts.

The writing will be handled by two well known technical authors. Gordon J. King will take care of basic fault finding in the electronics side and H. W. Hellyer will discuss servicing procedures, workshop methods and mechanical aspects.

Gordon J. King starts the ball rolling this month with Part 1.

THE FRONT END

The first electronics section to be considered is composed of the aerial, r.f. and frequency-changer stages, these being "the front end" of a set. All sets have an aerial circuit, but not all an r.f. stage. Usual a.m. practice caters for the aerial signal direct to the frequency-changer input, excepting highly sensitive a.m. models and most domestic f.m. sets where r.f. amplification is common.

The frequency-changer mixes the tuned aerial signal with a locally generated signal called the local oscillator signal, and the difference-frequency signal, called the i.f. signal, is developed at the frequency-changer output. The frequency-changer thus comprises two parts, the local oscillator and the mixer.

The first section is given in block diagram in Fig. 1 (a) without an r.f. stage and (b) with an r.f.

stage. Fig. 2 shows at (a) the first section circuit of an ordinary domestic-type a.m. set without r.f. stage and at (b) the equivalent circuit of an f.m. tuner using an r.f. stage.

In the a.m./f.m. set, the mixer of the a.m. frequency-changer is often switched as extra i.f. amplifier on f.m., looked at in the next "electronics" instalment.

Fig. 1a should be related to Fig. 2a. The aerial circuit of the latter includes the coils and switch sections up to the first grid of the hexode section of frequency-changer valve V1. VC1 is the aerial tuning gang section, handling the signal frequency (f_s). The main aerial signal (f_s) is applied through C1. Note the use of a capacitive aerial in this circuit, coupled to the secondary of the aerial coupling transformers. The primary windings couple



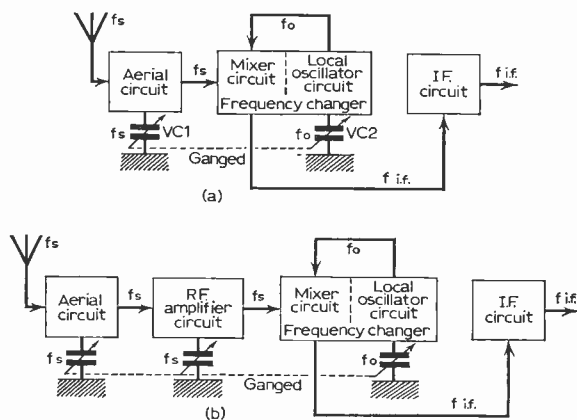


Fig. 1: (above) (a) Block diagram of superhet front-end less r.f. stage. (b) front-end block diagram with r.f. stage. f_s is signal frequency, f_o oscillator frequency and $f.i.f.$ is the intermediate frequency.

Fig. 2: (right) (b) Tuner of f.m. set or Band II front end of an a.m.—f.m. set.

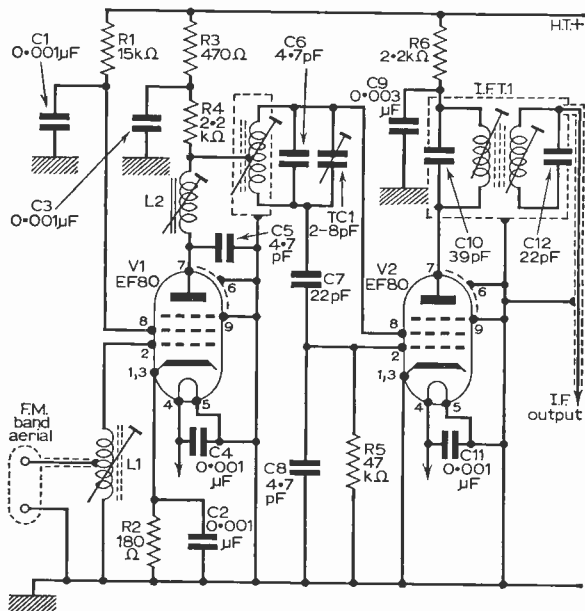

sets

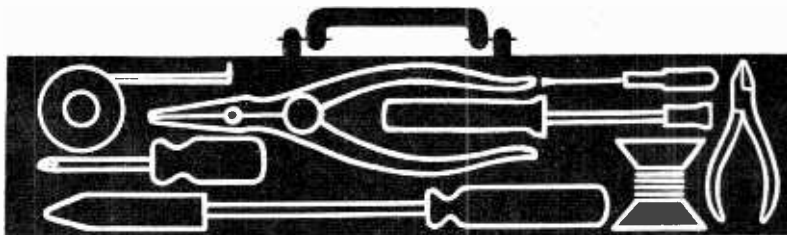

H. W. HELLYER & GORDON J. KING

in the main aerial, as is normal practice.

The local oscillator circuit comprises the triode of V1 and associated tuned and switched transformers between grid and anode. The local oscillator signal (f_o) is tuned by VC2 section of the gang.

The mixer hexode section thus receives f_o from the aerial circuit and f_o from the oscillator circuit. f_{if} is developed across the anode tuned circuits L8/C7 and L9/C10. This is the first i.f. transformer.

Fig. 2b has V1 as the r.f. amplifier and V2 as the frequency-changer. This differs from V1 in Fig. 2a in that it is a single pentode (not a double valve). It is what is called a self-oscillating mixer or frequency-changer. This is a common technique in valved f.m. front-ends.

Fig. 2b should be related to Fig. 1b. The aerial circuit is L1, the r.f. amplifier V1 with L2 in its anode, the local oscillator L3 and associated components (with the action of V2, of course), the mixer V2 and the i.f. circuit the tuned transformer in V2 anode circuit.

LOCATING THE SECTION

It is as well to locate these circuits in the set itself. The aerial circuit can quickly be traced by the lead from the aerial socket, the frequency

changer is generally the first valve on the chassis to the aerial socket, side of the tuning gang, while the i.f. circuit includes the i.f. transformer in a screening can the other side of the tuning gang.

The f.m. front-end (tuner) is generally contained in its own small metal box, separate from the set's main chassis or printed circuit board. Instead of capacitor tuning, dust-iron cores may be arranged to traverse the coil formers (as in Fig. 2b). The cores are attached to cords, spring-loaded at one end and the other end coupled mechanically to the a.m. tuning spindle. When the main tuning spindle is rotated, the cores thus move up and down inside the coil formers.

Tuning, of course, can be accomplished either capacitively (with ganged variable capacitors) or by varying the coil inductance as described, called *permeability tuning*. Moreover, r.f. and aerial circuits of f.m. front-ends are sometimes wideband (aperiodic), requiring no variable tuning.

Medium-frequency and short-wave sets with r.f. stages nearly always have an extra tuning gang section, totalling three sections as in Fig. 1b. Four sections are less common, but are found in highly sensitive communications sets. With only one r.f. stage a four-section tuning gang is used to give a tuned bandpass coupling, and a similar arrangement is used where a three-section gang is used without an r.f. stage. The most common arrangement, though, is that of Fig. 1a.

MISALIGNMENT

The front-end of a set will fail to work if the tuned circuits are incorrectly aligned. Correct alignment is just as important as the valves receiving their correct electrode voltages. Correct alignment means that over the tuning ranges the local oscillator frequency must lead (sometimes lag) the signal frequency by an interval equal to the i.f. The i.f. tuned circuit must also be correctly tuned.

Poor sensitivity will result if the i.f. is mistuned while the aerial and oscillator circuits are correctly

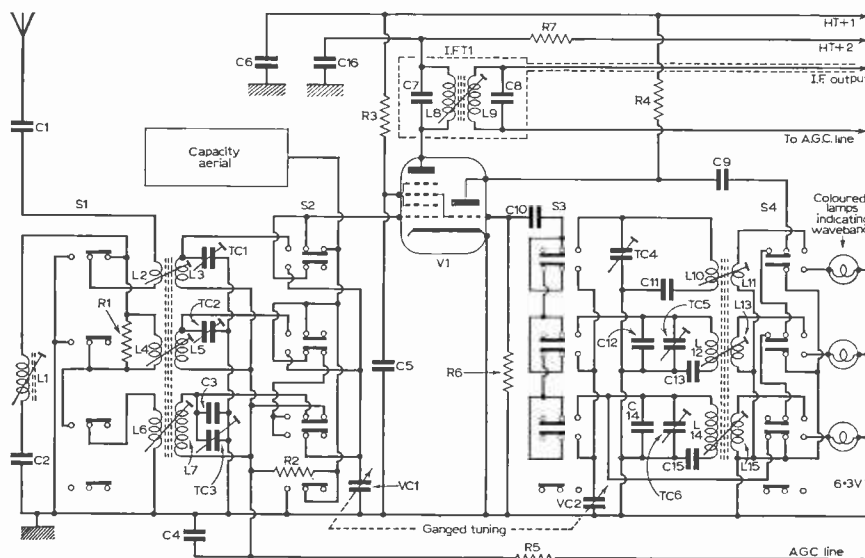


Fig. 2(a): First section of a typical mains superhet receiver.

tuned. If the oscillator is out of tune, stations will **★1** fail to appear at the correct dial markings, while aerial and/or r.f. misalignment will reduce the sensitivity and might cause background whistles and instability (oscillation). If all the circuits are mistuned, then one would be lucky to get a trace of signal through the set.

The tuned circuits are designed for correct *tracking* over the whole of the various bands, but this can only be finally tailored by adjustment to trimmers and dust-iron cores (tuning slugs).

The first action is to ensure that the i.f. circuit is tuned correctly. The i.f. is nowadays 470kc/s for a.m. (though it may differ on early sets), and 10.7Mc/s for f.m. The i.f. signal is injected into the first grid of the mixer section (or common frequency changer) with the local oscillator muted. This is best done by placing a large value capacitor (about 1 μ F) across the oscillator section of the tuning gang.

The i.f. signal is then monitored either at the output of the i.f. channel (i.e. detector) or at the output of the audio stages (i.e., loudspeaker). In the latter case, the i.f. signal will have to be modulated with audio tone so that it can be heard. Signal generators with tone modulation that can be switched on or off are readily available, and nothing elaborate is required for ordinary broadcast set alignment.

I.F. ALIGNMENT

If the i.f. tuned circuits (i.e., i.f. transformers) are all badly mistuned, a very strong signal will need to be applied until a trace of output is obtained. This will quickly rise as the circuits are brought into tune, starting with the i.f. nearest the detector and working back, so that L9 and then L8 in Fig. 2a would receive final attention. As the output rises, so the level of the generator signal should be reduced to avoid overloading.

It is best to have some sort of metering arrangement to detect changes in output as the transformers are tuned. A low-reading a.c. voltmeter

can be applied across the speaker or in place of the speaker across a suitable load resistor if the generator signal is modulated, while the voltage across the detector load resistor can be monitored with unmodulated generator signal. These output monitoring arrangements are shown respectively at (a) and (b) in Fig. 3.

With an f.m. set the voltage across the d.c. load of the ratio detector can be read on a low-reading voltmeter, as shown in Fig. 3c. Ratio detector alignment will be dealt with in a later article.

The i.f. transformer windings are nowadays nearly all tuned by dust cores threaded in the formers. Cores are used in both circuits in Fig. 2. Older sets may have trimmer capacitors instead of fixed ones, such as C7 and C8 in Fig. 2a, across the windings. Trimmer adjustment instead of core adjustment is then adopted for alignment.

R.F. ALIGNMENT

Having tuned the i.f. circuits, oscillator and aerial (and r.f. is fitted) alignment of each band in turn follows. The local oscillator is restored and the generator signal applied to the aerial socket (see later for frame and ferrite rod aerial sets). Tuning should first be to the high-frequency (low wave-length) end of the wave-band, and output indication as for i.f. tuning.

It is usual to start at the L.W. band, finishing with the lowest wavelength S.W. band (the f.m. is handled afterwards). The input signal should be tuned in wherever on the dial it falls and then the oscillator trimmer of that band should be carefully turned and the signal followed on the receiver tuning scale, working in the direction for correct dial location. The oscillator trimmers are preset capacitors in parallel with the oscillator coils, such as T4, T5 and T6 in Fig. 2a. The trimmer relating to the band under attention should be discovered either from a service sheet or by trial and error.

When the tuning is corrected at the h.f. end of the band, the l.f. end must be corrected. The generator frequency is altered to suit and the set

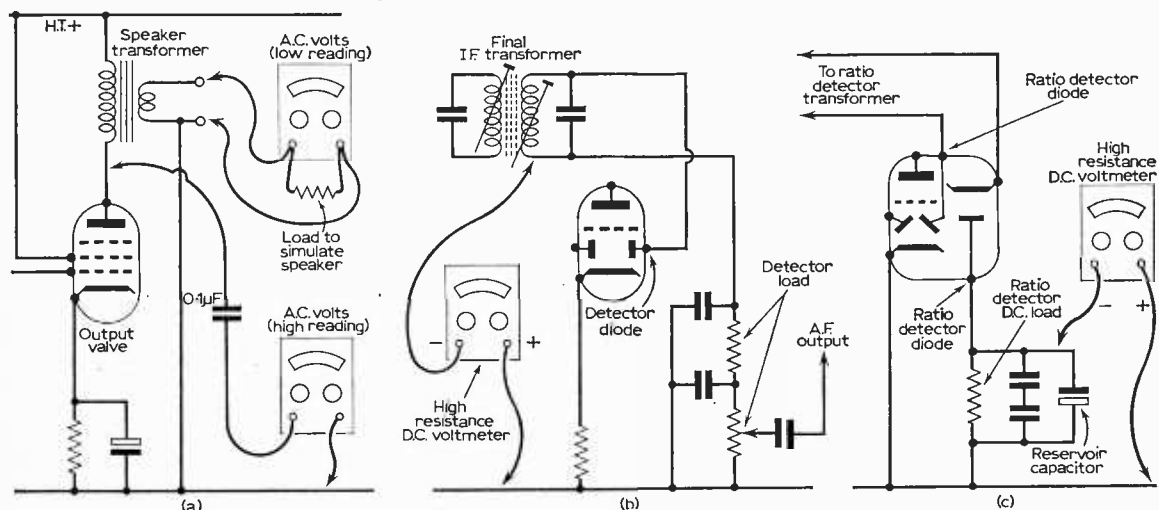


Fig. 3: Output monitoring arrangements. (a) monitoring the a.f. with the generator input signal modulated, (b) monitoring the detector load voltage on unmodulated carrier output and (c) monitoring the voltage across the d.c. load of an f.m. radio detector.



THE PW FAULT SYMPTOM RECORD

SOME NOTES ON THE 33 $\frac{1}{3}$ r.p.m. FLEXIBLE RECORD PRESENTED WITH THIS ISSUE AS A COMPANION TO THE SERIES OF ARTICLES NOW STARTING.

The PW Fault Symptom record illustrates ten different types of common faults in radio or audio equipment. These symptoms are referred to in the text where by an indented bold figure (as on page 926) and are as follows:

- Symptom 1: Instability in the r.f. or i.f. stages.
- Symptom 2: Adjacent channel interference.
- Symptom 3: Domestic interference (a) electric motor, (b) TV set.
- Symptom 4: R.F./i.f. overloading due to faulty a.g.c.
- Symptom 5: Component noise effects.

- Symptom 6: Low frequency instability.
- Symptom 7: Motor-boating.
- Symptom 8: Out-of-centre loudspeaker.
- Symptom 9: Audio distortion.
- Symptom 10: Worn pickup stylus and faulty pickup cartridge.

In all the symptoms except 2, the faults are recorded as they would be heard on the test passage from a radio station or gramophone recording. In symptom 2, the effect is recorded as though the receiver is tuned to an unmodulated carrier and the interference is experienced from another station radiating the test passage.

NOTES:

1. For obvious reasons, the record should be played on equipment which is not defective, otherwise results will be misleading.
2. Ensure that the pickup itself does not exhibit symptom 10!
3. The effects recorded will reproduce as well as the equipment will allow. To compensate for shortcomings in the equipment used it may be necessary to adjust the tone control(s) for best results, i.e., if (7) is not too clear, adjust for maximum bass response, if (10) is not too clear adjust for maximum treble response.

tuned to respond. Padding corresponding to the waveband is then adjusted to secure the l.f. end tuning point on the scale. Padding is effected by either a trimmer capacitor in *series* with the coil or a dust-iron slug in the coil former.

In Fig. 2a fixed padding capacitors (C11, C13 and C15) are used, padding adjustment being by cores in the coils. Re-adjustment at the h.f. end of the band with the trimmer should then be made, followed by a further l.f. end padding adjustment, repeating for the best possible tracking over the scale.

If the aerial and/or r.f. tuning is very badly adjusted, strong generator signals will be needed at the aerial input (via a dummy aerial). The generator signal should be left at the aerial for aerial and/or r.f. alignment.

Adjustments are now for maximum *sensitivity* as distinct from tuning scale accuracy, first at the h.f. end of each band using the trimmers and then at the l.f. end with padding adjustments (if fitted), repeating until best overall sensitivity is obtained. Aerial trimmers in Fig. 1a are T1, T2 and T3, and padding is adjusted by the coil cores again. The r.f. stage is handled in a like manner, always aiming for optimum sensitivity. That is, the least input signal for maximum output.

F.M. signal alignment requires an input Band II signal (about 95Mc/s) applied at the aerial socket across 75 ohms matching impedance. The idea is to adjust the oscillator (TC1 in Fig. 2b) for dial accuracy and then follow up for maximum sensitivity by adjusting any adjustable aerial and r.f. coils, such as L1 and L2 in Fig. 2b. These are wide-band, so separate alignment frequencies are not required, but a similar technique as for a.m. alignment might be needed in high-quality and complex receivers and tuners.

NO RESPONSE

A dead set can be quickly analysed by setting up as for alignment. If signals cannot be passed through the i.f. stages, the trouble is not likely to be in the front-end, excepting the frequency changer valve, which should be checked for emission and correct operating conditions. I.F. signal getting through the set from the mixer, but not signal frequency from the aerial, accompanied by lack of front-end response, signifies a defunct local oscillator. First try the frequency-changer valve, preferably by substitution. If there is still nothing, check the local oscillator circuitry.

There are several ways of doing this. One is to apply an unmodulated generator signal to the oscillator control grid with the set tuned to the L.W. Light Programme. Adjust generator frequency to the i.f. (say, 470kc/s) minus (or plus) the Light Programme L.W. frequency (200kc/s). If tuning the generator around this frequency fails to bring in the Light Programme, there is more than oscillator trouble. However, the set will probably respond.

Another test is to put a milliammeter in series with the oscillator anode (the h.t. side of R4 in Fig. 2a). The current should alter appreciably when the oscillator is muted by connecting a 1 μ F capacitor across the oscillator gang section. If there is no current change, there is no oscillation.

Another idea is to listen for the oscillator signal on a second set whose aerial input is coupled to the suspect set's oscillator circuit. The oscillator signal is unmodulated, of course, so will not be heard directly, but it often contains some hum modulation and if the signal is powerful enough it will not be missed when the test set is tuned.

If the test set has a tuning indicator, this will

—continued on page 949

The Home Workshop

I read Mr. Theasby's article with great interest. I did however notice one thing which did not appear to be in order.

Whenever I operate on a wireless network, I am required to keep an accurate log of all traffic, with RST's etc. How, then, is the operator going to be able to send morse with the right hand and write in the log with the left hand as is shown in Fig. 3? Surely it would be more logical to use the system I have adopted—namely the morse key at the left hand and the log at the right hand. It is easier for most people to tap the key with the left hand than to attempt to write with it—I know, I've tried it! The result? A mass of hieroglyphics!

J. McCarthy. London, S.E.22.

The Author Replies:

This is a point that I had not noticed when drawing the diagram to Fig. 3. Mr. McCarthy is, of course, correct in his observation.

I did state in my article that the layouts were only suggested, and no one need feel bound to stick directly to the diagrams or the text.

Jam on the Bands

Referring to Mr. Mugford's letter in the February issue of P.W., I agree there are a large number of distorted modulation jammers in the short wave broadcast bands. These jammers have also started in the 13m. band within recent weeks. The band that suffers most is 19m. They just follow one after the other when rotating the dial on the h.f. side. I have counted a number of jammers in each band covered on my receiver: there are 5 in the 49m. band, 5 in the 41m. band, and 6 in the 31m. band. There were no jammers in the 16 and 25m. bands. Upon listening in the next day, the count was: 6 in the 16m. band, 7 in the 19m. band, 5 in the 25m. band, 3 in the 31m. band and 1 in the 41m. band.

Another thing I deplore is the broadcasting of programmes on channels when another station is there already. This, I think is just as bad as jamming.

G. D. Gambold, Swansea, S. Wales.

Imported Radio Equipment

In the past two or three issues of this journal I have seen letters from readers who have said that they cannot get spares, etc. for Lafayette equipment.

I have a letter from Lafayette in America stating that all parts for my HE30 receiver can be obtained from their main headquarters in Syosset, the address of which is: Lafayette Radio Electronics Corporation, 111 Jericho Turnpike, Syosset, L.I., N.Y., 11791.

George Preston. Salisbury, Wiltshire.

NEWS AND..

DXing WORLDWIDE

For over three years Radio New York Worldwide has produced and broadcast DXing Worldwide. This is a programme designed by and for the international radio listener and broadcast twice weekly to listeners in Western Europe, Europe and Latin America.

From New York, DXing Worldwide compiles features on what's "news" in international radio, new product developments, technical tips on electronics, from microphones to how to build aerials and anything of technical topical interest.

The programme is produced by Irwin Belofsky with Steve Grayson as host and is broadcast by Radio New York Worldwide on Saturdays at 2307 GMT on 15-440 and 6-015 Mc/s and again on Sundays at 1607 GMT on 17-845, 15-440 and 17-730 Mc/s.

Further details of Radio New York Worldwide may be obtained from 485 Madison Avenue, New York, N.Y., 10022.


COLIN H. GARDNER

The death occurred recently of Mr Colin H. Gardner, who was with the Mullard Company for thirty-two years until his retirement in 1961. He was a past-President and Fellow of the Incorporated Practitioners in Radio & Electronics (I.P.R.E.). A radio ham since 1910, he made history in 1922 when he was the first man to transmit a radio message from a racing car engaged in breaking the world 24-hour speed record.

ELECTRONICS HOBBIES MANUAL

The 1967 edition of this book is now available for just 10/6d. post paid, and presents such a wealth of information on so many different items that it is quite impossible to begin to list them. This huge mail order catalogue of over 600 pages gives details of over 11,350 different parts from 85 leading manufacturers, and all items are obtainable from Messrs Electroniques. Even those obscure items are listed, like variable capacitance diodes, screw mounting feed-through capacitors, tubular trimmers and a host of other items ranging from ready made solid-state i.f. strips to stylus pressure gauges. The address to write to for your copy—Electroniques (Prop. STC Ltd.) Edinburgh Way, Harlow, Essex.

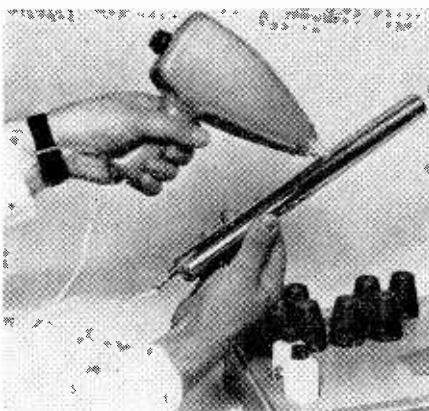NEW PORTABLE SELF-POWERED ELECTROPLATING GUN



This instrument is a fully portable electroplating "gun". It comes in a kit which consists of 'Plectro' gun, and nine separate cartridges for plating gold, silver, brass, tin, cadmium, zinc, copper, nickel and chromium. The gun is powered by its own self-contained battery, but very large areas of plating can be tackled by using a suitable accumulator.

The standard plating kit costs £27 8s. complete, and solutions are extra to choice. A descriptive leaflet is available from David Greenwood Ltd., Camden Works, Rickmansworth Road, Watford, Herts.

...COMMENT

STEREO RECORD PLAYER

A new addition to the *Perdio/Dansette* range is the *Stereophon* stereo-*phonic* record player. It has bass, treble, balance, volume and on/off controls; has a 5-pin DIN socket for tape input/output and has a power output of 3W per channel. The speakers are two 4in. round tweeters and two 8 x 5in. elliptical units. The amplifier employs ten transistors and power consumption is 80W at 240V. The size is 28½ x 10 x 28in., weight is 32lb. and the price is 47 guineas plus 13s. 8d. regulator tax.



ADDITIONAL ASSISTANT SECRETARY FOR IEE

John Stanley Raven, C.B., B.Sc., C.Eng., F.I.E.E. has been appointed an Assistant Secretary of the Institution of Electrical Engineers.

Mr Raven takes charge of a Qualifications Department formed by amalgamating and reorganising the present Membership and Education Departments, and will be responsible for executive control of the processes of election to membership, for tendering advice to applicants on the Institution's requirements for the various classes of membership, for controlling examinations, and for servicing all relevant Institution committees.

N. C. Stamford, the Assistant Secretary, will continue to be responsible for policy and external relations in connection with qualifications.

RADIO SOCIETY OF GREAT BRITAIN INSTALLATION OF THE PRESIDENT

Mr A. D. Patterson G13KYP, was installed as the thirty-third President of the Radio Society of Great Britain on Tuesday January 17th, 1967 at the Kingsley Hotel London. The retiring President, Mr R. F. Stevens G2BVN, expressed the fullest confidence in Mr Patterson, presented him with the chain of office, and wished him a happy and successful year. In his short speech the new President said that he did not envisage any startling changes during his term of office, but that increasing the membership was high on the list as was improving manners on the air. Following these remarks he presented the retiring President with a shillelagh much to the delight of the onlookers. Mr H. Wilson, President Irish Radio Transmitters Society, described Mr Patterson as a man of the very highest integrity, and said that the whole body of Irish amateurs was delighted when the news of the new President's election reached them. He then presented the new President and his (wife) with a vase of Waterford glass.

After the official installation members surged forward to the new President offering their congratulations, to which the staff of *Practical Wireless* now add theirs.

Imported Radio Receivers

I REFER to Cpl. T. K. Offord's letter in the February issue of *PRACTICAL WIRELESS*. This gentleman seems to be hostile towards imported receivers made in Japan but sold "under the guise" of American manufacture.

Firstly he seems to be under the impression that many radio dealers do not know where the Lafayette receivers and equipment are made. As virtually everything that comes with a Lafayette kit, including the packing box has the three well-known words "Made in Japan" prominently displayed, I am sure that he has misinterpreted the facts.

Secondly he refers to these so-called kits as being "junk" and having recently paid 25 guineas for a Lafayette KT-340 receiver which works extremely well, I should like to know if Cpl. Offord could name a new receiver with the same spec. as the KT-340 at the same price.

K. L. Kirk.

Chessington,
Surrey.

Transistor Terminology

I AGREE entirely with Martin Jessopp's views on Transistor Terminology (P.W. February, 1967). He remarks that he "used" to use valves; well, surely the same stupid mess existed and still exists with valve terminology. Nearly every octal based valve has different pin connections—which seems utterly stupid in my eyes, i.e. one man's grid is another man's anode and so on. Another point is, why does there exist a British Octal Base as well as the International Octal Base. I agree with Martin Jessopp, why can't the big boys sort this mess out—they've got the brains and the power.

D. Griffiths.

Cardiff,
Wales.

Cyprus Hams

I would like to inform you on behalf of the "First Cyprus Amateur Radio Club" that we will be going on the air by the end of this month.

Due to the limited facilities on this island, our progress has been considerably slow and it is very difficult for us to obtain any sort of technical advice. We would therefore be very grateful for any correspondence from other amateur clubs or from individuals. We will be transmitting on 160 and 80m.

Donald Wood,
President.

9 Aetoles Street,
Nicosia, Cyprus.

We are informed by Henry's Radio, 303 Edgware Road, London W2. that they can supply an equivalent to the BSY51 and BSY53 transistors featured in "Modernising Portable Record Players" (*PRACTICAL WIRELESS*, November, 1966). The alternative to both types is the 2N3705, available at 7s. 6d.

TOP BAND TRANSCEIVER

BY

T. SIMON *PART
TWO*

LAST month part one described the design considerations for a complete Amateur radio station measuring 12 x 6½ x 4½ in. Part two continues with constructional details and testing procedures.

Since the unit is so compact there is very little room for error in the placing of components. Because of this, it is essential that all components be collected first before any chassis layout is attempted. The chassis and front panel layouts for the prototype are shown in Figs. 3, 4 and 5, but would-be constructors are urged to use these only as a guide. Perhaps the best procedure is to place the components on the chassis approximately in the positions indicated in Figs. 3 and 4, and then juggle

pattern of holes may be drilled in the case directly below and directly above each valve. This allows the convection of hot air from the valves upwards, and thus away from the v.f.o. coil and components situated below chassis. Following this, the chassis and front panel should be bolted together, and the above-chassis front panel controls and components fitted. Strategic and generous placing of solder tags is strongly advised at the juncture. *NOTE:* None of the potentiometers should exceed one inch in diameter or trouble will be experienced in fitting due to space problems. Constructors able to layout a front panel to the nearest hundred thou. may use slightly larger pots., ordinary mortals like the writer should heed the warning.

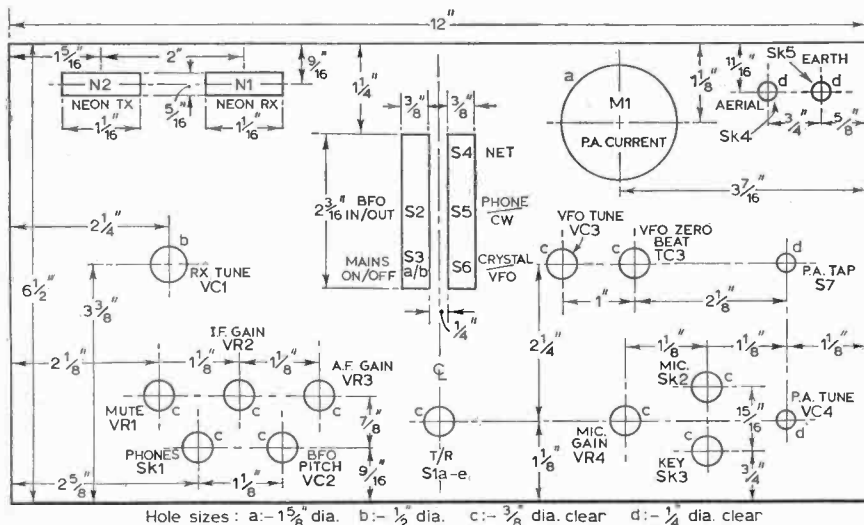




Fig. 5: Layout and drilling instructions for the front panel. Compare this figure with the heading photograph.

them to suit, thus catering for any slight differences which might occur.

After drilling the appropriate holes all chassis mounted components should be fixed securely in position, and all front panel controls below chassis should be fitted in their allotted places. Holes should be drilled around each valve base to allow good ventilation. Later, when the outer case is ready, a

Wire up the heaters first, twist the leads and tuck them well away from grid and signal wiring. Solder 0.01µF disc ceramics across the heater pins of each valve base using the shortest possible leads. Wire up leads to all front panel controls next, cutting them to length and leaving them floating if necessary. It is advantageous to postpone mounting the smoothing choke until last, as this allows for easier wiring up below chassis. It is also easier to leave the screens both above and below chassis until most of the wiring has been completed. The screen shown between the sections of S1 was already on the original switch and is probably superfluous, it should prove a simple matter to modify a standard switch by making a small screen out of aluminium.

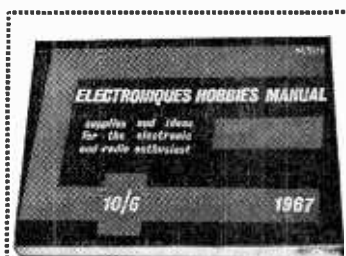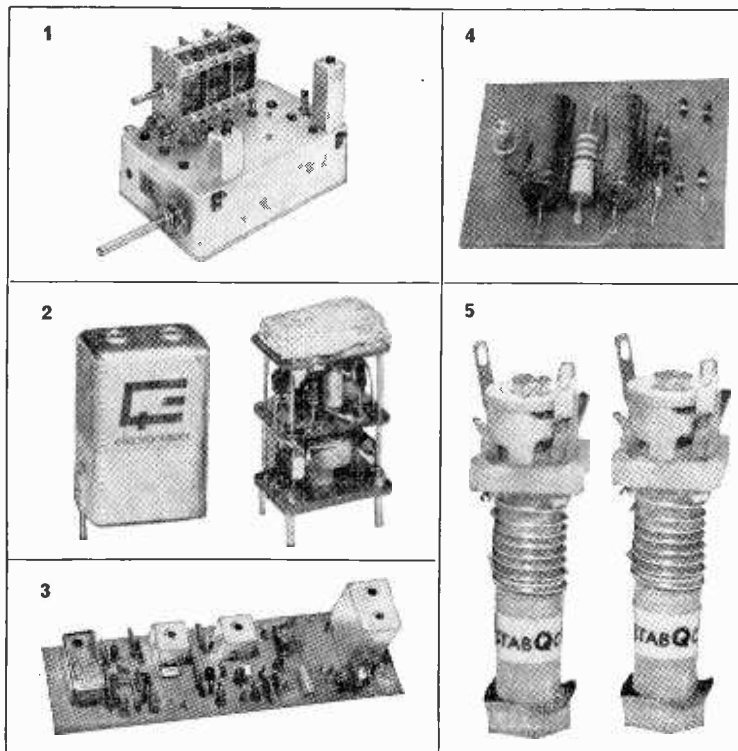The particular capacitor used for VC1 is a Jackson 208+176pF twin gang. The moving vanes on both gangs were pruned until two vanes per gang remained. This allowed the tuning swing to cover Topband with a few kc/s to spare at either end. The



I should like a copy of the Electroniques Hobbies Manual. Enclosed is a cheque/P.O. for 10/6.

NAME _____

ADDRESS _____

P.W.4

Below, we've summarised 2 pages from the Electroniques Hobbies Manual 606 PAGES REMAIN TO BE SEEN (when you've got your Manual)

With the new Hobbies Manual, you can obtain these—and over 11,000 other items—direct from Electroniques or through your Local Electroniques dealer! The service is fast; the range is the most comprehensive ever offered. And the components, which are supplied by 85 leading manufacturers, meet every kind of need—whether the project is advanced or elementary!

1 Transistor Coil Packs (Coilpax)

These silicon transistor units are available in General Coverage and Hamband versions. The IF frequency is 1620 Kc/s, ready for use with our filters and IF amplifiers as well as existing receivers as the second IF. The Manual contains comprehensive technical data and other useful information on these items.

2 Oscillator Modules

Fully transistorised, these oscillator units can be used for BFO, VFO or CIO applications. The BFO units include a variable capacitance diode as the tuning element, permitting remote control by linear law potentiometer. Extremely stable (better than .002% per degree C), they have an exceptionally pure oscillator waveform.

3 IF Strips and Filters

Two units are available—one at 1.62 Mc/s IF for use with Coilpax, the other for use at 455 Kc/s as a second conversion IF strip or as a main 455 Kc/s unit. Both include a half lattice crystal filter, AGC control, AM and SSB detection and BFO injection for CW reception. A third unit, also at 455 Kc/s, uses a ceramic filter.

4 Power Modules

These small stabilised power units operate directly from 6.3V AC heater supply. Two outputs available: 6.2V at 50mA Zener stabilised, and 9.0V at 70mA MAX unstabilised. Either polarity can be earthed providing AC supply is floating.

5 Coils (Stabcoils)

A comprehensive range of transistor coils is available for intermediate frequencies of 455 Kc/s and 1.62 Mc/s, together with a complementary range of IF transformers.

Send now for your Manual, on the coupon above, to this address: Electroniques (Prop.-STC Ltd.) Edinburgh Way, Harlow, Essex. Telephone: Harlow 26777.

High-grade components for amateur communications

electroniques

COMPARE THESE PRICES

ELECTROLYTIC CONDENSERS

64μF ..	2.5 volt	30μF ..	10 volt
125μF ..	2.5 volt	3μF ..	12 volt
640μF ..	2.5 volt	4μF ..	12 volt
0.25μF ..	3 volt	25μF ..	12 volt
2μF ..	3 volt	200μF ..	12 volt
40μF ..	3 volt	2.5μF ..	16 volt
4μF ..	4 volt	64μF ..	16 volt
500μF ..	4 volt	200μF ..	16 volt
5μF ..	6 volt	750μF ..	18 volt
20μF ..	6 volt	2.5μF ..	25 volt
25μF ..	6 volt	3μF ..	25 volt
30μF ..	6 volt	4μF ..	25 volt
50μF ..	6 volt	10μF ..	25 volt
100μF ..	6 volt	25μF ..	25 volt
3.2μF ..	6.4 volt	12.5μF ..	40 volt
40μF ..	6.4 volt	3.2μF ..	64 volt

All at 1/- each, 9/- per dozen or mixed packet (our selection.) 20 for 10/-.

150μF, 25 volt; 500μF, 25 volt, 2/6 each. 5,000μF, 12 volt, 4/- each. 200/100 275 volt; 200/200 275 volt; 125/300/50 275 volt, 5/- each; 3 for 10/-.

PAPER CONDENSERS SPECIAL CLEARANCE!

0.35μF, 150 volt; 0.02μF, 350 volt; A.C. 0.25μF, 350 volt; 0.5μF, 350 volt; 0.5μF, 500 volt; ALL at 15/- per 100. Mixed packet containing 0.0001μF, 200 volt, to 0.5μF, 500 volt. Very useful for service work! 50 condensers for 10/-.

RESISTORS. ½ watt, well assorted values, 10/- per 100; 55/- per 1,000. ¾ watt to 3 watt, well assorted values, 10/- per 100; 55/- per 1,000. TO CLEAR: 10 Meg. 1/6th watt resistors—to clear £1 per 1,000.

TRANSISTORS. Untested, mixed, 50 for 10/-. NPN Switching transistors, Min. 200 m/cs., 6 for 10/-. PNP Switching transistors, Min. 200 m/cs., 6 for 10/-.

DIODES. Suitable for keying electronic organs, 20 for 10/-. BY100 type rectifiers, 30/- per dozen. ORP12 light cells, 9/- each.

TRANSISTOR BATTERY ELIMINATOR—same size as PP9, 30/- PP6, £1.

BATTERY CHARGERS with meter, 4 amp., 6 or 12 volt. 55/- LAPEL MICROPHONES, crystal or magnetic, 10/- each.

MINIATURE EARPIECES complete with plug and lead, 5/- each.

SIGNAL INJECTOR, parts and circuit to make, 10/- each.

SIGNAL TRACER, parts and circuit to make, 10/- each.

MOTOR CAR REV. COUNTER, parts and circuit to make, 10/- each.

PORTABLE RADIOS—complete with leather case, earpiece etc., fully guaranteed, 79/6 complete.

ACOS PICK-UP HEADS, Mono, 10/-; Stereo, 12/6; Diamond, 17/6.

SAPPHIRE STYLII, TC8LP, GC2LP, GC8LP, BF40LP, GP67LP, TC8 Stereo LP, Studio O LP, GP37, GP59, ALL at 3/6 each.

POTENTIOMETERS—pre-set, 100 ohm to 680 K.ohm., 12 for 10/- (mixed).

MAGNETIC RECORDING TAPE

British made, fully guaranteed

Standard Play. 3", 150 ft., 3/6; 5", 600 ft., 10/6; 5½", 900 ft., 13/6; 7", 1,200 ft., 16/3.

Long Play. 3", 225 ft., 4/-; 5", 900 ft., 12/9; 5½", 1,200 ft., 15/9; 7", 1,800 ft., 21/6.

Double Play. 3", 300 ft., 6/6; 5", 1,200 ft., 20/-; 5½", 1,800 ft., 28/-; 7", 2,400 ft., 34/-; 2½", 300 ft., 6/9.

Triple Play, Polyester. 3", 600 ft., 12/6; 4", 900 ft., 16/6.

WELLER INSTANT HEAT SOLDERING KIT, 72/6 complete.

WELLER DUAL-HEAT SOLDERING GUN, only 57/6 complete.

SOLO 615 PENCIL BIT IRONS 25/-.

PHILIPS/STELLA/COSSOR remote control unit, value 3 gns., our price 10/-.

RUMBLE AND SCRATCH FILTER parts and circuit to make, 30/-.


TRANSISTORS, COMPONENTS, AND CIRCUIT to convert 1ma. meter to 0 to 10 Meg. ohmmeter, 10/-.

G. F. MILWARD

17 PEEL CLOSE, DRAYTON BASSETT, Nr. TAMWORTH
Staffs. TAMWORTH 2321 POST ONLY
231 ALUM ROCK ROAD, BIRMINGHAM, 8.

Due to recent heavy increase in parcel rates, please include part postage cost.

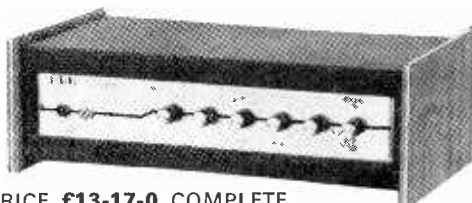VIKING STEREO 4 + 4 DE-LUXE HIGH QUALITY AMPLIFIER



PRICE £13-17-0 COMPLETE

A high quality stereo amplifier, built to meet the requirements of budget Hi-Fi. Elegant styled cabinet in black rexine and woodgrained ends. Brushed aluminium panel, black and silver knobs. Quality components throughout. Ganged Bass and Treble controls, separate volume controls for each channel. Valves (Standard Model) 2 x ECL86 (De-Luxe Model) 1 x ECL86 (2) x ECL86. Output 3 ohms matching, suitable A.C. mains 230-240 volt. Cabinet size, 16 1/2 in. wide 5 1/2 in. high, 8 1/2 in. depth. Full instructions and guarantee. Send for leaflet. S.A.E.

VIKING 10-12 A twelve watt amplifier for use on 230-240 volt A.C. mains. Inputs suitable Microphone, Record Player, Tuner, Tape Recorder, etc. Printed circuitry. Five Mullard valves, reliable components. Front panel contains 2 Input Jacks, 2 Volume Controls, 1 Tone, Neon and On/Off switch. Designed to fit into same type and size cabinet as Stereo. Fully guaranteed. Send for leaflet. PRICE £8-19-6 PLUS 12/6 P.P.

VIKING X.P.15. A frustrated order offered at a fraction of cost (original price 39 gns.). 15 watts output. Suitable for 210-240 Volt A.C. mains. Attractive Black chassis with slotted chromed steel top cover, size 15 x 7 1/4 x 7 in. 4 Input Jacks, 2 volume controls, 2 tone, 5 Mullard valves. Fully guaranteed. Send for leaflet.

Price Complete £12.19.6 plus 12/6 P. & P. and Ins.

L.P. TAPE BARGAIN

5 1/2 in. reels each containing 1,200ft. of top quality polyester recording tape (Limited quantity.)

Price 3 reels for 35/- P.P. free.

Terms: C.W.O., C.O.D. Money back guarantee.

VIKING (ELECTRONICS) LTD. 37 HILLSIDE,
STONEBRIDGE,
LONDON N.W.10

Telephone: ELG 3644

(MAIL ORDER ONLY)

YOUR CAREER in RADIO & ELECTRONICS?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.R.E. Exam.; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronic subjects only. Full details will be gladly sent without any obligation.

To: British National Radio School, Reading, Berks.

Please send FREE BROCHURE to:

NAME.....Block

ADDRESS.....Caps.

.....Please

4.67

BRITISH NATIONAL RADIO SCHOOL

spindle on this capacitor is very short and requires a coupler to extend it. This is a standard item and should present no problems, although it might be an idea to use a different component with a longer spindle and/or use a slow motion drive. If this is done, check the space available first.

The positioning of TC1 and TC2 is not unduly critical but their leads should be as short as possible. The coils in the receiver section can be any make of approximately similar range to those specified. The preset capacitors TC1/TC2 will "take up the slack". If coils other than those specified are used, it is possible that the padder capacitor C5 will be a different value, and the relevant manufacturer's literature should be consulted.

The push button unit in the receiver is really only a glorified bank of three switches and the top one as shown, is not used. Note that the receiver push-button unit is different from the one used in the transmitter. First the buttons are grey instead of white, and secondly, it possesses a mains rated switch. The wiring details for both receiver and transmitter switching units are shown in Fig. 6, the extra poles and switch sections available are ignored.

Although skirted valve holders were used in the prototype, screening of the valves in the receiver section was found to have negligible effect on performance. Fitting cans merely detuned the stages slightly, necessitating the tuned circuits and i.f.t.s to be re-tweaked. Other than this the use of valve cans appeared to be superfluous. Thus, in the interests of better ventilation screening cans were purposely omitted, although it might prove wise to use skirted valve holders any way as a precaution.

The remainder of the wiring in the receiver section is as for any other normal superhet, and other than using screened leads where indicated requires little comment.

Transmitter wiring

Construction and wiring of the remainder of the transmitter section requires some care since instability is easy enough to come by without encouraging it. Above chassis, the metal screen shown in Fig. 4 last month is a necessity. It is superior to valve cans since it provides better ventilation, and also completely screens the three valve sections, and the p.a. tank components, from each other. Note that the meter leads are passed through a hole in this screen directly into the p.a. compartment, down through a hole drilled in the chassis and into the screened p.a. section below chassis, thence to the h.t. and RFC2.

The p.a. coil and tapping switch take a little time and patience to wire up. The coil is wound first, 60 turns of 24s.w.g. enam. close wound on a 1½ in. diameter former. The tapping points being formed by twisting the appropriate turn into a loop. The loops are then cleaned and tinned, and the coil is positioned near the switch, as it will actually be in the transceiver. Short lengths of wire can then be cut measuring from the switch contacts to the loops. Bare and tin both ends of these wires and connect up the switch and the coil on the bench. When completed there should be three spare leads protruding, one from one end of the coil to connect to earth, another from the pole of the switch for the antenna connection, and one from the top of the coil to connect to the junction of C46, VC4,

C45, and Sle pole. When all is in order the switch and coil may be fixed in the case as one unit. Note the tin plate screens below chassis (Fig. 3) which shield each valve and associated components from its neighbour, also the extra screen directly across

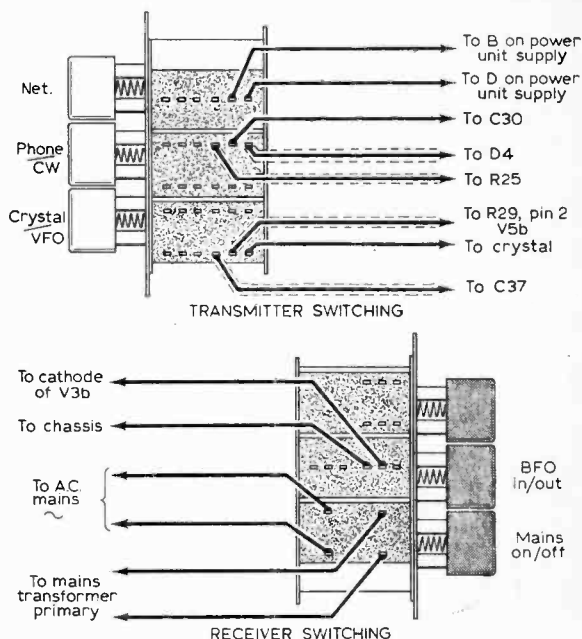


Fig. 6: Wiring details of the push-button units.

V5 valve base screening the triode from the pentode section. The screens must be securely earthed.

The v.f.o. coil consists of 90 turns of 34s.w.g. enamelled wire close wound on a ½ in. diameter former (Ekco type F804 minus the slug). This coil is unscreened and is bolted directly to the chassis. The tuned circuit in the pentode anode is resonant at 1.9Mc/s. The former of a Denco 1.6Mc/s i.f.t. was cut to ½ in. long, and the can was then pruned to fit. The coil former was then wound with 90 turns of 34s.w.g. enamelled wire scramble-wound, and paralleled with a 50pF fixed capacitor. It is probably easier to wire in a 100pF trimmer across the coil and, with the unit in position, grid-dip it to exactly 1.9Mc/s by adjusting the trimmer. It is possible to utilise one of the windings on the original transformer, in which case the top pi should be removed completely. The pruned can is held in position by bolting it to the chassis with a 6BA bolt.

The particular meter used is a 0-5mA which reads in reverse, that is, with no current passing through it the meter reads 5mA. This means that one tunes for a peak instead of a dip when resonating the tank circuit. The meter shunt was made from a small length of fire bar element ½ in. long, 1,000 watt 250 volt spiral wound type. A normal reading meter rated 0-50mA would be entirely suitable but check the size first, and remember in this case to tune for a dip when loading the transmitter. The wiring of the v.f.o. should be solid, and heavy gauge wire should be used.

The modulator diode is completely screened by wrapping it in a strip of insulation tape and then covering it with a strip of silver paper or aluminium

★ components list

Capacitors:

C1	0.01 μ F
C2	0.01 μ F
C3	0.001 μ F
C4	270pF S.M.
C5	2,500pF S.M.
C6	0.01 μ F
C7	0.01 μ F
C8	0.01 μ F
C9	0.01 μ F
C10	0.01 μ F
C11	0.01 μ F
C12	0.01 μ F
C13	0.01 μ F
C14	0.01 μ F
C15	100pF S.M.
C16	16 μ F 275/325V electrolytic
C17	25 μ F 25V electrolytic
C18	0.1 μ F
C19	0.1 μ F
C20	150pF S.M.
C21	100pF S.M.
C22	100pF S.M.
C23	16 μ F 350V electrolytic
C24	16 μ F 450V electrolytic
C25	100pF S.M.
C26	16 μ F 250V electrolytic
C27	25 μ F 25V electrolytic
C28	0.001 μ F
C29	25 μ F 25V electrolytic
C30	0.02 μ F
C31	16 μ F 250V electrolytic
C32	82pF S.M.
C33	1,000pF S.M.
C34	1,000pF S.M.
C35	100pF S.M.
C36	0.01 μ F
C37	0.01 μ F
C38	100pF S.M.
C39	0.01 μ F
C40	0.01 μ F
C41	100pF S.M.
C42	0.01 μ F
C43	0.01 μ F
C44	0.01 μ F
C45	0.001 μ F
C46	100pF S.M.
C47	0.01 μ F
C48	0.01 μ F
C49	82pF
TC1	300pF compression trimmer
TC2	300pF compression capacitor
TC3	30pF variable capacitor
VC1	208 + 176pF modified
VC2	15pF variable capacitor
VC3	140pF variable capacitor
VC4	140pF variable capacitor

Potentiometers:

VR1	10k Ω	VR3	500k Ω
VR2	10k Ω	VR4	500k Ω

Valves:

V1	ECF82/6U8	V4	12AX7/ECC83
V2	ECF82/6U8	V5	ECF82/6U8
V3	ECF82/6U8	V6	5763

Neons:

N1	Mains neon—Bulgin	N2	Mains neon—Bulgin
----	-------------------	----	-------------------

Resistors:

R1	150k Ω	R19	270k Ω
R2	100k Ω	R20	6.5k Ω
R3	1.2k Ω	R21	470k Ω
R4	1k Ω	R22	270k Ω
R5	47k Ω	R23	270k Ω
R6	27k Ω 1W	R24	3k Ω
R7	100k Ω	R25	100k Ω
R8	1k Ω	R26	56k Ω
R9	1k Ω	R27	1k Ω
R10	68k Ω	R28	5.6k Ω 5W
R11	47k Ω	R29	22k Ω 2W
R12	100k Ω	R30	47k Ω
R13	1k Ω	R31	15k Ω 5W
R14	1k Ω	R32	22k Ω
R15	27k Ω 5W	R33	5.6k Ω 2W
R16	1k Ω	R34	220k Ω
R17	47k Ω	R35	50 Ω carbon
R18	270k Ω	Rs	See text

Coils:

L1	Osmor QA4 or similar
L2	Osmor QO4 or similar
L3	LF Choke 10H 70mA
L4	See text
L5	See text

Transformers:

IFT1	Denco 465kc/s i.f.t.
IFT2	Denco 465kc/s i.f.t.
IFT3	Denco 465kc/s i.f.t.
T1	Output transformer Wharfedale type OP3
T2	Denco 465kc/s b.f.o. transformer
T3	250–0–250V at 80mA, 6.3V at 3A

Switches:

S1a-e	3 Pole 3 Way Two bank
S2	3 Button unit. Mains 2 pole on/off;
S3a-b	2 Pole 2 Way; 3 Pole 2 Way
S4	3 Button unit. 4 Pole 2 Way; 4 Pole
S5	2 Way; 2 Pole 2 Way
S6	
S7	1 Pole 23 Way

Sockets:

Sk1	Jack socket open circuit when jack removed
Sk2	Jack socket, shorts when jack removed
Sk3	Jack socket, shorts when jack removed
Sk4	Insulated terminal
Sk5	Insulated terminal



Diodes:

D1	OA81
D2	BY100
D3	BY100
D4	OA81

Miscellaneous:


Crystal 1.9Mc/s
 Crystal holder to suit
 RFC1 2.5mH
 RFC2 2.5mH 100mA
 Case—H. L. Smith, Edgware Road, London, W.2
 Tin plate for under-chassis screens.
 M1 0–5mA moving coil meter see text. (Henry's Radio)
 Valve holders—6 type B9A with skirts
 The push-button units are available from Messrs
 Henry's Radio, 303 Edgware Road, London, W.2.
 They are coded—Three button switch units type 40
 and 41 respectively.

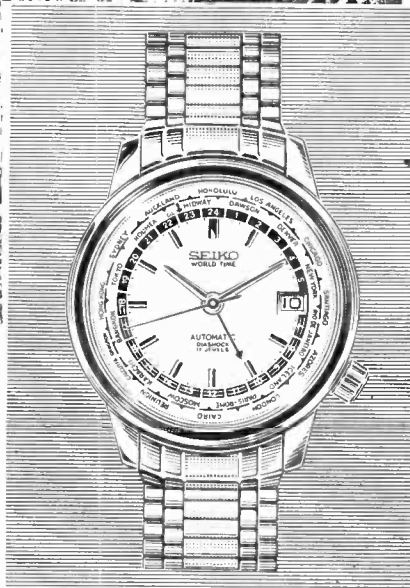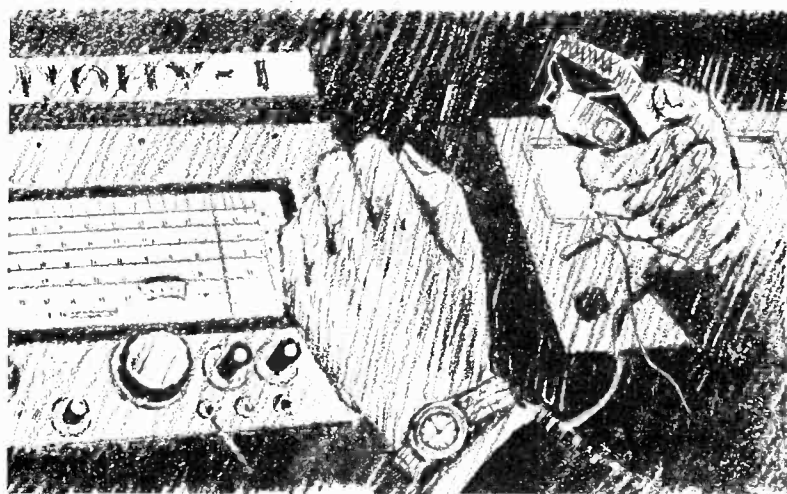know the time the world over with the fantastic SEIKO world time WATCH



The World Time watch actually tells you at a glance the time not only here at home, but also in places like Tokyo, Sydney, Auckland, Honolulu, Los Angeles, Chicago, Karachi, Calcutta, Bangkok or Hong Kong.

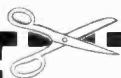An invaluable aid for the short wave enthusiast, this 17 jewel watch is made by SEIKO . . . which means guaranteed accuracy, superb finish and highest quality. Only SEIKO stop watches and sports timers were officially selected to time the Tokyo Olympics.



USE THIS 100% MONEY-BACK GUARANTEE FORM

The price ? £21 9s. 6d. for Practical Wireless readers, including post and packing and insurance. The World Time Watch is guaranteed for 12 months against any faults arising from defective material or manufacture and comes to you in an attractive presentation box. Your money will be refunded if you are not fully satisfied with this space-age watch.

Please send me a SEIKO WORLD TIME WATCH. My remittance for £21 9s. 6d. is enclosed and will be refunded if I am not completely satisfied.

MY NAME _____

ADDRESS _____

(W.1.)

Cheques and postal orders must be crossed and made payable to Watches Division, W.S.R. Limited, Dept. W.1, 30-32 Southampton Street, London, W.C.99. Cheques should have name and address on the reverse. This offer is available to U.K. readers only.



EVERYTHING YOU WANT IN COMPONENTS, accessories, equipment, service

TRS FM STEREO DECODER

Outstanding Value and Performance

Based on Mullard's proven circuitry, this is a six transistor, printed circuit unit size $5\frac{1}{2} \times 2\frac{1}{2}$ in. Two stage transistor Stereo Beacon Indicator is incorporated. Operates from 12 v. supply. Neg. earth. Basic Kit supplied suitable for Transistor Tuner input and Transistor Amplifier output. With simple modification (data supplied with Kit) the unit is easily adapted for Valve Tuners and Valve operated equipment. Kit and assembly instructions, complete with Mullard specified Inductors, Type WF2949 and WF2951. Complete kit as described

£4.19.6

With coils tested and pre-aligned

£5.5.0

Carriage either kit 2/6. 6d. stamp for circuit and data.

MULLARD FM DECODER COILS

Designed and made by Mullard, these inductors are as used in T.R.S. Decoder above. TYPE WF2949 and WF2951, each 25/-, Per pair 49/6. Post free.

ENAMELLED COPPER WIRE—2 oz. reels. 14 g.-20 g. 3/-; 22 g.-28 g. 3/6; 30 g.-34 g. 4/3; 36 g.-38 g. 4/9; 39 g.-40 g. 5/- etc.

TINNED COPPER WIRE. 16-22 g. 4/- 2 oz.

BONDAFOUST Speaker Cabinet Acoustic Wadding (lin. thick approx.) 18 in. wide, any length cut, 6/- yard, 2/5 per foot.

VEROBOARD—All sizes including 2 1/2 in. x 5 in. 3/8; 2 1/2 in. x 3 1/2 in. 3/4; 3 1/2 in. x 5 in. 5/2; 3 1/2 in. x 3 1/2 in. 3/8; 3 1/2 in. x 17 in. 12/6.

All accessories and tools in stock.

VOLUME CONTROLS. LOG and LINEAR. We carry very large stocks in the widest possible range of values, single and ganged. 5K-2 MΩ 3 in. Spindles Morganite Midget Type 1 1/2 in. diam. Guar. 1 year. LOG or LIN ratios less Sw. 3/6. D.P. Sw. 5/-. Twin Stereo less Sw. 7/6. D.P. Sw. 9/6 (100k to 2 Meg. only).

STEREO BALANCE CONTROLS. Log/Anti-Log 5K Ω. 1, 2 Meg. 9/- each.

ERSIN MULTICORE SOLDER. 60/40 4d. per yard. Cartons 6d. 1/-, 2/6 etc.

WIREWOUND RESISTORS. 25 ohm to 10 K 5 w. 1/3. 10 w. 1/6. 15 w. 2/-.

CONDENSERS Silver Mica. All values 2 pf to 1,000 pf. 6d. ea.

Ditto ceramic 9d. Tub. 450 v. T.C.C. etc. .001 mfd to .01 10d. and 1/1850 v. 10d. .02 MF to 0.1 MF. 500 v. 1/-. 35 T.C.C. 1/9.

.5 T.C.C. 2/-.

CLOSE TOL. S/MICAS. 100 Ω. 5 pf. 600 pf. 9d. 800-5,000 pf. 1/1-1 1/2.

2 pf.-100 pf. 11d. 100 pf.-250 pf. 1/2. 270 pf.-800 pf. 1/4. 800 pf.-5,000 pf. 2/-.

ALUMIN. CHASSIS. 18g. Plain undrilled folded 4 sides. 2in. deep. 6in. x 4in. 4/6; 8in. x 6in. 5/9; 10in. x 7in. 6/9; 12in. x 6in. 7/6; 12in. x 8in. 8/- etc.

ALUMIN. SHEET. 18 g. 6in. x 6in. 1/-; 6in. x 9in. 1/6; 6in. x 12in. 2/1; 12in. x 12in. 4/- each.

TYGON FRET (contem. patt.) 12in. x 12in. 2/-; 12in. x 18in. 3/-; 12in. x 24in. 4/- etc.

6 VALVE A.M./F.M. TUNER UNIT

In Kit Form with or without Power Pack

Med. 190 m., 550 m., V.H.F. -86 Mc/s-103 Mc/s, 6 valves Kit metal - contains self - contained power unit, Magic-eye, 3 push-button controls, on/off, Med. V.H.F. Diodes and high output sockets with gain control. Illuminated 2-colour perspex dial 1 1/2 in. x 4 in. chassis size 1 1/2 in. x 4 in. x 5 1/2 in. Strongly recommended for use with Mullard amplifiers. For A.C. mains 200/250 v. Unbeatable value. Complete kit, inc. Power Pack as illustrated, 11 gns. Carr. 7/6. Ditto less Power Pack, 10 gns. Carr. 7/6. Circuit and Construction details, 4/6. Free with kit.

TRS ALWAYS HAVE THEM!

Resistors in widest possible range of values and tolerances. Examples:

1% Hi-Stab 1 w. 10Ω-100Ω each 2/-.

1% Hi-Stab 1 w. values over 100Ω each 1/6

5% Hi-Stab 10Ω to 1 meg. 1 w. 5d. 1 w. 6d.

10% Hi-Stab 2 to 10 meg. 1 w. 5d. 1 w. 6d.

10% Standard 1 w., 1 w. 4d. 1 w. 6d.

Send to TRS first for all you want!

TRANSISTOR COMPONENTS

Midget I.F. Trans. 1 1/2 in. dia. Weyrad, etc. 1st, 2nd or 3rd IF ea. 5/6. Osc. Coil 1 1/2 in. dia. Med. and LW 5/-.

Ditto REPANCO 1 1/2 x 1 1/2 in. Standard type 1st, 2nd and 3rd IF, Osc. Med. and LW ea. 6/-.

Double Tuned type ea. 6/8. Miniature Push-Pull Driver Transf. (Type TT45) Ratio 9:1 6/-.

Miniature Push-Pull O/P Transf. to 3 ohms (Type TT46) Ratio 8:1 6/-.

Midget RF Chokes (for Med. and LW) 2.5mH, 6mH, 7.5mH, 10mH ea. 2/6.

POLYESTER MINI CONDENSERS—Ideal for P/et use.

200 v. w. .01 9d., .022 9d., .033 11d., .047 11d., .068 1/-; 1 1/2.

MIDGET TRANSISTOR ELECTROLYTICS—T.C.C. etc.

Std. range, all values 1 mfd-50 mfd. 15 volt, working

each 1/8. 100 mfd 12 v. 2/-, 1000 mfd 6 v. 2/3.

Special Electrolytics for Transistor Mains Units. 1000 mfd

25 v. 4/6; 2000 mfd 50 v. 6/8; mfd 75 v. 7/6; 3000 mfd

15 v. 5/9.

TRANSISTOR CONDENSERS—Hunt's, T.C.C. etc. 150 v.

working. 0.1 mfd. .02 mfd. .03 mfd. .04 mfd. .05 mfd.

1 mfd 1/-, 22 mfd 1/8, 47 mfd 1/6.

3 WATT TRANSISTOR AMPLIFIERS—(Newmarket

PC5-), 6 Transistor, 5 ohm output. Size 5 1/2 x 1 1/2 in.

5-8 mV sensitivity. Excellent High Gain Med. Imp.

Audio Amp. 75/-, Post 1/-, 9 v. PP3 battery 2/6 and 3 ohm speaker extra.

SUB-MIN. RESISTORS 1/10th watt, 10% tolerance, each 6d.

BATTERY HOLDER—Takes 4 U7 Batteries, 2/9.

MAINS UNIT for TRANSISTOR SETS—200/250 v. AC

for replacing or reactivating PP3 or PP6 Battery Units

24/6. Post 1/-, Ditto for PP3 batteries 29/6. Post 1/-.

TUNING CONDENSERS—J.B. "000", 208 pf x 176 pf 8/6.

Ditto with Trimmers 9/6, 220 pf x 105 pf with concentric

slide motion drive 10/6. 5in. 265pf 7/6. Sub-min.

4 in. J.B. DILEM 0008 or 0005 mfd 8/- each.

MIN. Slide Type WAY CHANGE SW—1 x 1 1/2 p. 2 way

2/6. 3 Way Push Button W/Change SW—3 push buttons

engraved Long, Med. Off. 1 1/2 x 1 1/2 in. Manufacturers

surplus. Bargain 5/6.

VOLUME CONTROLS—Midget Transistor type. 5K with

Switch, complete with edge Control Knob, ea. 4/9.

Ditto less Switch 3/9.

MINIATURE DEAF-AID EARPHONE. Continental

Type—high imp. Xtal Earpiece, supplied with earplug

insert, 3ft. lead and miniature Jack plug, ea. 8/-. Ditto

low impedance magnetic type, ea. 7/6.

ROCKER SWITCH—Mains voltage type. Chassis mounting

type 17/6. P. & P. 1/9. 8 ohms—2 1/2 in. 35 ohms—

Transistor Holders. 3 pin 1/-; 5 pin 1/3.

Ferrite Aerial Rods. 4 x 1/2 in. 1/6; 6 x 1/2 in. 2/-; 6 x 3/4 in.

2/-; 6 x 1 in. 2/8; 8 x 1 in. 2/8; 8 x 1 1/2 in. 3/-. Ferrite

Slab 3 x 1 in. 1/6.

TRANSISTOR DRIVEN SPEAKERS

3ohms—2 1/2 in. High-Flux EMI. Ideal for pocket Transistor

sets. 17/6. P. & P. 1/9. 8 ohms—2 1/2 in. 35 ohms—

Speaker. Exceptional value. 13/6. P. & P. 1/9. 35 ohms—

5in. Goodmans. 21/6. P. & P. 1/9. 75 ohms—2 1/2 in. Plessey.

Ideal Push-Pull. OC81 etc. BARGAIN 15/6. P. & P. 1/9.

80 ohms—2 1/2 in. Plessey. 15/6. P. & P. 2/-.

BARGAIN OPPORTUNITY

7 valve AM/FM/RG Replacement Chassis

A superbly powerful, high performance instrument which makes the ideal way to modernise old equipment whilst retaining good cabinet work. Provides tuning on long, medium and F.M. wavebands with permeability tuning on F.M. Large clear dial with stations clearly named. A.V.C., good neg. feedback. Magic eye. Connections for speaker, P.U. and Tape outlet. 3 w. output. A.C. 200/250 v. Circuit diagrams available.

Aligned, tested and ready for use.

£13.19.6

(Carr. and Ins. 8/6).

S.A.E. brings full details.

TRS MULLARD 3-3 AMPLIFIER. Kit £7.10.0. Built and tested £9.10.0.

TRS MULLARD 5-10 AMPLIFIER. Kit £29.19.6. Built and tested £12.1.6. Carr. on any of above items 7/6 each.

MULLARD Stereo Pre-amp and 10 + 10 watt Amplifier in process of production. AVAILABLE VERY SHORTLY.

PEAK SOUND STEREO AMP

With integrated pre-amp. Uses Cir-Kit for easy building. Model SA-8 has 14 matched transistors; 20-20,000 c/s ±3dB. Specially for use with high quality ceramic P.U.s. For 3-8 ohm speakers. Output 3.5 watts per channel. A high quality instrument for easy building and reliability. Will fit in safely under motor board to keep your cabinet work looking slim. Complete with instructions £12.19.6. P. & P. 4/-, PEAK SOUND POWER PACK 75/- (p/p 6/8)

"CIR-KIT" INSTANT CIRCUITS

Enables you to produce "printed circuits" quickly and cleanly without chemical or elaborate processes. Kit No. 3 includes baseboard, processed copper strip and sheet as advertised. 15/-

TAPE BARGAINS

1500ft. 7in. REEL. American professional tape. Leader and stop foils. In sealed boxes. 17/6 per reel (p. p. 1/- for one. 6d. each after first when ordered together). UNIQUE DOUBLE SIDED TAPE. 6 1/2 in. reels. Superb quality used normally. Ideal for experimenters too. 650ft. 9/-, 600ft. 8/6. MICRO FM (P. & P. 1/- per single reel. 6d. for each additional). PLASTIC REELS. 3in. 1/3; 4in. 2/-; 5in. 2/-; 6 1/2 in. 2/-; 7in. 2/3.

SINCLAIR KITS

We carry full stocks of these world-famous all-British designs including the very latest as advertised by this famous firm and give prompt delivery.

NEW MICROMATIC World's smallest radio as advertised. Kit 59/6. Ready built 79/6. MICRO FM 7 transistor FM Tuner Kit £5.19.6. Z12 Amp and pre-amp, built £4.9.6. STEREO 25 Pre-amp built £9.19.6. PZ3 Power Pack £3.19.6.

A UNIQUE TRANSFORMER SERVICE

We manufacture Transformers and Chokes of all types to stock or customer specification. Enquiries invited for prototype and small runs.

GARRARD UNITS & PLINTHS

LM.3000 Record Player with 9T.P. Stereo Cartridge. Limited number available. Brand new as from factory 8 gns.

AT.60 De-luxe Auto-change. 12in. turntable. Superbly engineered. Less cartridge 9 1/2 gns.

SP.25 De-luxe single record player, less cartridge 9 1/2 gns.

Packing and carriage on any one of above, 7/6 extra.

Garrard Plinth. The ideal modern mounting for the Garrard Units offered here. Will readily suit any hi-fi set-up. Beautifully finished in Teak. Complete with contemporary drop-on

plastic cover. Packing and carriage 5/-

Garrard Mono Cartridges from 15/-; Stereo from 25/-.

A SURPRISING 3d. WORTH

When you send a 3d. stamp for the latest TRS Bargain List (Feb. issue), you will find not only bargains galore to make genuine savings but even more advantages that come from buying the TRS way.

PACKING AND CARRIAGE

Terms: Cash with Order or C.O.D. Post and Packing—1lb. 1/-; 1lb. 1/8; 2lb. 3/6; 5lb. 5/-; 10lb. 8/6; 14lb. 8/-; over 10lb. Please mention P.W. when ordering.

★ VERY LARGE RANGES ALWAYS AVAILABLE

★ PERSONAL ATTENTION TO ALL ORDERS AND INQUIRIES

★ PROMPT RETURN SERVICE

★ GENUINE BARGAINS IN ALL DEPARTMENTS

★ SATISFACTION GUARANTEED ON ALL TRANSACTIONS

TRS RADIO COMPONENT SPECIALISTS

Est. 1946

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY

Phone: THO 2188

Daily 9.0 a.m. to 6.0 p.m.

Wednesdays 1.0 p.m.

A few doors from Thornton Heath Stn. S.R. from Victoria

foil. The foil is held on with a few turns of tinned copper wire which is then soldered to one of the tin plate screens. It is important that these screens be well bonded together, and dry joints or poor soldering should be avoided at all costs.

Setting up

The prototype receiver was aligned by setting the g.d.o. to 1.9Mc/s, tuning the capacitor VC1 to mid-position, and adjusting the oscillator trimmer TC2 for a signal. The i.f.t.'s were then peaked, and finally TC1 was adjusted for maximum volume. This setting up should be done with the tank circuit peaked for maximum signal. This is important because in the unpeaked state, the tank circuit presents a different load to the receiver input circuit and this was found to have an effect on the receiver tuning, and the setting of L1/TC1. With the b.f.o. switched in and the pitch control set at half mesh, the core of T1 was adjusted for a beat note, after which the swing of VC2 was checked.

The transmitter requires very little adjustment other than to make sure that the pentode anode load is resonant at 1.9Mc/s. The v.f.o. tuning capacitor and its parallel air spaced trimmer TC3 are both set to half mesh. Using another receiver as a monitor, TC3 is adjusted until a carrier is heard. At this point the swing of VC3 is checked. The actual coverage can be adjusted either by pruning VC3 or by slight alteration of the coil L4. If a 15 watt light bulb is now connected between the antenna and earth terminals and the key pressed the bulb should light. Adjustment of the tap via S7 and further adjustment of VC4 should enable the bulb to be lit to fair brilliance. The key should not be pressed while the taps are being altered, otherwise r.f. arcing will limit the life of the switch.

There are two slight drawbacks with this economy rig. One is that when the modulator is switched in the v.f.o. changes frequency due to the extra capacitive loading of the v.f.o. grid circuit by the diode and modulator circuitry. The v.f.o. is quite stable and functions well on f.m. but on switching back to the c.w. position the frequency will change again. In practise this means that the v.f.o. dial calibration is slightly different for c.w. and phone positions, however, since there is a ready made frequency marker built in, this is not too serious.

The other snag is that the peak r.f. output position of the p.a. tuning capacitor VC4 differs slightly from the peak receiving position. These faults were not found serious in practise and doubtless other readers will think of a way round them. The measured output for ten watts input was just over 6.5 watts.

Modifications

Since part one was published, various modifications have been tried and are offered as suggestions. The screens on L1 and L2 have been removed with negligible effect other than to warrant retuning. A 2½ in. 3Ω speaker has been connected to the secondary of the output transformer T2 via the spare push-button switch on the receiver bank. This functions as a speaker in/out switch. Results are quite good, and volume is sufficient for all local signals in the club net. There is room above the receiving section to fit a small bracket to wire in another valve on the audio side if required but the

rating of the mains transformer should not be exceeded. An 82kΩ resistor has been wired between the junction of C38 and the v.f.o./crystal switch, and earth. This forms a load for the v.f.o. when in the net position. Another 82kΩ has been substituted for R30. Using a small 8 watt audio amplifier, amplitude modulation (anode and screen) has proved highly successful and reports have been very favourable. For those who prefer to stick to f.m. the following modifications to the speech amplifier are recommended. Substitute a 3.3MΩ fixed resistor for VR4 and transfer this pot. to the input of the next triode, i.e. wire it in place of R21. A slow

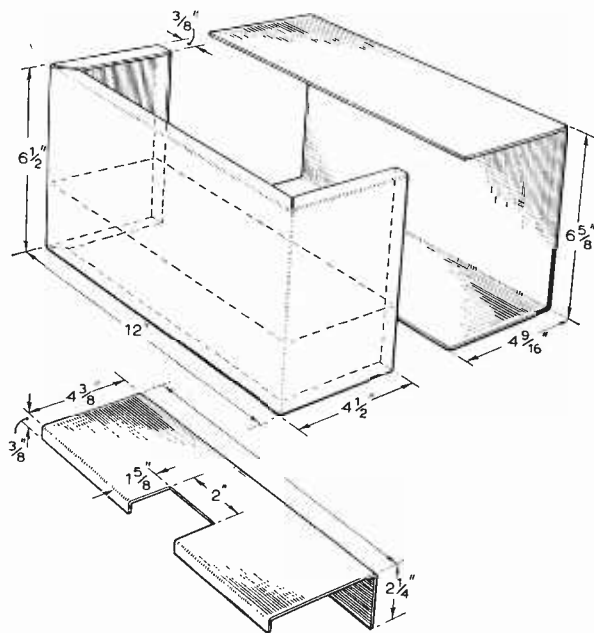


Fig. 7: Size and constructional details of the case.

motion drive on the v.f.o. would be a decided asset and make netting easier, although no great difficulty has been experienced with the prototype. In last month's article, the two capacitors shown unmarked in Fig. 3 next to the modulator valve V4, are C26 and C31.

The author is indebted to G3JDG for his assistance in testing the rig on the air. ■

FREE

Inside next month's issue of
Practical Electronics a
Component Selection Calculator

on sale March 17.

new books

SHORT WAVE ANTENNAS

By J. D. Nicholson. Published by World Publications, Denmark, and distributed by Wm. Dawson and Sons Ltd. 54 pages. Size 6½in. x 4½in. Price 10s.

YET another book with the customary 10 or so pages on the propagation of radio waves. After this comes a useful practical chapter dealing with general features of antenna construction. The remainder of the book is given up to details, illustrated with rough sketches, of a large variety of antennae varying from a simple vertical to triple dipole and fan vertical types.

Unfortunately, most of the designs assume the listener has plenty of space outdoors for his aerial. Poor town dwellers who are unable to erect great outdoor arrays are covered by a short chapter entitled "Novelty Antennas". To your reviewer's chagrin the picture rail long-wire antenna is given 2½ lines under this head. A town dweller, I have been using this aerial for years to pull in the rarest catches.—JMG

SHORT WAVE RECEPTION

By Bert Johansen. Published by World Publications, Denmark, and distributed by Wm. Dawson and Sons Ltd. 66 pages. Size 8½in. x 5½in. Price 19s.

"HOW to improve—and how to build" is the sub-title of this book which contains details of eight transistorised circuits designed to improve short wave reception. Constructional details are somewhat sketchy so this is not the book for the beginner.

Worse still the book covers some useful pieces of ancillary equipment but gives no real guide to operating them once constructed. For example, details are given for the construction of a 10-30Mc/s pre-selector—an extremely useful piece of equipment which can improve a cheaper receiver. Unfortunately there is no clue as to how the unit should be used once built. Admitted the experienced ham will know, but the beginner, and the book gives the impression that it is intended for the beginner, would be lost.—JMG

BBC HANDBOOK 1966

Published by The British Broadcasting Corporation. 260 pages. Size 7½in. x 4½in. Price 7s. 6d.

ON the face of it, the BBC Handbook does not seem the sort of book to review in these pages. Nevertheless, there is a great deal of useful information contained within its covers for readers of P.W. and P.T.V., including field contour maps of BBC TV and v.h.f. radio stations, together with technical information on those stations. There is also a section on frequency allocations and reception.

Among the wealth of information in the book there is certain to be much of interest to many readers. A handy, and inexpensive, book.—LB

RADIO AMATEURS' EXAMINATION MANUAL

By B. W. F. Mainprize, B.Sc.(Eng) G5MP.

A GUIDE TO AMATEUR RADIO

By Pat Hawker, G3VA. Published by the Radio Society of Great Britain. Size 9½in. x 7½in. Price 5s. 9d. each.

THESE are both, of course, new editions of old favourites. The RAE Manual now appears in its fifth edition, the first four having achieved sales of 20,000 copies. A number of minor revisions are made and some additional information included. A very useful addition is some advice on tackling the RAE prepared by members of the RSGB who serve on the City and Guilds of London Institute Advisory Committee for the RAE. The manual contains specimen answers to actual examination papers. For those contemplating their ticket—this is a "must".

The Guide reaches the venerable age of its twelfth edition. The revised edition takes into account changes recently introduced in UK amateur regulations and the constructional projects reflect the greater use of single sideband techniques and semiconductor devices. Both these new editions represent remarkable value for money.—CFB

OUTLINE OF RADIO AND TELEVISION

By J. P. Hawker. Published by George Newnes Ltd., London. 400 pages. Size 8½in. x 5½in. Price 30s.

AS the title suggests, this book outlines the principles and operation of radio and television reception. It is written by Pat Hawker, who has many radio and television books to his credit. He starts this one with fundamentals—electric currents, radio waves and so on—continues in depth with sound and vision receivers and concludes on aerials and tape recorders. In all, there are 22 sections. There is not enough material in the various sections of this book to consider it as a reference work, but for thirty-bob it is a good buy for those who have little or no knowledge of the subject. Also, readers who have a working knowledge of radio and television could well benefit from this work. Pat Hawker, who for several years has been the Communications Correspondent for *Electronics Weekly*, is in a unique position to know what's going on in the industry. He has made good use of this in his book, which takes a fresh look at the subject. In the preface, he writes: "No prior technical knowledge has been assumed, although it is appreciated that many readers are likely to have already absorbed some information from casual reading of technical and hobby magazines. Although a virtually non-mathematical approach has been adopted, it is nevertheless recognised that readers today do not want to be spoon fed with oversimplifications that will have to be discarded, should they wish later to gain a more advanced understanding of the subject".—DCR

RADIO • HI-FI • COMPONENTS • TEST EQUIPMENT

CP.110 11-PIECE CHASSIS PUNCH SET




Top grade machined steel. Contains 1", 1 1/2", 1" and 1 1/4" punches, complete with gripper and accessories in carrying case. £3.12.6.



ALL TRANSISTOR MONO & STEREO PRE AMPLIFIERS

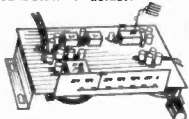Provide extra stage of amplification for use with magnetic cartridges, tape and microphone inputs. Both models feature wide band pass range, 20-20,000 cps. As reviewed in *The Gramophone*, Dec. 1965.
PRE 301 MONO £4.12.6
PRE 302 STEREO £5.15.0



EAGLE FMT41. FM TUNER

Sub-miniature 6 transistor 3 diode F.M. Tuner. Covers 88-108 Mc. Operates from 9-volt battery, micro miniature circuit giving brilliant FM reception. Ready to use, simply connect to your Hi Fi amplifier. Instructions supplied.

£8.10.0



REMOTE CONTROL STEREO HEADPHONE STATION LS.2

A junction box for connecting stereo headphones to a stereo or monaural system. Separate controls for each channel. On/off switch. Stereo sockets allow two sets of headphones to be used. With instructions and 20ft. of 5 conductor cable.

£3.5.0



EEK28. 28

PROJECT CONSTRUCTIONAL KIT This advanced educational kit is excellent for beginners as well as the more advanced experimenter. Not even a soldering iron is needed. Complete with 60 page booklet giving full details of suggested circuits.

£6.10.0



LA9P. AC ELIMINATOR

with a doublewound step down transformer to operate 9v Radios, etc., from A.C. Mains.

£1.8.6

SPECIAL OFFER!

GOOSENECK PENCIL TYPE DYNAMIC MICROPHONE

Imp: 50K ohm.


Output: 52db. Response: 40-13,500 c.p.s.

With base with on/off switch, stand adaptor and cable. USUAL PRICE 49s. SPECIAL OFFER PRICE

59/6



ALL ITEMS SENT POST FREE

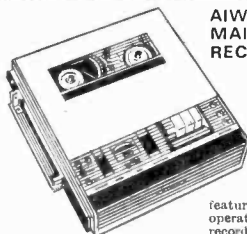

AIWA TP.712 2-SPEED 5" REEL MAINS AND BATTERY TAPE RECORDER

Loaded with features hitherto only found in more expensive tape recorders: AVC system automatically adjusts recording volume level. TWO-WAY OPERATION: A.C. mains or batteries TWO HOURS OF RECORDING TIME: Using 1.5 mil 600 ft. tape. REMOTE CONTROL. TONE CONTROL. LEVEL METER: Indicates recording and battery levels. Other features include 1 1/2 and 3 1/2 i.p.s. speeds, smooth operating push-button keyboard, input for radio, record player, TV, etc., socket for an external speaker. Complete with Dynamic microphone, earphone, 5in. 600ft. tape, 5in. empty reel batteries and A.C. lead. Size: 12 1/2in. x 10 1/2in. x 3 1/2in.

26 1/2 Gns.

EAGLE PRODUCTS

MAGNETIC STEREO CARTRIDGES

M1007G GOLD

Response: 20-20,000 cps

Output: 5mV at 1Kc/

5cm/sec

Stylus: 0.5 Mil diamond

Tracking Pressure

1-2.5 grams.

£6.12.6

M1007F SILVER

Response: 20-18,000 cps

Output: 10mV at 1Kc/


5cm/sec

Stylus: 0.7 Mil diamond

Tracking Pressure

2-4 grams.


£5.14.6

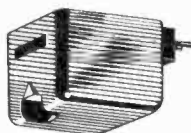

As reviewed in *Hi Fi News* Sept. 1965.

Both feature singularly smooth reproduction and incisive separation of stereo channels

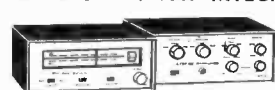EAGLE SA100. 10W INTEGRATED STEREO AMPLIFIER



EAGLE AFM100. AM-FM TUNER

Combines a host of advanced features that easily make it the finest AM-FM tuner in its class. A tuned RF stage on FM, AFC circuit and a heavy flywheel giving smooth but effortless tuning, built in AM Ferrite aerial. FM 88-108Mc. AM 535-1605 K/s.

£18.0.0

£29.0.0

MS80. 20W ROSEWOOD SPEAKER SYSTEM

The perfect answer for the music lover who wants full range fidelity in a compact system. Features an 8in. full range high compliance speaker with an output capacity of 20 watts RMS. Frequency response: 30-20,000 c.p.s. Resonant frequency: 30-40 c.p.s. Sensitivity: 97 db/w. Flux density: Over 12,000. Impedance: 16 ohm. Size 14 1/2in. high x 10 1/2in. wide x 8in. deep.

£14.14.0

As well as this beautifully designed speaker there are two other models MS65. 10 watts RMS at £12.12.0 and MS40 5 watts RMS £8.10.0.

All three speakers are finished in magnificent rosewood and the entire cabinet filled with acoustic damping material.




AIWA P.172 3-SPEED 3-BAND MAINS & BATTERY RADIO-RECORD PLAYER

Plays all records, 33 1/3, 45 and 78 rpm, plus built-in LW/MW/FM radio. All in, a smartly designed portable, offering the best of both worlds: battery or A.C. mains operation. Large oval speaker, gives exciting reproduction of your records and favourite radio stations anywhere and everywhere you go. 13-transistor circuit produces big power output. Complete with earphone, batteries, A.C. lead, carrying handle and 33 1/3 rpm test record. Size: 10 1/2" x 15 1/2" x 4".

29 1/2 guineas

SA.80N. 8-WATT INTEGRATED STEREO AMPLIFIER

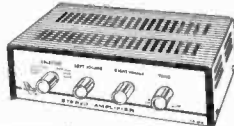Recognised as the leading low priced stereo amplifier, 4 watts per channel. Inputs for Pick-up (100mV) and Tuner (100mV). Frequency response. 50-15,000 cps. 200/250v. A.C. Styled in Grey and Silver with metal knobs. £12.0.0.



FOR FULL DETAILS OF THESE AND MANY OTHER ITEMS SEND FOR FREE COMPREHENSIVE CATALOGUE, EAGLE NEWS AND ORDER FORM. ALL ITEMS AVAILABLE POST FREE AND COVERED BY 12 MONTHS' GUARANTEE.

CALLERS WELCOME AT OUR HI-FI SHOWROOM

RELDA RADIO LTD

(Dept. P.W.16) 87 Tottenham Court Road, London, W.1.


TT.144 DYNAMIC TRANSISTOR TESTER

Tests in-circuit or out of circuit. Identifies PNP and NPN types. Indicates electrode open circuits, short circuits and current drain. Complete with instructions.

£4.10.0



KY.102 SEMI-AUTOMATIC BUG KEY

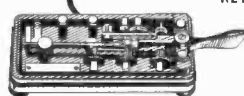


7 adjustments for speed and comfort. Key adjustable for tension, swing, speed etc. Precision tooled anti rust, nickel-plated brass and stainless steel operating parts. Variable speed capable of 5 to approx. 60 w.p.m. Complete with cord and transparent dust cover. £5.12.6.

RF.40 RF FIELD INDICATOR

Broad tuning covers 1-250 Mc/s in five calibrated bands. Can also be used as frequency checker. Detects undesired radiation or spurious frequencies. RF is measured on an accurate 200 uA panel meter.

£4.10.0

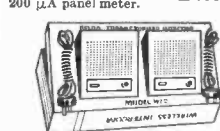

WI-2. TRANSISTORISED WIRELESS INTERCOM


No wires, no installation needed, simply plug them into AC power point and talk. Units have press-to-talk lock switch and on-off volume control. Ideal intercom or Baby Alarm for home, office, factory.

£14.12.0

DP303. DOOR PHONE INTERCOM

Ultra sensitive transistorized intercom designed so that you may answer the door from within for greater convenience and safety.

£4.12.6

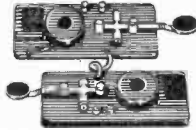

MCK.2. MORSE CODE KIT

Two station morse code kit supplied with instructions. 50ft. of connection wire and morse code charts.

£2.2.0

WIRELESS MICROPHONES

WM909 (as illustrated) Pocket FM Wireless transmitter complete with tie-pin microphone. Transmits clearly up to 100 yds. and is fully tunable over the entire FM band. Simply used with an FM radio or tuner.

£14.0.0

Also available WM808 Professional stick type FM Wireless Microphone.

£21.0.0

These cannot be operated in U.K.



Armstrong

MONO TUNER-AMPLIFIERS



227M MONO TUNER-AMPLIFIER	£40.1.6
(illustrated)	
127M MONO TUNER-AMPLIFIER	£29.18.9
127 STEREO TUNER-AMPLIFIER	£40.1.6
OPTIONAL CASE, teak and vinyl hide	£3.10.0

Three tuner-amplifiers, identical in size and similar in styling, each with the same high performance AM-FM Tuner incorporated. The 227M provides 10 watts power output whilst the 127M, with 5 watts output, is designed for those whose power requirements are more modest. The 127 is the stereo version of 127M, having two amplifiers, each of 5 watts output. All three have similar facilities; pickup and tape inputs, tape recording output, bass and treble tone controls.

For full details and technical specifications of all models, plus list of stockists, post coupon or write mentioning 4PW67.

ARMSTRONG AUDIO LTD.
WALTERS ROAD, N.7
Telephone: North 3213

AUDIO FAIR ENQUIRY ROOM 539
BOOTH 45 DEMONSTRATION ROOM 538

Name


Address

4PW67

Household Heating Supplies LTD brings central heating price down

*you save £150 on
D.I.Y installations!*

**OIL —
GAS —
SOLID FUEL**

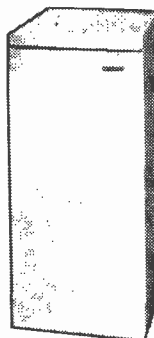

Powell Duffryn
G45 Gas Boiler

You can do better than buy Central Heating at "frozen" prices—you can save at least £150 by doing-it-yourself—and you get FREE advice before and during installation.

Free delivery to your home.
NO DEPOSIT—5 YEARS
TO PAY. Branches at
Croydon, Wood Green,
Tottenham, Bedford, Man-
chester and Leicester.




To: Household Heating Supplies Ltd.
7 Ilford Lane, Ilford, Essex ILF 5098/9
Please send further details.

Name

Address

Telephone P.W.4.67

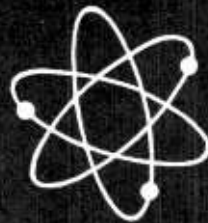

MODULATED LIGHT TRANSMISSION

H. L. MASON

THIS unit was designed to provide transmission by means of a light beam, with a reasonable frequency response, yet at low cost.

The circuit of the transmitter is shown in Fig. 1. The input signal is fed to the first half of an ECC82 valve. The signal appearing at the anode is fed to the grid of the second half of this valve, which has, as an anode load, a miniature neon tube with self contained resistor. With care, the plastic case may be removed, exposing the neon tube and resistor.

If one of these cannot be obtained, a miniature neon of the type used in neon tester screwdrivers

the voltage across the ORP12 does not exceed about 80-90 volts, and that the total dissipation *never* exceeds 200mW.

Construction

This is not critical but the layout of the prototype transmitter is shown in Fig. 3. The gain of the circuit is very low as it was only intended for high input use, so there are no problems regarding hum or instability. Heater wiring must be kept away from the grid pins of the ECC82 and the valveholder spigot earthed via the valveholder bolts, together with pins 9 and 8.

Wires to the neon should have 250 volt insulation, and pass through suitable grommets on the chassis. C2 should be new, not surplus with good insulation. If treble loss is experienced (none in the prototype) C2 may be reduced to 2,000 or 3,000 pF.

Aligning

The lenses should be as large as possible (2—3in. diameter) with about an 8in. focal length. The focal length can be found by the following method. Put a sheet of white paper on the floor under an electric light. Hold the lens horizontally about 8in. above the paper, and move it up and down until a sharp image of the bulb is obtained on the paper. The lens/paper distance is the focal length, and this is the correct spacing for the lens-to-photocell and lens-to-neon. The process is repeated for both lenses.

When the lenses are correctly positioned in front of the cell and neon respectively the two units should be placed about 10ft. apart for initial testing. This should be done in a fairly dark room. When the photocell is put at the focus of one lens, and the illuminated neon at the focus of the other (i.e. H.T. on) an orange "spot" should be seen on the photo-

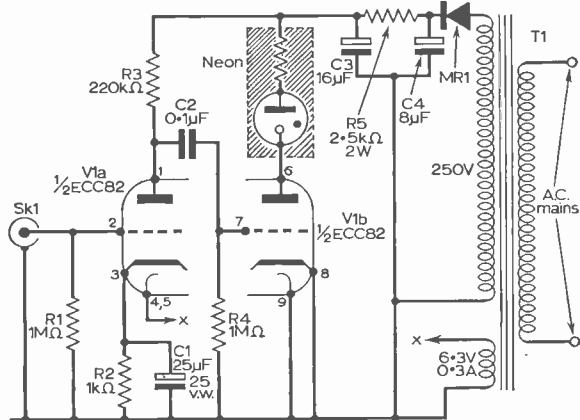


Fig. 1: Circuit of the transmitter.

may be used. The dropper resistor should be about 100kΩ. These tubes (when complete with resistor) draw a current of approximately 2mA, which is well within the rating of the ECC82 (10.5mA). The fluctuating anode current varies the neon's light output, thereby making an effective light transmitter.

Receiver

The receiver can be specifically made, or existing equipment modified. An experimental type of receiver is shown in Fig. 2a. The cathode bias components are replaced by an ORP12 photocell, the volume set at minimum and the valve used as a grounded grid amplifier. The valve (an ECC83) gave excellent quality, and was used as a preamplifier feeding a high power audio amplifier. A slightly improved circuit is shown in Fig. 2b. This uses an ORP12 to feed an OC71, which then feeds a power amplifier.

Whichever circuit is used, especially one using valves (i.e. H.T.), care must be taken to ensure that

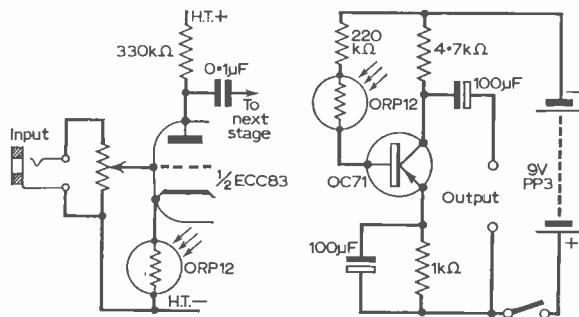


Fig. 2a: Valve receiver circuit.

Fig. 2b: Alternative transistor version.

cell, which is of course the image of the neon. The cell is moved about for best volume. In the original, the loudest position was when the image was on the edge.

Final notes

The circuit is very simple, lending itself to experiment. Using an ECC81 and reducing R2 to 220 Ω gave higher gain but results were inferior and the neon was over-modulated. The extinguishing volt-


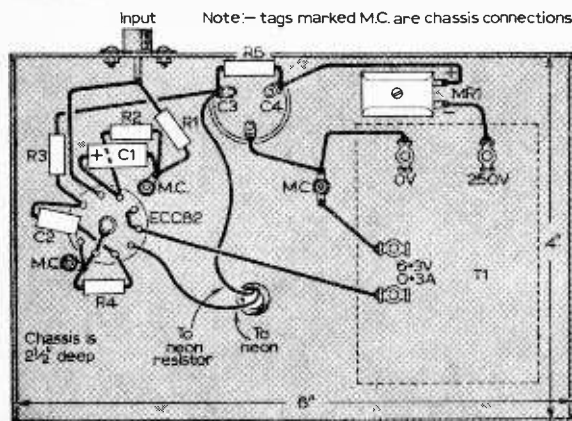


Fig. 3 (above): Layout of the prototype (Fig. 1).

Fig. 4 (below): Block diagram of the system.

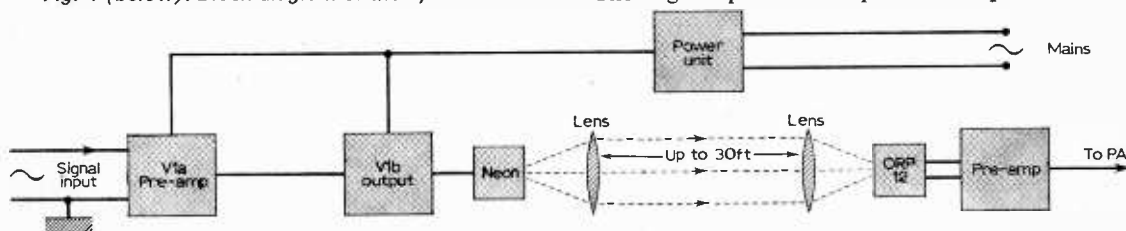

age and striking voltages of a neon are different, and with over-modulation the neon may be extinguished for part of the cycle. In this case the circuit will go into darkness, squaring or "clipping" will occur, and very heavy distortion will result. Optimum modulation occurs when the neon just dims on the loudest passages.

The transmission of music with the prototype was

★ components list

TRANSMITTER (Fig. 1)

Resistors:

- R1 1M Ω , $\frac{1}{2}$ W
- R2 1k Ω , $\frac{1}{2}$ W
- R3 220k Ω , $\frac{1}{2}$ W
- R4 1M Ω , $\frac{1}{2}$ W
- R5 2.5k Ω , 2W

Capacitors:

- C1 25 μ F, 25V electrolytic
- C2 0.1 μ F, 350V paper
- C3/C4 8-16 μ F, 350V electrolytic

Miscellaneous:

- V1 ECC82
- T1 Secondaries 250V, 20mA; 6.3V 0.3A
- MR1 Halfwave rectifier 250V, 20mA
- Neon tube with limiting resistor
- B9A valveholder, coax input socket, wire, bolts, etc.

RECEIVER (Fig. 2b)

Resistors: 1k Ω , 220k Ω , 4.7k Ω

Capacitors: two 100 μ F, 3V

Semiconductors: OC71, ORP12

quite good, reproducing the higher frequencies well and giving good volume over a distance of 60ft. The high-impedance output of a tape-recorder was

used. The output impedance was 15k Ω so R1 was adjusted to suit. With transformer input R1 may be omitted. The sensitivity is about 500mV.

If both neon and photocell are shielded, the instrument may be used in the light, providing it is not of the fluorescent variety, which produces a deafening hum at twice the mains frequency! A block diagram of the system is shown in Fig. 4. ■

PRACTICAL TELEVISION—MARCH 1967 ISSUE

U.H.F. AERIALS

The author discusses design requirements for u.h.f. aerials in an easy-to-follow manner. Full details of an experimental wide-band u.h.f. aerial with all dimensions and constructional details. Covers Channels 21-34, 39-51 or 52-68.

WIDE-RANGE WOBBULATOR

Full constructional details for this instrument which helps in the correct alignment of receivers of almost any type. Uses printed circuit technique and four transistors and two diodes. Covers i.f. frequencies from 400kc/s to 38Mc/s.

HUM IN TV RECEIVERS

The author advises on the different types of hum that may be encountered in TV receivers and how and when it might occur and outlines some of the cures of this sometimes very troublesome fault.

ON SALE NOW — PRICE 2 SHILLINGS

VALUABLE NEW HANDBOOK FREE TO AMBITIOUS ENGINEERS

Have you had your copy of "Engineering Opportunities"?

The new edition of "ENGINEERING OPPORTUNITIES" is now available—without charge—to all who are anxious for a worthwhile post in Engineering. Frank, informative and completely up to date, the new "ENGINEERING OPPORTUNITIES" should be in the hands of every person engaged in any branch of the Engineering industry, irrespective of age, experience or training.

On 'SATISFACTION or REFUND of FEE' terms

This remarkable book gives details of examinations and courses in every branch of Engineering, Building, etc., outlines the openings available and describes our Special Appointments Department.

WHICH OF THESE IS YOUR PET SUBJECT?

RADIO ENGINEERING
Advanced Radio — Gen.
Radio — Radio & TV
Servicing — TV Eng. —
Telecommunications — Sound
Recording — Automation —
Practical Radio — Radio
Amateurs' Exam.

ELECTRICAL ENG.
Advanced Electrical Eng. —
Gen. Electrical Eng. —
Installations — Draughts-
manship — Illuminating Eng.
— Refrigeration — Elem.
Electrical Science — Elec-
trical Supply — Mining Elec.
Engineering.

CIVIL ENGINEERING
Advanced Civil Eng. — Gen.
Civil Eng. — Municipal
Eng. — Structural Eng. —
Sanitary Eng. — Road Eng.
— Hydraulics — Mining —
Water Supply — Petrol Tech.

ELECTRONIC ENG.
Advanced Electronic Eng. —
Gen. Electronic Eng. —
Applied Electronics — Prac.
Electronics — Radar Tech. —
Frequency Modulation —
Transistors.

MECHANICAL ENG.
Advanced Mechanical Eng. —
Gen. Mechanical Eng. —
Maintenance Eng. — Diesel
Eng. — Press Tool Design —
Sheet Metal Work — Welding
— Eng. Pattern Making —
Inspection — Draughtsman-
ship — Metallurgy — Pro-
duction Eng.

AUTOMOBILE ENG.
Advanced Automobile Eng. —
Gen. Automobile Eng. —
Automobile Maintenance
Repair — Automobile Diesel
Maintenance — Automobile
Elec. Equipment — Garage
Management.

WE HAVE A WIDE RANGE OF COURSES IN OTHER SUBJECTS IN-
CLUDING CHEMICAL ENG., AERO ENG., MANAGEMENT, INSTRU-
MENT TECHNOLOGY, WORKS STUDY, MATHEMATICS, ETC.

Which qualification would increase your earning power?
A.M.I.Mech.E., A.M.S.E. A.M.I.C.E., A.M.I.E.R.E., B.Sc.,
A.M.I.P.E., A.M.I.M.I., A.R.I.B.A., A.I.O.B., A.M.I.Chem.E., A.R.I.C.S.,
M.R.S.H., A.M.I.E.D., A.M.I.Mun.E., CITY & GUILDS, GEN. CERT. OF
EDUCATION, ETC.

British Institute of Engineering Technology
316A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE

THIS BOOK TELLS YOU

- ★ HOW to get a better paid, more interesting job.
- ★ HOW to qualify for rapid promotion.
- ★ HOW to put some letters after your name and become a key man . . . quickly and easily.
- ★ HOW to benefit from our free Advisory and Appointments Depts.
- ★ HOW you can take advantage of the chances you are now missing.
- ★ HOW, irrespective of your age, education or experience, YOU can succeed in any branch of Engineering.

132 PAGES OF EXPERT
CAREER - GUIDANCE

PRACTICAL EQUIPMENT

Basic Practical and Theore-
tic Courses for beginners in
Radio, T.V., Electronics, Etc
A.M.I.E.R.E. City & Guilds
Radio Amateurs' Exam.
R.T.E.B. Certificate
P.M.G. Certificate
Practical Radio
Radio & Television Servicing
Practical Electronics
Electronics Engineering
Automation

INCLUDING TOOLS

The specialist Elec-
tronics Division of
B.I.E.T.
NOW offers you a
real laboratory train-
ing at home with
practical equipment.
Ask for details.

B.I.E.T.

You are bound to benefit from reading
"ENGINEERING OPPORTUNI-
TIES", and if you are earning less than
£30 a week you should send for your
copy now—FREE and without
obligation.

POST NOW!

TO B.I.E.T., 410A, ALDERMASTON COURT,
ALDERMASTON, BERKSHIRE.

3d. stamp if posted in
an unsealed envelope.

Please send me a FREE copy of "ENGINEERING
OPPORTUNITIES." I am interested in (state subject,
exam., or career).

NAME

ADDRESS

WRITE IF YOU PREFER NOT TO CUT THIS PAGE



THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

DE LUXE PLAYERS

4-Speed Players 2-tone Cabinets 17 x 15 x 8 in. High flux loudspeakers and High Quality Amplifiers ready built. Quality output. Volume and Bass control. Special instructions enable assembly in 30 minutes only 12 months guarantee.

TO BUILD YOURSELF

Post 2/6 per item

PORTABLE CABINET
As illustrated to fit standard player 69/6 or autotuner.

3 WATT AMPLIFIER.
Ready made and tested. With UCL86 triode pentode valve and 59/6

SINGLE PLAY UNITS

BSG GU7 £24.9.8

Garrard SRP12 £24.9.8

Garrard SP25 £10.9.6

Philips AG101C £12.9.6

Garrard A70 £19.9.8

Garrard LAB90 £24.9.8

Garrard 401 £29.9.8

Garrard Teak Wood Base WB1. Ready cut for mounting. 1000, 2000, 3000, SP25, AT60.

72/6

INTEGRATED STEREO AMPLIFIER. 4 watts per channel. A splendid example of functional design and value. Grey/Silver Crackle cabinet, size 10 x 8 1/2 x 3 in. 200/250v. A.C. Separate Gram and Tuner inputs

Self-contained pre-amp and controls. Post 2/6

Q MAX CHASSIS CUTTER

Complete: a die, a punch, an Allen screw and key

1in. 14/8 1in. 15/9 1in. 13/17 1in. 20/8 2 1/2in. 37/9

1in. 14/8 1in. 18/1 1in. 18/16 1in. 22/6 2in. 44/3

1in. 15/6 1 1/2in. 18/1 1 1/2in. 20/1 2in. 34/3 1in. sq. 31/6

BARGAIN XTAL PICK-UP ARM Complete with ACOS LP-78 Turnover Head and Styl 20/- Stereo 30/-

SPEAKER FRET Tyan various colours. 52in. wide from 10/- 1/2. 26in. wide from 5/- 1/2. Samples S.A.E.

EXPANDED METAL Gold or Silver 12 x 12in. 6/-

NEW GARRARD GRAM MOTORS 100-130v. A.C. 15/- pair for 200/250v. (in series), or 10/- each (Post 2/6).

FULL WAVE BRIDGE SELENIUM RECTIFIERS. 6 or 12v. outputs, 1 amp. 8/9; 2.5 amp. 11/3; 4 amp. 17/6.

CHARGER TRANSFORMERS P. & P. 2/6 Tapped 200/250 v. for charking at 2, 6 or 12 v., 1 amp., 17/6; 2 amps. 21/-; 4 amps. 25/- Circuit included. Amp meter 5 amp. 10/6

MOVING COIL MULTIMETER TK 25. 0-1,000 v. A.C./D.C. ohms 0 to 100k. etc.

MOVING COIL MULTIMETER EPIOX. 0-1,000 v. A.C./D.C. ohms 0 to 3 meg. etc.

MOVING COIL MULTIMETER EP20K. 0-2,500 v. D.C. 20,000 ohms per volt. 0-1,000 v. A.C. Ohms 0 to 6 meg. 50 Microamps full scale.

NEW MULLARD TRANSISTORS

OC71 6/-; OC72 7/6; OC81D 6/-; OC81 6/-; AF115 8/6; AF114 8/6; OC44 8/-; OC45 8/-; OC171 9/-; OC170 8/6; AF117/-; OC8612/6; AD14015/-; OC3515/-; Holders 1/3.

ARDENT TRANSISTOR TRANSFORMERS

D3035. 7.3 CT. 1 Push Pull to 3 ohms for OC72, OC81. 11/-

D3034. 1.75 CT. Push Pull Driver for OC72, OC81. 11/-

D3038. 11.5 CT. 1 Output to 3 ohms for OC72, OC81. 11/-

TRANSISTOR MAINS ELIMINATORS

Famous "Power-Mite" 9 volt. Same size as PP9 battery. Fully smoothed. 150mA. Full-wave circuit. 45/-

WEYRAD P50 Transistor Coils

RA2W 1 in. Ferrite Aerial with car aerial coil. 12/6

One P50/A10. 500/200. 5/4

470 kΩ I.F. P50/200. 5/7

3rd I.F. P50/300. 6/-

VOLUME CONTROLS

Long spindles. Midget Size 5 k. ohms to 2 Meg. LOG or LIN. L/S 3/- D.P. 5/-

STEREO L/S 10/6 D.P. 14/6.

COAXIAL PLUG 1/1. PANEL SOCKETS 1/1. LINE SOCKETS 2/1. OUTLET BOXES. SURFACE OR PLUSH 4/6.

BALANCED TWIN FEEDERS 6d. 4y. 80 or 300 ohms.

TELESCOPIC CHROME AERIAL. 6in. extends to 23 in. 6/6.

TV REMOTE CONTROL

For PHILIPS 197G111A. 121A, 125A, 142A, 237G111A, 113A, 121A, 131A STELLA

ST1033A. 39A. 43A. 53A. CSORR CT1910A. 21A. CT2310A. 21A. 31A. PHILIPS.

Price 3 gns. Post 2/6

Our Price 12/6 Post 2/6

Brand New, includes 11lt. 7-way cable, MULLARD OA81

2 pots, 3 switches, 5 resistors.

RETURN OF POST DESPATCH Minimum P.P. Charge 1/6 unless otherwise stated. C.O.D. 5/- extra. Full List 1/-

RADIO COMPONENTS SPECIALISTS 337 WHITEHORSE ROAD, WEST CROYDON

Written guarantee with every purchase. (Export—send remittance and extra postage, no C.O.D.) (Buses 133, 68 pass door). S.R. Stn. Selhurst. Tel. THO 1665

STELLA RECORD PLAYER AMPLIFIER

4 watt. 2 stage. 3 to 7 ohm. Neg. feed back. UCL82, UY85. 200-250v. A.C. tapped input. Chassis size 8 1/2 x 4 1/2 in. high. Gold/Walnut knobs. Volume and Tone controls on separate Polished Wood Panel 8 x 2 in. Brand new with makers' guarantee. Bargain price. Post 2/6 78/6

NEW TUBULAR ELECTROLYTICS

2/350 v. 2/3	100/25 v. 9/-	8/600 v. 9/6
4/350 v. 2/3	250/25 v. 2/6	16/600 v. 12/6
8/450 v. 2/3	500/15 v. 3/-	16+16/500 v. 7/6
16/450 v. 3/-	8+8/450v. 3/6	32+32/450 v. 6/-
32/450 v. 3/9	8+16/450 v. 3/6	50+50/350 v. 7/-
25/25 v. 1/3	16+16/450 v. 4/3	80+100/350 v. 10/6
50/50 v. 2/-	32+32/350 v. 4/3	100+200/275v. 12/6

PAPER TUBULARS

350v.-0.1 9d. 0.5 2/6; 1 mfd. 3/-; 2 mfd. 150v. 3/-
500v.-0.001 to 0.05 9d.; 0.1 1/-; 0.25 1/6; 0.5 3/-
1,000v.-0.001, 0.0022, 0.0047, 0.01, 0.02, 1/6; 0.047, 0.1 2/6.

E.H.T. CONDENSERS. 0.001mfd. 7kV. 6/6; 20kV. 10/6.

SUB-MIN. ELECTROLYTICS. 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 250mfd. 15v. 2/6; 500, 1000mfd. 15v. 3/6; 2,000mfd. 25v. 7/-

CERAMIC 500v. 1 pF. to 0.01mfd. 9d. Discs 1/-

SILVER MICA. Close tolerance (plus or minus 5 p.p.t.). 5 to 47 pF. 1/-; ditto 1/-; 50 to 800 pF. 1/-; 1,000 to 5,000 pF. 2/-

TWIN GANG. "0-0" 208 pF. + 176 pF. 10/6; 385 pF. miniatur. 10/-; 500 pF. standard with trimmers. 9/-; 500pF midget less trimmers. 7/6; 500 pF. slow motion, standard 9/-; small 3-range 500 pF. 18/6. Single "0" 385 pF. 7/6. twin 10/-

SHORT WAVE. Slide 10 pF. 28 pF. 50 pF. 75 pF. 100 pF. 150 pF. 5/6 each. Can be ranged. Couplers 9d. each.

TUNING. Solid dielectric. 100 pF. 300 pF. 500 pF. 3/6 each.

TRIMMERS. Compression ceramic. 30, 50, 70 pF. 9d.; 100 pF. 150 pF. 1/3; 250 pF. 1/6; 600 pF. 750 pF. 1/9.

250v. RECTIFIERS. Selenium 1/ wave 100mA 5/-; BY100 10/-.

CONTACT COOLED 1 wave 60mA. 7/6; 85mA. 9/6; Full wave 75mA 10/-; 150mA 19/6; T.V. rect. 10/-.

SPECIAL OFFER! NEW B.A.S.F. TAPE

7 in. L.P. 1,800 ft. (Cat. LGS35) 45/-

7 in. D.P. 2,400 ft. (Cat. LGS26) 70/-

Spare Spools 2/6. Tape Splicers 5/-, Leader Tape 4/6.

Tape Heads: Collaro 2 track 28/6 pair. B.S.R. 4 track 99/6.

MAINS TRANSFORMERS

E.M.I. 280-0-280, 100mA. 6.3 v. 4. 6.3 v. 2. 19/6

250-0-250, 80 mA. 6.3 v. 3.5 v. Rectifier 6.3 v. 25/-

1A or 5 v. 2. 2. ditto 350-0-350 6.3 v. 4. 29/6

MT.510 300-0-300 120 mA. 6.3 v. 4. 29/6

MINIATURE 220 v. 20 mA. A.C. 6.3 v. 1A. 10/6

MIDGET 220 v. 45 mA. 6.3 v. 2. 15/6

SMALL 300-0-300 70 mA. 6.3 v. 4. 19/6

HEATER TRANS. 6.3 v. 11 A. 7/6; 6.3 v. 4A. 10/6

Ditto tapped sec. 1.4 v. 2. 3. 4. 5. 6.3 v. 15 amp. 10/6

GENERAL PURPOSE LOW VOLTAGE. Outputs 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. at 2A. 25/-

1A. 5, 10, 15, 20, 25, 30, 40, 45, 50, 55, 60 29/6; 2A. 47/6.

AUTO TRANSFORMERS 0-115-230 volt Input/Output. 60 w. 15/6; 150w 25/-; 500 w. 92/6; 1,000 w. 175/-

CRYSTAL MIKE INSERTS

1 1/2 x 2in. 6/-; ACOS 1 1/2 x 2in. 8/-; BM3 1 1/2 x 2in. 7/6

TANNOY CARBON MIKE with Switch. 5/6

HEADPHONES 2000 ohms 12/6. 4000 ohms 15/-

1967 GRAM CHASSIS

Post 5/-

Three Wavebands: Five Valves: ECH81, EP89, EBC81, EL84, EZ80.

12-month guarantee. A.C. 200-250 v. Ferrite Aerial

5 watts 3 ohms Chassis 13 1/2 in. x 7 1/2 in. x 4 in. dial size

13in. x 4in. Two Pilot Lamps. Four Knobs. £10.10

Aligned calibrated. Chassis isolated from mains

DE-LUXE STEREO GRAM CHASSIS. V.H.F. M.W. S.W.L. 19-50cm. S.W.2. 60-180 m. Maric eye. push buttons. 6 valve + rect. AC only 200/250v.

Size 15 x 7 1/2 x 6in. h/bk. £19.19

HIGH GAIN TV. PRE-AMPLIFIER BAND 1 B.B.C.

Tunable channels 1 to 5. Gain 18 dB. ECC84 valve.

Kit price 32/6 or 55/- with power pack. Details 6d.

BAND III I.T.A.—same price. Tunable channels 7 to 13.

Band I or III. Coils and circuit only. 9/6. Chassis 4/9.

B.B.C.2 Super Booster. UHF Transistor Model ready made 75/-

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2 in. sides. x 4in. 5/6; 8 x 7in. 6/6; 11 x 13in. 6/6; 11 x 7in. 7/6;

3 x 8in. 9/6; 14 x 11in. 12/6; 15 x 14in. 15/-

ALUMINIUM PANELS 18 s.w.g. 12 x 12in. 5/6; 14 x 9in. 4/6; 12 x 8in. 3/6; 10 x 7in. 2/6; 8 x 6in. 2/-; 6 x 4in. 1/6.

ALL PURPOSE TRANSISTOR PRE-AMPLIFIER

Gain 14:1. 250v. or 9v. input. Ready built with Mu Metal

input transformer for Mikes, Pick-Ups, Tuners 15/-

Instructions and circuit supplied. Post 2/6.

THE INSTANT BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER

200/250 v. A.C. Leaflet S.A.E. Post 35/-

2/6.

BAKER 12 in. STANDARD

The Ideal High Fidelity Loudspeaker for high output at home or public address, etc. Built in concentric tweeter cone.

Voice Coil impedance 15 ohms. Max. Power 20 watts. Bass Res. 40/50 cps. Flux 14,000 gauss. Voice Coil diameter 1 1/2 in.

Response 40-14,500 cps. Chassis material Alomax, overall dia. 12in., overall depth 6in.

Price £8 Post Free

CATALOGUE S.A.E.

GROUP MODELS FOR VOCALS, BASS, LEAD AND RHYTHM GUITARS

30-10,000 cps. Voice Coils 15 ohms. Heavy Duty.

'Group 25' 'Group 35' 'Group 50'

12in. 5gns. 12in. 8 1/2 gns. 15in. 18 gns.

25w. 35w. 50w.

LOUDSPEAKERS P.M. 3 OHMS. 2 1/2 in., 3 in., 4 in., 5 in., 7 in. x 4 in., 15/6 each; 8 in., 22/6; 6 1/2 in., 18/6; 10 in., 30/-; 12 in., 37/-; (15 ohms 35/-); 10 in. x 6 in., 30/-; 8 in. x 3 in., 20/-; E.M.I. Double Cone 13 1/2 x 8 in., 3 or 15 ohm models, 45/-; Stentorian 10 in. HF1012. £5.10; 8 in. HF812. £4.10; Crossover 35/-; Horn Tweeters 3-16 Kcs/10, 10 v. 29/6; 20 w. 20 Kcs/99/6 JACK SOCKETS Std. open-circuit 2/6, close circuit 4/6, Chrome Lead Socket 7/6, DIN 3-pin 1/3; Lead 3/6.

Phono Plugs 1/-; Socket 1/1; Banana Plugs 1/-; Sockets 1/-

JACK PLUGS STANDARD. Chrome 3/-; DIN 3-pin 3/6.

WAVE-CHANGE SWITCHES WITH LONG SPINDLES. 2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way, 3/6 each.

1 p. 12-way or 4 p. 2-way, or 4 p. 3-way, 3/6 each.

Wavechange "MAKERS" 1 p. 12-way, 2 p. 6-way, 3 p. 4-way, 4 p. 3-way, 6/-; 2-way. Prices include click spindles, adjustable stops, spaces, etc., 1 water, 10/6; 2 water, 15/-; 3 water, 19/6; 4 water, 24/-; 5 water, 28/6; extra valves 4/6.

TOGGLE SWITCHES. sp. 2/-; sp. 2 d. 3/6; dp. 4/6; dp. 4/6.

DE LUXE TAPE SPLICER. Cuts, trims, joins. 14/6

For making and repairs. With 3 tapes.

4-CHANNEL TRANSISTOR MICROPHONE MIXER.

Four channel highlights and sound effects to recordists. Will mix microphone, records, tape and tuner

with separate controls into single output. 59/6

2-WAY INTERCOM AND BABY SITTER. All transistor. 2-way call buzzer. Desk or wall mounting. Good

Volume. For home, office and shop. With long leads, battery, etc. 59/6

AM TUNER MEDIAN WAVE Three Transistor Superhet. Ready built. Printed circuit. Ferrite aerial. 79/6

Size 5 1/2 x 3 1/2 x 1 1/2 in. Ideal for Tape Recorders.

3-WATT QUALITY AMPLIFIER 4 Transistor Push-pull. Ready built, with volume control. 75/-

NEW Manufacturers' SURPLUS UHF BBC-2 AERIALS BBC-2 Double Gold Ring Set, Top Model. 22/6

BBC-2 Five Element UHF Model 32/6. Outdoor 42/6

RADIO BOOKS ★ (Postage 9d.)

Radio, TV Valves, Diodes, Transistor equivalents. 10/6

High Fidelity Speaker Enclosures and Plans. 10/6

Transistor Superhet Commercial Receivers. 7/6

Mullard Audio Amplifier Manual. 8/6

Radio Valve Guide. Books 1, 2, 3, 4 or 5. each 5/-

Practical Audio Radio Inside Out. 4/6

Transistor Audio Amplifier Manual. 3/6

Shortwave Transistor Receivers. 5/-

Transistor Communication Sets. 6/-

International Radio Stations List. 2/6

Modern Transistor Circuits for Beginners. 7/6

Sub-Minature Transistor Receivers. 5/-

Wireless World Radio Valve Data. 9/6

At a glance Valve equivalents. 6/-

RESISTORS. Preferred values, 10 ohms to 10 meg.

1 w., 1 w. 20% 4d.; 1 1/2 w. 8d.; 2 w. 1/-; 3 w. 10% 6d.

HIGH STABILITY. 1 w. 1 w. 2/- Preferred values.

10 ohms to 10 meg. Ditto 5% 10 ohms to 22 meg. 5d.

5 watt 0.5 to 8.2 ohm resistors {1/9

THE MW COLUMN

FIRSTLY, apologies for those still waiting for details of the loop aerial. Response was overwhelming but I hope to clear the backlog in the near future. Several readers have asked for M.W. station lists. Apart from the well-known World Radio TV Handbook (which, of course, covers *all* broadcasting) an invaluable companion to Dx'ing is the World Medium Wave Guide, obtainable from specialist bookshops or direct from World Publications, Lindorfsalle 1, Hellerup, Denmark, at 16/3d.

Secondly, a few notes for our American readers. Dx in the USA is somewhat different and the fact that US and Canadian stations operate on a regular 10 kc/s spacing (with many stations on most channels) makes for severe interference problems since most of the Dx (outside of the European area) also use 10 kc/s spacing. This is where a loop becomes almost indispensable.

Transatlantic openings seem to start around June, peaking up in August/September. Some to look for include Dakar 764 kc/s, BBC Light 1214, Monte Carlo 1466, Spain on 584, 638 and 683, Agadir 935, French network stations on 1403 and Munich 1196. West Coast readers, of course, have exotic Pacific possibilities like Tahiti, Samoa, Tonga.

Dx conditions in the UK have generally been poor, but with a few brighter patches. North America has been unreliable, often not appearing until the very early hours. South America, however, has been excellent, some of the best being YVQB R.Carupano 940, YVRO R.Aeropuerto 910, YVNZ R.Calendario 1030, YVOZ R.Tiempo 1200, LR1 R.el Mundo 1070, LR5 R.Belgrano 950, Brazilians PRF4 940, PRA3 960, PRE8 980, PRG3 1280, PRB9 1000. Others include HJED 820, PJD2 1295, ZBM1 1235, Martinique 1310.

From Africa, Lagos has been noted on 1088 at 0500, Canakry (Guinea) on 1403 around 2330, and Tanzania on 638 at 0300 sign-on. Middle East has yielded Zahaden 777, Arwaz 1390, Baghdad 760, Kuwait 1345, and the Syrians on 746, 786, 953—all during the evening period.

Asia, after an excellent start late last year has been disappointing. India is still there at times between 0330-0200, but China is now poor, except for the ever-present Urumchi 1525 heard from early afternoon to late night.

By the time you read these notes, Far East opportunities may be lost until September; but last year there was a good late peak in late February-early March. Try late afternoons (around 1600) and between 2100-2330.

We have all been disappointed in the scarcity of West Coast openings, but KOMO 1000 and KING 1090, both Seattle, have been heard at times. The mid-West has also been poor and WCCO Minneapolis 830, WOWO Fort Wayne 1190, WOAI San Antonio, and KMOX St Louis 1120, have been far less frequent than last season.

To end on a note of optimism, March is usually a good month for USA and some may be audible as late as 0800—so there is still hope!

Alistair Woodland

CQ! CQ! CQ! CQ! CQ!

ISSUES WANTED

Sir,—Would any reader be kind enough to supply me with the issues containing the articles on modifications to the PCR receiver.—David Sutton, 83 St. Leonards Road, Leicester.

Sir,—I would be grateful if any reader could supply me with copies of Practical Wireless covering the RAE (lessons 1 to 12).—P. Vlietinck, 34 North Road, Islington, London, N.7.

Sir,—I am interested in building the Ten-Five receiver and require the October and November 1964 issues of Practical Wireless. I would be grateful if any readers could help me.—P. J. N. Davison, 1 Osborne Road, Clifton, Bristol 8.

Sir,—Please can anyone help me with the issue regarding the P.W. 35W Guitar Amplifier. I need the issue of the magazine and the blueprint.—H. Sarsfield, 6 Bellfields Road, London, S.W.9.

Sir,—Would any reader be kind enough to send me a copy of the December 1965 issue of Practical Wireless.—R. Austin, Arunside, Letchworth Lane, Letchworth, Hertfordshire.

Sir,—I would be grateful if any reader would be kind enough to loan me the July 1960 issue of Practical Wireless which contained conversion details of the RAF receiver type R1392.—R. G. Hayward, "Sunnyfields," Lighthouse Road, St. Margaret's Bay, Nr. Dover, Kent.

Sir,—I require the issues of Practical Wireless covering the 19 set Modifications by D. W. Dillon, commencing March 1960. I will pay the full postage on these.—M. B. Meenagh, ZL1ATW, 70 Whitmore Street, Kihikih, New Zealand.

ISSUES FOR DISPOSAL

Sir,—I have some 70 issues of Practical Wireless dating from 1955 to 1965. Most of these are in good condition, but as I have no further use for them due to studies, I am willing to let them go very reasonably. If readers would write to me, I will be glad to send them a list of the copies I have.—D. A. Webb, Londesborough Lodge, Church Road, Kenley, Surrey.

Sir,—I have a complete set of copies of Practical Wireless dating from June 1962 to April 1966 for disposal. If any readers are interested, I would be willing to dispose of these for 1s. per copy to cover postage etc.—M. J. Hall, 4 Bertram Road, Smethwick, Staffordshire.

Sir,—I have for disposal copies of Practical Wireless for May 1964 to September 1966, complete with blueprints. If any readers would like these at a reasonable cost, would they send a stamped addressed envelope to me for details.—S. G. Collard, 55 Mill Hill, Aylesford, Maidstone, Kent.

Sir,—I have the following issues for disposal. If readers care to write to me enclosing a stamped, addressed envelope, I will send them full details. The issues are: Practical Wireless 1960-1966 inclusive and Practical Television 1960-1966 inclusive. These issues all include blueprints, data books etc.—Harry Dodgson, 15 Chestnut Street, Parkinson Lane, Halifax, Yorkshire.

INFORMATION WANTED

... the manual of the C52 Marconi Ground Station.—F. W. Vann, 37 Vale Road, Haringey, London, N.4.

... the circuit, instructions and any other information on the ex-U.S. Army Combination tester, model No. 1183-SC, part of Test Set No. 1-56-C. This unit was made by the Triplett Instrument Co. Ltd.—D. Childs, 1 Dunton Court, Sydenham Hill, London, S.E.23.

... a copy of the Valve Testing book published by Taylor Instruments in 1960. Whatever its condition, I am prepared to pay more than the original cost.—W. H. Dixon, 73 Kimberly Road, Pen-y-lan, Cardiff.

... details of Radio Transmitter marked BC625A Bendix Radio, Bendix Aviation Corp., Baltimore, U.S.A. A second plate underneath the unit reads: Type T5017 Ref. No. 110D/146.—John G. Owen, Llwyn-Fryn, Penrynnydd Road, Llangefni, Anglesey.

... any information, i.e. ratio, connections etc. on transformer with the code X74086 and 980.—A. Bardell, The Mount, Albion Hill, Loughton, Essex.

... the circuit diagrams and/or manual for U.S. Army Rx/Tx type BC-620-A serial number 3499.—K. Meador, 8 Fir Grove, Meling Road, Liverpool, 9.

... the circuit diagram of the BC-624-C receiver and equivalents of the valves 9002 and 9003.—D. Torbell, 9 Pembroke Road, Framlingham, Suffolk.

... operating instructions, original or just written and abridged for the Pye TV Signal Generator ref. 940226-40-70Mc/s in the very heavy case.—Nykola Nyznyk, 54 Eldon Street, Glasgow, C.3.

... any information on converting the "receiver" section of a US Air Force radio altimeter (I believe it is type 455) to cover the 70cm amateur frequency. This particular receiver contains two 9004's—acorn valves and is in an aluminium case measuring 6 x 3½ x 2½in. One 9004 is strapped as a diode and all attempts to discover the i.f. frequency have failed.—D. Bailey, 163 Porters Avenue, Dagenham, Essex.

... a copy of the handbook for the A.M.R. 1132A receiver.—J. D. Morris, 14 Brook Drive, Kempton, Bedford.

... the instruction book for the DST 100 Mk. 2.—W. A. Gardner, 38 Brackley Street, Walsden Worsley, Manchester.

... the service sheet for the Brenell Mk. II tape recorder.—W. Wood, 2 Amberton Gardens, Leeds, 8.

... the layout plans or any other information on a radio called the Miami Minute, made by Concord Electronics in 1962.—A. Giles, 20 Fieldway, Dagenham, Essex.

... instruction manual, circuit diagram etc. of the ex-RAF R1475 Communications Receiver.—S. H. Glenn, Meadfoot, Pembroke Road, Woking, Surrey.

... the circuit diagram of a light-sensitive switch using either an ORP12 or an ORP60 transistor.—N. Lodge, Corner Colt. Armstrong Lane, Brokenhurst, Hants.

... the circuit diagram or information on Lafayette tape recorder model RK-137A serial No. 5884.—R. W. Stephenson, The Bungalow, Winstead Hall Hospital, Patrington, Nr. Hull, E. Yorks.


CORRESPONDENTS WANTED

... anyone using the Bendix RA10DB communications receiver.—Eric J. Symonds, 5 John Street, City Road, Cambridge.

... any beginner to radio or any short wave listener. I am 18 years old.—Christopher Attisogbul, Emil Institute, P.O. Box 3530, Accra, Ghana.

... any boy from 13 to 15 years of age who enjoys building radios and test equipment.—W. Cowell, 8 Quarters Road, Hulse, Portsmouth, Hampshire.

... anyone who has built the P.W. 35 Watt Guitar Amplifier.—T. Embleton, Berners House, Woolverstone Hall, Nr. Ipswich, Suffolk.

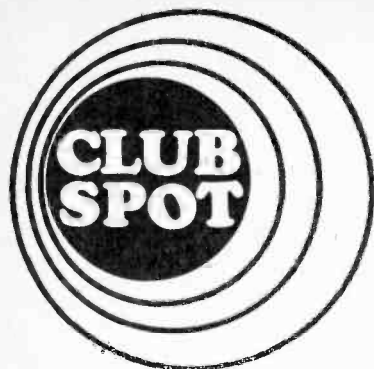

No. 15

SILVERTHORN RADIO CLUB

G3SRA

THE Silverthorn Radio Club was born some fifteen years back when G2HR and s.w.l. R. Cason thought there was a real need in Chingford for a Club, completely independent, and owing no allegiance to other organisations. Initially the membership was small, but regular meetings were held at private houses. Despite many vicissitudes, membership has risen steadily, and for the past few years the Headquarters has been at Friday Hill Community Centre, Chingford, where ample facilities exist for a working station and construction. Apart from a "hard-core" of "old-timers", the Club has attracted a very youthful membership, and contingent upon this a County grant is available when the need arises. The Club is justly proud of the successes scored by the younger element over the years in getting their "tickets". Although the lower age limit is 15, more youthful aspirants are occasionally admitted when it is clear they show promise. This policy has borne fruit. The two youngest licences were on the air at the age of 14, one of whom passed his morse test and R.A.E. when thirteen years old. Another of this age can copy nearly 20 w.p.m., and with other teenagers is studying hard for his R.A.E. under the guiding hand of the Club. The present officers are G2HR (Chairman), G3SGF (Secretary), G3ICY (Treasurer) and G3RJI (co-opted Secretary's Asst.).



Aerial erecting at the annual camp can be hard work, as the prostrate body indicates.

firmed one member's belief that the late Lady Heathcote who occupied the old and rambling country house last century, was indeed roaming around in disembodied disbelief at the twentieth-century desecration of her former residence! The particular member would have done justice to an ITV "natural break". All present affirm he was "whiter than white".

The "high-spot" of the year is the Club's own field event. This is arranged for three or four days over the August Bank Holiday under canvas when operation takes place on topband and 2m. The site, on private land, is one of the most superb spots in Epping Forest, some 300ft. a.s.l., with a vast panoramic view across Hertfordshire and beyond. One year 500ft. of wire was strung out for 160m. It seemed the entire British Isles came back to the "CQ's". The social side of this annual event is an enormous boost to the Club, as although operation is the primary object, not being a contest, full benefit is taken of other activities inseparable from a free-and-easy camping mini-holiday.

At the present time the Club is in the ascendant, as a number of new members have been enrolled. H.Q. is surrounded by a large amount of ground which removes the headache of sizeable aerials. The fact that the topband transmitter has been heard off Newfoundland with a bare ten watts adds force to the adage "spend as much money outside the shack as inside".

The Club meets every Friday except the first in the month. Any aspiring member is always welcome to visit, or alternatively telephone the Chairman (529-2932) or the Secretary (SIL 8550).



Affiliated Societies' Contest. On key G3UMO, right G3RKJ. Standing (left to right) G3RJI, s.w.l.'s Bean and Routledge, and G2HR.

Contests are always a popular feature, and when an all-night session is entailed and members "kip" on the premises, youthful ebullience often emerges. The tape-recording played in the "wee sma' hours" comprising ghostly groans on one occasion, con-

LOOK!

PRACTICAL!
VISUAL!
EXCITING!




a new 4-way method of mastering

ELECTRONICS

by doing — and — seeing . . .

1 ▶ OWN and HANDLE a

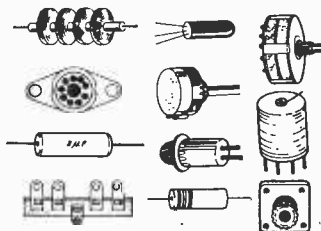complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**




2 ▶ BUILD and USE

a modern and professional **CATHODE RAY OSCILLOSCOPE**



3 ▶ READ and DRAW and

UNDERSTAND CIRCUIT DIAGRAMS

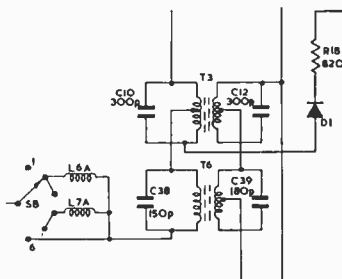

4 ▶ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .

- | | | |
|--------------------------|--------------------------|------------------------|
| ● VALVE EXPERIMENTS | ● PHOTO ELECTRIC CIRCUIT | ● A.C. EXPERIMENTS |
| ● TRANSISTOR EXPERIMENTS | ● COMPUTER CIRCUIT | ● D.C. EXPERIMENTS |
| ● AMPLIFIERS | ● BASIC RADIO RECEIVER | ● SIMPLE COUNTER |
| ● OSCILLATORS | ● ELECTRONIC SWITCH | ● TIME DELAY CIRCUIT |
| ● SIGNAL TRACER | ● SIMPLE TRANSMITTER | ● SERVICING PROCEDURES |

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: *we do not employ representatives*

NAME **BLOCK CAPS**

ADDRESS **PLEASE PW4**

Fully guaranteed Individually packed VALVES



The valve with
a guarantee

AC/H4 4/6	E88CC 12/-	EF95 5/-
AC/H4 6/-	E90CC 10/-	EF183 6/-
AC/PEN 5/-	E1148 2/6	EF184 6/-
AL60 5/-	E1266 5/6	EH90 7/6
AR3 3/-	E1416 3/6	EHT1 300/-
ARF12 2/6	E1524 2/6	EL32 3/6
AR21 3/6	EAS0 1/-	EL34 10/-
AR5 5/-	E173 7/-	EL36 5/-
ARTP1 6/-	EACB80 5/6	EL38 17/6
ATP4 2/3	EAC91 3/6	EL41 8/-
ATP7 5/6	EAP42 8/-	EL42 8/-
AU7 55/-	EB34 1/6	EL50 8/-
AZ81 9/-	EB91 3/-	EL81 8/-
B6H 15/-	EB223 6/-	EL84 4/3
BD78 40/-	EB441 8/6	EL85 7/6
RL63 10/-	EB821 5/6	EL91 4/6
B84 8/-	EBF80 6/6	EL95 5/-
B85 20/-	EBF83 7/6	EL360 20/-
B884 37/6	EBF89 6/6	EM80 6/-
BT134 16/-	EBL31 20/-	EM81 7/-
BT19 25/-	EC52 4/6	EM84 6/3
BT35 25/-	EC83 12/6	EN31 10/-
BT45 150/-	EC70 4/-	ESU74 20/-
BT83 35/-	EC90 2/-	ESU208 6/-
CC3L 2/-	EC91 3/-	EY51 5/6
CF23 10/6	EC81 4/6	EY46 6/6
CV71 3/-	EC82 5/6	EY91 3/-
CV77 5/-	EC83 6/6	EZ40 6/6
CV102 1/-	EC84 5/6	EZ41 6/6
CV103 4/-	EC85 6/6	EZ40 5/6
CV4004 7/-	EC88 9/-	EZ81 4/6
CV4014 3/-	EC91 4/-	F6607 5/-
CV4015 7/-	EC91 9/6	F6608 5/-
CV4025 10/-	EC90 9/6	F6603 4/-
CV4049 6/-	EC92 7/-	FW4/500 6/6
CY31 6/6	EC82 9/-	FW4/800 8/6
D1 1/6	EC81 5/-	G1236/129/-
D41 6/-	EC83 7/6	G1/370K
D41 6/-	EC84 6/6	GL30 10/-
D77 3/3	EC82 6/3	G50/23 5/-
D824 12/6	EC83 10/3	G180/2M15/-
DAP6 6/-	EC86 9/-	G134 45/-
DH1 4/-	EF36 3/4	GTE175M
DET5 8/-	EF74 7/-	PT74 7/-
DET20 2/-	EF40 3/-	G150 25/-
DET25 15/-	EF50 2/6	G232 10/-
DET3 5/-	EF52 6/-	G234 10/-
EF91 3/-	EF53 4/6	HK54 22/6
EF92 3/-	EF54 2/6	H12K 2/6
EF96 9/-	EF71 7/6	H123 6/-
DH43 5/-	EF72 5/-	H123DD 5/-
DK92 3/-	EF73 5/-	H141 4/-
DK96 6/6	EF74 4/-	HVR2 9/-
DL02 4/-	EF76 5/-	K3A 90/-
DL23 4/-	EF81 6/-	K78C 22/-
DL54 5/6	EF85 4/6	K732 8/-
DL96 7/-	EF86 6/6	K744 5/6
DL810 8/-	EF89 5/-	K733 4/-
DY86 7/6	EF91 3/6	K766 16/-
ES0F 25/-	EF92 2/-	K767 25/-

KT76 8/8	Q895/10 5/6	UCH42 8/-	1LA6 6/-	5X4G 8/6	6F5GT 5/9	8D2 2/6
KT88 22/-	Q8150/15	UCH81 6/-	1LA6 7/-	5Y3GT 5/-	6P6G 4/-	9D2 3/-
KTW61 4/6	Q81202 8/-	UCH82 8/-	1LH4 4/-	6Y3WGT 6/-	6P7 6/-	9D6 2/-
KTZ41 6/-	QV04/7 10/-	UCH83 9/-	1N21B 4/-	5Z4G 6/6	6P8G 6/6	10F9 9/-
KTZ63 5/-	R3 8/-	UF89 6/-	1N70 4/-	6AB6 4/-	6F12 4/-	12A8 2/6
ML100 5/-	RG1/240A	UL41 7/6	1R4 5/-	6AC7 3/-	6F14 5/-	10P14 15/-
ML141 12/-	25/-	UL84 5/6	1R5 3/6	6AG5 2/6	6F32 4/-	12A7 5/-
ML161 7/-	RG4/1250	UL5 7/6	1R4 5/-	6AG7 6/-	6F33 20/-	12AT7 4/-
ML14 60/-	60/-	UL19 8/-	2A3 3/6	6AH6 10/-	6F34 5/-	12AV6 6/-
ML16L010/		UY21 7/6	2C26 3/-	6AJ7 2/-	6H6M 1/6	12AU7 5/-
ML16 6/-		UY41 6/6	2A3 3/6	6AK5 5/-	6J4WA 10/-	12ATTWA 5/-
N78 15/-		UY85 5/-	2C26 3/-	6AK7 5/-	6J5 8/-	12A7 5/6
NE17 7/6		UY120 4/-	2C26A 3/-	6AK8 5/6	6J5G 2/6	12AX7 6/-
OB2 5/6		UY20 2/6	2C34 7/-	6AL5 2/6	6J6 3/6	12AX7 10/-
OB3 6/-		VP124 20/-	2C34 7/-	6AL5W 2/6	6J6W 2/6	12B6 7/6
OC3 5/-		VP23 3/-	2C45 22/6	6AM5 2/6	6J7 5/-	12B6 7/6
OC3 5/-		VP133 9/-	2C49 12/-	6AM6 4/-	6J7M 8/-	12B7 7/6
OD3 5/-		VR99 8/-	2D21 5/-	6AQ5 7/-	6K4GT 5/6	12C8 3/6
OZ4A 5/-		VR103/305/-	2X2 3/-	6AQ5W 9/-	6K7 2/-	12E1 17/6
PC86 9/6		VR150/305/-	2X2 3/-	6AS8 4/-	6K8G 3/6	12F4 7/6
PC86 9/6		VU34 4/-	3A4 4/-	6AS8W 9/-	6K8G 3/6	12F4 7/6
PC86 9/6		VU39 6/-	3A/108A20/-	6AS7G 15/-	6K8GT 8/3	12F4 7/6
PC86 9/6		VX3208 5/-	3A146J 55/-	6AT6 4/-	6K8M 6/6	12K7GT 2/6

TRANSISTORS

OC16 20/-	OC81D 5/-	OC201 12/6	XC141 10/-
OC22 23/-	OC81M 10/-	OC202 15/-	XC142 15/-
OC23 9/6	OC82 10/-	OC203 12/6	XC145 20/-
OC35 12/6	OC82DM 5/-	OC204 17/6	XC156 22/6
OC44 6/-	OC83 5/-	OC206 22/6	2N247 9/6
OC45 5/-	OC83B 5/-	AAZ12 7/6	2N242 7/6
OC71 4/6	OC122 5/-	AC128 7/6	2N502 47/6
OC72 5/-	OC170 6/-	BCZ11 7/6	2N585 10/6
OC73 9/6	OC170 6/-	BY38 7/6	2N1091 28/-
OC81 5/-	OC200 10/6	BY38 7/6	2N1091 28/-
TP22 5/-	VX3252 4/-	3A1/167M	6AV6 6/-
TP25 15/-	VX3154 4/-	3B7 25/-	6A3 17/-
TT1 5/-	VX19 24/-	3BT 25/-	6B4G 17/-
TT15 35/-	W21 5/-	3B24 9/-	6B7 6/-
TT15 35/-	W18 10/6	3D6 4/-	6B8G 2/6
TT2520 4/-	W19 8/-	3E29 50/-	6BA6 5/-
TZ20 16/-	X69 7/6	3Q4 6/-	6BA7 5/-
U81 18/-	X76M 7/6	3QGT 7/6	6B6 6/-
U124 8/-	X81M 18/-	384 5/-	6B7 7/6
U17 5/-	X118 8/-	3V4 5/6	6B7 7/6
U18 6/-	X145 8/-		6BQ7A 8/-
U25 13/-	Y3 5/-	4C27 35/-	6B7 7/6
U26 13/-	Y6 4/-	4D1 4/-	6B7 7/6
U27 8/-	Y6 8/-	5A173G 5/-	6C4 2/-
U52 4/6	Z8001 20/-	5A174G 5/-	6C5G 2/6
U91 11/6	Z801 10/-	5B251M 35/-	6C5GT 6/-
U91 11/6	Z801 10/-	5B252M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B253M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B254M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B255M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B256M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B257M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B258M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B259M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B260M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B261M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B262M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B263M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B264M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B265M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B266M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B267M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B268M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B269M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B270M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B271M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B272M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B273M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B274M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B275M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B276M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B277M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B278M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B279M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B280M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B281M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B282M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B283M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B284M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B285M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B286M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B287M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B288M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B289M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B290M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B291M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B292M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B293M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B294M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B295M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B296M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B297M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B298M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B299M 35/-	6C6 4/-
U91 11/6	Z801 10/-	5B300M 35/-	6C6 4/-

MANY OTHERS IN STOCK include: Cathode Ray Tubes and Special Valves. U.K. Orders below £1 P. & P. 1/-; over £1, 2/-; over £3, P. & P. free C.O.D. 3/6 extra. Overseas Postage extra at cost.

H.R.O. SENIOR TUBE MODEL TYPE M. 50 kc/s. 30 Mc/s with "S" meter and crystal filter in excellent fully checked and tested condition together with set of 8 general coverage coils and mains P.S.U. 110-220 v. £26.10.0. Carriage and packing 30/-.

RACK MODEL also available at the same price.

"S" Meter for H.R.O. Receivers. Brand new £2.10.0. Carriage paid U.K.

CRYSTALS for H.R.O. in Original National Union Housing. 25/- P. & P. 2/-.

VARIOMETER for No. 19 sets, 17/6. P. & P. 3/-.

INSET MICROPHONE for telephone handset 2/6. P. & P. 2/-.

2KW ULTRASONIC GENERATOR together with power supply unit for 200-250 v. A.C. Complete two chassis with interconnecting cables. Frequency 37 to 43 kc/s adjusted by fine control. Peak output 12 kw, average output 500 w. Completely new valves and manual. £65, carriage paid U.K.

A.R.88D. RECEIVERS. Fully reconditioned. £55. Rebuilt model £85. Carriage paid U.K.

SPARES for A.R.88D. RECEIVERS. Ask for your needs from our huge selection.

CR 150/6 RECEIVER. 2-32mc/s. in 4 bands. Double conversion. Miniature valves. 8 positions 1st oscillator selector, variable band with 100c-13kc built in calibrator, 4kc bandspread, valve metering and signal indicator. Noise limiter, £40. Original P.S.U. £7.10.0. Carriage 20/-.

BC 221 FREQUENCY METERS. 125-20,000 kc/s. Accuracy 0.01 %. Complete with individual calibration book. Fully tested in as new condition. With headphones. £35. Carriage 10/-.

MAINS P.S.U. for the above, specially built to fit battery compartment, £11.10.0. Carriage 5/-.

MARCONI SIGNAL GENERATOR TYPE TF144G 85 kc/s-25 Mc/s. Excellent laboratory tested condition with all necessary accessories. £45. P. & P. 15/-.

BOONTON STANDARD SIGNAL GENERATOR MODEL 80. Frequency 2-400 Mc/s in six ranges. A.M., 400 and 1,000 c/s. and external modulation. Provision for pulse modulation. Piston type attenuator, 0.1µV-100mV. Separate meter for modulation level and carrier level. Precision flywheeling. 117v. A.C. input. £95. Carriage 30/-.

SIGNAL GENERATOR TYPE TS 418. Signal frequency 400-1,000 Mc/s, direct calibration. Pulse rate 40-400 c (x 1 or x 10), pulse delay variable, less than 3µsec to more than 300µsec. Pulse width variable less than 1µsec. to more than 10µsec. Polarity—internal or external sources, positive or negative pulses, AM and CW. Output attenuator 0.2µV to 200mV, continuously variable. In fully tested condition. £150. Carriage paid.

C.R.100 RECEIVER. 60 kc/s-420 kc/s. 500 kc/s.-30 Mc/s. In 6 bands, 2 HF stages, 3 IF stages, AVC on both phone and CW. Excellent condition, correctly tuned and guaranteed. £31. Carriage 30/-.

TEST SET TS 125/AP 5 band RF power meter. Compact battery operated, UHF wattmeter used in checking the relative power output or Radar Tx. Can also be employed in measuring antenna radiation patterns and standing wave ratios. Freq. 2,400-3,335 Mc/s. Consists of a temperature compensated Thermistor Bridge, a multi-wattmeter and a horn type pick-up antenna. £30. Carriage 10/-.

32/44FT. AERIALS each consisting of ten 3ft., 1/4in. dia. tubular screw-in sections. 14ft. (7 section) whip aerial with adaptor to fit the 1/4in. rod, insulated base, stay plate and stay assemblies, pegs, reamer, hammer, etc. Absolutely brand new and complete ready to erect, in canvas bag, £3.9.6. P. & P. 10/6.

P. C. RADIO LTD.
170 GOLDHAWK RD., W.12
SHEPHERD'S Bush 4946

TELEPHONE HANDSET. Standard G.P.D. type; new 12/- P. & P. 2/-.

AVO ELECTRONIC MULTIMETER TYPE CT 38. AC mains operated 105-125v. & 195-255v. 45-66 c/s. 77 measurement ranges covering DC and AC current, voltage, resistance and power output. Accuracy on DC ranges ±2% FSD. Accuracy on AC ranges ±3% full FSD at 50 c/s. Ranges: DC volts 250mV-10,000V (10M ohms-110M ohms input resistance) DC current 10µA-25A. Ohms: 0-1,000M ohms. AC volts 100mV-250V (with RF measuring head to 250Mc/s) AC current-10µA-25A. Power output-50W-5W. Automatic movement protection against overload. Meter reverse, balanced measurement facilities. Complete with all accessories. Laboratory tested condition. £42.10.0. Carriage 15/-.

MICOVAC VALVEVOLTMETER BY ELECTRONIC INSTRUMENTS LTD. AC mains or battery operated. AC and DC voltage from 2-4,200v. AC voltages from 20 c/s to 200 Mc/s. Ohms from 0-10M ohms. Meter reverse, balanced measurement facilities. £19. P. & P. 10/-.

HAMMARLUND SP 600-JX RECEIVER. Dual conversion superhet. 540 kc/s to 54 Mc/s in 6 bands. Stability 0.01% or better. In as new, laboratory tested condition. Price on application.

SEMI-AUTOMATIC BATTERY CHARGER "Baby Estroon". Initial charging rate 3-5 amps DC automatically reducing to 1-5 or lower (depending on specific gravity of battery acid). As the battery receives the charge indication lights indicate visually the high current or when incorrectly connected. Meter incorporated. For 6 or 12v batteries. Mains voltage 200/240v A.C. Few left to clear at £2. P. & P. 5/-.

TELETYPEWRITER TEST SET TS 659/UG £15. Carriage 10/-.

TEST SET CALIBRATION TS 250A. Necessary for repairs and calibration of altimeters £12.10.0. P. & P. 10/-.

Open 9-5.30 p.m. except Thursday 9-1 p.m.

PERSONAL CALLERS WELCOME

repairing radio sets

—continued from page 927

respond when the oscillator signal is tuned in. It can then easily be identified. Remember that the oscillator frequency is different by the i.f. from that shown on the tuning scale.

LOCAL OSCILLATOR FAULTS

Typical causes of oscillator failure in Fig. 1a are open-circuit R4, open-circuit C9 and/or C10, oscillator switch (S3) trouble and oscillator coil open-circuit or leakage. Old sets which have been used in damp environment or stored for any length of time often develop oscillator coil leakage—coil measurement revealing low Q-factor.

Switch or coil troubles generally affect one waveband, while other faults affect all bands. Remember, too, that shorting or leaky trimmers may affect only one band.

BACKGROUND CRACKLES

An oscillator component failing can cause background fizzles and crackles which appear mainly when a station is tuned. A quick check to prove whether the oscillator section is responsible simply amounts to disconnecting the stage h.t. supply or muting the oscillator in some other way (this would be necessary in Fig. 2b to avoid killing the mixer action). Here it would be best to short out L3, while in Fig. 2a disconnecting R4 from the h.t. line would be the best bet.

The set will not receive, of course, but the volume should be fully advanced and lack of background noise now indicates that the oscillator must have been responsible. The high h.f. voltages produced by the oscillator highlight faulty associated parts by causing background noises or, more severe, complete failure. If the background noises persist with the oscillator muted, the trouble lies elsewhere in the set.

If the oscillator is producing noises, each smaller component is best tested in turn by replacement, after first making sure that the frequency-changer (or oscillating mixer) valve is noise-free. It is unlikely that the oscillator coil could be so checked, but if the noise remains after the other parts have been cleared, including wavechange switch sections, trimmers and padders, the coil or transformer should be investigated.

If the oscillator signal is monitored on a second set, as previously explained, any disturbance or crackle on its signal will be heard in the second set. This is a good test for oscillator signal purity.

OSCILLATOR INTERMITTENCY

Intermittent oscillator action can result from a low emission frequency-changer, and the l.w. seems first to suffer. The set suddenly cutting off is the symptom, to be restored possibly by switching the set off and then on again quickly or otherwise electrically disturbing the circuits. Tuning quickly from one end to the other of the band may bring the oscillator back on.

Battery and mains/battery portables are so affected by a low emission DK-series valve or by low l.t. voltage. A worn metal h.t. rectifier (on mains) is a frequent cause as this provides the filament current as well as h.t., the former through a ballast resistor. If the DK— filament voltage goes below about 1.2V oscillation ceases, but the actual voltage depends on the emission of the valve.

During periods of electricity power cuts, oscillators of mains/battery sets often fail, restoring when the voltage rises to normal or to that selected by the mains input adjustment. To obtain consistent operation it is sometimes necessary to replace both the valve and the h.t. rectifier.

Low filament voltage can be caused by unbalance of the filament chain, the filaments being series-connected in the *mains* position. The ballast (series dropper) resistor can increase in value and there can be changes in value of the small resistors shunting the filaments of the various valves. These are used to bypass the anode and screen currents to avoid unbalance of filament chain. Another factor often overlooked is change in filament characteristics of one or more of the valves. This means that low frequency-changer filament voltage could be due to a filament change of other valves on mains.

Front-end troubles are mostly round the oscillator circuits, assuming correct alignment. However, low sensitivity can result from aerial and r.f. tuned circuit faults. After a severe thunderstorm, for instance, local stations may be weak, yet at almost normal volume but with whistles, with the aerial connected to the first grid of the mixer section instead of the aerial socket. This is a sure indication of failed aerial coupling winding (L2, L4 and L6 in Fig. 2a).

POOR SENSITIVITY

A fractured ferrite aerial rod in a portable will reduce sensitivity. As a temporary measure use a ceramic cement for repair, making sure fractured ends are pushed *tight* together. This aerial is tuned for maximum sensitivity by sliding the coils along the rod, the inductance of the coils being maximum at centre. This is how the aerial circuit is tuned or trimmed in this type of set.

When aligning, direct connection should never be made to aerial windings, but a very loose coupling to the signal generator should be employed. Wind about 20 turns of wire round a piece of ferrite rod, connect this across the signal generator output and orientate the assembly for signal pickup on the portable under test. Then adjust the aerial tuning.

Fig. 4 shows the front-end of a portable set using a ferrite rod. S1A selects either L1 or L2 for M.W. and L.W., with VC1 the aerial tuning gang section. Notice that the aerial windings, in fact, represent the tuned circuits. The aerial is thus also the tuned front end and it cannot be removed. The other parts will easily be recognised from the previous descriptions of Fig. 2a circuits.

So far nothing has been said about the d.c. conditions of the valves. This is because the signal circuits give most trouble. D.C.-wise it is just a matter of checking h.t. voltage on the anodes and screen grid of the frequency-changer and l.t. voltage across the heater (or filament).


The conductivity of a valve can be checked by

If r.f. stage is fitted; the testing procedures are similar. This stage and most mixers are biased from the a.g.c. line for automatic control of gain (to be dealt with in a subsequent article), the bias being taken to the control grid via a coil winding and series feed resistor, as in Fig. 2a.

At medium-frequencies, worn or dirty wave-change switch sections disturb oscillator stability and

—continued from page 907

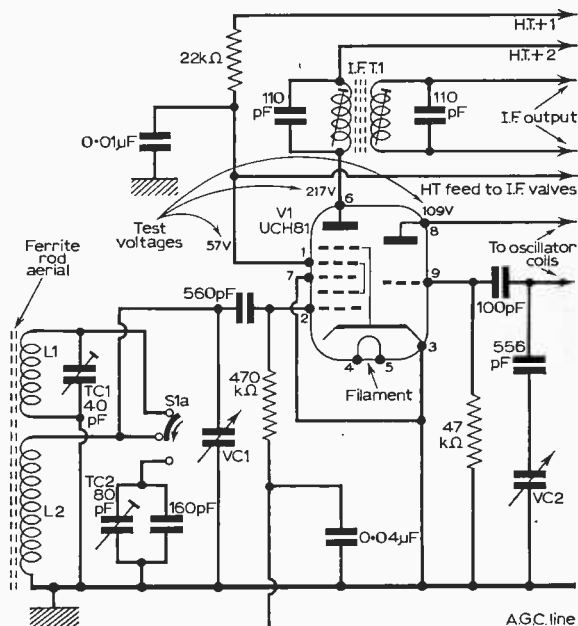A final note on construction is worth while. I use Veroboard, but I prefer not to use it in the conventional manner which is wasteful and clumsy. I prefer to mount most components with their axes at right angles to the board, as in Fig. 6, and do the construction straight off the circuit diagram. ■



Always make sure that the front-end is free from grease and dust accumulations. Keep valve pins clean and treat all switched and plugged contacts with Electrolube or similar cleaner after any service operation.

CONTINUED NEXT MONTH

★ components list

Resistors:		Capacitors:
R1 22Ω	} $\frac{1}{8}$ watt	C1 100μF 12V electrolytic
R2 6.8kΩ		C2 3-30pF trimmer
R3 220kΩ		C3 100μF 12V electrolytic
R4a 220Ω		C4 100μF 12V electrolytic
R4b 680Ω		C5 100μF 12V electrolytic
R4c 3.3kΩ		
R5 1kΩ		
R6 10kΩ		
R7 1kΩ		Transistors:
R8 100kΩ		Almost any type, see text

One pole three way yaxley—S1. Single pole single throw switch—S2. One 9 volt battery type PP3 or similar. Piece of Veroboard 9 holes x 15 holes, see Fig. 6.

NEW BARGAINS

Moving coil meter, 2 1/2 in. flush mounting 5-0-5 M.A. centre zero, 25/- each.

Moving coil meter, 2 1/2 in. flush mounting 250-0-250 micro amp centre zero, 25/- each.

50 ohm 50 watt wire wound pot-meter 8/6 each.

20 K wire wound pot-meter 20 watt type made by Colvern complete with control knob 10/- each.

1 meg miniature pot-meter Morganite standard 1/2 in. spindle 1/- each, 9/- per dozen.

1 meg miniature pot-meter Morganite pre-set screwdriver control, 8d. each, 8/- per dozen.

Pre-set 100 K by Welwyn with intricate bakelite knob, 1/- each, 9/- per dozen.

100 K pot-meter miniature type with double pole switch and standard 1/2 in. spindle, by Morganite 2/- each, 18/- per dozen.

25 K pot-meter standard size with double pole switch by Egan with full length 1/2 in. spindle 3/- each, 36/- per dozen.

Blanketostat glass enclosed, normally closed circuit, will open should blanket overheat, 4/6 each.

Thermal Relay, Can be used to delay the supply of HT while heaters warm up, or will enable 15 amp loads to be controlled by miniature switches or relays. Regular list price over £2, price 7/6 each.

Siemens high speed relay, Twin 1000 ohm coils. Platinum points changeover contacts. Ex equipment 8/6 each.

Electrolytic condenser 500 MF 50v. working, 5/- each, 48/- per dozen.

Waterproof heating element, 26 yards length, 70 watt, self regulating temperature control, 10/- post free.

Footswitch, Two snap-action switches in metal box with flex lead. Ideal to control tape-recorder, dark room lamp, etc. 18/6 plus 2/6 postage and insurance.

Toggle Switch Bargain, 10 amp 250 volt normal one hole fitting, 2/6 each or 30/- per dozen.

Electric Lock, 24 volt coil, but rewindable to other voltages, 4/6 each.

Compression Trimmers, Twin 100PF, 1/- each, 9/- per dozen.

Miniature Relay, American make, 630 ohm coil 20/30 volt operation, 2 pole changeover, 3/- each, 30/- per dozen.

Precision Wheatstone Bridge, Opportunity to build cheaply. 100K wire wound pot, 15 watt rating only 5/-.

Sheet Paxolin, Ideal for transistor projects, 12 panels each 5 x 8 in. 5/-.

3in. PM Loudspeakers, 3 ohm 12/6, 80 ohm 18/6.

Transistor Ferrite Slab Aerial with medium and long wave coils 7/6 each.

Slide Switch, Sub miniature double pole changeover 2/- each, 18/- per dozen.

Magnalips (Selsyn) American made transmitter and receiver 27/6 each. Post 4/6 for any one or the pair.

SEMI-CONDUCTOR BARGAINS

Type No.	Price	Type No.	Price	Type No.	Price
2N1727	15/-	MA7101	8/6	OC71	3/6
2N1728	10/-	MA7130	7/6	OC72	5/-
2N1742	25/-	MA7121	5/6	OC75	6/-
2N1747	25/-	OA5	5/-	OC76	5/-
2N1748	10/-	OA10	6/-	OC77	7/-
AC107	9/-	OA47	2/-	OC78	5/-
AC127	9/-	OA70	2/-	OC78D	5/-
AC171	8/6	OA79	2/6	OC81	5/-
AC18	6/6	OA81	2/6	OC81D	5/-
AC19	6/6	OA85	2/6	OC82	5/-
AC120	5/6	OA90	2/6	OC83	5/-
AC121	6/-	OA91	2/6	OC84	6/-
AC123	4/6	OA200	3/6	OC139	8/6
AF114	7/-	OA202	4/6	OC140	12/6
AF115	6/6	OC22	10/-	OC170	5/-
AF116	7/-	OC23	17/6	OC171	6/-
AF117	5/-	OC24	15/-	OC200	9/-
AF118	10/-	OC26	7/6	OC201	12/6
AF139	12/6	OC28	15/-	OC202	13/6
AF186	17/6	OC29	17/6	OC203	12/6
AF212	15/-	OC35	12/6	OC271	15/-
AS221	15/-	OC36	15/-	OP12	8/6
BC107	14/6	OC42	6/6	ORP60	5/-
BY100	4/6	OC44	4/-	SB078	8/6
BY213	7/6	OC45	3/6	SB305	8/6
MA7100	7/6	OC70	4/-	SB251	10/-

S.C.R.s (THYRISTORS)

100 v. 1 amp, 6/6, 3 amp, 7/6, 12-amp, 15/-, 400 v. 1 amp, 15/-, 3 amp, 17/6, 5 amp, 22/6, 25 amp, 23, 50 v. 1 amp, 6/6, 3 amp, 7/6, 10 amp, 10/-, 25 amp, 30/-.

SILICON RECTIFIERS

Tested and guaranteed

750 mA	100v. 1/8 3A 100v. 3/6 10 A 100v. 9/6
	200v. 1/6 200v. 5/- 200v. 12/6
	300v. 3/6 400v. 7/6 400v. 14/6
	600v. 9/6

1 Amp	100v. 3/-
	200v. 4/-
	400v. 6/-

Sub miniature glass enclosed—only approx. 1/2 in. long wire ended.

750mA 50v. 1/8 100v. 2/6

200v. 4/6 400v. 6/6

FLUORESCENT LIGHT KITS

Comprising choke, lampholders, starter and two chrome tube clips 20 watt 19/6. 40 watt 11/6. 60 watt 14/6. 80 watt 17/6. 65 watt 18/6. All 4/6 P. & P.

MINIATURE WAFER SWITCHES

4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole, 6 way—1 pole, 12 way. All at 3/6 each. 36/- dozen, your assortment.

Where postage is not definitely stated as an extra then orders over £3 are post free. Below £3 add 2/6.

HEAT AND LIGHT UNIT

Bring luxury to your bathroom—have comforting heat where you now only have light—all the parts to build a full size (16in. diameter) model are now available—you will build it in an hour—12in. 750 watt circular silica glass enclosed element—opal bowl for up to 100 watt lamp—non-rust spin reflector—white enamelled base heat shield—pull switch magnificent unit as sold normally at £4.5.0 only 42/6 plus 7/6 carr. and insurance.

NIM COMPUTER

This computer will play games and do simple tricks and will provide endless amusement as well as education into computerisation. Kit comprises all the components, the printed front panel and full instructions. The box is not included but this can be made very simply from plywood. Price £4.17.6, plus 3/6 post and insurance.


SUPERTONE G.C.V.

Saves you work—It's partly built Like its predecessors this latest Companion has full f performance—such as only a good wooden cabinet and biflux speaker can give, and due to its being partly built you will have it going in an evening. Note these features:

- All Mullard Transistors including 3 x AF17.
- Two-tone Cabinet, size 11 x 8 x 3in.
- All circuit requirements—Push-button output—A.V.C. and feed back, etc.
- Printed circuit board all wired up connections, e.g. to Volume control—W.C. Switch and Tuning Condenser.
- Pre-aligned IF stages complete with full instructions. Price only £3.19.6 plus 6/6 post and insurance.

THIS MONTH'S SNIP

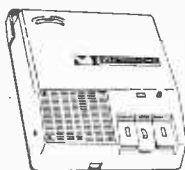THE VECTRONOME CAPSTAN DRIVEN TAPE RECORDER



batteries £9.19.6 (rather less than 1/3 original price). Postage and insurance 7/6. Unused and in perfect working order.

F.M. TUNER

of exceptional quality giving really fantastic results with virtually no noise. Suitable for mains or battery operation. 6 transistors—three IF stages—double tuned discriminator. Complete, new, and built up all ready to work on chassis. Size 3in. x 4in. x 2in. with tuning scale and slow motion drive. A £12.12.6 tuner for only £8.10.0.

FINE RECORD PLAYERS ARE GARRARDS

and because they have been making record players for so long, GARRARD are your best choice—big range always in stock, 7/6 for post and ins.

2000		£6 9 6	LAB80		£25 0 6
AT60		£7 10 6	SRP12		£3 0 0
AT90		£11 11 0			
SP25		£10 9 0			

3M SCOTCH TAPE

brand new, unused and guaranteed perfect and not second in any way—a connoisseur's tape on normal spools and in normal boxes.

Standard Play 5in.		400ft. 9/-	Long play 5in.		900ft. 11/6
5in.		900ft. 11/6	5in.		1,200ft. 16/-
7in.		1,200ft. 16/-	7in.		1,800ft. 23/-

£3 post free otherwise add 2/- post and ins.

NEON MAINS TESTER

Good length leads 2/6.

MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v. 9v. 12 volts for up to 500 mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP5, PP7, PP9, and others. Kit comprises: mains transformer, rectifier, smoothing and load resistor, 5,000 and 500 mfd. condensers, Zener diode and instructions. Real snip at only 14/6, plus 3/6 postage.

HI-FI SPEAKER BARGAIN

12in. High fidelity loudspeaker. High flux permanent magnet type with either 3 or 15 ohm speech coil. Will handle up to 10 watts. Brand new by famous maker. Price 29/6 with built-in tweeter 35/- plus 3/6 post and insurance.

TUBULAR HEATERS

New and unused made by G.E.C. rated at 60 watts per ft.—these are ideal in airing cupboards, bedrooms, offices, stores, greenhouses, etc. Curtains or papers can touch them without fear of scorching or fire. Supplied complete with fixing brackets and available in the following sizes. Prices which are about 1/2 of list price includes carriage by B.R.S. 8ft. 30/-, 10ft. 36/-, 12ft. 42/-.

Also in twin assemblies (one pipe above the other) 4ft. 40/-, 5ft. 46/-, 6ft. 52/-.

750mW TRANSISTOR AMPLIFIER

4 transistors including two in push-pull input for crystal or magnetic microphone or pick-up—feet back loops—activity 5 m/v.

Price 19/6

Post and insurance 2/6. Speakers 3in. 12/6; 5in. 13/6; 6 x 4 in. 14/6.

PHOTO ELECTRIC KIT

All parts to make light operated switch/burglar alarm/counter, etc. Kit comprises printed circuit, Laminated Boards and chemicals, Latching relay, Infra-red sensitive Photocell and Hood, 2 Transistors, cond., Terminal block, Plastic case. Essential d.v.ics including auto. car parking light, modulated light alarm. Simple invisible ray switch—counter—stray light alarm—warning tone electronic alarm—projector lamp stabiliser, etc., etc. Only 39/6 plus 2/- post. and insurance.

2 1/2 kW FAN HEATER

3 heat positions to suit changes in weather: 1kW, 1 1/2kW and 2 1/2kW; also blows cold for summer, has thermostatic safety cut out "Proper" price £5.17.6. Yours for only £3.15.0. Plus 7/6 post and insurance.

MOVING COIL METER BARGAIN

Panel meters are always being needed and they are jolly smart when you have to buy them in a hurry—so you should take advantage of this offer: 2in. moving coil flush mounting meters only 5/6. These are actually R.F. meters and cost about £3 each but if you don't want them for R.F. then all you have to do is to remove the thermocouple and you will have a 2-3 m.A. meter which you can make into almost anything by adding shunts or series resistor. These are ex-government, of course.

PP3 Eliminator—play your pocket radio from the mains! Save £'s. Complete component kit comprises 4 rectifiers—mains dropper resistances, smoothing condenser and instructions. Only 6/6 + 1/- post.

Be first this year SEED AND PLANT RAISING

Soil heating wire and transformer. Suitable for standard size garden frames, plus 3/6 post and ins. 19/6

Wall Mounting Thermostat


By Batchwell, intended for use to control tubular or any type of space heaters indoors or in a greenhouse—adjustable over 40/80 complete with mounting screws, 28/6, plus post 2/6 (normal price is at least twice this).

ELECTRONICS (CROYDON) LIMITED

(Dept. P. W.) 102/3 TAMWORTH RD., CROYDON, SURREY (Opp. W. Croydon Stn.)

also at 266 LONDON ROAD, CROYDON, SURREY

NOV

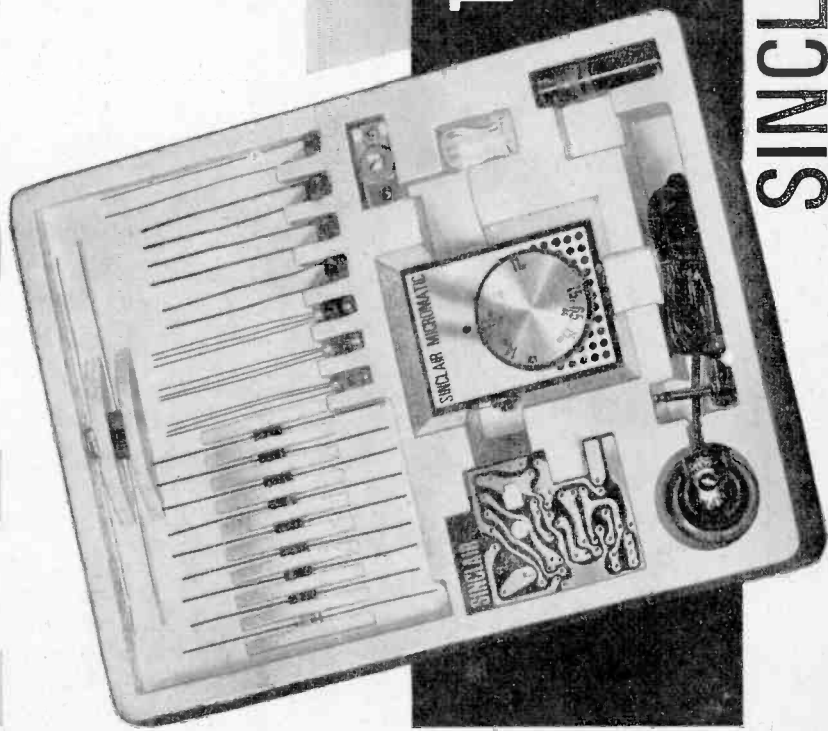


**THE WORLD'S SMALLEST RADIO
COMES TO YOU IN THE NEW "SEE
FOR YOURSELF" SEALED KIT PACK**

SINCLAIR MICROMATIC

59/6

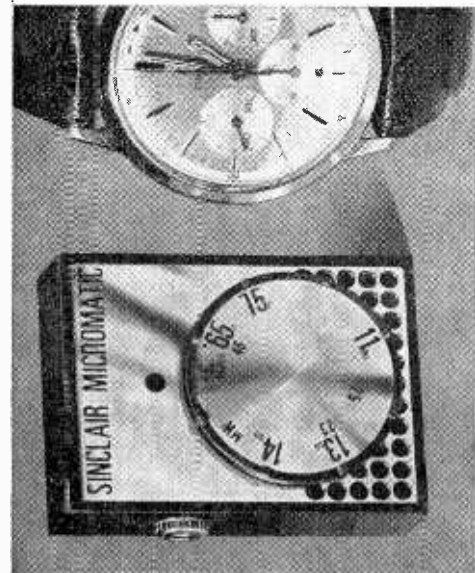Complete kit of
parts including ear-
piece, instructions
and solder in sealed
kit pack.



Photograph shows actual size of Sinclair Micromatic

- ★ **MEASURES ONLY**
1 4/5 in. x 1 3/10 in. x 1 1/2 in.
- ★ **BEAUTIFULLY STYLED CASE**
- ★ **POLISHED ALUMINIUM FRONT PANEL**
- ★ **CALIBRATED SPUN ALUMINIUM TUNING DIAL**
- ★ **AMAZING POWER, RANGE AND SENSITIVITY**
- ★ **NEW CIRCUITRY**
- ★ **BANDSPREAD TUNING PLUS A.G.C.**
- ★ **5 YEAR GUARANTEE**

SINCLAIR MICROMATIC

6 STAGE TRANSISTOR MICRO POCKET RECEIVER

now in the best kit pack ever made available to constructors

Now when you buy your Sinclair Micromatic Kit, you see every component instantly in the new sealed polystyrene Kit pack. Never before in the history of radio has any Kit been so elegantly presented. Your Micromatic reaches you factory fresh and guaranteed. Check for yourself at once that every component is in its proper place in the new case made and shaped to take specially the micromatic kit. Your Micromatic kit does not cost you a penny more

bought this way. Such is the appearance and performance of this brilliant new Sinclair design that you will want to build and use one immediately. There is no other set in the world as small, efficient and dependable as this. Reception both of home and overseas programmes is often much easier than with larger conventional radios. In fact, your Micromatic will virtually play anywhere. *It is also available ready built.*

TECHNICAL DESCRIPTION

The Sinclair Micromatic is housed in a neat plastic case with attractive aluminium front panel and aluminium tuning dial to match, calibrated in metres and kc/s.

Special Sinclair transistors are employed in a six-stage circuit of exceptional power and sensitivity. Two stages of powerful R.F. amplification are followed by a double diode detector from which the signal tuned in is passed to a high gain three stage audio amplifier. Automatic Gain Control counteracts fading from distant stations. The set is powered by two Mallory ZN312 Cells obtainable from radio shops, Boots Chemists, etc., for 1/- each. They give approximately 70 hrs. working life. Inserting the earpiece plug switches the set on, withdrawing it switches off. *Complete kit of parts including lightweight earpiece, instructions and solder*

59/6

79/6

SINCLAIR MICROMATIC, ready built, tested and guaranteed, with earpiece, complete in presentation case

Sinclair

SINCLAIR RADIONICS LTD., 22 NEWMARKET ROAD, CAMBRIDGE
Telephone: 52996 (STD Code OCA3)

ORDER FORM AND MORE
SINCLAIR DESIGNS APPEAR
ON PAGES FOLLOWING



SINCLAIR STEREO 25 DE-LUXE PRE-AMP CONTROL UNIT

THE SINCLAIR STEREO 25 has been designed specially to ensure the highest possible standards of reproduction when used with two Z.12s or any other first class stereo power amplifier. Best possible components are used in the construction of this superb unit, whilst its appearance reflects the professional elegance characteristics of all Sinclair designs in hi-fi, radio and TV. The front panel of the Stereo 25 is in solid brushed and polished aluminium with beautifully styled solid aluminium control knobs. Mounting the unit is simple, and power is conveniently obtainable from the Sinclair PZ.3 which can also be used to supply two Z.12s to make a complete stereo assembly. Hi-fi enthusiasts seeking the ultimate in domestic listening will find all they want from this combination of Sinclair units. With a Micro-FM for tuner, they will have an installation to compare favourably with anything costing from four to five times as much.

FOR USE WITH ANY GOOD STEREO SYSTEM

TECHNICAL SPECIFICATIONS

Performance figures obtained using Stereo 25, two Z.12s and a PZ.3.

■ **SENSITIVITY** for 10 watts into 1.5 ohms load per channel. MIC.—2 mV into 50K ohms. Pick-up—3 mV into 50K ohms. Radio—20mV into 4.7K ohms.

■ **FREQUENCY RESPONSE** (Mic. and Radio)—25 c/s to 30 kc/s ± 1 dB extending to 100 kc/s ± 3 dB.

■ **EQUALISATION**—Correct to within ± 1 dB on RIAA curve from 50 c/s to 20 kc/s.

■ TONE CONTROLS

Treble $+12$ dB to -10 dB at 10 kc/s. Bass $+15$ dB to -12 dB at 100 c/s.

■ **SIZE**—6 $\frac{1}{2}$ in. x 2 $\frac{1}{2}$ in. overall, plus knobs.

■ **FINISH**—Front panel sectioned in brushed and polished solid aluminium with solid aluminium knobs. Black figuring on front panel.

BUILT, TESTED AND GUARANTEED

£9.19.6

"Although a complete novice to radio I was able to assemble it (Micro-FM) without undue difficulty thanks to your clear and lucid instructions. I receive all B.B.C. programmes etc. very strongly."

H.T., Warrington, Lancs

"Far more sensitive (Micro-FM) than many commercial models."

M.M., New Romney, Kent

"Z.12 received in perfect order. It is wonderful to hear records properly."

J. de H.S., London, N.2

"I consider your after sales service is excellent. I wish very much that other suppliers treated their customers in the way you do. I have tried out the Micro-FM with the Z.12 and my Quad speaker and am very pleased with the results."

H.A., London, N.6

SINCLAIR MICRO-FM COMBINED FM TUNER AND POCKET FM RECEIVER

7 TRANSISTORS

• NO ALIGNING

• PULSE COUNTING DISCRIMINATOR

• A.F.C.

• TUNES 88-108 Mc/s

• SIZE—less than 3" x 1 $\frac{1}{2}$ " x $\frac{3}{4}$ "

FM superhet using 7 transistors and 2 diodes. The R.F. amplifier is followed by a self-oscillating mixer and three stages of I.F. amplification which dispense with I.F. transformers and all problems of alignment. The final I.F. amplifier produces a square wave which is converted to produce the original modulation exactly. A pulse counting discriminator ensures better audio quality. One output is for feeding to amplifier or recorder and the other enables the Micro-FM to be used as an independent self-contained pocket portable. A.F.C. "locks" programme tuned in. Signal to noise ratio 30dB at 30 microseconds.

Complete kit, including transistors, case, aerial, earpiece, etc.

£5.19.6




ANYONE CAN BUILD IT

FULL SERVICE FACILITIES AVAILABLE TO ALL SINCLAIR CUSTOMERS

SINCLAIR

SINCLAIR RADIONICS LTD, 22 Newmarket Rd., CAMBRIDGE

Telephone 52996 (STD Code OCA3)

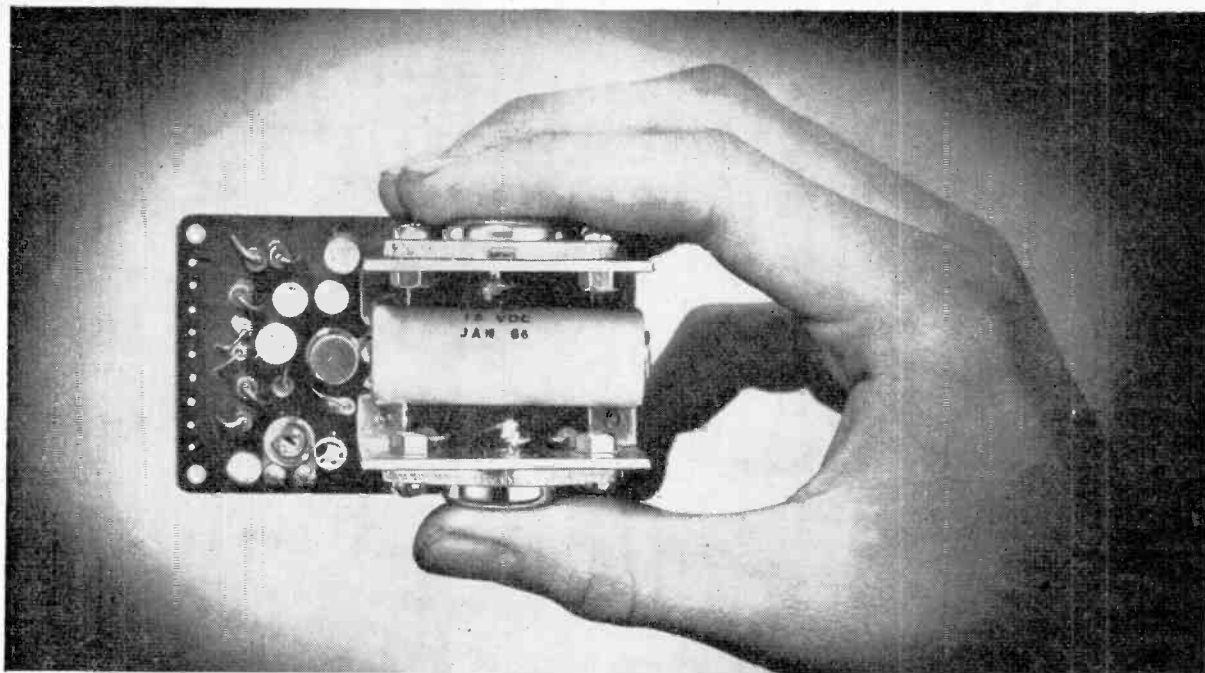


SINCLAIR Z.12

**COMBINED 12 WATT HIGH FIDELITY
AMPLIFIER AND PRE-AMP**

12 WATTS R.M.S. OUTPUT
CONTINUOUS SINE WAVE (24W PEAK)

**8 TRANSISTOR CIRCUIT WITH
CLASS B ULTRALINEAR OUTPUT**

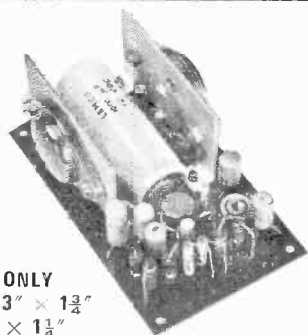**IDEAL FOR HI-FI (STEREO OR MONO)
CAR RADIO, ELECTRIC GUITAR, P.A.,
INTERCOM, ETC.**



ONLY
3" x 1 1/2"
x 1 1/4"

PZ.3 MAINS POWER SUPPLY UNIT

This special power supply unit uses advanced transistorised circuitry to achieve exceptionally good smoothing. Ripple is a barely measurable 0.05 V. The PZ.3 will power two Z.12s and a Stereo 25 with ease.

79/6

The amazing adaptability and rugged construction of this very powerful and exceptionally compact amplifier make it possible to use just one type of unit with outstanding success in an unusually wide variety of applications. Eight special H.F. transistors are used in a highly original circuit to achieve the characteristics demanded of any quality amplifier irrespective of price, yet this Sinclair unit costs well under £5, including its own integrated pre-amplifier. The Z.12 accepts radio, microphone and pick-up inputs. Detailed instructions for connecting

these in mono and stereo are given in the manual supplied with every unit. A number of different control networks are also shown. The Z.12 will operate efficiently from any supply between 6 and 20 V. d.c. making it very convenient to run the amplifier from a car battery. Where it is required to run the Z.12 from mains supply, the PZ.3 is recommended. Those wishing to have a ready made pre-amp control unit can feed inputs via the Stereo 25 which, with two Z.12s, will provide the finest stereophonic hi-fi possible—and the saving in cost is fantastic.

TECHNICAL SPECIFICATIONS

- Size 3 in. x 1 1/2 in. x 1 1/4 in.
- Class "B" ultralinear output.
- RESPONSE 15-50,000c/s $\pm$ 1dB.
- Suitable for 3, 7-5 or 15 Ω speakers. Two 3 Ω speakers may be used in parallel.
- INPUT—2mV into 2k Ω .
- OUTPUT—12 watts R.M.S. continuous sine wave (24 w. peak); 15 watts music power (30 w. peak).
- Signal to noise ratio better than 60dB.
- Quiescent current consumption—15mA.

*Built, tested and
guaranteed.
Ready for
immediate use.
With Z.12
manual.*

89'6

YOUR SINCLAIR GUARANTEE

If you are not completely satisfied when you receive your purchase from us, your money will be refunded at once in full and without question.

If you prefer not to cut this page, please quote PW.467 when writing your order.

To: SINCLAIR RADIONICS LTD., 22 NEWMARKET ROAD, CAMBRIDGE


Please send items detailed below:

NAME

ADDRESS


For which I enclose cash/cheque/money order

PW.467

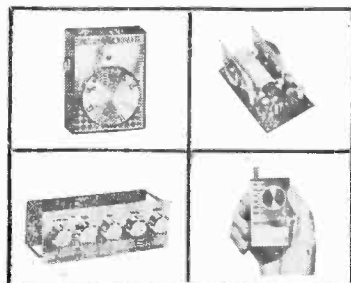

1/2 PRICE SPECIAL RADIO CHASSIS OFFERS

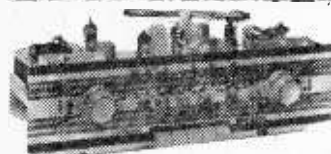HI-FI CONTINENTAL
STEREOPHONIC RADIOGRAM CHASSIS



Magnificent 'Continental' Stereophonic Radiogram Chassis with piano key switches, built-in ferrite rod aerial. Comes complete with two 10" elliptical loudspeakers, plus a mono/stereo 4-speed automatic record changer. Complete 29½ gns. (Units available separately if required. Chassis only, 21 gns.).

Special terms available of £10.6.6 deposit followed by 18 monthly payments of £1.7.3 (total H.P. of £34.17.0)+15/- P. & P. Send £11.1.6 now.

IMPERIAL HI-FI
STEREOPHONIC RADIOGRAM CHASSIS



The Imperial Stereophonic 4 waveband chassis has the most advanced specifications yet offered in this country. There is a built-in ferrite rod aerial, seven piano key buttons, controlling mono/stereo selection, GramLong-Medium-Short-FM-ON/OFF. The unit comes complete with two 10" elliptical loudspeakers plus a mono/stereo 4 speed automatic record changer. Complete £41.9.6. Chassis only, 29½ gns.

Special terms available of £13.16.6 deposit followed by 24 monthly payments of £1.8.10 (total H.P. £48.8.6)+17/6 P. & P. Send £14.14.0 now.

EMPRESS HI-FI
AM/FM STEREOPHONIC CHASSIS



This most advanced radiogram chassis with automatic push button selection covers short, medium and long wavebands plus V.H.F./F.M. Offered complete with 2 10 x 6 speakers 4 speed Stereo/Mono autochanger only £35.19.6. Chassis only, 25½ gns. Special terms available of £12 deposit followed by 18 monthly payments of £1.11.7. (total H.P. £40.8.6)+15/- P. & P. Send £12.15.0 now.

All Lewis Radio equipment including valves are fully guaranteed for one year free of charge. Send your cheque or P.O. today while stocks last to Dept. P.47.

LEWIS radio

LEWIS RADIO, 100, CHASE SIDE, SOUTHGATE
LONDON, N.14. Telephone: PAL 3733/9666

ELECTRONICS GALORE! IN THE NEW dca CATALOGUE

THE CONVENIENT WAY TO SHOP
FOR ALL YOUR ELECTRONIC
NEEDS.

EVERYTHING FROM SINGLE COM-
PONENTS TO COMPLETE EQUIP-
MENT ALL AT BEST VALUE PRICES.

SEND 1/6d. NOW FOR YOUR
COPY TO:—

Dept. PW/4

dca ELECTRONICS LIMITED
28 UXBRIDGE RD., EALING, W.5

NEW VALVES!

Guaranteed Set Tested
24-HOUR SERVICE

1R5	5/-	DK91	5/-	EF86	6/-	PY80	4/9
1R5	3/9	DK96	6/3	EF89	4/9	PY81	5/-
1T4	2/9	DL33	6/6	EL33	6/3	PY82	4/9
384	4/3	DL35	4/9	EL41	8/-	PY83	5/3
3V4	5/-	DL82	4/3	EL84	4/3	PY800	5/11
5V4G	7/9	DL94	5/-	EY51	5/11	R19	8/6
6F1	6/3	DL96	5/11	EY86	5/3	U25	8/9
6K7G	1/3	DY86	6/3	EZ40	5/6	U26	8/6
6K8G	3/3	DY87	6/3	EZ80	3/6	U191	10/-
6L18	7/3	EABC80	5/6	EZ81	4/3	U301	11/6
6V6G	9/-	EA442	7/-	GZ82	8/9	U801	18/-
10C2	11/3	EB41	6/6	K781	6/3	UABC80	5/-
10F1	9/6	EBF80	5/9	N78	14/6	UAF42	6/11
10P13	8/3	EBF89	5/9	PCC84	5/3	UBC41	6/6
20F2	10/3	ECC81	3/3	PCC89	9/9	UBF89	5/9
20P1	8/9	ECC82	4/6	PCF80	6/3	UCC84	7/9
20P3	8/9	ECC83	4/6	PCF82	5/9	UCC85	6/-
20P4	12/6	ECC85	5/3	PCL82	6/3	UCF80	8/-
30P5	9/9	ECH35	5/9	PCL83	8/3	UCH42	8/6
30P4	11/6	ECH42	8/9	PCL84	7/3	UCH81	5/9
30P19	11/6	ECH81	5/-	PCL85	7/9	UCL82	8/9
DAC32	6/9	ECL80	5/9	PL86	9/-	ULC83	8/6
DAF91	3/9	ECL82	6/-	PL81	6/3	UF41	7/9
DAF96	5/11	ECL86	7/6	PL82	6/9	UF89	5/6
DF33	7/6	EF39	3/6	PL83	5/11	UL41	7/9
DF91	2/9	EF41	5/9	PL84	6/-	UL84	5/3
DF96	5/11	EF80	4/3	PY32	8/3	UV41	4/9
DK22	7/-	EF85	5/-	PY33	8/3	UY86	4/9

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any parcel insured against damage in transit 6d. extra. Office address, no callers.

GERALD BERNARD

83 OSBALDESTON ROAD
STOKE NEWINGTON
LONDON N.16

GO AROUND THE WORLD
IN 396 DAYS


396
£2
POST FREE

On your own
TRANSISTOR PORTABLE!

- ★ Boosts Pirate and distant stations
- ★ No Plugs—No Connections! Just place Dewtron Wave Trap near radio.
- ★ Extends Battery life — reduces 'fading'.
- ★ Use in car, caravan, without aerial.
- ★ With PP3 battery (life several months).

D.E.W. LTD., Dept. P.W., Ringwood Road, FERNDOWN, Dorset.

LISTEN TO THE WORLD ON TELSTAR our

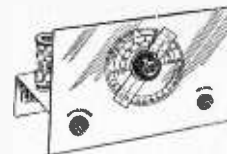

1-VALVE
SHORT WAVE
RADIO

Receives speech and music from all over the world. Price includes valve and one coil covering 40-100 metres. Can be extended to cover 10-100 metres. Can be converted to 2 or 3 valve and all-mains speaker use.
Total building costs **35/-** P. & P. 2/-
All parts available separately.

POCKET RADIO

Covers Medium waveband. No batteries needed. Complete with earpiece.
Only **12/6** P. & P. 2/-

MAINS POWER PACKS

The ideal economical and safe way of running any Transistor Radio, Record Player, Tape Recorder, Amplifier, etc. from A.C. Mains. The MAJOR "Power Plus" for 9v., 7.4v., 6v., 4.5v.; Single Output. P. & P. 2/6 **39/6**
For 9v. + 9v.; 6v. + 6v.; 4.5v. + 4.5v. Two separate outputs. P. & P. 2/6 **42/6**
Please state outputs required.

The BIJOU "Power Plus". For the smaller set using PP3 type battery. **17/6** P. & P. 2/6
All units are completely isolated from mains by double wound transformer ensuring 100% safety.

EASY TO BUILD SETS FOR THE CONSTRUCTOR

Crystal Radio with case. **8/6**

3-Transistor Set with speaker **37/6**

M.W. Tape Tuner for your recorder **20/-**

Supplied with easy to follow instructions. All parts available separately.

R.C.S. PRODUCTS (RADIO) LTD.
(Dept. P.W.), 11 Oliver Road, London, E.17

TV FAULT FINDING

405 & 625 lines
profusely illustrated

Revised & Enlarged Edition

by J. R. Davies

8/6

Postage 9d.

RADIO VALVE DATA, 8th edition.

Compiled by "W.W." 9/6. Postage 1/-.

TRANSISTOR POCKET BOOK, by R. G. Hibberd. 25/-.

Postage 1/-.

RAPID SERVICING OF TRANSISTOR EQUIPMENT, by G. J. King. 30/-.

Postage 1/-.

AMATEUR RADIO CALL BOOK, 1967 edition, by R.S.G.B. 6/-.

Postage 9d.

TAPE RECORDER SERVICING MANUAL, by H. W. Hellyer. 63/-.

Postage 2/6.

ELECTRONIC ORGAN HANDBOOK, by H. E. Anderson. 35/-.

Postage 1/-.

OUTLINE OF RADIO AND TELEVISION, by J. P. Hawker. 30/-.

Postage 2/-.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS

British and American Technical Books

19-21 PRAED STREET

LONDON W.2.

Phone: PADDington 4185

HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT

Type TA1

- Peak output in excess of 14 watts.
- All standard British components.
- Built on printed circuit panel, size 6 x 3in.
- Generous size Driver and Output Transformers.
- Output transformer tapped for 3 ohm and 15 ohm speakers.
- Transistors (GET 114 or 81 Mullard OC81D and matched pair of OC81 c/p).
- Everything supplied, wire, battery clips, solder, etc.
- Comprehensive easy to follow instructions and circuit diagram 1/6. (Free with Kit). All parts sold separately.


SPECIAL PRICE 45/-. P. & P. 3/-.

Also ready built and tested, £28/6. P. & P. 3/-.

A pair of TA1s are ideal for stereo.

STEREO AMPLIFIER

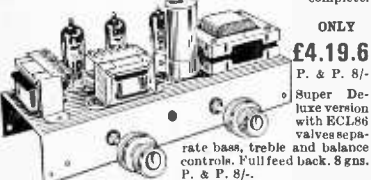Incorporating 2 ECL86s and 1 E280, heavy duty, double wound mains transformer. Output 4 watts per channel. Full tone and volume controls. Absolutely complete.



ONLY £4.19.6
P. & P. 8/-
Super deluxe version with ECL86 valves separate bass, treble and balance controls. Full feed back. 8 gns. P. & P. 8/-.

6 TRANSISTOR AND DIODE SUPERHET

A first-class 2 waveband transistor superhet. ● Printed circuit panel (size 3 1/2 x 2 1/2 in.). ● 3 pre-aligned IF transformers. ● High-gain Ferrite Rod Aerial. ● All First-grade transistors. ● Car aerial winding. ● Push-pull output. ● All parts supplied with simple instructions. All parts sold separately. Set of parts if purchased at one time ONLY £4.5.0. P. & P. 2/6 (Circuit diagram 2/-). Free with set of parts.

35 OHM SPEAKERS

Suitable for use with above. 2in. Goodmans. Ideal replacement for most pocket portables, 8/6; 3 1/2in. 12/6; 7 x 4in., 21/-; P. & P. 2/- per speaker.

PORTABLE CABINET

Size approx. 9 1/2 x 6 1/2 x 3 1/2 in. Suitable for above using 3 1/2 in. speaker, 25/-; P. & P. 2/6.

COIL AND TRANSFORMER SET FOR TRANSISTOR SUPERHET

3 IF transformers one oscillator coil one driver transformer and wound Ferrite aerial (tuned, long and car aerial coupling). 32/6 complete post 2/-; 6 transistor printed circuit board to match 8/6. Post 1/-; Circuit diagram 1/6 extra.

MINIATURE PRECISION AIR-SPACED TWO GANG TUNING CONDENSER. 170 pF to 176 pF. size 1 1/2 x 1 1/2 in. with vanes open. Built in trimmers 5/-; P. & P. 1/-.

BRAND NEW TRANSISTOR BARGAINS

GET 15 (Matched Pair) 15/-; V15/10p, 10/-; OC71 5/-; OC76 6/-; AF117 7/6.
Set of Mullard 6 transistors OC44, 2—OC45 OC81D matched pair OC81 25/-, ORP12 Cadmium Sulphide Cell 10/6.

EDISWAN MAZDA

PXA101 8/6; XA103 8/6.
R.F.1. Pack: 1—PXA102 Mixer; 2—PXA101 I.F. Amp. (Equiv. OC44 and OC45) 10/6
R.F. 2. Pack: 2—PXA101 I.F. 1—PXA102 Osc. 12/6
PXA102 Mixer 12/6
L.F.6 Pack: Consisting of PXB113 Driver Matched pair. PX171 mounted complete with heat sinks (Equiv. OC81D and OC81) 12/6
ALL TRANSISTORS POST FREE.

TAPE DECKS

B.S.R. MONARDECK (Single speed) 3 1/2 in. per sec. simple control, uses 5 1/2 in. spools, £6.15.0 plus 7/6 carr. and ins. (Tapes extra).
LATEST COLLAR MAGNAVOX 363 TAPE DECK DELUXE. Three speeds, 2 track, takes up to 7in. spools. 10 gns. Plus 7/6 Carr. & ins. on each (Tapes extra).

PORTABLE TAPE RECORDER CASE

Beautifully made and expensively finished in dark grey heavy grade rexine. Satin Chrome metal grille front and chrome fittings. Speaker aperture 9" x 4". Overall size 15 1/2" x 15" d. x 7 1/2" h. Will take any standard tape deck or single record player. Limited number only. Worth at least 25. OUR PRICE 49/6. P. & P. 8/6. Brand new and unused.

ACOS CRYSTAL MIKES. High imp. For desk or hand use. High sensitivity, 18/6. P. & P. 1/6.

TSL CRYSTAL STICK MIKE. Listed at 45/-. Our price 18/6. P. & P. 1/6.

QUALITY RECORD PLAYER AMPLIFIER

A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, E280 valves. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. x 3in. d. x 6in. h. Ready built and tested. PRICE 69/6. P. & P. 6/-.

AL80 AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE 59/6. P. & P. 7/6.

DE-LUXE QUALITY PORTABLE R/P CABINET

Uncut motor board size 14 1/2 x 12in. Clearance 2in. below, 5 1/2 in. above. Will take above amplifier and any B.S.R. or Garrard Autochanger or Single Player Unit (except AT60 and SP25) Size 18 x 15 x 8in. Price £28.6. Carr. 9/6.

4-SPEED PLAYER UNIT BARGAINS

All brand new in maker's original packing.

SINGLE PLAYERS

B.S.R. TU12 £3.6 Carr. 5/6.
GARRARD SP25 De Luxe £10.10 Carr. 5/6.
B.S.R. GU7 with unit mounted pickup arm. £4.18.5 Carr. 5/6.

AUTO CHANGERS

Latest B.S.R. UA25 Super slim £6.26
GARRARD 1000 with special Hi-Fi cartridge £8.19.6
GARRARD 2000 £7.10.6, GARRARD 3000 £8.15.0
GARRARD AT60. £9.19.6. Carr. 6/6 on each.
All the above units are complete with t/o mono head and sapphire stylus or can be supplied with compatible stereo head for 12/6 extra.

BRAND NEW CARTRIDGE BARGAINS!

ACOS OP87-1. Mono complete. List price 21/-. Our price 18/6. P. & P. 1/-.

BRAND NEW 3 OHM LOUSPEAKERS

5in., 12/6; 6 1/2in., 15/-; 8in., 21/-; 10in., 25/-; 7in. x 4in., 15/-; 10in. x 6in., 28/-.
E.M.I. 8" x 5" with high flux magnet, 21/-.
E.M.I. 13 1/2 x 8in. with high flux ceramic magnet, 42/- (15 ohm, 45/-). P. & P. 5" 2/-, 6 1/2" x 8" 2/6, 10" x 12" 3/6 per speaker.

SPECIAL OFFER!

Limited number of 12in. 10 watt "R.A." Speakers: 3 ohm 25/-; 15 ohm, 27/6. P. & P. 3/6.

E.M.I. PLASTIC CONED TWEETERS. 2 1/2" 3 ohm. Limited number 12/6 each. P. & P. 1/6.

BRAND NEW HEAVY DUTY 12in. SPEAKERS

Responses 45 c/s-13 K/c/s. 14in. voice coil. Available in 3 or 15 ohms. Guaranteed full 15 watts British rating. Heavy cast aluminium frame. These are current production by world famous maker and as they are offered well below list price we are not permitted to disclose the name. LIMITED NUMBER ONLY. UNREPEATABLE at 38/6 P. & P. 5/-; Also 25 watt Guitar Model available at 25.5.0. And 35 watt Guitar Model £8.5.0.

VYNAR AND REXINE SPEAKER AND CABINET FABRICS

Approx. 54in. wide. Usually 35/- yard. OUR PRICE 13/6 per yard length. 1". P. & P. 2/6 (min. one yd.) S.A.E. for samples.

SPECIAL OFFER!

GENUINE HIGH QUALITY TYGAN FABRIC. 48in. wide. Our price 10/- per foot run. P. & P. 1/6. 30/- per yard run. P. & P. 2/6.

SEMI SHROUDED DROP THRO' MAINS TRANSFORMER. Tapped pri 200/250v. Sec. 300-0-300 v. at 110mA. and 6.3 v. at 3 amp. (E28 screen). Stack size 3 1/2 x 3 1/2 x 1 1/2 in. 30/-; P. & P. 3/6.

MAINS TRANSFORMER. For Transistor power supplies. Pri. 200/240v. Sec. 0-0-5v. at 500mA. 11/-; P. & P. 2/6.

MAINS TRANSFORMER. For transistor power supplies. Tapped pri 200-250v. Sec. 40-0-40 at 1 amp (with electrostatic screen) and 6.3v at 5 amp for dial lamps etc. Drop thro mounting. Stack size 1 1/2 x 3 1/2 x 3 1/2 27/6. P. & P. 4/6.

MATCHED PAIR OF 2 1/2 WATT TRANSISTOR DRIVER AND OUTPUT TRANSFORMERS. Stack size 1 1/2 x 1 1/2 x 1 1/2 in. Output trans. tapped for 3 ohm and 15 ohm output. 10/- pair plus 2/-; P. & P. 6/-.

7-10 WATT OUTPUT TRANSFORMERS to match pair of ECL 86's in push-pull to 3 ohm output. ONLY 11/-. P. & P. 2/6.

WELL-KNOWN MAKERS SURPLUS ONE TRANSISTOR PRE-AMP

Suitable for use with Medium or High Impedance mikes, guitars, gram pickups, tape decks etc. For operation from 200/300 volt H.T. rail or 0 volt battery. Gain approx 14:1. Fully isolated input by Mu-Metal screened transformer. Size 4 1/2" x 1 1/2" x 1". Ready built complete with full circuit diagram and instructions. ONLY 15/-. Post free.

Dual Purpose Bulk Tape Eraser and Tape Head Demagnetiser. 85/-; P. & P. 3/6.

TWIN TELESCOPIC AERIAL. Comprising two 3-section heavily chromed rods. Closed 12-in. each extending to 32in. Completely adjustable from vertical to horizontal. Supplied complete with universal mounting bracket, coax lead and plug. Suitable for F.M. or TV. 12/6. P. & P. 2/6.

SPECIAL HARVERSON OFFER!

FM/AM TUNER HEAD

Beautifully designed and precision engineered by Harverson and Walsworth Ltd. Supplied ready fitted with twin .0005 tuning condenser for AM connection. Prealigned FM section covers 86-102 Mc/s. I.F. output 10.7 Mc/s. Complete with ECC85 (6L12) valve and full circuit diagram of tuner head. Another special bulk purchase enables us to offer these at 27/6 each. P. & P. 3/-. Order quickly! Limited number also available with precision geared 3:1 reduction drive, 30/-; P. & P. 3/-.
Comprising 1st I.F. and 2nd I.F. discriminator (465kc/s /10.7Mc/s). Size 1 x 1 1/4 x 2 1/4 in. high. Will match above tuner head. 11/- pair. P. & P. 2/-.

MATCHED PAIR AM/FM I.F.'s

Comprising 1st I.F. and 2nd I.F. discriminator (465kc/s /10.7Mc/s). Size 1 x 1 1/4 x 2 1/4 in. high. Will match above tuner head. 11/- pair. P. & P. 2/-.

SPECIAL PURCHASE! TURRET TUNERS

By famous maker. Brand new and unused. Complete with PC84 and PCF80 valves 34-58 Mc/s IF. Biscuits for Channel 1 to 5 and 8 and 9. Circuit diagram supplied. ONLY 25/- each. P. & P. 3/6.

GORLER F.M. TUNER HEAD

88-100 Mc/s 10.7 Mc/s I.F., 16/-, plus 2/- P. & P. (ECC85 valve 8/6 extra).

3-VALVE AUDIO AMPLIFIER MODEL HA34

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2 in. w. x 4 in. d. x 4 1/2 in. h. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker, separate Bass, Treble and volume controls. Negative feedback line. Output 41 watts. Front panel can be detached and leads extended for remote mounting of controls.

The HA34 has been specially designed for us and our quantity order enables us to offer them complete with knobs, valves, etc. wired and tested for only **£45.0** P. & P. 6/-.

HSL 'FOUR' AMPLIFIER KIT

A.C. Mains 200/250v., 4 watt, using ECC83, EL84, E280 valves.

● Heavy duty double-wound mains transformer with electrostatic screen.
● Separate Bass, Treble and Volume controls giving fully variable boost and cut with minimum insertion loss.
● Heavy negative feedback loop over 2 stages ensures high output at excellent quality.
● Suitable for use with guitar, microphone or record player. ● Provision for remote mounting of controls or direct on chassis. ● Chassis size only 7 1/2 in. wide x 4 in. deep. Overall height 4 1/2 in.
● All components and valves are brand new. ● Very clear and concise instructions enable even the inexperienced amateur to construct with 100% success. ● Supplied complete with valves, output transformer (3 ohms only), screened lead, wire, nuts, bolts, solder etc. (No extras to buy). PRICE 79/6. P. & P. 6/-.
● Comprehensive circuit diagram, practical layout and parts list 2/6 (free with kit).
This kit although similar in appearance to HA34 employs entirely different and advanced circuitry.

10/14 WATT HI-FI AMPLIFIER KIT

A Stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully arranged sound output transformer to match 3-15Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86, and E280 rectifier. Simple instruction booklet 1/6. (Free with parts.) All parts sold separately, ONLY 27.9.6. P. & P. 8/6. Also available ready built and tested complete with atd. input sockets, £95.0. P. & P. 8/6.
Carrying case for above 28/6. P. & P. 7/6.

NEON A.C. MAINS INDICATOR. For panel mounting, cut out size 1 1/2 x 1 1/2 in. deep inc. terminal. White case with lens giving brighter light. For mains 200/250v. 2/6 each. P.P. 6d. (6 or more post free).

Open all day Saturday
Early closing Wed. 1 p.m.

A few minutes from South Wimbledon
Tube Station.

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, S.W.19 CHERYWOOD 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES
QUOTED APPLY TO U.K. ONLY
P. & P. ON OVERSEAS ORDERS
CHARGED EXTRA.

Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 1/6d. per word (minimum order 18/-), box number 1/6d. extra. Semi-displayed setting £4. 12s. 6d. per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Advertisement Manager, PRACTICAL WIRELESS, George Newnes Ltd., Tower House, Southampton Street, London, WC2, for insertion in the next available issue.

METAL WORK

METAL WORK: All types cabinets, chassis racks, etc., to your specifications. PHILPOTTS METAL WORKS LTD. Chapman Street, Loughborough.

SITUATIONS VACANT

ALDERMASTON COURT POSTAL TRAINING for B.Sc. (Eng) Part I., A.M.I.E.R.E., A.M.S.E., City & Guilds, G.C.E., etc. prepares you privately for high pay and security as Technician or Technologist. Thousands of passes. For details of Exams & Courses in all branches of Engineering, Building, Electronics, etc. (including latest information on C.Eng.), write for 132-page handbook—FREE. Please state interest. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**, (Dept. 169K), Aldermaston Court, Aldermaston, Berks.

RADIO & TV Exam. and Courses by Britain's finest Home-study School. Coaching for Brit.I.R.E., City & Guilds Amateur's Licence, R.T.E.B., P.M.G. Cert., etc. FREE brochure from **BRITISH NATIONAL RADIO SCHOOL**, Russell Street, Reading.

RADIO TECHNICIANS

A number of suitably qualified candidates are required for permanent and pensionable employment (mostly in Cheltenham, but from time to time there are some vacancies in other parts of the UK, including London). There are also opportunities for service abroad.

Applicants must be 19 or over and be familiar with the use of Test Gear, and have had practical Radio/Electronic workshop experience. Preference will be given to candidates who can offer "O" level GCE passes in English Language, Maths and/or Physics, or hold the City and Guilds Telecommunications Technician Intermediate Certificate or equivalent technical qualifications.

Pay according to age, e.g. at 19—£747, at 25—£962 (highest age pay on entry) rising by four annual increments to £1,104.

Prospects of promotion to grades in salary range £1,032—£1,691. There are a few posts carrying higher salaries.

Annual Leave allowance of 3 weeks 3 days rising to 4 weeks 2 days. Normal Civil Service sick leave regulations apply.

Application forms available from:

Recruitment Officer (RT),
Government Communications
Headquarters
Oakley, Priors Road
CHELTENHAM, Glos.

SITUATIONS VACANT

(continued)

TV and Radio, City & Guilds, R.T.E.B., Certs., etc. on 'Satisfaction or Refund of Fee' terms. Thousands of passes. For full details of exams and home training Courses (including practical equipment) in all branches of Radio, TV, Electronics, etc. write for 132-page handbook—FREE. Please state subject. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**, (Dept. 137K), Aldermaston Court, Aldermaston, Berks.

UNIVERSITY OF ST. ANDREWS Electronics Technician

Applications are invited for the post of **ELECTRONICS TECHNICIAN** in the Department of Physics, University of St. Andrews. The work will entail construction of research apparatus, maintenance of commercial equipment, etc. A fully equipped electronics laboratory is available. Salary Scale £683-£968, with supplement of £50 for certain qualifications. It is intended to make the appointment in the upper range of the scale. The appointment will be initially for a period of three years. Applications, with the name of a referee, should be made to the Secretary, University of St. Andrews, College Gate, St. Andrews, Fife, before 18th March 1967.

EDUCATIONAL

RADIO OFFICER training courses. Write: Principal, Newport and Monmouthshire College of Technology, Newport, Mon.

I.E.R.E., City & Guilds and R.T.E.B. exams. Specialised ICS home-study course will ensure success. For details of wide range of exam. and diploma courses in Radio, T.V. & Electronics, also new practical courses with kits, write to: **ICS** (Dept. 542), Parkgate Road, London, S.W.11.

RADIO OFFICERS see the world! Sea-going and shore appointments. Trainee vacancies during 1967. Grants available. Day and Boarding students. Stamp for prospectus. **Wireless College, Colwyn Bay.**

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for I.E.R.E., City & Guilds (Telecoms and Radio Amateurs') R.T.E.B., etc. Many unique diploma courses incl. Colour TV, Electronics, Telemetry & Computers. Also self-build kit courses—valve and transistor.

Write for **FREE** prospectus and find out how **ICS** can help you in your career.

ICS DEPT. 541 PARKGATE ROAD
LONDON, S.W.11.

EDUCATIONAL

(continued)

"BECOME 'Technically qualified' in your spare time, guaranteed diploma and exam. home-study courses in radio, T.V. servicing and maintenance. T.T.E.B., City and Guilds, etc: highly informative 120-page Guide—free. **CHAMBERS COLLEGE** (Dept. 857K), 148 Holborn, London. E.C.1."

CITY & GUILDS (electrical, etc.) on 'Satisfaction or Refund of Fee' terms. Thousands of passes. For details of modern courses in all branches of electrical engineering, electronics, radio, T.V., automation, etc., send for 132 page Handbook—FREE. **B.I.E.T.** (Dept. 168K) Aldermaston Court, Aldermaston, Berks.

BOOKS & PUBLICATIONS

A GUIDE TO SURPLUS COMMUNICATION RECEIVERS

A detailed guide to thirty-one receivers, including the HR0, AR88, CR100, R107, R1155, PCR, 52 set, etc.
7/6, P. & P. 1/-, Mail order only to:
ADKINS, 72 Courtenay Ave, Harrow
Middlesex.

MISCELLANEOUS

CONVERT ANY TV SET into an Oscilloscope. Diagrams and instructions 12/6. **REDMOND**, 42 Dean Close, Portslade, Sussex.

ELECTRONIC MUSIC?

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing.

Write **NOW** for free leaflet and further details to **C. & S., 20 Maude Street, Darlington, Durham.** Send 3d. stamp.

ALUMINIUM CHASSIS, PANELS, etc. Quick service, 'One-offs' welcome. Send sketch for quotation (stamp please). Trade supplied. **FAIRISGRADES LTD.**, Barling, Nr. Southend, Essex.

BERNIESOUND (AUDIO ENGINEERS)

Design-Build-Repair-Modify

All types of Electronic Equipment

For estimates write to:—

Mr. Brown, 1 Effie Place, London, S.W.6.

TAPE RECORDERS, TAPES, Etc.

TAPES TO DISC—using finest professional equipment 45 rpm—18/-. **S.A.E.** leaflet. **DEROY**, High Bank, Hawk Street, Carnforth, Lancs.

RECEIVERS & COMPONENTS

TRANSISTORS. UNMARKED. UNTESTED. 40 for 10/-, p. and p. 1/-, 4 packets post free. Relays, thousands of types, special catalogue free. General catalogue of Mechanical and Electrical Gear, Tools, etc. (5,000 items), free. K. R. WHISTON (Dept. PRW), New Mills, Stockport.

BRAND NEW TELEVISION TUBES!

2 YEAR GUARANTEE. VAST RANGE


12" £3; 14" £4 (not CRM141)
17" £5.15.6; 19" £6.17.6 etc. etc.
Carriage 12/-

Also British valves, lists free!

PHILIP H. BEARMAN, 6 Potters Road,
New Barnet, Herts. Bar 1934/7873.

LARGE QUANTITY of New and Second-hand Radio, Television, Industrial Valves and Tubes. All tested. Down to earth prices. S.A.E. Enquiries, please. Box No. 66.

R.1475 RECEIVERS (TYPE 88)

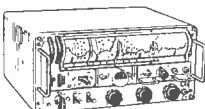

Highly stable, especially accurate, calibrated Marconi design R.A.F. Communication Receiver covering 2-20 Mc/s. in 4 bands with built-in 609

Kc/s. xtal reference oscillator for checking dial which can be reset by special panel trimmer control. 11 valves: 3-6K7, 6K8, 6J5, 3-6Q7, 686, Y83 tuning indicator and VR150/30 voltage regulator. Two-stage I.F. with 8 tuned circuit. Xtal controlled B.F.O. 4 position selectivity with audio filter; for narrow bandwidth. C.W. Pass and show A.V.C. High and low suppression. A plug-in unit with additional mixer provides a "listening through" guard channel of either 2-4 or 4-7.5 Mc/s. Receiver 16 1/2 in. x 9 in. x 11 in. Very good condition. Complete with mains power unit. Fully tested before despatch. £15.10.0. Carriage paid.

NATIONAL H.R.O. SENIOR RECEIVERS 5T MODEL



In excellent tested condition. Complete with 9 coils 50 Kc/s-30 Mc/s and Power Unit. £31.10.0. Carr. 30/-.

REJECTOR UNITS 1.2-10Mc/s
Switched, 4 ranges. Primarily designed as station rejector for R.C. Suitable for harmonic suppression and many other uses with slight alteration. Tuning dial with lock. Adaptor in and out sockets. Brand new 25/-, P. & P. 5/-.



4 VALVE 4 WATT AMPLIFIER



"C" One transformer A.C. Mains 110/230 volts 600 ohms of high impedance input. Output 3 or 600 ohms (state choice). Controls: On/Off switch (chain control). Indicator light. Valve inspection panel. 19 x 7 x 7 in. Brand new in maker's carton. 79/6. Carr. 10/-.

32ft. TELESCOPIC AERIAL MASTS
Comprising 20ft. 1 section tubular steel telescopic mast and 12ft. folding whip; can be erected in less than 5 minutes. Closes to 5ft. 9in. Weight 21 lbs. Must have cost well over £20. Price 67/6. P. & P. 7/6.

ROTARY TRANSFORMER

12v. D.C. input, 250v. D.C. output at 125mA. Size 3 1/2 x 5 1/2 in. Brand new, 17/8, P. & P. 5/-.

AMERICAN DYNAMOTOR UNIT

12v. D.C. input, 240v. output, 150 watts approx. Suitable for Universal A.C./D.C. equipment. 45/-, Carr. 7/6. Many other types.

R.F. ANTENNA TUNER (A.T.U.)

Calibrated scale, ideal 160/80/40 metres. Limited number only. Brand new with instructions, 17/6. P. & P. 7/6.

ALL 19 SETS AND PARTS AVAILABLE

Complete list of other bargains, 1/-, S.A.E. all enquiries. Credit Terms available.

A. J. THOMPSON (Dept. P.W.)

"EILING LODGE", CODICOTE, HITCHIN, HERTS.

Phone: CODICOTE 242

P.C.R. RXS.

These are a 6 valve long. med and short wave Rx. covering S.W. 6 to 18 Mc/s i.e. 50 to 16 metres. Fitted internal speaker, s.k.s. for phones. Tested and fitted with mains P.U. for 230v mains. Price £8.10.0 plus 10/- carr.

RECT. UNIT TYPE 7

This are a multi purpose unit that will either work off 12v D.C. or 200/250v mains to give the following O/Ps: 90v D.C. at 30 mA twice, i.e. 180v C.T. 40v A.C. at 30 mA, and 12v D.C. at 300 mA. It is also possible by making direct connection to trans to obtain any A.C. voltage between 240 and 100 v. All connections are brought out to terminal strips on top of unit, swt. fuses, ind. lamp are fitted with circ. and spare vibrator. In good condition in case, size 9 x 7 x 7 in. PRICE 25/- plus 6/6 carr.

INDICATOR UNIT TYPE 95

Contains valves VR65 (SP61) x 16, EB34 and EA50, CRT type VCR.97 green screen med persistence. CRT filament trans. controls: focus, brill, gain. 12 pre-set pots, Mu Metal shield, slow motion dial 50.1, 2500 pF tuning cond., 100 Kc/s crystal unit. 2 slow motion drives Waxley and key swts. etc. In good condition with outer cover size: 9 x 12 x 18 in. deep. PRICE £3.15.0 plus 10/- carr.

MINE DET. UNITS

Ideal for locating buried metal objects, complete with H/Phones. Search coil, control box ready wired in waterproof containers. Reg. 67/15v. Good condition and crated. PRICE 42/6 plus 10/- carr.

TYPE 88A WALKIE TALKIES

These are battery operated 4 channel crystal controlled unit intended to operate in the 3842 Mc/s band and as for F.M. Tx and Rx. These require 90/1.5 v. battery carbon mike and H/Phones. With crystals and circ. These would provide a good basis for Band 2 portable F.M. Rx. PRICE £4.10.0 plus 5/6 carr.

APQ-43 I.F. AMPLIFIERS

These are a 30 Mc/s 10 Mc/s bandwidth I.F. strip using the following valves: 6AK5x7, 6AG7, 6AL5, 12AU7, in good condition. PRICE 42/6 plus 4/6 post.

APQ-43 PRE-AMPS

These are a 30 Mc/s pre-amp for use with the above I.F. strip and uses valves 6J4 x 2, 6AK5 x 3. Good condition. PRICE 25/- plus 3/6 post. Power and B.N.C. plugs to fit both I.F. and Pre-amp 2/6 each.

TEST SETS TYPE 261/6

These are portable field test sets, the type 261 covers 175 to 305 Mc/s and the 266 covers 95 to 180 Mc/s. Both units are directly calibrated. No xtals are required. These units generate a modulated test signal that is radiated by a small aerial system that is supplied with unit. The modulation freq. can be varied. These units are intended to work off a 6v battery and a vibrator pack is built in to this provision is also made for fitting the battery inside the unit. Overall size 7 x 8 x 16 in. Good condition with circ. PRICE £23.5.0 plus 10/- carr. both types.

TABLE TOP CABINETS

These are an all cabinet with lift up lid and removable back. Overall size 25 x 15 x 17 in. Useful front size 22 x 9 in. Useful internal size 16 in. deep, 10 in. high. Good condition. PRICE 45/- plus 10/- carr.

AXIAL FLOW BLOWERS

I/P 27v D.C. at 4.6 amps, O/P 90 C.F.M. speed 7,600 r.p.m. Size 5 in. dia., 6 in. long. These are a high efficiency fan unit of recent manufacture removed from American radar gear. Will work on 5 and 12v at reduced o/p. PRICE 32/6 plus 4/6 post.

TEST SET TYPE 219

This is a variable frequency pulse generator covering 500 c/s to 10 Kc/s in 2 ranges. The pulse width can be adjusted from .5 to 5 µsec. and the O/P can be switched to +50, +10 and -10v and is variable down to 1 mil volt. There is also a 20 µsec. sync. O/P pulse; by making internal connection to unit it is possible to obtain a sq. wave and s/tooth O/P. Good condition with circ., untested. PRICE £4.10.0 plus 12/6 carr.

WIRELESS CONTROL UNIT II

Contains the following Key Swt. Yx swt 6p, 3w, 2b, Ind lamp, L.F. trans, 2 145+145 ohm coil relays high speed, P.O. relay, 3 small metal rect, all in box size 6 x 3 x 10 in. Brand new. PRICE 12/6 plus 4/6 post.

HEAD AND MIKE SETS

For use with 19 set in used condition but serviceable. PRICE 15/- for 2 pairs plus 3/6 post.

B. SLATER

55 HANDSWORTH RD. SHEFFIELD 9

RECEIVERS & COMPONENTS

(continued)

Rechargeable batt. two cell. Capacity at 10 HR. rate 225MAH. V per cell 1'22V. Charge at 22mA 1'45V per cell. Dis 22mA, 10HR rate. Overall size cyl. 1 in. dia., 3 in. H. 6/- each P.P. Electrolytics, 2,500mf 70v wkg, 14 can, 3 1/2 in. H. 6/- each P.P. HOLLY ELECTRONICS, Holly House, Ford End, Chelmsford, Essex.

COMPONENTS, transistors ex-W.D. and surplus. Call at ROGERS, 31 Nelson Street, Southport. (List 6d stamp.)

WILSON ELECTRONICS


2/- ea. AC126, 127, 128; 2G374B, S18T, S19T (OC83).
2/3 ea. OC81, OC81D, OC82, OC82D.
2/6 ea. OC44, OC45.
3/- ea. OC170, OC71, OC72.
3/6 ea. AF115, AF116, AF117.
4/- ea. AF114, OC171.

20 BRADBOURNE AVENUE, WILFORD NOTTINGHAM

JOHN'S RADIO (Dept. B)

OLD CO-OP, WHITEHALL ROAD DRIGHLINGTON, BRADFORD

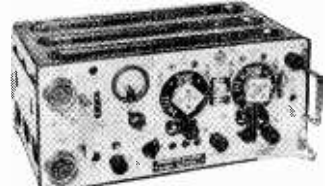FAMOUS ARMY SHORT-WAVE TRANSRECEIVER MK. III



This set is made up of 3 separate units: (1) a two valve amplifier using a 6V6 output valve; (2) (some only) a V.H.F. transreceiver covering 229-241 Mc/s. using 4 valves; (3) the main shortwave Transmitter/receiver covering, in two switched bands, just below 2 Mc/s.-4 Mc/s. and 4 Mc/s.-8 Mc/s. (approx. 160-37.5 metres) using 9 valves. For R.T., C.W. or M.C.W. The receiver is superheterodyne having 1 R.F. stage, frequency changer, two IF (465 Kc/s.) signal detector, A.V.C. and output stage. A B.F.O. included for C.W. or single side-band reception. TX output valve 807, other valves octal bases. Many extras, e.g. netting switch, quick flick dial settings, squeak etc. Power requirements LT 12 volts, HT receiver 275 volts D.C., HT transmitter 500 volts D.C. Size approx. 17 1/2 x 7 1/2 x 11 in. Every set supplied NEW in carton with a 12 pin connector and full book including circuits at only £4.10.0, carriage 15/- with V.H.F. TX/RX, 10/- extra. Brand New and boxed No. 10 head and mike set (made for this set), only 15/-, post 2/6. New 12 volt D.C. power unit for these sets 30/-, carriage 5/-. New aerial tuning unit, 20/-, post 7/6. We make a mains 200/60 volt A.C. power unit in louvered metal case to plug direct into set power socket in run (1) receiver, 70/-, post 5/-; (2) TX and RX, £8.10.0, post 7/6. A charge of 10/- to unpack and test the receiver of these sets is made only if requested. A few only 2nd grade sets as above ONLY £3, carr. and extras as above.

WALKIE-TALKIE MK III & CRYSTAL CALIBRATOR No. 9



This set is housed in a waterproof diecast aluminium case made by Murphy Radio for the Govt. having only reliability and quality in mind. Range 7.3-9 Mc/s. also on site of set is crystal calibrator No. 9 which gives pipe on marks provided on the Tuning dial. Set uses a total of 5 valves power required L.T. 4 volts D.C., H.T. 100-175 volts D.C. Sets supplied in NEW or as new condition, boxed, only 50/-, Carriage 10/-.

RECEIVERS & COMPONENTS (continued)

SAVE ON SILICON

2S302, 40 volt PNP Silicon transistors. Ideal for switching and general applications. Unmarked but fully guaranteed: 2/6 each or 5 for 10/-.
2S002, 45 volt NPN Silicon transistors. 4 Mc/s. ft. Ideal complementary to 2S302. Unmarked but fully guaranteed: 2/- each or 8 for 10/-.
1S130, 50v, 200 mA Silicon diodes, 6/- dozen.
1S131, 100 v, 200 mA Silicon diodes, 9/- dozen. Unmarked. Fully guaranteed.
BY100, 800 p.p.v., 550 mA, Silicon Rectifiers. Unmarked. Fully guaranteed. 3 for 10/-.

BRAND NEW MULLARD BARGAIN.

0C81 EACH 2/-

Postage and packing 9d. Catalogue 1/-. Callers welcome.

L.S.T. COMPONENTS

23 NEW ROAD, BRENTWOOD, ESSEX

R & R RADIO & TV SERVICE

Dept. P.W.
MARKET STREET, BACUP, LANCs.
Telephone 465

SALVAGE VALVES

Tested before despatch

6F13	4/6	U329	5/-	30PL1	4/-	20P4	6/6
6L18	4/6	10P14	5/-	PL36	6/-	PCC84	4/-
EF80	1/6	20P5	6/6	PL82	3/6	PY81	8/6
EC082	3/-	30P	7/-	U801	7/6	U301	6/-
ECL80	3/6	6F15	5/-	10F1	1/6	10P13	5/6
30P5	5/-	EB91	1/-	30FL1	5/-	20D1	2/-
PCF80	4/-	EF85	5/-	PY32	6/-	30P12	5/-
PL81	5/-	6/30L2	4/-	6U4GT	5/-	PY83	5/-
PZ30	5/-	20P3	6/-	EY86	4/-		

Speakers. Ex.T.V. 5in. round 6 x 4in., 3/6; 8in. round 8/-; post 2/-.

Line Output Transformers available. State set model No.

Turret Tuners, 8/-, post 2/-.


Scan Coils, etc. Quote set model No. with all enquiries and S.A.E. for prompt reply. All goods subject to satisfaction or money refunded.

EXPERIMENTER'S PRINTED CIRCUIT CHASSIS KIT

BUILD 30 TRANSISTORISED PROJECTS

on a printed circuit chassis with parts and transistors from your spare box. Latest very efficient designs for Radios, Amplifiers, Scientific Devices etc., etc., to suit everyone's needs and interests. The kit comprises 4 assorted PC laminate boards, etchant, resist, solvent, degreaser, 16-page etching manual "Printed Circuits for Amateurs", 2 miniature Radio Dials. Also Essential Design Data, Circuits and Printed Circuit. Chassis Plans for building

30 SUGGESTED PROJECTS

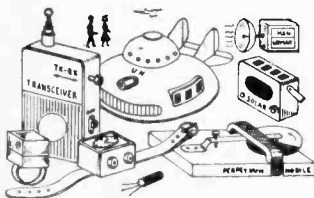

Many recently developed circuits published for the first time including THE SMALLEST 3 RADIOS IN THE WORLD: Ring Radio (70 x 70 x .55in.), Wristwatch Radio (1.15 x .80in.) Postage Stamp Radio (1.6 x .95in.). Recently invented Triple Reflex with self-adjusting regeneration. (Pat. Pen.). Neutralised Double Reflex. Pocket Transceiver (licence required). Solar Loudspeaker Radio. Bacteria Powered Radio. Control of Models by Induction (not radio). Light-Seeking Robot. Guided Missile. Electronic Man/Woman Discriminator. Perpetual Motion Machine. 4 Pocket Transistor Radios. 4 Amplifiers. 2 Intercoms. Burglar Alarm. 4 Unusual Crystal Sets, etc., etc. All designs suit PC boards enclosed. Price of Kit: 9/6. Post and Pack. 1/6. (U.K.) Send S.A.E. for full details & Photographs.

YORK ELECTRICS

181a YORK ROAD, LONDON S.W.11

RECEIVERS & COMPONENTS (continued)

B.C.221 FREQUENCY METER 125-20,000 Kc/s, Unused, Spare set of valves, Crystal calibration book and manual. Less phones, and P.S.U. £22 Carriage Paid. J. BOWDEN, 116 Cowhill, Chadderton, Nr. Oldham, Lancs.

300 m/W AMPLIFIER KITS

Comprising: Full instruction manual — Transformers — Printed circuit — Transistors — Resistors — Electrolytics — Potentiometer — Flex — Copper wire — and solder etc. Price 45/-. Post Free.

9-VOLT POWER PACK KITS

Comprising: Full instruction manual — Resistors — Transformer — Electrolytics — Mains lead — Flex — Printed circuit — Screws and nuts etc. Price 35/-. Post Free.

Pocket-Size TRANSISTOR TESTER

Tests Transistors in or out of set — Tests both P.N.P. and N.P.N. Price 30/- Battery and Post Free.

BROOK & HILL ELECTRONICS

695/697 SEVEN SISTERS ROAD
LONDON, N.15.
(50 yds. from Wards Corner).

NEW COMPONENTS

- ★ ASSORTED TRANSISTORS—6 Tested A.F. Devices 9/6
- ★ ASSORTED RESISTORS—Hi-Stab. 300 off (6% or better, worth £20) 15/-
- ★ SELECTED COMPONENTS—Over 100 Hi-Stab., Pots, Capacitors, Rectifiers, Switches etc. 10/-
- ★ TRANSISTORS—Matched Output Kit: OC81D and 2-OC81 9/6
R.F. Kit: OC44 and 2-OC45 9/6
OC44, 45, 70, 71, 72, 81 and 81D Equivalents, each 3/-
- ★ CAPACITORS—Polyester Foli: 160 VDC/100 VAC.
33 pF to 1.1µF: 5 off, one preferred value... 3/6
.15µF to .47µF: 5 off, one value 5/-
(P. & P. 1/6 per order C.W.O.)

ELMBRIDGE INSTRUMENTS LTD.

Island Farm Avenue, West Molesey, Surrey

SOUND RECORDINGS

A UNIQUE TAPE BUY! Top brand 7in. 2,400ft., 25/-; 5.5in. 1,200ft. 15/-; P. and P. 1 at 2/-, 2 at 2/9, 3-6 at 3/6. Bargains in all sizes. S.A.E. for list. E. C. KINGSLEY AND CO. LTD., 93 Tottenham Court Road, London W.1., EUSTon 6500.

FOR SALE

SPECIAL OFFER. GRUNDIG MA1. 2 Transistor Pre-amps for Tape Monitoring or Microphone Boosters, 47/6, post paid. LIST PRICE 4 GNS. LEE ELECTRONICS, 400 Edgware Road, Paddington 5521

LEE ELECTRONICS

The Tape Recorder and Hi-Fi Specialists

MINIFLUX 4-Track Stereophonic/Monophonic Record/Playback Heads. List Price 6 gns. Special Offer, 55/- each.

MINIFLUX 4-Track Stereophonic/Monophonic Ferrite Erase Heads. List Price £3.10.0 Special Offer 32/6 each, or supplied together (one of each) at £3.17.6. (Send S.A.E. for details.) All Heads are supplied complete with fixing plates and Technical Specifications.

Also available—Miniflux Heads Type SKN4 Low Inductance Transistor. Half Track Stereo at 55/- each. Full Track Erase 30/- Half Track Erase Mono with built-in Oscillator Coil Type LF50, 22/6

400 EDGWARE ROAD, PADDINGTON, W2
Paddington 5521. Closed for Easter Holidays and Stocktaking, 21st March to 1st April.

FOR SALE (continued)

TRANSISTORS SPECIAL OFFER

1 watt S.T.C. 300 mc/s N.P.N. Silicon Planar, Transistors limited stocks £1 for 6.

WITH DATA

3/- each. OC44, OC45, OC70, OC71, OC81, OC81D, OC200, GET16, GET20.

4/- each. AF114, AF115, AF116, AF117, OC170, OC171.

5/- each. OC139, OC140, GET7, GET8, GET9, XC141, BY100, OA211.

BSY27 7/6 each OC20 10/- each

ZENER DIODES

All volts between 3.9v. and 26v.
1/4w 3/6 each, 1.5w 5/- each,
7w 6/- each.

Send 6d. for full lists:—
inc., S.C.R., Zeners.

CURSONS

78 BROAD STREET
CANTERBURY, KENT

465 Kc I.F. trans size 1½ x 1½ x 3½in. New and boxed 7/- per pair. Miniature panel meters 1 mA 1½in. o.s.d. 14/-. Whip aerials 12ft. 3-section in case with insulated base 12/6 plus 5/6 carr. Meters 500 µA 2½in. o.s.d. 12/6. Lesdex Swts 24v 3 bank, 6 pole, 4 way 12/6. B.N.C. coax plugs and sks 2/6 each. Motors 12v D.C. with G.B. 6 r.p.m. 16/6. Tuning cond units 500 pF 2 for 10/-. Motors 24v D.C. 200 r.p.m. 14/-. Dynamometer units 12v I/P 250 at 125 mA O/P 9/6 plus 4/6 post. P.U. type 234 200/250 I/P, O/Ps 250 at 80 mA and 6.3v at 4 amps £2 plus 10/- carr. Morse keys 5/6. B7G valve holders 7/6 per doz. Blower unit 24v D.C. with air filter new unused 17/6. Trans 230v Prio. Type A 26/28/30v at 1 amp 12/6 plus 4/6 post. Type B 6.3v C.T. twice at 3 amps 6.3v at 1 amp 12/6 plus 4/6 post. Type C. Sec 275/225-0-225/275 at 60 mA 4v 1 amp, 6.3v 2 amp 15/- plus 4/6 post. A.F. O/P trans for phones Prio 10K Secs 60 K CT and 600 ohm CT 6/- plus 3/-. Modulation trans also available, all trans new and unused. All prices include postage unless stated as extra.

B. SLATER

55 Handsworth Road
Sheffield 9

FOR SALE (continued)

ELECTRIC SOLDERING IRON



FANTASTIC BARGAIN OFFER

Lightweight Pistol Grip handle
40 watt. 240/250v. A.C. Detachable
handle forms cover for iron when
not in use. With 4ft. Safety
3-core flex. Indispensable for
every home handy-
man. A boon to model
makers and a necessity
for every wireless en-
thusiast. Offered to
you at this new amazing
price.

ONLY
10/-
Post
Free

C. H. SERVICE (Dept. P.W.)
Lusted Hall Lane, Tatsfield, Kent.

HAMMERITE HAMMER PATTERN BRUSH PAINT FOR PANELS, METALWORK

3/6 TIN • JUST BRUSH ON •
WITHSTANDS 150°C. OIL, WATER ETC.
2 1/2 oz. tin 3/6 1 gallon 35/-
1 pint 7/6 1 gallon 58/-
1 pint 15/- (* sent by road)
Carriage: Orders up to 5/-, 9d.; up to 10/-, 1/9;
over 10/-, 3/-. Colours: blue, silver, black or bronze.
Return of post service, Monday to Friday.

From your component shop or direct from the
manufacturer.

FINNIGAN SPECIALITY PAINTS (PW)
Mickley Square, Stockfield, Northumberland.
Tel. Stockfield 2280.

**YUKAN, SO PROFESSIONAL THE YUKAN
SELF-SPRAY**
Get these AIR DRYING GREY HAMMER
or BLACK WRINKLE (CRACKLE) Finishers

Yukan Aerosol spraykit contains 16 oz. fine quality
durable easy instant spray. No stove baking required.
Hammers available in grey, blue, gold, bronze.
Modern Eggshell Black Wrinkle (Crackle) all at 14/11
at our counter or 15/11, carriage paid, per push-
button self-spray can. Also Durable, heat and water
resistant Black Mac finish (12 oz. self-spray cans
only) 13/11 carriage paid.
SPECIAL OFFER: 1 can plus optional transferable
snap-on trigger handle (value 5/-) for 18/11, carriage
paid. Choice of 13 self-spray plain colours and primer
*prior car quality also available.
Please enclose cheque or P.O. for total amount to:

YUKAN, Dept.
307a EDGWARE ROAD,
LONDON, W.2.
Open all day Saturday. Closed Thursday afternoons

Dept. PW/4

MORSE MADE EASY !

The Famous RHYTHM RECORDED COURSE
cuts the practice time down to an absolute
minimum.

One student, aged 20, took only 13 DAYS,
and another, aged 59, took under a week to
read 10 wpm. If you wish to read Morse easily
and naturally please enclose 8d. in stamps or
two international reply coupons for full explana-
tory leaflet to: G3CHS/P.
45 Green Lane, Purley, Surrey. UPLands 2896

WANTED

VALVES WANTED, brand new popular
types boxed. DURHAM SUPPLIES (C),
175, Durham Road, Bradford 8, Yorkshire.

WE BUY New Valves and Transistors. State
price. A.D.A. MANUFACTURING CO., 116
Alfreton Road, Nottingham.

WANTED: Popular Brand New Valves. R.H.S.
Stamford House, 538 Great Horton Road,
Bradford 7.

WANTED (continued)

WE BUY New Valves for cash, large or small
quantities, old types or the latest by return. Send
details. Quotations by return. WALTON'S
WIRELESS STORES, 15 Church Street,
Wolverhampton.

WANTED.—Circuit for Echo Sounder, meter
type. MIERS, Walton, Nr. Street, Somerset.

DAMAGED AVO METERS wanted. Models
7 and 8. Any condition. Any quantity. Send
for packing instructions. HUGGETTS LTD.,
2-4 Pawson's Road, West Croydon.

WANTED by advertiser: a voice actuated Tape
Recorder—details to HEIMS, 274a Kingston
Road, Leatherhead, Surrey.

WANTED Tuner AM/Medium waves prefer-
ably self powered Quad, Lowther or equal
quality. Must be first class working order. Box
No. 65.

WANTED NEW VALVES ONLY

Must be new and boxed
Payment by return

WILLIAM CARVIS LTD
103 North Street, Leeds 7

SERVICE SHEETS

RADIO TELEVISION over 8,000 models.
JOHN GILBERT TELEVISION, 1b Shepherds
Bush Rd., London W.6. SHE 8441.

SERVICE SHEETS

4/- each, plus postage

We have the largest display of Service
Sheets for all makes and types of Radios
and Televisions, etc., in the country. Speedy
service.

To obtain the Service Sheet you require
please complete the attached coupon.

Name:

Address:

To: S.P. DISTRIBUTORS

35/36 Great Marlborough Street,
London, W.1

Please supply Service Sheets for the following

Make:

Model No. Radio/TV

Make:

Model No. Radio/TV

Make:

Model No. Radio/TV

I require the new 1967 List of Service
Sheets at 1/6 each plus postage.

(please delete items not applicable)

enclose remittance of
(which includes postage)

MAIL ORDERS ONLY (Apr.) PW

SERVICE SHEETS (continued)

SERVICE SHEETS for all makes, Radio, T.V.,
Tape Recorders, 1925-1966. Prices from 1/-
Catalogue 6,000 models 2/6d. Free fault-
finding guide with all Sheets. Please send
stamped addressed envelope with all orders/
enquiries, HAMILTON RADIO, Western
Road, St. Leonards, Sussex.

SERVICE SHEETS, Radio TV, 5,000 models,
List 1/- S.A.E. inquiries. TELRAY 11
Maudland Bank, Preston.

SERVICE SHEETS (75,000) 4/- each. Callers
welcome. Always open. 5 South Street,
Oakenshaw, Bradford.

Please mention
"Practical Wireless"
when replying to
Advertisements

PADGETTS RADIO STORE
OLD TOWN HALL
LIVERSEDE, YORKSHIRE
Telephone: Cleekeheaton 2866

Special Offer. Ex R.A.F. Wave Meter, type
W1649. Beautifully made in solid brass, all
complete with slow-motion drive in wooden box.
Valves are used but in good condition. 17/6, or
new 30/-, plus post and packing 7/6.

Brand new TV Tubes. 14in. MW36/44. £2.0.0.
Plus 10/- carriage.

19 Set with outer case. Receiver section
complete with valves.

Parts Removed. 500 micro-amp meter, all
transmitter parts. Relay and 807 valve.
Condition fair. No dry rot 10/-, Carr. 10/-.

Reclaimed Tubes. Six months' guarantee.
AW43/80. 30/-, MW43/80. 30/-, MW43/80. 30/-,
CRM72. 30/-, CRM142. 17/-, 12in. Tubes. 10/-,
17in. Tubes perfect but without guarantee,
17/- each. Carriage on any Tubes in G.B. 10/-.
Specially Selected Nearly New Valves.
6 months' guarantee.

PY33	6/-	ARP12	1/6	EL38	5/-
PCC84	5/6	ECL80	3/6	5U49	4/-
PCF80	5/6	ECC83	5/-	6K7	1/9
PL81	5/6	ECC82	4/3	6V6	1/9
807	5/-	EF91	2/-	185BT	8/6

Single Valves. Post 7d.

VALVE LIST

Ex. Equipment.	3 months' guarantee.	Post 7d.
EF80 1/6	PCF80 2/-	10P13 2/6
ECL80 1/6	PCC84 2/-	10P1G 5/-
EF91 9d.	PCL82 4/-	20D1 3/-
EB91 9d.	PCL83 3/-	20L1 5/-
EBF80 3/-	PCL85 3/-	20P1 4/-
ECC81 3/-	PZ30 5/-	20P4 8/6
ECC82 3/-	PY81 1/6	U329 5/-
ECC83 4/-	PY82 1/6	U801 8/6
EL84 5/-	PL81 4/-	U301 5/-
EF50 1/6	PL36 5/-	U191 5/-
EY86 5/-	PY33 5/-	U281 5/-
6K25 5/-	B8 1/6	U282 5/-
6U4 5/-	EF1 1/-	U25 5/-
6P25 5/-	EF14 5/-	
KT36 5/-	6C2 5/-	

Breaking up 19 Sets.

Relays 100 ohm Coil 2/-, Post 2/6. 1 Doz. 28/-.

Post Paid. Jack Sockets, 7/6 doz. Post Paid.

Toggle Switches, 7/6 doz. Post Paid.

Pointer Knobs, 7/6 doz. Post Paid.

Top Grade Diodes, 3/6 doz. Post Paid. No duds.

Perfect Speakers. Removed from TV sets.

Goodmans 7 x 4, 5/-, Goodmans 8 x 5, 7/6, 6 x 4,
and 5ins. 3/-, Plus Post on any Speaker, 4/-.

New 2 1/2 inch Speakers, with built-in tweeter,
28/6, 3 or 15 ohm. Coil, 28/6, Post Paid.

New 24 volt Miniature Model Makers Motor
will run from 6 volts. 6/6. Post Paid. Motors

Single Phase Quarter H.P., 28/-, Sixth H.P.,
15/-.

Ex Washing Machines. Fully guaranteed.

Plus Carriage 10/-.

Type 46 Set, Complete with valves. Send receive
switch removed. 12/6. Post Paid.

Broadway ELECTRONICS

GARRARD 4 SPEED DECKS WITH CARTRIDGE:

Autochangers: AT6 Mk II £8.19.6.
Autoslim £5.5.0. AT60 £10.19.6.
3000, £8.8.0. 2000, £6.19.6.
1000, £5.19.6.
AT5—Mono £6.10.0.
P. & P. all changers 7/6.

SINGLE PLAYERS:

SP25 with cartridge stereo or
mono, £9.19.6. SRP 12, £4.5.0.
P. & P. 7/6.

CARTRIDGES:

Stereo: EV26, 25/- GP83, 15/-
Reuter, STD/2, 17/6. Mono: GC8,
15/- GC2, 15/- Sonotone, 21/SS,
15/- GP67, 15/- P. & P. 1/-.

MICROPHONES:

Xtal Hand Mikes.

BM3 and 200C, 30/- P. & P. 2/-
Stand for same 9/6 & 12/6. P. & P.
1/9. ACOS Mike 45, 21/- ACOS
Mike 40, 18/6. Dyn. Mike DM-391,
22/6. CM21 Xtal, 12/6. CM20 Xtal,
9/6. Magnetic Hm 63C with remote
control switch, 15/- Telephone
Pick-up 10/6. P. & P. 1/- Xtal
Lapel Mike, 7/6. Guitar Mike,
12/6. P. & P. 6d.

SPEAKER ENCLOSURES

Tony Corner Cabinet 20 x 10 x
7in. takes 10 x 6in. speaker
covered in Rexine and Vynair,
45/- P. & P. 5/-.

Blake cabinet size 18 x 24½ x
9½in. fabric covered £4.10.0.
P. & P. 10/-.

Haydon, 16½ x 15 x 7½in. fabric
covered suitable for 12in.
speaker, 45/- P. & P. 7/6.

Haydon enclosure fitted with
12in. speaker and volume
control. £4.17.6. P. & P. 10/-.

Hi-Fi Bookshelf speaker en-
closure foam lined, cabinet
size 10½ x 5½ x 7½in. Teak
finish, £3.0.0. P. & P. 3/6.

Woofer for above £3.0.0. P. & P.
2/6. Tweeter 12/6. P. & P.
1/6. Condenser for crossover
2/6. Terminals 2/6 pair. P. & P.
6d.

PLINTH Teak finish to match
above Hi-Fi speaker size
17½ x 14 x 4in. for Garrard
1000, 2000, 3000, AT60, SP25,
£2.17.6. P. & P. 4/6.

SPEAKERS:

Elac Heavy duty Ceramic
Magnets 11,000 line, 10in.
round 10 x 6in. 3 ohm or 15
ohm, 42/6. P. & P. 3/6. 8in.
round 15 or 3 ohm, 38/6. P. & P.
3/6. E.M.I. 13½ x 8in. 15 or
3 ohm, 42/6. P. & P. 3/6.
E.M.I. Tweeter, 12/6. P. & P.
1/6. R.T.C. 12in. 20 watt 15
ohm, Ceramic magnet £5.5.0.
P. & P. 3/6. 8 x 4in Elliptical
30 ohm, 30/- P. & P. 3/6. All
other speakers supplied—
Goodmans, Bakers, W.B.,
Wharfedale, Eagle, Tripletone.

BARGAINS IN TRANSISTORS:

AC127, AF114, 115, 116, 117,
118, 119, OC169, 170, 171, 172,
200, 202, 203, 204, 5/6.
OC72, 75, 82, 83, AAZ12,
BY38, BCZ11, 3/6. OC71, 81,
3/- R.F. Packs 1 OC44,
2 OC45 8/6. AF Packs 1
OC81D, 2 OC81 (Mullard),
8/6. A.F. Pack 1 GET119, 5/6.
GET113, Red Spot, 2/- OC26,
28, 29, 9/6. ORP12 Light Cell,
8/6. Diodes OA81, 2/3. OA91,
OA95, 1/9. P. & P. on above 6d.

TRANSISTOR ELECTROLYTICS:

1, 2, 4, 5, 8, 10, 16, 25, 32,
50, 100 mfd 15 volt working,
1/3. P. & P. 6d.
250 mfd DC 3/-.
500 mfd 12v DC, 3/-.
P. & P. 1/-.

RESISTORS, ½ watt 10% from
3.3 ohm to 10 meg 5d. each.
4/- doz. P. & P. 6d.

EARPIECES WITH CORD AND
3.5 mm. plug. 8 ohm magnetic, 3/-.
250 ohm, 4/- 180 ohm with clip
5/6. Xtal 4/- P. & P. 6d.

TRANSISTOR SPEAKERS 8 ohm
2in., 8/6; 3in. 10/6; 3½in. 12/6.
P. & P. 1/-.

PANEL LIGHTS, 6v. Red, Blue,
Green, Yellow, White (uses Lilliput
bulbs) 3/- each. P. & P. 6d.

NEON PANEL LIGHTS
200-250v. 2/6. P. & P. 6d.

PAPER CONDENSERS for Cross-
Over Units, 2 mfd. 2/6. P. & P. 6d.

ROTARY SWITCHES

2 pole Mains Switch, 3/- 1 pole
12 way, 2 pole 2 way, 3 pole 3 way,
3 pole 4 way, 4 pole 3 way, 3/6
each. P. & P. 6d.

PUSH BUTTON SWITCHES, 4
button, 2 banks of 6 S.P.C.O.,
1 bank of 5 S.P.C.O. 1 off button.
5/6. P. & P. 6d.

BATTERY CHARGER TRANS-
FORMERS AND RECTIFIERS 4
amp. GEC Rect., 15/- Heavy
Duty Transformer, 25/- P. & P.
3/6. 1 amp. Westinghouse contact
cooled rect., 7/6. Transformer 12/6.
P. & P. 3/- Large Croc. Clips, 2/6
per pair, P. & P. 6d.

FERROX ROD AERIAL, with
coils, 8 x ½in., 5/6. 4 x ½in. 4/6.
P. & P. 9d.

Stockists of ● Eagle Products
● Goodmans ● W.B. ● Wharfe-
dale ● Bakers ● Tripletone
● Linear, all makes of ampli-
fiers and speakers supplied.
S.A.E. please. Trade terms to
bona fide dealers.

92 MITCHAM ROAD, TOOTING BROADWAY,
LONDON, S.W.17 Telephone BALham 3984

Closed all day Wednesday
(four minutes from Tooting Broadway Underground Station)

THE BEST OF ALL CIRCUIT BOARD SYSTEMS

Best because it is the only one in the world by which you can produce a single circuit board to your own requirements without having to use chemicals, etching, heat or special tools, yet the end result equals a printed circuit in all respects and is even better in others. Applying this system, called "Cir-Kit" is very cheap, quick and it can be easily modified. As such, it is used in laboratories and by experimenters as well as all up-to-date constructors. Basically, "Cir-Kit" comprises 95% pure copper strip and sheet backed by a unique adhesive protected by an easily removed backing. "Cir-Kit" Pack No. 3 contains approx. 15ft. of ½in. strip, 6 x 4in. sheet and a 12 x 6in. laminate board—enough for about 10 average circuits. In sealed pack with instructions—15/-.

A 16 WATT HI-FI STEREO AMP USING "CIR-KIT" FOR ECONOMY AND EFFICIENCY

The Peak Sound SA.8-8 integrated stereo amplifier and pre-amp with tone controls is a first-class compact design using 14 matched transistors, "Cir-Kit" and ready-drilled metal chassis. Assembly is exceptionally simple. For use with high-quality ceramic or crystal stereo cartridges and 3-5 and 8-15 ohm loudspeakers. This Peak Sound constructor's kit is absolutely complete, even down to wire and solder and includes excellent step-by-step illustrated instructions. With front panel, 14 transistors, chassis, "Cir-Kit" etc.

£12.19.6 Peak Sound Mains Power Pack 75/-.

From good stockists or direct in case of difficulty

PEAK SOUND (HARROW) LTD. 10 ASHER DRIVE, MILL RIDE, ASCOT, BERKS. Winkfield Row 3217

Distributors to the radio wholesale and retail trade

TECHNICAL SUPPLIERS LTD., 63 GOLDHAWK ROAD, W.12. (01-603-2581)



GOODMANS HIGH FIDELITY MANUAL A Guide to full listening enjoyment

The Manual is much more than a catalogue of Goodmans High Fidelity Loudspeakers—it contains informative articles, including advice on stereo, special beginners page, and full cabinet drawings. You'll find it interesting as well as informative.

NEW MAXAMP 30 HIGH FIDELITY AMPLIFIER

MAXAMP 30 is a fully transistorised stereophonic High Fidelity Amplifier using Silicon Transistors throughout. It is precision engineered and fullest use is made of printed circuits. It will deliver continuously up to 15 watts of power on each channel and it looks as good as it is. 10½" x 5½" x 7¼" £49.10s.0d.

Full specification of the Maxamp 30 is given in the High Fidelity Manual - send the coupon for your FREE copy - or pay an early visit to your Goodmans dealer.

FREE

Please send Hi-Fi Manual together with name and address of my nearest Goodmans dealer.

Name

Address

PW4

GOODMANS INDUSTRIES

AXIOM WORKS · WEMBLEY · MIDDLESEX Tel: WEM 1200
A Division of Radio Rentaset Products Ltd.

No.1 Just Out!

A NEW MAGAZINE FOR
EVERY HOME HANDYMAN



No.1 OF THE **NEW** HOW-TO-DO-IT MAGAZINE
PRACTICAL MARCH 1966
Decorating & Building
PRICE 2/6

FREE!

**QUANTITY
CALCULATOR**

for Glass
Cemert, Paint
and Wallpaper

EXTRA!

8-page
Supplement

**ALL ABOUT
CEMENT &
CONCRETE**

EXTRA!

Fold-out
Data Sheet on
**FITTING
WINDOWS**



**Packed with new ideas and de-
tailed know-how on major
home improvements**



**Hurry—Make
sure of *your*
copy NOW! 2/6**

BI-PAK SEMICONDUCTORS

8 RADNOR HOUSE
93/97 REGENT STREET
LONDON W1

★ VALUE PAKS for '67
★ — NEW — UNTESTED —

PIV	LOW COST SILICON CONTROLLED RECTIFIERS (THYRISTORS) FACTORY TESTED	1 AMP (TO-5 can)	7 AMP (STUD)	16 AMP (STUD)	30 AMP (STUD)	Free SCR Literature, Circuits, etc. with SCR orders or on request.
25	7/8	7/8	10/8	30/-		
50	8/8	8/8	15/-	35/-		
100	12/6	15/-	20/-	45/-		
200	15/-	20/-	25/-	55/-		
300	17/8	25/-	35/-	80/-		
400		30/-	45/-	95/-		
500		30/-	50/-			
600						

FREE One 10/- Pack of your own choice free with orders valued £4 or over **FREE** LOGIC MODULES and/or, Gates, Memory Units, Timer Units, etc., details free **FREE**

VALUE PAK 50 TRANSISTORS MIXED UNTESTED **10/-** **10SCR's** UNMARKED, UNTESTED VOLTAGE RANGE 1 Amp 50-400 PIV **20/-**

3 OC139 Trans. NPN Mullard	10/-	3 High volt. AF Trans. PNP ACY17	15/-
2 Dritz Trans. 2N1225 100 M/Cs PNP	10/-	5 Sil. Rect. 750mA 100 PIV TEXAS	15/-
6 Matched Trans. OC44/45/81/81D	10/-	3 B8Y95A Sil. Trans. STC	15/-
4 OA10 Diodes Mullard	10/-	3 Sil. Trans. OC200 Mullard	15/-
15 Red Spot AF Trans. PNP	10/-	2 Sil. Power Rect. 6 Amp. 200 PIV BYZ13	15/-
15 White Spot RF Trans. PNP	10/-	1 AF139 GERM. Trans. 1500 M/Cs	15/-
4 Sil. Rects. 3A 100/400 PIV	10/-	1 Sil. Power Trans. 100 M/Cs TK 201A NPN	15/-
4 NPN Trans. OC139 2N1302, etc.	10/-	6 Zener Diodes 3-15 volts. Mixed 400 mW	15/-
2 10 Amp. Sil. Rect. 50/100 PIV	10/-	5 OA5 Gold Bonded Diodes Mullard	15/-
8 Diodes 4 OA70, 4 OA79	10/-	1 2N132 PNP PLANAR Trans. Sil.	15/-
1 5 AMP BCR 100 PIV	10/-	2 2N697 NPN PLANAR Trans. Sil.	15/-
3 Sil. Trans. 2N303 PNP	10/-	4 GERM. Power Trans. eqvt. OC16 Mullard	15/-
5 GET884 Trans. Equiv. OC44	10/-	1 UNIJUNCTION Trans. 2N2649 G.E.	15/-
10 Assorted Computer Diodes	10/-	2 Sil. Trans. 60VCB 200 M/Cs. ZT83/84	15/-
4 Zeners 5, 6.8, 10, 12 Volts	10/-	1 Sil. PLANAR Trans. B8Y25 NPN 100 M/Cs	15/-
4 2G417 Trans. Equiv. AF1116/117	10/-	1 Sil. Trans. 18104 150 M/Cs HFE 200 NPN	15/-
2 200 M/Cs Sil. Trans. B8Y26/27	10/-	2 SCR's 50 PIV 1 Amp. TO-5 can	15/-
2 Bi-directional Trans. 8BY66	10/-	1 Tunnel Diode IN3720 (TD-5) G.E.	15/-
4 High Current Trans. OC42 Equiv.	10/-	1 2N2160 UNIJUNCTION Trans. TO-5 can	15/-
2 Power Trans. OC26/35	10/-	2 Sil. Rect. 5 Amp. 400 PIV Stud	15/-
5 Sil. Rects. 400 PIV 250mA	10/-	1 Tunnel Diode AEY II STC. 1050 M/Cs	15/-
3 OC71 Trans. Mullard	10/-	2 GERM. Power Trans. OC28/29	15/-
3 OC75 Trans. Mullard	10/-	2 ZENERS 25 watt 18 and 22 volts	15/-
3 NPN Sil. Trans. 70 M/Cs	10/-	6 Sil. Rect. Type BY100 800 PIV 550mA	20/-
1 Power Trans. OC20 100 Volts	10/-	8 Sil. Rect. 400 PIV 200/500mA	20/-
5 OA47 Gold Bonded Diodes	10/-	1 Transistor Manual by G.E. 648 pages	30/-
4 OA202 Sil. Diodes Sub-Min.	10/-	1 Silicon Controlled Rect. Manual G.E.	30/-
3 OC77 Trans. Mullard	10/-	25 Mixed Sil. & GERM. Trans. New Marked	30/-
8 OA81 Diodes CV448	10/-	40 Mixed Semiconductors New Marked	40/-
3 Sil. Rects PIV. 400 500 mA	10/-	1 Logic Module Handbook & Catalogue	17/6

Our vast stocks change daily with hundreds of Semiconductor bargains becoming available. Just send 2/6 to cover 3 months mailing of our latest stock lists, eqvt. charts, circuits, etc.

Minimum Order 10/-. CASH WITH ORDER PLEASE. Add 1/- postage and packing per Order. GUARANTEED by return postal service Overseas add extra for Airmail.

120 DIODES 10/-

ALL TYPES MIXED VOLTS
20 ZENERS 10/-

SIL NPN 200 M/Cs
25 Transistors 10/-

1 Amp. GERM. up to 300 PIV
20 RECTIFIERS 10/-

SILICON 200 mA
60 DIODES 10/-

SILICON 750 mA TOP-HAT
16 RECTIFIERS 10/-

SILICON BRIDGE RECTIFIERS

NEW TESTED
600 PIV 2 Amp. at 55°C. 25/- EACH
800 PIV 2 Amp. at 55°C. 30/- EACH

A COMPLETE RANGE OF SILICON RECTIFIERS
750 mA TO 25 Amp. 50-1000 PIV NOW IN STOCK.
ASK FOR PRICE LIST.

WHEATSTONE BRIDGE KIT

Set of 18 x 1/4" Wirewound Resistors and 18 switches Measures 1Ω to 1mΩ. 70/6.

TRANSISTOR SQUARE WAVE GENERATOR

Useful for signal tracing or Morse practice. Variable amplitude. Parts to build 11/-.
300 Assorted 2 Watt Resistors. 1% to 20%, 13/6.

1% HIGH STABILITY RESISTORS

1 watt 1%, 2/- each. Full range 10Ω to 10mΩ. Selected to 1%, 6d. extra. Stock list available.

1% WIREWOUND RESISTORS

More stable than high stat. carbon, and wound to any value 1Ω to 5kΩ, 3/3; to 20kΩ, 4/6, 1% add 3d.

Circuits for Noughts and Crosses Machine, Demonstration Binary Adder/Subtractor. Analogue Multiplier/Divider, Football Pool Computer, Quadratic and Simultaneous Equation Solvers. Further details on request.

PLANET INSTRUMENT CO.

25 (W) DOMINION AVENUE. LEEDS 7.

WORLD RADIO & TV HANDBOOK 1967, 32/-

by JOHANSEN, postage 1/3

Guide to Broadcasting Stations new ed. by Wireless World 6/- P. & P. 7d.
T.V. Fault Finding, 405, 625 lines by Data 8/6. P. & P. 10d.
Circuits for Audio and Tape Recording by Judd. 7/6. P. & P. 10d.
Radio Valve Data, new 8th ed. by Wireless World 9/6. P. & P. 1/-.
Hi-Fi Year Book 1967 ed. 15/- P. & P. 1/6.
Transistor Specs. and Subs. Handbook 1967 ed. by Techpress 21/- P. & P. 1/-.
Multi Channel Radio Control by Warring 12/6. P. & P. 1/-.

Where possible 24-hour service guaranteed.

UNIVERSAL BOOK CO.

12 LITTLE NEWPORT STREET,
LONDON, W.C.2


(Leicester Square Tube Station)

2 METRES 4

The thrills of VHF Amateur Radio! Complete Kit, 70-150 Mc/s, costs only 47/6 (by post, UK, 3/3 extra) also now available new transistor Short-Wave kit model TR2 10-180 metres. Ideal for beginners to Ham radio via simplified "Easy-Build" step-by-step instructions from 79/6. Write today enclosing a stamped addressed envelope for literature and full details. Overseas enthusiasts note we despatch to all parts of the world—local stamp OK for literature. "GLOBE-KING" (Regd.) precision standard products tried and trusted by Amateurs everywhere.

JOHNSONS (Radio)

St. Martins Gate, Worcester

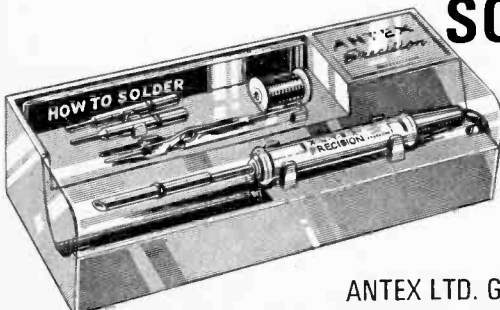

SOLDERING?—the complete answer!

Made by ANTEX—makers of the finest precision soldering irons in the world, this Soldering Kit contains everything you need for successful soldering. Unique plastic "tool-box" format (with space for iron stowage with plug) keeps everything where you want it.

ANTEX LTD. GROSVENOR HOUSE, CROYDON, SURREY. MUnicipal 2774/5

R.S.T. VALVE MAIL ORDER CO.

144-146 WELLFIELD ROAD, STREATHAM, S.W.16

Mon.—Sat. 9 a.m.
—5.45 p.m.
No Early Closing
Open Daily to Callers
Tel. STR 0199, 1649

All valves
brand new
and boxed

0A2 5/3	6B6 4/6	6K6GT 5/—	7R7 10/8	19A5 7/6	50L6GT 6/—	DF96 6/—	ECF*0 7/—	EM81 7/—	PC189 10/6	S130 25/—	UM80 7/—
0C3 5/3	6BH6 7/—	6K7M 5/3	787 17/9	20D1 10/7	5/—	DH77 3/6	ECF*2 7/—	EM84 7/—	PCF80 6/6	8P4 9/—	U6 13/6
1A7 7/9	6B3 7/—	6K7G 1/3	7Y4 7/6	20F2 11/—	78 4/6	DK32 7/9	ECH21 10/—	EM150 27/6	PCF82 6/6	8P41 1/6	U7 13/6
1D6 6/—	6BQ7A 7/—	6K7GT 4/6	98W6 8/—	20L1 15/—	80 5/—	DK91 5/—	ECH35 11/—	EY81 7/—	PCF84 6/—	8P61 1/—	U9 8/—
1H5 7/6	6BR7 10/6	6K8M 3/6	10C1 9/—	20P4 17/—	85A2 3/6	DK92 6/—	ECH42 9/—	EY85 6/6	PCF86 8/—	8P85 10/6	U91 7/6
1LD5 5/—	6BR8 7/6	6K8GT 3/3	10C2 12/—	20P5 16/—	150B2 14/6	DK96 6/6	ECH81 5/3	EZ35 4/9	PCF801 9/9	8U25 10/6	U91 7/6
1NDGT 8/—	6BR7 18/9	6K8GT 3/3	10F1 14/—	25A6 6/6	150C4 12/6	DL66 15/—	ECH83 7/—	EZ40 7/—	PCF802 9/9	8U2150 12/6	U91 7/6
1R5 5/—	6BW6 7/6	6K25 20/—	10F3 12/—	25L6GT 4/6	801 5/—	DL92 4/9	ECL80 6/6	EZ41 8/—	PCF805 10/9	T41 9/—	U91 7/6
1R4 5/—	6BW7 8/6	6L1 9/6	10F9 9/9	25Y5 6/—	807 7/9	DL93 3/6	ECL82 6/6	EZ80 5/—	PCF806 12/—	T41 9/—	U91 7/6
1R5 3/6	6C4 3/—	6L6G 7/—	10F18 9/—	25Z4 6/3	813 80/—	DL94 5/9	ECL83 8/—	EZ81 5/—	PCF808 11/6	T41 9/—	U91 7/6
1T4 3/6	6C5G 4/—	6L18 7/6	10L1 10/—	25Z5 7/—	866 10/—	DL95 6/9	ECL86 8/9	EZ82 5/6	PCF813 8/6	T41 9/—	U91 7/6
2A4 3/6	6C6 3/—	6Q7G 5/6	10LD11 10/—	25Z6 11/—	964 4/—	DL96 6/—	EPA 20/—	GZ22 9/6	PCF818 11/6	T41 9/—	U91 7/6
3Q4 6/6	6C8 3/—	6Q7GT 9/—	10L13 14/—	25D7 5/—	1625 5/—	DM70 5/—	EF36 3/—	GZ34 10/—	PCF82 7/—	T41 9/—	U91 7/6
3Q5 6/6	6C8G 6/—	6Q7GT 9/—	10L13 14/—	30C1 6/6	4022AR15/—	DY86 6/6	EF37A 7/6	KT36 22/6	PCF82 7/—	T41 9/—	U91 7/6
3R4 4/9	6C16 5/9	68C7 6/6	12A7 4/6	30C15 11/6	5763 10/6	DY87 7/9	EF39 6/—	KT61 17/6	PCF82 7/—	T41 9/—	U91 7/6
3V4 5/9	6CW4 12/—	68G7 4/—	12A77 3/9	30C17 12/—	7193 10/6	ES80C 12/—	EF41 8/—	KT66 20/—	PCF82 7/—	T41 9/—	U91 7/6
6R4G 8/9	6D5 2/9	68H7 2/6	12A7 4/9	30F5 13/—	7475 2/6	EA50 2/—	EP50 2/—	KT81 10/—	PCF82 7/—	T41 9/—	U91 7/6
6V4G 8/—	6E5 5/9	68J7 5/—	12A7 4/9	30F11 13/6	ATP4 1/9	EA50C80 5/9	EP80 5/—	KT88 27/6	PCF82 7/—	T41 9/—	U91 7/6
5Y3GT 5/—	6F1 9/—	68K7GT 4/9	12A7 4/9	30L15 12/6	ATP5 7/—	EAF42 7/6	EF85 6/6	KTW61 4/3	PCF82 7/—	T41 9/—	U91 7/6
5Z4G 8/—	6F6 9/—	68L7GT 4/9	12A7 4/9	30L17 12/—	ATP7 4/6	EB41 4/6	EF86 6/3	KTZ41 8/—	PCF82 7/—	T41 9/—	U91 7/6
6/30L12 11/3	6F6G 4/—	68N7GT 4/—	12A7 4/9	30P12 10/—	AU2 30/—	EB91 3/6	EF89 5/6	ML4 17/6	PCF82 7/—	T41 9/—	U91 7/6
6A7 15/—	6F8G 4/6	68Q7 6/—	12C1 19/6	30P19 14/—	AU5 6/—	EB93 3/6	EF91 3/3	ML6 12/6	PCF82 7/—	T41 9/—	U91 7/6
6ASG 12/6	6F11 12/6	6U3G 7/6	12C1 19/6	30P11 14/—	AZ1 5/9	EB94 8/3	EP92 2/6	MP4 12/6	PCF82 7/—	T41 9/—	U91 7/6
6AC7 3/—	6F13 5/—	6V6M 8/—	12J5GT 2/3	30P13 14/—	AZ31 7/9	EB90 3/9	EP98 6/—	MU14 4/—	PCF82 7/—	T41 9/—	U91 7/6
6AL5 4/6	6F14 12/6	6V6G 3/6	12J7GT 7/3	30PL14 14/—	CHL31 15/—	EBF80 6/6	EF183 6/6	MX40 12/6	PCF82 7/—	T41 9/—	U91 7/6
6AL5 3/—	6F23 11/—	6V6GT 7/—	12K7GT 3/—	35A5 17/—	OCH35 21/—	EBF83 7/—	EF184 6/6	N37 10/—	PCF82 7/—	T41 9/—	U91 7/6
6AM5 2/6	6G6 2/6	6X4 3/6	12K8GT 3/—	35L6 5/9	CL33 12/6	EBF89 6/6	EL32 3/—	N78 15/—	PCF82 7/—	T41 9/—	U91 7/6
6AM6 3/3	6H6 1/3	6X5G 4/9	12K9GT 3/—	35W4 4/6	CY31 10/6	EBL1 17/6	EL33 17/6	N105 15/—	PCF82 7/—	T41 9/—	U91 7/6
6AQ6 5/6	6J5M 6/6	6X5GT 7/6	12Q7GT 3/—	35Z3 10/—	JAC32 7/6	EBL21 10/6	EL34 9/6	NGT1 3/—	PCF82 7/—	T41 9/—	U91 7/6
6AR7G 19/6	6J5G 2/6	7B6 11/—	12S7 6/6	35Z4GT 3/9	DAF91 3/6	EBL31 27/6	EL41 8/6	NGT7 25/—	PCF82 7/—	T41 9/—	U91 7/6
6AT6 3/9	6J5GT 4/6	7B7 7/—	12S7 2/9	35Z5 5/6	DAF96 6/—	ECC81 3/9	EL42 7/6	OZ4 4/—	PCF82 7/—	T41 9/—	U91 7/6
6AU6 6/—	6J6 3/—	7C5 10/—	12S7 3/9	37 5/—	DOC90 3/—	ECC82 4/9	EL48 4/6	PC86 9/—	PCF82 7/—	T41 9/—	U91 7/6
6B8G 2/—	6J7M 8/6	7C6 8/—	12S7 3/9	42 4/6	DF33 8/—	ECC83 5/9	EL90 5/6	PC88 9/—	PCF82 7/—	T41 9/—	U91 7/6
6B4G 10/—	6J7G 4/9	7D5 8/—	12S7 3/9	50B5 6/6	DF70 5/—	ECC84 5/6	EL95 6/—	PC97 7/—	PCF82 7/—	T41 9/—	U91 7/6
6BA6 4/6	6J7GT 8/6	7H7 5/—	14H7 9/—	50C5 5/9	DF91 2/6	ECC85 5/—	ELL80 20/—	PC84 6/6	PCF82 7/—	T41 9/—	U91 7/6
				50CD6G32/6	DF92 2/6	ECC88 7/—	EM80 7/—	PC89 10/—	PCF82 7/—	T41 9/—	U91 7/6

SPECIAL 24 HOUR SERVICE
OBSOLETE TYPES A SPECIALITY
QUOTATIONS FOR ANY VALVE NOT LISTED
Postage 6d. per Valve C.W.O. No C.O.D.
Send S.A.E. for list of 2,000 Types
Manufacturers and Export Inquiries Welcome

Special 24 Hour
Express Mail
Order Service

SETS OF VALVES									
DAF96, DF96, DK94, DL96	...	...	...	...	...	...	...	...	Set of 4. 24/6
BRAND NEW TRANSISTORS									
AC127 8/—	OC25 11/—	OC71 4/6	OC81 4/—	OC82D 6/—	OC28 16/—	OC72 6/—	OC81m/pr 12/6	OC83 6/—	OC82D 6/—
AF114 7/—	OC35 16/—	OC75 6/—	OC81D 4/—	OC170 7/6	AF115 7/—	OC44 4/6	OC76 8/—	OC81D 4/—	OC170 7/6
AF116 7/—	OC45 3/6	OC77 8/—	OC82 6/—	OC200 5/—	AF117 6/—	OC45 3/6	OC77 8/—	OC82 6/—	OC200 5/—

PLEASE NOTE OUR NEW ADDRESS

TV TUBES REBUILT & RESCREENED

by Britain's largest
independent Tube
Rebuilder

SUFFOLK TUBES LTD.
1/3 Upper Richmond Road
Putney, London, S.W.15
Tel.: Vandyke 4304/5267

MIDLAND TUBES LTD.
467/483 Oldham Road
Manchester. 10
Tel.: Collyhurst 4412

BUILD YOUR CIRCUITS ON VERO BOARD

— the Universal Wiring Board —
obtainable from your local Retailer

Retail enquiries to:

NORMAN ROSE (ELECTRICAL) LTD.
8 ST. CHAD'S PLACE, GRAYS INN ROAD, LONDON, W.C.1

Technical enquiries to:

VERO ELECTRONICS LTD., Chandler's Ford, Hampshire

with the NEW Antex

PRECISION SOLDERING KIT

This is what the ANTEX Kit contains:

- Model CN240 15W Precision Iron with 3/16" bit, (used in electronic workshops and factories all over the world)
- Two spare Interchangeable Bits (5/32" and 3/32")
- Reel of resin-cored Solder
- Handy Heat Sink
- Cleaning Pad

BRING YOUR WORKSHOP UP-TO-DATE with the new ANTEX KIT

From electrical & radio
shops, or if unobtainable
locally apply direct to —

49/6

PLUS 36-page booklet on "How-to-Solder"—a mine of information for amateur and professional.

ANTEX LTD. GROSVENOR HOUSE,
CROYDON, SURREY. MUNICIPAL 2774/5

Imperial

- Illustrated in this advertisement are two fine cabinets from the Lewis Radio Range.
- These cabinets are just two of a really extensive range.
- Each one carefully made by British Craftsmen and soundly constructed from the best materials available.
- Fill in coupon below to obtain FREE catalogue showing this wonderful range of cabinets.



Designed to assist your choice of Cabinet.
The New Lewis Radio Cabinet Catalogue—the most comprehensive ever prepared. Sent absolutely FREE!
Please send your FREE cabinet catalogue.

NAME
ADDRESS
..... (Dept. P47)
Capitals please

LEWIS radio

100 Chase Side, Southgate, London N.14.
Tel.: Palmer's Green 3733/9666

Famous for over 30 years for Short-Wave Equipment of quality, "H.A.C." were the original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

IMPROVED 1987 RANGE

One-valve model "DX", complete kit—price 56/6
(Postage and packing 3/6.)

Customers say: "Definitely the best one-valve S.W. Kit available at any price." This kit contains all genuine short-wave components, drilled chassis, valve accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits still available, including the famous model "K" (recommended by radio clubs). All orders despatched by return. (Mail order only.) Send now for a descriptive catalogue, order form, etc. to —

"H.A.C." SHORT-WAVE PRODUCTS
29 Old Bond Street, London W.1



*The PUNCH
you need!*

HOLE PUNCHES

Instant Type	3/8" diameter	1/2" diameter	5/8" diameter	6/16" diameter
Screw-up Type				
1/2" diameter Toggle switch				8/6" ea
1/2" " " " " " "				8/6" "
1/2" " B7G				9/6" "
1/2" " B8A, B9A				9/6" "
1/2" " " " " "				10/8" "
1/2" " " " " " "				10/8" "
1/2" " " " " " "				11/8" "
1/2" diameter Int. Octal				13/4" "
1/2" " " " " " "				16/2" "
1/2" " " " " " "				18/10" "
1/2" " B9G				21/8" "
1/2" " " " " " "				24/4" "
2 3/4" " Meter				33/2" "

Complete Set £9.3.6.

*No extra charge for postage and packing
in the U.K.*

Now supplied by

TOMPKINS & LONGMAN LTD.

**237 GIPSY ROAD
WEST NORWOOD, S.E.27**
Tel. Gipsy Hill 5000

£6/9/6

Solve your communication problems with this new 4-Station Transistor Intercom (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals, Office and Home. Operates on one 9v battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 6/6.

INTERCOM/BABY ALARM

Usually ~~SIX~~ \$6.95
Our Price ONLY

49/6

Modernise business or home with this new two-way **Portable Transistor Intercom**. Consisting of **Master** and **Sub**, in strong plastic cabinets, with chromium stands. Designed as a two-way instant communication system. Call/talk/listen from **Master** to **Sub** and **Sub** to **Master**. Operates on one 9v battery. Complete with 60ft wire and battery. P. & P. 2/6.

Transistor TELEPHONE AMPLIFIER

Usually 6 cm.

55/-

Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. Indispensable in office/home. On/off switch. Volume Control. Operates on one 9V battery. P. & P. 2/6. Battery 2/6 extra. Full price refunded if returned in 7 days.

WEST LONDON DIRECT SUPPLIES (PW4)
169 KENSINGTON HIGH STREET, LONDON, W.8.

NEW RANGE U.H.F. AERIALS FOR BBC 2 (625) line transmissions

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.
Loft Mounting Arrays 7 element, 35/-,
 11 element, 42/6, 14 element, 50/-,
 18 element, 57/6. **Wall Mounting with**
Cranked Arm 7 element, 60/-, 11 element,
 67/-, 14 element, 75/-, 18 element, 82/6.
Loft Mounting 7 element, 2in. clamp, 52/6,
 42/6; 11 element, 55/-, 14 element, 62/-,
 18 element, 70/-, **Chimney Mounting Arrays**,
Complete 7 element, 72/6; 11 element, 80/-,
 14 element, 87/6; 18 element, 95/-. Complete
 assembly instructions with every unit.
 All aerials fitted with U.H.F. clamp
 from 75/- State clearly channel number
 required on all orders.

BBC • ITV • F.M. AERIALS



BBC (Band 1). Telescopic
loft, 21/-. External S/D.
30/-. "H" £2.10.0.

ITV (Band 3). 3 Element
loft array, 25/-. 5 element,
35/-. Wall mounting, 3
element, 35/-. 5 element,
45/-.

Combined BBC/ITV. Loft 1+3, 41/3; 1+5, 48/9; Wall mounting 1+3, 56/3; 1+5, 63/9; Chimney 1+3, 63/9; 1+5, 71/3.

VIII transistor pre-amps,
75/-.

F.M. (Band 2). Loft S/D, 12/6, "H", 30/-, 3 element, 52/6. External units available. Co-ax cable, 8d. yd. Co-ax plugs, 1/3. Outlet boxes, 4/6. Diplexer Crossover Boxes, 12/6. C.W.O. or C.O.D. P. & P. 5/-. Send 6d. stamps for illustrated lists.

Quotations for special arrays available
on request

K.V.A. ELECTRONICS (Dept. P.W.)
27 Central Parade, New Addington
Surrey
LOD 2266




(14)



(12)



(10)

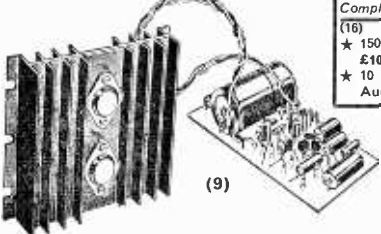

(9)

12 AND 20 WATT MONO AND STEREO TRANSISTOR AMPLIFIERS

(9) **POWER AMPLIFIERS.** 12 watts RMS output. 100mV input. 30 c/s to 20 kc/s -1dB. 6-transistor Push-pull. Panel size 4 x 2½ x 1in. H/S 4 x 4in. (leaflet on request). **MPA10/3** 3-5 ohm spkr. £4.10.0. p.p. 2/6. **MPA10/15** 8-16 ohm spkr. £5.5.0. p.p. 2/6. (Mains unit 1 or 2 amplifiers, 59/6, p.p. 2/6)

The Finest High Fidelity at Unbeatable Prices

25 WATT AMPLIFIER
8-Transistor design. Push-pull output for 7½ to 16 ohm speaker. 150mV input. 30c/s to 20kc/s-1dB. For use with valve or transistor pre-amplifiers as item (10) above.
PRICE BUILT £7.19.6 P.P. 3/-
(Mains unit 79/6, p.p. 2/6)

(13) **MULTIMETERS SCOPE**
PT34 1kV 39/6 EP30k 30kV £6.10.0
TP10 2kV 75/- EP50k 50kV £9.19.6
1T1-2 20kV 69/6 500 30kV £8.17.6
TP55 20kV £5.19.6 EP100k 100kV £10.10.0
● **CT52** Scopes £22.10.0. P.P. 10/-.
Complete range of test equipment in stock

(16) **NOMBEX TEST UNITS**
★ 150 kc/s-350 mc/s RF Generator £10.10.0. All Transistor.
★ 10 c/s-100 kc/s Transistor. £16.19.6 Audio Generator.

(15) **GARRARD BATTERY 2-SPEED TAPE DECK**
Brand New with R/P head, erase/osc. head, tape cassette Specifications and osc. circuits. 2 speed 2-track 9 volt operated. List Price 13 gns.
PRICE £8.19.6 P. & P. 3/6

COMPONENTS AND EQUIPMENT. The largest range in the country. 8/6 buys 200-page catalogue with discount vouchers (see back page)



(16)



(17)



(13)



(15)

HENRY'S RADIO LTD.
303 EDGWARE RD., LONDON, W.2
PADdington 1008/9 (STD 01-723-1008)
Open Mon. to Sat. 9-6. Thurs. 1 p.m.
Open all day Saturday

SEE BACK COVER FOR MORE ITEMS OF INTEREST

Loudspeakers and Loudspeaker Cabinets

A Philips Paperback


P. W. Van Der Wal

This book provides particulars of numerous different speaker boxes, and is intended to be a source of information on various matters which, although apparently incidental, must nevertheless be given due consideration if the best results are to be obtained. To enable the "do-it-yourself" enthusiast to deal with certain problems which may arise during the construction of the boxes, a chapter of practical hints is also included.

107 pp 15s net 8d postage

available from leading booksellers

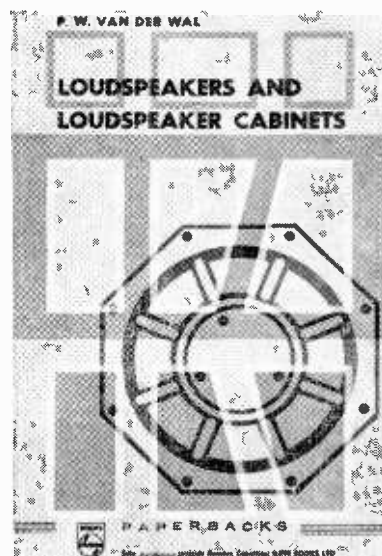ILIFFE BOOKS LTD. DORSET HOUSE, STAMFORD STREET, LONDON, S.E.1.



Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2
Tel. PARK 5641/2/3

Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to the Head Office

When sending cash with order, please include 2/6 in £ for postage and handling
MINIMUM CHARGE 2/-. No C.O.D. orders accepted

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel. LANgham 8403
Open all day Saturday

OA2	6/-	6AH6	10/-	6F7	5/-	10F9	10/-
OA3	10/-	6AK5	5/-	6F8G	5/-	10F18	9/-
OB2	6/-	6AL5	6/-	6F11	6/-	10F19	7/8
OC3	6/-	6AM6	4/-	6F12	4/-	10F13	15/-
OD3	6/-	6AN8	10/-	6F13	6/8	10F14	15/-
OZAA	5/-	6AQ4	5/-	6F14	15/-	11D3	7/-
LA3	4/-	6AQ5	5/8	6F15	11/-	11D5	7/-
1A5GT	7/-	6A7E	4/8	6F17	6/-	12AC8	9/-
1A7GT	8/-	6AR6	6/-	6F18	7/8	12AE6	7/8
1B3GT	8/-	6AR8	17/6	6F23	10/-	12AL5	7/-
1C5GT	5/-	6AR5	5/-	6F24	12/-	12AQ5	7/-
1D6	8/-	6AR8	6/-	6F25	12/-	12AT6	5/-
1D8GT	6/-	6AS7G	15/-	6F28	10/8	12AT7	4/-
1G4GT	6/-	6A7E	4/8	6H6	2/-	12AU6	6/-
1HG5T	7/-	6AU8	9/-	6J4	9/-	12AU7	5/8
1L4	2/8	6AV5GTA		6J6	3/8	12AV6	5/8
1NG5T	8/-	6AV6	11/-	6J7G	5/-	12AV7	8/-
1R4	6/-	6AW8A	12/8	6KG6	6/-	12AW6	20/-
1R5	6/-	6B4G	17/-	6K7GT	3/-	12AX7	6/-
184	5/-	6B8	7/-	6K8	9/-	12AY7	10/-
185	4/8	6B8G	2/8	6L8G	7/8	12BA4	9/-
1T4	3/-	6BA6	4/8	6L9C	5/-	12B6	5/8
1T5GT	6/-	6B7A	15/-	6L7	5/-	12B8	5/8
1U4	5/-	6BE6	4/8	6L7	9/-	12B7	10/-
1U5	6/-	6BE6	4/8	6L18	6/-	12C4	4/8
1V2	10/-	6BF7	15/-	6L19	5/-	12C5	4/8
1X2B	7/-	6CG6G	16/-	6N7GT	7/-	12C6	5/8
1X2B	7/-	6CG6G	16/-	6P25	12/-	12C7GT	7/8
2C34	7/8	6BJ6	7/8	6P28	12/8	12K8	8/-
2C51	10/-	6BK4	22/8	6Q5G	15/-	12Q7G	4/-
2CW4	12/-	6BK7A	9/-	6Q7	7/-	12R4	7/-
2D21	6/-	6BL7GTA		6P28	12/8	12R4	7/-
2E24	40/-			6SC7	9/-	12R4	7/-
2E26	22/8	6BN6	7/8	6SF5	7/-	12R4	7/-
3A4	4/-	6BQ7A	7/-	6SF7	7/-	12R4	7/-
3A5	7/-	6BR7	11/-	6SG7	6/-	12R4	7/-
3AV6	6/-	6BR8	5/-	6SH7	4/-	12R4	7/-
3B7	5/-	6B7	12/-	6SH7	4/-	12R4	7/-
3B28	40/-	6BW6	7/-	6SH7	4/-	12R4	7/-
3D6	4/-	6BW7	12/-	6SH7	4/-	12R4	7/-
3E29	60/-	6BZ6	6/-	6SH7	4/-	12R4	7/-
3Q4	7/-	6BZ7	11/-	6SH7	4/-	12R4	7/-
3Q5GT	6/8	6C4	3/8	6SH7	4/-	12R4	7/-
3V4	6/-	6CG5T	6/-	6SH7	4/-	12R4	7/-
4THA	8/-	6C9	11/-	6SH7	4/-	12R4	7/-
4T8P	8/-	6C31	12/-	6SH7	4/-	12R4	7/-
4X150A	100/-	6CB5	5/-	6SH7	4/-	12R4	7/-
5R4G	9/-	6CH6	6/-	6SH7	4/-	12R4	7/-
5R5GB	9/-	6C16	9/-	6SH7	4/-	12R4	7/-
5U8	9/-	6C16	9/-	6SH7	4/-	12R4	7/-
5V4G	5/8	6C16	9/-	6SH7	4/-	12R4	7/-
5Y3GT	5/-	6C16	9/-	6SH7	4/-	12R4	7/-
5Z3	7/8	6C16	9/-	6SH7	4/-	12R4	7/-
5Z4G	7/8	6C16	9/-	6SH7	4/-	12R4	7/-
6/3012	8/8	6C16	9/-	6SH7	4/-	12R4	7/-
6A8	8/-	6C16	9/-	6SH7	4/-	12R4	7/-
6B4	6/-	6C16	9/-	6SH7	4/-	12R4	7/-
6AB7	4/-	6C16	9/-	6SH7	4/-	12R4	7/-
6AC3GT10	8/-	6C16	9/-	6SH7	4/-	12R4	7/-
6AC7	4/-	6C16	9/-	6SH7	4/-	12R4	7/-
6AF4	10/-	6C16	9/-	6SH7	4/-	12R4	7/-
6AF6G	11/-	6C16	9/-	6SH7	4/-	12R4	7/-
6AG5	2/8	6C16	9/-	6SH7	4/-	12R4	7/-
6AG7	6/-	6C16	9/-	6SH7	4/-	12R4	7/-

First Quality Fully Guaranteed



ELECTRONIC VALVES

30P18	6/8	1267	20/-	DH63	6/-	ECC189	11/-
30P19	13/-	2050	12/-	DK32	8/-	ECC804	10/-
30P11	15/-	4313C	20/-	DK40	11/-	ECC807	7/-
30P13	15/-	5651	7/8	DK91	6/-	ECC827	7/-
30P14	15/-	5654	8/-	DK92	8/-	ECC828	7/-
35A3	10/-	5670	10/-	DK96	7/-	ECC830	9/8
35A5	10/-	5718	10/-	DL33	6/8	ECC835	11/-
35B3	12/-	5749	10/-	DL35	5/-	ECC842	9/8
35C5	6/8	5751	12/-	DL38	10/-	ECC841	9/8
35D5	12/-	5763	10/-	DL39	12/8	ECC843	7/8
35L6GT	6/-	5814	10/-	DL91	5/-	ECC184	9/8
35W4	4/8	5965	5/-	DL92	5/-	ECC185	9/8
35Z3	10/-	6000	5/-	DL93	4/-	ECC187	9/8
35Z4G	4/-	6080	25/-	DL94	6/-	ECC182	6/8
35Z4GT	8/8	6146	25/-	DL95	7/-	ECC183	9/8
35Z5GT	5/8	6159	32/-	DL96	7/-	ECC184	12/8
42	6/-	6293	60/-	DM70	5/8	ECC185	11/8
43U1	8/-	6360	30/-	DY30	8/-	ECC186	9/8
45A5	12/-	6539	45/-	DY86	6/8	ECC187	5/8
45B5	6/8	7551	30/-	DY902	8/-	ECC188	5/8
45C5	6/-	7588	22/8	E88CC	12/6	ECC189	8/-
45D5	22/8	7895	22/8	E90CC	10/-	ECC190	8/-
45E5	60/-	9002	5/8	E92CC	7/-	ECC191	9/-
45F5	7/-	9003	9/-	E93CC	8/-	ECC192	9/-
45G5	35/-	9008	15/-	E94	8/8	ECC193	9/-
45H5	6/-	9009	17/8	E95	8/8	ECC194	11/-
45I5	20/-	9012	23/-	E96	8/8	ECC195	23/-
45J5	13/-	9013	13/-	E97	8/8	ECC196	23/-
45K5	12/-	9014	12/-	E98	8/8	ECC197	23/-
45L5	12/-	9015	12/-	E99	8/8	ECC198	23/-
45M5	12/-	9016	12/-	E100	8/8	ECC199	23/-
45N5	12/-	9017	12/-	E101	8/8	ECC200	23/-
45O5	12/-	9018	12/-	E102	8/8	ECC201	23/-
45P5	12/-	9019	12/-	E103	8/8	ECC202	23/-
45Q5	12/-	9020	12/-	E104	8/8	ECC203	23/-
45R5	12/-	9021	12/-	E105	8/8	ECC204	23/-
45S5	12/-	9022	12/-	E106	8/8	ECC205	23/-
45T5	12/-	9023	12/-	E107	8/8	ECC206	23/-
45U5	12/-	9024	12/-	E108	8/8	ECC207	23/-
45V5	12/-	9025	12/-	E109	8/8	ECC208	23/-
45W5	12/-	9026	12/-	E110	8/8	ECC209	23/-
45X5	12/-	9027	12/-	E111	8/8	ECC210	23/-
45Y5	12/-	9028	12/-	E112	8/8	ECC211	23/-
45Z5	12/-	9029	12/-	E113	8/8	ECC212	23/-
46A5	12/-	9030	12/-	E114	8/8	ECC213	23/-
46B5	12/-	9031	12/-	E115	8/8	ECC214	23/-
46C5	12/-	9032	12/-	E116	8/8	ECC215	23/-
46D5	12/-	9033	12/-	E117	8/8	ECC216	23/-
46E5	12/-	9034	12/-	E118	8/8	ECC217	23/-
46F5	12/-	9035	12/-	E119	8/8	ECC218	23/-
46G5	12/-	9036	12/-	E120	8/8	ECC219	23/-
46H5	12/-	9037	12/-	E121	8/8	ECC220	23/-
46I5	12/-	9038	12/-	E122	8/8	ECC221	23/-
46J5	12/-	9039	12/-	E123	8/8	ECC222	23/-
46K5	12/-	9040	12/-	E124	8/8	ECC223	23/-
46L5	12/-	9041	12/-	E125	8/8	ECC224	23/-
46M5	12/-	9042	12/-	E126	8/8	ECC225	23/-
46N5	12/-	9043	12/-	E127	8/8	ECC226	23/-
46O5	12/-	9044	12/-	E128	8/8	ECC227	23/-
46P5	12/-	9045	12/-	E129	8/8	ECC228	23/-
46Q5	12/-	9046	12/-	E130	8/8	ECC229	23/-
46R5	12/-	9047	12/-	E131	8/8	ECC230	23/-
46S5	12/-	9048	12/-	E132	8/8	ECC231	23/-
46T5	12/-	9049	12/-	E133	8/8	ECC232	23/-
46U5	12/-	9050	12/-	E134	8/8	ECC233	23/-
46V5	12/-	9051	12/-	E135	8/8	ECC234	23/-
46W5	12/-	9052	12/-	E136	8/8	ECC235	23/-
46X5	12/-	9053	12/-	E137	8/8	ECC236	23/-
46Y5	12/-	9054	12/-	E138	8/8	ECC237	23/-
46Z5	12/-	9055	12/-	E139	8/8	ECC238	23/-
47A5	12/-	9056	12/-	E140	8/8	ECC239	23/-
47B5	12/-	9057	12/-	E141	8/8	ECC240	23/-
47C5	12/-	9058	12/-	E142	8/8	ECC241	23/-
47D5	12/-	9059	12/-	E143	8/8	ECC242	23/-
47E5	12/-	9060	12/-	E144	8/8	ECC243	23/-
47F5	12/-	9061	12/-	E145	8/8	ECC244	23/-
47G5	12/-	9062	12/-	E146	8/8	ECC245	23/-
47H5	12/-	9063	12/-	E147	8/8	ECC246	23/-
47I5	12/-	9064	12/-	E148	8/8	ECC247	23/-
47J5	12/-	9065	12/-	E149	8/8	ECC248	23/-
47K5	12/-	9066	12/-	E150	8/8	ECC249	23/-
47L5	12/-	9067	12/-	E151	8/8	ECC250	23/-
47M5	12/-	9068	12/-	E152	8/8	ECC251	23/-
47N5	12/-	9069	12/-	E153	8/8	ECC252	23/-
47O5	12/-	9070	12/-	E154	8/8	ECC253	23/-
47P5	12/-	9071	12/-	E155	8/8	ECC254	23/-
47Q5	12/-	9072	12/-	E156	8/8	ECC255	23/-
47R5	12/-	9073	12/-	E157	8/8	ECC256	23/-
47S5	12/-	9074	12/-	E158	8/8	ECC257	23/-
47T5	12/-	9075	12/-	E159	8/8	ECC258	23/-
47U5	12/-	9076	12/-	E160	8/8	ECC259	23/-
47V5	12/-	9077	12/-	E161	8/8	ECC260	23/-
47W5	12/-	9078	12/-	E162	8/8	ECC261	23/-
47X5	12/-	9079	12/-	E163	8/8	ECC262	23/-
47Y5	12/-	9080	12/-	E164	8/8	ECC263	23/-
47Z5	12/-	9081	12/-	E165	8/8	ECC264	23/-
48A5	12/-	9082	12/-	E166	8/8	ECC265	23/-
48B5	12/-	9083	12/-	E167	8/8	ECC266	23/-
48C5	12/-	9084	12/-	E168	8/8	ECC267	23/-
48D5	12/-	9085	12/-	E169	8/8	ECC268	23/-
48E5	12/-	9086	12/-	E170	8/8	ECC269	23/-
48F5	12/-	9087	12/-	E171	8/8	ECC270	23/-
48G5	12/-	9088	12/-	E172	8/8	ECC271	23/-
48H5	12/-	9089	12/-	E173	8/8	ECC272	23/-
48I5	12/-	9090	12/-	E174	8/8	ECC273	23/-
48J5	12/-	9091	12/-	E175	8/8	ECC274	23/-
48K5	12/-	9092	12/-	E176	8/8	ECC275	23/-
48L5	12/-	9093	12/-	E177	8/8	ECC276	23/-
48M5	12/-	9094	12/-	E178	8/8	ECC277	23/-
48N5	12/-	9095	12/-	E179	8/8	ECC278	23/-
48O5	12/-	9096	12/-	E180	8/8	ECC279	23/-
48P5	12/-	9097	12/-	E181	8/8	ECC280	23/-
48Q5	12/-	9098	12/-	E182	8/8	ECC281	23/-
48R5	12/-	9099	12/-	E183	8/8	ECC282	23/-
48S5	12/-	9100	12/-	E184	8/8	ECC283	23/-
48T5	12/-	9101	12/-	E185	8/8	ECC284	23/-
48U5	12/-	9102	12/-	E186	8/8	ECC285	23/-
48V5	12/-	9103	12/-	E187	8/8	ECC286	23/-
48W5	12/-	9104	12/-	E188	8/8	ECC287	23/-
48X5	12/-	9105	12/-	E189	8/8	ECC288	23/-
48Y5	12/-	9106	12/-	E190	8/8	ECC289	23/-
48Z5	12/-	9107	12/-	E191	8/8	ECC290	23/-
49A5	12/-	9108	12/-	E192	8/8	ECC291	23/-
49B5	12/-	9109	12/-	E193	8/8	ECC292	23/-
49C5	12/-	9110	12/-	E194	8/8	ECC293	23/-
49D5	12/-	9111	12/-	E195	8/8	ECC294	23/-
49E5	12/-	9112	12/-	E196	8/8	ECC295	23/-
49F5	12/-	9113	12/-	E197	8/8	ECC296	23/-
49G5	12/-	9114	12/-	E198	8/8	ECC297	23/-
49H5	12/-	9115	12/-	E199	8/8	ECC298	23/-
49I5	12/-	9116	12/-	E200	8/8	ECC299	23/-
49J5	12/-	9117	12/-	E201	8/8	ECC300	23/-
49K5	12/-	9118	12/-	E202	8/8	ECC301	23/-
49L5	12/-	9119	12/-	E203	8/8	ECC302	23/-
49M5	12/-	9120	12/-	E204	8/8	ECC303	23/-
49N5	12/-	9121	12/-	E205	8/8	ECC304	23/-
49O5	12/-	9122	12/-	E206	8/8	ECC305	23/-
49P5	12/-	9123	12/-	E207	8/8	ECC306	23/-
49Q5	12/-	9124	12/-	E208	8/8	ECC307	23/-
49R5	12/-	9125	12/-	E209	8/8	ECC308	23/-
49S5	12/-	9126	12/-	E210	8/8	ECC309	23/-
49T5	12/-	9127	12/-	E211	8/8	ECC310	23/-
49U5	12/-	9128	12/-	E212	8/8	ECC311	23/-
49V5	12/-	9129	12/-	E213	8/8	ECC312	23/-
49W5	12/-	9130	12/-	E214	8/8	ECC313	23/-
49X5	12/-	9131	12/-	E215	8/8	ECC314	23/-
49Y5	12/-	9132	12/-	E216	8/8	ECC315	23/-
49Z5	12/-	9133	12/-	E217	8/8	ECC316	23/-
50A5	12/-	9134	12/-	E218	8/8	ECC317	23/-
50B5	12/-	9135	12/-	E219	8/8	ECC318	23/-
50C5	12/-	9136	12/-	E220	8/8	ECC319	23/-
50D5	12/-	9137	12/-	E221	8/8	ECC320	23/-
50E5	12/-	9138	12/-	E222	8/8	ECC321	23/-
50F5	12/-	9139	12/-	E223	8/8	ECC322	23/-
50G5	12/-	9140	12/-	E224	8/8	ECC323	23/-
50H5	12/-	9141	12/-	E225	8/8	ECC324	23/-
50I5	12/-	9142	12/-	E226	8/8	ECC325	23/-
50J5	12/-	9143	12/-	E227	8/8	ECC326	23/-
50K5	12/-	9144	12/-	E228	8/8	ECC327	23/-
50L5	12/-	9145	12/-	E229	8/8	ECC328	23/-
50M5	12/-	9146	12/-	E230	8/8	ECC329	23/-
50N5	12/-	9147	12/-	E231	8/8	ECC330	23/-
50O5	12/-	9148	12/-	E232	8/8	ECC331	23/-
50P5	12/-	9149	12/-	E233	8/8	ECC332	23/-
50Q5	12/-	9150	12/-	E234	8/8	ECC333	23/-
50R5	12/-	9151	12/-	E235	8/8	ECC334	23/-
50S5	12/-	9152	12/-	E236	8/8	ECC335	23/-
50T5	12/-	9153	12/-	E237	8/8	ECC336	23/-
50U5	12/-	9154	12/-	E238	8/8	ECC337	23/-
50V5	12/-	9155	12/-	E239	8/8	ECC338	23/-
50W5	12/-	9156	12/-	E240	8/8	ECC339	23/-
50X5	12/-	9157	12/-	E241	8/8	ECC340	23/-
50Y5	12/-	9158	12/-	E242	8/8	ECC341	23/-
50Z5	12/-	9159	12/-	E243	8/8	ECC342	23/-
51A5	12/-	9160	12/-	E244	8/8		

The following blueprints are available from stock. Descriptive text is not available but the date of issue is shown for each blueprint. Send, preferably, a postal order to cover cost of the blueprint (stamps over 6d. unacceptable) to Blueprint Department, Practical Wireless, George Newnes Ltd., Tower House, Southampton Street, London, W.C.2.

The Strand Amplifier }	(Oct. 1962)	5/-	The Celeste 7-transistor Portable Radio }	(June 1963)	5/-
The PW Signal Generator }			The Spinette Record Player }		
The Berkeley Loudspeaker Enclosure }	(Dec. 1962)	5/-	Transistor Radio Mains Unit }	(June 1964)	5/-
The Luxembourg Tuner }			7 Mc/s Transceiver }		
The PW Troubadour }	(June 1962)	7/6	The Citizen (December 1961) }		5/-
The PW Everest Tuner }			The Mini-amp (November 1961) }		5/-
The PW Britannic Two }	(May 1962)	6/-	The PT Multimeter (October 1961) PT }		5/-
The PW Mercury Six }			The Beginner's Short Wave Superhet (Dec. 1964) }		5/-
Beginner's Short Wave Two S.W. Listener's Guide }	(Nov. 1963)	5/-	The Empire 7 Three-band Receiver (May 1965) }		5/-
Beginner's 10-watt Transmitter Transmitting and Aerial Data }	(Dec. 1963)	5/-	Electronic Hawaiian Guitar (June 1965) }		5/-
PW "Sixteen" Multirange Meter Test Meter Applications Chart }	(Jan. 1964)	5/-	Progressive SW Superhet (February 1966) }		5/-
			Beginners' 5-Band Receiver }	(Dec. 1966)	5/-
			Home Intercom Unit }		

★ PLEASE NOTE THAT WE CAN SUPPLY NO BLUEPRINTS OTHER THAN THOSE SHOWN IN THE ABOVE LIST. NOR ARE WE ABLE TO SUPPLY SERVICE SHEETS FOR COMMERCIAL RADIO, TV OR AUDIO EQUIPMENT. ★

Before using the query service it is important to read the following notes:

The PW Query Service is designed primarily to answer queries on articles published in the magazine and to deal with problems which cannot easily be solved by reference to standard text books. In order to prevent unnecessary disappointment, prospective users of the service should note that:

(a) We cannot undertake to design equipment or to supply wiring diagrams or circuits, to individual requirements.

(b) We cannot undertake to supply detailed information for converting war surplus equipment, or to supply circuitry.

(c) It is usually impossible to supply information on imported domestic equipment owing to the lack of details available.

(d) We regret we are unable to answer technical queries over the telephone.

(e) It helps us if queries are clear and concise.

(f) We cannot guarantee to answer any query not accompanied by the current query coupon and a stamped addressed envelope.

QUERY COUPON

This coupon is available until 7th April, 1967 and must accompany all queries in accordance with the rules of our Query Service.

PRACTICAL WIRELESS, APRIL 1967



1967 CATALOGUE 200 PAGES PLUS!

COMPLETELY NEW EDITION — HUNDREDS OF NEW LINES


● Contains the largest and most comprehensive range of components and equipment available. Over 5,000 stock lines with more data, more information and illustrations. Hundreds of bargain lines. You cannot afford to be without a copy of this catalogue. Supersedes all previous editions. PRICE 7/6, p.p. 1/-

● 5 FREE VOUCHERS
Total value 10/- for use on purchases. Pay for catalogue after use.

● Unbeatable value — 200 packed pages — 10/- value discount vouchers ●



(4)

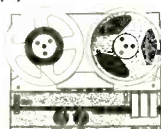

MARRIOT TAPE HEADS
1 Track R/RP/3 Med z. 7/8. R/RP/1 High z. 8/-.
2 Track L/RPS/12 High z 15/-.
L/RPS/7 Med z 19/6. L/ES 9 erase, 12/6.
Also 11 R-RP single track Rec Play Med z 6/6.

DEAC RECHARGEABLE BATTERY
● 9.6 volt 220mA II 20/- p.p. 1/6
DEAC CHARGER
To charge 3.6 volt and 9.6 volt packs.
Fully mains isolated **45/-** P.P. 2/-
in moulded case.

(1)



(4) **BUILD A QUALITY 2 OR 4 TRACK TAPE RECORDER**
3-speed version using '363' decks
● TWO-TRACK. Deck £10.10.0. Martin Amplifier. £14.19.6. Cabinet and speaker 7 gns. Complete kits with FREE 7in. 1200ft. tape, spare spool **27 gns.** P.P. 15/-
● FOUR-TRACK. Deck £13.10.0. Martin Amplifier. £15.19.6. Cabinet and speaker 7 gns. Complete kits with FREE 7in. 1200ft. tape, spare spool. **30 gns.** P.P. 15/-
Today's Value £50.

(7)



(6) **GARRARD DECKS — BRAND NEW FULLY GUARANTEED**

1000 mono	£5 19 6	SP25 stereo	£10 19 6	401 less cart. Arin	£27 10 0
AT5 mono	£6 9 6	SP25 Stereo	£13 19 6	AT6 mono Mk. II	£8 19 6
2000 mono	£6 9 6	AT60 less cart.	£10 19 6	AT6 stereo Mk. II	£9 10 0
2000 stereo	£6 19 6	AT60 mono	£11 10 0	AT6 Stereo	£11 19 0
3000 1 in stereo	£7 10 0	AT60 stereo	£11 19 6	Decade Mk. II	£17 17 0
SP25 less cart.	£9 19 6	AT60 Stereo	£14 19 6	A70 less cart.	£17 17 0
SP25 mono	£10 10 0	LAB80 less cart.	£25 0 0	(P. and P. 5/- any type)	

All other makes of decks and cartridge in stock. List on request

(8)



(7) **GLOBEMASTER MW/LW/SW PORTABLE RADIO TO BUILD**
Full 3-waveband tuning. Push-button wave-change. Superbet printed circuit design. Black-chromed cabinet 11 x 7 1/4 x 3 1/4 in. (SW 17-50 metres). Ear/Recon sockets. 11 watt Push/Pull output. 6 Mullard Transistors. Booklet on request.
TOTAL COST £7.19.6 P.P. 3/6
TO BUILD

(8)

TOURMASTER TRANSISTOR CAR RADIO
7-Transistor MW/LW Car Radio. 12 volt operated. 3 watt output. Push-button wave-change. RF stage. Supplied built, boxed, ready to use with speaker and battery. Car fitting kit and manufacturers' current guarantee. Special Bargain Offer. Buy Now! Leaflet on request.
List Price 15 gns. **£9.9.0** P.P. 3/6

(5)



VALVE AMPLIFIERS AND TUNERS IN CABINETS
● SA100. 5 + 5 watt. SA200 7 1/2 + 7 1/2 Stereo. 300mV Input. 500V version. Also Inc. FM Tuners, P.U.s, etc. puts for Mag. Mic. O/P 4 to 16 ohms. Mains Mag. P.U.s, etc. optrd **£15.15.0** P.P. 5/-
● AFM 100. AM/FM tuner to match SA100. etc. self-powered mains **£30** P.P. 7/6
● AFM 200. AM/FM tuner to match SA200 **£30** P.P. 7/6
5/- (AFM 100 and 200 may be used with any amplifier)

(6)



Complete range of hi-fi equipment in stock. Demonstration room open. Latest stock list on request. Special prices.

SUPPLIERS OF QUALITY COMPONENTS AND EQUIPMENT FOR MORE THAN 20 YEARS.

NEW! STEREO TAPE PLAYER FOR CARS 32 gns.

Mono version 28 gns. and F.M./Med. wave/Long wave Car Radio 25 gns. Leaflet on request.

TUNNEL DIODES

1mA 22/8; 5mA 15/-; 15mA 12/6. Brand new at fraction of normal price. Free Specs. supplied.

TRANSISTOR CATALOGUE

Completely new 24-page 1967 edition. Hundreds of new types with details. The largest range available. Send 1/- for your copy.

INVERTOR KITS

12 volt input, output 230 volts a/c approx. 5a/a. Transistorised designs.
● 15 watt 6/7.6, p.p. 3/6
● 40 watt 9/7.6, p.p. 6/6

REGENT-6 MW/LW POCKET RADIO TO BUILD

6-Transistor superbet. Geared tuning. Push-pull speaker output. Moulded cabinet 5 x 3 x 1 1/4 ins. Phone socket.
TOTAL COST 69/6 P.P. 2/-
TO BUILD

TINY TONE RADIO CONTROL

Miniature 27 Mc/s band, Radio Control Receiver. Size only 2 x 2 x 1/2 in. Sensitive 4 transistor design. Complete building instructions.
TOTAL COST 55/- P.P. 1/6
TO BUILD

WE CAN SUPPLY FROM STOCK MOST OF THE PARTS SPECIFIED ON CIRCUITS IN THIS MAGAZINE. SEND LIST FOR QUOTATION. OR BETTER STILL BUY THE NEW 1967 CATALOGUE. EVERYTHING YOU NEED IS LISTED.

"EXPLORER" (P.W. Jan. 1967) MW/VHF Receiver. All parts as specified (less chassis, etc.). 79/6. P.P. 2/6. Parts list on request.

HENRY'S RADIO LTD.

303 EDGWARE RD., LONDON. W.2
PA Ddington 1008/9 (ST1) 01-723-1008
Open Mon. to Sat. 9-6. Thurs. 1 p.m.
Open all day Saturday

★ MAYFAIR PORTABLE ELECTRONIC ORGAN

Build the World's first All-Transistor Portable Electronic Organ Kit

- Plug-in printed circuits ● 170 transistors and devices ● 10 selected tone colours
- Fully sprung keyboard ● Vibrato ● 6 Octaves of generators ● Simple locked-in tuning ● 110/250 volt mains unit ● Cabinet size 30 1/2" x 15 1/2" x 9"
- Weight 35lb. Cabinet with detachable legs, music stand and foot swell pedal
- Fully detailed building manual with photos, drawings and full circuits.

TO BUILD YOURSELF IN EASY STAGES.
ALL PARTS SOLD SEPARATELY.

Detailed leaflet
on request

Acclaimed
by everyone

DESIGNED BY
L. W. ROCHE



START BUILDING FOR AS LITTLE AS £5. BUILD THE MAYFAIR A SECTION AT A TIME.

- TRANSISTORISED REVERBERATION UNIT. For use with any organ or audio amplifier. 18 gns. p.p. 5/-

- ★ COMPLETE KIT 99 GNS. (CARR. 30/-).
- ★ HP FACILITIES AVAILABLE.
- ★ COMPLETE RANGE OF ORGAN COMPONENTS IN STOCK.

● SEE FOR YOURSELF
CALL IN FOR
DEMONSTRATION

SEE PAGE 967 FOR
FURTHER RANGE
OF STOCK ITEMS

Britain's best-selling hi-fi transistorised units 12 and 25 watt systems, test equipment, AM and FM tuners, etc. The new 1967 catalogue (see above) contains details and illustrations of hundreds of other stock lines. Order your copy now!