


# RADIO & ELECTRONICS CONSTRUCTOR

Vol. 26 No. 7

FEBRUARY 1973


20p

## TRANSMITTER-RECEIVER

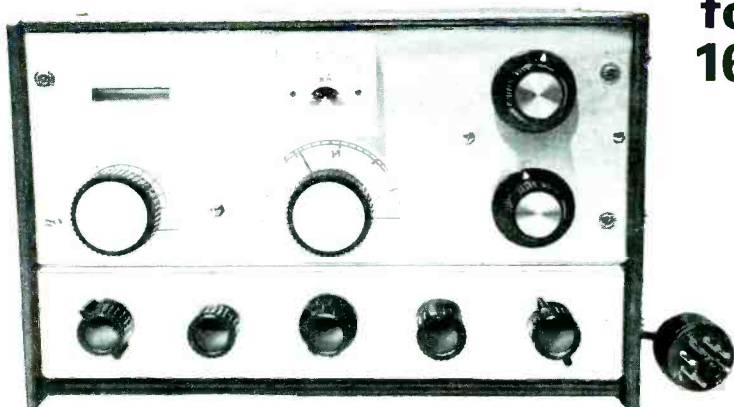

for  
160m

## TRANSISTOR CURVE TRACER

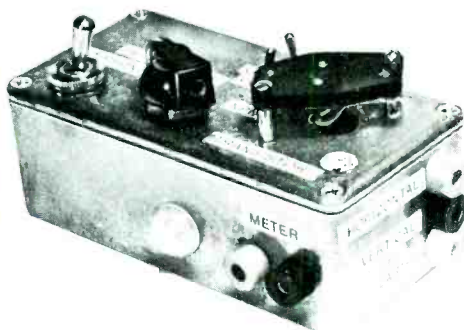

**ALSO  
FEATURED**

**BUILDING H. T. SUPPLIES**



**Each £3 unit of Home Unit Insurance gives you protection up to the limit shown**

This is the simplified insurance you have been waiting for. Not just cover on the contents of your home but a package of personal protection you and your family need. And it's how we save you so much money: just ONE policy to issue instead of nine! You can build up to the cover you need by additional units

(or 1/2 units after the first) up to a maximum of five. So simple. So easy. Apply to your Broker, Agent or local office of a General Accident company. The Home Unit Policy can replace your existing insurances. And remember - as you buy more possessions just add more Home Units at any time.

**THE GENERAL ACCIDENT FIRE & LIFE ASSURANCE CORPORATION LTD**

Metropolitan House, 35 Victoria Avenue,  
Southend-on-Sea, Essex, SS2 6BT

It pays to be protected by a **General Accident** company

Please send me further particulars of the Home Unit Insurance.

Name.....

Address.....

20/9468

# THE MODERN BOOK CO

## 110 THYRISTOR PROJECTS using SCRS and TRIACS

by R. M. Marston

£1.40

Postage 10p

**Electronic Music Production**  
by A. Douglas £2.75 Postage 12p

**HAM Radio A Beginner's Guide**  
by R. H. Warring £1.60 Postage 10p

**Radio, T.V. & Audio Test Instruments**  
by Gordon J. King £3.80 Postage 15p

**Making & Repairing Transistor Radios**  
by W. Oliver £1. Postage 12p

**Transistorized Radio Control For Models**  
by D. W. Aldridge £2.50 Postage 12p

**Servicing with the Oscilloscope**  
by Gordon J. King £1.80 Postage 12p

**Practical Integrated Circuits**  
by A. J. McEvoy 90p Postage 10p

**Electronics & Radio**  
by M. Nelkon £1.80 Postage 20p

**VHF-UHF Manual**  
by G. R. Jessop £1.60 Postage 15p

**50 Photoelectric Circuits & Systems**  
by P. S. Smith £1.30 Postage 6p

**How to Listen to the World**  
by J. M. Frost £1.90 Postage 10p

**HI-FI, P.A., Guitar & Discotheque Amplifier Design Handbook**  
by B. B. Babani 75p Postage 5p

**Transistor Audio & Radio Circuits**  
by Mullard £1.80 Postage 12p

**HI FI Year Book 1973**  
by IPC £1.50 Postage 20p

**Radio Technician's Bench Manual**  
by H. W. Hellyer £3 Postage 15p

**RSGB Amateur Radio Call Book 1973**  
by RSGB 60p Postage 6p

**Amateur Radio Techniques**  
by Pat Hawker £1.60 Postage 15p

**Radio Valve & Transistor Data**  
by A. M. Ball 75p Postage 12p

We have the Finest Selection of English and American Radio Books in the Country  
**19-21 PRAED STREET (Dept RC) LONDON W2 1NP**  
 Telephone 01-723 4185



### LOUDSPEAKER BARGAINS

Fane Pop 100 watt 18" 8/15 ohm	£19.50
Fane Pop 60 watt 15" 8/15 ohm	£11.15
Fane Pop 50 watt 12" 8/15 ohm	£ 9.25
Fane Pop 25/2 12 25 watt 8/15 ohm	£5.40
Fane Pop 15 12" 10 watt 8/15 ohm	£4.00
Baker Group 25 12" 3.8 or 15 ohm	£6.80
Baker Group 35 12" 3.8 or 15 ohm	£8.00
Celestion PS8 for Unilix	£2.35
EMI 13 x 8, 3.8 or 15 ohm	£2.25
EMI 13 x 8, 3.8 or 15 ohm	£2.80
EMI 13 x 8 twin/tw, 3.8 or 15 ohm	£3.60
EMI 13 x 8 type 350 15 watt 8 ohm	£8.00
Richard Allan 8" 3.8, or 15 ohm	£2.35
Richard Allan 12" dual cone 3 or 15 ohm	£2.50
Fane 8" d/cone 808T 8 or 15 ohm	£2.85
Fane 8" d/cone, roll surround, 807T 8 or 15 ohm	£3.50
Elac 9 x 5, 59RM109 15 ohm	£2.70
Elac 9 x 5, 59RM114 8 ohm	£2.70
Elac 6 1/2" dual cone 8 ohm	£2.25
Elac 6 1/2" d/cone, roll surround 8 ohm	£3.50
Elac 4" tweeter 8 ohm	£1.50
Crossover for above (p & p free)	£1.50
Goodmans 8" 8 or 15 ohm	£4.75
Goodmans 10P 8 or 15 ohm	£5.25
Goodmans 12P 8 or 15 ohm	£10.50
Goodmans 15P 8 or 15 ohm	£17.00
Goodmans 18P 8 or 15 ohm	£27.00
2" 2 1/2" or 3" 80 ohm	£1.65
Phillips 5" 8 ohm	£1.95
7 x 4 or 8" x 5", 3 or 8 ohm	£1.80
10" x 6" 3.8 or 15 ohm	£2.00

FREE with orders over £6.00 "HiFi loudspeaker enclosures" book.

All units guaranteed new and perfect.

Prompt despatch. P & P 25p per speaker.

Send for our free booklet "Choosing a speaker".

**WILMSLOW AUDIO**  
(Dept. RC)

10 Swan St., Wilmslow,  
SK9 1HF, Cheshire

### Vary the strength of your lighting with a DIMMASWITCH



The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The white mounting plate of the DIMMASWITCH matches modern electric fittings. Two models are available, with the bright chrome knob controlling up to 300 w or 600 w of all lights except fluorescents at mains voltages from 200-250 v, 50Hz. The DIMMASWITCH has built-in radio interference suppression:

600 Watt £3.20. Kit Form £2.70  
300 Watt £2.70. Kit Form £2.20

All plus 10p post and packing.  
Please send C.W.O. to:

**DEXTER & COMPANY**  
7 ULVER HOUSE, 19, KING STREET,  
CHESTER CH1 2AH. Tel: 0244-25883.  
As supplied to H.M. Government Departments.

### SAVE TIME AND MONEY

LIST PRICE £6.25

OUR PRICE £4.94



As supplied by us to SCHOOLS, TECHNICAL COLLEGES, SHOPS, OFFICES AND INDUSTRY. Silver grey stove enamelled steel cabinet with 48 transparent styrene drawers fitted with moulded handles and label slots. Dividers can be supplied at an extra charge to enable each drawer to be sub-divided into six compartments. Transparent drawers allow swift selection of components at a glance and eliminates duplication of stock. A really first class time saving unit. Size of cabinets 21" x 11 1/2" x 6 1/2". Size of drawers 6 1/2" x 2 1/2" x 1 1/2". Other sizes available. Callers welcome Mon-Sat. 9 a.m.-1 p.m. 2 p.m.-6 p.m. NEW as illustrated OUR PRICE ONLY £4.94 plus 35p carriage on orders less than £10. Money back guarantee. SEND FOR FREE COLOUR BROCHURE.

### TRADE AIDS

(DEPT RC5) 111 CHILTERN DRIVE,  
BERRYLANDS, SURBITON, SURRY

01-389 4383

100 yds. Berrylands Railway Station

# Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—you learn the *practical way.*

Learn basic Radio and Electronics at home - the fast, modern way. Give yourself essential technical 'know-how' - like reading circuits, assembling standard components, experimenting, building - quickly and without effort, and enjoy every moment. B.I.E.T.'s simplified study method and the remarkable **TECHNATRON** Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

and what's more, you will understand exactly what you are doing. The **TECHNATRON** Outfit contains everything you need, from tools to transistors - even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.

**You LEARN - but it's as fascinating as a hobby.**

Among many other interesting experiments, the Radio set you build - and it's a good one - is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the springboard for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this course - but it teaches the real thing. The easy to understand, practical projects - from a burglar-alarm to a sophisticated Radio set - help you master basic Radio and Electronics - even if you are a 'non-technical' type. And, if you want to make it a career, B.I.E.T. has a fine range of courses up to City and Guilds standards.

### Specialist Booklet

If you wish to make a career in Electronics, send for your **FREE** copy of "NEW OPPORTUNITIES". This brand new booklet - just out - tells you all about **TECHNATRON** and B.I.E.T.'s full range of courses.



## FREE

### BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. BRE 2 ALDERMASTON COURT, READING RG7 4PF  
Accredited by the Council for the Accreditation of Correspondence Colleges.

**POST THIS COUPON FOR FREE BOOK**

CL BRE 2

NAME..... AGE.....  
(BLOCK CAPITALS)

ADDRESS.....

.....


.....

SUBJECT OF INTEREST.....

410

**NOW AVAILABLE . . .  
LATEST  
BOUND VOLUME  
No. 25  
of**

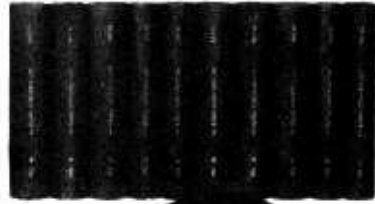**"The Radio Constructor"  
FOR YOUR LIBRARY**



Comprising  
768 pages  
plus index

AUGUST 1971  
to JULY 1972

**PRICE £2.00 P. and P. 28p**

**BOUND VOLUME NO. 23  
(August 1969 to July 1970)**

**BOUND VOLUME NO. 24  
(August 1970 to July 1971)**

Limited number of these volumes still available.

### PRICES

Volume 23 £1.88 P. & P. 28p

Volume 24 £2.00 P. & P. 28p

We regret all earlier volumes are now completely sold out.

Available only from

**DATA PUBLICATIONS LTD.,  
57 MAIDA VALE, LONDON, W9 1SN**

RADIO & ELECTRONICS CONSTRUCTOR

# THIS IS THE FIRST PAGE OF THE GREAT BI-PAK SECTION

## BRAND NEW FULLY GUARANTEED DEVICES

AC 107	20p AD 149	50p BC 143	30p BD 131	50p BF 179	30p C 444	35p 2G 301	2N 1613	20p 2N 2926(R)	10p 2N 3906	27p
AC 113	20p AD 161	33p BC 145	45p BD 132	60p BF 180	30p C 450	22p 2G 302	2N 1711	32p 2N 3010	10p 2N 4058	12p
AC 115	23p AD 162	33p BC 147	10p BD 133	65p BF 181	30p MAT 100	19p 2G 303	2N 1890	45p 2N 3011	70p 2N 4059	10p
AC 117K	20p AD 161 and	30p BC 148	10p BD 135	40p BF 182	40p MAT 101	20p 2G 304	19p 2N 1893	37p 2N 3053	17p 2N 4061	12p
AC 122	12p AD 162(MP)	55p BC 149	12p BD 136	40p BF 183	40p MAT 120	19p 2G 306	2N 2147	72p 2N 3054	44p 2N 4062	12p
AC 125	17p ADT 140	50p BC 150	18p BD 137	45p BF 184	25p MAT 121	20p 2G 308	2N 2148	57p 2N 3055	50p 2N 4284	17p
AC 126	17p AF 114	24p BC 151	20p BD 138	50p BF 185	30p MPF 102	42p 2G 309	2N 2160	60p 2N 3391	14p 2N 4285	17p
AC 127	17p AF 115	24p BC 152	17p BD 139	55p BF 188	40p MPF 104	37p 2G 319	2N 2192	35p 2N 3391A	16p 2N 4286	17p
AC 128	17p AF 116	24p BC 153	20p BD 140	60p BF 194	13p MPF 105	37p 2G 339A	2N 2193	35p 2N 3392	14p 2N 4287	17p
AC 132	14p AF 117	24p BC 154	30p BD 155	80p BF 195	13p OC 19	35p 2G 344	2N 2217	22p 2N 3394	14p 2N 4289	17p
AC 134	14p AF 118	35p BC 157	18p BD 175	60p BF 196	14p OC 20	63p 2G 345	2N 2218	20p 2N 3395	17p 2N 4290	17p
AC 137	14p AF 124	30p BC 158	12p BD 176	60p BF 197	14p OC 22	38p 2G 371	2N 2219	20p 2N 3402	21p 2N 4291	17p
AC 141	14p AF 125	25p BC 159	12p BD 177	65p BF 200	45p OC 23	12p 2G 371B	2N 2220	22p 2N 3403	21p 2N 4292	17p
AC 141K	17p AF 126	28p BC 160	45p BD 178	65p BF 222	95p OC 24	56p 2G 373	2N 2221	20p 2N 3404	28p 2N 4293	17p
AC 142	17p AF 127	28p BC 161	50p BD 179	70p BF 257	45p OC 25	38p 2G 374	2N 2222	20p 2N 3405	42p 2N 5172	12p
AC 142K	17p AF 139	30p BC 167	12p BD 180	70p BF 258	60p OC 26	25p 2G 377	2N 2368	17p 2N 3414	15p 2N 5457	32p
AC 151	15p AF 178	50p BC 168	12p BD 185	65p BF 259	85p OC 28	50p 2G 378	2N 2369	14p 2N 3415	15p 2N 5458	32p
AC 154	20p AF 179	50p BC 169	12p BD 186	65p BF 262	55p OC 29	50p 2G 381	2N 2369A	14p 2N 3416	28p 2N 5459	40p
AC 155	20p AF 180	50p BC 170	12p BD 187	70p BF 263	55p OC 35	42p 2G 382	2N 2411	24p 2N 3417	28p 25 301	50p
AC 156	20p AF 181	45p BC 171	14p BD 188	70p BF 270	50p OC 36	50p 2G 401	2N 2412	24p 2N 3525	75p 25 302A	42p
AC 157	24p AF 186	45p BC 172	14p BD 189	75p BF 271	30p OC 41	24p 2G 414	2N 2646	47p 2N 3646	9p 25 302	42p
AC 165	20p AF 239	37p BC 173	14p BD 190	75p BF 272	80p OC 42	24p 2G 417	2N 2711	21p 2N 3702	10p 25 303	55p
AC 166	20p AL 102	65p BC 174	14p BD 195	85p BF 273	15p 2N 388	55p 2N 388	2N 2712	21p 2N 3703	10p 25 304	70p
AC 167	20p AL 103	65p BC 175	22p BD 196	85p BF 274	35p OC 45	12p 2N 388A	2N 2714	21p 2N 3704	11p 25 305	84p
AC 168	24p ASY 26	25p BC 177	19p BD 197	90p BF 274	60p OC 70	10p 2N 404	2N 2904	20p 2N 3705	10p 25 306	84p
AC 169	14p ASY 27	30p BC 178	19p BD 198	90p BF 29	27p OC 71	10p 2N 404A	2N 2904A	21p 2N 3706	9p 25 307	84p
AC 176	20p ASY 28	25p BC 179	19p BD 199	95p BF 84	23p OC 72	14p 2N 524	2N 2905	21p 2N 3707	11p 25 321	56p
AC 177	24p ASY 29	25p BC 180	24p BD 200	95p BF 85	30p OC 74	14p 2N 527	2N 2905A	21p 2N 3708	7p 25 322	42p
AC 178	28p ASY 50	25p BC 181	24p BD 205	80p BF 86	23p OC 75	15p 2N 598	2N 2906	15p 2N 3709	9p 25 322A	42p
AC 179	28p ASY 51	25p BC 182	10p BD 206	80p BF 87	24p OC 76	15p 2N 599	2N 2906A	18p 2N 3710	9p 25 323	56p
AC 180	17p ASY 52	25p BC 182L	10p BD 207	95p BF 88	23p OC 77	25p 2N 696	2N 2907	20p 2N 3711	70p	20p
AC 181	20p ASY 54	25p BC 183	10p BD 208	95p BF 50	20p OC 81	15p 2N 697	2N 2907A	22p 2N 3819	28p 25 325	70p
AC 181K	17p ASY 55	25p BC 183L	10p BD 209	£1.00 BF 51	20p OC 81D	15p 2N 698	2N 2923	14p 2N 3820	50p 25 326	70p
AC 181K	20p ASY 56	25p BC 184	12p BF 115	24p BF 52	20p OC 82	15p 2N 699	2N 2924	14p 2N 3821	35p 25 327	70p
AC 187	22p ASY 57	25p BC 184L	12p BF 117	45p BF 53	17p OC 82D	15p 2N 706	2N 2925	14p 2N 3822	28p 25 301	42p
AC 187K	20p ASY 58	25p BC 186	28p BF 118	70p BFX 25	85p OC 83	20p 2N 706A	2N 2926(G)	12p 2N 3903	28p 40361	46p
AC 188	22p ASZ 21	40p BC 187	28p BF 119	70p BFX 19	15p OC 84	20p 2N 708	2N 2926(Y)	11p 2N 3904	30p 40362	45p
AC 188K	20p BC 107	9p BC 207	11p BF 121	45p BFX 20	15p OC 139	20p 2N 711	2N 2926(O)	10p 2N 3905	28p	
AC 17	25p BC 108	9p BC 208	11p BF 123	50p BFX 25	15p OC 140	20p 2N 717				
AC 18	20p BC 109	10p BC 209	12p BF 125	45p BFX 26	15p OC 169	25p 2N 718				
AC 19	20p BC 113	10p BC 212L	11p BF 127	50p BFX 27	15p OC 170	25p 2N 718A				
AC 20	20p BC 114	15p BC 213L	11p BF 152	55p BFX 28	15p OC 171	25p 2N 726				
AC 21	20p BC 115	15p BC 214L	14p BF 153	45p BFX 29	15p OC 200	25p 2N 727				
AC 22	16p BC 116	15p BC 225	25p BF 154	45p BFX 30	18p OC 201	28p 2N 743				
AC 27	18p BC 117	15p BC 226	35p BF 155	70p BFX 39	18p OC 202	28p 2N 744				
AC 28	19p BC 118	10p BCY 30	24p BF 156	48p BFX 40	28p OC 203	25p 2N 914				
AC 29	35p BC 119	30p BCY 31	26p BF 157	55p BFX 41	28p OC 204	25p 2N 918				
AC 30	28p BC 120	80p BCY 32	30p BF 158	55p BFX 95	12p OC 205	35p 2N 929				
AC 31	18p BC 125	12p BCY 33	22p BF 159	60p BFX 95A	13p OC 209	40p 2N 930				
AC 34	21p BC 126	18p BCY 34	25p BF 160	45p BFX 38	20p 2N 1131	20p BA 154				
AC 35	21p BC 132	12p BCY 70	14p BF 162	40p C 111E	50p P 397	42p 2N 1132				
AC 36	28p BC 134	18p BCY 71	18p BF 163	40p C 400	30p OCP 71	43p 2N 1302				
AC 40	17p BC 135	12p BCY 72	14p BF 164	40p C 407	25p ORP 12	43p 2N 1303				
AC 41	18p BC 136	15p BCY 10	20p BF 165	40p C 424	20p ORP 60	40p 2N 1304				
AC 44	35p BC 137	15p BCZ 11	25p BF 167	23p C 435	50p ORP 61	40p 2N 1305				
AD 130	38p BC 139	40p BCZ 12	25p BF 173	22p C 426	35p ST 140	12p 2N 1306				
AD 140	48p BC 140	30p BD 121	60p BF 176	35p C 428	20p ST 141	17p 2N 1307				
AD 142	48p BC 141	30p BD 123	65p BF 177	35p C 441	30p TIS 43	30p 2N 1308				
AD 143	38p BC 142	30p BD 124	60p BF 178	30p C 442	30p UT 46	27p 2N 1309				

## DIODES & RECTIFIERS

50p AA 119	8p BY 130	16p OA 47	7p
80p AA 120	8p BY 133	10p OA 70	7p
80p AA 129	8p BY 164	50p OA 79	7p
30p AA 30	9p BYX 38 30	42p OA 81	7p
20p AAZ 13	10p BYZ 10	30p OA 85	9p
14p BA 100	10p BYZ 11	30p OA 90	6p
30p BA 116	21p BYZ 12	30p OA 91	6p
21p BA 126	22p BYZ 13	25p OA 95	7p
14p BA 148	14p BYZ 16	40p OA 200	6p
12p BA 154	12p BYZ 17	35p OA 202	7p
22p BA 155	14p BYZ 18	35p SD 10	5p
14p BA 156	13p BYZ 19	SD 19	5p
14p BY 100	15p CG 62	IN 34	7p
17p BY 101	12p (Eq) OA 91	5p IN 34A	7p
9p BYX 105	17p CG 651 (Eq)	IN 914	6p
21p BY 114	12p OA 70-OA79	6p IN 916	4p
21p BY 126	14p OA 5	35p IN 414B	6p
23p BY 127	15p OA 5L	21p IS 021	10p
15p OA 10		35p IS 951	6p

Cut these 3 pages out and keep for reference

### NEW COMPONENT PAK BARGAINS

Pack No.	Qty.	Description	Price
C 1	250	Resistors mixed values approx. count by weight	0.50
C 2	200	Capacitors mixed values approx. count by weight	0.50
C 3	50	Precision Resistors .1%, .01% mixed values	0.50
C 4	75	1/4 W Resistors mixed preferred values	0.50
C 5	5	Pieces assorted Ferrite Rods	0.50
C 6	2	Tuning Gangs. MW/LW VHF	0.50
C 7	1	Pack Wire 50 meters assorted colours	0.50
C 8	10	Reed Switches	0.50
C 9	3	Micro Switches	0.50
C 10	15	Assorted Pots & Pre-Sets	0.50
C 11	5	Jack Sockets 3—3.5m 2 — Standard Switch Types	0.50
C 12	40	Paper Condensers preferred types mixed values	0.50
C 13	20	Electrolytics Trans. types	0.50
C 14	1	Pack assorted Hardware — Nuts/Bolts, Gromets, etc.	0.50
C 15	4	Mains Toggle Switches, 2 Amp D/P	0.50
C 16	20	Assorted Tag Strips & Panels	0.50
C 17	10	Assorted Control Knobs	0.50
C 18	4	Rotary Wave Change Switches	0.50
C 19	3	Relays 6 — 24V Operating	0.50
C 20	4	Sheets Copper Laminate approx. 10" x 7"	0.50

Please add 10p post and packing on all component packs, plus a further 10p on pack Nos. C1, C2, C19, C20. Component Lists for mail order available on request.

### JUMBO COMPONENT PAKS MIXED ELECTRONIC COMPONENTS Exceptionally good value


Resistors, capacitors, pots, electrolytics and coils plus many other useful items. Approximately 3lbs in weight. Price incl. P. & £1.50 only

### BRAND NEW POST OFFICE TYPE TELEPHONE DIALS

ONLY 35p each
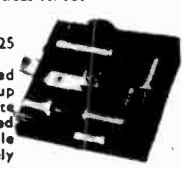
### THE NEW S.G.S. EA 1000 AUDIO AMP MODULE Guar. 3 Watts RMS. Module Tested and Guaranteed.

Qty. 1—9 £2.63; 10—25 £2.28. Price each. Larger quantities quoted on request. Full hook-up diagrams and complete technical data supplied free with each module or available separately at 10p each.



## SYSTEM 12 STEREO

Each kit contains two amplifier modules, 3 Watts RMS, two loudspeakers, 15 OHMS, The pre-amplifier, transformer, power supply module, front panel and other accessories as well as an illustrated stage-by-stage instruction booklet designed for the beginner. Further details available on request.



ONLY **£16.95** FREE P & P

# NOW-TURN OVER FOR MORE FANTASTIC OFFERS

# The largest selection

**NEW LOW PRICE TESTED S.C.R.'S.**

PIV	1A	3A	5A	5A	7A	10A	16A	30A
705	7066	7066	7064	7048	7048	7048	7048	7048
50	0.23	0.25	0.35	0.35	0.47	0.50	0.53	£1.15
100	0.35	0.33	0.47	0.47	0.50	0.58	0.63	£1.40
200	0.35	0.37	0.49	0.49	0.57	0.61	0.75	£1.60
400	0.43	0.47	0.56	0.56	0.67	0.75	0.83	£1.76
600	0.53	0.57	0.68	0.68	0.77	0.97	£1.26	—
800	0.63	0.70	0.86	0.86	0.90	£1.30	£1.50	£4.00

**SILICON RECTIFIERS—TESTED**

PIV	300mA	750mA	1A	1.5A	3A	10A	30A
50	0.04	0.05	0.05	0.07	0.14	0.21	0.80
100	0.04	0.06	0.05	0.13	0.16	0.23	0.75
200	0.06	0.09	0.06	0.14	0.20	0.24	1.00
400	0.06	0.13	0.07	0.20	0.27	0.37	1.25
600	0.07	0.16	0.10	0.23	0.34	0.45	1.80
800	0.10	0.17	0.11	0.25	0.37	0.55	2.00
1000	0.11	0.25	0.14	0.30	0.46	0.83	2.50
1200	—	0.33	—	0.38	0.67	0.75	—

**TRIACS**

VBOM	3A	6A	10A
TO-1	TO-18	TO-18	TO-18
5p	5p	5p	7p
100	30	50	76
200	50	60	90
400	70	75	110

**FULL RANGE OF ZENER DIODES**

**VOLTAGE RANGE**  
 3-33V 400mV (DO-7 case) 15p ea. 15W (Top Hat) 15p ea. 10W (80-10 Stud) 15p ea. All fully tested 5% tol. and marked. Stale voltage required.

**DIACS**

FOR USE WITH TRIACS

BR100 (D32) 37p each

**FREE**

One 50p Pak of your own choice free with orders valued £4 or over.

**BRAND NEW TEXAS INSTRUMENTS**

Coded and Guaranteed

Pak No.	EQVT
T1	8 2C3713
T2	8 1D1374
T3	8 1D1216
T4	8 2N3817
T5	8 2N3827
T6	8 2N3448
T7	8 2N3458
T8	8 2N3378
T9	8 2N399A
T10	8 2C6417

All 50p each pak

**CADMIUM CELLS**

ORP12 45p

ORP60, ORP61 40p each

**GENERAL PURPOSE NPN SILICON SWITCHING TRANS.** TO-18 SIM. TO 2N706/8, BSY27/28-95A. All usable devices to open or short circuits ALSO AVAILABLE in PNP Sim. to 2N2906/BCV70. When ordering please state preference NPN or PNP.

Ep 100 For 1.75  
 20 For 0.50 500 For 7.50  
 50 For 1.00 1000 For 16.00

**100VCB MIXIE DRIVER TRANSISTOR.** 9m. BRX21 & C407. 2N1993 FULLY TESTED AND CODED ND 120. 1-24 17p each. TO 5 NPN. 25 up 15p each.

**SIL. G.P. DIODES 5p**

300mW	30	0.60
40PIV (Min.)	100	1.50
Sub-Min.	600	0.80
Full Tested	1,000	0.90

Ideal for Organ Builders.

**POWER TRANS BONANZA!**

**GENERAL PURPOSE GERM. PNP**

Coded GP100. BRAND NEW TO-3 CASE. P088. REPLACER: OC23-28-29-30-35-36. NKT 401-403-404-406-408-410-412-413. T13027-3099. 2N2504. 2N458A-457A-458A. 2N611 A & B. 2G290-222. ETC. VCB0 80V VCB0 50V IC 10A FT. 30 WATTs Rtc 30-170.

1-24 25-99 100 up  
 45p each 50p each 35p each

**SILICON High Voltage 250V NPN TO-3 case. G.P. Switching & Amplifier Applications. Brand new Coded R 2400 VCB0 260V/CEO 100/IC 6A/30 Watta. HFE type 20/IT 5MHZ. OUR PRICE EACH:**

1-24 25-99 100 up  
 50p 45p 30p

**ADI61/ADI62 NPN**

M/P COMP. GERM TRANS. OUR LOWEST PRICE OF 55p PER PAIR.

**SILICON 50 WATTs MATCHED PNP/PNP BIP 19 NPN TO-3 Plastic. BIP 20 PNP. Brand new.**

1-24 25-99 100  
 90p 55p 50p

## KING OF THE PAKS Unequaled Value and Quality

### SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak. or money back.

Pak No.	Ep
U1	120 Glass Sub-Min. General Purpose Germanium Diodes
U2	60 Mixed Germanium Transistors AF/RF
U3	75 Germanium Gold Bonded Sub-Min. like OA5, OA47
U4	40 Germanium Transistors like OC81, AC128
U5	60 300mA Sub-Min. Silicon Diodes
U6	30 Sil. Planar Trans. NPN like BSY96A, 2N706
U7	16 Sil. Rectifiers Top-Hat 750mA Vltg. Range up to 1,000 50p
U8	60 Sil. Planar Diodes DO-7 Glass 250mA like OA200/202
U9	20 Mixed Voltages, 1 Watt Zener Diodes
U10	20 BA Y6 charge storage Diodes DO-7 Glass
U11	26 PNP Sil. Planar Trans. TO-5 like 2N1132, 2N2904
U12	12 Silicon Rectifiers Epoxy 500 mA up to 800 PIV
U13	30 PNP-NPN Sil. Transistors OC200 and 2S 104
U14	160 Mixed Silicon and Germanium Diodes
U15	26 NPN Sil. Planar Trans. TO-5 like BSY61, 2N697
U16	10 5Amp Silicon Rectifiers Stud Type up to 1,000 PIV
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22
U18	6 6Amp Silicon Rectifiers BY213 Type up to 600 PIV
U19	25 Silicon NPN Transistors like BC106
U20	12 1.5Amp Silicon Rectifiers Top-Hat up to 1,000 PIV
U21	30 AF Germanium Alloy Transistors 2G300 Series & OC71
U22	30 MDT's like MHz Series PNP Transistors
U23	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV
U24	26 300 MHz NPN Silicon Transistors 2N708, BSY27
U25	30 Fast Switching Silicon Diodes like IN914 Micro-Min.
U26	12 NPN Germanium AF Transistors TO-1 like AC127
U27	10 1Amp SCR's TO-5 can. up to 600 PIV CR51 25-600
U28	15 Plastic Silicon Planar Trans. NPN 2N2926
U29	20 Sil. Planar Plastic NPN Trans. Low Noise Amp 2N3707
U30	20 Zener Diodes 500mW DO-7 case 3-18 volts mixed
U31	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series
U32	30 Silicon PNP Alloy Trans. TO-5 BCY6 25302/4
U33	25 Silicon Planar Transistors PNP TO-18 2N2906
U34	26 Silicon Planar NPN Transistors TO-5 BSY60/51/52
U35	30 Silicon Alloy Transistors SO-2 PNP OC200, 25322
U36	30 Fast Switching Silicon Trans. NPN 400 MHz 2N8011
U37	30 RF. Germ. PNP Transistors 2N1308/5 TO-5
U38	10 Dual Transistors 6 lead TO-5 2N2060
U39	26 VHF Germanium Transistors TO-5, OC45, NKT72
U40	10 RFP Germanium PNP Transistors TO-1 NKT867, AP117
U41	25 Sil. Trans. Plastic TO-18 A F BC113/114
U42	30 Sil. Trans. Plastic TO-5 BC118/NPN
U43	7 3A SCR. Toss up to 600 PIV

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

**SILICON PHOTO TRANSDUCER.** TO-18 Lens end NPN 8im to BP 25 and P21. BRAND NEW. Full data available. Fully guaranteed. Qty. 1-24 25-99 100 up Price each 45p 40p 25p

**F.E.T.'S**

2N3819	50p
2N3820	50p
2N3821	50p
2N3823	50p
2N5488	50p
2N5489	50p
BFW 10	50p
MPP100	50p

**NEW EDITION 1971 TRANSISTOR EQUIVALENTS BOOK.** A complete cross reference and equivalent book for European, American and Japanese Transistors. Exclusive to BI-PAK 90p each. Red cover edition.

**A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX STOCK SEND FOR FREE LIST.**

VCBO 100V/CEO 50/IC 10A. HFE type 100/ft 3mHZ. OUR PRICE PER PAIR:

1-24 25-99 100  
 90p 55p 50p

## QUALITY TESTED SEMICONDUCTORS

Pack Description	Price 4
Q1	20 Red spot transistors PNP
Q2	16 White spot R.F. transistors PNP
Q3	4 OC 75 type transistors
Q4	6 Matched transistors OC44/45/81/81D
Q5	4 OC 75 transistors
Q6	5 OC 72 transistors
Q7	4 AC 128 transistors PNP high gain
Q8	4 AC 128 transistors PNP
Q9	7 OC 81 type transistors
Q10	7 OC 71 type transistors
Q11	2 AC 127/128 Comp. pairs PNP/NPN
Q12	3 AF 116 type transistors
Q13	3 AF 117 type transistors
Q14	3 OC 171 R.F. type transistors
Q15	7 2N2926 Sil. Epoxy trans. md colours
Q16	2 GE7880 low noise Germ. trans.
Q17	5 NPN 2 x ST 141 and 3 x ST 140
Q18	4 MDT's 2 x MAT 100 & 2 x MAT 120
Q19	3 MDT's 2 x MAT 101 & 1 x MAT 121
Q20	4 OC 44 Germanium transistors A.F.
Q21	4 AC 127 NPN Germanium transistors
Q22	20 NKT transistors A. F. R. coded
Q23	10 OA 202 Silicon diodes sub-min.
Q24	8 OA 81 diodes
Q25	15 IN914 Silicon diodes 75PIV 75mA
Q26	8 OA96 Germanium diodes sub-min
Q27	2 10A 600 PIV Sil. rectifiers IS425R
Q28	2 Silicon power rectifiers BYZ 13
Q29	4 Silicon trans. 2 x 2N696, 1 x 2N697, 1 x 2N698
Q30	7 Sil. switch transistors 2N706 NPN
Q31	6 Sil. switch transistors 2N708 NPN
Q32	3 PNP Sil. trans. 2x2N1131, 1x2N1132
Q33	3 Silicon NPN Transistors 2N1711
Q34	7 Sil. NPN trans 2N2399, 500MHz (code P387)
Q35	3 Sil. PNP TO-5, 2x2N2904 & 1x2N2905
Q36	7 2N3646 TO-18 plastic 300 MHz NPN
Q37	3 2N3053 NPN Silicon transistors
Q38	7 PNP trans. 4 x 2N3703, 3 x 2N3702
Q39	7 PNP trans. 4 x 2N3704, 3 x 2N3705
Q40	7 PNP trans. 4 x 2N3707, 3 x 2N3708
Q41	3 Plastic NPN TO-18 2N3904
Q42	6 NPN transistors 2N5172
Q43	7 BC107 NPN transistors
Q44	7 NPN trans. 4 x BC 108, 3 x BC 109
Q45	3 BC 113 NPN TO-18 transistors
Q46	7 BC107 NPN TO-5 transistors
Q47	6 NPN high gain trans 3 x BC167, 3 x BC168
Q48	4 BCY 70 PNP transistors TO-18
Q49	4 NPN trans 2 x BSY61, 2 x BSY62
Q50	7 BSY 26 NPN switch trans. TO-18
Q51	7 BSY 95A NPN trans. 300MHz
Q52	8 BY100 silicon rectifiers
Q53	25 Sil. & germ. trans md all mktd new £1.50

## ELECTRONIC SLIDE RULE

The MK Slide Rule, designed to simplify electronic calculations features the following scales—  
 Conversion of Frequency and Wavelength. Calculation of L, C and of tuned circuits. Reactance and self inductance. Area of circles. Volume of cylinders. Resistance of conductors. Weight of conductors. Decibel calculations. Angle functions. Natural Logs. & 'e' functions. Multiplication & division. Squaring, cubing and square roots. Conversion of kW and Hp.  
 A must for every electronic engineer and enthusiast. Size 23cm x 4 cm, complete with case and instructions. PRICE EACH: £3.35

## DTL & TTL INTEGRATED CIRCUITS

### INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Out" which include Functional and part Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about IC's and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
UIC00	12 x 7400	50p	UIC46	5 x 7446	50p	UIC86	5 x 7486	50p
UIC01	12 x 7401	50p	UIC47	5 x 7447	50p	UIC90	5 x 7490	50p
UIC02	12 x 7402	50p	UIC48	5 x 7448	50p	UIC91	5 x 7491	50p
UIC03	12 x 7403	50p	UIC50	12 x 7450	50p	UIC92	5 x 7492	50p
UIC04	12 x 7404	50p	UIC51	12 x 7451	50p	UIC93	5 x 7493	50p
UIC05	12 x 7405	50p	UIC53	12 x 7453	50p	UIC94	5 x 7494	50p
UIC06	8 x 7406	50p	UIC54	12 x 7454	50p	UIC95	5 x 7495	50p
UIC07	8 x 7407	50p	UIC60	12 x 7460	50p	UIC96	5 x 7496	50p
UIC10	12 x 7410	50p	UIC70	8 x 7470	50p	UIC100	5 x 74100	50p
UIC13	8 x 7413	50p	UIC72	8 x 7472	50p	UIC121	5 x 74121	50p
UIC20	12 x 7420	50p	UIC73	8 x 7473	50p	UIC141	5 x 74141	50p
UIC30	12 x 7430	50p	UIC74	8 x 7474	50p	UIC151	5 x 74151	50p
UIC40	12 x 7440	50p	UIC75	8 x 7475	50p	UIC154	5 x 74154	50p
UIC41	5 x 7441	50p	UIC76	8 x 7476	50p	UIC199	5 x 74199	50p
UIC42	5 x 7442	50p	UIC80	5 x 7480	50p	UIC199	5 x 74199	50p
UIC43	5 x 7443	50p	UIC81	5 x 7481	50p	UIC X1	25 Assmt.	—
UIC44	5 x 7444	50p	UIC82	5 x 7482	50p	74's	£1.50	
UIC45	5 x 7445	50p	UIC83	5 x 7483	50p			

Packs cannot be split, but 25 assorted pieces (our mix) is available as PAK UIC X1.

**BI-PAKS NEW COMPONENT SHOP NOW OPEN WITH A WIDE RANGE OF ELECTRONIC COMPONENTS AND ACCESSORIES AT COMPETITIVE PRICES 18, BALDOCK STREET (A10), WARE, HERTS. TEL: 61593. OPEN MON. - SAT. 9.15 a.m. to 6 p.m. FRIDAY UNTIL 8 p.m.**

All Mail Orders please add 10p post and packing. Send all Orders to Bi-Pak P.O. Box 6, Ware, Herts.

# -the lowest prices!

## 74 Series T.T.L. I.C.'S

Bi-Pak Still Lowest in Price.  
Full Specification Guaranteed.  
All Famous Manufacturers.




	1	35	100		1	35	100
SN7400	0.15	0.14	0.12	SN7490	0.67	0.64	0.58
SN7401	0.15	0.14	0.12	SN7491	0.03	0.06	0.30
SN7402	0.15	0.14	0.12	SN7492	0.67	0.64	0.58
SN7403	0.15	0.14	0.12	SN7493	0.67	0.64	0.58
SN7404	0.15	0.14	0.12	SN7494	0.77	0.74	0.68
				SN7495	0.77	0.74	0.68
SN7406	0.15	0.14	0.12	SN7496	0.87	0.84	0.78
SN7408	0.35	0.31	0.28	SN7400	1.55	1.60	1.55
SN7409	0.35	0.31	0.28	SN7404	0.97	0.94	0.98
SN7410	0.15	0.14	0.12	SN7405	0.97	0.94	0.88
SN7411	0.35	0.31	0.28	SN7407	0.40	0.38	0.36
SN7412	0.29	0.26	0.24	SN7410	0.55	0.53	0.50
SN7416	0.43	0.40	0.38	SN7411	1.25	1.15	1.10
SN7417	0.43	0.40	0.38	SN7418	1.00	0.96	0.90
SN7420	0.15	0.14	0.12	SN7419	1.35	1.25	1.10
SN7422	0.50	0.48	0.45	SN7412	1.40	1.30	1.10
SN7423	0.50	0.48	0.45	SN7423	2.20	2.20	2.20
SN7425	0.50	0.48	0.45	SN7441	0.67	0.64	0.58
SN7427	0.45	0.42	0.40	SN7445	1.50	1.40	1.30
				SN7490	1.00	1.00	1.00
SN7428	0.70	0.65	0.60	SN7451	1.00	0.96	0.90
SN7430	0.15	0.14	0.12	SN7453	1.20	1.10	1.00
SN7432	0.40	0.38	0.35	SN7454	1.30	1.20	1.10
SN7433	0.80	0.75	0.70				
SN7437	0.65	0.62	0.60	SN7455	1.40	1.30	1.20
SN7438	0.64	0.62	0.60	SN7456	1.40	1.30	1.20
SN7440	0.15	0.14	0.12	SN7457	1.90	1.80	1.70
SN7441	0.65	0.64	0.63	SN7460	1.90	1.70	1.60
				SN7461	1.80	1.70	1.60
SN7442	0.67	0.64	0.58				
SN7443	1.30	1.25	1.20	SN7462	1.40	1.35	1.30
SN7444	1.30	1.25	1.20	SN7463	1.70	1.65	1.60
SN7445	1.80	1.77	1.75	SN7464	1.20	1.15	1.10
SN7446	0.97	0.94	0.88	SN7465	1.20	1.15	1.10
SN7447	1.10	0.97	0.96	SN7466	1.25	1.20	1.15
SN7448	1.10	0.97	0.96	SN7466	1.30	1.25	1.20
SN7450	0.15	0.14	0.12	SN7474	1.20	1.20	1.20
				SN7475	1.50	1.50	1.50
SN7451	0.15	0.14	0.12	SN7476	1.50	1.50	1.50
SN7453	0.15	0.14	0.12				
SN7454	0.15	0.14	0.12	SN7477	2.50	2.40	2.30
SN7460	0.15	0.14	0.12	SN7480	2.00	1.90	1.80
SN7470	0.29	0.26	0.24	SN7481	2.50	2.50	2.50
SN7472	0.29	0.26	0.24	SN7482	2.00	1.90	1.80
SN7473	0.37	0.35	0.32	SN7484	2.50	2.25	2.00
SN7474	0.37	0.35	0.32	SN7485	1.90	1.80	1.80
SN7475	0.45	0.43	0.42	SN7486	1.90	1.80	1.80
SN7476	0.40	0.38	0.38	SN7489	1.90	1.80	1.80
				SN7490	1.00	1.00	1.00
SN7480	0.67	0.64	0.58	SN7493	2.00	1.90	1.80
SN7481	1.20	1.15	1.10	SN7494	2.30	2.20	2.10
SN7482	0.87	0.86	0.85	SN7495	2.00	1.90	1.80
SN7483	1.10	1.06	0.96	SN7496	1.90	1.70	1.60
SN7484	1.10	0.96	0.90	SN7498	1.80	1.70	1.60
SN7485	1.30	1.25	1.20	SN7499	1.80	1.70	1.60
SN7486	0.32	0.31	0.30	SN7499	2.50	2.50	2.50
SN7488	1.50	1.50	1.50	SN7499	2.50	2.50	2.50
SN7489	1.50	1.50	1.50				

## BI-PAK DO IT AGAIN!


### 50Wpk 25w (RMS)

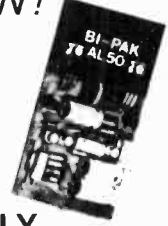0.1% DISTORTION  
HI-FI AUDIO AMPLIFIER  
THE AL50



- ★ Frequency response 15Hz to 100,000 - 1dB. **ONLY £3.25p each**
- ★ Load - 3, 4, 8 or 16 ohms.
- ★ Distortion - better than 0.1% at 1KHz.
- ★ Signal to noise ratio 80dB.
- ★ Supply voltage 10 - 35 Volts.
- ★ All over size 63mm x 105mm x 13mm.

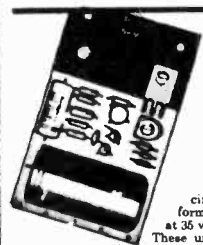Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and ALSO was conceived to fill the need for all your A.F. amplification needs. FULLY BUILT - TESTED - GUARANTEED.



## STABILISED POWER MODULE SPM80

AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (rms) per channel, simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 62mm x 106mm x 30mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including: Diaco Systems, Public Address, Intercom Units etc. Handbook available 15p. PRICE £2.95

## TRANSFORMER BMT80 £1.95 p. & p. 25p.

### STEREO PRE-AMPLIFIER, TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise MPN devices for use in the input stages. Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.



**SPECIFICATION**  
Frequency Response 20Hz - 20KHz ± 1dB  
Harmonic Distortion better than 0.1%  
Inputs: 1. Tape Head 1.25 mV into 50KΩ  
2. Radio, Tuner 35 mV into 50KΩ  
3. Magnetic P.U. 1.5 mV into 50KΩ  
All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within ± 1dB, from 20Hz to 20KHz.  
Base Control ± 15dB @ 20Hz Treble Control ± 15dB @ 20KHz  
Filters: Rumble (High Pass) 100Hz  
Scratch (Low Pass) 8KHz  
Signal/Noise Ratio better than - 65dB  
Input overload + 26dB Supply + 35 volts @ 20mA  
Dimensions 29mm x 82mm x 30mm Price £11.95

## SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 and 1 PA100 ONLY £23.00 FREE p & p.

All prices quoted in new pence. GPO No 388 700B  
Please send all orders direct to warehouse and despatch department

## LINEAR I.C.'S— FULL SPEC.

## LOGIC DTL 930 SERIES I.C.'S

### ROCK BOTTOM PRICES

Type No.	1-24	25-99	100 up
BP 201C—SL201C	63p	55p	45p
BP 701C—SL701C	63p	50p	45p
BP 702C—SL702C	63p	50p	45p
BP 702—72702			
	53p	45p	40p
BP 709—72709	36p	34p	30p
BP 709P—JA709C	36p	34p	30p
BP 710—72710	44p	40p	35p
BP 711—JA711	45p	45p	40p
BP 741—72741	75p	60p	50p
	32p	30p	24p
TA A283	70p	60p	55p
TA A283	90p	75p	70p
TA A350	170p	150p	150p

Type No.	1-24	25-99	100 up
BP930	11p	10p	10p
BP932	11p	10p	10p
BP933	11p	10p	10p
BP935	11p	10p	10p
BP936	11p	10p	10p
BP944			
	18p	15p	11p
BP946	25p	24p	20p
BP948	11p	10p	10p
BP948	35p	30p	25p
BP951	65p	60p	50p
BP962	11p	10p	10p
BP963	40p	35p	30p
BP964	40p	35p	30p
BP967	40p	35p	30p
BP969	40p	35p	30p

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series only).

## NUMERICAL INDICATOR TUBES



MODEL	CD66	GR 116	3015F
Anode voltage (Vdc)	170 min	175 min	5
Cathode current (mA)	2.3	14	
Numeral height (mm)	16	13	9
Tube height (mm)	47	32	22
Tube diameter (mm)	19	13	12
I.C. driver rec.	BP41 or 141	BP41 or 141	BP47
PRICE EACH	£1.70	£1.55	£1.90

All indicators 0.9 + Decimal point: All side viewing: Full data for all types available on request.

## RTL MICROLOGIC CIRCUITS

	1-24	25-99	100 up
Epoxy TO-5 case			
uL900 Buffer	85p	85p	87p
uL914 Dual 2/1/p			
gate	85p	85p	87p
uL923 J-K flip-flop	85p	85p	87p
Data and Circuits Booklet for IC's			
Price 7p.			

## DUAL IN LINE SOCKETS

Prof. Type No.	1-24	25-99	100 up
TSO14 pin type	30p	27p	25p
TSO16 pin type	35p	32p	30p
Low Cost No.			
BPS 14	15p	13p	11p
BPS 16	15p	14p	12p

# BI-PAK

P.O. BOX 6, WARE - HERTS

Postage and packing add 10p. Overseas add extra for airmail.  
Minimum order 50p. Cash with order please.  
Guaranteed Satisfaction or Money Back

# COMPONENTS

HOBBYIST - AMATEUR - DOMESTIC SURPLUS - INDUSTRIAL - BULK OFFERS

JUST A FEW OF OUR BARGAINS ARE LISTED BELOW - PAY US A VISIT OR SEND STAMPED ADDRESSED ENVELOPE FOR A QUOTE ON YOUR REQUIREMENTS

## VALVE BASES

Chassis or printed circuit B9A - B7G	3p
Chassis UX7 - B5 - UX5 - B9G	3p
Shrouded chassis B7G - B9A	4p
Octal chassis	4p
B8A chassis	5p
B12A tube base	3p

## TAG STRIP

6 way	2p	Single	1p
-------	----	--------	----

1 1/4 glass fuses— 250 m/a or 3 amp (box of 12)	6p
3" tape spools	4p
FX2236 Ferrox Cores	5p
PVC or metal clip on M.E.S. bulb holder	3p
All metal equipment Phono plug	2p
Bulgin, 5mm Jack plug and switched socket (pair)	20p
12 volt solenoid and plunger	25p
250 RPM 50 c/s locked frequency miniature mains motor	50p
200 OHM coil, 1 1/4" long, hollow centre	10p
Relay, P.O. 3000 type, 1,000 OHM coil, 4 pole c/o R.S. 12 way standard plug and shell	60p
	50p

## SWITCHES

Pole	Way	Type	
4	2	Sub. Min. Slide	10p
6	4		
1	11	} Wafer Rotary	12p each
4	3		
3	7		
2	5		
1	3		
1	3	+ off Sub. min. edge	10p
1	3	13 amp small rotary	12p
2	2	Locking with 2 to 3 keys	£1.50
2	1	2 Amp 250V A.C. rotary	20p
2	1	Toggle	10p

## VALVES - NEW AND BOXED

DY86	44p	EM87	90p	PL84	46p
EB91	26p	EL84	36p	PY81	40p
ECC82	36p	EY86	46p	PY82	42p
ECC83	36p	EZ80	30p	PY88	52p
ECH81	44p	PCC84	50p	UABC80	58p
EABC80	46p	PCC89	62p	UCL82	50p
EBF89	44p	PCF80	38p	UL84	50p
ECL82	44p	PCF82	50p	UY85	42p
ECL86	56p	PCL82	38p	UM84	32p
EF80	36p	PCL84	50p	UCH81	44p
EF85	44p	PCL85	64p	6BA6	26p
EF86	44p	PCL86	56p		
EF91	52p	PL36	78p	MANY	
EF183	40p	PL81	72p	OTHERS	
EF184	44p	PL83	56p		

## RESETTABLE COUNTER

English Numbering Machines LTD.  
MODEL 4436-159-989

6-14 volt, 6 digit, illuminated, fully enclosed. £2.50

TO3 Mica Washer	2p
3" Standard Tape - Boxed	15p
GP91-1 Cartridge, turnover stylii	65p

## RESISTORS

1/8 - 1/4 watt	1p
1 watt	1 1/2p
Up to 10 watt wire	8p
15 watt wire wound	10p

## SKELETON PRESETS

5K or 500K	3p
------------	----

## SAFETY PINS

Standard size, 10 for 4p

## THORN PTO2E 10-6s CHASSIS SOCKET 40p

5K switched volume control	15p
5K Log Pot	10p
1meg Tandem Pot	15p

## THERMISTORS

VA1055	
VA1066	10p each
VA1077	

## STEEL BOX WITH LID

10 x 5 1/2 x 3" grey hammer finish £1

## RELAY

6 volt, 2 pole c/o heavy duty contacts 50p

## ELECTROLYTICS

Mullard C426, TCC, CRL, HUNTS, STC SUB MINIATURE, ETC.

MFD	Volt	MFD	Volt	
16	50	20	12	} 4p each
260	12	500	6	
50	50	100	25	
100	18	100	6	} 2p each
125	10	6	3	
8	50	8	6	} 3p
12	20	25	6.4	
10	20	250	18	} 7p
8.2	20	400	16	
50	25	400	40	} 10p
2.5	64	8	500	
25	25	100	200	10p

## CONDENSERS

MFD	Volt	
0.005	500	} 2p each
0.001	1,250	
3.3PF	500	} 3p each
500 PF	500	
2,200PF	500	} 5% 3p each
3,300PF	500	
0.1	350	} 4p each
0.1	500	
0.25	150	} 5p each
0.056		
0.061		} 3p each
0.066		
0.069		} 350V 4p each
0.075		
0.08		} 5p each
0.1	1,500	
0.25	350	} 5p each
0.5	350	
0.22	250	} 75p
0.25	500	

## TUNING GANG

100PF, 50PF, 33PF  
20p each

## TRIMMERS

30PF Beehive	} 10p each
12PF P.T.F.E.	
2,500PF 750V	
33PF MIN. AIR SPACE	

## WIREWOUND POTS

250, 300 OHM, 1K, 4 watt, 10K, 20K, 50K, all at 10p each

## RECORD PLAYER CARTRIDGE

ER.5XME Mono, with turn over stylii, single hole fixing 35p

## GREEN INDICATOR

Takes M.E.S bulb 10p

## CONNECTOR STRIP

Belling Lee L1469, 12 way polythene. 5p each

## CAN CLIPS

1" or 1 3/8" or 3/4" 2p

## T.O.5 HEATSINKS

Style 154 high conductivity 5p

## PAXOLINE

2 3/8 x 4 3/4 x 1/8" or 3 x 2 1/2 x 1/8" 2p

4 3/8 x 1/2 x 3/8" 2 for 1p

220K 3 watt resistors 2p

VALVE RETAINER CLIP, adjustable 2p

## OUTPUT TRANSFORMERS

Sub-miniature Transistor Type 20p

SMALL ORDERS, ENCLOSE SUITABLE STAMPED ADDRESSED ENVELOPE

LARGE ORDERS, ADD SUFFICIENT FOR POSTAGE INSURANCE, ETC

# THE RADIO SHACK

161 ST. JOHNS HILL, BATTERSEA, LONDON S.W.11

Open 10 a.m. till 8 p.m. Monday to Saturday

Phone 01-223 5016



### SEMICONDUCTORS

Full spec. marked by Mullard, etc. Many other types in stock

AC127 .. 10p	AF117 .. 14p	8SV64 .. 40p
AC187 .. 14p	AF178 .. 40p	2N706 .. 8p
AC188 .. 14p	BC107/8/9 .. 7p	2N2219 .. 20p
AD149 .. 35p	BD131 .. 40p	2N2401 .. 15p
AD161 .. 27p	BD132 .. 50p	2N2904 .. 17p
AD162 .. 27p	BD135 .. 25p	2N2905 .. 21p
Matched pair .. 50p	BFY52 .. 10p	2N3055 .. 35p
AF116 .. 14p	BCY40 .. 25p	2N3503 .. 15p

### BRIDGE RECTIFIERS

Amp	Volt		Amp	Volt			
½	1,600	BYX10	30p	2	30	LT120	30p
1	140	OSH01-200	30p	0.6	6-110	EC433	
1.4	42	BY164	35p	Encapsulated with built-in heat sink .. 15p			

Plastic types

### 1 AMP RECTIFIERS

IN4002	100 volt	4p
IN4003	200 volt	5p
IN4004	400 volt	7p
IN4005	600 volt	9p
IN4006	800 volt	10p
IN4007	1,000 volt	15p

### OPTO ELECTRONICS

ORP12	43p	BPX29 Photo transistor	80p
BPX40	25p		
BPX42	£1		
BPY10	75p		
BPY68	75p	CQ11B Infra red transmitter	£4
BPY69	£1		
BPY77	75p		

Diodes

### THYRISTORS

Amp	Volt		
1	400	CRS1/40	30p
1	240	BTX18-200	30p
1	240	BTX30-200	30p
5.6	700	BT106	85p
6.5	300	BT102-300R	42p
6.5	500	BT102-500R	60p
6.5	500	BT107	90p
6.5	500	BT108	90p
6.5	500	BT101-500R	68p
6.5	500	BT109-500R	90p
20	600	BTW92-600RM	£3.00
15	800	BTX95-800R Pulse Modulated	£12

### TRIACS

Amp	Volt		
6	400	BT110-400 Plastic	75p
25	900	BTX94-900	£6.50
25	1200	BTX94-1200	£9

DIAC BRI00 .. 30p

PHOTO SILICON CONTROLLED SWITCH  
BPX66 PNP 10 amp .. £1

### HIGH POWER RECTIFIERS

	Amp	Volt	
BYX38-1200	2.5	1,200	30p
BYX49-600	2.5	600	25p
BYX48-1200	6	1,200	60p
BYX42-300	10	300	40p
BYX20-200	25	200	35p
BYX52-1200	40	200	£2

### F.E.T.'s

BFW10	40p
BSV79	90p
BSV80	80p
N. Channel	
BSV81 M.O.S.T.	£1

### PAPER BLOCK CONDENSER

0.25MFD	800 volt	30p
1MFD	400 volt	15p
2MFD	250 volt	20p
2MFD	1.5 kv	50p
15MFD	150 volt	25p

### WIREWOUND SLIDER

150 Ohm, 250 Ohm 5K  
4p each

### INDICATORS

12 volt red or mains neon amber, push fit round, chrome bezel  
15p each

N50 ohm free plug (UG21D/U) .. 50p

N50 ohm square socket (UG58 A/U) .. 50p

1" Terryclips, black plastic coated, or chrome finish .. 4p

Cinch 10-way terminal block .. 15p

Pair of LA2407 Ferroxc cores with adjuster .. 25p

Chrome Car Radio facia .. 15p

Rubber Car Radio gasket .. 10p

DLI Pal Delayline .. £2

Relay socket  
Take miniature 2PCO relay .. 12p

B9A valve can .. 2p

0-30 in 5 segments, black pvc, 360° dial, silver digits, self adhesive, 4½" dia. .. 15p

Phillips Iron Thermostat .. 15p

Bulgin 2-pin flat plug and socket .. 10p

McMurdo PP108 8 way edge plug .. 15p

300 ohm moving coil insert 4103D 1½" diameter. Make ideal mike or speaker for communication work .. 25p

8 way Cinch standard 0.15 pitch edge socket .. 20p

U.E.C.L. 10 way pin connector 2B6000 OA1P10 .. 20p

U.E.C.L. 20 way pin connector 2A60000A1P20 .. 30p

U.E.C.L. 10 way pin socket 2B606001R10 .. 20p

U.E.C.L. 20 way pin socket 2B60800A1R20 .. 30p

Rotor with neon indicator, as used in Seafarer. Pacific, Fairway depth finders .. 20p each

100MFD 250/275V electrolytic can .. 20p

### DEE PLUG

McMurdo DA15P 15 way chassis plug .. 20p

Fairway 18009 Coax. socket .. 5p

### TIE CLIPS

Nylon self locking 3½" 1p; 7" 2p

### CINCH 160

12 way edge socket .. 10p

### UNMARKED - TESTED

AC128	6p	OC44	6p
ACY17-20	8p	OC71	6p
BC179	10p	OC72	6p
BCY30-34	10p	OC200-5	6p
BY127	8p	2N2926	5p
BZY88 series	6p	Germanium diode	3p
OA200-5	6p		

SMALL ORDERS, ENCLOSE SUITABLE STAMPED ADDRESSED ENVELOPE

LARGE ORDERS, ADD SUFFICIENT FOR POSTAGE, INSURANCE, ETC.

# THE RADIO SHACK

161 ST. JOHNS HILL, BATTERSEA, LONDON S.W.11

Open 10 a.m. till 8 p.m. Monday to Saturday

Phone 01-223 5016

# How to make the digitronic solid-state digital clock using just 30 bits



Full instructions  
in this month's  
issue for versions  
with either four or six figures

And many other constructional  
features, including directions  
for making an electronic maze  
that will keep everyone amused  
for hours. It cost? Around £2

**PLUS**  
**free**  
a 6" x 5" transfer sheet  
of labels for  
audio equipment  
Easy to apply and ideal for an  
impressively professional finish

## PRACTICAL WIRELESS

All in the March issue on sale Feb 2 — price 20p

# BI-PRE-PAK



**COMPLETE TELEPHONES**  
Normal household type as supplied to the Post Office, ex. G.P.O. Only **95p** each. p. & p. 35p each.



**TELEPHONE DIALS**  
Standard Post Office type. Guaranteed in working order.  
**ONLY 25p**  
p. & p. 15p.

## TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries 0.3 to 0.5V 0.5 to 2mA	50p
B79	4	1N4007 Sil. Rec. diodes, 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors, Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors, Approx. quantity, counted by weight	50p
H7	40	Wirewound Resistors, Mixed types and values	50p
H9	2	OC7P1 Light Sensitive Photo Transistor	50p
H28	20	OC200/1/2/3 PNP Silicon uncodded TO-5 can	50p
H38	20	1-Watt Zener Diodes, Mixed Voltages 8.8 - 43V	50p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked	50p
H38	30	Short lead Transistors, NPN Silicon Planar types	50p
H39	10	Integrated Circuits: 6 Gates BMC 962.4 Flip Flops BMC 945	50p
H40	20	BFY50Z, 2N696, 2N1613, NPN Silicon uncodded TO-5	50p

## UNMARKED UNTESTED PACKS

B44	150	Germanium Diodes Min. glass type	50p
B63	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	100	Sil. Diodes sub min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1 2N706A, BS195A, etc.	50p
B1	50	Germanium Transistors PNP, A.F. & R.F.	50p
H6	40	250mW Zener Diodes DO-7 Min. Glass Type	50p
H14	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can	50p
H17	20	3 amp Silicon Stud rectifiers, mixed volts	50p
H15	30	Top Hat Silicon Rectifiers, 750mA, Mixed volts	50p
H16	15	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic, Mixed volts	50p

## MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

**£1 each**



## OVER 1,000,000 TRANSISTORS IN STOCK

We hold a very large range of fully marked, tested and guaranteed Transistors, Power Transistors, Diodes and Rectifiers at very competitive prices. Please send for Free Catalogue.

## 600,000 Silicon Planar Plastic Transistors. Unmarked, untested - Factory clearance. A random sampling showed these to be of remarkably high quality.

Audio PNP, similar to ZTX500, 2N3702/3, BCY 70 etc.

Audio NPN, similar to ZTX300, 2N3708/9, BC168/9 etc.

R.F. NPN and Switching NPN

Please state type of Transistor required when ordering.

ALL AT 500 for £3.00 1,000 for £5.00 10,000 for £40.00

P. & P. 10p/1000

## OUR VERY POPULAR 3p TRANSISTORS

TYPE "A": PNP Silicon alloy, TO-5 can.  
TYPE "B": PNP Silicon, plastic encapsulation.  
TYPE "E": PNP Germanium AF or RF.  
TYPE "F": NPN Silicon plastic encapsulation.  
TYPE "G": NPN Silicon, similar ZTX300 range.  
TYPE "H": PNP Silicon, similar ZTX500 range.

## POWER TRANSISTOR PRICE BREAKTHROUGH!

PLASTIC CASED SILICON POWER TRANSISTORS OF LATEST DESIGN - 40 WATTS and 90 WATTS. PNP & NPN TYPES.  
ALL TYPES AVAILABLE AT THE MOST SHATTERINGLY LOW PRICES OF ALL TIME. ALL ARE FULLY TESTED, MARKED AND GUARANTEED!

40W	NPN	20p	18p	16p
40W	PNP	21p	19p	17p
90W	NPN	24p	22p	20p
90W	PNP	25p	23p	21p

PAK - PACKS of complementary pairs  
MP 40 40W 40W 50p 48p 44p  
MP 90 90W 90W 40p 58p 54p  
Please state if NPN/PNP or NPN/NPN are required



## A CROSS HATCH GENERATOR FOR £3.50 !!!

YES, a complete kit of parts including Printed Circuit Board, A four position switch gives X-hatch, Dot, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This is a project in the September edition of Practical Television.

This complete kit of parts costs £3.50, post paid.

A MUST for Colour T.V. Alignment.

Our famous P1 Pak is still leading in value for money.

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P1, only 50p 10p P & P on this Pak.

## FREE CATALOGUE

FOR TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS.



## 8 RELAYS FOR £1

VARIOUS TYPES P. & P. 25p.

## INTEGRATED CIRCUITS

Clocked Flip Flop	BMC931	20p	18p	16p
Ex. 2/4-input Buffer	BMC932	12p	11p	10p
2/4-input Expander	BMC933	12p	11p	10p
Hex. Inverter	BMC934	12p	11p	10p
Hex. Inverter	BMC935	12p	11p	10p
Hex. Inverter	BMC936	12p	11p	10p
Hex. Inverter	BMC937	12p	11p	10p
Hex. Inverter	BMC940	12p	11p	10p
Hex. Inverter	BMC941	12p	11p	10p
Type D Flip Flop	BMC942	20p	18p	16p
Ex. 2/4-input Power	BMC944	12p	11p	10p
Clocked Flip Flop	BMC945	20p	18p	16p
4/2 Input NAND Gate	BMC946	11p	10p	9p
Clocked Flip Flop	BMC948	20p	18p	16p
4/2 Input NAND Gate	BMC949	12p	11p	10p
Pulsed Trig. Binary	BMC950	20p	18p	16p
Monostable Multivib.	BMC951	25p	23p	21p
Dual J/K Flip Flop	BMC953	20p	18p	16p
Dual J/K Flip Flop	BMC955	20p	18p	16p
Dual J/K Flip Flop	BMC956	20p	18p	16p
Quad 2-input Power	BMC958	12p	11p	10p
2/4-input Gate	BMC961	12p	11p	10p
3-3-input NAND Gate	BMC962	11p	10p	9p
3-3-input NAND Gate	BMC963	12p	11p	10p
Audio Amp 3-watts	SL403D	£1.50	£1.40	£1.36
Linear Op. Amp	709C	25p	20p	15p
Decade Counter	SN7490	65p	60p	55p

LOW COST DUAL IN LINE I.C. SOCKETS  
14 pin type at 15p each. New low low profile type.  
16 pin type at 16p each.

## BOOKS

We have a large selection of Reference and Technical Books in stock. These are just two of our popular lines:  
**B.P.I. Transistor Equivalents and Substitutes:** 40p  
This includes many thousands of British U.S.A., European and C.V. equivalents  
**The Iliffe Radio Valve & Transistor Data Book 9th Edition P & P 21p** 75p  
Characteristics of 3,000 valves and tubes. 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.  
Send for lists of these English publications

Please send me the FREE Bi-Pre-Pak Catalogue

NAME


ADDRESS

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE

# BI-PRE-PAK LTD

DEPT. C, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX, SSO 9DF  
TELEPHONE: SOUTHEND (0702) 46344

# The Catalogue you MUST have!

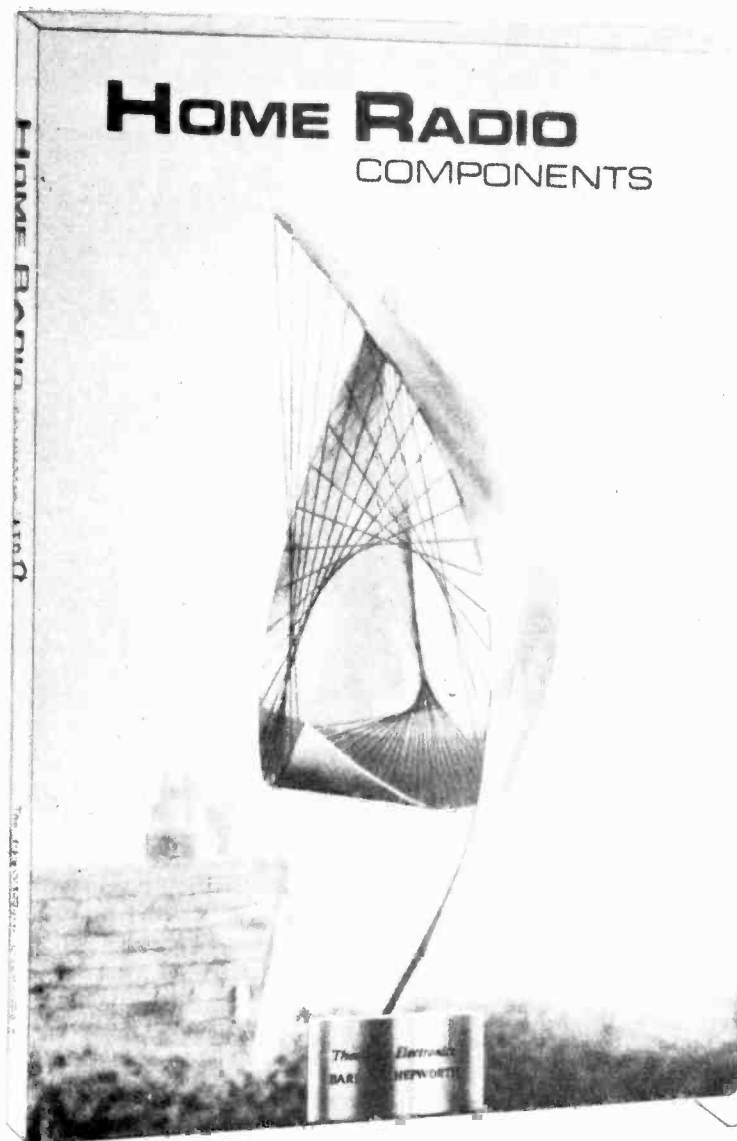

250 pages 11 1/4" x 8 1/4"

6,785 electronic components clearly listed and indexed

1,750 pictures

10 free Vouchers each worth 5p.

Price list regularly updated

Bookmark with useful list of technical abbreviations

*Details of our popular Credit Account Service and our Easy Ordering System are included in the catalogue.*

Only 55p. plus 20p POST AND PACKING

**POST THIS COUPON**  
with cheque or P.O. for 75p.

Name \_\_\_\_\_

Address \_\_\_\_\_



HOME RADIO (Components) LTD.  
Dept. RC, 234-240 London Road, Mitcham CR4 3HD

The price of 75p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

RADIO & ELECTRONICS CONSTRUCTOR

# RADIO & ELECTRONICS CONSTRUCTOR

FEBRUARY 1973

CONTENTS

Vol. 26 No. 7

Published Monthly (1st of Month)

First Published 1947

*Incorporating The Radio Amateur*

*Editorial and Advertising Offices*  
57 MAIDA VALE LONDON W9 1SN

Telephone                      Telegrams  
01-286 6141                      Databux, London

© Data Publications Ltd., 1972. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £2.70 (U.S.A. and Canada \$7.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers please pay by cheque or International Money Order.

*Technical Queries.* We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that such queries cannot be answered over the telephone; they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

*Correspondence* should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

*Opinions* expressed by contributors are not necessarily those of the Editor or proprietors.

*Production.*—Web Offset.

BUILDING H.T. SUPPLIES by F. G. Rayer, Assoc.I.E.R.E., G30GR	420
WINDOWS FOR VIEWING THE UNIVERSE by J. B. Dance, M.Sc.	425
NEWS AND COMMENT	426
TRANSISTOR CURVE TRACER by D. W. Nelson	428
INTEGRATED CIRCUIT OHMMETER (Suggested Circuit 267) by G. A. French	431
NEW PRODUCTS	435
R.F. AMPLIFIER USING DUAL GATE F.E.T. by N. Friel	436
CONSTANT CURRENT LAMP CIRCUIT by L. Stephenson	438
TRANSMITTER-RECEIVER FOR 160 METRES – Part 1 by F. G. Rayer, Assoc. I.E.R.E., G30GR	440
D.C. TO A.C. INVERTER Kit Review	447
SHORT WAVE NEWS by Frank A. Baldwin	448
COMPREHENSIVE TRANSISTOR ANALYSER – Part 2, by H. T. Kitchen	450
CROSSWORD	456
IN YOUR WORKSHOP	457
RADIO TOPICS by Recorder	463
CONSTRUCTOR'S DATA SHEET No. 71 (Coil Data IV)	iii

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London, W9 1SN

The Radio & Electronics Constructor is printed by Carlisle Web Offset.

MARCH ISSUE WILL BE  
PUBLISHED ON MARCH 1st



# BUILDING H.T.

by

F. G. Rayer, Assoc.I.E.R.E., G30GR

**Some notes, with examples, on the design and construction of h.t. supplies. Particular emphasis is placed on supplies for transmitters.**

**S**UPPLIES FOR EQUIPMENT SUCH AS AMPLIFIERS, TUNERS, harmonic markers, transmitters, transceivers and other equipment are often needed. The details given here should enable a supply to be constructed for any purpose, whether it be for a small item such as a tuner, or for small but more powerful equipment such as a Top Band or other transmitter, or for an s.s.b. transmitter.

## HALF-WAVE RECTIFIER

The circuit in Fig. 1 is a good starting point, and is wholly adequate for small valve amplifiers, tuners, harmonic markers, and similar equipment.

T1 is the mains transformer, with a 220V 45mA h.t. winding, and a 6.3V 1.5A heater winding. The silicon or other type of rectifier, D1, provides half-wave rectification. C1 is the reservoir capacitor, L1 the smoothing choke, and C2 the smoothing capacitor. R1 is a bleeder resistor and it discharges the capacitors after switching off.

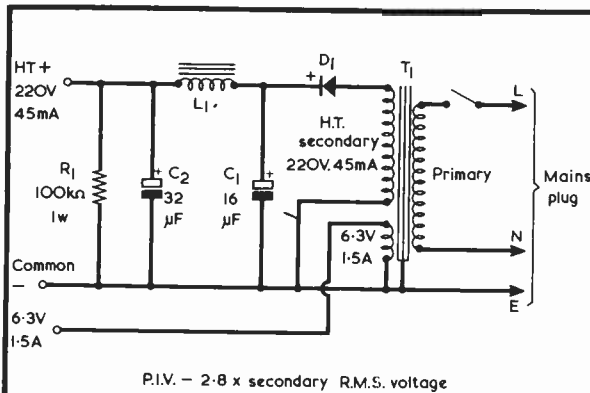


Fig. 1. A supply suitable for small equipment. This half-wave circuit is also employed to illustrate some of the basic concepts of h.t. supplies

Typically, D1 could be a 45mA 250V r.m.s. contact-cooled rectifier, L1 could be a 50mA 10 henry choke, C1 a 16μF 350 V.Wkg. capacitor, and C2 a 32μF 350 V.Wkg. capacitor. However, it is better to consider these items separately, because the points which dictate their minimum ratings will also apply to later circuits.

## TRANSFORMER

A transformer with a half-wave secondary is employed only for small supplies. Other supplies have a full-wave secondary, such as in Figs. 2, 3 and 4. Such a secondary may be rated, as an example, at 250-0-250V 60mA. This means that 250V is available each side of the centre-tap, or 500V across the whole winding, and that the current drawn should not average more than 60mA. Less than the rated current can of course be taken.

The 250-0-250V is the r.m.s. (root mean square) voltage rating, and is that which would be shown if an ordinary testmeter were used to check the voltage. The actual h.t. voltage obtained will depend on factors which are mentioned later. A transformer is chosen which can provide the maximum voltage and current wanted for the equipment being supplied.


Transformers other than small types have a tapped primary, as in Fig. 2. This allows a primary tapping to be used to suit the local mains voltage.

Since, normally, the transformer will provide heater current as well, the heater current ratings of all the valves to be operated should be added together. The total should not exceed the heater winding rating. Larger transformers usually have two or more heater secondaries, as in Fig. 2. The heaters can then be separated into two circuits, each operated from its own winding, as illustrated. Where an h.t. output only is required, the heater windings are left unused.

## RECTIFIERS

Rectifiers sometimes have an r.m.s. rating. A 250V r.m.s. rectifier can be used with any h.t. secondary of not over 250V.

# SUPPLIES

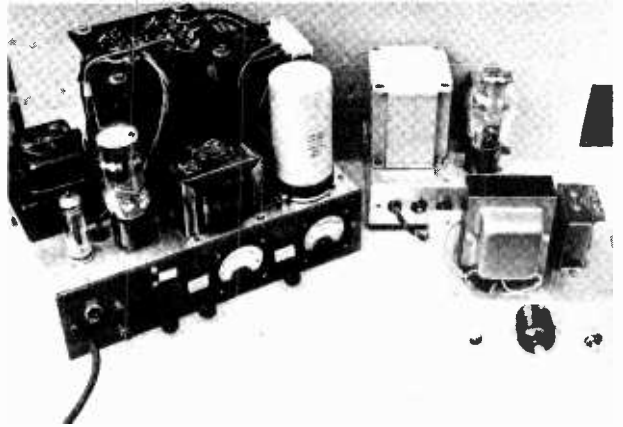

Three typical power supplies. The supply at the left is for powering a transmitter, and it offers 500V at 250mA, 240V at 100mA, 25V negative bias and two outputs of 6.3V at 3A. The pack at back centre is a useful unit made from surplus receiver components and it provides 250V at 60mA and 6.3V at 2.5A. The right-hand unit gives 400V at 100mA, and its front runner carries a neon indicator, octal outlet socket and mains switch

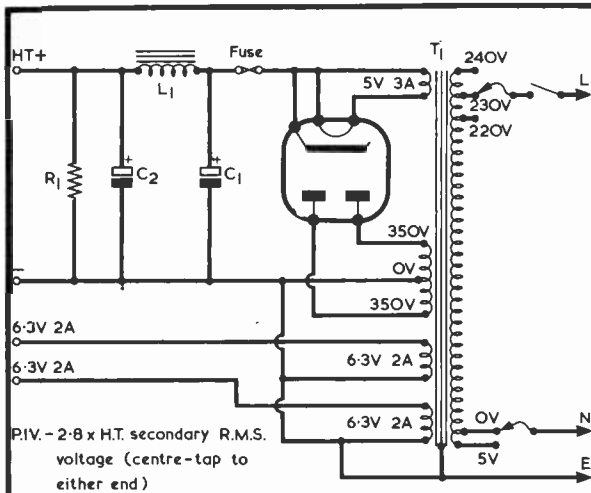


Fig. 2. Typical full-wave rectifier circuit, demonstrating also the use of mains transformer primary taps and the fitting of a fuse



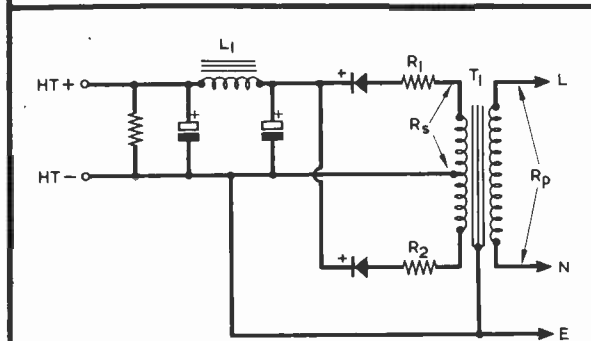


Fig. 3. A full-wave circuit with silicon rectifiers. R1 and R2 are included to increase the effective source resistance

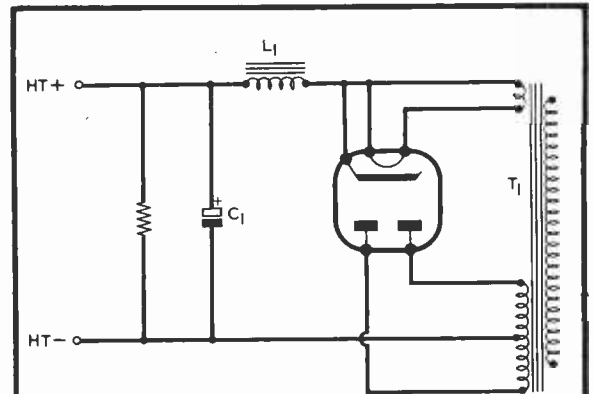

(a)

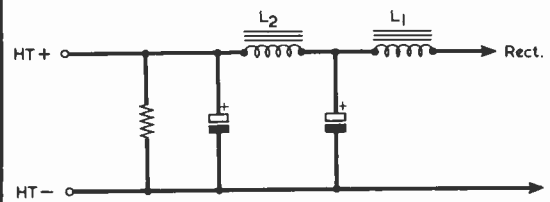

(b)

Fig. 4 (a). A choke input circuit with full-wave valve rectifier  
(b). Adding a further stage of smoothing

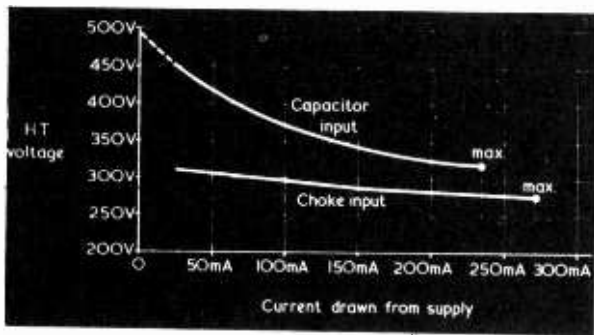


Fig. 5. As may be seen from these curves, which apply to a 5U4G rectifier fed by a 350-0-350V transformer secondary, the choke input circuit offers lower output voltage than the capacitor input circuit, but voltage regulation is better and a higher maximum current can be obtained

More frequently the p.i.v., or peak inverse voltage, rating is given. In Fig. 1, C1 may charge to about 1.4 times the r.m.s. rating of the h.t. secondary, while during negative half-cycles the secondary applies a similar peak voltage of opposite sign to it. The p.i.v. rating of the rectifier should thus be at least 2.8 times the secondary r.m.s. voltage. 800 p.i.v. rectifiers are convenient for 250V, and 1,000 p.i.v. rectifiers for 350V windings.

If silicon rectifiers are used in pairs in series in order to obtain a high overall p.i.v. rating, they should be of the same type and rating, and a resistor of about 470k $\Omega$  must be connected across each to equalise the reverse current and voltage.

The rectified current rating of the rectifier must at least equal the current wanted. Adequately rated silicon rectifiers are easily obtained. With valve rectifiers the valve data can be referred to, if necessary.

### SMOOTHING CAPACITORS

With no load the voltage across the reservoir and smoothing capacitors may rise to about 1.4 times the secondary r.m.s. voltage. Because of this, the capacitors should be rated at 350V Wkg. at least for a 250V secondary, or 500V Wkg. for a 350V secondary. A bleeder resistor can reduce the maximum voltage given when load current is small or zero.

With high voltage supplies, it is often necessary to use capacitors in series, as shown in Fig. 6.

Smoothing is improved by using large value capacitors. However, a large value in the reservoir position increases rectifier peak current. A 16 $\mu$ F component is usually suitable here, whilst less than 8 $\mu$ F is unusual. C2 can be about 8 $\mu$ F to 100 $\mu$ F.

### CHOKE

The current rating of the choke L1 should at least equal the current to be drawn.

Where the current is large or the h.t. voltage must be maintained stable, the choke needs a quite low resistance. Voltage drop, in volts, is equal to current in amps multiplied by resistance in ohms. Thus a 250 $\Omega$  choke passing 100mA would drop 0.1 times 250, or 25V. Under the same circumstances a 100 $\Omega$  choke would drop only 10V.

The choke inductance is commonly about 5 to 10 henrys. When using choke input with a valve rectifier (Fig. 4) the choke inductance should be at least the value specified for the rectifier.

### BLEEDER

The bleeder resistor, R1 in Figs. 1 and 2, can be fitted for safety reasons or the safety factor can be combined with the provision of improved voltage regulation. For the safety application, the resistor can be roughly 500 $\Omega$  per volt - say 100k $\Omega$  to 150k $\Omega$  for a 250V h.t. supply. A carbon resistor of adequate wattage should be employed. On this basis it can be 1 watt for 250V and 2 watts for 350V. The bleeder resistor discharges the reservoir and smoothing capacitors when the power supply is switched off.

If it is to improve voltage regulation, the bleeder resistor is of lower value and draws a larger current. Voltage regulation defines the extent to which the h.t. voltage varies with the current drawn from the supply, and regulation is stated to be good if the voltage change is small. The current drawn by the bleeder resistor is wasted, so this limits the choice of value. As an example, if the resistor draws 20mA and the mains transformer, rectifier and choke are intended to provide 100mA, only 80mA is available for the supplied equipment.


### FULL-WAVE RECTIFICATION

Apart from small supplies, it is usual to employ full-wave rectification. A typical instance is given in Fig. 2. Here, the rectifier is indirectly heated, having its own heater winding.

Some indirectly heated valve rectifiers are designed to allow a high direct voltage to appear between the heater and cathode. This enables the heater to be connected to the same heater winding as the heaters in the supplied equipment, provided that the rectifier cathode-heater voltage rating is at least equal to or greater than the peak h.t. voltage. Directly heated rectifiers, in which the heater is also the cathode, must have their own heater winding.
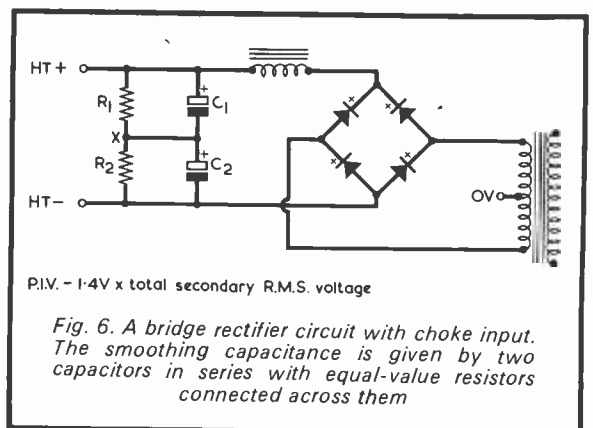
### H.T. FUSE

An h.t. fuse will protect the rectifier and transformer in the case of an h.t. short-circuit, and can be wired in as shown in Fig. 2. The fuse rating should be at



P.I.V. - 1.4V x total secondary R.M.S. voltage

Fig. 6. A bridge rectifier circuit with choke input. The smoothing capacitance is given by two capacitors in series with equal-value resistors connected across them



least equal to the normal current which flows but the rating should not be so low that the fuse blows when switching on. Surge current depends on the value of the reservoir capacitor, the supply resistance offered by the mains transformer secondary, and the rectifier, and it will often be helpful to use an anti-surge type of fuse. A 60mA or 100mA fuse will be satisfactory for small supplies, and 150mA, 250mA or 500mA for large supplies. The fuse may alternatively be connected between the centre-tap of the mains transformer secondary and the negative line.

### H.T. INDICATOR

A 'high tension on' neon indicator is useful as a reminder that voltage is present. It can be wired across the smoothing capacitor. The neon indicator should have an integral series resistor, as present in various lamp assemblies produced for this purpose, or the resistor must be added externally. It can be about 250k $\Omega$  for 250V, and 470k $\Omega$  for 350 to 500V.

An alternative is to fit a mains neon indicator across the primary of the transformer. Or, if a 6.3V winding and spare current are available, a 6.3V indicator lamp can be connected across one heater winding.

With experimental equipment, or a pack intended for some types of modulator or transmitting equipment, it is useful to have a current reading meter in the h.t. positive circuit. This can be a small panel instrument of 100mA, 250mA, or other suitable range, to suit the current drawn.

### MAINS LEAD AND TAPS

In Fig. 2, connections are chosen to suit 220V, 230V or 240V mains. Tappings provided vary. Some larger transformers also have a 5V tapping, thus allowing for 225V, 235V and 245V as well.

Current for the equipment is drawn from a 3-pin plug, and 13A type plugs should be fitted with a 2A or 3A fuse. Use the yellow-green conductor of the cord for Earth, blue for Neutral, and brown for Live, connected as in Fig. 2. (In old cords, green is Earth, red is Live, and black is Neutral.)

### SUPPLY RESISTANCE

If the transformer windings are of very low resistance, the peak rectifier current can be very large. So a minimum supply resistance or impedance is quoted for rectifiers. With circuits like Figs. 1 and 2, this is usually a few hundred ohms, and is provided by the resistance of the transformer windings.

With large, heavy-duty transformers, the windings may have insufficient d.c. resistance to limit peak rectifier current to a value which will not harm the rectifiers. This is particularly the case when using silicon rectifiers because of their low forward resistance. It is then necessary to make up sufficient series resistance by adding resistors R1 and R2, as in Fig. 3.

If the supply impedance needs to be found, measure the transformer\*primary resistance  $R_p$  with a meter, and also the secondary resistance  $R_s$  (from centre-tap

**TABLE**  
**Valve Rectifier Operating Conditions**

Type	Input Capacitor	Input Choke	Secondary r.m.s. voltage (centre-tap to one end)	Minimum Supply resistance	Maximum current
5Z4G	16 $\mu$ F	—	250V	210 $\Omega$	130mA
5Z4G	16 $\mu$ F	—	350V	300 $\Omega$	125mA
5Z4G	16 $\mu$ F	—	500V	435 $\Omega$	80mA
5Z4G	—	2H	350V	—	150mA
5Z4G	—	5H	500V	—	125mA
5U4G	16 $\mu$ F	—	250V	35 $\Omega$	235mA
5U4G	16 $\mu$ F	—	350V	90 $\Omega$	230mA
5U4G	16 $\mu$ F	—	550V	200 $\Omega$	150mA
5U4G	—	1H	350V	—	270mA
5U4G	—	2H	550V	—	220mA
5R4GY	8 $\mu$ F	—	500V	350 $\Omega$	270mA
5R4GY	8 $\mu$ F	—	750V	505 $\Omega$	250mA
5R4GY	8 $\mu$ F	—	1kV	395 $\Omega$	120mA
5R4GY	—	1H	500V	—	300mA
5R4GY	—	5H	1kV	—	170mA

**Silicon Rectifier Operating Conditions**

Type	Peak Inverse Voltage	Maximum Current
BY100	800V	550mA
1N4007	1kV	1A

to one end with windings like Fig. 3). Determine the secondary to primary ratio from the voltage ratings. The supply resistance is equal to:

$$n^2 R_p + R_s$$

where  $n$  is the full secondary to primary ratio in half-wave circuits or the half secondary (centre-tap to one end) to primary ratio in full-wave circuits. For example the ratio of a transformer with a 240V primary which gives 250 volts is near enough unity, or 1. If the primary resistance of such a transformer is  $100\Omega$  and the secondary resistance  $250\Omega$ , the supply resistance is equal to  $350\Omega$  approximately.

If the total is lower than quoted for the rectifier, add resistors  $R_1$  and  $R_2$ , as in Fig. 3. Suppose in the example just given that the minimum supply resistance must be  $450\Omega$ , then  $R_1$  and  $R_2$  would each be  $100\Omega$ . The resistor wattage should be at least twice that found from  $I^2$  times  $R$ . Thus, if  $I$  is  $100\text{mA}$  and  $R$  is  $100\Omega$ , then  $0.1$  times  $0.1$  times  $100$  equals  $1$  watt, and  $2$  watt resistors should be fitted.

### CHOKE INPUT

In Figs. 1, 2 and 3 a reservoir capacitor follows the rectifiers, and this type of circuit is termed 'capacitor input'. In Fig. 4(a) a choke follows the rectifier, and this is called 'choke input'. Choke input gives a lower h.t. voltage from a given h.t. winding, but can provide much better voltage regulation. It also limits peak rectifier current as compared with capacitor input.

The circuit of Fig. 4(a) has a single capacitor, and is much used for transmitting equipment. Fig. 4(b) employs a second choke and capacitor, for improved smoothing.

With choke input, the effective supply impedance can safely be zero ohms, so it is not necessary that some minimum series resistance be present as in the manner described for capacitor input circuits.

The choke  $L_1$  must have a certain minimum inductance value. If it is lower than this value the circuit will begin to operate as a capacitor input circuit at low currents. For maximum output, the windings of both  $T_1$  and  $L_1$  (and  $L_2$ , if used) should have a low d.c. resistance.

### RELATIVE REGULATION

Fig. 5 shows a typical comparison of results be-

tween capacitor input and choke input circuits. The curves are for a 5U4G rectifier and a 350-0-350V transformer.

With capacitor input, a maximum of  $235\text{mA}$  may be drawn, the rectified voltage then being  $320\text{V}$ . This rises to  $375\text{V}$  at  $100\text{mA}$ . At low currents, the voltage soars, reaching over  $420\text{V}$  at  $50\text{mA}$  and  $450\text{V}$  at  $25\text{mA}$ .

With choke input a maximum of  $270\text{mA}$  may be drawn, the rectified voltage then being about  $275\text{V}$ . With  $100\text{mA}$  taken the voltage has only risen to  $290\text{V}$ , while it is only a little over  $300\text{V}$  at  $50\text{mA}$ , and  $310\text{V}$  at  $25\text{mA}$ .

If a bleeder resistor drew  $50\text{mA}$ , with capacitor input the rectified voltage would rise from  $320\text{V}$  at maximum load current (now  $185\text{mA}$ ) to over  $420\text{V}$  with no load. With choke input and the same bleeder current, the voltage rise is only from  $280\text{V}$  on full load (now  $220\text{mA}$ ) to about  $300\text{V}$  with no load.

Choke input is thus preferable for supplies where the current drawn will change considerably, as with a modulator or transmitter. It also enables the rectifier to provide more current. Against this, the transformer secondary requires to have a higher voltage rating than when capacitor input is used.

### BRIDGE RECTIFICATION

Bridge rectification allows full-wave rectification with a half-wave type secondary, or gives twice the usual voltage with a centre-tapped secondary. See Fig. 6. A 300-0-300V secondary with choke input would provide about  $240\text{V}$  h.t. in Fig. 4. In Fig. 6 an h.t. supply approaching  $540\text{V}$  will be obtained.

For continuous working, the current rating of a centre-tapped secondary is halved. So if the transformer could provide  $200\text{mA}$  in Fig. 4, the drain should not exceed  $100\text{mA}$  in Fig. 6.

### INTERMITTENT RATING

Transformers sold for use in amplifiers, radio receivers, etc., are rated for continuous operation. For amateur transmitting equipment where periods of duty are followed by periods of stand-by, rating can usually be increased by some 20% or so without danger. In c.w. and s.s.b. equipment peak current is intermittent, and no harm would normally be expected with a 25% increase.

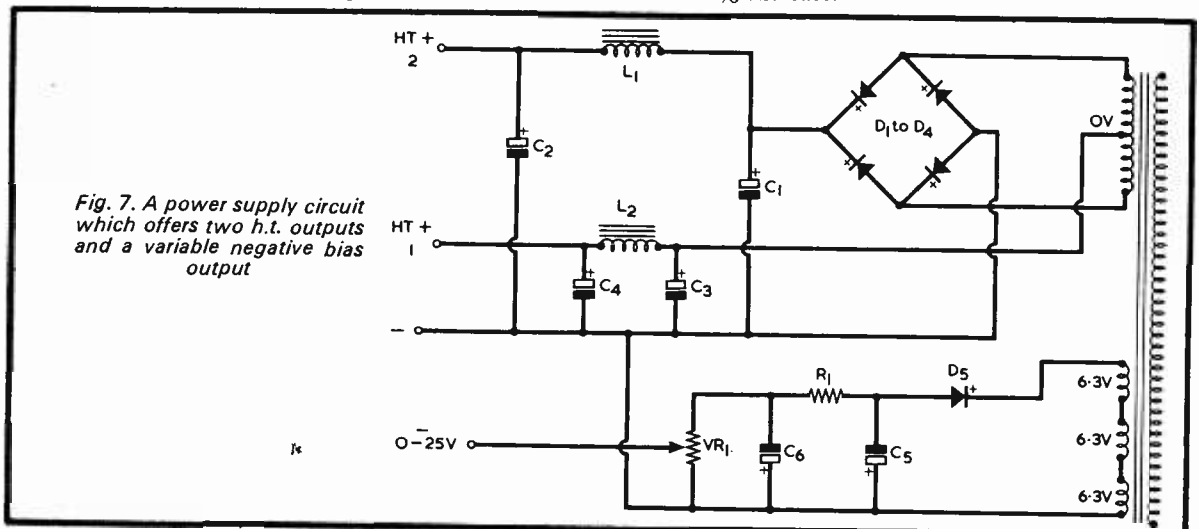


Fig. 7. A power supply circuit which offers two h.t. outputs and a variable negative bias output

## H.T. ADJUSTMENT

Where the transformer provides h.t. only, as in Figs. 3 and 6, it is usually in order to bring about a variation in the h.t. voltage by changing the mains primary taps. As an example, with a 500V h.t. supply, changing the primary taps up or down 10V can modify the h.t. obtained from about 480V to 520V, and this can be very useful. An increase in h.t. voltage of more than about 10% by this means is not recommended, though this depends on the individual transformer. Nor should changes to the primary taps be made if the transformer supplies heaters.

## SERIES CAPACITORS

Smoothing capacitors in series to cater for high voltage, as in Fig. 6 should be of equal value and rating, and each should have a resistor of equal value in parallel. As an example, with a 500V supply, two 450V 64 $\mu$ F capacitors in series will give the equivalent of 32 $\mu$ F, while each resistor could be 20k $\Omega$  5W (or of lower value if current is available).

## CONSTRUCTION

Any reasonable layout will be satisfactory. The smaller power supplies can usually be constructed with all h.t. positive and other live tags and connecting points under the chassis, and there is then no real need for a case or cover. If a chassis 2in., 3in. or 4in. deep is made from the readily available 'Universal Chassis' sides (Home Radio, Mitcham) flanges are available to enable a bottom plate to be screwed on for protection.

Provision to supply external equipment can be given by insulated terminals, separate insulated sockets, or a multi-way outlet into which matching plugs can be inserted.

Where the design of transformers, chokes, or other

items means that bare tags will be on top, a cover or case should be provided for the power supply.

There must be adequate ventilation for items which grow hot, including in particular valve rectifiers and resistors. Ventilation is provided by holes or slots in the chassis and case or cover, or by apertures covered with expanded or perforated metal.

## MULTIPLE SUPPLIES

For modulators or larger transmitters it is convenient to have a 250V or similar supply for early stages, and some 400V to 700V or as required for output stages. These supplies can be obtained from separate transformers, each with their own rectifiers and smoothing circuits, as in one of the packs illustrated in the photograph.

When a steady current is drawn it is practical to obtain lower voltages for early stages by means of voltage dropping resistors, but this process is wasteful of power for other than small currents. In a circuit such as Fig. 6, half the maximum voltage can be drawn at point X, but only at low current.

Fig. 7 shows a rectifier circuit which gives two outputs. That at H.T. +1 is approximately the same as is given by Fig. 3, while H.T. +2 gives about twice this voltage.

C1, C2 and L1 are rated for the high voltage supply, and C3, C4 and L2 for the lower voltage supply.

Three unused 6.3V windings in series, with D5, provide about 25V negative bias, at low current. The a.c. output of the windings is checked with a meter, and they are connected in the phase which gives a total voltage of 18.9V. C5 can be 25 $\mu$ F, and C6 100 to 250 $\mu$ F, 50V Wkg., R1 being 1k $\Omega$  and VR1 5k $\Omega$ .

The accompanying Table lists valve rectifier operating conditions, using a full-wave rectifier circuit as in Fig. 2 or Fig. 4(a). ■

---

# *Windows for viewing the universe*

by J. B. Dance, M.Sc.

## Some notes on present-day detection of space phenomena.

**F**OR MANY CENTURIES OUR ASTRONOMICAL IDEAS HAVE developed from information contained in the visible light reaching us from outside the earth's atmosphere. Rockets which can carry equipment above the atmosphere of the earth have enabled us to look at signals arriving from the sun and stars in the form of ultra-violet and X radiation.

### PULSARS

Radio-astronomy has provided us with another 'window', through which we can see a somewhat different view of the universe. It has, for example, led to the discovery of 'pulsars' which are believed to be neutron stars where gravitational forces are so great that electrons are forced into protons to form neutrons. The density of neutron stars is believed to be of the order of 10<sup>13</sup> grams/cm<sup>3</sup> - similar to the density of a

neutron or proton itself.

Other new windows for viewing the universe are becoming available. For example, various groups of workers have set up equipment to detect the neutrinos given out by reactions in the sun. These particles can travel through all matter almost unhindered and may enable us to view the inside of the sun.

It is almost certain that gravitational waves coming from the centre of our galaxy have been detected by Weber in the U.S.A. Like neutrinos, these waves can travel easily through the earth and are most difficult to detect, but it seems that the galactic centre is producing enormous amounts of energy in this form. The probable source of gravitational waves is collapsed neutron stars known as 'black holes' where matter has an infinite density and where the gravitational field is so great that no matter or light can escape. ■

# NEWS . . . AND .

## YACHTSMEN BEAT FLAT BATTERIES



*The Aerocharge Wind Generator shown fitted to the cabin roof of a yacht with the wind vane in position.*

A compact, portable wind generator, originally designed for charging boat batteries, has met with a large demand, not only from boat owners, but from users such as the Zambian Flying Doctor Service, the British Transport Docks Board and an oil Company operating inside the Arctic Circle.

The Aerocharge Wind Generator, developed by two Poole, Dorset, yachtsmen who are also professional engineers, is manufactured by Harber Ventus Limited, of Bridge Approach, Hamworthy, Poole. It comprises a 17 inch diameter impeller fan driven by the wind and a small built-in alternator which is free swivelling and kept into the wind by a small, detachable directional wind vane.

The electronic controls are mounted in a separate control box, which is fitted with an indicator light to show when the unit is charging.

Easily stored when not in use, it can, when required, be slipped on to a fixed mounting and the output leads connected to a battery circuit by simple plugs.

The unit gives an average charging rate of .25 amps at 12 volts with moderate wind conditions. A power input of 30 ampere hours is possible over five consecutive days.

The control unit is also so arranged that current from the battery cannot flow back to the generator and there is no risk, therefore, of the battery discharging when there is no wind.

The equipment ordered by the British Transport Docks Board is to test suitability for prolonging a state of charge in batteries located on an unmanned light vessel in the Humber estuary. The batteries being used to power radio-controlled fog alarms.

The wind generator is proving a boon to family yachtsmen, familiar with the predicament of returning to their boat after a week at the office only to find the battery flat.

The unit sells in the U.K. at £28.00p (Packing and Postage 50p).

## COMMERCIAL LOCAL RADIO

At an Advertising Association dinner in Bournemouth, Sir John Eden, Minister of Posts and Telecommunications, explained why there must be a limitation on the number of local radio stations, a matter which is not always understood by the general public.

Sir John pointed out that we are part of a continent in which radio frequencies ". . . are exploited until they are almost bursting at the seams . . . . a highly sophisticated garden in which there was room only for new plants of certain kinds and in certain quantities."

The Government's objective is that as many people as possible should be enabled to enjoy the new local radio service. In the circumstances it is anticipated that about 60 commercial local radio stations will be the maximum number which can operate without upsetting the proper ordering of frequencies, even so, they will add a new dimension to broadcasting in this country.

## CORDLESS SOLDERING IRON

The world's first cordless soldering iron from the USA is available in this country from the exclusive distributors, Pact International Electronics Ltd., P.O. Box 19, Royston, Herts SG8 5HH.

The completely portable soldering iron needs no mains power source during operation. It uses a power source which is automatically recharged from the stand which itself is connected to the mains. A working light near the soldering tip makes it easy to use, even in dark corners. This precision instrument is used by professional electronic engineers for all types of soldering.

With a special push-button operation and pilot light there is little chance of accidental burning - a useful safety feature.

This soldering iron heats up in 3-5 seconds and has indestructible iron-plated tips. The iron costs £9.25 complete with recharging stand and fine-point soldering tip. A spare heavy-duty tip is also available.



RADIO & ELECTRONICS CONSTRUCTOR

# COMMENT

## DIAMOND JUBILEE YEAR

We congratulate The Radio Society of Great Britain which this year celebrates the sixtieth anniversary of its foundation.

On the 5th January, Dr. J. A. Saxton, Ph.D. C.Eng., F.I.E.E., F.Inst.P., a former President of the Society, was installed as the thirty-ninth President, for this special Diamond Jubilee Year.

The Society is planning a number of special events in various parts of the country such as rallies, conventions, dinners, etc.

We wish the RSGB well in all the functions planned, and may it go from strength to strength in its sterling work for the radio amateur.

## LONGEST STRAIGHT LINE

*Dateline, London*, one of the BBC's Topical Tape programmes, recently reported on the new giant radio telescope designed and built by the Mullard Radio Observatory in Cambridge. It is, in fact, made up of eight separate radio telescopes which move into position along the world's longest true straight line.

This line does not just follow the curvature of the earth like a canal. It is a true geometric straight line cut through the curvature of the earth, three miles long and accurate to one millimetre.

Topical Tapes produced by the BBC Overseas Regional Services and distributed by the BBC Transcription Service are regular weekly programmes in English especially designed for rebroadcasters throughout the world.

Each week, over 300 high quality radio tapes are sent by air from London direct to 70 subscribers radio organisations. They are regularly used either direct, or in further copies made locally, by more than 240 stations in some 60 countries.

## IN BRIEF

● APT Electronics Ltd have delivered 600 specially-designed power supplies to GEC Telecommunications Ltd, for use in Lincompex equipment, since the late 1960s.

● Norwood Technical College, Knights Hill, London, SE27 0TX, commencing on Monday 12th February, are holding a short course of 7 lectures on Video Recording.

The course covers Monochrome and colour video recording and transmission systems, and tape, disc and electron beam techniques.


The fee is £3.00 and the lectures last from 6.30 to 8.30 p.m. Enquiries to Senior Administrative Officer.

● The MacRobert Award, often described as the Nobel Prize for engineering, for 1972 was awarded to Mr. Godfrey Hounsfield and EMI Ltd for the invention of a new X-Ray technique which forms the basis of a new computerised system for diagnosing brain disease.

HRH Prince Philip presented the £25,000 Award cheque to Mr. Hounsfield. The Gold Medal was presented to Sir Joseph Lockwood on behalf of EMI.

FEBRUARY 1973

## COMPUKIT 1 DELUXE MODEL

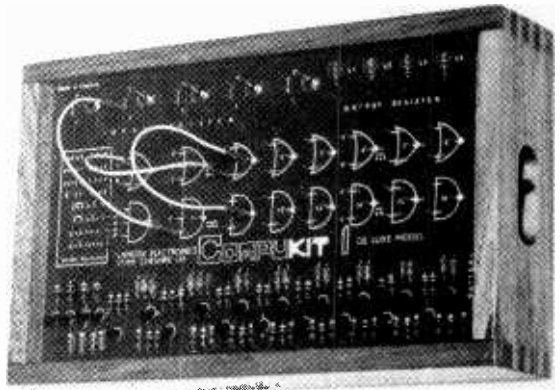

Limrose Electronics have announced improvements in the design of their very popular computer and logic teaching aid, CompuKit 1 Deluxe Model, which is now also available in kit form.


The assembled CompuKit 1 Deluxe Model consists of sixteen NAND and NOR gates. Logic inputs are provided by five high quality switches.

The discrete components used in the design of the logic gates not only help students to understand the electronics involved, but also permit Wired-OR operations to be performed. This makes the unit particularly suitable for teaching the fundamentals of logic to students of electrical and mechanical engineering.

Full instructions for assembly are provided with the kit form of the Deluxe Model and the assembly can be completed in about two hours.

Both kit and assembled forms of CompuKit 1 Deluxe Model are accompanied by a comprehensive instruction book entitled "Introduction to Logic and Digital Computers".

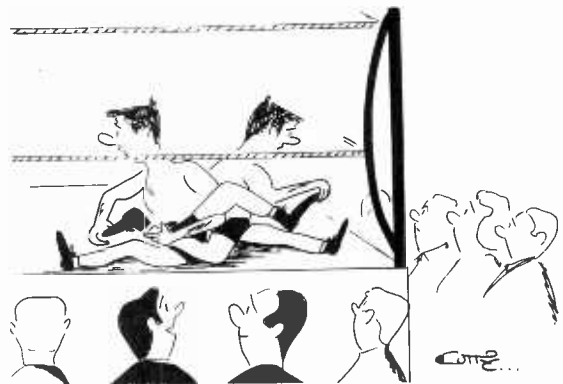The cost of CompuKit 1 Deluxe Model in kit form is £20 and that of the fully assembled and tested form is £24. Further information can be obtained from Limrose Electronics Limited, 8-10 Kingsway, Altrincham, Cheshire. WA14 1PJ.



That reminds me, I'm out of twisted pair cable



# TRANSISTOR CURVE TRACER

by D. W. Nelson

A low-cost unit employing standard components which enables collector voltage-collector current curves to be directly displayed on an oscilloscope.


WHEN OBTAINING THE CHARACTERISTIC CURVES OF individual transistors the normal procedure is to lay out the various components in a breadboard fashion with all the usual toggle switches, voltmeters, ammeters and variable voltage supplies taking up most of the available bench space. To obtain enough data for even one characteristic curve can be very time-consuming. For example, to obtain the characteristic curve of, say, collector current versus collector voltage it is necessary to increment one of the variables (e.g. collector voltage) whilst keeping the base current constant, and read off each new value of collector current. One such set of readings may take up to half an hour. By the time the results are plotted on suitable graph paper the experimenter usually feels he has done enough for one day. Imagine taking enough measurements to obtain a family of curves! To further investigate the effects of temperature on the transistor would require a prohibitive amount of time.

## PATIENCE

The author, having now, he hopes, convinced the reader that he will need the patience of a saint to make a reasonable number of measurements, will next describe a technique which is simplicity itself and which not only permits various characteristic curves to be obtained in about two minutes but also allows a permanent photographic record to be made of a whole family of curves. The apparatus required is extremely simple (except for an oscilloscope) and will be found in virtually any experimenter's 'junk box'. In fact, with a little thoughtfulness and care a very comprehensive unit can be constructed which will prove invaluable in understanding characteristic curves.
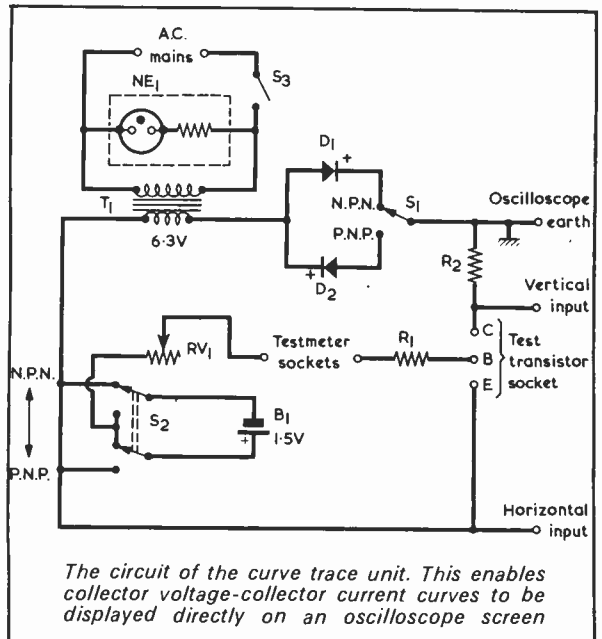
## CIRCUIT

The circuit of a device capable of producing transistor curves without wasting time is seen in the accompanying diagram. Base current for the transistor being checked is supplied by a small 1.5 volt cell, B1, and is adjusted by means of potentiometer RV1. The current is




measured by an external testmeter, which is switched to a suitable range and coupled to two sockets on the unit. In order to accommodate both p.n.p. and n.p.n. transistors, switches S1 and S2 are incorporated. There is no need to provide an on-off switch for B1 because current is only drawn from it when a transistor is inserted in the test transistor socket.

To obtain a complete curve on the oscilloscope it is necessary to 'sweep' the transistor through its operating range. This is accomplished by applying a half-wave rectified voltage from the 6.3 volt winding of a small heater transformer to the transistor emitter and collector. The half-wave rectified voltage has a peak value in the order of 8 to 9 volts.

To provide a voltage sweep on the oscilloscope which is directly proportional to the applied collector-emitter voltage, the half-wave rectified voltage is coupled to its horizontal input. At the same time, by using a small series resistor (R2 in the diagram) in the collector circuit of the transistor being checked, another voltage becomes available which is directly proportional to the transistor collector current. This voltage is applied to the vertical input of the oscilloscope. Thus, the oscilloscope is now capable of tracing out a curve which has collector-emitter voltage as the horizontal axis and collector current as the vertical axis.

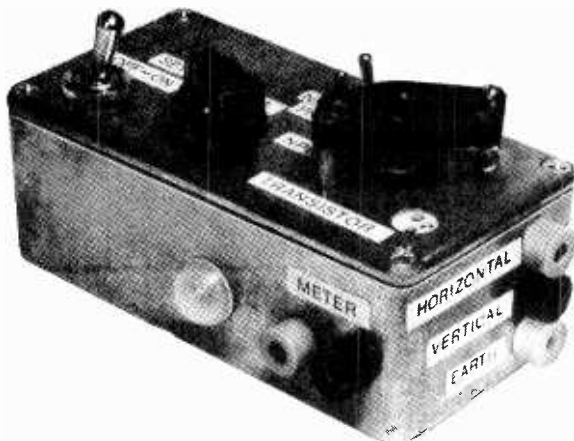In some cases the oscilloscope traces obtained with the aid of the unit will not be the 'same way up' as are the characteristic curves normally seen in text-books, but of course the latter curves are 'rationalised' in terms of sign conversion and are all drawn in the same V-I quadrant. The simplicity of the present unit would be lost if an attempt were made to have it present all curves



*External view of the prototype unit. The three wander plug sockets for the oscilloscope may be seen on the right, whilst those for the external meter are on the front edge. Also on this edge is the neon lamp*

in the same manner as text-book curves and, in practice, the operator of the unit very soon becomes used to seeing curves which are oriented away from those normally encountered. The curves will usually be inverted either for p.n.p. transistors or for n.p.n. transistors. Measurements can, of course, be made just as easily with any curve orientation.

## COMPONENTS

### Resistors

R1	100Ω ¼ watt 10%
R2	100Ω ½ watt 2%
RV1	25kΩ potentiometer, linear

### Transformer

T1	6.3V heater transformer
----	-------------------------

### Diodes

D1	1N4002 or similar
D2	1N4002 or similar

### Switches

S1	S.P.D.T. toggle
S2	D.P.D.T. toggle
S3	S.P.S.T. toggle

### Neon

NE1	240V neon lamp assembly with integral resistor
-----	--

### Battery

B1	1.5V cell
----	-----------

### Miscellaneous

5 wander plug socket	
Transistor sockets (as required)	
Knob	
Case	

## CONSTRUCTION


The layout of the unit is not at all critical and the dimensions of its housing depends on the size of the components employed. The writer constructed his unit in a small diecast box measuring 4½ in. by 2½ in. by 1½ in. This employed a miniature mains transformer and miniature switches for S1 and S2. Readers employing standard size components will need to use a larger box. Care should be taken to ensure that there is no risk of circuit points at live mains potential touching the inside of the case. The mains lead should be securely anchored inside the box and should pass out through a rubber grommet.

The box has five wander plug sockets for external connections, three of these being for the oscilloscope and two for the external current reading meter. The question of sockets for the transistor being checked is left to the reader's discretion. The author's version has one small socket primarily intended for TO5 transistors and another socket capable of taking TO3 power transistors.
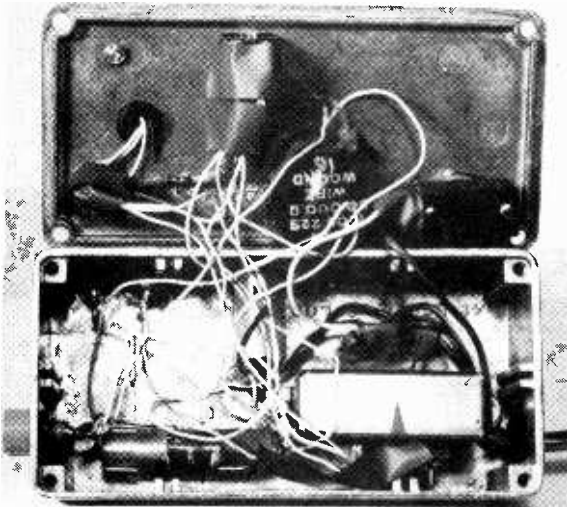
## USING THE UNIT

The unit is coupled to the oscilloscope with which it is to be used and the external testmeter connected to the two appropriate wander plug sockets. S1 and S2 are set to 'n.p.n.' or 'p.n.p.', according to the type of transistor to be checked, the latter is connected to the unit and the mains supply is switched on by means of S3.

The desired base current, as indicated by the testmeter, is set up by means of RV1 and the gain and shift controls of the oscilloscope adjusted for an optimum image size. If no quantitative measurements on the



Inside the diecast box are mounted the miniature mains transformer and the 1.5 volt cell

transistor are required, then this characteristic curve may be demonstrated, say, to a class of students or used for discussion as a teaching aid. However, in most cases it will be necessary to take measurements of the characteristic curve and this will incur taking advantage of the voltage calibration of the oscilloscope. The collector-emitter voltage output from the unit is directly in volts. The collector current output has an amplitude of 0.1 volt per milliamp.

Having set up the oscilloscope gain controls for a desired presentation or calibration level these are left alone, and further curves corresponding to different base currents are then displayed.

To obtain a permanent record of the characteristic curve (or family of curves) being studied, one of several techniques may be used. The simplest method is, of course, to simply trace the curve. Alternatively, the single curve may be photographed.

It is possible to obtain a whole family of curves on a single photograph in the following manner. First, all calibration adjustments are carried out and the origin of the curve (i.e. the zero voltage zero current point) positioned conveniently. Then the first curve is 'put up' on the screen and photographed in the usual way. The transistor base current is then adjusted, causing a new curve to be given on the screen. Another exposure is then made on the same film, and the procedure is repeated until a whole family of curves is obtained. If the oscilloscope has a graticule it may be possible to illuminate this also and photograph it, whereupon it becomes superimposed on the curves.

#### ALTERNATIVE APPROACHES

The approaches employed in the present design may be varied. For instance, a 12 volt mains transformer winding may be employed, thereby giving a higher emitter-collector voltage. Again, a Variac variable output transformer could be used, giving a continuously variable collector voltage. Obviously, the voltage applied to the transistor being checked should not exceed its maximum rating.

Other possibilities include the use of a resistor having a value lower than  $100\Omega$  in the R2 position. This will enable higher collector currents to be introduced. A  $10\Omega$  resistor will, for instance, produce a voltage of 10mV per milliamp.

The author's unit has been tried with several different oscilloscopes, and in particular with the Serviscope Type D31. An interesting experiment has been its use in the demonstration of the effect of temperature on transistor characteristics. The curve of a transistor is first displayed on the screen and a hot-air blower (hair dryer) is then directed onto the transistor. The results on the characteristic curve can be quite startling. ■



## UNDERSTANDING TELEVISION

by

J. R. DAVIES

Over 500 pages  
300 diagrams

£2-10

POSTAGE  
20p

- Principles of 405 line reception
- Principles of 625 line reception
- Nature of the television signal
- Receiver tuner units
- A.F. and video amplifiers
- Deflector coil assemblies
- Automatic gain and contrast control
- Receiver aerials

- The cathode ray tube
- Receiver i.f. amplifiers
- Vertical and horizontal timebases
- Synchronising
- Power supply circuits
- Colour television
- **COLOUR TELEVISION – 80 page section deals comprehensively with this subject**


Available from

Data Publications Ltd., 57 Maida Vale, London, W9 1SN



# INTEGRATED CIRCUIT OHMMETER

by G. A. FRENCH

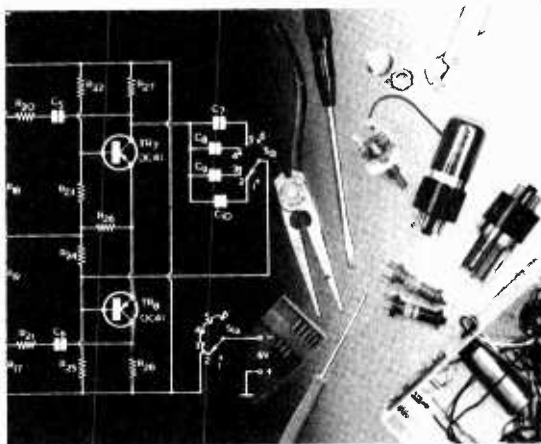

**I**N THE LAST TWO ARTICLES IN THE Suggested Circuit series the author described two items of test equipment incorporating the integrated circuit operational amplifier type ML741C. The first item (Suggested Circuit No. 265) was a voltmeter with a sensitivity of 200k $\Omega$  per volt, and the second (Suggested Circuit No. 266) was a microammeter having the ranges 0–5 $\mu$ A, 0–10 $\mu$ A and 0–20 $\mu$ A.

The 741 i.c. is an extremely useful device and it lends itself particularly well to the design of sensitive d.c. measuring instruments. Since the third d.c. quantity capable of measurement is resistance it was felt that an ohmmeter incorporating a 741 op-amp would complement the preceding two articles very well. Low-cost conventional ohmmeters are capable of measuring resistances above 1 $\Omega$  or so with sufficient accuracy for most everyday work, and so it was decided to incorporate the 741 in an instrument which could measure much lower values of resistance. The ohmmeter to be described is capable of measuring resistance from less than 0.01 $\Omega$  up to 10 $\Omega$ . An unusual feature is that resistance is indicated on a linear scale, and not on a non-linear scale which is cramped at one end as occurs with conventional ohmmeters.

## BASIC APPROACH

The basic approach to the ohmmeter design is illustrated in Fig. 1. In this diagram a known constant current is caused to pass through the 'test resistor', this being the resistor whose resistance it is desired to measure. A voltage which is proportional to its


resistance appears across the test resistor, and this voltage is applied to the operational amplifier circuit. An amplified voltage appears at the output of the op-amp and is passed to a voltmeter. In consequence, the voltmeter gives a reading which is proportional to the resistance of the test resistor.

The output of the op-amp in Fig. 1 is coupled back to the inverting input via  $R_Y$ . If the test resistance is very much lower in value than  $R_X$ , the voltage gain of the op-amp then becomes equal to  $R_Y$  divided by  $R_X$ .

The full practical circuit of the ohmmeter is given in Fig. 2. Here, the constant current device is a transistor type BC214L, the base of which is

held at a fixed potential by means of the four forward biased silicon diodes D2 to D5. The emitter current is selected by the range switch S2, the pre-set potentiometers R1, R2 and R3 being set up such that on Range 1 the BC214L passes a constant current of 0.5mA, on Range 2 a constant current of 5mA, and on Range 3 a constant current of 50mA. Power for the constant current circuit is provided by the 6 volt battery B3, and is present whenever push-button S4 is pressed.

On Range 1 the 0.5mA constant current causes a voltage of 5mV to appear across the test resistor when this has a value of 10 $\Omega$ . Lower values of resistance will cause smaller voltages to appear. On Range 2, the constant

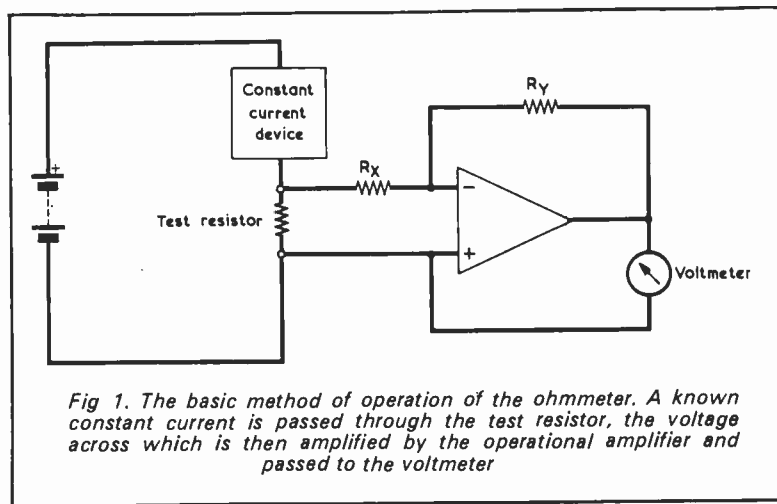

*Fig 1. The basic method of operation of the ohmmeter. A known constant current is passed through the test resistor, the voltage across which is then amplified by the operational amplifier and passed to the voltmeter*

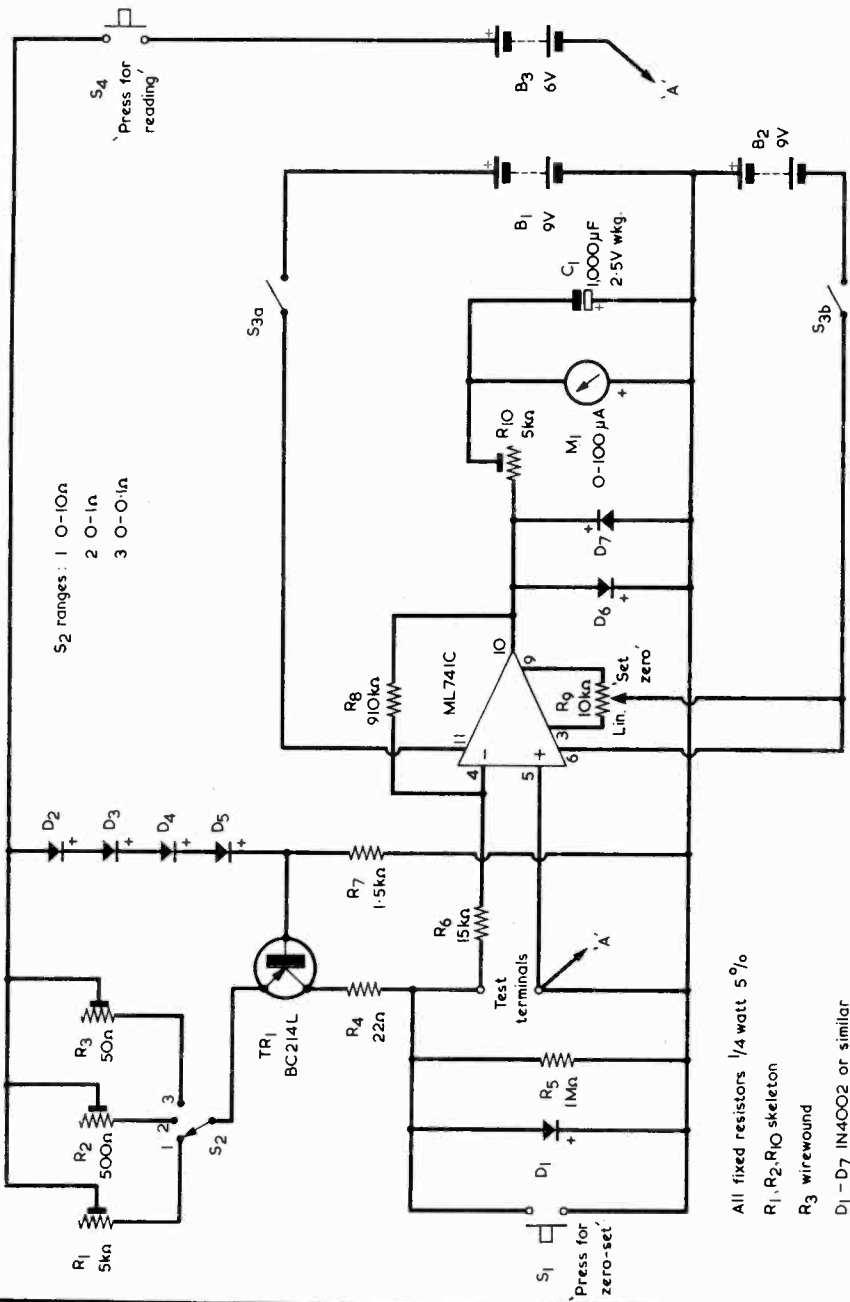


Fig. 2. Full circuit diagram for the ohmmeter. It is capable of measuring resistance down to less than 0.01Ω. The two circuit points marked 'A' are wired directly together

current of 5mA produces a voltage of 5mV if it flows through a test resistance of 1Ω. A constant current of 50mA, given on Range 3, produces a voltage of 5mV when the test resistance is 0.1Ω. If the op-amp circuit can be made to cause the following voltmeter to give an f.s.d. reading for an input voltage of 5mV, then the arrangement becomes an ohmmeter having ranges of 0-10Ω, 0-1Ω and 0-0.1Ω.

The voltmeter following the op-amp is given by M1 and R10 in series. A convenient voltage at which f.s.d. can be indicated by M1 is 0.3 volt, since this allows the meter to be protected against overload by the two silicon diodes D6 and D7, which become fully conductive at around 0.6 volt. The amplification required to step up an input voltage of 5mV to an output voltage of 0.3 volt is 60 times, and this is provided (approximately) by making R8 (which appeared as RY in Fig. 1) some 60 times greater than R6 (which was RX in Fig. 1). There is no necessity for R8 and R6 to be close-tolerance components since, provided the amplification given by the op-amp is reasonably close to 60 times, any small deviation from this figure can be readily taken up in the adjustment of R10 during calibration. A voltage gain of 60 times is a convenient figure in practice, since it is not so high as to make zero-set adjustments critical.

TR1 achieves a constant current performance because it is effectively operated in the grounded base mode. Under these conditions collector current remains virtually unaltered for very large changes in collector voltage. It would be possible to obtain constant current operation with only two series silicon diodes to hold the base at a fixed potential, whereupon the pre-set potentiometers R1, R2 and R3 would require lower values. This could, however, result in inaccuracies in measurements because the lower values of emitter resistance could become comparable with contact resistance in switch S2. Having four diodes enables the emitter resistance inserted by R1, R2 and R3 to be considerably higher than any contact resistance likely to be inserted by a good quality switch in the S2 position.

Resistor R4 is a limiter resistor which reduces power dissipation in TR1, particularly on Range 3. Assuming a drop of 2.4 volts across D2 to D5, the power dissipation in TR1 on Range 3 without R4 would be of the order of 180mW, which is within the maximum rated power figure for the BC214L of 300mW. But there is little point in running a transistor at a higher power than is necessary, and R4 reduces the dissipation in TR1 to around 125mW.

Diode D1 across the test terminals limits the voltage across these to 0.6 volt if S4 should happen to be accidentally pressed when the test terminals are open-circuit. R5 is included merely to provide an earth return for

the inverting input of the op-amp when the test terminals are open-circuit. Its high value has negligible effect upon the value of the resistance being measured. Since the inverting input is a virtual earth, R6 is also effectively in parallel with the resistance being measured. Its resistance is, nevertheless, much higher than the range of resistors it is intended that the ohmmeter should measure and it similarly has negligible effect on the test resistance.

It is essential that the current flowing in the test resistance be kept separate from the op-amp actuating currents as, otherwise, resistance in the wiring of the test instrument may give inaccurate results, particularly on Range 3. It is for this reason that the test resistance current is provided by a separate battery. The test resistance current should only encounter the op-amp circuit at the test terminals themselves, and the negative side of B3 connects into circuit at the lower test terminal itself, and at nowhere else in the circuit. Also, R4 connects directly to the upper test terminal and the operational amplifier inputs are taken direct from the test terminals as well.

As already stated, the gain of the operational amplifier is equal to R8 divided by R6, and is approximately 60 times. This gain is unaffected by the test resistance in series with R6, which is negligibly low in comparison. The output of the op-amp at f.s.d. is nominally 0.3 volt. In practice, the instrument is set up by connecting a close-tolerance 10Ω resistor across the test terminals and adjusting R10 for full-scale deflection in meter M1. Variances from a precise gain figure of 60 are thus taken up in the voltmeter section itself.

It is desirable to have a push-button in the test resistance current circuit since this helps to guard against the instance where test resistance current is accidentally applied when no resistor is connected across the test terminals. Under these circumstances a positive voltage of about 0.6 volt (limited by D1) is applied to the inverting input of the op-amp, the output of which swings negative until it is limited, also at approximately 0.6 volt, by D7. This output will also be given if the test resistance happens to be open-circuit or high value when S4 is pressed. The presence of D7 ensures that meter M1 cannot pass more than about twice its f.s.d. current. Capacitor C1 is included merely to damp the movement of the meter and it prevents the needle swinging hard against the end-stop under the circumstances just described. The capacitor causes a slight 'backlash' in meter reading: for an on-scale measurement the needle passes its final setting and then returns to it. This effect takes place quite quickly and does not detract from the usefulness of the instrument.

Zero setting is achieved with the aid

**RADIO & ELECTRONICS  
CONSTRUCTOR**

## IN OUR NEXT ISSUE

### LOGIC SUPPLY UNIT

by A. Foord

A supply unit for digital integrated circuits which offers two separate 5 volt outputs at currents up to 600mA each.

\*\*\*

### AR88 MODIFICATIONS

\*\*\*

### MAINS FAILURE WARNING DEVICE

\*\*\*

## PLUS

MANY OTHER

## FEATURES

price 20p

*Copies may also be obtained  
direct from the Publishers,  
26p. including postage*

Published by

**DATA PUBLICATIONS LTD**  
57 Maids Vale London W9 1SN

**RADIO & ELECTRONICS  
CONSTRUCTOR**

of R9, which couples into two transistor bases in the input differential amplifier inside the integrated circuit by way of pins 3 and 9. It is necessary for the test terminals to be short-circuited whilst adjusting R9 and this is achieved by pressing S1 during the operation.

Diode D6 limits the output voltage from the op-amp to 0.6 volt in the positive direction. An output voltage of this polarity will not occur during normal operation but could appear if R9 were set incorrectly. The op-amp does not need output current limiting because the output of the 741 i.c. is short-circuit proof.

## COMPONENTS

The op-amp is the same type as was employed in the preceding two 'Suggested Circuit' articles and it is a type ML741C obtained from Henry's Radio, Ltd., who advertise it as a '741C(DIL)'. This is a 14 pin d.i.l. integrated circuit and the top view given inset in Fig. 2 shows the pin layout. Other i.c.'s of the 741 type should function equally well, although the writer should mention that he has only checked circuit operation with the device purchased from Henry's Radio. Integrated circuits type 741 can be obtained in 8 pin dual-in-line, and the pin layout for these is also given in Fig. 2. It should be noted that both the i.c. pin layouts are shown as top views, with the pins pointing away from the reader. The inset showing the BC214L lead-outs has the lead-outs pointing towards the reader. Some integrated circuits may have a paint spot at the pin 1 end instead of the identifying groove illustrated.

The circuit uses rather a large number of silicon diodes and these can all be any small type of silicon rectifier. The writer used rectifiers type 1N4002, which appear to be becoming a 'standard' for low voltage applications these days.

All the resistors are  $\frac{1}{4}$  watt 5%. An improvement in long-term accuracy could result from the use of high-stability components for R6 and R8. The pre-set potentiometers are as specified in Fig. 2. R9 is a standard panel-mounting potentiometer. As already mentioned, a close tolerance 10 $\Omega$  resistor is also required, this being used for calibration.

Switches S1 and S4 are standard push-buttons which close when pressed. S2 is a good quality rotary wafer switch. It would probably be best, here, to avoid using one of the popular low cost miniature rotary switches which are currently available, and to employ instead a switch having true Yaxley operation in which the moving contact passes between two contact leaves at each fixed contact position. Switch S3(a)(b) is a double-pole toggle switch. Slide or rotary switches should not be employed for S3(a)(b) as it is desirable to have both the 9 volt batteries switched on and off at the same instant.

Meter M1 can be any panel-mounting 0-100 $\mu$ A movement. The circuit should accommodate any internal meter resistance likely to be encountered.

Both the 9 volt batteries can be small types, as the current drawn from them is low. They should be fitted and discarded in pairs, since the unit should not be operated with one battery new and one battery partly exhausted. The current drawn from the 6 volt battery is the constant current selected by S2 plus several milliamps flowing in R7 and diodes D2 to D5. Since this current can be in excess of 50mA on Range 3, the 6 volt battery needs to be fairly large. Two 3 volt cycle lamp batteries (Ever Ready type 800) in series would represent a good choice. The constant current circuit incorporating TR1 ensures that test resistance current does not vary with changing battery voltage. Nevertheless, the 6 volt battery should be discarded when its voltage on load on Range 3 falls below some 4.5 volts. Incidentally, there is no need to provide B3 with an on-off switch since current is only drawn from it when S4 is pressed.

Finally the two test terminals should be large, heavy duty insulated types. It will be found that surprisingly large values of resistance can be introduced on Range 3 by quite thick conductors.

## CONSTRUCTION AND SETTING UP

The ohmmeter can be housed in a plastic or wooden case with the meter, the four switches, R9 and the test terminals on the front panel. As already discussed, the negative terminal of the 6 volt battery must be wired directly to the lower test terminal, as also should the non-inverting input of the op-amp. R4 and R6 should be wired directly to the upper test terminal. The remainder of the wiring is not critical. It is preferable to use an integrated circuit holder for the i.c., the latter being fitted after the holder has been wired up.

Construction commences by wiring up R1 to R4, R7, S2, S4, D2 to D5, TR1, the test terminals and the 6 volt battery. The constant current potentiometers are then set up. Adjust R1, R2 and R3 to insert maximum resistance into circuit and connect a testmeter switched to read current to the test terminals with the positive lead to the upper terminal. It is essential at this stage that R1 to R3 insert *maximum* resistance. If any of these potentiometers offers a low resistance excess current can flow, with the risk of damage to TR1 and the testmeter. To guard against wiring errors, the testmeter should be initially switched to a high current range.

Set S2 to Range 1, press push-button S4 and gradually reduce the resistance inserted by R1 until the testmeter

indicates 0.5mA. Next set S2 to Range 2 and similarly reduce the resistance in R2 until the testmeter reads 5mA. Repeat on Range 3, adjusting R3 for a current of 50mA. Constant current operation on any range can be confirmed by temporarily short-circuiting R4, whereupon there should be negligible change in the current indicated by the meter.

Potentiometers R1 to R3 are now set up and should not be touched again. The remainder of the circuit may next be wired up. If it is desired later to confirm the constant currents, this may be done by first disconnecting D1, coupling a testmeter to the test terminals and then proceeding as before. It is necessary to disconnect D1 because the universal shunt circuits in many testmeters cause a relatively high voltage to appear across them on the current ranges, and this voltage can approach that at which forward current flows in the diode. The diode is reconnected after the currents have been checked.

When construction has been completed, the unit has to be calibrated. Initially, R10 should be adjusted so as to insert maximum resistance into circuit. The instrument is then switched on by means of S3(a)(b), push-button S1 is closed and the meter zeroed by R9. S1 is released, S2 is set to Range 1 and a close tolerance 10 $\Omega$  resistor is connected across the test terminals. Next, S4 is pressed and R10 adjusted for full-scale deflection in the meter. Since the voltmeter section is now more sensitive the sequence should be repeated, R9 being set again, if necessary, for zero reading and R10 readjusted for full-scale deflection. The ohmmeter is then set up for all three ranges.

It should be noted that if the instrument is switched on with no test resistor connected, so that only R5 appears across the test terminals, the meter needle will drift from the zero position. This effect is unimportant.

In use, the ohmmeter is switched on by means of S3(a)(b) and S1 is pressed to check the zero setting, which is adjusted if necessary. The instrument is switched off again, the resistance to be measured connected across the test terminals, and S2 set to the requisite range. The instrument is switched on once more and S4 is then pressed to find the test resistance. It should be remembered that the resistance indications are linear. On Range 2, for instance, a reading of 100 in the meter corresponds to a resistance of 1 $\Omega$ , a reading of 50 to a resistance of 0.5 $\Omega$ , and so on.

The prototype circuit functioned reliably as described and there were no problems in setting up or handling. The current drawn from each 9 volt battery was 1.4mA only. The sensitivity on Range 3 was exceptionally high and it was both fascinating and instructive to measure the resistance offered by quite short lengths of standard connecting wire. ■

# New Products




## ELECTRICIAN'S MULTIPURPOSE TOOL

A new product from Spiralux is a specialist Electrician's tool that would be useful around many homes. Basically, this ingenious gadget replaces three or four separate tools by combining their functions into one. It is a combination of wire stripper, wire looper and cutter together with a screwdriver. So in one handy tool, tradesman or handyman has the capacity to deal with most electrical jobs involving connections. The sturdy wire stripper is adjustable to various wire gauges. The Spiralux Wire Stripper is Tool No. 6075, is attractively cased and the recommended Retail Price is 40p.

For further information, please contact Hollands & Blair Ltd., Bensham Grove, Thornton Heath, Surrey.



## NEW VENTURE MULTIMETER

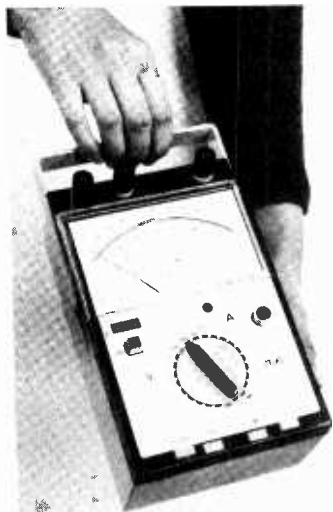

The Multimeter 3 is a compact, easily carried, 52-range instrument cleanly designed around a single 24-position rotary switch. Sensitivity of the taut-*ligament* movement is 31.6 kohms/V for d.c. and 5 kohms/V for a.c., with accuracies of  $\pm 1\%$  and  $\pm 1.5\%$  respectively.

A single standard 1.5 V leak-resistant cell energises the movement on all five resistance ranges covering 0.2 ohms to 50 Mohm.

A.v. and d.c. 10/10-ranged scales are identical, and are selected by push-button, as is the ohms range. With ohms selected there is only one 'ohms adjust' control for all ranges. There is a welcome simplification provided on the resistance ranges for testing unidirectional components such as capacitors and diodes without the need to reverse leads or terminals; press-buttons select the polarity of test voltage, and simultaneously reverse the meter movement. The case of the instrument is of two-tone grey impact-resistant a.b.s. plastic, with a slide-away carrying handle.

The patented safety cut-out is of a type newly introduced. Its high-speed action is achieved by an electrical circuit which reacts to the *rise time* of the applied signal; it does not rely on the movement of the pointer, but actually breaks the circuit before the pointer reaches full scale. It is equally sensitive in the forward or reverse direction, and the circuit cannot be reconnected while the overload condition persists. Delay fuse, diodes and neons give further protection.


Price of the Multimeter 3 is £38.50; For further information please contact: British Central Electrical Co., Ltd., Banner Street, LONDON EC1Y 8QD.

## RANGE OF SLIDER POTENTIOMETERS FOR CONSTRUCTORS

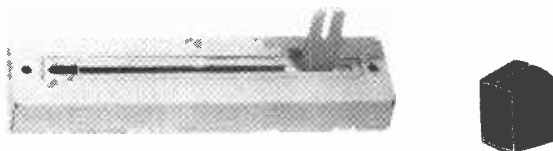D. J. Electronics Ltd. announce the launching of their branded range of accessories.

They are primarily aimed at the home constructor and enthusiast. Leading this range are a series of Slider Potentiometers, complete with knob and fixing screws. These are available as single or double gang sliders in both logarithmic and linear configurations. A separate range of mounting plates, to accept the sliders are available, thus enabling the enthusiast to easily construct units with our sliders. These plates are offered in three types:- single way, double or triple.

The Retail prices are:- Single Gang Sliders 61p



each, Double Gang Sliders 81p each.

Mounting plates will retail at 25p for the single way, 36p for the two way and 45p for the three way.

Further details from:- D.J. Electronics Ltd., 122 Balls Pond Road, London, N1 4AE.

# R.F. Amplifier using Dual gate F.E.T.

by  
N. FRIEL

An untuned aerial pre-amplifier which can boost the performance of low-cost communications receivers.

THE AUTHOR RECENTLY PURCHASED FOR HIS SON ONE of the cheaper communications receivers which are currently on the market, but its performance was found to be a little disappointing in terms of sensitivity due to the lack of an r.f. amplifier. Even when used with a 30 ft. wire aerial, the signal strength meter rarely moved above the S1 position.

## SIGNAL AMPLIFIER

This failing has been completely overcome by the addition of a pre-mixer signal amplifier, based upon a dual gate MOSFET type 40602. Fig. 1 shows the circuit arrangement. The 40602 is available from Electrovalue Ltd., 28 St. Judes Road, Englefield Green, Egham, TW20 0HB.

The incoming signal is fed via the coupling capacitor C1 to gate 1, this input circuit being untuned. The drain of the f.e.t. is returned to V<sub>DD</sub> positive (which is earthed) via the aerial input coil of the receiver, and so no additional tuned circuits are employed in the r.f. amplifier. The source bias is adjustable by means of RV1, which forms the r.f. gain control. Gate 2 is biased

## COMPONENTS

### Resistors

(All fixed values  $\frac{1}{4}$  watt 10%)

R1 100k $\Omega$

R2 150k $\Omega$

R3 100k $\Omega$

RV1 5k $\Omega$  potentiometer linear, with switch S1

### Capacitors

C1 100pF silver mica or ceramic

C2 0.02 $\mu$ F ceramic or plastic foil

C3 0.02 $\mu$ F ceramic or plastic foil

C4 0.1 $\mu$ F plastic foil

### Transistor

TR1 MOSFET type 40602

### Switch

S1 s.p.s.t., part of RV1

### Miscellaneous

9 volt battery

Knob

Veroboard, 0.15 in. matrix

Screened lead

Battery connectors


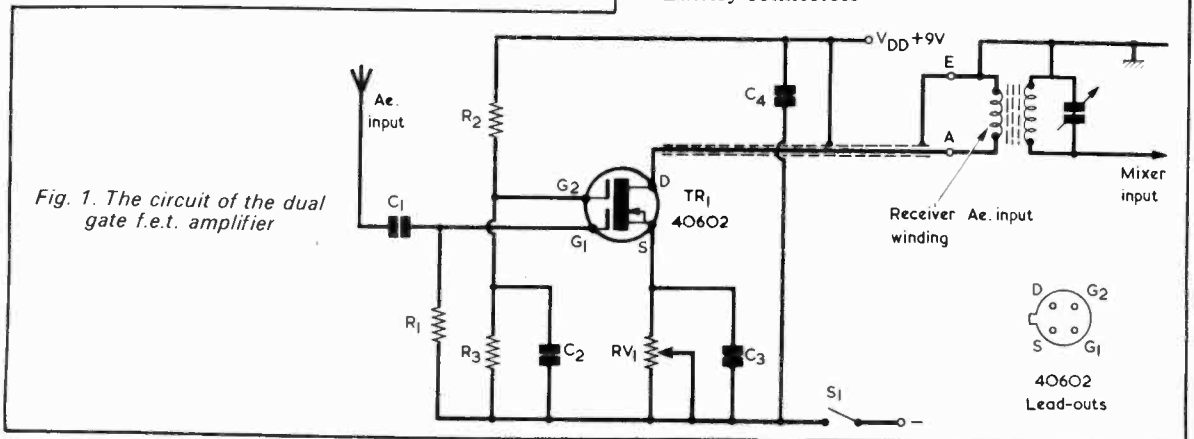


Fig. 2. If desired, current consumption at maximum gain may be reduced by inserting a 100Ω resistor in the source bias circuit

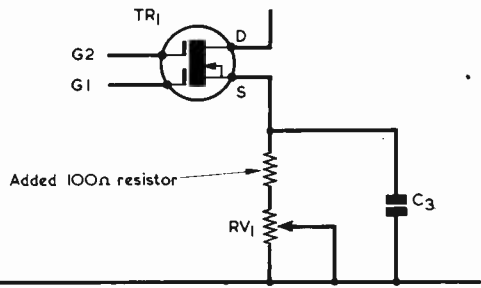

by means of the potential divider given by R2 and R3, these resistors having values which cause VG2 to be 0.4 times VDD. The capacitors C2 and C3 provide gate 2 and source decoupling and their values are in no way critical.

The current drawn from the 9 volt supply is 1.5mA when RV1 is set to insert maximum resistance and 18mA when RV1 inserts minimum resistance. If the maximum current figure is considered excessive it may be reduced by inserting a 100Ω resistor in series with RV1, as shown in Fig. 2.

#### ASSEMBLY

The original amplifier was constructed on a piece of 0.15 in. Veroboard as shown in Fig. 3. If this layout is followed and the output lead is screened no instability troubles should be encountered. Dual gate MOSFET's have very low feedback capacitance, a typical value being 0.02pF.

Special care should be exercised when handling MOSFET's and both gates should be kept short-

circuited to the source until the device has been soldered into circuit. The reason for this is that sufficient static charges can easily build up on the gates to break down the thin insulating layer of silicon dioxide which separates them from the channel, whereupon the transistor would be rendered inoperative.

The method adopted by the author is to wrap thin fuse wire around the MOSFET lead-out wires to effectively short-circuit all the electrodes together. Only after the transistor has been soldered into circuit and the gate and source circuits are completed to the negative line via R1, R3 and RV1 is this short-circuit removed.

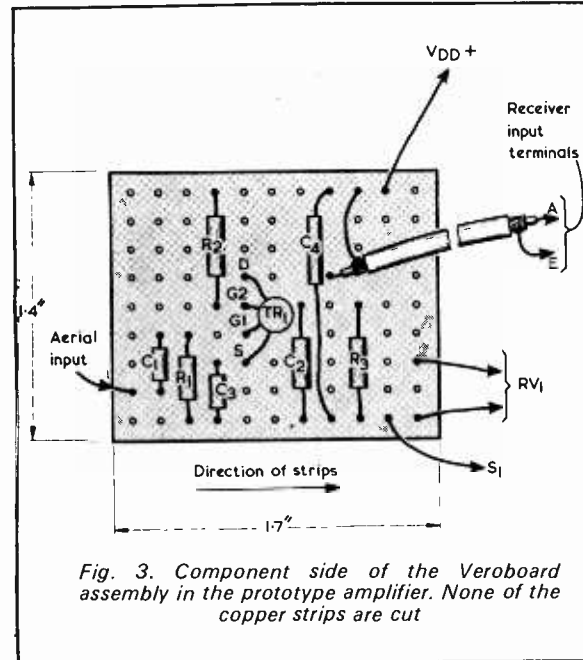


Fig. 3. Component side of the Veroboard assembly in the prototype amplifier. None of the copper strips are cut

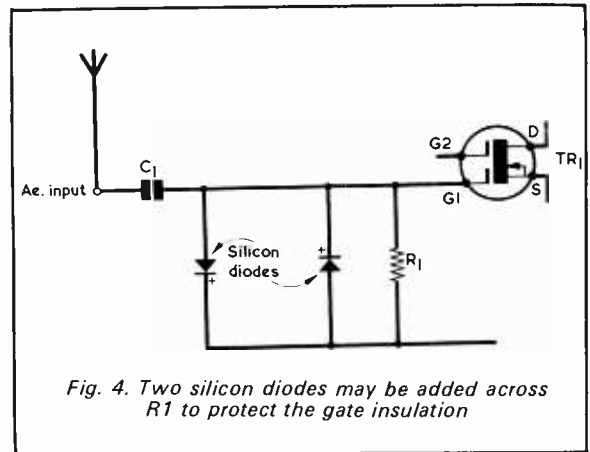


Fig. 4. Two silicon diodes may be added across R1 to protect the gate insulation

The prototype amplifier is housed in a small wooden box with its own PP6 battery. Unless the receiver has its positive rail earthed, it might prove difficult to power the r.f. amplifier from the receiver power supply, since the f.e.t. drain must be returned via the aerial input coil both to earth and to VDD positive. If there is a coupling capacitor in the receiver input circuit, this should be removed.

Should the amplifier be coupled to a large outdoor aerial there is a possibility that static 'spikes' could be passed to gate 1 during thundery weather and cause breakdown of the gate insulation. This risk may be overcome by connecting two silicon diodes across R1 in the manner shown in Fig. 4. These diodes become conductive at around 0.6 volt and would not therefore affect the much lower amplitude aerial input signals. The diodes were not considered necessary in the author's case, as the aerial normally employed is a relatively small indoor one.

# Constant Current Lamp Circuit

by  
L. Stephenson

The mysterious behaviour of three lamps connected in series.

HERE IS A SIMPLE AND INSTRUCTIVE LITTLE DEVICE which can mystify your electrically minded friends and acquaintances. It also demonstrates an important characteristic of the transistor.

## SHORT-CIRCUITED LAMPS

The device can be presented in the form of a small box on which are mounted a switch and three m.e.s. torch bulbs rated at 2.5V 0.3A. These bulbs are fitted in Bakelite bulbholders having screw terminals of the type sold in Woolworths' stores, and they are obviously connected in series. The two end wires from the chain disappear into the inside of the box through two holes. Also provided are two test prods connected together by a short length of flexible wire. See Fig. 1.

When the switch on the box is operated the bulbs light up. The person to whom the device is being demonstrated is then invited to take up the test prods

and short-circuit any one bulb, any two bulbs, or all three, by applying the prod ends to the bulbholder terminals. He will find, as is to be expected, that the short-circuited bulb or bulbs become extinguished. What is not so easy of explanation is that the remaining bulb or bulbs continue to glow at unaltered brilliance! Even when two bulbs are short-circuited, there is no change in the brightness of the third bulb which remains lit. If all three bulbs are short-circuited they all extinguish, but there are no sparks at the end terminal as would be evident if they were supplied by a battery in the normal way.

It is obvious that there is a mysterious element in the supply circuit which feeds the bulbs, and this is indeed the case. Fig. 2 shows the complete circuit, and it will be seen that the bulbs appear in the collector circuit of an AD162 transistor, this being connected so that it supplies a constant current. The additional components shown in Fig. 2 can be mounted inside the box on which the three bulbholders are fitted.

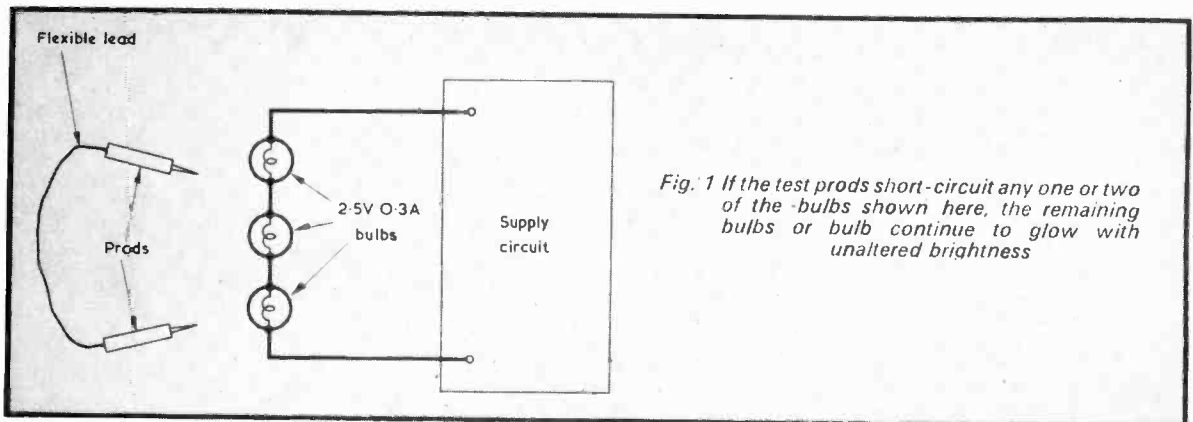


Fig. 1 If the test prods short-circuit any one or two of the bulbs shown here, the remaining bulbs or bulb continue to glow with unaltered brightness



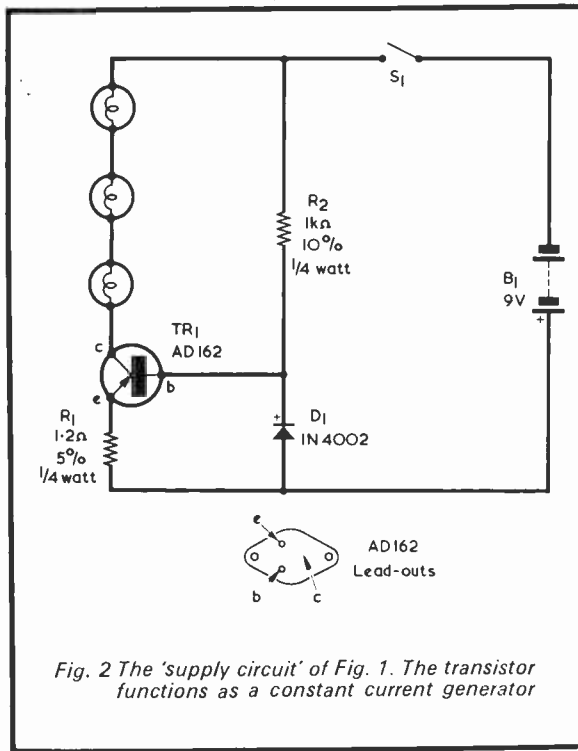


Fig. 2 The 'supply circuit' of Fig. 1. The transistor functions as a constant current generator

### GROUNDING BASE

In Fig. 2, the AD162 is employed, effectively, in the grounded base mode. Transistors connected in the grounded base configuration exhibit the collector current-collector voltage characteristics illustrated in Fig. 3. The different lines shown here correspond to different values of emitter current. It will be seen that, at any given emitter current, as soon as collector voltage (with respect to base) passes the zero voltage point the collector current obtained remains virtually unaltered for all further increases in collector voltage.

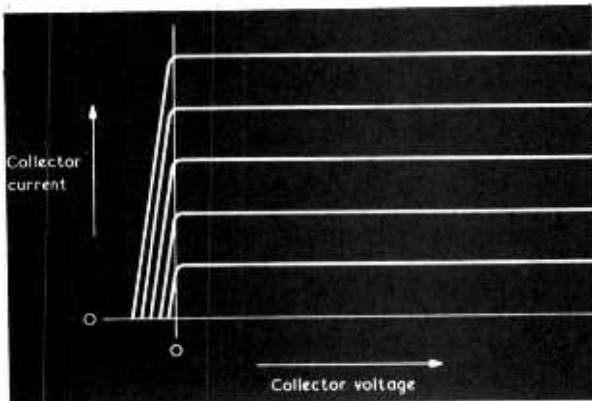


Fig. 3 Typical collector current-collector voltage characteristic curves for a grounded base transistor. The different curves correspond to different emitter currents

The collector voltage can be given any value (provided it isn't made so high as to cause the maximum ratings for the transistor to be exceeded) but there is no change in collector current.

In Fig. 2 the AD162 transistor is in the grounded base mode because its base is held at a constant potential with respect to the positive supply line due to the presence of silicon diode D1. This diode is made to pass forward current by R2 and, since it is a silicon component, a fixed voltage of about 0.55 volt appears across it. The transistor then has bias current applied to its emitter via R1. The AD162 is a germanium transistor, with the result that a voltage of approximately 0.2 volt appears across its base-emitter junction. In consequence, about 0.35 volt appears across R1, and from Ohm's Law ( $I = \frac{E}{R}$ ) a current of very nearly 0.3A flows through it.

The current gain for a transistor in the grounded base mode is always a little less than 1, so slightly less than 0.3A flows in the bulbs.

Since the collector current of the AD162 transistor is unaltered by the collector voltage all that happens, when short-circuiting any one or two of the bulbs, is that the collector voltage increases and that the same current continues to flow through the remaining bulb or bulbs. When all three bulbs are short-circuited the collector potential is equal to that on the negative terminal of the battery, but the same current still continues to flow. In this case it flows through the flexible wire joining the two test prods together (and, of course, in the remaining wires of the battery circuit).

The transistor configuration in Fig. 2 represents what is sometimes referred to as a 'constant current generator', and is frequently encountered in linear integrated circuits in which it acts as a common emitter supply element for two transistors in a differential amplifier. For the circuit to give as nearly unvarying a collector current as possible, the current flowing in D1 should be significantly larger than the collector current divided by the hFE of the transistor. The hFE of the AD162 transistor is quoted as 80-320, and if we choose the lower of these two figures (because it will give the highest current figure after division and thus correspond to the worst possible case) we find that the current in D1 should be greater than about 0.3A divided by 80, or about 3.75mA. The forward current in D1 provided by R2 (taking into account the 0.55 volt dropped across the diode) is approximately 8.4 volts divided by 1kΩ, which works out as 8.4mA. For present requirements, this current is adequately in excess of the 3.75mA which is required if an AD162 having the lowest gain figure for this type is used.

### COMPONENTS

Some difficulty may be experienced in obtaining the 1.2Ω resistor R1. A 1.2Ω 1/4 watt resistor is, however, available from Home Radio under Cat. No. R5/8. A 1.2Ω resistor having a higher wattage rating than the 1/4 watt figure shown in Fig. 2 can, of course, be used if available. Diode D1 can be any small silicon rectifier, instead of the 1N4002 indicated in Fig. 2. If the circuit is to be used for long periods, a good choice for B1 is given by three 3-volt cycle lamp batteries (Ever Ready No. 800) connected in series.

The AD162 transistor should be mounted on a metal heat sink measuring 1 1/2 by 2 in. This will provide more than adequate cooling.

# TRANSMITTER

## For 160 Metres

by F. G. Rayer

This article describes the circuit of a 160-metre transmitter-receiver and commences to give details of construction. These will be completed in the concluding article, to be published next month, which will also deal with the processes of setting up and operation.

**A**LTHOUGH THIS EQUIPMENT WAS BUILT TO GIVE A compact mobile station, it has proved highly satisfactory also at the author's permanent location. It covers 1.8 to 2.0MHz, with 10 watts input, adequately modulated, when transmitting. On reception the receiver section, which has a tuned r.f. stage, gives good sensitivity and freedom from second channel interference. An internal speaker is fitted. It is thus only necessary to provide a power supply, aerial and microphone to obtain a complete Top Band station.

### SWITCHING

In equipment of this nature it is possible to have one or more circuits common to both receiving and transmitting sections. After experiments, however, common stages were not incorporated in the present design, the benefit being that each stage could then be designed for its own particular purpose only, whereupon there is a considerable simplification in switching. Other transmitter techniques, such as using the transmitter p.a. coil for aerial tuning on reception, were also tried but discarded. In this particular case, a separate aerial coil for reception gives a worth-while improvement in rejecting second channel signals.

Instead of switching a single meter to indicate p.a. input when transmitting and signal strength when receiving, a permanently connected meter is used in the transmitting circuits and an EM84 tuning indicator in the receiver section. A result of this circuitry is that the transmitter and receiver sections are virtually separate. This simplifies testing or possible modification later, and means that either the receiver or transmitter could in fact be built alone.

### RECEIVER

The circuit of the receiver section is shown in Fig. 1. S1(a)(b) is a 2-pole 2-way Transmit-Receive switch. S1(a) couples the aerial to C1 on 'Receive', whilst S1(b), applies h.t. via R15. The full h.t. voltage of around 300 volts which is available is not required for the receiver, and it is reduced to about 220 volts by means of R15, R16 and the current drawn by the receiver valves.

L1 and L2 are the aerial and mixer signal frequency coils respectively, and L3 is the oscillator coil. Details of these, and the other coils in the equipment, are given in a Table which will appear in Part 2. Coverage is 1.8 to 2.0MHz with a little to spare, and this allows for easy tuning. VC2-VC3 is a 2-gang capacitor with ball tuning drive. VC1 is a panel aerial trimmer and is peaked for best reception to ensure that changes to the aerial do not cause loss of efficiency. VR1 is the r.f. gain control.

Diode D1 provides detection and a.g.c. bias, the latter being applied to V3 and the tuning indicator, V5. VR2 is the audio gain control, being followed by the double triode, V4, which functions as a 2-stage a.f. amplifier. The circuit has some simplifications, but it easily gives adequate speaker volume. H.T. drain is about 35mA.

S2(a) is part of a 2-pole 2-way switch. Its other section (shown in Fig. 2) applies h.t. to the transmitter v.f.o. and buffer amplifier when 'Net' is selected. When S2(a) is at 'Net' it inserts R7 in the cathode circuit of V3, thereby reducing the gain of this valve and ensuring that the output of the v.f.o. does not swamp the a.g.c. circuit. As a result, the tuning indicator, V5, may be used as an aid to tuning the receiver and transmitter to the same frequency, either to commence calling on a chosen frequency or to reply to a transmission whose frequency has been located by the receiver.

# RECEIVER



Cover Feature - 2

Part 1

Assoc. I.E.R.E., G30GR

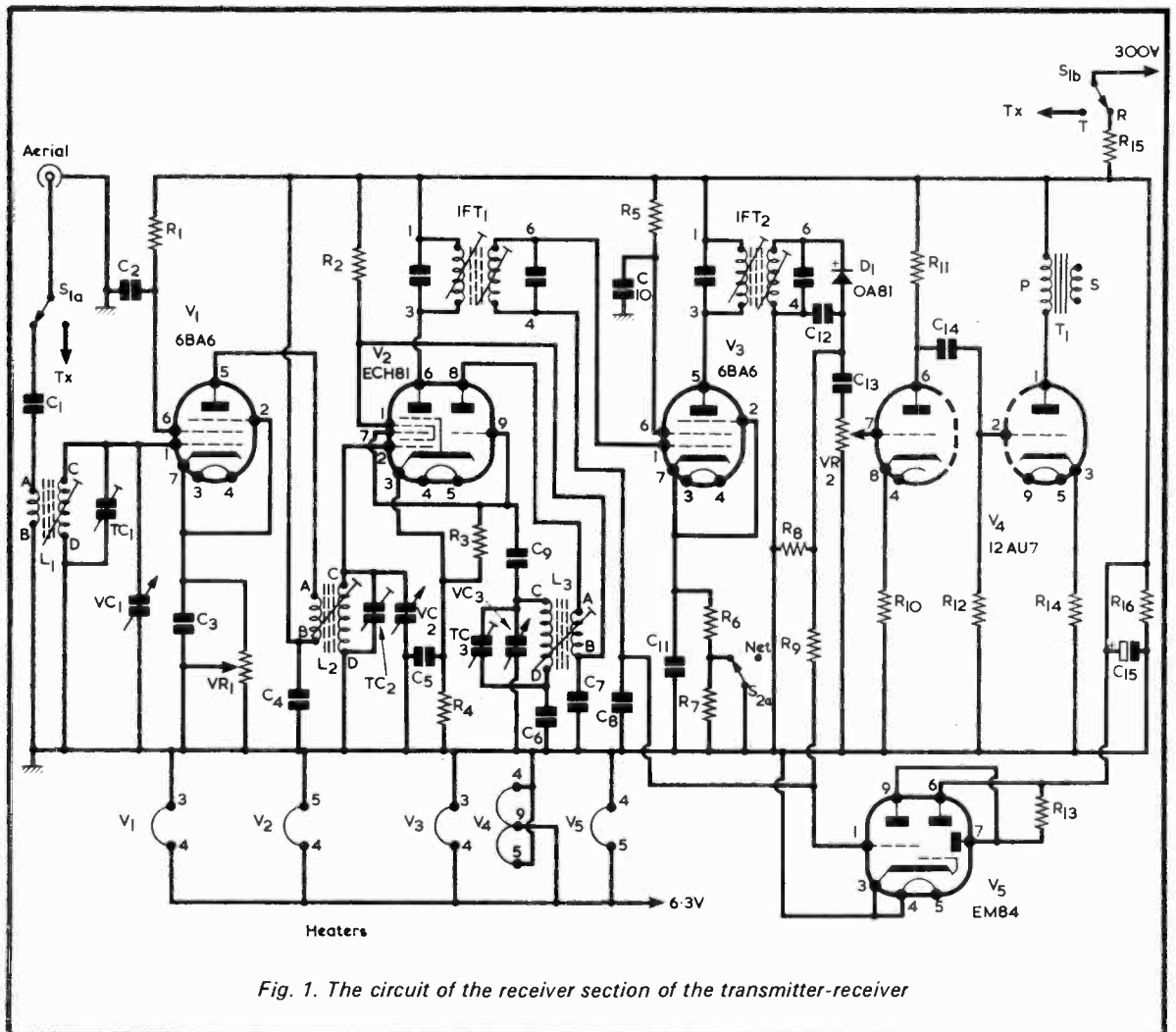
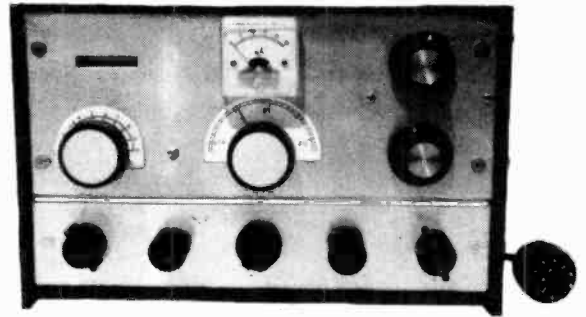


Fig. 1. The circuit of the receiver section of the transmitter-receiver

**COMPONENTS***Receiver Section**Resistors*

(All fixed values 10%)

R1	47k $\Omega$ 1 watt
R2	22k $\Omega$ 1 watt
R3	47k $\Omega$ $\frac{1}{2}$ watt
R4	220 $\Omega$ $\frac{1}{2}$ watt
R5	47k $\Omega$ 1 watt
R6	82 $\Omega$ $\frac{1}{2}$ watt
R7	220k $\Omega$ $\frac{1}{2}$ watt
R8	270k $\Omega$ $\frac{1}{2}$ watt
R9	2.2M $\Omega$ $\frac{1}{2}$ watt
R10	2.2k $\Omega$ $\frac{1}{2}$ watt
R11	220k $\Omega$ $\frac{1}{2}$ watt
R12	470k $\Omega$ $\frac{1}{2}$ watt
R13	470k $\Omega$ $\frac{1}{2}$ watt
R14	1k $\Omega$ $\frac{1}{2}$ watt
R15	5.6k $\Omega$ 5 watt
R16	22k $\Omega$ 3 watt
VR1	25k $\Omega$ 1 watt potentiometer, linear
VR2	500k $\Omega$ potentiometer, log.

*Capacitors*

(All fixed values 350 V.Wkg.)

C1	300pF silvered mica
C2	0.01 $\mu$ F plastic foil or ceramic
C3	0.01 $\mu$ F plastic foil or ceramic
C4	0.25 $\mu$ F plastic foil
C5	0.01 $\mu$ F plastic foil or ceramic
C6	400pF silvered mica
C7	0.02 $\mu$ F plastic foil
C8	0.02 $\mu$ F plastic foil
C9	45pF silvered mica
C10	0.01 $\mu$ F plastic foil or ceramic
C11	0.1 $\mu$ F plastic foil
C12	300pF silvered mica or ceramic
C13	0.01 $\mu$ F plastic foil
C14	0.01 $\mu$ F plastic foil
C15	8 $\mu$ F electrolytic
VC1	50pF variable, type C804 (Jackson Bros.)
VC2-VC3	25 + 25pF, 2-gang type U101 (Jackson Bros.)
TC1	30pF or 60pF trimmer
TC2	30pF or 60pF trimmer
TC3	30pF or 60pF trimmer

*Inductors*

L1-L3	See Table (to appear in Part 2)
IFT1	i.f. transformer type IFT11/465 (Denco)
IFT2	i.f. transformer type IFT11/465 (Denco)
T1	Small valve output transformer, ratio around 40:1, Home Radio Cat. No. TO43 or similar

*Valves*

V1	6BA6	V4	12AU7
V2	ECH81	V5	EM84
V3	6BA6		

*Diode*

D1	OA81
----	------

*Speaker* 3 $\Omega$  speaker, 3 or 3 $\frac{1}{2}$  in.*Miscellaneous*

- 2 epicyclic ball drives type 4511/F (Jackson Bros.)
- 2 B7G valveholders with skirts
- 3 B9A valveholders with skirts
- 1 spindle coupler
- Speaker fabric

**COMPONENTS***Transmitter Section**Resistors*

(All 10%)

R17	68k $\Omega$ $\frac{1}{2}$ watt
R18	4.7k $\Omega$ 1 watt
R19	15k $\Omega$ 3 watt
R20	10k $\Omega$ 1 watt
R21	33k $\Omega$ 1 watt
R22	100k $\Omega$ $\frac{1}{2}$ watt
R23	22k $\Omega$ 1 watt
R24	1k $\Omega$ $\frac{1}{2}$ watt
R25	6.8k $\Omega$ 1 watt
R26	1M $\Omega$ $\frac{1}{2}$ watt
R27	220k $\Omega$ $\frac{1}{2}$ watt
R28	470k $\Omega$ $\frac{1}{2}$ watt
R29	100k $\Omega$ 1 watt
R30	3.3k $\Omega$ $\frac{1}{2}$ watt
R31	470k $\Omega$ $\frac{1}{2}$ watt
R32	150 $\Omega$ 1 watt

*Capacitors*

(All fixed values 350 V.Wkg unless otherwise stated)

C16	150pF silvered mica 1%
C17	680pF silvered mica 1%
C18	680pF silvered mica 1%
C19	2,000pF silvered mica
C20	100pF silvered mica
C21	0.01 $\mu$ F plastic foil or ceramic
C22	0.01 $\mu$ F plastic foil or ceramic
C23	100pF silvered mica
C24	2,000pF plastic foil 500 V.Wkg
C25	2,000pF plastic foil 600 V.Wkg
C26	2,000pF plastic foil 600 V.Wkg
C27	22pF silvered mica or ceramic
C28	2,000pF silvered mica or plastic foil
C29	0.01 $\mu$ F plastic foil
C30	25 $\mu$ F electrolytic, 25 V.Wkg
C31	0.01 $\mu$ F plastic foil, 600 V.Wkg
VC4	100pF variable, type U101 (Jackson Bros.)
VC5	500pF variable, type E1 (Jackson Bros.) or similar
VC6-VC7	500 + 500pF, 2-gang, type L2 (Jackson Bros.) or similar
TC4	30 or 60pF variable, ceramic or air-spaced

*Inductors*

L4-L7	See Table (to appear in Part 2)
RFC1	2.5mH r.f. choke, type CH1 (Repanco)
RFC2	2.6mH r.f. choke, type RFC5 (Denco)

*Valves*

V6	6C4
V7	6AM6
V8	5763
V9	12AX7
V10	EL84
V11	OB2

*Meter*

M1	0-100mA moving-coil meter. Henelec 38 series, or similar. (See text)
----	--

*Miscellaneous*

- 2 B7G valveholders with skirts and cans (for V6, V7)
- 1 B9A valveholder with skirt and can (for V9)
- 2 B9A valveholders
- 1 B7G valveholder

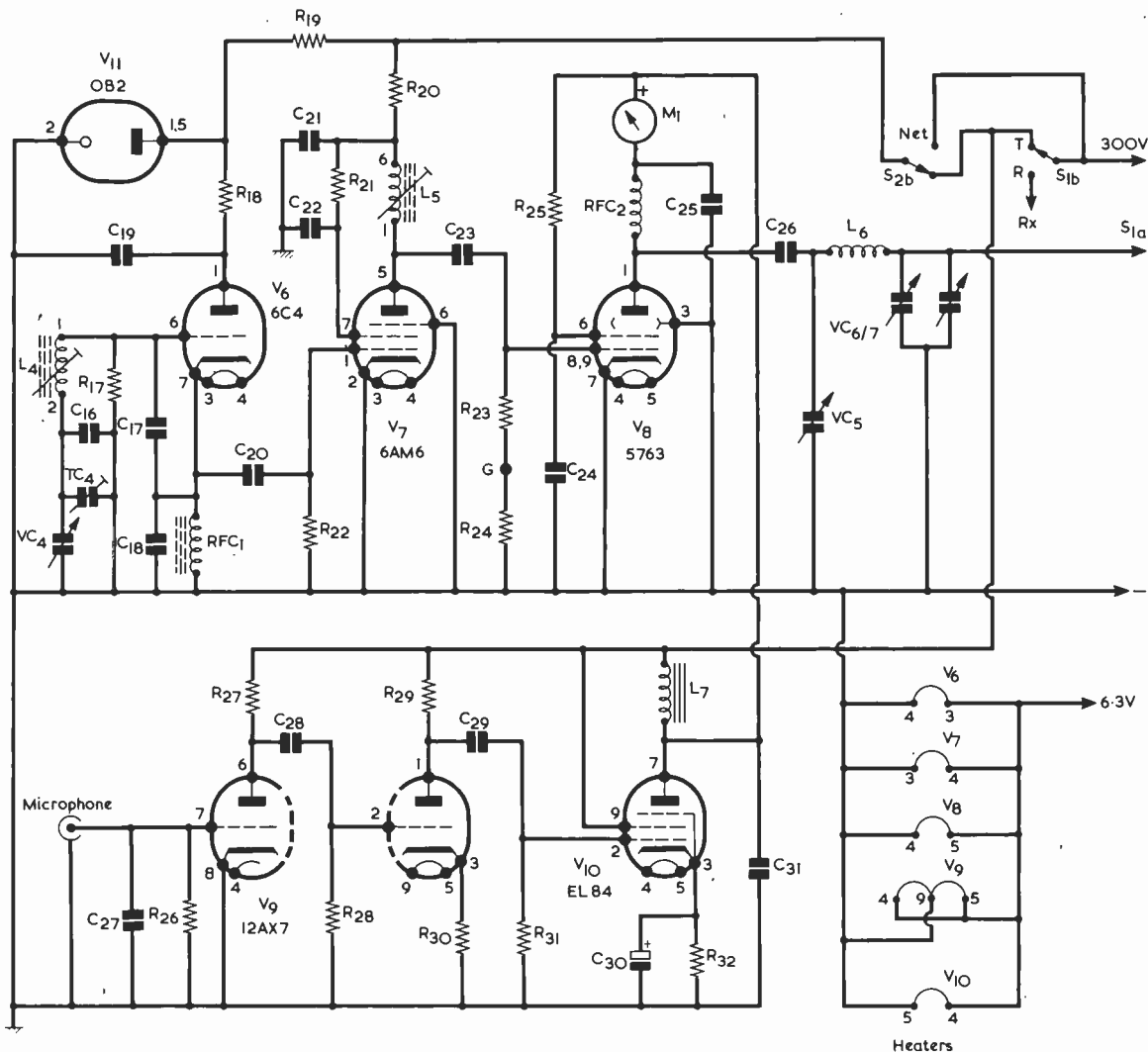


Fig. 2. The transmitter and modulator section

## COMPONENTS

### Common Items

#### Switches

- S1(a)(b) 2-pole 2-way rotary
- S2(a)(b) 2-pole 2-way rotary

#### Miscellaneous

- 2-off coaxial sockets
- 7-off  $\frac{3}{8}$  to 1 in. knobs
- 2-off  $1\frac{1}{2}$  in. knobs
- 2-off 'Universal Chassis' flanged members 10 by 4 in. Cat. No. CU58A (Home Radio)
- 2-off flanged members, 10 x 2 in., Cat. No. CU139 (Home Radio)
- 1-off flanged member, 9 x 2 in., Cat. No. CU138 (Home Radio)
- 1-off flat plate, 10 x 8 in., Cat. No. CU195 (Home Radio)
- 1-off flat plate,  $2\frac{1}{2}$  x  $3\frac{1}{2}$  in.
- Case sides, top and bottom (see text)
- Tagstrips, solder tags, etc.

## TRANSMITTER

The transmitter circuit is shown in Fig. 2. Here, V6 is the v.f.o., and is tuned by VC4. Its h.t. supply is stabilized by V11. The band coverage is adjusted for 1.8 to 2.0MHz, with a little extra at the extreme positions of VC4, by adjusting TC4 and the core of L4.

The particular capacitor specified for VC4 may be difficult to obtain from retail sources. It can, if necessary be purchased direct from its manufacturers, Jackson Brothers (London) Limited, Kingsway, Waddon, Croydon, CR9 4DG.

V7 is a buffer amplifier, L5 being broadly resonant at about 1.9MHz. S2(b) allows h.t. to be applied to V6 and V7 alone when 'Net' is selected. When S1(b) is set to 'Transmit', h.t. is applied to all the transmitter stages.

The power amplifier, V8, is easily capable of offering the full 10 watts allowed on the band. A meter clipped between point 'G' and chassis allows V8 grid current to be checked when initially setting up the circuit. The pi tank network given by VC5, L6 and VC6-7 allows loading of the p.a. stage by the usual aerials, and meter

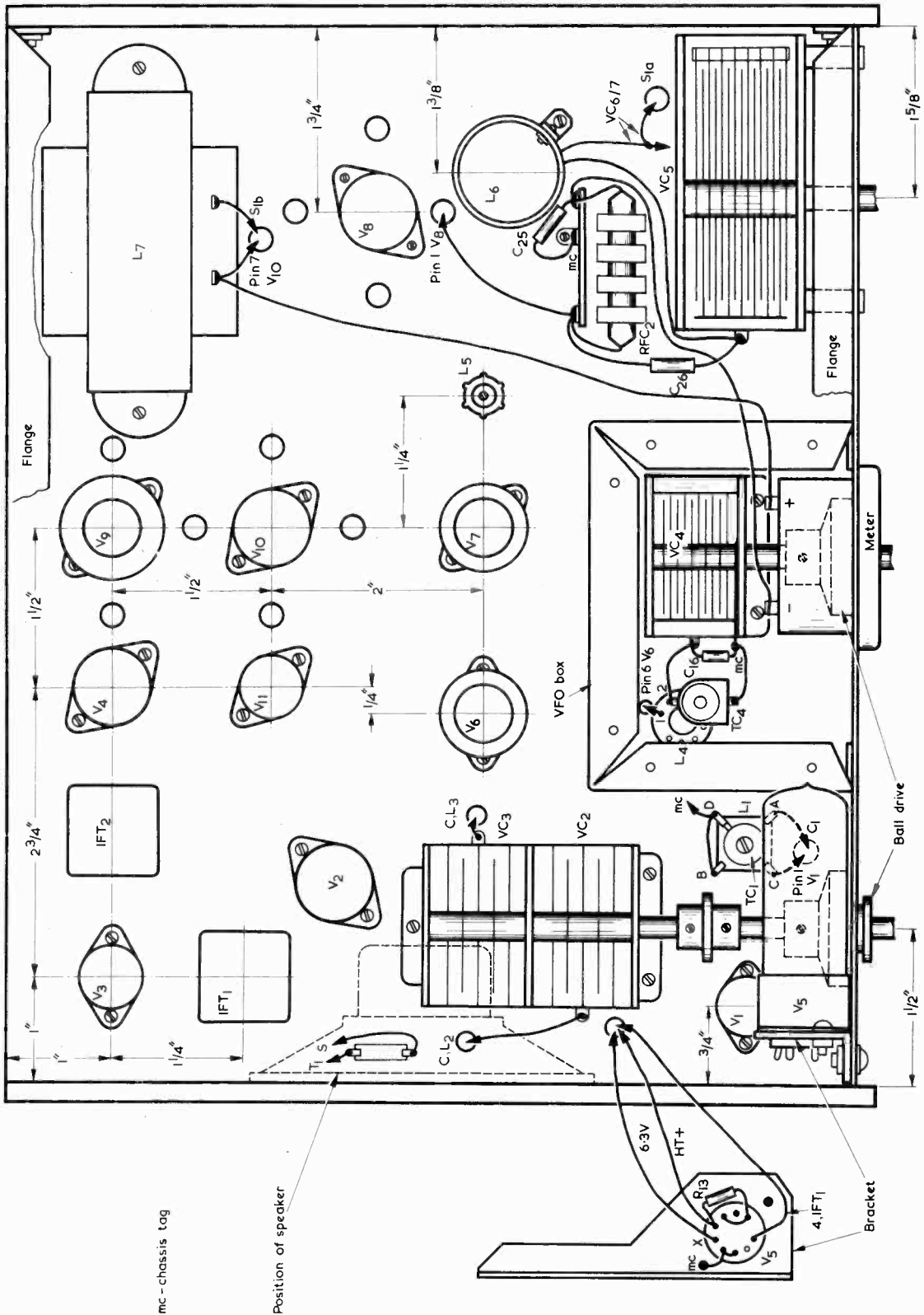


Fig. 3. Components and wiring above the chassis

M1 indicates the p.a. anode current.

V9 is a double-triode which provides two stages of a.f. amplification, and is followed by the choke modulator stage incorporating V10. The modulation amplifier given by V9 and V10 is intended for operation with a general purpose crystal microphone, with which it provides adequate gain. The gain can be increased a little by connecting a capacitor of around  $50\mu\text{F}$  at 6 V.Wkg across R30, but this was not found necessary with the prototype.

No general h.t. bypass capacitor is included in the modulation amplifier circuit. This was found to work quite satisfactorily with leads to the power supply about 4 ft. long. If any trouble does arise due to the lack of a bypass capacitor (caused perhaps by a high output impedance in the supply) a  $32\mu\text{F}$  450 V.Wkg capacitor could be added between the amplifier h.t. positive line and chassis.


The power output of V10 is about 6 watts and, bearing in mind inevitable circuit losses and the fact that the screen-grid of V8 is modulated in addition to the anode, this output is quite adequate.

The meter employed in the prototype had an f.s.d. of 50mA and proved satisfactory in practice. However, it may be found a little more convenient to use a 0-100mA meter instead, and such a meter is specified in the Components List.

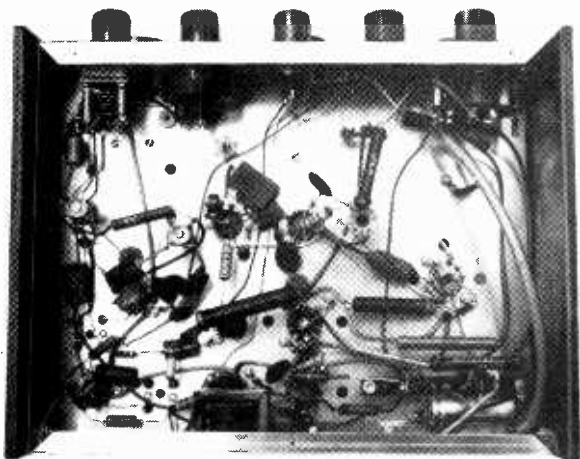
## CASE

An inexpensive, strong and satisfactory case for the transmitter-receiver is made up largely from Home Radio 'Universal Chassis' parts. The front panel consists of a 10 by 4 in. flanged member with a 10 by 2 in. flanged member below it. Similar parts are employed for the rear of the case. The valveholders and other chassis components are mounted on a 10 by 8 in. flat plate. This is sandwiched between the adjacent flanges of the flanged members which make up the front panel and the case rear.

The sides of the case are 3-plywood, varnished in advance, and they measure  $8\frac{1}{2}$  by  $6\frac{3}{4}$  ins. These dimensions allow a projection of about  $\frac{1}{4}$  in. at the front and top, and a projection of about  $\frac{1}{2}$  in. at the bottom which assists in providing ventilation. The front and rear panels are secured by bolts passing through the plywood



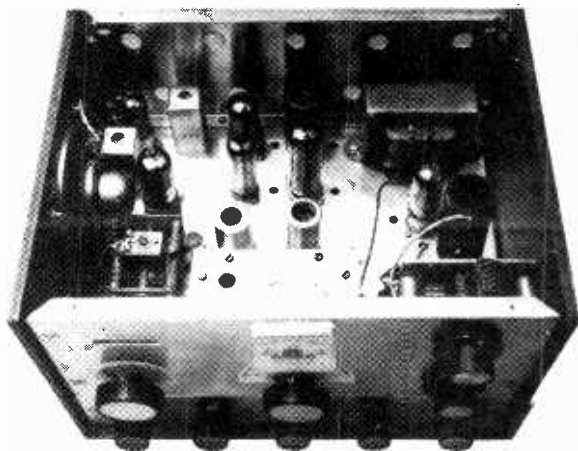*Wiring and components below the chassis*



*The components above the chassis.*

and the end flanges of the flanged members. The flanged members are supplied with holes pierced for assembly, and those which appear at the front are filled with 6BA chrome bolts and washers. It should be remembered that a 3 in. diameter cut-out for the speaker is required in the left-hand plywood panel. Its position is best adjudged with the aid of the speaker itself, and it should enable the speaker to be clear of VC2-VC3 when this is mounted.

The two sides could alternatively be made of metal, if desired. The top of the author's transmitter-receiver is plywood to match the sides but, here again, metal could also be employed. The bottom is perforated metal measuring 10 by 8 in., and is fitted to the bottom flanges of the front panel and case rear. Alternatively, a 10 by 8 in. flat plate with ventilation holes could be used. Both the top and the bottom should be mounted so that they can be easily removed for checks and adjustments.

Five holes for controls are required along the centre of the lower flanged member of the front panel. Spacing is as shown in Fig. 4. Holes are required in the lower flanged member of the case rear for the coaxial aerial socket, the microphone input socket and the power lead. The microphone socket is a little to the left of the V9 valveholder, as shown in Fig. 4, and the aerial socket and power lead hole (not shown in the diagram) are to the left of the microphone socket.

The upper flanged member of the front panel requires holes for VC2-VC3, VC4, VC6-VC7 and VC5. Those for VC2-VC3 and VC4 should be 1 in. diameter to take the ball drives and their height is marked out from the capacitors themselves. The remaining two holes for the capacitors are  $\frac{1}{2}$  in. diameter. The hole for VC6-VC7 (mounted below VC5) may be marked out with the aid of the capacitor, and that for VC5 is directly above it. These last two capacitors, are mounted by bolts which pass through the front panel, and further details concerning their mounting are given later, when the top of the chassis assembly is discussed.

If it is desired to have the front panel holes for VC2-VC3, VC4 and VC6-VC7 on a horizontal line it may be necessary for the first two capacitors to be mounted on spacing pillars. This should not be done if it results in VC4 fouling the top of the v.f.o box, which is 2 ins. deep. Next to be cut out in the upper flanged member of the front panel are holes for the meter and a rectangular opening,  $1\frac{3}{8}$  by  $\frac{1}{4}$  in., for the tuning indicator. These may be centred on a horizontal line with the spindle of VC5. Finally, two rows, each of five  $\frac{1}{2}$  in. diameter holes, are cut in the upper flanged member of the case

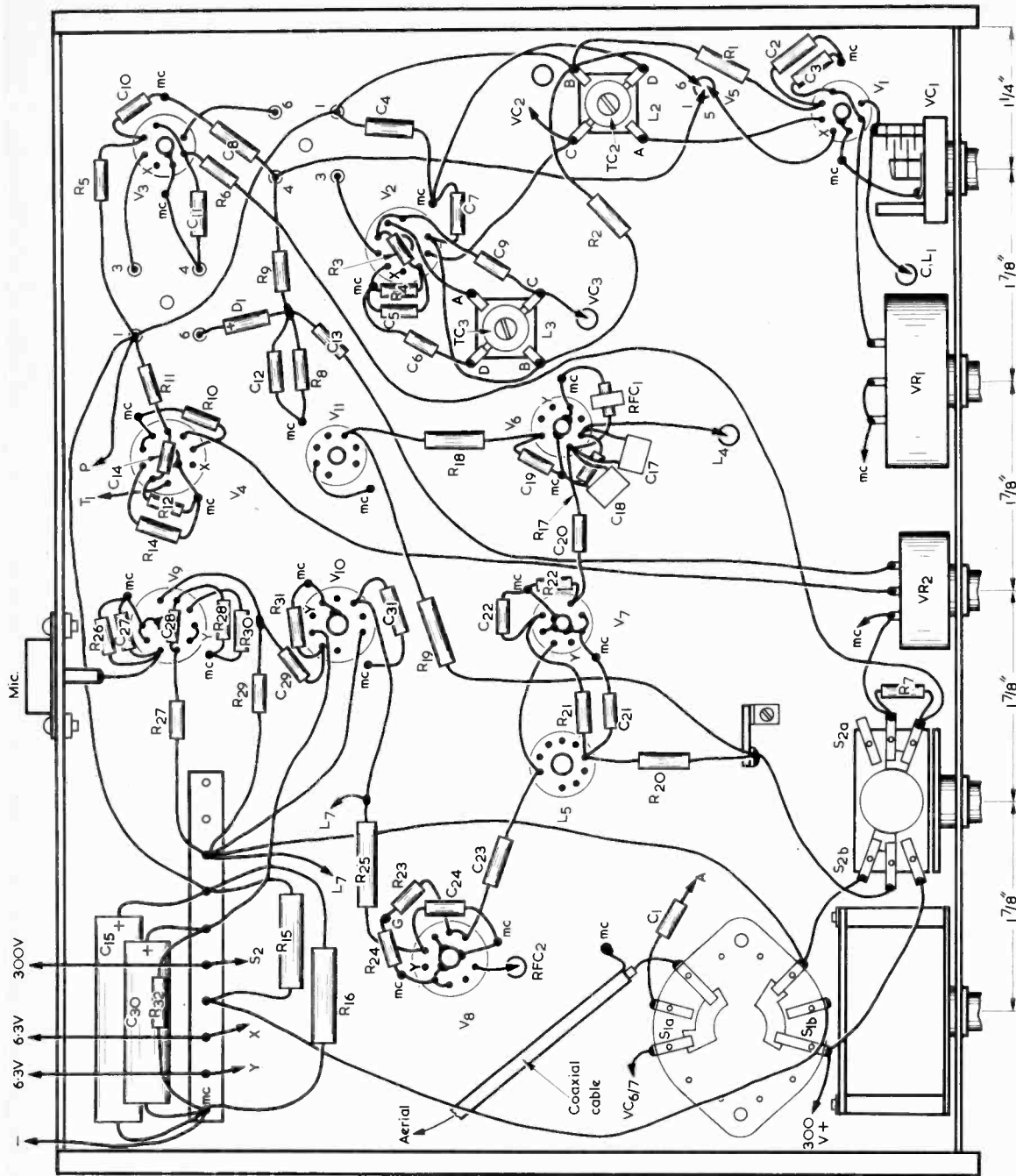


Fig. 4. Wiring and layout underneath the chassis

rear for ventilation.

Valveholder holes are next cut in the 10 by 8 in. flat plate. Orient the valveholders to the positions shown in Fig. 4 and use them to mark out their mounting holes. Drill these for 6BA bolts. A few  $\frac{1}{4}$  in. holes are drilled around the holders for V8 and V10 to provide ventilation. Note that some of the valves require skirted valveholders, these being noted in the Components List. V6, V7 and V9 are fitted, also, with screening cans. Drilling should, at this stage, be carried out for the i.f. transformers and other items, as indicated in Figs. 3 and 4. The holes for the i.f. transformer pins should be large

enough to ensure adequate clearance. Insulated sleeving may be passed over these pins when the transformers are mounted, to ensure full insulation.

#### NEXT MONTH


Details of construction will be continued in the concluding article, which will appear in next month's issue. Some of the parts specified in the Components List will also be discussed further next month, these including, in particular, the coils.

(To be concluded)

RADIO & ELECTRONICS CONSTRUCTOR



# KIT REVIEW . . .

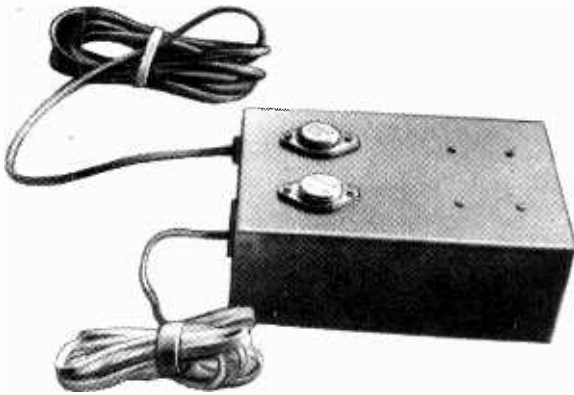


## D.C. TO A.C. INVERTER KIT

Easily assembled kits which provide a 240 volt a.c. output from a 12 volt input


WITH THE CURRENT WIDESPREAD INTEREST IN caravanning, camping and boating, the ability to obtain a 240 volt a.c. supply from a 12 volt accumulator becomes very attractive. Simple transistor inverter kits are available from Henry's Radio Ltd., 303 Edgware Road, London, W.2 and these offer an output of 240 volts a.c. at a nominal frequency of 50Hz. Typical facilities offered by the inverters are the operation of electric razors and fluorescent lamps.

The kit shown in the accompanying photographs is the Type TT51A. This was recently assembled by the writer and provides an output of 15 watts. The kit comes complete with chassis, transformer and transistors, together with miscellaneous hardware and wire.

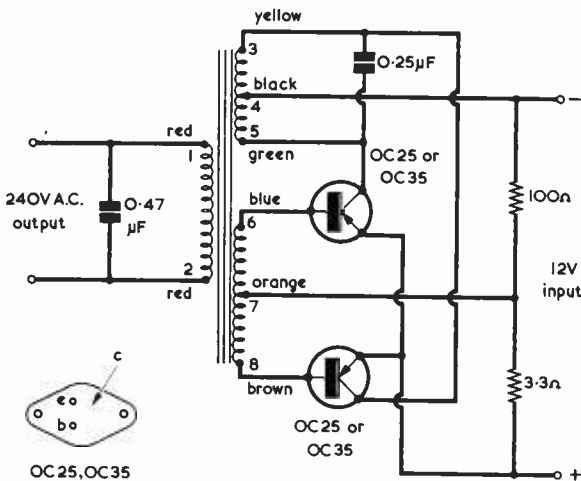Construction can be completed within a couple of hours or so and presents few difficulties, even for the newcomer to do-it-yourself electronic construction. The photograph of the chassis interior illustrates how the various parts are accommodated, and gives an idea of the general layout of the components.



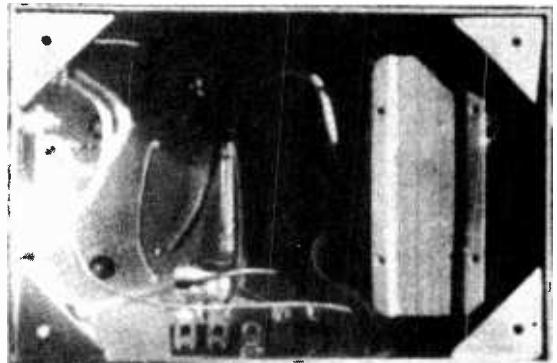The circuit of the transistor d.c. to a.c. inverter type TT51A. The two transistors oscillate to produce the a.c. output. Input current at full load is 2 amps.




The internal components fit neatly inside the chassis

The chassis is supplied ready drilled to take the two transistors, which have to be insulated from it by means of mica washers and insulating bushes. The transistors are still in close thermal contact with the chassis, which acts as a heat sink. It is important to connect up the transformer correctly, and failure of the unit to function on completion will most probably be due to incorrect transformer connections.

The writer had little difficulty in assembling the unit, which worked perfectly as soon as construction was finished.

# SHORT WAVE NEWS

## FOR DX LISTENERS

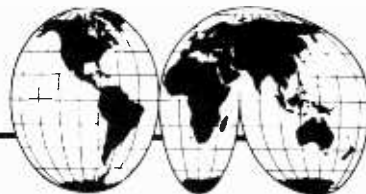

By Frank A. Baldwin

Times = GMT

Frequencies = kHz

Conditions on the short wave Broadcast Bands, up to the time of writing, have been rather poor to say the least. In fact, the writer cannot remember any other period in the past when worthwhile Dx signals were so hard to come by – and the memory goes back some forty years. Two well-known Dxers in recent conversations with the writer told how they even thought things were amiss with their respective receivers – no doubt others had the same thoughts! However, during the past few days breaks have appeared through the gloom and we have managed to log some interesting transmissions. Firstly, some news.

### ●BRAZIL

The Brasilia International Service now transmits as follows – in German from 1930 to 2030, French from 2030 to 2130, in Portuguese from 2130 to 2230, in English from 2230 to 2330 and in Spanish from 2330 to 0030 on **9665** (31.03 metres), **11720** (25.59m) and on **15447** (19.42m).

### ●GREECE

A new 100kW transmitter now radiates the Domestic Service (entirely in Greek) in various time-periods throughout the day from 0500 to 2250. That beamed to Europe is from 1900 to 1950 on **5960** (50.33m).

### ●TUNISIA

Radio Tunis, according to reports, is currently operating on **11925** (25.15m), **11970** (25.06m) and on **15266** (19.65m) from 0600 through to 1700.

### ●TURKEY

Radio Ankara now broadcasts to Europe in English from 2200 to 2230 on **11880** (25.25m).

### ●PAKISTAN

Radio Pakistan transmits to the U.K. in English from 2000 to 2130 on **7095** (42.28m), **7235** (41.46m) and on **9465** (31.69m).

### ●CONGO REPUBLIC

Brazzaville can be heard on **15190** (19.74m) carrying the local domestic service "The Voice of the Revolution" from 0600 to 1300 and from 1500 to 2130.

### ●FINLAND

Broadcasts in English to Europe from Helsinki may be heard on **15185** (19.75m) from 1400 to 1430, from 1800 to 1830 and from 2030 to 2100.

### ●KUWAIT

Radio Kuwait radiates in English from 1630 through to 1900 on **9750** (30.76m) and on **15415** (19.46m).

### ●CHINA

Radio Peking beams a programme in English to Europe from 2030 to 2130 on **6270** (47.84m), **6610** (45.38m) and on **7590** (39.52m).

## CURRENT SCHEDULES

### ●CANADA

Radio Canada International radiates the following programmes in English to Europe – from 0700 to 0730 on **5975** (50.20m) and on **9625** (31.16m); from 1217 to 1313 on **15325** (19.57m) and **17820** (16.83m); from 1515 to 1522 (News) on **15325**, **17820** and on **21595** (13.89m) and from 2115 to 2152 on **6165** (48.66m), **9610** (31.21m) and **11850** (25.31m) all on a daily basis. On Saturdays and Sundays only the last transmission period is subject to the following time change – from 2100 to 2152.

### ●SWITZERLAND

SBC Berne has the following schedule in English for Europe – from 0700 to 0730 on **3985** (75.28m), **6165** (48.66m), **9535** (31.46m), **9590** (31.28m), **11775** (25.47m), **15305** (19.60m) and on **21520** (13.94m).

From 1100 to 1130 on **3985**, **6165**, **9535**, **15430** (19.44m.), **17795** (16.85m), **21520** and on **21585** (13.89m).

From 1315 to 1345 on **3985**, **6165**, **9535**, **11870** (25.27m), **15305**, **17830** (16.82m), **21520**.

From 1530 to 1600 on **3985**, **6165**, **9535**, **9590**, **11870** and on **15305**.

From 2100 to 2130 on **3985**, **6165**, **9535**, **9590**, **11720**, **11870** and on **15305**.

### ●CZECHOSLAVAKIA

Radio Prague has the following schedule in English directed to the U.K. From 1500 to 1530 on **6055** (49.46m) and on **9505** (31.56m). From 1630 to 1700 on **5930** (50.59m) and on **7345** (40.84m); from 1900 to 1930 on **5930** and on **7345** and from 2200 to 2230 on **6015** (49.87m).

The Radio Prague "Inter Programme" for Europe in English is as follows, all on **6055** and on **9505**, from 0745 to 0800, from 0845 to 0900, from 0945 to 1000, from 1045 to 1100 and from 1145 to 1200.

### ●NETHERLANDS

Radio Nederland has the following schedule in English for Europe (Mondays to Saturdays inclusive) from 0930 to 1050 on **6140** (48.85m) and **7275** (41.23m) from the Lopik (Netherlands) transmitter. From 1400 to 1520 on **6020** (49.83m) and **21480** (13.96m) from Lopik and on **11740** (25.55m), and **17810** (16.84m) from Madagascar. From 1830 to 1950 on **6020**, **15350** (19.54m) and **17830** (16.82m) Lopik, also on **15375** (19.51m) from Bonaire (Netherlands Antilles).

### ●SWEDEN

Radio Sweden, in English for Europe, as follows – from 1100 to 1130 on **9630** (31.15m) and **21690** (13.83m); from 1230 to 1300 on **9630** and **9715** (30.88m); from 1600 to 1630 on **6065** (49.46m) and **11930** (25.14m) and from 2045 to 2115 on **6065** and **9715**.

## ●SOUTH AFRICA

Radio RSA "The Voice of South Africa", Johannesburg, radiates in English to Europe as follows – on weekdays from 1900 to 1950 on **7270** (41.26m), **11970** (25.06m) and on **15175** (19.76m); from 2215 to 2315 on **9525** (31.49m), **11900** (25.21m), **11970** and on **15220** (19.71m). On Sundays only from 1000 to 1150 on **21535** (13.93m).

A weekday omnidirectional transmission in the General Service is radiated in English from 0930 to 0946 on **17820** (16.83m), **21535** (13.93m) and on **25970** (11.55m).

## ●INDONESIA

"The Voice of Indonesia", Jakarta, has current programmes in English directed to Europe and the U.K. from 1900 to 2000 on **11715** (25.60m). Also in English as follows – from 0900 to 0930 on **6045** (49.62m) and **11715** to S.E. Asia and Pacific; from 1100 to 1200 on **9585** (31.29m) to Australia, N. Zealand and Pacific; from 1430 to 1530 on **9585** to S.E. Asia, India, Pakistan, Japan and N. America and from 2330 to 2400 on **7270** (41.26m) and **9585** to Malaysia, S.E. Asia and Pacific and to Singapore.

## ●NIGERIA

"The Voice of Nigeria", Lagos, broadcasts in English to Europe from 0545 to 0735 on **7255** (41.35m), **11900** (25.21m) and on **15185** (19.75m) and from 1800 to 1930 on **7275** (41.23m), **11770** (25.48m) and on **15185**.

Also in English to Africa and the Middle East from 1530 to 1700 on **7275**, **15120** (19.84m) and on **15185**; from 1800 to 1930 on **7275**, **11770** and on **15185**.

## ●HUNGARY

Radio Budapest transmits a programme for Dxers, in English to Europe, from 1615 to 1630 on **6025** (49.79m), **7220** (41.55m), **9833** (30.50m), **11910** (25.18m), **15160** (19.78m), **17890** (16.76m) and on **21505** (13.95m). Also from 2245 to 2300 on **6025**, **7220**, **9833**, **11910**, **15415** (19.46m), **17890** and on **21685** (13.83m).

## ●DX PROGRAMMES

Such programmes are radiated from many stations throughout the world on a regular basis. Listed here are those in English to Europe on Saturdays and Sundays.

### Saturday

Berne, Switzerland, on 2nd and 4th Saturdays in month, at 0710 on **3985** (75.28m), **6165** (48.66m) and on **9535** (31.46m); also at 1110, 1325 and at 1540 on the same channels.

Radio Canada International, at 0715 on **5975** (50.20m) and on **9625** (31.16m); also at 2124 on **6165** (48.66m), **9610** (31.21m) and on **11850** (25.31m) and at 2316 on **5990** (50.08m), **9625** and on **11945** (25.11m).

Trans-World Radio, Monaco, at 0930 on **9640** (31.12m) and at 1745 on **7180** (41.78m) or **7245** (41.40m).

### Sunday

Radio Australia at 0727 on **9570** (31.34m) and on **11765** (25.49m), and from 1300 on **9580** (31.31m) and on **11710** (25.61m) – this latter transmission to Eastern North America.

Radio Japan at 0810 on **17710** (16.93m) and on **17825** (16.83m); at 1010 on **5990** (50.08m), and on **9560** (31.38m), also at 1410 on the latter two channels and at 2040 on **7195** (41.69m) and on **9735** (30.81m) and from 2310 on **9735** (30.81m) and on **15105**

(19.86m). On the 1st and 3rd Sundays, an additional transmission is made in Swedish at 0650 on **17710** and on **17825**.

Radio Norway at 1220 on **6130** (48.93m) also at 1820, both on 1st Sunday in month only.

BBC World Service, 0815 on World Service channels.

## AROUND THE DIAL

### ●VATICAN

Vatican radio can be heard with a programme in English at 2045 on **6190** (48.46m), also heard in parallel on **9645** (31.10m).

### ●INDIA

All India Radio, Delhi, can be logged at 2100 on **9525** (31.49m) when a programme of Indian music with English announcements is usually featured. Delhi can also be logged on **4860** (61.72m), we heard them at 2220 in English with local music and identification and sign-off at 2230.

### ●MOZAMBIQUE

Radio Clube Mozambique can be logged on **4855** (61.79m) around 1930 onwards. We heard them at 1950 with announcements in French and light music.

### ●ALBANIA

Radio Tirana can be heard on 7065 (42.46m) at 2045 with a programme in English. May I call attention to the fact however that **7000** to **7100** is an Amateur allocation.

### ●GUINEA

The Republic of Guinea can be heard from 1830 (when we logged it) on **15310** (19.59m) with the news in French and Conakry identification at 1844.

### ●NETHERLANDS ANTILLES

Bonaire has found a very good channel in **11725** (25.58m) where we logged them at 2100 with the "Nightcall" programme, announced as being radiated every Friday and Saturday at the same time. Identification at 2127 "Trans-World Radio, Bonaire, Island of Flamingoes, famous for tea and sunshine".

### ●CHINA

Dxing some Chinese stations is quite a pastime in itself. The powerful Peking transmitters are easy to log but what of the local services stations? Try for the Peking Home Service 1 on **4800** (62.50m) around 2000, or the unlisted **6210** (48.30m) discovered by the writer and heard on several occasions, or the **6225** (48.19m) Home Service 1 or **6345** (47.28m) Home Service 2, all being heard between 2000 and 2330.

### ●COLOMBIA

HJQC Radio Nacional, Bogotá, has been logged on the regular **9635** (31.13m) channel at 0058 with Latin America music and station identification in Spanish at 0100.

### ●LATIN AMERICA

Several Latin American stations, apart from that listed above, have been recently logged on the higher frequency bands, such as –

CE959 Santiago, Chile, on **9590** (31.28m) at 0057 with talk in Spanish;

ZYV40 Radio Cultura de Pocos, Brazil, on **9645** (31.10m) with identification at 2100.

ZYR227 Radio Gazeta, Brazil, on **9685** (30.97m) at 2055 with 'futebol' (what else!).

ZYB22 Radio Rio Mar, Brazil, at 2055 on **9695** (30.94m) also with 'futebol'.

# COMPREHENSIVE TRANSISTOR ANALYSER

Part 2

by H. T. Kitchen

This concluding article describes the construction and setting-up of the wide-range test instrument whose circuit and functioning were discussed last month.

## CONSTRUCTION

THE PROTOTYPE WAS BUILT INTO THE 12 BY 7 BY 7 IN. commercially available metal cabinet described in Part 1 (published last month). The front panel area of 12 by 7 in. proved just adequate for all the controls required, and these are positioned according to Fig. 4.

The panel layout is the result of much thought and component juggling and is felt to be ergonomically correct. A major 'test component safety factor' is the very close proximity of the prototype indicating lamps to the test transistor sockets.

As far as the test transistor is concerned there are two ways of connecting it into the analyser circuit. One is by

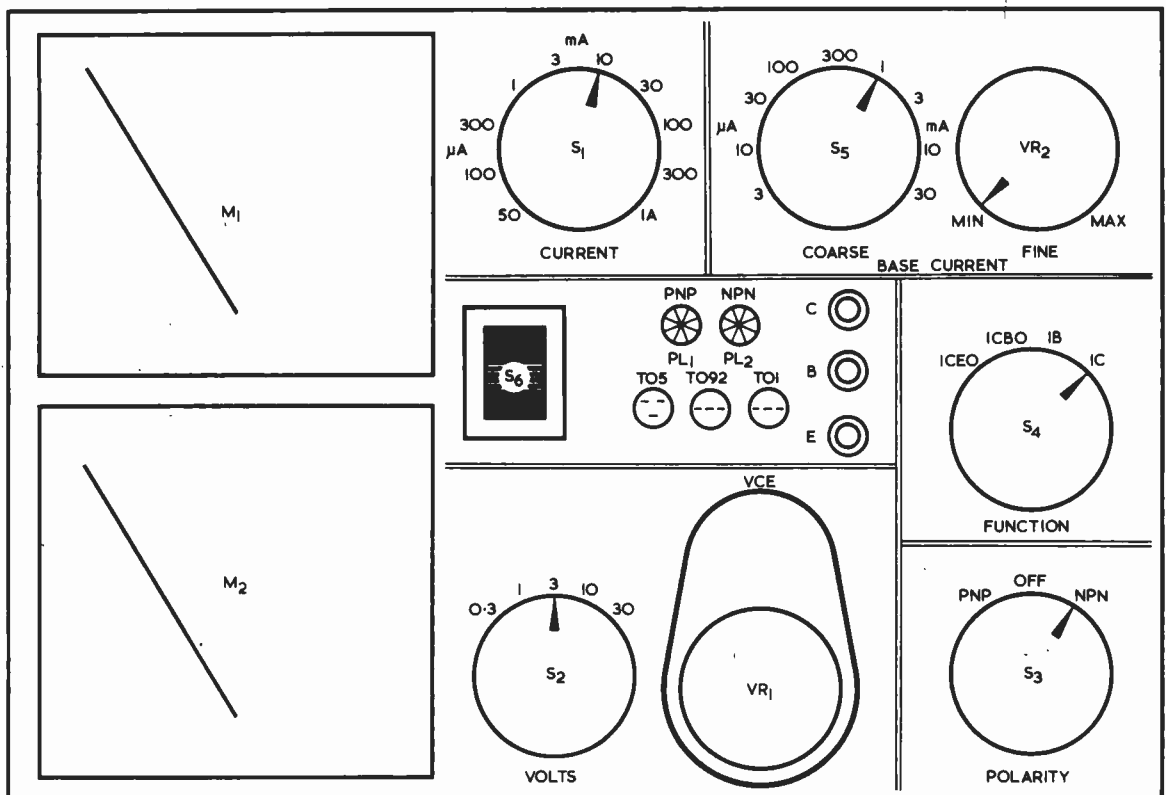


Fig. 4. The layout of the front panel of the prototype instrument

means of three separate 3 mm. sockets which enable 'outboard' testing to be accomplished by means of flying leads terminating in miniature crocodile clips. The other is by means of three panel mounted transistor sockets which enable 'inboard' testing to be accomplished. In order to accommodate the differences in lead configuration between TO5/TO18, TO1 and TO92 transistors, these sockets are wired to suit. Twisting and bending of transistor leads, with the resulting possibilities of inter-lead short-circuits, are thereby obviated. (The lead-outs of transistors in TO5/TO18, TO1 and TO92 are shown in Fig. 5.)


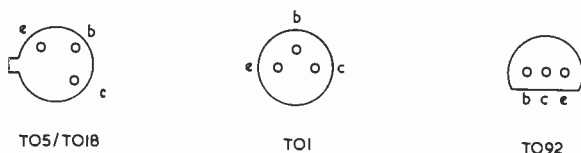


Fig. 5. The three transistor sockets are intended for TO5/TO18, TO1 and TO92 transistors. The lead-outs of these types are shown here

Finally, the two meters are mounted one above the other, so that both can be easily viewed without indulging in undue ocular contortions.

The back of panel wiring can be seen from the photographs. A detailed wiring diagram is not included, as components will vary from constructor to constructor, and such a diagram, it is felt, may cause errors in wiring up.

Three separate cableforms connect the front panel to the power supply contained within the cabinet. One cableform carries only mains voltage, to and from S6. The other two carry the main Vcc supply, the bias supply, the supplies for PL1 and PL2, and the connections for VR1 and VR2. The cableforms are secured under clips on the front panel, a rubber sleeve being interposed between the cableform and the panel to prevent chafing. P.V.C. covered 14/.0076 wire was used for these cableforms in varying colours. The use of properly laced cableforms is highly recommended, for not only do they result in a neat and durable assembly, but they also segregate the wires into groups, and so help in preventing wiring errors.

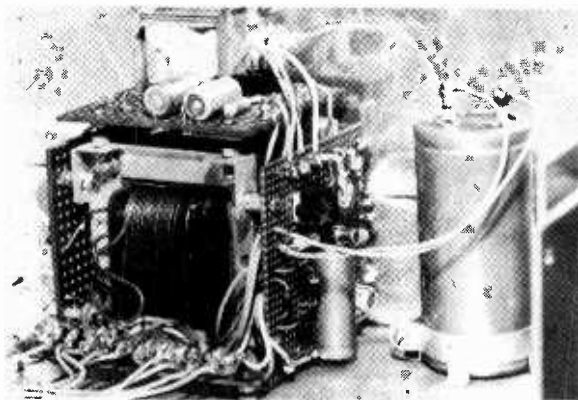

The three Veroboard panels in the power supply assembly are mounted on mains transformer T1. Capacitor C1 is mounted separately, as shown here

## Use the NEW Strip-fix Plastic PANEL SIGNS



★ SET 3 - Wording - WHITE

★ SET 4 - Wording - BLACK  
(Over 1,000 words in each set)

Illustration of actual size = RADIO

- Easy to fix - Just cut out words required remove backing and press down
- Staped in booklet form
- Designed to hang above workbench
- Pocket for loose cuttings
- Professional finish

**35p per set**  
(postage 3p)

The Perfect Transfer for  
the Home Constructor

Available from

Data Publications Ltd.  
57 Maida Vale, London W9 1SN

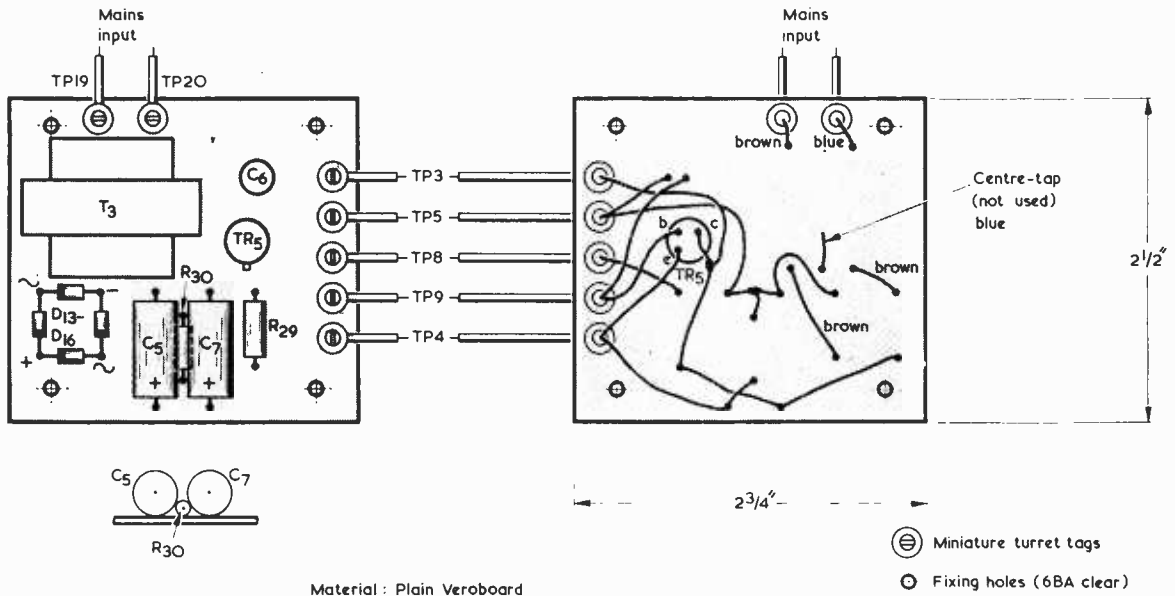


Fig. 6. Layout of the components on the bias voltage panel

VR1 should be wired up such that it inserts minimum resistance into circuit when it is fully anti-clockwise. VR2 is wired such that its slider is at the earthy end of its track (the end which connects to TP5) when it is fully anti-clockwise.

The power supply section comprises the three circuit panels of Figs. 6, 7 and 8. With the prototype it was possible to secure these to the universal mounting

flange of the Belclere transformer used for T1. A similar method of assembly should be possible with the Douglas transformer suggested as an alternative, but the positions of the mounting holes in the Veroboard panels may be different. It may also be necessary to use Veroboard panels that are a little larger than those illustrated in Figs. 6, 7 and 8. TR4 is external to the transformer and Veroboard assembly, being mounted

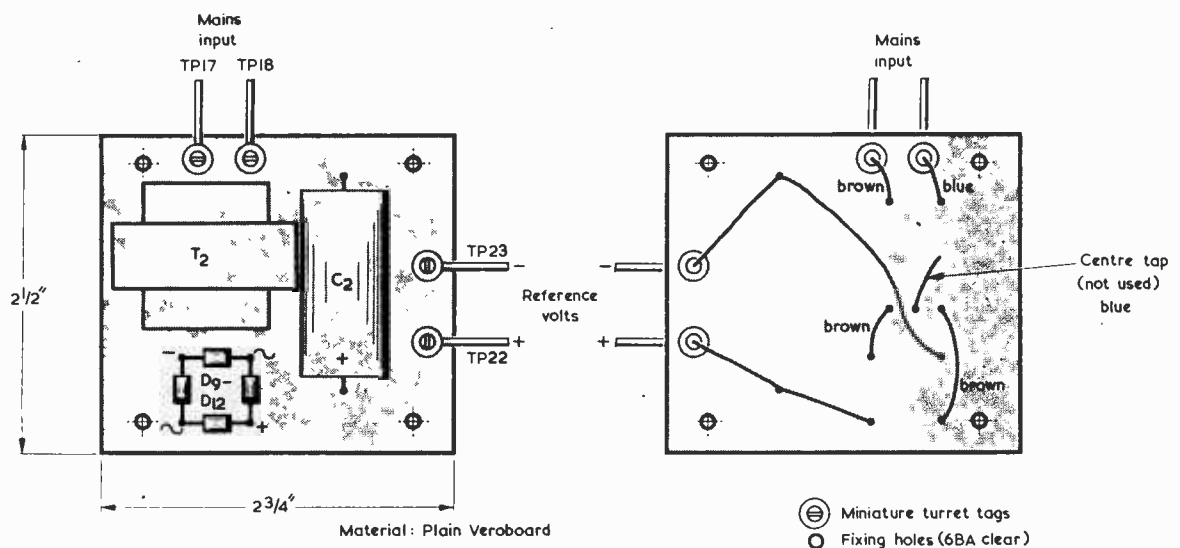


Fig. 7. Wiring and layout on the reference voltage panel

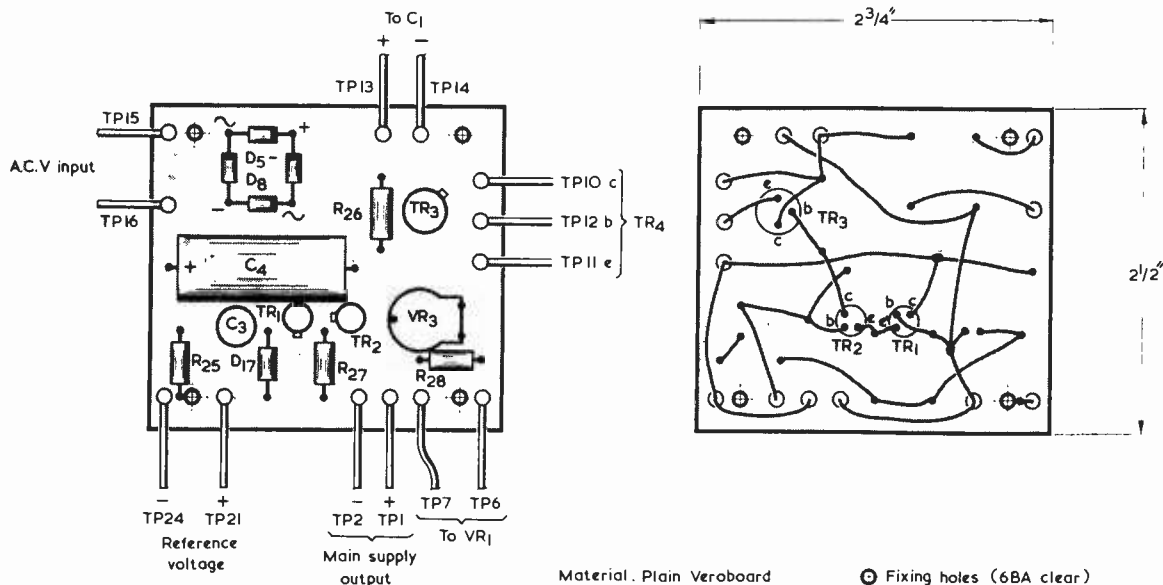


Fig. 8. The third Veroboard panel takes the main supply control components

on the rear wall of the cabinet. As previously mentioned, it is insulated from the cabinet wall by means of a mica washer and insulated mounting bushes. C1 is also external to the assembly, being fitted to the bottom of the case by means of its mounting clamp.

The three panels in the prototype comprise plain Veroboard cut into  $2\frac{3}{4}$  by  $2\frac{1}{2}$  in. pieces, each being secured to the transformer frame by means of 6BA nuts and bolts, but spaced away from it by  $\frac{1}{8}$  in. Four holes, 6BA clearance, must be drilled in each corner of each board, these corresponding to the hole spacing in the frame of T1. Small slots are filed in two of the boards for the securing tabs of T2 and T3. All interconnections between boards or between boards and external circuits are to Veroboard pins or to miniature turret tags as shown in the diagrams. It may be necessary to enlarge the Veroboard holes to take the turret tags. If it is difficult to obtain suitable turret tags, Veroboard pins can be used throughout. As was mentioned in Part 1, TR3 and TR5 are fitted with heat sinks.

As far as wiring up is concerned, the principal causes of possible difficulty will most probably be given at S3 and S4. Here, it is suggested that the switches are wired up wafer by wafer, straight off the circuit diagram. If any switch has more 'ways' than are required, these should be blanked off. Wiper orientation must be checked and correctly synchronised. If the switch wafer is of the fully enclosed pattern a continuity check will be necessary, otherwise the possibility of having wipers  $180^\circ$  out of synchronisation may be realised.

An error in wiper synchronisation, or a wiring error involving S3 and S4, may prove extremely difficult to detect once wiring is completed. A systematic, logical approach must be adopted, with plenty of time for re-thinks. Whilst it will sound 'old hat' to the really experienced constructor, the old dodge of crossing a line through each wire or component as it is soldered in is a

good one for the not so experienced to adopt.

S5 must have its wiper stop so adjusted that at no time can the wiper be connected directly to the emitter of TR5. Should this not prove possible, R15 must be mounted separately from the switch so that at all times it isolates the wiper of S5 from the emitter of TR5.

#### METER RESISTORS

Next to be dealt with are the meter range resistors R1 to R9 and R10 to R14. The simple calculations necessary were discussed in Part 1, and the values given in the Components List were arrived at by these means.




Another view of the power supply assembly

As was stated, these values apply to the particular R.S. Components meters referred to. Since the resistance of the coils in even these meters is subject to a tolerance of  $\pm 10^0$ , some variation from these calculations may be necessary.

For R1 to R9 in the prototype, a suitable stock of 5%  $\frac{1}{2}$ w high-stability resistors was assembled and, by comparison with a voltmeter and current meter known to be accurate, a number were selected for use. By these means, a nominal 2.4k $\Omega$  resistor was found that halved f.s.d. for the 100 $\mu$ A range (2,400 $\Omega$  calculated), a 470 $\Omega$  resistor was found for the 300 $\mu$ A range (480 $\Omega$  calculated), two resistors of 270 $\Omega$  each in parallel for 1mA, and so on. The 100mA shunt was made from 34 s.w.g. Eureka wire, and the 300mA and 1A shunts from 24s.w.g. Eureka wire. The 34 s.w.g. Eureka wire has a resistance of 10 $\Omega$  per yard approximately, and the 24 s.w.g. wire has a resistance of 1.7 $\Omega$  per yard approximately.

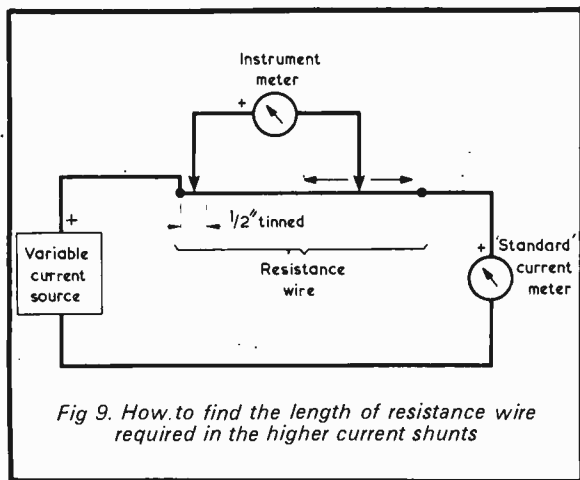The principle is very easy, and in conjunction with the shunts formula and wire having a known resistance per unit length, will enable any value of shunt to be constructed. Fig. 9 shows the essentials. A length of



resistance wire is cut somewhat longer than the calculated value, and one end is carefully scraped clean and tinned with solder for  $\frac{1}{2}$  in. This end is connected to one side of a variable current source. The other end is also cleaned and tinned, but only for  $\frac{1}{4}$  in. The second end is connected to a 'standard' current reading meter, its other terminal being returned to the current source so that all are in series. The current source is now adjusted to cause the requisite current to flow through the chain, as indicated by the 'standard' meter. One end of the meter to be used with the shunt is connected to the  $\frac{1}{2}$  in. tinned end of the resistance wire, and the other terminal is gradually 'tapped' along the shunt wire until the meter reads the same as the 'standard' meter. This point is carefully marked, and the wire is cut exactly  $\frac{1}{2}$  in. longer. This  $\frac{1}{2}$  in. of wire is also carefully scraped clean and tinned with solder. The complete length of wire is now wrapped round the body of a 1 watt resistor of high value, and the tinned ends are then wrapped round the resistor's own leads and carefully soldered to them. When cool, the shunt can be rechecked for accuracy. The same method is used for the other shunts. With care, very accurate shunts can be constructed in this manner. When complete, they should be coated with a moisture-repellant varnish.

It is of the utmost importance that the calibrating current is passed through the shunt as described, with the meter tapped across the shunt. Under these conditions, the meter cannot be harmed if contact with the shunt is momentarily lost. If the current were passed through the meter with the shunt being tapped across it, then any loss of contact would allow the full current to pass through the meter, and 1A through a 50 $\mu$ A movement is definitely not to the meter's advantage.

The voltage multiplier resistors R10 to R14 can similarly be found, again in comparison with a meter of known accuracy. Quite possibly, two resistors in series or parallel will be required for each multiplier. The starting point is a resistor which gives very nearly the required reading. If this reading is high, then an additional low value series resistor is required. Conversely, if the reading is low, then a high value parallel resistor is needed.

It must at all times be remembered that this is a measuring instrument, the future usefulness of which will depend upon care and skill exercised in constructing the series and shunt resistors in particular, and upon the quality of the components used and the workmanship in general.

## SETTING-UP

The setting-up procedure is carried out after the current meter and voltmeter circuits have been accurately assembled, as just described. The two meters are used to check some of the steps in the setting-up procedure.

Initially, the controls should be set to the following positions: S1 at 1A, S2 at 30V, S3 at 'Off', S4 at Ic, S5 at 3 $\mu$ A and S6 at 'Off'. VR1 should be set fully anticlockwise. VR2 should also be adjusted to the fully anticlockwise position. VR3 should be set at mid position.

S6 should now be switched 'On'. M2 should indicate a low voltage, and both indicator lamps should be illuminated. There should be no reading in M1. If there is, switch off and recheck the wiring and components. S3 can now be switched to 'n.p.n.', when the green lamp should extinguish, leaving the red lamp illuminated. Switch to 'p.n.p.', and the red lamp should be extinguished whilst the green lamp should become illuminated.

R24 is selected to pass only some 30mA through a 24V 1 watt bulb, when only a single bulb is illuminated. This ensures adequate lamp brilliance without over-running the filament; at the same time the load assists in keeping the voltage across C5 reasonably constant, and this in turn ensures a fairly consistent output from TR5.

VR3 can now be set for zero voltage output. S2 must be switched to a more sensitive range to enable this adjustment to be carried out more accurately. The zero voltage setting can be somewhat critical and, due to component tolerances, it may be necessary to settle for a minimum voltage output a few hundred millivolts above zero potential. S2 is restored to its 30V setting, and VR1 rotated clockwise, whereupon the output voltage should increase smoothly to a maximum of some 24V.

The bias voltage can next be checked by an independent meter connected across TP4 and TP5. A 330 $\Omega$  resistor should also be connected across TP4 and TR5 to act as a temporary load. Rotating VR2 clockwise should cause the voltage to rise smoothly to a maximum of some 10V. If it is significantly different from 10V, then R29 can be altered in value to provide the required



voltage. The meter and 330Ω resistor are now removed from TP4 and TP5.

The main supply voltage and the bias voltage polarities can now be checked across *all the output sockets*. S3 should be set to 'n.p.n.', when the voltages from collector to emitter and base to emitter should be positive. (S5 can be set at 30mA for this test). Switch S3 to 'p.n.p.', whereupon the collector to emitter and base to emitter voltages should reverse to negative. At the same time re-check that the appropriate lamp, red for 'n.p.n.', green for 'p.n.p.', is illuminated. With S3 at 'off' both lamps should be alight, and there should be no voltages present at the collector to emitter and base to emitter terminals.

If a current meter with a suitable f.s.d. is available, it can be connected between the base and emitter sockets. With S5 set at 30mA and VR2 fully clockwise, the meter should read approximately 30mA. The remaining base current ranges can be checked in a similar manner, whereupon current readings approximately equal to the setting indication of S5 should be given. The base current reading must not alter if S3 is switched from one polarity to the other, but it must, of course, drop to zero in the 'Off' position.

M1 can be checked by connecting a suitable resistance across the collector and emitter sockets. For instance, a 100Ω 10 watt resistor will cause 100mA to flow if V<sub>CE</sub> is 10V, 200mA if V<sub>CE</sub> is 20V, and so on. Obviously, if this test is to have any real significance, the load used must be of known accuracy.

The collector and emitter test sockets must *never* be directly short-circuited together. The internal resistance of the supply is very low, and under short-circuit conditions a current can flow of sufficient magnitude to cause damage to the meter, TR4, and the rectifier diodes. *During setting up, and during subsequent use, the greatest care must be exercised to prevent such a short-circuit from occurring.*

## USING THE ANALYSER

The completed instrument, though designed to analyse a wide range of bipolar transistors can, if incorrectly used, be the means of damaging the transistor under test. Care is therefore necessary when using the instrument, and a logical and definite sequence of operations is most essential, and should always be adhered to.

The recommended sequence of operations is as follows, and it should be employed after having referred to the published data on the transistor under test.

1. Set S1 to one range above required I<sub>c</sub>.
2. Set S2 to the V<sub>CE</sub> range required.
3. Set S3 to 'Off'.
4. Set S4 to I<sub>c</sub>.
5. Set S5 to 3μA.
6. Set S6 to 'Off'.
7. Set VR1 to minimum and VR2 to minimum.
8. Switch S6 'On'.
9. Insert device into appropriate socket.
10. Switch S3 to required polarity.
11. Set VR1 for required V<sub>CE</sub>.
12. Set S5 and VR2 for required I<sub>c</sub>.

13. Switch S4 to I<sub>B</sub>. Read I<sub>B</sub>. Compute h<sub>FE</sub> from  $\frac{I_c}{I_B}$
14. Switch S4 to I<sub>CEO</sub>. Read I<sub>CEO</sub> by reducing S1

setting as required.


15. Switch S4 to I<sub>CBO</sub>. Read I<sub>CBO</sub> by setting S1 as required.
16. Recheck I<sub>c</sub> and I<sub>B</sub>.

After each check reduce all 'active' controls (i.e. S5, VR1 and VR2) to minimum, and all 'passive' controls (i.e. S1 and S2) to maximum. Set S3 to 'Off' and S4 to I<sub>c</sub>. This is a 'fail-safe' routine and one that ensures that the next test can be safely commenced.

Though the tabulated check list may appear to be quite lengthy and formidable, this is a trait the analyser shares with many other instruments. After using the instrument for a short while, the modus operandi soon becomes second nature.

The transistor under test can be damaged by applying the incorrect polarity, or by its being inserted into the wrong socket. It can also be damaged by an *apparently correct test, due to incorrect interpretation of published data.*

An easy trap for the unwary or inexperienced to fall into concerns the two ratings B<sub>VCE</sub> and B<sub>VCB</sub>, or any similar symbols which indicate the absolute maximum ratings. Attempts to analyse a transistor with a V<sub>CE</sub> equal to B<sub>VCE</sub> or B<sub>VCB</sub> can result in the rapid destruction of the transistor. V<sub>CE</sub> should not be increased beyond 50% of these ratings.

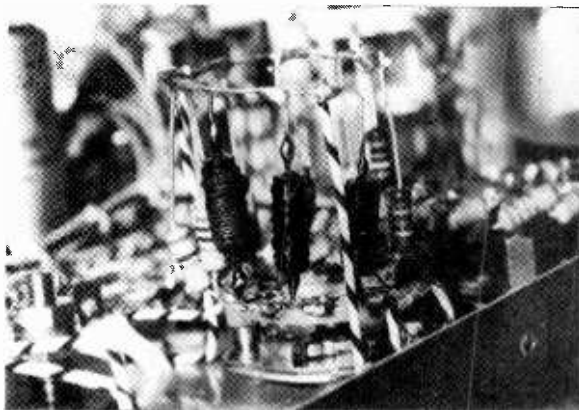

*The shunts for the meter M1 may be mounted directly to switch S1 in the manner shown here. The single wafer switch illustrated was later changed to a double wafer type, as described in the text*

Another parameter which must be carefully watched is P(τ<sub>OT</sub>), which is given by I<sub>c</sub> × V<sub>CE</sub>. This is a 'fairy tale' parameter, which must be suitably derated after allowing for thermal resistances, so that the resultant 'safe' value of P(τ<sub>OT</sub>) is perhaps only 20% or even less of the original value.

When a device is being analysed, a close watch must be kept on I<sub>c</sub>, as it is quite possible to increase V<sub>CE</sub> to the point where the transistor 'avalanches' even with the base current completely cut off. Under these conditions the very low internal resistance of the power supply will permit a destructive current to flow through the transistor.


Should  $I_C$  start to increase rapidly, switch  $S_3$  to 'Off' and reduce  $V_{CE}$  and  $I_B$ . The analysis can then recommence with a reduced  $V_{CE}$ ; this can slowly be increased and, by frequently checking  $I_C$ ,  $I_{CEO}$  and  $I_{CBO}$ , a rapid and accurate analysis can be arrived at.

By means of the analyser, families of graphs can be drawn showing collector characteristics (variation of  $I_C$  with  $V_{CE}$ ,  $I_B$  being fixed). Transfer characteristics can also be plotted, by means of which the relationship between  $h_{FE}$  and  $I_C$  can be seen.

Devices other than bipolar transistors can also be checked. Diodes can be checked for forward conduction and reverse leakage currents at the maximum voltage and current limits of 24V and 1A, using the collector and emitter sockets and the n.p.n.-p.n.p. positions of  $S_3$ . This is why  $M_2$  has a 0.3V range.

Zener diodes can be checked for zener voltage and current, though here only a single polarity of voltage is required. The maximum power rating, given by  $ZI \times ZV$ , must not be exceeded, and due allowance must be made where applicable for thermal derating.


The last application of the analyser is that of a good quality stabilised power supply. For this purpose the collector and emitter sockets are used, whereupon the 0 to 24V and 0 to 1A capabilities of the supply can be utilised. The base and emitter terminals allow  $V_{BE}$  to be employed as a variable current source, variable from 0-30mA to 1-3-10 steps, or as a variable voltage source having a capability of 0-10V at 30mA.

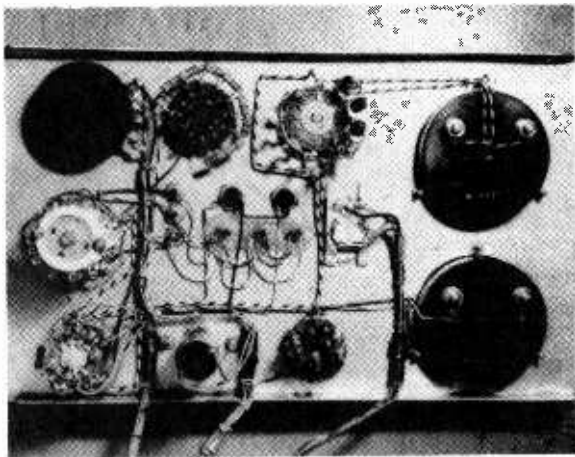

Rear view of the front panel, showing the cableforms

As a final point, it is possible for a few transistors offering high gain at very high frequencies to give misleading results due to the onset of oscillation. This will be indicated by apparently random fluctuations in the meter readings as the controls are operated. After considerable experience with the analyser, the author has encountered the effect with only a few transistors. It may be cleared by slipping a ferrite bead over each of the transistor lead-outs before it is inserted in its test socket. ■

## CROSSWORD

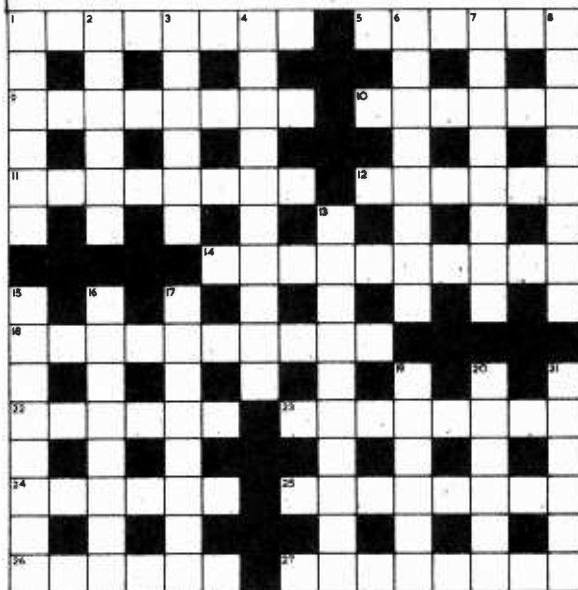

### Clues Across

1. Muddled stories and R denote this. (8)
5. Potential effect of high voltage. (6)
9. Lay version of bootstrap? (4-4)
10. Useful paper for power curves. (3, 3)
11. Circle in a circle as in the dial drive. (8)
12. These are singularly equal to 'perfect' in circuit design. (6)
14. Flicker and shot contribute to this. (5, 5)
18. Ignominious position for the binary 100's. (2, 3, 5)
22. Mongrel unit uses valves and transistors. (6)
23. Anti-rocker, refined, deceased, to regulate. (8)
24. 0% distortion. (6)
25. Describes unwanted signals. (8)
26. Drive. (6)
27. Covers the case where induced currents oppose motion. (5, 3)

### Clues Down

1. TV picture after close-down. (6)
2. Dim and thick. (6)
3. Synchro motor. (6)
4. Castrol oil furnishes this self-running device! (10)
6. Meter leads in shunning. (8)
7. Animated, as in frog's leg twitch. (8)
8. Data container. (8)
13. How to get that double peak. (10)
15. Piezoelectric seidlitz? (8)
16. Battery electrode controls the soda syphon acid. (8)
17. Challenger. (8)
19. Spoken breathalyser limits, frequency controller. (6)
20. Final winding. (1, 1, 4)
21. Playground phase-splitter. (6)

(Solution on page 464).

# In your workshop



In this month's episode Smithy the Serviceman enlightens his assistant, Dick, on a number of aspects of the transistor multivibrator, dealing in particular with some of the misconceptions which exist in relation to this simple circuit. The pair conclude by constructing a novel 2-tone multivibrator oscillator.

"PRODUCE A MULTIVIBRATOR DESIGN?" repeated Dick scornfully. "Blimey, that shouldn't be a particularly hard job for someone like you."

"I will agree," remarked Smithy mildly, "that the design of a conventional multivibrator is not excessively difficult. What I've been asked to do in the present instance is to make up a gadget which will produce an unusual warning note when a press-button is pushed. It's for one of our customers who has a small flat and who likes to be considered trendy and way-out. He wants a tone generator instead of a door-bell."

"Does he?" commented Dick. "Well, a tone generator would certainly make a welcome change from the usual ding-dong affair."

"I'm going," stated Smithy, "to use multivibrators in this tone generator. I've already worked out the circuit and what I want you to do today is to knock it up for me in practical form."

## MULTIVIBRATOR OPERATION

"Fair enough," said Dick loftily. "It doesn't seem to me that it will be very complicated, though. Dash it all, a multivibrator circuit must be one of the simplest things going."

"Must it?" queried Smithy in an irritated tone. "Well, if you're so  
FEBRUARY 1973

clever, just come over here and show me how a multivibrator functions."

"All right," replied Dick airily, as he took a ball-point pen from his overall pocket and walked towards Smithy's bench. "Let me have a bit of paper and I'll demonstrate exactly how a multivibrator works."

Smithy pulled his note-pad over. Dick concentrated, then drew out a circuit on the top sheet. (Fig. 1).

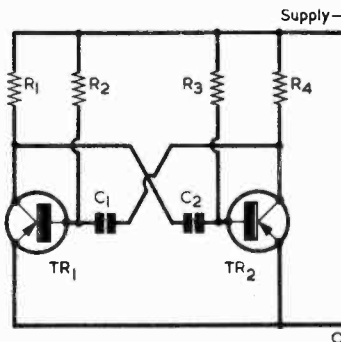


Fig. 1. A basic multivibrator. The transistors shown here are p.n.p.; if n.p.n. transistors are employed all polarities are reversed

"There you are," he pronounced triumphantly. "This is the circuit of a standard transistor multivibrator, and I've numbered the various components so as to make it easier to describe what they do. It so happens that I've used p.n.p. transistors here, but the circuit would work just as well with n.p.n. types if the supply polarity was changed over."

"Okey-doke," said Smithy, settling himself more comfortably on his stool. "Now explain its operation."

Dick marshalled his thoughts.

"When we apply the power to the multivibrator," he started, "both the capacitors are discharged. They then commence to charge. C1 commences to charge via R4 and the base-emitter junction of TR1, and C2 commences to charge via R1 and the base-emitter junction of TR2. This means that both the transistors start to pass collector current. Now, the rate of increase of collector current in one transistor is bound to be greater than that in the other because it would be impossible to have two devices that are exactly the same. Let's say that the transistor having the larger rate of increase in current is TR2."

"As you like," said Smithy obligingly. "What happens next?"

"The collector voltage of TR2," continued Dick, emboldened by his success so far, "drops more rapidly than that of TR1. Capacitor C1 is already partly charged, with its left-hand plate positive, whereupon the decrease in TR2 collector voltage causes the base of TR1 to go positive. TR1 passes less collector current than before, and its collector voltage increases. Since the collector of TR1 is coupled to the base of TR2 via C2, that base is pulled more negative. TR2 passes a greater collector current again and its collector goes even more positive. There is an overall regenerative effect and the final outcome is that TR2 becomes fully conductive and TR1 is fully cut off."

"Very good," commented Smithy approvingly. "Well, you've got the multivibrator started. How does it run?"

"We now," said Dick in reply, "have the situation where TR2 is turned on and TR1 is cut off. C2 now becomes charged up to nearly the full supply voltage via R1 and the base-emitter junction of TR2. C1 has a charge which causes its left-hand plate to be positive, but it now loses this charge because this left-hand plate couples to the negative supply rail by way of R2. After a period, the voltage on the left-hand plate of C1 becomes sufficiently negative to allow base current to flow in TR1. TR1 at once commences to draw collector current, whereupon its collector voltage goes positive. Since TR1 collector couples to TR2 base via C2, that base goes positive and TR2 draws less current. Its collector goes negative, causing increased base current in TR1. The

overall regenerative action takes place all over again and it results in a changeover which ends with TR1 fully on and TR2 cut off."

"That sums up the situation so far," agreed Smyth. "The first half-cycle immediately after switching on isn't representative of normal running operation because the cross-coupling capacitor concerned hasn't achieved a proper charge and the half-cycle is shorter than the subsequent ones. In the case you described it was C1 which didn't have the full charge. After TR1 had cut off, however, C2 was able to charge up to nearly the full supply voltage, whereupon all the subsequent half-cycles occupied the correct length of time."

"That's right," broke in Dick. "The multivibrator now commences to run continually, with the two transistors being alternately turned on and cut off as the circuit changes state. The length of each half-cycle depends upon the values of the capacitors and of R2 and R3."

"You've got it," confirmed Smyth. "The length of time during which TR1 is cut off during the cycle is dependent upon the values of C1 and R2. And the length of time during which TR2 is cut off during the cycle is dependent upon the values of C2 and R3. The values of R1 and R4 don't, with conventional component values, affect the length of each period. The length of the off time for each transistor is, incidentally, approximately 0.7 times the time constant of the associated base capacitor and resistor."

"I got that description all right, didn't I?"

"You did," confirmed Smyth. "Now, what can you tell me about the values of the four resistors in the circuit?"

### COMPONENT VALUES

"Oh," replied Dick nonchalantly, "the resistors aren't all that critical. All you've got to do is to find the values required in the base resistors to give the desired off periods for each transistor. The collector resistors can be any old value."

"Any old value?"

"Pretty well," said Dick carelessly. "They mustn't, of course, be too low, or the transistor concerned may pass too much current and overheat."

"Well, you won't get very far in the multivibrator stakes," commented Smyth drily as he pulled his note-pad towards him. "I'll draw out one half of your multivibrator circuit just to show how important the values of the collector resistors really are."

Smyth quickly scribbled out the circuit. (Fig. 2).

"Here are the components around TR1," he announced. "During the regenerative changeover action which causes this transistor to come on, its base current is mainly given by charging current in C1. When the changeover has taken place, though,

C1 becomes fully charged up, after which the base bias current for TR1 is provided entirely by R2. R2 must pass sufficient current to maintain TR1 in a condition where its collector voltage is as low as possible."

"Well?"

"That collector voltage won't be sufficiently low," continued Smyth, "if the value of the collector resistor is too small. Let's say that R2 is 100k $\Omega$ , that R1 is 1k $\Omega$  and that the current gain of TR1 is 50 times. Also, to keep things nice and easy, let's say that the supply potential is 10 volts. 10 volts across 100k $\Omega$  gives a current of 0.1mA and this will, assuming zero voltage drop in the base-emitter junction of TR1, be the bias current which flows in TR1 base via R2. Now TR1 has a current gain of 50 times, and so its collector current will be 5mA. But 5mA in the 1k $\Omega$  resistor we've chosen for R1 will result in a voltage drop of 5 volts only. So, our choice of values for R2 and R1 will cause TR1 to give quite a peculiar performance. Immediately after the changeover period its collector voltage will be very low because of the charging current in C1. But as soon as C1 becomes charged the collector voltage of TR1 will rise to 5 volts! The multivibrator won't run very well under these conditions, if it runs at all."

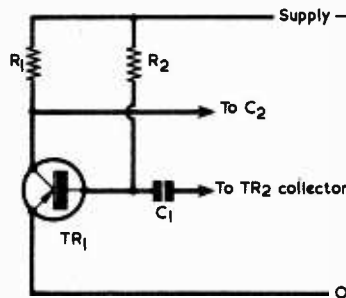


Fig. 2. Illustrating, as explained by Smyth, the importance of the relative values of the base and collector resistors for each transistor

"I can see what you mean, now," said Dick, crestfallen. "This makes things quite a lot more complicated than I'd realised."

"Don't be so glum about it," chuckled Smyth. "In practice the process of finding a suitable collector resistance is dead simple. The desired set of circumstances is given when the current in the base resistor causes very nearly the full supply voltage to appear across the collector resistor. Since both resistors will then have about the same voltage across them, the currents which flow in them are inversely proportional to their resistance values. The transistor will operate satisfactorily in the multivibrator if the value of the base resistor divided by the value

of the collector resistor is equal to or lower than the current gain of the transistor. The two resistances in the example we considered just now were 100k $\Omega$  and 1k $\Omega$ , and the result of dividing the first by the second is 100. The gain of the transistor is only 50 and so this combination of resistance values couldn't provide correct operation. If we'd made the collector resistor 2k $\Omega$ , the result of the division exercise would be 50, and the values would just scrape by as being suitable for proper multivibrator operation with a transistor having a gain of 50 times. The 5mA collector current we talked about would this time cause a voltage drop of 10 volts in a 2k $\Omega$  collector resistor. In practice, it would be better to play safe and use a slightly higher collector resistor than that which just meets the transistor gain requirement. Suitable values in our example would be around 3 to 5k $\Omega$ ."

"Why not," asked Dick, "make the collector resistor equal to the base resistor? The circuit would then work with any transistor provided it had a gain greater than 1!"

"Too high a collector resistor," stated Smyth, "raises another snag. Don't forget that the cross-coupling capacitor which couples to the collector in question has to charge up to nearly the full supply potential during the period when the transistor is cut off. If the collector resistor is too high in value the capacitor won't charge up to the desired potential. This may not stop the multivibrator from operating but the length of the period in which the remaining transistor is cut off won't be the figure calculated and it may vary a little from cycle to cycle. So you have to use a value of collector resistor which is high enough to meet the gain requirements of the transistor to which it connects, but which is not so high that the cross-coupling capacitor it feeds does not acquire a full charge."

### COLLECTOR WAVEFORM

"Darn it," snorted Dick. "I used to think that a multivib could run with pretty well any resistor values you choose to give it. I now find that you've got to be quite careful about these resistor values."

"Things aren't as bad as all that," soothed Smyth. "With most multivibrator circuits, there's plenty of latitude in the values of collector resistor you can use. All you've got to do is to keep within the extreme lower and upper limits which are liable to upset circuit operation."

"Well," announced Dick decisively, "there's one thing I can talk about without mistakes so far as a multivibrator is concerned, and that is the collector voltage waveform for each transistor."

He pulled Smyth's note-pad back towards him and drew a series of multivibrator half-cycles. (Fig. 3).

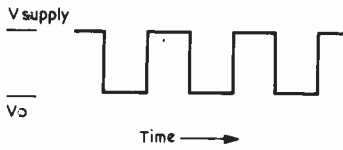


Fig. 3. It is commonly assumed that the collector voltage waveforms in a multivibrator have the form shown here

"Now this," he pronounced, "just can't be wrong. What I've drawn here is the collector voltage waveform for one of the transistors in a 50:50 multivibrator. That is to say, a multivibrator in which the values of both sets of base capacitor and resistor are equal, so that the off period in the cycle for each transistor is as long as its on period. The result is, of course, a square wave."

Smithy glanced briefly at Dick's waveform.

"It isn't, you know."

"It *must* be," retorted Dick heatedly.

"Dash it all, the transistor goes on and off at a regular frequency and so the collector waveform must be a square wave."

"You're forgetting the cross-coupling capacitor which connects to the collector," said Smithy, sketching out a further circuit. "This one."

Smithy indicated the circuit to his assistant. (Fig. 4.)

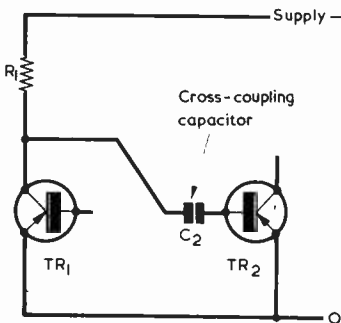


Fig. 4. When a transistor in the multivibrator turns off, the rise of its collector voltage is slightly delayed by the cross-coupling capacitor which couples to it. In this diagram the transistor and capacitor are TR1 and C2 of Fig. 1

"We've already seen," Smithy went on, "that the cross-coupling capacitor has to charge during the period when the transistor is off. The other end of the capacitor connects to the lower supply rail via the base-emitter junction of the opposite transistor, and that junction presents very little resistance. The consequence is that the collector to which the capacitor connects cannot rise immediately to

the supply rail voltage when the transistor cuts off because it is held back by the charging capacitor, and the leading edge of this part of the waveform gets rounded off. Like this."

Smithy drew a further waveform, illustrating the rounding off effect. (Fig. 5).

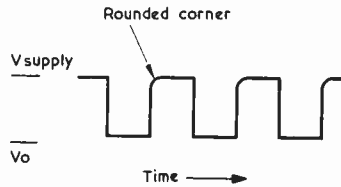


Fig. 5. The presence of the cross-coupling capacitor causes rounding off of the upward-going section of the collector waveform

"Lots of people," he continued, "seem to think that you can get a square wave from a multivibrator simply by connecting to one of the transistor collectors, but this just isn't so. Admittedly, the collector voltage goes down with a thump during the changeover which turns on the transistor concerned. But the rise in collector voltage after the changeover which turns the transistor off is by no means as abrupt, and it exhibits this rounded-off characteristic."

"Hell's teeth," groaned Dick. "That's another of my illusions shattered! Well, how do you get a square wave from a multivibrator?"

"There are quite a few methods," said Smithy. "One simple way of getting as true a square wave as possible consists of passing the multivibrator waveform through a clipper which removes the most rounded section of the upward-going waveform edge. Another method consists of adding a third transistor between the emitter of one of the multivibrator

transistors and the lower supply rail. Here's the idea."

Smithy scribbled out a circuit which included the additional transistor. (Fig. 6).

"How does that work?"

"The base-emitter junction of the third transistor," explained Smithy, "carries both the base and collector currents of the multivibrator transistor to which it connects. So, when the latter comes on, the third transistor does, too. Similarly, when the latter turns off, so does the third transistor. Since the third transistor has no capacitor to hold down its collector voltage, this can then rise immediately, giving you a proper square wave. The added transistor is very useful, too, if you want the multivibrator to drive a low resistance or low impedance load, since it also amplifies the current in the multivibrator transistor."

"Hang on a jiff," said Dick thoughtfully. "I think I saw that third transistor idea in one of G. A. French's 'Suggested Circuits' recently."

"You did," confirmed Smithy. "He used it to allow a multivibrator to drive a speaker, and I think it appeared last November. As it happens I'm using the same idea in the tone generator you're going to make up."

For the moment, however, Dick's thoughts were removed from the subject of multivibrators.

"Old G. A. French," he mused. "He's been contributing to the 'Radio Constructor' for quite a few years now, hasn't he?"

"'Radio and Electronics Constructor,'" corrected Smithy, "if you don't mind."

"So far as I can recall," resumed Dick, "those 'Suggested Circuits' of his are running well past No. 260 by now. As there are 12 'Suggested Circuits' each year, he must have been turning them out for at least 21 years."

"An achievement," remarked Smithy, "which is not to be sniffed at."

"He must," went on Dick, proceed-

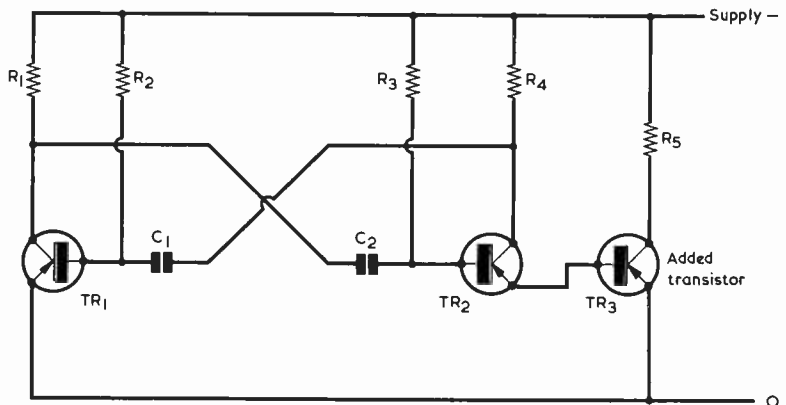


Fig. 6. A square wave is available at the collector of a third transistor, added to the multivibrator in the manner shown here. R5 represents the collector load of the third transistor

ing doggedly with his train of thought, "be really *ancient*, after all these years. Do you know, Smithy, I can visualise old G. A. French as an eccentric old geysier with a long white beard, shambling up Maida Vale every month to get his article in and tapping all the lamp posts as he passes by."

Smithy turned an irate glance on his assistant.

"It wouldn't half shake you," he said severely, "if a long bony finger came creeping over the edge of this page and dug you one in the lug-hole."

Dick looked hastily around him, then shivered violently.

"Don't talk like that, Smithy," he pleaded, "you'll scare the living day-lights out of me."

"Fair enough, then," returned Smithy sternly. "But in future be careful what you say about your elders and betters."

## REVERSE VOLTAGES

"All right, Smithy," said Dick, chastened. "Let's get back to those multivibrators. Are there any other points to look out for in multivibrator design?"

"There is a further important one," replied Smithy, "but before proceeding to this, I think I should mention that all the multivibrator circuits we are talking about today are those which have the conventional configuration where both emitters couple direct to the lower supply rail. There are other circuits which are less frequently encountered, these including the emitter-coupled multivibrator. Our comments today don't necessarily apply to these other types."

Smithy stopped for a moment to collect his ideas.

"Now," he went on, "the further important point in the conventional multivibrator concerns the reverse base-emitter voltage which is applied to each transistor when, during the cycle, it's turned off. At the instant before the transistor is turned off it is fully conducting and the capacitor which connects to its base is charged up to very nearly the full supply potential. The situation is then like this."

Smithy sketched out a circuit. (Fig. 7(a).)

"The changeover follows next," he carried on, "with the result that the first transistor comes on and the second transistor is turned off. Immediately after the changeover, the base of the transistor that's turned off is taken positive of the lower supply rail by the charged capacitor, the amount by which it is taken positive being very nearly equal to the supply voltage." (Fig. 7(b).)

"I see," commented Dick thoughtfully. "After that, the capacitor discharges and the reverse base-emitter voltage on the second transistor falls, doesn't it?"

"That's right."

"If the initial reverse base-emitter voltage is greater than the maximum base-emitter voltage rating for the transistor," queried Dick, "will the transistor become damaged?"

"Very probably not," said Smithy. "What will happen instead in most instances is that the base-emitter junction will function as a zener diode at its breakdown voltage. This will cause the capacitor connecting to the base to become partially discharged during the changeover process itself, and the subsequent off period for the transistor concerned would be shorter than the calculated period."

"Does that matter?"

"Oh, definitely. For a start, the multivibrator circuit is not being used in the manner in which it is intended to operate. Also, there will be quite heavy discharge currents from the capacitor into the base-emitter junction

which is acting as a zener diode and, whilst these currents may not be sufficiently high to cause eventual failure of the transistor, they obviously aren't going to do it any good. Another factor is that the manufacturer's reverse base-emitter voltage rating for a transistor represents a *minimum* figure only. The actual breakdown voltage for one transistor may be considerably higher than the minimum voltage rating, whilst that for another transistor of the same type number may be just above the rating figure. In consequence, in a multivibrator circuit where the reverse base-emitter voltage rating is exceeded, the first of these two transistors may not exhibit the zener diode effect at all and its off period will be equal to the calculated value. On the other hand the second of the two transistors, the one whose actual breakdown voltage is just a little higher than the rating, may exhibit the zener diode effect very noticeably and its off period will be shorter than the calculated value."

"That's awkward," commented Dick. "The circuit could give different off periods for two different transistors, even though they both had the same type number."

"Exactly," agreed Smithy. "Fortunately, there's a simple solution to this problem and it consists of selecting transistor types whose quoted reverse base-emitter voltage rating is greater than the multivibrator supply voltage. The zener diode effect cannot then take place at all with any transistors, and all transistors of the same type number will give an equivalent performance. Many of the popular low-cost silicon transistors which are available these days have quite low reverse base-emitter voltage ratings, these being of the order of 5 to 6 volts only. Germanium transistors, on the other hand, usually have much higher reverse base-emitter voltage ratings, and are frequently more useful than silicon types in multivibrators even though lots of people nowadays seem to think that germanium transistors are old-fashioned. The popular germanium transistors type ACY18 and ACY19 both have, for instance, a maximum reverse emitter-base voltage rating of 12 volts, which makes them suitable for use in any multivibrator having a power supply voltage that doesn't exceed this figure. And that brings me to my main topic."

## TWO-TONE OSCILLATOR

Smithy opened a drawer in his bench and, with a flourish, produced a sheet of paper on which he had already drawn a circuit diagram. (Fig. 8.)

"What's that?" asked Dick.

"It's the circuit of the multivibrator gubbins which started this discussion off," stated Smithy. "It's the tone generator you'll be making for our customer's flat, and it uses four ACY18's and one ACY19."

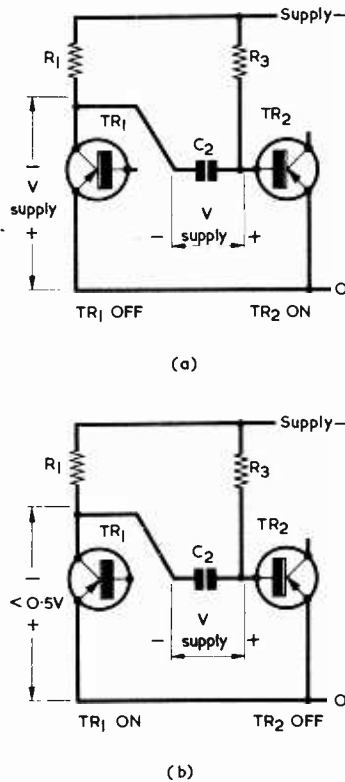


Fig. 7(a). The situation just before the changeover which causes one transistor ( $TR_2$  here) to be turned off  
(b). Immediately after the changeover nearly the full supply voltage is applied, as reverse bias, across the base-emitter junction of the cut off transistor. With n.p.n. transistors all the polarities would be reversed

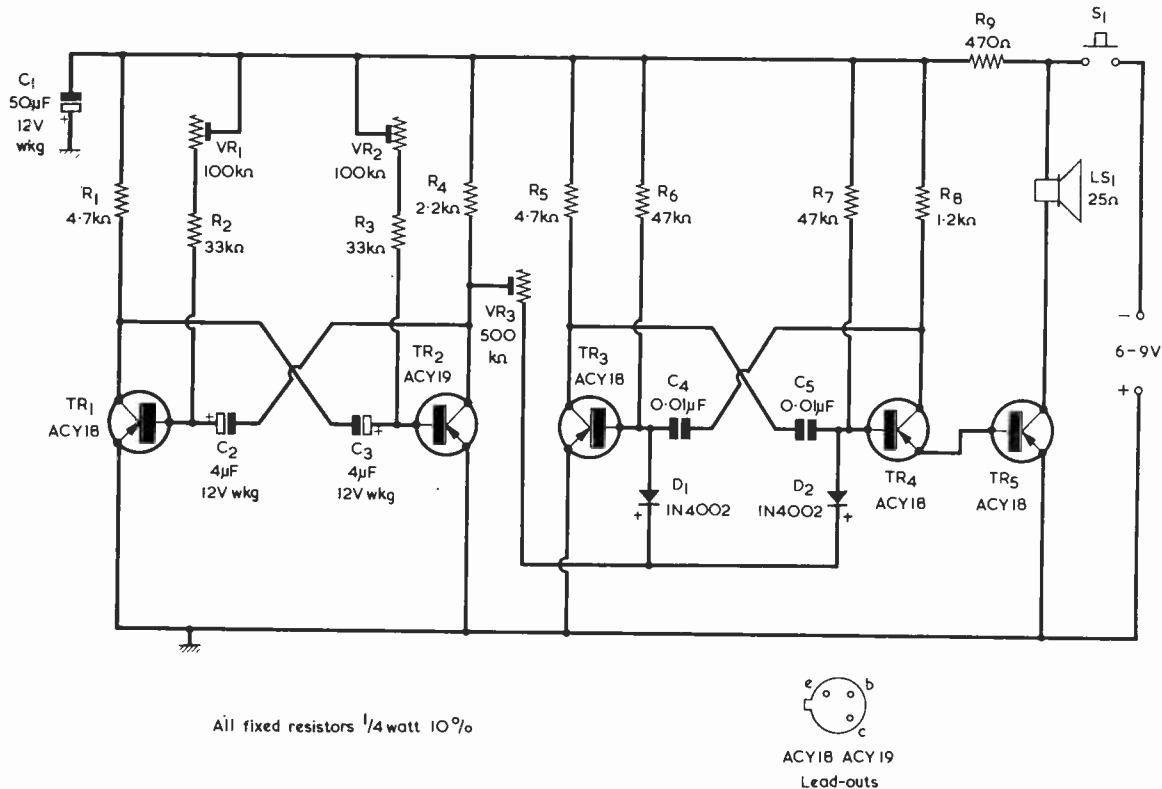


Fig. 8. A 2-tone generator incorporating two multivibrators. Push-button S1 may be a door bell-push coupled to the remainder of the circuit via twin wire

"That seems," remarked Dick suspiciously, "to be rather a lot of transistors."

"There are a few," admitted Smyth. "This is because there are two separate multivibrators in the circuit. One of these is given by TR3 and TR4. This multivibrator runs at an audible frequency and is coupled to the loudspeaker by TR5, which is inserted in the emitter circuit of TR4. This transistor enables the multivibrator to drive a low impedance load in the manner we discussed a short while ago. TR1 and TR2 form a second multivibrator and it runs at around 1 cycle per second."

"What does this second multivibrator do?"

"It varies the frequency of the multivibrator given by TR3 and TR4," explained Smyth. "The result is that you get a 'hee-haw' type of audio output which is reminiscent of that given by ambulances and fire-engines."

"Do you, indeed?" asked Dick, his interest rising. "That seems to be quite a knobby idea. I see that you've put pre-set pots in the base circuits of TR1 and TR2. Why is that?"

"The pre-set pots are to take up differences in actual capacitance in the cross-coupling capacitors C2 and C3," replied Smyth. "These capacitors need

a value of around 4µF each and, if the circuit is to be economical, should be electrolytic types. Unfortunately, electrolytic capacitors have a very wide tolerance on nominal value, and the discrepancies in value are taken up by adjusting VR1 and VR2. Both VR1 and VR2 can be conventional skeleton types. So also, incidentally, can VR3."

"How is the frequency of the audio multivib changed?"

"By way of diodes D1 and D2," said Smyth. "If you ignore these two diodes for a moment, you'll see that the multivibrator around TR3 and TR4 is a standard circuit, the off period for each transistor being the time required for the appropriate 0.01µF cross-coupling capacitor to discharge via the 47kΩ resistor which couples it to the upper supply rail. If D1 and D2 are now taken into account, a second discharge path can be seen. When TR3 is off, its base is at a positive potential and diode D1 conducts. The second discharge path is then given via D1 and VR3. This same discharge path is similarly provided, but via D2, when TR4 is off. In consequence, each base circuit has the same second discharge path by way of the diode which connects to it, the diode which conducts being that which couples to the base which is most positive."

"Blimey," said Dick, impressed. "That's a crafty way of controlling multivib frequency."

"It is a useful circuit," agreed Smyth. "Now, the other end of VR2 is coupled to the collector of TR2. When TR2 is turned on, its collector is approximately at the same potential as the lower supply rail, and the discharge path via VR3 is to this relatively low potential. When, on the other hand, TR2 is off, the discharge path via VR3 is to the upper supply rail by way of R4, and the cross-coupling capacitor to which this discharge path is presented discharges much more rapidly. The result is that the audio multivibrator runs at a higher frequency when TR2 is off than when TR2 is on. VR3 is adjusted to give the final audio frequency variation required. In practice the frequency variation will increase as the resistance inserted by VR3 reduces, until a setting is reached where VR3 inserts too little resistance and upsets the functioning of the multivibrator. A further point is that I've included a decoupling circuit, which is provided by R9 and C1. TR5 draws quite a heavy current when it conducts and, if there was a fairly high internal resistance in the supply, this could upset the operation of TR1 and TR2

## Your Local Supplier

LONDON

### THE MODERN BOOK CO.

Largest selection of English & American radio and technical books in the country.

19-21 PRAED STREET,  
LONDON, W2 1NP  
Tel: 01-723 4185/2926

## ST. HELEN'S RADIO

Hi-Fi Equipment  
Tape Recorders  
Radio Receivers  
Television

SPECIALISTS IN RADIO  
& ELECTRONIC TEXTBOOKS

ST. HELENS GARDENS  
LONDON, W.10  
Tel: 01-969 3657

HAMPSHIRE

## BOURNEMOUTH

LARGEST HI-FI AND  
RADIO COMPONENT  
STORE IN THE SOUTH

FORRESTERS NATIONAL  
RADIO SUPPLIES LTD.

70-72 Holcenhurst Road  
Bournemouth  
Telephone 25232

LEICESTERSHIRE

ENSIGN ELECTRONICS.

43" 8 Section Telescopic Aerials	35p
New Marked 2N3055 Transistors	35p
New Slide Switches. Special Offer 4 for	30p
Miniature Battery Level Meters. 0-600 Ma F.S.D.	50p
100 Mixed High Stability Resistors (New)	35p
New 12 Volt Plug in Relays. (11 Pin Base)	60p
Silicon Bridge Rectifiers. 5G volt 1 amp	30p
PLUGS STD Jack Plugs 12p. 3 pin Din Plugs	12p
10 1/2" Revox Tape Spools	40p
67 Foot Wire Aerials, Marked every foot	60p
Headphones with Boom Mic (used)	£1-45
Sets of Spare valves for 62 set (new)	£1-35
Geiger Counter - Contamination Meter No 1	
Separate Probe - Runs off 4 x HP7 Batteries	£4-25
Set of 6 U.S.A.F. maps - Large - All Different	60p
B7G Bases 7p B9A Bases 7p	
50 volt Disc Capacitors. 0.05 mjd, 0.02 mjd, 0.002 mjd 12 for 15p 50 for 50p.	

Send to: Dept R.C., 30 High Street, Quorn,  
Nr Loughborough, Leics.

if the decoupling circuit were omitted. The average current drawn by the unit will be of the order of 100 to 150mA."

Smithy passed the circuit over to Dick.

"Shall I," asked that worthy, "knock it up now?"

"If you would, please," requested Smithy.

### WORKING VERSION

Dick returned eagerly to his own bench, and Smithy proceeded to deal with some of his other work.

There was silence for nearly an hour, after which an excited call from Dick indicated that he had completed the assembly of the tone generator circuit. Smithy walked over and inspected his assistant's handiwork. Dick had wired up the components on a small neat chassis having two 2-way terminal blocks. One of these was intended for connection to the speaker and the other for connection to the supply via S1.

"Right," said Smithy. "Wire up a speaker now and fit two leads for connection to a 6 or 9 volt battery. We can couple direct to the battery for checking the generator out, and we won't need S1. Oh, and set VR3 to insert full resistance into circuit before you connect the battery."

Cheerfully, Dick carried out Smithy's instructions. As he connected the battery, a loud tone, a little higher than 1kHz, became audible from the speaker. This tone varied periodically in frequency by a small amount.

"Good," commented Smithy, rubbing his hands together. "Let's make a few adjustments now."

"Gosh," said Dick enthusiastically, as he listened to the sound from the speaker, "that sounds terrific."

"It's not too bad," confirmed Smithy, listening critically. "It's loud enough to replace a door bell in a small flat, although it wouldn't cope for a house."

"There seems," remarked Dick, "to be a slightly sharper transition from the high to the low frequency than in the other direction."

"That's true enough," agreed Smithy. "The difference between the two transitions is just about discernable. It's due, of course, to the rounding-off in the collector voltage waveform which I mentioned earlier. The collector voltage of TR2 drops abruptly when TR2 comes on, but it rises a little less abruptly when TR2 turns off. This doesn't detract from the overall effectiveness of the gadget."

"Could you," asked Dick, "use a mains power unit instead of a battery?"

"Definitely," stated Smithy. "One of those little bell transformers having secondary outputs of 3, 5 and 8 volts which they sell in Woolworth's would be just the job, and its 8 volt secondary could be coupled to a bridge rectifier and a 1,000µF reservoir capacitor. A power unit of this nature can be left permanently connected to the mains and it will draw negligible current. The d.c. output would be of the order of 8 volts when the push-button is pressed." (Fig. 9).

With a gesture of finality, Smithy disconnected the multivibrator circuit from its battery, and the piercing 2-tone output ceased.

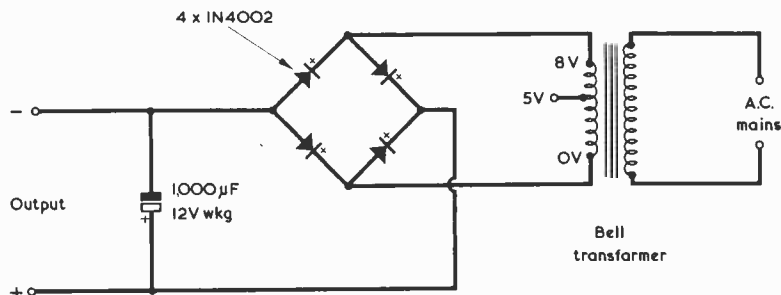


Fig. 9. The generator of Fig. 8 can be powered by a battery or by a small mains unit incorporating a bell transformer

He picked up a small screwdriver and slowly reduced the resistance inserted by VR3. The frequency changes became more and more pronounced as he adjusted the potentiometer, and he finally left it at a setting which he declared to be satisfactory. He next adjusted VR1 and VR2 until the two different frequency periods were equal and of a satisfactory length.

"Well," remarked Smithy philosophically, "that's another little job successfully completed. It's back to radio and TV servicing for you again now, my lad!"

And it wasn't long before Dick, the multivibrator unit already an item in the past, was completely immersed in the repair of a monochrome single-standard television receiver.



# Radio Topics

## By Recorder

**B**Y THE TIME THESE NOTES APPEAR our presentation issue of last October, with which we gave away a free sample piece of Veroboard, will be past history. Nevertheless it is worth while referring to it because Veroboard represents a particularly unique approach towards the assembly of electronic circuits, and because it enables such neat results to be obtained. There is, further, a special sense of achievement in constructing small items on a Veroboard panel using the minimum number of copper strips and holes.

### DESIGN APPROACH

Users of Veroboard tend to have their own pet techniques but my own experiences with this product may be of value, if only for newcomers. When a Veroboard unit is required in a hurry I find it slightly to advantage to cut the Veroboard so that the copper strips run across the width of a relatively narrow piece of board, in the same way that the lines of print run across the width of this column, rather than have the strips run the length of the board. This is purely for mental convenience since it enables each short strip to be assigned its own particular role, such as 'supply common', 'Vee positive', 'input', 'output', and so on, and few if any breaks in the strips are required. If one strip merely carries two connections there is still not, then, excessive wastage of the hole positions available. Similarly, if one strip does not have sufficient holes for all the connections that are to be made to it, there is no problem of connecting another strip to it by means of a jumper wire.

I find this approach is excellent for the case where I'm really rushed and I'm building up a circuit from scratch in as short a time as possible. And, of

FEBRUARY 1973

course, the result still looks good and neat.

If, on the other hand, I have more time to spare, I like to work out a layout design on paper first. Squared paper, such as is encountered in children's school exercise books, is excellent for this purpose. The intersections of the lines which form the squares represent the Veroboard holes. This method enables transistor lead-outs to fit into hole patterns, which correspond nicely with their lead-out layout, and also enables the larger capacitors to be installed between holes which just comfortably accommodate their length. If the circuit includes a transformer, a useful dodge consists of employing its two mounting lugs to jumper over one strip to another. The jumper connection is automatically carried over via the transformer frame itself. The transformer frame should normally be common with the earthy side of the supply, whereupon it can allow two separate strips to carry the earthy supply connection. Since the earthy side of the supply frequently takes more connections than any other conductor in a circuit, this idea can prove to be very convenient in practice.

Returning to the squared paper on which the initial design is worked out, I draw small circles in ink at the line intersections which correspond to the Veroboard holes, then sketch in the components, using circuit symbols, in pencil. 'Modifications' can then be carried out with an indiarubber. Also, the view is as seen from the component side of the board. With this method, incidentally, I find it better to have the copper strips run along the length of the Veroboard panel rather than across the width, as occurs with the quicker method of assembly. Naturally, there may be quite a few breaks in the strips.

I must stress that this pre-planning idea is simply one man's approach, and that many constructors will prefer to go straight to the Veroboard itself. Having assessed the size of board required for a particular project, they immediately start connecting up the components to it.

One final point about Veroboard which I like very much is its toughness. Ideally, once a component wire has been soldered at a Veroboard hole, it should be left alone. In practice, though, and provided reasonable care is used, it is surprising how many times, due to the trying out of different component values, connections can be soldered and unsoldered at a Veroboard hole before the copper foil and its adherence to the insulated board starts to suffer.

### KNOB TROUBLE

We all do a bit of servicing every now and again. This isn't usually an unwelcome chore, and quite a lot of

## Your Local Supplier

SURREY

### WITWORTH TRANSFORMERS TV Line out-put transformers

Manufacturers of the largest range in the country. All makes supplied.

Free catalogue.

Modern

BAIRD, BUSH, GEC, PHILIPS  
Replacement types ex-stock.  
For "By-return" service, contact London  
01-948 3702

Tidman Mail Order Ltd., Dept. R.C.  
236 Sandycombe Road,  
Richmond, Surrey TW9 2EQ

Valves, Tubes, Condensers, Resistors,  
Rectifiers and Frame out-put Transformers,  
Mains Transformers also stocked.  
Callers welcome.

SUSSEX

### E. JEFFRIES

For your new television set  
tape recorder, transistor radio  
and hi-fi equipment

PHILIPS, ULTRA, INVICTA  
DANSETTE, MASTERADIO, PERDIO,  
MARCONI, PHILCO FIDELITY

6A Albert Parade  
Victoria Drive,  
EASTBOURNE SUSSEX

YORKSHIRE

PASSINGHAM'S  
ELECTRONICS  
for Government Surplus  
Radio & T.V. Components  
Electronic Components  
also postal service

PASSINGHAM'S  
ELECTRONICS  
5 Dale Street  
Bradford 1  
Yorkshire

EIRE

### PEATS for PARTS ELECTRONIC COMPONENTS RADIO & TELEVISION

For the convenience of Irish  
enthusiasts we supply

The Radio Constructor  
Data Books and  
Panel-Signs Transfers

Also a postal service

Wm. B. PEAT & Co. Ltd.  
28 PARNELL STREET  
DUBLIN 1

The New Styled  
"MULTI-MINI" TWIN VICES



An extra "Pair of Hands" for those tricky jobs

ASSEMBLY - SOLDERING - GLUING - WIRING - DRILLING ETC.

- ★ INDEPENDENT ADJUSTMENT OF THE TWO VICE HEADS TO ANY ANGLE WITH POSITIVE LOCKING.
- ★ JAWS WILL FIRMLY GRIP ROUND, FLAT, SQUARE OR HEXAGONAL PARTS.

TWIN VICE: £8.95 (25p - p&p)

ALSO AVAILABLE

SINGLE VICE: £5.45 (21p - p&p)

Orders despatched before 1st April 1973. FREE of V.A.T.

CANLEY ENGINEERING (SALES) LTD.

Dept. C/RC4

OSBORNE ROAD, COVENTRY

Tel. (0203) 77163/4

CV5 6EA

RADIO & ELECTRONICS  
CONSTRUCTOR

**ANNUAL**  
**SUBSCRIPTIONS**  
to this magazine  
may be obtained  
through your  
newsagent  
or direct from the  
publishers  
**ONLY £2.70**  
per year, post free

Please send remittance with name and address and commencing issue required to:

**DATA PUBLICATIONS LTD**  
57 Maida Vale London W9 1SN

pleasure can be obtained from chasing down an obscure fault, repairing it and then seeing the equipment return to full working order.

Unfortunately, servicing has its minor vexations, these being caused not by the electronic team at the factory who designed the equipment to be repaired but by the presentation boys who set out to make it look attractive. I have no argument whatsoever over whether the finish of a set should be teak, veneer, plastic or anything else, but I would dearly love to have my own private aggro with those people, who dream up the nightmarish and impractical control knobs which appear on so many radio and TV receivers these days.

It is accepted practice for control knobs to be located on their spindles by means of springs, and this represents quite a happy state of affairs until the time comes to remove them. The knobs obviously have to be pulled off but the factory presentation team far too frequently design knobs which look highly decorative but offer no purchase whatsoever for their removal. One still occasionally also encounters knobs with long plastic extensions which pass right into the innards of the receiver before they encounter a spindle. It is only too easy to break the plastic whilst handling these knobs.

All these problems are infuriating enough, but I have now encountered what must be the ultimate in knob snags. It isn't even irritating - it's just ridiculous!

I recently had a fairly large transistor radio in for repair and, before taking the works out of its cabinet, I tried the effect of turning the wave-change switch from medium to long waves. The switch clicked over dutifully but the knob continued to turn. Somewhat mystified, I pulled the knob off the spindle, to find that I was holding its outer shell only. The plastic of the knob must have been badly cured during the moulding, and all its inside had simply crumbled away into a mass of floury powder!

STATIC

Nobody ever believes me when I say that I once got a sizeable belt, one hot Summer's day, on boarding a No. 16 bus at Marble Arch. I would hate to have to calculate how much static electricity a London Transport double-decker can pick up as it trundles along

Oxford Street but on that occasion quite a quantity found a path to earth via me when I put my hand on its rail.

Static electricity was, of course, known about thousands of years before our present times, and the word 'electricity' actually derives from the Greek 'eiktron', which means 'amber'. In those days, our forebears couldn't pop out and buy a PP9 battery; they had to generate their electricity by rubbing pieces of amber.

The earlier aircraft used to suffer from the effects of static electricity and they could pick up quite an unpleasant charge after they had been airborne for a while. The solution in those days consisted of developing landing wheel tyres which had a small percentage of graphite in their composition. The charge then leaked away to earth by way of these tyres when the aircraft landed. Older readers may recall that, during the war, barrage balloons were launched, on wire hawsers, from rubber tyred trailers. The metalwork of these trailers had to be earthed. Barrage balloon crews can tell hair-raising stories about the amount of static electricity picked up by the hawser if the earth connection to the trailer happened to be broken.

Static electricity can be a source of considerable trouble in electronic work. M. G. Scroggie in the latest edition of 'Foundations of Wireless' (Hilfe Books) points out that sufficient static electricity to break down the gate insulation of a MOSFET can be produced in the body simply by taking a step or two across a dry floor in rubber soled shoes. Car radio aerials can also pick up static, and car radios frequently have aerial input circuits which guard against damage due to static electricity. For many years now, nurses in hospital operating theatres have been advised not to wear nylon underclothes. The atmosphere in an operating theatre can reach explosive levels and a static spark due to a charge generated in the nylon could have, to say the least, disastrous effects.

Talking of ladies' underwear, I see that the latest sales campaign in these garments is centred around a new grade of what is described as 'anti-static' nylon. Charnos, who claim to be 'first with the non-cling thing' now produce a range which is manufactured from Monsanto 'Ultron' anti-static nylon. This is guaranteed to be free from the clammy sticky feeling given by ordinary nylon. Quite a change from the old days of Shocking Pink! ■

CROSSWORD

(Solution to the puzzle on page 456).

**Across.** 1. Resistor; 5. Danger; 9. Shoe-lace; 10. Log. Log.; 11. Epicycle; 12. I deals; 14. Valve Noise; 18. On All Fours; 22. Hybrid; 23. Modulate; 24. Linear; 25. Spurious; 26. Excite; 27. Lenz's Law.

**Down.** 1 Raster; 2. Stolid; 3. Selsyn; 4. Oscillator; 6. Avoiding; 7. Galv'anic; 8. Register; 13. Overcouple; 15. Rochelle; 16 Carbonic; 17. Claimant; 19. Quartz; 20. P. A. Coil; 21. Seesaw.

# WATFORD ELECTRONICS

35 CARDIFF ROAD WATFORD HERTS

C.W.O. PLEASE POST & PACKING, ADD 10p TO ORDERS UNDER £2.00

## RESISTORS

High stability, low noise, carbon film resistors

Tubular Miniature High Power Resistors.

Power Watts	Tolerance	Range	Values Available	Price 1-99 100+
$\frac{1}{4}$	5%	2-2-2.2M	E12	1p 0-8p
$\frac{1}{2}$	5%	2.2-10M	E12	1p 0-8p
1	5%	2.2-10M	E12	2p 1-5p
4	10%	1-10 ohm	E12	6p

Quantity prices available for any selection.

Ignore fractions on total order.

## CAPACITORS

ELECTROLYTICS, GENERAL PURPOSE, MINIATURE AXIAL LEAD.

MULLARDS 015, 016, 017 SERIES.

1uf	63V	6p
1.5uf	63V	6p
2.2uf	63V	6p
3.3uf	63V	6p
4.7uf	63V	6p
6.8uf	63V	6p
10uf	63V	6p
15uf	63V	6p
22uf	63V	6p
47uf	63V	6p
100uf	40V	6p
150uf	25V	6p
220uf	25V	11p
470uf	25V	13p
680uf	25V	20p
1000uf	25V	25p

## POLYESTER FILM CAPACITORS.

MULLARDS C296 SERIES.

400V DC.

uf: 0-001, 0-0015, 0-0022, 0-0033, 0-0047, 0-0068, 0-01, 0-015, 0-022, PRICE EACH 2½p.

uf: 0-033, 0-047, 0-068, 0-1 PRICE EACH 4p.

uf: 0-15 price 6p, 0-22 price 7p, 0-33 price 10p

uf: 0-47 price 13p.

160V DC.

uf: 0-1, 0-15 price 4p, 0-22 price 5p, 0-33 price 6p, 0-47 price 7p

0-68 price 10p, 1-0 price 13p

MULLARDS C280 SERIES. P.C. MOUNTING.

400V DC

uf: 0-01, 0-015, 0-022 price 3p, 0-033, 0-047 price 4p.

250V DC

uf: 0-068, 0-1, 0-15 price 4p, 0-22, 0-33 price 5p,

uf: 0-47 price 7p, 0-68 price 10p, 1-0 price 11p.

## CERAMIC DISC CAPACITORS

WORKING VOLTAGE 50V DC, Plaquette body with 25mm leads.

Range: 22pf-10,000pf price each: 2p.

## JACK PLUGS AND SOCKETS

Standard screened	12p	2.5 mm insulated	8p
Stereo screened	30p	3.5 mm screened	10p
Standard socket	12p	2.5 mm sockets	7p
Stereo sockets	15p	3.5 mm sockets	7p

## DIN PLUGS

2 pin, 3 pin, 5 pin (180 or 240)

plugs 10p, sockets 8p.

## SEMICONDUCTORS.

TRANSISTORS:

AC 126	12p	BD 131	60p	OC 45	10p
AC 127	12p	BD 132	60p	OC 70	10p
AC 128	12p	BF 194	15p	OC 71	10p
AD 161	30p	BF 195	15p	OC 72	10p
AD 162	30p			2N2926R	9p
AF 117	12p	BFY50	22p	2N29260	9p
BC 107	8p	BFY51	22p	2N2926V	9p
BC 108	8p	OC 26	40p	2N2926G	10p
BC 109	8p	OC 28	40p	2N3053	20p
BC 147	12p	OC 35	40p	2N3054	50p
BC 148	12p	OC 42	10p	2N3055	55p
BC 149	12p	OC 44	10p		

## ZENER DIODES

BZY88 Series. Power Dissipation 400mW. 5% tolerance.

Range: 3-3V to 30V. Price 12p each.

## LINEAR IC'S (DIL packaging).

709 30p DIL Sockets 14 and 16 pin. Price 20p each.

741 40p

723 80p

## DIODES & RECTIFIERS.

OA 85	7p	Bridge Rectifier
OA 90	5p	WO1 1A 100V price: 35p.
OA 91	5p	
1N4001	6p	
1N4004	7p	
1N4007	8p	

## POTENTIOMETERS

Carbon Track 1K-2M, log or linear, Single Gang, price 12p.

5K-2M, log or linear, Dual gang, price 37p.

5K-2M, log or linear, Single gang with switch 24p.

Knobs for above: 10p each

## SLIDER POTENTIOMETERS

SINGLE 10K, 25K, 50K, 100K, log or linear price: 35p

DUAL GANG 10K+10K, etc above values, log or linear price 50p

KNOBES for above price 10p

## PRESET POTENTIOMETERS SKELETON.

Horizontal or vertical mounting, 0-25W Miniature.

Price: 5p each.

## VEROBOARD

	0-1	0-15
	MATRIX	MATRIX
2½ × 3½	22p	16p
2½ × 5	24p	24p
3½ × 3½	24p	24p
3½ × 5	27p	27p
17 × 2½	75p	57½p
17 × 5 (plain)		82p
17 × 3½ (plain)		60p
17 × 2½ (plain)		42p
Pin insertion tool		52p
Spot face cutter		42p
Pkt of 50 pins	20p	20p

POST THIS COUPON FOR CATALOGUE

Please enclose 10p stamps for catalogue which contains details of items listed in this advert, and more. (Catalogues are free with order of £2 or more).

TO: WATFORD ELECTRONICS, 35 CARDIFF ROAD, WATFORD, HERTS.

NAME .....

(BLOCK CAPITALS PLEASE.)

ADDRESS .....

## THE 'PLUS' CATALOGUE

+ Technical data + Countless bargains + Discounts



+  
25p

### REFUND VOUCHER

The Electrovalue Catalogue now costs 25p (post free, surface mail) and is well worth it for its technical information. But we include with it a 25p refund voucher for spending on orders for £5 or more. You will find this catalogue a great money saver in every way.

- 96 Pages. (4th printing)
- Transistors, with technical specs.
- I.Cs with working diagrams
- Resistors, capacitors, components
- Diagrams, tables, information
- GENUINE DISCOUNTS

**ELECTROVALUE LTD.** Dept.  
R.C.2  
28 St. Judes Rd., Englefield Green, Egham, TW20 0HB  
9-6 daily: 1.0 p.m. Sat. Telephone Egham 3603

POTENTIOMETERS Lin or Log, 12p; with DP Switch, 23p; Dual Ganged, 36p; Special Offer, 5K with DP switch, 15p; WAVECHANGE SWITCHES, 22p; Special Offer, Miniature, 4P3W 16p; AMPLIFIERS: 1 Valve (EL84), £3; ½W Transistorised £1; 10W Transistorised, £3-75. JB3 Junction Box, £1-20. 5" Plastic Library Cases, 10p. 500uA TUNING METERS, 50p. CARTRIDGES: Compatible ACOS GP91-3SC, 90p; Stereo GP93-1, £1-15; Ceramic with Diamond Stylus, £1-80. CAPACITORS 100mF 25V, 5p; 220mF 25V, 5p; 400-200-50-16mF 300V, 30p; 0.1 500VDC, 300VAC, 3½p. MINIATURE INDICATOR LAMPS (5 colours), 11p; 6 or 12V Bulbs for above, 4p. MAINS NEONS panel mounting (red, green, clear), 15p. 100 MIXED RESISTORS, 45p. ROTARY SWITCHES (on/off) 250V 2A, 10p. PLUGS: Jack Standard, 10p; Screened, 13p; 2.5mm and 3.5mm, 6p; Screened, 8p. HEADPHONES: High Impedance (2,000 ohm), 90p; STEREO 8 ohm, £1-95; STEREO 8/16 ohm, £2-10. MICROPHONES: Lapel, 28p; ACOS MIC. 45, 90p; Dual Impedance Dynamic 600 ohm and 50k, £4-50. RECORDING TAPE: 5" LP 900ft., 45p; 5½" LP 1,200ft., 60p; 7" LP 1,800ft., 81p. RESISTORS: carbon film 5%, 1½p. ALUMINIUM CHASSIS from 6" x 3" to 16" x 10", all 2½" deep. Transistors, Rectifiers, etc. Large S.A.E. for list No. 4. Special Prices for quantity quoted on request. Add 10p for P&P on orders under £5.

**M. DZIUBAS**

158 Bradshawgate, Bolton, BL2 1BA. Lancs.

## DENCO (CLACTON) LIMITED

### 355-7-9 OLD ROAD, CLACTON-ON-SEA, ESSEX

Our components are chosen by Technical Authors and Constructors throughout the World for their performance and reliability, every coil being inspected twice plus a final test and near spot-on alignment as a final check.

Our General Catalogue showing full product range	..	18p
DTB4 Transistor & Valve circuitry for D.P. Coils	..	18p
DTB9 Valve Type Coil Pack Application circuitry	..	18p
MD.1 Decoder Circuitry for Stereo Reception	..	21p

All post paid, but please enclose S.A.E. with all other requests in the interests of retaining lowest possible prices to actual consumers

# SMALL ADVERTISEMENTS

Rate: 4p (9d) per word. Minimum charge 60p (12/-).  
Box No. 10p (2/-) extra.

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of advertisers. (Replies to Box Numbers should be addressed to: Box No. —, *The Radio Constructor*, 57 Maida Vale, London, W9 1SN

**SERVICE SHEETS** for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p. with free Fault Finding Guide. Catalogue 15p. Please send S.A.E. with all orders/enquiries. Hamilton Radio, 47 Bohemia Road, St. Leonards-on-Sea, Sussex. Telephone Hastings 29066.

**SHARPEN YOUR RESPONSES** with Vernitron ceramic i.f. resonators. Set of four **TF-04 442**, 455kHz, with associated capacitors for bandwidth 2, 4, 5.7, 7.5, 10 or 12kHz (state which), **£1.85**, U.K. post 5p. Mail order only. **AMATRONIX LTD.**, 396 Selsdon Road, South Croydon, Surrey CR2 0DE.

**BUILD IT in a DEWBOX** robust quality plastic cabinet 2 in. x 2½ in. x any length. S.A.E. for details. **D.E.W. Ltd.**, 254 Ringwood Road, Ferndown, Dorset. Write now - right now.

**FOR SALE: VHF KIT, 80 - 180 MHz.** Receiver, tuner, converter. World wide sales. Incomparable. **£4.00** or s.a.e. for literature. **Johnsons (Radio C), Worcester WR1 2DT.**

**FOR SALE: Widescreen cine outfit.** 9.5mm Prince camera fitted with Zenoscope Anamorphic lens, 9.5mm Specto projector with adaptor for Zenoscope lens, wide-screen 60 ins by 30 ins. Six 9.5mm cassettes for camera. £50 or would exchange for radio or other photographic equipment. Box No. G192.

**CATALOGUE NO. 18,** containing credit vouchers value 50p, now available. Manufacturers new and surplus electronic and mechanical components, price 23p post free. **Arthur Sallis Radio Control Ltd.**, 28 Gardner Street, Brighton, Sussex.

**COMPONENT KITS FOR "R & E.C." OSCILLOSCOPE:** £9.50 (Tube £4). P.W. reverb. £9.50 (spring line £7.50). P.E. Versatile lighting unit £9.50. Many others cheaper, also components. S.A.E. lists. **A. Gray**, 30 Baker Street, London W1M 2DS.

**BUILD THE MULLARD C.C. TV CAMERA.** Complete kits now available from Crofton Electronics. Send large s.a.e. for details to: 15-17 Cambridge Road, Kingston-Upon-Thames, Surrey. Reply by post. No callers please.

**"WORLD RADIO TV HANDBOOK" 1973, £2.90** "HOW TO LISTEN TO THE WORLD", £2.00. **CONFIDENTIAL FREQUENCY LIST**, stations' QSL policies, etc., £1.80. Callbooks: USA £3.95, rest of world £3.10, British Isles 70p. First class post included. **David McGarva**, Box 114 (REC), Edinburgh, EH1 1HP.

**WANTED: Early books on wireless, pre-1925.** Details to Box No. G198.

**CHROMASONIC ELECTRONICS.** New list 10p. post free. Data Dept., 56 Fortis Green Road, London, N10 3HN.

**TAPE-HEADS RECONDITIONED.** Guaranteed satisfaction. Send worn head enclosing £2 to Sara Electronics, Fawkham Avenue, Longfield, Kent.

(Continued on page 469)

## BENTLEY ACOUSTIC CORPORATION LTD.

The Valve Specialists

The Old Police Station, Gloucester Road, LITTLEHAMPTON Sussex. PHONE 6743

OA2 .30	12AV6 .28	EABC80	EL91 .23	PFL200.50	UL41 .54
OB2 .30	12BA6 .30		EL95 .32	PL36 .46	UL84 .28
3L4G .30	12BE6 .30	EAFA2 .48	EL180 .75	PL81 .42	UY41 .38
5V4G .33	12K5 .50	EAFA80.50	EM80 .37	PL82 .38	UY85 .23
5Y3GT.25	12SQ7 .50	EB34 .20	EM81 .37	PL83 .30	X41 .50
5Z4G .33	19A05 .24	EB91 .10	EM83 .75	PL84 .28	AC165 .25
6/30L2 .53	20P4 .89	EBFC41 .48	EM84 .31	PL504 .60	AD140 .36
6AH6 .50	30C15 .55	EBG81 .29	EM87 .34	PL508 .90	AD149 .50
6AJ5 .75	30C17 .74	EBF80 .30	EY51 .29	PL509 1.30	AD161 .45
6AQ5 .21	30C18 .58	EBF83 .38	EY81 .35	PL802 .75	AD162 .45
6AT6 .18	30F5 .61	EBF89 .26	EY83 .54	PY132 .50	AF114 .25
6AU6 .19	30F11 .58	ECY2 .34	EY87/6 .27	PY81 .24	AF115 .15
6AV6 .28	30F12 .58	ECC33.50	EY88 .40	PY82 .21	AF121 .30
6BA6 .19	30F14.66	ECC81 .16	EZ40 .40	PY83 .26	AF126 .18
6BE6 .20	30L15 .55	ECC82.19	EZ80 .19	PY88 .31	BC107 .13
6BH6 .43	30L17 .65	ECC83 .21	EZ81 .20	PY500 .95	BC108 .13
6BJ6 .39	30P12 .69	ECC84 .28	GY501 .75	PS800 .31	BC113 .25
6BR7 .79	30P19 .55	ECC85 .32	GZ34 .47	PY801 .31	BC118 .23
6BW6 .72	30PL1 .57	ECC88 .35	HVR2 .53	QOY01 .38	BC211 .38
6BW7 .50	30PL13 .75	ECF80 .27	KTW61.63	1.0	BF159 .25
6BZ6 .31	30PL14 .62	ECF82 .25	KTW62.63	R19 .28	BF161 .20
6C4 .28	30PL15 .87	ECF86 .64	KTW63.50	U19 1.73	BF180 .30
6C5 .55	35A3 .48	ECH35.50	K166 .80	U25 .62	BY100 .18
6E1 .59	35L6GT.42	ECH42 .57	PC86 .44	U26 .53	BY126 .15
6F1 .59	35W4 .23	ECH81 .25	PC88 .44	U191 .56	BY127 .18
6F18 .45	35Z4 .24	ECH83 .38	PC97 .36	U251 .62	OAB1 .09
6F23 .65	35Z5 .30	ECH84 .34	PC900 .36	U301 .40	OAS1 .09
6F28 .60	50C5 .32	ECL80 .28	PCC84 .27	U801 .76	OAS9 .09
6H6GT .15	50L6GT.45	ECL82 .28	PCC88 .39	UABC80	OC23 .38
6K7G .10	90C1 .59	ECL83 .52	PCC89 .42		OC24 .38
6K8G .16	90CG 1.70	ECL84 .54	PC189.46	UBC41 .45	OC25 .38
6L6GT .39	DAF91 .20	ECL86 .33	PCF80 .20	UBC81 .40	OC30 .32
6O7GT .43	DAF96 .33	EF22 .63	PCF82 .30	UBF80 .28	OC44 .10
6Q7(M).43	DF91 .14	EF41 .58	PCF84 .40	UBF89 .28	OC45 .11
6C4GT .60	DF96 .34	EF80 .21	PCF86 .44	UC92 .35	OC46 .15
6V6G .17	DK91 .26	EF83 .54	PCF801.28	UC98 .33	OC70 .13
6X4 .20	DK92 .35	EF85 .25	PCF802.37	UC985 .31	OC71 .11
7Y4 .60	DK96 .35	EF86 .27	PCF806.55	UCF80 .31	OC72 .11
9D7 .78	DL92 .23	EF89 .23	PCL82 .29	UCH42 .57	OC74 .23
10F1 .17	DL96 .35	EF91 .17	PCL83 .54	UCH81 .29	OC75 .11
10F18 .35	DY87/6.22	EF92 .28	PCL84 .32	UCL82 .30	OC78 .15
12A6 .63	DY802 .29	EF183 .25	PCL805.37	UCL83 .48	OC78D .15
12AC6 .40	E80C1.65	FF184 .27	PCL86 .36	UF41 .50	OC81 .11
12AD6 .40	E80T1.20	FF190 .34	PD500 1.44	UF80 .35	OC81D .11
12AE6 .44	EB8C .60	LL34 .44	PE845 .40	UF85 .34	OC82 .11
12AT6 .23	F180F .90	EL41 .53	PE845DD	UF86 .63	OC83 .20
12AV6 .21	FA50 .27	EL84 .21		UF89 .27	OC84 .24

All goods are unused and boxed, and subject to the standard 90-day guarantee. Terms of business: Cash or cheque with order only. No C.O.D. orders accepted. Post/packing charge 3p per item subject to a minimum of 9p per order. Orders over £5 post free. All orders despatched same day by first class mail. Complete catalogue with conditions of sale 7p post paid. Any parcel insured against damage in transit for only 3p extra per order. Business hours 9 a.m.-5.30 p.m., Mon.-Fri. Closed Saturdays. Please enclose S.A.E. with all enquiries.

## Learn to understand electronics for your hobbies

### 1. Lerna-Kit course

Step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered.

- (1) BUILD AN OSCILLOSCOPE.
- (2) READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS.
- (3) CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK.

### 2. Become a Radio-Amateur

Learn how to become a radio-amateur in contact with the wide world. We give skilled preparation for the G.P.O. licence.

**FREE** **23** Brochure, without obligation to:  
**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL**  
P.O. BOX 156, JERSEY, CHANNEL ISLANDS.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

BLOCK CAPS PLEASE

## PRECISION

### POLYCARBONATE CAPACITORS

**Fresh Stock - Fully Tested and Guaranteed**

Close tolerance professional capacitors by well-known manufacturer. Excellent stability and extremely low leakage. All 63V D.C.

0.47 $\mu$ F:	$\pm 5\%$	30p:	$\pm 2\%$	40p:	$\pm 1\%$	50p
1.0 $\mu$ F:	$\pm 5\%$	40p:	$\pm 2\%$	50p:	$\pm 1\%$	60p
2.2 $\mu$ F:	$\pm 5\%$	50p:	$\pm 2\%$	60p:	$\pm 1\%$	75p
4.7 $\mu$ F:	$\pm 5\%$	70p:	$\pm 2\%$	90p:	$\pm 1\%$	115p
6.8 $\mu$ F:	$\pm 5\%$	95p:	$\pm 2\%$	115p:	$\pm 1\%$	150p
10.0 $\mu$ F:	$\pm 5\%$	110p:	$\pm 2\%$	140p:	$\pm 1\%$	180p
15.0 $\mu$ F:	$\pm 5\%$	160p:	$\pm 2\%$	210p:	$\pm 1\%$	270p

### NEW! — TANTALUM BEAD CAPACITORS

Values available .22, .47, 1.0, 2.2, 4.7, 6.8  $\mu$ F at 35V, 10  $\mu$ F 25V, 15  $\mu$ F 20V, 22  $\mu$ F 15V, 33  $\mu$ F 10V, 47  $\mu$ F 6V, 100  $\mu$ F 3V. All at 9p each; 6 for 50p; 14 for £1.00. Special pack, 6 off each value (72 capacitors) for £5.00.

**TRANSISTORS:** BC107; BC108; BC109 (please state which), all at 9p each, 6 for 50p; 14 for £1.00; May be mixed to qualify for lower price. All brand new to full manufacturer's specification.

**POPULAR DIODES:** IN914 - 7p each; 8 for 50p; 18 for £1.00  
IN916 - 9p each; 6 for 50p; 14 for £1.00. IS44 - 5p each; 11 for 50p; 24 for £1.00. All brand new and marked.

**400mW ZENER DIODES:** Values available 4.7, 5.6, 6.8, 7.5, 8.2, 9.1, 10, 11, 12, 13.5, 15 volts. All new and marked. All at 10p each; 6 for 50p; 14 for £1.00.

**RESISTORS:** Carbon film  $\frac{1}{8}$  watt 5%. Range 2.2  $\Omega$ -2.2M  $\Omega$  E12. Series i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82, and their decades. All at 1p each, 8p for 10 of any one value; 70p for 100 of any one value. Special development pack 10 off each value 2.2  $\Omega$  to 2.2M  $\Omega$  (730 resistors) for £5.00.

**440V A.C. CAPACITORS:** 0.1  $\mu$ F: Size 1  $\frac{1}{8}$ "  $\times$   $\frac{1}{2}$ ", 25p each  
0.25  $\mu$ F: Size 1  $\frac{3}{8}$ "  $\times$   $\frac{3}{8}$ ", 30p each 0.5  $\mu$ F: Size 1  $\frac{3}{8}$ "  $\times$   $\frac{1}{2}$ ", 35p each  
1.0  $\mu$ F: Size 2"  $\times$   $\frac{3}{8}$ ", 45p each 2.0  $\mu$ F: Size 2"  $\times$  1", 75p each  
Suitable for use on C.D. ignition, 250V A.C. motors, etc.

5p post and packing on all orders below £5

V.ATTWOOD, Dept C.4., P.O. Box 8, Alresford, Hants.

## RSGB BOOKS FOR YOU

### TELEVISION INTERFERENCE MANUAL by B. Priestley, BSc., G3JGO

A wealth of tvf information. The causes of interference by amateur transmitters to television, and audio, equipment is examined and ways in which it may be avoided and suppressed are suggested.

100 pages.

90p post paid.

### RAE MANUAL

by G. L. Benbow, G3HB Sixth edition  
The standard work for all would-be licensed radio amateurs studying for the Radio Amateurs' Examination. A completely re-written edition brought fully up to date to meet the present examination syllabus requirements.

96 pages

90p post paid

### RADIO COMMUNICATION HANDBOOK

832 pages of everything in the science of radio communication. The Handbook's U.K. origin ensures easy availability of components. Complete coverage of the technical and constructional fields. A superb hard-bound volume.

£4.10 post paid.

These are three of a complete range of technical publications, log books and maps, all obtainable from:

**RADIO SOCIETY OF GREAT BRITAIN**


Doughty Street, London, WC1N 2AE

# NEW STYLE SELF-BINDER

for "The Radio Constructor"

The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

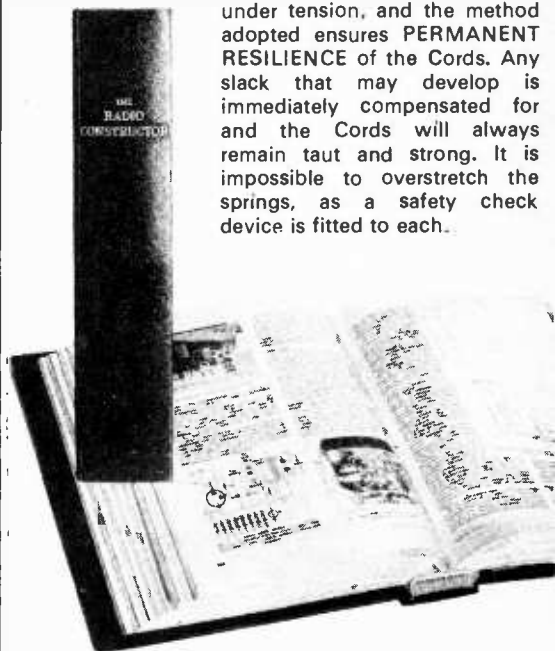

PRICE **75p** P. & P. 14p

Available only from:—

**Data Publications Ltd.**  
57 Maida Vale London W9 1SN

## SMALL ADVERTISEMENTS

(Continued from page 467)

**MASTER THE DIGITAL REVOLUTION.** Don't be left behind. "Digital Computer Logic & Electronics" a teach-yourself introduction to binary and octal number systems, logic elements, truth tables, Boole, De Morgan, circuit design, flip-flops and registers. Four separate books with more than 200 clear, helpful stage-by-stage questions. Show yourself you can design digital circuits. £3 incl. P. & P. Money back guarantee if dissatisfied. Dept. RC, Cambridge Learning, 8a Rose Crescent, Cambridge.

**VISCONOL CATHODRAY CONDENSERS** 0.0025 mfd. 2.5kV 30p each, 0.002 mfd 15kV 60p, 0.02 mfd 12.5kV 65p, 0.025 mfd 5kV 40p, 0.1 mfd 6kV, 0.5 mfd 2.5 kV, 1 mfd 2kV, £1 each. **CAPACITORS** 0.1 mfd 150 volt £1 per 100, 44,000 available. **MORSE KEYS** precision type 50p each. **STROBOSCOPE FORKS** 125 cycles £1.50 each. **JACK PLUGS** 2 point screw on cover 15p each. Send for Lists. L. Wilkinson (Croydon) Ltd., Longley House, Longley Road, Croydon, Surrey.

**FOR SALE:** 22,000  $\frac{1}{2}$ W to 10W resistors, assorted values. Offers? Please write to: N. Bacon, 16 Longbourne Way, Chertsey, Surrey. KT16 9EB.

**FOR SALE:** Back numbers of *The Radio Constructor*, Volumes one to twenty-four, also *Popular Electronics* from October 1969 to December 1971. Offers please. Box No. G205.

**ARE YOU A MOTORING ENTHUSIAST?** The Seventy-Five Motor Club caters for all types of motor sport-racing, rallies, hill climbs, etc. Monthly Bulletin free to members. For full details write to: The General Secretary, Colin Peck, "Dancers' End", St. Winifred's Road, Biggin Hill, Kent.

**JOIN THE INTERNATIONAL S.W. LEAGUE.** Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. - both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazines, etc., £2.00 per annum. (U.K. and British Commonwealth), overseas 6 Dollars or £2.50. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

**WANTED:** Copy of the original RTTY Manual produced by the British Amateur Radio Teleprinter Group. Box No. G206.

**FOR SALE:** 50 resistors 16p. 50 capacitors 40p. Magnetic counters 10p. 100 6BA bolts 10p. 50 nuts 10p. Intercoms. £2.20. Stereo headphones £1.99. Lists and samples 20p. Postage extra. Derwent Radio, 28 Hillcrest Avenue, Scarborough, Yorks.

**FOR SALE:** Kindermann Model 3163 stainless steel 35mm developing tank, plus two thermometers. £3.00. Box No. G207.

**WORLD DX CLUB** covers all aspects of SWLing on Amateur and Broadcast Bands through its monthly bulletin "Contact". Membership costs £1.38 a year. Enquiries to Secretary, WDXC, 11 Wesley Grove, Portsmouth, Hants.. PO3 5ER.

(Continued on page 471)

**Soksol De-Solder Kits:** All kits are supplied with copper braid which has a scientifically formulated weave to conform to all surface irregularities ensuring maximum solder lift-off; complete with chemical solution and full instructions. Type 1 with 9 ft braid 50p, post 10p. Type 2 with 20 ft braid £1.00, post 15p. Type 3 (industrial pack) 50 ft braid £2.50, post free.

Sample of processed braid 10p (P.O. or stamps).

**Visconol EHT Capacitors:** .001µF, 20KV 50p, .01µF 5KV 40p, .01µF 10KV 50p, .02 µF 5KV 40p.

**Electrolytic Capacitors:** UF/V 1250/25, 2000/35, 2200/25, 4700/16, 8000/30, 10,000/15, 10,000/25, 10,000/35, 1000+1000/40, 16+16/500. All at 35p each, post free.  
16 x 16/350, 32 x 16/350, 32 x 32/350, 40 x 40/250, 50 x 50/300, 80 x 80/450, 100 x 100/385, all at 25p each, post free.  
100 x 200/275, 100 x 400/275, 200 x 200/350, 60 x 250 x 10/300  
100 x 50 x 50/385, 100 x 50 x 150/350, 100 x 100 x 47/320, 100 x 100 x 200/275, 150 x 200 x 250/300, 200 x 250 x 250/275, 130 x 60 x 10 x 10/350, 200 x 100 x 10 x 10/300V, 200 x 100 x 50 x 2/300, 200 x 200 x 100 x 32/275. All at 60p each, post free.

**Photoflash Capacitors:** 2000µF, 275 volts £1.25, post 15p.

**Bargain Component Parcels** include Rotary and Slide Switches, Potentiometers, Valveholders, I'fs, Sockets, Capacitors, Transistor Panels, plus a generous selection of other components. Here's unbeatable value, 4 lb. nett weight £1.00, post 40p.

**Assorted Capacitors** including Silver Mica/Polystyrene/Ceramic. Special offer packs 5x20, different values, 50p, post 10p.

Huge selection of Capacitors, A.C. Motor Start, Block, Reversible Electrolytics, etc., etc. Let us know your exact requirements.

## ELEKON ENTERPRISES

224a St. Paul's Road, Highbury Corner  
London N. 1.

## FREE TO AMBITIOUS ENGINEERS


— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

### SEND FOR YOUR FREE COPY TO-DAY

**NEW OPPORTUNITIES** is a highly informative 76 page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern home study courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics courses administered by our Specialist Electronics Training Division - explains the benefits of our free Appointments and Advisory service and shows you how to qualify for five years promotion in one year.

### PRACTICAL EQUIPMENT INCLUDING TOOLS

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with all the practical equipment you need, plus basic practice and theoretical Courses for beginners in Radio, TV, Electronics, etc.

CUT OUT THIS COUPON 

Tick or state subject of interest. Post to address below.

AMSE (Elec)  City & Guilds Certificate  RTEB Certificate   
Radio Amateurs' Exam  DMG Certificate  Colour TV   
Electronic Engineering  Computer Electronics  Radio and TV  
Servicing  Practical Electronics  Practical TV and Radio

### BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. (BRE 13), Aldermaston Court, Reading RG7 4PF  
Accredited by the Council for the Accreditation  
of Correspondence Colleges

QC BRE 14

NAME .....

(BLOCK CAPITALS PLEASE)

ADDRESS .....

OTHER SUBJECTS..... AGE.....

# RADIO MODELLER

**RM**  
BOOK  
SERIES

## ELECTRONIC BOOKS

### ● MODEL RADIO CONTROL


Detailing both Theory and Practice, this book, by leading authority Paul Newell, will become the standard reference work. A brief historical survey leads up to a detailed description of proportional systems, with over 100 illustrations, including theoretical circuits and p.c. layouts for an advanced digital system. 134 pages. Price £2.25 U.K. Postage 13p

### ● SINGLET SET

The Singlet Transmitter, Superhet and Super-regen receivers, are now all three available in one book. Complete construction details with full size p.c. layout, components list etc. Ideal introduction to the hobby for the home constructor. 20 pages. Price 30p. U.K. Postage 3p
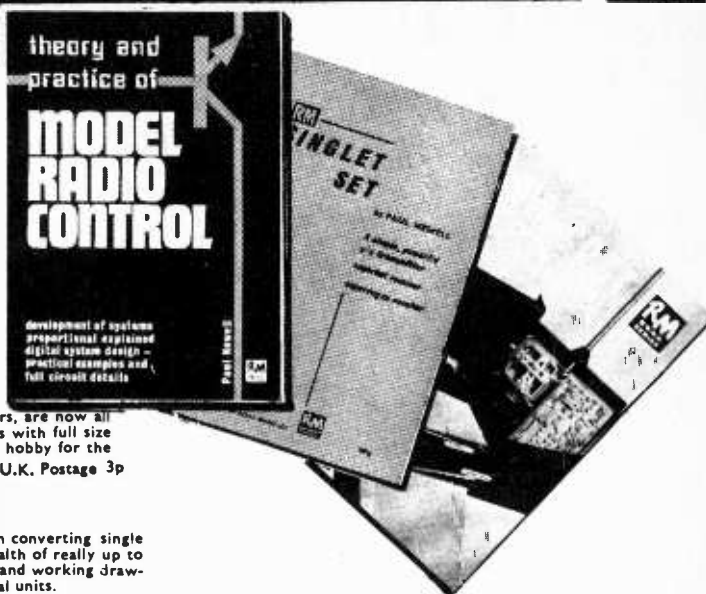
### ● LOW COST PROPORTIONAL

Modellers who want to save money buy this volume when converting single channel equipment to simple proportional. They find a wealth of really up to date information in the clear descriptions, full size practical and working drawings, plus over a dozen circuit modules for pulse proportional units. 118 pages. Price £1.05 U.K. Postage 11p



ON SALE NOW at all leading shops or direct from:—

RADIO MODELLER, BOOK SALES, 64 Wellington Road, Hampton Hill, Middx.

## PLAIN-BACKED NEW STYLE SELF-BINDERS

The "CORDEX" Patent Self-Binding Case will keep your copies in mint condition. Issues can be inserted or removed with the greatest of ease. Specially constructed Binding cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for, and the Cords will always remain taut and strong. It is impossible to over-stretch the springs, as a safety check device is fitted to each.

PRICE **70p** P. & P. 14p

Available only from:—

**Data Publications Ltd.** 57 Maida Vale London W9 1SN

for your other magazines  
(max. format 7½" x 9½")



COLOURS: MAROON OR GREEN  
(If choice not stated, colour available will be sent)



## SMALL ADVERTISEMENTS

(Continued from page 469)

**FOR SALE:** R1155B receiver with psu. Working order. £20, carriage extra. Miles, 17 Queen's Road, Blandford Forum, Dorset.

**FOR SALE:** Harmsworth's Wireless Encyclopedia. Three volumes. Collector's item. £5.00. Box No. G208.

**IF YOU HAVE ENJOYED A HOLIDAY** on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from:- The Hon. Membership Secretary, The Broads Society, "Icknield", Hilly Plantation, Thorpe St. Andrew, Norwich, NOR 85S.

**FOR SALE:** E.H.T. voltmeter £2. Electronic Ignition £6. Camera, new, £5. Copying machine £9. Chapman Radio Hi-Fi speaker, cost £50, offers? 4 Riversley Road, Gloucester, GL2 0QT.

**FOR SALE:** 9.5mm Specto projector, 100 watt lamp. Excellent condition. £12.00. Box No. G209.

**"MEDIUM WAVE NEWS"** Monthly during Dx season - Details from: K. Brownless, 7 The Avenue, Clifton, York.

**ESSEX GARDENERS.** Buy your bedding and rock plants, shrubs, etc., also cacti from May's Nurseries, 608 Rayleigh Road, Hutton, Brentwood, Essex. Callers only. Monday to Saturday.

**MECCANO FOR "CYCLOPS"** - Special Pack of all Meccano parts required - £3.39 including postage. Send off today to The Meccano Spare Parts Specialists and start building! "Everything Meccano" at M. W. MODELS, 165 Reading Road, Henley-on-Thames, Oxon. Telephone 3342.

**FOR ALL YOUR ELECTRONIC COMPONENT** requirements. Send for free list to:- B. C. Electronic Supplies, 7 Regent Road, Huddersfield, HD1 4NR.

**POSTAL ADVERTISING?** This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. - The Holborn Direct Mail Company, Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 1495.

**THE BRITISH AMATEUR ELECTRONICS CLUB.** A club for all who are interested in electronics as a hobby. Quarterly Newsletter sent free to members. Subscription 50p per year. Details from Hon. Secretary, J. G. Margetts, 17 St. Francis Close, Abergavenny, Mon.

**RECITALS OF RECORDED MUSIC.** The second Saturday evening of each winter month. Next recital: Feb. 10th, 1973, 8 p.m. at Woodford Green United Free Church Woodford Green, Essex. Bus routes 20, 20A, 179 and 275-alight at "The Castle" stop.

**Q MULTIPLIER COILS.** High efficiency pot core assemblies for use in the range 50kHz - 2MHz. Other frequencies to order. 50p. each plus 5p. p. & p. State frequency required and whether p.c. or single hole mounting. Overseas enquiries invited. Storey, 145 The Knarcs, Basildon, Essex.

### SITUATIONS VACANT

**SOUND EQUIPMENT INSTALLATION** and Service Engineer for Public-Address specialists. Interesting and varied work. 5-day week. Must have good working knowledge of audio, (radio might do), and clean driving licence. Contact Mr. N. Reder, Reder Sound Installations, Jubilee Works, Esther Road, London E.11. Telephone: 539 0136.

FEBRUARY 1973

# Get paid for your hobby!

Become an expert in Radio, Television and Electronic Engineering.

Take an ICS home study course, specially designed to help you gain the qualifications that will entitle you to higher pay and a more interesting career.

ICS individual tuition has a long-standing reputation for success in these important examinations: C & G Telecommunications Certs., Radio Amateurs Examination, General Radiocommunications Certs., C & G Radio Servicing Theory.

Alternatively, you can choose an ICS colour/mono T.V. servicing course or practical radio and electronics courses that provide essential practical experience as you build. Transistor portable receivers, signal generators, multi-test meters. And whatever you build is yours to keep. All components are supplied PLUS expert coaching in basic electronic theory and practice.

Post this coupon today for a FREE Course Guide and find out how to turn your hobby into money.

Please send me, without obligation, my FREE BOOKLET on Radio, Television and Electrical Engineering.

Name.....Age  
(BLOCK CAPITALS)

Address .....

..... Occupation .....

**ICS** your key to the door  
of opportunity

International Correspondence  
Schools, Dept. 733D, Intertext  
House, Stewarts Road, London  
SW8 4UJ

## THIS MONTH'S BARGAIN FOR BARGAIN HUNTERS

100 square ins. (min.) packs of best quality mixed veroboard only £1.15p post/packing free.

C.W.O. to PASSINGHAM'S ELECTRONICS

5 Dale Street, Bradford 1, Yorkshire.

Tel. Bradford 25388

## MORSE MADE EASY!!!

**FACT NOT FICTION.** If you start RIGHT you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.) Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18-W.P.M. in 4 weeks guaranteed. Beginner's Section only £3.50. Complete course £4.50 (Overseas £1 extra). Details only, 4p stamp. 01-866 2895

G3HSC/Box 38, 45 GREEN LANE, PURLEY, SURREY.

*Recent Publications	*KILRIMONT BOOKS	*No American reprints
110 I.C. Projects (Marston)	£1.20 (+5p post)	
Electronic Designer's Handbook (Hemingway)	£3.40	
Computer Science (Harvey)	£2.00	
Colour T.V. Picture faults (Bohman)	£2.50	
Understanding Electronic Components (Sinclair)	£3.50	
Audio Technicians Bench Manual (Earl)	£3.00	
Mazda Book of P.A.L. Servicing (Seal) (reprinted)	£3.80	

\*Post free unless indicated. \*S.A.E. for lists

KILRIMONT BOOKS©

Kilriment House. London Road. BRAINTREE. Essex. CM7 8QL

## SYNTHESISER MODULES

Voltage-controlled modules for synthesiser construction and other musical MIRACLES! Catalogue 15p. D.E.W. Ltd., 264 Ringwood Road, Ferndown, Dorset.

### CASED AMPLIFIER £3

Oak faced wooden case, size 14x13x9", contains very sensitive amplifier using 2 x ECC83, EL84, EZ80. 20 $\mu$ V I/P gives 2 watts O/P. Incorporates 4KHz tone detector. Tone and volume controls. 7x4" 3 OHM speaker with extrn. socket. Also included is a somewhat unusual solenoid operated tape deck with 4 pole motor. Standard mains operation, in good working condition £3 + £1 carr.

### 300 RESISTORS 60p

300 5% 60p (15p) 200 5% Hi-stab 60p (12p) 100 1% & 2% 60p (8p) 100 metal oxide 60p (8p) one of each pack £2 (25p). Ferric Chloride 1lb 40p (15p) 10lbs £3.50 (40p) 2N3055 35p BC107-8-9 8p.

GREENWELD (R2) 24 Goodhart Way, W.Wickham, Kent. Tel: 01-777 2001 up to 10.30p.m. Post in brackets SAE list.

## ESSENTIAL BOOKS

**HOW TO MAKE WALKIE-TALKIES FOR LICENSED OPERATION.** Only 40p post free. **MOBILE RADIO TELEPHONES.** Important reference book for users of commercial mobile communications equipment. Includes chapters on installation, operation and maintenance. Contains photos and diagrams etc. Price £2.60, including post. **THE SCATTERING & DIFFRACTION OF WAVES.** A goldmine of information for the experimenter, student, amateur & scientist. Profusely illustrated. Published by Oxford University Press. Price £1.60 post free. **GOVERNMENT SURPLUS WIRELESS EQUIPMENT HANDBOOK.** Contains circuits, data, illustrations and valuable information for British/USA receivers, transmitters, trans/receivers. With modifications to sets and test equipment. Latest impression £3.25, incl. postage. Available from: Dept. RC. GERALD MYERS, 18 SHAFTESBURY STREET, LEEDS LS12 3BT.

## MEN! £50p.w.can be yours

Jobs galore! 144,000 new computer personnel needed by 1977. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks!

Pay prospects? £2,500+p.a.

After training, our exclusive appointments bureau — one of the world's leaders of its kind — introduces you **FREE** to world-wide opportunities. Write or phone **TODAY**, without obligation.

London Computer Operators Training Centre  
P18, Oxford House, 9-15 Oxford Street W.1.

Telephone: 01-437-9906

127 The Piazza, Dept. P18, Piccadilly Plaza, Manchester 1  
Telephone: 061-236 2935

## FREQUENCY LIST TRANSFERS

We have a limited supply of sheets of Dial Frequency Transfers in black. Short Wave frequencies 1.8Mc/s to 32Mc/s and 144Mc/s and 146Mc/s. Includes amateur band marker frequencies at 100kc/s points and other short wave frequencies from 2 to 32Mc/s at every 500kc/s points. Each frequency is repeated. Two sheets for 5p, five sheets for 10p, postage 3p.

DATA PUBLICATIONS LTD.,  
57 Maida Vale, London W9 1SN.

## DATA BOOK SERIES

- DB5 TV FAULT FINDING  
124 pages. Price 50p, postage 6p.
- DB6 RADIO AMATEUR OPERATOR'S HANDBOOK  
80 pages. Price 45p, postage 6p.
- DB16 RADIO CONTROL FOR MODELS  
192 pages. Price 75p, postage 8p.
- DB17 UNDERSTANDING TELEVISION  
512 pages. Price £2.10, postage 25p.
- DB18 AUDIO AMPLIFIERS  
128 pages. Price 53p, postage 6p.
- DB19 SIMPLE SHORT WAVE RECEIVERS  
140 pages. Price 80p, postage 6p.

I enclose Postal Order/Cheque for \_\_\_\_\_ in payment for \_\_\_\_\_

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

(BLOCK LETTERS PLEASE)

Postal Orders should be crossed and made payable to Data Publications Ltd.

Overseas customers please pay by International Money Order.

All publications are obtainable from your local bookseller.

Data Publications Ltd., 57 Maida Vale, London W9 1SN

**PLEASE MENTION THIS MAGAZINE WHEN WRITING TO ADVERTISERS**

## COIL DATA IV

The Table gives calculated inductance values, in microhenrys, of single-layer air-cored coils having diameters of 1 and 1½ in. and lengths (l) as shown. Thus, a 35-turn coil of diameter 1½ in. and length 1½ in. has a calculated inductance of 23.0 $\mu$ H.

Turns	Dia. 1 in.				Dia. 1½ in.			
	l = ¾ in.	l = 1 in.	l = 1½ in.	l = 2 in.	l = ¾ in.	l = 1 in.	l = 1½ in.	l = 2 in.
	4	0.33	0.27	0.24	0.21	0.48	0.40	0.34
6	0.75	0.62	0.53	0.46	1.1	0.90	0.78	0.61
8	1.3	1.1	0.94	0.82	1.9	1.6	1.4	1.2
10	2.1	1.7	1.5	1.3	3.0	2.5	2.2	1.9
15	4.7	3.9	3.3	2.9	6.7	5.6	4.8	4.2
20	8.3	6.9	5.9	5.1	12.0	10.0	8.6	7.6
25	13.0	11.0	9.2	8.0	19.0	15.0	13.0	12.0
30	19.0	16.0	13.0	12.0	27.0	23.0	19.0	17.0
35	26.0	21.0	18.0	16.0	36.0	31.0	26.0	23.0
40	33.0	28.0	24.0	21.0	48.0	40.0	34.0	30.0
45								
50	42.0	35.0	30.0	26.0	60.0	51.0	44.0	38.0
55	52.0	43.0	37.0	32.0	74.0	63.0	54.0	47.0
60	63.0	52.0	44.0	39.0	90.0	76.0	65.0	57.0
	75.0	62.0	53.0	46.0	110.0	90.0	78.0	68.0

# U.K.'s LARGEST ELECTRONICS CENTRES! HENRY'S RADIO LTD. EDGWARE ROAD, LONDON, W.2.



**NOW OPEN!**


404-406 ELECTRONIC COMPONENTS & EQUIPMENT 01-402 8381  
354-356 HIGH FIDELITY & TAPE EQUIPMENT 01-402 5854/4736  
309 PA - DISCO - LIGHTING HIGH POWER SOUND 01-723 6963

303 BARGAIN STORE SPECIAL OFFERS All Mail to: 303, Edgware Rd., London, W2 1BW

ALL YOUR ELECTRONIC REQUIREMENTS WITHIN 200 YARDS. CALL IN AND SEE FOR YOURSELF.
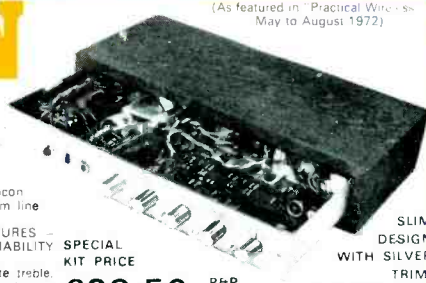
## BUILD THE TEXAN 20 + 20 WATT INTEGRATED I.C. STEREO AMPLIFIER

**FREE TEAK CABINET** with complete kits  
**FEATURES** New slim design with 6 - IC's, IC sockets, 10 silicon transistors 4 rectifiers, 2 zeners Special Gardeners low field slim line transformer Fibreglass PC panel. Complete chassis work  
**HIGH QUALITY AND STABILITY ARE PREDOMINATE FEATURES - DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION.**  
**FACILITIES** On/off switch indicator, headphone socket, separate treble bass volume and balance controls, scratch and rumble filters, mono/stereo switch, Input selector, Mag. P.U. Radio Tuner, Aux. Can be altered for Mic. Tape, Tape head etc. (Parts list Ref. 20 on request)  
(Parts list Ref. 20 on request)  
Constructional details Ref. No. 21 30p  
Designed approved kits distributed by Henry's Radio Ltd.



(As featured in "Practical Wire-ss" May to August 1972)

SPECIAL KIT PRICE

**£28.50** P5p 45p

(Complete with FREE TEAK CABINET)

SLIM DESIGN WITH SILVER TRIM

Overall chassis size 14 1/2" x 6" x 2" high

### REPLACEMENT CHASSIS

5P25/3	£10.25	H70	£14.50
MP60	£9.95	MP610	£12.95
AP76	£17.95	GL75	£28.50
PLINTH COVERS (State Model)			
5P25 MP60 610	£3.30	(Post 40p)	
AP76	£4.50	(Post 40p)	
CART PLINTH COVER (Post 70p)			
(HL) MP60 G800H/PC			£14.50
MP610/SCSMD TP02/PC			£19.95
AP76/M7565M/PC			£32.50
AP98/M7565M/PC			£39.95
(HL) AP76 G800H/PC			£28.25
(HL) 5P25 G800H/PC			£18.95
H70 G800/TPD1/PC			£24.50
(HL) 2025 9FAHCD/PC			£14.95
MP60 SCSMD/PC			£17.25
(HL) GL75 G800/PC			£41.95
(HL) GL75 G800/PC			£38.95

### ULTRASONIC TRANSDUCERS

Operate at 40K up to 100.000. Ideal remote switching and signalling. Complete with data and circuits.  
PRICE PER PAIR **£5.90** Post 10p

### LOW COST HI-FI SPEAKERS

E.M.I. Size 13 1/2" x 8 1/2" Large Ceramic Magnet.  
**TYPE 150** 6 watt, 3, 8 or 15 ohms **£2.20**, Post 22p.  
**TYPE 150TC** Twin cone version **£2.75**, Post 22p.  
**TYPE 450** 10 watt with twin tweeters and crossover, 3, 8 or 15 ohms. **£3.85**, Post 25p.  
**TYPE 350** 20 watt with tweeter and crossover, 8 and 15 ohms. **£7.70**, Post 28p.



**POLISHED CABINETS** 150 150TC 450 **£4.60**, Post 30p.  
ASSEMBLED IN POLISHED CABINETS (8 ohm)  
Series 6 (Assembled 150TC) per pair **£16.50** post 70p  
Series 8 (Assembled 450) per pair **£18.95** post 70p

### TEST EQUIPMENT

**JUST A SELECTION**

- SE2508 Pocket Pencil Signal Injector **£1.90**
- SE600 Pocket Pencil Signal Tracer **£1.50**
- THL33D Robust 2k Volt **£4.55** With case **£4.99**
- TE15 Grid Dip Meter 140 KHz - 280 mHz **£13.45**
- 500 30 K Volt Multimeter **£9.25** With leather case **£10.50**
- 200H 20K/Volt Multimeter **£4.20** With case **£4.95**
- AF105 50K Volt Multimeter **£8.50** With case **£9.50**
- U4341 AC, DC Multimeter with transistor tester **£10.50**
- TE20D RT Generator 120KHz 500MHz Carr 35p **£16.95**
- TE22D Audio Generator 20Hz - 200KHz Carr 35p **£17.50**
- C15 3 Pulse Scope 10Hz - 10mHz Carr 50p **£38.00**
- TE65 Valve Voltmeter 28 ranges Carr 40p **£17.50**

ALL NOMBEX MODELS IN STOCK



### NEW MW/LW TUNER TO BUILD ML-3

Uses Mullard Module  
Slow motion tuning  
Built in battery, Ferrite aerial Overall size 7" x 2 1/2" x 3 1/2"  
**TOTAL COST TO BUILD £4.85** Post 15p. All parts sold separately - Leaflet No. 6



### BUILD THIS VHF FM TUNER

5 TRANSISTORS 300 kc/s BAND-WIDTH PRINTED CIRCUIT HIGH FIDELITY REPRODUCTION MONO AND STEREO.  
A popular VHF FM Tuner for quality and reception of mono and stereo.  
There is no doubt about it - VHF FM gives the REAL sound. All parts sold separately - Free Leaflet No. 3 & 7.  
**TOTAL £6.97**, p.p. 20p. Decoder Kit **£5.97**.  
Tuning meter unit **£1.75**.  
Mains unit (optional) Model PS900 **£2.47**, Post 20p  
Mains unit for Tuner and Decoder PS1200 **£2.62**, Post 20p.



### "BANDSPREAD" PORTABLE TO BUILD

Printed circuit all transistor design using Mullard RF IF Module Medium and Long Wave Bands plus Medium Wave Bandspread for extra sensitivity. Also slow motion geared tuning, ribbon push-out output, fibre glass PVC covered cabinet, car aerial socket. Attractive appearance and performance. **TOTAL COST TO BUILD £7.98** p.p. 30p. (Battery 22p).  
All parts sold separately - Leaflet No. 2




### PA-DISCO-LIGHTING

UK's Largest Range Write phone or call in. Details and demonstrations on request.

- DJ50L 3 Channel sound to light unit 3Kw
- DJ40L 3 Channel Mic (built in) to light 3Kw
- DJ70S 70 watt Disco amp/mixer
- DISCOAMP 100 watt Disco amp/mixer
- DJ105S 30 watt Disco amp/mixer
- Anti-Fredtick Quality Mic
- DJ500 50 watt P.A. Amp
- DJ300 150 watt rms Group Valve Amp

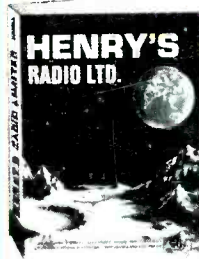● Portable Discos. Details on request  
● Credit terms for callers



### CATALOGUE

Fully detailed and illustrated covering every aspect of Electronics - plus data, circuits and information.

10,000 Stock lines at Special Low Prices and Fully Guaranteed.

PRICE **55p** Post Paid (40p FOR CALLERS)

PLUS! FIVE 10p VOUCHERS

Send to this address - Henry's Radio Ltd. (Dept. RC), 3 Albemarle Way, London EC1 - for catalogue by post only. All other mail and callers to '303' see above.

### SINGLAR PROJECT 60 MODULES

- SAVE POUNDS

Z30 £3.57 Z50 £4.37  
STEREO 60 £7.97 PZ5 £3.97  
PZ6 £6.37 PZ8 £4.77  
Transformer for PZ8 £2.95  
Active Filter Unit **£4.45**  
Stereo FM Tuner **£16.95**  
IC12 **£1.80** Q16's **£15** per Post etc. 20p per item



PACKAGE DEALS Post 25p  
2 x Z30 Stereo 60 PZ5 **£15.95**  
2 x Z30 Stereo 60 PZ6 **£18.00**  
2 x Z50 Stereo 60 PZ8 **£20.25**  
Transformer for PZ8 **£2.95**  
PROJECT 605 KIT **£19.95**

**7 SEC 6 XNIXE TUBES**  
(Post 15p per 150)  
XN13 GN40 9 Side view with data 85p  
GNP 7 GNP 8 0 9 Side view with decimal points and data 95p  
3015F 7 segment £2 each. £7 per 4 with data  
12 and 24 hour clock circuits for above. Ref. No. 31 15p

**MINIATURE AMPLIFIER**  
5 transistor 300mW o/p Fitted volume and sensitivity control 9 volt operated.  
**£1.75** each P/P 15p

**QUANTITY SLIDER CONTROLS**  
60mm slider, dials and ganged. Complete with knobs 5K, 10K, 25K, 100K, 250K, 500K 1 meg. Log and Lin. 45p each. 10K, 25K, 50K, 100K, 250K. Log and Lin. ganged 75p each.

### HIFI & TAPE EQUIPMENT

Acknowledged as UK's largest stockists with lowest prices plus 12 months guarantee. Write or call for FREE 16 page lists (Ref. 17)

TRANSISTORS - IC'S - RECTIFIERS - SCR'S - TRIACS etc. LATEST BROCHURE Ref. No. 36 on request

## MORE OF EVERYTHING AT LOW PRICES ALWAYS FROM HENRY'S

All the parts you need plus Data and Circuits - Get a Catalogue - it's all in there! Prices subject to change without notice. E 60 E

309-354-356-404-406 Open 6 days a week 9am - 6pm (303 closed Thurs.) All Stores open all day Saturday

**H MORE OF EVERYTHING AT THE RIGHT PRICE ALWAYS AT HENRY'S H**