



RADIO & ELECTRONICS CONSTRUCTOR

AUGUST 1975

30p

PART ONE
(IN TWO PARTS)

INTEGRATED CIRCUIT SIGNAL GENERATOR

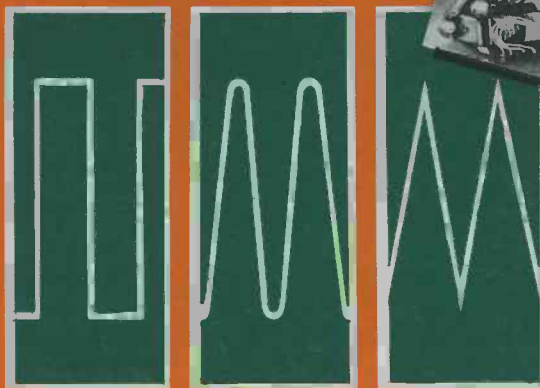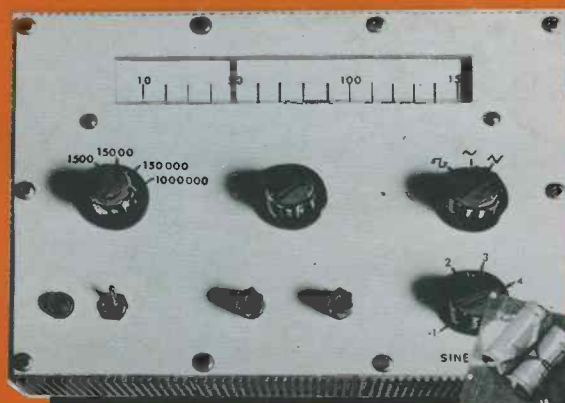

THIS CIRCUIT
OFFERS SQUARE WAVE,
SINE WAVE & TRIANGULAR
WAVE OUTPUTS FROM
1.0 Hz TO 1 MHz.

**ALSO
FEATURED**

IMPROVED COURTESY LIGHT FOR CARS
NEW MULTIPLE TUNING DIODES

www.americanradiohistory.com



Each £3 unit of Home Unit Insurance gives you protection up to the limit shown

This is the simplified insurance you have been waiting for. Not just cover on the contents of your home but a package of personal protection you and your family need. And it's how we save you so much money: just ONE policy to issue instead of nine! You can build up to the cover you need by additional units

(or $\frac{1}{2}$ units after the first) up to a maximum of five. So simple. So easy. Apply to your Broker, Agent or local office of a General Accident company. The Home Unit Policy can replace your existing insurances. And remember - as you buy more possessions just add more Home Units at any time. *Quote Ref. 20/9468*

THE GENERAL ACCIDENT FIRE & LIFE ASSURANCE CORPORATION LTD

Metropolitan House, 35 Victoria Avenue,
Southend-on-Sea, Essex, SS2 6BT

It pays to be protected by a **General Accident** company

Please send me further particulars of the Home Unit Insurance.

Name.....

Address.....

20/9468



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25, 3, 8 or 15 ohm	£8.64
Baker Group 35, 3, 8 or 15 ohm	£10.25
Baker Group 50/12, 8 or 15 ohm	£14.00
Baker Deluxe 12", 8 or 15 ohm	£13.75
Baker Major 3, 8 or 15 ohm	£11.87
Baker Superb 8 or 15 ohm	£18.12
Baker Regent 8 or 15 ohm	£10.00
Baker Auditorium 12"	£16.25
Celestion PST8 (for Unilux)	£3.75
Celestion G12H 8 or 15 ohm	£15.00
Celestion G12M 8 or 15 ohm	£12.00
Celestion G15C 8 or 15 ohm	£24.00
Celestion G18C 8 or 15 ohm	£33.00
Celestion MF1000 8 or 15 ohm	£10.95
EMI 13 x 8, 150 d/cone, 8 ohm	£2.94
EMI 13 x 8 type 350, 8 or 15 ohm	£9.56
EMI 13 x 8 20 watt bass	£7.69
EMI 5" 14A/730 mid-range 8 ohm	£3.50
EMI 6 1/2" 93850 4 or 8 ohm	£2.90
EMI 8 x 5, cer. mag. 8 ohm	£1.87
EMI 8 x 5, 10 watt, d/c roll/s 8 ohm	£3.44
EMI 10 x 6 93870 8 ohm	£2.69
EMI 2 1/2" tweeter 8 ohm	.77
Elac 9 x 5, 59RM109 15 ohm, 59RM114 8 ohm	£3.64
Elac 6 1/2" d/cone, roll surr. 8 ohm	£4.06
Elac 6 1/2" d/cone 8 ohm	£3.12
Elac TW4 4" tweeter	£1.75
Elac 10" 10RM239 d/c 8 ohm	£3.12
Elac 8" 3 ohm	£2.87
Eagle Crossover 3, 8 or 16 ohm	£1.75
Eagle CT5 cone tweeter 8 ohm	£2.06
Eagle CT10 tweeter 8 or 16 ohm	£3.00
Eagle DT33 dome tweeter 8 ohm	£6.31
Eagle FF5 3 way crossover	£3.62
Eagle SN75 crossover with tw. control	£4.69
Eagle FF28 multicell, horn	£9.00
Eagle HT15 horn tw. 16 ohm	£4.40
Eagle HT21 horn tw. 8 ohm	£6.81
Eagle MHT10 horn tw. 8 ohm	£4.44
Eagle FR4 4" full range	£6.12
Eagle FR65 6 1/2" full range	£9.62
Eagle FR8 8" full range	£12.31
Fane Pop 15 watt 12"	£5.25
Fane Pop 25T 30 watt 12"	£7.50
Fane Pop watt 12"	£12.00
Fane Pop 55 12" 60 watt	£12.95
Fane Pop 60 watt 15"	£13.75
Fane Pop 100 watt 18"	£25.95

SPEAKERS

Fane Crescendo 12A 8 or 15 ohm	£34.50
Fane Crescendo 12B 8 or 15 ohm	£36.50
Fane Crescendo 15, 8 or 15 ohm	£47.50
Fane Crescendo 18, 8 or 15 ohm	£62.95
Fane 910 horn	£14.95
Fane 920 horn	£33.95
Fane 152/12a 15" 15 ohm	£16.00
Fane 801T 8" d/cone roll surr.	£8.12
Fane 808T 8" d/cone	£3.44
Fane 807T 8" d/cone roll surr.	£4.62
Goodmans 8P 8 or 15 ohm	£5.50
Goodmans 10P 8 or 15 ohm	£5.80
Goodmans 12P 8 or 15 ohm	£13.95
Goodmans 12P-D 8 or 15 ohm	£16.95
Goodmans 12P-G 8 or 15 ohm	£15.95
Goodman 12AX 100 watt 8 or 15 ohm	£36.50
Goodmans 15AX 100 watt 8 or 15 ohm	£40.25
Goodmans 15P 8 or 15 ohm	£21.00
Goodmans 18P 8 or 15 ohm	£36.00
Goodmans Hifax 750	£16.00
Goodmans Axent 100 tweeter & crossover	£7.44
Goodmans Audiom 100, 8 or 15 ohm	£13.90
Goodmans Axiom 401, 8 or 15 ohm	£20.00
Goodmans Twinaxiom 8" 8 or 15 ohm	£10.14
Goodmans Twinaxiom 10" 8 or 15 ohm	£10.75
Gauss 12" full range 8 ohm	£69.50
Gauss 12" Bass 8 ohm	£69.50
Gauss 15" full range 8 ohm	£69.50
Gauss 15" Bass 8 ohm	£75.00
Gauss 18" full range 8 ohm	£80.00
Gauss 18" Bass 8 ohm	£80.00
All the above Gauss (American) speakers are fitted with 4 1/2" voice coils and can handle 200 watts RMS.	
Kef T27	£6.06
Kef T15	£6.94
Kef B110	£8.37
Kef B200	£9.50
Kef B139	£16.50
Kef DN8	£2.31
Kef DN12	£5.75
Kef DN13	£3.87
Richard Allan CGBT 8" d/c roll surr. 8 ohms	£7.37
STC 4001G super tweeter	£6.56
2 1/2" 64 ohm, 70mm 8 ohm, 70mm 80 ohm	.77
2 1/2" 75 ohm	.55
7" x 4" 3, 8 or 15 ohm	£1.63
8" x 5" 3, 8 or 15 ohm	£1.75
10" x 6" 6, 8 or 15 ohm	£2.69

SPEAKER KITS (Carr. 75p each. £1.50 pair)

Baker Major Module 3, 8 or 15 ohm	each	£13.44
Goodmans Mezzo Twinkit	pair	£47.19
Goodmans DIN 20 4 ohm	each	£13.44
Helme XLK25	pair	£25.44
Helme XLK30	pair	£17.19
Helme XLK50	pair	£46.25
Kefkit 1	pair	£48.44
Kefkit 3	each	£42.50
Peerless 3-15 (3 sp. system)	each	£17.19
Peerless 20/2	each	£17.44
Peerless 30/2	each	£24.38
Peerless 20/3	each	£26.56
Peerless 50/4	each	£40.50
Richard Allan Twinkit	each	£10.37
Richard Allan Triple 8	each	£15.94
Richard Allan Triple	each	£23.12
Richard Allan Super Triple	each	£27.50
Wharfedale Linton 2 kit	pair	£23.12
Wharfedale Glendale 3 kit	pair	£40.61
Wharfedale Dovedale 3 kit	pair	£63.12

PA/DISCO AMPLIFIERS (Carr. and ins. £1)

Baker Major 100 watt	£57.25
Linear 30/40	£30.00
Linear 40/60	£35.00
Linear 80/100	£58.95
Linear 100 watt slave	£75.00
Eagle PRO A120, 120 watts RMS	£129.00
Eagle PRO A65, 65 watts RMS	£98.50
Eagle PRO A35, 35 watts RMS	£77.00
Eagles TPA40 mains/12v mobile	£50.00
Eagle HHS 36 watts. mobile 12v.	£37.50
Eagle TPA20 paging amplifier	£45.00
Eagle RA859 Reverb (p. & p. 75p)	£18.25
Eagle RA856 Reverb (p. & p. 75p)	£12.50

MICROPHONES (p. & p. 50p)

Shure 515 SB Low Impedance	£17.31
Shure 515 SA High Impedance	£18.25
Shure 545 Dual Impedance	£34.69
Shure 588 SB Low Impedance	£23.12
Shure 588 SA High Impedance	£23.75

FREE with loudspeaker orders over £7 - "HiFi Loudspeaker Enclosures" book

All items guaranteed new and perfect

Prompt despatch

Carriage: 38p per speaker 12" and up 50p each, 25p per tweeter, crossover or 2 1/2"/70mm speaker kits 75p each (£1.50 pair)

Including VAT - 25% on Hi Fi and 8% on PRO and PA.

Send stamp for free booklet 'Choosing a speaker'

Big discounts on Grundig, ITT, Koyo, etc. Send stamp for list

WILMSLOW AUDIO

DEPT RC

LOUDSPEAKERS: SWAN WORKS
BANK SQUARE, WILMSLOW, CHESHIRE

AMPLIFIERS, RADIO ETC.
10 SWAN ST., WILMSLOW, CHESHIRE


The Ultimate Radio!

GRUNDIG SATELLIT 2000

You've got your yacht, private aircraft, Rolls Comiche? — then all you need for a full set of status symbols is this latest model Grundig Satellit. Germany's top radiol Radio performance, appearance and sound quality are all superb. VHF/FM, MW, LW 10 SW bands plus bandspread, 27 transistors and 22 diodes, Battery/Mains (110/240v.), 2 speakers, 57" telescopic aerial.

Our Price £149.95
inc. VAT, carr. & ins.

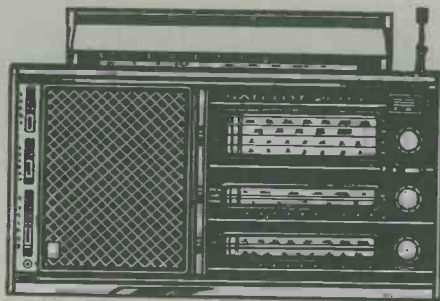Big discounts on Grundig, ITT, Koyo, etc. Send stamp for list.



WILMSLOW AUDIO, 10 SWAN STREET, WILMSLOW, CHESHIRE

COMPONENTS

HOBBYIST - PROFESSIONAL - DOMESTIC - SURPLUS - INDUSTRIAL
 JUST A FEW OF OUR BARGAINS ARE LISTED BELOW - SEND STAMPED
 ADDRESSED ENVELOPE FOR A QUOTE ON OTHER REQUIREMENTS.
 PAY US A VISIT. OVER 90% OF STOCK BELOW QUANTITY
 WHOLESALE PRICE. RETURN POSTAL SERVICE UNLESS CHEQUE.

Goods sent at customer's risk, unless sufficient payment for insurance included (2p per £1 Min 5p) U.K. only.

VALVE BASES	
Printed circuit B9A - B7G	2p
Chassis B7 - B9G - B7G	4p
Shrouded chassis B7G - B9A	6p
B8A - B9A chassis - B12A tube	6p

Speaker, 6" x 4", 5 ohm, ideal for car radio etc. £1

TAG STRIP - 6 way 3p	VHF Radio Tuner Head
9 way 5p Single 1p	Takes ECC 85

1 1/2 glass fuses - 250 m/a or 3 amp (box of 12)	18p
3" tape spools 8p	1 Terryclips chrome finish 4p
Brand new Boxed 6K7G 25p	Paameko 20H 12A potted choke 60p
PVC or metal clip on M.E.S. bulb holder	5p
Geared Knob, Inner to Outer Ratio 8:1	60p
Bulgin, 5mm Jack plug and switched socket (pair)	30p
12 volt solenoid and plunger	40p
250 RPM 50 c/s locked frequency miniature mains motor	50p
200 OHM coil, 2 1/4" long, hollow centre	10p
Belling Lee white plastic surface coax outlet Box	30p
R.S. 12 way standard plug and shell	30p

SWITCHES		
Pole	Way	Type
4	2	Sub. Min. Slide 18p
6	2	Slide 20p
4	2	Lever Slide 15p
2	2	Slide 10p
1	3	+ off Sub. min. edge 10p
1	3	13 amp small rotary 12p
2	2	Locking with 2 to 3 keys £1.50
2	1	2 Amp 250V A.C. rotary 24p
1	2	Toggle 10p
Wafer Rotary, all types 30p		
S.P.S.T. 10 amp 240v. white rocker switch with neon. 1" square flush panel fitting 30p		

PIANOKEY SWITCH UNIT	
5 lever, interlocking 2 pole mains + 3 pole 2 way	
+ 3 of 6 pole 2 way	15p

COMPUTER AND AUDIO BOARDS
 VARYING PANELS WITH ZENER, GOLD BOND, SILICON, GERMANIUM, LOW AND HIGH POWER TRANSISTORS AND DIODES, HI STAB RESISTORS, CAPACITORS, ELECTROLYTICS, TRIMPOTS, POT CORES, CHOKES ETC.
 3lb for 85p + 60p post and packing
 7lb for £1.75 + 80p post and packing

Skeleton Presets Slider, horizontal or vertical standard or submin. 5p	Clear Plastic Boxes For component storage or projects, sliding lid. 1 1/2" x 1" 10p
---	--

KNOBBS
 SILVER METAL PUSH ON WITH POINTER, OR WHITE PLASTIC, GRUB SCREW WITH POINTER AND SILVER CENTRE 8p EACH.
 1" DIAM. WITH 1 1/2" SKIRT SPUN ALUMINIUM GRUB SCREW FIXING, 1/2" 30p EACH.

ZM1162A INDICATOR TUBE
 0-9 Inline End View. Rectangular Envelope 170V 2.5M/A £2.00

RESETTABLE COUNTER
 English Numbering Machines LTD.
 MODEL 4436-159-989
 6-14 volt, 6 digit, illuminated, fully enclosed. £2.50
 Ferric Chloride, Anhydrous mil. spec. 1lb. bag 50p.

T03 or T066	
Mica Washer	2p
18 volt 4 amp charger, bridge rectifier	50p
GC10/4B	£3.00

Telescopic aerial
 Closed 9 1/2", open 38 1/2"
 Fitted right angle TV plug, 50p

1/8 1/4 1/2 watt	1p
1 watt	2p
Up to 5 watt wire	10p
10 watt wire wound	12p
15 watt	14p

RESISTORS	
Philips transformer, safety fused. In 200-220-240v. Out 240v 60ma + 6.3v 1a approx 2" x 2 1/2" x 2 1/2"	£1.50

POTS	
Log or Lin carbon	13p
Switched	25p
Dual Pots	38p
Dual & switch	50p
Lin wirewound	25p
Slider Pot	25p
Dual Slider	35p

THERMISTORS	
VA1008, VA1034, VA1039, VA1040, VA1055, VA1066, VA1082, VA1100	10p
VA1077, VA1005, VA1026	15p

RELAYS	
12 volt S.P.C.O. octal mercury wetted high speed	75p
P.O. 3000 type, 1,000 OHM coil, 4 pole c/o	60p
12 volt d.p.c.o. heavy duty octal	80p

Boxed GEC KT88 valve	£3
----------------------	----

JAP 4 gang miniature sealed tuning condensers 25p

ELECTROLYTICS MFD/VOLT. Many others in stock									
Up to 10V	25V	50V	75V	100V	250V	350V	500V	MFD	
10	4p	5p	6p	8p	8p	12p	16p	20p	
25	4p	5p	6p	8p	.8p	15p	18p	20p	
50	4p	5p	6p	9p	13p	18p	25p	—	
100	5p	6p	10p	12p	19p	20p	—	—	
250	9p	10p	11p	17p	28p	—	85p	£1	
500	10p	11p	17p	24p	45p	—	—	—	
1000	13p	17p	40p	75p	—	£1.50	—	—	
2000	23p	37p	45p	—	—	—	—	—	

As total number of values are too numerous to list, use this price guide to work out cost of your actual value requirements, i.e. 2MFD, 30V would be 5p, or 330MFD, 50V would be 14p, etc. etc.
 8/20, 10/20, 12/20 Tubular tantalum 15p each
 16-32/275, 32-32/275, 100-100/150, 100-100/275 50-50/300 20p each
 50/50-385 30p
 12,000/12, 32-32-50/300, 700/200, 100-100-100-150-150/320 50p each
 20-20-20/350 40p each

INDICATORS	
Bulgin D676 red, takes M.E.S. bulb	20p
12 volt red, small pushfit	20p
Mains neon, red, pushfit	20p

CAPACITOR GUIDE - maximum 500V
 Up to .01 ceramic 2p. Up to .01 poly 3p.
 Up to 1000PF silver mica 5p. 1,200PF up to .01 silver mica 10p. .013 up to .25 poly etc. 4p.
 .27 up to .68 poly etc. 6p
 Over 500 volt order from above guide and few others listed below.
 6p. .1/600: 10p. .01/1000, 1/350, 8/20, .1/900, .22/900, 4/16. .25/250 AC (600VDC) .1/1500 40p. 5/150, 9/275AC, 10/150, 15/150, 40/150.

TRIMMERS, 20p each
 100PF Ceramic, 30PF Beehive, 12PF PTFE 2500PF 750 volt, 33PF MIN. AIR SPACED 5PF, MIN. AIR SPACED, 50PF CERAMIC.

CONNECTOR STRIP
 Belling Lee L1469, 4 way polythene. 3p each

Strong grey plastic box same design as die cast ali 4 3/8" x 2 3/8" x 1 1/4" 40p

1" or 1 1/8" or 3/4" CAN CLIPS 2p

MAINS DROPPERS	
36 + 79 ohm	20p
66 + 66 + 158 ohm, 66 + 66 + 137 ohm	
17 + 14 + 6 ohm, 266 + 14 + 193 ohm	25p
50 + 40 + 1k5 ohm	
285 + 575 + 148 + 35 ohm	35p
25 + 35 + 97 + 59 + 30 ohm	

5 1/2" x 2 3/4" Speaker, ex-equipment 3 ohm	30p
2 Amp Suppression Choke	5p
3 x 2 1/2" x 1 1/2" PAXOLINE	2p
4 5/8" x 2 1/2" x 1 1/2" } 2 for 1p	
220K & 100 ohm 3 watt resistors	4p
VALVE RETAINER CLIP, adjustable	2p

OUTPUT TRANSFORMERS	
Sub-miniature Transistor Type	25p
Valve type, centre tapped or straight	40p

3 pin din to open end, 1 1/2yd twin screened lead 35p

Whiteley Stentorian 3 ohm constant impedance volume control way below trade at £1
 Drive Cord 1p per yd.

THE RADIO SHACK

161 ST. JOHNS HILL, BATTERSEA, LONDON S.W.11
 Open 9.30 a.m. till 8 p.m. Monday to Saturday Phone 01-223 5016
 also Sunday afternoons

SEMICONDUCTORS

Full spec. marked by Mullard, etc. Many other types in stock.

AC107 .. 14p	BC179B .. 14p	BF184/5 .. 15p
AC127/128/176 .. 11p	BC184C .. 10p	BF194/5/6/7 .. 8p
ACY28 .. 18p	BC186/7 .. 18p	BF194A/195C .. 12p
AD149 .. 40p	BC213L/214B .. 10p	BF200 .. 20p
AD161/2 matched pr. 69p	BC261 B .. 10p	BF258 .. 33p
AF116/7 .. 12p	BC327/8 .. 15p	BF262/3 .. 23p
AF124/6/7 .. 20p	BC337/8 .. 14p	BF336 .. 25p
AF139/178 .. 30p	BC547/558A .. 11p	BFS28 Dual Mosfet .. 92p
AF180/1 .. 30p	BC548 .. 11p	BFW10/11 F.E.T. .. 28p
AF239 .. 20p	BCX32/36 .. 12p	BFW30 .. £1.35
ASY27/73 .. 25p	BCY40 .. 60p	BFW57/58 .. 20p
BC107A or B .. 9p	BCY70/1/2 .. 9p	BFX12 .. 20p
BC107/8/9 .. 7p	BD112/3/5/6 .. 30p	BFX29/30/84/88 .. 16p
BC108A/B/109B/C .. 10p	BD131/2/3/5 .. 30p	BFY50/1/2 .. 12p
BC147/8/9 .. 7p	BD201/2/3/4 .. £1.00	BFY90 .. 50p
BC147A/B .. 8p	BD232/4/5 .. 47p	BR101 .. 30p
BC148A/B, 9B/C/S .. 8p	BDX77 .. £1.40	BR101 } Programmable Unj Junction
BC157/8/9 .. 9p	BF115 .. 12p	BR101 .. 34p
BC158A/B .. 11p	BF167/173 .. 15p	BR101 .. 34p
BC159B/C, 157A .. 11p	BF178/9 .. 25p	BSV64 .. 40p
BC178A/B .. 13p	BF180/1/2/3 .. 22p	BSV79/80 F.E.T.s .. £1
		BSV81 Mosfet .. 90p

BRIDGE RECTIFIERS

Amp	Volt	Part	Amp	Volt	Part
1	1.600	BYX10	2	30	LT120 type
1	140	OSH01-200	0.6	110	EC433
1.4	42	BY164	5	400	Texas

RECTIFIERS

Amp	Volt	Part	Amp	Volt	Part
IN4004	1	400	5p		
IN4005	1	600	6p		
IN4006	1	800	6p		
IN4007	1	1,000	6p		
BY103	1	1,500	15p		
SR100	1.5	100	7p		
SR400	1.5	400	8p		
REC53A	1.5	1,250	14p		
LT102	2	30	10p		
BYX38-600	2.5	600	40p		
BYX38-300R	2.5	300	36p		
BYX38-900	2.5	900	45p		
BYX38-1200	2.5	1,200	50p		
BYX49-600	2.5	600	34p		
BYX49-300	2.5	300	26p		
BYX49-900	2.5	900	40p		
BYX49-1200	2.5	1,200	52p		
BYX48-300	6	300	40p		
BYX48-600	6	600	50p		
BYX48-900	6	900	60p		
BYX48-1200	6	1,200	80p		
BYX72-150R	10	150	35p		
BYX72-300R	10	300	45p		
BYX72-500R	10	500	55p		
BYX42-300	10	300	30p		
BYX42-600	10	600	65p		
BYX42-900	10	900	80p		
BYX42-1200	10	1,200	95p		
BYX46-300*	15	300	£2.00		
BYX46-400*	15	400	£2.50		
BYX46-500*	15	500	£2.75		
BYX46-600*	15	600	£3.00		
BYX20-200	25	200	60p		
BYX52-300	40	300	£1.75		
BYX52-1200	40	1,200	£2.50		

***Avalanche type**

Amp	Volt	Part	Price
6	400	Plastic	74p
25	900	BTX94-900	£5.00
25	1200	BTX94-1200	£7.00
12-0-12 50M/A Min. Txfrmr. 90p			
Pair of LA2407 Ferroxc cores with adjuster .. 25p			
Chrome Car Radio facia .. 15p			
Rubber Car Radio gasket .. 5p			
DLI Pal Delayline .. 80p			
Relay socket .. 10p			
Take miniature 2PCO relay			
B7G or B9A valve can .. 2p			
0-30, or 0-15, black pvc, 360° dial, silver digits, self adhesive, 4 1/2" dia. .. 10p			

OPTO ELECTRONICS

ORP12	44p	Photo transistor	
BPX40	65p	BPX29	£1.00
BPX42	£1.50	OCF71	44p
BPY10	£1.00	BIG L.E.D. 0.2"	
(VOLT/AC)		2v 50m/A max.	
BPY68	} £1.00	RED	14p
BPY69		ORANGE	} 16p
BPY77		GREEN	
		YELLOW	
Diodes			

PHOTO SILICON CONTROLLED SWITCH BPX66 PNP 10 amp £1.00

3" red 7 segment L.E.D. 14 D.I.L. 0-9 + D.P. display 1.9v, 10m/a segment 73p

CQY11B L.E.D. Infra red transmitter £1 One fifth of trade

Wire ended glass neons 5p

Plastic, Transistor or Diode Holder 1p
Transistor or Diode Pad 1p
Holders or pads 50p per 100

Philips Iron Thermostat 15p
Bulgin 2-pin flat plug and socket 10p
McMurdo PP108 8 way edge plug 10p

TO3 HEAT SINK
Europlec HP1 TO3B individual 'curly' power transistor type. Ready drilled 20p

Tested unmarked, or marked ample lead ex new equipment

ACY17-20	8p	OC71/2	5p
ASZ20	8p	OC200-5	10p
ASZ21	15p	TIC44	24p
BC186	11p	2G240	2-50
BCY30-34	10p	2G302	6p
BCY70/1/2	8p	2G401	10p
BF115	10p	2N711	25p
BY127	8p	2N2926	7p
BZY88 series	5p	2N598/9	6p
HG1005	2p	2N1091	8p
HG5009	2p	2N1302	8p
HG5079	2p	2N1907	2-50
L78/9	2p	Germ. diode 1p	
M3	10p	GET120 (AC128 in 1" sq. heat sink)	
OA81	2p	GET872	20p
OA47	2p	2S3230	30p
OA200-2	3p		
OC23	20p		

BSX20/21	13p
BSY40	28p
BU105-01	93p
CV7042 (OC41 OC44, ASY63)	7p
GET111	40p
OC35	32 1/2p
ON222	30p
TIP30	52p
TIP3055	50p
TIS88A FET	33p
ZTX300	11p
2N393/MA393	30p
2N706	10p
2N929	14p
2N987	35p
2N1507/2219	18p
2N2401/2412/2483	25p
2N2904/5/6/7	13p
2N2907A	15p
2N3053	13p
2N3054/3055 (or equiv)	37p
2N3704	10p
2N3133	18p
2N3819 FET	16p
2N4037	35p
2N5036	60p
2SA141/2/360	31p
2SB135/6/457	20p
40250	60p

OTHER DIODES

IN916	6p
IN4148	1.5p
BA145/148	12p
Centercal	10p
BZY61	10p
BB103/110 Varicap	20p
BA182	24p
OA5/7/10	10p
BZY88 Up to 33 volt	6p
BZX61 11 volt	16p
BR100 Diac.	19p

INTEGRATED CIRCUITS

741 8 pin d.i.l. op. Amp	20p
TAD100 AMRF	£1.00
TAA570	£1.20
CA3001 R. F. Amp	£1.00
TAA300 1wt Amp	£1.25
NE555v Timer	42p
TAA550 Y or G	40p
TAA263 Amp	65p
7483	80p
7400/2/10/20/30	13p
7404	14p
ZN414 RX	88p
7414	60p
7438/74/86	27p
LM300, 2-20 volt	£1.50
74154	£1.50

THYRISTORS

Amp	Volt	Part	Price
1	240	BTX18-200	50p
1	400	BTX18-300	65p
1	240	BTX30-200	40p
6.5	500	BT102-500R	75p
10	700	BT106	90p
15	500	BT107	£1.00
6.5	500	BT101-500R	90p
6.5	500	BT109-500R	75p
20	600	BTW92-600RM	£3.00
15	800	BTX95-800R Pulse Modulated	£10.00
30	1000	28T10 (Less Nut)	£4.00

SOLDER

Multicore - 2 1/2p foot	
ENAM. COPPER WIRE	
SWG. PER YD.	
18	3p
20-24	2p
26-42	1p

GARRARD
GCS23T Crystal Stereo Cartridge £1.00

HANDLES

Rigid light blue nylon 6 1/2" with secret fitting screws	5p
14 D.I.L. socket, gold plated contacts, NOT cheap type	13p
Miniature Axial Lead Ferrite Choke formers	2p

DEE PLUG

McMurdo DA15P 15 way chassis plug	15p
Fairway 18009 Coax. socket	3p

TIE CLIPS

Nylon self locking 7" or 3 1/2"	2p
---------------------------------	----

CINCH 150

12 way edge socket	10p
1lb Mixed nuts, bolts, washers etc.	35p

SMALL ORDERS, ENCLOSE SUITABLE STAMPED ADDRESSED ENVELOPE
LARGE ORDERS, ADD SUFFICIENT FOR POSTAGE, INSURANCE, ETC.
TOTAL GOODS PLUS CARRIAGE. ADD V.A.T.

MAIL ORDER CUSTOMERS ONLY ADD 8% V.A.T.

ELECTROVALUE CATALOGUE 7



ISSUE 3

30p

including
25p Refund
Voucher

Up-dated
information
and prices.

The best yet!

112 pages (plus covers) and our best yet! Practically all items in catalogue 7 are there as the result of information fed by our computer, enabling us to control stock-buying in relation to demand with greater accuracy and real benefit to customers. This means that your orders, which we microfilm for record keeping, are handled with utmost speed and efficiency. EV prices remain keenly competitive and with our new 3-month period price-stabilization policy, you can order in confidence. In addition there are discounts as well, to give you further savings.

Send 30p now for EV Catalogue 7 Issue 3. It includes a refund voucher for 25p allowable on orders for £5 or more list value.

● PRICE STABILIZATION

Electrovalue prices are held for 3 month periods without change (except in cases of violent market fluctuation) and reviewed thereafter at the end of each one. This is instead of making day to day changes. Next price review is due Oct. 1. From Jan. 1 to July 1 EV prices were held without change.

● DISCOUNTS

Available on all items except for a few shown at NETT PRICE

5% on orders from £5 to £14.99 list.

10% on orders £15 and over.

● WE PAY POSTAGE

and packing in U.K. (except Baxandall speaker cabinets). For mail orders for £2 list value and under, there is an additional handling charge of 10p.

● GUARANTEE OF QUALITY

All items guaranteed fully to makers' specifications. Everything brand new—no "seconds", makers' rejects or clearance offers.

ELECTROVALUE LTD


Section 6/4 28 St. Judes Road, Englefield Green, Egham, Surrey
TW20 0HB Telephone Egham 3603 Telex 264475

All mail orders and communications to above address

- NORTHERN BRANCH
680 Burnage Lane, Manchester M19 1NA. Tel: 061-432-4945
Hours (both addresses) 9.00-5.30. Saturdays 9.00-1.00 p.m.

LATEST BOUND VOLUME No. 27

of
"Radio & Electronics
Constructor"

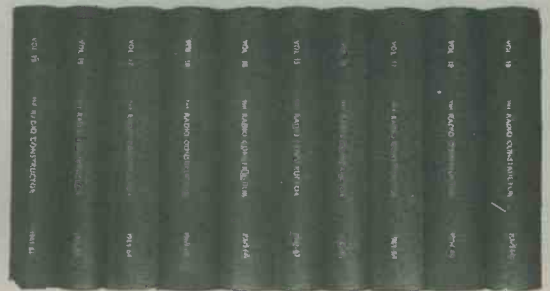

AUGUST 1973 to JULY 1974

Comprising
772 pages **PRICE £2.40 P&P 50p**
inc. index

BOUND VOLUME No. 25
(August 1971 to July 1972)

BOUND VOLUME No. 26
(August 1972 to July 1973)

PRICES

VOL. 25

£2.00 per volume. P&P 50p

VOL. 26

£2.10 per volume. P&P 50p

Limited number of these
volumes still available.

We regret all earlier volumes are now
completely sold out.

Available only from

DATA PUBLICATIONS LTD.,
57 MAIDA VALE, LONDON, W9 1SN

BI-PRE-PAK

Bargains in Semi-Conductors, components, modules & equipment.

Bargains from our FREE Catalogue

20 large pages, filled with real bargains in transistors, I.C.s, components, equipment, etc. Send large S.A.E. with 7p stamp for your FREE copy of 6th Edition by return. Meanwhile, for prompt delivery order from this month's ad. NOW.

TRANSISTOR PACKS ALL 50p each TESTED AND GUARANTEED

B79	4	IN4007 Sil. Rec. diodes. 1,000PIV 1 amp. plastic	H39	6	Integrated circuits 4 gates BMC 962. 2 flip flops BMC 945
B81	10	Reed Switches. 1" long 1/2" dia. High-speed P.O. type	H41	2	BD131/BD132 Complementary Plastic Transistors
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Un-marked	H65	4	40361 Type NPN Sil. Transistors TO-5 can comp. to H66
H38	30	Short lead Transistors, NPN Silicon Planar types	H66	4	40362. Type PNP Sil. Transistors TO-5 can comp. to H65

UNMARKED & UNTESTED

B1	50	Germanium Transistors PNP, AF and RF	H20	20	BY126/7 Type Silicon Rectifiers 1 amp. plastic. Mixed volts
B66	150	Germanium Diodes Min. glass type	H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	H67	10	3819N Channel FET's plastic case type
B86	100	Di. Diodes sub. min. IN514 and IN516 types			

SILICON POWER TRANSISTORS—

40 WATT ●	Gain	VCE	PLASTIC	Price
Type 40N1	15	15	NPN	20p
40N2	40	40	NPN	30p
40P1	15	15	PNP	20p
40P2	40	40	PNP	30p
90 WATT ●				
90N1	15	15	NPN	25p
90N2	40	40	NPN	35p
90P1	15	15	PNP	25p
90P2	40	40	PNP	35p

NEW X-HATCH GENERATOR Mk. 2



Essential for Colour T.V. alignment of 4 patterns. Featuring plug in IC's and a more sensitive sync. pick-up circuit. The case is virtually unbreakable—ideal for the engineer's toolbox—only measures 3" x 5 1/2" x 3". Operates from 3 U2 type batteries (extra).

P & P add 33p Complete kit **£7.93** Ready built unit only **£9.93**

OVER 1,000,000 TRANSISTORS IN STOCK!

CAPACITOR DISCHARGE IGNITION UNITS

Transistorised, Simple to Fit. Improves performance, cuts fuel costs
P & P add 27p **£7.50**

MNFRS. AM/FM CHASSIS

To clear. NO instructions or tuning drives, useful for experimenters. Not too difficult to get working. Make good portables
EACH £1

SUNDRY

Metrication Pocket Charts 12p. 8 assorted relays £1-00 (8%). Rev. counter device (for cars) £1-00. U.H.F./TV Tuner Units, 625 lines, Rotary Tuning £2-50. L.M.380 Audio I.C. £1-00 and technical books of all kinds.

TERMS OF BUSINESS

V.A.T. Prices shown do NOT include V.A.T. Please add 25% to total value of your order, except for items marked with a ●, or (8%) for which the V.A.T. rate is 8%. No V.A.T. on overseas orders.

POSTAGE Except where stated, add 22p for postage & packing in U.K. Overseas—add £1, any difference being charged or refunded.

PAYMENT Cash with order, Cheque or money order. Minimum value—£1. You can also pay by ACCESS.

IMPORTANT—Every effort is made to ensure accuracy of prices and description at time of preparing this advertisement and going to press. Prices are subject to alteration without notice.

BI-PRE-PAK LTD

Co Reg. No B20019

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SS0 9DF.

TELEPHONE: SOUTHEND (0702) 46344.


WRITE ORDER SEPARATELY AND ATTACH COUPON IF REQUIRED



Stirling Sound

challenging values!

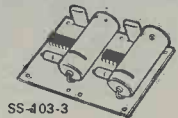STIRLING SOUND AUDIO MODULES come to you as basic units assembled on P.C.B.s enabling you to add required components in layouts of your own choice. Modules are tested and boxed before despatched and include well printed instructions.




SS-403-3

AMPLIFIER MODULES

Pre-amplifier: tone control


SS.100	Active tone control unit to provide bass, treble, balance and volume controls	£1.60
SS.101	Pre-amp for ceramic cartridge, tape and radio	£1.60
SS.102	Pre-amp for low output magnetic cartridge, tape and radio. With R.I.A.A. correction ...1dB at 1K	£2.25

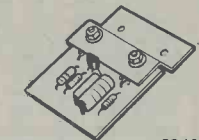

SS.105

POWER AMPLIFIERS


SS.103	Compact I.C. amp. with 3 watts R.M.S. output. Operating voltage 6 to 22. Size 3 1/2" x 2"	£1.75
SS.103-3	Stereo version of above using one I.C. on each channel	£3.25
SS.105 MK. 2.	A compact and useful all-purpose amplifier which will run excellently on a 12V supply. With 5 watt output, two make a good stereo amp. Size 2 1/2" x 1 1/2"	£2.25
SS.110 MK. 2.	Similar in size to SS.105 but with a 10 watt output. Ideal for many domestic and small-size P.A. applications. Operates from 26 to 32V.	£2.75
SS.140	Excellent designed 40 watt R.M.S. (into 4 ohms) hi-fi amplifier. S/N ratio better than 75dB. THD better than 0.2%. Power requirements—45V. d.c. With 0.15" centre edge connections. Two can be bridged to give 80 watts R.M.S. into 4 ohms	£3.60

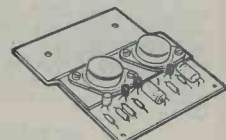

SS.140

THE MODULES TO BUILD A STEREO F.M. TUNER


SS.201	Ganged tuning condenser with accurately engineered slow-motion drive in rugged housing. Excellent sensitivity. Tunes 88-108MHz. With A.F.C. facility. Operates from 6V—16V	£6.25
SS.202	I.F. stage (with I.C.) Pre-tuned. A.F.C. connection. Operates from 4.5 to 14V.	£5.25
SS.203	Stereo Decoder. Designed essentially for use with SS.201 and 2, this module can also be used in most mono FM tuners. A LED type may be attached. Operating voltage 9-16V. d.c.	£5.62

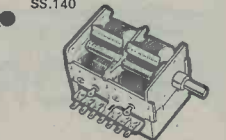

SS.201

POWER SUPPLY STABILIZER


SS.300	Add this to an unbalanced supply (say typically 45V. output) to obtain a steady powerful working output adjustable from 12 to 60V. Essential for your audio and special systems. Money saving and very reliable. Ideal for workbench use.	£3.25
--------	---	--------------

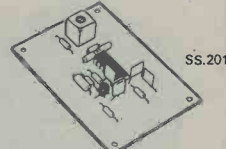

SS.202

MAINS TRANSFORMERS FOR ABOVE


Add 38p P. & P. per transformer	
Type A 18v/1A (Suit SS. 103)	£1.50
Type B 25v/2A (Suit SS. 110)	£2.00
Type C 30v/2A (Suit SS. 140)	£3.25
Bridge Rectifier Type A 27p	Type B/C 38p

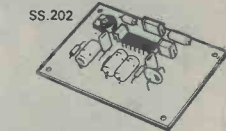

SS.203

STIRLING SOUND DISCO MINOR

Fully transportable. Console fitted twin turntables with cross fade, monitoring, L-R cueing, mic. with over ride. Ampower 40 loudspeaker has built-in mains powered 40 watt RMS power amp. Up to 10 Ampower may be added. With one Ampower and console **£100** plus V.A.T. at 25%. Carr. U.K. £3.50 (8%)

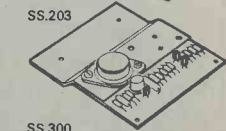

SS.300

To BI-PRE-PAK, 224-226 WEST RD., WESTCLIFF-ON-SEA, ESSEX

Please send

for which I enclose.....inc. V.A.T.

Name

Address

REC 8

PRECISION POLYCARBONATE CAPACITORS

ALL HIGH STABILITY - EXTREMELY LOW LEAKAGE

440V AC (+10%)	63V Range	+1%	+2%	+5%
0.1µF (1 x 10 ⁻¹)	0.47µF	56p	46p	36p
0.22µF (1 x 10 ⁻¹)	1.0µF	66p	56p	46p
0.25µF (1 x 10 ⁻¹)	2.2µF	80p	65p	55p
0.47µF (1 x 10 ⁻¹)	4.7µF	£1.30	£1.05	85p
0.5µF (1 x 10 ⁻¹)	6.8µF	£1.64	£1.29	£1.09
0.68µF (2 x 10 ⁻¹)	10.0µF	£2.00	£1.60	£1.40
1.0µF (2 x 10 ⁻¹)	15.0µF	£2.75	£2.15	£1.90
2.0µF (2 x 10 ⁻¹)	22.0µF	£3.50	£2.70	£2.55

TANTALUM BEAD CAPACITORS - Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 15V/25V or 35V; 10.0µF at 16V/20V or 25V; 22.0µF at 6V/10V or 16V; 33.0µF at 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V. ALL AT 10p EACH; 10 for 95p; 50 for £4.00.

TRANSISTORS:

BC107/8/9	9p	BC183/183L	11p	BF194	12p	BFY51	20p
BC114	12p	BC184/184L	12p	BF196	13p	BFY52	20p
BC147/8/9	10p	BC212/212L	14p	BF197	13p	OC71	12p
BC153/7/8	12p	BC547	12p	AF178	30p	2N3055	50p
BC182/182L	11p	BC558A	12p	BFY50	20p	2N3702/411p	

1N914 6p; 8 for 45p; 18 for 90p. 1N916 8p; 6 for 45p; 14 for 90p. IS44 5p; 11 for 59p; 24 for £1.00. IN4148 5p; 6 for 27p; 12 for 48p.

LOW PRICE ZENER DIODES: 400mW; Tol. +5% at 5mA. Values available: 3V; 3.6V; 4.7V; 5.1V; 5.6V; 6.2V; 6.8V; 7.5V; 8.2V; 9.1V; 10V; 11V; 12V; 13V; 13.5V; 15V; 16V; 18V; 20V; 22V; 24V; 27V; 30V. All at 7p each; 6 for 39p; 14 for 84p. SPECIAL: 100 Zeners for £5.50.

RESISTORS: High stability low noise carbon film 5%, 1/2 W at 40°C; 1/4 W at 70°C. E12 series only - from 2.2Ω to 2.2MΩ ALL AT 1p EACH; 8p for 10 of any one value; 70p for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2MΩ (730 resistors) £5.00.

SILICON PLASTIC RECTIFIERS - 1.5 Amp - Brand new wire ended D027: 100 P.I.V. - 7p (4/26p); 400 P.I.V. - 8p (4/30p).

BRIDGE RECTIFIERS: 2 1/2 Amp. 200V - 40p; 350V - 45p; 600V - 55p.

SUBMINIATURE VERTICAL PRESETS - 0.1W only: ALL AT 5p each; 50Ω, 100Ω, 220Ω, 470Ω, 680Ω 1K, 2.2K, 4.7K, 6.8K, 10K, 15K, 22K, 47K, 100K, 250K, 680K, 1M, 2.5M, & 5M.

PLEASE ADD 25% V.A.T. TO ORDERS. PLEASE ADD 15p POST AND PACKING ON ALL ORDERS BELOW £5.00.

Send S.A.E. for lists of additional ex-stock items. Wholesale price lists available to bona-fide companies. ALL EXPORT ORDERS ADD COST OF SEA/AIRMAIL.

MARCO TRADING

Dept. C6, The Old School, Edstaston, NR. WEM, Salop.
Tel: WHIXALL (Salop) 4645 (STD 094872) (Props: Minicost Trading Ltd.)

REVOR OPTICAL & TECHNICAL

12/13 HENRIETTA ST.,
LONDON W.C.2
Tel. 01-836 4536

**£6.00
POST
FREE**


4" dia. lens

FLEXIBLE MAGNIFIER

WITH CAST IRON BASE,
PRECISION GROUND AND
POLISHED LENS, CHROME PLATED
FRAME AND FLEXIBLE TUBE.
IDEAL FOR HOBBIES, AND
DETAILED WORK WHICH REQUIRES
BOTH HANDS FREE.

S.A.E. FOR CATALOGUE

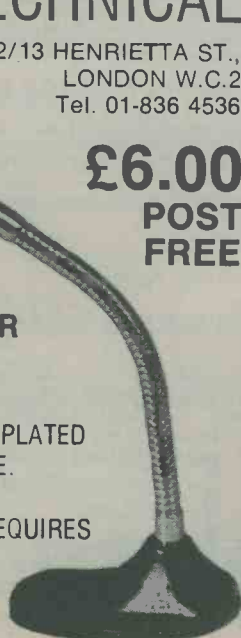(Subject to price ruling at the time of issue)



"I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner
than you would dream possible.

What a wonderful way to learn - and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio... a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy - making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

**No soldering - yet you
learn faster than you
ever dreamed possible.**

Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to read circuits - assemble components - build things - experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. AT NO EXTRA CHARGE! And this is a course anyone can afford. (You can even pay for it by easy instalments).

**So fast, so easy,
this personalised course
will teach you even if
you don't know a thing
today!**

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become a man who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the things and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire highpowered technical qualifications, because our famous courses go right up to City & Guilds levels.

**Send now for FREE
76 page book - see how
easy it is - read what
others say!**

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

**POST
TODAY FOR
FREE BOOK**

To: ALDERMASTON COLLEGE
DEPT. CRE 08, READING RG7 4PF

CRE 08

Also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London, EC2Y 5EJ Tel: 01-628 2721 Yes, I'd like to know more about your course. Please send me free details - plus your big, 76-page book that tells about all your courses.

NAME

ADDRESS

POSTCODE:




HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

New **BIGGER! BETTER!** **DORAM**

CATALOGUE 2nd Edition

SPECIFICALLY DESIGNED FOR THE AMATEUR
RADIO, ELECTRONICS AND HI-FI ENTHUSIAST.

- * MUCH, MUCH BIGGER RANGE OF QUALITY ELECTRONIC COMPONENTS AND AUDIO ACCESSORIES FROM TRUSTED BIG NAME MANUFACTURERS
- * THOUSANDS UPON THOUSANDS OF COMPONENTS – ILLUSTRATED, INDIVIDUALLY CODED AND PRICED. MANY NEW COMPONENTS ADDED FROM CUSTOMER REQUESTS
- * 16 EXTRA PAGE DATA SECTION
- * UNIQUE FREE UP-DATE PRODUCT INFORMATION SERVICE DURING LIFE SPAN OF CATALOGUE
- * ALL COMPONENT REQUIREMENTS SENT BY RETURN POST
- * POST AND PACKING FREE (only applies for Great Britain, N. Ireland plus B.F.P.O. Nos. – overseas orders F.O.B.)
- * NO-QUIBBLE REPLACEMENT PART SERVICE

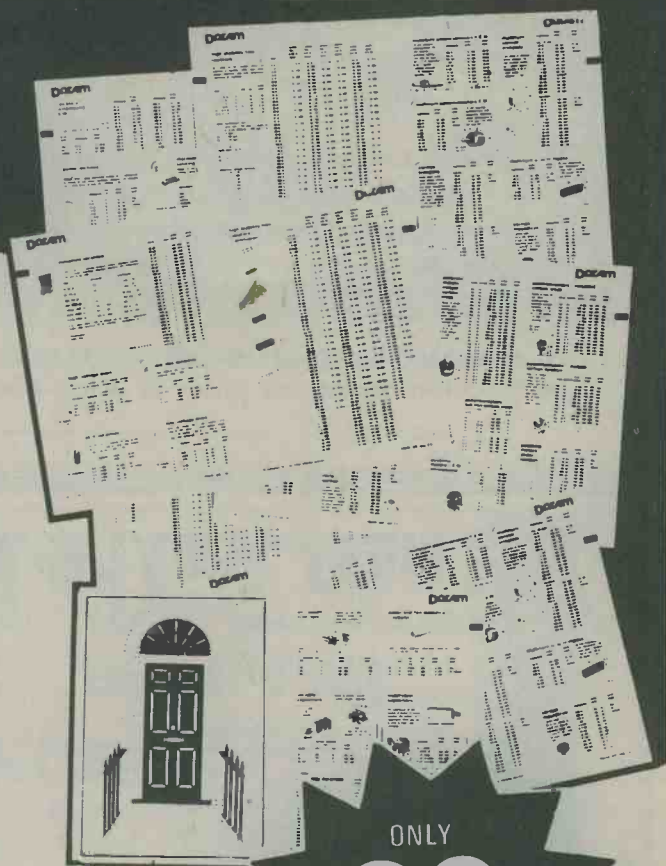

ONLY
60p
Inc. Post and Packing

All this and more ~ so don't delay


*send for
your new
catalogue
TODAY!*

The doorway to amateur electronics

DORAM

DORAM ELECTRONICS LIMITED
P. O. Box TR8
Leeds LS12 2UF

I enclose 60p. Please send me by return my new Doram Catalogue. (Overseas orders except for N. Ireland, please add 30p for post and packing surface only).

PLEASE PRINT BLOCK CAPITALS  REC

NAME _____

ADDRESS _____

Post Code _____

DENCO (CLACTON) LIMITED

355-7-9 OLD ROAD, CLACTON-ON-SEA, ESSEX

Our components are chosen by Technical Authors and Constructors throughout the World for their performance and reliability, every coil being inspected twice plus a final test and near spot-on alignment as a final check.

Our General Catalogue showing full product range	..	28p
DTB4 Transistor & Valve circuitry for D.P. Coils	..	28p
DTB9 Valve Type Coil Pack Application circuitry	..	28p
MD 1 Decoder Circuitry for Stereo Reception	..	28p

All post paid, but please enclose S.A.E. with all other requests in the interests of retaining lowest possible prices to actual consumers

NEW STYLE SELF-BINDER

for
"Radio & Electronics
Constructor"



The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

PRICE
£1.00

including V.A.T.


P. & P. 20p

Available only from:—

Data Publications Ltd. 57 Maida Vale London W9 1SN

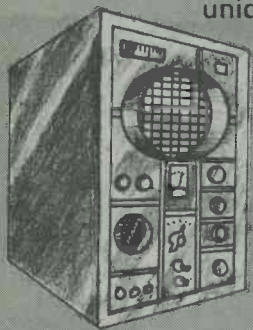1. Understand electronics.


Step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered using our unique Lerna-Kit course.



- (1) Build an oscilloscope.
- (2) Read, draw and understand circuit diagrams.
- (3) Carry out over 40 experiments on basic electronic circuits and see how they work.

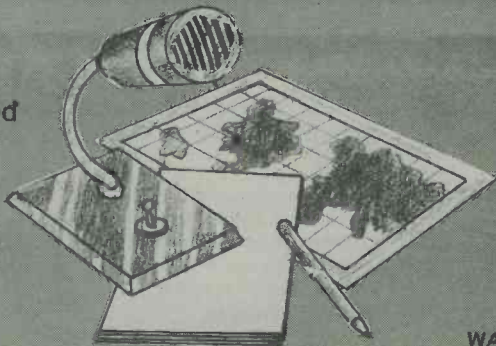2. Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.



WAA

Free!

Brochure, without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept AX 875
P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

Block caps please



CHINAGLIA

PROFESSIONAL QUALITY
TEST EQUIPMENT

THE MINOR

33 RANGES
20k Ω /V d.c.
4k Ω /V a.c.

WITH

- ROBUST CLASS 1.5 PRECISION MOVEMENT
- ACCURACY 2.5% D.C. AND 3.5% A.C.
- 12 MONTH GUARANTEE
- SELF-POWERED AND POCKET-SIZED
- OPTIONAL 30kV.D.C. PROBE

PRICE £19.00 Inc. VAT (P. & P. 80p)
PROBE £9.50

For details of this and the many other exciting instruments in the Chinaglia range, including multimeters, component measuring, automotive and electronic instruments please write or telephone:

CHINAGLIA
(U.K.) LTD. 19 Mulberry Walk, London
SW3 6DZ Tel: 01-352 1897

TRADE ENQUIRIES WELCOMED

DIRECT SUPPLY SERVICE TO READERS . . .

TOWERS INTERNATIONAL TRANSISTOR SELECTOR

This is dead!


If it takes you longer than 1 minute to find out all about these transistors then you need a copy of TOWER'S INTERNATIONAL TRANSISTOR SELECTOR. Its one of the most useful working books you will be offered this year. And probably the cheapest!

In it you will find a really international selection of 10,000 transistor types - British, Continental European, American and



Japanese. And we think that they will solve 90% of your transistor enquiries.

Would this replace it?

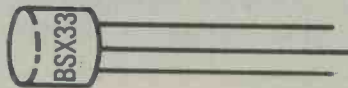

Current and widely used obsolete types were carefully selected and arranged in Numero-Alphabetical order by an author who was uniquely qualified to do the job. With his compendium, all you need to know is the type number

and you can learn all about a transistor's specification; who made it and where to contact them; or what to use to replace it.

Look at the entry for 2N909

TRANSISTOR NUMBER	PM OA LT	PACK-AGE	LEAD INFO	V _{CB} MAX	V _{CE} MAX	V _{EB} MAX	I _C MAX	T _J MAX	P TOT	F T MIN	C OB MAX	H FE	H FE BIAS	USE	MFR	EURO EQVT	USA EQVT	ISS
2N909	NS	TO18	LO1	60V	30V	5V	200MA	175C	500MW	50M	25P	110MN	50MA	AMG	SGI	BSX33	2N731	0

This is what you will learn from it

TYPE NO	POL & MAT	CASE OUTLINE	LEAD IDENTIFN	V _{CEO} MAX	V _{CE0} MAX	I _C MAX	T _J MAX	P _{TOT} MAX	F _T MIN	C _{OB} MAX	h _{FE} MIN	h _{FE} MAX	USE	SUPPLIER	UK SUB	USA SUB	ISS
(EXAMPLE) 2N909	NS	TO18	LO1	60V	30V	200 MA	175C	500 MW	50M	25P	110 MN	50 MA	AMG	SGI	BSX33	2N731	0

NUMERO ALPHABETIC LISTING

N - NPN
P - PNP
G - GERMANIUM
S - SILICON

REFER TO CASE OUTLINES APPENDIX C

REFER TO LEAD DETAILS - APPENDIX B

MAXIMUM PERMISSIBLE COLLECTOR - BASE VOLTAGE WITH EMITTER OPEN - CIRCUIT

MAXIMUM PERMISSIBLE COLLECTOR - EMITTER VOLTAGE WITH BASE OPEN - CIRCUIT

MAXIMUM PERMISSIBLE EMITTER - BASE VOLTAGE WITH COLLECTOR OPEN - CIRCUIT

MAXIMUM PERMISSIBLE COLLECTOR CURRENT

MAXIMUM PERMISSIBLE JUNCTION TEMPERATURE

MAXIMUM PERMISSIBLE DEVICE DISSIPATION - "F" - IN FREE AIR AT 25°C "C" - WITH CASE SURFACE HELD AT 25°C "M" - IN FREE AIR AT 25°C WITH METAL HEAT SINK ATTACHED TO DEVICE

MINIMUM FREQUENCY CUT OFF, F_c, INDICATED IN K - KILOHERTZ M - MEGAHERTZ G - GIGAHERTZ

F_c - FREQUENCY AT WHICH COMMON-EMITTER CURRENT GAIN DROPS TO UNITY. TYPICAL F_c CAN BE TAKEN AS ROUGHLY TWICE F_c MIN

FOOTNOTE

SUGGESTED EIA - JEDEC "2N" STANDARD POSSIBLE SUBSTITUTE

SUGGESTED PROELECTRON STANDARD POSSIBLE SUBSTITUTE

CODE INDICATION POSSIBLE SUPPLIER OF DEVICE - SEE SUPPLIER APPENDIX F

CODE INDICATION OF APPLICATION USAGE - SEE APPENDIX A

BIAS CURRENT AT WHICH CURRENT GAIN h_{FE} IS CHARACTERISED

CURRENT GAIN, NORMALLY D.C. (BUT SOMETIMES RELATED A.C. GAIN) AT I_C BIAS SPECIFIED - WHERE MIN ("MIN") ONLY IS SPECIFIED TYPICAL ("TYP") CAN BE TAKEN AS TWICE MIN AND VICEVERSA

MAXIMUM COLLECTOR CAPACITANCE (TYPICAL USUALLY 1/2 TO 1/3 MAX) - NORMALLY EMITTER OPEN - CIRCUIT AND INDICATED BY "P" PICOFARAD OR "N" - NANOFARAD - FOR HF DEVICES C_{in} IS GIVEN AND PICOFARADS THEN INDICATED BY "R" INSTEAD OF "P"

Tower's International Transistor Selector

by T. D. TOWERS
MBE, MA, BSc, C Eng, MIERE

£3.30
inc. post and packing

To:—DATA PUBLICATIONS LTD.
57 MAIDA VALE
LONDON W9 1SN

Please send me copy/copies
to the address shown below

NAME

ADDRESS

(Block capitals)

RADIO & ELECTRONICS CONSTRUCTOR

THE MODERN BOOK CO SOLID STATE HOBBY CIRCUITS

By RCA

Price £1.25

NEWNES RADIO ENGINEER'S POCKET BOOK
by H. W. Moorshead **PRICE £1.65**

ELECTRONICS AN ELEMENTARY INTRO. FOR BEGINNERS
by L. W. Owers **PRICE £1.65**

104 EASY PROJECTS FOR THE ELECTRONICS GADGETEER
by R. M. Brown **PRICE £1.40**

DIGITAL LOGIC BASIC THEORY & PRACTICE
by J. H. Smith **PRICE £1.85**

TRANSISTOR POCKET BOOK
by R. G. Hibberd **PRICE £3.00**

BEGINNER'S GUIDE TO TRANSISTORS
by J. A. Reddihough **PRICE £2.00**

RAPID SERVICING OF TRANSISTOR EQUIPMENT
by G. J. King **PRICE £2.10**

MAKING & REPAIRING TRANSISTOR RADIOS
by W. Oliver **PRICE £1.40**

PRINCIPLES OF TELEVISION RECEPTION
by W. Wharton **PRICE £1.85**

TRANSISTOR AUDIO & RADIO CIRCUITS
by Mullard **PRICE £2.05**

PRINCIPLES OF TRANSISTOR CIRCUITS
by S. W. Amos **PRICE £3.45**

HI-FI FOR THE ENTHUSIAST
by M. L. Gayford **PRICE £5.25**

HOW TO BUILD SPEAKER ENCLOSURES
by A. Badmaieff **PRICE £2.50**

TEST EQUIPMENT FOR THE RADIO AMATEUR
by H. L. Gibson **PRICE £2.10**

INTEGRATED CIRCUITS (IC's) TRANSISTOR GADGETS CONSTRUCTION HANDBOOK
by B. B. Babani **PRICE 70p**

PRACTICAL ELECTRONICS SCIENCE PROJECTS
by B. B. Babani **PRICE 85p**

COLOUR T.V. WITH PARTICULAR REFERENCE TO THE PAL SYSTEM
by G. N. Patchett **PRICE £5.15**

ELECTRONIC ORGAN SERVICING GUIDE
by R. G. Middleton **PRICE £2.80**

ALL PRICES INCLUDE POSTAGE

We have the Finest Selection of English and American Radio Books in the Country

19-21 PRAED STREET (Dept RC) LONDON W2 1NP

Telephone 01-723 4185

Don't miss your copy of

**HENRY'S
NEW 1975
CATALOGUE**

only
50p
Plus 20p
P&P



- ★ OVER 5,000 ITEMS – largest UK range of electronic components for home constructors.
- ★ 200 PAGES – every aspect of electronics and components for amateurs and hobbyists – kits, projects, test gear.
- ★ DOZENS of new lines and new ranges.
- ★ MANY price reductions throughout the new Catalogue.
- ★ A Discount Voucher with every copy, worth 50p.

ALL PRICES INCLUSIVE OF VAT

Write now for your copy, enclosing 70p remittance.

NOW OPEN: SUPERMARKET,
BROWSE ROUND THE NEW SUPER-
MARKET AT 404 EDGEWARE ROAD.

HENRY'S

Electronic Centres
404-406 Electronic Components & Equipment 01 402 8381
354 PA-Disco Lighting High power Sound 01 402-5854
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW

Hi Fi and
Electronics
Centres Open
9am - 6pm

Prices correct at time of preparation. Subject to change without notice. E 60 E

**ELECTRONIC FOOTBALL & TENNIS
WITH THE FABULOUS**

VIDEO SPORT
ON YOUR OWN TV

Play three exciting electronic ball games FOOTBALL, TENNIS, HOLE IN THE WALL on your own TV! Just plug Video Sports into the aerial socket of Your TV and away you go. Completely safe for you, your children and your TV. Mains operated.



**OUR INCREDIBLE PRICE
£29.50 INC VAT**

Demonstrations now in all CENTRES!

AM/FM MODULES
LP1179 LP1171

Combined AM/FM tuner modules, together with a small number of R C's Ferrite Aerial, made up a sensitive FM/HW/LW tuner, 6 Volts supply, supplied with data and circuit sheets.

LP1171 combined IF strip £4.60
LP1179 FM front end and AM gang £4.60.
£8.62 the pair.
Suitable Ferrite aerial 87p.



UHF TV TUNERS

625 line receiver UHF transistorised tuners U.K. operation. Brand new. (Postpacking 25p each)
TYPE A variable tuning slow motion drive £3.50.
TYPE B 4-button push button (adjustable) £4.60.
TYPE C variable tuning £2.90.
TYPE D 6-button UHF/VHF tuner £5.20.

**BUILD THE TEXAN
& FM TUNER**

TEXAN 20 + 20W STEREO AMP



Features glass fibre PC board, Gardners low field transformer, 6-1Cs, 10-transistors plus diodes, etc. Designed by Texas Instruments engineers for Henry's and P.W. 1972. Overall size with every kit.

15" 22" 6" in. Mains operated. Free teak sleeve with every kit.

£29.95 (carriage 50p) (also built and tested £39.95)

**HENELEC STEREO
FM TUNER**

Features capacity diode tuning, LED and tuning meter indicators, mains operated. High performance and sensitivity. Overall size in teak sleeve 8 22" 6 1/2 in. Complete kit with teak sleeve.

£26.25 (carriage 50p) (also built and tested £31.20)

JOIN THE LARGE BAND OF CONSTRUCTORS!

**SPECIAL OFFER
GARRARD CT4 STEREO CASSETTE
TRANSPORT MECHANISM**

Features:
★ Stereo Heads ★ Pause Control
★ Built in Motor Stabiliser ★ 12v DC Operation.
★ Auto Stop eject.

Robust, precision engineered mechanism based on the "STARR" patented design. Ideal for use in Car stereo cassette players, Hi-Fi stereo cassette recorders, industrial and many other applications. Suitable for the 'PW' Ascot Stereo Cassette Deck.



£13.50 incl. VAT P. & P. 35p

FREE

Send now for our free list No. 36 for our complete range of over 2,000 semiconductor devices at new low prices.





*I know ONE place
where Service
still means
something!*

Home Radio Components Ltd. of Mitcham are the people! I just don't know another firm that makes life so simple for their mail order customers.

First they devised a system whereby anybody who wanted to could have a credit account and pay monthly, thus saving the cost of several cheques or postal orders. Many credit account schemes are involved and awkward to join, but with Home Radio Components you simply have to complete a very simple form – not even references are called for. Then they send you a supply of order forms and pre-paid envelopes – another worthwhile saving. Then they really pamper you! They have installed an Answerphone system, so that you can phone orders through, any time of day or night – Sundays included! Very convenient – no wonder over 700 Credit Account customers use this service.

Of course, to order your components you first need the famous Home Radio Components Catalogue – just about the best catalogue of its kind you've ever seen. It costs 98p (65p plus 33p for post, packing and insurance). But Home Radio help you out even here – with the Catalogue they give you 14 vouchers each worth 5 pence when used against orders, so you can soon get the cost of the catalogue back, plus a bit towards postage! Just send the coupon below with your cheque or P.O. for 98p.

By the way, you'll find full details of the Credit Account system inside the catalogue, together with the necessary form. And here's your bonus – once you've joined the scheme you'll receive a new catalogue FREE each year. Yes – Home Radio Components still know the meaning of SERVICE. To prove it – send that coupon now.



65p. plus 33p POST AND PACKING

**Send off the coupon today.
It's your first step to solving
your component buying
problems.**

The price of 98p applies only to customers in the U.K. and to BFPO Addresses.

Please write your Name and Address in block capitals

NAME

ADDRESS

.....

.....

HOME RADIO (Components) LTD., Dept. RC
234-240 London Road, Mitcham, Surrey CR4 3HD

Regd. No.
912966, London



RADIO & ELECTRONICS CONSTRUCTOR

RADIO & ELECTRONICS CONSTRUCTOR

AUGUST 1975

Volume 29 No. 1

Published Monthly (1st of Month)
First Published 1947

Incorporating The Radio Amateur

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9 1SN

Telephone 01-286 6141 Telegrams
Databux, London

© Data Publications Ltd., 1975. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £4.00 (U.S.A. and Canada \$10.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers please pay by cheque or International Money Order.

Technical Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that such queries cannot be answered over the telephone; they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production.—Web Offset.

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London, W9 1SN

The Radio & Electronics Constructor is printed by Carlisle Web Offset.

CONTENTS

IMPROVED COURTESY LIGHT FOR CARS by J. Hart	14
THYRISTOR BISTABLE by J. R. Davies	16
NEWS AND COMMENT	18
F.M. SIGNAL BOOSTER by A. Sydenham	20
VOLTMETER WITH A MEMORY (Suggested Circuit 297) by G. A. French	23
CAN ANYONE HELP?	25
30 WATT TRANSMITTER – Part 2 by F. G. Rayer	26
TRADE NEWS	31
INTEGRATED CIRCUIT SIGNAL GENERATOR – Part 1 by John Lewis	32
LETTERS	39
SHORT WAVE NEWS – For Dx Listeners by Frank A. Baldwin	40
NEW MULTIPLE TUNING DIODES by J. B. Dance	42
ELECTRONIC SIREN by M. Harding	44
NEW EDUCATIONAL AID	46
QSL CARDS – How To Collect Them by Steve A. Money	47
BOOK REVIEW	49
IN YOUR WORKSHOP – Mains-Battery Supplies	50
RADIO TOPICS by Recorder	56
ELECTRONICS DATA No. 1 (For The Beginner – Series Resonance)	iii

SEPTEMBER ISSUE WILL BE
PUBLISHED ON 1st SEPTEMBER

IMPROVED COURTESY LIGHT FOR CARS

By J. Hart

An inexpensive unit which provides a delay facility found only in a few luxury models.

IN MOST CARS THE INTERIOR LIGHT IS CONNECTED TO switches fitted in the door pillars so that whilst a door is open the light is switched on, this being a convenience for anyone entering or leaving the vehicle. The simple circuits described in this article are designed to give a time delay between the closing of the car doors and the switching off of the interior light. The result is an improvement on the normal arrangement; for instance, when parked at night the delay is sufficient to allow the driver to put on his seat belt and to start the car before the light is automatically extinguished. It is also of benefit when leaving the car in an unlighted garage, the delay giving time for the driver to lock the car and to see his way out.

NEGATIVE EARTH

Fig. 1 shows a circuit suitable for cars having a 12 volt negative earth system with the door switches connected to earth. This arrangement is used in a wide range of popular cars, including the author's Hillman Imp in which the unit has been installed. A single component change will cater for positive earth systems.

The circuit operates in the following manner. When a door is opened the appropriate switch closes and extends the earth connection to the junction of resistors R1 and R2. Transistor TR1 is then forward biased by


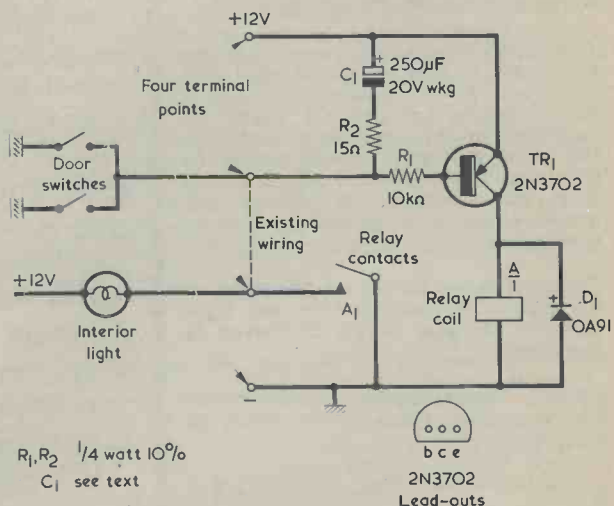


Fig. 1. The circuit of the delay unit as used with cars having a negative earth. The relay contacts are illustrated in the non-energised position. The existing wiring, which is now removed, is shown in broken line

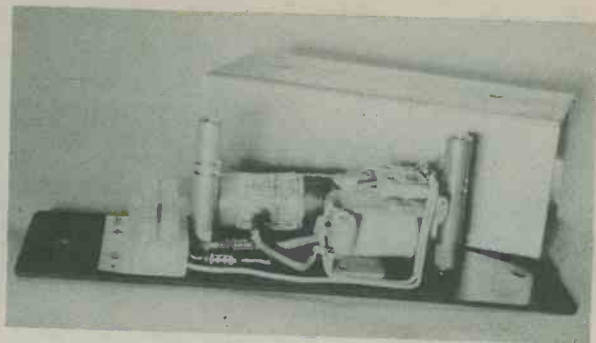Side view of the author's delay unit. Note the two internally threaded pillars and the folded aluminium cover



way of R1, its consequent collector current causes relay A/1 to energise, and the relay contacts A1 complete the earth circuit to the interior light which becomes illuminated. At the same time, capacitor C1 charges rapidly via R2.

When the door is closed the door switch contacts open. Capacitor C1 maintains a bias current for TR1, and relay A/1 remains energised. C1 then slowly discharges through R1 until the collector current of TR1 is insufficient to hold the relay energised. The breaking of the relay contacts causes the interior light to be extinguished and the circuit is back to its normal state.

With the values shown a delay of some 12 seconds was obtained, and this has proved to be quite adequate. The length of the delay may, however, vary from this figure in individual circuits according to the gain of the particular transistor used for TR1 and the release current value of the relay. The timing period may be altered by varying the value of C1 and constructors can, if they wish, determine in practice the capacitance required in this component for a particular time delay before installing the unit permanently.

The low value resistor R2 is included to limit the initial charging current when the door switch closes, whilst diode D1 prevents TR1 from being damaged by any high back e.m.f. which may appear across the relay coil when the relay de-energises. It is important that D1 be connected into circuit correct way round or excessive current may flow through it and the transistor.

RELAY

The construction will depend on the relay used. This is not a critical component; it should have a coil resistance of at least 200Ω and be capable of energising at some 10 volts or less. It requires a set of normally open contacts which should be capable of controlling the current for the interior light. In the author's case this was a 6 volt festoon lamp and so the relay contacts needed to be suitable for a switched current of 0.5 amp. A wide range of relays are suitable here. The relay employed in the prototype unit was a small ex-Services surplus type.

The relay and other components were mounted on a solid s.r.b.p. ('Paxolin') base, together with a plastic screw terminal block for connection to the car electrical circuits. A terminal block is recommended here as this avoids the need for soldering in the car. Two 2 in.

internally threaded pillars were also fitted to the s.r.b.p. board and these enabled a simple folded aluminium cover to be screwed down to complete the unit and protect the components.

After examination of the car wiring diagram the unit was firmly mounted under the instrument fascia, where it was convenient to pick up the battery and earth supplies and to intercept the cable connecting to the interior light and the door switches. It is, of course, essential that a delay unit of this nature be fitted only by someone who has an accurate knowledge of the electrical system in the car concerned.

For cars having a 12 volt positive earth system it is only necessary to change TR1 for an n.p.n. type and to reverse the polarities of C1 and D1. The transistor may be a BC108 and the circuit is shown in Fig. 2. The same comments apply to the components here as in Fig. 1.


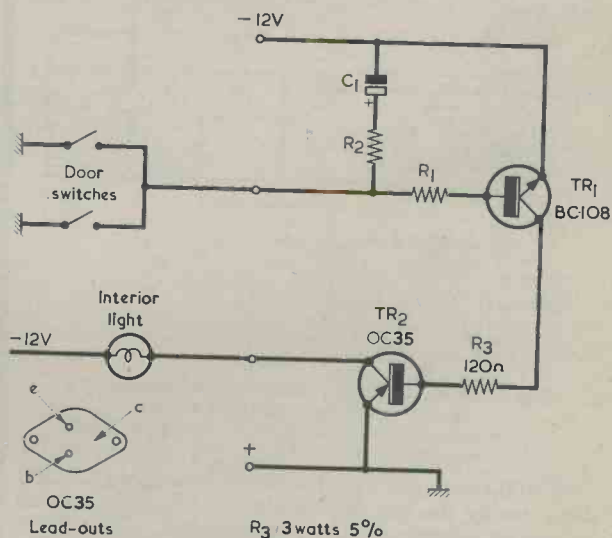


Fig. 2. The basic circuit of Fig. 1 may be employed in cars having a positive earth if TR1 is made an n.p.n. transistor and the polarities of C1 and D1 are reversed

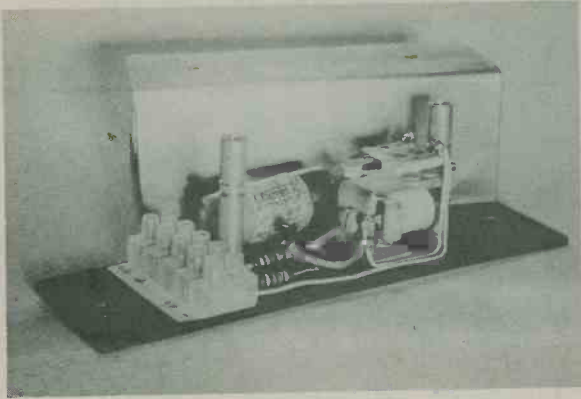

Another view of the unit showing, in particular, the type of terminal block employed. One of the terminals is unused and the remaining four correspond with those indicated in the circuit diagrams

Fig. 3 shows an all-electronic delay unit for cars having a positive earth, a power transistor being employed as an alternative to the relay. An OC35 can be used as a switch to handle the current drawn by the interior light, and its base is coupled to the collector of TR1 via the current limiting resistor, R3. With loads of the order of 6 watts, the OC35 does not need to be mounted on a heat sink.


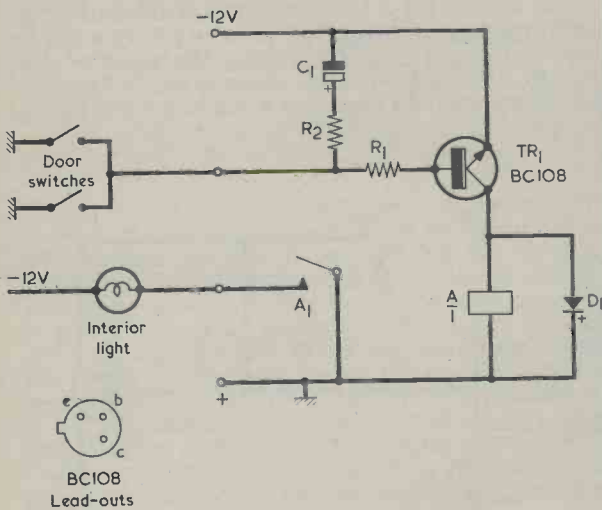


Fig. 3. An all-electronic delay unit incorporating a power transistor instead of a relay

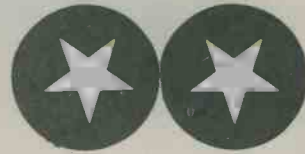With the circuit of Fig. 3, however, the light gradually dims during the last few seconds of the delay period before becoming finally extinguished. The more precise on-off action of a relay was preferred by the writer, and no failures with the unit whose circuit is shown in Fig. 1 have occurred since it was installed a year ago.



THYRISTOR BISTABLE

By J. R. Davies

A look at an infrequently encountered circuit

A SEMICONDUCTOR DEVICE WHICH HAS NOT, PERHAPS, received as much attention as is its due is the thyristor, or silicon controlled rectifier. As readers will be aware, a thyristor is a switching device which may be inserted in series with a load coupled to a source of direct current. If a small current is momentarily passed through the thyristor gate to its cathode the device becomes conductive and switches on the load. Provided that the load current is above its holding level the thyristor then remains conductive, and can only be turned off again by reducing the load current below the holding level. The polarity of the load current must be such that conventional current (from positive to negative) flows in at the anode and out at the cathode of the thyristor.

The gate current has to be applied continually if the load is powered by an alternating voltage, since the thyristor otherwise turns off on the half-cycles which take the anode negative of the cathode.

The thyristor has the advantages that it can pass relatively high currents and that, for direct voltage applications, it can be turned on by a momentary gate current only. When conductive, there is a voltage drop of the order of 1 volt across the anode and cathode of the device.

BISTABLE CIRCUIT

Two thyristors can be employed in a bistable circuit, as shown in Fig. 1. The thyristors used here are type CRS1/05 which, although encapsulated in a small TO5 can, can pass average currents up to 1 amp, and non-repetitive surge currents up to 15 amps.

RADIO & ELECTRONICS CONSTRUCTOR

When, in Fig. 1, the 9 volt supply is initially applied, both thyristors are non-conductive. If, now, S1 is pressed, a gate current flows to TH1 via R1, and this thyristor turns on. The anode of TH1 goes rapidly negative, and a holding current flows through R2. Capacitor C1 charges via TH1 and R3 with its right-hand plate positive. Further closure of S1 has no effect on thyristor operation and the circuit is in one of its two stable states.

If, on the other hand, S2 is pressed, a gate current flows into TH2 and this thyristor turns on. Its anode goes negative, taking the anode of TH1 negative also by way of the charged capacitor, C1. In consequence, TH1 turns off, and C1 charges up via R2 and TH2 with its left-hand plate positive. The circuit is now in the second of its two stable states. It may be brought back to the first state by pressing S1, whereupon TH1 turns on and TH2 is turned off by the consequent negative excursion of its anode due to C1.

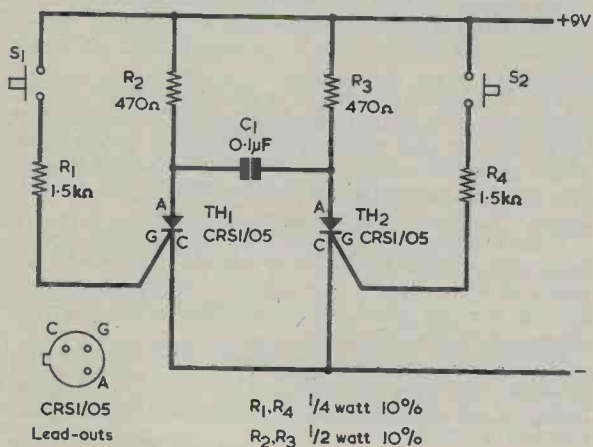


Fig. 1. The thyristor bistable. Turning on TH1 causes TH2 to turn off, and vice versa

Thus, a momentary closure of S1 causes TH1 to turn on and stay on, whilst a momentary closure of S2 causes TH2 to turn on and stay on. Apart from the instants of changeover only one thyristor is conductive at any time.

CAPACITOR VALUE

The value required for C1 depends on the anode loads (R2 and R3 in Fig. 1), supply voltage and the turn-off time of the thyristors, and is best determined empirically. With the thyristor types and component values shown in Fig. 1, it was found that the thyristors could not turn each other off when C1 had a value of 0.01µF, but that they did so reliably when C1 was made 0.02µF. The higher value of 0.1µF shown in the diagram is therefore comfortably above the minimum capacitance required.

A disadvantage with the circuit of Fig. 1 is that both thyristors are off when the 9 volt supply is initially applied, and that it is necessary to press one of the two switches to bring the circuit to one of its two operating states. The modification shown in Fig. 2 ensures that TH1 is always turned on at switch-on. In Fig. 2, R1

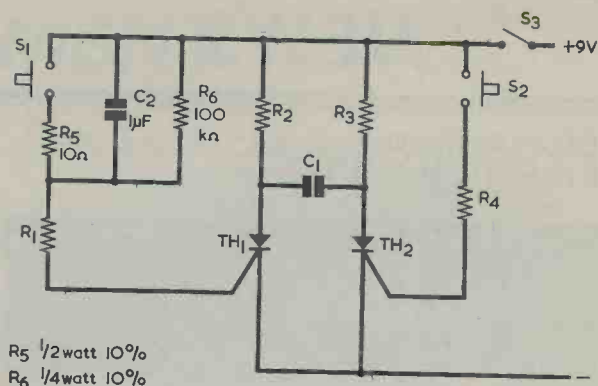


Fig. 2. A circuit modification which ensures that TH1 is always turned on when on-off switch S3 is closed

to R4, TH1, TH2, S1, S2 and C1 are the same as in Fig. 1, whilst R5, R6, S3 and C2 are added components. C2 is a plastic foil capacitor. When on-off switch S3 is closed a charging current for C2 flows through R1 to the gate of TH1. The current is sufficient to turn on this thyristor and the circuit then reverts to its previous mode of operation with TH2 turning on when S2 is closed and TH1 turning on when S1 is closed. Resistor R5 is included to limit surge current at S1 contacts when this switch is subsequently closed since it then discharges C2. When S3 is turned off, C2 discharges into R6 and is then ready to turn on TH1 when the circuit is next switched on. It is necessary for S3 to be a toggle switch which applies the supply abruptly when it closes. TH1 will not turn on automatically if switch-on is more gradual, as would occur if the 9 volt supply were provided by a mains power unit with the on-off switch at the mains input.

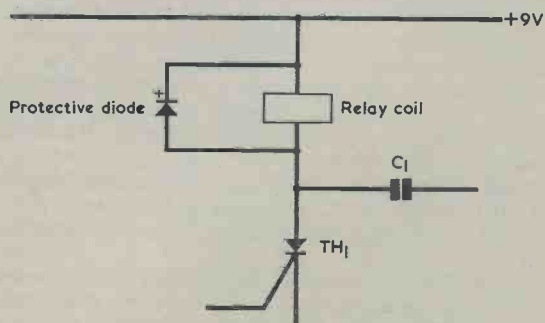


Fig. 3. If a relay coil is used as a load, a protective diode must be connected across it. Here, the relay coil replaces R2

Alternative loads can, of course, be employed in place of R2 or R3, with a possible consequent alteration in the value of C1. If a relay coil forms a load, a protective diode should be connected across it as in Fig. 3 to prevent the formation of a high back e.m.f. when the associated thyristor turns off. The diode can be a small silicon rectifier such as the 1N4002. ■

NEWS . . . AND . . .

DIGITAL RADIO DIRECTION FINDER



The new Heathkit MR-1010 Digital Radio Direction Finder, brings marine navigation into the digital age. What you see, is what you hear in the new revolutionary MR-1010. Just tune the dial to the stations you want on either of two switch-selected bands (AM broadcast and LW beacon).

Frequencies are read out directly in big bright digits on the Beckman planer gas discharge tubes on the front panel – with resolution down to 1 kHz and accuracy within ± 2 kHz. If the station is broadcasting, that's what you'll hear. No more fumbling with hard-to-reach dials at night or during a storm searching for elusive, hard-to-identify beacon stations. And the digital readout automatically dims at night for added convenience and safety.

While designed as a precision navigational aid, the MR-1010 serves double duty as a AM radio entertainment centre with impressive performance specifications.

The MR-1010 is designed to be used with a boat's 12 VDC electrical system – or it becomes completely portable with its own built-in power source consisting of 6 1.5V flashlight batteries (not included with kit). To prolong battery life, the digital readout display automatically shuts off after approximately 20 seconds – but can be recalled instantly at the touch of a front panel switch.

Kit K/MR-1010 £124.00 including 8% VAT and delivery within the United Kingdom.

FREE Catalogue with full details of the MR-1010 and the complete range of Heathkit kits, available from: Heath (Gloucester) Ltd., Bristol Road, Gloucester. GL2 6EE.

GREENWICH MEAN TIME

Throughout the world, local time is measured by how many hours it is before, or after, GMT. Why GMT?

The answer, explained an item on BBC World Service, lies with the Royal Observatory, which recently celebrated its 300th anniversary.

In 1675 there was no way of finding longitude at sea, nor of measuring currents. The consequences were shipwreck, death and destruction of valuable cargoes. King Charles II, who was expanding his navy, said: "I must have the stars anew observed and corrected for the use of my seamen"

So he appointed John Flamsteed to become the first astronomer Royal, and commissioned Christopher Wren – the greatest architect of his age – to build an Observatory on top of a hill at Greenwich.

The building still stands though Greenwich, then a riverside village, is now a pleasant part of inner London.

The first need was for a precise knowledge of the fixed stars. The second was to observe the movements of the moon and planets, and produce tables from which mariners could calculate their position at sea. The third was to make an accurate shipborne chronometer.

It took more than 40 years to produce the first British catalogue of stars from the thousands of observations taken by Flamsteed. It was this work which established him as the first great systematic astronomer since the invention of the telescope.

In 1766, the Royal Observatory published its first Nautical Almanac, and each year since it has provided tables of all astronomical information for navigators and astronomers.

All this data had to relate to a standard meridian and time, and in 1884, by international agreement, the Greenwich Meridian was adopted as the world's prime meridian, and the basis for the international time zone system – hence GMT.

Though the Wren building no longer houses the Royal Observatory – it moved to Herstmonceux Castle, Sussex, in 1948 – there is still much to see in Greenwich in 1975.

A special tercentenary exhibition at the National Maritime Museum throughout 1975 contains a magnificent array of ancient and modern maps, models, portraits, manuscripts and instruments to enable the visitor to follow the history of the oldest scientific institution in Britain.

● A radio programme about the Greenwich Observatory can be heard on BBC World Service on Saturday, August 9 at 0030 GMT; Sunday, August 10 at 1709 GMT and Tuesday, August 12 at 1130 GMT.

COMMENT

ELECTRONICS DATA

The Constructor's Data Sheets which appeared on our inside back cover reached maturity at No. 100 in our last issue. Starting in January 1968, they have covered the most important electronic information which can be satisfactorily presented in tabular form, and they now go into a well earned retirement.

Commencing with this issue, they are followed by a new series, 'Electronics Data', which will deal each month with a specific aspect of electronics. Starting with a series for the beginner each will feature a pictorial display combined with a brief and concise text.

LOW-DEFINITION A/TV ASSOCIATION INAUGURATED

Tape recording, stereo, the semiconductor revolution and the extension of its technology into opto-electronics, integrated circuits and improvements in flexible lightguides etc., has led a number of enthusiasts to consider using such aids to provide a modernised version of the original Baird TV system of 40 years ago.

In the Spring a LDTV Convention was held at the Nottingham College of Education, discussions resulted in the inauguration of a formal association.

F. C. Ward, G2CVV, Secretary of the Derby & District Amateur Radio Society accepted an invitation to become the association's first President.

A prime mover in the formation of the association was D. B. Pitt of 1 Burnwood Drive, Wollaton, Nottingham, from whom details may be obtained.

IN BRIEF

■ Henry's Radio Ltd., had to twice postpone the printing of their 1975 catalogue due to the V.A.T. changes in the Spring Budget. As soon as they received clarification of the changes to the rates for their components, the necessary alterations to the catalogue were made and the printers instructed to proceed.

Henry's Radio wish to apologise to those of our readers who may have been inconvenienced by the delays.

■ A Radio Amateur Course is to be held at the North East Essex Technical College, Sheepen Road, Colchester, Essex. For further information contact D. Mason of the Electrical Engineering Department at the College.

■ Coupled with the little publicised dissolution on 31st March, 1975, of the Permanent Magnet Association which has served both makers and users of Magnets so well over the past 30 years, has been the establishment of a Permanent Magnet Centre at Sunderland Polytechnic, Chester Road, Sunderland.

Details from Mr. W. Wright, or Dr. A. G. Clegg, at the Polytechnic.

SPECIAL PRE-PUBLICATION OFFER

We would draw readers' attention to the Special Pre-Publication Offer which appears on the outside back cover of this issue.

We have been able to arrange for our readers to obtain copies of *Linear I.C. Circuit Applications* by G. Clayton, published by MacMillan, at a special pre-publication price which will give a substantial discount over the full selling price.

Full details appear in the advertisement.

NEW AGFA CASSETTE ALBUM



This new album contains all the advantages of the old, but with the following improved features:-

Colour—each album contains 1 of each, C60 red, C60 lilac and C60 yellow, plus 1 of each C90 red, C90 lilac and C90 yellow AND corresponding, coloured index reference cards.

Presentation—each "Color Album" is attractively wrapped in an individual polythene bag complete with carrying handle and a colourful descriptive photograph on the back of the package.

Recommended retail price is £6.65 (incl. V.A.T.).



F.M. SIGNAL BOOSTER

By A. Sydenham

A Band II aerial pre-amplifier which was primarily designed to improve f.m. stereo reception.

THE PRE-AMPLIFIER TO BE DESCRIBED WAS BUILT FOR use with a commercially manufactured f.m. stereo tuner-amplifier, but it could without doubt be employed equally well with any other f.m. receiver or tuner, whether intended for stereo or for mono reproduction.

As is well-known, good hiss-free stereo reception requires a stronger aerial signal than that needed for adequate mono reception. Because of this, stereo reception in fringe areas may cause dissatisfaction even when a good multi-element beam aerial is being employed. Under these conditions the use of a pre-amplifier with a high gain level is worth consideration. It must be noted, however, that a pre-amplifier should never be used in an attempt to make up the losses incurred with a poor aerial system. It should, instead, be looked upon as a possible addition to a good aerial installation when all else fails.

CASCADE CIRCUIT

Of various pre-amplifiers tried by the writer, the one whose circuit is depicted in Fig. 1 has performed best. As may be seen, it employs two field-effect transistors in a cascode configuration, the first f.e.t. working as a grounded source amplifier and the second in a grounded gate stage. Both the input and the output of the pre-amplifier are at 75Ω impedance. Construction tends to fall into the subminiature category and it is essential to have a really small soldering iron with a pencil bit.

In the author's case the pre-amplifier obtains its power from the tuner-amplifier with which it is

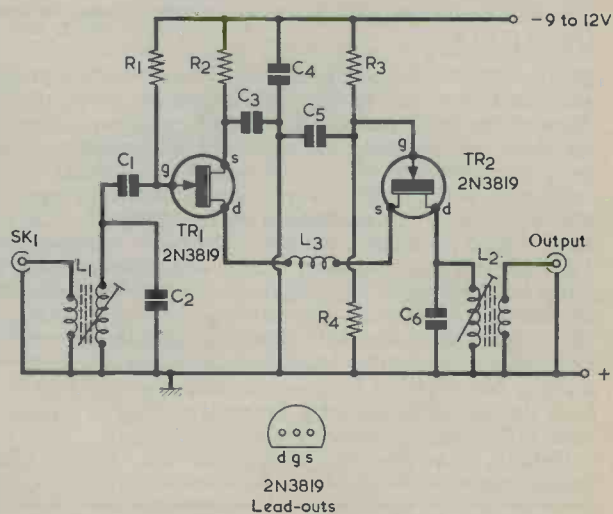


Fig. 1. The circuit of the f.m. signal booster. The aerial connects to SK1 and the booster output is then fed to the aerial input socket of the f.m. tuner or receiver


employed. The tuner-amplifier supply is negative of chassis, and it is for this reason that the pre-amplifier has a positive chassis connection. The pre-amplifier can, of course, alternatively be powered by a small mains power unit or a battery. The current consumption is of the order of 2 to 3mA only.

CONSTRUCTION

The parts are assembled on a piece of copper-clad board measuring 3 by 1½ in. Layout is as shown in Fig. 2, in which diagram the copper side of the board is towards the reader. There is ample space for two 6BA clear holes which can take screws for mounting the board, and these can be drilled at any convenient points.

The terminal point indicated as SK1 is the centre tag of a coaxial socket whose body is on the board side away from the reader. This socket is the largest item in the pre-amplifier! The resistors and wire-ended capacitors are all miniature types, and resistor and capacitor lead-outs are drastically pruned to produce a taut and almost lead-less assembly. The feed-through capacitors are fitted in suitably sized holes, and their skirts are soldered to the copper foil. The item marked 'SO1' is a miniature stand-off insulator.

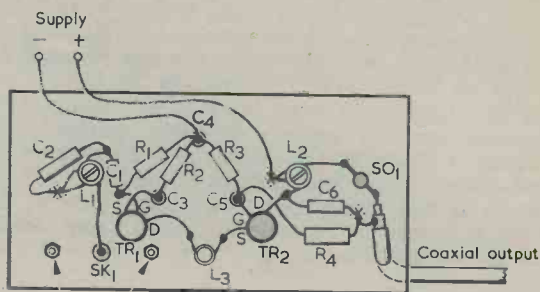The two r.f. transformers, L1 and L2, are wound on 5mm. formers fitted with dust cores. Formers of this size can often be obtained from the 'biscuits' of discarded TV tuners. 5mm. formers and dust cores, are, alternatively, listed in the Home Radio catalogue. The formers are fitted into holes of suitable size drilled in



Nuts securing coaxial socket

* - connection to board

Fig. 2. Layout of the pre-amplifier, which is assembled on a small piece of copper-clad board. The output is taken by way of a coaxial cable which passes through a hole in the board

the board. Each tuned winding consists of 6 turns of 28 s.w.g. enamelled copper wire with the turns spaced by wire thickness. The windings are not intended to peak sharply, hence the small values assigned to capacitors C2 and C6. If the tuned windings are first made around a drill shank or other round object slightly smaller in diameter than the coil formers, they can then be gently sprung onto the formers and a firm fit will result. Each coupling winding consists of 2 turns of thin plastic covered wire wound between the tuned winding wire at the earthy end. They are most easily fitted after the coil formers have been mounted on the board.

Coil L3 consists of 13 turns of 34 s.w.g. d.s.c. wire close-wound on a former with a diameter of approximately 3mm. This coil is not very critical, incidentally, and the pre-amplifier will function reasonably well without it.

The three feed-through capacitors provide anchoring points for some of the components, but there are also a few 'mid-air joints'. These joints are quite stable mechanically due to the short component lead-outs. Note that some connections are soldered directly to the copper of the board. The f.e.t.'s should be soldered in last of all, using a soldering iron whose bit is earthed.

TESTING

When completed, the pre-amplifier can be initially checked by measuring the current it draws from a 9 volt battery. This should be approximately 2 to 2.5mA. The f.m. tuner or receiver with which the pre-amplifier is to be used is then turned on with its aerial connected in the normal manner, and a weak signal is tuned in. This should, preferably, be at a central frequency in the f.m. band. The pre-amplifier is next introduced between the aerial and the tuner or receiver, and signal strength is noted as the cores of L1 and L2 are adjusted. Normally, the cores will need to be almost fully inside the coils for maximum signal strength. As already stated, the tuning of the two coils is not sharp. Once they have been adjusted the cores should be left alone. Comparisons can then be made

COMPONENTS

Resistors

(All ¼ watt 5%)

R1	220kΩ
R2	470Ω
R3	82kΩ
R4	82kΩ

Capacitors

C1	100pF ceramic
C2	4.7pF ceramic
C3	1,000pF ceramic feed-through
C4	1,000pF ceramic feed-through
C5	1,000pF ceramic feed-through
C6	4.7pF ceramic

Inductors

L1, L2, L3 see text

Transistors

TR1	2N3819
TR2	2N3819

Socket

SK1 coaxial aerial socket

Insulator

SO1 miniature stand-off insulator

Miscellaneous

Copper-clad board
Coaxial cable.

with the pre-amplifier in and out of circuit, whereupon it should be found that it gives a significant improvement in signal strength.

As a point of interest, at the writer's location in the West country the chimney-mounted stereo beam aerial is headed on Wenvoe, which is some 50 miles away with the Mendip Hills rising to over 800 feet above sea level in between. With no pre-amplifier in circuit stereo signals are not entirely hiss-free, particularly on Radio 3. Radio Solent (mono) at a distance of about 60 miles comes in on the back of the beam and is too weak to copy. When the pre-amplifier is inserted Radio Solent is another 'local' and stereo reception from Wenvoe Radio 3 is excellent.

MODIFICATIONS

An alternative pre-amplifier circuit which has the chassis negative is illustrated in Fig. 3. Component values are the same as in Fig. 1 and, since TR1 source bias resistor is now returned to chassis, there is no need for R1 and C1. The circuit could be assembled on a piece of copper-clad board with much the same basic layout as in Fig. 2, and with the copper corresponding to chassis. The author has not checked the circuit of Fig. 3 in practice, but there is little reason to doubt that it should not give equivalent results to that of Fig. 1.

As a final point, the design could also be modified to cover the 2 metre amateur band of 144 to 146MHz

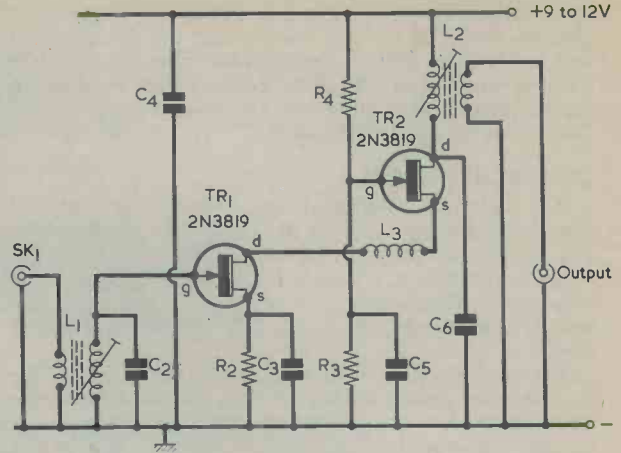


Fig. 3. An alternative circuit in which the chassis connection is common with the negative supply rail. R1 and C1 are not required in this version

All that would be required is to reduce the tuned windings of L1 and L2 to $4\frac{1}{2}$ turns each, and then tune these to the centre of the 2 metre band. ■

IN NEXT MONTH'S ATTRACTIVE ISSUE

NEW TRANSISTORISED OSCILLOSCOPE

Part 1
(3 Parts)


By R. A. Penfold

Regular readers will recall the popular and successful transistorised oscilloscope design published in the December 1972 and January 1973 issues of this magazine. Our contributor has now produced a more modern and up-dated version of this design which incorporates many important improvements.

The new oscilloscope is introduced, and constructional details are given of metal-work and the power supply section in part one.

PLUS
MANY OTHER ARTICLES

ON SALE 1st SEPTEMBER

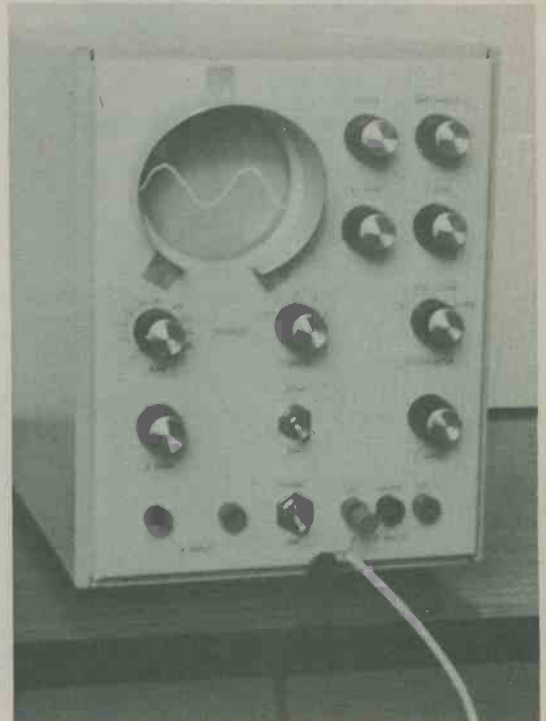

PRICE 30p

VOLTMETER WITH A MEMORY

By G. A. French

Suggested Circuit 297

ONE OF THE DIFFICULTIES OF TAKING voltage measurements when fault-finding on a small and crowded printed circuit board is that it is necessary to keep an eye on the board to ensure that the test prods are at the correct points whilst at the same time trying to observe the voltage reading indicated by the testmeter. The voltmeter design which forms the subject of this month's article in the 'Suggested Circuit' series overcomes the problem in a novel way: the voltmeter has a 'memory' which enables it to retain any 'voltage reading after the test prods have been removed from the circuit being checked. Thus it is possible to apply one's complete attention to applying the test prods to the appropriate points in the circuit being checked; the prods may then be removed, whereupon the voltmeter will continue to indicate the voltage that was last applied to them.

The voltmeter has a rather limited range with a maximum voltage reading of 20 volts, but this is adequate for nearly all battery operated transistor equipment. If the voltmeter is used with the memory facility switched out of circuit it draws a negligibly low current from the circuit points being checked. If the memory function is switched in, the voltmeter draws an initial current limited to a maximum of about $200\mu\text{A}$ for a very short period whilst a capacitor charges, after which the current falls to the same negligibly low value as is given with the memory switched out. The voltmeter may be built complete with its own meter movement and series multiplier resistors. Alternatively, these may be omitted and two terminals provided to which any testmeter with a resistance of $10,000\Omega$ per volt or better on its voltage ranges may be connected. If this second method of construction is adopted the voltmeter requires only

two inexpensive transistors and a small quantity of other components.

The voltmeter circuit has to be described as being slightly experimental because it is assumed that the transistors employed have leakage currents lower than the maximum figures specified by the manufacturer. As is explained later, general experi-

ence shows that the risk of any particular transistors not having the low leakage currents required for the present application is extremely small.

CIRCUIT DIAGRAM

The circuit of the voltmeter appears in Fig. 1. This consists basically of the

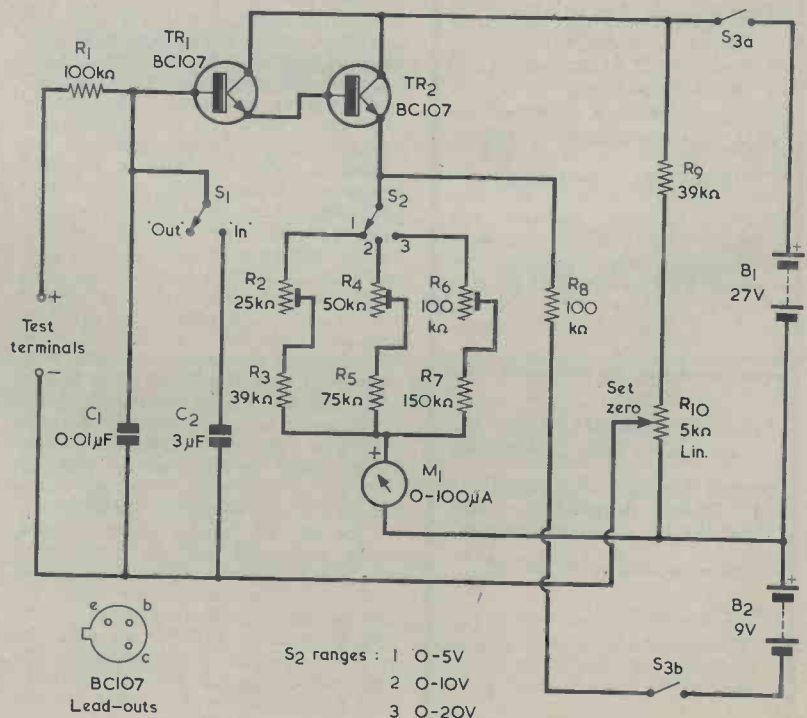


Fig. 1. The circuit of the voltmeter. The memory facility is switched in or out by means of S1

AUDIO AMPLIFIERS



16 Transistor & Valve Designs for the Home Constructor

Amplifiers for Tuner Units, Record Players, Tape Recorders, Public Address, etc., etc.

Includes contributions by such well-known authors as

A. S. Carpenter, A. Kinloch, E. Govier, G. A. French, F. G. Rayer, P. F. Bretherick, K. Jones, D. Aldous, R. Murray-Shelley, C. Swires, G. A. Stevens and V. E. Holley.

Edited by J. R. Davies

124 pages

PRICE 53p

P & P 12p.

To: DATA PUBLICATIONS Ltd.,
57 Maida Vale London W9

Please supply copy(ies) of "Audio Amplifiers", Data Book No. 18. I enclose cheque/crossed postal order for.....

Name.....

Address.....

.....

.....

.....RC
BLOCK LETTERS PLEASE

two BC107 emitter followers, TR1 and TR2, these coupling into the effective voltmeter given by M1 and whatever series resistors are switched into circuit by range switch S2. The use of two emitter followers in this manner is not new and a similar circuit was published several years ago in this journal.* In addition to incorporating the memory facility, the present circuit differs in several other aspects from the previous design.

The input resistance at the base of TR1 is very high and, in practice, it is possible to insert at least several megohms in series with the positive input without causing a significant alteration in any reading given by meter M1. This very high input resistance relies on the assumption, just mentioned, that the transistors employed for TR1 and TR2 will, in practice, have leakage currents lower than their maximum specified values. The author has used this particular circuit a considerable number of times in the past and has yet to encounter any BC107's or similar silicon planar transistors which did not function adequately in it. Also, no reports from readers have indicated that the previously published voltmeter design gave unsatisfactory results. Thus, whilst it is feasible that some BC107's may not have sufficiently low leakage currents to be employed in the present circuit, the possibility is extremely low. The transistors used should, of course, be properly branded specimens in good condition.

The voltage at the positive test terminal causes a corresponding voltage to appear at the emitter of TR2. Due to the voltage drop in the two base-emitter junctions, the second voltage is about 1.2 volts negative of that at the positive test terminal. The effective voltmeter given by M1 and its series resistors measures the voltage between TR2 emitter and the negative rail from battery B1, and M1 gives a zero reading when the positive test terminal is about 1.2 volts positive of this rail. The negative test terminal is taken up to the same potential by means of the Set Zero control, R10. R8 couples the emitter of TR2 to a potential, given by B2, which is 9 volts negative of the negative rail from B1. This ensures that emitter current still flows in TR2 when meter M1 is at a zero setting. In consequence, linearity is maintained when low voltages down to zero are applied to the test terminals.

Switch S2 selects three ranges, these being 0-5 volts, 0-10 volts and 0-20 volts. Meter M1 has an f.s.d. value of 100µA and so the sensitivity of the voltage measuring circuit switched in by S2 is 10,000Ω per volt. On the 0-5 range R2 is adjusted such that the total resistance offered by itself, R3 and the meter is 50,000Ω. On the

0-10 volt range R4 is adjusted for a total resistance of 100,000Ω, and on the 0-20 volt range R6 for a total resistance of 200,000Ω. In practice these potentiometers are set up with the aid of known voltages at the test terminals.

MEMORY FACILITY

S1 is the memory switch and, when this is set to 'Out', the voltage applied to the test terminals passes via R1 to the base of TR1 and the 0.01µF capacitor C1. C1 is included to ensure that the voltmeter is not affected by static or hum pick-up on the positive test lead. When S1 is put to 'In' the 3µF capacitor, C2, is connected across C1. C2 charges to the level of any voltage applied to the test terminals and, because of its relatively high capacitance, retains the charge for at least five seconds after the voltage has been removed. With the author's prototype circuit, C2 retained its charge for considerably longer than the five second period. In consequence, two test prods connected to the test terminals may be applied to any two points having a voltage between them and may then be removed. Meter M1 will then continue to indicate the voltage.

Resistor R1 is included in circuit to limit the input charge current to C2. If C2 is discharged and a voltage of 20 volts is applied to the test terminals, the initial charge current in the circuit is limited by R1 to 200µA. This current rapidly reduces as C2 charges. As a result R1 ensures that the circuit whose voltage is being checked is not unduly affected by charge current in C2. R1 also limits input current if a voltage of incorrect polarity is applied to the test terminals. Further, in company with C1, or C1 and C2 in parallel, it ensures that the meter is not affected by pick-up on the positive test lead, as was just stated.

As with all voltmeters, care should be taken to ensure that excessively high voltages or voltages of incorrect polarity are not applied to the test terminals. If a low voltage of incorrect polarity is applied, TR1 and TR2 are merely cut off and the meter gives a reverse reading. Should the applied voltage of incorrect polarity be sufficiently high to exceed the reverse breakdown voltages in the base-emitter junctions of TR1 and TR2, these junctions will function as zener diodes and allow a reverse current to flow. This reverse current flows also through meter M1, whose needle is in consequence once more deflected in the reverse direction. Unless the voltage of incorrect polarity is relatively high, i.e. well above 20 volts, the reverse current should not be sufficiently high to damage the transistors or the meter, but it obviously should not be allowed to remain at the test terminals for a long period. If C2 is switched into circuit, it will rapidly

*P. James, 'High Resistance Voltmeter', *Radio & Electronics Constructor*, April 1973.

discharge when a high voltage of incorrect polarity is removed.

Battery B1 can consist of three small 9 volt batteries, such as the PP3, connected in series. The current it supplies is of the order of 0.6 to 0.7mA. B2 can be another small 9 volt battery, and the current drawn from it is even lower, ranging from some 0.09 to 0.3mA according to the applied test voltage. The life of both B1 and B2 should not be much shorter than their shelf life.

The six fixed resistors may all be $\frac{1}{2}$ watt 10% types. R2, R4 and R6 are small skeleton pre-set potentiometers. R10 is a standard carbon-track potentiometer fitted to the front panel of the meter, as also are S1, S2, S3 and meter M1. S1 can be a single-pole toggle switch and S3 a double-pole toggle switch. S2 is single-pole 3-way rotary.

Capacitor C1 is a plastic foil component, as also is C2. An electrolytic capacitor must *not* be used for C2. The value of C2 is not particularly critical and capacitors having slightly higher values than 3 μ F may be employed if these are to hand. If necessary, it may be made up of two or more capacitors in parallel. In the prototype circuit the author used a parallel combination of three Mullard type C280 capacitors, each with a value of 1 μ F. The insulation around the positive input terminal and the base of TR1 must be of very good quality.

The parts may be assembled in a plastic case, or in a home-made plywood case. A metal case is not recommended because of possible small leakage currents between the batteries and their metal housings.

SETTING UP

After the meter has been completed it is necessary to set up R2, R4 and R6. This is done with the aid of known test voltages which are monitored by another external voltmeter.

First set the three pre-set potentiometers to a central setting. Put S1 to 'Out' and switch on at S3. Short-circuit the two test terminals and adjust R10 for a zero reading in M1.

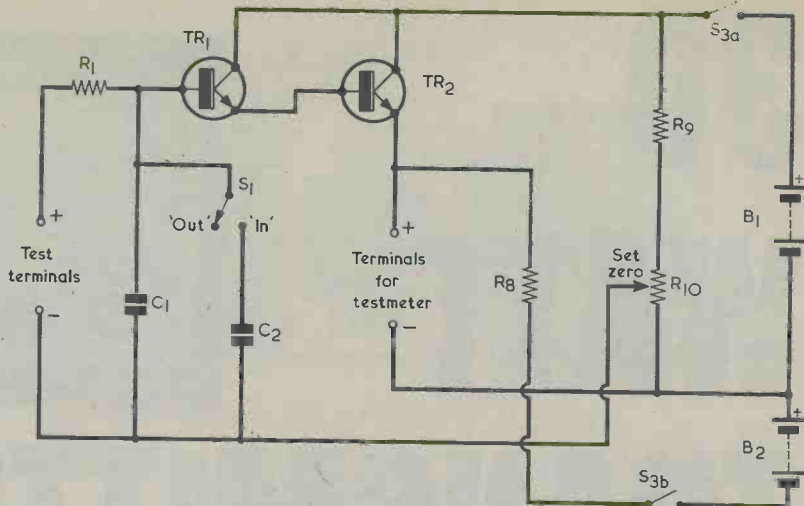


Fig. 2. A less expensive version of the circuit. This allows voltage indications to be given by a standard testmeter switched to a suitable volts range

Next put S2 to the 0-5 volt range and connect a 4.5 volt battery with the external monitoring voltmeter across it to the test terminals. Then adjust R2 for a reading in M1 which corresponds with that in the external voltmeter. If, for instance, the latter indicates 4.6 volts, R2 is adjusted so that M1 indicates 92 μ A. The process is then repeated with a 9 volt battery for the 0-10 volt range and with an 18 volt battery (two 9 volt batteries in series) for the 0-20 volt range. Alternative sources of test voltage, such as a variable voltage power supply, may also be employed if this is more convenient than using batteries.

After the pre-set potentiometers have been set up, S1 may be put to the 'In' position and the memory facility checked. There should be no significant change in the reading given by M1 after the removal of any test voltage between zero and f.s.d. on whatever range is switched in.

When the voltmeter is in use with

S1 in the 'In' position, C2 should be discharged between test readings by temporarily short-circuiting the test terminals together. The setting of the Set Zero control R10 should also be checked, with the test terminals short-circuited together, from time to time. With the prototype circuit it was found that there was very little drift in the zero setting.

As was stated at the start of this article an economy can be effected by providing two terminals to which a testmeter switched to a volts range can be connected. The revised circuit is shown in Fig. 2, in which R2 to R7 and meter M1 are omitted. The circuit is employed in the same way as is that of Fig. 1 so far as zero setting is concerned, but the voltage range given is that selected on the range switch of the testmeter itself. The testmeter scale can be read directly, and the voltage it indicates will be that applied to the test terminals. Test voltages should still be limited to a maximum figure of 20 volts.

CAN ANYONE HELP?

Requests for information are inserted in this feature free of charge, subject to space being available. Users of this service undertake to acknowledge all letters, etc., received for to reimburse all reasonable expenses incurred by correspondents. Circuits, manuals, service sheets, etc., lent by readers must be returned in good condition within a reasonable period of time.

Radio Constructor for March and April 1962 - T. R. Smith, 7 Purbeck Court, Park Barn, Guildford, Surrey - Borrow or purchase.


"How To Use Grid-dip Oscillators" - Hayden - E. J. Randall, 13 Charles Avenue, Greenfields, East London, South Africa - Borrow or purchase.

Contact cooled metal rectifier type ZA26612 (also marked 280 70 167C) - R. E. Simms, 18 Osborne Drive,

Sompting, Lancing, Sussex, BN15 9UY - Technical data and circuit information.

Roband Oscilloscope RO55 with Type B Plug-in Unit - D. L. Williams, P.O. Box 305, 24 Alexandra Street, Florida 1710, Transvaal, South Africa - Service Manual, Instruction Book, Wiring Diagram or Photostats - reasonable costs paid for this urgently required information.

30 WATT TRANSMITTER

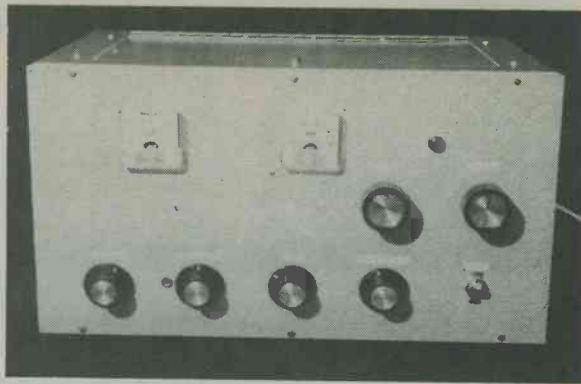

Part 2

By F. G. Rayer

This article concludes the description of the 30 watt transmitter whose circuit functioning was described last month. The final article in the 28MHz series will appear next month, and will deal with 10 metre aerials.

THE COMPONENTS FOR THE TRANSMITTER ARE ASSEMBLED on a type 'K' chassis measuring 13 by 8 by $2\frac{1}{2}$ in., this fitting into a type 'W' case measuring 15 by 9 by 8 in. Both the chassis and the case are available from H. L. Smith & Co. Ltd., 287/289 Edgware Road, London, W2. The case is supplied complete with front panel. There is a possibility, however, that the two mains transformers obtained may be significantly larger in physical size than those employed by the author. The constructor is advised to initially obtain the mains and modulation transformers and check whether these will fit into a chassis and case of the dimensions just given. If the chassis and case need to be larger to accommodate the transformers then the appropriate changes need to be made to their dimensions. In this instance, the case may need to be home-constructed.

CHASSIS PREPARATION

The positions for the valveholders and other items are shown in Fig. 3, whilst Fig. 4 shows the under-chassis wiring. V1, V3 and V4 are fitted in skirted valveholders with screening cans, the remaining valveholders being plain types without skirts. The valveholder holes should be made such that the valveholder tags will have the orientation shown in Fig. 4. Six holes, about $\frac{1}{4}$ in. or $\frac{3}{8}$ in. in diameter, are punched around V2 valveholder as shown in Fig. 3.

COMPONENTS

Chassis type 'K', 13 × 8 × $2\frac{1}{2}$ in. – see text (H. L. Smith & Co.)
Case type 'W', 15 × 9 × 8 in. having front panel 15 × 8 in. – see text (H. L. Smith & Co.)
Universal Chassis side, 4 × 5 in., (Home Radio)
4 knobs, $1\frac{1}{4}$ in.
2 knobs, $1\frac{1}{2}$ in.
4 rubber feet
2 metal strips, 7 × 1 in.
12 in. hinge
Valve top cap connector
Tagstrips (see Figs. 3 and 4)
Nuts, bolts, solder tags, etc.

With the transformers employed by the author for T2 and T3, the former requires a rectangular aperture to clear its tags whilst the latter has all its tags above the chassis. A grommet near T2 allows leads from T3 to pass through the chassis without running near audio circuits underneath.

When T1 is a modulation transformer type 747, as specified, its tag positioning will be different from that shown in Fig. 4 for this transformer. (The transformer initially used by the author became unobtainable just before preparation of this material. The transformer type 747 has been fully checked in the transmitter.) Clearance holes should be punched out to agree with the actual tag positions of the transformer. Alternatively a rectangular cut-out to clear all the tags may be made. The tag numbers of the type 747 transformer agree with the numbers shown in Fig. 4.

The crystal holder types fitted can be as chosen by the constructor. The author fitted one small holder for

RADIO & ELECTRONICS CONSTRUCTOR

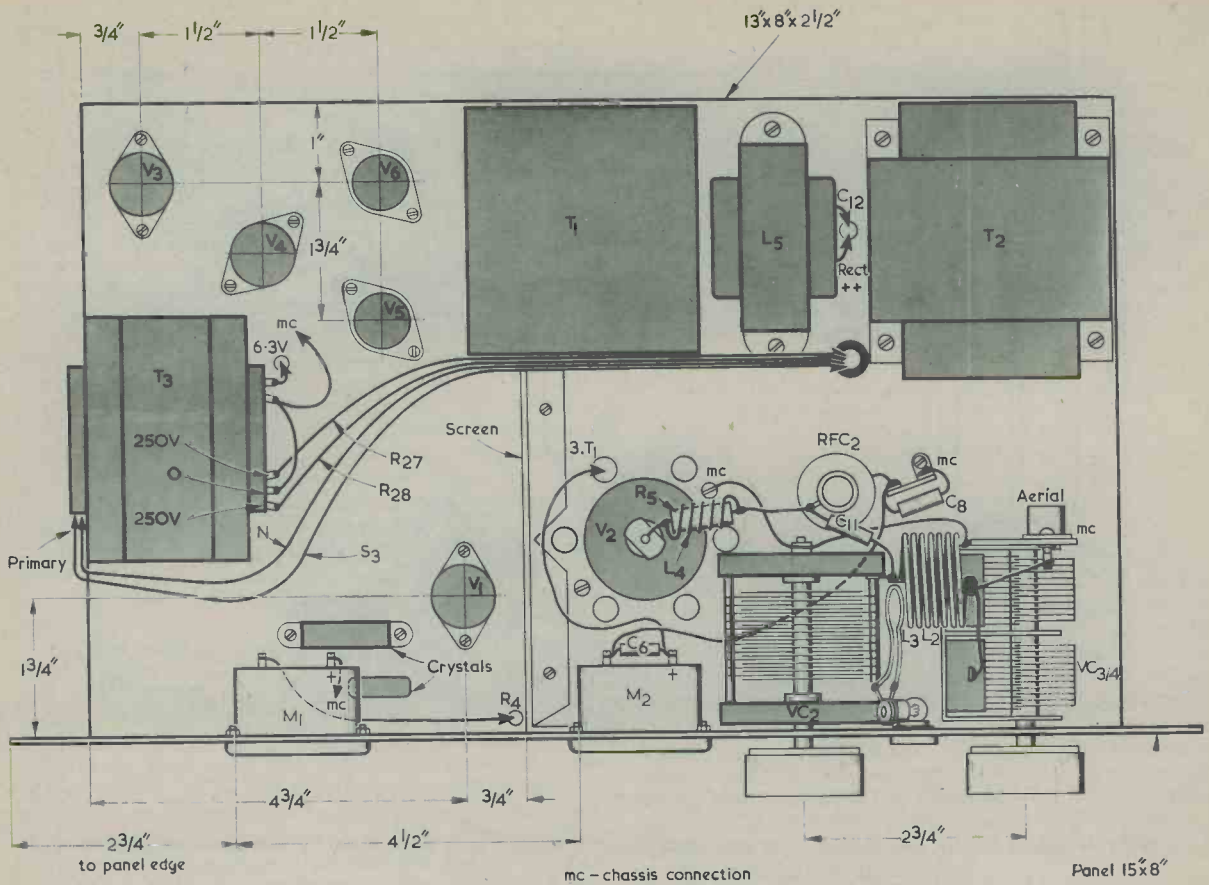


Fig. 3. The components and wiring above the chassis. Valve pin orientation should conform with that shown in Fig. 4


HC25U crystals, the other holder being a 3-socket type taking larger crystals with either $\frac{1}{2}$ in. or $\frac{3}{4}$ in. pin spacing. A few other small holes are also needed, as indicated.

Under the chassis, holes are required for the under-chassis controls, the 2-way external control socket, the microphone input socket and the v.f.o. input socket. The author used a phono socket for the v.f.o. input. The microphone input socket and aerial output socket (fitted later) were both standard 75Ω coaxial types.

With the case used here, the lower edge of the panel must project $\frac{1}{2}$ in. below the chassis. The chassis and panel are eventually fixed together by the mounting bush nuts of the under-chassis controls. Correct matching of holes can be assured by marking out the panel through the holes in the chassis runner.

Also required in the panel are holes for the meters and for VC2 and VC3,4, as illustrated in the photographs and Fig. 3. If VC2 and VC3,4 are the types specified in the Components List published last month they are mounted by screws passing through the panel into the tapped holes provided.

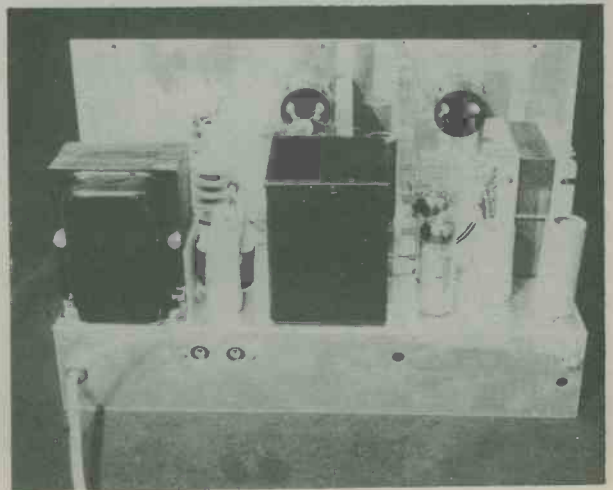The vertical screen shown in Fig. 3 can also be fitted now. This was cut from a Home Radio 'Universal
AUGUST 1975



Top view of the chassis, as seen from the rear


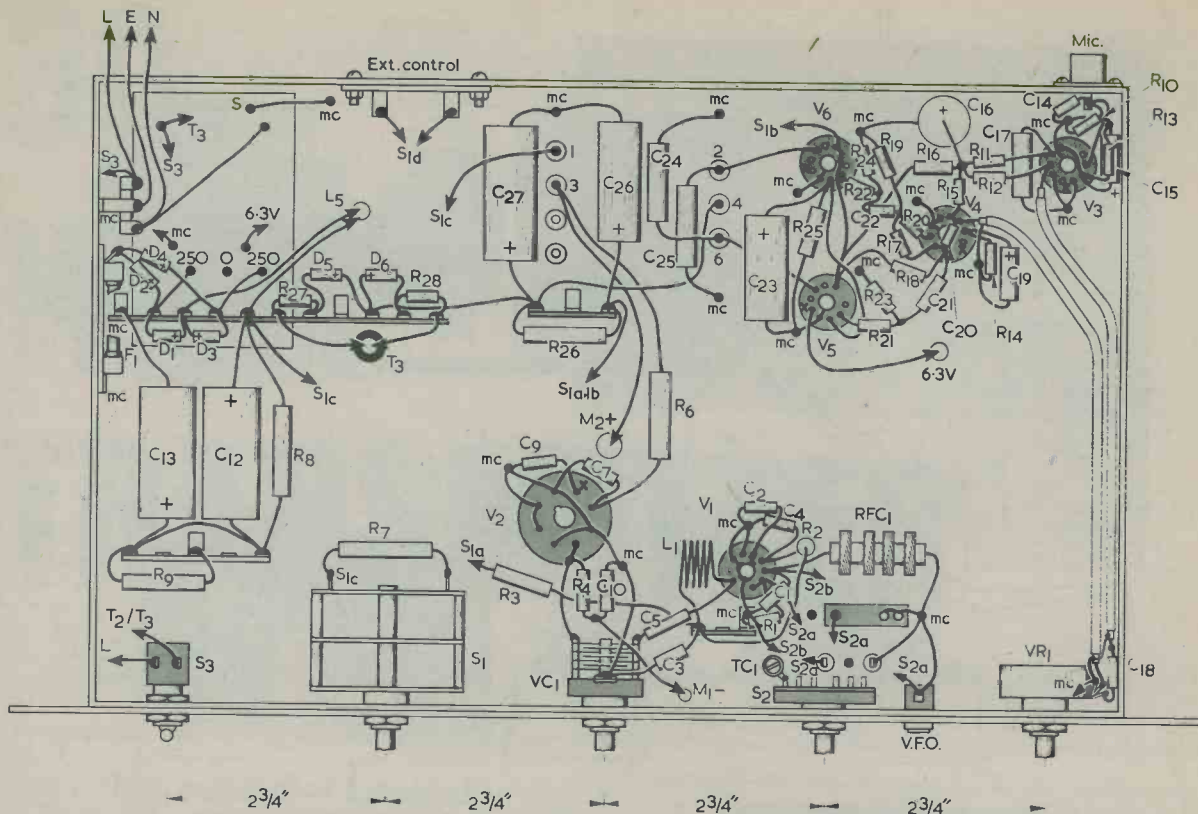


Fig. 4. Wiring below the chassis. The text should be consulted with respect to transformer connections

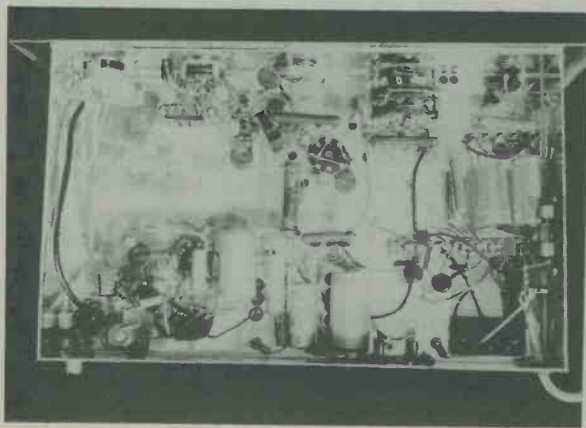Chassis' side measuring 4 by 5 in. and, when fitted, is 4 in. high and extends back from the front panel by approximately 4½ in. This screen separates the oscillator and the p.a. stage, and also makes the panel more rigid when the equipment is out of the case.



Quite a number of components appear under the chassis, but there is room for these to be spaced out comfortably

WIRING

Most of the wiring details can be seen from the diagrams, but a few further notes need to be made.

The heater current requirements for V1 and V2 total 2 amps, and the heaters of these two valves are supplied by the 6.3 volt secondary of T2. The heater current for V3 to V6 similarly totals 2 amps, and these heaters are supplied by the 6.3 volt secondary of T3. The non-earthed 6.3 volt wiring runs against the chassis underside to the valveholder tags marked 'X' in Fig. 4. Any spare heater secondaries which may be available are unused.

The connections to transformers T1, T2 and T3 shown in the diagrams apply to the particular transformers employed by the author. If the transformer used for T2 has its tags above the chassis, then the leads to these tags pass through suitably positioned holes fitted with grommets. If either mains transformer has a screen tag, this connects to chassis. Such a connection is shown at T2, where the tag marked 'S' is wired to chassis.

The 3-core mains wire is terminated at a 3-way tagstrip, as in Fig. 4. The neutral lead connects to the 'OV' tag of the primaries of T2 and T3. The live wire connects, via on-off switch S3, to the appropriate primary voltage tap (normally 240 volts) on T2 and T3. The mains earth lead connects to chassis. The mains wire should be suitably anchored inside the chassis.

The rectifier wiring to T2 h.t. secondary can be seen in Fig. 4. Note that the h.t. secondary centre-tap is *not* used. Mount the rectifiers by their lead-outs. The

negative lead-outs of D2 and D4 connect to the fuse, the other tag of which is returned to chassis. The positive lead-outs of D1 and D3 connect to the smoothing choke, L5. C12 and C13 are in series, supported by tagstrips, with R8 and R9 in parallel. If C12 is housed in a non-insulated metal can, this must not touch the chassis. Nor must it touch C13 if this is similarly in a non-insulated metal can.

The h.t. secondary centre-tap of T3 connects to chassis above the chassis surface. The two leads from the outside ends of the h.t. secondary pass through the grommet adjacent to T2, and then connect to R27 and R28 on the tagstrip shown. R27 and R28 then connect to D5 and D6, and these in turn connect to C27. Remember that h.t. remains permanently on the modulator output anodes.

In the audio section, grid and anode leads are kept close to chassis, especially in the earlier stages. The long leads to VR1 are screened, the braiding being earthed to the chassis. The pairs of resistors R18 and R19, R21 and R22, and R23 and R24, should be approximately matched in value by checking from a batch with an ohmmeter or by fitting 5% components here. It is not quite so important for R21 and R22 to be closely matched, although this assists in providing circuit symmetry.

All r.f. connections around the oscillator, V1, should be short and direct. The wiring to switch S2 is shown in Fig. 5. Before making connections here, ascertain with an ohmmeter the three outside contact tags corresponding to each centre tag, as their relative positioning may vary with some switches from that shown in the diagram. If a 2-pole 3-way switch cannot be obtained, a 4-pole 3-way switch may be used, with no connections made to two of the poles. One tag of the trimmer, TC1, is soldered to one of the outer switch tags. A tagstrip adjacent to the valveholder holds one end of coil L1, and C3 is wired directly between L1 and the moving vanes tag of VC1.

The valveholder for V2 is mounted under the chassis. Extremely short connections should be made to its tags. The earthing leads are connected as shown in Fig. 4 using stout tinned copper wire, this being soldered well down the valveholder tags and not at the tag ends. The grid lead to pin 5 should also be of stout wire and this is kept clear of the chassis as, similarly, are R4 and C5. A lead from the junction of R4 and C10 runs through the chassis to the negative terminal of meter M1. The positive terminal of the meter connects to chassis at the panel.

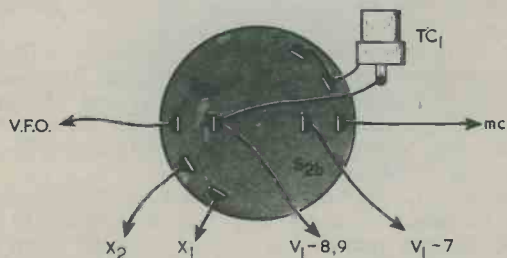


Fig. 5. Connections to the crystal-v.f.o. switch, S2

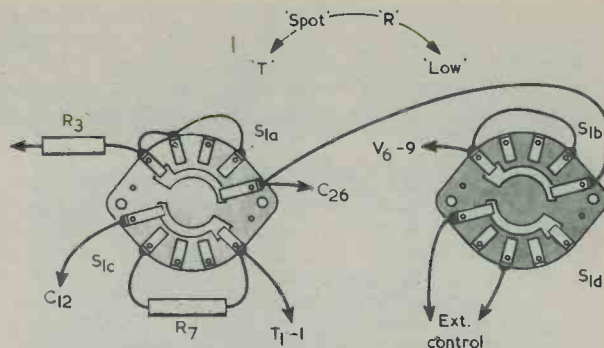


Fig. 6. The function switch, S1, has two wafers, these being wired as illustrated here

Above the chassis, the lead from R5 to the top cap of V2 is as short as possible, with just sufficient flexible wire to the top of RFC2 to allow the top cap connector to be fitted and removed. A 2-way tagstrip takes the lower end of RFC2 and capacitor C8. A wire from the junction of RFC2 and C8 runs along the chassis then up to the negative terminal of meter M2. A wire from the positive terminal of this meter runs through one of the holes around V2 valveholder to tag 3 of the modulator transformer, T1. As is shown in Fig. 3, a stout tinned copper wire runs from the frame of VC3,4 to the rotor tag of VC2 and from here to the 'MC' tag at V2 valveholder. A piece of scrap metal bolted to VC3,4 carries the aerial coaxial socket.

Because of the voltages at its contacts, switch S1 should be a standard sized switch with two wafers, and not a miniature component. Connections to it are made as illustrated in Fig. 6. These connections may be checked through with an ohmmeter after wiring has been completed to ensure that they are correct. The panel should be marked with the switch functions, these being 'Low', 'Receive', 'Spot' and 'Transmit'.

In Figs. 3 and 4, connections to chassis are, with one exception, made by way of solder tags or the earthed tags of tagstrips at the points marked 'MC'. The tags are secured under component mounting bolts or nuts at the places indicated. The exception just mentioned is at VR1, where the chassis connection is to the metal frame of the potentiometer.

COIL DETAILS

For operation with the 28MHz band equipment described in the preceding articles, only 28MHz coils are required in the L1 and L2 positions. These inductors may, then, be fitted permanently. Both are self-supporting.

L1 consists of 6 turns of 18 s.w.g. enamelled wire. Its outside diameter is $\frac{7}{8}$ in. and its length is $\frac{1}{8}$ in. It is soldered directly between tag 1 of V1 valveholder and the tag of the adjacent tagstrip, as shown in Fig. 4.

L2 has 7 turns of 16 s.w.g. tinned copper wire, and is $\frac{7}{8}$ in. long with a diameter of $1\frac{1}{8}$ in. Its ends are just long enough to solder to the variable capacitors.

If different coils are wound, a check should be made to ensure that they cannot be tuned to the wrong harmonics of the crystal fitted.

L3 is 1 turn of insulated wire about 1 in. in diameter, and it is positioned such that the indicator bulb lights at moderate brilliance when the p.a. stage is tuned. The power consumed by this lamp is not really significant.

The anti-parasitic choke, L4, has 5 turns of 18 s.w.g. enamelled wire with an inside diameter of $\frac{3}{8}$ in. and a length of $\frac{5}{8}$ in. It is slipped over the body of R5 and soldered to the resistor lead-outs. One resistor lead-out is soldered to the top cap connector for V2 and the other has a length of flexible wire soldered to it. As already mentioned, these connections are kept short.

It will be apparent that the transmitter can be used on other bands by employing a suitable crystal or v.f.o. and changing L1 and L2 only. Details of alternative coils are given later.

OSCILLATOR TUNING

With 14MHz band crystals, multiplying by 2 gives the working frequency of the transmitter. As an example, a 14.25MHz crystal will give 28.5MHz. with 7MHz crystals the frequency is multiplied by 4. All 14MHz and 7MHz amateur band crystals will give a frequency which, when multiplied by 2 or 4, falls into the 28MHz band.

With a 14MHz crystal plugged in and selected by S2, and with S1 at 'Spot', tune VC1 for grid current in M1. This may well be too great, so VC1 is adjusted for a reading of about 2mA. The drive can be lowered by reducing the capacitance of TC1. With an optimum adjustment of TC1, over 5mA grid drive was obtainable, so even sluggish crystals should work satisfactorily in the transmitter. It is because it provides such an ample drive that V1 is operated with the reduced voltage which is given by R3.

If it is intended to use only 7MHz or lower frequency crystals, TC1 can be changed for a 22pF silvered mica fixed capacitor, or a 30pF trimmer, with C1 being increased to 220pF silvered mica.

The transmitter is never switched to either 'Low' or normal transmission until M1 is indicating a grid current of approximately 2mA.

P.A. TUNING

An artificial load consisting of a 25 watt or 40 watt domestic mains lamp can be plugged into the aerial socket for initial tests. After tuning VC1 for grid current as just described, set VC3,4 to full capacitance and switch S1 to 'Low'. Tune VC2 for a dip in current in M2. The capacitance of VC3,4 is then reduced, with VC2 being re-adjusted to maintain the dip in current shown by M2. As the loading is increased by the reduction of capacitance in VC3,4, the current taken at the dip will rise. Provided that p.a. tuning is taking place in this manner, S1 can be set to 'Transmit' and the loading adjusted for a reading of about 75mA in M2, whereupon the artificial load bulb should be well lit. Grid tuning can then also be checked, to set grid current correctly. In no circumstance must the p.a. be left off-tune with a full h.t. input, as excess power is then dissipated in the p.a. valve itself.

If an oscilloscope is available this can be used to check modulation. If not, a receiver can be employed. Its aerial should be removed and its r.f. and i.f. gain controls turned back. It is then tuned in to the transmitter, and VR1 is adjusted until speech sounds clear and full. If the receiver has a loudspeaker, take care

that the sound from this does not reach the transmitter microphone or there will be acoustic feedback and howling. The super-regenerative receiver described in the third article in this series may also be used to monitor modulation quality.

CASE PREPARATION

The metal case, when this is as used by the author, is modified to provide extra ventilation, and is also fitted with a hinged lid.

First, cut out nine holes of about 1 in. diameter in the case bottom. These are distributed in three rows of three holes each. Then fit four rubber feet about $\frac{7}{8}$ in. high at the corners, to allow cool air to flow to the holes.

At the back, eight holes of $\frac{3}{4}$ in. diameter are cut in a row 1 $\frac{1}{2}$ in. from the case top. The coaxial aerial lead is passed through the end hole at the right to reach the aerial socket. A 1 in. hole is cut level with the microphone socket on the chassis. Two 1 $\frac{3}{8}$ in. holes are cut side by side level with the mains lead entry point. The metal between these holes is then cut away, giving a slot through which the mains plug can pass.

At the top, carefully mark out a rectangle measuring 12 by 6 $\frac{1}{2}$ in., this being 1 in. from the front of the case and central along its width. Drill enough small holes closely together to enable a small thin saw blade to be inserted, and cut the rectangle out completely. After cleaning up its edges, this becomes the lid. Obtain two strips, 7 by 1 in., of any suitable metal, and bolt these to the case top underside along the rectangle 6 $\frac{1}{2}$ in. sides, with $\frac{1}{4}$ in. projecting to support the lid when closed. Screw on a 12 in. hinge (available in metal or plastic from most 'do-it-yourself' shops) at the rear of the rectangle. Finally, fit the lid with a small knob or terminal near the front so that it can be raised.

OTHER BANDS

For operation on other bands, coils L1 and L2 can be wound in the following manner.

15 metres. For 15 metre working, L1 has 12 turns of 24 s.w.g. enamelled wire wound side by side on a $\frac{7}{16}$ in. diameter former. L2 is self-supporting and consists of 8 turns of 16 s.w.g. tinned copper wire with an outside diameter of 1 $\frac{1}{8}$ in. and a length of 1 in.

20 metres. For this band, L1 requires 25 turns of 24 s.w.g. enamelled wire wound side by side on a $\frac{7}{16}$ in. diameter former. L2 is again self-supporting and consists of 11 turns of 16 s.w.g. tinned copper wire with an outside diameter of 1 $\frac{1}{8}$ in. and a length of 1 $\frac{1}{8}$ in.

40 metres. Here, L1 has 30 turns of 24 s.w.g. enamelled wire wound side by side on a $\frac{1}{2}$ in. diameter former with dust core. L2 comprises 25 turns of 18 s.w.g. enamelled wire occupying 1 $\frac{1}{2}$ in. on a $\frac{7}{8}$ in. diameter former.

80 metres. For 80 metres, L1 consists of a Denco Miniature Dual Purpose Coil, valve usage, Red Range 2, with the small winding removed, and 28 turns removed from the remaining winding. L2 has 32 turns of 18 s.w.g. enamelled wire spaced to occupy 2 $\frac{1}{4}$ in. on a 1 $\frac{3}{8}$ in. diameter former.

160 metres. On this band, L1 is a Denco Miniature Dual Purpose Coil, valve usage, Blue Range 2, with the small winding removed. L2 consists of 70 turns of 24 s.w.g. enamelled wire wound side by side on a 1 in. diameter former.

All these coils permit operation into 75 Ω and similar loads.


Trade News . . .

VERO I.C. SOCKETS

The heart of the Vero Socket is the Dual Leaf Wiping Contact which makes contact with both of the wide flat surfaces of I.C. Leads. This provides considerably greater surface contact for positive electrical connection than I.C. Sockets which mate with the narrow edge of I.C. Leads.

To further improve the quality of the Vero Sockets received by customers they are all individually tested for continuity and contact performance before packing. A high quality pack then ensures the sockets reach the customer undamaged and they retain their good performance characteristics.

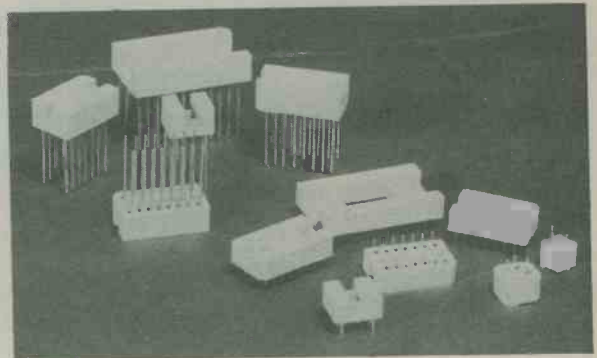8, 14, 16 and 24 way Sockets are now available in tin plated, gold plated, flow solder and mini wrap styles.



COMPONENT STORAGE


One of the minor problems which besets the home constructor is that of finding storage for small components including, in particular, transistors and integrated circuits. The idea of just throwing everything into the odd cardboard box cannot be countenanced these days, and something which enables different transistors and integrated circuits to be stored away according to type number or function is well-nigh essential.

We have just seen some very neat rectangular transparent plastic boxes which seem to provide all the answers here. Measuring approximately $1\frac{3}{4}$ by $1\frac{1}{2}$ by $\frac{3}{4}$ in. deep, these have a sliding lid which clicks into position when

pushed fully home. They are just the job for holding transistors and integrated circuits, as well as small resistors, capacitors and, of course, nuts and bolts. The fact that the boxes are transparent means that you don't necessarily have to stick labels on them. You can see what's inside simply by looking through the transparent sides or top.

The boxes are available from The Radio Shack, 161 St. Johns Hill, Battersea, London, SW11, and they could also lend themselves to use as attractive housings for small constructional projects.

THUNDER V-CUT SPANNERS

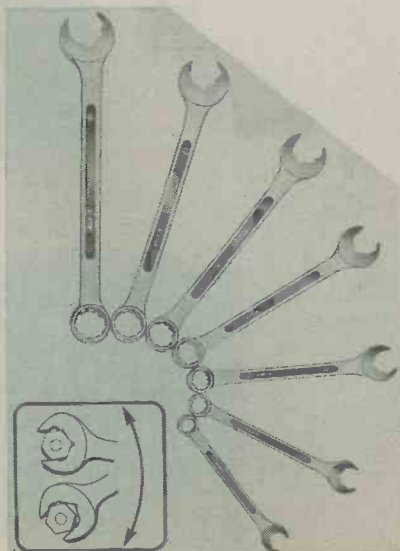

Thunder Screw Anchors Ltd., of the Industrial Estate, Southwater, Horsham, Sussex RH13 7HQ, have introduced a new design in combination spanners which enables the operator to use the open end of the spanner in a ratchet action. The nut is tightened as far as space permits, the spanner is then slipped back to its original position without removing it from the nut, then further torque is applied. The ratchet type action makes the spanner easier and quicker to use.

They are made from chrome vanadium steel and are available in seven metric sizes (10mm - 19mm) and seven A.F. sizes ($\frac{3}{8}$ " - $\frac{3}{4}$ "). They are packed individually or available in a wallet of seven. For resale display a unit is available holding six of each size of spanner. Prices range from £0.64 each (excl. VAT) to £1.10 each (excl. VAT). A complete set of seven £6.22 (excl. VAT). Delivery from stock.

INTEGRATED SIGNAL GENERATOR

ANYBODY WISHING TO TAKE UP ELECTRONICS SERIOUSLY soon feels the need for some items of test gear. An item which can be built very easily by the home constructor is a low frequency signal generator, and many designs have been published. These are frequently based on the Wien Bridge principle using circuits similar to that shown in Fig. 1. The amplifier may be built either from discrete transistors or from a suitable operational amplifier, and it produces a sine wave which has then to be passed through a suitable squaring circuit should a square wave be required. Typical drawbacks with circuits of this nature are that they require ganged potentiometers, and that the scale is non-linear and so will be cramped towards one end. Further, two sets of expensive close tolerance capacitors are required and the oscillator frequency can vary both with temperature and supply voltage fluctuations.

8038 I.C.

A relatively new integrated circuit, the 8038 Waveform Generator, can be used to overcome these problems and provide the basis for a very simple, yet versatile, signal generator. This is not only inherently stable but offers a frequency range from 0.001Hz to over 1MHz. The 8038 is available from Ambit International, 37 High Street, Brentwood, Essex, CM14 4RH.


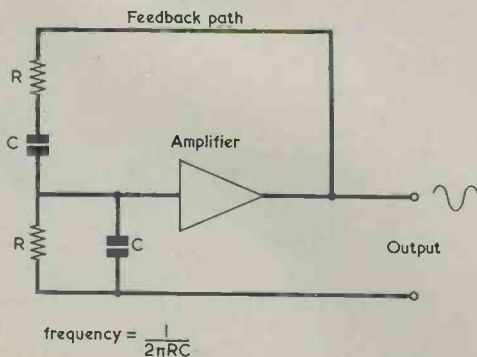
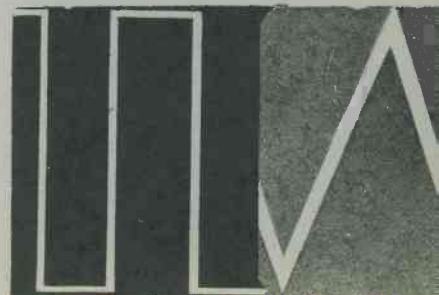


Fig. 1. A simple RC oscillator, commonly used for signal generator purposes

Pa

By Joh

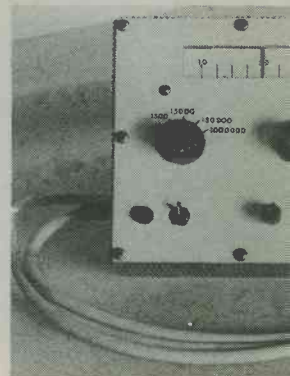Employing a recently introduced generator offers square wave, outputs from 10Hz to 1MHz. Conclude this issue, and methods of calibration concluding





ED CIRCUIT ENERATOR

t 1

n Lewis

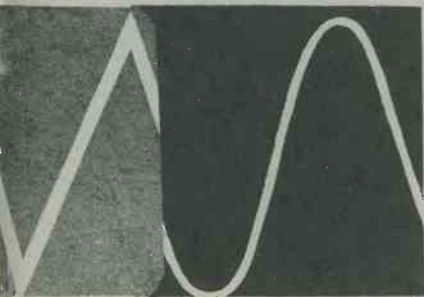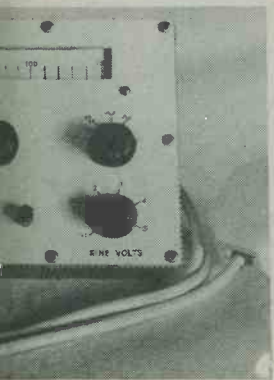and integrated circuit, this signal
triangular wave and sine wave
structional details are given in this
will be described in next month's
article.



A functional diagram for the i.c. can be seen in Fig. 2. Internally it contains over 50 transistors and 40 resistors on its chip to fulfil the functions shown. The two comparators sense the charging and discharging potential differences across the external capacitor, C. Comparator 1 is set to respond to a potential level of $\frac{2}{3} V_{CC}$ whilst Comparator 2 responds to $\frac{1}{3} V_{CC}$. As the capacitor charges up through Current Source 1 so the voltage across it increases uniformly until it reaches a value of $\frac{2}{3} V_{CC}$. At this point Comparator 1 triggers, causing the flip-flop to change state and allowing the capacitor to start discharging through Current Source 2. The current in Current Source 2 is normally twice that in Current Source 1, with the result that the effective discharge current is the same as the charge current.

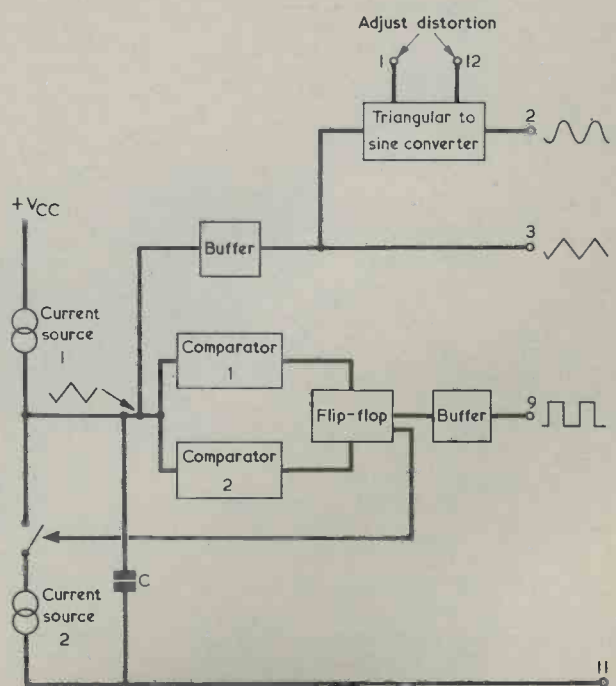


Fig. 2. Simplified functional diagram for the 8038 waveform generator

When the potential difference across the capacitor reaches $\frac{1}{3} V_{CC}$ Comparator 2 responds, the flip-flop changes state once more and the capacitor begins to re-charge through Current Source 1. The cycle will repeat itself, the frequency of operation obviously depending on the values of the capacitor and the charge and discharge currents. Note that the supply voltage does not enter into this calculation since the comparators are set to a certain proportion of V_{CC} and hence the output frequency remains constant even though the supply voltage may change. The quoted typical figure is 0.05% per volt change for frequency drift due to supply voltage variations, with a typical frequency drift due to temperature changes of 50 parts per million per °C.

From the diagram it will be seen that two waveforms are available, a square wave from the flip-flop output and a triangular waveform across the capacitor. These waveforms are fed to buffer amplifiers and are then available at pins 9 and 3 respectively. The triangular wave is also fed into a non-linear network of 16 transistors which produce a sine wave at pin 2. The amount of distortion on this sine wave can be adjusted externally by potentiometers connected to pins 1 and 12; by careful adjustment one can bring the distortion of the sine wave to less than 0.5%. However, at frequencies above some 10kHz the distortion starts to increase, rising to

about 12% at 1MHz. It will also be found that there are 'blips' on the sine wave which are due to internal switching transients.

The charge and discharge currents, and hence the frequency of oscillation, can be varied by two external resistors, RA and RB, connected between the positive supply rail and pins 4 and 5 of the integrated circuit. If a reference voltage of 0.8 V_{CC} is applied to pin 8 of the i.c. and if RA and RB are equal, then oscillator frequency in Hz is equal to $0.3 \frac{V_{CC}}{RC}$, where R is RA or RB.

(The connections to pins 4, 5 and 8 are not shown in the simplified diagram of Fig. 2.) This arrangement gives a square wave having a mark-space ratio of 1:1 and symmetrical sine and triangular waves. If RA and RB are not equal the charge time is not the same as the discharge time, with the result that a square wave of a different mark-space ratio is obtained together with non-symmetrical sine and triangular waves. Also, the equation for frequency becomes more complicated.

The reference voltage of 0.8 V_{CC} just mentioned is available at pin 7 of the i.c. and for fixed frequency operation this pin is connected direct to pin 8. If the voltage on pin 8 is varied, between V_{CC} and $\frac{2}{3} V_{CC}$, the output frequency can be swept over a theoretical range of 1,000:1. It is possible to frequency modulate the output frequency by way of this pin.

Fig. 3 (a) gives details of the pin assignments for the 8038, whilst Fig. 3 (b) shows typical output waveforms. Note the 'blips' at the sine wave peaks.


PROTOTYPE CIRCUIT

The circuit of the prototype signal generator appears in Fig. 4. The power supply section is a conventional dual voltage supply using zener diodes and transistors which provides one rail that is positive of earth and another rail that is negative of earth. This arrangement was chosen since a dual supply helps to reduce overall distortion and keeps the current flowing through RA and RB (which now appears as VR3 and VR4) constant, thereby assisting further in producing a good waveform. The 8038 is connected across the positive and negative rails and the various outputs from pins 2, 3 and 9 are taken to S2. This switch selects the required waveform, which is then fed to TR3 connected as an emitter follower to give a final output at low impedance.

The frequency is partly determined by VR3, VR4 and C4 to C8, and it was decided to give these values which produce frequencies of 100Hz, 1kHz, etc., according to whichever capacitor is switched in, when pin 8 of the 8038 is at 0.8 V_{CC} . This assists in the process of calibration later. The capacitors are 0.33 μ F, 0.033 μ F, 0.0033 μ F, 330pF and 33pF. From the formula $0.3 \frac{V_{CC}}{RC}$,

a combination of 10k Ω and 0.33 μ F produces a frequency of 90.9Hz. For 0.033 μ F the frequency is 909Hz, and so on. If, however, the value of R is made 9.09k Ω then the frequency becomes 100Hz with the 0.33 μ F capacitor, 1kHz with the 0.033 μ F capacitor, and so on for the other capacitors. To achieve the desired value in R of 9.09k Ω , VR3 and VR4 are specified as trimpots. An advantage to using trimpots here is that they can both be set to exactly the same value with the aid of an ohmmeter and thereby cause a symmetrical output waveform to be produced. The required capacitor is switched into circuit by range switch S1.

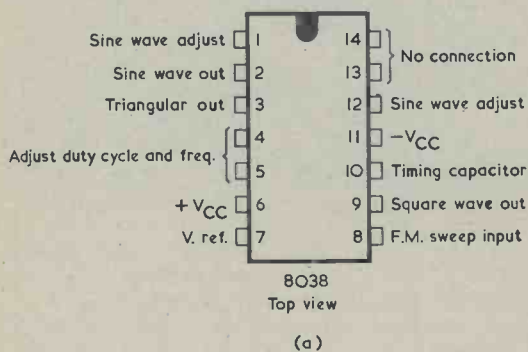The frequency is swept by VR5, which is the main frequency control, and it was decided to use a sweep



(a)



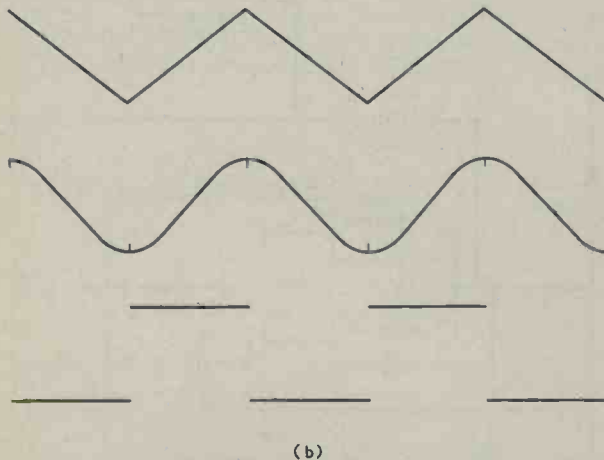


Fig. 3 (a). Pin functions for the waveform generator
(b). The appearance of the triangular, sine and square waves produced by the 8038

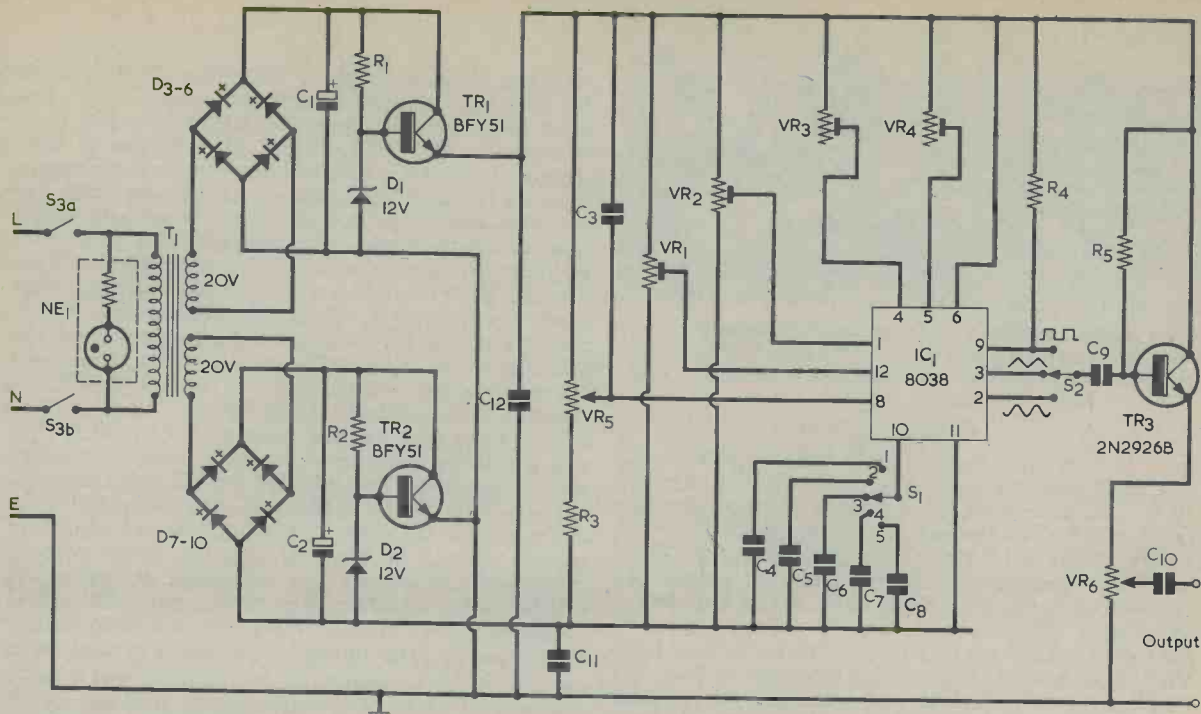

- S₁ ranges: 1 10-150Hz
 2 100-1500Hz
 3 1-15 kHz
 4 10-150kHz
 5 100-1,000kHz

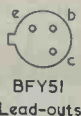

BFY51
Lead-outs



2N2926B
Lead-outs

Fig. 4. Complete circuit of the i.c. signal generator

COMPONENTS

Resistors

(All fixed values 1/4 watt 5%)

R1	6.8kΩ
R2	6.8kΩ
R3	20kΩ
R4	10kΩ
R5	270kΩ
VR1	100kΩ potentiometer, miniature skeleton
VR2	100kΩ potentiometer, miniature skeleton
VR3	10kΩ potentiometer, miniature trimpot
VR4	10kΩ potentiometer, miniature trimpot
VR5	10kΩ potentiometer, wire-wound
VR6	5kΩ potentiometer, linear

Capacitors

C1	1,000μF electrolytic, 40 V. Wkg.
C2	1,000μF electrolytic, 40 V. Wkg.
C3	0.1μF
C4	0.33μF close tolerance
C5	0.033μF close tolerance
C6	3,300pF close tolerance
C7	330pF close tolerance
C8	33pF close tolerance
C9	0.1μF
C10	0.1μF
C11	0.1μF
C12	0.1μF

Semiconductors

IC1	8038
TR1	BFY51
TR2	BFY51
TR3	2N2926 Brown
D1	12 volt zener type BZY88/C12
D2	12 volt zener type BZY88/C12
D3-D10	1N4001

Transformer

T1	Mains transformer, secondaries 20V 150mA (3VA), 20V 150mA (3VA), miniature (R.S. Components)
----	--

Neon


NE1	250 volt neon assembly, sub-miniature (R.S. Components)
-----	---

Switches

S1	1-pole 5-way rotary
S2	1-pole 3-way rotary
S3	d.p.s.t. toggle

Miscellaneous

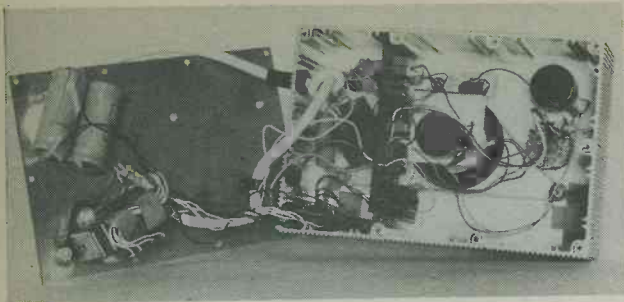Case (see text)
 2 terminals, 2 mm. (R.S. Components)
 4 knobs
 Veroboard, 0.1 in. matrix
 Pulley or tuning drum (see text)
 3 core mains lead
 2 TO5 heat sinks
 Nylon cord
 4 rubber feet.



The mains transformer and reservoir capacitors are mounted on the rear panel of the box. In this view the output terminals appear at the top and the tuning scale at the bottom

ratio of 1 to 15, with the 100Hz calibration frequency just mentioned corresponding to 10. Thus, Range 1 is 10 to 150Hz, with 100Hz appearing when pin 8 of the i.c. is at 0.8 Vcc. The subsequent ranges are 100Hz to 1.5kHz, 1kHz to 15kHz, 10kHz to 150kHz and 100kHz to 1MHz. Frequencies above 1MHz are outside the specified performance of the 8038. R3 is included in series with VR5 to ensure that the voltage applied to pin 8 does not fall below $\frac{2}{3}$ Vcc. When the voltage from VR5 slider is at its highest, i.e. the same as Vcc, the frequency is at its lowest, and when the voltage is at $\frac{2}{3}$ Vcc the output is at its highest frequency. Between these two extremes there is a linear frequency adjustment which enables a truly linear scale to be obtained.

VR1 and VR2 are pre-set potentiometers which are adjusted for minimum distortion of the sine wave output. VR6 acts as a simple attenuator for the final output.

CONSTRUCTION

Layout is not at all critical, and constructors may employ any reasonable method of assembly which they prefer. The author's unit is built in a Verobox measuring 158 mm. wide by 108 mm. high by 50 mm. deep.


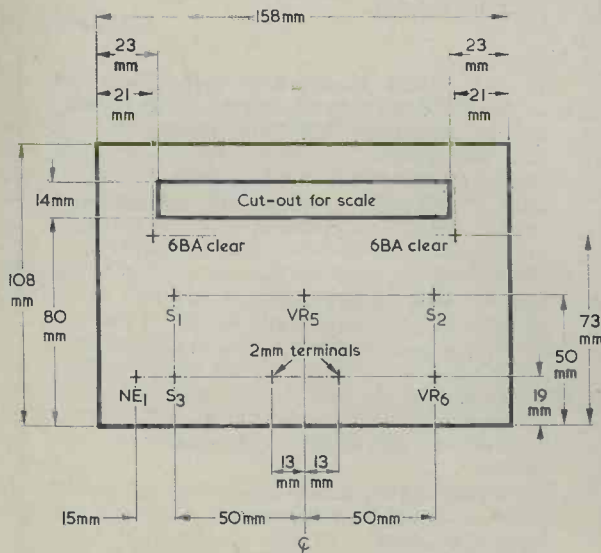


Fig. 5. Drilling details for the front panel, showing hole centres and the rectangular cut-out for the scale

This has the part number EVB/F/100-150/50, and can be obtained, in case of difficulty, direct from Vero Electronics Ltd., Industrial Estate, Chandlers Ford, Hampshire, SO5 3ZR. Fig. 5 gives details of front panel drilling. It will be noted that there is a rectangular aperture behind which is affixed a frequency scale. The two 6BA clear holes are for screws fitted with collars over which the scale cord can pass. The panel hole positioning is applicable for small or miniature controls. The two rotary switches employed by the author were made up from R.S. Components Miniature Maka-Switch kits, that for S1 employing a 2-pole 6-way wafer and that for S2 a 4-pole 3-way wafer. No connections are made to the unused poles. S1 was an R.S. Components sub-miniature toggle switch. Another R.S. Components part was the neon assembly, NE1. This was a sub-miniature neon assembly incorporating its own series resistor and intended for 250 volt operation.

Fig. 6 gives details of the scale cord assembly. In the author's case the pulley affixed to the potentiometer spindle was a 2 in. diameter Meccano pulley with its centre bush drilled out, this then being secured to the spindle with Araldite. An easier approach would consist of using a tuning Drum (Home Radio) instead of the pulley. The tuning drum has a central bush capable of being secured to a $\frac{1}{4}$ in. spindle, and it has a diameter of $1\frac{1}{4}$ in. The scale cord is standard nylon tuning drive cord and it is passed twice round the pulley or drum on the potentiometer spindle. The bracket on which the potentiometer is mounted is secured to the front panel at two holes corresponding with those for the output terminals. Mounting the terminals also holds the bracket in position. The scale is fixed at its two ends to the rear of the front panel with adhesive, suitable packing pieces being employed to space it back. The pointer is simply a piece of wire crimped onto the cord.

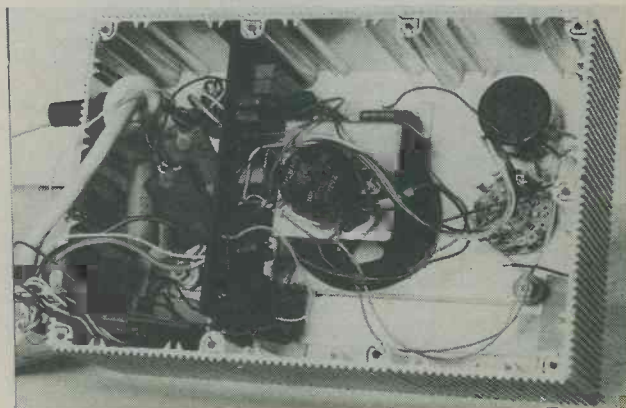The two sets of power supply rectifiers are assembled on the Veroboard panel shown in Fig. 7. This has a matrix of 0.1 in. Individual holes are not shown in the diagram as there is plenty of space for the components and precise positioning of these is unimportant. The copper strips should be cut at the points marked with crosses. Similarly, holes are not indicated in the Vero-



A closer look inside the case. Part of the pulley fitted to VR5 spindle and the scale drive assembly can also be seen

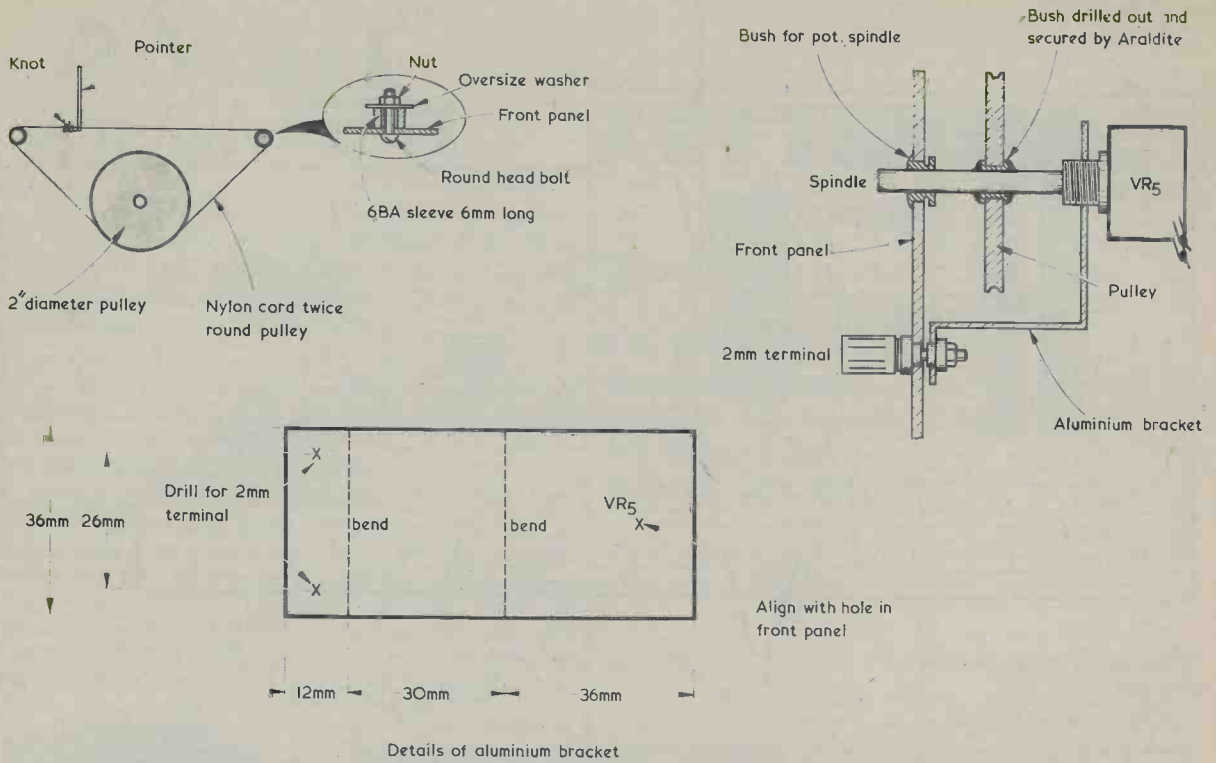


Fig. 6. The spindle of VR5 is coupled to the scale pointer. Details of the scale assembly and the bracket on which VR5 is mounted are given here

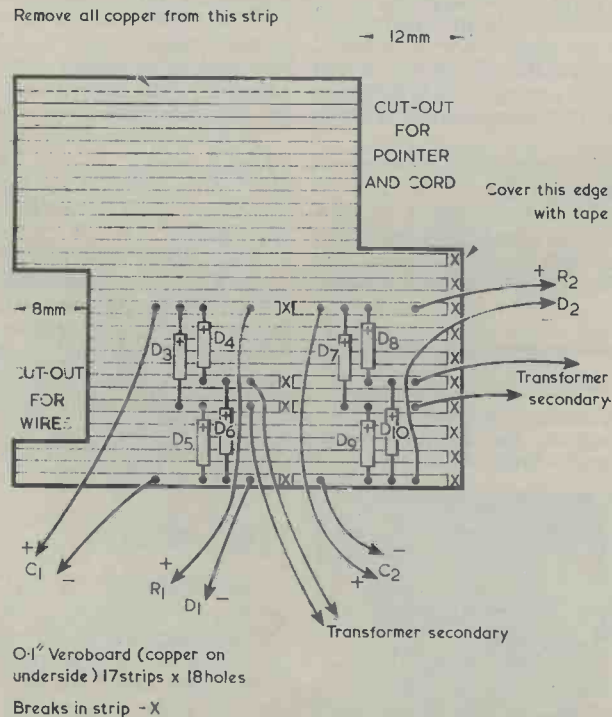


Fig. 7. The eight rectifier diodes are assembled on a small piece of Veroboard, as shown here. This view is of the component side of the board

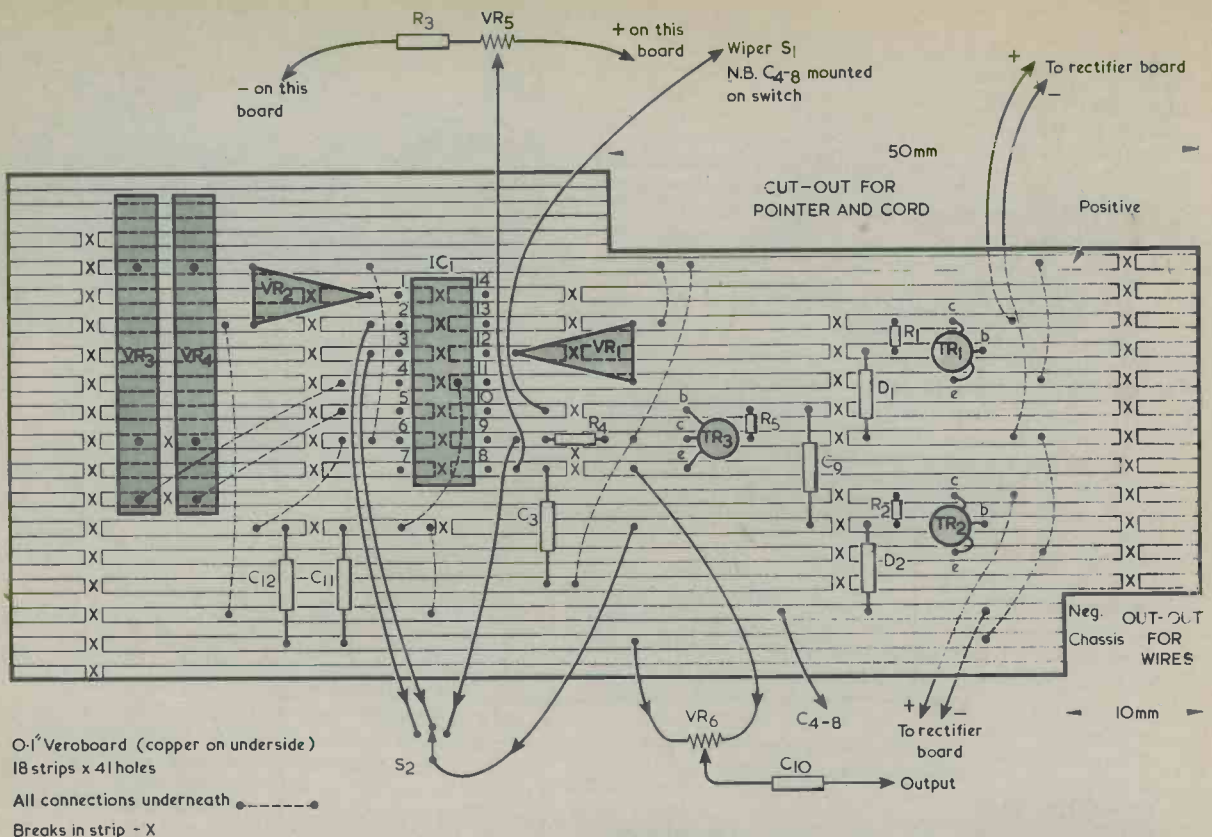


Fig. 8. The remaining small parts are fitted to a second piece of Veroboard. Again, the view is of the component side of the board

board assembly of Fig. 8. This Veroboard is, once again, of 0.1 in. matrix and strips are cut as indicated by the crosses. The two trim pots should be miniature types and it may be necessary to amend the Veroboard wiring to suit if their pins have different spacing to that shown in Fig. 8. TR1 and TR2 are fitted with TO5 heat sinks, these being the type H2 available from Henry's Radio, Ltd.

The large Veroboard panel is fitted, with the trim pots at the bottom, vertically between VR5 and S1, and the smaller board is positioned horizontally above the 6BA screw on the S1 side of the front panel. This board has one edge located in an internal Verobox groove. The other edge bears against the copper side of the larger


board and an additional means of securing it may be devised, if this is considered desirable.

The mains transformer and the two reservoir capacitors, C1 and C2, are fitted to the rear panel of the case in positions which ensure that they will not interfere with the internal components when the rear panel is fitted in place.

A 3-core mains wire is required and its earth lead should connect to the metal case. All mains wiring and connections in the unit must, of course, have the insulation and clearance which are needed at mains voltages.

The capacitors C4 to C8 are soldered direct to the tags of S1. These should all be close tolerance components. This is easy to arrange so far as C6 to C8 are concerned, since all three can be 1% silvered mica. The author was able to select C4 and C5 from wider tolerance components. If necessary, C4 could consist of a 1µF capacitor and a 0.5µF capacitor in series, and C5 of a 0.1µF and a 0.05µF capacitor in series. Wider tolerance capacitors can, of course, be employed at the expense of some accuracy of frequency calibration.

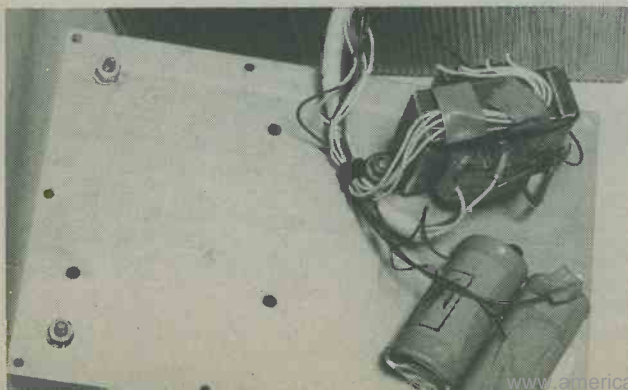The mains transformer is bolted to the rear panel. The two reservoir capacitors may be secured with a suitable clamp



NEXT MONTH

As is explained in next month's concluding article, setting up adjustments are required to VR3 and VR4 before they are finally soldered into circuit. Also, a modification may be required to the circuit incorporating VR1 and VR2 which results in these potentiometers being omitted. In consequence, the following article should be consulted before carrying out work involving these four potentiometers.

(To be concluded)

RADIO & ELECTRONICS CONSTRUCTOR


AMBIT

international 

A selection of products from the distributors of TOKO coils and filters, Larsholt FM tuner equipment and accessories, Kyodo ICs for radio, plus additional components and equipment - based on a theme of wireless.

In a hobby where it is getting increasingly difficult to locate 'specialized' components, AMBIT has established a specialist service that is concentrated on the topic of wireless; both entertainment stereo and communications applications.

A very broad range of coils for IF, RF and OSC applications is available by TOKO, and also a series of low cost ceramic and mechanical filters to sharpen the IF response of any design that uses either ICs, or discrete components. For MPX reception there are several accessories to ensure that reception is not hampered by unwanted hash or pilot tone - such as the BLR2007 filter shown here (use in audio line):-

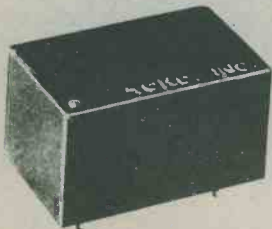

The BLR2007 measures 43x32x20mm, and is an IC filter for 19&38kHz, with a roll-off at 15kHz. It can easily be added into an existing decoder/tuner & being entirely passive, no power is required.

The all electric wireless

Motorola's new MVAM1 and MVAM2 varicaps have made electronic tuning of the MW a simple matter. AMBIT offers an AM MW radio tuner module with PCB, IC system for RF/OSC/MIX/IF, TOKO ceramic IF filter and coils. The complete kit costs £8.00 (ex VAT) and when used in conjunction with the unique 150mm slider potentiometer, the WS150-price £3.00, a really versatile and straightforward radio results. The long slider provides excellent scale resolution without recourse to geared drives, pointers etc. An alternative tuning mode might be provided with the IMI 9932 6 way preset potentiometer unit, which has been especially designed for varicap tuning at MF/VHF. (price £3.40). The MVAM1&2 are also available individually, priced £2.75 and £1.05 respectively. We recommend that you send an SAE for an up-to date price list and short form catalogue; or 40p will bring a full catalogue of TOKO coils, filters etc. plus many semiconductors and modules based on a theme of wireless - plus some other interesting linear ICs, like the 8038CC waveform generator (£3.10 with 12 pages of useful data.) VAT is extra, and generally 25%. Postage 20p per order. The address to write to is: 37 High Street, Brentwood, Essex. CM14 4RH. Callers are also welcome at the recently extended premises. The telephone number is (0277) 216029.

AUGUST 1975

LETTERS...

The Editor,
Readers' Letters,
Radio & Electronics Constructor,
57 Maida Vale,
London, W9 1SN.

Dear Sir,

In the December issue of your magazine you were kind enough to insert in your "Can Anyone Help?" feature a request for information concerning a South African manufactured radiogram which I have and for which I required the circuit.

I have just received from a gentleman there a copy of the circuit required, and an offer of any further assistance that I may require.

These are a few lines to express my grateful thanks for your valuable assistance, as without the help of this gentleman my set is useless. It also shows the extent of the circulation of your valuable magazine.

Again thanking you for your assistance, which was as you know, given free.

J. N. Shaw - Slough

Dear Sir,

About five years ago we formed a buying group among the small Electronic Component Retailers. The main object is to buy goods at cheaper prices by bulk buying, in addition, as we have no body to represent us over such thorny questions as V.A.T., we do this also. Our membership is at present twenty-five but for obvious reasons we would like to enlarge it. We have insufficient funds to advertise as our total revenue is derived from a modest £6 a year subscription.

I am confident that there are several hundreds who would join us if they knew we existed.

Would those interested please write to Alan Sproxtton, c/o Home Radio (Components) Ltd., 240 London Road, Mitcham, Surrey CR4 3HD.

Thanking you in anticipation,

A. Sproxtton - Mitcham

39

SHORT WAVE NEWS

FOR DX LISTENERS



By Frank A. Baldwin

Times = GMT

Frequencies = kHz

Now is the time for that late night and early morning (very early!) Latin American listening session, just before the summer ends and autumn commences. It is at this time of year that some of our best Dx log entries have been made.

It is probably true that most enthusiasts tend to favour the 60m band when Dxing for the LA's but a careful search over the 90m band may well result in even greater Dx rewards. A couple of good check points when ascertaining current conditions are 3325 for Radio Monogas, Venezuela, and 3375 for 'Radio Olinda, Pernambuco, Brazil. If these two stations are coming through at good signal strengths then that is the time to clap on the headphones and start operating. Of course, if you wish to be an unpopular member of the household you could use the speaker at 0200 or so!

Some of the LA stations on the 90m band being currently reported in the SWL press are - Radio Emisora Educacao Rural, Brazil on 2410; Ondas Panamericanas, Venezuela on 3215; La Voz del Napo, Ecuador, on 3280; Action Radio, Guyana on 3290; Radio Cultural, Guatemala on 3300; Puerto la Cruz, Venezuela on 3365; Cayenne, French Guyana on 3385; Radio Zaracay, Ecuador on 3390 and Radio Universidad, Venezuela on 3395.

Success on this band however is largely dependent on the selectivity of the receiver as commercial QRM abounds from end to end and this prerequisite will be in addition to the skill of the operator and the efficiency of the installation as a whole.

CURRENT SCHEDULES

● NETHERLANDS

"Radio Nederland", Hilversum, operate an External Service in English as follows - from 0200 to 0320 to North America on 6165; from 0500 to 0620 to North America (West Coast) on 6165 and 9715; from 0630 to 0750 to New Zealand on 11730; from 0800 to 0920 to Australia and New Zealand on 9715; from 0930 to 1050 to Europe on 5995, 6045 and 7210; from 1400 to 1520 to Europe, South and Southeast Asia on 5955, 6045, 11740, 15415, 17810 and on 21480; from 1830 to 1950 to Africa and Europe on 6020, 11730 and on 17700; from 2000 to 2120 to West Europe on 11730; from 2130 to 2250 to North America (not Sundays) on 9715 and 11730.

● AUSTRALIA

"Radio Australia", Melbourne, presents an Overseas Service in English from 0100 to 0300 to North America on 15320 and 17795; from 0400 to 0530 to Africa on

15290 and 17820; from 0700 to 0845 (in simple English) to Papua, New Guinea, on 9760, 11825 and 11885; from 0645 to 0745 to the U.K., Europe and the Pacific on 9570 and on 11765 from 0700; also from 0815 to 0830. From 1115 to 1245 to North America on 9580.

● SWEDEN

"Radio Sweden", Stockholm, radiates in English from 0230 to 0300 to North America on 9695 and 11705; from 1100 to 1130 to Europe and Africa on 9630 and 21690; from 1230 to 1300 to Africa, the Far East and North America on 15275, 15310 and on 21690; from 1400 to 1430 to North America and South Asia on 15240, 15310 and on 17770; from 1600 to 1630 to Europe and the Middle East on 6065, 9520 and on 15240; from 1830 to 1900 to Europe and Africa on 6065, 11790 and on 15240; from 2030 to 2100 to Europe, Africa and the Middle East on 6065, 9605 and on 11790 and from 2300 to 2330 to Europe and North America on 6035, 9605 and on 11705.

● SEYCHELLES

The "Far Eastern Broadcasting Association" (FEBA) Mahe, broadcasts to South Asia in English from 0600 to 0830 (Saturdays and Sundays) and from 0630 to 0830 (Mondays to Fridays) on 11915 and 15160; from 1530 to 1645 on 11810, 11865 and 15325. To the Middle East and Africa from 1745 to 1800 on Tuesdays and Wednesdays only on 11715 and 11865.

● PHILIPPINES

The "Far Eastern Broadcasting Company", Manila, operate in English from 0600 to 1000 (Sundays only) to South East Asia and Australasia on 15440 and 21515; from 0800 to 1000 (weekdays) on 11890 and 11920, also on 9505 from 0800 to 0900. To South East Asia from 1100 to 1130 on 11855; from 1245 to 1630 on 15440 and on 15300 from 1400; from 2330 to 0600 to South and South East Asia, Far East and Australasia on 9715 (from 0001 to 0100), 11855 (to 0001), 15440 (from 2330 to 2400, 0100 to 0600), 17810 (from 0001) and on 21515.

● PAKISTAN

"Radio Pakistan", Karachi, schedules a World Service to the U.K. from 1915 to 2145 on 7085 and 9460 (1915 to 2145 in Urdu, 2045 to 2100 in Sylheti, 2100 to 2145 in English). A World Service programme entirely in Urdu is directed to the U.K. from 0830 to 1100 on 15110 and 17665. A newscast read at slow speed is directed to West Europe from 1100 to 1115 on 15110 and 17665. Note however that the actual frequencies of

RADIO & ELECTRONICS CONSTRUCTOR

Radio Pakistan are apt to vary from nominal.

● **CHINA**

"Radio Peking", Peking, presents a programme in English to Europe from 2030 to 2130 on 6410, 6860, 7590 and on 11675; from 2130 to 2230 on 6860, 9030 and on 11675.

The Chinese Regional Services are of great interest to Dxers and the following information may assist in the logging of such transmissions.

Changsha, Hunan Provincial Service, from 0845 to 1620 and from 2105 to 0520 on Tuesdays and Fridays, from 2105 to 1620 (not Tuesdays and Fridays) on 4990 in Standard Chinese.

Kunming, Provincial Service No. 1, from 0920 to 1620 and from 2150 to 0600 (not Tuesdays and Sundays), from 2150 to 1620 (Tuesdays and Sundays) on 4760 in Standard Chinese.

Kunming, Provincial Service No. 2, from 1030 to 1605 and from 2155 to 0100 on 6937 in Standard Chinese and minority languages.

Kweiyang Provincial Service, from 0950 to 1605, 2115 to 0005 and from 0150 to 0620 on 3260 and on 7275 in Standard Chinese and Kweichow dialect.

● **NORTH VIETNAM**

Also of interest to Dxers are the following regional services -

Viet Bac, from 1130 to 1400 and from 2330 to 0200 on 3990, 6810 and on 7237.

Tay Bac, from 0930 to 1145, from 1200 to 1430 and from 0156 to 0400 on 4770, 6333 and on 9645. Note that all the regional service frequencies are subject to slight variations.

● **SOUTH VIETNAM**

Saigon Radio now radiates from 0400 to 1700 and from 2200 to 0300 on 4875, 6165, 7175, 7245, 9620 and on 9755.

● **CLANDESTINE**

"Radio Pathet Lao" now has two networks. The first, in Laotian, operates from 0900 to 1500 on 4250, 6200 and on 7310; from 2230 to 0230 on 4250, 6200 and on 7310; from 0400 to 0600 on 4250, 6200, 7310 and on 8660. The second network, in local languages (including French from 0045 to 0100) is from 1100 to 1415 and from 2300 to 0100 on 4600 and on 5100.

AROUND THE DIAL

On the higher frequencies our log shows the following entries.

● **NORWAY**

Oslo at 1403 on 21730 with a programme devoted to news of local affairs, Norwegian North Sea oil and shipbuilding industries.

● **SOUTH AFRICA**

Johannesburg at 1410 on 21535 with pop records programme, YL announcer.

● **ROUMANIA**

Bucharest at 1942 on 7225, news in English then talk about country life in Roumania.

● **ITALY**

Rome at 1935 on 7275 with identification, news of Italian domestic affairs then Italian/English language lesson.

● **CHINA**

Radio Peking at 1920 on the unlisted 6575 with programme in French, music and songs in the Chinese style.

● **ISRAEL**

Jerusalem at 2005 on 9815 with news in English of Israeli events and current foreign policy etc. Also heard in parallel on 12025.

For the Dixer, the following recent loggings may be of some interest.

● **CLANDESTINE**

"Voice of the Free Yemeni South" at 1725 on a measured 9962, OM with harangue in Arabic interspersed with local music. Schedule of this one is from 1630 to 2000 and the transmission is subject to jamming.

● **RHODESIA**

Gwelo at 1905 on 2425, programme of light orchestral music, just audible at times. This is the General Service with an evening schedule from 1700 to 2200.

Gwelo at 1820 on 3396, OM in English with a talk about composers and their music.

● **PAKISTAN**

Radio Pakistan at 1840 on 3329.5 (subject to nightly variations), local music, OM with songs, announcements with identification at 1859. Off suddenly at 1900 without National Anthem.

● **RWANDA**

Radio Rwanda, Kigali, at 1904 on 3330 (audible after Pakistan sign-off), OM in vernacular and local music heard through to 1024. This is the Home Service which has an afternoon/evening schedule from 1330 to 2100.

● **CAPE VERDE IS.**

Radio Clube Cabo Verde at 2044 on a measured 3886 (listed 3883), OM in Portuguese announcing dance music records, Schedule 2000 to 2400, power is 5kW and the channel is subject to severe commercial QRM.

● **CAMEROON**

Radio Buea at 2050 on 3970, typical African native music, songs by YL in vernacular.

● **INDONESIA**

Jakarta at 2200 on 4804.5, upsetting all previous experience by still being audible on odd occasions around this time, OM with news after series of chimes.

● **BURUNDI**

Radio Cordac at 1918 on 4900, YL with religious talk in French, OM with announcements at 1927, off suddenly, without National Anthem, at 1932.

● **ANGOLA**

Radio Clube do Huambo, at 1843 on 3345, OM with talk in Portuguese. Schedule is from 1900 to 2100 and the power is 10kW.

● **TANZANIA**

Zanzibar at 1848 on 3339, local orchestra with Arabic-type music, YL with songs. Announcements in Swahili and identification 1900. Schedule is from 1430 to 2000 and the power is 10kW.

NEW MULTIPLE TUNING DIODES

By J. B. Dance

Facts and figures on recently introduced varactor diodes having a very wide capacitance range.

VARICAP OR VARACTOR DIODES ARE WIDELY USED FOR tuning f.m. receivers, but up to the present time the only diodes suitable for tuning a.m. receivers have been rather expensive. For a.m. tuning it is necessary to have diodes with a capacitance swing of over 10:1, a maximum capacitance value of some hundreds of pF, a reasonably high Q factor and tight tolerances on the capacitance value at all voltages within the working range. The last requirement is difficult to meet.


The development and introduction by Motorola of a.m. tuning diodes is especially welcome, since it will facilitate the switched and remote tuning of a.m. receivers. In the past the f.m. section of f.m.-a.m. tuners has been tuned with a variable ganged capacitor, but the availability of the new diodes will enable a single potentiometer to be used for the varicap tuning of both the a.m. and f.m. bands.

THE MVAM-1

The MVAM-1 is a variable capacitance a.m. triple tuning diode which has recently been released. This device has a common cathode and three separate anodes in the 4 pin dual-in-line encapsulation shown in Fig. 1. Typical variation of capacitance value with applied voltage is shown in Fig. 2. The use of ion implantation techniques in the manufacturing process enables a guarantee to be given that the capacitance value of the three diodes in any one package will be matched to within $\pm 1.5\%$ throughout the whole of the working range (namely 1 volt to 25 volts).

The capacitance is between 400pF and 560pF at a reverse potential of 1 volt. The minimum capacitance swing is 15:1 over the bias range of 1 volt to 25 volts, but the typical swing is 26:1. The minimum Q factor is 150 at 1 volt and 1MHz, with a typical Q value of 575 increasing with applied voltage to over 1,000 at 4 volts and 4,000 at 20 volts.

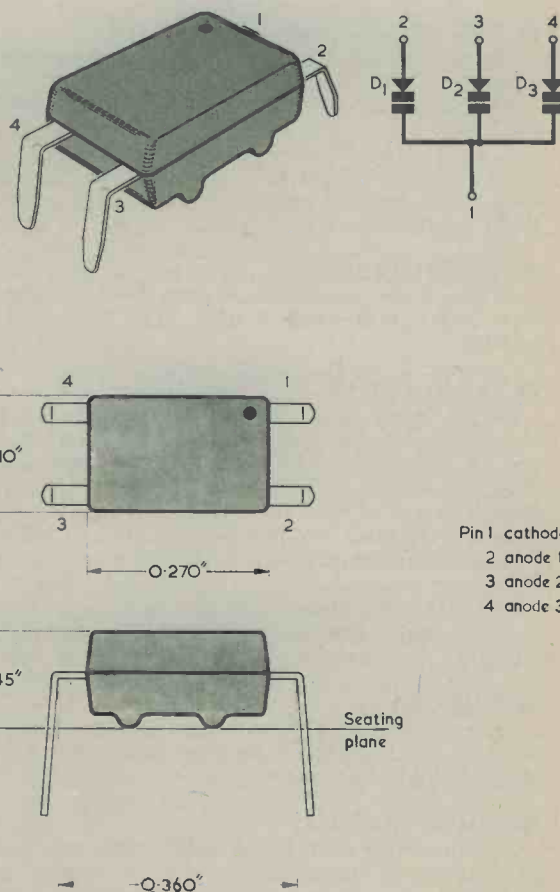The absolute maximum permissible reverse voltage (or minimum breakdown voltage) is 28 volts. The maximum reverse current is 0.15 μ A at 25 volts and 25°C, so the use of a 470k Ω series resistor will reduce the voltage across the diode by less than 0.1 volt. The temperature coefficient of capacitance is typically 435 parts per million per °C at 1 volt over the range -40°C to +85°C.



Pin 1 cathode
2 anode 1
3 anode 2
4 anode 3

Fig. 1. Basic details of pin layout and appearance of the MVAM-1 triple tuning diode. The dimensions shown are typical

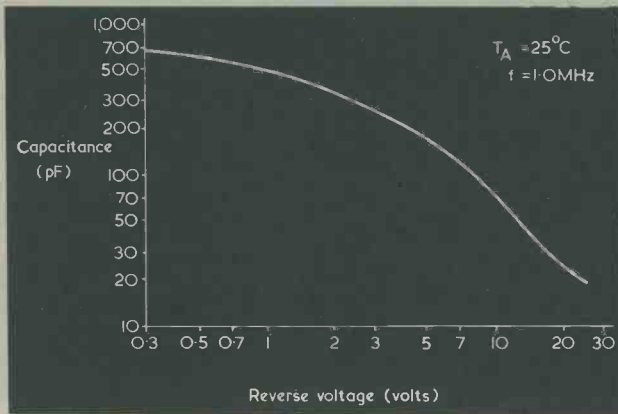


Fig. 2. Typical capacitance-voltage characteristic for an MVAM-1 diode

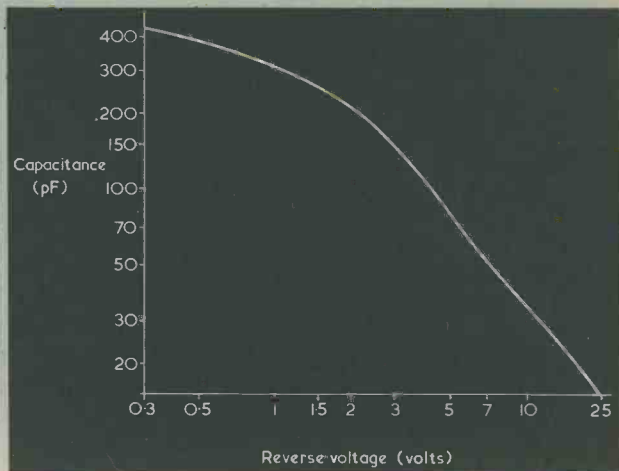


Fig. 3. Typical capacitance variation against tuning voltage for an MVAM-2 diode

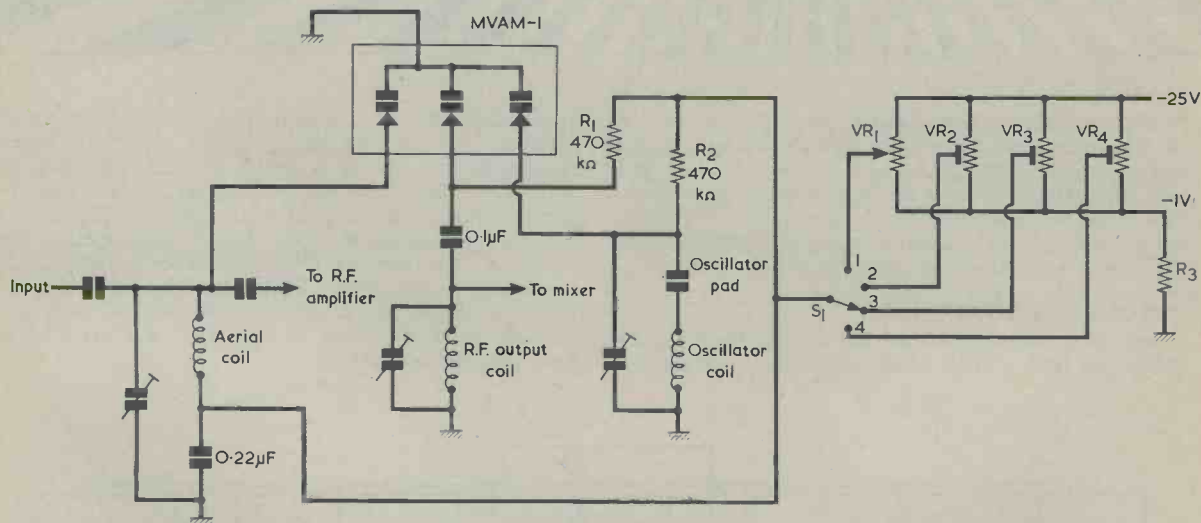


Fig. 4. Illustrating how the three diodes of the MVAM-1 may be coupled to the aerial, r.f. and oscillator tuned circuits of an a.m. receiver

THE MVAM-2

An even more recent device is the MVAM-2. This is a dual a.m. tuning diode in a TO92 encapsulation, the central lead being the common cathode. As shown in Fig. 3, the capacitance of each diode is somewhat lower than in the case of the MVAM-1. The capacitance swing has a minimum value of 18:1 for the range 1 volt to 25 volts, the two diodes of each diode being matched to within $\pm 1.5\%$ throughout the voltage range.

The MVAM-2 has a capacitance of $330\text{pF} \pm 10\%$ at 1 volt. The minimum Q factor and the breakdown voltage are the same as for the MVAM-1. Both the MVAM-1 and the MVAM-2 are available from Ambit International, 37 High Street, Brentwood, Essex, CM14 4RH.

RECEIVER CIRCUIT

The MVAM-1 may be used in the basic type of aerial, r.f. and oscillator circuit shown in Fig. 4. The switch S1 selects the tuning voltage from that provided by one of

the potentiometers. The writer has used a $100\text{k}\Omega$ Beckman 'Helipot' for continuous coverage and a number of pre-set potentiometers for switched tuning. The continuous tuning is provided when switch S1 in the circuit is set to position 1, and the pre-set tuning is given at positions, 2, 3 and 4. The tuning voltage is applied through the aerial coil to one of the tuning diodes and via R1 and R2 to the other diodes.

The oscillator voltage swing across the diode in the oscillator section should be kept small to prevent capacitance modulation of the oscillator frequency. Special circuits have been developed for this purpose. Work is being carried out on temperature compensation of circuits tuned by the diodes.

A Motorola Applications Engineering report has shown that the MVAM-1 can be used in high quality car radio receivers which are smaller and more easily manufactured designs, whilst being cost competitive. A d.c. to d.c. converter has been employed to generate a negative tuning supply voltage from the car supply. ■

ELECTRONIC SIREN

By M. Harding

This circuit employs two multivibrators and a linear integrator to produce a tone whose frequency rises and falls smoothly in the manner of a siren.

THE CIRCUIT TO BE DESCRIBED IS CAPABLE OF PRODUCING a sound very similar to the well-known siren wail of an American police car. As such it is suitable for use in any application where a distinctive alarm is required. The range of application could vary from that of intruder alarms to novelty circuits and party games. In fact the limit is only set by the constructor's ingenuity.

CIRCUIT DESCRIPTION

The circuit required is one that will produce a slowly rising and falling pitch which, of course, characterises

the well-known siren sound. Fig. 1 shows the circuit configuration. It can be seen that the main sound producing circuit is a multivibrator consisting of transistors TR4 and TR5. However, it will also be noticed that the base bias resistors R8 and R9 are not returned to the supply rail but are connected to the collector of transistors TR3. This is for a reason that will be explained shortly. Transistor TR3 functions as a linear integrator and produces a triangular waveform at its collector in response to a square wave drive at its base bias resistor, R5.

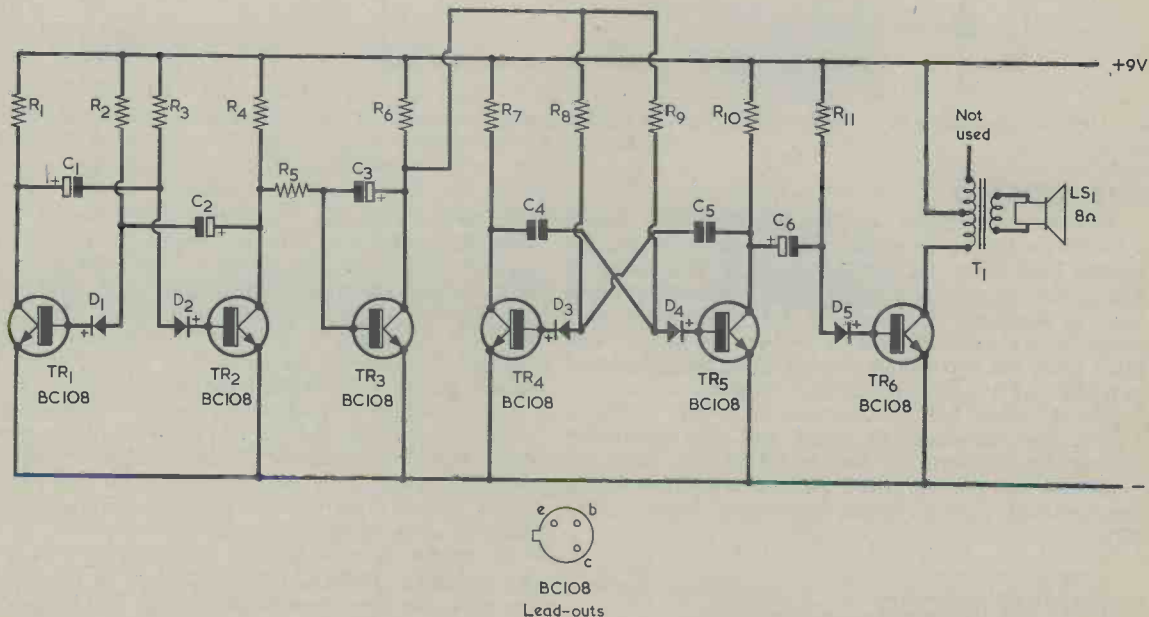


Fig. 1. The circuit of the electronic siren. This produces a tone which continually rises and falls in frequency

The square wave drive required by the integrator is provided by the multivibrator consisting of transistors TR1 and TR2. This is a low frequency multivibrator and completes one cycle in approximately 4 seconds. The waveform at TR3 collector is shown in Fig. 2, and it can be seen that the mean potential, with the component values specified, is just over 3 volts. When the square wave drive is applied from the low frequency multivibrator the collector potential runs smoothly up and down between the limits indicated in Fig. 2.

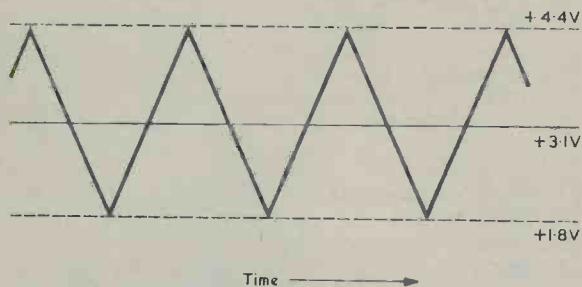


Fig. 2. The waveform produced at the collector of TR3

This voltage is used to frequency modulate the main tone producing multivibrator comprising TR4 and TR5, and thereby generate the characteristic rising and falling pitch of the siren sound. The pitch range produced by this circuit arrangement is approximately 660Hz to 1.2kHz, rising for about 2 seconds and falling for about 2 seconds.

The frequency modulated square wave output from the collector of TR5 is fed to the base of TR6 which acts

as a switching mode output stage. This transistor is transformer coupled to an 8Ω speaker using an Eagle LT700 miniature output transformer. Only half the centre-tapped primary winding is employed.

Five silicon diodes, D1 to D5, are included in the circuit in series with the bases of TR1, TR2, TR4, TR5 and TR6. These diodes ensure that the maximum reverse base voltage rating of 5 volts for the BC108's employed is not exceeded, and they do not have any other significant effect on circuit operation. The reverse base voltage rating would not be exceeded during normal operation of TR4 and TR5, but could be immediately after switch-on.

CONSTRUCTION

The author employed a compact form of construction and assembled the components on a small piece of 0.1 in. pitch plain Veroboard having 29 by 16 holes. The layout is shown in Fig. 3. Component lead-outs are simply passed through the board and then linked together, short pieces of 22 s.w.g. tinned copper wire being added where necessary to complete connections. Sleeving is passed over any leads where there is a risk of short-circuit to other wires.

It should be noted that the layout is in no way critical and that a less cramped form of assembly can be adopted, if desired.

The average current consumption from the 9 volt battery was 7mA with an 8Ω speaker connected. Because the output stage is operating in a switching mode it is highly efficient and the sound level from a small 3 in. speaker is adequate for many applications. A 3Ω speaker may alternatively be used, whereupon the current consumption increases to about 10mA and there is a consequent increase in the volume of the output.

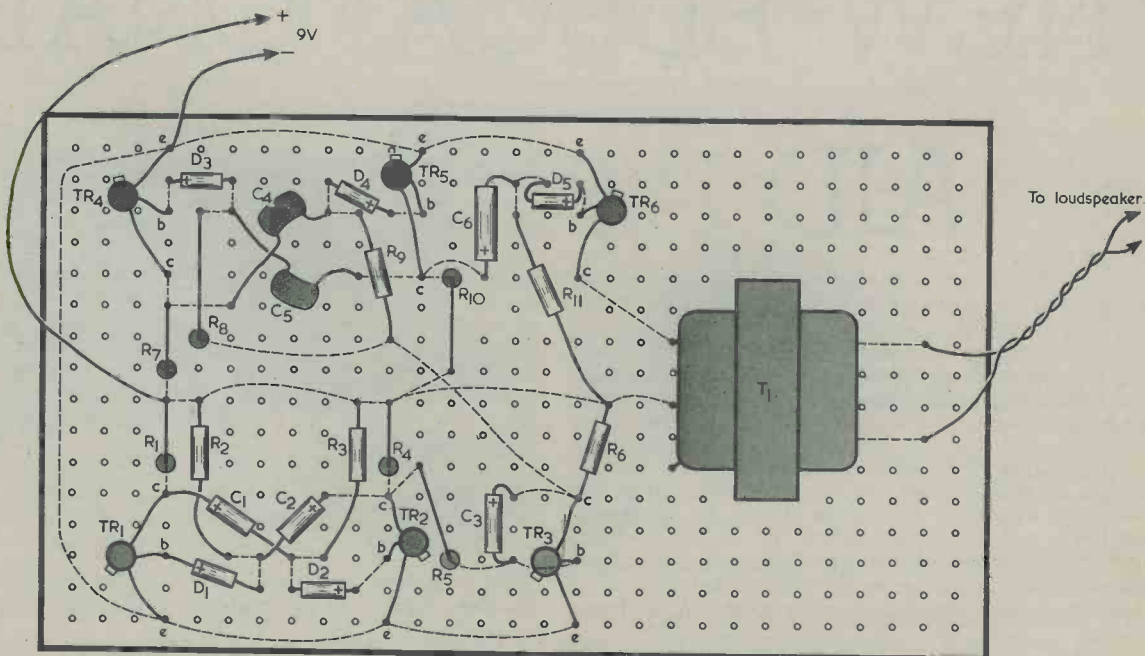


Fig. 3. The layout employed by the author. Components are assembled on a piece of plain Veroboard, with wiring under the board being indicated in broken line

Resistors

(All $\frac{1}{4}$ watt 5%)

R1	10k Ω
R2	120k Ω
R3	120k Ω
R4	10k Ω
R5	560k Ω
R6	5.6k Ω
R7	4.7k Ω
R8	39k Ω
R9	39k Ω
R10	4.7k Ω
R11	560k Ω

Capacitors

C1	20 μ F electrolytic, 10 V. Wkg.
C2	20 μ F electrolytic, 10 V. Wkg.
C3	1 μ F electrolytic, 10 V. Wkg.
C4	0.01 μ F plastic foil
C5	0.01 μ F plastic foil
C6	8 μ F electrolytic, 10 V. Wkg.

COMPONENTS

Transformer

T1	Output transformer type LT700 (Eagle)
----	---------------------------------------

Semiconductors

TR1-TR6	BC108
D1-D5	1N4148

Loudspeaker

LS1	8 Ω speaker, 3 in. round (see text)
-----	--

Miscellaneous

Plain Veroboard, 0.1 in. pitch
9 volt battery
Battery connectors
Wire, etc.

This has proved to be a useful circuit for novelty applications and for more serious alarm applications. When the output is fed into a public address system the


unit forms a useful 'stage effects' arrangement for appropriate productions. ■

NEW EDUCATIONAL AID

A low-cost analogue computer which can be used in schools and colleges for teaching the basic principles of analogue and hybrid computation has been developed by Limrose Electronics.

The Analog Tutor which is available in two sizes for student use and classroom demonstration respectively, uses solid-state electronics throughout. It has six operational amplifiers and six potentiometers and has many design features in common with large analogue computers. These advanced facilities include independent mode control of the integrators, single shot and repetitive operation and remote control.

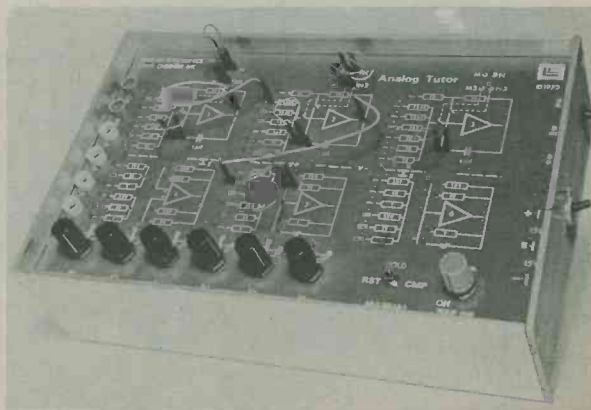Up to third order differential equations can be solved on a single unit and two or more units can be connected together for simulating higher order systems. Reaction kinetics, feedback control systems and social and economic systems



such as population growth are but a few examples of problems which can be simulated on the Analog Tutor.

An instruction book dealing with the subject from first principles entitled "Introduction to Analogue Computers" accompanies the Analog Tutor. Prices from £99. Further information can be obtained from Limrose Electronics Ltd., 8-10 Kingsway, Altrincham, Cheshire, WA14 1PJ.

QSL CARDS

How To Collect Them

By Steve A. Money

A varied collection of QSL cards will impress both friends and family. Here are some notes on how to set about this interesting side-line of short wave listening.

ONE OF THE FASCINATING SIDE ACTIVITIES OF SHORT WAVE radio listening is collecting QSL cards. What is a QSL card? For the uninitiated a QSL card is a printed postcard, or a letter, sent out by a short wave broadcast or amateur radio station in reply to a valid reception report sent in by a listener. The QSL verifies the report and confirms that the listener has received the station in question.

It seems that the practice of confirming radio contacts by exchanging QSL cards was originated by amateur radio operators. Possession of the appropriate QSL card was at least one way of convincing fellow enthusiasts that you really had made contact with some rare or exotic DX station. Later the international short wave broadcast stations also began to send out QSL cards to confirm reports from their listeners. Today most of the short wave broadcast stations around the world will confirm listener reports by sending either a QSL card or letter.

SIGNAL REPORTS

To obtain a QSL from a broadcast station you must first of all be able to hear the station. Then you need to send in a reception report on the transmission you heard. Many of the international broadcast stations transmit programmes in the English language at some time during the day and these should be easiest for making a report.

If possible, listen to the station for half an hour or more. If there are other frequencies in use, it may be worth-while to check for signals on these alternative frequencies as well. Note how strong the signal is and whether it is fading or not. Make a note also of any interference or noise on the signal.

In making the signal report you can use one of the signal report codes, such as the SINPO code. In this code each letter corresponds to one particular aspect of the reception conditions and is graded from 1 to 5. Firstly, the S stands for carrier Strength and runs from

S1 (just audible) up to S5 (excellent). The I is for Interference from other stations on the same or adjacent channels. Here the five steps proceed from I1 (very severe interference) up to I5 (nil interference). Noise, either from electrical storms or from local electrical equipment, is represented by N and the steps are the same as with I for Interference. Fading is covered by P, for Propagation disturbance, and ranges from P1 (very severe fading) to P5 (nil disturbance). Finally, the Overall reception conditions are assessed and graded from O1 (unusable) to O5 (excellent). As an example a local medium wave station might rate 55555 and a weak signal with bad fading underneath a jamming signal would rate 11111.

Although the SINPO code is a convenient shorthand way of indicating the signal conditions it is as well to make a full comment on each of the aspects of signal reception. For instance you might point out that there was some bad interference for a time from an adjacent channel station and that at another point in the programme the signal faded out almost completely for a minute or so. Try to give a word picture of how well or how badly the station was being received. If possible, attempt to provide a report covering two or three periods of reception on different days since this will give the station engineers a much better picture of the reception conditions. Of course with some of the rarer and more difficult to receive stations you may only get one chance but it is still worth-while to check again on the following day before sending the report, just in case the signal is still there.

PROGRAMME DETAILS

Don't just send in a bare signal report. In order to be able to verify that your report is genuine the station staff will need details of the programme you heard in order to check them against the entries in the station log. It has been known for some unscrupulous listeners to simply look up the station frequency and programme



AMATEUR STATIONS

In general amateur radio stations are not as interested in listener reports as their broadcast counterparts. Many of them will however send you their QSL card in return for a useful report. Note who the station is in contact with and the call signs of any other stations calling him. Basically the signal report can be much the same as that for a short wave broadcast station except that there are no programme details.


Amateur station addresses are listed in 'Amateur Radio Call Book' which is published annually by the Radio Society of Great Britain, 35 Doughty Street, London, W.C.1. Most countries also have QSL bureaux run by the national radio club which will handle cards for amateurs operating from that country.

PENNANTS

Many broadcast stations, especially in South America where the practice started, send listeners a pennant as well as their QSL card. These pennants come in various sizes and types from small paper ones 4 inches long up to large screen printed cloth ones more than a foot long. Usually they are brightly coloured, triangular in shape and carry the station name, call sign and slogan.

Some stations will send a pennant with the QSL card as a matter of course but others will send one only if you ask for it. Send in a good comprehensive report and mention that you collect pennants and would like to add theirs to your collection and you will probably have one sent to you.

In Britain it is possible to receive broadcasts from more than 120 different countries and out of these at least a hundred broadcast programmes in English at some time during the day. Naturally, not all of these stations are easy to receive and, in fact, some will require a lot of patient listening and a few late nights before you finally hear them. It is something of a thrill, though, when one night you suddenly hear the elusive station you have, perhaps for months, been searching for. So now all you have to do is start listening and send out those reports and soon you too can have QSL cards from around the world arriving in your mail. ■

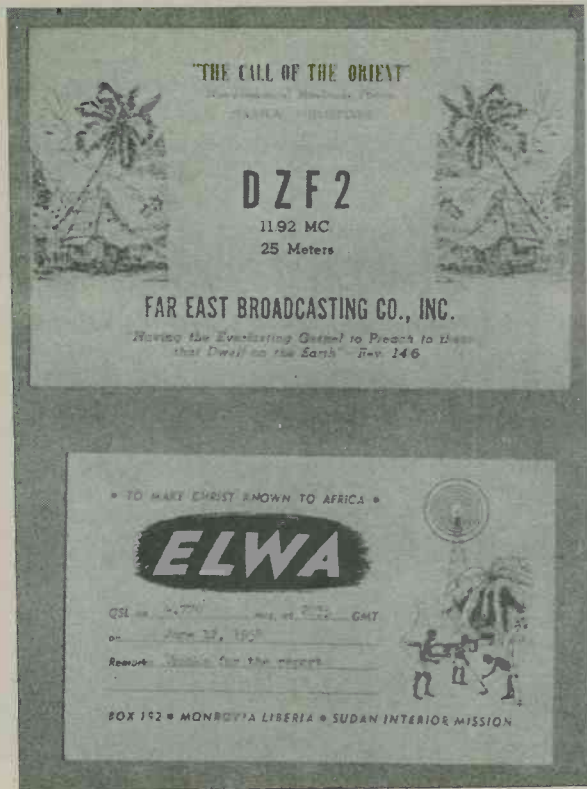

Two further examples of the QSL cards which may be obtained by the short wave listener

to the short wave listener since it gives frequencies and operating schedules for all radio and television stations around the world as well as much other useful information. It may be obtained from The Modern Book Company.


BOOK REVIEW

RADIO CONTROL HANDBOOK. By Howard G. McEntee. 326 pages, 215 x 130 mm. (8½ x 5½ in.). Published by Foulsham-Tab Limited. Price £1.90.

This is an American text with an introductory chapter for English readers, and it deals in considerable detail with radio control techniques intended mainly for use in model aircraft. The approach is largely towards the hobbyist who likes to make up his own mechanisms and electronic assemblies, and there are many mechanical and circuit diagrams to illustrate what is required here.

Amongst the subjects dealt with are sequence control systems, pulse proportional control systems, engine speed control, expanding proportional and multi-control systems, servos, receivers, transmitters, power supplies, relays, test instruments and component installation. The author is clearly an enthusiast in his field and the text is full of practical advice arising from his own experiences. The American radio control scene closely matches that over here, and the book will be of interest to the British RC devotee.

In your workshop

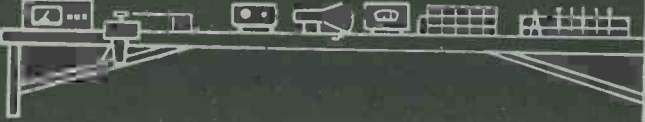

As is their custom at August, Dick and Smithy leave the Workshop this month and sally forth into the big wide world outside. Despite their circumstances, Smithy still takes the opportunity to expound to his assistant on circuits in which transistor base-emitter junctions have to be given particular consideration.

APPREHENSIVELY, DICK FOLLOWED Smithy through the doorway.

He looked around the small room they had entered. A worn sofa was ranged against one wall together with several small chairs. On one of these sat a young man engrossed in a copy of *Penthouse* magazine. A large anchor was tattooed on each of his wrists.

Facing Dick was a closed green door. Two of the chairs were positioned on either side of a small table; Smithy settled himself comfortably on one of these and Dick perched uncomfortably on the edge of the other. He glanced sideways and saw, through the torn lace curtain of the only window in the room, an unkempt garden. An emaciated cat prowled haphazardly through the weeds.

CHANGEOVER RELAY

"Is this all we have to do then, Smithy?" Dick whispered to the Serviceman. "Just walk in like this?"

"That's right," confirmed Smithy heartily. "I made a phone call yesterday to set it all up."

Dick gazed nervously around the room.

"And what happens next?" he went on, glancing uneasily at the green door. "Do we sit here and wait?"

"That's right," grinned Smithy. "Everybody takes their turn here. You'll be seeing the action soon enough."

Dick heaved a tremendous sigh.

"Well," he remarked tentatively, "it makes a change from the Workshop."

"True enough," agreed Smithy, "although I must admit that the Workshop has been rather congenial recently so far as I've been concerned."

"How's that?"

"For one reason or another," said Smithy, "I've found myself knocking

up gadgets for people. I love dreaming up gadgets because it makes such a pleasant break from ordinary servicing."

"What sort of gadgets?"

"Oh, simple little things," replied the Serviceman. "For instance, one customer wanted me to make a mains eliminator for a rather expensive transistor radio he's got. The unusual bit was that he wanted the supply to switch automatically to battery operation whenever there was a power cut or the mains supply was disconnected."

"A job like that," remarked Dick, hooked as ever by the discussion of any electronic matter, "seems to call for a relay."

"You *could*," conceded Smithy, "use a relay. This would have its coil connected across the output of the mains section of the supply. If it had a set of changeover contacts these could

switch the supplied equipment to the mains section when the coil was energised and to the battery when there was no output from the mains supply." (Fig. 1.)

"Well, you couldn't have anything much simpler than that," commented Dick. "Are there any snags in such a design?"

"There are two minor points which might be considered shortcomings," stated Smithy. "To start off with, people nowadays tend to look on relays as being old-fashioned, because most of the things they do can be done more neatly, and without moving parts, by semiconductors. Still, there are plenty of modern relays being offered for sale these days both for industrial and amateur use, so it would seem that the relay is by no means as outdated as all that. Also, a relay does have a *complete* switching effect. If a

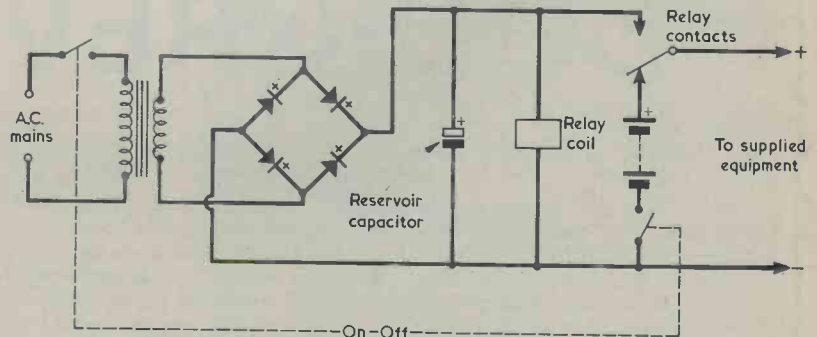


Fig. 1. A simple mains-battery power supply. The relay contacts are shown in the de-energised position, and the two switches are ganged to form a double-pole on-off switch. In the absence of a mains supply the relay de-energises and couples the battery to the output

relay contact set opens a circuit, that circuit is well and truly open. When, on the other hand, a semiconductor device opens a circuit there is still usually a small leakage current flowing, even if it's only a small fraction of a microamp."

"Humph," grunted Dick. "It sounds as though the disadvantages and advantages more or less cancel each other out. What's the second shortcoming of a relay in this power supply circuit?"

"The second snag," said Smithy, "is that the voltage fed to the supplied equipment can fall to a small value before the relay de-energises after the cessation of the mains supply, with the result that the supply voltage does not change instantaneously to the battery. Instead, it will fall to a relatively low value for a moment until the relay releases and the battery takes over. This could be a serious disadvantage if the supplied equipment has to have a continuous supply voltage."

"Fair enough," said Dick. "Can you overcome this second snag?"

"Without the relay it can be done quite easily," replied Smithy. "All you need to do is to couple the battery to the rectified mains supply via a silicon rectifier. If the rectified mains voltage is a little higher than the battery voltage the rectifier in series with the battery will be reverse biased when the mains supply is present. If the mains supply is removed, the output voltage to the supplied equipment will fall slightly until the rectifier starts to conduct, whereupon the supply current will then be provided by the battery. There will be a drop in output voltage when changing from mains to battery, after which the output will remain steady at the voltage provided by the battery. There won't be the intermediate fall to a relatively low voltage that occurs with a relay."

SWITCHING DIODE

At that instant there came a rattling sound from the handle of the green door. It turned, and the door swung slowly open to reveal a thick-set man of about thirty dressed in a jersey and jeans. He closed the door behind him, stretched luxuriantly then, with a slightly swaying walk, left by way of the door through which Dick and Smithy had entered. Open-mouthed, Dick gaped after him.

The green door opened again and a middle-aged woman with greying hair and a hard gaze looked out into the room. She gave a nod of recognition on seeing Smithy, then turned her eyes to the young man with the *Penthouse* magazine. She curled her finger and beckoned him towards her. Rising, he dropped his magazine on the table between Dick and Smithy, gave the now petrified Dick a knowing wink, then passed out of view. The green door closed behind him.

"Ye gods," breathed Dick. "It's a bit like a production line, isn't it?"

"I suppose," agreed Smithy, "it is a

bit soulless."

"I feel," remarked Dick unhappily, "as though someone's pouring cold water down my spine."

"There's nothing to be nervous about."

"It's all very well for you," complained Dick. "Don't forget that this is the very first time I've ever been here."

"There has," stated Smithy philosophically, "to be a first time for everything."

"Tell me," asked Dick, suddenly curious, "how long have you been coming here?"

"Oh," replied Smithy thoughtfully, "let me see now. I should say I've been popping in here off and on over the last fifteen years or so."

"Do you come often?"

"That," said Smithy, "depends on how I feel. If things are going well with me there might be quite a spell between visits. But whatever happens I make a particular point of coming here at least once every six months. Dash it all, your health can suffer if you don't pay attention to these things."

Dick threw a glance of reluctant admiration at the Serviceman.

"One thing I must say about you, Smithy," he remarked with thinly veiled respect, "you certainly know how to get yourself organised."

"If," replied Smithy loftily, "I can't get myself fixed up nobody else is going to do it for me. Now, let's get back to that battery rectifier circuit."

"Rectifier circuit?"

"I was telling you how you could couple a battery into a mains power supply by way of a series rectifier."

"Cripes, I'd forgotten all about that"

"Well, you'd better remember it again."

Smithy pulled the *Penthouse* magazine towards him, turned its pages until he found one with a fairly large clear area, then drew a ball point pen from his pocket. He scribbled out a circuit on the magazine page. (Fig. 2.)

"Here's the basic idea of the power

supply," he went on. "The mains part of the supply is quite straightforward and uses a bridge rectifier feeding into a reservoir capacitor. Any other sort of rectifier and reservoir capacitor arrangement will do equally well. The only important requirement is that the smoothed voltage from the reservoir capacitor must be equal to or greater than the battery voltage. Since the rectifier is a silicon type it will need a forward voltage of about 0.6 volt across it before it conducts. In consequence the rectifier is reverse biased when the rectified mains voltage is present, and the battery is then effectively out of circuit. As soon as the rectified voltage disappears, the voltage across the reservoir capacitor drops until it is 0.6 volt lower than the battery voltage. The series rectifier then conducts and the battery provides all the current for the supplied equipment. Should the mains come back on again the voltage across the reservoir capacitor will rise, and the rectifier in series with the battery will cease to conduct. All the power will then be provided once more by the mains circuit."

"That's neat," commented Dick. "Just a minute, though! Isn't the battery likely to discharge through the bridge rectifier when there's no mains supply?"

"It can't do that," said Smithy. "If you trace the circuit through you'll find that the bridge rectifier diodes are reverse biased so far as current through them from the battery is concerned."

LEAKAGE CURRENT

Dick passed a finger along Smithy's sketch, tracing the circuit from the battery back to the bridge rectifier.

"Yes, I see what you mean," he remarked. "What about leakage current through the rectifier in series with the battery when the mains is on?"

"This current will be very small," said Smithy. "Actually, it's advisable to keep it as low as possible because the leakage current represents a charge

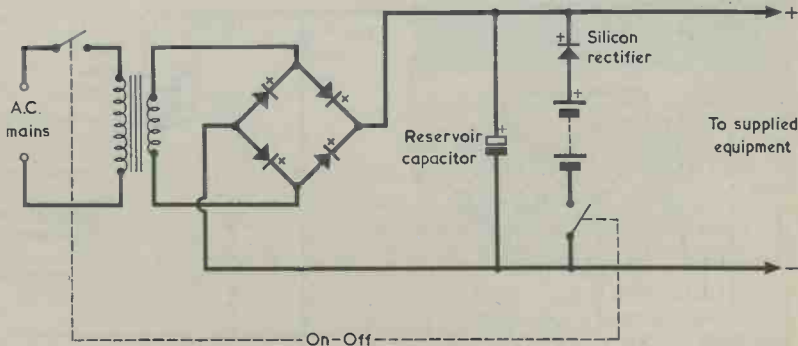


Fig. 2. Another mains-battery supply. On cessation of the mains input the voltage across the reservoir capacitor falls to a level which allows the silicon rectifier in series with the battery to become conductive. The battery then provides the output current

current for the battery. It's a little difficult to be precise about leakage current because all silicon rectifiers have very low leakage current figures when they are reverse biased. Nevertheless, a good choice here would be the BY100, which has a typical reverse current well below $0.1\mu\text{A}$ at room temperatures. The fact that this is a high voltage type doesn't prevent its being used in this present circuit. It also has a reasonably high forward current rating and this will enable it to withstand switch-on current surges if the circuit is switched on with the mains off. Initial switch-on current will in any case be provided by the battery even if the mains is present because it will take a moment or so for the voltage across the reservoir capacitor to reach full value from the bridge rectifier. Switch-on current surges will, of course, be due to the high value electrolytic capacitor which will in almost all cases be connected across the rails of the supplied equipment."

"If the leakage current in the series silicon rectifier charges the battery," asked Dick, "won't there be a slight risk that the battery will overcharge, so that it could generate internal gases and explode?"

"That is just about possible," agreed Smythy, "and the risk has to be mentioned when the circuit is discussed. In practice, the short stabs of current taken from the battery on switch-on should cancel out the minute leakage currents in the rectifier later on. If the circuit is continually switched on with the mains applied it might be advisable to disconnect the mains occasionally, just to draw a little current from the battery."

Smythy proceeded to sketch out another circuit. (Fig. 3.)

"Hullo," said Dick, "what's this?"

"It's another mains-battery power supply circuit," replied Smythy. "It's an extremely simple and effective circuit if you don't object to a little current being drawn from the battery when the mains supply is present. The output voltage is approximately the

same both for mains and battery operation and the battery also gives automatic electronic smoothing."

"This sounds interesting," said Dick. "How does it work?"

"Well," said Smythy, "let's start off by saying that we have the mains supply available. The mains part of the circuit is arranged so that the voltage across the reservoir capacitor is at least a couple of volts higher than the battery voltage. Under these conditions the transistor in the circuit functions as an emitter follower, and a voltage which is 0.6 volt lower than battery voltage appears at the output. Nearly all the output current is provided by the mains part of the circuit, with only a small current from the battery flowing into the transistor base."

"How small a current?"

"Let's say that the transistor has a current gain of about 50. This is what we could expect in practice because we would be using a power transistor here. If the supplied equipment consumes 50mA the current drawn from the battery is then only 1mA."

"That seems reasonable enough," said Dick. "What happens when the mains supply is cut off?"

"The collector voltage for the transistor disappears," replied Smythy, "and the total current consumed by the equipment is then drawn from the battery through the base-emitter junction of the transistor. This now acts as a forward biased silicon rectifier, and the output voltage is still 0.6 volt lower than the battery voltage. The battery voltage will drop a little when the full current is drawn from it because of its own internal resistance. But there will be no cessation of output voltage at all when the mains is cut off."

"Where," asked Dick, "does the automatic smoothing bit come in?"

"It's given," explained Smythy, "because the battery represents a low impedance reference voltage source coupled to the base of the transistor. Even if there's a ripple across the reservoir capacitor, this won't appear at the emitter of the transistor. So you

have a circuit with the advantage of extreme simplicity, the only disadvantage being that the battery gradually runs down, although at a much lower rate than would occur if it supplied the equipment directly."

POWER TRANSISTOR

"That certainly represents a neat approach," commented Dick. "Blimey, I've just thought about something!"

"What's that?"

"Why in heaven's name are we rabbiting on about electronics in a place like this?"

"You," retorted Smythy drily, "would be nattering about electronics on your death-bed. Or, come to think about it, on any other bed."

Dick's eyes darted nervously towards the green door.

"That chap," he said querulously, "seems to have been in there quite a bit."

"There's no exact time," explained Smythy. "With some people it's quick and with others it's slow. Aren't you glad you came?"

"I think so," said Dick dubiously. "You certainly went to a lot of trouble persuading me."

"That was entirely for your own benefit," stated Smythy. "There's no reason why you shouldn't enjoy the same facilities that I do. Also, I know that you'll be in capable and experienced hands here."

Dick blenched, then turned hastily to the circuit Smythy had drawn in the *Penthouse* magazine.

"It's the waiting that's hard to take," he said. "Let's get back to that circuit of yours, even if only to pass the time."

"Fair enough," replied Smythy. "Now, this last circuit arrangement is the one I employed for the customer I was telling you about. I used a small heater transformer in the mains part of the circuit. This had two 6.3 volt windings which I connected in series to give 12.6 volts. Since a heater transformer secondary has a much lower resistance than is given in transformers specifically intended to supply low current transistor equipment I also inserted a 10Ω surge limiting resistor in series with the bridge rectifier. This isn't entirely essential but it does reduce reservoir capacitor switch-on surge currents. The rectifiers were 1N4002's. The rest of the circuit is the same as the theoretical one. The battery is a PP9 and the transistor a 2N3055."

As he spoke, Smythy drew a further circuit giving the component details he had outlined. (Fig. 4.)

"A 2N3055?" repeated Dick incredulously. "That's using a whacking great sledgehammer to crack a very tiny nut, isn't it?"

"The 2N3055 is considerably under-run," agreed Smythy. "The only reason for using it here is because its base-emitter junction will stand the high switch-on current surges from the

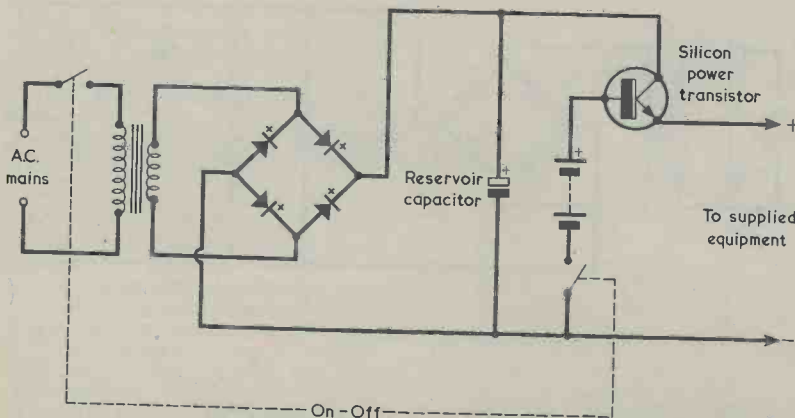


Fig. 3. In this circuit the output voltage is 0.6 volt less than battery voltage both on mains and battery operation

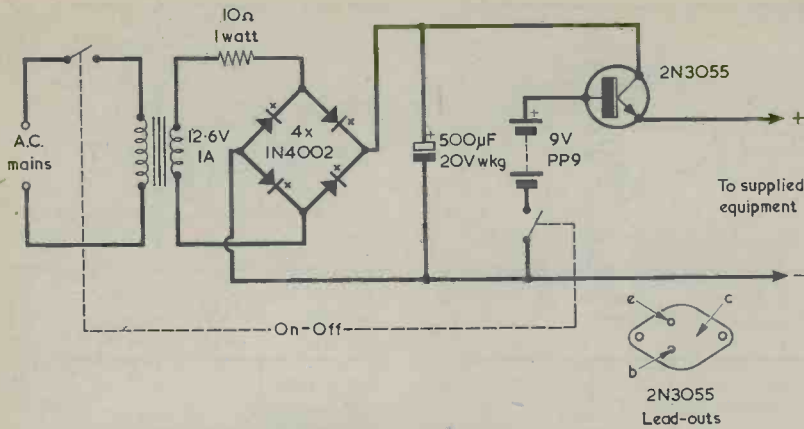


Fig. 4. A practical version of the circuit of Fig. 3. This was employed by Smithy in a supply unit for a transistor radio

battery which pass through it. As I said just now, the supplied equipment is almost certain to have a high value electrolytic across its supply rails, and at a first approximation this can be looked upon as a dead short at the instant of switch-on. At the same time, a new PP9 battery has an internal resistance of around 6Ω and so instantaneous switch-on surge current can theoretically be greater than an amp. In practice, there'll be an ohm or two in the electrolytic in the equipment but, even so, it's desirable to use a transistor which can withstand currents of the order of an amp in its base-emitter junction. The 2N3055 will run quite cool and it won't need to be mounted on a heat sink."

"I must say," remarked Dick, "that this business of the transistor changing over from an emitter follower to a forward biased rectifier is quite fascinating."

"It is rather," agreed Smithy. "Incidentally, the effect I've just described can cause some quite

puzzling fault symptoms in practical emitter follower circuits."

"How do you mean?"
 "Take a look at this circuit arrangement I'm drawing now," remarked Smithy. "It's for a standard emitter follower configuration." (Fig. 5 (a).)

"That seems pretty straightforward to me," commented Dick, looking critically at Smithy's sketch. "It's the sort of thing you bump into quite frequently."

"True," agreed Smithy. "Now, you'll notice that the base of the transistor is taken up to the positive rail by way of a resistor to which I've given a value of 100kΩ. At the same time the emitter load is a second resistor having a value of 1kΩ. If we assume that the transistor has a current gain of about 100 times, what will be the potential at its emitter?"

"If the current gain is about 100," remarked Dick, "then the current flowing in the 100kΩ resistor will be one-hundredth of the current flowing in the 1kΩ resistor."

"So?"

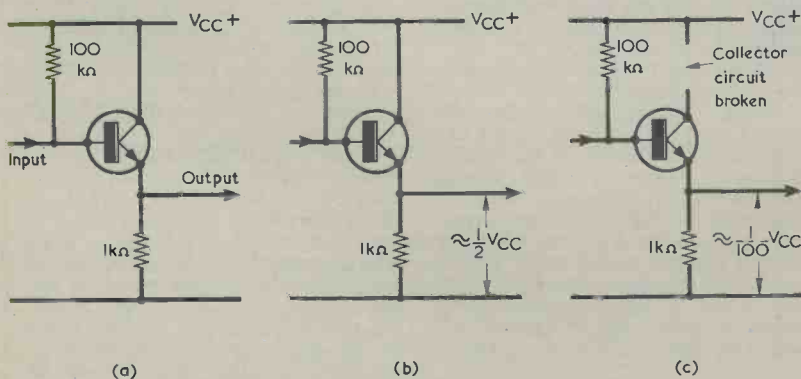


Fig. 5 (a). A standard emitter follower circuit
 (b). If the current gain of the transistor is about 100 times, the emitter potential is approximately half supply voltage
 (c). The emitter voltage falls to a very low level if the collector circuit is interrupted

Your Local Supplier

LONDON

THE MODERN BOOK CO.

Largest selection of English & American radio and technical books in the country.

19-21 PRAED STREET,
LONDON, W2 1NP
Tel: 01-723 4185/2926

ST. HELEN'S RADIO

Hi-Fi Equipment
Tape Recorders
Radio Receivers
Television

SPECIALISTS IN RADIO
& ELECTRONIC TEXTBOOKS

ST. HELENS GARDENS
LONDON, W.10
Tel: 01-969 3657

HAMPSHIRE

BOURNEMOUTH

LARGEST HI-FI AND
RADIO COMPONENT
STORE IN THE SOUTH

FORRESTERS NATIONAL
RADIO SUPPLIES LTD.

70-72 Holdenhurst Road
Bournemouth
Telephone 25232

SURREY

WITWORTH TRANSFORMERS

TV Line out-put transformers
Manufacturers of the largest range in the country. All makes supplied.

Modern
BAIRD, BUSH, GEC, PHILIPS
Replacement types ex-stock.
For "By-return" service, contact
London 01-948 3702

Tidman Mail Order Ltd., Dept. R.C.
236 Sandycombe Road,
Richmond, Surrey TW9 2EQ

Callers welcome.

"So," went on Dick, his brow furrowed, "since the resistance of the base resistor is 100 times that of the emitter resistor the voltages across them will be - let me see now - why, the voltages will be equal."

"And what will be the result of that situation?"

"Well," continued Dick, "the voltage at the emitter will be approximately half the supply voltage." (Fig. 5 (b).)

"Good," commended Smithy. "Now what will happen if, for some reason, the collector goes open-circuit?" (Fig. 5 (c).)

"Let's think now," said Dick, resuming the frown that inevitably accompanied cerebral exercise on his part. "If the collector is open-circuit the effect will be the same as we had with that power supply of yours. The base-emitter junction will act like a forward biased rectifier and current will simply flow through the 100kΩ resistor, through the base-emitter junction and then through the 1kΩ emitter resistor."

"And the voltage on the emitter?"

"It will be much lower now. With the resistor values you've chosen, it will be around one-hundredth part of the supply voltage."

"That's it," confirmed Smithy. "In this little exercise we've been ignoring the voltage drop across the base and emitter and we have in any case been dealing with approximate quantities. But it does show you one thing."

"What's that?"

"In an emitter follower circuit, the main thing that holds the emitter voltage up is the collector current!"

COMPOUND AMPLIFIERS

"That's a new way of looking at it," commented Dick.

His face grew more serious as he looked up and surveyed his surroundings.

"Gosh, Smithy," he said, his earlier nervousness returning, "that chap is taking ages."

"Don't get so agitated," said Smithy soothingly. "Your turn will come soon enough. Let me show you another circuit in which a transistor base-emitter junction is of importance."

"Oh, all right, then," said Dick reluctantly. "But this hanging around is beginning to be quite an ordeal."

"It will soon be over," comforted Smithy, "and then you'll really be grateful to me for having brought you here. Now, take a look at a circuit which is often used when it is required that small currents be used to turn on heavy current loads."

Smithy turned the leaves of the *Penthouse* magazine and drew a circuit in the margin of a new page. (Fig. 6 (a).)

"This," he continued, "is a very common switching circuit, and it comprises two silicon transistors. The first transistor acts as an emitter follower with its emitter connecting to the base of the second transistor,

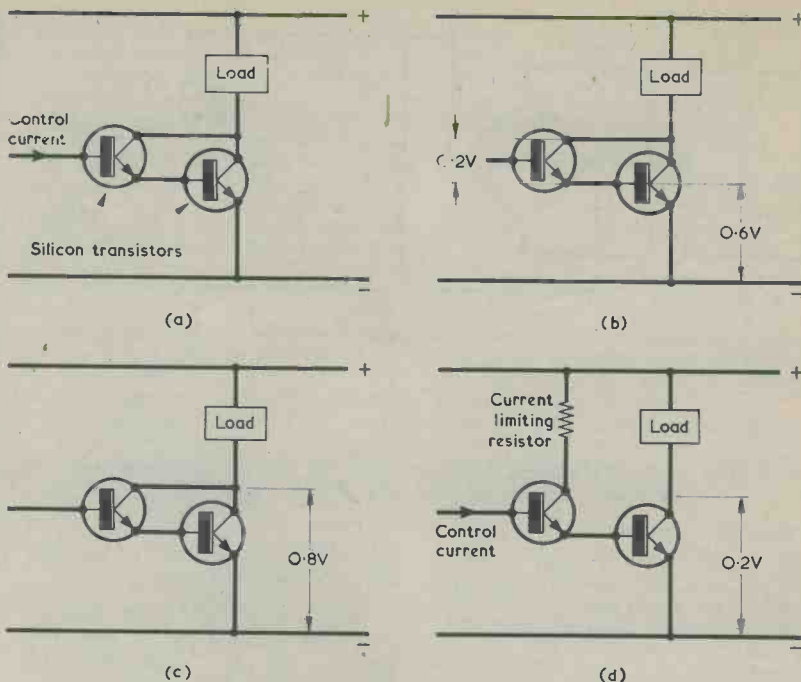


Fig. 6 (a). A commonly encountered switching circuit. A small control current flowing into the base of the first transistor allows the second transistor to turn on a high current load (b). Voltages appearing in the circuit when the load is switched on (c). The voltage across the second transistor cannot be made less than the sum of the two voltages shown in (b) (d). If the circuit is modified in the manner shown here, it is possible to achieve a much lower voltage across the second transistor when it is turned on

which is a common emitter amplifier. Both the collectors are connected together. When the circuit is used as a switch the two transistors are turned off when there's no base current flowing to the first transistor. The two transistors are then turned on when a base current is fed to the first transistor. Due to the combined amplification in the two transistors that base current can be quite low."

"What about power dissipation in the two transistors?"

"That," said Smithy, "is the next thing I want to discuss. When the two transistors are turned on the second transistor passes a high current because this is the current which is consumed by the load. The current passed by the first transistor need only be that which is needed at the base of the second transistor. The result of all this is that in most applications the second transistor will be a power type whilst the first transistor can be a small signal type."

"If," remarked Dick, "the controlling base current to the first transistor is applied and removed quickly, will that mean that the two transistors will spend nearly all the time either turned off or fully turned on, so that the

overall average dissipation will be quite low?"

"That's the general idea," confirmed Smithy. "When the two transistors are turned off the dissipation in them is, obviously, zero. When the two transistors are turned on the dissipation will be relatively low because of the low voltage which appears across them. The dissipation in each transistor is, of course, the product of its collector current and the voltage between its collector and emitter."

"Well," queried Dick, "what's wrong with this set-up?"

"Not a great deal, really," replied Smithy, "apart from the fact that it's possible to reduce the turned on dissipation in the second transistor by more than a half just by a slight rearrangement of the circuit. Now, a fully turned on silicon transistor has the voltage drop of about 0.6 volt between its base and emitter which we've already been talking about. At the same time, the voltage between its collector and emitter is much lower, being about 0.1 to 0.3 volt. For the sake of explanation, let's say that it's 0.2 volt. If we look at these two transistors of ours we can say that, when they are turned on, the voltage

across the collector and emitter of the first transistor is 0.2 volt, whilst the voltage across the base and emitter of the second transistor is 0.6 volt."

Smithy added the voltages to the transistors in his sketch. (Fig. 6 (b).)

"I think I see what you're driving at here," remarked Dick thoughtfully. "Does it have to do with the fact that the two transistor collectors are connected together?"

"It does," confirmed Smithy. "Now, the first transistor has to have its 0.2 volt between collector and emitter if it is to pass the requisite base current into the second transistor. Since the emitter of the first transistor connects directly to the base of the second transistor the two voltages can be added together, whereupon the voltage between the collector and emitter of the second transistor comes to no less than 0.8 volts. No matter how much current within reason you put into the base of the first transistor, the voltage between the collector and emitter of the second transistor cannot become less than 0.8 volt." (Fig. 6 (c).)

"0.8 volt, eh?" repeated Dick. "If there are a few amps flowing in the collector of the second transistor it could be dissipating several watts even when the transistors are considered to be fully turned on."

"Exactly," agreed Smithy. "Now, this dissipation can be considerably reduced by disconnecting the collector of the first transistor from the collector of the second transistor and connecting it, instead, to the upper supply rail by way of a current limiting resistor."

Smithy sketched out the new circuit. (Fig. 6 (d).)

"This time," he continued, "we have quite a different set of circumstances. If no bias current is applied to the base of the first transistor then both transistors are turned off, just as before. If a bias current of sufficiently high value is applied to the base of the first transistor, both transistors turn on. In this case, though, the second transistor is able to turn fully on, with the result that the voltage between its collector and emitter can fall to 0.2 volt, instead of to the 0.8 volt given with the previous arrangement. So the dissipation in the output transistor is considerably reduced."

The 'Slide Rule' Receiver Cum Capacitance Meter

In Part 1 of the 2-part article describing this equipment, which appeared in the last May and June issues, it was stated that range switch S1 is set to medium waves when measuring capacitances above 56pF. A better method of measuring capacitance consists of maintaining the range switch in the central position for all three capacitance ranges. Radio 1 is then tuned in for test capacitances from zero to 56pF, Radio 3 for test capacitances from 56pF to 560pF, and Radio 2 for test capacitances from 560pF to 5,000pF.

"What value should the limiting resistor have?"

"A value which allows rather more than enough base current to flow into the second transistor to turn it on," responded Smithy. "Hello, something seems to be happening."

EXTRACTION

And, indeed, something was happening. The green door opened and the young man who had previously entered came out, smiling broadly.

"Phew," he remarked. "That's a relief. I've been meaning to have it away for ages."

The middle-aged woman put her head round the door, and looked at the trembling and now virtually inarticulate Dick.

"Is he the one?" she asked Smithy.

"That's him," confirmed Smithy.

"Right," she said, beckoning Dick towards the door.

Dick turned an anguished glance at the Serviceman.

"Go on," urged Smithy. "If you don't go now you never will."

Quaking, Dick rose and tottered precariously through the green door. It closed behind him firmly.

"What," Smithy asked the young man, "did you have away?"

"This tooth," replied the young man, opening his mouth and pointing to a very evident gap in his top front teeth. "It's been giving me gyp for weeks and I've only just plucked up the courage to come in here today and get it pulled out."

Spying the *Penthouse* magazine on the table alongside Smithy, he picked it up and, unaware of the circuit diagrams which had been added to its pages, walked out happily with it tucked under his arm.

Left to himself, Smithy settled back comfortably on his chair in the dentist's waiting-room, reflecting that it wouldn't be long before he was in here again on his own account for his next six-monthly check-up. He then mused cheerfully on the fact that after considerable exhortation he had at last overcome Dick's obsessional fear of dentists, and had now persuaded him to visit Smithy's own dentist for the very first examination of his teeth since leaving school. ■

Your Local Supplier

SUSSEX

JEFFRIES

For your new television set
tape recorder, transistor radio
and hi-fi equipment

PHILIPS, ULTRA, INVICTA
DANSETTE, MASTERADIO, PERDIO,
MARCONI, PHILCO FIDELITY

6A Albert Parade
Victoria Drive,
EASTBOURNE SUSSEX

EIRE

PEATS for PARTS

ELECTRONIC COMPONENTS
RADIO & TELEVISION

For the convenience of Irish
enthusiasts we supply
Radio & Electronics
Constructor
Data Books and
Panel Signs Transfers
Also a postal service

Wm. B. PEAT & Co. Ltd.
28 PARNELL STREET
DUBLIN 1

RADIO & ELECTRONICS CONSTRUCTOR

ANNUAL
SUBSCRIPTIONS
to this magazine
may be obtained
through your
newsagent
or direct from the
publishers
ONLY £4.00
per year, post free

Please send remittance with name
and address and commencing issue
required to:

DATA PUBLICATIONS LTD
57 Malda Vale London W9 1SN

Radio

Topics

By Recorder

ONE WAY OF GIVING A REALLY professional appearance to a home-built electronic project is to assemble the parts on a printed circuit board. There is a certain almost creative pleasure to be obtained from this process, particularly if the design of the copper pattern is carried out by the constructor himself.

ETCHING KIT

These words are prompted as a result of examining a new etching kit which is now available from Home Radio (Components) Ltd. The contents of the kit are comprehensive, consisting of pieces of copper-clad board, ferric chloride crystals, an etch resist pen, a plastic dish, plastic tweezers, a plastic spoon (for measuring out the ferric chloride crystals), a laminate cutter and, most important of all, a set of detailed instructions.

We have rather a personal interest in these instructions as they draw freely from A. C. Gee's article 'Making Printed Circuit Boards', which appeared in *Radio & Electronics Constructor* for May, 1974. The instructions are both helpful and amusing and include an account of the lessons learned by the compiler in his own first steps in making up ferric chloride solution. For instance, when he added the crystals to the water in a plastic dish the resultant heat melted a hole in the dish! It is finally recommended that the ferric chloride crystals be added slowly to the water in an old jam jar which is then thrown away afterwards. The crystals should always be added to the water and not the other way round. If water is poured on the crystals they may 'spit' and fly around; this is a dangerous situation since the ferric chloride could then get on the skin or, worse, in the eyes.

The instructions also give very useful advice on the actual designing and etching of a printed circuit board, and there are a number of tips on the most economical use of the copper-clad board, of the etch resist pen and, also, of the ferric chloride crystals

themselves.

Just to show how old I am I can still refer to the ancient story in which the young lady is allured to her admirer's flat so that he can show her his etchings. Perhaps, in this all-electronic age, successfully completed printed circuit boards could provide an equally attractive enticement.

MCM AND ALL THAT

Much TV time these days is taken up by old films, and it is always a matter of interest to find out when they were released. You can of course always tell really old films because everyone wears hats and they kiss with their mouths closed, but there is a more precise method of determining the year of issue.

All films carry a copyright notice in the credits which consists of the word 'Copyright', or a letter C inside a circle, followed by the year when the film was released. Film producers are not at all keen on stating too obviously the year of issue of a film because it may then appear dated if it appears in a cinema some two or more years later. In consequence, the copyright year is nearly always given in Roman numerals which, the producers fondly hope, will not be understood by many of their audiences.

They're right, too. On checking with friends and acquaintances I have been amazed to find how few are able to work out those Roman copyright year figures on the films they see.

Fortunately, it's dead easy. The Roman letter for 1000 is M and that for 100 is C. So MCM, the first three letters to be found with all films, stands for 1900. You put a C in front of an M to make 1000 minus 100, or 900, in just the same way as you put an I in front of an X on a clock face to make 10 minus 1, or 9. So, MCM means 1000 (the first M) plus 900 (the following C and M), or 1900.

The Roman numerals after MCM are then added to 1900, and all you have to remember here is that L stands for 50. The remaining charac-

ters are X, V and I, which are familiar from the clock face. MCML is 1950, MCMLI is 1951, MCMLV is 1955 and MCMLVII is 1957.


MCMXL is, wait for it, 1940. The X in front of the L gives 50 minus 10, or 40. MCMXLII is 1942 and MCMXLVI is 1946. For the 1930's you have MCMXXX followed, for years above 1930, by the final year figure. Thus, MCMXXXIV is 1934.

Coming up to more recent times, MCMLX is 1960 and MCMLXX is 1970. And our present year of grace? MCMLXXV. But you'll have to go to the cinema if you want to see a non-TV film with that copyright year on the screen.


HIGH CURRENT S.C.R.

Both of the accompanying photographs illustrate items which are now available from Jermyn Industries, Sevenoaks, Kent.

The first shows examples of a new range of high current silicon controlled rectifiers, or thyristors, which are manufactured by the American General Electric Company. These are rated at 63 amps r.m.s. and are available in twelve different voltage grades from 100 to 1,200 volts. The range is known as the C147 series and is recommended for applications where a high surge current rating is required. The maximum capability is achieved when the thyristor is mounted on a Jermyn HP55 heatsink, as is the thyristor illustrated. Particularly useful for work at U.K. mains voltage is the

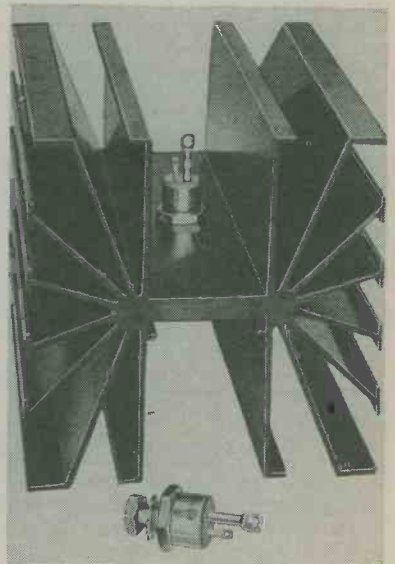

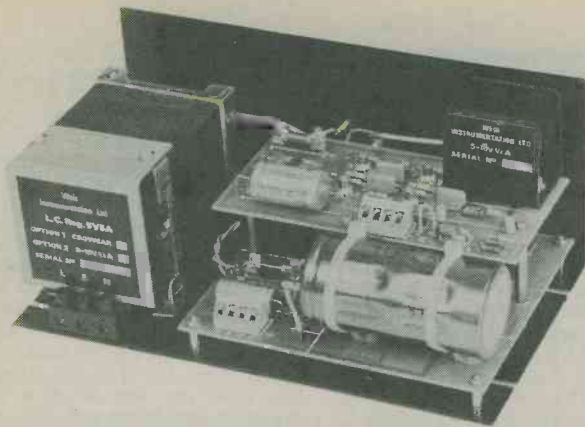Mounted on a really man-sized heatsink, the G.E. thyristors shown here are rated at 63 amps at voltages ranging from 100 to 1,200 volts



The Weir Instrumentation power supply type 5V5A, with 5-18V circuit board fitted. This combination is suitable for powering hybrid systems incorporating both t.t.l. and CMOS logic

thyristor type C147D, which is rated at 400 volts.

A power supply capable of powering hybrid systems incorporating t.t.l. and CMOS logic appears in the second photograph. Made by Weir Instrumentation, Ltd., the basic supply type 5V5A produces an output of 5 volts at 5 amps. The output is fused and has foldback current limiting. If desired an optional crowbar over-voltage protection circuit may be fitted.

Alternatively, a second supply offering currents up to 250mA at a voltage variable from 5 to 18 volts can be added. This accessory is the type 5-18V unit, and it consists of the upper circuit board seen in the illustration.

THE U.S. SCENE

A 2N3055 costs about 1 dollar by mail order, a 709 i.c. costs about 29 cents, a 741 some 35 cents and a 555 timer about 99 cents. I've just been doing a little window-shopping through the advertisement pages of our U.S. contemporary *Radio-Electronics*, and these are some of the prices currently quoted by American mail order suppliers. If we work to two and a third dollars to the pound, a dollar becomes equal to approximately 44 pence, and it would appear that the American home-constructor can buy his transistors and integrated circuits rather more cheaply in terms of real cash (if such a concept still exists in these inflation-cursed times) than we can.

Whereas many of our English mail order advertisers list a very large number of transistors in their magazine advertisements the American practice is to quote quite a small range. The large ranges may of course be given in advertisers' catalogues which I haven't seen. However, one advertiser does quote a long list reminiscent of English advertising style, but this is for Japanese transistors in the 2SA to 2SD range. Advertisements for t.t.l. 74 series i.c.'s are much the same as in this country, with the full range listed.

AUGUST 1975

It is always interesting to visualise the scene on the other side of the Atlantic, but what is even more fascinating is the international flavour of electronics as a hobby. In this country both the R.S. Components and Doram Electronics catalogues employ the pleasant practice of quoting 'country of origin' for some of their semi-conductors, and one finds oneself making a mini-world tour stopping here at Singapore and then at Japan, W. Germany, Israel, Italy and finally, for a few rectifiers in the 1N4000 series, at no less exotic a place than Taiwan.

The world gets tinier and tinier. You can almost feel its surface contracting under your feet.

ELECTRONIC IGNITION

Quite a lot of argument still continues about the usefulness or otherwise of electronic ignition for cars. One of our contributors, Frank Osborn, G2CVO, has just had some practical experience with a commercially made electronic ignition unit and his findings may well be of interest to readers who are contemplating a similar modification to their cars.

'I suppose a lot of people like myself,' writes G2CVO, 'have thought electronic ignition a bit gimmicky. However, the recent heavy increase in the price of petrol made me turn a jaundiced eye on my car which was not presenting any startlingly economical consumption figures. Understandably so, as this is a Hillman Minx of 1969 vintage with automatic transmission and around 70,000 miles on the clock. It was also approaching its 6,000 mile service, so it could hardly be called in fine fettle.

'On the reasonable assumption that with any small improvement I must eventually recoup my outlay on fitting electronic ignition, I invested in a Sparkrite ready made unit at a little under £14. It was claimed that in addition to better miles per gallon, one could expect longer life on points,

GREENBANK ELECTRONICS

FREE!

Data and circuit diagram for Digital Alarm Clock Chip AY-5-1224, Digital Alarm Clock Chip MK 50253, also data sheet for DL-704E, DL-707E, DL-747E and DL-750 LED displays. (A stamped addressed envelope with enquiries is a great help to us, but is not essential.)

CLOCK CHIPS (ex. VAT)

AY-5-1224, 4 digit, 12/24 hr., 50/60 Hz, TTL compatible, zero reset, easy display interface, 16 pin DIL package: £3.66
MK 50253, 4/6 digit alarm clock chip, 50 Hz, 12/24 hr., AM/PM and activity indication, 'snooze' feature, intensity control, simple time setting, 28 pin package, compatible with earlier type MK 50250: £5.50

LED DISPLAYS (ex. VAT)

DL-704E 0.3" LED 7 Seg. Display C. Cathode 85p
DL-707E 0.3" LED 7 Seg. Display C. Anode £1.70
DL-750 0.6" LED 7 Seg. Display C. Cathode £2.45
DL-747E 0.6" LED 7 Seg. Display C. Anode £1.70

CLOCK KITS (ex. VAT)

SOK/1 Many parts for 4 x 0.6" LED Clock £14.95
SOK/2 Many parts for 4 x 0.3" LED Alarm Clock £13.50

Add VAT .. 8% to all above prices. (If in doubt, ask for a quotation, or send 25% VAT and we will refund any excess). Post etc. 10p + 8% VAT per order.

GREENBANK ELECTRONICS
(Dept. C8R), 94 New Chester Road,
New Ferry, Wirral, Merseyside,
L62 5AG. Tel: 051-645 3391.

GAREX

Modulation transformers

Valve type 747, as specified for 30W Tx £2.60

Transistor type, p/p NKT404 to QVQ03-20a (or QVQ03-10), with driver transformer to match - special offer - the two £1.45.

Audio transformers - driver and output (2W) p/p NKT404 to 3Q the two 70p
NKT404 power transistors

17p each, 4 for 60p

Mains transformers (multitap primaries)
250-0-250V 200mA, 6.3V 5A, 5V 2A, fully shrouded, (suitable for 30W Tx - matching style to mod. transf.) £5.70
345-0-345V 150mA, 5V 2A £5.45
6.5-0-6.5V 2.3A, 6.5-0-6.5V 2.9A,
6.5-0-6.5V 4.2A, 6.5V 2.7A,
37V 30mA £5.45

H.T. chokes 5H 80mA, 1.8H 125mA £1.10

Toroidal Inverter Transformer
Input 12V DC, output 170/380V
180mA £2.05

Relays GPO type 2400, 12V coil,
8A contacts, 4PCO or 2P make
any 4 for £1.00

Connection data or circuits supplied with transformers.

Components are ex-equipment, in good condition, your satisfaction guaranteed.

Prices inclusive of UK Post, Packing and VAT at 25%

Mail order only. Sole address:

GAREX ELECTRONICS
7 NORVIC ROAD, MARSWORTH,
TRING, HERTS HP23 4LS
Cheddington (STD 0296) 668684

plugs, coils and batteries. Also quieter running, better acceleration and top speed, and complete burning of the mixture.

'This unit retained the use of the contact breaker, was extremely easy to fit and the operation was carried out on a wet and wintry February day. A careful log of mileages and types of journey has been kept and some very interesting figures emerge.

'Before fitting the electronic unit petrol consumption for local shopping runs within an 8 mile radius was 22 m.p.g., whilst on runs on trunk roads at 50 m.p.h. it was 30 m.p.g. After the unit had been installed the consumption for the local shopping runs remained at 22 m.p.g., but the figure increased to 36.6 m.p.g. for runs on trunk roads at 50 m.p.h. Also, on trunk roads plus some local runs the consumption, at 34 m.p.g., was still a significant improvement.

'After the 6,000 mile service, when the clean plug points amazed me, the trunk road mileage remained at the 36 m.p.g. figure but the local mileage had improved to 25 m.p.g. It will be readily seen that regular servicing also plays an important part in enabling the electronic device to give of its best. Local stop-start motoring is the most damaging to engines, creating wear from the use of the choke and the subsequent rich mixture, together with oil sludging in wintry conditions. The

man on the trunk road has the best of it and the modern high speed engine then clearly shows the improvement in miles per gallon.'

HUNTING

Most engineers who have had experience with servo systems have encountered the phenomenon known as 'hunting'. A servo system is an automatic control system in which the output is intended to follow the input. Generally, there is an amplifier between the input and the output together with a feedback loop from the output back to the input. A servo system can be employed, for instance, in the control of a rotatable outdoor aerial. A dial at the receiving or transmitting position is set up for a particular direction and an outside motor then turns the aerial to the desired position.

Continuing with this rotatable aerial example, hunting occurs if the system allows the outside motor to be a little too energetic. Say, for instance, that the inside controller is adjusted to change the aerial position from due west to due north. The outside motor turns the aerial to the north position, but the inertia in the system causes it to go a little beyond north to, say, a few degrees to the east. The motor stops, the system senses the error and the motor reverses to take the aerial

back to north. Again it passes the due north position and stops a few degrees to the west. And thus the system settles down to a hunting condition, with the aerial motor continually taking the aerial a few degrees on either side of the desired north setting, first in one direction and then in the other.

This hunting situation appears in many facets of life which are quite remote from electronic or mechanical operation. A classic example is given when two people bump into each other in a corridor. Each moves sideways in the same direction to get past the other, and it is not until several moves have been made that they decide to move in opposite directions and thus get by. Hunting is particularly noticeable in the governing patterns of democratic countries. There is no precise government party policy which can please the greatest number of the electorate and so the government hunts first to one side of centre and then to the other side of centre. In the U.K. the government hunts continually between Tory and Labour. There is, of course, considerable inertia in the electoral system because the feedback is made via general elections which may be spaced apart by up to some four years or so. But the hunting is there for all to see.

If you can accept that you are part of an enormous servomechanism then I need only add: Happy Hunting! ■

Use the NEW Strip-fix Plastic PANEL SIGNS

- ★ SET 3-Wording-WHITE Over 1,000 words and symbols, covering more than 300 terms, in each set
- ★ SET 4-Wording-BLACK

Illustration of actual size = RADIO

★ SET 5-DIALS

6 sheets containing one Large and two Medium scales, Large Horizontal Tuning scale, Frequencies, 12 Control Panels

PRICE SET 3: 38p SET 4: 50p SET 5: 38p
(P. & P. 5p per set) ALL PRICES INCLUDE V.A.T.

- Easy to fix
- Stapled in booklet form
- Designed to hang above workbench
- Pocket for loose cuttings
- Professional finish



To Data Publications Ltd., 57 Maida Vale, London, W.9 1SN

Please supply Panel Signs as follows : Set 3..... Set 4..... Set 5..... (Tick which set is required)

I enclose cheque/crossed postal order for.....

NAME

ADDRESS.....

(BLOCK LETTERS PLEASE)

SMALL ADVERTISEMENTS

Rate: 5p per word. Minimum charge 75p
Box No. 10p extra.

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of Advertisers. (Replies to Box Numbers should be addressed to: Box No. —, *Radio and Electronics Constructor*, 57 Maida Vale, London, W9 1SN

UNIQUE VHF KITS, 80-180MHz. Receiver, tuner converter. World wide sales. Send £5 or s.a.e. for literature. Johnsons Radio (C), Worcester, WR1 3QQ.

LOUD 6V SIRENS. £1.20p, add 15p P. & P. BC108 12p, 10 for 95p. Grimsby Electronics, 64 Tennyson Road, Cleethorpe, Humberside. List No. 10 8p. (Callers to Lambert Road, Saturdays only).

FOR SALE: Polarised relays, suitable for RTTY terminal units. £1.00. Box No. G235.

SERVICE SHEETS for Radios/TV's etc. 50p and s.a.e. Catalogue 20p and s.a.e. Hamilton Radio, 47 Bohemia Road, St. Leonards-on-Sea, Sussex.

WANTED. Early radio books, prior to 1925. Box No. G236.

BUILD THE MULLARD C.C. TV CAMERA. Complete kits now available from Crofton Electronics. Send large s.a.e. for details to:- 124 Colne Road, Twickenham, Middlesex, TW2 6QS. Telephone: 01-898-1569.

FOR SALE: Regulated power supply. PU189, 0-15V, 0.4 amps, meter to monitor voltage. £14.40. Touch sensitive switch drive TTL or relay, £1.25. T. Edwards, Box No. G263.

BURGLAR/FIRE ALARMS. Emergency lighting. Professional and D.I.Y. equipment. Catalogue 25p. Castle Alarms, Box W06, Windsor, Berks.

WANTED for cash or loan, circuit details of "Lerna-Kit" oscilloscope also *Practical Wireless* April 1971 and other issues containing "Workshop Oscilloscope". Box No. G264.

TREASURE HUNTERS! Construct highest performance electronic metal detector for under £2. Equals models costing up to £50. For simple illustrated plans send £1. Colin Lucas, 241 Upminster Road South, Rainham, Essex.

VALVES, RADIO, TV, TRANSMITTING. 1930 to 1975. 2,000 types stocked. Many obsolete. X78-TH41-2P-N78-EBLI - EBL31 - ECC31 - EL37 - EN31 - TH4 - MKT4 - PENDD4020 - PX4 - X81M - W61 - X101 - X109 - X145 - X147 - Z21 - Z319 - 2359 - 6F33 - 61BT - etc. List 20p. We wish to purchase new and boxed valves. Cox Radio (Sussex) Ltd., The Parade, East Wittering, Sussex. Telephone: West Wittering 2023.

FOR SALE: *Wireless World* April 1964 - December 1974, *Television* August 1971 - December 1974. 10p each plus postage. S.A.E. for enquiries. Box No. G265.

SHACK CLEARANCE. Diodes (from 1p), transistors (from 3p), valves, transformers, resistors, capacitors, computer boards, PSU, etc. S.A.E. list. Box No. G266.

(Continued on page 60)

BENTLEY ACOUSTIC CORPORATION LTD.

All prices inclusive of V.A.T. at 25%

The Old Police Station, Gloucester Road, LITTLEHAMPTON Sussex. PHONE 6743

OB2	.50	10P13	.88	E180F	1.17	EH90	.53	PCL82	.45	UM80	.60
1A7GT	.70	10P14	2.34	EAS0	.32	EL32	.59	PCL83	.53	UY41	.53
3V4	.82	12A6	.75	EAB00	.88	EL34	1.17	PCL84	.47	UY85	.50
504G	.47	12AC6	.82	EA91	.45	EL41	.59	PCL805	.70	X41	1.00
5Y3GT	.53	12AD6	.76	EAC80	.65	EL84	.35	PCL86	.55	X68	1.46
5Z4G	.53	12AE6	.76	EAF42	.88	EL506	1.05	PFL200	.82	X76M	.85
6B0L2	.70	12AT6	.47	EAF801	.90	EM80	5.03	PL36	.70	Z759	5.85
6A116	.70	12AU6	.53	EB91	.23	EM81	.76	PL81	.53	AC165	.33
6A05	.53	12AV6	.59	EB441	.88	EM83	.64	PL82	.43	AD149	.64
6AT6	.53	12BA6	.53	EB81	.41	EM84	.47	PL83	.47	AD149	.64
6AU6	.35	12BE6	.59	EBF80	.46	EM87	.82	PL84	.47	AD161	.59
6AV6	.53	12BH7	.59	EBF83	.50	EY51	.50	PL84	.82	AD162	.59
6BA6	.41	12BY7	.85	EBF89	.38	EY87/6	.39	PL508	1.10	AF114	.33
6BE6	.41	12K5	1.17	EC92	.53	EY88	.47	PL509	1.70	AF115	.20
6BH6	.70	19AQ5	.59	ECC33	1.76	EZ40	.59	FY332	.53	AF121	.39
6B16	.64	20P4	1.17	ECC35	1.11	EZ41	.64	PY81	.41	AF126	.23
6B07A	.64	30C15	.82	ECC40	1.17	EZ80	.33	PY82	.35	BC107	.16
6BR7	1.17	30C17	.94	ECC81	.40	EZ81	.34	PY83	.45	BC108	.16
6BR8	1.25	30F5	.88	ECC82	.39	GY501	.82	PY88	.47	BC109	.16
6B16W	.64	30FL1	.78	ECC83	.39	GZ32	.59	PY500	1.11	BC113	.33
6BW7	.82	30FL2	.78	ECC84	.41	GZ34	.70	PY800	.47	BC118	.29
6BZ6	.57	30FL14	.82	ECC85	.47	KTW61	.65	PY801	.47	BC121	.49
6C4	.47	30L15	.82	ECC87	.50	PZ30	.50	PY818	.23	BF158	.23
6C6	.47	30L17	.76	ECC80	.2	KTW62	1.76	QQV03/10	.67	BF159	.33
6C9	1.17	30P12	.76	ECF80	1.41	KTW63	1.76	R19	2.05	BF163	.26
6CL6	.76	30P19	.88	ECF80	1.41	KTW63	1.76	R19	2.05	BF180	.39
6CL15	.88	30P11	1.00	ECF82	.53	PAB00	1.17	U25	.70	BY100	.23
6E5	1.17	30P13	1.11	ECF86	.88	KT66	2.93	U26	.77	BY126	.20
6F1	.88	30P14	1.29	ECF80A	1.41	PAB00	1.17	U91	.59	BY127	.23
6F23	.59	35L6GT	.88	ECF83	.53	PC86	.70	U91	.76	OA91	.12
6F18	.64	35W4	.59	ECH35	1.46	PC86	.70	UAB00	.76	OA95	.12
6F28	.82	35ZAGT	.82	ECH42	.82	PC88	.70	UAF42	.47	OC23	.49
6E28	.78	50B5	1.00	ECH41	.39	PC97	.55	UB42	.70	OC24	.49
6HG6T	.29	ANCS	.70	ECH83	.52	PC900	.47	UB41	.70	OC25	.49
6J5GT	.53	50L6GT	.76	ECH84	.52	PC84	.55	UB81	.60	OC44	.13
6J6	.35	85A2	.70	ECL80	.47	PC85	.52	UBF80	.47	OC45	.14
6K7G	.35	807	1.17	ECL82	.50	PC88	.70	UBF89	.47	OC46	.20
6K8G	.53	5763	1.76	ECL83	.82	PC89	.60	UC9	.60	OC70	.16
6L6GT	.68	ATP4	.59	ECL86	.47	PC189	.36	UC84	.88	OC71	.14
6Q7G	.59	AZ31	.70	EF22	1.76	PCF80	.47	UC85	.60	OC72	.14
6GTG	.59	DAF91	.35	EF40	.88	PCF82	.47	UC80	.90	OC76	.29
6SG7	.52	DAF96	.59	EF41	.82	PCF84	.69	UCH42	.88	OC75	.14
6S17	.64	DF91	.35	EF80	.29	PCF86	.56	UCH81	.47	OC78	.20
6V6G	.20	DF96	.59	EF83	1.17	PCF200	1.00	UC182	.45	OC78D	.14
6V6GT	.53	DK91	.35	EF85	.35	PCF201	1.00	UC184	.64	OC81	.14
6X4	.47	DK92	.82	EF86	.53	PCF201	1.00	UF41	.32	OC81D	.14
6X3GT	.53	DK96	.70	EF89	.35	PCF201	1.00	UF42	.32	OC82	.14
7B6	.88	DL92	.47	EF91	.43	PCF801	.65	UF80	.41	OC82D	.14
7Y4	.88	EL96	.64	EF92	.59	PCF802	.65	UF85	.52	OC83	.26
9D7	.76	DY87/6	.41	EF98	.94	PCF805/10	UF89	.47	OC84	.31	
10F1	.88	DY802	.41	EF183	.35	PCF806	.59	UL41	.70	OC202	.55
10F18	.64	EB8CC	1.20	EF184	.41	PCF806	.59	UL84	.49	OC205	.55

All goods are unused and boxed, and subject to the standard 90-day guarantee. Terms of business: Cash or cheque with order only. Despatch charges:—Orders below £10, add 25p extra per order. Orders over £10 post free. Same day despatch. Terms of business available on request. Any parcel insured against damage in transit for only 5p extra per parcel. Please enclose S.A.E. with any enquiries. Many other types in stock.

ENGINEERS

FREE



YOURSELF FOR A

BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through our low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.

CUT OUT THIS COUPON
CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.

Build-As-You-Learn

PRACTICAL RADIO AND ELECTRONICS (with kit)

Computer Programming

General Radio and TV Engineering

Radio Servicing, Maintenance and Repairs

Electrical Draftsman-ship

Electrical Mathematics

Electronic Engineering

Computer Electronics

Computer Programming

General Radio and TV Engineering

Radio Servicing, Maintenance and Repairs

Transistor Technology

CITY & GUILDS Installations and Wiring

CITY & GUILDS Electrical Technicians

CITY & GUILDS Telecommunications

Radio Amateurs' Exam etc. etc.

G.C.E. 58 '0' & 'A' LEVELS

Coaching for many major examinations

To ALDERMASTON COLLEGE, Dept. ERE 08, READING RG7 4PF
Also at our London Advisory Office, 4 Fore Street
Avenue, Moorgate, London, EC2Y 5EJ Tel: 01-628 2721

ERE 08

NAME (Block Capitals Please)

ADDRESS

POSTCODE

Other subjects

Accredited by C.A.C.C.


Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

PLAIN-BACKED NEW STYLE SELF-BINDERS

for your other magazines

(max. format 7½" x 9½")

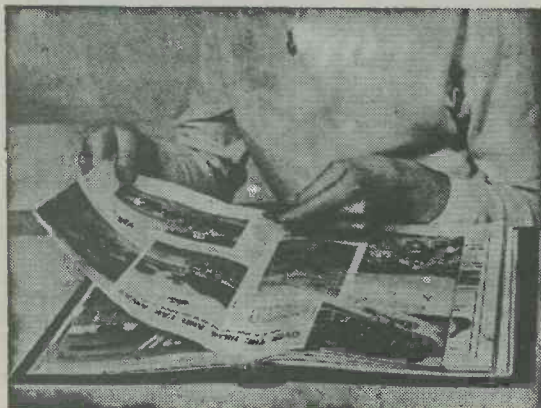

The "CORDEX" Patent Self-Binding Case will keep your copies in mint condition. Issues can be inserted or removed with the greatest of ease. Specially constructed Binding cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for, and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

COLOURS: MAROON OR GREEN

(If choice not stated, colour available will be sent)

PRICE 95p P. & P. 20p

Available only from:—

Data Publications Ltd.
57 Maida Vale London W9 1SN

SMALL ADVERTISEMENTS

(Continued from page 59)

FOR SALE: Heathkit oscilloscope IO-102, plus electronic switch ID-101 for double trace display; low capacitance and demodulator probes. New and perfect. £165 the lot, or v.n.o. Toms, 6 St. Mary Road, London E.17. Telephone: 01-520-6954 evenings.

COLLECTORS: Dinky toys in fair condition, of approx. 1945 vintage. Offers? Box No. G267.

POSTAL ADVERTISING? This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning design and artwork, printing and stationery. Please ask for price list. — The Holborn Direct Mail Company Capacity House, 2-6 Rothsay Street, Tower Bridge Road London, S.E.1. Telephone: 01-407 1495.

FOR SALE: Touch sensitive switch, rain detector; drive TTL or relay, £1.25. Regulated power supply PU189 0-15V 0.4 amps, meter to monitor voltage, £14.40. Kilton Electronics. Box No. G268.

JOIN THE INTERNATIONAL S.W. LEAGUE. Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. — both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazines, etc., £3.75 per annum. (U.K. and British Commonwealth), overseas \$10.00 or £4.00. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

FOR SALE: 1,000 mixed resistors £1.00. 100 mixed 3-5-7W resistors £1.00, postage 25p. Switch cleaner 70p, 5 tins £2.50. Stereo cassette mechanism (just requires power supply and amplifier) £20.00. New 50cc 2-stroke engine £17.50. 100 new records £10.00. Sample free. Box No. G269.

FOR SALE: Selenium solar cells 10p. 16 digit 2 memory calculator £75.00. 100 unmarked BZY88 50p. 50 unmarked 2W zeners 75p. 50 unmarked BC107/8/9 50p. Closed circuit camera construction manual £2.00. Low-band Pye Rangers, tested, £10.00. 8mm zoom cine camera £15.00. Box No. G270.

FOR SALE: Philips GA212 record deck, £50. Pair Wharfedale Glendale 3, £50. Atlas AD3 5A battery charger, £3.75. Marnett Radio, "Roundabouts", Five Ashes, Sussex. Telephone: 082-585-372.

WANTED: 'Radio Constructor' General Purpose power supply unit, as featured in January 1971. Box No. G271.

FOR SALE: R1132 Receiver. Frequency range 81.5 to 107. With power unit. £15. Sutton, 23 Lambourne Gardens, Earley, Reading, Berks.

FREQUENCY LIST TRANSFERS. We have a limited supply of sheets of Dial Frequency Transfers in black. Short Wave frequencies 1.8Mc/s to 32Mc/s and 144Mc/s and 146Mc/s. Includes amateur band marker frequencies at 100kc/s points and other short wave frequencies from 2 to 32Mc/s at every 500kc/s points. Each frequency is repeated. Two sheets for 5p., five sheets for 10p., postage 4p. Data Publications Ltd., 57 Maida Vale, London. W9 1SN.

(Continued on page 61)

RADIO & ELECTRONICS CONSTRUCTOR

SMALL ADVERTISEMENTS

(Continued from page 60)

WANTED URGENTLY: Circuit diagram of Indicator Unit A.M. Ref. No. 110 QB/13 and/or manual of equipment of which this unit is part. Unit incorporates 2 x 5FP7, 2 x 6H6, and 2 x DPCO 24V relays type BA-11755-2. Any reasonable payment. Box No. G272.

FOR SALE: Half price, slightly used valves. QQVO3-10 90p, QQVO2-6 £1.25, 6AS6 50p, 5R4GY 50p. Postage included. Box No. G273.

TO CLEAR BOOKSHELVES: *Handbook of Satellites and Space Vehicles* by R. Haviland, £3. *Medical Radiation Biology* by F. Ellinger, £3. *Space* by Patrick Moore, £2. *Rocketry and Space Exploration* by Haley, £2. *Health Physics* by Rees, £3. Box No. G274.

ANTIQUE RADIO ENTHUSIASTS. For all your requirements in radio 1920 to 1945, contact Tudor Rees's Antique Wireless Service. Our full 1975 catalogue now available, price 40p post paid. Tudor Rees, 64 Broad Street, Staple Hill, Bristol, BS16 5NL. Telephone: 0272-565472.

FOR SALE: Partially completed model patrol launch. 42 inch overall. Fitted Taplin Twin I/C engine, and steering control for twin rudders. Ideal for R/C. S.A.E. for details and offers? Box No. G275.

EXPERIMENTERS AND CONSTRUCTORS. Hundreds of items cheap. S.A.E. for List No. 10. Sample pack send 25p. Grimsby Electronics, Lambert Road, Grimsby, Humberside.

FOR SALE: Complete Widescreen film outfit. 9.5mm camera and projector with widescreen lens, screen, film, etc. Would exchange for other photo or radio gear or w.h.y.? S.A.E. for details to Box No. G276.

HARDWARE SUPPLIES. Sheet aluminium, screws, nuts, washers, etc. Fascia panels in aluminium, individual requirements. Printed circuit boards, one-off or small runs, individual and for patterns published in this magazine. Send 10p for list. Ramar Constructor Services, 29 Shelbourne Road, Stratford-upon-Avon, Warwicks. CV37 9JP.

WANTED: Prism type spectrometer, suitable demonstration purposes, school, etc. Must be cheap. Repairable instrument would be suitable. Box No. G277.

FIBRE OPTICS, OPTOELECTRONICS. Complete range fibre optics, photo-detectors, LED's, lenses, retroreflectors, polarisers, ultrasonic transducers. Send 9" x 6" s.a.e. for shortform price list: FIBRE OPTIC SUPPLIES, 2 Loudoun Road Mews, London NW8 0DN.

FOR SALE: 2m converter, mains operated. 24-26MHz. £8. Box No. G278.

RADIO & ELECTRONICS CONSTRUCTOR. Due to loss in warehouse fire, we require copies of the June and July 1973 issues. Cover price paid, remittance by return. Send to Data Publications Ltd., 57 Maida Vale, London W9 1SN.

COMPONENT CLEARANCE: AC128's, new, marked, 5p each. OA81, brand new, 4p. Tested ex TV valves 12p each. 20 assorted potentiometers 50p. S.A.E. for list. Box No. G279.

(Continued on page 63)

AUGUST 1975

RADIO MODELLER

ELECTRONIC BOOKS

● **MODEL RADIO CONTROL**
Detailing both Theory and Practice, this book, by leading authority Paul Newell, has become the standard reference work. A brief historical survey leads up to a detailed description of proportional systems, with over 100 illustrations, including theoretical circuits and p.c. layouts for an advanced digital system.
134 pages.

U.K. Packing & Postage 32p
Price £2.25

ON SALE NOW
at all leading shops
or direct from:-


**RADIO MODELLER
BOOKS DIVISION,
64 Wellington Road,
Hampton Hill, Middx.**

theory and
practice of

MODEL RADIO CONTROL

development of systems
proportional explained
digital system design—
practical examples and
full circuit details.

Paul Newell

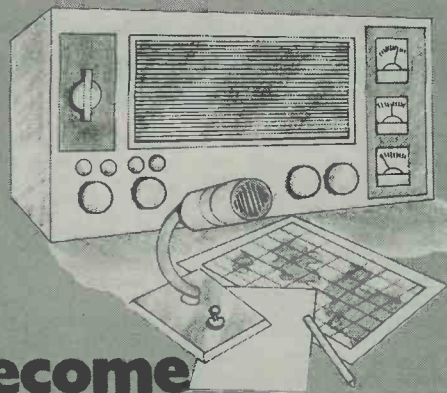

Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

WAA

Brochure, without obligation to:

RECR 8/75

BRITISH NATIONAL RADIO
& ELECTRONICS SCHOOL, Dept

P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

(Block caps please)

Free!

ESSENTIAL BOOKS!

POWER SUPPLIES FOR ELECTRONIC EQUIPMENT. J. R. Nowicki. Published recently in 2 vols. A full treatment of all power supplies is given. Includes rectification, inverters, transverters, silicon diodes and other electronic devices. With full circuit diagrams and component values. Originally published at £4.50 per volume. Bargain price £4 for the 2 volumes incl. postage.

THE MOBILE RADIOTELEPHONE EQUIPMENT HANDBOOK. Gives circuits, data and illustrations plus some valuable modification details for COMMERCIAL RADIOTELEPHONE equipment. Price of this edition including postage £6.25.

HOW TO MAKE WALKIE-TALKIES FOR LICENSED OPERATION. 40p, p.p. 15p.

HOW TO MAKE 2M & 4M CONVERTORS FOR AMATEUR USE. Fully comprehensive. Contains circuits layouts, component lists, diagrams and full instructional notes. Price 60p, p.p. 15p.

THE GOVERNMENT SURPLUS WIRELESS EQUIPMENT HANDBOOK. Gives circuits, data and illustrations plus valuable information for British/USA receivers, transmitters, trans/receivers. £4 including postage.

DIRECTORY OF GOVERNMENT SURPLUS WIRELESS EQUIPMENT DEALERS! Gives details of surplus wireless equipment stores and dealers including addresses plus equipment and spares that they are likely to have available. A valuable book only 50p, p.p. 15p.

GETTING THE BEST FROM YOUR COLOUR TV. R. Maude. Essential advice for colour TV engineers and owners. Could save you pounds. 50p, p.p. 15p.

THE THEORY OF GUIDED ELECTROMAGNETIC WAVES. The most comprehensive book yet written about waveguides, transmission lines, cavity resonators. Over 500 pages. Ideal for anyone interested in Radar and UHF. Published at £11.50. Special offer £4.50 p.p. 50p.

INTERNATIONAL DICTIONARY OF SEMICONDUCTORS. A 2-volume electronics dictionary published at £16 available at less than half price. In 7 languages it proves an invaluable addition to any collection of electronics reference books. Contained are 1373 pages packed with information. In leather styled finish. Only £6.50, p.p. 50p.

THE RADIO CONTROL MANUAL. Contains numerous plans, photographs and instructions. A large format hardback book published at £1.25. Bargain price 60p, p.p. 20p.

THE THEORY AND DESIGN OF MAGNETIC AMPLIFIERS. 487 pages. Published at £1.75. Bargain price 75p, p.p. 25p.

WORKED EXAMPLES IN ALTERNATING CURRENT. A must for the student, technician and electrical engineer. Contains numerous examples and how they were arrived at. Published at £1.25. Bargain price 60p, p.p. 20p.

THE BARGAIN BOOK GAZETTE. Contains thousands of interesting new and out of print books at bargain prices. Subjects include all types of hobbies, collecting, 1001 interests. Published regularly and sent free on request.

Dept. R. C. GERALD MYERS (Publisher & Bookseller), 138 Cardigan Rd., Headingly, Leeds 6, Yorks. (Callers Welcome).

SOCKET SETS



£6.99 p+p 35p

Construction and repairs made easy with this 1/2 sq. drive high quality steel socket set. Bright chrome plated parts,

strong metal box with snap catches. 39 piece (as illus.) with 11AF, 11MM & 11BA sockets. Reversible ratchet, 2 extensions, sliding T-bar, flexible handle, tommy bar. 17 piece in plastic box with either 11AF, 11MM or 11BA sockets, same accessories as 39 piece £4.49 p&p 35p. (State AF, MM or BA when ordering).

SILHILL PRODUCTS Dept. REC8
226 Mary Street, Birmingham B12 9RJ. Tel. 021-440 3600

MORSE MADE EASY BY THE RHYTHM METHOD!

FACT NOT FICTION. If you start RIGHT you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.)
Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it. It's as easy as learning a tune. 18-W.P.M. in 4 weeks guaranteed. For Complete Course 3 Records & Books send £4.95 including P.P.I. etc. (overseas surface mail £1 extra.)
For further details of course Ring 01-660 2896 or send large S.A.E. for explanatory booklet to:—S. BENNETT, G3HSC (Box 38) 45 GREEN LANE, PURLEY, SURREY

BUY THIS BEST SELLER

NEW EDITION OF T.V. FAULT FINDING 405/625 LINES



REVISED & ENLARGED
Edited by J. R. Davies
132 pages PRICE 90p

Over 100 illustrations, including 60 photographs of a television screen after the appropriate faults have been deliberately introduced.

Comprehensive Fault Finding Guide cross-referenced to methods of fault rectification described at greater length in the text.

Price 90p from your bookseller.
or post this Coupon together with remittance for £1.02 (to include postage) to

DATA PUBLICATIONS LTD.
57 Maida Vale, London, W9 1SN

Please send me the 5th revised edition of TV Fault Finding. Data Book No. 5

I enclose cheque/crossed postal order for

NAME

ADDRESS

.....

BLOCK LETTERS PLEASE

SMALL ADVERTISEMENTS

(Continued from page 61)

WANTED: *Everyday Electronics* Volume 1 Nos. 1-5, May 1973. Also *Practical Wireless* January 1973. Price please to:- J. W. Farrar, 11 Constantine Road, North Bitchburn, Crook, Co. Durham.

WANTED: To purchase sheet music, light classical, musicals, etc. Box No. G280.

WANTED: Decoder Type 6, ex Grundig radiogram KS560. Also wanted Tannoy truncated horn speaker. Leeves, Kingsnympton, North Devon.

PERSONAL

JANE SCOTT FOR GENUINE FRIENDS. Introductions to opposite sex with sincerity and thoughtfulness. Details free. Stamp to: Jane Scott, 3/Con North St. Quadrant, Brighton, Sussex, BN1 3GJ.

IF YOU HAVE ENJOYED A HOLIDAY on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from: — The Hon. Membership Secretary, The Broads Society, "Icknield", Hilly Plantation, Thorpe St. Andrew, Norwich, NOR 85S.

ARE YOU ADVENTUROUS? If so, you can make exciting new friends. Write: S.I.M. Computer Dating, (REC/3), 109 Queens Road, Reading, Berks.

SPONSORS required for exciting scientific project. Norwich Astronomical Society are building a 30" telescope to be housed in a 20' dome of novel design. All labour being given by volunteers. Already supported by Industry and Commerce in Norfolk. Recreational. Educational. You can be involved. Write to: NAS Secretary, The Manse, Back Lane, Wymondham, Norfolk.

YOUNG MAN DISABLED needs work at home. Electronic/wire assembly. Would collect and deliver. Mr. B. Grimes, Llainwen, Glanrhyd, Cardigan, Wales, SA43 3PE.

ESSEX GARDENERS. Buy your Bedding and rock plants, shrubs, etc., also cacti from May's Nurseries, 608 Rayleigh Road, Hutton, Brentwood, Essex. Callers only. Monday to Saturday.

BARGAIN COMPONENT PARCELS contain some very useful bits and pieces. Save yourself £s on these well selected parcels 2 kilos nett weight £1.80.

BRAND NEW WIRE-WOUND RESISTORS 1-7 watts, good selection, 100 for £1.55.

ASSORTED CAPACITORS, Silver Mica, Tubular and Disc Ceramics, Polystyrene. Tremendously good selection 300 for £1.55.

SPECIAL OFFER — Metallised Polyester Capacitors by Brie, Mullard, etc. Values include .01/160V, .01/250V, .015/160V, .022/160V, .033/160V, .047/160V, .068/160V, .1/160-250V, .22/160V, etc. This is a bargain not to be missed, 100 for £1.95.

Please note all prices include Postage and V.A.T.

**MAIL ORDER ONLY
XEROZA RADIO
1, EAST STREET,
BISHOPS TAWTON,
DEVON**

INTERNATIONAL SHORT WAVE LEAGUE



Membership £3.75 per annum (U.S.A. \$10.00) including 12 monthly issues of *Monitor* — the League journal. Including free use of all Services, QSL Bureau etc.

THE LARGEST S.W.L. ORGANISATION IN THE WORLD

For full details write to:

**The Secretary,
I.S.W.L.,
1, GROVE ROAD, LYDNEY,
GLOS. GL15 5JE.**

ENGINEERS

FREE

YOURSELF FOR A

BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through our low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.



CUT OUT THIS COUPON
CHOOSE A BRAND NEW FUTURE HERE!
Tick or state subject of interest. Post to the address below.

<input type="checkbox"/> Inst. Motor Ind. M.A.A./L.M.L. Man. Dip. Gen. Auto Eng. Auto Diesel Maint. Motor Mech. Service Station & Garage Man.	<input type="checkbox"/> Radio Serv. Maint. & Rep. Pract. Radio & Elec. (with self-build kit) Radio Ans. Exam Electronic Eng. Gen.	<input type="checkbox"/> Gen. Diesel Eng. Carpentry & Joinery Painting & Dec. C.E.I. (Part 1) Works Man. etc. etc.
<input type="checkbox"/> Tech-Prim. Gen. Elec. Eng. AERONAUTICAL ENGINEERING Air Reg. Board Certificates Gen. Aero Eng.	<input type="checkbox"/> TELECOMMS. C & G Telecomm.	<input type="checkbox"/> DRAGHTS-MANSHIP Inst. of Eng. D'men & Designers Gen. D'manship Architectural D'manship
<input type="checkbox"/> AUTO ENGINEERING C & G Auto Eng. Pract.	<input type="checkbox"/> MECHANICAL ENGINEERING Soc. of Eng. General Mech. Eng. Welding Maint. Eng.	<input type="checkbox"/> CONSTRUCTION & BUILDING Inst. of Build. Clerk of Works Diploma Gen. Building Heat, Vent. & Air Con.

To ALDERMASTON COLLEGE, Dept. TRE 08, READING RG7 4PF
Also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London, EC2Y 5EJ Tel: 01-628 2721

NAME (Block Capitals Please) _____ TRE 08
ADDRESS _____ POSTCODE _____
Other subjects _____ Age _____
Accredited by C.A.C.C. Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

SMALL ADVERTISEMENTS

Use this form for your small advertisement

To: The Advertisement Manager, Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please insert the following advertisement in theissue of RADIO & ELECTRONICS CONSTRUCTOR

➔			

15 words at 5p
= 75p.

**ALL WORDING
IN
BLOCK LETTERS
PLEASE**

I enclose remittance of.....being payment at 5p a word. **MINIMUM 75p.**
Box Number, if required, 10p extra.

NAME.....

ADDRESS.....

Copy to be received four weeks prior to publication. Published on the 1st of every month.

DATA BOOK SERIES

- DB5 TV FAULT FINDING**
132 pages. Price 90p, P. & P. 12p
- DB6 RADIO AMATEUR OPERATOR'S HANDBOOK**
88 pages. Price 70p, P. & P. 10p
- DB16 RADIO CONTROL FOR MODELS**
Now out of print
- DB17 UNDERSTANDING TELEVISION**
512 pages. Revised edition available September
- DB18 AUDIO AMPLIFIERS**
128 pages. Price 53p, P. & P. 12p
- DB19 SIMPLE SHORT WAVE RECEIVERS**
140 pages. Price 80p, P. & P. 12p

I enclose Postal Order/Cheque for.....in payment for.....

NAME.....

ADDRESS.....

(BLOCK LETTERS PLEASE)

Postal Orders should be crossed and made payable to Data Publications Ltd.

Overseas customers please pay by International Money Order.

All publications are obtainable through your local bookseller.

Data Publications Ltd., 57 Maida Vale, London W9 1SN

PLEASE MENTION THIS MAGAZINE WHEN WRITING TO ADVERTISERS

FOR THE BEGINNER



SERIES RESONANCE

In (a) an alternating voltage whose frequency can be varied is applied to a series tuned circuit consisting of an inductor (or coil) and a capacitor in series. At a low frequency the capacitive reactance of the capacitor is greater than the inductive reactance of the inductor and at a high frequency the reverse applies. There must then be a frequency in between at which the two reactances are equal. This is the resonant frequency.


At the resonant frequency the two reactances cancel out and the only opposition to alternating current flow is the inevitable resistance in the tuned circuit. At frequencies below some 20MHz this resistance is mainly provided by the wire of the inductor. Typical response curves for the circuit appear in (b). The curve peaks appear at the resonant frequency and the sharper curve corresponds to a tuned circuit with lower resistance.

The alternating voltages across the inductor and capacitor at resonance are equal and opposite in phase, and are greater than the applied voltage. The ratio between the voltage across the inductor or capacitor and the applied voltage represents the magnification factor of the tuned circuit. This is also equal to the quality factor, or Q, of the tuned circuit. Q increases as the resistance in the tuned circuit decreases.

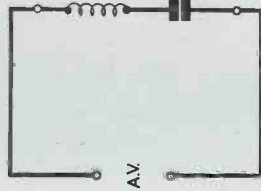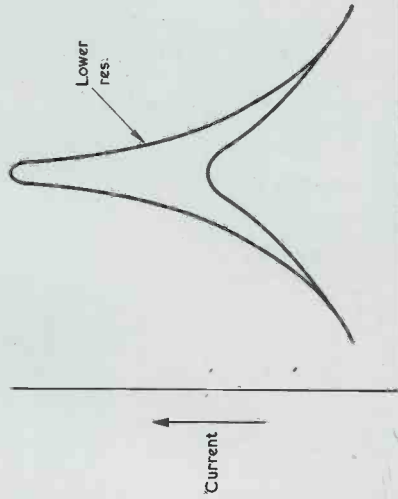Resonant frequency is defined by the equation in (c), where f is in Hz, L is in henrys and C is in farads. It may be varied by making the capacitance variable, as in (d), or the inductance variable, as in (e). A typical method of varying inductance consists of moving an iron-dust core into or out of the windings of the inductor.



(a)

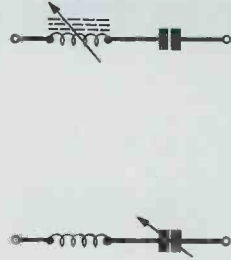

(d)

(e)

$$f = \frac{1}{2\pi\sqrt{LC}}$$

(c)

J68E

SPECIAL PRE-PUBLICATION OFFER

Paperback edition


(Published price £3.35) **£2.65** – Save 70p

Hardback edition

(Published price £6.90) **£5.25** – Save £1.65

Both prices include P. & P.

THIS OFFER ENDS ON THE 30th SEPTEMBER

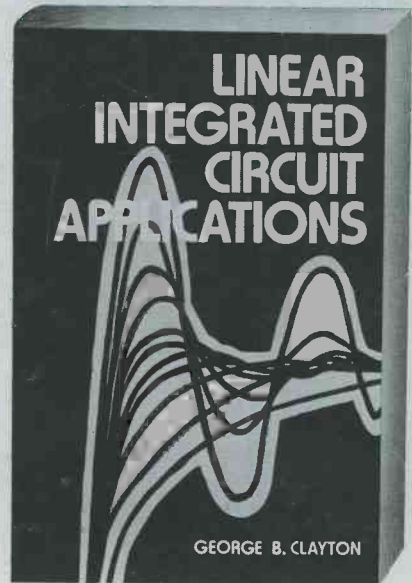

Published by Macmillan

The great practical value of integrated circuits is now fully established in the design of electronic circuits and systems. However, it has only been in recent times following the general acceptance of the first linear integrated circuits—operation amplifiers—that manufacturers have turned their efforts to a wider range of linear integrated circuits.

This book is concerned with these newer circuits now available which find their main use in signal measurement and processing systems.

A practical approach is emphasised throughout and the reader is encouraged to try out the devices for himself.

In this book the applications of operational amplifiers as measure-

ment amplifiers and the use of operational amplifiers in active filter circuits are dealt with. Subsequent chapters are concerned with the more recently introduced linear integrated circuits, monolithic integrated circuit modulators, four quadrant multipliers, timers, waveform generators and phase locked loops.

Numerical exercises are included at the end of each chapter. The book should prove useful to both the practising experimental scientist and the undergraduate student in scientific or engineering disciplines. The practical approach which it adopts should serve as a balance to the rather intensive theoretical treatment given in many undergraduate courses in electronic engineering.

To: **Data Publications Ltd., 57 Maida Vale, London W9 1SN**

Please send to me when published in October copy/ies of

LINEAR INTEGRATED CIRCUIT APPLICATIONS

..... Paperback edition

..... Hardback edition (Please tick required edition.)

I enclose Postal Order/Cheque for

Name:

Address:

.....

..... (Block letters please)