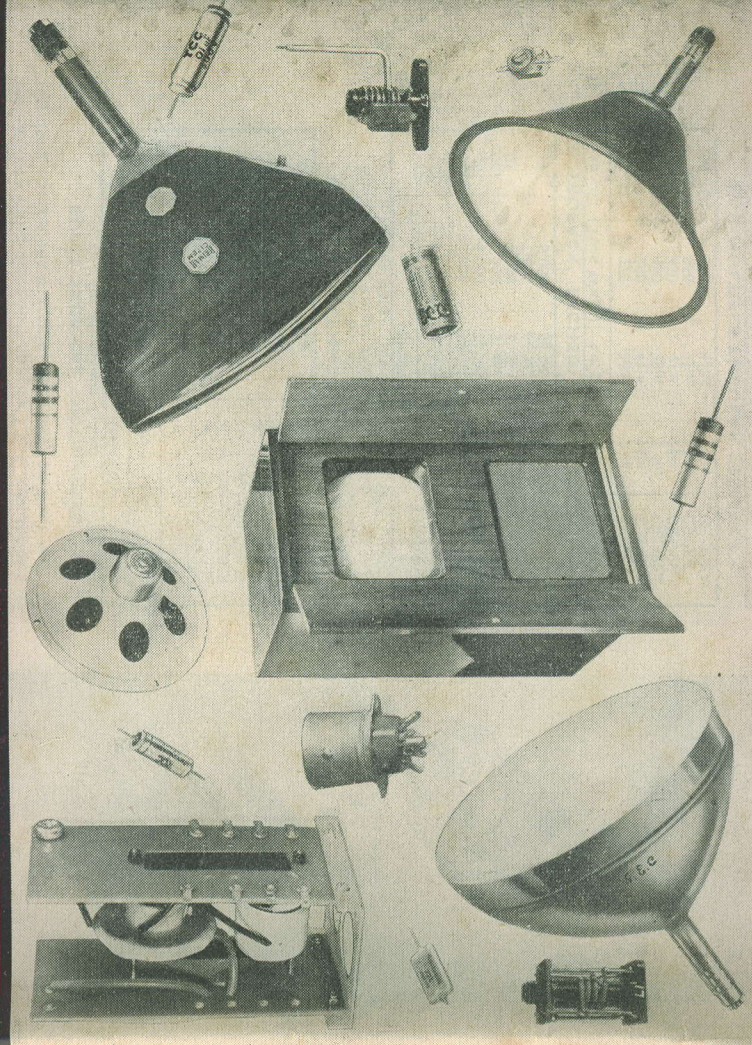


The RADIO CONSTRUCTOR

for the Radio and Television Enthusiast



IN THIS ISSUE . . .


- LARGE SCREEN TV • MAGNETIC TAPE RECORDER • REMOTE CONTROL BY RADIO • DESIGN FOR "ECONOMY" MAINS RECEIVER
- TWO-STATION RF UNIT • Simple Long Wave Conversion • NFB Compensating Volume Control • Query Corner • In Your Workshop Mainly for the Beginner

etc., etc.

16

RADIO CONSTRUCTOR

? WHAT IS WRONG ?

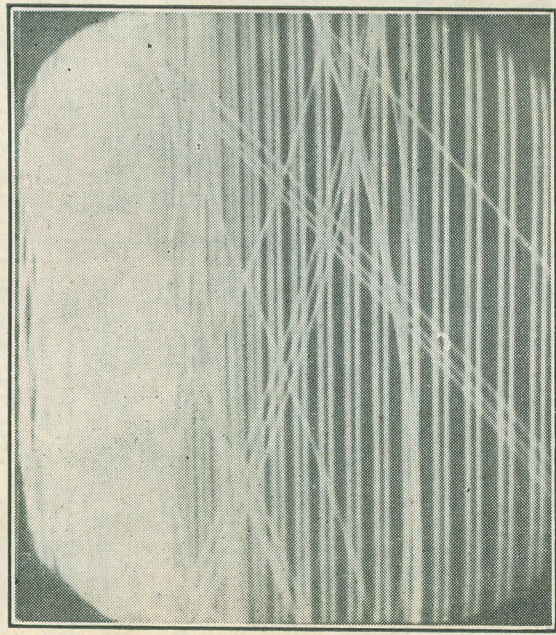

This, and many other faults, are described and illustrated in our latest publication . . .

TV FAULT FINDING

Data Book Series No. 5

This is a completely new production—not a reprint—and is unique in that it is lavishly illustrated by photographs taken from the screen of a television exhibiting the faults under discussion. A handy fault-finding guide is incorporated, and this is cross-referenced to the book itself.

100 illustrations and diagrams


80 pages, high quality paper with heavy art board cover

PRICE 5 SHILLINGS, Postage 3d.

Available from your usual supplier, or direct.
(Trade enquiries invited)

AMALGAMATED SHORT WAVE PRESS LTD.
57 MAIDA VALE, LONDON, W.9.

Tel.: CUN 6518

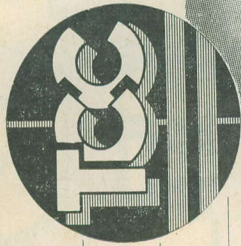

Fully specified for the

“RADIO CONSTRUCTOR”

Large Screen TV

The condensers listed here are representative of a vast range of all known types. We have been Condenser Specialists since 1906, and the fact that so many well-known radio designers specify T.C.C. condensers as standard equipment is ample testimony to their worth.

SUPER TROPICAL 'METALMITES'
(in Aluminium Tubes)

Capacity µF.	Wkg. Volts D.C.		Dimensions		Type No.
	at 71°C.	at 100°C.	Length	Dia.	
.001	1000	750	1 1/2 in.	1 in.	CP49W
.002	1000	750	1 1/2 in.	1 in.	CP49W
.001	500	350	1 in.	.34 in.	CP30S
.01	500	350	1 in.	.34 in.	CP33S
.05	500	350	1 1/2 in.	1/2 in.	CP37S
.005	350	200	1 in.	.22 in.	CP31N
.01	350	200	1 in.	.25 in.	CP32N
.1	350	200	1 1/2 in.	1/2 in.	CP37N
.05	200	120	1 1/2 in.	.34 in.	CP34H

'VISCONOL CATHODRAY' CONDENSERS

For Television and allied H.V. applications.
Cap. Range: .0005µfd. to 1µfd.
Voltage Range: 750 to 75,000 at 60°C.

Cap. in µF.	Max. Wkg. at 60°C.		Dimens. (Overall)		Type No.
	Length	Dia.	Length	Dia.	
.0005	25,000	1 1/2 in.	5 1/2 in.	1 1/2 in.	CP-57.HOO
.001	6,000	3 1/2 in.	3 1/2 in.	1 1/2 in.	CP-55.QO
.01	12,500	3 in.	3 in.	1 3/8 in.	CP-56.VO
.1	6,000	6 1/2 in.	2 in.	1 1/2 in.	CP-58.QO
.25	7,000	5 3/8 in.	2 1/2 in.	2 1/2 in.	CP-59.MO

'LECTROPACK' ETCHED FOIL ELECTROLYTICS

Cap. µF.	Peak Wkg.	Dimensions		Type No.
		Length	Dia.	
8-32	275	2 1/2 in.	1 in.	CE34HE
60-100	350	4 1/2 in.	1 in.	CE37LEA
8-16	450	2 1/2 in.	1 in.	CE34PEA
32-32	450	4 1/2 in.	1 in.	CE37PE
100	350	2 1/2 in.	1 1/2 in.	CE10LE
100-100	350	4 1/2 in.	1 1/2 in.	CE36LEA



HI-K MULTIPLE TUBULAR CERAMICS

Capacity pF.*	Wkg. Voltage		Dimensions		Type No.
	D.C.	A.C.	Length	Dia.	
500	500	250	10 mm.	4.5 mm.	2CTH 310/W
2X 500	500	250	10 mm.	4.5 mm.	2CTH 310/W
2X 1500	500	250	15 mm.	4.5 mm.	2CTH 315/W
2X 2200	500	250	22 mm.	6 mm.	2CTH 422/W
3X 500	500	250	15 mm.	4.5 mm.	3CTH 315/W
3X 1000	500	250	15 mm.	4.5 mm.	3CTH 315/W
3X 2200	500	250	22 mm.	6 mm.	3CTH 422/W

*Guaranteed not less than stated values at 25°C.


● SEE US AT STAND 72
AT THE RADIO SHOW

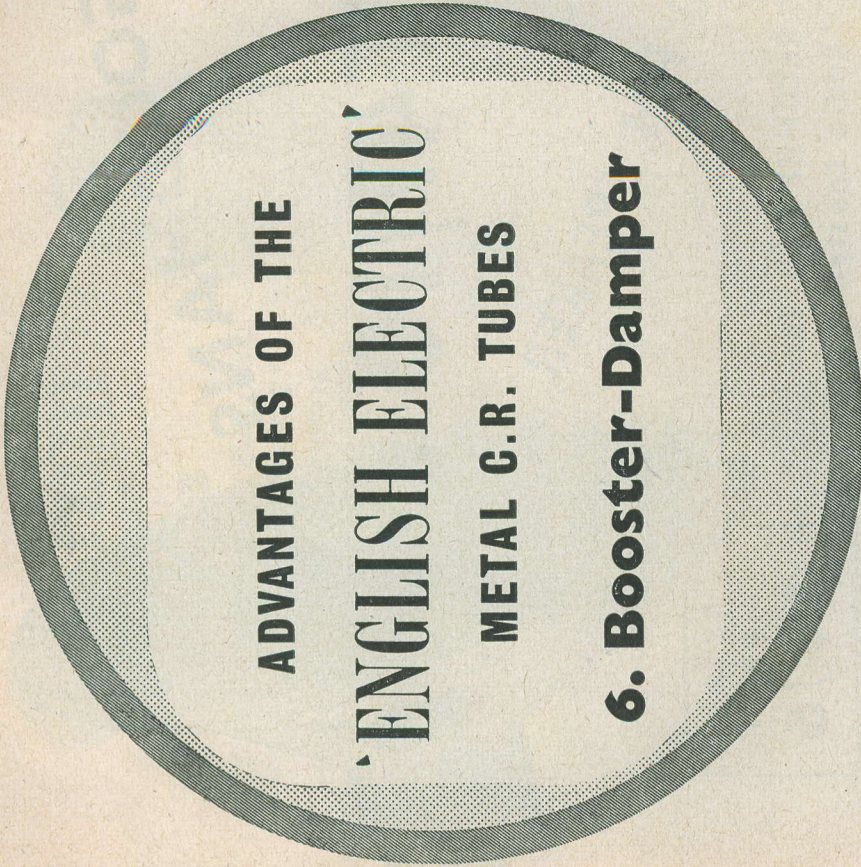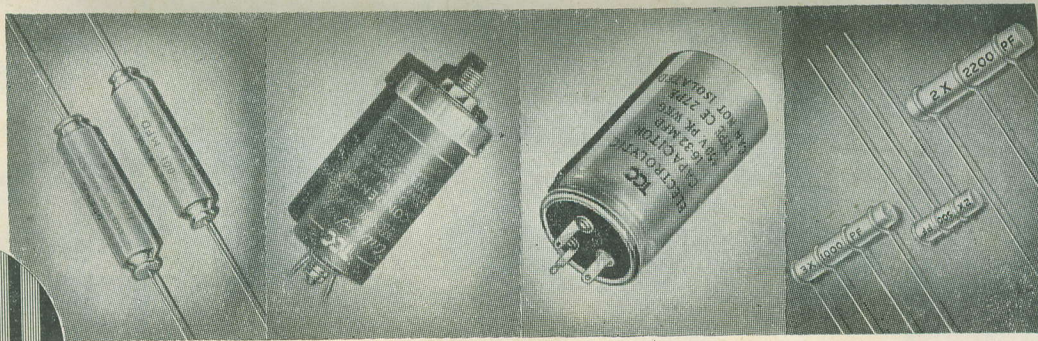THE TELEGRAPH LTD.
CONDENSER CO. LTD.
RADIO DIVISION W.3
NORTH ACTON W.3
Telephone: ACORN 0061



ADVANTAGES OF THE
'ENGLISH ELECTRIC'
METAL C.R. TUBES
6. Booster-Damper


The requirements of scanning power for the T901 wide angle tube are considerable, it is therefore necessary to obtain a high degree of efficiency in the scanning circuits in order to reduce the H.T. current drain to a reasonable figure.
For this reason the Booster-Damper type of circuit is recommended, as it is the most efficient yet known.
In the Booster-Damper arrangement a diode is connected in the deflector circuit to arrest the oscillation which occurs during the flyback period, the current, after the natural overswing, being forced to decay in an approximately linear manner in the deflector coils — thereby providing the power for the first part of the subsequent scan.
The rectified voltage obtained by use of the diode is added in series with the receiver H.T. supply to the driver valve, thus the greater part of the energy stored in the deflecting inductance at the end of each scan is returned to the circuit.
The H.T. current drains of this form of circuit may be no greater than that required for a resistance-damped scanning circuit driving an ordinary narrow-angle tube, at a low E.H.T. voltage. The high "Boost" voltage existing at the damper cathode after smoothing can be used to supply the first anode of the T901.

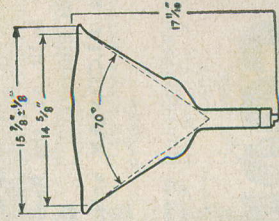

PRICE £24.6.5
Tax Paid

BRITISH MADE BY 'ENGLISH ELECTRIC'

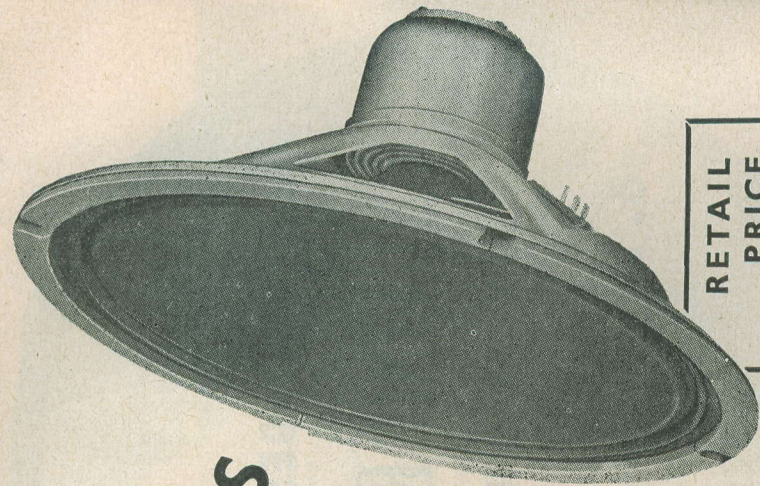THE ENGLISH ELECTRIC COMPANY LTD., TELEVISION DEPT., QUEENS HOUSE, KINGSWAY, LONDON, W.C.2



GOODMANS

T47/10

10" P.M. SPEAKER

As RECOMMENDED for the
 "Radio Constructor"
 16" TELEVISOR

being built at the Radio Show by Brimar, G.E.C. and English Electric. Centre-pole and pot construction. Latest ALCOMAX anisotropic magnet — low leakage.

RETAIL PRICE
44/6

See it at the
RADIO SHOW
 Earl's Court
 London
 Aug. 26—Sept. 6
STAND 41




GOODMANS

GOODMANS INDUSTRIES LIMITED, AXIOM WORKS, WEMBLEY, MIDDX.

Osram

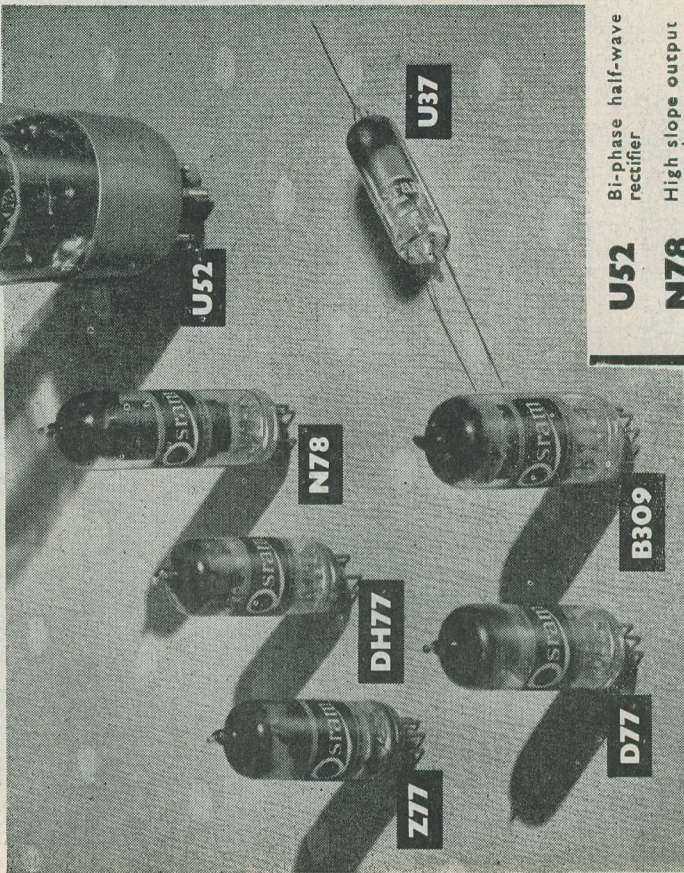VALVES
 ARE RECOMMENDED FOR THE
 "RADIO CONSTRUCTOR'S"
 LARGE SCREEN TELEVISOR



- U52** Bi-phase half-wave rectifier
- N78** High slope output pentode
- DH77** Double-diode triode
- Z77** High slope R.F. pentode
- D77** Low impedance double diode
- B309** Medium impedance double triode
- U37** Miniature E.H.T. rectifier


★ Only by using the valves specified can you be sure of the best results from your television.
 ★ The designers have found that the valves illustrated are the best for the job.
 ★ Use Osram valves for their proved consistency of performance.

Also specified :- G.E.C. 16" Aluminised cathode ray tube Type 6901 A. Further details will be given in the October issue of "Radio Constructor."

The General Electric Co., Ltd., Magnet House, Kingsway, W.C.2


LARGE SCREEN TELEVISION

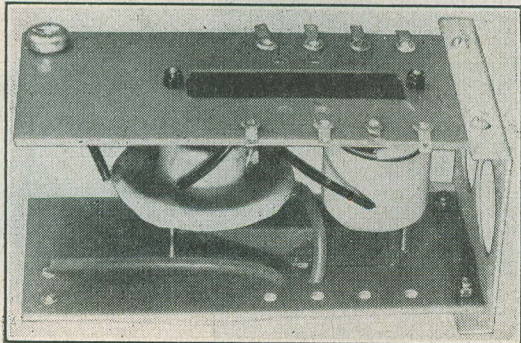Wide range Scanning can only be accomplished by using **HIGH EFFICIENCY COMPONENTS** and "ALLEN" can supply the **WHOLE** range necessary for this **NEW TECHNIQUE**.



THE LINE/SCAN TRANSFORMER

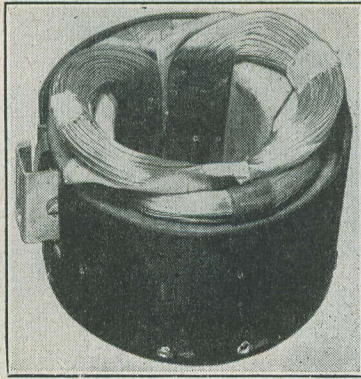Capable of fully scanning any C.R. Tube from 9" up to 17" (Double D) Scan at 16 KV.



THE DEFLECTOR COILS designed for a 70° Scan

FOCUS COILS - FRAME TRANSFORMERS LINEARITY - WIDTH CONTROLS are all available to complete the range for 16" C.R. Tubes.

Circuit Diagram given **FREE** with every complete set of components.
Circuit Diagram supplied separately - Please send 9d. and s.a.e.
All details on request - Please send s.a.e.

Why not write for the complete range of Quality Components made in our "CROWN" Works under expert supervision.

ALLEN COMPONENTS LIMITED

(SPECIALISTS IN THE MANUFACTURE OF L.T. TRANSFORMERS)

Crown Works, 197 Lower Richmond Road, Richmond, Surrey.
Telephone PRO. 9013


Use the

BRIMAR C17BM

for the **LARGE SCREEN TELEVISOR**

This 17-inch all-glass triode C.R. Tube has a Rectangular face the exact shape and size of the pictures it presents, and thus avoids the wasted screen area of round tubes. The Aluminized Screen gives a picture 30 per cent. brighter than equivalent non-aluminized types, and freedom from ion burn is secured without an ion trap to adjust.

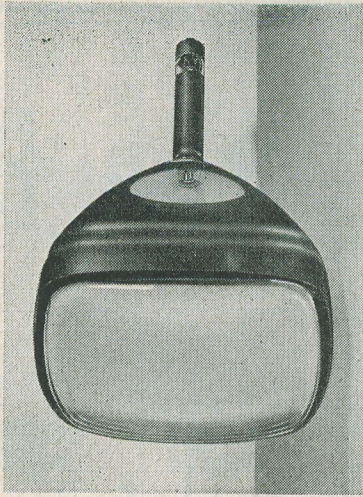On the outside of the glass envelope is a conductive coating which, when earthed, forms with the anode the E.H.T. reservoir condenser, thus saving the cost of this component. The earthing of the tube exterior also reduces shock hazards and mounting difficulties.



CHARACTERISTICS

Heater Voltage 6.3 v.
Heater Current 0.6A.
Anode Voltage (nominal) 14kV.
Grid Bias (for cut off)—60V (nominal)
Overall dimensions:— Length 19 $\frac{7}{8}$ "
Height 12 $\frac{1}{4}$ " Width 15 $\frac{3}{8}$ "
Picture size 140 sq. in.

This C.R. Tube can be used in the receiver described in this Journal without any additions to the circuit. The following Brimar Valves are also specified:—

- | | |
|-----------------------------|---------------------------|
| 6AM6 Miniature R.F. Pentode | 6CD6G Line output Tetrode |
| 6AL5 " Double Diode | 6U4GT Efficiency Diode |
| 12AX7 " Double Triode | 1T2/R16 E.H.T. Rectifier |
| 6AQ5 " Output Tetrode | RM 4 Metal Rectifier |
| 12AU7 " Double Triode | |

Standard Telephones and Cables Limited.


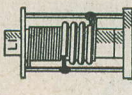
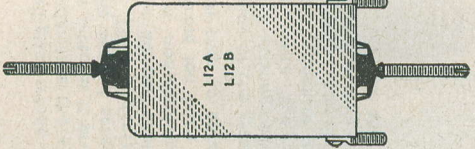
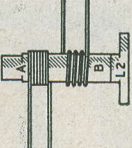
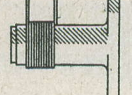
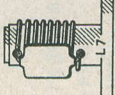
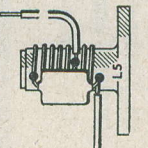
BRIMAR VALVE WORKS, FOOTSCRAY, SIDCUP, KENT

FOOTSCRAY 3333



Edited by C. W. C. OVERLAND, G2ATV

DENCO SUPERHET SOUND & VISION COILS FOR LARGE SCREEN TELEVISION

		
CH.1. CH.2. CH.3. 2/6d. EA. L.1.	4/6d. EA.	L.12A/B. 8/6d. EA.
		
L.2A/B. 2/9d. EA.	L.3.4.6 & 8. 2/6d. EA.	L.7. 3/6d. EA.
		
L.5. 3/9d. EA.		

- Each coil is complete with an Iron Dust Slug, Marked with its appropriate number and each packed in a small cardboard carton.
- Brass slugs for L1 and L2A/B are available price 4d. each.
- Also in the course of production are the Focus, Line Linearity, Width and Deflector Coils, Frame Blocking Oscillator and Line Output Transformer which will be readily available in Mid-August.

DENCO (CLACTION) LIMITED.

357/9, Old Road, Clacton-on-Sea, Essex.

CONTENTS

Suggested Circuits: NFB Compensating Volume Control, by G. A. French - - - - -	9
Radio Miscellany, by Centre Tap	10
Remote Control By Radio, Part One, by F. C. Judd, G2BCX	12
A Simple Long Wave Conversion by F. L. Bayliss, A.M.I.E.T.	15
It Darned Well Did, Too! by H. Dudley Stilton - - - - -	17
A Magnetic Tape Recorder, Part One, by L. F. Sinfield, A.M.I.P.R.E. - - - - -	18
In Your Workshop, by J.R.D. - - - - -	24
Mainly for the Beginner: Resistance, by H. E. Smith, G6UH	26
Large Screen TV—The Radio Constructor's 16" Television, Part Seven - - - - -	30
Mounting the Brimar C17BM CRT - - - - -	35
Query Corner - - - - -	40
From Our Mailbag - - - - -	42
Two-Station RF Unit, by R. W. Hill - - - - -	43
Design for an "Economy" Mains Receiver, Part One, by R. K. Vinycumb, B.Sc. - - - - -	48
Trade News - - - - -	51

Editorial

THE series of articles which we are featuring on the construction of a Large Screen Television seems to have aroused the interest of a good many readers, to judge by our correspondence. This is no doubt due to the fact that this periodical is the first in this country to deal with wide angle deflection on a practical basis; it also shows that the radio constructor, as hitherto, is not content merely to go on building the same old stuff.


We cannot, naturally, fill our pages with nought but the most modern techniques—there are all grades amongst our readers, from the beginner to those who can, and do, tell us a few things! We must, therefore, in all fairness include articles which are "kid stuff" to some, and others which cater adequately for the more advanced.

If you have a suggestion to make about a subject you would like covered, let us have it. If you can write an article about a subject which you think will be of interest to other readers, again, let us have it. A copy of the Index to Vol. 5, which is now available, will enable you to assess quickly the field covered by past issues.

Harking back to our Large Screen Television, readers will be interested to know that they will be able to see completed models at the National Radio Show at Earls Court—see announcement on page 47. We are glad to take this opportunity of expressing our thanks to those manufacturers who have assisted us, not only through their advertising support in these pages, but also with advice and practical help on the constructional and other problems involved.

A Companion Journal to *THE RADIO AMATEUR*

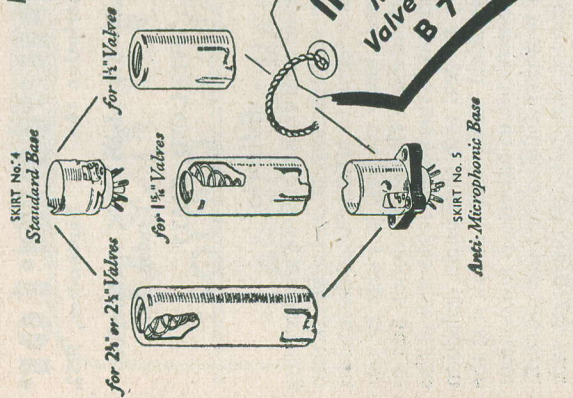Recognised as the Most Reliable Valveholders



B7G Valveholders

are now available moulded in:—
Phenol Formaldehyde (Black).
Nylon loaded Phenol
Formaldehyde (Natural Brown).

P.T.F.E.
and now **MYCALEX.**

Wholesale Enquiries:—

CYRIL FRENCH LTD.,
High St., Hampton Wick,
Middlesex. KIN. 2240.

Manufacturers' Enquiries: THE McMURDO INSTRUMENT CO. LTD., VICTORIA WORKS,
ASSTEAD, SURREY ASSTEAD 3401

Suggested Circuits for the Experimenter


The circuits presented in this series have been designed by G. A. FRENCH specially for the enthusiast who needs only a circuit and the essential relevant data.

No. 21: NFB COMPENSATING VOLUME CONTROL

This circuit does not, as its title might perhaps imply, control volume by varying negative feedback. Instead, it controls volume in the normal fashion, with the difference that it also automatically increases feedback as volume is reduced. Thus, when the associated amplifier is working at a low level, a relatively large amount of feedback is possible; whilst, when the amplifier works at a high level, this feedback is reduced, allowing a greater degree of amplification to be obtained than would otherwise be the case.

In the diagram, negative feedback is obtained by applying the voltage appearing across the output transformer secondary to the potentiometer R3, R4, from which a suitable feedback voltage is obtained and applied to the bottom end of R2. Assuming that C has negligible impedance at audio frequencies, this feedback voltage can be considered as being fed to a potentiometer formed by R2 and R1 in series, the slider of R2 tapping into this potentiometer. At the same time, the input voltage appears across R1 and R2 in parallel. Thus, so far as the grid of the first AF valve is concerned, the input voltage has its greatest effect when the slider of R2 is at the top end, whilst the feedback voltage has its greatest effect when the slider is at the bottom end.

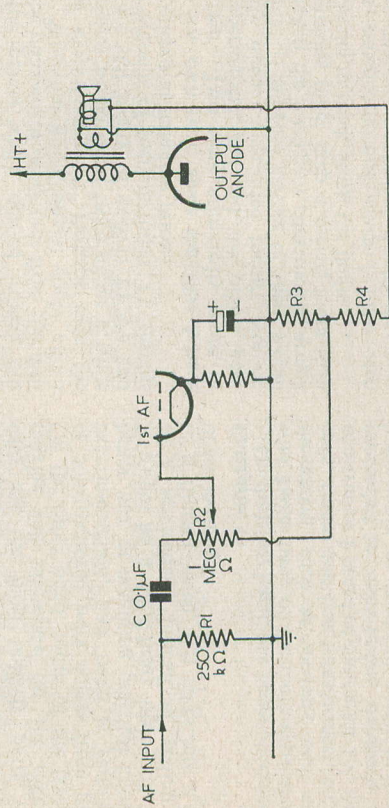This is, admittedly, a rather vague explanation of the functioning of the circuit, but it would be difficult to go into greater detail in a short descriptive text of this type. Mathematically-minded readers would probably find it interesting to undertake a more detailed analysis.



C720

SMITH'S OF EDGWARE ROAD

THE COMPONENT PEOPLE

can now supply

Allen Components for
Wide Angle (70°) C.R. Tubes
as specified in "Radio Constructor"

Deflector Coils DC300	...	42/-
Width Coil GL18	...	10/-
Linearity Coil GL16	...	35/-
Focus Coil FC302	...	50/-
Linescan Transformer LO308	...	20/-
Frame Transformer FO305	...	48/-
Electrovoice Transformer 104C	...	60/-
104D
COD or CWO. All orders over £1 carr. paid		

H. L. SMITH & CO., LTD.

287/9 Edgware Road, London, W.2

Telephone: Paddington 5891

Hours 9 till 6 (Thursday, 1 o'clock)

Near Edgware Road Stations, Metropolitan and Bakerloo

TELEVISION CABINETS

All Sizes up to 16" Tube

Specially Designed for 'Radio Constructor' Set, and illustrated on this Month's Front Cover.

Price **£18:10** Carriage £1

SEND FOR ILLUSTRATED LEAFLET

H. ASHDOWN

98 HERTFORD ROAD,
EDMONTON, N.9

TOT 2621

The Circuit in Practice

In practice, the circuit should be simple enough to bring into operation. After ascertaining which method of connection to the speaker transformer gives negative instead of positive feedback, all that remains to be done is to find experimentally suitable values for R3 and R4. It would be advisable to keep these values fairly low; together they should add up to a figure between 250 and 1,000 ohms.

The most suitable values for R3 and R4 will be those which cause a small attenuation for high volume settings and a relatively large attenuation for low volume settings. For comparative tests, the negative feedback can be brought in and out of circuit by

interrupting the lead between the speaker transformer secondary and R4.

It will have been noticed that a capacitor has been connected between R1 and R2. This has been done in order to show how the circuit may be applied to practical use. In a receiver, for instance, R1 could be the DC load of a diode detector. Alternatively, with a slight alteration in value for matching purposes, it could be the anode load of a previous AF valve.

Before concluding, it must be pointed out that an increase in feedback will reduce the output impedance of the amplifier. This fact may limit the change in feedback which will be permissible, especially when certain types of output valve are used.

RADIO MISCELLANY

HOME-BUILDING — FIXATIVES — SOLDERING IRONS

CENTRE TAP talks about

I have been greatly pleased to see such widespread television constructional activity not only continuing, but expanding, despite the lack of realism among those who forecast that TV receivers would be beyond amateur construction and home adjustment. Oddly enough, few of the home-built sets I have seen worked properly straight-away, even in the kit and wiring diagram class! Perhaps that is simply my experience, and most of those I haven't seen needed only minor adjustment before as-good-as-a-bought-set performance was obtained. With the kit sets, no doubt, the little points which needed ironing out were the outcome of departures from specified parts. Who but a millionaire could afford to buy everything new? Perhaps even the millionaires would think twice about it while there are still plenty of ex-WD EF50's and a fair amount of manufacturers' TV surplus being offered at tempting prices.

For my own part, since the War I have built four. Two were admittedly more or less experimental, but did the others perk properly when I first tried them? Not on your life! I suppose neither of them would have taken the intelligent constructor, armed with nothing other than a meter, more than a few hours to track down the faults.

This experience, and what I have seen among amateurs generally, almost convinces me that, even with detailed instructions,

TV building is not a job for the beginner unless he has the help of a friend with a fairly good background of radio experience. By this I do not mean to imply expert knowledge of TV practice. The reader who can take most of the articles in Radio Constructor with reasonable understanding should be adequately able to methodically (if slowly) track down the little difficulties that inevitably seem to arise.

Perhaps my conclusions are also coloured by hearing much of those who do have trouble in getting proper results, or of the optimists who use the most unlikely parts without making full allowance for the differences. On the other hand, much of the fascination of constructional work comes from personal experimentation, and there is certainly no better way of acquiring practical knowledge. It would be a faint heart who took his set to a serviceman, instead of getting down to it himself—even if it takes him a half-a-dozen evenings.

Enterprise

On the other hand, one hears of constructors who make many of the more expensive parts themselves, such as focusing and scanning coils, frame and line transformers, etc. One constructor I heard of built a kit TV, and then proceeded to more-or-less duplicate it with home-made or modified parts, testing them in the working receiver as he finished them.

Versatility

Thinking still of TV construction reminds me that a couple of recent visitors congratulated me on the neat and clean soldering on one of my latest chassis. By careful planning and the use of specially selected components, I had managed to get everything into a compact space. With TV, of course, a tinned steel chassis (or one to which you can solder direct) is simply a "must." It's asking for trouble to use aluminium, except for the power supply and time bases.

The earth returns to this particular chassis had been soldered with an extra heavy bit and a little judicious "rubbing" with the iron, the easy (and only) method of getting the solder to run smoothly around the joint. Many of the $\frac{1}{2}$ -watt resistors, B7G valveholders and small mica capacitors had to be wired with a bit scarcely bigger than a thick wire. Yet they were all made with the same electric iron; a standard model fitted with a pencil bit. One of the first things I did after buying it was to make a heavy bit to use in place of the pencil. It was cut from an inch diameter copper rod which I hammered slightly oval at the business end. It was not, however, until fairly recently (when an urgent need arose) that I thought of making a fine-point bit on the same lines. Manufacturers would do well to market interchangeable bits to cover the wider range of work modern constructional practice requires. True, one can get a fairly heavy bit by using the iron with the pencil point removed, but one often needs something heavier, and it is always possible to use a little supplementary heat on the heavy attachment by standing it in a gas-ring if one is impatient to get it thoroughly hot.

With mine, it is only the matter of a few seconds work to change over the bits, and the uses I have found for them have amply justified the time spent in making them. The extremely thin one is on the longish side, which not only enables tiny components to be soldered without overheating them while allowing time for neat joints to be made, but eliminates the risk of scorching the adjacent components or the nearby insulation sleeving.

Overdue Replies

An apology is due to readers who have received no answer to communications addressed to me. A package of correspondence forwarded to my home from Maida Vale has failed to arrive, and is now three weeks overdue. Readers who have received no answer or acknowledgment from me relating to letters etc., sent before the 20th June, are asked to be good enough to write again. Mention of the fact will ensure top priority attention.

When he completed the second set he sold the first to a ready customer, pricing it on a cost-of-the-parts basis. Actually, he made quite a useful profit as the first set had been built some twelve months ago. Nearly all the main parts, including valves, have gone up 33 per cent. or more in the last year.

The 16-inch receiver, currently being described in the Radio Constructor, offers the opportunity for readers to build a de-luxe class receiver at a very considerable saving. With home construction the bigger the tube, the bigger the saving. There is no doubt that this set is going to prove very popular in the coming Season. To an even more marked degree than most home constructed TV's, it gives one a very solid advantage over its commercial counterpart, inasmuch as it can be readily modified at a later date to meet each advance in TV technique.

I had been Warned

Every reader who has done any coil or transformer winding will have read warnings regarding the choice of fixatives for anchoring enamelled wire in position. Ironically, I have warned readers myself on more than one occasion. Now I have had a horrible example of what happens.

A few weeks back I used some wire and, to avoid the remainder slipping off the well-filled reel, I bound the end in position, as a temporary measure, with a short length of adhesive tape. I should, perhaps, point out that it was not electricians' insulating tape.

This week when I needed the wire, I stripped off the tape only to find, to my great disgust, that it had played havoc with the enamel. Not only on the surfaces it had touched, but even to a depth of a couple of layers down. The enamel had turned a dirty yellowish-white and it fell away in powder when touched. This happened in the course of a few weeks, although the chemical action may have been accelerated by the warm sunlight it received. The reel had been left standing on a shelf beside the window.

One cannot be too careful with enamelled wire. Even the methylated spirits used to dissolve the shellac in making up varnishes used to "set" windings, may contain injurious substances.

The "commercial" grade of meths is safe in this respect. Unless you have solid shellac in hand, the use of uncoloured French polish is to be recommended. This, of course, is simply shellac dissolved in commercial methylated spirits, and it is not only ready for use but is perfectly safe for reasonably high-voltage insulation and, more important, harmless to the enamel.

REMOTE CONTROL BY RADIO

By F. C. JUDD, G2BCX

Applications of the Super-Regenerative Receiver and simple Self-Excited Transmitters for the Radio Control of Models, etc.

PART I.

Foreword

Many radio constructors have, no doubt, been intrigued at one time or another by the application of radio as the 'link' without wires' in remote control systems. As is probably well known, Radio Control of models is an extremely popular hobby, especially among model aircraft and boat enthusiasts, and whilst articles have, from time to time, been written on the subject, little information has been given beyond descriptions of commercially made apparatus and very simple servo-mechanisms. To take into account actual working models, as well as radio control circuits and systems, is beyond the scope of this article which will be confined strictly to circuit design, but it may be mentioned that there are many commercial kits of model aircraft, and boats, which are not beyond the skill of anyone with average abilities to construct, and which are quite suitable for radio control work.

The writer, who had never previously constructed a working model of anything, has with little or no difficulty built two model aeroplanes, one with an 8 ft. and one a 6 ft. wing span; an R.A.F. launch and a model six-wheeled Foden lorry. The aircraft and launch were made from kits, and the lorry, with the exception of the model tyres, was for the most part constructed from scrap metal and bits from the junk box.


Just a word of advice with regard to models; choose one that is capable of carrying the equipment, e.g., 5 to 8 ft. wing span for aircraft and 30 in. minimum length, with a 9 in. beam (min.) for boats. A model boat is probably the best type of vehicle for the experimenter to have, since aircraft have a nasty habit of either flying away or crashing when something goes wrong with the radio.

Other applications of radio control are many, but one or two examples are mentioned here which will no doubt appeal to the radio constructor. Radio control of other radio equipment, such as a distant receiver or transmitter, has in fact been carried out by the writer, who quite successfully controlled a 160 metre (fixed station) from a portable low power 10 metre transmitter which not only provided the control link, but carried the modulation for re-transmission over the main transmitter, through the medium of the remote control receiver. Another example of control of this nature was a system in which the carrier of an incoming signal, through the medium of the main receiver, switched on or off the main transmitter.

To enlarge on this a little, assume the writer to be in contact with another station on the same band but on a different frequency. The other station signs over, and directly his carrier goes off, the writer's transmitter comes on, the necessary switching being carried out by means of sensitive relays operated from the AVC circuits of the main receiver. All sorts of devices can be controlled by radio in the same way that control can be maintained over wires, for example teleprinters and facsimile transmission and even automatic Morse recording systems are, in effect, remote control by radio.

Radio Control Systems

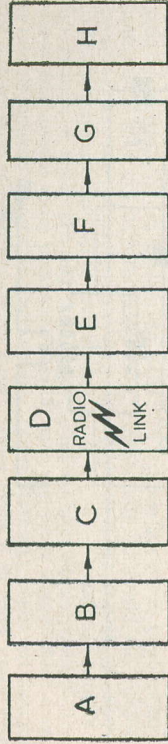Before describing such circuits as are used in more simple systems, some information on Frequency allocations, etc., will be given. The two Frequency Bands allocated by the Post Office are *licence free*. Permission does not have to be asked for the use of them, and providing a careful check is kept on frequencies, equipment may be used anywhere



741

Fig. 1. Block Diagram showing the various stages of a complete radio control system.

in the U.K. The power input to the transmitter must not exceed 5 watts. (PW in = E × I) where E is the anode voltage, and I the anode current to the valve or valves feeding the aerial.

The Frequencies allocated are as follows:—

27 Mc/s band—26.96 to 27.28 Mc/s.

456 Mc/s band—464.0 to 465.0 Mc/s.

They must under no circumstances be used for communication purposes.

It is possible for both the transmitters and receivers, when on 27 Mc/s, to cause interference; to television especially. In the event of interference being reported or a complaint being made, the apparatus should be switched off immediately. You have no priority. Don't spoil it for others by abusing the facility. You would be very unpopular if it were lost through your negligence or failure to keep within the allotted bands and/or misuse of the frequencies.

There is at least one commercially made frequency meter available for 27 mc/s, which is an absorption type meter specially made for the band.

Tone modulation may be used on the transmitter and provides the basis of one system in which resonant reeds are used to select a number of control channels. For example, say three different audio tones are used and made to modulate the transmitter, usually to 100 per cent. These are demodulated through the receiver detector, amplified and passed to a tuned reed unit. The reeds are each tuned to the modulated frequencies, and each will vibrate in sympathy only with its own tone. Vibration is of sufficient amplitude to cause the reed to move far enough to make with a fixed contact. The frequency of vibration, even over the audio range, is sufficiently fast enough to make the contact continuous as far as DC is concerned. The reeds will, of course, only handle low current, and they are used to operate relays with heavier contacts.

The second system, and the one most used, is that of carrier control which, although only providing a single channel, is by far the

most reliable. Here the receiver, usually a super-regenerative single valve detector with a relay on the anode circuit, is used with a simple self-excited transmitter (non-modulated). When a signal is present at the detector grid its anode current falls and allows the relay to open, it having been held closed by the steady anode current through the valve. Multi-channel operation can be achieved by a sequential selector system; this, in turn, switching power to the servo-mechanisms. The servos are, of course, mechanically coupled in the case of working models to the actual control, e.g., the rudder for steering. All the components in a radio control system, right from the controlling switch or selector at the transmitter to the final servo-mechanisms following the receiver and its selector, have not only correct names, but follow a definite order. Most readers of this magazine will no doubt be familiar with the names given to a complete transmitting and receiving system for communication in speech, where the system is made up of the following components: The microphone, an amplifier, modulator, transmitter, and aerial—the radio link—aerial, receiver, demodulator (detector), amplifier, and loudspeaker. This makes a complete system, and radio control has a similar one with correct names for all the components that go to make it up. The block diagram of Fig. 1 may help to make this clear. The system is as follows:

- A. The COMMAND source (The human operator).
- B. The CODER (Can be a simple switch controlling the transmitter).
- C. The TRANSMITTER.
- D. The RADIO LINK.
- E. The RECEIVER (Generally a single or two valve arrangement).
- F. The DECODER (A relay only, or a relay and selector, or reed unit).
- G. The SERVO-MECHANISM (Small motor-driven or electro-mechanical devices).

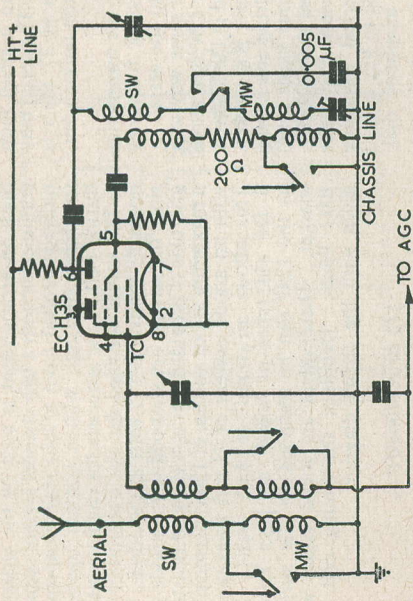


Fig. 1. The frequency-changer circuit before modification.

C708

The receiver, in this case, is of a well known make—by a firm that originally invaded us from America—and seems to promise results from the modifications I have in mind. I carefully check the frequency changer wiring, drawing the circuit on paper as I trace every wire and component, and find eventually that I am presented with circuit of Fig. 1. Now, apart from the fact that the designer has taken advantage of the very few turns of the short wave coil to wire both medium and short wave coils in series, there is nothing very remarkable about the circuit.

On short waves, the medium wave coils are shorted out of circuit (except the oscillator tuned windings) whilst on medium waves the short wave coil remains in circuit, since the inductance of these makes little difference. Wave changing is effected by a four pole, two way rotary switch, only one pole of which is used as a full changeover, that serving the oscillator tuned winding.

Coils

As the coils were small, air-cored types having paxolin formers, they were easily

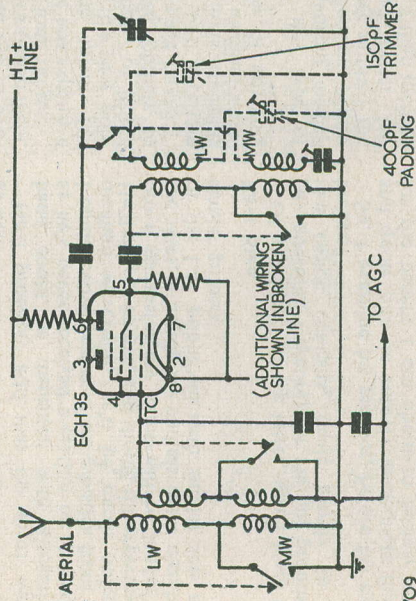


Fig. 2. The frequency-changer circuit modified for long wave working.

C709

replaceable by Wearite "P" types—although Osmor "Q," Denco and others could have been used, with perhaps even better results. It was just a question of availability and cost. The use of the smaller iron-dust cored types is, however, well worth considering in such a conversion even if only on account of the restricted space available in such receivers. They may cost a little more, but results probably justify it.

Accordingly, the two short wave coils were removed altogether, and long wave aerial and oscillator coils fitted in their places. The inductance of the new coils, however, does not permit them to be in series with the medium wave coils when tuning the latter waveband. Consequently, additional wiring to the first three poles of the switch is inserted as shown in Fig. 2.

The fourth pole, that serving the oscillator tuned winding, was completely re-wired (Fig. 2) and the 0.005 μF fixed short wave padding capacitor replaced by a 400 pF ceramic preset for long wave padding.

A twin preset was available having sections of 400 pF and 150 pF, and this was wired

into circuit, the 150 pF section being used as the new long wave trimmer.

The 200 Ω resistor separating the short and medium wave oscillator coupling coils was removed, its original function—the boosting of the valve oscillation on short waves—no longer being necessary.

Adjustments

No difficulty whatever was experienced in adjusting the paddler and trimmer, the paddler being first screwed in to bring in the Light Programme a little more than halfway round the dial (which, of course, was not marked for long waves). Then, both paddler and trimmer were alternately set to receive Luxembourg loudly, clearly, and as free as possible from objectionable "off-tune" mush.

—And "Trimmings"

An old razor blade was used to erase "SW" from the cardboard dial, and "LW" was neatly scribed in its place with a Biro pen. Finally, the Light Programme and Luxembourg positions were "Blackened-in" with a small square mark on the dial, and designated "Light" and "Lux'b'g" in readable capitals.

IT DARNED WELL DID, TOO!

by H. DUDLEY STILTON

A set came in the other day, "Twas quite a good one in its way. The fault was only something small, A fault which could occur in all. It cracked!

I stood it up upon the bench, And prised the knobs off with a wrench; I swept the chassis clear of fluff. Switched it on, and sure enough, It cracked!

I turned it o'er and cleaned the switch, Thought perhaps that there's the hitch. Although it looked too clean to blame, I tried anew but just the same, It cracked!

The iron was hot, the joints looked dry. I thought at least, I could but try I soldered here, I soldered there; I soldered damn near everywhere, — It cracked!!!!

I changed the valves; I tried the coil And smoothed the gang with drops of oil; I switched it on and probed about. One thing sure, I did find out— It cracked!!!!

I changed the coils and I.F.s, too, Tried some more of higher 'Q,' Stripped the auto grid to ground; Then the strangest thing I found— It cracked!!!!

I wracked my brains; I tore my hair; I beat the bench in mad despair, I screamed aloud and swore my fill; It cracked!!!!

I checked the wiring piece by piece, And found a part all splashed with grease, The joint had arced and dropped the fat, So little wonder, was it, that It cracked!!!!

I took it back and plugged it in, The owner turned and with a grin Handed o'er a handsome fee, I won't say what, but gosh oh gee— It cracked!!!!

TV. See Page 30

best frequency response, maximum versatility and ease of construction.

Much of the input switching, with its attendant feedback troubles, has been eliminated by utilising the switches on the jack sockets. Four of the latter are provided, as follows:—

A. High Impedance Input

A crystal or other high impedance microphone (or an external high impedance recording head) may be inserted here and used for recording (or normal playback with ext. head) or for normal sound amplification purposes.

B. Low Impedance Input

Functions exactly the same as 'A', except that inputs should be low impedance.

C. Radio or Gram Input

A radio or pick-up can be fed in, to be recorded or amplified direct, or mixed with inputs 'A' or 'B' to be recorded or amplified.

D. Extension Speaker Socket

An external speaker can be plugged in. This outlet is operative always, but to prevent acoustic feedback to microphone it is best not used whilst recording. For aural monitoring whilst recording, a pair of moving

coil phones of some 50 Ω impedance can be employed. The output during recording will sound a trifle shrill, due to treble boost in this position, but it is not objectionable.

Input Transformer


This was rewound from a miniature type with mumetal core, to give a ratio of about 45 : 1. The actual ratio is not particularly critical, and almost any ratio from 45 : 1 to 100 : 1 will do, if the transformer is of high quality.

As this component is mounted only a few inches from the mains transformer, rather elaborate screening is necessary. Altogether, three mu-metal cans were fitted (cut from CRT shields), with two intermediate copper cans. *The separate mu-metal shields should not touch each other*, hence the copper spacing cans which also act as shorted turns to any flux getting through the mu-metal. This may seem to make the transformer bulky, but the final overall size of the writer's unit was only 1½" diameter and 2" long. The screening is so effective that with OC primary no hum is audible at full gain. A 47 kΩ resistor across the secondary correctly loads the transformer for matching purposes.

Input Valve

A pentode with top cap grid is required for this stage, and either 6J7 or 6F37 will

A MAGNETIC TAPE RECORDER

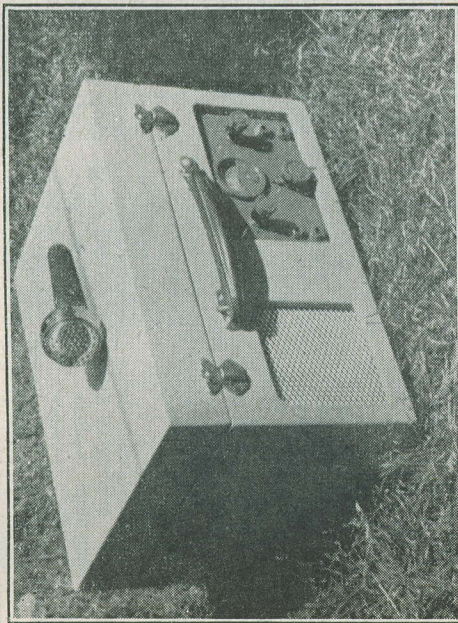

by L. F. SINFIELD, A.M.I.P.R.E.

Due to the lack of engineering facilities amongst radio constructors in general, it was decided to use a commercial deck as the basis of the unit described here. The 'Qualtape' unit was chosen on the grounds of economy.

Qualtape Unit Modifications*

Several mechanical modifications were made to the tape drive unit by the writer; these are optional improvements which may be incorporated as desired by individual constructors.

A. The switch was made to operate mechanically the motors, and to push them off the rubber drive wheels, with the object of preventing flats on the rubber, and eliminating adjustment of spool spring tension. In the 'forward' position, the Collaro motor is energised and lowered on to the capstan, the rewind motor is switched off and lifted away from the wheel. In the 'off' position, both motors are switched off and lifted away from wheels. In the 'rewind' position, the rewind motor is energised and lowered on to the wheel, while the Collaro motor is still switched off and away from the capstan. To prevent the rewind spool being completely free, and so that the correct tension is given to the tape whilst recording, a felt pad is pressed against the rewind drive wheel in the 'off' and 'forward' positions.

B. The rewind spool is locked to the spindle by tapping a 4BA hole in the top washer, so that a 4BA screw engages in one of the spool holes.

C. To increase rewind torque and speed, a metal sleeve was fitted over the rewind motor spindle to increase the diameter to about ⅜". (Torque is increased due to greater area of contact, as it was found that the spindle contact was slipping too much after some use).

D. As the rewind motor is used only for short periods, it was connected to the 220V tapping.

E. The complete recorder is so compact that air does not freely circulate around the Collaro motor. This tends to run hot, being a shaded pole type, so the metal below the motor was cut away to allow free passage of air over the coils, and a small fan was fitted on the motor shaft to increase air circulation.


F. A mumetal shield was made to enclose the head completely, with a ¼" slot to admit the tape. This also serves to keep the tape centrally located on the head.

G. A rubber sleeve was fitted over the bakelite pressure roller, to increase the grip. The edges of the rubber "give" to the thickness of the tape sufficiently that they touch the capstan.

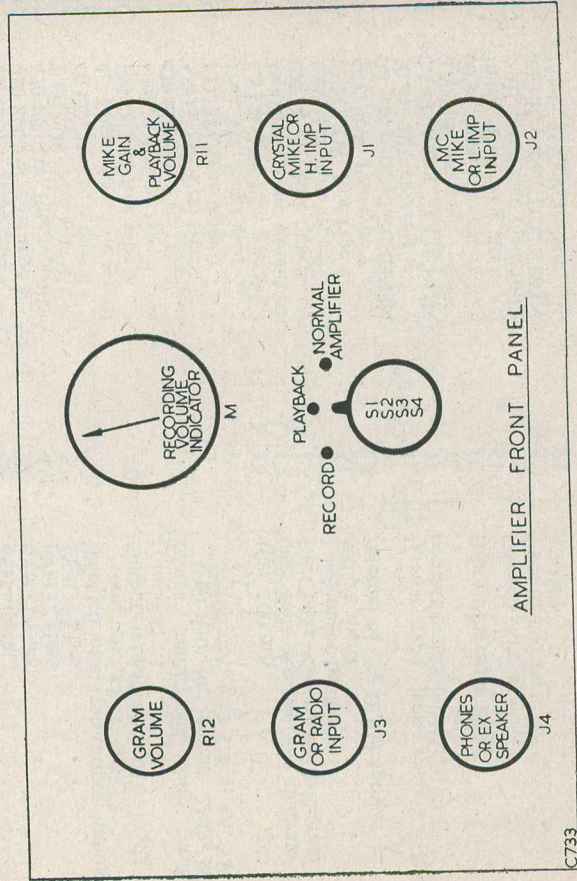H. Sponge rubber mounting pads were stuck under the Qualtape panel to absorb mechanical noise when mounted in the cabinet.

The Record/Playback Amplifier

This has been developed after some considerable experimental work to produce the



do. In the writer's model, a metal 6J7 was used, as this is physically smaller than the 6F37. The 15 kΩ stopper and 3.3 MegΩ leak are both mounted inside the screened top cap.

Frequency Compensation

To obtain maximum signal/noise ratio, it is desirable that the tape be magnetized by the head as strongly as possible throughout the range without, of course, going into magnetic saturation at any time. This means that constant current recording be used, but, as there are normally recording losses due to the "gap effect," etc., at high frequencies, some degree of treble boost is desirable. This recording characteristic is obtained by the network shown when in position 'R' (Record).


As the output from a magnetic circuit is dependent upon the rate of change of flux, if a constant flux density exists on the tape then the output, when played back, will fall as the frequency falls, like the fall when constant amplitude disc recordings are played with magnetic pick-ups. Thus, a loss of 6 dB per octave occurs towards the lower frequency end of the range.

To compensate for this, it is necessary to boost the low frequencies by this amount during playback. Also, as the same gap losses, transfer losses, etc., which occurred on recording will also exist on playback, treble boost will again be necessary.


On the playback position (P), both bass and treble boost is incorporated.

Parts List

- R1 47 kΩ, ½W, Erie type 9
- R2 3.3 MegΩ, ½W, Erie type 9
- R3 15 kΩ, ½W, Erie type 9
- R4 470 kΩ, ½W, Erie type 9
- R5 100 kΩ, ½W, Erie type 8
- R6 1 kΩ, ½W, Erie type 9
- R7 20 kΩ, ½W, Erie type 9
- R8 100 kΩ, ½W, Erie type 9
- R9 15 kΩ, ½W, Erie type 9
- R10 100 kΩ, ½W, Erie type 9
- R11 1 MegΩ volume control, carbon
- R12 220 kΩ, ½W, Erie type 9
- R13 15 kΩ, ½W, Erie type 9
- R14 220 kΩ, ½W, Erie type 8
- R15 470 kΩ, ½W, Erie type 9
- R16 1 kΩ, ½W, Erie type 9
- R17 10 kΩ, ½W, Erie type 9
- R18 10 kΩ, 1W, Erie type 8
- R19 4.7 MegΩ, ½W, Erie type 9
- R20 100 Ω, ½W, Erie type 9
- R21 1 kΩ, ½W, Erie type 9
- R22 470 kΩ, ½W, Erie type 9
- R23 300 Ω, 1W, Erie type 8
- R24 3 Ω, 3W, wire wound
- R25 47 Ω, 2W, Erie type 1
- R26 1.5 kΩ, ½W, Erie type 9
- R27 25 kΩ, 4W, wire wound pot.
- R28 100 Ω, ½W, Erie type 9
- R29 1 kΩ, ½W, Erie type 9
- R30 27 kΩ, ½W, Erie type 9
- R31 50 Ω, ½W, Erie type 9
- C1 0.1 μF, paper, TCC CP45N
- C2 50 μF, 12V electrolytic
- C3 0.1 μF, paper, TCC CP45N
- C4 0.005 μF, mica
- C5 60 pF max. trimmer
- C6 16 μF, 450V wkg. elect.
- C7 8 μF, metal can, plain foil
- C8 0.1 μF, paper, TCC CP45N
- C9 25 μF, 25V electrolytic
- R1 0.01 μF, paper, TCC CP45W
- C10 0.002 μF, mica
- C11 25 μF, 25V electrolytic
- C12 0.03 μF—See text
- C13 0.1 μF, paper, TCC CP45N
- C14 ? (0.002-0.005 μF—Osc. to be 45 kc/s)
- C15 0.002 μF, mica
- C16 0.25 μF, paper, TCC CP48N
- C17 16 μF 450V wkg. elect.
- C18 8 μF, metal can, plain foil
- C19 6J7 metal
- V1 6SH7 metal
- V2 6V6GT glass
- V3 6V6GT glass
- V4 5Y3GT glass
- V5 Shielded input transformer, mu-metal core, ratio 45 : 1—100 : 1
- T1 Output transformer, 6V6 to 2½ Ω, ratio 45 : 1
- T2 Mains transformer, drop through type with top shroud. 250/0/250V at 100 mA. 6.3V CT at 4A. 5V at 3A
- T3 10H, 100 mA
- L1 Osc. coil—See text and diagram
- L2 RF Choke—See text and diagram
- L3 1 mA meter rectifier
- MR1 500 μA meter
- M Internal 6½" 2½ Ω PM speaker
- LS Igranitic type jack sockets. (Rear contact breaks on entry)
- J1 Record/Playback Head
- J2 Ganged switches
- J3 4 pole 3 way on
- J4 3 wafers
- H S1 S2 S3 S4

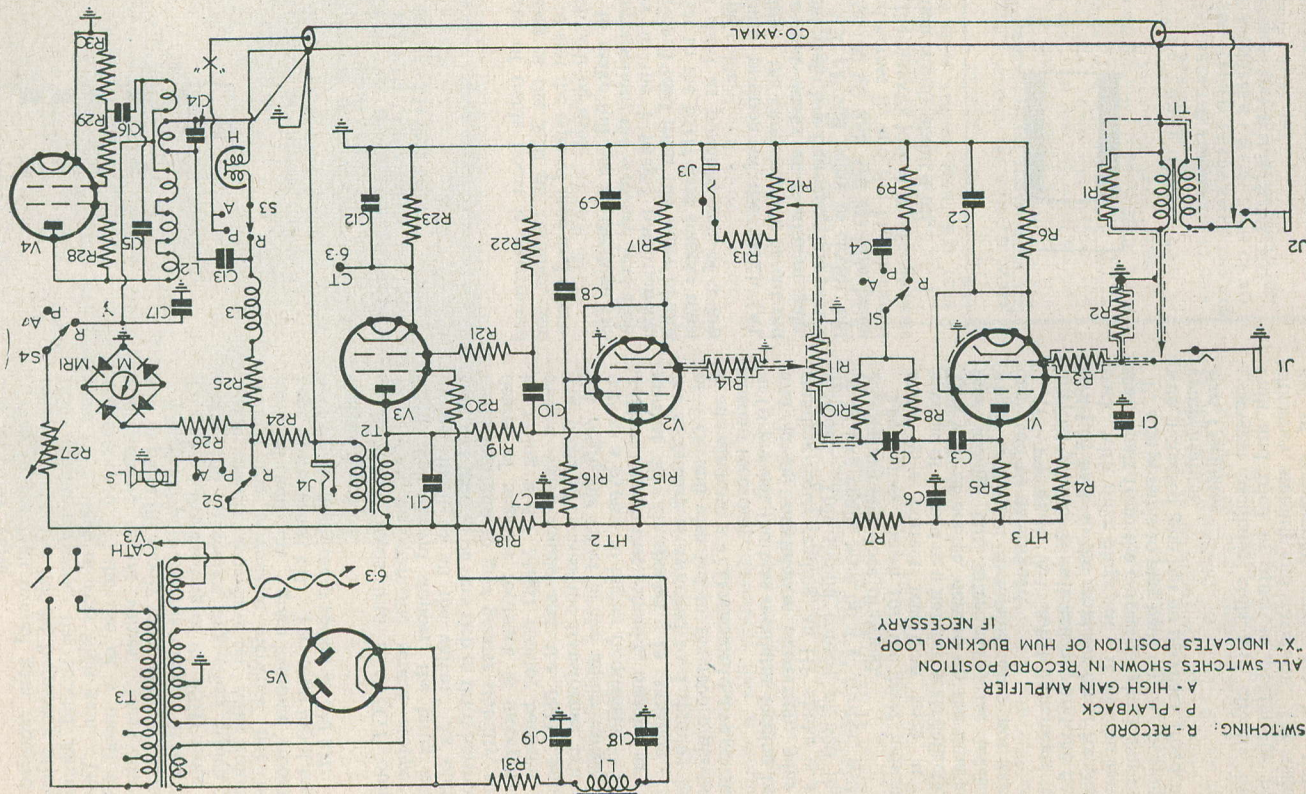

Complete Circuit of the Amplifier

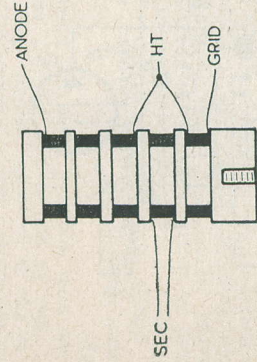

HF OSC COIL (L2)
HALF SIZE SECTION, EBONITE FORMER
TAPPED 4BA HOLE IN BASE $\frac{1}{8}$ DEEP

WINDINGS IN FIVE SLOTS ALL IN SAME DIRECTION. PRIMARY 4X200 TURNS (800 TOTAL) OF 32 SWG ENAMELLED. SECONDARY IN SLOT BETWEEN GRID & ANODE SECTIONS C739 80 TURNS 24 SWG ENAM.

The degree of treble boost is determined by the setting of the 3-30 pF trimmer, and is adjusted to suit the type of tape and microphone which will be used.

In order to make full use of the high frequency compensation, the screened lead from the trimmer to the 1 Meg Ω potentiometer and the screened lead from the slider of this potentiometer to the 6SH7 grid stopper must both be as short as possible, and of a low capacity type cable.

In the third position of the switch (A), as an amplifier, the compensation is cut out so that the unit works at maximum gain. It is true that slight low frequency loss occurs due to the 3-30 pF still being in circuit, but owing to the 100 k Ω and 470 k Ω now being in series and across it, and the higher circuit impedance, the network loss at low frequencies in this position is only about 4 dB.



RF CHOKE (L3)
EBONITE FORMER

20 SWG TINNED LEADS FIXED THROUGH ENDS, WINDING 8 LAYERS EACH OF 40 TURNS. 32 ENAMELLED, TOTAL 320 TURNS.

2nd Amplifier Valve

Due to the high overall gain required on playback, and the middle frequency attenuation of the network, the second amplifier must be a stage of very high gain. This is accomplished by the use of a metal 6SH7 and suitable circuit values. This valve is still in plentiful supply from ex-Govt. dealers.

The gram/radio input is mixed in at the grid. To prevent overloading of the 6SH7 from the input, and to reduce any effect which the 'gram volume' may have on 'mike volume', the attenuator network has been included and the 'gram volume' control kept down to 50 k Ω . The total input resistance at the gram/radio socket is 270 k Ω .

Output Stage

The 6SH7 feeds into a 6V6GT output valve. An anti-parasitic screen stopper is fitted, also a grid stopper, the latter being in fact fitted to all the valves. As output pentodes tend to be very rich in third harmonic distortion, and to give greater stability, some degree of negative feedback is incorporated by fitting a 4.7 Meg Ω resistor between the output valve anode and the 6SH7 anode. The 0.002 μ F across the transformer primary has negligible effect in the audio range, but acts as a bypass to higher frequencies.

The transformer should match to the normal 2 $\frac{1}{2}$ Ω speaker. In position 'R', the secondary is switched to a dummy load of 3 Ω , and also fed to the record/playback head switch via a 47 Ω resistor to give constant current recording.


To prevent the bias oscillator feeding back and giving modulation distortion, plus a standing meter reading, an HF choke is also included. This should consist of 320 turns of 32 swg enam. wire on a $\frac{1}{4}$ " former, with a $\frac{1}{2}$ " long winding (See drawing).

The values shown for the level indicator meter give correct recording level at an average of a third to a half full scale deflection. This will, of course, depend on the tape and bias settings but, after trials, the level at which saturation distortion does not occur can soon be determined.

At 'P', and 'A', switch positions the internal speaker is switched on, and the head switched back to the amplifier input for playback, with mike plugs out. It will be noted that, apart from the correct playback position 'P', it is possible to play back on 'A' position, with increased gain but no playback frequency compensation.

Bias Oscillator

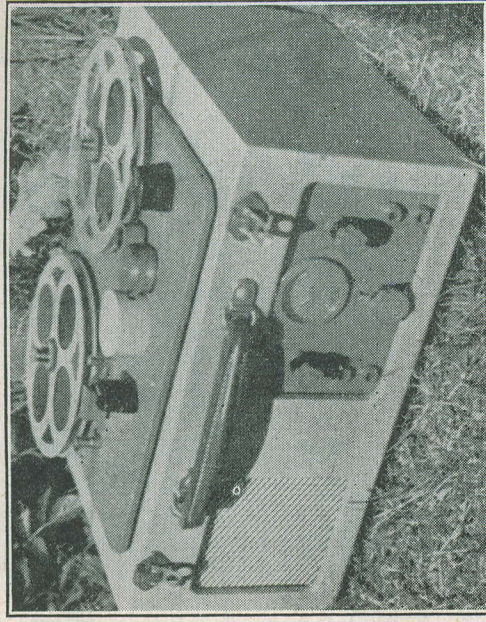Several oscillator coils and circuits were built and tried in order to obtain the best efficiency, stability and waveform. The majority of commercial coils are too tightly



Three-quarter view of complete recorder, with lid removed.

coupled to give a good sinusoidal wave form (See coil data).

The circuit shown should work at about 45 kcs, and it may be necessary to alter the tuning capacity (C15) to obtain this desired frequency. The 0.1 μ F across the secondary coil can be eliminated, if desired, as the output is still sinusoidal, but its inclusion boosts the oscillator output quite a bit, and it does make doubly sure of good waveform.

For high coercivity tape the grid leak can be around 27 k Ω , and for low coercivity tape around 47 k Ω to give similar results at similar bias control settings, but 27 k Ω can be used for both and the bias control adjusted to suit either tape.

Instead of the usual bias output control, the bias level is adjusted by varying the HT, as this also economises on HT current. The stability and waveform remain perfect at all settings. The head itself is series tuned by a 0.03 μ F condenser, although if a head of different inductance is used this value should be changed.

Grid and screen stoppers are incorporated to prevent any possibility of parasitics.

The HT to the oscillator is switched off in the 'P' and 'A' positions to reduce HT current consumption, and to prevent any possible interference when using the high gain required for playback.

To be continued

THE RADIO AMATEUR—AUGUST

TV Linkage of England and Scotland. Efficiency in the Transmission Line. The S-9'er. Constructional feature. The Design of Mains Transformers. Workshop practice. The QSL Problem. together with the usual Amateur Band, S.W. Programme and Broadcast Commentaries, VHF and Club News, etc., etc.

G4GZ'S BARGAINS

VALVES: 6AC7M, 6C4, 6C5GT, 6J5GT, 6N7GT, 9002, 9003, VS110A, 15D2, 6J6, 954, 955, 956, VU111, 2X2, 5J-, 12A6M, 6F8G, 6K7GT, 6J5M, 6J7G, 6AG5, 6X5GT, S130, AC6Pen, 7J6, 65G7M, 6L7M, 6N7M, 6I7M, 8J6, 6SA7M, 6F6G, 6V6G, 8012, 1T4, 155, 154, 9J6, 5Z4M, 6SQ7M, 6F7, 1R5, 10J6, 6AQ5, 6F6M, 11J6, KT66, 65N7GT, 6V6M, 65C7M, 6K8G, 12J6.

NEW GOODS IN STOCK!! include all View-master components, Haynes and Allen TV components; THE NEW Lane 3 motor, Tape Tables £16.10.0 (car. 7/6) 1200' reels Scotch Boy MCI-111, 35'-. Spare reels 4/6. Lane osc. coils 10'-. BSR 4 pole shaded pole motors 38/- each (clock or anti-clock). Collaro, Garard and BSR Auto changers and single players. Acco, Pickups, Goodmans Speakers etc. US HUGE range of valves and components. LET US HAVE YOUR ENQUIRIES.

All goods despatched by return of post. Please add post/packing AND ORDER FROM THE EAST COAST'S LEADING COMPONENT SUPPLIERS.

J. T. ANGLIN,
160, CLEETHORPE ROAD, GRIMSBY, Lincs.
Tel. 56315.

IN YOUR WORKSHOP

In which J. R. D. discusses Problems and Points of Interest connected with the Workshop side of our Hobby, based on Letters from Readers and his own experiences.

How many of the old hands are there who regret, just a little, the passing of the early days of radio? It is in human character to review memories of the past under a favourable light; we tend to remember the good things only, and forget the bad. Nevertheless, those early days had a charm which cannot perhaps be entirely recaptured at the present time. The first amateur constructors were fired with a pioneering spirit because they were experimenting with something new; they realised that, since there were so many potential discoveries to be made in the new science, such discoveries were just as likely to be found with an experimental kitchen-table rig as they were in a manufacturer's laboratory. Nowadays, when radio design has become stabilised, the field for experiment

by the amateur is correspondingly more limited.

However, the amateur, like the Elephant's Child, has a 'satiable curiosity'. If he loses a source of experiment in one direction, he finds another elsewhere. Nowadays much experimental work is being carried out in the search for really adequate high fidelity reproduction. This is an interesting branch of radio, and has the added advantage of not necessarily requiring the expenditure of an excessive amount of money. It is true that the prices of some high fidelity loudspeakers soar to almost astronomical heights, but it is also true that quite a few of the well-known units offered for sale are within the pockets of many amateur constructors. Recording-playing gear can also be fairly expensive, particularly so when new equipment is being bought, as the buyer then has to pay the crippling Purchase Tax which is levied on such items.

Despite all this, high-fidelity reproduction still offers an attractive interest for the experimenter. The amplifier itself can be made at home using the constructor's own ideas, and being built to his own design and layout. Most of the components needed—resistors, capacitors, and so on—are cheap and easy to obtain; and even the valves need not necessarily incur too great an expense. Many amateurs, desiring a good and cheap amplifier, design one which, without any loss in performance, can still make use of components which they have already on hand.

Readers will have noticed that this growing attention to sound reproduction has been reflected in the space devoted to the subject in this magazine. The writer is, himself, keenly interested in high fidelity work and is always very pleased to hear from readers who are getting good results from interesting or unusual amplifiers of their own design.

Electronic Guitars

Several musically—but not very technically-minded—friends of the writer approached him recently for some information on the


conversion of ordinary guitars to electrical working. Since nowadays, for certain reasons, such conversions are much easier than they used to be, it might be of interest to pass along the information here as well.

The simplest method of making an electric guitar consists of taking an ordinary guitar and mounting small bobbins wound on continually magnetised cores close to the individual strings. The vibration of these strings (which must be of steel, of course) is then changed to corresponding electrical currents by the magnetic variations induced in the bobbins. Two views of the scheme are shown in Fig. 1. Some people prefer to have the bobbin cores mounted progressively closer to the strings at the "bass end" to ensure that each string induces a similar voltage value, but this point is not necessarily of great importance.

To house the bobbins in the guitar it is necessary to cut an oblong slot in the face of the instrument close to the bridge (See Fig. 1). The tonal qualities of the guitar are of little importance once it has been converted, and so it is wise to alter only a very cheap instrument. An expensive guitar would, of course, be practically ruined after the slot had been cut. A friend of the writer who has built several electric guitars usually makes the whole guitar framework himself, using any suitable wood.

Electric guitar technique is a little more complex than is that needed for a normal instrument. A fairly sensitive amplifier and a volume control on the instrument itself are essential. A typical instance of what may be obtained is given by the fact that notes can be "held" for what is almost an amazingly long space of time. If a string is plucked with the volume turned down, the volume may be gradually advanced whilst the vibrations die away, giving the effect of a continuous tone at a constant audible level.

The reasons for stating that guitar conversions are nowadays very easy is due to the fact that most of the ex-RAF headphones now being sold as surplus contain bobbins which are ideal for the job. Previously, to ensure that the bobbin cores were magnetically polarised it was normal practice to use a single horse-shoe magnet to energise them all, with the result that construction was difficult and awkward. The bobbins used in the ex-RAF headphones have the construction shown in Fig. 2, the bottom member joining the two cores being also a magnet. This design allows the bobbins to be mounted side by side in pairs quite simply; and there

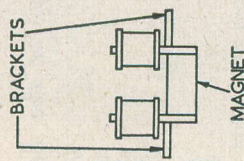


C730

Fig. 2: The design of the core assembly used in the headphones mentioned in the text, illustrating how the energising magnet forms part of the construction

is no need to worry about magnetising the cores as this is done automatically by their construction. Before mounting the pairs of bobbins side by side it will probably be necessary to cut off the small brackets shown in Fig. 2. The spacing between cores should approximate to the spacing between strings in most cases, but, if this does not occur, the bridge can usually be modified. Alternatively the bobbins can be "staggered" in pairs, or spaced out, as the case may be, to ensure that the cores fall more or less underneath the strings.

High-resistance ex-RAF headphone bobbins give excellent results when used in this manner. The bobbins should be connected in series; and the output, after passing through the volume control circuit, can be applied directly between grid and chassis of the amplifier. The writer has had no experience of low-resistance bobbins of the same construction but, if these were used in conjunction with a transformer, they would probably work just as well. If the pairs of bobbins were, in this case, connected in parallel they should match reasonably well into a microphone transformer. The transformer would need to be mounted in the guitar itself so that the volume control could be used in its secondary circuit.

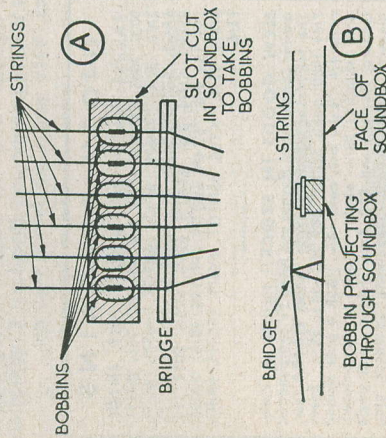The writer would like to state finally that it is, of course, impossible to guarantee that all ex-RAF headphones have the bobbin construction shown in Fig. 2. Nearly all those offered for sale use this design, but the constructor should try to make certain of this point before finally making his purchase.



C729

Fig. 1: Top view (a), and side view (b), showing how bobbins and cores may be fitted to an ordinary guitar to convert it to electrical working. The method used to polarise the cores is not shown here. The bobbins are fitted on the fingerboard side of the bridge

Mainly for the Beginner . . .

RESISTANCE

By H. E. SMITH, G6UH

Resistance

Of the three components which are the main ingredients of all Ohms Law calculations, Voltage (E), Current (I), and Resistance (R), the latter usually presents more of a problem to the beginner and is fundamentally more difficult to grasp. A few basic facts, once assimilated, will make for easier calculation and a better understanding of the actual necessity for the use of resistors in all radio and associated apparatus.

Resistance of Materials

The resistance of any material is directly related to its "opposition" to a steady flow of electrons. In other words, if the composition of the material is such that it is easy to detach electrons from its atomic structure, its opposition to electron flow will be low and it can be said to have a *low resistance*. The actual amount of opposition present will also depend on the temperature of the material. With most *metals* the resistance increases with an increase in temperature. With other substances, including carbon, the resistance *decreases* with an increase in temperature.

Many of the small resistors used in radio and amplifier work today are of the carbon or carbon composition type, and it will be appreciated that any undue heating up during operation is undesirable because of the effect of heat on the resistance value. Special types of resistor have been developed in recent years. These are known as High Stability types and are, in the main, unaffected by changes in temperature. Another type of resistor is the Wire Wound variety. These will usually handle heavier currents and withstand higher temperatures for a smaller change in resistance value than the carbon and composition types. Wire wound resistors should not be used indiscriminately in the construction of radio receivers, however, because unless marked otherwise most wire wound resistors are *inductive*. Many cases have been known of such resistors causing instability and self oscillation, due to their being resonant at some particular frequency. If wire wound resistors must be used, especially

in a part of the circuit where self-resonance might be expected (RF or Detector circuits) always specify *Non-inductive* types. If you are contemplating winding your own resistors, use a good make of double silk and enamelled Nichrome or Eureka wire and wind it to the method shown in Fig. 1(b). A point to remember regarding resistance wire is that if one yard equals one ohm, 1' 6" will be half an ohm and two yards will be two ohms. If you have a supply of resistance wire it is a good plan to cut off about a yard and get it measured up on a reliable bridge. You will then be in a position to wind up any value of resistor, as far as your stock will allow, to within less than 1 per cent. merely by using a rule.

In cases where extreme accuracy and stability is required, such as a meter shunt for a milliammeter, a wire wound type of resistor is a necessity. Many of the surplus 5 mA meters on the market are quite readily adapted to 50 mA by shunting directly across the terminals. The resistance value of the shunt should be one ninth that of the meter itself. The meter resistance is usually indicated on the lower part of the scale.

Voltage dividers

One of the most useful purposes for which resistors are used in present day design is as voltage dividers. The HT battery has a series of sockets providing a limited choice of voltage. With an AC power supply we can fit a voltage divider and obtain any value of HT voltage from zero to the full amount given by the unit. A simple method is to fit a string of resistors across the output and take a tapping from the junction of each, or we can use a potentiometer of the variable type in series with the whole or a section of the fixed portion. Remember that the *Wattage* rating of the resistors should be of such an order that they will withstand the current flow *through* them plus the current flow to the circuit being supplied from the tapping. Fig. 2 should make this quite clear. The total current drain through R1, R2 and R3 is approximately 10 mA. R1 must, therefore, stand 10 mA plus 20 mA for

the 250 volt tap, plus 5 mA for the 100 volt tap. R2 has to stand 10 mA plus 5 mA for the 100 volt tap, and R3 the 10 mA of the divider network.

Suitable wattage ratings for the resistors would be:— R1—10 watt, R2—2 watt, and R3—1 watt. If no resistors of such wattage are available, it is quite a simple matter to wire two resistors of lower wattage in parallel. The value of each would of course be twice the value of the required resistance. Where two odd value resistors are used in parallel, the following simple equation is used:—

$$R = \frac{R1 \times R2}{R1 + R2}$$

If the required resistor value is known, it is a simple matter to calculate what value is required in parallel with the existing resistor to produce the desired value:—

$$Rr = \frac{R1 \times R}{R1 - R}$$

Where R is total value required,

R1 is existing resistor value,

Rr is the value of the resistor required to produce R when paralleled with R1.

For *more than two* resistors in parallel the resultant value is equal to the reciprocal of the sum of the various reciprocals of the resistors used, or:—

$$R = \frac{1}{\frac{1}{R1} + \frac{1}{R2} + \frac{1}{R3} + \frac{1}{R4} \text{ etc.}}$$

A helpful point to remember is that where several resistors are used in parallel, the resultant resistance is always lower than the lowest value resistor used.

For resistors in series it is, of course, merely a matter of adding the various values together to obtain the total resistance.

The Anode resistor

No valve will operate effectively unless its anode circuit is "loaded" with the appropriate impedance or resistance as specified by the makers. This loading is necessary because the following valve requires an alternating voltage applied to its grid before it will operate, and it is across the anode load resistor that this voltage is generated. The data supplied with the valve should be carefully followed. Any major departure from the operating conditions as set down by the manufacturer will result in disappointment. If too high a value of anode resistor

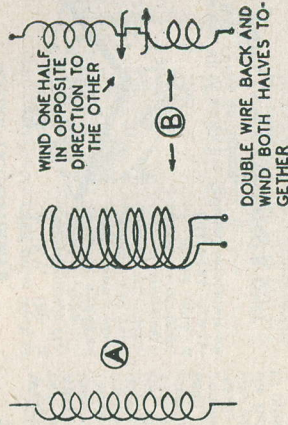


FIG. 1. WIRE WOUND RESISTORS

A—ORDINARY INDUCTIVE TYPE.

B—TWO METHODS OF WINDING NON-INDUCTIVE TYPES. C750

is used, distortion will result, due to excessive voltage drop across the resistor. If too low a value, there will be loss of gain, as the resistor is too low in value for the proper development of the alternating voltage to drive the following stage. In some special amplifiers, the gain is often deliberately cut by this method in order to keep the distortion percentage down to the absolute minimum.

Cathode Resistors

The cathode bias resistor should always be of sufficiently high wattage rating to comfortably withstand the combined anode and screen current of the valve. If the anode and screen current and grid bias voltage requirements of a valve are known, the value of the cathode resistor may be calculated from the following:—


$$R = \frac{Vg}{Ia/s}$$

Where Vg is the grid bias voltage required, Ia/s is the combined anode and screen current of the valve.

The resistor method of biasing a valve is far more satisfactory than the battery method because the bias voltage varies with changes in HT voltage, thus tending to maintain the anode current at one level. Cheap resistors of unknown make are to be avoided, as not only are they probably nowhere near the indicated value but are often noisy in operation and responsible for intermittent operation and crackles.


ELPREQ PAGES

RADAR TRANSFORMER

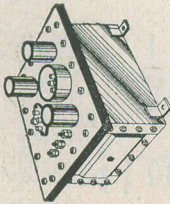

For pulse work at 4 KV, this is a Minity style No. 2, 224261 type fitted with two valve holders and ceramic pillars. Internally it contains a pulse transformer, a choke and a filament transformer, all of which are designed to operate on 4 KV. Price on request.


INDUCTANCE CONDENSER UNIT

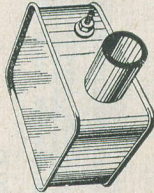

TYPE 21

Intended to operate with the above pulse transformer. Ministry No. 10C/11335. This again is made for 4 KV work.

HIGH VOLTAGE ISOLATION TRANSFORMER

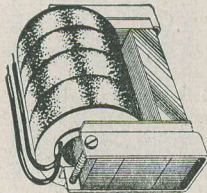

Ratio 1 to 1 made for voltages up to 4 KV but probably would be safe on even higher voltage.

THERMOSTATS




All thermostats are fitted with heavy silver contacts and can be adjusted to operate between 30° and 300°F. Suitable for use with aquariums, electric blankets, space heaters, greenhouse heaters, etc.

A.C. rating 1 Amp 250v. 3/6d.
2 Amp 250v. 5/6d.
A.C. " 5 Amp 250v. 14/6d.

Note. The two amp model is fitted with patent devices which gives it a quick make and break action.

METAL RECTIFIER

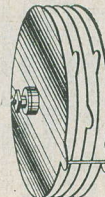

The one illustrated is a special bargain being available at considerably below cost. It is a selenium type rectifier rated at 12v. 24 Amp, it is of course a full wave type highly suitable for battery chargers. Limited quantity. Also available:

6 v. 1 Amp Type Price 5/-d. each
12v. 1 Amp Type Price 9/-d. each

TELEVISION CAN BE YOURS FOR ONLY £7

We offer Hire Purchase terms on two alternative sets—P.T. ARGUS. This was described in three recent issues of *Practical Television* and we have had good reports about the quality of reception. This Telesvisor uses the Government surplus tube Type VCR97 which is now firmly established in the domestic T.V. field. The total price of all components and tube is approximately £20 (list on request) or if you prefer send only £7 deposit the balance can be spread over 12 months.

VIEWMASTER. This set we need not describe, the name being almost a household word, the total cost depends largely on the type of tube used and as from time to time we have perfect tubes to offer at half current price due to the fact that they have had slight use, we suggest that you leave purchase of the tube until last. The total cost of the Viewmaster is approximately £35 plus the tube, but you only need send £12 deposit, the balance can be spread over 12 months.


If you would rather study the data then send 2/6d. for P.T. Argus or 7/6d. for Viewmaster, we are quite willing to refund your cash if you return the data within 7 days.

T.V. CABINET

This is a very handsome walnut finished cabinet ideal for Viewmaster or practically any other T.V. using up to a 12" tube. A platform is fitted but it is a small matter to alter the position to suit your own chassis. Baffle board for 10" loudspeaker is also included as is a hardwood back. Internal dimensions: 27" high x 18" deep. Price £9 9.0d. carriage and packing 10/- extra.

THE SUPERIOR FIVE


A.C. mains superhet built by one of our famous manufacturers—Covers long-wave 800-2200 metres, Medium-wave 200-500 metres and short wave 16-50 metres, made on heavy gauge chassis, size 15 1/2 x 8 x 2 1/2" edge-lit dial, printed and calibrated in three colours, size 7 1/2 square, 8" P.M. speaker—two speed tuning B.V.A. valves types 6K8, 6V7, 6R7, 6V6, and 6X5. Pick-up and speaker sockets delayed A.V.C. I.F. Filter—4 watts undistorted output—circuit diagram and 12 months' written guarantee. Price complete ready to work, £10 19/6d. Hire, Purchase Terms, £3.13.0d. deposit, then nine monthly payments of 18/9d. Non-callers please add 10/6d. to cover carriage and insurance.

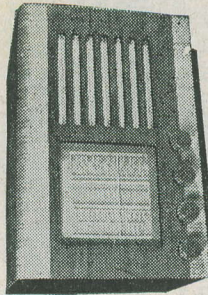

SUPERIOR CABINET

With beautifully veneered full grained and highly polished finish, dimensions 19" wide x 10" deep x 12 1/2" high. This cabinet will take our "Superior Five" also the set being advertised by Messrs. Lasky's Radio. In this cabinet the set will look well worth £18-£20. Price 5 gns. each, post, packing and insurance 7/- extra.

ELPREQ TAPE RECORDER

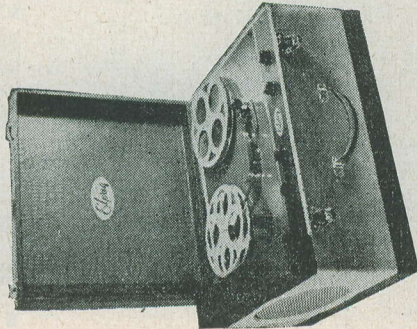

£29 5s. CASH

or

£9 15s. DEPOSIT

Tape Deck. Fitted with 3 motors giving fast rewind/forward run and no friction. High fidelity record/play back giving approximately 1 hour playing from standard 1,200 ft. tape. Tape 35/-d. per reel.

Amplifier. High gain enables recording to be made from microphone, pick-up or loud speaker. Separate bass and treble lift controls.

Cabinet. Portable is rexine covered. Table model is polished walnut.

Constructor Envelope. Shows in close detail exactly how to assemble and operate the recorder, is free with kit or available separately at 5/-d. In which case it is supplied on the understanding that if after having 14 days to study it, you decide against making the recorder send data back clean and we will refund your cash less postage.

Price. Complete kit of parts including 6 B.V.A. valves, loudspeaker and cabinet (state whether portable or table model required), £29.5.0d. or £9.15.0d. deposit and balance over 12 months. If required we will assemble and test for £4 extra. Suitable crystal hand-table microphone £1.15.0d. extra.


RADIO STETHOSCOPE

A novel device aptly called a Radio Stethoscope is described in a recent edition of the *Radio Constructor*, this is compact and can be slipped into the pocket rather like a fountain pen. With it in most districts a receiver can be checked from the grid of the first valve right through to the output without a signal generator, in both L.F. and R.F. circuits without alteration. It is complete fault finder.

The only parts needed to make the simple circuit tracer are a pair of crocodile clips, a germanium crystal, and a paper tubular condenser and we will supply whole outfit for 6/6d., post free, and with each outfit we will give re-print of the article as it appeared in the *Radio Constructor*. NOTE.—If you wish to make it up as a pocket unit then you will need a few other odds and ends, solder tags, etc., from your spares box.

BLANK CHASSIS

Made of 18 S.W.G. Aluminium.

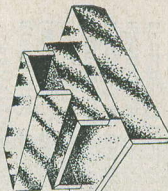

Size	Price
10" x 8" x 2 1/4"	7/-
10" x 8 1/2" x 2 1/4"	6/6
12" x 9" x 3 1/4"	7/3
12" x 9 1/2" x 3 1/4"	7/6
14" x 10" x 3 3/4"	8/-
16" x 10" x 3 3/4"	8/3
16" x 8" x 10" x 3 3/4"	8/-
16" x 12" x 3 3/4"	7/6
19" x 8" x 2 1/4"	8/3
20" x 10" x 3 3/4"	10/-
21" x 9 1/2" x 2 1/4"	10/6

SPEMET

Made from polished aluminium, an excellent material for fronts of cabinets or for special cabinets you are making, and for air conditioners, etc.

Close mesh 8 holes to the inch, 24" x 12", 10/-, 12" x 12", 5/3, 6" x 6", 1/9.
Wide mesh 4 holes to the inch, 24" x 12", 9/-, 12" x 12", 4/9, 6" x 6", 1/6.
Postage and special packing 1/6 extra for any quantity up to 12 sheets. Over 12 sheets post free.

Orders by post are dealt with by our RUISLIP depot. To avoid delay address to: E.P.E. Ltd., Dept. 3, Windmill Hill, Ruislip, Midxs.

Except for heavy and delicate items where carriage charge is specified, orders over £2 are post free, under £2 add reasonable amount bearing in mind a 15lb. parcel costs 2/6. Postable items can be sent C.O.D. additional charge approx. 2/6. List 6d.

Early closing, Wednesday—Ruislip, Saturday—City.

PRECISION EQUIPMENT

WINDMILL HILL, RUISLIP MANOR
MIDDLESEX AND AT
152-153 FLEET STREET, LONDON E.C.4.

LARGE SCREEN TV.

THE RADIO CONSTRUCTOR'S 16 inch TELEVISOR

PART SEVEN

No difficulty should be encountered in building the five-channel vision and sound strip. Cross reference to the photographs and lay-out guide will clearly give all the direction that is required.

Valveholder holes and fixing points are given and by studying the valve connections (see last issue), valveholders may be bolted into position to form a logical sequence as seen in the circuit. Thus, anode pin adjacent to grid 1 of the next valve, and so on. Readers should take careful note of the chassis drilling sketch. This is shown as the underside; perhaps a slightly unusual procedure, but it obviously maintains visual relationship to the photographs. R11, shown in the time-base picture (July issue), can be seen again here, and by placing these two issues side by side a composite layout can be achieved. Note that L7 and L8 are on top of the chassis, unscreened.

The aerial connecting coaxial cable under the chassis is not shown to avoid overcrowding the layout photographs, but this is simply taken round the inside of chassis to L1 at the rear.

Insulation of the aerial socket from the chassis is essential, and the end view shows a piece of paxolin mounted to carry the aerial input.

The McMurdo valveholders used in this receiver lend themselves to a fortunate component assembly.

Wire in the heater and heater/chassis connections first. It is advisable not to use too many valves in chain wiring. Narrow gauge wire is apt to drop volts, and this can cause foldover at the left of the picture.

Bring up a chassis connection to the centre spigot of each valveholder; all small condensers and resistors to chassis may then be nicely grouped to one point. Components to HT can be taken across to the tag strips

provided. The photograph will present this method of construction very graphically.

All coils will be suitably marked, and here again a thorough study of the circuit should be made to ascertain that wires from all components may take the shortest possible course. Note the clean uncluttered appearance of this chassis, and dispose all items in this fashion.


When mounting the focus coil, remove rubber grommet, which is supplied for fitting to 9" or 12" tubes, and ascertain that this gap, which is incidentally the magnetic gap, is adjacent to the deflection coils.

Some consideration must be given to setting up the tube, and reference must again be made to the May issue. Study the notes on the iron trap and focus coil. There will usually be some amount of wriggling with these components and if no raster is observed when switching on, the raster can be sure these two components are completely out of position, thus failing to bring the beam into true axis line. The line-output transformer is such that if the customary fly-back whistle is heard, and the EHT rectifier filament is heated up, one can be practically certain that the EHT is present on the tube. So don't test with your fingers!!

For this purpose there can be no better tool available than the "Kilovolt", a recent acquisition by your writer which has proved absolutely invaluable in setting up this receiver.

With a range of up to 30 kV, a complete reading of EHT voltages is available at all times during the setting-up period of this receiver.

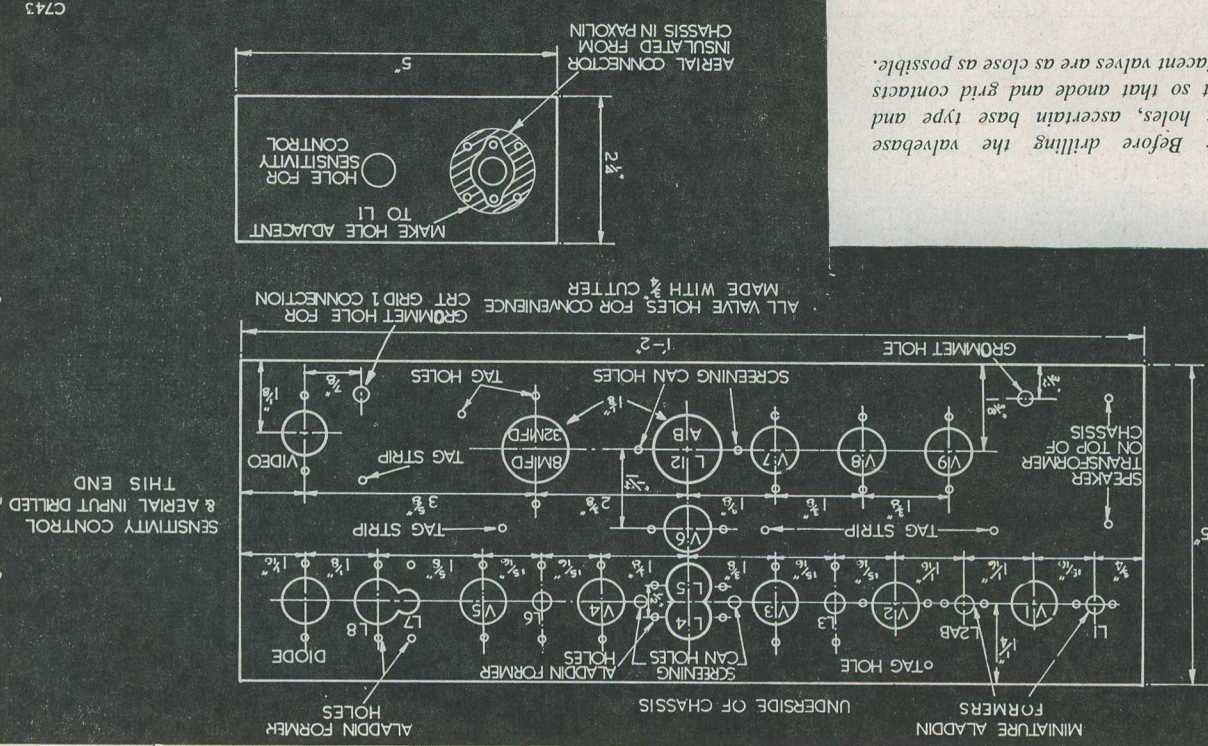The EHT lead is also not shown in the illustrations, but this is carefully soldered to the point provided on the line-output transformer and thus to final EHT smoothing.



Note: Before drilling the valvebase fixing holes, ascertain base type and mount so that anode and grid contacts of adjacent valves are as close as possible.

the sketch.

Note the convenient method of mounting the Focus pre-set and Focus control. HT + "B" and HT + "C" were soldered to a rigid tag board beside the line-output transformer, and thus these two voltages were available for the time-base and focus circuit. The deflection connections were also made to this tag-board, resulting in a tidy arrangement.

The revised voltage supply mentioned in the last issue for Grid 2 can be obtained from the seven-pin plug on the rear focus board, where the line deflection coils pick up No. 7 on the line-output transformer. Once again it was shown to be a wise decision to use paxolin or plastic for the rear board. Four bolts forming a solder-tag strip attached to this board supplied a simple means of connecting the 0.1 μ F decoupling condenser and 470 k Ω series resistor. The other side of the bolts also carried solder tags, and connections for this to No. 7 (No. 1 of deflection coils) were found on the seven-pin connector.

The leads from this connector to the deflection coils should be long enough to allow of change-over, should the picture be incorrectly polarised. If upside-down, reverse the Frame leads; if mirror-wise, change the Line leads.

Returning to the vision and sound strip, component values for the detector and video stage are to be found in the June issue; in the underside view of the chassis these are enclosed in the small dotted-line area.

The Grid 1 connecting wire may be un-

screened, but should be kept as short as possible and brought out at the rear well clear of the field created by the line-output transformer. The effect of such interference on the picture would be seen as a series of vertical black bars.

The connections to the Volume control are not likely to need screening, but a convenient method could be the use of standard screened two-way cable. The screening then forms the chassis connection.

NOTE: The Brilliance network is returned to chassis in this manner—see sketch of control panel. Unless this is done, the tube will be blacked out at all times. Before switching on, the drive control should be turned down and all controls should be adjusted to provide normal working conditions. Only then should the drive control be brought up to about half swing position.

Once again referring to power supplies, for the best average working the voltage at HT + "B" should be about 180V. The total current required is approx. 180 mA.

Thus it is probably the wisest course to include temporarily a large limiting resistor, say 1000 Ω 20W working, from the power pack, and make several readings with a meter before taking the resistor out of circuit.

In actual practice, using the metal rectifier circuit shown from a 230V AC mains supply, 250V DC was obtained after the reservoir condenser. When passing through the Allen Components choke and the focus coil, the voltage at HT + B was, in fact, exactly 180V DC, which is ideal for large screen TV.

MOUNTING THE BRIMAR C17BM CRT

This 17" rectangular tube lends itself admirably to the installation design given in the Feb./Mar. and April issues.

These copies should be referred to, and with the information and illustrations given here a clear picture of the required constructional work will be seen.


The cabinet specially made for the Radio Constructor's television is identical for all the variations of design given in these articles, and the tube screen opening in the front is also uniform. The battens inside the cabinet for supporting these installations are adjustable to cover any discrepancy which may occur during construction.

Note: There was an error in Fig. 4, April issue; the actual cut-out in the mask board should have been given as $14" \times 10\frac{3}{4}"$. For the Brimar C17BM tube, this cut-out will be increased horizontally and vertically by $\frac{3}{4}"$, to $14\frac{3}{4}" \times 11\frac{3}{4}"$.


Prepare the baseboard (Feb./Mar. issue) but increase in depth by $\frac{1}{2}"$.

Prepare focus board and drill hole $1\frac{1}{2}"$ diam. for the tube neck, exactly $10"$ up from the bottom edge. Also drill the hole for the 7-pin connector, and the holes for the focus coil fixing bolts.

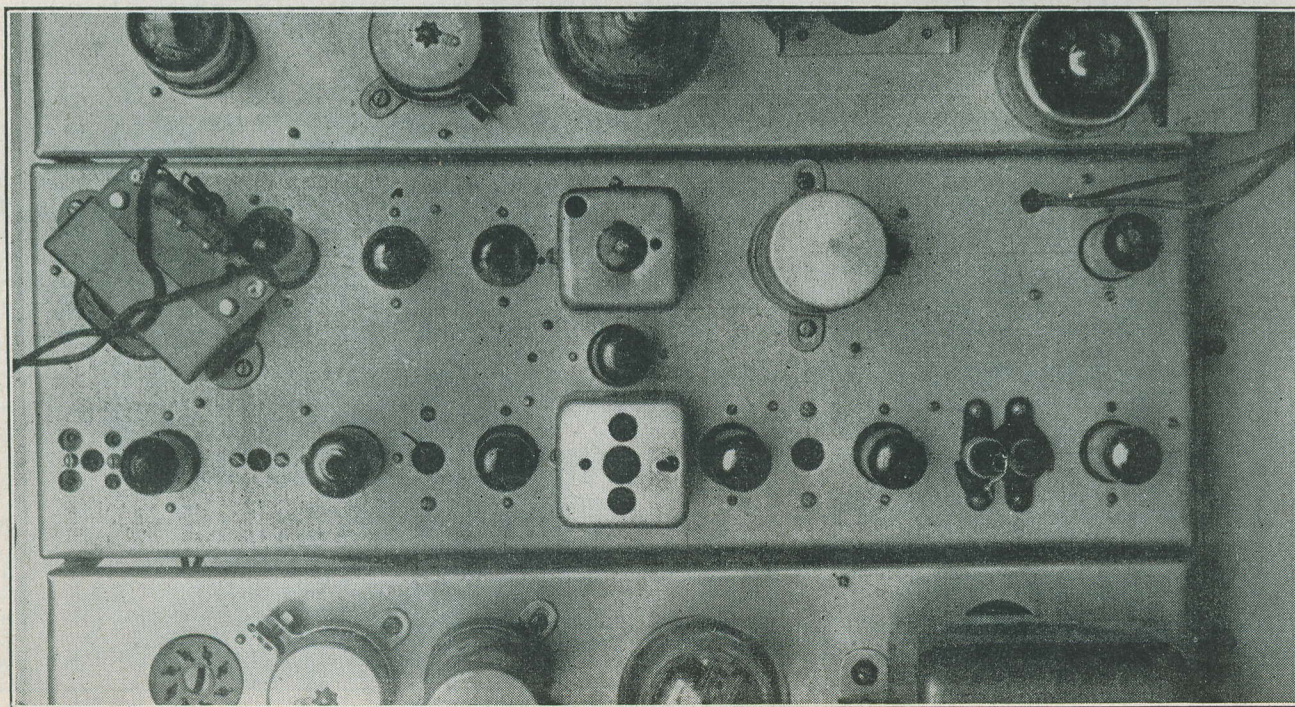Note the method shown in the photograph of obtaining HT + B and HT + C for the focus



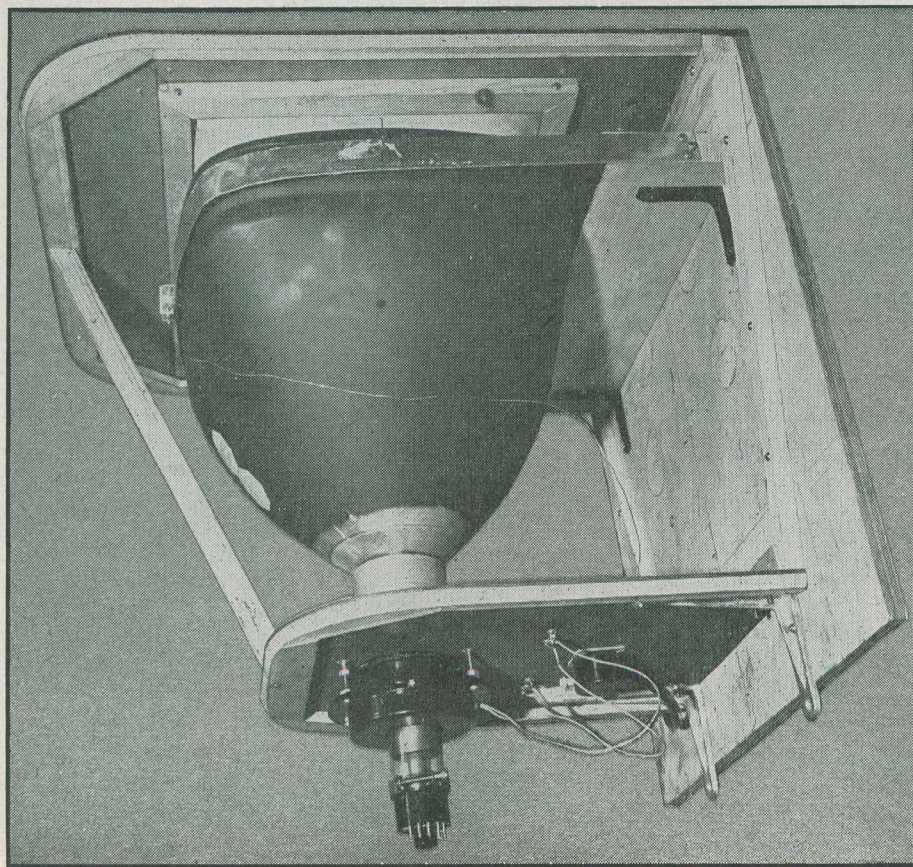Top View of Vision/Sound Chassis. Parts of the Timebase and Power Supply Chassis will be seen on either side.



The C17BM Tube Mounted.

Take care not to damage the EHT nipple. Slide on the deflector coils, which should have loose connecting wires, colour coded, all ready for connection to the 7-pin plug.

Gently slide on the focus board, and bring both deflector coils and focus board forward up the neck until the coils are firmly against the cone of the tube.

Screw down the brackets at rear of focus board.

Fix blanking-off fillets on the base board, as shown in the Feb./Mar. issue.


coil. Two 6-BA bolts are put through the paxolin board close to the 7-pin plug, where these two HT voltages may be carried from the chassis. Solder tags are placed both sides of the board, and thus the dust proof scheme is effectively maintained.

Now make the tube support as in the sketch (this issue) and screw down on the base, exactly 2" in from the front edge of the base-board to the front of the tube support. Make sure this is parallel.

Enter the two 1" 4-BA bolts into the dural straps at the top, and place the tube in position.

VAD/392 15

CATHODE RAY TUBE C 17 BM

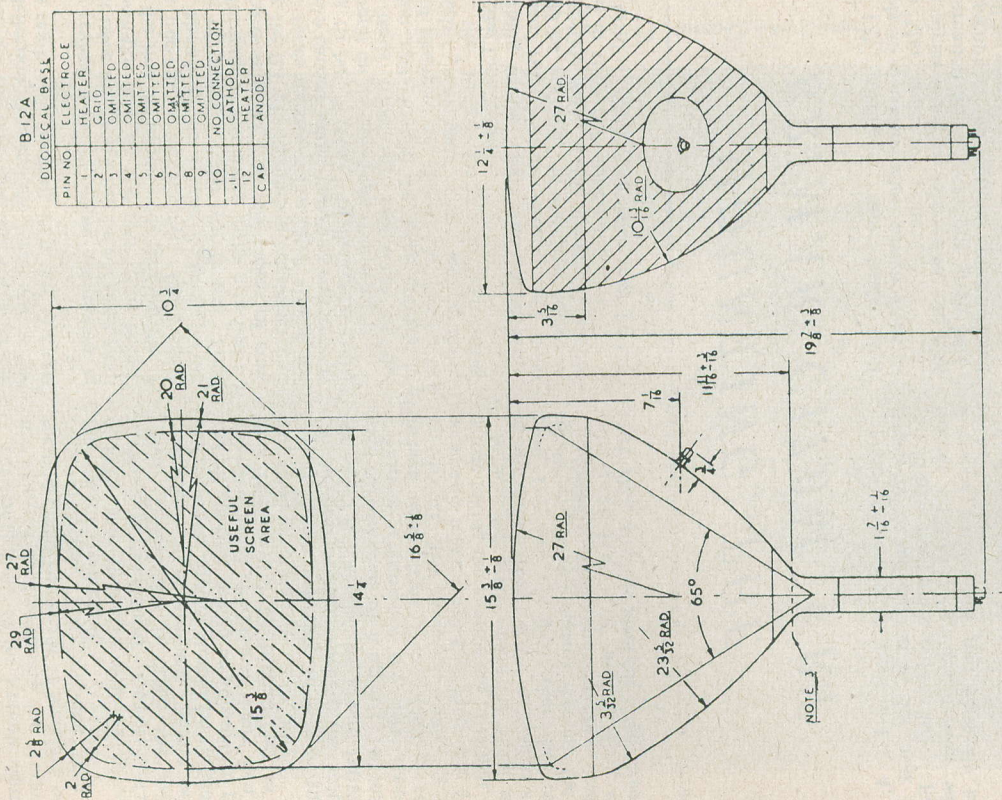

Details of the Brimar C17BM Tube.

Make the mask board, and either mark out from the centre of the tube using paint spot as previously explained, or if the tube support and other construction is accurately carried out this can be done from the measurements shown in the small sketch of part of the mask board.

Construct the mask itself (April issue) and fit the safety glass.

Notes

The Brimar tube is longer than the English Electric one, and it may be necessary to fit a tube base protection, known as a "bowler hat," to the cabinet backing.

Considerable improvement was obtained over the method previously described for padding the hole for the tube neck. Some channelled sorbo rubber was discovered at Burtleigh's Rubber Shop, 303 Edgware Road, London, W.2., and when this was cemented around the hole with Bostik a really good dustproof fit was obtained.

No air space is required between the tube and the mask, so that constructors may follow the screen contour exactly.

No final smoothing for the EHT is required with this tube. The tube coating should be connected to chassis (see photograph). This provides a condenser of approx. 0.0016

μF, which is just right.

The C17BM is a triode, and no connection is required for pin 10 on the base.


Full scanning and some slight additional EHT is obtainable by adjusting the width control and (VR5) the drive control.

Should any difficulty arise in centring the picture, a simple method of so doing is to fit a single-field ion-trap magnet and rotate in position as required for the English Electric tube.

Although the Brimar tube does not expose any area live to EHT, other than the connections, there is everything to be said for the dustproof design of installation given in this series. One of the annoying features of most TV sets, not excluding those of commercial manufacture, is the difficulty in maintaining a clean screen. Indeed, it often entails dismantling the whole thing to do so. Occasionally, too, blow away the dust from the line output transformer.

You are again advised to wear goggles at all times when constructing; there is always an attendant risk when handling highly evacuated tubes.

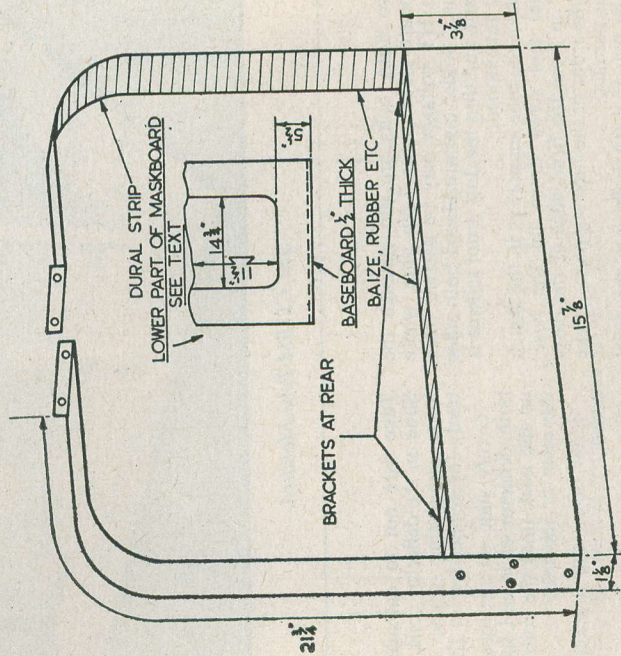Finally, we found the Brimar C17BM to be a most excellent tube, easy to instal and possessing a high degree of resolution and brilliance.



MOUNTING FOR BRIMAR C17BM

C749B

It's your choice

IF THE COMPONENTS ARE BELOW STANDARD, THERE'S NOT MUCH JUSTIFICATION FOR EXPECTING FIRST CLASS RESULTS. IT HAS BEEN OUR EXPERIENCE AND THAT OF MANY SATISFIED CUSTOMERS THAT IN BUILDING TELEVISORS IT DEFINITELY PAYS TO USE THE BEST COMPONENTS. ALL ITEMS SUPPLIED ARE NEW AND GUARANTEED.

LARGE SCREEN TELEVISOR

5 CHANNEL SOUND & VISION UNIT.

	Each
32-1/2 wt. Resistors	6d.
1-1wt. 1.5K	1/-
2-25K Colvern Pots	6/4
1-500K Morgan Pot	5/-
6-B7G Ceramic Valve Holders	1/9
1-B9A Nylon Valve Holder	1/6
1-Output Transformer 117	17/3
1-1 Coil Denco	4/6
1 ea. L2A, L2B Coils Denco	2/6
1-17 Coil Denco	3/6
1-L17A Coil Denco	8/6
5-6AM6 or 777	25/1
1-12AT7 or 8309	25/1
1-6AT6 or DH77	17/3
1-6AL5 or D77	12/11
1-6AQ5	18/8
16-TCC 100pf	3/-
7- " 47pf	1/9
1- " 10pf	1/9
1- " 22pf	1/9
1- " 100pf	1/8
1- " .01mid	2/-
1- " 320pf	2/-
1- " .05mid	2/-
1- " 220pf	2/-
1- " 32mid 450v	10/-
1- " 50mid 12v	2/9
1- " .001mid 1000v	2/2
1-Chassis Drilled	Not yet fixed

TIME BASE UNIT.

	Each
37-1/2 wt. 20% Resistors	6d.
1-6.8K 1/2 wt. 10%	8d.
1-10K 2 wt. 10%	1/6
1-47K 2 wt. 10%	7/-
1-100K Morgan Pot with Switch	5/-
1-2Meg Morgan Pot	5/-
4-100K Colvern Pots	6/4
2-500ohm Colvern Pots	42/-
1 set Allen Deflection Coils	35/-
Allen Focus Unit	10/-
Allen Linearity Control	10/-
Allen Width Control	21/-
Allen Frame Transformer	50/-
Allen Line Transformer	Not yet fixed
The above six items made by Denco, will be available in August.	
1-6AL5 or DH77	12/11
2-N78	18/8
3-12AU7 or 6SN7	25/1
1-6U4CT	23/3
1-6CD5G	32/3
1-RT16 or 6AG6	28/8
1-KT16 or U37	2/6
3-Deco Video Chokes	1/9
4-TCC .001mid	1/9
1- " 10pf	1/9
1- " .05mid	2/6
1- " 85mid 350v	3/6
1- " 2200pf	2/6
1- " 1mid 350v	2/3
1- " 32mid 450v	10/3
1- " 22pf	1/9
1- " 10pf	1/8
1- " 1mid 750v	3/6
1- " 5mid 750v	3/6
1- " 1mid 500v	2/6
1- " 50mid 12v	2/6
1- " 32mid 450v	7/6
1- " 32mid 500v	1/10
1- " 47pf	1/9
1- " .001mid CP57H00	18/9
1- " 805mid	1/9
1- " 680pf	1/8
1- " 390pf	1/2
1- " 5mid 350v	3/3
1-Chassis Drilled	Not yet fixed

POWER SUPPLY UNIT.

	Each
1-Allen Auto Transformer	35/-
AT 310V	22/6
1-Allen 3H, 250mA Choke	37/1
1-Rectifier 4A3Z	10/-
1-TCC 32mid 450v. CE37P	14/-
1-TCC 100mid 350v. CE10LE	£24-6-5
1-English Electric T901 16" C.R.T.	£24-6-5

SEND FOR DETAILED PRICE LIST, POST FREE. PROMPT DELIVERY. TERMS C.W.O. OR C.O.D. POSTAGE EXTRA.

We offer the best - it's up to you

TELE-RADIO (1943) LTD.

177a, EDGWARE ROAD, LONDON, W.2

TEL: PAD 6116
PAD 5606

Shop Hours:
Monday-Saturday 9 a.m.-6 p.m.
Thursday 9 a.m.-1 p.m.

QUERY CORNER

A "Radio Constructor" Service
for Readers

Sound on Vision

I have a commercial television receiver which has given a very good picture for over a year, but lately a fault has developed which is similar to the effect associated with sound on vision. However, with the aid of a borrowed signal generator the alignment of the vision and sound channels was checked but with no improvement. Is there some other fault which can cause the picture to be modulated from the sound channel?

E. Edwards (Manchester).

In view of the fact that the receiver alignment has been carefully checked it would appear that the cause of the trouble is microphony in one of the valves in the timebase unit. Microphony in the vision circuit of a television receiver usually manifests itself as a jitter on the picture, the affect only being apparent on loud sound passages from the speaker. The most likely valves to suffer from microphony are those in the frame timebase, the output valve being particularly susceptible. However, the check for microphony is a simple one as it is only necessary

to remove the back of the receiver and very lightly tap the suspected valves in turn, whilst noting the effect upon the picture. If one of the valves is faulty a very pronounced jitter will be apparent on the picture during the tapping test.

If the trouble is traced to one of the valves it is always a good plan, if the receiver employs more than one of the faulty type, to change the valves around. For example, a valve which is slightly microphonic may upset the picture if it is used in the frame output stage; but in the sound output stage the same valve will in all probability function very satisfactorily.

AC Televisor on DC

Having recently removed to an area which is still on DC mains I wish to convert my pre-war AC television receiver for use on DC. Would you recommend any modification to the receiver, or is the best plan to purchase a DC-to-AC converter?

B. Mowlam (London).

Two factors have largely been responsible for making the AC/DC type of television receiver an economical proposition. The first was the introduction of a range of TV valves all of which had a common heater current, and the second factor was undoubtedly the use of the flyback method of obtaining the EHT voltage for the cathode ray tube. Whilst this latter feature can be incorporated in a receiver of pre-war vintage, it is a costly business to change the majority of the valves to more modern types having a common heater current to allow for series connection. Such a modification is also complicated by the fact that in many instances the newer valves will have rather different characteristics, which in turn will demand changes in some component values.

Thus the simplest, and in the majority of cases, the most economical plan, is to purchase a DC/AC converter such as is manufactured by Valradio Ltd. However, if there are others of our readers who are faced with this problem of running an AC televisor from a DC supply, we shall be

QUERY CORNER

RULES

- (1) A nominal fee of 2/6 will be made for each query.
- (2) Queries on any subject relating to technical radio or electrical matters will be accepted, though it will not be possible to provide complete circuit diagrams for the more complex receivers, transmitters and the like.
- (3) Complete circuits of equipment may be submitted to us before construction is commenced. This will ensure that component values are correct and that the circuit is theoretically sound.
- (4) All queries will receive critical scrutiny and replies will be as comprehensive as possible.
- (5) Correspondence to be addressed to "Query Corner," Radio Constructor, 57 Maida Vale Paddington, London, W.9.
- (6) A selection of those queries with a more general interest will be reproduced in these pages each month.

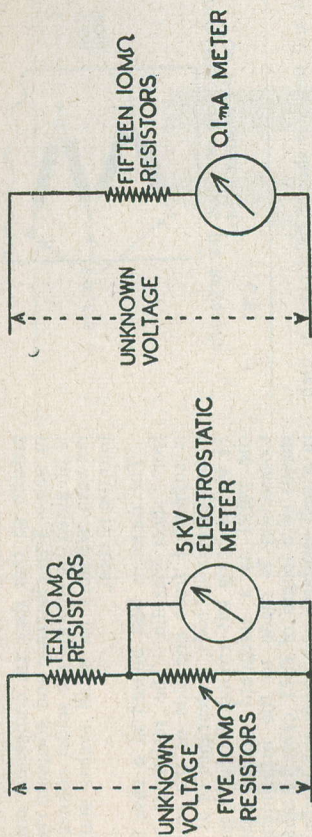


FIG. 1A. ALTERNATIVE 15KV VOLTMETER ARRANGEMENTS. FOR DETAILS OF THE RESISTANCES SEE TEXT.

FIG. 1B.

C752

pleased to advise them regarding the work involved in making a conversion to their specific set.

EHT Measurement

I am frequently asked to repair television receivers, and have often felt the need for a voltmeter which is capable of measuring the EHT potential for the CR tube. A search of Government surplus stores has only provided one electrostatic voltmeter, which is capable of reading between 1 and 5 kV. Would you recommend me to extend the range of this meter, or is there some suitable instrument which is available at a reasonable price?

D. Askwith (Guildford).

Ideally, a voltmeter which is designed to indicate EHT voltages should present a negligibly small load on the voltage source. This condition is fulfilled by the electrostatic voltmeter, and also by the calibrated adjustable spark gap. An example of the latter type of instrument is already on the market at a reasonably low price, but unfortunately the availability and cost of electrostatic voltmeters which are capable of measuring up to 15 kV puts them rather outside the grasp of many constructors. A compromise can, however, be made by using components which are readily available, this compromise being in respect of the impedance of the meter. For normal use in the design and service of TV receivers a meter which requires a full scale current of 0.1 milliamps is quite satisfactory, and such an instrument can be made using one of the 5 kV electrostatic voltmeter which can still be found in very limited numbers on the surplus market. The general arrangement is shown in Fig. 1A and can be seen to consist merely of a potential divider with the meter joined across the lower limb. The divider consists of fifteen 1 watt

resistors each of 10 megohms, the meter being connected across the lower five resistors. The accuracy of the meter may be adjusted by slightly varying the value of the most earthy resistor. Adjustment is made by either shunting the resistor with others to decrease the value, or by adding additional resistances in series with it to increase the value. Such final adjustment can of course only be made where a known EHT voltage is available. If this is not the case, a reasonably good accuracy can be obtained by choosing all fifteen resistors to be of substantially the same value. The help of a local dealer can probably be enlisted in this connection when the resistors are purchased. It will be appreciated that within the normal manufacturing tolerances the actual value of each resistor is unimportant, but for the accuracy of the meter they must either all be of substantially the same value or some final adjustment made to one of them as already described.

An alternative arrangement which will appeal to those who possess a 0.1 milliamp meter is to employ a similar resistive network, but to connect the meter in series in the earthy end as indicated in Fig. 1B. With this circuit it is necessary that the total resistance in series with the meter be 150 megohms if the instrument is to accurately measure 15 kV.

Whichever arrangement is used, great care is necessary in constructing the resistive network. The fifteen 10 megohm resistors are mounted in ladder formation on a sheet of high grade paxolin as shown in Fig. 2. The spacing between resistors is 1 inch, and solder joints should be made at least $\frac{1}{2}$ inch from the body of the resistors. To prevent trouble with corona all sharp points left on solder connections should be carefully rounded with a fine file. When the network is com-

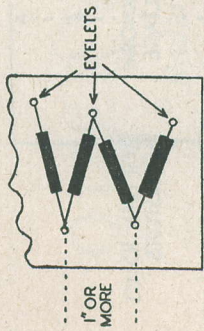


FIG. 2. METHOD OF MOUNTING THE RESISTORS ON THE PAXOLIN PANEL.

C753

pleted and tested it should be dipped in high grade molten wax for several minutes, then removed and the wax allowed to harden. The resistors should preferably stand clear of the

paxolin so that they are completely encased in wax. This clearance and adequate rigidity is obtained by making the solder connections between resistors on small eyelets stamped into the paxolin.

The meter is best housed in a case made from sheet paxolin. The resistance panel is supported from one side of the case by means of ebonite rods, a clearance of at least 1½ inches being left around the EHT end of the panel as a safeguard against corona. Connection is made to the instrument by means of a length of EHT cable terminating in a well insulated test prod; the earthy lead may be ordinary PVC-covered flex and is conveniently terminated in a crocodile clip for making contact with earthing points.

from our



Mailbag

VOLTAGE REGULATORS

Dear Sir,

With reference to "Mailbag" in the July "Radio Constructor," Mr. Thompson discusses voltage stabilising tubes in a parallel circuit for DC operation; this circuit is seldom used for DC, for the reason outlined by Mr. Thompson. Two tubes can be parallel connected in the opposite sense to provide a regulated AC supply (Fig. 1), but for a stabilised DC voltage either series, or series-parallel, circuits are usually used (Figs. 2 and 3).

With the circuit in Fig. 2 a high voltage at medium current output is available. R1 is adjusted, before any load is put on the tubes, so that 30-40 mA is passing through them. R2 is approximately 100-250 kΩ, and is adjusted to ensure even striking.

In Fig. 3, four tubes are used in a series-parallel arrangement to give high voltage at high current, stabilised output. A low voltage tap is provided at the centre tap of the tubes. R1 and R2 are adjusted as before to allow correct working characteristics.

Hoping this information will be of use to the "Radio Constructor."—C. R. West (Derby).

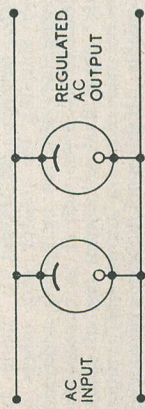


FIG. 1

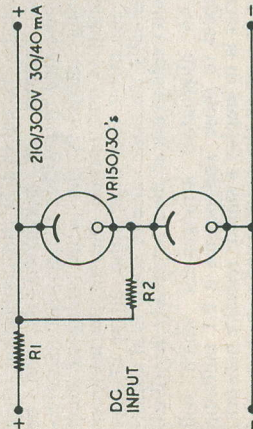


FIG. 2


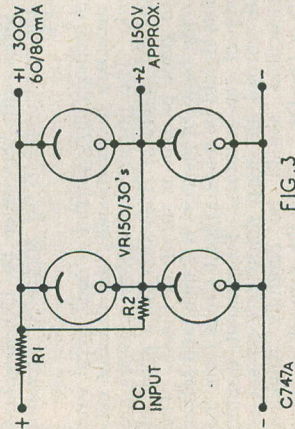


FIG. 3

C747A

TWO STATION R.F. UNIT

by R. W. HILL

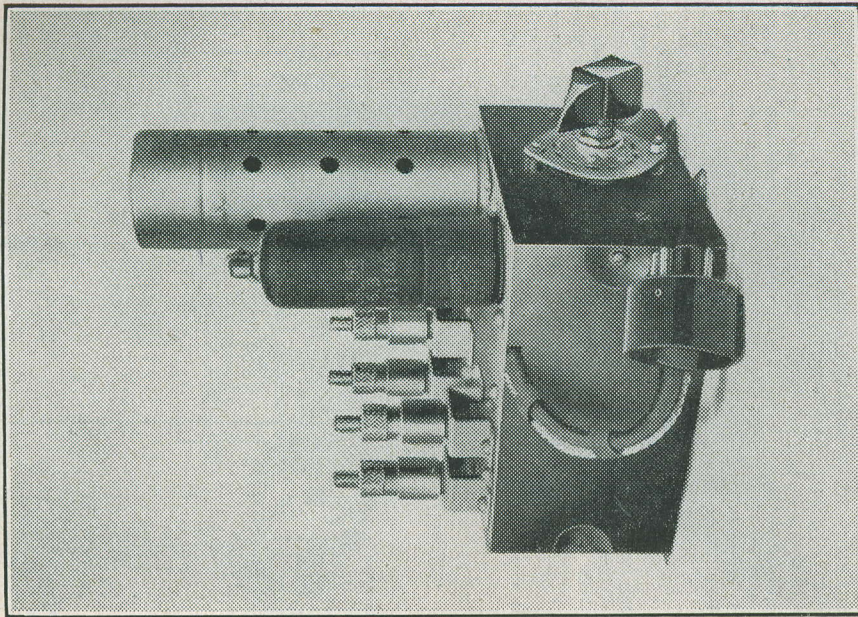

Constructional details of a useful local station tuner made from surplus TR1196 gear

Do you ever suffer from those pieces of ex-service equipment which lumber up the workshop, after having been stripped from a larger piece of apparatus? You know, those sub-assemblies which come away nicely in one piece and look too good to strip down into component parts; you show them to friends, and one and all agree that they will be very useful for something or the other, and back they go on the shelf again to wait for that something or other to turn up.

Now I have been haunted recently by one of these potentially useful bargains, for having done the right thing as expected of every keen Radio Constructor reader and converted

the TR1196 to an all-wave superhet, I found that one of the pieces left over was the top deck tuning unit with the four pre-set air-spaced capacitors, coil and Yaxley switch, which had been tossed aside in the early stages of dismantling. This thing looked extra useful, and had been leering at me so hard from the shelf that it immediately sprang to mind when I promised to make an "Old Folks" local station receiver, and just right it proved to be.

Home and Light were the only requirements, and the four pre-sets were just right for an RF-Detector circuit. I made up the chassis as an independent RF unit, with the circuit

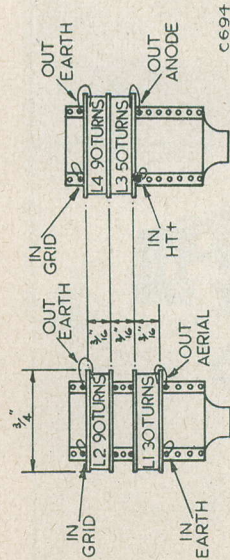


Fig. 3: The coils, giving constructional details and winding data.

from a very old 110 kc/s IF transformer and, despite the fact that L2 and L4 bulked to different sizes owing to the presence of wax on the wire for the latter, the difference in inductance was unimportant in this application—they both read about 150 μ H and the Light on 1214 kc/s and Home on 908 kc/s are well within the range of the trimmers. The wire needs very careful handling as all strands have to be intact and bonded properly at the ends, otherwise performance will suffer. I don't know the professional method of cleaning the ends, but the easiest way I found was to pass the end through a match flame for a second and wipe off the burnt enamel with a cloth. If it is left too long in the flame there won't be any wire to clean, so it would be advisable to get the procedure right before trying it on the short end of a carefully wound coil!

The Chassis

Removal of the top paxolin panel will reveal two square holes, and amphenol valve-

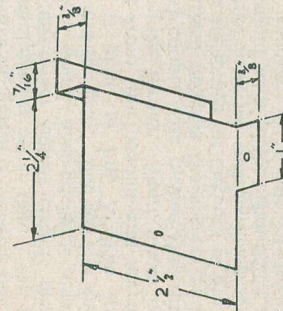


Fig. 4: The screen, made from 20 swg aluminium, or similar.

holders will fit across the corners of these with the judicious aid of a few washers. Next remove all unwanted components, the coil and the spindle of the switch. The switch is operated from the other end, as the space between the capacitors is needed for the aerial coil. A screen is needed in this compartment and the dimensions are given in Fig. 4; one of the fixing lugs from the original coil is retained and holds one side of the screen, the other side is bolted to the deck of the chassis. This leaves room for the aerial coil to be held through one of the existing holes and the late switch spindle hole will take an aerial socket nicely. While on the subject of saving the mechanical work, room for the wires going across the chassis and out the side can easily be made by snipping the edge of the chassis and bending a piece down; this saves drilling, and a small length of insulating tape will protect and hold the wires in position.

The switch is a bit awkward, as the movement between two contacts is 90° instead of the usual 30°, and there is no locator. On the aerial switch wafer the two contacts on the side nearest the aerial trimmers are used, and the rotating portions of the other two wafers are moved through 180° to bring the contacts used away from the rest of the wiring. As the locator needed is non-standard, an attempt was made to manufacture one from the original round disc, cut out and worked with a few levers and springs. It worked well enough, but used though I am to Heath Robinson contraptions, this one frightened even me, so recourse was made to modifying a standard locator. This is mounted so that it comes outside the chassis. The spigot or spindle should be 2 1/4-in. and the 6BA fixing rods 3 1/8-in. long; these can either be cut and threaded from the original rods or fresh screwed rod can be used. The locator is held away from the front of the chassis by two 1/4-in. spacers. The stops will probably be in the wrong position; they can be punched flat and replaced by small rivets. Flattening

out the middle "click" also helps to give a positive location in the desired position.

The use of a metal switch spindle gave rise to instability, due to coupling between the two adjacent switch wafers. This was cured by fixing the brass collar close to the centre screen and earthing it to the screen by a flying lead. Other precautions against instability were screened grid leads and a can for V1; the latter may not be necessary if the circuit is otherwise stable. The decoupling components R7 and C14 were needed to prevent RF feedback from the AF amplifier. L3/L4 is mounted below V2, and the earthing of the various components around this valve-holder is kept reasonably compact.

The value of R3 will need to be found on test; it is shorted out—giving full gain—on the weaker station, and left in circuit on the stronger station. This gives more pleasant listening by saving the listener from being deafened when switching over to the louder station. The value can easily be found after a few trials; I found 3 k Ω right for my locality.

In bad areas, a little fixed reaction could be introduced by means of a 40 pF trimmer slung in the wiring between the anode of V1 and the anode of V2. This would seem to be a little unorthodox as there is no mention of chokes or reaction windings, but it works surprisingly well, and the increase in gain and selectivity is very considerable.

OUR 16in. TV AT EARLS COURT

(August 26th to September 6th)

We are pleased to inform readers that visitors to the Exhibition will be able to see complete models of the Large Screen Televisor on the following stands:— Brimar (Stand 6), English Electric (Stand 67) and G.E.C. (TV Demonstration Room D6).

The Editor Invites

articles from readers, of a nature suitable for inclusion in this magazine. Articles submitted for publication should preferably be typewritten, but ordinary writing is acceptable if clearly legible. In any case, double spacing should be used, to allow room for any necessary corrections. Drawings need not be elaborately finished, as they will usually be redrawn by our draughtsmen, but details should be clear. Photographs should preferably be large (half-plate) but in any case the focus must be good. Much useful advice to prospective writers is given in our "Hints for Article Writers", which will be sent free on request.



THOSE who wish to supplement their existing knowledge with a sound technological background or pass qualifying examinations, can do so by means of I.C.S. Home Study Courses. These include RADIO ENGINEERING · RADIO SERVICE ENGINEERING · ELEMENTARY ELECTRONICS, RADAR · ADVANCED SHORT WAVE RADIO · RADIO · TV TECHNOLOGY and training for the following examinations—B.I.R.E. · P.M.G. CERTIFICATES FOR WIRELESS OPERATORS · C. & G. TELECOMMUNICATIONS · C. & G. RADIO SERVICING CERT. (R.T.E.B.) · C. & G. RADIO AMATEURS · etc., etc. Students are coached until successful. Fees are moderate and include all books required.

GENEROUS DISCOUNT TO H.M. FORCES.

WRITE TODAY for FREE BOOKLET describing complete facilities for the successful study of Radio and TV technology.

INTERNATIONAL CORRESPONDENCE SCHOOLS LTD.
Dept. 163a, International Bldg., Kingsway, London, W.C.2
Name..... Age.....
Please send booklet on subject.....
(BLOCK LETTERS PLEASE)
Address.....

DESIGN FOR AN "ECONOMY" MAINS RECEIVER

by R. K. VINYCOMB, B.Sc.

This set has been titled "Economy" for three reasons: Firstly, the design has been worked out so that the maximum efficiency can be obtained from two valves and the total mains consumption is only about 40 watts, although no transformer is used and the set will operate from either AC or DC mains. Secondly, the parts list has been chosen to include only components which are at present cheaply available. Thirdly, the construction of the set is simple; there are no tricky layout problems and beginner or old hand will find a real economy on labour when building this set compared to many others.

Now, what sort of performance can be expected from this set? Well, it is not intended to be fully portable and in most areas some sort of external aerial will be required. Except in difficult locations, however, an indoor one, round the picture rail, say, will be quite adequate. The original model was arranged to tune only two pre-set stations on the medium waveband—the Home Service on 908 kc/s and the Light Programme on 1214 kc/s. Operating fifty miles from London, the volume was more than adequate for bedroom and personal listening with a short indoor aerial. With an outdoor aerial, tests showed that the Third Programme on 647 kc/s and several Continental stations could be received at good strength. Although the set itself could be packed into a small space, this has not been carried to the extent where the result is a "midget" receiver. A set with a fairly open layout is easier to construct, has a longer life of components (because midget highly-rated parts are avoided and the heat generated is more easily dissipated) and enables a larger loudspeaker to be used. In all, this results in better tone and volume. Having made this point about size, it is not proposed to give dimensioned drawings

of the prototype receiver, since the layout is not at all critical. It will also depend, to some extent, on the actual components which the constructor buys or has available. Considerable latitude is allowable in most of the components, but any special points will be mentioned when we come to the business of discussing the design of the set. Instead of giving exact details, from which readers could make a "Chinese copy" of the original set, the purpose of this article is to give, as fully as is practical, the methods used in selecting the circuit, designing the set and choosing the components. Individual constructors can then design their own set on the same lines, making variations from the original where necessary. Firstly, then, we come to the choice of circuit.

Circuit

If loudspeaker results are desired, the minimum number of valves needed is two (excluding the rectifier). The detector-plus-output arrangement is the best one for local station reception and this is, in fact, the one adopted. The application of regeneration to the detector stage is almost a necessity, and there are several ways of doing this. Most readers will be familiar with the usual "reaction" circuits using an anode coil closely coupled to the tuning coil. These can be quite satisfactory with most triode detectors and with some RF pentodes used for detection. They all suffer to some extent from disadvantages. Changing the amount of "reaction" shifts the tuning (a serious difficulty with pre-set tuning) and a volume control is required in addition to the reaction control, since the latter is not able to reduce the gain to zero. Both these difficulties can be avoided by using the electron-coupled regeneration circuit, which has, in the writer's opinion, been sadly neglected in the past except for specialised short-wave receivers.

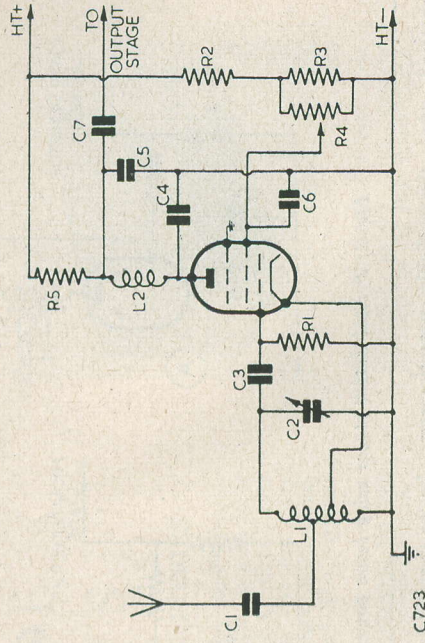



Fig. 1: The basic circuit for an RF pentode used as an electron-coupled regenerative leaky-grid detector.

It is shown in basic form in Fig. 1. A high-gain RF pentode with "sliding screen" characteristics is necessary for best results and, fortunately, valves of this type are readily available. The screen of the valve is fed from a potentiometer which acts as a combined volume and reaction control. It will be found that the volume can be gradually increased from nothing up to the point where the set slides smoothly into oscillation. As there is no "backlash," the control can be backed off slightly and the set operated at good volume without any signs of instability.

Suitable valves for the detector position are 12K7, 12SK7, 6K7, 6SK7, EF39, etc. Since an AC/DC set is contemplated, the valves will have their heaters in series and we should therefore choose, in the interests of economy, either the 12K7 or the 12SK7, having 12-volt heaters which pass only 150 mA. The 12K7 has a top-cap grid while the 12SK7 is single-ended. The latter was used in the original receiver. The electron-coupled circuit (Fig. 1) consists of a tuning inductance L_1 having two tapings. The variable condenser C_2 across the whole of the coil forms the tuning control. The aerial is connected through a small condenser C_1 to a tapping near the middle of the coil. This removes some of the damping effect of the aerial on the grid circuit without losing much of the signal voltage. The tapping near the "earthy" end of the coil is connected direct to the cathode of the detector valve. It is this that provides regeneration since the bottom of the coil is common to both the grid and cathode circuits of the valve. The

amplified RF signals which appear between anode and cathode of the valve are thus fed back in positive phase to the grid. Whether this positive feedback is sufficient to cause oscillation depends on the amount of feedback and upon the gain of the detector stage. RF voltages at the valve anode are prevented from reaching subsequent stages by the choke L_2 and are bypassed to earth by the condenser C_4 . Providing that the capacity of C_4 is adequately large, the amount of feedback depends on the position of the lower tapping on the tuning coil. For maximum efficiency, therefore, this tapping should be such that the stage just oscillates when the gain of the valve is at its maximum. Since the design must allow for variations in mains voltage, valve characteristics and aerial length, this ideal is not readily attainable, but it can be approached closely enough to give very satisfactory results.

The gain of the detector stage is varied by means of the screen voltage. This is obtained from a fixed potentiometer R_2 and R_3 , across the HT supply. Across the lower half of the fixed potentiometer is a variable potentiometer, R_4 ; the slider of this is bypassed by C_6 and connected to the screen of the valve. It is important that R_4 has a high-resistance, as that part of the potentiometer through which the screen current must pass has a valuable self-regulating effect on the gain of the valve. Since an RF pentode has a maximum gain as a detector when the screen voltage is less than that *actually* at the anode, the values of resistors R_2 and R_3 are chosen so that the optimum screen voltage is

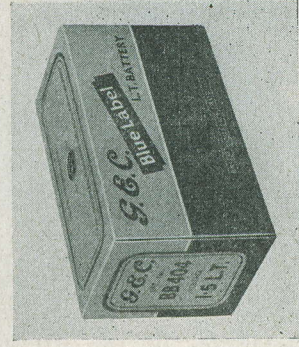

One of the attractive new style designed all-dry low tension batteries in the Blue Label range of radio dry batteries.

TRADE NEWS

NEW RADIO DRY BATTERIES

Seven popular new all-dry low tension batteries in attractive new-style cartons have been introduced into the G.E.C. Blue Label range of radio dry batteries. At the same time two new layer batteries have been added to the Red Label range of The General Electric Co. Ltd.

All of these batteries are designed for the latest battery portable and combined mains/battery operated receivers. Full details of all nine batteries are shown on leaflet BB.1721 obtainable from The General Electric Co. Ltd., Magnet House, Kingsway, W.C.2.

INDEX TO

Vol. 5. 1951-1952

A four-page index covering the issues Aug. 1951 to Aug. 1952 is available free of charge. Just send in a stamped, addressed envelope of suitable size, marked "Index RC" in the top left-hand corner, to A.S.W.P., 57 Maida Vale, London, W.9.

"ECONOMY" MAINS RECEIVER

Continued from previous page.

The value of C_9 is determined by the fact that the "time-constant" of the decoupling circuit should be high enough to ensure adequate bypassing. The time-constant in micro-seconds is given by the product $R_9 \times C_9$. For normal applications this should not be less than 50,000. If, for example, the value of R_9 is calculated to be 20,000 ohms, then condenser C_9 should be at least $2.5 \mu\text{F}$ and would, in practice, be made $4 \mu\text{F}$ for safety.

(To be Continued)

ARTHURS HAVE IT!

LONDON'S OLDEST RADIO DEALERS
LARGE VALVE STOCKS
 AVOMETERS IN STOCK
 Avo Test Meters and Signal Generators and Taylor Meters.
 Leak Point One Amplifiers and Tuning Units.
 Chapman Tuning Units.
 Crystal and Moving Coil Mics.
 Decca Replacement Heads and Pickups.
 Goodman's Astrom 150 Speakers.
 Partridge Output Transformers for Williamson Amplifier.
 All Components for the Radio Constructor's 16" Televisor.

Wear & Wright Tape Deck £35
 LATEST VALVE MANUALS
 Mullard, Osram & Brimar No. 4 5/- each
 Mazda 2/- each
 Postage 6d. extra


TELEVISION SETS, WIRE AND TAPE RECORDERS ALWAYS IN STOCK
 Goods offered subject to price alterations and being unsold.

Arthurs

Est. 1919 first

PROPS: ARTHUR GRAY LTD.
 OUR ONLY ADDRESS: **Gray House**
 150-152 Charing Cross Road
 London, W.C.2

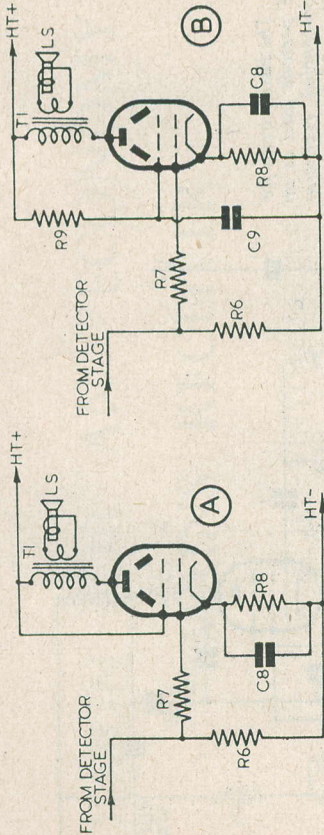TEMPLE BAR 583314 and 4765 WRITE FOR LISTS



C724

Fig. 2: Typical output stages using beam power valves.

obtained when the variable potentiometer slider is set about one-quarter of its travel from its high-potential end. The lower tapping on the tuning coil L_1 is then chosen so that oscillation occurs just as this position is approached. The gain of the detector stage may then be smoothly increased from a very low value (with zero volts on the screen) to the maximum obtainable (when oscillation just commences).

The operation of detection, or demodulation, is carried out at the grid of the detector valve by the conventional "leaky grid" system. C_3 is the grid condenser and R_1 the leak, which must be returned to earth, not to the cathode.

The AF load of the detector stage is provided by R_5 . If unlimited HT voltage were available, this resistor could be made very large, with a consequent increase in gain. With a simple AC/DC power pack, however, the HT voltage is unlikely to be more than about 200 volts. The value of R_5 must not be great enough to reduce the voltage at the valve anode too much, as this would, in its turn, reduce the gain of the detector. R_5 must therefore be chosen to give the best compromise between high load impedance and high voltage drop.

Condenser C_5 ensures that any remaining RF signal is bypassed to earth rather than being passed on to the output valve. Condenser C_7 is the conventional coupling to the output stage. The latter stage may be quite straightforward, adhering to the operating conditions recommended by the valve manufacturer. No volume control is necessary, since complete control is achieved by the screen potentiometer in the detector stage. Since the detector valve is already chosen, we should pick an output valve with the same

heater current rating. Output valves having 150 mA heaters are the 50L6, 35L6 and the 12A6. The latter is more readily available and, besides, has the advantage of being able to take up to 250 volts on the screen, whereas the 50L5 and 35L6 are limited to a screen voltage of 110 and would thus require a dropping resistor and decoupling condenser when used on standard British mains voltages. Typical output stages are shown in Fig. 2a and 2b. R_6 is the grid leak and R_7 a grid stopper to prevent parasitic oscillation. R_8 provides cathode bias and is fully bypassed by condenser C_8 . The output transformer T_1 should match the loudspeaker to the output valve so that the recommended load is presented to the latter. The ratio, r , of the output transformer is calculated in the following manner.


$$r = \sqrt{\frac{Z_1}{Z_2}}$$

where Z_1 = optimum load of valve
 Z_2 = voice coil impedance.

Fig. 2a shows the simpler arrangement when the screening grid of the valve may be connected direct to the HT line, while Fig. 2b shows how decoupling components R_9 and C_9 are added when a lower voltage is required at the screen. The value of R_9 can be calculated from Ohm's law as follows, if the voltage to be dropped is known and the valve screen current is obtained from the makers' data:

$$R_9 = \frac{V_{ht} - V_s}{I_s} \times 1000 \text{ ohms}$$

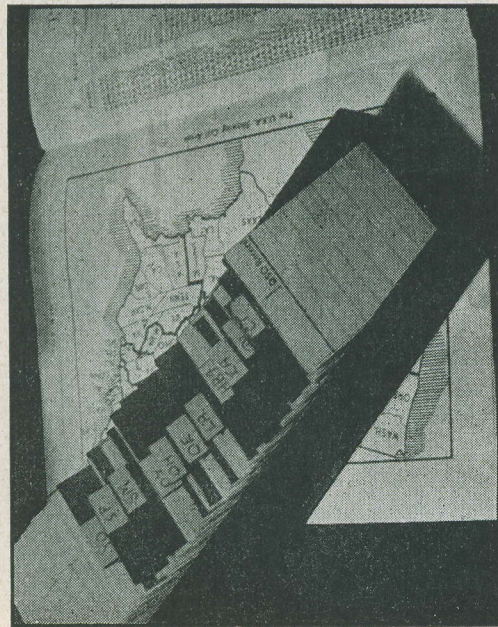Where, V_{ht} = HT voltage
 V_s = required screen voltage
 I_s = screen current, in mA.



Useful Accessories

'Minicard' Record Cards

from— **A.S.W.P.**
57 Maida Vale
Paddington
LONDON, W9

QSO RECORD CARDS 2½ ins. x 2¾ ins. printed both sides, available for Amateur Station records, at 3/3 per 100 post paid. Metal filing trays as shown, heavy gauge steel, green enamel to hold 500 cards, 3/3 post paid. Indices not available.

SUCCESS?

In Radio, Television and Electronics, there are many more top jobs than engineers qualified to fill them. Because we are part of the great E.M.I. Group we have first-hand knowledge of the needs of employers, thus our Home Study courses are authoritative and based upon modern industrial needs.

POST THIS COUPON NOW --- **START HERE**

E.M.I. INSTITUTES, Postal Division, Dept. 179,
43, GROVE PARK RD., CHISWICK, LONDON, W.4.
Please send, without obligation, your **FREE BROCHURE**
I have marked the subjects which interest me.

Mechanical Eng. Electrical Eng. Draughts-
manship. Radio. Television. Production
Eng. Automobile Eng. Aeronautical Eng.
 General Cert. of Education (Metric). Civil
Service.

Also Courses for—
A.M.I.Mech.E., A.M.I.C.E., A.M.Brit.I.R.E.,
A.F.R.A.E.S., CITY and GUILDS EXAMS in
Mech. Eng., Elect. Eng., Telecommunications,
etc.

NAME.....
ADDRESS.....

E.M.I. INSTITUTES — The College backed by an Industry
IC3

RADIO BOOKS

- Valve Technique (RSGB) 3/9
- Receivers (RSGB) 3/9
- Television Interference (RSGB) 2/3
- Simple Transmitting Equipment (RSGB) 2/3
- RSGB Call Book 3/9
- World Radio Valve Handbook (O. Johansen) 11/9
- World Radio Handbook (O. Johansen) 8/9
- How to Listen to the World (O. Johansen) 1/11
- Inexpensive Television (ASWP, Ltd.) 2/8
- TV Fault Finding (ASWP, Ltd.) 5/3

Above prices inclusive of postage, etc.
DATA PUBLICATIONS
LYON COURT, 57 MAIDA VALE,
LONDON, W.9.
Telephone CUN 6579

IKOPATENTS LTD.

Managing Director
E. G. O. ANDERSON

Consultants

- RADIO
- TELEVISION
- ELECTRONICS

17 CRISP ROAD, W.6
RIVERSIDE 2678

Join the
INTERNATIONAL SHORT WAVE LEAGUE

H.O., 123 Sturla Rd., CHATHAM KENT, ENG.

Send for Membership details at once.

ADCOLA
(Regd. Trade Mark)

SOLDERING INSTRUMENTS

Reg. Design No. 860302
(British, U.S. and Foreign Patents)

Designed for wireless assembly and maintenance. Supplied for all volt ranges from 6/7v to 230/250v.

3/16" Dia. Bit Standard Model 22/6

Sole Manufacturers **ADCOLA PRODUCTS LTD.**
Sales Office and Works: Cranmer Court,
Clapham High St., London, S.W.4. (MAC 4272)

HENRY'S

5, HARROW ROAD, LONDON, W.2.
Tel.: PAD 1008/9 and 0401.

- 9" ESCUTCHEON. Brown bakelite. Suitable plate glass and mask for 9" tube. Price 7/6 complete.
E.H.T. TRANSFORMER for VCR97. Input 230v, output 2,500v 4v 2-0.2. 45/-
E.H.T. TRANSFORMER for 5CP1. Input 230v, output 3,250v 6.3v 2-0.2v 45/-
MAINS TRANSFORMERS. 250-0-250, 90m/a, 6.3. 3amp. 5v. 2amp. Input 110v/250v. £1. Post 9d.
EX-MANUFACTURERS. 350-0-350, 100m/a, 6.3v. 4amp. 5v. 2amp. Input 200/250. 26/-
REPLACEMENT TYPE. 350-0-350, 90m/a, 4v. 6amps, 4v. 3amps, Input 200/250. 18/6d.
DUAL PURPOSE TYPE. 350-0-350, 80m/a, 6.3v tapped 4v at 3 amps, 5v tapped at 2 amps. 4v. 20/- Post 9d.
WE STOCK ALL TYPES OF STANDARD CATHODE RAY TUBES AND VALVES. WE HAVE ALSO OVER 10,000 EX-GOVT. AND U.S.A. VALVES AT COMPETITIVE PRICES. SEND FOR LIST!
- MOVING COIL METERS (Brand New)**
- 0-5m/a square panel mounting 2" scale ... 7/6d.
 - 0-50m/a " panel mounting 2" scale ... 7/6d.
 - 0-40v. " panel mounting ... 7/6d.
 - 0-20amps " panel mounting ... 7/6d.
 - 0-300v " panel mounting ... 12/6d.
 - 0-40/120m/a double reading round scale ... 12/6d.
 - 2½" Round flush mtg. drilled frame. ...
 - Range 0/1750 volts 200 ohms per v each ... £12.6d.
 - Range 0/1500 volts 250 ohms per v each ... £12.6d.
 - Range 0/3000 volts 200 ohms per v each ... £13.-d.
- L.T. RECT'S.**
- 12v. 2½ amp. Westinghouse ... 12/6d
 - 12v. 4 amp. S.T.C. ... 17/6d
 - 12v. 8 amp. S.T.C. ... 37/6d
- S.T.C. RECT'S. E.H.T.**
- K3/25 650v. 1m/a. ... 4/7d
 - K3/40 1000v. 1m/a. ... 6/-d
 - K3/100 8,000v. 1m/a. ... 14/8d
 - K3/200 10,000v. 1m/a. ... 26/-d
- H.T. RECT'S**
- S.T.C. 300v. 75m/a. ... 6/-d
 - S.T.C. 150v. 120m/a. ... 4/6d
 - S.T.C. 250v. 250m/a. ... 18/-d
 - G.E.C. 1m/a. Meter Rect. ... 11/6d.
- WEARITE.**
- 705 Coil Pack 3 wave band ... 37/10d.
 - 400B Min. I.F. 465kc. pair ... 15/-d.
 - 501 and 502, 465kc. pair ... 15/-d.
 - 800's pair ... 15/-d.
- RECEIVER R1355.** As specified for Inexpensive Television. Complete with 8 valves VR65 and 1 each 504G, VU120, VR92. Only 55/-d. carriage 7/6d. Brand New in original Case.
RF24 25/-d., RF25 25/-d., RF26 59/6d., RF27 59/6d. Owing to limited quantities, these Units supplied only with R1355's.
- CATHODE RAY TUBES.**
- VCR97. Guaranteed full picture 40/-d. carriage 5/-d.
 - 3BP1 Suitable for scopes 25/-d., carriage 3/-d.
- PYE 45 Mc/s STRIP.** Special purchase of M.O.S. Type 3583 Units. Size 15" x 8" x 2". Complete with 45 mc/s Pye Strip, 12 valves; 10 EF50, EB34 and EA50, volume controls and hosts of Resistors and Condensers. Sound and vision can be incorporated on this chassis with minimum space. New condition. Modification data supplied. Price £5., carriage paid.
- INDICATOR UNIT TYPE 182A.** This unit contains VCR517 Cathode Ray 6" Tube, complete with Mu-metal screen, 3 EF50, 6 SP6 and 1 5U4G valves, 9 wire-wound volume controls and quantity of Resistors and Condensers. Suitable either for basis of Television (full picture guaranteed) or Oscilloscope. Offered BRAND NEW (less relay) in original packing case at 79/6d. Plus 7/6d. carr.

RADIUS

3, HOMER ST., LONDON W.1.
TELEPHONE PADDINGTON 9396 or 1968

RADIO : TV : ELECTRICAL AND ALL ELECTRONIC SPARES : TERMS—CASH WITH ORDER

BLOCKING OSC. TRANS. approved by RADIO CONSTRUCTOR for Large Screen T.V.

All components for Wide Angle 16 ins. Television in stock. Sold in Kit form or separately.

- A selected few of our Bargains:
 - 32 + 32 MFD. CONDENSERS, 450 volt. ALI Can 4/6
 - 16 + 16 MFD. CONDENSERS, 350 volt. ALI Can 3/6
 - 8 + 8 MFD. CONDENSERS, 500 volt. ALI Can. 3/-
 - 11, .05 500 VOLT WKG. ... 6d. each
 - ALL RESISTORS $\frac{1}{2}$ TO 1 WATT ... 3d. each
 - 2 GANG .0005 TUNING CONDENSERS ... 5/-
 - 3 + .15 DROPPERS ... TRANSFORMERS ... 3/6
 - STANDARD OUTPUT TRANSFORMERS ... 5/-

WATCH FOR OUR NEW F.M. RECEIVER KIT.

ANY CIRCUIT SUPPLIED—2/6

SEND S.A.E. FOR COMPLETE LIST.

CAN YOU

measure up to 50 mid. i. to 5 any resistor up to 5 megohms 1

IF NOT

it's our guess that you have £5 worth of good components of unknown value lying idle.

DO YOU

check all your components before building new gear?

IF NOT

we'll bet you often get some disappointing results. Only one component of the wrong value means poor performance.

THE ANSWER

is, of course, a Res./Cap. Bridge to measure each part quickly.

THE RADIO MAIL 30/- RES./CAP. BRIDGE KIT IS THE BEST RADIO VALUE OBTAINABLE TO-DAY

5 megohms-50,000 ohms 50 mid.-2 mid.
1,000 ohms-10 ohms .01 mid.-.0005 mfd. (5000PF.)
NO CALIBRATING. An accurately calibrated panel with each kit.
NEW COMPONENTS. Specially selected for accuracy. EASILY ASSEMBLED. Instructions, circuit and diagrams.

RADIO MAIL, 4 Raleigh St., Nottingham
Stamp for list and with all enquiries, please.

"YOU CAN RELY ON US"

BRIMAR OSRAM MULLARD
Valve Manuals 5/- each

- SELENIUM RECTIFIERS
 - 36EHT50 — 24/6 New Westinghouse—
 - 36EHT 100-30/6, 14A86-20/-, 14D36-12/-,
 - WX3-3/9, WX6-3/9 36EHT45, 20/6.
- LINE CORD 3 WAY
 - 0.2amp 100Ω per foot—8d. Ft.
 - 0.3amp 60Ω per foot—8d. Ft.
- DROPPERS
 - Standard 0.3A 800Ω 5/-, 0.2A 950Ω 5/-.
 - Midget 6/3 each 2 1/2" high.
- SURPLUS VALVES
 - Here are a few—write for our "Valve Bargain List", with over 120 types.
 - 6AG5-9/6, 6H6-4/6, 12A6-8/-, 3A4-7/6,
 - 6K6-8/6, 30S-0/6, 6L5-6/6, 6S7 metal-7/6,
 - 6BW6-12/6, 6BE6-15/-, 6AT6-10/6, 6BA6-12/6,
 - 50C5-13/6, 6U5 6.3v octal Magic Eye-7/6.
- TUBULAR CONDENSERS
 - 0.001, 0.002, 0.004, 0.005, 0.01, 0.1 6d. each
 - 0.25uF 1/- each, 0.5uF 1/6 each.
- MICA CONDENSERS
 - 0.001, 0.002, 0.003, 0.005, 0.01, 0.002, 0.005, 6d. each.
- VALVE CANS
 - 3 piece aluminium (Octal valves) 1/6 each.
- TRIMMERS
 - 50pF 50pF-75pF, 100pF 150pF-1/-, 250pF-1/7,
 - 500pF-2/-, 750pF-2/3.

And we sell "TV Fault Finding" 5/3 post paid. Write for our 32 page catalogue No. 11 Price 6d.

RADIO SERVICING COMPANY (Dept. K)
444, WANDSWORTH ROAD, LONDON, MACAULAY 4155. S.W.8.

SMALL ADVERTISEMENTS

Readers' small advertisements will be accepted at 2d. per word, minimum charge 2/-. Trade advertisements will be accepted at 6d. per word, minimum charge 6/-. If a Box number is required, an additional charge of 1/- will be made. Terms: Cash with order. All copy must be in hand by the 12th of the month for insertion in the following month's issue.

PRIVATE

MCR1 for sale, offers over £6.10.0d. Perfect condition, 4-plug-in coils. S. Pearson, 19 Banklands, Newburgh, Fiffe.

SX24 excellent condition £25. BPL Super Ranger 1000 o.p.v., brand new and unused £12. HomeLab Signal Generator, charts, terminating units, brand new, unused, 5s.

CAXTON'S MODERN RADIO AND TV, four volumes, mint condition £2. Donaldson, Hillview Terrace, Old Kilpatrick, Glasgow.

FOR SALE, MCR1 with coils and power pack. Good condition. £7.5.0d. Allerott, 50 Bovill Street, Nottingham.

R107 little used, with Handbook £8. Owner in Nigeria. Reply to Hensby, 65a Ely Road, Littleport, Cambs.

S640 Eddystone Receiver, sound condition £15. Manning, 34 Chandos Road, East Finchley, London, N.2.

R1155 Power/Output Unit, perfect, cost £4.10.0d. Offers over £3. L. Andrew, 15 Central Avenue, Church Stretton, Shropshire.

EDDYSTONE S640. Good condition, with small cabinet type speaker. £21 or offer. Box No. B202.

HAMMARLUND COMET PRO. Top Band coils. Xtal models, very good condition. £10 or offer. BC 376 VHF Oscillator with Xtal, 75 Mcs, output modulated £5. Absorption Wavemeter, 1.6 to 18 Mcs, Neon indicator, switched bands, 25". D. Outram, 1 Culross Buildings, Battlebridge Road, London, N.W.1.

PREMIER TELEVISOR, VCR97, Cabinet, Magnifier, Spare Tube, Spare EHT Transformer, Perfect order £20. Buyer collects. 66 Crescent Road, London, N.22. Tel: Boves Park 27506.

FOR SALE. Radiovision High Gain Preselector, immaculate condition, 2 stages of EF50, 9-90 metres, Self contained 200-250v AC power pack. Bargain £9.10.0d. Wanted urgently. Instruction Manual and alignment data for Canadian Marconi "52" set. Please help. F. W. Hardstone, 43, Strubbery Road, Streatham, London, S.W.16.

R1355 and RF25, with power pack, working for London Vision signal. Offers. Box B201.

FOR SALE, Eddystone S640 receiver, very good condition, little used, with 6" Speaker, S Meter and Instruction Manual £20. Delivered free London area. J. J. Watson, 20 Edencourt Road, Streatham, London, S.W.16.

TRADE

I.P.R.E. PUBLICATIONS, 5,500 Alignment Peaks for superhets 5/9. Sample copy *The Practical Radio Engineer* 2/-. Membership-examination particulars 1/-. Syllabus of TV and radio courses free and post free. Secretary I.P.R.E., 20 Fairfield Road, London, N.8.

FREE. Brochure giving details of Home Study Training in Radio, Television, and all branches of Electronics. Courses for the Home Enthusiast or for those aiming at the A.M.B.I.B.T.R., City and Guilds, Professional communications, R.T.E.B., and other Professional examinations. Train with the College operated by Britain's largest electronic organisation. Moderate fees. Write to: F.M.I. INSTITUTE, Postal Division, Dept. RC28, 143, Grosvenor Park Road, London, W.4. (Associated with H.M.V.).

(Continued on Page 56)

TRANSFORMERS—Manufactured to our specification, and fully guaranteed. Normal Primaries. 425 v.-0-425 v. 200 ma., 6.3 v. 6 a., 6.3 v. 5 a., 5 v. 3 a., 0-2-4-6.3 v. 3 a. ONLY 7/6. 425 v.-0-425 v. 200 ma., 6.3 v. 4 a., 6.3 v. 4 a., 5 v. 3 a. ONLY 50/-, 350 v.-0-350 v. 160 ma., 2.3 v. 6 a., 3 v. 3 a., 5 v. 3 a. ONLY 42/6. 250 v.-0-250 v. 100 ma., 6.3 v. 6 a., 5 v. 3 a. ONLY 32/6. The above are fully shrouded, upright mounting. Universal Mounting 350 v.-0-350 v. 80 ma., 0-4-6.3 v. 4 a., 0-4-5 v.-0-260 v. ONLY 18/6. Top shrouded, drop through, 260 v.-0-260 v. 70 ma., 6.3 v. 3 a., 5 v. 2 a. ONLY 16/6. The following are upright mounting. EHT for VCR97 Tube, 2,500 v. 5 ma., 2 v.-0-2 v. 1.1 a., 2 v.-0-2 v. 2 a. ONLY 37/6. EHT 5,500 v. 5 ma., 2 v. 1 a., 2 v. 1 a. ONLY 82/6. 7,000 v. 5 ma., 4 v. 1 a. ONLY 82/6.

PLEASE ADD 1/6 PER TRANSFORMER POSTAGE

TRANSFORMER, for use on trains, models, etc., giving outputs of 3 v., 4 v., 5 v., 6 v., 8 v., 9 v., 10 v., 15 v., 18 v., 20 v., 24 v., 30 v., at 2 amps., from normal mains input. ONLY 17/6 (postage 1/-).

TRANSFORMERS—Ex W.D. and Admiralty, built to more than 50 per cent. safety factor, with normal A.C. Mains Primaries. All Brand New and Unused. 300 v.-0-300 v. 200 ma., 5 v. 3 a., 6.3 v. 5 a., C.T., 20 v. 750 ma., 70 v. 100 ma. Weight 12 lb. ONLY 42/6 (postage, etc., 2/6). 330 v.-0-330 v. 100 ma., 4 v. 3 a. Weight 7 lb. ONLY 22/6 (postage 1/6). L.T. 5 v.-0-5 v. 5 a., 5 v.-0-5 v. 5 a., 5 v.-0-5 v. 5 a. By using combination of windings will give various voltages at high current. Weights 11 lb. ONLY 35/- (postage, etc., 2/6). L.T. 6.3 v.-7.7 v., 4.2 v.-2.5 v., 4 v. 1 a. ONLY 19/6 (postage 1/6). EHT 1,400 v. 2 ma., 520 v. 10 ma., 300 v. 10 ma., 2 v. 1.5 a. ONLY 21/- (postage, 1/6). Cash with order, please, and print name and address clearly. Amounts given for carriage refer to inland only.

U.E.I. CORPORATION

The Radio Corner
138 Gray's Inn Rd., London, W.C.1.
Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Stn.) and 5 mins. by bus from King's Cross.

NORMAN H. FIELD 68, HURST STREET, BIRMINGHAM, 5
Mail Order Department.
64-65, CHURCH LANE WOLVERHAMPTON.


SPECIAL OFFER.
PRE-AMPLIFIERS Ultra S.W. uses EF54 with Coax Input and Output sockets also plug and socket for Power Supply. Broad Band slug tuned for use on T.V. Frequencies or 10 Metres ... list below) (Valves to suit, available in our list below) 5/-

CHEAPER VALVES
At 12/6: 6SN7, 6K8, X61, 607g, KT63, KT66, ECC32, 5Y3/5Z4, All Brand New and Boxed. At 11/6: KT61, At 10/6: EP91, EL91. At 10/-: 354, 12C7, 1616, PEN46, 12SL7, 50YG/GT, 6F7, 807, ARP6, IT4, 154, IR5, 1S5. At 7/6: VT52, EL32, EB33, VR55, 7R7, 77, 6K7, 6I7, VR150, 6G6/GT, 1A5/GT, 7C7, VR119, 6Y7/G, 7C5, ARTP2, TP25, OZ4, 12A6, 12C7, At 7/-: 6B8, 6B8/G, 6K7G, 1G6/GT, C.M.4, VR53, EF9, EF88. At 6/6: 6AB7, 6D6, VT24, RK34, 2C34, AR8, HL23DD. At 5/6: 6S57, 6R7, 6R7/GT, 12C8, 12S67, 6C5/GT, 6I7, 1215, 6I7/G, 6SH7/G, VR91, EF50, 306, 6S7K, TT11, VT501. At 5/-: ARP12, VP23, 6F5, 12SK7, 2A3, VUI33, 2V3G, 1625, VT51, PEN20A, VR118, KT2. At 4/6: 6I5/G, 6I5/GT, 12SH7, 12H6, VUI120. At 3/6: RK672, ARP3, 9D2, 6H6. At 3/3: VR18, 2155G, 2X2, VU111, HL2, VR21, VR66, P61, VR55, SP61, VR65A, SP41, At 2/6: VR54, EB34, VR92, EA30, VR78, D1, 7193. All boxed, Tested and Guaranteed.

CHOKES shrouded 20H 80M/1a ... 8/6
CHOKES shrouded 10H 60M/1a ... 2/6
CHOKES L.T. Smoothing 5 Ohms ... 2/6
TRANSFORMERS MAINS input 230V A.C. Output 18V: 26V: 44V at 2 Amps. ... 12/-
TRANSFORMERS EHT 2,500V 5M/1a 4V 2 Amps 0.24V at 4 Amps, 210-250V 50 Cycles Completely Wax impregnated for Argus or Viewmaster. Guaranteed ... 42/6

CLYDESDALE

Bargains in Ex-Services Equipment

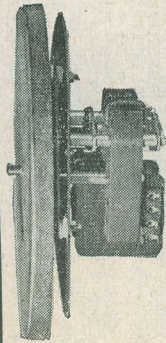

A.C. MAINS 200/250 volts GRAMPHONE MOTORS.
Fitted with 9-inch turntable and mounted on 8-inch metal plate for crystal pick-up. Mfg. special line.

ASK FOR No. B/H320 58/6d. EACH POST PAID
ROTARY TRANSFORMER
Type 44. Ref. 10KB/409

Input 18V 3.13A. Output 450V 0.05A. with extension spindle both ends. Length 8 1/2 in. x 3 1/2 in. x 3 1/2 in. finish grey.

27/6. Each Post Paid
Ask for No. B/H845
NEW LIST No. 8C Now Ready—Price 1/6d.
Price Credited on first purchase of 10/-, or over.

Order direct from:
Tel. SOUTH 2706/9
CLYDESDALE SUPPLY CO. LTD.
2 BRIDGE STREET, GLASGOW C.5.
Branches in Scotland, England and North Ireland.

Have Your Copies

Bound

VOLUMES OF RADIO CONSTRUCTOR AND SHORT WAVE NEWS FULLY BOUND IN IMITATION LEATHER, WITH GOLD LETTERING. 7s. 6d. POST FREE. PRICES FOR OTHER PUBLICATIONS ON APPLICATION.

IF NOT REQUIRED TO BE BOUND IN, REMOVE COVERS BEFORE SENDING.

JEROME ALCOCK
CHEADLE, STOKE-ON-TRENT

Small Advertisements—cont.

TRADE (continued from page 55)

PANL celebrates first anniversary. During past year many thousands of constructors have turned to PANL, the air drying black crackle. PANL is easy to apply, requires no special skill, costs 4/6d. 4oz. jar, inc. postage, from L. Miller, 8 Kenton Park Crescent, Kenton, Middlesex.

PIMBLE OFFERS—Electro Magnetic Counters 4/6. BC 454 Receivers with valves but less dynamotor, soiled only 3/6. Valves VR21 1/9, VR18 3/3, VT51 3/9, 6K7G 7/6, 6K8G 10/9, 6S7G 7/6, HL23 2/6, VP23 3/9, QP22B 3/9, Y63 9/9, 8D2 5/6, VR34 2/6, 6H6 2/6, 6J5 5/6, 20 mfd 50v. electr. 1/6, 50mfd 12v 1/6, 4mfd 350v 2/6, 8mfd 350v 3/6. Sel. Rect. 350v. 40ma 3/3, 0-1ma. Meters 12/6. All Post paid. Pimble, 12 Liverpool Road, Newcastle, Staffs.

METALWORK. All types cabinets, chassis, racks, etc., to your own specifications. Philipott's Metalworks, Ltd., (Dept. R.C.) Chapman Street, Loughborough.

"GLOBE-KING" (Regd) Miniature Single Valve Receiver gets real Dx-Amateur Radio enthusiasts should send for free copy of interesting literature and catalogue (enclose stamp for postage). Write to makers: Johnsons (Radio), 46, Friar Street, Worcester.

BOOKBINDING. Volumes of Radio Constructor and Short Wave News fully bound, imitation leather, gold lettering. 7s. 6d. post free. Prices for other publications on application. Jerome Alcock, CHEADLE, Stoke-on-Trent.

HOME CONSTRUCTORS. Radio, television, send for realistic components, valves, kits, speakers, etc. The Radio Equipment Company (RC Dept.), Casnor Road, Brixnani, Devon.

TV COILS, ALL TYPES.—Bell Sound Products Co., Marborough Yard, London, N.19. ARC 5078.

JOIN THE ISWL. Over twenty free services to members including QSL Bureau, Translation, Technical and Identification depts. Dx certificates, contests and activities for the SWL together with over seventy local Groups in this country. Monthly magazine 'MONITOR', twenty pages plus cover, duplicated, containing articles of general interest to the SWL and League member. 8/- per annum, post free. ISWL HQ, 123, Sturlia Road, Chatham, Kent.

* **PANL**—the air drying black crackle for the amateur, 5/6 per 4 pt. can, from L. Miller, 8, Kenton Park Crescent, Middx.

ANOTHER MILLER EXCLUSIVE. "Motl," the hammer finish, as used on commercial tape recorders, amplifier cases, etc. Grey, Green or Blue. For brush application, air drying. 4/6 inc., or SAE for details. Miller, 8, Kenton Park Crescent, Kenton, Middx.

VIEWMASTER, exact specified parts at list price by return of post, also Valves and CRT's stamp for list. James H. Martin and Co., Dept. RC, BCM/EDHWA, London, W.C.1.

BLUEPRINTS. High Gain 10 Metre Converter, with a de-luxe circuit comprising EF91 RF stage, ECC91 double triode mixer and oscillator, EF92 IF amplifier, with stabilised voltage supply via a 7475. 1s. 8d. post free with full instructions.

REPRINT. Converting the TR1196 Receiver. Full details on converting this unit, which may be purchased quite cheaply, into a very sensitive all-wave receiver. 6d. post free. All the above from A.S.W.P., 57, Maida Vale, London, W.9.

CAR RADIOS, Transmitters, spares. Different types for disposal. Stamp for details. Brown, 40 Stanshaw Road, Forrismouth, Hants.

THE MODERN BOOK CO.

TV Fault Finding compiled by 'The Radio Constructor'. 5s. 0d. Postage 4d.

Inexpensive Television for the Home Constructor. 2s. 6d.. Postage 2d.

The De Luxe Home Built Televisor and Radiogram by W. I. Flack. 6s. 6d. Postage 4d.

Television Servicing Manual by E. Bradley. 4s. 6d. Postage 4d.

Thermonic Valve Circuits by E. Williams. 21s. 0d. Postage 9d.

Foundations of Wireless by M. G. Scroggie. 12s. 6d. Postage 9d.

The Radio Amateur's Handbook by the A.R.R.L. 30s. 0d. Postage 1s. 0d.

Amplifiers by G. A. Briggs and H. Garner. 15s. 6d. Postage 6d.

Sound Recording and Reproduction by J. W. Godfrey and S. W. Amos. 30s. 0d. Postage 6d.

The Williamson Amplifier. 3s. 6d. Postage 3d.

Magnetic Recording by M. L. Quertainne. 4s. 6d. Postage 3d.

Ostram Valve Manual. Part One. 5s. 0d. Postage 6d.

Brimar Radio Valve and Teletube Manual. 5s. 0d. Postage 6d.

Radio Valve Data compiled by 'Wireless World'. 3s. 6d. Postage 3d.

We have the finest selection of British and American radio books in the Country. Complete list on application.

19-23 PRAED STREET (DEPT.), LONDON, W.2

PADDINGTON 4185.



SCOTTISH INSURANCE CORPORATION LTD.

62-63 CHEAPSIDE LONDON, E.C.2.

TELEVISION SETS AND SHORT WAVE TRANSMITTERS

Television Sets and Short Wave Transmitters/Receivers are expensive to acquire and you no doubt highly prize your installation. Apart from the value of your Set, you might be held responsible should injury be caused by a fault in the Set, or injury or damage by your Aerial collapsing. A "Scottish" special policy for Television Sets and Short Wave Transmitters/Receivers provides the following cover:—

(a) Loss or damage to installation (including in the case of Television Sets the Cathode Ray Tube) by Fire, Explosion, Lightning, Theft or Accidental External Means at any private dwelling house.

(b) (i) Legal Liability for bodily injury to Third Parties or damage to their property arising out of the breakage or collapse of the Aerial Fittings or Mast, or through any defect in the Set. Indemnity £10,000 any one accident.

(ii) Damage to your property or that of your landlord arising out of the breakage or collapse of the Aerial Fittings or Mast, but not exceeding £500.

The cost of Cover (a) is 5/- a year for Sets worth £50 or less, and for Sets valued at more than £50 the cost is in proportion. Cover (b) (i) and (ii) costs only 2/6d. a year if taken with Cover (a), or 5/- if taken alone.

Why not BE PRUDENT AND INSURE your installation—it is well worth while AT THE VERY LOW COST INVOLVED. If you will complete and return this form to the Corporation's Office at the above address, a proposal will be submitted for completion.

NAME (Block Letters)
(If Lady, state Mrs. or Miss)
ADDRESS (Block Letters) /JB