

RADIO



BOOKS

Tape and Wire Recording. A selection of articles reprinted from the pages of *The Radio Constructor*, covering both the theory and practical applications. A really useful book on this latest development of the hobby. 2/8

Receivers, Preselectors and Converters. Practical articles, again reprinted from past issues of *The Radio Constructor*, which will prove of interest to many radio enthusiasts. 2/8

TV Fault Finding. Profusely illustrated with photographs taken from a television screen depicting the faults under discussion, and containing a wealth of technical information, with circuits, enabling those faults to be eradicated. 5/3

Inexpensive Television. Build yourself a television from surplus. Latest edition includes all the data necessary for any area. 2/8

World Radio Handbook (1955 edition). The S.W. broadcast enthusiasts' handbook. You are missing something from your hobby if you have not a copy of this excellent publication. 9/6

Report Pads. If you need that QSL card, send a comprehensive report. A convenient and accurate form for reporting. 3/9

Radio Amateur Operator's Handbook. An indispensable aid to the amateur transmitter and listener, containing all details of information which are constantly required. Prefix Lists, Zone Boundaries, Call Areas, Codes, and Mileage Tables, together with Maps and much other useful operating data. Revised edition now in preparation.

Inexpensive Car Radio. In which two versions, one constructed from surplus and one from new components, are described. 1/8

Radio Control for Model Ships, Boats and Aircraft, by F. C. JUDD, G2BCX. A comprehensive work on this fascinating subject. Standard edition, 8/9. Cloth bound edition 11/9

All above prices include postage and packing

All available from your local bookseller, or from:

DATA PUBLICATIONS LTD

57 MAIDA VALE LONDON W9

Telegrams Databux London

Telephone CUNningham 6518

Printed in Great Britain for the Proprietors and Publishers Data Publications Ltd., 57 Maida Vale, London, W9, by A. Quick & Co. Ltd., Oxford House, Clacton-on-Sea, Essex. Is obtainable abroad through the following: Collets Subscription Service, Continental Publishers & Distributors, Ltd., William Dawson & Sons Ltd. Australia and New Zealand: Gordon & Gotch Ltd. South Africa: Central News Agency. U.S.A.: Gilfer Associates. Holland: "Radio Electronica." Scandinavia: Intrapress. Registered for transmission by Magazine Post to Canada (including Newfoundland).




The

RADIO CONSTRUCTOR

for the Radio and Television Enthusiast

Volume 8
Number 8
MARCH
1955

ELECTRONIC RESISTANCE

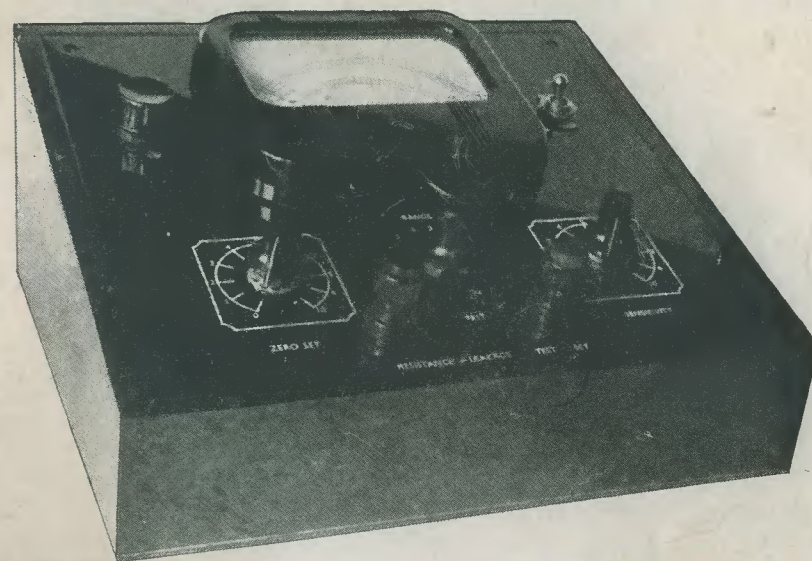

AND LEAKAGE TEST SET

ALSO IN THIS ISSUE

THE PARAGON TAPE RECORDER Part 3

MODERN LINE TIMEBASE CIRCUITS


IMPROVING SIMPLE "UNIVERSAL" RECEIVERS

FURTHER NOTES ON THE 182A 'SCOPE' · SYNTHETIC BASS CIRCUIT
FOR DOMESTIC AMPLIFIERS · NOTES ON RADIO CONTROL, Part 5
VALVE VOLTMETERS · The G3XT Chassis · Query Corner
Simple Probe Construction, etc. etc.

16

MAXI-Q
Regd.

PDT.1

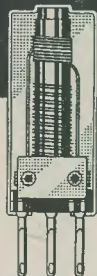

General Catalogue covering technical information on full range of components, 1/- post free. Obtainable from all reputable stockists or direct from works.

BE SURE OF SUCCESS IN RECEIVING F.M. PROGRAMMES BY BUILDING THE "MAXI-Q" F.M. FEEDER UNIT


Full constructional details, Point to Point wiring diagram and alignment instructions are given in our Technical Bulletin DT88, price 1/6. The guaranteed components described below have been acclaimed by thousands as the finest obtainable.

F.M. SCALE AND POINTER MECHANISM WILL SHORTLY BE AVAILABLE at an appr. price of 9/-

RATIO DISCRIMINATOR TRANSFORMER 10.7 Mc/s. Ref. RDT1. A 10.7 Mc/s. transformer for use in ratio discriminator type circuits. Can size 1 1/2 in. square x 2 1/2 in. high. Secondary winding of bifilar construction. Iron dust core tuning, polystyrene former and silver mica condensers. Price 12/6 each.

PHASE DISCRIMINATOR TRANSFORMER 10.7 Mc/s. Ref. PDT1. A miniature 10.7 Mc/s. transformer for use in frequency modulation detector circuits where the limiter/Foster-Seeley type of circuit is employed. Designed for carrier deviation of ± 75 kc/s. Qk = 1.5 Wound on black Bakelite former, complete with iron dust slugs and two 6 B.A. threaded fixing holes on .532 in. centres. Screening can 1 1/2 in. x 1 3/16 in. square. Price 9/- each.

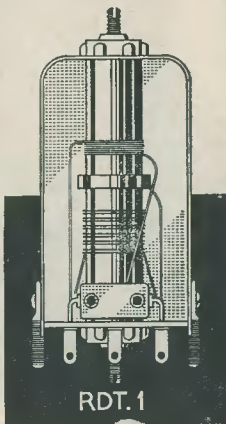I.F. TRANSFORMER IFT.11/10.7 A miniature I.F. Transformer of nominal frequency 10.7 Mc/s. The transformer is primarily intended for the I.F. stages of frequency modulation receivers and converters. The Q of each winding is 90 and the coupling critical. Construction and dimensions as PDT.1. Price 6/- each.



DENCO (CLACTON) LTD • 357/9 OLD ROAD • CLACTON-ON-SEA

STOP PRESS: "Osram" "912" and "Mullard" "5-10" Amplifier Chassis and Bronze finished Front Panel — Price 21/- each. The "P.W. Fury Four" uses the Maxi-Q Yellow (3/11) and Green Chassis Mounting Coils (4/9) (please state frequency range when ordering). Also available are the "Fury Four" Chassis and Paxolin Front Panel, 19/6. Long and Medium Wave T.R.F. Coils, wound on Polystyrene Formers, 9/- per pair.

NEW!

EXPERIMENTAL KITS in Radio, T.V. etc.

LEARN THE PRACTICAL WAY

Specially prepared sets of radio parts (which you receive upon enrolment) with which we teach you, in your own home, the working of fundamental electronic circuits and bring you easily to the point when you can construct and service radio sets. Whether you are a student for an examination; starting a new hobby; intent upon a career in industry; or running your own business — these Practical Courses are intended for YOU — and may be yours at Very Moderate Cost.

EASY TERMS FROM 15/- A MONTH

POST THIS COUPON TODAY

To E.M.I. INSTITUTES, Dept. 179X,
Grove Park Road, London, W.4.

SUBJECT(S) _____

NAME _____

ADDRESS _____



COURSES WITH PRACTICAL EQUIPMENT INCLUDE:-
Radio (Elementary and Advanced), Television, Mechanics, Electricity, Chemistry, Photography, Carpentry. Also Draughtsmanship, Commercial Art, Amateur S.W. Radio, Languages, Etc.

E.M.I. INSTITUTES

The only Postal College which is part of a world-wide Industrial Organisation

IC96

LINE OUTPUT TRANSFORMER TYPE L.O.352

Type L.O.352 is the type number of an entirely new Allen line output auto-transformer now available to manufacturers and the home-Constructor. It functions in conjunction with PL81 PY81 valves, and provides an E.H.T. voltage whose regulation is better than 5MΩ. The associated components are the D.C.605/C scanning yoke, G.L.16 linearity control, and G.L.18 width control.

Line Output Transformer type L.O.352, 42/6.

Scanning Yoke type D.C.605/C 39/6.

Width Control type G.L.18, 7/6.

Linearity Control type G.L.16, 7/6.

Our standard, well proven components are also available:

Line Output Transformer type L.C.308, 40/-.

Scanning Yoke type D.C.300/C, 39/6.

All the above are available direct from

ALLEN COMPONENTS LIMITED

Crown Works 197 Lower Richmond Road Richmond Surrey
Telephone PROspect 9013

Send 9d. and S.A.E. for recommended Wide-Angle Circuit Diagrams

Instrument cases in steel, complete with light alloy front panel. Colours Black (Red and Green 10 per cent extra). Back punched for ventilation.

Type "9," 8" x 9" x 8" is 18/6 with panel in light alloy.

Type "12," 10 1/2" x 12" x 10 1/2" is now 25/- with panel in light alloy.

Type "9-12," 9" x 12" x 9" is now 21/- with panel in light alloy.

Chassis at the following prices. These are in aluminium of 18G.

6 x 4 x 2 1/2	5/6	6 x 5 x 2 1/2	7/6
8 x 6 x 2 1/2	8/-	10 x 6 x 2 1/2	8/6
10 x 7 x 2 1/2	9/-	10 x 8 x 2 1/2	9/6
12 x 8 x 2 1/2	10/6	10 x 9 x 2 1/2	11/-
14 x 8 x 2 1/2	13/9	14 x 9 x 2 1/2	14/-
16 x 8 x 2 1/2	14/9	16 x 9 x 2 1/2	15/6

Suppliers of technical publications. A full range of components, by well-known manufacturers, are stocked, Mullard, Brimar, Cossor, T.C.C., Dubilier, Erie, R.E.P., Wearite, Elstone, Morganite, etc. High stability 1, 2 and 5 per cent resistors available from stock or to order.

INTRODUCING RADIO RECEIVER Price Post
SERVICING by E. M. Squire 10/6 6d.

RADIO RECEIVER CIRCUITS

HANDBOOK by E. M. Squire 6/- 6d.

RADIO RECEIVER SERVICING AND

MAINTENANCE by E. J. G. Lewis 12/6 6d.

RADIO SERVICE TEST GEAR

by W. H. Cazaly 6/- 6d.

SHORT WAVE RADIO

by J. H. Rayner 10/- 6d.

ELECTRONIC MEASURING INSTRUMENTS

by E. H. W. Banner 45/- 1/1

TELEVISION SIMPLY EXPLAINED

by R. W. Hallows 10/6 5d.

RADIO LABORATORY HANDBOOK

by M. G. Scroggie 25/- 6d.

FOUNDATIONS OF WIRELESS

by M. G. Scroggie 12/6 6d.

RADIO DESIGNERS HANDBOOK

F. Langford-Smith 42/- 1/6

Any book on Radio T.V. or Electronics

can be supplied either from stock or to

order at short notice.

KENDALL AND MOUSLEY LIMITED

Electronic Engineers and Laboratory Equipment Manufacturers

18 MELVILLE ROAD

BIRMINGHAM 16

Smith's
of
EDGWARE ROAD

Component Specialists since
Broadcasting Started, invite all
those interested in—

ELECTRONIC COMPONENTS
(both Regular and Surplus) to
send for their latest Price-lists.

H. L. SMITH & CO. LTD

287/289 EDGWARE ROAD · LONDON · W2

Hours 9 till 6 (Thurs. 1 o'clock). Tel.: Paddington 5391
Near Edgware Road Stations, Metropolitan and Bakerloo

OSMOR radio
products
limited

418 BRIGHTON RD. SOUTH CROYDON SURREY
Dept. R.C.21 Telephone CROYdon 5148/9



COILPACKS. A full range available for Superhet and T.R.F. Mains or Battery. Size only 1 1/2" x 3 1/4" x 2 1/4". Ideal for the reliable construction of new sets, also for conversion of the 21 RECEIVER, TR 1196, TYPE 18, WARTIME UTILITY and others.

SEPARATE COILS 4/- each
A full range available for all popular wavebands and purposes.
★Only 1in. high. ★Packed in damp-proof containers. ★Variable iron-dust cores. ★Fitted tags for easy connection. ★Low loss Polystyrene formers.



I.F.s Standard 465 k/c. Permeability-tuned with flying leads. Size 1 3/8" x 1 3/8" x 3 1/4". For use with OSMOR coilpacks and others, 14/6 pair. **MIDGET I.F.s 465 K/c.** 3/4" x 3/4" x 2 3/8", 21/- pair. **REALIGNED 1/6 extra.**

FREE Send 5d. (stamps) for fully descriptive literature, including The really efficient 5 valve Superhet Circuit and practical Drawings. 6-valve ditto, 3-valve (plus rectifier) T.R.F. circuit, Battery portable superhet circuit, Chassis Cutter, Coil & Coilpack leaflets and full radio & component lists and interesting Miniature circuits etc.

Our Technical Dept. will be pleased to answer (by letter only) any enquiry relating to circuits in which Osmor Coils or Coil Packs are used or are intended to be used.

ARTHURS HAVE IT!

LONDON'S OLDEST RADIO DEALERS
LARGE VALVE STOCKS

AVOMETERS IN STOCK
Avo Test Meters and Signal Generators
and Taylor Meters
Leak Point One Amplifiers and Tuning Units

Chapman Tuning Units
Crystal and Moving Coil Mics.
Decca Replacement Heads and Pickups
Goodman's Axiom 150 Speakers
Partridge Output Transformers for Williamson Amplifier
All Components for the Radio Constructor's 16" Televisor

Weare & Wright Tape Deck, £35

LATEST VALVE MANUALS

Mullard, Osram & Brimar No. 4, 5/- each

Mazda 2/- each Postage 6d. each

TELEVISION SETS, WIRE AND TAPE RECORDERS ALWAYS IN STOCK

Goods offered subject to price alterations and being unsold.

Arthurs first Est. 1919

Proprietors: ARTHUR GRAY LTD.

OUR ONLY ADDRESS **Gray House**
150-52 Charing Cross Road
London WC2

TEmple Bar 5833/4 and 4765 WRITE FOR LISTS

Frequency Modulation Tuner

described in the July and Sept. 1954 issues.

JACKSON BROS. dial and condenser **£1 5 3**

Completely drilled chassis **8 0**

All coils with S.M. Condensers and cans **£1 2 6**

Complete Set of Parts, (less valves) including pair of matched Germanium crystals and small items such as nuts and screws **£5 0 0**

Complete Tuner, assembled and aligned **£10 0 0**
(P.T. extra)

JASON MOTOR COMPANY

328 CRICKLEWOOD LANE
LONDON NW2

DATA BOOK SERIES, NO. 9



Radio Control

FOR MODEL SHIPS, BOATS AND AIRCRAFT

BY F. C. JUDD, G2BCX

To operate a model ship or aircraft is a most interesting hobby. But how much more fascinating it would be if one could emulate the skipper or pilot and remain in control after the model has been set off on its course. This, thanks to radio control, can now be done, and enthusiasm for it is steadily mounting. With the publication of this book, we really believe that we have produced what will become a recognised handbook in this field.

Standard Edition, art board cover . . . 8s. 6d.

Cloth bound, with gold lettering . . . 11s. 6d.

Postage 3d.

A really comprehensive work on this fascinating subject

144 pages


135 diagrams and illustrations

TRADE ENQUIRIES INVITED

DATA PUBLICATIONS LTD

57 MAIDA VALE LONDON W9

Telephone CUNingham 6518

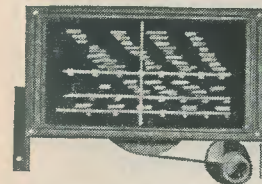

The
S.L.8
Spin Wheel
Drive

Complete with 3-wave band glass scale 9" x 4 1/2" 27/6

The S.L.8 Spin Wheel Drive gets easy control through a ratio 24:1. Fitted with constant velocity coupling, it eliminates strain on the Condenser, providing mechanical and electrical isolation from vibration and noise.

S.L.5, similar, but fitted with reverse vernier drive, gives ratios of 18:1 search and 50:1 reverse vernier. 26/6.

Please write for our list of Condensers and Drives

JACKSON BROS.
(London) Ltd.


KINGSWAY · WADDON SURREY

Telephone CROYDON 2754-5

Telegrams WOLFILCO, SOUPHONE, LONDON

WORLD-WIDE DX IS CERTAIN

with the
Labgear 150 Watt TRANSMITTER

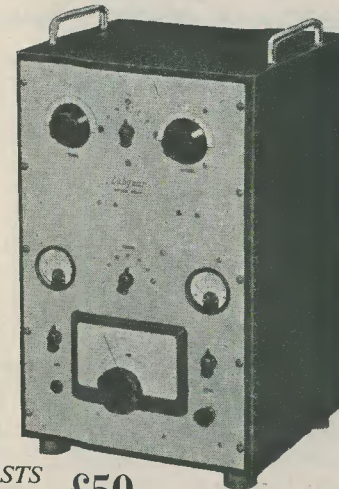

COSTS UNDER £50 Send S.A.L. for leaflet RC5035

Labgear (Cambridge) Ltd
WILLOW PLACE · CAMBRIDGE · Telephone 2494-5



**POST TODAY FOR OUR BROCHURE ON
THE LATEST METHODS OF HOME
TRAINING FOR OVER 150 CAREERS
& HOBBIES**

PRIVATE & INDIVIDUAL TUITION IN YOUR OWN HOME

City and Guilds Grouped Certificates in Telecommunications: A.M.Brit. I.R.E. Examinations, Radio Amateur's Licence, Radio and Television Servicing Certificates, General Radio and Television Courses, Radar, Sound Recording, etc. Also Courses in all other branches of Engineering and Commerce.

The advantages of E.M.I. training

★ The teaching methods are planned to meet modern industrial requirements. ★ A tutor is personally allotted by name to ensure private and individual tuition. ★ Free advice covering all aspects of training is given to students before and after enrolling with us.

**NEW LEARN THE PRACTICAL WAY
COURSES WITH EQUIPMENT**

With many of our courses we supply actual equipment which is sent upon enrolment and remains your property. Courses include: Radio, Television, Electronics, Draughtsmanship, Carpentry, Photography, and Commercial Art, etc.

**Courses
from 15/-
per month**

POST THIS COUPON TODAY

Please send without obligation your FREE book.
E.M.I. INSTITUTES, Dept. 179K, Mar.
Grove Park Road, London, W.4.

NAME _____
ADDRESS _____
SUBJECT(S) _____ IC.38

EMI INSTITUTES

The only Postal College which is
part of a world-wide Industrial Organisation.

LANES (RADIO) LTD The Amateur's ... Paradise ...

11 GARDNER STREET · BRIGHTON · Telephone BRIGHTON 20773

ALL LEADING MAKES OF STANDARD COMPONENTS FROM STOCK ★ LET US QUOTE INCLUSIVE PRICE FOR YOUR FULL REQUIREMENTS

FREE To introduce our service to *Radio Constructor* readers a free copy of Denco's FM Feeder Unit booklet will be given with all orders of £1 or over.

ELECTROLYTIC CONDENSERS

16mfd 450V	3/8
8mfd 450V	2/-
32 x 32mfd 350V	4/6
0.001 mica	4d.

**COMPLETE RANGE OF RESISTORS
from 10 ohm to 10 meg**

¼, ½, 1W, also 3.5 10.15W

**CRYSTAL DIODES 1/6 each
FILAMENT TRANSFORMERS
230V 6.3 1.5A 5/- each**

**LANE
OSCILLATOR
UNITS**

DENCO DETAILED PRICE LIST AND AERIAL DATA

TERMS.—Cash with order or C.O.D. (over £1). Please add postage and packing on orders below £1. Over £1 POST FREE

For FM Units 1/6
Drilled Chassis 7/6
Set of Fixed Condensers 31/-
Set of Resistors 10/6

★ **LANE
Mk. 6
TAPE
TABLES
£18.10.0**

SCREWDRIVER MAINS TESTER 6/9 ea. RODING COIL PACKS 3-WAVE BAND L.M.S. £2.9.9

The **Radio Constructor**

incorporating THE RADIO AMATEUR



CONTENTS FOR MARCH

- 456 Suggested Circuits: A Synthetic Bass Circuit for Domestic Amplifiers, *by G. A. French*
- 459 In Your Workshop, *by J.R.D.*
- 463 Modern Line Timebase Circuits, *by S. Welburn*
- 469 Notes on Radio Control, Part 5, Two Simple Transmitting Units, *by Quench Coil*
- 475 Book Reviews
- 476 The "Paragon" Tape Recorder: Pt. 3, *by J. W. Walker*
- 480 Can Anyone Help?
- 481 An Electronic Resistance and Leakage Test Set, *by James S. Kendall, M.I.P.R.E.*
- 484 Club News
- 485 The G3XT Chassis, *by G3XT*
- 488 Query Corner
- 491 Let's Get Started: Pt. 21, Valve Voltmeters, *by A. P. Blackburn*
- 496 Radio Miscellany, *by Centre Tap*
- 498 Simple Probe Construction, *by W. R. Burrows*
- 499 Improving Simple "Universal" Receivers, *by F. G. Rayer*
- 503 Notes on the Modification of the 182A Unit to an Oscilloscope, *by A. P. Blackburn*
- 504 Trade News

VOL. 8 NO. 8

ANNUAL SUBSCRIPTION 18/-

MARCH 1955

*Editorial and
Advertising Offices*

57 MAIDA VALE LONDON W9

Telephone
CUNNINGHAM 6518

Telegrams
DATABUX, LONDON

Editor
C. W. C. OVERLAND, G2ATV

Advertising Manager
F. A. BALDWIN, A M I P R E

THE CONTENTS of this magazine are strictly copyright and may not be reproduced without obtaining prior permission from the Editor. Opinions expressed by contributors are not necessarily those of the Editor or proprietors


NOTICES

THE EDITOR invites original contributions on construction of radio subjects. All material used will be paid for. Articles should preferably be typewritten, and photographs should be clear and sharp. Diagrams need not be large or perfectly drawn, as our draughtsmen will redraw in most cases, but all relevant information should be included.

All MSS must be accompanied by a stamped addressed envelope for reply or return. Each item must bear the sender's name and address.

TRADE NEWS. Manufacturers, publishers, etc., are invited to submit samples or information of new products for review in this section.

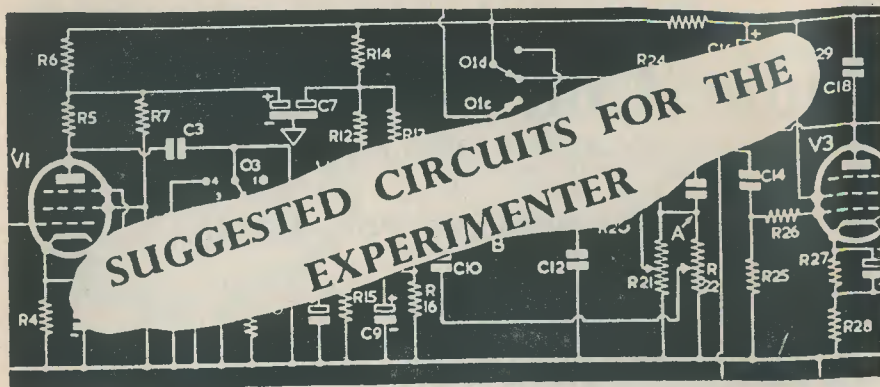ALL CORRESPONDENCE should be addressed to THE RADIO CONSTRUCTOR, 57 Maida Vale, London, W.9 Telephone CUN. 6518



The circuits presented in this series have been designed by G. A. FRENCH, specially for the enthusiast who needs only the circuit and essential relevant data

No. 52. A "SYNTHETIC BASS" CIRCUIT FOR DOMESTIC AMPLIFIERS

ONE OF THE GREATEST PROBLEMS INCURRED when reproducing sound in the home is given by the difficulty of preventing attenuation of bass frequencies due to insufficiently dimensioned loudspeaker enclosures. To obtain a note of 50 c/s without noticeable losses it is necessary to mount the reproducing loudspeaker on a baffle which is at least ten feet square. A baffle of this size is, of course, far too bulky to be introduced into a conventional living room, and alternative solutions have to be sought.

Of these, the best choice is provided by fitting the loudspeaker into a properly designed enclosure which is intended expressly for high fidelity reproduction. This solution suffers only on the question of initial cost.

A more frequently encountered answer to the problem of reproducing bass at full level is given by the introduction of resonances (in the loudspeaker and/or its cabinet) which centre around the lower audio frequencies. These resonances then tend to boost, usually with considerable coloration, the frequencies which are lost by reason of the insufficient baffle area.

This month's Suggested Circuit takes advantage of a different idea altogether, and demonstrates a method of obtaining apparently enhanced bass reproduction (usually described as "Synthetic Bass") even when the loudspeaker is fitted to a baffle of quite small dimensions. Whilst the methods employed may not appeal to the high-fidelity enthusiast, they definitely represent an interesting field for experiment and, given the

right conditions, are capable of quite impressive results. A particularly intriguing application is given by the introduction of a synthetic bass circuit into the amplifying chain of an electronic musical instrument. Such a circuit could effectively increase the tonal range of an instrument of this type without incurring condemnation on the grounds of deliberate misrepresentation of an original sound. This is, of course, due to the fact that the primary purpose of an electronic instrument is that of the creation of sound, and not that of reproduction only.

There is not a great deal of information concerning synthetic bass in "the literature," but readers who are interested may find a brief description of the principles involved, together with a commercial application, in the *Radio Designer's Handbook*¹. Also, a full-length article describing a practicable circuit has been published in *Wireless World*².

The Principles

To understand the principles employed in a synthetic bass arrangement it is first of all necessary to appreciate a particular idiosyncrasy of the human ear.

Should one hear a musical note, consisting of a fundamental tone together with its family of harmonics, one is able immediately to recognise and classify the fundamental. However if, by some agency, the fundamental is removed, leaving only the harmonics, the ear is apt to replace the fundamental of its own accord; with the result that the note retains its original character. Indeed, so

developed is this property of the ear that it is very difficult to ascertain, merely by listening, whether the fundamental of a particular note has been removed or is still in existence!


This peculiarity of the human ear has been well known in musical circles for many years. In particular, especial advantage of the fact has been taken by the manufacturers of pipe organs. If a proposed organ pipe, which is intended to resonate at a very low frequency, is considered to be too long to fit into a particular building, or too expensive, it can be replaced by an "equivalent"; the latter consisting of several much shorter pipes designed to give the requisite harmonics in the correct proportion. So far as the subjective impression of the ear is concerned, the effect given by the equivalent set of pipes is virtually the same as that which would be provided by the single long pipe resonating at the fundamental.

within the range of the loudspeaker, are next reproduced. The ear, itself, supplies the missing fundamentals; and the impression of full reproduction of the bass frequencies is then provided.

The Circuit

The circuit in this issue illustrates a synthetic bass arrangement which could be fitted into an amplifier which is already in existence. The circuit provides no amplification (apart from that of bass fundamentals and harmonics), and should not in normal circumstances introduce any noticeable reduction in gain. For greatest advantage, the circuit should be introduced between the penultimate stage of the amplifier and the output valve grid (providing, of course, that a negative feedback loop is not in existence over these two stages).

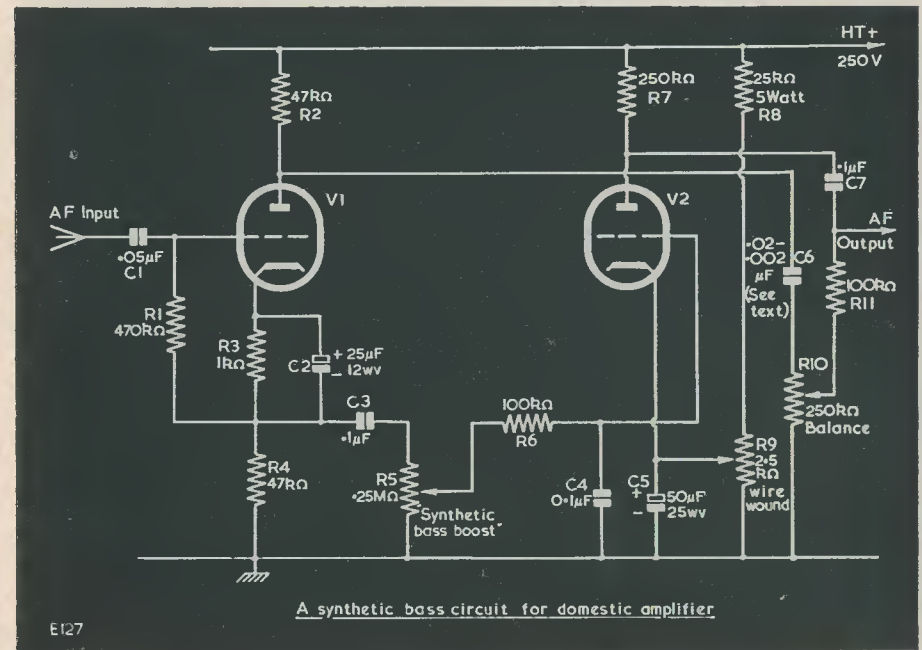The functioning of the circuit is quite simple. The input AF voltage is applied to



Synthetic bass, as applied to electronic amplifiers, embodies the same principles. It is assumed that the reproducing loudspeaker and its enclosure are incapable of fully reproducing the lower bass frequencies. These frequencies are, therefore, deliberately distorted in order to add harmonics to the original fundamentals. The harmonics, being

the grid of V1, which functions as a phase-splitter. The AF voltage appearing on the anode of this valve is next fed, via C6, to the "Balance" control R10. The AF appearing on the slider of this control is then passed to the subsequent grid. As will be appreciated, the amplification offered by this process is nil and, apart from the fact that some attenua-

tion of bass frequencies may take place due to the value of C6 (to be discussed later), no distortion of any sort is introduced.

Built up across the cathode load, R4, of V1 is an AF voltage similar in amplitude and phase to that applied to its grid. This voltage is applied, via C3, to the "Boost" control R5. The AF voltage tapped off by this control is then applied to the low-pass filter R6, C4. The values of R6 and C4 are such that only frequencies below about 100 c/s effectively reach the grid of V2. By reason of the bias voltage tapped off by R9 (combined with the effect of the rather high value chosen for R7), V2 is made to distort the voltages which are fed to its grid. Its output, rich in harmonics, is then passed to the subsequent grid via C7.

It will be noted that the outputs of V1 and V2 are in phase, and that no feedback can occur.

Setting Up

Setting up the circuit initially should not present too many problems, although an imaginative approach is essential if the effects given by altering different circuit values are to be judged correctly.

It would most probably be advisable to start off by choosing a value around $0.02\mu\text{F}$ for C6. A source of programme should next be fed to the amplifier, setting the "Boost" control to minimum and the "Balance" control to maximum. The "Boost" control should then be advanced, experimentally adjusting the "Bias" control at the same time, until the requisite amount of distortion, and apparent bass boost, is obtained. The greatest amount of distortion will be given when R9 is set nearly to cut-off point, although intermediate voltages may provide more pleasing results. R9 should not be taken beyond the cut-off point or V2 will not function on low amplitudes.

(An alternative method of obtaining bass distortion would consist of removing R8, R9 and C5 from the circuit altogether, and con-

necting the cathode of V2 direct to chassis. Final adjustments could then be made by varying the value of R7. This process would not provide as high a degree of distortion as that just described, however.)

Should it be found that the amount of apparent bass boost is too small to be effective, the "Balance" control should be retarded. This will reduce the level of the undistorted AF, increasing thereby the effect of the boosted bass harmonics. It is probable that in most cases this course would not be required however, whereupon, after the experimental stage has been completed, it would be possible to replace R10 by a fixed resistor. Also, in such circumstances, R11 could be removed, and C7 connected directly to the top of R10.

Although the primary function of V2 is to provide bass harmonics it will also, of course, amplify the fundamentals as well. If there is evidence of overloading of the output stage by these fundamentals when they are combined with those from the anode of V1, the value of C6 should be reduced experimentally until the overloading is cleared.

The Speaker

The success of the circuit will depend mainly upon the loudspeaker employed. If this has a high bass resonance, say above 100 c/s, the results given may not be as pleasing as they could be. The best speaker to employ is one with a low bass resonance, and having a fairly large-diameter cone with a soft and compliant suspension.

Valves

The choice of valves is not very critical. Either valve may be a low- μ triode (such as the 6J5); or both valves may be combined in a single 6SN7 or 12AU7.

References

- 1 "Synthetic Bass". F. Langford-Smith; *Radio Designers Handbook*, 4th edition; pp 616, 676.
- 2 "Bass Without Big Baffles". K. A. Exley; *Wireless World*; April 1951

WOLF SAVINGS SCHEME FOR HANDYMEN

Wolf Accredited Dealers throughout the country are now operating an Easy Stage Savings Scheme for the benefit of prospective purchasers of Wolf Cub equipment. The scheme, which already has achieved high popularity, consists of a special savings card

issued to each customer and upon which is entered the amount of money paid in. As equipment is purchased from the funds accumulated the amount withdrawn and balance outstanding can be entered up in columns provided on the card.

IN YOUR WORKSHOP



In which J. R. D. discusses Problems and Points of Interest based on Letters from Readers and his own experience

IT ALL STARTED OFF IN THE SEPTEMBER issue! In this copy of *The Radio Constructor* I referred to the circuit shown in Fig. 1, describing it as a "Mystery Circuit," which was thought, in the early days of radio, to give push-pull working merely by adding another output valve. As I said at the time, however, this assumption is quite untrue—the circuit is *not* push-pull.

Controversy


No sooner had the September issue been printed than I received several letters from readers telling me how wrong I was, and that the circuit was a long-tailed pair which most definitely did give push-pull results. One reader enclosed a "proof" of this (which I published in December); but, unfortunately, this jumped from amps to mA half-way through the working! As a result of this, even more letters are now rolling in.

I wish I could quote from all of them but, obviously, space would not allow this. One London engineer raises an interesting point.

"The reason," he writes, "why the 'Mystery Circuit' does not produce a true push-pull output is due to the fact that a sufficiently high value resistor in the cathode circuit cannot be used. If it were, and the grid voltages made suitable, considerable power would have to be wasted in the resistor.

"This may be overcome by using a choke in the cathode circuit, as shown in the diagram (Fig. 2). The resistance of this choke must, of course, be less than the required bias resistance and extra resistance added to make up the value. The second grid may be earthed or used to mix in another signal."

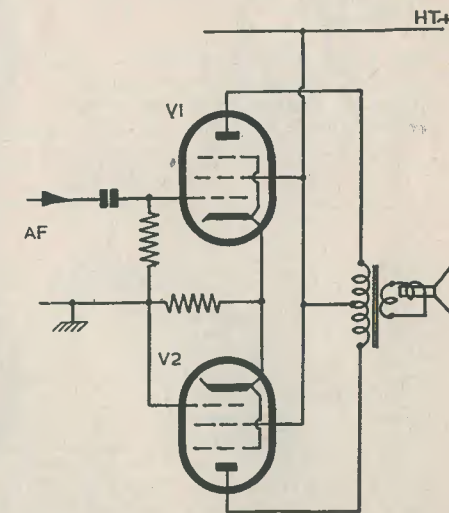The only snag with this idea, of course, is that the choke in the common cathode circuit would have to be a pretty hefty component if



E62

Fig. 1. The supposedly "push-pull" circuit which was printed in the September, 1954, issue of *The Radio Constructor*, and which has been the subject of a large number of letters from readers.

a balanced bass response is to be obtained. Assuming, for instance, that two 6V6's were

employed, the resultant steady DC current through the choke would be at least some 70 mA at normal HT voltages, and a small component would lose quite a lot of its effective inductance if it continually had to pass

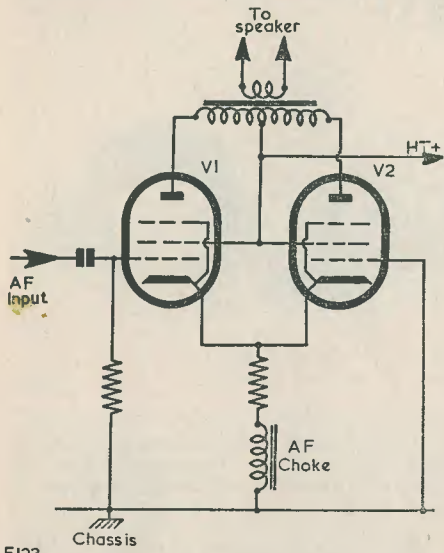


Fig. 2. A possible alternative to the circuit of Fig. 1. In this arrangement a high AF impedance in the common cathode circuit is obtained by means of a choke.

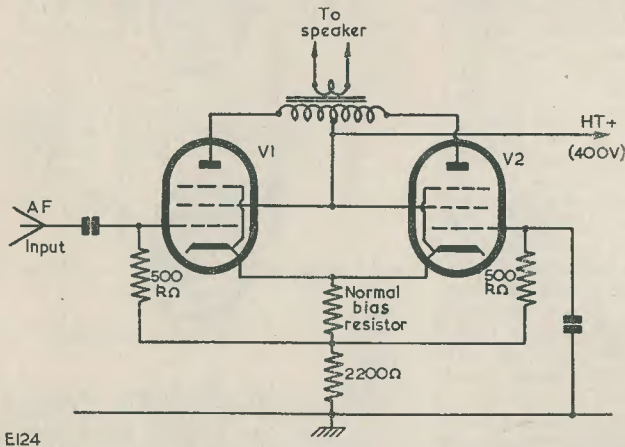


Fig. 3. The Schmit phase-split circuit, described in a letter from J. Kendall

this current. On the other hand, the circuit of Fig. 2 might not be at all unattractive when small output valves are used and fidelity of reproduction is not of primary importance.

J. Kendall, whose articles and books are well known to readers, has also commented on the subject.

"The 'Mystery Circuit,'" he says, "was originally developed by an engineer named Schmit, and is known as the 'Schmit Phase-Split Circuit.'" However, like most circuits that were properly developed by competent engineers, it has been butchered to cut the cost. When the circuit was developed by Schmit about 20 to 25 years ago, he calculated that the circuit must have a cathode coupling resistor of at least ten times the value of the bias resistor required for two valves in push-pull. If, then, two valves of the 6V6 type are to be used with, say, 15 volts bias, then a cathode voltage of 150 volts above chassis is required. This necessitates a higher value of HT: i.e. 400 in place of 250. The normal method of designing the circuit is to return both grids to the bottom of the bias resistor (using the original value) by means of a suitable resistor around 500 kΩ. The 'spare' control grid is then 'earthed' via a 0.1 μF condenser. The 'coupling' resistor is connected between the bottom of the cathode bias resistor and chassis. (A circuit of this type is illustrated in Fig. 3.)

"I have recently made a directly coupled amplifier using this circuit. With a pair of EL84's I use a coupling resistor of 1.5 kΩ, joining one grid to the anode of the drive valve. Both grids are connected via a 470 kΩ resistor, the second grid connecting to earth via a 0.1 μF condenser. The balance is, as far as I can check, perfect."

J. D. Herring (Salisbury) includes, in a long letter, a circuit which does give push-pull

working from a pair of output valves using normal HT voltages (Fig. 4). "This is not a very nice arrangement, however," he writes, "and is seldom used in practice. Since the

grid leaks of output valves normally should not exceed 250 kΩ, condenser C will have to be large—say 1 μF—in order to preserve balance at low frequencies, and will have to be quite leak-proof at the full HT voltage. Also, the HT supply to the output valves will require extra smoothing as any ripple is fed differentially to the grid of the second valve. In addition, the chief merit of the circuit, its self-balancing action, is largely lost owing to the small voltage gain in the final stage; and balance will have to be set up by careful adjustment of the tap on the resistors joining the anodes."

Another reader, L. F. Sinfield, has sent a similar circuit, with the difference that the cathode by-pass condenser (shown as an electrolytic in Fig. 4) is omitted.

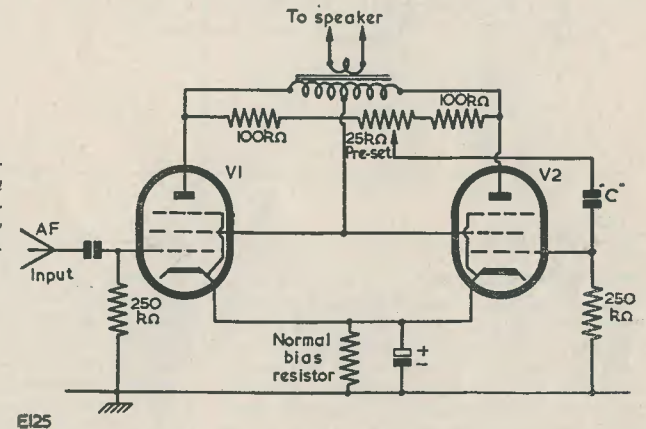


Fig. 4. Another version of Fig. 1, in which a largely self-balancing action may be obtained at normal HT voltages.

As mentioned earlier, I have received quite a few other letters as well concerning the "Mystery Circuit," nearly all of these concurring with the views just quoted; and I would like to take this opportunity of cordially thanking those readers who were good enough to write to me on this subject.

FM

I have recently started playing around with an FM tuner which is more or less of my own design, and I have obtained a considerable amount of satisfaction from the process. There is, indeed, quite a lot of pleasure to be had from FM construction, quite apart from the fact that the completed receiver ensures that programmes can be received at good quality and free from background. The first thing to do, so far as FM experimental work is concerned, is of course to try and get the practical "feel" of the circuits and techniques

employed. Unfortunately, unless one has a suitable wobulator and oscilloscope, one has to work in the dark until one's first receiver is nearly completed. Only after the frequency-changer and IF stages have been built is it possible to pick up the BBC test signals and really get to grips with the working of the circuits.

Those who are contemplating the design of their own FM sets (including, possibly, the coils and IF transformers) but do not have a great deal of test equipment on hand can find a reasonably useful short-cut by initially treating their receivers as if they were intended for AM. It is probable that, in most cases, the proposed receiver will incorporate a ratio discriminator circuit, such as is shown in Fig. 5. If this is the case, the electrolytic

stabilising condenser may be removed temporarily from circuit and an AF amplifier connected to the load resistor, as illustrated in the diagram. The set then becomes, to all intents and purposes, an AM receiver with a somewhat inefficient detector circuit. Using an amplifier in this manner even allows the discriminator transformer itself to be initially tested. Should this transformer "peak" within the range of movement of its iron-dust slugs then one can say that at least a part of the battle has been won!

By connecting an output meter across the output of the amplifier and injecting a modulated signal into the IF stages one can also obtain a reasonably good idea of their bandwidth. A fairly flat-topped bandwidth of some 200 to 300 kc/s appears to be most desirable, and this should primarily be aimed at. Unfortunately, although over-coupled IF transformers seem to offer a

very attractive method of obtaining such a bandwidth, they should not be used over-extensively since they may introduce phase-shift, with consequent distortion at the discriminator. More preferable are slightly staggered IF transformers which are just short of critical coupling.

When the AF amplifier is used, the signal injected into the IF stages for initial alignment should be as small as is consistent with a measurable output from the amplifier.

the VHF signal frequency band should, preferably, do so on fundamentals and *not* on harmonics. If a signal generator working on harmonics is used it is very easy to waste a lot of time chasing the wrong harmonic.

I daresay that quite a few readers, like myself, possess one of the more inexpensive commercial signal generators having a frequency range which extends up to some 100 Mc/s or so. These signal generators are

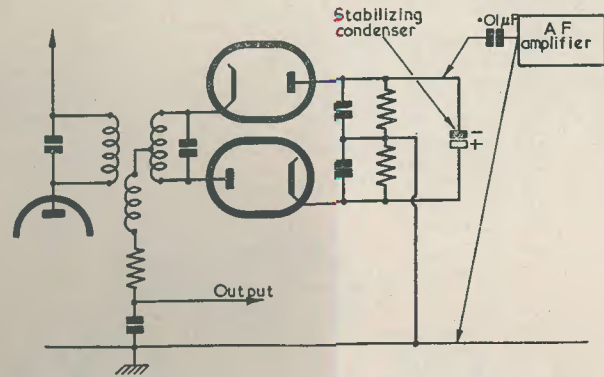


Fig. 5. A typical FM discriminator circuit. Experimenters who have not yet had practical experience of FM may find it helpful to disconnect the stabilizing condenser and treat the circuit as an AM detector for initial alignment

E126

The Frequency-Changer

One of the more difficult parts of the FM receiver to get into operation, when one is "starting from scratch," is the frequency-changing stage. Unless coils especially made for the job are available a signal generator covering the VHF band is well-nigh essential. Here, again, it is possible to start off by treating the set as an AM receiver and by setting up the frequency-changer to receive AM signals at the requisite frequency. It is worth while mentioning that the signal generator employed to cover

excellent jobs (for their purpose), and adequately fulfil the performance to be expected at the price one pays for them. However, at frequencies around 90 to 100 Mc/s it is possible for their attenuator readings to become somewhat erratic, and such readings as are given should be taken with a very large grain of salt. The reason, of course, lies in the self-capacities in the attenuator network of the signal generator itself.

As an illustration of the precautions one has to take with regard to this point, a friend of mine told me recently that he had experienced considerable trouble in attempting to line up an FM receiver when using one of the more inexpensive types of signal generator. Even when both attenuator controls (coarse and fine) were turned fully anti-clockwise, sufficient RF output was still given at 90 Mc/s to completely overload the receiver! The only solution consisted of completely disconnecting the signal generator from the receiver, moving it several yards away, and connecting a foot or so of un-screened wire to its output terminal. The radiation from this piece of wire was then just sufficient for it to be picked up by the receiver input coil and wiring, whereupon the set was capable of being finally lined up in a more-or-less normal manner.

MODERN LINE TIMEBASE CIRCUITS

by S. WELBURN

The first of two articles describing modern line timebase circuits which are intended especially for the home-constructor and experimenter

SOME TIME AGO THE WRITER CONTRIBUTED to *The Radio Constructor* a short series of articles whose subject was the "Repair and Maintenance of Line Output Transformers."¹ As a result of these articles a number of readers were good enough to correspond with him on one or two of the points raised. Some of the letters from readers were concerned with particular line output stage faults, and these were passed on to "Query Corner" where, of course, they rightfully, belonged. Quite a few correspondents mentioned that, so far as television components were concerned, there appeared to be a dearth of new designs in the home-constructor field. They remarked that manufacturers appeared to be quite happy to carry on with the same designs year in, year out. Several readers, also, were interested in the possibility of using "direct-drive" line output stages in home-constructed televisions. (This type of transformer was dealt with in the first article of the series just mentioned).

The Present Scene

Taking the first question into consideration, the statement that manufacturers of home-constructor television components are content to jog on year after year is not entirely true, even though the facts appear to point that way. Let us take the case of scanning components. As many readers may be aware, there are several manufacturers of home-constructor scanning gear who have now been marketing the same components for quite a few years. (In passing, one cannot help but remark that the fact that these components are as popular as they were at their introduction goes a long way towards showing that their initial design and specification have been well proven in practice).

Whilst the writer does not wish to commit himself to any dogmatic statement, he would

like to point out that much of the apparent hold-up in the development of home-constructor scanning equipment is, most probably, due to the non-availability of new tube types. Quite some time has gone by since the present 70 degree 14 to 17-inch (and, much more recently, 21-inch) tubes were introduced; yet there appears to be little likelihood of any dramatic increase in tube size for some considerable time. One cannot help but reflect a little sadly on the slowness of tube development in this country, especially when one considers the large advances that are being made in America.

The second point, that of the possibility of direct-drive components for the home-constructor, is rather easier to handle. So far as the writer is aware, it is doubtful if such components would ever be put on the home-constructor market at all; and, at any rate, certainly not for the time being. The reason for this is that there are too many snags to their operation. (This does not obviate the fact that direct-drive components might not be available from some suppliers in the form of manufacturers' surplus).

When compared with the auto-transformer circuit the direct-drive line output stage has one single advantage, and that is in the saving of cost in the materials which make up the line output transformer itself. Even then, the saving is not large and consists of a few shillings only. Against this one advantage have to be set the several disadvantages which are essentially inherent in the direct-drive circuit, viz, EHT generation in the scanning coils, with consequent risk of breakdown and corona in wiring and the yoke itself; heavy radiation of radio interference by *all* the line output wiring (including that to the yoke); and poor final performance, so far as EHT regulation is concerned. At the time of writing, the direct-drive system is only attractive to those home-constructors who have a reasonable

¹ *The Radio Constructor*, September, October, November, 1954.

RADIO COMPONENT SHOW

APPLICATION CARDS OUT

Application cards for badges for admission to the Radio Component Show, to be held at Grosvenor House from 19 to 21 April can be obtained by written request to the Secretary, Radio & Electronic Component Manufacturers' Federation, 22 Surrey Street, Strand, London, W.C.2.

The exhibition is intended primarily for engineers and technicians in all the user industries and in the Services. The wide list of those eligible covers research and education and the manufacturing, wholesale (not retail) and export sides of the electronic industries. Every bona fide applicant will receive a badge.

There will be 142 exhibitors—a record number.


amount of test equipment immediately available, together with some practical working experience of the circuit.

A New Transformer

It is refreshing at this stage to be able to comment on the fact that a completely new line output transformer has recently been released on the home-constructor market, this transformer having been especially designed to cater for existing conditions and, so far as new CRT types are concerned, for what can reasonably be expected to develop in the next three to four years. The manufacturers² have introduced the transformer³ not only to make their home-constructor range more up to date but also to ensure that a component is at once available to provide the higher EHT voltages which will be required for 21-inch tubes.

applied to the line output valve, this process reducing the line flyback EHT voltage generated by the transformer. The line output transformer which has now been introduced goes one step further. It is intended to scan the existing range of 14 to 17-inch tubes, whilst a slight increase in line output HT rail voltage is all that will be required to generate the additional EHT needed for 21-inch tubes when these are fitted. The new transformer is not really intended for use with the smaller, narrow-angle tubes.

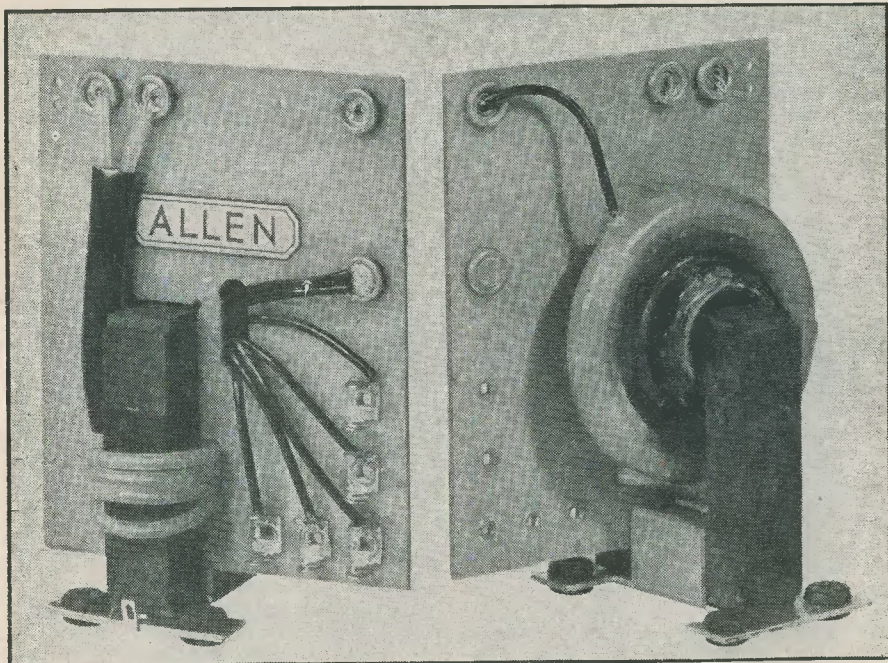The construction of the transformer involves a considerable break-away from present home-constructor practice. A point of interest is given by the fact that the metal base of the transformer is fitted to the television chassis by means of grommets, this assisting considerably in the reduction



Front and rear views of the New Allen LO352 Line Output Transformer

Readers who have built the Magna-View and similar receivers may remember that the wide-angle line output transformers used were not only suitable for 14 to 17-inch tubes, but also for 9 and 12-inch tubes as well. The smaller tubes were driven successfully by slightly reducing the HT rail voltage

of audible whistle radiation. Further, this metal base is fitted with a solder tag for a direct earthing connection to chassis; this connection earthing also the Ferroxcube cores themselves and preventing, thereby, the formation of static voltages which in previous designs were liable to build up in these cores. Photographs of the transformer accompany this article.

² Allen Components Ltd. ³ Lo 352

It is important to note that the transformer does not match into existing home-constructor yokes, as the design requires a higher line impedance than that previously employed. A new scanning yoke⁴ is therefore also available, this having the same frame impedance as the yoke it supersedes⁵. Thus, the new line output circuit may be built into existing televisions without the necessity of having to alter any frame circuits which may at present be in use.

Circuits

The circuit of the line output transformer and its immediately associated components is shown in Fig. 1. There is little of especial note in this diagram apart from the fact that an auto-transformer design is employed, and that a feedback tap is available from an extension of the anode winding. Although the manufacturers state that the transformer

this stage, especially insofar as no "Drive" control is needed at all. The reason for this omission is that the output stage has, largely, the characteristics of an inductive timebase and can consequently be driven either by a saw-tooth or by a square-wave. Under such conditions the inclusion of a "Drive" control is not merited and it can safely be dispensed with.

The multivibrator is synchronised by negative-going pulses, these being applied to the grid of the left-hand triode. Values have not been shown for R1 and C1 in the circuit, as these depend somewhat upon the type of sync separator employed and the amplitude of the pulses. For normal purposes, however, it will usually be satisfactory to employ a value of 330Ω for R1. The value of C1 may then be found by experiment, the best value being that which affords a positive lock over approximately one-third

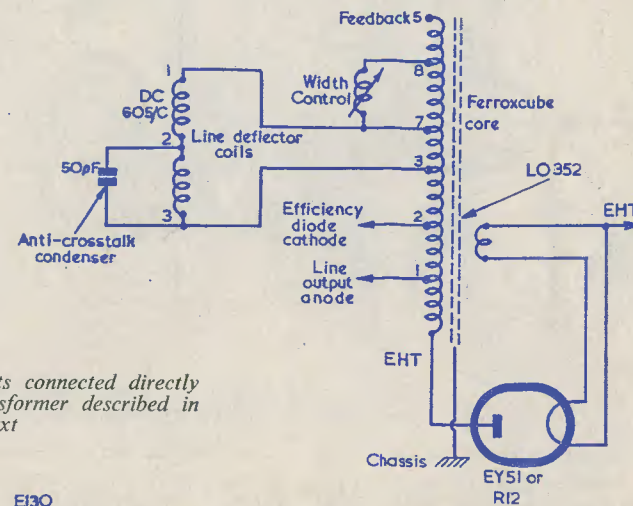


Fig. 1. The components connected directly to the line output transformer described in the text

functions at its best when the line output valve is driven by a separate oscillator, the feedback tap has been included for those who wish to experiment with self-running timebase arrangements.

Fig. 2 gives a typical example of a line timebase circuit employing the new transformer, in which the line output valve is driven by a multivibrator. This circuit, incidentally, is that recommended by the manufacturers for home-constructor use.

As may be seen, the line oscillator consists of a simple cathode-coupled multivibrator. Some economy of components is effected in

to one-half of the total travel of the "Hold" control R7. Normally, C1 would have a value lying between 10 and 50pF. Neither R1 nor C1 should be considered as being very "critical."

The output of the multivibrator appears across the discharge condenser C4, and is then applied, via C5, to the grid of the line output valve. The latter is a PL81 and feeds into the auto-transformer itself. All that then remains in the diagram are the components around the efficiency diode, PY81, and the linearity control. It will be apparent that the arrangement employed in this part of the circuit, also, is quite noticeably

⁴ Type DC 605/C ⁵ DC 300/C

simpler than those used in previous home-constructor designs. As is conventional in this type of circuit, a boosted HT voltage is available from the transformer, this being applied back to the multivibrator. The boosted voltage may also be employed by the frame discharge circuit, using normal practice.

Whether it is fitted or not in individual televisions is left to the constructor's own judgment.

A word of warning is also worth while with regard to the screen-grid resistor R10. This resistor serves a very important function in that it limits the screen-grid current of the PL81 whilst the PY81 is warming up to

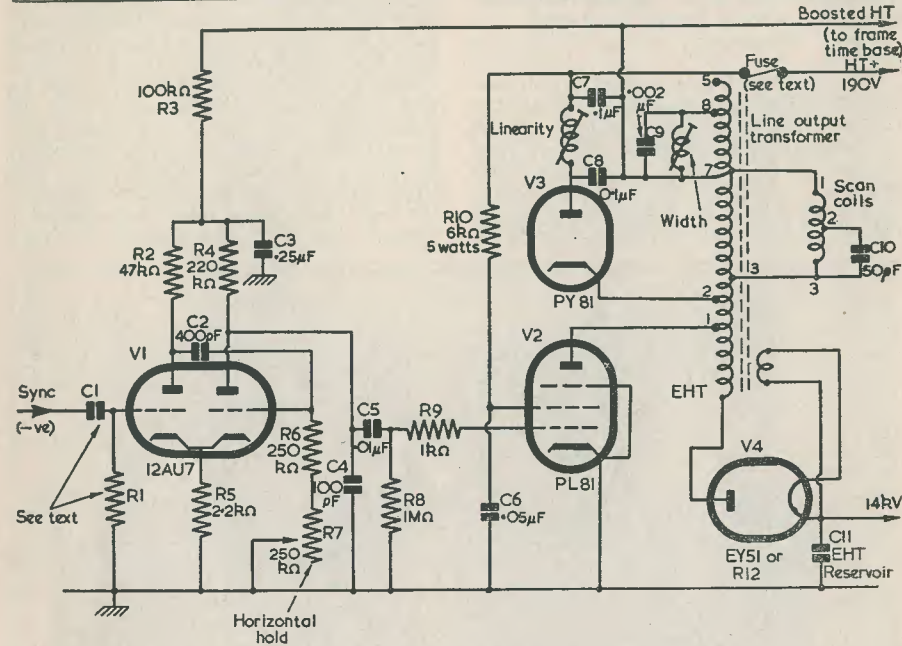


Fig. 2. A particularly serviceable line time-base circuit employing the transformer of Fig. 1

A further point of interest is given by the fact that a fuse has been inserted in series with the HT feed to the line output valve. The purpose of this fuse is to protect this valve in the event of cessation of oscillations from the multivibrator. Due to the self-biasing action at the grid of the PL81, cessation of oscillations would cause a continual zero grid bias, whereupon the valve might suffer damage. A fuse rated at 150mA will cope here. The fuse chosen should, however, be capable of passing the steady current of approximately 80 to 85mA which is taken by the valve when working normally. (The specified maximum safe cathode current of the PL81 is 180mA). The fuse is not entirely essential, of course, and a protective device of this nature is rarely fitted to commercial receivers in which similar eventualities are liable to occur.

full emitting temperature. (The PY81 takes considerably longer to warm up than does the PL81 owing to the high-voltage insulation which exists between its cathode and heater). On no account should R10 be reduced below the value shown (6kΩ) or the PL81 screen-grid may pass excessive current during this warm-up period.

Practical Considerations


The writer has been able to try out the circuit illustrated in Fig. 2, and is therefore able to pass on some points concerning its performance to readers.

The first fact that was noted was that the multivibrator circuit recommended had excellent frequency stability. Synchronising was positive, even when values as low as 5pF were used for C1. (A single-valve sync separator, operating from the video output

stage, was employed in the associated television). The absence of a "Drive" control was also appreciated, since it obviated the necessity of having to make fiddling adjustments when setting up. Once the timebase was locked there was no need to worry

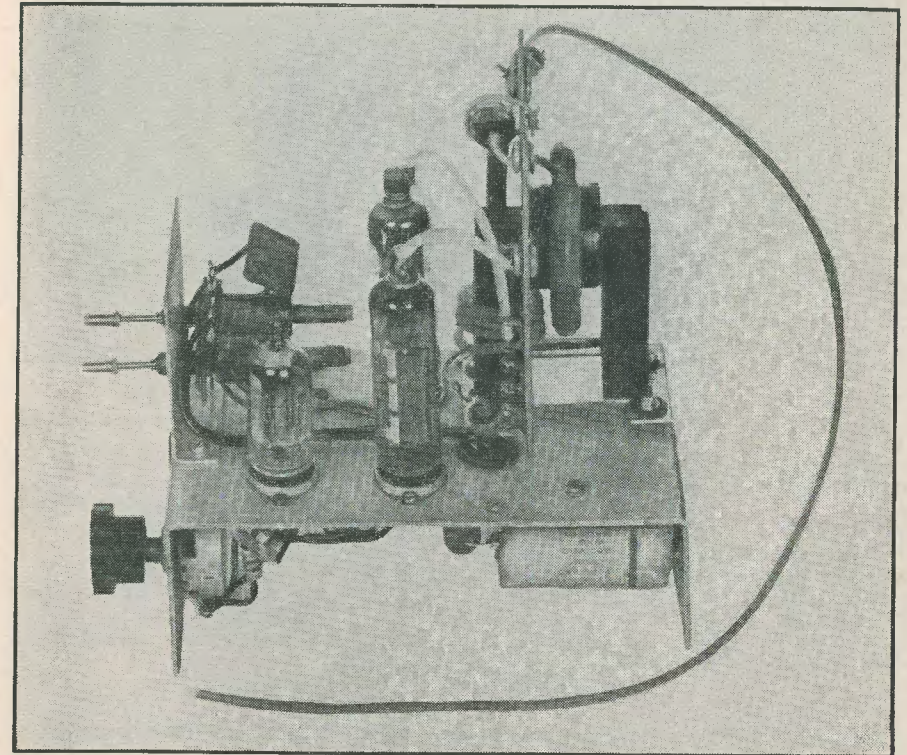0.001 and 0.0025μF; the smaller capacity giving the narrower picture.

What impressed the writer most was the excellent EHT regulation given by the transformer. The manufacturers quote an EHT source impedance of better than 5MΩ, and




View of Prototype Timebase using the Allen Lo 352 Line Output Transformer

about the multivibrator any more.

Owing to the largely inductive nature of the line output anode load, the width and linearity controls have a slightly smoother effect than is the case in the earlier home-constructor circuits. The width control gives a variation of approximately one-seventh of the total scan, although this may be increased by removing its lock-nut and adjusting the threaded portion so that its end is nearly flush with the mounting assembly. Such a setting, that of extreme narrowness, as it were, would rarely be required in practice. An effective secondary control of width is also available by varying the value of C9. This condenser, which should normally be 0.002μF, may be varied between

this certainly appears to be borne out in practice. Typical figures given in the writer's set-up, using an HT rail voltage of 185, are as follows. With the brilliance control backed off such that no picture was visible at all, the EHT given at the CRT final anode was 14.5kV. When the brilliance control was turned up to give a good, bright picture, the EHT dropped to 14kV. When the control was further advanced to a position whereby brilliance was obviously much too high, the EHT dropped only very slightly, to a figure around 13.7kV. It was only when the brilliance control was grossly advanced, far beyond its correct position, that the EHT began to drop noticeably, and, even then, only to some 11 to 12kV. The

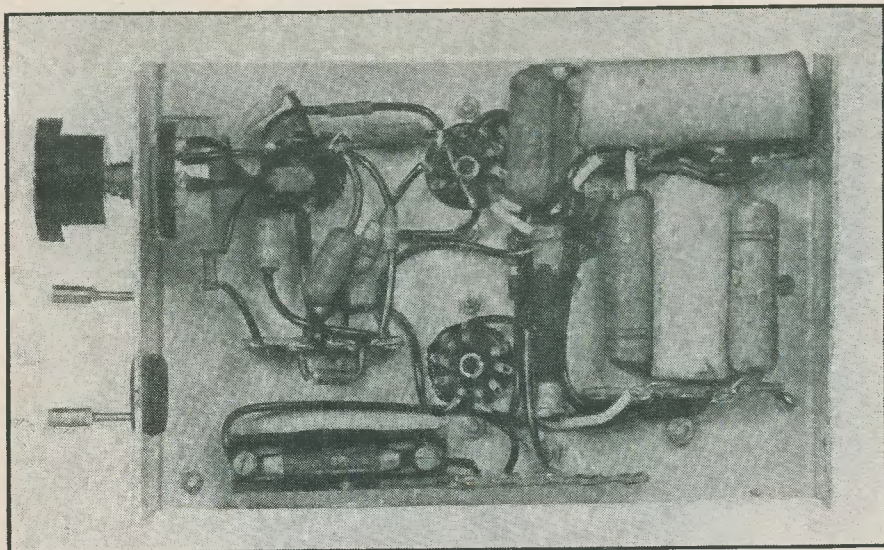

Underneath view of the chassis shown on previous page

writer would like to see some commercial receivers with regulation as good as this!

Photographs

For the purpose of his experiments, the writer constructed a small chassis to hold the necessary timebase components. This chassis is illustrated in the photographs which accompany this article, and these give an excellent idea of the appearance of the new

transformer when it is fitted into a typical television layout. As was mentioned earlier, a photograph of the new transformer itself is also reproduced.

Next Month

Next month the writer will introduce some alternative circuits suitable for use around the new components discussed in this article.

FM COMPETITION

The *Radio Constructor* is offering prizes of (1) 2 guineas, (2) 1 guinea, and two consolations of 10s 6d to the senders of the most informative report of reception at distances greater than 80 miles from Wrotham. The report should be concise, but should cover the following points:

- (1) Type of aerial (1, 2 or 3 elements), and height.
- (2) Approx. height of location above sea level, if known, or whether the site is shielded by hills from Wrotham.
- (3) Comparison of reception with the local medium wave service.
- (4) Details of FM Tuner or Receiver.
- (5) Details of other equipment in use, e.g. 8-Watt push-pull output with 10" speaker in bass reflex cabinet.
- (6) Reliability of reception, and any other useful information.

ALL REPORTS SHOULD BE SENT TO ARRIVE AT:

"FM Contest," The *Radio Constructor*, 57 Maida Vale, London, W.9.,
NOT LATER THAN MARCH 10TH 1955.


NOTES ON RADIO CONTROL

5: TWO SIMPLE TRANSMITTING UNITS

By QUENCH COIL

HAVING DEALT WITH VARIOUS RECEIVER circuits and the installation of the radio control equipment in the model, we will turn our attention to the transmitting side of the system. Here again, one must emphasise that care in construction and good design pay dividends in reliability of operation. It is just as important to have the transmitter working as reliably as the receiver, if fault-proof operation is to be had.

the feedback required for oscillation being obtained by cross connection of the grids and anodes through small condensers. The circuit is shown in Fig. 1, in the form in which the components are arranged on the chassis. Very little skill is needed to construct this unit, and it is thus ideal for the newcomer to radio control. Wire up with 22 swg tinned copper wire and sleeving, keeping all wires as short as possible.

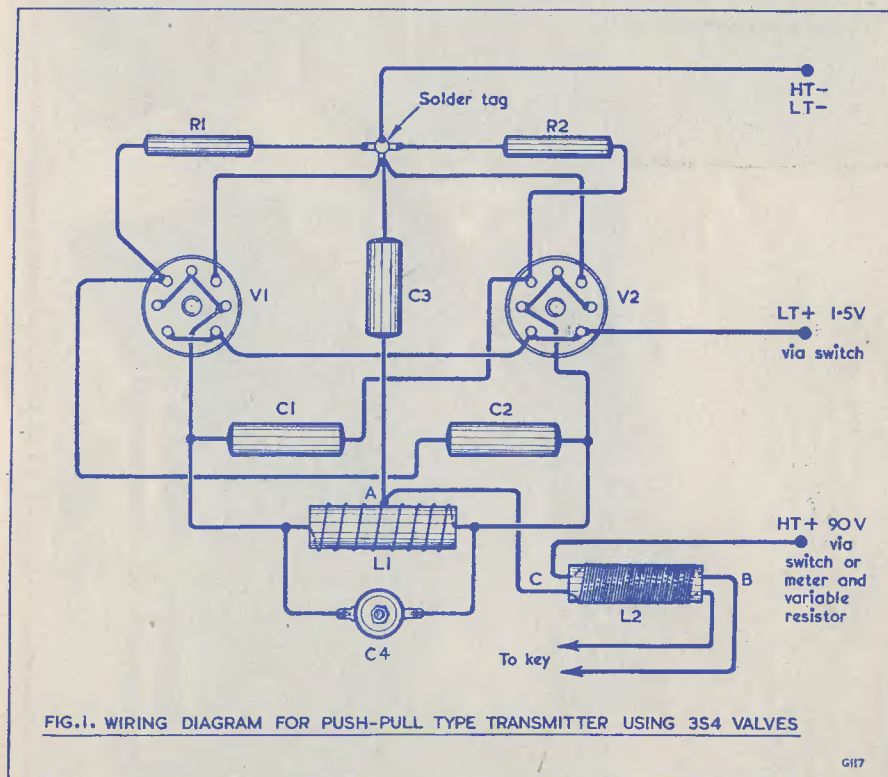

For key, see page 475

The first transmitter described is a simple one which will do well as a "first effort" for those who have not built equipment of this sort before. It uses two type 3S4 valves in a push-pull circuit and requires only one coil,

Testing

Check wiring carefully and if correct connect a 0-30 mA meter in the HT positive lead. Switch on LT and HT. The meter should read about 10 mA. Now connect the

Figs. 2 and 3. Photos show front and rear view of twin transmitter. Unit on left (rear view) two-valve using two 3S4 valves. Right, two-valve using two DL35 valves. Both transmitters operate from 90 volt HT. Note metal case enclosing unit and hole for adjusting tuning condenser. Note (front view) keying lead and clean lines of panel. Note aerial mounting; see drawing of same. Both transmitters have operated receiver over a distance of 1,000 yards


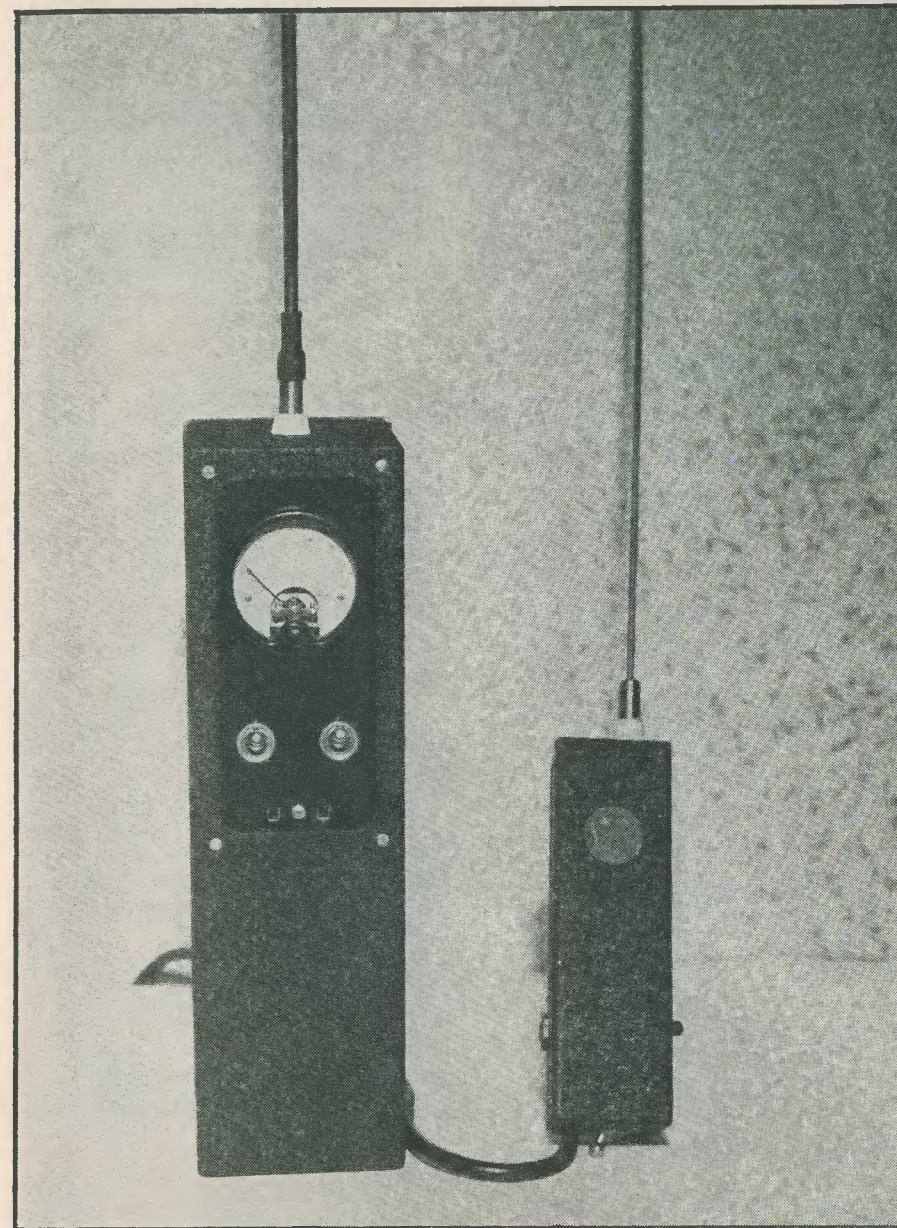
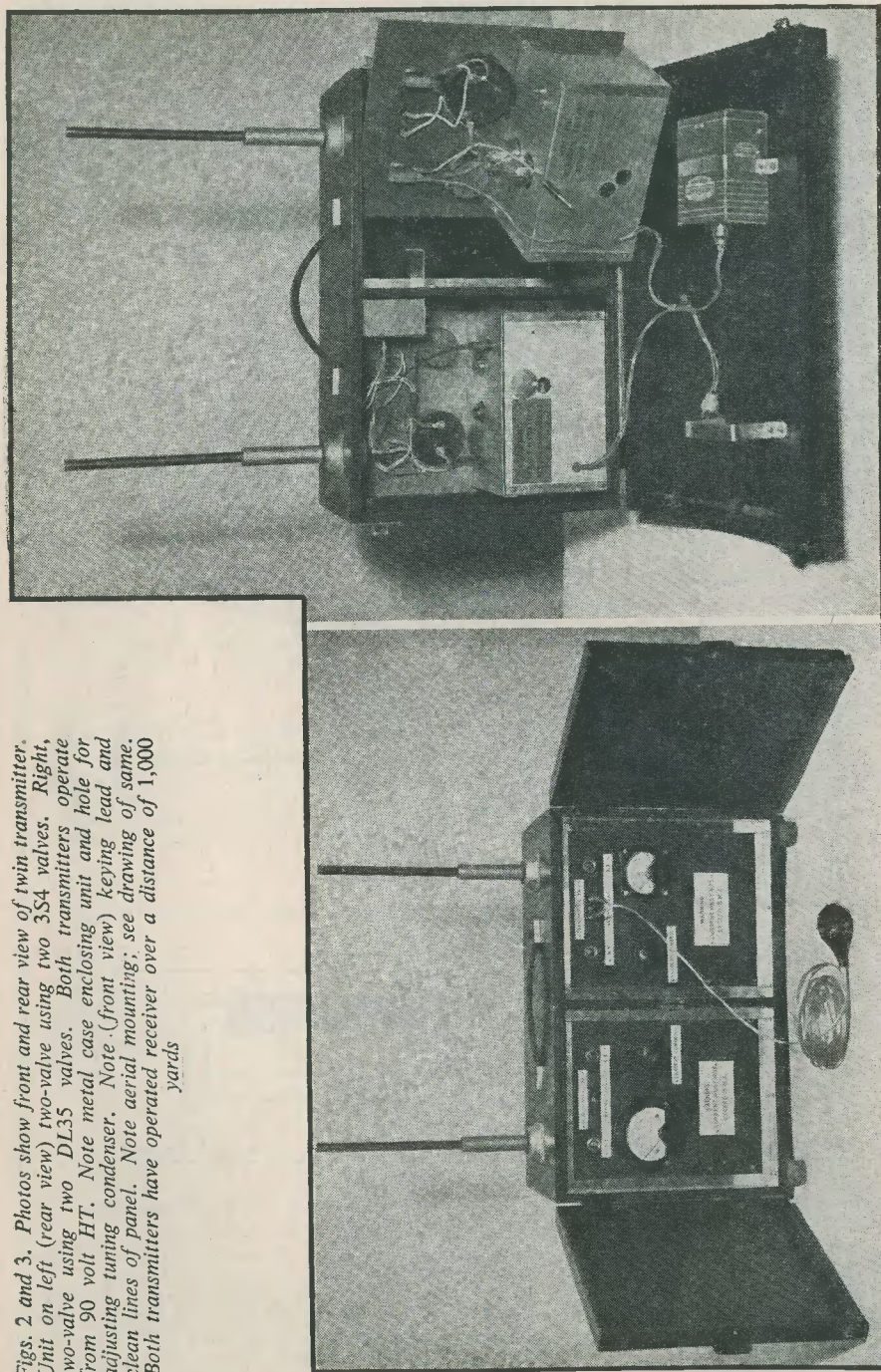
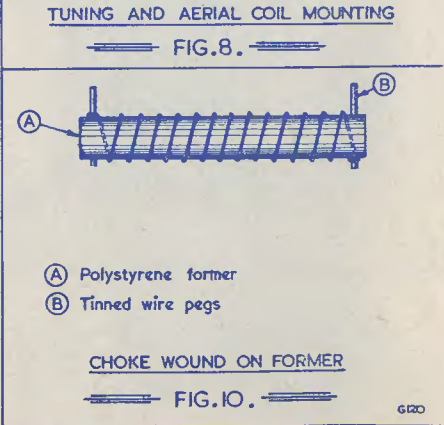
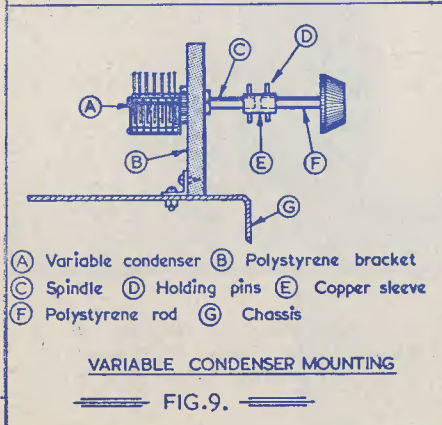
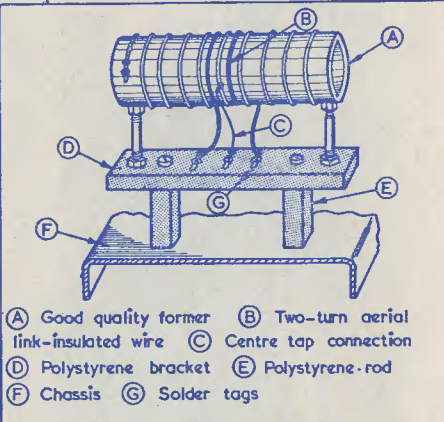
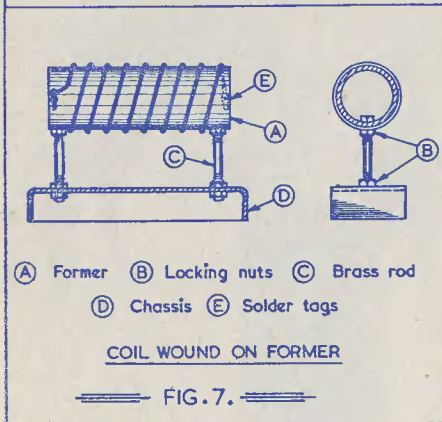
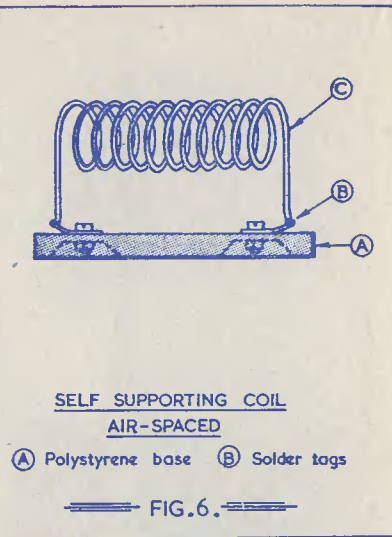


Fig. 4. Two small portable transmitters. (Left to right) Two-valve using 90 volt HT and LT $1\frac{1}{2}$ volt, both batteries carried in bottom part of case. Extra small transmitter using two DL70 valves. Batteries carried in small battery pack in pocket



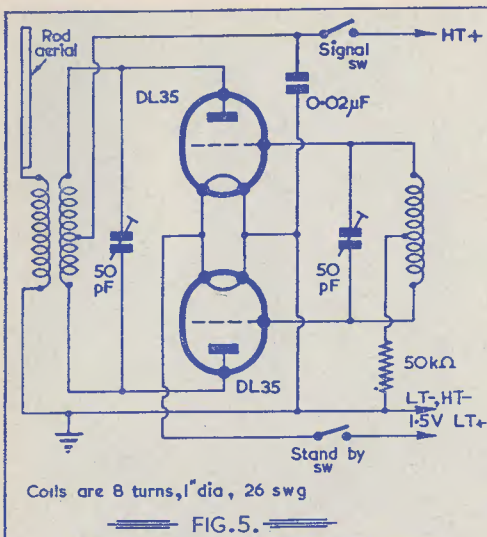


aerial. The meter reading should rise to about 15 mA, which is a safe current for this type of valve. Should the current be incorrect, it can be raised by lowering the resistor values; if too high, increase resistor values, keeping both resistors (R1 and R2) of the same value.

The unit should now be fitted in a metal case, and the whole unit, with batteries, enclosed in some form of carrying case. Various ideas for the latter can be gleaned from the photographs of some of the transmitters made by the writer, illustrating this

valves protruding through holes in the lid. The meter, etc., batteries and so on are attached to the case as shown. In Fig. 4, on the left, an arrangement in which the transmitting unit is housed in the top of a metal case, with the batteries in the bottom, is shown. On the right is a smaller unit housing the transmitter only, the batteries being carried in a separate pack in one's pocket.

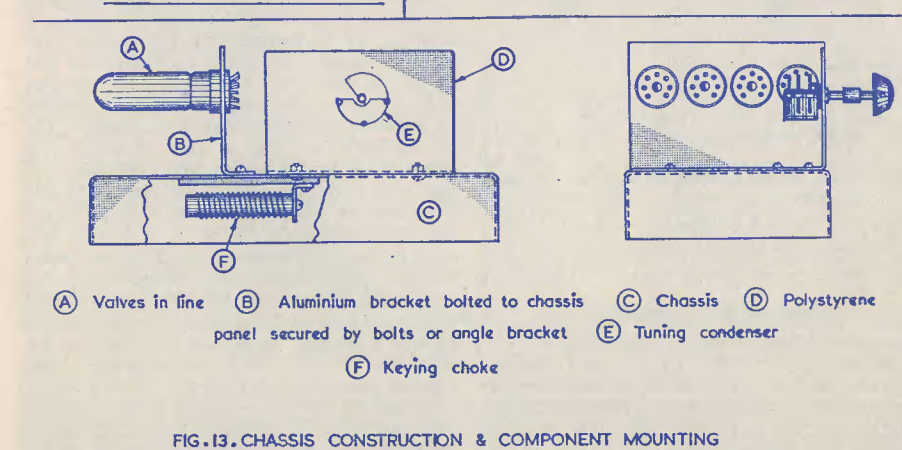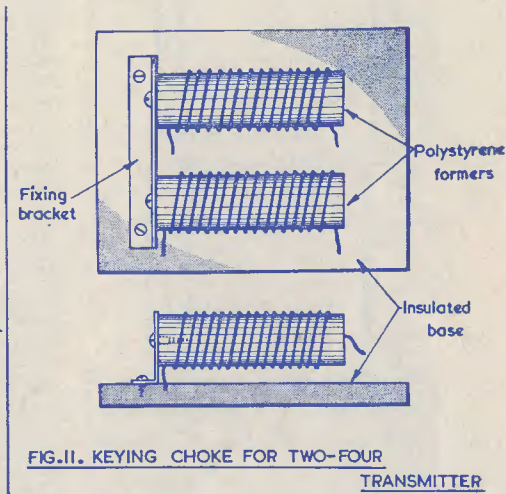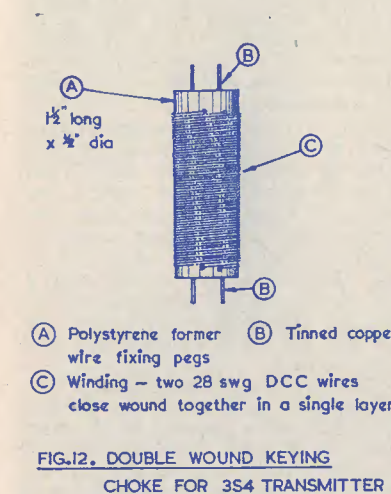
The transmitter must now be tuned to the correct frequency. This requires the use of an absorption wavemeter set to the frequency required. A suitable wavemeter will be



article. In Figs. 2 and 3, a unit housing two small transmitters is shown. From Fig. 2, the arrangement of the transmitter in a screening box is shown, the tops of the two

described later in this series, and the beginner is advised, if he cannot borrow one, or get some other enthusiast to help him, to consult his radio dealer or a local amateur radio

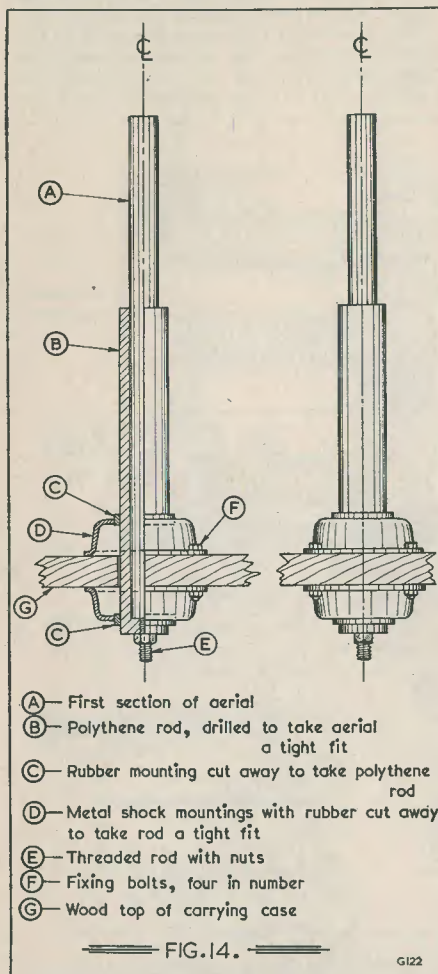operator. If he should have a good short-wave receiver which is accurately calibrated, he can use this by setting the tuning at 27 Mc/s and tuning the transmitter frequency on to this frequency. Tuning must, of course, be done with an insulated tool, and the full length of aerial it is proposed to use on the transmitter must be fitted.



We can now test with the receiver. Switch receiver on and tune it until the receiver meter drops to nearly zero. When the transmitter is then switched off, the reading should rise again. Once this is in order, check the receiver relay and adjust for positive action. Then make range tests every 50 yards until the limit is reached, some slight adjustment to receiver trimmers being made for best results during these tests. In the

writer's case a nine-foot-whip aerial is used, but the length of this is not critical.

The second transmitting circuit shown, Fig. 5, is of the tuned-grid, tuned-anode type, using two low drain battery pentodes of the DL35 type. The American equivalent is the type 1Q5GT. This circuit uses two coils instead of one only as in the first transmitter, and the design will give first class results. It forms the logical 'next step' for the beginner. A 0-50mA meter should be used this time, and construction carried through as with the first model.

To conclude this article, a few remarks about the construction of the coils, keying chokes, aerial mountings etc., may be of value to the newcomer. The more experienced worker will no doubt have his own methods, but he may find the writer's ideas on these components of interest.

The coils, or tuning inductances as they are called technically, can be either self-supporting or wound on a former. When only a few turns of wire are needed, the self-supporting variety can be used, the wire then being of a gauge firm enough to keep its shape, such as Nos. 14, 16, 18 or 20 swg. The coil is then wound over a mandrel of the correct diameter and a soldering tap attached at each end, by means of which it can be attached to a base as shown in Fig. 6.

If so many turns are needed that a thin gauge of wire has to be used, then the coil must be wound on a former; which must, of course, be of some insulating material such as polystyrene, paxolin and so on. The coil can be attached to the former as shown in Fig. 7, which also illustrates a method of mounting the completed coil on the chassis. Where a coupling coil has to be wound over the centre of another coil, as is necessary for the aerial coupling in a push-pull transmitter, for instance, the arrangement of Fig. 8 can be used, the small two- or three-turn link coil being of insulated wire and fixed as shown. Similarly a centre-tap connection can be taken as shown, if required.

Variable condensers should be mounted as near their inductances as possible, and they must frequently be mounted so that they are insulated from the chassis. Such an arrangement is shown in Fig. 9, an extension rod (F) being used to reach to the control knob on the panel.

Where an "RFC"—radio frequency choke—is specified, this can be made up of 30-40 turns of thin wire on a 1-inch long by ¼-inch diameter piece of polystyrene rod, and the wire fixed as shown in Fig. 10.

"Keying chokes" are frequently specified for connection in the leads from the "key" or switch used to actuate the transmitter.

These may consist of two separate coils wound and fixed as shown in Fig. 11, or a "double-wound" choke may be specified as shown in Fig. 12, which is the type used in the 354 valve transmitter. Here, two separate wires are wound on to the former as shown. Each coil is kept separate from the other electrically, as insulated wire is used, but the turns are physically in touch if described as "close-wound." If described as "open-wound" or spaced, then they should not touch.

The general arrangement of the various components on the chassis is usually indicated in the building instructions if critical, otherwise it is in order to get a close approximation to the photos. Fig. 13 shows a typical method of laying out a transmitter, using four valves, which will be described later in this series.

KEY TO COMPONENTS AND VALUES OF FIG. 1

V1 and V2, 354 Valves. C1 and C2, 27 to 30pF condensers. C3, 0.001µF Condenser. C4, 50pF trimmer or miniature variable condenser. R1 and R2, 10 or 15kΩ fixed resistors. L1, Tuning coil. Wind on former 8 turns of 18 swg tinned copper wire, completed 1" long, 1" diam., make tap at centre 'A'. Aerial coil. Two turns of insulated wire wound round tuning coil. One end taken to earth, the other to aerial socket. L2, Double-wound choke in key lead. Wind with two 28 swg DCC wires, wind together close in a single layer, secure at each end on tinned pegs. Mount on small bracket. Size of former 1½" long, ½" diam. Mount components on 18 swg aluminium chassis. Keep tuning condenser and coil clear of chassis. Whole unit should be enclosed in a metal case

BOOK REVIEWS . . .

PRACTICAL AERIAL TV MANUAL FOR BANDS I AND III, by R. Laidlaw. 72 pages, 72 diagrams. Price 4s. 6d.

This book has been received from the Technical Book Department, Kendall and Mousley Ltd., 18 Melville Road, Edgbaston, Birmingham. It is an excellent investment for those who wish to make their own TV aerials or experiment with different types to obtain the best reception in their particular locality.

The theory of the various types of aerial is clearly explained in a way that is very easy to understand. Matching of aerial to feeder, and feeder to receiver, is given due regard, and it is pleasing to find the characteristic impedances of the different arrays quoted so freely.

The methods of construction are simple yet sound, though many will perhaps wish to improve upon them for their own purpose.

There are two Appendices. The first deals with attenuators; the second comprises a series of tables which give details of the lengths and spacing of elements for all types of aerial described in the earlier parts of the book.

Those who read the book will perhaps realize that similar principles apply to aerials for FM reception, and it is a pity that there is no mention of this subject. Similarly, something more than a passing mention of tilted wire, half-rhombic and kindred types of aerial might have rounded off an already wide coverage of modern antennas.

The mounting of the aerial requires some ingenuity. One arrangement which the writer has found successful is shown in Fig. 14. The aerial itself consists of a nine-foot length of tubing, which may be made from narrow dural in convenient lengths, made to slip one into the other. Alternatively a war surplus whip aerial, which are still readily obtainable, can be used. A piece of polythene rod is drilled to take the lower end of the tube which passes right through as shown, a bolt and nuts being fitted at the lower end to take the lead to the transmitter. Two rubber shock mountings of suitable size are fitted as shown, a suitable hole being made through the rubber to take the polythene tube. These shock mountings can be obtained in various sizes from most ex-service stores. The drawings in Fig. 14 show the general assembly of the aerial mounting quite clearly.

TELEVISION VIEWERS' HANDBOOK, by A. C. Armstrong, A.I.MECH.E. 190 pages. Price 6s. Published by The English Universities Press Ltd., St. Paul's House, Warwick Square, London, E.C.4. A non-technical book dealing with many aspects of television receivers and principles. The many facets of the subject which are discussed include installation of receiver and aerial, correct use of controls, alternative programme reception, features of modern circuit design, use of the tuning charts, etc.

There is much to be learnt from this book, even by those who have possessed a receiver for a long time. It also imparts essential knowledge to the uninitiated in such a way that they cannot fail to obtain the best from their sets and readily appreciate how it functions.


The book naturally follows the tradition of the now wide series of *Teach Yourself* books and is considered to be well in keeping with the accepted standard of the library.

PRACTICAL TRANSISTORS, by J. S. Kendall, ASSOC. BRIT. I.R.E. 48 pages, 36 illustrations. Price 3s. 6d. Published by Bernard's (Publishers) Ltd., The Grampons, Western Gate, London, W.6.

This is one of the latest additions (No. 128) to the series of Bernard's Radio Books. It deals with a simple method of constructing one's own transistors at home from readily available germanium diodes. Methods of forming and testing the home-made product are also given.

Several circuits are described, which can form the basis for further experiment. For those who wish to acquire basic knowledge in authoritative and lucid form, this book is ideal. The author is already well-known for his ability to write in this way, and this latest contribution is typical of his style.

W. E. THOMPSON

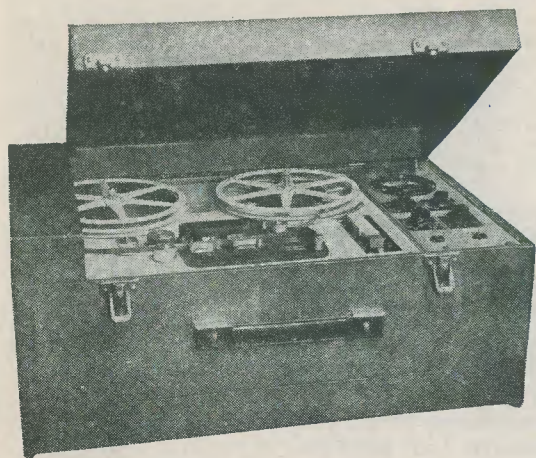

THE Paragon TAPE RECORDER

PART 3

by J. W. WALKER

Final details of this simple Tape Recorder, which has been designed expressly for the home-constructor

LAST MONTH WE DESCRIBED THE METHOD of fitting some of the more important parts of this recorder into the cabinet, and gave details of the construction of the amplifier chassis. We now carry on, in this month's article, to the remainder of the constructional work involved.

The Power Pack

As was evident from the circuit of Fig. 2, the power pack is of extremely simple design. In its practical form all the components, with the exception of the mains transformer, are mounted on a small chassis which is fitted inside the cabinet. The dimensions of this chassis, together with the layout of the component parts, are given in Fig. 16.

A word of explanation may be necessary concerning the resistor R33. In Fig. 16, one end of this resistor is illustrated as being connected to a "terminal." It may be remembered that R33 is the resistor through which passes the 150 mA braking current to the Truvox tape-deck. The "terminal" of Fig. 16 then refers to any suitable anchoring point capable of taking a fly-lead from the tape-deck motor-board. In the prototype a vitreous resistor, clipped to the power unit chassis, was employed. Since this resistor had metal ends it was possible to fit a 6BA terminal assembly to the component itself.

However, if such a resistor is not available to the constructor any other type of "terminal" mounted on suitable insulating material could be used instead. A banana socket, for instance, would present an eminently suitable alternative.

The Mains Transformer

The mains transformer presents a small difficulty. This is not due to any trouble incurred in its mounting but to the fact that its position with relation to the Record/Playback head is somewhat critical from the point of view of hum pick-up.

Whilst the hum picked up by the Record/Playback head from the mains transformer was not too troublesome in the prototype, this state of affairs cannot be guaranteed in all models constructed to the same design. It is for this reason that the transformer has not been mounted on the same chassis as are the other power pack components.

It was found, in the prototype, that the best position for the mains transformer was on its side, as shown in Fig. 17. In this position it induced minimum hum into the Record/Playback head; and it could be mounted very easily with the aid of two angle brackets.

It is probable that this position for the transformer will cope in most models built to this design but, as has just been stated, such


a state of affairs cannot be completely guaranteed. In cases where hum pick-up occurs, therefore, it will be necessary to rotate the transformer until a position corresponding to minimum hum is obtained. Care should be maintained to ensure that the position taken up by the transformer does not allow it to foul the tape-deck mechanism when fitted. It has been the writer's experience that, in really bad cases of hum pick-up, the trouble may be alleviated considerably, if not com-

taking care to avoid damaging the heads and the associated wiring.

It is worth-while stating, at this point, that hum pick-up will only be apparent when switch S1 is in the Playback position; and that the hum may, of course, be picked up from external sources other than the recorder mains transformer.

The Cabinet

Fig. 17, besides showing the method of

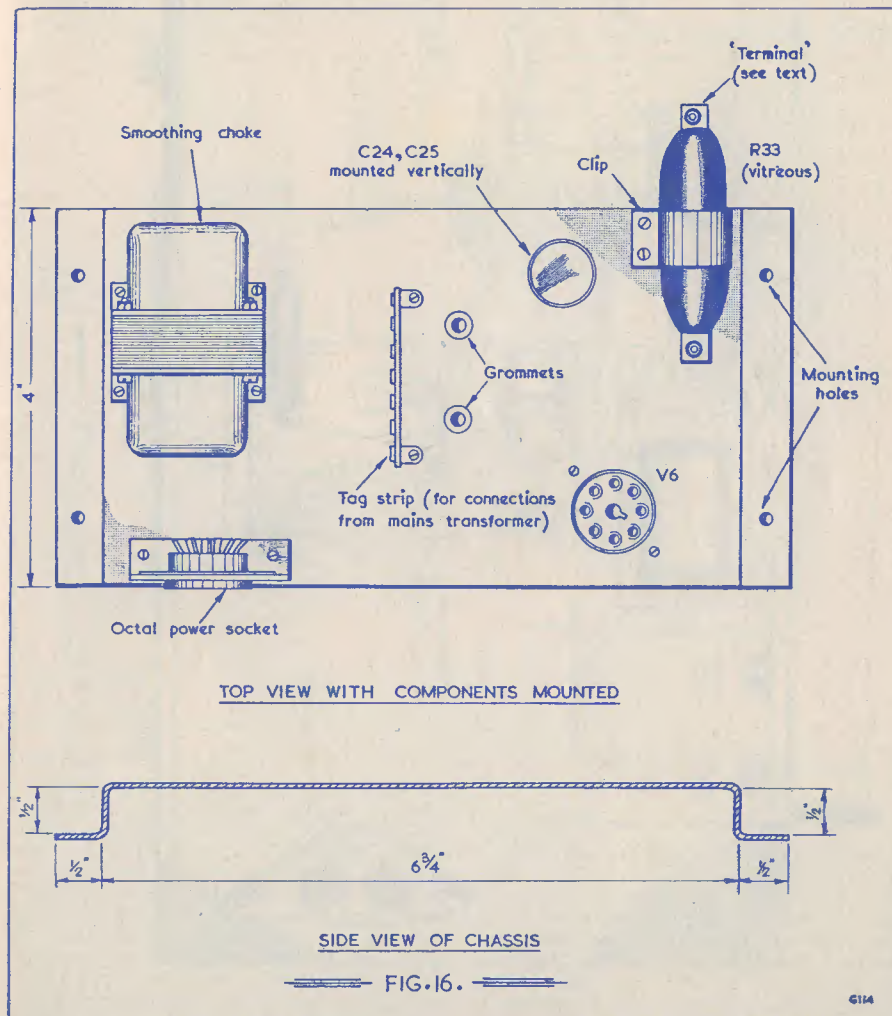

pletely, by fitting additional mu-metal shielding to the head assembly. In the case of the Truvox tape-deck such shielding should be fitted between the heads and their cover,

mounting the mains transformer, also illustrates the position of the various components which fit inside the cabinet. As may be seen, these include a 3-way mains voltage selector

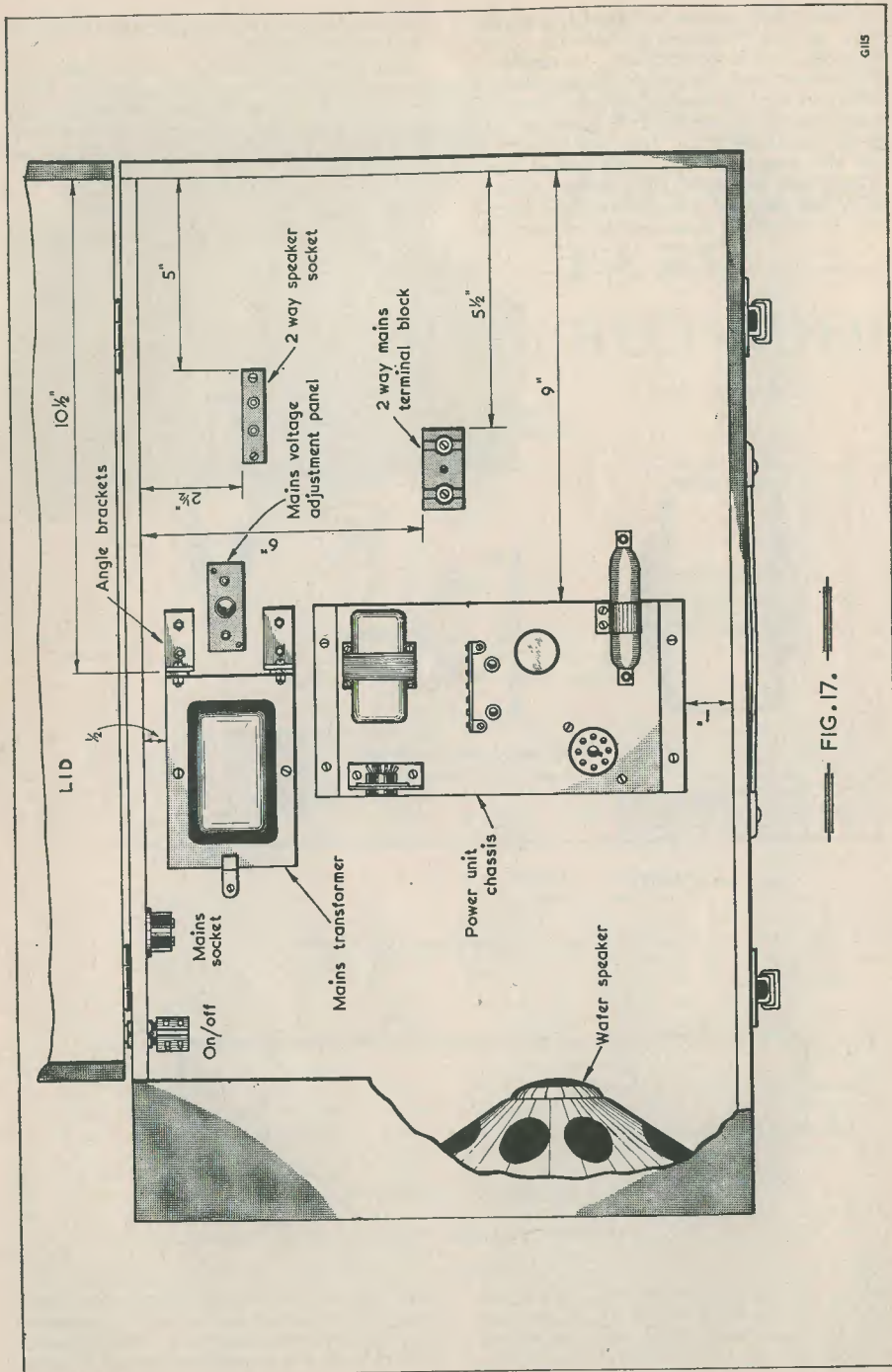



FIG. 17.

board (210-230-250 volt), a small two-way socket, and a two-way terminal block. The two-way socket connects to the loudspeaker, and is intended for the speaker plug illustrated in Fig. 15. The two-way terminal block carries the mains supply (after switch S4), and connects to a two-way fly-lead from the tape-deck. If desired, a plug and socket arrangement can be employed here instead.

It is important to ensure that the chassis and components illustrated in Fig. 17 are positioned as shown. If this is not done they are liable to foul the mechanism underneath the tape-deck motor-board.

“black” tag of the tag-strip. Strictly speaking, such a connection should not be necessary, but it ensures that a good earth connection is obtained at the motor-board for the 150 mA braking current. Unfortunately, this link forms a “loop” with the possibility of hum induction. It can be dispensed with, if desired, so long as the constructor satisfies himself that the earth connection between the “black” tag of the 5-way tag-strip and the tape-deck chassis is adequate for the braking current. The link caused no trouble in the prototype.

The two 16-inch screened leads connected

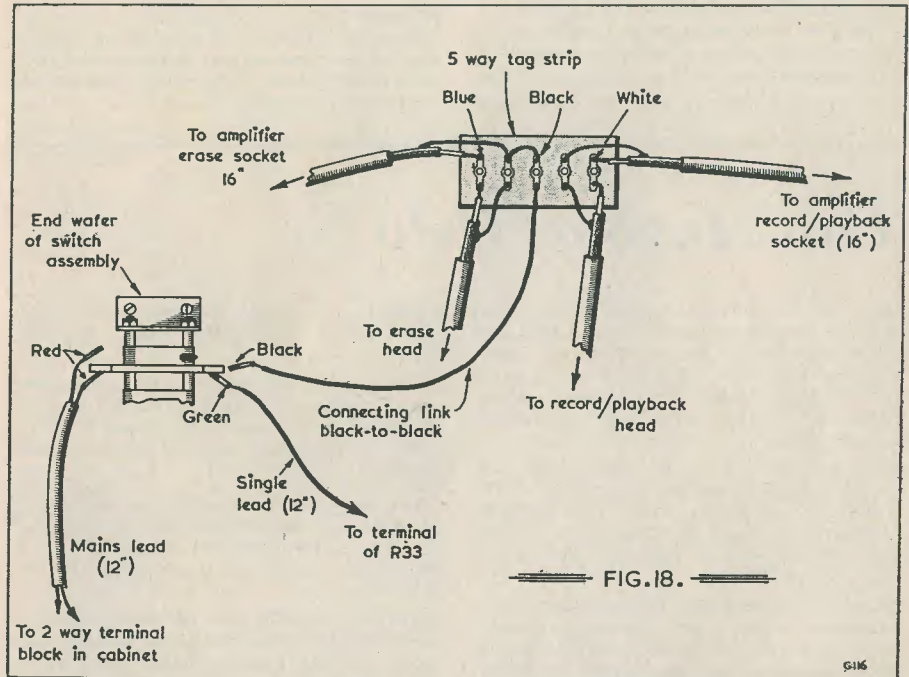

The Tape-Deck

The connections to the tape-deck itself are quite simple, and consist of various fly-leads, mostly terminated in plugs. These are illustrated in Fig. 18, which indicates also the recommended lengths for each lead.

Two points of some consequence are raised by this diagram. It will be noted, firstly, that the screening of the lead from the Record/Playback head is not earthed at the 5-way tag-strip. Instead, the screening is “carried on” to the amplifier chassis, at which point the earthing connection is finally made. This method of connection prevents the formation of “loops,” and possible hum induction.

Secondly, a link is fitted between the “black” tag of the switch wafer and the

to the 5-way tag-strip consist of conventional insulated single-screened cable.

Assembly

The process of assembling the recorder is quite simple and need take little time.

After the power pack, mains transformer, and loudspeaker have been mounted inside the cabinet, the tape-deck motor-board may be fitted. This should be put into position with a little care, in order to prevent the motors underneath from fouling the rectifier valve. If the constructor feels a little uncertain about the safety of this valve when the recorder is being assembled for the first time, it may be fitted in its socket after the tape-deck has been pushed up against the left

hand side of the cabinet. Access to the rectifier and the various plugs and sockets inside the cabinet can be obtained by tilting the tape-deck motor-board. This should be done by raising the right hand edge only.

For the first trial run it may prove helpful to keep the amplifier outside the cabinet. The connecting leads provided are sufficiently long to allow this to be done. Testing then proceeds in normal fashion.

After the amplifier has been checked, it next becomes necessary to reduce any hum pick-up that may be caused by the field around the mains transformer. The process of clearing up this trouble has already been detailed.

The final adjustment needed is that to the volume level indicator potentiometer, R20. This potentiometer is best adjusted at this stage by checking the volume level indication

in the meter as compared with the sound obtained from the speaker.

Sufficient volume level for recording is obtained when the volume from the loud-speaker is just adequate for comfortable listening under normal conditions. This is by no means intended to be an accurate statement, of course, but it is sufficient for the purpose of primarily adjusting R20. After the recorder has been in use for some time and the constructor has found, by experience, the best volume levels for good recording, he may then set R20 to its final, accurate, position.

A Radio Unit

A simple plug-in radio unit for the Paragon was under construction whilst these articles were being written. This will be described in next month's issue.

Can Anyone Help?

DEAR SIR,—As a regular reader may I appeal through your columns for any details and circuit diagram of Admiralty Pattern Cathode Ray and Rectifier Unit W3664A, Design A. I would gladly defray any expenses.—D. C. Glanville, 88 Ermine Road, Lewisham, London, S.E.13.

DEAR SIR,—Could any of your readers help me by supplying details and circuit of the Admiralty Responder Unit Type W4790, Model A? I should be most grateful for any help received.—R. G. Williams, 30 Prospect Park, Exeter, Devon.

DEAR SIR,—Could any fellow reader please inform me where I can obtain (purchase) a G.E.C. "Miniscope" Wobulator attachment, also a double beam attachment for same? I have unsuccessfully scoured the radio market and would appreciate any available assistance.—R. Taylor, Waterside Farm, Wharf Lane, Send, Woking, Surrey.

DEAR SIR,—Can I, as a regular reader, appeal through your excellent journal for any details on an ex-service Valve Tester? The only reference on the instrument is 10S/658 on the left-hand panel and 10S/556 on the right-hand panel.—Yours faithfully, E. Evans, 8 Wobaston Road, Fordhouses, Wolverhampton, Staffs.

DEAR SIR,—Can I, as a regular reader, appeal through your columns for any details or diagrams of the AM Unit R3118, Ref. No. 10DB/545 and Unit R-18/APS-3 NXS 11272 425CPR? I would gladly pay for any

literature or circuit diagrams.—J. Baldwin, The Dingle, Habberley Road, Bewdley, Worcs.

DEAR SIR,—Could any of your readers help me by kindly supplying circuit and conversion details of ex A, Set TR9H, please?—Yours truly, R. W. Jessup, 5 Holly Road, Ipswich, Suffolk.

DEAR SIR,—Could any fellow reader supply me with any information etc., on the PCR 6 valve Communication Receiver?—J. T. Saunders, 40 Granard Avenue, Putney, S.W.15.

DEAR SIR,—Could any of your readers be kind enough to let me know where I can obtain circuits, either on loan or on sale, of the following units: R9/APN/4; ID6/6B/APN4; BC-733/D; R3/ARR/2X; BC/229 and Control Box BC231?—Yours truly, E. W. Bithell, 61 Banbury Road, Stratford-on-Avon.

DEAR SIR,—Can any reader supply me with Manual or Service Sheet for Philips TV & Radio Console Model A 250 or the Mullard TV & Radio Console Model MTS 521? Any expense defrayed.—Yours truly, W. Akam, 203 Lyon Park Avenue, Wembley, Middx.

DEAR SIR,—May I, as a reader of the magazine, ask if anyone could supply me with a Service Sheet for a Derwent radio Model S1844? Willing to purchase.—J. H. Andrews, 43 Musgrave Road, Sheffield, 5.

AN ELECTRONIC RESISTANCE AND LEAKAGE TEST SET

by JAMES S. KENDALL, M.I.P.R.E.

THERE OFTEN OCCURS, IN THE WORKSHOP, the need for a meter which will carry out resistance measurements from a few ohms to a megohm or so, and yet do this with the application of a very low voltage. The instrument to be described here uses only a matter of 0.67V for resistance testing, and 67V for insulation measurement. These low potentials ensure that there is no danger of damaging a component when in use. Certainly, many multi-range meters may be adapted to read up to 10M Ω , or higher, with the aid of external power supplies—but usually the value of the external voltage needed is so high that it will exceed the working voltage rating of the component under test, and will cause damage either to insulation or by passing too much current through the component.

The circuit of the Test Set is by no means new or original, and is merely an old design used for audio work. Basically, it is the Schmitt phase-split circuit. The valves used are two of the Mullard DL96 battery output pentodes strapped as triodes. The common "cathode" resistor has a value of 1k Ω and is of the half-watt type, as is the grid stopper component, this having a value of 10k Ω . The primary function of this latter resistor is the suppression of any parasitic oscillations which may occur.

The overall accuracy of this Test Set is some $\pm 2\%$, which is considerably better than that of many compensated Ohm Meters. The balance and compensation of the unit are electronically isolated from the measuring circuit, thus ensuring the maximum accuracy. For resistance measurements the meter is set to full scale reading by the application of a voltage via a series resistor. One "standard" resistor has to be used for each resistance range; "standards" are also employed for the insulation ranges. Those used in the prototype are Dubilier 1% high stability types, and may, as in the original, be a series combination of 100 Ω , 900 Ω and 9k Ω ; alternatively, they can be switched separately, in which case the values will be 100 Ω , 1k Ω and 10k Ω .

The meter is one which has been specially designed for this instrument by Measuring Instruments (Pullin) Ltd., and it has two scales, one calibrated for the resistance ranges and the other for insulation.

The cabinet is in polished hardwood, and is both durable and pleasing to the eye. It is 2" deep at the front, 4" deep at the rear, and takes a metal panel 9" long by 8" deep. This panel is stove enamelled black and, as may be seen from the cover illustration, combines very well with the use of Panel-Signs transfers.

Fig. 1 gives the complete circuit of the instrument. There are two anode load resistors, which should be equal in value to within 2% or better; the use of high stability types is recommended here, as there will be less drift with these. The balance control is a 5k Ω potentiometer; a Dubilier carbon track type was used in the prototype as it proved smoother to handle than a wire-wound one. The latter type is, however, quite satisfactory for the sensitivity control (500 Ω).

The action of the balance control is to so adjust the anode loads that the same potential is present on each valve anode; when this condition obtains, there will be no current flow through the meter.

When the potential of the control grid of V1 is varied, this will in turn affect the potential at V1 anode, and current will flow through the meter; the sensitivity control is, in effect, a variable shunt which is so adjusted, on the resistance ranges, as to prevent the maximum current flow through the meter exceeding the full scale value.

The basic circuit for resistance measurements is shown in Fig. 2. The two resistors are such that the one between HT+ and the "standard" is exactly 100 times the value of the "standard." This means that if a resistor of equal value to the "standard" is connected in parallel with it, the deflection of the meter will fall to half scale (if previously set to full scale). On the other hand, if a resistor of 100 times the value of the "standard" is connected in parallel with it, the reading

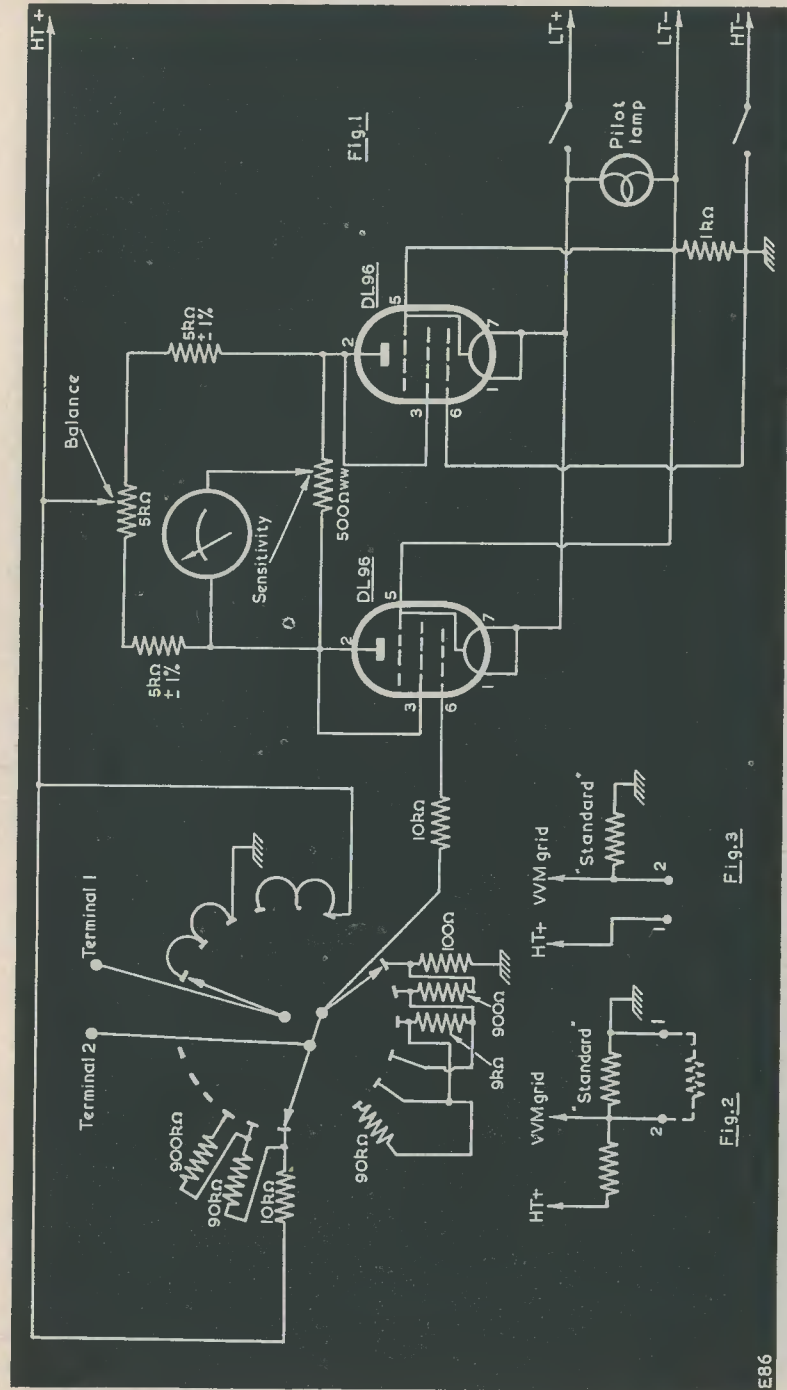


Fig. 1 shows the circuit of the complete instrument. Figs. 2 and 3 show respectively, the basic circuits for measurement of resistance and leakage.

Component List

- Set out for easy reference to Fig. 1
- 1 specially calibrated 100 μ A Pullin meter, Kendall and Mousley
 - 1 Instrument box and panel, Kendall and Mousley
 - 2 B7G valveholders, McMurdo
 - 2 DL96 valves, Mullard
 - 3 type K107 Knobs, Bulgin
 - 1 type D/430/RED/A Indicator Lamp, Bulgin
 - 1 type S/437 Switch, 3-pole 6-way, Bulgin
 - 1 type S300 Switch, 2-pole on-off, Bulgin
 - 1 500 Ω wire-wound potentiometer, Colvern
 - 1 5k Ω carbon potentiometer, Dubilier
 - 1 100 Ω $\frac{1}{2}$ W 1% high stability resistor, Dubilier
 - 1 900 Ω $\frac{1}{2}$ W 1% high stability resistor, Dubilier
 - 1 9k Ω $\frac{1}{2}$ W 1% high stability resistor, Dubilier
 - 1 10k Ω $\frac{1}{2}$ W 1% high stability resistor, Dubilier
 - 2 90k Ω $\frac{1}{2}$ W 1% high stability resistor, Dubilier
 - 1 900k Ω $\frac{1}{2}$ W 1% high stability resistor, Dubilier
 - 2 5k Ω $\frac{1}{2}$ W 1% high stability resistor, Dubilier
 - 1 10k Ω $\frac{1}{2}$ W 20% high stability resistor, Dubilier
 - 1 1k Ω $\frac{1}{2}$ W 20% high stability resistor, Dubilier
 - 2 Terminals, Belling-Lee
 - 1 B114 Battery, Every-Ready
 - 1 Panel-Signs, either Set 1 or Set 2.


will drop in value by approx. one-hundredth.

The scale of the special meter—obtainable from Kendall and Mousley—is calibrated from 0.05 to 100, and in use the reading

applied voltage of 67.5. The effect is to connect a resistance of unknown value between HT+ and the top end of the "standard"; the voltage dropped across the "stand-

Fig. 4

Range	min	centre	max
1	5 Ω	100 Ω	10R Ω
2	50 Ω	1R	100R Ω
3	500 Ω	10R Ω	1M Ω
4	100R	10M Ω	10M Ω
5	1M Ω	100M	100M
6	10M Ω	1000M	1000M

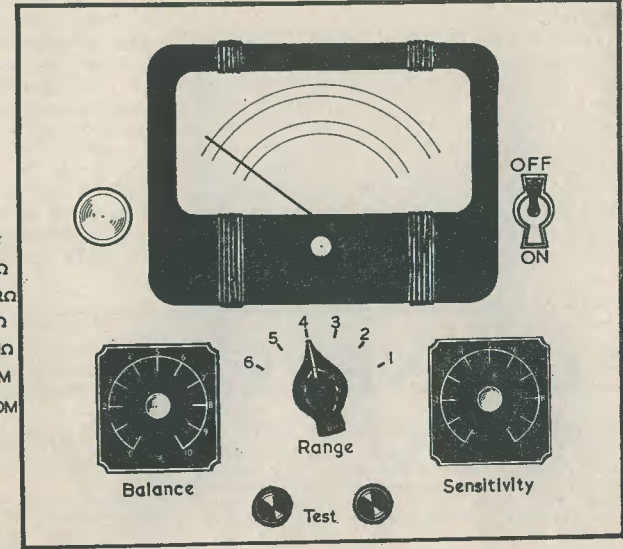

E87

indicated is multiplied by the value of the "standard" on the particular range being employed. Thus, a reading of 0.05 with a "standard" of 100 Ω will give a value of 50; a reading of 50 and a "standard" of 10,000 Ω will give a value of 500k Ω ; and so on.

Fig. 3 shows the basic circuit employed for the measurement of insulation, with an "ard" is then "measured" and read off the scale as the value of the insulation resistance. As on the resistance ranges, an "unknown" of 100 times the value of the "standard" will result in a full scale reading on the meter; doubling the value of the "unknown" to 200 times the "standard" will result in the voltage drop across the latter being halved,

and the meter will read half scale. With a "standard" of $10,000\Omega$ and a full scale reading, the "unknown" will be $100 \times 10,000 = 1M\Omega$; with the same "standard" and the smallest scale calibration of one-hundredth FSD, the "unknown" will be $100M\Omega$.

There is little that need be said about the construction. In the original the job was split into two sections, the panel holding the majority of components, with a small chassis on which were mounted the valves. Kendall and Mousley will supply the panel ready drilled and finished in stoved black enamel; alternatively, they can supply a plain panel for readers who wish to employ a layout of their own choosing. In the latter case, it is suggested that readers might very

well use Panl crackle paint to obtain a finish in keeping with other test gear.

The initial setting-up of the instrument is achieved as follows. Turn the range selector switch to one of the insulation ranges, and set the sensitivity control to zero. Switch on, then increase the sensitivity until the meter pointer moves off the zero mark. Next, set the balance control to the position where the pointer is on zero. Repeat the foregoing procedure until the sensitivity control is at its maximum with the pointer set on zero. The instrument is now balanced.

Next, set the sensitivity control at zero, switch to one of the ohms ranges, and then increase the sensitivity until the pointer is at full scale (zero ohms). The instrument is now ready for use.

CLUB NEWS

Details for insertion in this section should reach us not later than the 8th month before publication.

AMATEUR TAPE RECORDING SOCIETY

Asst. Secretary, G. A. Widdup, 92 Halifax Road, Rochdale, Lancs. Are you building the tape recorder now being described in this magazine, or do you already possess one? If so, why not join the above Society? A cordial welcome awaits you. All enquiries to Asst. Secretary.

BIRMINGHAM & DISTRICT SHORT WAVE SOCIETY

Hon. Secretary, R. Yates, 28 Daimler Road, Yardley Wood, Birmingham, 14. The Club have now acquired new headquarters at the YMCA, 20 Soho Road, Hockley, Birmingham, 19, at which site it is proposed to erect and operate the club transmitter. Meetings are held on the second Monday of each month at 7.45 p.m., and new members are welcome. Forthcoming subjects include: March: "Power Supplies," by H. Burdett; April: the Club Station; May: "Aerials," by T. Burton.

THE EAST KENT RADIO SOCIETY

Hon. Secretary, D. Williams, "Llandogo," Bridge, Nr. Canterbury, Kent. The next meeting will take place on 15th March at 8 p.m. Meeting place "The Two Brothers," Northgate Street, Canterbury. Meetings are held fortnightly. The Society has varied interests including transmitting, television, tape recording, short wave listening, radio control, VHF, and many other subjects connected with radio. A cup is presented to the member who constructs the best item of equipment during the year. Frequent lectures, sales, raffles, etc., have been given and are again being arranged this year. The Society welcomes new members and also visitors to the district.

ACTON, BRENTFORD & CHISWICK RADIO CLUB

Secretary, R. G. Hindes, 51 Rushall Avenue, Bedford Park, Chiswick, W.4. At the A.G.M. on 25th January, W. Dyer (G3GEH) was elected President, the Secretary, R. G. Hindes (G3GIM), and Treasurer, R. Baker (G3IRB), were re-elected. The Committee for 1955 is G5LQ, G3EJT and G3JVL. The Treasurer reported a notable improvement in the Club's financial position. The Club is now active on 160 metres phone each Tuesday (G3IIU).

CLIFTON AMATEUR RADIO SOCIETY

Plans have now been made for this summer's outdoor events and it is proposed to hold three D.F. competitions and a portable transmitting field day. The transmitting

field day is a new venture for this Society and if well supported will become an annual event. All these activities will take place in the vicinity of Farnborough, Kent.

Programme for March: 4th, Junk Sale; 11th and 25th, Constructional Evenings; 18th, "The Voyage of the M.V. Ariès," by E. Skelton (G3JOQ).

New members are always welcome and details of membership can be obtained upon application to the Hon. Secretary.

Meetings are held every Friday at 7.30 p.m. at 225 New Cross Road, London, S.E.14.

Hon. Secretary, C. H. Bullivant (G3DIC), 25 St. Fillans Road, Catford, S.E.6.

ROMFORD AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec., N. Miller, 55 Kingston Road, Romford. At the recent AGM the officers elected were Chairman, F. Simmons (G2FWJ); Treasurer, E. Boxer (G3AUG); Hon. Sec., N. Miller, and a committee consisting of G3EBF, G2BVN and G. Creevey.

Future lectures include "Transistors," by J. Missen, B.Sc., of the G.E.C. Research Laboratories, on 22nd March, and TVI "Suppression," by Louis Varney, A.M.I.E.E. (G5RV), on 12th April.

Work has commenced on NFD gear and a workshop is being fitted up at the Club headquarters.

New members and visitors will be welcomed at the weekly meetings held on Tuesdays at 8.15 p.m. at RAFA House, 18 Carlton Road, Romford.

THE SLADE RADIO SOCIETY

Headquarters: The Church House, High Street, Erdington, Birmingham, 23.

4th March, 7.30 p.m., special meeting to consider adoption of amendments to Society's Rules; 7.45 p.m., Display of members' apparatus.

18th March, Lecture by Mr. W. E. Merrill (Member).

Full particulars of the Society and its activities may be obtained from the Honorary Secretary, Mr. C. N. Smart, 110 Woolmore Road, Erdington, Birmingham, 23. Visitors to the Society's meetings, which commence at 7.45 p.m. prompt, are cordially welcome.

The Club Station at the Church House is now completed, and is open every day of the week for the use of members. Transmitting and receiving equipment is being installed, constructional facilities are available, and Morse and theory classes are being arranged.

THE G3XT CHASSIS

THE MAJORITY OF CONSTRUCTORS TAKE IT for granted that every receiver should be built on a flat metal chassis. This has now been standard practice for so many years that no one seems to think of improving upon it!


In an attempt to get out of this rut, I have been experimenting for some time with less conventional types of chassis, and have at last evolved a design which offers a number of advantages over the ordinary standard arrangement.

The G3XT chassis is most suitable for the smaller class of receiver, employing one to four valves. It is cheap, light, rigid, easily constructed, readily adaptable to any sort of box

Easy Construction

Any constructor who is capable of tackling the simplest metal-working should find no difficulty in making this chassis. It is fashioned out of a single, flat, rectangular sheet of suitable metal (aluminium, mild steel, etc.) by simply bending it to the shape indicated in Fig. 1. The exact angles and dimensions can, of course, be varied to suit the individual requirements of any particular set. (As a rough guide, a development sheet $15" \times 8"$ will bend into a finished chassis about $7" \times 8"$).

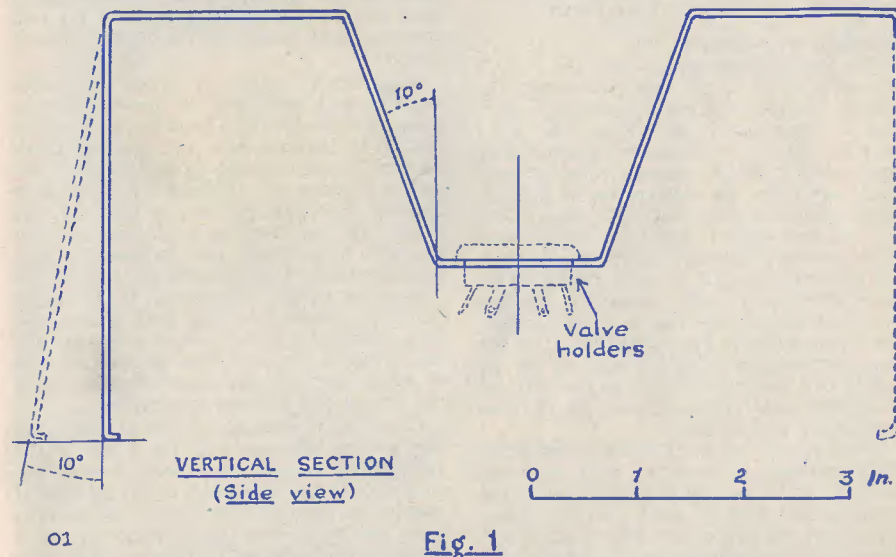For example, the front panel (which is separate from the chassis) can be either a vertical or sloping type. There is a good deal to be said for letting the panel have a



or cabinet, and specially designed to give maximum accessibility of components and wiring.

The fact that all the parts of a set built on this special chassis are so easily "get-at-able" is a great asset, not only in the initial construction and wiring but also in testing, fault-tracing and maintenance. A faulty component can be replaced quickly and easily with a minimum of disturbance to the rest of the set.

backward slant of a few degrees, as it makes for much easier dial-reading, when the set is on a table below eye-level. A sloping panel is difficult to fit to the normal standard chassis, but dead easy in the case of the G3XT chassis; all you have to do is to adjust the angle of the front portion to suit the desired slant of the control-panel.

The various bends in the chassis are all parallel to one another and to the front and rear edges of the metal sheet. They can be

formed very easily over the straight edge of a hard piece of wood or a metal right-angle girder. The bends greatly improve the rigidity of the chassis, in much the same way as the corrugations lend strength to a sheet of corrugated iron. The metal can therefore be of thinner gauge than would be needed for an ordinary flat type of chassis.

Small steel brackets, obtainable for a few pence at any ironmongers, can be used if desired to strengthen the chassis and improve rigidity still further. A pair of the metal handles found on many ex-Government surplus sets can be mounted across the ends of the valve trough, to improve rigidity and at the same time serve as lifting-handles for moving the chassis about. They also give a pleasingly professional-looking finish to the job.

The larger holes, such as those for the valveholders, can be cut or drilled before bending the chassis (i.e. while the metal sheet is still in its original flat state) if desired. But although this makes the drilling easier, the holes naturally tend to weaken the metal and make it less easy to bend neatly.

Accessible Valveholders

The outstanding feature of the G3XT chassis is the "trough" which traverses the central part of the chassis from side to side. This accommodates the valves and their holders. When the chassis is turned upside down, this "valley" naturally becomes a "hill," with the valveholders on its "crest." Their numerous soldering-tags (usually 7, 8 or 9 to each holder, involving about three dozen soldered connections in the average set) are thus brought up to a height which places them in a readily accessible position for easy soldering (see Fig. 2). Fault-tracing and testing are also greatly facilitated by the valve connections being so easy to get at, instead of being tucked away in odd corners at under-chassis level amidst a mass of other components and wiring!

The majority of the smaller components (fixed resistors and condensers, for example) are also carried on this trough, those in the anode circuits slanting away from the valveholders on one side of the central ridge, and those in the cathode circuits on the opposite side. Grid condensers and resistors, and midget IF transformers, can be carried on the flat part of the trough between valveholders.

The metal sides of the valve trough form a double screen which helps the stability of the set and reduces any risk of unwanted interaction between components in different parts of the circuit.

Simplified Layout

This chassis makes the task of planning a layout very simple indeed, as most of the

components can occupy the same relative positions as their corresponding symbols occupy in the theoretical circuit diagram! This would be difficult to achieve on an ordinary flat chassis without making the whole set unduly large and unwieldy.

The details of the layout will depend, of course, on the circuit and components used, so only a general idea can be given here. The tuned-circuit components (coils, variable condensers, etc.) will of course be located in the front section of the chassis. Valveholders and the smaller components associated with them will be carried on the trough, with suitable tag-boards for mounting the fixed resistors, etc. Output transformer, loud-speaker jack, etc., can best be located in the rear section of the chassis.

It is strongly advisable, for several reasons, to use a separate power pack with any receiver built on the G3XT chassis. (Personally, I think it is always better to have the power pack separate in every set.) The power pack chassis can be an ordinary standard type of fairly small dimensions. It need not be in a separate cabinet; the two chassis can be housed in the same cabinet if desired.

If, however, the set is to be used occasionally as a portable, or *non-built-in* car radio, it is far better to have the power pack in a small separate case, with a short multi-core cable terminating in safety plug and socket to carry the HT and LT supplies to the set. For portable use, or in a car, the mains unit can then be unplugged and put aside, its place being taken temporarily by a small car-radio type power pack running off a 6-volt or 12-volt car battery. If the output circuit of this pack is fitted with a cable and plug identical to that used for linking the mains unit to the set, two alternative sources of supply are instantly interchangeable without having to make any alterations.

One word of warning! Some of the wiring connections will pass over the bends of the valveholder trough. Insulated connecting-wire should be used; but as an additional precaution against short-circuit to chassis from any bare wires (such as the wire ends of fixed resistors), it is advisable to stick a length of insulating tape along the bends on the underside of the chassis.


Limitations!

This chassis, like everything else, has its limitations! I have used it successfully for about ten different sets up to the time of writing; but all of these have been relatively small ones, employing one to four valves in straight or superhet circuits of fairly simple type. I would not recommend the G3XT chassis for more elaborate sets, such as

complicated communication receivers. (There is, however, some scope for experiment in this field with the basic principle of a bent or corrugated type of chassis as opposed to the usual flat type.)

plan in every detail. Being such an unconventional type of chassis, it does not lend itself to the average orthodox layout designed for an ordinary flat chassis.

In all other respects, I have found this

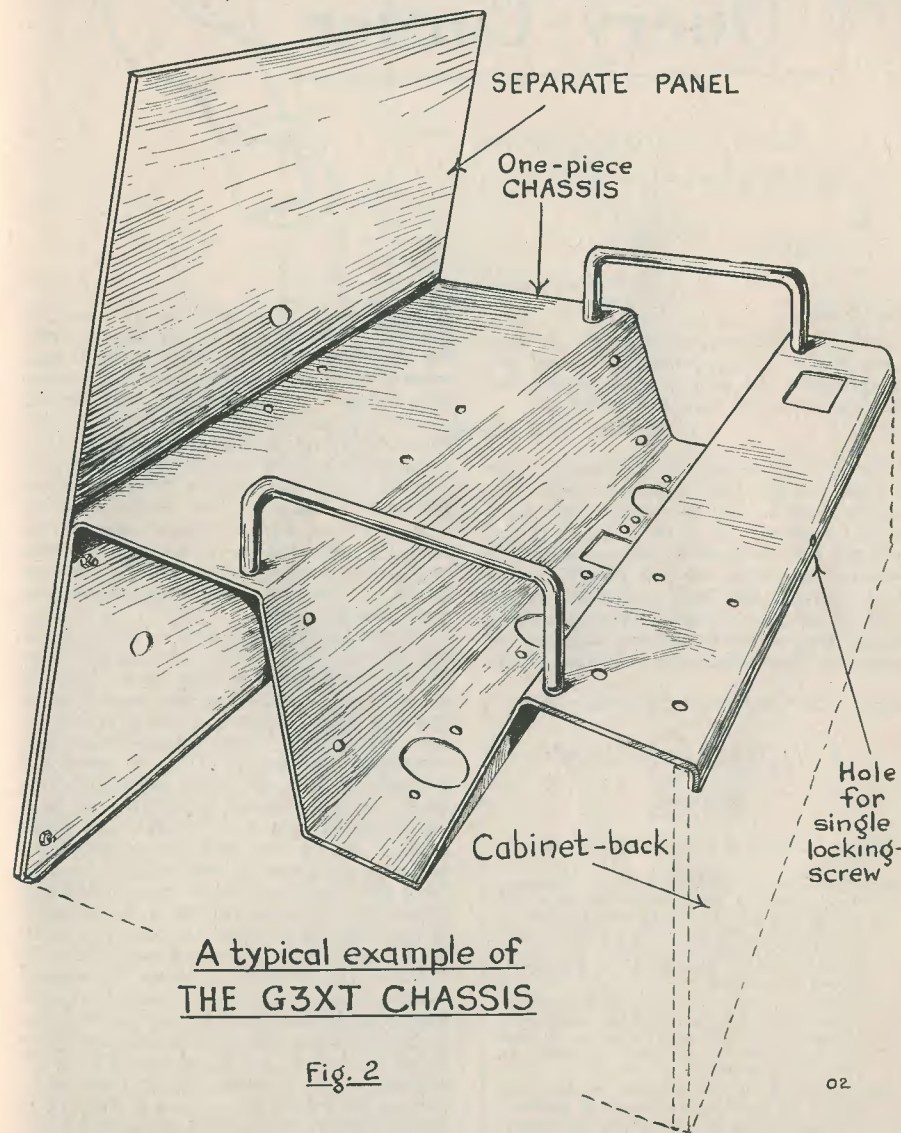

Finally, it should be borne in mind that this chassis is not suitable for beginners who find it necessary to follow a published layout

novel chassis entirely free from snags, and I would be very reluctant to return to the ordinary standard type!

Query Corner

A Radio Constructor Service for Readers

Spot Wobble

I find the scanning lines on my 17" television tube very distracting and would like to experiment with some form of spot wobble. Can you suggest a suitable circuit?

L. Mayhew, York

The idea of employing an elliptical spot in a cathode ray tube is by no means new. Such a spot having its major axis in the vertical direction could be adjusted in size until the gaps between the scanning lines of a television picture are just filled in. This would prevent the illusion that the picture is being viewed through a venetian blind, and, providing the horizontal width of the spot is not increased, the definition of the

picture would not be impaired. However, to design a tube having a spot size which meets the required specification is not practical, and some other means must be used to fill in the gaps between the scanning lines. The method usually adopted is known as spot wobble, and consists of vibrating the scanning beam of the picture tube in the vertical direction, whilst it is being deflected in the usual manner to form the raster. The amplitude of the vibration is adjusted so that the gaps between the lines are just filled in. It is important that no overlap occurs, as this has the effect of producing another line pattern along the overlapping portions.

This additional movement or vibration of the spot is achieved by placing an extra pair of small deflector coils on the neck of the tube and applying a sine wave current to them. The frequency of vibration is made very high when compared with the line repetition frequency. This is necessary because a low frequency would merely cause the spot to traverse the tube face in a wavy line of sine wave form. The upper limit is set by the difficulty of providing adequate deflection at very high frequencies from the small amount of power which is economically available from a normal type of receiving valve. The minimum frequency used with a sharply focused spot is around 8 Mc/s, and a value of about 12 Mc/s is often chosen. Some adjustment of the frequency is usually required to prevent a harmonic of the spot wobble frequency from being picked up on either the RF or IF channels of the receiver, thus causing a beat pattern on the screen. There is little point in adding spot wobble to a receiver in which the overall focus is poor or the interlace bad. Unless both these features are above reproach the addition of the wobbling oscillator will only further degrade the picture definition.

Query Corner

RULES

- (1) A nominal fee of 2/6 will be made for each query.
- (2) Queries on any subject relating to technical radio matters will be accepted, though it will not be possible to provide complete circuit diagrams for the more complex receivers, transmitters and the like. Queries relating to ex-W.D. surplus or commercial equipment cannot be accepted.
- (3) Complete circuits of equipment may be submitted to us before construction is commenced. This will ensure that component values are correct, and that the circuit is theoretically sound.
- (4) All queries will receive critical scrutiny and replies will be as comprehensive as possible.
- (5) Correspondence to be addressed to "Query Corner," Radio Constructor, 57 Maida Vale, Paddington, London, W.9.
- (6) A selection of those queries with a more general interest will be reproduced in these pages each month.

The complete circuit of the spot wobble oscillator is shown in Fig. 1. A single high slope pentode is employed in a conventional

cotton. They are then bent round the neck of the tube with the short side parallel to its axis. Having thus formed the coils they are


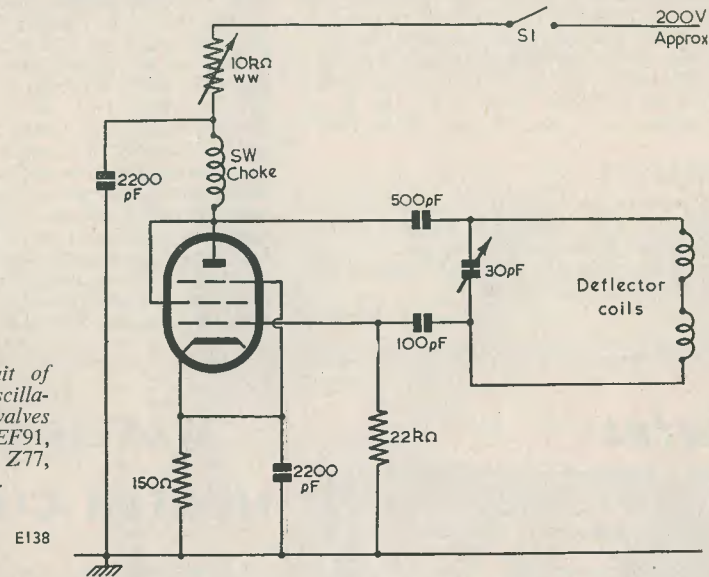


Fig. 1. Circuit of spot wobble oscillator. Suitable valves are EF50, EF91, EF80, 6AM6, Z77, VR91, etc.

circuit. In order to obtain the highest degree of efficiency the deflector coils are made part of the oscillatory circuit, the frequency of oscillation being adjusted by means of a 3-30pF Philips concentric trimmer. The amplitude of oscillation is varied by controlling the HT supply voltage to the valve by means of a series resistor. Bias for the valve is provided by a combination of grid leak and cathode resistors; an arrangement which has the advantage that should the valve cease to oscillate because of some circuit fault it will not be ruined by passing excessive current. When setting up the wobbler it is important to first ensure that the tube focus is set to optimum. For this purpose the HT switch S1 is provided to cut the oscillator out of circuit to permit of accurate setting of the focus control.

The only components which must be made are the small saddle type deflector coils. These are positioned as close behind the main deflector coils as possible, and as space on the tube neck is limited the width of the coils has been restricted to 1-in. Reduction in the width will decrease the sensitivity of the coils and may result in insufficient deflection. Each coil consists of five turns of 26 swg enamelled copper wire wound on a former 1-in by 1½-in. Each coil is carefully slid off the former and the turns tied together with

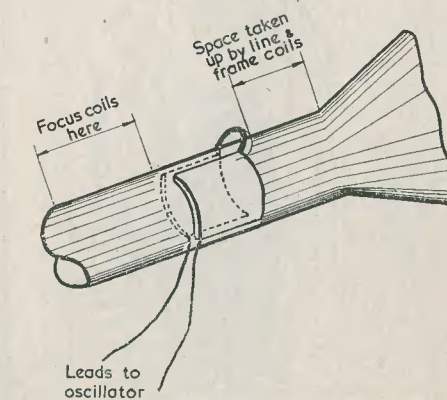dipped in wax or coated with glue and allowed to harden. The coils are then connected in series so that the direction of turns on each is the same, that is, with the magnetic fields assisting each other. Fig. 2 shows the



E139

Fig. 2. Shows method of bending deflector coils around tube neck.

manner in which they are finally positioned on the tube neck, where they are held in position by two turns of insulating tape.

The leads connecting the coils to the oscillator form a part of the oscillatory circuit and should be kept as short as possible, preferably less than 6 in. in length. An H.T. supply voltage of 200 is adequate if a valve of the EF80 class is employed. Should an EF50 or EF91 be used it will be found preferable to increase the voltage to 250.

Glow in CRT

I recently purchased a 14" television tube and am a little alarmed to notice a pinkish glow which appears within the neck when the tube is in operation. Does this indicate that the tube has a poor vacuum?

J. Blackley, Bradford

Should the vacuum of a CRT become slightly impaired a very faint light blue glow may be detected coming from within the electron gun assembly. This glow will completely disappear when the tube is biased off, so that no beam current flows, and it will gradually reappear and increase in intensity as the bias is reduced. If the tube is slightly gassy the focus may also become less sharp. The important point to notice is that the glow appears from within the gun, actually right in the path of the main electron stream. If, however, the glow only appears on some outer part of the gun, or on ceramic or mica supports, then this is simply fluorescence caused by bombardment of the glowing part by stray high velocity electrons. This form of glow varies in colour from blue to light pink, and is a phenomenon which in no way detracts from the normal life of the tube.

Rufus



"What clot crossed the fast-forward belt on my tape-recorder!"

WATCH YOUR HEATER CURRENT

A possible but little-known cause of premature cathode ray tube failure is the over-running of the heater with consequent undue rise of cathode temperature. Cases have been known, in which such an increase has impaired the interelectrode insulation of the tube, ultimately resulting in either a heater-to-cathode or grid-to-cathode short.

Replacing the tube will, of course, form a temporary cure of the trouble, but unless the cause has been removed the replacement tube may in due course fail in a similar manner.

Over-running of the heater can be the result of many possible causes. The use of the receiver on an incorrect mains tapping is one obvious cause, but in those types of receivers designed for series operation there is another possibility which should be checked. Such receivers almost invariably have a surge limiting resistor in series with the heater chain, and failure of this component may result in a short circuit with consequent rise of voltage throughout the chain.

It is therefore highly advisable to check the cathode ray tube heater voltage in a parallel operated receiver, or in the case of a set in which the valves and tube are series operated, to check the heater current, when replacing a faulty tube in a receiver, in order to guard against a repetition of the trouble.

It is recommended that the heater current of a series connected tube should be within 5 per cent of its nominal, and for a parallel connected heater the voltage should be within 7 per cent of the nominal. Measurements should be made with the nominal supply voltage connected to the appropriate tap.

(Courtesy Mullard Outlook)

Let's Get Started 21:

VALVE VOLTMETERS

By A. P. BLACKBURN

HAVING CONSIDERED VERY BRIEFLY SOME of the sources of signals used in receiver and amplifier testing last month, the next step is to detect this signal at any point in the system under test, and to estimate what the system has effected. Don't be put off by the use of such a pedantic word as system, since it only means "receiver," "amplifier" or "transmitter" in a shorthand form.

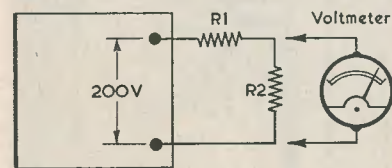


FIG. 1. G123

In order to carry out this estimate, it is necessary to be able to measure, with a reasonable degree of accuracy, the parts of the signal. It may, of course, be necessary to know the frequency, or the amplitude, at that point in the circuit.

First of all, however, we shall attempt the measurement of amplitude, or more recognisably, voltage.

Voltage

The methods for normal measurement of AC and DC voltages are well known. A previous article in this series* was, in fact, devoted to this very subject. In that article it was mentioned that the impedance of the source of voltage to be measured had some bearing on the accuracy of the reading. The time has now come when a closer look into this matter would be useful.

Fig. 1 shows a power supply which produces 200V at its terminals. Now if we wanted to step down this voltage to 100V, R₁ and R₂ must be of equal value. For a start we will make them 100kΩ each. Having rigged this up, naturally we just check the voltage by applying the voltmeter to R₂

as shown in the figure. The voltmeter has a sensitivity of 1,000Ω/volt.

Incredibly, the voltmeter reads 66.7 volt, and not 100, as we had expected. The reason is, of course, that the voltmeter on the 100V range has a resistance of 100kΩ. Now when it is connected in parallel with R₂, which also has a resistance of 100kΩ, the resultant resistance of R₂ and the voltmeter is 50kΩ. The actual voltage across the voltmeter (and R₂) is:

$$\frac{50}{100+50} \times 200 = 66.7 \text{ volts.}$$

If the voltmeter had a sensitivity of 10,000Ω/volt, the reading would be 95.2 volts, which certainly is nearer to the 100 volts that we should expect, but the error is still nearly 5%.

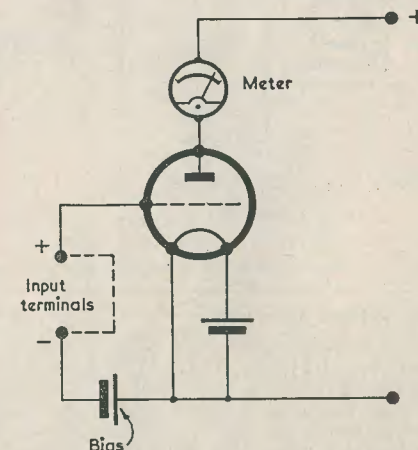



FIG. 2. SIMPLEST VALVE VOLTMETER G124

We can see, then, that the higher the resistance of the voltmeter (in the latter case it was 1MΩ on the 100 volt range) the more accurate becomes the reading. It is not

* P.538, April 1954

possible, however, to go on increasing the sensitivity of the meter indefinitely without increasing its cost and delicacy. Our first meter was a 1mA movement (1,000Ω/volt) and the latter 100μA (10,000Ω/volt).

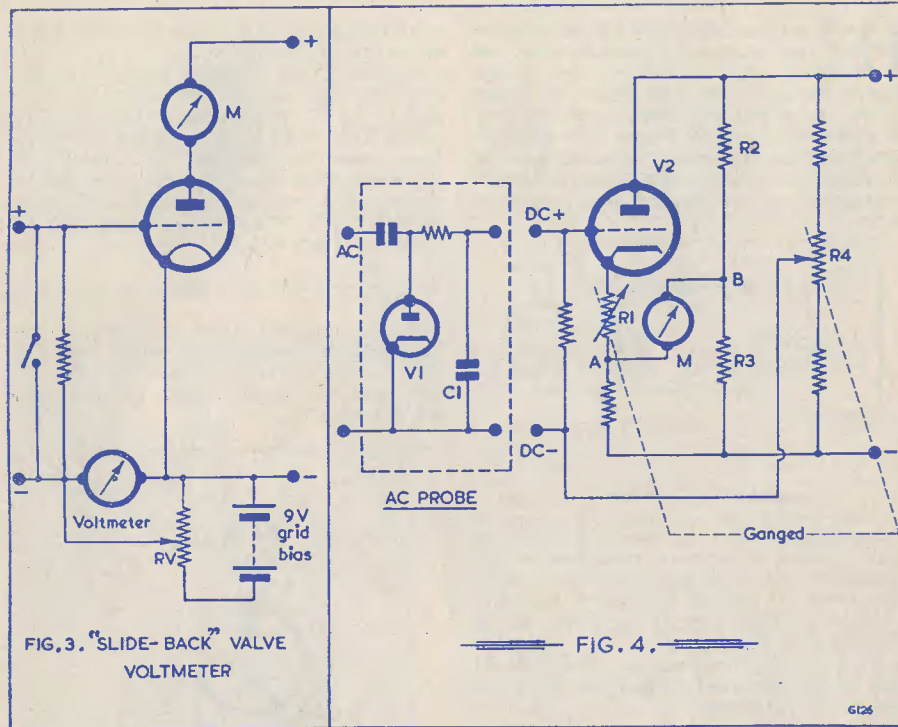Ideally, we want a meter of infinite impedance (and minimum cost) so that it does not load the source at all. The nearest practical approach to this is the valve voltmeter.



The Valve Voltmeter

The basic idea behind all valve voltmeters is shown in Fig. 2. The grid bias battery voltage has such a value that the current through the valve is almost entirely cut off. The meter in the anode circuit, therefore, reads almost zero when the input terminals are connected together. Connecting the input terminals to an unknown positive voltage will cause the current through the valve to increase. The anode current meter will take up some new reading, and if the scale of the meter has been calibrated, a measure of the unknown voltage is obtained.

The input resistance of the voltmeter is the resistance of the valve base, between the grid and cathode pins, and may have a

value of hundreds of megohms. Such a high resistance as this, placed across R₂ in Fig. 1, would have such a small effect upon the circuit that the reading it would give would be accurate.

The simple circuit of Fig 2 has many disadvantages, however. One is that the meter will not read zero unless the valve is exactly at the bias voltage required for anode current cut-off. The non-linearity of the

V_g/I_a characteristic would make the calibration very non-linear, and at measured voltages below 2V the instrument would be very insensitive. Changes in the valve characteristics would invalidate the calibration and frequent re-calibration would be necessary.

Various methods have been adopted to overcome these disadvantages. One is to use a value of bias that would bring the valve to the straight portion of the V_g/I_a characteristic and then back off the standing current reading of the meter with a battery. This, however, does not overcome the objection that the calibration depends upon the valve characteristics.

The Slide-back VVM

The improvement to be had from the slide-back principle is that the circuit is arranged in such a way as to enable comparison to be made between the unknown voltage and a known one. A circuit is shown in Fig. 3.

The principle is much as before, but with one important difference. To begin with, the anode current is adjusted to a very low value by adjustment of the bias potentiometer, R_v. The anode current should not exceed 1μA, which means that M should be a 50μA movement. It will be noticed that an ordinary voltmeter has been introduced to measure the bias voltage. When the valve has been set almost to cut-off, the reading of this voltmeter should be noted. The unknown voltage is now connected to the input terminals and the anode current will increase, as before. The bias is again adjusted until the anode current meter reads 1μA again. The new bias voltage is noted.

As the valve has been brought back to its original condition by an adjustment of bias voltage, this voltage must be equal to the applied voltage. Subtracting the two bias readings, therefore, gives us the value of the unknown voltage. Compared to the far more elegant direct-reading technique, this method seems cumbersome and complex, but it has the saving grace that the accuracy is unaffected by valve characteristics. The purpose of the switch on the grid circuit is to short the grid resistor in order that no hum pick-up or other effects upset the initial setting of the anode current.

This circuit has another important advantage over Fig. 1. It can be used to measure AC voltages. This facility comes about because the valve is biased well back, beyond the "knee" of the I_a/V_g curve. In this condition, rectification of the AC grid voltage occurs, so producing a change in the mean anode current.

As in the DC case, the anode current is adjusted to a very small value. The AC signal is then applied and the bias re-adjusted until the meter reads the initial value once again. The difference in grid voltage readings is then equal to the peak value of the applied voltage.

If two meters are not available, it is possible to arrange switching to transfer the anode current meter to the grid circuit, where, with suitable multipliers, it may be used to measure the grid voltage. Alternatively, the potentiometer controlling the grid bias voltage could be calibrated in voltage, and the calibration checked occasionally to ensure that the battery had not run down.

The slide-back type of valve voltmeter is not very popular today, for a number of

reasons. It requires a very sensitive meter for the anode circuit, with a full scale deflection of no more than 50μA, and capable of reading 0.5μA. Such a luxury is not to be found, of course, in every radio amateur's shack.

Its great advantage is that the calibration does not depend on valve characteristics, etc., and the "reading" meter need not be monopolised by the instrument.

Direct Reading Types

In more general use today are the many forms of direct-reading valve voltmeters. These are used like any normal multi-range meter—just apply the volts and read off the result on a meter. The first type described above is direct-reading, but is rather too crude for serious work.

One type of direct-reading instrument is shown in Fig. 4. It is split into two parts. When an AC measurement is required, the "probe" is used. The diode V₁ rectifies the AC and the valve V₂ operates the indicating meter. Range changing is carried out by switching the value of R₁. This resistor produces negative feedback, and its value determines the gain of the valve, and therefore the sensitivity.

The resistance chain R₂ R₃ is used to set the zero on the meter. In the "no signal" condition, the voltage at point A is arranged to be the same as at point B. The meter will therefore read zero. Fine zero adjustment is made by setting the grid potential with the potentiometer R₄. It is also necessary to switch the grid potential as the range is changed, because a change in R₁ produces a change in the standing potential at point A. In order to get a zero reading on the meter, the potential at point B must be changed also. The grid to cathode potential is also changed with R₁, so the potentiometer is arranged to be switched simultaneously with R₁ to maintain the zero from range to range.

This instrument may be used on either AC or DC. For AC measurements, the diode probe is connected. The probe is normally made as small as possible, with the input lead either very short, or in the form of a rigid prod. If care is taken in the construction of this probe, voltage readings can be obtained up to 10 Mc/s or more with fair accuracy. The R-C network associated with the diode is a filter for removing any residual AC after rectification.

The actual operation is quite straightforward. When a DC signal is applied to the grid, the anode current changes. This change produces a change in potential at point A. As point B is fixed on any particular range, the meter will be deflected by the difference in potential between A and B.

Although this type of valve voltmeter can be quite sensitive, one limitation to its sensitivity is the zero drift.

resistance, of equal value to the "resistance" of V_1 . The operation of the circuit is otherwise the same as Fig. 4.

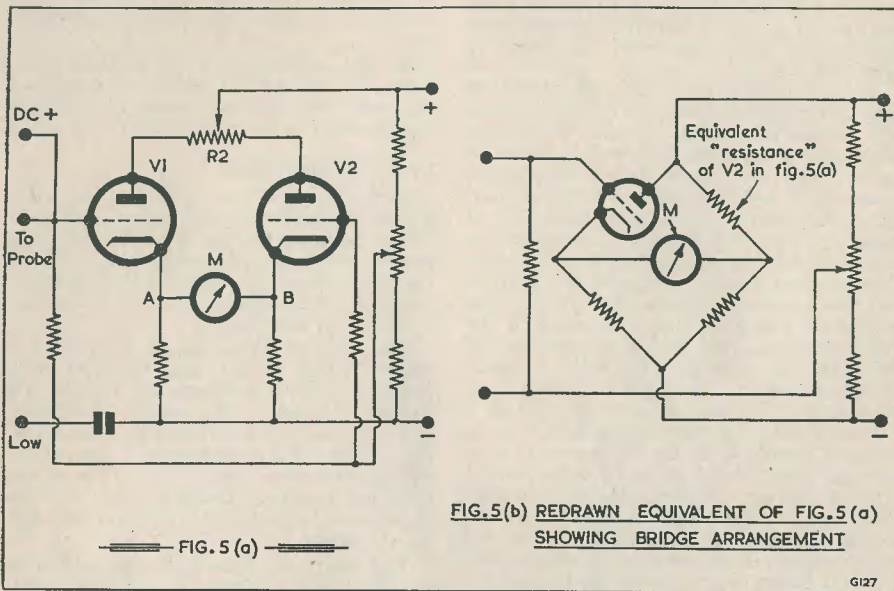


FIG. 5(b) REDRAWN EQUIVALENT OF FIG. 5(a) SHOWING BRIDGE ARRANGEMENT

The Bridge VVM

The "bridge" circuit has been developed in an attempt to obtain a stable zero. Drift in the zero setting is caused by small changes in the valve. If, for example, a small change in the current flowing through the valve occur-

If the circuit of Fig. 5b were used, there would be no improvement, from the zero drift point of view, on the circuit of Fig. 4. If, however, a valve is used in place of R_1 , the two valves would tend to heat up together and the change in valve characteristics with temperature would be minimised. You will notice particularly that no signal is applied to V_2 —it is used purely as a "resistance."

Further improvement can be brought about by making V_1 and V_2 a double triode. Both valves would then be under very similar thermal conditions. Zero setting is achieved by the use of R_2 . Dissimilarity between V_1 and V_2 is cancelled by varying the current flowing through the valves by use of this control. The potentials of the points A and B in Fig. 5a can be made equal, giving zero reading of the meter.

Ranges

There are many ways of range setting in valve voltmeter design. One of the most popular is to arrange a potential divider to deliver a certain fraction of the unknown voltage to the valve voltmeter. This is shown in Fig. 6. It can be seen that it resembles a volume control, except that the steps are fixed.

When measuring DC, this type of range setting has the advantage that only one

switch is required. It is not necessary to alter grid potentials, etc., as with the negative feedback arrangement in Fig. 4.

In the measurement of AC however, the diode probe will be connected. A strange feature of the diode is that if the heater is switched on, and a high resistance connected between anode and cathode, a small negative potential will appear at the anode, despite the absence of any external source of voltages. We will not try to find any explanation for this phenomenon at the moment, but its effect on the valve voltmeter is obvious. The instrument will read this small DC voltage. But why not adjust the zero set? That, of course, is the answer, but if a network like Fig. 6 is in use, changing the

range will change the value of the diode "contact potential," as it is called, applied to the voltmeter.

It is necessary, therefore, to gang another switch to this one, and automatically reset the zero when the range is changed.

There is still much that could be said about valve voltmeters. Their accuracy, the strange effects they can have on RF circuits, their many uses in measuring AVC voltages—the list is a long one.

And, of course, the range of test gear only begins with valve voltmeters. It includes a great number of other instruments, some highly specialised, and these, too, will be covered in succeeding articles.

PRINCESS ROYAL TO OPEN NORTHERN RADIO SHOW

H.R.H. The Princess Royal has consented to open the Northern Radio Show, City Hall, Manchester, on Wednesday 4th May next.

This has been announced by the organisers, the Radio Industry Council, whose director, Vice-Admiral J. W. S. Dorling, said: "Her Royal Highness has a double interest in radio. She is a music lover and listener and as Colonel-in-Chief of the Royal Corps

of Signals closely follows technical developments and training."

All space in the exhibition is taken. The exhibitors include the leading manufacturers of radio and television receivers, and the RIC is to build a studio within the exhibition from which the BBC will broadcast sound and TV programmes.

The Northern Radio Show, which is the second to be held since the war, closes on Saturday 14th May.

The Decoupling Resistor and Condenser

THE MOST USUAL PURPOSE OF THE AF decoupling resistor and condenser is, of course, to prevent hum in the HT line from affecting the early stages of an audio amplifier, common values being 50k Ω and 16 μ F.

There are, though, at least two other functions which are now often seen in the modern television receiver, and which may at first seem a little puzzling. For instance, it is often the output stage of the audio amplifier which is decoupled, and not the first stage. Because other circuits demand a hum-free HT line there is, in fact, often no need to decouple the audio stage, but it is vital that the audio variations from the output stage should not be allowed to affect the HT line, because these variations in turn affect the other stages. One typical trouble is frame "jitter." The frame bounces a tiny amount in time with the audio signal.

Another function of the decoupling may therefore be seen. It not only keeps out hum, but in the last case keeps in the audio variations.

Another function is where the decoupling

is necessary to keep out other forms of interference, even though the hum level is low. This is found, for instance, in a television receiver where the audio stage is decoupled to keep out line whistle. It is also found in high gain amplifiers where it is used to prevent low frequency oscillation or motor-boating.

The same function is, of course, seen in a television receiver in the high frequency amplifiers, where every stage will be found to be adequately decoupled. In this case, only high frequency troubles are to be expected, and so the usual values are 5k Ω and 0.001 μ F.

The same circuit may, of course, be used for dropping the voltage of the supply, and in this case the only object of the condenser is to prevent negative feedback in the valve concerned. Two examples of this are the screen circuit of a video output stage, and the screen circuit of a 470 kc/s IF amplifier. Decoupling, as such, is unlikely to be necessary, but the valve itself demands lower voltages to prevent too great an internal heat dissipation.

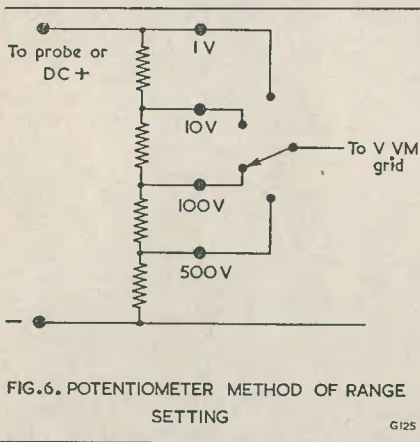


FIG. 6. POTENTIOMETER METHOD OF RANGE SETTING

red, the meter would be deflected from zero.

The circuit is as shown in Fig. 5a. Fig. 5b illustrates the way in which V_2 is used as a

Radio Miscellany

IN MY FINAL PARAGRAPH LAST MONTH I mentioned the return of an American radio acquaintance from a short visit to Europe. He certainly made a busman's holiday of it, and as far as I could judge his chief relaxation seemed to be watching our TV programmes. While he was with me the programme timing seemed worse than usual—so much so he became somewhat exasperated with the "interval films" of angel fish swimming aimlessly, potters' wheels, waves breaking on the shore or fingers plucking harp strings. At home he has the choice of some half-dozen programmes, and the idea of losing the customers' attention to other advertisers because of poor timing seemed Bad Business.

The repetition of interval films does not seem to worry our viewers. They have got used to them, and perhaps even look on them with some affection. I once heard of a household where they run a sweepstake on which night of the week a new interval film will turn up. As new ones are so rare I suppose it adds interest to the in-between-times. If the BBC only had a few more of them one could run a pool on the order of the three which get the most showings in any one month!

Pot Pourri

From interval films we got round to viewers and programmes. Accustomed as he is to being able to switch from programme to programme, he found it difficult to understand how British viewers used their receivers so much.

When you come to think of it, it is amazing how people can settle down to promiscuously watch ballet, table tennis, crooning sisters, swimming races, old-fashioned films, incomprehensible plays, foolish parlour games with smirking panel ladies and irascible old gentlemen, snooker, and politicians discussing almost non-controversial affairs, and grow so hypnotised by it all that they become quite incapable of turning the wretched

thing off. I can only think it must be due to a strange belief that however bad it is now there is always a chance it might get better later on!

Maybe it is different with American viewers who have the opportunity of switching round to a half-dozen stations. If they are all bad, disillusionment ought to come six times as quickly!

Broad Acres

Naturally, I had questions to ask about the continuing popularity of radio as a hobby. It is, of course, difficult for anyone, however well informed, to give a true picture of a hobby in a country which is the size of a continent. We ourselves can hardly judge the growth or contraction of interest in our own country, let alone a nation of some 3,000 odd "steam" radio transmissions and about 400 TV stations. His opinion, for what it is worth, was that the decline in amateur transmitting radio is about the same as it is over here, and he suggested that the decline in enthusiasm is greater than that in numbers. That is, many amateurs are continuing with their licences but are generally less active. With ourselves, the number is still about three times as many as pre-war, but I think we shall shortly reach the "hard core" and the number will remain fairly constant around that level.

He was diffident about expressing an opinion on constructional radio interest, but was inclined to think it was about holding its own. If the advertising space in magazines catering for the hobbyist is any guide (and it is generally considered a fair indication), any diminution can only be very slight. The love of the American male for gadgets is proverbial, and interest in electronic gear which is closely allied to radio is likely to continue unabated for years to come. I was happy to be able to reassure him that over here there is a regular and continuing influx of youngsters coming into the hobby, and recent correspondence from old-timers

proves they still get a lot of fun out of it even after twenty or more years of radio.

Deep Depression

From programmes, our conversation got round to announcers. Direct comparison between the BBC and American TV announcers is quite out of the question. However, I asked him which of ours he preferred. To my astonishment he opted, without hesitation, for one of the meteorological experts. I pointed out that he wasn't an announcer, but merely someone borrowed from the Air Ministry to prove to overseas visitors how unpredictable our climate is! Not only did he stick to his choice, but he almost talked me into agreeing with him that the met. man would make a better job of it than those picked by the BBC.

Oddly enough, this particular met. man a few weeks later mentioned he wasn't feeling too happy. Everything had gone

how trouble-free most of our better-known makes are, and was even more surprised to learn just how many years' use the average viewer expects to get out of them.

I think he was quite converted to our vertically polarised signals. Over there aerial erection is quite a problem, and apparently a lot of bother is caused by their getting out of orientation during windy spells. Quite what would have happened during the recent gales if we had had horizontal aerials over here is anybody's guess. Quite a number of 2-metre beams came down despite the generous use of guy wires.

Incidentally, I cannot think of any other important country in the world where vertical polarisation is used. Even in Russia it is horizontal. Despite what the Left-wing propagandists tell us, much of their TV is still in the planning stage. Twice to my knowledge they have made big changes. They started with 343 line scanning, then to

CENTRE TAP

talks about

AMERICAN VIEWPOINT
AMATEUR RADIO

wrong. Yesterday's forecast had misfired, the one he was about to read would make everybody feel miserable and on top of it all he had just broken his favourite pipe! I have since been wondering how many viewers sent him a new one.

Simple But Good

Of course, we also talked of technicalities. When he was last in Britain, shortly after the war, our TV service had scarcely got into its stride. He was quite impressed at the picture quality we get from our "low definition" system—they use 525 lines—and the odd hundred is noticeably better on the larger size screens now coming into more general use. He was charmed at the simplicity of our sets. On the sound side, American receivers are necessarily more complicated since they use FM audio which means at least one more "toob." Nor did he think our sound reproduction was in any way inferior to their "hi-fi" FM.

On the video side, too, we get away with less IF stages. He had read of the type of sync circuits popularly used over here, and said he used to wonder if they were really satisfactory. He thought they looked too simple, yet apparently the picture lock on their receivers gives them far more trouble. He scarcely believed me when I told him

441, and now they use 625. I can't think what would happen in a democracy if the Big Brother of TV started mucking about like that.

Old Timers' Corner

Reverting back to my recent paragraphs re free gifts, Mr. R. S. Forster of Sea View, Lowestoft, writes to say he still has a number of relics from the earlier days. He also has a set of ST500 coils (canned) which he will pass on to any reader wishing to try out how such a receiver would behave under modern conditions.

An interesting letter also comes from Mr. N. F. Smallwood (Publicity Officer, Southgate Group RSGB), who still has in regular use many of the tools from a kit given under a coupon gift scheme. Among the tools is a $\frac{3}{8}$ " dental mirror for "round-the-corner" inspection. It is a good idea for other readers to make up such a mirror, and a de-luxe version fitted with a small spot light is bound to come in useful on frequent occasions.

I am sorry I haven't yet found time to get round to answering all the letters from old-timers, but I have enjoyed reading them immensely. It is most encouraging to think that our hobby is such a permanent affair for so many of us.

SIMPLE PROBE CONSTRUCTION


by W. R. BURROWS

MANY GOOD DESIGNS FOR SIGNAL TRACERS have been made available in recent years, but often the amateur constructor with only limited skill is deterred by the difficulty of making the probe itself. Usually a cylindrical container is suggested, and the wiring of a valve and sundry small items in such a small space can be decidedly tricky.

The probe illustrated obviates these difficulties, and is based on one of the narrow

valve but makes the wiring of the capacitor and resistors really easy.

The point at the business end consists of a nail with the head cut off, gripped by a single pin plug which in turn fits into a Clix socket fixed into one end of the tin as shown. An additional advantage of this arrangement is that if it is desired to hold the probe on to any particular point of a set under examination, while still leaving both hands free, a tiny length of flex with a crocodile clip at one end

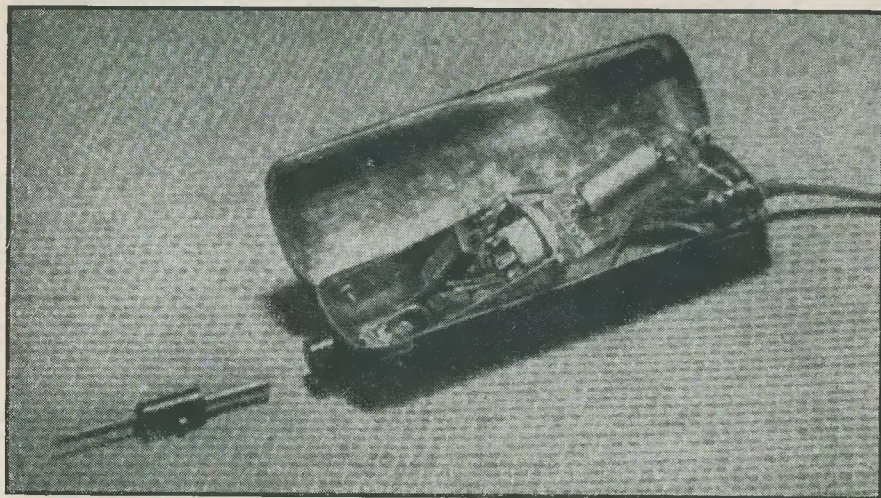

The probe with lid open, showing valve assembly partially raised on its "hinge," and details of the prod

tins used for containing cycle tyre repair outfits. The miniature valveholder is supported by two short strips of sheet metal, which are in turn fixed to the sides of the container by 8-BA bolts and nuts to give a hinge effect. This not only facilitates replacement of the

and a plug at the other can be substituted for the "prod" shown.

If the completed probe is given a coat of black enamel it will assume quite a professional appearance and will fit the hand very comfortably.


IMPROVING SIMPLE "UNIVERSAL" RECEIVERS

by F. G. RAYER

OF THE MANY AC/DC CIRCUITS EMPLOYED, both in commercial receivers of cheap type and in the less expensive home-construction models, components and circuit complications have been reduced to the minimum. Though such receivers can give good results, a number of modifications can be tried out with comparative ease, and will generally result in an improvement in overall sensitivity. It is also frequently possible to reduce the level of background hum, which is quite high in many of the cheaper receivers.

Nevertheless, the simpler types of AC/DC receiver, especially if home-built from a circuit designed with low cost in mind, can be improved very considerably.

A typical circuit such as usually employed in the type of set in view is shown in Fig. 1, and uses the minimum number of components. Though good results can be obtained, a number of limitations are imposed by the simplified circuit, and these may best be considered individually, together with means of overcoming them.

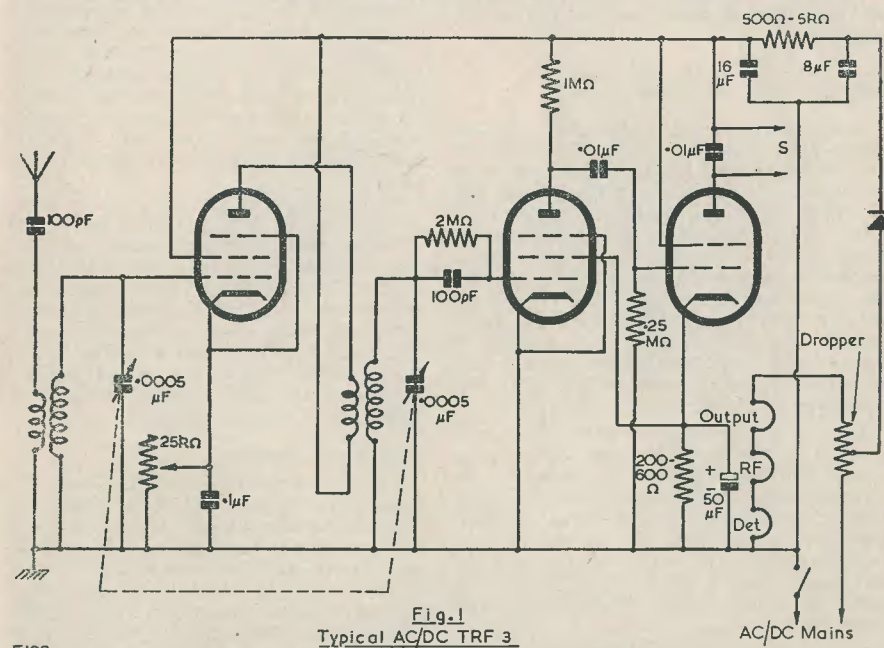

EL29

Fig. 1
Typical AC/DC TRF 3

When considering such improvements, and the results to be expected from them, it will be realised that some may not apply to particular receivers as such circuits may already exist. Nor is it suggested that all the modifications necessarily be carried out at one time.

Extra Wavebands

Long waves are useful in some parts of the country, while good loudspeaker reception of the more powerful short wave transmitters may be expected from such a circuit. If single-range coils are used, the

simplest method of adding a long wave band is to use a 4-pole 2-way rotary switch wired in as shown in the complete circuit in Fig. 2. When this switch is in one position, the existing medium wave coils will operate exactly as before the modification, and any tuning scale fitted will continue to be satisfactory. In the second position, a pair of long wave coils are switched in. These should be of "RF and Detector" type, and may conveniently be the small dust-cored components available from many sources.

If a short wave band is to be used in addition, a 4-pole 3-way switch is necessary, and a further pair of coils for about 19 to 50 metres. Leads to the switch should be reasonably short and direct, and the aerial coils may best be mounted above the chassis, with the detector coils underneath. The switch itself may be positioned near the tuning control, or on the side of the chassis if no space exists for a further knob on the cabinet front.

For maximum results, a 50pF trimmer should be wired across each coil, as shown, and each band separately aligned for highest sensitivity.

Changes in the RF Stage

As reference to Fig. 2 will show, further points arise when maximum efficiency from the RF stage is required. The simple form of volume control shown in Fig. 1 does not always permit of the local station being kept down to the required level, and this can be overcome by re-wiring it as in Fig. 2. Here, as bias is increased, so is the signal input to the first stage reduced, so that control of volume down to zero is possible. A fixed resistor of about 300 ohms is also added in the cathode circuit so that the valve is not left operating wholly without bias when the control is set for maximum volume.

In some simple designs the RF screen grid is wired directly to HT positive. An increase in gain will arise if the anode voltage can be increased, and a SG dropper, as shown, then becomes necessary since valves of the 6K7 type have a maximum SG voltage of 125. In some circuits, this voltage may already be exceeded. If so, a SG dropper should certainly be added, about 50kΩ being most generally suitable.

It is also worth noting that the aerial condenser, present to keep mains voltages out of the aerial wire, should be of high quality with insulation above reproach. As reception of weak stations is usually improved by adding an earth, a further 750V working condenser, of about 0.05μF capacity, may be connected to the chassis for this purpose, as indicated.

Detector Stage

The method of obtaining a low SG voltage from the output valve cathode shown in Fig. 1 is largely used in simple circuits. As the output cathode voltage is not always most suitable, and some forms of feed-back may arise, a separate SG dropper, with by-pass condenser, is preferable. These are shown in Fig. 2. The resistor value of 4MΩ is most generally suitable for the 6J7 valve and similar types.

Fig. 2 also shows the circuit for anode-bend detection, with best values for a 6J7 or similar type. This type of detection generally results in less hum, since the control grid of this valve is now returned to the chassis, as regards hum frequencies. The anode resistor value may require changing to that shown in Fig. 2, and the anode bypass condenser of about 0.001μF should not be omitted.

If maximum possible volume from weak stations is required, especially in an experimental receiver, reaction can be added. It can result in a considerable increase in sensitivity, and standard coils with reaction winding can be used. If the receiver is for general use, however, it is not really necessary.

In Fig. 2 the HT supply to the RF and detector stages is further smoothed and decoupled by the 50kΩ resistor and 8μF condenser. This helps to preserve complete stability, and can prove very helpful in reducing hum caused by ripple in the HT circuit.

If clear-glass valves are used in RF or detector stages, it is frequently worth while enclosing these in screening cans, or adding screens made from aluminium, bolted to the chassis. If the receiver becomes unstable as the volume control is advanced towards maximum, such screening may be essential. The 0.1μF bypass condenser in Fig. 2, wired from the HT end of the coil primaries to chassis, keeps RF currents out of the remainder of the HT circuit.

Output and Rectifier

These are best considered together. With 0.3 amp type valves, a 25A6 or 43 is frequently found in the output stage, and have maximum SG and anode voltages of 135 and 160 respectively. In Fig. 1, the total HT voltage is kept down to about 135V by using a tapping on the mains dropper. It is preferable, however, to increase the HT voltage to the maximum rating of the output valve anode, adding a SG dropper of about 5kΩ. This increases power output and amplification, and also the gain of the RF and detector stages. In 0.2 amp and 0.15 amp heater circuits, a 12A6 is commonly used, and may receive up to 250V on both anode and screen grid.

A simple form of tone control may readily be added as shown, the 50kΩ potentiometer

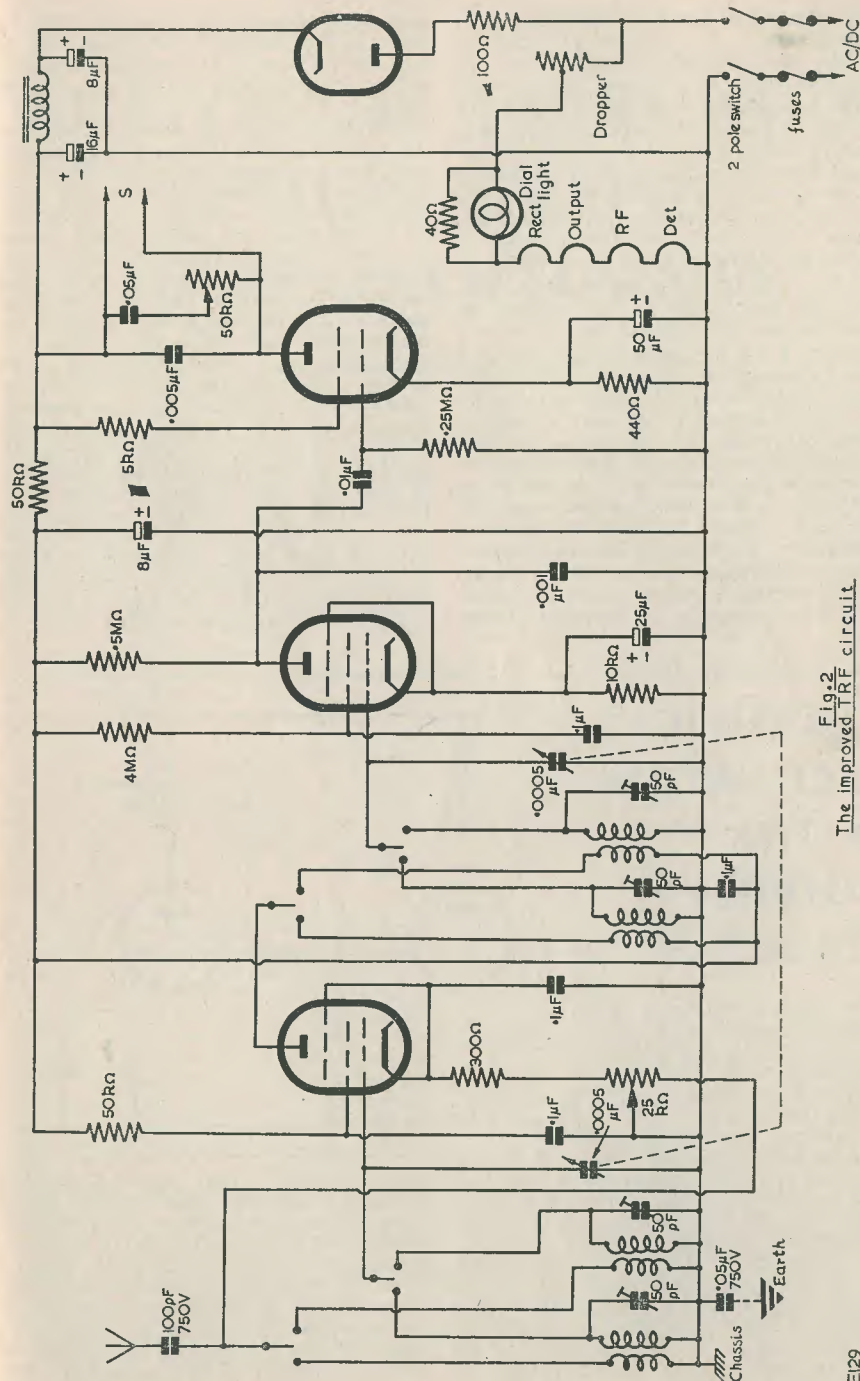


Fig. 2
The improved TRF circuit.

being mounted at any convenient position. In order that a fair amount of treble is possible, any condenser already wired in parallel with the transformer primary may require reducing in value, as indicated.

Small receivers of this type frequently use a resistor, as in Fig. 1, instead of a smoothing choke. However, a choke will provide better smoothing and also be of lower DC resistance, so that the receiver HT voltage increases. Any small smoothing choke is satisfactory, its rating being about 60mA.

In Fig. 2, a valve rectifier is shown, and gives less hum, with a given degree of smoothing, due to its infinite back-resistance.

The 25Z4 is a good type for this position. If the metal rectifier is in good condition and of good make, it may, of course, be retained. But if a replacement is necessary, a valve is worth considering as a substitute. To limit the peak anode current, a 100Ω resistor is included in the anode lead. At the same time the mains dropper circuit may be adjusted as required to obtain the maximum permissible HT voltage for the output stage.

If no dial light is present, this may be added as shown, a resistor of about 40 ohms being wired in parallel to prevent the initial

surge when switching on causing the bulb to blow. Alternatively, a 0.3 amp bulb may be used for 0.15 and 0.2 amp heater circuits, and a 0.5 amp bulb for 0.3 amp heater circuits.

Finally, a single pole switch included in the position shown in Fig. 1 is frequently used, but double-pole switching (Fig. 2) is preferable as the chassis is then safe to touch when the receiver is off. In Fig. 1, when the switch is opened, the circuit to the chassis from one mains lead is still completed, via dropper and heaters. It is also worth while connecting the receiver in such a way that the chassis is at the —ve or neutral side of the mains circuit, with AC mains. (This is a useless precaution with switching as shown in Fig. 1, as when the switch is open the chassis would become at high-potential relative to earth, via the unbroken mains lead.) Two fuses of quite low rating (0.5 amp) may also be included in the input leads, to avoid any fault blowing the main house fuse, and to afford maximum protection in the event of breakdown or leakage into the aerial or earth leads. If possible, it is best to use a non-reversible (e.g. 3-pin) mains plug, *neutral* going to chassis and *line* terminal going to mains dropper.

NOTES ON THE MODIFICATION OF THE 182a UNIT TO AN OSCILLOSCOPE

by A. P. BLACKBURN

SINCE THE ORIGINAL ARTICLES APPEARED in these pages (May, June and July, 1954), some queries have been received which may be of interest to other readers who are attempting the conversion.

Before going any further, it has been pointed out by one reader that an error appears in one of the diagrams. On page 709 of the July issue, R₁₉ and C₁₇ are shown as connected to C₁₆ on tagboard 1 (Fig. 17). Reference to the circuit diagram (May issue, Page 588, Fig. 2) shows R₁₉, C₁₇ as connected in the cathode circuit of V₃ and C₁₆ in the anode circuit. The circuit diagram is, of course, correct.

In Fig. 17, R₁₉ C₁₇ should be shown as being connected to the spare tags between C₁₆ and R₉, on the upper edge of the tagboard. This tag is then connected to the cathode of V₃, the tag merely serving as a "jump off" or anchoring point for these components.

A point which has worried some readers is the fact that there are twelve terminals on the rear input panel, but the circuit only accounts for ten of them. A layout of this panel was not suggested in the article, because it was felt that each constructor would prefer his own arrangement of the terminals. Two spare terminals were added, in case anyone should need them for a purpose that had not occurred to the author, e.g. a cathode follower probe input, or an additional sync input position in direct connection with the plates.


A suggested arrangement for the use of the terminals is

- Top row Y₁ plate and input to attenuator
- Second Row X₁ plate and output from attenuator
- Third row Y₂ plate one spare (small terminals)
- Bottom row X₂ plate one spare (small terminals)

PARASITIC OSCILLATION IN THE OUTPUT STAGE

As its name implies, parasitic oscillation consists of unwanted high frequency oscillations in the output stage. High mutual conductance valves are very prone to this trouble if no precautions are taken. The trouble may also be caused by bad layout with, for instance, anode and grid wires too near to each other. The trouble often shows up as a rattling noise in the loudspeaker as though there were an iron filing caught in the speech coil. The fault is difficult to detect without an oscilloscope, and so it is worth while always including these extra resistances. The increase in cost is negligible, the performance of the stage will not be affected, but parasitic oscillation will be

most unlikely. The parasitic stopping resistances must be mounted close to the valve-holders to be effective. For instance, when wiring a 6V6 base, the 5kΩ is connected between pins 5 and 6 while pin 1, which is blank, is connected to HT and the 100Ω resistance may be mounted across the holder between pins 4 and 1. Before wiring other types of valve it should be ascertained that there is no internal connection to pin 1. G.B.

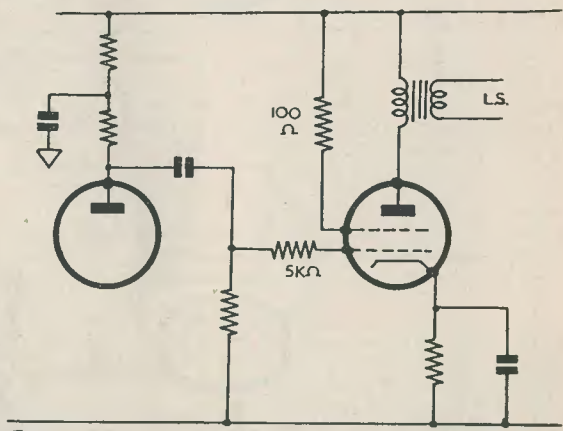

Queries

One reader has asked if a VU120A valve can be used to replace the specified VU120. The answer is that, in this circuit, they are directly interchangeable.

Another asks if a sweep amplitude control could be fitted. In this circuit the trace length should not exceed the diameter of the tube. There is little to be gained, therefore, in fitting a control which would only make the trace shorter. Trace amplitude controls are normally fitted to oscilloscopes when the timebase is expanded and may sweep two or three times the diameter of the tube. If, for some specialised reason, an amplitude control is imperative, the simplest way is to make the anode load R₆ of V₁ a potentiometer. The track would be wired between anode and HT+ and the slider connected to R₉.

One reader who is using the circuit, but not the 182A unit, has requested further details of the compensating coil L₁ in Fig. 3, "Y amplifier." No winding details are available because the coil used in the author's instrument was modified by unwinding as described, but for anyone in a similar predicament, who requires the correct coil, it can be supplied by the Teletron Company, of 266 Nightingale Road, London, N.9.


A small omission has been noticed on page 708 of the July issue. Under "setting up," the expression should read:

$$\text{Gain} = \frac{\text{Output voltage (peak to peak)}}{2 \times 1.41 \times \text{input voltage (RMS)}}$$

Although they were not available at the time the author undertook the conversion, the panel signs now being marketed by Data Publications Ltd., are recommended to give a really professional finish to your instrument.

The interest shown by readers in this conversion has been very gratifying, and I am very pleased to hear from the number of readers who have expressed their satisfaction with the operation of this design.

TRADE NEWS

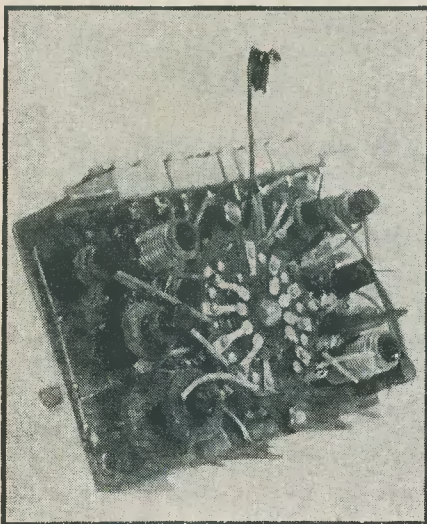

This new pack is for use with a two-gang 500pF condenser and is composed of aerial and oscillator coils wound on "Neosid" formers complete with iron dust tuning cores. Both the wavechange switch and the mica compression trimmers are mounted on an aluminium plate. The complete assembly is fixed by an additional nut on the wavechange switch. The IF is 465 kc/s and the pack may be used with any standard frequency changer. The retail price is 49s. plus purchase tax of 16s. 4d., total 65s. 4d.


Wolf Electric Tools Ltd.

Wolf Electric Tools Ltd. are the first to introduce to the field of "home handyman" equipment an electric bench planer of high performance and accuracy. It is powered by the Cub Drill and fitted with a cleverly designed planing head. Continuous cutting action eliminates difficulties of planing against the grain and the patent conical high speed cutters—virtually self-sharpening—should last indefinitely under normal usage. Owners of the Cub Drill can add this useful set to their equipment for the low inclusive cost of £3 9s. 6d., whilst the complete Bench Planer, including the Wolf Cub Drill, Bench Clamp, Pillar and No. 10 Planer Set, costs £10 13s. 3d.

Also introduced is the No. 9 Bench Sander Set at a cost of £1 18s. 6d., or for those who do not possess the Cub Drill the complete Bench Sander, comprising the No. 9 Sander Set, Bench Clamp, Pillar and Wolf Cub Drill, can be had for £9 2s. 3d. Fine accurate finishing is easily obtained at high speed on wood, metal, plastics and similar materials to a depth of 2¼in. To ensure maximum performance, self-adhesive sanding discs are provided in assorted grades to suit different work, and these can be instantly fixed to, or removed from, the faceplate as desired. The set includes a handy bevel attachment which enables mitres and other angles to be sanded with accuracy and speed. Inexpensive conversion packs to convert planers to sanders and vice versa are also available.

The range now embraces a veritable power work-shop, with facilities for Bench Sawing, Wood Turning, Portable and Bench Drilling, Grinding, Bench Planing, Polishing, Portable and Bench Sanding, Fretsawing, etc.

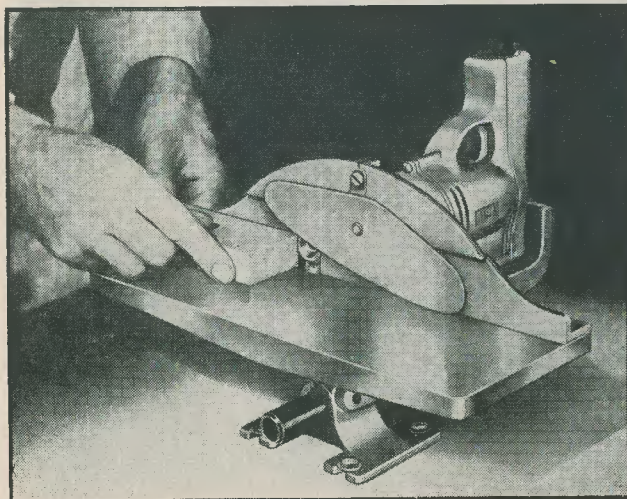Fully descriptive literature of the above Sets can be obtained from Wolf Electric Tools Ltd., Hanger Lane, London, W.5.



Labgear (Cambridge) Ltd.

The illustration on the right shows the workmanlike appearance of the new table-top transmitter manufactured by Labgear (Cambridge) Limited, of Willow Place, Cambridge. For all that it occupies only one square foot of table space, excluding power pack and modulator if used, this transmitter is capable of giving the full 150 watts input allowed by the G.P.O. It uses an 813 in the PA, a heater transformer for which is included, and this stage uses a pi-filter tank output circuit to assist in the reduction of harmonic radiation, a matter which has received great consideration in the design. Cooling of the PA stage is by convection, air being drawn through the bottom of the cabinet so that it flows past the 813 and out of the perforations in the top of the case.


5763's are used in the bandswitched exciter, and the VFO is provided with a full vision calibrated dial. The transmitter covers all the low frequency bands from 3.5Mc/s to 28Mc/s. A descriptive leaflet may be obtained from the manufacturers in return for an SAE.

New Mullard Tuning Indicator of Novel Design

The Mullard EM80 is a cathode-ray tuning indicator ("magic eye") for AC mains-operated broadcast radio receivers. Unlike conventional tuning indicators, in which the luminescent screen is viewed through the end of the valve, the EM80 is designed for viewing from the side. Thus, although the valve is a miniature all-glass type, the area of the display is quite large (14.5mm wide and 19mm high), and is clearly visible over a wide angle. When a station is being tuned in, alternate bands of light and shadow in the display vary in size, the shadow diminishing as tuning becomes more correct.




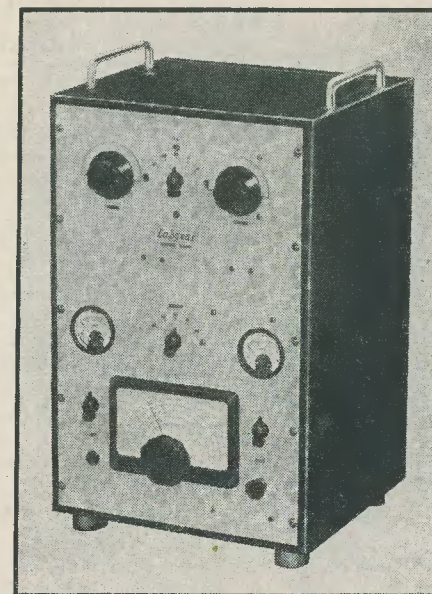On right, two specimens of the Mullard EM80 tuning indicator placed side by side to provide front and rear views. The valve on the left is seen as it would be looking from the front of a set. At left, drawing showing the indicator pattern of the Mullard EM80. B is one of the illuminated "petals".



The valve is sufficiently sensitive to ensure that small changes in tuning which cannot be detected by ear are nevertheless clearly visible.

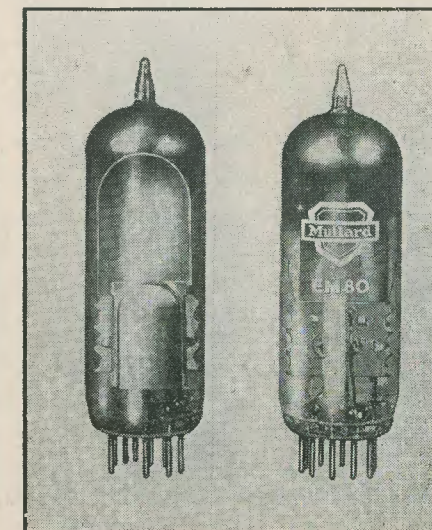The EM80 is on the B9A noval base, and has a heater rating of 6.3V., 0.3A. Mounting position is unrestricted, and the design of the valve makes it easy and economical to mount so as to give a clear indication of tuning, and at the same time be aesthetically pleasing.



★ "RF 26" F.M. CONVERTER UNIT—88/100 mc/s ★

This well-known RF26 Unit is now adaptable for F.M. reception using 2—I.F. stages and separate local Oscillator and tuned by a Muirhead graduated vernier drive, and can be converted Low cost, 92/6.

Send 2/- for 8-page Descriptive Booklet containing full wiring instructions, circuits and lay-out diagrams.

COMPONENTS OFFERED TO COMPLETE F.M. UNIT
New RF26 UNIT WITH THREE VALVES—VR137, EF54, EF54. Chassis stamped out for easy conversion £1 15 0
COMPLETE SET OF ALL COMPONENTS FOR CONVERSION, including 2-6BA6 and EB91, tuning condenser, I.F.T.'s and OSC coils, resistors and fixed condensers, plugs, wire and tag strips ... £4 12 6
INSTRUCTION BOOK with technical circuit and complete lay-out diagrams ... 2 0
SPECIAL OFFER OF ALL ABOVE ITEMS, INCLUDING RF26 and book ... £6 5 0

Postage 3 0
CHARGE FOR ALIGNMENT WHEN COMPLETED 7 6
COMPLETE SET as above and 6 valves—aligned and ready for use ... £8 10 0
N.B.—VOLTAGE REQUIRED: 250V 50 M/a and 6.3V 2 amps.

CATHODE-RAY TUBES

VCR97. Guaranteed full TV picture (carr. 2/-), £2.

VCR517C full TV picture, £1 15s.

Mu-Metal Screens for above 10s.

VCR139A (ACR10). For TV or 'scope, brand new and boxed £1 15s.

VCR97 Brand new, slight cut-off but suitable for 'scopes. 15/-.

Post and package, 2/-.
3PBI Boxed. 30 -

R.F. UNITS

post free
RF24, 20-30 Mc/s. ... 15/-
RF25, 40-50 Mc/s. ... 19/6
RF26, 50-65 Mc/s. ... 35/-
RF27, 60-80 Mc/s. ... 35/-
All Brand New with Valves

INDICATOR UNIT TYPE 182A

Limited Quantity Available
Suitable for TV or Oscilloscope. "Radio Constructor" 'Scope constructional circuit included.

Offered BRAND NEW (less relay) at 67/6 (plus 7/6 carr.).

U.S.A. INDICATOR UNIT BC929A

Complete with 3BPI C/R Tube and Shield. 7 valves. 2-6SN7GT. 6G6, 2X2, 6X5G volume controls, etc. Black crackle case, 1 1/2" x 9" x 9". Ideal for portable 'scope. Brand new condition 65/-.

CRYSTALS

200 kc/s 2 pin U.S.A. 10/-
465 kc/s 2 pin U.S.A. 10/-
500 kc/s 2 pin British 15/-

Postage up to £1 11/- f.2 or over, 2/-, unless otherwise stated
SEND STAMPS FOR 28-PAGE CATALOGUE

WE HAVE OVER 50,000 VALVES IN STOCK AT VERY COMPETITIVE PRICES. SEND 3d. FOR 28 PAGE CATALOGUE

LATEST TYPES NOW IN STOCK

EBC41	10/-	ECL80	12/6
EY51	12/-	50B5	10/-
EF41	11/-	PL81	12/6
EL41	11/-	PL82	10/-
EZ40	10/-	PY81	10/-
EM34	10/-	PY82	10/-
UL41	11/-	PCC84	12/6
UY41	11/-	PCF82	12/6
UF41	11/-	50C5	10/-
UCH42	12/6	12AT6	8/-
UBC41	10/-	12AT7	9/-
DK40	10/-	12AU6	9/-
EF80	10/6	12BA6	9/-
EABCC80	10/-	12BE6	10/-
ECC85	10/-	6X4	8/6
EL80	9/-	35W4	8/-

SPECIAL REDUCTION FOR SETS OF VALVES

1A7GT, 1N5GT, 1H5GT, 1A5GT (or 1Q5GT), 40/- set; 10EF50 (Ex-Brand New Units), 5/- each, 45/- set; 10 6AM6 valves, £4 set; 6K8G, 6K7G, 6Q7G, 5Z4G, 6V6G, 37/6 set; 1R5, 1S5, 1T4, 1S4 or (3S4 or 3V4), 27/6 set; TP25, HL23/DD, VP23, PEN25 (or QP25), 25/- set; 6K8G, 6K7G, 6Q7G, 25A6G, 25Z5 (or 25Z6G), 37/6 set; 12K8GT, 12K7GT, 12Q7GT, 35Z4GT, 35L6GT (or 50L6GT), 37/6 set; 12SA7GT, 12SK7GT, 12SQ7GT, 35Z4GT, 35L6GT or 50L6GT, 37/6 set.

RCA 931A PHOTO-ELECTRIC CELL AND MULTIPLIER

For facsimile transmission, flying spot telecine transmission and research involving low light-levels, 9-stage multiplier. Brand new and guaranteed, only £7 10s. Special 11-pin base, 2/-.

"38" SPECIAL OFFER "38" WALKIE TALKIE SETS

We have purchased large quantity of the above "38" Trans/Rec. sets, and can now offer same complete with five valves, 4-VP23 & ATP4, Throat Microphones, Headphones, Junction Box and Collapsible Aerial in absolutely new condition and guaranteed Air Tested. Freq. range 7.4 to 9 Mc/s. Range approx. 5 miles. 59/6. Carriage 5/-.

U.S.A. PACKARD-BELL PRE-AMPLIFIER

Complete with 6SL7GT and 28D7GT Relay Condensers and Resistors. Brand new with Instruction Book, 12/6. P.p., 2/-.

HENRY'S

(RADIO LTD.) SHOP HOURS

Mon.-Sat. 9 a.m.-6 p.m. Thursday 1 p.m.

Telephone Paddington 1008/9 & 0401

5 HARROW RD. LONDON W.2

SMALL ADVERTISEMENTS

Readers' small advertisements will be accepted at 3d. per word, including address, minimum charge 2/-. Trade advertisements will be accepted at 8d. per word, minimum charge 6/-. If a Box Number is required, an additional charge of 1/- will be made. Terms: Cash with the order. All copy must be in hand by the 10th of the month for insertion in the following month's issue.

PRIVATE

TELEVISOR UNITS, Premier 12", London, complete with valves. Power Unit, 70/-.

R1155N, modified, needs attention, 50/-.

RADIO SPARES, components, large stock of valves.

FOR SALE, Truvox Mark III Tape Deck, little used.

WHAT OFFERS? "Wireless World," Nov. 1949 to Dec. 1954.

FOR SALE, Windsor model 260A Television Wobbulator.

AMATEUR SURPLUS, "Wireless World," 6d. copy.

FOR SALE, Williamson Amplifier to spec., twin chassis.

FOR SALE, Radiogram Cabinet, walnut, 32" x 30" x 18".

FOR SALE, AVO Battery Oscillator, reconditioned by makers.

AMATEUR'S SURPLUS, Mixed condensers, resistors, valvebases, knobs, 1/- per dozen.

Large Purchase of E.M.I. Test Equipment for Amateurs

SPOT FREQUENCY MARKER, Type No. AD/U405 Operating on a frequency of 1 Mc/s and generating harmonics at 1 Mc/s intervals up into the V.H.F. range.

GRID DIP OSCILLATOR, Type No. AD/U407 The Oscillator described above is similar in design with different frequency ranges.

ABSORPTION WAVE METER, Type No. AD/U408 This consists of a variable tuned circuit, across which is connected a germanium crystal in series with a 500 microammeter.

GENERAL PURPOSE POWER SUPPLY UNIT, Type No. AD/U410 L.T. supply being isolated from earth.

NOTE: Orders and Enquiries to Dept. 'R'.
PROOPS BROS. LTD. 52 Tottenham Court Road W1

All above units £4.10.0 (plus 5/- New and Boxed £4.10.0 each postage)

Hours 9-6 p.m. Thursday to 1 p.m. LAngham 0141

SPEAKERS 12/9

P.M. 8", 6 1/2", 5 and 3 1/2" used, tested and guaranteed 2-5 ohms. Postage 1/9.

SPEAKERS 4/9. M.E. 8" 1K, 1 1/2 K and 2K field, used, tested, guaranteed. Post 1/9.

O.P. TRANSFORMERS 1/9. Standard size. Salvage, tested and guaranteed. Post 6d.

VHF 1124 RECEIVER 17/6. Complete with valves. 30.5-40Mc/s. 6-channel switching covers TV, sound, fire, amateurs, etc. Convertible to mains (AC or AC/DC). Drawings free. Post 2/-.

2-gang Condensers 2/9. Standard size, 0.0005. Post 6d. Salvaged guaranteed.

TRANSFORMERS 9/9. 350-0-350, 6V and 5V heaters, also at 5/9, 350-0-350 12V and 4V heaters. Primary 100 to 250V (this makes ideal auto-transformer). Post 2/-.

1% Resistors 2/9. 1 meg wire wound IRC U.S.A. Post 3d.

0.2 Droppers 1/3. Used, tested. Post 4d.

IF COILS 2/9 pair. Standard size 465 f/s. Post 6d-per pair.

AMPLIFIERS. 7 watts, push-pull, universal, 77/6. 4 watts 57/6 AC or universal. Ideal for p.u. or mike. Post 2/6.

AMPLIFIER 97/6. 10 watts AC. Special for mike and p.u. triple controls or 5 valve giving extra pre-am stage, £5 17s. 6d. Post 3/6.

DUKE & CO

621 ROMFORD ROAD · LONDON · E 12

Telephone GRA 6677

(continued on page 511)

RADIOVISION

4 PRAED STREET
LONDON W2
Telephone AMB 4670

We have a very large selection of Valves and Spares at the Lowest Possible Prices

We have a Large Selection of used but perfect C.R. Tubes. Every Tube carries a 6 week guarantee. Callers can see picture on premises.

9"	£4 0 0
12"	£6 0 0
15"	£8 10 0

Post, Packing and Insurance, 10/-

URGENTLY WANTED

COMMUNICATION RECEIVERS TEST EQUIPMENT. RADIOS—and TELEVISION SETS, TAPE RECORDERS. Best Prices Given

Phone or Call

TELEKIT SUPPLY

CHANNY LANE
BROMLEY · KENT

When ordering, please mention
RADIO CONSTRUCTOR and enclose 6d. postage

VALVES, New and Surplus		Guaranteed			
1B24	35/-	6BE5	6/-	5763	8/-
1L4	5/6	6BR7	8/6	9D2	5/-
*1LN5	3/-	6BS7	7/-	11D3	6/-
1S5	6/-	6BV6	6/6	*12A6	5/-
1T4	6/6	6CH6	6/6	12AT6	7/6
1U5	6/-	6I5	5/-	12BE6	6/6
3V4	6/6	6K7	4/-	*1299	5/-
6AL5	6/-	6SL7	7/6	14S7	7/-
6AM6	6/-	6U5	6/-	15D2	4/-
6AQ5	8/-	6X4	6/6	19AQ5	10/-
6AT6	7/6	6X5	7/-	EF50	5/-
6A8	8/-	7D5	6/-	OZ4	4/-
6B8	6/-	7D8	6/-	13D1	7/-
6BA6	6/-	7H7	6/-	50C5	8/-
W77	5/-	757	6/-		

* Soiled

NEW RETAIL SHOP NOW OPEN
AT 104 HIGH STREET BECKENHAM KENT

Telephone BEC 3720

SMALL ADVERTISEMENTS

continued from page 509

EQUIPMENT. Engineer forced to sell through loss of workshop, offers for sale—Test Instruments, Components, Radiogram with auto-change, Transformers (Mains and IF), Chokes, Chassis, Cabinets, Speakers, Valves, etc. (many new), over £150 worth. May be viewed Herne Hill. Box No. D145.

FOR SALE. AP sound, vision, BCR97, BC455 receivers. 6" time bases. BCR97 and 517C. Pye strips. 12V Vibrator Packs. Hosts of R's, C's etc etc., etc. What offers the lot? Vickers, 100 Vicarage Road, Chelmsford.

PRIVATE TUITION given for the R.T.E.B. Radio Servicing Certificate Examination (London). Box No. D134.

TRADE

BUILD YOUR OWN TEST EQUIPMENT. Kits, Circuits, and spares available. SAE for list. Electronic Services, 50 Kelmscott Crescent, Leeds, 15.

BLUEPRINTS. High Gain 10 Metre Converter, with a de-luxe circuit comprising EF91 RF stage, ECC91 double triode mixer and oscillator, EF92 IF amplifier, with stabilised voltage supply via a 7475, 1/8 post free with full instructions. Data Publications, 57 Maida Vale, London, W.9.

KENDALL AND MOUSLEY LTD. Manufacturers of Laboratory Equipment, chassis and instrument cases, also suppliers of B.V.A. valves, Radio and TV components. 18 Melville Road, Birmingham 16.

COILS, COILS, COILS. We can supply coils for all frequencies, RF Chokes, Filters, etc. Coils wound to specification—send details for estimate. Send SAE for circuits and data. The Teltron Co., 266 Nightingale Road, London, N.9

I.P.R.E. PUBLICATIONS. 5,500 Alignment Peaks for superhets, 5/9. Sample copy *The Practical Radio Engineer*, 2/-; Membership examination particulars, 1/-; Syllabus of TV and Radio Courses free and post free. Secretary, I.P.R.E., 20 Fairfield Road, London, N.8.

FREE! Brochure giving details of Home Study Training in Radio, Television, and all branches of Electronics. Courses for the hobby enthusiast or for those aiming at the A.M.Brit.I.R.E., City and Guilds, Telecommunications, R.T.E.B. and other professional examinations. Train with the College operated by Britain's largest Electronic Organisation, moderate fees. Write to E.M.I. INSTITUTES, Postal Division, Dept. RC28, E.M.I. Institutes, London, W.4.

MEDICAL BOOKS. In addition to radio publications, you can obtain from us the following popular works on health subjects. *Smoking and Cancer*, 2/-; A comprehensive discussion on this important subject. *So You're Grown Up Now*, 1/-; Personal information for the Teen-ager. *So You're Expecting a Baby*, 9d. A most helpful book for the young Mother-to-be. Please add 2d. for postage. Data Publications, Ltd., 57 Maida Vale, London, W.9.

OSMOR—for efficient coils, coilpacks, etc. Send 5d. stamp for FREE circuits and lists. Dept. RCC, Osmor Radio Products, Ltd., 418 Brighton Road, South Croydon, Surrey, Telephone Croydon 5148/9.

JOIN THE ISWL. Free services to members including QSL Bureau, Translation, Technical and Identification depts. DX certificates, contests and activities for the SWL. Monthly magazine "MONITOR" duplicated, containing articles of general interest to the SWL and League members, 12/6 per annum, post free. ISWL HQ., 86 Barrenger Road, London, N.10.

New Government Surplus catalogue No. 12 containing over 400 items price 1/6 post free. 2/6 overseas seammil.

ARTHUR T. SALLIS (R.C.)

93 NORTH ROAD · BRIGHTON · SUSSEX
Telephone BRIGHTON 25806

H.A.C. SHORT-WAVE EQUIPMENT

Suppliers for over 18 years of Radio S.W. Receivers of Quality One Valve Kit, price 25/-; Two Valve Kit, price 50/-; Improved designs with Denco coils. All kits complete with all components, accessories and full instructions. Before ordering, call and inspect a demonstration receiver, or send stamped addressed envelope for descriptive catalogue.

H.A.C. SHORT-WAVE PRODUCTS (DEPT. R)
11 OLD BOND STREET LONDON W1

SPECIAL CABINET OFFER!



12" x 7" x 7"
18 S.W.G. Steel, 14 S.W.G. Alum. Front Panel. Black Ripple Finish, Rubber Feet. With 18 S.W.G. Alum. Chassis, Fitted and rivetted ends 27/6 p.p.

Burn Engineering
HALL LANE WORKS,
HALL LANE, AINTREE, LIVERPOOL.

GUARANTEED VALVES — Over 3,000 in Stock

6AM6, 6C4, EF92, 6AL5, EAC91, 6J6, 5/-; 12AT7, 12AX7, 6AK5, 6F33, EC91, EL91, 6SN7, 6SL7, 6SK7, 6S17, R10, 6BA6, 6F17, 6CH6, 6BW6, 7/6; 12AU7, 12E1, 2D21, 85A1, 85A2, 9/-.

A. A. W. SKILLMAN
74 FRANCHISE STREET · WEYMOUTH


HIGH FIDELITY

COMPONENTS IN STOCK FOR THE
MULLARD 5-10 CIRCUITS 2s. 6d.
OSRAM 912 CIRCUITS 3s. 6d.
DENCO FM CIRCUITS 1s. 6d.

Price lists available on request

J. T. FILMER MAYPOLE ESTATE
BEXLEY · KENT
Telephone BEXLEYHEATH 7267

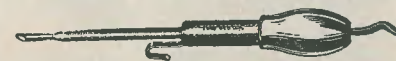ADCOLA (Regd. Trade Mark) SOLDERING INSTRUMENTS



Reg. Design No. 860302 (British, U.S. and Foreign Patents)

Designed for wireless assembly and Maintenance
Supplied for all volt ranges from 6/7V to 230/250V
3/16" Dia. Bit Standard Model, 25/6
Sole Manufacturers ADCOLA PRODUCTS LTD.

Sales Office and Works Cranmer Court
Clapham High St. London SW4 (MAC 4272)

TELETRON SUPER Inductor Coils



Miniature dust core types

Specified for the "RC" Mini-Preselector and Signal Generator. HFA1-3-4-5-7, 3/3 each. HFA9, 4/6, RFC4, 2/6. "Sensitive TRF Receiver" Type OCA and OCHF, 7/6 pair. Dual wave TRF matched pairs (as illustrated) 7/-. The original selective Xtal Transformer coil Type HAX, 3/-. HAX.L (1w), 3/6. E.C.O. coils, IFT's wavetraps.

Stamp for complete list and circuits

The Teletron Co. Ltd.
266 Nightingale Road London N9

Telephone HOW 2527

Trade enquiries to sole distributor, S. MOZER
95 KENDAL AVE. N18 Telephone EDM 7707

HANNEY of BATH offers


OSRAM 912 Erie resistor-pot, kit with ceramic tube resistors, very highly recommended, 29/6; Lab resistor kit, 32/4; T.C.C. condensers, 55/-; PARTRIDGE Components, with loose lead terminations, Mains trans., 44/-; Smoothing Choke, 29/6; Output trans., 76/9. Price includes Partridge carriage-packing charge. Printed panel, 14/6. W.B. chassis, 28/6. DENCO 16 S.W.G. All-Chassis with beautiful Bronze Front Panel, 21/- (Printed). S.A.E. List.

MULLARD 5 VALVE, 10 WATT AMPLIFIER; T.C.C. Condensers, 45/-; Erie resistor-pot kit, 37/6. Elstone Mains trans., 36/-; Elstone Output trans., 45/- (both types); Denco chassis, 14/6. Small parts as per our list. Matched pairs of valves are available for both the above designs.

COILPACKS. DENCO, CP4/L and CP 4/M, 33/4; CP 3/370 pf and CP 3/550 pf., 42/8. OSMOR "Q" HO, 48/-; LM, 40/-; Batt., 50/-; TRF, 40/-; HF stage for HO pack, 20/-; ETA 4-Station pack, 43/8.

WIDE ANGLE COMPONENTS. ALLEN. Teleking Chassis, 50/-; Coilsets (TK & Super-Visor), 44/6; LO 308, 40/-; FO, 305, 21/-; DC, 300c., 39/6; FC, 302, 31/-; GL, 16 & 18, 7/6 each; SC, 312, 21/-; AT, 310, 30/-; OP, 117, 9/-; BT, 314, 15/-; DENCO Chassis Magnaview, 37/6; Chassis, Super-Visor, 51/6; Coilsets, Magnaview, 41/2; WA/DCAL, 43/-; WA/FCA1, 31/-; WA/LC1 and WC1, 7/6 each; WA/FMA1, 21/-; WA/LOT1, 42/-; WA/FBT1, 16/-; Send 6d. stamps for our General List of components for Viewmaster, Soundmaster, Williamson Amplifier, Teleking, Magnaview (Brimar & English Electric large screen TV), Super-Visor, Mullard Universal, Close tolerance Silver Micas, etc., etc. Please add 2/- postage to orders under £3.

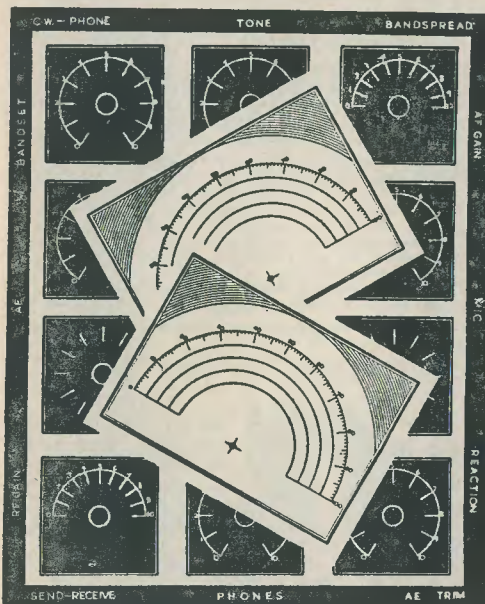L. F. HANNEY
77 LOWER BRISTOL ROAD BATH
Telephone 3811



PANEL-SIGNS TRANSFERS

Set No. 1: Receivers and Amplifiers
Five sheets $8\frac{1}{4}'' \times 5\frac{1}{4}''$ containing one Large scale, twelve control panels and wording. 3s. 6d.

Set No. 2: Test Instruments
Five Sheets $8\frac{1}{4}'' \times 5\frac{1}{4}''$ containing two Medium scales, twelve control panels and wording. 3s. 6d.

Set No. 3: Wording
Wording for Receivers, Amplifiers, Transmitters, Test Equipment and other Radio Apparatus.

4 Sheets, Approx. 400 Words 2/6

Panel-Signs Transfer Fixing Varnish
1s. per bottle.

Trade Enquiries Invited

Published by

DATA PUBLICATIONS
57 Maida Vale London W9

PANL

Most of the Nationally known mail order houses now stock this popular air-drying crackle finish as a regular line at 3/- per 1/2 pt. can, in black, green and brown. If you have any difficulty in obtaining your supply, send 3/6 to—G. A. MILLER, 8 Kenton Park Crescent, Kenton, Middx.

DATA BOOK 6

"RADIO AMATEUR OPERATOR'S HANDBOOK"

The above booklet is now completely revised and the printing of the new edition will commence shortly. Our stocks of the last edition are now completely exhausted, and an announcement will be made in these pages as soon as the new printing is available. Price 3/2 post paid.

DATA PUBLICATIONS LTD
57 MAIDA VALE · LONDON · W9

TELETRON FERRITE ROD AERIALS

Wound on high permeability Ferroxcube rod & designed for use with 500 pf. (max) tuning condenser. Nominal Inductance for type. FRM. 165. u/h. Q at 1 Mc. 185. Waveband 550 kc/2 Mc.—8/9d. FRD. 2.2.MH. Waveband 150 kc/2 Mc/s. LW and MW. 12/9d. 3d. postage.

THE TELETRON CO LTD

266 NIGHTINGALE ROAD · LONDON N9

Telephone HOW 2527

REPORT PADS

REPORT/REPLY RATIO LOW?

Then send a report which contains all the information a station requires. Each pad contains 50 printed forms detailing the headings under which reports should be made. Your QSL returns will be much higher if you use these properly prepared reports. Printed on a high quality paper suitable for airmail transit they cost only 3/9 post paid.

Orders with remittance to

DATA PUBLICATIONS LTD
57 MAIDA VALE LONDON W9

CONSTRUCTORS build these at low cost!

PERSONAL PORTABLE RADIO 30/-


Post Free
This little set was designed to give you a real personal portable radio that you can enjoy anywhere without disturbing others. Use it on camping trips, in bed, in your office, or just anywhere.



Send 2/- for layout, Wiring diagram and Components Price List.

ALL-WAVE RADIO 30/-

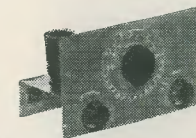
Ideal for the beginner or for those requiring a simple standby receiver.



This 1 valve S.W. receiver can be built for 30/-, from our list of components, which can be purchased separately. It includes valve and 1 coil covering 20-40 metres. Provision is made to increase to 2 or 3 valves if required, and all components are colour-coded so that the beginner can build this set quite easily. Send 2/- for specification, wiring diagram, layout and price list.

POWER UNIT TYPE PUI 120v @ 20ma, 6·3v @ 1·5A 32/6

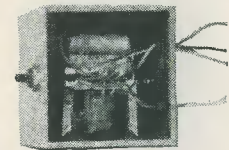Replace those expensive batteries with one of these power units. Supplied in component form together with easy to follow constructional details.



An ideal power supply for both these Receivers and for inclusion in Home-Built Test Equipment.

R.C.S. PRODUCTS (RADIO) LTD
11 OLIVER ROAD (Mail order only) LONDON E17

YOU CAN RELY ON US

Radio and TV Component Bargains

VALVES

6V6G 7/6, 6X5G 7/6, 6X5gt 7/6, 6SN7 9/6, EM34 7/6, 6USG 7/-, ECC40 9/-, EL42 8/-, ECC81 9/6, 6K7G 7/6, 6K7 (metal) 8/-, KT63 7/6, EF54 6/-, EF50 7/-, EL32 7/6, 12A6 7/-, 12SC7 6/6, 617G 7/6, 76 6/6, 12J5 4/6, EB34 3/6, EF36 6/6, 6B4 7/6, 6B8 7/-, 6K8G 8/6, 12K8gt 8/6, 1T4 7/6, 1S5 7/6, 1R5 8/6, 3A4 7/6, R3 9/-, 35Z4 7/6.

TRANSFORMERS TV

WB107 Line 32/6, WB106 Frame 25/6, WB103 Heater 42/-, WB103A Heater, 52/6, Denco WA/LOT1 Line 42/-, WA/FMA1 Frame 21/-, WA/FBT1 F/Blocking 16/-, Allen LO308 Line 40/-, FO305 21/-, BT314 15/-, and Haynes (when available). Osram 912 Amplifier Book 3/6, all parts stocked.

VOLUME CONTROLS

5K, 10K, 25K, 50K, 100K, 250K, 500K, 1mg, with switch 4/-, Less S/W 2/6, DP switch 5/6, Wire wound Pre-set from 100Ω to 30K 3/2 each. Standard 3W Colvern 6/4.

TRANSFORMERS

Speaker Trans. Pentode O/P 4/6, Midget Mains 3/9, Battery Stand-ard 4/-, Super-Midget for P/Portables 5/-, Charging Transformers 2V, 6V and 12V, charging at 2a 19/6, 1V, 2V, 4V, 6V, 10V, 15V, 20V, 30V, up to 15V at 4a, 30V at 2a 22/6. Midget Mains Transformer 60m/a 250-0-250V 6.3v at 3a, 5V 2a 21/6. Elstone SR/250 or SR350 28/6.

SOLDERING IRONS

Tyana Pencil Bit 14/11, Adcola Pencil Bit 25/6, Detachable Bit 33/6, Henley Small Pencil Bit 19/8, Solon Standard Pencil 25/4, Oval Bit 23/8.

LINEAR POTS

1/2mΩ, 1/2mΩ, 1mΩ, 2mΩ 6/6. As above with centre tap 7/6.

COILS

Osmor Full Range 4/- each, Weymouth 'H' Type 3/9, 'K' Type 5/-, CS3W3 12/3 per pair, CT2W2 10/- per pair, Denco Maxi-Q Midget Chassis or Plug-in Type 3/11 each. Full range of Osmor and Weymouth Coilpacks.

IF TRANSFORMERS

Denco IFT11 12/- pair, P4 (Weymouth) 15/- pair, Wearite M800 21/- pair, 501/502 20/- pair.

Q-MAX CHASSIS

PUNCHES
3/8", 3/4", 12/4, 3/4", 1 1/8", 1 1/4", 1 1/2", 1 3/4", 1 1/2" square 24/- (all inclusive of keys).

RESISTORS

1/2W, 1/2W 4d., 1W 8d., Midget 'T' 1/2W max. 6d., Type 'R' 1W max. 8d. Full range 2% high stab. 1/6 each. 100 ohms to 10K only.

A BARGAIN

New Tubular 8mf 500V Wire-End Electrolytics 1/11 each. 2 for 3/6.

Orders Despatched Promptly. C.O.D. by Return (over £1). Please add P/Pkg. fee up to £1, 1/-; £2, 1/6. Over £2 free. Catalogue of Surplus ready soon, 6d. each. Catalogue of New Proprietary Components (250 illustrations, 70 pages), 3/- Returnable on order over 30/-.

Next Door South Ealing Tube Station. 6 o'clock, 1 p.m. Wed.

82 SOUTH EALING ROAD
LONDON W5 Telephone EAL 5737

RADIO SERVICING CO