

PUBLISHED IN CONJUNCTION WITH
THE
RADIO CONSTRUCTOR

★ *The Radio Reprint Series* ★

		Price	Postage
RR3	The "Argonaut" AM/FM—MW/VHF Tuner Receiver—A Jason design	2/-	4d.
RR4	The "Eavesdropper". 3-Transistor local station pocket receiver	1/6	2d.
RR5	The "Mercury" Switched-Tuned FM Tuner—A Jason design	2/-	2d.
RR6	The Cooper-Smith B.P.I. High Fidelity 10-12 watt Amplifier and Control Unit	2/6	4d.
RR7	A Versatile 2-Valve Audio Pre-Amplifier—A Mullard design	1/-	2d.
RR8	High-Gain Band-3 Pre-Amplifier	1/-	2d.
RR9	The "Jupiter" Stereophonic Amplifier and Pre-Amplifier	2/6	4d.
RR10	The Cooper-Smith "Prodigy" 6-watt High Fidelity Amplifier	2/6	4d.
RR11	The Mullard Designed Type "C" Tape Pre-Amplifier	2/6	4d.

Send stamped addressed envelope for

BROCHURE

giving details of ALL PUBLICATIONS

DATA PUBLICATIONS LTD

57 MAIDA VALE LONDON W9

Telegrams Databux London

Telephone CUNningham 6141/2

Published in Great Britain by the Proprietors and Publishers
Data Publications Ltd 57 Maida Vale London W9

Printed by A. Quick & Co. (Printers) Ltd 125 High Holborn London WC1 England also at Clacton-on-Sea
Obtainable abroad through the following Collets Subscription Service Continental Publishers & Distributors Ltd
William Dawson & Sons Ltd Australia and New Zealand Gordon & Gotch Ltd South Africa Central News Agency
Holland "Radio Electronica"
Registered for transmission by Magazine Post to Canada (including Newfoundland)

COOPER-SMITH HI-FI STEREO MAIN AMPLIFIER

VOLUME 13
NUMBER 10
MAY
1960


The
**RADIO
Constructor**



RADIO · TELEVISION · AUDIO · ELECTRONICS



"A POINT-TO-POINT
TWO"

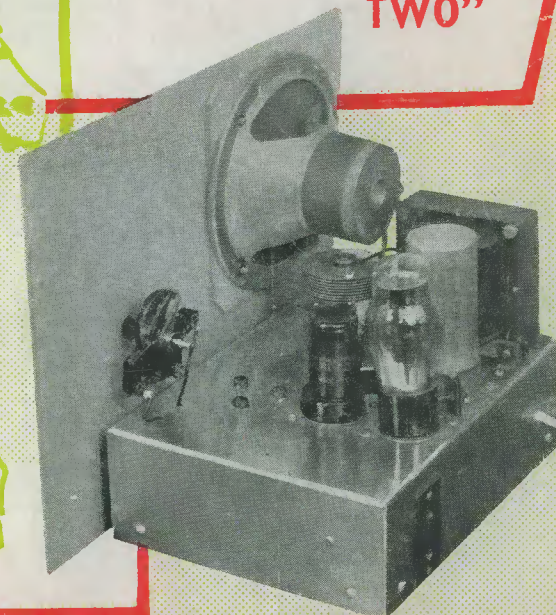

A Miniature
A/C-D/C Receiver
for LW, MW & SW

Included in this issue

"LITON" TRANSISTOR PARKING LIGHT SWITCH, Pt. 2
RTTY—IN THEORY AND PRACTICE
IS THAT TUBE REALLY FINISHED?
A TEST LOUSPEAKER
IN YOUR WORKSHOP

**DATA
Publications 1/9**

THE MODERN BOOK CO

Amateur Radio Handbook. By A.R.R.L. 1960. 32s. 6d. Postage 2s.

Model Radio Control. By E. L. Safford. 21s. Postage 1s.

Hi-Fi Made Easy. By N. H. Crowhurst. 23s. Postage 1s.

How to Get the Most out of Your VOM. By T. Jaski. 23s. Postage 1s.

TV Fault Finding. A Data Publication. 5s. Postage 6d.

Valve and Teletube Manual. By Brimar. No. 8. 6s. Postage 1s.

Single Sideband for the Radio Amateur. 14s. Postage 1s. 3d.

Short Wave Receivers for the Beginner. A Data Publication. 6s. Postage 6d.

Using an Oscilloscope. By D. W. Easterling. 6s. 6d. Postage 6d.

World Radio Handbook for Listeners. Broadcasting Television. 1960. 15s. 6d. Postage 1s.

Stereo Handbook. By G. A. Briggs. 10s. 6d. Postage 1s.

Guide to Broadcasting Stations. "W.W." 3s. 6d. Postage 6d.

R.S.G.B. Amateur Radio Call Book. 1960 ed. 3s. 6d. Postage 6d.

Radio Valve Data. 6th Ed. 5s. Postage 9d.

We have the Finest Selection of British and American Radio Books in the Country

Complete catalogue 1/-

19-23 PRAED STREET (Dept RC) LONDON W2

Telephone PADDington 4185

Modern Car Radio Receivers

Another in our Data Book Series

by Richard Myers,
and H. R. Major of the Jason Motor and Electronic Co.

This Data Book (DB13) contains three up-to-the-minute designs, each being fully described with point-to-point wiring. Of those featured, the "Maykit" uses the new 12V valves with output transistor stage while the Jason-designed "Everest 6" and "Everest 7" employ transistors throughout.

All the receivers cover the Medium and Long Waves. The Jason sets are contained in compact cases and are easily removable from the car for use as ordinary portables, operating from internal batteries and ferrite rod aeriels. The "Maykit" car radio is, of course, a permanent fixture within the car.

Fully illustrated with photographs and circuit diagrams, this Data Book should prove of interest to all car owners requiring a car radio.

40 pages, with varnished board cover

PRICE 3/6 POSTAGE 4d.

DATA PUBLICATIONS LTD 57 MAIDA VALE LONDON W9



MAY 1960

More

for less... with the

MULTIMINOR

Use PRODCLIPS (Pat. No. 748811)
with the Multiminor

These cleverly designed spring-loaded insulated prods are the complete answer to a long-standing problem. Press the trigger to open, release to grip. Keep your hands free no matter how difficult of access your test points may be!

15/- per pair

AVO
App. Trade Mark

19 Ranges

D.C. Voltage	A.C. Voltage
0—100mV	0—10V
0—2.5V	0—25V
0—10V	0—100V
0—25V	0—250V
0—100V	0—1000V
0—250V	
0—1000V	D.C. Current
	0—100µA
	0—1mA
	0—10mA
Resistance	0—100mA
0—20,000Ω	0—1A
0—2MΩ	

List price **£9. 10s.**
complete with Test Leads
and Crocodile Clips
Leather case if required 39/-
Size 5½" x 3½" x 1½"
Weight 1 lb. approx.

AVO LTD

DESIGNED to offer the widest possible range of accurate and reliable measurements at the lowest possible price, the versatility and usefulness of the Multiminor are now further extended by specially designed leads. These new leads, available at no extra cost, will accept crocodile clips or PRODCLIPS.

The Multiminor takes full advantage of the possibilities of printed circuit techniques to achieve outstanding compactness and economy of weight. The scale is clear and open. The fine red coloured pointer and effectively damped movement facilitate easy and rapid reading. For use in radio, TV, electronics, motor vehicles, domestic appliances, workshop equipment, you'll find the Multiminor a great little meter!

MULTIMINOR

Use PRODCLIPS (Pat. No. 748811)
with the Multiminor

These cleverly designed spring-loaded insulated prods are the complete answer to a long-standing problem. Press the trigger to open, release to grip. Keep your hands free no matter how difficult of access your test points may be!

15/- per pair

MULTIMINOR

FITS THE POCKET

FILLS THE BILL

Write now for illustrated literature to:-
**AVOCET HOUSE . 92-96 VAUXHALL BRIDGE ROAD
LONDON . SW1**
VICtoria 3404 (12 lines)

A MEMBER OF THE METAL INDUSTRIES GROUP OF COMPANIES
MM.12

721

723

**For the Discerning who require
the Best Performance at Minimum Price**

HI-FI FM TUNER



This model is available as two units which, for your convenience, are sold separately. They comprise a Tuner Unit, Model FMT-4U (£32.00 including Purchase Tax) with I.F. output of 10.7 mc/s and an Amplifier Unit complete with attractively styled cabinet, power supply and valves, Model FMA-4U (£10.10.6) making a total cost for the equipment of £13.12.6.

**ELECTRONIC SWITCH Model S-3U
(Oscilloscope Trace Doubler)**



This extremely useful low-priced device will extend the application of your single-beam oscilloscope by enabling it to give simultaneous traces of two separate and independent signals. £9.18.6




Have you had details of our NEW 2 3/4" Service 'Scope yet? Model OS.1, 5" x 8" x 14". Weight 10 1/2 lb. £18.19.6.

TRANSCRIPTION RECORD PLAYER, Model RP-1U This new RP594 Collaro Transcription Unit has a Ronette Stereo Pick-up, giving excellent results on stereo or mono (33, 45, or 78 r.p.m.) discs. Complete with furniture-grade wooden plinth. £12.10.0

THE "GLOUCESTER". It will house Tape Deck and/or Record Player—as well as FM Tuner and Stereo Amplifier, and storage space is provided for records, tapes and power amplifiers. Furthermore to meet the needs of those with whom room-space is an overriding consideration, provision is made in the cabinet ends for matched Hi-Fi Stereo Speaker Systems.

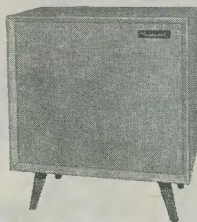
- Mk. 1. Tape Deck or Record Player. £15.18.6
- Mk. 2. Tape Deck and Record Player. £17.8.6




THE "COTSWOLD"

THE "COTSWOLD". This is an acoustically designed enclosure 26" x 23" x 15 1/2" housing a 12" bass speaker with 2" speech coil, elliptical middle speaker together with a pressure unit to cover the full frequency range of 32-20,000 c/s. Capable of doing justice to the finest programme source, its polar distribution makes it ideal for really Hi-Fi Stereo. Delivered complete with speakers, grille-over unit, level control, Tygan cross cloth, etc. All parts pre-cut and drilled for ease of assembly and left "in the white" for finish to personal taste. £19.18.6

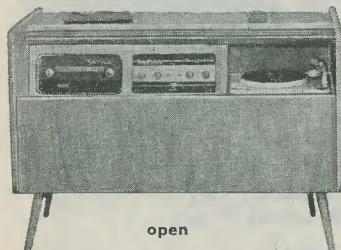**BUY YOUR HI-FI EQUIPMENT ALL TOGETHER AS ONE OF OUR
'PACKAGED DEALS' AND SAVE YOURSELF MORE MONEY!**



open

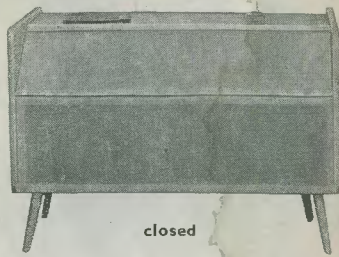


closed

DAYSTROM LTD DEPT. RCS GLOUCESTER ENGLAND

THE
"GLOUCESTER"


DEPT. RCS GLOUCESTER ENGLAND

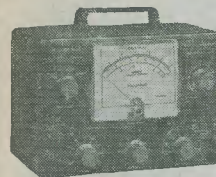**Easily-built equipment of
excellent quality at much
lower cost**



AG-9U

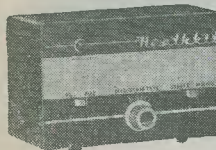AUDIO GENERATOR: AG-9U. 10 volts, 10 c/s to 100 kc/s pure sine-wave. Switch-selected frequencies/attenuation. £19.3.0



USP-1


HI-FI SPEAKER SYSTEM: SSU-1. Ideal twin speaker/ducted-reflex cabinet for stereo/mono. in average room (left "in the white"). Legs £1.7.0 extra. £10.5.6

HI-FI STEREO 6 WATT AMPLIFIER: S-33. Low-priced but high quality; less than 0.3% distn at 2 1/2 watts per channel. £11.8.0

TRANSISTOR PORTABLE: UXR-1. In elegant solid hide case, with golden relief. Six transistors, dual-wave, fine reproduction, very easy to build. £15.18.6

HI-FI STEREO BOOSTER: USP-1. Input of 2 to 20mV gives output adjustable from 20mV to 2V. Negligible distn. Also suitable as a high gain monaural amplifier. £5.19.6

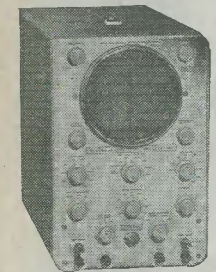HI-FI STEREO 16 WATT AMPLIFIER: S-88. Superb reproduction for the man who wants the best in Hi-Fi. Only 0.1% distortion at 6 W/chnl. Many special features. £25.5.6



O-12U

5" OSCILLOSCOPE: O-12U. "Y" sensitivity 10mV/cm., 3 c/s to over 5 Mc/s. Rise time, 0.08 µsecs. or less. Sweep, 10 c/s to 500 kc/s. Electronically stabilised. £34.15.0

VALVE VOLTMETER: V-7A. The World's largest-selling VVM. Measures Volts to 1,500 (DC & RMS) and 4,000 pk. to pk.; Resistance 0.1Ω to 1,000MΩ D.C. Sensitivity: 7,333,333 ohms per volt. £13.0.0

(Following models not illustrated)

CAPACITANCE/RESISTANCE BRIDGE: C-3U. Measures capacity, 10pF to 1,000µF. Resistance 100Ω to 5MΩ; Pwr. Factor. £7.19.6

"HAM" TRANSMITTER: DX-40U. 75 W. CW; 60 W. pk. c/c phone; 40 W. into Aerial. £29.10.0

VARIABLE FREQUENCY OSCILLATOR: VF-1U. 10V output; covers 10 to 160 metres. £10.12.0


AUDIO WATTMETER: AW-1U. Up to 25 W. continuous, 50 W. intermittent. £13.18.6

AUDIO VALVE-MILLIVOLTMETER: AV-3U. 1mV to 300V A.C. 10 c/s to 400 kc/s. £13.18.6




S-33

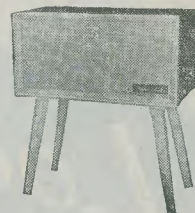Two Tape Decks (Collaro and Truvox) and Eight New Models Available this Month.



SSU-1

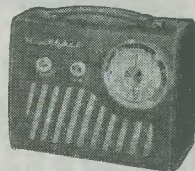

UXR-1



V-7A



S-88

**Money Saving "Packaged Deals" of Complete Stereo
Equipment from £42.10.0**

All prices include free delivery in U.K. Deferred terms available on orders above £10.

★ SEND THIS COUPON NOW FOR FURTHER INFORMATION

Without obligation please send me (Tick here)

BRITISH HEATHKIT CATALOGUE

FULL DETAILS OF MODEL(S)

(Please write in BLOCK CAPITALS)

NAME


ADDRESS

DAYSTROM LTD DEPT. RCS GLOUCESTER . ENGLAND

A member of the Daystrom Group, manufacturers of the
WORLD'S LARGEST-SELLING ELECTRONIC KITS

Patents pending

Look

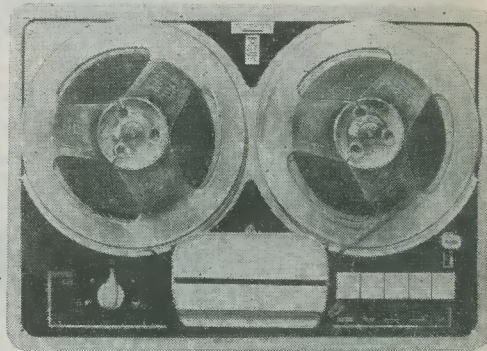

Incorporating many new features and greater frequency response.

the NEW MOTEK 3 SPEED TAPE DECK

K10



Now restyled in two tones of grey —you must see the new, attractive Motek K.10.

Enlarged drive wheel on the rev. counter ensures accurate tape positioning.

Frequency response better than 40 c/s—12,000 c/s at 7.5" per sec. with extremely low hum pick-up.

21 GNS


MOTEK

*makes a better
Recorder*

MODERN TECHNIQUES

Wedmore Street London N19 Telephone ARChway 3114

More and more manufacturers are installing Motek Tape Decks in their recorders.

LOTS & LOTS of 

**TINKERS, TAILORS,*
SOLDIERS, SAILORS,
AIRMEN, APPRENTICES & Ordinary Chaps
like You and Me Are Learning
BASIC ELECTRICITY & BASIC ELECTRONICS
THIS NEW 'PICTURE BOOK' WAY
Why don't you too?**

Now available to Civilian Readers, in eleven illustrated Manuals, is this NEW-STYLE Training Course, developed for the United States Navy by VAN VALKENBURGH, NOOGER, & NEVILLE, INC., the New York firm of Management Consultants, and adapted by a special team investigating the most modern methods of teaching Electricity and Electronics at Training H.Q. of the Royal Electrical and Mechanical Engineers.

IT HAS ALREADY BEEN ADOPTED for Training by:

R.E.M.E.—Royal Signals—Technical Training Command, R.A.F.—N.Z. & S. African Air Forces—Army of Pakistan—National Cash Register Co.—Richard Thomas & Baldwins—Uganda Electricity Board—Addressograph-Multigraph—Mullard.

*To be honest, we're not yet 100% sure of either the Tinkers or the Tailors. But there's no shadow of doubt that they all could learn Electricity and Electronics this wonderfully simple "PICTURE-BOOK WAY" if they wanted to!

COUPON - SEND NOW !

To THE TECHNICAL PRESS LTD

1 Justice Walk Lawrence St. London SW3

Please send me your FREE prospectus, describing "BASIC ELECTRICITY" and "BASIC ELECTRONICS"

NAME

ADDRESS


BUILD THE OG.10 OSCILLOSCOPE

with an
authentic

Jason kit

Britain's Finest kits

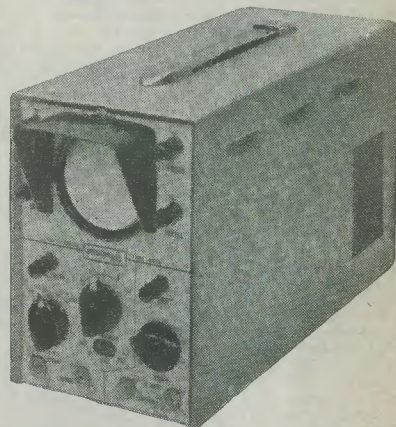For absolute assured results, build this excellent Oscilloscope with an authentic Jason kit. All parts exact to author's specification. Amongst the many uses to which this instrument may be put, TV servicing and audio amplifier checking are important examples. Sensitivity—10mV/cm with a bandwidth of 2 c/s to 1.5 Mc/s. Complete with case, Mullard C.R.T. and all valves as specified.



£22.10.0 with tube

OTHER KITS IN THE JASON PROGRAMME

AUDIO GENERATOR AG.10

Excellent stability with output held constant over entire band. Tunes from 10 c/s to 100 kc/s over four switched stages and two scales. Switch for square or sine wave. Square wave rise time less than 2 microseconds. At all frequencies. Min. calibrated output 100mV. With case, valves and calibrated scale £14.5.0 (Built £17.10.0)

CRYSTAL CALIBRATOR CC.10

Enables the exact frequency of a generator to be found between 10 kc/s and 250 Mc/s. A basic accuracy of 0.01% is achieved from a 1 Mc/s crystal. Self-powered unit complete with valves, crystal oscillator, speaker and case. £16.19.0 (Built £21.0.0)

WOBBULATOR W.11

Enables FM signals, IF signals for AM sets and TV sound and vision channels to be correctly aligned. RF circuits may also be aligned from the 40-70 Mc/s output, the second and third harmonics of which serve for Bands II and III respectively. Return trace is blanked when using a 50 c/s sine wave sweep frequency to provide a reference base line not found on most commercial instruments. £14.19.0 (Built £19.19.0)

STABILISED POWER PACK PP.10M

175mA at 300V Mains variation of ±10% produces output change of less than 0.15%. Ripple less than one millivolt. Available with or without meter. Polarity change switch. With valves, meter and case. £19.0.0

Details of the above instruments and others in the Jason range, including audio and radio units gladly sent on request. Please quote this journal when writing.

THE JASON MOTOR & ELECTRONIC COMPANY

3-4(E) GREAT CHAPEL ST. OXFORD ST. LONDON W1 Telephone GERrard 0273/4

GET YOUR AERIALS RIGHT BEFORE WINTER

HEADPHONES. H.R. type, 4,000 ohms, very sensitive. Only 12/6 pair. P. & P. 1/6. C.L.R. (low res.) 8/6. P. & P. 1/6.

NATIONAL H.R.O. CRYSTAL FILTER UNITS. 455 kc/s with crystal. Sel. and phasing controls. New boxed. ONLY 19/6. P. & P. 1/6.

MULTI-WAY CABLE. 3/8" diam. 7 colour coded wires. Ideal for mobile or inter-chassis connection. Any lengths cut, 1/3 per yard. P. & P. 1/6 min.

10-WAY CABLE (5 pairs). Screened and plastic covered. Any length cut, 2/- per yard. P. & P. 1/6 min. 7-way (unscreened), 1/3 yard.

TRANSMITTER/RECEIVER AN/PPN-2. Freq. 214/234 Mc/s. Complete in carry pack with 9 valves (5-3A5, 3-155, 1-1R5) with DUAL VIBRATOR PACKS (2V), HS '30' Phones and Antenna. Full instruction book, £3.19.6. Carriage 7/6.

ABSORPTION WAVEMETERS. 3.00 to 35.00 Mc/s in 3 switched bands, marked on scale. Complete with indicator bulb. A MUST for any ham shack. ONLY 19/6. Post free.

SPECIAL OFFER

ROTARY CONVERTERS

6V input, 250VmA output. Only 5 1/2" x 3" x 3". 17/6 each. P. & P. 3/-.

12V MINIATURE ROTARIES

Only 4 1/2" x 2 1/2" overall. Output 360V, 30mA or 310V, 70mA. NEW LOW PRICE 12/6 each or 22/6 for 2. P. & P. 1/6.

AR88 POWER TRANSFORMERS. Genuine R.C.A., few only. £2 each, carr. paid.

RELAYS (SEALED) 12 VOLT 1 1/2" x 1" x 2" d.p.s.t. contacts. Beautiful job. ONLY 5/- each. P. & P. 9d.

AR88 (D. MODEL) I.F. TRANSFORMERS (with over-coupled winding). ONLY 7/6 each. P. & P. 1/6.

VARIABLE CONDENSERS. All brass with Ceramic End Plates and Ball Race Bearings. 50pF, 5/9, 100 —6/6, 160—7/6, 240—8/6 and 300pF 9/6. Extension for ganging. P. & P. 1/-.

RACK MOUNTING PANELS. 9" x 5 1/2", 7", 8 1/2" or 10 1/2" black crackle finish, 5/9, 6/6, 7/6 and 9/- respectively, postage and packing 2/-.

► AERIAL EQUIPMENT

COPPER WIRE. 14g. h.d.: 140' 17/-; 70' 8/6; 7/25 stranded: 140' 10/-; 70' 5/- plus 2/- P. & P.

RIBBED GLASS INSULATORS. 3" 1/6 each or 6 for 7/6. P. & P. 1/6.

TWIN FEEDER. 300 ohm twin ribbon feeder, similar K25, 6d. per yard. K358 Telcon (round) 1/6 per yard. Post on above feeder and cable 1/6 any length.

SUPER AERAXIAL CABLE 1/8 per yard. P. & P. 1/6.

CERAMIC FEEDER SPREADERS. Type F.S. 6" 9d. each or 8/- doz. P. & P. 2/-.

CERAMIC "T" PIECES. Type AT for centre of dipoles, 1/5 each or 3 for 4/- P. & P. 1/6.

MOSLEY TRI-BAND BEAMS T33, JR, 3 EL ... £24.15.0
TA32, JR, 2 EL ... £17.10.0
V3 JR, Vertical 3 Band ... £7.10.0
PLACE YOUR ORDER EARLY

NEW MOSLEY POWER BEAMS. Write for details. 300 watt, 50 ohm COAX, 3/8" dia., very low loss, 1/6 yard or 20 yards 27/6. P. & P. 1/9.

CHAS H. YOUNG LTD (Dept. R)
110 DALE END BIRMINGHAM 4 (Tel. all departments) CEN 1635

FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

**We definitely Guarantee
"NO PASS—NO FEE"**

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £20 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Incorporating E.M.I. Institutes)
(Dept. SE/23), 29 Wright's Lane, London, W.8

WHICH IS YOUR PET SUBJECT?

Mechanical Eng.,
Electrical Eng.,
Civil Engineering,
Radio Engineering,
Automobile Eng.,
Aeronautical Eng.,
Production Eng.,
Building, Plastics,
Draughtsmanship,
Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

A.M.I.Mech.E.
A.M.I.C.E.
A.M.I.Prod.E.
A.M.I.M.I.
I.L.O.B.
A.F.R.Ae.S.
B.Sc.
A.M.Brit.I.R.E.
City & Guilds
Gen. Cert. of Education
Etc., etc.

PRACTICAL EQUIPMENT

Basic Practical and Theoretical Courses for beginners in Radio, T.V., Electronics, Etc., A.M.Brit.I.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation


INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. (Incorporating E.M.I. Institutes) NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T. SCHOOL OF ELECTRONICS

POST COUPON NOW!

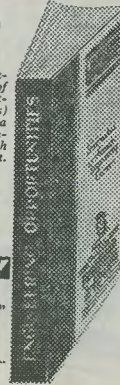■ Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES"
(Write if you prefer not to cut page)
■ NAME.....
■ ADDRESS.....
■ SUBJECT OR EXAM THAT INTERESTS ME.....



THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD

NEW!

DO-IT-YOURSELF TRAINING TECHNIQUE in RADIO & ELECTRONICS

You **LEARN** while you **BUILD**...

SIMPLE...PRACTICAL...FASCINATING...

ANNOUNCING—after many years of highly successful operation in the U.S.A. and in Europe—the latest system in home training in electronics is now introduced by an entirely new British training organisation.


AT LAST—a comprehensive and simple way of learning—by practical means—the basic principles of radio and electronics, with a minimum of theory.

YOU LEARN BY BUILDING actual equipment with the components and parts which we send you. You advance by simple steps using high quality equipment and performing a whole series of interesting and instructive experiments. No mathematics!

INSTRUCTION MANUALS and our teaching staff employ the latest techniques for showing clearly how radio works in a practical and interesting manner. You really have fun whilst learning! And you end by possessing a first rate piece of home equipment with the full knowledge of how it operates and—very important—how to service and maintain it afterwards. A full library of magnificent illustrated textbooks is included with the courses.

IN FACT for the “Do-it-Yourself” enthusiast, the hobbyist or those wanting help with their radio career training, or to set up their own full or part-time servicing business—then this new and exciting instructional system is exactly what is needed and it can all be provided at very moderate cost. Easy payments available. Post the coupon now, for full details. There is no obligation of any kind.

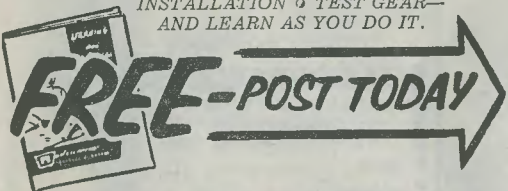BUILD YOUR OWN: • RADIO EQUIPMENT • HI-FI INSTALLATION • TEST GEAR—AND LEARN AS YOU DO IT.




RADIOSTRUCTOR

BRITAIN'S LEADING RADIO TRAINING ORGANISATION.




LOTS OF INSTRUCTIVE EXPERIMENTS AT HOME!


Power supply circuits

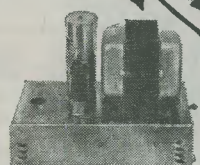


Test equipment supplied

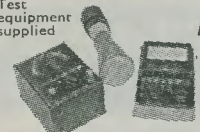

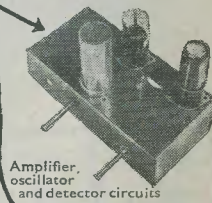Amplifier, oscillator and detector circuits



Basic 1st stage receiver

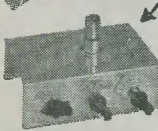

Servicing of commercial receivers



No Mathematics!

To: RADIOSTRUCTOR (Dept. G31)
40 Russell St., Reading, Berks.

Please send full details of your Radio Equipment Courses without any obligation to

Name.....

Address.....

BLOCK CAPS PLEASE

(802) We do not employ representatives 5.60

You can't help earning more!

WITH NEWNES

Radio & TV Servicing

NEW 1960 EDITION IN SIX VOLUMES



Here is the New Edition of Newnes Complete Library of Radio and TV Servicing Data. In six packed volumes it provides all the circuits, component and layout diagrams you must have for speedy, efficient repair work, tuning and general maintenance—over 2,300 models pre-1954 right up to 1960. All the famous makes below are included—everything you want for years to come. If you've never seen previous editions be sure to see this one!

TELEVISION • RADIO • RECORD REPRODUCERS
TAPE RECORDERS • TRANSISTOR PERSONALS

Servicing data for all these popular makes—

Ace, Alba, Ambassador, Argosy, Armstrong, Baird, Banner, Beethoven, Berac, Brayhead, Bush, Capitol, Champion, Channel, Collaro, Cossor, Cydon, Dansette, Decca, Defiant, Dynatron, E.A.R., Eddystone, Ekco, Elizabethan, E.M.I., Emerson, English Electric, Ever Ready, Ferguson, Ferranti, G.E.C., Grundig, H.M.V., Invicta, K-B, McCarthy, McMichael, Marconiphone, Masteradio, Motorola, Murphy, Pageant, Pam, Perdio, Peto Scott, Philco, Philips, Pilot, Portadyne, Pye, Pye Telecommunications, Radiomobile, Rainbow, Raymond, Regentone, R.G.D., Robert's Radio, Sobell, Spencer-West, Stella, Strad, Ultra, Valradio, Vidor, Walter, Webcor.

Increases your earnings for years to come

Ready for instant use are thousands of diagrams—TV receivers from single band sets to latest 13-channel 110°-tube models, including transportables, and combined TV/FM sets. Also radios, including Transistor and VHF/FM models, Radiograms, Portables, Transistor Personals, Tape Recorders, Car Radios, Record reproducers (including Stereo).

OVER
2,300
POPULAR
MODELS

MORE THAN
3,800
CIRCUIT AND
COMPONENT
LAYOUT DIAGRAMS

OVER
3,750 pages

2 years' FREE Postal
Advisory Service

EXAMINE IT AT HOME

FREE FOR 7 DAYS

WITHOUT OBLIGATION

ACT TO-DAY—PROVE ITS AMAZING VALUE

George Newnes Ltd., 15-17 Long Acre, London, WC99
Send me Newnes RADIO AND TELEVISION SERVICING without obligation to purchase. I will return it in 8 days or send 11/- deposit 8 days after delivery, then 20 monthly subscriptions of 11/- paying £11 11s. 0d. in all. Cash price in 8 days is £11.

Name.....

Address.....

Occupation.....

Your Signature.....

(Or your Parent Signs if you are under 21) **RV107**

Tick (✓) where applicable


HouseOWNER	<input type="checkbox"/>
Householder	<input type="checkbox"/>
Living with Parents	<input type="checkbox"/>
Lodging Address	<input type="checkbox"/>

HOME RADIO OF MITCHAM


Shop hours: 9-6.30 (Weds. 1 p.m.)

Telephone MIT 3282

Dept. AC
187 LONDON ROAD
MITCHAM SURREY

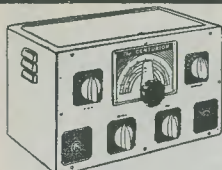


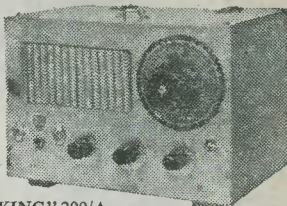**EASY-TO-BUILD
SHORT WAVE RECEIVERS**
"GLOBE-KING" 100/A one-valve kit. World-wide reception. Three matched coils covering 10 to 100 metres. Easy to build and really amazing results. Price £3.19.6 post 1/-.



"GLOBE-KING" 200/A two-valve battery set in cabinet and covering 10 to 180 metres with four matched coils. Circuit and constructional details price 2/3 post paid. All parts standard and sold separately. "GLOBE-KING" 300/A similar to above but for a.c. mains operation. All brand new high quality parts and high efficiency coils make this a real station-getter. Circuit and constructional data 2/3 post paid.

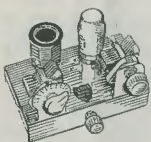"THE CENTURION" a beginner's all-wave progressive battery receiver. Can be constructed as a one-valver, then an audio amplifier stage can be added and finally a high gain r.f. stage can complete the receiver. All parts are standard and sold separately. Ready punched cabinet and chassis. Full constructional details in "Short Wave Receivers for Beginners" price 6/-, post 6d.



EVERY KEEN CONSTRUCTOR NEEDS THIS CATALOGUE

128 PAGES

4,000 ITEMS

HUNDREDS OF
ILLUSTRATIONS

ALL BULGIN AND
EDDYSTONE PARTS



BEAUTIFULLY
PRINTED


TECHNICAL
INFORMATION

ALL COMPONENTS
IN STOCK

WILL SAVE TIME
AND MONEY

DELIVERY BY RETURN — PRICE 2/- PLUS 9d POST

S.W. TUNING CONDENSERS

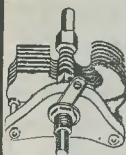


WAVE-MASTER high-grade tuning condensers with brass vanes, air-spacing and ceramic insulation. Single hole mounting and easily ganged. 15pF 4/3, 25pF 4/6, 40pF 4/9, 50pF 5/-, 60pF 5/3, 75pF 5/6, 100pF 5/9, 160pF 6/-, 200pF 7/9. Add 9d. post please.

TRANSISTORS

All brand new and tested. Audio 6/-, R.F. 9/-, Ediswan XB102 10/-, XA103 15/-, XA104 18/-, Mullard OC71 14/-, OC72 17/-, OC78 17/- (matched pairs available) Goltops Output 10/-, I.F. Amp. 10/-, R.F. Osc. 14/-, Please add 6d. postage. Transistor holders 1/-, Ardenite sub-miniature 2/9

MIDGET RADIO CABINETS

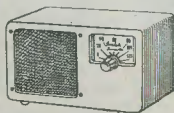

Strong well finished white plastic cabinets designed for midget radio or portables. Ideal for transistor sets or intercom. systems, etc. Size 6 3/8" x 4" x 2 1/4". Complete with back and speaker grille, etc. PRICE 10/6, post 1/-, Useful plastic speaker, grille size 3 1/2" x 6 1/2", PRICE 2/6, post 6d.

EQUIPMENT CABINETS

Well-made steel equipment cabinets, brand new and finished in latest light grey hammer stove enamel. Complete with detachable lid and front panel with undrilled chassis. Overall dimensions 12" x 7" x 7". Ideal for testgear, receivers, tuners, transmitters, etc. Similar in appearance to the Centurion set at top of this page. PRICE £2 plus 3/6 postage.

CIRCUITS FOR AUDIO AMPLIFIERS

Latest MULLARD book on audio design including constructional data on 12 different amplifiers, pre-amplifiers, tape amplifiers, mixers, stereo equipment, etc., etc. An exciting and informative book covering all aspects of audio design and practice. PRICE 8/6, post 1/-, WE STOCK ALL THE PARTS FOR THESE DESIGNS including punched chassis and special components, etc. PRICE LISTS 6d.

ALL JASON KITS

We are main stockists for all the JASON tuner and test equipment kits. Detailed price lists available on most of these on request. FMT1 f.m. tuner, FMT3 fringe area f.m. tuner, Mercury switched f.m. tuner, Mercury 11 f.m. and t.v. sound tuner, JTV2 f.m. and t.v. sound tuner, etc.

The Radio Constructor

Incorporating THE RADIO AMATEUR



CONTENTS FOR MAY

- 734 Suggested Circuits: A Visual Bell Indicator
by G. A. French
- 737 Book Reviews
- 738 In Your Workshop
- 744 Understanding Television, Part 28
by W. G. Morley
- 751 A Simple Morse Practice Buzzer.
- 752 The "Liton"—A Photo-Electric Parking Light Switch,
Part 2 described *by J. M. Ankers*
- 754 Useful Power Unit, *by J. Hillman*
- 757 Further Notes on the A.C. Millivoltmeter
by A. Bartlett Still
- 759 A Point-to-Point Two—A Miniature A.C./D.C.
Receiver for L.W./M.W. and S.W.
by A. S. Carpenter
- 764 The Cooper-Smith High Fidelity Stereo Main
Amplifier
- 771 Radio Topics, *by Commentator*
- 774 RTTY—In Theory and Practice, Part 1
by J. B. Tuke, G3BST
- 776 Increasing Tuning Indicator Sensitivity
by A. G. Pillidge
- 779 Twenty Years of Amateur Radio, *by G5UJ*
- 781 Is that Tube really Finished?
by P. S. F. Jackson
- 783 A Test Loudspeaker, *by K. E. Marcus*

Vol. 13, No. 10

MAY 1960

Annual Subscription 25/-
(including postage)

Editorial and
Advertising Offices

57 MAIDA VALE LONDON W9

Telephone
CUNningham 6141
(2 lines)

Telegrams
Databux, London

NOTICES

THE CONTENTS of this magazine are strictly copyright and may not be reproduced without obtaining prior permission from the Editor.

ARTICLES appearing in this magazine which describe kits are inserted only on condition that such kits, or special components thereof, are freely available at a trade discount to all retail advertisers.

OPINIONS expressed by contributors are not necessarily those of the Editor or proprietors.

THE EDITOR invites original contributions on construction of radio subjects. All material used will be paid for. Articles should preferably be typewritten, and photographs should be clear and sharp. Diagrams need not be large or perfectly drawn, as our draughtsmen will redraw in most cases, but all relevant information should be included.

ALL MSS must be accompanied by a stamped addressed envelope for reply or return. Each item must bear the sender's name and address.

TRADE NEWS. Manufacturers, publishers, etc., are invited to submit samples or information of new products for review in this section.

TECHNICAL QUERIES should be submitted in writing. We regret that we are unable to answer queries, other than those arising from articles appearing in this magazine; nor can we advise on modifications to the equipment described in these articles.

ALL CORRESPONDENCE should be addressed to THE RADIO CONSTRUCTOR 57 Maida Vale London W9. REMITTANCES should be made payable to "DATA PUBLICATIONS LTD."

suggested circuits

No. 114 A Visual Bell Indicator

The Circuits presented in this series have been designed by G. A. FRENCH, specially for the enthusiast who needs only the circuit and essential data

THE WRITER HAS RECENTLY RECEIVED several requests from readers for the circuit of a device which will give visual warning, by causing a lamp to be illuminated, whenever a bell is rung. A device of this nature may then be used for such purposes as advising television viewers or those who are hard of hearing that a front door bell has been rung. An important feature asked for by the writer's correspondents was that the warning light should remain illuminated for about a minute or so after the appropriate bell-push had been released. This would ensure that the visual warning was not missed, and it would also enable lighting circuits to be operated at the bell-push itself. Another requirement was that the warning lamp circuit should be capable of being easily connected into existing bell wiring.

Bell Transformers

A device of this nature must inevitably employ some form of switching device, the obvious choice here being a simple relay. The necessity of having the switching circuit remain completed for a period as long as a minute after the bell-push has been released raises another complication. This period is far longer than could be accommodated by capacity in direct combination with a relay coil without the introduction of high operating potentials, and so the use of a valve or transistor becomes almost inevitable.

In consequence of these factors, some form of power supply for the lamp switching circuit becomes necessary. A further point is that this power supply will have to be available continually, even if the switching circuit is called upon to operate as infrequently as once a day.


The writer decided that the best solution to the power supply problem would consist of employing a bell transformer, this transformer serving also to provide operating current for the bell itself. In many cases such a transformer would already be in use, with the result that the switching device would merely need to be added to it. If the existing bell circuit was powered by batteries, the introduction of a bell transformer would not upset bell operation or wiring and would offer an inexpensive method of obtaining the power required from the mains.

A bell transformer is intended to operate with its primary connected permanently to the mains supply, the bell circuit being fed from its secondary. The current drawn from the mains by the continually-connected primary is negligible. It is usual for the secondaries of bell transformers to offer 8 volts, with a tap at 3 or 4 volts. As the transformers are called upon to give low secondary currents at occasional times only, secondary voltage regulation is markedly inferior to that given by mains transformers of the type encountered in electronic work.

In order to ascertain whether a bell transformer, with its attendant poor regulation, would be suitable for the proposed switching circuit the writer decided to check the performance of a typical component of this type. An inexpensive transformer was purchased at a popular chain store, this claiming a total secondary output of 8 volts at 0.5A. The transformer was very small in physical size, measuring in its plastic case 2½ in x 1½ in x 1½ in. When tested it was found that the total secondary voltage was 8.3 off load, this dropping to 6.9 volts at a current of 0.3A. It was felt that the source resistance of the transformer secondary calculated from these figures—approximately 5Ω—was sufficiently

ary are rectifier W_1 and condenser C_1 . In consequence, a steady potential close to the peak value of the secondary voltage is continuously available across C_1 , and this is applied to the relay coil in series with the emitter-collector terminals of the transistor. Normally, the base of the transistor is at the same potential as its emitter, and negligible collector current is passed.

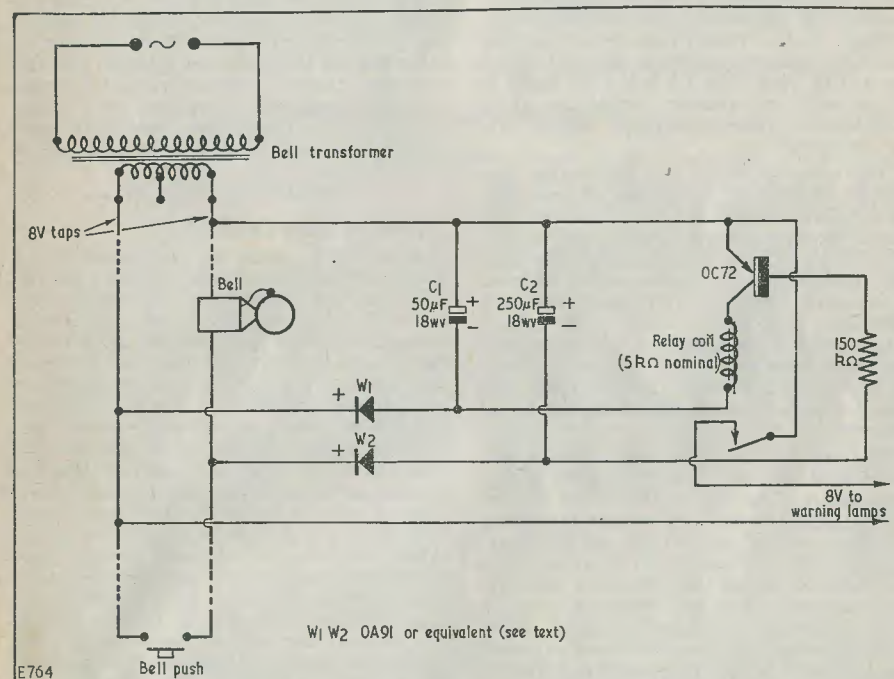When the bell-push is pressed, the transformer secondary is connected across the bell, which then rings. The secondary voltage is also applied to rectifier W_2 and condenser C_2 , causing the condenser to charge and a negative voltage to be applied to the 150kΩ resistor connecting to the base of the tran-



low for the requirements of the switching circuit, and would be representative of typical bell transformer performance. Indeed, the 5Ω figure might well be higher than that offered by larger and more expensive components.

The Circuit

The warning light switching circuit employing the bell transformer as a source of power accompanies this article. The secondary of the transformer connects, via the bell, to the bell-push in conventional fashion. Connected permanently across the transformer second-

istor. The transistor at once conducts and energises the relay, whereupon the relay contacts connect the transformer secondary to the warning lamp circuit.

Whilst the bell-push is depressed C_2 remains fully charged. As soon as the bell-push is released this condenser commences to discharge, discharge currents flowing through the 150kΩ resistor and the base-emitter circuit of the transistor, and through the back resistance of W_2 and the bell. After a period, C_2 discharges such that the transistor collector current is sufficiently low to

allow the relay to de-energise. The warning lamps become extinguished, and the circuit is ready for the next operating cycle.

Practical Points

There are a number of practical points in the circuit which need to be discussed.

The first of these concerns the warning lamps. Paying regard to the 0.5A secondary rating of the transformer employed in the prototype, it was considered advisable for the warning lamps to consume a current of 0.3A maximum. Such a current is sufficiently high to enable conventional flash lamp bulbs to be employed. One or more 0.3A bulbs may then be employed in series in the warning lamp circuit, a series resistor being inserted, if felt necessary, to drop excess voltage. In the writer's case it was felt that, since the secondary voltage dropped to 6.9 for a 0.3A load, two 3.5 volt 0.3A bulbs in series with no resistor would be quite satisfactory. This combination was used in the prototype.

The relay employed is a lightweight type which energises at a current of less than 2mA.* For operation in this circuit the relay should be set up to energise at a coil current of 1.75mA. Under this condition the relay will de-energise at approximately 0.5mA. It is usual, when a relay is energised via a transistor, to connect a diode across the coil to prevent the formation of high voltages if the relay energising current suddenly drops. In this circuit the energising current falls gradually, and a diode across the coil is not necessary.

The rectifiers W_1 and W_2 , actually germanium diodes, are specified as OA91's or equivalents. The requirements here are not critical, apart from the fact that the diodes employed should have a maximum inverse voltage rating in excess of 20 volts. It is desirable to ensure that W_2 does not have an excessively low back resistance, or C_2 will discharge too rapidly. The writer checked several diodes of different type and manufacture in the W_2 position, however, and encountered no undue trouble on this count.

Similarly, in order to prevent too rapid a discharge in C_2 , it is advisable to ensure that this component has a high leakage resistance. A new component of reliable manufacture should be fitted here. The length of time over which the relay remains energised may, of course, be increased or decreased by modifying the value of this condenser.

It will be noted that the rectifier circuit W_1 , C_1 , and the transistor and relay coil, are connected across the bell transformer secondary permanently. This method of operation is quite permissible, as the standing

current drawn by these components is negligible.

Operation

It was found that, after completion, the circuit worked with complete reliability. The relay energised immediately the bell-push was pressed, and it remained energised for 55 to 75 seconds after the bell-push had been released. The reason for this variation in times was that relay energising current decayed very gradually after the first 40 seconds or so of discharge in C_2 had taken place. In consequence, slight variations in relay de-energising current had an exaggerated effect on timing periods.

The voltage across C_1 was 11.5 before the bell-push was pressed. With the bell operating, it dropped to approximately 7, rising to 9.5 when the bell-push was released and the warning lamps were drawing current. Despite continual repetition of circuit operation the transformer remained completely cool, and there was no evidence of over-running.

Alternative Lamp Circuits

Apart from giving an indication that a door bell has rung, the circuit may be employed for other uses. A particularly attractive idea consists of having the relay energise a heavier relay capable of switching mains voltages. Pressing the door bell may then cause a porch light to be switched on and remain illuminated during the time needed to allow a visitor to enter. An alternative idea, for use when the device is used by those who are hard of hearing, consists of having a warning lamp illuminate a panel near the bell-push. This panel could then bear a legend such as: "Visual Door Alarm—Please Be Patient". Only one additional lead from the switching circuit to the bell-push is needed for this facility, as one of the leads to the bell-push is already common to one side of the warning lamp circuit. A suitable printed panel, which may be cut out if desired, appears with this article.

DEAF

VISUAL DOOR ALARM PLEASE BE PATIENT

* A suitable relay is available from Home Radio (Mitcham) Ltd., under Catalogue No. Z.70.

OBITUARY

It is with deep regret that the Directors of Data Publications Limited have to announce the sudden and unexpected death, on Wednesday 23rd March, of their friend and colleague, Mr. C. W. C. Overland.

Mr. Overland was, of course, Editor of *The Radio Constructor*, and his untimely passing is a sad and personal loss to all connected with this magazine.

Mr. Overland, who was only 48 years of age, was educated at Haberdashers' Aske's Hampstead School, and before becoming a technical journalist was a radio engineer. He was a founder member of Short Wave Press, as Data Publications Limited was then called, and an original Director. In 1949 he became Editor of *The Radio Constructor*. In addition to his other activities he took a leading part in the formation of the International Short Wave League and was a prominent radio amateur with the call sign G2ATV.

Cremation took place at the West London Crematorium on Tuesday 29th March, the service being conducted by the Revd. George E. Easter. Many friends and business acquaintances attended.

To his widow and two sisters we extend our deep sympathy and sincere condolences.

BOOK REVIEWS

W. E. Thompson

EXPERIMENTAL RADIO ENGINEERING (4th Edition). By E. T. A. Rapson, M.Sc. (ENG.) LONDON, A.C.G.I., D.I.C., M.I.E.E., M.B.R.I.T.R.E. 201 pages, 207 diagrams. Published by Sir Isaac Pitman & Sons Ltd., Pitman House, Parker Street, Kingsway, London, W.C.2. Price 12s. 6d.

Since this book was first published in 1940, students of radio technology have regarded this book as a standard textbook on experiments and measurements. From time to time the author has revised his text, deleting out-of-date experiments and introducing modern methods, and taking each opportunity to keep abreast of the times.

The original pattern has not changed; indeed, it does not need to. The text consists of 95 experiments. The subject is stated, and the procedure to be adopted is described. The results of the experiment are then set down, and the conclusions to be drawn are briefly stated. The procedure and results contain diagrams of the circuit or function to be investigated, and curves, tables, or other parameters illustrate the results. At the end of the book, the conclusions for each experiment are described in detail.

The student is thereby enabled to take any experiment he chooses and learn by making his own tests and measurements far more than he would by merely reading about it. The book has thirteen sections, dealing with series and parallel tuned circuits, coupled circuits, static characteristics of thermionic valves and transistors, dynamic constants of thermionic valves, characteristics of amplifiers, rectifiers and demodulators, valve oscillators, audio-frequency measurements, radio-frequency measurements, attenuators and filters, radio receiver tests, electro-acoustic tests, cathode-ray tubes, timebases and applications.

AUTO RADIOS. By Jack Darr. 154 pages, 100 diagrams and illustrations. Published by John F. Rider Publisher Inc., 116 West 14th Street, New York. Available in England from Messrs. Chapman & Hall Ltd., 37 Essex Street, London, W.C.2. Price 26s.

The business of fitting and maintaining car radio installations is more prolific in America than in this

country. It is inevitable, therefore, that a book which originates in the U.S.A. should deal exclusively with car radios made there, but much of the material and information available in this book can apply to a great extent to similar installations over here. One needs to have a fair acquaintance with terminology used for American cars, in order to follow correctly some of the statements made, otherwise it might be easy to mount a whip aerial in some inaccessible and ridiculous position!


There is a lot of good advice, practical experience, and sensible diagnosis to be found in Jack Darr's book. He deals very well with the problems of interference sources and the methods of suppression, and the servicing of the car radio receiver and power supplies. Transistorised and hybrid receivers are very well described, and a useful chapter on the service workshop provides plenty of valuable know-how for the service engineer. A short chapter discusses ways of converting from 6V to 12V supplies.

FUNDAMENTALS OF RADIO AND ELECTRONICS (2nd Edition). Edited by W. L. Everitt. 805 pages, 592 diagrams and illustrations. Published by Constable & Co. Ltd., 10 Orange Street, London, W.C.2. Price 57s. 6d.

As is to be expected with a book of this size, the field covered is fairly wide. It delves far deeper into fundamentals than many other smaller books can hope to do, mainly because these latter are primers rather than textbooks. The first three chapters introduce the reader to the mathematics applicable to radio, and take a brief look into d.c. and a.c. theory. From this point onwards, progress becomes more rapid and advanced, taking into consideration en route many aspects of radio technique which less pretentious books would have no room for.

Although some matters are not dealt with as fully as the title suggests, there are other textbooks from which more could be learned. If this statement seems to counter what has been said in the previous paragraph, it should be explained that to deal fully with, say, all the aspects of low-frequency amplification, rectifier circuits, and transmitter techniques, the book would extend somewhat beyond the concepts of fundamentals; it therefore seeks to give a good insight into many subjects, and frequently touches upon high-power equipment. It follows that those seeking specialised knowledge on a particular subject will find in this book enough to take them well on the road of understanding, and lead them to the wider fields to which other works can steer them.

In your Workshop

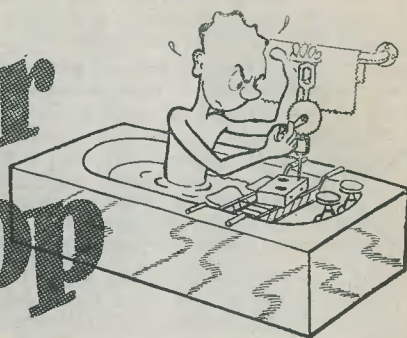

This month Smithy the Serviceman and his able assistant, Dick, discuss a number of diverse subjects, these ranging from television tuner drift to film projection cues

RUSH, RUSH, RUSH", COMPLAINED DICK, "rush, rush, rush!" Smithy the Serviceman glanced round at his assistant.

"Last month", he pointed out, "you were grumbling because things were too quiet."

"That may be", said Dick, "but the present situation is ridiculous!"

Smithy's assistant glanced round at the chock-full "awaiting-repair" rack.

"Dash it all", he remarked, "the sets are overflowing from the rack on to the floor!"

Hum on F.M.

"All the more reason", said Smithy, "for you to apply some really speedy troubleshooting tactics on them."

"That's all very well," replied Dick hotly, "but some of the faults I'm getting aren't too easy. For instance, I've got an a.m./f.m. job on the bench now which hums on f.m. only. And you should just see the wiring around the wave-change switch!"

"A.M./F.M. switching circuits do get a little complicated in some receivers," conceded Smithy. "But the fault needn't necessarily be in the switch wiring. Does your set hum all the time, or just on stations?"

"It hums a bit between stations, and a lot when a signal is tuned in."

"Sounds like modulation hum."

"That's what I thought," said Dick. "So my first reaction was to change the double-triode r.f. and oscillator bottle."

"A very obvious step," approved Smithy.

"A little leakage between heater and, say, oscillator grid (Fig. 1 (a)) can cause enough 50 c/s a.c. to appear on the latter to give you quite heavy modulation hum. What happens, of course, is that the oscillator frequency then becomes frequency modulated at 50 c/s, and frequency modulates any incoming signal in consequence."

"With the result", chimed in Dick, "that the 50 c/s frequency modulation is detected by the discriminator. Whose job it is to do just that! Anyway, I'd have thought that cathode-heater leakage would have been a more probable snag than grid-heater leakage."

"Not these days," said Smithy, "because almost all modern v.h.f. oscillators have their cathodes anchored very securely down to deck. In earlier times, manufacturers used to use e.c.o.s (Fig. 1 (b)), with the result that cathode-heater leakage could cause quite a lot of trouble."

"Is that why e.c.o.s aren't used now in v.h.f. receivers?"

"Partly," said Smithy, "and partly because the heater used to jump around in the cathode occasionally, causing a very disconcerting change in frequency because of the alteration in stray capacities. Anyway, to return to your set, do I presume that swapping the double-triode didn't clear your trouble?"

"You do," replied Dick. "The next things I thought of were such terrible subjects as leaks in its valveholder, but as the one in this set was pot I decided it should be safe enough."

"Pot?"

"Ceramic."

"Ah, yes," said Smithy. "A ceramic valveholder should be safe enough. Besides, one doesn't go around changing valveholders just like that. Especially valveholders in v.h.f. circuits. There are plenty of other things to suspect before that stage is reached."

"So I proceeded", continued Dick, "to take a perfunctory at the h.t. supply to the oscillator. A bit of ripple on that could easily give modulation hum." Smithy nodded approvingly. "So I temporarily popped an extra 200 μ F which was lying around across the oscillator h.t. supply." Smithy winced. "But the hum remained."

"I've been wondering where the sparks were coming from," commented Smithy. "I don't disagree with popping extra capacity across a suspect smoothing condenser, but there's no need to go mad. 16 μ F is quite big enough for sound receiver servicing."

"I think, anyway," continued the Serviceman, "that you're following the classic approach to this particular problem. But I would, myself, have tried one or two more valves before delving into the works and checking smoothing. If the hum only appears on f.m. you should say to yourself: what valve performs a different function on f.m. to that which it performs on a.m.? The very first valve that comes to my mind in answer to this question is the triple-diode-triode (Fig. 2.) This has two diodes and the triode around one cathode, and a completely separate diode around a second cathode. In conventional circuits, the separate diode is only used for f.m. Another valve which changes functions when you switch from a.m. to f.m. is the triode-heptode or -hexode frequency-changer. The heptode, or hexode, section normally becomes a straightforward 10.7 Mc/s i.f. amplifier on f.m. In most sets the triode section is killed on f.m., but in some it is switched into circuit as an extra a.f. voltage amplifier. So I should certainly check the triple-diode-triode and frequency-changer in your set before looking anywhere else, the triple-diode-triode being the more likely suspect so far as modulation hum is concerned."

As Smithy spoke, Dick was already rummaging around in the valve cupboard. He soon found a new triple-diode-triode and plugged this into the faulty receiver.

"Ah," he remarked in a pleased tone, as the receiver came to life, "that's cleared the hum!"

"Good," said Smithy. "It turned out to be easy enough after all, didn't it? I should guess that there's a bit of heater-cathode leakage in the separate diode of the bottle which caused the hum."

"It seems a pity to throw it away, though," said Dick, "especially when you consider that only a quarter of it has gone up the wall! The receiver I've been fixing is a universal one, so couldn't I try it in a set with a mains tranny, where the heaters wouldn't have so high a potential above chassis?"

"I think you'd be wasting your time," remarked Smithy. "Because you'll very probably find that the triple-diode-triode is at the earthy end of the heater string in your set anyway. However, if you feel all that hard-up I suppose you could use it in a

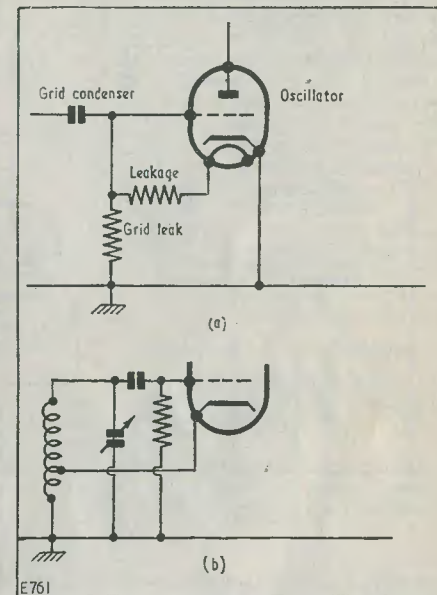


Fig. 1 (a) Leakage between grid and heater of the oscillator in an f.m. receiver may cause modulation hum. (b) A type of oscillator (actually a modified Hartley) which is commonly referred to as an electron coupled oscillator (e.c.o.). For true electron coupled operation the valve would be a screen-grid or pentode type, an output at oscillator frequency being obtained from its anode

conventional a.m. circuit, ignoring the separate diode."

Drifting Tuner

By now Dick had replaced the cabinet on his receiver and was carrying it to the "repaired" rack. He next selected a very new-looking television receiver for repair, and Smithy returned to his own work.

But not for long.

"Hey, Smithy."

The Serviceman grunted a non-committal reply which Dick decided was an invitation for further conversation.

"This t.v.'s slipped a channel!"

"What?"

"That's right," said Dick. "Our local Band III transmitter's on Channel 9 but I can only get it on Channel 8 on this tuner! Also, it's rather weak."

"Try Band I," suggested Smithy.

A quick succession of loud clicks from

receiver.

"Hmm," he said. "The fine tuner has to go right over to the full capacity end to get a correct signal. It seems as though the oscillator tuned circuit section in the innards of the tuner has lost a bit of capacity, or, perhaps, inductance somehow; that would explain why I have to put the fine tuner over to maximum capacity on Band I to make up for the loss. The loss in capacity probably has much more effect at Band III, and you have to put extra inductance in as well to make up for it. That's why you get Channel 9

complained Smithy.

"The turret's meant to be turned," said Dick in an injured tone, "and the insides of all t.v. tuners I've seen are definitely of the heavy engineering variety."

"But the knob isn't," said Smithy. "There may be as much as two inches of horrible brittle plastic between the bit of the knob that you handle and the point where it couples to the shaft. I'm not saying that you should treat the knob as though it's going to fall to pieces in your hands, mum, but there's no sense in tempting fate. You know," continued Smithy, completely forgetting the fault Dick had presented for his attention, "the fragile knobs that manufacturers put on sets these days really give me the willies. Indeed, if there's one thing that has taken the fun out of engineering it's knobs!"

Dick, perceiving that Smithy had mounted one of his favourite hobby-horses, hastily interrupted him.

"We're on Channel 8."

"Are we?" said Smithy absent-mindedly.

"Oh, yes, so we are. Right, now, let's have a look. This time we get our picture, but only just, with the fine tuner hard over at its low capacity end. What I think is happening here is that the fine tuner has got a pretty wide range on Band III, and it's not to be unexpected that we can just raise Channel 9 on the extreme end of Channel 8. The signal is rather weak because the r.f. coils are, obviously, adjusted for Channel 8."

"What do I do now?" asked Dick. "Re-align the oscillator cores on Channel 9 and the Band I channel and send the set out again?"

"How long has the receiver been in the customer's house?"

"Just about a week, I should guess," said Dick, examining the card wedged into its back.

"The weather has been a bit damp over the last few months," said Smithy, returning to his bench.

Dick looked a little baffled at this apparently inconsequential remark.

"But what shall I do?" he asked again.

"I should switch the set back—gently this time—to the Band I channel," said Smithy over his shoulder. "And pop it on soak with a locked picture for twelve hours or so. Then re-align the oscillator cores and send it out. I would say that the receiver was stored before sale in a dampish place, with the result that enough moisture got into the tuner to increase the internal stray capacities and throw the oscillator off tune. Very probably, the oscillator cores on the two local channels were re-aligned when the set was installed in the customer's house. Now that the set's started to dry out again with use, the

oscillator cores want to go back to the position they held when they were aligned in the factory. If you put the set on soak you should dry the tuner out sufficiently for it to become stable again."

"Well, that's a queer howdyedo," remarked Dick.

"Not really," said Smithy. "You've got an oscillator running at 200-odd megs in that tuner. It doesn't take much to throw it off a wee bit."

"Why have the set soak with a locked picture?"

"Because," said Smithy patiently, "you then keep the line timebase running at correct frequency and there is less risk of e.h.t. voltage variation. If the e.h.t. voltage rose too high over long periods something might go quite unnecessarily pop. Incidentally, I'm surprised to note that your customary curiosity hasn't caused you to ask why I told you to try Band I after your announcement that the set had slipped a channel."

"I did miss that," admitted Dick. "What was the reason?"

"It was that I didn't want a repetition of a true case I heard about recently where the tuner had slipped a channel on both Band III and Band I. The service engineer on the job swapped two tuners unsuccessfully before he found the fault."

"What was it?"

"The tuner knob had been fitted incorrectly with the little plastic slip which shows the channel numbers!"

Dick laughed.

"Well, I can't say I'd fall for that one."

"I'm not so certain," remarked Smithy. "Anyway, you'd better get that set on soak."

Reedy Output

Dick did as he was bid, and the Serviceman was allowed to continue uninterrupted with his own job as his assistant selected yet another television receiver from the rack.

"Smithy," he called out after a moment.

The Serviceman placed his screwdriver down on the bench with quite unnecessary violence.

"What is it now?"

"I've got a set like what you talked about last month," replied his assistant ungrammatically. "Listen, it's giving a thin and reedy sound output."

"Your first horrible sentence," remarked Smithy dispassionately, as he wearily walked over again to his assistant's bench, "reminds me of the little boy in bed who said: 'What did you bring that book I don't like to be read to out of from up for?'"

However, Smithy's comments on syntax were lost on Dick, who was interested only in his faulty receiver. He turned its volume control to full, whereupon the sound of weak

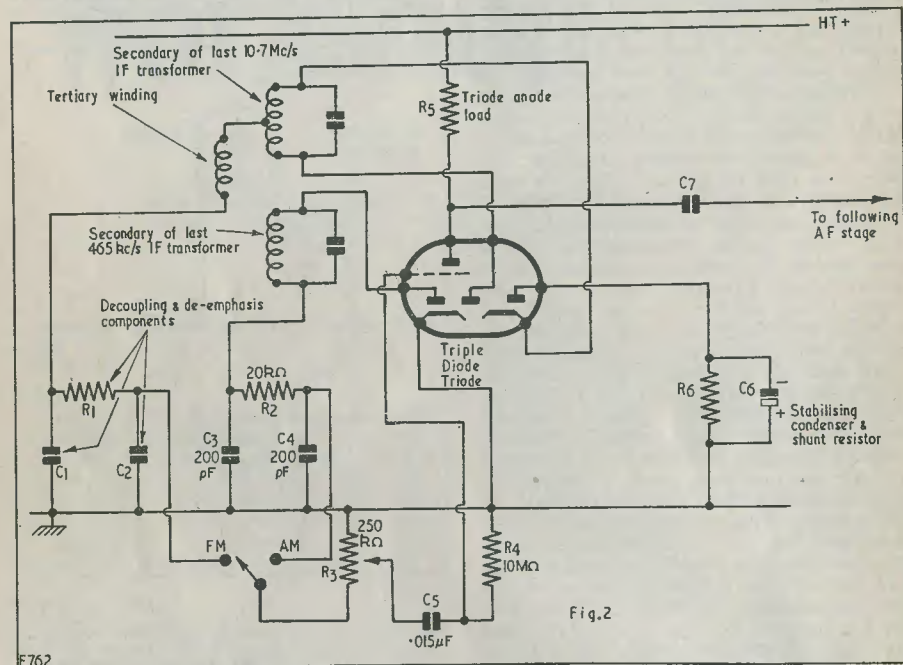


Fig. 2. Illustrating, in simplified form and with representative component values where generally applicable, the type of circuit likely to be encountered at the triple-diode-triode stage of an a.m./f.m. receiver. The 465 kc/s secondary has one end connected to the left-hand diode, and the other end to the decoupling filter C₃, R₂, C₄. When the switch is in the "a.m." position, the detected 465 kc/s signal appears across the volume control R₃. The 10.7 Mc/s secondary connects via the centre and right-hand diodes to the stabilising condenser and shunt resistor, following normal ratio discriminator practice. A.F., available from the tertiary winding, passes through the filter and de-emphasis components, C₁, R₁, C₂, and the switch (when in the "f.m." position), to the volume control R₃. Leaky-grid bias for the triode voltage amplifier is provided by C₅ and R₄

Dick's bench announced that he was energetically obeying Smithy's instructions.

"It's O.K. on Band I," he announced. "At least it's coming up on the right channel, and at proper strength. The fine tuner isn't half 'endey', though."

Smithy left his bench to look at Dick's

by going down a channel. Switch back to Channel 8."

The turret indexing mechanism, subjected to Dick's muscular handling, clattered briskly as he wrenched the knob to its new position.

"I do wish you wouldn't be so vigorous,"

and high-pitched music came from the cabinet. Smithy applied his ear to the speaker, and then to the back of the cabinet.

"What you've got there," he said, "is an o/c loudspeaker speech coil circuit. The sound you can hear is coming from the unloaded a.f. output transformer!"

"You mean, the output tranny is operating as a loudspeaker?"

"That's right. It makes a very insensitive speaker and it is hardly in the hi-fi class, but it can still give an audible output. I should turn down the volume before you break down the primary. There are probably some pretty fantastic a.f. voltages appearing across it if its secondary isn't loaded."

Obediently, Dick turned the volume control half-way back, whereupon the weak and tinny sound of music became inaudible.

"Well, the speaker secondary circuit looks O.K.," he remarked, after a quick visual examination. "There are two leads well and truly soldered to the speaker transformer tags, and these go to two pins which are fully inserted into two sockets at the speaker. And the wires from the sockets to the speaker are perfectly soldered as well."

"I should waggle the pins about a bit," said Smithy laconically.

"But they're fully inserted into the sockets."

Smithy sighed. Dick could be very trying at times.

"Just waggle them," he said patiently.

Dick gave the pins an exploratory poke with a screwdriver. Immediately the sound of music at good quality came from the previously silent loudspeaker.

"Well, I'm dashed," remarked Dick.

"So you ought to be," growled Smithy. "The trouble with you is that you don't listen to what your elders and betters see fit to tell you."

With this somewhat pompous statement Smithy strode majestically back to his neglected bench. The dignity of the occasion was, unfortunately, marred as he accidentally caught his feet in the lead to his soldering iron; with the result that it flew smartly into the air and crashed to the floor, to be followed by the clattering fall of its stand. Commendably, Dick maintained a straight face.

"You should always look out," continued Smithy, grinning despite himself as he picked up the lately airborne iron, "for snags of this type in speech coil circuits. These circuits are pretty low impedance, and I've had quite a lot of trouble in the past with speaker plugs and sockets which look as though they're making contact but which, in actual fact, are not. In your case I should pull out the plugs and tighten the contacts up a bit

before you finally count the set as being fixed."

"Fair enough," said Dick, briskly. "Consider the job done!"

Film Projection

Smithy was in process of finally aligning a receiver when his assistant's startled voice upset his concentration.

"Do you know what time it is?" exclaimed Dick in a shocked voice. "It's nearly lunch time!"

"So it is," remarked Smithy equably, as he finally adjusted the r.f. trimmer. "Dear me, the time *does* fly when you're busy."

"Well, I've certainly been busy, myself," said Dick boastfully. "The successful repair of a radio and two TVs isn't bad for a beginner."

Smithy forebore to answer this last remark.

"I suppose it won't kill us to have a break for the next few minutes or so," he remarked, after a moment. "Besides, I've got a letter I want to read out to you concerning our recent conversation on film signals.¹ Do you remember?"

"Shall I forget? After you told me that signals appear near the end of each part to warn the operator that a change-over is due, I haven't enjoyed a single film. I've been looking for signals in the top right-hand corner ever since."

"Well," replied Smithy, "listen to what my correspondent has to say.² 'As a cinema projectionist I was very interested to read January's episode of the *In Your Workshop* series.

"As a conscientious operator I would like to raise a cry at your expression "big scratches in the film emulsion, and all sorts of things like that". This is like accusing a serviceman of joining a flexible p.v.c. lead to the end of a resistor with a "twisted" connection, no sleeving, and stretching the wire around a valve pin to keep the joint taut off the chassis! All the more respectable cinemas nowadays are equipped with a stencil device which clamps the film and makes a neat cue almost indistinguishable from a printed one.

"Several modern theatres do not use cues at all, but are equipped with electronic apparatus which not only makes change-overs automatically but also performs all the other important operations, such as closing and opening curtains, switching sound disc/film, raising and dimming lighting (by saturable reactors); in fact, running the whole show automatically.

¹ "In Your Workshop", January 1960 issue.

² This letter was sent by David Fenner of Dunstable, who is a projectionist at the Odeon, Luton.

"The heart of the device is a thyatron (GT1C) actuated by short lengths (about $\frac{3}{8}$ in) of metallic adhesive tape stuck on the edge of the film by the projectionist beforehand. Contact is made over the two halves of a split roller, which are connected in the grid circuit of the valve. As a mark passes over the roller, the grid bias is lowered, allowing an electrolytic of large capacity to discharge through the valve, closing relays in the anode circuit.

"Hoping these remarks have given you a fraction of the interest that *In Your Workshop* gives to me.

"Yours truly,

"DAVID FENNER.

"P.S.—The interval between cues is 8 secs., not 10."

"Well, that's very nice," remarked Dick. "And I always did think that your 10 second

figure was wrong. I've been checking with my watch at the cinema and I've made it eight seconds every time."

Smithy looked suspiciously at his assistant, but Dick's expression was completely guileless.

"Also," continued Dick, "the only times I've seen bad scratches on the emulsion has been on Continental 'X' films which have been going around for years."

Smithy looked slightly embarrassed.

"Well, I suppose," he remarked, "that as one gets older one tends to search for film entertainment which is a little more sophisticated than the ordinary run of things. Films," continued the Serviceman, "whose subject matter is a little *meatier* . . ."

By now, Dick had completely failed to retain his straight face, and the remainder of Smithy's remarks were lost in derisive laughter.

I.A.R.U. REGION I CONFERENCE

An International Amateur Radio Union (Region I Division) Conference will be held at the Grand Hotel, Folkestone, Kent, from Monday 13th June to Friday 17th June, 1960, with the Radio Society of Great Britain acting as Host Society.

Invitations to attend the Conference have been sent to all subscribing I.A.R.U. Member Societies in Region I and acceptances have been received from Denmark (E.D.R.), Finland (S.R.A.L.), France (R.E.F.), Germany (D.A.R.C.), Ireland (I.R.T.S.), Italy (A.R.I.), the Netherlands (V.E.R.O.N.), Norway (N.R.R.L.), Poland (P.Z.K.), Spain (U.R.E.), Sweden (S.S.A.), Switzerland (U.S.K.A.), Yugoslavia (S.R.J.). Replies are awaited from Belgium (U.B.A.) and Luxembourg (R.L.).

In addition to the delegates officially appointed by the Member Societies, observers will be permitted to attend the Conference provided their names and addresses are submitted to the General Secretary of the R.S.G.B. at least two weeks before the opening of the Conference.

Visitors to the Conference will be accommodated at the Grand Hotel at the specially reduced inclusive charge of 50s. per day which will cover service and all meals (breakfast, lunch, afternoon tea and dinner). The hotel—situated on the famous Leas—has a commanding view of the English Channel and is one of the best appointed on the south coast.

The Conference will be opened at 2.30 p.m. on Monday 13th June by the Mayor of Folkestone, after which a Plenary Meeting will be held to elect the chairmen and secretaries of committees. Three main committees will be set up, namely, Administrative

and Operational, Technical and V.H.F., plus an *ad hoc* Credentials and Finance Committee.

A tentative programme of events is set out as follows:

Sunday 12th June
Delegates assemble at the Grand Hotel

Monday 13th June
9.30 a.m. Meeting of the Executive Committee
2.30 p.m. Official Opening
3.00 p.m. Plenary Meeting
4.00 p.m. Meetings of main Committees
5.00 p.m. Meeting of Credentials and Finance Committee
9.00 p.m. Film show "The Geneva Radio Conference" by Major Per-Anders Kinnman, SM5ZD (Vice-Chairman Executive Committee)

Tuesday 14th June
9.30-5.30 p.m. Meetings of Committees
9.00 p.m. Display of colour transparencies by Mr. Arthur Milne, G2MI, and Dr. Arthur C. Gee, G2UK

Wednesday 15th June
9.30-5.30 p.m. Meetings of Committees
8.00 p.m. Evening Coach Trip

Thursday 16th June
9.30 a.m.-12.30 p.m. Free for shopping
2.30 p.m. Visit to Canterbury and the Weald of Kent as guests of the Mayor and Corporation of Folkestone

Friday 17th June
9.30-5.30 p.m. Plenary Meeting
7.30 p.m. Conference Dinner

Saturday 18th June
Delegates depart

The cost of the Conference Dinner is not expected to exceed 21s. a head.

The Folkestone Corporation is to issue trilingual privilege tickets which will enable delegates, observers, and their ladies to enjoy many local facilities free of charge.

Further details can be obtained from the General Secretary of the R.S.G.B. (Mr. John Clarricoats, O.B.E.), 28 Little Russell Street, London, W.C.1.

UNDERSTANDING TELEVISION

PART 28

By W. G. MORLEY

The twenty-eighth in a series of articles which, starting from first principles, describes the basic theory and practice of television.

IN LAST MONTH'S ARTICLE IN THIS SERIES WE discussed the construction of the line output transformer, and dealt with line output stage circuits which differ from the more conventional arrangements described earlier. We now carry on to methods of improving e.h.t. voltage regulation, to the question of interference generated by the line output stage, and to width controls.

Improving E.H.T. Regulation

Several circuit devices may be encountered in television line output stages whose function is that of improving e.h.t. regulation and of keeping e.h.t. voltage stable despite changes in mains supply voltage or long-term line output valve aging.

The simplest, and probably most frequently encountered, stabilising circuit takes advantage of the Metrosil (manufactured by Associated Electrical Industries), a device whose resistance decreases sharply as the voltage applied to it increases.¹ It is usual to connect a Metrosil rod of suitable rating directly between the cathode of the e.h.t. rectifier and chassis. If, for any reason, e.h.t. voltage rises, the Metrosil rod draws an increased current which counteracts the rise. The reverse action—reduced current through the Metrosil rod—occurs if e.h.t. voltage drops. Thus, a stabilising effect takes place.

Another, more complex, technique which has been introduced in recent receivers employs a Voltage Dependent Resistor

(V.D.R.).² As with the Metrosil, the resistance of a V.D.R. decreases as the voltage across it increases. Use is made of this property to cause varying grid bias voltages to be applied to the grid of the line output valve, these bias voltages being such as to counteract the effects of rises or falls in e.h.t. voltage. A typical basic circuit application appears in Fig. 163. In this diagram flyback pulses having an amplitude around 1,500 volts are taken from a tap in the anode winding of the line output transformer and are fed, via C_1 , to the V.D.R. The resistance of the particular type of V.D.R. used in this application drops steeply around 1,000 volts, with the result that C_1 becomes charged such that the tips of the pulses take up a position, when measured on the upper terminal of the V.D.R., approximately 1,000 volts above chassis, as in Fig. 164 (a). If, for some reason, the e.h.t. voltage rises, the flyback pulses will increase in amplitude, as they do in Fig. 164 (b). However, the steeply falling resistance of the V.D.R. around 1,000 volts causes the tips of these higher-amplitude pulses, as measured on the V.D.R. upper terminal, to take up a position which is only slightly higher than that held in Fig. 164 (a).

¹ The current flowing through a Metrosil product varies as the fourth or fifth power of the voltage applied across it.

² Voltage Dependent Resistors for the application described here are manufactured under the trade name Varites, by Mullard Ltd.

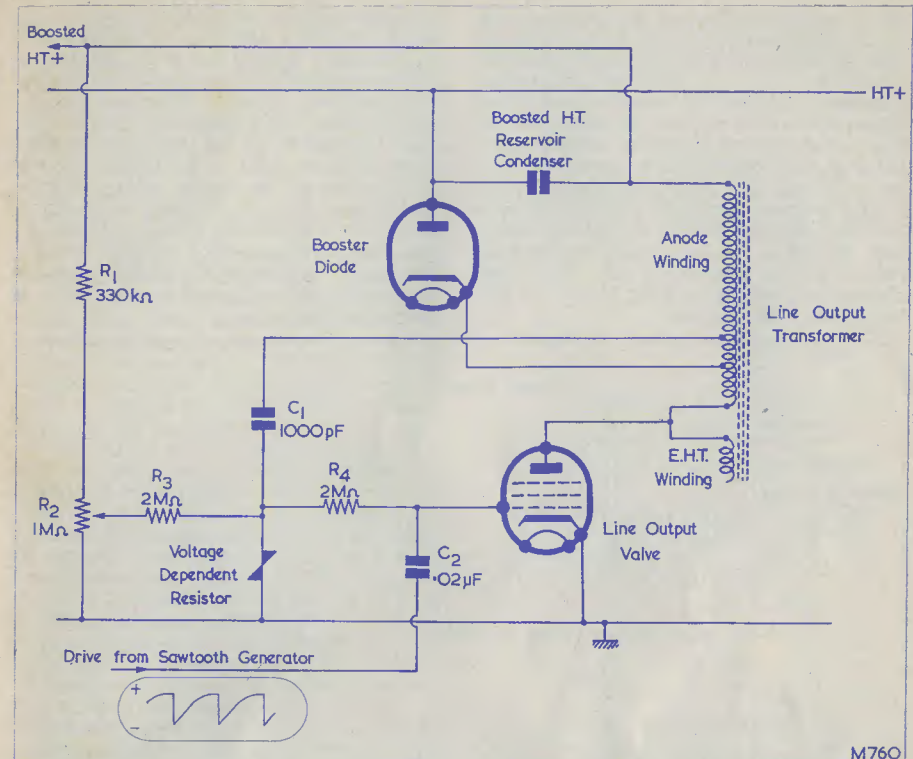


Fig. 163. Basic circuit of a line output stage having its e.h.t. voltage stabilised with the aid of a Voltage Dependent Resistor

(The effect of the V.D.R. is rather similar to that of a diode which is cut off below 1,000 volts and which commences to conduct at that figure; with the exception that the increase in current through the V.D.R. due to increasing voltage is not as abrupt as it would be with the diode.) It will be noted, in Fig. 164 (b), that the waveform between pulses is shifted to a significantly lower potential than it held in Fig. 164 (a). Since the pulses occupy a very small fraction in time of each cycle the average voltage of the waveform is very close to the voltage existing between pulses. In consequence the average voltage in Fig. 164 (b) is also markedly lower than is that in Fig. 164 (a). The circuit diagram of Fig. 163 shows that the voltage on the upper terminal of the V.D.R. is applied to R_4 . This resistor, in combination with C_2 (whose lower plate connects to the relatively low impedance of the preceding "sawtooth-forming circuit"), causes the pulses to be removed and the average voltage of the waveform to be applied to the

line output grid. We thus have the case where, when flyback pulses increase in amplitude, the grid bias of the line output valve is made to go negative. In other words, a stabilising loop has been set up by means of which an increase in e.h.t. voltage causes a counteracting decrease in line output valve anode current. The resistors R_1 , R_2 and R_3 in Fig. 163 are used to initially set up the V.D.R. to its correct operating point, and to ensure that the average voltage applied to the line output valve grid is within its control range.

Line Output Stage Interference

Due to the relatively high potentials and frequencies involved in line output circuit operation, this stage is liable to give rise to parasitic oscillations which, on being picked up by the aerial or early circuits in the receiver, appear on the cathode ray tube screen as interference. When they exist, such parasitic oscillations normally occur at the same point during the deflection cycle,

whereupon they appear at the same position on each line reproduced by the cathode ray tube. The result is a fixed vertical bar or line (normally white in positive modulation receivers and black in negative modulation receivers) on the picture. Parasitic oscillation bars may occur anywhere on the picture, although they usually tend to appear between the left-hand side and the centre. They should not be confused with the vertical striations (stripes) caused by leakage reactance ringing in the line output transformer, (which will be discussed later). The latter always have highest amplitude on the left-hand side of the picture.

of by connecting a very high frequency tuned circuit (usually a pair of short parallel rods, or "resonant lines") to grid and anode, whereupon oscillations occur at the frequency of the tuned circuit. Reverting to line output stages, the supposition is made that, since the anode of the line output valve might at some point in the deflection cycle be negative of its screen grid, the basic requirement of a Barkhausen oscillator is brought into existence. Barkhausen oscillations may, in consequence, occur at resonant frequencies dictated by the circuit constants around the valve including, especially, its connecting leads.³

with the anode of the line output valve and, less frequently, with the cathode of the booster diode. Such chokes are normally inserted in the flying leads to these electrodes, being positioned close to the appropriate valve connector. It is, also, very common practice to connect a resistor having a value between 400Ω and $1k\Omega$ between the grid of the line output valve and its drive circuit, this resistor being mounted close to the appropriate valve pin.

In a number of magazines covering television servicing it has been stated that Barkhausen oscillations in receivers under repair have been successfully cleared by fitting permanent magnets close to the line output valve envelope. These magnets are intended to alter the paths taken up by electrons inside the valve and to modify, therefore, the Barkhausen effect.

Other causes of line output stage interference are frequently such obvious faults as corona or poor connections in the line output stage or transformer, the latter causing the appearance of small sparks. The effects of interference of this type may be evident during the flyback period only, with the result that no visible effects may be seen on the cathode ray tube screen. Such interference may, however, be picked up on a neighbouring receiver tuned to another transmitter and whose line sawtooth generator is not, in consequence, exactly in synchronism with that of the interfering receiver. In such a case the interference will be evident as a vertical bar moving randomly from side to side of the picture.

A further type of interference from line output stages is that resulting from r.f. radiation. Unless the line output stage is adequately screened, harmonics of the line frequency may cause interference on the lower frequency bands of neighbouring radio receivers.

Width Controls

The function of a width control is that of varying the width of the picture reproduced on the cathode ray tube screen, this being done in most instances by varying the sawtooth currents flowing in the line deflector coils. Ideally, a width control should not cause alterations in line linearity. In practice, however, there is almost always a slight interdependence between width and line linearity controls inasmuch that an adjustment of one requires a compensatory adjustment in the other. In a good design this interdependence is kept to a low order, and small changes may be made in width control settings without seriously affecting linearity. It is also possible for large width control adjustments to vary the e.h.t. voltage

generated by the line output stage. In this instance it is usual practice to ensure that correct e.h.t. voltage is obtained when the

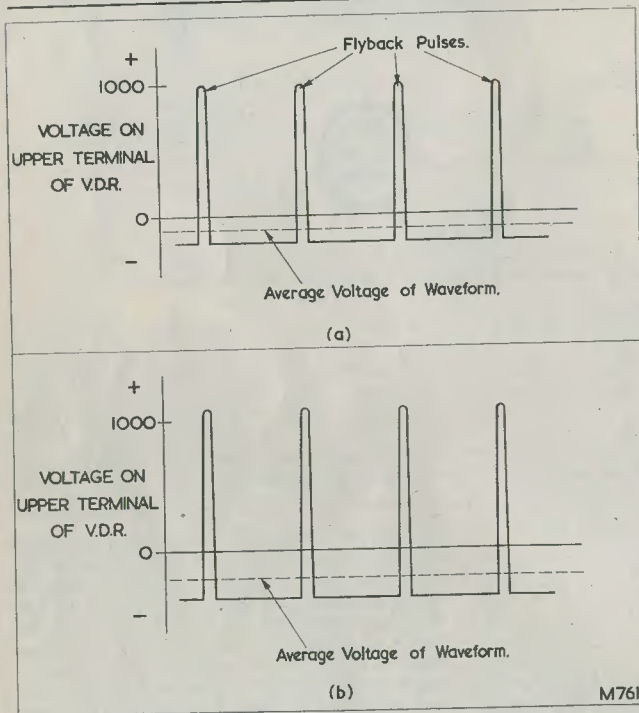


Fig. 164. The voltages appearing across the V.D.R. of Fig. 163. The flyback pulses increase in amplitude in (b) but, because of the steeply falling resistance of the V.D.R. around 1,000 volts, their tips take up a position only slightly higher than that in (a). In consequence, the average voltage in (b) is more negative than it is in (a)

Line output stage parasitic oscillations are frequently described as Barkhausen oscillations. The basic Barkhausen (more accurately Barkhausen-Kurtz) oscillator employs a triode whose grid is positive and its anode negative of cathode. The inertia of electrons emitted from the cathode causes many of them to pass through the wires of the positive grid, only to be repelled by the negative anode. Many of the repelled electrons again pass through the grid, to become repelled once more by new electrons from the cathode. This continual movement back and forth of electrons may be taken advantage

of by connecting a very high frequency tuned circuit (usually a pair of short parallel rods, or "resonant lines") to grid and anode, whereupon oscillations occur at the frequency of the tuned circuit. Reverting to line output stages, the supposition is made that, since the anode of the line output valve might at some point in the deflection cycle be negative of its screen grid, the basic requirement of a Barkhausen oscillator is brought into existence. Barkhausen oscillations may, in consequence, occur at resonant frequencies dictated by the circuit constants around the valve including, especially, its connecting leads.³

³ The valve conditions referred to here would also theoretically cause dynatron oscillations. However, it appears unlikely that dynatron oscillations occur in practice.

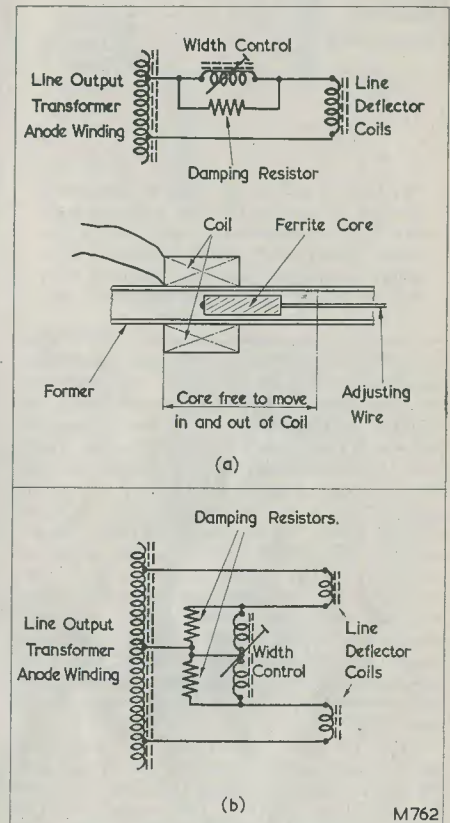


Fig. 165 (a). A Series reactance width control. Varying degrees of core insertion into the coil cause different reactances to appear in series with the line deflector coils, thereby controlling the sawtooth current flowing in them. A cross-section through a typical assembly is also shown. (b) Occasionally, the width control coils may be wound in two sections, as shown here

width control is at the design centre setting for the run of receivers being produced.⁴

The width control arrangements employed

⁴ "Design centre" refers to the conditions existing when all components are in the centre of their tolerance.

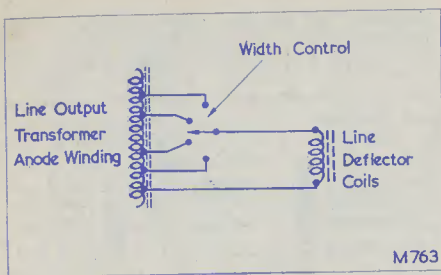


Fig. 166. A control of width is sometimes effected by tapping the line deflector coils into different numbers of turns in the line output transformer anode winding. Usually, the variable taps are obtained with the aid of a short-circuiting plug and socket assembly

in domestic television receivers vary considerably so far as principles of operation are concerned. They may, nevertheless, be roughly categorised into the following different types: circuit arrangements which insert a variable reactance in series with the line deflector coils, circuits which allow the deflector coils to be tapped into different sections of the line output transformer anode winding, circuits which vary the inductive constants in the "sawtooth-forming circuit" provided by the line output transformer winding and the deflector coils, circuits which alter line output valve operating conditions, and devices which vary the deflection efficiency of the line deflector coils. We shall deal with the controls in this order.

Fig. 165 (a) illustrates a commonly encountered width control of the type which inserts variable reactance in series with the line deflector coils. The width control consists of a coil, together with a ferrite core, which is capable of being moved in or out of it.⁵ When the ferrite core is fully in the coil the latter offers maximum inductance. In consequence, moving the ferrite core in and out of the coil causes the latter to present a varying reactance in series with the line deflector coils, thereby altering the current which flows through them. A control of picture width results. Unless precautions are taken, the width control coil of Fig. 165 (a) is liable to be shock-excited by the rapid change of current which occurs in the flyback period, with the result that ringing currents may become superimposed upon the sawtooth current fed to the deflector coils by the line output transformer. Ringing is

⁵ The term "ferrite" is applied to non-ferric (non-iron) magnetic materials such as Ferroxcube or Ferramic, in order to differentiate them from dust-iron materials (such as are used in r.f. and i.f. coils).

obviated by connecting a low-value damping resistor (normally 1 to 3k Ω) across the coil. There is also the fact that the effective inductance of the coil may reduce as current increases owing to the greater magnetising force exerted on the core. Different amounts of core insertion can, therefore, offer different degrees of change in inductance during the scan period, with the result that adjustments of the width control cause alterations in linearity. This effect may be reduced by using a fairly large core, typical examples having diameters of the order of $\frac{1}{4}$ -inch, and by designing so that only a small amount of core insertion is needed for correct width in the average receiver of a production run. Occasionally the circuit arrangement of Fig. 165 (b) is employed in order to reduce the effect of varying inductance. In this diagram two coils with equal numbers of turns are employed in the width control, the current flowing in one being in the opposite direction to that in the other. Due to this, the total magnetising force on the core decreases considerably, thereby reducing changes in linearity for changes in width control setting. A basic disadvantage with the series reactance width control of Fig. 165 (a) or (b) is that it incurs an unavoidable waste of power, the line output valve and transformer having to provide scanning power greater than that needed for full picture width in order to make up for that lost in the series width control.

Fig. 166 illustrates a width control circuit arrangement which allows the line deflector coils to be tapped into different numbers of turns in the line output transformer anode winding, maximum width being given when the deflector coils tap into the greatest number of turns. This method of width control causes picture width to be varied in discrete steps, and does not allow for incremental adjustment between taps. A step-by-step adjustment of this type is acceptable enough in practice owing to the usual custom of slightly "overscanning" the picture reproduced by the cathode ray tube.⁶ The width control of Fig. 166 is adjusted to the lowest tap which causes overscanning, the viewer being unconscious of the amount of overscan. Tapping into the line output transformer winding is usually achieved with the aid of a simple short-circuiting plug and socket assembly, the socket being made such that the plug may be inserted into a number of different positions corresponding to different line output transformer tapings. The circuit of Fig. 166 has the advantage that no scanning power is wasted. On the other

⁶ When a picture is "overscanned" its edges fall outside the mask area, or outside the screen area if a "push-through" method of cathode ray tube presentation is employed.

hand, it possesses the disadvantage that the line output transformer anode winding has to have a relatively large number of taps, thereby increasing winding time in production, and complicating mechanical design.

Fig. 167 (a) illustrates a width control circuit which alters the effective inductance of the line output transformer anode winding, thereby varying the constants of the "sawtooth-forming circuit" formed by the anode winding and line deflector coils. A coil with an adjustable ferrite core is connected across part of the anode winding of the line output transformer. The combined inductance of the anode winding, deflector coils and width control coil is then at its greatest when the core of the coil is fully inserted, this setting corresponding to maximum width. No scanning power is needlessly dissipated with this arrangement. A minor disadvantage with the parallel width coil of Fig. 167 (a) is that it usually requires a relatively high range of inductance variation if it is to exert sufficient control, and this results in the coil having to be wound with many more turns than would be required for the series reactance control. There is also the fact that, being ferrite cored, varying currents in the coil are liable to cause varying inductances, with consequent effects on line linearity. It is not necessary to damp the parallel width control coil to prevent ringing, as its inductance and stray capacity enter into the composite inductance and stray capacity offered by the anode winding and deflector coils.

Frequently, the width control arrangements of Figs. 165 (a) and 167 (a) are combined together in the manner shown in Fig. 167 (b). In this arrangement two sets of coils are wound on one former, along the inside of which a ferrite core is free to move. The two windings are so positioned that as the core leaves one coil it commences to enter the other. When the core is fully inserted into the series coil, L_2 , this offers maximum reactance to the flow of deflector coil current. At the same time the core is fully out of the parallel coil, L_1 , with the result that the latter causes minimum effective inductance to be offered by the line output transformer anode winding. Both L_1 and L_2 are, in consequence, in conditions which correspond to minimum width. As the core is moved out of L_2 and into L_1 , the former offers less series reactance whilst the latter causes the effective inductance offered by the anode winding to increase. In consequence, the picture reproduced by the cathode ray tube widens. When the core is completely out of L_2 and fully inserted into L_1 , the former offers minimum series reactance and the latter maximum inductance. Picture width is, then, at its maximum. By

combining the two types of width control in this fashion it becomes possible for each to have a reduced range of control with the result that, under practical conditions, each coil requires fewer turns than it would if it

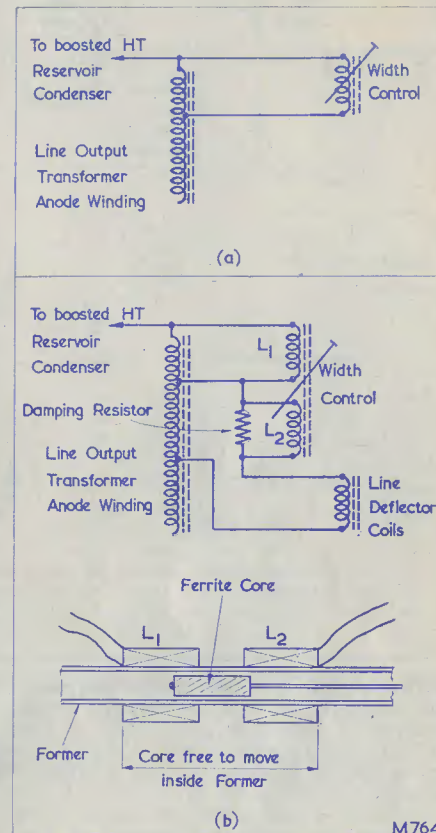


Fig. 167 (a). A width control consisting of a ferrite cored coil connected across part of the line output transformer anode winding. The ferrite core is capable of being moved in and out of the coil, as in Fig. 165 (a), thereby varying its inductance and, in consequence, the combined inductance of the anode winding and line deflector coils. In order to reduce the potentials above chassis existing on the coil, it is usual to tap it into the boosted h.t. reservoir condenser end of the winding. (b) Frequently, the series reactance control of Fig. 165 (a) is combined with that of Fig. 167 (a) in the manner shown here. The ferrite core moves out of one coil into the other as shown in the cross-sectional view

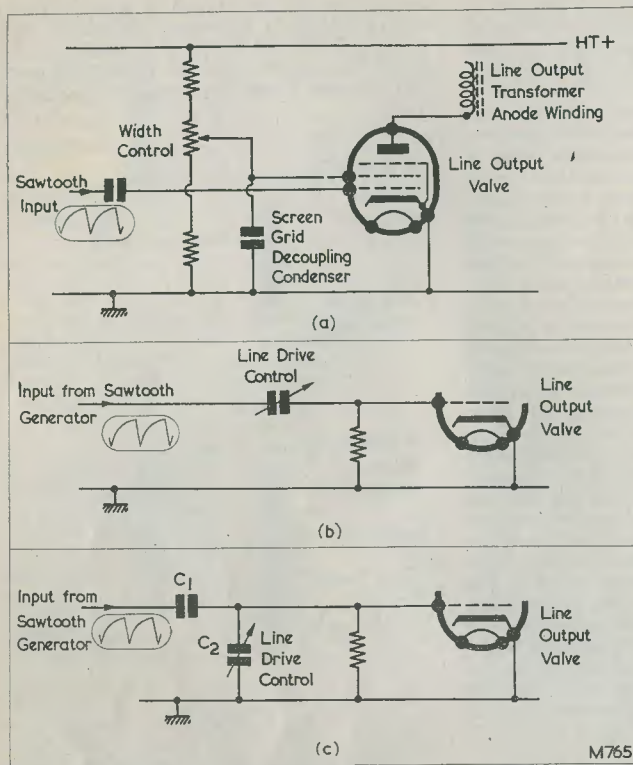


Fig. 168 (a) A width control which varies line output valve operating conditions. By altering screen-grid potential, the potentiometer controls the anode current drawn by the valve. (b) A line drive control which alters the amplitude of the sawtooth waveform applied to the line output valve. (c) A version of (b) which enables the moving vanes of the variable condenser to be at chassis potential

were employed on its own and that magnetising forces on the core are correspondingly lowered. Occasionally, the circuit of Fig. 165 (b) is combined with that of Fig. 167 (a) in a similar manner to the composite arrangement of Fig. 167 (b).

A circuit which varies line output valve operating conditions is illustrated in Fig. 168 (a). In this diagram the width control consists of a potentiometer which varies the screen grid potential of the line output valve. In so doing it controls the anode current drawn by the valve during the scan period of the cycle and, therefore, the magnitude of the current flowing through the line output transformer anode winding and the deflector coils. A control of width is thereby effected. This particular arrangement has been occasionally employed, mainly in American receivers. Another type of width control which falls more or less in the same category is shown in Fig. 168 (b). This control should, more accurately, be described as a "drive control", as it varies the amplitude of the sawtooth waveform applied to the line output valve grid. The control is provided by a variable condenser and it offers a variable

reactance in series with the output of the sawtooth generator. Another version of this circuit is illustrated in Fig. 168 (c). In this case the variable condenser C_2 forms a condenser potentiometer with the fixed condenser C_1 . When C_2 is at maximum capacity, it offers least reactance and the input waveform to the output valve grid has minimum amplitude. The circuit of Fig. 168 (c) has the advantage over that of Fig. 168 (b) that the moving vanes of the variable condenser may be at chassis potential, thereby easing assembly problems. Both of the arrangements of Figs. 168 (b) and (c) are common in American receivers. Their main function is that of ensuring that the line output stage works under correct conditions, insofar as line output valve anode current and e.h.t. voltage are concerned, and they assist in providing a control of picture width.

Fig. 169 illustrates a device which varies the deflection efficiency of the line deflector coils. The control consists basically of a thin-wall cylinder of non-magnetic metal, such as brass or copper, which is free to slide partly under the deflector coil assembly

on the cathode ray tube neck. The changing magnetic field generated by the line deflector coils induces currents in the cylinder which, in their turn, generate an opposing field. As the cylinder is moved into the space between the deflector coils and the tube neck the opposing field it produces increases, with the result that line deflection of the electron beam decreases. A control of picture width is, in consequence, conveniently available by movement of the cylinder, maximum insertion corresponding to minimum width. The cylinder also produces a magnetic field opposing that generated by the frame deflection coils but, since the rate of change of field in this instance is much lower, the currents induced in the cylinder and, hence, the opposing field, are considerably smaller. For the amounts of insertion employed in practical designs the effect of the cylinder on frame deflection efficiency is negligible. The device of Fig. 169 has been used extensively in recent years, especially in American receivers, and it has the advantages of considerable cheapness and simplicity. In practical applications it is usual to design the deflector circuit such that only a small amount of insertion of the cylinder is necessary for correct width. This is to prevent unnecessary dissipation of deflection power, and to avoid excessive induced current flow in the cylinder and resultant overheating.

Next Month

The writer had hoped to discuss line linearity controls and to introduce the

subject of deflector coils this month, but we have already come to the end of our available space. We shall, in consequence, carry on to line linearity circuits and deflector coil assemblies in next month's issue.

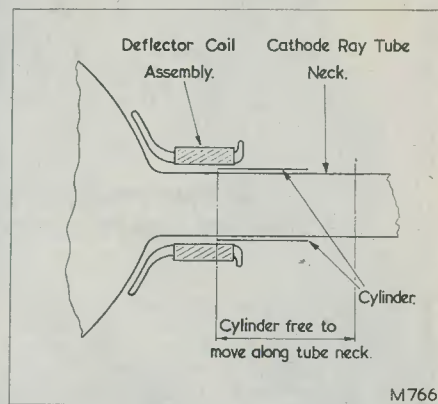


Fig. 169. Cross-sectional view showing a type of width control assembly in which a thin-wall metal cylinder is moved along the cathode ray tube neck, partly under the deflector coil assembly. The line deflector coils induce currents in the cylinder which, in their turn, generate an opposing field; the effect being greater as the cylinder is inserted further under the deflector coil assembly

A Simple Morse Practice Buzzer

FOR THE BEGINNER NEEDING MORSE practice, this simple buzzer may prove useful. The few components required are all cheap, and readily obtainable. They are: a small Morse key, a single low resistance earphone, a single carbon microphone insert, a three volt cycle lamp battery, a short length of insulation tape and some bell flex. A glance at Fig. 1 will give an idea how it functions.

As will be seen, the single earpiece and carbon microphone are physically strapped together (insulation tape does this nicely), and these and the Morse key are all series-connected with the battery. On pressing the key, the circuit is completed, and due to the close proximity of the microphone to earphone, a loud audio note will be produced. The tone, though not quite T9, is perfectly

easy to copy, and much useful code practice is possible using this simple arrangement.

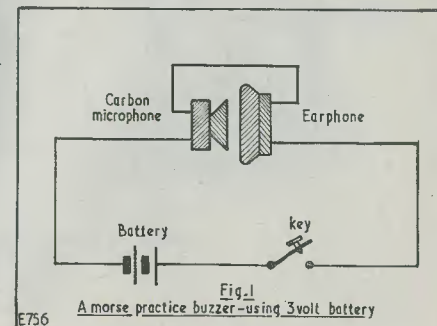


Fig. 1 A Morse practice buzzer—using 3 volt battery

The LITON



A PHOTO-ELECTRIC PARKING LIGHT SWITCH

Described by J. M. Ankers
Part 2

THE PARKING LIGHT ASSEMBLY, DESCRIBED in the last issue, is only capable of switching on or off a 6 or 12V single bulb. With suitable modifications, and the addition of a secondary relay, the unit may

be used to control either a parking light or the side and tail lights, according to the car owner's requirements, simply by operating an integral switch.

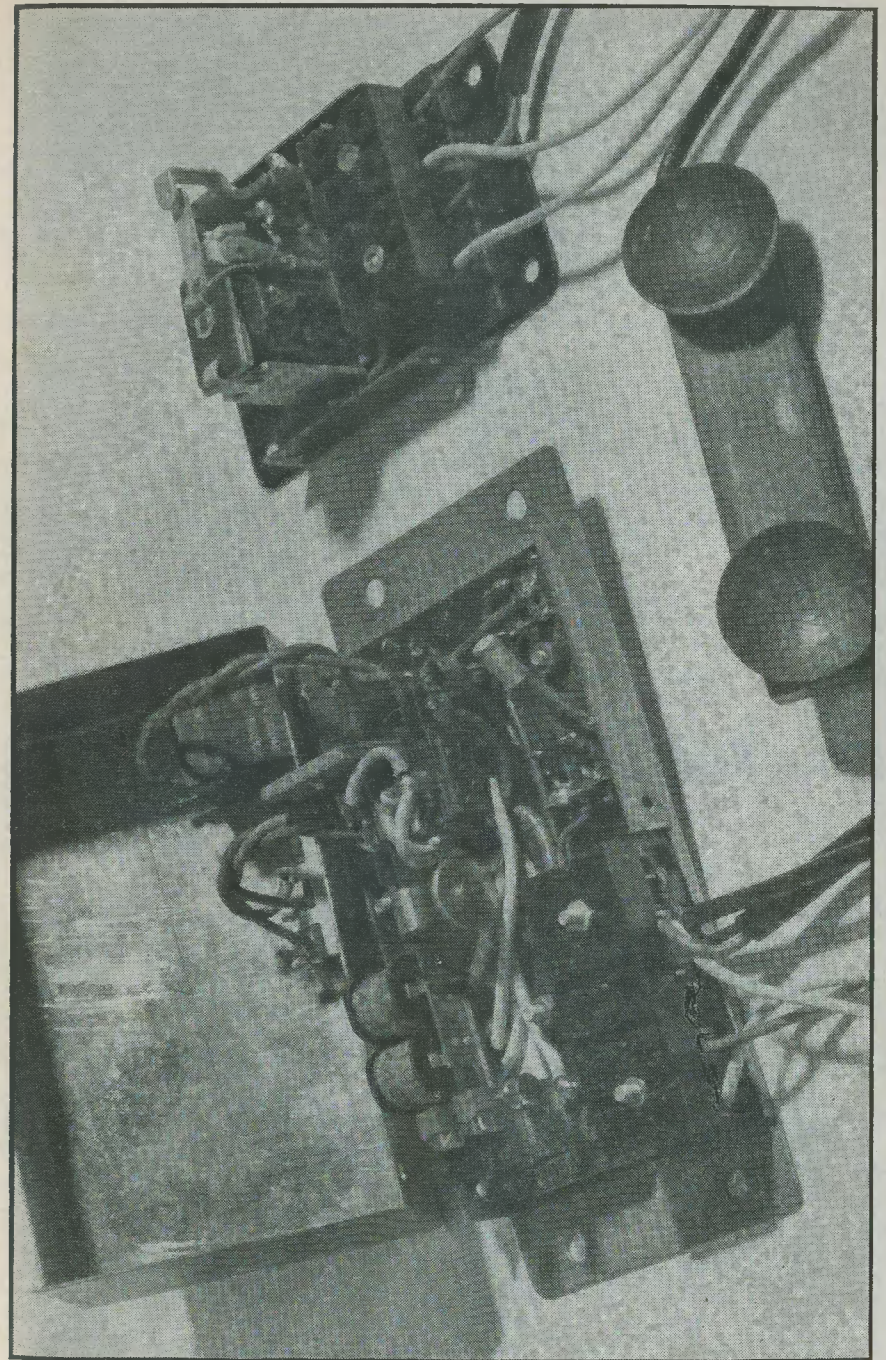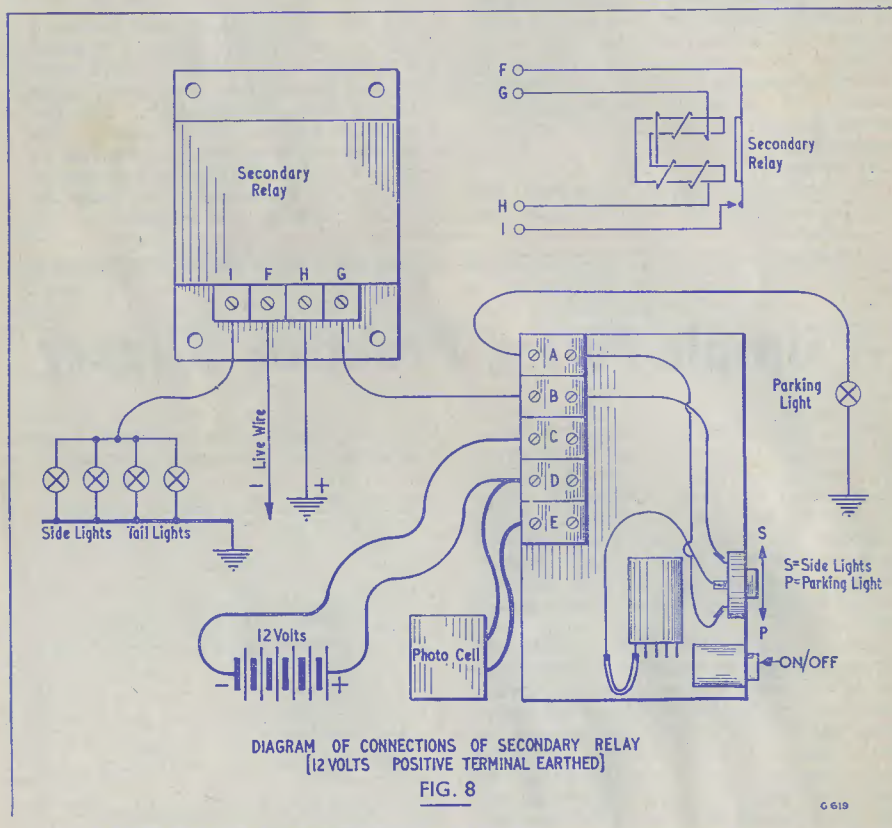Before further continuing with a descrip-



tion of these alterations and additions, a word or two about adjusting the relay of the original unit may not come amiss. The relays themselves are adjusted correctly as supplied, but the do-it-yourself fraternity being of an experimental nature, the relays are often altered in an attempt to "improve" the action. The usual result is that the "improver" is unable to correctly re-set the relay with the end result being—no result! The most reliable operation is obtained when the relay is adjusted to pull at $4\text{mA} \pm 0.5\text{mA}$ and to release at $2\text{mA} \pm 0.5\text{mA}$. The gap should be set at about 0.004 in.; which, for those who have some, is the thickness of a one-pound note!

After completing the assembly, as described, some constructors are unable to get the switch working at all. It has been found from experience that the most common cause of a non-working unit is that the transistor, or the photocell, has been connected the wrong way round. Connecting the full voltage to the photocell will, in most cases, permanently damage the cell.

Modifications

In Fig. 8 all the modifications and additions to the original unit are shown. The position of the added slide-switch may be

clearly seen. The sequence of these modifications is as follows.

(1) Remove the link between contacts (B) and (D) on the connecting block of the "Liton" unit. (See Fig. 4, page 689, April issue.)

(2) Connect a wire from terminal (I) of the "Liton" relay to the centre of the slide switch instead of to (A) of the terminal block.

(3) Connect the terminal of the changeover switch, near the on/off switch, to (A) on the connecting block, and the terminal furthest from the on/off switch, to (B) on the connecting block.

(4) Join (B) to (G) on the added secondary relay block.

(5) Connect the live and neutral wires to (F) and (H).

(6) With a length of wire, join (I) to one wire of the car wiring going to the side and tail lights.

(7) Connect the parking light between (A) and chassis.

The modifications are now completed. Moving the slider switch towards (P) will operate the parking light; and towards (S), side lights and tail lights. The secondary relay can, of course, be mounted under the bonnet and not necessarily in the car body itself. (To be continued)

Useful Power Unit

By J. HILLMAN

Description

THIS UNIT IS INTENDED FOR USE WITH various pieces of test gear and avoids having to use power packs for each unit. It will supply 350 volts at 80mA h.t., 1kV at 1mA e.h.t., 4 or 6 volts at 4 amps l.t., 6 volts 1.5 amps for supplying c.r.t. heaters.

Construction

First take a piece of aluminium 9in by 8in and mark off as in Fig. 1. Drill the holes first and then bend the edges at right-angles. Now paint with black crackle paint and put aside to dry. Take a piece of aluminium 15in by 12in and mark off as in Fig. 3 and cut out as shown, then bend the sides and back at right-angles to form the chassis. Place the front panel up to the chassis and mark off holes to join the two pieces together, after having bolted the chassis at its corners. The finished unit should now appear as in Fig. 4.

Mount the components as shown in Figs. 5 and 6, and cut out the holes from the bunt of the chassis as shown in Fig. 2, then mock the valveholders. The warning light is mounted at the left side of the front panel, whilst the mains switch is mounted on the right. The sockets at the bottom of the front panel are, reading from left to right, 0V, 4V, 6V, l.t.; 1kV e.h.t.; h.t.+; h.t.-.

Wire up as shown in Fig. 7; note that only the middle socket at the back of the chassis carries the e.h.t. and c.r.t. heaters—the other two are wired in parallel for h.t. and l.t.

If only 600 volts e.h.t. are required, then the $0.1\mu\text{F}$ condenser at pin 4 of the 5Z4G and the final K3/25 rectifier can be removed. A warning light is wired across the 6V heater winding to indicate when the unit is switched on. The h.t. circuit is protected by a 100mA fuse in the h.t.- side and the mains transformer is protected by two 1 amp fuses in the leads from the transformer to the switch.

No cover is used for the top of the chassis

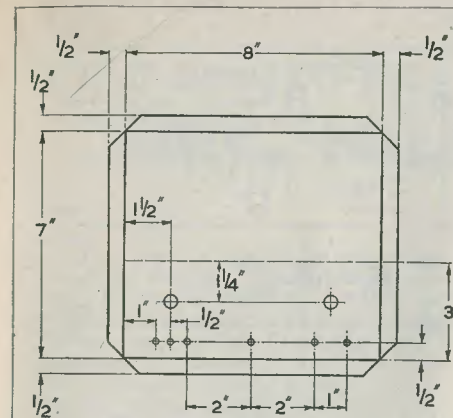


FIG. 1
Front Panel

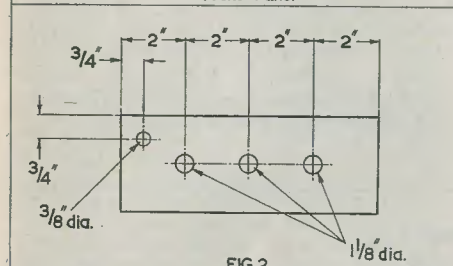


FIG. 2
Back Panel

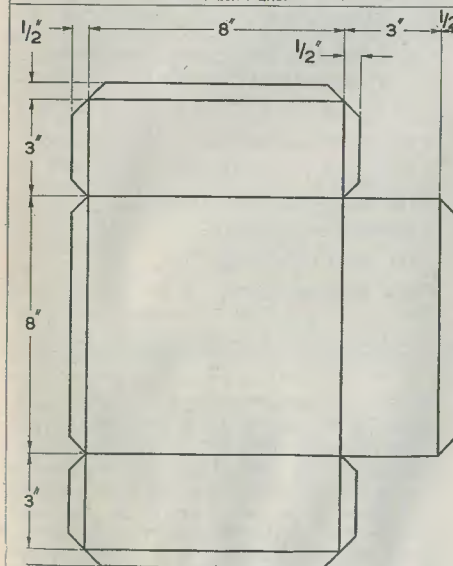


FIG. 3
Chassis

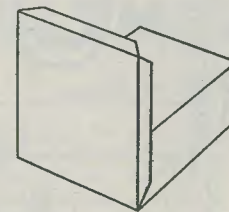


FIG. 4

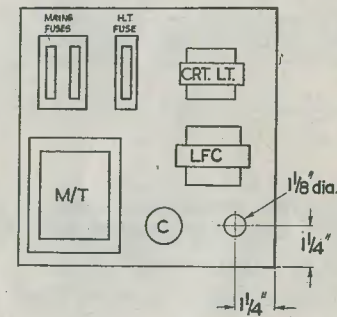


FIG. 5
Above-chassis Layout


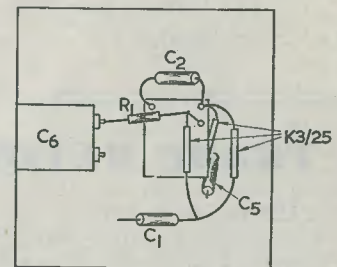


FIG. 6
Below-chassis Layout

M738

Further notes on the A.C. MILLIVOLTMETER

By A. Bartlett Still

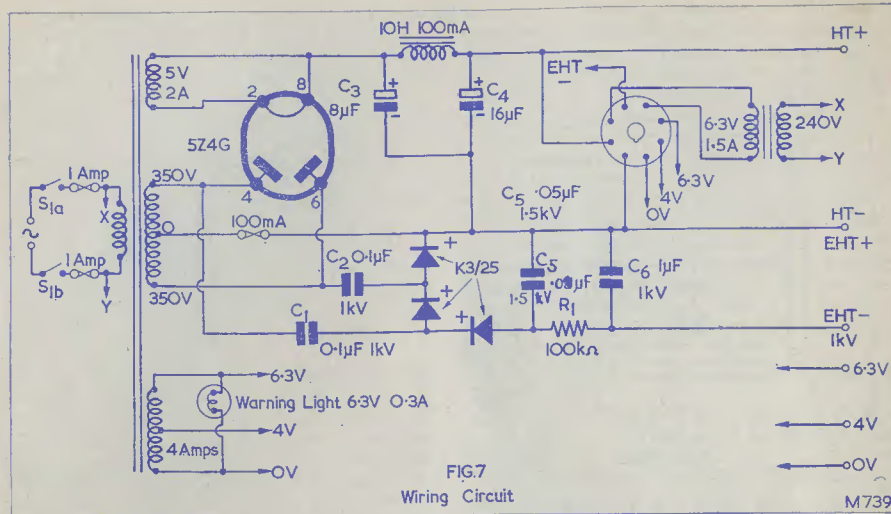

as it was not felt necessary, but if one is used then make sure that adequate ventilation is provided. A suitable cover can be made out

of perforated zinc sheet, as this gives plenty of ventilation as well as protection.

Components List

- | | |
|----------------------------------------------------------------------|----------------------------------------------------------------------|
| 1 mains transformer 350-0-350V 80mA 5V 2A; 0, 4, 6V, 4 amps, Elstone | C ₁ , C ₂ 2 0.1 μ F 1kV tubular condensers |
| 1 d.p.s.t. toggle switch | C ₃ 1 0.05 μ F 1.5kV tubular condenser |
| 1 twin fuseholder, baseboard type | C ₄ 1 1 μ F 1kV block paper condenser |
| 1 single fuseholder, baseboard type | R ₁ 1 resistor 100k Ω |
| 2 1 amp 1 $\frac{1}{4}$ in glass fuses | 1 5Z4G valve |
| 1 100mA glass fuse | 4 int. octal valveholders |
| 1 10H 100mA l.f. choke | 1 6.3V 1.5A l.t. transformer |
| C ₃ , C ₄ 1 8+16 μ F can elect. 450V wkg | 1 red panel light—Radiospares |
| 3 K3/25 e.h.t. rectifiers | 1 bulb 6.3V 0.3A m.e.s. |
| | 3 int. octal valve plugs |
| | 6 wander plug sockets |

TRADE REVIEW

STEADFAST PAD SAW

J. Stead & Co. Ltd., Manor Works, Cricket Inn Road, Sheffield 2, have forwarded to us, for test purposes, this latest addition to their well-known range of high grade tools. This multi-purpose pocket tool incorporates two pad saw blades, together with a knife edge cutter, contained within a

translucent amber plastic handle—this being specially designed and shaped to give a strong and comfortable grip. The coarse tooth padsaw is for cutting soft materials whilst the fine tooth blade is that for hard materials. All three blades, when not in use, fit snugly within the plastic handle—the whole tool then being contained in a strong plastic wallet. Spare blades are available and the complete pad saw may be obtained from most tool dealers and ironmongers at 6s. each.

IT HAS BECOME APPARENT FROM CORRESPONDENCE that the type of instrument described in the February issue was of interest to a wide range of readers, and the Editor has suggested that I take this opportunity to clarify a few points and answer one or two queries that have been raised.

The two voltage amplifying stages of the amplifier circuit (Fig. 1, February 1960, page 520) seems to have been accepted as straightforward, but it is believed that some further explanation of the input and output stages would be helpful. The input cathode follower was quoted as having an input impedance of 10M Ω . This is not a calculated figure, but was measured by the simple device of applying a suitable signal to give an f.s.d. reading on the meter. Series resistance was then inserted in the input, making a potential divider with the internal input impedance, until the reading dropped to half scale. At this point the series resistance must equal the input impedance. The output impedance (1,000 ohms) can be similarly checked, though in this instance the test resistance should be in parallel with the meter, as an additional load. It should be noted that although these figures can be calculated, this is difficult, due to the fact that the valve information available will probably not be correct for the conditions of use that apply here.

Another query concerns the conditions of use of the attenuator, and the function of the resistor R₃ (or R₄). The attenuator is of the ladder type, having a constant input impedance of 68k Ω ; this being, in fact, the cathode load of V₁. This figure of 68k Ω , and the attenuation of 10dB per step, is only correct if the network of 100k Ω and 150k Ω resistors continues for an infinite number of steps on either side. To simulate this we have AR₁ of 200k Ω , as also are R₃ and R₄. With this arrangement the operating conditions of V₁ do not vary, although the attenuator represents the cathode load which, in itself, means that there is no attenuator insertion loss.

The meter shown was built up around a 100 μ A movement, but it is not necessary to insist on this. Any value up to 1mA can be used without affecting the calibration of the amplifier in any way, but it should be

remembered that the type of rectifier used will affect the frequency response, not of the amplifier but of the indicator.

Calibration of the completed instrument does not seem to have been completely understood. I suspect that readers cannot believe it is so simple! Here is the complete procedure, step by step, taking an AVO as a standard.

(1) Connect the AVO and the Indicator to (say) a 6.3V transformer winding and adjust the meter series resistance as necessary.

(2) With the attenuator all in, connect the AVO to the output of the amplifier and apply the 6.3V signal to the input. Adjust the 1M Ω preset R₁₃ until the AVO reads correctly. Replace the AVO by the Indicator as a check.

(3) Check the value of R₁₃ as set (about 500-600k Ω) and replace by 100k Ω preset together with appropriate fixed resistor. Repeat 1 and 2.

(4) Switch to Attenuate, apply a known signal of 20-30V, and, with the attenuator all out, set R₆ to give a voltage drop of 10dB.

It will have been noted that SW₁ has three positions. The central, off, position will be found very useful for isolating the indicator to prevent damage to the movement.

With the meter disconnected, the Amplifier unit can be used in a variety of ways. The 30V r.m.s. limitation on input and output is due to the saturation level of the cathode followers. The lower limit of signal handling is dictated by noise. On the unit described, this was equal to an input of 150 μ V with a minimum output of 5mV. The setting of the humdinger R₂₄ will have an effect on the noise voltage, and this may be adjusted as necessary.

The scaling of the Indicator was not too clear in the photograph, so a word or two may be helpful. The original scale on the meter was 0-10 x 50 divisions. This is used for the 10V, 1V, and 100mV ranges. To this was added a second scale in Indian ink, 0-3, used for 3V, 300mV and 30mV. Care should be taken to try and maintain the correct ratio, 3.16, between the two scales. Depending on the type of work to which the unit will be put, and the steadiness of the hand, consideration can be given to a third scale of decibels.

DETAILS of DRILLING

A	=	5/8"	Dia	for	V1
B	=	3/4"	"	"	V2
C	=	3/4"	"	"	V5
D	=	3/4"	"	"	V4
E	=	1/2"	"	"	C9
F	=	1"	"	"	C12, C13
G	=	1/4"	"	"	Input
H	=	3/8"	"	"	SW3
J	=	3/8"	"	"	SW1
K	=	1/4"	"	"	Output
L	=	3/8"	"	"	SW2

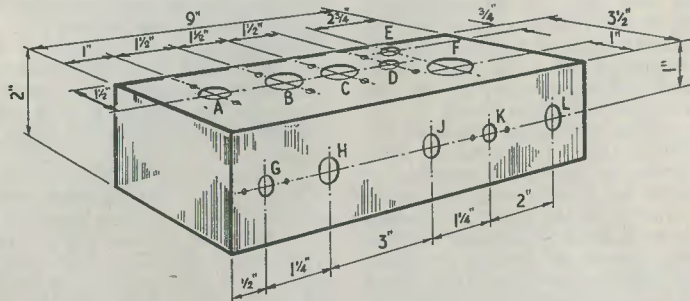


FIG. 4. DETAILS OF CHASSIS. AMPLIFIER UNIT

Suggested material DURAL .048 thick —
Bottom cover .032 thick (fixed with self —
tapping screws)

G 615

The original instrument was made up of components gleaned from various sources, and it was for this reason that details were not given of the chassis. As some interest has been expressed, however, Fig. 4 gives the major dimensions and may be found of

assistance to some readers. It is suggested that in the event of a steel chassis being used, packing, such as a piece of hardboard be used under the transformer. This will be found to effect a marked reduction in the induced hum voltage.

BRITISH SOUND RECORDING ASSOCIATION

Almost every year since 1948, the British Sound Recording Association has held an "Amateur Competition", in which its members have entered equipment which they have constructed themselves.

This year for the first time, it is renamed the "Home Constructors Competition", and will include a section for work by non-members of the Association.

Entries are invited for this competition, which will be held at the Royal Society of Arts, London, on Saturday 21st May, 1960. There are two classes as follows:

(a) Entries submitted by B.S.R.A. members. In addition to the President's Trophy, there will be the *Wireless World* award

of 10 guineas and the Guy R. Fountain award of technical books to the value of 10 guineas.

(b) Entries submitted by non-members. The winner in this class will receive the *Hi-Fi News* award of 10 guineas.

Apparatus submitted for the competition should be associated with the recording and reproduction of sound, including appropriate test equipment. Exhibits will be judged on the score of technical originality, suitability for purpose, design and finish.

Application forms may be obtained from the Association offices at "Greenways", 40 Fairfield Way, Ewell, Surrey, and entries should be submitted not later than 14th May, 1960.

A Point-to-Point Two

A miniature A.C.-D.C. Receiver for LW, MW & SW

By A. S. CARPENTER


HERE IS A LITTLE RECEIVER EMINENTLY suitable for the kitchen, sick room, garage, etc. It is not an ambitious design; rather one which is simple to make and easy to operate. It is capable, too, of giving a wide range of listening pleasure—also it is cheap to construct.

Fig. 1 reveals the circuit—a two valve arrangement, V₁ being a leaky grid demodulator plus audio amplifier, feeding into V₂ the output pentode.

To improve sensitivity, regeneration is employed; and whilst the writer confesses a dislike of this type of feedback he has to admit that the method employed results in

extremely smooth control so that there is no sudden changeover from full sensitivity to ear-splitting oscillation. The control components chosen make this possible and the oscillation point is reached gently.

Three wavebands are covered: Short, 15-50 metres; Medium, 190-560 metres; and Long, 1,000-2,000 metres. For these ranges three miniature iron-cored coils are employed, the secondaries acting normally as the tuned windings and the primaries as reaction coils. Those specified have been chosen deliberately—they are h.f. coils in each case. Normal aerial types are, of course, available; but by using the former

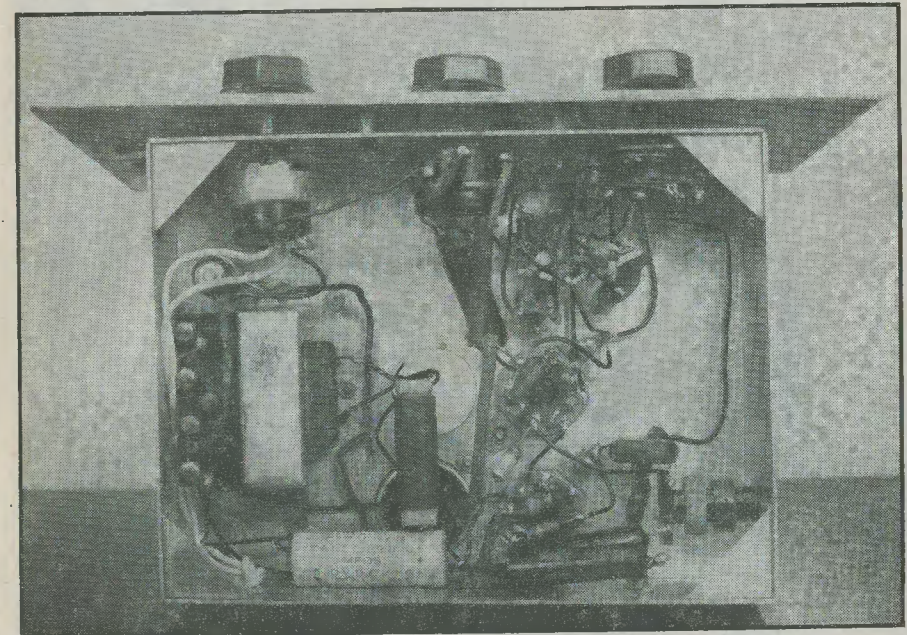

Underside chassis view of the point-to-point receiver showing the main component layout

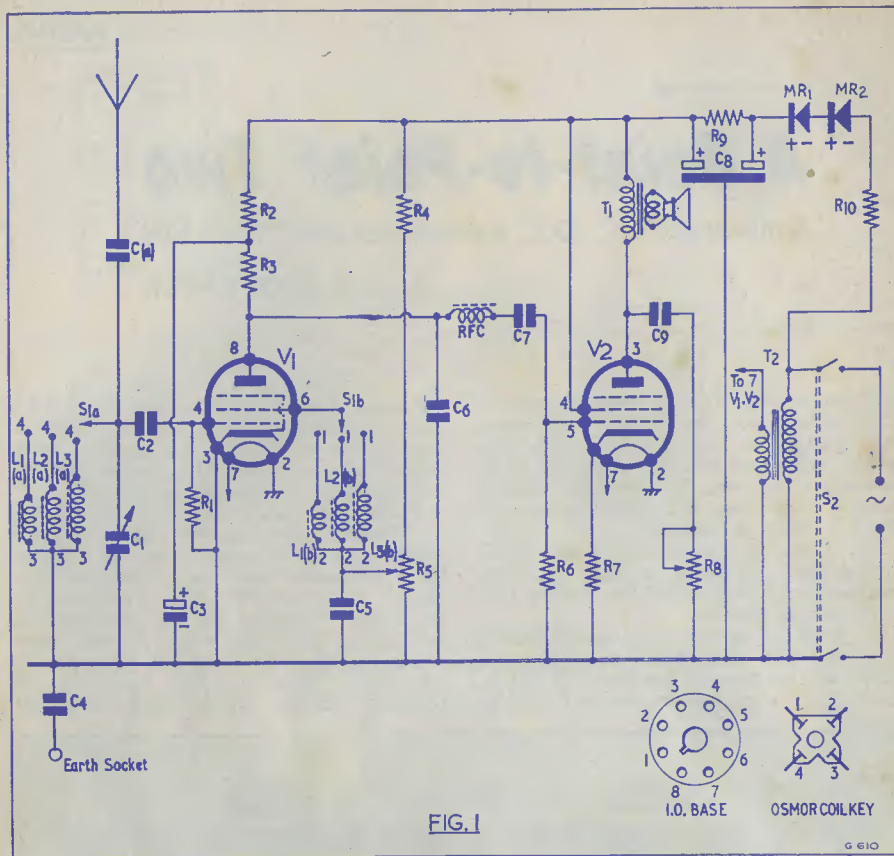


FIG. 1

Components List

Capacitors

- C_a 100pF mica
- C₁ 500pF variable
- C_{2, 6} 100pF mica
- C₃ 8μF electrolytic 350 volts
- C₄ 2,000pF 1,000 volts
- C_{5, 7, 9} 0.01μF
- C₈ 16+16μF electrolytic 350 volts, can 1 1/4 in diameter

Resistors

- R₁ 4.7MΩ
- R₂ 4.7kΩ
- R_{3, 6} 470kΩ
- R₄ 47kΩ 1 watt
- R₅ 5kΩ potentiometer, wirewound
- R₇ 470Ω 1 watt
- R₈ 250kΩ potentiometer and d.p. switch
- R₉ 1.5kΩ, 3 watt

R₁₀ 100Ω, 1/4 watt

Miscellaneous

- L₁ Osmor QHF2
- L₂ Osmor QHF11
- L₃ Osmor QHF12
- V₁ 6SH7
- V₂ 6G6
- Two metal rectifiers, RM2-125 volt, 100mA
- Output transformer, 10kΩ-3Ω
- Filament transformer, 230 volts; 6.3 volts, 1.5 amp.
- Chassis 8 in x 6 in x 2 1/2 in
- Speaker, 5in, Truvox
- RFC-Osmor, QC1
- Two International Octal valveholders
- Sundries: nuts, screws, solder tags, non-metallic speaker fret, connecting wire, etc.


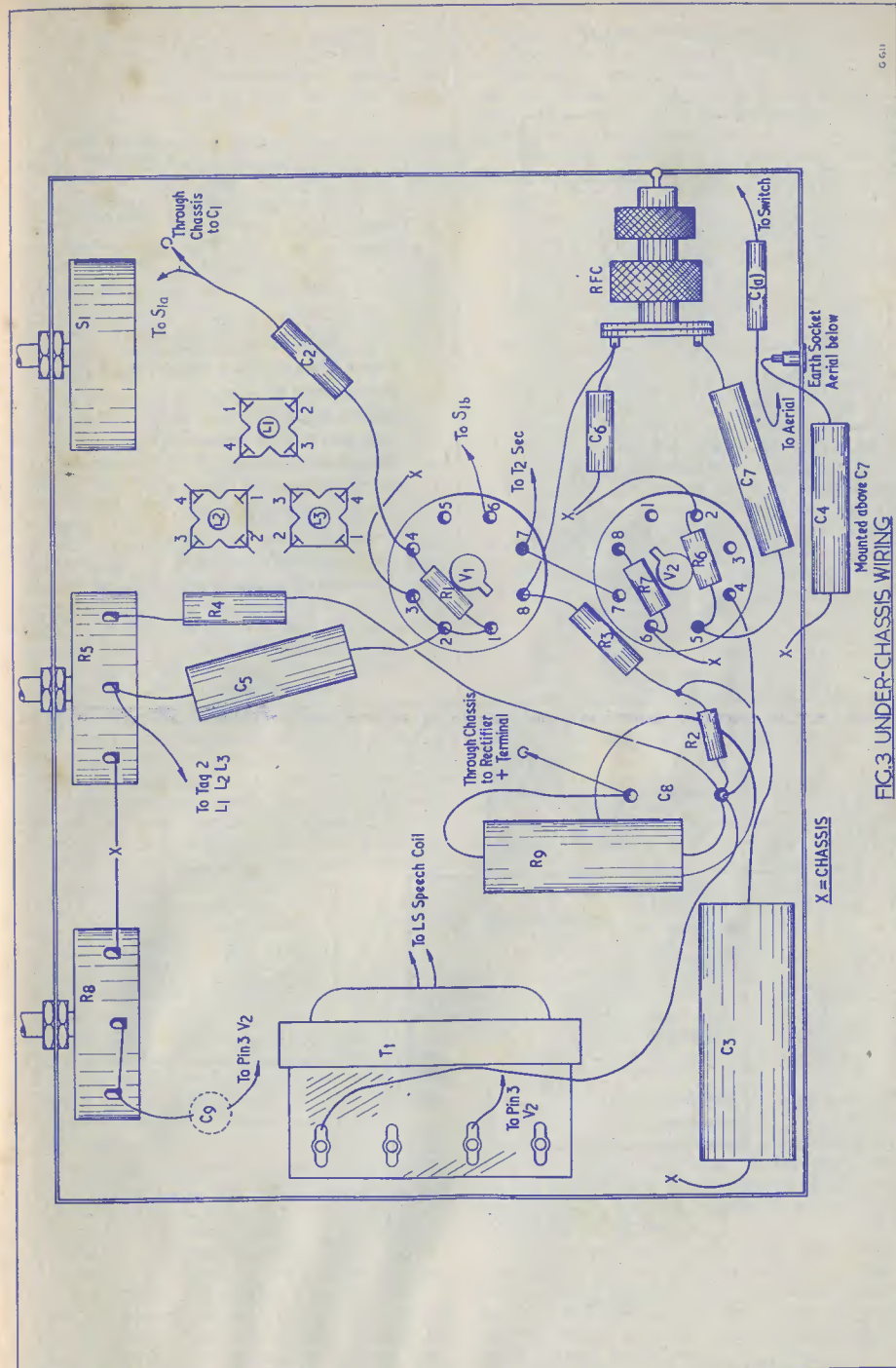


FIG. 3 UNDER-CHASSIS WIRING

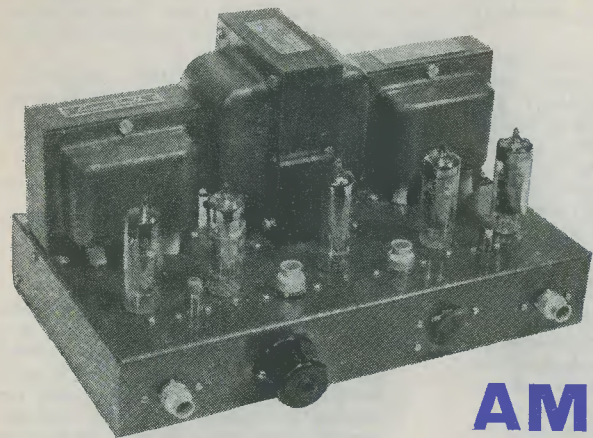

THE COOPER-SMITH HIGH-FIDELITY STEREO MAIN AMPLIFIER

TECHNICAL SPECIFICATION

- Input Sensitivity*
800mV for full output
- Power Output*
6 Watts rated, 9 Watts peak (each channel)
- Harmonic Distortion*
Better than 0.2% at 6 Watts
- Frequency Response*
30 c/s-30,000 c/s at 1W
40 c/s-25,000 c/s at 6W
- Hum and Noise*
-80dB
- Negative Feedback*
15dB
- Output Impedances*
3.75Ω, 7.5Ω, 15Ω
- Valves*
Ultra-linear ECL82s (4), EZ81
- Mains Input*
200-210, 220-230, 240-250V a.c.
- Mains Socket for Motor. Output Socket for Control Unit*
- Dimensions* Length 12in
Width 7in
Height 6 1/4in
- Weight* 17 1/2lb

CIRCUIT DESCRIPTION

(See Fig. 1)

THE CIRCUIT IS, IN FACT, A DOUBLE version of the "back end" of the now famous Cooper-Smith "Prodigy" amplifier with a single heavy duty power supply. Similar output transformers have been used, resulting in a stereo amplifier with an extremely low level of distortion, and

an output more than adequate for domestic use, in view of the fact that its output capabilities are equal to those of a 12-15W monaural amplifier. Except for the power supply and R₁₈, the two channels are exactly similar and all further remarks will apply to both.

The input is applied to the grid of the triode portion of V₁, which forms one half of the "paraphase" phase inverter. The action of this is as follows: after amplification the signal leaves the anode of V₁ 180° out of phase and is fed via C₄/R₉ to the grid of the pentode section. A portion of the signal is then tapped off and applied to the triode grid of V₂, is amplified, and then fed via C₅ and R₁₂ to the pentode section of V₂.

The benefits of push-pull amplification are many, the chief one being that each half-cycle of the signal is amplified separately. In order for this to be done successfully, the impulses reaching the output valves must be 180° out of phase. This has been achieved in this amplifier in the following manner. Let us say that the input to the grid of V₁ is "going negative". Now in a valve amplifier the signal leaving the anode is always out of phase with that applied to its grid, so our signal will be positive when it reaches the pentode grid (pin 3) and will return to negative at the pentode anode. We now have an amplified version of the original negative signal—no overall phase reversal has taken place.

The other half of our push-pull amplifier must now be provided, the output of which

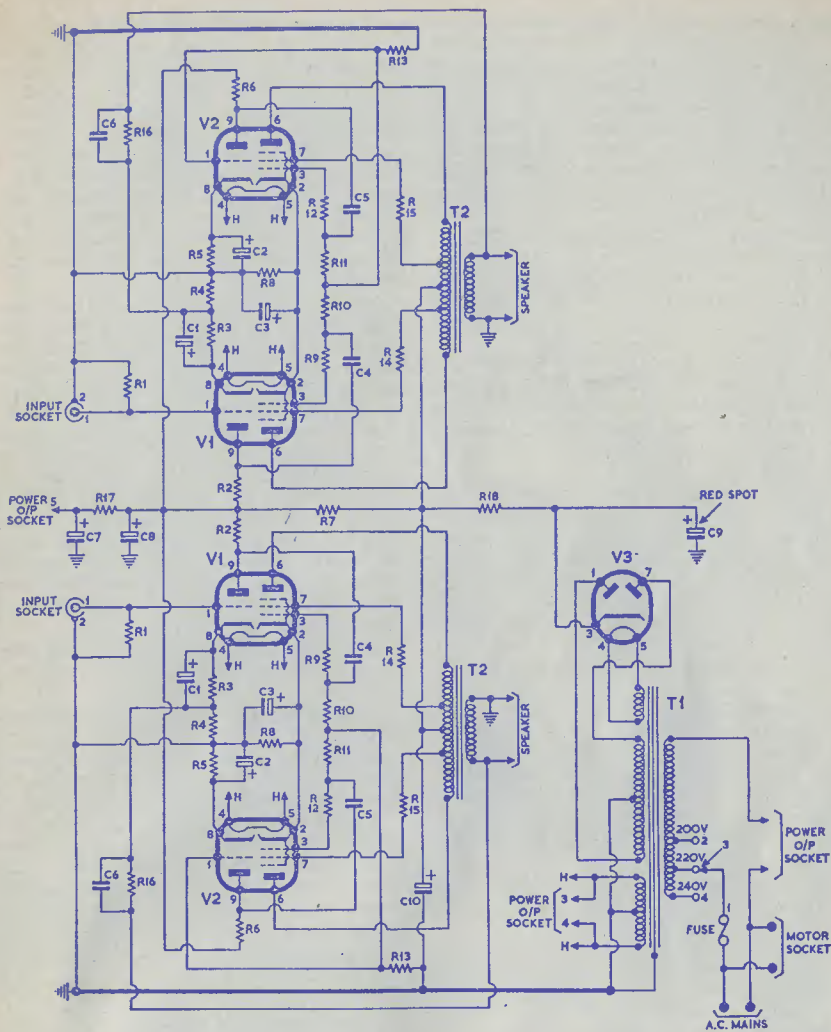


Fig. 1
THEORETICAL DIAGRAM

SMA 1

must be opposite in phase. Therefore the input to this half must be *positive*. We have only a single input source, and that is negative, so we have to find a positive source—the anode of triode V₁ being the nearest. This positive signal is now fed to the triode grid (pin 1) of V₂. Amplification takes place in the same manner as in the first half, except that the output will be positive. Our phase reversal is now complete and when the signal is applied to our input socket, the negative

half-cycles will be amplified by V₁ and the positive by V₂.

As well as being 180° out of phase, the amplified signals must also be equal in amplitude. The circuit used in this case is one which has been in use for many years and which has proved highly successful in its present application.

The pentode sections of the ECL82's are connected in the well-known "ultra-linear" fashion, where the screens are connected to

tappings on the output transformer windings 43% from the centre tap. This arrangement leads to a more nearly linear operation of the output valves, resulting in an output stage closely resembling triodes as regards distortion and pentodes regarding efficiency. Negative feedback is connected from the output transformer secondary to the cathodes of the input stage via a potential divider formed by R_{16}/R_4 .

The benefits of negative feedback may be summarised as follows:

- (1) Decreased hum and noise.
- (2) Increased and more level frequency response.
- (3) Decreased overall distortion.
- (4) Higher loudspeaker damping factor.

All these benefits are obtained without sacrificing anything other than input sensitivity, and as voltage amplification is cheap and easy to obtain, no sacrifice has really been made at all.

The power supply is conventional but for one point. To obtain a greater degree of smoothing, the h.t.+ supply to the output transformer is taken from the low side of the smoothing resistor R_{13} and not, as in some designs, straight from the rectifier cathode. This results in a slightly higher impedance power supply, but it has been found to be in no way detrimental in this instance.

The mains transformer (Electro-Voice type A246) is made specially for this amplifier with the high degree of regulation necessary for good quality amplification, and is fitted with an electrostatic shield between primary and secondary (brown lead). It is finished in bronze (as are the output transformers) to match the chassis.

The output voltages are as follows:

- H.T. 250-0-250V at 120mA
(orange-white-orange)
- Valve heaters 3.15-0-3.15V at 5A
(white-pink-white)
- Rectifier heater 6.3V at 1A
(mauve-mauve)
- Inputs—Common (black)
- 200V (yellow)
- 220V (green)
- 240V (red)

The output transformers, as stated above, are of the same type as used in the "Prodigy" amplifier, the specification being as follows:

- Primary 10,000 Ω anode to anode, ultra-linear taps 43%.
- Secondary wound in three separate sections.
- Speaker matching achieved by series-parallel arrangement, 15 Ω , 7.5 Ω , 3.75 Ω .
- Primary inductance 58 Henrys at 30V 50 c/s.
- Leakage inductance 0.5mH at 1V, 1,000 c/s.

CONSTRUCTION

First fit all the sockets to the chassis with the screws and nuts provided. Fig 2 shows their respective positions when viewed from the underside of the chassis, one side of which is flattened in the drawing to show the components more clearly. All sockets are fitted from the inside except that for the mains. Note that on the loudspeaker output sockets numbers 3 and 4 are wider apart than 1 and 2 and that the blank position on all the valve sockets points towards the group board.

Next take the two output transformers (T_2) and cut all the secondary leads (those covered with sleeving) down to about 5in in length, snip about $\frac{1}{4}$ in of the sleeving from each, and carefully scrape *all* the enamel off the wires. (Do not remove the length of plastic sleeve; this indicates the "double yellow" lead referred to.) The leads may now be tinned, and after making sure that the solder has run all round each wire, the transformers should be bolted to the chassis with the 2BA screws and nuts, first passing the leads through the holes provided. Reference to the drawing shows which colour goes through each hole. Fit an earthing tag under the nut as shown.

The mains transformer (T_1) should now be fitted in the same way, but do *not* cut the leads first.

The clip for the 50+50 μ F capacitor having been bolted to the side of the chassis, the capacitor R_9-10 , with the resistor R_{13} firmly attached, can now be fitted in place, with the red spot furthest from the side of the chassis.


All the wiring shown in Fig. 2 should be completed before fitting the group board. The wiring sequence is given below. Check with the drawing after each operation. Valve heater leads should be twisted; other pairs of leads look neater if so treated.


T_1 leads:

- White pair—3 and 4 on power output socket
- Mauve pair—4 and 5 on V_3
- Orange pair—1 and 7 on V_3
- Pink, brown and white—earthing tag
- Yellow, green and red—2, 3 and 4 on mains selector
- Black—1 on motor socket and mains plug

T_2 leads (both):

- Blue pair—5 on loudspeaker output socket
- Single yellow—4 on loudspeaker output socket
- Double yellow—3 on loudspeaker output socket
- Brown pair—2 on loudspeaker output socket
- Red—1 on loudspeaker output socket

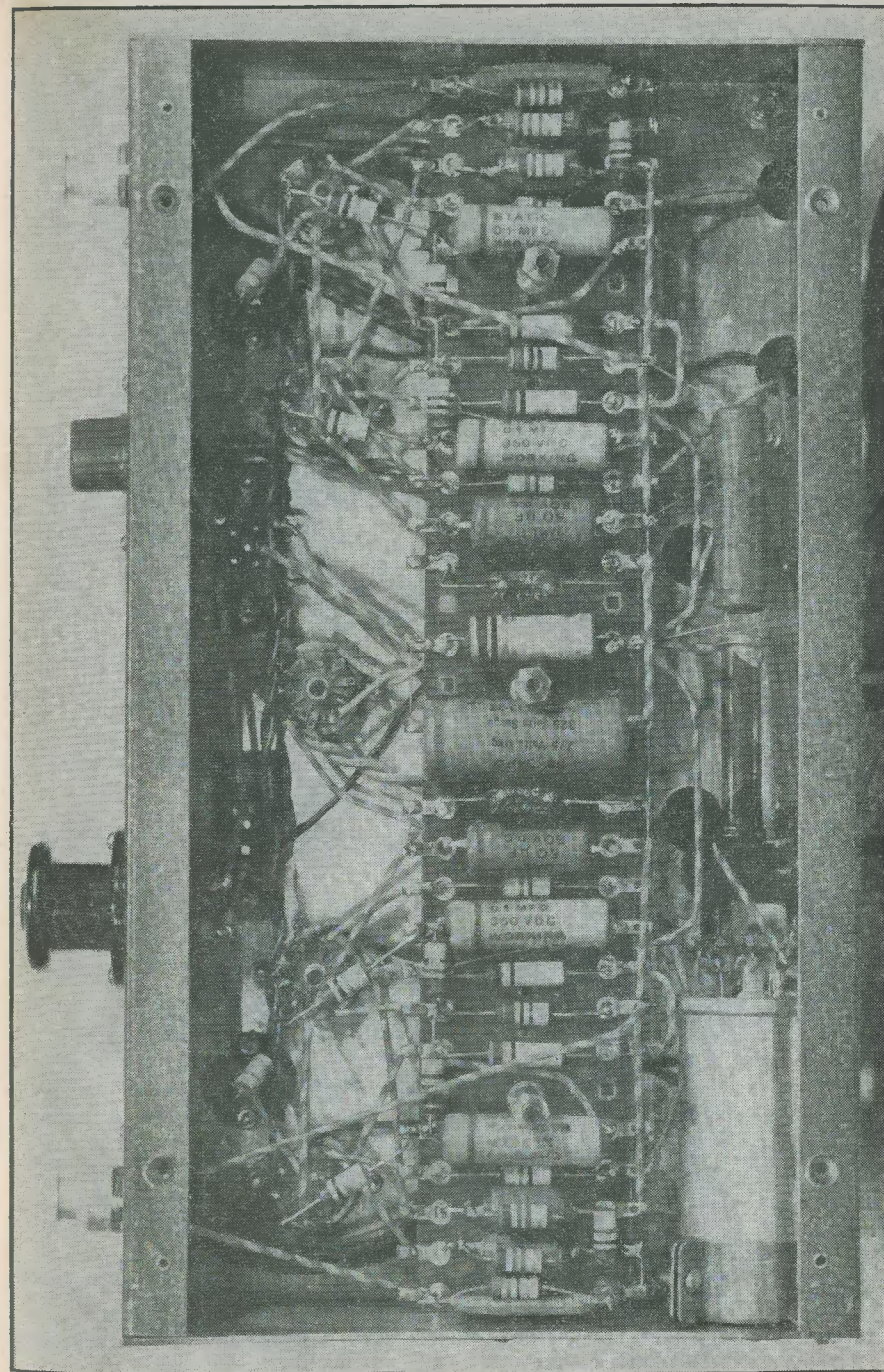

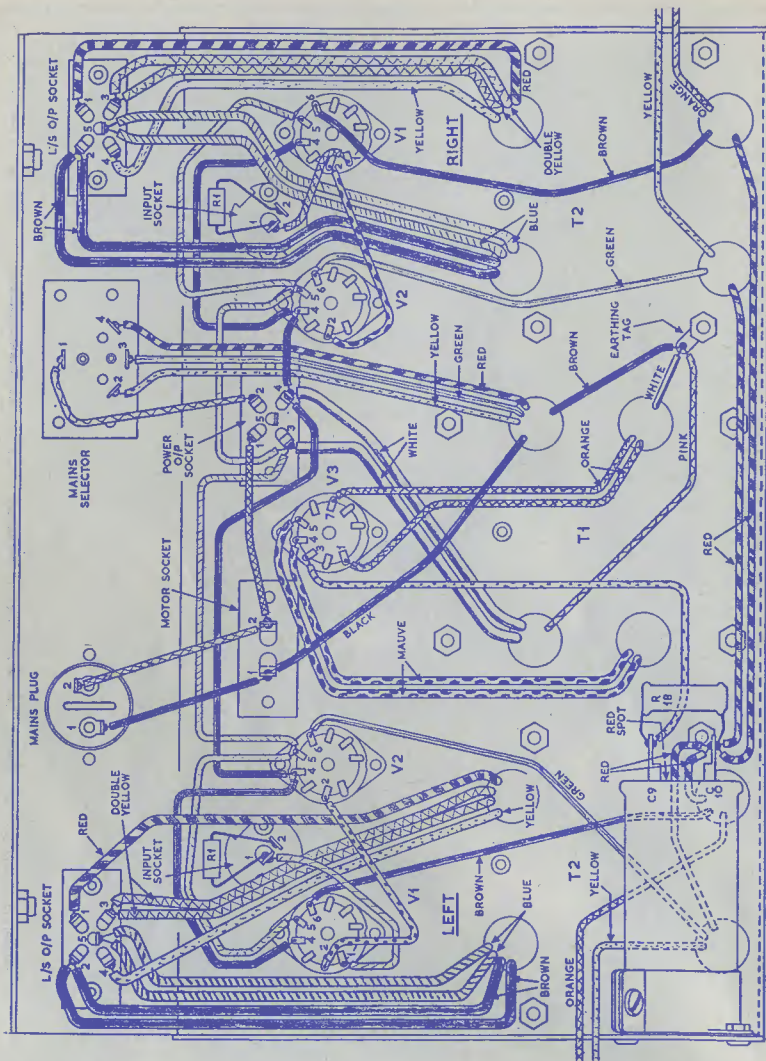

SMA2

Fig. 2
PRELIMINARY WIRING

Green flex—6 on V₂
Brown flex—6 on V₁
All red flex—C₁₀ (50+50μF capacitor, tag nearest chassis)

Heater leads (use the twisted flex provided):

4 and 5 on V₁ and V₂ (both)—3 and 4 on power output socket

Rest of wiring:

C₉ (red spot)—3 on V₃

2 on V₁—2 on V₂ (both)

1 on V₁—1 on input socket (both)

2 on mains plug—2 on motor socket—1 on power output socket

2 on power output socket—1 on mains selector

1 on input socket—R₁ (yellow/mauve/yellow)—2 on input socket (both)

Wiring the Group Board

This can be done before fitting in chassis or *in situ*. Refer to Fig. 3 and fit capacitors and resistors as follows:


A1 C₆ (3,000pF)/R₁₆ (blue/grey/brown)—B1

- A2 C₁ (50μF 12V)/R₃ (brown/red/red)—B2 (red end to A)
A3 C₂ (50μF 12V)/R₅ (brown/red/red)—B3 (red end to A)
B2 R₄ (brown/black/brown)—B3
A4 R₁₄ (yellow/mauve/black)—B4
A5 C₄ (0.1μF)—B5 (either way round—keep away from fixing holes)
A6 R₂ (brown/black/yellow)—B6
A7 R₁₃ (brown/black/green)—B7
A8 R₆ (brown/black/yellow)—B8
A9 C₅ (0.1μF)—B9

- A5 R₁₀ (brown/black/green)—A7
A9 R₁₁ (brown/black/green)—A7
A10 R₁₅ (yellow/mauve/black)—B10
A11 C₃ (50μF 25V)—B11 (red end to A)
A12 R₈ (390Ω)—B12
Repeat above from other end
A13 C₇ (32μF)—B13 (red end to A)
A14 R₁₇ (brown/black/orange, smaller of the two large ones)—B14

Wire up as follows (both ends):

- A6—B5
A8—B9

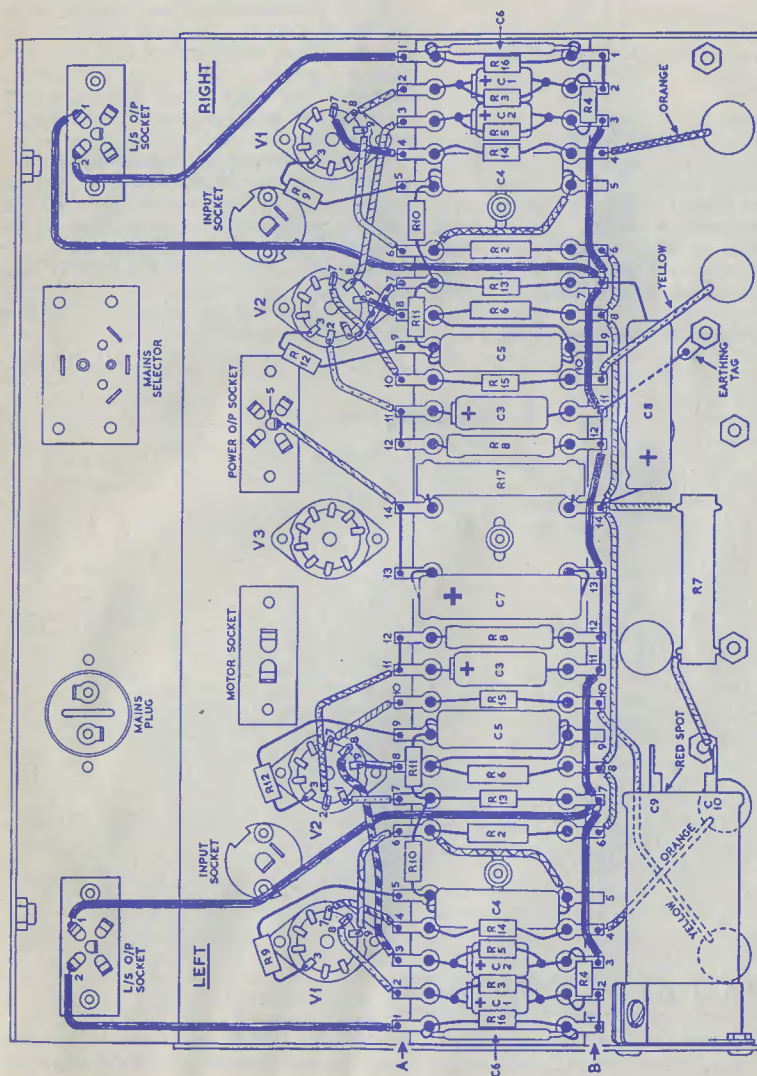

SMA3

Fig. 3
COMPLETION OF WIRING

A11—A12
 B1—B2
 B3—B7—B11—B12—B13
 B6—B8—B14
 Connect A13 to A14

To fit group board, adjust the three loose nuts to about $\frac{1}{8}$ in from the chassis, then place washers on them. Fit group board in position, then three more washers and finally secure with three more nuts. Wiring can then be completed as follows:

A1—2 on loudspeaker output socket
 A2—8 on V₁
 A3—8 on V₂
 A4—7 on V₁
 A5—R₉ (brown/black/orange)—3 on V₁
 A6—9 on V₁
 A7—1 on V₂
 A8—9 on V₂
 A9—R₁₂ (brown/black/orange)—3 on V₂
 A10—7 on V₂
 A11—2 on V₂
 Orange flex from T₂—B4
 Yellow flex from T₂—B10
 Repeat above on other channel
 B11 (right only)—earthing tag
 B14—C₈ (8 μ F)—B7 (right only) (red end to B14)
 B14—R₇ (brown/black/orange)—C₁₀

A14—5 on power output socket
 B7—1 on loudspeaker output socket

CHECK FOR DRY JOINTS!

Fitting the Base Plate

Screw three nuts on the group board mounting screws and adjust so that the base plate just rests on them when fitted. Secure with three more nuts. The chassis is fitted with 4BA locknuts for securing to cabinet.

Connecting Loudspeakers

The main amplifier, as described, is matched to two 15 Ω loudspeakers. Connections to the speaker plugs are as follows:

Short the two wider spaced plugs (3 and 4 on the socket) by soldering a piece of wire across. Then solder the speaker leads to the opposite pair (1 and 2). No 5 is not connected. The plug from your right-hand speaker will go to the socket marked "R" and *vice versa*.

If 3 Ω speakers are used the leads will go to the same two plugs (1 and 2), but short 1 to 3 and 2 to 4 instead of 3 and 4. It will also be necessary to change the feedback resistor R₁₆ to 470 Ω and the capacitor C₆ to 4,000pF. For 7 Ω or 8 Ω speakers short out 3 and 4 on the plug and connect leads to 1 and 5. 2 will not be used. Change R₁₆ to 560 Ω , C₆ to 3,500pF.

Components List

Resistors

R₁ 470k Ω $\frac{1}{4}$ W (2)
 R₂, R₆ *100k Ω $\frac{1}{2}$ W (2 pairs)
 R₃, R₅ 1.2k Ω $\frac{1}{4}$ W (4)
 R₄ 100 Ω $\frac{1}{4}$ W (2)
 R₇ 10k Ω 2W
 R₈ 390 Ω 3W (2)
 R₉, R₁₂ 10k Ω $\frac{1}{4}$ W (4)
 R₁₀, R₁₁, R₁₃ *1M Ω $\frac{1}{4}$ W (2 sets)
 R₁₄, R₁₅ 47 Ω $\frac{1}{4}$ W (4)
 R₁₆ 680 Ω $\frac{1}{4}$ W (2)
 R₁₇ 10k Ω 1W
 R₁₈ 200 Ω 10W
 * Matched to within 5%

Capacitors

C₁, C₂ 50 μ F 12V (4)
 C₃ 50 μ F 50V (2)
 C₄, C₅ 0.1 μ F 350V (4)
 C₆ 3,000pF mica (2)
 C₇ 32 μ F 275V
 C₈ 8 μ F 350V

C₉, C₁₀ 50+50 μ F 350V

Valves

V₁, V₂ ECL82 (4)
 V₃ EZ81

Miscellaneous

Mains Transformer R₁ (see text)
 Output transformer T₂ (see text) (2)
 Voltage selector, fused
 Mains plug and socket
 Output plug and socket (2) 5-pin
 Power output plug and socket 5-pin
 Motor plug and socket 2-pin
 Coaxial plug and socket (2)
 Valveholders, 9-pin (5)
 Nuts, screws, solder tags
 Wire, 22 s.w.g., tinned copper (3 yds.)
 Flex, twin, heater wiring (18in)
 Sleeving, 1mm (2 yds)
 Chassis, base plate, tagboard, screws with nuts and washers

FIRST PA \emptyset RTTY CONTACT

The first two-way RTTY QSO was made by PA \emptyset FB and G2UK on March 16th on the 80 metre band. Subsequent QSOs have since been made between PA \emptyset FB and G3CQE and G2UK.



Topics

By Recorder

THERE ARE FEW THINGS AS ANNOYING AS finding that the various parts of an assembly, after purchase, don't "fit together". The bits which fail to achieve a satisfactory marriage may consist of nuts which are tight or loose on the accompanying bolts, valves which don't reliably fit their holders (and, believe it or not, one of the harder things to mass-produce, even these days, is a valveholder which is 100 per cent satisfactory!), or other parts of similar type. Problems of this nature used to be infinitely more troublesome in the early days of radio than they are at present; and the main reason for their reduction has been that engineers, somewhere, have sat down and started work on drawing up standards which have closely defined such things as physical dimensions, chemical make-up and electrical properties of the component parts intended for electronic equipment. Today, the radio industry works to standards which cover almost every item of manufacture from the hardness of the mild steel from which chassis are stamped out to the activity and possible corrosive qualities of the flux with which joints are soldered.

The manner in which standards, whether published or "generally accepted", come into being provides a fascinating background to technological progress. In many cases, what later becomes a published standard requirement may well have originally been the arbitrary choice of a designer which, because of general approval, became "accepted in the trade". To take an example, it is standard practice, in this country and in the States, for most potentiometer spindles and the like to have diameters of a quarter of an inch. It isn't *essential*, however, for such a diameter to be used. What has happened here is that, many years ago, somebody commenced to use quarter-inch spindles (possibly because of readily-available quarter-inch stock) and, since this dimension proved to be convenient

for most purposes, it became generally accepted. I know of an instance in recent years when a new type of insulated wire was introduced to the market. The manufacturers quoted maximum diameters, including insulation, for the various gauges of wire in their range, but no minimum diameters. An engineer working for a firm using the wire found it necessary to set a standard for minimum as well as maximum diameters so that physical tolerances on coils wound with the wire could be evaluated. He suggested suitable figures, together with the means of calculating them from a consideration of the appropriate gauge, to the wire-maker. These figures were considered acceptable by the wire-manufacturer, who then advised all other users of the new set of limits applying to the product. And, in that manner, a standard was born!

Some of the more important standards in this country are published by the British Standards Institution. British Standard specifications are drawn up after extensive consultation between manufacturers, consumers, distributors and other bodies who may be affected or who are in a position to offer advice. Frequently, a British Standard specification incorporates requirements which have been common trade practice for many years before the specification was published. Alternatively, it is possible for a British Standard specification to lay down a single requirement where, previously, individual manufacturers have been following slightly different but, nevertheless, incompatible practices. It is in cases of this second type where the issuing of published standards is most valuable. It should be pointed out, however, that neither manufacturers nor consumers are ever bulldozed by a British Standard specification into accepting requirements with which they cannot agree. A British Standard specification is only published if it has the substantial support of

the manufacturers and users concerned.

It is generally agreed in the electronics trade that standardisation is wholly beneficial. Even if it does mean that the sockets of the radio set made by one manufacturer are capable of taking somebody else's valves as well as his own!

Hi-Fi Plugs and Sockets

A typical instance of the introduction of a standard has occurred in recent months, this being the result of work carried out by the recently formed Audio Manufacturers' Group of B.R.E.M.A. The A.M.G., which was formed in May 1959 and which includes such names as E. K. Cole Ltd., Decca Record Co. Ltd., Jason Motor and Electronic Co., and Standard Telephones and Cables Ltd., has applied itself to making good two of the main deficiencies in the audio equipment field. The first of these was a standard method of measuring and expressing the performance of amplifiers, and the second a standard range of inter-unit connectors. At the time of writing, work is still in progress on the first project, although it is hoped to publish recommendations shortly. So far as the second project is concerned a published standard* has now become available.

In its introduction the A.M.G. standard states that its requirements apply only to apparatus employing a double wound mains transformer, so that both mains leads are isolated from the chassis. The first section of the standard concerns the mains input wiring. The mains cable may either be permanently connected into the chassis with connections which are not accessible to the user under operating conditions and secured with a clamp to relieve strain, or it may be connected via a 3-way 5-amp socket and chassis-mounted plug, the latter having recessed pins. Dimensions for the plug and socket are specified in the standard. A 1.5-amp 3-way plug and socket should be used for mains outlets to auxiliary units such as gram motors.

Inter-unit power wiring between main amplifier and pre-amplifier or mixer unit should employ International Octal connectors. Such connectors may be fitted at both ends of the cable, or at the power amplifier end only. In each plug and socket assembly, the plug must always be that which is on the "dead" side of the junction. The accompanying table shows the recommended connections to be made to the pins of the octal connectors. These pins enable the main on-off switch to be fitted to the pre-amplifier control panel, pins 1 and 4 carrying the mains

input to the pre-amplifier on/off switch, and pins 5 and 6 returning the switched supply to the mains transformer in the power amplifier. Where a radio tuner unit requiring h.t. and heater power is to be supplied from the main amplifier the same arrangements are employed, with the exception that pins 1, 4, 5 and 6 are not used.

Pin Number	Service
1	Mains (N) from supply
2	Heater
3	H.T. positive
4	Mains (L) from supply
5	Mains (L) to transformer
6	Mains (N) to transformer
7	Heater
8	H.T. negative and Earth

As may be seen from the table, the interconnections via the octal plugs and sockets do not cater for a.f. In domestic installations, a.f. coupling between pre-amplifier or mixer unit and power amplifier should be obtained with the use of "phono-plugs". Microphone inputs for domestic installations should be made via jack-plugs and sockets. Screw terminals or a terminal block should be provided for loudspeaker connections. Alternatively, where frequent disconnection and re-connection of the loudspeaker is liable to occur and output power is low, a non-reversible two-pin plug and socket of the type employed for balanced aerial input connections may be employed. The final requirement in the standard is that all sockets shall be marked with their functions and that, where stereo channels are employed, the left-hand channel shall be colour coded grey and the right-hand channel brown.

And there it is, a group of manufacturers has got together and has created a standard where previously no standard existed. As time goes by we will almost certainly see hi-fi amplifiers confirm to the requirements of this standard. In years to come, people will be wiring up power supply sockets in the manner defined in the table, because it is "accepted practice", without even realising that, back in 1960, a group of people decided to recommend an arbitrary method of making interconnections!

The Collecting Instinct

Every now and again at this time of the year the do-it-yourself magazines tend to publish those look-Spring-is-here-and-now's-the-time-to-clear-out-all-that-junk sort of article. I'm afraid that exhortations of this

nature leave me absolutely cold because, whilst I *do* have a clear-out every now and again, I only do so when the space problem is getting quite impossible. And, even then, only junk of the most antedeluvian order gets thrown out.

Still, I'm not as bad as a friend of mine. He produced a box of odds and ends some weeks ago which really took me back through the years. Whilst they weren't of that era wherein constructors had to assemble their own tuning condensers, they represented a period which was not all that much later. Part of my friend's collection consisted of four-pin valveholders in which the four individual sockets were coupled to their terminals via a complicated spiral of springy metal. These valveholders were really sprung. If a valve inserted in one were tapped it would vibrate for at least half a minute before settling down. There were several of those beautifully-made and very solid Ferranti intervalve transformers. The collection boasted also one of those large Telsen medium and long wave coils with a series aerial condenser on the top, and wound with bright green cotton-covered wire. And, of course, all components had bright, shiny, nickel-plated terminals. The vintage was 1930 (a good year, that!) when, I sometimes think, radio had rather more enchantment than it has now. But all that statement means is that I'm becoming a bit of a fuddy-duddy.

Of course, in those days you built a radio which was then liable to become the centre of the family circle's ether-borne entertainment; whereas nowadays the one-eyed monster has caused many radio sets to be relegated to the background. But I am forgetting the very considerable enthusiasm for home-constructed television sets which became apparent in the years following the war, this being particularly strong when wide-angle tubes were introduced in 1952. *The Radio Constructor* launched two very successful wide-angle designs around that time, many of which are still giving yeoman service. When Band III came on the air, this magazine also covered, amongst other designs, the construction of the highly popular cascode Teletron converter. So, perhaps I had better qualify my statement

concerning home-construction and the telly by saying that what the home-constructor is waiting for always is something new to get his teeth into. Look out, Bands IV and V!

The Tunnel Diode

Finally, a few words about the latest semiconductor device to enter the electronic field. If you haven't heard about the tunnel diode yet you soon will. Already, at least one firm of semi-conductor manufacturers in this country is actively carrying out development work prior to going into production on this new device. The tunnel diode, invented in 1958 by a Japanese scientist, Leo Esaki, is a two-terminal unit which, when biased in a certain way, exhibits negative resistance. The manner in which the diode functions is complex, but it can be stated that the currents which appear when the negative resistance effect takes place are not composed of electrons in physical movement—as occurs in a valve or transistor. Instead, particles disappear in one section of the diode and pop up instantaneously in another, this constituting the "tunnelling current". The process is far quicker than occurs when electrons move in transistors and valves and, because of this, tunnel diodes are theoretically capable of oscillation at 100,000 Mc/s. Due to their high speed of operation, tunnel diodes will first of all probably find their way into calculating machines and the like. This application will then provide a sufficiently large market to enable manufacturers to iron out production problems. Eventually, they should be as readily available as germanium rectifier diodes are now. To give an idea of what tunnel diodes can do, General Electric engineers in America have built a miniature f.m. transmitter which consists of a tuned circuit, a resistor, a microphone, and a tunnel diode, together with a battery to put the diode on its correct biasing point. The negative resistance of the diode counteracts the losses in the tuned circuit, whereupon the latter just oscillates!

We shall be hearing a lot more about the tunnel diode in the future. In all seriousness I think that it may well represent almost as big a step forward in practical electronics as was provided by the transistor.

Next Month . . .

The "REGENT"

A 4-Valve Portable Battery Operated Receiver Incorporating Low Consumption Valves, Printed Circuit and Ferrite Rod Aerial

RTTY In Theory and Practice

by J. B. Tuke, G3BST

PART 1

THE RADIO TELEPRINTER SYSTEM OF COMMUNICATION as applied to Amateur Radio offers a number of very definite advantages. These are: (a) high speed of communication exceeding that available on CW; (b) a printed record of the printed material is available; (c) more effective use is made of the permitted power compared to A₃ transmission, resulting in greater intelligibility at the receiving end; (d) freedom from certain types of interference; (e) absence of "shock effect" at the transmitting terminal which may, in some cases, reduce TVI.

However, before consigning all A₁ and A₃ equipment to the nearest scrap heap, it would be as well to note some of the disadvantages as well. From the amateur's point of view these are (a) the necessity to own (and therefore service) a teleprinter; (b) in order to make full use of advantage (a) one must be able to type—or rather teleprint since there are some minor differences; (c) more complicated receiving apparatus is required and a slight modification must be made to the transmitter; (d) the transmitter is run under "key-down A₁" conditions throughout the whole transmission, so that valves and components must be run within normal manufacturer's ratings.

Each of the advantages and disadvantages listed above are due to some particular peculiarity of the system and if, therefore, we study it (mainly from the amateur's viewpoint) in detail it will be possible to assess it as a communication system intelligently.

The printer itself is the first essential, and a short study should be made of its method of working. From a practical point of view this can be followed by turning the machine over by hand and watching the various mechanical actions. One will rapidly come to the conclusion that its inventor must have been a mechanical genius of the first order.

Let us, at this point, look upon the teleprinter as two completely separate instruments—a transmitter and receiver,

driven by a common motor. The result of the mechanical functions of the keyboard is to move a single-pole-double-throw switch into alternate positions—these positions being known conventionally as Mark and Space. The "at rest" position is Mark; the alternate, Space. If, while a letter on the keyboard is depressed, the mechanical action is followed slowly, it is found that subsequent to the engagement of a pawl and ratchet the initial move of the switch is from Mark to Space, following which there will be five further movements which may be to Mark or Space according to which keyboard character was depressed. For example, depression of the letter Y results in, first, the initial Space which precedes all characters and then the sequence Mark, Space, Mark, Space, Mark, whereas if the letter R is depressed the sequence (again after the initial Space) is Space, Mark, Space, Mark, Space. It will further be observed that following every character there is a definite "rest" period with the switch in the Mark position, and that the next character cannot be depressed until that period is completed.

We may now represent this action graphically—imagining the Mark contact on the switch to be connected to a positive voltage and the Space to a negative voltage, while the centre moving tongue is connected to a centre zero meter. The resultant voltage/time graph for depressing the letter Y is shown in Fig. 1.

At this point it would be appropriate to give the initial Space and the final Mark signals which are present on all characters their correct names—they are called the Start and Stop signals respectively. The reason for this will be seen as study of the system progresses.

The dispositions of the Mark and Space signals in between Start and Stop, which represent the character depressed on the keyboard, follow a definite international code—known as the Murray Code. It should not be forgotten that there are other versions of

this method of signalling—due sometimes to the particular model of teleprinter in use, or to the country from which the signals originate. It is quite possible when intercepting random radioteleprinter signals to receive strings of meaningless characters due, not to a different language, but to the use of a different code. However, completely different codes are mostly used by Eastern countries and need not concern us here. It should, however, be borne in mind that different models of teleprinter have slightly different character representations—mostly those on the "Figure Shift" or connected with non-typing mechanical functions of page-copy printers. Some incompatibility is to be expected, therefore, when operating old type 3 machines in connection with modern page-copy machines.

To return to the operation of the transmitting keyboard, it will be obvious that the speed at which the switch movement (and therefore the speed at which the Mark and Space signals) are transmitted will be dependent only on one thing—the speed of the motor. It will have no connection whatever with the speed at which the teleprinter keyboard is being manipulated by the operator.

If the mechanical action of the switch and therefore its voltage output is followed in relation to time, it will be found that the Start and the following five signals are all the same length, while the Stop signal is half as long again. If we consider the length of the Start signal as one unit, then the entire character sequence will consist of 7½ units—that is, Start, 5-Mark/Space, Stop. Consequently this particular teleprinter code is quite often called the 7½-unit code.

In the British system the motor speed is such that the length of one unit is 20 milliseconds. This means that any device handling the signals transmitted by the teleprinter must be capable of responding accurately to a signal of 20 m.sec length. While signals longer than 20 m.sec may appear due to Mark following Mark, or Space following Space, signals shorter than 20 m.sec cannot occur with this particular motor speed. Since the length of the basic signalling unit is obviously of prime importance, telegraph engineers use a term called the Baud to describe it. The speed of operation of any particular system in Bauds is equal to the number of basic signalling units which could (theoretically) be transmitted in one second. In the case under

discussion this will be $\frac{1}{0.02}$ (since 20 m.sec equals 0.02 seconds)—that is 50. We can, therefore, say that our teleprinter is operating at a speed of 50 bauds, which as we will see

later tells us all about the speed at which any relays in the circuit between transmitter and receiver may have to operate, and also about the bandwidth requirements.

The American system uses 45.5 bauds—that is to say, the basic signalling element is slightly longer. In order to be compatible with that system it would be necessary for the owner of a British machine to slow down the motor slightly, thereby lengthening the signalling element—and this may be done by adjustment to the motor governor.


Referring back once more to our own British system, we have said that the basic signalling element is 20 m.sec long and that each character is 7½ units in length. A single character transmission will therefore occupy $7\frac{1}{2} \times 20 \text{ m.sec} = 150 \text{ m.sec}$ (0.15 sec). Providing a series of such characters were depressed by a "perfect" operator, each commencing at exactly the instant the previous one had finished, the maximum number of characters which could be sent

in one minute would be $\frac{60}{0.15} = 400$. The average "word" may be said to consist of five letters plus a space, making six in all, and the maximum number of words per minute that the system can handle is therefore $\frac{400}{6} = 66.6 \text{ w.p.m.}$ From a practical point

of view, if 55 w.p.m. can be maintained then one can be well satisfied with one's teleprinting prowess. The near-maximum speeds can only be continuously maintained by automatic transmission equipment, which is unlikely to concern the amateur at present.

Having studied the essentials of the transmission side, let us now turn and brush up our knowledge about the receiving mechanism.

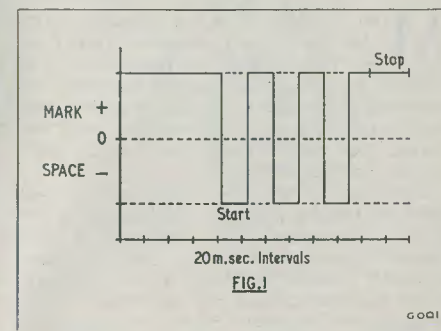It will be known that incoming signals from a "distant" printer keyboard are fed to an electromagnet which is normally neutrally biased—that is to say, it will lie at rest in either position. Turning the machine



over by hand will reveal that in one position no printing action takes place since the pawl and ratchet mechanism is disengaged and the main camshaft does not rotate. This is the magnet position corresponding to the transmission of a Mark signal from the distant machine. Directly the magnet moves over to the opposite, or Space position, the pawl and ratchet engages and receiving action commences. This magnet movement will, of course, be as the result of the "Start" signal from the distant printer. The magnet now operates a striker blade which, according to whether it is in the Mark or Space position will, via a pin, move any of five fingers on the receiving mechanism, causing them to be pushed inward if a Mark signal is received. Once the five fingers have been set up at the end of the character transmission, they operate a series of slotted circular combs deciding which bell crank may be allowed to fall. This in turn controls the position of the rotating typehead and therefore which letter will be printed. During this time the magnet has returned to the Mark position as a result of the distant Stop signal, and nothing further happens until the next Start signal is received. It should be noticed that the character now set up will be printed during the early part of the succeeding character transmission—so that the printed character is always "one behind".

The letter/figure shift is operated by a certain Mark/Space combination (sometimes different for different models) and its action is to operate a sixth comb, thereby doubling

the number of characters already obtainable. Those with experience of typing only who are interested in the teleprinting system should note that once the "Figures" key has been operated, the instrument is on figures until the "Letter shift" key is depressed. On the type 3 machine these keys are called "Letter Space" and "Figure Space". It is impossible to transmit G3BST exactly as written—it will appear as G 3 BST. On the page copy printer the operation of figure and letter shifts are not associated with the space bar, and do not operate the carriage, so that a combination of letters and figures without the intervening spaces is possible. These characters are the "Non-typing mechanical functions" mentioned earlier. Having now studied—albeit rather briefly—the action of transmitting and receiving separately, it is suggested (as already recommended in earlier articles) that keyboard and receiving mechanism should be connected together and the machine operated by turning the motor over by hand—the "modus operandi" will then become perfectly clear.

While direct connection between transmitting and receiving portions of the teleprinter present no difficulty, reference to Fig. 1 reminds us that we are dealing with what is, in fact, practically a square waveform. We can, therefore, expect trouble when we attempt to transmit this waveform down a long line, or over a radio link. The type of trouble that occurs, how serious it is, and what can be done about it will be discussed in the next article.

RADIO

INCREASING TUNING INDICATOR SENSITIVITY

by A. G. PILLIDGE

MOST READERS WILL BE FAMILIAR WITH the reasons why accurate tuning of an f.m. receiver is necessary. The problem of providing a simple and sensitive indicator is not easily solved, however, and many constructors will have felt, with the writer, that the conventional "magic eye" circuit is rather inadequate.

Undoubtedly the best solution is a null point indicator such as that published in *The Radio Constructor* and reprinted in the "Jason" tuner handbook. This method, however, entails the use of a double triode and a milliammeter and will add substantially to the cost of building a tuner.

The tuning indicator circuit described here provides a considerable increase in sensitivity compared with the usual circuit, but costs little more. The argument which led to its use is as follows.

Let us begin with the usual arrangement, shown in Fig. 1. Here a negative voltage derived from the ratio-detector reservoir capacitor is applied to the grid of a "magic eye" tuning indicator. The negative voltage is, in theory, almost constant over the ratio-detector pass-band but, in practice, a shallow peak usually occurs at the mid point. The tuning indicator should show this peak. It does so, but for two reasons the indication

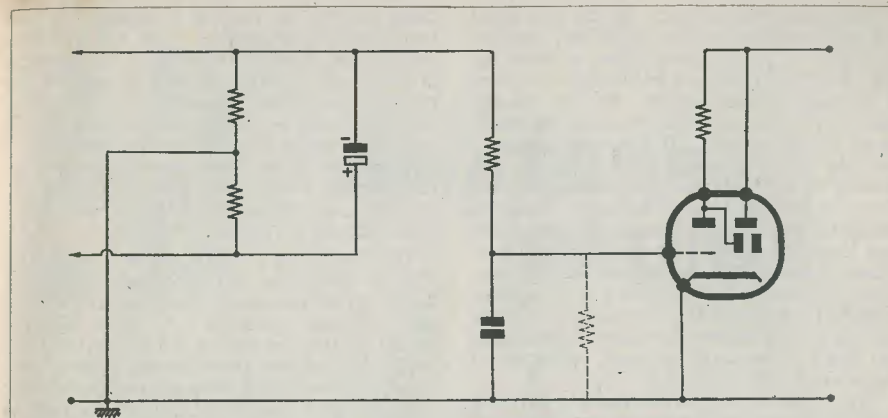


FIG. 1.
Normal Indicator Connection.

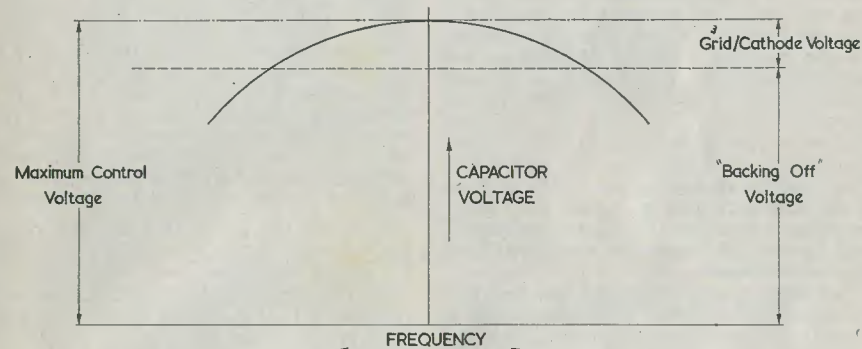


FIG. 2.
Diagram of "Backing Off" Method.

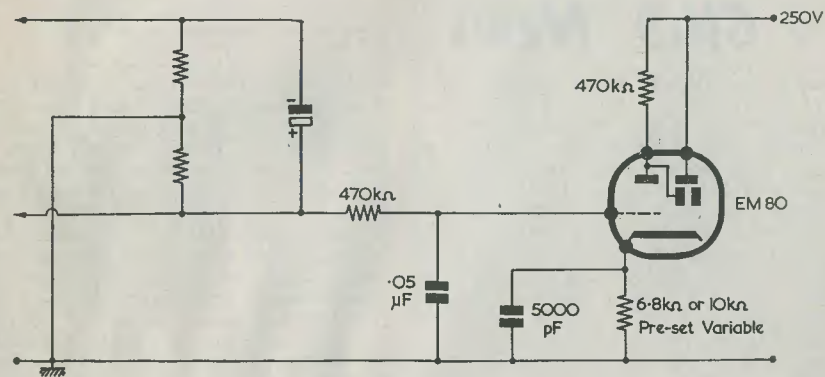


FIG. 3.
Indicator with Cathode Bias.

M722

is often a very poor one. In the first place the grid voltage may be sufficient, particularly with a "local" transmitter, to close the eye. For this reason the eye is often fed from a voltage divider (given by the dotted resistor in Fig. 1) which reduces the sensitivity of the system. The second reason is that the triode grids of most indicators are wound with "variable—mu" characteristics. This means that the indicator becomes progressively less sensitive as the eye closes and leaves us with the dismal alternatives of either working the indicator in its least sensitive region or reducing the applied voltage (and hence the sensitivity) to bring the eye to a more sensitive state. In each case the result is the same—a poor indication of the correct tuning point.

The variation of reservoir capacitor voltage with i.f. frequency is shown diagrammatically in Fig. 2. It is fairly obvious that if we could "back off" part of this voltage as shown by the horizontal dotted line, we could work the indicator in its sensitive region. This "backing off" could be achieved by applying a positive potential to the grid of the indicator, but the practical problems of doing so are quite considerable. In particular, no positive potential must be allowed to "leak back" to the ratio-detector, or its a.m. limiting properties will be drastically upset. A more promising way of achieving the same thing is to apply a negative voltage to the cathode of the indicator. This is, in fact, quite easily arranged—particularly in "new construction"—but may not be so simple when modifying existing equipment.

In a receiver with a balanced ratio detector, however, another "twist" can be given to the circuit which gets round the above difficulties. Suppose that a positive voltage is applied to the cathode of the indicator. This can be

done merely by putting a resistor in the cathode-earth connection. The eye will now close in the absence of a signal. If now the grid is supplied from the positive side of the reservoir capacitor, the eye will open as a signal is tuned in. By suitable choice of the cathode resistor the eye can be brought to its most sensitive state (i.e. nearly open) when the receiver is correctly tuned. This is, in practice as well as in theory, a very great improvement on the circuit of Fig. 1.

The circuit used by the writer is shown in Fig. 3. The value of the cathode resistor is fairly critical and may require adjustment to suit different receivers. A good method would be to substitute a pre-set variable of, say, 10kΩ for the fixed cathode resistor and to adjust this so that the eye is not more than, say, one-fifth closed when the receiver is correctly tuned to any of the three "local" transmissions.

If the receiver must be suitable for use with widely different signal strengths, the indicator can be modified to give variable sensitivity levels. Several possibilities come to mind. For example, the cathode resistor may be split into two parts, one of which can be short-circuited by a single-pole switch. With the switch closed the indicator will work on small signals but will "overload" (i.e. open fully) on strong ones. Opening the switch increases the positive bias and enables the indicator to cope with a strong signal.


It should be noted that the use of the positive side of the balanced ratio-detector for tuning indication does not in any way affect the negative potential required in some receivers for a.v.c. When modifying such a receiver, care must be taken to see that the a.v.c. line remains connected to the negative side of the reservoir capacitor.

Club News . . .

Harlow and District Radio Society. Hon. Sec. B. H. Wynn, "Black Cat", Abbess Roding, Ongar, Essex. A mobile rally is to be held at the Village Hall, Magdalene Laver, near Harlow New Town, Essex, on the 5th of June. Two members of the club will be "on the air" to guide visitors—G3ERN on 160 metres and C3JMA operating on 2 metres. Club members will be very pleased to see anyone who cares to come along. In addition to displays of radio equipment, etc., there will be features of interest for the wives and children. Refreshments will be available at reasonable prices. Cray Valley Radio Club. Hon. Sec. H. W. Mills, 59 Amherst Drive, St. Mary Cray, Kent. An invitation is extended to all inter-

ested in amateur radio transmitting and kindred subjects. Meetings are held on the fourth Tuesday of each month at the Station Hotel, Sidcup, Kent. On 24th May, at 8 p.m., a brains trust session will be held.

Halifax & District Amateur Radio Society. Hon. Sec.: A. Robinson, G3MDW, Candy Cabin, Ogden, Halifax. On 9th April the members paid a visit to a television studio in Manchester and on 12th April they met at the Sportsman Inn, Ogden, to hear a lecture on Fire Prevention. The A.G.M. will be held on 3rd May and an informal meeting on 24th May. A lecture on Workshop Practice will be held on 14th June. New members are welcome and application should be made direct to the Hon. Secretary.

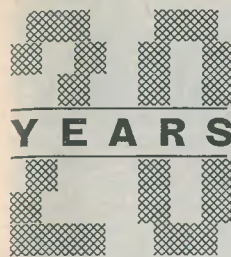


20 YEARS of AMATEUR RADIO

by G5UJ

HOW LONG IT SOUNDS—20 YEARS—YET how soon it passes, especially when applied to ham radio! Nineteen thirty-six was the year, though "tests" were made with an artificial aerial some 12 months earlier, using the call sign 2BSF. But it was in April, 1936, that the writer—using a simple home-built single-valve ECO—managed to raise his first contact, OK2MM, on 7 Mc/s (C.W.).


The input was just eight watts, to an "end-on" aerial sixty-seven feet long! The Rx in use was a "straight" 0-v-1 "home-brewed," and battery-powered! Contacts with OH, SM, LA, OZ, and DL quickly followed using the same rig, until the writer—tiring of "forty"—ventured on to 160! A "Goyder-locked" oscillator (PX4) together with a 2-stage modulator and a carbon mike, produced quite encouraging results, with the 67ft aerial now tuned Marconi fashion against ground. Indeed, some eleven or twelve countries were raised on the key on "top band" within 18 months.

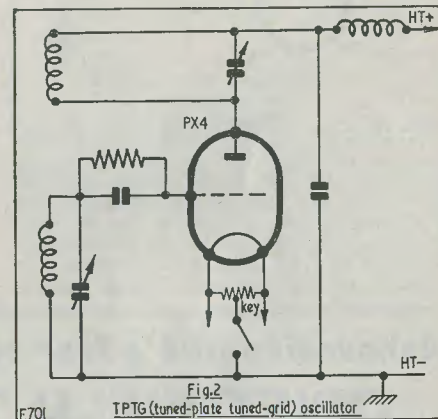

During the following three years many popular circuits were tried, with varying results, but power input never exceeded ten or twelve watts. Perhaps the best Dx results were obtained with the series-fed Hartley (shown in Fig. 1). Close in order of efficiency and all-round usefulness was the TPTG, (Fig 2) or when in push-pull termed the TNT (Fig 3).


As will be noted, all these oscillators were "self-excited," necessitating very rigid and careful construction, especially in the tank circuits in order to obviate frequency drift. Tone reports—as can be imagined—often left much to be desired, and it was not until the inception of the quartz crystal, as a stable oscillator, that the standard of transmission improved. About this time, also, more efficient power valves became available, such as the Taylor T40 and T55, etc., and the beam-tetrode (6L6) was becoming fashionable.

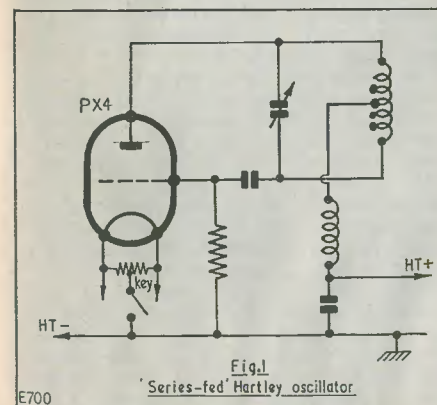All this tended to bring about a change for the better in amateur radio, and, broadly



Is that tube Really Finished?

By P. S. F. JACKSON

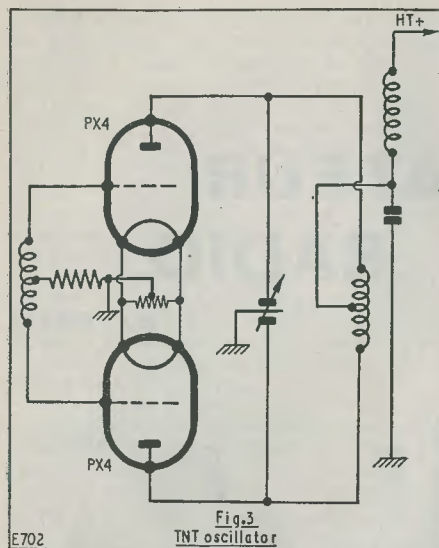

speaking, amateur transmissions generally took on a "new look" as regards quality, and some excellent speech could often be heard on 80m, sometimes bearing comparison with the B.B.C! By this time, however, the shadow of war lay over Europe, and by

September 1939 all amateur activity, as such, ceased, and all equipment was impounded for the duration! The termination of hostilities in 1945 saw the return of all impounded gear (February 1946 in the writer's case) and the ban on amateur activity was lifted. In the general scramble to get back "on the air," ten metres came in for a fair share of popularity, and many Dx records were set up; and some firm friendships were made "across the pond" with our friends in W-land! By this time many Ex-service receivers, both British and American, made their appearance, notable amongst which were the AR88/77, BC348/2, and, of course, that "evergreen," the ex-R.A.F. 1155 (still in use at G5UJ)!

Attention now began to turn in the direction of v.h.f. and the 144 Mc/s and 70cm bands became of interest and valves of the 832 and 829B type were becoming familiar. Beam aerials (although long popular in the States) began to make their appearance in G-land, and stacked-arrays were to be seen in many parts of the country. Another innovation was the commercially-built Tx—a thing completely unheard-of in British shacks pre-war. Many really fine jobs were produced.

Which brings us to the present, with its quota of QRM on our "shared"-bands, and which finds the writer wrestling with a couple of transistors in a matchbox! Progress, or second childhood?

Announcing RCA's four new DRIFT-FIELD TRANSISTORS

Specifically Designed for FM and AM/FM Radio Receivers and Tuners

R.C.A. is pleased to announce to the industry four new drift-field transistors of the germanium p-n-p alloy type specifically designed for use in f.m. and a.m./f.m. radio receivers and tuners—the 2N1177, 2N1178, 2N1179, respectively, for r.f.-amplifier, r.f.-local-oscillator, and r.f.-mixer service at frequencies up to 120 Mc/s; the 2N1180 for i.f.-amplifier service at frequencies up to 10.7 Mc/s.

Because of their small physical size and use of R.C.A.'s drift-field construction, these transistors have small effective base width, low feedback capacitance, and a high collector-to-base breakdown voltage features which, for the first time make possible top oscillator and amplifier performance in the f.m. band. In addition, the low-frequency characteristics of these transistors are carefully controlled to ensure dependable performance in the standard a.m. broadcast band. As a result, these transistors provide the equipment

designer with a transistor complement which makes practicable quantity produced f.m. and a.m./f.m. radio receivers and tuners having high gain, high sensitivity, excellent stability, good signal-to-noise ratios, and good a.g.c. capabilities.

For example, in a typical f.m. tuner operating at a frequency of 100 Mc/s, the 2N1177 is capable of providing a power gain of 14dB; and the 2N1179, a conversion power gain of 17dB when followed by a 10.7 Mc/s i.f.-amplifier stage.

The 2N1180 in a 3-stage 10.7 Mc/s i.f.-amplifier circuit is capable of providing a useful power gain of 65dB with neutralisation or 57dB without neutralisation.

The 2N1178, when operated in local-oscillator service at a frequency above that of the incoming r.f. signal, can supply a 2N1179 r.f. mixer stage with the required oscillator-injection voltage for optimum mixing throughout the f.m. band.

WHENEVER THE PICTURE DISAPPEARS, THE service engineer is nearly always asked "Is the tube done?" Whilst this is often the case, a great deal can often be done before finally consigning the tube to the scrap heap.

The first step is to decide if the tube is to blame. If, when the brightness control is turned up, a raster appears and can be controlled, the vision circuits should be suspected. It is worth mentioning that if a raster does not appear when turning the brightness up, the ion trap should be rotated and slid along the tube neck before condemning the tube as faulty or unserviceable. The ion trap position may change as the tube ages. Also, components immediately associated with supplies to the tube should be checked by voltage tests to all electrodes (e.g. the decoupling condenser from a₂ should be checked for short- or open-circuit or resistors to the grid used in frame blanking may be open circuit).

When it is finally decided that the tube is faulty we must now see if anything can be done. Before going further it would be best to see what causes tubes not to deliver the "goods". Summed up, these are:


- (1) Shorts between electrodes.
- (2) Internal disconnections of electrodes.
- (3) Heaters burnt out.
- (4) Soft or gassy tubes.
- (5) Dry joints in the soldering of the lead-in wires and the pins on the base.
- (6) Cathode poisoning.

Some of these may seem pretty deadly, but with a little patience and perseverance it is surprising what can be achieved.

Dealing with them in the above order, the method of removing shorts between electrodes is quite simple and requires nothing else other than high capacity electrolytics such as are commonly used in the smoothing circuits of television receivers. Remove the base holder from the tube and, after charging the electrolytic between h.t. and chassis, apply the leads to the pins of the shorted electrodes. Incidentally, it may be difficult to find which electrodes are shorted as it is only when the tube is "hot" that these shorts may show and cause trouble, and if tested when cold, no reading will be obtained on the

meter. To test for this, all connections to the tube except the heaters should be removed and the tube allowed to warm up, then test for shorts. It may take several applications to burn out the short. It is interesting to note that these shorts are caused by an electrolytic action on the metal parts of the tube causing a thin film of deposit between the electrodes.

The next fault cannot be permanently cured except for open-circuited heaters; the latter we will deal with in a moment. When any of the other electrodes become disconnected internally, it is generally caused by an inherent weakness in the metal or welding which has not stood up to the expansion and contraction when the heaters are switched on or off. Often the tube can be made to give temporary service by tapping the base with the handle of a screwdriver. This should be done carefully and not with great force, and whilst looking at the screen to find where to tap. At a certain point flashes will appear on the screen, and the base should be carefully tapped until the picture or raster reappears. The writer had one tube working for some six months after this procedure (without any tapping during that time). If the grid becomes open-circuited the brightness control will have no effect, and the picture will be lost in dazzle. If the cathode is disconnected there will be no raster or picture. In pentode or tetrode tubes, disconnection of the subsidiary anodes will show up as very poor focusing and sometimes

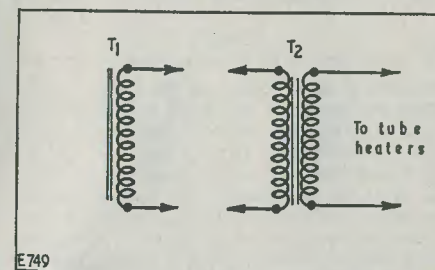


can be cured by increasing the flux of the focus magnet or, in the case of self-focusing tubes, the use of a very weak flux magnet

suitably placed (an ion trap magnet has been used with success in a similar situation).

When one looks at the neck of the tube and after scraping away the dirt is dismayed by the absence of the glow from the heaters,

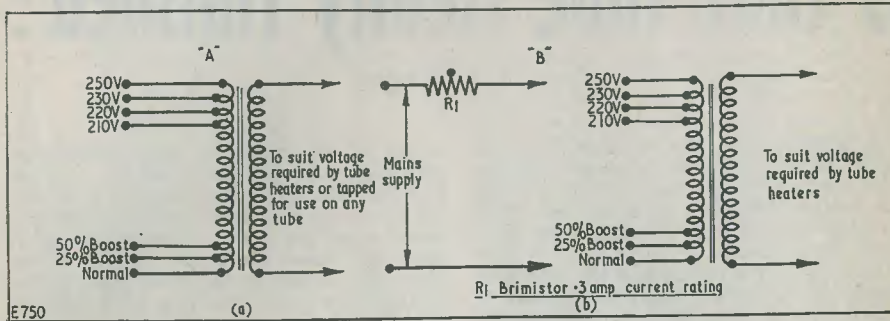across the heaters is obtainable it may mean that the heater is shorted part way up the spiral or hair pin. Great care should be taken, as in a.c./d.c. sets when the tube is in series with the valves to switch on may mean



all is not lost. If one of the instruments for welding disconnected heaters is available this can be done without removing the tube; however, not everyone can afford forty-odd pounds for such an instrument, yet it is still possible to salvage what seems a hopeless mess. First, put a shorting link across the

burning out a valve or valves due to excess current of the tube being drawn through the valve chain. As a protection it is wise to use a Brimistor in series with the heaters on a.c./d.c. or in series with the primary of the mains transformer on a.c. sets. However, if the heater is checked by the use of an i.t. transformer of the correct voltage, one can generally judge from the brightness of the heater what the condition is, though it has been known for new tubes to have drawn more current than rated and, whilst they would not work in a.c./d.c. sets, work perfectly in a.c.-only receivers where the heaters are supplied from a transformer.

In the case of a soft or gassy tube, nothing can be done. It shows up as a flat picture, probably defocused, and without correct contrast brightness settings being obtainable. If positive proof is required, connect a 500 microamp meter in series with the cathode, and if the reading is over 275 microamps this tube can only be condemned. Whilst it is possible to get the tube re-gassed, this is often not successful as air has filtered into the tube either through a flaw or crack in the glass of the tube or between the glass seal and the metal lead-outs at the base of the tube, the latter being caused by the co-efficients of expansion of the glass lead and metals not being properly matched.

Occasionally a dry joint in the soldering of the pins and the lead-out causes a poor or intermittent picture. The cure is to run some solder down the pins, keeping the iron on long enough to ensure a good joint. In cases where the base has become loose, if twisting gently on the base causes the fault to come and go, one can fix the base in a working position with Sellotape or, as the writer had to do, remove the base and solder the supply leads directly to the lead wires.

A TEST LOUDSPEAKER

by K. E. Marcus

The Loudspeaking Headphone

ANNNOYED BECAUSE HE HAD TO WEAR headphones for long hours while checking communications gear with only 'phone or line output, the author modified, many years ago, the final stage of an old a.c./d.c. broadcast receiver to act as a "loudspeaking headphone".

In principle this piece of ancillary equipment was a huge success, as it did away with the wearisome "earblinkers". But physically it was an abomination and it has been the source of quite a few nasty shocks ever since.

The Test Loudspeaker

Again, a few years later, another piece of equipment was knocked together. It consisted of a plug-line, which could be inserted into the 'phone or line jack of the gear under test, and it ended in an output-power meter. A five-position switch laid either the speech coil of a loudspeaker, or a transformer, across this line. Diagram No. 1 shows how this was done.

The transformer itself is the output transformer of an ex-army P.C.R. In position 1 of the switch the speech coil is across the line in parallel with the output meter. In position 3 the 600Ω secondary is across the line and the 3Ω secondary is connected to the speech coil. In position 5 the primary of the output transformer in series with a 4μF paper capacitor is across the line and, again, the 3Ω secondary is connected to the speech coil. In positions 2 and 4 the loudspeaker is disconnected, and the output meter only is in circuit. The plug-line is left floating, being nowhere earthed, except if the gear jack provided an earthing of the plug body.

For years this rather crude piece of equipment has given yeoman service to the author, since it permitted him to align gear to tone and output meter observation, while a flick of the switch to the blind positions allowed correct meter readings. This test loudspeaker was technically a success, but rather unsightly.

The New Test Equipment

There appeared, recently, on the surplus


market an RCA loudspeaker in a handsome black crackle steel cabinet, and it was decided to combine the old loudspeaking headphone, this time, of course, in a.c., with the test loudspeaker. This rationalisation produced a very useful piece of laboratory gear, the circuit of which is given in diagram No. 2.

The old five-position switch was fitted into the lower right-hand corner of the front, with the output transformer (T₁) and the block capacitor (C₁) next to it behind the switch inside the steel cabinet. Into the right-hand wall was fitted a jack for the output meter plug. Thus the output meter became mobile, if required. Thereafter the wiring of the old pattern was restored with vastly shortened connections, and tested.

The fitting of a "loudspeaking headphone" into the left half of the cabinet seemed at first to be a bit of a problem, as there is not much room. However, a solution was found finally: there was in the spares box a mains transformer of the Civilian Wartime Receiver, which proved eminently useful for the application in hand. It is a rather sturdy job of 0-200-250V primary, 250-0-250V, 70mA h.t. secondary, plus two heater windings; of these the 4V rectifier winding was left unused. It has a paxolin board fitted on top, which contains a rectifier base; this board was removed and an aluminium platform fitted instead, which was cut to fit snugly into the left-hand corner of the cabinet.

The layout Fig. 3 shows its shape. Near the frontplate an octal valveholder for the KT61 was fitted; above the transformer came one for the 6X5. A pilot lamp holder was soldered across the heater line directly below the KT61, so that the lamp will come opposite the telephone indicator lens, when the unit is inserted into the cabinet. The two electrolytics were fitted near the left side wall to the platform in an insulated manner.



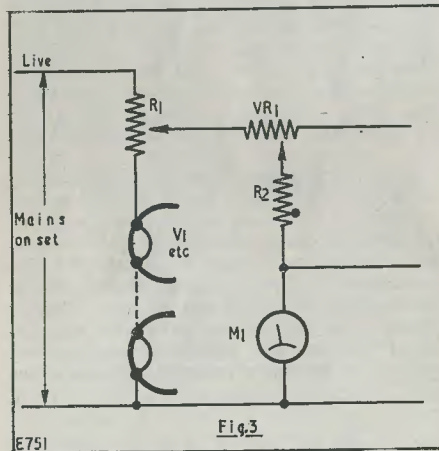
The wiring-up of the amplifier unit should be completed before it is inserted, and must be carried out with care. Since the plug-line is to be left floating again, the chassis cannot be used as the reference line, but a neutral



tube holder after removing the tube. Next, connect a length of insulated wire from the live side of mains to one of the heater pins, then another length from a suitable tap on the mains supply so as to obtain 40-50 volts a.c. and, after switching the set on, touch momentarily to the other heater pin, when the heater should start to glow. It is worth trying several times and, if still not successful, increase the voltage. It must be emphasised that to apply this voltage too long may repair the break in the heater and then completely burn it out. Even if a continuity reading

connecting wire has to be used throughout. It is recommended to check that this neutral line is nowhere in metallic contact with the body of the amplifier unit, which is earthed

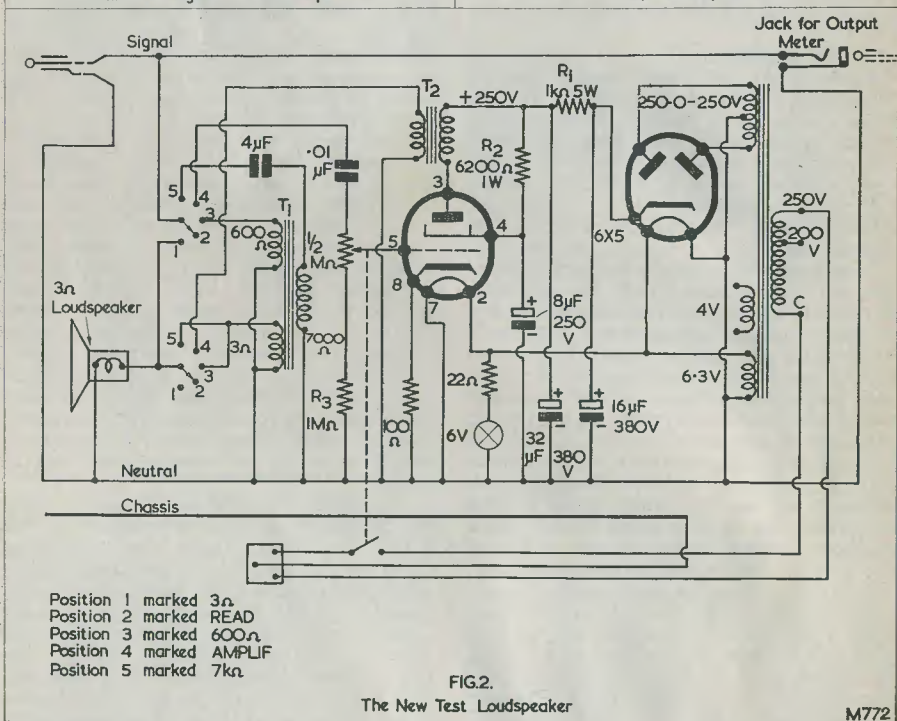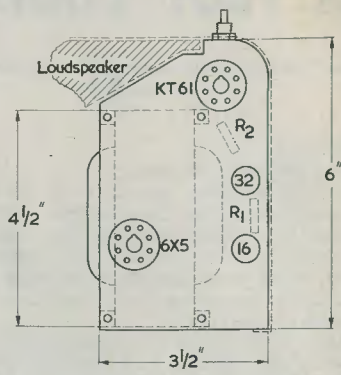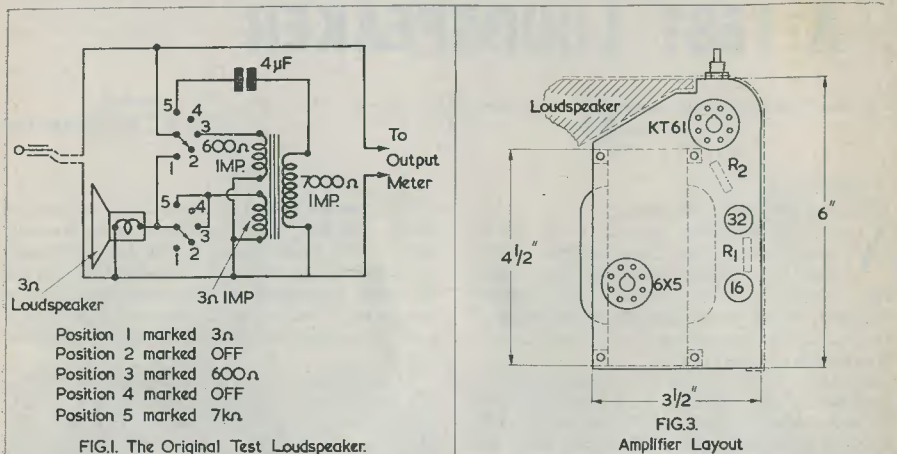the left-hand lower corner of the frontplate of the cabinet, corresponding to the switch on the other side, and a small telephone indicator lens is fitted about 1in above. With



through the cabinet.

The Assembly

The volume control plus switch goes into

the help of a small paxolin tagstrip fixed to a convenient loudspeaker bolt, the connections to the volume control (C_2 and R_3) can

now be completed and C_2 be connected to the loudspeaker switch. For the amplifier facility the position 4 of the switch is used.

The amplifier unit can now be inserted. As there is not much room, the soldering-in of the grid lead from the output valve to the potentiometer slider will prove a little bit of a game of skill and patience; but finally, I trust, the impossible will be achieved, and all that is left to do is to screw another small output transformer (T_2) to the bottom plate and to connect up its primary to flying leads from the output valve anode and from h.t.; while the 3Ω secondary is brought on one side to position 4 on the output side of the switch, on the other to the neutral reference line.

It was first contemplated to use T_1 as the amplifier output transformer as well, but since this would involve nightmarish switching arrangements, a renewed dig into the spares box was undertaken and a serviceable 40:1 transformer unearthed, which filled the bill, and, incidentally, the remaining bottom space inside the cabinet.

The Function

Very weak signals can now be monitored in the amplifier position 4. Due to its short grid base, the KT61 produces a clear tone with about 1/2V audio on its grid, which, in a 600Ω line, corresponds to a power output of just over 400µW from the gear under test. In this region no output meter gives reliable readings; but because of the clearness of the tone the amplifier allows a first alignment of, say, the i.f.s with a low-level input from the beginning.

With about 2V audio in the plug-line, the output meter is in its proper reading range, and the alignment can now be done by the meter. The strongest signal the amplifier will take without distortion will be about 6V audio in the 600Ω line, of which 4V are supplied to the KT61 by turning down the volume control fully; in this case the power output from the gear under test is about 60mW.

For stronger signals the amplifier can be switched off and the test loudspeaker used directly. In practice the "600Ω" position 3 will be generally acceptable. The monitoring tone comes quite clearly, even if a phone line is mismatched anywhere between 150Ω and 2,500Ω: as soon as the switch is brought into the "reading" position 2 there is no interference by the test loudspeaker to the impedance matching of the output meter and the meter registers correctly.

The same applies to the "3Ω" position 1 and the "7kΩ" position 5. It should be mentioned that both these facilities have been used only very occasionally over the last few years; they were included into the new set-up only to make the equipment as flexible as possible.

The Economic Side

The "bits and pieces" are enumerated in the accompanying list. Since most of them were either available on the surplus market, or, still cheaper, were found in the spares box, the cost of this very useful piece of equipment was very low indeed, most likely below £4.

Components List

- | | |
|---------------------------------------------------------------------------------------------------------------------------------------------------|----------------------------------------------------------------------------------|
| 1 RCA loudspeaker in black crackle steel cabinet (surplus) | C_1 1 capacitor paper 4µF 150V block type |
| T_1 1 output transformer (surplus ex-Army PCR, or equivalent) 48:14:1 Prim: 7,000Ω Imp.; 1st Secondary 600Ω Imp.; 2nd Secondary 3Ω Imp. | C_2 1 capacitor paper 0.01µF |
| T_2 1 output transformer 40:1 | R_1 1 resistor wirewound enamelled 1kΩ 5W |
| 1 mains transformer (surplus ex-Civ. Wart. Rec., or equivalent) Prim: 0-240V or as required; HT-Second: 250-0-250V 70mA; Heater-Second: 0-6.3V 2A | R_2 1 resistor carbon 6,200Ω 1W
1 resistor 100Ω 1/2W
1 resistor 22Ω 1/4W |
| 2 valve bases International Octal | R_3 1 resistor 1MΩ 1/2W |
| 1 valve KT61 (Marconi—GEC) | 1 lampholder plus bulb 6V |
| 1 valve 6X5 (any make) | 1 telephone indicator lens, colour as required |
| 1 capacitor electrolytic 16µF 380V upright | 1 paxolin tagstrip, 2 insulated tags |
| 1 capacitor electrolytic 32µF 380V upright | 1 volume control 1/2MΩ plus switch |
| 1 capacitor electrolytic 8µF 250V | 1 switch body 2-pole 5-way |
| | 2 plug-lines with 2-way telephone plugs |
| | 1 telephone jack |
| | 1 mains line with plug |
| | Piece of aluminium or paxolin, about 6in x 3 1/2in |

SMITH'S of Edgware Road

1910 GOLDEN JUBILEE YEAR 1960

BLANK CHASSIS

Precision made in our own works from commercial quality half-hard aluminium of 16 s.w.g. (1/16") thickness. These chassis go all over the world (and off it—in rockets!). Same day service for ANY SIZE, to nearest 1/16" and up to 17" of straightforward two, three or four-sided chassis. Orders for specials dealt with promptly if sent with clear instructions.

SOLDERED CORNERS. While these chassis, owing to their thickness, hardness and efficient folding, will carry components of considerable weight and normally require no corner strengthening, we can do this, if required, by a special soldering technique at 6d. extra for each corner.

FLANGES. 1/4", 3/8" or 1/2" flanges (inside or outside) 6d. extra for each bend.

PRICE GUIDE (normal chassis only)

Work out total area of material required, including waste, and refer to table below:

48 sq. in.	4/-	176 sq. in.	8/-	304 sq. in.	12/-
80 sq. in.	5/-	208 sq. in.	9/-	336 sq. in.	13/-
112 sq. in.	6/-	240 sq. in.	10/-	368 sq. in.	14/-
144 sq. in.	7/-	272 sq. in.	11/-	and pro rata	

Post 1/3 Post 1/6 Post 1/9
Discount for quantities. Trade enquiries invited. Spray finish arranged for quantities of 25 or over.

PANELS. The same material can be supplied for panels, screens, etc. Any size up to 3ft at 4/6 sq. ft. (sq. in. x 1/4"). Post, up to 72 sq. in. 9d., 108 sq. in. 1/3, 144 sq. in. 1/6, 432 sq. in. 1/9, 576 sq. in. 2/-.

287/289 EDGWARE ROAD LONDON W2
Telephone PAD 5891/7595

A FIRST COURSE IN WIRELESS

by "Decibel" 4th edition
Illustrated

The fourth edition of a non-technical introduction to radio. It has been generally revised and also a new chapter has been added covering transistors which now replace thermionic valves for many applications.

Price 12/6 net
FROM ALL BOOKSELLERS

PITMAN

Parker Street Kingsway London WC2

Terrific performance - Remarkable size - Staggering value—




We can only show a small selection from our vast stocks in this advert. Write now for full Bargain Lists, 3d.

THE TOURIST PORTABLE

light-weight Battery Radio. Size only 8" x 5 1/2" x 4", weight 3 1/2 lb. Uses B.114 Battery, 8/- extra
2 WAVEBAND—4 LOW CONSUMPTION VALVES "96" SERIES—FERRITE ROD AERIAL

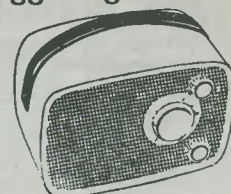Receiver Components Kit 57/6 P. & P. 1/6
5" Speaker and o/p Trans. 21/- P. & P. 1/6
Set of 4 Miniature Valves 36/- P. & P. 9d.
Cabinet, Dial and Knobs, etc. 22/6 P. & P. 2/-



Latest circuitry, A.V.C. and neg. feedback. Instruction Booklet 1/6 (Free with Kit)

MAINS UNIT KIT
45/- P. & P. 1/6

COMPLETE KIT ONLY £6.10.0
Post Free

RECORD PLAYER BARGAINS

All Brand New and Latest 4-speed Models

SINGLE PLAYERS. B.S.R. (TU-9) 90/-; Collaro Junior with latest Studio pick-up, £4.10.0; Garrard (4SP) £6.17.6; Garrard (TA Mk 2) £7.19.6. Carr and Ins. 3/6.

AUTO CHANGERS. B.S.R. (UA8) £6.19.6; Collaro (Conquest) £7.19.6; B.S.R. (UA12) with stereo and monaural cartridge, 10 gns. Garrard (RC121/4D/Mk 2) plug-in head and stereo adapted, with latest GC8 crystal, 10 gns. Carr. and ins. 4/6. Garrard GCS/10 stereo head £2 extra. Replacement Sapphire Stylus available all units.

RE-GUNNED TV TUBES

new budget prices

... and now 12 months guarantee!

All tubes rebuilt with new heater, cathode and gun assembly-reconditioned virtually as new:

12"- £6, 14"- £7, 17"- £8.10.0 etc
10/- part exchange allowance on old tube
Carr. and ins. 10/- Comprehensive Stocks—quick delivery

BAND III TV CONVERTER

180 Mc/s-205 Mc/s (Channels 6-13)

Suitable London, Birmingham, Northern, Scottish, Welsh and I.O.W. ITA transmissions.

Mk. 2 Model. Latest cascade circuit using ECC84 and EF80 valves giving improved sensitivity (18 dB) over standard circuits, built-in power supply a.c. 200-250V. Dimensions only 6 1/2" x 3", ht. 4". Simple and easy to fit—only external plug-in connections. Wired, aligned and tested ready for use. State channel required. Guaranteed. Bargain offer—good results or full refund. **ONLY £3.19.6** Carr. and pkg. 2/6

Recommended Addition—Band I/Band III changeover switch and B.B.C. aerial socket fitted and wired internal with converter, 8/- extra.

7 VALVE AM/FM RADIOGRAM CHASSIS

BARGAIN OFFER MANUFACTURERS' SURPLUS

Latest type ECC85 series valves with 3 watt EL84 Output Med., Long and V.H.F. Wavebands with Switched Gram. position. Magic Eye tuning. Illuminated glass dial 1 1/2" x 3 1/2". 4 controls. Chassis size 13 1/2" x 6 1/2" x 7 1/2" ht. A.C. 200/250V. Aligned and tested ready for use. Carr. **£13.10.0** and ins. 5/-

Complete with 4 knobs—walnut or ivory to choice P.M. speakers only required, 8" 20/-, 10" 25/-

TRANSISTORS—BVA 1st Grade—ex Mfrs.

Mazda XA102 (OC44), 16/6; XA101 (OC45—14/6; XC101 (OC72), 10/6; OC70, 9/6; OA70, 2/9.




Est. 1946

RADIO COMPONENT SPECIALISTS

70 Brigstock Road Thornton Heath, Surrey Telephone THO 2188
Terms: C.W.O. or C.O.D. Post and packing up to 1/6. 7d., 1/6 1/1 3/6 1/6 5/6 2/- 10/6 2/9

SUPER CHASSIS

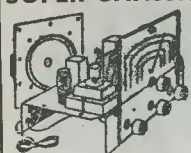

79/6 or 5/1

Initial payment and 19 weeks at 3/11. 5 valve superhet chassis, including 8" p.m. speaker and valves. Four control knobs (tone, volume, tuning and w/change). Four wavebands with position for gram, p.u. and ext. speaker. A.C. Ins. & Carr. 5/6.

HOME RADIO



79/6 or 5/1

Initial payment and 19 weeks at 3/11. A.C. or Universal Mains. 5 valve octal superhet 3-waveband receiver can be adapted to gram p.u. In attractive polished cabinet 9 1/2" x 18 1/2" x 11 1/2". Ins. & Carr. 7/6.

EXCEPTIONAL OFFER

RECORD PLAYER CABINET 19/6

A lightweight portable Record Player Cabinet, by a famous manufacturer. Size: 14 1/2" x 11 1/2" x 6". Colours: cream and rust. Complete with moulded deck board of attractive design. Takes B.S.R. TU9 single player; 2 control amplifier and a 5" round speaker. P. & P. 4/6.

CHASSIS 1/-. 6 or 8 valve. Brand new. Midget valve design for a.m. or f.m. 12 1/2" x 7 1/2" x 2 1/2". P. & P. 1/9.

Send for FREE catalogue

DUKE & CO

(Dept. K5) ILF 6001/3
621/3 ROMFORD RD.
MANOR PARK E12



For Safety's Sake use

AVO Prodclips

Patent No. 748811

... with Trigger-Action Spring-Loaded Clips

PRESS TRIGGER TO OPEN

RELEASE TO GRIP

Safety first every time with these patented spring-loaded AVO Prodclips.

Cleverly designed for use as insulated prods they are invaluable for reaching and holding test points which are difficult of access.

Suitable for use with AvoMeter, Multiminor and Avo Electronic Test Meter Leads Post Free 15/- per pair

AVO LTD AVOCET HOUSE

92-96 VAUXHALL BRIDGE RD., LONDON, SW1
Victoria 3404 (12 lines)

A Member of the Metal Industries Group of Companies
2PC


Multi - Purpose
VALVE FILAMENT TESTER

MODEL VT41

- ★ Pocket Size
- ★ Battery operated

GIVES INSTANT CHECK OF

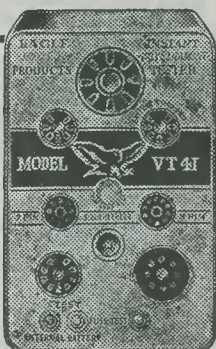All TV and Radio Valves and Fuses. All pilot lamps. Circuit Continuity. Built-in 7 and 9 pin Valve Straighteners. Built-in Battery Test.



Finished in black hammer case with gold front panel. Complete with internal batteries and ready for use. From your local dealer or in difficulty order direct:

30/-

With this revolutionary instrument you can test a wide range of radio parts. All components tested shown "good" or "faulty" on panel indicator.

EAGLE PRODUCTS (Dept. R.C.3.)

Eagle Works . Coptic Street . London . WC1

12" Speaker and 5" Tweeter with coupling condenser by leading maker, 75/- (£8.15.0 list price.)
Mains Transformers. Input 200/250V. Output tapped 3 to 30V 2A or 5, 11, 17V 5A. Each 24/6.
F.W. Metal Rectifiers. 12/6 volt 1A, 7/6; 3A, 13/-; 4A, 17/6; 6A, 27/6.
Mains Transformer and Rectifier, giving 12V 1A d.c. output, 19/6. Ideal for model supply.
Relays. We hold large stocks. Any contact combination and operating coil voltage supplied from 3/-.
Special Offer. 12V or 6V relays with 4-make contacts, 6/-; 2 for 11/6; 3 for 16/6; 4 for 21/-.
Key Switches from 3/-.
Toggle Switches d.p.d.t., 3/-.
Micro Switches, M. & B., 5/6.
Nickel Nife Batteries. 1.2V 2.5A. Size 3" x 2 3/4" x 1". Practically everlasting, 6/-; or 3 for 16/-; 4, 21/-.
Army Morse Keys, 3/- and 8/6.
Lightweight H.R. Phones, 17/6.
H.S. Twist Drills. Chrome Vanadium Steel. Set 7, 1 1/2", 1", 4/-; also Full Size in Plastic Wallet, 6/-.
5" Side Cutters, 5/-.
5" Plated Round Nose Tapered Pliers, 5/-.
Pocket Neon Testers with retractable Screwdriver, 5/-.
7" Flat Nosed Tapered Pliers, 8/6.
Very Powerful Geared Small 12V d.c. Motor. Instant stop. 3" x 1 3/4", 16/6.
New 12" Speakers. 3 ohm, 32/6.
Paxolin Panels, 12" x 6" x 1/8", 3/6.
Paxolin Tubing, 1 1/2" x 3/16" x 72", 17/6. Ideal for masts.
Studio "O" Cartridges, 21/-.

All items post paid, new and guaranteed
LISTS SENT ON REQUEST

Post orders only to

THE RADIO & ELECTRICAL MART


29 STATION APPROACH SUBBURY TOWN WEMBLEY MIDDX

CLYNE RADIO LTD.



Specialists in Equipment for Home Construction (Send stamp for complete list)

TWO-TRANSISTOR PERSONAL PORTABLE

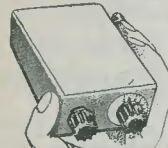


This is an amazing little receiver with built-in aerial, and small enough to be held in the palm of the hand. Medium wave reception at wonderful volume. Supplied with drilled chassis and colour coded components. Easily assembled with the aid of the easy-to-follow assembly instructions provided. Total cost of all necessary components, including transistors, deaf-aid earpiece, wiring wire and even solder. **ONLY 69/6** plus 1/6 P. & P. Parts price list and Easy Lay-out Plans 2/- post free.

New! New! The "Wavemaster" 7-Transistor Luxury Portable

400 milliwatts output

To build yourself! Medium and Long Waves—Push-Pull Superhet A.V.C. Perfect Car Radio reception. Size 10" x 6 3/4" x 4 1/2" at base tapering to 4" at top. Very attractive two-tone Vynide covered cabinet with cream and gold printed escutcheon plate, cream and gold knobs, handle and cabinet fittings. Weight complete with long-life 7 1/2 volt battery—4 1/2 lb. Mazda high-grade transistors throughout, high-flux 7" x 4" elliptical speaker, slow motion tuning, co-axial socket at rear for direct connection to car radio aerial. Improved reception by use of seven-section plated telescopic aerial disappearing into cabinet when closed, 34" above cabinet when fully extended. Construction simplified by bakelite chassis board with the following components already mounted: i.f. transformers (3), oscillator coil, trimmer bank, output transformer, interstage transformer, aerial brackets and earth bar. **SPECIAL INCLUSIVE PRICE** for all required components, full assembly instructions—nothing more to buy—is **£10.19.6** plus 3/6 P. & P. Alignment service available. Full assembly instructions and individually priced parts list, all of which are available separately 2/6 post free.

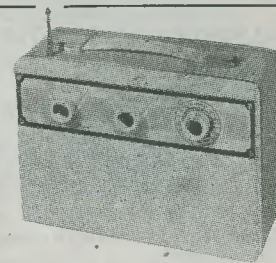

New City Branch now open at
99 CHEAPSIDE EC2

Midway between Bank, Mansion House and St. Paul's Stations, and no more than one min. from each. Mon. to Fri., 9 a.m.—6 p.m. Sat. 1 p.m.

Get these
FREE CIRCUITS & WIRING DIAGRAMS

T.R.F. Circuits Single Valve FM Tuner, 2 Valve FM
Battery Circuits Complete Set. Same on Printed
Portable Circuits Circuit, etc., etc.
S'het Circuits Postage 1/- (stamps)

OSMOR COILS are regularly used and recommended by designers writing in "Practical Wireless," "Wireless World" and "Radio Constructor." Why not follow the experts?

"Q COILS" All ranges • POTTED COILS • FM COILS

SPEAKER CROSS-OVER COILS

TAPE COILS • ROD AERIALS
SUB MINIATURE COILS

COILS and I.F.s for Transistor Circuits • MIDGET I.F. TRANS With ferrite cores

OSMOR

418 Brighton Road South Croydon

Telephone CRO 5148/9

REPANCO TRANSISTOR AMPLIFIER AND FEEDER UNIT CIRCUITS

Envelope of theoretical and practical layout diagrams for:

- 350/500 milliwatt Transistor Amplifier
- Simple TRF Band Pass Feeder Unit
- Medium wave TRF Feeder Unit with R.F. Stage
- Medium and Long wave Unit with RF Stage
- Medium and Long wave Superhet Feeder Unit
- Microphone Pre-amplifier

Send now 2/- (post free) for envelope

RADIO EXPERIMENTAL PRODUCTS LTD
33 MUCH PARK STREET COVENTRY



The Jupiter

Stereophonic Amplifier and Pre-Amplifier

This well-known Jason design, reproduced here in booklet form, consists of a main stereo amplifier and a stereo pre-amplifier design, complete with circuits and point-to-point diagrams, illustrations, and a chapter on setting up the equipment once construction is completed. An introductory chapter deals with such matters as The Difference in Level and Phase, Stereo on Tape and Disc, and Stereo on Radio, etc. 28pp, plus laminated plastic cover
Price 2s. 6d., postage 4d.

The Mercury

Switched FM Tuner


In this Jason design, the r.f. and frequency changer stages are supplied as a built and tested unit by the manufacturer, this being described with circuit diagram. The constructor completes, to the published design, the i.f., limiter, and discriminator stages, the result being the Mercury Switched FM Tuner. Drilling details, voltage tables, and much other useful information is also given. 20pp, plus stiff card cover
Price 2s., postage 2d.



DATA PUBLICATIONS LIMITED 57 Maida Vale London W9

Telegrams DATABUX LONDON

Telephone CUNningham 6141/2

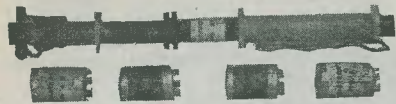

TELETRON MINIATURE TRANSISTOR 42/-

Superhet coil kit (as illustrated)

470 kc/s I.F. Transformers and Oscillator coil in screening cans $\frac{3}{4}$ " x $\frac{1}{2}$ " dia. Dual wave Ferrite rod aerial $5\frac{1}{2}$ " x $\frac{1}{8}$ " dia. Designed for the TRANSIDYNE miniature superhet receiver.

Descriptive folder with circuit and assembly instructions Price 9d.

FERRITE ROD AERIALS Wound on high permeability Ferroxcube rod. Medium wave, FRM 4" x $\frac{5}{16}$ ", 8/9. Dual wave FRD, 8" x $\frac{5}{16}$ ", 12/9.


Send 5d. in stamps for complete data and circuits. All types available from advertisers in this Magazine and local component stockists

THE TELETRON COMPANY LIMITED

112b Station Road . Chingford . London E4 Telephone SIL 0836

TELETRON TAPEJAK

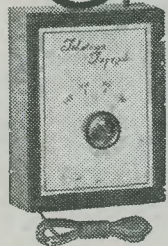The first Transistorised Radio Tuner, specially designed for use with Tape Recorders. Converts your Recorder to a high quality Radio receiver. Direct recording on Tape. 5" x 3 $\frac{1}{2}$ " x 1 $\frac{1}{4}$ "



- High Sensitivity
 - Twin tuned circuits
 - Pre-setting for MW Programmes
 - Fxd. tuned for 1500 M
 - Switched prog. selector. ● Self Powered
- Tested and ready for use Battery extra

£5-9-0



LAST MONTH OF SALE

(Pending reorganisation)
with lowest ever prices

- (a) Prices shown are only examples from large stocks.
(b) Intending purchasers are asked to send s.a.e. and list of requirements leaving space for prices.

Assorted Resistors, 6/- for 50; or selected to your choice, 2/- dozen. Hi Stabs, from 4d. each. Subminiature Electrolytic Capacitors, 2/6 each. Diodes (glass), 9d. each. Transistors, from 4/6. Valve Bases, from 6d. Lightweight Soldering Irons, 18/- . Paper and S/Mica Capacitors, from 6d. Electrolytics, from 1/- . Reaction and Tuning Capacitors, from 2/9. Subminiature Components, Coils, etc., etc.


(All subject to remaining unsold)

R. FAGELSTON

Mail Order

46 HARDWICKE RD LONDON N13

Fully Guaranteed Components

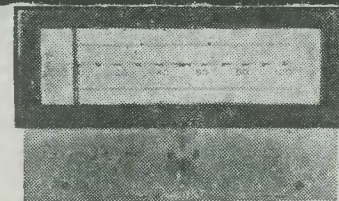

S. L. 16 DRIVE

A general purpose slide rule drive for FM/VHF units, short-wave converters, etc. Printed in two colours on aluminium, with a 0-100 scale, and provision is made for individual calibrations. Complete with bronze escutcheon and glass.

PRICE 13/9

It's reliable if it's made by Jacksons

JACKSON BROS

(LONDON) LTD.

Kingsway · Waddon · Surrey
Telephone CROydon 2754/5



★ VALVES NEW TESTED AND GUARANTEED

1R5	5/6	6X4	7/6	DH77	7/6	EL41	9/-
1S5	6/6	6X5GT	6/6	DK91	6/6	EL84	10/6
1T4	4/6	12AH8	10/6	DK96	8/-	EL91	7/6
3S4	6/9	12A7	7/6	DL92	6/9	EY51	9/6
3V4	7/6	12AU7	7/6	DL94	7/6	EZ40	6/6
5U4G	6/-	12AX7	9/-	DL96	8/-	EZ80	6/6
5Y3GT	7/6	12BH7	10/6	EB91	4/6	EZ81	7/-
5Z4G	9/-	12K7GT	8/6	EBF41	9/6	PL81	13/6
6AK6	6/6	12K8GT	13/6	EBF80	10/6	PL82	10/6
6AL5	4/6	12Q7GT	6/6	ECC81	7/6	PY81	8/-
6AM6	4/-	25A6G	10/6	ECC82	7/6	PY82	7/-
6AT6	7/6	25L6GT	9/-	ECC83	7/6	PCC84	9/6
6BA6	8/6	35Z4GT	8/6	ECC84	9/-	PCF80	9/-
6BE6	7/6	35L6GT	9/6	ECH82	11/-	PCF82	11/-
6BR7	10/6	53KU	11/6	ECH81	10/6	PCL82	10/6
6BW6	8/6	807	6/9	ECH42	8/6	U76	8/6
6J7GT	8/6	5763	10/6	ECL80	9/6	UBC41	10/-
6K7G	7/6	DAF91	6/6	EF41	8/6	UCH42	10/6
6Q7G	7/6	DAF96	8/-	EF80	8/-	UF41	10/-
6SL7GT	8/-	DF91	4/6	EF86	11/-	UL41	8/-
6SN7GT	8/6	DF96	8/6	EF91	4/-	UY41	8/-
6V6G	7/6	DH76	8/6	EF92	5/6	W76	8/6

Matched Pairs. EL84, 23/-; EL85, 25/-; 6V6G, 17/-; 6BW6, 18/-; KT33C, 19/6; 807 14/6 pair

1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DK92, DL92, DL94, any four, 24/-; DK96 series, 29/6 per set
P.P. Op. Transformers. MR 3-15 ohms for EL84, 6V6, 6BW6, etc., 18/6; Op. Pen. 50mA, 5/6; 30mA, 4/6
Volume Controls. All values, long spindle. L/S 2/9, s.p. 3/9, d.p. 4/3; ext. spkr. control 3/-
W.W. Pots. Pre-set 3/-; 3W long spindle 5/6, s.p. 6/6
P.M. Speakers. 3 ohm 5" 16/6, 6 $\frac{1}{2}$ " 17/6, 8" 21/-, 10" 25/-; 12" 30/-, Bakers 12" 15 ohm 15W, 90/-
Coaxial Cable. 75 ohm $\frac{1}{4}$ " stranded, 8d. yd; semi-air spaced 9d. yd; screen cable single and twin, 9d. yd
Coaxial Plugs 1/- each; Sockets 1/- each

P. and P. 9d. to £1; 1/6 to £2; over £2 post free. C.O.D. 2/6

R. COOPER G8BX 32 SOUTH END CROYDON SURREY CROYDON 9186

C.R.T. Isolation Transformers with nil, 25% and 50% boost, low capacity a.c. mains 200/250V for 2V 4V, 6.3V and 13V tubes. All 10/6 each. P. & P. 1/6

Valveholders. 4, 5, 7 pin English and U.S.A. B7G, 59A, 10, M0, B8G, 9d. each; B7G, B9A with screening can, 1/6; B12A, 1/3; Aladdin formers $\frac{1}{4}$ " with core, 8d. each

Scotch Boy Recording Tape. 1,200ft reel, 27/-
Jack Plugs. Miniature standard 3/-; Sockets 3/-
2-Gang Condensers. 0.0005 μ F, small size, 7/6

I.F. Transformers. 465 kc/s, small size, 7/6 pair
Capacitors. Small mica, 5%, 1pF to 100pF, 8d.; 120pF to 1,000pF, 9d.; 1,000V wkg. .01, .0015, .0025, .004, .005 μ F, 1/- each

Crystal Diodes. G.E.C., 1/6 each
Headphones. Lightweight, 4,000 ohm, 16/6 pair

Ceramic Capacitors. Close tol. 500V for V.H.F., 9d.
Paper Tubular. .001-1 500V, 9d.; .25, 1/-; .5, 1/6; .01 1,000V, 1/-

Paper Blocks. 4 μ F, 1,000 wkg., 3/6; 4 μ F 250V, 2/6
Rectifiers. Contact cooled, 250V 50mA, 7/6; 85mA, 9/6

Reaction Condensers. .0001, .0003, .0005 μ F, 4/6 each
Heater Trans. 200/240V, 6.3V, 1.5A, 7/6

Resistors. $\frac{1}{2}$ and $\frac{1}{4}$ W, insulated, 4d. and 6d.; 1W, 8d.; 6W W.W., 1/-; 10W, 2/-

Electrolytics. Wire ends. 25/25V, 1/6; 50/50V, 2/-; 12/50V, 9d.; 8/450V, 2/-; 16/450V, 2/9; 16/500V, 3/6; 32/450V, 4/-; 8+8/450V, 4/6; 8+16/450V, 4/6; can types: 16/450V, 3/6; 16+16/500V, 6/-; 32/500V, 6/6; 32/450V, 6/6; 20+20/450V, 4/6; 64+120/275V, 7/6

Wavechange Switches. Midget: 1p 12V, 2p 6W, 3p 4W, 4p 3W, 4p 2W, long spindles, 4/6

Toggle Switches. QMB, s.p.s.c.t., 2/-; s.p.d.c.t., 3/3; d.p.s.c.t., 3/6; d.p.d.c.t., 4/-; rotary s.p., 3/-

Chokes. 65mA 10H, 5/6; 80mA 15H, 8/6; 100mA 10H, 10/6; 150mA 10H 14/6

Solder, Multicore, 4d. yd; Sleeving 2mm., 3d. yd

Powerful! Personal! Portable!

★ Sturdy metal case

★ No holes to drill

★ Detachable rod aerial

★ All batteries self-contained

★ Can be built in 1 hour


★ Covers medium waves

★ Loud clear tone

★ Selective tuning

★ All parts are sold separately

FOR ONLY 35/-

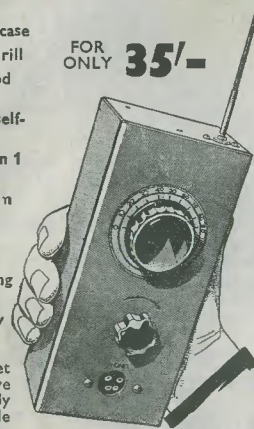

This delightful set is designed to give you a completely personal portable radio.

Bronze-finished case. Ideal for the beach, the bedroom, the office—in fact, anywhere.

Send 2/- for wiring diagram and component price list

R.C.S. PRODUCTS (RADIO) LTD
11 Oliver Road London E17 Mail Order only

Ask "ARTHURS" First

NOTE NEW ADDRESS AT
125 Tottenham Court Road
London WC1
Close to Warren Street Station

You will have the same service and obtain all your requirements in Radio Components, Electrical Goods, Accessories and Television as previously.

Test Instruments in stock include Avo, Advance, Cossor and Taylor. List on request

VALVE MANUALS AVAILABLE
Mullard 10/6 Brimar No. 8 6/-
Osram Part 1, 2nd Edition 7/6
Post and packing 9d. each extra

Arthurs first

Est. 1919

Proprietors ARTHUR GRAY LTD

Gray House
125 Tottenham Court Road
London WC1

Telephone EUSton 5802/3/4

CRYSTAL MICROPHONES

ACOS 39-1 Stick Microphone with Stand (List 5 gns.), 39/6. P.P. 1/6.
ACOS 40 Desk Microphone with built-in stand (List 50/-). 25/- P.P. 1/6.

CATHODE-RAY TUBES (IDEAL FOR 'SCOPES)

2AP1	2"	25/-
VCR139A	2 1/2"	35/-
3BP1	3"	30/-
3FP7	3"	12/6
3AP1	2 1/2"	30/-
3FP7	3"	12/6
3AP1	2 1/2"	30/-
Mullard DG7/5	2 1/2"	45/-
5FP7	5"	20/-
VCS17C	6"	30/-
VCR97	6"	40/-
Screens for VCR97		7/6

P.P. 2/- any type.
ALL GUARANTEED.
FREE LIST and Data on request..

TRANSMITTER/RECEIVER Army Type 17, Mark II


Complete with Valves, High Resistance Headphones, Handmike and Instruction Book and circuit. Frequency Range 44.0 to 61 Mc/s. Range approximately 3 to 8 miles. Power requirements: Standard 120V H.T. and 2V L.T. Ideal for Civil Defence and communications.

BRAND NEW 45/- P.P. 5/-.
44-61 Mc/s. Calibrated Wave-meter for same, 10/- extra. P.P. 2/-.

TELESCOPIC CHROME AERIAL

7-Sections, 3' 6" open; 6" closed. Ideal for Portable Receivers. Walkie-talkies, Radio Control, etc. 12/6. P.P. 1/-.

SHORT-WAVE RADIO

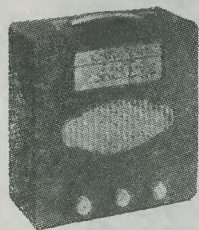

Chassis Size 10" x 10" x 4".

- ★ 3 Wavebands (10 to 550 metres)—650 kc/s to 2 Mc/s, 3 to 11 Mc/s, 11 to 30 Mc/s.
- ★ 5-valve Marconi Superhet.
- ★ A.C./D.C. 200 to 250V mains.
- ★ 7" x 4" Speaker; Gram. input.
- ★ Slow-motion Drive.

NOW £6.15.6 P.P. 3/6, incl. Speaker
OR COMPLETE IN PORTABLE CABINET, £7.12.6. P.P. 4/-.

- ★ ALTERNATE MODEL MEDIUM, LONG AND SHORT WAVEBANDS.

— THE WORLD IN YOUR HOME —

SEND 6d. STAMP FOR FREE LISTS BY RETURN OF POST

VALVES : CHOKES : METERS : TUBES : TRANSISTORS : MAINS TRANS. SWITCHES : CONTROLS : TEST UNITS : QUARTZ CRYSTALS : SOCKETS : VIBRATORS : CONDENSERS : AUDIO TRANS. : MINIATURE COMPONENTS : DO-IT-YOURSELF UNITS : SURPLUS EQUIPMENT, TX/RX, ETC., ETC.

HENRY'S RADIO LTD • 5 HARROW ROAD • LONDON W2

Opposite Edgware Road Tube Station. PADDINGTON 1008/9 OPEN MONDAY TO SAT. 9-6, THURS. 1 o'clock

Special Offer of MERCURY BATTERIES

1.3 volts, 500 mA/H
Size 3/8" diam. x 3/8" length
ONLY 1/3 ea. P.P. 3d. ea.
or 12/- dozen. P.P. 9d.

IDEAL FOR ALL TRANSISTOR WORK

Continental Transistors

Direct Equivalent OC44, 15/-
Direct Equivalent OC45, 12/6.
BRAND NEW GUARANTEED
LIMITED QUANTITY ONLY

"Practical Transistors Circuits"

14 Circuits for the Home Constructor, including date, prices and information. 1st Edition, 2/-, post free.

VALVE DEDUCTIONS

(WHEN PURCHASED IN SETS)

TP25, VP23, HL23/DD, PEN25 (or QP25)	25/-
1A7GT, 1N5GT, 1H5GT, 1C5GT (or 3Q5GT)	35/-
X66, KTW61, DH63, KT63, U50 6K8G, 6K7G, 6Q7G, 5Z4G, 6V6G	32/6
1R5, 1S5, 1T4, 1S4 (or 3S4 or 3V4)	25/-
DK96, DF96, DA96, DL96	35/-
6K8G, 6K7G, 6Q7G, 25L6GT, 25Z5 (or 25Z6G)	35/-
12K8GT, 12K7GT, 12Q7GT, 35Z4GT, 35L6GT (or 50LGT)	40/-
12SA7GT, 12SK7GT, 12SQ7GT, 35Z4GT, 35L6GT (or 50L6GT)	32/6

P.P. 1/- per set of valves

TRANSISTORS FREE COMPLETE LIST AND DATA ON REQUEST FULLY GUARANTEED

EDISWAN
XA131 250 Mc/s Ideal for F.M. 35/- ea.
XC121 400mW in Push-Pull 34/- pr.
XC101 325mW in Push-Pull 32/- pr.
XA104 6 Mc/s osc/mixer, R.F. 18/- ea.
XA103 4 Mc/s R.F., I.F. amp. 15/- ea.
XB104 Audio Output Driver 10/- ea.
XB104 Pairs, 250mW Output 20/- pr.
XA102 9 Mc/s osc/mixer, R.F. 26/- ea.
XA101 5 Mc/s, R.F., I.F., amp. 23/- ea.
XC131 Matched prs., 500mW 34/- pr.

SEMICONDUCTORS
SB078 20 Mc/s Short Wave, R.F. 10/- ea.
SB305 25 Mc/s Radio Control 15/- ea.
SB231 30 Mc/s Radio Control 22/6 ea.
SB231 35 Mc/s, H.F. osc/mixer 30/- ea.
Above are direct equivalents of SB344; SB100; SB101, etc.

MULLARD
OC72 Power Driver 16/- ea.
OC45 6 Mc/s, R.F., I.F. 18/6 ea.
CO71 Audio Driver 10/- ea.
OC72 400mW Push-Pull 30/- pr.
OC170 70 Mc/s Short Wave 35/- ea.
OC139 N.P.N. 4 Mc/s 66/- ea.
OC140 N.P.N. 6 Mc/s 72/- ea.
OC16 Power Output 54/- ea.
OC76 R.C. Switching 15/- ea.

SURPLUS
Red Spot Audio Driver 5/- ea.
White Spot R.F., I.F., amp. 7/6 ea.
Photo-Transistor (General) 10/- ea.

NEWMARKET
V15/10P Power Output, 2 watt 15/- ea.
V15/20P High Gain Power 39/- ea.
V15/10P Up to 10 watt pairs 30/- pr.
V15/20P Intermediate Power 25/- ea.
V30/30P High Gain Power 57/- ea.

Largest Range in the Country
Transistor Reductions when purchased in sets. Send for New List.

WE ARE ABLE TO SUPPLY MOST OF THE COMPONENTS USED ON CIRCUITS PUBLISHED IN THIS AND OTHER MAGAZINES AND BOOKLETS. WHERE THE EXACT ITEM IS NOT AVAILABLE WE CAN RECOMMEND A SUITABLE SUBSTITUTE.

TRADE INQUIRIES INVITED ON ALL ITEMS AND DO-IT-YOURSELF UNITS

CRYSTAL MICROPHONE INSERTS

Latest ACOS 19-4, 2" round Hi-Fi Insert, 14/-, P.P. 6d.

ALSO:
1 1/2" square or round, 7/6. P.P. 6d.
ACOS 6-9, 2" round, 12/6. P.P. 6d.
3/4" square, 3/6. P.P. 6d.

Type 38 Transmitter/Receiver

Complete with 5 valves. In new condition. These sets are sold without guarantee, but are serviceable.

7 to 9 Mc/s 22/6 P.P. 2/6
Headphones 7/6 pair. Junction Box 2/6. Throat Mike 4/6. Canvas Bag 4/-, Aerial Rod 2/6.

COMBINED PORTABLE/CAR RADIO

Medium and Long Wave Full Tuning

- ★ Plessey Printed Circuit
- ★ 6 "Top Grade" Ediswan Transistors
- ★ 5" High Fidelity Speaker
- ★ 400mW Push-Pull Output
- ★ Internal Ferrite Aerial
- ★ Slow Motion Tuning
- ★ Easy to follow Instructions
- ★ Printed Circuit marked out
- ★ Car Radio aerial socket and A.V.C.
- ★ ALL COMPONENTS GUARANTEED
- ★ Double Tuned IFs

ALL COMPONENTS AVAILABLE SEPARATELY

Just right for a day's outing "CONTINENTAL-6"

Total Cost of all Components

£11.10.0

including Cabinet, Battery, Transistors, Car Radio, AVC and all necessary items

A highly sensitive and selective portable fully tuneable on medium and long waves. Performs equally well as a car radio. Low running costs, good looks and ease of construction combine to produce a radio equal to any commercial receiver in the 20 gns. class.

(Size 9 1/2" x 7" x 3 1/2" Weight 4lb)

OUR CUSTOMERS SAY:

- "Results and quality first class."
- "Excellent results even before alignment."
- "Best I've seen in 14 years of radio work."
- "More than satisfied with result."
- "All parts easily identified—no difficulties."
- "My first venture into this field—delighted with performance."


Send for descriptive leaflet and prices

CALL FOR DEMONSTRATION

★ NO EXTERNAL AERIAL OR EARTH — NO REACTION CONTROLS ★

MAJOR-2

(Two-Transistor Pocket Radio)

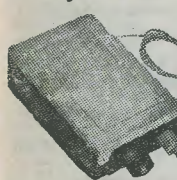

- ★ 4-stage reflex
- ★ Medium wave; tunable
- ★ Very sensitive
- ★ No aerial or earth
- ★ Complete layout
- ★ Over 6 months on one battery
- ★ 4 1/2" x 3" x 1 1/4"
- ★ Weight only 4 oz.
- ★ Personal phone incl.

TOTAL COST 69/6 P.P. 1/6

NEW BOOKLET FREE: All components sold separately.

RECEPTION GUARANTEED ANYWHERE!

MAJOR-3

(Three-Transistor Radio)

- ★ 5-stage Reflex Circuit
- ★ No Aerial or Earth
- ★ Min. Volume Control
- ★ 3 Ediswan Transistors
- ★ Medium Wave Tuning
- ★ Size 4 1/2" x 3" x 1 1/4"
- ★ Personal phone

(As described in R.C., Sept. '59)


Total Cost 87/6 P.P. 1/6 NEW BOOKLET FREE

FANTASTIC OUTPUT, TERRIFIC RECEPTION GUARANTEED ANYWHERE

RED-SPOT TRANSISTORS 5/- each

WHITE-SPOT 7/6 each

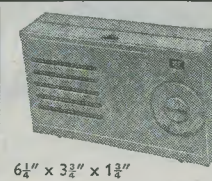NEW FREE LIST ON REQUEST
Fully Guaranteed



6 1/4" x 3 3/4" x 1 3/4"

3-TRANSISTOR HEARING AID

High-gain circuit with built-in crystal microphone and battery. Includes miniature earphone. Size 3" x 2" x 3/4". All components, 89/6. P.P. 1/-

2 WATT OUTPUT TRANSISTOR AMPLIFIER

For connection to any battery portable to give up to 2W output. Works from 12V battery. Ideal for car radio use. Size 4 1/2" x 3" x 2 1/2", uses power transistor. All components (less speaker) 52/6. P.P. 2/-
Ideal for use with Continental, etc.

TRANSISTOR TRANSMITTER

1.8 to 2 Mc/s coverage. 3 transistors unit size 4 1/2" x 3" x 1 1/4". Range of 3-section rod aerial up to 300 yards. Includes built-in microphone, battery and 3-section rod aerial. All components, 57/6. P.P. 1/6.

SPECIAL OFFER—LIMITED PERIOD

The Teletron "TRANSIDYNE" 6-transistor superhet

- ★ Medium and Long Waves Includes cabinet, battery, transistors, etc.
 - ★ 2 1/2" Rola Speaker
 - ★ All Ediswan transistors
 - ★ Marked printed circuit
 - ★ Illustrated instructions
- FREE LEAFLET, BOOKLET 1/- POST FREE
NOW ONLY £9.10.0
P.P. 2/-

RF, IF AND AUDIO SIGNAL TRACER

Ideal signal peaker or quick fault-finder for receivers, amplifiers, etc. Size 4 1/2" x 3" x 1 1/4". All components, with 'phones, 37/6. P.P. 1/6. Less 'phones, 32/6. P.P. 1/6

250mW PUSH-PULL OUTPUT AMPLIFIER

For use with any 2, 3 or 4 transistor, earpiece or head-phone radio to give room-filling volume on 3" speaker. All components including 2 Ediswan transistors, speaker, battery, special input socket to take earpiece plug, cabinet, etc., 59/6. P.P. 1/6.
Ideal for use with Major-2 or Major-3.

27 Mc/s RADIO CONTROL RECEIVER

3-Transistor regen. circuit. Size 2" x 1 1/2" x 1 1/4". Weight with batteries, 1 1/2 oz. Uses SB305 transistor. Multi-channel reed operated. All components (less reed), 50/-, P.P. 1/-.

ALL PARTS SOLD SEPARATELY: FULL AFTER SALES SERVICE: ALL RECEIVERS AND UNITS ARE EASY TO BUILD: TECHNICAL KNOWLEDGE NOT REQUIRED: TRADE ENQUIRIES INVITED ON ALL UNITS AND COMPONENTS. DEMONSTRATION MODELS ALWAYS ON VIEW— PLEASE CALL IN

ADDRESS

EDDY'S (NOTTM) LTD

172 Alfreton Road Nottingham

LOOK! at these New Valve Prices

ALL NEW OR SURPLUS
GUARANTEED AND TESTED
BY RETURN OF POST!

1A7GT	11/9	6O7GT	9/-	9001	3/11	EF86	10/-
1C5	7/11	6SA7M	5/9	9004	3/11	EF89	7/3
1H5GT	9/6	6SG7M	4/9	9006	3/11	EF91	3/6
1L4	3/6	6SH7M	4/3	AZ1	12/6	EF92	4/6
1N5	9/6	6SJ7M	5/11	CY31	9/6	EF95	6/6
1R5	6/-	6SK7GT	5/-	DAF96	7/9	EL41	8/3
1S5	5/11	6SN7GT	4/3	DF96	7/9	EL42	9/3
1T4	3/11	6C6G	4/11	DH77	6/3	EL84	6/6
3D6	4/11	6C6GT	6/11	DK92	7/11	EL85	10/3
3Q5GT	8/6	6X4	5/11	DK96	7/9	EL91	4/6
3Q4	7/-	6X5G	4/11	DL96	7/9	EY51	8/6
3S4	6/3	7C5	4/6	DM70	7/6	EY86	7/11
3V4	7/-	7C6	7/3	EABC80		EZ40	6/6
5U4G	5/-	7D3	19/11		6/11	EZ80	6/-
5Y3GT	5/11	7H7	19/6	EAF42	8/3	EZ81	6/11
6A7	10/11	7R7	10/3	EAL91	4/3	GT1C	6/11
6AG5	4/-	7S7	9/3	EB34	1/3	KT33C	6/11
6ALS	3/9	7Y4	7/6	EB41	6/11	OZ4	4/11
6AM6	3/6	10P14	9/3	EB91	3/6	P61	2/-
6AT6	6/11	11D5	17/3	EBC33	4/11	PCC84	7/3
6B8G	2/11	12AH7GT		EBC41	7/9	PCF80	7/3
6BA6	5/11		6/6	EBF89	3/3	PCL82	8/6
6BE6	5/11	12AH8	9/6	ECC35	6/6	PCL83	11/3
6BG6G	12/3	12AT6	7/6	ECC40	19/11	PCL84	7/11
6B16	5/6	12K7G	5/3	ECC81	5/3	PEN36C	8/6
6BW6	8/6	12K8GT11/3		ECC82	5/11	PL81	9/-
6C4	3/3	12SC7	11/7	ECC83	6/11	PL82	7/3
6C6	4/-	12SH7	4/11	ECC84	8/11	PL83	7/3
6C9	9/3	12SJ7	5/3	ECC85	7/11	PY32	10/11
6CH6	9/-	12SK7M	5/3	ECC93	5/3	PY80	6/11
6D2	3/6	12SQ7GT		ECF80	9/6	PY81	6/-
6F1	6/6		5/11	ECF82	9/6	PY82	6/6
6F6G	6/-	12Q7G	5/3	ECH35	6/6	U25	10/11
6F13	6/6	19AQ5	6/11	ECH42	8/3	UAF42	8/11
6H6	1/11	25A6G	6/11	ECH81	3/-	UB41	7/11
6J5G	2/6	25L6GT	6/11	ECL80	7/6	UBC41	7/6
6J5GT	3/6	25Z4G	7/6	ECL82	9/11	UBF80	8/3
6J5M	4/11	25Z5G	7/11	EF36	3/11	UCH42	7/6
6J6	3/11	35A5	10/3	EF37	8/3	UCL82	11/3
6J7G	5/-	35L6Gt	8/11	EF37A	7/11	UF41	8/-
6J7M	7/6	35W4	6/6	EF39	4/-	UF42	7/3
6K7G	1/11	35Z3	9/11	EF40	13/3	UF89	6/11
6K7M	5/6	35Z4G	5/3	EF41	8/3	UL41	7/3
6K8G	5/6	90AV	4/3	EF42	7/3	UL84	7/3
6L6G	7/3	807B	3/6	EF50	1/9	UY41	6/3
6L6M	9/6	954	1/6	EF55	5/11	UY1N	10/11
6Q7G	6/-	955	3/6	EF80	5/3	VP23	3/3
		956	2/6	EF85	6/3	VP41	5/11

BUILD YOUR OWN CAR RADIO!



7 Transistors Long and Medium Waves. Two watts output. RF stage and automatic gain control. (6 or 12 volts, please state.) Supplied with full instructions at **10½ gns.** Size: 7½" x 7¼" x 2½" Speaker 17/11 extra (7 x 4 ellipt.) if required. Postage and packing 5/- extra per kit.

Any parcel insured against damage in transit for only 6d. extra per order. All uninsured parcels at customers' risk. Postage and Packing 6d. per valve extra. Over £3. free. C.O.D. or C.W.O. only. C.O.D. charge 3s. extra. S.A.E. with all enquiries.

VIDIO 'REBUILDS' COST LESS - BECAUSE THEY ARE BETTER!

TOP QUALITY and NEW GUN UNITS

New Alumina

A Special Service

Right up to Vidio-high standards, all types of re-screened and aluminised tubes are available now—immediate free delivery

All Tubes Guaranteed for One Year

Get full details NOW from

VIDIO REPLACEMENTS LTD
HALES ST. DEPTFORD HIGH ST.
LONDON SE8 Telephone TID 4506

HI-FI NEWS

The Magazine for ...
... The Sound Enthusiast

● HI-FI NEWS carries regular Constructors' features, reviews of all high fidelity and good quality audio equipment, and articles for both beginners and experienced readers. It is well produced and illustrated. We think you will like it—but sample it at our expense. Send 6d. for a specimen copy. Annual subscriptions are 27/6, or 30/- with annual index.

Price 2/- Monthly

HI-FI NEWS
99 MORTIMER ST LONDON W1

SMALL ADVERTISEMENTS

Readers' small advertisements will be accepted at 3d. per word, including address, minimum charge 2/- . Trade advertisements will be accepted at 9d. per word, minimum charge 6/- . If a Box Number is required, an additional charge of 2/- will be made. Terms: Cash with order. All copy must be in hand by the 12th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the bona fides of advertisers.

PRIVATE

FOR SALE. Avometer 7, Avobridge, Modern Valves, 17in and 12in Television chassis complete. Transistors, components, amateur giving up. Offer for lot?—E. Cracknell, 6 Coronation Street, Cambridge.

WANTED. Accurate Signal Generator covering broadcast bands, in exchange for R107 Communications Receiver.—Albans, 17 Fern Road, Cropwell-Bishop, Notts.

WANTED. Circuit—Manual APG73, W2508 Wave-meter Sig. Gen. Price please.—Murnan, 13 Bridge Street, Risca, Mon.

FORMER RADIO ENTHUSIAST wishes to sell a variety of radio components: Resistors, 2s. doz.; Valves, 6s. average. Transformers, tuning condensers, meters, speakers, etc.—I. Paton, Ambassador College, Brickett Wood, St. Albans, Herts. Garston 4649. Except Saturdays and Tuesday evenings.

FOR SALE. "Hiwayman" Portable. Working but needs alignment. Offers?—14 Woodlands Gardens, E.17.

WANTED. Mullard Tape Amp. "Type C". Price, etc.—22 Pendine Street, Cheetham, Manchester 8.

FOR SALE. Truvox Mk. IV Deck. Precision Counter, £18 10s.; Truvox Type "C" Amplifier, £12 10s.; together £28 15s.—Goodman, 26 Killarney Road, Wandsworth, S.W.18.

FOR SALE. Five volumes *Wireless World*, 1948, 1955-1958. 6s. per set.—N. Dibley, 52 St. Andrews Road, Gosport, Hants.

AMATEUR disposing meters, condensers, ex-manufacturers, etc. All very cheap.—Phone Wembley 2281.

FOR SALE. Argonaut, £10; Jason F.M., £3; both including valves. Lane Mark VI Tape Deck, £10. Mains transformers; secondaries 350-0-350V, 80mA; 6.3V, 4A; 6.3V, 2A, £1. Output transformer, £1, Brand New (suitable Mullard 3W amplifier). Ceramic wafer switch: 3 wafers, each 4 bank, 3 way, 5s. Valves (used, tested) PCL81, ECC40, EF40, 6BA6, 1S5, UCH42, EL84, ECC83, EF86, UL41, EZ80, EF80, 5Y3, 5s. each. Garrard TPA12 Pick-up arm (less cartridge), in original box, £3. All the above being sold in order to improve Hi-Fi system.—Bland, 5 Cumberhill Road, Duffield, Derby. S.A.E. for further details.

FOR SALE. CRTs, VCR97, 3BP1, 5s. Non-synchronous 12 volt Vibrators, 2s. 6d. Carbon mike inserts, 2s. 6d. TV pre-amp Birmingham freq., 12s. 6d. Diplexers, 2s. 6d. Mains motor 200/250 volt fitted ¼in chuck, 30s. ½ h.p., BTH 200/220 fitted four step pulley, 45s. Cyldon turret tuner P38h, 50s. Telleng T/T 13 turret tuner, 35s. New, unused. Few ITV Converters, Aerialite, Apex, J.Vs. to clear, 45s. Post paid.—O.D.B., 25 Ramshead Approach, Leeds 14.

continued on page 799

AS FEATURED IN APRIL ISSUE "LITON" PHOTOELECTRIC PARKING LIGHT SWITCH

will switch your lights on at dusk—off at dawn, automatically, while you are at work, in bed, or away from home. Controlled by light. Transistorised. Negligible consumption (.005 amp.). Avoid accidents, fines. Save your battery. Many other uses.

Kit of parts 52/6
Built and tested 57/6

Send 6d stamp for pamphlet

Pat. applied for Money back guarantee

ST. JOHN'S RADIO

156 ST. JOHN'S HILL SW11 BATtersea 9838

NEW SURPLUS . . . BY RETURN

1L4	5/-	6SA7M	6/-	DC70	5/-	EZ80	6/6
1R5	6/6	6SG7M	6/6	DET24	12/6	EZ81	7/-
1S5	6/6	6SJ7M	6/6	DF73	5/-	GT1C	7/6
1T4	5/-	6SK7M	6/6	DL70	5/-	GZ32	10/6
2A3	8/6	6SL7GT	6/6	EAS0	1/6	HK24G	25/-
2X2	3/6	6SN7GT	4/6	EABC80/10/-		KT33C	7/6
3A4	4/6	6ST7	7/6	EAC91	4/6	KT66	11/6
3A5	9/-	6T6	6/6	EAF42	9/-	KT66	11/6
3Q4	6/6	6V6	7/6	EB34	2/-	OA2	8/-
3S4	8/6	6X4	5/6	EB91	4/-	PCC84	10/-
3V4	7/6	6X5G	6/6	EBC33	5/-	PCC85	9/6
5R4GY	8/6	7B7	7/-	EBC41	8/6	PCF80	7/6
5Y3GT	7/6	7C5	7/-	EBF80	9/6	PCF82	7/6
6AC7M	5/-	7C6	7/-	EBF89	9/6	PCL82	10/-
6AG5	3/6	7S7	9/-	EC80	11/6	PEN25	4/-
6AK5	5/-	7Y4	7/-	ECC82	6/6	PL81	12/6
6AL5	4/-	12A6M	5/6	ECC83	7/6	PL82	7/6
6AM6	4/-	12AT6	8/6	ECC84	9/-	PL83	8/6
6AQ5	8/6	12AT7	7/6	ECC85	8/6	PY80	6/6
6AT6	7/6	12AU7	6/6	ECF80	10/6	PY82	7/6
6AU6	7/6	12AX7	7/6	ECF82	10/6	PY83	8/-
6B8G	3/6	12AU6	9/-	ECH42	8/6	TT11	4/-
6BA6	7/6	12BE6	8/6	ECH81	10/-	UAF42	9/-
6BE6	7/6	12C8M	7/6	ECL80	10/6	UBC41	8/6
6BH6	6/6	12K7GT	6/6	ECL82	10/6	UBF89	9/6
6BJ6	6/6	12K8M	10/-	EF36	2/6	UCC85	9/6
6BR7	10/6	12Q7GT	6/6	EF39	4/6	UCH42	8/6
6C4	4/-	12SC7M	2/6	EF41	9/6	UCH81	9/6
6F32	2/6	12SJ7M	5/-	EF50	2/6	UF42	8/-
6F6M	5/6	12SK7M	5/-	EF50(S)	4/6	UF89	9/-
6J5GT	4/6	12SQ7M	8/6	EF80	6/6	UL41	9/-
6J5M	5/-	35Z5GT	8/6	EF85	1/6	UL84	9/-
6J6	3/6	35Z4GT	6/6	EF86	11/6	UY41	7/6
6J7G	6/6	42	7/6	EF89	8/6	UY85	8/6
6K7G	3/6	50L6GT	9/6	EF91	4/-	UABC80	
6K8G	6/-	80	6/6	EL32	4/-		10/6
6K8M	9/6	446A	10/6	EL41	9/6	VLS631	10/-
6H6M	2/6	830B	8/6	EL84	8/6	VP23	4/-
6L6G	8/-	959	5/-	EM80	9/6	VR150/30	
6L6M	10/-	1629	4/-	EY51	10/6		7/6
6Q7G	7/6	5763	10/6	EY86	9/6	VS70	3/-
6Q7GT	9/6	ARP12	4/-	EZ40	6/6	Z77	4/-

SPECIAL OFFERS!!

EF50, 6B8G, 12SC7, 1626, 1629, 6H6, 6AG5, 2X2, EL32, TT11, 6 for 10/- (P/P 1/6), 959, 6J6, DC70, DF73, DL70, EB91, EF91, 3 for 10/-.

Screened Valveholders. B9A moulded, 10/6 doz. For callers only, large selection of miscellaneous units, including CRT Indicators from 15/-.

10H 100mA Shrouded Chokes, 3 for 15/- (P/P 3/6). Post 9d. to £1, 1/6 to £2. S.A.E. enquiries

JOHN ANGLIN

385 CLEETHORPE ROAD GRIMSBY LINGS
Telephone 56315


Premier RADIO

23 TOTTENHAM COURT ROAD LONDON W1 Telephone MUSEum 345172



The "Petite" PORTABLE
MAY BE BUILT FOR **£7.70** plus 3/- P. & P.

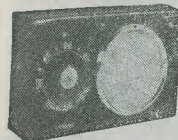Batteries extra.
HT 10/- (Type B126) or equivalent.
LT 1/6 (Type AD35) or equivalent.
★ Size only 8" x 8" x 4 1/2".
★ Instruction book 1/6.
Battery Eliminator, available in component form price 37/6 plus 2/- P. & P.




THE TRAVELLER'S FRIEND

Cosser Pocket Transistor Receiver may be built for only **£7.19.6** plus 2/- p. and p. This receiver uses the most up-to-date printed circuit method and with the aid of the easy to follow point-to-point instructions

assembly is simplicity itself. Four first-grade Edison Swan transistors are used, one XA102, two XA101, one XC101 and two diodes. The receiver covers 190/550 metres on medium wave operating on a P.P.4 9-volt battery. When constructed it is housed in an attractive beige leather case. Size 5 3/8" x 3 3/8" x 1 1/2", weight 17 oz. Ins. books available 2/6 Battery 2/6

THE BERIC


Battery Receiver for only **£4.19.6** plus 5/- p. & p., or £1 deposit and 5 monthly payments of 19/-. This receiver is ideally suitable for use in the home or where normal electricity supply is not available, remarkable reception on both medium and short wavebands, incorporating the following latest type miniature battery valves: DK92, DF96, DAF96, DL96, and operates on an external B103 battery or equivalent. It is housed in an attractive two-tone metal case. Size 11 1/2" x 7 1/2" x 5 1/2" Battery EXTRA, 18/6.

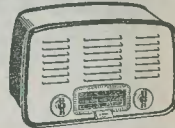

The "MID-FI"

A NEW DESIGN AMPLIFIER KIT

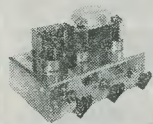4 1/2 WATT
MAY BE BUILT FOR **95/-** plus 3/- P. & P.



A new circuit for the home constructor requiring a good quality medium powered amplifier for reproduction of records or f.m. broadcasts. Technical specifications: separate bass and treble controls. Valve line-up EF86, EL84, EZ80. Voltage adjustment for a.c. mains from 200/250 volts, 3 or 15 ohms impedance. Negative feedback. Size 7" x 5" x 2", overall height 5". Silver hammered finished chassis.

Visit our new branch at 309 EDGWARE ROAD, LONDON W2 Telephone PADdington 6963

THE ARGONAUT

AM—FM MW—VHF
TUNER—RECEIVER

This high quality tuner-receiver has proved to be very popular with home constructors. Containing the circuit diagram, point-to-point wiring diagram, drilling details, and illustrations, together with full constructional details, the text has been revised and enlarged, and additional diagrams, including a map of present and projected coverage areas, have been included as a result of suggestions by readers

28 pp. plus stiff card cover
Price 2/- postage 4d.

Published by

DATA PUBLICATIONS LTD

57 MAIDA VALE · LONDON W9

Telephone CUNningham 6141 (2 lines)

Telegrams Databux London

A Versatile 2-Valve Audio Pre-Amplifier

One of our Radio Reprint series (RR7), this 8-page booklet contains complete constructional details of a Mullard designed audio pre-amplifier. Complete with circuit and main component layout, together with photographic illustrations. The latest Mullard modification data is included.

Price 1/- postage 2d.

continued from page 797

TRADE

FOR SALE. Six bound volumes *The Radio Constructor*. Volumes 6 to 11 with Indexes. As new, £4 17s. 6d. —14 Deanecroft Road, Eastcote, Pinner, Middx.

FOR SALE. Mullard "510" Main and Pre-amplifier. As new. £12 o.n.o.—Box No. F108.

LEARN RADIO AND ELECTRONICS the NEW Practical way. Very latest system of experimenting with and building radio apparatus—"as you learn". FREE Brochure from: Dept. RC10 Radiostructor, 40 Russell Street, Reading, Berks.

MORSE CODE TRAINING. Special courses for Beginners. Full details from (Dept. R.C.) Candler System Company, 52 Abingdon Road, London, W.8.

PANL, recognised for many years as the unique one-coat black crackle finish. Brush applied, no baking. Available by post in eighth pint cans at 3s. 9d. from G. A. Miller, 255 Nether Street, London, N.3.

"WORLD RADIO HANDBOOK." Copies available, 1960 Edition, 16s. 6d., inc. post and packing, from ISWL, 12 Gladwell Road, London, N.8.

1,000 INTERESTING ITEMS. List 3d.—Rogers, 31/33 Nelson Street, Southport, Lancs.

TECHNICAL WRITING IN ELECTRONICS. Radio and TV Instruction Books, Service Manuals, Brochures, Technical Drawings, etc.—F. C. Judd, A.Inst.E., Rotech, 152 Maybank Road, London, E.18. Telephone BUCKhurst 9315.

HIGH CLASS DUPLICATING. Electronic Stencil Illustrations, circuits, etc. Sheets or booklets. —Rotech, 152 Maybank Road, London, E.18. Telephone BUCKhurst 9315.

INCORPORATED Practical Radio Engineers home study courses of radio and TV engineering are recognised by the trade as outstanding and authoritative. Moderate fees to a limited number of students only. Syllabus of Instructional Text is free. *The Practical Radio Engineer*, journal, sample copy 2s. 6,000 Alignment Peaks for Superhets, 5s. 9d. Membership and Entry Conditions booklet, 1s., all post free from the Secretary, I.P.R.E., 20 Fairfield Road, London, N.8.

THE INTERNATIONAL HAM HOP CLUB is a non-profit-making organisation open to RADIO AMATEURS and SHORT WAVE LISTENERS. OBJECT: To improve international relationships through an organised system of hospitality. MEMBERS offer overnight hospitality to visiting members, entrance fee 2s. 6d. ASSOCIATE MEMBERS invite radio amateurs to visit their stations. S.A.E. for FREE Associate membership. FAMILY EXCHANGE holidays arranged, also FRIENDSHIP LINKS between radio clubs. H.H.C.s official journal, *Ham Hop News*, 5s. per annum. Hon. Gen. Secretary: G. A. Partridge, G3CED, 17 Ethel Road, Broadstairs, Kent.

CATALOGUE No. 14. Government surplus and model radio control, over 500 illustrated items, 2s. (refunded on purchase), p.p. 6d.—Arthur. Sallis Radio Control Ltd., 93 (E) North Road, Brighton.

JOIN THE INTERNATIONAL S.W. LEAGUE. Free Services to members including Q.S.L. Bureau. Amateur and Broadcast Translation. Technical and Identification Dept.—both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, "MONITOR" containing articles of general interest to Broadcast and Amateur SWLS, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes. QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazine, etc., 21s. per annum. —Secretary. ISWL 12 Gladwell Road, London, N.8.

The Radio Constructor Bound Volumes

Attractively bound in blue cloth
with gold-block spine

Vol. 12, Aug. 58 to July 59 £1.5.0, p. 1/9

Where all issues of a volume are returned
for exchange 12s. 6d., p. 1/9

"Easibinders" for temporary or permanent binding 12s. 6d., p. 9d.

Please note: Indexes are available for Volume 12, August 58 to July 59 inc., price 6d., postage 2d. A limited number of indexes are also available for volumes 4, 6, 8 and 11 at the same price.

DATA PUBLICATIONS LTD
57 MAIDA VALE · LONDON · W9

L. F. HANNEY

77 LOWER BRISTOL ROAD BATH

TRANSISTORS

Red Spot, 5/-; White Spot, 6/6; Brimar TS1, 6/- (Audio). Ediswan XA104, 18/-; XA103, 15/-; XB102, 10/-; XB104, 10/-.

JUST ARRIVED:

The new Garrard Tape Deck, £15.7.3
Small quantities only. All Garrard Gram. units, heads and styli ex-stock.

Shopping List available for Mullard Amplifiers described in "Circuits for Audio Amplifiers."

S.A.E. for LIST please

TV Chassis for Spares 9/6

56 Resistances including 7 variable controls. 45 condensers, including electrolytics, coils, 7 i.f. and r.f. transformers. 13 valve holders (8-B8A, 2-B7G, and 3 octal) 4 transformers—Mains—Output—Line—Frame. Chokes 250mA. Metal rectifiers—300V at 250mA. Fuse panel, scanning coils for focus magnets, plugs, sockets, switches, chassis screws, tagstrips, etc. I.F. strip can be separated. Power pack can be used without dismantling. These chassis have been used, but were working when stored. 6-page circuit and instructions. Carr. 7/6.

P. P. COMPONENTS LIMITED

219 Ilford Lane Ilford Essex Mail Order Only

TRANSFORMERS

Suppliers to B.B.C., I.T.A. and leading radio manufacturers, single or long runs, prompt delivery, home and export.

rewinds to all makes

H. W. FORREST (TRANSFORMERS) LTD.,
Shirley, Solihull, Warwickshire
Telephone 511rley 2483

NYLON . P.T.F.E.

ROD BAR SHEET TUBE STRIP WIRE
No quantity too small List on application

BRASS COPPER BRONZE
ALUMINIUM LIGHT ALLOYS
H. ROLLET & CO LTD

6 Chesham Place SW1 BELGRAVIA 4300
Also at Liverpool Birmingham
Manchester Leeds

Teleprinters, Perforators, Reperforators, Tape Readers, Terminals and V.F. Telegraph multi-channel units, Test Meters and Testing Equipment, Telephone Carriers and Repeaters, Signalling Rectifiers and Relays, Transformers, Transmits and Receive Filters, Repeating and Retardation Coils, Uniselectors, Racks, Relay Bases, Remote Control Transmitters: British, American, Italian and German Equipment.

BATEY & CO.

Gaiety Works Akeman Street Tring Herts.
Telephone Tring 2183 and 2310

SERVICE SHEETS. 14 Days Free Hire

Line Output Transformer Specialists. All Makes/Models from 65/- Volume Controls 3/-, Switched 4/9. Resistors 1/2 watt, 1/2 watt 6d each. Hystab 10% 1/2 watt 10d. Wirewound 10% 5 watt 1/3, 10 watt 1/6. Sub-Miniature Electrolytics 1µF, 2µF, 4µF, 5µF, 25µF, 50µF, 100µF, 15V. 3/- each. Coax. Cable 6d. per yd. Crystal Diodes 2/-, GEX34 4/- Hax. Coils 3/- each. R.E.P. DRR2 4/-. All Repanco and Teletron components in stock. All transistors stocked.

Service sheet free hire on all orders over 25/- Deposit 5/- extra returnable. P. & P. 1/-, over £2 free. S.A.E. all enquiries.

WYNDSOR TELEVISION SERVICE
ST. ALBANS ROAD BARNET HERTS.
Telephone BAR 1769

QUALITY COMPONENTS FOR CONSTRUCTORS

capacitors, resistors, coils, valves, diodes, controls, chassis, transformers, speakers, pick-ups, cart-ridges, styli and all types of components in stock.

CONSTRUCTIONAL PUBLICATIONS

Mullard Circuits for Audio Amplifiers ...	8/6
Mullard Tape Pre-amp "C" ...	2/6
Quality Amplifiers, 7 designs ...	4/6
Jason F.M. Variable Tuners ...	2/6
Jason F.M. and T.V. Sound Tuner ...	3/6

Price lists available on request

J. T. FILMER 82 DARTFORD ROAD
DARTFORD KENT
Telephone Dartford 24057

H.A.C. THE ORIGINAL SUPPLIERS OF SHORT-WAVE KITS

One valve Super Sensitive All-dry Short-wave Receiver Model "K". Complete kit including valve and chassis 77/- (Other S.W. kits from 25/-) Before ordering call and inspect a demonstration receiver, or send stamped envelope for full specification, catalogue and order form.

H.A.C. SHORT-WAVE PRODUCTS (DEPT. R)
11 OLD BOND STREET LONDON W1

"GLOBE-KING"

WORLD-FAMOUS KITS AND RECEIVERS

for the Radio Amateur and S.W. Listener. Catalogue Free, enclose stamp for postage. Kits from 79/6 obtainable at your dealers or direct from sole manufacturers

JOHNSONS (Radio)

ST. MARTINS GATE — WORCESTER

POCKET TRANSISTOR RADIO. All parts, plans and instructions supplied for 19/6—CRYSTAL SET 8/6

All parts, plans, instructions, etc.
Send stamp for details of above sets and lists of Valves, Books, Service Sheets
TRANSISTORS

Red Spot 4/- White Spot 4/6. Postage 3d.
HAMILTON RADIO (R)
237 Sedlescombe Rd. N. Hastings Sussex

RTTY

Brand New Combination Heads for Morse Teleprinters only £4 each. Morse and 5-unit Perforators and Reperforators—Ink Recorders, etc.

R. GILFILLAN & CO. LTD

29 South Street Worthing Telephone 30188

RADIO AMATEURS . . .

get your Licence in

Half The Usual Time!

You must be a good Morse operator! A "slap-dash" 12 w.p.m. neither satisfies the authorities yourself, nor your operator friends. Morse operating is an exacting art unless your training is made simple and is based on sound fundamentals. For this reason, the Candler System was invented to take the "grind" out of Code tuition, turning a tricky subject into a pleasurable pursuit.

★ Send 3d. stamp for the "Book of Facts"

CANDLER SYSTEM CO

(Dept. 55 RC) 52b Abingdon Rd London W8
Candler System Company Denver Colorado U.S.A.

CATFORD Telekit Supply

of 104 HIGH STREET BECKENHAM

Have now opened another branch at
30 CATFORD HILL SE6

RADIO, TV, TRANSISTOR COMPONENTS
(Everything for the Constructor)
Telephone FOR 9658

SCOTTISH INSURANCE CORPORATION LTD



62-63 Cheapside London EC2

TELEVISION SETS, RECEIVERS AND TRANSMITTERS

Television Sets, Receivers and Short Wave Transmitters are expensive to acquire and you no doubt highly prize your installation. Apart from the value of your Set, you might be held responsible should injury be caused by a fault in the Set, or injury or damage by your Aerial collapsing.

A "Scottish" special policy for Television Sets, Receivers and Short Wave Transmitters provides the following cover:

- Loss or damage to installation (including in the case of Television Sets the Cathode Ray Tube) by Fire, Explosion, Lightning, Theft or Accidental External Means at any private dwelling-house.
- (i) Legal Liability for bodily injury to Third Parties or damage to their property arising out of the breakage or collapse of the Aerial Fittings or Mast, or through any defect in the Set. Indemnity £10,000 any one accident.
- (ii) Damage to your property or that of your landlord arising out of the breakage or collapse of the Aerial Fittings or Mast, but not exceeding £500.

The cost of Cover (a) is 5/- a year for Sets worth £50 or less, and for Sets valued at more than £50 the cost is in proportion. Cover (b) and (ii) costs only 2/6 a year if taken with Cover (a), or 5/- if taken alone.

Why not BE PRUDENT AND INSURE your installation—it is well worth while AT THE VERY LOW COST INVOLVED. If you will complete and return this form to the Corporation's Office at the above address, a proposal will be submitted for completion.

NAME (Block Letters).....

If Lady, state Mrs. or Miss

ADDRESS (Block Letters).....

/JB

THE SELRAY BOOK CO

specialists in RADIO AND ALLIED PUBLICATIONS

High Fidelity Loudspeaker Enclosures. Babani. 5s. Postage 3d.
Practical Stereo Handbook. Sinclair. 3s. 6d. Postage 3d.
Transistor Superhet Receivers. 96 pages. Sinclair. 7s. 6d. Postage 6d.
Portable Transistor Radio and Radiogram. Gregory. 3s. 6d. Postage 3d.
Crystal Set Construction. Babani. 1s. Postage 3d.
40 Circuits Using Germanium Diodes. 3s. Postage 3d.
Radio Circuits Manual. Feeley. 2s. 6d. Postage 3d.
Boys' Book of Crystal Sets and Simple Circuits. 2s. 6d. Postage 3d.
Practical Transistor Receivers. Sinclair. 5s. Postage 3d.

Transistor Circuits Manual. Gregory. 2s. 6d. Postage 3d.
Beginners' Guide to Radio. Camm. 7s. 6d. Postage 6d.
Servicing Transistor Receivers. Pettit. 6s. Postage 4d.
Guide to Broadcasting Stations. New Edition. 3s. 6d. Postage 3d.
Grundig Book. New Edition. 12s. 6d. Postage 9d.
Mullard. Circuits for Audio Amplifiers. 8s. 6d. Postage 9d.
Radio Valve Data. Sixth Edition. Wireless World. 5s. Postage 6d.
Jason. Mercury 2. Switched Tuner for FM & TV Sound. 3s. 6d. Postage 3d.
Jason. JTV/2 Tuner for FM & TV Sound. 3s. 6d. Postage 3d.

When ordering kindly add postage up to a total of 1s. only

Dpt. RC • 60 HAYES HILL • HAYES • BROMLEY • KENT • Telephone HURstway 1818