


Vol 20 No 1

**AUGUST 1966**  
**2/6**

A DATA PUBLICATION

# THE Radio Constructor

RADIO • TELEVISION  
ELECTRONICS • AUDIO

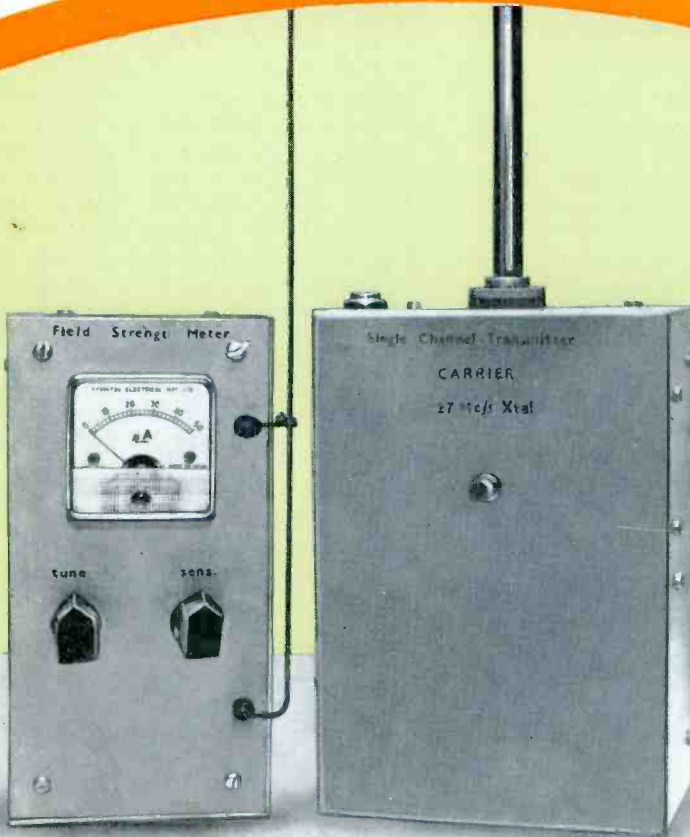

**Transistorised  
Radio Control  
Transmitter**

2.25kV Power  
Supply



Tape Recorder  
Tuner



CR100  
Modifications



Circular  
Timebase



# Eddystone RECEIVER

OF MAJOR INTEREST TO ALL RADIO ENTHUSIASTS

## EC 10 transistorized communications receiver

A most efficient transistorized communications receiver of light weight, compact dimensions, and capable of a really good performance. Five ranges give continuous coverage from 550 kc/s to 30 Mc/s (545 to 10 metres), and included are the medium-wave broadcast band, the marine (coastal) band from 1500 to 3000 kc/s, and all the short-wave broadcast bands. Also available are the six major amateur bands and many services in between.

The EC10 receiver accepts normal AM telephony and CW telegraphy, a special filter being provided to increase selectivity (and also reduce noise) in the CW mode, as is often desirable. Single sideband signals can



be successfully resolved by appropriate setting of the BFO for carrier reinsertion. A total of 13 transistors and diodes is used, leading to high sensitivity and consistent results on all ranges. The main scales occupy a length of nine inches and are clearly calibrated direct in frequency. The standard Eddystone precision slow-motion drive controls the tuning, which is exceptionally smooth and light to handle. An auxiliary logging scale permits dial settings of chosen stations to be recorded.

An internal speaker gives good aural quality and a comparatively high audio output is available—one can easily believe the set is mains operated. For personal listening, a telephone headset can be plugged into the socket on the front panel, the speaker then being out of action.

Alternative aerial sockets are provided, for dipole, long wire, or short rod or wire. Power is derived from six cells housed in a separate detachable compartment. Current consumption is related to audio output and, for long life, HP2-type heavy-duty cells are recommended.

The receiver is housed in a metal cabinet, and, with robust construction throughout, it will stand up to hard usage over a long period with a high degree of reliability. The finish is an attractive two-tone grey. The dimensions are width 12½", height 6½", depth 8"; weight with batteries is 14 lb.

## Eddystone Radio Limited

Eddystone Works, Alvechurch Road, Birmingham 31


Telephone: Priory 2231 · Cables: Eddystone Birmingham · Telex: 33708

LTD/EDS

# SINCLAIR Z.12
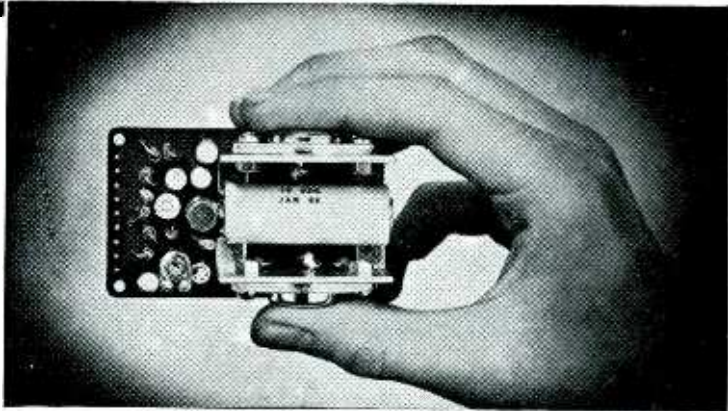
## INTEGRATED 12 WATT AMPLIFIER AND PRE-AMP

For size alone, the Z.12 marks an important advance in quality design, for its amazing compactness opens up exciting new vistas in amplifier housing and application. Combined with this are fantastic power and superb quality which can provide an effortless output of 12 watts R.M.S. continuous sine wave from the unique eight transistor circuit used. Basically intended as the heart of any good mono or stereo hi-fi system, the size and efficiency of this Sinclair unit make it equally useful for a car radio (with the Micro-6 for example), a high quality radio with the Micro FM, in a guitar, P.A. or intercom system, etc. Other applications are certain to suggest themselves to constructors. The manual included with the Z.12 details mono and stereo tone and volume control circuits by which inputs can be matched (and switched in) to the pre-amp. The size, performance and price of the Z.12 all favour the constructor seeking the finest in transistorised audio reproduction—it is in fact today's finest buy in top grade high fidelity.



**12 WATTS R.M.S. OUTPUT** CONTINUOUS SINE WAVE (24 W. PEAK)  
**15 WATTS R.M.S. MUSIC POWER (30 WATTS PEAK)**

- ★ Ultra-linear class B output and generous neg. feedback.
- ★ Response—15 to 50,000 c/s  $\pm 1$ dB.
- ★ Output suitable for 3, 7.5 and

- 15 ohm loads. Two 3 ohm speakers may be used in parallel.
- ★ Input—2mV into 2K ohms.
- ★ Signal to noise ratio—better than 60dB.

Built, tested and guaranteed.

# 89/6

## SINCLAIR MICRO FM COMBINED FM TUNER RECEIVER

Less than 3" x 1 1/2" x 1/2" and professional in every way, 7 transistor FM using pulse counting discriminator for superb audio quality. Low I.F. makes alignment unnecessary. Tunes 88-108 Mc/s. The telescopic aerial suffices for good reception in all but poorest areas. Signal to noise ratio—30dB at 30 microvolts. Takes standard 9 v. battery. One outlet feeds to amplifier or recorder, the other allows set to be used as a pocket portable. Brushed and polished aluminium front, spun aluminium dial. A fascinating set to build.



Complete kit inc. aerial, case, earpiece and instructions.

# £5.19.6

## SINCLAIR MICRO-6

The world's smallest radio. Unequaled for power, selectivity and quality. Six stage M.W. receiver. 2 R.F. amplification, double diode detector, 3 stage A.F. amplifier. A.G.C., etc. The Micro-6 is completely self-contained in white, gold and black case, 1 1/2" x 1 3/16" x 1/2". Plays anywhere. Easy to build. Complete kit of parts with earpiece and instructions.



# 59/6

## FULL SERVICE FACILITIES AVAILABLE TO SINCLAIR CUSTOMERS GUARANTEE

If you are not completely satisfied when you receive your purchase from us, your money will be refunded at once in full and without question.

BUILT, TESTED AND GUARANTEED **£9.19.6**

## A HI-FI STEREO ASSEMBLY FOR £22.18.0

All you require is one Stereo 25 Unit (£9.19.6) two Z.12's (£8.19.0) and one PZ.3 (£3.19.6). As an optional extra, you could include the Micro FM (£5.19.6).

Transistorised mains power unit specially designed for Z.12. Will power two Z.12's and Stereo 25 with ease.

# 79/6

**SINCLAIR RADIONICS LTD., 22 NEWMARKET ROAD, CAMBRIDGE**

Please send \_\_\_\_\_

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

for which I enclose cash/cheque/money order value £.....s.....d.

RC8



**SINCLAIR RADIONICS LIMITED**  
 22 NEWMARKET ROAD, CAMBRIDGE  
 Telephone: OCA3-52731



# HI-FI AMPLIFIERS ~~~~~ TUNERS ~~~~~ RECORD PLAYERS



3+3W  
STEREO  
AMP.  
S-33H



10W  
POWER  
AMP.  
MA-12



GARRARD  
PLAYER  
AT-60



20+20  
STEREO  
AMP.  
AA-22U

**10W POWER AMPLIFIER. Model MA-12.** 10W output, wide freq. range, low distortion. For use with control unit. Kit £12.18.0 Assembled £16.18.0

**3 + 3W STEREO AMPLIFIER. Model S-33.** An easy-to-build, low cost unit. 2 inputs per channel. Kit £13.7.6 Assembled £18.18.0

**DE LUXE STEREO AMPLIFIER. Model S-33H.** De luxe version of the S-33 with two-tone grey perspex panel, and higher sensitivity necessary to accept the Decca Deram pick-up. Kit £15.17.6 Assembled £21.7.6

**HI-FI STEREO AMPLIFIER. Model S-99.** 9 + 9W output. Ganged controls. Stereo/Mono gram., radio and tape inputs. Push-button selection. Printed circuit construction. Kit £28.9.6 Assembled £38.9.6

**TRANSISTOR PA/GUITAR AMPLIFIER, PA-2.** 20W amplifier. Four inputs. Variable tremolo. Kit £44.19.0 Assembled £59.10.0

**50W VALVE PA/GUITAR AMP., PA-1.** Kit £54.15.0 Assembled £74.0.0

**TRANSISTOR MIXER. Model TM-1.** A must for the tape enthusiast. Four channels. Battery operated. Similar styling to Model AA-22U Amplifier. With cabinet. Kit £11.16.6 Assembled £16.17.6

**20+20W TRANSISTOR STEREO AMPLIFIER. Model AA-22U.** Outstanding performance and appearance. Kit £39.10.0 (less cabinet). Assembled £57.10.0 Attractive walnut veneered cabinet £2.5.0 extra.

**GARRARD AUTO/RECORD PLAYER. Model AT-60.** less cartridge £13.1.7 With Decca Deram pick-up £17.16.1 incl. P.T. Many other Garrard models available, ask for Lists.

**HI-FI MONO AMPLIFIER. Model MA-5.** A general purpose 5W Amplifier, with inputs for Gram., Radio. Attractive modern styling. Kit £11.9.6 Assembled £15.15.0



## The World Leader in Quality Kitsets

Easy-to-follow instruction manuals show you how to build the models

### INSTRUMENTS

**3" LOW-PRICED SERVICE OSCILLOSCOPE. Model OS-2.** Compact size 5" x 7 1/4" x 12" deep. Wt. only 9 1/2 lb. "Y" bandwidth 2 c/s-3 Mc/s ± 3dB. Sensitivity 100mV/cm. T/B 20 c/s-200 kc/s in four ranges, fitted mu-metal CRT Shield. Modern functional styling. Kit £23.18.0 Assembled £31.18.0

**5" GEN-PURPOSE OSCILLOSCOPE. Model 10-12U.** An outstanding model with professional specification and styling. "Y" bandwidth 3 c/s-4.5 Mc/s ± 3dB. T/B 10 c/s-500 kc/s. Kit £35.17.6 Assembled £45.15.0

**DE LUXE LARGE-SCALE VALVE VOLTMETER. Model IM-13U.** Circuit and specification based on the well-known model V-7A but with many worth-while refinements. 6" Ernest Turner meter. Unique gimbal bracket allows operation of instrument in many positions. Modern styling. Kit £18.18.0 Assembled £26.18.0

**AUDIO SIGNAL GENERATOR. Model AG-9U.** 10 c/s to 100 kc/s, switch selected. Distortion less than 0.1%. 10V sine wave output metered in volts and dB's. Kit £23.15.0 Assembled £31.15.0

**VALVE VOLTMETER. Model V-7A.** 7 voltage ranges d.c. volts to 1,500. A.c. to 1,500 r.m.s. and 4,000 peak to peak. Resistance 0.1Ω to 1,000MΩ with internal battery. D.c. input resistance 11MΩ. dB measurement, has centre-zero scale. Complete with test prods, leads and standardising battery. Kit £13.18.6 Assembled £19.18.6

**MULTIMETER. Model MM-1U.** Ranges 0-1.5V to 1,500V a.c. and d.c.; 150μA to 15A d.c.; 0.2Ω to 20MΩ. 4 1/2" 50μA meter. Kit £12.18.0 Assembled £18.11.6

**R.F. SIGNAL GENERATOR. Model RF-1U.** Up to 100 Mc/s fundamental and 200 Mc/s on harmonics. Up to 100mV output. Kit £13.18.0 Assembled £20.8.0

**SINE/SQUARE GENERATOR. Model IG-82U.** Freq. range 20 c/s-1 Mc/s in 5 bands less than 0.5% sine wave dist. less than 0.15μ sec. sq. wave rise time. Kit £25.15.0 Assembled £37.15.0

**TRANSISTOR POWER SUPPLY. Model IP-20U.** Up to 50V, 1.5A output. Ideal for Laboratory use. Compact size. Kit £35.8.0 Assembled £47.8.0



OS-2



IM-13U



V-7A



RF-1U



IG-82U

Prices and specifications subject to change without notice

### NEW! TRANSISTOR FM TUNER

Designed to match the AA-22U Amplifier. Available in separate units comprising Models TFMT-1 RF Tuning Unit £5.16.0 incl. P.T. and TFA-1M (Mono) IF Amplifier, power supply, etc. £15.3.0 kit or TFA-1S (Stereo) IF Amplifier, etc. £19.2.0 kit. TFM-1 14 transistor circuit. Pre-assembled and aligned "front-end". 4 stage IF Amplifier. AFC. Printed circuit construction. Walnut veneered, finished cabinet available as optional extra. Can be built for:

Total Price kit (Mono) £20.19.0 incl. P.T.

Total Price kit (Stereo) £24.18.0 incl. P.T.

Cabinet £2.5.0 extra. Send for full details.



### TRANSISTOR RECEIVERS

**"OXFORD" LUXURY PORTABLE. Model UXR-2.** Specially designed for use as a domestic, car or personal portable receiver. Many features, including solid leather case. Kit £14.18.0 incl. P.T.



UXR-2

**TRANSISTOR PORTABLE. Model UXR-1.** Pre-aligned I.F. transformers, printed circuit. Covers L.W. and M.W. Has 7" x 4" loud-speaker. Real hide case. Kit £12.11.0 incl. P.T.



UXR-1

**JUNIOR EXPERIMENTAL WORKSHOP. Model EW-1.** More than a toy! Will make over 20 exciting electronic devices, incl: Radios, Burglar Alarms, etc. 72 page Manual. The ideal present! Kit £7.13.6 incl. P.T.



UJR-1

**JUNIOR TRANSISTOR RADIO. Model UJR-1.** Single transistor set. Excellent introduction to radio. Kit £2.7.6 incl. P.T.

WELCOME TO OUR LONDON HEATHKIT CENTRE  
233 Tottenham Court Road

We open MONDAY - SATURDAY 9 a.m. - 5.30 p.m.  
THURSDAY ... 11 a.m. - 2.30 p.m.  
Telephone No: MUSeum 7349

WHEN YOU ARE IN TOWN, WE HOPE YOU WILL VISIT US THERE

**TAPE AMPLIFIERS      TAPE DECKS      CONTROL UNITS**



**FM TUNER  
FM-4U**



**MAGNAVOX  
DECK**

**HI-FI FM TUNER. Model FM-4U.** Available in two units. R.F. tuning unit (£2.15.0 incl. P.T.) with I.F. output of 10.7 Mc/s, and I.F. amplifier unit, with power supply and valves (£13.13.0). May be used free standing or in a cabinet. Total Kit **£16.8.0**

**MAGNAVOX "363" TAPE DECK.** The finest buy in its price range. Operating speeds: 1½", 3¼" and 7½" p.s. Two tracks, "wow" and "flutter" not greater than 0.15% at 7½" p.s. **£13.10.0**  
MAGNAVOX deck with TA-1M Kit **£31.5.6**

**HI-FI AM/FM TUNER. Model AFM-1.** Available in two units which, for your convenience, are sold separately. Tuning heart (AFM-T1—£4.13.6 incl. P.T.) and I.F. amplifier (AFM-A1—£22.11.6). Printed circuit board, 8 valves. Covers L.W., M.W., S.W., and F.M. Built-in power supply. Total Kit **£27.5.0**



**TRUVOX  
DECK**



**AM/FM  
TUNER**

**TRUVOX D-93 TAPE DECKS.** High quality stereo/mono tape decks. D93/2, ¼ track, **£36.15.0** D93/4, ¼ track, **£36.15.0**

**TAPE RECORDING/PLAYBACK AMPLIFIER.** Thermometer type recording indicators, press-button speed compensation and input selection. Mono Model TA-1M. Kit **£19.18.0** Assembled **£28.18.0**  
Stereo Model TA-1S. Kit **£25.10.0** Assembled **£35.18.0**

**MONO CONTROL UNIT. Model UMC-1.** Designed to work with the MA-12 or similar amplifier requiring 0.25V or less for full output. 5 inputs. Baxandall type controls. Kit **£9.2.6** Assembled **£14.2.6**

**STEREO CONTROL UNIT. Model USC-1.** Push-button selection, accurately matched ganged controls to ±1dB. Rumble and variable low-pass filters. Printed circuit boards. Kit **£19.19.0** Assembled **£27.5.0**

**First in dependability - first in performance**

Convenient credit terms available in U.K. over £10



**SSU-1**

**SPEAKER SYSTEMS**

**HI-FI SPEAKER SYSTEM. Model SSU-1.** Ducted-port bass reflex cabinet "in the white". Two speakers. Vertical or horizontal models with legs, Kit **£12.12.0**, without legs, Kit **£11.17.6** incl. P.T.

**THE BERKELEY Slim-line SPEAKER SYSTEM,** fully finished walnut veneered cabinet for faster construction. Special 12" bass unit and 4" mid/high frequency unit. Range 30-17,000 c/s. Size 26" x 17" x only 7½" deep. Modern attractive styling. Excellent value. Kit **£19.10.0** Assembled **£24.0.0**

**COTSWOLD SPEAKER SYSTEMS.** Outstanding performance for price.

**MFS:** Size 36" x 16½" x 14" deep. Kit **£25.12.0** Assembled **£33.17.0**

**STANDARD:** Size 26" x 23" x 14½" deep. Kit **£25.12.0** Assembled **£33.17.0**



**Berkeley**

**HI-FI CABINETS**

A wide range available including:

**GLOUCESTER.** Kit **£18.10.0** incl. P.T.

**MALVERN.** Kit **£18.1.0** incl. P.T.

**CHEPSTOW.** Kit **£11.18.6** incl. P.T.

We can also make available the well-known RECORD HOUSING range of fully finished cabinets.



**Malvern**

**SEND FOR THE LATEST FREE CATALOGUE**

INSTRUMENT AND AMATEUR RADIO BROCHURES AVAILABLE ON REQUEST

Prices quoted are Mail Order prices.

**DAYSTROM LTD** DEPT. RC.8 GLOUCESTER

**"AMATEUR" EQUIPMENT**

**THE "MOHICAN" GENERAL COVERAGE RECEIVER. Model GC-1U.** With 4 piezo-electric transfilters, variable tuned B.F.O. and Zener diode stabiliser, this is an excellent fully transistorised general purpose receiver for Amateur and Short wave listeners. Printed circuits, telescopic aerial, tuning meter and large slide-rule dial. Kit **£37.17.6** Assembled **£45.17.6**

**AMATEUR BANDS RECEIVER. Model RA-1.** To cover all the Amateur Bands from 160-10 metres. Many special features, including: half-lattice crystal filter; 8 valves; signal strength "S" meter; tuned R.F. Amp. stage. Kit **£39.6.6** Assembled **£52.10.0**

**160-10M TRANSMITTER. Model DX-100U.** Careful design has achieved high performance and stability. Completely self-contained. Kit **£81.10.0** Assembled **£106.15.0**

**COMMUNICATIONS TYPE RECEIVER. Model RG-1.** A high performance, low cost receiver for the discriminating listener. Frequency coverage: 600 kc/s-1.5 Mc/s and 1.7 Mc/s-32 Mc/s. Kit **£39.16.0** Assembled **£53.0.0**

**REFLECTED POWER METER and SWR BRIDGE. Model HM-11U.** Indicates reliably, but inexpensively, whether the RF power output of your TX is being transferred efficiently to radiating antenna. Kit **£8.10.0** Assembled **£10.15.0**



**GC-1U**



**RG-1**



**HM-11U**

**OUTSTANDING "AMATEUR" EQUIPMENT**

A wide range of American Amateur SSB equipment is now available in the U.K. Why not send for full details of range, for example:

**FILTER TYPE SSB TRANSCEIVERS.** Models for 80, 40 or 20 metre bands.  
Model HW-12 (80M) **£67.10.0**, Kit. incl. **£66.0.0**, Kit. duty, etc.  
Model HW-22 (40M) **£66.0.0**, Kit. duty, etc.  
Model HW-32 (20M) **£66.0.0**, Kit. etc.



**80M Transceiver  
HW-12**

Without obligation please send me  
**FREE BRITISH HEATHKIT CATALOGUE** (Tick here)  
**FULL DETAILS OF MODEL(S)**  
 (Please write in BLOCK CAPITALS)  
 NAME \_\_\_\_\_  
 ADDRESS \_\_\_\_\_  
 DEPT. RC.8

# Scottish Insurance Corporation Ltd

38 EASTCHEAP · LONDON · EC3



## TELEVISION SETS, RECEIVERS AND TRANSMITTERS

Television Sets, Receivers and Short Wave Transmitters are expensive to acquire and you no doubt highly prize your installation. Apart from the value of your Set, you might be held responsible should injury be caused by a fault in the Set, or injury or damage by your Aerial collapsing.

A "Scottish" special policy for Television Sets, Receivers and Short Wave Transmitters provides the following cover:

- (a) Loss or damage to installation (including in the case of Television Sets the Cathode Ray Tube) by Fire, Explosion, Lightning, Theft or Accidental External Means at any private dwelling-house.
- (b) (i) Legal Liability for bodily injury to Third Parties or damage to their property arising out of the breakage or collapse of the Aerial Fittings or Mast, or through any defect in the Set. Indemnity £10,000 any one accident.
- (ii) Damage to your property or that of your landlord arising out of the breakage or collapse of the Aerial Fittings or Mast, but not exceeding £500.

The cost of Cover (a) is 5/- a year for Sets worth £50 or less, and for Sets valued at more than £50 the cost is in proportion. Cover (b) (i) and (ii) costs only 2/6 a year if taken with Cover (a), or 5/- if taken alone.

Why not BE PRUDENT AND INSURE your installation—it is well worth while AT THE VERY LOW COST INVOLVED. If you write to the Corporation's Office a proposal will be submitted for completion.

---

Write for full details, quoting reference 5304, to:—

**THE MANAGER**  
**SCOTTISH INSURANCE CORPORATION LTD.,**  
**38 EASTCHEAP, LONDON E.C.3**

---



# BENTLEY ACOUSTIC CORPORATION LTD.

38 Chalcoot Road, Chalk Farm,  
LONDON, N.W.1.

47 Norfolk Road,  
LITTLEHAMPTON, Sussex,  
Littlehampton 2043

Please forward all mail orders to Littlehampton

0A2	5/9	6/30L2	8/9	AZ31	7/9	EF36	3/6	GZ34	10/-	PY801	6/3
0B2	6/-	9D7	7/6	DAF96	6/6	EF37A	7/6	GZ37	14/6	U25	8/6
1L4	2/3	10C1	12/6	DF96	6/6	EF39	5/-	HABC80	9/3	U26	8/6
1R5	4/-	10C2	12/6	DK92	8/-	EF41	8/-	KT66	12/3	UI91	9/6
1S5	3/3	10F1	9/9	DK96	7/6	EF80	4/3	PABC80	7/6	U301	11/-
1T4	2/6	10F18	9/9	DL96	6/9	EF85	4/6	PC86	9/-	U329	9/-
2D21	5/6	10LD11	14/6	DM70	5/6	EF86	4/6	PC88	9/-	U404	6/-
3D6	3/9	10P13	12/-	DY87	6/9	EF89	4/6	PC95	6/9	U801	15/-
3Q4	5/3	10P14	11/6	E88CC	12/-	EF91	3/-	PC97	5/9	UABC80	5/3
3V4	5/3	12AT6	4/6	EABC80	5/9	EF92	2/6	PC900	9/6	UAF42	7/9
354	4/9	12AU6	5/9	EAF42	5/9	EF97	10/6	PCC84	5/6	UBC41	6/6
3V3GT	4/9	12AV6	5/9	EB91	2/3	EF90	9/9	PCC85	6/9	UBC81	6/6
5Z4	4/6	12BA6	5/3	EBC41	6/6	EF183	6/9	PCC88	10/6	UBF80	5/6
6AQ5	4/9	12BE6	4/9	EBC81	6/3	EF184	6/9	PCC89	11/6	UBF89	5/9
6AT6	3/6	12BH7	6/-	EBF80	5/9	EH90	9/6	PCC189	3/9	UBL21	10/9
6AU6	5/9	19AQ5	7/3	EBF83	7/3	EL33	6/6	PCF80	6/6	UC92	6/3
6AV6	5/6	20D1	10/-	EBF89	5/9	EL36	8/9	PCF82	6/-	UCC84	8/6
6BA6	4/6	20F2	11/6	EBL21	10/3	EL41	7/6	PCF84	8/6	UCC85	8/6
6BE6	4/3	20F1	14/6	EC92	6/6	EL42	7/9	PCF86	8/3	UCF80	8/3
6BH6	5/3	20P3	12/-	ECC40	10/6	EL44	6/6	PC801	9/6	UC121	8/-
6BJ6	5/6	20P4	13/-	ECC81	3/6	EL85	7/6	PCF802	10/-	UC142	8/-
6BQ7A	7/6	20P5	11/6	ECC82	4/6	EL86	7/3	PCL82	6/6	UCH81	6/6
6BR7	8/3	30C15	10/-	ECC83	4/6	EL95	5/-	PCL83	8/9	UCL82	7/3
6BV6	7/6	30C17	11/9	ECC84	5/6	ELL80	14/-	PCL84	7/6	UCL83	9/-
6CD6G	22/-	30C18	8/-	ECC85	5/3	EM71	14/-	PCL85	8/6	UF41	7/9
6CH6	3/-	30F5	8/3	ECM80	8/9	EM80	6/9	PCL86	8/6	UF42	4/9
6F1	9/6	30FL1	9/3	ECC189	11/6	EM81	7/9	PEL45	7/-	UF80	6/3
6J5G	3/9	30FL14	11/-	ECCF80	7/3	EM84	5/9	PCF200	14/6	UF85	6/9
6J7G	4/6	30L15	10/3	ECF82	6/3	EM85	12/-	PL36	9/-	UF86	9/6
6K7G	1/3	30L17	11/6	ECF86	10/-	EM87	6/6	PL81	6/9	UF89	5/6
6K8G	3/3	30P12	10/-	ECH21	10/-	EY51	5/6	PL82	5/3	UL41	8/9
6L6GT	7/3	30P18	12/-	ECH31	6/-	EY81	7/3	PL83	6/6	UL84	5/6
6L18	10/-	30P11	13/-	ECH42	8/6	EL4	6/3	PL84	6/3	UM80	8/3
6LD20	6/6	30PL13	10/6	ECH81	5/6	EY84	9/6	PY33	8/9	UY21	9/-
6Q7G	5/6	30PL14	11/-	ECH83	6/6	EY86	5/9	PY80	4/9	UY41	5/-
6SL7	4/9	30PL15	9/6	ECH84	9/-	EY88	8/9	PY81	5/-	UY85	4/9
6SN7	4/6	35V4	4/6	ECL80	5/9	EZ40	5/6	PY82	4/9	VP48	12/-
6V6G	3/6	85A2	6/6	ECL82	6/6	EZ41	6/3	PY83	5/6	X41	10/-
6X4	3/9	85B2	11/9	ECL83	6/3	EZ80	3/9	PY88	7/3	X78	26/2
6X5	5/3	5763	7/6	ECL86	8/-	EZ81	4/3	PY800	5/9	X79	40/9

Terms of business: Cash with order only. No C.O.D. Post/packing 6d. per item. Orders over £5 post free. All orders despatched same day as received. Complete catalogue including transistor section and components with terms of business 6d. Any parcel insured against damage in transit for 6d. extra. We are open for personal shoppers 9 a.m.-5 p.m. Saturdays 9 a.m.-1 p.m.

## Any holes in your knowledge of TRANSISTORS?

Whatever your interest in transistor circuitry, you will find the Mullard "Reference Manual of Transistor Circuits" and "Transistor Radios—Circuitry and Servicing", valuable sources of reference.

The former describes more than sixty circuits for both domestic and industrial applications.

The latter is an introduction to the subject and describes the basic properties of semiconductors, their function, elementary circuitry and servicing.

REFERENCE  
MANUAL OF  
TRANSISTOR  
CIRCUITS  
U.K. PRICE  
12/6  
Post extra 1/-

TRANSISTOR  
RADIOS  
Circuitry and  
Servicing  
U.K. PRICE  
5/-  
Post extra 6d.



Get your copies from your radio dealer, or send remittance with order to:

MULLARD LTD - MULLARD HOUSE - TORRINGTON PLACE - LONDON WC1

## NEW BRITISH RECORDING TAPE

Famous Mfr. Bulk Purchase — Genuine recommended Tape Bargain. Unconditional Guarantee. Fitted Leader and Stop Foils (except 3").

Sp'd. (PVC base)	L.P. (PVC base)	D.P. (Milar base)	Triple Play
3" 150ft. ... 3/9	225ft. ... 4/9	300ft. ... 6/6	3" 450ft. ... 12/6
5" 600ft. ... 11/6	900ft. ... 13/-	1,200ft. ... 23/6	4" 900ft. ... 25/-
5 1/2" 850ft. ... 14/6	1,200ft. ... 17/6	1,800ft. ... 29/6	
7" 1,300ft. ... 17/6	1,800ft. ... 22/6	2,400ft. ... 37/6	

Post and Packing — 3" Reels 6d. Each additional Reel 3d. 4" to 7" Reels 1/- Each additional Reel 6d. All tape accessories stocked.

EMPTY TAPE REELS (Plastic): 3" 1/3, 4" 2/-, 5" 2/-, 5 1/2" 2/-, 7" 2/3.

PLASTIC REEL CONTAINERS (Cassettes): 3" 1/3, 5" 1/9, 5 1/2" 2/-, 7" 2/3.

### TRANSISTOR COMPONENTS

Midget I.F.'s—465 kc/s  $\frac{1}{2}$ " diam., second or third, each 5/6  
 Osc. coil M. & L.W.  $\frac{1}{2}$ " diam. 5/-  
 Midget Driver Trans. 9/1  
 Ditto O/Put Push-pull 3 ohms 6/-  
 Elect. Condensers—Midget Type 15V 1mf-50mf. ea. 1/9, 100mf, 2/-, 2.5mH, 5mH, 7.5mH, 10mH R.F. Chokes 2/6 each.  
 Condensers—150V wkg. .01mf. to .04mf., .9d., .05mf., .1mf., 1/-, .25mf., 1/3, .5mf., 1/6, etc.  
 Tuning Condensers—1.B. "OO" 208+176P. 8/6, Ditto with trimmers, 9/6, 365P single, 7/6, Sub-min. 2" DILEMIN 100pF, 300pF, 500pF, 7/-.  
 Midget Vol. Control with edge control knob, 5k $\Omega$  with switch, 4/9, ditto less switch, 3/9.

### TUB-ELECTROLYTICS-CAN

25/25V, 50/12V, 1/9; 8+8/450V, 4/6; 50/50V, 100/125V, 2/-; 32+32/275V, 4/6; 8/450V, 4/350V, 2/3; 50/50/350V, 6/6; 16+16/450V, 5/6; 60/250/275V, 12/6; 32+32/450V, 6/6; 100+200/275V, 12/6.

ENAMELED COPPER WIRE  
 —2oz. reels 14g-20g, 3/-; 22g-28g, 3/6; 30g-34g, 4/3; 36g-38g, 4/9; 39g-40g, 5/-, etc.

TINNED COPPER WIRE  
 16-22g, 4/- 2oz. reels.

ERSIN MULTICORE SOLDER  
 60/40, 4d. per yard, Cartons 6d., 1/-, 2/6, etc

### TYGAN FRET (Contem. pat.), 12 x 12", 2 1/2" x 18", 3/-; 12 x 24", 4/-, etc.

EXPANDED ANODISED METAL  
 —Attractive gilt finish  $\frac{1}{4}$ " x  $\frac{1}{4}$ " diamond mesh 4/6 sq. ft. Multiples of 6" cut. Max. size 4' x 3', 47/6 plus carr.  
 BONDACOUST Speaker Cabinet  
 Acoustic Wadding (1" thick approx.) 18" wide, any length cut, 6/- yd.  
 Volume Controls—5K-2 Meg-ohms, 3" Spindles Morganite Midget Type. 1 1/2" diam. Guar. 1 year. LOG or LIN ratios less Sw., 3/6. DP. Sw. 5/-. Twin Stereo less Sw., 7/6. D.P. Sw., 9/6 (100 k to 2 Meg. only).

Condensers—Silver Mica. All values 2pF to 1,000pF, 6d. each. Ditto Ceramics, 9d. Tub. 450V T.C. etc. 0.001 mfd to 0.01, 9d. and 0.1/350V, 10d. 0.01-0.1/500V, 1/-, 0.25 Hunt, 1/6. 0.25 T.C.C., 1/9, etc., etc.

Close Tol. S/Micas—10% 5pF-500pF, 8d. 600-5,000pF, 1/-, 1% 2pF-100pF, 9d. 100pF-500pF, 11d. 575pF-5,000pF, 1/6. Resistors—Full Range 10 ohms-10 meg. ohms 20%



Est. 1946

Send for detailed bargain lists, 3d. stamp. We manufacture all types Radio Mains Transf. Chokes. Quality O/P Trans., etc. Enquiries invited for Specials, Prototypes for small production runs. Quotation by return.

### RADIO COMPONENT SPECIALISTS

70 Brigstock Road, Thornton Heath, Surrey THO 2188. Hours: 9 a.m.-6 p.m., 1 p.m. Wed. Terms C.W.O. or C.O.D. Post and Packing up to 1/6, 1/-, 11b. 1/9, 3/6, 3/-, 5/6, 3/9, 8/6, 4/6.

## 6 VALVE AM/FM TUNER UNIT



Med. and VHF 190m-550m, 86 Mc/s-103 Mc/s, 6 valves and metal rectifier. Self-contained power-unit, A.C. 200/250V operation. Magic-eye indicator, 3 push-button controls, on/off, Med., VHF. Diode and high output sockets with gain control, illuminated 2-colour perspex dial 1 1/2" x 4", chassis size 1 1/2" x 4" x 5 1/2". A recommended Fidelity Unit for use with Mullard "3-3" or "5-10" Amplifiers.

**BARGAIN PRICE.** Complete kit of parts, inc. Power Pack (as illustrated) Price £10.19.6, Carr. 7/6. Ditto, less Power Pack, £9.19.6, carr. 7/6. Circuit and constr's details, 4/6, free with kit.

## MULLARD "3-3" & "5-10" HI-FI AMPLIFIERS

**3 OHM & 15 OHM OUTPUT**  
 "3-3" Amp. 3-valve, 3 watt Hi-Fi quality at reasonable cost. Bass Boost and Treble controls, quality sectional output transformer, 40 c/s-25 kc/s  $\pm$  1dB, 100mV for 3W, less than 1% distortion. Bronze escutcheon panel. Complete Kit only 7 gns. Carr. 5/-. Wired and tested £8.10.0.

**MULLARD "5-10" AMPLIFIER**—5 valves 10W, 3 and 15 ohms output. Mullard's famous circuit with heavy duty ultra-linear quality output trf. Basic amplifier kit price £9.19.6. Carr. 7/6. Ready built 11 1/2 gns.

**2-VALVE PRE-AMP. UNIT**  
 Based on Mullard's famous 2-valve (2 x EF86) circuit with full equalisation with volume, bass, treble, and 5-position selector switch. Size 9" x 6" x 2 1/2". Complete kit £6.6.0. Ready built £7.19.6, carr. 3/6d.

1/2 and 1/4W, 3d., 1/2W, 5d., 1W, 6d., 2W, 9d., 1 1/2W and 1 1/4W, 4d.  
 Hi-Stab. 5% 1W, 1 1/2W, 6d. (100 ohms-1 meg.). Other values 9d. 1% 1/2W, 1/6, etc., etc.  
 Wire-wound Resistors—25 ohms to 10K ohms, 5 watt 1/3d, 10 watt 1/6d, 15 watt 1/9d.

**ALUMIN. CHASSIS.** 18 g. Plain Undrilled folded 4 sides, 2in, deep. 6in. x 4in., 4/6; 8in. x 6in., 5/9; 10in. x 7in., 6/9; 12in. x 6in., 7/6; 12in. x 8in., 8/-, etc.  
**ALUMIN. SHEET.** 18g. 6in. x 6in. 1/-; 6in. x 9in., 1/6; 6in. x 12in., 2/-; 12in. x 12in., 4/6 ea.

Jack Plugs. Standard 2 1/2" Igranite Type, 2/6. Screened Ditto, 3/3. Miniature scr. 1 1/2", 2/3. Sub-min., 1/3.  
 Jack Sockets. Open Igranite Moulded Type, 3/6. Closed Ditto, 4/-. Miniature Closed Type, 1/6. Sub-min. (deaf aid) ditto, 1/6. Stereo Jack Sockets, 3/6. Stereo Jack Plugs, 3/6.

Phono Plugs, 9d. Phono Sockets (open), 9d. Ditto (closed), 1/-. Twin Phono Sockets (open), 1/3.

# THE MODERN BOOK CO

**GEC Inter: Transistor Manual.** 7th ed. 18s. Postage 1s 6d.

**Basic Theory and Application of Transistors.** U.S. Dept. of Army. 10s. Postage 1s.

**New Skill-Building Transistor Projects and Experiments.** By L. E. Garner. 24s. Postage 1s.

**Transistor Pocket Book.** By R. G. Hibberd. 25s. Postage 1s.

**Everyday Electronics.** By T. Roddam. 22s. 6d. Postage 1s.

**Electronics Pocket Book.** By J. P. Hawker and J. A. Reddihough. 21s. Postage 1s.

**Bench Servicing Made Easy.** By R. G. Middleton. 24s. Postage 1s.

**The Radio Amateur's Handbook 1966.** Ed. by A.R.R.L. 40s. Postage 2s.

**Transistor Ignition Systems Handbook.** By B. Ward. 22s. 6d. Postage 1s.

**Troubleshooting with the Oscilloscope.** By R. G. Middleton. 20s. Postage 1s.

**Hi-Fi Stereo Handbook.** By W. F. Boyce. 32s. Postage 1s.

**Troubleshooting with Test Meters (VOM and VTVM).** By R. G. Middleton. 21s. Postage 1s.

**Transistor Receivers and Amplifiers.** By F. G. Rayer. 30s. Postage 1s.

**Transistor Electronic Organs for the Amateur.** By A. Douglas and S. Astley. 18s. Postage 1s.

**Wireless Servicing Manual.** By W. T. Cocking. 25s. Postage 1s. 6d.

**Worked Examples in Electronics and Telecommunications.** By B. Holdsworth and Z. E. Jaworski. Vol. 2, 22s. 6d. Vol. 1, 25s. Postage 1s.

Complete Catalogue 1s.

We have the Finest Selection of English and American Radio Books in the Country

**19-21 PRAED STREET (Dept RC) LONDON W2**

Telephone PADdington 4185

## THE DUCHESS OF KENT PERMANENT BUILDING SOCIETY

Member of the Building Societies Association

Savings in this old established Building Society combine sound investment with an attractive return

Shares are in units of £25 each (maximum investment £5,000) . . . BUT, for the smaller saver, Subscription Share accounts may be opened with any sum from 1/- upwards. Interest is payable half-yearly on Fully Paid Shares—credited annually on Subscription Shares—all interest accrues monthly

WITHDRAWALS AT SHORT NOTICE

**INTEREST IS AT 4% PER ANNUM**

(There is NO DEDUCTION FOR INCOME TAX, as this is paid by the Society)

FOR FURTHER INFORMATION APPLY TO

**DUCHESS OF KENT  
PERMANENT BUILDING SOCIETY**

289/293 Regent Street London W.1

Telephone MUSEum 4876-9



ESTABLISHED

1865

Please send to me, without obligation, free brochure and a copy of the audited statement of accounts. (I understand that I shall not be troubled with calls by representatives)

Name .....

(If lady, please state Mrs. or Miss)


Address .....

..... R.C.  
(Please use Block Capitals for both name and address)



A Mullard inspiration

# 10 + 10 STEREO

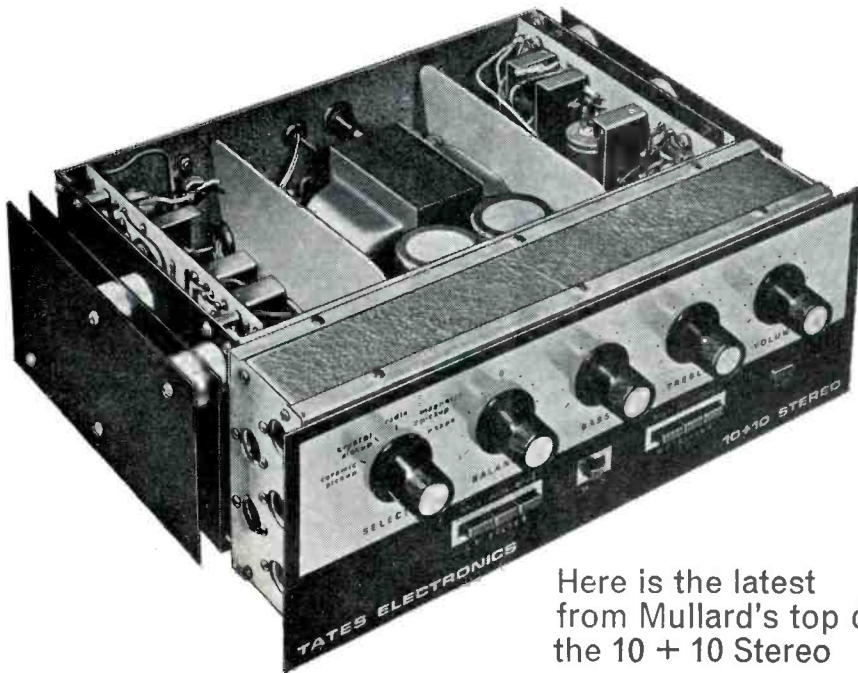

Here is the latest  
from Mullard's top designers,  
the 10 + 10 Stereo





This remarkable pi-mode stereo amplifier has been engineered by Bates to very high standards. Gain experience and enjoyment in the thrill of constructing this superb amplifier. Undoubtedly a piece of electronic precision, the Mullard designed 10 + 10 costs no more than ordinary equipment, and building can commence for as little as £5. 5. 0. Circuits, parts lists and assembly procedure are fully detailed in the 10 + 10 Construction Manual. Send for your copy today, 12/6d, post paid.

Tates Electronic Services Ltd., Waterloo Road, Stockport, Cheshire. Telephone: Stockport 7301.
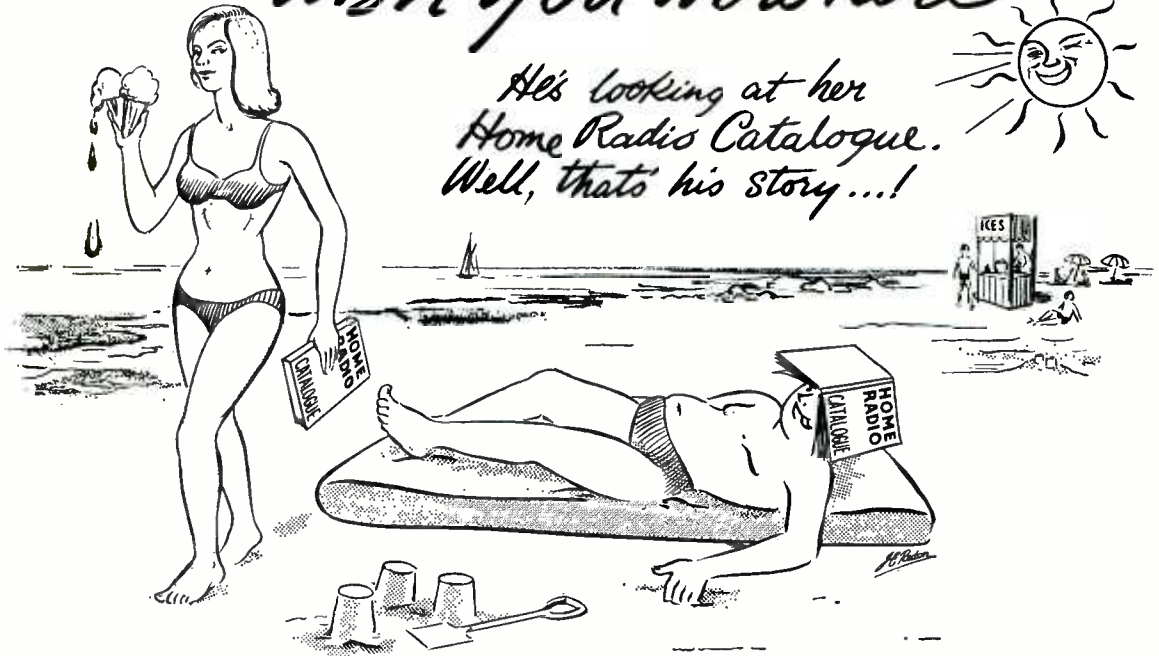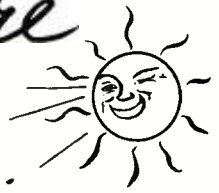
# TATES ELECTRONICS

*"Wish you were here"*

*He's looking at her  
Home Radio Catalogue.  
Well, that's his story....!*



You really should not go on holiday without a Home Radio Catalogue! Not only does it make a wonderful sunshade and a useful fly swatter, but it is ideal as a cover to hide the fact that you are keeping a sly look out for the local talent. We have even provided a blank page at the back for jotting down phone numbers. One chap we know reads his in bed. The catalogue, not the phone numbers! This does not surprise us, for this world-renowned components catalogue is of absorbing interest to every radio constructor.

The latest edition (reprint No. 12 just off the press) is bigger and better than ever. It has 215 pages, lists over 6,000 items, over 1,000 of them illustrated. Like its predecessors, it contains five vouchers, each worth 1/- when used as directed, and with each catalogue we supply *free* a complete Price Supplement, a special Bargain List.

If the sun is hot, if the flies are bothersome, or if the girls are calling—send for your catalogue today. It costs 7/6 plus 1/6 post and packing. If you've already had your holidays *still* send for a copy—it's more than worth the money even if you only use it for the purpose for which we originally produced it—as a simple, interesting, time saving method of ordering your radio and electronic components.

*Send the coupon with your cheque or postal order for 9/-.*

Please write your Name and Address in block capitals

Name .....

Address .....

.....

.....

Home Radio Ltd., Dept. RC, 187 London Rd., Mitcham, Sy.

# THE Radio Constructor



Incorporating THE RADIO AMATEUR

## AUGUST 1966

Vol. 20, No. 1  
Published Monthly  
(1st of month)

*Editorial and  
Advertising Offices*  
57 MAIDA VALE LONDON W9

*Telephone*  
CUNningham 6141

*Telegrams*  
Databux, London

First Published  
1947

A 2.25kV Power Supply, <i>by Arthur C. Gee, G2UK</i>	10
Can Anyone Help?	14
Simple Add-On B.F.O. Unit (Suggested Circuit No. 189), <i>by G. A. French</i>	15
Recent Publications	17
Tape Recorder Tuner, <i>by G. Maynard</i>	18
News and Comment	22
Modifications to the CR100, <i>by W. Studley</i>	24
Comprehensive Volume Control Circuit, <i>by Sir Douglas Hall, K.C.M.G., M.A. (Oxon)</i>	27
Circular Timebase, <i>by M. W. Shores, N.Z.I.S.T.</i>	30
In Your Workshop	32
Simple Combination Lock	37
Basic Radio Control, Part 2, <i>by F. L. Thurston</i> (Field Strength Meter, Single Channel "Carrier" Transmitter, Output Monitor)	38
The Design and Construction of Measuring Bridges, Part 2 <i>by W. Kemp</i>	47
Understanding Radio, <i>by W. G. Morley</i> ("Squegging" and Receiver Reaction)	53
Courses of Instruction	58

© Data Publications Ltd., 1966. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription 36s. (U.S.A. and Canada \$5) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers please pay by cheque or International Money Order.

Published in Great Britain by the Proprietors and Publishers Data Publications Ltd. 57 Maida Vale London W9  
Printed by A. Quick & Co. (Printers) Ltd. Clacton-on-Sea England



# A 2.25kV POWER SUPPLY

By **ARTHUR C. GEE, G2UK**

*This compact power unit for amateur transmitter use employs solid-state rectifiers and offers an output of 2.25kV at 250mA (less bleeder current). It must be emphasised that very high voltages and currents appear in the circuit, that the risk of lethal shock is high, and that full safety precautions must be observed when building, testing and using the unit*

THE HOME CONSTRUCTION OF LINEAR R.F. AMPLIFIERS for single sideband transmission is a comparatively simple project as far as the amplifier itself is concerned, but the high voltage d.c. supply required to operate many of the published designs is not so easy to build in the home workshop. Also, surprisingly little information of a constructional nature on this type of equipment appears to have been published in the amateur radio literature of this country.

The most helpful article which the writer has encountered in this respect is that written by E. Lawrence entitled "Transmitter Power Supply Using Semiconductors", which was published on page 280 in the November 1964 issue of *The Radio Constructor* (Vol. 18, Number 4). The design described therein appealed particularly to the writer as it made use of silicon rectifiers, thus enabling a very compact unit to be constructed. The unit was designed to give 1,000 volts at 220mA. The author of the article concluded by stating: "Initial tests both

at reduced voltage with the aid of a Variac and then with full mains applied were successful, and there was every indication that the unit would perform as desired. Subsequently, with the transmitter in the hands of a relatively inexperienced operator, this has been confirmed.

"With this experience the writer is now a convert to solid-state rectifiers and hopes this article will encourage others to investigate their use in similar situations."


## The Present Design

The power requirements of the present writer were considerably greater than those of the author of the previous article. The linear amplifier used by the writer requires some 2,500 volts d.c. at about 200mA for maximum p.e.p., and the first problem was to find a suitable mains transformer.


Amongst radio amateurs, there is a system known as "ways and means", and once the writer's requirements were passed along the "bush telegraph" one of his friends produced a massive surplus transformer with a secondary rated at 1,300-0-1,300 volts at 250mA, and with the usual British rated tapped primary winding. This was handed over with the instruction: "Mind you don't kill yourself with it!" The transformer provided an excellent starting point from which to design the final unit.

At this point, the reader is advised to read the previous article by E. Lawrence since it will save repeating essential design considerations here. Following these considerations, the writer decided to use the same type of bridge rectifier circuit, with the appropriate number of BY100 silicon rectifiers which would be needed for the higher voltages involved.

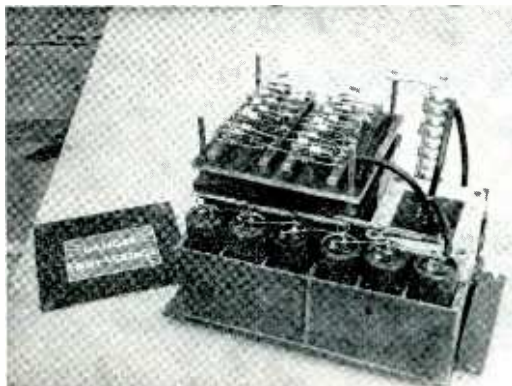The next consideration was the type of smoothing circuit to be employed. In view of the fact that the power supply was to be used with an s.s.b. linear amplifier, where the voltage regulation in the



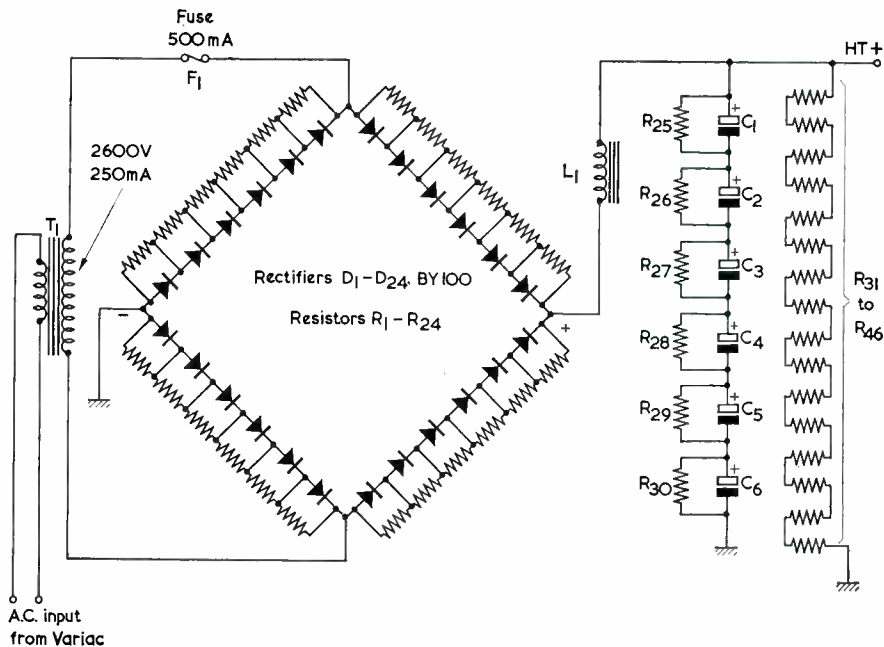Side view, illustrating the layout of the electrolytic capacitors and the bridge rectifier components



The circuit of the power supply unit. It is recommended that the supply to the primary of  $T_1$  be obtained by way of a Variac, thus enabling voltage to be gradually increased from zero, both for testing and for later use. The supply output is fed to an s.s.b. linear amplifier, to which is fitted a voltmeter for monitoring the output voltage. Capacitors  $C_1$  to  $C_6$  each consist of a  $100 \pm 64\mu\text{F}$  dual capacitor, the two sections being paralleled to form a single  $164\mu\text{F}$  capacitor.

### Components List

#### Resistors

- $R_1$ – $R_{24}$  24 resistors,  $1\text{M}\Omega$ , 2 watt, 10%
- $R_{25}$ – $R_{30}$  6 resistors,  $47\text{k}\Omega$ , 5 watt, 10%
- $R_{31}$ – $R_{46}$  16 Radiospares Power Resistor Sections,  $2.2\text{k}\Omega$ , 65mA each section (Home Radio (Mitchan) Ltd.)

#### Capacitors

- $C_1$ – $C_6$  6 dual electrolytic capacitors,  $100 \pm 64\mu\text{F}$ , 450V wkg.

#### Transformer

- $T_1$  Mains transformer, secondary 1,300–0–1,300V, 250mA (see text)

#### Choke

- $L_1$  Swinging choke 5–25H, 250mA max. current

presence of a greatly varying current must be as good as possible, a choke input filter was a foregone conclusion. In the interests of compactness, it was also decided to try and work with a single section filter; that is, to use one choke only. This could be of the "swinging choke" variety. The fact that the output voltage of a choke filter is lower than that of a capacitor input filter was of no concern, since

#### Rectifiers

- $D_1$ – $D_{24}$  24 silicon rectifiers type BY100 (Mullard)

#### Fuse

- $F_1$  500mA (see text)


#### Ancillaries

- 1 Variac, 2.5A rating (Service Trading Co., 47–49 High Street, Kingston-upon-Thames)
- 1 Voltmeter, 0–3,000 or 0–3,500V (see text)
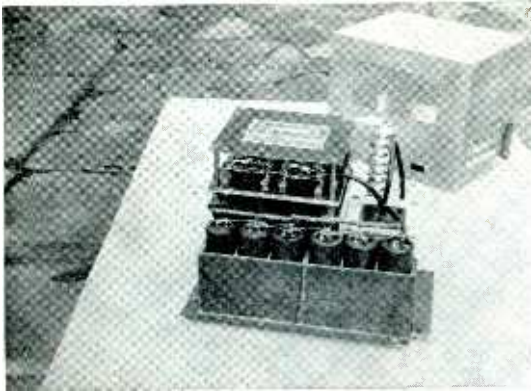
#### Miscellaneous

- "High Voltage" warning sign (Panel Signs Transfer from either Set No. 3 or Set No. 4)
- 2BA studding (for  $R_{31}$ – $R_{46}$ )
- Mains plug and socket
- High voltage output plug and socket, type L.623/P and L.623/S (Belling-Lee)
- High voltage wire
- Chassis, case, etc.

the secondary voltage of the transformer was, if anything, higher than the voltage really required. The output voltage from a choke input filter following a bridge rectifier is, in fact, 0.9 times the input r.m.s. voltage. On checking the transformer, it



A protective sheet of Paxolin covers the bridge rectifier circuit after assembly

was found that, by using the highest primary tapplings, the actual voltage across the secondary was 2,500 volts a.c. Ignoring the d.c. voltage drop through the silicon rectifiers and choke, we can therefore expect an output voltage from the choke filter of  $2,500 \times 0.9 = 2,250$  volts d.c. This figure was adopted for the ensuing design calculations.

The characteristic of the swinging choke is that its inductance is high at low currents, decreasing in value as the current increases. A typical choke of this type gives an inductance of 25 henrys at 50mA, whilst at 250mA its inductance falls to 5 henrys. In order that a swinging choke circuit may function properly a minimum value of current must flow through the choke and this current is given by the equation:


$$\text{Current in mA} = \frac{\text{d.c. voltage}}{\text{Max. inductance in henrys}}$$

In the case under consideration:

$$I = \frac{2250}{25} = 90\text{mA}$$

Thus, a current of not less than 90mA should always be drawn through the choke.

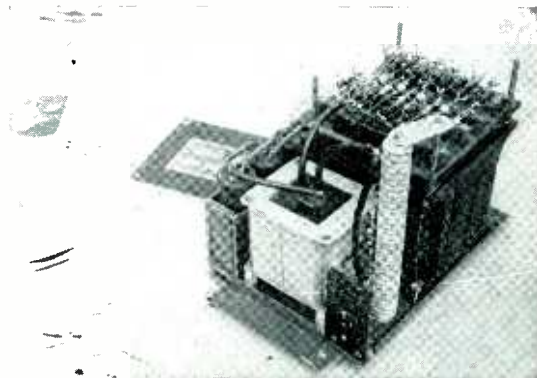The minimum current drawn by the transmitter



The assembly of the Radiospares resistor units for the bleeder is clearly shown here

will usually be lower than the critical minimum current required in the choke. In consequence, a bleeder resistor is added to bring the minimum choke current up to the required value. The bleeder resistor also ensures that the smoothing capacitors are reliably discharged when the mains supply is turned off.

In the writer's case, the linear amplifier has a standing current of 30mA. There is also a further drain of about 10mA through the resistors bypassing the smoothing capacitors (which will be dealt with later). The bleeder resistor must therefore provide a drain of 90mA less (30+10mA); that is, 50mA.

The dissipation in a resistor passing 50mA at 2,250 volts is 112.5 watts, and it would seem that a very large component, and one that is difficult to obtain, would be required. However, this problem was very neatly solved by using Radiospares "Power Resistor Sections", these consisting of round wirewound resistance units which, in the value employed by the writer, have a diameter of 1in and a height of 0.5in. The resistance units also have a centre hole and a quantity of them may be assembled, one above the other, on a length of 2BA studding. The units employed by the writer each have a value of 2.2kΩ and are rated at 0.065 amps. Sixteen of these units connected in series make up the bleeder and give a total resistance of 35,200Ω, with the result that a bleeder current of 60mA flows at the power unit output voltage of 2,250. This current is comfortably above the minimum figure of 50mA just mentioned and is nicely within the rated current of the resistance units.<sup>1</sup>

### Smoothing Capacitors

Next to be considered were the smoothing capacitors. G. R. Jessop, G6JP, describing the design for a linear amplifier on page 290 in the *R.S.G.B. Bulletin* for May 1964 (Vol. 40, No. 5) states: "As with all linear amplifiers it is important that the h.t. supplies should be adequately smoothed and of good dynamic performance in order to maintain the voltages substantially constant during the changing operating loads". Continuing with the design considerations for his linear amplifier: "To obtain good dynamic performance of the anode supply, a capacitance of not less than 24μF will be required in the smoothing circuit."

Again, as with the bleeder resistor, suitable high voltage, large value, capacitors are not readily available, as single units, to the home constructor. The best the writer could locate were 3,000 volt 0.5μF components which, even at surplus prices, become a little costly for 48, quite apart from the volume taken up by such a quantity of capacitors!

<sup>1</sup> We are informed by Radiospares Ltd, that the minimum breakdown voltage between the studding and the resistor element in an assembly of this nature is 5kV d.c., whereupon it becomes possible to assemble all the sixteen units on a single piece of 2BA studding. The units may only be obtained through retail channels and not direct from Radiospares Ltd.—Editor.



So the writer fell back on lower voltage electrolytic components. Six dual electrolytic capacitors, each rated at  $100 + 64\mu\text{F}$ , 450 volt working, and with each dual section paralleled, would give a working voltage of 2,700 volts and a total capacitance of  $27\mu\text{F}$ , both figures being just on the right side of the values required. When capacitors are connected in series in this manner, it is necessary to shunt them with equal-value resistors to ensure that the total voltage is equally divided. The writer employed  $47\text{k}\Omega$  5 watt 10% resistors across each dual electrolytic capacitor. This values ensures that correct voltage division occurs even when capacitor leakage current is relatively high. Also, the six  $47\text{k}\Omega$  resistors connected in series cause a constant drain from the power unit output of slightly less than 10mA, thus helping to keep the current through the swinging choke above the critical value.

### The Bridge Rectifier

The final consideration is the design of the silicon rectifier circuit, the obvious choice being a bridge circuit. With this type of circuit, the peak inverse voltage per arm is 1.4 times the r.m.s. voltage presented by the transformer secondary winding. Remembering that there are four arms in a bridge rectifier circuit, this gives us  $2,500 \times 1.4 = 3,500$  volts. The recommended maximum p.i.v. for the BY100 silicon rectifier is 800. Five in each arm would theoretically cope but, to be on the safe side, it was decided to use six, the whole bridge thus requiring twenty-four BY100's. It may be considered that this number is rather extravagant, but the writer felt it was better to err on the side of too many than too few as a weakness in this part of the circuit might well lead to disaster! The rectifiers are, of course, subjected to any "spikes" in voltage which may appear in the mains supply, so one cannot be too careful in providing plenty of reserve in regard to the p.i.v. requirements. The conventional way of smoothing out the effect of these surges is to connect equal-value capacitors of about 1,000pF across each rectifier but, in view of the safety factor afforded by using six rectifiers per arm instead of of five, it was decided to omit these capacitors. Constructional problems are considerably eased by this omission, and no trouble has been experienced in practice. It is still necessary to provide bridging resistors across each rectifier to ensure correct reverse voltage division, and the writer shunted each rectifier with a  $1\text{M}\Omega$  2 watt 10% resistor.

### Constructional Features

Next to be dealt with were constructional details. As has already been inferred, the general size and layout of the unit was partly determined by the dimensions of the transformer. The writer was anxious to make the unit as small as was reasonably practicable, so that it could be stowed away on the floor under the bench. It was, of course, to be totally enclosed in an earthed metal case. The linear amplifier itself is a separate table-top unit,



*The complete power supply unit in its ventilated case and with the associated Variac alongside. The "High Voltage" warning notice is provided in Panel Signs Transfers, Sets Nos: 3 and 4*

a.c. power to the power supply being switched at, and taken down to the unit, from the linear amplifier itself. The h.t. supply is then brought up from the power supply unit to the linear amplifier by heavily insulated cable.

As can be seen from the photographs a very convenient arrangement of components was arrived at, and the writer had the good fortune to have on hand a well ventilated cabinet of suitable proportions to house all the components, with just a little room to spare. The cans of the electrolytic capacitors are, of course, at high potential, so a six-section container to take them was made from sheet Paxolin panels glued together with Araldite, the capacitors being push-fits in their individual compartments. Each capacitor is first covered with a rubber sleeve cut from a bicycle inner tube, and the container dimensions allow it to fit in tightly without further fixing. The capacitor box is mounted to the cabinet base by six small counter-sunk bolts, the heads of which are flush with the surfaces of small blocks of Paxolin, the latter being stuck with Araldite to the bottom of the box. Do *not* drill through the bottom of the box and insert the bolts through direct, or the bottoms of the electrolytic capacitor cans will short-circuit to the metal base.

The swinging choke is mounted on stand-off insulators as it was felt that there was no point imposing an additional strain on its insulation by earthing its metal casing. The bridge rectifier was assembled on a Paxolin frame fixed to the top of the transformer. Paxolin strip, ready drilled with holes at about  $\frac{1}{2}$ in centres can be obtained, into which soldering pins can be inserted. This makes an excellent framework for mounting the BY100's, the layout being clearly apparent from the photographs.

The a.c. power supply is brought in by way of a plug and socket, the h.t. output being taken back to the linear amplifier via a high voltage plug and socket and a length of petrol engine ignition cable.

Two types of this cable are available at motor cycle shops, one being plastic covered and the other rubber covered. The rubber covered variety should be used for the connection to the linear amplifier as it is much more flexible. On the other hand, the h.t. wiring in the unit is better carried out with the plastic covered type, as the lack of flexibility in this is a useful feature in keeping the leads short and in the positions required. Reference to the photographs will illustrate this point.

#### Fuse

In the design by E. Lawrence, referred to earlier, a fuse was inserted in the earthed lead from the bridge rectifier. Subsequent correspondence in *The Radio Constructor*,<sup>2</sup> suggested that a better location for the fuse would be in one of the leads from the transformer secondary, as this would prevent currents circulating through one arm of the bridge rectifier if the rectifiers in an adjacent arm broke down. The fuse in the writer's unit was accordingly inserted in one of the leads from the secondary.

#### Voltage Control

Again referring to the article by E. Lawrence, it is very prudent indeed to test this unit by gradually increasing the primary voltage on the transformer from zero and observing the results. If the constructor uses a Variac for this purpose, he will

immediately realise how useful such a power control unit can be if included as a permanent feature of the power supply. Apart from the fact that the circuit is working fairly close to the maximum working voltage of the electrolytic capacitor network, it is also desirable to avoid sudden surges of voltage as an on/off switch in the primary might produce. Again, it is extremely useful to be able to reduce voltage when tuning up a linear amplifier for s.s.b. or for operating it in continuous mode as for a.m. or R.T.T.Y.

The writer therefore decided to include a Variac in the primary circuit of the transformer. This stands on the operating bench alongside the linear amplifier, so that the voltage to the power supply can be brought up to the required level steadily, and with the surges resulting from on/off switching completely avoided. Excellent bench type Variacs, fully shrouded, can now be obtained at most reasonable prices. One carrying 2.5 amps will be adequate. If Variac control is included, a high reading voltmeter is almost essential to make the most of this power control facility. This feature is included on the panel of the writer's linear amplifier. Suitable meters reading up to 3,500 volts d.c. can be obtained from dealers in surplus equipment at very reasonable prices.

Finally, it must be stated that very high voltages at quite considerable current values are given in this unit. Treat it therefore with great respect and always remember that one moment of thoughtlessness may very easily lead to sudden DEATH.

<sup>2</sup> See "Radio Topics" in the April 1965 issue.

## CAN ANYONE HELP?

*Requests for information are inserted in this feature free of charge, subject to space being available. Users of this service undertake to acknowledge all letters, etc., received and to reimburse all reasonable expenses incurred by correspondents. Circuits, manuals, service sheets, etc., lent by readers must be returned in good condition within a reasonable period of time*

**H.M.V. Radiogram Model 800.**—J. B. Sladen, 213 Milnrow Road, Rochdale, Lancs,—service manual, willing to purchase.

\* \* \*

**Grundig TK20 Tape Recorder.**—J. Cowley, 10 Westways, Bedhampton, Havant, Hants,—service sheet, circuit diagram or any other details.

\* \* \*

**Philips Record-Changer.**—C. H. Leedham, St. Elmo, Sandersfield Gardens, Banstead, Surrey,—service sheet or manual for this type A.G.1015 changer, all expenses met.

\* \* \*

**Ferguson 204XL Receiver.**—D. Witt, 3 Woodside, Cottages, Spital Road, Bromborough, Wirral,

Cheshire,—any information. Also circuit or service sheet for Fidelity tape recorder Argyle Minor.

\* \* \*


**R1949 V.H.F. Receiver.**—J. Donnelly, 19 Ashbrook Road, Old Windsor, Berks,—circuit or service manual, loan or purchase, all expenses met.

\* \* \*

**Power Supply and L. F. Amplifier.**—J. Ayres, 7 Berrylands Road, Surbiton, Surrey,—circuit diagram loan or purchase. Unit bears the legend "Unit No. 2 ZA35737".

\* \* \*

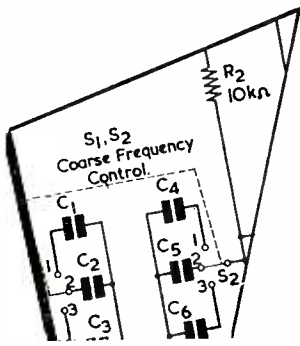**Pilot Record-Player.**—P. S. Thomas, 6 Stevenson House, Boundary Road, London, N.W.8.—purchased some 8 years ago, this model is fitted with a Monarch BSR deck—circuit or any information.



# Simple Add-On B.F.O. Unit

**SUGGESTED CIRCUIT No. 189**

**By G. A. FRENCH**

**M**ANY TRANSISTOR AND VALVE superhet radio receivers intended for domestic listening have short wave bands. Whilst the majority of these receivers give quite acceptable sensitivity and selectivity, they are not attractive for the keen short wave listener because they are not fitted with beat frequency oscillators to enable morse c.w. transmissions to be read.

It is, however, quite a simple matter to construct a separate b.f.o. unit which may be easily coupled to a domestic receiver of this type, and a suitable circuit is given in this month's article. The b.f.o. unit to be described employs a single transistor, and the complete circuit, together with its own battery, may be housed in a small metal case. A screened lead from this case couples into the receiver i.f. amplifier circuits. Advantages of the unit are that no direct connection to the receiver is required, that it may be employed with both transistor and valve sets having an i.f. between 450 and 475 kc/s, and that complete isolation is given if the receiver has a chassis which is connected to one side of the mains supply.

A secondary feature, and one which may appeal to the more experimentally minded, is that only two connections are needed to the oscillator tuned circuit. Experimenters interested in the arrangement may visualise other applications in which two-terminal connection to an oscillator tuned circuit can be of advantage. Despite the somewhat unusual method of oscillator operation, the circuit requires no more components than would be needed by a conventional oscillator with thermal stabilising.

### The Circuit

The circuit of the add-on b.f.o. unit appears in Fig. 1. In this dia-

gram the oscillator tuned circuit consists of the parallel combination of  $L_1$ ,  $C_1$  and  $C_2$ . Feedback from the collector to the base occurs via this tuned circuit and  $C_3$ , and the tuned circuit provides the requisite  $180^\circ$  reversal of phase needed between collector and base. A chassis connection (in this case a connection to the metal case which houses the unit) has to be made into the oscillator circuit at some convenient point. In Fig. 1 it is made at the collector itself since this enables the bush of  $C_1$ , which will be common to its moving vanes, to be mounted direct to the metal panel of the unit. It should be noted that the emitter of  $TR_1$  is *not* at the same r.f. potential as the collector. The 1,000pF capacitor,  $C_4$ , in series with the emitter, offers a reactance of about  $350\Omega$  at the frequency of oscillation. Resistors  $R_1$ ,  $R_2$  and  $R_3$  provide stabilising in normal fashion, and have the conventional values associated with thermal stabilising circuits.

Further details concerning the oscillator are given later in this article.

As readers will be aware, a beat frequency oscillator in a superhet receiver operates close to the intermediate frequency, with the result that an audible heterodyne is formed with the i.f. resulting from any received carrier. If the received signal is a c.w. transmission the heterodyne is only given when the carrier is present, whereupon the morse signal is reproduced as an audible tone which is only present when the transmitting key is down. The pitch of the tone may be adjusted by varying the frequency of the b.f.o. In the circuit of Fig. 1 this change in pitch is achieved by  $C_1$ , which offers a limited range of control over b.f.o. frequency. Capacitor  $C_2$  is a fixed silver-mica component having a value around 300 to 350pF, which has to be found experimentally, whilst  $L_1$  is a standard medium wave coil with iron dust core. In the prototype a Denco Miniature Dual-

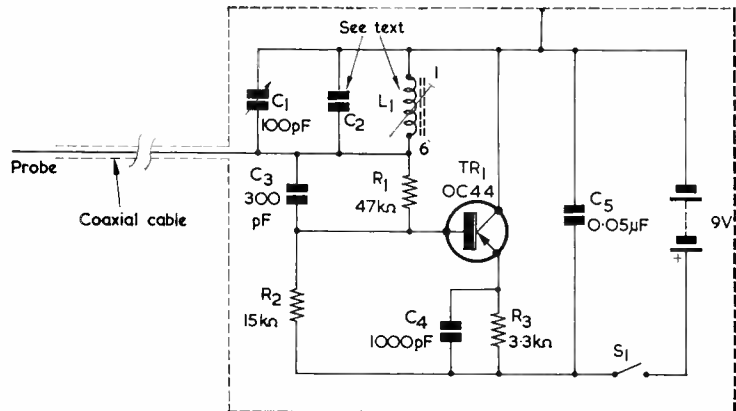


Fig. 1. The circuit of the add-on b.f.o. unit. All components are mounted in a metal case with only the coaxial cable protruding



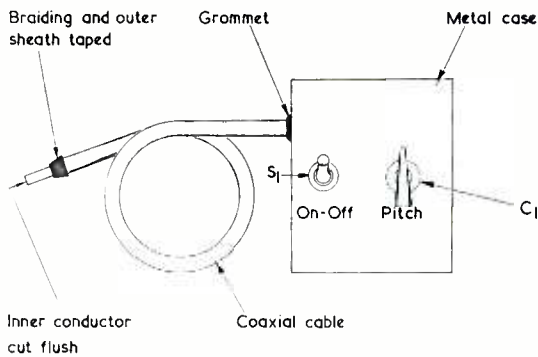


Fig. 2. How the unit may be made up in practical form. Component layout is not critical and if a battery such as the Ever Ready PP3 is used, the metal case can have small dimensions. The unscreened length of centre wire at the end of the coaxial cable forms a probe for coupling the oscillator into the i.f. circuits of the associated receiver

Purpose Coil, Yellow, Range 2, was used here. This is an intervalve coupling coil intended for medium waves and connection was made at pins 1 and 6 to the tuned winding only, the coupling winding being ignored.

Of the remaining components,  $C_3$  should be silver-mica.  $C_4$  can be silver-mica or ceramic, and both capacitors should have a tolerance of  $\pm 20\%$  or better.  $C_5$  may be a paper or plastic foil component. The resistors should have a tolerance of  $\pm 10\%$ , and can be either  $\frac{1}{4}$  watt or  $\frac{1}{2}$  watt.

The whole assembly may be mounted in a metal case, as shown in Fig. 2, from which only the coaxial cable used for coupling into the receiver protrudes. The metal case then provides complete screening for the b.f.o. components.

### Receiver Coupling

Receiver coupling is achieved by simply placing the unscreened centre wire at the end of the coaxial cable close to an anode or grid connection, or to a collector or emitter connection, in the receiver i.f. amplifier stages. A capacitive coupling is then provided. The unscreened centre wire forms a probe and the level of b.f.o. injection, relative to signal strength, varies according to the distance between this probe and the wiring in the receiver, and the stage in the receiver i.f. amplifier at which the coupling takes place. Obviously, b.f.o. injection will be at a higher level relative to signal strength if the probe couples in at an early stage in the receiver i.f. amplifier than at a later stage. Most receivers have

an a.g.c. delay, whereupon optimum b.f.o. injection occurs when the injection level is just below that which overcomes the delay. However, it is a relatively simple matter to obtain a satisfactory injection level, after the unit has been set up, by working from audible results. The anode and grid circuits in valve receivers operate at high impedance and adequate injection will occur with quite loose coupling from the probe. Transistor i.f. stages work at low impedance and fairly tight coupling from the probe will in consequence be needed. It may, in this case, be necessary to have the probe wire run close to an emitter or collector connection in an early i.f. stage. The degree of coupling depends also on the length of unscreened wire forming the probe. For most applications this could be about an inch in length.

The probe end of the coaxial cable is prepared by initially stripping back the braiding and outer sheath so as to leave about 3in of inner insulated wire exposed. The sheath should be neatly cut away by passing a razor blade around the cable, the strands of braiding then being cut back to the same point. The centre wire is next held in a pair of pliers and the centre insulation over it pushed back to cause it to become compressed. The centre wire and its insulation is then cut about an inch from the end of the outer sheath and braiding. The centre insulation may now be eased back to its natural length whereupon it will extend beyond the end of the centre wire and cause it to be completely covered. The end of the outer sheath and

braiding are finally covered with p.v.c. tape to ensure that there is no risk of short-circuits to odd strands of braiding, whereupon the finished cable resembles that shown in Fig. 2. This method of finishing the cable causes both the inner conductor and braiding of the coaxial cable to be covered with insulating material, and the insulation should be adequate to enable the probe to be inserted into the chassis of a working receiver without risk of short-circuits. If further and more reliable insulation is required, the end of the centre lead could also be taped up. *It is essential that this additional tape to the centre lead be applied if the receiver has a chassis which is "live" to one side of the mains.* It will be noted that no connection is made to the receiver chassis.

The coaxial cable may have any convenient length up to about a yard or so. In the b.f.o. unit its braiding is connected to the metal case and its centre lead to the tuned circuit as shown in Fig. 1.

### Setting Up

Setting up takes place after construction has been completed, and it consists of finding the value needed in  $C_2$  which causes the oscillator to run at the intermediate frequency when  $C_1$  is at mid-capacitance. Because of a number of variable factors, the value of  $C_2$  has to be found by experiment. The variable factors include the self-capacitance applied across the tuned circuit by the coaxial cable, the effective capacitance applied across the tuned circuit by other components in the oscillator circuit, and the actual intermediate frequency, in the range of 450 to 475 kc/s, employed in the receiver.

A useful approach is possible if the receiver has a medium wave band. The receiver should be switched to this band and the probe of the oscillator unit loosely coupled into the frequency changer by positioning it close to the signal frequency wiring. The b.f.o. unit need not be completely screened at this stage. Also,  $C_2$  is not fitted but is replaced by a 500pF variable capacitor connected temporarily into circuit by short leads.  $C_1$  is set to mid-capacitance, and the core of  $L_1$  about half way into its coil. The receiver is then tuned to a station at around 400 to 450 metres and the 500pF capacitor adjusted to produce a heterodyne. This will occur with the 500pF capacitor vanes nearly fully open, and establishes the fact that the oscillator is running. The correct heterodyne will be stronger

than any others which may be heard as the 500pF capacitor is adjusted. The receiver is then tuned to a station at a lower frequency (higher wavelength) and the capacitance of the 500pF capacitor increased to produce the heterodyne again. This process is repeated until the last station at the low frequency end of the medium wave band is reached. The receiver is then kept tuned to this station and the 500pF capacitor further increased in value until another strong heterodyne is formed. This will be given by the b.f.o. running at intermediate frequency and can be confirmed by the fact that heterodynes are now given on *all* stations tuned in on the medium wave band of the receiver.

If the constructor has a capacitance bridge, the value of the 500pF capacitor may then be measured and a fixed capacitor of the same value fitted in the  $C_2$  position. In the absence of a bridge, known fixed capacitors may be connected across the temporary 500pF capacitor, proceeding in "steps" of, say, 100pF, then 50pF, 20pF and so on, until the required capacitance has been "built up" and causes the b.f.o. to run at desired frequency with the 500pF capacitor disconnected. These fixed capacitors may then be replaced by a single capacitor equal to the

sum of their values, this being permanently wired into the  $C_2$  position. Any final adjustments which may be needed, as would occur when the probe unit is completely screened, should be within the range of the iron dust core of the coil. It should be added that the use of a temporary 500pF variable capacitor in the manner just described is very helpful because it first of all assures the constructor that the oscillator is operating at intermediate frequency, and it obviates the risk of setting up the oscillator at an incorrect frequency.

After the unit has been set up, the probe may be inserted into the receiver i.f. amplifier circuits as described above.

#### Oscillator Operation

Some further points concerning the oscillator, and which are not necessarily applicable to the present design, may be of interest. The fact that only two connections are needed for the tuned circuit can be of advantage in some applications. A disadvantage of the circuit is that oscillator components external to the tuned circuit cause additional capacitance to appear across it. These external components are  $C_3$  and  $C_4$  which, due to the forward-conducting base-emitter junction of  $TR_1$ ,

add capacitive reactance across the tuned circuit. In consequence, a wide tuning range with the aid of a variable capacitor is not feasible, since it is impossible to obtain a low value of minimum capacitance in the tuned circuit. With the values for  $C_3$  and  $C_4$  shown in Fig. 1, the tuned circuit behaves as though an effective capacitance of about 100pF were connected permanently across it.

The circuit was checked with two transistors type OC44. With one transistor the circuit continued to oscillate at battery voltages down to 1.4 but, with the second transistor, it ceased to oscillate at 2.3 volts. As a result, it was felt that the supply voltage of 9 specified in Fig. 1 should be more than adequate to cope with all OC44's likely to be encountered. The constructor may, however, reduce this supply voltage to 4.5 or 3 if he desires, provided that the particular OC44 employed oscillates reliably at such voltage.

The coil employed in the  $L_1$  position should not be critical and any iron-dust cored medium wave coil of reasonable Q should function satisfactorily. The writer checked the circuit with a medium wave ferrite rod aerial winding, and found no change in operation.

The current drawn by the prototype with a 9 volt supply was 0.8mA.

---

## Recent Publications

**FOULSHAM-SAMS POCKET DICTIONARY OF COMPUTER TERMS.** Compiled by the Howard W. Sams Technical Staff. 98 pages, 4 x 6½ in. Published by W. Foulsham & Co. Ltd. Price 10s. 6d.

This dictionary is of very convenient size for the pocket and contains some 1,000 words and terms, each having a definition taking up about one to three dozen words. Also included are several truth tables to illustrate particular terms. After the dictionary section proper, seven pages are devoted to abbreviations and acronyms, together with a list of computer manufacturers and their addresses.

In common with other titles in the Foulsham-Sams Technical Books series, this book has an American text with a short introductory chapter for English readers. This point is reflected in the fact that all the computer manufacturers listed are American.

The computer field is expanding at an almost fantastic rate, and new words are being continually coined as development proceeds. Any permanent record of such terms offers, therefore, a long-term advantage, especially in the prevention of future ambiguity. It should be noted that the dictionary under review deals with American terminology which is, in nearly all cases, common to English usage. The definitions are concise and to the point, and there are extensive cross-references. This will be a helpful book for the newcomer to computer work.

**ABC'S OF ELECTRONIC ORGANS.** By Norman H. Crowhurst. 102 pages, 5½ x 8½ in. Published by W. Foulsham & Co. Ltd. Price 16s.

This book, which also appears in the Foulsham-Sams Technical Book series, deals with electronic organs at a fairly elementary level.

The first chapter discusses the nature of music and takes the reader from pipe organs to a general description of modern electronic organs. Chapter 2 covers sound synthesis as provided, for instance, by tone wheels or reeds, and also deals with square waves, sawtooths, vibrato, percussion and sustain. The third chapter gives brief details of electronic organ fundamentals at block diagram level, whilst the fourth covers organ mechanics with details drawn mainly from commercially made instruments. Chapter 5 is entitled "Choosing An Organ", and uses examples of American manufacture. The next chapter has some 15 pages on organ electronics, and includes basic circuits for transistor, valve and neon tone generators, for keying and vibrato, and for swell control. The final chapter deals with maintenance and trouble-shooting and is followed by a glossary of terms applicable to organs.

# TAPE RECORDER TUNER

by G. MAYNARD

*This simple receiver will give good medium wave reception for application to a tape recorder. It may also function as a headphone receiver in its own right. An optional feature is the provision of a jack socket for an external battery*

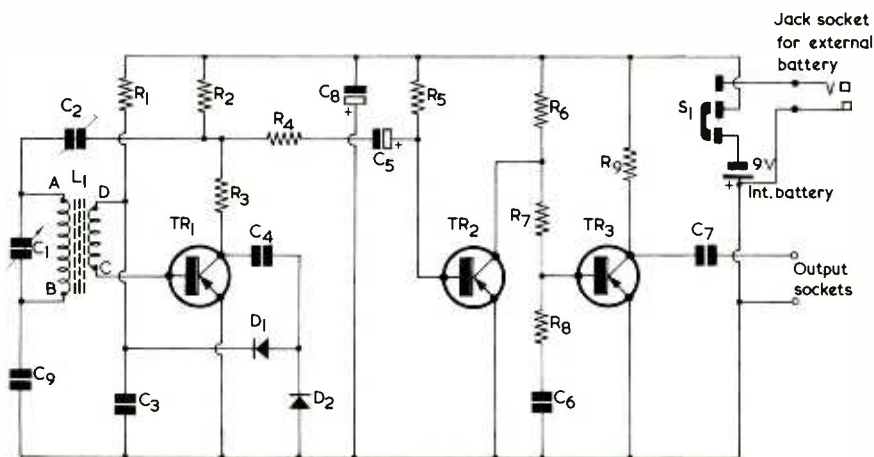


Fig. 1. The circuit of the tuner unit

## Components List

N.B. As is described in the text, some components may not be needed if the 2-transistor version is built.

### Resistors

(All resistors  $\frac{1}{10}$  watt 10%)

- R<sub>1</sub> 220k $\Omega$
- R<sub>2</sub> 1k $\Omega$
- R<sub>3</sub> 1k $\Omega$
- R<sub>4</sub> 10k $\Omega$
- R<sub>5</sub> 220k $\Omega$
- R<sub>6</sub> 3.9k $\Omega$
- R<sub>7</sub> 100k $\Omega$
- R<sub>8</sub> 22k $\Omega$
- R<sub>9</sub> 1k $\Omega$

### Capacitors

- C<sub>1</sub> 500pF variable, solid dielectric (see text)
- C<sub>2</sub> 250pF trimmer
- C<sub>3</sub> 0.02 $\mu$ F ceramic disc
- C<sub>4</sub> 250pF silver-mica or ceramic
- C<sub>5</sub> 10 $\mu$ F electrolytic, 9V wkg.

- C<sub>6</sub> 0.01 $\mu$ F ceramic disc
- C<sub>7</sub> 0.1 $\mu$ F paper or polyester
- C<sub>8</sub> 500 $\mu$ F electrolytic, 9V wkg.
- C<sub>9</sub> 60pF silver-mica or ceramic (see text)

### Semiconductors

- TR<sub>1</sub> OC44
- TR<sub>2</sub> OC71
- TR<sub>3</sub> OC71
- D<sub>1</sub> OA71
- D<sub>2</sub> OA71

### Inductor

- L<sub>1</sub> Ferrite aerial with feedback winding (see text)

### Switch

- S<sub>1</sub> d.p.d.t. slide switch

### Miscellaneous

- Output sockets
- Jack socket and plug (see text)
- 9-volt battery type PP3 (Ever Ready)



THE WRITER ENJOYS GOOD QUALITY MUSIC AND frequently makes tape recordings of broadcast programmes. Originally, the tape recorder microphone was held near the radio receiver loudspeaker, but an obvious lack of fidelity resulted from this method of recording. Also, it was impossible to stop people coming into the room and spoiling the recording just when it was reaching its most important point!

This provided the motive for constructing the tuner described here. The design is versatile and the tuner can be employed as a 2-transistor unit, or as a 3-transistor unit with bass boost. It may feed high impedance headphones instead of the tape recorder, if desired, and an optional jack socket can be fitted for running from an external battery.

A reflex circuit is employed, and this obviates the alignment problems necessary with a superhet.

### The Circuit

The circuit of the receiver, in its 3-transistor form is given in Fig. 1.

The tuned signal is applied to the base of TR<sub>1</sub> via the coupling coil, CD, and is amplified at r.f. The amplified r.f. signal appears at the collector of TR<sub>1</sub> and some of this is fed back to the tuned coil, AB, via R<sub>3</sub> and C<sub>2</sub> to provide regeneration. The output from the collector of TR<sub>1</sub> is fed to the detector circuit, D<sub>1</sub> and D<sub>2</sub>, by way of C<sub>4</sub>, and the detected signal is next fed back to the base of

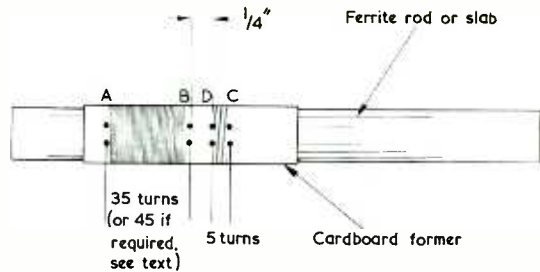


Fig. 2. Details of the ferrite aerial windings

TR<sub>1</sub> through the coupling coil CD. The amplified a.f. signal at the collector of TR<sub>1</sub> is passed to the base of TR<sub>2</sub> via R<sub>3</sub>, R<sub>4</sub> and C<sub>5</sub>. The signal is amplified by TR<sub>2</sub> then taken through a bass boost circuit given by R<sub>7</sub>, C<sub>6</sub> and R<sub>8</sub>, to the base of TR<sub>3</sub>. Resistors R<sub>6</sub> and R<sub>7</sub> provide base bias for TR<sub>3</sub>. The amplified a.f. signal at the collector of TR<sub>3</sub> is finally passed to the output sockets via C<sub>7</sub>.

In most reflex circuits a choke would be used instead of R<sub>3</sub>, whilst C<sub>2</sub> would have a much smaller value and it would be directly coupled to the collector of TR<sub>1</sub>; but the writer feels that these arrangements make the circuit more critical than the design shown here.

Another point worth noting is the presence of R<sub>4</sub>. Without this resistor no reaction could take

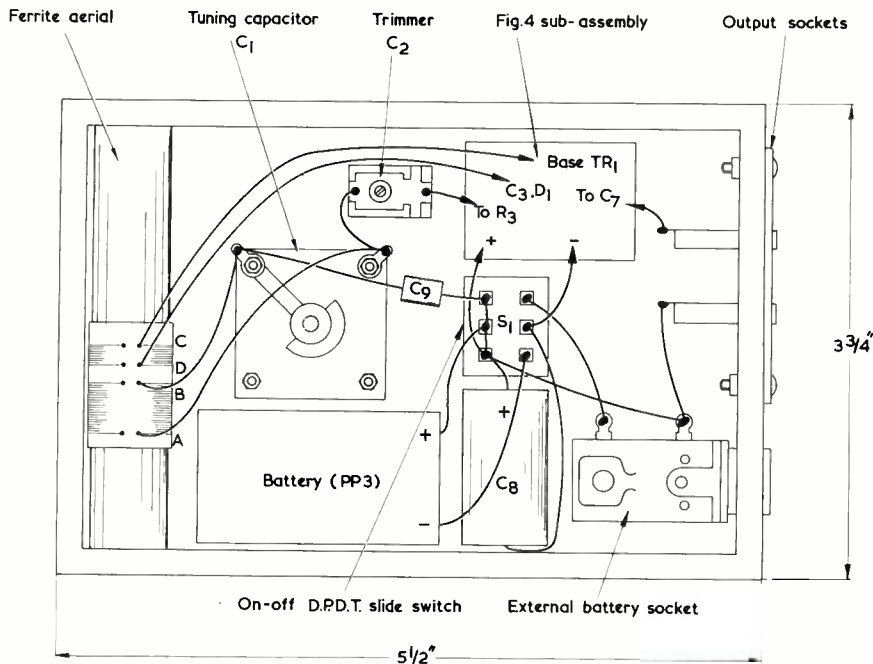


Fig. 3. The layout employed in the author's receiver for the larger components

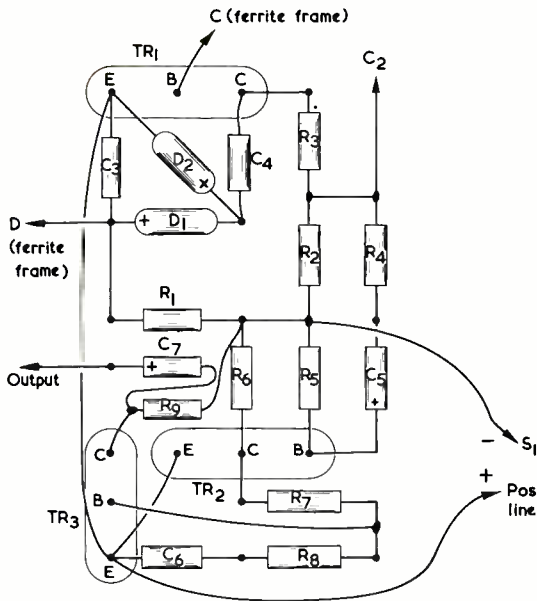


Fig. 4. The smaller components are fitted to a piece of Paxolin, making up a sub-assembly with the layout shown here. Note that the connection point for the collector of TR<sub>2</sub> is between the connection points for the emitter and base. With TR<sub>1</sub> and TR<sub>3</sub> it is the connection point for the base which is in the centre

place, since much of the feedback signal would be passed to the positive line by way of C<sub>5</sub> and TR<sub>2</sub>.

No stabilisation is employed for any of the transistors, and no trouble has been experienced, over a considerable period of use, from thermal runaway or any similar effects.

If the constructor is interested in economy, the design may employ TR<sub>1</sub> and TR<sub>2</sub> only. R<sub>7</sub>, C<sub>6</sub>, R<sub>8</sub>, R<sub>9</sub> and TR<sub>3</sub> may then be omitted, C<sub>7</sub> connecting directly to the collector of TR<sub>2</sub>.

The small internal battery has a working life of at least 2 months but a saving can still be made, if desired, by using a large external battery when, for instance, the receiver is operated at home. When slide switch S<sub>1</sub> is set to disconnect the internal battery, it connects the negative line to the jack socket. If a jack plug connected to an external battery is then applied, the receiver will function from that battery. It should be noted that, with some jack sockets, a momentary short-circuit of the jack plug may occur when it is inserted. In consequence, the connections to the terminal clips of the external battery should only be completed after the plug has been inserted. The negative terminal of the external battery connects to the jack plug tip and its positive terminal to the jack plug sleeve. If the external battery facility is not required the jack socket can be omitted, whereupon S<sub>1</sub> functions as a simple on/off switch.

C<sub>9</sub> is included to obviate a breakthrough effect which is liable to occur when the output of the unit is connected to mains-driven equipment. Without this capacitor, connection to the mains equipment can result in excessive pick-up of local signals by way of the mains wiring. However, the low capacitance of C<sub>9</sub> prevents this effect and gives a considerable increase in selectivity. If the unit is to be used only as a receiver, without any connections to mains-driven equipment or to any other external wiring, C<sub>9</sub> may be omitted. The lower terminals of C<sub>1</sub> and winding AB then connect directly to the positive supply line.

The prototype picked up many stations, both home and Continental. When used as a receiver, acceptable results are given with an earpiece having an impedance of 1kΩ or more.

### The Ferrite Aerial

Details of the ferrite aerial are shown in Fig. 2. The author employed a ferrite slab measuring 2½ x ¾ x ¼ in, but a short rod of approximately similar dimensions would also cope. The tuned winding, AB, has 35 turns, close-wound, of 36 s.w.g. enamelled wire, this being suitable for medium wave coverage with a 500pF tuning capacitor in the C<sub>1</sub> position. A 200pF tuning capacitor may also be used, in which case winding AB should have 45 turns. A slight adjustment in the number of turns may be required for ferrite rods or slabs having dimensions markedly different from the slab used by the author. Some adjustment of inductance is also, of course, given by sliding the coil along the ferrite core. Winding CD consists of 5 turns of 36 s.w.g. enamelled wire close-wound, spaced about ¼ in from winding AB. Both coils are wound on a cardboard former giving a sliding fit over the ferrite core. The letters A, B, C and D in Fig. 2 indicate coil terminations, and correspond to the same letters in Fig. 1.

### Construction and Testing

The writer built the prototype 3-transistor version in a cigar box using the general layout shown in Fig. 3. This layout may be modified, as desired, to suit alternative cases or components of different size. The semiconductors, resistors and most of the capacitors were fitted to a sub-assembly having the component layout shown in Fig. 4. This sub-assembly employed a small sheet of Paxolin to which the parts were secured and, by using miniature resistors and capacitors, the writer's version measured only slightly more than 1 x 1½ in. However, there is no necessity to make the sub-assembly as small as this, and some constructors may favour a more open layout on a larger piece of Paxolin.

Fig. 3 shows the wiring to the sub-assembly, and it includes the optional jack socket for the external battery mentioned earlier. The writer used a double pole slide switch for S<sub>1</sub>, the three unused tags being connected together and employed as anchor tags for the positive supply line connections.

When soldering the semiconductors or miniature components (if used) always use a heat shunt such as a pair of long nosed pliers. Never cut the transistor wires too short because, apart from the risk of overheating during wiring, it may be impossible later to unsolder them without damage.

After completion, make a careful check of the wiring before switching on. To test if the receiver is working, touch the base of TR<sub>1</sub> with a screwdriver

against whose blade a finger is held. This should cause a click to be heard in the headphones connected to the output (or in an amplifier speaker if the unit is coupled to an amplifier). Rotate the tuning capacitor until a station is heard, then increase the value of C<sub>2</sub> until more stations can be tuned in. Next, select a station at the high frequency end of the band, such as Luxembourg, and adjust C<sub>2</sub> until the receiver is just on the point of oscillation. The tuner is then ready for permanent use.

**BUY**

**THE Radio Constructor**

**REGULARLY**

AND BUILD SOME OF THE FASCINATING DESIGNS  
FEATURED EACH MONTH

SEPTEMBER ISSUE INCLUDES THREE SPECIAL FEATURE ARTICLES —

- ★ *VHF/FM Feeder Unit*
- ★ *12V Adding Machine*
- ★ *Radio Control Receiver*

On Sale 1st September      Price 2/6

**THE Radio Constructor**

**MAKE SURE  
OF YOUR COPY**

— hand this form  
to your newsagent  
today!

To .....

(Name of Newsagent)


Please reserve/deliver the September issue of THE RADIO CONSTRUCTOR (2/6), on sale September 1st, and continue until further notice.

NAME .....

ADDRESS .....



# NEWS . . . AND .

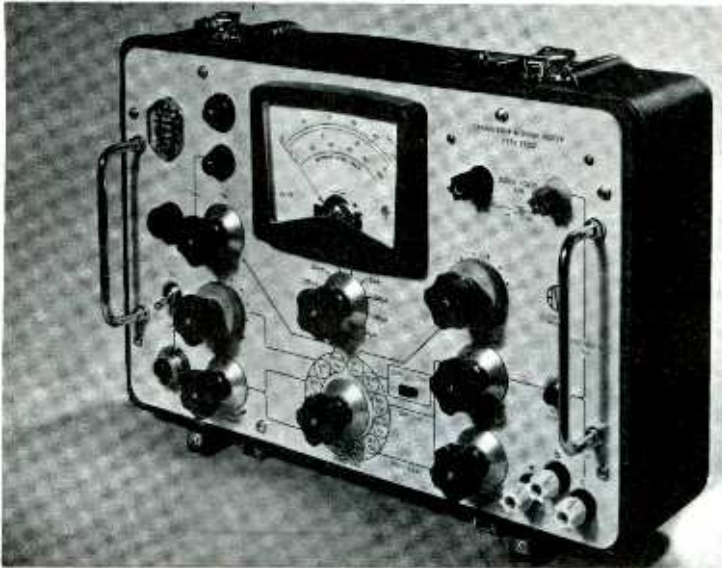

## Transistor and Diode Tester Type TT537

The Avo Transistor and Diode Tester type TT537 provides, in one instrument, facilities for both transistor and diode testing. The tester is a compact, simple to operate, direct reading instrument providing an accurate and convenient method for the measurement of transistor and diode characteristics.

Provision is made for the rapid and accurate measurement of transistor  $h_{fe}$  up to 1,500 at a frequency of approximately 1 kc/s and the measurement of leakage current with a first indication of  $1\mu A$  for both p.n.p. and n.p.n. low medium power germanium or silicon transistors.

Both the forward and reverse characteristics of diodes can be measured, the reverse characteristics at voltages up to 1,000V under current limiting conditions.

The design of the instrument enables accurate measurements to be made with the minimum of adjustments and setting-up. The layout of the panel controls is such that operation of the instrument, which centres around a function switch and a transistor diode selector switch is largely self-explanatory. The panel markings are colour-coded and these features together with the protective devices incorporated in the instrument provide an ideal tester for use not only by engineers and technicians but also by unskilled personnel.

---

## Announcement from Denham & Morley Ltd.

Tate Electronic Services Limited have been appointed Service Agents for servicing in and out of guarantee mains radios distributed by Denham & Morley Limited. Depots who will accept service are: The Grange, Hoole Road, Hoole, Chester. 31 Chapel Street, Halton, Leeds. 44a New Chester Road, Rockferry, Nr. Birkenhead. 21 Crossgates, Durham. Mandervell Road, Oadby, Leicester. Vicar Street, Sedgley, Staffordshire. 3 Waterloo Road, Stockport. The Green, Chorlton-cum-Hardy, Manchester 21.

## Self Binders

Our advertisement columns contain details of a new type of self-binder available for those who like to retain their copies of *The Radio Constructor* in good condition.

These self-binders are quite the best that we have seen. They are immensely strong, most attractive in appearance and delightfully simple in the ease with which copies can be inserted or removed. This latter is achieved by the use of especially constructed binding cords made from Super Linen very hard twisted and twice doubled attached to strong rustless springs.


We can recommend these binders with every confidence

---
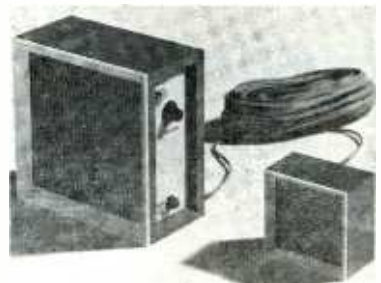
## New Baby Alarm

An intercom system with the great advantage of two-way communication is being produced as a baby alarm by Rovex Scale Models Ltd. Being a two-way system, mother can reassure her child without being disturbed or having to go to its nursery.

The Tri-onic baby alarm is battery operated and transistorised in a neatly designed modern housing made of polystyrene which is assembled with the aid of adhesive developed to give maximum efficiency with this material. The special adhesive used is one of a range of custom made adhesives supplied by BX Plastics Ltd. of Manningtree, Essex under the trade name Bexol.



The new baby alarm by Rovex Scale Models Ltd.

# COMMENT

## World Championships for Control Line Model Aircraft

Our many readers interested in radio control should find the above event of absorbing interest for, in addition to the championships, there will be the attraction of aerobatic displays in jet aircraft by pilots of the R.A.F.

The Royal Air Force, through its Technical Training Command station, R.A.F. Swinderby, near Lincoln, will be host from 26th to 30th August to the World Championships for Control Line Model Aircraft, for which 17 nations ranging from the U.S.S.R. to the U.S.A. have already entered, and for which entries are expected from a further 12 ranging from Japan to Monaco.

This will be the first time that world control line championships, of which the Duke of Edinburgh is 1966 Patron, will have been held in England, and the first time in which they will have been held on a fully-equipped Service airfield, with the variety of amenities and facilities which an R.A.F. station can provide.

Some 280 competitors, managers and others will be housed and fed at R.A.F. Swinderby, home of No. 7 School of Recruit Training, with the R.A.F. Model Aircraft Association handling the organisation jointly with the sponsor of the event, the Society of Model Aeronautical Engineers. Air Marshall M.K.D. Porter, Air Officer Commanding-in-Chief, R.A.F. Maintenance Command, is president of the R.A.F.M.A.A., and Air Vice-Marshal B.A. Chacksfield, Commandant-General, R.A.F. Regiment, is president of the S.M.A.E.

The Championships will open with a flying display to include formation aerobatics by the aerobatic team from No. 1 Flying Training School, R.A.F. Linton-on-Ouse, Yorkshire, flying Jet Provosts, solo aerobatics in a jet fighter, gliding aerobatics by a pilot of the R.A.F. Gliding and Soaring Association, and possibly a display by the "Sky Divers", the Army's parachute display team. Cadets of the Northumberland Wing, Air Training Corps, will be helping in various ways with the organisational side. There will be a large static exhibition of models in a hangar, including those of the famous Peter Farrar Collection from Exeter. All proceeds from the admission charge to the exhibition will go to the R.A.F. Benevolent Fund.

The countries already entered—the U.S.S.R.'s party of over 16 will be the largest contingent—are Belgium, Canada, Czechoslovakia, Denmark, Eire, Finland, France, Great Britain, Holland, Hungary, Israel, Poland, Sweden, U.S.A., West Germany, and Yugoslavia. Countries from which entries are still awaited are Austria, Bulgaria, Italy, Japan, Luxembourg, Monaco, Norway, Portugal, Roumania.



### Wirewound Potentiometers for Printed Circuits

W. Greenwood (London) Limited have introduced a new wirewound adjustment potentiometer specifically designed for direct mounting on to printed circuit boards.


This precision component is a single turn potentiometer with outstanding humidity performance. It has a power rating of 1.5 watts at 50°C. and is available in a resistance range from 10Ω to 50Ω. The solder pins are gold plated.

The principal features of this potentiometer are: side mounting unit for printed circuit boards, screwdriver adjustment for accurate self-locking electrical settings, outstanding humidity performance, precious metal contacts, nickel and goldplated solderpins, stops provided at each end of travel, excellent shock and vibration stability. The potentiometer is one of a comprehensive range manufactured by Contelec from Switzerland.
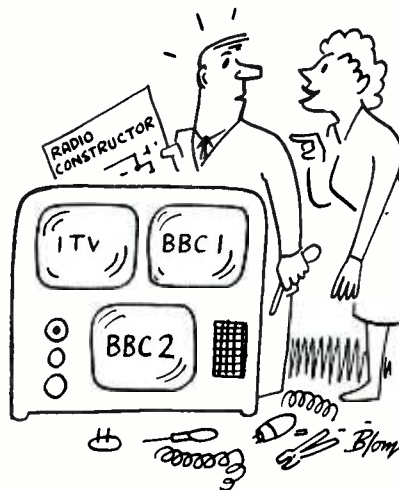
### Company Name Change

To bring the company name into line with its product range, the name of Standard Telephones and Cables (Transistors) Limited has been changed to S.T.C. Semiconductors Limited.

The company is the newly formed subsidiary of S.T.C. in which the semiconductor operations at Footscray, Kent, and Harlow, Essex, are now consolidated. Its product range covers transistors, integrated circuits, signal diodes, silicon rectifiers, Zener diodes and thyristors.



"... Any Pirate TV?"

# Modifications to the

# CR100

by W. STUDLEY


*Some simple modifications which can be carried out on the CR100 and similar receivers*

MANY AMATEUR AND SHORT WAVE LISTENING stations are equipped with Marconi CR100/B28 receivers. These receivers offer good value for money and can do an excellent job even in these so called "modern days" of high QRM and QRN levels! One criticism fairly aimed at the CR100, however, is that it tends to drift, since no stabilised h.t. supply for either the b.f.o. or local oscillator is fitted. The problem of local oscillator drift does not normally cause much inconvenience in practice and is simply overcome if the receiver is switched on for some time prior to operation. It is with the b.f.o. that the drift problem is most serious, because this is normally only switched in for c.w. or for s.s.b. reception and no preliminary running period can take place. Drift in the b.f.o. is particularly aggravating when attempts are made to resolve s.s.b. as constant resetting of the b.f.o. control is needed. Due to this factor it is not unusual for most of an "over" to be missed completely, and such a state of affairs is intolerable.


Stabilising the h.t. supply to the b.f.o. is, therefore, essential. Fortunately, this can be done fairly easily without any serious alterations to the receiver.
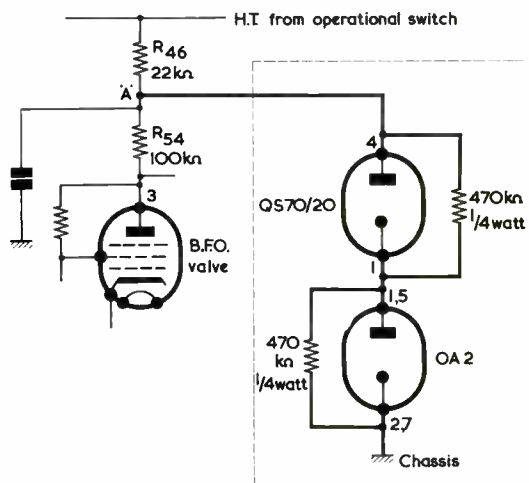
### Stabilising the BFO Supply

Normally, h.t. is applied to the b.f.o. valve when the operational switch is set to either "CW—AVC" or "CW—MAN". Referring to Fig. 1(a), resistor  $R_{54}$  ( $100k\Omega$ ) is the b.f.o. valve anode load resistor and  $R_{46}$  ( $22k\Omega$ ) the decoupling resistor. A voltage slightly in excess of 220 should appear at the junction of these two resistors, and series connected voltage stabilisers may be connected to this point as is indicated by the heavy lines. It should be noted that if the d.c. potential at point "A" in the diagram is reduced overmuch, inadequate b.f.o. injection might result. Whilst this may not



(a)

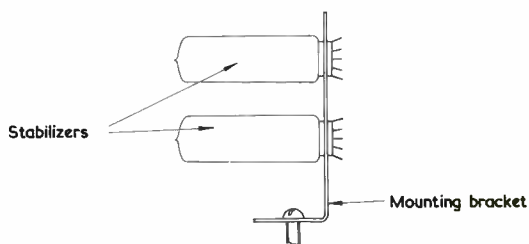

(b)

Fig. 1(a). Adding an h.t. stabilising circuit to the b.f.o. The additional circuit is shown in heavy line (b). Mounting the stabiliser valves



be serious with c.w. reception, when s.s.b. signal are sought, difficulty will be experienced in reading them unless the r.f. gain is retarded excessively. The b.f.o. output needs to be as large as is conveniently possible and the use of a single stabiliser tube is thus ruled out. A single OA2 for example, would only permit a potential of some 150 volts to appear at point "A", and this may be considered inadequate as has been found by experiment. By using the two tubes specified, however, little difficulty will be experienced.\*

### Mechanical Details

If the CR100 is turned upside-down and its base plate removed it will be found possible to mount a small sub-chassis at the rear of the b.f.o. screening can. The B7G valveholders for the stabilisers are fitted to a small L-shaped piece of aluminium as indicated in Fig.1(b). This sub-chassis is wired beforehand and fitted with a flying lead for connection to point "A", the connection to chassis being made automatically when the assembly is bolted in position. The underside of the assembly—the pins of the tubes—should face the panel. Looking at the receiver chassis from the front, a strip carrying seven vertically mounted resistors and a capacitor will be seen along the left-hand side. The flying lead from the added sub-chassis should be connected to R<sub>46</sub> the second resistor from the front panel (22kΩ), on the side more difficult to get at; i.e., the end of the resistor nearer the receiver chassis underside surface.

To test the modification set the Operational switch to "MOD—AVC". With the receiver switched on both stabiliser tubes should remain dead, but they should glow when the Operational switch is adjusted to "CW—AVC" or "CW—MAN".

### Adding Side-tone/Muting Facilities

The CR100 and other receivers not equipped with side-tone and muting facilities can easily be adapted, although the modification is only normally required when a transmitter is to be used close by. The "front end" of a receiver not suitably operated can be heavily overloaded if left running whilst a transmitter tuned to the same frequency is radiating nearby (as occurs at amateur stations) and damage can result. For this reason it is advisable either to mute the receiver completely, perhaps by switching it off manually on "Transmit" (and the CR100 does have a "Stand-by" position accommodated on the Operational switch) or to silence it via a relay operated automatically by the transmitter. Partial and automatic muting is even better, for the operator may then monitor his own signals via the receiver when

\* The OA2 has a burning voltage of 150 and the QS70/20 a burning voltage of 70, and it might be considered that these would not strike reliably when the voltage at point "A" is of the order of 220 volts only. However, the author confirms that the stabilisers work excellently and never fail to strike in the CR100 modified by himself. Should difficulty be experienced in this respect, R<sub>46</sub> could be reduced in value by connecting another 22kΩ resistor across it. The position of R<sub>46</sub> in the chassis is discussed later in the text.—Editor.

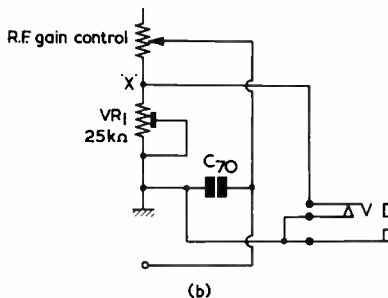
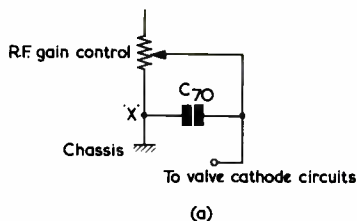


Fig. 2(a). The existing r.f. gain control circuit.  
(b). Adding a preset gain control (VR<sub>1</sub>) to give side-tone and muting facilities. The additional control is only brought into circuit when a plug is inserted in the jack

phones are in use. One practical system which can be adopted is illustrated in Fig. 2, where the existing r.f. gain control is shown connected to chassis at point "X", as in (a). By lifting the earthy end of the r.f. gain control from chassis and fitting a closed-circuit jack socket and a 25kΩ preset potentiometer, as in (b), it is clear that nothing is functionally until a jack plug is inserted, whereupon extra resistance due to VR<sub>1</sub> is introduced. If the leads to the jack plug are connected to a relay energised and operated by the transmitter, VR<sub>1</sub> can be switched in and out of circuit automatically via the "Transmit/Receive" switch. The relay contacts should be open during "Transmit". The effectiveness of VR<sub>1</sub> is determined by its precise resistance setting, and it should be adjusted so that when the associated transmitter is operating, the receiver passes sufficient signal for monitoring purposes. It should be added that a circuit of this type is already fitted to the CR100/2 which does not, in consequence, require altering.

### Practical Modification

Fitting the additional items to a CR100 is simple. First remove all knobs and the front panel. Locate the earthy end of the r.f. gain control and disconnect the lead to this tag. Potentiometer VR<sub>1</sub> may then be mounted on the tuning capacitor frame, or nearby, by means of a small L-shaped bracket in such a position that its control shaft points upwards towards the lid of the receiver for subsequent adjustment

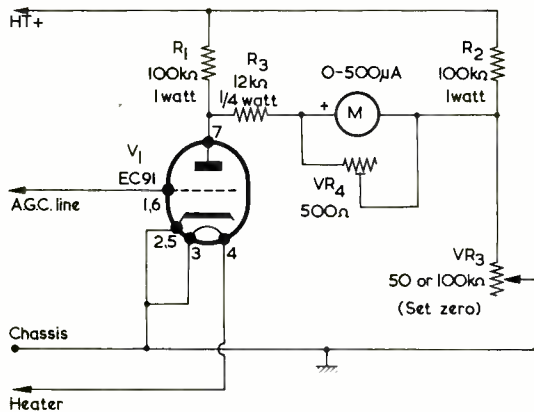


Fig. 3. An add-on circuit which enables a forward-reading S-meter to be incorporated

purposes. At the rear of the chassis a suitable point for locating the closed-circuit jack socket exists alongside the aerial connector. A single lead is then run from the jack to point "X" of Fig. 2(b) and VR<sub>1</sub> and the r.f. gain control wired appropriately. The receiver will now function as if unmodified in this respect, until switching due to an external transmitter-controlled relay is introduced via the jack.

#### Adding a Signal Strength ("S") Meter

Although S-meters are normally calibrated rather arbitrarily, they tend to give only approximate indications of received signal strength. They are, however, very useful aids when tuning or netting. Some operators rely on their S-meters more than others but it is thought that a great many of the "S" reports heard over the air have been aurally rather than visually assessed. Even so, an S-meter is of definite value, provided the limitations of the device are appreciated, at both amateur and s.w.l. stations.

There are various ways of adding an S-meter to a receiver, the usual plan being to sample the a.g.c. line voltage and use it to deflect the pointer of a meter. To avoid interfering with receiver constants excessively a small "add-on" type of meter actuating circuit is suggested, and a suitable bridge-type, forward-reading circuit is shown in Fig. 3. Here, under no signal conditions, V<sub>1</sub> passes a current through R<sub>1</sub>, and the potential appearing at the anode of the valve is balanced out by the adjustable potentiometer circuit given by R<sub>2</sub> and VR<sub>3</sub>. Provided VR<sub>3</sub> is correctly adjusted, the result is that the meter pointer remains at zero. If, now, the potential at the valve grid goes negative due to reception of a signal, the current passed by the valve falls and the potential at its anode goes positive, resulting in a deflection of the meter pointer. The amount of deflection depends on the negative potential applied to the valve grid

and it follows that, by connecting this directly to the receiver a.g.c. line, changes in signal strength may be indicated by the meter. The fact that no grid resistor is shown in Fig. 3 is of no consequence, for the a.g.c. diode load resistor provides the necessary return circuit to chassis.

Preset resistor VR<sub>4</sub> is a meter sensitivity control, and enables full-scale deflection to correspond to the strongest signal it is anticipated will be received.

#### Modification Details

The EC91 valve is on the B7G base and it is an easy matter to build the oddment of added circuitry shown in Fig. 3 on a small L-shaped sub-chassis equipped with three colour-coded flying leads, the fourth (chassis) lead connection being automatically made when the assembly is mounted.

In the CR100 a small assembly can, with care, be contained under the chassis in the i.f. stages compartment that runs along the right-hand under-side, looking from the front. The heater fly-lead can be soldered to pin 2 of V<sub>5</sub> and the h.t. fly-lead to the receiver h.t. positive lead where it connects to R<sub>21</sub>, the screen-grid feed resistor for V<sub>5</sub>.

With the receiver switched off, locate R<sub>4</sub> (47kΩ), which is the second resistor from the front on the right hand side of the chassis (chassis upside-down and knobs to the front). R<sub>4</sub> is the a.g.c. feed resistor for V<sub>5</sub> and it connects, via the second i.f. transformer, to the top cap of V<sub>5</sub>. Confirm this point with an ohmmeter. The end of R<sub>4</sub> remote from the i.f. transformer (which will, of course, measure 47kΩ to the top cap of V<sub>5</sub>) connects to the main a.g.c. line and should show a resistance of approximately 1MΩ to chassis when the Operational switch is in one of the two "AVC" positions, and zero resistance to chassis when the switch is in either "MAN" position. Having confirmed these points, connect the flying lead from pins 1 and 6 of the EC91 to the end of R<sub>4</sub> remote from the i.f. transformer (as just determined).

The meter movement itself may be mounted to the left of the main tuning dial and VR<sub>3</sub> may be located on the panel between the r.f. gain control and the tuning knob. If maximum S-meter indications are required it is beneficial to reduce the a.g.c. delay voltage, and this can be done by short-circuiting the 10kΩ resistor connected between the earthy end of the volume control and the chassis.

#### Testing the S-meter

With the receiver switched on and the Operational switch set to "MOD-AVC", VR<sub>3</sub> should be adjusted to give a zero meter reading when no aerial is connected. Immediately the aerial is connected and the r.f. gain advanced any signal tuned in should cause the S-meter pointer to move in the full-scale direction. If a commercial transmission is sought somewhere near the 40-metre band, where signal strengths tend to vary rather widely, the effectiveness of the S-meter may be

assessed. The effect of the receiver aerial trimmer, the r.f. gain control and any externally used tuning

unit will also be observable and it will soon be appreciated how useful the added S-meter can be.

# Comprehensive Volume Control Circuit

by SIR DOUGLAS HALL  
K.C.M.G., M.A. (Oxon.)

*The provision of an adequate volume control in straight and reflex receivers is not a simple matter. This article describes a comprehensive circuit which allows a single potentiometer to control regeneration, r.f. gain and a.f. gain*

**A**LTHOUGH THE SUPERHET CIRCUIT is a good deal more complicated than most straight or reflex circuits, manual volume control is easier to design as the large amount of r.f. and i.f. amplification allows for the use of a considerable amount of automatic control. Manual control can be looked after by a simple potentiometer in the a.f. section.

Most straight and reflex circuits rely to a fair extent on reaction to provide the necessary amplification of weak signals. With some designs, reaction is fixed and a.f. volume control is used, as with superhets; but this often results in loss of sensitivity at some points on the tuning scale, and throughout the scale as the battery ages. Others rely on a variable reaction control, alone, to regulate volume. But with this arrangement it is often impossible to reduce volume satisfactorily when a powerful local station is being received. This difficulty applies with greater force when there is a good deal of high frequency amplification in addition to reaction. For satisfactory control in these circumstances it is preferable for a single control to regulate both reaction and some other form or forms of amplification used by the circuit. A possible solution is to apply pre-set reaction and control the voltage available for either the base or the collector of the transistor in the reaction circuit. But this is not ideal as it can result in overloading and bad volume stability at low volume

settings, and there is sometimes interaction with the tuning control when critical reaction is used on weak signals.

## A New Approach

Fig. 1 shows, in skeleton form, the circuit of a t.r.f. receiver employing TR<sub>1</sub> as a tuned radio frequency amplifier, TR<sub>2</sub> as a detector or reflex amplifier, and TR<sub>3</sub> as a transformer coupled a.f. amplifier. There would probably be a further a.f. stage or stages. VR<sub>1</sub> is the volume control, and to start with we may consider only that part of its track which lies between the slider and the end connected to the reaction coil, L<sub>2</sub>. As there is a winding offering high im-

pedance at a.f. in the output of TR<sub>2</sub>, C<sub>1</sub> is kept down to about 1,000pF to preserve the high notes. It will be seen that, as the slider moves towards the end connected to L<sub>2</sub>, reaction will take place. This is because the resistance between L<sub>2</sub> and earth is progressively reduced, earth being represented by the negative battery line. VR<sub>1</sub> is a 5kΩ linear control, preferably wirewound.

The decoupling resistor R<sub>1</sub> is an essential part of the circuit since it performs another function in addition to decoupling. It should have a value which will cause a voltage drop of about 0.33V across it. If, for instance, TR<sub>1</sub> passes 1mA, which is a typical figure, it is clear from Ohm's law that R<sub>1</sub> should then be 330Ω. The value of R<sub>1</sub> is, therefore, dependent upon the current passing through TR<sub>1</sub>. R<sub>2</sub> has a value of 39kΩ. It will be seen that there is a diode between the high potential end of L<sub>1</sub> and the low potential end of L<sub>2</sub>.

Let us assume that a weak station is being received and that, therefore, the slider of VR<sub>1</sub> is adjusted to be close to L<sub>2</sub> in order that reaction may take place. The resistance part of VR<sub>1</sub> being considered will be very small compared with the resistance of R<sub>2</sub>, so that the negative end of D<sub>1</sub> (its "anode") will be at nearly -9V. The positive end of D<sub>1</sub> (its "cathode") will be at a potential of 0.33V positive to the -9V line owing to the voltage drop across R<sub>1</sub>. The result is that the "cathode" of D<sub>1</sub> will be positive with respect to its "anode". In other words, D<sub>1</sub> is reverse-biased and, provided it is

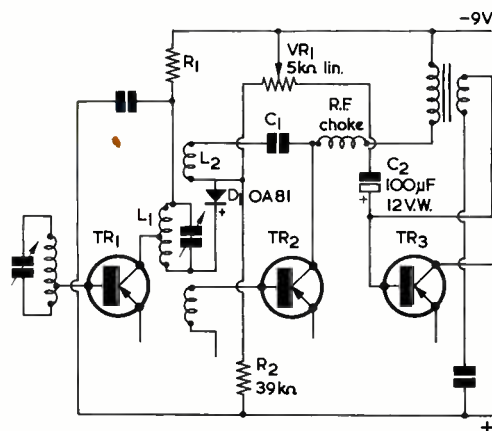


Fig. 1. The volume control circuit fitted in a typical t.r.f. receiver.



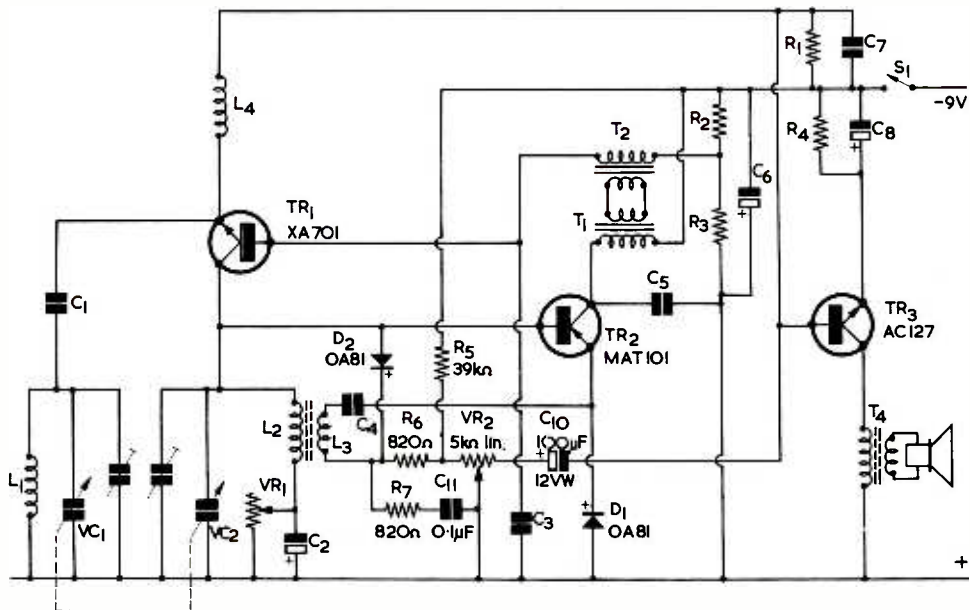


Fig. 2. Incorporating the volume control in the author's "D.R.4." receiver. This is shown switched to 3-transistor operation for reasons of simplicity.

diode of the OAB1 type, will have a very high resistance which will cause negligible damping of  $L_1$ . Such damping can, in any case, be cancelled out by reaction.

Let us consider the instance where a powerful signal from the local station is received. As the slider of  $VR_1$  will now be adjusted to a point well away from  $L_2$  there will be a resistance of nearly  $5k\Omega$  between the negative battery line and the "anode" of  $D_1$  which will find itself more positive than the "cathode". In consequence,  $D_1$  will be forward-biased and will have a low resistance which, in series with  $VR_1$ , will damp  $L_1$  considerably. There will still be a tuned circuit, unaffected by  $D_1$ , at the input of  $TR_1$ , which will provide such selectivity as is required at the low volume control setting used for the local station.

Many readers will see that the circuit just described is similar to the a.g.c. diode damping often used in superhets. The present circuit is, however, adapted for manual control.

#### A.F. Amplifier Control

It will now be found that there is good control over a powerful local station, though it may still be impossible to reduce it to zero volume level, as  $L_1$  will still offer some impedance despite the shunting

effect. This is looked after by a third action on the part of the volume control, this time on the a.f. signal. The section of  $VR_1$  between the slider and  $C_2$  is in parallel with the input to  $TR_3$ . At high volume settings the near  $5k\Omega$  involved will have little effect. But the signal will disappear when  $VR_1$  is at zero because there is then a short-circuit at a.f., across the input to  $TR_3$ .

Complete control is now possible, but even though it will be found to be very smooth from zero to overload on strong signals, there is still the probability that, with weak signals which require critical reaction, there will be rather sudden increase in volume as the control is adjusted. One solution would appear to be to use a graded volume control for  $VR_1$ , so that variation of resistance is gradual at the high volume end. But this would require an anti-log control, which is something of a rarity, unless there were no objection to employing a long control wired in such a way that volume increased in an anti-clockwise direction. A more serious difficulty is that, as  $VR_1$  carries a small current, it is important, in the interests of quietness and long life, that it should be wirewound. And wirewound log controls are rare indeed! Yet another snag is that a log control would result in rapid

variation of the a.f. signal as zero was approached.

#### Modifying the "D.R.4."

It is possible to obtain some of the characteristics of a log control by using a fixed resistor across one half of a linear control. This, of course, leaves the other half of the potentiometer unaffected, which is what is wanted, and this dodge will often be found to improve results with reaction circuits. For example, readers who have made the receiver described by the author in the issue for November 1965 ("Simplicity and Sensitivity with 3 Transistors") may find an improvement if they shunt a resistor across the high sensitivity end of its volume control. Different resistors of from  $390\Omega$  to  $1.8k\Omega$  should be tried for best results. At the cost of slight extra complication, it is possible to arrange something a little better in a way which is especially suitable for circuits having a high degree of constancy in the setting for critical reaction. Such a circuit is the Spontaflex, and Fig. 2 shows how the "D.R.4. Receiver", described in the issue for March 1966 may be modified to incorporate a very satisfactory form of volume control\*. Existing relevant components are numbered as in the earlier issue, and the circuit is shown in its 3-transistor

form for the sake of simplicity.

First, the original panel control, VR<sub>3</sub>, is removed, and the lead which had been taken to its slider is joined instead to the negative battery line. VR<sub>2</sub>, originally used as a pre-set control, should be removed from its position inside the receiver and may, if it is suitable, be mounted on the panel and rewired as shown in Fig. 2. If the existing component is not a wirewound type it would be as well to replace it.

In studying Fig. 2 let us at first assume that R<sub>6</sub> is short-circuited and that R<sub>7</sub> and C<sub>11</sub> are out of circuit. The only purpose of C<sub>11</sub>, incidentally, is to prevent biasing arrangements being upset. It will then be seen that the volume control arrangements are similar to those in Fig. 1, necessary modifications having been made to suit the use of n.p.n. transistors for TR<sub>1</sub> and TR<sub>3</sub>. VR<sub>1</sub> performs the duty of R<sub>1</sub> in Fig. 1. If an existing Spontaflex "D.R.4" is being modified, VR<sub>1</sub> will already have been adjusted in accordance with instructions in the earlier article. If the receiver is being built from scratch, VR<sub>1</sub> should be adjusted so that oscillation at the long wave end of the tuning scale starts with VR<sub>2</sub> set at the lowest point possible. This setting will be found correct both for bias for the base of TR<sub>2</sub> and for satisfactory working of the new volume control arrangements. R<sub>5</sub> is the 39kΩ resistor marked R<sub>2</sub> in Fig. 1, C<sub>4</sub> is the equivalent of C<sub>1</sub>, and C<sub>10</sub> of C<sub>2</sub>. D<sub>1</sub> in Fig. 2 is the receiver's existing detector. D<sub>2</sub> in Fig. 2 takes the place of D<sub>1</sub> in Fig. 1.

In the Spontaflex circuit, using the coil specified for the "D.R.4", it will be found that oscillation starts when there is about 550Ω between L<sub>3</sub> and earth. This assumes that the full negative voltage is applied to the collector of TR<sub>2</sub>, as results

from the removal of VR<sub>3</sub> from the original circuit. It will also be found that, on a really weak station, the effects of reaction begin to be obvious when there is a resistance of about 600Ω between L<sub>3</sub> and earth. If we still assume that R<sub>6</sub> is short-circuited and R<sub>7</sub> is out of circuit it will be seen that a variation from 550Ω to 600Ω is achieved by a movement of only 1% of the total possible travel of VR<sub>2</sub>, and that the useful range for reaction purposes on a weak station will be from 88 to 89% of the total rotation of the potentiometer.

If R<sub>6</sub> remains short-circuited, but R<sub>7</sub> is connected into circuit in parallel with the high potential end of VR<sub>2</sub>, it will be necessary to make a readjustment to produce an overall resistance of 550Ω and it can be shown from the formula governing resistances in parallel that approximately 1,600Ω of the track of VR<sub>2</sub> will be required, and 2,200Ω when an overall resistance of 600Ω is needed. The useful part of the track of VR<sub>2</sub> for a weak station now extends from about 56 to 68% of total rotation scale—a more satisfactory range. But about one third of the scale, from 68% upwards, is of no use.

If the short-circuit across R<sub>6</sub> is removed, it will be seen that the necessary 1,600Ω or 2,200Ω requires a resetting of VR<sub>2</sub> because of the constant resistance of 820Ω which is now in series with it. 1,600Ω minus 820Ω is equal to 780Ω, and 2,200Ω minus 820Ω is equal to 1,380Ω. In other words, to achieve a movement from 600Ω to 500Ω will now require a setting of VR<sub>2</sub>

\* Sir Douglas Hall, "Simplicity And Sensitivity With 3 Transistors", *The Radio Constructor*, November 1965. Sir Douglas Hall, "The 'Spontaflex' D.R.4. Transistor Portable", *The Radio Constructor*, March 1966.

varying between about 72 and 84% of total rotation. The range is still 12% of available rotation, and most of the track of VR<sub>2</sub> is useful. The top 16% provides a reserve as the battery fails.

An additional useful effect of R<sub>7</sub> is that it makes the r.f. shunting effect at low settings of the control more marked, the effective resistance across L<sub>2</sub> being reduced from the resistance of D<sub>2</sub> plus nearly 5kΩ to the resistance of D<sub>2</sub> plus less than 820Ω. Thus the control of powerful signals benefits as compared with the arrangement shown in Fig. 1.

### General Applications

This circuit, using R<sub>6</sub> and R<sub>7</sub>, can, of course, be used in any straight or reflex circuit provided, preferably, that there are at least two tuned circuits, and that the oscillation point is fairly constant throughout the tuning scale. The position or size of the reaction coil should be adjusted so that oscillation starts with about 500Ω to 700Ω between the coil and the slider, R<sub>6</sub> being short-circuited and R<sub>7</sub> out of circuit. There is no need to use an ohmmeter as, if a scale is fitted to VR<sub>2</sub>, the resistance of its track in circuit can be evaluated. R<sub>6</sub> and R<sub>7</sub> should each be 1.5 times this resistance.

The volume control circuit will be found to be unusually smooth from zero to maximum for all signals, and there will be no interaction with the tuning control. It is not recommended for use with circuits which offer wide variations of oscillation point for different settings of the tuning control, as the otherwise valuable spreading effect brought about by R<sub>6</sub> and R<sub>7</sub> will tend to make such variations even more marked.

## KUWAIT NATIONAL BROADCASTING STATION

A contract was signed recently for the supply and installation of broadcasting equipment which will give Kuwait the most powerful national broadcasting station in the world. The contract, with the Ministry of Guidance and Information, covers the supply of three Marconi 750kW High Power transmitters of the very latest design, which will provide the Voice of Kuwait with medium frequency programme transmissions giving extensive coverage of the Middle Eastern countries.

Each transmitter has an output of 750 kilowatts, probably the highest power output available from any single transmitter on the market. This is nearly twice the power of the 200 kc/s Light Programme transmitter of the BBC at Droitwich, the most powerful national service in Britain.

This order, worth over £1 million, was won in competition with offers from leading manufacturers in Europe, Russia, Japan and the United States. The transmitters, which are at present being assembled at Marconi's Chelmsford works, are due for delivery next year.

Engineers from The Marconi Company will install and commission the three transmitters, and the contract also provides for the training of six Kuwaiti engineers in the operation and maintenance of the transmitters. This training will take place at the Company's establishments in the Chelmsford area.

The 750kW transmitters are of the very latest design, and are fully transistorised throughout the low power driving circuits. Crystal control is used to give very high stability of the radiated frequency. Vapour cooled tetrode valves are employed in the modulator and high power radio frequency output stages. These valves have a much higher gain than the more conventional triode valves, and together with the use of patented high efficiency circuits, give the transmitters a very high overall efficiency.

# CIRCULAR TIMEBASE

By M. W. SHORES, N.Z.I.S.T.

*A simple experimental method of displaying circular and elliptical traces for purposes of frequency measurement*


THE SUBJECT OF CIRCULAR AND ELLIPTICAL TIMEBASE traces was originally pursued by the writer out of interest only, but at a later stage the practical advantage led to regular use.

The study and manipulation of audio tones and associated circuitry, particularly in the province of Radio Control, indicated a need for an uncomplicated method of establishing frequency. The writer found that the more conventional Lissajous figures in oscilloscope work tended, for him at least, to be confusing. A series of alternative methods were tried and the timebase described in this article was finally adopted as being most satisfactory.

The fundamental requirements for producing a circular trace on the c.r.t. screen are two sine waves of identical frequency  $90^\circ$  out of phase one with the other. One of these signals is applied to the vertical (Y) deflection plates and the other to the horizontal (X) plates.
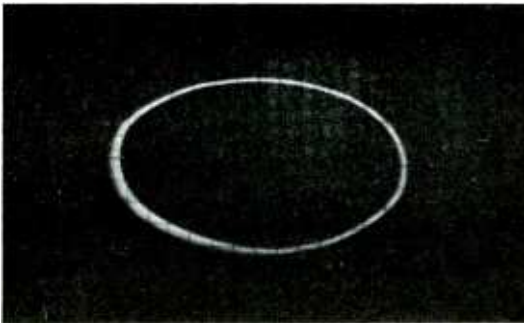
## The Circuit

The circuit employed by the writer appears in the accompanying diagram, and the component values shown relate to the mains frequency of 50 c/s, this being a very useful and stable standard. The use of a 50 c/s standard means that the c.r.t.



A 50 c/s ellipse, with no additional tone applied

## Components List

### Resistors

R <sub>1</sub>	5k $\Omega$	Potentiometer, linear track
R <sub>2</sub>	5k $\Omega$	Potentiometer, linear track
R <sub>3</sub>	2.2k $\Omega$	$\frac{1}{2}$ W 10%
R <sub>4</sub>	2.2k $\Omega$	$\frac{1}{2}$ W 10%
R <sub>5</sub>	1M $\Omega$	$\frac{1}{2}$ W 10%
R <sub>6</sub>	1M $\Omega$	Potentiometer, linear track
R <sub>7</sub>	500k $\Omega$	Potentiometer, linear track
R <sub>8</sub>	100k $\Omega$	Potentiometer, linear track


### Capacitors

(The working voltage of C<sub>3</sub> and C<sub>4</sub> depends on the oscilloscope being used)


C <sub>1</sub>	0.5 $\mu$ F paper 250V wkg.
C <sub>2</sub>	0.5 $\mu$ F paper 250V wkg.
C <sub>3</sub>	0.25 $\mu$ F paper
C <sub>4</sub>	0.25 $\mu$ F paper
C <sub>5</sub>	0.05 $\mu$ F paper 250V wkg.
C <sub>6</sub>	0.05 $\mu$ F paper 250V wkg.
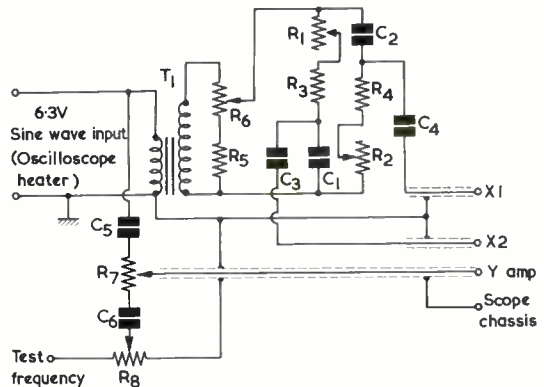
### Transformer

T<sub>1</sub> Step-up transformer (see text)



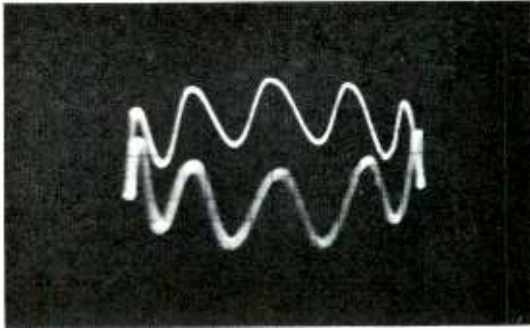The timebase employed for frequency measurement




The trace given when a 500 c/s sine wave is applied

spot takes  $1/50$  second to traverse the full  $360^\circ$ .  $R_1$  and  $R_2$  are variable, allowing for adjustment to offset any difference between the values of  $C_1$  and  $C_2$ . Ideally, these capacitors should be identical, as mismatching causes distortion of the trace. However, a considerable amount of correction may be made with the aid of  $R_1$  and  $R_2$ .  $R_1$  and  $R_2$  may be preset if good quality components are used, whose value is unlikely to drift. If the amplitudes of the out-of-phase voltages are varied with relation to one another, an ellipse appears instead of a circle.\*

Having reached thus far, it only remains to superimpose the tone whose frequency is to be measured. This is applied in the vertical plane only and is mixed with the vertical signal through  $R_7$ . The combination of the two signals fed at each end of  $R_7$  appear at its wiper, and are applied to the Y amplifier of the oscilloscope. Using this control in conjunction with Y gain gives the desired visual amplitude of the tone.

Transformer  $T_1$  dispenses with the need for an X amplifier, this being a luxury absent from the writer's home-built oscilloscope. The writer used an old speaker transformer with the 6.3 volt supply


\* To obtain a true circular trace, the deflecting voltages at X and Y plates should be exactly  $90^\circ$  out of phase, a state of affairs not necessarily provided by the circuit shown here. However, a phase difference of other than  $90^\circ$  can allow an ellipse to be produced, which may be similarly used for frequency measurement. Also, the potentiometers in the circuit provide a wide range of amplitude adjustment and consequent control over the shape of the trace. The oscilloscope timebase is, of course, kept out of action when the circuit is used. —Editor.

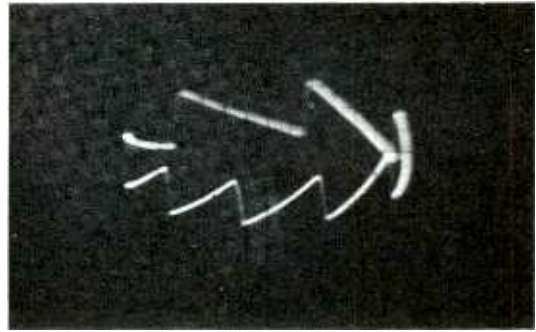

A sawtooth voltage having a frequency of 400 c/s gives this trace

applied to its original secondary, whereupon approximately 130 to 150 volts r.m.s. appeared across  $R_5$  and  $R_6$ . The 6.3 volt supply was obtained from the heater winding of the oscilloscope mains transformer, and has one side earthed.

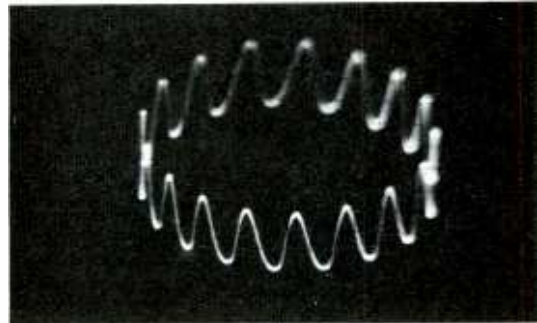It was found necessary to use X shift with the circuit. This raises no problems as  $C_3$  and  $C_4$  isolate any d.c. voltage on the X plates.



Applying an 850 c/s sine wave

The results shown in the photographs illustrate that it is only necessary to count the peaks and multiply by 50 to obtain the exact value of the tone being applied. This allows frequencies at 50 c/s intervals to be established, but a double trace gives the intermediates at 25 c/s intervals. For example if a double trace gives a count of 17 peaks then divide by 2 and multiply by 50 and the frequency is 425 c/s.

## SUPER-SPEED GaAs DIODE

One of the factors which limits the speed of operation of computers is the storage of charge in diodes. A point contact gallium arsenide sub-miniature diode has been introduced by the Mullard Company under the development number 54CAY. The switching speed of this device approaches the limit of conventional measuring instruments. The reverse recovery time is only 300 picoseconds and the stored charge 6 picocoulombs. (The prefix pico signifies one million millionth.) Axial wire leads are used.

The diode is finding applications in super-speed switching circuits, oscilloscopes, sampling gates and circuits for measuring particle velocities, apart from a large number of microwave applications.



# In Your Workshop

*As is his normal practice during August, Smithy the Serviceman, accompanied by his able assistant, Dick, leaves the confines of the Workshop to sample the great out-of-doors. On this occasion the pair still, however, manage to find time to discuss the problems of mass-production and the question of tolerances*

"ARE YOU," ASKED SMITHY sympathetically, "having trouble with your rowlocks?"

Dick raised his hand to a perspiring brow, but returned it hastily as he saw the oar it had been holding pass quickly over the side of the boat.

"I'll say I'm having trouble," he complained bitterly, catching hold of the oar just before it finally disappeared over the wale. "As soon as I pull one of these flaming oars it comes right out of the rowlock. What that darned rowlock needs is re-designing, that's what."

Again, Dick pulled on the oars, and again, half-way through the stroke, one of them abruptly disengaged itself and caught him sharply in the chest.

### The Serviceman's Approach

Smithy leaned forward and peered inquiringly at the boat fitting which was causing his assistant so much trouble. A light of understanding suddenly gleamed in his eye.

"The fault is obvious," he exclaimed, "you've got it 180 degrees out of phase!"

Smithy turned the rowlock through the 180 degrees of his diagnosis, and manoeuvred the oar back into it.

"Now, try it."

Distrustfully, Dick pulled at the oars once more, to find that, this time, they both pivoted at the rowlocks without further trouble. Encouraged, he repeated the process.

"Now this," he admitted grudgingly, "is a bit more like it. But I don't quite understand what you did just then."

"If you look at that rowlock," explained Smithy, "you'll see that it's shaped like the letter 'C', the open bit being where the oar goes in. That open bit should be away from you but you had it towards you. With the result that, every time you pulled on the oar it just came out of the rowlock."

"Well, I'm dashed," said Dick, impressed. "Dead simple, isn't it?"

"Of course it is," replied Smithy. "But you were talking about re-designing it."

Dick forebore to reply and directed his energies to the oars. They were soon moving through the water at a very gratifying speed.

"I must confess," said Smithy, trailing a negligent hand in the water, "that this makes a very pleasant change from the Workshop. I think it was quite a good idea on my part to suggest that we pass part of our Summer outing this year with an hour on the local boating lake."

Dick pulled vigorously at the oars.

"I must admit that it is rather a bright idea," he said. "It's funny, though, that our conversation went on to this subject of re-designing."

"Why's that?"

"Because I'd just been thinking," explained Dick, "about the question of re-designing from the point of view of the service engineer."

Smithy sighed.

"And I was mistaken enough," he remarked sorrowfully, "to imagine that we would be getting away from the Workshop this afternoon. Blimey, Dick, you don't half keep the hangar door open, you know!"

But Dick had espied a clump of overhanging trees which would shade them from the hot August sun. Resolutely, he rowed the boat towards them and then, equally resolutely, shipped the oars. The boat came to rest, to float undisturbed on the lapping, gentle, water.

"There must," continued Dick inexorably, "be times when you do a bit of a re-design on a job that you're servicing."

"Not these days, there aren't," replied Smithy firmly. "I'll agree that we used to get up to tricks like that during and immediately after the war when parts were scarce, but I wouldn't do anything like that nowadays. And certainly not with modern receivers."

"I had a TV in the other day," offered Dick, "and the cathode bypass capacitor for the audio output valve had broken down. It was a 25 $\mu$ F 12 volt working job."

"I presume," said Smithy, his interest aroused despite his previous protestations, "that you carried out the normal service procedure of checking to see what had caused the capacitor to break down before you replaced it?"



"I did," confirmed Dick, "and I could find nothing wrong in the circuit whatsoever."

"The coupling capacitor from the preceding anode," suggested Smyth, "might have gone a little leaky. This wouldn't upset the audio quality too much if the leakage was slight, but it could cause the output cathode to rise a little in potential due to cathode-follower action." (Fig. 1).

"I thought of that," said Dick, "and as I looked at the coupling capacitor, I suddenly realised that both this and the electrolytic were spares of the type we keep in the Workshop. What is more, I then recognised the set as one I'd fixed about three months ago for exactly the same fault. There had been a slight suspicion of leakiness in the coupling capacitor on the previous occasion and so I'd swapped it, as well as the electrolytic, just to be on the safe side. Everything else, including the valve and the cathode bias resistor, had checked good on that occasion. They still did yesterday, and the coupling capacitor I'd fitted previously was still perfectly O.K., so I just wired in another electrolytic. This time, though, I put in one with a working voltage of 25."

#### Different Tolerances

"That," agreed Smyth, "is a reasonable course to take. There might be an intermittent in the set causing the cathode potential to go above 12 volts every now and again and make the capacitor break down. Alternatively, it could just be that a combination of high ambient temperature about the capacitor, plus a build-up of tolerances in component values in the circuit around it, has caused it to be on the verge of breaking down all the time."

"The point I now want to make," said Dick, "is this. If the manufacturers put in a 12 volt capacitor and I replace it with a 25 volt one, I'm changing the design. Aren't I?"

"Well, yes you are," admitted Smyth, "but only in a very minor way. Also, we've got to be realistic here. We're not going to get a good name for servicing if that TV you fixed has to come in every three months to have another 12 volt electrolytic fitted in it, are we?"

"What happens," argued Dick, "if it is an intermittent which is causing the capacitor to keep breaking down?"

"If there is an intermittent," said Smyth, "it will probably

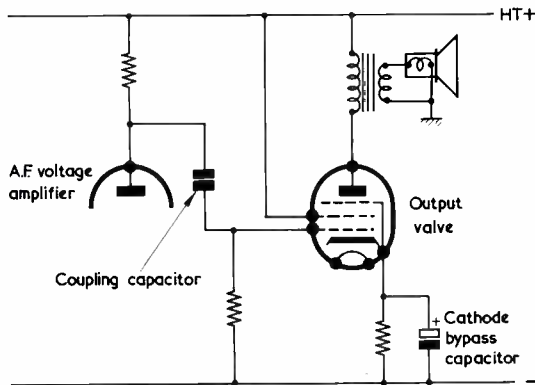


Fig. 1. A high resistance leak in an a.f. coupling capacitor may not seriously affect the quality of reproduction, but it can cause the cathode voltage of the following valve to become increased. A cathode bypass capacitor with a low voltage rating could then suffer risk of breakdown

appear again. Should it cause the 25 volt electrolytic to break down as well, we'll then know we've got something serious to look for. And if it doesn't break down the electrolytic it will do something else, whereupon we'll have a helpful guide as to where the intermittent is. Incidentally, I'd have swapped the audio output valve in that set as well, just to be on the safe side."

"I did," said Dick, "on the second occasion it came in. The valve might have had an intermittent internal short. Although it seems a little doubtful, since you'd have to have the cathode short over to the screen-grid or the anode."

"The valve would also," Smyth reminded him, "have drawn excessive cathode current if the grid had shorted over to the screen, or to the cathode for that matter."

"That's a point," admitted Dick.

The pair fell silent for a moment. It was very peaceful in the shade of the trees. Smyth relaxed and allowed his thoughts to wander from matters electronic.

"In this servicing business," said Dick suddenly, "you've got to put in different replacement components sometimes. Which means, again, that you're making a change to receiver design."

Reluctantly, Smyth tore himself from his reverie.

"Have you?" he asked vaguely. "When?"

"If you're out of stock of the exact component," replied Dick. "Say a 20% resistor needs changing, and you've only got 10 per cent's in stock."

"There's no problem there," said Smyth, a little irritably. "It's

always perfectly O.K. to change a resistor for another of the same value and a closer tolerance."

"What about the other way round?" asked Dick. "That is, replacing the resistor with another of wider tolerance."

"In that case you want to be a bit careful," said Smyth. "Manufacturers don't normally fit close tolerance resistors if they can use cheaper ones having a wider tolerance. I'll admit that, in practice, you'll very often get away with fitting a 20% resistor in place of a 10% one, and you'll find that the associated circuit still carries on O.K. But there could be a slight degradation of performance which isn't evident in bench tests. So far as particular circuits are concerned, TV timebases are probably the most fussy here. You should never use a wider tolerance resistor as a replacement in a TV timebase because you can easily run into difficulties with picture linearity, timebase speed control, and things like that. It's possible, of course, that the 20% resistor you use for a replacement just happens to have a value which is within the 10% tolerance. But you can't rely on this, unless you check its value on a resistance meter which is a bit more accurate than the ohms range of the average knock-about multi-testmeter. A further point is that if a resistor of 5% tolerance, or closer, has gone faulty, you should always replace with the same or a tighter tolerance regardless of the circuit it appears in. There'll be a very good reason for a manufacturer of domestic equipment using close tolerances in

resistors of the order of 5% or less. So far as general servicing is concerned, a sensible approach here is to stock replacement resistors in 5%, or even closer if they're not too expensive. You're then covered for all replacements of that tolerance and wider, without any further worry at all."

"That," remarked Dick, "seems to be a good idea. Incidentally, whilst we're on the subject of re-design, the manufacturers of TV sets are doing it all the time!"

"How d'you mean?"

"Well," said Dick. "The manufacturers start a new model and then, whilst it's in production, keep on introducing mods all the time. What's more, they send out details about them in their bulletins and other publications. If they're going to make all these changes, why didn't they incorporate them in the original design?"

"That," said Smithy, "is one of the things the service engineer has to live with and learn to accept. As you know, some commercial TV designs are very good and have no changes at all during production, whilst others are shockers. But you have to look at the overall picture in the light of mass-production of a complicated product. A TV set is probably the most complex domestic device which is produced at a competitive price by largely unskilled labour. The initial design of a new TV set is thoroughly tested before it's put into production, and there may also be pre-production runs as well. All the bugs which appear on these first tests are ironed out, and the set then goes into full production. After that, it's just a question of numbers."

"How do you mean—a question of numbers?"

"There may," explained Smithy, "be an unforeseen snag which only occurs in one set in a thousand. To find what that snag is, you've got to *make* a thousand! And to see whether it's a snag which is likely to be recurrent, you've got to make quite a few thousand more, as well. The large manufacturers keep a very sharp eye open for recurrent snags on a model, and one or two of them even have reps travelling all over the country whose only job is to pick up gen from retailers in this respect. Manufacturers also rely on the reports which come back from their own service departments. If a recurrent snag seems to be in existence in a particular model, changes are made to the sets in production to ensure that it doesn't occur in the future

sets leaving the factory. If the change is of sufficient importance, dealers and service departments are also advised. Other changes may also be introduced while a set is in production because they result in an improvement in performance. If these are of sufficient importance, the appropriate advice again goes out to the service engineer."

"Blimey," said Dick, impressed. "There's a bit more to it than I thought."

"There is," replied Smithy cheerfully. "If you think life is hectic as a service engineer, you want to have a spell on the manufacturing side!"

### Build-Up Of Tolerances

The silence of the shade was suddenly broken by the splash of oars, and the sound of quiet music from a radio. The pair turned round, to see a slim young girl rowing very competently across the lake despite the fact that, due to the weight of her companion in the stern, her end of the boat was almost entirely out of the water. This companion, a heavily made-up, over-dressed and peroxided lady would, in the eyes of the un gallant, have notched up an obvious fifty summers with an equally obvious fifteen stone, and Dick threw a glance of vague repulsion at her before concentrating his gaze on the girl in the prow. This vision combined a trim figure with a comely face and flowing light brown hair. Dick's jaw had sagged to its fullest extent by the time the boat passed out of sight, and the music of the little portable radio in it had faded away.

"Now that," remarked Smithy appreciatively, "is what I *call* a pretty girl."

Dick brought his thoughts back to his immediate surroundings.

"I'll say," agreed enthusiastically.

"Especially," continued Smithy warmly, "the blonde hair. I really go for that."

"The *blonde* hair" repeated Dick. "You must be going colour-blind."

"No, I'm not," snorted Smithy indignantly. "I mean the blonde hair on the one who was sitting at the square end."

"That old horror?" gasped Dick incredulously. "Blimey, Smithy, she was diabolical!"

"No, she wasn't," said Smithy firmly. "She was a very pretty girl. What you forget is that a man of my age appreciates the finer points in the opposite sex."

"If," pronounced Dick, "that's an example of what old age does

for you, I think I'll go out and shoot myself on my next birthday!"

"I don't think," said Smithy stiffly, "that remarks of that nature are called for. Perhaps we'd better get back to TV again."

"All right," said Dick hastily. "Why, blow me, I've forgotten what we were talking about!"

"Mass-production of TV sets."  
"Oh, yes," said Dick. "So we were. Anyway, I think you've told me all I want to know about that. At the same time, there's something you mentioned just now which has been puzzling me."

"What's that?"  
"You referred to a build-up of tolerances. What does that mean?"

"I think the best way of explaining that," said Smithy thoughtfully, "is by means of a mechanical example. Now, let's see if I can dream up a simple assembly which would demonstrate a build-up of tolerances to you."

The Serviceman stroked his chin thoughtfully.

"Ah, yes, I've got it," he said, suddenly. "Now, here's a nice little example which will show what I mean. Let's assume that we're designing a radio receiver for mass-production and that we intend to use a two-gang tuning capacitor which is mounted by way of three holes tapped 4BA in its base."

"Well," remarked Dick, "that's a good start at any rate! I've seen plenty of two-gang capacitors like that."

"Good," said Smithy. "Let's next assume that, when the capacitor is bolted to a flat chassis, the height of the spindle centre above the chassis surface is 0.875 inch plus or minus 0.01 inch." (Fig. 2(a)).

"Why 0.875 inch?"

"No particular reason," said Smithy. "It's a fairly commonly encountered dimension for tuning capacitor spindle height, and that's why it came to my mind. Incidentally, it's the decimal equivalent of seven-eighths!"

"Why, so it is!"

"Anyway, that's by the way," said Smithy. "Now we want to drive this tuning capacitor by way of a gear train, and the only requirement of this gear train that concerns us here is that the spindle centre must be 1.875 inch, plus or minus 0.02 inch, above the surface of the chassis." (Fig. 2 (b)).

"That seems easy enough," said Dick. "All you've got to do is to space the base of the capacitor away from the chassis surface by an inch to give you the 1.875 inch dimension. You could, for instance,



use long 4BA bolts and put spacing pillars over them."

"How about," asked Smithy artlessly, "having four spacers for each bolt? Each of these spacers having a length of 0.25 inch plus or minus 0.005 inch?" (Fig. 2(c)).

"That would be fine," said Dick, promptly. "You've got to meet a tolerance of plus or minus 0.02 inch to satisfy the gear train requirements, so the 0.005 inch tolerances on the spacers should be more than close enough."

Smithy chuckled.

"If," he grinned, "they let you loose on mechanical design, the production line would come screaming to a halt every two minutes!"

"Hey?"

"I'm afraid," continued Smithy, "that the use of those four spacers would be quite unworkable for mass-production purposes. And I shall now explain why. For a start, it could easily happen that, in one of the assemblies, all the four spacers are at top tolerance. That means that they all have a length of 0.25 inch plus 0.005 in. Each one then becomes 0.255 inch long and the total amount of spacing they give is 4 times 0.255, or 1.02 ins."

"Blimey," said Dick. "That's 0.02 inch too much."

"I know it is," said Smithy. "Let's further assume that the 0.875 inch spindle height of the capacitor is also on top tolerance. That would give you 0.885 inch which, together with the 1.02 inch spacing from the chassis, results in the spindle centre height being no less than 1.905 inches above the chassis surface. (Fig. 2(d)). The maximum that can be accepted by the gear train is 1.875 plus 0.02 inch which is 1.895 inches so the spindle becomes 0.01 inch out of bank!"

"I'd forgotten about the tolerance in the capacitor spindle height."

"It's one of those things," remarked Smithy, "that do tend to get forgotten. If we repeat the exercise with all the spacers and the capacitor spindle height on bottom tolerance, we'll find that the final spindle height is 0.01 inch below the lowest tolerance acceptable by the gear train. Again, the parts won't fit together properly. Now, the whole point of this exercise is to show you what a build-up of tolerances is. In the example, we've had a build-up of tolerances all in one direction, whereupon the final displacement is a lot greater than a casual first examination of the individual tolerances would lead you to expect. In a good

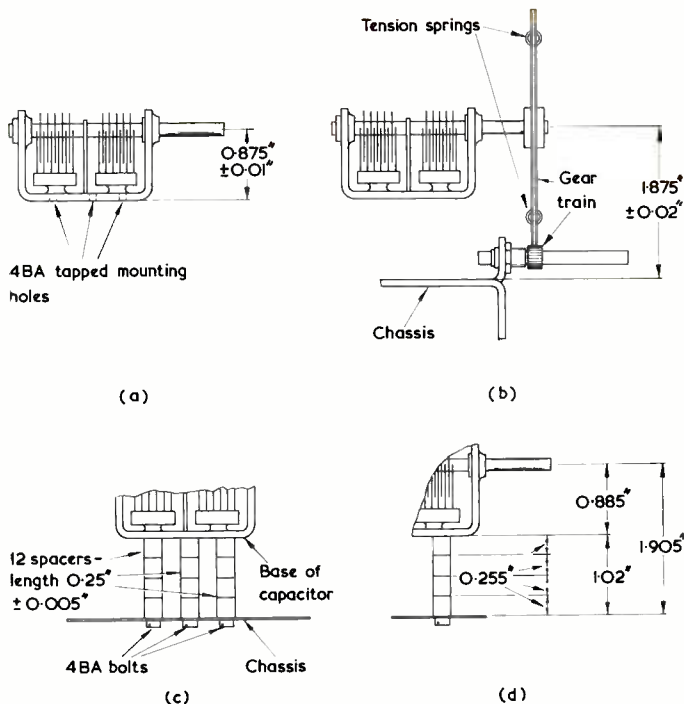


Fig. 2. Illustrating by a simple mechanical example how tolerances can "build up". It is desired to couple the variable capacitor of (a) to the gear train of (b). One method of spacing the capacitor away from the chassis surface could consist of using the spacing pillars shown in (c). If, however, all dimensions are at top tolerance level, as occurs in (d), the spacing between the capacitor spindle centre and the upper surface of the chassis becomes too great to meet the requirements of the gear train

mechanical design all individual tolerances in a system are taken into account whenever there is a possibility of their adding together in this manner. I must admit that the example I chose was a bit exaggerated, but it demonstrated the point quite well. A better approach towards mounting that capacitor would have consisted of using single 1 inch spacers, each with a tolerance of plus or minus 0.005 inch, whereupon the total build-up affecting the spindle height couldn't exceed 0.015 inch, and we'd have satisfied the requirements of the gear train, with a bit in hand."

"I see what you mean," said Dick thoughtfully. "In practice, though, would it really happen that the dimensions all went up to top tolerance, or down to bottom tolerance, at the same time?"

"It's certain to happen at some time or another," said Smithy, "if only because of the natural cussedness exhibited by inanimate objects when you try to assemble

them together. Don't forget that, in our example, the individual dimensions don't have to go to the actual top tolerance figures to get you into trouble. You'd still be in trouble if they just approached the top tolerance figures. Or, of course, if they all just approached the bottom tolerance figures."

"Why," asked Dick, "do we have to have these tolerances anyway?"

"Because," replied Smithy, "it's impossible to make anything exact. You can only make things to a dimension with a tolerance on either side."

#### Back To Base

Smithy looked at his watch.

"It looks as though our time on this boat is nearly up," he remarked. "We'd better start getting back."

"Okey-doke," said Dick, inserting the oars into the rowlocks which, he was careful to check, were now correctly orientated. "Incidentally,



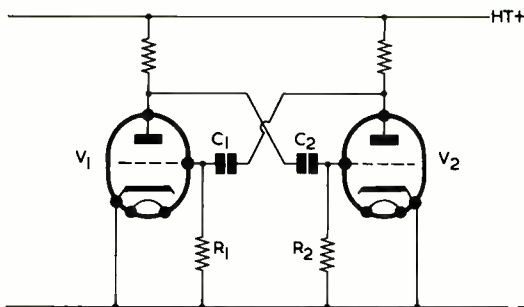


Fig. 3. A symmetric multivibrator. The time that  $V_1$  is cut off during the multivibrator cycle is proportional to  $C_1 R_1$ , and the time that  $V_2$  is cut off is proportional to  $C_2 R_2$

how is it that I've been doing all the rowing this afternoon?"

"It's just the natural order of things," explained Smithy airily. "When we got into the boat I took the initiative by sitting in the stern first, whereupon you had to sit on the other seat. After which, the only obvious conclusion was that you also had to do the rowing."

"Trust me," grumbled Dick, as he pulled at the oars, "to get caught. Anyway, how does this build-up of tolerance affect things like TV circuits?"

"You can get a build-up of tolerances in such things as resistors and capacitor values," replied Smithy. "One instance which comes to mind is given in a timebase employing a valve multivibrator. (Fig. 3). As you know, the length of time that one of the valves is cut off during the multivibrator cycle depends on the time needed for its grid capacitor to discharge, into its grid leak, sufficiently far for the valve grid to go above cut-off. This time is proportional to the product of the capacitance and resistance. If the capacitor and resistor had maximum values, within their tolerance, the time the valve was cut off would be disproportionately longer than if they both had their nominal values. Let's say for the sake of argument, that the resistor is  $100k\Omega$ , that the capacitor is  $100pF$ , and that both are 20% components. If both were on top tolerance they would have values of  $120k\Omega$  and  $120pF$  respectively. The cut-off time is proportional to the product of the resistance and

capacitance so it now goes up by a factor of 120 times 120 divided by 100 times 100, which is 1.44. So the time has gone up by 44%. The grid cut-off voltage is liable to vary for different valves and, if this were at the low end of the range offered by the valve type employed, the cut-off period would be longer. However, you can't talk of tolerances on grid cut-off voltage because the appropriate figures aren't normally quoted by valve manufacturers. Nevertheless, the multivibrator example gives an idea of the sort of build-up that can occur with electrical components. Hallo, we're getting near the landing point."

Dick turned round briefly. A young couple on the shore were chatting amicably together, waiting for the return of one of the boats so that they could have their turn. Out of the corner of his eye, he espied another boat which was also approaching the landing point.

"There's the boat with those two we saw in," he remarked, redoubling his efforts at the oars.

Dick was nothing if not opportunist, and the boat bearing Smithy and himself arrived at the landing at just the right time to enable him to jump out, tie up the girl's boat as it came alongside, and then offer a gentlemanly hand of assistance to its young female occupant.

"Thank you, dearie," came a hoarse voice from his rear, and the discomfited Dick suddenly found the hand of the peroxidized lady clutching at his arm. A considerable amount of his time was then taken

up in the process of hoisting up the bulk of this lady, and Dick's irritation at the unexpected turn of events was not reduced when he saw that Smithy had wandered up and was now in deep conversation with the young girl, who still sat in the prow of the boat. The couple on the shore had already claimed the boat he and Smithy had vacated, and were pushing her off.

When, at length, Dick finally succeeded in getting his charge safely ashore, he was further disconcerted to see Smithy hop into the boat and take her place. The brown-haired girl deftly unhitched the line and gave an expert pull at the oars.

"You might," said Smithy nonchalantly, as he glided past his dumbfounded assistant, and out into the lake, "do me a favour and pay the man for another hour on this boat. This young lady's transistor radio seems to have gone wrong, and I'm going to fix it for her."

Smithy's voice faded as the boat bore him away.

"Well now, dearie, isn't it kind of your friend to offer to help my niece like that?"

Shuddering, Dick turned to look at his companion.

"You know, dearie," she continued, "I always do love being rowed about on the lake, and I'm certain that a handsome young man like you would be only too happy to oblige. Wouldn't you, dearie? Why, there's another boat coming back now, and it will be all nice and cosy for the two of us."

An arch smile created a network of deep ravines in the face-powder, and the lumbered Dick gritted his teeth. As he walked furiously to the little office at the landing-place he mentally fought down his rage at all the outrages to which he had just been subjected: his having to pay for both Smithy's boat and the one he was now about to take out; his having to pull the bulk of Madame Peroxide about the lake for a full devastating hour; and the thought of Smithy now taking his ease whilst the girl of the light brown hair rowed him around.

By a superhuman effort, Dick managed to keep his fury within bounds. A build-up of tolerances, indeed.

# SIMPLE COMBINATION LOCK

By J. DAICH

**T**HIS LOCK WAS DESIGNED SO THAT ONLY OPERATIONS in the right order would open it. Incorrect operations cause it to be re-set.

The basic requirements are: 3 relays with 2 single pole make contact sets each, 9 press switches, of which 3 are push-to-make and 6 are push-to-break, and a battery. The battery can be of small size as current is only drawn when buttons are pressed in the correct sequence.

## The Circuit

The circuit is shown in Fig. 1. It will be seen that when  $S_1$  is closed relay A operates and, in so doing, short-circuits  $S_1$  by its contacts  $A_1$  and latches itself on. Contacts  $A_2$  also close, so that pressing  $S_2$  causes relay B to operate. Relay B

Fig. 1. The circuit of the lock. A solenoid or other device is energized when contacts C2 close, thereby causing the lock to open. Each relay has two sets of contacts which close on energizing, these being identified as A1, A2, B1, B2, C1 and C2. Relay coils are shown as rectangles

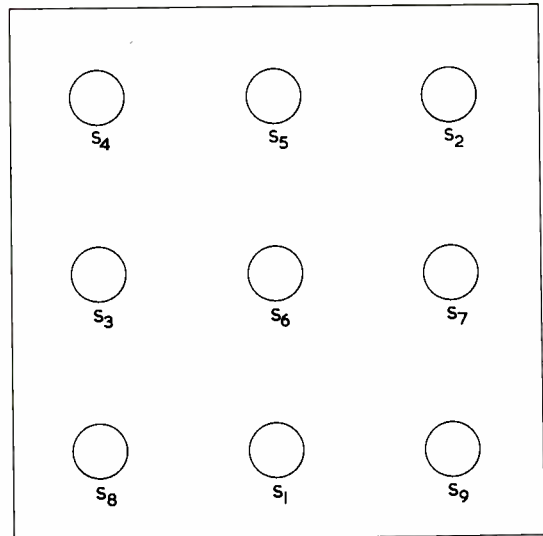
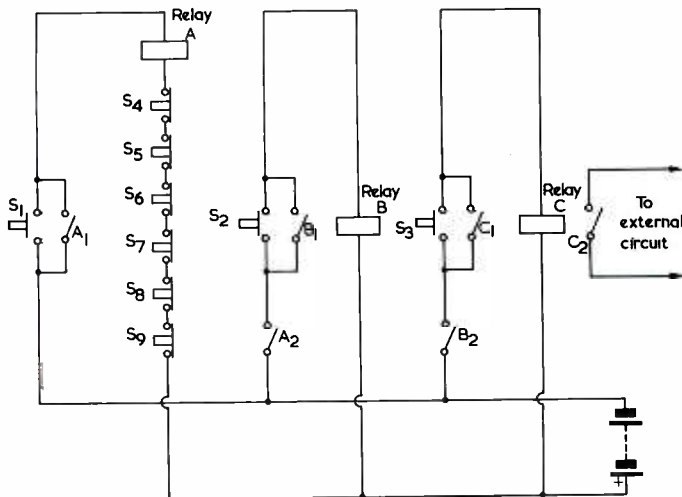


Fig. 2. The press switches may be laid out in random fashion, as in the example shown here

latches on by short-circuiting  $S_2$ . At the same time, contacts B2 close, enabling relay C to be energized by  $S_3$ , whereupon it latches on and its contacts C2 complete the external circuit and open the lock.

## Components List

### Relays

3 relays, each with 2 single pole make contact sets

### Switches

$S_1$  to  $S_3$  3 push-to-make switches  
 $S_4$  to  $S_9$  6 push-to-break switches

### Battery

Battery of suitable voltage to energise relays

There are 6 push-to-break switches in series with relay A. Pressing any of these causes this relay to de-energise and the lock to re-set.

A suitable panel layout for the press switches is shown in Fig. 2. The switches are positioned in random fashion, and any other random layout can be employed instead.

It will be noted that a considerable number of combinations is available, of which only one, the pressing of  $S_1$ ,  $S_2$  and  $S_3$  in sequence, is successful in opening the lock. The number of combinations can be made greater by increasing the number of stages or by increasing the number of push-to-break switches in series with the coil of relay A.

# BASIC RADIO CONTROL

Part 2

By F. L. THURSTON

- ★ **Field Strength Meter**
- ★ **Single Channel "Carrier" Transmitter**
- ★ **Output Monitor**

*Last month our contributor introduced the subject of radio control by discussing the various systems which are currently in use. In this month's issue he describes a single channel "carrier" transmitter, whilst next month's article will be devoted to a super-regenerative receiver which is designed to work in conjunction with the transmitter*


**S**INGLE CHANNEL "CARRIER" CONTROL SYSTEM. As was mentioned in last month's article, the most simple of all radio control systems, and thus the easiest to start with from the constructional point of view, is that using the single channel "carrier" principle. Here, no modulating signal is needed at the transmitter, and its design can thus

be fairly simple and, consequently, comparatively inexpensive. At the receiver end of the system, a simple super-regenerative detector circuit is used, in conjunction with an audio amplifier and filter circuit and a noise operated switch. This system relies on the fact that, when no carrier signal is present, the output of the super-regenerative detector contains a great deal of noise, this noise disappearing when the carrier signal is picked up by the receiver aerial. In this month's issue we shall give a practical example of a transmitter of this type, to be followed by full constructional details of a suitable receiver system next month.

It must be pointed out that the advantages and disadvantages of single channel "carrier" systems should be evaluated before embarking on the building of the transmitter. These are discussed in this article immediately after the description of the field strength meter. A radio control licence is also required to operate the transmitter, and application for this should be made to Radio Services Department, Radio Branch, Amateur Licensing Section, G.P.O. Headquarters Building, St. Martins-le-Grand, London, E.C.1.
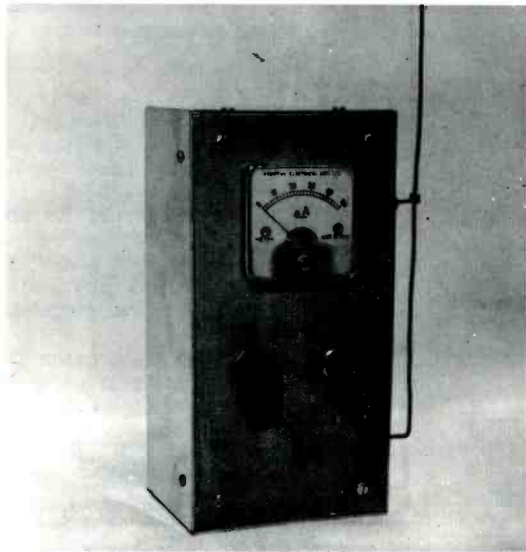
## Field-Strength Meter

One of the snags of building one's own electronic circuitry is that a certain amount of test equipment is needed if optimum results are to be obtained. In the case of home-built radio control transmitters one particular piece of test gear, not normally found in the electronic workshop, is essential. This is a



*The field strength meter with its aerial fitted*

field-strength meter. Fortunately, a field-strength meter is a very simple device, and is inexpensive and very easy to construct. It is used to indicate the relative strength of the "field" radiated by the transmitter aerial. The transmitter and aerial are adjusted to obtain the best possible reading on the field-strength meter, this ensuring that the radiated signal, and thus the range of the system, is at maximum.

Fig. 1 shows the circuit diagram of a suitable field-strength meter; and this piece of test gear should be built before any attempt is made to construct a transmitter. The radiated carrier signal is picked up by the field-strength meter aerial, which consists of a 24in length of stiff wire, and is fed, via  $C_1$ , to the tuned circuit formed by  $L_1$ ,  $C_2$  and  $C_3$ .  $C_3$  is a small variable capacitor, and enables the frequency of the tuned circuit to be varied by a small amount about a pre-set value. The signal from the tuned circuit is rectified by  $D_1$  working into  $C_4$ , and the resulting d.c. is applied to the meter circuit given by  $M_1$  and  $R_1$ .  $M_1$  is a  $50\mu\text{A}$  moving coil meter, and  $R_1$  is used as a sensitivity control.

If preferred, the field-strength meter may be simply "lashed" together, using any meter that happens to be available, and acceptable results will no doubt still be obtained. It should be remembered however, that the unit may have to be used "in the field", and may take a certain amount of physical punishment in the process. It is therefore recommen-

### Components List

(Fig. 1)

#### Resistors

$R_1$   $50\text{k}\Omega$  variable

#### Capacitors

$C_1$  50pF silver-mica

$C_2$  12pF silver-mica

$C_3$  25pF variable. Type C.804 (Jackson Bros.) or similar.

$C_4$   $0.005\mu\text{F}$  ceramic

#### Inductor

$L_1$   $12\frac{1}{2}$  turns of enamelled 24 s.w.g. copper close-wound on former with iron dust core. Coil former 0.27in diameter (Radiospares)

#### Diode

$D_1$  OA70 or similar

#### Meter

$M_1$   $50\mu\text{A}$  f.s.d. moving coil with  $1\frac{1}{8} \times 1\frac{1}{8}$ in face. Imported. (Newbury Radio (Forest Gate) Ltd.)

#### Miscellaneous

2 aerial plugs (miniature plugs—Radiospares)


2 aerial sockets (miniature sockets—Radiospares)

$6 \times 3 \times 2\frac{1}{2}$ in chassis and panel to fit

24in stout copper wire, or similar

2 knobs

Self-tapping screws (see text)

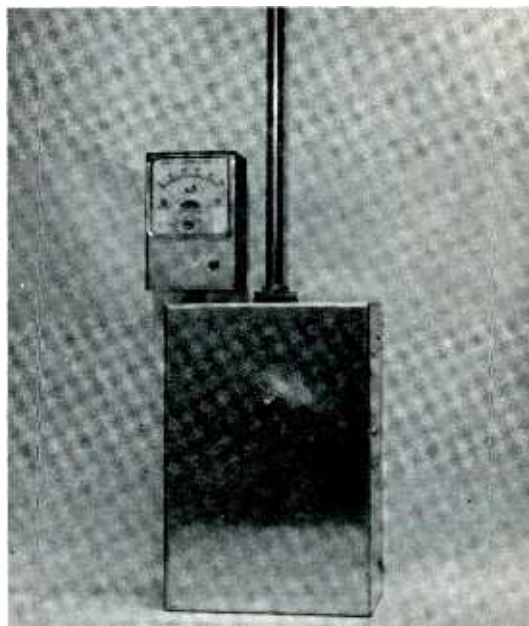

The remote control transmitter, complete with output monitor

ded that the unit be made as neat and robust as possible; in this context, the method of construction shown in Fig. 2 and in the photographs is strongly recommended.

Here, the unit is housed in a strong and presentable case, which is in fact a standard  $6 \times 3$ in aluminium chassis with strengthened corners and having a depth of  $2\frac{1}{2}$ in. Construction of the instrument is started by cutting and drilling an aluminium front panel to size, as shown in Fig. 2 (a). In the absence of a special cutting tool, the best way to cut the hole for

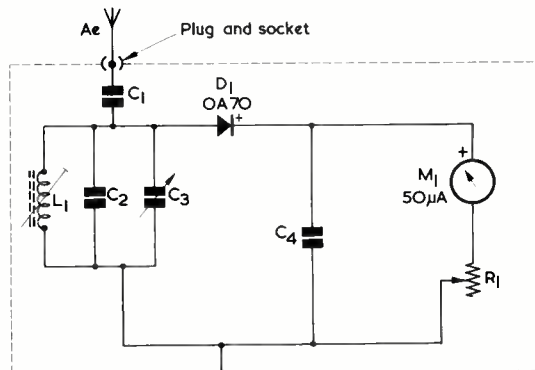


Fig. 1. The circuit of the field-strength meter. This must be constructed before commencing work on the transmitter



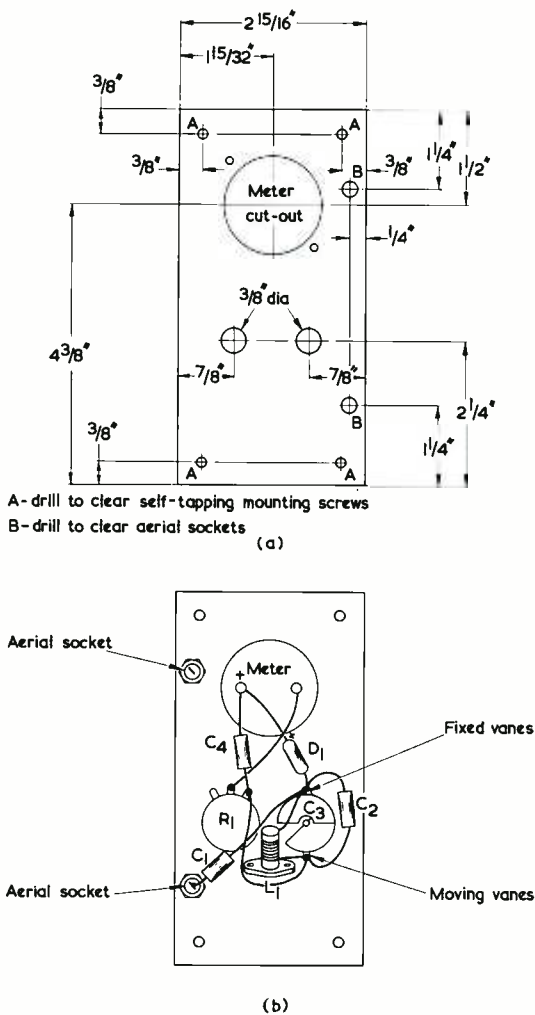


Fig. 2 (a). Front view of the aluminium panel for the field-strength meter. The four holes designated "A" take self-tapping screws which pass into angled strengthening brackets fitted in the case, and which enable the panel to fit flush  
 (b). The rear of the panel, showing the wiring and components. In the prototype the moving vanes of  $C_3$  connect to the metal panel by way of its mounting bush

the meter is to mark out its outline with a pair of compasses, and then make the cut-out with a fret-saw fitted with a metal cutting blade; these blades are available from most tool stores for a few coppers. In the prototype, the meter was an inexpensive Japanese type having a face measuring  $1\frac{3}{8}$  by  $1\frac{1}{2}$  in. Next, secure the meter, the tuning control ( $C_3$ ) and the sensitivity control ( $R_1$ ) to the front panel. Note that the aerial is secured to the instrument by a pair of Radiospares miniature sockets bolted to the front

panel, and these should also be carefully secured in place at this stage.

Next wire up the unit as shown in Fig. 2 (b). The coil,  $L_1$ , is made by close-winding  $12\frac{1}{2}$  turns of 24 s.w.g. enamelled copper wire on a standard Radiospares 0.27in diameter coil former fitted with an iron dust core. After winding, the coil is secured to the coil former by a few dabs of polystyrene dope or similar fixative.

The aerial may be made, as in the case of the prototype, from heavy gauge copper wire, and it should have a total length of approximately 24in. Note that one side of the tuned circuit is connected to the metal front panel and case (via  $C_3$  spindle in the prototype), and that this connection is essential for best results.

If a calibrated signal generator is available, the unit may be set up by coupling a 27 Mc/s signal to the field-strength meter aerial via a loop of wire (an actual physical connection is not necessary here) whereupon, with  $R_1$  set to minimum and  $C_3$  set to mid-travel, the iron dust core of  $L_1$  should be adjusted for peak reading on the meter. If a signal generator is not available there is no need to worry, since this test is not essential but merely a matter of convenience. All transmitters to be described in this and subsequent articles are crystal controlled, and no trouble with carriers being radiated outside the permitted frequencies should be experienced.

Finally, the field-strength meter can be completed by securing the front panel to the case by means of self-tapping screws secured into angled strengthening brackets fitted at the corners of the case.<sup>1</sup> The front panel can be marked, if required, with the aid of Panel-signs or direct lettering.

### The Transmitter

Before dealing with the constructional details of this particular transmitter, it is necessary to give the reader a few words of warning on the advisability or otherwise of using the unit.

First, it must be stressed that, as well as being the most simple of all radio control systems, the single-channel "carrier" type is the most interference-prone and inefficient. It should not, however, be thought that the system is "useless"; indeed, the system can be very effective as long as its limitations are recognised. These limitations are (1) that the system is exceptionally prone to interference from other transmitters and other sources of r.f. radiation, and (2) that the effective range of the system is far less than that obtained with other systems.

In practice, these two limitations mean that the system is not recommended for use in aircraft, where an incorrect reaction (due to interference) may result in the destruction of the model, but that it is still very useful for the control of model boats and motor vehicles, particularly where range is to be kept to far less than a couple of hundred yards. The effective (reliable) range of the "carrier" system to be

<sup>1</sup> The self-tapping screws used in the prototype field strength meter and transmitter were No. 4 P.K. (full diameter 0.112in.) by  $\frac{1}{4}$  in with pan head (similar to cheese head).—Editor.

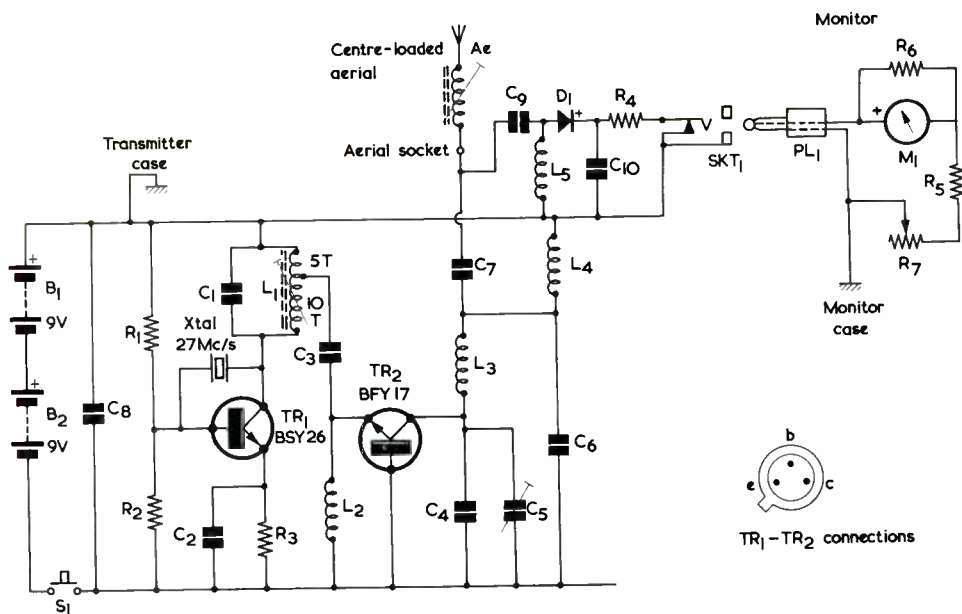


Fig. 3. The circuit diagram of the transmitter. The monitor unit is an optional extra, and it fits into the transmitter by means of an integral jack plug

### Components List

(Fig. 3)

N.B. Components marked with an asterisk are only required if the monitor unit is to be used

#### Resistors

(All fixed resistors  $\frac{1}{4}$  watt carbon, 10%)

- R<sub>1</sub> 22k $\Omega$
- R<sub>2</sub> 10k $\Omega$
- R<sub>3</sub> 120 $\Omega$
- \*R<sub>4</sub> 2.2k $\Omega$
- \*R<sub>5</sub> 68k $\Omega$  (may require adjustment)
- \*R<sub>6</sub> 330 $\Omega$
- \*R<sub>7</sub> 50k $\Omega$  skeleton pre-set

#### Capacitors

(Fixed capacitors should be as small as possible and could be, for instance, subminiature ceramic. C<sub>1</sub>, C<sub>4</sub> and C<sub>6</sub> should, however, be miniature silver-mica. Unless otherwise stated, working voltages are 18 or greater. The prototype employed sub-miniature capacitors obtained from Newbury Radio (Forest Gate) Ltd.)

- C<sub>1</sub> 22pF
- C<sub>2</sub> 0.01 $\mu$ F 12V wkg.
- C<sub>3</sub> 0.01 $\mu$ F
- C<sub>4</sub> 33pF
- C<sub>5</sub> 3-30pF concentric trimmer (Mullard)
- C<sub>6</sub> 47pF
- C<sub>7</sub> 0.005 $\mu$ F
- C<sub>8</sub> 0.1 $\mu$ F
- \*C<sub>9</sub> 56pF
- \*C<sub>10</sub> 0.01 $\mu$ F

#### Inductors

- L<sub>1</sub> 5+10 turns 24 s.w.g. enamelled wire on Radiospares 0.27in diameter former, with iron-dust core. Close-wound
- L<sub>2</sub> 50 turns of 36 s.w.g. enamelled silk-covered wire on 100k $\Omega$   $\frac{1}{4}$  watt 20% resistor (see text). Scramble or pile-wound
- L<sub>3</sub> 10 turns of 18 s.w.g. enamelled copper wire,  $\frac{3}{4}$ in i.d.
- L<sub>4</sub> As L<sub>2</sub>
- \*L<sub>5</sub> As L<sub>2</sub>

#### Transistors

(Transistors are available from Newbury Radio (Forest Gate) Ltd.)

- TR<sub>1</sub> BSY26 (S.T.C.)
- TR<sub>2</sub> BFY17 (S.T.C.)

#### Diode

- \*D<sub>1</sub> OA70 (Mullard)

#### Crystal

Brush Clevite, midget radio control type in 27 Mc/s range. A matched pair (see text) is recommended if future projects are to include superhet receivers. (Teleradio, 325-327 Fore St., London, N.9.)

### Aerial

Teleradio antenna type CLV80, with insulated socket. (Teleradio, 325-327 Fore St., London, N.9.)

### Meter

\*M<sub>1</sub> 50μA f.s.d. moving coil with 1½ x 1½ in face. Imported. (Newbury Radio (Forest Gate) Ltd.)

### Switch

S<sub>1</sub> Miniature Push-Button Switch, Push-To-Make (Radiospares)


### Batteries

B<sub>1</sub>, B<sub>2</sub> 9-volt battery type DT7 (Exide)

described is approximately 150 to 200 yards ground-to-ground.

The second point that must be stressed is that, since the articles which will follow this 3-part series are intended to be progressive, (in that a whole range of systems, becoming progressively more complex, are to be described), components have been employed that are suitable for use with a whole range of circuits, and are not necessarily the least expensive types available for any *one* particular circuit. In particular, a fairly expensive centre-loaded aerial is specified for all transmitters to be described, although this may be considered as a luxury for some of the single channel equipment. Again, it is recommended that a special pair of matched sub-miniature crystals, at approximately £3 per pair, be purchased initially, bearing in mind that it may be decided to use a superhet receiver for radio control at a future date. For many applications, however, a normal crystal, costing approximately 25s., could be used.<sup>2</sup> Thus, the cost of building some of the equipment to be described is not as low as it could be.

<sup>2</sup> The matched pairs are intended for superhet working, one being fitted at the transmitter and the other at the receiver, and they are available with difference frequencies of 455, 465 and 470 kc/s. The radio control articles planned for publication later will require 465 kc/s spacing between the matched pair of crystals and readers should, in consequence, obtain matched pairs with this difference frequency. —Editor.

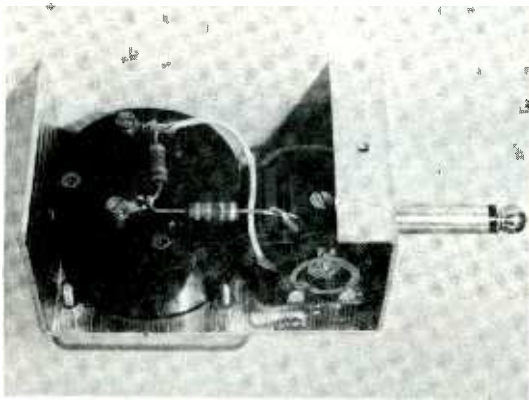

Internal view of the plug-in monitor unit

### Plug and Socket

\*PL<sub>1</sub> "Standard" jack plug (Radiospares)

\*SKT<sub>1</sub> Closed circuit jack (Radiospares)

### Miscellaneous

3-pin transistor holder, Cat. No. TR34 (Home Radio (Mitcham) Ltd.)

Veroboard, 0.1 in hole matrix, dimensions as in Fig. 4 (a), (Newbury Radio (Forest Gate) Ltd.)

Battery connectors

Self-tapping screws (see text)

Material for chassis and brackets, etc.

### NOTES:

1. The address of Newbury Radio (Forest Gate) Ltd. is 274 Romford Road, Forest Gate, London, E.7.

2. Radiospares components may only be obtained through retailers.

Having cleared up these points, it is now possible to get down to the details of the practical transmitter. Fig. 3 shows the circuit diagram of this unit.

As can be seen, the circuit uses only two transistors, both n.p.n. types, in a fairly simple circuit. TR<sub>1</sub> is wired as a crystal oscillator. For practical purposes this part of the circuit can be regarded as a conventional common emitter amplifier, with the base-bias network being given by R<sub>1</sub> and R<sub>2</sub>, and with emitter bias resistor R<sub>3</sub> bypassed by C<sub>2</sub>. The collector load is the tuned circuit L<sub>1</sub>, C<sub>1</sub>, and this, in conjunction with the crystal, gives 180° phase shift from the collector to the base at the crystal frequency of 27 Mc/s, whereupon the circuit oscillates at this frequency.

A fraction of the oscillator signal is fed, via C<sub>3</sub>, to the emitter of the power amplifier stage, TR<sub>2</sub>, which is wired in the grounded base configuration. The signal at the collector of TR<sub>2</sub> is fed into a complex tuned circuit, which includes the centre-loaded aerial and C<sub>4</sub>, C<sub>5</sub> and L<sub>3</sub>. This tuned circuit is necessary in order to suppress harmonic radiation, which would otherwise cause excessive TV interference on Band I channels. The p.a. stage is effectively a.c. decoupled from the supply line by L<sub>4</sub> and C<sub>6</sub>.

The transmitter is "keyed" by means of a push-button On-Off switch wired in series with the negative supply line from the batteries. An 18 volt supply is used.

Also shown in the diagram is a "luxury" feature, which may, if preferred, be omitted. This is an output monitor, which is fitted into the transmitter case by means of a jack plug and socket. The signal that is fed into the aerial has a small part tapped off and fed, via C<sub>9</sub>, to the inductive load L<sub>5</sub>, and that signal is then rectified and filtered by D<sub>1</sub> and C<sub>10</sub>, the d.c. output being fed to the meter socket and thence to the meter. This gives an indication of the presence of a signal at the base of the aerial. It must be emphasised that, in this particular transmitter, the output meter can *not* be relied on for use as a tuning meter, and a separate field-strength meter is still essential when setting up the transmitter. If the output meter facility is not required, C<sub>9</sub>, C<sub>10</sub>, L<sub>5</sub>, D<sub>1</sub>, R<sub>4</sub> and the socket need not be fitted in the transmitter.

- A - drill to clear self-tapping screw
- B - drill to clear BBA screw
- C - 1/4" dia
- D - drill to clear 18 s.w.g. wire

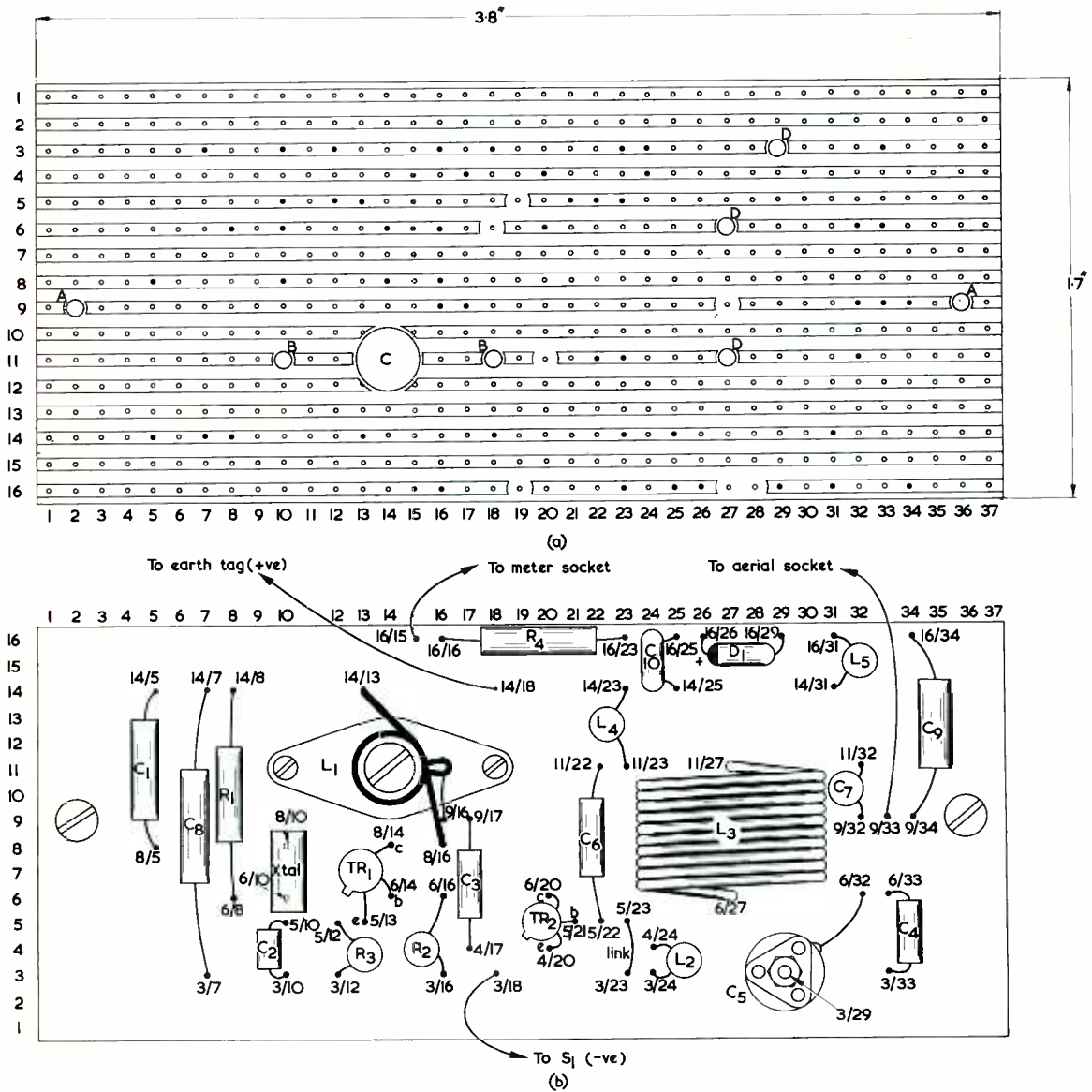


Fig. 4 (a). The copper side of the Veroboard after the strips have been cut and the holes drilled  
 (b). The plain side of the Veroboard with components mounted. Each connection has a two-figure code, the first figure indicating the strip and the second figure the hole along the strip

**Construction**

The circuit is wired up on a piece of Veroboard panel, with 0.1in hole spacing. It should be noticed that this is a far smaller matrix than that usually

used. In case of difficulty, suitable panels can be obtained from Newbury Radio (Forest Gate) Ltd. at the address shown in the Components List.

Start construction by cutting the Veroboard panel



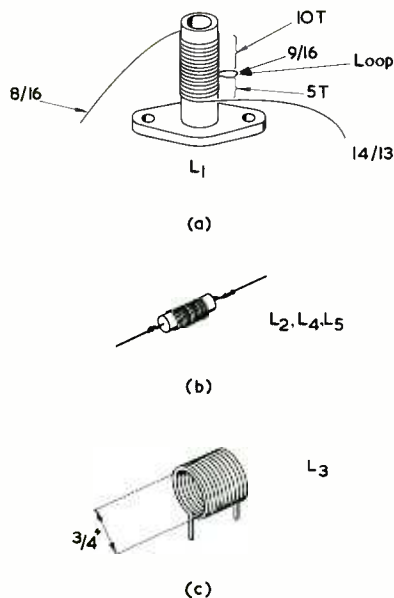


Fig. 5 (a). How coil  $L_1$  is wound

- (b). Coils  $L_2$ ,  $L_4$ , and  $L_5$ . These each consist of 50 turns on a high value resistor  
 (c). Coil  $L_3$  is self-supporting, and has 10 turns

to size and carefully break the continuity of the copper strips, as shown in Fig. 4 (a), with the aid of a small drill or special cutting tool that is available for this operation. Next, drill the small holes in the panel, as indicated.

Wiring up of the panel should be carried out "by numbers", in the following manner:

(1) Secure the 0.27in diameter Radiospares coil former, with iron-dust core, in place on the panel with the aid of two 8BA screws and nuts. Now, using 24 s.w.g. enamelled copper wire, close-wind the coil  $L_1$  on the former, as shown in Fig. 5 (a). Wind clockwise from the base upwards for 5 turns, form a loop, and then continue the winding, still clockwise, for another 10 turns, finally soldering the free end of the wire in place on the Veroboard. Solder a lead from the tap to the Veroboard panel, as shown in Fig. 4 (b).

(2) Take a small 3-pin transistor holder (see Components List) and remove the centre pin; now solder the modified holder in place on the panel by means of the two remaining pins. Press the sub-miniature 27 Mc/s crystal in place in the holder.

(3) Wire  $R_1$ ,  $R_2$ ,  $R_3$ ,  $C_1$ ,  $C_2$ , and  $C_8$  in place. Also solder transistor  $TR_1$  in place, taking care to ensure that it is wired with correct connections, and using a heat shunt on the leads when soldering. Check the rear (copper side) of the panel and make sure that no short-circuits are occurring across the lands between the copper strips. The circuit can be given a simple functional check at this stage by temporarily connecting the 18 volt supply to strips 3 and 14,

taking care to use the correct polarity (See Fig. 4 (b)), and placing the aerial of the field-strength meter very close to  $L_1$ . If no reading is obtained, adjust the core of  $L_1$  until the circuit oscillates correctly.

(4) Remove the temporary battery connection and wire  $C_3$  and  $TR_2$  in place. Wire in the shorting link from the negative line to the  $TR_2$  base circuit.


(5). Wind the three small inductors,  $L_2$ ,  $L_4$ , and (if the output meter is to be fitted)  $L_5$ , in the following manner. Take a high value (100k $\Omega$ )  $\frac{1}{4}$  watt 20% resistor; take a coil of 36 s.w.g. enamel and silk covered copper wire, bare  $\frac{1}{2}$ in at one end and solder the bared wire to one lead of the resistor, close up to the resistor body<sup>3</sup>. Now wind 50 turns of wire tightly around the resistor body and finish off by baring the free end of the wire and soldering to the remaining lead of the resistor. The windings may be scramble or pile-wound. Wire these inductors in place on the Veroboard panel.

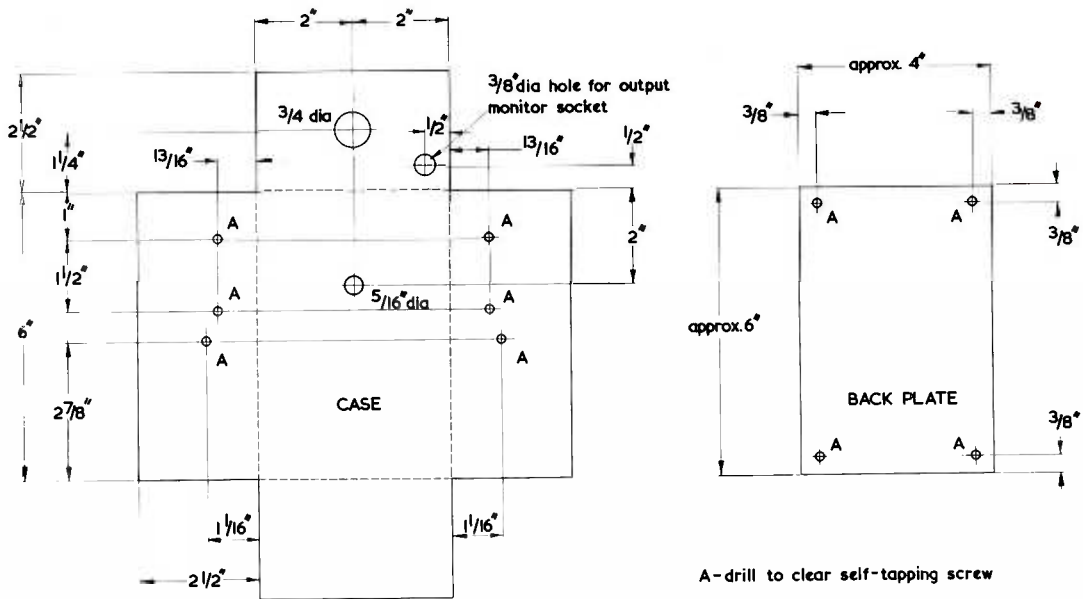(6). Make coil  $L_3$  by close-winding 10 turns of 18 s.w.g. enamelled copper wire on a  $\frac{3}{4}$ in diameter former; remove the coil from the former and solder


<sup>3</sup> The resistors available in the home-constructor market under the nominal description "quarter watt" vary somewhat in dimensions. The resistors used in the prototype for  $L_2$ ,  $L_4$  and  $L_5$  had a body length of  $\frac{3}{4}$ in and a diameter of approximately  $\frac{1}{4}$ in, and resistors of similar dimensions should be employed by constructors—Editor.




An internal view of the transmitter. This also shows the angled corner brackets, to which the back plate is secured




(a)

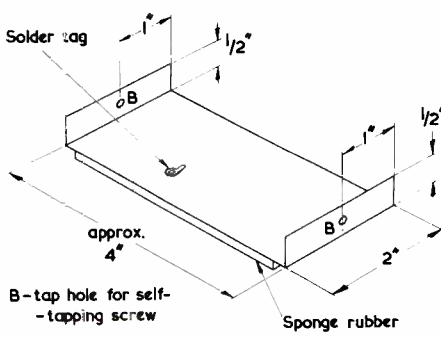

(b)

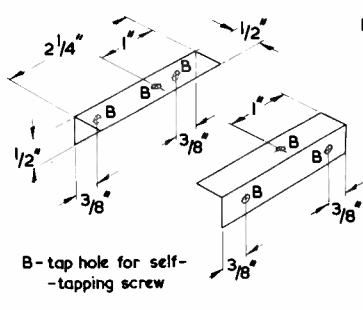

(c)

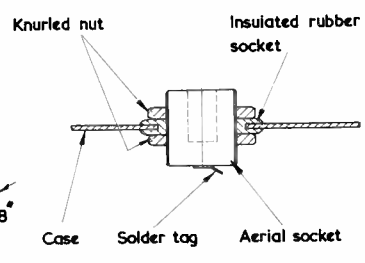

(d)

Fig. 6 (a). The case and back plate of the transmitter. The case is a standard 6 x 4 x 2 1/2 in chassis to which angle brackets are fitted (not shown here). The back plate is secured to these brackets  
 (b). The battery bracket. A piece of 1/4 in sponge rubber is glued to the underside of this and rests directly on the battery terminals  
 (c). The brackets used for mounting the Veroboard. A rubber grommet is glued above each "B" hole, as described in the text  
 (d). How the aerial socket is fixed to the case

in place on the Veroboard. Now wire the remaining circuit components, including, if required, those of the meter circuit, in place on the panel. Do not, at this stage, connect the battery supply to the circuit.

(7). Make the transmitter case and metal-work, as shown in Fig. 6(a). On the prototype, a standard 6 x 4 x 2 1/2 in chassis, with angled corner brackets, was used as a case. The aerial specified, which screws into the holder fitted in the hole at the top of the case, must be used. The two batteries are held in place by the sponge-rubber faced bracket, which, in turn, is held in place by self-tapping

screws. The Veroboard panel is held in place on the two small, angled brackets of Fig. 6(c), which, in turn, are secured to the side of the case by self tapping screws. To prevent the underside of the Veroboard panel short-circuiting against the angle brackets, a pair of rubber grommets are glued to the brackets with Bostik, and act as shock absorbing stand-off insulators. If the meter jack is to be fitted, short circuits can be prevented between the jack and the case by sticking a few pieces of Fablon or a similar self-adhesive insulating material to the inside of the case at the "danger" spots. The small push-button On-Off switch,

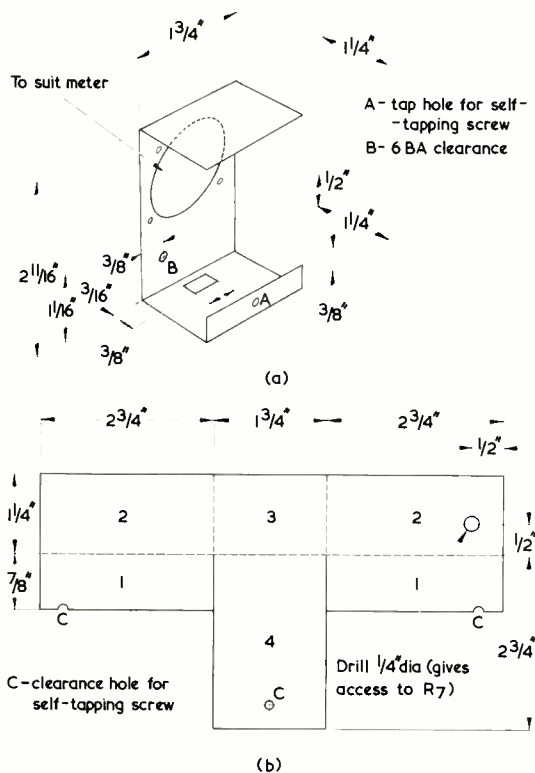


Fig. 7 (a). The front panel of the output monitor  
 (b). The monitor cover, before bending

which *must* be of the type specified, is mounted to the inside front of the case. The case is "earthed" to the positive supply line via an earth tag bolted to the battery securing bracket. See Fig. 6(b). The back-plate is secured to the case by means of self-tapping screws, which screw into the angled corner brackets on the case.

(8). When the case, metal work, and Veroboard circuitry are complete, solder one end of a 2½ in length of insulated wire to a battery terminal (for the positive connections) and the other end to the earth tag on the battery bracket; solder an additional length of wire (approximately 5 in long) from the earth tag to the positive supply connection on the Veroboard. Now take a 4 in length of wire, solder one end to the negative battery terminal, and the other end to one side of the push-button On-Off switch. Solder an additional length of wire, approximately 4 in long, from the remaining side of the On-Off switch to the negative supply connection on the Veroboard panel. Now solder a 2½ in lead from the aerial point on the Veroboard panel to the aerial socket at the top of the case. If the monitor is to be fitted, wire the lead from the panel to the monitor jack. Finally, mount the Veroboard panel over the two rubber grommets

and secure the panel to the small angled brackets by means of self tapping screws.

(9). Fit the two 9 volt batteries in place, joining them electrically by two terminals soldered to a short length of wire, and, after fitting the positive and negative output leads in place, clamp the batteries down with the battery bracket, making sure that no short-circuits occur to the case. Fit the centre-loaded aerial in place and extend it fully. Now place the field-strength meter a couple of feet away from the transmitter, and press the keying button; an indication should be obtained on the field-strength meter. Adjust the iron-dust core of L<sub>1</sub> for maximum signal strength, then turn the core back a full turn. Next trim C<sub>5</sub>, for maximum signal, moving the field-strength meter to about 10–12 feet away from the transmitter, then alternately adjust the aerial and C<sub>5</sub> for maximum signal strength. As an indication of the results to expect, at a range of 10 feet with the centre of the field-strength meter aerial in the same plane as the centre of the transmitter aerial, the two aeriels being parallel, an indication of between half and full scale should be obtained on the field strength meter when set for maximum sensitivity. The transmitter battery drain should be approximately 28mA when transmitting.

Once these adjustments have been made, the transmitter is complete and ready for use. **It must be noted that the keying button must not be pressed when the aerial is removed or fully retracted, as damage to the output transistor may result.**<sup>4</sup> The back panel can be secured to the case, any small adjustments for maximum output being made at the aerial tuning slug from this point on.

### Output Monitor

Fig. 7 shows the constructional details of the output monitor, if required. The front panel is made in light gauge aluminium to the dimensions shown in Fig. 7 (a), the meter hole being cut, with the aid of a fret-saw fitted with a metal cutting blade, *after* the panel has been bent to shape. The jack plug is a Radiospares "Standard" type and it is locked in position by the body of the moving coil meter.

In Fig. 7 (a), hole "B" is 6BA clear. A solder tag is fitted at this hole, one tag of the skeleton potentiometer, R<sub>7</sub>, being soldered to this tag.

The cover is made of very light gauge aluminium. It is initially cut as shown in Fig. 7 (b). Then, bend parts 1 upwards at right angles to parts 2. Next, bend parts 2 upwards at right angles to part 3. Coat the rear of parts 1 and the front of part 4 with Araldite adhesive, and bend part 4 upwards at right angles to part 3 until parts 1 and 4 are in contact. Bind with elastic bands and leave until the adhesive has set. Next drill hole "C" in parts 1 and 4 to line up with hole "A" in the front panel. A self tapping screw passed through these holes secures the assembly

<sup>4</sup> If desired, a separate on-off switch, in series with the negative supply lead, could be incorporated to obviate the risk of damage should S<sub>1</sub> be pressed inadvertently.—Editor.

together. Before assembly, the  $\frac{1}{4}$ in hole which provides access to R<sub>7</sub> must also be drilled.

The wiring inside the monitor is of a simple nature and may be carried out after consultation of the circuit diagram and the photograph of the internal view. When completed, the case may, if desired, be covered with Fablon or a similar self-adhesive decorative plastic. Other finishes will also suggest themselves to the constructor. It should be noted that the value of R<sub>5</sub> may require adjustment after completion of the transmitter and monitor, in order to obtain best meter indications.

#### Finishing

To give a neat finishing touch to the transmitter

and monitor, appropriate wording may be applied to the front panels by means of Panel-Signs transfers or direct lettering.

#### Next Month

This particular series of three articles will be concluded next month when constructional details of a super-regenerative single channel "carrier" receiver, suitable for use with this transmitter, will be given. Scheduled for the near future are further articles by the same author describing the construction of more complex equipments.

---

# THE DESIGN AND CONSTRUCTION OF MEASURING BRIDGES

Part 2

by W. KEMP

*In this second article in our 3-part series on general attributes of bridge circuits, our contributor discusses the design of a precision Wheatstone bridge for resistance measurement, and describes a novel design for a low-cost decade resistance box. Also introduced is the subject of a.c. bridges*

IT WAS MENTIONED IN THE LAST ARTICLE that a practical limit is set to the maximum resistance which the bridge can read by the voltage available and the sensitivity of the indicator. There is also a practical limit to which the bridge can accurately read low values of resistance, and this is set by the contact resistance of the switches and by the unwanted resistance of the bridge wiring.

While neither of these problems can be completely eliminated, they can be reduced. The wiring should be kept as short as possible and should be of a reasonably heavy gauge in order to reduce trouble from its resistance, and all soldered joints must be well made.

Regarding the switching, there is of course a certain amount of resistance between the contacts and the wiper of any switch, and unfortunately this resistance is not constant. While it might only be of the order of 0.05 $\Omega$  or less, it must be remembered that this represents an error of 5% to a 1 $\Omega$  resistor. Special switches are available with very low contact resistance for use in precision instruments, but these only serve to reduce and not eliminate the problem, and they are rather on the expensive side. If desired, switching can be eliminated altogether from the bridge, terminals

being used instead, but this will result in a bridge that is rather unwieldy to use, and it is not recommended unless it is essential that very low values of resistance be known to a great accuracy.

As in most cases in electronics, the best solution seems to be to arrive at a compromise and accept a unit that has a high degree of accuracy over most of its range, but a slight deterioration on its lowest range, and thus retain the advantage of ease of use.

Because of the errors that may be introduced by the switch contact resistance it is preferable not to use resistors of lower values than 10 $\Omega$  as standards in the bridge unless absolutely necessary.

#### Designing a Wide Range Precision Bridge

Let us assume that it is desired to build a Wheatstone bridge capable of reading to an accuracy of better than 1% over the resistance range of 10 $\Omega$  to 100M $\Omega$  and as accurately as possible down to a fraction of an ohm.

As a starting point, consider the variable arm R<sub>2</sub>. (This is shown in Fig. 1, repeated from last month's article). Here, decade units are recommended. If only three decades are used the maximum accuracy over the entire range (say, when reading 112.5 $\Omega$



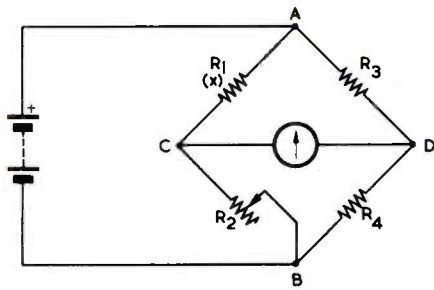


Fig. 1. The basic Wheatstone bridge. (This diagram is reproduced here for reference)

on the 1000Ω range) that can possibly be obtained is slightly better than 0.5%, i.e. a reading of either 112 or 113Ω. If, therefore, a higher degree of accuracy than this is required, it will be necessary to use a four decade unit.

The lowest value of resistance that can be used with any degree of reliability of calibration in the decade box will be 1Ω, as already mentioned, and even here an error of several per cent may be expected.

Two possibilities now present themselves. Either a four decade box with the first decade reading in steps of 1Ω giving a total of 10,000Ω overall, may be used, or alternatively, a three decade box preceded by a calibrated wire-wound potentiometer of 1Ω or 10Ω may be used.

There is a great deal to be said in favour of the second alternative, using a potentiometer of 1Ω value, as it is by far the easiest to construct and can still be built to give a guaranteed accuracy, under even the worst conditions, of better than 0.1%, and will generally read better than 0.05%. Such a decade box will therefore have an overall value of 1,000Ω, and from this the values of the remaining components can be deduced.

The maximum reading on the lowest range of the bridge will be 10Ω (see the Table) and successive ranges will go up in multiples of 10. As mentioned earlier, the lowest value of standard that will be used in the ratio arms is 10Ω.

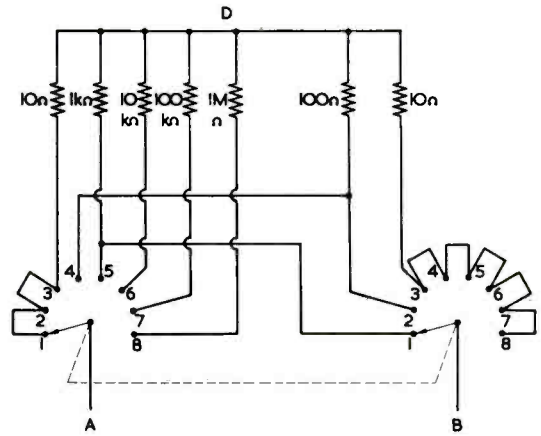


Fig. 6. A switching circuit which provides the ratio arms for a Wheatstone bridge with the minimum of resistors

Remembering that  $R_2$  has an overall value of 1,000Ω and that the maximum reading on the lowest range is 10Ω, from the formula  $R_1 \times R_4 = R_2 \times R_3$  it can be seen that  $10 \times R_4$  must equal  $1,000 \times R_3$ . The minimum value for  $R_3$  is 10Ω so that to satisfy the formula  $R_4$  must be 1,000Ω. The component values for the first range, which will be called Range 1, have thus been deduced, and by a similar process the values of the remaining seven ranges can be established. The Table gives a tabulated list of the results obtained.

It will be noticed from the Table that the only time that two resistors of the same value are in circuit together is on Range 3, when two 10Ω resistors are used. It is therefore possible to arrange the switching of the ratio arms in such a way that only seven resistors need be used to cover the complete range of the bridge. Fig. 6 shows the switching layout that can be employed to achieve this. It can be seen that one 8-way 2-pole switch is used, but in practice this will probably consist of a ten way switch suitably modified. One end of each resistor is joined to a common point or bar. The

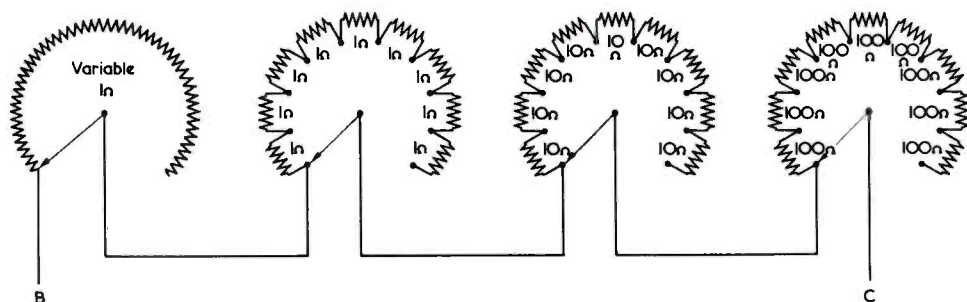


Fig. 7. A decade box which offers continually variable values of resistance from less than 1Ω to 1,000Ω

references A, B and D correspond to the similarly marked points in Fig. 1.

There are two possible ways in which the decade boxes may be built. Fig. 7 shows one method, in which three 10-way single pole switches and one potentiometer are used in conjunction with 27 resistors.

The alternative to this is based on quite a different system. It is a fact that if a series of numbers, starting with 1, are taken up to the power of two, i.e., 1,2,4,8,16,32, etc., then any number can be obtained from the sum of some of these. For example,  $15 = 8 + 4 + 2 + 1$ . Again,  $19 = 16 + 2 + 1$ .

In our case it is only necessary to go up to 9 and this can be done using resistors of 1,2,4, and 8 units value, so that it can be arranged that, instead of using nine resistors in each decade, only four need be used. A price has to be paid for this reduction in components in the form of more complex switching arrangements.

It will be noticed that with this four-resistance method that in order to obtain a value of  $7\Omega$  it is necessary to sum three resistors, i.e., 1,2 and  $4\Omega$ . This will necessitate the use of a 3-pole switch. If the  $8\Omega$  resistor is changed for one of  $7\Omega$ , however, the switching can be carried out with a 2-pole switch, as long as numbers greater than 9 are not required. Fig. 8 shows the wiring layout for the complete decade box using this system. Three

TABLE

Resistance values in  $R_3$  and  $R_4$  for Ranges 1 to 8 ( $R_2 = 0-1,000\Omega$  variable resistor)

Range	$x(\Omega)$	$R_3$	$R_4$
1	0-10 $\Omega$	10 $\Omega$	1k
2	0-100 $\Omega$	10 $\Omega$	100 $\Omega$
3	0-1k $\Omega$	10 $\Omega$	10 $\Omega$
4	0-10k $\Omega$	100 $\Omega$	10 $\Omega$
5	0-100k $\Omega$	1k $\Omega$	10 $\Omega$
6	0-1M $\Omega$	10k $\Omega$	10 $\Omega$
7	0-10M $\Omega$	100k $\Omega$	10 $\Omega$
8	0-100M $\Omega$	1M $\Omega$	10 $\Omega$

10-way, 2-pole switches and one  $1\Omega$  potentiometer are used, in conjunction with twelve resistors. The references B and C correspond to the similarly marked points in Fig. 1.

#### Choice of Resistors as Standards

The type of resistors used as standards in the bridge will depend on the accuracy required from the instrument. If only "rough" indications are required then 2% to 5% carbon resistors may be used. If it is required to have a final accuracy

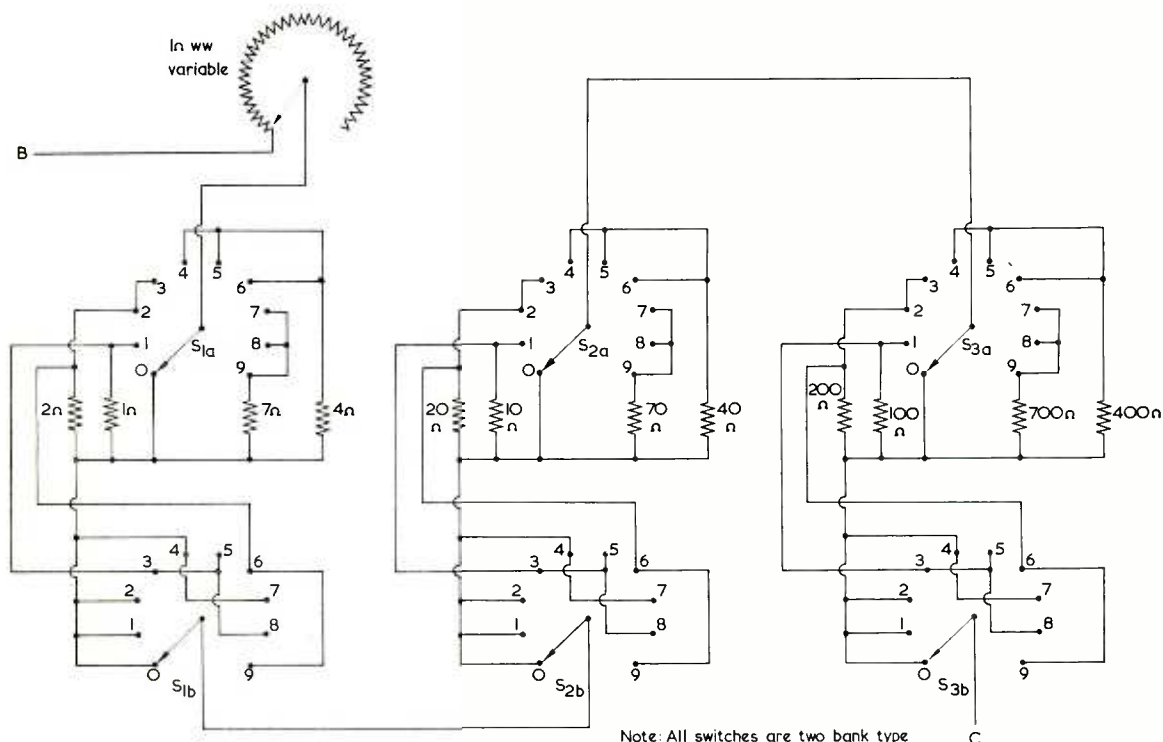


Fig. 8. A switching circuit which offers the same range as is given by Fig. 7, but with much fewer resistors

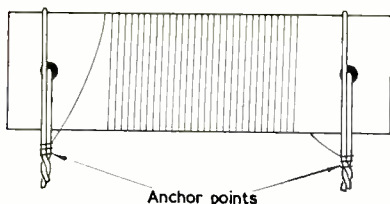


Fig. 9. Winding a resistor on a flat strip of Paxolin

of about 2% then 1% high stability or wirewound types must be used. At accuracies greater than this the cost of commercial components becomes prohibitive, and the amateur will probably find it necessary to make his own. This is a time-consuming but not difficult job, and there is no reason why the patient constructor should not end up with a bridge that can measure to an accuracy of a fraction of 1%.

Before going on to the actual construction of the resistors, it will be as well to make a few notes about the different types of resistance wire that can be used. Broadly speaking, there are three types, Eureka or Constantan, Manganin, and Nickel-chrome.

Nickel-chrome has a resistivity about 61.5 times that of copper which is the highest for the normal resistance wires, so that it is most used where very high resistances are needed and other types of wire would have to be excessively long. It can also be run at a high temperature without damage. Its temperature coefficient per degree Centigrade is 0.0002.

Eureka or Constantan has a resistivity about 28.5 times that of copper. Its temperature coefficient is 0.00001, far better than that of Nickel-chrome. It is easily soldered, but does not stand up well to excessive temperatures.\*

Manganin has a resistivity slightly less than that of Eureka, but has an even better temperature coefficient. It is very difficult to solder and will

\*There appear to be discrepancies between the temperature coefficients quoted by different sources for resistance wires and, whilst these discrepancies do not detract from the author's argument, they may be briefly referred to. Thus, London Electric Wire Company and Smith's Ltd. quote a temperature coefficient of  $\pm 0.00004$  per  $^{\circ}\text{C}$  for their Eureka wire, 0.000098 per  $^{\circ}\text{C}$  for their "Vacrom 80/20" Nickel Chrome wire, and 0.000202 per  $^{\circ}\text{C}$  for their "Vacrom 15%" Nickel Chrome wire.—EDITOR.

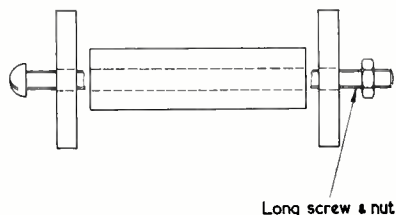


Fig. 10. Long lengths of resistance wire may require the use of a bobbin



Resistance wire twisted together and then wound on former

Fig. 11. Preparing resistance wire for a non-inductive resistor

normally need to be silver-soldered at red heat. After winding has been completed it should be completely coated with shellac varnish. It must then be annealed for at least 24 hours at about  $135^{\circ}\text{C}$ . This process can result in resistors that have a temperature coefficient of almost zero at normal temperatures, and for this reason Manganin is generally used for the better types of standard resistors.

It is unlikely that the reader will be willing to take all the trouble involved in the construction of the Manganin types. Eureka is nearly as good, and is definitely good enough for the present purpose, so it will be assumed that Eureka wire will be used.

The general procedure for making the resistors is to first decide which gauge of wire to use, and then look up a set of tables and work out the length of wire needed to give the desired resistance. When this has been decided, cut off a length slightly longer than that indicated.

A former is now made up from a strip of Paxolin or similar material, as shown in Fig. 9. The dimensions will generally be about  $\frac{1}{4}$  in by 1 in. The heavy wires shown locked to the Paxolin in the diagram are used as anchor points for the resistance wire. One end of the resistance wire is soldered to one of the anchor wires and the rest is wound round the former. The other end is temporarily soldered to the remaining anchor point. The overall resistance should now be checked against a standard, and adjusted as necessary. When the adjustments have been finalised the soldered joints should be firmly made and the resistance re-checked. On the larger resistors, where considerable lengths of wire may

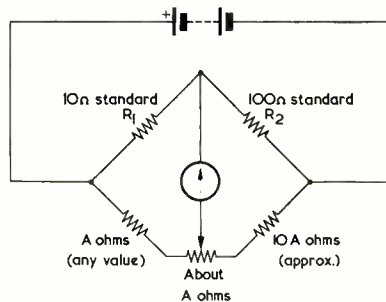


Fig. 12. A set-up which enables highly accurate resistors to be made up with the aid of two standards only

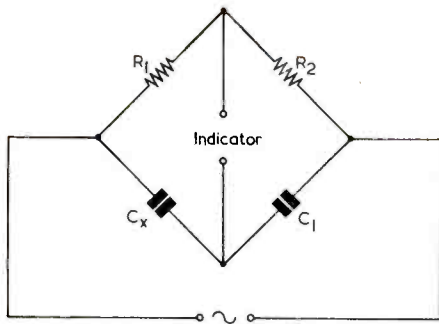


Fig. 13. The De Sauty bridge

be used, it may be necessary to make them up on bobbins, as shown in Fig. 10.

If any of the standards made in this way are to be used in a.c. circuits they must be non-inductively wound by winding the resistance wire back on itself so that the magnetic field set up by a current flowing in the wire is cancelled by an opposing field in another part of the wire, as shown in Fig. 11.

It has been mentioned that when making a resistor it is necessary to check it against a standard. Some readers will have such a facility at their place of work, but those that have not will probably find that the local technical college has one of very high accuracy, and if a letter is written to the Principal of the establishment explaining things he will no doubt give permission to use it.

Failing this, a third method is available. It will be necessary to purchase two resistors of as high an accuracy as possible at least 0.2% of 10Ω and 100Ω values. These are put in a temporary bridge. With reference to Fig. 1, the 10Ω resistor will be  $R_1$  and the 100Ω resistor will be  $R_2$ .  $R_3$  and  $R_4$  are formed by a resistor, a potentiometer, and another resistor of about ten times the value of the first one in series. See Fig. 12. The indicator is connected between the junction of  $R_1$  and  $R_2$  at one end and to the slider of the potentiometer at the other.



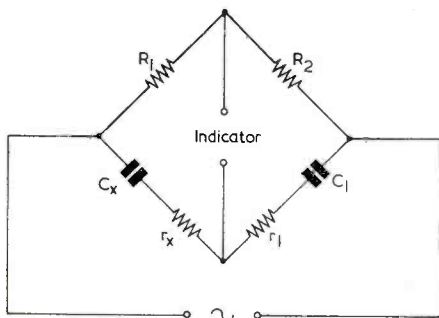


Fig. 14. The circuit which results when capacitor resistance is taken into account

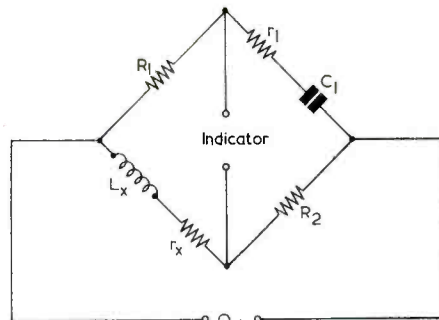

(a)

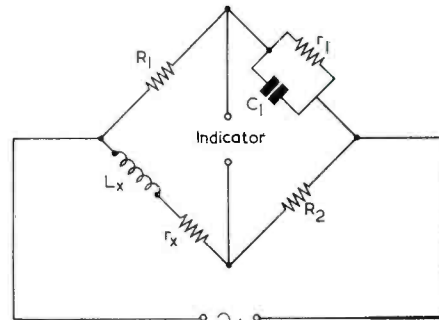

(b)

Fig. 15(a). The Hay bridge  
(b). The Maxwell bridge

The potentiometer is now adjusted until the indicator shows a null. The ratio arms,  $R_3$  and  $R_4$ , will now be in the exact ratio of 1 : 10.  $R_1$  can now be removed and a home-made 10Ω resistor tried in its place, and adjusted if necessary. Any number of 10Ω resistors can be made in this way. When a sufficient number have been constructed  $R_1$  should be replaced and  $R_2$  removed, and any desired number of 100Ω resistors made in the same way.

$R_2$  should again be removed and replaced by  $R_1$ , the 10Ω resistor. In the  $R_1$  position a 1Ω resistor will be needed to give balance, so any number of 1Ω resistors can be made. In the same way, when  $R_2$  (100Ω) is removed and put in the  $R_1$  position, 1,000Ω resistors can be made in the  $R_2$  position. The resistors made in this way can then be substituted in the ratio arm positions and a further series of higher value resistors made.

When the decade box is made, the 1Ω potentiometer should first be calibrated at the 1Ω point only. Then a 1Ω resistor is made up, as above.  $R_3$  and  $R_4$  are next made, say, 10Ω each, so that a ratio of 1 : 1 is obtained. The 1Ω potentiometer and 1Ω resistor are now put in series in the  $R_2$  position, giving 2Ω overall resistance. A 2Ω



resistor can then be made up in the  $R_1$  position. This is then put in series with the  $1\Omega$  resistor and potentiometer, making  $R_2$   $4\Omega$  overall, and a  $4\Omega$  resistor can then be made up in the  $R_1$  position. This procedure is repeated for the remaining resistors.

When making resistors of over, say,  $1,000\Omega$  it will probably be found best to buy a high stability resistor of just under the required value and put it in series with a home-made one to bring it up to the required value.

As a guide to the lengths and gauges of wire needed to give certain resistance values, the following list, for Eureka wire, should be of help. The lengths given are approximate only.

$1\Omega = 9$ ins. of No. 28 s.w.g.

$10\Omega = 23.5$ ins. of No. 36 s.w.g.

$100\Omega = 65$ ins. of No. 42 s.w.g.

$1000\Omega = 55$ feet of No. 42 s.w.g.

The Eureka wire used may conveniently be d.c.c. or similar.

#### A. C. Bridges

When considering the Wheatstone bridge it was pointed out that at balance  $\frac{R_1}{R_2} = \frac{R_3}{R_4}$ . This of course is true in a d.c. circuit only. In an a.c. circuit, impedances must be considered and the formula becomes  $\frac{Z_1}{Z_2} = \frac{Z_3}{Z_4}$ , so that reactances as well as resistances must be taken into account.

The basic Wheatstone bridge can therefore be modified to form the basis of a large variety of a.c. bridges, each with its own particular advantage

and disadvantages, for the measurement of inductance and capacitance, etc.

The choice of a.c. bridges is so great that space does not permit a description of them all, and only the three that are of most use to the amateur will be dealt with here.

A suitable circuit for measuring capacitance is shown in Fig. 13. From what we have seen up to now, the circuit is self-explanatory. The bridge is to a large degree, independent of frequency. At balance

$C_x = \left(\frac{R_2}{R_1}\right)C_1$ . In practice all capacitors and inductors have some value of series resistance, so that the true circuit becomes as shown in Fig. 14. To obtain a true reading on the bridge this series resistance must also be balanced out. In Fig. 14  $r_x$  represents the inherent series resistance of the unknown capacitor, and  $r_1$  is the control used to balance it out.

At balance  $r_x = \left(\frac{R_1}{R_2}\right)r_1$ . The  $r_1$  control can be calibrated to give an indication of the power factor of the component under test. The bridge of Fig. 13 is sometimes described as the DeSauty bridge.

Two circuits for the measurement of inductance are shown in Fig. 15. It will be noticed that the reactive components are in opposite arms and that the inductance is balanced by a capacitor. The two bridges shown are the Hay (Fig. 15 (a)) and the Maxwell (Fig. 15 (b)). In each case it is found that at balance  $L_x = C_1 \times R_1 \times R_2$ . The Hay bridge is better for measuring large values of inductance.

In an actual test instrument one bridge can be converted to another type by suitable switching.

*(To be concluded)*

---

## RSGB NATIONAL MOBILE RALLY

**Woburn Abbey, Bedfordshire**

*by kind permission His Grace the Duke of Bedford*

**SUNDAY, SEPTEMBER 11, 1966**

- |   |                                     |
|---|-------------------------------------|
| ★ Park opens 11 a.m.                                  | ★ 160 metre Pedestrian D/F Hunt     |
| ★ State Apartments open                               | ★ Children's and Novelty Sports     |
| ★ More than 3,000 acres and 2,000 animals             | ★ Children's Lucky-dip              |
| ★ Children's Playground, Pets Corner and Boating Lake | ★ Surplus Sale and Trade Exhibition |
| ★ Restaurants and Snack Bars                          | ★ Grand Raffle (Ladies and Gents)   |

**CAR PARKING — Specially reserved Rally Car Park**

**TALK-IN STATIONS — GB2VHF and GB3RS**

on 2 metres (144.86 Mc/s); 4 metres (70.260 Mc/s); 80 metres (3.75 Mc/s — s.s.b.) and 160 metres (1940 kc/s)

**ORGANISED BY THE RADIO SOCIETY OF GREAT BRITAIN**

**I**N THE LAST ARTICLE IN THIS SERIES WE INTRODUCED the subject of oscillator frequency stability and noted that there are four main reasons for variation in oscillator frequency after switching on. These consisted of thermal effects resulting from, in particular, the rise in temperature given by the warming up of the oscillator valve; changes in supply potentials; ingress of moisture into components; and mechanical factors. We considered the first two or these factors in detail in the previous article, and we shall next carry on to briefly examine the remaining two.

#### Ingress of Moisture

Ingress of moisture into oscillator components can cause variations in oscillator frequency, these


due to vibration or handling. Another example which falls into this category is *microphony*. Microphony describes the condition where oscillator frequency varies due to vibration or noise impinging on the oscillator components. A common instance of microphony occurs with air-spaced variable capacitors, whose plates may vibrate in sympathy with sound or vibration. If a capacitor of this type is employed in an oscillator circuit it can vary oscillator frequency at the frequency of the sound or vibration. This effect can prove troublesome in radio receivers when the sound from the loudspeaker reaches a variable tuning capacitor, either via the air or by way of the chassis. The capacitor may be mounted on soft rubber or p.v.c. grommets to prevent this trouble.

# understanding

## “Squegging” and Receiver Reaction

By W. G. Morley

# radio

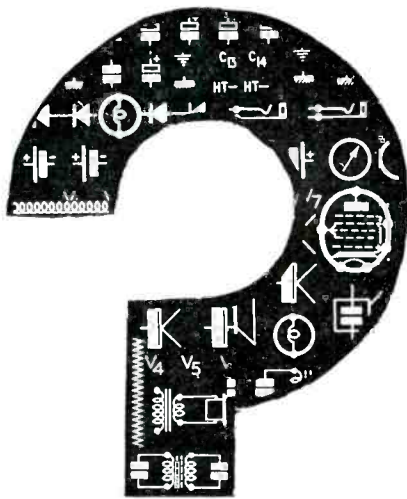

usually being of a long term nature. A short term effect under severe conditions is also feasible, if water is driven out of the components under local heat from valves and other components.

Since it is common practice to protect coils by impregnation with wax, varnish or similar materials, and to employ protective coatings for capacitors, frequency variation due to the effects of moisture ingress is not liable to give trouble provided that good-quality components are employed in the oscillator circuit. Nevertheless, the possibility of moisture ingress should not be completely dismissed from mind, particularly with oscillators which are required to have a high degree of long term stability.

#### Mechanical Factors

Mechanical factors may cause variations in oscillator frequency. A typical example is given by a poor mechanical design which allows components in the oscillator tuned circuit to move in position

#### Amateur Transmitter Oscillators

When, in the June issue, we described the Franklin oscillator, we saw that it was possible to couple the single tuned circuit that this oscillator requires to the remainder of the circuit by way of two small fixed capacitors having values of the order of several picofarads or less. As was stated then, this gives the tuned circuit a high level of isolation from stray capacitances in the remainder of the circuit. We may now see that the benefit conferred is that the oscillator frequency is less likely to vary due to changes in self-capacitances in valves and other components during warm-up. If the capacitance across the tuned circuit is high compared with the small-value coupling capacitors, a very high degree of frequency stability is feasible.

This frequency stability makes the Franklin circuit attractive for amateur transmitter applications, since it is capable of providing a transmitter frequency which has good stability and is also

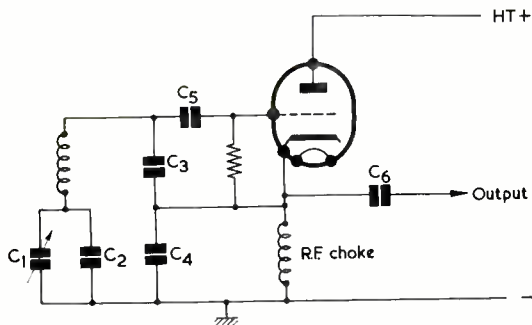


Fig. 1. The basic Clapp oscillator.  $C_5$  is the grid capacitor, whilst  $C_6$  is a coupling capacitor

capable of being varied by a panel control. In amateur transmitter parlance the oscillator then functions as a *variable frequency oscillator*, or v.f.o. The term "variable" distinguishes the oscillator, in this application, from the crystal oscillator (discussed later) which has a fixed frequency.

A variable frequency oscillator that is very popular for amateur transmitting work is shown in basic form in Fig. 1. This is the *Clapp oscillator*, and it will be seen that it is very similar to the Colpitts oscillator illustrated, in the June issue, in Fig. 347 (c). The two capacitors  $C_3$  and  $C_4$  have relatively high values, of the order of 2,000pF each, with the consequence that changes in stray capacitances in the grid-cathode circuit of the valve have proportionately less effect on oscillator frequency. The resonant frequency is adjusted by the variable capacitor  $C_1$ , which may have a maximum value, typically, of some 50 to 100pF. The fixed capacitor  $C_2$ , across  $C_1$ , may have a value of the same order, and it prevents the capacitance in series with the coil from falling to too low a value, whereupon oscillator output is liable to drop. The circuit oscillates with good stability over the relatively small range of frequencies which can be selected by  $C_1$ , this range being adequate for amateur transmitter applications. A practical Clapp oscillator will normally employ a valve having more electrodes than a triode, but this point will have to be discussed in a later article when we deal with such valves.

### Crystal Oscillators

It is common to employ a quartz crystal in fixed frequency oscillators requiring a very high degree of frequency stability, the crystal providing frequency control instead of a tuned circuit.

The crystal consists of a thin slab cut from the natural quartz crystal along a specific axis, and it is placed between two parallel metal plates which form the electrodes. Due to piezo-electric effect the crystal vibrates when an r.f. signal is applied to the two plates. The crystal can exhibit a mechanical resonance (whose frequency depends on its dimensions) and, if an r.f. signal at a mechanical resonant frequency is applied to the plates, crystal

vibration takes place at a very high amplitude. The crystal assembly then functions as though it were a tuned circuit having a very high value of  $Q$  and, when incorporated in an oscillator circuit, offers an extremely high degree of frequency stability. It is not proposed to go into any further detail here on the crystal oscillator, and it is only mentioned at this stage to present a balanced overall picture.

### "Squegging"

We have seen that it is normal practice to employ a grid leak and capacitor to provide bias for an oscillator, and these are shown in the typical oscillator circuit given in Fig. 2. When grid leak bias functions correctly the capacitor becomes charged during each positive peak of the oscillatory signal appearing at the upper terminals of the tuned circuit, and partly discharges into the grid leak during the remainder of the cycle. It then receives a charge at the next positive peak. This process results in the oscillator valve receiving the correct amount of bias needed to maintain reliable oscillation, and the amplitude of the oscillation across the tuned circuit remains constant.

Let us now take our examination of the grid leak bias circuit a little further and follow its operation from the instant of applying h.t. to the oscillator when the valve cathode is at emitting temperature. There will be, initially, a small oscillatory voltage across the tuned circuit which, due to the positive feedback and the amplification provided by the valve, very quickly rises to its full operating amplitude. At this amplitude the circuit enters a state of equilibrium. If the oscillator amplitude tended to increase, the valve would receive more bias and the duration of the positive peaks which cause anode current to flow would be shorter. The feedback currents from the anode would then be weaker, with the consequence that oscillator amplitude would reduce, reverting to its previous level.

However, should the grid capacitor be given a value which is grossly too large, the oscillator works in quite a different manner. In this instance

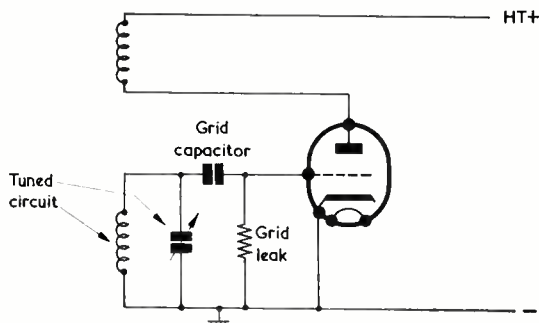


Fig. 2. The tuned grid oscillator. In company with other tuned circuit oscillators employing grid leak bias, this is subject to "squegging" if the grid capacitor has too large a value

we have the same increase in oscillation amplitude from the moment of switching on, but this time the grid capacitor charges and discharges more slowly. The oscillation amplitude rises to a level higher than occurred previously when the grid capacitor had the correct value, because the large-value capacitor takes longer to charge up to the potential which causes the requisite bias to be applied. Moreover, when the voltage across the capacitor reaches this potential, the still high amplitude of oscillation can cause it to slightly exceed the potential. The valve cannot then offer sufficient amplification to maintain the oscillation, whose amplitude commences to fall. A grid capacitor of correct value would cause the grid bias to fall at once to compensate for the reduced amplitude, but our present high-value capacitor cannot do this. The potential across its plates drops at a lower rate than the fall in oscillation amplitude, with the result that the oscillation ceases altogether. The grid capacitor continues to discharge into the grid leak until the slowly reducing grid bias on the valve becomes sufficiently low to allow oscillation to commence once more. Again, oscillation amplitude increases, and the whole process is repeated.

The overall result is that the valve goes continually in and out of oscillation, the effect being referred to as "squegging". The frequency at which squegging occurs depends mainly upon the values of the grid leak and capacitor and it can fall within the audio frequency range or it can occur at frequencies above the audio range.

It is, fortunately, a simple matter to avoid squegging since all that is required is to choose a grid capacitor whose value is not too great. A practical approach consists of employing an oscillator grid leak of 20 to 50k $\Omega$  and a grid capacitor of around 50 to 100pF; and these values should cope for most oscillators working between 500 kc/s and 10 Mc/s. Since, however, the onset of squegging is partly governed by factors in the oscillator circuit other than the grid leak and capacitor, these including the amplification provided by the valve and the tightness of coupling in the positive feedback circuit, it is difficult to state values for the grid leak and capacitor which will prevent squegging in all practical oscillators. But should squegging occur, and its existence may normally be readily recognised by the behaviour of the equipment in which the oscillator is fitted, all that is required is that the value of the grid capacitor be reduced until the effect clears.

We used the tuned grid oscillator of Fig. 2 to provide an example for our discussion of squegging. The effect can similarly occur with any other tuned circuit oscillator employing a grid leak and capacitor.

### Reaction Circuits

We have already discussed the grid leak detector,<sup>1</sup> and a typical circuit incorporating this detector

<sup>1</sup> In the October 1965 issue.

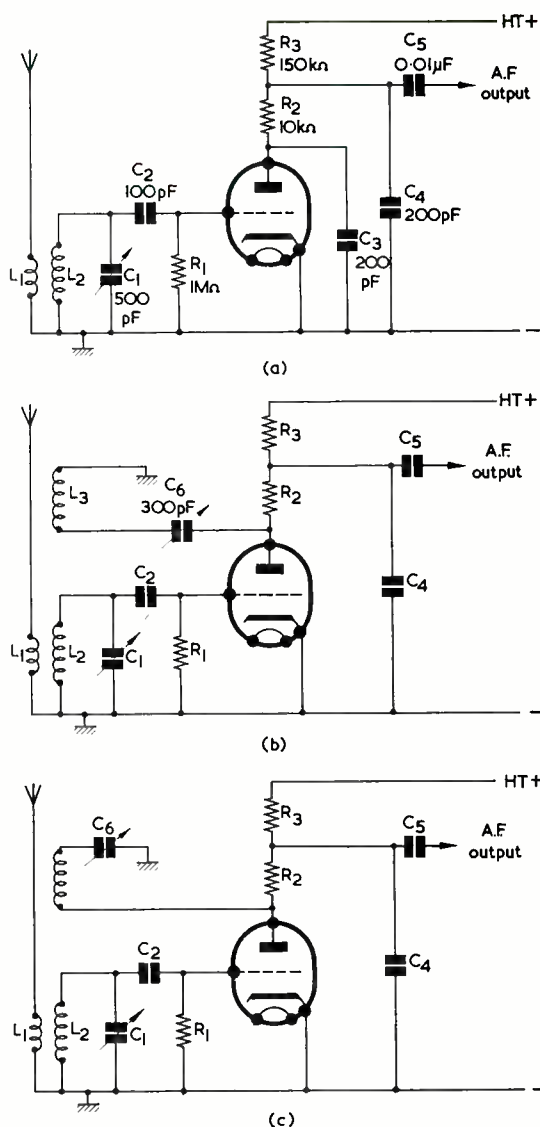


Fig. 3 (a). A typical grid leak detector circuit, with representative component values for medium wave operation. A subsequent a.f. amplifier feeding a loudspeaker or phones is assumed  
 (b). In this circuit  $C_3$  is omitted, and is replaced by the reaction components  $L_3$  and  $C_6$ . Adequate filtering of r.f. from the a.f. output is still provided by  $R_2$  and  $C_4$  when  $C_6$  is set to minimum capacitance  
 (c). If  $C_6$  is inserted on the chassis side of  $L_3$ , the frame of this capacitor may be mounted direct to chassis

is given in Fig. 3 (a). In this diagram the aerial is applied to winding  $L_1$ , which couples to the tuned winding  $L_2$ . The latter, in combination with  $C_1$ , forms a tuned circuit, and the aerial signal selected by this circuit is then applied, by way of



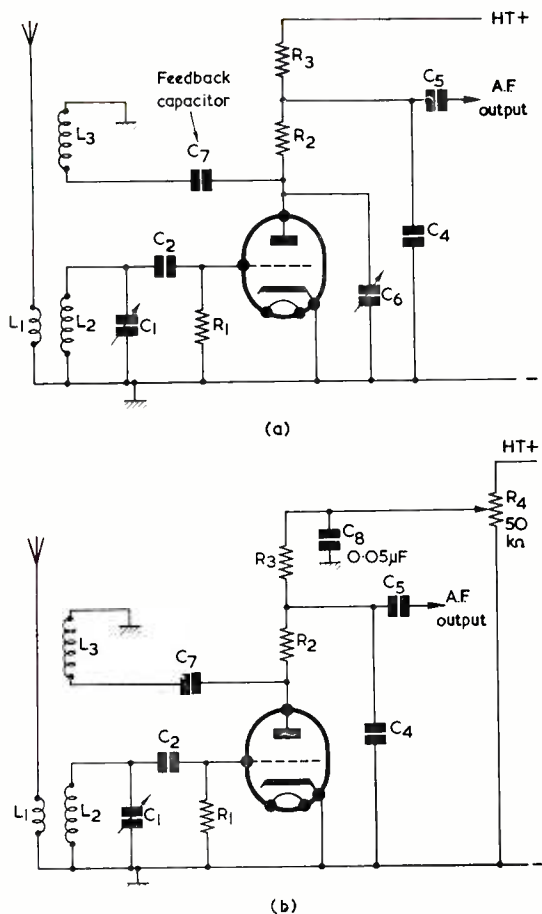


Fig. 4 (a). An alternative method of obtaining a variable control of reaction. The fixed feedback capacitor,  $C_7$ , would have a value, typically, of 100pF. The remaining capacitors and resistors have the same values as in Fig. 3

(b). Obtaining a control of reaction by means of a potentiometer.  $C_8$  is an a.f. bypass capacitor and can have the typical value shown. Since  $R_4$  will dissipate a small amount of power, it would preferably be a wirewound component

grid capacitor  $C_2$  and grid leak  $R_1$ , to the grid of the triode. An amplified version of the detected signal appears at the anode. So also does an amplified version of the radio frequency applied to the grid and, since it is normally undesirable to feed an r.f. signal to a following a.f. amplifier, this is removed by the low-pass filter given by  $C_3$ ,  $R_2$  and  $C_4$ .  $R_3$  is the a.f. anode load for the triode and  $C_5$  the a.f. coupling capacitor to a subsequent a.f. amplifier stage. Typical values for medium wave operation are given for the resistors and capacitors.

In Fig. 3 (b) we introduce a second coupling winding,  $L_3$ , this being coupled to the triode anode

by way of variable capacitor  $C_6$ . The amplified r.f. signal which previously passed through  $C_3$  now passes through  $C_6$  and  $L_3$ . It can at once be seen that we have the basic circuit for a shunt-tuned grid oscillator and that, if the value of  $C_6$  is high enough to provide sufficient feedback, the circuit will go into oscillation. In a circuit using conventional components and coils, this will occur when  $C_6$  has a value of the order of 100 to 200pF.

At capacitances in  $C_6$  below that which allows the circuit to go into oscillation, a proportion of the amplified r.f. signal is still fed back to the tuned circuit, whereupon the amplitude of the signal across this circuit increases. When we considered the basic characteristics of tuned circuits<sup>2</sup> we saw that the current magnification factor which occurs in a parallel tuned circuit is equal to its quality factor, or  $Q$ . In the circuit of Fig. 3 (b) we are, by positive feedback, increasing the current at radio frequency which flows in the tuned circuit, whereupon we are causing an increase in its *effective*  $Q$ . As a result the tuned circuit offers increased selectivity together with an increase in signal level.

The increase in selectivity and signal level becomes more and more evident as  $C_6$  is adjusted to insert more capacitance, and is at its greatest when the capacitance in  $C_6$  is just below that at which oscillation occurs. If a circuit of the type shown in Fig. 3 (b) is designed carefully, the increase in selectivity and sensitivity it provides can be extremely high. The design aim is to so arrange component values and coupling between coils that the circuit goes "smoothly" into oscillation as the capacitance inserted by the variable reaction capacitor increases. It then becomes possible to bring the circuit extremely close to the oscillation point without actually going into oscillation. The audible effect from the audio amplifier loudspeaker or earphones when a circuit of this nature goes into oscillation is the appearance of a low level hiss. In a badly designed circuit, oscillation may occur suddenly as  $C_6$  is advanced, the change in state resulting in a "plop" from the loudspeaker or earphones. An even worse condition is *backlash* in which oscillation, once commenced, can only be stopped by reducing  $C_6$  to a significantly lower value than that which caused the onset of oscillation. Neither of these conditions allows a fine setting in  $C_6$  which is just below oscillation point, and which enables the considerable increase in sensitivity and selectivity of which the circuit is capable, to be realised.

Feedback circuits of the type shown in Fig. 3 (b), in which the degree of feedback is controlled, are described as *reaction* or *regeneration* circuits. In American terminology, the feedback winding ( $L_3$  in Fig. 3 (b)) is given the colourful name of *tickler* winding. Domestic and home-constructor receivers using detectors with reaction were very

<sup>2</sup> In the February 1963 issue.

popular before the war, but they have now been largely superseded by the superhet receiver, whose functioning will be described later in this series of articles. The superhet is more complex in operation than a receiver employing a detector with reaction, but it offers improved selectivity and sensitivity without the necessity of adjusting the reaction control. Nevertheless, a receiver employing a detector with reaction is an excellent project for the home-constructor, and particularly the beginner, because it is very simple to set up and its operation is easy to understand.

In detector circuits employing reaction, it is usual to give the grid leak a value considerably higher than would be employed in the corresponding oscillator circuit. Typical values range between 200k $\Omega$  and 3M $\Omega$ , the grid capacitor being of the order of 25 to 150pF. When a directly-heated battery valve is employed as the detector, it is normal practice to return the lower end of the grid leak (which, in Fig. 3 (b), connects to the cathode of an indirectly-heated valve) to the positive rather than the negative end of the filament, it being found that this method of connection improves the "smoothness" of reaction control due to the small positive grid current which then flows below the oscillation point.

In practical circuits, it is preferable to have the reaction capacitor,  $C_6$ , on the chassis side of the reaction coupling winding, as in Fig. 3 (c), rather than on the anode side, as was illustrated in Fig. 3 (b). The capacitor still controls the feedback current flowing through coupling winding  $L_3$ , but its frame may now be mounted directly to the chassis or to a metal front panel. The method of connection shown in Fig. 3 (b) has the further disadvantage that *hand-capacitance* effects are possible. As the hand approaches the capacitor, its capacitance to the capacitor spindle can upset the balance of capacitances to chassis in the circuit, and make it difficult to reliably approach the optimum reaction point. The relatively large mass of the body would have, in this instance, a sufficiently high capacitance to the receiver chassis for the effect to occur. Hand-capacitance effects will be absent with the circuit of Fig. 3 (c), particularly if  $C_6$  is fitted to a metal front panel connected to chassis.

A fairly commonly encountered variant to Figs. 3 (b) and (c) is illustrated in Fig. 4 (a). In this case the feedback capacitor is fixed, and the variable capacitor,  $C_6$ , is connected between anode and chassis.  $C_6$  controls reaction because, as it is increased in value, it reduces the r.f. current flowing in the feedback circuit. An interesting feature is that  $C_6$  works "backwards" since, when it is set to maximum capacitance, minimum r.f. current flows in the feedback circuit. As the

capacitance in  $C_6$  is reduced, more and more r.f. current flows in the feedback circuit until the detector eventually goes into oscillation. Such a circuit is sometimes referred to as a "throttle" reaction circuit.

Another variant is illustrated in Fig. 4 (b), where  $C_7$ , the feedback capacitor, is again a fixed component. In this circuit, reaction is controlled by the potentiometer  $R_4$ . When the slider of  $R_4$  is advanced from the chassis end of its track, an increasing h.t. voltage is applied to the anode load of the valve until the circuit eventually goes into oscillation. The value of  $C_7$  will be such that oscillation occurs when the potentiometer slider is near the h.t. positive end of its track, this ensuring that the valve receives an adequate h.t. voltage at the point immediately below oscillation. This circuit has the minor advantage that the potentiometer also functions partly as a volume control. Very strong signals can be reduced to a low level by setting the potentiometer slider near the chassis end of the track, whereupon the detector has a low h.t. potential. Another advantage is that, whereas a reaction capacitor has to be mounted close to the valve and tuned circuit to enable short interconnecting leads to be used (as is necessary in leads carrying r.f. currents), the potentiometer can be mounted at any convenient point on the chassis or front panel since it only varies the direct voltage applied to bypass capacitor  $C_8$ . This point can be helpful in easing layout problems.

In all the reaction circuits we have seen, the resistor  $R_2$  in the anode circuit may be replaced by an r.f. choke. It should be pointed out that, when the detector goes into oscillation, the circuit functions as a transmitter and radiates at oscillator frequency by way of the aerial, with the risk of interference with neighbouring receivers.

A final point is that, when a signal is tuned in on a receiver having a detector whose reaction is advanced so far that oscillation is occurring, a *heterodyne* or *beat note* is formed. This consists of an a.f. tone whose frequency is equal to the difference between the transmitted carrier and the detector oscillation frequency, and it decreases as the detector comes more and more into tune, falling below the audio frequency range when the detector oscillation frequency is very close to that of the carrier.

#### Next Month

A great deal of ground has been covered in this series up to the present, and it now becomes possible to put all the theoretical points dealt with into use by building practical demonstration equipment. It is hoped to give more details of this approach in next month's issue.

---

## RODING BOYS' SOCIETY

Following the resignation of the leader of the Roding Boys' Society on the 29th April, 1966, this society has now been disbanded. However, some of the ex-members of the Society have now formed the REDBRIDGE SCIENTIFIC SOCIETY, meeting at the same premises, Wanstead Community Centre, The Green E.11.

# Courses of Instruction . . .

## London Borough of Hounslow Education Committee

Brentford Centre for Adult Education, Clifden Road, Brentford  
Tuesday evenings for 1st year students and Thursday evenings for 2nd year students 7-9 p.m.  
Starting 26th September, 1966 Fee 30s. for Course of three terms

### 1. Radio and Television Servicing

Electron theory, magnetism, resistors, capacitors and inductors. Valves and transistors. Test equipment. Circuits. Fault finding. The course should enable the layman to keep his radio and television set in good repair, and prevent accidents from ignorant handling.

Enrolment dates: 15th, 16th, 19th, 20th and 21st September, 1966, 7-9 p.m.

Brentford Centre for Adult Education, Clifden Road, Brentford

Monday evenings 7-9 p.m. commencing 26th September, 1966. Fee 30s. for three terms.

### 2. Radio Amateurs' Course

This course is in preparation for the City and Guilds Examination which qualifies the successful candidate for recognition by the Postmaster-General for the purpose of Radio Transmission. The work includes; simple magnetism and electricity, principles of radio, valves and transistors and circuits, radio receivers, low-power transmitters, aerials, measurement of frequency meters. After the examination the course will include lectures on equipment design.

Brentford Centre for Adult Education, Clifden Road, Brentford

Fee 20s. for two terms

### 3. High Fidelity and Tape Recording

The course is designed to give an insight into the technique of high fidelity, tape reproduction and recording and to get the best out of existing apparatus and machines, including notes on construction and maintenance. Of special interest to teachers will be lectures dealing with the application of recorders in the classroom and notes on the teaching of languages by tape recorders and language laboratories. Programming and special applications, both stereo and mono, will be dealt with, as will be sound on tape or film for cine work.

Enrolment dates: 15th, 16th, 19th, 20th, and 21st September, 1966. 7-9 p.m.

## Isleworth Polytechnic Department of Science and Engineering Prospectus

### Telecommunication Technician's Course (FT1. FT2).

The course is for prospective entrants into the Radio and Telecommunication industries and services. Students attend college full-time for two years and take external examinations for the City and Guilds intermediate and final certificates for Telecommunication Technicians.

Applicants should have a genuine desire to enter the industry and must already possess the General Certificate of Education at "O" level in Mathematics, English and, either Physics, Physics-with-Chemistry, or General Science. Alternative qualifications will be sympathetically considered.

Subjects taken are listed below:

#### Telecommunication

Elementary Telecommunication Practice, Principles, Radio and Line Transmission. Telecommunication Laboratory.

#### General

Mathematics, Engineering Drawing.

#### Liberal Activities

Students' preference, selected from Visual Arts, Music, Dramatics, Sport etc.

#### Fees

Free to students under eighteen years of age. Minimum age of entry 16 years.

Application forms for course FT. from: The Principal, Isleworth Polytechnic, Science and Engineering Department, St. John's Road, Isleworth, Middlesex.

## Radio Amateurs' Examination

Those wishing to study for the above examination, a pass in which is necessary before a Radio Transmitting Licence will be issued by the Post Office, can do so as follows:

Venue—New Technical Block, Hay Currie School, Byron Street, London E.14.

(Ten minutes walk approx., from Chrisp Street Market or from the East India Dock Road Entrance to Blackwall Tunnel). Day and Time—Thursdays, 6.45 to 8.45 p.m. (Note: Efforts are being made to change above times to 7.30 to 9.30 p.m.).

Enrolment—Monday, 19th September to Friday, 23rd September inclusive 7.00 to 9.00 p.m. or by post to: The Principal, Bow and Poplar Institute, Marnar School, Devas Street, London E.3. any time after 1st September. Fee for the course 25s.

Course to commence 29th September, 1966 and meet weekly for two or three terms as required. Autumn Term—26th September to 16th December, 1966. Spring Term—9th January to 17th March, 1967. Summer Term—3rd April to 30th June, 1967.

We will gladly send a brochure to anyone who wishes to have one—we only need the names and addresses—the brochures are usually sent out about the end of August.

# SMALL ADVERTISEMENTS

Use this form for your small advertisement

To: The Advertisement Manager, Data Publications Ltd., 57 Maida Vale, London, W.9  
 Please insert the following advertisement in the ..... issue of **THE RADIO CONSTRUCTOR**


16 words at 9d.  
 = 12/-

**ALL WORDING  
 IN  
 BLOCK LETTERS  
 PLEASE**

I enclose remittance of ..... being payment at 9d. a word. **MINIMUM 12/-**.  
 Box Number, if required, 2/- extra.

NAME .....

ADDRESS .....

*Copy to be received four weeks prior to publication. Published on the 1st of every month*

# LEARN ELECTRONICS AS YOU BUILD 25 CIRCUITS ... EXPERIMENTS ... TEST GEAR ...

including

## ● CATHODE RAY OSCILLOSCOPE

- VALVE EXPERIMENTS
- SQUARE WAVE GENERATOR
- SIGNAL TRACER
- BASIC AMPLIFIER
- SIMPLE TRANSMITTER
- BASIC COMPUTER CIRCUIT
- BASIC RECTIFIER
- TRANSISTOR EXPERIMENTS
- BASIC RADIO RECEIVER
- PHOTO ELECTRIC CIRCUIT
- BASIC OSCILLATOR
- MORSE CODE OSCILLATOR
- TIME DELAY CIRCUIT
- ELECTRONIC SWITCH
- ETC. ETC.

This complete practical course will teach you all the basic facts of electronics by making experiments and building apparatus. You learn how to recognise and handle all types of components—their symbols and how to read a circuit diagram. You see how circuits are built and how they work **BY USING THE OSCILLOSCOPE PROVIDED**. Applications of all the main electronic circuits are

demonstrated—radio reception and transmission; photo-electrics; computer basics; timers; control circuits; etc.; including servicing techniques. **NO MATHS USED OR NEEDED. NO THEORY NEEDED. NO PREVIOUS KNOWLEDGE OR EXPERIENCE NEEDED.** Tutor service available. No extras needed—tools provided. Send now, for *Free Details* without obligation, to address below

To **RADIOSTRUCTOR**, Dept. K3, **READING, BERKS.** Please send free details of your electronics kit set to:

**POST  
 NOW**

NAME .....

ADDRESS .....



## CIRCUITS FOR AUDIO AND TAPE RECORDING

A comprehensive selection of practical audio and tape recording circuits compiled by F. C. Judd, Editor of *Amateur Tape Recording*.

Six separate sections cover **Tape Recording—Audio Amplifiers, Simple Radio Tuners, Test Equipment, Miscellaneous Audio Electronics, Building from Kits and a Useful Appendix of Symbols and Units.** Nearly 50 practical circuits include tape recording and replay amplifiers, hi-fi pre-amplifiers and power amplifiers (valves and transistors), an audio signal generator, microphone and signal mixers and power units etc.

For the audio experimenter there are circuits such as a Ring Modulator—Vibrato amplifier—Electronic Tone Generator—an Electronic Echo Unit—with two stage mixing amplifiers and an Electronic Theremin etc.

A handy circuit book for all tape and audio enthusiasts—Price 8s 6d post paid. Fill in the coupon below and get your copy now.

To: Haymarket Press Ltd, 9 Harrow Rd, London W2  
Please send me ..... copies of *Circuits for Audio and Tape Recording* at 8s 6d. each post free. I enclose cheque/PO for ..... to cover the cost.

Name \_\_\_\_\_

Address \_\_\_\_\_

RC8

## BI-PAK SEMICONDUCTORS

8 RADNOR HOUSE, 93/97 REGENT STREET LONDON, W.1

### LOW COST SILICON CONTROLLED RECTIFIERS

50 PIV 1 Amp. .... 8/6    400 PIV 7 Amp. .... 30/-  
100 PIV 7 Amp. .... 10/6    100 PIV 16 Amp. .... 16/6  
Free Circuit Diagrams with SCR orders

**FREE** One 10/- Pack of your own choice with orders valued £4 or over **FREE**

50 Trans. mixed untested.....	10/-
3 OC139 Trans. NPN Mullard.....	10/-
2 Drift Trans. 2N1225 100 Mc/s.....	10/-
6 Matched Trans. OC44/45/81/81D.....	10/-
4 OA10 Diodes Mullard.....	10/-
15 Red Spot AF Trans. PNP.....	10/-
15 White Spot RF Trans. PNP.....	10/-
4 Sil. Rects. 3A, 100/400 PIV.....	10/-
4 NPN Trans. OC139, 2N1308.....	10/-
2 10 Amp Sil. Rect. 50/100 PIV.....	10/-
8 Diodes 4 OA70, 4 OA79.....	10/-
1 12 Amp SCR 100 PIV.....	10/-
3 Sil. Trans. 2S303 PNP.....	10/-
10 Assorted Computer Diodes.....	10/-
4 Zeners 5, 6.8, 10, 12 Vits.....	10/-
4 2G417 Trans. Eqvt. AF1116/7.....	10/-
2 200 Mc/s Sil. Trans. BSY26/7.....	10/-
2 Bi-directional Trans. ASY66.....	10/-
4 High Current Trans. OC42.....	10/-
2 Power Trans. OC26/35.....	10/-
5 Sil. Rects. 400 PIV 250mA.....	10/-
3 OC71 Trans. Mullard.....	10/-
3 OC75 Trans. Mullard.....	10/-
3 NPN Sil. Trans. 70 Mc/s.....	10/-
1 Power Trans. OC20 100 Vits.....	10/-
5 OA47 Gold Bonded Diodes.....	10/-
4 OA202 Sil. Diodes Sub-Min.....	10/-
8 OA81 Diodes Sub-Min.....	10/-
3 Sil. Rects. 400 PIV 500mA.....	10/-
Tunnel Diodes IN3720.....	15/-
Unijunction Trans. 2N2646.....	15/-
6 BY100 Sil. Rects.....	20/-

100s of semiconductor bargains incl. Logic Modules send 2/6 for 3 months mailing. Add 1/- post & packing per order.  
CASH WITH ORDER PLEASE. MAIL ONLY.

## SMALL ADVERTISEMENTS

Rate: 9d. per word.

Minimum charge 12/-.

Box No. 2/- extra.

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of advertisers. (Replies to Box numbers should be addressed to: Box No.—, *The Radio Constructor*, 57 Maida Vale, London, W.9.)

**SERVICE SHEETS, 1925–1965.** From 1s. Catalogue 6,000 models, 2s. 6d. S.A.E. enquiries.—Hamilton Radio, 13 Western Road, St. Leonards, Sussex.

**GOVERNMENT SURPLUS** electrical and radio equipment. Our new catalogue No. 16 ready now, 2s. 6d. post free, cost refunded on purchase of goods over £2.—Arthur Sallis Radio Control Ltd., 93 North Road, Brighton, Sussex.

**FOR SALE.** Oscilloscopes—Galvanometers—Evershed & Vignolles Meggers. Also other items and components. Free list. Stamp please.—R. & E. Mart, Box 9 G.P.O., Tunbridge Wells, Kent.

**CONVERT ANY TV SET INTO AN OSCILLOSCOPE.** Instructions and diagrams, 12s. 6d.—Redmond, 42 Dean Close, Portslade, Sussex.

**SEMICONDUCTORS—**Good quality, close equivs., OC35, 4s. 9d., OC72, 2s., OC71, 1s. 9d., OC44, 2s., OC170, 2s. 6d., BY100, 4s. 3d., OA70, 8d. P. & P. 9d.—A. P. Wise, 19 Harbeck Road, Bournemouth, Hants.

**ANY PRINTED CIRCUIT BOARD SUPPLIED** against your full size drawing. 6d. sq. in. plus 2s. 6d. processing, including drilling.—Temple, 12 Beech House Road, Croydon, Surrey.

**WANTED.** Information on meteorological FAX radio reception systems, brochures, circuits, surplus equipment, etc.—Box No. F250.

**WANTED.** To purchase secondhand classical L.P. records in good condition. Reasonable.—Box No. F251.

**EXCITING HOLIDAYS** with Adventure, Variety and Fun. Sailing, Snorkelling, Pony Trekking, Canoeing, Caving. Please write for our attractive brochure.—P.G.L. Holidays, Department 82, Commerce Lane, Letchworth, Herts.

**WANTED.** Modern aircraft transceiver complete. Full details to:—E. J. Roe, 3 South Avenue, Stoke Park, Coventry, Warwickshire.

**FOR SALE.** Heathkit Balun Coil Unit, B-1U. £4.—Box No. F259.

**FOR SALE.** Two 1155 trawler band P.S.U.'s. Working, good condition. £12 each.—Witherington, 60 Kenilworth Avenue, Walthamstow, London E.17.

continued on page 61

## SMALL ADVERTISEMENTS

continued from page 60

**BOOKS TO CLEAR.** "Man in Space" (Haber) 10s. "Realities of Space Travel" (Carter) 10s. "The Story of Astronomy" (Draper and Lockwood) 5s. "Santos-Dumont" (Peter Wykeham) 17s. 6d. "Teach Yourself Russian" 5s. "The Manual of Rugby Union Football" 5s. "How to develop a Super-Power Memory" (Harry Lorayne) 10s. "The Principles of Modern Book-Keeping" (Hamilton) 5s.—Box No. F260.

**TRANSFORMERS,** burnouts rewound. Specials for transistor projects and electronic organs. S.A.E. enquiries.—Ratcliffe, 27 Station Road, Holmfirth, Yorks.

**RESERVE CAPACITY AVAILABLE** mechanical, electro-mechanical assembly, electronic assembly and wiring. Lead time six weeks. Top quality assurance and supporting technical service. Based North Wales.—Box No. F262.

**YOUNG MAN REQUIRED.** Keen on audio electronics, to learn testing and service of sound equipment. Holborn area.—Telephone Mr. Weir, CHAncery 6141.

**WANTED.** Copy of *The Radio Constructor* April 1962 issue. Cover price and postage paid. Box No. F265.

**OC170.** About 1s. 6d. each. Mounted on circuit board. Full board (12 OC170's and 50 diodes) 25s. Half board (6 OC170's and 24 diodes) 15s. Or send s.a.e. for details—Box No. F266.

**YOUR KITS EXPERTLY ASSEMBLED.** Radios, amplifiers, test gear of every description. S.a.e. for enquiries to:—W. Thomas, 106 Wynnville, Ruabon, Nr. Wrexham.

**TECHNICAL DRAWINGS,** Artwork, etc. Electronic and Radio Circuits a speciality. Moderate charges.—B. P. Meaney, 43 Forest Road, Worthing, Sussex.

**ARE YOU A MOTORING ENTHUSIAST?** The Seven Fifty Motor Club caters for all types of motor sport—racing, rallies, hill climbs, etc. Monthly Bulletin free to members. For full details write to: The General Secretary, Colin Peck, "Dancer's End", St. Winifred's Road, Biggin Hill, Kent.

**POSTAL ADVERTISING?** This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list.—The Holborn Direct Mail Company, 2 Mount Pleasant, London, W.C.1. Telephone: TERminus 0588.

**"MEDIUM WAVE NEWS"** Monthly during DX season—Details from: B. J. C. Brown, 60 White Street, Derby.


**TRANSISTORS.** OC71, OC75, OC81, OC81D, XA103, NKT213 3/-. 2N1225 4/-. GET111 5/-. Silicon rectifiers DD236 2/6. IS020 4/-. Post Free. The Radio Constructors Centre, 363 Westborough Road, West-cliff-on-Sea, Essex.

continued on page 63
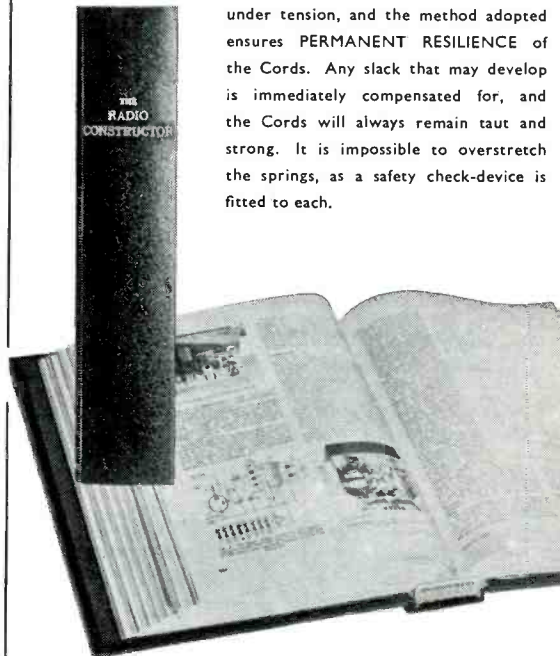
# NEW STYLE SELF-BINDER for "The Radio Constructor"

The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease.


Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for, and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check-device is fitted to each.



PRICE **15/-** Post Free

Available only from:—

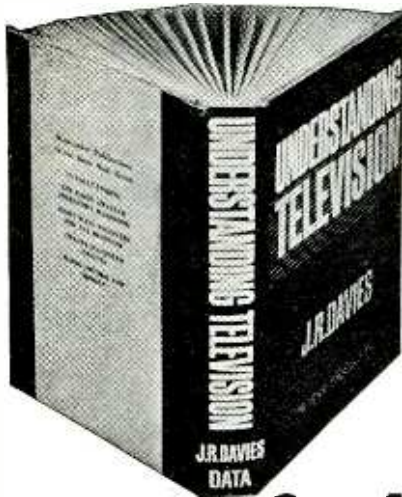**Data Publications Ltd.**  
**57 Maida Vale London W9**



# UNDERSTANDING TELEVISION

by

J. R. Davies

Over 500 pages 300 diagrams **37'6**  
Postage 2/6d

UNDERSTANDING TELEVISION deals with:—

- Principles of 405 line reception
- Nature of the television signal
- Receiver tuner units
- A.F. and video amplifiers
- Deflector coil assemblies
- Automatic gain and contrast control
- Receiver aerials
- COLOUR TELEVISION—80 page section deals comprehensively with this subject
- Principles of 625 line reception
- The cathode ray tube
- Receiver i.f. amplifiers
- Vertical and horizontal timebases
- Synchronising
- Power supply circuits
- Colour television

The reader is required to have only a basic knowledge of elementary radio principles. The treatment is non-mathematical throughout, and there is no necessity for any previous experience in television whatsoever. At the same time, UNDERSTANDING TELEVISION is of equal value to the established engineer because of the very extensive range it covers and the factual information it provides.

---

**To Data Publications Ltd., 57 Maida Vale, London, W9**

Please supply.....copy(ies) of your latest publication "Understanding Television", Data Book No. 17. I enclose cheque/crossed postal order for .....

NAME.....

ADDRESS .....

.....

.....

## SMALL ADVERTISEMENTS

continued from page 61

**TEST EQUIPMENT FOR SALE.** Mullard high speed valve tester, extras, signal generators, 5" oscilloscope. Capacitance bridge. Test meters. V.T. V.M. meter. Much more. All as new and very cheap. S.A.E. to arrange call.—Olive, 43 Fulham High Street, London, S.W.6.

**JOIN THE INTERNATIONAL S.W. LEAGUE.** Free Services to members including Q.S.L. Bureau. Amateur and Broadcast Translation. Technical and Identification Dept.—both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes. QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazine, etc., 35s. per annum.—Secretary, ISWL, 60 White Street, Derby.

## MORSE MADE EASY !!

The famous RHYTHM RECORDED COURSE cuts practice time down to an absolute minimum!

One student, aged 20, took only 13 DAYS and another, aged 70, took 1 WEEK to obtain a G.P.O. pass certificate. If you wish to read Morse easily and naturally, please enclose 8d. in stamps for full explanatory booklet to:

G3HSC/D · 45 GREEN LANE · PURLEY · SURREY

## HAMMERITE HAMMER PATTERN BRUSH PAINT FOR PANELS, METALWORK, ETC.

3/6 TIN ● JUST BRUSH ON ● WITHSTANDS 150°C, OIL, WATER ETC. COLOURS: blue, silver, black, or bronze. 2½oz tins, 3/6. ½ pint, 7/6. 1 pint, 15/-. ½ gallon, 35/-\* 1 gallon, 58/-\* Carr. up to 5/-, 9d., up to 10/-, 1/9, over 10/-, 2/9. \* Sent by road.

From component shops or direct from the manufacturer: FINNIGAN SPECIALITY PAINTS (RC), Mickley Square, Stocksfield, Northumberland. Telephone: Stocksfield 2280

**YUKAN SELF-SPRAY** AIR DRYING MODERN WRINKLE (CRACKLE) FINISH EGG SHELL

Black same price as Hammer finishes (see our main advert., page 64.)

Like our hammers?  
Now have a crack  
at our — **WRINKLES!**

## Radio Control

### SINGLE CHANNEL TRANSMITTER

With 1 watt output  
Kit of parts £8.0.0  
Assembled £8.10.0  
(LESS CASE AND AERIAL)

Also 10 & 12 channel from £12

Receivers from £4.10.0

demonstrated at  
**TELERADIO  
ELECTRONICS**

325/7 FORE ST.  
LONDON N9 TYPE 200/RC



## SITUATIONS VACANT



## TELECOMMUNICATIONS

Vacancies exist for Young Men keen to make Electronics their career who have not necessarily acquired great practical or theoretical knowledge, but who have suitable interest and who have possibly already constructed some equipment themselves. Training will be provided and applicants will be encouraged to take technical studies to further their careers.

Applications to Personnel Manager,  
**Cambridge Works Ltd.,**  
Haig Road, Cambridge.  
Telephone: Cambridge 51351.

The most accurate  
pocket size  
**CALCULATOR**  
in the world

Send a postcard today for free booklet, or if you prefer, send 75/- for this invaluable spiral slide rule on approval, with money back guarantee if not satisfied.

## CARBIC LTD.

(Dept. RC1)  
54 Dundonald Road  
London SW19



**FREE**  
BOOKLET ON  
REQUEST



# CHASSIS and CASES by



287/9 Edgware Road  
London W2

TELEPHONE  
PADDINGTON 5891/7595

## BLANK CHASSIS—Same Day Service

Of over 20 different forms made up to YOUR SIZE.  
(Maximum length 35", depth 4".)

SEND FOR ILLUSTRATED LEAFLETS or order straight away, working out total area of material required (including waste) and referring to table below which is for four-sided chassis in 16 s.w.g. aluminium.

48 sq. in.	4/6	176 sq. in.	9/10	304 sq. in.	15/2
80 sq. in.	5/10	208 sq. in.	11/2	336 sq. in.	16/6
112 sq. in.	7/2	240 sq. in.	12/6	368 sq. in.	17/10
144 sq. in.	8/6	272 sq. in.	13/10	and pro rata	
	P. & P. 3/-		P. & P. 3/6		P. & P. 4/-

Discounts for quantities. More than 20 different sizes kept in stock for callers.


FLANGES (1/2" or 3/4"), 6d. per bend.  
STRENGTHENED CORNERS, 1/- each corner.  
PANELS

Any size up to 3ft at 6/- sq. ft. 16 s.w.g. (18 s.w.g. 5/3).  
Plus postage and packing

## CASES

ALUMINIUM, SILVER HAMMERED FINISH

Type	Size	Price	Type	Size	Price
U	4 x 4 x 4"	10/-	Y	8 x 6 x 6"	26/6
U	5 1/2 x 4 1/2 x 4 1/2"	15/6	Y	12 x 7 x 7"	41/-
U	8 x 6 x 6"	21/-	Y	13 x 7 x 9"	46/-
U	15 x 9 x 9"	44/6	Y	15 x 9 x 7"	48/6
W	8 x 6 x 6"	21/-	Z	17 x 10 x 9"	66/-
W	12 x 7 x 7"	34/-	Z	19 x 10 x 8 1/2"	71/-
W	15 x 9 x 8"	44/-		* Height	

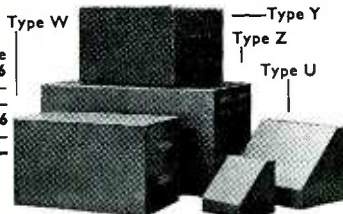

Type Z has removable back and front panels.  
Type Y all-screwed construction.

## BRASS · COPPER · LIGHT ALLOYS · ALUMINIUM BRONZE · STAINLESS STEEL

ROD, BAR, SHEET, TUBE, STRIP, WIRE. 3,000 STANDARD STOCK SIZES  
No Quantity too small List on application

H. ROLLET & CO LTD  
HOWIE ST. LONDON SW11 BATTERSEA 7872  
Also at Liverpool, Birmingham, Manchester, Leeds, Glasgow

the unique **PANL** black crackle paint

4/-d. per 1/8 pt. Can  
(We regret we can only supply on cash with order basis)

BRUCE MILLER LTD.,  
219 Coastal Chambers,  
Buckingham Palace Road, S.W.1.

Thinking of using Semiconductors?—Then you'll probably find that all the items you require are available, at highly competitive prices, through our Mail Order service.

Send a 1/3 P.O. for a price listing of over 1000 transistors, many of which are available from stock; or, alternatively, send a 2/- P.O. and receive in addition: specimen transistor data summaries—covering approx. 200 common types held in stock, and also details of our SEMI-CONDUCTOR INFORMATION SERVICE, (which will be brought into operation later this year).

Examples of our stock: OC 83, 6/-; OC 139, 12/-; OC 171, 9/-; OC 200, 10/-; AC 127, 9/6; AF 124, 11/-; AF 181, 14/-; 2G 302, 5/8; 2G 371, 4/-; 2N 697, 13/6; 2N 706, 9/-; 2N 2926 (red), 4/-; 2N 2926 (green), 4/9; 2N 3053, 12/-; 2N 3391, 11/-; 2N 3663, 14/9; 2N 3702, 7/-; etc.

Please add 1/- P. & P. on all orders of £2 or less.

TERMS: C.W.O. MAIL ORDER ONLY PLEASE.

**M. R. CLIFFORD & CO. (C5)**

66, OLD OSCOTT LANE, BIRMINGHAM, 22A.

# NEW TRANSISTOR CATALOGUE

Please send two shillings for catalogue

## marlison "Dual-tone" 49/- test oscillators

Printed circuit construction, 9v batt. conns for PP3. Output: 100mV, 10K ohms, co-ax socket (1Kc & 2.5Kc standard) mixed, but separately switched. Suitable for testing 55B transmitters. Easily mounted or built into other equipment. 3 1/2" X 1 1/2"

JOHN WILLIAMS ELECTRONICS LIMITED  
176 HAGLEY ROAD, HALESOWEN, BIRMINGHAM

## YUKAN SELF-SPRAY

SO PROFESSIONAL  
... THE YUKAN  
AEROSOL WAY!

GET THIS AIR DRYING HAMMER FINISH  
NOW!

YUKAN Aerosol spraykit contains 16 ozs. fine quality, durable, easy instant spray. No stove baking required. Available in Grey, Blue, Gold, Bronze at 14/11 at our counter or 15/11, carriage paid, per pushbutton self-spray can. SPECIAL OFFER: 1 can plus optional transferable snap-on trigger handle (value 5/-) for 18/11 carr. paid.



Choice of 13 self-spray plain colours and primer (motor car quality) also available.

Please enclose cheque or P.O. for total amount to:

YUKAN · DEPT RC/8 · 307a EDGWARE ROAD · LONDON · W2

# THE RADIO CONSTRUCTOR — BOUND VOLUMES

Volume 18, August 1964 to July 1965. Price £1 10s. 0d. Postage 3s. 6d.

Where all issues are returned: Price £1. Postage 3s. 6d.

We regret earlier volumes now sold out.

Send for list containing details of our other publications

**DATA PUBLICATIONS LTD 57 MAIDA VALE LONDON W9**

Please mention **THE RADIO CONSTRUCTOR** when writing to advertisers

---

# BOOK LIST

---

## DATA BOOKS SERIES

### DB5 TV Fault Finding

96 pages. Price 6/-, postage 6d.

Profusely illustrated with photographs taken from a television screen depicting the faults under discussion and containing a wealth of technical information, with circuits, enabling those faults to be eradicated. Covers both B.B.C. and I.T.A.

"... A book that should be in every television dealer's service workshop, and in every home-constructor's, for that matter."—*Journal of the Television Society*.

### DB6 The Radio Amateur Operator's Handbook

64 pages. Price 5/-, postage 5d.

Contains Amateur Prefixes, Radio Zone Boundaries, Amateur Band Frequency Allocations, Call Areas, Charts and Maps, Areas, Codes, Mileage Tables, Prefixes/Directional Bearings, Post Office Regulations, and much other useful operating data. For the beginner there are notes on how to use the mass of information given to obtain the greatest satisfaction from the hobby.

"... For concise knowledge in this field a few shillings well worth spending."—*Electronics* (Australia).

### DB14 Short Wave Receivers for the Beginner

72 pages. Price 6/-, postage 6d.

Contains a selection of both battery and mains operated short wave receivers, circuits, point-to-point wiring diagrams and many illustrations. Introductory chapter gives much information on the Short Wave Spectrum, Clubs, QSL'ing, Aerials, Amateur and Broadcast Band Listening, Frequencies, etc. This book has been specially prepared for the beginner interested in short wave receiver construction and operation.

### DB15 Twenty Suggested Circuits

48 pages. Price 3/6, postage 5d.

By G. A. French. Covers subjects ranging from electronic laboratory equipment to the simplest of periodic switches. Includes: simple and inexpensive two-valve capacity bridge, short wave regeneration preselector, one-valve speech operated switching circuit, transformer ratio analyser, series noise limiter, receiver remote mains on-off control, and many other circuits.

### DB16 Radio Control for Models

192 pages. Price 15/-, postage 9d.

By F. C. Judd. Contains both theory and practical designs of simple and advanced transmitters and receivers; basic concepts, aerials, uses of radio components, transistorised receivers, multi-channel operation, etc. Sections on servo-mechanisms by Raymond F. Stock. More than 200 illustrations. Circuits, photographs, tables and working diagrams.

### DB17 Understanding Television

512 pages. Price 37/6, postage 2/6

By J. R. Davies. This book, which deals with the principles of 625 line reception as fully as 405 line reception, fully explains: the nature of the television signal; the cathode ray tube; receiver tuner units; receiver i.f. amplifiers; a.f. and video amplifiers; vertical and horizontal timebases; deflector coil assemblies; synchronising; automatic gain and contrast control; power supplies and receiver aerials. Also includes a comprehensive introduction to colour television.

"... one of the best books that aims to explain television in simple language ...". R.S.G.B. Bulletin.

I enclose Postal Order/Cheque for ..... in payment for .....

NAME .....

ADDRESS .....

(Please use Block Capitals for both name and address)

Postal Orders should be crossed and made payable to Data Publications Ltd.

Overseas customers please pay by International Money Order

All publications are obtainable from your local bookseller

Data Publications Ltd., 57 Maida Vale, London W.9

**PRICE REDUCTIONS FOR MANY ITEMS THIS MONTH**




(4)



(3)




(1)

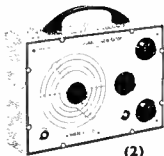

(2)



(16)

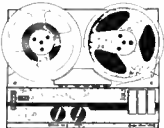

(8)



(7)



(9)




(11)



(10)



(12)

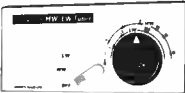


(14)



(5)



(13)

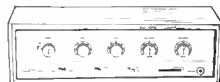

(15)

**LET US QUOTE FOR COMPONENTS AND EQUIPMENT FOR YOUR CIRCUIT**

**TRANSISTOR CATALOGUE**

Send 3d. stamp for New Edition. SCRS, Rectifiers, Accessories Etc. Over 500 types in stock

**COMPONENTS & ACCESSORIES**

We can supply most of the items specified for Published Circuits. Let us quote—send List for speedy reply.

**(1) GLOBEMASTER MW/LW/SW PORTABLE RADIO TO BUILD**

Special purchase reduces prices Full 3-waveband tuning. Pushbutton wavechange. Superhet printed circuit. Black-chromed cabinet 11 x 7½ x 3½". (SW 17-50 metres). Ear/Record sockets.

**TOTAL COST £7.19.6** P.P. 3/6.

**10 AND 20 WATT MONO AND STEREO TRANSISTOR AMPLIFIERS**

**(9) POWER AMPLIFIERS.** 10 watts RMS output. 100mV input. 30 c/s to 20 kc/s ± 1dB. 6-Transistor Push-pull. Panel size 4 x 2½ x 1½". HJS 4 x 4". TPA10/3 3-5 ohm spkr. £4.10.0, p.p. 2/6 TPA10/15 12-16 ohm spkr. £5.5.0., p.p. 2/6

(Mains unit for 1 or 2 amplifiers. 59/6, P.P. 2/6)

**The Finest High Fidelity at Unbeatable Prices**

**(8) BUILD A QUALITY TAPE RECORDER**

Three speeds—3 watts. Complete kits with new "363" decks. Supplied as preassembled sections. Complete with portable cabinets and Speaker—excellent quality. 7" 1,200ft. tape and spool and Aco 45 microphone. "363" decks with tape.

(2 track 10 gns. 4 track £13.10.0. p.p. 5/-)  
★ TWO TRACK ★ FOUR TRACK  
**27 gns** P.P. 10/- **30 gns** P.P. 10/-

**(13) REGENT-6 MW/LW POCKET RADIO TO BUILD**

6-Transistor superhet. Gearing tuning. Push-pull output. Moulded cabinet 5 x 3 x 1½". Phone socket

**TOTAL COST 69/6** P.P. 2/-  
Special purchase reduces price

**(6) 25 WATT AMPLIFIER**

New 8-Transistor design. Push-pull output for 7½ to 16Ω speaker. 150mV input. 30c/s to 20kc/s ± 1dB. For use with valve or transistor preamplifiers as item (10) above. Size 2½ x 2½ x 6½"

**PRICE BUILT AND TESTED £7.19.6** P.P. 3/-

(Mains unit 79/6, p.p. 2/6)

**(11) GARRARD DECKS**

(p.p. 5/- any type)  
1000 mono £5.19.6, stereo £6. 6.0  
2000 mono £6. 6.0, stereo £6. 6.0  
\*SP25 mono £10.10.0, stereo £10.19.6  
Autoslim mono £5. 9.6, stereo £5. 9.6  
\*AT6 mono £8.19.6, stereo £9.10.0  
\*AT6 mono £10.10.0, stereo £10.19.6  
3000LM stereo £8.8.0

(\*Deram cartridge add 60/- to mono price). All autochange (except SP25), complete with cartridge. Brand new.

**(7) VHF FM TUNER**

Supplied as 2 Preassembled Panels, plus metal work Superhet design, 88-108 Mc/s, 9 volt operated.  
Total cost to assemble £12.17.4, p.p. 2/6.

**HENRY'S RADIO LTD.**  
303 EDGWARE RD., LONDON, W.2

PADddington 1008/9  
Open Mon. to Sat. 9-6. Thurs. 1 p.m.  
Open all day Saturday.

**CATALOGUE**

150 page 1966 Edition over 5,000 stock items at value for money prices. Fully detailed and illustrated. Discount Vouchers FREE with every Edition.

PRICE 6/- post paid

Catalogue costs nothing after using the discount vouchers



**(16) VHF FM TUNER TO BUILD**

87/105 Mc/s Transistor Superhet. Gearing tuning. Terrific quality and sensitivity. For valve or transistor amplifiers. 4 x 3½ x 2½".

**TOTAL COST £6.19.6** P.P. 2/6

(Cabinet Assembly 20/- extra)

**(10) PREAMPLIFIERS.** 8 input selector. Treble, bass, volume, filter controls. 1µV to 300mV inputs. Battery operated or from Mains Unit. Output up to 150mV RMS.

MP2 Mono 9½ x 2½ x 2". £5.10.0, p.p. 2/6 (brown and gold front panel 8/6)

SP4 Mono/Stereo. 9 x 3½ x 1½". £10.19.6, P.P. 3/6 (front panel plate 12/6)

● ALL UNITS BUILT AND TESTED

**(3) 5 WATT AMPLIFIER**

6-Transistor Push-pull, 3 ohms. 6mV into 1K. 12/18V supply. 2½ x 2 x 1½". **BUILT AND TESTED 69/6** P.P. 2/- (optional mains units 54/-) 2-1½ watt version 59/6. New matching Preamplifier, 6 inputs, treble/bass/selector/volume controls. 6-10mV o/put. 9-18V supply. 79/6, p.p. 2/-

For use with any Transistor Amplifier

**DEAC CHARGER**

To charge 3.6 volt and 9.6 volt packs. Fully mains isolated **45/-** P.P. 2/- in moulded case.

**(4) DEAC CELLS**

Rechargeable Batteries  
● 3.6 volt 500 mA/H. Size: 1½" x 1½" dia. . . 12/6, p.p. 1/6  
● 9.6 volt 225 mA/H. Size: 2½" x 1" dia. . . 20/-, p.p. 1/6  
BRAND NEW—Offered at a fraction of normal retail price

**(5) TOURMASTER**

7-Transistor MW/LW Car Radio. 12 volt operated. 3 watt output. Push-button wavechange. RF stage. Supplied built, boxed, ready to use with Speaker and Baffle. Car fixing kit and manufacturers' current guarantee. Special Bargain Offer. Buy Now!

**PRICE £9.9.0** P.P. 3/6

**(12) MULTI-METERS**

PT34 1kV 39/6 TP55 20kV £5.19.6  
M1 2kV 49/6 EP30k 30kV £6.10.0  
TP10 2kV 75/- EP50k 50kV £8.15.0  
EP10k 10kV 79/6 500 30kV £8.17.6  
IT1-2 20kV 69/6 EP 100k 100kV £10.10.0  
EP20k 10kV 99/6

**(14) MW/LW QUALITY TRANSISTOR RADIO TUNER**

Fully tunable superhet with excellent sensitivity and selectivity. Output up to ½ volt peak. Complete with front panel, etc. 9 volt operated. For use with any amplifier or tape recorder.

**TOTAL COST £3.19.6** P.P. 2/6

**(2) NOMBREX TEST UNITS**

\*150 kc/s—350 m/cs RF Generator £9.10.0  
All Transistor  
\*10 c/s—100 kc/s Transistor  
Audio Generator £16.15.0