

THE

RADIO CONSTRUCTOR


Vol 21 No 1

AUGUST 1967
2/6

A DATA PUBLICATION

RADIO · TELEVISION
ELECTRONICS · AUDIO

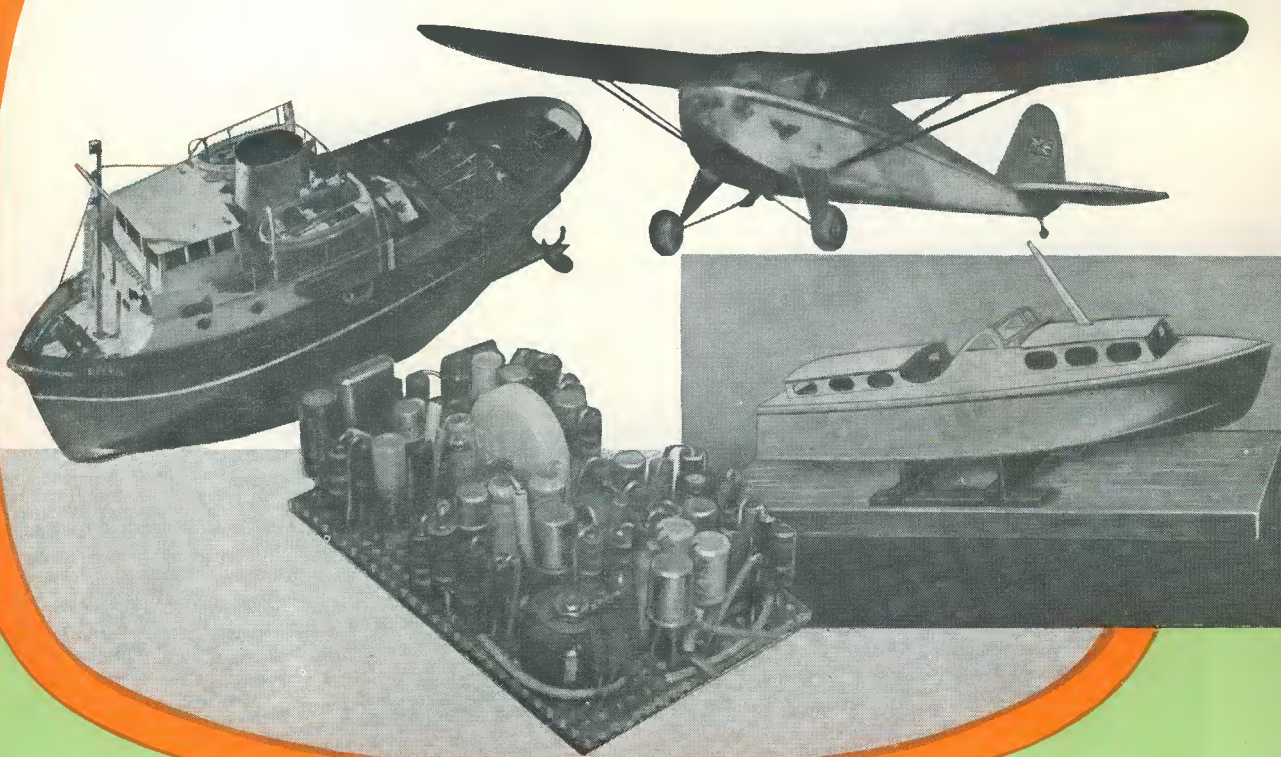The SCT/RS1 Superhet Model Control Receiver



10 Watt
P.A. Amplifier



Windscreen Wiper
Programmer



Simple Short
Wave Converter



Combined AF/RF
Signal Generator

Scottish Insurance Corporation Ltd

66-67 CORNHILL · LONDON · EC3



TELEVISION SETS, RECEIVERS AND TRANSMITTERS

Television Sets, Receivers and Short Wave Transmitters are expensive to acquire and you no doubt highly prize your installation. Apart from the value of your Set, you might be held responsible should injury be caused by a fault in the Set, or injury or damage by your Aerial collapsing.

A "Scottish" special policy for Television Sets, Receivers and Short Wave Transmitters provides the following cover:

- (a) Loss or damage to installation (including in the case of Television Sets the Cathode Ray Tube) by Fire, Explosion, Lightning, Theft or Accidental External Means at any private dwelling-house.
- (b) (i) Legal Liability for bodily injury to Third Parties or damage to their property arising out of the breakage or collapse of the Aerial Fittings or Mast, or through any defect in the Set. Indemnity £10,000 any one accident.
- (ii) Damage to your property or that of your landlord arising out of the breakage or collapse of the Aerial Fittings or Mast, but not exceeding £500.

The cost of Cover (a) is 5/- a year for Sets worth £50 or less, and for Sets valued at more than £50 the cost is in proportion. Cover (b) (i) and (ii) costs only 2/6 a year if taken with Cover (a), or 5/- if taken alone.

Why not BE PRUDENT AND INSURE your installation—it is well worth while AT THE VERY LOW COST INVOLVED. If you write to the Corporation's Office a proposal will be submitted for completion.


Write for full details, quoting reference 5304, to:—

THE MANAGER
SCOTTISH INSURANCE CORPORATION LTD.,
66-67 CORNHILL, LONDON E.C.2

SINCLAIR Z.12

INTEGRATED 12 WATT AMPLIFIER AND PRE-AMP

For size alone, the Z.12 marks an important advance in quality design, for its amazing compactness opens up exciting new vistas in amplifier housing and application. Combined with this are fantastic power and superb quality which can provide an effortless output of 12 watts R.M.S. continuous sine wave from the unique eight transistor circuit used. Basically intended as the heart of any good mono or stereo hi-fi system, the size and efficiency of this Sinclair unit make it equally useful for a car radio (with the Micro-6 for example), a high quality radio with the Micro FM, in a guitar, P.A., or intercom system, etc. Other applications are certain to suggest themselves to constructors. The manual included with the Z.12 details mono and stereo tone and volume control circuits by which inputs can be matched (and switched in) to the pre-amp. The size, performance and price of the Z.12 all favour the constructor seeking the finest in transistorised audio reproduction—it is in fact today's finest buy in top grade high fidelity.

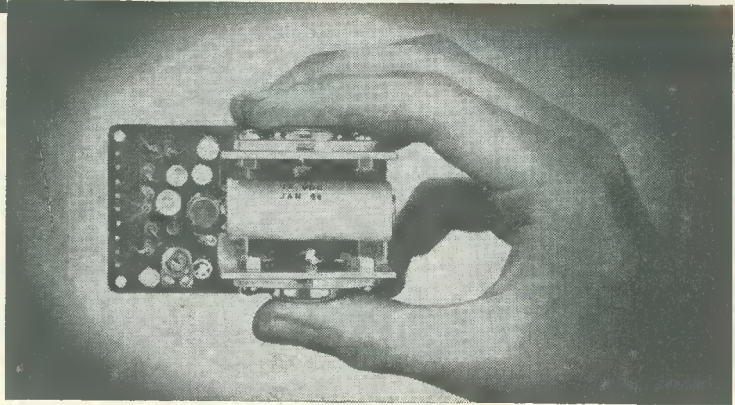

12 WATTS R.M.S. OUTPUT CONTINUOUS SINE WAVE (24 W. PEAK)
15 WATTS MUSIC POWER (30 WATTS PEAK)

Built, tested and guaranteed.

89/6

- ★ Ultra-linear class B output and generous neg. feedback.
- ★ Response—15 to 50,000 c/s ±1dB.
- ★ Output suitable for 3, 7.5 and

- 15 ohm loads. Two 3 ohm speakers may be used in parallel.
- ★ Input—2mV into 2K ohms.
- ★ Signal to noise ratio—better than 60dB.

SINCLAIR MICROMATIC



THE SMALLEST SET IN THE WORLD

Unequaled for power, selectivity and quality. Six stage M.W. receiver. 2 R.F. amplification, double diode detector, 3 stage A.F. amplifier. A.G.C., bandspread, etc. This Sinclair masterpiece is completely self-contained in black case, 1 1/2" x 1 3/10" x 1/2". With brushed aluminium front and spun aluminium calibrated dial. Plays anywhere. Easy to build. Available as complete kit in "check for yourself" pack, or ready built.


Kit with earpiece
Solder and Instructions
59/6

Built, tested & guaranteed **79/6**

SINCLAIR MICRO FM

COMBINED FM
TUNER RECEIVER

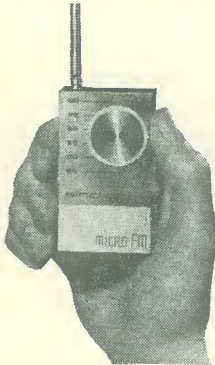No aligning. Less than 3" x 1 1/2" x 3/4" 7 transistor FM using pulse counting discriminator. Tunes 88-108 Mc/s. Telescopic aerial suffices for good reception in all but poorest areas. Signal to noise ratio—30dB at 30 microvolts. One outlet to amplifier, the other allows set to be used as a pocket portable. And aluminium front.



Complete kit inc. aerial, earpiece and instructions.

£5.19.6

SINCLAIR STEREO 25

A SPECIAL DE-LUXE PRE-AMPLIFIER AND CONTROL UNIT

Designed specially to obtain the very finest results used with two Sinclair Z.12's for stereo. The best quality components, individually tested before acceptance, are used in its construction, whilst the overall appearance of this compact de-luxe pre-amp and control unit reflects the professional elegance which characterises all Sinclair designs. The front panel is in solid brushed and polished aluminium with beautifully styled solid aluminium knobs. Mounting

is simple, and the PZ.3 will comfortably power the Stereo 25 together with two Z.12's. When fitted, the Sinclair 25 will grace any type of hi-fi furniture. Frequency response 25 c/s to 30 kc/s ±1dB connected to two Z.12's. Sensitivity Mic. 2mV into 50kΩ; P.U. —3mV into 50kΩ; Radio —20mV into 4.7kΩ. Equalisation correct to within ±1dB on RIAA curve from 50 to 20,000 c/s. Size 6 1/2" x 2 1/2" x 2 1/2" plus knobs.

BUILT, TESTED AND GUARANTEED

£9.19.6

A HI-FI STEREO ASSEMBLY FOR £22.18.0
 All you require is one Stereo 25 Unit (£9.19.6) two Z.12's (£8.19.0) and one PZ.3 (£3.19.6). As an optional extra, you could include the Micro FM (£5.19.6).

FULL SERVICE FACILITIES AVAILABLE TO SINCLAIR CUSTOMERS

GUARANTEE If you are not completely satisfied when you receive your purchase from us, your money will be refunded at once in full and without question.

SINCLAIR PZ.3

Transistorised mains power unit specially designed for Z.12. Will power two Z.12's and Stereo 25 with ease. **79/6**



SINCLAIR RADIONICS LIMITED
 22 NEWMARKET ROAD, CAMBRIDGE
 Telephone: OCA3-52731

SINCLAIR RADIONICS LTD., 22 NEWMARKET ROAD, CAMBRIDGE

Please send

.....


 for which I enclose cash/cheque/money
 order value £.....s.....d.

NAME

ADDRESS.....

.....
RC8

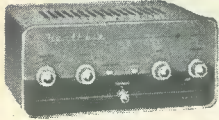HI-FI AMPLIFIERS ~~~~~ TUNERS ~~~~~ RECORD PLAYERS




**3+3W
STEREO
AMP.
S-33H**



**10W
POWER
AMP.
MA-12**



**GARRARD
PLAYER
AT-60**

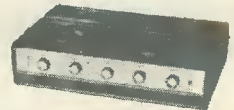

**20+20W
STEREO
AMP.
AA-22U**

10W POWER AMPLIFIER. Model MA-12. 10W output, wide freq. range, low distortion. For use with control unit. Kit **£12.18.0** Assembled **£16.18.0**

STEREO CONTROL UNIT. Model USC-1. Ideal for use with the NA-12 power amplifiers. Push button selection, ganged controls, tumble and variable low-pass fitters. Kit **£19.19.0** Assembled **£27.5.0**

DE LUXE STEREO AMPLIFIER. Model S-33H. 3+3 watt output with two-tone grey perspex panel, and higher sensitivity necessary to accept the Decca Deram pick-up. Kit **£15.17.6** Assembled **£21.7.6**

HI-FI STEREO AMPLIFIER. Model S-99. 9+9W output. Ganged controls. Stereo/Mono gram., radio and tape inputs. Push-button selection. Printed circuit construction. Kit **£28.9.6** Assembled **£38.9.6**

TRANSISTOR PA/GUITAR AMPLIFIER, PA-2. 20W amplifier. Four inputs. Variable tremolo. New Low Price Kit **£39.19.0** Assembled **£54.10.0**

50W VALVE PA/GUITAR AMP., PA-1. Kit **£54.15.0** Assembled **£74.0.0**

TRANSISTOR MIXER. Model TM-1. A must for the tape enthusiast! Four channels. Battery operated. Similar styling to Model AA-22U Amplifier. With cabinet. Kit **£11.16.6** Assembled **£16.17.6**

20+20W TRANSISTOR STEREO AMPLIFIER. Model AA-22U. Outstanding performance and appearance. Kit **£39.10.0** (less cabinet).. Assembled **£57.10.0** Attractive walnut veneered cabinet **£2.5.0** extra.

GARRARD AUTO/RECORD PLAYER. Model AT-60. less cartridge **£14.12.10** With Decca Deram pick-up **£19.7.4** incl. P.T. Many other Garrard models available, ask for Lists.

HI-FI MONO AMPLIFIER. Model MA-5. A general purpose 5W Amplifier, with inputs for Gram., Radio. Attractive modern styling. Kit **£11.9.6** Assembled **£15.15.0**



ENJOY YOURSELF AND SAVE MONEY

Finished models provide years of superlative performances

INSTRUMENTS

3" LOW-PRICED SERVICE OSCILLOSCOPE. Model OS-2. Compact size 5" x 7 1/2" x 12" deep. Wt. only 9 1/2 lb. "Y" bandwidth 2 c/s-3 Mc/s ± 3dB. Sensitivity 100mV/cm. T/B 20 c/s-200 kc/s in four ranges, fitted mu-metal CRT Shield. Modern functional styling. Kit **£23.18.0** Assembled **£31.18.0**

5" GEN-PURPOSE OSCILLOSCOPE. Model 10-12U. An outstanding model with professional specification and styling. "Y" bandwidth 3 c/s-4.5 Mc/s ± 3dB. T/B 10 c/s-500 kc/s. Kit **£35.17.6** Assembled **£45.15.0**

DE LUXE LARGE-SCALE VALVE VOLT-METER. Model IM-13U. Circuit and specification based on the well-known model V-7A but with many worth-while refinements. 6" Ernest Turner meter. Unique gimbal bracket allows operation of instrument in many positions. Modern styling. Kit **£18.18.0** Assembled **£26.18.0**

AUDIO SIGNAL GENERATOR. Model AG-9U. 10 c/s to 100 kc/s, switch selected. Distortion less than 0.1%, 10V sine wave output metered in volts and dB's. Kit **£23.15.0** Assembled **£31.15.0**

VALVE VOLTMETER. Model V-7A. 7 voltage ranges d.c. volts to 1,500. A.c. to 1,500 r.m.s. and 4,000 peak to peak. Resistance 0.1 Ω to 1,000M Ω with internal battery. D.c. input resistance 11M Ω. dB measurement, has centre-zero scale. Complete with test prods, leads and standardising battery. Kit **£13.18.6** Assembled **£19.18.6**

MULTIMETER. Model MM-1U. Ranges 0-1.5V to 1,500V a.c. and d.c.; 150µA to 15A d.c.; 0.2 Ω to 20M Ω. 4 1/2" 50µA meter. Kit **£12.18.0** Assembled **£18.11.6**

R.F. SIGNAL GENERATOR. Model RF-1U. Up to 100 Mc/s fundamental and 200 Mc/s on harmonics. Up to 100mV output. Kit **£13.18.0** Assembled **£20.8.0**

SINE/SQUARE GENERATOR. Model IG-82U. Freq. range 20 c/s-1 Mc/s in 5 bands less than 0.5% sine wave dist. less than 0.15µ sec. sq. wave rise time. Kit **£25.15.0** Assembled **£37.15.0**

TRANSISTOR POWER SUPPLY. Model IP-20U. Up to 50V, 1.5A output. Ideal for Laboratory use. Compact size. Kit **£35.8.0** Assembled **£47.8.0**



OS-2



IM-13U



V-7A



RF-1U



IG-82U

MO Prices quoted
Retail Prices in
general slightly higher.

Complete your motoring pleasure with this outstanding **CAR RADIO, Model CR-1**




Will give you superb LW and MW entertainment wherever you drive. Tastefully styled to harmonise with any car colour scheme. Available for your convenience in two separate parts, RF Amp. Kit **£11.13.6** incl. P.T. IF/AF Amp. Kit **£11.3.6**

Total Price Kit (excl. Loudspeaker) **£12.17.0** incl. P.T. 8" x 5" Loudspeaker **£1.16.1** incl. P.T.

TRANSISTOR RADIOS

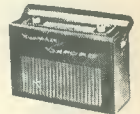"OXFORD" LUXURY PORTABLE. Model UXR-2. Specially designed for use as a domestic, car or personal portable receiver. Many features, including solid leather case. Kit **£14.18.0** incl. P.T.



UXR-2

TRANSISTOR PORTABLE. Model UXR-1. Pre-aligned I.F. transformers, printed circuit. Covers L.W. and M.W. Has 7" x 4" loudspeaker. Real hide case. Kit **£12.11.0** incl. P.T.



UXR-1

JUNIOR EXPERIMENTAL WORKSHOP Model EW-1. More than a toy! Will make over 20 exciting electronic devices, incl: Radios, Burglar Alarms, etc. 72 page Manual. The ideal present! Kit **£7.13.6** incl. P.T.

STEREO TRANSISTOR FM TUNER

(Mono version also available)
14 transistor, 5 diode circuit. Tuning range 88-108 Mc/s. Designed to match the AA-22U Amplifier. Available in separate units, can be built for a total price.

Kit (Stereo) **£24.18.0** incl. P.T.

Kit (Mono) **£20.19.0** incl. P.T.

Cabinet extra **£2.5.0**.



FM Tuner

SEE HEATHKIT MODELS AT THE HEATHKIT CENTRE
233 Tottenham Court Road, London W.1


We open MONDAY - FRIDAY 9 a.m. - 5.30 p.m.
SATURDAY 9 a.m. - 1.0 p.m.
Telephone No: 01-636.7349

WHEN YOU ARE IN TOWN, WE HOPE YOU WILL VISIT US THERE

TAPE AMPLIFIERS TAPE DECKS CONTROL UNITS



**FM
TUNER
FM-4U**

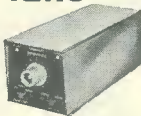

**STEREO
DECODER
SD-1**

HI-FI FM TUNER. Model FM-4U. Available in two units. R.F. tuning unit (£2.15.0 incl. P.T.) with I.F. output of 10.7 Mc/s, and I.F. amplifier unit, with power supply and valves (£13.13.0). May be used free standing or in a cabinet. Total Kit **£16.8.0**
(Multiplex adapter available, as extra.)

HI-FI AM/FM TUNER. Model AFM-1. Available in two units which, for your convenience, are sold separately. Tuning heart (AFM-T1—£4.13.6 incl. P.T.) and I.F. amplifier (AFM-A1—£22.11.6). Printed circuit board, 8 valves. Covers L.W., M.W., S.W., and F.M. Built-in power supply. Total Kit **£27.5.0**
(Multiplex adapter available, as extra.)

STEREO DECODER. Model SD-1. Converts FM Mono receivers to stereo at low-cost. Styled to match Heathkit models FM-4U and AFM-1 Tuners. Kit **£8.10.0** Assembled **£12.5.0**



**TRUVOX
DECK**



**AM/FM
TUNER**

MAGNAVOX "363" TAPE DECK. The finest buy in its price range. Operating speeds: 1½", 3¾" and 7¼" p.s. Two tracks, "wow" and "flutter" not greater than 0.15% at 7¼" p.s. **£13.10.0**

TRUVOX D106 TAPE DECKS. High quality stereo/mono tape decks. D106, ¼ track, **£39.15.0** D108, ¼ track, **£39.15.0**

TAPE RECORDING/PLAYBACK AMPLIFIER
Mono Model TA-IM kit **£19.18.0** Assembled **£28.18.0**
Stereo Model TA-IS kit **£25.10.0** Assembled **£35.18.0**

HI-FI CABINETS. A wide range available for example: Malvern Kit **£18.1.0** incl. P.T. Gloucester Kit **£18.10.0**


MONO CONTROL UNIT. Model UMC-1. Designed to work with the MA-12 or similar amplifier requiring 0.25V or less for full output. 5 inputs. Baxandall type controls. Kit **£9.2.6** Assembled **£14.2.6**

Build Britain's Best Electronic Kits

No special Kit-building skills or Electronic Knowledge required



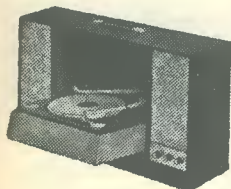New! Portable Stereo Record Player, SRP-1



Automatic playing of 16, 33, 45 and 78 rpm records. All transistor—cool instant operation. Dual LP/78 stylus. Plays mono or stereo records. Suitcase portability. Detachable speaker enclosure for best stereo effect. Two 8in x 5in. special loudspeakers. For 220-250V a.c. mains operation. Overall cabinet size 15¼" x 3¼" x 10¼in.

Compact, economical stereo and mono record playing for the whole Family—plays anything from the Beatles to Bartok. All solid-state circuitry gives room filling volume.

KIT £27.15.0 Assembled price on request.




SSU-1

SPEAKER SYSTEMS

HI-FI SPEAKER SYSTEM, Model SSU-1
Ducted-port bass reflex cabinet in the white: Two speakers, vertical or horizontal models with legs. **KIT £12.12.0**, without legs, **KIT £11.17.6** incl. PT.

AVON MINI SPEAKER SYSTEM

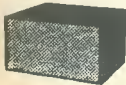6¼" Bass, 3¼" Treble speakers and crossover unit. Kit **£4.18.0** incl. PT. Beautiful. Walnut veneered fully-finished cabinet, **£8.18.0**, Total price Kit **£13.16.0** incl. PT.



"AMATEUR" EQUIPMENT

THE "MOHICAN" GENERAL COVERAGE RECEIVER. Model GC-1U. With 4 piezo-electric transmitters, variable tuned B.F.O. and Zener diode stabiliser, this is an excellent fully transistorised general purpose receiver for Amateur and Short wave listeners. Printed circuits, telescopic aerial, tuning meter and large slide-rule dial. Kit **£37.17.6** Assembled **£45.17.6**

AMATEUR BANDS RECEIVER. Model RA-1. To cover all the Amateur Bands from 160-10 metres. Many special features, including: half-lattice crystal filter; 8 valves; signal strength "S" meter; tuned R.F. Amp. stage.


Kit **£39.6.6** Assembled **£52.10.0**

160-10M TRANSMITTER. Model DX-100U. Careful design has achieved high performance and stability. Completely self-contained.


Kit **£81.10.0** Assembled **£106.15.0**

COMMUNICATIONS TYPE RECEIVER. Model RG-1. A high performance, low cost receiver for the discriminating listener. Frequency coverage: 600 kc/s-1.5 Mc/s and 1.7 Mc/s-32 Mc/s.

Kit **£39.16.0** Assembled **£53.0.0**

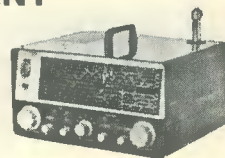

GC-1U

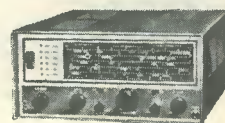

RG-1

Low-cost 3 + 3W Transistor Stereo Amplifier, TS-23



Incorporating all the essential features for good quality sound reproduction from record, radio and other sources. 16 Transistor, 4 diode circuit. Good frequency response 6 position selector switch. Modern slim line styling.

Kit (less cabinet) **£17.15.0**

Kit (with handsome finished cabinet) **£18.19.0**

To **DAYSTROM LTD., GLOUCESTER**
Please send me **FREE BRITISH CATALOGUE**
Please send me details of models

Please send a
Catalogue to my
friend

NAME _____
ADDRESS _____

Name _____
Address _____

RC-8

RC-8



Send for this
Catalogue . . .

. . . it's FREE!

36 pages packed with Britain's largest selection of electronic Kits. Mail coupon or write:

**DAYSTROM LTD., Dept. RC-8
GLOUCESTER. Tel. 20217.**

THE DUCHESS OF KENT PERMANENT BUILDING SOCIETY

Member of the Building Societies Association



ESTABLISHED

1865

Savings in this old established Building Society combine sound investment with an attractive return
Shares are in units of £25 each (maximum investment £5,000) . . . BUT, for the smaller saver, Subscription Share accounts may be opened with any sum from 1/- upwards. Interest is payable half-yearly on Fully Paid Shares—credited annually on Subscription Shares—all interest accrues monthly

WITHDRAWALS AT SHORT NOTICE

INTEREST IS AT 4 $\frac{1}{2}$ % PER ANNUM
(There is NO DEDUCTION FOR INCOME TAX, as this is paid by the Society)

FOR FURTHER INFORMATION APPLY TO

**DUCHESS OF KENT
PERMANENT BUILDING SOCIETY**

289/293 Regent Street London W.1

Telephone MUSEum 4876-9

Please send to me, without obligation, free brochure and a copy of the audited statement of accounts. (I understand that I shall not be troubled with calls by representatives)

Name

(If lady, please state Mrs. or Miss)

Address

R.C.

(Please use Block Capitals for both name and address)

THE MODERN BOOK CO

Amateur Radio Construction Projects. By Caringella. 20s. Postage 1s.

Basic Television Part I. TechP. 21s. Postage 1s.

Beginner's Guide to Electronics. By T. L. Squires. 15s. Postage 9d.

Outline of Radio and Television. By J. P. Hawker. 30s. Postage 2s.

Transistor Pocket Book. By R. G. Hibberd. 25s. Postage 1s.

Multi Channel Radio Control. By R. H. Warring. 12s. 6d. Postage 1s.

Transistors for Technical Colleges. By L. Barnes. 25s. Postage 1s.

Television Servicing Handbook. By G. J. King. 35s. Postage 1s. 6d.

Circuit for Audio Amplifiers. By Mullard. 8s. 6d. Postage 1s.

Service Valve and Semiconductor Equivalents. By G. R. Jessop. 5s. Postage 6d.

Radio Amateur Operator's Handbook. A Data Pub. 5s. Postage 6d.

TV Fault Finding 405-625 lines. A Data Pub. 8s. 6d. Postage 6d.

Rapid Servicing of Transistor Equipment. By G. J. King. 30s. Postage 1s. 6d.

Computers for the Amateur Constructor. By R. H. Warring. 20s. Postage 1s.

Radio and Audio Servicing Handbook. By G. J. King. 30s. Postage 1s. 6d.

Radio Handbook. By W. I. Orr. 84s. Postage 3s.

Transistor Receivers and Amplifiers. By F. G. Rayer. 30s. Postage 1s. 6d.

Radio Valve Data 8th ed. Compiled by "WW". 9s. 6d. Postage 1s.

We have the Finest Selection of English and American Radio Books in the Country

19-21 PRAED STREET (Dept RC) LONDON W2

Telephone PADdington 4185

FREE TO AMBITIOUS ENGINEERS

—THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 132-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronic Courses, administered by our Specialist Electronics Training Division—explains the benefits of our Appointments Dept. and shows you how to qualify for five years promotion in one year.

SATISFACTION OR REFUND OF FEE

Whatever your age or experience you cannot afford to miss reading this famous book. If you are earning less than £30 a week send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

WHICH IS YOUR PET SUBJECT

- RADIO
- TELEVISION
- ELECTRONICS
- ELECTRICAL
- MECHANICAL
- CIVIL
- PRODUCTION
- AUTOMOBILE
- AERONAUTICAL
- PLASTICS
- BUILDING
- DRAUGHTMANSHIP
- B.Sc.
- CITY & GUILDS
- GENERAL CERTIFICATE OF EDUCATION
- ETC., ETC.

PRACTICAL EQUIPMENT

Basic Practice and Theoretical Courses for beginners in Radio T.V. Electronics Etc. A.M.I.E.R.E. City & Guilds Radio Amateur's Exam. R.T.E.B. Certificate. P.M.G. Certificate. Practical Radio, Radio & Television Servicing Practical Electronics Electronics Engineering Automation

INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T.

NOW offers you a real laboratory training at home with practical equipment.

Ask for details.



POST COUPON NOW!

- Please send me your FREE 132-page "ENGINEERING OPPORTUNITIES" (Write if you prefer not to cut page)

■ NAME

■ ADDRESS

■

■

■ SUBJECT OR EXAM THAT INTERESTS ME 409B

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

(Dept. 409B), Aldermaston Court, Aldermaston, Berkshire

THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

BI-PAK SEMICONDUCTORS (Dept. C) 8 Radnor House, 93/97 Regent St., London W.1

NEW AND TESTED VALUE PACKS

One 10/- Pack of your own choice free with orders valued £4 or over.

2 Drift Trans. 2N1225 Germ. PNP 100 Mc/s	10/-
6 Matched Trans. OC44/45/81/81D	10/-
4 OA10 Diodes Mullard 30 PIV IA	10/-
15 Red Spot AF Trans. PNP	10/-
15 White Spot RF Trans. PNP	10/-
4 Silicon Rects. 3A 100/400 PIV	10/-
2 10A Silicon Rects. 50 and 100 PIV	10/-
8 Germ. Diodes OA70 Mullard	10/-
2 OC139 Trans. NPN Switching	10/-
1 12A SCR 100 PIV	10/-
3 Sil. Trans. 25303 PNP	10/-
10 Assorted Computer Diodes	10/-
3 NPN Med. Speed Switching Trans.	10/-
4 Zener Diodes 250mW 3-12V	10/-
4 2G417 Trans. Eqvt. AF17	10/-
2 200 Mc/s Sil. Trans. NPN BSY26/27	10/-
2 Bi-directional Trans. ASY66 PNP	10/-
3 Zener Diodes 400mW 33V 5% Tol	10/-
4 High Current Trans. OC42 Eqvt.	10/-
2 Power Transistors 1 OC26 1 OC35	10/-
5 Silicon Rects. 400 PIV 250mA	10/-
3 OC71 Transistors Mullard Type	10/-
3 OC75 Transistors Mullard Type	10/-
3 NPN Silicon Trans. 70 Mc/s	10/-
1 Power Trans. OC20 100V	10/-
5 OA47 Gold Bonded Diodes	10/-
4 OA202 Sil. Diodes Sub-min	10/-
2 Low Noise Trans. NPN 2N929/30	10/-
1 Sil. Trans. NPN VCB 100 ZT86	10/-
8 OA81 Diodes (CV448)	10/-
3 OC72 Transistors Mullard Type	10/-
3 OC77 Transistors Mullard Type	10/-
5 Metal Alloy Transistors Mat Type	10/-
5 Sil. Rects. 400 PIV 500mA	10/-
5 GET84 Trans. Eqvt. OC44	10/-
5 GET883 Trans. Eqvt. OC45	10/-
2 GET20 Germ. PNP Trans. with Heat-sink	10/-
3 VHF Sil. Epoxy Trans. NPN 100 Mc/s	10/-
2 2N708 Sil. Trans. 300 Mc/s NPN	10/-
2 GT41/45 Germ. Trans. FNP Eqvt. OC71	10/-
2 GT31 LF Low Noise Germ. Trans. PNP	10/-
6 IN914 Sil. Diodes 75 PIV 75mA	10/-
8 OA95 Germ. Diodes Sub-min IN69	10/-
3 NPN Germ. Trans. NKT773 Eqvt. AC130	10/-
2 OC22 Power Trans. Germ.	10/-
2 OC25 Power Trans. Germ.	10/-
2 OC73 Mullard Trans.	10/-
4 AC128 Trans. PNP High Gain	10/-
2 AC127/128 Comp. pair PNP/NPN	10/-

10 Assorted Gold Bonded Diodes	10/-
5 TK22C Germ. Switching Trans.	10/-
3 2N1307 PNP Switching Trans.	10/-
3 OC76 Mullard Trans.	10/-
20 Germ. Diodes General Purpose	10/-
7 CG52H Germ. Diodes Eqvt. OA71	10/-
3 OC170 Trans. Mullard Type	10/-
3 AF116 Mullard Type Trans.	10/-
12 Assorted Germ. Diodes Marked	10/-
1 30 Amp Power Rectifier 100 PIV	10/-
4 AC126 Germ. PNP Trans.	10/-
5 1 Amp Germ. Rect. 200 PIV	10/-
4 OA5 Gold Bonded Diodes	10/-
1 ORP61 Photo-conductive cell	10/-
4 Silicon Rects. 100 PIV 750 mA	10/-
3 AF117 Trans. Mullard Type	10/-
3 OC81 Type Trans.	10/-
3 OC171 Trans. Mullard Type	10/-
1 ORP12 Photo-conductive cell LDR03	8/6
2 10A 600 PIV Sil. Rects. IS425R	15/-
3 BC108 Sil. NPN High Gain Trans.	15/-
2 Zener Diodes 25W 18 and 22V	15/-
1 2N910 NPN Sil. Trans. VCB100 80 Mc/s	15/-
2 1000 PIV Sil. Rect. 1.5A RS310 AF	15/-
3 High Volt. AF Trans. PNP ACY17	15/-
3 BSY95A Sil. Trans. NPN 200 Mc/s	15/-
3 OC200 Sil. Trans. Mullard	15/-
2 Sil. Power Rects. BYZ13	15/-
1 AF139 VHF Germ. Trans. 1500 Mc/s	15/-
1 Sil. Power Trans. NPN 100 Mc/s TK201A	15/-
6 Zener Diodes 3-15V Sub-min	15/-
1 2N1132 PNP Epitaxial Planar Sil. Trans.	15/-
2 2N697 Epitaxial Planar Trans. Sil.	15/-
4 Germ. Power Trans. Eqvt. OC16 Mullard	15/-
1 Unijunction Trans. 2N2646 Eqvt. D5E29	15/-
2 Sil. Trans. 200 Mc/s 60Vcb ZT83/84	15/-
1 Sil. Planar Trans. NPN 100 Mc/s BSY25	15/-
1 Sil. Trans. IS104 150 Mc/s HFE 200 NPN	15/-
2 SCRs 50 PIV IA TO-5 can	15/-
1 Tunnel Diode IN3720 (TD5) G.E.	15/-
1 Unijunction Trans. 2N2160 TO-5 can G.E.	15/-
2 Sil. Rects. 5A 400 PIV Stud Type	15/-
2 Germ. Power Trans. OC28/29	15/-
1 10A Sil. Stud Rect. 800 PIV	15/-
1 Tunnel Diode AEY111 1050 Mc/s STC	15/-
2 2N2712 Sil. Epoxy Planar HFE225 max.	15/-
1 2N1257 PNP Sil. Planar TO-5 can	15/-
1 Sil. Power Trans. NPN 25721 85W	15/-
6 2N2926 NPN Sil. Planar Trans.	20/-
6 BY100 Type Sil. Rects.	20/-
25 Sil. and Germ. Trans. Mixed all Marked New	30/-

Minimum Order 10/-, CASH WITH ORDER PLEASE. Add 1/- postage and packing per Order. GUARANTEED by return postal service. Overseas add extra for Airmail.

Our vast stocks change daily with hundreds of Semiconductor bargains becoming available. Just send 2/6 to cover 3 months mailing of our latest stock lists, eqvt. charts, circuits, etc.

VALUE PACKS FOR '67 NEW UNTESTED

120 GERM. SUB-MIN. DIODES	10/-
50 MIXED TRANSISTORS	10/-
16 SILICON 750mA TOP-HAT RECTIFIERS	10/-
20 ALL TYPES MIXED VOLTS ZENERS	10/-
25 SIL. NPN 200 Mc/s TRANSISTORS	10/-
10 STUD 2 AMP SILICON RECT	10/-
75 GERM DIODES GOLD-BONDED	10/-
30 PNP/NPN MIXED SILICON TRANSISTORS	10/-
60 SILICON 200 mA DIODES	10/-
40 ZENERS RECTIFIERS MIXED TOP HAT	10/-
20 1 AMP GERM. UP TO 300 PIV RECTIFIERS	10/-
40 LIKE OC81 AC128 TRANSISTORS	10/-
10 50-400 PIV 1 AMP SCR'S	20/-

Value in the Shops 80/9

THE RADIO CONSTRUCTOR
SPECIAL PRIVILEGE PRICE OF

THE *NEW*
TOLTEC
HAIR DRYER



SPECIFICATION

Moulded in beautiful symmetrical pastel blue impact resisting thermoplastic casing.
Quiet in operation.
Hot or cold air.
No radio or T.V. Interference—meets British standard specification.

Fitted with safety cut-out.
12 months & money refund guarantee. 230-250 volts A.C. only.
Value 80/9 in the shops

Send the coupon below with the sum of only 57/- (this includes 4/6d to cover postage, packing and insurance, unless you are collecting personally).

Please send me one Toltec Hair Dryer at the special privilege price as advertised in *The Radio Constructor*.

I enclose cheque/postal order value


Name.....

Address.....

(Block Capitals please)

To: Toltec Electronic & Trading Co. Ltd.
Hatton House, Hurst Green, Etchingam, Sussex

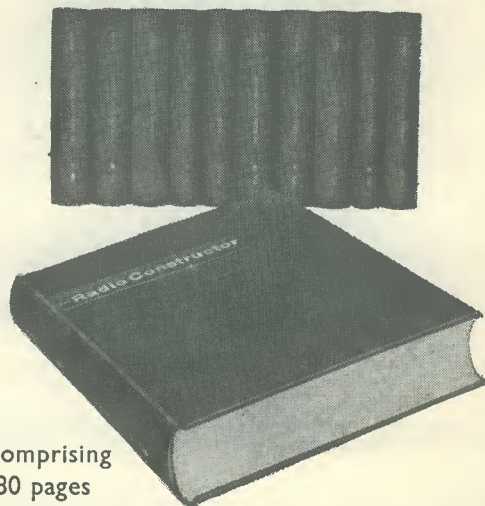BOUND VOLUME No. 19 of "The Radio Constructor" FOR YOUR LIBRARY



Comprising
780 pages
plus index

Volume 19

August 1965 to July 1966

PRICE 30/- Postage 4/6

Special discount of 10/- for regular readers

Where the 12 monthly issues making up the volume are returned, the price is only 20/- plus 4/6 postage

BOUND VOLUME No. 20
August 1966 to July 1967
will be available late August

Available only from:—

Data Publications Ltd.
57 Maida Vale London W9



**Bargains
for
August**

7 Valve AM/FM RG Chassis

A powerful high performance instrument. L/M/FM. Large clear dial. A.V.C., neg. feedback. Magic eye 3 w. output. A.C. Circuit diagrams available. Aligned, tested and ready for use (Carr. and ins. 7/6) S.A.E. for details. **£13.19.6**

GARRARD PLAYERS AND PLINTHS

LM.3000 Record Player with 9 T.A. Stereo Cartridge. Brand new 8 gns.

Plinths. The ideal mounting for Units offered here. Will readily suit any hi-fi set-up. Teak finish with soft plastic dust cover. Packing and carriage 5/-. Clear-view rigid plastic cover 57/6, (P. & P. 3/6).

AT.60 Mk.11 De-luxe Auto-change-over Die-cast T/ Table. Less cart- ridge. **£11.19.6**

SP.25 De-luxe single record player, less cart- ridge. Die cast T/ Table. Packing and carr. on any- one of above, 7/6 extra.

Garrard Cartridges. Hi-fi quality turnover mono and stereo cart- ridges. Mono from 25/- All post free.

T.R.S. MULLARD 3-3 V/With basic controls, 45 distortion. Bronze escu- cheon panel. Complete Kit only £7.10.0. Carr. 7/6. Wired and tested, £9.10.0. Carr. 7/6.


T.R.S. MULLARD 5-10 3-valve. Hi-Fi quality. 5 valves 10W, 3 and 15 ohms output. Heavy duty ultra-linear O/P. Basic for 3W, less than 1% amplifier kit price £9.19.6. Carr. 7/6. Ready built 11½ gns. (Carr. 8/6) Two Valve Pre-Amp Unit (Mullard Design) Kits £6.12.6. Built. £8.10.0. Carriage 5/6.

TRS Mullard Stereo 10-10

Valve amplifier by T.R.S. to exact Mullard spec. Complete with pre-amp and o/p transformers tapped for 3 and 15 Ω Bass, treble, volume, balance controls. Outlet for H.T. and L.T. for tuner. Switching for mono/stereo and speaker phasing. Shrouded pre-amp. Complete with plugs, sockets, escutcheon knobs, etc. Kit **£17.10.0** Wired and tested. £19.10.0. (C/P 10/-).

TRS RADIO COMPONENT SPECIALISTS *Established 1946*

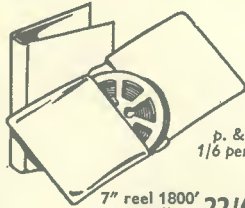70 Brigstock Road, Thornton Heath, Surrey
01-684 2188. Hours 9 a.m.—6 p.m. 1 p.m. Wednesdays
A few doors from Thornton Heath Stn. (S.R. Victoria section.)



p. & p.
1/6 per reel

7" reel 1800' with wallet **22/6**

Exclusive Tape Offer from TRS

FREE LIBRARY WALLET WITH EVERY REEL OF TAPE
With each reel of this tape by an internationally famous manufacturer we give you a beautifully made wallet strongly made in simulated leather with space for a reel of tape each side. This is professional quality full frequency tape with metallised leader/stop foils. These library wallets solve once and for all the problems of storing tapes efficiently and tidily.

5 1/2" reel, 1200' with wallet **17/6**
5" reel, 900' with wallet **12/6**
TAPE REELS—7"-2/3; 5 1/2"-2; 5"-2; 3"-1/3. (p/p 6d.)

LARGE STOCKS OF TRANSISTORS, TRANSISTOR COMPONENTS, COILS, SWITCHES, VALVES, SPEAKERS, ETC. - ALWAYS AT KEENE'S BEST PRICES AVAILABLE.
TYGAN FRET or Vynair loudspeaker fabric, 12 x 12in. 2/-; 12 x 18in. 3/-; 12 x 24in. 4/-. etc. **BONDACOUST** Speaker Cabinet Acoustic Wadding, approx. 1in. thick, 18in. wide, any length cut, 2/3 ft. 6/- yd. **EXPANDED ANODIZED METAL.** Attractive gilt finish 1/2 x 1/4in. diamond mesh 4/6 sq. ft. Multiples of 6in. cut. Max. size 4 x 3ft. 47/6 plus carr. **VOLUME CONTROLS—**

5K-2 Meg. ohms. 3in. spindles. Morganite Midget Type 1 1/4in. diam. Guar. 1 year. LOG or LIN. ratios less Sw. 3/6. DP. Sw. 5/-. Twin Stereo less Sw. 7/6. 100K to 2M ohms. with DP. Sw. 9/6. **STEREO BALANCE CONTROLS.** Log/Anti-Log 5K, 1/2, 1 or 2 Meg., 9/- ea. **VEROBOARD—**All standard sizes including 2 1/2in. x 5in. 3/8; 2 1/2in. x 3 1/2in. 3/8; 2 1/2 x 5in. 5/2; 3 1/2 x 3 1/2in. 3/8; 2 1/2 x 17in. 12/6. All accessories and tools in stock. **RESISTORS—**Modern ratings, full range 10 ohms to 10 megohms, 10% ± w. 4d. ea., 5% Hi-Stab., 1/2 w. 6d. ea., (below 100 ohms and over 1 meg. 9d. ea.), 1% Hi-stab., 1/2 w. 1/6 ea. (below 100 ohms 2/- ea.)

WIREWOUND RESISTORS 25 ohms to 10 K, 5 w. 1/3; 10 w. 1/6; 15 w. 2/-. **CONDENSERS Silver Mica.** All values 2 pf. to 1,000 pf. 6d. ea. Ditto ceramics 9d. Tub. 450 v. T.C.C., etc., .001 mfd. to 0.1 mfd., 1/350 v. 10d., .02 mf. to 0.1 mf. 500 v. 1/-, .25 T.C.C. 1/6. 5 T.C.C. 1/9. **CLOSE TOL. S/MICAS.** 10% 5 pf. 500 pf. 8d. 600-5,000 pf. 1/-, 19% 2 pf.-100 pf. 9d. 100 pf. 9d., 100 pf., 500 pf. 11d. 575 pf. 5,000 pf. 1/6. **ALUMIN. CHASSIS.** 18 g. Plain un-drilled folded 4 sides 2in. deep. 6 x 4in. 4/6d, 8 x 6in. 5/9; 10 x 7in., 6/9; 12 x 6in. 7/6; 12 x 8in. 8/-. etc. Please send S.A.E. with all enquiries.

OUR LATEST LIST is brimful of bargains and hard-to-find components. Send 6d. stamp for free copy.

PRE-PAK SEMICONDUCTORS

DISTRIBUTED EXCLUSIVELY BY

DAVIS & WHITWORTH LTD., DEPT. E. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX PHONE: SOUTHEM (0702) 46344

No.	DESCRIPTION	PRICE
A1.	6—Silicon rectifiers BY100 type	20/-
A2.	10—Relays mixed types and voltages	20/-
A3.	20—Mixed marked and tested trans.	20/-
A9.	1—2N174 real power trans. 80V 150W	20/-
A15.	2—Power Comp. Pair. AD161/2	20/-
A17.	3—Sil. stud recs. 6 amp. 400 PIV. BYZ12	20/-
A18.	2—Sil. stud recs. 10 amp. 800 PIV	20/-
A20.	1—AU10 VHF power trans. 60 Mc/s 70V	20/-
B1.	50—Unmarked untested, trans., new	10/-
B2.	4—Solar cells, inc. Book of Instructions	10/-
B3.	4—OAS gold bonded, diodes Mullard	10/-
B5.	7—Matched set, OC44, 45/81D/81 + diode	10/-
B6.	15—Red spot AF. trans. or white spot RF	10/-
B8.	2—Power trans. OC26/35 type	10/-
B9.	1—Light sensitive cell, ORP12 type	9/-
B10.	10—50V trans. germ. PNP latest type	10/-
B44.	1—Tunnel diode, AEY11, 1050 Mc/s	10/-
B21.	2—Sil. recs. 10 amp., 50-100 PIV	10/-
B52.	30—Trans. new tested, but unmarked	10/-
B42.	5—Switching trans. TK22C STC	10/-
B45.	1—Power trans. ADY22/TK400A VCB60 IC 8 amps. PNP	10/-
B47.	10—Sil. stud recs. 3 amp. unmarked untested	10/-
B49.	2—Power trans. GET 9 VCB64 IC 8 amp. germ. PNP	10/-
B50.	2—Light sensitive cells ORP60 type	10/-
C2.	1—Uni junction, 2N2160 or 2N2646	15/-
C4.	2—RF power trans., OC22 and BUY11	15/-
C31.	4—Sil. recs. 800 PIV 1/2 amp. top hat	15/-
C32.	2—Power trans. TK400A/NKT404 VCB64 IC 8 amp.	15/-

FANTASTIC! BARGAINS OF THE YEAR!

GENUINE TRANSISTORS NOT REMARKS			
OC45	IF transistor	1/9	OA9 Equal to OAS 2/-
OC44	Osc. transistor	1/11	OC36 Power transistor (better than OC35) 7/6

NEW FACTORY TESTED PRE-PAKS. ALL PERFECT BUT UNMARKED

50	Germ. Min.	DIODES 10/-	30	All types	TRANSISTORS 10/-
10	Silicon 750 mA Top Hat	RECTIFIERS 10/-	40/-	Silicon Sub. Min.	DIODES 10/-
5	3 amp. Silicon	STUD RECS. 10/-	10	NPN Silicon	TRANSISTORS 10/-

TRANSISTORS	PRICE	BFY50	...	15/-	OC170	...	2/6	2N1309	...	7/6
AC107	...	6/-	BSY25	...	10/-	OC171	...	25303	...	2/6
AC126	...	2/6	BSY26	...	5/-	OC200	...	5/-	POWER TRANSISTORS	10/-
AC127	...	2/6	BSY27	...	5/-	OC201	...	2/6	OC20	10/-
AC128	...	3/-	BSY28	...	5/-	2G301	...	2/6	OC23	10/-
ACY17	...	5/-	BSY29	...	5/-	2G303	...	2/6	OC25	8/-
AF114	...	4/-	BSY95A	...	5/-	2N697	...	5/-	OC26	5/-
AF115	...	3/-	OC41	...	2/6	2N706	...	5/-	OC28	5/-
AF116	...	3/-	OC71	...	2/6	2N711	...	10/-	OC35	5/-
AF117	...	2/6	OC72	...	2/6	2N1302	...	4/-	DIODES	...
AF118	...	3/6	OC73	...	5/-	2N1303	...	4/-	AA472	2/-
AF119	...	3/6	OC81	...	2/6	2N1304	...	5/-	OA10	2/-
AF178	...	10/-	OC81D	...	2/6	2N1305	...	5/-	OA70	1/9
ASV66	...	2/-	OC83	...	4/-	2N1306	...	6/-	OA79	1/9
BCZ11	...	7/6	OC139	...	2/6	2N1307	...	6/-	OA81	1/9
			OC140	...	5/-	2N1308	...	8/-	OA182	2/-
									IN914	1/6

FREE ★★
Packs of your own choice to the value of 10/- with all orders over £4.

SEND FOR OUR FREE LISTS AND CATALOGUE OF ALL OUR PRODUCTS. CHECK YOUR OWN EQUIVALENTS WITH OUR FREE SUBSTITUTION CHART.

NO CONNECTION WITH ANY OTHER FIRM MINIMUM ORDER 10/- CASH WITH ORDER PLEASE. Add 1/- post and packing per order. OVERSEAS ADD EXTRA FOR AIRMAIL.

Great News ★
We now give a written guarantee with all our semi-conductors.



Two Home Radio directors making a quick exit from the Crazy Horse Saloon, following an unsuccessful attempt to find some new components. (What we did see was certainly not new—neither was it very adequately insulated!)

You can take the above cartoon just as seriously or as unseriously as you choose. The fact is that two of us from Home Radio did go to Paris last April to visit the Electronic Components Exhibition. It is one of the finest exhibitions of its kind in the world—we have been regular visitors for several years. Moreover, **wherever** there is an important exhibition of this kind you will find us there, for we are keen to keep up with the very latest developments in electronics, and to list the cream of the components in our catalogue. Only in this way can we ensure that our catalogue is really comprehensive and up to the minute, and that it will maintain its reputation as one of the finest component catalogues available.

If you wish to keep up to the minute, electronically, you certainly need not spend a fortune and weeks of your time touring

round the world's exhibitions. You simply have to spend nine shillings (our catalogue costs 7/6 plus 1/6 p. & p.) and a minute or two of your time sending the cheque or P.O. with the attached coupon. Your catalogue will be sent by return post. We guarantee you will be delighted with its contents—especially with the page containing 5 vouchers, each worth a shilling when used as directed!

Please write your Name and Address in block capitals

Name.....

Address.....

Home Radio Ltd., Dept. RC, 187 London Road, Mitcham, CR4 2YQ



Vol. 21, No. 1

Published Monthly (1st of month)

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9

Telephone *Telegrams*
CUNningham 6141 Databux, London

© Data Publications Ltd., 1967. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription 36s. (U.S.A. and Canada \$5) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers please pay by cheque or International Money Order.

Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. Queries should be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production.—Letterpress/contact litho.

Published in Great Britain by the Proprietors and Publishers
Data Publications Ltd. 57 Maida Vale London W9
Printed by A. Quick & Co. (Printers) Ltd.
Clacton-on-Sea England

10 Watt P.A. Amplifier,	10
by L. Mason	
Simple D.C. Heater Supply for A.F. Amplifiers	17
(Suggested Circuit No. 201),	
by G. A. French	
Can Anyone Help?	18
Windscreen Wiper Programmer,	19
by T. J. Daborn	
Simple Short Wave Converter,	21
by R. L. A. Borrow, B.Sc.	
News and Comment	24
Stereo Decoder Unit	26
An "Integrated" Crystal Oscillator,	27
by James M. Bryant, B.Sc.	
Home-Constructed Radio Alarm,	30
by A. G. Blewett	
The SCT/RS1 Superhet Receiver	32
(Basic Radio Control, Part 7),	
by F. L. Thurston	
A Logical Approach to Logic,	38
by S. J. Houghton, B.Sc.	
Understanding Radio	41
(Classes of Amplification),	
by W. G. Morley	
Combined AF/RF Signal Generator,	44
by W. Kemp	
In Your Workshop	50
Radio Topics,	55
by Recorder	




10 WATT P.A. AMPLIFIER

by L. MASON

One method of obtaining public address without tears is to fall back on the tried and trusty valve designs which have given such dependable service over the years. Our contributor describes two amplifiers built up to a sure-fire 10 watt circuit whose operating principles are easy to follow and which employs low-cost valves. Many of the parts should be found in the average spares box and, since layout is not very critical, it is possible to press a discarded radio chassis into service and thereby avoid time-consuming metalwork

IN THESE DAYS OF HI-FI, 0.1% DISTORTION, AND all that goes with first class musical reproduction, it must not be forgotten that there is still a need for high gain amplifiers with less exacting requirements and at a reasonable cost. For public address systems, sound reinforcement in large halls and even for party music, 5% distortion would hardly be noticeable and is probably much better than is given by the average TV or radio.

Moreover, a considerable saving of cost can be made if existing components from the spares box can be used and a former radio chassis is adapted for rebuilding. Many radio sets of twenty years vintage and using octal valves are ready for dismantling, and will yield a good chassis complete with valve-holders. The reliability of octal valves which are still easily and cheaply obtainable, makes them ideal for p.a. work.

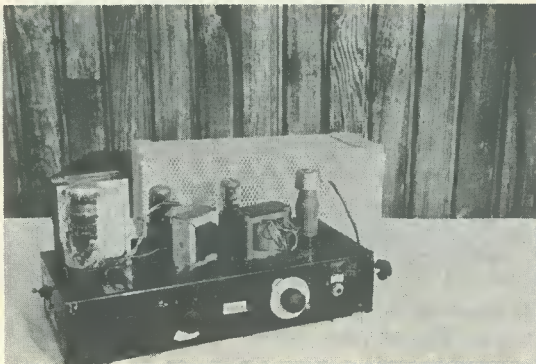

The amplifier of Fig. 2 with the cover removed. Note the screened top-cap connector for V_1 .

The writer uses an extremely trouble-free octal amplifier design offering 10 watts output for p.a. work.¹ This amplifier has no negative feedback, and an output of 10 watts with only 5% distortion can be obtained from a microphone input of 15mV. Musical reproduction is also quite satisfactory. The writer has built two of these amplifiers on old radio chassis, one of which has had two years' regular use for speech reinforcement in a Church building measuring approximately 60 by 40ft. It drives two column units, each containing three loudspeakers.

Circuit design

The first stage, see Fig. 1, consists of a pentode voltage amplifier. If particularly low noise and hum qualities are required, the Mullard EF37A is ideal here. The phase splitter is a Schmitt cathode coupled stage using a high- μ double triode type 6SL7GT. The first stage is resistance-capacitance coupled to one grid of the phase splitter and the Gram input is fed into the second grid, each input being governed by a volume control. The output stage consists of two 6V6G or 6V6GT beam tetrodes in push-pull, with a common cathode bias resistor and bypass capacitor. The screen grids are fed from a potential divider which includes the cathode resistor and maintains very stable working of this stage. The high wattage ratings of these resistors must be adhered to. R18 in particular gets quite hot and must be given adequate ventilation and kept clear of adjacent components.

Construction

Component layout depends entirely upon the

¹This is based on a design published in the Brimar valve manual series, and due acknowledgement is given to Thorn—A.E.I. Radio Valves and Tubes, Ltd.

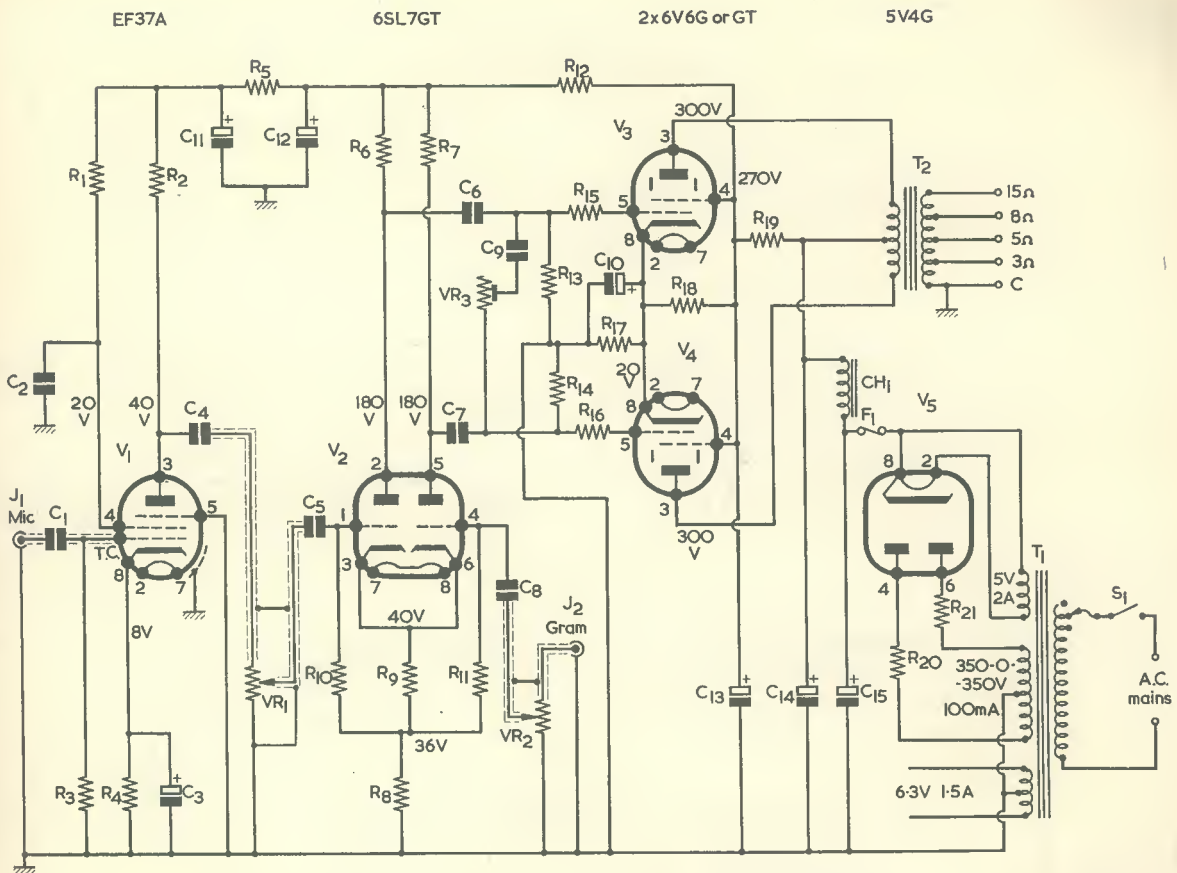


Fig. 1. The circuit of the push-pull 6V6 amplifier. The voltage readings shown were obtained with a 2,000 ohm per volt meter. The current ratings given for T_1 heater secondaries are minimum figures, and currently available mains transformers with the requisite h.t. secondary will normally have higher heater current ratings


chassis available and, to give an idea of what is required, two practical layouts are shown. Small components can be mounted on tagboards, the exact size and location of which again depends upon availability. It is best to use one board for the h.t. resistors and one for the grid and cathode components. Double-ended tags are preferred. The chassis wiring can then be soldered to one end of the tags and the components to the other, making any component replacement easier. Since the electrolytic capacitors are of low value, small tubular types of adequate voltage rating can be used, these being mounted under the chassis.

The two greatest difficulties in high gain amplifiers are the elimination of mains hum and the avoidance of feedback causing instability. With the adequate h.t. decoupling used on this amplifier, instability is easily avoided if anode, grid and cathode wires are kept separate to avoid capacitive coupling between these circuits. The elimination of hum will be discussed as the construction of different parts of the circuit is described.


A chassis of approximately 12 x 8in or equivalent area, and 3in deep, will give ample room for all the components, and a steel chassis will give greater freedom from hum than an aluminium one. Valve and transformer positions should first be decided upon. The existing valve positions will usually suffice. If there are not enough valveholders, one can be fitted in a hole originally provided for an upright electrolytic capacitor or an intermediate frequency transformer.

Since a new mains transformer of sufficient current rating will probably have to be purchased, an upright mounting one will be easier to fit and will give greater freedom from hum. It will also take up no under-chassis space, as would a drop-through type. Its size will probably decide its location, which should be nearer the rectifier and output valves.²

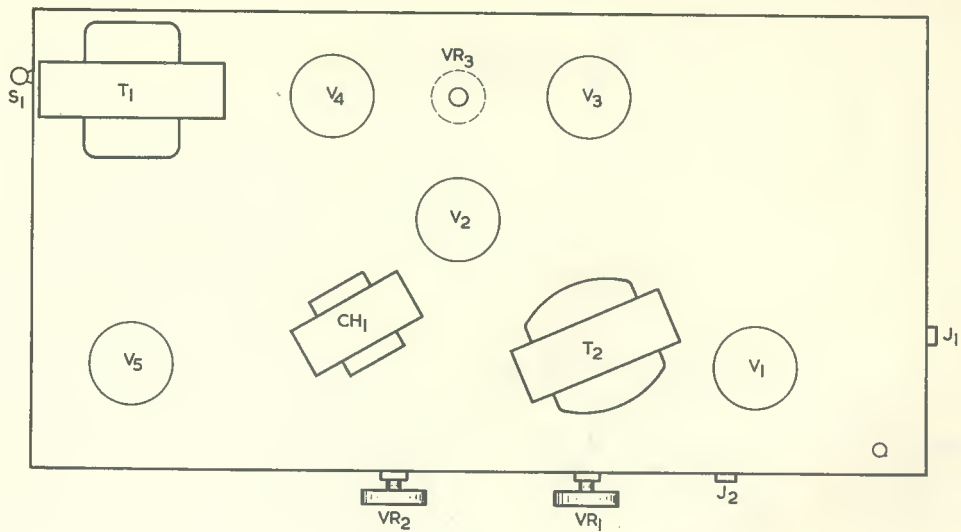²The advertisements for the mains transformer specified in the Components List do not normally mention the existence of a centre-tap on the 6.3 volt heater winding, as is shown in Fig. 1. R.S.C. Hi-Fi Centres Ltd. advise us, however, that such a tap is in practice provided with this transformer.—Editor.



(a)

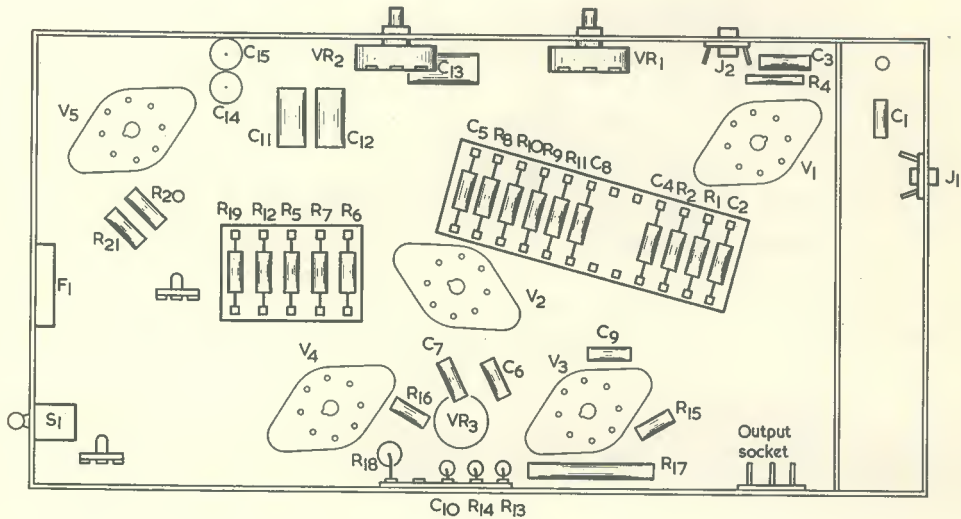

(b)

Fig. 2. Above-chassis view (a) and below-chassis view (b) of one of the amplifiers built by the author. This is constructed on a discarded radio chassis which already had five convenient holes suitable for octal valveholders

Any isolated valve position is best used for the first valve and the valves may be located as nearly as possible in the order in which they appear in the circuit.

Having determined the best location of the valves and mains transformer, the choke can now be positioned for minimum hum pick up. The choke requires an adequate current rating and a former TV choke will often prove suitable. To insure that no mains hum will be induced into the choke from the

mains transformer, a pair of headphones is connected to the choke and, after making quite certain that its secondary leads are safely insulated and not shorting, the mains transformer can be connected to the mains supply temporarily by means of a small terminal block. When the choke is held close to the mains transformer, a slight hum will be heard in the phones. The choke should then be moved an inch or so away and rotated until a hum-free position is found. The output transformer can be positioned similarly,

COMPONENTS

Resistors

(All fixed values $\frac{1}{2}$ watt 10% unless otherwise stated)

R ₁	1 M Ω , high stab.
R ₂	220k Ω , high stab.
R ₃	220k Ω , high stab.
R ₄	1k Ω
R ₅	47k Ω
R ₆	100k Ω , 5%
R ₇	100k Ω , 5%
R ₈	47k Ω
R ₉	2.2k Ω
R ₁₀	1M Ω
R ₁₁	1M Ω
R ₁₂	22k Ω
R ₁₃	220k Ω , 5%
R ₁₄	220k Ω , 5%
R ₁₅	4.7k Ω
R ₁₆	4.7k Ω
R ₁₇	220k Ω , 5 watt
R ₁₈	15k Ω , 10 watt
R ₁₉	1.5k Ω , 5 watt
R ₂₀	100–500 Ω (see text)
R ₂₁	100–500 Ω (see text)
VR ₁	500k Ω potentiometer, log
VR ₂	500k Ω potentiometer, log
VR ₃	250k Ω potentiometer, linear, preset

Capacitors

(All capacitors 450V wkg. unless otherwise stated)

C ₁	0.01 μ F, 150V wkg.
C ₂	0.1 μ F
C ₃	12 μ F, electrolytic, 6V wkg.
C ₄	0.02 μ F
C ₅	0.01 μ F, 250V wkg.
C ₆	0.01 μ F
C ₇	0.01 μ F
C ₈	0.01 μ F, 250V wkg.
C ₉	0.002 μ F, 150V wkg.
C ₁₀	50 μ F, electrolytic, 25V wkg.

C ₁₁	4 μ F, electrolytic
C ₁₂	4 μ F, electrolytic
C ₁₃	8 μ F, electrolytic
C ₁₄	8 μ F, electrolytic
C ₁₅	8 μ F, electrolytic

Inductors

T ₁	Mains transformer, upright mounting. Secondaries: 350–0–350V, 100mA; 6.3V, 4A, c.t.; 0–5–6.3V, 3A. (See caption to Fig. 1)
T ₂	Push-pull 10–12 watt, to match 2 6V6's to 3, 5, 8 or 15 Ω
CH ₁	10H, 100mA

(All inductors may be obtained from R.S.C. Hi-Fi Centres Ltd., 102 Henconner Lane, Bramley, Leeds 13)

Valves

V ₁	EF37A
V ₂	6SL7GT
V ₃	6V6G or 6V6GT
V ₄	6V6G or 6V6GT
V ₅	5V4G

Fuse

F ₁	250mA fuse, with holder
----------------	-------------------------

Switch

S ₁	s.p.s.t., toggle
----------------	------------------

Sockets

J _{1,2}	Input jacks
	5 octal valveholders
	Speaker outlet socket (see text)

Miscellaneous

	Screened top cap connector (for V ₁)
	2 knobs
	Screened wire
	Chassis (see text)

with the headphones connected to the primary winding. If a new output transformer has to be purchased, one of adequate wattage rating, to match two 6V6 valves in push-pull, should be obtained. It will be worth the few extra shillings to obtain a transformer with a tapped secondary winding to suit any combination of loudspeakers likely to be used. The transformers and choke can now be bolted to the chassis using any available holes, and near enough to the suitable positions. This partly accounts for the angles at which the components appear in the typical layouts of Figs. 2 and 3.

The tagboards are then fixed under the chassis. Often some of the bolts can be used both for transformers above and tagboards beneath. There will probably be enough holes in the front or ends of the

chassis for the volume controls and input sockets. If there are no end pieces, it will be advisable to make some from sheet metal to protect the components and to give complete screening.

The position of the small components has now to be determined and a sketch may be made of the tagboards and valveholders, showing point to point wiring. The h.t. electrolytic capacitors may be held in clips and additional small tagstrips will be required for the heater connections to the mains transformer and the rectifier anode stopper resistors. Coloured wiring helps in identification and the drawing can be similarly coloured. Usual colours are:

H.T. and anode wiring	—Red
Screen grid wiring	—Orange
Control grid wiring	—Green

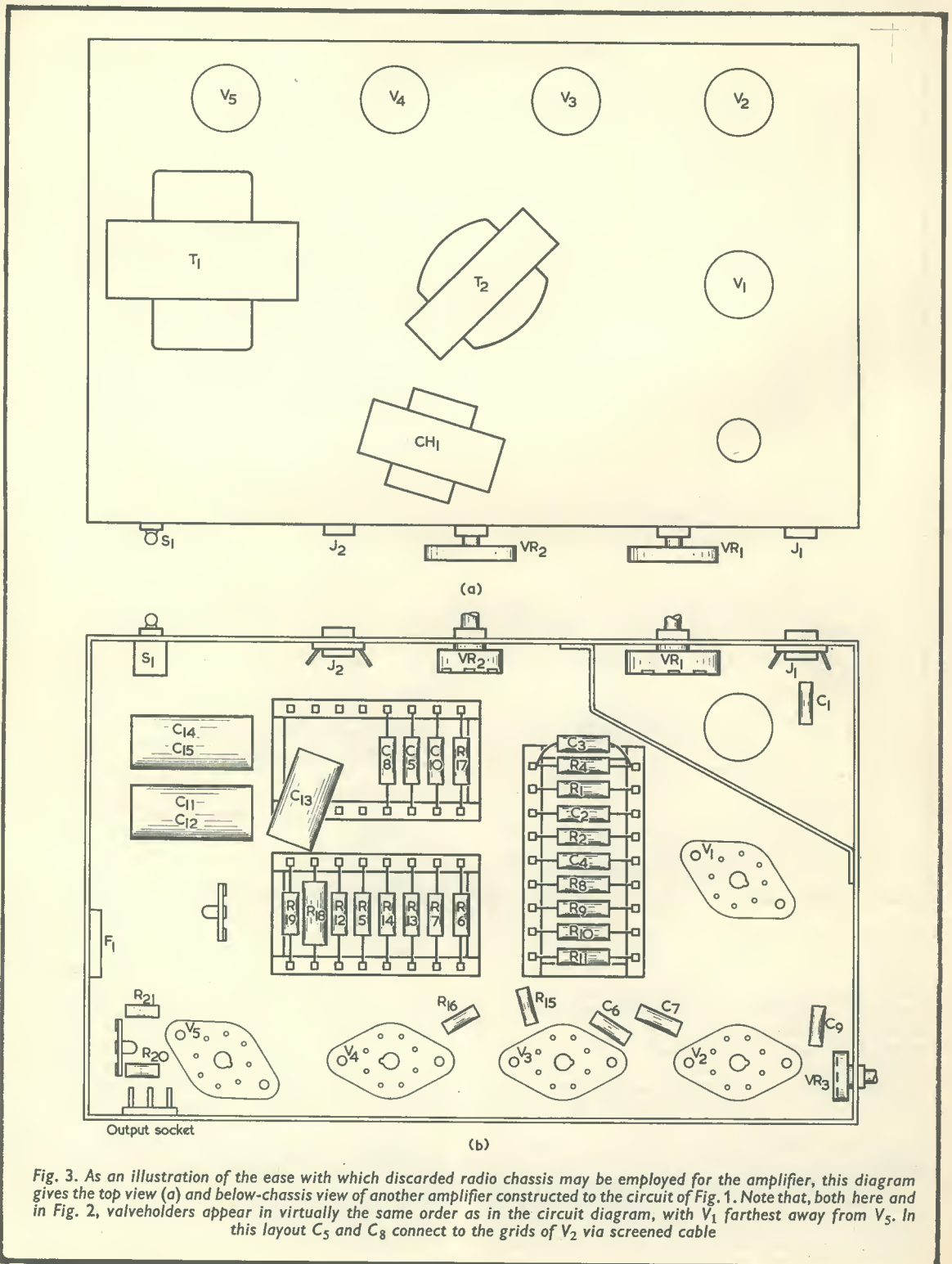


Fig. 3. As an illustration of the ease with which discarded radio chassis may be employed for the amplifier, this diagram gives the top view (a) and below-chassis view of another amplifier constructed to the circuit of Fig. 1. Note that, both here and in Fig. 2, valveholders appear in virtually the same order as in the circuit diagram, with V_1 farthest away from V_5 . In this layout C_5 and C_8 connect to the grids of V_2 via screened cable

Cathode wiring —Yellow
 Earth wiring —Black or bare
 High voltage a.c. wiring —Blue or violet.


When wiring passes through the chassis, the holes should always be fitted with grommets. The provision of an h.t. fuse is a wise precaution.

Wiring

Chassis wiring commences with the valve heater leads. Mains twin flex, p.v.c. covered is ideal. Flex with "figure-8" section should be twisted before fitting, and twisted flex should be more tightly twisted to cancel hum fields. The heater leads from the mains transformer can be connected to the heater wiring via a three-way tagstrip with the centre tap on the earthed fixing tag. This tag should also be used for earthing the h.t. secondary winding centre tap and the h.t. electrolytic capacitor negative leads. Heater wiring should run close to the chassis and be isolated from all other wiring as far as is practicable. The rectifier valve heater is of course wired to the appropriate winding on the mains transformer, one end of which is at h.t. potential.

The remainder of the chassis wiring can next be proceeded with. Particular attention should be given to the wiring that will earth the appropriate components to the chassis, since bad earthing is one of the chief causes of hum. There are two basic systems of satisfactory earthing. With a steel chassis, common earthing of each stage will probably be quite satisfactory. All the necessary components related to a particular stage are earthed to one tag bolted to the chassis at the nearest convenient point. With an aluminium chassis, bus-bar earthing is often recommended. In this system, a bus-bar of thick wire is looped into all the tags connecting the earthy ends of the components. This bus-bar is connected to the chassis at one point only, this being at the microphone input socket. However, this system is not infallible, since its success depends upon the order of connecting the components to the bus-bar, which is an experimental matter in each amplifier built. A good arrangement can work well, whilst a bad one is worse than separate earthing of each stage. Since one of the purposes of this article is to encourage the constructor to learn the principles of amplifier building by experience, it is hoped that he will work in this spirit and be prepared to experiment. The writer can only say that both of the amplifiers shown were quite satisfactory, the separate stage earthing used with the steel chassis (Fig. 2) being actually better than the bus-bar earthing used on the aluminium chassis (Fig. 3). Screening of the microphone input socket may be required to obviate high frequency instability, which makes itself evident by a very high pitched whistle.

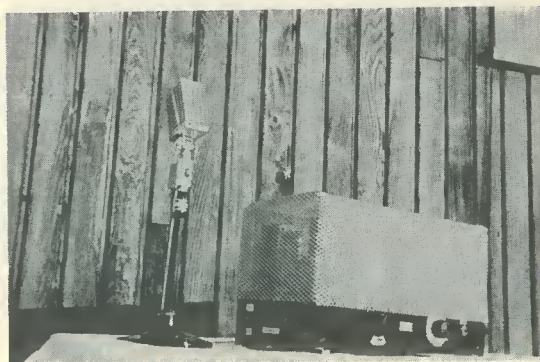The components may next be mounted on the tagboards and it will be advisable to have the high wattage resistors stand clear on longer leads to ensure sufficient ventilation and to prevent them overheating adjacent components. The grid stopper resistors of the output valves should be wired direct from the tagboards to the valveholders, and the coupling capacitors can, if desired, be wired from



The Fig. 2 amplifier installed in a Church building, complete with microphone

the appropriate anode pins to the tagboards. All wiring to the volume controls should be screened, as should also the lead from the microphone input socket to the first valve top cap. A screened top cap connector should be used, with the grid resistor soldered into the cap. A preset potentiometer will suffice for the tone control. This control provides just a little treble cut to remove stylus scratch from old records or any pronounced sibilants from a crystal microphone.³ It will probably only require occasional adjustment and can be mounted in any position convenient for wiring.

Testing

Before switching on, a check should be made with an ohmmeter to ensure that there are no short-circuits between h.t. positive wiring and the chassis or between grid wiring and either h.t. lines or the chassis. The cathode bias resistors can be likewise checked. It is advisable to test the output stage first, then add the other valves successively, checking each in turn. The amplifier should be switched off before inserting a fresh valve. To avoid the appearance of excessively high a.f. voltages across the primary of T₂, the amplifier should not be operated without a speaker connected.

With the rectifier and output valves in place, the amplifier may be switched on and the h.t. voltages checked. The output anodes may have up to 350 volts on them, but 300 volts would be a good value for long life whilst still giving sufficient output. The h.t. voltage may be varied by changing the value of the rectifier anode limiter resistors, R₂₀ and R₂₁. These should both have the same value, between 100 and 500Ω, and must be of adequate wattage rating (1 to 2 watts, according to value). With the h.t. voltage adjusted, the cathode voltage of the output

³A crystal microphone should not be used with the amplifier if good quality reproduction is required, as the relatively low input impedance of the amplifier will cause attenuation of the lower audio frequencies. On the other hand, a crystal microphone may be useful for testing purposes or where reduced low frequency response is not considered important. This problem is absent if a moving-coil microphone is employed, as discussed later in the article. It may be helpful to insert a 1MΩ resistor in series with the Gram input to VR₂ in order to reduce low frequency attenuation with crystal or ceramic pick-ups.—Editor.

valves should be of the order of 18 to 20 volts and the screen grid voltage about 30 volts lower than the anode voltage. There should be slight back-ground noise in the loudspeaker, but no hum.

The phase splitter valve may next be inserted and its voltages should be of the order shown on the diagram. A signal from a record player pick-up or radio may be applied to each volume control in turn, and the amplifier should be found to give satisfactory reproduction.

The first valve should finally be inserted and the complete circuit tested. Since any hum or noise in the first stage receives the greatest amplification, particular attention must be given to this stage. Noise reduction will be improved if high stability resistors are used for the anode load, and screen grid and control grid resistors. It should also be remembered that noise will be much more apparent in a small loudspeaker used for testing than in larger speakers used in a hall, so it might be as well not to be too critical at first. Any hum, more noticeable now that the first stage is complete, may be reduced if the chassis is connected to a real earth via the earth continuity conductor of the mains lead. Also a metal base panel may effect an improvement, by completely screening the chassis, provided it is electrically connected to the chassis. Neither of the writer's amplifiers actually required a metal base and only the one with the aluminium chassis required a real earth. If a metal base is used, it should be perforated to allow for ventilation.

Unless perfection is sought, the criterion for hum and noise level will be the proportion that can be tolerated for the amount of gain at which the amplifier will normally be used. With a microphone connected, the gain will be limited to the point at which acoustic howl feedback is developed. This will vary according to the positioning of the microphone and loudspeaker, and also according to the type of microphone and the design of the loudspeaker cabinet. If felt necessary it may be worth experimenting with a damping resistor of, say, 100k Ω to 500k Ω across the input terminals to achieve greater gain before howling occurs. The theory of this may seem rather doubtful since the resistor attenuates the input somewhat, but it often works quite well in practice, perhaps by damping out a resonant frequency at which the howling occurs. When the best acoustic

conditions have been found, the user will then be in a position to decide whether the hum and noise level is sufficiently low.

A moving coil microphone is the best all-round type for p.a. work so far as the amateur is concerned. A high impedance microphone (50k Ω) may be connected directly into the amplifier. If a very long lead is necessary, the low impedance setting (50 Ω) of a dual-impedance microphone can be used with ordinary flex for the lead, provided that a screened microphone transformer is fitted at the amplifier end of the lead. Only a special mu-metal screened transformer can be fitted inside the amplifier. If an ordinary microphone transformer is used in a metal screening box it will probably have to be at least 18in from the amplifier to avoid hum pick up. The high impedance lead from the transformer must, of course, be screened cable.

Final Finish

Unless a metal base has been found necessary, the amplifier should be completed by the provision of a light base panel to protect the components under the chassis. This may be made from peg-board or from the back fret from an old TV or radio set. Rubber feet should be added to avoid jarring the amplifier when it is set down and to give clearance for cool air to be drawn in through the base panel. A top cover may be folded from expanded metal and handles added if much carrying is anticipated. Alternatively, a ready made cover may be obtained of approximately the right size, and wood fillets added if necessary to make up any differences.

Conclusion

It may be gathered from this article that the building of simple but very effective p.a. amplifiers using the circuit of Fig. 1 is not at all difficult, provided the constructor is prepared to experiment a little and to use a little commonsense judgement with regard to choosing a suitable layout. The accompanying photographs show two views of the amplifier of Fig. 2. The microphone employed is a Calrad DM16HL dual-impedance moving-coil unit. Its 50k Ω output is applied directly to the amplifier without a transformer.



10th Annual Mobile Radio Rally Rykneld Schools, Derby—Sunday August 13th 1967


The above event is one of the most popular attractions in the Amateur Radio enthusiasts calendar. It is a social event that is eagerly awaited every year by large numbers of mobile Radio Amateurs and their families.

The Derby Rally has always been known as a family event and this year's attractions will have all the family in mind. Last year there were over 6,000 visitors, no fewer than 8 Special Displays and 12 Trade Stands.

Events will include all the old favourites, i.e. Treasure Hunt, Prize Draw, Junk Sale, Film Show, Radio Controlled Model Aircraft, etc., etc.

Admission and parking at the Rally is FREE. There is also ample indoor accommodation should the weather be unkind. The usual Ice-Cream, Coca-Cola and Refreshments will be available at very reasonable charges.

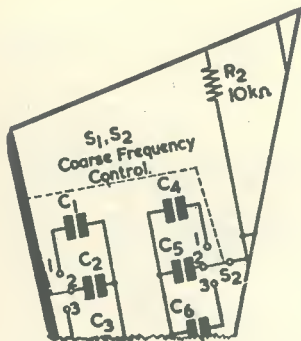Any further information required can be obtained by contacting Mr. Tom Darn G3FGY, Hon. Rally Organiser, "Sandham Lodge", 1 Sandham Lane, Ripley, Derbyshire. Ripley 2972.



Simple D.C. Heater Supply for A.F. Amplifiers

SUGGESTED CIRCUIT No. 201

by G. A. FRENCH

ONE OF THE MAJOR DESIGN problems with sensitive mains-driven a.f. amplifiers is the reduction of hum caused by the a.c. supply. If the amplifier employs valves, hum is particularly likely to result from unwanted couplings between the signal circuits and the heater wiring, and considerable care has to be taken with component and wiring layout to ensure that such couplings are kept to a minimum.

The first stage of the amplifier is, of course, that which is most susceptible to hum, and it is common practice to use a low-noise pentode, such as the EF86, in this position. The EF86 can exhibit a hum level of $1\mu\text{V}$ only when fed with a centre-tapped a.c. heater supply, but it is still necessary to pay careful attention to the valveholder type, valveholder wiring and component positioning if a figure as low as this is to be achieved in a practical working circuit.

Hum in the first stage due to unwanted couplings with the heater wiring can be completely eradicated if the heater of the first valve is fed with d.c. instead of a.c. Whilst this represents an obvious solution to the hum problem, there is a tendency to assume that the provision of the necessary direct current involves the use of special mains transformers and expensive rectifier circuits, whereupon it becomes economically unattractive. Now that small silicon rectifiers and high-value electrolytic capacitors are available, however, the situation is changed, and the cost of a d.c. heater supply need not be as excessive as would have occurred with earlier components.

This month's "Suggested Circuit" presents a simple method of applying a d.c. supply to the first valve of an a.f. amplifier, the alternating voltage being obtained from a normal 6.3V centre-tapped mains trans-


former secondary. The suggestion will be of greater interest from the point of view of application than of circuit operation, since the circuit consists quite simply of a standard bridge rectifier plus several "trimmings". The circuit has the advantages that few components are required, that a standard mains transformer can be employed, and that the heaters of the remaining valves in the amplifier may be run in normal manner from the same 6.3V winding. It must be emphasised that the circuit does not provide a completely pure direct current, since the voltage applied to the valve heater carries a ripple having a peak-to-peak value of the order of 0.2V. However, this figure is much lower than the peak-to-peak value of an alternating 6.3V heater supply with the result that the circuit can offer a very significant reduction in hum pick-up in the first stage of an amplifier, even though it may not give the complete eradication of hum that would result from a fully

smoothed d.c. supply. With the components specified, the circuit is suitable for feeding the heater of an EF86 or any other valve requiring a heater voltage of 6.3 at a current of 200mA.

The Circuit

The circuit of the d.c. supply is given in the accompanying diagram and it consists of a full-wave bridge rectifier running direct from a 6.3V heater winding of the mains transformer. For the circuit to function it is essential that the rectifiers have a low forward resistance and that the capacitor following the bridge has a large value. The rectifiers specified for the bridge are silicon types and thereby meet the first requirement, whilst the capacitor is an electrolytic component having a value of $3,200\mu\text{F}$.

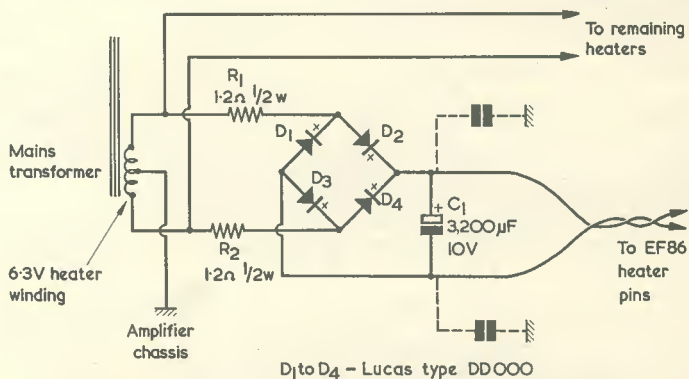In order to keep switch-on surge currents to a low value it is desirable to insert limiting resistance between the transformer winding and the rectifiers. This limiting resistance



By means of this simple rectifier circuit, the first valve of a sensitive a.f. amplifier may be heated by direct current (plus a small ripple) whilst the remaining valve heaters are supplied in normal manner. The two capacitors shown in dotted line may be required in some instances.

must not, however, be too high or the required rectified voltage will not be obtained. In the present circuit the limiting resistance is 2.4Ω , this representing a compromise figure. With a limiting resistance of 2.4Ω the rectified voltage applied to the heater of an EF86 is 6.1V, and it was considered that this is sufficiently close to the nominal value of 6.3V to be acceptable.

The 2.4Ω limiting resistance is split up into two physical resistors of 1.2Ω , as shown, in order to maintain symmetry. It will be appreciated that, on succeeding half-cycles, each of the d.c. heater lines becomes effectively coupled first to one side of the 6.3V secondary and then to the other, whereupon it is desirable to keep the circuit symmetrical in order that the d.c. lines remain balanced about chassis potential. This approach ensures that the 0.2V ripple on the d.c. lines has minimum effect. In this context it is important to note that the 6.3V transformer winding *must* be centre-tapped, with the centre-tap connected to chassis. If, instead, one end of the 6.3V winding were connected to chassis, each of the d.c. heater lines would be taken through some 6.3V on alternate half-cycles and the whole object of the circuit would be defeated!

Components

As is shown in the diagram, the four rectifiers, D_1 to D_4 , are Lucas type DD000, these having a peak inverse voltage of 50 and a forward current rating of 500mA. The electrolytic capacitor employed for C_1 in the prototype was a Mullard component in the C431BR series, with a value of $3,200\mu\text{F}$ and a voltage rating (which should not be exceeded) of 10V. It may be added that the rectified voltage across C_1 will rise to nearly 9V should the EF86 be removed from its valveholder, and this fact has to be borne in mind when deciding upon the working voltage of the capacitor. In general, it would be preferable to switch off the power supply if the EF86 is to be removed and re-fitted, since a slightly excessive current could momentarily flow in its heater if it were plugged in with the supply switched on and C_1 charged to peak rectified voltage.

It will probably be necessary to make up R_1 and R_2 from short lengths of resistance wire, as their value is outside the range normally available for fixed resistors from home-constructor retail sources. Care should be taken to ensure that the resistors have the required value within $\pm 5\%$.

When the d.c. supply circuit is fitted to an a.f. amplifier all the rectifier components should be mounted near the mains transformer. A tightly twisted pair may then be used to couple the rectified voltage across C_1 to the heater pins of the EF86. A twisted pair is recommended since the d.c. supply still carries the 0.2V ripple voltage.

As was stated earlier, the prototype circuit provided 6.1V at 200mA for an EF86 heater using the components specified. The writer does not recommend that the circuit be employed for valves requiring 6.3V at 300mA since the greater current would necessitate reducing the values of R_1 and R_2 , whereupon switch-on surges could become excessively high.

A final point is that the rectified voltage across C_1 is "floating" during the periods in the cycle when the diodes are not conducting and it is feasible that, under some conditions, this could result in a modulation hum being imposed on the a.f. signal being handled. Should this occur, both terminals of C_1 should be coupled to chassis via $0.5\mu\text{F}$ capacitors, as shown in dotted line in the diagram.



CAN ANYONE HELP ?

Requests for information are inserted in this feature free of charge, subject to space being available. Users of this service undertake to acknowledge all letters, etc., received and to reimburse all reasonable expenses incurred by correspondents. Circuits, manuals, service sheets, etc., lent by readers must be returned in good condition within a reasonable period of time

Jason Oscilloscope Model OG10.—B. C. Herring, 710 N.B.S. Building, Port Elizabeth, South Africa, —borrow or purchase circuit diagram. Please write airmail—payment in sterling.

Indicator Type 62A (10Q/37).—A. Thompson, Thursley Cottage, Church Road, East Molesey, Surrey—this unit is fitted with VCR97 tube and EF50 (VR91) valves. Any information on modifying this to an oscilloscope or a circuit using the valves and tube in an oscilloscope, loan or purchase.

F. M. Tuner.—P. G. Tanner, 48 The Crescent, Mortimer, Berks—has constructed this unit (published in Brimar Valve Manual some years ago) and requires advice from any reader who has been successful with this tuner unit.

V.H.F. Receiver Type AP67590A.—T. D. Hackney, 3a Clumber Crescent South, The Park, Nottingham

—would like to purchase or borrow the circuit or any other information.

Wavemonitor Type 1464A.—E. R. Bellas, 41a Nevill Street, Southport, Lancs—wishes to communicate with a reader who has any experience with this equipment, help is required in obtaining a horizontal trace.

S.T.C. Receiver B46.—A. Whipp, 1 Bridge Street, Lumb, Rossendale, Lancs—manual or any information.

March 1961 Issue.—J. R. Owen, 40 Kingslea Road, Withington, Manchester, 20—urgently requires this copy of "The Radio Constructor", expenses met.

'Panda Explorer' 150W Transmitter.—R. P. Neave, 24 Mayfield Road, Writtle, Chelmsford, Essex, —manual, purchase or loan.




Windscreen Wiper Programmer

by T. J. Daborn

Intended for the reader who is conversant with the simple car electrics involved, this article describes an ingenious programming unit which allows the windscreen wipers of a car to operate once every 2 to 30 seconds as desired under conditions of light rain or drizzle

THE WINDSCREEN WIPERS OF MOST MODERN cars are very efficient; they manage to clear the screen under all conditions except perhaps an exceptionally heavy downpour. Drizzle or light rain is usually cleared by one wipe, after which the wiper rubbers scrape on the dry screen. This means that the wipers must continually be switched on and off, which is not desirable in today's driving conditions when all one's attention needs to be on driving itself. A variable speed facility seemed to provide an answer for this problem, but was rejected due to the high current, high wattage components required. It was also felt that slow moving wiper blades would be more distracting than if they moved quickly.

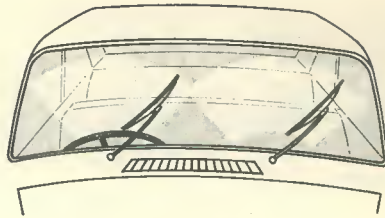

Programming Circuit

The programming circuit shown in Fig. 1 was eventually evolved and can be fitted to most cars having wipers with *self-parking facility*. The circuit is basically a Schmitt trigger, and it operates in the following manner.

On closing S_1 , TR_2 conducts heavily and TR_1 is cut off. The normally closed contacts, A1 and A2, of the relay, then open. C_1 begins to charge via R_1 and VR_1 until the base voltage of TR_1 rises above its emitter voltage. TR_1 then starts to conduct and the base and emitter voltages of TR_2 begin to fall, causing TR_1 to conduct more heavily and resulting in the circuit switching rapidly to the state when TR_1 is fully conductive and TR_2 is cut off.

Contact A1 then closes, discharging C_1 via R_2 . At the same time A2 closes across the windscreen wiper switch (see Fig. 2) causing the wipers to commence to wipe. As (due to the discharge in C_1) the base of TR_1 falls below its emitter voltage, the circuit switches rapidly back to its original state, and is ready to start the cycle again. Contact A2 opens, but the wipers carry on until they return to the self-park position, where they stop.

The self-parking facility is normally a switch in series with and powered by the motor, as shown in Fig. 2, and is open when the wipers are in the self-park position. The manual on-off switch is then put in parallel with this self-parking switch. Contact

COMPONENTS

Resistors

(All fixed resistors $\frac{1}{2}$ watt 10%)

- R_1 1.5k Ω
- R_2 100 Ω (see text)
- R_3 10k Ω
- R_4 200 Ω (see text)
- VR_1 50k Ω potentiometer, linear

Capacitor

- C_1 2,000 μ F electrolytic, 25V wkg.

Transistors

- TR_1 OC71
- TR_2 OC72

Switch

- S_1 (a), (b) d.p.s.t. switch, 5 amp rating

Relay

- A/2 See text

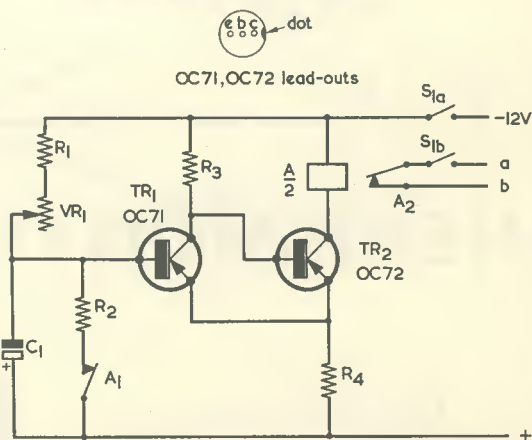


Fig. 1. The circuit of the programmer unit. Relay contacts A1 and A2 are both normally closed

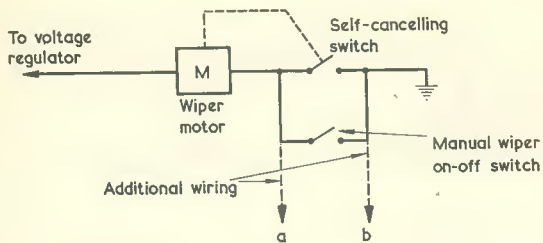


Fig. 2. How the unit is wired to the wiper motor. The "additional wiring" couples to points a and b of Fig. 1

A2 is wired via one pole of S_1 across the manual wiper switch.

When TR_2 is cut off during the cycle, contact A1 immediately begins to discharge C_1 via R_2 and quickly returns the circuit to its original state. The time that A1 and A2 stay closed must be long enough for the wiper motor to start wiping and close its self-park switch (approximately 0.5 second). This time can be varied, if necessary, by adjusting R_4 and R_2 slightly. VR_1 determines the charging rate of C_1 and hence the time between wipes. With the prototype, VR_1 offered a range of 2 to 30 seconds.

VR_1 and S_1 can be mounted side by side on a bracket or on the dashboard. Under normal rain conditions the wipers are turned on in the usual

way; in drizzle, however, the wiper on-off switch is turned off and S_1 is closed instead. VR_1 is then adjusted to keep the screen clear without the annoying scraping of the wiper rubbers.

The writer's unit was built on a small piece of tagboard and mounted with the relay in a convenient place under the dashboard.

Before making up the unit and connecting it into the windscreen wiper system, the reader should take care to check from the car-maker's handbook that the car circuit is the same as in Fig. 2. The author's car, to which the prototype is fitted, is a 1961 Triumph Herald saloon.

The relay employed by the author was a Post Office type which was to hand, this having a $2,000\Omega$ coil. Both contact sets are normally closed, and contacts A2 should be capable of switching at least 3 amps. Readers may be able to obtain a suitable relay through surplus channels.

Editor's Note

It will be noted that no protective diode is connected across the relay coil (to prevent the application of a high back-e.m.f. to TR_2 when the relay de-energises) since this was not found to be necessary with the prototype.

Suitable relays are available from L. Wilkinson (Croydon) Ltd., Longley House, Longley Road, West Croydon, Surrey, at 21s. each. When ordering please specify as: Post Office Type 3000 relay, $2,000\Omega$ coil, with one set of light-duty N/C contacts and one set of 3 amp N/C contacts, energising voltage 10 or less.



RADIO CONSTRUCTOR

SPECIAL



NEXT MONTH

Price 2/6

or 3/- by post from

Data Publications Ltd.

57 Maida Vale, London W.9.

★ 2-BAND REFLEX Rx

★ SAMPLING V.H.F.

★ THE JUNIOR RADIOGRAM

RADIO CONSTRUCTOR

THE CONVERTER DESCRIBED IN this article was designed for use with a car radio, but it can be used with any medium wave receiver having aerial coils instead of a ferrite rod aerial.

When using the converter the higher frequency end of the medium waveband of the receiver is employed for the final stages of intermediate frequency amplification, consequently any signals picked up on medium wave frequencies will interfere with the short wave signals. This difficulty does not usually occur with a car radio because of the good screening of all of the radio frequency circuitry of the receiver. On the other hand the portable type of medium wave receiver is designed to pick up signals without an external aerial. When using this type of receiver it is necessary to first tune it to some frequency where no signals are present, although it may be difficult to find a suitable point at night-time. With a car radio this difficulty does not occur and it is possible to use the car radio tuning to obtain a similar facility to that provided by a bandspread tuning control.

The circuit of the converter is shown in Fig. 1. A single transistor was used as a mixer-oscillator and the output was taken from a broadly tuned inductor, L_5 , in the collector circuit of the transistor. The converter was coupled to the receiver aerial and earth terminals via coaxial cable.

The converter was constructed on an aluminium chassis which formed part of the containing box. The power supply was taken from a small 3-volt battery housed inside the case.

Chassis Construction

The chassis and cover were made from 16 s.w.g. aluminium sheet, as shown in Fig. 2. Two pieces of sheet were used, one being $5 \times 5\frac{1}{2}$ in and the other $10\frac{1}{4} \times 5\frac{1}{8}$ in. The first piece formed the chassis and the second piece formed the cover. The cover was attached to the chassis by means of self-tapping screws passed through the holes shown in Fig. 2 (b).

The construction of the battery holder is shown in Fig. 3. To prevent short-circuits, a strip of insulating material should be interposed between the base of the battery holder and the chassis surface when the holder is secured in place.

All the major components, with the exception of the battery holder and oscillator coil (L_3 , L_4), were mounted on the vertical 2×5 in section of the chassis. See Fig. 4.



Simple Short Wave Converter

by R. L. A. Borrow, B.Sc.

This self-contained single-transistor converter operates over the range 15 to 30 Mc/s, and provides an output at medium waves. It may be used with any medium wave receiver having screened aerial coils instead of a ferrite frame, which would pick up interfering medium wave signals at night-time—although a ferrite frame receiver could possibly be used in a screened environment such as a car

The battery holder was mounted on the horizontal 3×5 in section and the oscillator coil on the end plate of the 2-gang capacitor.

The 2-gang capacitor was a $150 + 150$ pF component, and was fitted with its own trimmers, these appearing as C_1 and C_8 in Fig. 1.

The coils were wound on polystyrene $\frac{1}{4}$ in diameter formers with adjustable iron dust cores. The aerial tuning coil, L_2 , was wound with 7 turns of 28 s.w.g. enamelled wire spaced by winding in a second

wire of 28 s.w.g. which was later removed. The aerial coupling winding, L_1 , consisted of 5 turns of 28 s.w.g. enamelled wire close-wound and positioned close to the earthy end of the tuned coil.

The oscillator tuned coil, L_3 , was wound with 8 turns of 28 s.w.g. enamelled wire spaced as for L_2 . The collector winding, L_4 , has 5 turns of 28 s.w.g. enamelled wire, these being wound in the spaces between the tuned winding at the earthy end.

The coil used for the output



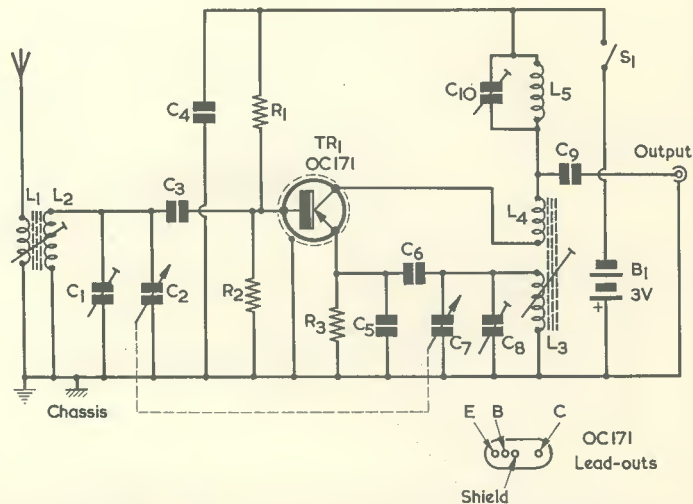


Fig. 1. The circuit of the short wave converter. L_2 is the signal frequency tuned coil, and L_3 is the oscillator tuned coil. L_5 is an air cored medium wave coil

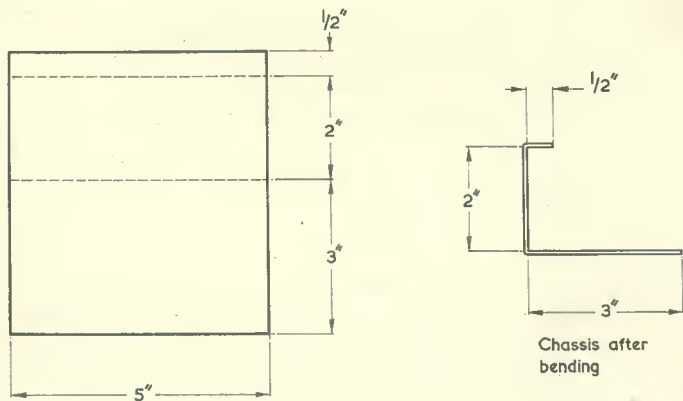

Chassis after bending

(a)

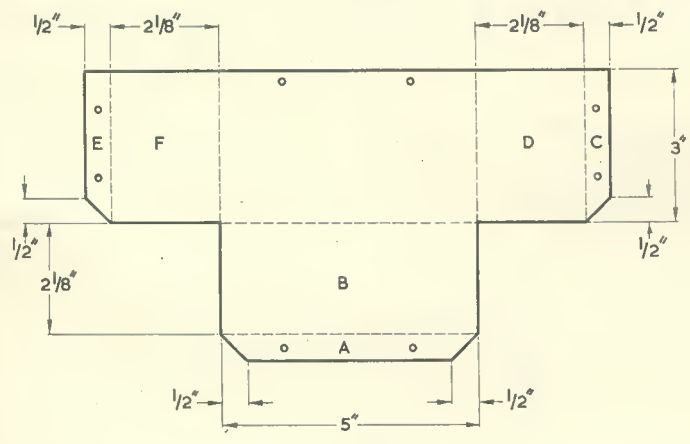

(b)

Fig. 2 (a). Details of the chassis. This is bent as shown (b). The cover. All parts are bent inwards (i.e. towards the reader) along the dashed lines. A convenient order of bending would follow the order ABCDEF. The holes are clearance for self-tapping screws


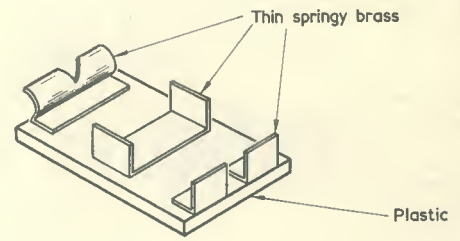


Fig. 3. The battery holder. Dimension the springy brass parts to take two U12 cells. Any convenient insulating material may be used for the base. Connections are taken from the two single contacts

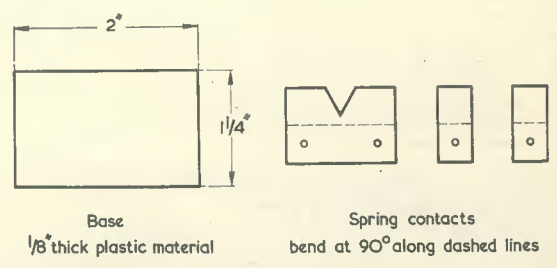

Base
1/8" thick plastic material

Spring contacts
bent at 90° along dashed lines

inductor, L_5 , was an air cored medium wave r.f. coupling coil type PHF2, with no connections made to the coupling winding.

Alignment

The converter is connected to a car radio, or a similarly suitable receiver, which is tuned to slightly higher than mid-scale on the medium wave range, and an aerial is connected to the converter input terminal. The oscillator trimmer, C_8 , is set to about mid-capacitance. A weak signal is obtained at the high frequency end of the converter range and the aerial trimmer, C_1 , adjusted for maximum response. The converter is then set to the low frequency end of the scale and the aerial coil adjusted by means of its iron dust core. Finally, the trimmer across the output coil, C_{10} , is adjusted for maximum signal. Adjustments to the oscillator coil core and trimmer may be made, if required, to improve tracking or alter the range covered.

The converter frequency range is about 15 to 30 Mc/s but this can of course be altered to suit the user's requirements by changing the number of turns on the aerial and oscillator coils.

The converter as described has been found to bring in a very large number of stations, particularly from across the Atlantic.

Due to lack of selectivity before the mixer it may sometimes be found that transmissions from local high power v.h.f. transmitters are heard. This is due to their combining with harmonics of the oscillator. To overcome this difficulty, if it occurs, it will probably be necessary to introduce an extra circuit tuned to signal frequency between the aerial and the converter, this possibly incorporating an r.f. amplifier stage. The writer hopes to include these refinements in a more sophisticated design of converter.

Editor's Note

The 150 + 150pF 2-gang capacitor with trimmers specified for C_2 , C_7 may not be readily available through home-constructor channels, but a suitable alternative would be the 176 + 176pF capacitor type "00" with screen made by Jackson Bros. Small 20 or 30pf trimmers can be added to this capacitor. If desired, a simple epicyclic slow-motion drive, or similar, may be fitted to the front panel for tuning. Any medium wave single tuned coil (or medium wave r.f. coupling coil with the coupling

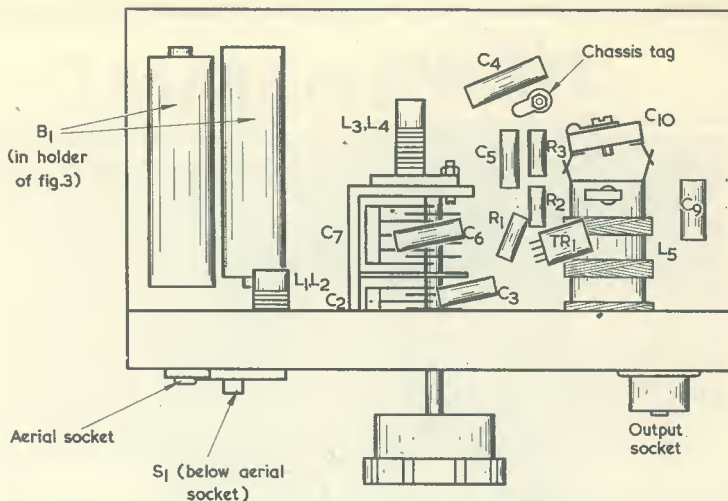


Fig. 4. Component layout used in the prototype. The $\frac{1}{2}$ in flange of the chassis is nearest the reader and partly obscures the components which are secured to the 2 x 5 in front panel. The tags of C_2 , C_7 and L_5 provide anchor points for most of the resistors and capacitors. The emitter of TR_1 is anchored at the junction of R_3 , C_5 and C_6 , and the base is anchored at the junction of R_1 , R_2 and C_3 . If components having fairly stiff lead-outs are employed, these anchor points are quite stable

winding unused) intended for valve receivers may be employed in the L_5 position instead of the PHF2 coil specified. Avoid using a medium wave aerial coupling coil, as the unused aerial coupling winding may give undesirable absorption effects.

Good tracking could be achieved with either the oscillator frequency above or below the signal frequency, but it will probably be found better here to have the oscillator frequency below. Bad tracking will, of course, occur if the oscillator frequency is above the signal frequency at one end of the band and below it at the other.

If it is found that C_{10} does not provide sufficient capacitance for the medium wave frequency required, a fixed silver mica capacitor of around 100pF may be connected across it.

- C_1 , C_8 trimmers (fitted to C_2 , C_7)
- C_2 , C_7 2-gang 150+150pF (see text)
- C_3 47pF silver mica
- C_4 0.01 μ F paper or plastic foil
- C_5 100pF silver mica
- C_6 47pF silver mica
- C_9 100pF silver mica
- C_{10} 140pF trimmer

Coils

- $L_{1,2}$ See text
- $L_{3,4}$ See text
- L_5 R.F. coupling coil type PHF2 (Wearite)

Transistor

- TR_1 OC171

Switch

- S_1 Miniature on-off slide switch

Battery

- B_1 Two U12 cells (Ever Ready) in series


Miscellaneous

- 1 aerial input socket
- 1 coaxial socket
- 2 coil formers $\frac{7}{8}$ x $\frac{1}{4}$ in dia. Cat. No. CR4 (Home Radio)
- 2 iron dust cores, Cat. No. CR5 (Home Radio)

COMPONENTS

Resistors

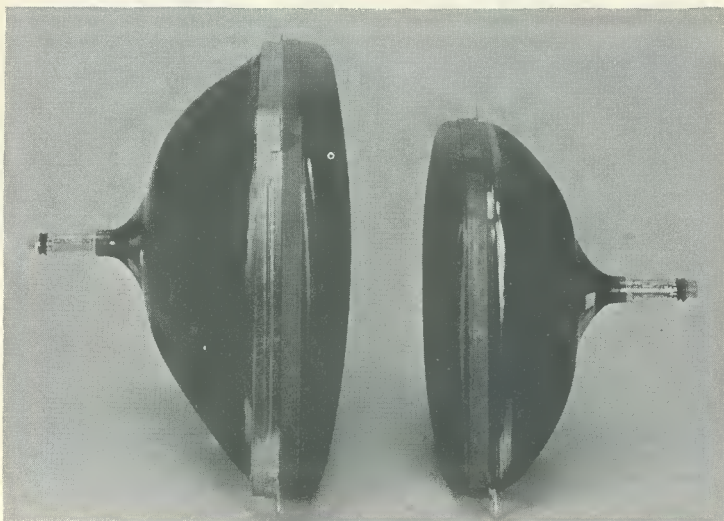- (All $\frac{1}{2}$ watt 10%)
- R_1 39k Ω
- R_2 22k Ω
- R_3 5.6k Ω



New Mazda CRTs for Push-Through Presentation

The use of cathode ray tubes which do not require separate implosion protection panels is now well established in the field of domestic television. MAZDA have played a prominent part in the development of this new trend in styling and have introduced to the trade, successively, Twin Panel, Rimguard I, Rimband and Rimguard II implosion protected tubes.

MAZDA now introduce the Rimguard III system of implosion protection which retains the advantage of light weight but offers the additional attraction of being able to be used in "push-through" presentations.

In both the 19in and 23in sizes, illustrated above, the Rimguard III reinforcement consists of a metal shell fitting closely to the bulb in the rim region and bonded to the glass with a specially selected resin. Over this shell a band of steel strip is applied and tightened to an accurately controlled tension. The important feature in which Rimguard III reinforcement differs from Rimguard I and II is that the shell does not extend so far forwards towards the face, so permitting "push-through" presentation.

The metal shell is in the form of two halves which meet with an overlap in the centres of the vertical sides.

In the case of the 19in size this shell is close-fitting to the bulb to which it is bonded by a special resin.

On the 23in tube this shell fits tightly at its forward edge but is separated from the glass at its rear edge by a gap of a few millimetres. This gap is filled with a suitable resin. Strengthening ribs are formed in the shell, parallel and close to its rear edges.

In both 19in and 23in tubes an accurately tensioned steel band is applied over the shell which carries brackets for mounting the tube.

This reinforcement results in an extremely strong tube which will not fail in a violent manner when subjected to such thermal or mechanical shocks as are likely to be encountered even in extreme circumstances.

ALCONBURY

Radiowise, Alconbury is in the news on two counts.

Firstly, it was the venue, on 18th June, of the Amateur Radio Mobile Society's International Mobile Rally. This event is claimed by the organisers to have been the biggest and most successful amateur radio event ever held.

Although estimates as to the number of people attending varied from just under 4,000 to nearly 5,000, based on the average number of passengers per car, the police say they checked in a thousand vehicles, and apparently the double line of parked cars stretched for a mile, which meant a long walk for late-comers. So if you intend going to next year's rally—to save your legs—get there early!


Also at Alconbury is the USAFE/UK Redistribution and Marketing Centre. Here are held, from time to time, auction sales of electrical and radio equipment of all kinds.

The sales are not conducted like an ordinary auction. The bidder fills in a bid form stating the price he is prepared to pay for the item listed in the catalogue, and enclosing a deposit of 20% of the bid value. These are known as spot bids.

There are also sealed bids; a similar form is completed and placed by the bidder not later than a fixed time before the sale commences.

Both types of bid may be sent by post.

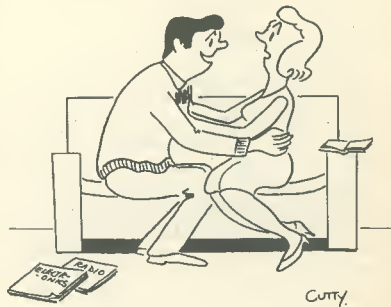If you would like further information write to Mr. David Peller, Chief Contracting Officer, Marketing Branch, USAFE/UK Redistribution & Marketing Centre, R.A.F. Alconbury, Huntingdon.



"Proper little resistor, aren't you"

COMMENT

Society's Progress

It is very pleasant to record the progress of The Institution of Electrical and Electronics Technician Engineers.

In the report of the Council for the year ended 31st March, 1967 it is shown that the Institution made further substantial progress; lecture programmes; regional development work expanded; the designatory initials denoting corporate membership more widely used; establishments of further education included the IEETE qualifications in their lists of nationally-recognised awards. This latter point is an indication of the growing standing of the society as a professional body.

Incorporated in February 1965 the membership at the end of March stood at 7,800, an increase over the year of 1,300 members.

The report quotes from the speech of Sir Harold Bishop at the first Annual Dinner referring to those technician engineers, holding senior positions, who possess no academic qualifications. He said that the IEETE had such engineers especially in mind and he pointed out that the Institution's Associate Grade had been designed particularly to meet their needs.

Another interesting item culled from the report mentioned a one-day conference, organised in collaboration with the National Council for Quality and Reliability, on "Quality and Reliability and the Technician Engineer". The conference, held at Queen Mary College, University of London, in April, was staged not only as the Institution's contribution to Quality and Reliability Year but to increase awareness of the technician engineer regarding factors contributing to the reliability of electrical and electronic equipment.

Quote

Pilfering at a large Birmingham jewellers has been cut by 70% since the installation of a television operated security system. But while it has been successful in scaring away the light-fingered gentry, the television is proving to be almost too popular with customers. Some leave their children in the store to amuse themselves spotting each other on the screens, and a group of regular viewers have put in a request for colour.

From *The Times Business News*.

New Method of Checking Small Printed Circuits and Transistors


A new method of checking small printed circuits and transistors is being used by major aircraft and electronics companies, following a joint operation by C & D Scientific Instruments Limited of Boxmoor, Herts, and Plannair Limited, the air thermal specialists.

The result of this joint exercise is a projection microscope, illustrated below, which shows an enlarged image of the components on a hooded screen, to enable careful inspection and hair line precision adjustments to be made accurately and without strain on the operator.


The microscope has a ten times magnification with light provided by a high intensity quartz iodine lamp. Plannair's aid was sought to reduce the heat produced by the 150 watt lamp working in a small enclosed space. It was essential that the cooling fan, although running at 2,600 r.p.m., should be vibration-free, and Mr. E. Chandler, one of the directors of Scientific Instruments, said: "the fan was easy to fit and very good indeed because it works completely without vibration. We are so satisfied with the performance of this unit and with the large range of cooling equipment Plannair has, that we are shortly going to start making a smaller version of the projection microscope with a smaller fan from the Plannair range. Already hundreds of this smaller version have been ordered by large electronic companies".

The present projection microscope is already being used by one major aircraft company for the inspection of guided weapons components; similar equipment is being used to inspect circuits and transistors for international firms in the electronics industry.

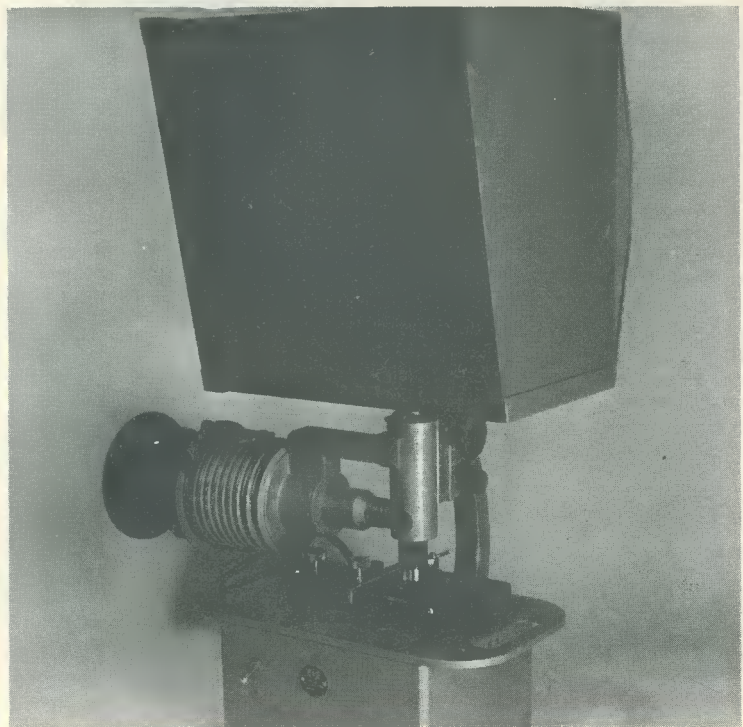This is one of the many ways in which Plannair is helping highly specialised companies at the heart of the changing industrial scene to overcome difficult design problems. The company has over a thousand fans and blowers of all shapes and sizes and supplies a wide range of industry from avionics to computers.



STEREO DECODER UNIT

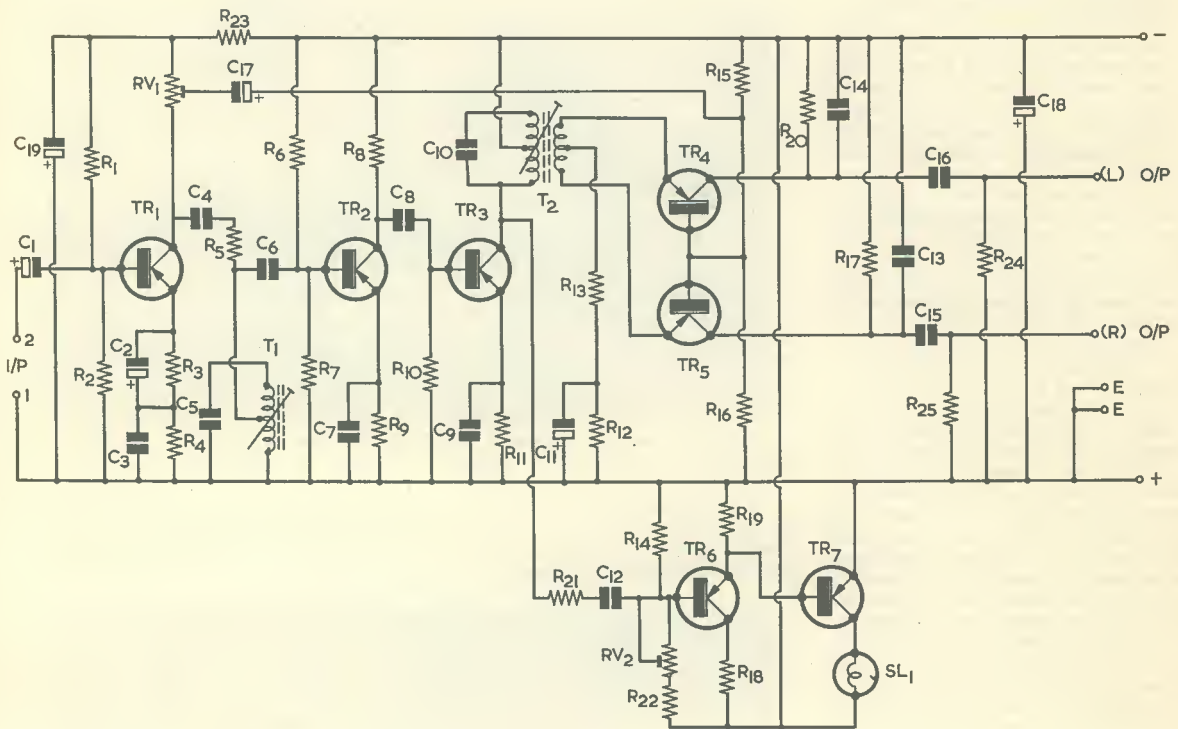

Available from Henry's Radio, Ltd. is a 7-transistor stereo decoder in kit form, this being intended for use with any valve or transistor f.m. tuner having a minimum bandwidth of 300 kc/s. The decoder offers compatible operation and, during mono broadcasts, allows the single signal then transmitted to pass straight through to the subsequent left and right channel amplifiers. The decoder may be operated from a 12 or 9 volt supply. When stereo transmissions are in progress current consumption is of the order of 50mA whilst, during mono transmissions, consumption is 10mA or less.

A special feature of the circuit is the provision of an indicator lamp which lights up when stereo transmissions are in progress. The assembled kit is simple to set up and align, and its circuit appears in the accompanying diagram.

Circuit Operation

Readers interested in stereophonic broadcast reproduction will recall that B.B.C. stereo transmissions use the Zenith-G.E. multiplex system. At the transmitter, the left hand channel (A) and the right hand channel (B) are summed to give an A+B signal which frequency modu-

lates the transmitter carrier in the normal manner. Thus, a mono receiver reproduces the A+B signal, this being sufficiently close to a normal single-source signal to provide satisfactory mono reception. At the same time, an A-B signal is also formed, this being amplitude modulated on a suppressed 38 kc/s subcarrier, resulting in the production of a range of sidebands from about 23 to 53 kc/s. These are above the frequencies to which a mono receiver can respond. Also, when the A and B signals are equal (whereupon A-B=0) the sidebands drop out. In order that the 38 kc/s subcarrier may be reclaimed at the receiver a 19 kc/s pilot tone is transmitted, this being doubled to the required 38 kc/s in the decoder. The 19 kc/s pilot tone also has no effect with a mono receiver. For decoding to take place, the decoder has to mix the two signals so that the following results are obtained:

$$\begin{aligned}(A+B) + (A-B) &= 2A \\ (A+B) - (A-B) &= 2B.\end{aligned}$$

Thus, with suitable mixing, the original left and right hand channels may be recovered from the transmitted A+B and A-B signals.

In the Henry's Radio decoder, the input from the

discriminator of an f.m. tuner is applied to capacitor C_1 . This input consists of the A+B modulation, plus the 19 kc/s pilot tone and the modulation on the suppressed 38 kc/s subcarrier. Transistor TR_1 amplifies all signals and enables an adjustable multiplex signal to be available from RV_1 . Transformer T_1 is resonant at 19 kc/s and causes the 19 kc/s pilot tone to be applied to TR_2 . TR_2 amplifies the 19 kc/s tone and feeds it to TR_3 , which operates without a base bias resistor from the negative supply rail. The consequent distortion in TR_3 allows doubling to take place and the 38 kc/s signal at its collector appears across the primary of T_2 and C_{10} , these forming a tuned circuit resonant at that frequency.

The centre-tapped secondary of T_2 feeds the 38 kc/s signal in anti-phase to the emitters of TR_4 and TR_5 , whilst the multiplex signal from RV_1 is fed to the bases in phase. The requisite mixing then takes place, enabling the left and right hand outputs to be obtained, as shown. The two points marked "E" in the circuit diagram are the earthy terminals for the left and right hand outputs respectively.

In the absence of a stereo signal no 19 kc/s pilot tone is transmitted, and no 38 kc/s signal appears at TR_3

collector. On the other hand, a relatively high amplitude 38 kc/s signal is given at TR_3 collector when a stereo signal is being transmitted. This 38 kc/s signal is passed through limiter resistor R_{21} to the base of TR_6 . An amplified signal is next applied to the base of TR_7 , which passes sufficient current to cause pilot lamp SL_1 to be illuminated. The sensitivity of the pilot lamp circuit is controlled by RV_2 , since too high a sensitivity may cause the lamp to occasionally flash when tuning across the v.h.f. band.

One method of alignment of the assembled decoder consists of adjusting the cores of T_1 and T_2 for maximum brightness in the indicator lamp whilst a stereo broadcast is in progress. Final adjustments are made with RV_2 adjusted for low lamp sensitivity. RV_2 is then set for the desired operational sensitivity. The output of the decoder is approximately 1 volt per channel which can be reduced, as necessary, by RV_1 .

The design has been developed by S. Neagle, and the complete kit is available from Henry's Radio Ltd., 303 Edgware Road, London, W.2., at £5-19-6d, plus 2s postage and packing.



An "Integrated" Crystal Oscillator

by James M. Bryant, B.Sc.

Micro-miniaturisation for the home-constructor! By employing sub-miniature components it is possible to fit a complete oscillator circuit inside the case of an FT241A crystal, thereby obtaining an "integrated" 2-pin crystal oscillator module.

An instrument soldering iron and a steady hand are necessary

FT241A QUARTZ CRYSTALS ARE PLENTIFUL ON the surplus market and cost only a few shillings each. They cover the range 22-36 Mc/s on the 54th harmonic, so their fundamental frequencies lie between some 400 to 650 kc/s. Their lower

harmonics fall within several of the amateur bands and these crystals also find uses in i.f. filters, crystal markers, clocks and simple frequency meters. In these days of micro-miniaturisation, a drawback of most quartz crystals is their comparatively large size. The present article describes an oscillator circuit which may be built into the crystal case to save space.

COMPONENTS

Resistors

(Sub-miniature $1/8$ or $1/10$ watt, excluding R_1 if fitted externally)

R_1 3.3k Ω
 R_2 470k Ω

Capacitors

(Both sub-miniature ceramic or polystyrene)

C_1 200 to 1,000pF (see text)
 C_2 100pF

Transistor

TR_1 2N2926, 2N3904, 2N3708 or BC118 (see text)

Crystal

Crystal type FT241A

The Circuit

The circuit of the oscillator, shown in Fig. 1,


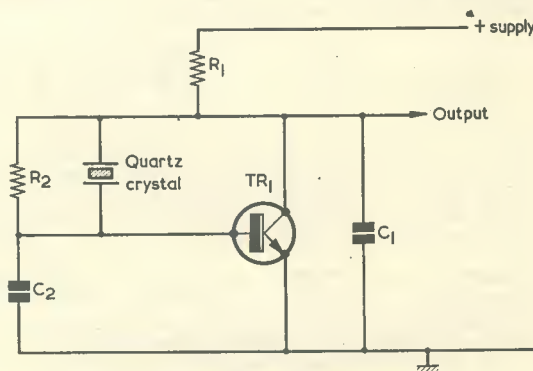


Fig. 1. The circuit of the crystal oscillator

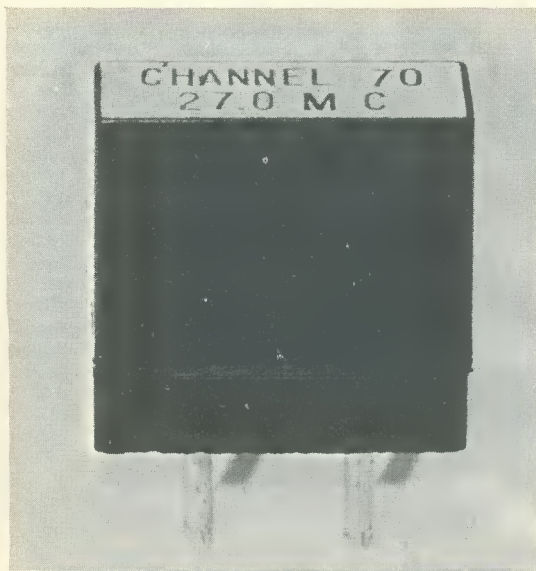

The crystal case. This contains the complete oscillator of Fig. 1 less, in this instance, resistor R_1

contains only six components including the crystal. If the collector load resistor, R_1 , is left outside the crystal case only two connections need be made to the remainder of the circuit and the original crystal pins may be used. It is perfectly possible to fit R_1 into the crystal case but an extra connection must then somehow be made.

The transistor is a plastic encapsulated silicon planar n.p.n. type. A similar p.n.p. type could be used if the power supply were reversed. In the original oscillator a Motorola transistor type 2N3904 was used but the General Electric type 2N2926 (widely advertised at about five shillings), the Texas Instruments type 2N3708 and the S.G.S.-Fairchild BC118 all work in the circuit.* Lead-out connections to these various transistors are shown in Fig. 2.

*The 2N2926 is available from L.S.T. Components, 23 New Road, Brentwood, Essex. The FT241A crystal used for the prototype oscillator was obtained from Henry's Radio Ltd.—Editor.

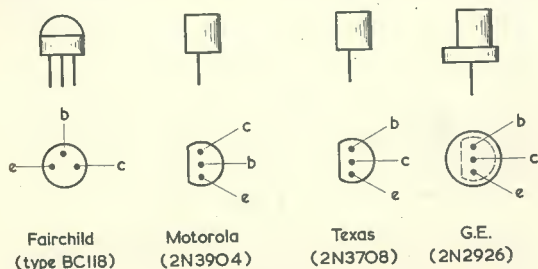


Fig. 2. Illustrating transistor lead-out connections. Any of the transistors shown here may be employed in the oscillator


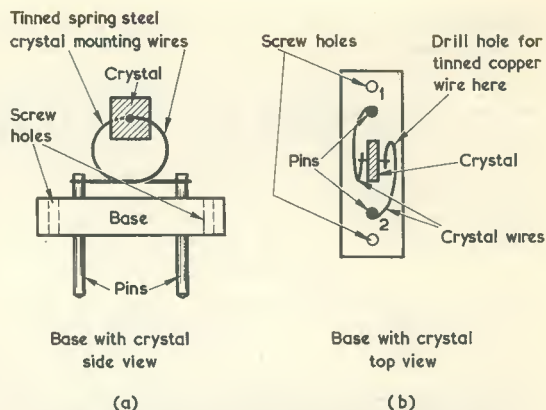


Fig. 3 (a). When the crystal cover is removed, the crystal plate may be seen supported on its two mounting wires
(b). The additional tinned copper anchor wire is fitted as illustrated here

The resistors are 1/8 or 1/10 watt hearing aid types and the capacitors sub-miniature polystyrene or ceramic components. The capacitance of C_1 affects the shape of the output waveform and stops oscillation altogether if it becomes too large. A low capacitance gives an irregular waveform, rich in harmonics, which may be used as a marker, or a drive to a frequency multiplier. A higher one gives a waveform of smaller amplitude, but one more nearly approaching a sine wave. If desired, a temporary circuit with components outside the crystal case can be initially set up to find the value of C_1 which best meets the requirements of the constructor. The components may then be fitted into the crystal case.

The power supply may be any value between 3 and 20 volts at not more than 5mA.

If other than FT241A crystals are used, the capacitances should be increased or decreased as the frequency of oscillation decreases or increases (e.g. if a crystal giving 100 kc/s were used, C_1 would be 1,000 to 5,000pF, and C_2 500pF; for 1 Mc/s they would be 100 to 500pF and 50pF respectively). The whole circuit may be used in a crystal oven up to 100°C without damage if the supply is less than 12 volts.

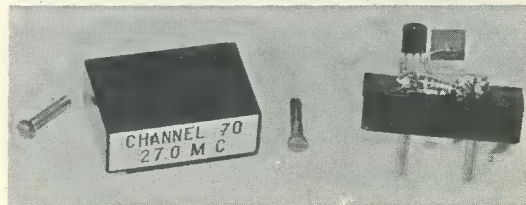

The crystal oscillator disassembled. The two screws are removed, enabling the base, with its added components, to be withdrawn from the case

Construction


If the two screws at the base of the FT241A case are removed, the assembly may be dismantled into three parts: the case, the base with pins and crystal, and a rubber washer between them. The base and crystal are illustrated in Fig. 3 (a). Care should be taken at all times not to handle or chip the crystal, which is fragile.

A small hole should be drilled in the base as shown in Fig. 3 (b) and a piece of tinned copper wire fixed into it, this touching the adjacent crystal wire. The tinned copper wire is used as an anchor for the crystal wire, and the two wires are soldered together quickly, using a hot iron. After this, the rest of the crystal wire from this junction to pin 2 is removed. (The pins are arbitrarily numbered 1 and 2 in Fig. 3 (b) for convenience of explanation.) Capacitor C_1 should then be soldered between pins 1 and 2, R_2 between pin 1 and the piece of tinned copper wire just introduced, and C_2 between pin 2 and the tinned copper wire. The leads should be kept as short as possible and the components as near to the centre of the base as possible. The leads should be sleeved if necessary.

Resistor R_1 should be soldered to pin 1 if it is desired to fit it in the case and the positive lead brought out past the rubber washer or through a hole drilled in the case or the base.

Finally, cut the transistor base and collector leads to $\frac{1}{16}$ in and solder thin flexible insulated leads to them. Cut the emitter lead to $\frac{3}{16}$ in and solder the transistor by it to pin 2 so that the transistor is directly over pin 2. Now solder the collector and base leads to pin 1 and the tinned copper wire respectively.

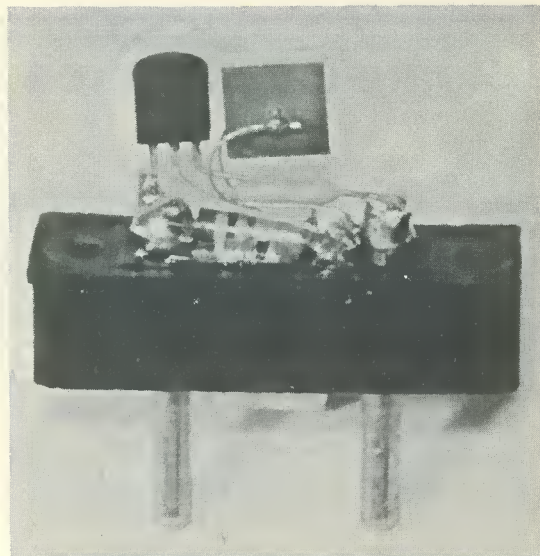A red spot is painted near pin 1 (which corresponds to the output terminal in Fig. 1) to identify it, and the case is reassembled. Take care that neither the circuit nor the crystal fouls the case during assembly.



Another view of the prototype oscillator. The crystal is the central square plate, with the transistor to its left, above pin 2. C_1 , R_2 and C_2 are beneath the crystal plate and transistor. Component dimensions may be adjudged from the fact that the two pins have $\frac{1}{2}$ in spacing

Testing and Use

If power is now applied to the oscillator an output may be detected at pin 1 by an oscilloscope, wavemeter, or a suitable radio receiver.

When the oscillator is in use, the output may be taken from pin 1 by a capacitor. If the input impedance of the stage being driven is low, the coupling capacitor should not be too large.

New Trimmer Potentiometer

A low-cost trimmer potentiometer just developed by Potentiometer Division, Standard Telephones and Cables Limited, the Type T10, has a body volume of less than half a cubic inch (0.417 cu. in.) and yet has a power rating of 3W—three times that of conventional units of similar size.

Intended as a more efficient replacement of the now obsolete W2 and W3 trimmers, the T10 is a precision device of a completely non-hygroscopic construction designed to provide accurate dependable settings in control circuit applications employing wide-tolerance components.

Both body and shaft are moulded in "Delrin" a highly stable non-hygroscopic plastic which has excellent high-temperature characteristics.

Another construction feature of this new trimmer is that, unlike conventional trimmers which are wound on a composition fibre card, the T10 is wound on a rectangular insulated copper mandrel which provides good resolution and is also non-hygroscopic.

Suitable for printed circuit mounting, the T10 is available in nine values from 100 ohms to 50k ohms.

Home-Constructed Radio Alarm

by A. G. Blewett

How to modify a domestic alarm clock so that it switches on your transistor radio in the morning

THE RADIO ALARM TO BE DESCRIBED CAN UTILISE almost any make of alarm clock and transistor radio, and it provides a highly effective means of being woken up in the morning. A very simple

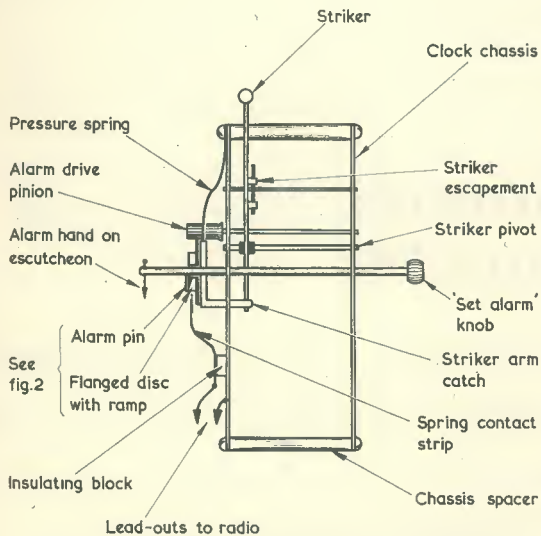


Fig. 1. The basic mechanism of an alarm clock. Also shown is the contact strip introduced by the modification

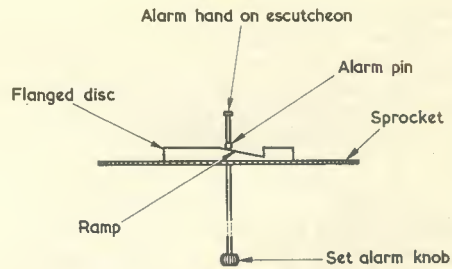


Fig. 2. Detail illustrating the disc and sprocket assembly

modification to each item is required, and both the alarm clock and the radio can be used normally and separately, as before, after the modifications.

The completed unit has been in continual use by the author (who would sleep through an air raid) for over a year, and has never let him down once.

Alarm Clock Mechanism

It is first necessary to understand how the alarm clock rings at the appropriate time. Fig. 1 gives details of a typical alarm mechanism, and it will be seen that the heart of this comprises an axle, which has the "Set Alarm" knob at one end, and the alarm hand on the clock escutcheon at the other end. The axle also carries an alarm pin, on which a flanged disc bears under the influence of a pressure spring attached to the chassis. The flanged disc is free to rotate on the axle, and is driven round by a pinion in train with the main clock drive. Fixed to the pressure spring is a striker arm catch which prevents the bell striker from operating until the catch is withdrawn.

As the main clock drive rotates it carries with it the flanged disc, which has a ramp, as shown in Fig. 2. When the alarm pin reaches the vertical part of the ramp, the whole disc and sprocket assembly moves forward under the influence of the pressure spring, whereupon the striker arm catch is withdrawn and the alarm rings. The time at which the clock rings is determined by the relative position of the ramp and the alarm pin, the latter being preset by the "Set Alarm" knob at the back of the clock.

This basic method of operation should be found in practically all spring-wound alarm clocks. The reader should first examine the particular clock mechanism he intends to modify in order to confirm that this is so and, also, to identify the clock part which moves forwards when the striker mechanism is set off. The modification consists of adding a contact strip which will connect to the disc and sprocket assembly when the latter moves forward, thereby allowing a circuit to be completed

via the chassis of the clock. The added contact strip is shown in Fig. 1. The circuit completed via the contact strip and the clock chassis switches on the transistor radio.

Modifying The Clock

The main modification required to the clock is to fit the contact strip, insulated from the chassis, such that it makes reliable contact with part of the disc and sprocket assembly when this moves forward. In the prototype the strip was made from thin shim brass $\frac{1}{8}$ in wide, and was secured to the insulator (which can be made from ebonite or Perspex, etc.) with a small self-tapping screw. The insulator was then fixed to the clock chassis with Araldite. A hole is drilled in the clock case at a convenient place to take the lead-out wires, which in the prototype were made from miniature twin flex from an old hearing aid earpiece, although any small flexible twin wire would do. One of the flex leads connects to the added contact, and the other to the clock chassis at any convenient point. The flex is terminated with a miniature jack plug which fits into a socket on the radio.

Modifying The Radio

Most transistor radios have an earphone socket. In the author's prototype, this socket was disconnected and used as the power switching socket. See Fig. 3. If, however, it is desired to retain the earphone facility, a separate miniature jack socket, with switching contact, will have to be fitted where space permits in the receiver. Normally, the receiver operates with its internal speaker connected via the closed contacts of the earphone socket, but when the earphone plug is introduced the internal speaker circuit is broken and the output is fed to the earphone. The dotted resistor, R in the diagram, is used in some receivers to protect the output circuit from damage with high resistance loads, and where fitted should be retained *in situ* after the modification.

Alternative earphone circuits will be found in some radios and the reader should check that receiver performance is not altered when disconnecting the existing wires to the earphone socket. If the existing socket does not have a switching contact, it will have to be replaced with one which has.

With the modification incorporated, one of the leads from the internal battery to the radio chassis is routed via the closed contacts of the socket, as shown in Fig. 3(c). When the plug from the alarm clock is inserted these contacts open, whereupon the battery connection is completed, at the preset time, by the contacts in the clock.

In the evening, the author pretunes his radio to the Light Programme at the required volume with the plug out, plugs in the clock and—presto!—an unflinching early call results.

Other Applications

The alarm switch can also be used for switching on any other low-current battery-operated equipment requiring a time delay, or operation at any preset

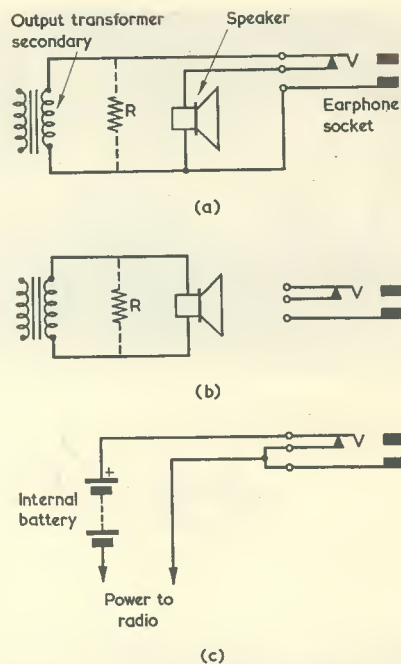


Fig. 3 (a). The original earphone socket circuit in the author's receiver
 (b). The connections to the socket were removed, and the speaker wired directly to the output transformer secondary
 (c). One lead of the internal battery of the radio was then routed via the contacts of the earphone circuit, as shown here


time. The author's clock switches on and stays on for approximately 45 minutes. The time during which the clock contacts remain closed depends on the gradient of the ramp, and this will vary with different clocks.

It is most important to note that the chassis of the clock is common to one side of the alarm switch, and that the switch should not on any account be used to control high voltages or to switch mains-operated equipment on and off. The alarm switch should only be employed to control low voltage battery circuits such as are encountered in battery-operated transistor radios and similar equipment.

The exposed metalwork (including aeri-als) on the cases of some transistor radios may be at a different potential to the battery lead switched by the clock. The clock should not therefore be allowed to touch such metalwork.

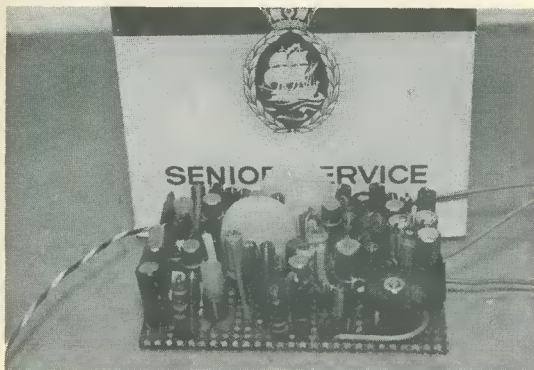Finally, it should be mentioned that a few transistor radios have two internal batteries in series, their junction also connecting into the receiver circuit. These radios require a double-pole on-off switch, and the single-pole switching circuit offered by the modified alarm clock could not then be used.





FOLLOWING LAST MONTH'S DESCRIPTION OF THE SCT/RR1 super-regenerative receiver, we deal now with the alternative superhet receiver which has been specially designed for use in conjunction with the SCT/T1 single channel "tone" transmitter. This new receiver uses a total of eight transistors and embodies a number of unique features which give it a really superlative performance. Sensitivity is better than $2\mu\text{V}$, giving a ground-to-ground control range of over 1,000 yards, and a ground-to-air range of well over 1 mile. Also, the unit is crystal controlled and features a tuned filter relay-less output stage, this combination giving near-perfect interference rejection and making it possible to operate as many as 50 independent models at the same time.

A further point is that the normal i.f. transformers have been eliminated from the circuit and replaced by transfilters, so that no i.f. lining-up procedure is required. The receiver operates from a 9 volt supply, and draws a no-signal current of

approximately 5mA; the complete unit measures $2\frac{3}{4} \times 1\frac{3}{8} \times \frac{7}{8}$ in. A kit of parts is available from Teleradio Electronics.

Basic Design Considerations

Most readers will no doubt be familiar with the basic block diagram for a normal superhet receiver, as shown in Fig. 1 (a). Here, radio signals are picked up by the antenna and the required band of frequencies is then selected by the r.f. stage and passed on to the mixer, where it beats with a signal provided by the local oscillator to produce an i.f. (intermediate frequency) signal at the mixer output. This i.f. signal is equal to the difference between the r.f. and the local oscillator frequencies. Thus, if the r.f. signal being received is 27,000 kc/s, and the local oscillator frequency is 26,535 kc/s, the difference frequency, or i.f. will be 465 kc/s. This i.f. signal, which retains the same modulation as the original r.f. signal, is next subjected to several stages of i.f. amplification. The

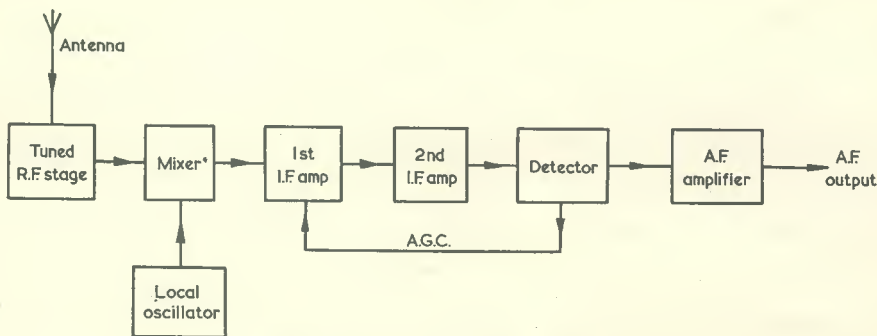


Fig. 1. Block diagram for a conventional superhet

The SCT/RR1 Receiver

In last month's issue the SCT/RR1 super-regenerative receiver was fully described. We now introduce a superhet receiver which may also be employed as a "tone" transmitter. Despite the fact that this receiver offers a ground-to-air range of well over a mile, the use of transfilters obviates the need for

Basic Radio Construction
by [unclear]

RS1 Superhet Receiver



Cover Feature

regenerative receiver for model control
 a more sensitive and sophisticated
 employed with the SCT/T1 single channel
 this receiver measures only $2\frac{3}{4} \times 1\frac{5}{8} \times \frac{7}{8}$ in,
 a mile. An attractive feature is that the
 necessity for i.f. alignment



amplified i.f. signal is then demodulated in the detector stage and the resulting audio signal is passed on to the a.f. (audio frequency) amplifier and finally on to the output of the circuit. Part of the signal from the detector is also fed back to the first i.f. amplifier in the form of an automatic gain control (a.g.c.) signal. This compensates for different strengths of r.f. signal and prevents overloading of the amplifier stages on receipt of powerful signals.

The basic *principles* outlined above apply to all superhet circuits irrespective of the actual application in which the circuit may be used, but considerable differences in design *details* may be encountered in practical circuits, these depending on the precise performance that is required. In an ordinary broadcast receiver, for example, the tuning

of the r.f. and local oscillator circuits must be variable so that different stations may be selected, while in a radio control circuit the tuning must be fixed and exceptionally stable. Again, an ordinary broadcast receiver does not require a particularly high degree of sensitivity, and a figure of $200\mu\text{V}$ is usually regarded as acceptable in pocket superhets. In radio control work, on the other hand, far greater sensitivity is required, and a figure of at least $10\mu\text{V}$ is regarded as essential. Finally, a broadcast receiver is required to faithfully reproduce, without distortion, the complex audio signals that are used to modulate the carrier signal at the transmitter, but in radio control equipment the same distortionless performance is not *necessarily* required.

The considerations just discussed have to be


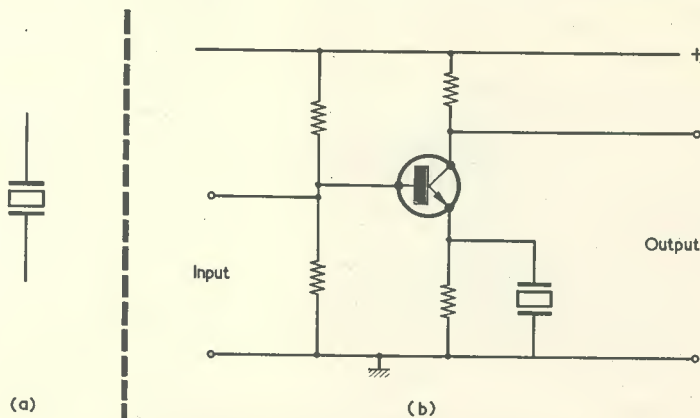


Fig. 2 (a). The symbol for a "TF" transfilter
 (b). When a "TF" transfilter replaces the emitter bias capacitor, the amplifier becomes frequency selective

Control (7)
 F. L. Thurston

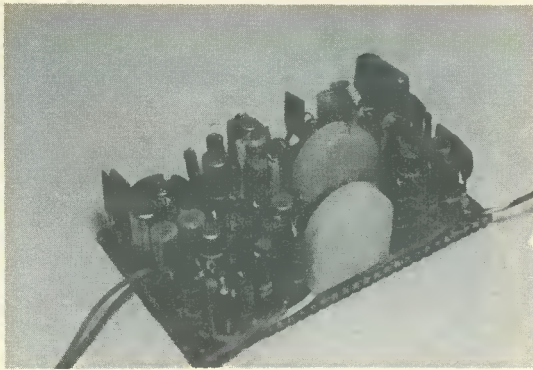

The extremely compact layout of the complete 8-transistor receiver may be judged from this illustration, which shows all the components mounted on the $2\frac{3}{4} \times 1\frac{1}{8}$ in Veroboard panel

taken into account before starting the design of any new piece of equipment, since such equipment will have its own unique performance requirements. The design considerations taken into account when developing the SCT/RS1, and the solutions accepted, were as follows:

(a). Fixed tuning, with very high stability, is essential. This can be achieved by the use of a pre-set r.f. filter and a crystal controlled local oscillator.

(b). For maximum possible control range a very high degree of receiver sensitivity is required, which means that the circuit must give a very high overall gain. Extra gain can be achieved in a number of ways, e.g. by including an extra stage of r.f. amplification, an extra stage of i.f. amplification, an extra stage of a.f. amplification, or by a combination of these methods. In the SCT/RS1 the extra gain is achieved in the i.f. and a.f. stages.

(c). Very good rejection of interference from electric motors, etc., is required. Interference is particularly troublesome in high gain circuits, so that the requirements of (b) and (c) do in fact conflict. With the SCT/RS1, however, this problem is overcome by incorporating a tone filter in the a.f. stages so that only the correct tone modulation signal can reach the output circuitry, and interference has no effect on the output of the receiver.

(d). So far as distortion is concerned, a single-channel tone receiver is required simply to reproduce the single modulation tone frequency that is applied at the transmitter, and it is therefore of no importance if this signal happens to be distorted. In the SCT/RS1 distortion is deliberately introduced in the a.f. stages, and contributes to the high performance that is obtained from the circuit. In multi-channel tone work, of course, complex modulation signals may have to be reproduced, and in such cases it may be necessary to keep distortion to a minimum.

(e). Since the circuit is intended for assembly by the amateur, it is important that it should be possible to complete the unit without difficult lining-up

procedures, and in the SCT/RS1 this is achieved by replacing the conventional i.f. transformers with ceramic transfilters, which require no adjustment.

Transfilters

Transfilters are piezoelectric ceramic devices which give a performance that is not unlike that of a conventional crystal, and they can therefore be used to simulate normal L-C tuned circuits. Two basic types of transfilter are available.

The first of these basic types consists of a ceramic disc with a silvered electrode on each of its two faces. When an a.c. signal is connected across these electrodes the disc vibrates mechanically; or, alternatively, if the disc is mechanically made to vibrate an a.c. signal is generated across the electrodes. The ceramic disc has, like a normal crystal, a fundamental resonant frequency at which it is particularly active, and this frequency will depend on the dimensions of the disc and the mode in which it is used; the operating frequency can be established during the manufacturing process with considerable accuracy. Transfilters are designed to resonate in the radial mode, since the overtones of operation are not then harmonically related, the first overtone being 2.6 times the fundamental resonant frequency and the second overtone being 3.9 times the fundamental.

These two-electrode transfilters, which are manufactured by the Brush Clevite Company, are given the symbol shown in Fig. 2 (a). They appear in the Brush Clevite TF series, and are intended to operate on their fundamental frequency. At its fundamental frequency, a TF transfilter presents an impedance of about 15Ω , but at other frequencies its impedance is relatively high. In consequence, a TF transfilter can be used to replace the emitter bypass capacitor of a common emitter amplifier, as shown in Fig. 2 (b), thereby making the circuit sharply frequency selective, since at the resonant frequency the emitter is effectively bypassed via the low impedance of the TF transfilter and the stage gain is high, while at other frequencies the transfilter exhibits a high impedance and the stage gain is low. The TF transfilter used in the SCT/RS1 circuit has the code number TF-O1B, and is designed to resonate at 465 kc/s.

The second basic type of transfilter appears in the TO series, and is given the symbol shown in Fig. 3 (a). Here, one face of the ceramic disc is silvered over its complete surface, the silvering being used as a common terminal; whilst the other face has two electrodes on it, one being a central "dot", to which the input is connected, and the other a "ring" around the dot, which forms the output connection. When an a.c. signal (at the resonant frequency) is connected to the input of the transfilter (between the dot and the common terminal), the ceramic disc resonates mechanically, and this mechanical movement then generates a sympathetic a.c. signal at the output terminals (between the ring and the common terminal) although no d.c. path exists between input and output. Since the dimensions of the dot and the ring are different, a transformation takes place between the impedance levels of the input and

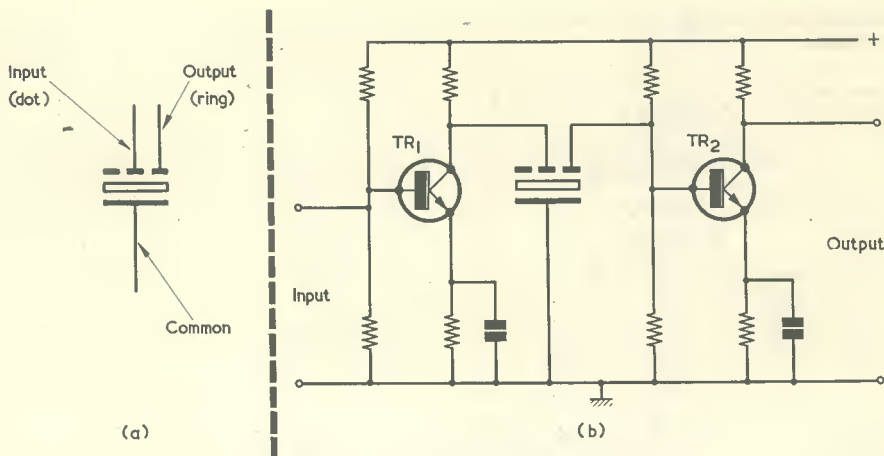


Fig. 3 (a). The symbol for a "TO" transfilter

(b). A "TO" transfilter employed in a simple i.f. amplifier


output circuits, so that the complete device closely simulates the action of a normal i.f. transformer.

The TO type of transfilter may be used in the type of circuit shown in Fig. 3 (b). Here, TR₁ and TR₂ are wired as conventional common emitter amplifiers, with the transfilter interposed between TR₁ collector and TR₂ base. At its resonant frequency the input of the transfilter presents a low impedance, so that a substantial amount of power is absorbed from TR₁ and transferred to the base of TR₂, thereby enabling a high degree of overall gain to be achieved. At other frequencies the transfilter presents a high impedance, so that very little power is absorbed from TR₁ and passed to TR₂, and the overall gain is low.

There is only one major snag in using the TO type of transfilter, and that arises in the following manner. For entirely practical reasons the physical dimensions of the ceramic disc must be kept reasonably small, although not so small that it becomes difficult to handle during the manufacturing process or in use. It is found that the size requirements are such that the disc must in practice operate on a fundamental frequency of only one or two hundred kc/s, so that for operation in the normal i.f. range the transfilter must be operated on its first overtone frequency. Thus, a TO transfilter, such as the TO-O2B, which is used in the SCT/RS1 receiver and is intended for operation at 465 kc/s, also responds to signals on its fundamental frequency of approximately 180 kc/s; hence, in a practical circuit, additional measures must be taken to suppress signals at the fundamental frequency. This can be achieved quite simply by either incorporating a simple L-C tuned circuit in some part of a multi-stage design, or by using a TF transfilter in conjunction with a TO type. It is this second solution that is adopted in the SCT/RS1 receiver.

The SCT/RS1 Circuit

The full circuit diagram of the SCT/RS1 single channel receiver is shown in Fig. 4. Here, the carrier signal is picked up by the antenna and fed to the r.f. tuned circuit L₁-C₂ and thence on to the base of the mixer transistor, TR₁. The local oscillator signal is developed in the crystal controlled stage, TR₂, and is fed, via C₄, to TR₁ emitter, so that mixing of the r.f. and local oscillator signals takes place, in this transistor producing a beat signal at TR₁ collector. The 180 kc/s and 465 kc/s products of this beat signal are accepted by transfilter TF₁ and passed on to the base of the first i.f. amplifier, TR₃, but the emitter of this transistor is bypassed by transfilter TF₂ so that the amplifier tends to reject the unwanted 180 kc/s component and accept only the 465 kc/s signal, which then appears in amplified form at TR₃ collector. The 465 kc/s signal from TR₃ collector is next selected by transfilter TF₃ and passed on to the base of the second i.f. amplifier, TR₄, which

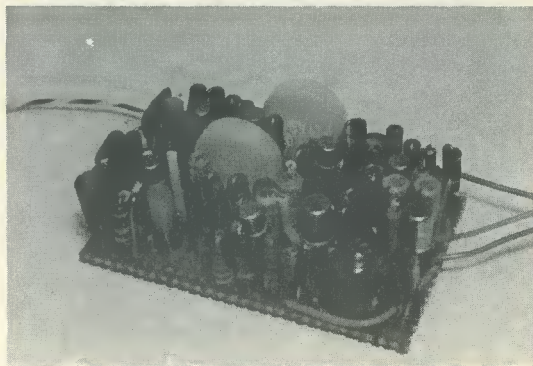

The other side of the receiver. The pot core assembly, L₃, is clearly visible on the right

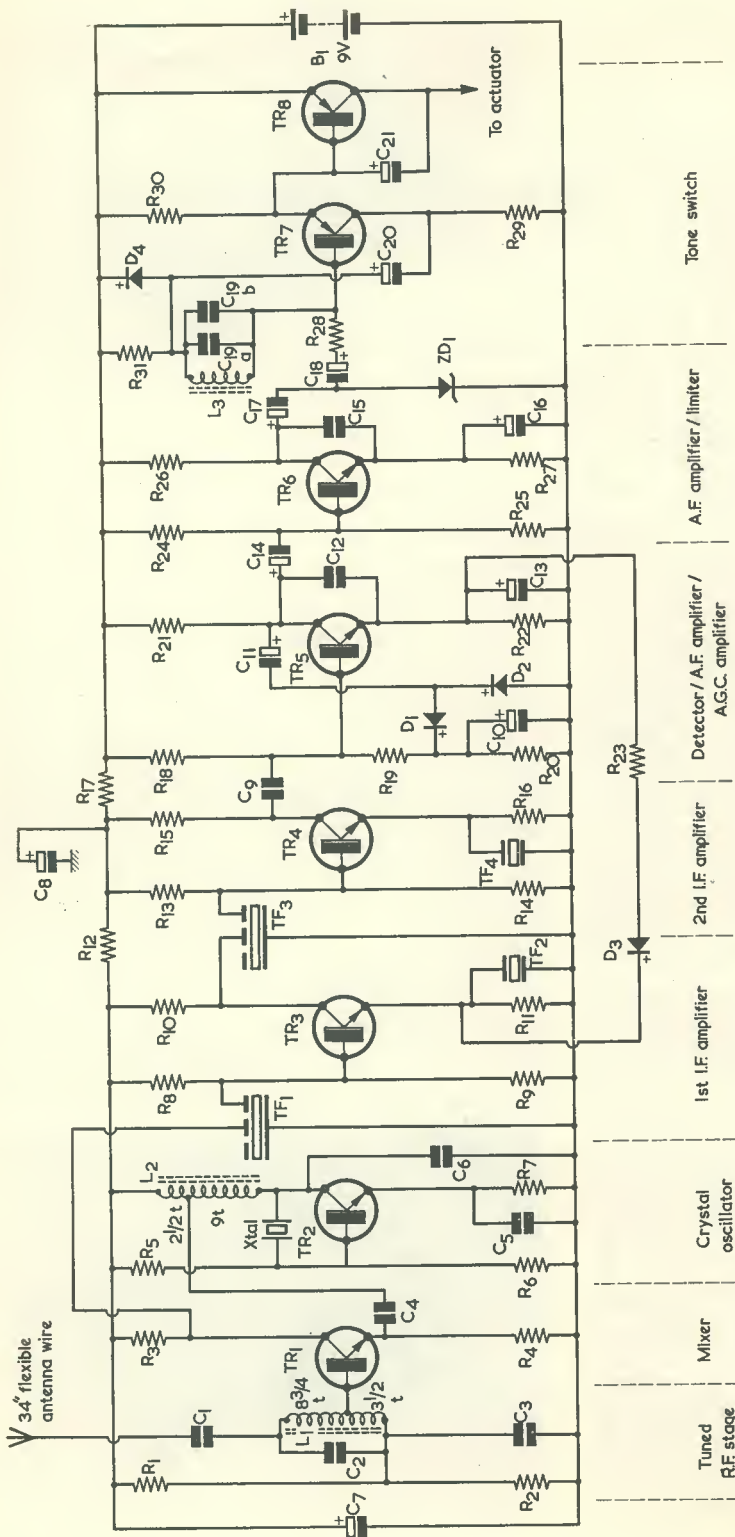


Fig. 4. The complete circuit of the SCT/RS1 single channel tone receiver

Resistors

(All resistors 1/4 watt 10%)

- R1 10kΩ
- R2 6.8kΩ
- R3 10kΩ
- R4 10kΩ
- R5 47kΩ
- R6 6.8kΩ
- R7 390Ω
- R8 47kΩ
- R9 12kΩ
- R10 4.7kΩ
- R11 2.7kΩ
- R12 120Ω
- R13 27kΩ
- R14 18kΩ
- R15 4.7kΩ
- R16 47kΩ
- R17 180Ω
- R18 100kΩ
- R19 6.8kΩ
- R20 5.6kΩ
- R21 8.2kΩ
- R22 4.7kΩ
- R23 470Ω
- R24 56kΩ
- R25 12kΩ
- R26 5.6kΩ
- R27 1kΩ
- R28 22kΩ
- R29 330kΩ
- R30 1kΩ
- R31 10kΩ

Capacitors

(All capacitors sub-miniature types)

- C1 12pF polystyrene
- C2 33pF silver mica
- C3 0.002μF Mylar
- C4 0.005μF Mylar
- C5 0.002μF Mylar
- C6 56pF silver mica
- C7 16μF electrolytic, 10V wkg.
- C8 16μF electrolytic, 10Vwkg.
- R22 4.7kΩ
- R23 470Ω
- R24 56kΩ
- R25 12kΩ
- R26 5.6kΩ
- R27 1kΩ
- R28 22kΩ
- R29 330kΩ
- R30 1kΩ
- R31 10kΩ

Diodes

- C9 0.01μF Mylar
- C10 8μF electrolytic, 6V wkg.
- C11 2μF electrolytic, 10V wkg.
- C12 0.005μF Mylar
- C13 8μF electrolytic, 6V wkg.
- C14 1μF electrolytic, 10V wkg.
- C15 0.005μF Mylar
- C16 16μF electrolytic, 10V wkg.
- C17 1μF electrolytic, 10V wkg.
- C18 1μF electrolytic, 10V wkg.
- C19 (a) 0.02μF Mylar
- C19 (b) 0.01μF Mylar
- C20 0.5μF electrolytic, 10V wkg.
- C21 1μF electrolytic, 10V wkg.

COMPONENTS

- R22 4.7kΩ
- R23 470Ω
- R24 56kΩ
- R25 12kΩ
- R26 5.6kΩ
- R27 1kΩ
- R28 22kΩ
- R29 330kΩ
- R30 1kΩ
- R31 10kΩ

further rejects any unwanted 180 kc/s components via TF₄ and accepts the 465 kc/s signal. The 465 kc/s signal then appears in its final amplified form at TR₄ collector and is passed on to the following circuit via C₉.

The i.f. signal from C₉ is fed to the base of TR₅, and this stage provides a total of three functions, these being detection, a.f. amplification, and a.g.c. amplification. It is this TR₅ stage which is largely responsible for the high performance that is obtained from the complete receiver, and it is therefore worth-while considering its operation in some detail.

Basically, TR₅ is wired as a common emitter amplifier, with collector load R₂₁, base-bias resistors R₁₈, R₁₉ and R₂₀, and emitter bias resistor R₂₂ bypassed by C₁₃. The values of these bias components are so chosen that TR₅ operates with a collector current of only a few tens of microamps, so that the emitter-base junction of the transistor is operated on a non-linear part of its characteristics, near cut-off. Thus, when the i.f. signal from C₉ is fed to TR₅ base, the transistor is driven on by positive-going parts of the signal and off by negative-going parts, and detection takes place. This type of detector has two distinct advantages over the conventional diode detector, the first being that it is far more sensitive to signals of very small amplitude, and the second being that the transistor type has an input impedance some 50 times greater than the diode version, so that negligible loading of the i.f. stages takes place and an effective increase in the i.f. gain is therefore made available.

The detected signal that appears in the TR₅ base-emitter junction is subjected to normal amplification in the transistor, but the collector load R₂₁ is decoupled to high frequency components by C₁₂, so that the basic 465 kc/s components of the signal are

rejected. At the same time, the modulation signal is subjected to considerable amplification and appears as an a.f. signal at TR₅ collector, to be fed to the following stage, TR₆, via C₁₄.

Part of the a.f. signal at TR₅ collector is also fed, via C₁₁, to rectifiers D₁ and D₂, which convert the a.f. to a d.c. signal of positive polarity. This is then smoothed by C₁₀ and applied to the base of TR₅ via R₁₉, so that the actual base bias of TR₅ varies with the strength of the i.f. signal from C₉. TR₅ functions as an emitter follower to the d.c. voltage applied to its base, with impedance transformation taking place in the transistor, so that the emitter potential, which varies between about 350mV under no-signal conditions and 1.5V on receipt of powerful signals, is at a low impedance level and is suitable for use as an a.g.c. voltage. This a.g.c. voltage is fed, via R₂₃ and D₃, to the emitter of TR₃. On receipt of a powerful signal the a.g.c. line raises the potential of TR₃ emitter, thereby reducing the base bias and the gain of that transistor, with the result that the magnitude of the a.f. signal at TR₅ collector remains fairly constant over a wide range of r.f. input signal strengths. Diode D₃ ensures that no a.g.c. potential is applied to TR₃ until the magnitude of the r.f. signal exceeds 100μV, so that the maximum possible gain is available to signals below this level.

The a.f. "tone" signal from TR₅ collector is fed, via C₁₄, to the base of TR₆, which is wired as a common emitter amplifier with its collector decoupled to high frequency signals by C₁₅. TR₆ further amplifies the a.f. signal, and passes it on, via C₁₇, to zener diode ZD₁, which clips the signal and converts it to a rectangular form with an amplitude of 4.7 volts. The magnitude of this final a.f. signal is constant within 3dB over r.f. input signal levels in the range 5μV to 200mV.

Inductors
(Formers, dust cores and pot core are available from Teleradio Electronics)
L₁ 3½T + 8½T of 28 s.w.g. enamel wire on 5mm former with dust core
L₂ 9T + 2½T of 28 s.w.g. enamel wire on 5mm former with dust core
L₃ FX2236 pot core with Teleradio wound bobbin

Semiconductors
TR₁ ST141 (Sinclair)
TR₂ ST141 (Sinclair)
TR₃ ST140 (Sinclair)
TR₄ ST141 (Sinclair)
TR₅ ST141 (Sinclair)
TR₆ ST140 (Sinclair)
TR₇ 2G381 (Texas) or NKT218 (Newmarket)
TR₈ 2G381 (Texas) or NKT218 (Newmarket)
ZD₁ 4.7V ¼ watt zener diode (Z4.7 or similar)
D₁-D₄ OA90 or similar

Transfilters
TF₁, TF₃ TO-O2B (Brush Cle vite)
TF₂, TF₄ TF-O1B (Brush Cle vite)

Miscellaneous
Veroboard panel with 0.1in hole matrix,
2½ × 1½in. (16 strips by 27 holes)
Midjet radio control crystal (one of matched pair, 465 kc/s i.f.)
3-pin transistor holder
34in flexible antenna wire
Wire, insulated sleeving, etc.

All components are available from Teleradio Electronics, 325/7 Fore Street, London, N.9, who supply a complete kit of parts.

(N.B. The values given for R₂₈, C₁₉ (a) and C₁₉ (b) are those used in the prototype and may need adjusting. Also required for testing (as described next month) are a 6V 0.1A bulb (cycle dynamo type), a crystal earphone, an OA90 diode and a 0.002μF capacitor.)

The a.f. signal from ZD₁ is fed, via C₁₈ and R₂₈, to the tone-operated "switch" given by TR₇ and TR₈. This circuit was fully described in the last part of this series and it will be remembered that, in the absence of the correct tone signal, TR₈ is cut off, so that an actuator connected in its collector circuit will be inoperative under this condition. On receipt of a correct tone signal of suitable amplitude, TR₈ is driven hard on, thereby operating the external actuator. The operating frequency of the tone switch can be adjusted by C₁₉, and the sensitivity of the switch can be adjusted by R₂₈. With correct selection

of the value of R₂₈ the overall sensitivity of the receiver can be made such that actuator operation is achieved with r.f. input signals of less than 2μV, although the tone switch is immune to operation by harmonics of tone signals other than the designed ones.

The manner in which adjustments are made, if necessary, to C₁₉ and R₂₈ are described in the next part of this series, which will appear next month. The next article will also give full details of construction and final testing of the receiver.

(To be concluded)



A LOGICAL APPROACH TO LOGIC

by S. J. Houghton, B.Sc.

Boolean algebra, logic circuits and truth tables tend to be a little awesome to the uninitiated. But they provide a useful means of solving some knotty switching problems, as the example in this article illustrates

Editor's Note


In this article conventional logic symbols are used. A + sign indicates OR, and can appear in an expression such as A + B. A multiplication sign (a full-stop is used here) indicates AND, as in A.B. A line drawn over a term means NOT; thus \bar{A} means NOT-A and is the exact inverse of A. Remember that all processes are carried out under binary conditions, where each quantity can only exist in one of two states: viz, 0 or 1; or, again, A or \bar{A} .

Astute readers will note that an unnecessary complication appears in the truth table for the worked example, and that this complication is eliminated very quickly by the application of Boolean algebra principles, resulting in the simplest possible solution.

Circuit Operation

In order to understand the operation of a radio receiver, almost all that is required is an understanding of the operation of each circuit. The knowledge of the order in which the circuits are connected may be deduced from the action of each particular circuit.

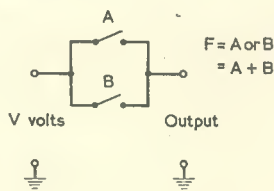As systems increase in complexity the understanding is based, in general, more and more on the method of interconnection of the circuits, less emphasis being put on the finer details of circuit operation.



(a)

A	B	F
open	open	0 volts
closed	open	V volts
open	closed	V volts
closed	closed	V volts

(b)

A	B	F
0	0	0
1	0	1
0	1	1
1	1	1

(c)

Fig. 1 (a). Two switches connected as shown are representative of an OR gate
 (b). A truth table covering all the possible combinations of A and B
 (c). The corresponding truth table in which 1 represents the presence, and 0 the absence, of a conducting path

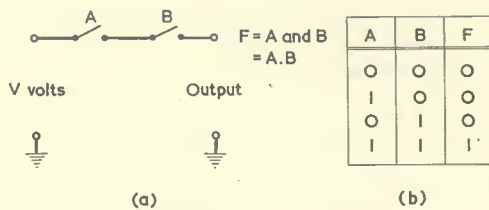


Fig. 2 (a). Two switches in series represent an AND gate
(b). The truth table for an AND gate

the 1 and the 0 is different from their use in normal arithmetic, and it must be borne in mind that they do not directly represent numbers. In this example, they merely represent the presence or absence of a conducting path. Similarly, we represent F by 1 or 0 depending on the presence or absence of a conducting path through the element and finally we represent OR by “+” which, again, must not be confused with the arithmetical plus sign.

These ideas may be clearly seen by an examination of the “truth table” of Fig. 1 (b), which is made up by trying all possible combinations of the variables. The corresponding truth table using 1 and 0 is shown in Fig. 1 (c). The 1 and 0 may be taken to represent the “true” and “false” of symbolic logic, i.e. Boolean Algebra. Hence, $F=A+B$ would be interpreted as “ F is true if either condition A or condition B or both is true”.

A similar consideration of the switching arrangement in Fig. 2 (a), which represents a logic AND element, gives the truth table of Fig. 2 (b). In this case there is a conducting path ($F=1$) only when both A and B are closed. The symbol “.” is used to indicate AND and must not, once again, be confused with the sign corresponding to algebraic multiplication. Hence $F=A.B$ is interpreted as “ F is true if and only if condition A is true and condition B is true”.

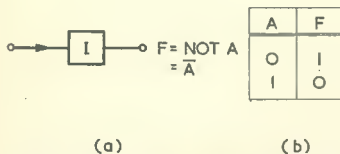


Fig. 3 (a). Symbolic representation for an inverter or NOT element
(b). The truth table for the inverter

A further element to be considered is the inverter or NOT element of Fig. 3 (a), which could in practice be given by a device such as a common emitter transistor where an input 0 gives an output 1 and vice versa. This element is represented by $F=\bar{A}$ (where, since \bar{A} may only have the values 1 and 0, \bar{A} corresponds to 0 and 1 respectively). This is interpreted as “ F is true if and only if A is not true”.

Simple relations		Laws	Simplification rules
$0+0=0$ (1)	$A+A=A$ (9)	<u>Commutation</u>	$A+A.B=A$ (22)
$0 \cdot 0=0$ (2)	$A \cdot A=A$ (10)	$A+B=B+A$ (17)	$A+\bar{A}.B=A+B$ (23)
$1+1=1$ (3)	$\bar{A} \cdot A=0$ (11)	$A \cdot B=B \cdot A$ (18)	$A \cdot (A+B)=A$ (24)
$1 \cdot 1=1$ (4)	$\bar{A}+A=1$ (12)	<u>Association</u>	<u>De Morgan's Theorem</u>
$0 \cdot 1=0$ (5)	$0+A=A$ (13)	$(A+B)+C=A+(B+C)$ (19)	$\bar{A} \cdot \bar{B}=\overline{A+B}$ (NAND)
$0+1=1$ (6)	$0 \cdot A=0$ (14)	$(A \cdot B) \cdot C=A \cdot (B \cdot C)$ (20)	$A+\bar{B}=\overline{A \cdot \bar{B}}$ (NOR)
$\bar{0}=1$ (7)	$1+A=1$ (15)	<u>Distribution</u>	
$\bar{1}=0$ (8)	$1 \cdot A=A$ (16)	$A \cdot (B+C)=A \cdot B+A \cdot C$ (21)	

Fig. 4. Useful relationships in symbolic logic

Some useful relationships are shown in Fig. 4. Here we encounter such equations as $1+1=1$, which is not, of course, at all like the sort of thing we encounter in ordinary arithmetic. This particular relationship is, however, an OR relationship such as that of Fig. 1 (a) where 1 may stand for a conducting path. Reading it as “a conducting path or a conducting path is a conducting path”, the statement is meaningful and logical.

The last two simplification rules (known in symbolic logic as DeMorgan's Theorem) refer to NAND and NOR circuits. NAND is equivalent to NOT(A AND B) and NOR to NOT(A OR B). These should be noted as they are very useful in more advanced logic work.

Example

Let us now see how logic principles may be used to solve a switching problem.

Consider a simple example of the use of logic in a factory, in the form of a control for a hot-air heating system where it is desirable to control a fan for circulating the air and a motor ignition for turning on a furnace (oil heating) automatically.

We are presented with three conditions.

(a). The furnace must be turned on whenever the building temperature is below a given value. Hence a thermostat remote from the furnace supplies a variable “T” which is 0 when the temperature is too low and 1 when it is higher than the required temperature.

(b). The fan should not operate until the furnace is warm enough to heat the air. Thus a thermostat in the furnace supplies a variable “L” which is 1 when the temperature is sufficiently high and 0 otherwise.

(c). To prevent overheating the furnace must be switched off above a certain temperature defined by a third thermostat. This supplies a variable “H” which is 0 if the temperature is not excessive but 1 otherwise.

We approach this problem by drawing up a truth table (Fig. 5) which takes into account all the possible variations of T, L and H, with the corresponding values of the functions F (fan) and M (motor ignition). Note that the first three columns present all the combinations that can be offered by T, L and H. Impossible conditions are ignored, such as are given in the second and sixth lines of the table, where the furnace has an excessively high temperature ($H=1$) but is not hot enough to actuate the fan ($L=0$).

To examine this truth table in more detail, we may start with the conditions which affect M. Over the first four lines of the table, T at 0 indicates that the room temperature is too low and this is one of the requirements for switching on the furnace motor. The other requirement is that the motor must switch off when H is at 1 (i.e. the third

T	L	H	F	M
0	0	0	0	1
0	0	1	Not possible	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	0
1	0	1	Not possible	0
1	1	0	1	0
1	1	1	1	0

Fig. 5. Truth table covering all the possibilities in the example described in the text

thermostat indicates excessive temperature). In the first and third lines both T and H are at 0 and these allow M to become 1 (i.e. the motor switches on).

The truth table similarly indicates the conditions which allow the fan to operate, i.e. F to become 1.

This truth table now shows all the possible circumstances controlling M and F. Dealing first with M, we know that M is 1 when T, L and H are 0 (first line) or when T is 0, L is 1 and H is 0 (third line). So we may say:

$$\begin{aligned}
 M &= \bar{T}.\bar{L}.\bar{H} + \bar{T}.L.\bar{H} \\
 &= \bar{T}.\bar{H}.(L + \bar{L}) \quad (\text{from relation 21}) \\
 &= \bar{T}.\bar{H}.1 \quad (\text{from relation 12}) \\
 &= \bar{T}.\bar{H} \quad (\text{from relation 16})
 \end{aligned}$$

Let us repeat the process for F. F is 1 for the conditions of T, L and H shown in the third line or the fourth line or the seventh line or the eighth line. Following the same procedure as with M we may say:

$$\begin{aligned}
 F &= \bar{T}.L.\bar{H} + \bar{T}.L.H + T.L.\bar{H} + T.L.H \\
 &= \bar{T}.L.(H + \bar{H}) + T.L.(H + \bar{H}) \quad (\text{from relation 21}) \\
 &= \bar{T}.L.1 + T.L.1 \quad (\text{from relation 12}) \\
 &= \bar{T}.L + T.L \quad (\text{from relation 16}) \\
 &= L.(T + \bar{T}) \\
 &= L
 \end{aligned}$$

The resultant switching arrangement is shown in Fig. 6. Since we have found that $F=L$, it is merely necessary for the first furnace

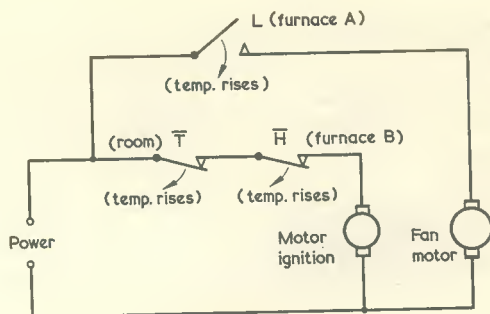


Fig. 6. The final switch logic worked out in the example

thermostat to control F. When L is 1 the thermostat switch closes and switches on the fan.

We have also found that $M = \bar{T}.\bar{H}$. This is the AND condition given by the two switches of Fig. 2 (a) and so we may similarly have two switches in series to control the furnace motor. However, since we are dealing with \bar{T} and \bar{H} , the thermostat switches are open for the 1 condition (temperature too high) and closed for the 0 condition (temperature too low), which is the inverse of the switch logic conditions of Fig. 2 (a).

The circuit of Fig. 6 meets all the control requirements originally stated and does so in the simplest possible form. *

Silicon Glass Rectifiers with 50A Surge Current Capability

The SGR100 and IN4384-6 silicon glass rectifiers comprise a new series of subminiature glass (DO-29) hermetically sealed units capable of conducting 1A average forward current at 100°C ambient and withstanding non-repetitive single cycle surge currents of up to 50A, announce Transtron Electronic Ltd., Gardner Road, Maidenhead, Berks.

Constructed with double diffused junctions rated at d.c. blocking voltages of up to 1,000V, and exhibiting specified maximum forward voltage drops as low as 1V at 1A, these units are especially suited for military, industrial and consumer applications where space is at a premium and robustness in the face of overload surge current transients is required. Typical applications are for bridge rectifiers with heavy capacitance smoothing, relay slugging and d.c. motor surge suppression. In effect, the series fills the gap between existing subminiature glass diodes which are unable to handle high currents and metal case stud or axial lead rectifiers with all their attendant mounting and heat sinking problems.

New Society

A Flint and District Radio Society was inaugurated at a well-attended meeting held at the Central Library, Flint on Friday, 30th June.

The Society intends to promote all aspects of amateur radio, including construction of equipment, operation of a Flint transmitter and preparation of members for the Radio Amateur Examination and the Post Office Morse tests.

Lectures are to be held at the Central Library, Church Street, Flint and the Society also has accommodation available for its varied programme of practical activities.

A debate on "valves or transistors in amateur radio" is to be held on Friday, 14th July at 7.30 p.m.

The Society is affiliated to the Flint Association for the Arts and joins the highly-successful Flint Photographic Society and the Flint and District Art Society, which were also formed in association with Flint Public Libraries.

LAST MONTH WE DISCUSSED THE USE OF A.F. output valves in parallel or push-pull under Class A₁ conditions (in which no grid current flows) and Class A₂ conditions (in which grid current flows during part of the input cycle). We noted that push-pull operation is preferable because, when the valves work in Class A, the even harmonics introduced by distortion in the valves are cancelled out, no d.c. magnetising force is exerted on the output transformer core, and negligible current at signal frequencies is drawn from the h.t. supply.

We shall now turn our attention to other classes of amplification.

Class B Operation

In Class A₁ and A₂ operation, as we saw last month, the input signal is applied to the most linear part of the I_aV_g curve of the valve. This ensures that only a low amount of distortion is introduced by the valve itself.

cannot be operated as an audio frequency amplifier in Class B₁ or B₂ because the signal voltage at the anode would be an excessively distorted version of the input signal voltage.

Two valves in push-pull can, on the other hand, be operated in Class B₁ or B₂ to provide an a.f. output stage, as is shown in Fig. 2. In Fig. 3 (a) we see the anode currents for each valve over several cycles of the input signal. As is to be expected from Fig. 1, each anode draws current during alternate half-cycles. These anode currents flow in opposing directions through each half of the output transformer primary, whereupon they recombine to produce the original signal, as illustrated in Fig. 3 (b). It is worth examining this process in a little more detail, as it is quite different from that occurring with the Class A push-pull amplifier we discussed last month. If, during one half-cycle of the input signal, the grid of the upper valve of Fig. 2 is negative, then this valve is cut off and

UNDERSTANDING RADIO

Classes of Amplification

$$f = \frac{1}{2\pi\sqrt{LC}}$$






by W. G. Morley

An alternative method of operating a valve is shown in Fig. 1. Here we have the same I_aV_g curve as we had when we previously considered Class A₁ and A₂ operation, but the bias point is now at, or very near, the grid cut-off voltage. We apply our input signal as before and we produce, graphically, the corresponding anode current. As may be seen, no anode current flows during the negative input half-cycle (or nearly all of the negative input half-cycle) and all we obtain at the anode is a series of half-cycles resulting from the positive half-cycles at the grid.

This method of working is known as Class B₁ operation when no grid current flows during the input cycle, or Class B₂ operation when grid current flows during part of the positive input half-cycle.

It is possible to operate a single valve in Class B₁ or B₂ as an r.f. amplifier if a parallel tuned circuit resonant at the frequency being handled forms the anode load. Although only half-cycles of the signal frequency appear at the anode, the tuned circuit between the anode and the h.t. positive rail oscillates at its resonant frequency and provides the missing half-cycles itself. At the same time, a single valve

draws no current. The grid of the lower valve has a positive half-cycle applied to it and its anode current varies to provide an amplified half-cycle. When the next half-cycle commences, the grid of the lower valve goes negative and the grid of the upper valve goes positive. This time it is the lower valve which is cut off and the upper valve which provides the amplified half-cycle. Thus, on one half-cycle the upper valve is cut off and no current flows in the upper half of the output transformer primary, and on the next half-cycle the lower valve is cut off and no current flows in the lower half of the output transformer primary.

Push-pull Class B₁ and B₂ operation does not, in consequence, offer the automatic distortion-cancelling advantage which is given by Class A push-pull operation. Also, the current drawn from the h.t. supply is not constant, but varies considerably with input signal amplitude. If no input signal is applied both valves are cut off, or very nearly cut off, and the h.t. current drawn is at a minimum. When an input signal is applied, the valves draw h.t. current on alternate half-cycles, the current increasing with signal amplitude. In consequence,

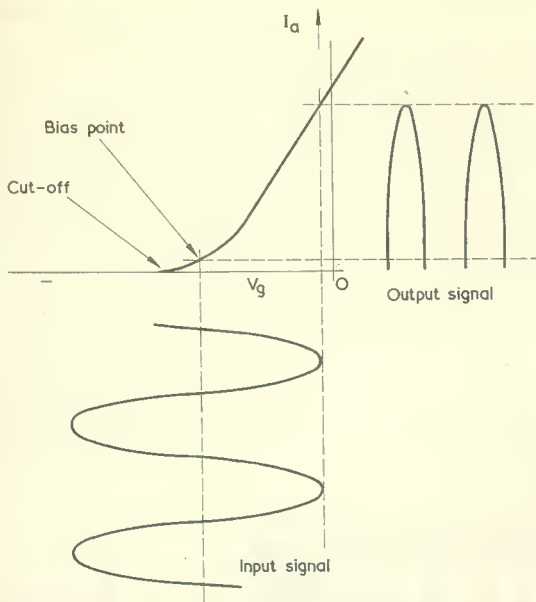


Fig. 1. When a valve is operated in Class B, the bias point is at, or very near, its cut-off voltage, so that only amplified half-cycles appear in the anode circuit

it is necessary for the h.t. supply fed to a Class B₁ or B₂ push-pull stage to be well regulated.

Since the point along the $I_a V_g$ curve at which the valves are biased will normally be non-linear, a form of distortion can be introduced by the output stage which is shown, in exaggerated form, in Fig. 4. In this diagram sine wave half-cycles at each anode are distorted over the range where the anode

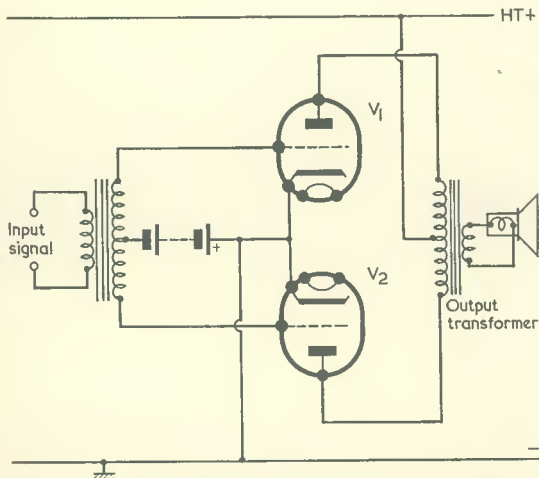


Fig. 2. A Class B push-pull output stage. Due to varying anode currents, cathode bias cannot be used and an external source of grid bias (shown here as a battery) has to be provided

current is low, with a consequent distortion in the combined waveform as illustrated below. It is interesting to note that the percentage distortion due to this effect increases as signal amplitude decreases. If the valves handle a large signal, the distorted section is only a small fraction of the overall waveform whereas, if the valves handle a small signal, the distorted section becomes a very large fraction of the overall waveform.

The main advantage of a Class B₁ or B₂ push-pull a.f. output stage is that it has a very high efficiency in terms of the ratio of h.t. power consumption to a.f. power output. Also, it is possible to obtain a much higher power output from two valves in a Class B push-pull output stage (especially when Class B₂ working is used) than would be given by the same two valves in a Class A push-pull output stage. Class B₂ working is, therefore, attractive for public address amplifiers and similar applications where a high output power is required, and particularly where batteries are used for the power supply.

Because the main reason for using a Class B push-pull a.f. output stage is to obtain a high power, such stages are almost always operated in Class B₂, in which grid current flows during part of the positive input half-cycles applied to the grids. The output stage has, in consequence, to be driven by a preceding power stage. Since operation in Class B₂ is much more common than operation in Class B₁, it can normally be assumed that reference to a Class B push-pull amplifier infers the Class B₂ condition.

It will be noted that, in Fig. 2, grid bias is provided by an external source, shown in the diagram as a battery. Cathode bias cannot be used for Class B stages because of the wide variations in anode and, hence, cathode current for different input signal amplitudes.

Class C Operation

A third method of working is described as Class C operation, and this is illustrated in Fig. 5. As may be seen, the grid bias point in this diagram is negative of cut-off so that the valve only passes anode current during *part* of the input positive half-cycles.

Because of the high degree of distortion introduced by Class C operation, this mode of working cannot be employed for a.f. amplification. On the other hand, it is very useful for r.f. amplification when a parallel tuned circuit forms the anode load, since it offers a high efficiency in terms of output power. Oscillatory effect in the anode tuned circuit ensures that the missing sections of the cycles appear across it, even though the valve does not itself pass anode current during these periods.

Due to the high efficiency of r.f. power amplifiers in Class C, this mode of operation is very frequently used for the output valve or valves of transmitters. Class C output valves are employed singly or in push-pull; in the latter case the two anodes may be coupled to the two ends of a tuned winding having a centre-tap which connects to the h.t. positive supply.

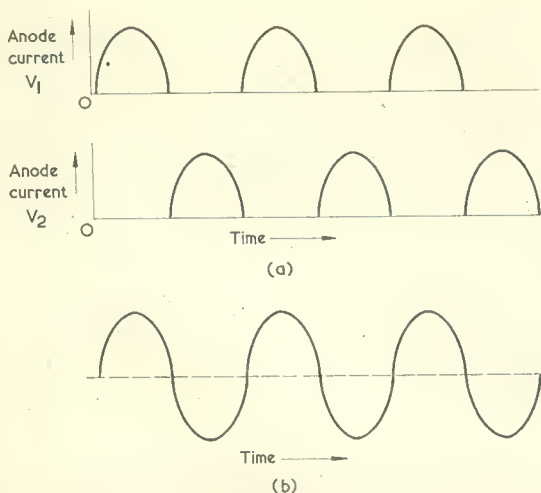


Fig. 3 (a). With a sine wave input signal applied in Fig. 2, anode current in the two valves flows on alternate half-cycles
 (b). Since the anodes are connected to the opposite ends of a centre-tapped transformer primary, the two anode currents combine to reproduce the original signal

Greatest efficiency is obtained when the input drive to the grid of a Class C amplifier is sufficiently high to allow grid current to flow during the more positive parts of the positive half-cycles. This is the method of working most commonly used and can be referred to as Class C₂. If grid current does not flow, the mode of operation may be described as Class C₁. References to r.f. power amplifiers normally state "Class C", whereupon Class C₂ operation can usually be assumed.

As is to be expected from a consideration of the manner in which it works, the h.t. current drawn by a Class C amplifier varies with input signal amplitude. At very low signal amplitudes (too low for correct operation) the valve is cut off all the

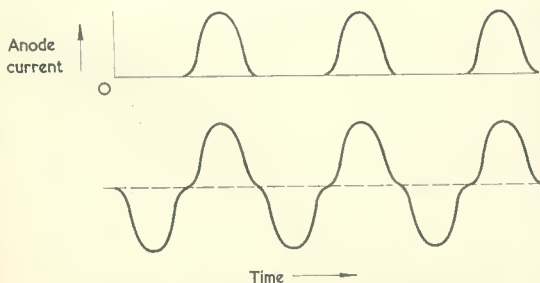


Fig. 4. Showing in exaggerated form a type of distortion which can be introduced by a Class B output stage. The half-cycles at each anode may have the shape shown in the upper section, whereupon the combined waveform has the distortion shown below

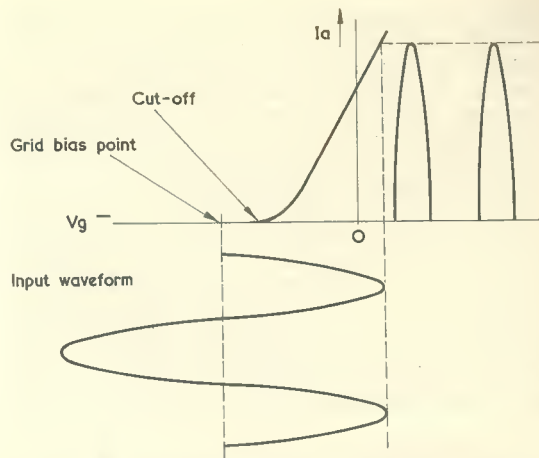


Fig. 5. In Class C the bias point is negative of cut-off, with the result that the valve passes current only during part of the positive input half-cycles. It is usual for the positive input peaks to pass into the grid current region, as is shown here

time and it draws no anode current. When the signal input amplitude is sufficient for positive half-cycle peaks to pass beyond cut-off the valve commences to draw anode current, this current increasing as input amplitude increases.

Class AB Operation

We have seen that, in Class A, the input signal is applied over the most linear part of the $I_a V_g$ characteristic. In Class B the valve is biased at (or very slightly positive of) the cut-off point so that it only amplifies the positive input half-cycles. And, in Class C, the valve is biased negative of cut-off so that it only amplifies part of the positive input half-cycles. Of these three classes, Class A and Class B can be used for a.f. output circuits.

A fourth mode of working is known as Class AB. As the name infers, Class AB relates to the case where the grid bias point lies between those which apply for Class A and Class B operation. Class AB working can be used with two valves in an a.f. push-pull output circuit, and it enables a higher power output to be achieved than would be given by the same valves in Class A.

A Class AB amplifier functions in the same manner as a Class A amplifier for small signal inputs, because the input waveform is still applied to a linear part of the $I_a V_g$ characteristic. As input signal amplitude increases, the negative parts of the grid waveform become applied to the more non-linear section of the $I_a V_g$ characteristic, and the distortion offered by each valve increases. However, the ability to cancel out even harmonics which is given by a Class A amplifier tends to apply here also, and this distortion is reduced. At yet higher input signal amplitudes each valve may be cut off during negative input peaks, whereupon one valve only passes anode current during these periods.

Since two valves in Class AB offer a greater power than the same valves in Class A, Class AB operation is attractive for applications where an increased distortion at high output powers is acceptable. With reasonably careful design, Class AB operation can also be used for the output stages of domestic high quality amplifiers.

Class AB stages may be divided into Class AB₁ (where no grid current flows) and Class AB₂ (where grid current flows during part of the positive input half-cycle). It is normal practice for the Class AB₂ grid bias point to be closer to cut-off than occurs in Class AB₁, and Class AB₂ gives a greater power output. One sometimes encounters the statement that "Class AB₂ is intermediate between Class AB₁ and Class B". For domestic amplifiers, Class AB₁ is preferred because the output stage can be

preceded by a simple voltage amplifier circuit, instead of by a power amplifier as would be required with Class AB₂. Also, the distortion introduced by the output stage will be lower with Class AB₁.

Unlike a Class A push-pull output stage, a Class AB push-pull stage draws an increased h.t. current as input signal amplitude increases. The increase in h.t. current is not as marked as with Class B operation, and does not preclude the use of cathode bias for Class AB₁ working. An external source of grid is, however, required for Class AB₂.

Next Month

In next month's issue we shall consider the various types of valve which are employed in a.f. output stages.



Combined AF/RF Signal Generator

Tracer! (JBS)

by W. Kemp

A neat item of test equipment which can be used as a probe for both r.f. and a.f. signals without switching. Although intended primarily for testing transistorised equipment, it may also be employed with valve equipment by adding an input isolating capacitor

THIS SIMPLE LITTLE UNIT, WHICH USES ONLY TWO transistors, makes a useful combined a.f. and r.f. signal tracer, and is unique in that no external r.f. probe is required. The circuit works from a 9 volt battery and draws a total current of only 2mA, giving a working battery life of hundreds of hours with most small batteries.

The output of the unit, which measures $2\frac{1}{2} \times 1\frac{1}{8} \times 1$ in and includes a built-in volume control, is taken to a crystal earpiece. The complete and independent piece of test equipment can be built for less than 25s.

The Circuit

The full circuit diagram of the unit is shown in Fig. 1, and consists basically of a simple 2-stage direct coupled audio amplifier designed around v.h.f. transistors.

As far as a.f. signals are concerned, the circuit operates in the following manner.

The a.f. input signal is connected to the input terminals and fed, via C₁, to the variable resistor RV₁. A proportion of this signal is then tapped off at RV₁ slider and fed via C₂ to the base of TR₁, which is connected as a common emitter amplifier with collector load R₁. An amplified version of the input signal is thus made available at TR₁ collector, and this signal is fed directly to the base of TR₂, which is also wired in the common emitter mode with collector load R₂, so that further signal amplification takes place and a final large amplitude a.f. signal appears at TR₂ collector. This is fed directly to the crystal earpiece. C₃ bypasses high frequency signals and restricts the bandwidth of the amplifier to the a.f. range.

A standing bias voltage is set up at TR₂ emitter via R₃, which is decoupled to a.c. by C₄. The magnitude of this bias voltage is approximately equal to the d.c. potential at TR₂ base, which, in turn, is at the same potential as TR₁ collector. The bias potential

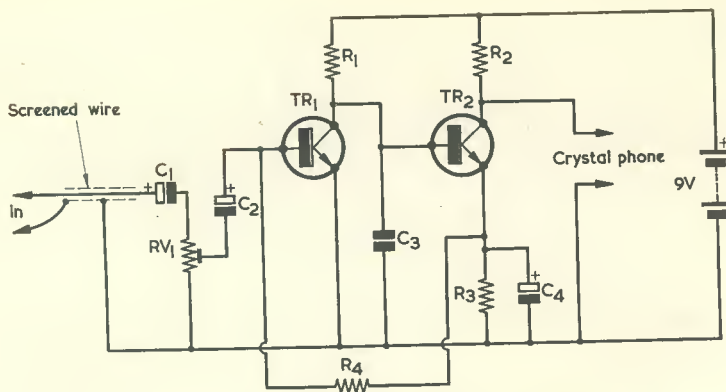


Fig. 1. The circuit of the combined a.f.—r.f. signal tracer

at TR₂ emitter is then used to provide the base-bias to TR₁ via R₄.

A d.c. negative feedback loop is thus set up in the transistor biasing network, and a large degree of self-compensation against shifts in the biasing levels, due to variations in transistor characteristics and supply line potentials, is obtained. Suppose, for example, that for some reason the standing current of TR₁ tends to increase above the design level, causing the potential at TR₁ collector to fall. If this occurs, the potential at TR₂ base, and thus at TR₂ emitter, will also fall. Since TR₁ base-bias is derived from TR₂ emitter, the base current (and

hence the collector current) of TR₁ will automatically be reduced, thereby countering the original change in TR₁ collector current. A high degree of d.c. stabilisation is therefore obtained.

This completes the description of the d.c. and a.f. working of the circuit, and we can now consider the r.f. operation of the unit.

In "conventional" practice, an external r.f. probe is used in conjunction with an a.f. amplifier when tracing modulated r.f. signals, the probe circuit being similar to that shown in Fig. 2 (a). The simple explanation usually given for the action of such a probe is that the r.f. signal is applied across diode D via blocking capacitor C, and that the diode then rectifies or demodulates the r.f. signal, making the demodulated a.f. signal available at the output terminals of the probe. In fact, the action is a little more complex than is implied by this explanation, and to understand this we must first look at the typical forward characteristic curve of a normal diode, as shown in Fig. 2 (b).

COMPONENTS

Resistors

(All fixed values $\frac{1}{2}$ watt)

- R₁ 5.6k Ω 10%
- R₂ 5.6k Ω 10%
- R₃ 1.8k Ω 10%
- R₄ 27k Ω 10%
- RV₁ 10k Ω skeleton potentiometer

Capacitors

(All miniature types)


- C₁ 8 μ F, 15V wkg. electrolytic
- C₂ 16 μ F, 15V wkg. electrolytic
- C₃ 0.05 μ F, ceramic
- C₄ 50 μ F, 6V wkg. electrolytic

Semiconductors

- TR₁ ST140 (Sinclair)
- TR₂ ST141 (Sinclair)

Miscellaneous

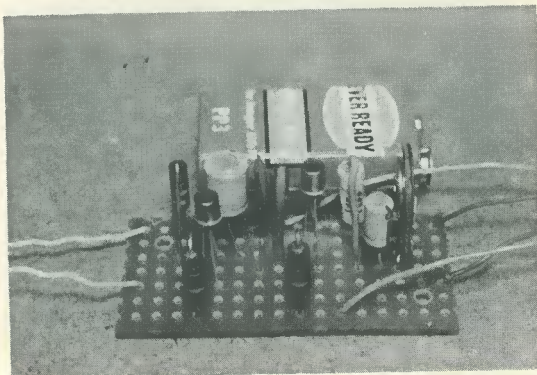- Veroboard with 0.15in hole spacing, 2 $\frac{1}{2}$ by 1 $\frac{1}{2}$ in (7 strips by 16 holes)
- Crystal earpiece
- Wire, insulated sleeving, screened wire, 9 volt battery and battery terminals, etc.



The completed signal tracer, shown alongside a PP3 battery to demonstrate its small size. This photograph was taken immediately after tests of the prototype, and screened wire is recommended for the input instead of the unscreened leads shown here

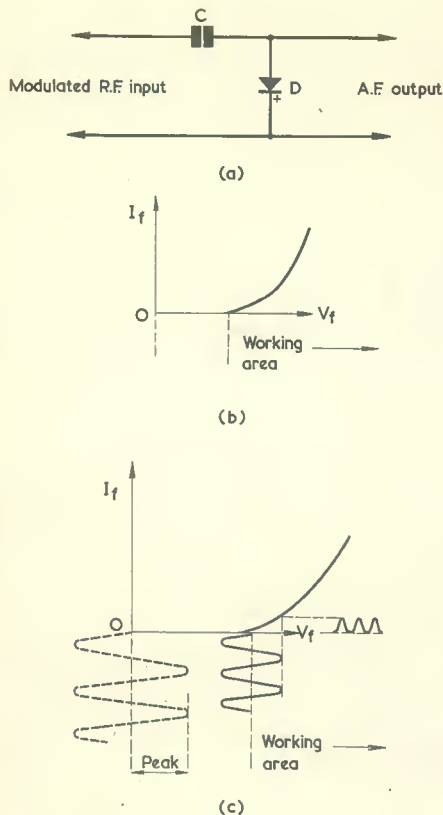


Fig. 2 (a). A typical signal tracer r.f. probe
 (b). Simplified diagram showing the forward characteristic of a germanium diode
 (c). The characteristic results in more efficient detection of low-level signals if the diode is given a slight forward bias

This diagram shows, in simplified form, the forward characteristic of a typical junction diode, I_f indicating the forward current obtained for a given forward voltage, V_f . The most important points to notice about this diagram are that little forward current flows until the forward potential reaches the start of what is shown in the diagram as the "working area", and that I_f then increases sharply and in a non-linear fashion as V_f increases. Typically, the "working area" of a germanium diode starts at 200mV. Since the curve represents voltage against current, an impedance is also implied, so that we can say that the forward impedance of the diode varies with forward voltage, the impedance being relatively high below the "working area" voltage and low and very non-linear after the "working area" is reached.

Now, if an a.c. signal is applied across the diode, as in the case of the r.f. probe, the input signal will swing about the zero volts line, as shown by the


dotted waveform in Fig. 2 (c), and if the peak value of this waveform does not reach the "working area" of the diode very little forward current will flow on any part of the waveform. Thus, a germanium junction diode may offer little demodulation action to input signals with peak-to-peak amplitudes of less than 400mV. If the peak amplitude of the input signal enters the "working area" of the diode, efficient demodulation commences to take place.

Suppose, now, that we manage to find some way of applying a bias potential to the diode, so that with no input signal applied the diode is biased to the start of its "working area" voltage. If we now apply an alternating input signal across the diode, the signal will swing about the voltage to which the semiconductor is biased, as shown by the full line waveform of Fig. 2 (c), and signal amplitudes of only tens of millivolts will be sufficient to cause efficient detection to occur.

The simplified characteristics shown in Figs. 2 (b) and (c) refer to forward currents of the order of 50 to 100 μ A and above. A forward current can still flow in a germanium diode before the start of the "working area" shown in the diagrams, but this will be relatively low. The function of Fig. 2 (c) is to show that detection of low-level signals is much more efficient when the diode is suitably biased in the forward direction.

The normal demodulator probe, of course, has no bias potential applied, and thus suffers from the disadvantage of being inefficient when fed by small amplitude signals. If, however, we look at a transistor, we find that a junction diode is naturally formed between the base and emitter, this "diode" passing a current I_e when biased by a voltage V_{be} . It follows that, if we use the transistor correctly, we can obtain efficient detection by suitably biasing the base-emitter junction, while at the same time obtaining gain by normal transistor action, and this is the technique used in Fig. 1.

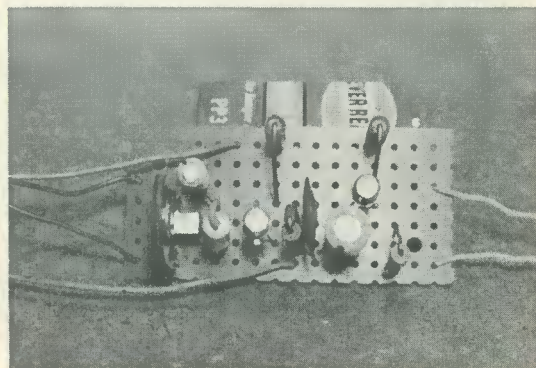Returning now to the circuit diagram of Fig. 1, the r.f. action of the unit may now be described. The r.f. input signal is applied to TR₁ base via C₁, RV₁, and C₂, and appears across the base-emitter junction of the transistor. If the amplitude



A top view of the prototype signal tracer

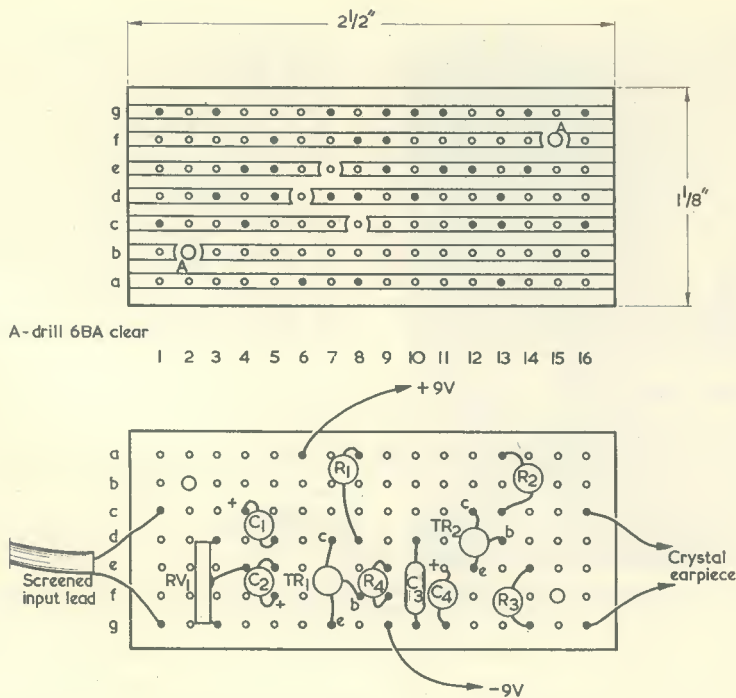


Fig. 3. The copper and component sides of the Veroboard after assembly

of this signal is greater than, say, 20mV, substantial distortion of the signal will be obtained, since the transistor is biased into its operating region, and detection will be obtained. This detected signal is then amplified by the transistor and appears at TR₁ collector, where C₃ bypasses any remaining r.f. components to the negative supply line, leaving the demodulated a.f. part of the signal to be fed on to TR₂. Here it is further amplified and finally fed to the crystal earpiece.

Note that, for efficient detection to take place in the TR₁ stage, the internal base-emitter capacitance of the transistor must be very low, and this condition is only met on v.h.f. transistor types. The capacitance on the Sinclair ST140 transistor specified is a mere 2.5pF, and is thus ideally suited to this application.

When the circuit is used purely as an a.f. amplifier, the signal applied to TR₁ base has an amplitude of less than 20mV, so that appreciable distortion of the signal does not then take place.

Construction

The unit is wired up on a small piece of Veroboard panel with 0.15in hole spacing, and construction should be started by cutting this panel to size and drilling the two small mounting holes to clear 6BA screws, as shown in Fig. 3. Next, break the copper strips, with the aid of a small drill or the special cutting tool that is available, where indicated.

The components and leads can now be soldered in place on the panel, as illustrated in the diagram. Note that all components are mounted vertically, and that insulated sleeving should be used where there is any danger of components short-circuiting against one another. The mounting tags of RV₁ should be reduced in diameter with the aid of a file, so that they fit in the holes in the panel, before attempting to solder this component in place.

The screened input lead should be kept fairly short, a length of 18in or less being adequate for signal tracing in transistorised equipment. The centre lead ends in a test prod, or probe, whilst the outer conductor may be terminated by a short flexible lead fitted with a crocodile clip.

When construction is complete, the unit can be given a functional check by connecting a 9 volt battery in place and checking that a signal is heard in the earpiece when a test signal is connected to the input of the unit.

Using The Unit

When using the unit for signal tracing, the earthy input terminal should be made common to the negative supply line of the equipment under test, and the remaining probe terminal should be connected to appropriate test points. When testing defective equipment, initial tests should, generally, be made at the "front end" of the equipment, and successive tests should work backwards towards

the rear of the circuitry until the faulty part of the circuit is located. If, for example, tests are being made on a faulty superhet receiver, the first test should be made by setting RV_1 for maximum sensitivity and connecting the probe to the r.f. stage of the receiver, checking that some kind of signal is heard in the earpiece. If that test is satisfactory, move the probe to the first i.f. stage, slowly working through the circuit towards the loudspeaker until a point is reached at which no signal is heard in the earpiece, the faulty part of the circuit then being that which is under test. It will be helpful to gain experience by using the tracer with a serviceable receiver before employing it for fault-finding.

All electrolytic capacitors, including C_1 and C_2 , exhibit a small amount of inductance, so that their impedances actually increase above certain frequencies. Because of this, it is recommended that, if the unit is to be used for signal tracing at frequencies above about 7 Mc/s, small 1,000pF bypass capacitors be wired in parallel with C_1 and C_2 .

Note that the signal tracer is primarily intended for testing transistorised equipment. If it is to be used on valve equipment, a $0.5\mu\text{F}$ capacitor, with a working voltage of 500, should be inserted in series with the probe lead.



25th GERMAN RADIO EXHIBITION 1967 — BERLIN

There are only three more weeks till the Great German Radio Exhibition in Berlin. For the twenty-fifth time the public will be made acquainted with a great achievements show of technical progress in the field of Radio and Television. The grand attraction of this Anniversary-exhibition is that of coloured television, the official commencement of which will be the telecasting of the opening celebration on 25th August, 1967. The programme will be simultaneously telecast on both stations (ARD and ZDF).

During the Exhibition a joint coloured programme will be produced by both television stations, which will be receivable on channel 39 in Berlin from 10.00 a.m. till 7.00 p.m. daily. The Exhibition's black and white television programmes of the ARD and ZDF stations will also be telecast over channels 7 (ARD) and 33 (ZDF) from 10.00 a.m. till 7.00 p.m.

The industry will display its newest products, special shows being presented by the German Federal Post, the Electric Handicraft Trade, the German Amateur Radio Club, Lufthansa Airlines and the German Red Cross. A special exhibition concerning the themes "Parallel Ways" (black and white and coloured television), "Stereophony—Hifi" and "Portables" will also be offered. The ARD station and the ZDF station are setting up their studios in the R (Sachsen) and A (Berlin) halls.

In addition, the visitors to the Radio and Television Exhibition will be offered an extensive programme. In the summer garden of the fair grounds, athletic events, variety shows and concerts will be held daily; in the "Palais am Funkturm" fashion shows may be viewed. Theatregoers will be interested to know that the Berlin theatres, in spite of the summer holidays, will be presenting a complete programme; and for those interested in sports, there are also a few events in store. The social highlight of the Exhibition is the ball, which is completely in line with the TV colour theme—A Dance under the Rainbow.

MAKE SURE OF RECEIVING THE RADIO CONSTRUCTOR REGULARLY

Complete and hand in this coupon to your newsagent


Please reserve for me each month THE RADIO CONSTRUCTOR (Published 1st of month).

NAME.....

ADDRESS

.....
(Block Capitals)

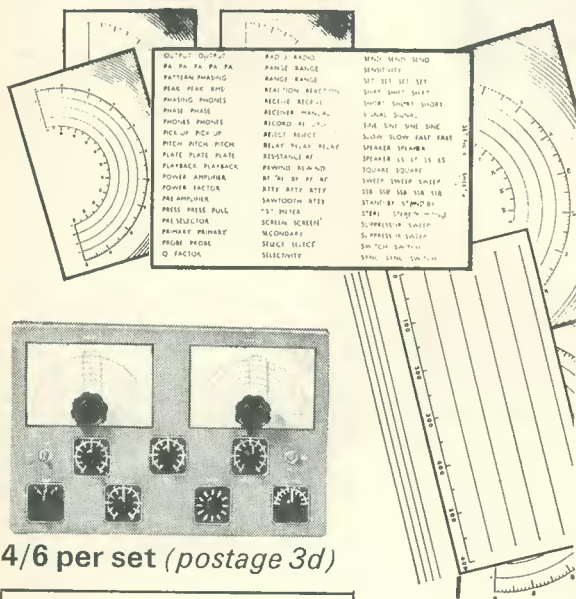YOUR FINISHED ASSEMBLY DESERVES A REALLY PROFESSIONAL FINISH -USE 'CONSTRUCTOR' PANEL SIGNS PERMANENT PAINT TRANSFERS



4/6 per set (postage 3d)

- ★ Set 3 Wording—WHITE
- ★ Set 4 Wording—BLACK
- ★ 6 Sheets, over 1,000 words, etc.
- ★ Set 5 DIALS—clear background
- ★ Set 6 DIALS—black background

Send to:
DATA PUBLICATIONS LTD., 57 MAIDA VALE, LONDON, W.9.

Please send me PANEL SIGNS
I enclose cheque/crossed postal order for

NAME

ADDRESS

.....

.....

BLOCK LETTERS PLEASE



I should like a copy of the Electronics Hobbies Manual. Enclosed is a cheque/P.O. for 10/6.

NAME

ADDRESS

.....

RC8

The radio constructors' greatest-ever components guide!

Over 600 pages packed full of tips, kits and details of over 11,350 different parts from 85 leading manufacturers!

Whatever your particular interest in electronics, you'll find the **Electronics Hobbies Manual** a first-class investment.

It saves you time. No searching around for the parts you need. Every type of equipment—from stock components to sophisticated professional items—is here. Supplied by over 85 leading manufacturers, this equipment is *all* available by mail order on fast despatch.

It aids your projects. Complete designs, and details of kits available for beginners and experts, are all contained in the Manual. Inside, too, there's a wealth of technical data, practical tips and formulae to help you build with confidence.

It costs just 10/6 post free. And it puts the whole electronics industry at your service, including the specialised knowledge of Electronics. Behind this brilliant new venture are the vast resources of STC and ITT, so you're assured of a first-class service!


Be sure of your Electronics Hobbies Manual. Clip the coupon, and send today—while stocks last!
Electronics (Prop. STC Ltd.) Edinburgh Way, Harlow, Essex. Telephone: Harlow 26777.



High-grade components for amateur communications

67/10MG

In your workshop

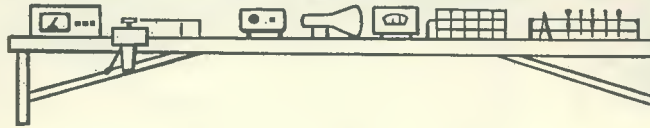

"Ah," SAID SMITHY WITH satisfaction as he mopped his brow, "here's the place."

Tearing his attention from a garish display of seaside postcards featuring ladies of immense and improbable proportions, Dick looked doubtfully at the two doors, flanked by flyblown windows, to which Smithy was now pointing.

The brilliant August afternoon sun shone down and harshly illuminated the pair as they stood on the pavement amongst the cheerful gaily-clad crowds, some intent on going to the beach and others just returning. Resolutely, Smithy pushed open one of the two doors and entered, to be followed by his dubious assistant. Dick blinked for some moments until his eyes, previously attuned to the sunlight glare of the street, became accustomed to the gloom inside. Glancing round he saw about a dozen square tables, each covered with a stained greyish-white cloth and each adorned with a large bottle of chop sauce together with a second sauce dispenser in the shape of a plastic orange. An all-pervasive odour of stale onions hung in the air.

Smithy's Treat

"Cor love us," breathed Dick eventually. "What's *this* dump?"

"Dump?" repeated Smithy,

shocked. "I would have you know that this is the place I was telling you about—where a mate of mine and I came two years ago. We had a good old technical chin-wag together, and an excellent meal in the bargain."

"Trust you," commented Dick bitterly, "to pick a crummy joint like this. When you suggested we should take a day off down at the sea, I was all for it. And when you also said that you'd stand me a meal I was beginning to look forward to something *really* groovy. I certainly didn't expect I'd have to eat in a clapped-out nosher like this."

"Nonsense," replied Smithy briskly.

He walked over to a table, pulled out a chair, sat down and looked about him.

"I see we're nice and early," he remarked. "Which means we've got the whole place to ourselves."

"I'm not surprised," grumbled Dick, sitting down and repressing a shudder as he glanced at the flaking plaster on the walls. "I should imagine that all the people who've eaten here in the past are now down with cholera or bubonic plague."

The scent of stale onions suddenly increased in strength as a door opened. A large lady of forbidding mien, and with a physique reminis-

cent of the sumo wrestlers of Japan, glared at them.

"Yerse?"

"Two teas, please," called out Smithy firmly.

The lady withdrew.

"Hell's teeth," snorted Dick. "Is that to be the meal, then? Two teas?"

"Don't be silly," replied Smithy shortly. "I'm just getting the essentials sorted out first."

"If all you're going to do here," complained Dick, "is swill tea all the time, we might as well have stayed back in the Workshop."

A sudden thought crossed his mind and he brightened.

"Talking about the Workshop," he continued, "reminds me about something you were saying a couple of days ago. About these new integrated circuit things."

"Oh, those," replied Smithy absently. "If I remember correctly, I said that integrated circuits are quite likely to replace many of the standard circuits and components we've got used to in present-day radios and TV's. They're already doing so in computers."

"Yes, that's what you did say," remarked Dick impatiently, "but what you didn't do was explain just exactly what integrated circuits are."

"Integrated circuits," said Smithy in reply, "are devices which comprise an actual circuit, with its circuit elements incorporated in the device itself. These elements can be resistors or capacitors and, in some cases, transistors and diodes as well, and everything is interconnected together within the device to form a working circuit. Integrated circuits have terminations to which you can connect any further external circuits. Most integrated circuits are fantastically tiny, and the manufacture and use of these is usually referred to as 'microelectronics'. But the main point of an integrated circuit is that it is a unit which consists of a *circuit* on its own. You can't break it down into separate circuit elements like you can with a circuit which consists of components assembled on a printed board."

"What are the advantages of integrated circuits?"

"The big advantages," replied Smithy, "are reliability and a potential very low cost. Plus, with certain types, exceptionally small size. One of the reasons for reliability is that, since all the component parts of an integrated circuit are connected together within the integrated circuit itself, the number of electrical joints between them is

considerably reduced. To explain this, let's take an example. We'll suppose that, using conventional components mounted on a printed circuit board, we connect, say, the collector of a silicon transistor to one end of a resistor. Let's now see how many joints there are between the transistor collector and the resistor. Starting at the collector itself, we go from the silicon of the collector to its metallising, and from the metallising to the wire inside the transistor can. The next joint is the one between the wire from the collector to the lead-out wire. That's three joints before we've even left the can. After this you get the following joints: lead-out wire to solder, solder to printed board copper foil, copper foil to solder, solder to resistor lead-out wire, and resistor lead-out wire to resistor composition. That last joint at the resistor will, in practice, probably consist of more than one actual junction but, even assuming that it's a single joint, there are still no less than eight joints in that little lot. A connection between a transistor collector and a resistance element in an integrated circuit of the semiconductor type would involve only two joints."

"Well, that should certainly improve reliability," conceded Dick. "You don't have to be long in the servicing game to realise how many snags are caused by trouble at joints, where the circuit path changes from one conductor to the next. What about the cost and the very small size?"

"The cost," said Smithy, "is reducing all the time as manufacturers carry out further research and improve production methods. Don't forget that initial tooling and development costs for integrated circuits are high, and that this fact is liable to be reflected in the earlier designs. To get a low price for any mass-produced article you have, of course, to make it in large quantities, which means that you've got to find a market for it. Most of the present integrated circuits are going into computers, although a few are already finding their way into the entertainment market, in radios and in TV sets. Once integrated circuits really break the price barrier and become obviously cheaper than present-day circuits with their separate components and assembly costs, you and I, Dick, will be seeing stacks of them!"

Dick frowned.

"I used to think that that's what would happen with transistors replacing valves," he remarked. "But it's taking a dickens of a time for

transistors to completely oust valves in TV sets, for instance."

"True enough," agreed Smithy. "Although TV does represent rather a special case, with its well-established valve circuits and techniques. However, the step from transistors to integrated circuits is not so big as that from valves to transistors. Current TV transistorised design lends itself well to the use of integrated circuits in the i.f., a.f. and timebase oscillator sections. But I'm getting ahead of myself now, because you don't really know what integrated circuits are, anyway."

Thin-Film Circuits

"I don't," agreed Dick. "As you may have gathered from what I've been saying, I haven't the vaguest idea about how they're made or what they do."

"Fair enough," said Smithy. "It looks as though I'll have to give you a bit of background on them, then. I'm not going to go into any great detail, but what I'll tell you should enable you to understand some of the terms that are used, and help you to follow the more detailed references you'll encounter in technical articles and things like that."

At that moment the door opened and the large lady appeared, bearing two cups of tea. She deposited them upon the table, then turned to another to pick up a card, which she also placed in front of Dick and Smithy.

During this brief period, Smithy, used to enormous quantities of tea in the Workshop, had already

emptied his cup, and he handed it back to the lady.

"Let's have another cup," he said cheerfully. "We'll be ordering in a minute."

The woman frowned and cast a sudden quizzical glance at Smithy. However, she said nothing, picked up his cup and retired to her onion-saturated limbo behind the door.

"That's better," said Smithy, wiping his mouth. "Now, let's return to these integrated circuits. There are three main types of integrated circuit, these being the thin-film integrated circuit, the thick-film integrated circuit and the semiconductor integrated circuit. The last one is also known as the silicon integrated circuit. We'll do the thin-film and thick-film circuits first because these are the easiest. I won't be able to deal with the semiconductor integrated circuit this time, so I'll leave that for a later date."

Smithy paused for a moment to collect his thoughts.

"Now, the thin-film circuit," he went on, "consists of a substrate, which is usually ceramic, on to which the circuit elements are deposited."

"Hold on a minute!" interrupted Dick. "What's a 'substrate'?"

"It's the bottom layer of material on which the other bits of the circuit are built," explained Smithy, "and it provides the mechanical strength for the circuit. As a rough analogy you could say that, when you put butter on toast, the toast is the substrate. High conductivity

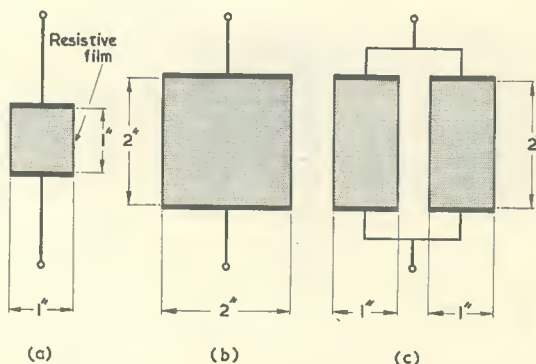


Fig. 1 (a). A square of resistive film measuring 1in by 1in. Connections are made to the entire length of opposite sides
(b). The same resistance is given if the size of the square is increased to 2in by 2in
(c). The larger square can be split into two 2in by 1in rectangles. Being twice as long as the 1in by 1in square each rectangle has twice its resistance. Since the rectangles are effectively in parallel in the larger square, its total resistance then becomes the same as for the 1in by 1in square

metals such as gold or aluminium, or resistance alloys such as nickel-chrome, are deposited on to the surface of the substrate to provide the interconnections between circuit points, or to provide resistors. This process has to be done in a vacuum and one way of depositing the metal consists of having the metal evaporate close to the substrate, the latter having a mask in front of it which acts like a stencil. Since the metal is evaporated in a vacuum, the molecules of metal which boil off travel in straight lines. Those that pass through the mask fall on to the substrate and cool there, whereupon you have a metal deposit, or film, on the substrate which follows the pattern of the mask. Obviously, the high conductivity metal and resistance alloy deposits have to be made at different times and with different masks."

"I see," said Dick. "This means, then, that you can produce thin-film integrated circuits by suitable masking and depositing processes, these circuits having patterns of conductive and resistive material on them which represent resistors and the interconnections between them."

"That's right," replied Smithy. "The account I've given of the process is simplified, but what I've told you is the basic idea."

"How," asked Dick, "do you get different values in the resistance bits? Do you use different types of alloy?"

"Not generally," replied Smithy.

"The main approach with thin-film circuits is to use a standard alloy and thickness of deposited film, and to change the outline of the resistance section deposited on the substrate. This enables all resistor elements to be deposited in one operation. A nickel-chrome film can, for instance, be deposited at a thickness which gives, say, 250Ω per square."

" 250Ω per square what?"

"Per square nothing," replied Smithy. "Just 250Ω per square."

"Dash it all, Smithy," protested Dick. "You can't just say ' 250Ω per square'. It's got to be 250Ω per square inch or square centimetre, or something like that!"

"No, it hasn't," said Smithy. "Just hang on a jiffy and I'll show you."

The Serviceman pulled out a ball-point pen and proceeded to apply it to the tablecloth in front of him.

"If," he continued, "you have a film of resistive material with a square outline and having the same thickness at all points, and you connect to the entire length at opposite edges, you will get the same resistance regardless of the size of the square. Say, for instance, you've got a square which is 1 inch by 1 inch. (Fig. 1 (a)). If you increase the size to 2 inches by 2 inches (Fig. 1 (b)) you'll still get the same resistance. The new square is equivalent to two rectangles measuring 1 inch by 2 inch connected in parallel. (Fig. 1 (c)). Each of the two rectangles has the

same width and is twice as long as the original 1 inch by 1 inch square, and so it will have twice the resistance. But the two rectangles are in parallel in the larger square and so the total resistance is the same as for the original square. This analysis can be applied to any size of square, and it will always prove that you get the same resistance between two opposite edges. Fascinating, isn't it?"

"I'll say," agreed Dick. "So, to get different values of resistance, you start off with a fixed number of ohms per square and then use different shapes of rectangle."

"That's the idea," confirmed Smithy. "If you want a 500Ω resistor and the film you deposit gives 250Ω per square, you arrange the mask pattern so that the deposit is a rectangle which is twice as long as it's wide. (Fig. 2 (a)). This means that the resistor consists of two squares in series. Regardless of the actual dimensions, you'll always get 500Ω if the length is twice the width. For $1,000\Omega$ the length must be four times the width, (Fig. 2 (b)), whereupon you've got four squares in series. For higher resistances you need a longer rectangle, whereupon you fold it around a bit, so that it doesn't take up too much space." (Fig. 2 (c)).

"Well, blow me," said Dick. "That's neat, isn't it? What about capacitors?"

"To get capacitors with the thin-film process," said Smithy, "the usual approach is to use a sandwich construction. One plate consists of metal deposited direct on to the substrate, after which a layer of insulating material is deposited on top of it. (Fig. 3). Silicon dioxide is a suitable material and this forms the dielectric of the capacitor. A further metal deposit on top of the silicon dioxide then gives the second plate, whereupon your capacitor is complete. This basic procedure can produce capacitors having values ranging from a few pF up to $0.03\mu\text{F}$ or so."

No Inductors Or Transistors

At this moment, Smithy's eye fell on the card which the lady of the establishment had placed on the table.

"Blimey, Dick," he said, "we'd better start ordering. What'll you have?"

Dick, brought forcibly back from the world of integrated circuits to his present surroundings, gazed with a marked lack of enthusiasm at the dog-eared card in front of them. This, under the brave heading of "The Commodore Restaurant",

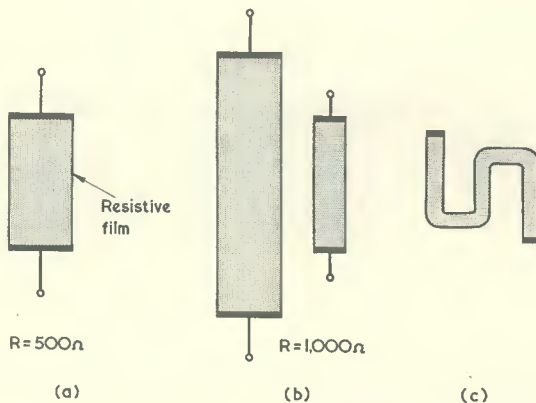


Fig. 2 (a). A rectangle whose length is twice its width. With a resistive film of 250Ω per square, the resistance of the rectangle is 500Ω
 (b). Two rectangles, both having a length which is four times the width. Despite the difference in actual dimensions, both rectangles exhibit a resistance of $1,000\Omega$
 (c). When a long rectangle of resistive material is required on a thin-film or thick-film circuit, the rectangle may be folded, in the manner shown here, to conserve space

outlined the delights of the establishment in an uneven typescript which, in places, was obscured by cigarette burns, blobs of solidified gravy and, in the lower right hand corner, an irregular contour of what appeared to be fossilised cabbage.

"Let's see now," said Smithy brightly, as he scanned the items listed on this noisome tablet. "Would you like sausage and chips, egg and chips, or bacon and chips? Or, again, you can have sausage, egg and chips, or bacon, egg and chips, or sausage, bacon and chips."

"That's a charming choice, I must say!"

"Oh, I don't know," replied Smithy. "I always feel there's nothing like a bit of variety in a menu. Lower down, now they've got the same things but with beans."

"Haven't they got any food?"

"Really," commented Smithy, profoundly offended, "that's hardly the attitude of a guest. You'd better look for yourself."

Dick took the menu from Smithy, and a look of increasing horror spread over his face as he examined the remainder of the items listed.

"'Liver and chips'," he read out.

"Cor blimey, we've got 'liver, bacon and chips' next and then they go through the permutations all over again with 'liver, sausage and chips' and 'liver, egg and chips'. Below 'liver, egg and chips' they've got 'mixed grill and chips'. I suppose that's the bits listed above all laid out on one plate."

"That's right," said Smithy appreciatively. "Mixed grill and chips was what I had last time I was here. I got liver, bacon, egg, sausage, beans and chips all together. Smashing it was."

"Ye gods," broke in Dick. "What's this? *Chipatty* and chips?"

"I don't know what that's like," confessed Smithy. "I usually avoid the foreign dishes."

"I'm not surprised," said Dick, still studying the list. "Right at the bottom of the menu they've got what they call 'Speciality of the House'. It's '*Chipatty*, shish-kebab, mixed grill and chips'. Blimey, that *would* be something!"

"Shall I order it for you?"

"No thanks," said Dick hurriedly. "Ask them if they'll do me a fried-egg sandwich."

"A fried-egg sandwich?" snorted Smithy. "What are you trying to do, show me up or something?"

The door opened and Smithy quickly moved the menu-card so that it covered the sketches he had scribbled on the tablecloth. Orders were placed. Smithy asked for his mixed grill and chips, whilst Dick

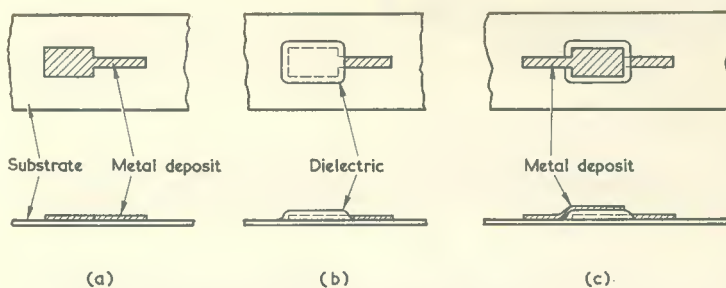


Fig. 3 Simplified diagram illustrating, by top and side views, the manner in which a capacitor may be formed on a thin-film or thick-film circuit. For purposes of illustration film and dielectric thicknesses are shown much greater than would occur in practice, and the dielectric outline may vary in actual circuits. In (a) the first metal deposit provides the bottom plate of the capacitor, whilst the dielectric is added in (b). The second plate is deposited in (c), giving the complete capacitor. The extensions on each metal deposit allow interconnection to other circuit elements

eventually, and with very great reluctance, chose sausage and chips. The lady returned to her regions, once more carrying Smithy's empty cup for replenishment.

"Let's get back to those thin-film circuits," said Dick. "From what you've told me it's possible to make up circuits on them using resistors and capacitors."

Smithy nodded in agreement.

"What," asked Dick, "about inductors?"

"Inductors," replied Smithy, "can be made up by depositing spirals of metal on the substrate, these working in the same way as the spirals which make up the inductors in printed circuit biscuits for TV tuners. But the inductances obtained are too low to be of much use in practice and, inductors are normally avoided in the initial design of the circuit."

"What about transistors and things like that?"

"So far as I know," said Smithy, "it isn't possible as yet to produce truly integrated transistors in a thin-film assembly. Manufacturers haven't been able to build up practical transistors with deposits of material using basic thin-film processes, although it seems that research is still pressing on in this direction. But you can add a transistor to a thin-film circuit in the form of a flip-chip."

"A what?"

"A flip-chip."

"Corluvaduck," commented Dick. "Talk about chips with everything! We couldn't get away from chips in that menu and stap me if they don't now come up in integrated circuits!"

"Don't let it worry you," chuckled Smithy. "To start off with, a 'chip' is a flat tiny square of silicon in which a transistor, or other component, has been formed. You can even have a second integrated circuit in the chip, but how that is done I'll have to leave till our next gen-session together. All I'll say now is that a thin-film circuit can be laid out so that the terminations of a chip, laid face downwards on the substrate, can be soldered or otherwise connected into the thin-film circuit. A chip used in this manner is then called a 'flip-chip'. I should add that flip-chips can also consist of diodes, capacitors or any other device which can be built up on a chip. Sometimes, it is preferred to add capacitors as flip-chips instead of having them in the thin-film circuit itself."

Smithy took a large draught from his cup.

"And that," he said, "should give you a general basic idea of thin-film integrated circuits. They consist of a composite structure which is complete with resistors, and capacitors if desired, and to which you can add further components such as transistors by the flip-chip technique. When a thin-film circuit has been made up, it is covered in some sort of plastic resin to keep it protected. The sizes of thin-film integrated circuits vary quite a bit. Some may be quite large affairs having a side of about an inch or so, whilst others are a lot smaller. They are, of course, made in quantity. A large number of thin-film circuits, each with its own mask, will pass through each of the depositing processes together."

Thick-Film Circuits

"What," asked Dick, "about thick-film integrated circuits?"

"Apart from the way they're produced," replied Smithy, "thick-film circuits are basically similar to thin-film circuits. The film deposited on the substrate is thicker than with the thin-film circuit, hence the names given to the two different types. Thick-film integrated circuits have the great advantage that they don't need a vacuum for the conducting or resistive layers to be deposited on to the substrate. This makes the manufacturing process simpler and less expensive. It is also said that thick-film circuits are physically stronger than thin-film circuits."

"How are the film deposits made?"

"By a sort of screen printing process," replied Smithy. "Over the substrate you have a mask or screen which acts like a stencil and allows, to continue the printing analogy, specially prepared 'inks' to be printed on the surface of the substrate. The substrate is, once again, usually ceramic. The result of the printing process is that you get an 'ink' pattern on the substrate which corresponds to the pattern imposed by the mask. The substrate is then heated, whereupon the 'ink' changes to a conducting or resistive path, as required. To provide a conducting path the 'ink' could consist of gold or silver powder dispersed in a fluid which gives the mixture the liquid properties needed for application. When fired, the liquid evaporates and you have a deposit of metal left on the substrate. For resistance, the 'ink' can contain a resistive mixture instead of a highly conductive metal. Another advantage with the thick-film circuit is that, by varying the resistive mix, you can get a wider range of resistance values than with the thin-film process. With thick-films you can obtain resistances well in excess of $1M\Omega$."

"Any other differences?"

"Speaking," replied Smithy, "in the simple basic terms we've been using today, there aren't many more. As with the thin-film circuits, thick-film circuits are limited to conductors, resistors and capacitors in the

integrated circuit proper. Alternatively, capacitors can be added as flip-chips. Transistors and other devices which can be made up on a chip can also be added as flip-chips."

Smithy Was Here

"I must say that all this seems very far removed from the sort of stuff we normally handle," commented Dick. "Still, I suppose that if you can get all the resistors you need for, say, a transistor stage into a thin-film or thick-film integrated circuit, after which you only have to add a few other components as flip-chips, you *must* have something which is, if nothing else, a lot smaller than the same thing using individual resistors, capacitors and semiconductors."

"True enough."

"How," asked Dick, "do you connect the integrated circuit into the main circuit into which it is incorporated?"

"In the same manner as any other small component," replied Smithy. "You have lead-outs which protrude through the protective covering of the circuit."

Smithy paused.

"Now don't forget," he went on, "that I've only given you half the story concerning integrated circuits. The most exciting types are the ones which use a semiconductor substrate, and you can actually build transistors *into* these! The two-joint connection between a transistor collector and a resistor which I mentioned at the beginning is typical of what you get with a semiconductor integrated circuit. But I'll have to leave semiconductor integrated circuits until the next time we have a gen-session together. Hallo, it looks as though our order's coming."

Again, the door opened. The large lady appeared with a tray bearing two plates and Smithy's teacup. Helpfully, Smithy moved the menu-card out of the way, whereupon she placed the tray on the table with a resounding crash. Surprised, Smithy looked up to find himself gazing at a censorious finger.

"I *knew* as 'ow it was you," said the woman accusingly. "As soon as

you started to get me traipsing back and forth with cups of tea, I knew as 'ow it was you."

For once, Smithy was completely dumbfounded. His mouth opened and closed silently, like a goldfish after the ant-eggs have been dropped in.

"Two years ago," continued the woman aggressively, "you was in 'ere. Wasn't you?"

Dumbly, Smithy nodded.

"I *knew*," said the woman triumphantly. "Drinking tea like an 'orse you was then, just as you are now. And wot did I find after you'd gone?"

"I don't know," stammered Smithy. "What did you find?"

"The same as I've found now," snorted the woman pointing a scornful finger at the table and Smithy's diagrams. "Our best tablecloth all covered over with ink scribbles, like this one 'ere is. We 'ad to buy a new cloth last time to replace it and it looks like we'll 'ave to buy a new one again now. So, mate, when you pays yer bill, you can also fork out for two ruined tablecloths as well."

Outraged indignation caused her to rise to even higher standards of contumely as she glared at the hapless Serviceman.

"Dead common you day-trippers is," she pronounced with finality. "There's *walls* for the likes of you to scribble on!"

After which statement the lady stationed herself forbiddingly at the entrance, thereby barring any possible escape. Thus entrenched, she glowered at the now completely demoralised Smithy, as he floundered through his mixed grill without even the benefit of a fourth cup of tea.

When, later, the pair came blinking into the harsh sunlight of the street, with Smithy the poorer by the price of two meals and two tablecloths, Dick felt that his best approach under the circumstances would be to thank Smithy quickly and quietly for the food he had provided.

He decided, wisely, not to thank Smithy for the entertainment that had gone with it.



EMI TV FOR NEW ZEALAND

EMI Electronics have been awarded a contract for the supply of complete video equipment for the New Zealand Broadcasting Corporation's latest News Studio in Hamilton, North Island.

The installation includes two of the popular Vidicon Cameras type 201 fitted with Angenieux zoom lenses, a complete production vision mixer using the latest EMI solid-stage technique with vertical interval switching, telecine, pulse and video distribution systems, and EMI's newly developed solid-state monitors. Installation will be carried out by N.Z.B.C.'s own engineers and the Studio will be operational by late 1967.

Radio Topics

By Recorder

IT'S ALWAYS THE COBBLER'S CHILD who is the worst-shod.

This adage is, of course, intended to emphasise the point that the only work that a tradesman can't find time for is that which exists in his own home. For instance, a self-employed painter and decorator friend of mine who alternates between indoor and outdoor work (you can always tell when he's on an outdoor session because that's when the rain starts) has been nagged by his wife for as long as I can remember to re-decorate their front room. It's just human nature to put off any outstanding spare-time jobs which show no profit and which involve no change from normal work.

Cobbler's Confessions

Rather to my surprise, I find that I fall into the cobbler category with the precise fit of the proverbial square peg in its square hole. In my own den-cum-workshop, which is pretty well full to the brim these days with radio parts, chassis, books and publications, I rely for occasional sound radio broadcasts of background music or news bulletins on an f.m. tuner I knocked up way back in 1955. It's a completely home-built design using an r.f. pentode, double-triode oscillator and mixer, two i.f. pentodes and a ratio discriminator incorporating a couple of GEX34 diodes. That tuner was the apple of my eye after I'd made it but, as happens so often with these things, it became more and more neglected and forgotten as later projects captured my attention. For many years now, if no other radio has happened to be available

I'd switch it on and see the heaters of its valves glowing through the dust. The a.f. amplifier which follows the tuner tells a tale of even more shameful abuse. This is a unit I made a long time before the tuner, and it now struggles away to give a travesty of its previous performance.

Nevertheless, these two Old Faithfuls have been pressing on, whenever called upon, to provide me with the odd radio programme. But the performance of the tuner has gradually been deteriorating and I suddenly realised a month ago that it couldn't raise sufficient output to provide even background music. Following the example of the cobbler I put off doing anything about it for several weeks, then I finally decided that I should at least give the tuner a quick look-over before I finally discarded it for something more modern with a few transistors in it.

As I shall now recount, the look-over and complete repair took exactly fifteen minutes! A very quick check with the testmeter showed that all the anodes and screen-grids were getting a reasonable h.t. voltage and so I coupled the signal genny up to the grid of the mixer. A little of its (supposed) a.m. modulation became audible from the speaker as I swung the generator around 10.7 Mc/s. It is pointless to attempt the alignment of an f.m. i.f. strip on results from the speaker and so I next coupled the testmeter across the discriminator stabilising electrolytic capacitor. By dint of screwing up the signal genny to full output and switching the testmeter to its lowest voltage range

Your Local Supplier

LONDON AREA

Established 1910

H. L. SMITH & CO. LTD.

Comprehensive stocks of components
by all leading makers.

287-9 EDGWARE ROAD
LONDON W.2

Tel: 01-723 5891

THE MODERN BOOK CO.

Largest selection of English and
American radio and technical books
in the country.

19-21 PRAED STREET,
LONDON, W.2

Tel: PADDington 4185/2926

CRESCENT RADIO LTD

North London's electronic centre.
Quality components at competitive
prices.

Transistors, Diodes, Valves,
Speakers, Resistors, Condensers,
Cables, Plugs and Sockets, etc., etc.

40 MAYES ROAD,
WOOD GREEN,
LONDON, N.22

TELERADIO ELECTRONICS

For Radio Control Devices, Miniature
components, Special Transistors,
Circuits and data on boat and
aircraft control.

(S.A.E. Enquiries REF. D/P)

325/7 FORE STREET,
EDMONTON (3719)
LONDON, N.9.

Your Local Supplier

LONDON AREA

G. W. SMITH & Co (Radio) Ltd.

3-34 LISLE STREET,
LONDON, W.C.1.
Tel. GERrard 8204/9155
Open 6 days a week

CATALOGUE

Over 150 pages of electronic components, test, communication and Hi Fi Equipment. Fully illustrated. 5/- p & p 1/-

ELECTRONICS GALORE!

in the NEW

dca CATALOGUE

Send 1/6 now for your copy
to: DEPT. R/C

dca ELECTRONICS LIMITED

28 UXBRIDGE ROAD,
EALING, W.5

WHY BI-PAK?

FOR SEMICONDUCTORS

- ★ Fastest by return mail service
- ★ Lowest possible prices
- ★ Largest range available
- ★ Satisfaction guaranteed
- ★ For further proof see page 5

BI-PAK SEMICONDUCTORS

8 Radnor House,

93/97 Regent St., London W.1

ESSEX

MARKET CENTRE

For Semiconductors

Prompt, efficient mail order service for Mullard, Newmarket, Texas, Sinclair, S.T.C., Fairchild Semiconductors. We also offer a comprehensive selection of miniature components for transistor circuitry. Catalogue 1s.

L.S.T COMPONENTS

23 New Rd., Brentwood, Essex

I got a slight movement in the needle. All over the range from about 10.2 to 11.5 Mc/s!

Out came the insulated core adjuster and, with the generator set to the correct i.f. of 10.7 Mc/s, I tackled the i.f. transformers. One core needed about two turns, another needed about three turns and, almost before I realised what was happening, I had to start attenuating the signal generator to keep the testmeter needle from bashing away at its end-stop. A final quick run-through up to the primary of the discriminator transformer took hardly any time at all. The set has a balanced discriminator, so I next coupled the testmeter between chassis and the audio take-off point. The holes and electrons in those old GEX34's must have wondered what had hit them as the diodes started passing the first sizeable currents they'd experienced for years. But they proceeded to give of their very best, and a touch on the discriminator secondary core was all I needed to achieve the delightful situation where the voltmeter needle went nicely and linearly in one direction as I swung the signal generator frequency up, and just as nicely and linearly in the other direction as I swung the signal generator frequency down.

All that now remained was to disconnect the signal generator and hitch on the aerial. And hurriedly turn down the gain of the a.f. amplifier as the local signals came belting in.

Marvellous, isn't it? I had nearly been on the point of ditching that old tuner, when all it needed was an adjustment to six cores! I must confess that I'm at a loss to understand why the i.f. trimming had drifted off all that much. The i.f. coils were home-wound and, perhaps, the dope I had used fairly liberally to hold them in position had decided to change its electrical characteristics over the last decade or so.

Being now the proud owner of an f.m. tuner having an excellent performance I'm turning a questioning eye on the a.f. amplifier which follows it. This venerable piece of equipment once sported two 6V6's in push-pull in the output stage but it now runs on one only, the other valvholder remaining vacant. Once, the amplifier developed a crackle which cleared when one of the 6V6's was removed, and I left it "temporarily" with only half the output stage operative until I could find the time to look at it properly. That would be about five years ago now, so I suppose

I'll get round to it one of these days.

One comforting thought arises from this shocking maltreatment of my own gear. If ever there's a dearth in electronics I've got all the qualifications to start up my own shoe repairing business.

Microelectronics Gag

As the silicon integrated circuit engineer remarked resignedly when, after a busy day's work on n-type diffusions, his wife asked him to change the baby: "Ah well, it is at least a different polarity."

Multiple Transistors

I note, from an article appearing in the July issue of our American contemporary *Electronics Illustrated**, that some of the importers of transistor radios into the U.S.A. aren't playing exactly fair. The radios in question are pocket types sold usually at low cost as "loss leaders", and are advertised as being 14-transistor, 15-transistor or 16-transistor models. The claimed multiplicity of transistors may cause an unwitting member of the public to make a purchase in the hope of obtaining superior performance but, in fact, the sets work no better than normal models using about 7 or 8 transistors.

Electronics Illustrated checked a number of the receivers in question. In some the additional transistors did appear in the receiver circuit, although any advantage given by their presence was problematic. Whenever a diode was required a transistor was fitted instead, one of its junctions functioning as the diode. Also, the a.f. and output stages of these radios had many more transistors than would appear in a normal set. In one receiver, for instance, a group of four diode-connected transistors in series-parallel operated presumably as a temperature dependent resistor for the control of output transistor bias.

Other receivers were worse. In these, about half the transistors fitted to the board were not in circuit at all. On the underside of the board their leads were merely soldered to each other and to nothing else.

In this country we don't seem to be suffering from this type of consumer exploitation. It is not unknown, incidentally, for a British manufacturer to use a transistor junction as a diode, but this approach is more probably intended to obtain a specific performance with relation to temperature or to

*H. M. Gregory, "The Transistor Radio Scandal", *Electronics Illustrated*, July 1967

use up surplus transistor production than as an excuse for obtaining an increase of one in the transistor count.

Nevertheless, it is worth-while keeping a watchful eye open to ensure that radios which claim excessive quantities of transistors do not make their appearance here. Judging from the American experience, it will be imported radios which are advertised in this manner.

Negative Ions

Negative ions are good for you.

This is the view of a group of medical researchers who contend that people subjected to a field of negative ions in the air become very much invigorated as a result. Investigations into this effect have been carried on for many years, notably in Russia, and recent newspaper reports have referred to ionising devices for installation in offices or homes. So far as one can judge from the reports, these devices work by applying a high voltage, negative of earth, to a needle which then proceeds to ionise the air around it. In consequence, the inhabitants of the office or room become stimulated by the ions which are generated by the device.

Positive ions, on the other hand, are stated to have a depressing effect. Which, at long last, solves a

problem which has baffled me for ages: why are regular television viewers so apathetic and lethargic? The answer is now, of course, quite obvious. The high voltage e.h.t supply to the TV receiver picture tube is positive with respect to earth, with the consequence that all the viewers around the set are being continually sprayed with excessive quantities of dejection-causing positive ions.

In oscilloscopes whose cathode ray tubes require a fairly high e.h.t. voltage, a conventional approach consists of having the final anode only slightly positive of chassis, the requisite e.h.t. being then applied, *negative* of earth, to the tube cathode. I now propose that this approach be employed for all future TV sets as soon as the necessary design work can be carried out. Following oscilloscope usage, these sets should have a negative e.h.t applied to the cathode group of components for the tube instead of a positive e.h.t to the final anode, whereupon viewers will not only obtain pleasure and entertainment from the programmes displayed but will also be bathed in an atmosphere rich in negative ions, with the result that a session of television viewing will leave them rejuvenated, revitalised and reinvigorated!



FURTHER TV TRANSMITTING STATIONS FOR BBC-2

The BBC welcomes the announcement by the Postmaster General that he has approved in principle the following further group of high power UHF transmitting stations for BBC-2.

Carmarthen, Blaen-Plwyf (Cardiganshire), Dorset, Rosemarkie (Inverness), Caldbeck (Cumberland), West Cornwall, Selkirk, Herefordshire, Ayrshire, North Kent, Stockland Hill (East Devon), Presely (Pembrokeshire), South Devon, Arfon (Caernarvonshire), West Sussex, and Dumbarton.

These 16 additional stations will serve some 2½ million people and together with the 28 high power stations already approved will make BBC-2 available to 90% of the population of the United Kingdom.

A number of low-power BBC-2 relay stations are being built to fill in the gaps in the coverage of the main stations caused by the screening effect of high ground. Four of these relay stations are already in operation in the London area, and a further three in the Midlands. Some twenty relay stations in the Midlands, the North of England and in South Wales have so far been approved, and the majority of these are under construction. Relay stations in the West of England and in Northern Ireland are also planned. It is hoped to bring most of them into service during 1967 and the first half of 1968.

All these BBC-2 stations will be capable of transmitting the colour programmes.

'BASIC OSCILLOSCOPE'—JULY issue

With reference to the above article the VCR139A cathode ray tube specified is also available from Henry's Radio Ltd., 303 Edgware Road, London, W.2.

Your Local Supplier

LANCASHIRE

BERWICK ELECTRONICS LTD.

Stockists of radio components for the constructor. Cabinet coverings—Tygan, Vynair, Metal Fret etc.


100 Tib Street, Manchester 4
Telephone Blackfriars 4416

NEW CROSS RADIO

Electronic components and Equipment,
Transistor Panels,
all at competitive prices

6 Oldam Road, Newcross
Manchester 4
Telephone CEN 1541

SURREY

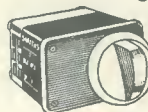

SMITHS PRECISION
6 MINUTE DELAY
ACTION SWITCH

Clockwork actuated

10/6 EACH
Post 2/6

(3 or more post free)

Separate switching up to 6 mins. Each action for loading up to 15 amps. 250 volts. For photographic timer, sequence switching operations, etc., etc. Brand new units at a fraction of their value. Connection sheet supplied.

Radio Component Specialists

337, WHITEHORSE ROAD,
WEST CROYDON, SURREY

THO 1665

LIST 1/-

SUSSEX

E. JEFFERIES

For your new television set,
tape recorder, transistor radio,
and hi-fi equipment.

PHILIPS, ULTRA, INVICTA, DANSETTE,
MASTERADIO, PERDIO, MARCONI,
PHILCO, FIDELITY.

6A Albert Parade,
Victoria Drive,
EASTBOURNE SUSSEX



Happy Families

These are the times when Simon and Clare know that it has all been worthwhile. But they know too that such moments of happiness are only complete when there is also a feeling of security for the future. And Simon's "Family Unit" Policy with the "Yorkshire" guarantees them *all* a future - if the worst should happen.

Happiness in *your* family too—but for how long? If you or *your wife* should die, how would the rest of the family fare? A Yorkshire "Family Unit" policy provides for both these eventualities in a comprehensive way at a sensible premium. Just ask for a leaflet at your local "Yorkshire" branch and then see the manager. He'll be glad to tell you why . . .

it's YORKSHIRE for INSURANCE

THE YORKSHIRE INSURANCE COMPANY LIMITED
 Chief Offices: Rougier Street, YORK
 and Becket House, 36-37 Old Jewry, LONDON, E.C.2.

Branches and Agencies throughout the world

Please send me details of the Family Unit Policy, without obligation.

Name.....

Address.....

J.B.

SMALL ADVERTISEMENTS

Use this form for your small advertisement

To: The Advertisement Manager, Data Publications Ltd., 57 Maida Vale, London, W.9
Please insert the following advertisement in the issue of THE RADIO CONSTRUCTOR

16 words at 9d.
= 12/-

ALL WORDING
IN
BLOCK LETTERS
PLEASE


I enclose remittance of being payment at 9d. a word. MINIMUM 12/-.
Box Number, if required, 2/- extra.

NAME.....

ADDRESS

Copy to be received four weeks prior to publication. Published on the 1st of every month

BE TRANSISTOR-WISE !

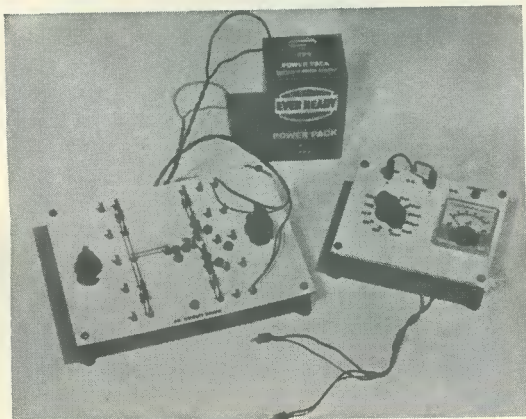

Our course of 20 experience-packed transistor experiments imparts perfect understanding! No theory! Easy-to-follow instructions! Common emitter, common base, emitter follower operations; current, voltage and power amplifications; switching transistors; temperature effects; leakage currents, etc., etc. Germanium and silicon pnp and npn transistors.

AB TRANSISTOR CHARACTERISTICS KIT including Circuit Board, but less 9 volt battery **£5.10.0**

METER KIT: 50 μ A—50mA, 50mV—50V, 20,000 o.p.v. **69/6**
Also **BASIC TRANSISTOR CIRCUITS KIT** **85/-**

Write for FREE DETAILS to:

Electronic Experiments
Brinklow, RUGBY.

QUALITY-QUANTITY TRANSISTORS

DISCOUNT PRICES (in brackets) for FIVE OR MORE OF SAME TYPE.

First grade, no surplus. Data and circuits supplied.

B-5000	10/- (9/-)	2N3705	4/3 (4/-)	HK101 (ME101) hfe =
BC107	5/6 (5/-)	2N3707	5/6 (5/-)	30-60 2/- (1/9)
BC109	5/- (4/6)	2N4058	7/- (6/-)	50-100 2/3 (2/-)
2N2926 hfe =		2SB197	2/- (1/9)	90-180 2/6 (2/3)
55-110	3/- (2/9)	GET693	1/6 (1/3)	150-450 3/- (2/6)
90-180	3/3 (3/-)	HK041 (PNP) hfe =		HK301 (ME301) hfe =
150-300	3/6 (3/3)	20-60	2/6 (2/3)	20-60 2/- (1/9)
235-470	3/9 (3/6)	50-100	2/9 (2/6)	50-100 2/3 (2/-)
2N3702	4/3 (4/-)	90-180	3/- (2/9)	90-180 2/6 (2/3)
2N3704	4/6 (4/3)	160-600	3/6 (3/-)	150-450 3/- (2/6)

RECTIFIERS. IS557 Silicon wire-ended 800piv, 0.5A 3/6 (3/-)
Min. 30V selenium bridges. 150mA 4/-, 700mA, 7/-.

TRANSISTOR OF THE MONTH — HK101

"Amazing value", writes one of our customers. It's not surprising. What other h.f. silicon Planar with such performance sells at 2/- — 3/-? Low feedback capacitance (2pF), 200Mc/s cut-off frequency, useful Ic range 0.5-20mA, VCEomax. 20V. Use it for your r.f., f.c., and i.f. stages up to 30Mc/s. Amatronix graded gain groups simplify circuit design.

KITS AND PACKAGES

9V, 80mA Battery Eliminator Kit. Builds into PP6 space. 17/6.

Miniature Amplifier Kit. Convert your headphone set to speaker with this efficient transformerless complementary Class B circuit. Operates 3-12V, either polarity. State voltage when ordering. Only 13/-.

Simple TRF Package. Transistors only. (4 matched planars) for easy sensitive MW/LW TRF. 3V operation, outstanding component economy. Only 11/-.

Fairchild AF10 Package. 5 planars, 2 diodes, with makers' cct. & hints on building 10W amplifier. SEPP transformerless Class B. 40V wkg., 15 Ω load, 2% max. dist., 30-30,000 c/s. 30/-.

C.W.O. Mail order only. UK post paid over 5/- List 3d.

AMATRONIX LTD.

396 SELSDON ROAD, CROYDON, SURREY, CR2 ODE

THE RADIO AMATEUR OPERATOR'S HANDBOOK

Data Book No. 6

- ★ AMATEUR PREFIXES
- ★ AMATEUR CODES
- ★ LOCAL TIME CONVERSIONS
- ★ OPERATING TECHNIQUE
- ★ FREQUENCY/WAVELENGTH CONVERSION TABLES
- ★ POST OFFICE REGULATIONS

Many other essential items

64 PAGES Only 5'-

POSTAGE 5d.




SHORT WAVE RECEIVERS for the BEGINNER

Data Book No. 14

This book has been specially prepared for the beginner interested in short wave receiver construction and operation. **FEATURES** the "NIGHTRIDER" 5/7 valve communications receiver. Altogether 8 versions of 4 basic receiver designs, 2 of these including step-by-step building instructions. *Contents also include:* Introduction to the Short Waves; Soldering Notes, etc. Introductory chapter gives much information on the Short Wave Spectrum, Clubs, QSL'ing, Aerials, Amateur & Broadcast Band Listening, Frequencies, etc.

72 PAGES Only 6'-

POSTAGE 6d.

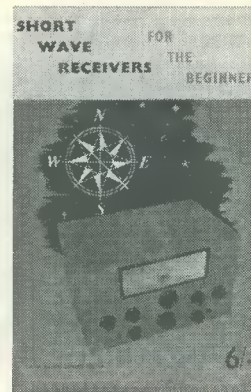

Essential for the Short Wave Enthusiast

TO DATA PUBLICATIONS LTD 57 Maida Vale London W9

Please supply.....copy(ies) of "Radio Amateur Operator's Handbook", Data Book No. 6.

.....copy(ies) of "Short Wave Receivers for the Beginner", Data Book No. 14.

I enclose cheque/crossed postal order for.....

NAME.....

ADDRESS.....

BLOCK LETTERS PLEASE

SMALL ADVERTISEMENTS

Rate: 9d. per word. Minimum charge 12/-
Box No. 2/- extra.

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of advertisers. (Replies to Box numbers should be addressed to: Box No.—, The Radio Constructor, 57 Maida Vale, London, W.9.)

SERVICE SHEETS, 1925-1967. From 1s. Catalogue 6,000 models, 2s. 6d. S.A.E. enquiries.—Hamilton Radio, 13 Western Road, St. Leonards, Sussex.

100 PAGE ILLUSTRATED CATALOGUE NO. 17 of Government and manufacturers' electronic and mechanical surplus, also a complete new section of the latest semi-conductors and miniature components, includes a credit voucher for 2s. 6d. Send for your copy now. Price 3s. post free. Arthur Sallis (Radio Control) Ltd., 93 North Road, Brighton, Sussex.

FOR SALE. Oscilloscopes—Galvanometers—Evershed & Vignolles Meggers—Relays—Uniselector Switches—Solenoids. Also other items and components. Free list. Stamp please.—R. & E. Mart, Box 9 G.P.O., Tunbridge Wells, Kent.

TELEPRINTERS 7B complete from £10. Also Auto-transmitters, Reperforators, Signalling Rectifiers, etc., from William Batey & Co. (Exports) Ltd., Gaiety Works, Akeman Street, Tring, Herts. Please ring Tring 3476.

TORIOD COILS for sale. Suitable RTTY, etc. Mostly 88mH but some values above and below. S.A.E. for details. 7s. 6d. each. Box No. F289.

TRANSFORMERS REWOUND. Specials made to order. Reasonable charges. S.A.E. enquiries. Ratcliffe, 27 Station Road, Holmfirth, Yorks.

FOR SALE. Rectifier Units, Type 43A. 50s. plus carriage. Box No. F292.

14/0076 SINGLE P.V.C. COVERED WIRE on 100 yd. reels, red or green 8/4d. post 4/6d. 3 reels post 6/- Polypropylene twine 6/- 100 yds. coil. S.A.E. for samples. Better quality mixed parcels radio parts etc., 5½ lbs. approx., 12/6d. G. Hart, The Bungalow, Lings Lane, Chelmondiston, Ipswich, Suffolk.

BRIGHTEN UP YOUR ADVERTISING! Break the ice with a cartoon, "tailor made" for your product. Reasonable charges. Box No. F294.

TECHNICAL DRAWINGS, Artwork, etc. Electronic and Radio Circuits a speciality. Moderate charges.—B. P. Meaney, 43 Forest Road, Worthing, Sussex.

HIGH GRADE SWISS AND ENGLISH LEVER WATCHES OVERHAULED, REPAIRED. Chronographs and electric watches. 12 months guarantee. Estimates free. Write for details and prices or send registered to: B. Thornton, C.M.B.H.I., Kimtarn, Clay Hill, Beenham, Reading, Berks.

continued on page 62

BENTLEY ACOUSTIC CORPORATION LTD.

38 Chalcot Road, Chalk Farm, LONDON, N.W.1. 47 Norfolk Road, LITTLEHAMPTON, Sussex. Littlehampton 2043

Please forward all mail orders to Littlehampton

IR5	4/9	10C2	12/-	AZ31	7/9	ECL82	6/3	EZ41	6/6	PY88	7/3
ISS	3/3	10F1	9/9	DAF96	6/-	ECL83	9/-	EZ80	3/9	PY800	6/-
IT4	2/6	10F18	9/-	DF96	6/-	ECL85	11/-	EZ81	4/3	PY801	6/-
3Q4	5/3	10LD11	10/-	DK40	10/6	ECL86	7/9	GZ34	10/-	PZ30	9/6
3S4	4/9	10P13	12/-	DK92	7/6	EF36	3/-	HABC80	9/3	U25	11/-
3V4	5/6	10P14	13/-	DK96	6/6	EF37A	7/-	KT66	16/6	U26	8/6
5Y3GT	5/-	12AT6	4/6	DL96	6/-	EF39	5/-	PABC80	7/6	U191	10/-
5Z4	7/6	12A06	4/9	DM70	6/-	EF41	9/-	PC86	8/6	U301	12/6
6AQ5	4/9	12AV6	5/9	DY87	5/9	EF80	4/6	PC88	8/6	U329	9/-
6AT6	3/9	12BA6	5/-	E88CC	12/-	EF85	4/6	PC95	6/9	U404	6/-
6AU6	5/6	12BE6	5/3	EABC80	5/9	EF86	6/3	PC97	5/9	U801	18/-
6AV6	5/-	12BH7	6/-	EAF42	7/6	EF89	4/9	PC900	8/-	UABC80	5/3
6BA6	4/6	19AQ5	7/3	EB91	2/3	EF91	3/3	PC884	5/6	UAF42	7/9
6BE6	4/3	20D1	10/-	EB441	7/3	EF92	2/6	PC885	6/9	UBC41	6/6
6BH6	6/6	20F2	11/6	EB881	6/3	EF97	8/-	PC888	10/6	UBC81	6/9
6BJ6	7/-	20L1	13/-	EBF80	5/9	EF98	9/3	PC889	9/9	UBF80	5/6
6BQ7A	7/-	20P3	15/-	EBF83	7/-	EF183	6/3	PC8189	8/3	UBF89	5/9
6BR7	9/-	20P4	16/-	EBF89	5/9	EF184	5/9	PCF80	6/3	UBL21	9/6
6BV6	7/-	20P5	16/-	EBL21	10/3	EH90	7/6	PCF82	6/-	UC92	5/6
6BZ6	6/-	30C15	10/6	EC86	11/6	EL33	12/-	PCF84	8/-	UCC84	8/-
6CD6G	19/6	30C17	11/6	EC88	10/6	EL41	8/-	PCF86	8/-	UCC85	6/6
6CH6	6/-	30C18	9/6	EC92	6/6	EL42	7/6	PCF801	8/6	UCF80	8/3
6F1	9/6	30F5	9/9	ECC40	9/6	EL84	4/6	PC802	6/3	UCH21	9/-
6F23	8/-	30FL1	13/-	ECC81	3/6	EL85	7/6	PC882	6/3	UCH42	8/6
6F24	10/-	30FL12	13/-	ECC82	4/6	EL86	8/-	PC883	8/6	UCH81	6/-
6J7G	4/9	30FL14	11/6	ECC83	4/6	EL95	5/-	PC884	7/-	UCL82	7/-
6K7G	1/3	30L15	12/-	ECC84	5/6	EL80	13/-	PC885	8/3	UCL83	8/9
6K8G	3/-	30L17	12/-	ECC85	5/-	EM71	14/-	PC886	8/-	UF41	7/9
6L6	7/6	30P4	11/6	ECC88	7/-	EM80	5/9	PFL200	13/6	UF42	4/9
6L18	7/6	30P4MR	13/-	ECC189	9/-	EM81	6/9	PL36	9/-	UF80	6/9
6LD20	6/6	30P12	9/-	ECCF80	7/-	EM84	6/-	PL81	6/9	UF85	7/3
6Q7G	5/-	30P19	10/6	ECCF82	6/9	EM85	11/-	PL82	5/9	UF86	9/-
6SN7	4/6	30PL1	12/9	ECCF86	8/6	EM87	6/6	PL83	6/-	UF89	5/6
6V6G	3/6	30PL13	13/3	ECH21	6/6	EY51	5/6	PL84	6/3	UL41	8/9
6X4	3/6	30PL14	13/3	ECH35	6/-	EY81	7/-	PL500	13/6	UL84	5/6
6X5	5/3	30PL15	13/6	ECH42	8/9	EY83	9/-	PY33	8/6	UM80	5/-
6/30L2	9/6	35V4	4/6	ECH81	5/-	EY84	9/6	PY80	5/-	UY41	5/6
7Y4	6/6	85A2	8/6	ECH83	7/-	EY86	5/9	PY81	5/-	UY85	4/9
9D7	7/6	807	11/9	ECH84	6/6	EY88	7/6	PY82	5/6	VP48	11/-
10C1	9/-	5763	10/-	ECL80	6/-	EZ40	6/-	PY83	5/6	X41	10/-

Terms of business: Cash with order only. No C.O.D. Post/packing 6d. per item. Orders over £5 post free. All orders despatched same day as received. Complete catalogue including transistor section and components with terms of business 6d. Any parcel insured against damage in transit for 6d. extra. We are open for personal shoppers: 9 a.m.-5 p.m. Saturdays 9 a.m.-1 p.m.

BUILD THIS Radio Control

SINGLE CHANNEL TRANSMITTER

STT/1 FULLY DESCRIBED IN
JUNE 1967 RADIO CONSTRUCTOR

PARTS £4.4.6

Plus Case 25/-; Crystal 20/-; Aerial 45/-
Matching Receiver also available

ST140 TRANSISTORS 4/- each
ST141 „ 6/- each

MATERIALS AVAILABLE FOR ALL DESIGNS
EXPLAINED IN THIS MAGAZINE.
QUOTATIONS ON REQUEST

BOOKS

Single channel R/C 6/9 post free
Multi channel control 13/6 post free
Model boat control 8/6 post free
Radio control components 1/-
Full lists on transmitters and receivers 1/-.

Get into this interesting hobby now


TELERRADIO ELECTRONICS,
325/7 FORE STREET, EDMONTON,
LONDON, N.9.



NEW STYLE SELF-BINDER for "The Radio Constructor"

The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for, and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check-device is fitted to each.

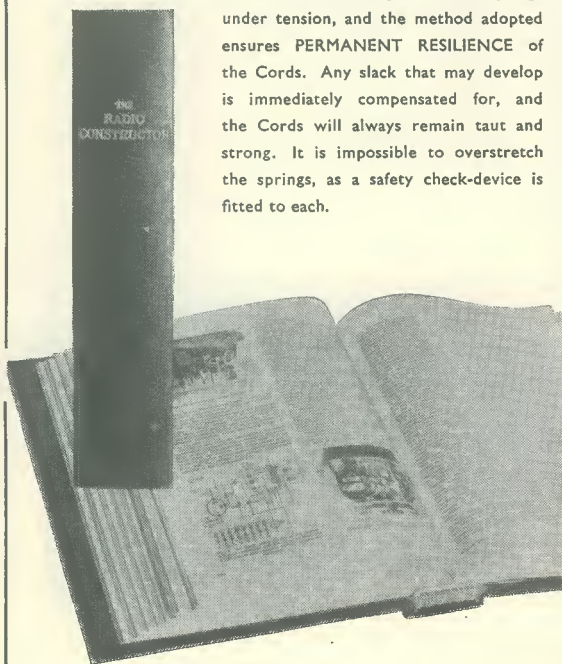

PRICE **15/-** Post Free

Available only from:—

Data Publications Ltd.
57 Maida Vale London W9

SMALL ADVERTISEMENTS

continued from page 61

BOOKS FOR SALE. *Hi-Fi Projects for the Hobbyist*, Fieldman, 10s. *Radio Operating Questions & Answers*, Nilson, 5s. 6d. *Electronic Valves in A.F. Amplifiers*, Rodenhuis, 3s. 6d. *Tubes for Computers*, Philips, 5s. 6d. *Industrial Rectifying Tubes*, Philips, 5s. 6d. *U.H.F. Tubes for Communication and Measuring Equipment* 5s. 6d. *Instructions to Radio Constructors*, Warring, 7s. 6d. All post free. Box No. F297.

FOR SALE. B.P.L. Signal generator (mains) £3, (cost £21). 53 assorted valves £2. Hemingway, 9 Hitherwood, Cranleigh, Surrey.

WANTED. Alco/Sirius steam portable generator, made by Lyons Co., as used in WW2 for battery charging by troops in Burma.—Box No. F299.

FOR SALE. Japanese dynamic microphone and stand. Small, neat unit. Hand held mic. Piezo make, £3.—Box No. F300.

WANTED. 8 and 10 way socket connectors for SCR522 transceiver. Will pay reasonable price. D. Scott, 8 Clayfarm Road, London S.E.9.

YOUR KITS EXPERTLY ASSEMBLED. Radios, amplifiers, test gear of every description. For estimate simply send price and type of kit to: W. Thomas, No. 6 North Avenue, Ruabon, Nr. Wrexham.

FOR SALE. Crystal controlled Holme Moss F.M. tuner less valves £4. 5. 0d. o.n.o. or crystals 35s. Modified Mullard tape pre-amp. £4. 5. 0d. o.n.o. with EF86's £5 o.n.o. Elstone OT8 trans. 20s. Matched EL41's 10s. Details s.a.e. Box No. F306.

"MEDIUM WAVE NEWS" Monthly during DX season—Details from: B. J. C. Brown, 60 White Street, Derby.

RADIO SKY. Journal of the Society for Amateur Radio Astronomers. Vol. 1. No. 2, price 7s., contained articles on a 3 cms. radio telescope and a basic introduction to the subject with an extensive guide to further reading. Additional details on application. Box No. F307.

JOIN THE INTERNATIONAL S.W. LEAGUE. Free Services to members including Q.S.L. Bureau. Amateur and Broadcast Translation. Technical and Identification Dept.—both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes. QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazine, etc., 35s. per annum.—Secretary, ISWL, 60 White Street, Derby.

continued on page 63

SMALL ADVERTISEMENTS

continued from page 62

JOIN BRITAIN'S LEADING DX CLUB by joining The World Communication Club, Great Britain. Details from: S. Green, 26 Tolhouse Street, Great Yarmouth, Norfolk.

FOR SALE. Lafayette MW/SW broadcast receiver, model HA-63A. Practically new £18. Box No. F308.

FOR SALE. Complete 2 metre station. Rx is that described in the March 1966 issue of *The Radio Constructor*. Companion Tx, QVO 4/7 p.a.; pp 6BQ5's modulator; with power supply and aerial changeover relay all on one chassis. Complete with xtal mic. and speaker. £20. G2UK, "East Keal", Romany Road, Oulton Broad, Lowestoft, Suffolk.

FOR SALE. Collection early radio valves. Would suit technical museum or school. Box No. F309.

POSTAL ADVERTISING? This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service campaign planning, design and artwork, printing and stationery. Please ask for price list.—The Holborn Direct Mail Company, 2 Mount Pleasant, London, W.C.1. Telephone: TERminus 0588.

WANTED. Ships Chronometer and Sextant; pay cash, or preferably exchange radio gear. Box No. F310.

FOR SALE. 8-day clock by Waltham Watch Co. 3¼" diam. panel mounting, with second hand and date dial, £5. Deck watch by Jolay, 2½" diam., rotatable navigational ring graduated to 360° in fitted wooden case. £10, p.p. paid. Box No. F311.

MESSERSCHMITT Four wheel TG 500 sports car. Enthusiast seeks damaged or part vehicles, spares etc. Details to C. E. Jaques, 33 Middleton Road, Shenfield, Essex.


ULTRA SENSITIVE BUTTON SIZE MICROPHONE. 9mm square, 4mm thick, 12s 6d., Lipstick size (including battery) wireless microphone £7 10s. 0d. Box No. F312.

ARE YOU A MOTORING ENTHUSIAST? The Seven Fifty Motor Club caters for all types of motor sport—racing, rallies, hill climbs, etc. Monthly Bulletin free to members. For full details write to: The General Secretary, Colin Peck, "Dancer's End," St. Winifred's Road, Biggin Hill, Kent.

ESSEX GARDENERS. Buy your bedding and rock plants, shrubs, etc., also cacti, from May's Nurseries, 608 Rayleigh Road, Hutton, Brentwood, Essex. Callers only, Monday to Saturday.

PROPERTIES for sale and to let in London and suburbs. Apply to Maggs & Stephens, Estate Agents, 229 Maida Vale, London, W.9. MAIda Vale 8123.

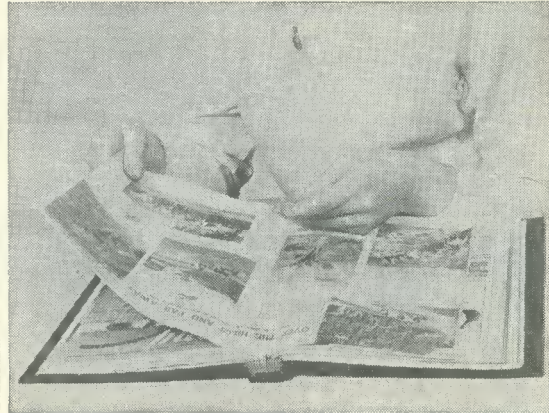PLAIN-BACKED NEW STYLE SELF-BINDERS for your other magazines (max. format 7½" × 9½")



The "CORDEX" Patent Self-Binding Case will keep your copies in mint condition. Issues can be inserted or removed with the greatest of ease. Rich maroon finish. Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for, and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check-device is fitted to each.

PRICE **14'6** Post Free

Available only from:—

Data Publications Ltd.
57 Maida Vale London W9

CHASSIS and CASES by




H. L. SMITH & CO. LTD.
287/9 Edgware Road
London W2
TEL: 01-723 5891

BLANK CHASSIS—Same Day Service

Of over 20 different forms made up to YOUR SIZE.
(Maximum length 35", depth 4".)

SEND FOR ILLUSTRATED LEAFLETS or order straight away, working out total area of material required (including waste) and referring to table below which is for four-sided chassis in 16 s.w.g. aluminium.

ALUMINIUM, SILVER HAMMERED FINISH			
Type	Size	Price	Size
U	4 x 4 x 4"	10/-	W 15 x 9 x 8"
U	5 1/2 x 4 1/2 x 4 1/2"	15/6	Y 8 x 6 x 6"
U	8 x 6 x 6"	21/-	Y 12 x 7 x 7"
U	9 1/2 x 7 1/2 x 3 1/2"	22/-	Y 13 x 7 x 7"
U	15 x 9 x 9"	44/6	Y 15 x 7 x 7"
W	8 x 6 x 6"	21/-	Z 17 x 10 x 9"
W	12 x 7 x 7"	34/-	Z 19 x 10 x 8 1/2"

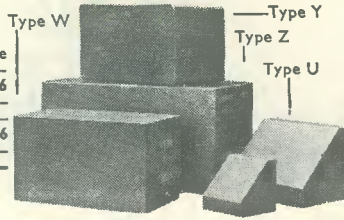

Type Z has removable back and front panels.
Type Y all-screwed construction.

48 sq. in.	4/6	176 sq. in.	9/10	304 sq. in.	15/2
80 sq. in.	5/10	208 sq. in.	11/2	336 sq. in.	16/6
112 sq. in.	7/2	240 sq. in.	12/6	368 sq. in.	17/10
144 sq. in.	8/6	272 sq. in.	13/10	and pro rata	
	P. & P. 3/-		P. & P. 3/6	P. & P. 4/6	

Discounts for quantities. More than 20 different sizes kept in stock for callers.


FLANGES (1/2" or 3/8"), 6d. per bend.
STRENGTHENED CORNERS, 1/- each corner.

Any size up to 3ft at 6/- sq. ft. 16 s.w.g. (18 s.w.g. 5/3).
Plus postage and packing

HAMMERITE TRIAL TIN

State colour: Blue, Silver, Black or Bronze (Air Drying). 2 1/2 oz. tins 3/6, 1/2 pint 7/6, 1 pint 15/-. CARR., up to 5/-, 9d. up to 10/-, 1/9, over 10/-, 3/-. VERY SPECIAL PRICES FOR LARGER SIZES. AMAZING RESULTS, JUST TRY IT.
FIREPROOF THINNERS, PANEL TRANSFERS, TINTERS, ETC. LAM FREE.
FINNIGAN SPECIALITY PAINTS (RC) Mickley Square, Stocksfield, Northumberland. Telephone: Stocksfield 2280

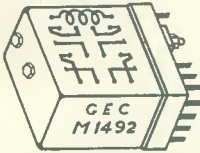HAMMER PATTERN BRUSH PAINT FOR PANELS, METALWORK, ETC.



WANTED

This and similar scrap relays
BEST PRICES PAID

S.a.e. to "Lanco", 76 Sedgemoor Rd., Willenhall, Coventry, Warwickshire

COMPUTER CONSTRUCTION KIT

Digi-Comp is a complete mechanical equivalent of a giant electronic brain, designed so that you can see just what it is that makes a computer function. Digi-Comp calculates, solves problems and plays games, and is accompanied by an instruction and programming manual that explains binary methods and elementary logic in terms comprehensible to anyone who can count—primary school to Ph.D! Send 59/11 or write for details to:

I-COR SYSTEMS (File RC1)
18 STAMFORD HILL, LONDON N.16

MICRO-MICROPHONES

Super sensitive $\frac{7}{8}$ " x $\frac{5}{8}$ " x $\frac{5}{16}$ " Low impedance
only 17/6 each

G. A. BOBKER
ELECTRONICS, DESIGN
AND EXPERIMENTAL

64 CHOIR STREET
SALFORD 7
LANCS.

2N 2926 SERIES

This versatile silicon NPN transistor series is

DOWN IN PRICE AGAIN!!!

2N 2926 Red	(55—110)hf _e	Now 3/- each.
2N 2926 Orange	(90—180)hf _e	Now 3/3 each.
2N 2926 Yellow	(150—300)hf _e	Now 3/3 each.
2N 2926 Green	(235—470)hf _e	Now 3/9 each.

AND A 10% DISCOUNT (if bought in lots of 5 or more, per type).

Also available are hundreds of other semiconductors, including:

ACY 18, 5/-; ACY 20, 4/9; ACY 21, 5/3; ACY 22, 4/-; AF 139 12/6;
BC 107, 5/6; NKT 211, 4/5; NKT 212, 4/3; NKT 217, 8/-; NKT 218, 3/11;
NKT 271, 3/4; NKT 274, 3/4; NKT 675, 4/3; NKT 676, 4/-; NKT 773, 4/8;
OC 170, 8/6; MAT 121, 8/6; 2G 302, 5/4; 2N 270, 9/9; 2N 384, 18/-;
2N 697, 9/-; 2N 706, 4/3; 2N 2147, 18/-; 2N 2646, 14/-; 2N 3638, 8/-.
Transistor price list (800/2) covering over 1500 items, will be sent on receipt of 2/- P.O. (inclusive of addition to mailing list).

MAIL ORDER ONLY PLEASE.

TERMS: C.W.O. or C.O.D.

M. R. CLIFFORD & COMPANY (C5M)

209A, Monument Road, Edgbaston, Birmingham, 16.

Please add 2/- Postage & Packing on all orders of £1 or less.

RADIO MODELLER

"the magazine for the practical enthusiast"

★ LATEST TRENDS & TECHNIQUES
in RADIO CONTROL

● CIRCUITS ● TESTS ● DESIGNS

2/6d monthly — send 6d stamp for free specimen copy!

64 WELLINGTON ROAD, HAMPTON HILL, MIDDXX.

THE RADIO CONSTRUCTOR ANNUAL SUBSCRIPTIONS to this magazine may be obtained direct from the publishers ONLY 36/- per year, post free

Please send remittance with name and address and commencing issue required to:

DATA PUBLICATIONS LTD 57 MAIDA VALE LONDON W9

Please mention THE RADIO CONSTRUCTOR when writing to advertisers

DATA BOOKS SERIES

NEW REVISED AND ENLARGED EDITION

DB5 TV Fault Finding

124 pages. Price 8/6, postage 8d.

Profusely illustrated with photographs taken from a television screen depicting the faults under discussion and containing a wealth of technical information, with circuits, enabling those faults to be eradicated. Now includes B.B.C.II as well as B.B.C.I and I.T.A.

"... A book that should be in every television dealer's service workshop, and in every home-constructor's, for that matter."—*Journal of the Television Society*.

DB6 The Radio Amateur Operator's Handbook

64 pages. Price 5/-, postage 5d.

Contains Amateur Prefixes, Radio Zone Boundaries, Amateur Band Frequency Allocations, Call Areas, Charts and Maps, Areas, Codes, Mileage Tables, Prefixes/Directional Bearings, Post Office Regulations, and much other useful operating data. For the beginner there are notes on how to use the mass of information given to obtain the greatest satisfaction from the hobby.

"... For concise knowledge in this field a few shillings well worth spending."—*Electronics* (Australia).

DB14 Short Wave Receivers for the Beginner

72 pages. Price 6/-, postage 6d.

Contains a selection of both battery and mains operated short wave receivers, circuits, point-to-point wiring diagrams and many illustrations. Introductory chapter gives much information on the Short Wave Spectrum, Clubs, QSL'ing, Aerials, Amateur and Broadcast Band Listening, Frequencies, etc. This book has been specially prepared for the beginner interested in short wave receiver construction and operation.

DB15 Twenty Suggested Circuits

48 pages. Price 3/6, postage 5d.

By G. A. French. Covers subjects ranging from electronic laboratory equipment to the simplest of periodic switches. Includes: simple and inexpensive two-valve capacity bridge, short wave regeneration preselector, one-valve speech operated switching circuit, transformer ratio analyser, series noise limiter, receiver remote mains on-off control, and many other circuits.

DB16 Radio Control for Models

192 pages. Price 15/-, postage 9d.

By F. C. Judd. Contains both theory and practical designs of simple and advanced transmitters and receivers; basic concepts, aerials, uses of radio components, transistorised receivers, multi-channel operation, etc. Sections on servo-mechanisms by Raymond F. Stock. More than 200 illustrations. Circuits, photographs, tables and working diagrams.

DB17 Understanding Television

512 pages. Price 37/6, postage 3/-.

By J. R. Davies. This book, which deals with the principles of 625 line reception as fully as 405 line reception, fully explains: the nature of the television signal; the cathode ray tube; receiver tuner units; receiver i.f. amplifiers; a.f. and video amplifiers; vertical and horizontal timebases; deflector coil assemblies; synchronising; automatic gain and contrast control; power supplies and receiver aerials. Also includes a comprehensive introduction to colour television.

"... one of the best books that aims to explain television in simple language. . . ." R.S.G.B. Bulletin.

I enclose Postal Order/Cheque for..... in payment for.....

NAME

ADDRESS

(Please use Block Capitals for both name and address)

Postal Orders should be crossed and made payable to Data Publications Ltd.


Overseas customers please pay by International Money Order

All publications are obtainable from your local bookseller

Data Publications Ltd., 57 Maida Vale, London W.9

NEW SOLID STATE HIGH FIDELITY EQUIPMENT ★★★★★

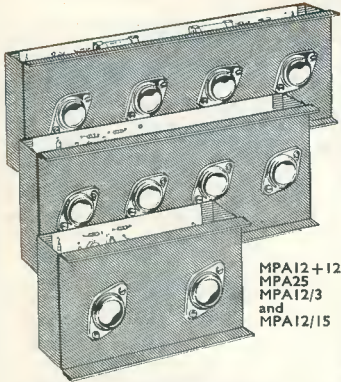IMPROVED PERFORMANCE—NEW STYLING—NEW MODELS—MONO & STEREO



MPA12+12
MPA25
MPA12/3
and
MPA12/15



SP6-2



MP3

MP3. Mono preamplifier. All silicon low noise zener stabilised circuit. Full range of controls—fully equalised inputs for xtal pu, dyn/xtal mic, radio tuners, tape head and preamp, replay. Supplied built and tested on metal chassis complete with grey/silver front panel, alu. knobs and handbook. Output 250mV. Supply 12 to 60 volts 3mA. Overall size 9½ x 1½ x 1½in. **MP3 Price £6.19.6, P.P. 3/-**

SP6-2. Mono/stereo preamplifier. Uses 8 silicon/germanium devices. Zener stabilised. Completely new low noise design. Full range of controls and filters. Inputs for magnetic/xtal/ceramic cartridges, radio tuners, tape preamp, microphones, tape head, etc. Record output socket. Supplied built and tested on metal chassis with grey/silver front panel and matching knobs. Complete with input sockets and handbook. Output 250mV per channel. Supply 9 to 60 volts 4mA. Overall size 12 x 3½ x 3½in. **SP6-2 Price £14.19.6, P.P. 5/-**

SP4. Mono/stereo preamplifier as previously advertised. Complete with front panel and knobs. Size 9 x 3½ x 1½in. **SP4 Price £10.19.6, P.P. 3/6**

MPA12/3 and MPA12/15. 12 watt power amplifiers for use with above preamplifiers. Improved response and performance with even lower distortion levels. MPA12/3 for 3 to 5 ohm speakers, 24/28 volt supply MPA12/15 for 10 to 16 ohm speakers, 40/45 volt supply, uses 8 silicon and germanium devices. Inputs 100mV for 12 watts, response ± 1dB, 30 c/s to 20 kc/s. THD 0.2% at 12 watts. High gain stable push-pull output designs. Built on metal chassis as illustrated. Overall size 5 x 2 x 3in. Complete with handbook. **MPA12/3 Price £4.10.0, P.P. 2/6** **MPA12/15 Price £5.5.0, P.P. 2/6**

MPA12+12. Twin amplifier for mono/stereo use with above preamplifiers. Consists of two matched MPA12/15 amplifiers (see above) on single chassis. Output for 10 to 16 ohm speakers. 40/45 volts supply. Overall size 10 x 2 x 3½in. **MPA12+12 Price £9.19.6, P.P. 4/-**

MPA25. 25/30 watt power amplifier for use with above preamplifiers. New design and layout with improved response and overall performance. Output for 7½ to 16 ohm speaker systems. Input 180mV for full output. Push-pull circuit. Uses 10 silicon and germanium devices. Supply 50/60 volts. Overall size 8 x 2 x 3½in. **MPA25 Price £7.10.0, P.P. 3/6**

CHOICE OF PREAMPLIFIERS POWER AMPLIFIERS MAINS UNITS

MAINS UNITS

110/240 volt 50/60 c/s input. AC/DC fused. Fully smoothed and isolated. MU series has additional choke/capacitor filtering and panel voltage selectors. All types on metal chassis. **PS24/40.** Output 24 and 45 volts 1 amp. For use with 1 or 2 MPA12/3, MPA12/15, or MPA12+12. Price 70/-, P.P. 3/- **MU24/40.** Choke smoothed. Output 24 and 45 volts 1 amp. For use with 1 or 2 MPA12/3 and MPA12/15 or 1 MPA12+12. Price 87/6, P.P. 3/6.

MU60. Choke smoothed. Output 50 volts 1 amp. For use with 1 or 2 MPA25. Price 98/-, P.P. 4/-

RECOMMENDED SYSTEMS

MP3+MPA12/15+PS40

£14.12.6, P.P. 6/6

MP3+MPA12/3+PS24

£13.17.6, P.P. 6/6

MP3+MPA25+MU60

£18.5.0, P.P. 8/-

SP6-2+MPA12/15+12 or 2 MPA12/15+MU40

£28.5.0, P.P. 10/-

SP6-2+2 MPA12/3+MU24

£26.15.0, P.P. 10/-

SP6-2+2 MPA25+MU60

£33.5.0, P.P. 10/6

SP4+2 MPA12/15+PS40

£24.0.0, P.P. 9/-

SP4+2 MPA12/3+PS24

£22.15.0, P.P. 9/-

MP3+2 MPA12/15+MU40


£20.17.6, P.P. 8/-

MP3+2 MPA12/3+MU24

£19.7.6, P.P. 8/-

COMPLETE BROCHURE
FREE ON REQUEST

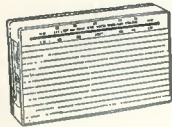THE FINEST VALUE IN HIGH FIDELITY—FULLY GUARANTEED CHOOSE A SYSTEM TO SUIT YOUR NEEDS & SAVE POUNDS



REGENT-6 MW/LW POCKET RADIO TO BUILD
6-Transistor superhet. Geared tuning. Push-pull speaker output. Moulded Cabinet 5 x 3 x 1½in. Phone socket. **TOTAL COST £3.9.6** P.P. 2/-
TO BUILD Full tuning on both bands.

GLOBEMASTER MW/LW/SW PORTABLE RADIO TO BUILD
3 Waveband portable superhet. As previously advertised. **TOTAL COST £7.19.6** P.P. 3/6
TO BUILD Circuit and Details on request.


TOURMASTER TRANSISTOR CAR RADIO British Made
7-Transistor MW/LW Car Radio. 12 volt operated. 3 watt output. Push-button wavechange. RF stage. Supplied built, boxed, ready to use with Speaker and Baffle. Car fixing kit and manufacturers' current guarantee. Special Bargain Offer. Buy Now! **LIST PRICE £7.19.6** P.P. 4/6

VHF FM TUNER TO BUILD
87/105 Mc/s Transistor Superhet. Geared tuning. Terrific quality and sensitivity. For valve or transistor amplifiers. 4 x 3½ x 2½in. Complete with dial plate. 5 Mullard Transistors, plus 4 Diodes. (Cabinet Assembly 20/- extra). Leaflet on request. **TOTAL COST £6.19.6** P.P. 2/6
TO BUILD

BUILD A QUALITY 2 OR 4 TRACK TAPE RECORDER
3-speed version using '363' decks
*TWO-TRACK. Deck £10.10.0.
*Martin Amplifier. £14.19.6. Cabinet and speaker 7gns. Complete kits with FREE 7in. 1,200ft. tape, spare spool. Today's Value £45. **27 gns.** P.P. 15/-
*FOUR-TRACK. Deck £13.10.0.
*Martin Amplifier £15.19.6. Cabinet and speaker 7gns. Complete kits with FREE 7in. 1,200ft. tape, spare spool. Today's Value £50. **30 gns.** P.P. 15/-

27 Mc/s B'ND RADIO CONTROL
Sub-miniature crystals 17/6 each Matched pairs for superhet 35/- pair (State 455 kc/s or 470 kc/s I.F.)

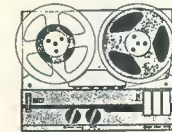STEREO DECODER KIT
For use with all F.M. tuners
£5.19.6. P.P. 2/6



WE CAN SUPPLY FROM STOCK MOST OF THE PARTS SPECIFIED ON CIRCUITS IN THIS MAGAZINE. SEND LIST FOR QUOTATION. OR BETTER STILL—BUY THE NEW 1967 CATALOGUE. EVERYTHING YOU NEED IS LISTED AND AVAILABLE FROM STOCK.

Mayfair Portable Electronic Organ

NOW AVAILABLE AS:

- COMPLETE KIT OF PARTS
- BUILT AND TESTED
- PRE-BUILT ASSEMBLIES.

REVERBERATION UNITS AND RECOMMENDED SPEAKERS AND AMPLIFIERS IN STOCK.

Designed by L. W. ROCHE

STRAIGHT FORWARD TO BUILD AND TUNE—EASY TO PLAY—FULLY GUARANTEED. ALL PARTS AVAILABLE SEPARATELY—ASTOUNDING VALUE AND PERFORMANCE.

● Plug-in printed circuits ● 170 transistors and devices ● 10 selected tone colours ● Fully sprung keyboard ● Vibrato ● 6 Octaves of generators ● Simple locked-in tuning ● 110/250 volt mains unit ● Cabinet size 30½in x 15in x 9½in ● Weight 35 lb. Cabinet with detachable legs, music stand and foot swell pedal ● Fully detailed building manual with photos, drawings and full circuits. Complete range of organ parts in stock. H.P. facilities available. Trade/Export supplied. Fully detailed leaflet and Price List on request. Call for demonstration and play the Mayfair.

RELAYS, MOTORS, SWITCHES, MINIATURE COMPONENTS, TRANSISTORS AND DEVICES

Complete range in stock all types for every purpose. Also panel and multimeters, precision components, radio control crystals and parts, transistors, tunnel diodes, thyristors, LDR's, zeners, rectifiers and diodes. Everything you need for amateur and professional applications—see 1967 catalogue. The largest range in the country. Suppliers of quality components and equipment for over 20 years.

LISTS AVAILABLE

- (incorporated in full catalogue)
- * Transistors/Rectifiers/SCR's/Valves/Crystals/Zeners, etc. 24 pages, 1/-.
- * 4-page hi-fi stock list with discounts.
- All popular makes. Free on request.
- * Car radio and tape recorders. Free.
- * Organs and components lists. Free.

HENRY'S RADIO LTD.

303 Edgware Road, London, W.2 PAddington 1008/9 (STD 01-723 0008) Open Mon. to Sat. 9-6. Thurs. 1 p.m. Open all day Saturday.

1967 CATALOGUE

Have you a copy? Fully detailed and illustrated. Over 200 pages of components, equipment, etc. Over 5,000 stock items. FULLY DETAILED AND ILLUSTRATED. Price 8/6, post paid. 5 Free discount vouchers, value 10/- with every catalogue.



5 FREE VOUCHERS value 10/- with every catalogue