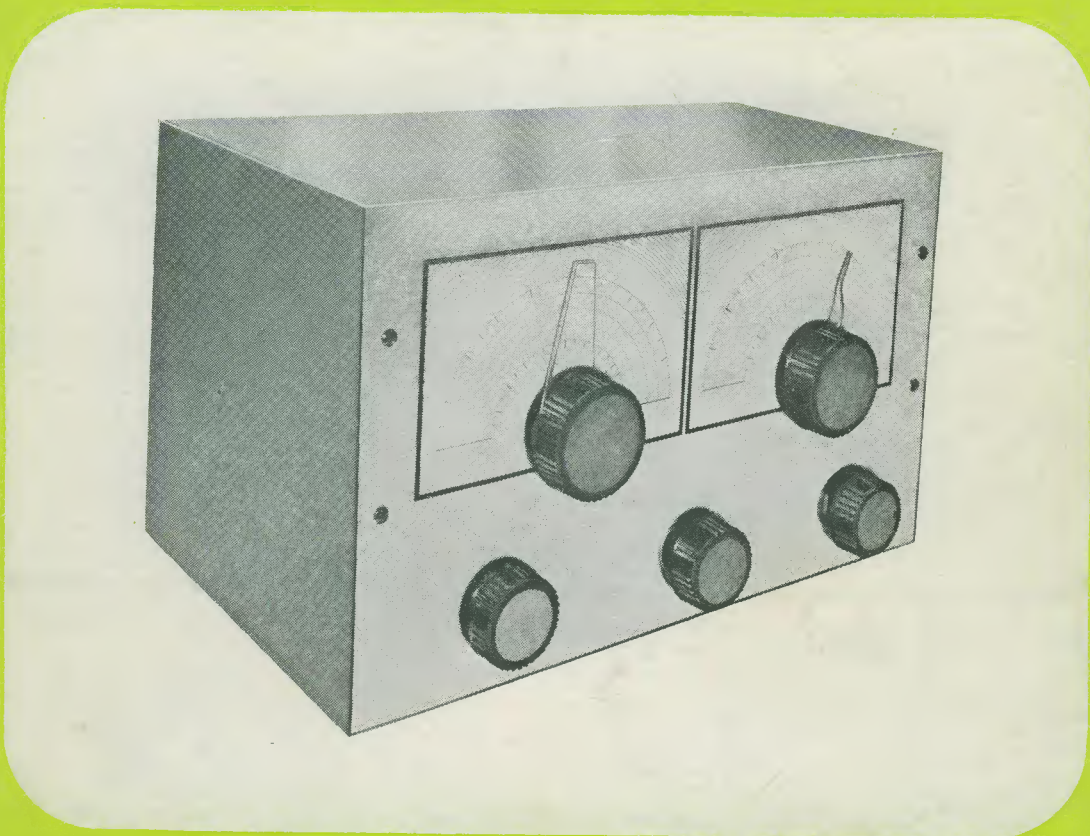


THE RADIO CONSTRUCTOR

Vol. 23 No. 6

JANUARY 1970

THREE SHILLINGS



HIGH SELECTIVITY T.R.F. RECEIVER

A 2-valve (6BR7, ECL82) all-wave design with super-efficient regeneration providing performance comparable with a superhet

**FEATURED
IN THIS ISSUE**

2-Transistor Record Player Amplifier
Versatile A.C. Millivoltmeter

L.S.T. ELECTRONIC COMPONENTS LTD.

AA119 2/1	BC137 8/6	BY21 25/-	NKT217 13/-	OC24 10/-	1N4001 2/9	2N2368 6/6
AA119 2/1	BC138 8/6	BY23 26/3	NKT218 5/3	OC25 6/9	1N4005 5/6	2N2369 6/6
AA121 17/6	BC142 15/-	BY25 31/9	NKT221 5/3	OC26 12/-	1N4007 5/6	2N2380A 6/6
AC107 14/6	BC143 15/-	BY142 3/9	NKT222 4/6	OC28 12/-	1844 1/6	2N2432 58/4
AC126 6/6	BC147 8/6	BY210 9/-	NKT223 6/6	OC29 15/-	2G247 18/-	2N2477 18/-
AC127 6/6	BC148 8/6	BY212 6/-	NKT224 3/6	OC35 9/5	2G239A 5/6	2N2484 10/-
AC127Z 8/6	BC149 4/7	BY213 4/7	NKT224 4/6	OC39 15/-	2G237 5/6	2N2613 7/6
AC128 4/6	BC150 12/6	C106F1 3/6	NKT225 3/6	OC40 4/6	2G238 1/6	2N2614 8/6
AC131 8/8	BC151 7/6	C116 18/-	NKT226 10/6	OC42 4/6	2G237B 4/6	2N2615 10/6
AC176 7/6	BC172 9/6	C117E 12/-	NKT227 5/6	OC43 4/6	2G237B 4/6	2N2684 13/6
AC187 12/6	BCY30 7/2	C120 9/6	NKT228 6/6	OC44 3/6	2N174 24/6	2N2694 13/6
AC188 12/6	BCY31 9/2	C226 8/3	NKT231 5/6	OC45 3/6	2N301 8/6	2N2694A 13/6
AC189 3/6	BCY33 4/11	CG85 2/-	NKT232 5/6	OC71 3/6	2N109 13/6	2N2924 5/6
AC197 5/9	BCY32 20/5	CG86 4/6	NKT270 3/6	OC72 3/6	2N109 13/6	2N2925 5/6
AC198 3/6	BCY33 4/11	CG88 2/-	NKT271 5/6	OC73 3/6	2N384 17/-	2N3038 3/2
AC199 4/5	BCY34 3/6	D131 10/-	NKT272 5/6	OC70 4/6	2N386 12/-	2N3038 3/2
AC200 3/6	BCY38 28/6	EA403 3/6	NKT273 4/6	OC73 3/6	2N384 17/-	2N3053 8/6
AC201 3/11	BCY40 16/-	EA404 3/6	NKT274 5/6	OC75 5/6	2N385A 15/-	2N3054 15/-
AC202 2/7	BCY40 16/-	EA405 3/6	NKT275 5/6	OC76 2/6	2N385A 15/-	2N3055 15/-
AD100 9/6	BCY42 4/6	EA406 3/6	NKT276 3/6	OC77 3/6	2N109 13/6	2N3056 15/-
AD101 15/6	BCY43 4/6	EA407 3/6	NKT277 3/6	OC77 3/6	2N384 17/-	2N3057 15/-
AD102 15/6	BCY44 4/6	EA408 3/6	NKT278 2/6	OC81D 3/6	2N404 4/2	2N3525 25/-
AD103 15/6	BCY45 17/4	EA409 3/6	NKT281 5/6	OC81 4/6	2N410 5/6	2N3525 25/-
AD161 5/6	BCY46 17/4	EA410 3/6	NKT301 16/6	OC82 4/6	2N511A 50/3	2N3702 3/6
AD162 6/6	BCY71 8/8	EA411 3/6	NKT302 11/2	OC82D 3/6	2N513A 118/5	2N3704 3/6
AD170 12/6	BCY72 4/8	EA412 3/6	NKT303 10/2	OC83 4/6	2N514B 192/6	2N3705 3/6
AF102 18/6	BD167 8/6	EA413 3/6	NKT304 9/8	OC84 4/6	2N599 12/6	2N3706 3/6
AF106 7/6	BD211 10/8	EA414 3/6	NKT351 8/6	OC123 7/6	2N601 4/6	2N3707 4/6
AF114 4/4	BD119 15/6	EA415 3/6	NKT352 7/6	OC139 9/6	2N602 5/6	2N3708 2/5
AF115 4/4	SD121 18/6	K8/15 4/6	NKT402 24/6	OC140 12/6	2N606 5/6	2N3709 3/6
AF116 4/4	BD123 23/6	K8/30 9/6	NKT403 16/6	OC169 6/6	2N609 5/3	2N3710 3/10
AF117 4/4	BD124 15/2	K8/50 8/3	NKT404 8/6	OC170 7/6	2N608 4/6	2N3711 3/6
AF118 16/6	BD125 15/8	MAT100 5/6	NKT405 15/6	OC171 6/6	2N608 4/6	2N3819 8/6
AF121 4/4	BF152 13/8	MAT101 5/6	NKT406 13/8	OC172 6/6	2N608 4/6	2N3820 18/6
AF124 6/6	BF159 15/-	MAT120 5/6	NKT452 13/4	OC201 10/-	2N708 4/6	4N3826 6/6
AF126 3/9	BF163 15/6	MAT121 5/6	NKT453 12/6	OC202 18/10	2N711 7/6	2N3906 7/6

PRICES FOR QUANTITIES IN EXCESS OF 100 PIECES ON APPLICATION

FIRST GRADE + FAST SERVICE

When enquiring for types not listed please enclose a STAMPED ADDRESSED ENVELOPE

AF127 12/-	BF167 6/6	ME4103 6/6	NKT674 6/6	OC203 8/3	2N711A 7/6	2N4958 7/9
AF159 4/6	BF173 6/6	MK209 6/6	NKT675 6/6	OC206 8/6	2N715 7/6	2N4288 3/6
AF178 14/-	BF178 14/-	MPF102 9/6	NKT676 5/6	OC205 9/6	2N716 7/6	2N4288 3/6
AF186 11/6	BF179 12/-	MPF103 9/6	NKT677 5/6	OC206 10/6	2N718 7/6	2N4288 3/6
AF209 12/6	BF180 9/6	MPF104 9/6	NKT703 9/6	OC207 7/6	2N743 5/6	2N4288 3/6
AF211 14/-	BF181 7/6	MPF105 9/6	NKT713 7/6	ORP12 9/6	2N744 5/2	2N4288 3/6
AF212 11/9	BF184 7/6	MPF106 9/6	NKT713 7/6	ORP60 8/6	2N753 5/6	2N4288 3/6
ASV28 4/5	BF194 6/8	MJ480 2/1	NKT774 5/4	ORP61 8/6	2N863 12/6	2N4289 3/6
ASV27 6/6	BFK13 4/10	MJ481 21/-	NKT10013 12/6	ORP63 9/6	2N811 7/6	2N4291 3/6
ASV28 4/5	BFK39 8/6	MK491 30/3	NKT10419 13/-	ORP93 24/6	2N814 4/6	2N4292 3/6
ASV29 6/6	BFK44 6/5	NKT121 10/11	NKT10519 12/6	OC309 12/6	2N814 4/6	2N4303 15/-
AS221 11/-	BFK87 6/6	NKT122 7/9	NKT10338 10/3	P3M6A 6/6	2N929 5/3	2N4871 6/9
AT100 40/6	BFK90 4/6	NKT123 9/2	NKT10429 11/3	RAS10DAF 15/-	2N929 5/3	2N5002 15/-
AUY10 39/6	BFV51 3/9	NKT124 9/8	NKT20329 12/6	RAS50DAF 15/-	2N131 9/6	2S004 23/-
BF119 15/10	BFV52 3/2	NKT125 5/2	NKT16229 11/-	ST2 9/8	2N1132 7/6	2S017 15/6
BA110 8/6	BFV53 3/2	NKT127 5/8	OAS 3/8	ST140 3/8	2N143 26/6	2S016 12/6
BA111 6/6	BSX20 3/4	NKT128 6/6	OA10 1/6	ST141 5/6	2N1302 4/6	2S020 15/-
BA112 18/6	BSX21 3/4	NKT129 6/6	OA11 1/6	T154 1/7	2N1302 4/6	2S024 25/-
BA115 2/8	BSY27 4/6	NKT141 6/11	OA10 1/6	T154 1/7	2N1303 4/6	2S024 25/-
BA130 3/6	BSY95A 3/4	NKT142 5/10	OA73 1/6	U23AAA 5/6	2N1305 5/6	2S102 10/6
BAV31 2/6	BTX387 1/6	NKT143 5/4	OA79 1/6	VAS1A 9/3	2N1305 5/6	2S104 12/6
BAV38 3/6	600R 120/-	NKT144 8/6	OAB1 1/6	XA102 6/6	2N1306 6/6	2S104 12/6
BC107 2/9	BTX407 1/6	NKT145 8/6	OAB5 1/6	XA102 6/6	2N1307 6/6	2S101 7/6
BC108 2/9	600R 120/-	NKT161 5/8	OAB9 1/6	Z122 19/6	2N1308 8/6	2S202 6/6
BC109 2/9	BTY87 1/6	NKT182 5/8	OAG1 1/6	Z122 19/6	2N1309 8/6	2S204 15/6
BC113 5/6	150R 31/-	NKT183 5/4	OAG2 1/6	Z1220 19/6	2N1307 6/6	2S209 12/6
BC114 7/6	BTY191 3/6	NKT184 5/4	OAG2 1/6	1N23A 20/-	2N1613 6/6	2S232 8/6
BC115 7/11	300R 47/-	NKT185 5/4	OAG2 1/6	1N24A 4/6	2N166 3/6	2S201 10/6
BC116 8/6	BY122 3/6	NKT211 6/6	OA20 1/6	1N64 4/6	2N171 7/6	2S702 12/6
BC118 5/6	BY125 2/6	NKT212 6/6	OA21 1/6	1N64 4/6	2N147 17/6	2S711 23/3
BC125 12/6	BYX10 3/6	NKT213 6/6	OC19 5/6	1N82A 9/6	2N2148 12/6	2S712 30/3
BC126 12/6	BYX36/150 2/6	NKT214 4/6	OC20 33/6	1N87A 4/6	2N2160 14/9	2S733 9/9
BC134 5/6	BYX36/200 2/6	NKT215 4/6	OC22 13/6	1N191 5/6	2N2161 14/9	40361 10/3
BC136 7/11	BYX36/600 3/6	NKT216 10/5	OC23 15/6	1N914 3/6	2N2163 3/2/7	40362 16/3

2N3819 Texas FET 8/-
25 + 6/9 100 + 5/9

2N4871 MOTOROLA Unijunction 6/9
25 + 5/9 100 + 4/9

2N3055 1/2 WATT POWER 15/-
25 + 13/- 100 + 11/-

56CAV Gallium Arsenide Infra-Red emitter 29/6 each. (Incl. data)

BC107/8/9 Planars 2/9

SL403 PLESSEY 3 WATT INT. CIRCUIT AMPLIFIER 49/6

OC711 1ST EQUIVALENT PHOTO TRANSISTOR 9/6

LOGIC

1-6 7-11 12+

uL900 9/9 9/- 8/-
uL914 9/9 9/- 8/-
uL923 13/- 12/- 11/-

Five Page Data and Circuits article 2/-
Larger quantity prices (100+ and 1,000+) on application.

Plastic Spreader 1/6

SILICON RECTIFIERS

PIV	200mA	750mA	2 Amp	10 Amp
50	6d	1/-	2/3	-
100	9d	1/6	2/3	4/6
200	1/3	2/-	2/9	5/-
400	-	2/6	4/-	8/-
600	-	3/9	5/-	11/3
1000	-	6/-	6/6	14/-

THYRISTORS-SCRs

PIV	1A	3A	10A	30A	100A
50	7/6	9/-	7/6	25/-	20/-
100	-	10/-	10/-	30/-	22/-
200	8/6	-	12/6	42/-	35/-
300	-	11/-	-	51/-	-
400	9/6	12/6	15/-	60/-	45/-
600	-	-	20/-	84/-	120/-
800	-	-	-	-	-

NEW SPECIAL ITEMS!!

40G02 - Dual Gate MOS-FET 9/- each
L14B - Photo-Darlington Amplifier 28/6
MGA100 - Gallium Arsenide Infra Red Source Light 35/-
31F2 - Infra Red Detector Diode 28/6
3N84 - Silicon Controlled Switch 29/6
TAA320 - Monolithic IC with MOS-FET input followed by Bi-Polar transistor 13/6

Datasheets 1/- on request - free with above items.

COMPONENTS

RESISTORS 1 or 1/2 Watt 5% LOW NOISE CARBON FILM. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 ohms and decades (x 10, x100, x1,000, x10,000) 1 Meg etc. to 8.2 Megohms (10% tolerance). PRICES: 1-25 4d, 26-99 3d, 100+2d (your selection) and/or 1/2 Watt mixed).

SKELETON PRESET POTS. 20% Tol. Linear. Low noise. Available in sub-miniature or standard size, horizontal or vertical. 100, 250, 500, 1 Meg, 2.5 Meg, 5 Meg, 10K, 25K, 50K, 100K, 250K, 500K, 1 Meg, 2.5 Meg, 5 Meg. NEW PRICE: 1/- each or any selection of 12 pieces 10/-.

ELECTROLYTIC CAPACITORS (Mullard). -10% to +50% tol. Subminiature (all values in µF).

4V	8	32	64	125	250	400
6.4V	6.4	25	50	100	200	320
10V	4	16	32	64	125	200
16V	2.5	10	20	40	80	125
25V	1.6	6.4	12.5	25	50	80
40V	1	4	8	16	32	50
64V	0.64	2.5	5	10	20	32
Price	1/6	1/3	1/2	1/-	1/1	1/2

MIN. POLYESTER CAPACITORS. Printed circuit type 250 Vdc working. 0.01, 0.015, 0.022, 7d each; 0.033, 0.047, 8d each; 0.068, 0.10, 9d each.

VEROBOARD 0.15" Matrix FLUX COATED. 2 1/2 x 3 1/2, 3 1/2 x 5 1/2, 3 1/2 x 3 1/2, 3 1/2 x 3 1/2, 3 1/2 x 5 1/2, 5 1/2 x 3 1/2, 1 1/2 x 1 1/2. BARGAIN PACK of 36 square inches all good size pieces only 10/- pack.

VEROBOARD 0.1" Matrix. 3 1/2 x 2 1/2, 3 1/2.

VEROPINS for 0.15", 36 pieces 3/-.

VER CUTTER 9/- (including free sample pieces).

S-DeCs Single "DeC" with accessories and enclosed project manual... 29/6

"DeC" kit contains two "DeC" component tray accessories, instruction book, all packed in attractive plastic box... 117/6

"4-DeC" kit contains four "DeCs", accessories, manual, etc. ... 117/6

BOOKS FROM STOCK

General Electric Transistor Manual, 660 pages of data and circuits... 29/6

RCA Transistor Manual, 554 pages includes SCR circuits... 28/6

Designers' Guide to British Transistors. Excellent data book lists over 1,000 common types plus Computer-selected substitution chart... 25/-

(ADD 2/6 POST & PACKING FOR ALL BOOKS)

NEONS

Signal neons for many types of circuit, type "N" Price 1/6 each or 16/- dozen.

HEATSINKS. Suitable for 2 x OC35, etc. As used in commercial equipment. Type 10D ... 65/6

ALUMINIUM CHASSIS

6 x 4 x 2 1/2" with reinforced corners 6/9 each (P & P 1/6). Atty. panel to fit 1/6. MaxW pin to fit 2/-. Many other sizes in stock up to 12 x 8 x 2 1/2" (see catalogue).

ZENER DIODES. 400mW 10% Tolerance. Complete range preferred values 3 volt to 30 volt, each ... 3/6

SOLAR CELLS

B2M 0.2-0.4 volts @ 2mA Selenium type ... 12/6

B3M 0.2-0.4 volts @ 11-21mA Selenium type ... 19/6

SIM 0.3-0.4 volts @ 10-16mA Silicon ... 12/6

S4M 0.3-0.4 volts @ 25-40mA Silicon ... 33/6

ULTRASONIC TRANSDUCERS

Operate at 40Kcs. Can be used for remote control systems without cables or electronic links. Type 1404 transducers can transmit and receive.

FREE: With each pair our complete transmitter and receiver circuit.

PRICE £5.10 Pair (Sold only in pairs)

"YOU'LL BE KNOCKED OUT BY OUR NEW CAT."

Prices quoted are current at time of going to press and may be subject to variation. Semiconductors offered bear Manufacturers' original markings and are subject to our full replacement guarantee if not to published specifications.

WE DO NOT offer "Re-marked" Semiconductors.

Our 1969/70 Catalogue is available free on request.

Please enclose a stamped addressed envelope with any queries. Quantity Prices on application.

Retail: Cash with order, please. Trade: Please furnish usual references if Credit facilities required.

Post & Packing 1/- per order (FIRST CLASS).


MAIL ORDER DEPT. & RETAIL SHOP -
LST, 7 Coptford Road, Brentwood, Essex
Telephone: 226470/1 (Sales Department)
EXPORT ENQUIRIES PARTICULARLY WELCOME

VALUE ALL THE WAY

QUALITY-TESTED PAKS

6 Matched Trans. OC44/45/81/81D	10/-
20 Red Spot AF Trans. PNP	10/-
16 White Spot RF Trans. PNP	10/-
5 Silicon Rects. 3 A 100-400 PIV	10/-
2 10 A Silicon Rects. 100 PIV	10/-
1 OC1140 Trans. NPN Switching	10/-
1 12 A SCR 100 PIV	10/-
3 Sil. Trans. 25303 PNP	10/-
200 Mc/s Sil. Trans. NPN BSY26/27	10/-
3 Zener Diodes 1W 33V 5% Tol.	10/-
4 High Current Trans. OC42 Evt.	10/-
4 Power Transistors 1 OC26 1 OC35	10/-
5 Silicon Rects. 400 PIV 250mA	10/-
4 OC75 Transistors	10/-
1 Power Trans. OC20 100V	10/-
10 OA202 Sil. Diodes Sub-min.	10/-
2 Low Noise Trans. NPN 2N929/30	10/-
1 Sil. Trans. NPN VCB 100 ZT86	10/-
4 OA81 Diodes	10/-
4 OC72 Transistors	10/-
4 OC77 Transistors	10/-
4 Sil. Rects. 400 PIV 500mA	10/-
5 GET884 Trans. Evt. OC44	10/-
5 GET883 Trans. Evt. OC45	10/-
2 2N708 Sil. Trans. 300 Mc/s NPN	10/-
3 GT31 LF Low Noise Germ. Trans.	10/-
6 IN914 Sil. Diodes 75 PIV 75mA	10/-
8 OA95 Germ. Diodes Sub-min. IN69	10/-
3 NPN Germ. Trans. NKT773 Evt.	10/-
2 OC22 Power Trans. Germ.	10/-
2 OC25 Power Trans. Germ.	10/-
4 AC128 Trans. PNP High Gain	10/-
4 AC127/128 Comp. pair PNP/NPN	10/-
2 2N1307 PNP Switching Trans.	10/-
3 AF116 Type Trans.	10/-
3 AF117 Type Trans.	10/-
7 OC81 Type Trans.	10/-
3 OC171 Trans.	10/-
2 2N2926 Sil. Epoxy Trans.	10/-
7 OC71 Type Trans.	10/-
2 2S701 Sil. Trans. Texas	10/-
10 A 600 PIV Sil. Rects. 1S45R	10/-
3 BC108 Sil. NPN High Gain Trans.	10/-
1 2N910 NPN Sil. Trans. VCB 100	10/-
2 1000 PIV Sil. Rect. 1 S A R5310 AF	10/-
3 BSY95A Sil. Trans. NPN 200 Mc/s	10/-
3 OC200 Sil. Trans.	10/-
2 GET880 Low Noise Germ. Trans.	10/-
1 AF139 PNP High Freq. Trans.	10/-
3 NPN Trans. 1 ST141 & 2 ST140	10/-
4 Mad's 2 MAT100 & 2 MAT120	10/-
3 Mad's 2 MAT101 & 1 MAT121	10/-
4 OC44 Germ. Trans. AF	10/-
3 AC127 NPN Germ. Trans.	10/-
1 2N3906 Sil. PNP Trans. Motorola	10/-
2 Sil. Power Rects. BZY13	15/-
1 Sil. Power Trans. NPN 100 Mc/s	15/-
1 TK201A	15/-
2 2N1132 PNP Epitaxial Planar Sil.	15/-
2 2N697 Epitaxial Planar Trans. Sil.	15/-
4 Germ. Power Trans. Evt. OC16	15/-
1 Unijunction Trans. 2N2646	15/-
2 Sil. Trans. 200 Mc/s 60Vcb ZT83/84	15/-
1 Tunnel Diode AEX111 1050 Mc/s	15/-
2 2N2712 Sil. Epoxy Planar HFEZ25	15/-
8 BY100 Type Sil. Rects.	20/-
25 Sil. and Germ. Trans. Mixed, all marked, New	30/-

GIRO No. 388-7006

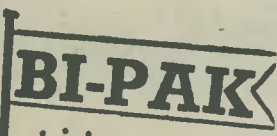

500, Chesham House,
150 Regent Street,
LONDON, W.1.

KING OF THE PAKS Unequalled Value and Quality SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No. 120 Glass Sub-min. General Purpose Germanium Diodes	10/-
U2 60 Mixed Germanium Transistors AF/RF	10/-
U3 75 Germanium Gold Bonded Diodes sim. OAS, OAA7	10/-
U4 40 Germanium Transistors like OC81, AC128	10/-
U5 60 200mA Sub-min. Sil. Diodes	10/-
U6 40 Silicon Planar Transistors NPN sim. BSY95A, 2N706	10/-
U7 16 Silicon Rectifiers Top-Hat 750mA up to 1,000V	10/-
U8 50 Sil. Planar Diodes 250mA OA/200/202	10/-
U9 20 Mixed Volts 1 watt Zener Diodes	10/-
U11 30 PNP Silicon Planar Transistors TO-5 sim. 2N1132	10/-
U13 30 PNP-NPN Sil. Transistors OC200 & 2S104	10/-
U14 150 Mixed Silicon and Germanium Diodes	10/-
U15 30 NPN Silicon Planar Transistors TO-5 sim. 2N697	10/-
U16 10 3-Amp Silicon Rectifiers Stud Type up to 1000 PIV	10/-
U17 30 Germanium PNP AF Transistors TO-5 like ACY17-22	10/-
U18 8 6-Amp Silicon Rectifiers BZY13 Type up to 600 PIV	10/-
U19 30 Silicon NPN Transistors like BC108	10/-
U20 12 1.5-amp Silicon Rectifiers Top-Hat up to 1,000 PIV	10/-
U21 30 A.F. Germanium alloy Transistors 2G300 Series & OC71	10/-
U23 30 Mad's like MAT Series PNP Transistors	10/-
U24 20 Germanium 1-amp Rectifiers GJM up to 300 PIV	10/-
U25 25 300 Mc/s NPN Silicon Transistors 2N708, BSY27	10/-
U26 30 Fast Switching Silicon Diodes like IN914 Micro-min	10/-
U28 Experimenters' Assortment of Integrated Circuits, untested, Gates, Flip-Flops, Registers, etc., 8 Assorted Pieces	20/-
U29 10 1 amp SCR's TO-5 can up to 600 PIV CRS1/25-600	20/-
U31 20 Sil. Planar NPN trans. low noise AF 2N3707	10/-
U32 25 Zener diodes 400mW D07 case mixed Volts, 3-18	10/-
U33 15 Plastic case 1 amp Silicon Rectifiers IN4000 series	10/-
U34 30 Sil. PNP alloy trans. TO-5 BCY26, 2S302/4	10/-
U35 25 Sil. Planar trans. PNP TO-18 2N2906	10/-
U36 25 Sil. Planar NPN trans. TO-5 BFY50/S1/52	10/-
U37 30 Sil. alloy trans. SO-2 PNP, OC200 2S322	10/-
U38 20 Fast Switching Sil. trans. NPN 400 Mc/s 2N3011	10/-
U39 30 RF Germ. PNP trans. 2N1303/5 TO-5	10/-
U40 10 Dual trans. 6 lead TO-5 2N2060	10/-
U41 30 RF Germ. trans. TO-1 OC45 NKT772	10/-
U42 10 VHF Germ. PNP trans. TO-1 NKT667 AF117	10/-

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

NEW LOW PRICE TESTED S.C.R.'S SIL. RECTS. TESTED

1 Amp (TO-5) 3 Amp (TO-66) 7 Amp (TO-48)	PIV 750mA 3A 10A 30A
PIV Each 50 50 50	5/- 2/9 4/3 9/6
50 4/6 100 6/6 100 10/6	100 1/3 3/3 4/6 15/2
100 7/- 200 7/6 200 11/6	200 1/9 4/- 4/9 20/6
400 8/6 400 9/6 400 13/6	300 2/3 4/6 6/6 22/6
600 10/6 600 11/6 600 15/6	400 2/6 5/6 7/6 25/6
800 12/6 800 14/- 800 18/-	500 3/3 6/- 8/6 30/6
	600 3/6 6/9 9/- 37/-
	800 3/6 7/6 11/- 40/-
	1000 5/- 9/3 12/6 50/-
	1200 6/6 11/6 15/-

16 Amp (TO-48) 30 Amp	PIV Each 25 20 Eakh
50 10/6 50 20/6	100 12/6 50 23/-
200 15/- 100 28/-	400 18/6 200 32/-
600 25/- 400 35/-	800 30/- 800 80/-

2 Amp POTTED BRIDGE RECTIFIERS	200V, 10/-, 600V, 15/-, 800V, 20/-
--------------------------------	------------------------------------

TRANSISTOR EQUIVALENT & SPECIFICATION BOOK

(German publication). A complete cross reference and equivalent book for European, American and Japanese Transistors. Exclusive to BI-PAK. 15/- each.

PRINTED CIRCUITS EX-COMPUTER

Packed with semiconductor components, 10 boards give a guaranteed 30 trans. and 30 diodes. Our price 10 boards 10/-, Plus 2/- P. & P.

PLEASE NOTE. To avoid any further increase Postal Charges to our Customers and enable us to keep our "By Return Postal service" which is second to none, we have re-organized and streamlined our Despatch Order Department and we now request you to send all your orders together with your remittance, direct to our Warehouse and Despatch Department, postal address: BI-PAK SEMICONDUCTORS, Despatch Dept., P. O. BOX 6, WARE, HERTS. Postage and packing still 1/- per order. Minimum order 10/-.

SILICON HIGH VOLTAGE RECTIFIERS

10-Amp 3-K.V. (3000 P.I.V.) Stud Type with Flying Leads. 16/- each

UNIUNCTION

UT46, Evt. 2N2646, Evt. TIS43, BEN3000
5/6 EACH
25-99 5/- 100 up 4/-

NPN SILICON PLANAR
BC107/8/9, 2/- each; 50-99, 1/10; 100 up, 1/8 each; 1,000 off, 1/6 each. Fully tested and coded TO-18 case.

PNP SIL. PLASTIC TRANS.
Similar to 2N3702, uncoded but fully tested, 1/6 each; 25-99, 1/3 each; 100 up, 1/- each.

PHOTO TRANS. OCP71 Type. 8/6

INTEGRATED CIRCUITS

BI-PAK MONOLITHIC AMPLIFIERS (TO-5 8 lead)

BP709C, Operational amplifier, 15/- each.
BP701C, Operational amplifier (with Zener output), 12/6 each.


BP702C, Operational amplifier (with direct output), 12/6 each.
BP501, Wide band amplifier, 18/- each.

BP521, Logarithmic wide band amp., 14/- each.
BP201C, General purpose amplifier (TO-5 8 lead), (voltage or current amp.), 12/6 each.

I.C. Operational Amplifier with Zener output. Type 701C. Ideal for P.E. Projects. 8 Lead TO-5 case. Full data.

Our price 12/6 each
5 off 11/- each. Large Qty. Prices quoted for.

AMPLIFIER As used in 'P.E.' projects

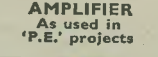

Identical encapsulation and pin configuration to the following: SL402-3, IC10 and IC403. Each circuit incorporates a 2.5-amp and class A.B. Power amp stage capable of delivering up to 3 watts RMS. Fully tested and guaranteed. Supplied complete with circuit details and data. CODED SP.1010. OUR LOWEST PRICE 30/- each. 10 up 25/- each.

OTHER MONOLITHIC DEVICES

BP424, Zero voltage switch, 8/6 each. This device is a monolithic I.C. that acts as combined threshold detector and trigger circuit for controlling a triac. It is designed to pulse the gate of a thyristor at the point of zero supply voltage, and therefore eliminate radio frequency interference when used with resistive loads.

D13D1 Silicon Unilateral switch 10/- each. A Silicon Planar, monolithic integral circuit having thyristor electrical characteristics, but with an anode gate and a built-in "Zener" diode between gate and cathode. Full data and application circuits available on request.

FAIRCHILD (U.S.A.) RTUL MICROLOGIC INTEGRATED CIRCUITS

Epoxy case T8-5 lead temp. range 15°C to 55°C. UL900, Buffer, 10/6 each. UL914, Dual two-input gate, 9/9 each. UL923 J-K-flip-flop, 13/6 each.

Complete data and circuits for the Fairchild I.C.'s available in booklet form priced 1/6.

MULLARD I.C. AMPLIFIERS

TAA243, Operational amplifier, 70/- each. TAA263, Linear AF amplifier, 18/6 each. TAA293, General purpose amplifier, 21/- each.

CA3020 RCA (U.S.A.) LINEAR INTEGRATED CIRCUITS

Audio Power Amplifier, 30/- each.

CADMIUM CELLS

ORP12 8/6
ORP60, ORP61 8/- each

AD161 AD162

NPN PNP MATCHED COMPLEMENTARY PAIRS OF GERM. POWER TRANSISTORS.

For mains driven output stages of Amplifiers and Radio receivers. OUR LOWEST PRICE OF 12/6 PER PAIR.

HIGH POWER SILICON PLANAR TRANSISTORS. TO-3. TEXAS 25034 NPN VCB100 1c 4A

FT. 15M/cs VCE100 Prot. 40W VEB8 hFE(mf) 60

Price 15/- each

2N3055 115W. SIL POWER NPN OUR PRICE 12/6 each

FULL RANGE OF ZENER DIODES

VOLT. RANGE 2-20V 400mW (DO-7 Case) 2/6 1-5W (Top-Hat) ... 3/6 10W (SO-10 Stud) 5/-

All fully tested 5% tol. and marked. State voltage required.

BRAND NEW TEXAS GERM. TRANSISTORS

Coded and Guaranteed Pak No. EQVT.

T1 8 2G371A OC71
T2 8 2G374 OC75
T3 8 2G376A OC81D
T4 8 2G381A OC81
T5 8 2G382T OC82
T6 8 2G344A OC44
T7 8 2G345A OC45
T8 8 2G378 OC78
T9 8 2G394 2N1302
T10 8 2G417 AF17

All 10/- each pack

2N2060 NPN SIL. DUAL TRANS. CODE D1699 TEXAS. OUR PRICE 5/- each.

120 VCB NIXIE DRIVER TRANSISTOR Sim. BSX21 & C407. 2N1893 FULLY TESTED AND CODED ND120. 1-24 3/6 each. TO-5 NPN 25 up 3/- each

Sil. trans. suitable for P.E. Organ. Metal TO-18 Evt. ZTX300 1/- each. Any Qty.

FREE One 10/- Pack of your own choice free with orders valued £4 or over.

NPN DIFFUSED SILICON PHOTO-DUO-DIODE TYPE 1S701 (code 175) for Tape Readout, high switching and measurement indicators. 50V. 250mW. OUR PRICE 10/- EACH, 50 OR OVER 8/6. EACH. FULL DETAILS.

FET'S

2N 3819..... 8/-
2N 3820..... 25/-
MPF105..... 8/-

LOW COST FET'S

Fully Tested, Guaranteed Parameters equit. to 2N3819, MPF102, 2N5459, 1-24 7/- each; 25-99 6/3 each; 100 up 5/6 each. CODED FE19. Full data sent. TO-72 case.

BI-PAK MONOLITHIC DIGITAL CIRCUITS (10 lead T-5)

BP305A, 6-Input AND gate, 9/6 each.
BP314A, 7-Input NOR gate, 9/6 each.

BP54A, Dual 3-Input NOR gate, 9/6 each.
BP316A, Dual 2-Input NOR gate (expandable), 9/6 each.

BP320A, J-K-Binary element, 11/6 each.
BP322A, Dual 3-Input OR gate, 9/6 each.

KING OF THE PAKS BI-PAK GUARANTEE SATISFACTION OR MONEY BACK

GUARANTEED TRANSISTORS

AD161-2	12/-	GET693	1/3	2N3055	16/6
AF239	10/-	HK041	2/6	2N3707	4/-
B5000G	11/3	HK101	2/-	2N3794	3/-
BD121	18/-	HK601	2/6	2N3983	5/8
BC107B	3/-	IS44	1/4	2N4058	4/6
BC168B	2/3	MEM564C	16/-	2N4285	3/-
BC169C	2/6	SF115	3/-	2N4289	3/-
BF167	5/3	TIS18	7/-	2N4291	3/-
BF178	9/-	TIS60M	4/8	2SB187	2/-
BF224	4/-	TIS61M	4/11	2SB405	5/-
BF225	4/-	2N706	2/7	2SD72	5/-
BFY51	4/-	2N2926G	2/6	40468A	7/6

RECTIFIERS:

800piv, 500mA Si. IS557, 3/-; 50piv, 100mA, 1/- Submin. Selenium Bridge, 30Vrms, 150mA dc, 3/6; Contact-cooled Sel. Bridge, 30Vrms, 700mA dc, 6/-; Silicon Bridge, 80Vrms, 1Adc, 10/- All new and perfect.

I.C. BARGAIN

Push-pull 0.5W amplifier, R.C.A. type CA 3020 ('In Your Workshop', Feb., '68). Uses from d.c. to v.h.f. are described in the makers' own APPLICATION NOTES, FREE WITH EACH I.C. Operable 3-9V, brand new, direct from makers.

BEST-EVER PRICE: ONLY 26/-

COMPONENT KITS

AMPLIFIER PACKAGES, Reliable and efficient, and still far cheaper than i.c.'s!

AX2	9V, up to 300mW	12/6
AX3	9V, up to 800mW in 8 ohms	22/6
AX4	24V, 5W, 8 ohms, 3W, 15 ohms	30/-
AX5	12-15V, 3W, 3-5 ohms. NEW!	35/-

RECEIVER PACKAGE. AX9, sensitive t.r.f., all-silicon circuit, no adjustments, reliable, adaptable, low drain. Printed circuit and all parts - still only 45/-

MINI MAINS PACK COMPS. 17/6



Mini Mains Transformers

MT9	9-0-9V, 80mA	12/6
MT6	6-0-6V, 100mA	13/6
MT12	12-0-12V, 50mA	13/6

CAPACITORS

Polystyrene: 160 V, small, low-loss, tol. 1pF or 2½% according to size. Prices: 10-39pF, 6d; 47-1500pF, 9d; 2200-15,000pF, 1/-; 22,000pF, 1/3. Stock list: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 82, 100, 120, 150, 180, 220, 270, 330, 390, 560, 680, 820, 1000, 1500, 2200, 3300, 4700, 6800, 8200, 10,000, 15,000, 22,000 pF.
Miniature Metallised Polyester: .01uf, 8d; .1uF, 10d; .22uF, 1/-.
Tuning: 300pF max. Jacksons Dilemin sub-min single tuner, 10/-.

RESISTORS

Carbon Film, ¼W, miniature, low noise. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82Ω and so on to 10M. Tol. ± 5% to 1M, 10% above 1M. All 3d. each.
Carbon Skeleton Presets. Submin., vertical, linear, 100mW. 50, 150, 500Ω and so on to 1.5M. Egen Type 467, 1/6 each.
Volume Control, 10K log. with d.p. switch and long aluminium spindle with flat. Standard size, Egen. 5/6 each.
R. F. CHOKES. Repanco: CH1, 2.5mH, 2/6; CH2, 5mH, 3/-; CH3, 7.5mH, 3/-; CH4, 10mH, 3/-; CH5, 1.5mH, 2/6. All small, ferrite-cored.
FERRITE RODS: 4in. or 4½in. x ½in., wound for MW (300pF), 5/-; unwound, 2/-; oval, unwound, 2 x ½ x ½in., with data, 2/6.
TRANSFORMERS, MINI. A.F.: Eagle LT700, 1200Ω c.t. to 3Ω, 280mW, 5/-; Repanco TT47 driver for single ended push-pull, 4.5 to (1) + (1), 6/-.
TELESCOPIC AERIAL: 7½in. opening to 47in., 9/-.
BATTERY HOLDER BH2 for two 1.5V pen cells, with snap connector, 2/6.
EARPIECES, all 3.5mm plugged, crystal, 4/9; magnetic, 8Ω, 2/6.

Read all about building a —

DIGITAL PROPORTIONAL

6-CHANNEL RADIO CONTROL OUTFIT

in "RADIO MODELLER" magazine

● SPECIAL OFFER —

TWO ISSUES—Containing the 2-part article on building up the Remcon "QUANTUM SIX" six function digital proportional superhet receiver and transmitter

for only 5/- (normally 7/-)

Send now, enclosing 5/- P.O. or cheque to:—

● RADIO MODELLER, (Dept. S.O.),
64 WELLINGTON ROAD, HAMPTON HILL, MIDDLESEX

There's Something for Everyone in the NEW HEATHKIT CATALOGUE!



- AUTO TUNE-UP METER
- D.I.Y. SPEAKER SETS
 - SEVERN AM/FM RADIO
- STEREO RECORD PLAYER
 - ELECTRONIC METRONOME
- FABULOUS STEREO HI-FI COMPACTS
- POWER SUPPLIES ● CAR RADIO
- D.I.Y. RADIOGRAM PACKS
- AIRCRAFT MONITOR RECEIVER
- GUITAR PRACTICE AMPLIFIER ● HI-FI SYSTEMS
- GENERATORS, RF, AUDIO, TV
- AMBASSADOR SPEAKERS ● TECHNICIANS' LOW-COST VVM
- MANY OTHER MODELS TOO NUMEROUS TO MENTION

Send for this
FREE Catalogue
and see for yourself, Today!



DAYSTROM LIMITED,
HEATHKIT DIVISION,
GLOUCESTER, GL2-6EE
Tel: Glos 29451. Telex 43216


To DAYSTROM LTD., GLOUCESTER, GL2-6EE
Please send me my free copy of the
1970 HEATHKIT CATALOGUE

NAME.....

ADDRESS.....

53/1

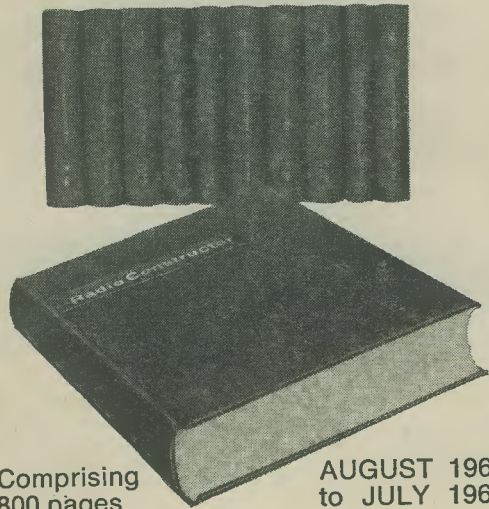BOUND VOLUME No. 22 of "The Radio Constructor" FOR YOUR LIBRARY



Comprising
800 pages
plus index

AUGUST 1968
to JULY 1969

PRICE **35/-** Postage 4/6

Special discount of 10/- for regular readers
Just cut the heading from each month's contents page, including title and month of issue, and this will be sufficient evidence of readership to qualify for the discount.

Thus regular readers will still retain their copies for workbench use, while having a splendid bound volume containing issues in mint condition.

PRICE 25/- Postage 4/6

Limited Number of Volume 21
(August 1967 to July 1968) still available
Price 35/- Postage 4/6

Available only from:-

Data Publications Ltd.
57 Maida Vale London W9

Now! A FAST EASY WAY TO LEARN BASIC RADIO AND ELECTRONICS



Build as you learn with the exciting new
TECHNATRON Outfit! No mathematics.

No soldering—but you learn the *practical* way.

Now you can learn basic Radio and Electronics at home—the *fast, modern* way. You can give yourself the essential technical 'know-how' sooner than you would have thought possible—read circuits, assemble standard components, experiment, build . . . and enjoy every moment of it. B.I.E.T.'s Simplified Study Method and the remarkable new TECHNATRON Self-Build Outfit take the mystery out of the subject—make learning *easy and interesting*.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

and what's more, **YOU'LL UNDERSTAND EXACTLY WHAT YOU ARE DOING.** The Technatron Outfit contains everything you need, from tools to transistors . . . even a versatile Multimeter which we teach you how to use. You need only a little of your spare time, the cost is surprisingly low and the fee may be paid by convenient monthly instalments. You can use the equipment again and again—and it remains your own property.

You **LEARN**—but it's as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build—and it's a good one—is really a bonus; this is first and last a *teaching* Course. But the training is as rewarding and interesting as any hobby. It could be the springboard for a career in Radio and Electronics or provide a great new, spare-time interest.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. Bite-size lessons—wonderfully clear and easy to understand, practical projects from a burglar-alarm to a sophisticated Radio set . . . here's your chance to master basic Radio and Electronics, even if you think you're a 'non-technical' type. And, if you want to carry on to more advanced work, B.I.E.T. has a fine range of Courses up to A.M.I.E.R.E. and City and Guilds standards.

Send now for free 164-page book. Like to know more about this intriguing new way to learn Radio and Electronics? Fill in the coupon and post it today. We'll send you full details and a 164-page book—'ENGINEERING OPPORTUNITIES'—Free and without any obligation.



BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. 370B, Aldermaston Court,
Aldermaston, Berkshire.

To: B.I.E.T., Dept. 370B, ALDERMASTON COURT,
ALDERMASTON, BERKS.

I would like to know more about your
Practical Radio & Electronics Course. Please
send me full details and FREE 164-page book.

name.....
address.....
.....age.....

POST
THIS
COUPON
NOW!

THE MODERN BOOK CO

TRANSISTOR, AUDIO AND RADIO CIRCUIT

For Radio Receivers, Radiograms, Record Players,
Tape Record Players and Hi-Fi Equipment

30s.

A Mullard Publication

Postage 1s.

Transistor Substitution Handbook
No. 19. 18s. Postage 1s.

Colour Television PAL System
by G. N. Patchett. 40s. Postage 1s.

Radio and Line Transmission, Vol. 3
by G. L. Danielson. 45s. Postage 1s.

Solid State Hobby Circuits Manual
by R.C.A. 17s. 6d. Postage 1s.

Transistor Manual
by General Electric Company. 21s.
Postage 1s. 6d.

SCR Manual
by General Electric Company. 25s. Postage 2s.

Transistor Transmitters for the Amateur
by Donald L. Stoner. 21s. Postage 1s.

110 Semiconductor Projects for the Home
Constructor by R. M. Marston. 18s. Postage 1s.

Practical Integrated Circuits
by A. J. McEvoy & L. McNamara. 18s.
Postage 1s.

Servicing with the Oscilloscope
by Gordon J. King. 28s. Postage 1s.

Hi-Fi in the Home
by John Crabbe. 40s. Postage 1s. 6d.

VHF-UHF Manual
by G. R. Jessop. 21s. Postage 1s.

Television Engineers' Pocket Book
by J. P. Hawker & J. A. Reddihough. 21s.
Postage 1s.

Questions & Answers Transistors
by Clement Brown. 10s. Postage 6d.

We have the Finest Selection of English and American Radio Books in the Country

19-21 PRAED STREET (Dept RC) LONDON W2

Telephone PADdington 4185

DENCO (CLACTON) LIMITED

355-7-9 OLD ROAD, CLACTON-ON-SEA, ESSEX

Our components are chosen by Technical Authors and Constructors throughout the World for their performance and reliability, every coil being inspected twice plus a final test and near spot-on alignment as a final check.

Our General Catalogue showing full product range	2s. 6d.
DTB4 Transistor & Valve circuitry for D.P. Coils	2s. 6d.
DTB9 Valve Type Coil Pack Application circuitry	2s. 6d.
MD.1 Decoder Circuitry for Stereo Reception	4s. 0d.

All post paid, but please enclose S.A.E. with all other requests in the interests of retaining lowest possible prices to actual consumers.

BARGAIN GIFT OFFER

SUPER SWISS WATCHES



GENTS WRISTWATCH

Ultra-modern styled watch complete with expanding bracelet in luxurious golden finish. 21-jewelled Swiss movement with automatic DAY and DATE indication in black and white clearcut figures. Centre second hand. All hands and 5-minute batons in attractive gold colour. One of the cleanest and clearest dials we've seen. Water protected and anti-magnetic. Electronically timed and tested. Screwback stainless steel back. SIX MONTHS WRITTEN GUARANTEE. List Price £6.14.0

Special Offer Price **89/6** plus 3/- P&P



LADIES WRISTWATCH

Very attractive ladies watch in a luxurious golden finish, with matching expanding bracelet. 21-jewelled Swiss movement with automatic date change. Handsome white dial with golden colour batons and numerals. Centre second sweep hand, minute and hour hands also in gold. This watch was specially selected for its attractive and easy-to-read dial design. Water protected and anti-magnetic. Electronically timed and tested. Screwback stainless steel back. SIX MONTHS WRITTEN GUARANTEE. List Price £4.19.6

Special Offer Price **67/6** plus 3/- P&P

RUSSIAN OPTICAL PRECISION

SUPERB 35mm CAMERA

TAKES NEEDLE-SHARP PICTURES BLACK & WHITE OR COLOUR




FREE CASE ENABLES ANYONE TO TAKE PROFESSIONAL QUALITY PHOTOGRAPHS

COSMIC 35 CAMERA

This camera is without doubt the best value camera on the market today. Reviewed by 'Amateur Photographer' in 1964 who judged it excellent value for money and 'capable of making first class exhibition prints of 20 x 16 inches'. SPECIFICATION: 3 element F.4 lens.

5-speed shutter 1/15th to 1/250th sec. 5 stops f.4 to f.16. Delayed action mech. allows self portraits. Depth of field indicator. Accessory shoe. Flash socket. Supplied complete with instruction booklet & superb P.V.C. Ever Ready Case. LIST PRICE £6.14.6. **Special Offer Price £5.0.0** plus 3/6 P&P

CAR COMPASS

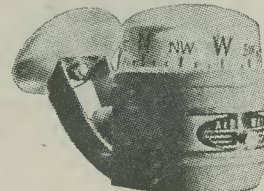

Extremely accurate compass manufactured by Sherrill Corporation of America, suppliers to the U.S. Government and Armed Forces. Fully compensatable with aviation type regulator magnets controlled by nylon gears. Leakproof under a wide range of temperatures. A scientifically designed instrument for all motorists and especially 'mobile' transmitter operators. Easily fitted. List Price 39/6.

Special Offer Price **29/6** plus 2/6 P&P

FLOAT ON AIR!



INFLATABLE ARMCHAIRS

Float on Air in a Bubble Chair. Trendsetting inflatable furniture that stores in a drawer. Tough vinyl material ensures long life. (Accidental punctures easily repaired). Available in gorgeous colours: Orange, Blue, Yellow, Black and Transparent. List Price 90/-.

Special Offer Price **69/6** plus 4/6 P&P

EMBOSSING PRESS

Grange Park, A41

ANSTAY HILL A42

Sunningdale A44



CONWAY VALE A46

1. ALBERT ROAD A43

Emboss your own notepaper, etc. and eliminate printing costs. Most useful home and office accessory that brings prestige to correspondence and avoids errors in replies. Choice of five print styles, as illustrated. (Print styles shown approx. half size). Choice of 'in line' or 'staggered' setting. New dies readily available when required. (Please note that there is a limit of 20 letters or figures per line).

SPECIAL PRICE: **39/6** for 4 lines **49/6** for 5 lines POST FREE

Please send the following:
(TICK WHERE APPLICABLE)

- Gents Wristwatch.....
- Ladies Wristwatch.....
- Cosmic 35 Camera.....
- Car Compass.....
- Inflatable Armchair.....
(Colour required
- Embossing Press.....
(Style of type required.....)
(Address 'in line' or staggered)

I enclose cheque/crossed postal order (made payable to Flairline

Supplies) for £.....

NAME.....

ADDRESS.....

BLOCK CAPITALS PLEASE

ALL GOODS SUPPLIED UNDER SEVEN-DAY MONEY-BACK GUARANTEE

FLAIRLINE SUPPLIES SUITE 11/12, SECOND FLOOR, 52 SHAFTESBURY AVENUE, LONDON, W.1

BI-PRE-PAK LIMITED

FULLY TESTED AND MARKED

AC107	3/-	OC170	3/-
AC126	2/6	OC171	4/-
AC127	2/6	OC200	3/6
AC128	2/6	OC201	7/-
AC176	5/-	2G301	2/6
ACY17	3/-	2G303	2/6
AF114	4/-	2N711	10/-
AF115	3/6	2N1302-3	4/-
AF116	3/6	2N1304-5	5/-
AF117	3/6	2N1306-7	6/-
AF186	10/-	2N1308-9	8/-
AF139	10/-	2N3819	9/-
AF239	12/6		
BFY50	4/-	Power Transistors	
BSY25	7/6	OC20	10/-
BSY26	3/-	OC23	10/-
BSY27	3/-	OC25	8/-
BSY28	3/-	OC26	5/-
BSY29	3/-	OC28	7/6
BSY95A	3/-	OC35	5/-
OC41	2/6	OC36	7/6
OC44	2/6	AD149	10/-
OC45	2/6	AUY10	30/-
OC71	2/6	2N3055	15/-
OC72	2/6	Diodes	
OC73	3/6	AAY42	2/-
OC81	2/6	OA95	2/-
OC81D	2/6	OA70	1/9
OC83	4/-	OA79	1/9
OC139	2/6	OA81	1/9
OC140	3/6	IN914	1/6

TRY OUR X PACKS FOR UNEQUALLED VALUE

XA PAK

Germanium PNP type transistors, equivalents to a large part of the OC range, i.e. 44, 45, 71, 72, 81, etc.

PRICE £5 PER 1,000
POST & PACKING 4/6 U.K.

XB PAK

Silicon TO-18 CAN type transistors NPN/ PNP mixed lots, with equivalents to OC200-1, 2N706A, BSY27/29, BSY95A.

PRICE £4.50 PER 500 £8 PER 1,000
POST & PACKING 2/6 U.K.

XC PAK

Silicon diodes miniature glass types, finished black with polarity marked, equivalents to OA200, OA202, BAY31-39 and DK10, etc.

PRICE £4.10.0 PER 1,000
POST & PACKING 2/6 U.K.

ALL THE ABOVE UNTESTED PACKS HAVE AN AVERAGE OF 75% OR MORE GOOD SEMI-CONDUCTORS. FREE PACKS SUPPLIED WITH THESE ORDERS. ORDERS MUST NOT BE LESS THAN THE MINIMUM AMOUNTS QUOTED PER PACK.

NEW TESTED & GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. .3 to .5V, .5 to 2mA.	10/-
B77	2	AD161-AD162 - NPN/PNP Trans. Comp. output. Pair	10/-
B81	10	Reed Switches. Mixed types large and small.	10/-
B89	2	5SP5 Light Sensitive Cells. Light res. 400Ω, Dark 1MΩ.	10/-
B91	8	NKT163/164 PNP Germ. to -5. Equiv. to OC44, OC45.	10/-
B92	4	NPN Sil. Trans. A06=BSX 20, 2N2369, 500 MHz, 360 mW.	10/-
B93	5	GET113 Trans. equivalent to ACY17-21 PNP Germ.	10/-
B94	6	NPN Sil. Planar Epitaxial Trans. CS4 similar to BSY38 or BC108.	10/-
B96	5	2N3136 PNP Sil. Trans. TO-18. HFE100-300. IC.600mA. 200 MHz.	10/-
B98	10	XB112 & XB102 equiv. to AC126, AC156, OC81/2, OC71/2, NKT271, etc.	10/-
B99	200	Capacitors, Electrolytics, Paper, Silver Mica, etc. Postage on this pak 2/6.	10/-
H4	250	Mixed Resistors. Post & packing 2/-.	10/-
H7	40	Wirewound resistors. Mixed values. Postage 1/6.	10/-

FREE! Packs of your own choice up to the value of 10/- with orders over £4.

LOOK! TRANSISTORS ONLY 1/- EACH

TYPE A

PNP SILICON ALLOY TO-5 CAN

Spec:- hFE 15-100. ICER at VCE=20V 1mA Max. These are of the 2S300 range which is a direct equivalent to the OC200-205 range.

TYPE B

PNP SILICON PLASTIC ENCAPSULATION

Spec:- hFE 10-200 ICER at VCE=10V 1mA Max. These are of the 2N3702-3 and 2N4059-62 range.

TYPE C

NPN SILICON TO-18 CAN

Spec:- hFE 50-900 ICER at VCE=20V 1mA Max. These are similar to BC108-9 Types.

NEW UNMARKED UNTESTED PAKS

B78	12	Integrated Circuits, Data & Circuits of types, supplied with orders.	10/-
B80	8	Dual Trans. Matched O/P pairs NPN. Sil. in TO-5 can.	10/-
B82	10	OC45, OC810 & OC81 Trans. Mullard glass type.	10/-
B83	200	Trans. Makers rejects. NPN/ PNP. Sil. & Germ.	10/-
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202.	10/-
B66	150	High quality Germ. Diodes. Min. glass type.	10/-
B86	50	Sil. Diodes sub. min. IN914 & IN916 types.	10/-
B87	100	Germ. PNP Trans. equiv. to OC44, OC45, OC81, etc.	10/-
B88	50	Sil. Trans. NPN. PNP. equivalent to OC200/1, 2N706A, BSY95A, etc.	10/-
B60	10	7 Watt Zener Diodes. Mixed voltages.	10/-
H5	16	1 Amp. Plastic Diodes. 50-1000 Volts.	10/-
H6	40	250mW. Zener Diodes DO-7 min. Glass Type.	10/-

Return of the unbeatable P.1 Pak.

Now greater value than ever

Full of short lead semiconductors and electronic components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP and NPN, and a host of diodes and rectifiers. Mounted on printed circuit panels. Identification chart supplied to give some information on the transistors.

P.1 PLEASE ASK FOR PAK P.1 ONLY 10/-
2/- P & P on this Pak.


MAKE A REV. COUNTER for your Car. The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a perfectly linear and accurate rev. counter for 20/- each any car. State 4 or 6 cylinder.

FREE CATALOGUE AND LISTS for:- ZENER DIODES TRANSISTORS, RECTIFIERS FULL PRE-PAK LISTS & SUBSTITUTION CHART

MINIMUM ORDER 10/- CASH WITH ORDER PLEASE. Add 1/- post and packing per order. OVERSEAS ADD EXTRA FOR AIRMAIL.

MULLARD DATA BOOK

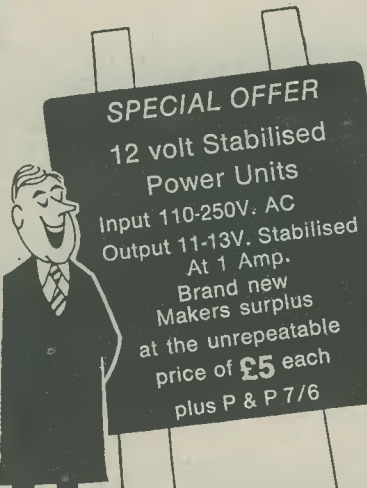Semiconductor & Valve Data & equivalents. 3/6
Postage 6d. EACH



SPECIAL OFFER
12 volt Stabilised Power Units
Input 110-250V. AC
Output 11-13V. Stabilised At 1 Amp.
Brand new Makers surplus at the unrepeatable price of £5 each plus P & P 7/6

FREE! A WRITTEN GUARANTEE WITH ALL OUR TESTED SEMICONDUCTORS

BI-PRE-PAK LTD DEPT. C, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

IF YOU HAVE

A HOME RADIO CATALOGUE

Ordering components is easier and quicker with our new

Credit Account Service



Just a phone call away

Our aim in life at Home Radio Components Ltd. is to make *your* life happier and less complicated! To this end we have recently introduced a Credit Account Service, one advantage of which is that you can order components by telephone *any time, any day*. If you phone out of shop hours a recording machine will take your message for us to deal with as soon as we open shop next day.

There are *other* advantages to the new Service – if you want to order by post we provide Order Forms and *Prepaid* Envelopes. You settle your account just once per month. We stipulate *no* minimum order value. Of course for ordering your components you first need our Catalogue, and after you have been in the Service 12 months we regularly send you an up-to-date catalogue – FREE!

For full details of our Credit Account service just drop us a line or phone 01-648 8422.

IF YOU HAVEN'T...



Whether or not you want to use the Credit Account Service described above, you certainly need the Home Radio Components Catalogue if you construct or repair radio and electronic gadgets. The catalogue has 350 pages, lists 8,000 components and has over 1,500 illustrations. It contains six vouchers, each worth 1/- when used as indicated. Post the coupon with 12/- (8/6 plus 3/6 postage and packing) and we will send a catalogue by return of post. By the way, we supply *free* a 30-page Price Supplement and a Bookmark giving electronic abbreviations.

Please write your Name and Address in block capitals

Name.....

Address.....

.....

.....

HOME RADIO (Components) LTD., Dept RC,
234-240 London Road, Mitcham, Surrey CR4 3HD



THE Radio Constructor



Incorporating THE RADIO AMATEUR

JANUARY 1970

Vol. 23 No. 6

CONTENTS

Published Monthly (1st of Month)
First Published 1947

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9

Telephone 01-286 6141 Telegrams Databux, London

© Data Publications Ltd., 1970. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription 42s. (U.S.A. and Canada \$5) including postage. Remittances should be made payable to "Data Publications Ltd.". Overseas readers please pay by cheque or International Money Order.

Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. Queries should be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production.—Letterpress.

TORCH BATTERY POWER PACK	330
EXPERIMENTAL RECORD PLAYER AMPLIFIER (Suggested Circuit No. 230)	333
QSX	335
NEWS AND COMMENT	336
SPACE DX	338
LOW-COST REGENERATIVE RECEIVER	339
ELECTRICAL FAULT-FINDING 'DOWN UNDER'	341
VERSATILE A.C. MILLIVOLTMETER	342
DESIGN FOR A CLASS 'A' BATTERY AMPLIFIER	349
HIGH-SELECTIVITY T.R.F. RECEIVER	352
CAN ANYONE HELP ?	359
CONSTANT CURRENT GENERATOR FOR OHMMETER CONVERSION	360
CURRENT TRENDS	362
METER SHUNTS (Understanding Radio)	363
CURRENT SCENE - TOP BAND DX	368
IN YOUR WORKSHOP	369
RADIO TOPICS	376
LAST LOOK ROUND	377
RADIO CONSTRUCTOR'S DATA SHEET No. 34 (R.M.S., Peak and Average Values)	iii

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London, W.9.

The Radio Constructor is printed by Kent Paper Company Ltd, London and Ashford, Kent.

**FEBRUARY ISSUE WILL BE PUBLISHED
ON FEBRUARY 1st**

TORCH BATTERY POWER PACK

by


R. L. GRAPER

Quite a few constructors, including in particular the younger enthusiasts, prefer to power transistor receivers and similar equipment with torch batteries rather than with the standard batteries that are specifically intended for transistor work. Apart from the possibility of initial cost saving, this approach certainly makes it possible for the batteries to serve a double function during their useful life. The article published here describes a simple home-built battery case with external connectors which can accommodate two 1289 torch batteries

THE BATTERY UNIT DESCRIBED CONSISTS OF A SIMPLE home-constructed case in which two 1289 torch batteries are fitted. These are automatically connected in series when the case lid is fitted, with the result that a 9 volt supply becomes available for transistor radios and similar equipment. One advantage with the unit is that it is not necessary to solder any connections to the battery terminal strips, and the batteries can at any time be employed for other uses, if desired.

ASSEMBLY

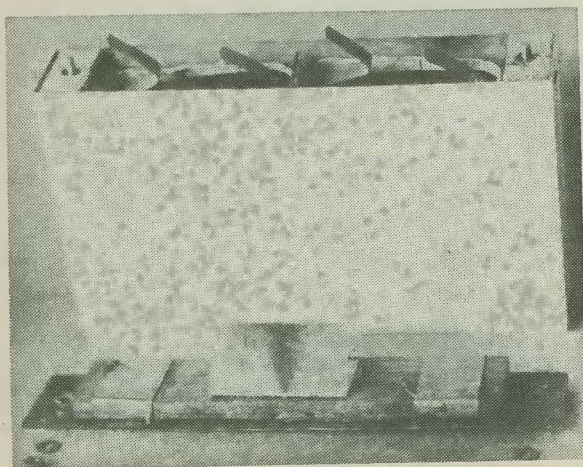The completed assembly is illustrated in Fig. 1. This diagram shows one side panel partly cut away



The unit with its lid removed

to reveal construction and the positions of the batteries. Above these appears the contact cover and lid. This is shown partly assembled, illustrating the contact strips at the ends for positive and negative connections, and the central springy contact for connecting the batteries in series. The end strips are wrapped around the plywood and then glued. The top panel is glued to the plywood panel, and has clearance holes for the plug and socket connections. The latter are taken from an old PP9 battery or similar, the insulated panel on which they are mounted being cut, as required, to fit the present assembly.

The various parts forming the unit are shown in Fig. 2. Six lengths of $\frac{1}{2}$ in. square planed stripwood are cut and glued to form two U-shaped sections. These are then glued together, in their turn, to give a single cradle 1in. wide. On to this are glued the two side and two end panels, these being cut from Formica laminate $\frac{1}{32}$ in. thick. Due allowance has been given in the sizes of these panels so that the edges can be bevelled at 45° and a knife edge fitting secured. There is no Formica panel at the bottom of the case. The bottom consists of the four bottom panel edges and the bottom surfaces of the wood, these all being cleaned up flush.

The top cover is formed from a rectangle of $\frac{1}{8}$ in. plywood, size $4\frac{1}{8}$ in. by 1in. This is carefully sanded down to fit into the top opening of the box. A recess is cut out for the battery connector panels. After soldering appropriate lengths of wire to them, these are glued in position as also are the two end contacts. Note that a groove is needed for the wire to the negative connector, and that the wires must be soldered to the end contact strips. A V-shaped piece of brass foil, as illustrated in Fig. 1, is also glued at the centre of the plywood. This contact connects together the inner terminal strips of the batteries,

THE RADIO CONSTRUCTOR


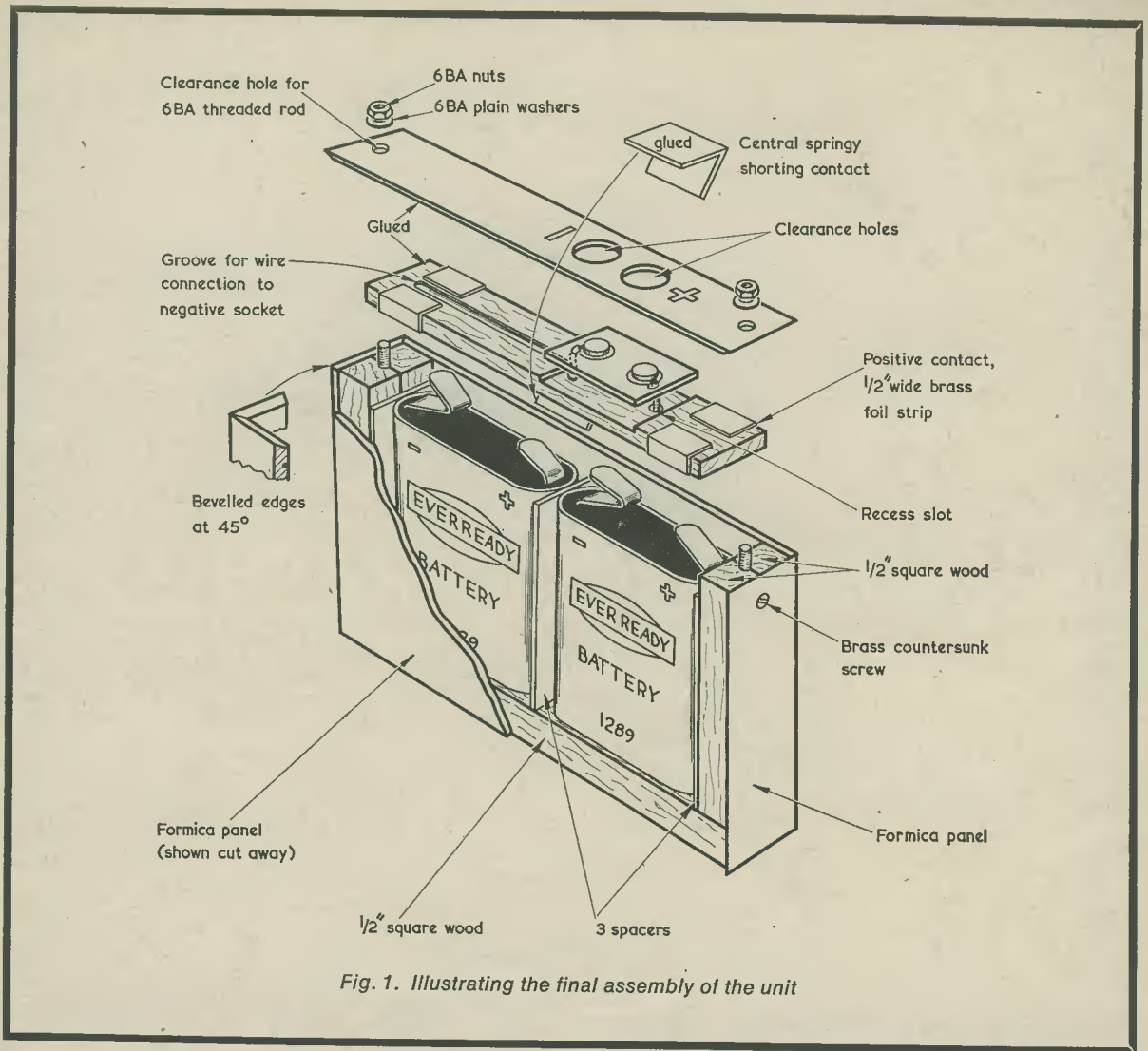


Fig. 1. Illustrating the final assembly of the unit

causing them to be in series. No external connection is made to this centre contact. Finally, the top surface of the contact panel is treated with Evo-Stik, as also is the Formica top panel above, and the two brought into contact to form the complete lid. The output connectors are then marked "+" and "-" to show their polarity. This should, of course, correspond to their polarity when fitted to a standard battery.

Two 3/4 in. lengths of 6BA brass studding act as fixtures for the lid. These lengths are sunk into suitably drilled holes in the wooden cradle as shown. They project by about 1/4 in. and are securely fixed at this height by short countersunk brass wood-screws which engage them through the end panels. See Fig. 1. The three spacers illustrated can be of cardboard or plastic laminate, and are pushed in after the batteries have been lowered into the case. They prevent excessive movement of the batteries.

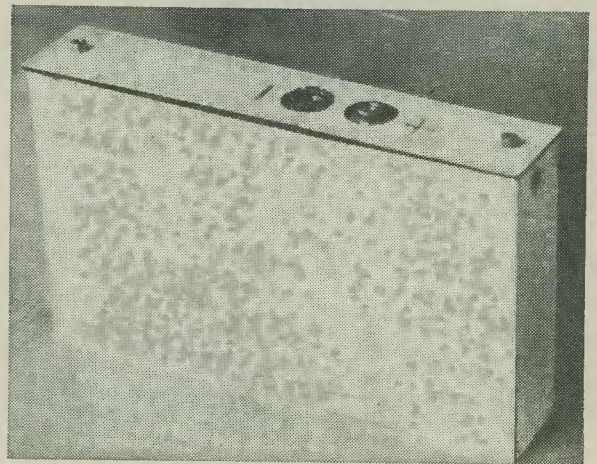The top strips of the batteries should be bent as shown in Fig. 1 and should be nearly level with the top of the box. Very good contact will then be obtained when the cover is fitted and the 6BA nuts



When the lid is secured in place a 9 volt output is available at the two top connectors

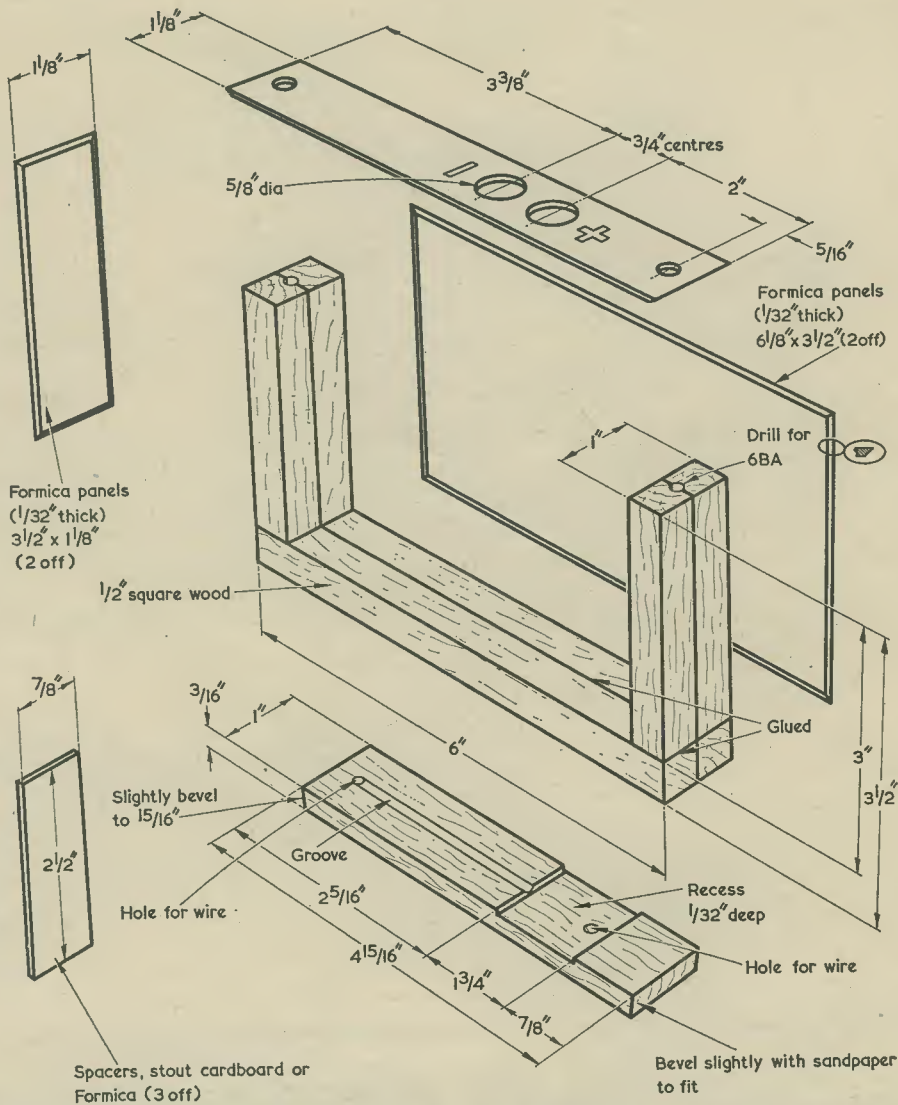


Fig. 2. The component parts of the unit have the dimensions given here

screwed down. The form of construction described gives a very robust unit, and replacement of the two batteries takes but a few moments.

Although this unit was intended for a 9 volt output, there is no reason why a larger model could not be made for higher voltages. ■

SGS PUBLICATIONS

Currently available from SGS (United Kingdom) Ltd. are two manuals giving full details of SGS semiconductor devices. These are entitled respectively 'Professional Discrete Devices' and 'Consumer Devices' and are both printed on an 11 1/2 by 8 1/2 in. format. Both manuals contain a 'Planar Selector' guide which enables specific devices to be chosen from clearly laid-out tables, the guides being followed by very comprehensive information on all the devices listed. The latter sections constitute the major parts of the manuals. Both manuals are fully up to date as of August 1969.

Items in 'Professional Discrete Devices' include transistors for a.f., r.f. and high voltage applications, multiple transistors, phototransistors, reference diodes, high speed diodes and thyristors. The contents of 'Consumer Devices' include general purpose transistors, u.h.f./v.h.f. transistors, high voltage and video output transistors, and integrated circuits.

Readers of *The Radio Constructor* may obtain either or both of these publications from SGS (United Kingdom) Ltd., Planar House, Walton Street, Aylesbury, Bucks, at the price of 21s. each.

EVERY NOW AND AGAIN THE writer includes, in the *Suggested Circuit* series, a design which has to be categorised as being "strictly experimental". The circuit to be discussed this month falls into this class because both the transistors it employs are operated under conditions which are well removed from those in which they would normally function. For this reason, the circuit is not recommended for the beginner who wishes merely to follow a tailor-made design which requires no setting up and which employs conventional circuitry. On the other hand, the circuit will be of interest to the more experienced experimenter who likes trying out unconventional applications. The fact that the transistors in the circuit are operated under unusual conditions involves the risk that not all transistors of the types quoted may offer the same results. Such a risk should not be particularly high in the present case but its existence has to be mentioned and accepted.

THE CIRCUIT

The unit to be described is an experimental record player amplifier intended to be coupled to a low-cost crystal pick-up, and its circuit appears in Fig. 1. The r.m.s. output available is of the order of 100mW. However, when coupled to a reasonably sized speaker of the order of 6in. or more, the audible signal is more than adequate for a small room. The quality of reproduction is not in the high fidelity class, but it is certainly comparable with that offered by a conventional transistor amplifier having a low power Class B output stage. The main advantage of the circuit is its exceptional simplicity. The circuit complications inherent in a more conventional amplifier employing a Class B output stage are completely absent.

The input signal from the crystal pick-up is applied to the volume control, R1, and is then fed, via R2 and C1, to the base of TR1. The collector of TR1 couples direct to the base of TR2, which functions as an emitter follower feeding into the output transformer primary. The latter is one half of the primary of a standard "Eagle" LT44 output transformer, the secondary of this component coupling to a 3Ω speaker.

Base bias for TR1 is provided by R4 and R3, and it will be noted that these components have much higher values than are usually encountered in circuits of this nature. It was found empirically, nevertheless, that these values enabled the amplifier to func-

tion as intended, even though the result is that TR1 is operating at a very low collector current. The rather wide voltage swing from the crystal pick-up is changed to a corresponding current swing at the base of TR1 due to the presence of R2 plus, at settings other than full volume, whatever track resistance happens to appear above the slider of R1. Some non-linearity in TR1 is inevitable but, as was found experimentally by the writer, any resultant distortion in the output of the amplifier appears to be well within acceptable limits for a low-cost design such as this.

Capacitor C1 is a d.c. blocking capacitor and it is essential that it be a good quality paper or plastic


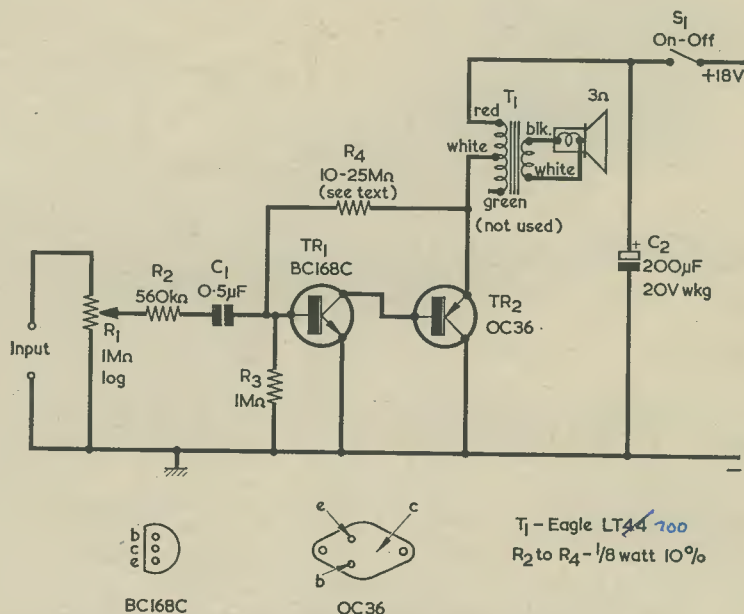


Fig. 1. Circuit of the experimental record player amplifier


Experimental Record Player Amplifier

by G. A. FRENCH

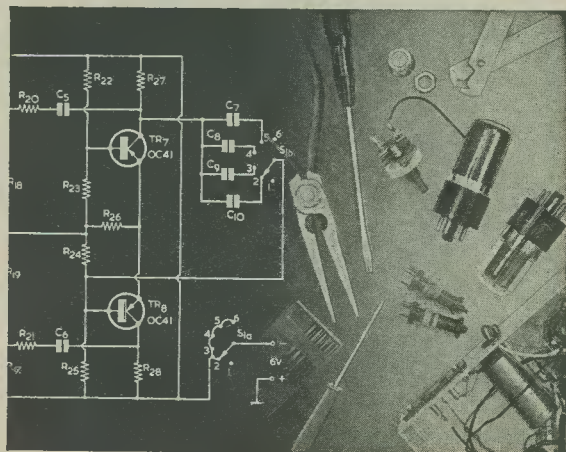

BUY THIS BEST SELLER

**T.V. FAULT FINDING
405/625 LINES**

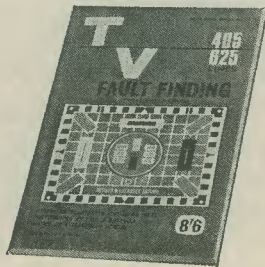

REVISED & ENLARGED

Edited by J. R. Davies

124 pages only 8/6

Over 100 illustrations, including 60 photographs of a television screen after the appropriate faults have been deliberately introduced.

Comprehensive Fault Finding Guide cross-referenced to methods of fault rectification described at greater length in the text.

Price 8/6 from your
Bookseller

or post this Coupon together
with remittance for 9/2
(to include postage) to

DATA PUBLICATIONS LTD.
57 Malda Vale, London, W.9

Please send me the 4th re-
vised edition of TV Fault Find-
ing, Data Book No. 5.

I enclose cheque/crossed postal order
for

NAME

ADDRESS

R.C. Block Letters Please

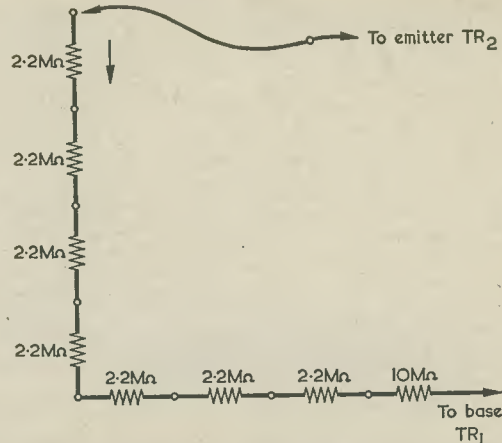


Fig. 2. A suggested method of finding the value required in R4. The flying lead may be terminated in a crocodile clip

foil component. If an electrolytic capacitor is used in the C1 position the amplifier will not function.

The output stage draws a standing current of 20mA, which means that TR2 dissipates 360mW all the time that the amplifier is switched on. The circuit offers no protection against thermal runaway in TR2 (due to the small resistance of T1 primary, the level of d.c. feedback via R4 is negligibly low) and the solution to this problem consists, quite simply, of choosing a much larger transistor for TR2 than the signal conditions warrant. In the prototype, TR2 was operated continually for several hours without any heat sink at all and, whilst growing perceptibly warm, still passed exactly the same emitter current at the end of this period as it did at the beginning. It would be wise, nevertheless, to mount TR2 on a small heat sink in order to provide extra thermal stabilisation. Since the collector of TR2 is at chassis potential, the heat sink can be provided by bolting this transistor direct to a small metal plate or chassis on which are mounted all the other components. During early experiments the author used a small TO-5 transistor in the TR2 position and this gave definite evidence of thermal instability. It is necessary, therefore, to employ the large transistor specified.

The transistor used in the TR1 position is a BC168C (available from Amatronix Ltd.). It is essential that TR1 be a silicon transistor with a collector voltage rating in excess of 18 volts.

SETTING UP

The circuit is set up by finding the value in R4 which causes a standing current of about 20mA to be drawn from the 18 volt supply. A word of warning is necessary here. The OC36 in the TR2 position is capable of

passing very high currents if the value of R4 is accidentally made too low, and so the setting up of R4 must be carried out very carefully. The method employed by the author consisted of wiring up a single 10MΩ resistor in series with a string of 2.2MΩ resistors, as shown in Fig. 2. The resistance was then reduced, from its maximum, in 2.2MΩ steps until the desired 20mA was drawn from the supply. In the writer's case it was found that about 17MΩ (10MΩ in series with four 2.2MΩ resistors) produced the desired current, whereupon the circuit was finally wired up with a 10MΩ and 6.8MΩ resistor connected in series.

THE SUPPLY

As has already been stated, the current drawn from the 18 volt supply is 20mA. This current is not so high as to preclude the use of batteries to power the amplifier, even though the efficiency is not as good as is given by an amplifier with a Class B output. If a mains supply unit is employed there is no need to pay attention to voltage regulation so far as signal handling performance is concerned since the output transistor operates in Class A. Apart from small deviations during overload, the current drawn remains steady at 20mA. The supply voltage should not be allowed to rise above 20 volts, however, as this is the maximum collector voltage rating of TR1. Should the unit be powered by a poorly regulated mains supply it would be advisable to connect an 18 volt zener diode across the supply lines. The function of this diode would be merely that of ensuring that excessive voltage is not accidentally applied to TR1, and it need not draw any zener current when the amplifier and power supply are operating under normal conditions.



Q S by X

FRANK A. BALDWIN
(All Times GMT)

● TOPIC

Short wave listeners, like any group of human beings, tend to be a highly individualistic lot – some eventually obtain an amateur transmitting licence whilst others are quite happy to remain s.w.l.'s and to thoroughly master the craft. Others drift in and out of the hobby over a period of some years. There are those, of course, who remain in the hobby for some time, become quite well known in the world of short wave listening and then, for reasons best known to themselves, vanish completely from the scene, never to return to the fold. The writer can recall s.w.l.'s of the past whose names became a byword in the hobby, even prior to the last war. Others have been on the short wave listening scene for many years and these old timers tend, as a group, to be conversant with all aspects of the hobby, constructing their own equipment – either from published or their own designs – testing and evaluating the results, and operating over both the Broadcast and Amateur bands. On the Amateur bands, both phone (a.m. and s.s.b.) and c.w. stations are logged, the ability to read c.w. being necessary to become an all-rounder.

It is probably true, however, that the majority of short wave listeners tend to specialise in one aspect of the hobby or another. In the main, most listeners operate over the Amateur bands, using a.m. or s.s.b. phone transmissions as their prime targets. Unable to read c.w. they are confined to the phone portions of these bands, thus restricting their sphere of activity and interest and, in the writer's opinion, only gaining a small part of the interest which the short waves offer. If a continued and lasting interest is to be taken in the hobby, such a listener is advised to learn the dots and dashes. The ability to read c.w. widens the horizons of the operator who has previously only used the phone sections of the bands, it following that an increased report/reply ratio is the result, especially when Morse transmissions are reported upon. Licence holders who operate on c.w. tend to receive far fewer s.w.l. reports than do their phone counterparts.

Amateur band listeners tend to crowd on to the 14 MHz band, this being the most favoured range of frequencies for the reason that they produce the most varied and choicest Dx signals throughout the year than any of the other bands. Comparatively few listeners are primarily interested, or even operate to any extent, over the lower frequency Amateur bands. It is a truism that Dx is relative, among other considerations, to the band in use – and many choice catches may be made on the lower frequencies. Moreover, these transmissions are reported upon by very few s.w.l.'s, and this implies that a comprehensive report to such a station would stand a very good chance of obtaining a reply.

To be an all-rounder s.w.l., operation over the Broadcast bands should also be included in the spread of interest. Broadcast band operation makes a complete change and a break from the Amateur bands. Many Dx stations are there for those who care to search for them and their reception often represents a major feat of short wave listening.

● AMATEUR BANDS

Top band has shown some promise of improvement on last year with signals being heard from across the Atlantic since early October. The dates of Trans-Atlantic Tests still to be held are – 11th January and 1st, 15th of February from 0500 to 0730.

1.8MHz

CW: DL2PB, DL9KRA, EI9BJ, EI9J, GM3BGW, GM3HLQ, GM3YOR, GW3RHC, GW3VPL, GW3XJC, GW3XST, HBØNL, OK1ATX, OK1JR, OK2BLH, OK3CJE, OL2AIQ, OL2AKS, OL5ALY, OL5AMT, OL6ALT, OL9AY.

Trans-Atlantic Dx signals logged to time of writing are:– K1BPW (0525, 1804kHz); W1EXI (0545, 1803kHz); W1BB/1 (0515, 1804kHz) and VP9GW (0530, 1802kHz).

3.5MHz

CW: K3JH, VE1AJK, VE1AVN, WA1FSU, WA2CPQ.

SSB: CN8HD, KV4FZ, VE3DJE, VO1AC, XE1KB.

7MHz

CW: HP5CFW, HP6ASD, K4DJN, K5AZX, VE3DHC.

14MHz

CW: CR6AL, CR6KB, CX1JM, HC2HM, HP1BR, KP4DDY, PZ1AV, VP8JV, VQ8CC, ZE1DL, ZM3ABC, ZS1JJ, ZS5SG, ZS6GG, 9J2XZ.

SSB: CP6HQ, CR4BP, EL6UN, ET3USA, HC1RF, HC2OA, KP4AC, KZ5NG, PZ1CR, TR8MC, VK2SG, VK7KX, VP2LA, VP2VI, VP7DL, VP7NF, VP8KO, VP9BO, ZM3FT, ZP5GJ, 6Y5RA, 9K2BF.

For those interested, 9K2BF gave his QTH as P.O. Box 1083 Kuwait.

● BROADCAST BANDS

Several readers have written stating they are Broadcast band beginners and have not, up to the time of writing, heard an Indonesian station, although they have logged some of the signals from the Indian sub-continent. The Indonesian stations on the I.f. bands are all comparatively low-powered and conditions must be good before any hope can be held out of successful reception and recognition.

As a tip, the most consistent Indonesian signal here is that of YDK6 Djambi on 4927kHz – listen around 1530 to station close down at 1600. The receiver must be selective, this channel often being surrounded with CW and teletype QRM. The station closing ceremony – for want of a better term – commences at about 1550 with an Eastern type chanting song rendered by a young woman and this is followed by identification in Indonesian and a most haunting melody rendered on a Hawaiian guitar.

Other Far Eastern stations logged were:–

4725kHz 1612 Rangoon, Burma, with drama programme in vernacular.

4740kHz 1620 Radio Maldives, with American religious programme.

4790kHz 1610 Penang, Malaysia, radiating recorded 'pop' music.

4877kHz 1545 Saigon, S. Vietnam, with drama programme in vernacular.

4907kHz 1434 Radio Cambodia, with a drama complete with many gong and cymbal clashes – most impressive!

Still on the lower frequencies, Dx'er Alan Thompson tells me that Radio Botswana is heard on 4845kHz with BBC news at 1800 and station identification in English at 1809. He also mentions that Brazzaville (ex-4795kHz) is – or was at the time of writing – on 4801.5kHz.

17770kHz 0532 Karachi, Pakistan, with sports commentary in English.


21535kHz 0800 Tokio, Japan, with identification and news in English.

21545kHz 0800 RSA, South Africa, station identification and music.

Whilst dealing with the higher frequencies, Alan Thompson also brought to my notice the following – 11855kHz Saudi Arabia in English, good signal between jamming of Tirana (Peking relay) on same channel, try around 1900-1930 when channel is clear. 15540kHz Tanzania with English programme at 1700-1830. 15723kHz at 1730 Omdurman in English/Arabic.

PRESSAC 'AUTOSPlice' CONNECTION SYSTEM

1969-70 FARADAY LECTURE TOUR

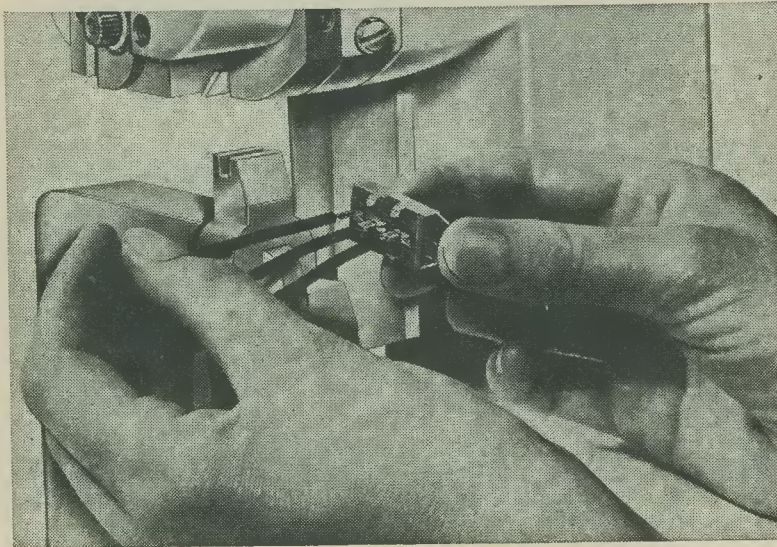

'Autosplice' connections being applied to slider switch.

'Autosplice' makes its own connectors directly from one coil of correctly grain-oriented conductor ribbon. The press feeds the correct length, cuts it, forms a connector and compresses it securely around the conductors it is joining, in less than a fifth of a second.

Various conductor diameters and tag sizes are accommodated by changing dies and adjusting the connector ribbon feed.

Using just one width of ribbon and as few as one pair of dies, 'Autosplice' stockholding is reduced to a minimum. There is no longer a need to maintain stocks of thousands of tiny preformed connectors or expensive soldering equipment.

INTRODUCTION TO COLOUR TELEVISION

The advent of colour TV on all major channels has stimulated interest in the technical aspects of colour television.

We would draw the attention of new readers to our Data Book - *Understanding Television* by J. R. Davies, which contains an 80 page comprehensive introduction to colour TV. The book covers TV as a whole and has more than 500 pages and over 300 diagrams, costs 37/6, postage 3/6, and is of equal value to those who only have a basic knowledge of radio principles and to established radio engineers.

JAQUET RECORDER TYPE 400

The KSQ 400 series has recently been added to the Radiatron range of Jaquet recorders. Compared with the existing KSQ 300 series the new recorders have been reduced in size by nearly 50% and in cost by approximately 30%. In frontal presentation and accuracy the new recorders are identical to the earlier type. The price and size reductions have been achieved by using the latest electronic techniques and simplifying the circuitry of the instruments. This results in slightly reduced sensitivity and increased response speed, but does not impair accuracy or any other aspects of performance compared to the earlier KSQ 300 series.

Brief specifications: 1-6 channels; plug-in range cards; input impedance not less than 20k Ω ; sensitivity 0.15% of measuring range; accuracy 0.5% FSD; prices from £212.

The forty-first in the series of Faraday Lectures arranged by the Institution of Electrical Engineers is to be given by J. H. H. Merriman on the subject of 'People, Communications and Engineering'. Mr. Merriman is the senior director (development) with the British Post Office and also member for technology on the board of the Post Office Corporation.


The deputy lecturer is C. H. May who is staff engineer in the P.O. Telecommunications Development Department.

Starting in Rugby, Staffordshire on the 18th November, the Faraday Lecture is to be given in thirteen towns in the British Isles, finishing in Belfast on the 17th April 1970.

The Faraday Lecture series is intended to spotlight various aspects of modern electrical and electronic science and technology in straightforward language for the general public. Special presentations for students are being arranged at all the towns on the tour. Members of the public are admitted by ticket, free of charge, to these lectures.

The lectures will be given at the following centres: Albert Hall, Nottingham, 13.1.70; Victoria Hall, Hanley, Stoke on Trent, 15.1.70; Philharmonic Hall, Liverpool, 29.1.70; City Hall, Sheffield, 10.2.70; Sophia Gardens, Cardiff, 17.2.70; Central Hall, Westminster, London, 19/20.2.70; City Hall, Newcastle, 17.3.70; Usher Hall, Edinburgh, 19.3.70; Royal Dublin Society Hall, Dublin, 15.4.70; William Whitla Hall, Belfast, 17.4.70.

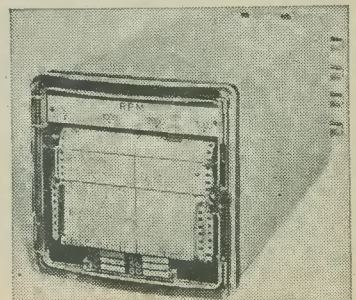Details and tickets may be obtained from The Institution of Electrical Engineers, London, W.C.2.



THE RADIO CONSTRUCTOR

COMMENT

ELECTRONICS AID TRAINING TIME CUT

A new method of basic training for teleprinter operators and telegraphists has recently been introduced by the Royal Air Force at R.A.F. Cosford, main training centre for operators of all R.A.F. communications equipment.

Using the Videomatic Tutor pioneered by Sight and Sound Ltd. initial touch-typing speeds of 15-20 words per minute is achieved in less than half the time necessary with conventional methods. Estimates are that the consequent two-week reduction in the present 11-week course will trim more than 20% of the training bill.

A system which has also found favour with the public, the Videomatic Tutor is a machine which incorporates a panel, representing the typewriter keyboard, placed on a wall facing the class. Connected to the panel is an electronic unit consisting of a computer-programmed magnetic tape deck which simultaneously relays instructions through loudspeakers and signals to illuminate the appropriate keys represented on the wall panel. By this means each student is shown the position of his fingers on the blank keys of the typewriter in front of him. Visual indication of the next movement is given on the wall panel fractions of a second before the verbal instruction.

The R.A.F. has found that a pupil's concentration and receptivity are improved to the extent that the entire keyboard is memorised within four hours and finger movements are made without conscious effort.

With the reduction in training time now possible, R.A.F. Cosford will be able to handle more than 200 students a year, in courses of 20 at a time. Fully fledged operators fan out all over the world to maintain the R.A.F.'s vital communications links.

A HAPPY NEW YEAR TO YOU

Avoid disappointment in 1970 by ordering
The Radio Constructor regularly

JANUARY 1970

EXPANSION AT LIND-AIR AUDIO CENTRE



The newly extended Lind-Air Audio Centre at 18/19 Tottenham Court Road. The Centre, which includes two hi-fi demonstration studios and a colour television showroom, now covers 6,000 square feet.

CONNECTING CABLES — NEW COLOUR CODING


The change in the colour coding for the insulating material covering each core of the 3 cores in a.c. mains connecting cable, the possibility of which we were among the first to announce more than a year ago, comes into effect on 1st July, 1970.

Existing electrical apparatus already purchased will not be affected but it will be an offence, after 1st July 1970, for a dealer in electrical goods to sell appliances where the cable does not conform to the new colour code.

Although we feel that our present code is more logical and superior to the new, obviously an international standard is highly desirable. The confusion arising between various colour codings by different countries has led to accidents, some fatal, both here and abroad: large quantities of electrical equipment are both exported and imported. Some idea of the existing dangers can readily be envisaged when it is realised, for example, that West Germany uses red for earth, and a number of countries use black for the live wire. Also it appears that colour blind people will be less likely to confuse the earth and live wires, under the new regulations.

The coding will be:—

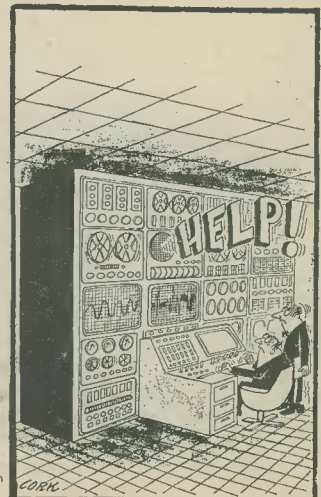- Earth — Green and Yellow striped core
- Live — Brown core
- Neutral — Blue core



TRANSISTORISED CRYSTAL MARKER

by


S. G. WOOD, G5UJ

This simple and inexpensive circuit can produce detectable 100kHz harmonics up to 28MHz

A 100kHz CRYSTAL OSCILLATOR CAN BE A USEFUL adjunct to any "ham-shack" and it need not be expensive or difficult to build. Apart from the cost of the crystal – and these have been on the market for as little as 7s. 6d. – the total expenditure can be very low.

Good results have been achieved with the circuit shown in the accompanying diagram, using general-purpose germanium transistors such as the Mullard OC70 or OC71. Even the old Red-spot types have been found to function satisfactorily.

The oscillator is of the Pierce type and sufficient r.f. output for most purposes is available when the circuit is powered by a 4.5 volt battery. Resistors R1 and R2 can be $\frac{1}{4}$ or $\frac{1}{2}$ watt 10% components. Switch S1 may be a normal toggle or slide type; alternatively a push-button can be employed, this being pressed to switch on the oscillator when required. Choke L1 can be a small 2.5mH component such as the Repanco CH1. However, the writer employed a home-wound choke, this consisting of 45 turns of 30 s.w.g. enamelled wire pile-wound on a short length (about 1in.) of ferrite rod. The choke inductance is not critical.

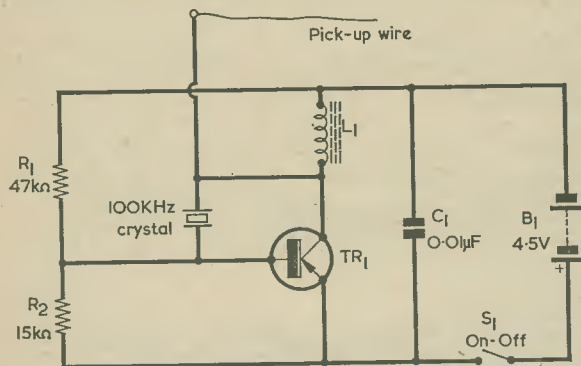

Circuit of the 100kHz marker oscillator. Suitable components for L1 and TR1 are discussed in the text

The various uses to which this little unit may be put need hardly be enumerated here. It is possible – with care – to pick out the harmonics on a sensitive receiver at 100kHz intervals up to as high as 28MHz. Should any difficulty be experienced due to receiver screening, etc., a short length of "pick-up" wire may be introduced into the collector circuit of the transistor, as shown in the diagram. This can then be positioned near the receiver aerial lead or aerial terminal to increase coupling.

SPACE DX

Have you ever had secret dreams of receiving signals from another civilisation in our galaxy from way across the other side of the Milky Way? If you have then you are normal; if you haven't then you must be unimaginative!

Has a listening watch ever been made for such signals? Yes, the first and only attempt to receive intelligent signals from another planet was made in 1960 and termed the Ozma Project – during which a listening session of 150 hours was made using directional aeriels beamed to our nearest solar type stars, Tau Ceti and Epsilon Eridani, at a distance from Earth of some 11 light years, and around which planetary systems may be orbiting. The project was dismally unsuccessful.

WHICH FREQUENCY?

From experience gained in the field of radio astronomy, the choice of wavelength would lie between 3 to 30cms at which the effects of cosmic noise and atmospheric absorption on a signal would be at a minimum. It has been suggested that the best frequency would be 1,420 MHz – this being the emitting frequency of neutral hydrogen clouds around the spiral arms of our galaxy – the reasoning being based on the assumption that other galactic civilisations may also be conducting surveys of hydrogen distribution.

SUCCESS OR FAILURE?

At the present time, success is miserably zero. We need more sensitive equipment and improved techniques, much time and investigation before the odds against success are anything like evens. Careful listening will have to be maintained out into space, to distances of hundreds of light years. One powerful radio astronomy transmitter, the 1,000ft. dish in Arecibo, Puerto Rico, is claimed to be able to transmit radio pulses of sufficient power to be detected at a distance of 1,400 light years from Earth.

WHO WILL LISTEN?

How many intelligent civilisations are there in our galaxy of sufficiently advanced technology able to receive our signals? Well, astronomers have calculated that the number of single solar-like stars that have accompanying planetary systems formed during the 10 billion years of the existence of our galaxy, is something like 50 billion. With these sun-like stars, the forming of accompanying plants is a common event. Of the planet total however only a relatively few will be able to support intelligent life with the required conditions – atmosphere, temperature, water, etc. With the remainder, not all will see the emergence of life, and, where it does emerge, not all species will be technically competent to take part in space communications – and some that are may not be interested in making contact with others.

One authority has calculated that there ought to be something like four million civilisations capable of communicating with each other.* Of course, all these civilisations will not attain a culture peak at the same period. Nevertheless, there should be sufficient overlap of civilised periods to make interstellar communication possible.

With a total of four million communications minded galactic civilisations, we may yet – at some future date – be holding regular Dx schedules with another far across the vast distances of space!

*L. Berman, K6BW, writing in CQ, November, 1969.

LOW-COST REGENERATIVE RECEIVER

by

A. SAPCIYAN

This simple little medium wave receiver can be built as a 2-transistor set driving an earphone, or as a 3-transistor set driving a speaker at moderate volume level. Few components are required, and there is opportunity for experiment with some of these to obtain best results with the particular transistors employed

REGENERATIVE RECEIVERS ARE ideal for those who wish to build simple and reasonably sensitive sets. It has to be remembered, however, that they are rather tricky to operate when compared with commercially made sets, and that their performance can never match a superhet in terms of sensitivity and selectivity. Nevertheless, satisfactory results can be obtained in areas of good signal strength and local stations can be tuned in without interference, which is what most people want. Provided, therefore, that their limitations are appreciated, receivers of this class can be instructive to build and can offer a very useful performance.

The receiver described in this article uses a simple circuit and may be built in either a 2-transistor or a 3-transistor version. If desired, the 2-transistor version can be constructed first and the third stage added at a later date. The 2-transistor receiver drives an earpiece, whilst the 3-transistor receiver drives a loudspeaker at moderate level.

2-TRANSISTOR RECEIVER

The circuit of the 2-transistor receiver appears in Fig. 1. The ferrite rod aerial coil, L1, is tuned by C1, its tap being coupled to the base of TR1. Detection takes place due to non-linearity in TR1 and TR2, with the result that the primary function of TR1 is to amplify at radio frequency. The transistor in the first stage is an AF126, which

has a relatively high gain at medium wave frequencies. R.F. transistors such as the OC44 have also been tried, but they did not offer the same degree of sensitivity, particularly at the high frequency end of the band. When set up for best amplification, the collector current for TR1 is around 1mA.

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 10%)

R1	47k Ω
R2	1M Ω potentiometer, linear, with switch S1
R3	3.9k Ω
R4	560k Ω
R5	5.6k Ω

Capacitors

C1	365pF variable, air-spaced
C2	0.01 μ F, paper or plastic foil
C3	0.01 μ F, paper or plastic foil
C4	5 μ F electrolytic, 10V wkg. (see text)

Inductors

L1, L2	See text
--------	----------

Transistors

TR1	AF126
TR2	OC75

Battery

B1	9-volt battery
----	----------------

Switch

S1	s.p.s.t., part of R2
----	----------------------

Miscellaneous

1,000 Ω magnetic earphone with jack plug and socket (not needed with 3-transistor version)
2 knobs

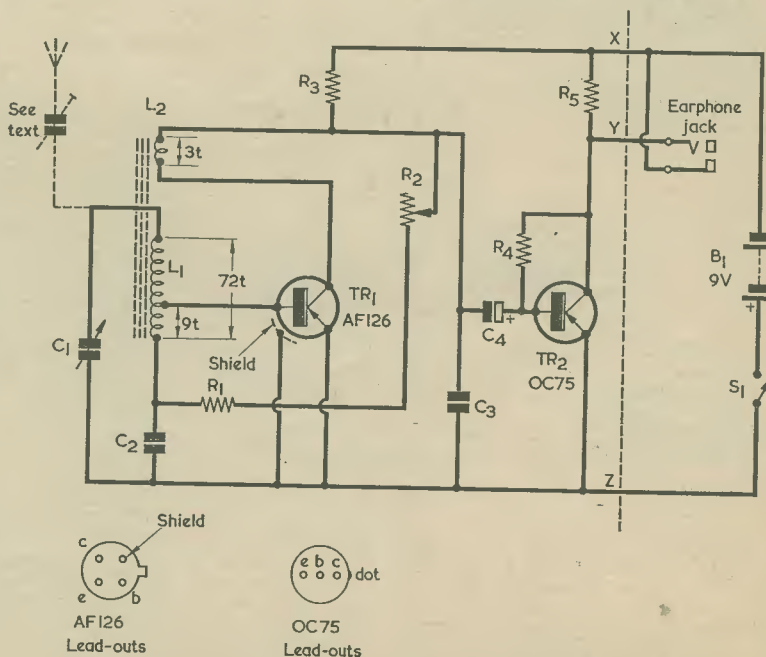


Fig. 1. The 2-transistor version of the regenerative receiver

Coil L2 provides regenerative feedback. The variable resistor R2 controls the base current to TR1 and hence operates both as a volume control and as a reaction control. It is adjusted normally so that TR1 is just below the oscillation point. R2 has a high value in order to accommodate transistors having both low and high gain figures.

The second stage incorporates an OC75 and drives a high impedance (1,000Ω) magnetic earphone. The miniature earphones used with commercially made sets are not satisfac-

tory here since they have low impedances, of the order of 10Ω. Their use will cause disappointment. A measure of stabilisation, which has proved adequate in practice, is given by taking the base bias current for TR2 from its collector via R4. The total current consumption of the first two stages is approximately 2.5mA.

If the constructor wishes to add a third stage of amplification, the circuit shown in Fig. 2 is employed. The components to the right of the dashed line in Fig. 1 (including the

off switch and is ganged with R2. R2 should be wired up such that it inserts maximum resistance into circuit when S1 is switched off.

When the receiver has been completed and the adjustment procedure (to be described later) carried out, it is worth experimentally changing C4 for a 0.25μF capacitor. With some AF126 transistors it may be found that this gives a very useful increase in sensitivity. If it does not, the electrolytic capacitor should, of course, be retained in circuit. It may even be found, in the 3-transistor version, that there is an improvement in performance when a 0.25μF capacitor is similarly connected into circuit in place of C6.

FERRITE AERIAL WINDINGS

The aerial coil, L1 may be wound on a ferrite rod 4in. long and with a diameter of ¼in. using 28 s.w.g. enamelled copper wire. The total number of turns is 72 close-wound, with the tap at nine turns from the end which connects to C2. Be prepared to add or take off a few turns at the end remote from C2 in order to get the range exactly right. In this respect, it will prove helpful to wind the coil on a paper sleeve which can be moved along the rod to provide small changes in inductance, if desired. In general, best results will be given with L1 at, or near, the centre of the rod.

Other ferrite rods of about the same dimensions may be employed, remembering that a longer rod will require fewer turns, as also will a thicker rod. The writer checked the receiver with a ferrite slab which was 4in. long, 1in. wide and ¼in. thick. This slab required 64 turns with a tap eight turns from the C2 end. The position of the tap in the coil is not very critical and acceptable results are given when the number of turns between the tap and the C2 end of the coil is approximately one-eighth of the total number of turns.

The beginner will find it quite easy to adjust the number of turns on L1. Provided that approximately the correct number are initially wound on, he will find it possible to receive stations near the middle of the medium wave band. He may then, later, search for stations at the high and low frequency ends. If stations at either of these ends are outside the tuning range, the number of turns can be adjusted accordingly.

The feedback coil L2 is also wound on the ferrite rod (or slab) and consists of three turns of 28 s.w.g. enamelled copper wire. It should be wound on a paper sleeve or former which is free to slide along the rod.

General construction of the receiver presents few problems, and the stages of either the 2-transistor

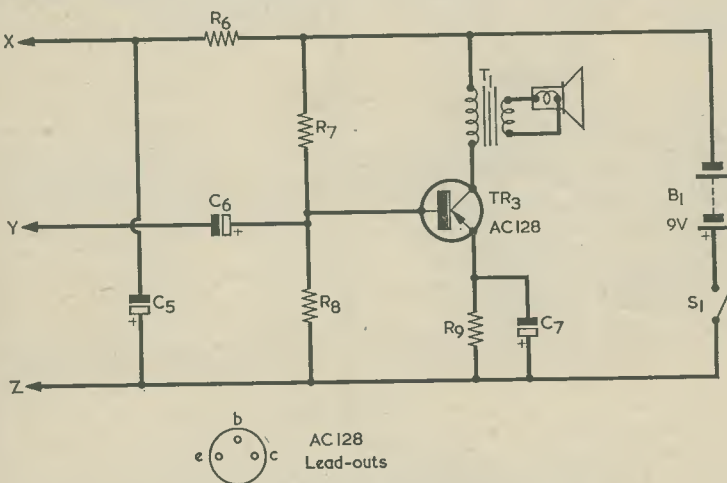


Fig. 2. This extra stage is added to provide the 3-transistor version

COMPONENTS

Resistors

(All fixed values ¼ watt 10%)

R6	1kΩ
R7	27kΩ
R8	3.9kΩ
R9	150Ω

Capacitors

C5	50μF electrolytic, 10V wkg.
C6	5μF electrolytic, 10V wkg. (see text)
C7	100μF electrolytic, 6V wkg.

Inductor

T1	See text
----	----------

Transistor

TR3	AC128
-----	-------

Speaker

See text

Battery

B1	Included with Fig. 1 Components List
----	--------------------------------------

Switch

S1	Included with Fig. 1 Components List
----	--------------------------------------

earphone and jack socket) are not then required, and the circuit of Fig. 2 couples to that of Fig. 1 at points X, Y and Z. TR3 is an AC128 and its base couples to the collector of TR2 via C6. R6 and C5 are decoupling components, and prevent unwanted couplings to the preceding stages via the negative supply line. Without these components there would be instability, evident as "motorboating", when the battery ages and its internal resistance rises. Total current consumption of the 3-transistor version is approximately 10mA.

It is desirable to use a fairly large speaker, say 4in. in diameter or more, to take greatest advantage of the fairly low audio output available. The output transformer, T1, should have a ratio which presents an impedance of some 150Ω to 250Ω to TR3. A suitable type, for use with a 3Ω speaker, would be the Radiospares transformer Type T/T4. (Radiospares components may only be obtained via retailers.—Editor.) If a speaker with an impedance of 130Ω or so can be obtained, this may be connected direct in the collector circuit of TR3, whereupon no output transformer is required.

Switch S1, in both the 2-transistor and 3-transistor versions, is the on-

or 3-transistor version may proceed along the board or chassis on which they are assembled in the same order as they appear in the circuit diagram. The wiring around TR1 and TR2 should be kept reasonably short. In the 3-transistor version, transformer T1 should be farthest away from the ferrite rod, and its laminations should be at right angles to the rod.

ADJUSTMENT AND OPERATION

When all wiring has been completed and checked, the battery should be connected with correct polarity and the receiver switched on. It should be possible, with either version, to receive at least one station by adjusting C1. If no station is received, adjust R2 towards its "maximum" position (minimum resistance in circuit) until

oscillation occurs. Should there be no oscillation with R2 at "maximum", move L2 towards L1 until oscillation commences. If there is still no oscillation, even when L2 is very close to L1, reverse the connections to L2, whereupon the oscillation should commence.

If oscillations are too strong they may be reduced by adjusting R2 towards "minimum" and/or moving L2 away from L1. L2 should be finally positioned so that oscillation is available over all of the band at a setting in R2 which gives best performance with received signals. In general, oscillation should begin with R2 about a quarter of the way from the "minimum" end when a new battery is fitted. However, much depends on the specific transistor used for TR1, and final adjustments in the position of L2 should be for the best overall results, as adjudged on received signals. The sensitivity

of the receiver is at its greatest when R2 is just below the oscillation point. If a howl is evident in the 3-transistor version when the receiver goes into oscillation, transpose the connections to T1 primary.

Should the constructor so desire, a short aerial may be coupled to the receiver via a 100pF trimmer as shown in dotted line at the left of Fig. 1. This trimmer and L2 positioning are then adjusted experimentally for the best compromise between sensitivity and selectivity. The external aerial can, incidentally, be the springs of the bed if the set is to be used as a bed-side receiver!

As a final point, R2 is adjusted to its optimum position for each station received. It will need to be advanced further towards its "maximum" setting as the battery ages and its voltage falls.

ELECTRICAL FAULT-FINDING "DOWN UNDER"

Two methods of tracing an intermittent fault, using Electrolube Freezer, have been described by a correspondent to *Electronics Australia*, a leading Australian Technical Journal. In one, groups of components were heated and individually cooled in turn, whereas the reverse procedure was employed in the second case. The first involved a close circuit TV system. After about an hour's operation, the picture on the monitor began to expand and contract at approximately a 1 sec pulse rate. The simple act of opening the side of the control-unit case was sufficient to cure the fault because of the loss of heat. An infra-red lamp was therefore used to raise the temperature of the equipment while the side was open.

The lamp was arranged to provide local heating of various sections of the equipment in turn. By this means



it was established that the section including the master oscillator and the first divided chain contained the fault.

Leaving the heat lamp on so that the fault remained in evidence, the correspondent then applied Electrolube freezer to each component in turn. The fault disappeared when a mica capacitor in the master oscillator was cooled by the spray. Fitment of a new capacitor provided a remedy.

The second case concerned a tape recorder which would not record or play until it had been switched on for about 10-15 minutes.

"It occurred to me", wrote the correspondent, "that I might be able to identify the faulty component by heating each component after mass cooling and note which one restored the performance most rapidly".

A group of components was cooled with the aerosol and the writer placed his finger on each in turn to apply heat. A faulty transistor was discovered in this way to the correspondent's surprise as he did not suspect that a transistor could be temperature-conscious. A colleague, however, suggested that the transistor contained a broken bonding wire or faulty junction to either the chip or pigtail, with only a microscopic gap.

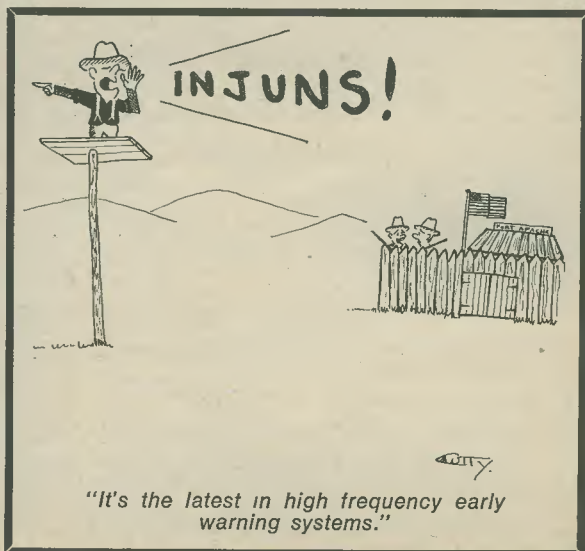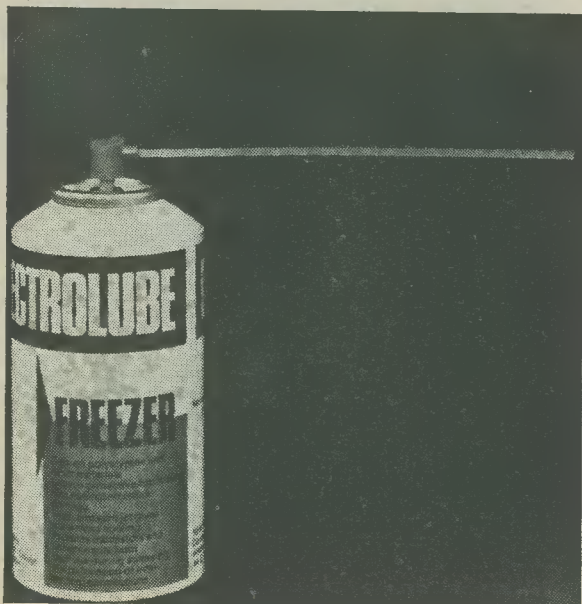

"It's the latest in high frequency early warning systems."

VERSATILE A.C. MILLIVOLTMETER

by

G. W. SHORT

Intended for the more experienced constructor, this article describes a versatile and inexpensive millivoltmeter design which incorporates many attractive features. These include low battery consumption and the ability to operate with any moving-coil meter having an f.s.d. within the limits $500\mu\text{A}$ to 5mA . Measuring ranges depend on the existing scale marking on the meter and may be, typically, 5mV to 500V . The frequency response within 5% error extends from 20Hz to 30kHz

MOST MILLIVOLTMETERS ARE DESIGNED AROUND meters of a specific sensitivity, usually $100\mu\text{A}$ instruments. The transistor a.c. millivoltmeter described here is different. It has been deliberately designed to accept a wide range of indicating meters so that the constructor, by following some simple rules, can adapt it to accommodate whatever meter he happens to have, the only requirements being that it should be a d.c. instrument with a linear scale and a sensitivity of $500\mu\text{A}$ to 5mA approx. The amplifier part of the instrument may be used as a general-purpose audio amplifier with an output of up to 2.5V r.m.s. The amplifier will deliver over 30mW to a 70Ω speaker.

SPECIFICATION

Input impedance: greater than $1\text{M}\Omega$.
Measuring ranges: 5mV - 500V approx., full-scale.
Standby consumption: 9V , 2.5mA approx.
Overload capacity: 240V , 50Hz on most sensitive range.
Frequency response: $20\text{--}30,000\text{Hz}$, $\pm 5\%$.
Indicating meter: $500\mu\text{A}$ to 5mA , any linear scale.
Amplifier section usable for other purposes.

BATTERY DRAIN

The usual type of transistor millivoltmeter (see Fig. 1) incorporates a Class A amplifier. This drives a rectifier meter, which is placed in a negative feedback path to improve the linearity.


The drawback with this type of circuit is that if a relatively insensitive meter has to be used the battery drain becomes too large. Suppose a 5mA meter is to be used. If the input signal is a sine wave then, to drive the pointer to full scale deflection, the input current to the meter must be 5mA r.m.s., or 7mA peak. The peak current is what matters, because it fixes the minimum current which the second transistor must pass. In the present case, this must be over 7mA d.c. or the peaks of the sine wave will be clipped and the millivoltmeter will be inaccurate. Unfortunately most millivolts meters will also be called upon to handle speech and music voltages. These have rather peaky waveforms, and to handle them without clipping calls for a much higher standing current, perhaps four times the meter full-scale current. By the time the drain of the earlier stages has been added the consumption will be about five times the meter f.s.d. current, or some 25mA for a 5mA meter, which imposes a severe drain on the battery.

SELF-RECTIFYING OUTPUT STAGE

The battery drain can be reduced by using a Class B output stage with a low standby current. A Class B amplifier can deliver large peak currents

RADIO CONSTRUCTOR

FEBRUARY ISSUE

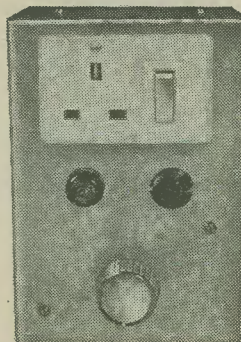

ELECTRIC DRILL SPEED CONTROLLER

This simple-to-build device enables the speed of an electric drill to be smoothly varied from near-zero up to maximum or set at any intermediate point, taking advantage of the facilities offered by a currently available triac. The speed controller will prove to be very useful to the home handyman when using an electric drill for such jobs as sanding, buffing, polishing, sawing or when drilling large-sized holes.

COMPREHENSIVE TIMING UNIT

A small battery powered unit utilising 7 transistors and 2 diodes in an interesting timing circuit providing a good insight into pulse circuit techniques. The circuit can easily be adapted to time almost anything from eggs to the daughter's phone calls! Operation is simple - only one toggle switch - and even this could be dispensed with!

EXPERIMENTER'S POWER SUPPLY

Offering a continuously variable output voltage from zero to 25 volts, this power supply circuit also includes an overload protection circuit enabling output current to be limited to any desired level up to 1 amp and an optional trigger circuit giving a visual indication when the overload circuit begins to operate.

PLUS

- OTHER CONSTRUCTIONAL PROJECTS
- DATA SHEET 35
- SUPPORTING FEATURES

ON SALE 1st FEBRUARY

on demand, which is just what is needed for dealing with peaky waveforms. A possible method of using it would be to substitute the Class B output stage for the second stage of Fig. 1, driving the meter from the Class B pair in much the same general way. This, however, is needlessly complicated. An alternative arrangement, shown in Fig. 2, saves the rectifier by making use of the fact that the lower output transistor of the complementary Class B pair conducts only on alternate half cycles, and therefore acts as a half-wave rectifier to drive the meter.

The only problem that now arises is that the meter registers the standby current of the transistor even when there is no input signal. The remedy is to bias the transistor exactly to cut-off. In practice, however, it is better to adjust the bias until the meter registers a tiny current and then move the pointer back into position by means of the zero adjuster screw.

This last approach gets rid of the problem of the standing current, but it creates a new one. An amplifier biased in this way suffers from crossover distortion. Such distortion is not important in itself in a measuring instrument, but it does spoil the linearity. The answer is to apply heavy negative feedback. Some negative feedback is introduced automatically by the d.c. bias resistance RB, which of course allows a.c. to pass from output to input as well, but the feedback given here is not enough. An additional a.c.-only negative feedback resistance, RF, is therefore added.

DESIGN STRATEGY

Constructors familiar with the Fig. 2 type of circuit will realise that it is not going to be much use when very high sensitivity is required, because the gain is not very high. More amplifying stages are needed. At this point, however, it pays to forget about the exact circuit configuration and think about the essentials of the feedback arrangement.

These are shown in Fig. 3, and as many textbooks will point out, the performance of such an amplifier


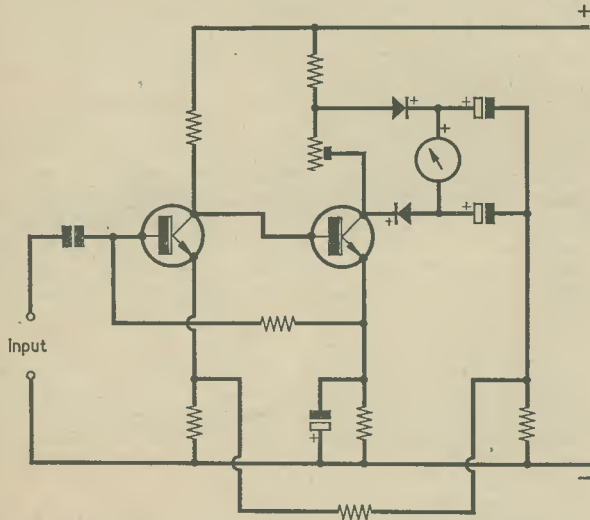


Fig. 1. Typical transistor a.c. millivoltmeter circuit. To avoid clipping the peaks of the signal waveform, the collector current of the second transistor must be several times the meter full-scale current

NEW HANDIPAK PANEL SIGNS

IDEAL FOR WORKSHOP USE

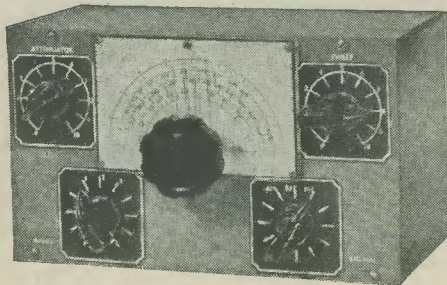

- Easy to fix
- Permanent and durable
- Staped in booklet form
- Designed to hang above workbench
- Pocket for loose cuttings
- Professional finish

- ★ Set 3 Wording—WHITE
- ★ Set 4 Wording—BLACK
- ★ Set 5 DIALS—clear background
- ★ Set 6 DIALS—black background

The Perfect Transfer for
the Home Constructor

Each Set contains Six Sheets

5/- per set
(postage 4d.)

To Data Publications Ltd.
57 Maida Vale, London, W.9

Please supply:

.....Set 3Set 4Set 5Set 6

I enclose cheque/crossed postal order for.....

Name.....

Address.....

BLOCK LETTERS PLEASE

is governed very largely by the three resistances shown, regardless of what is inside the "box", provided that the gain inside the box is very high. For practical purposes, the following statements can be taken as true:

$$\begin{aligned} \text{Input impedance of whole circuit} &= R_S \\ \text{Voltage gain, } V_{out}/V_{in} &= R_F/R_S \\ \text{Current gain, } I_{out}/I_{in} &= R_F/R_L \end{aligned}$$

These equations tell us that, provided we leave the feedback resistance R_F alone, we can adjust the current gain (by changing R_L) without affecting the voltage gain. Alternatively, we can adjust the voltage gain (by changing R_S) without affecting the current gain. This is just what is needed for adapting the circuit to a wide range of meter sensitivities and scale markings.

RANGE SETTING

Different voltage ranges could be selected by switching in different values of R_S . In this respect, R_S acts in exactly the same way as a "multiplier" in any ordinary voltmeter circuit. The idea is attractive if only a few relatively high voltage ranges are required. With a reasonable amount of amplification, the overall sensitivity can be $1M\Omega$ per volt, which is a lot higher than the sensitivity of even the most sensitive non-electronic multi-range meters. But it is still not high enough. For a range of $3mV$ f.s.d., for example, R_S would only be $3K\Omega$, which is much too small.

For this reason, the complete millivoltmeter described here uses a high input impedance buffer stage in front of R_S , and carries out its range selection by means of a potential divider in front of the buffer stage.

BUFFER AMPLIFIER

A mosfet makes an ideal buffer from the point of view of high input impedance. Fig. 4 shows a suitable circuit, incorporating an R.C.A. mosfet type 40468A, which is the successor to the well-known 40468. (The 40468A is available from Amatronix, Ltd., as indeed are all the other semiconductors employed in the instrument).

The mosfet is connected as a "source follower" with a "gain" of less than 1, and having good stability, virtually infinite input resistance, and a fairly low output resistance. The low output resistance enables fairly small values for R_S to be used if need be. The input potential divider shown has six 10 to 1 steps and covers input ranges such as $5mV$ to $500V$. All the resistances except R_7 are common standard values, and R_7 can be made up from two 22Ω resistors in parallel without much loss of accuracy.

Series resistance R_1 and the diodes D_1 and D_2 perform the very important job of protecting the gate of the mosfet against high voltages. No damage results from a sustained overload of $240V$ on the most sensitive setting of the range switch. Note that R_1 must be able to dissipate $1W$ under these conditions.

COMPLETE CIRCUIT

Those extra amplifying stages inside the "box" of Fig. 3 appear in full in the complete circuit of Fig.

THE RADIO CONSTRUCTOR

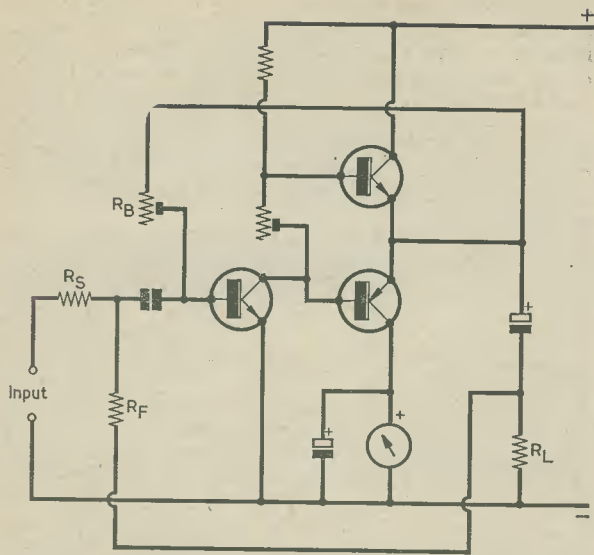


Fig. 2. A linear class B amplifier draws only a small idling current. It can also be made to do its own rectifying: a meter connected as shown receives d.c. equal to half the mean a.c. output current

5. The whole of the main amplifier is direct-coupled in the simplest possible way, advantage being taken of the ability of silicon transistors to operate with collector to emitter voltages which are the same as their base to emitter voltages. Using a fairly close tolerance transistor (type BC168C) in the first stage, the d.c. conditions for all stages can be set by means of one preset resistor, R15. This is adjusted so that the standing voltage at the emitters of TR5 and TR6 is 4.7V above the negative supply rail. Setting the bias of the output pair is carried out by R18, which trims the voltage across the stabilising diodes D2 and D3. These diodes can be almost any type of silicon junction diodes.

For calibration purposes, the a.c. gain has to be made adjustable, and this is allowed for by putting a potentiometer, R20, in the negative feedback circuit.

An extra transistor, TR7, is placed across the meter. Its job is to protect the movement from switch-on surges and overloads. TR7 conducts when the voltage across the meter coil exceeds about 500mV. This is quite a lot more than the normal drop at full-scale deflection for most meters, and if desired the drop across the movement can be artificially increased to, say, 400mV at f.s.d. by inserting a series resistor of appropriate value at the point marked with a cross. The author used a BC168 for TR7, but any other silicon p.n.p. type will be satisfactory provided it has a low bottoming voltage and is capable of taking about 100mA peak collector current.

ADAPTING TO THE METER

With a sine wave input the amplifier can deliver a little over 2.5V r.m.s., but to allow for peakier waveforms it is advisable to design for full-scale deflection at an output of only 1V r.m.s. This output

must drive a current through the load resistor R21 which is equal to twice the meter current. The first step in adapting the circuit to a given meter is to select a value for R21 which gives the required current, working from the equation:

$$R_{21} = \frac{\text{(Output voltage)}}{\text{(Twice meter current)}} = \frac{500}{I_m}$$

(where I_m is the meter full-scale current in milliamps and R21 is in ohms). Thus a 1mA meter calls for a value in R21 of 500Ω. A 470Ω resistor may in practice be used.

The meter current having been dealt with, we next have to select ranges which correspond to the existing meter scale markings. This is quite simple. The most sensitive range should be between 3 and 30mV, and we choose a figure that fits the scale markings. If, for example, the meter is marked 0-500, the lowest range can be 0-5mV. Having done this, we then use a value for R10 with as many kilohms as the lowest range has millivolts: e.g. 5kΩ for 0-5mV. Once again, it is quite in order to use a resistor of standard value slightly below the calculated value; e.g. 4.7kΩ instead of 5kΩ.

The design is now complete as far as adapting the circuit to the meter is concerned. There is still, however, a further important point to consider, and we shall next turn to this.

VOLTAGE LIMITATION

In the writer's opinion, it is always better to be safe than sorry where high voltages are concerned. In the present case, the wattage rating of R2 imposes an upper limit on the input voltage of 700V r.m.s. However, it is quite possible that an even lower limit will be imposed by the voltage ratings of certain components. If, for instance, a co-axial input cable is employed, how much voltage can safely be applied between its inner and outer conductors? Again, how much voltage will the input socket stand? Or the insulation between adjacent tags on the wafer switch? Or between the wafer and the spindle?

These are likely to be unknown quantities, and when dealing with unknown quantities it is always safest to be pessimistic about them. In consequence, it is recommended that the upper limit to the millivoltmeter ranges should not exceed 500V. On this basis the ideal meter scaling is 0-5 (or 0-50, or 0-500) because this gives six ranges starting from 5mV (which covers the signals likely to be obtained from audio sources such as pickups) and ending at

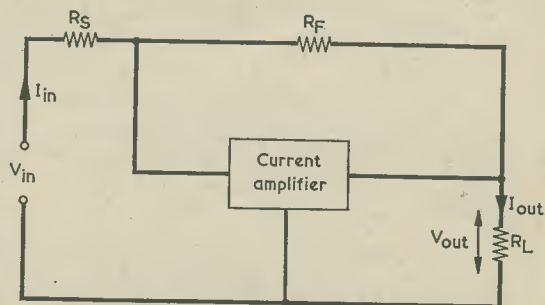


Fig. 3. General picture of a current amplifier with negative feedback, showing only the important resistances which define the gain and input impedance

COMPONENTS

Resistors

(All fixed resistors high stability, and $\frac{1}{4}$ watt unless otherwise stated. R2 to R8 inclusive 5% or better. All other fixed resistors 10% or better. See text for details on potentiometers).

R1	100k Ω 1 watt
R2	1M Ω $\frac{1}{2}$ watt
R3	100k Ω
R4	10k Ω
R5	1k Ω
R6	100 Ω (see text)
R7	22 Ω (see text)
R8	22 Ω (see text)
R9	3.3k Ω
R10	See text
R11	1M Ω
R12	1.5M Ω
R13	10k Ω
R14	4.7k Ω
R15	5M Ω potentiometer, preset
R16	15k Ω
R17	4.7k Ω
R18	15k Ω potentiometer, preset
R19	330 Ω
R20	5k Ω potentiometer, preset
R21	See text
R22	10 Ω

Capacitors

C1	0.1 μ F, 250V wkg.
C2	125 μ F electrolytic, 10V wkg.
C3	2.5 μ F electrolytic, 64V wkg.
C4	330pF
C5	320 μ F electrolytic, 2.5V wkg.
C6	125 μ F electrolytic, 10V wkg.
C7	250 μ F electrolytic, 6V wkg.

Semiconductors

TR1	40468A
TR2	BC168C
TR3	BC168C
TR4	BC168C
TR5	2N3794
TR6	2N4291
TR7	See text
D1	IS44
D2	IS44
D3	IS44, or any silicon junction diode
D4	IS44, or any silicon junction diode

Meter

M1	moving-coil meter, see text
----	-----------------------------

Switches

S1	1-pole 6-way wafer
S2	s.p.s.t., toggle or wafer

Miscellaneous

Coaxial sockets, terminals (as required)	
9V battery	

SUPPLY VOLTAGE


The millivoltmeter is not unduly affected by variations in supply voltage, and no voltage regulation is provided. The prototype, when adjusted for f.s.d. with a sine wave input and a 9V supply, showed an error of less than 3% when the supply was 6V, and less than 10% with 4.5V. The error at 4.5V was due to peak clipping and not to falling-off of gain. The error is, of course, smaller at less than f.s.d. By the same token, the error is larger if the meter is used to measure peaky waveforms. In general, the battery should be replaced when its voltage has dropped to 6V.

CONSTRUCTION

The instrument still has to be made, of course, and this is not a task to be undertaken in a slap-happy way, using odd bits and pieces from the junk box. A prime consideration is to make sure, well before beginning, that there is going to be plenty of room for everything inside the cabinet and on the front panel. Last-minute alterations and the cramming of components into odd corners are likely to spoil the performance by introducing stray capacitances and couplings which, even if they do not cause instability, may still play havoc with the accuracy. The following points should be given due attention.

Screening. It is essential to house the millivoltmeter in a metal box. In addition, the input connections and range switch should be put in a separate screened compartment. This may seem over-elaborate for an audio instrument, but experience with the prototype showed it to be essential. Without screening, the meter registered a reading on all settings of the range switch when a 50kHz input at 15V was applied, even when TR1 was taken out of circuit! This explained a rather striking rise in the frequency response above about 20kHz. Screening the input connections eliminated the effect.

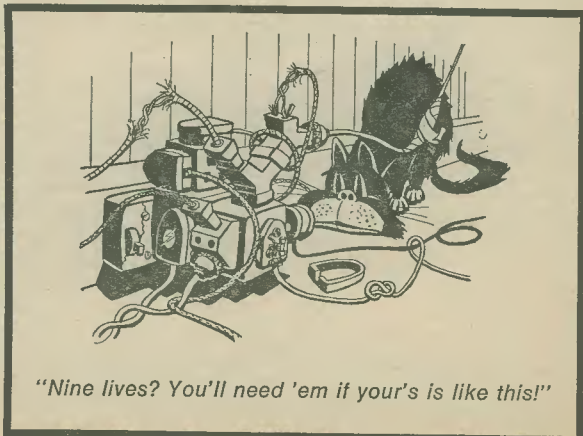Input wiring. The range resistors should be small and wired directly between the tags on the range switch. This keeps down the stray capacitance. Careful attention to the placement of the "earth" connection of the input circuit is essential. The important thing is to return the bottom end of the range attenuator (R7 and R8) to the earthy side of the input socket with a short, thick wire. If, as is



ances increase by 10% increments, whereas 220 Ω (and all other resistances in the diagrams) belongs to the more popular E12 Series, with successive increments of 20%.

desirable, a coaxial input socket is used, then the "earth" connection can be made to a solder tag clamped to the metal front panel by one of the bolts that fix the socket. Failing this, make a connection to the panel close to the socket. If an actual earth connection is used, it should go to the same point. All the negative wiring should be carried out with thick wire, to reduce couplings between output and input via the wiring.

Buffer stage. The mosfet should be connected last, after all the other components, and especially after diodes D1 and D2 are connected into circuit. When soldering, remember to earth both the bit of the iron and the circuit. When handling the 40468A, always pick it up by the case, never by the leads. Since the gate presents a very high impedance, it should be kept away from the input socket. It is quite a good idea to mount the buffer on a little circuit board or tagstrip supported behind the range switch. The bolts which hold the switch wafer can often be used to support the buffer circuit, and the whole lot can then be put inside the screening compartment for the input circuit.

Main amplifier. Use a logical layout, with the input at one end and the output at the other, and positioned so that the input lies near the buffer stage

resistor tolerance which can be accepted is 5%, and 1% is worth having if the meter scale is reasonably long. All resistors in the millivoltmeter should be high-stability. The tolerance of R1 is not important, but it should be rated at 1W.

The weakest link in the calibration circuit is R20. Ideally, it should be wire-wound, but economy will usually dictate a carbon preset component. Use a good make such as Egen type 467, and check the calibration from time to time. (The Egen type 467 potentiometer and suitable potentiometers for R15 and R18 are available from Amatronics, Ltd.)

If an audio generator with a monitored output is available, check the frequency response. Taking the reading at 1kHz as a reference, the error should not exceed 5% between 20Hz and 30kHz, with the possible exception of the second most sensitive range, where the h.f. response may tail off at a lower frequency because of the effect of stray capacitance across the potential divider output.

It will be appreciated that the bandwidth of the amplifier between 3dB points is much larger than the "useful measuring bandwidth" of the instrument. An error of 3dB amounts to some 30%, which is far too great in a measuring instrument. A wider bandwidth can, however, be used when making com-

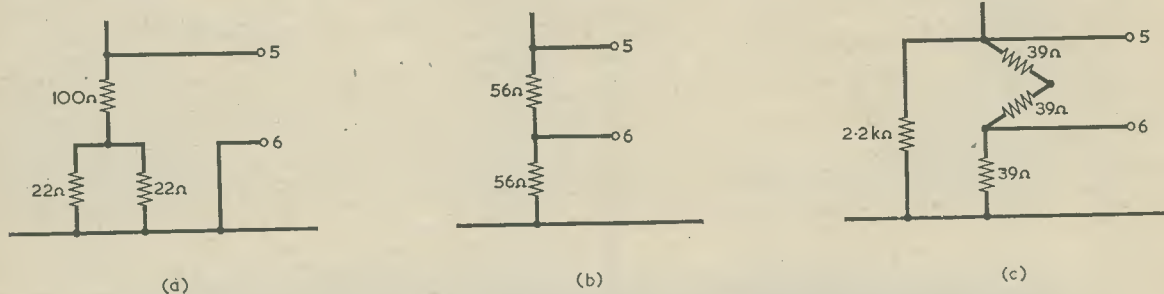


Fig. 6. Modified "highest range" connections to S1. The circuit of (a) is used when only five ranges are needed but the switch has six positions, whilst (b) gives a sixth range which is twice the fifth range. The configuration in (c) gives a sixth range which is three times the fifth range

whereupon the connection between these two is kept short. Any of the usual constructional techniques, including pin-board, will do.

Terminals. Co-axial connectors are best, and are probably essential if hum pickup is to be avoided, but it is a good idea to provide wander-plug sockets as well. Keep the output terminals away from the input.

CALIBRATION

Calibration can only be done with the aid of a known input voltage, which usually means monitoring the input with another meter of known accuracy. The applied frequency should not be too high, and should be well inside the range of accurate measurement for the other meter. (Many multimeters are only accurate up to 2kHz). In general, 50Hz will be a good bet. If possible, choose a voltage such that the extra meter reads near full scale but the millivoltmeter reads about half scale. Adjust R20 so that both instruments read the same. Only one adjustment is needed; the other ranges will be right if the range resistances are correct. The worst range

parative measurements at a fixed frequency outside the normal measuring band. Indications up to about 3MHz are obtained.

If linearity is unimportant, the sensitivity can be greatly increased by short-circuiting the output terminals. If this is done, the meter will register a reading with no input; the reading being due to noise in the amplifier. (If the wiring layout is poor, short-circuiting the output may cause the circuit to break into oscillation, in which case the meter reads full scale.)

The lower limit of the frequency response can be pushed below 20Hz if desired, by increasing the value of C3. Note, however, that C3, if electrolytic, must have low leakage. This is because its leakage current, if appreciable compared with the base current of TR2 (which is less than 1μA), will upset the biasing of the whole amplifier. The easiest way of ensuring low leakage is to use a capacitor with a much higher voltage rating than the actual voltage across it in the circuit, which is above 1V. This is why a 64V working capacitor is specified in the parts list. (2.5μF, 64V is one of the values in the Mullard miniature range.)

Design for a Class A Battery Amplifier

by

SIR DOUGLAS HALL, K.C.M.G., M.A. (Oxon)

Incorporating a field effect transistor, this comprehensive design may be either constructed in the form of an a.f. amplifier, or as an a.f. amplifier combined with a single transistor medium wave tuning head. In the latter instance, some of the components perform dual functions at a.f. and r.f.

IT DOES NOT SEEM THAT EITHER commercial firms or designers of equipment for home constructors cater very frequently for the listener who wants to be able to hear records, or local broadcast stations, using a battery amplifier which will give really good quality at ordinary room levels of volume. Most home listening is done at an average output level of less than 50mW, and for this purpose, a total of 150mW undistorted output allows for the peaks to be reproduced without distortion.

The output of the amplifier to be described is about 150mW, and this is at a very high level of quality which deserves to be fed into a good speaker. The amplifier draws 18mA from an 18 volt battery, and provided fairly large cells are used—the U2 size is recommended—it will prove economical to use, giving very many hours service from a set of 12 of these cells.

BASIC CIRCUIT

The circuit is shown, in its simplest form, in Fig. 1. The output from a crystal pick-up, or a similar high impedance source of signal, is applied to a high resistance volume control, and thence to the gate of a field effect transistor. The drain of the f.e.t. is directly coupled to the base of a medium power silicon p.n.p. transistor, the drain current of the f.e.t. being the base current of this output transistor. At the time of writing there is still a dearth of silicon p.n.p. transistors which will maintain their amplification factor when more than about 1 or 2mA pass through them, but the inexpensive 2N3702 will maintain an hFE of from 60 to 300 in the conditions applying in this circuit. Typical specimens may be expected to show

a gain of about 120 times. The maximum dissipation of the 2N3702 is 300mW at 25°C and with about 16 volts available from emitter to collector (about 2 volts are lost across the relevant part of the 250Ω preset potentiometer) a maximum current of 18mA is permissible. The output transformer chosen has a ratio of 9.2:1 and will therefore cause a reflected load of about 250Ω to appear across its primary when connected to a 3Ω speaker. With a typical 2N3702 this will produce a load of $250 \times 120 = 30k\Omega$ at the base, and this is the drain load for the f.e.t. which will ensure good amplification from that device.

Source bias for the f.e.t. appears across the lower half of the 250Ω pre-set potentiometer. This potentiometer should be a standard 1 watt component, and not a miniature.

There is 2-stage negative feedback of d.c., and the circuit is consequently very stable. The large electrolytic capacitor prevents negative feedback of the signal, though a small amount of negative feedback results from the top half of the potentiometer being in the source lead without a bypass capacitor. This feedback is not large as the resistance involved is small in comparison with the drain load.

A capacitor appears across the input to the amplifier, this being found necessary to avoid excessive treble and consequent distortion. Constructors may experiment with different values. The 0.001μF value shown in Fig. 1 proved to be the best compromise for various pick-up cartridges tried with the prototype.

MODIFICATIONS

The circuit in Fig. 1 will function as an efficient amplifier as it stands with almost all specimens of the 40468. It is set up by first setting the slider of the potentiometer close to the end connected to the source and then, with a meter in one of the battery leads, adjusting the potentiometer until a reading of 18mA is given.

However, there are various modifications which are worth while, and some of these are shown in Fig. 2.

It will be noted that an a.f. choke now appears between the drain of the f.e.t. and the positive supply line. This component was omitted in Fig. 1 because the great majority of 40468's pass negligible leakage current. But the f.e.t. type 40468 has now been superseded by the 40468A which, while offering certain improvements, is no longer restricted for leakage current, and the latter can, in rare examples, be as high as 100μA. Let us consider the case where a high leakage f.e.t. is

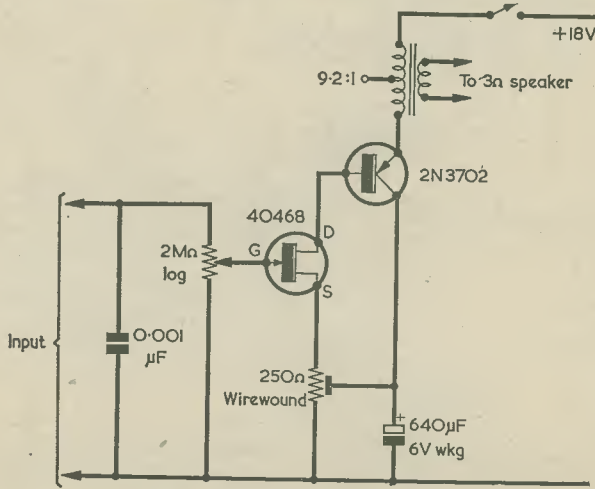


Fig. 1. Basic amplifier circuit, illustrating the combination of f.e.t. and output transistor

used in combination with a 2N3702 offering a current amplification of 300. If this output transistor passes 18mA, a base current of 18mA divided by 300, i.e. 60 μ A, will be required. But such a current is lower than the f.e.t. leakage current alone, so the circuit will not function.

At first sight it might appear that a resistor of about 1k Ω between the drain of the f.e.t. and the positive supply line would put matters right, as the f.e.t. would then pass a total of about 700 μ A whilst the output transistor was passing a base current of 60 μ A. The leakage current of the f.e.t. then becomes a small proportion of the total current passing through it. However, the 1k Ω resistor would reduce the drain load of the f.e.t. and amplification would fall drastically. A better scheme is to use the primary of an Eagle LT44 interstage transformer instead of the resistor. The primary of this transformer offers a d.c. resistance of about 1k Ω , and presents the a.f. signal with a high inductive load, whereupon all is well. The transformer primary inductance is damped by the output impedance of the f.e.t. and the input impedance of the 2N3702, and no noticeable deterioration of quality accompanies its inclusion in the circuit. The green lead and outer red lead are used here, the central red lead and the black and white leads being left disconnected. (Make sure that the LT44 is an Eagle component. This will be sold in a box and its clamp

will have stamped into it "20k Ω 1.0k Ω ". There are inferior imitations which have "LT44" applied by what appears to be a rubber stamp. These imitations are not suitable for the present requirement, as both the d.c. resistance and the inductance of the winding will be found to be far too low.)

In both Figs. 1 and 2, the substrate of the f.e.t. is left unconnected.

Turning to other points in the circuit of Fig. 2, the non-earthly input lead is now taken to a 330k Ω resistor which is isolated from the volume control by a 0.01 μ F capacitor. The capacitor should be rated at 250 volts working. Also, two silicon diodes (not germanium) are connected back to back between the slider and the earthy end of the volume control. The 0.01 μ F capacitor protects the gate of the f.e.t. from any direct voltage which might accidentally find its way there, and the diodes limit alternating voltage on the gate to about 0.5 volt so that accidental applications of, say, mains hum, are rendered harmless. Whatever other refinements are added it is particularly recommended that the diodes be included in the circuit, or the f.e.t. may die a mysterious death one day. It is also very wise, incidentally, to use a transistor holder for the f.e.t. Although an iron can be used for wiring it up with all due precautions, it is only too easy for a lethal dose of a.c. to be applied to the gate. It is better to make all the connections to

a transistor holder first, and then insert the f.e.t. afterwards.

A tone control has been added in Fig. 2, this consisting of a 500pF

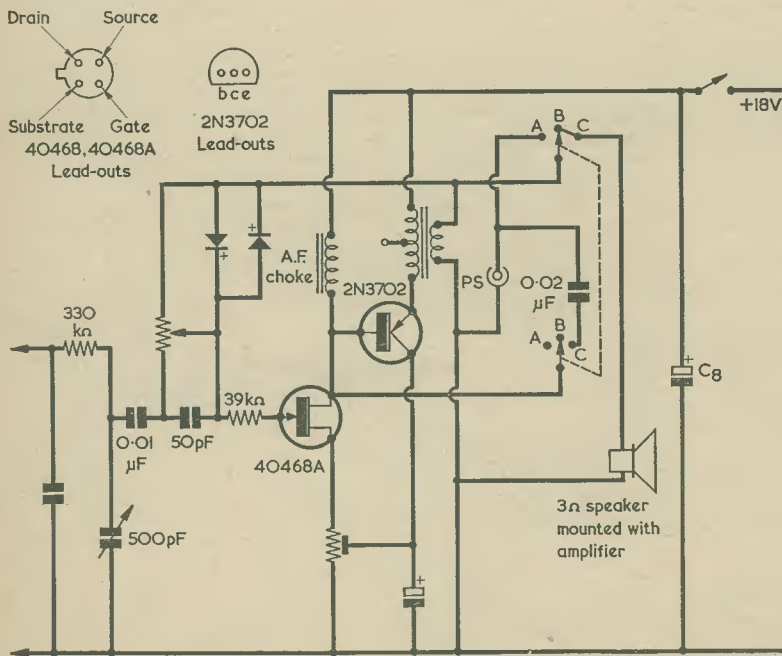


Fig. 2. A more comprehensive circuit, developed from Fig. 1. Unmarked components have the same values as in the basic circuit

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 10%)

- R1 3.3M Ω
- R2 330k Ω
- R3 39k Ω
- VR1 2.5k Ω or 5k Ω , preset potentiometer, miniature
- VR2 2M Ω potentiometer, log, with switch S3
- VR3 250 Ω , preset potentiometer, wirewound, 1 watt

Capacitors

- C1 4 μ F electrolytic, 6V wkg.
- C2 640 μ F electrolytic, 6V wkg.
- C3 0.01 μ F
- C4 0.001 μ F
- C5 0.01 μ F, 250V wkg.
- C6 50pF
- C7 0.02 μ F
- C8 1,000 μ F electrolytic, 25V wkg.
- VC1 500pF variable air-spaced or solid dielectric (see text)
- VC2 500pF variable solid dielectric

Inductors

- L1, 2 (see text)
- T1 Output transformer type T/T7 (Radiospares)
- T2 Interstage transformer type LT44, primary connected only (Eagle)

Semiconductors

- TR1 BC168C
- TR2 40468 or 40468A
- TR3 2N3702 or TIS61
- D1 OA81
- D2,3 silicon diodes (e.g. IS44)

Switches

- S1 2-pole 2-way rotary
- S2 2-pole 3-way rotary (or 3-pole 3-way (see text))
- S3 s.p.s.t., combined with VR2

Sockets, etc.

- PS1, 2 phono sockets
- 1 transistor holder (for TR2)
- 3 battery holders for 4 U2 cells each

Battery

12 U2 cells

Speaker

3 Ω speaker

Miscellaneous

- 8in. x $\frac{3}{4}$ in. ferrite rod
- Control knobs, as required
- Cabinet, etc.

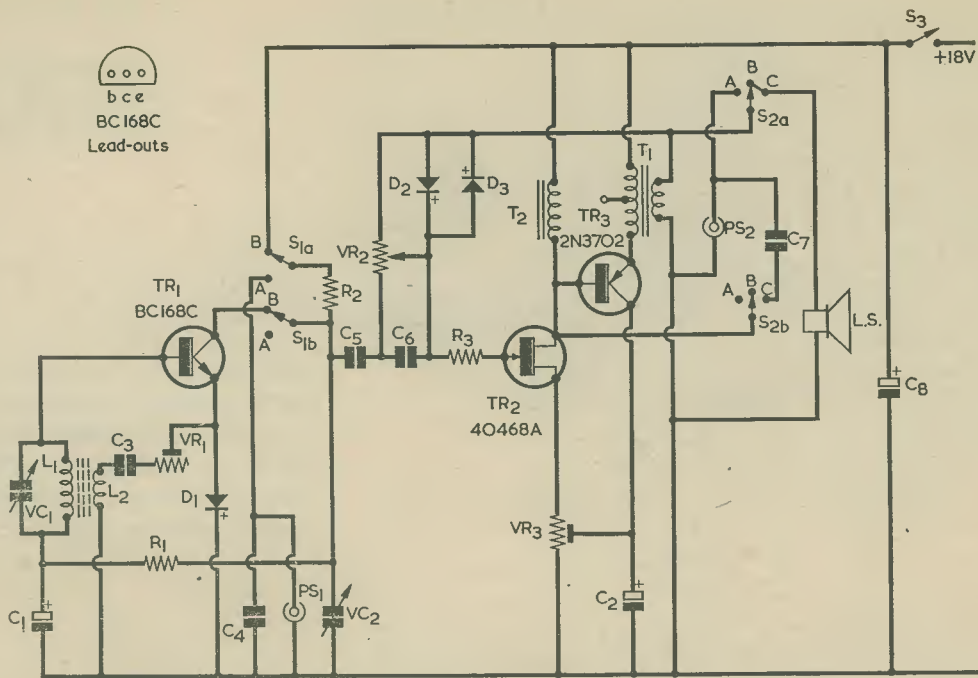


Fig. 3. Adding a medium wave tuning head. All components in this diagram are specified in the Components List

variable capacitor. Enmeshing the vanes of this component causes a very smooth loss of the highest audio frequencies. The range of control available is improved at intermediate settings of the volume control by the presence of the 50pF capacitor across the non-earthly half of the volume control circuit, this giving a degree of treble lift when the variable capacitor is set to minimum. Finally, the 39kΩ resistor prevents any possibility of spurious oscillation by the f.e.t.

So much for modifications at the input end. At the output end a 2-pole 3-way switch is employed to make provision for an internal or external speaker, and to take the output direct from the f.e.t. when it is wished to use the amplifier to record on to tape. As shown in Fig. 2, the switch is at position B, and an internal speaker, built together with the amplifier, is in use. If the switch is turned to position A the output is taken to a phono socket, into which a lead from an external speaker may be plugged. If the switch is turned to C, the output is taken to this same socket direct from the f.e.t. and a tape recorder may be used. The internal speaker remains connected and may be used as a monitor though volume will be reduced owing to the additional load across the f.e.t. So far as the switch

itself is concerned, it will probably be found easier to obtain a 3-pole 3-way component rather than a 2-pole 3-way switch. In this case the unwanted pole is ignored.

It will be seen that the earthy end of the volume control is now taken to the negative supply line via the secondary of the output transformer. This provides a useful additional degree of negative feedback which considerably improves quality. At first sight the amount of feedback might appear excessive, but it should be remembered that the output transistor functions as an emitter follower, which means that although it is an efficient power amplifier it gives no voltage gain. So the additional feedback introduced is, in effect, over the f.e.t. stage alone. It may be necessary to try both ways of connecting the leads on the secondary of the output transformer. If connected wrong way round, positive feedback will be given with consequent oscillation.

TUNING HEAD

Fig. 3 shows how, if desired, a simple medium wave tuning head may be added. As the amplifier has a high input impedance it is useful for the output of the tuner to be similarly at high impedance. The author's single transistor "Sponta-

flex" design is very suitable here, offering in this case an output impedance of about 330kΩ.*

All the components to the right of the new switch, S1 in Fig. 3, have already appeared in Fig. 2, and the wiring of this part remains unchanged, although some of the components now have a radio frequency function to perform in addition to their duties at audio frequencies.

The radio signal appears across L1 which is wound on a length of ferrite rod, and is tuned by VC1. The whole of this tuned circuit forms the base input of TR1 which, at radio frequencies, is a common collector amplifier with a high input impedance. The r.f. output, much amplified as to current, appears across diode D1 in the emitter circuit. The diode next functions as an audio frequency load and TR1 amplifies again, this time as a common base audio amplifier. A combination of comparatively high direct voltage from the battery and a type of transistor which maintains good amplification when passing only 50μA means that a very high output


*The author's "Spontaflex" circuit was originally introduced in the June 1964 issue. The latest and most up-to-date version was described in "Modifying the 'Spontaflex' Circuit for Silicon Transistors", published in the May 1969 issue. —Editor.

(Continued on page 359)

HIGH-SELECT T.R.F. R

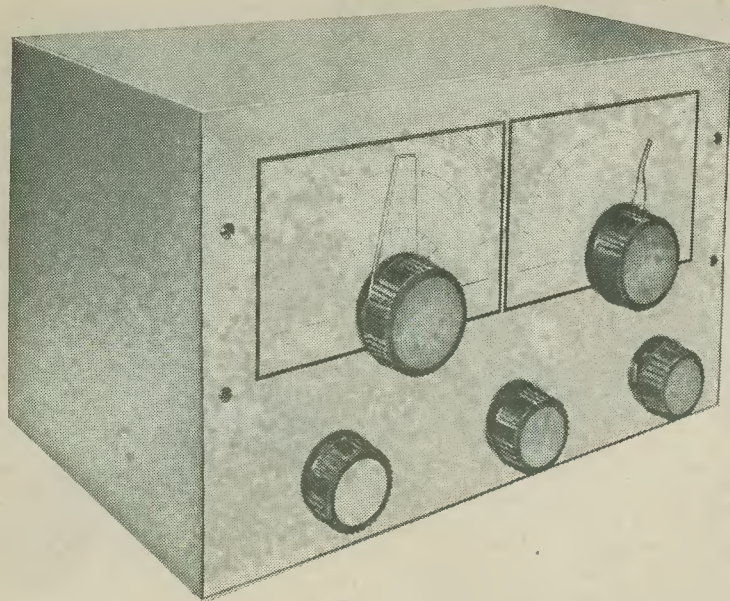F. G. RAYER, A

Our contributor recently turned his receiver and decided to re-examine the design and construction of a simple t.r.f. receiver taken to ensure that efficient regeneration of the receiver is described in this article of the tests he carried out on his design between its performance a



FEW CIRCUITS CAN PROVIDE SUCH GOOD RESULTS with so little complication as an efficiently operated t.r.f. receiver. The writer recently returned to the use of a small t.r.f. circuit for compact equipment required for /A operation. The performance obtained, together with subsequent tests, show that the t.r.f. receiver is in fact an excellent project when the complicated circuitry of a superhet is to be avoided.

This article will describe the t.r.f. receiver used. First, however, the writer would like to give details of the tests he carried out, if only to demonstrate to those who automatically advocate the superhet that the t.r.f. receiver can offer a comparable short wave performance. And, of course, the t.r.f. receiver is much easier to construct and bring up to full working order.

REGENERATION

Before making comparisons between t.r.f. and superhet receivers, it must be noted that the results

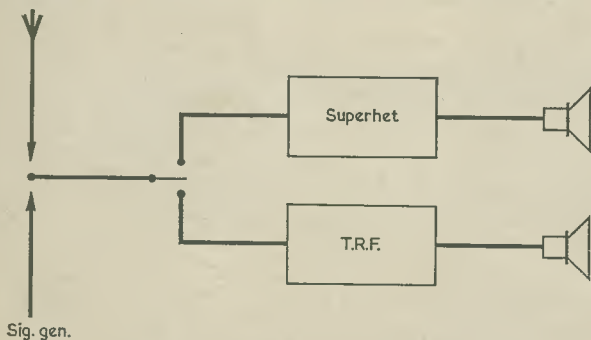


Fig. 1. The method employed for comparison of t.r.f. and superhet receiver performance

obtainable from a t.r.f. set depend almost entirely on regeneration. F. E. Terman, in discussing regenerative detectors, points out that "Although regeneration represents an inexpensive means of increasing the radio-frequency amplification, it increases the selectivity excessively"

Nobody tuning a crowded amateur or other short wave band these days is likely to feel that selectivity can be excessive, and it is worth recalling that the adjunct to some expensive communication receivers is a Q-Multiplier, this being a circuit which takes advantage of regeneration to increase selectivity.

*F. E. Terman, "Radio Engineers' Handbook" (First Edition, page 574), Mc-Graw Hill.

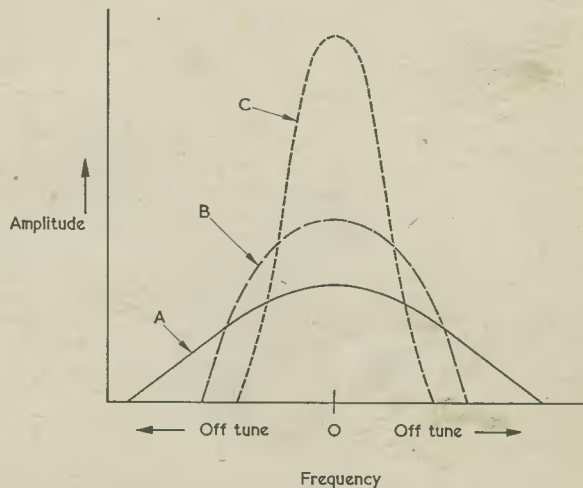


Fig. 2. Illustrating the sharpening of selectivity which results from the use of regeneration

SELECTIVITY RECEIVER

by

A.I.E.R.E., G30GR

attention from the superhet short wave
its t.r.f. counterpart. The result was the
t.r.f. circuit in which particular care was
ration was obtained. The construction of
le, and the author begins by giving details
sign, these tests giving direct comparison
and that of a superhet receiver

One way of comparing t.r.f. and superhet receiver performance is shown in Fig. 1. Each receiver has a speaker, with muting switch if wanted. Input is first applied from the signal generator. The method is to tune in the signal generator output accurately with both receivers, then check for individual off-tune response by retuning the generator. The superhet a.g.c. is switched out or temporarily disabled for this test.

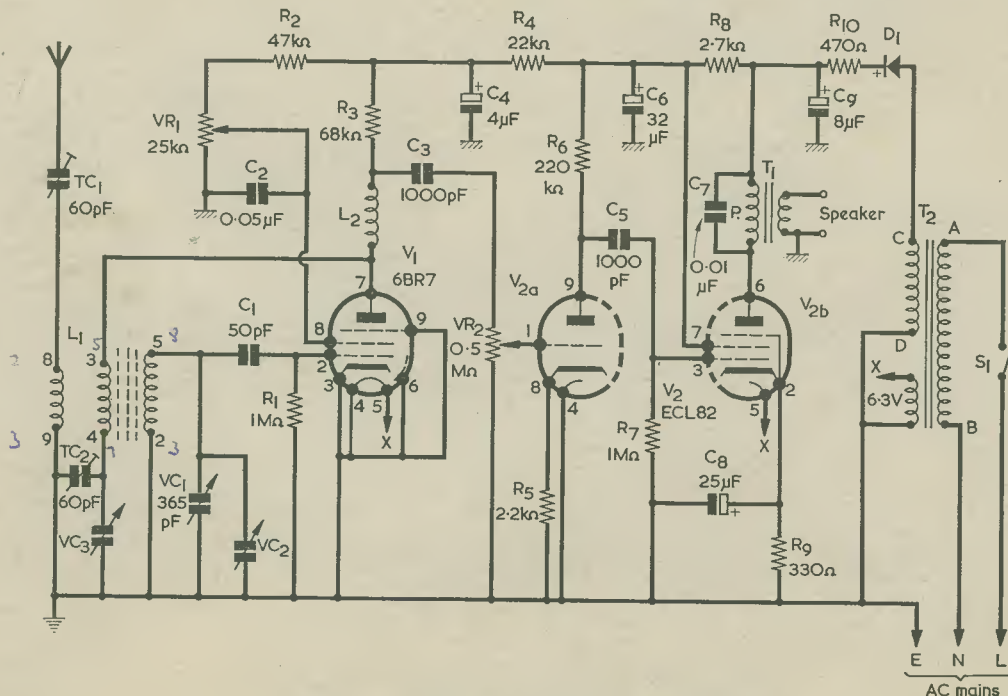


Fig. 3. Complete circuit of the t.r.f. receiver



Cover Feature

Fig. 2 indicates the effects of regeneration with the t.r.f. receiver. With no regeneration, tuned circuit selectivity is broad, as in curve A. Introducing regeneration increases selectivity, and the response is sharpened, as in curve B. With critical regeneration, a high and very sharp curve is obtained, as shown by C.

In tests made in conditions favourable to the t.r.f. receiver (that is, with weak and relatively weak signals over the frequency range 15 to 3MHz) curve C was on the average indistinguishable from that obtained with a superhet having two i.f. transformers incorporating four 465kHz tuned circuits. The superhet also had one r.f. stage but this contributed virtually nothing to adjacent channel selectivity, being provided to reduce second channel interference. This interference arises with a superhet from signals spaced by twice the intermediate frequency from wanted signals, and can be a troublesome effect. It is of course wholly absent with a t.r.f. receiver.

At frequencies higher than 15MHz or so good results were still obtainable with the t.r.f. set, but more care in setting up was required. At lower frequencies, very strong signals may be present, as from medium wave stations, and these tend to swamp a t.r.f. receiver. Strong local signals on any frequency tend to swamp weaker adjacent signals, but this effect can be reduced by suitable means.

TABLE I
Frequency Ranges
 (Coils employed are Denco Miniature Dual-Purpose,
 Green.)

Range	Coverage
1	150-500kHz
2	500-1,600kHz
3	1.5-5MHz
4	5-18MHz
5	15-36MHz

SENSITIVITY

Sensitivity was checked using a laboratory type signal generator as input, as shown in Fig. 1, the t.r.f. receiver being that to be described here. This receiver employs Denco plug-in coils, the ranges covered being listed in Table I. To compare the results given for differing L/C ratios in the tuning circuit, tests were carried out at 16MHz, which is both at the low frequency end of Range 5 and at the high frequency end of Range 4. Table II gives the results, and it will be seen that readings were also taken at a frequency near the highest tunable, 30MHz, and at 9MHz. The input figures quoted in Table II are for the weakest signal capable of being copied with the t.r.f. receiver, using its loudspeaker, in conditions of insignificant background noise. They vary somewhat, depending on absolute optimum adjustment of regeneration. If there is local ambient background noise, headphones would give better results.

Practical results with an aerial appear to confirm the tests. Stronger distant signals, such as 28MHz U.S. amateurs, and those on 21 and 14MHz, could be received in great number with a modest aerial when propagation was suitable. The best Dx was Australia. In fact, with the arrangement of Fig. 1, it was quite difficult to find a signal with the superhet which could not also be brought in with the t.r.f. set. The signals lost with the t.r.f. receiver were very weak transmissions, and weak or other signals too near a strong transmission. Over the 30 to 1.8MHz range, the t.r.f. set will receive literally hundreds of amateur and other short wave signals.

The t.r.f. receiver employed in the tests will now be described. It should be mentioned that equally good results could have been obtained with any similar type of t.r.f. receiver in which particular attention has been paid to obtaining efficient regeneration.

CIRCUIT NOTES

A few points should next be mentioned regarding the receiver circuit, which is given in Fig. 3. Commercially made plug-in coils are used for simplicity in band changing and wiring. As may be seen from Table I, five coils cover all short wave bands as well as medium and long waves, should these last two ranges be required. Due partly to slightly different tuning and stray capacitances, and the adjustment of

dust cores, some of the ranges listed in the Table differ slightly from the nominal range figures quoted in Denco literature.

VC1 is for coarse tuning, or band-setting. For short wave tuning and critical attention to a narrow band of frequencies, such as in an amateur band, the small variable capacitor VC2 is employed, this giving fine tuning. VC2 should operate smoothly. Its exact value is to some extent a matter of choice, because a valve which gives adequate coverage on lower frequencies is too large for easy band-spreading of higher frequencies. If operated without a slow-motion ball drive a value of about 5 to 10pF is suggested. A value of some 15 to 20pF will be satisfactory if VC2 is fitted with a ball drive or if the main listening interest is in the low frequency bands. A recommended component is the Jackson type C804 variable capacitor.

Trimmer TC1 is practically essential in the circuit, and it reduces aerial loading with all but short aeri-als. Since one of the prime objects in the receiver design is the ability to obtain smooth, easily controlled regeneration, there are three variable components which affect performance in this respect. The first of these is VC3, the reaction control proper. This has a relatively small capacitance and it is paralleled by trimmer TC2. The result is that a wide angle of rotation in VC3 is possible for a relatively small change in overall capacitance, and its adjustment is consequently eased. The third variable component is VR1, which varies the screen-grid potential of V1 and enables this valve to be in the optimum condition for smooth regeneration. With long aeri-als, adjustment of trimmer TC1 will assist in obtaining best regeneration performance.

The 6BR7 specified for V1 is particularly suitable as a detector, being a high gain type of rigid mechanical design. VR2 is an audio gain control, and the following triode and pentode sections of the ECL82 provide audio amplification. The h.t. supply is obtained from a half-wave rectifier circuit with adequate smoothing, particularly to the early stages.

MECHANICAL CONSTRUCTION

Construction must be rigid, so a 4-sided chassis is used, with 3in. brackets to give additional support to the panel. The brackets were actually a 4 by 3in. Home Radio "Universal Chassis" side cut from opposite corners at 45 degrees. The chassis is drilled for components as in Fig. 4.

TABLE II
T.R.F. Sensitivity

Frequency	Input Signal Voltage	
	a.m.	c.w.
30MHz	4 μ V	2 μ V
16MHz (Range 5)	10 μ V	4 μ V
16MHz (Range 4)	5 μ V	2 μ V
9MHz	8 μ V	3 μ V

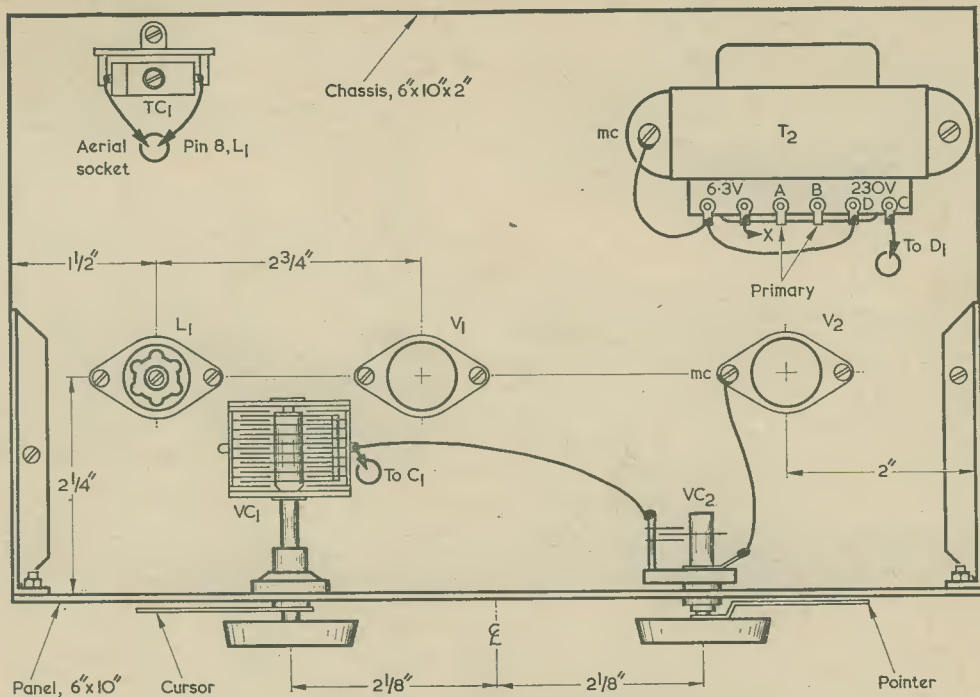


Fig. 4. Top view of the chassis, giving the more important dimensions

VC1 is bolted to the chassis, and its spindle must match up with the ball drive. Spacing washers are essential between chassis and this capacitor. A bolt secures the ball drive lug to the panel. If a drive is to be used with VC2, set this capacitor back sufficiently, and mount it on a strong bracket.

Fig. 5 shows the underside. Holes for VR1, VR2, VC3, the mains lead grommet, and to provide clearance for the speaker and aerial/earth sockets are most readily made with a $\frac{3}{8}$ in. chassis punch, before chassis assembly. (The type of chassis listed consists actually of a 6 x 10 in. flat plate, with separate 6 x 2 in. and 10 x 2 in. flanged sides which are bolted on.)

WIRING NOTES


Heater and a.f. leads run against the chassis. R.F. leads and components are clear of the chassis. The wires from T2 run down through a grommet (See Fig. 4). The rectifier, R4, C4, R10 and several other items and leads are anchored on a 9-way tagstrip, as shown in Fig. 5. A small tagstrip anchors the positive leads C6 and C9. On top, TC1 is soldered to the tags of a similar strip, this being bolted above the Aerial-Earth sockets.

If difficulty is experienced in obtaining a 9-way tagstrip having earthed tags in the positions shown in Fig. 5, a suitable alternative is a 9-way tagstrip with the two end tags earthed, this being available from Henry's Radio, Ltd.

The mains lead is 3-core flex, taken to a 3-pin plug with 3 amp fuse. With the new mains lead coding, use green and yellow striped for earth, this being

taken to chassis as in Fig. 5. Blue is neutral, going to "B" on T2 (see Fig. 3). Brown is live, running from the plug fuse to S1, which in turn connects to "A" on T2.

It is important to note that the tag positioning for T2 shown in Fig. 4 is typical only, and that individual transformers may have different tag positions or may have wire lead-outs. The mains transformer should be connected up so that it agrees with the circuit diagram of Fig. 3. Suitable components for both T2 and T1 are available from Home Radio, and the appropriate Catalogue Numbers are given in the Components List.

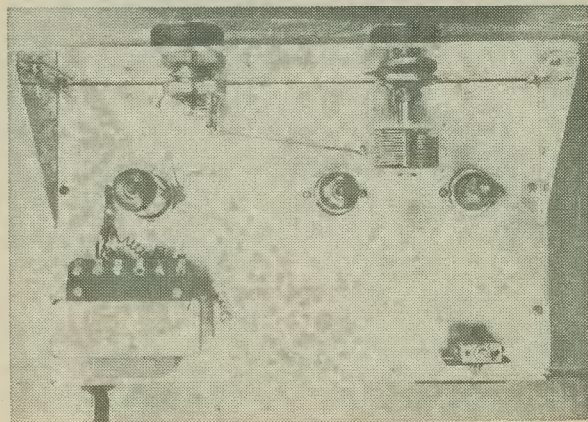

Looking down on the top of the chassis.

For chassis wiring, use insulated wire or sleeving where necessary. The connecting wire in the r.f. circuit around the coil and the variable capacitors should be 20 s.w.g. or thicker. All r.f. leads are short and direct. Wiring details should be clear from Figs. 4 and 5. In these diagrams, "MC" indicates earthing tags which are bolted securely to chassis. The tag of VR1 which connects to chassis is that corresponding to the maximum anti-clockwise position of the slider.

EXTERNAL CONNECTIONS

The receiver should not be operated without a speaker or suitable alternative load connected across the output, as high a.f. voltages may then appear in the primary circuit of T1. For weak signals or personal short wave reception, phones may be connected in parallel with the speaker. If it is intended to occasionally use phones on their own, a 10Ω 1 watt resistor should be permanently connected across the speaker socket terminals to function as a load. This resistor will not cause any significant reduction in speaker output. Low impedance phones will give greatest sensitivity but remember to keep the a.f. gain control at a low setting when searching for signals, because of the high power available from V2(b).


Since the h.t. voltage depends on the mains voltage and several other factors, a voltage check can be made across C9 if wished. The voltage here should be about 180 to 200 volts, and R10 can, if necessary, be changed in value to obtain this figure.

The aerial will probably depend upon what is available—such as an end-connected wire for all bands, or perhaps an aerial made for one band only. Aerial tuners of the usual type may be connected between aerial and receiver.

The receiver will, of course, have an earth connection via the mains socket, but it is desirable to augment this with a more efficient (for r.f.) earth connection run over the shortest route possible. A good earth connection can give a considerable improvement with weak low frequency band signals.

BAND COVERAGE AND TUNING

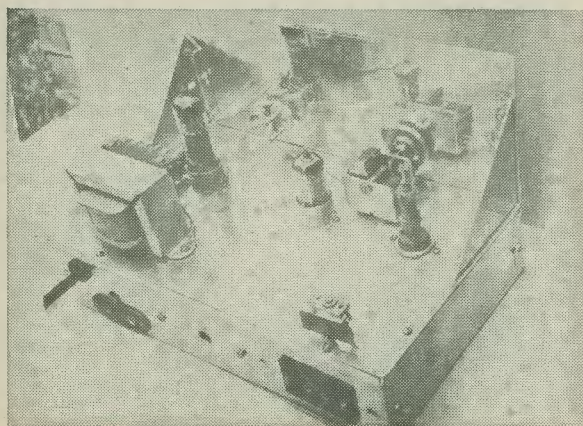As already mentioned, five plug-in coils are available, the actual frequency coverage obtained being listed in Table I.



Rear upper view. The two panel-strengthening brackets are clearly visible.

TABLE III

Frequency/Dial Readings			
Range 1.		Range 4.	
150 kHz	100	5.0 MHz	100
160	93	5.5	83
170	78	6.0	71
180	70	6.5	61
200	58	7.0	52
220	49	7.5	46
240	40	8.0	41
260	35	9.0	33
300	27	10	27
350	21	11	22
400	17	12	19
500	10	13	16
		14	14
		15	11
		16	9
Range 2.			
500 kHz	100	17	7
550	83	18	5
600	71		
650	61	Range 5.	
700	53	15 MHz	52
750	46	16	45
800	42	17	41
900	33	18	37
1,000	27	20	31
1,100	22	22	26
1,200	20	24	22
1,300	17	26	19
1,400	14	28	17
1,500	12	30	14
1,600	9	32	12
		34	10
		36	8
Range 3.			
1.5 MHz	100		
1.6	88		
1.7	78		
1.8	70		
1.9	63		
2.0	57		
2.5	37		
3.0	27		
3.5	20		
3.8	16		
4.0	14		
4.5	10		
5.0	6		

Coverage at the low frequency end of each range depends considerably on the position of the adjustable cores. The full swing of VC1 is not used for Range 5. Ranges 1 and 2 are the usual long wave and medium wave sectors, while Range 3 is very useful for certain amateur and other transmissions. A very large number of short wave transmissions fall into Range 4. Range 5 is primarily for h.f. bands capable of long distance propagation, but these are much subjected to seasonal and other variations.

As a guide, Table III gives frequencies and dial readings obtained with the prototype with VC2 at half-capacitance. VC1 is fully closed when its cursor

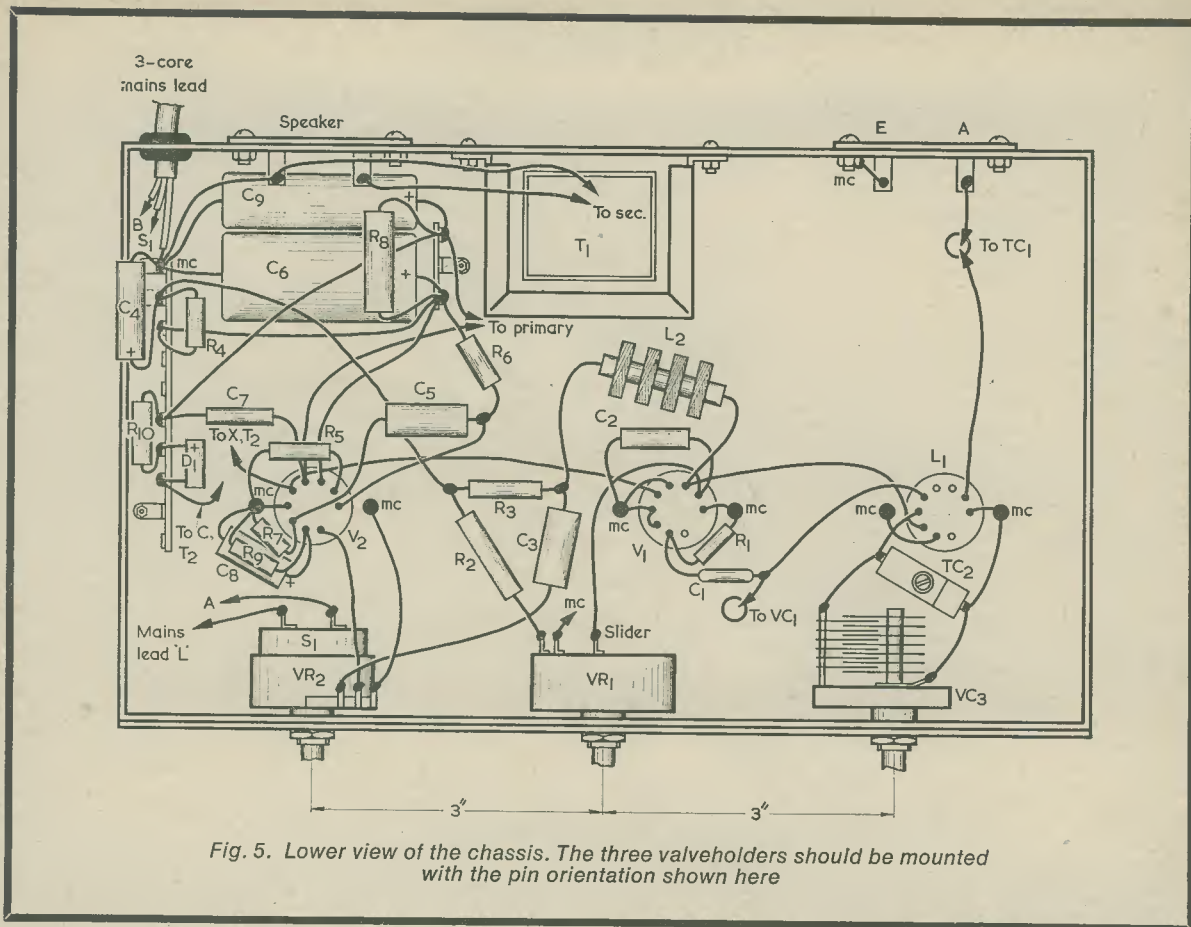


Fig. 5. Lower view of the chassis. The three valveholders should be mounted with the pin orientation shown here

is at 100 on the scale. Slight differences at the high frequency end of the ranges may occur, due mainly to varying values chosen for VC2.

Bandspreading with the aid of VC2 does not increase selectivity or the actual separation between stations, but it does help by causing a very narrow band of frequencies to be covered with full 180 degree rotation.

VC1 is used for general tuning, to find a band, or to set the cursor to a previously logged spot. During this time VC2 may be left half-closed (50 on its scale). Signals at nearby higher and lower frequencies can then be tuned in with VC2.

REGENERATION

Correct regeneration is the point upon which virtually the whole of the receiver selectivity and sensitivity depends. VR1 has a considerable effect on regeneration, due to its changing the screen-grid voltage of V1. Closing VC3 increases regenerative feedback, as does increasing the value of TC2. VC3 and VR1 are never merely turned to the maximum clockwise position, as is possible with an audio or r.f. gain control.

Initially set TC2 and VC3 to about half their maximum capacitance. Rotate VR1 from its minimum (anti-clockwise) position until a heterodyne whistle is heard when VC1 is tuned through a transmission. Opening VC3 slightly should reduce regen-

eration sufficiently to stop this whistle. The most sensitive condition for a.m. reception is obtained when VC3 is *very slightly* opened from the setting which causes oscillation and the appearance of heterodynes.

If VR1 is advanced too far, VC3 will need to be near minimum capacitance to stop oscillation, and its adjustment will be critical and difficult. Should TC2 insert too much capacitance, oscillation is likely even with VC3 at minimum. But should TC2 insert too little capacitance, the benefit it gives in easing adjustment of VC3 is largely lost. The optimum setting for this trimmer will soon be found after a little experience.

Regeneration is influenced by the position of the coil cores. If these are set up for the range coverages given in Table III they will also be in suitable positions for good regeneration. The cores should be locked, with 6 BA nuts passed over the protruding threaded stems, to retain calibration.

With certain aerials an abrupt loss of regeneration may arise at some frequencies, this being due to resonances in the aerial system. Should this occur, TC1 is adjusted to clear the effect.

There should be no great difficulty in setting up TC2 and VR1 so that VC3 provides an extremely smooth control over regeneration. Once adjusted, TC2 can be left. VR1, on the other hand, will have to be readjusted when making considerable changes in frequency, or after changing coils.

For c.w. reception, it is necessary to maintain V1

COMPONENTS

Resistors

(All fixed values $\frac{1}{2}$ watt 10% unless otherwise stated)

R1	1M Ω
R2	47k Ω 1 watt
R3	68k Ω
R4	22k Ω
R5	2.2k Ω
R6	220k Ω
R7	1M Ω
R8	2.7k Ω 1 watt
R9	330 Ω 1 watt
R10	470 Ω 2 watt (see text)
VR1	25k Ω potentiometer, linear wire-wound, 1 watt (Home Radio Cat. No. VR25)
VR2	500k Ω potentiometer, log, with switch S1

Capacitors

C1	50pF silver-mica
C2	0.05 μ F paper or plastic foil, 250V wkg
C3	0.001 μ F paper or plastic foil, 350V wkg.
C4	4 μ F electrolytic, 350V wkg.
C5	0.001 μ F paper or plastic foil, 350V wkg.
C6	32 μ F electrolytic, 350V wkg.
C7	0.01 μ F paper or plastic foil, 350V wkg.
C8	25 μ F electrolytic, 25V wkg.
C9	8 μ F electrolytic, 350V wkg.
VC1	365pF variable, Jackson type 01 (Home Radio Cat. No. VC1A)
VC2	(see text)
VC3	50pF variable, Jackson type C804
TC1	60pF mica trimmer
TC2	60pF mica trimmer

Inductors

L1	Denco Miniature Dual-Purpose (Valve) coil, Green, ranges as required (see Table I)
L2	2.6mH r.f. choke, type RFC5 (Denco)

T1	Output transformer, 40:1 (Home Radio Cat. No. TO43)
T2	Mains transformer, secondaries 230V 45mA and 6.3V 1.5A (Home Radio Cat. No. TM26A)

Valves

V1	6BR7
V2	ECL82

Rectifier

D1	250V (1,000 p.i.v.) silicon rectifier, BY100 or equivalent
----	--

Switch

S1	s.p.s.t., part of VR2
----	-----------------------

Valveholders, Sockets

2	B9A valveholders with skirts (for V1 and V2)
1	B9A valveholder without skirt (for LI)
1	Socket strip, "Ae/E" (Home Radio Cat. No. Z101A)
1	Socket strip, "LS" (Home Radio Cat. No. Z101C)

Miscellaneous


1	chassis, 6 x 10 x 2in. (Home Radio Cat. No. CU26)
1	plate (for panel), 6 x 10in. (Home Radio Cat. No. CU180)
2	brackets, made from single flanged chassis side, 3 x 4in. (Home Radio Cat. No. CU144)
1	epicyclic ball drive, 6:1, type 4511/F (Jackson Bros.)*

* If desired, a second ball drive may be employed with VC2 (see text).

2	knobs 1 7/16in. dia. (Home Radio Cat. No. KN63)
3	knobs 1 1/8in. dia. (Home Radio Cat. No. KN64)
2	cursors or pointers (home constructed)
2	3-way tagstrips, centre tag earthed
1	9-way tagstrip, 2 tags earthed (see text)
	Tuning scales, from Data Panel-Signs, Set No. 5.

in the oscillating condition and slightly off-set the tuning to produce a heterodyne. S.S.B. transmissions can be received above certain signal levels by a

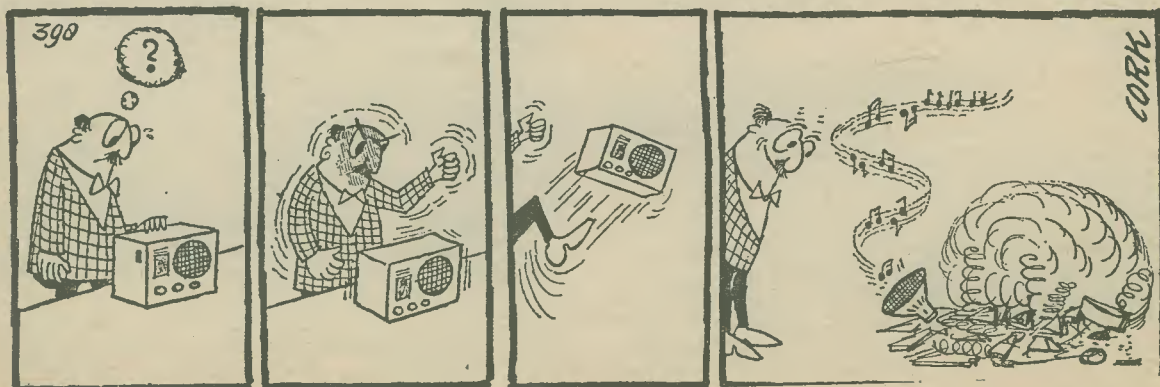similar process, the tuning being adjusted to the missing carrier frequency.



DESIGN FOR A CLASS A BATTERY AMPLIFIER

(Continued from page 351)

load can be used with considerable voltage amplification. It will be seen that, with S1 in position B, the 330k Ω and resistor R2, used by the amplifier on its own as part of the tone control arrangements, now becomes the collector load for TR1.

TR1 will not function as a common collector radio frequency amplifier unless its collector is at earth potential for radio frequencies. With VC2 fully open, therefore, only a very small proportion of the signal across the tuned circuit will find itself across the diode, such proportion as does appear being due to the minimum capacitance of VC2. But as the vanes of VC2 are engaged TR1 then starts to function correctly. L2 is a small coupling coil which allows feedback to occur between the emitter and base circuits, and VR1 is set so that VC2 functions as a reaction control. To set VR1, the vanes of VC1 and VC2 should both be fully enmeshed and VR1 next adjusted so that oscillation just starts, denoted by a hiss, or a whistle if a station is present at the low frequency end of the band. It will then be found that with the vanes of VC1 fully open oscillation will start with the vanes of VC2 about half way in. This setting will remain fairly constant for about the first half of the movement of VC1 but, as the vanes of this capacitor are further enmeshed, it will be found necessary to further increase the value of VC2 to obtain oscillation. This applies when a solid dielectric capacitor is employed for VC1. If an air-spaced component is used, the setting of VC2 will remain rather more constant throughout the tuning range.

L1 and L2 are wound, over a paper sleeve, on a ferrite rod 8in. long with a diameter of $\frac{3}{8}$ in. L1 consists of 70 turns of 32 s.w.g. enamelled wire close-wound, whilst L2 has 9 turns of the same gauge wire, close-wound and spaced by about $\frac{1}{4}$ in. from L1. The windings are phased as shown in the circuit diagram, the same ends of both connecting to TR1 base and C3 respectively.

It will be seen that bias for the base of TR1 is taken from its collector circuit. This provides a measure of d.c. feedback and is preferable to the use of a separate potentiometer network. (The BC 168C specified for TR1, together with the 40468A f.e.t., is available from Amatronix Ltd.)

It is assumed that the correct connections for the secondary winding of T1 have already been made to ensure that negative, as against positive feedback, takes place in the amplifier part of the circuit. However, even when this has been done it may be found that a different form of instability takes place when switched to radio. The instability may only be noticeable when VC2 is adjusted to the point of oscillation and, if it does occur, it indicates unwanted coupling between T1 and the ferrite rod assembly. It can be cured by reversing the connections to both the windings of T1. Both sets of connections have to be changed over because reversal of the connections to one winding only would introduce positive feedback in the amplifier.

C6 has been mentioned with respect to its function as part of the tone control network. On radio there

is no variable tone control since VC2 has become a reaction control, but C6 still plays its part by preventing a slight change in tuning or reaction as VR2 is adjusted when its slider is at or near the maximum volume position. If C6 is removed from circuit this effect can be rather annoying and is due to small internal capacitances within VR2 which are easily swamped by C6.

AUTHOR'S PROTOTYPE

The author's prototype, which has been through all the stages described in this article, and many others which were abandoned for one reason or another, now takes the form of Fig. 3. It is built into a wooden case which houses an 8in. round loudspeaker, and the 12 U2 cells. These are kept in three plastic containers, for four cells each, made by Eagle Products. An external speaker is frequently used. Results from records are extremely good, and the amplifier is fully loaded by an input of the order of 250mV, the exact sensitivity depending on the characteristics of the transistors used. Local stations give splendid results on either internal or external speaker and 20 or 30 other stations can be received at reduced volume after dark.

It has been found that during the hours of daylight a number of stations which are scarcely loud enough for normal listening will produce an amply sufficient signal for recording on tape. At the author's home in South Devon this applies particularly to Radio 3 on 194 metres, which produces a weak but interference-free signal during daylight hours.

Layout may follow the constructor's whim provided that input and output circuits are sensibly separated. It is especially important to keep T1 well away from the ferrite rod assembly, and to arrange for the axis of the coils of T1 to be at right angles to the axis of L1 and L2.

CAN ANYONE HELP?

Requests for information are inserted in this feature free of charge, subject to space being available. Users of this service undertake to acknowledge all letters, etc., received and to reimburse all reasonable expenses incurred by correspondents. Circuits, manuals, service sheets, etc., lent by readers must be returned in good condition within a reasonable period of time.

R3673.—A. Howard, 2 Castle Close, Reffley Estate, Kings Lynn, Norfolk—circuit, manual, modification details or any other information.

Radio Altimeter APN1.—R. K. Lloyd, P.O. Box 1164, Lusaka, Zambia—circuit or manual.

Communications Receiver Type G12.—B. Lawrence, 32 Bridle Path, Beddington, Croydon, CRO 4SB—circuit diagram, manual, or any other information. Loan or purchase.

CONSTANT CURRENT GENERATOR FOR OHMMETER CONVERSION

by
J. C. MAYCOCK

The constant current generator circuit described here enables resistance to be measured directly with the aid of a high impedance voltmeter. If the voltmeter has sufficient sensitivity, very low resistance readings are feasible

THERE MUST BE MANY CONSTRUCTORS WHO HAVE built themselves high input impedance voltmeters and who lack the means to measure resistance. This article describes a simple unit which can be employed with a high resistance voltmeter to enable resistance measurements to be carried out. It requires no modifications to the existing voltmeter. Also, it causes only a low current to be passed through the resistance being measured and is therefore suitable for all but the most delicate of components.

The basis of the technique consists of feeding a known current through the unknown resistor, R_x . The potential developed across R_x is then a measure of its resistance, and can be read off from the scale of a high impedance voltmeter.

The circuit of the constant current generator is shown in Fig. 1 with R_x connected across the output terminals.

CIRCUIT OPERATION

The unknown resistor R_x forms the collector load of silicon transistor TR2, this operating from a 15 volt supply in what is effectively a grounded base configuration. A large change in collector voltage produces a relatively small change in collector current, and therefore the current through R_x remains constant for a very wide variation in its value.

The collector current of TR2 is controlled by the emitter current. The latter is adjusted to give load

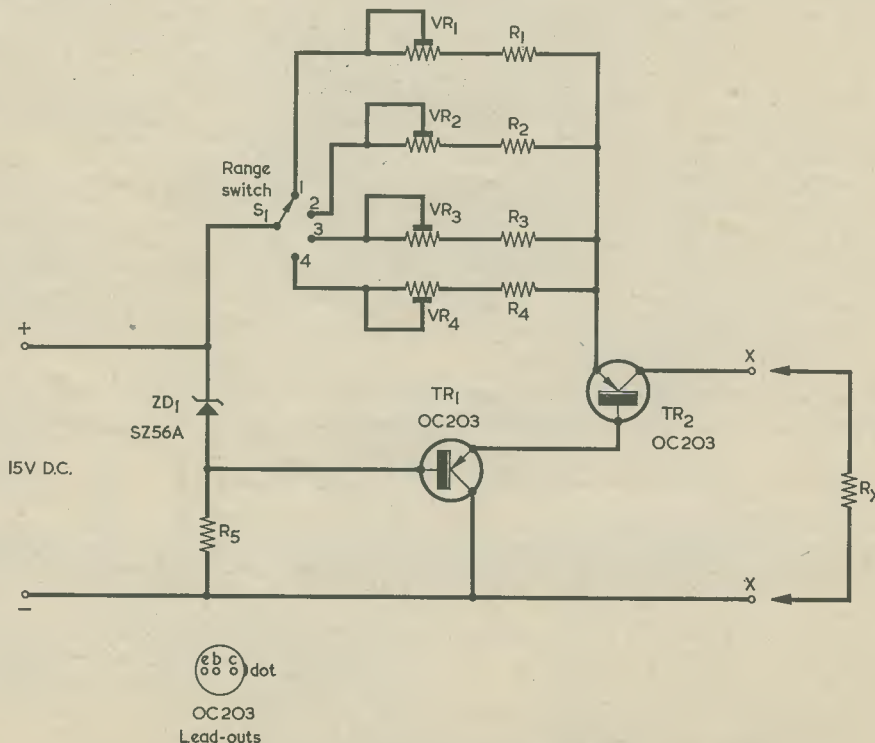


Fig. 1. Circuit of the constant current generator. R_x is the resistor whose value is to be measured

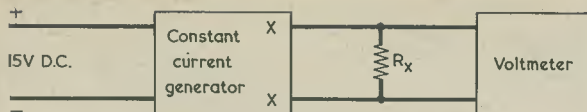


Fig. 2. Showing correct connections for the two units required

currents in R_x of 10mA, 1mA, 100 μ A and 10 μ A by means of range switch S1 and preset controls VR1, VR2, VR3 and VR4 respectively.

To make the emitter-collector current independent of fluctuations in the supply, the base voltage is stabilised by zener diode ZD1. A 5.6 volt zener diode rated at 1 watt was used. Should a stabilised power supply be available, then the zener diode may be replaced by a 560 Ω resistor. The maximum current drawn from the 15 volt supply is approximately 20mA.

The potentiometers VR1 to VR4 should all be wirewound and, sufficient to say, of good quality. Colvern 1 watt types were used in the original.

VOLTMETER

The voltmeter used with this circuit should be either a valve voltmeter or the transistor equivalent. A digital voltmeter is ideally suited and was in fact used with the original circuit.

RANGE OF THE UNIT

The voltage appearing across the output terminals under open circuit conditions is about 10 volts.

The maximum effective voltage for which the present circuit is intended is about 2 volts, since a fall-off in accuracy exists above this voltage. Range calculations may be based on this. Thus, 2 volts and 10 μ A give a maximum measurable resistance on Range 4 of 200k Ω . The accompanying Table gives details of the maximum resistance reading offered, at 2 volts, by each range. Since the resistance values are multiples of voltage readings, the value of any resistance being measured may be quickly judged from the corresponding voltmeter indication. For example, a voltage reading of 1.5 on Range 3 corresponds to a resistance in R_x of 15k Ω . The minimum useful resistance reading for each range depends upon the lowest voltage the voltmeter can reliably measure.

Should a range higher than 200k Ω be required, a further range offering 1 μ A could be added, although this has not been tried out in practice by the author. The values of the preset potentiometer and range resistor in the emitter circuit of TR2 would be 1M Ω and 3.3M Ω respectively, and the maximum resistance

TABLE

Range	Load Current	Maximum Resistance Reading (for 2 Volts across R_x)
1	10mA	200 Ω
2	1mA	2k Ω
3	100 μ A	20k Ω
4	10 μ A	200k Ω

COMPONENTS

Resistors

(All fixed values $\frac{1}{2}$ watt 5%)

R1	330 Ω high-stability
R2	3.3k Ω high-stability
R3	33k Ω high-stability
R4	330k Ω high-stability
R5	1k Ω
VR1	100 Ω wirewound potentiometer
VR2	1k Ω wirewound potentiometer
VR3	10k Ω wirewound potentiometer
VR4	100k Ω wirewound potentiometer

Semiconductors

TR1	OC203
TR2	OC203
ZD1	SZ56A (Henry's Radio, Ltd.)

Switch

S1	single pole 4-way, rotary
----	---------------------------

reading would be 2M Ω . A range switch offering a fifth position would also, of course, be required.

A 12 volt supply may be employed instead of the 15 volt supply, if desired. In this case, the values of the ranging resistors should be changed to multiples of 22, commencing with 220 Ω for R1 and ending with 220k Ω for R4. R5 should then be 820 Ω and the zener diode a 4.7 volt component (or a 470 Ω resistor if a stabilised supply is used).

CALIBRATION

Calibration is best carried out using standard resistors of known values and adjusting the potentiometers on each range until the voltage indicated is the required multiple or sub-multiple of the resistance.

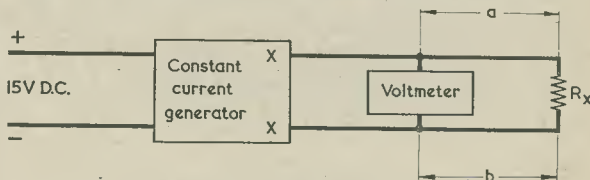


Fig. 3. Showing errors that may occur through incorrect connection of leads

TRANSISTORS

Any silicon transistors in the series OC200, OC201, OC202 and BZY11 may be used with success in the circuit, though differences in stability may be found. The current stability of the circuit is about 0.05% and thus the accuracy is similar.


USING THE UNIT

On the low ohms range trouble can be experienced with lead resistance unless the voltage sensing output and current input are both connected directly to resistor R_x , as in Fig. 2. Fig. 3 shows an incorrect method of connection which causes the resistances of the leads "a" and "b" to be added in series with R_x .

CURRENT TRENDS

● NEW BULGIN SIGNAL LAMP


The new Signal Lamp illustrated here has been designed specifically for mounting directly into a printed circuit assembly. The body is moulded in high grade black phenolic material and accepts two different lens types – either with a flat or a domed end. Both lenses are available in a choice of five transparent colours, red, amber, green, blue and water clear and five translucent colours, red, orange, green, blue and white, all of which are a push-fit to the body.

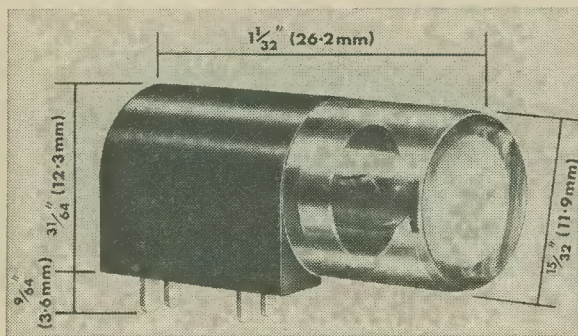

Removal of the lens provides access to the anti-vibration i.e.s. lampholder accepting BS. 98/E.5 tubular lamps 5.5mm diameter by 15mm long. Four mounting pins are employed for stability (2 per lamp contact) which are silver plated for ease of soldering and are on 0.1 x 0.3in. centres, therefore fitting in any required position on proprietary printed circuit boards of 0.1in. standard matrix, as well as specially designed boards. Their length, $\frac{9}{64}$ in., caters for most common thicknesses of board. Working rating is 30V at 0.5A maximum.

● NEW COMARK INSULATION METER

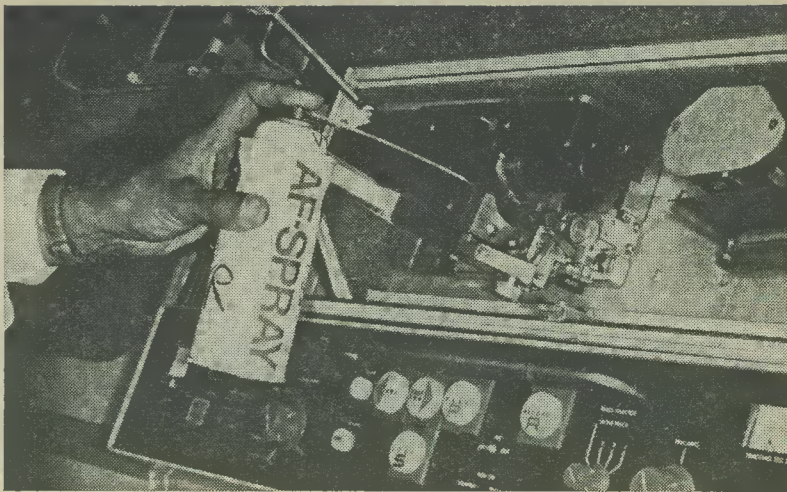The new Comark Insulation Meter Type 1905 has been allocated JS No.



AF-Spray in use at Thames Television's Teddington Studios for cleaning Ampex videotape record-playback machines

6625-99-111-2740 for general Service use. The instrument provides six test voltages from 25V to 1,000V and will measure leakage resistance between 0.1 Megohm and 10,000 Megohm to $\pm 5\%$.

The 1905 is battery powered and easily portable; test voltages are generated by a transistor converter and the output is electronically stabilised to limit the maximum current to 10 microamps. The test voltage falls proportionally and the risk of destructive breakdown is virtually eliminated; semiconductor diodes and rectifiers may be checked with safety for leakage current.

The instrument has a push-button On/Off switch for instant one hand operation, eliminating unnecessary

battery drain. The dry cells have a very long shelf life and provide a compact power source capable of giving more than 25,000 average operations. The 4.7in. scale, 10 microamp meter movement has taut band suspension.

● AF-SPRAY AIDS TV


With ITV broadcasting in colour, Thames Television viewers will obtain video-tape-recorded programmes of high quality, the degree of which is considerably assisted by AF-Spray aerosols.

At Thames Teddington studios there are two Ampex VR 1200 and three VR 2000 models having electronic editing facilities. The machines are used to record programmes on 2-inch tape for future broadcasting.

A fresh tape is placed on each machine several times a day, and this is preceded by the application of AF-Spray to remove dirt and oxide. The cleanser is applied to all components over which it passes, tension arms, idler, erase head, video heads, vacuum tape guides, control track head, audio and cue track heads, capstan and pinch roller, time counter idler and final tension arm.

The aerosols 5in. nylon extension tube is particularly useful for cleaning the control track head, which, owing to its inaccessible position, is very hard to clean by conventional means. AF-Spray aerosols also greatly simplify the cleaning of the three slots of the vacuum guide shoe which was normally an extremely time-consuming operation.

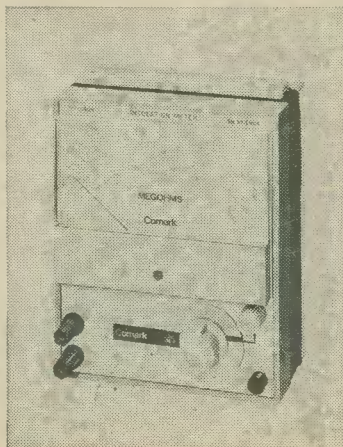
Before AF-Spray was adopted, cleansing solvent for application by rags was bought in bulk and decanted into smaller containers. Thames Television report that the large evaporation and spillage losses occurring with this method have now been totally eliminated.



UNDERSTANDING RADIO

METER SHUNTS

$$f = \frac{1}{2\pi\sqrt{LC}}$$

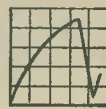

by W. G. Morley

IN LAST MONTH'S ISSUE WE EXAMINED THE MECHANISM of the pointer measuring instrument which is used far more frequently than any other type in electronic work, this being the moving-coil meter. We concluded by introducing the concept of the shunt, this being a resistor whose function is to cause the meter to indicate a higher current than that which it indicates on its own.

We shall now deal with the subject of shunts in greater detail.

SHUNT RESISTORS

In the introductory example we discussed last month, we had a 0-1mA moving-coil meter which we wished to give a full-scale deflection of 100mA, and we connected a shunt across it as shown in Fig. 1. (In this and succeeding diagrams, the arrows indicate the flow of "conventional" current, i.e. from positive to negative.) As we saw last month, we give the shunt a value which causes 99mA to flow through it when 100mA flows through the combination of shunt and meter. The remaining 1mA must then flow through the meter, with the result that it gives an indication of this value when the actual current flowing through the combination of meter and shunt resistor is 100mA. The same relationship holds true for meter scale indications lower than 1mA. If these are multiplied by 100 they will show the actual current flowing through the combination of meter and shunt.

To find the value of resistance needed in the shunt it is necessary, first of all, to know the resistance of the meter (i.e. the resistance offered at the meter terminals due to its coil and the connections to that coil). Let us say that the resistance of the meter in our example is 100Ω. We may next consider the voltage dropped across the meter when, on its own, it is indicating 1mA. From the equation associated with Ohm's Law, $E = IR$ (where E is e.m.f. in volts, I is current in amps and R is resistance in ohms), this voltage must be $\frac{1}{1000} \times 100$, or $\frac{1}{10}$ volt, and it is

indicated in Fig. 2(a). In Fig. 2(b) we add the shunt and increase the current flow to 100mA whereupon the current flowing through the meter is once more 1mA. Again, $\frac{1}{10}$ volt will be dropped across the meter

and it is obvious, by inspection, that $\frac{1}{10}$ volt must also

appear across the shunt. The current flowing in the shunt is 99mA so, from $R = \frac{E}{I}$, the shunt resistance

must be $\frac{1}{10}$ volt divided by $\frac{99}{1000}$ amp, which works out as $\frac{100}{99}$ Ω.

This simple example shows us that the shunt resistance required is exactly one ninety-ninth part of the meter resistance. It also demonstrates that there is no necessity to know the voltage dropped across the meter at full-scale deflection, since the same voltage is also dropped across the meter and shunt combined. To find the value of any shunt, all we need to know is how many times greater than the meter f.s.d. value is the current it has to pass when the meter indicates full-scale deflection. Fig. 2(c) shows a 0-1mA meter having a shunt whose function is to cause the meter to read f.s.d. when 10mA flows through the combination of shunt and meter. Obviously, the shunt has to pass 9mA, whereupon it follows that its resistance needs to be one-ninth of the resistance of the meter. If the meter resistance in Fig. 2(c) is 100Ω then the shunt resistance required is $\frac{100}{9}$ Ω. Should

the meter resistance be 75Ω, the shunt resistance required is $\frac{75}{9}$ Ω, and so on.

It is desirable to employ a common equation to cover all simple shunt resistance calculations and this may be conveniently based on the "scale multiplying factor" which results from the addition of the shunt.


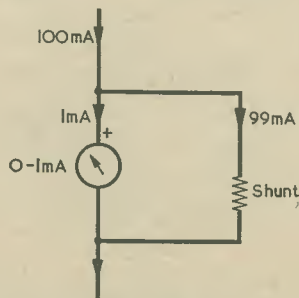


Fig. 1. Connecting a shunt across a 0-1mA meter to cause it to read 100mA f.s.d.


In the two examples we have considered the scale multiplying factors have been 100 (1mA to 100mA) and 10 (1mA to 10mA). The actual current flowing through the shunt for f.s.d. is then the current in the meter multiplied by the scale multiplying factor minus one. Thus, a scale multiplying factor of 100 means that the current in the shunt has to be 100 minus 1, or 99, times meter current, this agreeing with what we have already seen.

The general equation for calculating shunt resistance is:


$$R_s = \frac{R_m}{N-1}$$

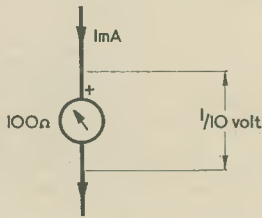


(a)

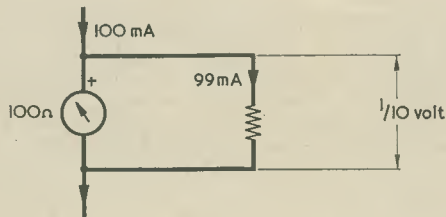

(b)

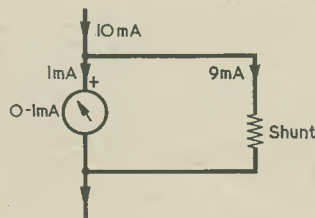

(c)

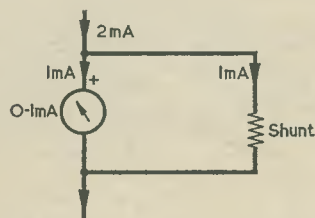

(d)

Fig. 2(a). Indicating the voltage dropped across the meter of Fig. 1 at f.s.d. when the meter has a resistance of 100Ω

(b). The same voltage appears across the shunt resistor when the overall current flow is 100mA

(c). Adding a shunt to make a 0—1mA meter read 10mA f.s.d.

(d). In this instance, the shunt causes the meter to indicate twice its normal f.s.d. value

where R_s is shunt resistance, R_m is meter resistance and N is scale multiplying factor.

The writer has introduced this equation by way of several intermediate steps because it has been his experience that beginners tend to be confused by the appearance of the "minus one" on the right hand side. It is, of course, necessary to include the "minus one" in order to allow for the current flowing in the meter. To reiterate, the equation tells us that for, say, a scale multiplying factor of 10, the shunt resistance is the meter resistance divided by 10-1, or 9. Note that there is no necessity to include in the equation the actual currents passed by the meter or the shunt as these are automatically catered for by working in terms of the "scale multiplying factor".

An interesting case arises when it is desired to have a scale multiplying factor of 2, as shown in Fig. 2(d). This will occur if we want, say, a 0-1mA meter to read 2mA f.s.d. (as is indicated in the diagram), a 0-50mA meter to read 100mA f.s.d., or any other meter to read twice its scale value. The term N in the general equation for shunt resistance now becomes 2, whereupon we have

$$R_s = \frac{R_m}{2-1}$$

giving us the result that R_s is equal to R_m . This is to be expected since, for a scale multiplying factor of 2, equal currents must flow in the meter and in the shunt.

MULTIPLE SHUNTS

A very large number of measurements in electronic work are carried out with the aid of an instrument which is usually referred to as a "testmeter" or a "multi-testmeter". This instrument employs a single basic moving-coil meter and, by means of suitable switches and/or sockets, can be set up to give an f.s.d. indication for a wide range of different currents and voltages. Testmeters of this nature also have one or more ranges capable of indicating resistance values.

So far as the current measuring function of a testmeter is concerned, it would appear that a number of different current ranges could be obtained by the simple expedient of connecting different values of shunt resistance across the single basic meter. A system of this nature is in fact used, but the circuit employed has to incorporate features which are designed to protect the basic meter against accidental overload and to reduce the risk of errors in readings on the higher current ranges.

At first sight, it would seem that the switching circuit required is that shown in Fig. 3. In this diagram, the basic meter is coupled all the time to the terminals of the testmeter, and the range selector switch simply brings into use the shunt required for the particular range selected. At one switch position there is no shunt at all. This would correspond to the lowest current range, and the readings indicated would be those given by the basic meter on its own.

In practice, the circuit of Fig. 3 represents extremely poor design approach, and should not be employed in a working testmeter. The reason for this is that it is possible for excessively high currents to pass through the basic meter due to faulty operation of the range switch. To take an example, let us assume that the testmeter is switched to a high current range and that a correspondingly heavy current is being passed through the instrument. Very nearly all of this

current should flow through the shunt selected by the switch. If, however, the switch contacts happen to become momentarily open-circuit or should momentarily present a relatively high resistance, virtually all the current will flow through the basic meter itself whereupon the latter can be seriously damaged. The possibility of a momentary open-circuit or high resistance contact is likely to occur in any switch, this being particularly true when the switch is being turned from one range position to the next. A further disadvantage is that the inevitable resistance offered by the switch contacts appears in series with the shunt. Shunts for high current ranges may have resistances considerably lower than 1Ω , and the consequent risk of inaccuracies due to even extremely low values of switch contact resistance becomes very high.

These disadvantages can be overcome in testmeter current range switching circuit design by following the principle that currents greater than the f.s.d. value of the basic meter must always flow directly through the appropriate *shunt*, and that the meter should *then* be connected to that shunt. This principle is followed in the simple circuit shown in Fig. 4(a). Here, there are three current ranges and the current to be measured flows through R_1 , R_2 and R_3 in series. The highest current range is selected by position 3 of the switch, whereupon the appropriate shunt is R_3 . On position 2 of the switch, the shunt is provided by R_2 and R_1 in series. Position 1 of the switch selects the lowest current range, the shunt being given by R_3 , R_2 and R_1 in series. It will be seen that only the meter current flows through the switch contacts, with the result that errors in meter indication due to switch contact resistance become correspondingly reduced. In no instance, also, can open-circuit or high resistance switch contacts allow excessive current to flow accidentally through the meter. Whilst Fig. 4(a) ably demonstrates the correct approach for switching shunt resistors, the circuit has the disadvantage that, due to the relatively high resistances of R_1 and, in turn, R_2 , excessively large voltages will be dropped across the chain of resistors when measuring the larger currents.

An alternative switching circuit is illustrated in Fig. 4(b), in which the two switches shown are ganged. The current to be measured, if higher than the f.s.d. value of the basic meter, passes first through S_1 and then flows through the shunt selected. The meter is then coupled by S_2 to the same shunt. The circuit meets all the requirements for correct design procedure. The current to be measured must always



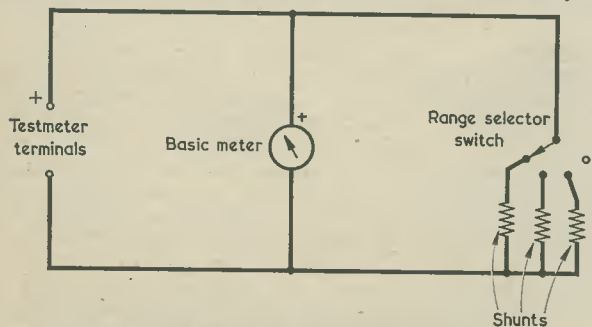


Fig. 3. This method of current range selection in a testmeter may appear attractive at first sight but in practice it represents a poor design approach and its use is not advised

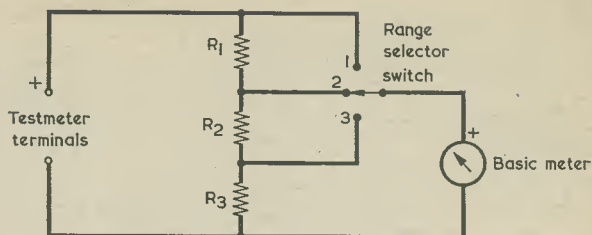

(a)

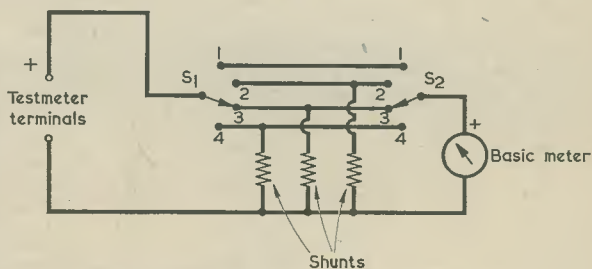

S_1, S_2 — range selector switch

(b)

Fig. 4(a). A circuit which, although not practicable for reasons explained in the text, demonstrates the preferred method of switching shunts in a testmeter

(b). A range switching circuit which is suitable for use in a testmeter. S_1 and S_2 are ganged

pass through the shunt, the meter being then connected to that shunt. Only the relatively low meter current flows through S_2 . The current being measured passes through S_1 , but the accuracy of the instrument will not be impaired if this switch should exhibit a small contact resistance. Such a contact resistance merely results in a slight increase in the voltage dropped across the terminals of the testmeter as a whole. The circuit has the slight further advantage of enabling the test terminals to be applied direct to the basic meter on the lowest current range (at switch position 1 in the diagram) with no shunt in circuit at all. The only disadvantage of the circuit is that it requires a range switch having two ganged banks of contacts.

UNIVERSAL SHUNT CIRCUIT


A current range selection circuit which embodies nearly all the advantages of that shown in Fig. 4(b), and which has the added advantage that a single-gang switch with one bank of contacts can be used, is shown in Fig. 5(a). This is known as the *universal shunt* circuit. It is shown with four switch positions in Fig. 5(a); but the principle may be readily adapted for fewer or more positions.*

The lowest current to be measured is given by the switch in position 1, whereupon the basic meter is shunted by R_1 , R_2 and R_4 in series. The next higher


* As is explained later in this article, the basic meter will have an external resistor in series with one of its terminals, whereupon the effective meter resistance presented to the universal shunt circuit is equal to the actual meter resistance plus this external resistance. For the present discussion it can be assumed that the meter resistance is that provided by the meter on its own.

current range is provided by position 2, whereupon the shunt is given by R2, R3 and R4 in series, with R1 appearing in series with the meter. The resulting circuit is shown in Fig. 5(b), and it should be noted that, so far as the shunt is concerned, the effective meter resistance is the actual meter resistance *plus* R1. The values of R2, R3 and R4 are such as to take this fact into account. On the next higher current range, selected by moving the switch to position 3, R3 and R4 provide the shunt whilst the effective meter resistance is the actual meter resistance plus R1 and R2. On the highest current range, given at switch position 4, R4 is the shunt and the effective meter resistance is the actual resistance plus R1, R2 and R3.

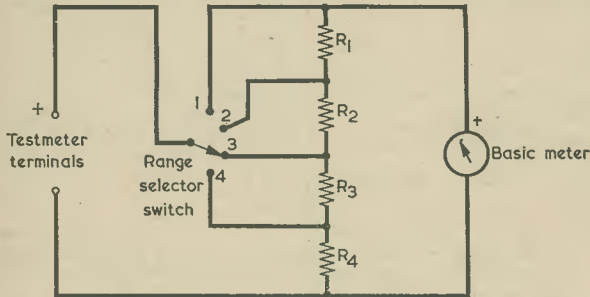
Calculations for resistor values in the universal shunt circuit are complicated by the fact that, in switching to a higher current range, further resistance



(a)

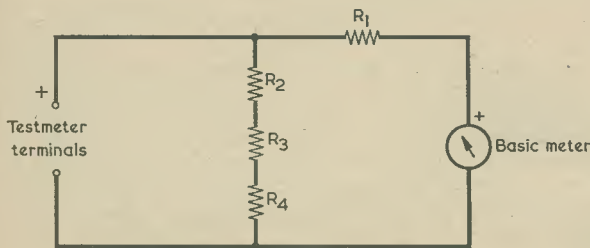

(b)

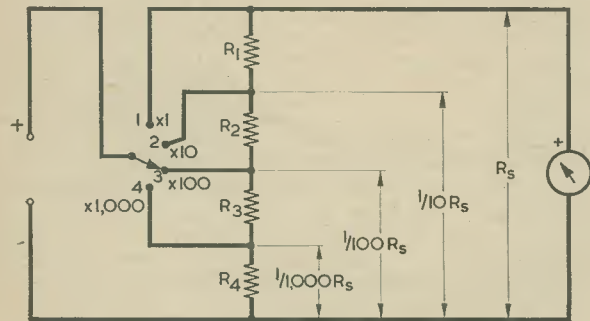

(c)

Fig. 5(a). An example of the universal shunt circuit
 (b). The circuit conditions existing when the range selector switch is in position 2
 (c). Illustrating the procedure required for finding shunt values

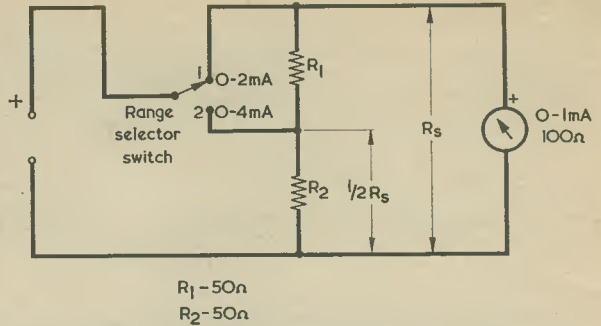


Fig. 6. A very simple universal shunt circuit

is automatically added in series with the meter. Thus, the values of resistors in the shunt and series sections for each switch position tend to be interdependent. Fortunately, calculations for universal shunt resistor values may be considerably eased by following the general procedure illustrated in Fig. 5(c), which assumes that each switch position increases the current f.s.d. reading by 10 times. It is first of all necessary to determine the lowest current range to be used and calculate the total value required for R1, R2, R3 and R4 in series. This value is then referred to as R_s . Switch position 2 multiplies the f.s.d. reading by 10. For the circuit to function correctly, the sum of R2, R3 and R4 must be equal to $\frac{1}{10} R_s$.

The process continues to R4, which needs, in this example, to be $\frac{1}{1,000} R_s$. Since R_s is known the value of R4 may then be determined. The value of R3 then becomes $\frac{1}{100} R_s$ minus the value of R4, the value of R2 becomes $\frac{1}{10} R_s$ minus R3 and R4

in series, and the value of R1 becomes R_s minus R2, R3 and R4 in series. It will be found that calculations along these lines can be applied to any number of resistors employed in a universal shunt chain.

The scale multiplying factor, as the switch moves from one range to the next, need not be 10, and any other factor can be used, as is illustrated in the simple numerical example shown in Fig. 6. This depicts a universal shunt circuit where position 2 of the switch doubles the f.s.d. reading of the meter. For simplicity it is assumed that the meter has an f.s.d. of 1mA and a resistance of 100Ω. It is required that the lowest current range, given on switch position 1, will be 0-2mA. The value of R_s is then equal to meter resistance, i.e. 100Ω. On position 2 the f.s.d. value is doubled whereupon the value of R2 needs to be one-half of R_s . This is 50Ω. Since R_s is 100Ω, R1 must also be 50Ω.

On switch position 1 in Fig. 6, therefore, we have a 1mA meter of 100Ω resistance with a shunt (R1 plus R2) of 100Ω across it. The f.s.d. reading is thus 2mA. On position 2 we have a 50Ω shunt (R2) and an effective meter resistance (the actual meter resistance plus R1) of 150Ω. The result is that three times more current must pass through R2 than through the meter and R1. If 4mA is applied, 3mA will flow through R2 and the remaining 1mA through the meter and R1, whereupon the f.s.d. of the instrument becomes 4mA, as is desired.

The universal shunt circuit is incorporated in vir-

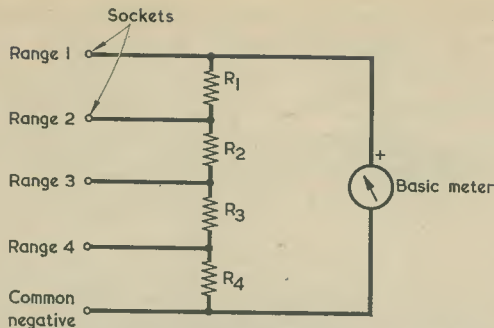


Fig. 7. The simplicity of the universal shunt circuit makes it possible to dispense with the range selector switch and use sockets instead. This is a version of Fig. 5(a) with sockets

tually all conventional commercially manufactured testmeters. Its advantages have already been referred to. It has the disadvantage that, since resistance is inserted in series with the meter when higher current ranges are selected, the voltage drop across the instrument as a whole is somewhat greater than in a circuit similar to that of Fig. 4(b). If readers care to work the figures out, they will find that the resistance offered by the circuit of Fig. 6 with the switch in position 2 is 37.5Ω whereas, if a basic meter of the same type had been made to read 4mA f.s.d. by the provision of a single shunt connected directly across its terminals, the resistance offered to the external circuit would be 25Ω . Thus, the universal shunt circuit causes rather greater power to be absorbed from the circuit into which it is connected than does that of Fig. 4(b). A slight disadvantage is that no range is available which connects directly to the meter, thereby preventing the minimum possible f.s.d. reading from being available at the testmeter terminals. In practice, this disadvantage is not of great consequence, and it is usual to make R_s such that the minimum current range selected by the switch is only some 20 to 35% greater than the actual f.s.d. rating of the basic meter.

The simplicity of the universal shunt circuit makes it possible to dispense with the range selection switch altogether. Instead, a number of sockets may be provided, as illustrated in Fig. 7. The test leads of the instrument are then simply plugged into the sockets corresponding to the particular range required.

FERRANTI LTD. ENLARGE SEMI-CONDUCTOR ASSEMBLY PLANT

The Electronics Department of Ferranti Ltd. plans to double the size of its semiconductor assembly plant at Ormskill, Barrow-in-Furness, Lancs. This expansion, which will double the size of the present 26,000 sq. ft. factory, will provide a production capacity of more than 20 million semiconductor components per annum. The present production capacity at Barrow is nine million components per annum.

The first batch of equipment for the new extension will be commissioned in July, and the enlarged plant is scheduled to be fully operational by the Autumn.

Ferranti's plans for the new extension will provide a further employment boost for the Barrow area. The present workforce of some 250 workers will be increased to over 700 employees by the end of this year.

JANUARY 1970

SWAMP RESISTOR

The shunt resistors employed in testmeters are made up with resistive materials (usually one of the resistance wire alloys) having a very low temperature coefficient of resistance. The coil of the moving-coil meter has, on the other hand, to be wound with copper wire, and copper wire has the relatively high temperature coefficient of 0.0039 per degree Centigrade. As a result, the resistance of the meter coil increases with ambient temperature and, possibly, with any heating effect due to the current which passes through it. Changes in coil resistance due to temperature variations can be surprisingly high. For instance, an increase in wire temperature of 13°C results in an increase in winding resistance of 13×0.0039 , which is equal to 0.05 , or 5% . Variations such as this can cause serious inaccuracies in testmeter readings if the basic meter is connected directly to the current shunts.

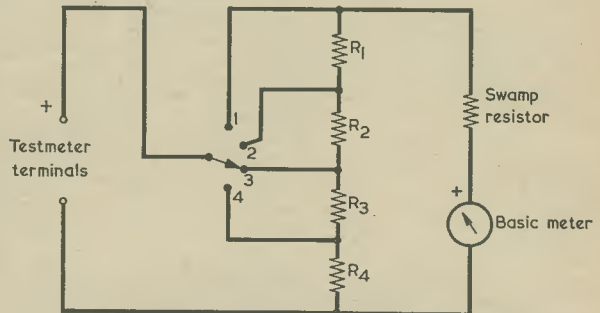


Fig. 8. To reduce the effect of errors due to variations in meter resistance with changes in coil temperature, a testmeter incorporates a swamp resistor in series with the basic meter. Here, the swamp resistor has been added to the circuit of Fig. 5(a)

This problem is overcome in a testmeter by inserting a swamp resistor in series with the basic meter, as shown in Fig. 8. The swamp resistor has a value which is some 3 to 6 times the resistance of the meter coil and employs resistance wire having a negligibly low temperature coefficient. Changes in the resistance offered by the meter and swamp resistor in series are then reduced to an acceptably low value, and shunt resistance values are calculated on the assumption

COMPONENTS

Where the above appears in this magazine, readers can rest assured that each and every item quoted is currently available from most component suppliers. Where an item is supplied from an individual source, the address is stated.

We take great care to ensure that all parts quoted in the various lists are not only obtainable by readers at the time of publication but also for some time ahead. Current catalogues are consulted, letters written and/or telephone calls made to suppliers confirming the present and future stock positions during the pre-publication processing of all articles.

From time to time however, and unknown to us, manufacturers change specifications of a particular product or, unfortunately from the constructors point of view, cease producing a particular item - this is a fact of life over which we have no control!

that the meter resistance is equal to its actual resistance plus the swamp resistance. The swamp resistor is so called because it "swamps out" the variations in the resistance of the meter coil which result from changes in temperature.

Since the only requirement of the swamp resistance is that its value should be at least several times the resistance of the meter coil, it is possible to give it a value which results in the total swamp plus meter resistance becoming a convenient round number of ohms. This can result in the shunt resistor values being expressed in similarly convenient round numbers. A further point follows from the fact that, due to variations in thickness within tolerance of the copper wire employed, it is difficult to produce meter coil windings to a precise value of resistance, this being especially true in the case of sensitive meters having a very large number of turns on their windings. It is possible to take up variations in individual meter coil resistance by pairing up each meter with a swamp resistor whose value allows the total resistance to have the desired round number of ohms. The process of setting up swamp resistance to give the requisite total resistance is carried out at the factory where the testmeter is produced.

A swamp resistor is also required with the circuit of Fig. 4(b), and it may be inserted directly in series with either terminal of the meter. Once again, shunt resistor values are calculated on the assumption that meter resistance is the actual meter resistance plus that of the swamp.

A fact which is not generally realised is that, since a testmeter incorporates a swamp resistor for its current ranges, the voltage drop across the testmeter terminals for any current reading is significantly greater than would be given by a standard moving-coil meter without a shunt which indicates the current directly. The voltage drop in a testmeter is increased further by the fact that the universal shunt circuit is almost always employed. In practice the voltage drop in a good quality commercially manufactured testmeter is not sufficiently high to cause undue disturbance of operating conditions in any normal circuit into which the testmeter is inserted, but the effect can be troublesome on occasion and its presence needs to be borne in mind.

NEXT MONTH

The writer had intended to introduce the use of the moving-coil meter for the measurement of voltage in this article, but lack of space now prevents this. In consequence, we shall turn to the question of moving-coil voltmeters in next month's issue.

GUNN EFFECT – A MULLARD PAMPHLET

Readers may care to know that an article on Gunn effect, devices and their applications, originally published in *Mullard Technical Communications*, is now available as a pamphlet.

It contains an explanation of the Gunn effect, describes the construction of the device and gives advice on the design of oscillator cavities for Gunn devices. Factors affecting stability are discussed and information is given on noise, frequency locking and pulsed operation.

Requests for the pamphlet should be made on company-headed notepaper to I.E.D./Valves Sales, Mullard Limited, Mullard House, Torrington Place, London, W.C.1.

CURRENT SCENE

TOP BAND DX

If you are a sleepy head don't bother to read this column!

If you can clamber – somewhat sleepily maybe – out of that warm, snug and comfortable bed at the unearthly hour of 0530 clock time on a Sunday morning, and be ready to enter the shack at 0600BST (0500 GMT) you will be in time for the Top Band Trans-Atlantic Tests!

The Tests held so far were on 30th November, 14th and 28th of December. Tests still to be held are on 11th January, 1st and 15th of February between 0500 and 0730 (0600 to 0830 BST or clock time).


During alternate five minute periods, call "CQ DX Test", the W's and VE's commencing at 0500, unless in QSO, keep to these periods. Eastern W/VE stations operate between 1,800 and 1,820kHz; western W/VE's between 1,975 and 2,000kHz. European stations will use 1,823 to 1,830 kHz or 1,851 to 1,861 kHz.

It is not necessary however to confine trans-Atlantic Dx contacts within the date limits of these tests. Activity "across the pond" has been noted since last October. During the last two weeks of that month, the following Dx stations had been heard busily making contacts on this side of the Atlantic – K1BPW (0525, 1,804kHz); W1BB/1 (0515, 1,803kHz) and W1EX1 (0545, 1,803kHz). The Bermudan VP9GW (0530, 1,802kHz) has also been active.

By the time these notes appear in print many more signals will be coming through from across the Atlantic with the season moving to its climax. Last year a veritable spate of Dx was apparent from the W eastern coastal region and reported in our feature **QSX**. This year it is hoped that more stations will join in the tests and attempt to span the Atlantic with a successful QSO.

For short wave listeners the tests are a trial of Dx-capability both of the listener and the station equipment. Reception of a W on Top Band represents quite a feat of Dx – much more so than some of the transmissions logged on the 14Mhz band.

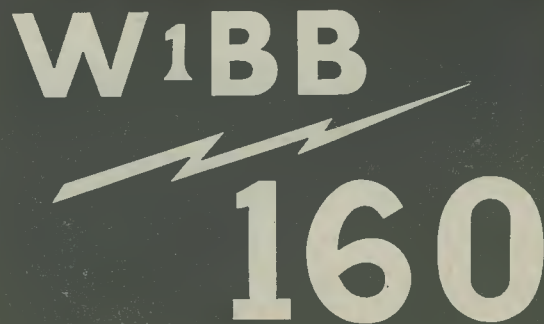So, if you can make it for opening time – of the tests we hasten to add – why not join in the fun and games?



QSL card from W1BB/1 received for a period reception report sent last year. Of six such reports sent, each produced a reply in the form of a card, three had accompanying appreciative letters and one a bulletin of Top Band activity and news

This month we find Smithy the Serviceman, aided as always by his able assistant Dick, starting the New Year in a Workshop which contains no equipment for repair whatsoever! But Smithy is not one to waste time, and he takes advantage of the situation to discuss with Dick the latest hints received from readers

"HAPPY NEW YEAR, SMITHY!"
 "And the same," replied Smithy affably, "to you my boy."

Dick glanced warily at the Workshop clock, the hands of which indicated that normal starting time had occurred at least ninety minutes earlier.

"Sorry I'm late," he offered.

"Not to worry, Dick, I've only just got in myself," admitted Smithy. "As I told you before we packed up last night, there was no need for you to come in early today."

The pair looked at the 'For Repair' racks. They were completely bare.

"Thank goodness," commented Dick, "that there are no sets to be fixed. All I want to do today is to take things nice and easy."

He stretched himself luxuriantly then removed his raincoat and hung it up on the hook behind the door.

READERS' HINTS

"Did you," asked Smithy, "have a good New Year's Eve celebration last night?"

"I had quite a pleasant little do," replied Dick. "Rather quiet, but otherwise very nice."

"You didn't," queried Smithy slyly, "get another false beard stuck on you, did you?"

Dick winced, then hurried quickly over towards the motley array of utensils ranged alongside the Workshop sink.

"I think," he remarked, hastily changing the subject, "that it would be an excellent idea if I put the kettle on for tea."

"A very sensible suggestion," responded Smithy warmly. "Also, seeing that we've got a nice quiet New Year's Day in front of us, how would it be if we had another session with readers' hints?"

"That would be fine," said Dick eagerly, as he returned to his stool.

"Good," remarked Smithy, opening a drawer in his bench and extracting a sheaf of letters. "Well, I won't waste any more time. We'll have a look at the first one right away."

The Serviceman opened one of the letters and surveyed its contents closely.

"Now here's a jolly good hint," he continued, "and it's just what we need to start the ball rolling. Our correspondent states that he recently had to make up a housing for a small electronic gadget he'd

In your work-shop

built. When he considered the situation, however, he found that wood was rather too cumbersome for the housing, whilst Perspex didn't quite seem to fit the bill. And so he used copper-clad laminate instead."

"Copper-clad laminate?"

"That's right. In other words, ordinary plain printed circuit board before the circuit pattern is etched on it. This material proved ideal for the purpose, and all that had to be done was to cut the front, sides, top and bottom to size, and secure them together with the copper on the inside to form a small cabinet." (Fig. 1).

"How did he join the bits together?"

Smithy consulted the letter once more.

"He soldered internally at the corners," he replied. "Our correspondent says it's best to spot solder the sections together, rather than to run the solder all along each corner. The case which results is attractive

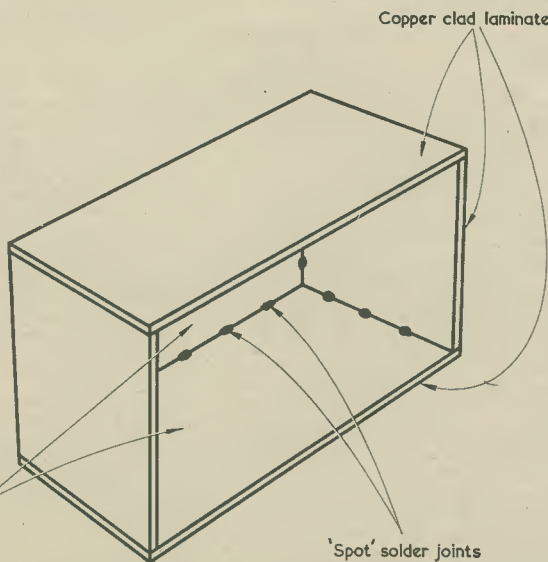


Fig. 1. An unusual but effective method of assembling a small equipment case



in appearance. In addition, the copper surface on the inside provides screening. Another advantage is that small components can be mounted to the inside walls by soldering them direct to the copper surface."

"That," remarked Dick, "is what I call a proper copper-bottomed hint!"

"It's certainly a novel idea," chuckled Smithy, as he picked up another letter. "Now, this letter describes quite a simple sort of tip, but it's still one which can save a lot of time and trouble. As you know, the process of soldering components to printed circuit boards and to Veroboard may seem easy in principle, but in practice you can sometimes run into the odd minor difficulty."

"That's true enough," interrupted

"I'll say it is," said Dick. "Dash it all, why on earth didn't I think of that myself?"

"The solutions to most problems," pronounced Smithy, "are usually obvious once you've been told what they are. A final point which is made in this letter, incidentally, is that the idea of using rubber bands to hold components in place can be just as useful when you're working with really large boards as it is with small ones."

Smithy picked a further letter from the pile on his bench.

"Here," he announced after a moment's perusal, "is a hint which enables you to fit an extension volume control to a TV set. I'd better add quickly that the scheme doesn't apply to all TV receivers and that, since it involves a direct connection to the chassis of the

Dutifully Dick picked up his stool, carried it over to Smithy's bench and settled himself on it comfortably. He then looked at the circuit accompanying the letter Smithy was holding. (Fig. 2).

"As you can see," remarked Smithy, "the idea is not at all complicated. At the extension control point you have an on-off switch in series with a 250k Ω log pot, and these are coupled to the set by twin lighting flex. The volume control in the receiver is set up to provide adequate volume level for quiet speech when the switch at the extension point is open. If the sound programme changes over to loud music the remote switch is then closed, whereupon the extension volume control can be adjusted to allow the music to be reproduced at a comfortable level. In most cases, after the extension volume control has been initially adjusted to the desired level, it will only be necessary to operate the switch. This is just the thing, I might add, to have positioned on the arm of your favourite armchair."

"Won't there be trouble," asked Dick, "due to hum pick-up on the leads to the extension point?"

"There wasn't any trouble on this score in our correspondent's set-up," replied Smithy. "And he simply uses about fourteen feet of ordinary unscreened twin lighting flex. However, you would very definitely get trouble with hum if the extension volume control circuit were introduced any earlier in the receiver a.f. amplifier stages than at the grid of the output valve. Even when the extension circuit appears in the output grid circuit it will still be necessary to connect the TV set to the mains such that its chassis is common with the neutral and not the live side. It would also be preferable to keep the wire to the extension volume control spaced well away from any other mains wiring in the room. Actually the circuit is a wee bit experimental in this respect because, in houses which are wired up with p.v.c. cable, it may be impossible to completely eradicate hum pick-up on the extension lead. Apart from the question of picking up hum, it is extremely important to pay attention to the safety factor. The extension volume control components and wiring are all at mains potential, and the remote potentiometer and switch must be completely enclosed in an insulated case which ensures that none of the connection points can be touched. Also, the wire to the remote control must have insulation suitable for mains voltages. If the remote volume control connects to the receiver by way of a socket fitted to the back of its cabinet the socket must offer insulation suitable for mains voltage. It could, in practice, be a socket intended for mains use, and a suitable

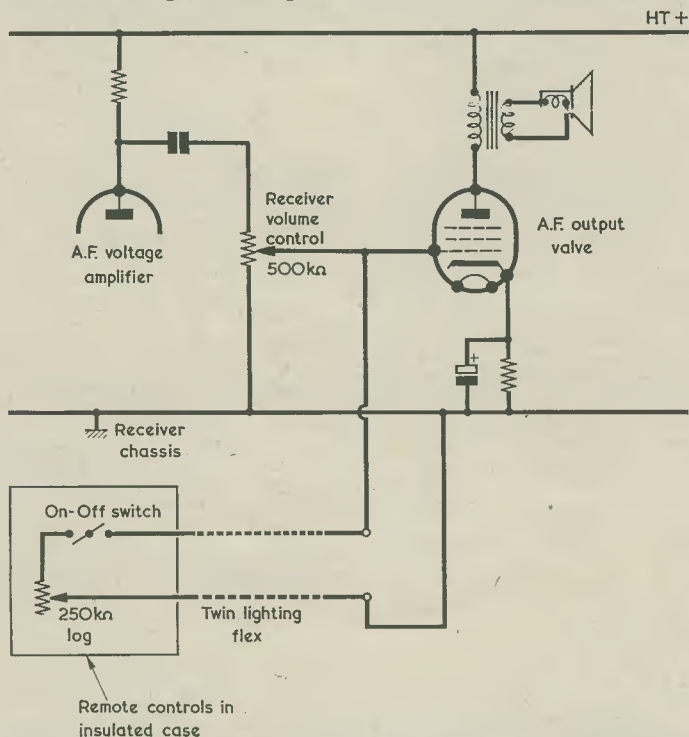


Fig. 2. A simple extension volume control for use with television receivers whose existing volume control appears in the grid circuit of the a.f. output valve. All insulation in the extension circuit must be adequate for mains voltage

Dick. "What happens every now and again is that, when you turn the board over to solder the lead-outs to the copper, one or more of the components drops out or moves out of its proper position."

"Exactly," agreed Smithy. "Well, the answer to this problem is to get in a stock of rubber bands of various sizes and just slip one or two of these over the board to keep the more insecure components in place whilst you're soldering them into circuit. Simple, isn't it?"

set, all the circuit points in the extension wiring require insulation which is fully suitable for mains voltages."

"What sort of TV set," asked Dick, "can the volume control be used with?"

"It can be employed," replied Smithy, "with sets in which the slider of the internal volume control couples to the control grid of the a.f. output valve. Bring your stool over here and have a look at the circuit."

type would be one of those small 2-amp 2-way types."

CORRUGATED STRIP

Smithy turned back to his bench and picked up the next letter. As he removed the contents from its envelope, a length of corrugated strip slipped out and fell to the floor. Dick picked this up and examined it with interest. Fig. 3(a).

"Hello," he remarked. "What's this, then?"

"It's original function," said Smithy, "is to provide a means of positioning drawer partitions. But the use to which our correspondent puts it is rather different. He fits it inside equipment housings to enable printed circuit boards or Veroboard to be supported at the ends along the slots between the corrugations."

Smithy pulled his notepad towards him, and sketched out the application. (Fig. 3(b)).

"Gosh," said Dick, impressed.

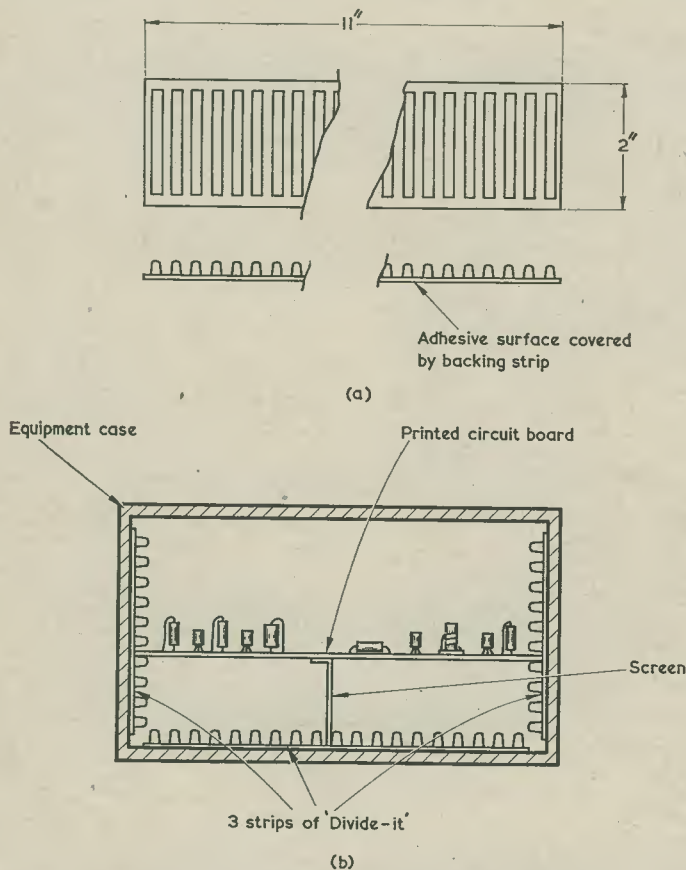


Fig. 3(a). The appearance of 'Divide-It' strip
(b). Employing three strips of 'Divide-It' to position a printed circuit board and a screen in an instrument case

"It's a strip of special material," replied Smithy, as he studied the letter, "which is known as 'Divide-It', and which you can buy for a few shillings at most Do-It-Yourself stores. One side is flat, and has an adhesive surface which is revealed after pulling off a backing strip. The other side is deeply corrugated and, as you can see if you dig at it with your thumb nail, the corrugations are quite strong physically. The material of which the strip is made offers good insulation along its surface."

"What's the strip intended for?"

"That's a neat idea."

"It is, isn't it?" commented Smithy. "Incidentally, I must say that it's rather surprising to find how many uses there are in electronic work for simple domestic gadgets such as this."

At that instant, the Workshop kettle gave voice to an ear-splitting whistle, and further activity ceased whilst Dick set about the all-important task of preparing the tea. Eventually, he placed Smithy's disgraceful tin mug, brim-full with the precious beverage, alongside the Serviceman.

"Ah," said that gentleman as, after

Your Local Supplier

LONDON

Established 1910

H. L. SMITH & CO. LTD.

Comprehensive stocks of components by all leading makers.

287-9 EDGWARE ROAD
LONDON W.2

Tel: 01-723 5891

THE MODERN BOOK CO.

Largest selection of English & American radio and technical books in the country.

19-21 PRAED STREET,
LONDON, W.2

Tel: PADDington 4185/2926

ST. HELEN'S RADIO

Hi-Fi Equipment
Tape Recorders
Radio Receivers
Television

SPECIALISTS IN RADIO & ELECTRONIC TEXTBOOKS

ST. HELEN'S GARDENS
LONDON W.10

Tel: 01-969 3657

HAMPSHIRE

BOURNEMOUTH

LARGEST HI-FI AND RADIO COMPONENT STORE IN THE SOUTH

FORRESTERS NATIONAL RADIO SUPPLIES LTD.

70-72 Holdenhurst Road
Bournemouth
Telephone 25232

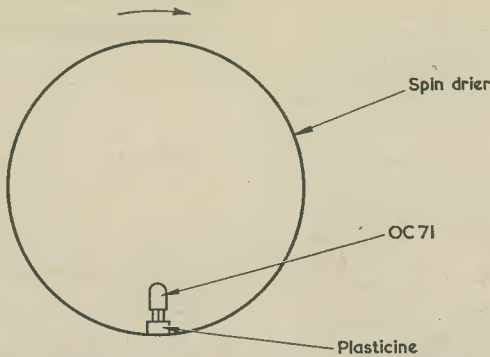


Fig. 4. A suggested method of displacing the opaque filling in a glass-cased OC71. The transistor can then function as a phototransistor

judicious blowing over the surface of the mug, he drank deeply of its contents, "that's the stuff to give the troops!"

Smithy noisily smacked his lips in appreciation. Despite the many years he had known the Serviceman, Dick had still retained his sense of wonder at the vast quantities of tea which Smithy was capable of absorbing.

"I've never," he remarked conversationally, "known *anyone* who drinks as much tea as you do."

Smithy quaffed even more mightily at his mug, then placed it back with a clatter on his bench.

"There's nothing like it," he responded cheerfully. "In fact, I rely on a really good intake of tea each day to keep my kidneys fully flushed out!"

Dick shuddered.

"There are times," he complained, "when you're really *horrible*, Smithy. Shall we carry on to the next letter?"

"Half a jiff," responded Smithy, taking a further gargantuan draught from his mug. "Let's get this little lot filled up again first."

Disdainfully, Dick picked up Smithy's empty mug and carried it over to the battered Workshop teapot. He returned with the mug, charged once more with the fluid so vital for the smooth operation of Smithy's renal functions, and placed it carefully on the Serviceman's bench. Smithy snatched it up greedily and again imbibed deeply.

"Ye gods," snorted Dick in disgust. "You're nothing but a tea-junkie, that's all you are. I bet you've got a dirty great hypodermic syringe full of the stuff back home, kept handy for the times when you're *really* in need of a fix."

"Nonsense," replied Smithy indignantly. "And if you must know, it so happens that I acquired my taste for tea during those perilous war years when I was defending this country, so that the future generation - including *you*, mate - could be brought up in a state of peace and tranquility."

"You defended this country?" queried Dick incredulously. "From what they tell me, all you ever did was to rise to the rank of acting unpaid lance-corporal in the Pioneer Corps."

Smithy scowled at his assistant. "We ex-Service types," he remarked loftily, "don't talk about our wartime careers."

"Much."

"Let me tell you," growled Smithy furiously, "that I did my fair turn of service with all the rest. Brothers-in-arms, that's what we were."

Dick turned and addressed the empty Workshop.

"We shall next," he announced derisively, "have a vocal rendition of 'Comrades' with an accompaniment on the spoons!"

It was obvious that this last remark on Dick's part was the cause of deep offence to the Serviceman.

"I have no wish," he commented icily, "to pursue this subject any further. I shall, instead, turn to the next letter."

"As you wish," said Dick obligingly.

Smithy gazed suspiciously at his assistant, but that worthy's face carried no expression other than that of interest in the next hint to be discussed.

"Hmm," grunted Smithy, turning back and foraging amongst the

letters on his bench. "Well now, let's see what we've got here."

Smithy selected a letter and read it with what was patently a continually increasing interest.

"This one," he chuckled eventually, "is a real dilly! Tell me, Dick, do you remember the old business of using OC71's as phototransistors?"

Clearly, the contents of this last letter had caused Smithy to dismiss from his mind, at least temporarily, the displeasure which had followed Dick's ribald observations on his wartime activities.

"Using OC71's as phototransistors?" repeated Dick. "Why, certainly I do. The early OC71's had glass cases covered with opaque paint to keep the light out. The thing to do was to scrape the paint away, whereupon you had a first-class phototransistor!"

"You've got it," said Smithy. "In fact, I've converted quite a few of those old OC71's in that way myself."

"After the early period, though," cut in Dick, "the design of the OC71 was changed. It still had the opaque paint on the outside of the glass housing but, in addition, the filling inside was made opaque, too."

"That's right," confirmed Smithy. "The result was that, even if you *did* scrape off the paint, you still couldn't use the OC71 as a phototransistor. Eventually, the OC71 changed over to a metal case, but there must still be plenty of glass ones with the opaque filling knocking around."

"All this," remarked Dick, "sounds intriguing. Go on, Smithy."

Smithy returned to the letter.

"What our correspondent has succeeded in doing," he resumed, "has been to shift the opaque filling inside a glass OC71 away from the internal transistor junction by taking advantage of centrifugal force! The scheme consists of pushing the transistor leads into a half-inch cube of Plasticine, and of then fixing the Plasticine to the inside wall of a washing machine spin drier (Fig. 4). He found that, after some two to three minutes spinning around in the drier, the opaque filling of the OC71 was all forced to the bottom

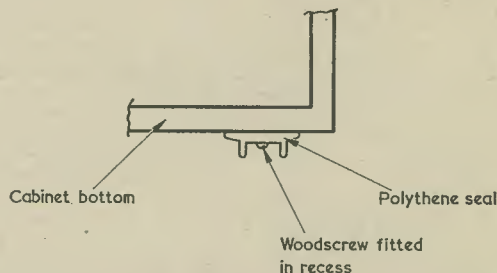


Fig. 5. Using the polythene seal from a flagon cap as a non-scratch cabinet foot

of the transistor, leaving the junction free and clear. The OC71 then functioned as a perfectly good phototransistor."

CABINET FEET

"That idea," grinned Dick, "is very definitely one for the book!"


"It certainly represents a jolly crafty approach," replied Smythy, as he took up a further letter.

There was silence as the Serviceman read its contents.


"Here's another simple one," he announced, after a moment. "Our correspondent advises that the polythene seals inside the caps of flagons should not be thrown away, as they make perfect improvised non-scratch feet for small cabinets.

Smythy detached a sheet bearing the diagrams from the remainder of the letter and laid it down on his bench (Figs. 6(a) and (b)).

"The idea behind this hint," he went on, "is to provide temporary screening for a wire or cable if it is suspected of picking up or radiating hum or interference, or of causing instability whilst in the un-screened condition. What you do is to fit a sheath of aluminium foil or aluminium paper around the wire, and it is possible to apply this temporary screening over quite long lengths. Aluminium coated paper is to be preferred because it is tougher, but aluminium kitchen foil is nearly as good and is more readily obtainable since most grocers sell it. It's available in widths of

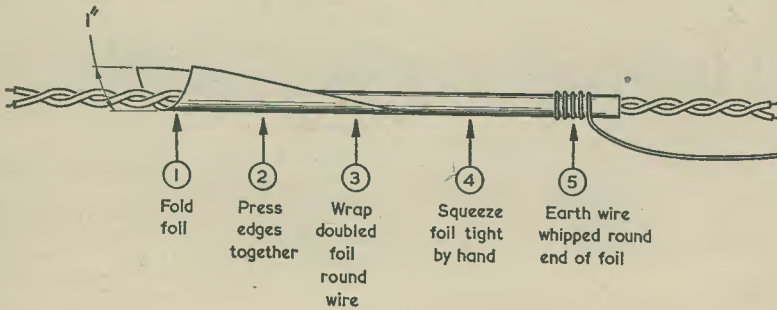

(a)

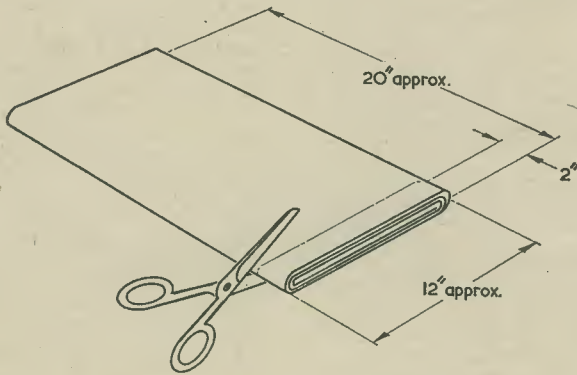

(b)

Fig. 6(a). Successive steps in wrapping a 2 inch strip of aluminium foil or aluminium coated paper around a wire to provide temporary screening

(b). How the 2 inch strip is obtained

There's a sketch in the letter too, and it shows one of these seals being used in this manner."

Smythy showed Dick the sketch (Fig. 5) then proceeded to the following letter.

"This is quite a long hint," he remarked. "Also, there are several diagrams which have to be looked at if you're going to understand the general scheme of things."

about 10 or 20 inches, the 20 inch width being better because it works out cheaper."

"How do you apply the foil to the cable?"

"You first of all cut it," replied Smythy, "so that you have a long strip two inches wide. You then lay the two inch strip along the cable to be screened and cut it to the length required, allowing your-

Your Local Supplier

KENT

EMSAG BASIC ANTENNA SYSTEMS

CN1 Nuvistor 2 metre converter. IF 28MHz. Absolutely complete with separate mains power supply, £11.10.0. Converter only, £8.10.0. P&P 4/6.

GD1 A G5RV type multi-band dipole. 102 ft. top, 100 ft. feeder. Complete and ready to go! 68/-.

GV1 General purpose vertical, usefull range 1.8MHz to 28MHz. Adjustable 7 ft. to 23 ft. 92/-.

TU2 Receiver antenna tuning unit. Amateur and SW broadcast bands 1.5 to 30 MHz. 90/-.

Send SAE for details. Open weekends. Carriage extra.

G31AR

**ELECTRONIC & MECHANICAL
SUB-ASSEMBLY CO. LTD.**
Highfield House, West Kingsdown, Kent.
Tel: West Kingsdown 2344.

SURREY

Portable Transistor Amplifier plus Dynamic Microphone

A self-contained fully portable mini p.a. system. Many uses — ideal for Parties, or as a Baby Alarm, Intercom Telephone or Record Player, Amplifier, etc. Attractive rexine covered cabinet, size 12 x 9 x 4in., with powerful 7 x 4in. speaker and four transistor one watt power amplifier plus dynamic microphone. Uses PP9 battery. Brand new in Makers' carton with full makers' guarantee. World famous make with full makers' guarantee. Only 90/- Post Full List 1/-



RADIO COMPONENT SPECIALISTS
337 Whitehorse Road, West Croydon,
Surrey. Phone 01-684-1665

SUSSEX

E. JEFFRIES

For your new television set,
tape recorder, transistor radio,
and hi-fi equipment.

PHILIPS, ULTRA, INVICTA,
DANSETTE, MASTERADIO, PERDIO,
MARCONI, PHILCO, FIDELITY.

6A Albert Parade,
Victoria Drive,
EASTBOURNE SUSSEX

EIRE

PEATS for PARTS

**ELECTRONIC COMPONENTS
RADIO & TELEVISION**

For the convenience of IRISH
enthusiasts we supply:

The Radio Constructor,
Data Books and
Panel-Signs Transfers

Also a postal service

Wm. B. PEAT & Co. Ltd.
28 PARNELL STREET
DUBLIN 1

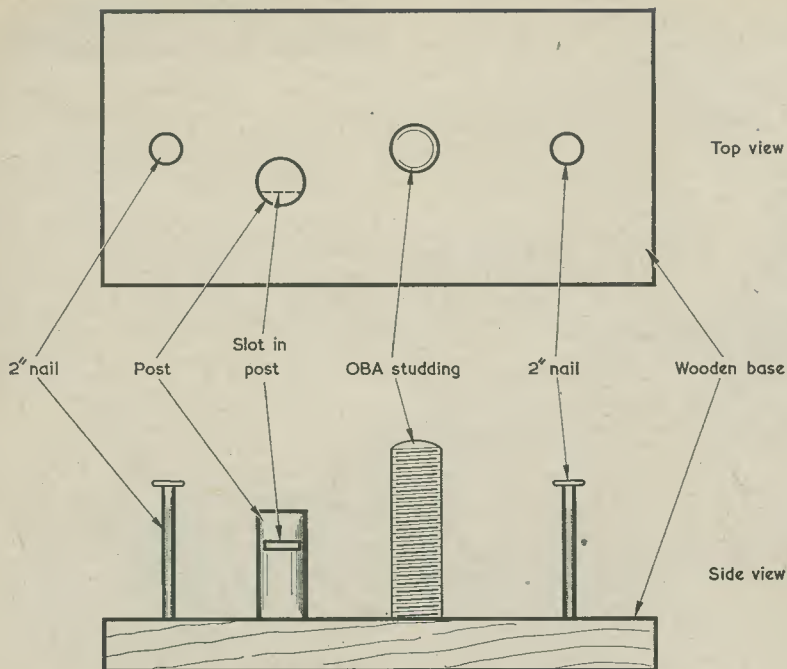


Fig. 7. The construction of a simple coil winding jig

self a little extra just to be on the safe side. The strip is then folded in two along its length and the cable is either placed in the fold, or the fold placed over the cable, according to which is more convenient. You then wrap the foil around the cable, holding it in place at one end by wrapping some thin bare tinned copper wire around it for several turns. The other end is similarly held in place with the aid of thin bare copper wire. After a little practice it is possible to make quite a neat job along the whole length of the wire and, despite the temporary nature of the job, the screening which results can be looked upon as being of a semi-permanent nature. Of course, the main intention behind the scheme is the provision of temporary screening in order that causes of pick-up or radiation may be isolated. After this, the temporarily screened wire may then be replaced by proper screened cable as necessary.

"How," asked Dick, "do you cut out the two inch wide strip?"

"You start," replied Smithy, "by unrolling the paper or foil and then folding it up in the same way as they fold lengths of cloth in the draper's. The first fold is made after one foot, and then you simply continue to wrap the succeeding foil or paper around the initial one foot length. The end result is a flat pack measuring roughly 20 inches by slightly in excess of 12 inches. You obtain a two inch strip by cutting across the pack two inches in

from the end. Curiously enough, blunt scissors are to be preferred for this operation because very sharp scissors cause the cut edges to stick together, whereupon the two inch strip is liable to tear when it's unfolded."

"That's certainly an original idea," commented Dick. "How much wire can you cover with one roll of the paper or foil?"

"A roll of 20 inch foil," said Smithy, consulting the letter again, "should be sufficient to screen rather more than 100 feet of wire."

"Blimey," said Dick. "A roll of the foil should last for ages, then. I'll have to have a dig round our kitchen when nobody's looking and see if I can find any!"

But Smithy was already deeply engrossed in the next letter.

"There are two hints here," he announced, "and they both have to do with coil winding. The first describes a coil winding jig for single-layer coils. Here's the diagram for it."

Smithy showed Dick the sketch in the letter. (Fig. 7).

"As you can see," he continued, "all the bits and pieces are mounted on a block of wood. There are two two-inch nails, a piece of OBA studding, and an upright post which can be made of any convenient material and which has a horizontal slot in its surface. Many coil formers of the type intended to take threaded iron dust cores can be screwed onto OBA studding, and the jig is specifically intended for

formers of this nature. You first of all screw the former onto the studding so that the lower starting point of the winding is level with the slot in the post. You then anchor the end of the coil wire by wrapping it several times round the left hand nail, after which you lay it in the slot and pass it round the former. You next wind the coil on the former, making a close-wound or spaced winding as desired. When all the turns have been put on, the wire is taken over to the right hand nail and anchored there by wrapping it round several times. You now have the coil wound on the former in its correct position, and with the wire under slight tension. The final process is to dope the coil. When the dope is dry you have a nice neat coil which is all ready to be connected up."

"That's a jolly useful gadget," said Dick thoughtfully. "It would be just the job for making up 10.7MHz i.f. transformers and things like that, where you use those black Aladdin-type formers with the square bases."

Smithy cast a mildly surprised glance at his assistant.

"That's a very perceptive remark," he commented, "because 10.7MHz transformers are one of the main classes of winding which our correspondent uses the jig for."

"What's the other hint in the letter?"

"It's also to do with coil winding," replied Smithy. "And again there are some diagrams to show you. (Figs. 8(a) and (b)). This second idea is designed to assist in the winding of close-wound coils on plain formers. Before winding the coil, a doubled loop of fine string is placed on the former. The wire at the start of the coil is passed through the loop at one end, after which the coil is wound on top of the fine string. The wire at the finish of the coil is then passed through the other loop of the string. The two free ends of the string are next carefully pulled tight, whereupon the wires at both the start and finish of the coil are held securely under the two loops of string. The coil is then doped and the excess lengths of string cut off."

HEALING THE RIFT

With a gesture of finality, Smithy returned the last letter to the surface of his bench.

"And that," he remarked, "is the end of this present session with readers' hints."

"We certainly had a good selection this time," remarked Dick.

"They were, as always, excellent," agreed Smithy. "I always find that going through these hints represents a very pleasant task."

He picked up his mug and drained it of its contents.

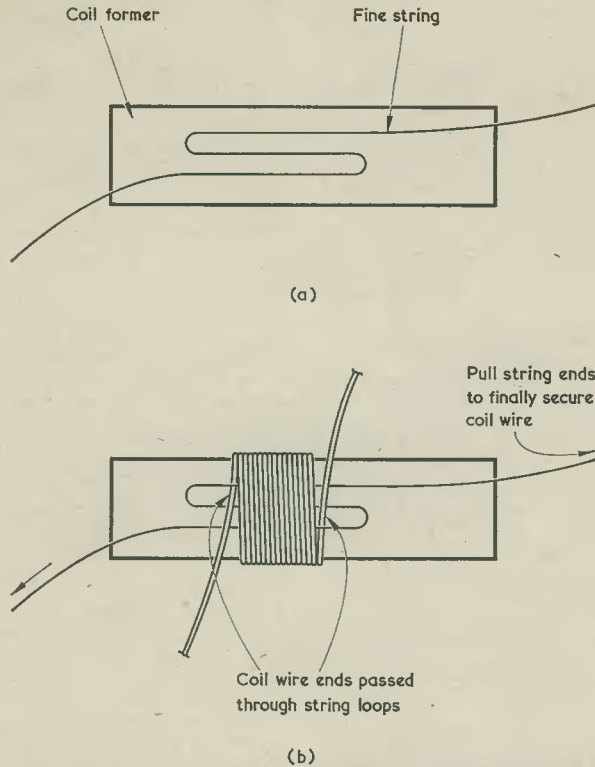


Fig. 8. How to secure a close-wound coil on a plain former. In (a) a double loop of fine string is laid on the surface of the former. The coil is then wound over the string (b), after which the string ends are pulled tight to secure the coil wires

"Would you," asked Dick helpfully, "like some more tea?"

Smithy suddenly recalled his previous altercation with his assistant.

"Not," he remarked irritably, "if you're going to make silly comments about my habits and, in particular, about what I did during the war."

"I'm sorry, Smithy," said Dick contritely. "Actually, I was indulging in a little bit of leg-pulling just now. After all, it's only fair that I should do so. You take the mickey out of me quite often, you know."

"Do I?" responded Smithy, mollified. "Oh, very well then! I must say that a spot of tea wouldn't be at all a bad idea. All this talking has made me thirsty again."

Whilst Dick busied himself with the preparation of a further mug of tea, Smithy carefully returned the sheaf of letters to the drawer under his bench. Dick came back and placed the third mug of tea for that morning on Smithy's bench.

"An excellent brew," remarked the Serviceman, sipping appreciatively. "I must commend you, Dick, on your ability to make really good tea."

Dick beamed.

"Going back," he commented, "to our earlier conversation, I suppose

we younger generation can't really appreciate what did go on during the war."

"Probably not," replied Smithy. "In any case there's one point on which I must definitely correct you. My eventual rank during the war was acting unpaid corporal."

"Was it really?" said Dick, assuming the expression of the suitably impressed. "Gosh, that was pretty high up."

"I had to fight for that rank," said Smithy darkly.

"I bet you did," said Dick.

"If this," continued Dick happily, "is a sample of what the New Year is going to be like, I reckon that I'm really going to enjoy living in 1970!"

EDITOR'S NOTE

The hints published in this episode of 'In Your Workshop' were submitted, in the order in which they appear, by S. Webb, G. M. Watson, A. Luty, J. P. Carlile, D. Playle, D. A. Bishop, T. E. Millsom and J. Rankin. Further hints for this feature are welcomed, and payment is made for all that are published.

Stella Nine Range Cases

Manufactured in Black, Grey, Lagoon or Blue Stelvetite and finished in Plastic-coated Steel, Morocco Finish with Aluminium end plates. Rubber feet are attached and there is a removable back plate. There is also a removable front panel in 18 s.w.g. Alloy.

Now all Aluminium surfaces are coated with a stripable plastic for protection during manufacture and transit. All edges are polished.

LIST OF PRICES AND SIZES which are made to fit Standard Alloy Chassis

Width	Depth	4" Height		6" Height		7 1/2" Height	
		£ s. d.	£ s. d.	£ s. d.	£ s. d.		
6 1/2"	3 7/8"	12 6	15 0	18 0			
6 1/2"	4 3/8"	13 6	18 0	1 0 0			
8 1/2"	3 3/8"	15 0	1 0 0	1 1 0			
8 1/2"	6 3/8"	1 1 0	1 6 6	1 11 3			
10 1/2"	7 3/8"	1 8 6	1 15 6	1 18 9			
12 1/2"	3 3/8"	1 1 0	1 6 6	1 11 0			
12 1/2"	5 3/8"	1 8 0	1 14 0	1 17 0			
12 1/2"	8 3/8"	1 16 0	2 3 0	2 7 3			
14 1/2"	3 3/8"	1 5 0	1 11 6	1 14 0			
14 1/2"	9 3/8"	2 3 0	2 15 9	2 18 6			
16 1/2"	6 3/8"	1 18 6	2 6 3	2 11 6			
16 1/2"	10 3/8"	2 10 0	3 5 0	3 11 9			

Cases—Post 4s. 6d. per Order.
Discounts available on quantities.

CHASSIS in Aluminium, Standard Sizes, with Gasket Plates

Sizes to fit Cases All 2 1/2" Walls			
s. d.	s. d.	s. d.	
6" x 3"	5 6	10" x 7" 8 6	14" x 3" 7 3
6" x 4"	5 9	12" x 3" 6 9	14" x 9" 14 6
8" x 3"	6 6	12" x 5" 7 6	16" x 6" 10 9
8" x 6"	7 9	12" x 8" 10 9	16" x 10" 16 0

Chassis—Post 3s. 0d. per Order.
Discounts available on quantities.

E. R. NICHOLLS

MANUFACTURER OF ELECTRONIC INSTRUMENT CASES

(DEPT. R.C.) 46 LOWFIELD ROAD
STOCKPORT - CHESHIRE

Tel: 061-480 2179

NEW VHF KIT

Receives Television Sound, Ambulances, Aircraft, Radio 2, 3 and 4 on VHF etc.

This novel little set will give you endless hours of pleasure and can be built in one evening. The Kit comes with easy to follow instructions and circuit. Powered by 9v Battery. Complete with built-in Jack Plug Socket for use with Earphones or Amplifier.

ONLY 57/-, P & P FREE UK ONLY

Postal Orders, Cheques to

Dept. R.C.3.,

Galleon Trading Co.,

298A Lodge Lane,

Romford, Essex

FANTASTIC SALE

1,000 of the following Amplifier Kits to clear -

	List Price	Sale Price	P.S.
5 watt amplifier	£3.15.0	£1.15.0	9v
7 watt amplifier	£6.15.0	£2.5.0	9v
10 watt amplifier	£8.19.0	£2.15.0	9v

If two are required deduct the following: 2 x 5 watt 5/-. 2 x 7 watt 7/6. 2 x 10 watt 10/-. Please add 2/6 P&P.

M. GLEAVES AND BROTHER

28 WENNY ESTATE

CHATTERIS

CAMBS

Radio Topics

By Recorder

JANUARY 1970 ?

Yes, it's true - the calendar cannot lie - and another New Year is upon us again. This is the period when journalists are expected to take a surreptitious shift into the future and, conscientious as ever, Old Moore Recorder is now in process of setting the regeneration on his crystal ball so that it is just below the oscillation point.

Let us, therefore, examine what is to happen to us in the electronic world during this year.

PREDICTIONS FOR 1970

January. There is an encouraging start to the year as a spokesman for the Ministry of Technology states that 1970 will be marked by outstanding new developments in British integrated circuit production. At the same time, the manufacture and introduction of new types of discrete semiconductor components continues to increase unabated and, during the month, 476 new transistor types are released. Defence Ministry sets up monster surplus sale for excess stocks of transistors - notably 10,000,000 of type CV111057. Latest American Moon-shot vehicle returns with further samples of Moon-dust.

February. Board of Trade shocks radio retailers by stating that used radio and TV trade-in prices must, in future, be certified as representing true market value by specially appointed B.O.T. Inspectors. Leading semiconductor manufacturer introduces sensational new integrated circuit, claiming that this replaces virtually all the circuitry of a standard monochrome television receiver. An interesting feature of the new integrated circuit is its dual row of connecting terminals, 150 on each side. Post Office Corporation promises further improvements in telephone and postal services, these being directed at attracting increased custom and revenue.

March. Mysterious development at Defence Ministry surplus sale - the entire stock of 10,000,000 transistors type CV111057 is purchased for £5,000 by bearded individual in dark glasses and hippy outfit. Ministry of Technology announces that, due to the uncontrollable multiplicity of transistors currently available, it is making available a computer service to other Ministries to enable them to locate specific types of transistor after feeding in details of the characteristics required. The computer can also advise on equivalents and near-equivalents. Unmanned Soviet Moon-shot capsule returns to Earth with samples of the Moon's surface. 724 new transistor types released.

April. Working model of TV receiver incorporating new integrated circuit shown to Trade Press. The only components external to the integrated circuit are 60 fixed resistors, 40 capacitors, 22 preset potentiometers, 7 i.f. transformers, the tube, the scanning yoke, the line and field output transformers and a u.h.f. tuner. Cooling of the integrated circuit is achieved by means of a motor-driven blower rated at $\frac{1}{4}$ h.p. Mysterious bearded individual in dark glasses and hippy outfit registers new company under the name of Transistors (Soho) Ltd. Retailers shocked by 100% Budget increase in S.E.T. for service engineers.

May. Under pressure from radio retailers, Board of Trade announces that certification of trade-in prices may also be carried out by retailers' engineering staff - details of qualifications required to be announced later. Ministry of Technology states that, due to a disappointing lack of response on the part of other Ministries, the new computer service for advising on transistor types is to be made available also to *bona fide* companies in the public sector. Defence Ministry invites tenders for supply of new semiconductor devices, notably 10,000,000 of transistor type 2N152765A. American research scientists state that recently recovered Moon-dust contains high percentage of silicon with n-type characteristics. 910 new transistor types released.

June. Front page 6-column story in *Pravda* reveals that superior U.S.S.R. unmanned space vehicle has retrieved material from Moon's surface containing large quantities of silicon having p-type characteristics. Post Office Corporation engineers fit rectangular plugs to the slots of public telephone coin boxes to prevent insertion of sixpenny pieces. Transistors (Soho) Ltd. consults Ministry of Technology computer with respect to devices type CV111057 and 2N152765A. Radio retailers shocked by Board of Trade pronouncement that minimum staff qualifications for trade-in value certification are B.Sc., M.Sc., or

Ph.D., together with readiness to sign the Officials Secrets Act.

July. N.A.S.A. announces preparations for forthcoming American Moon flight to carry out geological investigations. It is proposed to survey for strata faults by passing electric currents between remote points of the Moon's surface. Transistors (Soho) Ltd. set up small working plant in a cellar in Greek St., London, W1. The production equipment consists of one high-speed transistor re-coding machine operated by two middle-aged ladies during the periods when they are not required upstairs. 1,116 new transistor types released.

August. Retailers shocked by plans of Post Office Corporation to transfer to them the administration of TV and radio licence issues. Rumours leaking from the U.S.S.R. persistently refer to a potential new Russian unmanned Moon-shot to investigate magnetic phenomena. A senior Soviet physicist is quoted as saying that the low temperature on the dark side of the Moon enables superconducting electro-magnets of exceptional power to be set up without the necessity for complex cooling apparatus. Meanwhile, the high ambient temperature on Earth resulting from an unusually hot Summer necessitates modifications to the TV receiver with the integrated circuit. Engineers increase the blower motor power to $\frac{1}{2}$ h.p.

September. Defence Ministry purchases, for £2,500,000, a quantity of 10,000,000 transistors type 2N152765A from Transistors (Soho) Ltd. Post Office Corporation, as first step towards metrication, changes maximum weight for First Class 5d. postal packages from 4oz. to 2 gr. N.A.S.A. announces that next American Moon-shot will take place in early December. 1,251 new transistor types released. After an extensive Trade Press advertising campaign stating that each set "consists of little more than a single integrated circuit", a pilot quantity of 10,000 TV receivers incorporating the new integrated circuit is offered to the retail trade.

October. Total pilot quantity of 10,000 TV receivers is purchased, at a price only slightly greater than that of the integrated circuits, by Transistors (Soho) Ltd., after threats on the part of the purchaser to invoke the Trade Description Act concerning the phrase "little more than". Post Office Corporation engineers fit rectangular plugs to public telephone coin box slots to prevent insertion of shilling pieces. Reports filtering out of the U.S.S.R. state that next Russian Moon probe firing is scheduled for mid-December.

November. 1,523 new transistor types released. Transistors (Soho) Ltd. dispose of transistor re-coding machine and purchase two screwdrivers, two pairs of pliers and two pairs of side-cutters. Excited French

scientists studying American Moon-dust samples state that the n-type material coalesces into a homogeneous n-type mass when subjected to magnetic and electric fields positioned at right angles to each other.

December. Extra police called in to control vast crowds of radio home-constructors in Lisle St., London, W.C.2, where, using temporarily rented premises, Transistors (Soho) Ltd. successfully dispose of 600,000 fixed resistors, 400,000 capacitors, 220,000 preset potentiometers, 70,000 i.f. transformers, and 10,000 each of cathode ray tubes, scanning yokes, line and field output transformers, u.h.f. tuners and $\frac{1}{2}$ h.p. blower motors. Americans set up Moon surface electrical probes along a line of Moon's latitude. Post Office Corporation announces immediate withdrawal of all coin box telephones due to lack of use by public. *Isvestia* announces that the unmanned Russian space capsule is now set up to produce an intense magnetic field along line of Moon's longitude. Radio retailers shocked by new Home Office regulations for mains lead coding, the new colours being red for earth, black for neutral and green for live. Fortunately, Americans and Russians switch on their apparatus on the Moon's surface simultaneously. Militant Cleansing Department operatives jostle G.L.C. officials whilst demanding bonus pay for clearing 10,000 television chassis, each bare except for one integrated circuit, from a cellar

in Greek St., London, W.1. Mass panic occurs throughout the world as Moon suddenly bursts into self-sustained oscillation, emitting electromagnetic radiation over the entire spectrum from 10kHz to the ultraviolet. Under cover of the resultant communications black-out, a mysterious bearded individual wearing dark glasses and a hippy outfit slips off contentedly to the Bahamas.

THE "SPONTAFLEX" S.A.4

Well, let's hope that the New Year won't be *quite* as bad as that! And my humble apologies to any company whose name even remotely resembles that of the fictitious "Transistors (Soho) Ltd."—all the above is, of course, just a gag.

And now let me turn to a matter which has been raised by Sir Douglas Hall, the popularity of whose receiver designs continues unabated. One of the most ingenious of these is the "Spontaflex" S.A.4 Transistor Portable, which was described in our May, 1968 issue. Although that issue appeared nearly two years ago, readers are still embarking on the construction of the S.A.4 receiver.

A minor difficulty experienced by a few constructors has risen in districts where a very strong signal from Radio 2 on 1,500 metres is received, the effect being that this cannot be sufficiently reduced in volume. The trouble arises from the fact that the long wave coil is too far from the reaction coil for short-

circuiting of the latter to cause adequate damping.

The following modification clears this problem, and the components referred to are all shown in Fig. 1 on page 594 of the May 1968 issue. First, remove L3. Then, connect the arm of S1 (a) to the junction of VC1 and C1. Add a 680pF silver mica capacitor between the base of TR1 and the top contact of S1(a) (this is the contact to which the switch is turned in Fig. 1). These alterations will result in a much better control of volume and they still allow the whole of the long wave band to be tuned. If an upper wavelength of a little over 1,500 metres is enough, a 500pF capacitor may be used instead of the 680pF component. There will be some drop in sensitivity owing to the lowering of the inductance/capacitance ratio, but if the Radio 2 signal is strong enough to make the modification worth-while, there will still be plenty in hand. This occurs even in South Devon, where Sir Douglas Hall has checked the operation of the altered circuit.

BRAND NEW YEAR

And so I have now come to the end of my contribution for this brand new year of ours. Whereupon, there's nothing better I can do, in finishing, than wish readers all the very best of luck together with an exceptionally Prosperous and Happy New Year. ■

NEW ITT-COMPONENTS PUBLICATION

ITT Components Group Europe has just published the first of a set of components summaries which heralds a new style for presenting a concise run-down on all the ITT component ranges.

The first publication is the *Passive Components Summary* (ref. 6000/301). This 116-page short-form catalogue covers such products as: Quartz Crystals and Filters, Magnetic Materials, Transformers, Capacitors, Resistors (fixed and variable), Infra-red filters, etc. The books are available in English, French and German languages.

Copies are available free on application to ITT Components Group Europe, Publicity Department, Edinburgh Way, Harlow, Essex. Please use company letter-head and state job title.

LAST LOOK ROUND

● ALL CHANGE

Are you confused by the decimal coinage relationship with the present currency?

If so, we feature next month a *Decimal Coinage Calculator*—a simple calculating device enabling direct conversion from current pennies to New Pence by way of a potentiometer circuit and a meter. We certainly ring the changes!

● BIRDS OF A FEATHER

Ever tried tape recording birds?

If not, you will find that one on tape is worth two in the bush! Try it and see with the advice given in *Tape Recording Birdsong*—also to be included in our next issue.

● 349

On that page in this issue you will have noted another article by our popular contributor Sir Douglas Hall, K.C.M.G., M.A. Always a source of great interest, his circuits are nothing if not ingenious!

In the next issue we shall be publishing another of his interesting articles entitled *Developing the "Spontaflex" Short Wave Receiver*—make sure you get your copy!

INTERNATIONAL SHORT WAVE LEAGUE




Membership 35s. 0d. per annum (U.S.A. \$5.00) including 12 monthly issues of *Monitor* — the League journal. Including free use of all Services, QSL-Bureau, etc.

**THE LARGEST S.W.L. ORGANISATION
IN THE WORLD**

For full details write to:
**The Secretary,
I.S.W.L.,
60 WHITE STREET, DERBY**

The “NEOPHYTE” AMPLIFIER

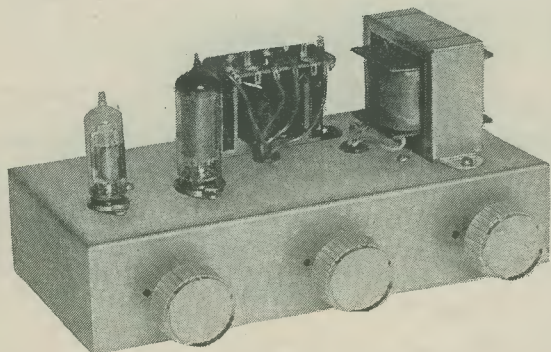

TELERADIO new Hi Fi dept
are stocking all parts to build
this interesting project.
(SEE OCTOBER ISSUE)

Full details on request to
**TELERADIO ELECTRONICS
325-7 Fore St., Edmonton, London N9**

AUDIO AMPLIFIERS



**16 Transistor and Valve Designs for the
Home Constructor**

*Amplifiers for Tuner Units, Record
Players, Tape Recorders, Public Address,
etc., etc.*

Includes contributions by such
well-known authors as

A. S. Carpenter, A. Kinloch, E. Govier,
G. A. French, F. G. Rayer,
P. F. Bretherick, K. Jones, D. Aldous,
R. Murray-Shelley, C. Swires,
G. A. Stevens and V. E. Holley.

Edited by J. R. Davies

PRICE 10s. 6d.

124 pages

Postage 8d.

To: DATA PUBLICATIONS LTD.,
57 Maida Vale London W9

Please supply copy(ies) of "Audio
Amplifiers", Data Book No. 18

I enclose cheque/crossed postal order for.....

NAME.....

ADDRESS.....

.....
.....
.....

BLOCK LETTERS PLEASE

SMALL ADVERTISEMENTS

Rate: 9d. per word Minimum charge 12/-
Box No. 2/- extra.

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of advertisers. (Replies to Box Numbers should be addressed to: Box No. —, *The Radio Constructor*, 57 Maida Vale, London, W.9.)

SERVICE SHEETS. Radio, Television, Transistors, Tape Recorders, Record Players (1925-1969). S.A.E. enquiries.—Hamilton Radio, 54 London Road, Bexhill, Sussex.

BUILD IT in a DEWBOX robust quality plastic cabinet. 2in. x 2½in. x any length. S.A.E. for details. D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset. Write now—right now.

FOR SALE: T.C.C. Lectroflash capacitors, 250µF, 500 volts, 3in. x 1½in. 15/-. Miniature precision Swiss silent motors, reversible, 6 to 12 volts: a marvellous bargain, 25/- 13 amp. white fused plugs, 2/- each or 22/6d. dozen. SenTerSel bridge metal rectifier type C3B, 250 volts, 120mA, 12/6d. A.E.I. SJ302A silicon rectifiers 300 p.i.v. at 2.3 amp. 9/6d. Write today for Super Free Bargain Lists. Xeroxa Radio, Dept. ZA99A, V. V. Collett & Co., 1 East Street, Bishops Tawton, Devon.

BOOKS FOR SALE: *Earth's Envelope*, Theo Lobsack 10/-, *Space Research & Exploration*, D. R. Bates 15/-, *Practical Yacht Racing*, Schiottz 15/-, *Yacht Racing*, Sturgess £1, *Faster Sailing*, Bavier 10/-, *The Story of Atomic Energy*, Soddy 7/6d., *Atomic Medicine*, Behrens 15/-, *Medical Radiation Biology*, Ellinger £1, *Sunday Times & Life World Library Volumes: Brazil, S.E. Asia, Israel, Italy, Russia, Mexico, Greece, Africa, Germany, France, India, Britain, Japan, Scandinavia*, 12/6d. each, *Life Science Library: Man & Space, Planets, Energy*, 12/6d. each, *The Colour of Canada*, £1, *Science Survey 3*, Vista Books, £1, *Science Today & Tomorrow*, 10/- Box No. F364.

TRANSISTORS. Silicon NPN similar to BC108. Unmarked but tested and guaranteed. 1/- each. P. & P. 6d. F. W. Rookes, 79 The Walronds, Tiverton, Devon.

FOR SALE: Metal Rectifier, Radiospares Type REC22, 30/- Push-pull Interstage transformer, Repanco Type TT4, 7/6d. Pair Mullard OC36 transistors, unused, 35/- Heat sink to match, 10/- 0-200mA meter, 2½in. diam., flush mounting, 10/- 0-40mA meter, 2in. sq. f.m., 15/- 50 assorted resistors, £1. 25 assorted capacitors, £1. Box No. F379.

TRANSISTOR SALE: Mixed, germ, PNP, 10 - 2/9d.; 50 - 12/6d. Reject germ, Sil. PNP, NPN, mixed, 10 - 2/-; 50 - 8/6d. D. G. Perry, Graymare, Lostwithiel, Cornwall.

"MEDIUM WAVE NEWS" Monthly during DX season.—Details from: K. Brownless, 7 The Avenue, Clifton, York.

MUSICAL MIRACLES. Send s.a.e. for details of Drum Sound Modules, versatile bass-pedal accompaniment unit, self-contained with unique effects. Kits for Waa-waa pedals 47/-. Also 50µA meters 25/- each. New. D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

FOR SALE: Four Mullard RG1-240A rectifier valves, with high voltage insulation filament transformer, suitable use in pairs. £5. Box No. G100.

ATTENTION. Radio Constructors, Amateurs, Hi-Fi and Electronic addicts. We can supply all you need at competitive prices. Send 9d. for lists to: Inventronics, 14 Elizabeth Drive, Ferrybridge, Yorkshire.

(Continued on page 381)

BENTLEY ACOUSTIC CORPORATION LTD.

38 Chalcot Road, Chalk Farm,
LONDON, N.W.1.
01 - 722 9090

The Old Police Station
Gloucester Road
LITTLEHAMPTON, Sussex
PHONE 6743

Please forward all mail orders to Littlehampton

5Z4G	7/-ECC86	8/-PC95	8/3U404	7/6AC156	4/-BY210	5/-	
6AQ5	5/6ECC88	7/-PC97	8/6U801	19/6AC157	5/-BY211	5/-	
6AT6	4/-ECC189	9/6PC900	8/3UABC80	6/-AD140	7/6BY212	5/-	
6/30L2	12/6EFC80	6/6PC884	6/3UBC81	7/-AD149	8/-BY213	5/-	
6BW6	12/9ECF82	6/6PC885	6/6UBF80	5/9AD162	9/-OA70	3/-	
6BW7	11/-ECF86	9/-PC888	9/9UBF89	6/9AF106	10/-OA79	1/9	
6E23	13/3ECH402	10/-PC889	9/6UC92	5/6AF114	4/-OA81	1/9	
6L6GT	7/9ECH81	5/9PC8189	10/6UCC84	8/-AF115	4/3OA90	2/6	
9D7	9/-ECH83	8/-PCF80	6/6UCC85	6/9AF119	3/-OA91	1/9	
20P4	18/6ECH84	7/6PCF82	6/3UCF80	8/3AF121	6/-OA95	1/9	
30C15	13/-ECL80	6/6PCF84	8/-UCH21	9/-AF126	5/-OA200	1/1-	
30C17	16/-ECL82	6/-PCF86	9/-UCH42	13/-AF139	13/-OA202	2/6	
30C18	11/6ECL83	9/-PCF801	7/-UCH81	6/6AF180	9/6OC22	5/-	
30F3	16/-ECL86	8/-PCF802	9/-UCL82	7/-AF186	11/-OC23	5/-	
30FL1	15/-EF22	12/6PCL82	7/-UCL83	10/-AF239	7/6OC24	5/-	
30FL12	16/-EF41	10/-PCL83	9/-UF41	10/-BA102	9/-OC25	5/-	
30FL14	12/6EF80	4/6PCL84	7/6UF80	6/9BA115	2/8OC26	5/-	
30L15	13/9EF85	5/3PCL85	9/-UF85	6/9BA129	2/6OC28	5/-	
30L17	15/6EF86	6/3PCL86	8/6UF86	9/6BA130	2/-OC35	5/-	
30P4	12/-EF89	5/-PEN45DD	12/-UF89	6/-BCY33	5/-OC36	7/6	
30P4MR	17/6	EF91	3/3PFL200	12/6UL41	10/6BC108	3/6OC38	8/6
30P12	13/9EF183	6/-PL36	6/-UL84	6/6BC113	5/-OC41	10/-	
30P19	12/-EF184	6/-PL81	7/3UM80	6/6BC118	4/6OC44	2/-	
30P19	15/-EH90	7/6PL82	6/6UY41	7/-BCY10	5/-OC45	1/9	
30PL13	15/6EL33	12/-PL83	6/6UY85	5/9BCY12	5/-OC46	3/-	
30PL14	15/-EL41	10/3PL84	6/6ZN404	6/-BCY33	5/-OC70	2/3	
CL33	18/6EL84	4/9PFL500	13/-ZN1756	10/-BCY34	4/6OC71	2/-	
DY87	5/9EL95	5/3PL504	13/6ZN2147	17/-BCY38	5/-OC72	2/-	
EBBCC	12/-EM80	7/-PL509	28/9ZN2297	4/6BCY39	4/6OC74	2/6	
EABCC80	6/-EM81	7/6PL802	15/-ZN2369	4/3BCZ11	3/6OC75	2/-	
EA42	8/9EM84	6/6PY33	10/-ZN2613	7/9BD119	9/-OC78	3/-	
EB91	2/3EM85	11/-PY81	5/3ZN3053	6/6BFY50	4/-OC78D	3/-	
EBC41	9/6EM87	7/6PY82	5/-ZN3121	50/-BFY51	4/-OC81	2/-	
EBC81	5/9EY51	7/6PY83	5/9ZN3703	3/9BFY52	4/6OC81D	2/-	
EBF80	6/9EY87	6/6PY88	6/9ZN3709	4/-BF159	5/-OC82	2/3	
EBF83	8/-EZ40	7/6PY800	7/6ZN3866	20/-BF163	4/-OC83	2/-	
EBF89	6/3EZ80	4/6PY801	6/9ZN3988	10/-BF173	7/6OC84	3/-	
EC92	6/6EZ81	4/9UJ19	34/6ZS323	10/-BF180	6/-OC123	4/6	
ECC81	3/9HY82	8/9UJ25	13/-AA119	3/-BY100	3/-OC78D	3/6	
ECC82	4/6KTY62	10/-UZ26	11/9AA120	3/-BY105	3/-OC172	4/-	
ECC83	4/6PABC807/3	U37	34/11AC113	5/-BY114	3/6OC200	4/4	
ECC84	5/6PC86	10/3UJ91	12/6AC127	2/-BY126	3/-OC202	4/6	
ECC85	5/6PC88	10/3UJ301	11/-AC154	5/-BY127	3/6OC203	4/6	

Terms of business: Cash with order only. No C.O.D. Post/Packing 6d. per item. Orders over £5 post free. All orders despatched same day as received by first class mail. Complete catalogue including transistor section and components with terms of business 10d. Any parcel insured against damage in transit for 6d. extra. Business hours 9 a.m.-5.30 p.m. Saturdays 9 a.m.-1 p.m.



TECHNICAL TRAINING IN RADIO, TELEVISION AND ELECTRONIC ENGINEERING

First class opportunities in Radio and Electronics await the ICS trained man. Let ICS train YOU for a well-paid post in this expanding field.

ICS courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success.

Diploma courses in Radio TV Engineering and Servicing Electronics, Computers, etc. Expert coaching for:

- * C. & G. TELECOMMUNICATION TECHNICIANS CERTS.
- * C. & G. ELECTRONIC SERVICING
- * R.T.E.B. RADIO AND TV SERVICING CERTIFICATE
- * RADIO AMATEURS EXAMINATION
- * P.M.G. CERTIFICATES IN RADIO TELEGRAPHY

Examination Students Coached until Successful.

NEW SELF-BUILD RADIO COURSES

Build your own 5-valve receiver, transistor portable, signal generator, multi-test meter and professional-type valve voltmeter—all under expert guidance.

POST THIS COUPON TODAY and find out how ICS can help YOU in your career. Full details of ICS courses in Radio, Television and Electronics will be sent to you by return mail.

MEMBER OF ASSOC. OF BRITISH CORRESPONDENCE COLLEGES.

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 248, Intertext House, Stewarts Road, London, S.W.8.

NAME _____
Block Capitals Please
ADDRESS _____
1.70

RADIO OPERATORS

There will be a number of vacancies in the Composite Signals Organisation for experienced Radio Operators in 1970 and in subsequent years.

Specialist training courses lasting approximately nine months, according to the trainee's progress, are held at intervals. Applications are now invited for the course starting in September 1970.

During training a salary will be paid on the following scale:-

Age 21	£800 per annum
22	855 " "
23	890 " "
24	925 " "
25 and over	965 " "

Free accommodation will be provided at the Training School.

After successful completion of the course, operators will be paid on the Grade 1 scale:-

Age 21	£965 per annum
22	1025 " "
23	1085 " "
24	1145 " "
25 (highest age point)	1215 " "

then by six annual increases to a maximum of £1,650 per annum.

Excellent conditions and good prospects of promotion. Opportunities for service abroad.

Applicants must normally be under 30 years of age at start of training course and must have at least two years' operating experience. Preference given to those who also have GCE or PMG qualifications.

Interviews will be arranged throughout 1970.

Application forms and further particulars from:-

**Recruitment Officer,
Government Communications
Headquarters,**

**Oakley,
Priors Road,
CHELTENHAM,
Glos., GL52 5AJ.
Tel: Cheltenham 21491. Ext. 2270.**

There is scope, variety and responsibility as a RADIO TECHNICIAN in Air Traffic Control

Join the National Air Traffic Control Service of the Board of Trade as a Radio Technician and you have the prospect of a steadily developing career in a demanding and ever-expanding field.

Entrance qualifications: you should be 19 or over, with at least one year's practical experience in telecommunications. Preference will be given to those having ONC or qualifications in telecommunications.

Once appointed and given familiarisation training, you will be doing varied and vital work on some of the world's most advanced equipment including computers, radar and data extraction, automatic landing systems, communications and closed-circuit television. Work is based on Civil Airports, Air Traffic Control Centres, Radar Stations and specialist establishments. Vacancies exist in various parts of the United Kingdom.

Salary: £985 (at 19) to £1,295 (at 25 or over): scale maximum £1,500 (higher rates at Heathrow). Some posts attract shift-duty payments. Promotion prospects are excellent and ample opportunity and assistance is given to study for higher qualifications.

The annual leave allowance is good and there is a non-contributory pension scheme for established staff.

Send this coupon for full details and application form
To: A. J. Edwards, C.Eng., M.I.E.E., M.I.E.R.E., Room 705,
The Adelphi, John Adam Street, London WC2
marking your envelope 'Recruitment'.

Name.....

Address.....

Not applicable to residents outside the United Kingdom. RC/A1

NATCS National Air Traffic Control Service

THE RADIO CONSTRUCTOR

SMALL ADVERTISEMENTS

Continued from page 379

ASSORTED LOTS OF USED COMPONENTS. Resistors 15/- for 50. Capacitors 10/- for 20. Box No. G102.

UFO DETECTOR CIRCUITS. Data, 10s. (refundable). Para-physical Laboratory (UFO Observatory), Down-ton, Wilts.

TOROIDS FOR SALE: 550, 475, 500, 395, 480, 270, 210mH, 5/- each. Box No. G104.

WANTED: Line output transformer, Murphy television V310A. Reasonable. Weaver, 53 Kennylands Road, Sonning Common, Reading, Berkshire.

FOR SALE: Taylor 88A Multimeter, 20kΩ/V, wood case, 74 ranges to 5,000 volts and 10 amp., a.c./d.c. Resistance to 50MΩ. £15. EICO 249 VTVM, 7½in. Meter, to 1,500V, a.c./d.c. Measures p-p Complex waves to 3MHz, measures resistance to 1,000MΩ. £18. Heathkit Millivoltmeter AV3U. £10. All with manuals and leads. Box No. G106.

JOIN THE INTERNATIONAL S.W. LEAGUE. Free Services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept.—both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazine, etc., 35s. per annum. Secretary ISWL, 60 White Street, Derby.

FOR SALE: TW "Communicator", Shure push-to-talk mic., speaker, ground plane antenna and 30ft. coax., all leads, battery clips, 20 volt battery meter and switch. Complete 2 metre station ready to go on the air. Immaculate. £80 o.n.o. Box No. G107.

ARE YOU A MOTORING ENTHUSIAST? The Seven Fifty Motor Club caters for all types of motor sport—racing, rallies, hill climbs, etc. Monthly Bulletin free to members. For full details write to: The General Secretary, Colin Peck, "Dancer's End," St. Winifred's Road, Biggin Hill, Kent.

FOR SALE: Collection of stamps. £125. S.A.E. for details. Box No. G109.

FOR SALE: Cossor 1049 MK. III Oscilloscope in good condition. £25. K. Beswick, 11 Chestnut Walk, Stratford, Warwickshire.

TO CLEAR. Back numbers of "The National Geographical Magazine", to January 1959. 3/6d. each post paid. Box No. G110.

WORLD DX CLUB covers all aspects of SWLing on Amateur and Broadcast Bands through its monthly bulletin "Contact". Membership costs 25s. a year. Enquiries to Secretary, WDXC, 17 Taunton Road, Bridgewater, Somerset.

BOOKS TO CLEAR: "The Upper Atmosphere", Massey & Boyd, 50/-; "KEOEIT", story of the Aurora Borealis 20/-; "The Living Brain", Grey Walter, 10/-; "Teach Yourself Russian", 5/-; "Principles of Modern Book-keeping", 5/-; "Outlook", elementary weather forecasting, 7/6d.; "Marine Signalling Methods", Pomphrey, 10/-; "Practical Nucleonics", experiments in Nuclear Physics, Pearson & Osborne, 25/-; "Health Physics", principles of radiation protection, Rees, 50/-; "Violent Universe", Calder, 15/-. All plus postage. Box No. G111.

FOR SALE: 500 I.T.A. converter tuners. Send 3/- to cover postage and packing for sample to: E. Graley, 15 Roskell Road, Liverpool 25.

(Continued on page 383)


JACKSON

the big name in **PRECISION** components



The Latest Transmitter Capacitor

Type TX 5 Variable Capacitor

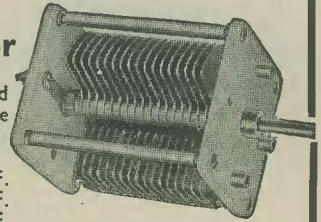

Ceramic insulation. End area 2½ x 2½". Heavy gauge aluminium vanes with radiused edges.

.128" air gap up to 150pF.

.064" air gap up to 500pF.

.036" air gap up to 1000pF.

Designed for use in radio transmitting and power oscillators. Split stator models also available to order.

Write for details



JACKSON BROS. (London) LIMITED

Dept. RC, KINGSWAY-WADDON, CROYDON, CR9 4DG
Phone Croydon 2754-5 (01-688); Grams Walfilco, Croydon. U.S. Office: M. Swedgal, 258 Broadway, N. York. N.Y. 10007.

FREE TO AMBITIOUS ENGINEERS

—THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?
ENGINEERING OPPORTUNITIES is a highly informative 164 page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronic Courses administered by our Specialist Electronics Training Division — explains the benefits of our Appointments Dept. and shows you how to qualify for five years promotion in one year.

"Satisfaction or refund of fee" terms

Whatever your age or experience you cannot afford to miss reading this famous book. Send for your copy of "ENGINEERING OPPORTUNITIES" today — FREE.

Practical Equipment including Tools

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Basic Practice and Theoretical Courses for beginners in Radio, T.V., Electronics, etc. Ask for details.

Which is your pet subject

A.M.I.E.R.E. City & Guilds Radio Amateur's Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

The B.I.E.T. is the leading Institute of its kind in the world.

Please send
Free Books and
Full Information

**British Institute of
Engineering Technology**

NAME

ADDRESS



Subject
of interest..... Age.....


ALDERMASTON COURT, Dept D13. Aldermaston, Berks.

NEW STYLE SELF-BINDER

for "The Radio Constructor"

The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for, and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check-device is fitted to each.

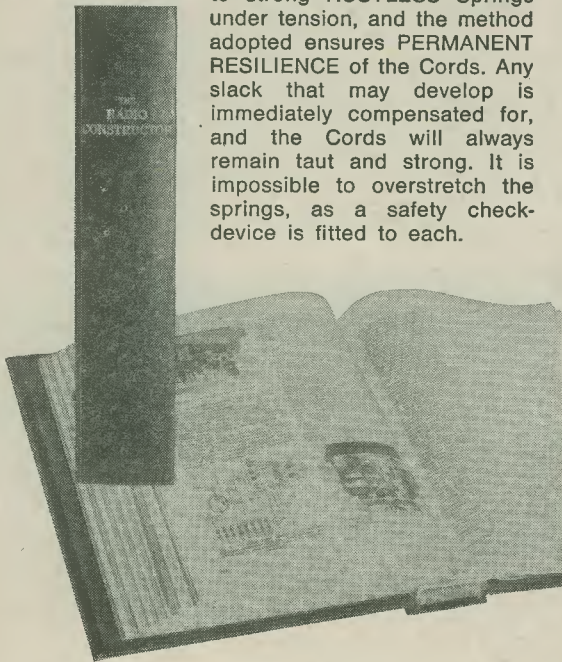

PRICE **14/-** Postage 1/6

Available only from:—

Data Publications Ltd.
57 Maida Vale London W9

TRAINEE RADIO TECHNICIANS

A PROGRESSIVE CAREER IN THE FIELD OF
RADIO AND ELECTRONICS

Applications are now invited for an intensive training course of two years, leading to appointment as a fully qualified RADIO TECHNICIAN, with further prospects of progression to the Telecommunications Technical Officer Class.

Generous Pay and Conditions while under training.

Candidates must be over 16 and under 21 years of age as at 7 September 1970, on which date training commences.

Minimum educational qualifications required are passes at GCE 'O' Level in English Language, Mathematics and Physics (already held or expected to be obtained in the Summer, 1970). Equivalent passes in Scottish or Northern Ireland Certificates and CSE Grade I passes are also acceptable.

Closing date for receipt of applications 27 February 1970.

Apply for full details and application form to:—
**THE RECRUITMENT OFFICER (TRT/63),
GOVERNMENT COMMUNICATIONS
HEADQUARTERS,
OAKLEY, PRIORS ROAD,
CHELTENHAM, GLOS.
GL52 5AJ.**

HENRY'S RADIO LTD. 303 EDGWARE ROAD, LONDON, W.2

HAVE THE FOLLOWING VACANCIES IN THEIR ORGANISATION
SALES ASSISTANT: Young man with good general knowledge of electronic components required for our retail sales dept. Please telephone 723-1008/9 ext. 1.

SALES ASSISTANT, HI-FI DEPT. Young man with a good general knowledge of HIGH FIDELITY EQUIPMENT required for our retail HI-FI SALES DEPT. Please contact MR. STEVENS, Telephone 723-6963.

3 TRANSISTOR RADIO KIT

The small transistor radio, supplied complete with earphone and powered by a small mercury battery, is mounted in a stout plastic box measuring 3" x 2" x 1". The radio is capable of receiving Radios 1, 3, 4 and Luxembourg, together with a number of Continental stations after dark. Supplied with instructions for easy assembly.

29/6

**ISHERWOODS ELECTRONICS 98/100 NORTHGATE
BLACKBURN, LANCs.**

A MUST FOR THE HI-FI PERFECTIONIST AUDIO ADAPTOR UNITS

TYPE AAU-2. Provides switching between 2 pairs of speakers and 1 pair of Stereo Headphones to 1 Stereo Amplifier, which can be either switched singly or simultaneously.

TYPE AAU-3. Provides switching between 3 Stereo inputs to a common Amplifier input. A general purpose unit suitable for pick-ups, tuners, mics, tape, etc. Two inputs at rear and 1 via front DIN socket. Rear inputs are alternately switched to front socket for feeding external equipment.

TYPE AAU-4. Provides Stereo Record/Replay connections between 2 Stereo or Mono Tape Recorders, to 1 Stereo Amplifier. One Recorder can be permanently installed in the cabinet with amplifier, connected via the rear sockets. The other can be used externally, and be connected to the front socket as required.

TYPE UUA-TV. Provides a ready means of connecting external equipment to a TV receiver with complete safety.

We stock all the above and many other units manufactured by M.A.C. Ltd. Write for full details to:
W. E. C. LTD. (AC), 74 The Street, Ashted, Surrey

SMALL ADVERTISEMENTS

Continued from page 381

FOR SALE: G2DAF Linear Amplifier and power supply. £50 o.n.o. S.A.E. for details. Box No. G108.

FOR SALE: Mains transformers: Woden RMS 12A, 350-0-350V, 120mA, 6.3V 4A, 6.3V 2A, £2. Woden fil. 3.75-0-3.75V, 5A, £1. 350-0-350V, 250mA, 5V 2A x 2, 6.3V 2A, 2V 1A, £1. 250-0-250V, 100mA, 4V, 6.3V, 2A, 15/- 0-140V tapped out, 250V a.c. tapped in, 10/- Postage paid. Box No. G112.

POSTAL ADVERTISING? This is the Holborn Service, Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list.—The Holborn Direct Mail Company, Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London; S.E.1. Telephone: 01-407-1495.

FOR SALE: 200 pathological specimen slides. Suit medical student. £3. G2UK, East Keal, Romany Road, Oulton Broad, Suffolk.

IF YOU HAVE ENJOYED A HOLIDAY on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from:—The Hon. Membership Secretary, The Broads Society, "Icknield", Hilly Plantation, Thorpe St. Andrew, Norwich, NOR 85S.

FOR SALE: Tannoy hand mic. £1. Eddystone P.A. coil formers, 10/-. Parmeco mains choke, 10H, 250mA, £2. 2 metre converter £3. 20W motor generator, ex-A.M., 12V 4A in, 400V 0.05A out, £2. Bubble sextant Mk. IX, £3. Box No. G113.

PROPERTIES for sale and to let in London and suburbs. Apply to Maggs & Stephens, Estate Agents, 229 Maida Vale, London, W.9. MAIDA VALE 8123.

MAGAZINES TO CLEAR: *CQ* 1947–November, 1955–April, 1957–February to June, 1959–July to December, 1960–complete, 1961–all except August, 1962, 1963–complete, 1964–March missing, 1965–complete, 1966–all except October, 1/6d. per copy. *QST*, 1948 October, 1961 October to December, 1962 September, 2/- per copy. *RSGB Bulletin*, 1956–May, September, October, 1957–August, September, 1958–February, July to December, 1959–60–complete, 1961–August, September missing, 1962–February to May, 1/- per copy. *73*, 1963–July, August, September to November, 1967–January, October, 1968 January, February, April & November, 1/6d. per copy. *Wireless World*, 1947–December, 1958–September, 1960–January, April, June, September to December, 1964–January, December, 1965–January to June, 2/- per copy. Box No. G114.

INNOVATION IN DX CLUBS ANNOUNCED! Formed in October, 1965, the Radio New York Worldwide Listeners Club now has 3,600 members in 86 countries! A unique club offering shortwave listeners monthly magazines containing listening tips and technical features, numbered wallet-sized membership cards and gold 8½in. by 11in. membership certificates. Multi-lingual report forms available for cost of postage. "We must be doing something right!" "Find out . . . join now!" Send 7s. 2d. (crossed domestic money order) for one year's membership to: The Radio New York Worldwide Listeners Club, 485 Madison Avenue, New York 10022, U.S.A.

RECITALS OF RECORDED MUSIC. The second Saturday evening of each winter month. Next recital: January 10th, 1970, 8 p.m. Woodford Green United Free Church, Woodford Green, Essex. Bus routes 20, 20A, 38A and 179—alight at "The Castle" stop.


ESSEX GARDENERS. Buy your bedding and rock plants, shrubs, etc., also cacti from May's Nurseries, 608 Rayleigh Road, Hutton, Brentwood, Essex. Callers only. Monday to Saturday.

JANUARY 1970

PLAIN-BACKED NEW STYLE SELF-BINDERS

for your other magazines

(max. format 7½" x 9½")

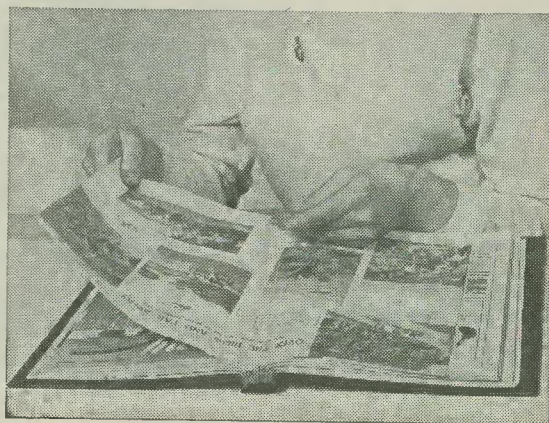

The "CORDEX" Patent Self-Binding Case will keep your copies in mint condition. Issues can be inserted or removed with the greatest of ease. Specially constructed Binding cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for, and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check-device is fitted to each.

COLOURS: MAROON OR GREEN

(Please state choice)

PRICE 13/6 Postage 1/6

Available only from:—

Data Publications Ltd.
57 Maida Vale London W9

CHASSIS and CASES by



H. L. SMITH & CO. LTD.
287/9 Edgware Road
London W2
TEL: 01-723 5891

BLANK CHASSIS


FOUR-SIDED 16 SWG ALUMINIUM

Size	Price	Base	Size	Price	Base
6x4x2"	6/3	2/11	10x8x2 1/2"	12/-	5/6
7x4x1 1/2"	6/-	3/2	12x7x2 1/2"	12/-	5/11
7x5x2 1/2"	7/6	3/5	12x9x2 1/2"	13/9	7/-
8x4x2"	7/-	3/4	13x8x2 1/2"	13/9	6/11
8 1/2 x 5 1/2 x 2"	8/-	3/9	14x7x3 1/2"	14/6	6/6
9x7x2"	9/3	4/10	14x10x2 1/2"	16/-	8/7
10x4x2 1/2"	9/-	3/9	15x10x2 1/2"	16/6	9/1
12x4x2 1/2"	10/-	4/3	17x10x3"	19/6	10/1
12x5x3"	12/-	4/9			

CASES ALUMINIUM, SILVER HAMMERED FINISH

Type	Size	Price	Type	Size	Price
N	8x6x2"*	18/-	W	12x7x7"	37/6
N	6x6x3"	17/6	W	15x9x8"	48/6
N	4x4x4"	11/-	Y	8x6x6"	29/-
U	4x4x4"	11/-	Y	12x7x7"	45/-
U	5 1/2 x 4 1/2 x 4 1/2"	17/-	Y	13x7x9"	50/6
U	8x6x6"	23/-	Y	15x9x7"	53/6
U	9 1/2 x 7 1/2 x 3 1/2"	24/-	Z	17x10x9"	72/6
U	15x9x9"	49/-	Z	19x10x8 1/2"	78/-
W	8x6x6"	23/-			*Height

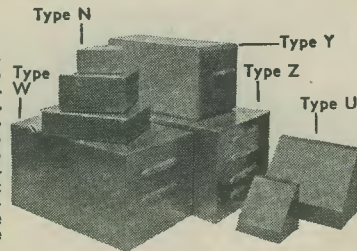Type N has removable bottom, Type U removable bottom or back, Type W removable front, Type Y all screwed construction, Type Z removable back and front Plus p. & p.




TO FIT OUR CASES

7x5 1/2 x 1 1/2"	7/-	3/9	12x6 1/2 x 2"	10/9	5/11
7x5 1/2 x 2"	7/9	3/9	14x8 1/2 x 2"	13/6	7/11
11x6 1/2 x 1 1/2"	10/-	5/6	15 1/2 x 9 1/2 x 2 1/2"	17/-	9/6
11x6 1/2 x 2"	10/-	5/6	17 1/2 x 9 1/2 x 2 1/2"	18/6	10/6

Plus post & packing
PANELS: Any size up to 3ft. at 6/- sq.ft. 16 s.w.g. (18 s.w.g. 5/3). Plus postage and packing.

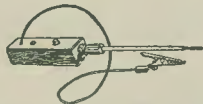THE IMPROVED WILSIC SIGNAL INJECTOR. Now all-silicon circuit for extra high frequency harmonics. Light and compact, measuring only 3 1/2" x 1 1/2", excluding probe. Price ready for use, including battery, 32/6 post free.



BUILD A WAH-WAH PEDAL: SELECTIVE AMPLIFIER MODULE. Basis of Wah-Wah Pedal. All components to build two transistor circuit, including sockets, control, battery and clip, resistors, capacitors and Veroboard. Full instructions provided. 30/- post free. Assembled and tested £2.

WILSIC REVERBERATION UNIT. Owing to fantastic demand for this unit, we are temporarily out of stock of this popular kit. We shall be able to resume supplies in February.

BUT YOU MAY RESERVE ONE NOW! PLEASE ENQUIRE.

Send 1/- for our catalogue of components, testmeters, musical electronics and more details of the above items. Callers welcome.

WILSIC ELECTRONICS LIMITED

6 Copley Road, Doncaster, Yorkshire

YUKAN SELF-SPRAY SO PROFESSIONAL THE YUKAN AEROSOL WAY-
Get these air drying GREY HAMMER
NOW! OR BLACK WRINKLE
(CRACKLE) finishes

Yukan Aerosol spraykit contains 16 ozs. fine quality, durable easy instant spray. No stove baking required. Hammers available in grey, blue, gold, bronze. Modern Eggshell Black Wrinkle (Crackle) all at 15/11 at our counter or 16/11, carriage paid, per push-button self-spray can. Also Durable, heat and water resistant Black Matt finish (12 ozs. self-spray cans only) 13/11 carriage paid.

SPECIAL OFFER: 1 can plus optional transferable snap-on trigger handle (value 5/-) for 18/11, carriage paid. Choice of 13 self-spray plain colours and primer (Motor car quality) also available.

Please enclose cheque or crossed P.O. for total amount direct to:

DEPT: N/1 YUKAN, 307a, EDGWARE ROAD, LONDON, W.2.

We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organisations—We can supply you too.

Open all day Saturday. Closed Thursday afternoons.

Other Yukan Air Drying Aerosols, 16 ozs. or 18/11 carriage paid include: Zinc Chromate Clear Lacquer Metallics: Grey, Blue, Bronze and Gold.



DATA BOOK SERIES

- DB5 TV FAULT FINDING**
124 pages. Price 8/6, postage 8d.
- DB6 THE RADIO AMATEUR OPERATOR'S HANDBOOK**
64 pages. Price 6/-, postage 6d.
- DB15 TWENTY SUGGESTED CIRCUITS**
48 pages. Price 3/6, postage 5d.
- DB16 RADIO CONTROL FOR MODELS**
192 pages. Price 15/-, postage 1/-.
- DB17 UNDERSTANDING TELEVISION**
512 pages. Price 37/6, postage 3/-
- DB18 AUDIO AMPLIFIERS**
128 pages. Price 10/6, postage 8d.

I enclose Postal Order/Cheque for..... in payment for.....

NAME

ADDRESS

(Please use Block Capitals for both name and address)
Postal Orders should be crossed and made payable to Data Publications Ltd.
Overseas customers please pay by International Money Order
All publications are obtainable from your local bookseller
Data Publications Ltd., 57 Maida Vale, London W.9

RADIO CONSTRUCTORS DATA SHEET

34

R.M.S., PEAK AND AVERAGE VALUES


The Table lists, to three significant figures, peak values, twice peak values, and average values for sinusoidal alternating voltage or current from 1 to 1,000 r.m.s. units. The column giving twice peak values is included to cover voltage doubling circuits and peak inverse voltage ratings for capacitor input half-wave rectifier circuits; twice peak values are, also, equal to peak-to-peak values.

R.M.S.	Peak	2 x Peak	Average	R.M.S.	Peak	2 x Peak	Average
1	1.41	2.83	0.901	150	212	424	135
2	2.83	5.66	1.80	200	283	566	180
3	4.24	8.48	2.70	250	354	707	225
4	5.66	11.3	3.60	300	424	848	270
5	7.07	14.1	4.51	350	495	990	315
6	8.48	17.0	5.41	400	566	1,130	360
7	9.90	19.8	6.31	450	636	1,270	405
8	11.3	22.6	7.21	500	707	1,410	451
9	12.7	25.4	8.11	550	778	1,560	496
10	14.1	28.3	9.01	600	848	1,700	541
20	28.3	56.6	18.0	650	919	1,840	586
30	42.4	84.8	27.0	700	990	1,980	631
40	56.6	113	36.0	750	1,060	2,120	676
50	70.7	141	45.1	800	1,130	2,260	721
60	84.8	170	54.1	850	1,200	2,400	766
70	99.0	198	63.1	900	1,270	2,540	811
80	113	226	72.1	950	1,340	2,690	856
90	127	254	81.1	1,000	1,410	2,830	901
100	141	283	90.1				

HENRY'S RADIO LTD.

ENGLAND'S LEADING COMPONENT AND EQUIPMENT CENTRES


BUILD A QUALITY 4 TRACK TAPE RECORDER

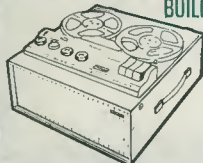


To get the best out of your MAGNAVOX DECK, you need a MARTIN RECORDAKIT. This comprises a special high quality 6 valve amplifier and pre-amplifier which comes to you assembled on it's printed circuit board - in fact everything for making a superb Tape Recorder. You need no experience or technical skill to bring this about. THE INSTRUCTIONS MANUAL MAKES BUILDING EASY, AND SUCCESS IS ASSURED. Kit comprises: Deck, Amplifier, Cabinet and speaker, with microphone, 7" 1200 Hz. tape, and spare spool. ASK FOR BROCHURE 6. TODAY'S VALUE £60. PRICE 39 gns. p.p. 22/6. NOTHING ELSE TO BUY

SCOOP! STAAR RECORD PLAYER

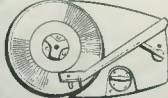Deck plays 33, 45, 78, R.P.M. records, 9 volt operated, with mono cartridge. BRAND NEW... as illustrated.



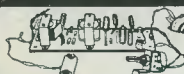PRICE 59/6. p.p. 3/6. Send for leaflet No. 2.




MULLARD 1WATT AMPLIFIER

Portable Transistor Unit-ideal for Intermcoms, Baby Alarms, Tele phone, Record Players or Guitar Practice. 9 Volt 5 transistors with volume control, output 3 ohms. Ideal for use with STAAR RECORD DECK. PRICE 45/- p.p. 2/6.

OTHER ITEMS. Suitable 7 x 4 inch. 3 ohm speaker 17/6 p.p. 1/6. Revine cover cabinet 12 x 9 x 4 12/6 p.p. 2/6. P.P. 9-volt battery 3/9. Write for leaflet No. 2.

GARRARD RECORD DECKS

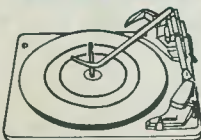


All the latest models BRAND NEW and guaranteed - TERRIFIC SAVINGS!

- *2025 STEREO £ 9.19.6.
- *2025C DIAMOND, 9TAH C. £ 9.19.6.
- *3000 STEREO 9TAH C. £ 9.19.6.
- *SP 25 Mk.II £11.19.6.
- *SL 95 £11.19.6.
- A70 Mk.II. £12.10.0.
- *AT 60 K.II. £13.10.0.
- *SL 65 £14.10.0.
- AP 75 £19.0.0.
- 401 £28.7.6.
- SL 75 £29.0.0.
- SL 95 £35.0.0.
- GL 75 GOLDRING £32.0.0.
- GL 75 P £46.15.0.

ALSO IN STOCK - THORENS - Lenco - B.S.R. Carriage/insurance 7/6 extra on any model. W84 BASES £3.19.6. PERSPEX COVERS £3.10.0. *Special offer base and cover available for these models at £4.15.0. Carriage 5/-. Complete range of Cartridges/Pilnths/Covers. SEND FOR 8-PAGE BROCHURE 16/17 TODAY.

BUILD YOURSELF A QUALITY RADIO

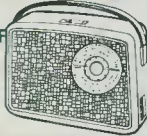

New printed circuit design with full power output. Fully tuneable on both mw/lw. bands. 7 Mullard transistors, Fitted 5" speaker, Room Filling Power. Easy to build with terrific results. All local and continental stations. Complete detailed instructions. TOTAL COST £6.19.6. p.p. 4/6. Ask for Leaflet No. 1.

TRANSISTORS DIODES RECTIFIERS

WE HAVE THE MOST COMPREHENSIVE STOCK IN GREAT BRITAIN. NEW 1969 LIST OF 1000 TYPES. SEND FOR FREE COPY TODAY (LIST 36) Whether you require one or 1000, devices we can fulfil your order from stock! For quantity quotations telephone: (01) 723 0401 Ex. 4. or (01) 402 6823.


HENELEC 5-5 STEREO AMPLIFIER

Excellent low priced British designed Stereo Amplifier for use with Record Decks, Mike, Tuners. 16 transistor mains operated. Output 5+5 watts for 8-15 ohm speakers. Black, silver and wood finish, size 13" x 3" x 6". PRICE £13.0.0. p.p. 7/6. (Leaflet on request). Complete Stereo System 5-5. Garrard 2025 stereo, 5-5 Amplifier, Pilnth/Cover, Two 10 watt speakers with tweeters in polished cabinets. Usual price £47.0.0. OUR PRICE £39.10.0. p.p. 20/- ASK FOR BROCHURE 13



SINCLAIR EQUIPMENT

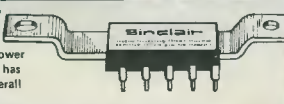The SINCLAIR IC-10 is the worlds first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself has an output power of 10 watts, yet with an overall size of 1 x 0.4 x 0.2 in.




- | | | | |
|------------------------------------|----------|------------------|------|
| IC-10 Integrated Circuit Amplifier | 59/6 | | |
| Z30 | 89/6 | | |
| Stereo 60 | £9.19.6. | RCA. CA3014 | 29/6 |
| P25 Power Supply | £4.19.6. | RCA. CA3018 | 22/6 |
| Q16 Loud Speaker | £8.19.6. | RCA. CA3020 | 29/6 |
| Z12 Amplifier | 89/6 | RCA. CA3030 | 18/6 |
| PZ 4 Power unit | 99/6 | Sinclair I.C.10. | 59/6 |
| Stereo 25 | £9.19.6. | G.E. PA230* | 22/6 |
| Q14 Speaker system | £7.19.6. | G.E. PA234* | 20/0 |
| | | G.E. PA237* | 37/6 |

- | | | |
|-------------------------------------|---|------|
| OTHER TYPES OF INTEGRATED CIRCUITS* | G.E. PA246* | 52/6 |
| | SL402 Plessey | 45/0 |
| | SL403 Plessey | 49/6 |
| | S.G.S. UL910 | 10/0 |
| | S.G.S. UL900 | 10/0 |
| | S.G.S. UL914 | 11/0 |
| | Mullard TAA263 | 15/0 |
| | *Data sheets 3/6 set for these, for others see catalogue. | |

BUILD THIS VHF FM TUNER

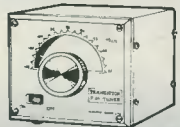5 MULLARD TRANSISTORS. 300 kc/s BANDWIDTH. PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION MONO & STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it - VHF FM gives the REAL sound.



PARTS TOTAL COST £6.19.6. DECODER £5.19.6. ASK FOR LEAFLET No. 3. (FOR STEREO)

HENRY'S RADIO Fully Illustrated CATALOGUES

ALL TYPES OF ELECTRONIC COMPONENTS TEST EQUIPMENT KITS BUILT UNITS



HIGH FIDELITY & GENERAL AUDIO EQUIPMENT CATALOGUE

COMPREHENSIVE · CLEAR · CONCISE · CATALOGUES

A Over 300 pages fully detailed and illustrated with more than 6,000 stock items. Everything for amateur and professional use. Complete with 5 vouchers 10/- value, for use with purchases.

ORDER AS CATALOGUE A PRICE 7/6. p.p. 2/-

B New audio and high fidelity catalogue. 120 pages containing ideas and equipment for every application. Special low prices for all leading makes. Plus 12/6 extra discount voucher.

ORDER AS CATALOGUE B. PRICE 7/6. p.p. 1/-

WHY NOT SEND AWAY TODAY!


AUDIO EQUIPMENT

Mono or Stereo Audio equipment developed from Dinsdale Mk. II - each unit or system will compare favourably with other professional equipment selling at much higher prices.

£11.12.5. to £38.17.6. (all units available separately).


THE FINEST VALUE IN LOW COST HIGH FIDELITY - CHOOSE A SYSTEM TO SUIT YOUR NEEDS AND SAVE YOURSELF POUNDS.

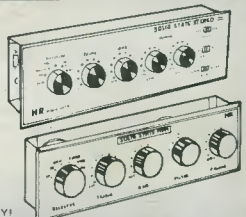SEND FOR BROCHURES No. 12/14 and 21 TODAY!



HI-FI equipment to suit EVERY POCKET

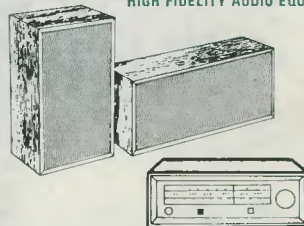HIGH FIDELITY AUDIO EQUIPMENT CATALOGUE 5/- p.p. 1/-



VISIT OUR NEW HI-FI CENTRE AT 309 EDGWARE ROAD, for all leading makes of - AMPLIFIERS, TUNERS, DECKS, SPEAKERS, MICROPHONES, TEST EQUIPMENT. ALL WITH DISCOUNTS - IT WILL PAY YOU TO PAY US A VISIT. AUDIO SYSTEMS £40 - £300 TO SUIT EVERY POCKET. DEFERRED TERMS AVAILABLE. SEND FOR ILLUSTRATED BROCHURE 16/17. TWO DEMONSTRATION ROOMS

ELECTRONIC ORGANS

COMPLETE KITS FOR THE HOME CONSTRUCTOR

STAR FEATURES "ALL TRANSISTOR PRINTED CIRCUIT DESIGNS. "BRITISH DESIGN. "STEP BY STEP DETAILED INSTRUCTIONS. "SAVES UP TO 50% ON COMMERCIAL EQUIVALENT. "EVERYTHING SUPPLIED DOWN TO THE LAST ITEM. "FULL AFTER-SALES SERVICE & ADVICE. "CREDIT SALE & H.P. TERMS AVAILABLE.

We are pleased to offer the choice of FOUR British designs from a single manual portable at £99 THE MAYFAIR for light or classical music - to a two manual five octave de-luxe model with OAK CONSOLE from £285 for the serious musician. These kits are the result of years of research and design and offer the best that is essential to good organ designs, coupled with excellent value are within the reach of most pockets. No technical skill or knowledge is required in construction, with the aid of the STEP BY STEP illustrated manuals will produce an instrument that will be a delight to own and use and will give years of trouble free entertainment for the whole family.

SEND FOR ILLUSTRATED BROCHURES 9/10/11 TODAY! When in LONDON. CALL IN SEE, HEAR, PLAY FOR YOURSELF

Organ Demonstration Room 1st Floor. PRACTICAL ELECTRONICS ORGAN COMPONENTS

We are able to supply all items for this series, details on request.

Start building for as little as £10

MODELS FROM £99 - £350.

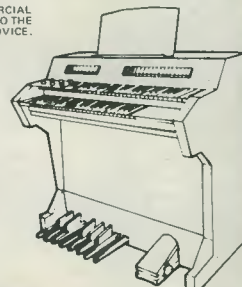


ILLUSTRATION OF GROSVENOR ELECTRONIC ORGAN

Built models available from £124.

HENRY'S RADIO LTD.

Mail Order Dept. Components. Organ Dept. 303 EDGWARE ROAD, LONDON W.2. Telephone: 01-723 1008/9

High Fidelity and Equipment Centre 309 EDGWARE ROAD, LONDON W.2. Telephone: 01-723 6963

OPEN MON-SAT 9am-6pm THURS 9am-1pm