


THE

RADIO CONSTRUCTOR

Vol. 25 No. 3

OCTOBER 1971

20p

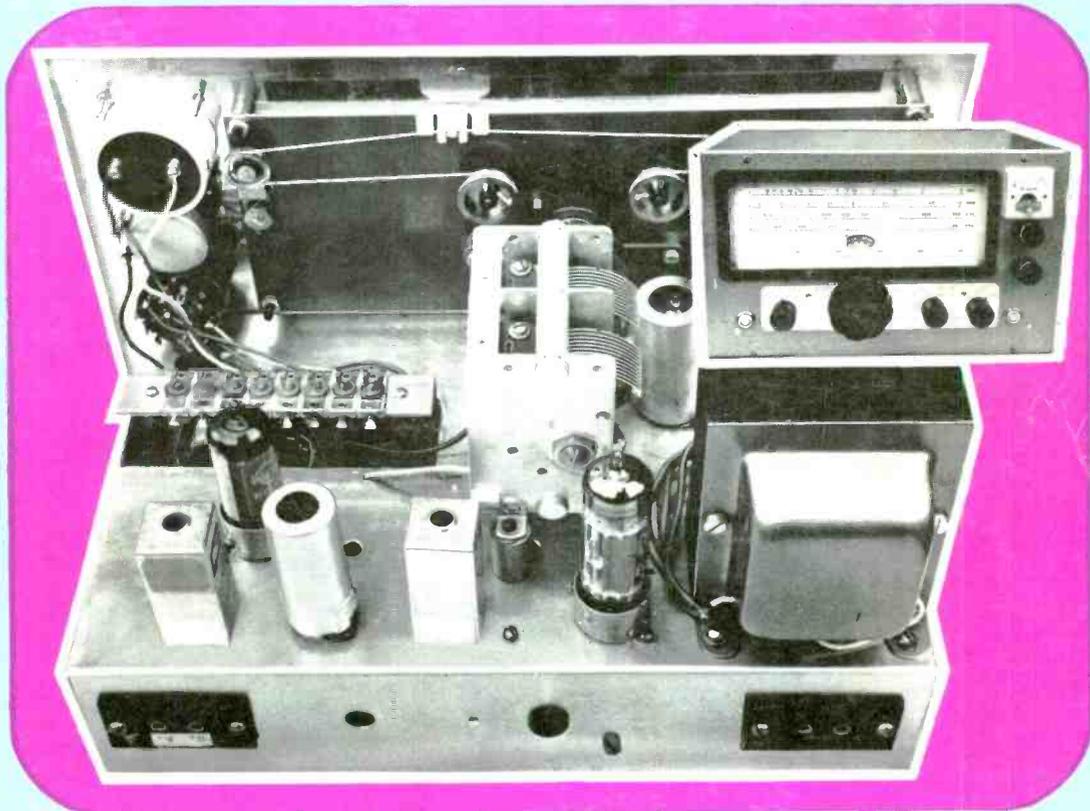


COIL-PACK COMMUNICATIONS RECEIVER - Part 1

Covers long and medium waves as well as
short wave bands from 1.8 to 18.75 MHz.

Special
IN THIS ISSUE

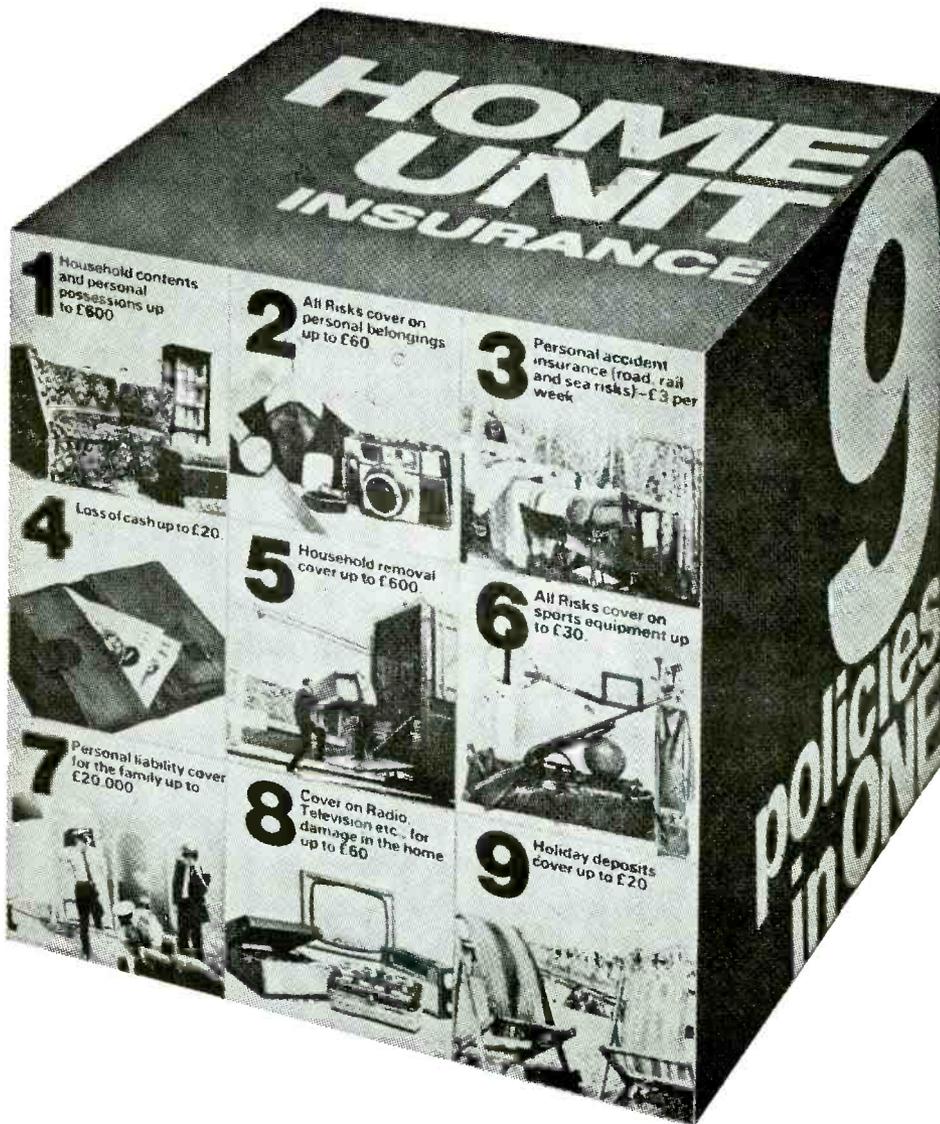SOUND-OPERATED CAMERA FLASH
THE 'MINIFLEX' MARK IV
PORTABLE RECEIVER



1 Household contents and personal possessions up to £800



2 All Risks cover on personal belongings up to £60



3 Personal accident insurance (road, rail and sea risks) - £3 per week



4 Loss of cash up to £20



5 Household removal cover up to £600




6 All Risks cover on sports equipment up to £30



7 Personal liability cover for the family up to £20,000



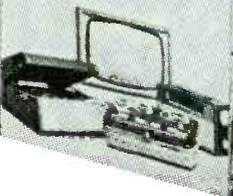8 Cover on Radio, Television etc. for damage in the home up to £60



9 Holiday deposits cover up to £20



Each £3 unit of Home Unit Insurance gives you protection up to the limit shown

This is the simplified insurance you have been waiting for. Not just cover on the contents of your home but a package of personal protection you and your family need. And it's how we save you so much money: just ONE policy to issue instead of nine! You can build up to the cover you need by additional units

(or 1/3 units after the first) up to a maximum of five. So simple. So easy. Apply to your Broker, Agent or local office of a General Accident company. The Home Unit Policy can replace your existing insurances And remember - as you buy more possessions just add more Home Units at any time.

THE YORKSHIRE INSURANCE COMPANY LIMITED

Becket House, 36-37 Old Jewry, LONDON, E.C.2.

It pays to be protected by a **General Accident** company

Please send me further particulars of the Home Unit Insurance.

Name.....

Address.....

REVERBERATION UNIT KIT

6 transistor reverberation chamber to which microphones, instruments, etc., may be connected for added dimensional effect. The output is suitable for most amplifiers and the unit is especially suitable for use with electronic organs. A ready-built spring and transducer assembly is used.



Complete easy-to-build kit, with constructional notes and circuits £7.50. Pre-drilled and printed case £1.70 extra. All parts available separately.

WAH-WAH PEDAL KIT



The Wilsic Wah-Wah pedal comprises a SELECTIVE AMPLIFIER MODULE KIT, containing all the components to build a two transistor circuit module, which may be used by the constructor for his own design or fitted to the FOOT VOLUME CONTROL PEDAL (as photo) converting it to Wah-Wah operation. This pedal is in strong fawn plastic and fitted with output lead and screened plug. Selective amplifier module kit £1.75. Foot Volume control pedal £5.13. COMPLETE KIT £6.50. Add 38p for assembly of module.

THE WILSIC BOOK OF CIRCUITS contains the full instructions for the Reverb unit & Wah-Wah pedal (above) and our Vibrato unit. PRICE ONLY 15p.

WILSIC I-C STEREO AMP

A constructional project to build a Hi-Fi stereo amplifier using INTEGRATED CIRCUITS. 2.7 Watts per channel with full tone controls. The chassis may be built into a simple but attractive veneered cabinet, or into the turntable plinth. Chassis only 10" x 6 1/2" x 2 1/2". COMPLETE KIT £18.50, all parts available separately. Full plans & prices 10p.



SEND 5p in stamps for latest catalogue (Autumn 1971) of Hi-Fi, components, guitars, etc., etc. Friendly, high-speed service.



WILSIC ELECTRONICS LTD.

6 COPLEY ROAD, DONCASTER, YORKS

**A true bargain
by Post:**



**The famous
PA 263**

plus
heatsink/
pc board
for **£1.75!**

The PA263 monolithic audio power amp, provides 3.5W rms, 10W peak, to a 16 ohm load. Ideal for mono or stereo players, tape, disc or intercom amplifiers, FM or AM receivers, Op. Amp. boosters etc.

Now we supply it complete with a specially designed heavy duty pc board ready drilled for PA263 and up to 12 other components (not supplied) all ready for soldering. No other heatsink is necessary. ONLY £1.75 COMPLETE, + p & p £0.15. Or stereo £3.50 plus £0.15 p & p. Delivery by return. FREE 4-PAGE PA263 DATA SHEET PLUS DESIGN INFORMATION WITH ALL ORDERS.

Jermyn Industries,
Vestry Estate, Sevenoaks, Kent.

JERMYN

Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new TECHNATRON Outfit! No mathematics. No soldering—you learn the practical way.

Learn basic Radio and Electronics at home – the fast, modern way. Give yourself essential technical 'know-how' – like reading circuits, assembling standard components, experimenting, building – quickly and without effort, and enjoy every moment. B.I.E.T.'s Simplified Study Method and the remarkable TECHNATRON Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

... and what's more, you will understand exactly what you are doing. The TECHNATRON Outfit contains everything you need, from tools to transistors – even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.

You LEARN – but it's as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build – and it's a good one – is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the springboard for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this Course – but it teaches the real thing. The easy to understand, practical projects – from a burglar-alarm to a sophisticated Radio set – help you master basic Radio and Electronics – even if you are a 'non-technical' type. And, if you want to make it a career, B.I.E.T. has a fine range of Courses up to City and Guilds standards

New Specialist Booklet

If you wish to make a career in Electronics, send for your FREE copy of 'OPPORTUNITIES IN TELECOMMUNICATIONS / TV AND RADIO'. This brand new booklet – just out – tells you all about TECHNATRON and B.I.E.T.'s full range of courses.



FREE

**BRITISH INSTITUTE
OF ENGINEERING
TECHNOLOGY**

Dept. B9, ALDERMASTON COURT, READING RG7 4PF

Accredited by the Council for the Accreditation of Correspondence Colleges.

POST THIS COUPON FOR FREE BOOK

Please send books and full information – free and without obligation.

NAME..... AGE.....
(BLOCK CAPITALS PLEASE)

ADDRESS.....



OCCUPATION.....

To B.I.E.T. Dept B9, Aldermaston Court, Reading RG7 4PF

The largest selection

NEW LOW PRICE TESTED S.C.R.'S.

PIV	1A	3A	7A	10A	16A	30A
	TO-5	TO-66	TO-66		TO-48	TO-48
50	\$0.23	\$0.25	\$0.47	\$0.50	\$0.53	\$1.15
100	\$0.25	\$0.33	\$0.53	\$0.58	\$0.63	\$1.40
200	\$0.35	\$0.37	\$0.57	\$0.61	\$0.75	\$1.60
400	\$0.43	\$0.47	\$0.67	\$0.75	\$0.93	\$1.75
600	\$0.53	\$0.57	\$0.77	\$0.87	1.25	—
800	\$0.63	\$0.70	\$0.90	1.20	1.50	4.00

SILICON RECTIFIERS—TESTED

PIV	300mA 750mA		1A		1.5A		3A		10A		30A	
	\$p	\$p	\$p	\$p	\$p	\$p	\$p	\$p	\$p	\$p	\$p	\$p
50	0.04	0.05	0.05	0.07	0.14	0.21	0.47					
100	0.04	0.06	0.05	0.13	0.16	0.23	0.75					
200	0.05	0.09	0.06	0.14	0.20	0.24	1.00					
400	0.06	0.13	0.07	0.20	0.27	0.37	1.25					
600	0.07	0.16	0.10	0.23	0.34	0.45	1.35					
800	0.10	0.17	0.13	0.25	0.37	0.55	2.00					
1000	0.11	0.25	0.15	0.30	0.46	0.63	2.50					
1200	—	—	0.33	—	0.33	0.75	—					

TRIACS

VBOM	2A	6A	10A
	TO-1	TO-60	TO-86
	\$p	\$p	\$p
100	0.50	0.63	1.00
200	0.70	0.90	1.25
400	0.90	1.00	1.60

2A POTTED BRIDGE RECTIFIERS 200V 50p

UNIJUNCTION
UT745, Eqty. 2N2948, Eqty. TS43, 2BN3000
27p each. 25-99 25p
100 UP 20p.

NPN SILICON PLANAR BC107/8/9, 10P each.
50-99, 8p; 100 up, 8p each; 1,000 off, 7p each. Fully tested and coded TO-18 case.

FREE

One 50p Pack of your own choice free with orders valued \$4 or over.

AP239 PNP GERM. SIEMENS VHF TRANSISTORS. RF MIXER & OSC. UP TO 900 MHz. USE AS REPLACEMENT FOR AP109-AP166 & 100's OF OTHER USES IN VHF. OUR SPECIAL LOW PRICE—1-24 37p each. 25-99 34p each 100+30p each.

FET'S

2N 3819	35p
2N 3820	83p
MPF105	40p

CADMIUM CELLS
ORP12 43p
ORP60, ORP61 40p each

PHOTO TRANS.
OCF71 Type. 43p

SIL. G.P. DIODES 5p
300mW. 50 0.50
40PIV (Min.) 100 1.50
Sub-Min. 500 5.00
Full Tested 1,000 9.00
Ideal for Organ Builders.

D18D1 Silicon Unilateral switch 50p each.
A Silicon Planar, monolithic integrated circuit having thyristor electrical characteristics, but with an anode gate and a built-in "Zener" diode between gate and cathode. Full data and application circuits available on request.

LUCAS SILICON RECTIFIERS

35-Amp. 400 P.I.V., Stud Type £1.10 each.

DIACS FOR USE WITH TRIACS BR100 ... 37p each

ADI61 NPN

ADI62 PNP

MATCHED COMPLEMENTARY PAIRS OF GERM. POWER TRANSISTORS.

For mains driven output stage of Amplifiers and Radio receivers.
OUR LOWEST PRICE OF 63p PER PAIR

2N3055 115 WATT PNP POWER NPN

OUR PRICE 63p EACH

FULL RANGE OF ZENER DIODES VOLTAGE RANGE 2-33V. 400mW. (DO-7 Case) 13p ae. 11W (Top-Hat) 18p ae. 10 W (30 Stud) 25p ea. All fully tested 1% tol. and marked. State voltage required.

BRAND NEW TEXAS GERM. TRANSISTORS

Coded and Guaranteed

Pak No.	Eqvt	Eqvt
T1	8 2G371A	OC71
T2	8 2G374	OC75
T3	8 2G3744A	OC81D
T4	8 2G381A	OC81
T5	8 2G382T	OC82
T6	8 2G344A	OC44
T7	8 2G345A	OC45
T8	8 2G378	OC78
T9	8 2G399A	2N1302
T10	8 2G417	AF117

2N2060 NPN SIL. DUAL TRANS. CODE D1699 TEXAS. Our price 25p each.

Sil. trans. suitable for P.E. Organ. Metal TO-18 Eqvt. ZTX300 5p each. Any Qty.

KING OF THE PAKS Unequaled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	Description	Price
U1	120 Glass sub-min. general purpose germanium diodes	0.50
U2	60 Mixed germanium transistors AF/RF	0.50
U3	75 Germanium gold bonded diodes sim. OA5, OA47	0.50
U4	40 Germanium transistors like OC081, AC128	0.50
U5	60 200mA sub-min. Sil. diodes	0.50
U6	30 Silicon planar transistors NPN sim. BSY9A, 2N706	0.50
U7	16 Silicon rectifiers Top-Hat 750mA up to 1,000V	0.50
U8	50 Sil. planar diodes 250mA, OA/200/202	0.50
U9	20 Mixed volts 1 watt Zener diodes	0.50
U11	25 PNP silicon planar transistors TO-5 sim. 2N1132	0.50
U13	30 PNP-NPN sil. transistors OC200 & 2S104	0.50
U14	150 Mixed silicon and germanium diodes	0.50
U15	25 NPN Silicon planar transistors TO-5 sim. 2N897	0.50
U16	10 3-Amp silicon rectifiers stud type up to 1000 PIV	0.50
U17	30 Germanium PNP AF transistors TO-5 like ACY 17-22	0.50
U18	8 6-Amp silicon rectifiers BY213 type up to 600 PIV	0.50
U19	25 Silicon NPN transistors like BC108	0.50
U20	12 1.5-Amp silicon rectifiers Top-Hat up to 1,000 PIV	0.50
U21	30 A. F. germanium alloy transistors 2G300 series & OC71	0.50
U23	30 Madt's like MAT series PNP transistors	0.50
U24	20 Germanium 1-Amp rectifiers GJM up to 300 PIV	0.50
U25	25 300Mc's NPN silicon transistors 2N708, BSY27	0.50
U26	30 Fast switching silicon diodes like IN914 micro-min	0.50
U28	Experimenters' assortment of integrated circuits, untested. Gates, flip-flops, registers, etc. 8 assorted pieces	1.00
U29	10 1-Amp SCR's TO-6 can up to 600 PIV CRS1/25-600	1.00
U31	20 Sil. Planar NPN trans. low noise amp 2N3707	0.50
U32	25 Zener diodes 400mW DO7 case mixed volts, 3-18	0.50
U33	15 Plastic case 1 amp silicon rectifiers IN4000 series	0.50
U34	30 Sil. PNP alloy trans. TO-6 BCY26, 2S302/4	0.50
U35	25 Sil. planar trans. PNP TO-18 2N2906	0.50
U36	25 Sil. planar NPN trans. TO-6 BFY50/51/52	0.50
U37	30 Sil. alloy trans. SO-2 PNP, OC200 2S322	0.50
U38	20 Fast switching sil. trans. NPN. 400Mc's 2N3011	0.50
U39	30 RF germ. PNP trans. 2N1303/5 TO-5	0.50
U40	10 Dual trans. 6 lead TO-5 2N2060	0.50
U41	25 RF germ. trans. TO-1 OC45 NK772	0.50
U42	10 VHF germ. PNP trans. TO-1 NKT867 AF 117	0.50

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

GENERAL PURPOSE GERM., NPN POWER TRANSISTORS

Coded GP100. BRAND NEW TO-3 CASE. POSS. REPLACEMENTS FOR:—OC25—28—29—30—35—36. NKT401—403—404—405—406—450—451—452—453. T13027—3028, 2N250A, 2N456A—457A—458A, 2N511—511 A & B. 2G290—292, ETC.

SPECIFICATION
V_{CEO} 60V V_{CEO} 50V IC 10A PT 30 WATTS HFE 30-170.
PRICE 1-24 25-99 100 up 43p each 40p each 38p each

GENERAL PURPOSE SILICON NPN POWER TRANSISTORS

Coded GP300. BRAND NEW TO-3 CASE. POSSIBLE REPLACEMENT FOR:—2N3055, BDY20, BDY11.

SPECIFICATION
V_{CEO} 100V, V_{CEO} 60V, IC 15AMPS, PT. 115 WATTS. Hfe 20-100. FTI MHZ.
PRICE 1-24 25-99 100 55p each 50p each 47p each

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM.
TO 2N706.8, BSY27 28/95A. All usable devices no open or short circuits. ALSO AVAILABLE in NPN Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP.

20 For	5p	100 For	17p	1000 For	13.00
50 For	1.00	500 For	7.75		

SILICON PHOTO TRANSISTOR
TO-18 Lens end. NPN Sim.
to BP x 25 & P 21. BRAND NEW. Full data available. Fully Guaranteed.
Qty. 1-24 25-99 100 up. Price each. 45p 40p 35p

RTL MICROLOGIC CIRCUITS
Price each
Epoxy TO-5 case 1-24 25-99 100 up
u1900 Buffer 35p 33p 27p
uL914 Dual 2/1p
gate
uL923 J-K flip-flop 50p 47p 35p
Data and Circuits Booklet for I.C's. Price 7p.

NEW QUALITY TESTED PACKS

Pack	Description	Price
Q1	20 Red spot trans. PNP	0.50
Q2	16 White spot R.F. trans. PNP	0.50
Q3	4 OC77 type trans.	0.50
Q4	6 Matched trans. OC44/45/81/81D	0.50
Q5	4 OC75 transistors	0.50
Q6	4 OC72 transistors	0.50
Q7	4 AC128 trans. PNP high gain	0.50
Q8	4 AC126 trans. PNP	0.50
Q9	7 OC71 type trans.	0.50
Q10	7 OC127/128 comp. pairs PNP/NPN	0.50
Q11	3 AP116 type trans.	0.50
Q12	3 AP117 type trans.	0.50
Q13	3 OC171 H.F. type trans.	0.50
Q15	5 2N3926 sil. epoxy trans.	0.50
Q16	2 GE7860 low noise germ. trans.	0.50
Q17	3 NPN 1 8T141 & 2 8T140	0.50
Q18	4 Madt's 2 MAT 100 & 2 MAT 120	0.50
Q19	3 Madt's 2 MAT 101 & 2 MAT 121	0.50
Q20	4 OC44 germ. trans. A.F.	0.50
Q21	3 AC127 NPN germ. trans.	0.50
Q22	20 NKT trans. A.F. R.F. coded	0.50
Q23	10 OA492 sil. diodes sub-min.	0.50
Q24	8 OA81 diodes	0.50
Q25	6 IN914 sil. diodes 75PIV 75mA	0.50
Q26	8 OA95 germ. diodes sub-min. IN69	0.50
Q27	2 10A 600PIV sil. rect. 1845 B	0.50
Q28	6 Sil. power rect. BYZ13 & 2N697.	0.50
Q29	4 Sil. trans. 2 x 2N696; 2 x 2N697; 1 x 2N698	0.50
Q30	7 Sil. switch trans. 2N706 NPN	0.50
Q31	6 Sil. switch trans. 2N708 NPN	0.50
Q32	3 PNP sil. trans. 2 x 2N1131, 1 x 2N111	0.50
Q33	3 Sil. NPN trans. 2N1711	0.50
Q34	7 Sil. NPN trans. 2N2369, 500MHZ	0.50
Q35	3 Sil. PNP TO-5 2 x 2N2904 & 1 x 2905	0.50
Q36	7 2N3846 TO-18 plastic 300MHZ NPN	0.50
Q37	3 2N3053 NPN sil. trans.	0.50
Q38	7 PNP trans. 4x 2N3703, 3x 2N3702	0.50
Q39	7 PNP trans. 4x 2N3704, 3x 2N3705	0.50
Q40	7 PNP amp. 4x 2N3707, 2x 2N3708	0.50
Q41	3 Plastic NPN TO-18 2N3904	0.50
Q42	6 NPN trans. 2N5179	0.50
Q43	7 BC107 NPN trans.	0.50
Q44	7 PNP trans. 4x BC108, 3x BC109	0.50
Q45	3 BC113 NPN TO-18 trans.	0.50
Q46	3 BC118 NPN TO-5 trans.	0.50
Q47	6 NPN high gain 3x BC167, 3x BC168	0.50
Q48	4 BCY70 NPN trans. T-7-18	0.50
Q49	4 NPN trans. 2x BFY51, 2x BFY52	0.50
Q50	7 BSY28 NPN switch TO-18	0.50
Q51	7 BSY95A NPN trans. 300MHZ	0.50
Q52	8 BY100 type sil. rect.	1.00
Q53	25 Sil & germ. trans. mixed all marked new	1.50

PRINTED CIRCUITS—EX-COMPUTER

Packed with semiconductors and components, 10 boards give a guaranteed 50 trans and 30 diodes. Our price 10 boards, \$50. Plus 10p P & P. 100 Boards £3. P & P. 30p.

TRANSISTOR EQUIVALENTS BOOK. New Edition '71

A complete cross reference and equivalent book for European, American and Japanese Transistors. Exclusive to BI-PAK 90p each

GERM. POWER TRANSISTORS

Type	Price each	Type	Price each
OC20	50p	OC29	40p
OC22	30p	OC25	35p
OC23	35p	OC36	40p
OC25	25p	AD140	40p
OC26	25p	AD142	40p
OC28	40p	AD149	45p

JUMBO COMPONENT PAKS

Mixed Electronic Components. Exceptionally good value (no rubbish) Resistors, capacitors pots, Electrolytics & Coils + many other useful items. Approximately 3 lbs in weight. Price incl. P & P. £1.50 only. Plus our satisfaction or money back guarantee.

OUR STOCKS of individual devices are too numerous to mention in this advertisement. send S.A.E. for our listing of over 1,000 Semiconductors. All available Ex-Stock at very competitive prices.

Dual-in-Line Low Profile Sockets
14 and 16 Lead Sockets for use with Dual-in-Line Integrated Circuits

Order No.	Price each
TS0 14 pin type	1-24 25-99 100 up 35p 27p 25p
TS0 16 pin type	35p 32p 30p

-the lowest prices!

74 Series T.T.L. I.C.'s DOWN AGAIN IN PRICE



Check our 74 Series List before you by any I.C.'s. Our prices are the lowest possible. All devices ex-stock. Full spec. guaranteed.

BI-PAK Order No.	Similar Types to:—Description	Price and qty. prices		
		1-24 2p	25-99 1p	100 up 10p
BP00 - 7400	Quadruple 2-input NAND gate	0.15	0.14	0.12
BP01 - 7401	Quadruple 2-input positive NAND gate (with open collector output)	0.15	0.14	0.12
BP02 - 7402	Quadruple 2-input positive NOR gates	0.15	0.14	0.12
BP08 - 7403	Quadruple 2-input positive NAND gates (with open-collector output)	0.15	0.14	0.12
BP04 - 7404	Hex Inverters	0.15	0.14	0.12
BP05 - 7405	Hex Inverter (with open-collector output)	0.15	0.14	0.12
BP10 - 7410	Triple 3-input positive NAND gates	0.15	0.14	0.12
BP13 - 7413	Dual 4-input Schmitt trigger	0.29	0.28	0.24
BP20 - 7420	Dual 4-input positive NAND gates	0.15	0.14	0.12
BP30 - 7430	8-input positive NAND gates	0.15	0.14	0.12
BP40 - 7440	Dual 4-input positive NAND buffers	0.15	0.14	0.12
BP41 - 7441	BCD to decimal nixie driver	0.67	0.64	0.58
BP42 - 7442	BCD to decimal decoder (4-10 lines, 1 of 10)	0.67	0.64	0.58
BP46 - 7446	BCD-to-Seven-Segment Decoder Driver	2.00	1.75	1.50
BP47 - 7447	BCD-to-seven-segment decoder/drivers (15V outputs)	0.97	0.94	0.88
BP48 - 7448	BCD-to-Seven-Segment decoder Driver	0.97	0.94	0.88
BP50 - 7450	Expandable dual 2-input AND-OR-INVERT	0.15	0.14	0.12
BP51 - 7451	Dual 2-wide 2-input NAND-OR-INVERT gates	0.15	0.14	0.12
BP53 - 7453	Quad 2-input expandable NAND-OR-INVERT	0.15	0.14	0.12
BP54 - 7454	4-wide 2-input NAND-OR-INVERT gates	0.15	0.14	0.12
BP60 - 7460	Dual 4-input expander	0.15	0.14	0.12
BP70 - 7470	Single-phase J-K flip-flop	0.29	0.28	0.24
BP72 - 7472	Master-slave J-K flip-flop	0.29	0.28	0.24
BP73 - 7473	Dual master slave J-K flip-flop	0.37	0.35	0.32
BP74 - 7474	Dual D type flip-flop	0.37	0.35	0.32
BP75 - 7475	Quad latch	0.47	0.45	0.42
BP76 - 7476	Dual J-K with pre-set and clear	0.43	0.40	0.38
BP80 - 7480	Gated full adders	0.67	0.64	0.58
BP81 - 7481	16-bit read/write memory	0.97	0.94	0.88
BP82 - 7482	2-bit binary full adders	0.97	0.94	0.88
BP83 - 7483	Quad full adder	1.10	1.05	0.95
BP86 - 7486	Quad 2-input exclusive NOR gates	0.32	0.30	0.28
BP90 - 7490	BCD decade counter	0.67	0.64	0.58
BP91 - 7491	8-bit shift registers	0.87	0.84	0.78
BP92 - 7492	Divide-by-twelve counters	0.67	0.64	0.58
BP93 - 7493	4-bit binary counters	0.67	0.64	0.58
BP94 - 7494	Dual entry 4-bit shift register	0.77	0.74	0.68
BP95 - 7495	4-bit up-down shift register	0.77	0.74	0.68
BP96 - 7496	6-bit parallel in parallel out shift-register	0.77	0.74	0.68
BP100 - 74100	8-bit bistable latches	1.75	1.65	1.55
BP104 - 74104	Single J-K Flip-Flop equiv. 9000 Series	0.97	0.94	0.88
BP105 - 74105	Single J-K Flip-Flop equiv. 9001	0.87	0.84	0.88
BP107 - 74107	Dual Master Slave Flip-Flops	0.40	0.38	0.38
BP110 - 74110	Gates Master-Slave Flip-Flops	0.55	0.53	0.50
BP111 - 74111	Dual Data Lock-out Flip-Flop	1.25	1.15	1.00
BP118 - 74118	Hex set-reset latches	1.00	0.95	0.90
BP119 - 74119	Hex Set-Reset latches. 24 pin.	1.35	1.25	1.10
BP121 - 74121	Monostable multivibrators	0.67	0.64	0.58
BP141 - 74141	BCD-to-decimal decoder/driver	0.67	0.64	0.58
BP145 - 74145	BCD-to-decimal decoder/driver, O/C.	1.50	1.40	1.30
BP150 - 74153	10-Bit Data Selector	1.80	1.70	1.60
BP151 - 74151	8-bit data selectors (with strobe)	1.00	0.95	0.90
BP153 - 74153	Dual 4-line-to-1-line data	1.20	1.10	0.95
BP154 - 74154	4 to 16 Line Decoder	1.80	1.70	1.60

Devices may be mixed to qualify for quantity prices. Larger quantities—prices on application. (TTL 74 Series only.)

Data is available for the above series of I.C.'s in booklet form. price. 13p.

TTL INTEGRATED CIRCUITS


Manufacturers' "Fall outs"—out of spec. devices including functional units and part function but classed as out of spec. from the manufacturers' very rigid specifications. Ideal for learning about I.C.'s and experimental work.

PAK No.	PAK No.	PAK No.
UIC00 - 12 x 7400N	50p UIC45 - 5 x 7450N 50p	PAK00 - 5 x 7480N 50p
UIC01 - 12 x 7401N	50p UIC50 - 12 x 7450N 50p	UIC80 - 5 x 7482N 50p
UIC02 - 12 x 7402N	50p UIC51 - 12 x 7451N 50p	UIC83 - 5 x 7483N 50p
UIC03 - 12 x 7403N	50p UIC60 - 12 x 7460N 50p	UIC86 - 5 x 7486N 50p
UIC04 - 12 x 7404N	50p UIC70 - 8 x 7470N 50p	UIC90 - 5 x 7490N 50p
UIC05 - 12 x 7405N	50p UIC72 - 8 x 7472N 50p	UIC92 - 8 x 7492N 50p
UIC10 - 12 x 7410N	50p UIC73 - 8 x 7473N 50p	UIC93 - 5 x 7493N 50p
UIC20 - 12 x 7420N	50p UIC74 - 8 x 7474N 50p	UIC94 - 5 x 7494N 50p
UIC40 - 12 x 7440N	50p UIC75 - 8 x 7475N 50p	UIC95 - 5 x 7495N 50p
UIC41 - 5 x 7441AN	50p UIC76 - 8 x 7476N 50p	UIC96 - 5 x 7496N 50p
	UICX1 = 25 x Ass'd 74's £1.50	

Packs cannot be split but 20 assorted pieces (our mix) is available as PAK UICX1. Every PAK carries our BI-PAK Satisfaction or money back GUARANTEE.

ANOTHER BI-PAK FIRST!

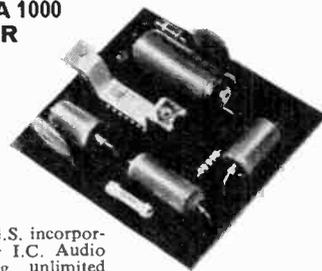THE NEW SGS EA 1000 AUDIO AMPLIFIER MODULE



* GUARANTEED
NO LESS THAN
3 WATTS RMS

Especially designed by S.G.S. incorporating their proven Linear I.C. Audio Amp. TA4621 providing unlimited applications for the enthusiast in the construction of radios, record players, Audio and Stereo units. Also ideal for inter-com systems, monitoring applications and phone answering machines. Other uses: portable applications where supply rails as low as 9V are of prime importance.

- Sensitivity 40 mV for 1 watt Voltage gain 40 dB but can be varied up to 75 dB for some applications.
- Signal to Noise Ratio 80 dB.
- Frequency response better than 50 Hz to 25 KHz for -3 dB.
- Normal supply Voltage 9-24V.
- Suitable for 8-16 ohm loads.
- Overall size 2" x 3" x 1".
- Typical Total Harmonic distortion at 1 Watt less than 1%.

* Supply Voltage (Vs) = 24V 15 ohm load.

Module Tested and Guaranteed.

Qty **1-9** **10-25**
Price each **£2.63** **£2.28**

Larger quantities quoted on request.

Full hook-up diagrams and complete technical data supplied free with each module or available separately at 10p each.

ROCK BOTTOM PRICES!—CAN'T BE BEATEN

LOGIC	DTL 930 SERIES	I.C.'s
Type No.	Function	Price 1-24 25-99 100 up
BP930	Expandable dual 4-input NAND	12p 11p 10p
BP932	Expandable dual 4-input NAND buffer	13p 12p 11p
BP933	Dual 4-input expander	13p 12p 11p
BP935	Expandable hex inverter	13p 12p 11p
BP936	Hex inverter	13p 12p 11p
BP944	Dual 4-input NAND expandable buffer without pull-up	13p 12p 11p
BP945	Master-slave JK or RS	25p 24p 22p
RP946	Quad, 2-input NAND	12p 11p 10p
BP948	Master-slave JK or RS	25p 24p 22p
BP951	Monostable	65p 60p 55p
BP952	Triple 3-input NAND	12p 11p 10p
BP959	Dual Master-slave JK with separate clock	40p 38p 35p
BP9594	Dual Master-slave JK with separate clock	40p 38p 35p
BP9597	Dual Master-slave JK with Common Clock	40p 38p 35p
BP9099	Dual Master-slave JK Common Clock	40p 38p 35p

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series only.)

BRAND NEW LINEAR I.C.'s—FULL SPEC.

Type No.	Case	Leads	Description	Price 1-24 25-99 100 up
BP 201C—SL201C	TO-5	8	G.P. Amp	63p 53p 45p
BP 701C—SL701C	TO-5	8	OP Amp	63p 50p 45p
BP 702C—SL702C	TO-5	8	OP Amp Direct OP	63p 50p 45p
BP 702—72702	D.I.L.	14	G.P. OP Amp (Wide Band)	53p 45p 40p
BP 709—72709	D.I.L.	14	High OP Amp	53p 45p 40p
BP 709P—UA709C	TO-5	8	High Gain OP Amp	53p 45p 40p
BP 711—UA711	TO-5	10	Dual comparator	55p 50p 45p
BP 741—72741	D.I.L.	14	High Gain OP Amp (Protected)	75p 60p 50p
UA 703C—UA703C	TO-5	6	R.F.—I.F. Amp	43p 35p 27p
TAA 263—	TO-72	4	A.F. Amp	70p 60p 55p
TAA 283—	TO-74	10	G.P. Amp	90p 78p 70p

All prices quoted in new pence Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE, HERTS

Postage and packing add 7p. Overseas add extra for airmail. Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back

THE MODERN BOOK CO

COLOUR TELEVISION

PICTURE FAULTS

There are over 120 illustrations, including 88 colour photographs

£2.50

Postage 5p

Q. & A. on Radio and Television
H. W. Hellyer. 60p

Postage 5p

Solid-State Hobby Circuits Manual
R.C.A. £1.05p

Postage 10p

T.V. Technician's Bench Manual
G. R. Wilding. £2.50

Postage 7p

20 Solid State Projects for the Car & Garage
R. M. Marston. £1.20p

Postage 5p

Transistor Audio & Radio Circuits
Mullard. £1.50

Postage 7p

Radio & Audio Servicing Handbook
Gordon J. King. £3.00

Postage 10p

Transistor Substitution Handbook No. 10
Foulsham-Sams. £1.00

Postage 7p

T.V. Fault Finding, 405-625 Lines
J. R. Davies. 50p

Postage 5p

T.V. Servicing Made Easy
Wayne Lemons. £1.75

Postage 7p

Television Servicing Handbook
Gordon J. King. £3.80p

Postage 10p

SCR Manual 4th Ed.
General Electric. £1.25

Postage 10p

Radio Communication Handbook
R.S.G.B. £3.15p

Postage 25p

Amateur Radio Techniques
Pat Hawker. £1.00

Postage 10p

Radio Valve & Transistor Data
A. M. Ball. 75p

Postage 10p

We have the Finest Selection of English and American Radio Books in the Country

19-21 PRAED STREET (Dept RC) LONDON W2 1PN

Telephone 01-723 4185

Give us six months, and we'll turn your hobby into a career.

You have a hobby for a very good reason. It gives you a lot of pleasure.

So if you can find a job that involves your hobby, chances are you'll enjoy your work more, and you'll do better work.

Now CDI can help you find such a job. A job where you'll be responsible for the maintenance of a computer installation. A job that pays well too. If you're interested in mechanics or electronics (without necessarily being a

mathematical genius), have a clear, logical mind and a will to work, then we can train you to be a Computer Engineer inside six months.

So give us a call. CDI. We're the Education Division of one of the world's largest computer manufacturers. And we have the experience to know if you can make it. A ten minute talk with us, and you could be on the way to spending the rest of your life with your hobby.

It's quicker and easier to phone, but if you prefer, send this coupon to: Control Data Institute, Wells House, 77 Wells Street, London, W.1.

Please give me further information.

Name _____

Address _____

Age _____

Phone _____

6/1

**CONTROL DATA
INSTITUTE**

**CONTROL DATA
LIMITED**

The Education Division of one of the world's largest Computer manufacturers.

Ring

01-637 2171

between 9 a.m. and 9 p.m. and ask for Mr Reed

DENCO (CLACTON) LIMITED

355-7-9 OLD ROAD, CLACTON-ON-SEA, ESSEX

Our components are chosen by Technical Authors and Constructors throughout the World for their performance and reliability, every coil being inspected twice plus a final test and near spot-on alignment as a final check

Our General Catalogue showing full product range	... 16p
DTB4 Transistor & Valve circuitry for D.P. Coils	... 16p
DTB9 Valve Type Coil Pack Application circuitry	... 16p
MD.1 Decoder Circuitry for Stereo Reception	... 20p

All post paid, but please enclose S.A.E. with all other requests in the interests of retaining lowest possible prices to actual consumers

RSGB BOOKS FOR YOU

VHF-UHF MANUAL

By G. R. Jessop, C.Eng., M.I.E.R.E., G6JP

2nd edition. Considerably enlarged and revised. Transmitters, receivers and test equipment for use at vhf and uhf are all fully covered on a practical basis in this new edition. **£1.80 post paid**

RADIO COMMUNICATION HANDBOOK

832 pages of everything in the science of radio communication. The Handbook's U.K. origin ensures easy availability of components. Complete coverage of the technical & constructional fields. A superb hard-bound volume. **£3.50 post paid**

A GUIDE TO AMATEUR RADIO

By Pat Hawker, G3VA

Fourteenth edition. 100 pages. The latest edition of this indispensable aid to all who want to know more about amateur radio. Designed to assist the newcomer to this unique hobby. Revised and expanded. **47p post paid**

These are three of a complete range of technical publications, log books and maps, all obtainable from:

RADIO SOCIETY OF GREAT BRITAIN
35 DOUGHTY STREET, LONDON, WC1N 2AE

TOO MUCH STOCK!!



—to list on one advertisement!

Yes, LST would need half this magazine to show their full range.

But 5p for postage will bring you our FREE components catalogue. 44 pages of semiconductors, integrated circuits, passive components, tools, kits, etc., etc.

Send this coupon to:

LST ELECTRONIC COMPONENTS LTD
MAIL ORDER DEPT RC
7 COPTFOLD ROAD
BRENTWOOD
ESSEX

Please send your "cat" to:

Name:

Address:

.....

.....

NEW R.M. BOOKS LOW COST PROPORTIONAL

The theory and practice of simple proportional control systems for models, plus:

- Over a dozen special circuits.
- Theoretical diagrams.
- Component lists.
- Full-size and twice-size practical diagrams.
- Full-size and twice-size Printed Circuit designs.
- Clear description of operation of each.
- Practical application gen.

Build yourself: ● Transmitter ● Coders
● Pulsers ● De-coders ● Switchers
Plus a wealth of ancillary
electro-mechanical items

A really practical book on the updating of single channel control systems to proportional, from the simple rudder-only, to full dual proportional, plus engine control.

ALL THIS GEN FOR ONLY £1.5 (21/-)

Plus 5p. (1/-) postage and packing

THE SINGLETSET

Stage-by-stage instructions to build a . . .

- Single channel transmitter
- Superregen receiver
- Superhet receiver

All clearly illustrated with actual-size and enlarged placement and p.c. diagrams, theoretical circuits, & easy-to-understand "how-it-works" descriptions. Just the thing for modellers starting electronics and electronic hobbyists starting modelling! All in this 16-page booklet - price only 30p (6/-).

Plus postage and packing 2½p. (6d.)

ON SALE NOW at all leading model shops or direct from:-



RADIO MODELLER, BOOK SALES,
64 Wellington Road, Hampton Hill, Middx.
IMMEDIATE DELIVERY

NOW AVAILABLE . . .

LATEST BOUND VOLUME No. 24

of

"The Radio Constructor" FOR YOUR LIBRARY

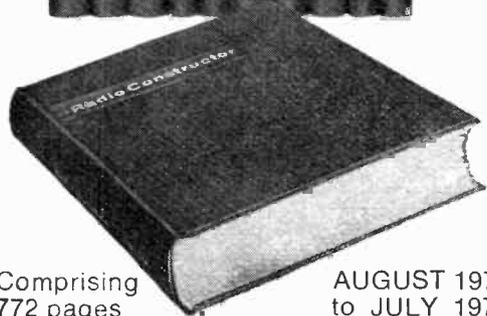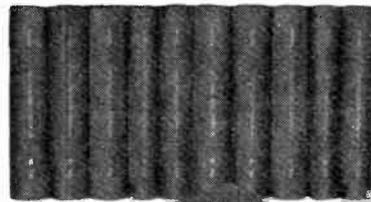

Comprising
772 pages
plus index

AUGUST 1970
to JULY 1971

PRICE £2.00 Postage 28p

BOUND VOLUME NO. 23

OF

**"THE RADIO CONSTRUCTOR"
AUGUST 1969 to JULY 1970**

Limited number of this volume still available

PRICE £1.88 Postage 28p

We regret all earlier volumes are now
completely sold out.

Available only from

DATA PUBLICATIONS LTD.,
57 MAIDA VALE, LONDON, W9 1SN

BI-PRE-PAK LIMITED

FULLY TESTED AND MARKED

AC107	.15	OC140	.17
AC126	.13	OC170	.23
AC127	.17	OC171	.23
AC128	.13	OC200	.25
AC176	.25	OC201	.25
ACY17	.15	2G301	.13
AF139	.13	2G303	.13
AF186	.37	2N711	.50
AF239	.37	2N1302-3	.20
BC154	.25	2N1304-5	.25
BC171		2N1306-7	.30
= BC107	.13	2N1308-9	.35
BC172		BC113	.10
= BC108	.13	Power	
BF194	.15	Transistors	
BF274	.15	OC20	.50
BFY50	.20	OC23	.30
BSY25	.37	OC25	.25
BSY26	.13	OC26	.25
BSY27	.13	OC28	.30
BSY28	.13	OC35	.25
BSY29	.13	OC36	.37
BSY95A	.13	AD149	.30
OC41	.13	AUY10	1.25
OC44	.13	2N3055	.63
OC45	.13	2S034	.25
OC71	.13	Diodes	
OC72	.13	AAY42	.10
OC73	.17	OA95	.09
OC81	.13	OA79	.09
OC81D	.13	OA81	.09
OC139	.13	IN914	.09

CLEARANCE LINES

COLOUR T.V. LINE OUTPUT TRANSFORMERS
Designed to give 25KV when used with PL509 & PY500 valves. As removed from colour receivers at the factory.
NOW ONLY 50p EACH. Post and Packing .25

1 Amp. Plastic Rectifiers. These are voltage, reverse polarity and other rejects from the BY127 range. Ideal for low voltage Power Units, etc. Price: £1 per 100.

BB105 Varicap Diodes	1-10	10-50	50+
OC71 or 72 Fully tested	10	8	6
Unmarked	5	5	4
Matched sets, 1-OC44 & 2-OC45's, Per Set	25	20	15
Matched Sets of OC45's 1st & 2nd IF.	15	12	10
OA47 Gold Bonded Diodes, Marked & tested.	3	3	2
1 Watt Zener Diodes 7.5, 24, 27, 30, 36, 43, Volts	5	4	3
10 Watt Zener Diodes 5.1, 8.2, 11, 13, 16, 24, 20, 100v.	20	17	15
Micro Switches, S/P, C/O.	25	20	15
1 Amp. Brdge Rect. 25v.	25	22	20

INTEGRATED CIRCUITS

SL403D Audio Amp. 3 Watt	2.00	1.95	1.80
709C Linear Opp. Amp.	50	40	35
Gates Factory Marked & Tested by A.E.I.	25	22	20
J. K. Flip Flops Factory Marked & Tested, A.E.I.	40	35	30
PA234 1 Watt Audio Amp.	1.00	90	80
UL914 Dual 2 I/P Gate.	40	35	30

NEW TESTED & GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. 0.3 to 0.5V, 0.5 to 2mA.	50p
B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV 1 amp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitor. Postage 13p. Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Postage 10p. Approx. quantity, counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values. Postage 8p	50p
H8	4	BY127 Sil. Recs. 1000 PIV. 1 amp. plastic	50p
H9	2	OC71 Light Sensitive Photo Transistor	50p
H12	50	NKT155/259 Germ. diodes, brand new stock clearance	50p
H18	10	OC71/75 uncoded black glass type PNP Germ.	50p
H19	10	OC81/81D uncoded white glass type PNP Germ.	50p
H28	20	OC200/1/2/3 PNP Silicon uncoded TO-5 can	50p
H29	20	OA47 gold bonded diodes coded MCS2	50p

FREE! Packs of your own choice up to the value of 50p with orders over £4.

OUR VERY POPULAR 3p TRANSISTORS

FULLY TESTED & GUARANTEED.

TYPE "A" PNP Silicon alloy, metal TO-5 can. 2S300 type, direct replacement for the OC200/203 range.
TYPE "B" PNP Silicon, plastic encapsulation, low voltage but good gain, these are of the 2N3702/3 and 2N4059/62 range.
TYPE "E" PNP Germanium AF or RF - please state on order. Fully marked and tested.
TYPE "F" NPN Silicon, plastic encapsulation, low noise amplifier, of the 2N3707/8, 9, 10, 11 range

BULK BUYING CORNER

NPN/PNP Silicon Planar Transistors, mixed untested, similar to 2N706/6A/8, BSY26-29, BSY95A, BCY70, etc.
£4.25 per 500. £8.00 per 1,000.

Silicon Planar NPN Plastic Transistors, untested, similar to 2N3707-11, etc.
£4.25 per 500. £8.00 per 1,000.

Silicon Planar Diodes, DO-7 Glass, similar to OA200/202, BAY31-36.
£4.50 per 1,000.

NPN/PNP Silicon Planar Transistors, Plastic TO-18, similar to BC113/4, BC153/4, BF153/160, etc.
£4.25 per 500. £8.00 per 1,000.

OC44, OC45 Transistors, fully marked and tested.
500 plus at 8p each. 1,000 plus at 6p each.

OC71 Transistors, fully marked and tested.
500 plus at 6p each. 1,000 plus at 5p each.

3823E Field effect Transistors. This is the 2N3823 in plastic case.
500 plus, 13p each. 1,000 plus, 10p each.

1 Amp. Miniature Plastic Diodes
1N4001 500+ 3p each. 1,000+ 3p each.
1N4004 500+ 5p each. 1,000+ 4p each.
1N4006 500+ 6p each. 1,000+ 5p each.
1N4007 500+ 8p each. 1,000+ 7p each.

NEW UNMARKED UNTESTED PAKS

B80	8	Dual Trans. Matched O/P pairs NPN. Sil. in TO-5 can.	50p
B83	200	Trans. Makers rejects. NPN/ PNP. Sil. & Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202.	50p
B86	50	Sil. Diodes sub. min. IN914 & IN916 types.	50p
B88	50	Sil. Trans. NPN. PNP equivalent to OC200/1, 2N706A, BSY95A, etc.	50p
B60	10	7 Watt Zener Diodes Mixed voltages.	50p
H6	40	250mW. Zener Diode: DO-7 min. Glass Type.	50p
H10	25	Mixed volts 1 1/2 watt Zeners Top Hat type.	50p
B66	150	High quality Germ. Diodes Min. glass type	50p
H15	30	Top Hat Silicon Rectifiers 750mA. Mixed volts.	50p
H16	8	Experimenters' Pak of Integrated Circuits. Data suppd.	50p
H20	20	BY126/7 type Silicon Rectifiers. 1A. plastic to 1,000v	50p

F.E.T. PRICE

BREAKTHROUGH !!!

This field effect transistor is the 2N3823 in a plastic encapsulation coded 3823E. It is also an excellent replacement for the 2N3819. Data sheet supplied with device.
1-10 - 30p, 10-50 - 25p, 50 plus - 20p.

MAKE A REV. COUNTER for your Car. The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a perfectly linear and accurate rev. counter for
£1 each any car.

FREE CATALOGUE AND LISTS for:-
DIODES, INTEGRATED CIRCUITS, TRANSISTORS, RECTIFIERS, FULL PRE-PAK LISTS, & SUBSTITUTION CHART

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE.

8 RELAYS FOR £1

Various Contacts and Coil Resistances. No individual selection. Post and Packing 25p

FREE! A WRITTEN GUARANTEE WITH ALL OUR TESTED SEMICONDUCTORS

BI-PRE-PAK LTD

DEPT. C, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

C
HOME RADIO
HOME RADIO
P
HOME RADIO
HOME RADIO
N
HOME RADIO
E
HOME RADIO
N
T
S

HOME RADIO (Components) LTD.
 Dept. RC, 234-240 London Road,
 Mitcham CR4 3HD. 01-648 8422

**When you think
 of COMPONENTS
 think of HOME RADIO**

Some things in life are just about inseparable – eggs and bacon, sausage and mash, Tweedle Dum and Tweedle Dee! Think of one and you think of the other. That's how thousands of radio and electronic enthusiasts think of Components and Home Radio Ltd. When they need the first they automatically contact the second. They simply flip through their Home Radio Catalogue, locate the items they need and telephone or post their order.

If you have not yet experienced the simplicity and satisfaction of linking Components and Home Radio, why not make a start now? First of all you'll need the catalogue . . . in its 315 pages are listed more than 8,000 components, over 1,500 of them illustrated. Every copy contains ten vouchers, each worth 5p when used as instructed. The catalogue costs 70p including postage and packing. Drop us a line or use the coupon below.

**POST THIS
 COUPON
 with your
 cheque or
 postal order
 for 70p**



Please write your Name and Address in block capitals

Name _____

Address _____

HOME RADIO (COMPONENTS) LTD., Dept. RC,
 234-240 London Road, Mitcham, Surrey CR4 3HD.



**24-hour
 Phone
 Service.
 Ring
 01-648 8422**

Ask for
 details of
 our Credit
 Account
 Service.

The price of 70p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

THE Radio Constructor



Incorporating THE RADIO AMATEUR

OCTOBER 1971

Vol. 25 No. 3

CONTENTS

Published Monthly (1st of Month)
First Published 1947

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9 1SN

Telephone 01-286 6141 Telegrams
Databux, London

© Data Publications Ltd., 1971. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £2.70 (U.S.A. and Canada \$6) including postage. Remittances should be made payable to "Data Publications Ltd." Overseas readers please pay by cheque or International Money Order.

Technical Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that such queries cannot be answered over the telephone; they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production.—Letterpress.

SOUND OPERATED CAMERA FLASH	138
NEWS AND COMMENT	142
WIDE RANGE LOW FREQUENCY SIGNAL GENERATOR	144
SOLID-STATE 'RELAY' (Suggested Circuit No. 251)	151
RECENT PUBLICATIONS	154
REMOVING ELIMINATOR HUM	155
NEW PRODUCT	158
NOW HEAR THESE	159
COIL-PACK COMMUNICATIONS RECEIVER (Part 1)	160
EUROCON '71	168
COMMUNICATION AND ELECTROLYSIS	169
CURRENT SCHEDULES	171
LATE NEWS	171
THE 'MINIFLEX' MARK IV PORTABLE RECEIVER	172
IN YOUR WORKSHOP	179
RADIO CONSTRUCTOR'S DATA SHEET No. 55 (Foreign Language Broadcasts)	iii

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London, W9 1SN.

The Radio Constructor is printed by Kent Paper Company Ltd, London and Ashford, Kent.

**NOVEMBER ISSUE WILL BE
PUBLISHED ON NOVEMBER 1st**

SOUND OPERATED CAMERA FLASH

by

M. G. ARGENT

Intended for use with portable electronic flash guns, this unit is capable of triggering off flash at very low levels of sound

THIS IS AN AID FOR THE PHOTOGRAPHER AND enables him to utilise the high speed of the electronic flash to produce impact-triggered photographs. Due to the fast switching of thyristors, or silicon controlled rectifiers as they are also called, it is now possible to switch apparatus remotely within microseconds of the initial triggering pulse.

CIRCUIT OPERATION


The circuit is given in Fig. 1, and is basically an amplifier used to amplify the monitored sound, and a trigger circuit to operate the electronic flash.


The sound to be monitored is picked up by the crystal microphone (a crystal microphone insert was

used by the author) and amplified by TR1, a high gain common emitter amplifier. C1 is used to block d.c. from the microphone, whilst R9 compensates for microphones having different output levels.

C2 blocks d.c. from RV1. A low noise transistor BC109 is used for TR1, as the overall circuit has a large signal gain, and hence any noise in the first stage will be amplified by TR2 and TR3, with the possibility of spurious triggering off SCR1. This is the reason why RV1 is inserted after TR1, thereby reducing noise at lower settings of required sensitivity.

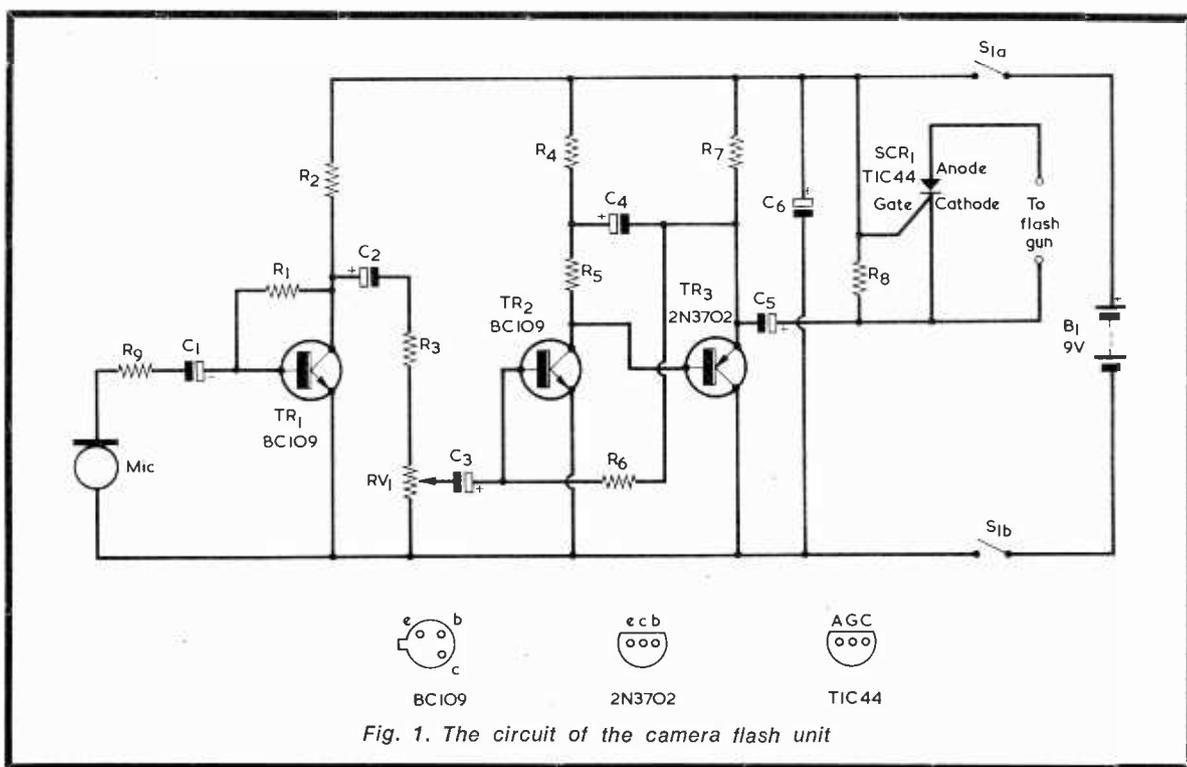The output from RV1 wiper is fed by way of C3 to the base of TR2 which, in turn, is directly coupled to TR3. High gain is achieved by feeding the signal at TR3 emitter via C4 to the junction of R4 and R5.



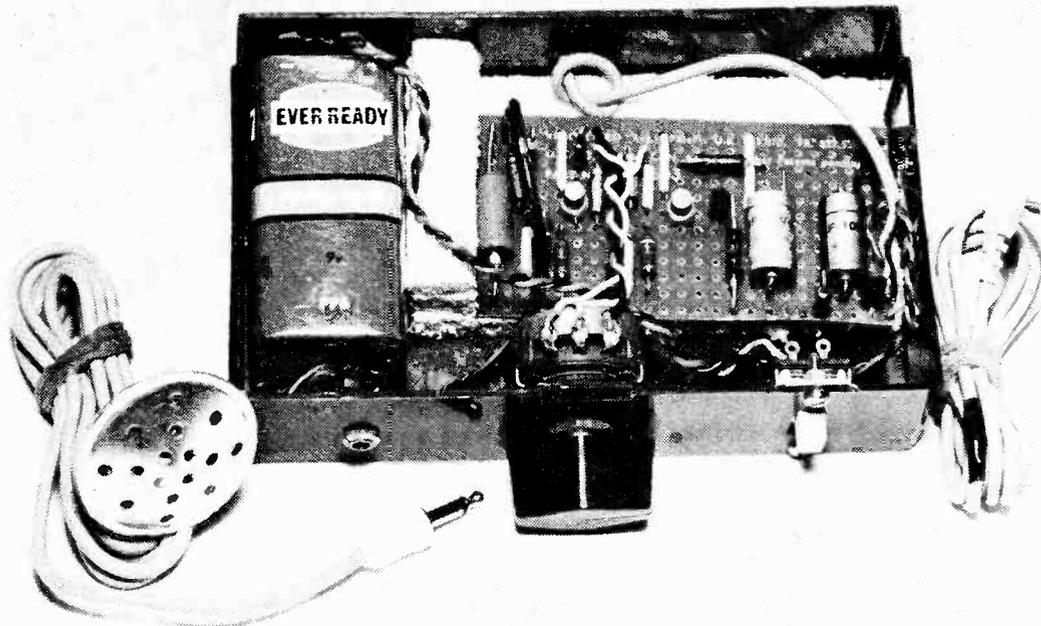

The prototype flash unit. The lead to the flash gun passes through a hole at the rear of the case

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 10%)

R1	270k Ω
R2	5.6k Ω
R3	3.3k Ω
R4	2.2k Ω
R5	4.7k Ω
R6	560k Ω
R7	4.7k Ω
R8	470 Ω
R9	150k Ω
RV1	10k Ω potentiometer, linear

Capacitors

(All capacitors 10V wkg.)

C1	4 μ F electrolytic
C2	4 μ F electrolytic
C3	4 μ F electrolytic
C4	125 μ F electrolytic
C5	200 μ F electrolytic
C6	100 μ F electrolytic

Semiconductors

TR1	BC109
TR2	BC109
TR3	2N3702
SCR1	TIC44

Switch

SI(a)(b) d.p.s.t. slide switch

Battery

B1 9-volt battery

Microphone

MIC1 Crystal microphone or insert

Miscellaneous

Veroboard, 0.15in. matrix, $1\frac{7}{8}$ x $3\frac{3}{8}$ in.
(see Fig. 2)
Miniature jack and plug
Pointer knob
Flash gun extension lead (see text)
Screened lead for microphone
Plastic case, or similar


This feedback is in phase with the signal present at TR2 collector, and hence as the a.c. voltage at both ends of R5 is equal in phase and practically equal in amplitude, little a.c. current will flow through it. This makes the resistance of R5 appear, to a.c., as having a much higher value than the actual resistance, namely $4.7k\Omega$. This technique is known as 'bootstrapping' and gives the circuit a higher voltage gain for a.c. without upsetting the d.c. conditions.

D.C. stability is achieved by biasing TR2 base from TR3 emitter. This, being negative feedback, gives good stability against temperature variations.

The output from TR3 emitter is applied via C5 to SCR1. At first glance the circuit used may seem an unconventional way to trigger a thyristor, but as

the gate and cathode are across R7 so far as a.c. is concerned, it follows that the presence of a signal voltage across R7 of sufficient amplitude will trigger off SCR1. Only positive signals on the gate, with respect to the cathode, will trigger a thyristor, and one might think of using a diode in series with the gate to eliminate the negative signals. However, as no harm will come to the thyristor with their presence, there is no point in including the diode, especially when extra amplification would be required to overcome the voltage drop across it.

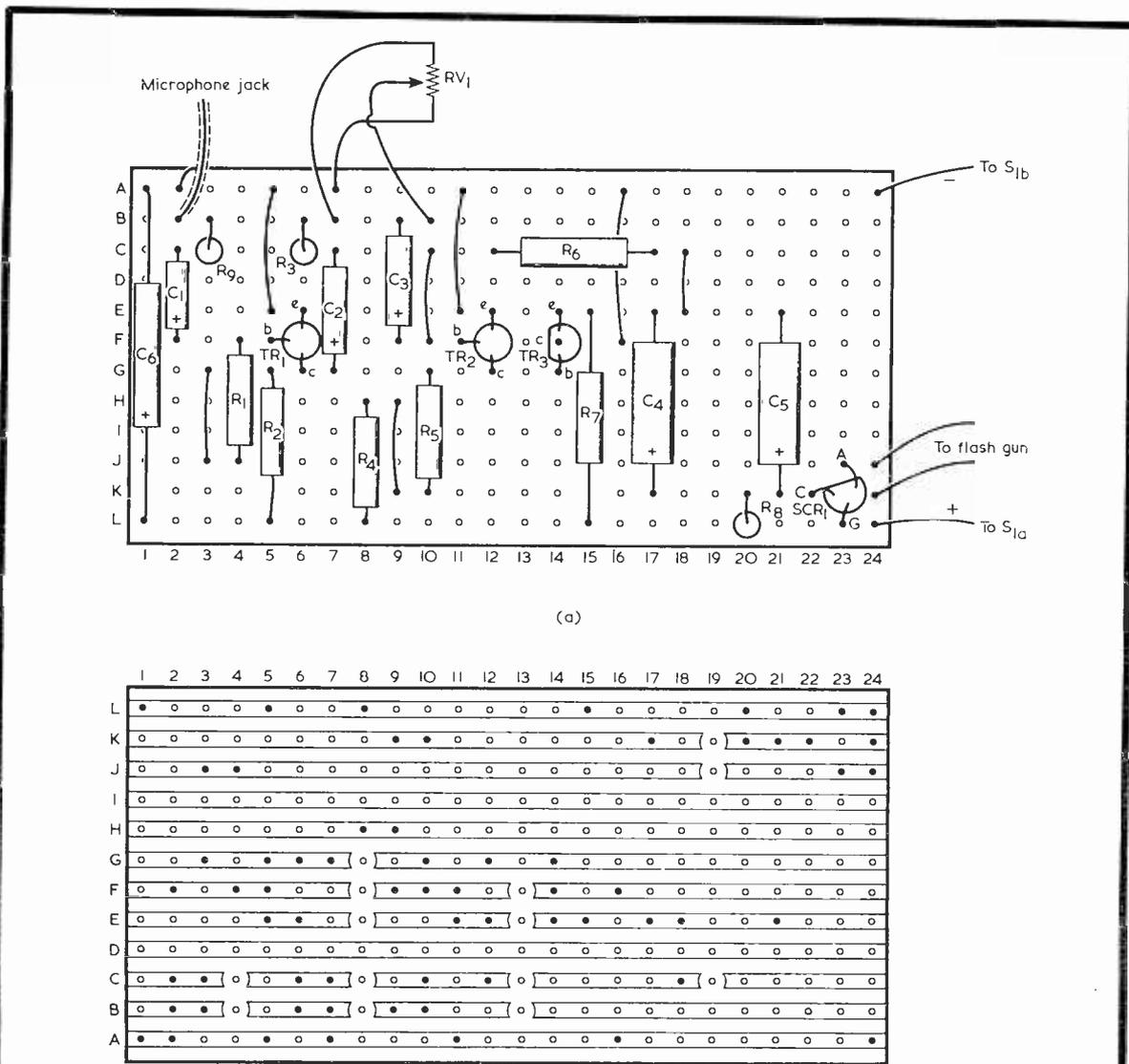The thyristor employed in the prototype is a Texas Instruments TIC44. It was obtained from A. Marshall and Sons Ltd., 28 Cricklewood Broadway, London, N.W.2.



(a)

(b)

Fig. 2(a). Component side of the Veroboard
 (b). The copper side of the Veroboard. The strips are cut at the points indicated

Total current consumption from the 9 volt supply is 4mA.

CONSTRUCTION

No trouble should be experienced in construction if the layout is followed carefully.

The complete unit is built on a piece of 0.15in. Veroboard with 24 holes one way and 12 the other, as shown in Figs. 2(a) and (b). Fig. 2(a) gives the component layout, whilst Fig. 2(b) shows the reverse side and indicates the points where the copper strips are cut. This is done using a small drill or the special spot face tool.

The unit was housed, together with a PP6 battery, in a plastic case measuring $5\frac{1}{2}$ by $3\frac{1}{2}$ by $1\frac{1}{2}$ in. deep, pieces of polystyrene ceiling tile being employed to keep the Veroboard in position. Any similar housing can be used for units built up to the circuit. A miniature phone jack is fitted for the microphone, and the latter couples to the unit via screened lead.

FLASH GUN CONNECTION

The standard portable flash guns available, which plug into the camera for operation off the normal camera shutter, require two terminals of the plug to be short-circuited together to fire the flash. With the present unit this is achieved electronically by the thyristor.

Firstly, an extension lead for flash guns (which is available from most chemists and photograph shops) is purchased. It will be seen that there are male and female connectors at each end of the lead. One of the connectors fits the plug on the flash lead. The connector on the other end of the extension lead is not required and can be cut off, after which the two wires are bared back. What now remains is a lead which plugs into the existing lead on the flash gun, and which has two bare wires at the other end. These two wires are now connected to the thyristor anode and cathode, at holes J24 and K24 of the Veroboard.


For the thyristor to fire, when a signal is present across the gate and cathode, the correct polarity must be applied across the anode and cathode. With the flash gun used for the prototype, the positive lead of the flash gun was the inside contact of the plug, the negative lead being the outer casing. It is the positive lead which is connected to the anode and the negative to the cathode.

If incorrect polarities are connected across the thyristor anode and cathode no harm will result, and the unit will just not operate. The easiest course consists of connecting up the flash gun with the centre contact of the plug to the anode and the outer contact to the cathode, and if the unit does not operate reversing them. An earpiece temporarily connected across R8 will monitor any sound picked up by the microphone, and hence prove that the amplifier section (TR1, TR2 and TR3) is working.

The flash gun used by the writer is the Japanese SUNPAC DC3. This is in no way special, and is readily available. The design is common to the majority of electronic flash guns.

Practically any portable *electronic* flash gun can be operated by the circuit. Bulb type flash units, of the type which require a replacement bulb after every flash, are not suitable due to the high surge current drawn. They could be used if a higher rating thyristor

OCTOBER 1971

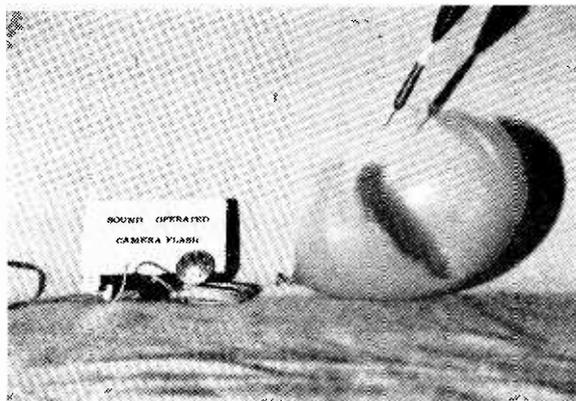

Here, the sound operated flash has enabled the camera to photograph the balloon in the process of bursting

were employed, but this would reduce the sensitivity. Also, their speed is very slow compared with the electronic versions, which operate within one thousandth of a second.


TESTING

Always remember to switch the unit on before connecting the flash gun, as there may be a spurious operation of the flash during switch-on.

Two of the accompanying photographs show the unit in operation. In one photograph, the flash operated at a suitable time to catch the balloon collapsing.

The other photograph of the balloon, in which the balloon is still intact, gives an ideal example to emphasise the speed of the unit. In this picture the microphone was placed near the balloon and the unit set up so that the flash operated at the slightest sound. Note that the flash fired as soon as the dart touched the balloon, even before the balloon had a chance to burst.

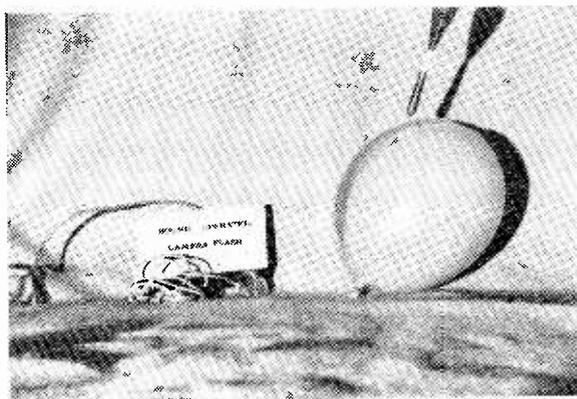On maximum sensitivity, the prototype operated at the flick of the fingers from the other side of the room.




At a higher sensitivity setting, the camera photographs the dart as it enters the balloon

EDITOR'S NOTE

It should be pointed out that the author has applied for a patent on the device described in this article. ■

HIGH QUALITY LOW COST SWITCHES

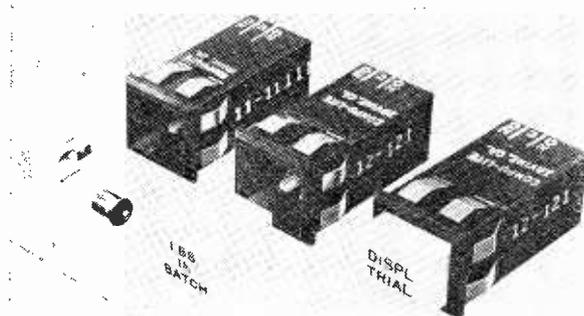

Competitively priced yet with many features previously associated only with high priced products, a new range of illuminated multi-pole Compu-Lite Series 11 push button switches from Guest International Limited of Brigstock Road, Thornton Heath, Surrey, are ideal for use in virtually any application from computer systems to domestic appliances.

Designed for front panel fixing they are fully enclosed and sealed and switch up to 5A at 250V. Typical life is 2 million switching operations and each switch is programmable in that one pole is switched in before the remaining poles make contact – a particularly desirable feature in communications and digital applications. Special gold contacts are available for low-level switching.

Versatility within the range enables a wide range of coloured bezels and screen split or full legends to be supplied, and a number of different switching actions is also available.

Where space is at a premium, a useful feature of the complete Compu-Lite range is the very small amount of space taken up behind the panel – maximum depth is only 1½ in. All Series 11 switches can be made available with AMP-type terminals.

VARTA INTRODUCE RANGE OF TRANSISTOR RADIO BATTERIES TO U.K.

VARTA AG, one of the largest battery manufacturers in Europe, with a new marketing subsidiary company in the U.K., namely VARTA Batteries Limited, announce the introduction of several new battery types, for transistor radio and other applications, to their range.

These batteries made in West Germany are high quality products with high performance being a major characteristic.

Specially designed for power demanding equipment, the four transistor radio battery types have exceptionally long life. Developed in Hanover and Stuttgart, to compete with Europe's best, the exceptional qualities of these VARTA batteries have already established their popularity in Europe.

They are factory sealed and arrive by fast container service via Rotterdam and Harwich. Attractive-

THE COMPUTER AND EDUCATION

Much is being done in the field of computers and their relevance to education, and the value of computer-aided instruction is now generally appreciated and the potential of the next step, computer-managed instruction, is now being recognised. Therefore, it is not surprising to find the computer and its educational uses the central theme of the British Computer Society's 1971-72 Educational Yearbook.

The section on computer-aided instruction and computer-managed instruction commences with a paper by Dr. A. Molnar, National Centre for Educational Research and Development, United States Office of Education, Washington.

Monsieur J. Donio, Director of Research, Institut de Recherche en Information et en Automatique, Paris, considers the growth of computers in world markets and how they have affected our lives; so making the point that the computer must become an integrated part of our educational activity.

Dr. K. Zinn, Centre for Research on Learning and Teaching, University of Michigan, shows how the small number of instructional programming languages that existed five years ago have expanded into at least forty different dialects!

In addition to all the information on computer-aided instruction, the BCS Educational Yearbook also contains standard reference sections on: the educational activities of the BCS Regional Boards; the development of the BCS qualifications; a list of computer courses offered by schools, colleges, universities and private organisations; a comprehensive coverage of all educational activities of the International Federation for Information Processing.

Educational Yearbook 1971-72 is published by The British Computer Society, 29 Portland Place, London, W1N 4AP, price £1.75 plus 25p post and package.

ly designed and presented, they will easily be recognised by the familiar blue and yellow label that has already established VARTA batteries in the United Kingdom.



THE RADIO CONSTRUCTOR

COMMENT

IN BRIEF

● British radio communications systems costing over £100,000 are to be installed in helicopters operating in the Italian mountains by the Carabinieri.

The order was recently placed by the Italian Government with Marconi-Elliott Avionic Systems and will be built at Basildon, Essex.

● A.P.T. Electronic Industries Ltd., of Chertsey Road, Byfleet, Surrey have produced a leaflet on their multi-socket Distribution Panel, LKU-413, a recent addition to their well-known Letrokit range. Copies of the leaflet which gives full technical data are available on request.

● Stephen Hearst, who as Head of Arts Features for BBC Television was responsible for the award-winning series 'Civilisation', has been appointed Controller of Radio 3.

● Nigerian short wave transmitters will be using the prefix 5N5 during October, in commemoration of the 11th Anniversary of Independence. Stations expected to be active are: 5N2AAE: AAJ: AAK: AAV: AAU: ABG: and ABH. It is hoped that 5N5BSN (Scouts) will be active during the Jamboree week-end.

● The Independent Television Authority's first VHF local relay station has been brought into programme service at Pendle Forest, Lancashire. This station will improve the reception of Granada 625-line colour/black-and-white programmes for about 150,000 people living in Nelson, Colne and parts of Burnley.

The ITA plans to build about 450 local relay stations over the next eight years to supplement the coverage of main high-power UHF stations.

● A course on evening lectures on video recording systems commences at Norwood Technical College, Knight's Hill, London, S.E.27 on 19th October. Course Fee is £2.

● The first holder of EMI's Research Fellowship in electronic engineering, Dr. Donald E. Hirst, B.Sc., Ph.D., recently completed three years of his appointment at Brunel University, Uxbridge, Middlesex. To mark the occasion, Dr. Hirst gave a presentation of some of the university's research topics to EMI scientists and senior staff during a day long seminar at the university.

● There will be a London Area Rally for model aircraft enthusiasts who are members of the S.M.A.E. and R.A.F.M.A.A., on 17th October at R.A.F. Wyton, Nr. St. Ives, Huntingdonshire. For details of the radio control event sent S.A.E. to M. Dilly, 20 Links Road, West Wickham, Kent.


● The Millbank Electronics Group, manufacturers of audio and communications equipment, have moved to a new 5,000 sq. ft. factory and administrative headquarters at Bellbrook Estate, Uckfield, Sussex. Tel: Uckfield (0825) 4166.

● Sir Martin Ryle, Director of the Mullard Radio Astronomy Laboratory, has been awarded one of the Institute of Electrical and Electronics Engineers highest honours, the Martin N. Liebmann Award.

The award was made for his application of aperture synthesis to extend the capabilities of radio telescopes.

OCTOBER 1971

HEATHKIT AR-2000 TUNER-AMPLIFIER

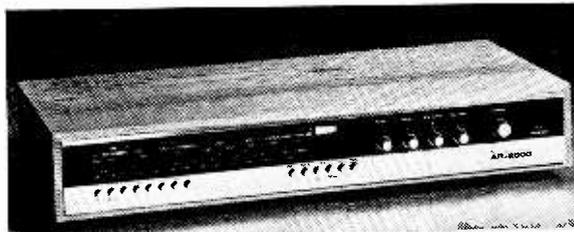

Heath (Gloucester) Limited announce an outstanding new Tuner-Amplifier kit. Designated Model AR-2000 this Tuner-Amplifier has been designed by Heath (Gloucester) Limited especially for the British and European Hi-Fi markets.

Its main features are listed here:-

Output power 20 watts r.m.s. per channel
LW, MW, SW, and FM stereo

All solid-state

Completely new styling

F.E.T. front end F.M. Tuner


I.C. stereo decoder.

FM IF uses I.C.'s and ceramic filters

With this specification and direct-from-factory kit price of only £89.90 plus £7 for a teak or walnut cabinet this is clearly an exciting new addition to the well known Heathkit range of hi-fi equipment. This kit, like all Heathkit products, includes an extremely comprehensive construction manual, making it easy to build the kit without the need for any technical knowledges or special skills.

For further details write to:-

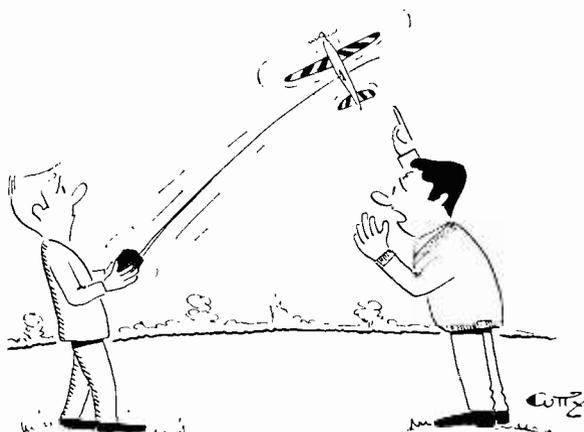Heath (Gloucester) Limited, Bristol Road, Gloucester GL2 6EE.



"You're flying it too low!"

WIDE RANGE LOW FREQUENCY SIGNAL GENERATOR

by

P. CAIRNS, M.I.P.R.E., R.Tech.Eng., G31SP


Incorporating thermistor stabilisation, this Wien bridge circuit offers a constant amplitude sine wave output at frequencies from 15Hz to 150kHz in four switched ranges. An oscilloscope is required for calibration if the latter is to be precise, whilst rough calibration can be carried out with the aid of the graph given

THIS ARTICLE DESCRIBES AN EXTREMELY WIDE range l.f. transistor signal generator. Its principal features are wide frequency coverage in four decade steps, good frequency stability and waveform, simple construction at moderate cost, and internal battery operation. Other features are extremely compact layout using standard components, ample output voltage for most test purposes, and very low output impedance with constant amplitude control over the whole frequency range. The specification is given in Table I.

CIRCUIT OPERATION

As can be seen from the circuit diagram of Fig. 1 and the Components List, the instrument uses the minimum number of components consistent with good specification and reliable performance. The circuit is basically a Wien bridge oscillator with emitter follower output. To function correctly the Wien bridge circuit must meet certain requirements. Such a circuit consists of a very high gain amplifier, which must have high input impedance and low output impedance with R-C coupling between output and input to provide the positive feedback necessary to maintain oscillation. The time constants of this feedback are usually made of a variable nature to provide variations in frequency of oscillation. The gain of the amplifier must also be substantially independent of frequency over the range of operation envisaged. This entails a very low output impedance so that the shunting effect of the R-C feedback network has negligible effect on the output. Again, the high input impedance is required to prevent the bridge network being loaded by the amplifier. Also, the phase shift through the amplifier must be strictly controlled so as to maintain oscillation over the complete frequency range. The total phase shift over the complete amplifier and bridge circuit must always be zero or a multiple of 2π radians.

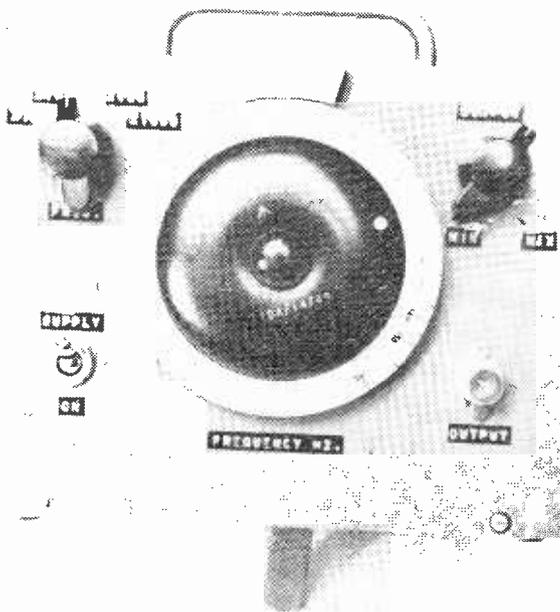These requirements are met by the circuit shown in Fig. 1. TR1 and TR2 form the first stage of the amplifier, these being connected as a Darlington or super-alpha pair so as to achieve a very high gain, R3 being the load resistor. The output from this stage is d.c. coupled into the base of TR3 which forms the



Front view of the signal generator. An ex-W.D. dial and drive were used for the prototype

THE RADIO CONSTRUCTOR

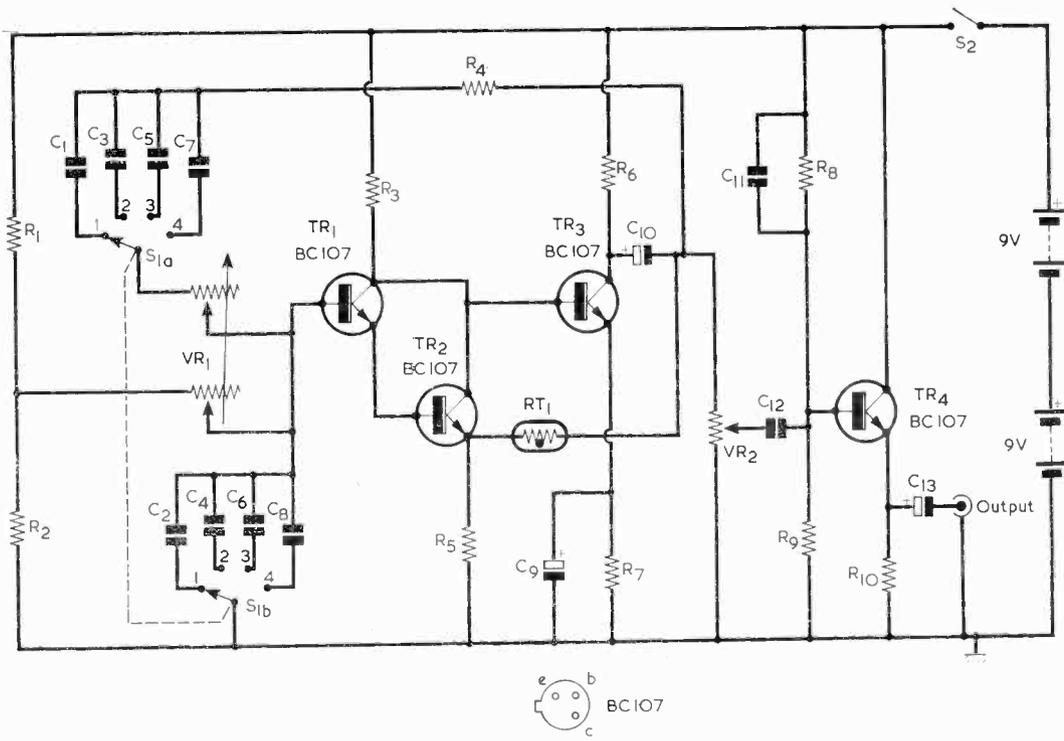


Fig. 1. Circuit diagram of the wide range I.f. signal generator

COMPONENTS

Resistors

(All fixed values $\frac{1}{2}$ watt 5%)

- R1 4.7k Ω
- R2 620 Ω
- R3 2.7k Ω
- R4 1.8k Ω
- R5 270 Ω
- R6 470 Ω
- R7 820 Ω
- R8 33k Ω
- R9 33k Ω
- R10 1k Ω
- VR1 10k Ω + 10k Ω twin gang potentiometer, log
- VR2 10k Ω potentiometer, linear

Thermistor

- RT1 S.T.C. type R54 (Henry's Radio Ltd.)

Capacitors

- (See text for tolerances of C1 to C8)
- C1 1 μ F polyester or polycarbonate
 - C2 1 μ F polyester or polycarbonate
 - C3 0.1 μ F polyester or polystyrene
 - C4 0.1 μ F polyester or polystyrene
 - C5 0.01 μ F polyester or polystyrene
 - C6 0.01 μ F polyester or polystyrene

- C7 1,000pF silver-mica
- C8 1,000pF silver-mica
- C9 100 μ F electrolytic, 12V wkg
- C10 100 μ F electrolytic, 12V wkg
- C11 470pF silver-mica or ceramic
- C12 2.2 μ F Mullard miniature foil
- C13 100 μ F electrolytic, 25V wkg

Transistors

- TR1 - TR4 BC107 (Mullard)

Switches

- S1(a)(b) 2-pole 4-way Yaxley
- S2 s.p.s.t. toggle

Batteries


- 2-off 9-volt batteries type PP7 or equivalent

Miscellaneous

- Veroboard, 0.15in. matrix (see Fig. 3)
- Coaxial socket
- 2-off pointer knobs
- Drive and dial (slow-motion or direct as required)
- Material for panel, chassis, struts and brackets
- Cabinet type W, 8 x 6 x 6in. (H. L. Smith & Co. Ltd.)

second stage of the amplifier. The d.c. coupling between stages prevents unwanted phase shift. R6 is the final load resistor, the output being taken from this via the blocking capacitor C10. The emitter resistor R7 is bypassed by C9 to maintain the overall stage gain. A small measure of voltage feedback is applied to the emitter of the first stage via the divider network given by R5 and RT1. RT1 is a thermistor whose resistance varies inversely with the current flowing through it. This allows amplitude control to be maintained and also keeps the circuit stable under varying conditions of frequency change. The action of the thermistor is therefore extremely important to the functioning of the circuit as a whole.

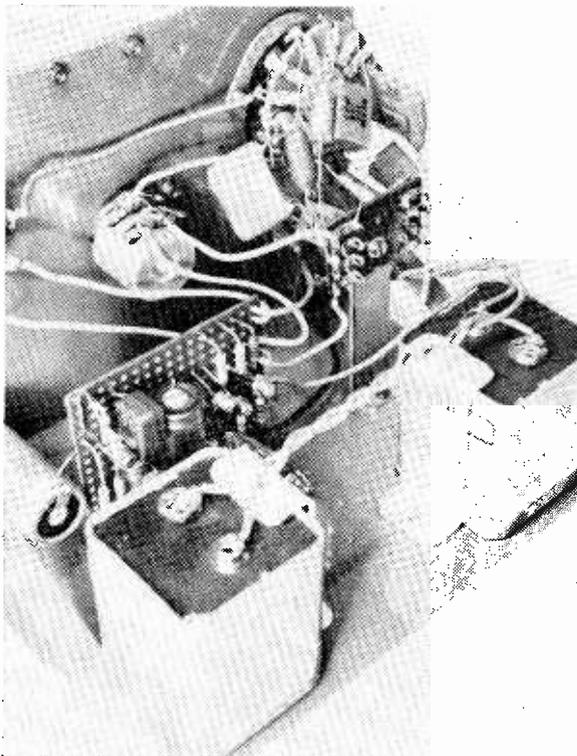Feedback is also applied from the same C10 output via R4 to the principal bridge network consisting of VR1 and C1 to C8, these all being variable and thus providing the wide range of frequencies covered.



Rear view of the generator. Note the capacitors connected between the range switch and the tagboard behind it

Correct d.c. working conditions for the first amplifier stage are also provided by divider R1 and R2, and as these components are interconnected with the bridge network they also affect the frequency of oscillation. Following conventional practice, fine frequency shift control is the function of the twin gang potentiometer VR1, while the coarser ranges, in this case decade steps, are selected by means of switched capacitors C1 to C8 in the alternate limbs of the bridge network. By using logarithmic potentiometers for VR1 the normal non-linear exponential type of scale which would result from a C and linear R time

constant is obviated and a more even overall calibration scale is obtained.

The signal output is also taken from C10 to the amplitude control VR2, then via the blocking capacitor C12 to the base of the emitter follower output stage, TR4. The purpose of this stage is to provide a very low output impedance while presenting a reasonably high input impedance to the amplifier output circuit. It thus performs the function of an impedance matching circuit, isolating the final output and load from the actual oscillator circuit. R8 and R9 form a d.c. divider for the base of TR4, C11 being included for h.f. compensation. The final output signal is developed across the emitter load R10 while C13 provides d.c. blocking to the output socket.

The d.c. supply, which is isolated by S2, is obtained from an internal battery supply. Two batteries of the type used for transistor radios are connected in series. Types PP7, RR7, VT7 or similar are quite suitable, the current drain being only in the 25mA region.

TABLE I

Specification

Frequency coverage:	15Hz to 150kHz in four decade steps.
	Range 1, 15Hz – 150 Hz.
	Range 2, 150Hz – 1,500Hz.
	Range 3, 1.5kHz – 15kHz.
	Range 4, 15kHz – 150kHz.
Stability:	Change in frequency for $\pm 10\%$ change in supply voltage is less than 1%.
Output:	5 volts peak-to-peak ± 1 db over entire frequency range; continuously variable from zero.
Output impedance:	Less than 500 Ω .
Supply:	18 volts d.c., 25mA, from internal batteries.
Dimensions:	8in. wide, 6in. high, 6in. deep.

CALIBRATION ACCURACY

A single dial calibration is used for all four ranges. The accuracy of the calibration on individual ranges will naturally depend on the accuracy of capacitors C1 to C8 and also the accuracy of matching between similar pairs. While 5% types have been specified, 1% or 2% types are naturally preferable, though they are of course more expensive. If a capacitor measuring bridge is available, capacitors which are low in value can always be "padded up" by the addition of smaller values in parallel. The 5% tolerance specified should prove adequate for most everyday applications, however. If high accuracy is essential, the only answer is the use of more expensive higher tolerance components. In this respect it may be added that all the capacitors specified for C1 to C8 are available from Home Radio at 1% tolerance, whilst the 0.1 μ F and 0.01 μ F values are also available at 5% tolerance.

The extent of overlap on each range is controlled by R4. The value quoted for R4 should provide an overlap of approximately 10 to 15% using average components in the bridge network. Should the range overlap be not quite unity or if a larger overlap between ranges is required, a slight adjustment to the

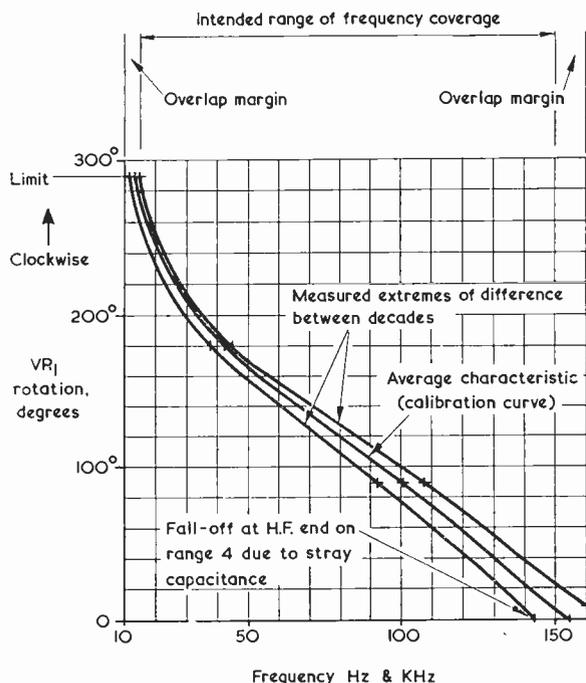


Fig. 2. Calibration curves for frequency versus rotation in VR1, as obtained with the prototype

value of R4 will effect the necessary alteration. Reducing R4 gives a wider range of overlap and vice versa.

The curves in Fig. 2 show frequency versus rotation of VR1 in the basic circuit as calibrated, together with the minimum and maximum calibration errors and deviations encountered between ranges due to differences in tracking. The actual tolerances on capacitors used by the writer, and with which the curves were made, were measured. They are as follows: Range 1, $1\mu\text{F}$, -3% and -4% ; Range 2, $0.1\mu\text{F}$, -0.02% and -1.5% ; Range 3, $0.01\mu\text{F}$, $+3.5\%$ and -0.5% ; Range 4, $1,000\text{pF}$, -0.25% and -0.1% .


The actual range of the generator can be extended to at least a further decade if required (i.e. up to 1.5MHz). The only drawback is that the existing calibration scale would no longer be accurate as the range and spread would become effectively smaller due to

the increased effect of stray and self capacitance in relation to bridge capacitance. This fall-off in frequency due to stray and self capacitance is already slightly noticeable at the upper end of Range 4, at 150kHz . This can be seen in the curves in Fig. 2 and in the list of measured frequency limits given in Table II. To maintain accurate calibration another scale would very likely be required for the fifth decade if it were added. It may be of interest however that the writer has had the circuit working in excess of 4MHz . It therefore offers plenty of scope for those who like to experiment a little.

CONSTRUCTION

The construction of the instrument is quite straightforward and should offer no difficulties. All components except the switched bridge capacitors and C13 are mounted on a piece of 0.15in. Veroboard approximately $2\frac{1}{4}$ by $2\frac{1}{2}\text{in.}$ This makes construction much simpler and neater while also helping to standardise the final result with regard to specification. The Veroboard layout with full details is given in Fig. 3. Outgoing flyleads should be soldered to the appropriate points before the board is mounted vertically to the chassis by means of a small aluminium angle bracket. Strip M is at the bottom and, since this is at chassis potential, it may be in contact with the angle bracket.

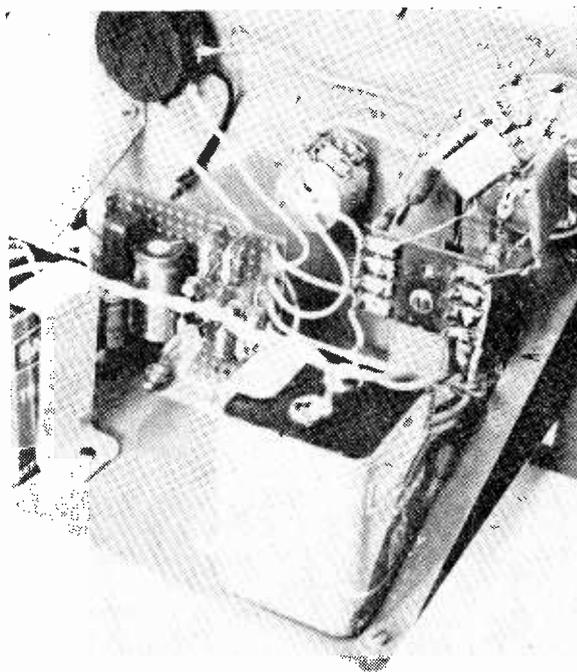The chassis can be simply made from a piece of aluminium sheet with a lip bent along the front edge for mounting to the front panel. Side struts can be fixed between front panel and chassis for added



Another view of the rear. The thermistor may be seen between the two batteries

TABLE II

Voltage and Frequency Measurements

(All voltage readings on $20\text{k}\Omega$ per volt meter with respect to negative line.)

Supply: 18V . Current drain: 24.7mA .

TR1: emitter 1.6V ; base 1.9V ; collector 8.8V .

TR2: emitter 0.9V ; base 1.6V ; collector 8.8V .

TR3: emitter 8.3V ; base 8.8V ; collector 13.55V .

TR4: emitter 7.85V ; base 8.15V ; collector 18V .

Minimum and maximum frequencies measured:

Range 1, $14.5\text{Hz} - 162\text{Hz}$;

Range 2, $135\text{Hz} - 1,570\text{Hz}$;

Range 3, $1.325\text{kHz} - 15.5\text{kHz}$;

Range 4, $12.75\text{kHz} - 145\text{kHz}$.

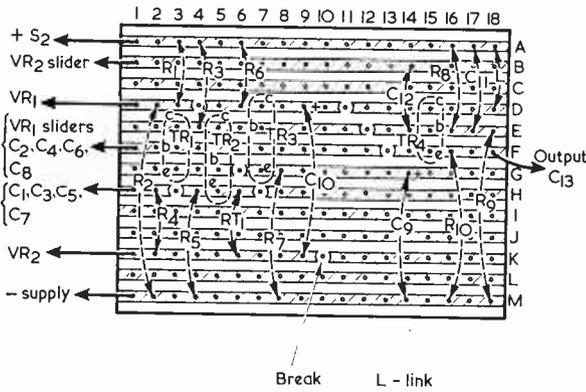


Fig. 3. The Veroboard layout, as seen looking at the copper side of the board

strength. Fig. 4 shows the complete chassis layout, together with all relevant dimensions. The bridge capacitors are connected directly between the switch contacts and a tag strip or tagboard mounted above the chassis by means of a bracket. C13 is connected directly between the Veroboard and the output socket. The two 9-volt batteries are mounted on the rear of the chassis, simple retaining clips being made from a strip of aluminium.

The front panel should be drilled and have all panel components fitted before being mounted into position. Front panel details and dimensions are given in Fig. 5. The type of dial and drive assembly used is a matter of individual choice. While a simple direct drive with pointer scale is quite adequate, a good-quality slow-motion drive with a complete dial assembly is much better though, of course, more expensive. The author employed a surplus slow-motion dial, its scale being calibrated from 14 to 155. The positions of the decade switch, S1, are designated "X1", "X10", "X100" and "X1000".

Interconnecting wires should be as short and direct as possible. One point which requires mention is the wiring of VR1, this being a logarithmic type potentiometer. This component should be wired up with the common junction from the base of TR1 connecting to the two centre tags (wiper arms) of VR1, and with the two separate connections from S1(a) and the junction of R1 and R2 passing to the open end of each potentiometer track which, with standard log potentiometers, is at the anti-clockwise end of rotation. These connections can be seen in Fig. 4. This method of connection helps to obviate the cramped exponential type of scale calibration which would result if linear potentiometers were used. When wired up as described, the control and dial should give an increase in frequency when rotated anti-clockwise. The layout and appearance of the completed instrument can be clearly seen in the photographs.

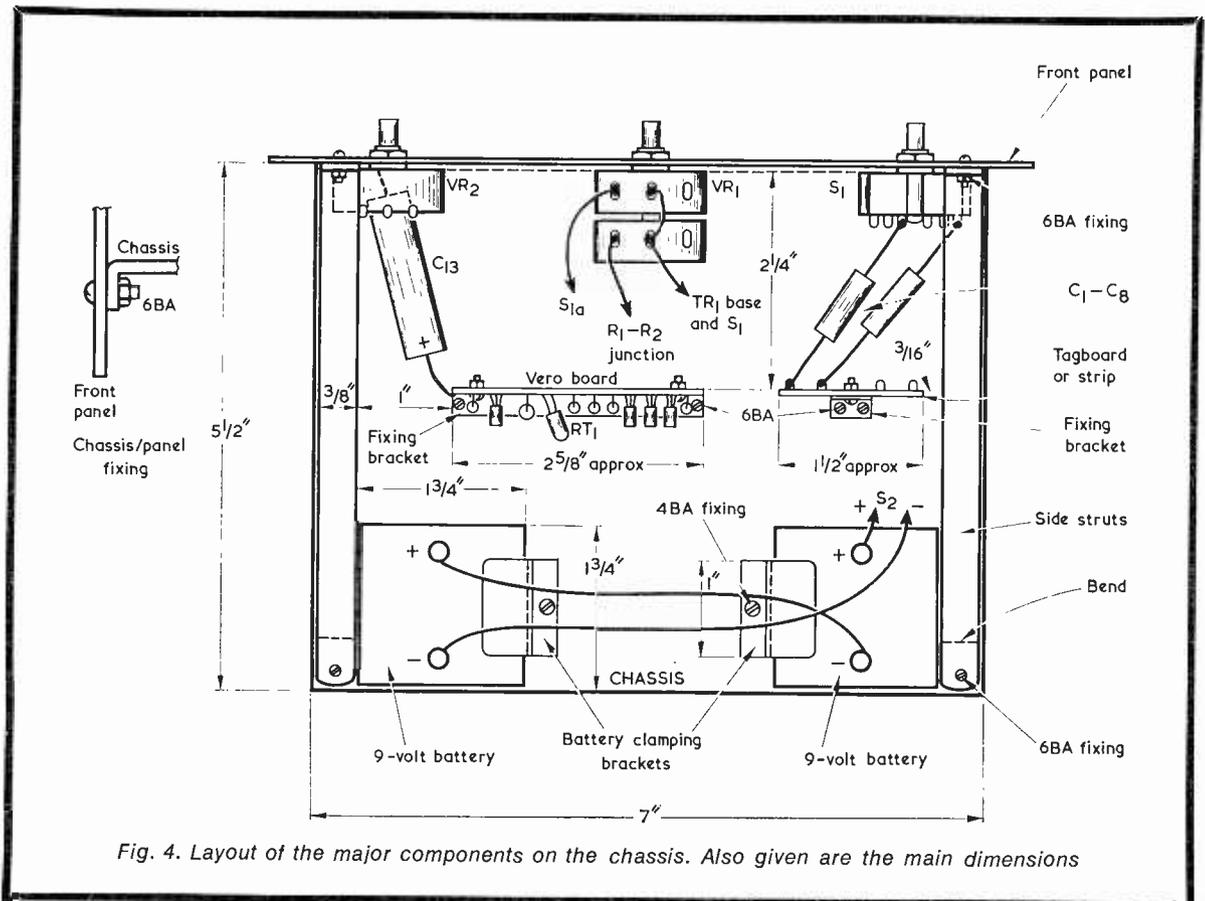


Fig. 4. Layout of the major components on the chassis. Also given are the main dimensions

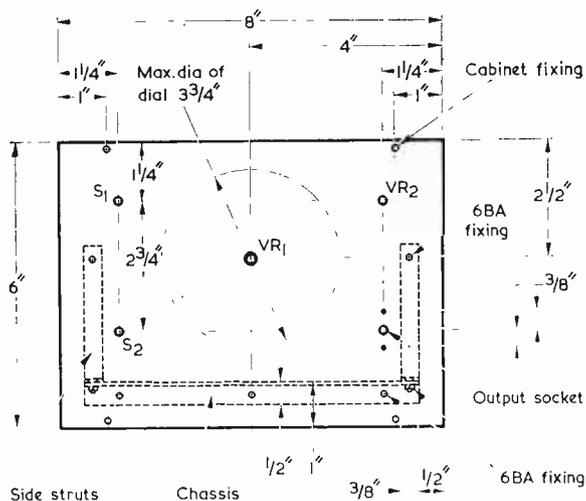


Fig. 5. The front panel layout


TESTING AND CALIBRATION

Testing and calibration of the generator depend very much upon what instruments are available. An oscilloscope is almost a necessity while if another i.f. generator can be borrowed for calibration purposes the work becomes quite straightforward. When first switched on the generator should be allowed 15 to 20 seconds to settle down, this being necessary because of the thermal time constant of the thermistor. To check that the instrument is working correctly connect an oscilloscope to the output socket. Ensure that the resultant signal displayed is a good sine wave and that its amplitude can be varied between zero and the maximum quoted by means of VR2. Then swing VR1 over its full range and check that the output remains constant within the limits quoted over all four decade ranges. If no oscilloscope is available a headphone connected to the output will give an audible check that the generator is working on Ranges 1, 2 and 3. Range 4 will be too high in frequency for an audible check. VR2 should vary the volume of the audible tone from zero upwards. In the event of difficulty and for future reference, voltage measurements are included in Table II. Typical output waveform oscillograms can be seen in the accompanying photographs.

Having checked that the generator is working correctly, there only remains the calibration. If an oscilloscope is not available there is no simple alternative and the only practical method is to transfer the calibration curve shown in Fig. 2 to the scale on VR1 by means of a protractor, measuring off degrees of rotation in terms of frequency. Such a method is of course rather inaccurate as, due to differences within tolerances in component values, scale differences will occur both in frequency limits and frequency spread.

If both an oscilloscope and a signal generator are available there should be no problems. The generator to be calibrated is connected to the Y input of the oscilloscope and the generator used as the calibration source to the X input, the time base being switched off. This allows the use of Lissajous figures for cali-

bration. Set the Y plate generator switch S1 to Range 1 and VR1 to one extreme of rotation then swing the X plate generator over the expected frequency range, say, 10 to 200Hz. The X and Y sensitivities should be adjusted to give similar deflections on the screen in both X and Y axes. When the two frequencies coincide the resultant trace will be a stationary circle. Note this frequency. Next set VR1 to its other extreme and repeat. Again note the resultant frequency. These two figures give the total frequency swing, which should be slightly greater than the nominal range. Now set the calibration generator to some definite frequency near the lower end of VR1 limit, say, 15Hz, then carefully adjust VR1 until the circular trace is observed. When this is completely stationary the two frequencies are identical. This point is now marked on VR1 scale. Next set the calibration to a higher frequency, say, 20 or 25Hz, and repeat. The complete scale should be calibrated in this way up to the next decade, i.e. 150Hz. Mid-calibration points can be made in steps to suit individual choice and the type of scale used. 25Hz steps are normally adequate,

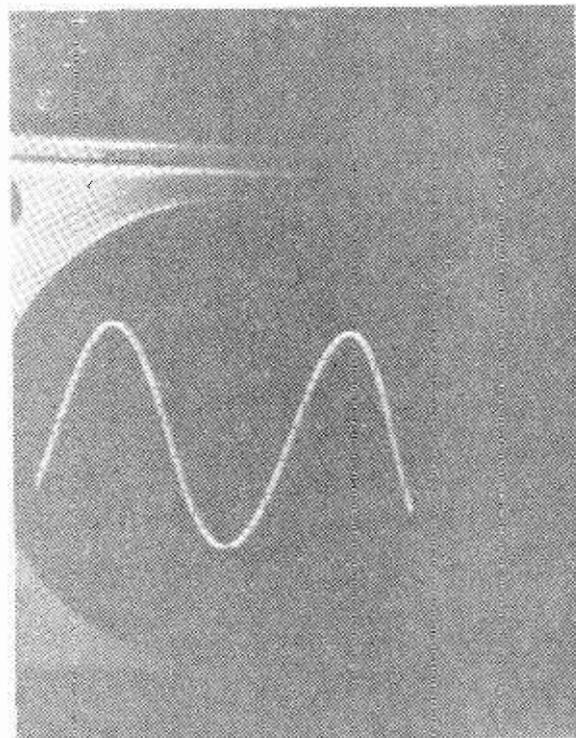


Output waveform at 100Hz

though 10 or 5Hz steps will provide a fuller scale. The tracking between ranges can be checked if desired by switching to Ranges 2, 3 and 4, and repeating the tests on a few spot points on the scale calibration. Any slight differences in tracking between ranges can be noted for future reference.

If no generator can be begged or borrowed for calibration purposes but if an oscilloscope is still available, a reasonable calibration can be made using the 50Hz mains as a standard and working with Lissajous figures. A low voltage 50Hz supply is connected to the X input, the output from a filament or

other low voltage transformer being quite suitable. With Range 1 selected by S1, adjust VR1 until the circular trace is obtained. This will indicate the 50Hz point on the scale. Decrease the frequency selected by VR1 until a pattern with two peaks in the vertical plane is obtained; this is the 25Hz point (first sub-harmonic). VR1 is then increased until a two peak pattern appears in the horizontal plane, this being the 100Hz point (second harmonic). A further increase in frequency will produce a three peak pattern (third harmonic), this being the 150Hz point. These points provide the principal calibration marks on the scale. The patterns are illustrated in Fig. 6.

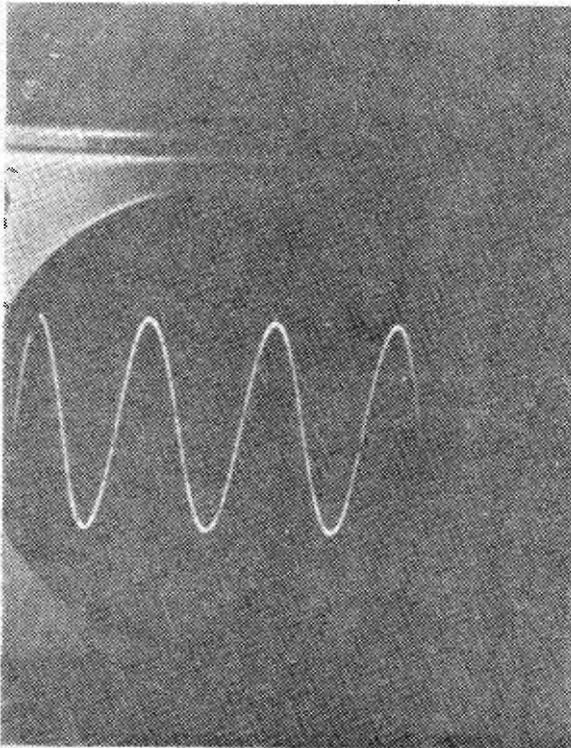Now switch to Range 2 and reduce VR1 until the third harmonic is found at the lower end of the scale. This is the 150Hz point on that range but can be marked as 15Hz on the scale as the oscillator is now



This trace, given at 100kHz, indicates the same clean sine waveform

working at a higher decade level. Increase VR1 until a four peak pattern is observed. This is the 200Hz point, which is marked on the scale as 20Hz. Similarly, a five peak pattern is given at 250Hz; this should correspond with the 25Hz mark already made from the lower decade calibration. Any slight difference between these two points gives the error between the first two decade ranges.

The remainder of the scale is calibrated in a similar manner, the six peak pattern being marked as 30Hz, the seven peak pattern as 35Hz and so on. The upper end of the scale will be more difficult to calibrate due to the difficulty of maintaining the trace stationary for sufficiently long to count the peaks on the screen trace.

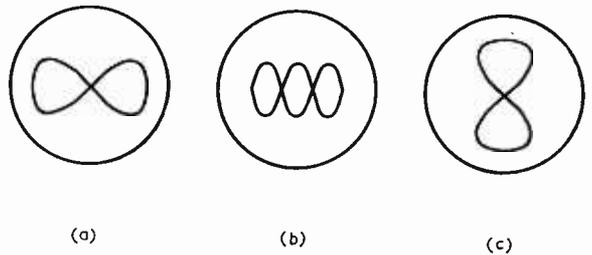


Fig. 6. The Lissajous figures given for different frequency relationships. In (a) the vertical frequency is twice the horizontal frequency, whilst in (b) the vertical frequency is three times the horizontal frequency. In (c) the vertical frequency is half the horizontal frequency

Calibration by spot wheel pattern is simpler at the upper end of the scale. Here, a circular trace is obtained by injecting equal amplitude 50Hz signals which are 90° out of phase into the X and Y inputs. See Fig. 7. The output from the signal generator is then injected into the Z modulation input on the oscilloscope. The resultant number of spots on the circular trace are then counted and computed to give the particular harmonic in relation to 50Hz.

Calibration with the aid of the 50Hz mains is not quite as accurate as when another signal generator is used as a calibration source since it tends to take in the errors between the first two ranges. For most everyday purposes, however, it should prove adequate enough.


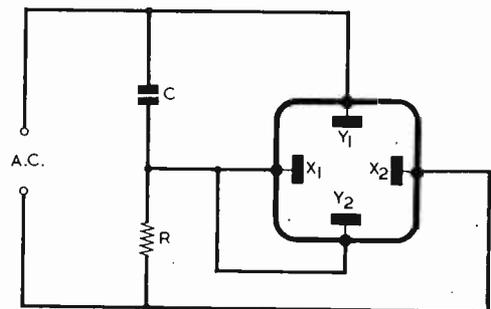


Fig. 7. Obtaining a circular trace on an oscilloscope. The reactance of C must be equal to the resistance of R. At 50Hz, suitable values are 0.2μF and 16kΩ respectively

The completed instrument should be found both simple and reliable in use, and will meet many applications in all branches of audio and ultrasonic work. Its compact size and the use of internal batteries make it equally useful in both field work and on the test bench. ■

SOLID - STATE 'RELAY'

by G. A. FRENCH

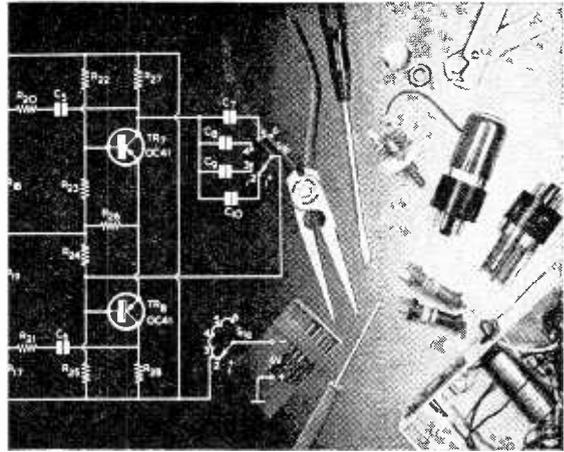

THE GREAT ADVANTAGE OFFERED by the electromagnetic relay as a switching device is that its actuating circuit (i.e. the circuit which causes current to flow in its coil) is completely isolated from the circuit or circuits which it switches. Apart from this consideration, very many of the tasks carried out by a relay can be carried out equally well, or better, by solid-state semiconductor devices, these offering the benefit that no mechanical movement of contacts is involved. With these devices, however, it is impossible to separate the actuating and switched circuits from each other unless special isolating circuitry is incorporated.

This month's 'Suggested Circuit' describes a semiconductor switching device offering facilities similar to those of a relay, and which also achieves complete electrical isolation between the actuating and switched circuits. The device can also be made to operate by direct application of the mains supply to the actuating circuit, the switched circuit having no direct connection whatsoever to this supply. The switched circuit may operate at d.c. potentials up to 30 volts, and at currents up to 0.5 amp. The circuit has some minor experimental features, which will be discussed later, and is intended for use by the more experienced constructor who is capable of adapting it as required.

RELAY CIRCUIT

A simple relay application, in which the relay has one set of normally-open contacts, is shown in Fig. 1. Until a suitable supply is

connected to the relay coil the contacts remain open. They close when an energising supply is applied to the coil.

The solid-state equivalent which forms the basis of the present article appears in Fig. 2. In this case the energising supply is applied to the pilot lamp PL1 which, together with photoconductive cell PC1, is mounted in a light-proof case. Since there is no direct connection between the pilot lamp and the circuit around the photoconductive cell, the desired isolation between actuating and switched circuits is achieved.

When PL1 is not illuminated the photoconductive cell exhibits a high resistance, of the order of $1M\Omega$ or more. In consequence, the voltage across R2 is lower than that at which forward base-emitter current can flow in TR1, and this transistor is cut off and passes leakage current

only. In its turn, the voltage across R3 due to this leakage current is below base-emitter turn-on potential in TR2, and this second transistor is similarly cut off. A negligibly low leakage current flows in the load which appears in the collector circuit of TR2.

If the actuating supply is connected to PL1 the bulb becomes illuminated and PC1 exhibits low resistance. Under conditions of bright illumination this resistance can be lower than 300Ω . Current now flows in limiting resistor R1 and the base-emitter junction of TR1. An amplified current flows in the base-emitter junction of TR2, causing this transistor to become fully saturated. The full load supply voltage, minus a fraction of a volt which is lost across the bottomed TR2, is now applied to the load. The currents flowing through R2 and R3 under these circumstances

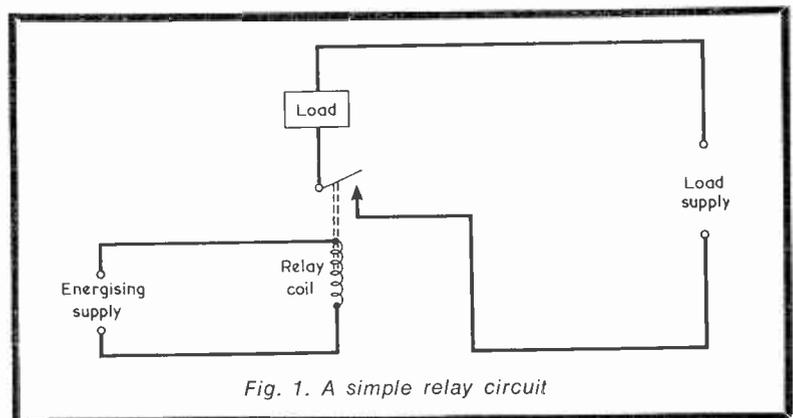


Fig. 1. A simple relay circuit

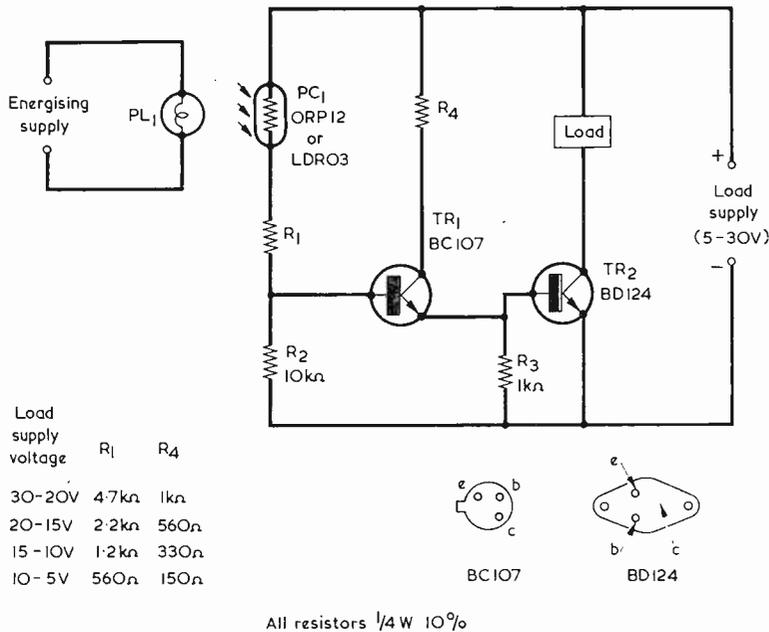


Fig. 2. The solid-state 'relay'. PL1 and PC1 are enclosed in a light-proof box

are much lower than those flowing in the base-emitter junctions of the transistors, and the two resistors can be ignored.

When the energising supply is disconnected from the bulb, this extinguishes. The photoconductive cell once more exhibits a high resistance, whereupon TR1 and TR2 become cut off and the circuit reverts to its former state. Thus, the circuit achieves the same function as the relay of Fig. 1, but it does so without mechanical movement of switch contacts. If the semiconductors are operated well within their maximum ratings the arrangement of Fig. 2 should have a far longer useful life than the relay of Fig. 1, and it requires no maintenance (such as periodic cleaning of contacts, etc.) whatsoever.

CIRCUIT RATINGS

To examine the usefulness of Fig. 2 it is necessary to consider the ratings and performance data of PC1, TR1 and TR2. The BC107 specified for TR1 has a maximum collector voltage rating of 45 volts, as also has the BD124 in the TR2 position. It would seem reasonable, therefore, to make an arbitrary choice of 30 volts maximum for the load supply potential, since this provides a generous safety margin by leaving an adequate voltage level 'in hand'. A minimum load supply potential of 5 volts is also

specified. Operation is possible below this voltage, but it may be found that TR2 does not fully bottom at load currents around 0.5 amp.

Next to be considered is the power dissipation permissible in PC1. For temperatures of 40°C or less this is quoted as 200mW maximum, and at 50°C it is quoted at 100mW maximum. In this instance it would seem sensible to work to a maximum figure around 50mW. In use, greatest dissipation occurs in PC1 when it exhibits a resistance which causes the voltage across its terminals to be half the supply voltage. At this resistance the base-emitter junctions in both TR1 and TR2 will be conductive whereupon, ignoring the relatively small voltages dropped in these junctions, it can be assumed that PC1 and R1 are connected in series directly across the load supply lines. The resistance in PC1 which causes half the supply voltage to appear across it is then equal to the value of limiter resistor R1. With a load supply voltage of 30, the half supply voltage is 15 and this causes a dissipation of about 50mW in a resistance of 4.7kΩ. In consequence, R1 is specified in Fig. 2 as 4.7kΩ for load supply voltages of 20 to 30, and to corresponding values causing about the same dissipation in PC1 at half supply voltage for lower load supply potentials.

Next to be examined are the

current gain figures for TR1 and TR2. The lowest hFE figure quoted for the BC107 is 110 and that for the BD124 is 25. The lowest theoretical current gain for the two transistors in tandem is therefore 110 by 25, or 2,750 times. However, it is desirable for the BD124 to be very hard on when it applies the load supply voltage to the load, and this argues a base current in TR2 that is significantly higher than that which is just sufficient to allow the load current to flow. In consequence, and taking up also practical losses due to transistors operating at voltages other than those for which hFE figures are quoted, a factor of ten times overall is realistic, whereupon a good operational margin would be given by saying that the solid-state 'relay' switches on reliably when the desired load current is 275 times (say 300 times) greater than base current in TR1 when PC1 is illuminated. This figure is justified from experience with the prototype circuit, particularly at low load supply voltage figures. For load currents of 0.5 amp the base current in TR1 therefore needs to be 300 times smaller, i.e. 1.7mA. The values chosen for R1 ensure that a current in excess of this figure can flow when PC1 is fully illuminated.

We turn next to dissipation in TR2. At 30 volts load supply voltage the maximum load current of 0.5 amp (when TR2 is hard on) is given by a load resistance of 60Ω. Maximum dissipation occurs in TR2 when half the supply voltage appears between its emitter and collector and in the present instance this will be equal to 15 volts times 0.25 amp (the latter being the collector current at half supply voltage) or 3.75 watts. The maximum quoted junction temperature for a BD124 is 175°C and its thermal resistance from junction to case is 7.5°C per watt. The BD124 is in an SO-55 encapsulation which has a thermal resistance, case to heat sink, of 0.5°C per watt without a mica washer or 1.5°C per watt with a mica washer. Assuming, under worst conditions, an ambient temperature of 50°C and no mica washer, the requisite heat sink thermal resistance to air (Rth) can be calculated from 3.75 watts = (175-50)/(7.5 + 0.5 + Rth). This works out at a thermal resistance from heat sink to air of 25°C per watt. With a mica washer, the figure becomes 24°C per watt. A flat heat sink about 1½ in. square would be more than adequate for TR2.

A component not mentioned up to now is R4. The function of this resistor is to limit power dissipation in TR1 reasonably well below its maximum specified value of 300mW. It is calculated under half supply voltage conditions for the instance

where PC1 inserts lowest resistance into circuit.

It will be appreciated from the above that the circuit of Fig. 2 provides very conservative operating conditions for all components. This point becomes even more evident when it is realised that PC1 and TR2 have power dissipation evaluated for the half supply voltage condition whereas, under normal operation, PC1 and TR2 will only pass through this condition momentarily as the 'relay' changes from the 'off' state to the 'on' state and from the 'on' state to the 'off' state. The only component which can possibly approach a relatively high dissipation level is TR1. In any case, and as is explained later, dissipation in TR1 can be reduced in practice by adjustment of the value of R4 to suit specific load currents.

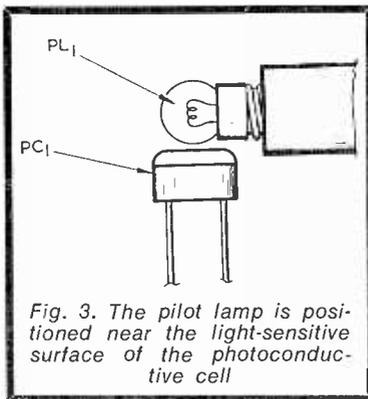


Fig. 3. The pilot lamp is positioned near the light-sensitive surface of the photoconductive cell

PRACTICAL POINTS

The choice of bulb for the PL1 position is not critical, although it is desirable to employ a type which does not draw excessive current. For the prototype circuit the writer used a 6 volt 60mA m.e.s. pilot lamp positioned close to the surface of the photoconductive cell, as shown in Fig. 3. This caused the photoconductive cell to be more than adequately illuminated when the full 6 volts was applied to the bulb, and it was found possible to actuate the 'relay' by running the bulb from a 3 volt supply, from which it drew approximately 35mA. Con-

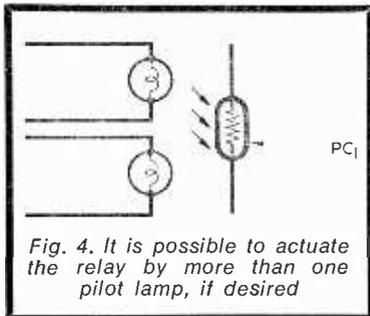


Fig. 4. It is possible to actuate the relay by more than one pilot lamp, if desired

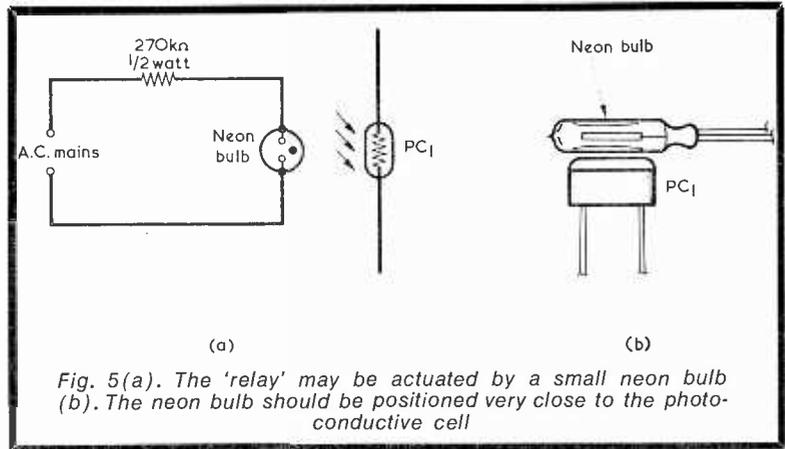


Fig. 5(a). The 'relay' may be actuated by a small neon bulb (b). The neon bulb should be positioned very close to the photoconductive cell

structors wishing to take advantage of this fact may, if desired, experiment along similar lines. The bulb and the photoconductive cell are mounted inside a small light-proof case.

It is interesting to note that the 'relay' can be operated by more than one bulb, as shown in Fig. 4, each of the bulbs being in reasonably close proximity to the light-sensitive surface of the photoconductive cell. The circuit then acts as an OR-gate since the 'relay' is actuated by any one or all of the bulbs.

The 'relay' may also be actuated by a small wire-ended neon bulb of the type which is available from Henry's Radio as Hivac type 16L or 34L, or from Home Radio under Cat. No. PL32A. The neon bulb, with a series 270kΩ resistor, may be run direct from the mains supply, as shown in Fig. 5(a). The neon bulb needs to be mounted very close to the ORP12, in the manner illustrated in Fig. 5(b). The illumination provided by the neon bulb is not sufficient to bring the ORP12

down to a very low resistance and the 'relay', when operated in this manner, may not be able to control load currents as high as 0.5 amp. Judging from the writer's experience, however, it should be able to cope with load currents of the order of 0.4 amp.

When the 'relay' circuit has been assembled and checked out, it is desirable to see whether it is capable of switching the particular load connected to it when the value of R4 is made approximately double that indicated in Fig. 2. If this can be done, the increased value of R4 should be retained in circuit. This increased value will result in reduced dissipation in TR1 and greater long-term reliability. The voltage across TR2 emitter and collector should be checked when the 'relay' is actuated. If it is less than 1 volt it may be assumed that TR2 is adequately bottomed. The actual voltage obtained will vary with different BD124's; with the prototype it was less than 0.2 volt. The leakage current in the BD124

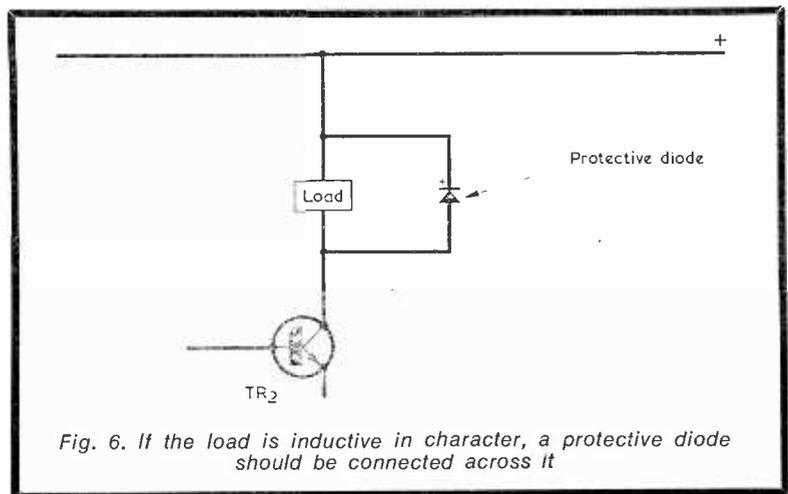


Fig. 6. If the load is inductive in character, a protective diode should be connected across it

when the 'relay' is not actuated should be very low. The writer found that, with the BD124 at room temperature, the leakage current caused no discernable deflection in the needle of a testmeter switched to read $0 - 50\mu\text{A}$. This check was carried out at a load supply potential of 15 volts.


If the load switched by the 'relay' is inductive in character, it will be necessary to connect a protective

diode across it to prevent the formation of a high back-e.m.f. voltage when TR2 cuts off. See Fig. 6. The diode may be any silicon rectifier having a p.i.v. of 50 or more, and a forward current rating of at least 0.5 amp. The Lucas type DD000 would be suitable.

As a final point it may be restated that the component values and performance figures quoted are all very conservative, as befits a device

which is intended to exhibit a high level of reliability. Readers who care to experiment may find that particular 'relays' built up to the circuit are capable of switching load currents in excess of 0.5 amp. However, performance in this respect is dependent upon the characteristics of the particular transistors employed and cannot be reliably predicted.

RECENT PUBLICATIONS

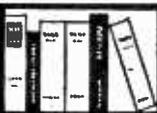

A DICTIONARY OF ELECTRONICS, Third Edition. By S. Handel. 413 pages, $4\frac{1}{2} \times 7\frac{1}{4}$ in. Published by Penguin Books, Ltd. Price 45p.

It is pleasant to see a good book prove its success over the years. The reviewer has relied considerably on the first edition of "A Dictionary of Electronics", which appeared in 1962, both for journalistic and for engineering work. Now the dictionary is in its revised and enlarged third edition, having taken in the new words and terms which have appeared in the intervening time of nearly ten years. As Mr. Handel says in his introductory note to the new edition "... this is a long time in the life of a technology which is growing as fast as electronics".

The book, which is in the Penguin Reference Books range, has the familiar Penguin paperback format. All aspects of electronics are covered, including radio, radar, television, integrated circuits and computers. Entries appear alphabetically in normal dictionary form and cross-references are indicated by words or terms in italics. A non-technical reader can work, through the cross-references, from a complicated item to its simple basic concepts, these being expressed in 'standard dictionary' words.

The dictionary represents excellent value to anyone who is connected with electronics, be he student, amateur constructor or experimenter, engineer or technical writer; and Penguin Books are to be praised for presenting an outstanding reference book at such exceptionally low cost.

TEST YOUR KNOWLEDGE OF TELECOMMUNICATIONS. By L. Ibbotson. B.Sc., A.Inst.P., C.Eng., M.I.E.E., M.I.E.R.E. 94 pages, $4\frac{1}{2} \times 7\frac{1}{4}$ in. Published by Iliffe Books. Price 80p.

TEST YOUR KNOWLEDGE OF PHYSICAL ELECTRONICS. By T. Wilmore. B.Sc., A.R.C.S., A.Inst.P. 96 pages, $4\frac{1}{2} \times 7\frac{1}{4}$ in. Published by Iliffe Books. Price 80p.

TEST YOUR KNOWLEDGE OF APPLIED ELECTRONICS. By R. W. J. Barker. M.Sc., B.Sc., C.Eng., M.I.E.E. 96 pages, $4\frac{1}{2} \times 7\frac{1}{4}$ in. Published by Iliffe Books. Price 80p.

These three titles are the first in a series of revision texts designed to cover a first degree course in electrical engineering. They should also be suitable for H.N.C., H.N.D. and C.E.I. examinations. They are intended to provide revision only and are not presented as a first study course. A student using a "Test Your Knowledge" book should do so a little time before his examinations, whereupon he will soon find the strengths and weaknesses in his knowledge and understanding.

In each of the books questions are listed on the right hand pages. The reader then turns the question page to find the corresponding answers printed on its other side. Each question is followed by four suggested answers of which only one is correct. The reader selects what he thinks is the right answer, then consults the following page to check whether his choice is correct. In addition to showing the proper answer, the following page also gives explanatory text to augment the process of revision.

These useful little books are of small and handy size, and each contains some four to eight questions per question page. Not only are the books of assistance to the student, but they can also provide entertaining reading for the practising engineer who wants to check on his own knowledge of the subjects covered.

COLOUR TELEVISION PICTURE FAULTS. By K. J. Bohlman, A.M.Inst.E. 126 pages, $5\frac{1}{2} \times 8\frac{1}{2}$ in. Published by Norman Price (Publishers) Ltd. Price £2.50.

This well-presented book is intended to provide, with the aid of colour photographs taken under receiver fault conditions, a reference for technicians in the identification and repair of faults in colour television receivers. There are over 120 illustrations, including 88 colour photo graphs. The latter are reproduced extremely well and with a depth of detail and truth in colour that is more than adequate to demonstrate the fault being indicated.

The main section of the book is taken up by the photographs together with concise explanations of the faults they represent and the appropriate remedial action. Thirty picture faults are covered, these ranging from impure raster to the PAL switch operating on the wrong phase, and include misconvergence, absence of clamping pulses, loss of colour or bands of colour, Moire effect and 4.43MHz dot patterning. This section is followed by a useful appendix which gives colour bar waveforms, PAL decoder arrangements, u.h.f. channels, a fault-finding chart and details of colour television Test Card F. The book then finishes with an index.

"Colour Television Picture Faults" fills a gap which has been evident since the inception of colour television transmissions in this country, and will be of considerable help to all service engineers including, in particular, those who are just commencing or who are just graduating from monochrome to colour.

REMOVING ELIMINATOR HUM

by

G. W. SHORT

Battery eliminators reduce the running costs of transistor radios very considerably, but they can also introduce hum. This article describes a number of approaches which combat this problem

CONVERTING A BATTERY SET TO mains operation is on the face of things a simple operation, and one which in the long run can save a lot of money, since mains power is so much cheaper than battery power. However, there is no rose without a thorn, and in this case the thorn is mains hum, which can be quite a problem. This article describes how hum gets into equipment when it is converted to mains operation and shows how to overcome the problem.


ELIMINATOR TYPES

Before we get down to details, let's get one thing clear. There are two distinct types of battery eliminator, one with a double-wound step-down transformer and the other with no transformer, only some kind of 'voltage dropper' to reduce the mains to the required 9V or so. This article is concerned only with the first kind, that is the type which uses a double-wound transformer. The 'voltage dropper' type can be made cheap and very compact, but it suffers from the fatal flaw of not providing an output isolated from the mains. This is dangerous, and the non-isolated type of eliminator is not recommended for that reason.

Returning to the transformer type, then, a typical circuit is shown in Fig. 1. This example delivers a nominal 9V d.c. at up to 120mA, which is enough for nearly all portable transistor radios. As can be seen, it is just about the simplest arrangement possible: a full-wave rectifier charging a 1,000 μ F electrolytic 'reservoir' capacitor. Note that the transformer secondary voltage is 7-0-7V r.m.s. not 9-0-9V. This is because the d.c. output voltage is

more than the r.m.s. input voltage. In theory, at zero load, i.e. no output current, the d.c. output is 1.4 times the r.m.s. input, which is 10V d.c. for 7V r.m.s. As the current taken from the unit increases, the output voltage falls, eventually approaching the r.m.s. voltage. With the MT7 transformer and other components as shown the output is

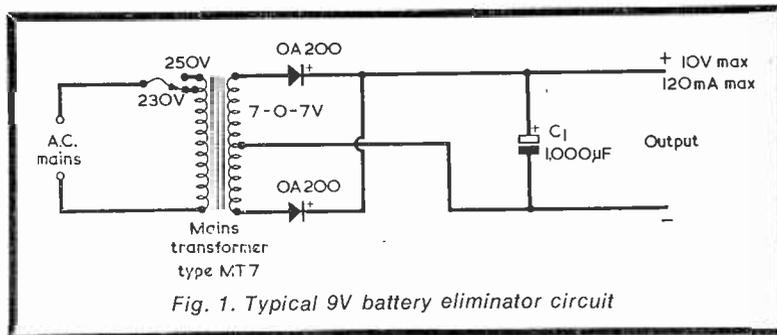imposed on the d.c. The frequency is 100Hz - twice the mains frequency - because we are using full-wave rectification which charges C1 twice every mains cycle. Careful observation of the waveform shows that alternate cycles of the sawtooth are not quite the same size. This is because of unbalance in the resistances of the two halves of the trans-



9V at 70mA approx. and 8V at the maximum rated output of 120mA. (The MT7 transformer is available from Amatronics Ltd., 396 Selsdon Road, South Croydon, Surrey.)

MAINS HUM

We are concerned with mains hum, however. The most obvious source of hum in the case of Fig. 1 is simply the result of the imperfect smoothing provided by this simple circuit. At zero output current the d.c. supply is quite smooth, but as the current taken increases so the output becomes less and less smooth. Looked at on an oscilloscope, the output is seen to have a sawtooth ripple voltage super-

posed on the d.c. The frequency is 100Hz - twice the mains frequency - because we are using full-wave rectification which charges C1 twice every mains cycle. Careful observation of the waveform shows that alternate cycles of the sawtooth are not quite the same size. This is because of unbalance in the resistances of the two halves of the trans-

former secondary, and it implies that there is a small 50Hz component mixed up with the 100Hz ripple. It is usual to specify the amplitude of a ripple voltage as a peak-to-peak quantity, because this is easiest to measure. (The r.m.s. equivalent for a sawtooth wave is very nearly half the peak-to-peak value.) In the circuit of Fig. 1 the ripple rises to some 400mV peak-to-peak at full output. At lesser outputs the ripple falls more or less in proportion. Thus at half output (60mA) the ripple is about 200mV peak-to-peak, at 30mA it is about 100mV, and so on. If this ripple finds itself into the audio circuitry of a set powered by the eliminator

This
saves
this



Prevention is best –
you know it makes sense!

Endorsements are expensive! Our unique radar spotting device gives earliest possible warning of radar speed checks – up to 1/3rd of a mile on give and take roads (1½ miles on motorways) and helps you to be a better and safer driver. Self-contained, only 10½ ozs. Clips on sun visor. **DON'T WAIT UNTIL IT'S TOO LATE – ORDER NOW.**

To: Belding & Bennett, 01-668, 3255 & 01-660 2896, (Box 38), 45 Green Lane, Purley, Surrey.
 Send me Spotters at £13.75p each
 Enclosed PO/Cheque £.....
 Name
 Address
 Phone No.
 Details only: Send 4p in stamps.
 Trade enquiries welcome.

**The
RADIO CONSTRUCTOR**

**ANNUAL
SUBSCRIPTIONS**

to this magazine
may be obtained
through your
newsagent
or direct from the
publishers

**ONLY £2.70
per year, post free**

*Please send remittance with name
and address and commencing issue
required to:*

DATA PUBLICATIONS LTD
57 Maida Vale London W9 ISN

it may be strong enough to cause hum. This is not, in fact, very likely in the average set, but it can happen.

If it does, what can be done about it? The simplest way to reduce ripple is to increase C1. Doubling the capacitance halves the ripple, and so on. This, however, is an expensive method where large amounts of extra smoothing are needed. To reduce the ripple to 10% of its initial value, for instance, would call for an extra 9,000µF. The working voltage must be at least 12V to allow for mains surges, so a bulky and expensive component is required.

LOW-COST ALTERNATIVE

What are the alternatives? It comes as a pleasant surprise to learn that in many cases a vast improvement is produced by adding to Fig. 1 one twopenny resistor! This is put in series with the non-earthly leg of the d.c. output, as shown in Fig. 2. The reason for the improvement is that many battery sets already have inside them a large value electrolytic capacitor (of a few hundred microfarads) across the battery. Its job is to decouple the battery when the latter is used and provide some measure of reservoir capacitance to help a class B audio output stage get along when the battery runs down. It is shown here as C2, and of course it reduces ripple by forming, in conjunction with R1, an extra RC smoothing filter section.

other current from the formula:

$$R1 = \frac{1,000}{\text{current in mA}}$$

where R1 is in ohms.

But what is the current? Battery sets nearly always have Class B audio amplifiers, and with these the current drawn depends on the volume. If the standby current (at zero volume) is 10mA, and the current taken at full volume is 100mA, do we make R1 10Ω or 100Ω?

The most likely answer is, neither. Some sort of compromise value will be best, so that a reasonable amount of smoothing is obtained without undue sacrifice of volume.

We could take the average of 10 and 100Ω, which is 55Ω. But this, it may well be felt, is a bit too high, since at 100mA it will drop 5.5V, which seems a lot. Something a bit less than 55Ω may be better.

At this point mathematics comes to our aid. Mathematicians recognise several different 'average values'. The one we just used is called the arithmetic mean. For our sort of compromise, however, a much better 'average' is the geometric mean. To find the geometric mean of two numbers you multiply them together and then take the square root of the answer. In our case we have 10 and 100Ω. The geometric mean of these values is the square root of 10 x 100, which is 31.6Ω. This is our compromise resistance.

The advantage of the geometric mean is that it compromises by giving a value which is proportionately wrong by the same amount at each

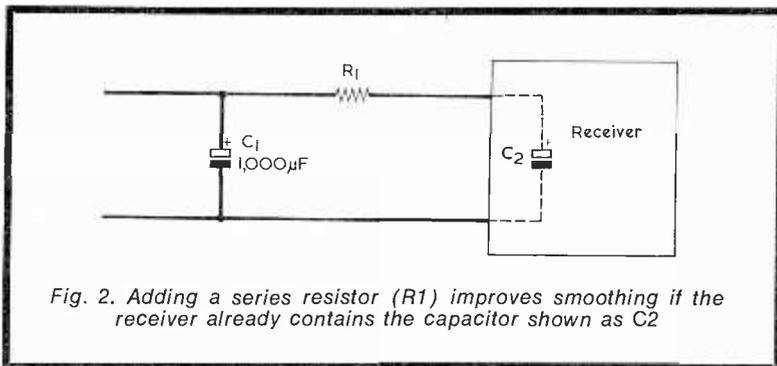


Fig. 2. Adding a series resistor (R1) improves smoothing if the receiver already contains the capacitor shown as C2

What value should R1 have? This depends on the current drawn by the set. If R1 is too large, too much voltage will be lost. If it is too small, not enough smoothing will be obtained. It is usually quite safe to sacrifice 1V, since a well-designed battery set will go on working when the battery voltage falls below 9V. If, then, the set takes 10mA, we can use 100Ω for R1 for the loss of 1V. And we can calculate the value of R1 which will drop 1V with some

end of the range of current. In our case, it gives an R1 which is 3.16 times too small at 10mA and 3.16 times too large at 100mA. (The arithmetic mean gave a value which was about two times too small at 10mA but 5.5 times too large at 100mA.) There is no guarantee, of course, that in particular cases the geometric mean will yield the best possible value for R1, but generally speaking it gives a much better one than the other 'average' does.

If there is no C2 in the set, or if the existing one is too small, an additional smoothing capacitor can be added. Once R1 is known, the value of C2 which will attenuate the 100Hz ripple by a factor of at least 10 (=20dB) is calculable, being

$$\frac{16,000}{R1} \mu F$$

(R1 being expressed in ohms). So, if R1=100Ω, C2=160μF for 20dB ripple reduction.

What does this mean in terms of the amount of hum you actually hear? Subjectively, every 10dB reduction roughly halves the volume. So an extra 20dB of smoothing halves it twice, i.e. reduces it to a quarter of the original volume. In fact, the R1, C2 technique usually does slightly better than this, because it gives more than 20dB reduction of the harmonics of 100Hz which are present in the sawtooth ripple voltage, and which are more audible than 100Hz.

If further reduction is needed, C2 could be increased, but once again it turns out that this is the expensive way of doing things. It is better to use two RC smoothing sections, each with a resistance which is half the calculated value of R1.

DIFFERENT HUM ROUTE

Long before reaching this stage of complexity, however, we should be asking ourselves whether the hum isn't getting to our loudspeaker by some quite different route.

Whenever mains transformers or mains wiring are close to a circuit hum can be induced into that circuit. In high-impedance or low-level signal areas, a nearby live mains lead, however well insulated, can cause capacitive hum injection. Also, the magnetic field of a mains transformer can induce hum voltages into wiring and especially into nearby inductive components such as driver transformers, r.f. chokes, i.f. coils and ferrite aerials.

It is easy to find out whether this kind of hum is being picked up. All you do is separate the set from the eliminator on long leads. The farther apart they are the less hum there should be, and at a foot or more the hum, if induced, will have disappeared.

Having proved by this test that induced hum is the problem, how can it be dealt with? For a start, keep the mains wiring as far away as possible from audio circuitry. Orient the mains transformer so

that no hum is induced into inductive components – a trial-and-error job.

If these things cannot be done, why not just keep the eliminator well away from the set? It is often possible to find space on the cabinet of a set for two miniature sockets to which the d.c. output of the eliminator can be fed by way of suitable plugs on a long lead. One plug and socket should be coloured red and the other plug and socket black to ensure that the eliminator is connected with correct polarity.

If hum is getting into a set via the ferrite aerial it may be possible to filter it out by adding a simple CR high-pass filter to the base circuit of the first transistor. The method is illustrated in Fig. 3, which shows the base circuit of a frequency changer transistor before and after modification.

It may be surprising to find that hum voltages in a ferrite aerial can cause trouble in a superhet. After all, 100Hz or 50Hz is rejected most efficiently by the i.f. transformer in the collector circuit! Unfortunately, by the time it gets there the damage is already done. What happens is that a strong hum voltage in the base circuit amplitude-modulates all

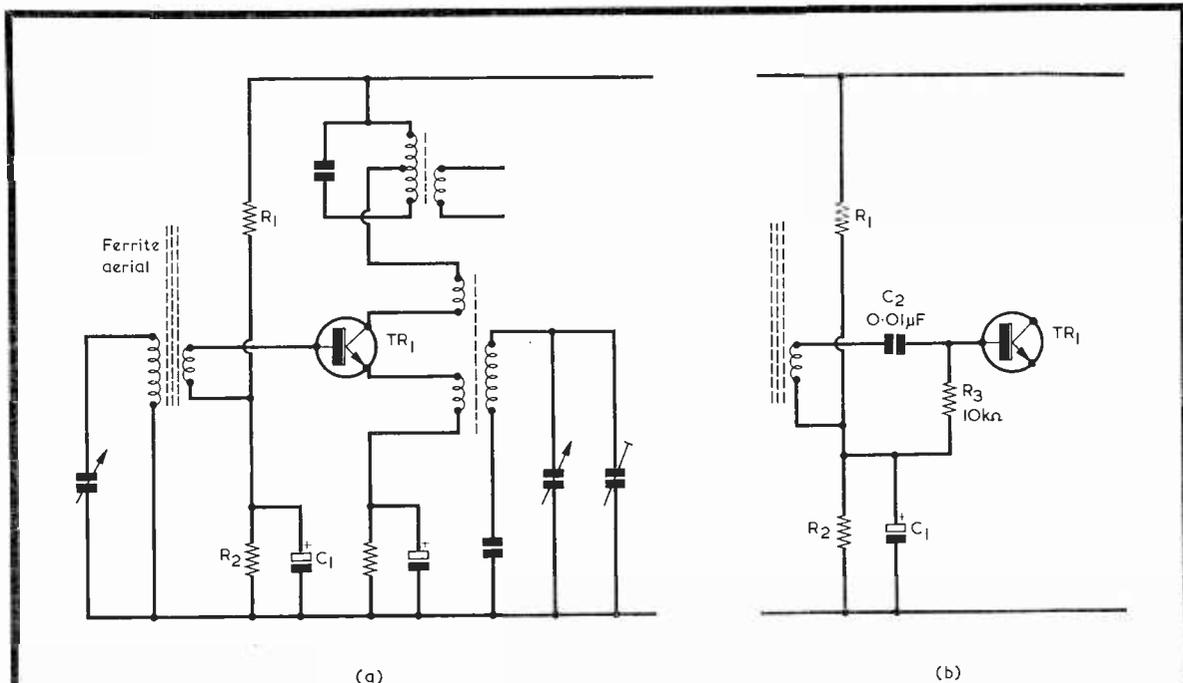


Fig. 3. Hum induced in a ferrite aerial can often be attenuated by a simple CR filter. The typical frequency changer in (a) is modified by the addition of C2 and R3 in (b). These allow r.f. signals to pass but block hum signals. R2 may have to be altered to restore the original collector current in TR1

the incoming signals. Thereafter the hum is impressed on the carrier frequencies, and gets changed in frequency and ultimately detected along with the wanted modulation.

Finally, there is a puzzling sort of hum which might be called power-lead hum. To see how it occurs, you have to remember that C1 in Fig. 1 is charged by the rectifiers in brief, high-current pulses. When the d.c. output is 100mA, these pulses might readily have a peak value of 500mA. Large currents like this can set up significant hum voltages in very low resistances such as the resistance of a connecting lead. To take an example, suppose a lead has a resistance of 0.01Ω . Nothing to worry about there, one would think. Yet 500mA in 0.01Ω sets up 5mV. If this gets into a low-level audio stage it will cause a loud hum. And it certainly can get in if the power-lead wiring is bad. Fig. 4 shows how it can happen. Here we have a typical low-level a.f. amplifier in a very bad wiring layout. Any hum voltage set up across connection AB is effectively in series with the input signal. It goes straight into the a.f. amplifier!

The remedy is obvious, once the cause of the trouble is known. Con-

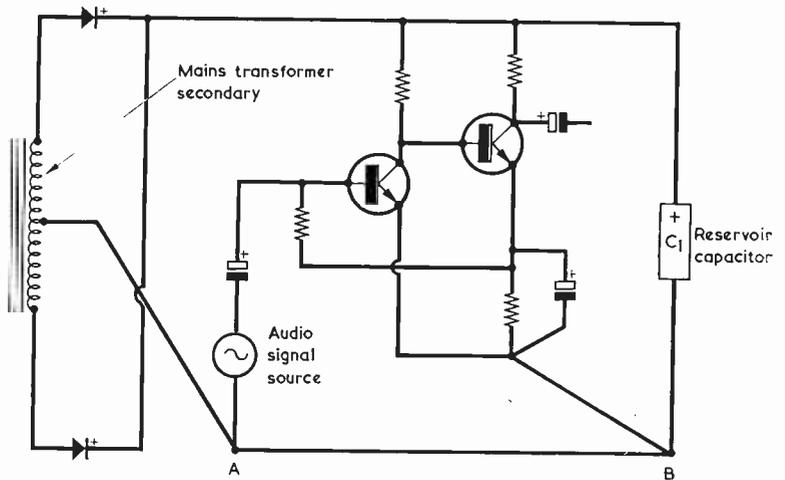


Fig. 4. 'Power-lead hum'. Any hum voltage in the connection between A and B finds its way into the audio amplifier

nect the earthy side of the a.f. signal source directly to point B, not point A. In other words, don't use a wiring layout in which leads which carry signals also carry the current from the rectifiers to the reservoir capacitor. Take the signal

'earths' directly to the earthy tag of the capacitor. This kind of hum is more likely to occur when a mains unit is built into original equipment than when it is used as a battery eliminator, but it is always as well to bear it in mind. ■


NEW PRODUCT -

ADCOLA 'INVADER' RANGE

A new range of lightweight, thermally controlled, electrical soldering instruments has been introduced by Adcola Products Ltd., Adcola House, Gauden Road, London, S.W.4. Described as the 'Invader' range, the new models incorporate a tried and proven element combined with a new 'pencil-slim' handle.

The handle, moulded in a self-extinguishing grade of Noryl plastic, has been designed to give operators a fine degree of control when soldering intricate circuits or contacts. The centre heat shield is rectangular in shape to allow the instrument to be placed securely on any surface without rolling, and the iron is balanced to ensure that the working bit is always clear of the surface. An integral hanging hook is moulded into the handle.

The 'Invader' range employs the reliable Adcola 'A' series element and existing replacement elements and spares can be used. The collet can also accommodate the complete range of 70 standard and special purpose bits. Standard 'Invader' models are available in seven stock voltages: 6V, 12V, 24V, 50/55V, 110V, 220V and 230/250V. Three collet sizes - $\frac{1}{8}$ in., $\frac{1}{16}$ in. and $\frac{1}{32}$ in. - are also available. Any specific bit temperature between 250°C and 410°C can be supplied at no extra charge.

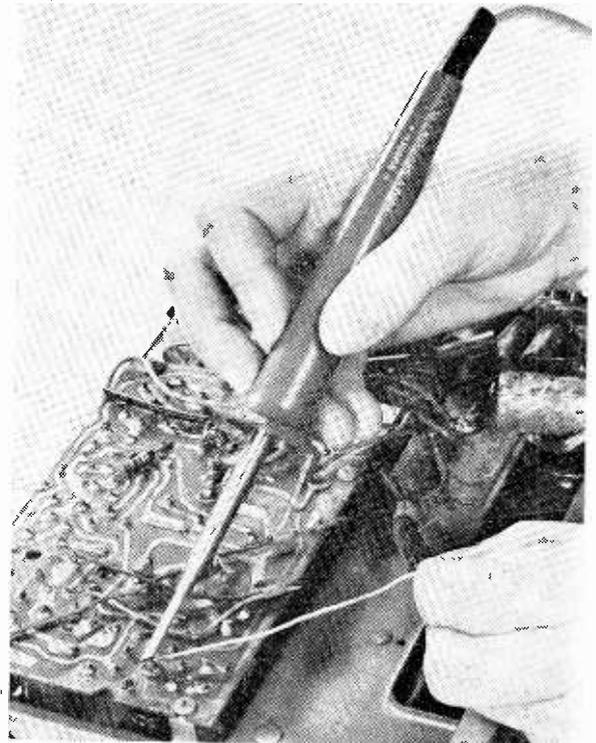

The new Adcola 'Invader' soldering iron features close temperature control and a slim-line low-heat handle

The RADIO CONSTRUCTOR

NOVEMBER ISSUE

FEATURES

AUDIO FREQUENCY METER

(Part 1)

by J. T. NEILL

PLUS

★ MORE CONSTRUCTIONAL PROJECTS

★ NEWS COVERAGE


★ SUPPORTING FEATURES

ON SALE NOVEMBER 1st

PRICE 20p

Copies may also be obtained direct from the Publishers
24p including postage.

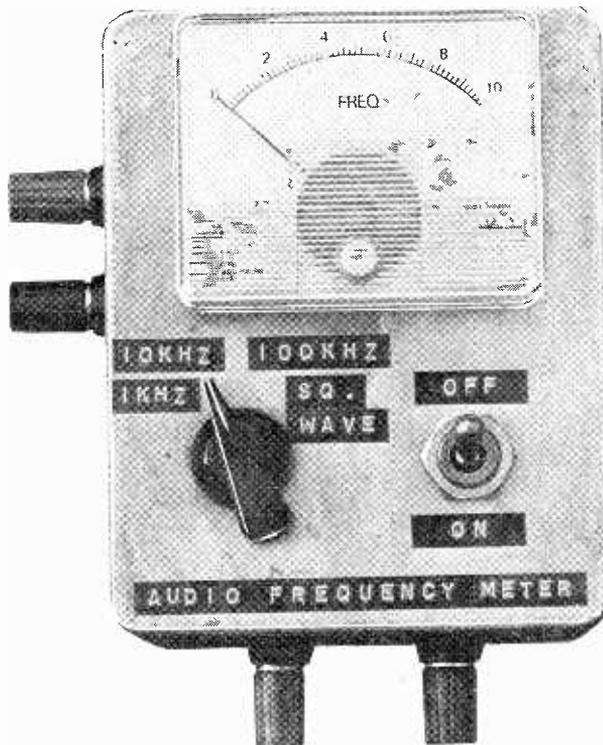Published by:
Data Publications Ltd.,
57 Maida Vale, London W9 1SN



NOW HEAR THESE

Times = GMT

Frequencies = kHz

● ECUADOR

A new station reported heard is HCSA Quito, when signing off at 0200 on 6310.

● HAITI

4VEH Cap Haitien has been heard on the regular 11835 channel (2.5kW) 25.35 metres, with a religious programme in English at 0130.

● CLANDESTINE

There are quite a number of such transmissions on the short waves these days. B. Walsh of Romford, Essex, logged and directed our attention to a station announcing as "Fala Radio Portugal Libre" at around 1855 and onwards, in Portuguese on approximately 15500. We measured the channel as 15482.

A later letter from B. Walsh informed us that the transmissions could be picked up on 11595 but that the 15482 channel was silent. Our informant tells us that an interval signal is radiated at 1855 and at 1925, consisting of seven notes played on an organ, repeated several times and followed by an unrecognisable anthem.

● MEXICO

XERMX, "Radio Mexico", on 21705, is another of the 'catches' attributable to B. Walsh. Programming is in Spanish with typical Latin American music. Identifications are made frequently in Spanish, German and occasionally in English. We logged an identification in English at 2115. The frequencies 9705, 11770 and 17835 are used in parallel. The power is 100kW.

OCTOBER 1971

● IRAN

This country may be logged on 3778 (100kW) from around 1900, when a programme of Arabic-type music, with announcements in Farsi (Persian) were heard. Other channels used by Radio Teheran are - 7044, 12176 and 15084.

● SOUTH AFRICA

Several channels in the LF bands are used by the South African Broadcasting Corporation (SABC) when radiating their local services. Dx'ers in the U.K. often report such transmissions. Listen on the following channels - 2326 (20kW) English Service; 2346 (20kW) Afrikaans Service; 2376 (20kW) National Commercial & All Night Service; 3250 (20kW) National Commercial & All Night Service; 3285 (20kW) English Service; 3320 (20kW) Afrikaans Service; 3965 (20kW) English Service and 3997 (20kW) National Commercial Service. Listen from 2100 onwards.

● REUNION


The Ile de la Reunion, a French possession in the Indian Ocean between Mauritius and Malagasy, is reported being heard by BADX (British Association of Dx'ers) on the regular 2446 channel, a Dx feat of no mean calibre. Programmes from the capital, St. Denis, can also be heard on 4807 if conditions are right. Both transmitters have a power of 4kW, programming is in French. Address for reports is - ORTF, B.P.309, St. Denis, La Reunion.

● IRAQ

Baghdad, the capital city on the banks of the river Tigris, may be heard on the LF bands on the following channels - 3235, 3240 and 3960.

Acknowledgements:- BADX, Our Listening Post, SCDX.

159

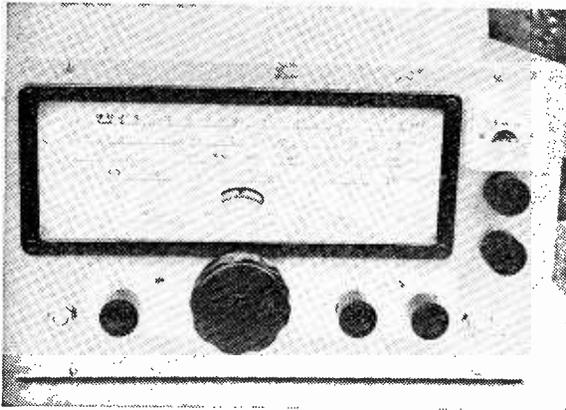

The front panel of the Coil-Pack Communications Receiver

COIL COMMUNICATI

This superhet receiver, covering long short wave bands from 1.8 to 18.75 MHz, provides s.s.b. signals in addition to standard AM and CW. It features an S-meter and an exceptionally sensitive volume control. A concluding article, to be published in the next issue, and see

THE USE OF A READY-MADE COIL-PACK GREATLY eases the construction of a multi-band superhet receiver, and avoids all the difficulty which may be found in wiring the many coils, together with the associated wave-change switch, padders and trimmers that are otherwise required. The receiver described here has a compact 4-band coil-pack, covering long, medium, and two short wave ranges. The latter provide reception of ordinary broadcast and Amateur frequencies from 18.75MHz to 1.8MHz, so including the 20, 40, 80 and 160 meter Amateur bands. Provision is made for c.w. and single-sideband reception, as well as for the usual a.m.

A quite compact cabinet houses the receiver, which employs an external speaker as is usual with this type of equipment. A tuning meter is fitted, and this is helpful for providing comparisons in signal strength, or for adjusting an aerial tuner or coupler, etc.

The receiver, as described here, will be found adequate for most purposes. The enthusiast who is always looking for a bit extra, and who is especially interested in the h.f. bands, can add a pre-selector or r.f. amplifier later. An article describing a suitable pre-selector amplifier is in course of preparation, and this will be published at a future date.

CIRCUIT DETAILS

Fig. 1 shows the complete circuit. For the benefit of anyone who has so far only constructed the simpler type of receiver, a brief description of the stages and other features should be of help.

Coil-Pack. This incorporates eight coils, eight trimmers and three padders, these being ready wired as a complete assembly which is mounted by the

switch bush. It is only necessary to complete five connections to the pack, as in Fig. 1. 'Black' is the aerial connection, and 'Green' the connection to the aerial tuning capacitor VC1. 'Red' and 'Blue' are for the oscillator circuit, and 'Yellow' is the chassis return.

V1. This is the frequency-changer, and pins 8 and 9 connect to the triode section, used as oscillator. Signals pass to the heptode grid (pin 2) and the output from the heptode anode (pin 6) is taken to the first intermediate frequency transformer, IFT1.

I.F. Amplifier. V2 is the intermediate frequency amplifier, operating at 465kHz, and IFT2 is the second i.f. transformer.

D1 and A.G.C. The diode D1 provides detection of amplitude modulated, or a.m., signals. These are the ordinary long and medium wave transmissions, as well as ordinary short wave broadcast signals, and Amateur a.m. signals. D1 also provides an automatic gain control bias across R10. This bias increases with signal strength, and is applied to V1 and V2 through R9, R2 and the secondary of IFT1. The bias automatically reduces gain in these stages on the reception of strong signals, and thus helps to reduce the effects of 'fading'.

Tuning Meter. With no signals, the cathode current of V2 through R8 is at maximum. VR1 is then adjusted so that no potential exists across the tuning meter, which accordingly shows zero on the scale. Signals tuned in produce an a.g.c. voltage, as described, and the a.g.c. bias reduces the cathode current of V2, whereupon less voltage is dropped across R8. The circuit is no longer balanced, and the meter shows a reading which rises as signal strength increases. (The actual meter employed has a full-scale deflection of 1mA and has front dimensions of 1½ in. square. Suitable meters are available from a number of suppliers, including Henry's Radio, Ltd.)



Cover Feature

PACK INS RECEIVER


PART I

by

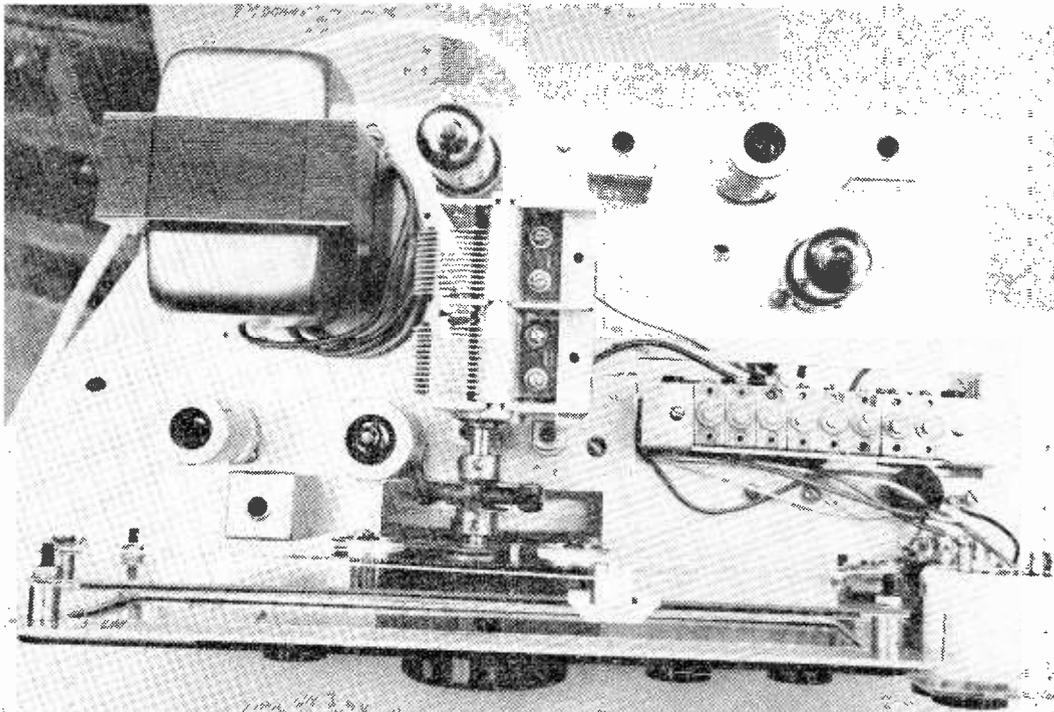
F. G. RAYER,

Assoc.I.E.R.E., G30GR

and medium waves as well as the
Hz, is capable of receiving c.w. and
1. transmissions. Further features are
both dial drive. The construction is
dy assembled pre-aligned coil-pack.
next month, deals with calibration
ng-up



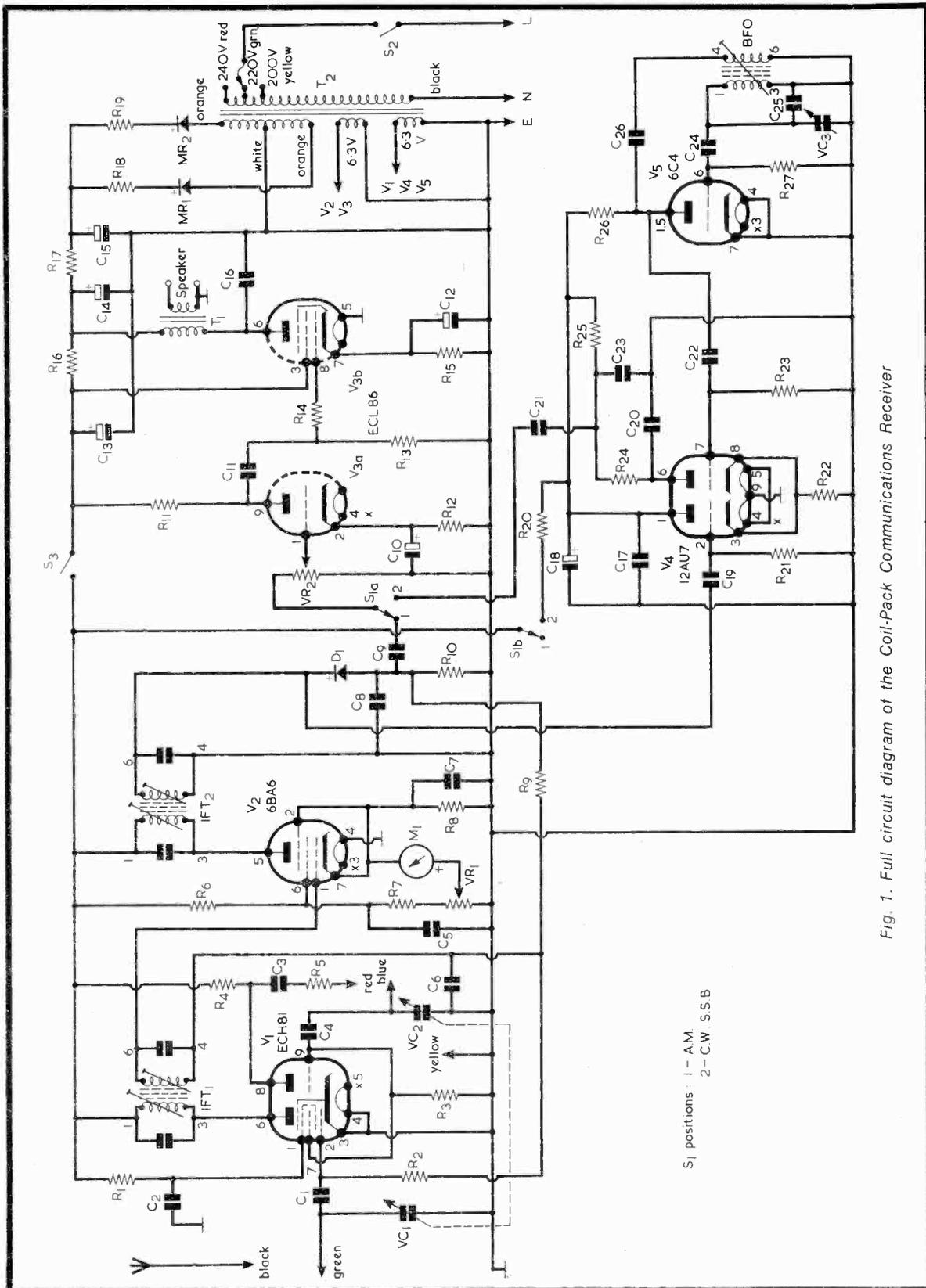*Top view of the receiver. The eight coil-pack trimmers appear
in a row behind the S-meter*



S₁ positions : 1 - AM
2 - C-W SSB

Fig. 1. Full circuit diagram of the Coil-Pack Communications Receiver

COMPONENTS

Resistors

(All fixed values $\frac{1}{2}$ watt 10% unless otherwise stated)

R1	22k Ω
R2	1M Ω
R3	47k Ω
R4	33k Ω 1 watt
R5	150 Ω
R6	27k Ω 1 watt
R7	68k Ω
R8	68 Ω
R9	2.2M Ω
R10	270k Ω
R11	330k Ω
R12	4.7k Ω
R13	470k Ω
R14	47k Ω
R15	180 Ω 1 watt
R16	2.7k Ω 2 watts
R17	1k Ω 5 watts
R18	100 Ω 1 watt
R19	100 Ω 1 watt
R20	22k Ω 1 watt
R21	100k Ω
R22	1k Ω
R23	100k Ω
R24	22k Ω
R25	47k Ω
R26	68k Ω
R27	47k Ω
VR1	500 Ω potentiometer, wirewound linear
VR2	500k Ω potentiometer, log

Capacitors

C1	100pF silver-mica
C2	0.01 μ F disc ceramic, 350V wkg
C3	100pF silver-mica
C4	47pF silver-mica
C5	0.01 μ F disc ceramic, 350V wkg
C6	0.25 μ F paper or plastic foil, 150V wkg
C7	0.25 μ F paper or plastic foil, 150V wkg
C8	250pF silver-mica
C9	0.01 μ F paper or plastic foil, 150V wkg
C10	4 μ F electrolytic, 6V wkg
C11	0.01 μ F paper or plastic foil, 350V wkg
C12	100 μ F electrolytic, 15V wkg
*C13	16 μ F electrolytic, wire-ended, 450V wkg
*C14	8 μ F electrolytic, wire-ended, 450V wkg

*C13, C14 in single can.

C15	8 μ F electrolytic, wire-ended, 450V wkg
C16	0.01 μ F paper or plastic foil, 500V wkg
C17	0.01 μ F disc ceramic, 350V wkg
C18	8 μ F electrolytic, wire-ended, 450V wkg
C19	22pF silver-mica
C20	470pF silver-mica
C21	0.01 μ F paper or plastic foil, 350V wkg
C22	47pF silver-mica
C23	470pF silver-mica
C24	100pF silver-mica
C25	150pF silver-mica, 1%
C26	100pF silver-mica
VC1,2	2 x 500 pF (nominal) Jackson Bros. E2 gang, with feet (Cat. No. VC7, Home Radio)

VC3 15 pF variable, Jackson Bros. type C804

Inductors

IFT1	I.F. transformer type IFT11/465 (Denco)
IFT2	I.F. transformer type IFT11/465 (Denco)
B.F.O.	Coil Type BFO.2/465 (Denco)
T1	Speaker transformer (Cat. No. TO46, Home Radio)
T2	Mains transformer; secondaries 250-0-250V 65mA, 6.3V 1A, 6.3V 1A (Cat. No. TM5, Home Radio)

Coil-Pack

Coil-pack type CP3/F

Valves

V1	ECH81
V2	6BA6
V3	ECL86
V4	12AU7
V5	6C4

Diode, Rectifiers

DI	OA81
MR1	FC116 or 18RA1-1-16-1 (Cat. No. MR32, Home Radio)
MR2	FC116 or 18RA1-1-16-1 (Cat. No. MR32, Home Radio)

Meter

M1	Miniature S-meter, 1mA, f.s.d. (see text)
----	---

Switches

S1(a)(b)	2-pole 2-way, rotary
S2	s.p.s.t. toggle
S3	s.p.s.t. toggle

Valveholders, Sockets

3	skirted B9A holders
1	B9A screening can (for V4)
2	skirted B7G holders
2	B7G screening cans
	Aerial/Earth twin socket strip
	Loudspeaker twin socket strip

Drives, Knobs

1	Slow-motion dial and drive type E898 (Eddystone)
5	black knobs (Cat. No. KN84C, Home Radio)
4	pointers (Cat. No. KN88D, Home Radio)
	Flexible shaft coupler
	Solid shaft coupler

Miscellaneous

1	chassis, type I, L 6 $\frac{1}{2}$ in., W 10 $\frac{1}{2}$ in., D 2in. (H. L. Smith & Co.)
1	case type W, 12 x 7 x 7in. (H. L. Smith & Co.)
1	2-way tagstrip
2	3-way (centre-earthed) tagstrips
2	4-way (1 earthed) tagstrips
4	plastic feet (Cat. No. Z146, Home Radio)
	3-core mains lead
	Bolts, nuts, connecting wire, etc.

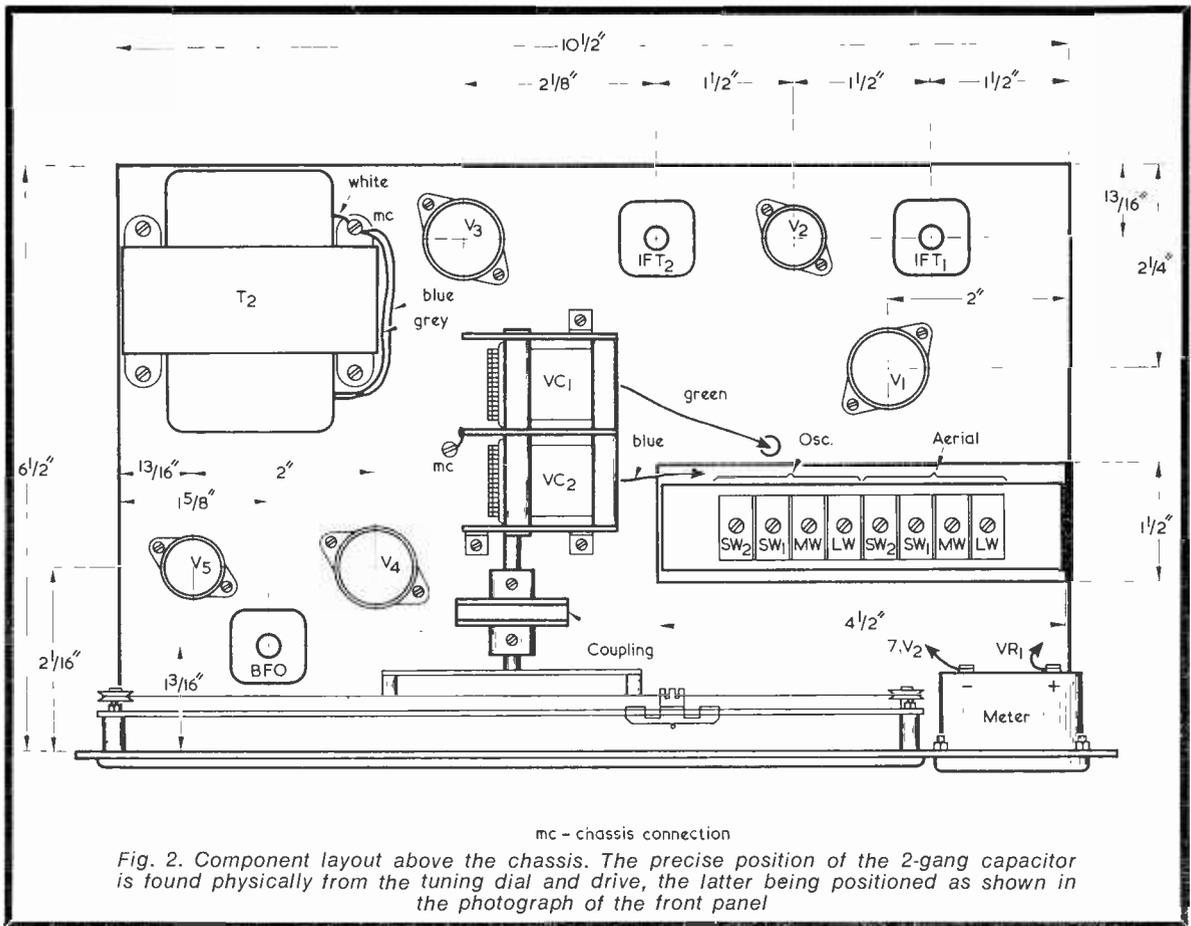


Fig. 2. Component layout above the chassis. The precise position of the 2-gang capacitor is found physically from the tuning dial and drive, the latter being positioned as shown in the photograph of the front panel

Audio Amplifier. V3 is a 2-stage amplifier, with VR2 acting as the volume control or audio gain control. Output is coupled to the external speaker by the speaker matching transformer T1. It should be noted that the receiver should not be operated without a speaker connected, as excessively high a.f. voltages can then appear across the transformer primary.

Product Detector. V4 is the product detector, and is employed for c.w. and s.s.b. signals only. With s.s.b. signals the carrier frequency, eliminated before transmission, is supplied by oscillator V5, and mixing in the double-triode V4 re-inserts this carrier so that audio output is available through C21. The performance of this type of detector for the reception of s.s.b. signals is much superior to that given by using a b.f.o. only, as was often done with the older type of communications receiver.

S1(a) selects the a.m. detector D1 or product detector V4, while S1(b) applies h.t. to V4 and V5. If desired the receiver may be built as shown but with V4, V5 and their immediate components omitted, and initially used for reception of ordinary a.m. signals only. V4 and V5 could then be added later, if wished, without disturbing existing circuitry.

Power Pack. The mains transformer T2 has two 6.3 volt 1 amp secondaries. One supplies the heaters of V2 and V3. The other supplies the heaters of V1, V4 and V5.

The h.t. secondary connects to two contact-cooled rectifiers, MR1 and MR2, and then to the surge limiting resistors R18 and R19. Smoothing for the anode circuit of V3 is carried out by C15, C14 and R17, while the screen-grid of V3 and earlier stages have additional smoothing, given by R16 and C13.

S3 interrupts the h.t. supply to the early stages only. This gives instant on-off switching, or a 'standby' position, with heaters at operating temperature. Such a feature is of most use when operating the receiver in conjunction with transmitting equipment, but it also allows V3 to be used as a 2-stage audio amplifier by taking the audio signal from a pick-up, Morse oscillator, or other equipment, to VR2.

S2 is the mains on-off switch.

CHASSIS PREPARATION

The positions of valveholders and other items can be seen from Fig. 2. The valveholder holes are best made with a screw-up chassis cutter - $\frac{5}{16}$ in. holes are required for B7G valveholders and $\frac{3}{16}$ in. holes for B9A. Valveholder orientation may be determined from Fig. 3. Mark, through each holder, fixing holes to drill for the 6BA bolts which will secure them later.

The coil-pack is set back 2 in. to clear the drive,


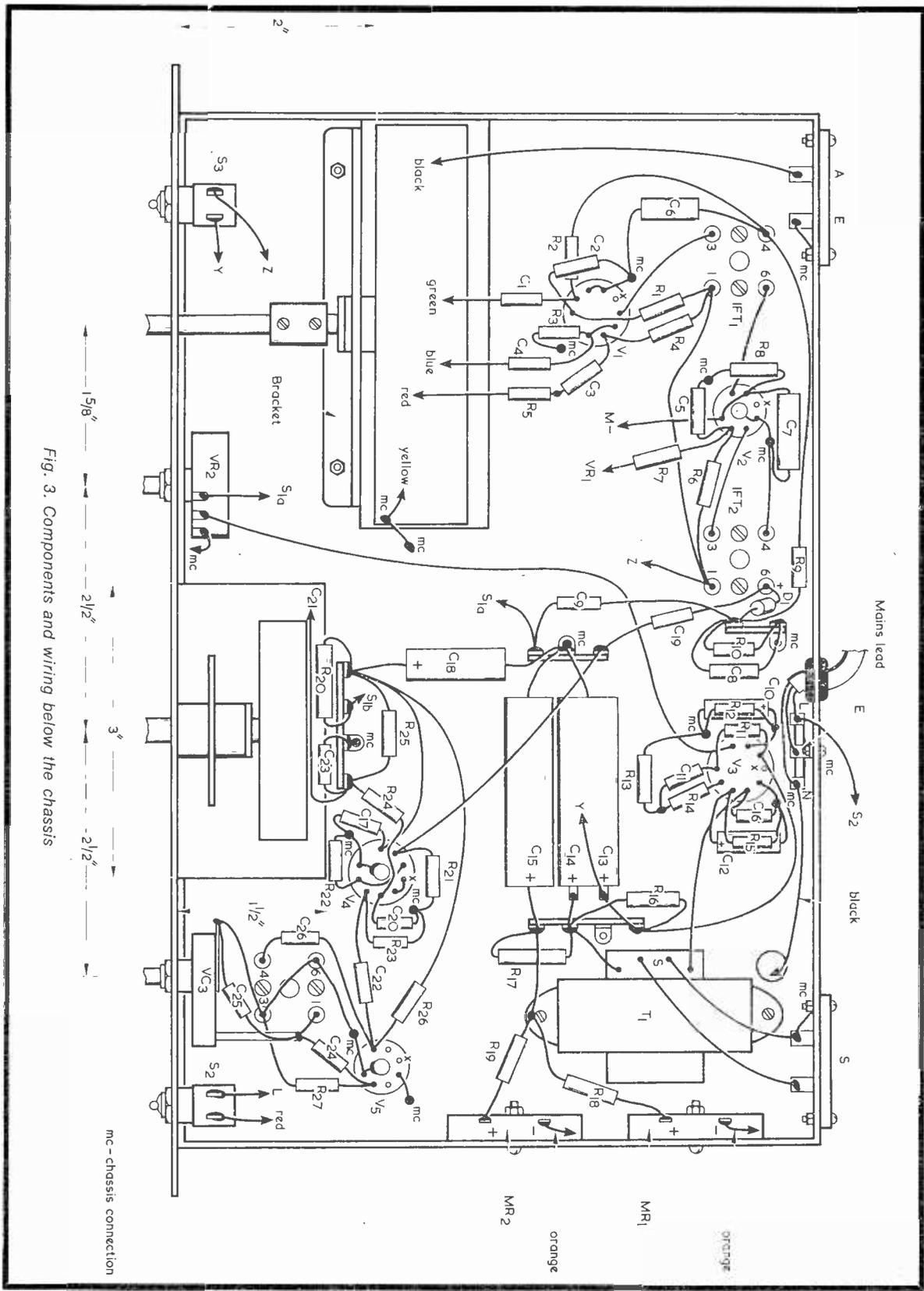


Fig. 3. Components and wiring below the chassis

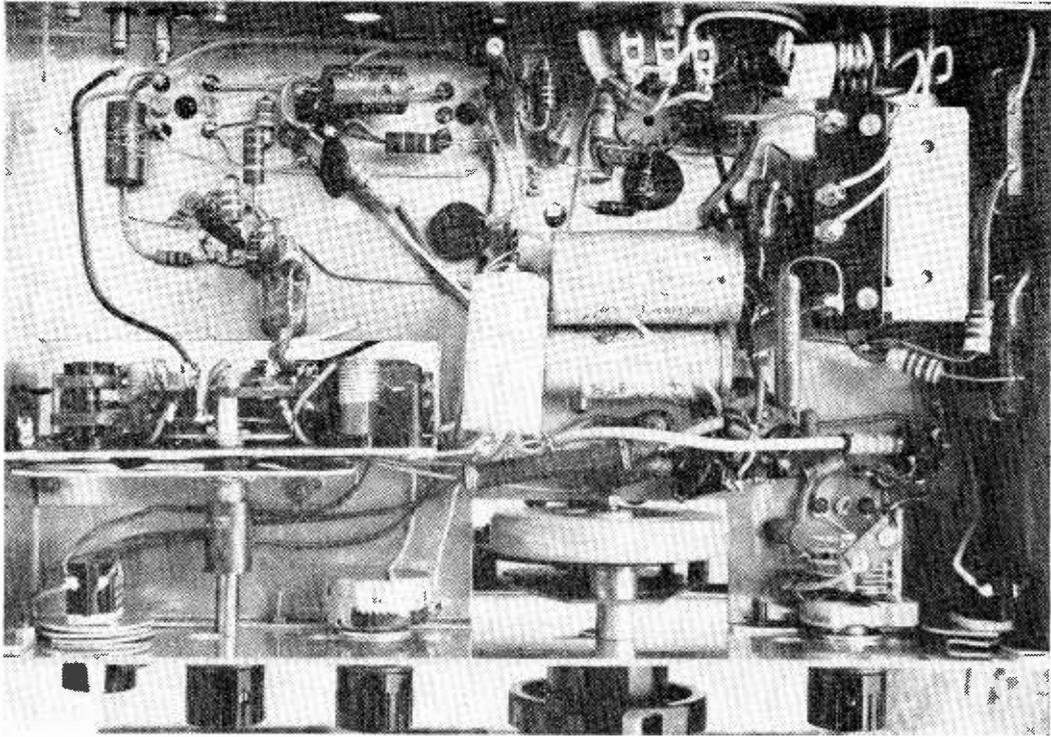

Wiring and components below the chassis

and fits in an aperture measuring $4\frac{1}{2}$ in. by $1\frac{1}{2}$ in. This can be cut by drilling a row of small holes close together where necessary to enable a metal saw to be inserted, smoothing the edges afterwards with a file.

Drill holes for IFT1, IFT2 and the b.f.o. coil as illustrated in Fig. 3. Make sure there will be adequate clearance for the pins.

Holes are drilled or punched in the back runner for the socket strips and mains lead. Leads from T2 pass down through holes which are clear of T1 below. All holes through which wires pass, including those from R7 to VR1 and from the coil-pack to VC1, should be fitted with grommets.

An opening about 3 in. by $1\frac{1}{2}$ in. is cut in the front of the chassis, to clear the drive flywheel. See Fig. 3. The chassis is a type with small front flanges, to which the panel is bolted.

If any small holes are missed, these can be drilled later. But the large holes should be made before mounting any components, and metal fragments should be cleaned away.

An important point is concerned with the output transformer T1. The type specified is available from a number of different manufacturers, and individual transformers may be supplied either with wire lead-outs or with tags. It is necessary to ensure that the transformer, when positioned as in Fig. 3, does not project below the bottom surface of the chassis, and if it has wire lead-outs this requirement should be

satisfied without any further difficulty. If the transformer has tags, check that these will be well clear of contact with the inside of the metal case when the transformer is fitted. This may necessitate bending the tags down, and/or bending the tagstrip mounting. If clearance from the tags to the case is still likely to be small, a piece of thin Paxolin may be taped over them later, after connections have been made. In cases where this approach is not satisfactory, unsolder the coil lead-outs from the transformer tags and add lengths of thin flex to them, covering the joints with sleeving. Avoid putting strain on the lead-out wires. The lengths of flex can then connect to the appropriate circuit points in the receiver. Yet another alternative consists of mounting the transformer on the side runner of the chassis. One rectifier would then need to be moved a little nearer to the front, whilst the other could be fixed in the position taken up by the speaker socket strip, the latter being shifted a little nearer the centre at the rear. It is doubtful whether these precautions will be needed in most instances, but it is of course necessary for the reader's attention to be drawn to them. The points just outlined should be checked before drilling the holes for T1, the rectifiers and the speaker socket strip. If doubt exists as to which connections are for primary and secondary, the primary will exhibit a resistance of several hundred ohms, as checked with a testmeter, whilst the secondary will have nearly zero ohms.

PANEL AND COIL-PACK

Holes for the drive are marked by using the paper template supplied with it. The large window is cut in a similar way to the coil-pack aperture, afterwards levelling to a scribed line with a file.

The tuning meter occupies a hole made with an adjustable washer or tank cutter, large screw-up punch, or by drilling a ring of small holes and finishing with a half-round file. Also drill or punch holes for the panel controls.

Note that the case listed is made in such a way that the bottom edge of the panel must lie about $\frac{1}{4}$ in. lower than the bottom of the chassis.

The drive is next fitted, and panel and chassis are bolted together. Carefully line up the spindle of the ganged capacitor with the drive, using spacers, washers or extra nuts to raise the capacitor. Couple up the drive and capacitor with the flexible shaft coupler. Mark and drill for the fixing screws. Solder blue and green leads to the lower fixed vane tags of VC1 and VC2, as in Fig. 2, then finally mount the capacitor. Check that the drive works freely. Connect a lead from the centre rotor tag to a tag bolted to the chassis, as in Fig. 2.

The coil-pack is mounted on a flanged bracket about 4 in. by 1 $\frac{1}{2}$ in. and with a $\frac{1}{2}$ in. flange. See Fig. 3. The bracket is fixed to the chassis by three bolts, for rigidity. A solid spindle coupler connects to a length of $\frac{3}{4}$ in. diameter rod (which was actually unwanted excess from the spindle of the volume control).

A black lead from the coil-pack is run to the aerial socket, as in Fig. 3. The green lead from VC1 (Fig. 2) passes down through a hole in the chassis, and is soldered to the green tag of the pack, to which C1 is also soldered. See Fig. 3. The blue lead is for VC2, and C4 is also connected here. R5 is soldered to the red tag. A length of connecting wire is soldered to the yellow tag of the pack, and to the adjacent coil-pack chassis tag. From here, the lead runs to a nearby tag bolted to the receiver chassis.

The trimmers are above the chassis, as in Fig. 2, and the pack projects $\frac{1}{4}$ in. above its surface, so that the cores of the four coils near the trimmers can be reached with a trimming tool above the chassis.

The controls VR3 and VR2 are fitted at the same horizontal level as the coil-pack spindle. The two switches are slightly lower and are level with each other. VR1 and S1 are on the same vertical line as the centre of the meter.

I.F. TRANSFORMERS, B.F.O. COIL

Mount the i.f. transformers so that the numbered pins appear as in Fig. 3. Sleeving may be put on the pins to avoid possible short-circuits due to fragments of solder or other causes.

As mentioned, the receiver can be built and used (for a.m. only) with V4, V5 and the accompanying items omitted, these being added as a later project.

MAINS TRANSFORMER

Bare and connect the white, blue and grey leads of the mains transformer to a tag bolted to the chassis, as in Fig. 2. Two orange leads emerge with the white lead. Pass these down through the chassis and solder them to rectifiers MR1 and MR2. These

are contact-cooled rectifiers, bolted direct to the chassis.

Stout enamelled orange and pink leads emerge on the other side of the transformer. These are from the 6.3 volt windings. Take the pink lead through and solder it to pin 4 of V3. This winding also supplies the heater of V2. The orange wire runs to V4 heater tag, which is also connected to V1 and V5.

The primary leads are black, yellow, green and red. Take black to a tagstrip at the chassis rear, as in Fig. 3, used also to anchor the Neutral lead of the mains cord. For 240 volt mains, take red to S2. For 220 volt mains, use green instead, and for a 200 volt supply connect yellow to S2. Tape up separately the ends of the unwanted leads (e.g. green and yellow with 240 volt mains) so that they cannot come into contact with each other or other items.


Connect S2 to L (Live) at the mains cord tagstrip at the rear of the chassis. Use a 3-core cord, with blue for Neutral, brown for Live, and green-yellow striped for Earth, running the latter to the receiver chassis, as in Fig. 3. The mains connection is best made with a 13 amp plug having a 2 amp or similar fuse. The mains cord should pass through a rubber grommet. All leads should be adequately insulated, especially where they pass through the chassis from T2.

RECEIVER WIRING

The wiring in Fig. 3 can next be carried out, and it is useful to have several colours of connecting wire or sleeving for the various circuits. Run heater and h.t. wiring against the chassis. Similarly deal with the wiring in the grid and anode circuits of V2, and the wires running to VR2 and S1(a).

The wire ends of resistors and small capacitors are cut so that they are reasonably short and direct.

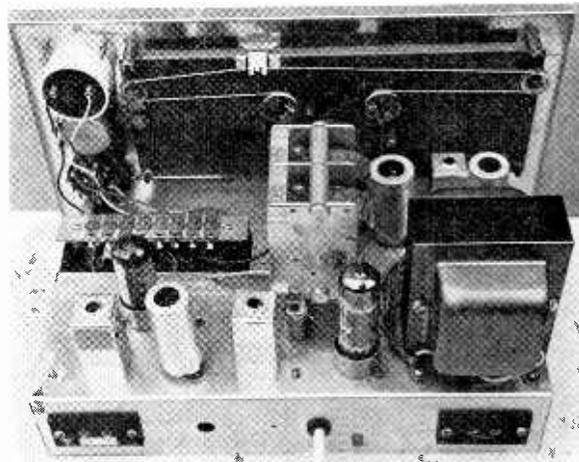A number of small tagstrips are used to secure various parts and leads. All the points marked 'MC' are connections to solder tags bolted to the chassis. Note the polarity of diode D1 and the electrolytic capacitors.



A top rear view. Note the spacing washer under the rear foot of the 2-gang tuning capacitor

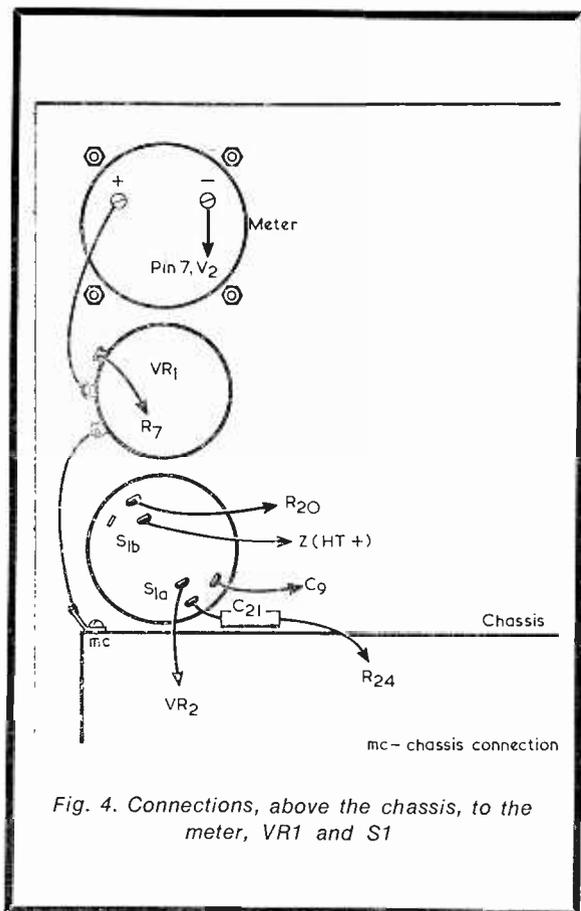


Fig. 4. Connections, above the chassis, to the meter, VR1 and S1

When wiring T1, identify the primary and secondary connections, if these are not marked, in the manner already discussed.

A.M./S.S.B.-C.W. SWITCH

Section S1(a) of this switch transfers the volume control VR2 from C9 (a.m. detector) to C21 (product detector). See Fig. 4. In the latter position S1(b) closes the h.t. circuit so that h.t. is applied to V4 and V5.

No screening of audio circuit was necessary, provided these were kept near the chassis when wiring S1(a) and VR2, etc.

TUNING METER

Fig. 4 shows connections for VR1 and the meter. Coloured leads run to pin 7 of V2, and to VR1 and R7.

The meter gives a reading when the receiver is first switched on, but falls back as the cathodes reach working temperature. With no aerial connected or no signal tuned in, rotate VR1 until the meter reads zero.

All receiver tuning meters, or S-meters, give an indication which depends on the strength of the signal at the aerial terminal of the receiver. This means that readings are *comparative*. A transmission which, for instance, gives a reading of S5 with a short indoor aerial may easily give S9 or over with an improved aerial.

Where any external means of tuning or matching the aerial will be used, adjust the tuner for maximum meter reading. This also applies to the tuning of a pre-amplifier. Where alternative aerials are available, the better aerial (for the particular frequency being received) will give the higher reading.

(To be concluded)

EUROCON '71

Over 170 papers from 20 countries are promised for the first EUROCON Convention, and it has already become a new international meeting of major importance. It will be held in Lausanne, Switzerland, on 18th to 22nd October, 1971.

The Convention subjects are information processing in large systems, long distance communications, solid state circuits, distribution of electric power, and biomedical engineering. In addition, this will be the first convention to give detailed consideration to electronic watches, which may well revolutionise the watch making industry within the next decade.

Special features of the Convention are student and tutorial lectures as well as survey papers in each subject for the non-specialist.

EUROCON 71 is organised by Region 8 of The Institute of Electrical and Electronics Engineers, and supported by national societies with a number of companies providing financial support. Further information is available from the EUROCON 71 Secretary, 24 Chemin de Bellerive, CH-1007 Lausanne, Switzerland.

The survey papers will be arranged in sequence, so that all of them can be attended by non-specialist participants and by students. Further student facilities are a much reduced registration fee, at least 12 tutorial lectures, and arrangements for accommodation in the homes of Swiss students.

The sessions on electronic watches include the choice of systems, time bases, circuitry, and display, and herald a change from the traditional precision manufacture of the mechanical watch to the wholly electronic watch.

The papers on display will cover techniques applicable to pocket size computers.

Papers on information processing in large systems cover the use of computers in traffic control, radio astronomy, high energy physics, space systems, meteorology, and education.

Among the subjects covered by papers on biomedical engineering are ongoing research, health care systems, automated diagnosis, a television-computer system to study micro-organisms, implanted micro-electronic devices, standards, safety, and education and training.

COMMUNICATION AND ELECTROLYSIS

by

D. P. NEWTON, B.Sc.

A simple communications system which establishes a link with the start of the nineteenth century

COMMUNICATION AND ELECTRICITY HAVE LONG been linked. We all know our debt to Marconi, Fleming, de Forest and Edison, and yet their work did not begin in a vacuum. Theirs was the century of the inventor – a few made it, most didn't. There was Salva who planned to use the twitch of a frog's leg as a detector of galvanism and so devise a communicator based on this. More recently we have Baird's television, only to be replaced by the more

Von Sommering's ingenuity turned, therefore, to telegraphy by electrolysis. His final device had one wire for each letter of the alphabet situated in a line along the base of a tank containing acidified water. These wires could be made negative with respect to a bar in the liquid above them. When the appropriate switch was pressed, a column of bubbles would rise from the corresponding wire to the bar. In this way, he was able to send signals over considerable distances, independent of weather or time of day.

Such a device can be constructed fairly easily today. Figs. 1 and 2 show the receiver. A trough made from Perspex sheet about 3 to 5mm. thick is constructed with the dimensions given. Thirteen letter strips are made from copper foil, each being 6cm. by 0.5cm., and are shaped as in Fig. 3. These are glued along one side of the trough using a rubber-based glue. A brass rod, about 50cm. in length and 2mm. in diameter, is bent as shown in Fig. 1 to form the positive rail. The letter strips are labelled as in Fig. 2. Note that single strips represent the first half of the alphabet while two together represent the letters of the second half, apart from 'Z'. Any three may be taken for 'Z'. This allows the number of strips needed to be halved. The trough is now almost filled with dilute sulphuric acid.

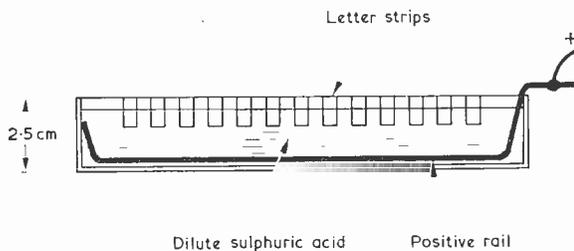


Fig. 1. Side view of the Perspex trough, illustrating the letter strips and positive rail

sophisticated cathode ray tube. But both contributed to the pool of knowledge; the basic idea was there. Salva, indeed, saw that the escape of gases at an electrode in electrolysis could be the basis of a means of communication, but this idea was dormant until von Sommering completed such a telegraph in 1809.

SIGNAL TRANSMISSION

Galvanism could be transmitted over considerable distances but the problem was one of how to make the signal apparent. Electricity was only incompletely understood and the relationship between magnetism and electricity was not well known until Oersted's work in 1820, so Wheatstone's telegraph was still in the future. Similarly, the discovery of radio waves was not to happen until 1888 with Hertz.

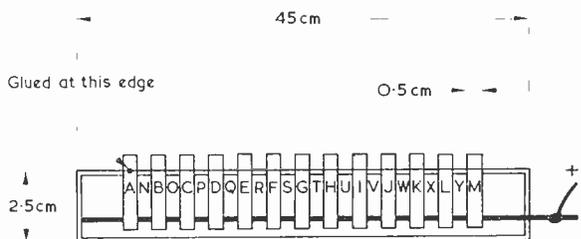


Fig. 2. This view from above shows the letters which the strips represent

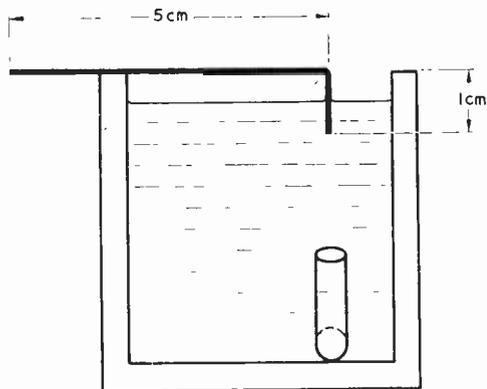


Fig. 3. The letter strips are shaped in the manner shown in this end view

The sulphuric acid should be diluted to one part of concentrated acid in ten parts of water, and most chemists will provide this. Readers without experience of concentrated sulphuric acid should not attempt to carry out the dilution process themselves. Take all sensible precautions whilst handling the acid, ensuring that it is kept away from clothes, the body and, in particular, the eyes. Corrosion of the letter strips and brass bar is not great at this level of dilution and the trough can, in any case, be emptied and washed out after a period of use has been completed.

THE TRANSMITTER

The transmitter consists of 13 switches, one pole of each being connected together, as in Fig. 4. These switches may be constructed from springy metal, as in Fig. 5. Alternatively, of course, normal switches purchased from a component retailer can be used. The switches are labelled in the same manner as the letter strips, a wire from each being connected to the corresponding letter strip by means of a wire ter-


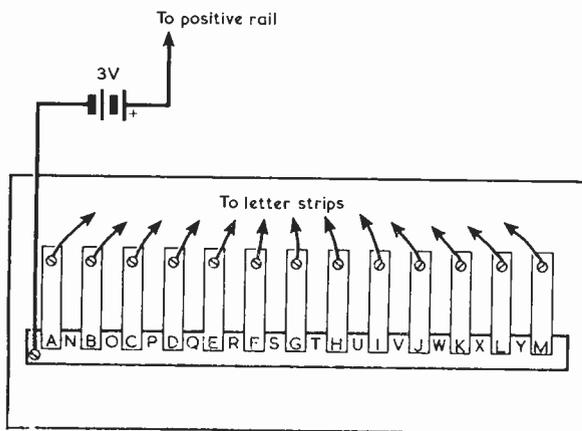


Fig. 4. A suitable construction for the transmitter. The switch strips are mounted on a base made of insulating material

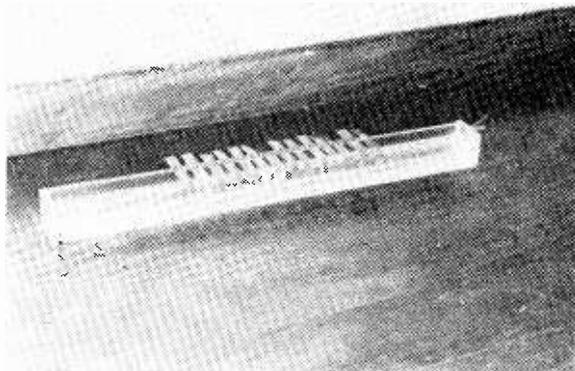

A practical example of the receiver assembly

minated in a crocodile clip. The other side of the switches is connected to the positive rail via a 3-volt battery.

When a switch is pressed, bubbles appear at the corresponding letter in the receiver. For a letter such as 'S', the letters 'F' and 'G' would be pressed together. The diagrams show that the receiver is 'upside down' when compared with that of von Sommering. This proved to be a convenient arrangement since it allows strips to be easily replaced if damaged and it allows any build-up of gases around the cathodes to be dispelled by simply vibrating the free end. The distance between the transmitter and the receiver can be considerable, but this soon shows the disadvantage where fourteen wires are involved.

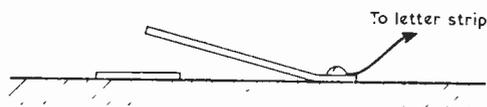


Fig. 5. How the switches of Fig. 4 are made up

Like Baird's equipment, von Sommering's telegraph was superseded and almost forgotten. In making such a model now we little appreciate the difficulties experienced at that time. The wires themselves had each to be carefully bound and insulated. Even batteries were uncertain and expensive pieces of equipment, still being stacked with dissimilar metals like the original voltaic pile. However, coming as it does from the times of George III, Napoleon and the birth of Dickens, the telegraph remains a fascinating idea and provides an amusing model. ■

'F.E.T. REFLEX RECEIVER'

In 'F.E.T. Reflex Receiver', which appeared in the August 1971 issue, the references should have included earlier articles describing the basic reflex circuit incorporated. These were 'Simplicity and Sensitivity with Two Transistors' and 'Simplicity and Sensitivity with Three Transistors'. They were both by Sir Douglas Hall, and were published in the April 1964 and November 1965 issues of *The Radio Constructor* respectively.

CURRENT SCHEDULES

Times = GMT

Frequencies = kHz

★ ITALY

RAI now radiates three programmes daily in Russian. From 0330 to 0345, from 0535 to 0555 and from 1605 to 1625 on **6075** (60/100kW) 49.38 metres; **7275** (60/100kW) 41.24m; **9575** (60/100kW) 31.33m; **11810** (60/100kW) 25.40m and **11905** (60/100kW) 25.20m.

★ AUSTRALIA

The European Service of Radio Australia transmission from 0645 to 0745 may now be heard on **11765** (100kW) and on **15125** (100kW), 25.50 and 19.82 metres respectively. After 0745, the Asian and Pacific Services are radiated on these two channels. Another English transmission from R. Australia can be heard from 0700 to 0800 on **9680** (10kW) from Melbourne - if you are lucky!

Afternoon transmissions from the station at Darwin, directed to Asia, may be heard from 1500 to 1730 on **6055** (250kW) 49.55m and on **6100** (250kW) 49.18m.

★ CANADA

Radio Canada, with the new 250kW transmitters in service, can be heard with a programme in German from 1735 to 1815 on **15325** 19.58m.

★ GAMBIA

Radio Gambia has an extended schedule on the regular **4820** (3.1kW) 62.24m channel. From Mondays to Fridays 0630 to 0800, 1200 to 1300 and

from 1700 to 2300. Saturdays from 0630 to 0900, from 1200 to 1400 and from 1700 to 2300. On Sundays from 0900 to 1400 and from 1700 to 2300.

★ ALBANIA

Radio Tirana may be heard with a programme in English from 0000 to 0028 on **9780** (50/500kW) 30.67m; from 0233 to 0252 on **6210** 48.31m and from 0100 to 0139 on **9780**.

★ CZECHOSLOVAKIA

Radio Prague radiates a 55 minute programme, in English, daily to Europe, New Zealand and Australia at 0700 as follows - **6055** (200kW) 49.55m beamed to Europe; **9505** (200kW) 31.56m beamed to Europe and the Far East; **11800** (100kW) 25.42m beamed to Europe and Far East; **15310** (100kW) 19.60m to Europe and Far East; **21690** (100kW) 13.83m to Europe and Far East and **21700** (100kW) 13.82m beamed to the Far East and Africa.

The Afro-Asian Service of Radio Prague, also of 55 minutes duration, to East Africa and Asia, is from 1530 to 1625 on **6055**, **11990** (100kW) 25.02m, **15240** (100kW) 19.69m, **17840** (100kW) 16.82m and on **21735** (100kW) 13.81m.

To West and Southern Africa, from 1730 to 1825, on **5930** (100kW) 50.59m, **7345** (100kW) 40.85m, **9605** (100kW) 31.23m, **11990**, **15240** and on **17840**.

★ GHANA

The Ghana Broadcasting Corporation has an English Service, beamed to Europe, from 2045 to 2215 on **9545** (100kW) 31.43m, with a newscast at 2045 and at 2100.

Acknowledgements:- Our Listening Post, SCDX.

LATE NEWS

Times = GMT

Frequencies = kHz

★ AMATEUR BANDS

● PUERTO RICO

To get Zone 8 the hard way, why not brave the QRM of 'forty' and try around midnight for the CW signals of KP4CBI on, or around, **7042**?

● SURINAM

PZ1AD is a devotee of the key and his signals are often to be heard on 14MHz. Logged recently on **14035** at 2035.

● FAROE ISLANDS

Signals from these islands are not all that plentiful but OY2EL has been very active of late on **14065**, or thereabouts, using CW at 2000.

● LABRADOR

VO2AW is another CW man, listen at the 'high' end of the 14MHz CW band (**14098**) around 2000, to log this one.

● BRAZIL

Signals from Brazil are in profusion but at the CW end of 14MHz listen for PY7AHO on, or around, **14030** where he usually works strings of Europeans. One of the best 'fists' in Brazil.

● 21MHz

A recent short morning session at the CW end ended with the following 'in the bag', JAIANG, JAIKRU, JAI1MQM, JAI1OMH, JAI1QIJ, KZ5EK, PJ2RB, PZ1AV and ZS6AJS.

OCTOBER 1971

★ BROADCAST BANDS

● MAURITIUS

Forest Side is reported to have moved from the **4850** channel to that of **4895** (10kW), heard when signing off at 1830. From 1430 to 1830 (according to the schedule) the programme is in English and French, with news in English at 1800.

● INDIA

The new 250kW transmitters at Aligarh are radiating on the following channels - **9590**, **11755**, **11790**, **11850**, **11945**, **15160**, **15335**, **15340** and on **17705**. Those at New Delhi radiate on **11740** and on **15205**.

● BOLIVIA

CP97 Radio Pirai, Santa Cruz de la Sierra, has changed from the 90 metre band frequency of **3320** to that of a 31 metre band channel, **9607** (1kW).

● NEW CALEDONIA

Noumea is reported by BADX on the old channel of **3355**, a move from the listed **7170**. Also in parallel on **4913**, **9510** and **11710**.

● INDONESIA

BADX (British Association of Dx'ers) report a new RRI transmitter on **3900** around 1300, location - Palangkaraya.

● CEYLON

BADX also report that the Sinhala Service commences at 0000 on **3385**.

Acknowledgements:- BADX, Our Listening Post, SCDX.

THE 'MINIFLEX' MARK IV PORTABLE RECEIVER

by

SIR DOUGLAS HALL, K.C.M.G., M.A.(Oxon)

Employing three transistors, including an f.e.t., this medium and long wave receiver provides a loudspeaker output level at the exceptionally low battery current of 3mA. Construction is compact, with all circuits built virtually around the loudspeaker itself

THIS IS A SMALL PORTABLE receiver using a further developed form of the author's Miniflex circuit.* It is sensitive and selective, and the modest output is ample for those who use a receiver of this type for their own entertainment rather than as a source of annoyance to others. It gives continuous coverage from 190 metres to 2,200 metres.

An unusual feature of the design is the use of a field effect transistor in the output stage. As this device is fully loaded, in the present design, by less than 0.5 volt input, its gate is protected very simply by two silicon diodes connected back to back.

CIRCUIT DESIGN


The circuit is shown in Fig. 1. S1, the wave-change switch is in position for medium waves. The signal is picked up by L1, wound on a ferrite rod, and applied to the base of TR1 which is wired as a common collector device offering a high input impedance and allowing the whole of the tuned circuit to appear at the base. The output of TR1 is across R1 which is the input resistor for TR2, a common emitter high frequency amplifier. The further amplified output appears across the choke L3 and is demodulated by D1 - a high impedance selenium diode which must be used. *Do not attempt to use a silicon or germanium diode in this circuit.*

Audio signals now appear at the base of TR1 which, in conjunction with TR2, forms a super alpha pair resulting in a very low impedance across R2. Thus, it is possible to use a high step-up transformer between R2 and the input of TR3, giving a voltage gain of 25 times. Because of the damping of its windings by R2 and the output of TR2, this component will not introduce distortion.

Direct voltage to operate TR1 and TR2 is taken from the source

bias current of TR3. This receiver has a very small appetite for batteries!

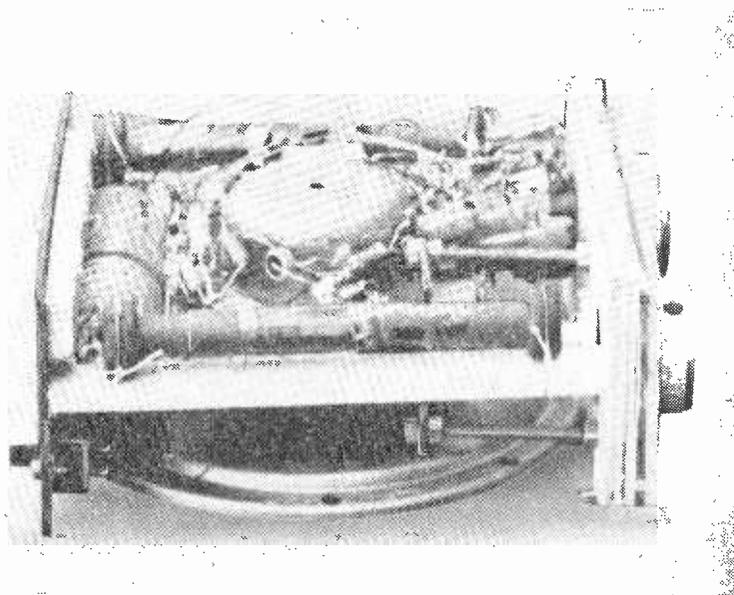The original output transformer employed in the prototype is a Radiospares miniature valve type with a ratio of 50:1 and intended for use with battery valves of the DL94 type. This offers a load of about $8k\Omega$ to the output of TR3. Since completing the design the writer has, however, learned that this particular transformer is liable to go out of production, and so he



Side view, illustrating how the platform and the front and rear panels appear in relation to the speaker

*Sir Douglas Hall, 'The "Miniflex" Dual Purpose Personal Receiver', *The Radio Constructor*, June 1968; Developing The "Miniflex" Circuit', *The Radio Constructor*, July 1968.

has checked alternative components for suitability. This article will, in consequence, describe the prototype circuit with the Radiospares transformer since, even if it is out of production, there may still be stocks on dealers' shelves or in constructors' spares boxes. At the end of the article instructions will then be given for an alternative output transformer arrangement, which can be used by readers unable to obtain the Radiospares transformer. It should be mentioned, incidentally, that Radiospares components can only be obtained via retailers. Radiospares do not deal direct with individual constructors.

Returning to Fig. 1, positive audio frequency feedback is made available by feeding back a small proportion of the amplified signal in the secondary of the output transformer to the gate of TR3. L4 prevents excessive feedback of the highest audio frequencies though the higher frequencies will still be favoured. This is an advantage in counteracting a loss of these frequencies which takes place due to sideband cutting when full radio frequency reaction is being used on weak stations. VR4 sets the degree of audio feedback to a suitable level at high settings of VR2. Setting back VR2, as will be done when receiving powerful stations, reduces the audio frequency feedback because of the damping of the primary of T1 by VR2 when this is set to a low level. It will be seen that VR2 functions as an audio frequency volume control in addition to being

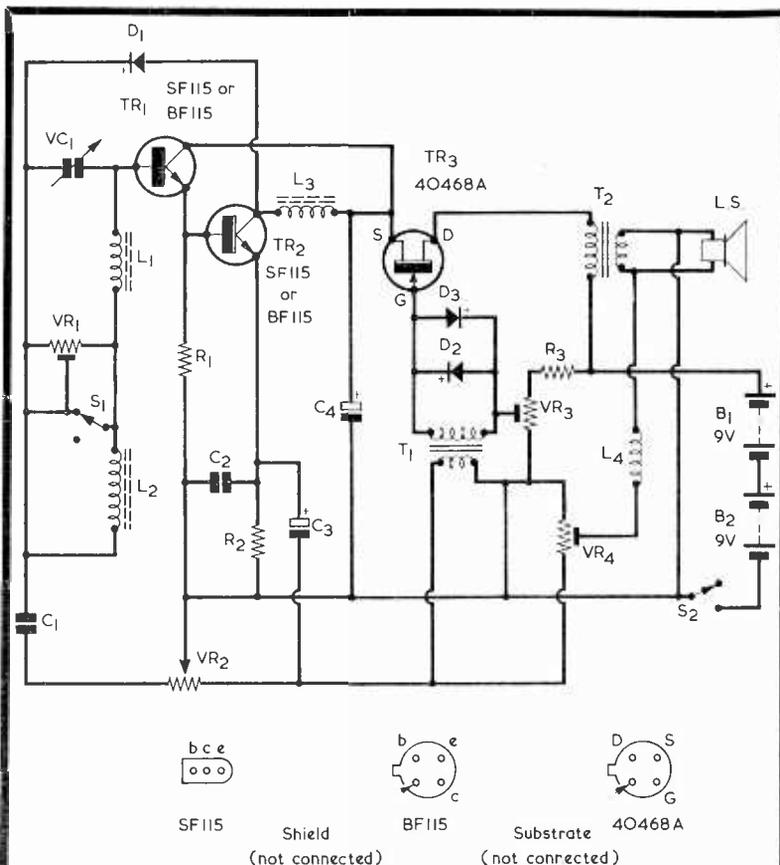


Fig. 1. Circuit diagram of the 'Miniflex' Mk. IV receiver. Note that the output stage incorporates an f.e.t.

COMPONENTS

Resistors

(All fixed values ¼ watt 10%)

R1	5.6kΩ
R2	100Ω
R3	150kΩ
VR1	500kΩ potentiometer, miniature preset
VR2	250Ω potentiometer (see text)
VR3	25kΩ potentiometer, skeleton preset
VR4	500Ω potentiometer, miniature preset

Capacitors

C1	1,000pF silver-mica
C2	0.1μF paper or plastic foil
C3	320μF electrolytic, 2.5V wkg
C4	320μF electrolytic, 2.5V wkg
VC1	300pF variable, Dilemin (Jackson Bros.)

Inductors

L1	(see text)
L2	(see text)
L3	2.5mH r.f. choke, type CH1 (Repanco)
L4	19mH r.f. choke, type RFC7 (Denco)
T1	Microphone transformer, type TT53 (Repanco)
T2	Output transformer (Radiospares miniature valve type or Repanco types TT49 and TT46 - see text)

Semiconductors

TR1, TR2	SF115 or BF115
TR3	40468A
D1	Half-wave meter rectifier type M3 (Henry's Radio)
D2, D3	Silicon 'bias diodes'

Switches

S1	slide switch, standard size
S2	slide switch, standard size

Batteries

B1, B2	9-volt batteries type PP4 (Ever Ready)
--------	--

Speaker

3Ω moving-coil, 5in. diameter (see text)

Miscellaneous

- 2 ferrite rods, 4in. by ½in. dia.
- 2 knobs
- Epicyclic ball drive with flange, type 4511/F (Jackson Bros.)
- 18-way tagboard, Radiospares standard size (Cat. No. BTS10, Home Radio)
- Transistor holder
- Spindle coupler
- 2-off 2in. 4BA countersunk bolts
- ½in. plywood, Paxolin, Perspex, Fablon or Contact, nuts, bolts, screws, etc.

a radio frequency reaction control.

Some of the radio frequency signal will bypass D1. This will appear at the bottom end of the tuned circuit, and C1 is chosen to give a suitable capacitive tapping into the circuit to provide reaction in the Colpitts configuration. The half of VR2 which connects to C1 varies the impedance between the bottom of the tuned circuit and the negative supply rail. All signals can be set at any value between zero and oscillation point.

Long waves are received with S1 in the open position, this bringing L2, on its own rod, into circuit. A damping resistor, VR1, is set so that oscillation starts with VR2 near maximum.

For best results TR1 and TR2 need to pass a current of about 3mA at a little over 2 volts d.c. Nearly all of the 3mA current passes through TR2. TR3 has its bias adjusted so that it passes 3mA, and TR1 and TR2 become the necessary source bias 'resistor' for TR3. They are consequently fed with 'free' current. As a little over two volts is more bias than the source of TR3 requires in order for this device to pass 3mA, a small amount of positive bias, of the order of one volt, is applied to the gate by means of the potentiometer network given by VR3 and R3, VR3 being adjusted so that the f.e.t. passes 3mA. If the Radiospares output transformer is used this will represent a drop of 0.75 volt across its primary, which has a resistance of 250Ω.

Although an 18-volt supply is used, the low current of 3mA allows very small batteries to be employed economically, and the cost of operating the receiver is low. A small battery passing 3mA will last more than twice as long as it would if it passed 6mA.

FRAME ASSEMBLY

Construction should start with making the plywood and Paxolin pieces illustrated in Fig. 2, starting with the Paxolin plate for VCI which is shown in Fig. 2(a). The two 6BA clear holes here are for mounting, later, the tuning capacitor VCI. The diagram shows these as being spaced by 0.6in. but, to be precise, the mounting centres for the capacitor specified are at 0.625in. The constructor is not expected to drill Paxolin to dimensions involving thousandths of an inch, but he will find it helpful to verge slightly on the generous side so far as the spacing between the two holes is concerned. The two 4BA clear holes are drilled at the points indicated; their positions do not have to be measured precisely.


When the Paxolin plate has been cut and drilled it should be put on one side and the plywood platform shown in Fig. 2(b) should be made. A fretsaw is the proper tool to use for all the cutting operations. The large central hole in the platform is for the speaker magnet and should be just slightly larger than the diameter of the magnet of the actual

speaker to be used, in order that the platform can offer a reasonably tight fit on the magnet after several turns of Sellotape have been wound round it. The magnet of the speaker should have a diameter not greater than 1½in., and preferably less. This is because the magnet hole in the platform, if too large, will too closely approach the adjacent corner of the 1in. by 1in. recess. In all instances, care has to be taken to ensure that an adequate amount of wood is retained at this point.

Next, cut the front panel, also of plywood, as shown in Fig. 2(c). The exact positions of the two holes for the 4BA bolts are found by using the Paxolin piece of Fig. 2(a) as a template. Fig. 2(c) looks at the front of the panel, and the Paxolin piece should be placed over it so that the centre of the large hole in the Paxolin is exactly over the centre of the largest hole in the plywood piece of Fig. 2(c). The 4BA holes can now be marked through onto the plywood panel. They are drilled out 4BA and then countersunk on the side nearest the reader, as shown in Fig. 2(c).

The Paxolin back, which carries S1 and S2 is cut as shown in Fig. 2(d). Slots for the switch slide dollies should be cut to fit, and the holes drilled for the fixing screws. The switches are fitted underneath the panel so that only the slide dollies and the heads of the mounting screws appear on the side shown in Fig. 2(d). The switches take up the approximate positions indicated in Fig. 2(d).

Now fit the tuning capacitor, VCI, to the Paxolin piece shown in Fig. 2(a). With the Paxolin piece as shown, the body of VCI will be away from the reader, its spindle pointing towards the reader, and the two terminal strips of the capacitor at the top. Be careful to use short bolts to fix VCI in place, or the component may be damaged. Now pass two 2in. long 4BA bolts, with countersunk heads, through the two countersunk holes in Fig. 2(c), with the heads towards the reader. Lock with nuts, one bolt passing through the locating lug on the epicyclic drive, which is mounted *behind* the panel in Fig. 2(c). Place about ¼in. of insulated ¼in. rod (which may be excess cut from a potentiometer spindle) in the bush of the drive, and push a brass spindle coupler on the other end of the insulated rod. Slide VCI, on its Paxolin piece, onto the ends of the 4BA bolts, having first threaded a second nut on each. Pass the spindle of VCI into the coupler. The rear of VCI should be just slightly less than 2¼in. from the rear of the panel; if it is more, slightly reduce the length of the insulated rod accordingly and re-assemble. Finally, put a third nut on each 4BA bolt and tighten up

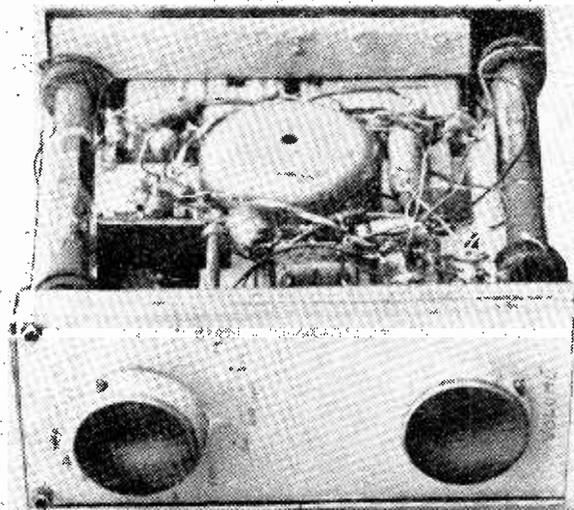

Front view, showing the knobs for VC1 and VR2, behind which are the tuning scale and its Perspex cover

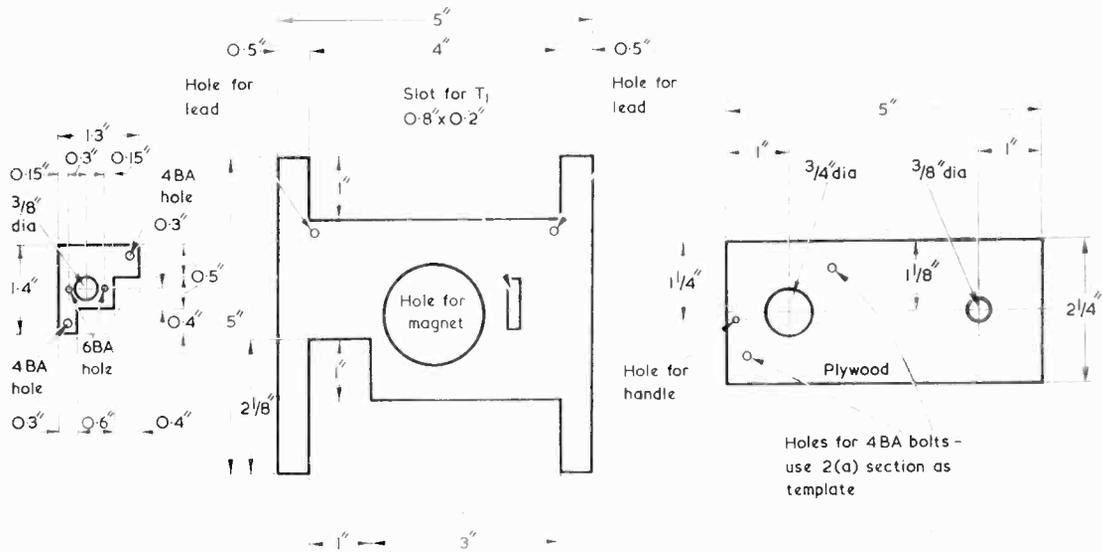


Fig. 2(a) Fig. 2(b) Fig. 2(c)

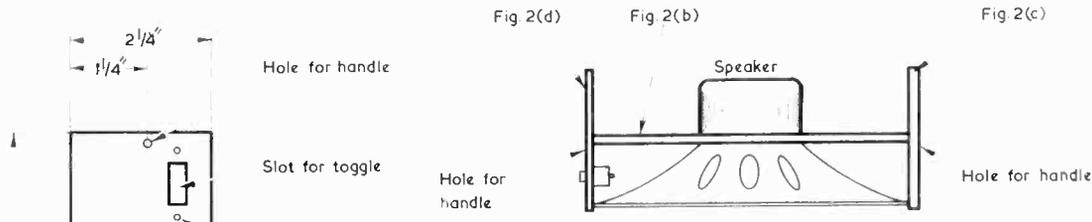


Fig. 2(c) Fig. 2(d)

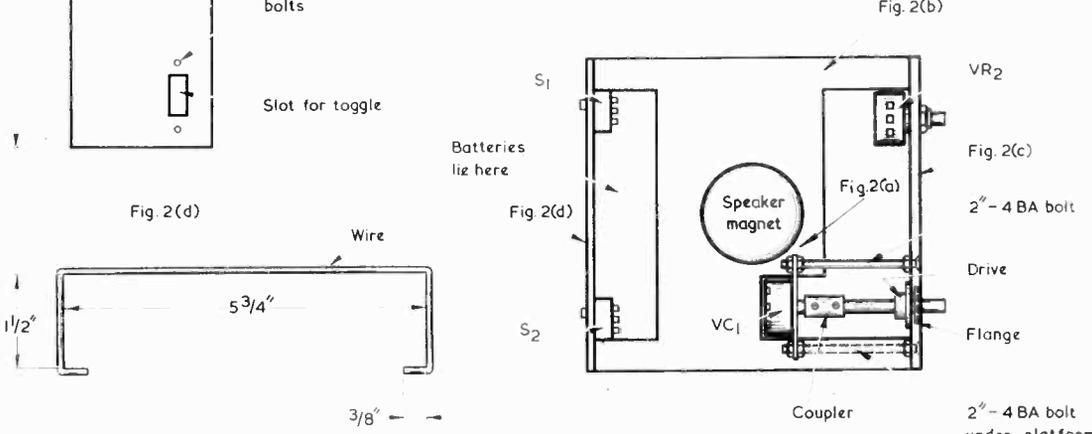


Fig. 2(e) Fig. 2(f)

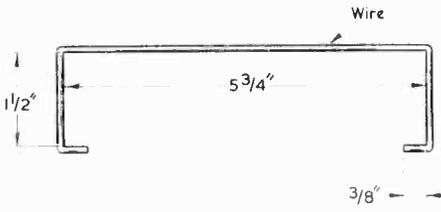


Fig. 2(g)

Fig. 2(a). The Paxolin member on which VC₁ is mounted. (b). The main platform. (c). The front panel. (d). The rear panel. Switches are mounted at the approximate positions indicated. (e). Side view, showing the assembly in place on the loudspeaker. (f). Top view of the assembly and the speaker. (g). How the wire handle is made up

the assembly. See Fig. 2(f).

Next, push the speaker magnet through the hole in the plywood panel of Fig. 2(b), and screw (or fit, using small angle brackets) the two pieces shown in Figs. 2(c) and (d) to the platform so that the assembly takes up the shape shown in Figs. 2(e) and (f). Fit VR2 as shown. Remove the speaker for the time being.


FITTING THE COMPONENTS

Turn next to Fig. 3. Two tagstrips are required, one with ten tags and the other with six. These were cut from a Radiospares standard size tagboard as the tags on this are shorter than on individual tagstrips. These portions of the tagboard are screwed into position with the aid of small woodscrews passed through suitably drilled holes. A piece of thin Paxolin sheet should be inserted under each strip to prevent the tag undersides touching the wood. Failing this, a layer of p.v.c. tape could be used provided care is taken not to overheat the tags. Next T1 is cemented into its slot. Assuming the use of the Radiospares output transformer, the mounting feet of T2 are soldered to the appropriate tags; note that this method of mounting also causes the first and third tags of the six-way tagstrip to be electrically connected together.

The other components may next be wired in as shown. For clarity, TR1, TR2, R1, R2 and C2 are shown in positions which would make it impossible for the batteries to be housed. These components must, in practice, be positioned so as to leave the battery space clear. Similarly, no wiring or tag connections must pass over or near the battery space. Again for clarity, the front panel is shown screwed into position, whilst the back panel is shown lying flat. A further point is that the long leads from VC1 and from the second tag from the left of the ten-way tagstrip to VR1 should, in practice, pass through the small hole through which the leads from L2 pass, and should not lie across the battery space as shown.

It is important that a transistor holder should be used for TR3. The leads of this semiconductor should not be soldered direct.

L3 should have a turn or two of Sellotape wrapped round its windings, and one of its leads will need to be extended by a length of single strand insulated wire, the negative lead of D1 being soldered to the extension point on the lead of L3. L3 needs to be oriented during setting-up, and if the size of the speaker magnet is such as to leave insufficient room for this to be done, the other lead may also be extended and L3 placed in a position behind

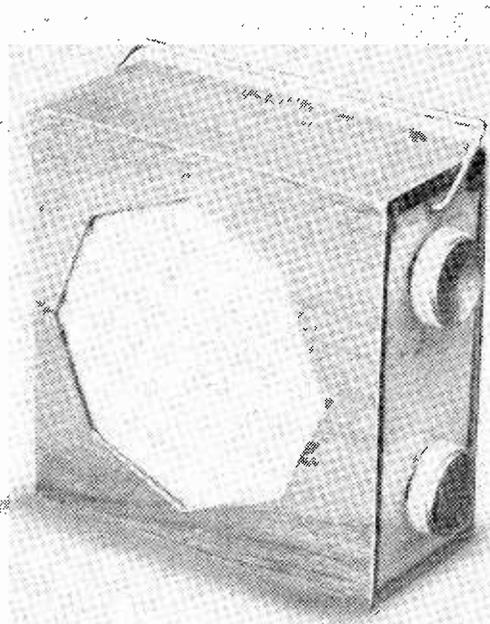

When housed in its case, the receiver presents a neat appearance

VC1. C1, D2 and D3 will each also require one of their leads to be extended.

L1 has 65 turns close-wound of 32 s.w.g. enamelled wire on a paper sleeve of a size which allows it to be moved on the rod. L2 is similarly wound on a paper sleeve and has 250 turns of 38 s.w.g. enamelled wire wound in a pile to a length of about 1½ in. It is convenient for VR1 and VR4 to be miniature components, and VR3 a standard size skeleton component. The tags will then fit neatly to the relevant connecting points.

The two ferrite rods have rubber grommets at their ends which are tied with cord (not wire) round the arms of the platform. This method of mounting secures the rods adequately. Small cuts in the arms of the platform will hold the cord steady.

The lead which passes from the left hand tag of the speaker to the negative line should be soldered to the speaker tag, and one end of L4 should be soldered to the right hand speaker tag before the speaker is pushed into position. L4 lies between the speaker and the platform and it is advisable to wind a turn or two of Sellotape around its windings. Make sure that room is left for L4 as the speaker is pushed into position.

A strip of plywood about 4 in. long and of a width dependent on the exact dimensions and positions of S1 and S2 should next be cut and bolted to the back panel to hold the batteries steady. This strip

will need to be removed when the batteries are replaced.

SETTING-UP

Setting-up adjustments may now be carried out. Turn VR4 so that its slider is nearly, but not quite, fully anticlockwise. Set VR3 to half-way. Clip a voltmeter across the primary tags of T2. Switch on at S2 and adjust VR3 so that a reading of 0.75 volt is given.

Set S1 to select medium waves. Turn VC1 to near maximum capacitance. Adjust the angle of L3 so that oscillation starts with VR2 not less than about 180° from minimum. If this cannot be achieved, change round the connections to L1. Movement of L1 winding on the rod will act as an additional vernier control over the oscillation position.

Now turn VR1 to half-way and switch to long waves. Adjust VR1 so that oscillation starts with VR2 at the full on position when VC1 has its vanes fully enmeshed. Do not alter the angle of L3. The position of L2 winding on the rod will have little effect.

It is a normal characteristic of the circuit that when the receiver is first switched on and tuned to a weak signal at the high frequency end of the medium wave band, requiring a critical setting of VR2, there will be a tendency to spill over into oscillation during the first few seconds. The opposite effect may be noticed when listening to stations on the long wave band. The effect very soon passes

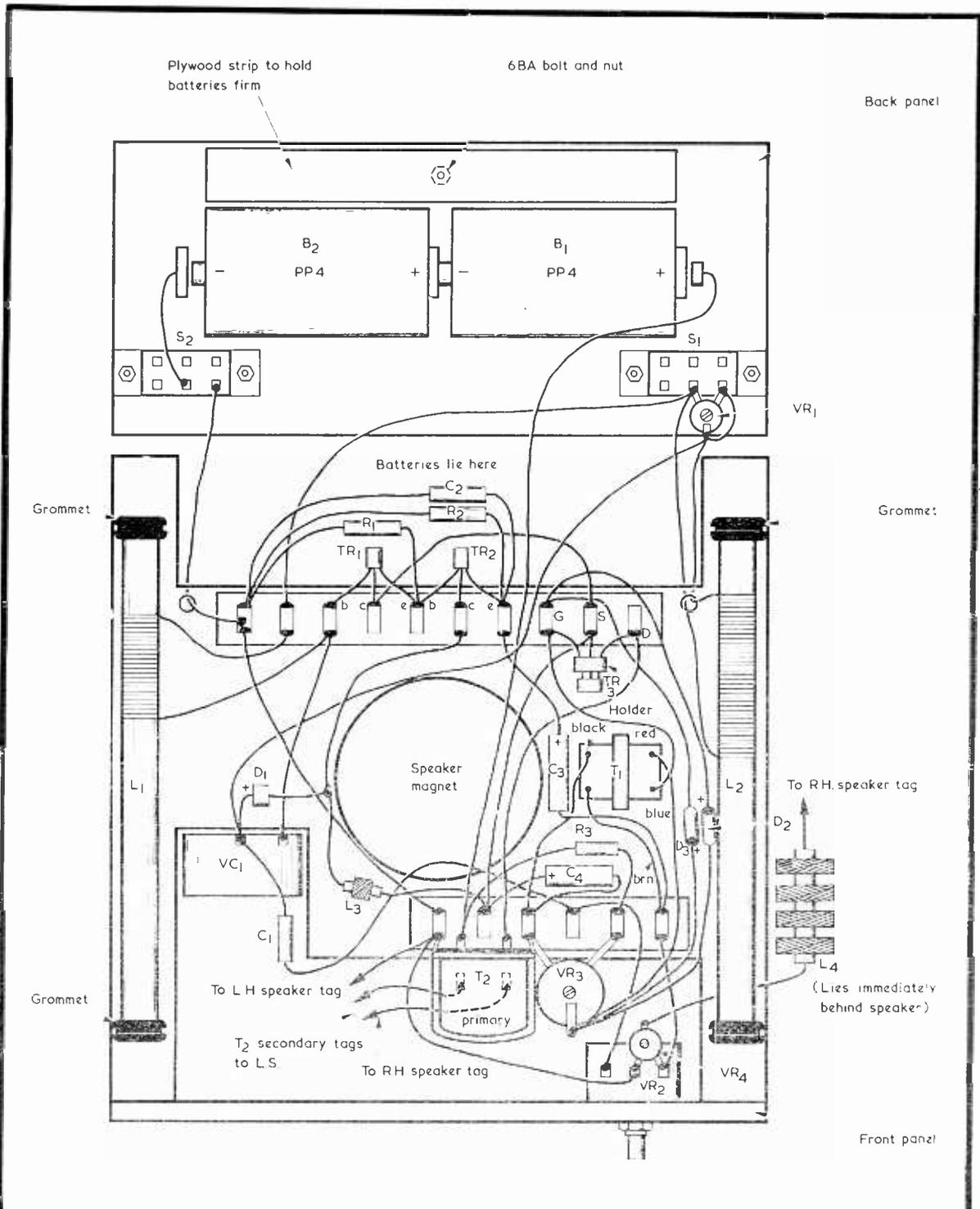


Fig. 3. The component and wiring layout. Check with the text on the positioning of components shown here in the battery space

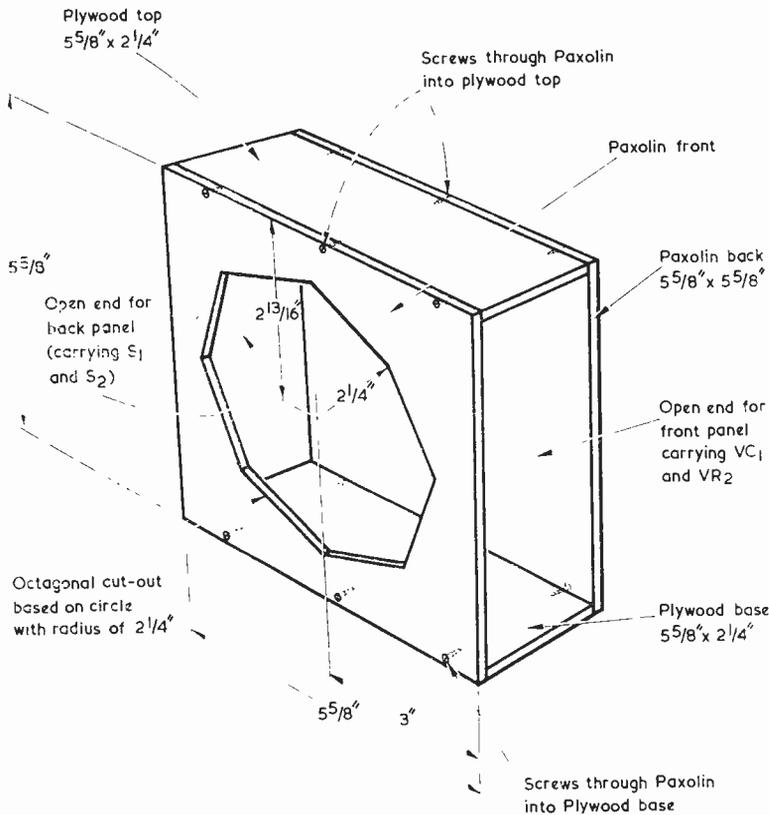


Fig. 4. A simple case may be built in the manner shown here

off, but may require re-adjustment of VR2 after a short interval.

Finally, VR4 should be adjusted. First tune to a weak station and set VR2 so that the receiver is nearly oscillating. Turn VR4 clockwise, whereupon volume will increase until, first, there is distortion and, later, low frequency oscillation. Leave VR4 at a satisfactory setting. The extra gain will not be large, but it is useful.

CABINET

A simple case may be made along the lines shown in Fig. 4. The large sides are made of Paxolin and the small side pieces of $\frac{1}{4}$ in. plywood. The receiver slides into the case, match-box fashion. Before cutting the pieces, make sure that the receiver will fit. Some dimensions may not be exactly as specified due to small mistakes in construction, whereupon the dimensions in Fig. 4 should be modified accordingly. Note that the octagonal hole for the speaker is slightly to the left of centre to leave room for the tuning scale and its Perspex cover. The Paxolin pieces are screwed to the plywood pieces and the whole is covered with Fablon or Contact.

To make entirely certain that no errors appear, it is advisable to fit the tuning scale and its Perspex cover before cutting out the parts for the case.

Place a piece of white card over the front panel of the receiver and make two small wire pointers to be screwed to the flange of the epicyclic drive. Calibrate the dial — an easy task as many stations will be received after dark. Cut a piece of Perspex, 5 in. by 2 $\frac{1}{2}$ in., with appropriate holes for VC1, VR2 and the handle, and place it over the spindles. Using thick 6BA nuts as spacers, to leave clearance for the pointers, screw the Perspex to the panel. Cut a piece of expanded metal grille to cover the speaker and slip the receiver into the case from the left hand side. Make a stiff wire handle, as shown in Fig. 2(g), and spring its ends into the appropriate holes in the receiver, which will then be held firmly in the case.

COMPONENTS

A final word or two about components. The constructor must use the specified transistors, all available from Amatronix Ltd., 396 Selsdon Road, South Croydon,

Surrey, who also stock D2 and D3. The M3 diode is obtainable from Henry's Radio Ltd. T1 is generally available, and there is no easy alternative for this component. If VR2 is more than about $\frac{1}{4}$ in. in diameter, it may be necessary to make the adjacent foot of the platform a little narrower. A suitable component is the Radiospares 250 Ω wirewound semi-precision control, but this has to be ordered through a retailer. An alternative which can be used instead is the 220 Ω linear type P20 carbon track potentiometer, less switch, available from Electrovalue, 28 St. Judes Road, Englefield Green, Egham, Surrey. This has a body diameter of 0.79 in. and should fit into the receiver comfortably. The speaker should be within the maximum limits of 1 $\frac{1}{4}$ in. magnet diameter and 2 $\frac{1}{4}$ in. overall depth.

If the Radiospares transformer cannot be obtained for T2, it may be replaced by two Repanco transformers, types TT49 and TT46, coupled together in tandem, as shown in Fig. 5. They are mounted on a small piece of Paxolin and, in the diagram, are behind the Paxolin, their spills passing through small holes in it. The spills are then bent round to secure the transformers, and the assembly is bolted to the front panel between VC1 and VR2.

With this assembly the wiring in Fig. 3 is modified slightly. R3 now connects to the TT49 transformer, as shown in Fig. 5, and its lead may require extending. Since the first and third tags of the six-way tagstrip are not now bridged by the mounting feet of the Radiospares trans-

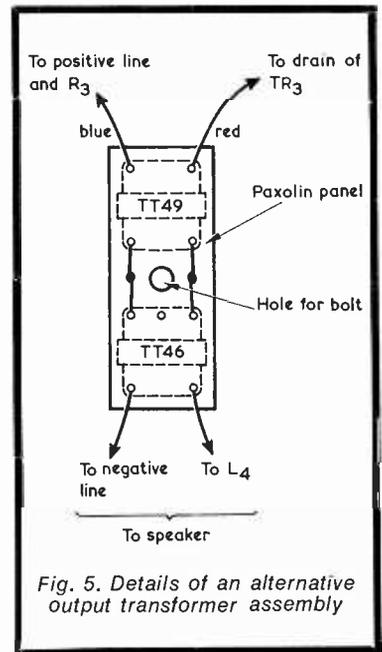


Fig. 5. Details of an alternative output transformer assembly

former, they need to be joined by a short length of insulated wire.


The primary of the TT49 transformer has a resistance of 150Ω, so that VR3 is adjusted to cause 0.45 volt to appear across it at the required current of 3mA. The two transformers offer an overall ratio

of 36:1.

It will be apparent that if, for any reason, the coupling between the drain of TR3 and the connection to L4 is of opposite phase to that existing in the prototype, the feedback to T1 will be negative instead of positive, with a consequent

reduction in gain as VR4 is advanced. It is unlikely that this will occur if either of the alternatives for T2 is connected as described, and it can, in any case, be corrected by transposing the primary connections in the drain circuit of TR3. ■

In your workshop

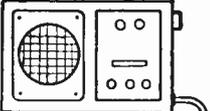

“FOR REPAIR IF ECONOMICAL-ly justifiable.”

Dick looked again at the ticket attached to the large mains radio on the ‘For Repair’ rack and scratched his head. To one of Dick’s tender years the set appeared to be a very old receiver indeed. Its large wooden cabinet had collected a considerable amount of dust, and Dick blew some of this away so that he could peer at the tuning scale. So far as he could ascertain through the grime, the set was intended for long, medium and short waves.

Reluctantly, Dick picked up the set, carried it over to his bench and plugged it into one of the mains sockets at the rear of his bench. He tentatively tried the knobs on the front of the receiver and found the one which was coupled to the volume control and on-off switch. He turned this round. A weak pallid light behind the tuning scale gave witness of the electrical marvels of an earlier age.

After allowing a reasonable time for warm-up (since, as Dick correctly surmised, the receiver had been assembled before the junction transistor was even a gleam in W. Shockley’s eye) Dick advanced the volume control to its fullest setting. There was no sound from the speaker. Dick turned back the volume control and experimented

This month Dick and Smithy leave the realm of semiconductor devices and travel back in time to a subject which is of continual interest amongst readers: the repair and rejuvenation of old valve a.m. radios. Dick encounters a typical example of the receivers in this genre, whereupon Smithy is able to demonstrate the stock faults to which such receivers are prone, and to discuss their rectification

with the other knobs. The wave-change switch clicked mechanically in an encouraging manner, but there was no corresponding sound from the speaker. The tuning knob caused a cursor to move horizontally behind the tuning scale but it had, otherwise, no noticeable effect on receiver performance. A fourth control, which must obviously have been for tone, similarly failed to produce any audible results from the speaker. Dick switched the receiver off again.

A.M. VALVE RECEIVER

“Hey, Smithy!”

“What’s up?”

“It’s this weird radio I’ve got here,” called out Dick. “I’ve never seen anything so old and grotty for ages.”

Patiently, Smithy the Serviceman put down his test prods and turned round from the chassis he was working on. A gleam of recognition came into his eyes as he saw the receiver on Dick’s bench.

“Well, well, well,” he remarked. “Now, that’s a model I’ve handled stacks of times in the past. It came out just after the war.”

“The note tied to it,” said Dick, looking at the ticket once more. “is something I’ve never seen in here before. It says the set’s in for repair ‘if economically justifiable’. All I’ve done up to now is to plug it in to the mains, and it seems to be completely dead.”

“Economically justifiable, eh?” repeated Smithy. “Well then, the next thing you’d better do is to whip the back off and see what it looks like inside.”

Smithy ambled over as Dick took the mains plug of the receiver out of the bench socket, turned the set round and then removed its back. Smithy looked inside interestedly.

“Ah yes,” he remarked. “That chassis brings back a few memories

to me. Almost all the radio sets in those days were four-plus-one jobs. This is one of them.” (Fig. 1).

“Four-plus-one?”

“That’s right. They were called four-plus-one sets because they all had four signal-handling valves and one h.t. rectifier valve. The signal-handling valves were a triode-hexode or triode-heptode frequency changer, a pentode i.f. amplifier, a double-diode-triode in which the diodes acted as signal and a.g.c. detectors and the triode as audio a.f. voltage amplifier, and an a.f. output pentode. This represented a stock receiver design and, to be frank, it used to work very well indeed. This set is a typical four-plus-one and, as you’ll note, all the valves are on octal bases. It’s also got a mains transformer, too.”

“Will it be capable of being repaired without too much expense?”

“Oh, quite probably,” said Smithy. “If there isn’t anything excessively wrong with it, and it has been kept in a reasonably dry place, it may only need a few new components to get it working quite well once more. From the look of this particular set, I’d say it has been stored away in somebody’s lumber room for years, and that that somebody has suddenly decided to see whether it’s worth bringing it back to life again.”

“Well,” conceded Dick, “there’s certainly enough dust, both on the cabinet and on the chassis, to support that last remark. It looks as though it hasn’t been used for years.”

“Fair enough,” said Smithy. “Anyway, the first thing to do is to see whether anybody’s been messing about in it and has started changing a lot of components around. The set will be too much trouble to bother about if we’ve got to first of all put right a lot of poor work carried out by some ham-handed Henry in the past.”

“So far as I can see,” said Dick,

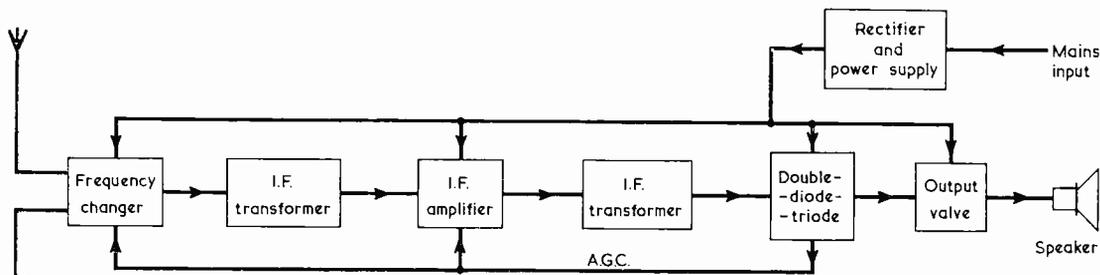


Fig. 1. Block diagram of a 'four-plus-one' a.m. valve receiver

taking a closer look inside the cabinet, "it looks all right above the chassis."

"Good," replied Smithy. "Let's next go through some other items which are likely to make the repair of sets of this nature uneconomical. To start off with, if the set has a push-button wave-change or station selection switch it would probably be best to forget about fixing it. These push-button switches tend to wear out more quickly than the rotary type and, to my mind, the replacement of what could well be a non-standard push-button switch would incur far too much trouble. See, also, that the tuning drive is in good condition. If a complicated mechanical drive is used and it's gone faulty, the set is again not really worth the bother of fixing."

"The tuning drive appears to be okay," remarked Dick. "And the wave-change switch on this set is a rotary one and it seems to have at least a good clicking action."

"That sounds promising," commented Smithy. "Well, you'd better get the chassis out and clean some of that dust off it."

Smithy returned to his bench, whilst Dick removed the chassis from the cabinet. He then took from its corner the Workshop's battered vacuum cleaner, in whose bag at some time had resided dust from most of the households in the locality, and proceeded to clean the top of the chassis. As a final act he coupled the hose of the cleaner to its blower end and blew away the final remaining traces of dust from odd crannies. On turning the chassis over, he was pleasantly surprised to find that the underside was quite clean, and bore only that particular patina which is peculiar to old radios. He examined the chassis underside carefully.

"This doesn't look too bad, Smithy," he called out. "I've taken a look at the wave-change switch, too, and it seems all right. Somebody in the past has changed one of the resistors, but he's made a nice neat job of it so that should be okay."

MAINS TRANSFORMER

"Fair enough," said Smithy, returning. "Now the set has got a mains transformer. If that proves to be all right then I think it might well be worthwhile getting this receiver to go again."

Smithy looked into the chassis, then picked up Dick's testmeter. He switched this to a resistance range and clipped one of the test leads to the chassis.

"We'll first check that the h.t. secondary is all right," he explained. "This set uses a standard full-wave rectifier circuit so there will be a centre-tapped h.t. winding to test."

The Serviceman applied the remaining test prod successively to two of the rectifier valve pins (Fig. 2) and looked at the meter needle.

"There's several hundred ohms in each half of the secondary," he said, "so that will be all right."

"The primary should be all right, too," put in Dick. "The tuning scale light lit up when I switched the set on."

"Did it?" said Smithy. "Then there's no point in carrying out any further tests, and we can say that the mains transformer is satisfactory."

"What," asked Dick, "is the next thing to do?"

"Make certain there are no shorts between h.t. positive and chassis," replied Smithy. "Seeing that you got no sound out of the set when you switched it on just now, it would seem reasonable to check that there are no broken-down h.t. smoothing electrolytics or any thing like that. We don't have to actually locate the positive h.t. line because we can, of course, check directly at the tags of the h.t. electrolytics themselves. I see that this set has three electrolytics in a single can with smoothing resistors between them."

Smithy applied the test prods of Dick's meter to the tags of the electrolytic capacitors. (Fig. 3).

"This is quite encouraging," he remarked cheerfully. "I got a sizeable kick in the meter needle when I first put the prods on, which

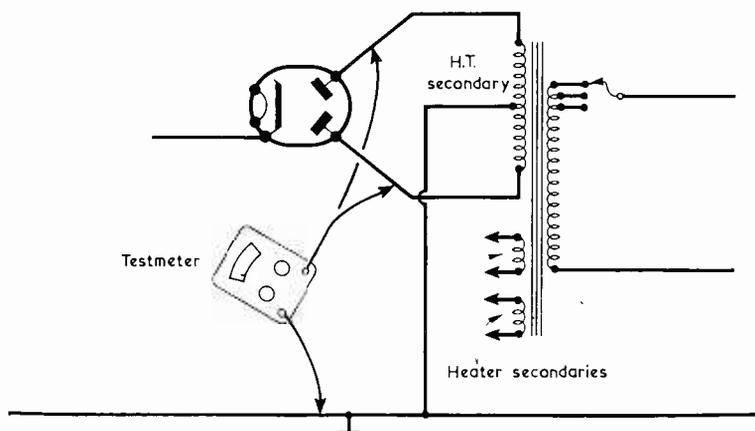


Fig. 2. Smithy checked the two halves of the mains transformer h.t. secondary by checking for continuity between chassis and first one anode and then the other anode of the full-wave valve h.t. rectifier

Your Local Supplier

LONDON

Established 1910

H. L. SMITH & CO. LTD.

Comprehensive stocks of components by all leading makers

287-9 EDGWARE ROAD
LONDON W.2

Tel: 01-723 5891

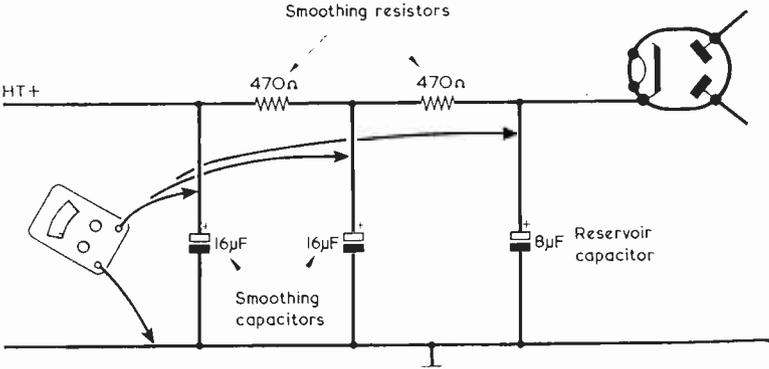


Fig. 3. Checking for h.t. short-circuits, Smithy tested between chassis and the positive tags of the h.t. electrolytic capacitors. This also enabled open-circuits in the smoothing resistors to be checked. The component values shown are typical

means that there's still a useful bit of capacitance in the smoothing circuit. And the final resistance to chassis at each of the positive tags was about 100kΩ. Sets of this nature don't usually have potential dividers in the receiver circuits, so that 100kΩ resistance is probably leakage resistance in the electrolytics. The fact that I got the same resistance reading on each of the tags also indicates that neither of the smoothing resistors is open-circuit. A figure of 100kΩ is a wee bit low for leakage resistance, but I think we can still switch the set on, nevertheless. Plug it in, Dick."

Smithy switched Dick's meter to a suitable voltage range, then re-connected it between chassis and the positive tag of the final electrolytic smoothing capacitor. At the same time, Dick put the receiver plug back in the socket at the rear of his bench. Smithy switched on the set. The tuning scale light, now relieved of its cocoon of dust, shone brightly. The heaters of the five valves in the receiver started to glow, shortly reaching full brilliance. The needle of Dick's meter suddenly shifted from its zero setting. As the seconds passed it ascended up its scale then slowed down to finish at a steady and triumphant 260 volts.

"There's plenty of h.t. there," remarked Dick. "Let's turn the volume up."

He reached over and turned the volume control spindle fully clockwise. As had occurred when the set was in its cabinet, there was still no sound from the speaker. Dick next attempted to adjust the wave-change switch, but it was too stiff to turn by means of its spindle only. Dick fitted its knob, then turned it experimentally from one position to the next.

There was a sharp crack, and a spark jumped between two pins of

a valveholder on the other side of the chassis.

Dick turned the switch back to its previous position. Again there was a sharp crack, accompanied by the spark.

"Corluvaduk," exclaimed Dick, startled. "What have we got here?"

"We've got a symptom," replied Smithy, "which explains why this set is so silent. What you haven't realised is that the valveholder where that spark is occurring is the one that holds the output valve. Switch the set off, then trace for an open-circuit between the secondary of the speaker transformer and the speech coil of the speaker."

LF. INSTABILITY

Impressed by this immediate diagnosis of the cause of the spark, Dick turned off the set, located the speaker transformer and traced through its secondary circuit to the speaker.

"Blimey, Smithy," he called out suddenly. "You must be a magician, mate! It's just as you said; what's happened is that a wire from the speaker has broken off at the transformer secondary tag. It was still positioned close to the tag and it wasn't till I waggled it that I found it wasn't actually connected."

Dick indicated to Smithy the break in the circuit (Fig. 4) then picked up his iron.

"We'll soon get this fixed," he called out jubilantly. "Incidentally, what made you so sure that the transformer secondary circuit was open?"

"It was almost certain to be," replied Smithy. "If, in a single-ended valve audio output stage, as we have here, the secondary of the output transformer isn't loaded by the speaker, the impedance presented to the output anode is the inductance of the transformer primary

THE MODERN BOOK CO.

Largest selection of English & American radio and technical books in the country.

19-21 PRAED STREET,
LONDON, W2 1NP

Tel: 01-723 4185/2926

ST. HELEN'S RADIO

Hi-Fi Equipment
Tape Recorders
Radio Receivers
Television

SPECIALISTS IN RADIO
& ELECTRONIC TEXTBOOKS

ST. HELEN'S GARDENS
LONDON, W.10

Tel: 01-969 3657

BEDFORDSHIRE

SURPLECTRONICS

THE SELF-SERVICE
COMPONENTS SHOP
THAT SAVES YOU MONEY

CHOOSE FROM 1200
ASSORTED BOXES
AT YOUR LEISURE

9 a.m. to 5.30 p.m. every day.
Closed all day Wednesday

WE ARE IN LUTON
AT 216 LEAGRAVE ROAD
LUTON, BEDS

Your Local Supplier

HAMPSHIRE

BOURNEMOUTH

LARGEST HI-FI AND
RADIO COMPONENT
STORE IN THE SOUTH

FORRESTERS NATIONAL
RADIO SUPPLIES LTD.
70-72 Holdenhurst Road
Bournemouth
Telephone 25232

SUFFOLK

RADAR & ELECTRONIC PUBLICATIONS

Transistor Optical Burglar/Fire Alarm Detector Circuit, 10-12 transistors, 3 relays. 'Memory' Circuit. Tested at 2,000 yards. May pick up burglar's torch at 70 yards! 60p. All-night Radiation/Optical Detector Circuit, 45p. Two simple Valve Optical Circuits, neon flasher/audio/scope indication, 30p.

(Publications only).

'Highlands', Needham Market, Suffolk

SUSSEX

E. JEFFRIES

For your new television set
tape recorder, transistor radio
and hi-fi equipment

PHILIPS, ULTRA, INVICTA,
DANSETTE, MASTERADIO, PERDIO,
MARCONI, PHILCO, FIDELITY

6A Albert Parade
Victoria Drive,
EASTBOURNE SUSSEX

YORKSHIRE

WILSIC ELECTRONICS LTD.

Your local supplier for
EAGLE PRODUCTS
CYBERNAT MOTORING AIDS
WILSIC HI-FI, MUSICAL
EQUIPMENT, KITS AND
COMPONENTS

Send 15p (3/-) for our Catalogue
Eagle Products Catalogue 20p (4/-)

6 COPLEY ROAD
DONCASTER

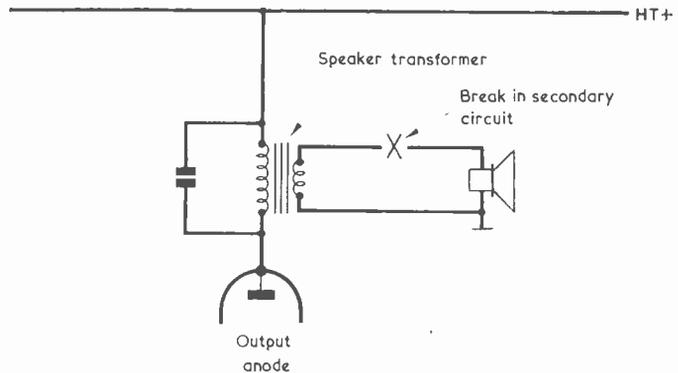


Fig. 4. The break in the speaker transformer secondary circuit. (The capacitor across the primary, normally around 0.1 μ F, is intended for 'tone-correction' and it reduces the shrill effect of third harmonic distortion in the output pentode.)

itself. This impedance is much higher than the normal anode load impedance, with the result that much higher a.f. voltages appear across it. If that secondary circuit hadn't been open just now there would have been a loud click from the speaker each time you moved the wave-change switch, this click being particularly loud since, as I noticed, you had the volume control at a full setting. With the speaker disconnected, though, that click became a large voltage pulse at the output anode instead, whereupon a spark jumped from the anode pin to the adjacent pin, which happens to be one of the heater connections. Incidentally, sparking at the output anode pin when the output transformer secondary circuit is open is quite a common occurrence. High level music or speech fed to the output valve can also cause it to happen.

"Well, that's something I didn't know before," said Dick. "Anyway, I've now repaired that secondary circuit connection, and I'm going to switch on again."

Dick turned the receiver on again. After a short wait, an h.t. voltage was once more indicated on the testmeter. Also, and much to the gratification of Dick's assistant, a hiss at comfortable level became audible from the speaker.

"We're really getting somewhere now," said Dick exuberantly. "I'd better see if we can tune in a station."

He looked at the wave-change knob.

"We're switched to long waves," he continued. "Let's see if we can get Radio 2 on 1,500 metres."

"Plug an aerial in first," advised Smithy. "There were no such things as ferrite rods when this set was made. A few feet of wire will be enough for the time being."

Dick found an odd length of wire and inserted it in the aerial socket of the receiver. A comforting crackle was audible from the speaker at the instant of making the connection. Dick grinned. He then turned the tuning drive spindle between finger and thumb, whereupon a steady succession of further crackles was heard, these ceasing as he stopped turning. Dick's grin vanished abruptly and his expression changed to one of dismay.

"There's no point," he said gloomily, "in going any further with this set, Smithy."

"Why on earth not?"

"Didn't you hear those crackles when I turned the tuning drive spindle? The vanes in the tuning capacitor must have a shocking intermittent short-circuit between them somewhere."

"Nonsense," retorted Smithy. "Put the knob on that tuning drive spindle and try again."

Unwillingly, Dick fitted the knob to the spindle and turned it experimentally. Much to his amazement, he found that the crackles had disappeared completely.

"Stap me, Smithy, how do you do it?" he asked wonderingly. "And where did all those crackles go?"

"What was happening," said Smithy, "was that your body was acting as a counterpoise earth to that short aerial you fitted. The chassis of this set isn't earthed, and you were making an intermittent connection to it as you turned the spindle, the intermittent connection being given between the spindle and the holes in the chassis to which it's fixed."

Smithy indicated the points of contact. (Fig. 5).

"This intermittent connection," continued the Serviceman, "caused the effective counterpoise - you - to be coupled to the chassis by a

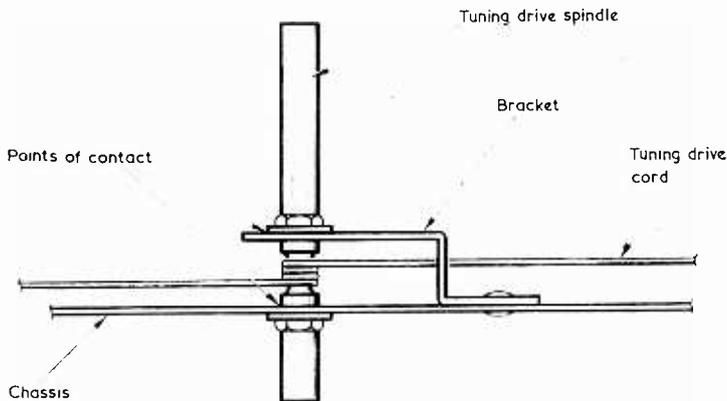


Fig. 5. In this typical tuning drive spindle mounting, the spindle simply revolves in holes in a mild steel chassis and support bracket. In consequence, the electrical contact between the spindle and the chassis, as the former is rotated, is of an intermittent character

'crackly' connection. After you'd put the knob on you were insulated from the spindle and so there were no more intermittent connections between you and the chassis, and hence no crackles. Okay?"

Dick looked at the receiver with a newly acquired respect.

"Servicing these old sets," he remarked, "involves a lot of tricks you don't encounter with modern receivers. Anyway, now that we've got the crackles out of the tuning, let's have another bash at picking up a station."

He turned the knob further and was rewarded by a high pitched whistle with a background of distorted music. The whistle descended in frequency as he turned the tuning drive and he was able to reach a

position of zero-beat. The sound of heavily distorted music was loudly audible from the speaker.

"That's i.f. instability," remarked Smythy laconically. "The i.f. amplifier is oscillating at the intermediate frequency so that, when you tune in a signal, you get the same beat frequency effect as when you tune in a signal on a straight receiver in which the reaction has gone past oscillation point. Let's see if we can clear it up."

Smythy went to the spares cupboard and returned with a $0.5\mu\text{F}$ polyester capacitor. He applied this across the third electrolytic capacitor in the h.t. smoothing circuit. (Fig. 6). The beat frequency effect cleared immediately. With his free hand, Smythy turned the tuning

drive of the receiver. The signal could now be tuned in and out in perfectly normal fashion, with no trace of the previous whistle. When tuned in correctly, the signal still exhibited a measure of distortion, but this was of a different nature and much less evident than that which had previously been present.

"You've done it again!" pronounced Dick incredulously. "That's the third snag you've cleared up first go. How on earth did adding that capacitor clear the instability?"

"To answer that question," replied Smythy, switching off the set again. "I must first tell you that quite a lot of these old valve sets have no anode decoupling for the individual stages at all. The frequency-changer anode load, the i.f. amplifier anode load, the a.f. voltage amplifier anode load and the output pentode anode load all go to the h.t. positive line direct. This is bypassed to chassis by the smoothing electrolytic capacitor which connects to the h.t. positive line, and there are no other anode bypass circuits whatsoever. It only requires the electrolytic capacitor to develop a little series impedance and the whole set takes off! The usual result is that oscillation takes place at the intermediate frequency because that's the frequency at which most amplification takes place."

NEW CAPACITOR

"Isn't it a bit naughty," queried Dick, "to expect an electrolytic capacitor to act as a bypass at intermediate frequencies?"

"It is rather, I suppose," said Smythy. "But the use of an electrolytic in this manner was an extreme-

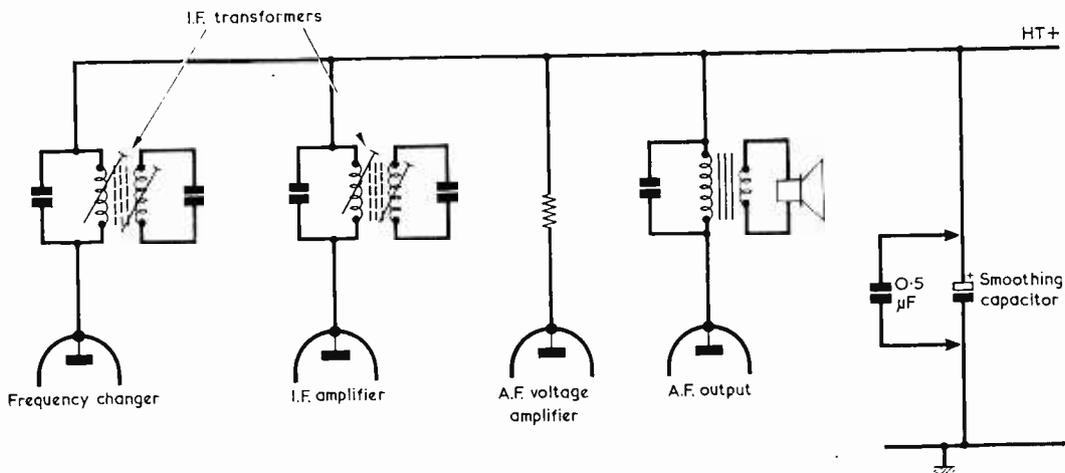


Fig. 6. In many a.m. valve receivers the final smoothing electrolytic capacitor bypasses the anode loads of all the stages. Smythy connected an $0.5\mu\text{F}$ capacitor across this capacitor to see whether it was causing i.f. instability

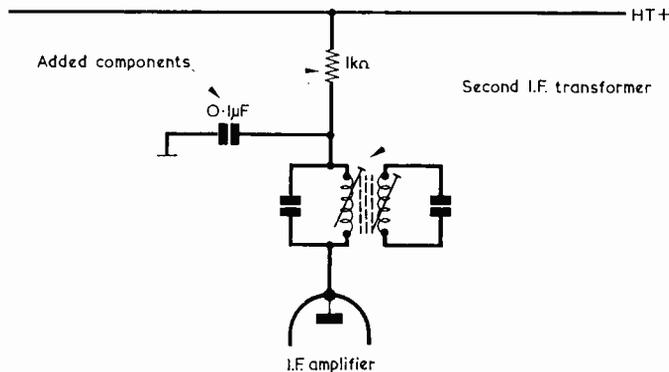


Fig. 7. An added h.t. decoupling circuit at the second i.f. transformer can, in some instances, cause an improved performance in valve a.m. receivers

ly common practice at the time. You'll have noticed, incidentally, that I only needed a $0.5\mu\text{F}$ capacitor to provide the bypassing that was required to clear the i.f. instability, so perhaps employing an electrolytic for the job isn't such bad practice after all. By the way, if you ever want to improve the i.f. response of one of these old sets, it's a good plan to add an h.t. decoupling circuit to the primary of the second i.f. transformer. A $1\text{k}\Omega$ resistor and $0.1\mu\text{F}$ capacitor will be quite adequate." (Fig. 7).

"What does the decoupling circuit do?"

"It increases the isolation between the two i.f. transformer primaries," explained Smyth. "There is then less chance of regeneration from the anode circuit of the i.f. valve back to its grid circuit, and you can align the transformers to give really symmetrical responses. Adding the decoupling circuit doesn't always produce a significant improvement in receiver performance, but it's worth trying, just on spec."

"That's something I'll bear in mind for the future," said Dick. "At the time being, though, it looks as if I'd better fit a new electrolytic to this set."

"It does, rather," agreed Smyth. "As a matter of fact I would probably have suggested that you replaced the h.t. electrolytics in any case, even if they hadn't given rise to trouble or were allowing excessive hum to appear. Electrolytics as old as these ones are tend to fall into the category of components that are liable to give trouble at any time."

Dick walked over to the spares cupboard and selected a suitable triple electrolytic capacitor for replacement. Smyth watched him thoughtfully as he mounted it on the chassis and then soldered it into circuit.

"Whilst talking about i.f. instability," Smyth remarked, "another component which was likely to give rise to trouble on this score is the screen-grid bypass capacitor for the i.f. valve. This connects, of course, between the screen-grid and chassis."

"Why should it cause trouble?"

"Because the i.f. amplifier valve is expected to provide a very high level of amplification," explained Smyth. "With the result that, in many of these old sets, its screen-grid had to be tied down to chassis really good and tight. If you had a faulty screen-grid capacitor, or if the leads to it were too long, the set could similarly go unstable. Another cause of i.f. instability, in the really old sets, was the result of the metallising on the glass envelope of metallised valves becoming unstuck from its earth lead."

"Valve metallising? Blimey you're going back a bit, aren't you?"

"Perhaps I am," confessed Smyth, "but if we're going to talk about old sets, we might as well cover the subject completely. These valves were octal types with the control grid brought out to a top

cap. and they were screened by a layer of metallising on the outside of the glass, this metallising connecting to a wire which went down to an earth pin. Very often the glass used to come adrift from the bakelite base of the valve and the connection to the earth pin would then break away. If the valve was an i.f. amplifier the set would probably go into i.f. oscillation as a result. The cure was to re-stick the glass of the valve to its base and then wrap a few turns of thin bare tinned copper wire round the metallising at the bottom. This wire was then run down the outside of the base to the earth pin and soldered to it at the point where its pin left the base." (Fig. 8).

"I had a go myself once," commented Dick thoughtfully, "at soldering to one of the pins of an octal valve. I had a dickens of a job getting the solder to take."

"You need to give the pin a touch with a file first," advised Smyth. "Just enough to remove the plating at one point and show the brass underneath. Have you got that new electrolytic in yet?"

A.F. DISTORTION

"Just finishing," said Dick.

Carefully, he completed the last connection, then he placed his soldering iron on its rest and switched on the receiver. Both of them listened critically to the music, without whistle, that the set now reproduced.

"The new electrolytic," remarked Dick, "has certainly cleared the i.f. instability. But the sound still seems a little distorted to me."

"Yes, it is a bit," agreed Smyth, picking up a screwdriver with an insulated handle. "Let's check the a.f. coupling capacitor to the output grid."

Smyth put the blade of the screwdriver on the chassis alongside the output pentode valveholder and touched its metal shaft to the control grid tag. With a crackle, the sound ceased. (Fig. 9). Smyth re-

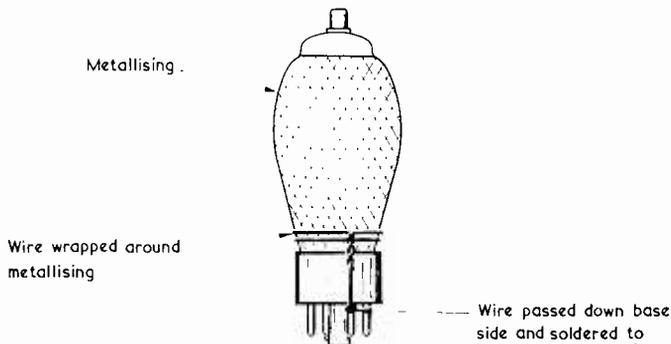


Fig. 8. The metallising of a valve may be connected to its earth pin externally

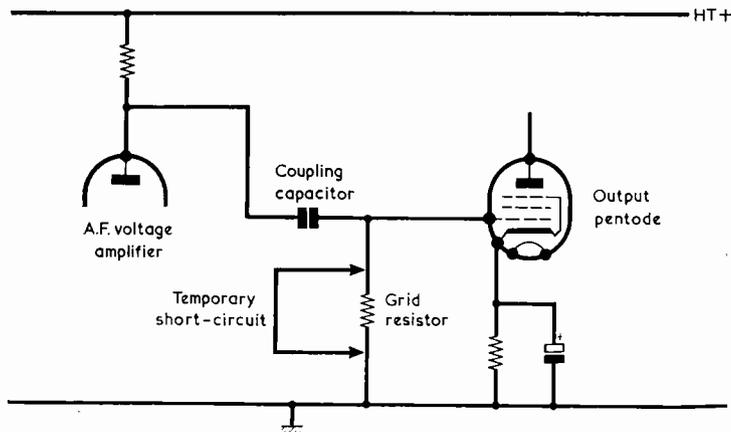


Fig. 9. Checking for a leaky a.f. coupling capacitor. If a crackle is heard when the grid resistor is short-circuited the coupling capacitor is leaky

moved the screwdriver whercupon, with a further crackle, the sound resumed.

"The coupling capacitor between the output grid and the previous anode has gone leaky," Smithy pronounced decisively. "New capacitor to be fitted, please!"

"Blow me," protested Dick, "you aren't half diagnosing faults in a hurry today. How the deuce can you be so sure that the coupling capacitor is leaky?"

"Because that output grid has got a standing direct voltage on it," replied Smith, "which is why I got a crackle when I short-circuited its grid resistor. If it hadn't had a direct voltage on it, the sound would simply have ceased without a crackle. This test is a reliable and quick one, but make certain you know which is the control grid pin if you carry it out. You can do a lot of damage if you accidentally short the wrong pin to chassis!"

Dick went to the spares cupboard and found a new replacement coupling capacitor. He switched off the set, soldered the capacitor in, then switched on again. The distortion was now completely cleared.

"Do you know, Smithy," remarked Dick after some moments, "this set sounds really good. The quality seems to be a darned sight better than what you get on many of the modern solid-state jobs we handle."

"When they're working properly," commented Smithy, "these old valve sets can sound very nice indeed. To start off with, they've got a straightforward Class A output stage with no complications, instead of the present-day transistor Class B circuits. Secondly, the sets were built in large wooden cabinets, which means that their speakers, which themselves are quite a big size, have a good effective baffle area to

bring up the bass. I'll be the first to agree that the sound these sets give isn't high fidelity and that it isn't up to the high quality mark, even. And I'd agree also that the i.f. stages are usually sharply selective, so that you get an output which has a fair amount of top-cut to add to any bass thump that may be given by the large speaker and cabinet. Nevertheless, I still feel that these receivers can give quite a good performance. Try the other hands on the set."

Dick proceeded to put the set through its paces and found that it performed remarkably well. Long and medium wave reception was very good, and the set produced the usual staccato stream of signals as he swung over the short wave band. The more powerful short wave stations could be resolved with ease.

"Not bad at all," commented Smithy. "I think we can say that we have now achieved an acceptable repair at quite a reasonably low cost, both in components and in time. Admittedly, we were lucky to find that the set had the more usual stock faults on it. I tell you what: now that we've got it going, how about giving the cabinet a bit of a polish up?"

"Why not," replied Dick enthusiastically. "To tell you the truth, I'm beginning to fell quite a lot of affection for this old-stager, and I'd be only too happy to give its box more than the average amount of bull."

Dick found some rags and a tin of furniture polish, these being employed occasionally to give the more expensive receivers a final finishing. He polished away cheerfully to the accompaniment of mellow music from the old radio.

Smithy's assistant gave the cabinet of the receiver a final rub and then

put the polishing cloth on one side. The receiver, its early post-war cellulose covering restored to its original splendour, gleamed in front of them. The tuning panel, now cleaned and fully illuminated, was radiant with a tuning scale pattern of many colours.

"The owner of this set," said Dick proudly, "can certainly be grateful to us for the work we've put in on it."

A thought suddenly occurred to him.

"Hang on a minute," he went on, frowning, "I've just remembered something. The ticket tied to that set didn't have any owner's name and address written down on it."

Smithy turned a guileless eye towards the ceiling.

"There's something fishy here," continued Dick, a tone of suspicion rising in his voice. "It's the rule that all the fault-tickets used here should have the set-owner's name and address on them. I must say it's funny that the first unusual job I've tackled for ages should also be accompanied by a label with no name and address on it."

The innocence exhibited in Smithy's face had now become so intensified as to approach the imbecile. Dick turned an accusing glance at him.

"Don't tell me," he intoned furiously, "that that set is yours!"

"I cannot," replied Smithy sweetly, assuming the mantle of the infant George Washington, "tell a lie. Yes, it is my set. As it happens, I found it when I was cleaning out the loft the other day."

"Why, you rotten old devil," spluttered Dick, "You *planted* that set on the rack. You snuck it in first thing this morning, before I got to work, and you darned well secreted it amongst all the other sets on the shelves."

Dick's sense of outrage grew even keener at the recollection of a further affront.

"Flaming heck," he fumed, "I've actually been vacuum-cleaning and polishing up that set, when it's your private job! No wonder there's a generation gap these days. It's because the people in the older generation are all like you - shy-sters and con-men!"

"You must at least admit," said Smithy soothingly, "that I've given you a chance to get in some experience in rejuvenating old sets."

"Well," conceded Dick grudgingly, "I suppose that that is true. But I still think you've been taking a liberty. However, I'll forget all about it on one condition."

"And what's that?"

"That you let me have a really good long gen-session with you during today's lunch-break."


And to that Smithy wearily agreed. ■

PANEL SIGNS

IDEAL FOR WORKSHOP USE

- Easy to fix
- Permanent and durable
- Stapled in booklet form
- Designed to hang above workbench
- Pocket for loose cuttings
- Professional finish

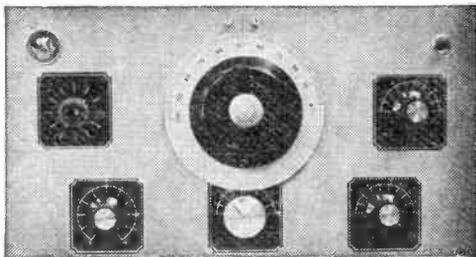WORDING (Sets 3 and 4) COMPLETELY REVISED. Over 1,000 words. Height of Letters $\frac{3}{32}$ in. FREQUENCY LISTS (Sets 5 and 6). Now in kHz and MHz.



- * Set 3 Wording—WHITE
- * Set 4 Wording—BLACK
- * Set 5 DIALS—clear background
- * Set 6 DIALS—black background (as per illustration)

PANEL SIGNS

Permanent Paint Transfers

SET No. **4** **BLACK WORDING**

Six sheets containing more than 1,000 words, letters and symbols: Receivers, Amplifiers, Transmitters, Test Equipment, Safety Notices, etc. (2 Safety Notices have black wording on red background). Full instructions inside.

5s
25p

Published in conjunction with the monthly magazine

THE RADIO CONSTRUCTOR

The Perfect Transfer for
the Home Constructor

Each Set contains Six Sheets

25p per set

(postage 3p)

To **Data Publications Ltd., 57 Maida Vale, London, W9 1SN**

Please supply:

Set 3..... Set 4..... Set 5..... Set 6.....

I enclose cheque/crossed postal order for.....

Name

Address

R.C.

BLOCK LETTERS PLEASE

SMALL ADVERTISEMENTS

Rate: 4p (9d) per word. Minimum charge 60p (12/-).
Box No. 10p (2/-) extra.

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of advertisers. (Replies to Box Numbers should be addressed to: Box No. —, *The Radio Constructor*, 57 Maida Vale, London, W9 1SN

NEW CATALOGUE NO. 18, containing credit vouchers value 50p, now available. Manufacturers new and surplus electronic and mechanical components, price 23p post free. Arthur Sallis Radio Control Ltd., 28 Gardner Street, Brighton, Sussex.

VHF KIT, 80-178MHz. Receiver, tuner, converter. World Wide Sales. £4.13 or S.A.E. for literature. Johnsons (Radio C), Worcester, WR1 2DT.

SERVICE SHEETS (1925-1971) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 13p. Please send S.A.E. with all orders/enquiries. Hamilton Radio, 54 London Road, Bexhill, Sussex. Telephone: Bexhill 7097.

CONSTRUCTORS USED COMPONENTS. Parcels at 50p each, including postage, 50 assorted resistors. 50 assorted capacitors. 10 electrolytic capacitors. 10 assorted knobs. 5 assorted potentiometers. 20 assorted valve bases. Please state which parcel required. Broadcast type twin gang variable capacitors at 18p each. Speakers at 50p each. 7 inch, 5 inch, 5½ x 3½ inch elliptical. P. & P. 18p. Box No. G142.

BUILD IT in a DEWBOX robust quality plastic cabinet 2in. x 2½in. x any length. S.A.E. for details. D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset. Write now - right now.

RECORD TV SOUND using our loudspeaker isolating transformer. Provides safe connection to recorder. Instructions included. 70p plus 10p P. & P. Crowborough Electronics (R.C.), Eridge Road, Crowborough, Sussex.

NEW COMPONENTS Capacitors, 1000/30V. 100/25V. 14p; 350/12V. 25/50V. 8, 150V. 8p; 16/275V. 1/125V. 0.5/250V. 6p. 4-pole 3-way wafer switches. 12p. Appliance suppressor cap. (lead thro') .025+005. 15p. Min. order 60p plus 10p P. & P. Many other items. Send s.a.e. for free list. Balfour Supplies, 2 Church Lane Cottages, Chalfont St. Peter, Bucks.

200 MIXED RESISTORS, ¼ - ½ - 1 watt. All preferred values. No uncommon types. Brand new. only 60p post paid. Manley, 13 Randisbourne Gardens, Bromley Road, London S.E.6.

JOIN THE INTERNATIONAL S.W. LEAGUE. Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. - both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazines, etc., £1.75 per annum. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

(Continued on page 189)

BENTLEY ACOUSTIC CORPORATION LTD.

38 Chalcot Road, Chalk Farm
LONDON, N.W.1.
01-722-9090

The Old Police Station
Gloucester Road
LITTLEHAMPTON Sussex
PHONE 6743

Please forward all mail orders to Littlehampton

1S4	.22	30PL13	.75	ECH83	.39	PCF82	.30	UBC81	.40	BC108	.13
3A4	.25	3SA3	.48	ECH84	.34	PCF84	.40	UBF80	.30	BC113	.25
5Z4G	.35	150B2	.58	ECL80	.30	PCF86	.44	UBF89	.30	BC118	.23
6AJ5	.43	DAF91	.20	ECL82	.30	PCF81	.30	UCF92	.35	BC211	.38
6AN8	.49	DAF96	.33	ECL83	.52	PCF802	.40	UCF84	.32	BF159	.28
6AQ5	.22	DF91	.14	ECL84	.55	PCF806	.58	UCF85	.34	BF163	.20
6AT6	.18	DF96	.33	ECL86	.35	PCL82	.32	UCF80	.34	BF173	.38
6AV6	.28	DK91	.26	EF22	.63	PCL83	.58	UCH42	.60	BF180	.30
6BA6	.20	DK92	.38	EF41	.58	PCL84	.34	PCL81	.34	BY100	.18
6BC8	.50	DK96	.35	EF80	.22	PCL805/	.30	UCL82	.33	BY126	.15
6BE6	.21	DL92	.26	EF85	.26	85	.40	UCL83	.48	BY127	.18
6BJ6	.49	DL94	.32	EF86	.29	PCL86	.38	UF41	.50	BY210	.25
6J30L2	.55	DL96	.35	EF89	.23	PD506	1.44	UF80	.35	BY211	.25
6BR7	.79	DY87/6	.24	EF91	.17	PFL200	.52	UF85	.34	BY212	.25
6BW6	.72	DY802	.37	EF92	.35	PL36	.47	UF86	.63	BY213	.25
6BW7	.54	EBRC	.60	EF183	.26	PL81	.44	UF89	.27	OA81	.09
6BZ6	.31	EBACC	.40	EF184	.29	PL82	.30	UL41	.54	OA91	.09
6C4	.28	E180F	.90	EH90	.38	PL83	.32	UL84	.31	OA95	.09
6E5	.50	EABC80	.20	EL34	.46	PL84	.30	UY41	.48	OA200	.09
6F1	.59		.30	EL41	.53	PL504/		UY85	.25	OA202	.10
6F23	.68	EAF42	.48	EL84	.22	PL500	.62	AC113	.25	OC23	.38
6F28	.70	EB34	.20	EL86	.38	PL508	.90	AC127	.17	OC24	.38
6K7G	.10	EB91	.11	EL95	.33	PL509	1.30	AC128	.20	OC25	.38
6L6GT	.39	EBC41	.48	EM80	.38	PX4	.16	AC134	.25	OC26	.24
6X4	.20	EBC81	.29	EM81	.39	PX25	1.16	AC156	.20	OC28	.60
9D7	.78	EBF80	.30	EM83	.75	PY33/2	.50	AC157	.25	OC35	.32
10F18	.35	EBF83	.38	EM84	.31	PY81	.24	AD140	.36	OC36	.43
12A6	.63	EBF89	.27	EM87	.35	PY82	.24	AD149	.50	OC38	.43
12BA6	.30	EC92	.35	EY85	.33	PY83	.26	AD161	.45	OC44	.10
12BH7	.27	ECC32	.30	EY87/6	.30	PY88	.33	AD162	.65	OC5	.11
20P4	.89	ECC33	1.50	EZ40	.40	PY500	.95	AF114	.25	OC46	.15
30C15	.60	ECC33		EZ80	.21	PY800	.33	AF115	.15	OC70	.13
30C17	.77		1.50	EZ81	.22	PY801	.33	AF119	.23	OC71	.11
30C18	.60	ECC81	.16	HV82	.53	QV03/		AF121	.30	OC72	.11
30E5	.65	ECC82	.19	KTYW62	.63	10	.20	AF126	.18	OC74	.23
30FL1	.60	ECC83	.20	R19				AF139	.65	OC75	.11
30FL2	.60	ECC84	.28	PC86	.47	U19	1.73	AF180	.48	OC78	.15
30FL14	.68	ECC85	.25	PC88	.47	U25	.64	AF186	.55	OC78D	.15
30ML5	.58	ECC86	.40	PC97	.36	U26	.56	AF239	.38	OC81	.11
30L17	.67	ECC88	.35	PC900	.32	U191	.58	BA102	.45	OC81D	.11
30P19/4	.58	ECH80	.27	PCC84	.29	U251	.65	BA115	.14	OC82	.11
30P4MR		ECF82	.26	PCF82	.43	U301	.40	BA116	.25	OC83	.20
		ECF86	.65	PCC89	.45	U801	.93	BA129	.13	OC84	.24
30P12	.69	ECH42	.61	PCC189	.48	UABC80		BA130	.10	OC123	.23
30PL1	.59	ECH81	.27	PCF80	.28			BC107	.13	OC139	.23

All goods are unused and boxed, and subject to the standard 90-day guarantee. Terms of business: Cash or cheque with order only. No C.O.D. orders accepted. Post/packing charge 3p per item subject to a minimum of 9p per order. Orders over £5 post free. All orders despatched same day by first class mail. Complete catalogue with conditions of sale 7p post paid. Any parcel insured against damage in transit for only 3p extra per order. Business hours 9 a.m.-5.30 p.m. Sats. 9 a.m.-1 p.m. Littlehampton closed Sats. No enquiries answered unless S.A.E. enclosed for reply.

TECHNICAL TRAINING in Radio, Television and Electronic Engineering

Let ICS train YOU for a well-paid post in this expanding field. ICS courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success. Diploma Courses in Radio, TV Engineering and Servicing, Colour TV Servicing, Electronics, Computers, etc. Expert coaching for:

- * C.&G. TELECOMMUNICATION TECHNICIANS CERTS
- * RADIO AMATEURS EXAMINATION
- * RADIO OPERATOR CERTIFICATES

CONSTRUCTOR COURSES

Build your own transistor portable, signal generator, multi-test meter—all under expert guidance. POST THIS COUPON TODAY and find out how ICS can help YOU in your career. Full details of ICS courses in Radio, Television and Electronics will be sent to you by return mail.

Member of Association of British Correspondence Colleges

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 248, Intertext House, Stewarts Road, London SW8 4UJ

Name
BLOCK CAPITALS PLEASE

Age

Address



EST 1891


10.71

NEW STYLE SELF-BINDER

for "The Radio Constructor"

The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

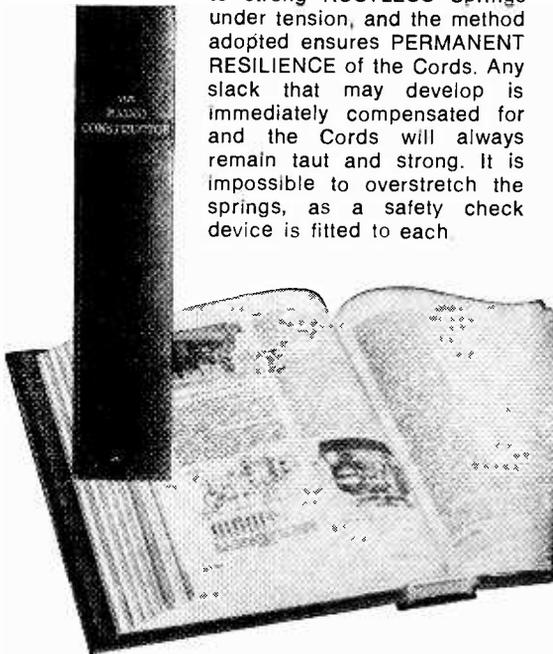

PRICE **75p** Postage 10p

Available only from:-

Data Publications Ltd.
57 Maida Vale London W9 1SN

One year's electronics experience + ONC or C & G?

Then become a Radio Technician with the National Air Traffic Services. You would work on the installation and maintenance of a wide range of sophisticated electronic systems and specialised equipment throughout the U.K. You would be involved with RT, Radar, Data Transmission Links, Navigation Aids, Landing Systems, Closed Circuit T.V. and Computer Installations. You could also work on the development of new systems.

To qualify for entry to our training course you must be aged 19 or over, have at least one year's experience in electronics and preferably O.N.C. or C. & G. (Telecoms). Your starting salary would be £1,143 (at 19) to £1,503 (at 25 or over), scale max. £1,741 - shift duty allowances. Good career prospects.

Send NOW for full details of how you can become a Radio Technician. Complete the coupon and return to A. J. Edwards, C.Eng., MIEE, Room 705, The Adelphi, John Adam Street, London WC2N 6BQ, marking your envelope 'Recruitment'.

I meet the requirements, please tell me more about the work of a Radio Technician.

NAME _____

ADDRESS _____

(A/R/C/18)

Not applicable to residents outside the United Kingdom.

NATS

National Air Traffic Services

SMALL ADVERTISEMENTS

Continued from page 187

SERVICES FOR CONSTRUCTORS:- Etched aluminium fascia panels to specification. Plain aluminium panels to individual sizes. Labels, dials, nameplates. Instrument scales. Drafting tapes for printed circuit layouts. S.A.E. for details. R. A. Marsh, 29 Shelbourne Road, Stratford on Avon, Warwick.

RELAYS. Sigma type 72AOZ, octal base, £1.50; Carpenter polarised, £1; D164816, £1.50. Box No. G155.

POSTAL ADVERTISING? This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. - The Holborn Direct Mail Company, Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 1495.

5 TRANSISTOR 1 WATT AUDIO AMPLIFIERS, for 7½-15V supply. Standard 3 ohm output. Only £1 each. Manley, 13 Randisbourne Gardens, Bromley Road, London S.E.6.

"THE ANSWER" BUREAU, PRINCES RISBOROUGH, BUCKS. For sincere and genuine marriage/friendship introductions. Details free.

"GOVERNMENT SURPLUS WIRELESS EQUIPMENT HANDBOOK". Contains circuits, data, illustrations, components lists for British/U.S.A. receivers, transmitters, trans/receivers: includes modifications to sets and test equipment. Surplus/commercial cross-referenced transistor and valve guide. A gold mine of valuable information. Price £2.84. P. & P. 16p. Myers. 112 Stainburn Crescent, Leeds 17, Yorks.

WORLD DX CLUB covers all aspects of SWling on Amateur and Broadcast Bands through its monthly bulletin "Contact". Membership costs £1.38 a year. Enquiries to Secretary, WDXC, 11 Wesley Grove, Portsmouth, Hants., PO3 5ER.

HOLIDAY ACCOMMODATION. Burwood Lodge Hotel, Dawlish Road, Teignmouth, S. Devon. Especially for parents with young children. Facing south, on the cliffs, direct access by private path to sea. Mothers' kitchen, automatic washing machines, baby listening service. Licensed lounge. Ample free parking.

RESISTORS, CAPACITORS, POT'S, Electrolytics, Transistors, Diodes, Valves at very reasonable prices. Beginners specially catered for. S.A.E. for list. 24 resistors on card with values marked, 20p. Hope, Pentalardd, Maesycerugiau, Pencader, Carmis.

FOR SALE: Creed Teletax transceiver type TR 105, £15. Ex-R.A.F. tuning fork drive unit type 114. £12. Box No. G167.

IF YOU HAVE ENJOYED A HOLIDAY on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from:- The Hon. Membership Secretary, The Broads Society, "Icknield", Hilly Plantation, Thorpe St. Andrew, Norwich, NOR 85S.

FOR SALE: CR 150 receiver. 2/60 MHz with p.s.u. Good condition. new valves, £20. BC221, mains operated, £10. Box No. G.168.

WANTED: Marconi AD 8882B receiver manual circuit diagram, p.s.u. details, etc. for loan or purchase. Postage refunded on all correspondence. Pring, 89A High Street, Chard, Somerset.

WANTED: 9.5mm cine equipment. Cameras, projectors, editors, splicers, film reels, etc. Details to: Box No. G169.

(Continued on page 191)

RADIO OPERATORS

Do you Hold
PMG II OR PMG I OR
New General Certificate
OR had Two Years' Radio
Operating Experience?

**LOOKING FOR A
SECURE JOB
WITH GOOD PAY
AND CONDITIONS?**

Then apply for a post with the Composite Signals Organisation. These are Civil Service posts, with opportunities for service abroad, and of becoming established i.e. Non-Contributory Pension Scheme.

Specialist Training Courses (free accommodation) starting January, April and September, 1972.

If you are British born and resident in the United Kingdom, under 35 years of age (40 for exceptionally well qualified candidates), write NOW for full details and an application form from:

**Government Communications
Headquarters,**

Recruitment Officer

Oakley,

Priors Road,

CHELTENHAM,

Glos., GL52 5AJ.

Tel: Cheltenham 21491. Ext. 2270.

SMALL ADVERTISEMENTS

Use this form for your small advertisement

To: The Advertisement Manager, Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please insert the following advertisement in the issue of THE RADIO CONSTRUCTOR

16 words at 4p
= 64p.

ALL WORDING
IN
BLOCK LETTERS
PLEASE

I enclose remittance of being payment at 4p a word. MINIMUM 60p.
Box Number, if required, 10p extra.

NAME.....

ADDRESS.....

Copy to be received four weeks prior to publication. Published on the 1st of every month.

FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

SEND FOR YOUR FREE COPY TO-DAY

ENGINEERING OPPORTUNITIES is a highly informative 74 page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses administered by our Specialist Electronics Training Division — explains the benefits of our free Appointments and Advisory service and shows you how to qualify for five years promotion in one year.

'SATISFACTION OR REFUND OF FEE' TERMS

We give a written agreement that if after completing one of our courses, you do not pass your examination or are dissatisfied in any other way we will refund your complete fee.

PRACTICAL EQUIPMENT INCLUDING TOOLS

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with all the practical equipment you need, plus Basic Practice and Theoretical Courses for beginners in Radio, TV, Electronics, etc.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. (B10), Aldermaston Court, Reading RG7 4PF

SEND OFF THIS COUPON TO-DAY!

Tick subjects that interest you:

- AMSE (Elec) City & Guilds Certificate RTEB Certificate
 Radio Amateurs' Exam DMG Certificate Colour TV
 Electronic Engineering Computer Electronics Radio and TV
 Servicing Practical Electronics Practical TV & Radio
 Please send booklets & full information without cost or obligation.



NAME..... AGE.....
(BLOCK CAPITALS PLEASE)

ADDRESS.....

OCCUPATION.....

To: BIET Dept. B10, Aldermaston Court, Reading RG7 4PF
Accredited by the Council for the Accreditation
of Correspondence Colleges.

To All Users of Industrial Electronics

Take advantage of our very competitive prices and high quality workmanship.

DESIGN AND CONSTRUCTION OF INDUSTRIAL ELECTRONICS EQUIPMENT. INDUCTION HEATING GENERATORS. METAL DETECTORS, POWER SUPPLIES, AUTOMATION AND CONTROL EQUIPMENT.

HIGH QUALITY
SHORT DELIVERY TIMES.
TWO YEARS GUARANTEE

DESIGNS CONSTRUCTED TO CUSTOMERS OWN SPECIFICATIONS.

WRITE FOR FULL DETAILS TO:-

“E.B.E.H. A. KYPRIOTIS”

LABORATORIES OF INDUSTRIAL ELECTRONICS

OFFICE
ANDROMAHIS 50, KALLITHEA
ATHENS, GREECE

FACTORY
PAPAFLESSA 3, TSAKOS
AGHIA PARASKEVI
ATHENS, GREECE

SMALL ADVERTISEMENTS

(Continued from page 189)

ARE YOU A MOTORING ENTHUSIAST? The Seventy Motor Club caters for all types of motor sport-racing, rallies, hill climbs, etc. Monthly Bulletin free to members. For full details write to: The General Secretary, Colin Peck, "Dancers' End", St. Winifred's Road, Biggin Hill, Kent.

FOR SALE: Electronic Devices (Cheltenham) Ltd. electric "bug" morse key. £10. Box No. G170.

FREE GIFT when you request our quality stamps, supplied on approval. Generous discounts. Details from: Watson's Philatelic Service, 6 Beech Avenue, Brentwood, Essex.

FOR SALE: Small stamp collection £5. Box No. G.171.
STAMPS. 100 different Europe 25p. plus 100 different free. Hope, Pentalardd, Maescrugiau, Pencader, Carm.

FOR SALE: Raven radio control Tx & Rx. Multichannel reed. £25. S.A.E. for details. Box No. G172.

ESSEX GARDENERS. Buy your bedding and rock plants, shrubs, etc., also cacti from May's Nurseries, 608 Rayleigh Road, Hutton, Brentwood, Essex. Callers only. Monday to Saturday.

"MEDIUM WAVE NEWS" Monthly during Dx season - Details from: K. Brownless, 7 The Avenue, Clifton, York.

RADIO AMATEUR EXAMINATION COURSE. Wednesday 6.30 to 9.00 p.m. To secure a place, enrol as soon as possible at ACTON TECHNICAL COLLEGE (opposite Town Hall). Telephone 992 3248. Lecturer: W. G. Dyer, M.I.E.E. G3GEH. Syllabus embraces Theory, Licence Conditions and Morse instruction; no prior knowledge is assumed or required.

JOHN SAYS . . .

RING MODULATOR by Dewtron is professional, transformerless, 5 transistor, has adjustable F1/F2 rejection. **Module £7.** Unit **£8.90** WAA-WAA Pedal kit of all parts, incl. all mechanics & instr. **ONLY £2.45.** **AUTO RHYTHM** from Dewtron modules. Simple unit for waltz, foxtrot, etc. costs **£16.55** in modules. **SYNTHESISER MODULES** and other miracles. Send 15p for illust. list. **D.E.W. LTD., 254 Ringwood Road, FERNDOWN, Dorset.**

200 Mixed Resistors $\frac{1}{2}$, $\frac{1}{4}$, 1 watt types all preferred values from 10ohm - 2meg. **only 50p**

RELAYS moving coil, very small sealed type 350 + 350ohm **15p each**

Miniature, 700 ohm 2 pole 2 way. **10p each**

1 WATT Transistor Amplifiers, 5 transistor, 3-15 ohm output. **£1.00 each**

$7\frac{1}{2}$ - 15v supply. **£1.00 each**

3 WATT Amplifiers, 6 transistor, 18 - 24v supply. **£2.50 each**

Please include 10p postage per order. **MAIL ORDER ONLY**

A. J. Manley, 13 Randisbourne Gardens, Bromley Road, London S.E.6

CIRCUITS! CIRCUITS!

Ten exciting circuits per month with instructions to build. Every month a completely new set. This month's circuits cover

"MISCELLANEOUS PROJECTS"

only 50p per set of ten

Postage and packing free

Free Data and Technical A-Z cards. Build up the complete set month by month. Cheques and P.O's to Dept. R/C, Photonics, 3 Whitehall Gardens, London, E.4.


SYNTHESISER MODULES

Send s.a.e. for details of voltage-controlled modules for synthesiser construction to D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

PLAIN-BACKED NEW STYLE SELF-BINDERS

for your other magazines

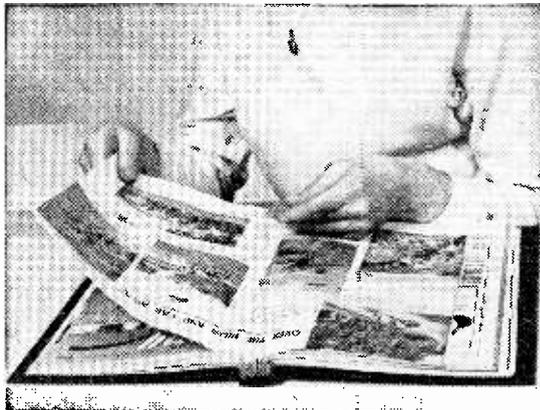(max. format 7 $\frac{1}{2}$ " x 9 $\frac{1}{2}$ ")



The "CORDEX" Patent Self-Binding Case will keep your copies in mint condition. Issues can be inserted or removed with the greatest of ease. Specially constructed Binding cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for, and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

COLOURS: MAROON OR GREEN

(If choice not stated, colour available will be sent)

PRICE 70p Postage 10p

Available only from:-

Data Publications Ltd.
57 Maida Vale London W9 1SN

CHASSIS and CASES by



H. L. SMITH & CO. LTD.
287/9 Edgware Road
London W2 1BE
TEL: 01-723 5891


BLANK CHASSIS

FOUR-SIDED 16 SWG ALUMINIUM

Size	Price	Base	Size	Price	Base
6x4x2"	34p	17p	10x8x2½"	66p	30p
7x4x1½"	33p	18p	12x7x2½"	66p	33p
7x5x2"	40p	19p	12x9x2½"	76p	38p
8x4x2"	38p	19p	13x8x2½"	76p	38p
8½x5½x2"	44p	21p	14x7x3"	80p	36p
9x7x2"	50p	26p	14x10x2½"	88p	47p
10x4x2½"	50p	21p	15x10x2½"	92p	50p
12x4x2½"	55p	22p	17x10x3"	£1.10	55p
12x5x3"	66p	26p	Plus post and packing		

CASES ALUMINIUM, SILVER HAMMERED FINISH

Type	Size	Price	Type	Size	Price
N	8x6x2"	£1.00	W	12x7x7"	£2.00
N	6x6x3"	£1.05	W	15x9x8"	£3.15
N	4x4x2"	80p	Y	8x6x6"	£2.25
U	4x4x4"	95p	Y	12x7x7"	£2.80
U	5½x4½x4½"	£1.15	Y	13x7x9"	£3.15
U	8x6x6"	£1.45	Y	15x9x7"	£3.35
U	9½x7½x3½"	£1.55	Z	17x10x9"	£4.15
U	15x9x9"	£3.00	Z	19x10x8½"	£4.50
W	8x6x6"	£1.90	*Height		

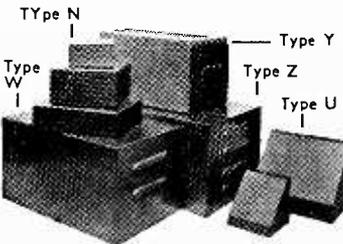

Type N has removable bottom. Type U removable bottom or back, Type W removable front, Type Y all screwed construction, Type Z removable back and front. Plus p. & p.

TO FIT OUR CASES

7x5½x1½"	38p	12x6½x2"	60p	33p
7x5½x2"	43p	14x8½x2"	74p	44p
11x6½x1½"	48p	15½x9½x2½"	94p	52p
11x6½x2"	55p	17½x9½x2½"	£1.05	59p

Plus post & packing

PANELS: Any size up to 3ft. at 36p sq. ft. 16 s.w.g. (18 s.w.g. 32p). Plus postage and packing

FREQUENCY LIST TRANSFERS

We have a limited supply of sheets of Dial Frequency Transfers in black. Short Wave frequencies 1.8Mc/s to 32Mc/s and 144Mc/s and 146Mc/s. Includes amateur band marker frequencies at 100kc/s points and other short wave frequencies from 2 to 32Mc/s at every 500kc/s points. Each frequency is repeated. Two sheets for 5p. five sheets for 10p, postage 3p.

DATA PUBLICATIONS LTD.,
57 Maida Vale, London W9 1SN.

YUKAN SO PROFESSIONAL THE

SELF-SPRAY YUKAN AEROSOL WAY -

Get these air drying GREY HAMMER
NOW! OR *BLACK WRINKLE*
(CRACKLE) finishes

Yukan Aerosol spraykit contains 453g. fine quality, durable easy instant spray. No stove baking required. Hammers available in grey and blue, 90p carr. pd. Modern Eggshell Black Wrinkle (Crackle) producing a 3D textured finish, 90p carr. pd. all at 85p per push-button self-spray can at our counter. Also durable, heat and water resistant Black Matt finish (339g self-spray cans only) 75p carr. pd.

SPECIAL OFFER. One can plus optional transferable snap-on trigger handle (value 25p) for 96p carr. pd. Choice of 13 self-spray plain colours and primer (motor car quality) also available.

Please enclose cheque or crossed P.O. for total amount direct to:

DEPT: N/5 YUKAN, 307a EDGWARE ROAD, LONDON W2 1BN

We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organisations—We can supply you too. *Now British—Open all day Saturday. Closed Thursday afternoons.*

Other Yukan Air Drying Aerosols, 453g. at 90p carr. pd. include:

- Zinc Chromate
- Clear Lacquer
- Metallics: Grey, Blue.

DATA BOOK SERIES

- DB5 TV FAULT FINDING**
124 pages. Price **50p**, postage 6p.
- DB16 RADIO CONTROL FOR MODELS**
192 pages. Price **75p**, postage 8p.
- DB17 UNDERSTANDING TELEVISION**
512 pages. Price **£1.88**, postage 20p.
- DB18 AUDIO AMPLIFIERS**
128 pages. Price **53p**, postage 6p.
- DB19 SIMPLE SHORT WAVE RECEIVERS**
140 pages. Price **80p**, postage 6p.

I enclose Postal Order/Cheque for.....in payment for.....

NAME.....

ADDRESS.....

(Please use Block Capitals for both name and address)

Postal Orders should be crossed and made payable to Data Publications Ltd.

Overseas customers please pay by International Money Order.

All publications are obtainable from your local bookseller.

Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please mention **THE RADIO CONSTRUCTOR** when writing to advertisers

Foreign Language Broadcasts

The Table lists B.B.C. transmissions in the languages shown. Two-figure numbers indicate Metre Bands and three-figure numbers indicate Metres. Where applicable, days are quoted in brackets. Time is in GMT. The list will be completed in Data Sheets 56 and 57


AIRABIC 0345-0545 16, 19, 25, 31, 41, 49 and 198, 417, 428, 470m. 1300-2100 11, 13, 16, 19, 25, 31, 41 or 49 and 198, 417, 428 or 470m.	Cantonese 1245-1300 13, 16, 19, 25, 31, 41 2215-2230 19, 25, 31, 41, 49, 75	(Africa ctd.) 0630-0700 19, 25, 31, 41 1200-1330 13, 16 1830-1930 13, 16, 19, 31 2115-2130 25, 31 2130-2145 16, 25, 31
BENGALI 0130-0145 19, 25, 31, 41 0930-1000 13, 16 (W) 1415-1430 13, 16, 19, 25 1615-1645 25 (W)	CZECH/SLOVAK 0615-0630 25, 31, 41, 49 1115-1130 16, 19, 25, 31 (Slovak) 1345-1400 19, 25, 31 (Su, Tu, Th, Sa) 1400-1430 19, 25, 31 1430-1445 19, 25, 31 (Su) 1600-1615 19, 25, 31 (Slovak) 1845-1900 19, 25, 31, 41, 49 1945-2015 19, 25, 31, 41, 49 and 232m. 2045-2115 19, 25, 31, 41, 49 and 232m. until 2100 (Slovak) 2145-2200 25, 31, 41, 49	Europe 0530-0545 232m. 0630-0645 31, 41, 49 and 232m., also 464m. (Sa, Su) 0715-0730 31, 41, 49 and 232m. 1115-1230 19, 25, 31, 49 and 371m. 1800-1900 31, 41, 49 and 232m. 2130-2145 41, 49, 75 and 232m.
BULGARIAN 0445-0500 16, 19, 25, 31, 41 1130-1145 13, 16, 19, 25 1400-1415 13, 16, 19 1645-1730 16, 19, 25, 31 1915-1930 41, 49 (Tu, Th, Sat) 2130-2200 19, 25, 31, 41, 49	FINNISH 1530-1600 19, 25, 31 (Su) 1545-1600 19, 25, 31 (M, W, Th, Sa) 1600-1645 19, 25 1930-1945 31, 41	GERMAN 0415-0500 31, 41, 49, 75 and 232, 464m. 0515-0600 25, 31, 41, 49 or 75 1145-1215 19, 25, 31, 41 1615-1630 371m. and 90.2MHz 1630-1700 25, 31, 49 and 232m. 1900-2100 31, 49, 75 and 232m. until 1945 2245-2300 41, 49, 75 and 232m.
BURMESE 0015-0030 19, 25, 31 1345-1415 13, 16, 25, 31 2330-2345 31, 49	FRENCH <i>Africa</i> 0430-0445 19, 25, 31, 41 0515-0545 19, 25, 31, 41	Also broadcast on 371m. and 90.2MHz for listeners in Greater Berlin)
CHINESE <i>Standard Chinese</i> 1000-1030 13, 16, 19, 25, 31, 41 1200-1245 13, 16, 19, 25, 31, 41 2230-2245 19, 25, 31, 41, 49, 75		

HENRY'S RADIO LIMITED

ENGLAND'S LEADING ELECTRONIC CENTRES

HI-FI · COMPONENTS · TEST · PA · DISCOTHEQUE · ELECTRONIC ORGANS · MAIL ORDER

COMPLETELY NEW
10th EDITION
CATALOGUE

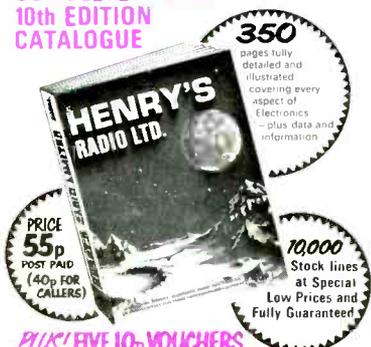

350 pages fully detailed and illustrated covering every aspect of Electronics - plus data and information

PRICE 55p POST PAID (40p for CALLERS)

10,000 Stock lines at Special Low Prices and Fully Guaranteed

PLUS! FIVE 10p VOUCHERS FOR USE WITH PURCHASES

Send to this address - Henry's Radio Ltd. (Dept. RC), 3 Albemarle Way, London, E.C.1 - for catalogue only.

(All other mail to '303' as below).

A NEW HENRY'S CATALOGUE IS A MUST FOR ELECTRONICS TODAY!

TEST EQUIPMENT For Every Purpose



AF105 50k/V multimeter (illus.). Price £8.50, p.p. 20p. Leather case £1.42
200H 20k/V Price £3.87, p.p. 20p. Case 62p
500 30k/V multimeter, Price £8.87, p.p. 20p. Leather case £1.50
TH133 2k/V Price £4.12, p.p. 15p. Leather case £1.15
TE65 Valve voltmeter (illus.) Price £17.50, p.p. 40p
SE250B Pocket pencil signal injector. Price £1.75, p.p. 15p

SE500 Pocket pencil signal tracer. Price £1.50, p.p. 15p
TE20D RF generator. Price £15, p.p. 40p
TE22D Matching audio generator. Price £17, p.p. 40p
TE15 Grd dip meter. Price £12.50, p.p. 40p
TO3 Scope 3in. tube. Price £37.50, p.p. 50p
TE22 Audio Generator. Price £17, p.p. 40p
C1-5 Pulse Scope £39.00 p.p. 50p



PANEL METERS

Complete range in stock. 38, 65 and 85 types plus large range Edge types also 240-250 types. (Get a copy of our latest catalogue for full specifications and further ranges.)

MORE OF EVERYTHING AT LOW PRICES ALWAYS FROM HENRY'S

★ COMPONENTS IN STOCK FOR ALMOST ALL PUBLISHED DESIGNS. YOUR ENQUIRIES INVITED. SEND LARGE S.A.E. (WITH LIST) FOR PARTS QUOTE FOR ALL CIRCUITS.

TRANSISTORS - I.C.'s
The largest range available. Send for free list No. 36

HENRY'S SUPPLY ALL YOUR AUDIO · ELECTRONIC NEEDS

TRANSISTOR AMPLIFIERS



(Leaflets Ref. No. 6 and 8) Post, etc., 20p

4-300 4TR 9V 300mW	£1.75	PA7 6TR 16V 7W	£3.62
104 4TR 9V 1W	£2.12	608 6TR 24V 10W	£4.12
304 4TR 9V 3W	£2.47	410 4TR 28V 10W	£4.97
555 6TR 12V 3W	£2.75	MPA12/3 6TR 18V 12W	£4.50
		MPA12/15 6TR 36V 12W	£5.25

OPTIONAL POWER SUPPLIES Post, etc., 20p

PE00 (1 or 2) for 104, 304	£2.62
PS20 (1 or 2) for PA7	£3.47
MU24/40 (1 or 2) for MPA12/3 or MPA12/15	£4.50
P11 for 608	£2.87
P15 for 410	£2.62

SINCLAIR PROJECT 60 PACKAGE DEALS - SAVE POUNDS!

2x230 amplifier, stereo 60 pre-amp, PZ5 power supply, £16.75, Carr. 40p. Or with PZ6 power supply £18.25, Carr. 40p. 2x250 amplifier, stereo 60 pre-amp, PZ6 power supply, £20.25, Carr. 40p. Transformer for PZ3 £2.45 extra. Any of the above with Active Filter unit add £4.75 or with pair C16 speakers add £16. Also new FM Tuner £21, 2000 Amplifier £24.50, p.p. 50p, 3000 Amplifier £31.50, p.p. 50p. Also IC12 £2.50.



LOW COST HI-FI SPEAKERS

E.M.I. Size 131" by 81"
TYPE 150 6 watt, 3, 8 or 15 ohms £2.12, Post 22p
TYPE 150TC Twin cone version £2.75, Post 22p
TYPE 450 10 watt with twin tweeters and crossover, 3, 8 or 15 ohms. £3.50, Post 25p
TYPE 350 20 watt with tweeter and crossover, 8 and 15 ohms £7.50, Post 28p



POLISHED CABINETS FOR 150, 150TC and 450 £4.50, Post 30p
TERRIFIC RANGE OF SPEAKERS, KITS AND CABINETS IN STOCK - SEE CATALOGUE OR YOUR ENQUIRIES INVITED.

MONO, STEREO AND MIXING EQUIPMENT, HIGH QUALITY WITH LOW PRICES



SELF-POWERED SILICON-FET CONTROL UNITS/PREAMPLIFIERS

FET 9/4 Mono or single channel. Adjustable levels. All facilities plus microphone. Mixing Price £12.50

FET 154 Stereo with all facilities, magnetic cart. input, etc. Price £16.50
SILICON POWER AMPLIFIERS FOR USE WITH ABOVE
PA25 25 watts into 8 ohms £7.50
PA50 50 watts into 4 ohms £9.50
MJ442 Power Supply for 1 or 2 PA25's or 1 only PA50 £6.00, Post 20p

FREE BROCHURE No. 25 on REQUEST
NO SOLDERING - ALL UNITS INTERCONNECTING ON DEMONSTRATION AT "356"

NIXIE TUBES

XX3 or XX13 0-9 side view, with data sheet 85p each
GN4 end view 0-9 with socket & data £1.75
All I.C.'s for Digital Clocks in stock.
HENRY'S CLOCK CIRCUIT - No. 29 10p

BUILD THIS VHF FM TUNER

5 MULLARD TRANSISTORS 300 kc/s BANDWIDTH. PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it - VHF FM gives the REAL sound. All parts sold separately. Free leaflet Nos. 3 & 7.
TOTAL £6.97 p.p. 20p
Cabinet £1.00, Decoder Kit £5.97, Tuning Meter £1.75, Mains unit (optional) Model PS900 £2.47
Mains unit for Tuner and Decoder PS1200 £2.62



NEW "BANDSPREAD" PORTABLE TO BUILD

Printed circuit all-transistor design using Mullard RF/IF Module. Medium and Long Wave bands plus Medium Wave Bandspread for extra selectivity. Also slow-motion geared tuning, 600mW push-pull output, fibre glass PVC covered cabinet, car aerial socket. Attractive appearance and performance. TOTAL COST TO BUILD £7.98 p.p. 32p (Battery 22p)



All parts sold separately - Leaflet No. 2
77 PORTABLE (as previously advertised) £6.98 p.p. 35p. From stock. (Leaflet No. 1)

HI-FI TO SUIT EVERY POCKET



TELETON '206 Garrard SP25 Mk III. Goldring G800 Series Carr. Plinth/Cover. 10 watt 3 way bookshelf Speaker Systems. All leads, etc. (Rec. Price £81)

SAVE £29.00 **£54.95** Carr. £2

(or with U.K. made HL SA 707 (same performance) £58.95)

Plus free pair Stereo headphones

TELETON F2000 Med. Wave. Stereo FM Tuner Amplifier, Garrard 2025 TC, 9TAHC Diam. Plinth/Cover, 10 watt Speaker Systems as above all leads, etc. (Rec. Price £91)

SAVE £31.00 **£59.95** Carr. £2

Plus free pair Stereo headphones

THE TWO MOST POPULAR SYSTEMS EVER - PLUS FULL 12 MONTHS GUARANTEE AS WITH ALL "HENRY'S" OFFERS!

FREE 10 page Audio - Hi-Fi Stock and Stereo Systems Discounts Lists. Save up to 40%! Demonstrations and Credit Terms (50 callers) Plus 12 months guarantee.

Electronic Components, Audio and Test Gear Centre
356 EDGWARE ROAD, LONDON, W.2.
Tel: 01-402 4736

High Fidelity Sales & Demonstrations Centre
354 EDGWARE ROAD, LONDON, W.2.
Tel: 01-402 5854

Electronic Organs, P.A. & Discotheque Centre
309 EDGWARE ROAD, LONDON, W.2.
Tel: 01-723 6963

Mail Orders, Special Bargain Shop, Industrial Sales
303 EDGWARE ROAD, LONDON, W.2.
Tel: 01-723 1008/9

"354" & "356" OPEN SIX FULL DAYS A WEEK 9 am to 6 pm MONDAY TO SATURDAY