

RADIO - ELECTRONICS


APRIL 1953

LATEST IN TELEVISION • SERVICING • AUDIO

HUGO GERNEBACK, Editor

SOLVING U.H.F.
ANTENNA PROBLEMS

See page 4

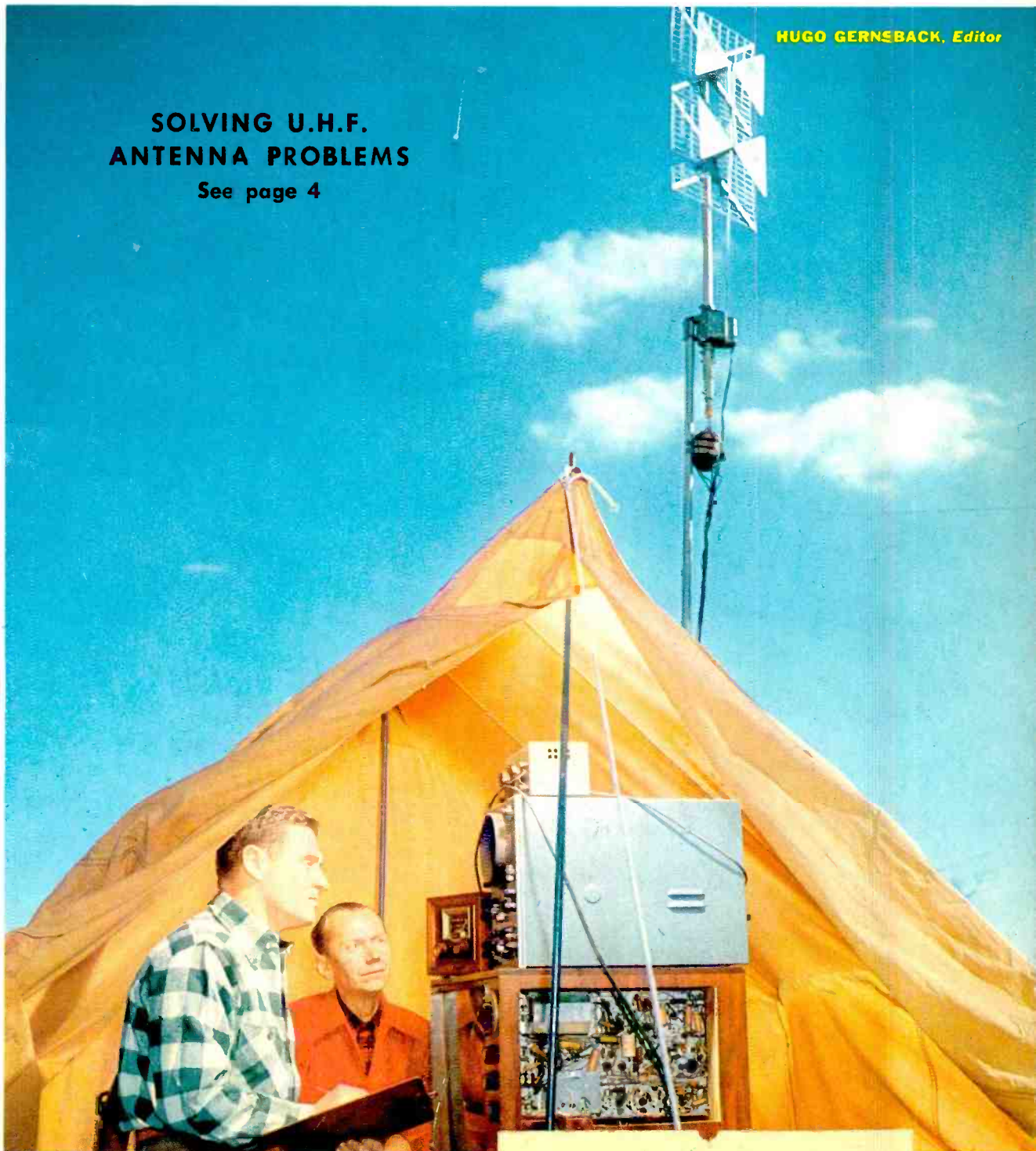

30¢

U. S. and
CANADA

In this issue: Long-Distance
TV Signal Tracing

STEVEN WELSH 1-54
6240 N TRIPP AVE
CHICAGO 30 ILL

-D.C.

You'll reap a harvest of sales...

with these RCA Radio Battery Sales Aids

RCA Radio Battery Tester and Tester Display Unit

With this RCA Battery Tester displayed on your sales counter, you'll cultivate and close *more* sales of RCA Batteries. You can demonstrate, on a plainly marked scale, the actual playing condition of popular types of radio batteries.

The specially designed Battery Tester WV-37A comes straight from the famous line of RCA Test Equipment.

Ask your local RCA Radio Battery Distributor how you can obtain the Radio Battery Tester and Counter Display Unit at an amazingly low cost, with your RCA Battery purchases.



Counter Merchandiser (3F439)

You'll see plenty of sales action with this RCA Radio Battery point-of-purchase merchandiser on your counter. Three-tier, step-back shelves for battery stock and forceful sales messages remind portable-radio owners to buy batteries—now. Sturdily constructed of steel wire reinforced to support more than 50 pounds of batteries.



Floor Stand (3F438)

Put this self-selling and supermarket-type floor stand to work on your sales floor and watch RCA Radio Battery sales zoom. It's a self-contained sales department that occupies only 18 inches x 18 inches of floor space, stands 44 inches high. Three-tier, step-back shelves and two lower shelves display batteries and suggest impulse purchases to prospective customers. Constructed of sturdy steel wire reinforced for extra strength.



Window Display (3F443)

This modern window display unit with hanging sign will tell sidewalk traffic your store is the headquarters for RCA Radio Batteries. Display it in your window and watch radio battery and portable radio sales grow. Size 15 inches wide x 10 inches deep.



Repeat-Business Stamp and Pad (3F413)

Stamp your name and address on all radio batteries you sell. It will remind customers to come to your store again for radio battery replacements and service. Three-line stamp.



See your local RCA Battery Distributor for the battery line and the battery sales aids that are geared to radio trade distribution



RADIO CORPORATION of AMERICA

RADIO BATTERIES

HARRISON, N. J.

TRANSOCEANIC TELEVISION

... *Intercontinental TV programs are feasible* ...

By HUGO GERNSBACK

DURING the past year we have heard from time to time about various intercontinental television projects. The idea is not new; indeed when television was in its infancy, Baird, as early as 1928, succeeded a number of times in bridging the ocean between England and the U. S.

It is true that Baird used low radio frequencies to achieve this; nevertheless, he proved that television *could* span distances over 3,000 miles. Of course in those days we had no cathode-ray TV—all transmitters and receivers used the rotating Nipkow disc as a scanner. Nor were the transatlantic transmissions accompanied by simultaneous sound.

Present-day TV transmissions require much higher frequencies, which limit the transmission range. To use these for transoceanic purposes, it is necessary to build many relay stations and skip from island to island—if possible—to reach our distant destination. Technically, this is feasible today. To cross the Atlantic, relay points can be established along the east coast of the North American continent; then jump to Greenland, thence via a chain of other islands to the Northernmost point of Scotland. This completes the chain. A similar arrangement could be worked out in the Pacific via Alaska and the Aleutian Islands, thence to Japan and the Asiatic mainland.

Other more expensive means of spanning the oceans would be via man-made floating, but moored, steel caissons, or "iron islands," carrying the relay towers. We also could use coaxial cables under the ocean. Both of these methods today seem impractical, mainly on account of the very high cost.

There remains another method. Recent researches indicate that long-distance reception of v.h.f. signals is possible without anything more spectacular than high power and directional antenna equipment. Reception at the Washington National Bureau of Standards from Cedar Rapids, Iowa, a distance of 775 miles, was consistent though very weak. It seems that here we have to do with a little-understood upper atmospheric, ionic layer effect. It would seem possible that using new and special antennas and other equipment, reliable long distance TV transmissions could be achieved in the future.

Let us now consider transocean television from an entirely different viewpoint. Let us assume in advance that all technical difficulties have been overcome. Let us also suppose that the economics of the physical transmission have been solved satisfactorily.

Now comes the crux of the problem: *Who will pay for the personnel in charge, cost of the programs, day after day, year after year?* Will these expenses be met by sponsors? That seems hardly likely if you but consider the language obstacle. Admittedly, U. S. programs in English, received in Great Britain would work out satisfactorily. Likewise British programs received in U. S. would no doubt be more than welcome. But again who would bear the program cost?

Evidently the only sensible arrangement would be that most of such programs would of necessity have to be paid

for by the various participating governments. These would then be goodwill programs in the main, aimed primarily to promote better understanding between nations. In this respect, International Television is certainly more than worthwhile.

For a number of obvious reasons, such international programs must remain a long-term project—it may be a great many years before even a modest exchange of such programs can become a reality. To begin with, only the U. S. at present has a population-wide television system—over 20 million receivers. By 1960 there will be over 50 million sets, enough to blanket the country effectively. Great Britain at present has a mere 1½ million TV receivers—while the rest of the world together has probably less than 2 million receivers.

It is almost certain that by 1960 the entire world—outside the U. S.—will still have considerably less than 10 million television receivers. Consequently, however much television is talked about in other countries, the fact remains that the U. S. could not hope to bring our programs to several hundred million people of the world for a long time to come.

Yet, it is possible to bring such programs to a vast foreign audience by using theater-type television screens, enabling thousands of persons to witness a single program simultaneously. But again we must consider the high cost of such an undertaking. Who would pay for it? Most governments probably might not. Should the U. S. finance such a world-wide project? Would it help in the long run to secure World peace? We do not profess to know the answer—maybe it might be an excellent investment.

International television programs of the future must also cope with the language problems. It is unthinkable to broadcast TV programs in *English* to such countries as France, Germany, Italy, and Spain. Nor would it be realistic to export such programs in foreign languages from a single center in the U. S.

The ideal method naturally would be an electronic language translator. But we must doubt if such a machine can ever be perfected. The voices of no two people are alike. There are vast differences in pitch, overtones, timbre, etc. Then, few people pronounce the same words alike. All this would help to confuse any machine that we could think up today.

The best workable method probably is simultaneous translation by special linguists, expert in such an endeavor. This system has worked exceedingly well at the United Nations, where all talks in any given language are translated with such rapidity that the translator is rarely more than 3 seconds behind the speaker.

In practice, the English sound part of a TV program arriving from the U. S. in France would *not* be broadcast. Instead, the expert French linguist will listen to the sound over his headphones. As fast as the U. S. sound comes in, he translates it and speaks into the microphone before him; his voice—in French—is now combined with the video part of the program and broadcast to the French audience.

Performance data
and characteristics
on several
popular commercial
forms of

UHF

ANTENNAS and TRANSMISSION LINES

By JOE ROCHE*

U.H.F. antenna installation may be new to most of us, but it's an old story to a picked group of Du Mont engineers and technicians. Long before the end of the freeze they were assigned the job of finding the answers to u.h.f. installation problems. This article describes the antennas and transmission lines that gave the best results in their tests.

U.h.f. antennas fall into two categories: dual-band v.h.f.-u.h.f. types, and those designed to cover only the u.h.f. channels. The ideal antenna for home receivers would be an all-channel unit providing high gain and good directivity in both the v.h.f. and u.h.f. bands. As might be expected, no such antenna has yet been found; however, several types have been developed which have sufficient gain on both bands to meet most requirements.

These antennas are called the "double V," the "stacked V," and the "trombone." They are all based on the familiar V-antenna design shown in Fig. 1. A single-wire antenna more than one-half wavelength long has the directional pattern shown at *a*. When two such long wires are arranged in a V which encloses an angle equal to twice angle θ , the directivity pattern shown in Fig. 1-b is obtained. The V antenna is bidirectional, with maximum gain along the line bisecting the angle formed by the legs of the V. The angle which gives maximum gain and directivity is determined by the lengths of the legs and the operating frequency. When the V is used as a broad-band antenna, a compromise between the

*Technical Editor, *Teleset* Service Dept., Allen B. Du Mont Laboratories, Inc.

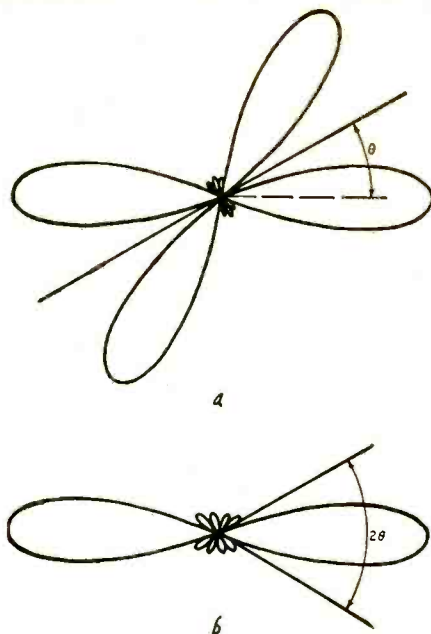


Fig. 1—(a) Directivity pattern of long-wire antenna. (b) The bidirectional directivity pattern when two long-wire antennas are combined to form a V.

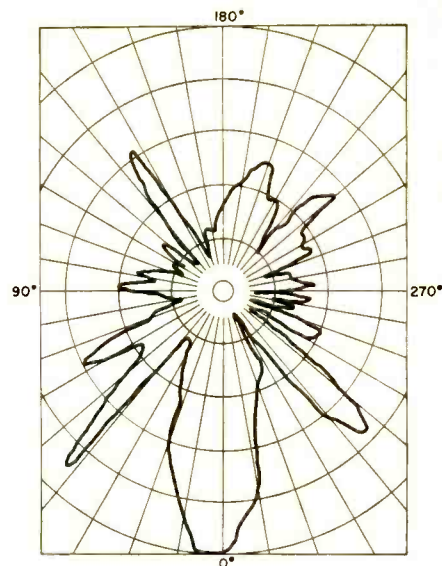


Fig. 3—Directivity pattern of double-V antenna. Note the strong forward lobe, and the relatively narrow minor lobes at intervals of approximately 45°.

angles giving maximum gain at either end of the range over which the antenna is used is selected.

The double-V antenna

Increased gain and directivity can be obtained by combining two V antennas to form an array, as shown in Fig. 2. Placing one V an *odd number of quarter-waves* behind the other, and exciting them 90 degrees out of phase, gives a unidirectional pattern with maximum sensitivity in the direction of the open ends of the V's. See Fig. 3. This configuration is known as the double V.

The double V is sturdy, light, and easy to assemble and mount. It has sufficient gain on both the u.h.f. and v.h.f.

bands to give good results in strong- and medium-signal television areas.

As mentioned previously, the gain and directivity of V antennas are determined to some extent by the angle between the legs. The antenna shown in Fig. 2 has provisions for varying the enclosed angle. Experiment showed that an angle of approximately 60 degrees gives the best results on both the v.h.f. and u.h.f. bands. Increasing the angle to 90 degrees gives better results on v.h.f., but the gain and directivity on u.h.f. channels suffers. Reducing the angle to 45 degrees has the opposite effect. It increases the u.h.f. gain at the expense of v.h.f. performance. The angle actually used is not too critical;

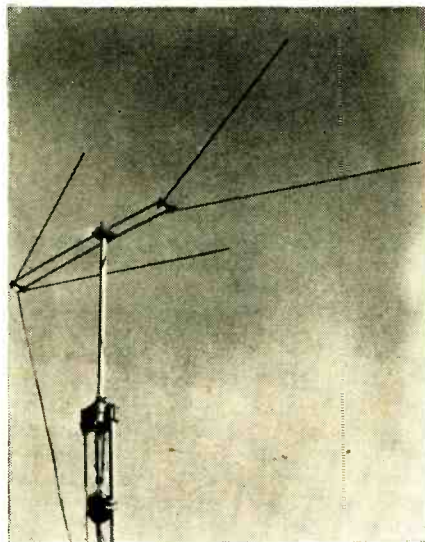


Fig. 2—A commercial double-V antenna.

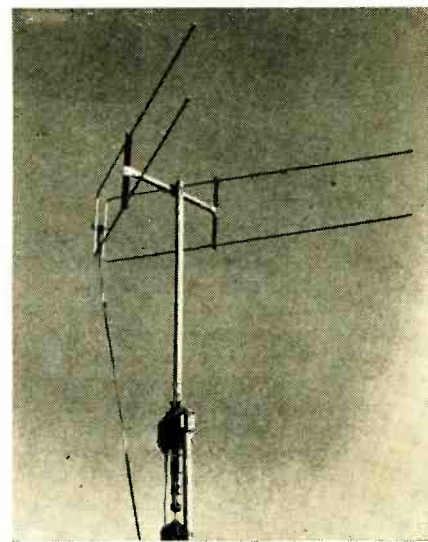


Fig. 4—A vertically-stacked V antenna.

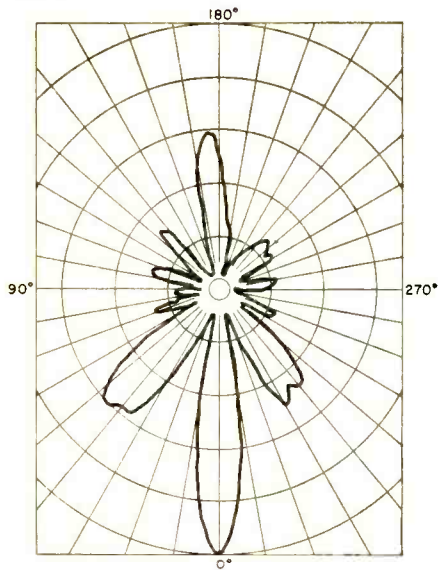


Fig. 5—Higher forward directivity obtained with vertically-stacked V antenna.

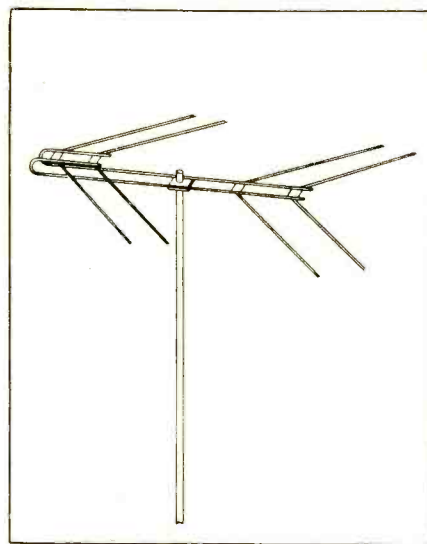


Fig. 6—Four-element "trombone" antenna. Both sets of elements may be adjusted to vary the terminating impedance, and the directivity of the antenna.

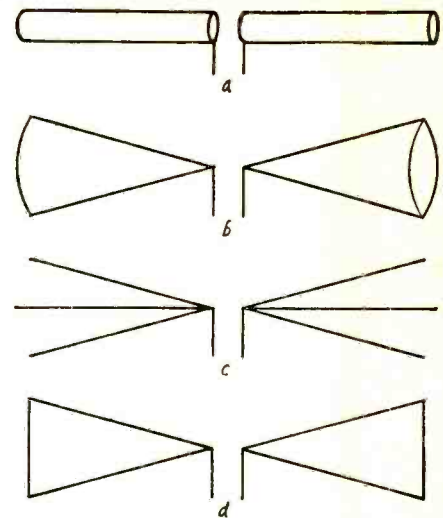


Fig. 7—(a) Increasing diameter of elements increases bandwidth. (b) Biconical dipole covers wide frequency range. (c) Fan-dipole form of conical antenna. (d) "Bow-tie" solid-sheet dipole for u.h.f.

but, wherever possible, it should be determined experimentally for conditions in the area in which the antenna is used. If the u.h.f. channels to be received are at the upper end of the band, an angle of less than 60 degrees will give best results. If only the lower end of the u.h.f. band is in use, the angle may be increased a few degrees.

By this time, you have undoubtedly recognized the double V as an antenna which has been used for v.h.f. reception with considerable success. The v.h.f.-u.h.f. version differs only with respect to the angle between the elements. If you have a double V and can change the angle, you can make yourself a good all-channel antenna.

The comparative voltage gains of the double V and the other antennas to be described are given in Table I. Note that the front-to-back ratio of the an-

tenna is approximately 1.5 to 1. This low front-to-back ratio can be a source of difficulty if ghosts are encountered. As indicated by the directivity pattern shown in Fig. 3, the double V has a number of secondary lobes. If a reflected signal is received on the axis of one of these secondary lobes, there is nothing to prevent it from reaching the receiver and producing a ghost.

There may be occasions when you can use these high-amplitude secondary lobes to advantage. When stations must be received from different directions, it is often possible to orient the antenna so that the weakest signal is picked up by the major lobe, and one or more strong signals by the minor lobes. The major lobe is wide enough to overcome slight differences in the angles between the antenna lobes and the received signals.

The stacked V

Another way to obtain additional gain from the V antenna is to stack one

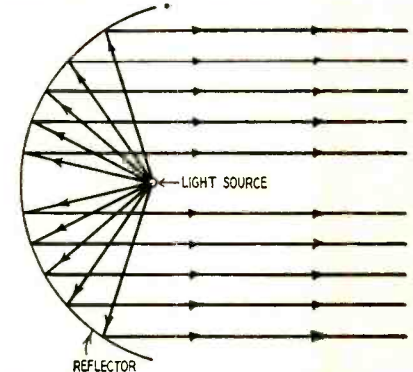


Fig. 10—Parabolic reflector collects light rays emitted by source and radiates them in unidirectional parallel rays.

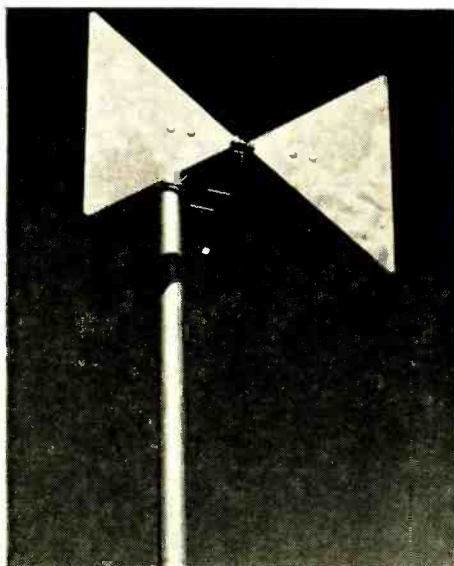


Fig. 8—A "bow-tie" in commercial form.

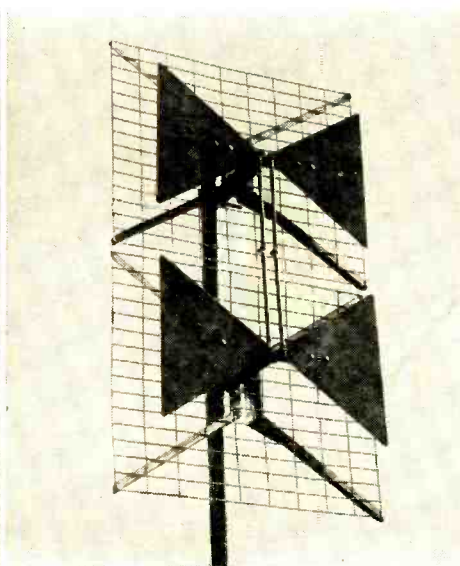


Fig. 9—Stacked "bow-ties" with reflector.

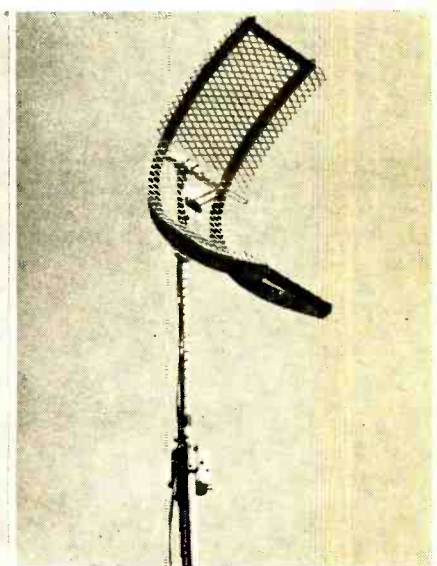


Fig. 11—Folded-dipole u.h.f. antenna with paraboloidal wire-screen reflector.

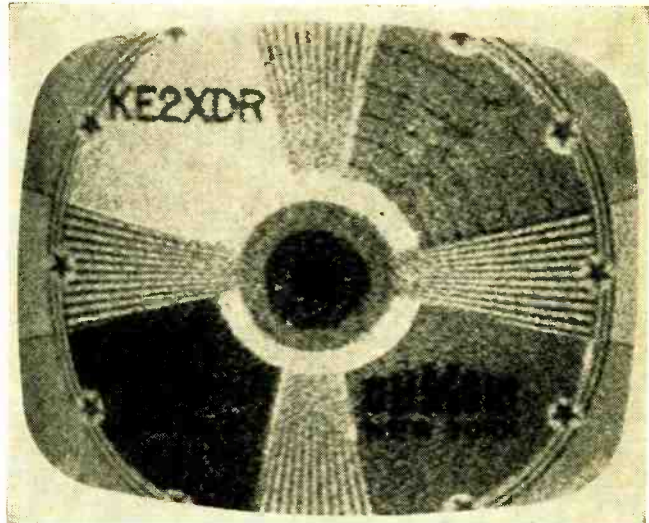
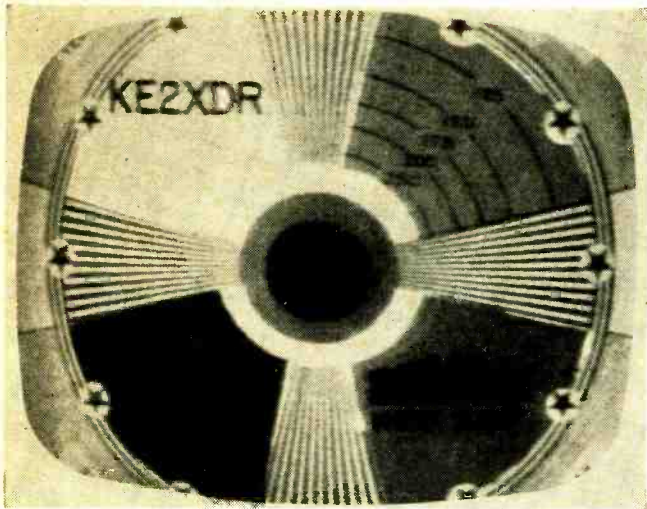


Fig. 12—(Left) U.h.f. signal received with a short length of low-loss u.h.f.

transmission line connected between antenna and receiver. (Right) Effect of

substituting a 200-foot lead-in of type RG-59/U coaxial cable on the picture.

V above another to form the antenna shown in Fig. 4. The stacked-V antenna provided the highest gain and front-to-back ratio of all the dual-band types tested. It is economical, light in weight, and easy to handle. Several commercial models will undoubtedly be available by the time this article is in print.

As indicated by the directivity pattern shown in Fig. 5, the stacked V has a narrower forward lobe than the double V, but also has the multiple minor lobes exhibited by all V antennas, a possible source of difficulty when ghosts are encountered.

A third type of V antenna, called the "trombone," is shown in Fig. 6. It consists of four driven-V antennas. The results obtained with this antenna are

Table I

Type	Gain	
	Front	Back
Double V	15	9.5
Stacked V	20	11.5
Trombone	12.5	8
Single bow-tie	6.5	5.5
Single bow-tie with reflector	8	2
Stacked bow-tie	11	10
Stacked bow-tie with reflector	21	3
Parabolic	12.5	4.5

roughly equivalent to those obtained with the double V, and there is little preference for one over the other. In fact, any of the V-type arrays described will do an excellent job wherever fairly strong signals are available and ghosts are not a problem.

U.h.f. antennas

Where the customer already has a v.h.f. antenna or where receiving conditions call for higher gain or better directivity, a separate u.h.f. antenna provides the answer.

Many types of straight u.h.f. antennas were tested, and two were found that met the requirements of all but very weak-signal locations. These are the bow-tie antenna and the parabolic antenna. Commercial versions of both types are now on the market.

An ordinary dipole made of thin wire

or tubing behaves like a high-Q resonant circuit. At frequencies slightly above and below its resonant frequency it becomes reactive, its efficiency and gain fall off sharply, and it performs rather poorly as an antenna. The resonant peak can be reduced by increasing the thickness of the conductors, as shown in Fig. 7-a. This lowers the Q of the dipole, providing more uniform response over a wide band of frequencies. Carrying this idea further the conductors can be constructed in cone form (Fig. 7-b), to cover a still greater frequency range. This is the true biconical antenna from which several of the types now in use are derived. The biconical suffers from the major disadvantage of being difficult to construct and mount.

The physical disadvantages of the biconical are overcome in the familiar fan dipole of Fig. 7-c, which is widely used in v.h.f. antennas. The fan antenna, however, does not possess the full bandwidth capabilities of the true biconical. Replacing the multiple conductors with flat metal triangles to form a bow-tie (Fig. 7-d), brings the performance closer to the true biconical.

Several versions of the bow-tie are available. A single version is shown in Fig. 8. Table I shows the comparative voltage gains of the single bow-tie, the stacked bow-tie, and the single and stacked bow-ties with reflectors. The stacked bow-tie with reflector, shown in Fig. 9, gave the best gain and front-to-back ratio of all the u.h.f. antennas tested.

The reflector used with the bow-tie is a flat screen referred to as a "bedspring" or "sheet." This reflector performs very much like a tuned parasitic reflector; however, it overcomes the critical spacing and length requirements of the tuned reflector and is much more efficient. For maximum efficiency the reflector must be somewhat wider than the bow-tie. The size and shape of the openings in the reflector are not critical, but their longest dimension must be kept shorter than 0.2 wavelength.

The parabolic antenna

At ultra-high frequencies radio waves exhibit many of the qualities of light rays. In a searchlight the light source is located at the focal point of a parabolic mirror, as shown in Fig. 10. The mirror reflects the light which strikes it from the source, forming a beam of parallel rays. The same principle is used in the u.h.f. antenna shown in Fig. 11, in which a folded dipole is mounted at the focal point of a parabolic-shaped metal reflector.

Radio waves striking the reflector are concentrated at the dipole. The reflector is actually a compromise between the flat bedspring type and a true parabola. It produces a very narrow vertical lobe, while the horizontal directivity is approximately equivalent to that obtained with a flat-surface reflector.

Although the parabolic antenna did not give quite as good results as the stacked bow-tie with reflector, it is an excellent antenna and will give satisfactory results in many areas.

Transmission lines

In the u.h.f. television band special attention must be given to the selection and installation of the transmission line. At ultra-high frequencies transmission-line losses are several times those which we have become accustomed to in the v.h.f. band.

Fig. 12 shows the effect the transmission line can have on u.h.f. reception. The same receiver and antenna were used to obtain both pictures. The pattern on the left was obtained with a short length of low-loss line between the antenna and receiver. The pattern on the right was obtained with 200 feet of RG-59/U connected between the antenna and receiver.

A comparison of the losses of several popular types of transmission line in the v.h.f. and u.h.f. bands is shown in Table II. The losses of each type of line are several times as great in the u.h.f. band (700 mc), as compared to the v.h.f. band.

The figures in the table indicate that

moisture has a drastic effect on 300-ohm ribbon. Its losses when wet are so great that the use of 300-ohm ribbon is not advisable if more than 25 feet of line is required.

The effects of moisture are overcome to a great extent in tubular 300-ohm line. In this line the conductors are attached to the outside of a polythene tube. The construction provides a longer leakage path and keeps moisture out of the space between the conductors. Because of its economy, this type of trans-

Table II

Type	Loss in Db per 100 feet			
	100 mc		700 mc	
	Dry	Wet	Dry	Wet
300-ohm ribbon	1.2	7.3	3.6	26.5
300-ohm tubular	1.2	2.5	3.6	8.2
450-ohm air-spaced	0.35	0.35	0.9	0.9
RG-59/U coaxial	3.7	3.7	11.7	11.7
RG-11/U coaxial	1.9	1.9	6.2	6.2

mission line will undoubtedly be highly popular for u.h.f. installations.

Coaxial lines such as RG-59/U and RG-11/U do not suffer from the effects of moisture; but the losses of RG-59/U prohibit its use in weak-signal areas if more than 50 feet of line are required.

Installation effects

Due to absorption from the transmission line can be severe when lines of either the ribbon or tubular types are used. With a 500-ohm signal at the antenna, an incoming 100 feet of 300-ohm ribbon gives an excellent picture when the transmission line was entirely clear of objects. When the line was placed on the roof of the building the signal gradually disappeared. 300-ohm ribbon suffers from absorption to the same extent as 300-ohm ribbon. Both should be kept away from all other metal objects, especially those containing metal, at least 6 inches from walls, floors, and other surfaces; and avoid running the line over pipes, drains, wires, or other structures.

A transmission line must be installed at a reasonable distance inside a building. It is not possible to keep a transmission line close to the antenna for use in u.h.f. installations.

For use in u.h.f. installations, 300-ohm air-spaced line has the lowest losses of any types available. It is affected by moisture, and absorption effects must be kept in mind. It must be kept away from other metal objects. It is ideal for use in weak-signal locations. It must be run, but it is not ideal for installations where long runs are required.

The requirements of a transmission line can be summed up as follows: 1. Signals are available in weak-signal areas. 2. Type of line will

2. When the line is 50 feet or longer, either 300-ohm tubular or coaxial line will usually give best results.

3. If the line is more than 50 feet long and cannot be kept clear of other objects, use coaxial line. If the signals are strong, or if the line is less than 100 feet long, RG-59/U is suitable. With weak signals or longer lines, RG-11/U will give better results.

4. In a weak signal area when a very long line is required, 450-ohm air-spaced line should be considered.

When separate v.h.f. and u.h.f. antennas are used, it is often desirable to use a single transmission line. Several commercial crossover filters are available which permit this to be done. The filter is mounted near the antennas and connected to them by short lines. A single transmission line carries the output of the filter to the receiver.

Many of the u.h.f. converters on the market are intended for use with separate v.h.f. and u.h.f. transmission lines. If the transmission line is connected directly to the v.h.f. and u.h.f. terminals of the converter, a proper match will not be obtained. To provide a correct match, a network is required. Commercial networks are available for this purpose. Some of these networks may be used at either the antenna end of the line to permit the use of a single line as described above, or at the receiver end to match a single line to separate v.h.f. and u.h.f. input terminals.

Installation problems

You may have noticed when installing v.h.f. antennas that raising an antenna a few feet does not always produce a stronger signal. This effect, called "height cancellation," is much more pronounced in the u.h.f. band. Due to phasing differences between the direct signal and the ground-reflected signal, cancellation and addition occur at various heights above ground. As a result, layers of minimum and maximum signal level are created. When installing u.h.f. antennas, always raise and lower the antenna a few feet to probe for the height which gives maximum signal.

At ultra-high frequencies, the shielding effects of hills, buildings, and other obstructions produces shadow areas in which very little signal is available. Several such areas have been found around Portland, Oregon. In many cases, it was possible to get fair reception with high-gain antennas; in others, nothing could be done.

Most new u.h.f. stations will probably go on the air with effective radiated powers of approximately 20 kw. In most cases, this will give dependable reception within 20 to 30 miles from the transmitter. Future power increases will raise this distance.

Since u.h.f. signals are reflected more efficiently, ghosts are much more common than on v.h.f. This is partially compensated for by the availability of highly directional antennas. Multipath pickup also results in signal cancellation. Moving the antenna a few feet will often greatly increase or decrease the signal pickup.



APRIL marks a seasonal turning point for the TV dx enthusiast. After a period of several months when TV dx has been seen seldom, if at all, he can now look forward to better times for at least the next three months.

There will not be many dx openings in April, and the observer in the northern states may find little evidence of it at all. Because the dx cycle is associated in a general way with climate, the viewer in the deep south is likely to get the first break in both tropospheric and ionospheric dx.

The last major auroral disturbances of the spring cycle occur in April, and though the magnitude of auroral activity has been generally low in recent months there is always a chance of a marked change in this respect. Auroral effects on TV reception are probably the least understood of any of the principal factors that may account for TV dx. Observers interested in learning more of this will find useful information in the January, 1953, issue of IRE Proceedings, wherein some Cornell University photographs of TV pictures made during an aurora are reproduced.

Ever since the appearance of the summary of 1952 TV dx observations in the January RADIO-ELECTRONICS, reports have been coming in from readers who recorded TV dx reception during the past year, but did not send it in at once. While such reports are valuable for long-term study, they do not get proper acknowledgment in the pages of this magazine, and of course they do not figure in the compilation of the published report for the year.

To be of greatest value, TV dx observations should be sent in soon after the incidents reported. A monthly log is a convenient way to handle it, and useful to us. The time, date, and channel are important, and information on the equipment used is helpful. END

DEDICATED TO ALL TV KIBITZERS AND DIAL-TWISTERS

By Caroline J. Beckner

I think that I shall never see
More cause for strong profanity
Than when I twist the TV dial
And others scream: "Your taste is vile!"

They raise a loud, insistent clamor
For quiz shows or for melodramer.
Or movies old—half-hid in snow—
That give me chills and vertigo.
They take turns at the little knobs
Nor hearken to my tears and sobs.
Radio's made for wrecks like me,
Red's all that I see on TV.

Another installation is not affected by moisture, but it suffers from absorption effects. It is ideal for use in weak-signal areas. It must be run, but it is not ideal for installations where long runs are required. The requirements of a transmission line can be summed up as follows: 1. Signals are available in weak-signal areas. 2. Type of line will

value A
r than
ICS

WHAT ABOUT THE ION TRAP?




(Above)—The author with an ion-trap magnet (below)—This inexpensive strength meter can be used to check relative strength of magnets. Deflection of needle indicates field of the near-

By ALVIN B. KAUFMAN

THE service technician takes the ion-trap magnet and the new PM centering assemblies casually, as a rule. However, measurement of their field strength is an important factor that should not be overlooked when certain types of service trouble are encountered.

Either of these units may be single- or dual-magnet assemblies. The better manufacturers of ion-trap and centering magnets use Alnico V. These magnets have a silvery color, while other materials do not. This choice of material and the importance to the service technician is indicated because both ion-trap and centering magnets operate pretty much under open-circuit conditions and thus are subject to demagnetization due to heat, handling, or vibration. In addition, the centering magnet is close to the deflection yoke with its heavy demagnetizing effect, which may seriously affect its strength.

Appreciable reduction in the field strength of the centering magnet assembly may reduce its ability to center the beam or raster to the point where it has to be discarded. A simple check of its field strength will indicate whether the trouble is in this component or if a breakdown has occurred in the deflection-yoke circuits. Replacement by another unit, off the shelf, may not remedy the trouble if this new unit should be of a type employing magnetic com-

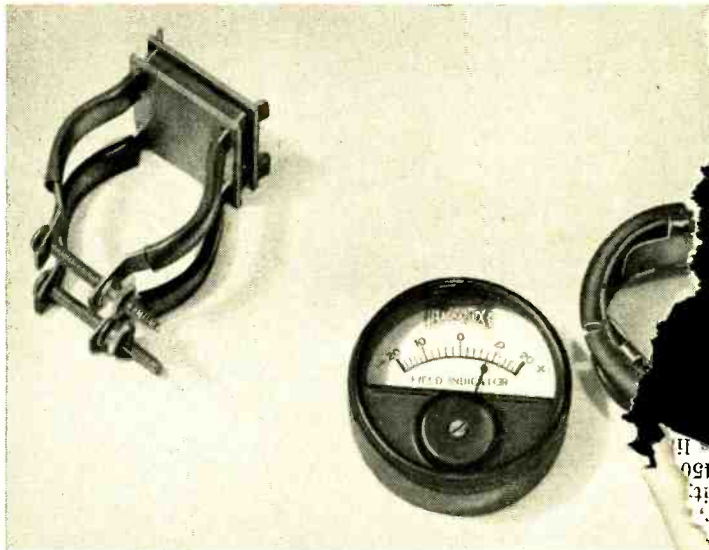

ponents which also might have a weak field (from one of the causes previously indicated). The centering magnet produces a field which moves the electron beam before it reaches the yoke.

The ion-trap magnet presents a different problem. Normally where field strength is correct it is possible to bend the electron beam through the proper course until it again hits the gun structure. Cases of ion trap magnets being overly strong are just about an impossibility, as the trap can be positioned

far back if necessary. A common trouble is a weak magnetic field. Where a trap magnet is weak there is lack of brilliance, neck shadow, and centering, parallel to pipes, wherever possible, parallel to walls, roofs, and ceilings. Space the tubes in the line in the rear, bridging, and it is a considerable problem. Where a trap magnet is weak there is lack of brilliance, neck shadow, and centering, parallel to pipes, wherever possible, parallel to walls, roofs, and ceilings. Space the tubes in the line in the rear, bridging, and it is a considerable problem. Where a trap magnet is weak there is lack of brilliance, neck shadow, and centering, parallel to pipes, wherever possible, parallel to walls, roofs, and ceilings. Space the tubes in the line in the rear, bridging, and it is a considerable problem.

RADIO-ELECTRONICS

Absorption Losses


that specified distorts the focused spot, changes the focusing voltage of the tube, and also requires a shift in the position of the magnet on the neck of the tube."—Editor)

In the electrostatically deflected cathode-ray tube the ions and electrons produced by the cathode of the tube are both deflected equally and the screen is thus bombarded evenly and not burnt. In the electromagnetically deflected tube, due to difference in mass, only the electrons are deflected appreciably, and the ions—hitting the screen at one point in a steady stream—would produce a burnt spot. This was remedied in modern C-R tubes by directing the ions and electrons against some portion of the electron gun, as in the bent gun design. The ion-trap magnet straightens out the electron stream and allows it to go down the tube to the screen. This magnet does *not* affect the ions, which continue in a straight line into the tube structure where they do no harm. As Fig. 1 shows, the magnet is adjusted until the electron beam is just straightened out. Improper adjustment or weak field strength will allow the beam to hit the gun structure (aperture), limiting screen brilliance and producing secondary ion burns due to disintegration of the structure. A discussion of these ion burns was presented very thoroughly in the February, 1952, issue¹.

At this time it is too early to evaluate whether much trouble will be encountered with centering units, for electrostatic and electromagnetic focusing cathode-ray tubes. In checking with a large service organization and numerous dealers not many bad ion-trap magnets have been turned up. But as they were normally unexpected these cases led to many hours of needless trouble shooting before the ion-trap magnets were finally identified as the elements responsible for the difficulties.

A magnet checker

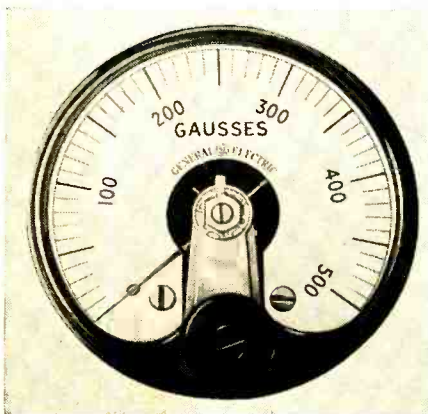A simple tester to check the field strength of these magnets may pay for itself even if it just clears the atmosphere by showing that the magnet is not the cause of raster misalignment, loss of brilliance, or ion burns on the picture-tube screen.



High-grade General Electric Gaussmeter. This instrument is portable and indicates field strength with 5% accuracy.

The magnetic field strengths employed in these assemblies run between 5 and 40 gauss. Therefore the gauss meter should preferably cover this range as closely as possible. Numerous commercial meters are available, among which General Electric's field meter is particularly adaptable and inexpensive. These field type portable indicators have an accuracy of $\pm 5\%$ and are supplied with standard reference magnets. GE bulletin GEC-777 describes all available models including one of 0-100 gauss range (Cat. No. 416X29) which sells for \$72.00. Besides commercial units, home-built designs have been featured in several publications^{2,3}. However, for the experimenter or technician who does not wish to either build such a gauss meter, or wants to limit his expenditure to a more modest sum, another meter is available.

Magnaflux Corporation sells a pocket field indicator model No. 2480 for the small sum of \$2.60. It is intended for use with the Magnaflux inspection system to allow a check of tested structures or parts to insure that no residual magnetic field has been left after test. As such it was not intended to be a highly accurate instrument, and is not calibrated in gauss. It simply has a scale of plus or minus 20 which corresponds somewhat to the field strength

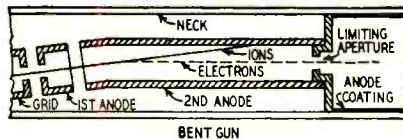


Fig. 1—Electron and ion paths through gun at correct ion-trap-magnet setting.

in gauss $\pm 50\%$. Individual units vary by as much as 25% among themselves.

However, this is of little consequence in TV work, as will be indicated shortly.

The types and forms of ion-trap and centering magnet assemblies vary widely, as does the field strength of the magnets. There are ion-trap units with single bar magnets (mounted either across or parallel to the tube neck), double ring types, bar and ring, and double bar, to mention some of the most common kinds.

The field strengths of these magnets vary widely among the different types. The two-magnet assembly delivers a strong and a weak magnetic field, whether of bar or ring construction. The apparent value of the field strength will also vary with the point at which it is measured. This means that regardless of the type of field strength indicator used, some measurement configuration must be used for each type of assembly if comparative strengths of assemblies are to be measured.

Therefore some position and distance between the magnet assembly and indicator must be selected and noted on a chart along with the value of the flux meter reading for each type of assembly. Use a *known good unit* for the check. From then on it will only take a moment to check an unknown unit of the same type. Absolute values cannot be given in the article, because of the variation in flux meters, and the subject components. A variation of 50% from the selected standard, should allow good units to pass; all other units being eyed with suspicion. END

References:

1. *Ion Burns* RADIO-ELECTRONICS Feb. 1952
2. *Magnetic Phenomenon* RADIO-ELECTRONICS Nov. 1951
3. *Magnetic Flux Comparator* Radio and Television News Engr. Edition Mar. 50


RELAY RHOMBIC BRINGS TV TO SHADOW AREA

A SIMPLE but sizable twin-rhombic antenna system developed at the University of Denver picks up high-strength TV signals on a mountain top and reradiates them to receivers in a signalless canyon far below.

The pickup rhombic on top of the mountain is beamed with scientific accuracy at the transmitter 55 miles away. An open-wire transmission line several hundred feet long links it to the reradiating antenna. This one is aimed with equal precision at the receiver site more than a mile distant.

The final antenna at the receiver may be any standard type, but in this installation a third rhombic was used to provide the ultimate in sensitivity.

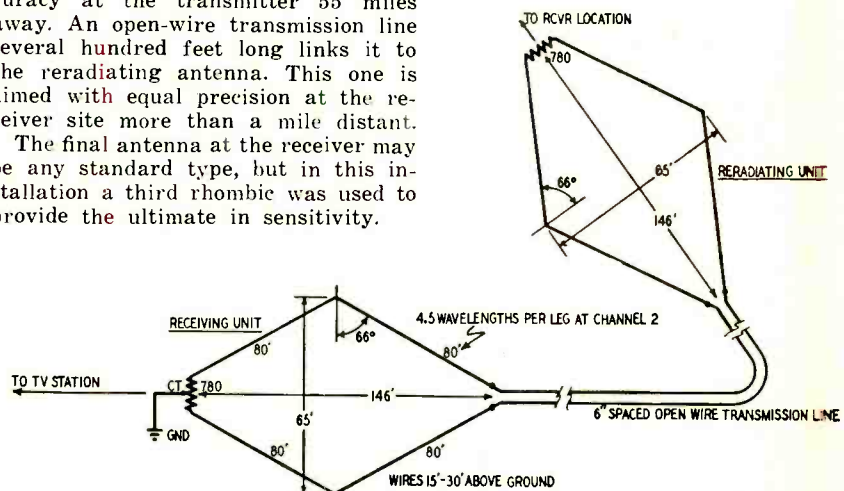The diagram shows the dimensions of the all-channel rhombics used in the Colorado installation. Increasing the included angle from 66° to 70° improved the response on channels 7-13. END



Design Data

Part II—How to compensate for loss of gain at low frequencies

ON VIDEO AMPLIFIERS

By ALLAN G. SORENSEN

IN AN R-C coupled amplifier stage (Fig. 1) the drop in low-frequency response below F_1 is a result of the following:

1. The reactance of coupling capacitor C rises to very high values at low frequencies, and delivers less signal voltage to the grid of the next tube.
2. The reactance of the cathode-by-pass capacitor rises and permits signal-voltage variations to vary the grid-bias voltage.
3. The reactance of the screen-by-pass capacitor rises and permits signal-voltage variations to vary the screen voltage.

4. The internal impedance of the power supply rises and creates a coupling path between the video-amplifier stages via the B plus line.

As a result of these factors not only will the response fall off, but there will be a relatively large phase shift, and oscillation may also occur.

Any appreciable phase distortion in a television receiver will result in a very poor picture. At low frequencies the phase angle will be leading, and only a few degrees shift are required to displace the low-frequency elements of the picture noticeably to the right. The result is the same as a ghost. There will also be smearing of the picture.

Considering C first: C and the grid resistor R_g act as a voltage divider. As shown by the equation for capacitive reactance

$$X_c = \frac{159,000}{fC}$$

(where f is the frequency in cycles per second and C is the capacitance in μf), the reactance of this capacitor will rise from almost zero at very high frequencies to several hundred thousand ohms at very low frequencies. This results in a substantial reduction of the low-frequency voltage fed to the following tube. When the reactance X_c equals the resistance of R_g , the signal voltage on the grid will be down 3 db, or 29.3%. For this reason the grid resistor is made as large as possible.

Even more important than the loss in gain is the shift in signal phase at low frequencies. The amplifier must be capable of flat response down to the lowest frequency that it will be expected to pass. Even a small drop in gain may produce excessive phase shift.

As an example, where the amplification drops only to 99.62% of the mid-frequency gain, the phase will shift by 5° . From this it can be seen that a flat response is very important.

The answer to the first problem would be to make both the coupling capacitor and the grid resistor large in value, but there are practical limitations to this approach. If the capacitor is made too large (physically), the increased shunt capacitance to ground will reduce the high-frequency response. (See Part I, in the March, 1953, RADIO-ELECTRONICS.) C should not be larger than 0.1 or 0.25 μf . The size of the grid resistor is limited by the characteristics of the tube. For example, 1 megohm is the maximum resistance that may be used in the grid circuit of a 6AG7.

As a result of very small traces of gas in the tube, positive ions will collect on the grid. These ions produce a positive grid current of a few microamperes. If the grid resistor is very large, even a minute gas current will develop a sizeable voltage across the resistor. This voltage will be positive at the grid end, thereby upsetting the normal grid-bias voltage. Since this ion current has a constantly changing value, it will generate a small amount of noise.

For flat response down to very low frequencies the cathode bypass capacitor must be very large. Values as large as 1,000 μf are often used. If its reactance increases appreciably at low frequencies, some of the signal voltage at the cathode will be fed back, in opposite phase, to the grid. This is degenerative feedback.

When the signal voltage at the grid rises, the plate current increases. This causes a larger voltage drop across the cathode resistor R_k , and consequently, more negative bias on the grid. When the grid bias is made more negative, the plate current is decreased, reducing the gain of the tube.

The problem of degenerative feedback can be handled in several ways. In most applications it is easier, as well as cheaper, to leave the cathode un-bypassed. This will give equal degeneration at all frequencies. The over-all stage gain will be reduced but the cathode will be eliminated as a source of

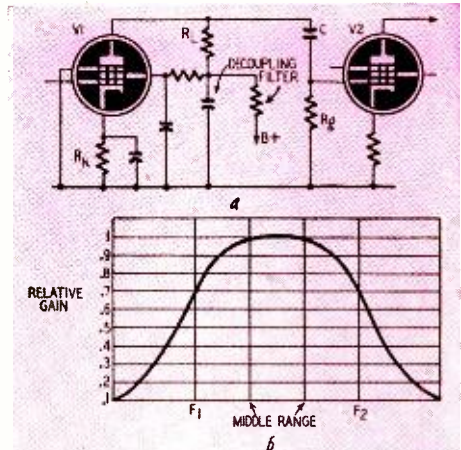


Fig. 1—(a) Basic circuit of two-stage resistance-coupled amplifier. (b) Generalized frequency-response curve of the amplifier. F_1 and F_2 are points where the frequency response falls noticeably.

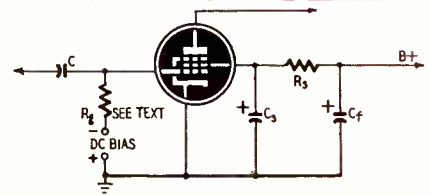


Fig. 2—Grounding the amplifier cathode and supplying grid bias from a fixed d.c. source eliminates cathode degeneration.

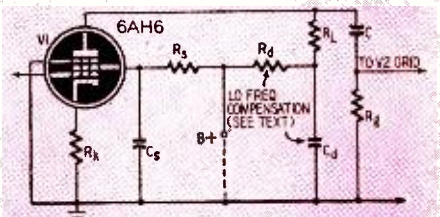


Fig. 3—Part of a two-stage video amplifier with circuit elements affecting the response at low frequencies.

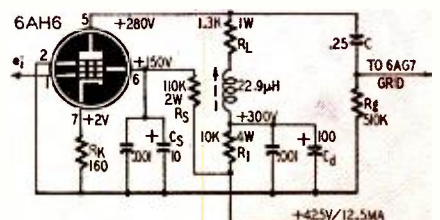


Fig. 4—Video amplifier compensated for flat response from 5 cycles to 4 mc.

moisture has a drastic effect on 300-ohm ribbon. Its losses when wet are so great that the use of 300-ohm ribbon is not advisable if more than 25 feet of line is required.

The effects of moisture are overcome to a great extent in tubular 300-ohm line. In this line the conductors are attached to the outside of a polythene tube. The construction provides a longer leakage path and keeps moisture out of the space between the conductors. Because of its economy, this type of trans-

Table II

Type	Loss in Db per 100 feet			
	100 mc		700 mc	
	Dry	Wet	Dry	Wet
300-ohm ribbon	1.2	7.3	3.6	26.5
300-ohm tubular	1.2	2.5	3.6	8.2
450-ohm air-spaced	0.35	0.35	0.9	0.9
RG-59/U coaxial	3.7	3.7	11.7	11.7
RG-11/U coaxial	1.9	1.9	6.2	6.2

mission line will undoubtedly be highly popular for u.h.f. installations.

Coaxial lines such as RG-59/U and RG-11/U do not suffer from the effects of moisture; but the losses of RG-59/U prohibit its use in weak-signal areas if more than 50 feet of line are required.

Absorption effects

Losses due to absorption from the transmission line can be severe when open-wire lines of either the ribbon or tubular types are used. With a 500-microvolt signal at the antenna, an installation using 100 feet of 300-ohm ribbon produced an excellent picture when the transmission line was entirely clear of surrounding objects. When the line was laid on the roof of the building the picture practically disappeared. 300-ohm tubular suffers from absorption to the same extent as 300-ohm ribbon. Both types must be kept away from all other objects, especially those containing metal. Space the line at least 6 inches from all walls, roofs, and other surfaces; and wherever possible avoid running the line parallel to pipes, drains, wires, or other metal parts of a structure.

Where a transmission line must be run a considerable distance inside a building, and it is not possible to keep the line in the clear, use coaxial line.

Another possibility for use in u.h.f. installations is 450-ohm air-spaced, open-wire line. This line has the lowest losses of the various types available. It is not affected appreciably by moisture, but it suffers from absorption effects and must be supported away from other objects. It is ideal for weak-signal locations where long lines must be run, but it is rather difficult to handle. It is not generally needed for installations requiring less than 200 feet of line.

Other types of u.h.f. transmission line are now available, but were not checked in these tests.

The transmission-line requirements of u.h.f. installations can be summed up as follows:

1. If very strong signals are available and less than 25 or 30 feet of line are required, almost any type of line will prove satisfactory.

2. When the line is 50 feet or longer, either 300-ohm tubular or coaxial line will usually give best results.

3. If the line is more than 50 feet long and cannot be kept clear of other objects, use coaxial line. If the signals are strong, or if the line is less than 100 feet long, RG-59/U is suitable. With weak signals or longer lines, RG-11/U will give better results.

4. In a weak signal area when a very long line is required, 450-ohm air-spaced line should be considered.

When separate v.h.f. and u.h.f. antennas are used, it is often desirable to use a single transmission line. Several commercial crossover filters are available which permit this to be done. The filter is mounted near the antennas and connected to them by short lines. A single transmission line carries the output of the filter to the receiver.

Many of the u.h.f. converters on the market are intended for use with separate v.h.f. and u.h.f. transmission lines. If the transmission line is connected directly to the v.h.f. and u.h.f. terminals of the converter, a proper match will not be obtained. To provide a correct match, a network is required. Commercial networks are available for this purpose. Some of these networks may be used at either the antenna end of the line to permit the use of a single line as described above, or at the receiver end to match a single line to separate v.h.f. and u.h.f. input terminals.

Installation problems

You may have noticed when installing v.h.f. antennas that raising an antenna a few feet does not always produce a stronger signal. This effect, called "height cancellation," is much more pronounced in the u.h.f. band. Due to phasing differences between the direct signal and the ground-reflected signal, cancellation and addition occur at various heights above ground. As a result, layers of minimum and maximum signal level are created. When installing u.h.f. antennas, always raise and lower the antenna a few feet to probe for the height which gives maximum signal.

At ultra-high frequencies, the shielding effects of hills, buildings, and other obstructions produces shadow areas in which very little signal is available. Several such areas have been found around Portland, Oregon. In many cases, it was possible to get fair reception with high-gain antennas; in others, nothing could be done.

Most new u.h.f. stations will probably go on the air with effective radiated powers of approximately 20 kw. In most cases, this will give dependable reception within 20 to 30 miles from the transmitter. Future power increases will raise this distance.

Since u.h.f. signals are reflected more efficiently, ghosts are much more common than on v.h.f. This is partially compensated for by the availability of highly directional antennas. Multipath pickup also results in signal cancellation. Moving the antenna a few feet will often greatly increase or decrease the signal pickup. **END**



APRIL marks a seasonal turning point for the TV dx enthusiast. After a period of several months when TV dx has been seen seldom, if at all, he can now look forward to better times for at least the next three months.

There will not be many dx openings in April, and the observer in the northern states may find little evidence of it at all. Because the dx cycle is associated in a general way with climate, the viewer in the deep south is likely to get the first break in both tropospheric and ionospheric dx.

The last major auroral disturbances of the spring cycle occur in April, and though the magnitude of auroral activity has been generally low in recent months there is always a chance of a marked change in this respect. Auroral effects on TV reception are probably the least understood of any of the principal factors that may account for TV dx. Observers interested in learning more of this will find useful information in the January, 1953, issue of IRE Proceedings, wherein some Cornell University photographs of TV pictures made during an aurora are reproduced.

Ever since the appearance of the summary of 1952 TV dx observations in the January RADIO-ELECTRONICS, reports have been coming in from readers who recorded TV dx reception during the past year, but did not send it in at once. While such reports are valuable for long-term study, they do not get proper acknowledgment in the pages of this magazine, and of course they do not figure in the compilation of the published report for the year.

To be of greatest value, TV dx observations should be sent in soon after the incidents reported. A monthly log is a convenient way to handle it, and useful to us. The time, date, and channel are important, and information on the equipment used is helpful. **END**


DEDICATED TO ALL TV KIBITZERS AND DIAL-TWISTERS

By Caroline J. Beckner

I think that I shall never see
More cause for strong profanity
Than when I twist the TV dial
And others scream: "Your taste is vile!"

They raise a loud, insistent clamor
For quiz shows or for melodramers.
Or movies old—half-hid in snow—
That give me chills and vertigo.
They take turns at the little knobs
Nor hearken to my tears and sobs.
Radio's made for wrecks like me,
Red's all that I see on TV.

WHAT ABOUT THE ION TRAP?

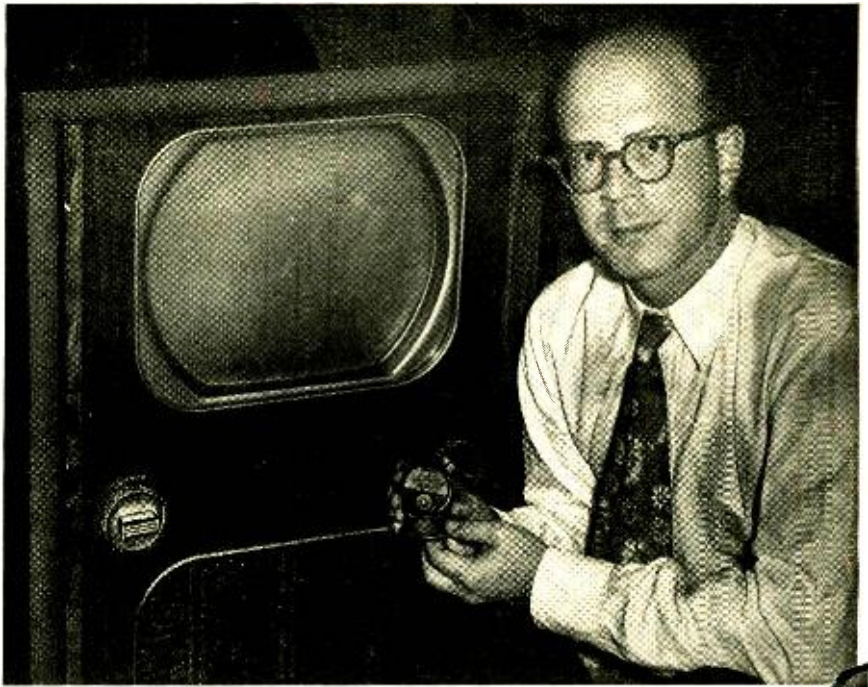


(Above)—The author checks an ion-trap magnet. (Below)—This inexpensive field-strength meter can be used to check relative strength of magnets. Deflection is due to field of the nearby ion trap.

By ALVIN B. KAUFMAN

THE service technician takes the ion-trap magnet and the new PM centering assemblies casually, as a rule. However, measurement of their field strength is an important factor that should not be overlooked when certain types of service trouble are encountered.

Either of these units may be single- or dual-magnet assemblies. The better manufacturers of ion-trap and centering magnets use Alnico V. These magnets have a silvery color, while other materials do not. This choice of material and the importance to the service technician is indicated because both ion-trap and centering magnets operate pretty much under open-circuit conditions and thus are subject to demagnetization due to heat, handling, or vibration. In addition, the centering magnet is close to the deflection yoke with its heavy demagnetizing effect, which may seriously affect its strength.

Appreciable reduction in the field strength of the centering magnet assembly may reduce its ability to center the beam or raster to the point where it has to be discarded. A simple check of its field strength will indicate whether the trouble is in this component or if a breakdown has occurred in the deflection-yoke circuits. Replacement by another unit, off the shelf, may not remedy the trouble if this new unit should be of a type employing magnetic com-

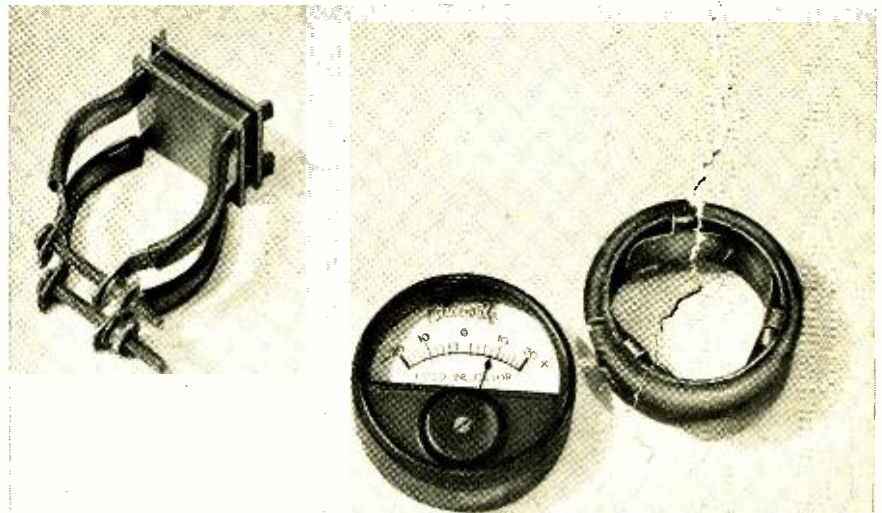

ponents which also might have a weak field (from one of the causes previously indicated). The centering magnet produces a field which moves the electron beam before it reaches the yoke.

The ion-trap magnet presents a different problem. Normally where field strength is correct it is possible to bend the electron beam through the proper course until it again hits the gun structure. Cases of ion trap magnets being overly strong are just about an impossibility, as the trap can be positioned

far back if necessary. The usual trouble is a weak magnet, in which case there is lack of brilliance, difficult centering, neck shadow, and danger of the screen developing ion burns.

(According to "Design and Adjustment of Kinescope Centering Magnets and Ion-Trap Magnets" [RCA *Electron Tubes Application Note No. AN-152*] "For a kinescope utilizing electrostatic focus, it is important that the field strength be close to the given value. A field strength appreciably higher than

Design Data

ON VIDEO AMPLIFIERS

Part II—How to compensate for loss of gain at low frequencies

By ALLAN G. SORENSEN

IN AN R-C coupled amplifier stage (Fig. 1) the drop in low-frequency response below F_1 is a result of the following:

1. The reactance of coupling capacitor C rises to very high values at low frequencies, and delivers less signal voltage to the grid of the next tube.
2. The reactance of the cathode-by-pass capacitor rises and permits signal-voltage variations to vary the grid-bias voltage.
3. The reactance of the screen-by-pass capacitor rises and permits signal-voltage variations to vary the screen voltage.

4. The internal impedance of the power supply rises and creates a coupling path between the video-amplifier stages via the B plus line.

As a result of these factors not only will the response fall off, but there will be a relatively large phase shift, and oscillation may also occur.

Any appreciable phase distortion in a television receiver will result in a very poor picture. At low frequencies the phase angle will be leading, and only a few degrees shift are required to displace the low-frequency elements of the picture noticeably to the right. The result is the same as a ghost. There will also be smearing of the picture.

Considering C first: C and the grid resistor R_g act as a voltage divider. As shown by the equation for capacitive reactance

$$X_c = \frac{159,000}{fC}$$

(where f is the frequency in cycles per second and C is the capacitance in μf), the reactance of this capacitor will rise from almost zero at very high frequencies to several hundred thousand ohms at very low frequencies. This results in a substantial reduction of the low-frequency voltage fed to the following tube. When the reactance X_c equals the resistance of R_g , the signal voltage on the grid will be down 3 db, or 29.3%. For this reason the grid resistor is made as large as possible.

Even more important than the loss in gain is the shift in signal phase at low frequencies. The amplifier must be capable of flat response down to the lowest frequency that it will be expected to pass. Even a small drop in gain may produce excessive phase shift.

As an example, where the amplification drops only to 99.62% of the mid-frequency gain, the phase will shift by 5° . From this it can be seen that a flat response is very important.

The answer to the first problem would be to make both the coupling capacitor and the grid resistor large in value, but there are practical limitations to this approach. If the capacitor is made too large (physically), the increased shunt capacitance to ground will reduce the high-frequency response. (See Part I, in the March, 1953, RADIO-ELECTRONICS.) C should not be larger than 0.1 or 0.25 μf . The size of the grid resistor is limited by the characteristics of the tube. For example, 1 megohm is the maximum resistance that may be used in the grid circuit of a 6AG7.

As a result of very small traces of gas in the tube, positive ions will collect on the grid. These ions produce a positive grid current of a few microamperes. If the grid resistor is very large, even a minute gas current will develop a sizeable voltage across the resistor. This voltage will be positive at the grid end, thereby upsetting the normal grid-bias voltage. Since this ion current has a constantly changing value, it will generate a small amount of noise.

For flat response down to very low frequencies the cathode bypass capacitor must be very large. Values as large as 1,000 μf are often used. If its reactance increases appreciably at low frequencies, some of the signal voltage at the cathode will be fed back, in opposite phase, to the grid. This is degenerative feedback.

When the signal voltage at the grid rises, the plate current increases. This causes a larger voltage drop across the cathode resistor R_k , and consequently, more negative bias on the grid. When the grid bias is made more negative, the plate current is decreased, reducing the gain of the tube.

The problem of degenerative feedback can be handled in several ways. In most applications it is easier, as well as cheaper, to leave the cathode un-bypassed. This will give equal degeneration at all frequencies. The over-all stage gain will be reduced but the cathode will be eliminated as a source of

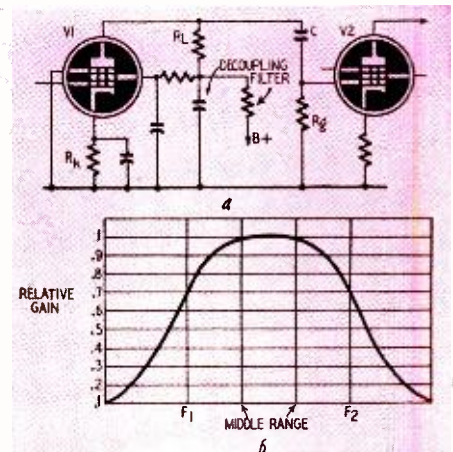


Fig. 1—(a) Basic circuit of two-stage resistance-coupled amplifier. (b) Generalized frequency-response curve of the amplifier. F_1 and F_2 are points where the frequency response falls noticeably.

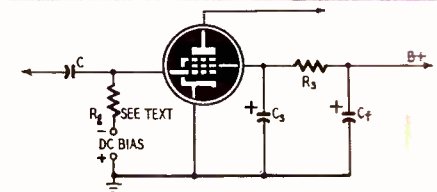


Fig. 2—Grounding the amplifier cathode and supplying grid bias from a fixed d.c. source eliminates cathode degeneration.

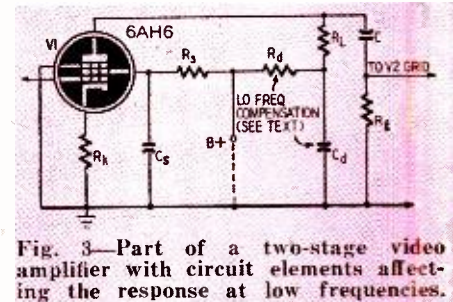


Fig. 3—Part of a two-stage video amplifier with circuit elements affecting the response at low frequencies.

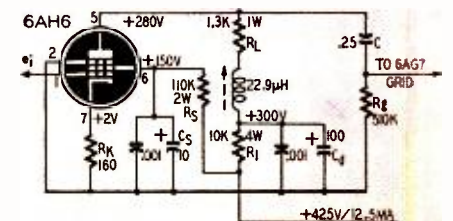


Fig. 4—Video amplifier compensated for flat response from 5 cycles to 4 mc.


that specified distorts the focused spot, changes the focusing voltage of the tube, and also requires a shift in the position of the magnet on the neck of the tube."—Editor)

In the electrostatically deflected cathode-ray tube the ions and electrons produced by the cathode of the tube are both deflected equally and the screen is thus bombarded evenly and not burnt. In the electromagnetically deflected tube, due to difference in mass, only the electrons are deflected appreciably, and the ions—hitting the screen at one point in a steady stream—would produce a burnt spot. This was remedied in modern C-R tubes by directing the ions and electrons against some portion of the electron gun, as in the bent gun design. The ion-trap magnet straightens out the electron stream and allows it to go down the tube to the screen. This magnet does *not* affect the ions, which continue in a straight line into the tube structure where they do no harm. As Fig. 1 shows, the magnet is adjusted until the electron beam is just straightened out. Improper adjustment or weak field strength will allow the beam to hit the gun structure (aperture), limiting screen brilliance and producing secondary ion burns due to disintegration of the structure. A discussion of these ion burns was presented very thoroughly in the February, 1952, issue¹.

At this time it is too early to evaluate whether much trouble will be encountered with centering units, for electrostatic and electromagnetic focusing cathode-ray tubes. In checking with a large service organization and numerous dealers not many bad ion-trap magnets have been turned up. But as they were normally unexpected these cases led to many hours of needless trouble shooting before the ion-trap magnets were finally identified as the elements responsible for the difficulties.

A magnet checker

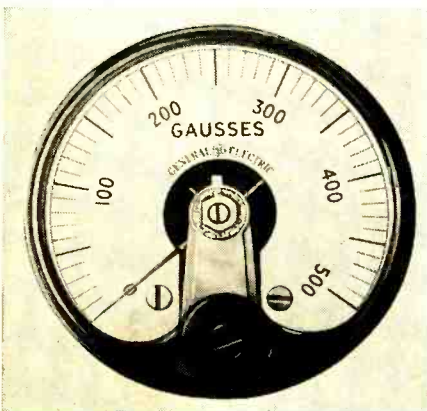A simple tester to check the field strength of these magnets may pay for itself even if it just clears the atmosphere by showing that the magnet is not the cause of raster misalignment, loss of brilliance, or ion burns on the picture-tube screen.



High-grade General Electric Gaussmeter. This instrument is portable and indicates field strength with 5% accuracy.

The magnetic field strengths employed in these assemblies run between 5 and 40 gaussses. Therefore the gauss meter should preferably cover this range as closely as possible. Numerous commercial meters are available, among which General Electric's field meter is particularly adaptable and inexpensive. These field type portable indicators have an accuracy of $\pm 5\%$ and are supplied with standard reference magnets. GE bulletin GEC-777 describes all available models including one of 0-100 gauss range (Cat. No. 416X29) which sells for \$72.00. Besides commercial units, home-built designs have been featured in several publications^{2,3}. However, for the experimenter or technician who does not wish to either build such a gauss meter, or wants to limit his expenditure to a more modest sum, another meter is available.

Magnaflux Corporation sells a pocket field indicator model No. 2480 for the small sum of \$2.60. It is intended for use with the Magnaflux inspection system to allow a check of tested structures or parts to insure that no residual magnetic field has been left after test. As such it was not intended to be a highly accurate instrument, and is not calibrated in gaussses. It simply has a scale of plus or minus 20 which corresponds somewhat to the field strength

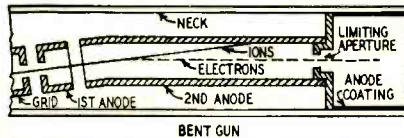


Fig. 1—Electron and ion paths through gun at correct ion-trap-magnet setting.

in gauss $\pm 50\%$. Individual units vary by as much as 25% among themselves.

However, this is of little consequence in TV work, as will be indicated shortly.

The types and forms of ion-trap and centering magnet assemblies vary widely, as does the field strength of the magnets. There are ion-trap units with single bar magnets (mounted either across or parallel to the tube neck), double ring types, bar and ring, and double bar, to mention some of the most common kinds.

The field strengths of these magnets vary widely among the different types. The two-magnet assembly delivers a strong and a weak magnetic field, whether of bar or ring construction. The apparent value of the field strength will also vary with the point at which it is measured. This means that regardless of the type of field strength indicator used, some measurement configuration must be used for each type of assembly if comparative strengths of assemblies are to be measured.

Therefore some position and distance between the magnet assembly and indicator must be selected and noted on a chart along with the value of the flux meter reading for each type of assembly. Use a *known good unit* for the check. From then on it will only take a moment to check an unknown unit of the same type. Absolute values cannot be given in the article, because of the variation in flux meters, and the subject components. A variation of 50% from the selected standard, should allow good units to pass; all other units being eyed with suspicion.

References:

1. *Ion Burns*
RADIO-ELECTRONICS Feb. 1952
2. *Magnetic Phenomenon*
RADIO-ELECTRONICS Nov. 1951
3. *Magnetic Flux Comparator*
Radio and Television News Engr. Edition Mar. 50


RELAY RHOMBIC BRINGS TV TO SHADOW AREA

A SIMPLE but sizable twin-rhombic antenna system developed at the University of Denver picks up high-strength TV signals on a mountain top and radiates them to receivers in a signalless canyon far below.

The pickup rhombic on top of the mountain is beamed with scientific accuracy at the transmitter 55 miles away. An open-wire transmission line several hundred feet long links it to the reradiating antenna. This one is aimed with equal precision at the receiver site more than a mile distant.

The final antenna at the receiver may be any standard type, but in this installation a third rhombic was used to provide the ultimate in sensitivity.

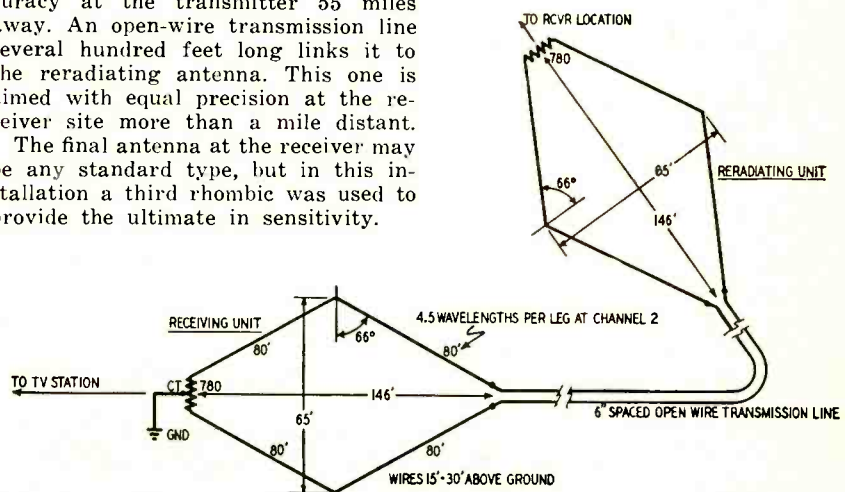The diagram shows the dimensions of the all-channel rhombics used in the Colorado installation. Increasing the included angle from 66° to 70° improved the response on channels 7-13. END



low-frequency losses and phase shift.

Another method is to use fixed bias. Ground the cathode and apply a negative d.c. voltage to the grid through resistor R_k , as shown in Fig. 2. Consult the tube manual for the maximum value of R_k that may be used with fixed bias. The advantage of this method is that there is no reduction in gain from degenerative feedback.

The third approach is to bypass the cathode resistor with a very large capacitor—perhaps 1,000 μf . This value will bypass all but the very lowest frequencies and the gain of the tube will not suffer from degenerative feedback.

Degeneration can also be introduced in the screen-grid circuit. If the screen is not bypassed effectively, the gain of the tube will be reduced and phase shift will result. When a signal voltage is applied to the control grid there will be variations not only in the plate current, but in the screen current as well. This varying screen current will develop a varying voltage across any impedance in the screen circuit. The screen bypass capacitor C_s in Fig. 2 represents an impedance.

For adequate screen bypassing the reactance of C_s must not be more than about 1/10 or 1/20 that of the screen-dropping resistor R_s . For example, if the screen resistor is 50,000 ohms, the reactance of C_s should not exceed 5,000 ohms at the lowest frequency to be amplified, and should preferably be even smaller. For most applications a value of 10 μf will be satisfactory.

The final source of reactance is the power supply. If the reactance of the output filter capacitor C_f rises appreciably at low frequencies, the video-amplifier stages, which are all connected to the common B plus line, will not be decoupled effectively. Signal voltages will circulate on the B plus line. This may cause oscillation at a low frequency and create flickering on the screen of a television set.

For this reason the output filter capacitors in well-designed television sets are always quite large. Electronically regulated power supplies are often used in elaborate equipment to provide the lowest possible internal impedance.

Thus far we have covered the theory behind the R-C-coupled amplifier relating to its low-frequency performance. We have shown how the effects of the cathode and screen and of the power supply can be minimized. The only source of frequency and phase distortion left is the coupling capacitor C. We shall see how the effects of this capacitor can be compensated for.

Low-frequency compensation

In Part I we found the best values for all the parts that affect the high-frequency response. Now we will find the correct values of the parts contributing to the low-frequency response. See Fig. 3. The cathode resistor R_k is left unbypassed. This gives equal degeneration at all frequencies but reduces the stage gain. With the cathode

bypassed, or with fixed-bias operation (Fig. 2) the gain A of the 6AH6 is given by $A = gm \times Z_L$. The gm of a 6AH6 is 9,000 micromhos, and Z_L can be assumed equal to R_L , which was fixed at 1,300 ohms for high-frequency compensation. (See Part I, in the March RADIO-ELECTRONICS.) Without degeneration, then $A = .009 \times 1,300 = 11.7$. When the cathode of the 6AH6 is left unbypassed we use this equation for the gain A_1 :

$$A_1 = \frac{A}{1 + (gm \times R_k)}$$

where A is the gain without degeneration (11.7). Thus

$$A_1 = \frac{11.7}{1 + (.009 \times 160)} = 4.8.$$

Before we can find the other values it would be well to explain how the R_d-C_d compensating circuit enters into the problem. Its basic purpose is to decouple the stage from the common B plus line and eliminate low-frequency oscillations. But with the proper choice of values it can also compensate for the effects of capacitor C.

The theory behind the combination is not at all difficult to understand. It has been explained how the reactance of the coupling capacitor C rises at low frequencies and delivers a smaller voltage to the following grid. At medium and high frequencies the plate-load impedance of V1 is equal to resistor R_L , since C_d has negligible reactance at these frequencies. However, when the frequency is lowered, C_d will no longer be an effective short circuit to ground, but may have appreciable reactance.

While the increasing reactance of C reduces the signal voltage at the grid of V2, the reactance of C_d is increasing as well. The parallel combination R_d-C_d becomes part of Z_L and raises the gain of V1. The two work together. When the reactance of C_d is equal to the resistance of R_d the total load impedance Z_L will be very nearly equal to R_L plus one-half the resistance of R_d . This will greatly increase the gain of V1.

Resistor R_d should be made as large as possible. This will be limited, of course, by the power-supply voltage. The higher this resistance the lower the frequency to which compensation can be carried. A value of 10,000 ohms is a good choice. In our sample problem with the 6AH6 drawing a plate current of 12.5 ma, a 10,000-ohm resistor would create a drop of 125 volts. If a 425-volt supply is available we can use this value of resistor and still get the required 300 volts for the tube. If not, we will have to use a smaller value resistor for R_d .

$$\begin{aligned} E &= I \times R \\ &= .0125 \times 10,000 \\ &= 125 \text{ volts.} \\ W &= E \times I \\ &= 125 \times .0125 \\ &= 1.56 \text{ watts.} \end{aligned}$$

For safety, R_d should have a rating of at least 3 watts. Two 20,000-ohm, 2-watt resistors in parallel will do nicely.

When R_d is very large the system will almost exactly compensate for the effects of C if the time constant $R_d C_d$ exactly equals the time constant $R_k C$.

This time constant should be quite large, somewhere between 0.025 and 0.5 second. As mentioned before, there is a limit to the resistance that may be placed in the grid circuit of V2. For a 6AG7 the maximum resistance is 1 megohm.

Suppose we choose a time-constant t of 130,000 microseconds and a value of 0.25 μf for C.

$$C_d = \frac{t}{R_k} = \frac{130,000}{1,300} = 100 \mu\text{f}$$

$$R_k = \frac{t}{C} = \frac{130,000}{0.25} = 520,000 \text{ ohms}$$

This will give flat response almost all the way down to d.c. and would be fine if the video amplifier is to be used in an oscilloscope for observing frequencies down around 5 cycles.

The requirements are not so severe for television applications, and a time-constant of 52,000 microseconds would be adequate. C could have a value of 0.1 μf . This will give a response well within the required range. Then

$$C_d = \frac{t}{R_k} = \frac{52,000}{1,300} = 40 \mu\text{f}$$

$$R_k = \frac{t}{C} = \frac{52,000}{0.1} = 520,000 \text{ ohms}$$

A 510,000-ohm (standard value) resistor can be used in both cases.

The last item to find is the value of the screen resistor R_s . The screen of a 6AH6 requires 150 volts at a current of 2.5 ma. A 10- μf screen bypass capacitor will do nicely. Both C_s and C_d are shunted with .001- μf mica or ceramic capacitors to provide better bypassing at the high frequencies. With a 425-volt supply the drop in R_s is

$$425 - 150 = 275 \text{ volts}$$

$$R_s = \frac{E}{I} = \frac{275}{.0025} = 110,000 \text{ ohms}$$

$$W = I \times E = .0025 \times 275 = 0.6875 \text{ watts}$$

A 2-watt resistor should be used for safety. This can be made up of two 220,000-ohm, 1-watt resistors in parallel.

Fig. 4 shows the final circuit with all values derived thus far for high- and low-frequency compensation.

Part III of this series will take up other types of high-frequency compensation. So far we have covered only the shunt peaking method (RADIO-ELECTRONICS, February, 1953).

(TO BE CONTINUED)

Third Conversation—

"What Is Electronics" also interests Ken and Will this month. After defining electronics, they discuss the electron gun and C-R tube



TELEVISION?

...it's a cinch!

By E. AISBERG

From the original "La Television? . . . Mais c'est très simple!" Translated from the French by Fred Shunaman. All North American rights reserved. No extract may be printed without the permission of RADIO-ELECTRONICS and the author.

Will—There's still one thing I can't get. When we were talking last time, you said mechanical TV systems had been abandoned in favor of electronic ones. Well, I think the Nipkow disc is electronic.

Ken—How did you get that idea?

Will—Aren't its atoms made of protons, electrons, and neutrons? What could be more electronic?

Ken—When we say electronic, we are talking about electrons in the pure state, separated from the protons; that is, electrons all by their lonesome. Now, where would you find that kind of electrons?

Will—Why, in vacuum tubes, of course; or at least in the part of the vacuum tube where the electrons make their jump from cathode to anode.

Ken—Correct! And—practically up to the invention of the transistor, every branch of the technique called *electronics* dealt with currents of electrons in vacuum tubes.


Will—Let's stick to television. Just how do they get the electrons that these modern systems use?

Ken—Just as they do in radio—by making them jump off a hot cathode.

Will—And then what do these electrons do?

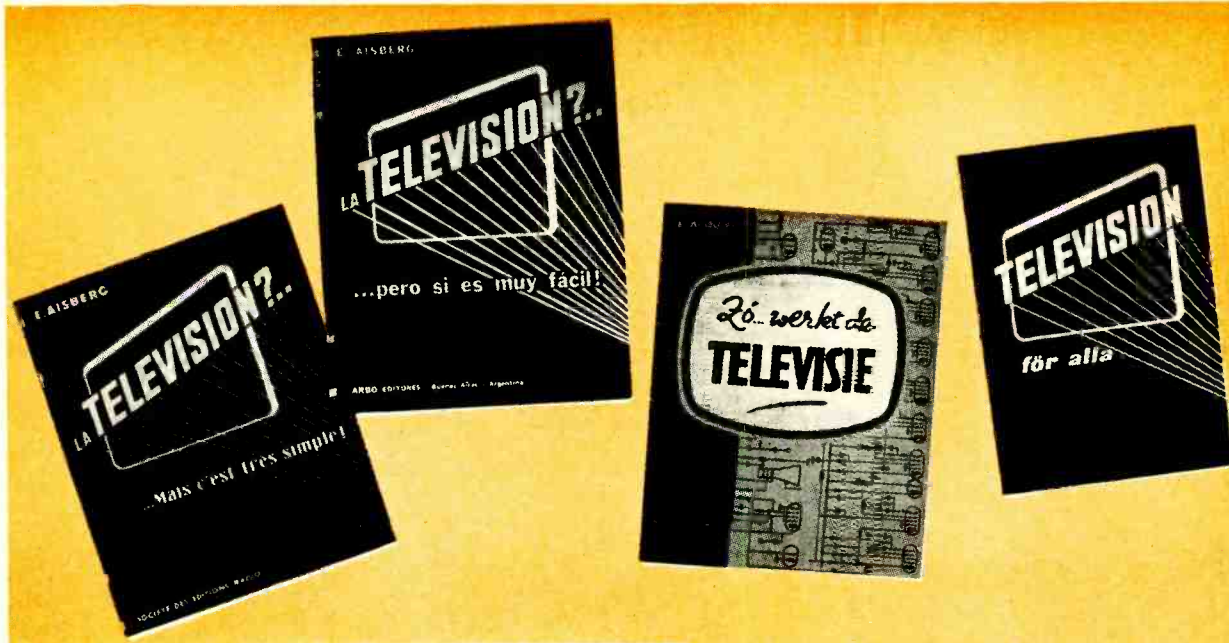Ken—Plenty! It's those electrons that turn your image into an electric signal at the transmitter, and then back to light at the receiver. Remember how the beam of light sweeps across the picture in the Nipkow disc? Well, in the electronic system, a *beam* of electrons scans the image, reading the elements line by line.





Will—I can understand electrons flowing from cathode to plate in an ordinary tube. But how can electrons be concentrated into a fine ray or beam, and then be moved across the image like the beam of light from the holes in the scanning disc?

Ken—That's what we're going to find out right now. The *cathode-ray tube* is the device which takes the place of the Nipkow disc and makes all these things possible. And—if it will make you feel more at home—we can start our cathode-ray tube out in life as a triode, much like those in radio. It has its differences, of course. First, it uses a cathode with a very small emitting surface (a so-called "point cathode") to concentrate the electrons.

Will—Get all your electrons together at the start, eh? Then they'll all follow the same path and stay in a tight beam.

Ken—My young friend, remember these electrons all carry the same (negative) charge, so they repel each other every step of the way. They're like those rugged individualists who won't co-operate to do useful labor unless they're compelled to. They try to get as far apart as possible unless some outside force makes them act sociable in spite of their own feelings.

A peculiar tube

Will—Then where and how do you get these electrons together, if they keep spreading apart?

Ken—We usually start forcing them into a beam just after they've passed the anode.

Will—Say, what kind of a tube is this? You mean the electrons keep on going after they pass the plate?

Ken—That's just what I said. It has a hole in its center, and is kept at a high positive voltage, so it speeds up the electrons quite a bit before they pass through the hole, to finish their course a lot farther on.

Will—Funny kind of a tube!


Ken—Funnier than you imagine! If the electrons going through a hole in the plate looks funny to you, what would you say to a *grid* that's really a cylinder around the cathode?

Will—How could a grid like that work?

Ken—Same as any other grid. If it's very negative, it repels the electrons back toward the cathode, so that a very few get by. When it's less negative, most of the electrons from the cathode can get through on their way to—and beyond—the plate.

Will—Is this flow of electrons large?

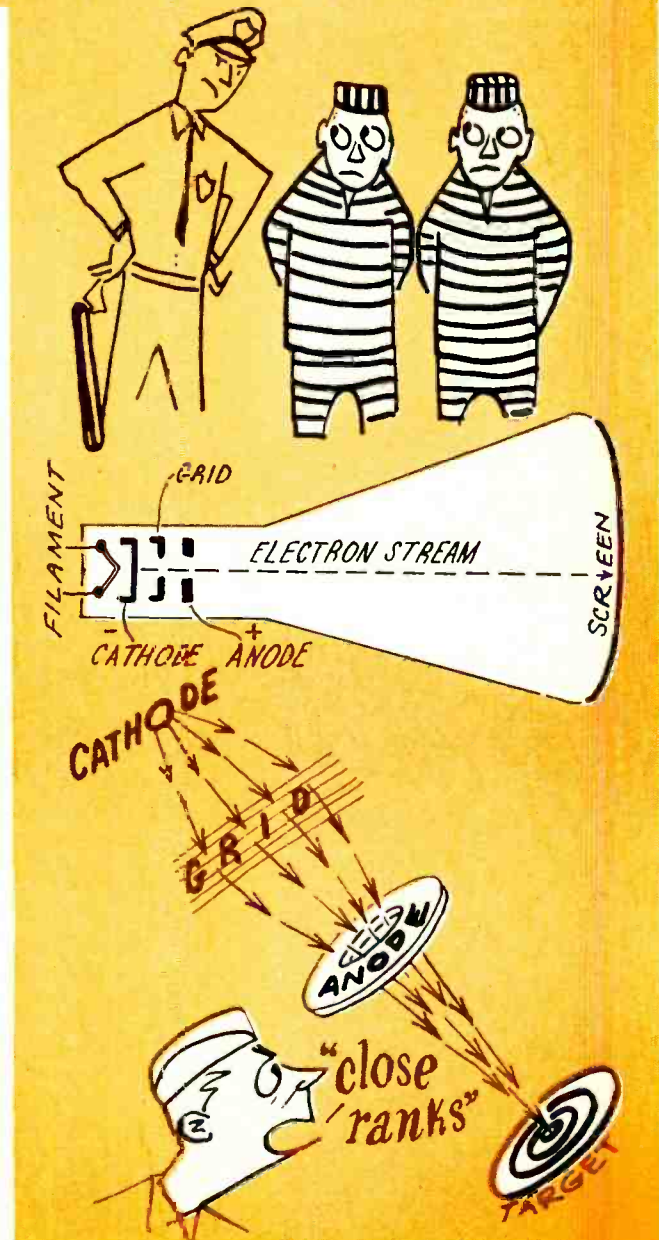Ken—No, the current in a television picture tube is a lot smaller than in a receiving triode. It can be in the order of a hundred microamperes. And the cathode-ray tube would be pretty useless as an amplifier, too. Its transconductance



is only a few microamperes per volt, and its internal resistance is likely to be in the order of a hundred megohms!

Light artillery

Will—So if it won't amplify, what *does* it do?

Ken—It acts like an electronic machine gun. Television needs a device that will produce quantities of electrons and—more important—regulate that quantity. So, in a receiving cathode-ray tube, or *kinescope*, you find this piece of electronic artillery (actually called an *electron gun*) at the rear of the tube, next to the socket.

Will—I take it that these kinescopes are real vacuum tubes—there's no air in them?

Ken—Of course. Otherwise our electrons would collide with heavy molecules of air and lose their speed. You need a vacuum as near perfect as possible in a cathode-ray tube, on account of the long distance the electrons have to travel as compared with ordinary receiving tubes.

Will—I'm like Nature; I "abhor a vacuum." But this one in the picture tube looks worse than most to me. Have you stopped to think that the surface of the tube has to support all the pressure of the atmosphere, or about 15 pounds per square inch?

Ken—I know. Now, surely you remember how to calculate the area of a circle? Suppose you tell me just what the pressure is on the face of, say, a 16-inch tube.

Will—Let's see. . . . A little more than 200 square inches. . . ! Why, over a ton and a half!

Ken—And if you figure in the sides of the cone and the rest of the tube, you run up about another ton and a half. Altogether, you have the weight of about 40 people pressing in around your tube.

Will—A bus-load of people! A tube like that must have to be fantastically strong!

Ken—Yes. Maybe you've noticed that the face of almost every tube is curved slightly outward for greater strength. And the cone is often made of steel.

Will—In spite of all that, I think I'll do my television experimenting up on a mountain.

Ken—A mountain. . . ? ?

Will—To keep the tube from exploding. The higher up you go, the lower the air pressure.

Ken—That's true, but come back to earth long enough to correct a mistake. The word is "implode," not "explode." And implosions are rare, which is a good thing. It's dangerous to be around when a picture tube comes apart; besides, they cost money!

The fluorescent screen

Will—What happens to the electrons from the gun when they get to the end of the tube?

Ken—The inside of the tube face is covered with a translucent layer that glows where the electrons hit it.

Will—Is that the same kind of stuff the hands of my watch are painted with?

Ken—No, that material is *luminescent*—a substance that glows by itself without being excited by light or some other radiation. A picture-tube screen is covered with *fluorescent* material—stuff that glows when it's excited by some other (usually invisible) radiation of a shorter wavelength than visible light.

Will—Is that the principle behind fluorescent lighting?

Ken—Yes. In a fluorescent lamp, an electric discharge in the mercury vapor inside the tube produces invisible ultraviolet rays. When they strike the inside of the tube, which is covered with fluorescent material, it glows and produces visible light.


Will—Your fluorescent tube is a sort of superheterodyne, then?

Ken—What?

Will—Doesn't it change the very high frequencies of ultraviolet light to the lower visible frequencies?

Ken—You're right, at that. But let's get back to the job. We have an electron gun that shoots its projectiles to the screen and makes it glow. But because the bullets spread out, we get a large bright spot on the screen. Trying to outline an image with a spot like that would be like trying to paint the fine details of a picture with a whitewash brush.

(TO BE CONTINUED)

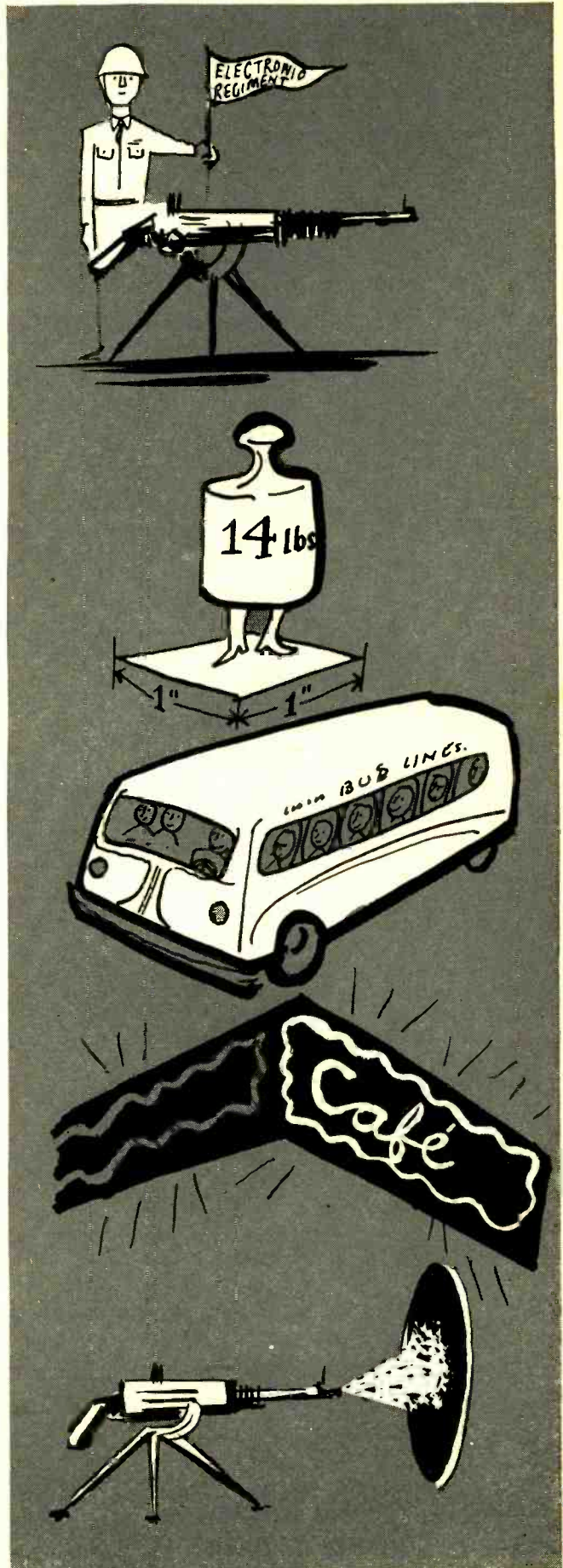

DX

PROSPECTS FOR UHF TV

Hams work u.h.f. dx with negligible power—Why not TV?

ABOUT twenty-five years ago one of the leading technical journals published a learned article on wave propagation. Based on all that was known of the subject, it tried to predict what we would find when we started to use that portion of the radio-frequency spectrum now known as v.h.f. and u.h.f. It was a masterful job, and it set the pattern of wave propagation reasoning for years to come. There was only one thing wrong: the authors of the article had no way of knowing that there were many factors that would soon rise to complicate their neat picture of a "line-of-sight" world above 30 mc or so.

As soon as amateurs—then invariably the first mass users of new radio frequencies—started to make general use of their 5-meter band, they began to run across things that caused much head-scratching in scientific circles. In one of the finest pieces of original research ever done by an amateur in any field, a 5-meter enthusiast established the basic correlation between weather and v.h.f. propagation, and in the middle '30s first stated the now-accepted theory of air-mass boundary bending of v.h.f. waves.

The amateur discovery of sporadic-E dx on 56 mc followed soon after. Then 5-meter hams found that they could bounce their signals off the aurora to points several hundred miles away. Showing how far off were the early estimates of the potentialities of the v.h.f. region were: reflections from ionized meteor trails; 50-mc dx of world-wide proportions with the passing of a sunspot cycle peak in the years immediately following World War II; several as yet incomplete studies of tropospheric and ionospheric scattering and other forms of v.h.f. dx. *Line-of-sight* indeed!

It was the great error in properly assessing the dx possibilities of the frequencies assigned to v.h.f. television that led to the allocations freeze just recently lifted. V.h.f. assignments have been reshuffled in the light of present-day propagation knowledge, and com-

mercial use of the new u.h.f. band is now getting under way. Will we run into the same confusion with u.h.f., too? Will there be u.h.f. dx, and if so, what will it be like?

Right now it's anybody's guess, though scientific research and amateur operation have combined to give us some clues. The field has been extensively investigated by competent propagation scientists, and much more is known of u.h.f. today than was known of v.h.f. when the first modern TV stations went on the air. Then, too, we have the benefit of several years of use by amateurs of their 420-450-mc band, not far below the low end of the u.h.f. TV band. As they have done many times in the past, hams have been making good use of their u.h.f. assignment, and some of their experiences may be of interest.

Just as with v.h.f. in the early '30s, hams started in on 420 mc with the line-of-sight concept thoroughly accepted. At first everyone thought that the only way to work any distance was to make for the highest mountain-top in the area. We know now that altitude helps, of course, but some of the best distances yet covered in the 420-mc band have been between ordinary home locations at or near sea level. There have been several contacts of more than 250 miles between stations in southern New England and the Washington, D. C., area. In September, a southern New Jersey ham on 435 mc was heard not far from Cleveland, Ohio, nearly 400 miles. Over in Algiers, a North African amateur worked across the Mediterranean to Toulon, France, 500 miles, on 435 mc. Did someone say "line-of-sight"?

It takes something rather special in the way of weather to bring about this sort of thing, but the signs are much the same as with tropospheric dx in the v.h.f. channels. Followers of RADIO-ELECTRONICS' monthly TV dx predictions have come to know these signs well. We know that under normal conditions the u.h.f. signal doesn't get through quite as well as the v.h.f. one,

and here we have many amateur comparisons between the 144- and 420-mc bands for evidence; but when there is pronounced tropospheric bending on v.h.f. it is really hot on u.h.f. When we get some good receivers and antennas going, there are some surprises due in u.h.f. TV, especially at distances out to 200 miles or so!

All the evidence points to considerably more variation in signal level at u.h.f. Weather variations, atmospheric turbulence, the summertime coastal inversions, dense fog—all these will affect u.h.f. signal levels to a marked degree. There will be more fading on u.h.f., and it will show up at closer range than on the v.h.f. channels.

On one 210-mile path where two amateurs have run frequent tests on 50, 144, and 435 mc, the strongest signal ever heard over the distance was on 435. Normally the u.h.f. signal doesn't get through at all, although v.h.f. signals are usually reliable. When the 144-mc signal begins to build up markedly, the 435-mc signal gets through too. When things are hot the 435-mc signal is stronger than the lower frequencies.

There are many things we don't yet know. A commercially conducted experiment has demonstrated that u.h.f. signals can be reflected off the moon, raising the possibility of world-wide u.h.f. dx if the technique can be sufficiently improved. Propagation peculiarities as yet not well evaluated may turn up many interesting results.

Amateurs, too, have succeeded in bouncing signals off the moon and recording the results. (See "The Radio Month" in this issue.—*Editor*)

Yes, there will be u.h.f. TV dx, too, and once again the TV dx enthusiast has a chance to contribute to our store of propagation knowledge. Dx observations by thousands of viewers have turned up much useful and interesting information. It goes without saying that history will repeat itself soon in the u.h.f. field. What say, dx-ers—who will send in the first u.h.f. dx report?

END

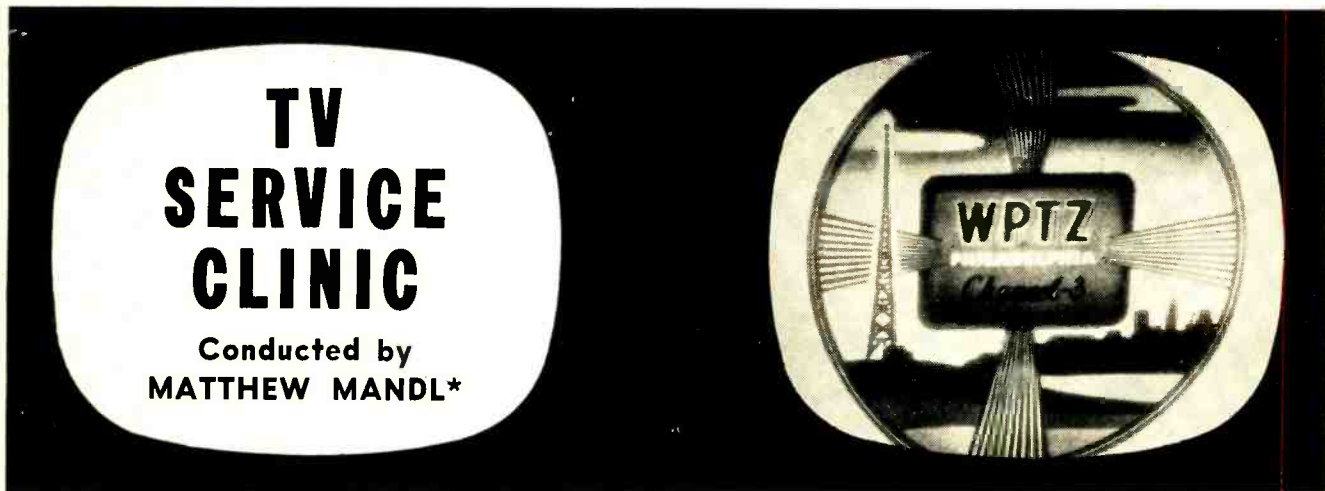


Fig. 1—Bending of vertical picture lines may have several causes. See text.

THE television technician must always be prepared for dual troubles when the apparently obvious solution does not solve the problem. Thus, loss of picture and sound with a raster present would normally mean trouble ahead of the sound take-off point. Sometimes, however, this is caused by trouble in *both* the sound and video-amplifier circuits.

Another reason for failure of normal corrective procedures could be manufacturing changes. For instance, Arthur Moreton of Morrisville, Pa., wrote about an Admiral 20B1 combination he took in for servicing. The complaint was a loud hum which was present only when a station was tuned in. Suspecting a cathode-filament short in the local oscillator, Mr. Moreton tried tube substitutions, which did not help. Upon pulling the chassis he found the fine-tuning unit saturated with oil which apparently had leaked to it from too much lubrication between the fine-tuning shaft and the channel-selector shaft.

The excess oil was removed and the receiver now had considerably less hum than before. The fine tuning was able to eliminate most of the hum, where before it had little effect. The hum was still audible, however, and much higher than on similar models.

A check of the supplemental information for this receiver disclosed that tunable hum in some of these models (early runs) could be corrected by connecting a 2,200-ohm, ½-watt resistor and a 0.1-μf, 400-volt capacitor from the a.g.c.-tube anode (pin 5) to ground. Another recommendation was to connect 25 inches of ½-inch bonding braid under the bracket holding the webbing for the picture tube (side nearest the audio lead). The other side of the braid connected under the power supply chassis, at the mounting screw nearest the audio lead.

Another problem which technicians often encounter is an adequate check of coils and transformers. A simple continuity check with an ohmmeter

often will not disclose any fault, yet the inductor may act up when the receiver is on and upset normal circuit functions.

Paul Barks of Winfield, Iowa, reports such a condition in a number of Motorola receivers using chassis TS-401, and in earlier production models using similar horizontal sweep circuits. Usual symptoms are picture tearing without complete loss of sync, plus sectional picture tearing which breaks up portions of an actor's face or body.

The first time Mr. Barks encountered this symptom he checked the phase detector and the cathode-coupled multivibrator horizontal-sweep generator. Tubes, voltages, resistors, and capacitors all checked satisfactorily. He disconnected the ringing coil, checked it for continuity, and found nothing wrong. He finally resorted to changing parts in the horizontal oscillator circuit, and when the ringing coil was replaced the trouble disappeared. Subsequently he corrected a number of other similar receivers by replacing the coil. He recommends doing this when such symptoms appear because considerable time can be saved in checking tubes and components needlessly.

Picture pulling

In a Hoffman model 637 receiver there is severe picture pull and the vertical lines tend to weave. Intermittently on severe pulling the screen goes black and picture is lost for a while. I have replaced all tubes in the horizontal and vertical sweep circuits and have checked parts. What could cause this trouble?—F. K., Norfolk, Va.

When the picture bends or weaves as shown in Fig. 1, the trouble could be caused by any one of the following conditions:

- Improper adjustment of horizontal lock system.
- Defective tubes or parts in the horizontal sweep system.
- Defective tubes or parts in the sync-separator stages.
- Improper sync amplitude caused by poor tuner tracking or video-i.f. alignment.
- Signal overload or defective a.g.c.

Video-amplifier tubes sometimes contribute to pulling by clipping a portion of the sync tip. This can happen even in a tube which checks all right in an emission tube checker. Tube cutoff occurs sooner than it should and clips the highest level of the signal (the sync tips).

The intermittent blanking out, however, seems to indicate a.g.c. trouble, and you should try a new 6AU6 a.g.c. rectifier. Insufficient a.g.c. voltage can cause overload by allowing excessive gain, and sufficient overload can blank out the picture.

Delta-match Yagi

I am constructing a channel-4 Yagi antenna and want to use a delta match as shown in the sketch (Fig. 2). Are these dimensions all right? What is the gain of this antenna, both single and stacked?—P. T., Ontario, Canada.

Your specifications are substantially correct for channel 4. The antenna length of 81.2 inches is satisfactory and favors the audio carrier slightly. Some manufacturers use 80 inches, which hits the center of the band more accurately. The extra 1.2 inches will make little difference at the relatively low frequencies of channel 4 as compared with the higher channels.

A single Yagi of this type has a gain of approximately 10 db compared with a matched reference dipole. Stacking

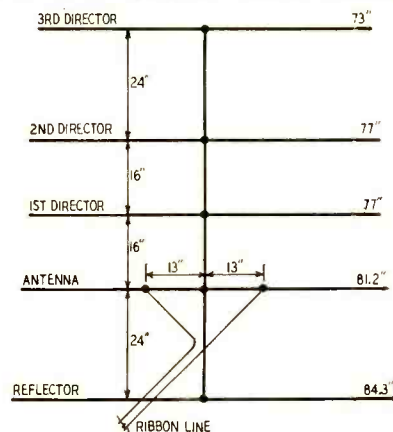


Fig. 2—Details of a channel-4 Yagi.

increases the gain an additional 3 db.

The delta match permits an impedance match to the transmission line and eliminates the need for an insulator. The impedance is zero where the antenna connects to the mast and rises as the lead-in connection moves away from the center of the antenna. Thus a variety of transmission-line impedances can be matched. The points to which the lead-in connects to the dipole (in the diagram) are approximate for 300-ohm line. Experiment for best results.

Trailing smears

In an Emerson 711 receiver there are trailing smears to the right of large objects. Please detail the various causes for this.—R. G., Uniontown, Pa.

This is usually caused by poor low-frequency response in one or more of the circuits carrying the video signal to the picture tube. Initially, all tubes should be checked from the tuner through the video i.f. stages, detector, and video amplifier. If this doesn't help, check for defective components in the video amplifier and detector circuits. In particular look for leaky coupling capacitors as well as for open capacitors in the R-C networks feeding voltages to the various tubes (the decoupling networks).

Finally, the tuner-tracking and video-i.f. alignment will have to be checked. If the video carrier is too far down on the response curve, the low-frequency video-signal components are not amplified sufficiently, with resulting poor low-frequency response and trailing smears.

Contrast in RCA 17T160

In an RCA 17T160 receiver I can't get sufficient contrast. I've tried adjusting the a.g.c. control and also have replaced the a.g.c. tube. The a.g.c. voltage changes with a change of received signal strength. What could cause the poor contrast?—H. P., Olney, Ill.

In this receiver the 6AV6 first-audio amplifier acts as a bias clamp for the a.g.c. This tube and the a.g.c. amplifier should be checked when trouble symptoms are present. From your description, however, it appears that the a.g.c. system is working all right. First, try new tubes in the tuner, video i.f. stages, and video amplifier. Also check the crystal video detector. Make sure the closed-circuit jack in the cathode of the video amplifier (6AG7) actually connects the .0033- μ f capacitor to the cathode, otherwise degeneration will result and the contrast level will decrease. The antenna system should also be checked for possible defects which could reduce signal input to the receiver.

If these measures fail to disclose the trouble, check all supply voltages and alignment.

TVI in radios

What can be done to minimize the squeals and whistles which are set up in radios from nearby television receivers?

Which television circuits are the cause for such interference?—E. G., St. Albans, N. Y.

Any television-receiver wires carrying the 30-cycle to 4-megacycle video signal can radiate and cause radio interference. The span of video frequencies falls not only in the broadcast band, but also includes the i.f. of the radio receiver. Another—and much more common—interference source is the high-voltage compartment. This produces 15,750-cycle pulses which are rich in higher-frequency harmonics. (Considerable radiation of these frequencies may take place from the picture tube itself. This is especially true of metal-shell types, in which almost the entire body of the tube is insulated from ground and forms an effective radiator for high-frequency harmonics of 15,750 cycles. In some cases this interference can be reduced by connecting a 500- μ f, 20,000-volt capacitor between the tube-rim contact and the TV-receiver chassis.—Editor) In addition, the 75-kilocycle signal established by yoke resonance and the transients developed by the collapsing horizontal-deflection field contribute to radio interference. The latter can be reduced (but not eliminated) by more adequate shielding of the television receiver. Unshielded high-voltage compartments should be covered, and the inside of the cabinet can be lined with aluminum foil grounded to the chassis. The cable from the television receiver chassis to the picture tube can be shielded, but if the shielding is too close to the wires some of the higher-frequency video signals will be shunted. This will decrease fine detail.

Interference can be reduced also by increasing the radio's efficiency. This can be done by peaking up the tuner tracking, i.f. alignment, and replacing old tubes to restore maximum gain. In some cases an outside antenna will increase the signal pickup and reduce the effect of TVI. All these procedures help, but if the radio is moved too close to the television set, interference will still be heard. Owners of table radios should keep them in rooms remote from the television receiver, and change their positions so the loop antennas are oriented for minimum interference pickup. Careful tuning of the radio and adjusting the drive control in the TV receiver for the proper level also help.

Blooming and focus

In servicing a Du Mont RA-113 receiver, I am unable to get good focus. An advance of the brilliancy control causes blooming and an additional advance causes picture loss. The focus control starts to clear the picture only at full clockwise rotation. I have checked the focus coil and the focus control with its resistive network. I've also replaced the 6BG6, 6W4, and the two 1X2 tubes but no change. Sound is normal. What other defects could cause this? I've tried a new picture tube, but symptoms were the same.—W. R., Detroit, Mich.

Blooming indicates insufficient high voltage. This reduces the velocity of the electron beam within the picture tube to the point where it cannot dislodge the space-charge electrons on the phosphor screen. As the brightness control is advanced, more electrons accumulate on the tube face, until eventually the beam cannot penetrate the space charge.

This will result in loss of picture and raster. Focus is usually affected and the range of the focus control is changed. You could, of course, alter the resistance of the focus-control circuit until the control gives best focus at center setting. First, however, correct the blooming.

Make sure the ion-trap magnet is at the setting which gives maximum brilliancy, regardless of corner shadows or its effect on beam position. Corner shadows can be eliminated by adjusting the focus unit (picture positioning).

Check for defective components in the horizontal-output circuit, as well as for low B voltages. Try a new low-voltage rectifier and check the filter capacitors for leakage which might be loading down the low-voltage supply. Also check the horizontal drive. This should be set just below the point where left-hand stretch or center compression occurs.

Resistor failures

In a Regal 630-type chassis I am getting repeated burnout of the 1,800- and 270-ohm resistors in the focus-control circuit. Occasionally the focus control also becomes defective.—J. M., Greenwich, Conn.

These resistors, plus the focus control and focus coil, are part of the network feeding the ion-trap coil and the minus 2- and minus 18-volt circuits. (Fig. 3) An overload in any section of the receiver fed by this network would

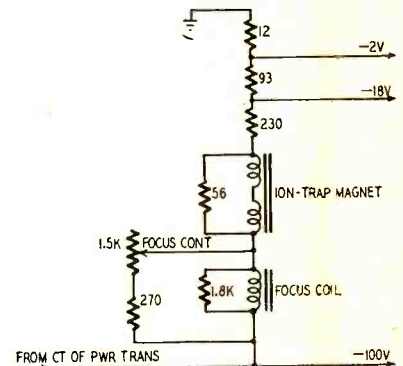


Fig. 3—Focus-control and negative-d.c. supply circuits in 630-type TV receivers.

cause excessive current through the focus-control network and the associated resistors. Overloads could be caused by defective filter and bypass capacitors, gassy tubes, or partial shorts. You may have to check a great many parts, for the trouble may be remote from the focus-control circuit. Take resistance readings of the various circuits involved to find where resistance is below normal. END

TV SIGNAL TRACING

TV presents other problems and requires different equipment than radio service

By **ENGINEERING STAFF**
SCALA RADIO CO.*

SIGNAL tracing in TV receivers differs in several respects from signal tracing in radios. First, the range of frequencies found in TV circuits is very much broader than in radio. Second, the supply and signal voltages in TV chassis cover a much wider range than in radio work. Third, the circuit impedances in TV receivers range from less than one ohm to as high as 10 megohms or more. Fourth, signal tracing in radios is usually concerned with sine-wave signals, while these are the exception rather than the rule in TV. TV circuits often operate with two signals present at the same time, such as the FM sound signal and AM picture signal, or 60-cycle vertical sync signal and 15.75-kc horizontal sync signal.

Other important differences will be developed later in this article.

The operating frequencies in the r.f., i.f., and—under some conditions—in the video amplifier of a TV receiver are too high for the usual service scope to display directly. For this reason, signal tracing in the r.f. and i.f. amplifiers requires *demodulator*, or detector, probes,


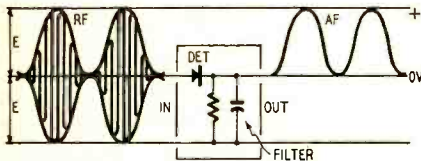


Fig. 1—Most service-type scopes cannot reproduce a h.f. carrier. If the wave is modulated and rectified by a crystal-detector probe, the low-frequency envelope can be seen on almost any scope.

which rectify the modulated waveform and recover the modulation envelope. For example, the carrier frequency of a modulated wave may be 30 mc, while the modulation envelope may represent a frequency of perhaps 1,000 cycles. The scope can display the 1,000-cycle output from the demodulator probe, although it cannot reproduce the modulated 30-mc carrier. The average value of a symmetrical sine-wave-modulated carrier is zero, as shown in Fig. 1.

Demodulator probes are usually built around crystal-diode detectors, because these devices are compact, have good frequency response, and do not require a source of heater voltage.

Both series- and shunt-type detectors

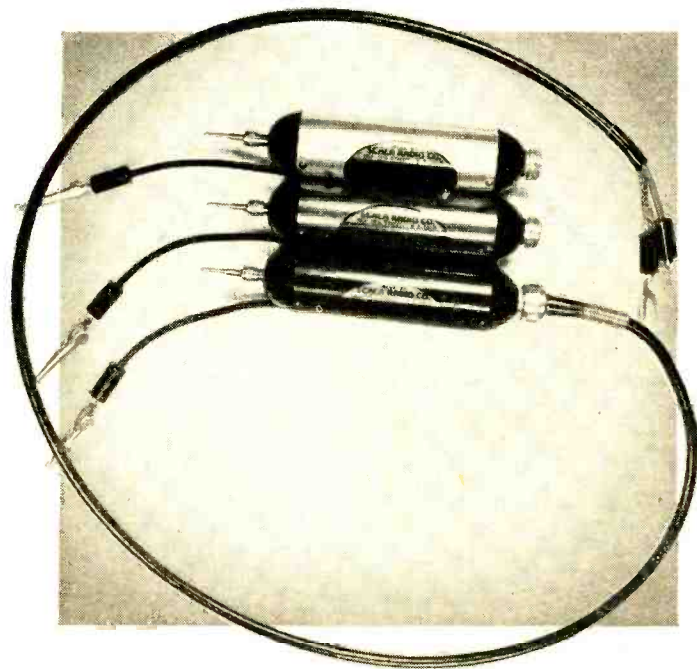

Three types of oscilloscope probes used in TV test work. (Top) Crystal-demodulator signal-tracing probe; (center) low-capacitance high-impedance 10-1 voltage-divider probe; (bottom) 100-1 capacitance-divider high-voltage probe.

(see Fig. 2) are used in commercial probes, and it will be found that the series type is the more sensitive for signal-tracing purposes. However, it will also be found that the series probe is the least suitable for video-amplifier testing, and will seriously distort the sweep output waveform.

For this reason, practical crystal demodulator probes usually have moderate sensitivity, an input capacitance approximately equal to that of a picture tube, and a time-constant suitable for demodulating carrier frequencies which have been modulated by frequencies as low as 60 cycles.

Shunt-type probes are generally found most suitable for signal tracing as well as for video-amplifier checking.

Testing video amplifiers

There are two general methods of

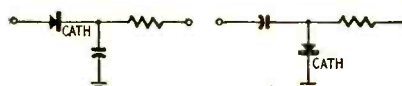


Fig. 2—Series (left) and shunt detectors. The series resistors prevent the scope input capacitance from shunting the detector and reducing the output.

testing a video amplifier. One technique is to apply a sweep signal to the input of the amplifier, and to display the amplifier output on the scope screen. Most service scopes will not respond to frequencies of 4.5 or 5 mc, and a demodulator probe must be used to develop the visual-response curve. The video

sweep signal used in such tests varies from a low frequency of about 100 kc to 5 or 6 mc, 60 times a second.

A demodulator probe which is satisfactory for i.f. signal tracing may be quite useless for video-amplifier testing. The reason is that the response of the video amplifier depends in great part on the *shunt capacitance* across the output. If this shunt capacitance is greater than the input capacitance of the picture tube, the high-frequency response will appear to be very poor. On the other hand, if the shunt capacitance of the test circuit is less than the input capacitance of the picture tube, the frequency response will appear to be better than it really is.

Obviously, the input impedance of the demodulator probe must equal the picture-tube input impedance. The probe must also have good response to 60-cycle square waves, because the demodulated sweep output is of the same general form as a 60-cycle square wave, and if the time-constant of the probe is too long, the scope will indicate a true rise but a false fall of the response curve.

Square-wave testing

The square-wave test is more informative than the sweep-frequency test, because it shows up phase distortion as well as frequency distortion in the video amplifier. Phase distortion is just another way of expressing abnormal time delay, which means that small picture elements may arrive slightly later or slightly earlier than large picture

* San Francisco, California

elements regardless of their positions in the original picture. Accordingly, phase distortion causes the small picture elements to be displaced horizontally with respect to the larger picture elements, and the observer describes the picture as "smeary."

For accurate square-wave tests on video amplifiers, the vertical-deflection

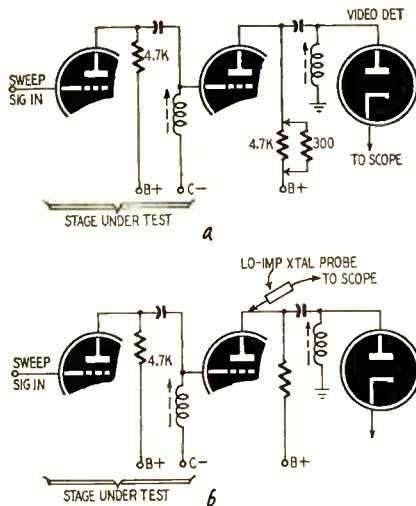


Fig. 3—(a) In stage-by-stage alignment using the video-detector output to feed the scope, intermediate stages must be shunted as shown to prevent their resonant peaks from affecting the scope trace. (b) A low-impedance demodulator probe automatically shunts the following stage and feeds the scope.

amplifier in the scope must have better frequency and phase characteristics than the TV receiver. Otherwise, the output from the video amplifier must be applied directly to the vertical-deflection plates of the scope. (This gives the best possible frequency and phase re-

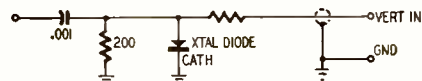


Fig. 4—Low-impedance probe circuit.

sponse from the scope, but has the disadvantage of providing only $\frac{3}{8}$ -inch to $\frac{5}{8}$ -inch deflection on the scope screen.)

Never feed the output of the video amplifier directly through a cable to the input of the scope. Any usable length of cable will have very much greater capacitance than the grid-cathode circuit of the picture tube, and the square-wave response on the scope screen will be grossly misleading.

To avoid such distortion, a low-capacitance probe must be used, and this probe should have the same input capacitance as the picture tube.

If the output of the video amplifier is applied directly to the deflection plates of the scope, the connection must be made with a short, unshielded test lead.

Of course, the socket is removed from the base of the picture tube in all such tests, because the input capacitance of the scope setup is substituting for the input capacitance of the picture tube.

Stage-by-stage response

The reader no doubt will point out that he requires another important application from his crystal probe—namely, the ability to reproduce stage-by-stage i.f. response curves. Some TV receiver manufacturers suggest this method of i.f. alignment.

There are two general methods of making such a stage-by-stage alignment, one of which requires a crystal probe. These two methods are indicated in Fig. 3. In the first method (a), the picture detector serves as a demodulator for the alignment of any one stage. In b the demodulator probe serves this purpose, and the use of a number of shunting resistors is avoided.

A low-impedance probe is usually considered necessary for this sort of work, as illustrated in Fig. 4. However, if a 300-ohm resistor is shunted temporarily across the plate load of the circuit to which the crystal probe is applied, the usual crystal probe will serve quite well. The shunt resistor swamps out the unwanted resonance of the plate load, and the crystal probe demodulates the sweep output from the stage under test.

Accordingly, a low-impedance crystal probe is not necessarily required, and a probe that is satisfactory for video-amplifier work also serves satisfactorily for stage-by-stage i.f. work.

Sweep-circuit testing

Unlike radio testing, TV testing is concerned with shapes of waves in very many cases, and with various types of voltages. For example, a normally operating TV receiver may produce the typical waveforms indicated in Fig. 5, while a "sick" receiver may produce the variants shown in Fig. 6. And every little variant has a meaning all its own; the problem of the technician is to learn to read this new language, and to be able to spot the receiver component responsible for the waveform distortion.

These waveforms also represent different kinds of voltages. The TV technician hardly ever speaks of r.m.s. voltages used so widely in radio work. Instead, he speaks of peak-to-peak voltages, positive-peak voltages, and negative-peak voltages. These relations are shown in Fig. 7.

The probes used to apply these waveforms to the input of the scope must also attenuate their voltages by known factors, so that their peak-to-peak (or other) values can be read from the scope screen. It is customary in probe design to make the attenuation factor either 10-to-1, or 100-to-1. That is, if we apply a 100-volt wave to the input of a 10-to-1 probe, 10 volts will be applied to the input of the scope. Then, if the scope screen has been calibrated for a sensitivity of 1 volt per square, the 100-volt wave will produce 10 squares of deflection of the screen.

The technician does not want to recalibrate his scope every time he plugs in a probe, and he does not have to—provided he uses such a decimal probe—that is, a 10-to-1, or 100-to-1 probe;

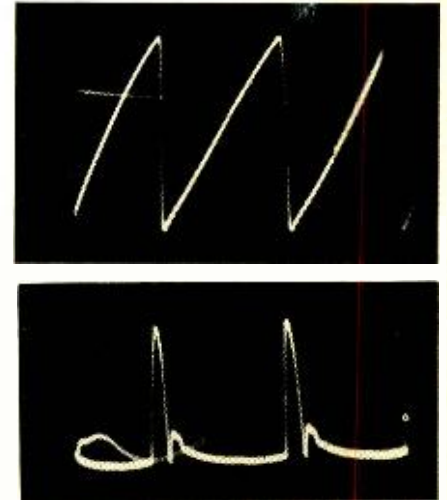


Fig. 5—(Top) Normal current trace in horizontal yoke windings. There is only slight non-linearity, and a trace of ringing at the start of each sawtooth. (Bottom) The 15,750-cycle ripple component in the high-voltage d.c. output. (Both waveforms were fed to the scope vertical-input circuit through capacitive voltage-divider probes.)

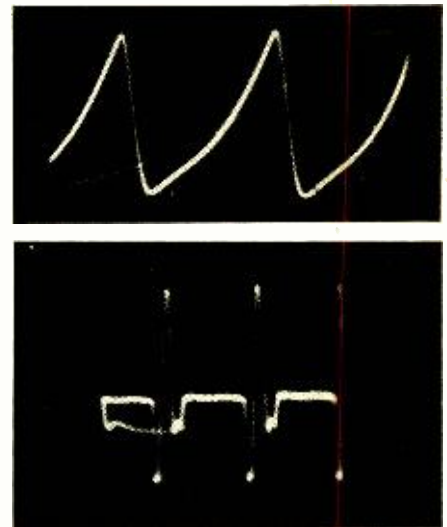


Fig. 6—(Top) Distortion in horizontal yoke current. Nonlinearity shown would compress left side of picture. (Bottom) Negative undershoot in high-voltage waveform drives the plate of the horizontal-output amplifier negative. This may generate Barkhausen oscillations, causing vertical bars on screen.

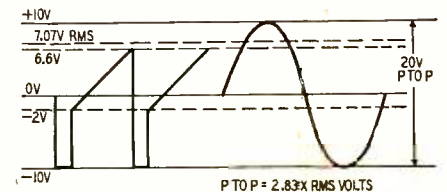


Fig. 7—Effective (r.m.s.) voltages can be applied accurately only to the measurement of symmetrical sine waves. The amplitudes of trapezoids, pulses, and other irregular waveforms are generally expressed in terms of peak-to-peak, positive-peak, or negative-peak voltages, which can be read on a scope.

he merely adds *one zero* to his original calibrating factor.

When checking the waveform across the horizontal-deflection coils, the low-capacitance probe, which is also an attenuating probe (usually 10-to-1), can be utilized to advantage, not to provide increased input impedance, but to attenuate the source voltage to a point at which the scope amplifier is not overloaded.

Another important consideration concerns checking the waveform at the grid of the vertical blocking oscillator. In this circuit the oscillator grid leak is sometimes as high as 10 megohms.

The technician who attempts to test such a circuit will find that the input impedance of a direct cable to the scope is *far too low* for this application. Its capacitance will shunt the oscillator tank circuit, will cause a loss of signal voltage, and may seriously disturb circuit operation.

To avoid this difficulty, the technician may try a low-capacitance probe. Although the probe will eliminate the first difficulty, it usually will introduce another: The *input resistance* of the probe, being less than 10 megohms, will drain away too much of the d.c. bias voltage, again seriously disturbing circuit operation. When this difficulty is encountered, the technician must use a blocking capacitor in series with the low-capacitance probe.

Special low-capacitance probes are available which do not offer a d.c. path to ground, and thus eliminate grid-bias disturbances.

Checking high-voltage circuits

High voltage can do harm in these ways: It may *overload* the scope amplifier and distort the displayed waveform, without doing actual physical damage to the scope. It may puncture blocking capacitors, and char or burn out attenuator resistors. It may arc through insulating washers and carbonize terminal strips.

The plate of the horizontal output tube represents a typical circuit point that is potentially dangerous to the scope input system.

The voltage at the plate of the horizontal output tube, or at the plate of the high-voltage rectifier tube is always "high" as far as conventional scopes are concerned. To protect the scope against physical damage in such tests, a high-voltage a.c. probe is required. Such probes are constructed as capacitance dividers.

Looking ahead

The reader has now been introduced to some of the fundamental properties of special scope probes which are useful in TV service applications. In the next article he will be taken on a tour through a practical servicing situation. He will learn what various distortions mean in TV waveforms, how to calibrate a scope, and how to obtain true waveforms.

We'll be seeing you.

(TO BE CONTINUED)

PEAK-TO-PEAK CALIBRATOR

By GEORGE E. ROW

THE ability to measure *peak-to-peak* voltages of sweep and video-signal waveforms can help the service technician save considerable time in trouble-shooting TV receivers. Some late-model v.t.v.m.'s read peak-to-peak voltages directly, but generally the most convenient method is to use a calibrated oscilloscope, as this allows you to check waveform and voltage in one operation. Expensive laboratory-type scopes have built-in voltage calibrators, but the average service instrument requires an external calibrating unit.

The circuit selected (Fig. 1) combines simplicity with adequate accuracy for service applications. Sine-wave voltage from the power line (adjustable over a range of about 20 to 100 volts) is stepped up in the transformer and applied to a tapped voltage-divider network. At full input (with the 100-ohm resistor shorted out), the *effective* secondary voltage is 400. With a perfect sine wave this is equivalent to 1,120 volts *peak-to-peak* (2.8×400). The powerline waveform is so nearly sinusoidal that there is no appreciable error. By reducing the input with the 100-ohm resistor we can make the maximum peak-to-peak output exactly 1,000 volts. (This is equivalent to an *effective* voltage of 350, which will push 10 ma through the meter circuit.) Thus 10 on the meter corresponds exactly to 1,000 volts peak-to-peak, and lower readings represent proportional voltages.

The voltage divider allows you to tap off fixed fractions of the output, so that any peak-to-peak voltage from 1 to 1,000 can be obtained by adjusting the divider switch and the 500-ohm potentiometer.

The a.c. milliammeter is a *moving-iron* type, *not* a rectifier-type d.c. instrument. This simplifies the circuit, and gives maximum accuracy, since the circuit operates only on the 60-cycle frequency for which the meter is designed. The values of the resistors in the meter multiplier and bleeder are such that the maximum error introduced by the shunting effect of a 1-megohm oscilloscope input is limited to 2%. The total resistance of the meter and multiplier is 35,200 ohms.

The entire assembly fits conveniently into a standard 4 x 6 x 9-inch steel cabinet. An old booster chassis was used for mounting the transformer and bleeder network. The transformer



The completed oscilloscope calibrator.

was mounted in the center of the chassis to concentrate the weight in the middle of the completed instrument. The potentiometer and high-wattage section of the bleeder were mounted in the upper left-hand corner of the cabinet to avoid overheating the meter.

Materials for Calibrator

Resistors: 1—23,333 ohms, 1—100 ohms, 5 watts; 1—6,666 ohms, 1—2,333 ohms, 1—666.6 ohms, 1—233.3 ohms, 1—66.6 ohms, 1—23.33 ohms, 1—6.66 ohms, 1—2.33 ohms, 1—1 ohm, 1 watt; 1—35,000 ohms approx., 10 watts (see text); 1—500-ohm, 25-watt potentiometer; 1—100 ohms, 5 watts, adjustable.
Miscellaneous: 1 power transformer, 400 volts c.t. at 20 ma; 1 single-pole, 10-position selector switch; 1—0-10 a.c. milliammeter (Triplett type 3375 or equivalent); 1 s.p.s.t. toggle switch; 1—117-volt pilot light and socket; 1—chassis; 1—4 x 6 x 9-inch steel cabinet; 1 TV-type interlock line cord and receptacle; terminals; knobs; wire; solder; hardware.

Ventilating holes 1½ inches in diameter were made in each end of the cabinet and in the bottom and covered by copper mesh. The output terminals are two banana jacks on the panel. A TV "cheater" receptacle was installed on the rear panel in preference to an ordinary line cord which would dangle and drag when the instrument would be moved from place to place.

The calibrator is easy to use. Feed the voltage to be measured into your oscilloscope and adjust the vertical gain to give a trace about one inch high. Note the exact spread and without disturbing the oscilloscope gain control move the probe to the output of the calibrator. Adjust the range switch and potentiometer to give a sine wave of exactly the same height on the scope. The meter reading multiplied by the range factor is the peak-to-peak value of the wave. END

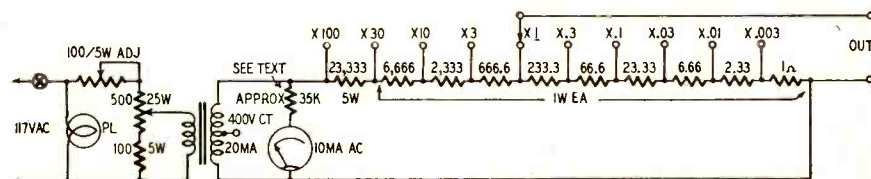


Fig. 1—Schematic diagram of the peak-to-peak voltage oscilloscope calibrator.

REWIRING BATTERY SETS FOR AC DC OPERATION


By RICHARD LAURENCE

OVER the past ten years the Rural Electrification Administration (REA) has brought power to the vast majority of farm homes. This has opened an entirely new market for the sale of electrical appliances and has brought radio technicians opportunities for additional profit by converting battery radios to line operation.

Most battery sets now in use utilize 1.4-volt tubes and the familiar 1.5-volt and 90-volt battery pack. A good battery set designed for reception in location as far from broadcast stations will have excellent sensitivity and selectivity, far above the average a.c.-d.c. table model. The owner is used to good reception and has a considerable investment in the set. If the set is reasonably new he can be usually sold on the idea of converting it.

If your locality has steady line voltage, a converter can be substituted for the battery pack; this is a very simple installation. In many locations, however, the REA voltage drops greatly under load conditions, and the converter will not furnish enough filament power. If you step up the filament voltage, it will be excessive when the line voltage returns to normal and will soon burn out the tubes. Under such circumstances, the most satisfactory way to convert is to rewire the set for power-line operation.

A typical battery set that I converted is the Philco 46-131, using 1LA6, 1LN5, 1LH4, and 1A5 tubes. To replace these I chose a 7A8 converter, 14A7 i.f. amplifier, and 50L6 power-output tube, since these have socket connections nearly identical to the original tubes. It was necessary to change the parallel filament wiring to a series hookup, using a 250-ohm, 10-watt resistor in the string to drop the extra voltage that would ordinarily be taken up by a rectifier tube (See Fig. 1). The resistor is first in line, and prolongs tube life by absorbing part of the initial current surge through the cold heaters. The battery on-off switch is a double-pole single-throw type; I disconnected the A plus

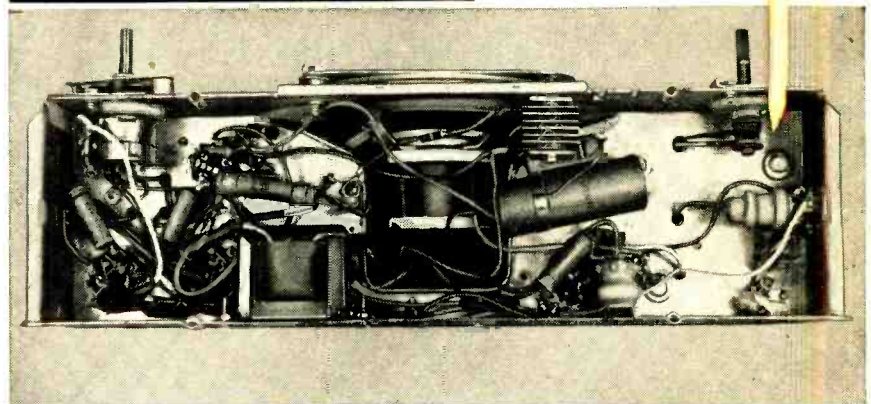

Philco 46-131 battery receiver after conversion to power-line operation.

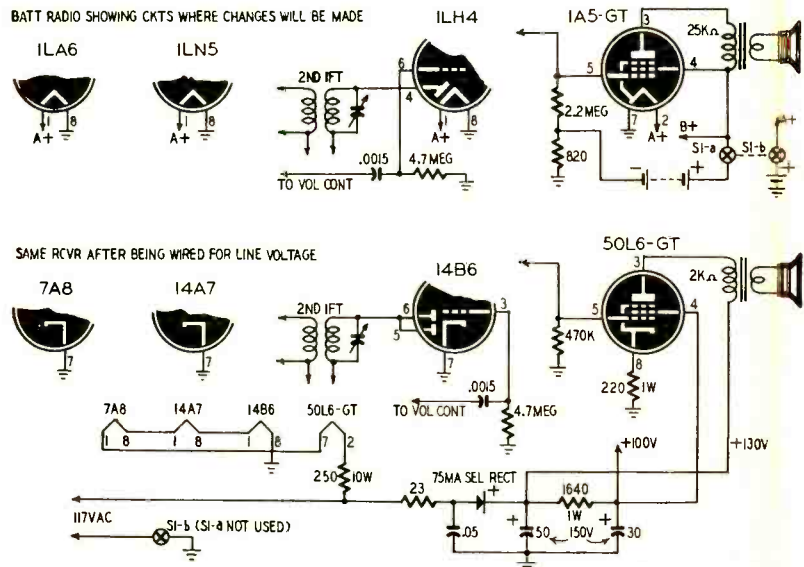


Fig. 1—(Top) Tube lineup of Philco model 46-131 battery-operated receiver, showing only socket connections and components that must be changed for conversion to power-line operation. (Bottom) New tubes and required circuit changes.

wires from one side and used it as a line switch, this side of the line connecting directly to the chassis. This is the only bad feature of this type of conversion, but a power transformer would make the expense prohibitive. The line-connected chassis is standard

with many manufacturers, and will give no trouble so long as a ground connection is not attempted. I always clip the ground wire and stick a piece of adhesive tape on the back of the radio, with a warning in red letters *not to attempt a ground connection.*

Incidentally, the set should be in top-notch playing condition before conversion is attempted. It's a little embarrassing to quote a set price and then find that the volume control or speaker will have to be replaced before the completed job is acceptable.

Ground the cathodes on the 7A8, 14B6, and 14A7 tubes. The No. 7 pins on the battery-tube sockets were used as tie-points for a.v.c. and B plus circuits, so you will have to disconnect these wires and float the connections (taping them thoroughly), or anchor them to terminal strips. The cathode of the 50L6 is connected to chassis through a 220-ohm bias resistor. (This value may seem a little high to most service technicians. The usual value is 150 to 180 ohms—*Editor*). The original B minus circuit was returned to ground through an 820-ohm resistor to provide bias for the 1A5 tube, with the 2.2-megohm grid resistor returned to the high side of this bias resistor. Both these units should be removed, and a 470,000-ohm grid resistor should be connected between pin 5 of the 50L6 socket and the chassis.

More extensive changes are necessary on the 14B6, since its socket connections differ considerably from the original 1LH4. The control-grid connection must be changed from pin 6 to pin 3; the diode plate is pin 4 on the 1LH4, and this connection must be transferred to pins 5 and 6, which are now tied together. Note that the 14B6 has two cathode pins—4 and 7—and both of these should be grounded.

I used a 75-ma selenium rectifier, since this is much easier than cutting a hole for another tube socket. A 27-ohm resistor is connected between the rectifier plate and line, and a .05- μ f, 600-volt capacitor from the a.c. side of the rectifier is connected to chassis to eliminate modulation hum. The filter capacitors are a 50- μ f (input) and a 30- μ f (output), both rated at 150 volts. The filter resistor is a 1,640-ohm unit, but any value between 1,500 and 2,200 ohms (1 watt) will do. All B plus lines are taken from pin 4 of the output tube.

The original output transformer had a primary impedance of 25,000 ohms. This must be changed to a 2,000-ohm unit, returning the B plus side directly to the rectifier cathode.

The oscillator grid resistor in the battery circuit has a value of 220,000 ohms, and theoretically this should be changed to about 50,000 ohms. In practice, the original resistor works perfectly with the 7A8 tube, and shows absolutely no tendency to block, so I left it in. After careful realignment this set really works well; with a 30-foot antenna I logged stations at nearly every division across the dial, with even the more distant ones completely free of converter noise. On practically all stations a quarter turn of the volume control drives the speaker to full power. There is none of the tendency to oscillate at the low end of the dial such as is so common to many small radios, and the selectivity is very good. END

“WHAT IS ELECTRONICS?” CONTEST

ANNOUNCEMENT OF AWARDS

First Prize \$100

John D. Goodell, The Minnesota Electronics Corp., St. Paul, Minn.

Second Prize \$50

Lt. Sheldon Jones, Valley Forge Army Hospital, Phoenixville, Penna.

Third Prize \$25

Richard H. Dorf, 255 West 84th St., New York 24, N. Y.

Fourth Prize (Two \$10 prizes awarded)

ET3 Stanley H. Dinsmore, U.S.S. Eversole, c/o FPO San Francisco, Calif.

Robert K. Rickard, Warnerville, N. Y.

Our prize contest "What Is Electronics?" was initiated (RADIO-ELECTRONICS, Nov. 1952, P. 45) to discover a better definition of the science than any heretofore offered. The perfect definition of electronics is in our opinion still to be written, however. Though some of the definitions are excellent, readers will note that important points that appear in one are played down in another. Definitions might have been improved by inserting phrases from other ones, but of course this is a contest, and the definitions had to be presented exactly as received.

The most complete and best worded definition was—in the opinion of our Board of Editors—that of John D. Goodell of the Minnesota Electronics Corp., printed below:

ELECTRONICS: The science that deals with phenomena produced by electrons, and techniques for controlling electrons to generate, change, combine, program, display, apply or transmit energy or information.

The second prize went to Signal Corps Lieutenant Sheldon Jones, a patient at Valley Forge Army Hospital, Phoenixville, Penna., for a very broad and well worded definition:

Electronics is the science and technology of the transfer of information or energy by electron emission, electromagnetic radiation, or devices employing the principle of semi-conduction in solids.

The third prize was awarded to Richard H. Dorf, audio and television consultant of New York City, well known to many readers of this magazine through his articles on electronic music. Though it lacks the scope of the first two definitions, it refers to the important feature: ". . . electron flow or potential in one circuit controls electron flow or potential in another. . . ."

Science and technology in which electron flow or potential in one circuit controls electron flow or potential in another, or in which emission or radiation of electrical energy is utilized.

The fourth place had four contestants running almost neck and neck. It was impossible to select one outstanding entry here, so two fourth prizes were awarded. One of these was to Electronics Technician Third Class Stanley H. Dinsmore,

U.S.S. Eversole, apparently somewhere in the Pacific:

Electronics is the utilization of free electrons, ionized particles, and electromagnetic waves for control, generation, reception, amplification, dissemination, and display of all types of physical information.

The other fourth prize goes to Robert K. Rickard of Warnerville, N. Y. for the definition:

Electronics is the scientific art of controlling the motion of electrons and associated electromagnetic fields, photoelectric effects, and ionization, so that information is processed, transmitted, and presented in usable forms.

Honorable mention is due Charles M. Dougherty of Los Angeles, and Howard J. Waters, Silver Spring, Md., who were runners-up for the fourth prize.

While we do not believe that any of the above definitions is perfect, we are sure that among them they contain the essentials for a workable definition of electronics. Readers may amuse themselves by putting it together—or we may hire a staff of experts and combine the best features of each into an "official" RADIO-ELECTRONICS definition of electronics!



NEW KIT SOLVES TUBE PROBLEMS

By PROF. ADOLPH
GLOCKENSPIEL*

THIS tube kit is capable of producing fifty tubes for \$1.00! Miniature, octal or Loktal types can be produced in your own shop at a cost of little more than two cents each, including the heavier television tubes that cause so much customer ill-will and unhappiness when they have to be replaced. Because of the cost of the meter, pump and other equipment, the first few dozen tubes will be a little more expensive, but after that, it will be necessary only to order replacements of tube envelopes, small elements, and the occasional bottle of gas or cement, bringing the cost down to a laughable figure.

Any intelligent service technician with a minimum amount of experience can make his own tubes after reading the simple instructions that come with the kit. The vacuum pump, hitherto the almost insuperable obstacle to tube-making on a small scale, has been made unnecessary by the newly discovered *Celosine* gas. This wonderful substance comes in a solid form. When placed inside a tube, it explodes as soon as the filament is heated and consumes all the gases in the tube, creating a very high vacuum.

Everyone knows how tubes are constructed. All the service technician needs to know is what tube he desires to make. Then, with the help of the latest tube manual, which contains all the graphs and characteristics of the tubes, he can assemble and employ any variable characteristics and mutual

transconductance. Tubes not exactly like any now in commercial production can easily be made.

The filaments are all supplied with the kit. Some of these are already fabricated, as they are too delicate to handle. A spool of filament wire is also furnished. This wire and other components of the kit can be used to repair tubes with burnt-out filaments. By doubling the wire for greater carrying power, the larger and more expensive television tubes can easily be restored to use. The marvelous *Celosine* gas—invented by Woufhausen—makes this possible.

The author has long been impressed with the need for a good vacuum-tube kit. There are radio and television receiver kits, amplifier kits, and test equipment kits on the market, but no tube kits. The complexity and expense of the equipment made such kits seem unfeasible. Fortunately, skilled design—and *Celosine*—have changed all that.

The various tube manufacturers have tried to keep this kit off the market, but the inventor—seeing the great need for such equipment—wouldn't let the radio technicians down. In spite of favorable offers, pressure, and even threats, he went ahead with production and sale of the kits.

The equipment contains bases, envelopes, filaments, grids, cathodes and plates. Extra parts can be ordered at a low cost when the items supplied with the kits are exhausted. The base cement is a new discovery almost as important to the new equipment as the *Celosine* gas. Heat has no effect on it, and it

dries immediately. Soldering the pins is of course no problem to the service technician.

After assembly and insertion of the *Celosine* gas the tube is inserted in the tester supplied with the kit. It is first set at "flash" and the filament heated. This fires the gas and evacuates the tube. The meter is set at "test" and the tube checked. If the needle (normally in neutral position) does not move, the tube can be assumed to be good. If it is poorly constructed or shorted the needle will drop back to indicate "Bad." If it swings up to "Good" the tube is better than average and can be used in critical circuit positions.

The tube evacuation pump is used only for rectifier tubes. It is self-contained with air which when squeezed, has a vacuum pulling power of 30.6; therefore no getter is used.

Fusing the glass envelopes to bases is very simple. The base cement furnished with the kit softens the glass like putty and adheres very well. Metal tubes are sweated together by using both cathode coating and base cement, which combined create a heat of 1,800 thermal units, making the materials very pliable.


Tube Kits, Inc., is at present overloaded, but is expanding its factory, and hopes to reduce its long waiting list in the near future. It will take considerable time for this product to reach the general market, so you will be well advised to order and wait. If estimated production is reached, you will probably receive your kit by next **APRIL FIRST** END

*Professor of Elektroniker and Noisivelet Engineering, Krausekopf-on-Rhine (Germany).

THE VERSATILE Neon Tube

By R. P. HAVILAND

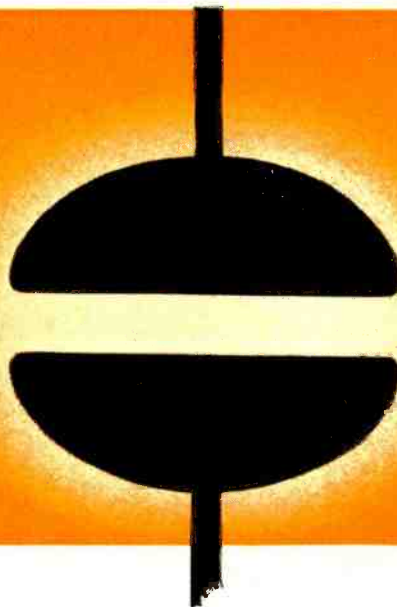*Voltage regulator—generator—
protector—and circuit tester*



ONE of the most useful components in electronics is the glow tube, also known as the glow lamp or neon lamp. One reason for this usefulness is the fact that it provides a link between electrical and visual phenomena; another lies in the electrical characteristics of the discharge.

Basically a glow tube contains two electrodes separated by a small gap and surrounded by a gas under reduced pressure. The gas is usually neon, although in some cases it may be argon or a mixture of these plus other rare gases. When a voltage of sufficient magnitude is impressed across the electrodes, the gas ionizes and current flows through the tube. This is accompanied by a visible discharge, which occurs as a glow covering part or all of the *negative electrode* or cathode.

The voltage-current relation in the tube does not follow Ohm's law. Instead, within limits, the voltage across the tube is almost independent of the current. A typical voltage-current relation is shown in Fig. 1. No discharge occurs until the voltage reaches a certain value, known as the *striking voltage*. Once the discharge has started, the voltage across the tube drops to the operating value. As current through the tube increases, the voltage rises very slightly until a point is reached at which the discharge changes from a glow to an arc. At this point the voltage rises rapidly. However, since the arc discharge damages the electrodes, tubes are normally not operated above the arc point. If the current through the tube is reduced, the voltage between the electrodes will drop below the operating value, and at a certain critical value the glow will disappear. This value is known as the *extinction voltage* of the tube.

Because of this nonlinear voltage-current characteristic, the glow tube must be supplied from a current-limited source if excessive currents are to be avoided. In the simplest case this is

obtained by a series resistor. The tube must always be operated from a source having higher voltage than the striking potential.

The color of the glow depends on the nature of the gas and the current. For neon the normal glow is a reddish orange, which becomes more yellow at high current. The color of the glow is also affected to some extent by the frequency of the currents, being more reddish for high-frequency currents. For argon the glow is a weak blue-violet, with an appreciable amount of ultraviolet radiation present. However, all but the lowest u-v frequencies (near violet) are filtered out by the glass of the bulb.

Available designs

Two general types of glow tubes are available at present. One of these is designed primarily for illumination and the other primarily for electrical applications (especially voltage regulation). These two types are electrically similar, although generally the illumination type shows considerably greater variation in characteristics. In general, the illumination type uses the same bulbs and bases as conventional lamps, while the electrical types use bulbs and bases similar to those used in radio tubes.

The illumination types are available in ratings from $\frac{1}{25}$ watt to 3 watts, and are supplied unbased and with four types of bases, which vary with the size of the bulb and the type of application. The electrical types are rated by *current*, which ranges from 2 to 40 milliamperes, and are available in three types of bases.

Important characteristics of commercial bulbs are given in Table I, and regulator tubes are shown in Table II. These show the type of base, the wattage rating, operating current, and voltage, the approximate striking voltage, value of built-in resistor if used, and the regulation where important. Note that only those tubes with screw-type bases have built-in resistors.

Circuit applications

One of the major applications of the glow tube arises out of its relatively constant voltage drop. The tubes are therefore useful for holding a voltage relatively constant regardless of load-current variations—within limits. This type of regulation is normally used for d.c., but may be used on a.c. voltages with some wave-form distortion.

Typical regulator circuits are shown in Fig. 2, together with design information for selecting the series-dropping resistor. In applying these circuits note that there must not be too great a variation in output current, since if the load current becomes too great, the drop in the series resistor will reduce the load voltage below the striking potential, and the discharge will stop. If the load current becomes too low there may be danger of tube damage due to an arc discharge.

In regulator service there is appreciable variation in output voltage from tube to tube. The output voltage is also affected by the past history of operation, external illumination, operating current, temperature, and age. For these reasons, gaseous regulator tubes should not be depended on to hold the voltage closer than within about 5% of the rated operating value. The only exception to this is the special high-stability 5651, which is rated at a stability of ± 0.1 volt. This stability is maintained only with constant current through the tube, and special circuits have been developed to meet this requirement.

The glow-tube a.c. regulator is not widely used, primarily because of low power-handling ability, and the poor waveform that it yields. It is useful wherever constant voltage is more important than these other factors. This regulator must use two tubes connected back-to-back if the tubes have different-size anode and cathode electrodes. Certain glow tubes have symmetrical electrodes, as shown in Table I, and there-

fore any single tube of this type may be used for a.c. regulation.

Since the glow tube has some of the characteristics of a resistor, it may be used in many places to replace a resistor. Some of these applications are shown in Fig. 3.

The voltage divider at *a* is constructed by operating glow tubes in series. With available types, voltage steps from about 50 up to 2,000 volts can be obtained. Care must be taken in design to keep the current through the top tube within the allowable operating limits. The requirements for this section are the same as for the simple voltage regulator shown in Fig. 2.

The characteristics of the glow tube also make it useful as a cathode-bias device (Fig. 3-b). The major limit on such use is the relatively large minimum-bias voltage of at least 60 volts which results.

A very useful circuit element may be constructed from a pair of glow tubes and a pair of resistors, connected in a bridge. See Fig. 3-c. This circuit will function as a discriminator, giving zero output for a certain voltage, *negative output* for input voltages less than this, and *positive output* for inputs greater than this. The input voltage for zero output is equal to the sum of the voltage drops across the two tubes, and can thus vary from 100 volts minimum up to several hundred volts or more if several tubes are connected in series in each leg. This circuit is useful for control applications.

The glow tube can also be used to couple the plate and grid circuits of an amplifier (Fig. 4), replacing the usual coupling capacitor or coupling resistor. In this application the gain of the amplifier may be made to approach the gain achieved with capacitor coupling. This method is often used in d.c. amplifiers.

Glow tubes are used widely as indicators, because of their high visibility, low power requirements, and low heat output. The types with internal resistors may be used directly on normal 110- and 220-volt power circuits exactly as conventional light bulbs are used. The other types require an external limiting resistance when used on power-line voltages, but may not require this on other circuits. For example, the tiny 1/2-watt tubes are widely used in binary and decade counters to indicate the count at the end of a counting cycle. Numerous applications of this type will be found in the literature.

Under some conditions it may be desirable to have an intermittent or flashing indication rather than a continuous glow. This can be obtained by connecting a small capacitor across the tube. The design of flashing circuits is discussed below under "Glow-tube Test Equipment."

A special application of glow-tube indicators is to show component failure. Small glow lamps are sometimes bridged across fuses to show when these are open. This is a considerable

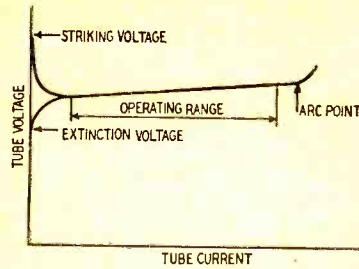


Fig. 1—Neon-lamp operating characteristic. Striking and extinction voltages vary widely for lamps of the same type.

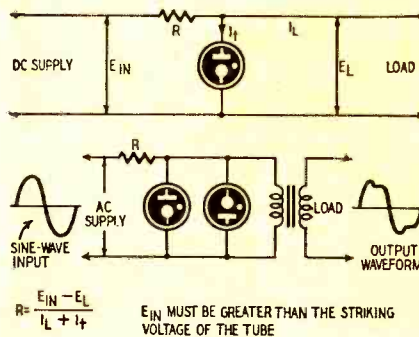


Fig. 2—Basic circuits for regulating d.c. and a.c. voltages with glow tubes.

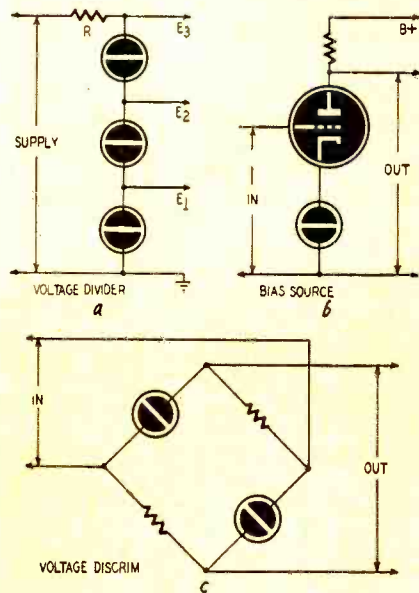


Fig. 3—(a) Neon-lamp voltage divider. (b) A neon lamp as a cathode-bias resistor. (c) Voltage-discriminator circuit.

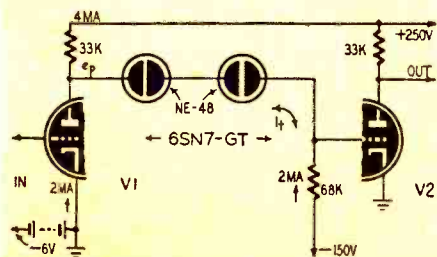


Fig. 4—Neon-lamp interstage coupling circuit for audio and d.c. amplifiers.

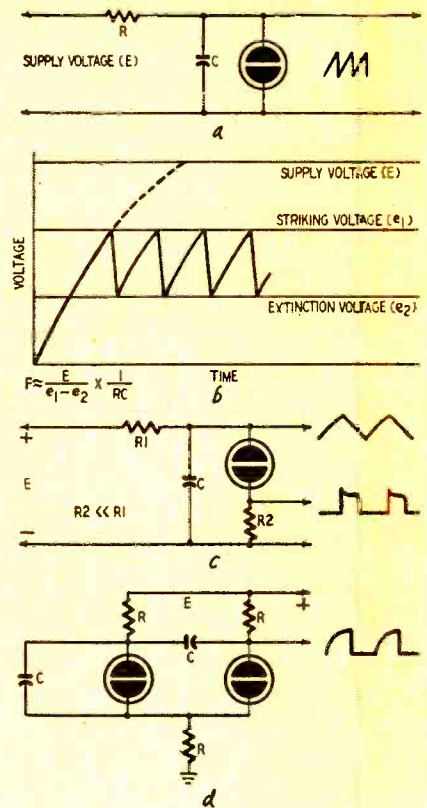


Fig. 5—(a) Neon-lamp relaxation oscillator. (b) Derivation of sawtooth waveform. (c) Dual-output oscillator yields pyramidal waves and trigger pulses. (d) Circuit for producing quasi-square waves.

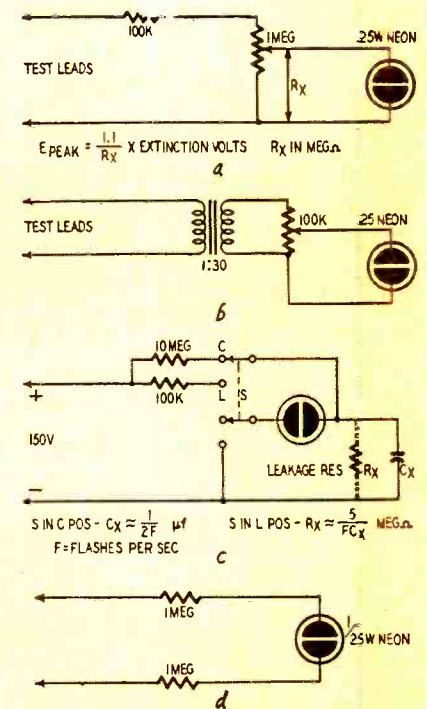


Fig. 6—(a) Simple slideback voltmeter. (b) Neon-tube output indicator. The transformer steps up low voice-coil voltages to the striking potential of the tube. (c) Combination capacitance-leakage-resistance checker. (d) Circuit tester.

Table I—Glow lamps for lighting and indicator service.

Type	Base	Wattage	Max. Current (ma)	Approx. Striking Voltage	Internal Resistor	Electrodes	Remarks
NE-2	Leads	1/25	0.5	90	None	RR	
NE-51	SC	1/25	0.5	90	None	RR	
NE-15	SC	1/25	0.5	90	None	RR	
NE-20	SC	1/25	0.5	80	None	RR	
NE-21	SC	¼	5	70	None		
NE-48	DC	¼	5	90	None	PP	
NE-45	Cand.	¼	5	90	30,000	PP	110 volts
NE-16	DC	¼	5	87	None	PP	d.c. only
NE-17	DC	¼	5	70	None	PP	
NE-57	Cand.	¼	5	70	30,000	CW	110 volts
NE-58	Cand.	½	10	90	100,000	PP	220 volts
NE-29	DC	½	10	105	None	CW	a.c. only
NE-32	DC	1	20	85	None	CW	
NE-30	Edison	1	20	85	7,500	CW	110 volts
NE-31	Cand.	1	20	85	7,500		110 volts
NE-56	Edison	1	20	85	33,000	CW	220 volts
NE-36	DC	2	40	85	None	PP	
NE-34	Edison	2	40	85	3,500	PP	110 volts
NE-40	Edison	3	60	85	2,200	PP	110 volts
NE-42	DC	3	60	85	None	PP	
AR-1	Edison	2	40	90	3,500	PP	Argon
AR-2	DC	2	40	90	None	PP	Argon
AR-3	Cand.	¼	10	115	15,000	PP	Argon
AR-4	DC	¼	10	115	None	PP	Argon

SC—Single-contact miniature bayonet base.
 DC—Double-contact candelabra bayonet base.
 Cand.—Candelabra screw-base.
 Edison—Edison screw-base.

RR—Both electrodes are rods.
 PP—Both electrodes are plates.
 CW—One electrode is cylinder and the other is wire.

Table II—Voltage-regulator and protective glow-lamps

Type	Base	Current (ma)	Operating Voltage	Supply Voltage	Regulation Volts	Remarks
0A2	7 pin button	5-30	150	185	2	6073 similar
0B2	7 pin button	5-30	108	133	2	6074 similar
1B47	7 pin button	1-2	82	225		
874	4 pin medium	10-50	90	125	7	
991	DC bayonet	1-3	48-67	87	11	
1265	Octal	5-30	90	130		
1266	Octal	5-40	70			
5651	7 pin button	1.5-3.5	82-92	115		Stability 0.1 volt
6073	7 pin button	5-30	150	185	2	Premium type
6074	7 pin button	5-30	108	133	2	Premium type
0A3/VR-75	Octal	5-40	75	105	5	
0B3/VR-90	Octal	5-30	90	125	6	
0C3/VR-105	Octal	5-40	105	135	4	
0D3/VR-150	Octal	5-40	150	185	5	
VXR-130	Leads	1-2.5	130	160	5	Subminiature
5841	Leads	2-50	900	930		Corona type
5950	Leads	2-50	700	730		Corona type
5962	7 pin button	5-55	700	730		Corona type
6143	Leads	2-100	1,200	1,230		Corona type
6119	Leads	2-50	2,000	2,100		Corona type

Note: While these data have been checked for accuracy, it is recommended that manufacturers' literature be consulted for data in critical applications.

time saver in trouble-shooting. Other applications are possible: For example, it would be possible, by judicious design, to have a single glow tube associated with each vacuum tube in a circuit.

These could be arranged to show no glow if the tube fails to draw current, a normal glow if the tube draws normal current, and a more intense (or even a flashing) glow if the tube draws excessive current. A very great and almost untouched field in the design of electronic equipment exists in this type of application.

Special glow tubes

A number of glow tubes of special design have been made in the past, although most of these have gone off the market due to improvements in other techniques. An example is a voltage regulator-potential divider combination which has been used in Europe for quite a number of years. This multielectrode tube was designed to have a drop of approximately 60 volts between each adjacent pair of electrodes. Thus a single tube replaced the conventional resistance voltage divider, with improved regulation characteristics.

Another type, since discontinued, was used as a tuning indicator in a number of early radio-receiver designs. In this tube one electrode was considerably longer than normal. Increasing current caused the glow to extend further along this electrode, furnishing a visual indication of the amount of current flowing, and thus indicating relative signal strength. This same tube was also used as a simple oscilloscope, with the time base furnished by a rotating mirror. This design became obsolete as the cathode-ray oscilloscope was improved.

Other special designs are widely used for photoflash units. These tubes are designed to carry very large peak currents and to give a high light output. Photographically these are quite useful because of the short flash duration possible.

The argon tube, which yields a small amount of near ultraviolet light, also has special applications. One of these is in photo printing, where a number of argon tubes are mounted in a grid under a contact printer. These are generally arranged so they can be switched on and off individually for "dodging". The ultraviolet radiation from argon tubes is also used to excite fluorescence in mineral specimens.

Glow-tube test equipment

The factors that make the glow tube useful as a circuit component also make it useful as a test element. A number of designs based on these factors are shown in Figs. 5 and 6.

When connected as shown in Fig. 5-a, the glow tube makes a useful oscillator. As shown in Fig. 5-b, the output is a sawtooth wave, which will be almost perfectly linear if high supply voltages are used. The oscillation frequency may

HIGH-SPEED SERVICING

Checking Tubes and Capacitors First Saves Trouble-Shooting Time

By FAIRBANKS TRYON

be computed from the equation given in the figure. The exact frequency will vary considerably, due to the relatively poor regulation of the tube and normal differences in commercial glow-tube characteristics.

The sawtooth output may be modified by introducing additional elements. For example the circuit of Fig. 5-c will yield a pyramidal wave at the top terminal and a trigger pulse at the lower terminal. The circuit shown in Fig. 5-d will give an output approximating a square wave. Other connections are possible which will yield a variety of waveforms.

When connected as shown in Fig. 6-a the glow tube may be used as a voltmeter. The potentiometer is adjusted until the tube just ceases to glow. The potentiometer may be equipped with a calibrated scale showing the multiplication factor by which the extinction potential of the tube must be multiplied to give the unknown voltage. This circuit is reasonably accurate, being almost as good as a pocket voltmeter, and is usable and safe over the range of about 50 to 500 volts a.c. or d.c. This circuit is also a polarity indicator, since only the negative electrode will glow on d.c., while both electrodes will glow on a.c.

This same circuit may be used as an output meter for aligning radio receivers. For this application the potentiometer would be set to give a small glow which would then increase or decrease in intensity with the aligning adjustments. When used across speaker terminals, a step-up transformer will be necessary, as shown in Fig. 6-b, to raise the output voltage to a value greater than the striking potential of the tube.

The glow tube is also widely used as a test device to show the presence of r.f. current. If the r.f. field is strong enough, it is not necessary to have a continuous path through the tube. Thus it may be used to show the presence of power on an antenna; to check the standing wave pattern on a transmission line; or as an indication of proper neutralization by coupling the neon tube to the output circuit of the stage being neutralized *with the plate supply disconnected*, and adjusting the neutralizing controls for *minimum* output.

When connected as shown in Fig. 6-c—with the switch in C position—the glow tube becomes a useful capacitor checker. The value of the capacitor can be determined by counting the number of flashes per second. With the switch in position L the lamp indicates leakage resistance.

Finally, if provided with an internal resistor and a pair of test probes (Fig. 6-d), the glow tube becomes a very useful universal tester. With a little experience it is possible to estimate the voltage reasonably well, to determine polarity, and to determine whether the voltage is a.c. or d.c. (See "Quick Capacitor Checker," by George Kelly, in RADIO-ELECTRONICS, January, 1953.)

END

FOR the past 12 years I have used a system of radio servicing which has enabled me to repair 95 of every 100 sets in an average of one hour. The paramount rule is: **Do not plug the set in—fix it first.** The system is simple. Master it and you can work faster and more efficiently with a minimum of equipment. Follow these rules and see how simple most servicing jobs can be:

1. Do not plug the set in. Fix it first.

A.c.-d.c. sets having 150-ma tubes are the most common. If the set is new, the customer may be right when he says that the set has a loose wire or a burned-out tube.

a. Without removing the chassis, turn the switch on, set your ohmmeter to its lowest range, and measure the resistance between prongs of the line plug. No reading indicates an open line cord or a burned-out tube. If the set has a 117-volt pilot lamp, a reading of 250 to 300 ohms indicates an open heater.

b. Don't stop to check the tubes. Save 20 minutes. Pull the rectifier tube. Check continuity between pins 2, 3, and 7 on a 35Z5-GT; 3, 4, and 6 on a 35W4; 1 and 6 on a 25Z5, or 2 and 7 on a 25Z6. Replace the tube if there is an open circuit between any two points. If the rectifier is good, check heaters of the remaining tubes until you find the open one. Replace the bad tube.

c. Check the resistance across the line plug. Plug in the set if the meter shows approximately 150 ohms (70 to 100 ohms with a 117-volt pilot) or 250 to 300 ohms in sets having 6- and 25-volt tubes of the 300-ma variety.

d. If it works and sounds O.K., bounce it twice on the bench. If you don't hear microphonics or noise, return the set to the customer.

2. The procedure for a.c. sets is slightly different.

a. If the set is new, check all tubes on the checker. On an old set, check only the rectifier. Use the ohmmeter on the other tubes. If any tube is burned out in a new set, that may be the only trouble.

b. If the rectifier shows little or no emission, the chances are 10 to 1 that something else is wrong.

c. While the rectifier is out of its socket, set the ohmmeter to the 20,000-ohm range and measure resistance between the filament (cathode on heater-type tubes) and ground. A low reading indicates leaky or

shorted bypass or filter capacitors.

d. If the resistance between rectifier filament and ground is reasonably high, you can check the set on the a.c. line. Hang onto the plug and be ready to yank it if the rectifier tube shows anything except the usual orange glow from the filament. This saves the rectifier tube if anything is wrong.

3. This step applies to any type of set in which the trouble was not located in steps 1 and 2.

a. Remove the chassis.

b. Check all tubes which were not checked previously. Check all filters.

c. Use the ohmmeter to measure resistance between each plate and ground.

d. Look for burned resistors, loose or shorted wires, solder shorts, etc. Use a flashlight to look at all connections.

It takes only a few minutes to perform these three steps on most sets. In this time you will have repaired about half of the sets coming in. If you are still stuck with the set, don't reach for the aspirin bottle.

4. Set the ohmmeter on the 20-megohm range (the 30-megohm is better).

a. Start taking capacitors loose at one end and applying the ohmmeter. If there is no deflection, look closely, reverse the prods, and try again. No deflection—except on very small capacitors—indicates the possibility of an open capacitor. If the meter reads below 20 megohms, the capacitor is leaky and must be replaced. You will find most of the leaky capacitors in the circuits of tubes which checked weak.

b. If the speaker has a field coil, check it for an open or short to ground.

c. Check the speaker socket for loose contacts.

By now you will have removed and replaced all shorted or leaky capacitors so you can check the set on the line without fear of damaging any tubes which you may have replaced. Any set which has not been repaired by following these four steps will probably be a hard nut to crack. Look for smoke, feel overheated resistors, smell, check voltages, and measure resistances. Drag out the signal generator, scope, signal tracer, or what have you. Keep up the fight with no holds barred.

END

NARROW GAUGE Motion Pictures

present a new field for the versatile electronic technician and service dealer

By **RONALD A. LANE**

OPPORTUNITIES for the technical and business skills of radio technicians are expanding rapidly in the field of narrow-gauge motion pictures. This field has extended enormously in the past year, largely because of the introduction of magnetic soundtracks. These give the narrow-gauge film a versatility and flexibility not possible with the optical tracks previously used. This dramatic increase in the value of the medium was naturally accompanied by an increase in the demand for it. That demand is still growing.

The opportunities for radio technicians include servicing, especially electronic servicing. Every narrow-gauge sound-film projector contains an audio-frequency amplifier. This is excited by the soundtrack. Optical soundtracks are reproduced by a photoelectric cell, the output of which becomes the amplifier input signal; magnetic tracks are similarly reproduced by a magnetic "head". All magnetic sound projectors embody provisions for erasing an existing soundtrack and recording a new one. Because of this, microphones are now normally associated with narrow-gauge projectors. A loudspeaker (or speakers) completes the electronic equipment. All of them need more or less servicing and maintenance, and the electronic technician is qualified for this work.

Circuit schematics are always available in the manufacturer's instruction book. Tubes, resistors, and the like are standard; only the magnetic erase and playback heads are apt to be specific products of the projector manufacturer.

Aside from electronic circuits, narrow-gauge film projectors always incorporate simple electrical wiring for the projection lamp, the drive motor,

switching, and appliances. These also must be serviced occasionally.

Other opportunities include owning equipment and renting or leasing it out for use; and acting as agent both for the equipment and for the narrow-gauge film.

Fig. 1 shows a standard 16-mm projector. There are two general types of narrow-gauge motion picture film, 16-mm and 8-mm. The former is by far the more important at present. These film widths, 16 and 8 millimeters, were chosen originally to avoid arithmetical relationship with the 35-mm film, which is the standard commercial type used in motion picture theaters. This was done for a very important reason.

A safety measure

Commercial film was (and to some extent still is) a very dangerous and almost explosive product. Its base is cellulose nitrate, not nitrated far enough to be as unstable as guncotton, but far enough so that if it catches fire, water can't put it out. Neither can the fire be smothered by depriving it of air. The material supplies all the oxygen needed. Highly poisonous fumes are given off when the stuff burns—nitric acid fumes that rot the lungs. For these reasons, many legal precautions surround the use of commercial film in theaters.

Narrow-gauge film has always been made of "safety" stock. This base, cellulose acetate, is no more dangerous than paper. At first, a narrow-gauge width of 17½ millimeters was proposed, but this would have left an opportunity for unscrupulous characters to split 35-mm nitrate film in half and offer it as safety film. Therefore 16-mm was chosen as the first narrow-gauge stand-

ard. Later, when invention and improvement made still smaller and still less expensive film practicable, 8-mm film was chosen. This was conveniently obtained from 16-mm, and no harm could result since no dangerous 16-mm stock has—to the writer's knowledge—ever been manufactured.

At present, as said, by far the greater opportunities in the narrow-gauge field lie with 16-mm. Fig. 2 illustrates two of the general types of film now used. They differ as to soundtrack, not otherwise. Those shown here have either magnetic track alone, or both magnetic and optical track, either of which can be played at will. Other 16-mm types, not pictured here, have only optical soundtrack or no sound at all. These last, relics of the nearly forgotten days of silent pictures, can now be modernized by processors who "strip on" a blank magnetic ribbon. The owner then magnetically records any sound he wants.

Scope of usefulness

The field of 16-mm activity ranges from near-theatrical equipment and audiences down to living-room and amateur scale. Users include business firms, schools, churches, small theaters, private individuals, and television studios.

Most of these users benefit greatly by the fact that magnetic recording now permits them to add their own sound accompaniment. A business firm may need one soundtrack for an audience of potential customers and an entirely different track when showing the same film to a convention of its own salesmen. Teachers in school or Sunday school often want to use the identical film with a different narration suited to the age level of each class. A foreign-

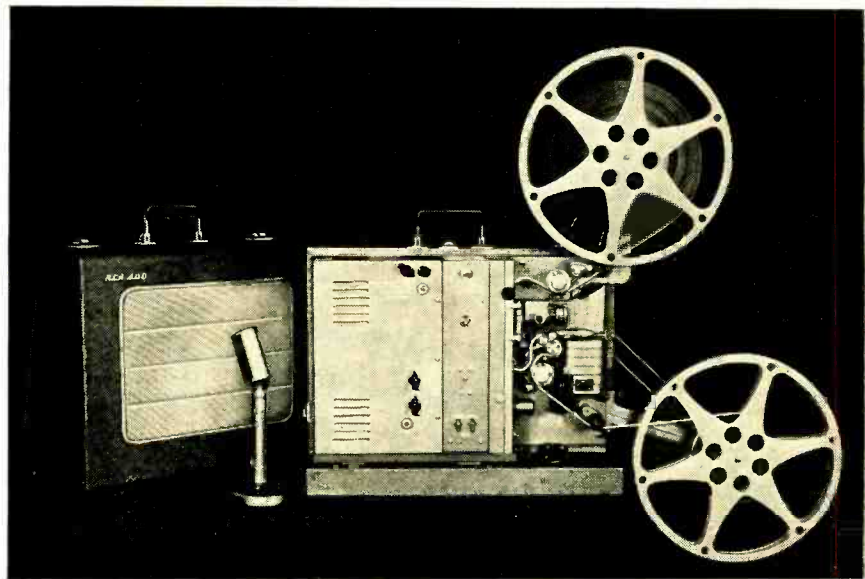


Fig. 1—RCA 400, a standard home-type moving-picture projector of the kind described in this article.

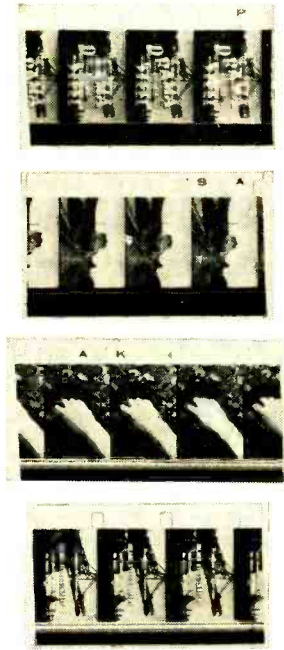


Fig. 2—Magnetic sound is a broad dark strip; optical, a jagged white line.

made film, with its own language optical track, may be given an additional (magnetic) recording in English, either of which can be played at will; both may be played alternately in a foreign-language class.

A radio technician who contemplates entering the 16-mm field may want first of all to inquire if there are enough users of such equipment in his vicinity to justify the step. Following is a somewhat detailed list of those who use this apparatus and for what purposes. These institutions and persons may be checked by questionnaire or direct approach:

Industrial and business firms use 16-mm for several purposes, such as training employes in manufacturing operations, training foremen and supervisors, and entertaining employes during lunch hours and other rest periods. Sales and advertising use of 16-mm motion pictures has already been mentioned. In addition to motion pictures, film strips—which are sequences of still pictures shown one after another and accompanied by explanatory sound from a record player or tape player—are also used for sales and advertising purposes.

Schools use 16-mm motion pictures extensively for instruction. The advantages of placing before the student a vivid, moving presentation of a foreign country or historical occurrence are obvious. Cartoon films teach abstract concepts: for example, the physics class may learn the action of a vacuum tube by seeing “electrons” move through space and rush ahead or slow down or turn back, in response to changing accumulations of electrons in a grid wire. Schools also use film strips in addition to motion pictures.

Churches use films for religious instruction and the same equipment with

a different film for entertainment at “socials,” gatherings and festivals.

Stores and other places of business sometimes use 16-mm to entertain or attract customers, especially if they consider available TV programs not attractive enough to their particular clientele.

Individuals use 16-mm for home movies, for their own amusement, or to entertain guests. Perhaps the most attractive home use is at children’s parties, for the youngsters seem delighted and thrilled to have movies at home instead of in a theater; most small fry feel that this is something ultra-special.

Operating the equipment

Operating 16-mm apparatus is basically simple. Detailed instructions are always given in the manufacturer’s instruction book which accompanies every unit sold. There are three general processes: projecting the film, picture and sound; then rewinding the film back on the original reel so it can be projected again; and using the projector as a recorder to make a new magnetic recording.

Putting the film into the machine is called *threading*. Manufacturers simplify this as much as possible. In the equipment of Fig. 1, the path the film must follow is indicated by a curving rib on the main-frame casting. The user threads the film through the various parts in exact parallel to that rib. In other common equipment the film path is shown on a diagram inside the projector door. The details of engaging the film sprocket holes in the sprocket-wheel teeth, and of opening and relocking the *gate, shoes*, and other items that restrain the film from leaving its proper path, differ with each make of machine, but are thoroughly explained in each manufacturer’s instruction book, usually with the help of many pictures.

Functional details

How the electronic portions of the equipment operate will be obvious to every radio technician, but the optical and mechanical details may be less familiar. They are not very complex.

A motion picture film consists of a series of photographs of progressive stages of action. When these are exposed to the eye in rapid succession the illusion of motion is produced. In a projector, they are exposed by passing them, one at a time, through a strong beam of light. Each is thus presented as an appropriate pattern on a viewing screen.

The film unwinds from an upper reel, passes through the mechanism, and is taken up on a lower or *takeup* reel. A row of holes, called *sprocket holes*, runs along one side of the film—the side opposite to the soundtracks. In the mechanism are toothed wheels called *sprockets* which engage the sprocket holes and thus move the film along.

The film is pulled down from the upper reel by a *pull-down sprocket*.

Thence it proceeds to the *gate*. It slides downward through the gate, rigidly positioned by guides. But it must not move continuously through the gate, because this is the place where light shines through it to project the picture. It must remain motionless in the gate while one picture is projected, then move downward, and again remain motionless while the next is projected; its motion through the gate is therefore *intermittent*. This motion is created by one of two devices; either there is a shuttle-action “*claw*” with sprocket-teeth on it, or an intermittently moving sprocket wheel just below the gate. The claw is more common than the intermittent sprocket. A projector has either one or the other, never both.

After film has passed through the gate the intermittency must be filtered out of its motion, for if permitted to remain it would produce frequency modulation in the sound. Therefore the film is looped around one or more sprockets or other mechanical damping devices. A steady, unvarying motion is necessary where it passes the photoelectric cell or magnetic reproducer.

The takeup reel is driven by a slipping clutch of some kind, usually of felt or leather, for its speed of rotation must vary in accordance with the amount of film wound up on its hub at any given moment.

One additional part that every projector must have, not yet mentioned, is the shutter. The film must be pulled downward 24 times in each second, and the light must be cut off while this happens. A rotating shutter intercepts the light during the pull-down interval. However, a 24-cycle-per-second light frequency would be plainly visible as a highly annoying flicker. Therefore most shutters are provided with two blades, and intercept the light a second time halfway through each period of exposure. The resultant 48-cycle flicker is not annoying and is practically invisible. One make projector uses a single-blade shutter revolving at double speed to achieve the same optical effect by projecting 48 separate images every second.

Finally there is always a *framing* device. (A single picture is called a *frame*.) The film is always so threaded that one frame fits squarely opposite the aperture through which the projection light shines. Otherwise the screen would show the top part of one image and the bottom part of the next one. In spite of careful threading, the picture may “get out of frame” during the showing because of faults in either the mechanism or the film. Mechanical means for correcting the condition without stopping the show are built into every projector.

The service technician will find these machines—intended for the unskilled operator—easy to understand and work on. The second part of this article will deal with their servicing, both electronic and electro-mechanical.

(TO BE CONTINUED)

R-E'S ASSOCIATE EDITOR REPORTS ON PENNA. U.H.F.



F. D. Coslett (center) and Milan J. Krupa (right) interview editor.

MAINTAINING its policy of bringing its readers first-hand information on new developments, RADIO-ELECTRONICS sent its Associate Editor Mort Bernstein on a second visit in January to new u.h.f. TV areas in Pennsylvania. Besides studying u.h.f. problems, he was invited to speak at meetings of local service organizations in Wilkes-Barre and Scranton.

The success of the visit to Wilkes-Barre was largely due to the enthusiastic co-operation of Milan J. Krupa, Secretary of the Radio Servicemen's Association of Luzerne County, and Chief Engineer of WBAX. Mr. Krupa not only handled all the details of the meeting, but made it possible to study operating problems at Wilkes-Barre's new u.h.f.-TV station WBRE-TV, and arranged to have Bernstein interviewed on WBRE-TV's main evening news program. He even got us excellent hotel accommodations in spite of a shortage due to exceptional local business activity.

As a result of the interview—which was held at about 6:30 p.m., with 100% potential audience coverage—the meeting was attended by a much larger number of Association members than expected, as well as by several non-members whose interest had been aroused by the telecast.

After the meeting Messrs. Krupa and Bernstein prepared a press release to be published the following day (January 21) in final editions of the Times-Leader, Wilkes-Barre's evening paper with the largest circulation.

On the morning following the meeting R-E's Associate Editor visited WBRE-TV's transmitter and learned about the difficulties the station has been having with equipment (see technical report, column 3). Later that day the TV interview was restaged for still photographs. These were taken by Dick Paul, of the Wilkes-Barre Junior Chamber of Commerce.

In spite of hazardous weather conditions on January 21, which prevented

many members (including Secretary Leon Helk) from attending, and a last-minute change in location due to a "Scranton Home Industries" show which had taken over the original meeting hall, the Scranton meeting of the Lackawanna Radio Service Engineers was exceptionally well attended. As in Wilkes-Barre, Bernstein spoke on business methods and ethics, and u.h.f.-TV service problems. After the formal session, he explained the operation and characteristics of transistors and described some of the recent developments in transistor-operated equipment. (The audience was particularly enthusiastic about this.)

In both Wilkes-Barre and Scranton, technicians attending the meetings were eager to get the speaker's attitude toward licensing. Open discussions brought out the fact that they were unanimously for it.

In any event, both organizations did their best to indicate that they had got a good deal out of the talks.

U.h.f.-TV Problems

The impression gleaned from this trip and recent visits to York and Williamsport, Pa. (P. 102, RADIO-ELECTRONICS, March, 1953) is that u.h.f.-TV troubles are divided about equally between the transmitters and the receivers.

In York, just at the height of the critical period when harassed service technicians were struggling to install and check a tremendous number of u.h.f. converters and new u.h.f.-v.h.f. receivers on the one local station, the transmitter's sound carrier went haywire. A defective crystal oven sent the oscillator frequency down to the point where it was modulating the video carrier, and sound herringbones were all over the received picture. No sound could be heard at all in intercarrier sets. (The difference between the sound and picture carriers was no longer exactly 4.5 mc.) Of course, once this transmitter trouble was cleared up conditions returned to normal, but

there was a period of several days that had technicians frantic.

In Wilkes-Barre, transmitter troubles were far more numerous and serious. Many units of brand new studio equipment were defective when received from the factory. Weak and burned-out tubes, unsoldered and incorrect connections, shorted or leaky capacitors—were found in cameras, monoscope, sync generator, and other units. Even after returning these to the factory they came back with some of the original defects still in them. Instruction books and schematics for many of the units were missing.

One main terminal block forming a junction between several pieces of control equipment was wired painstakingly according to the diagram. Over 50 separate leads from multiconductor cables had to be cut to exact length, trimmed, laced, dressed, and soldered. When the job was completed, checked, and double-checked, the units failed to work. Finally, after the station engineers made a trip to the factory in desperation, it was discovered that the identifying numbers on the terminal block had been stenciled incorrectly—completely reversed, in fact.

Of course, all these problems were solved—had to be—before the station went on the air. Even bigger headaches showed up after transmissions started. WBRE-TV's u.h.f. transmitter uses lighthouse-type triodes in the final amplifier. These are tuned by cavity resonators which are pretuned and sealed at the factory and labeled "Do not adjust!" Tubes failed to load up properly, ran red hot, and cavities began popping. Even after more than three weeks' operation and testing by the manufacturer's own engineers, the solution had not been found. The only way to keep the station on the air was to operate at less than one-fourth normal power. They were down to one spare tube—the last one in the country.

Other troubles showed up in the transmitting antenna. The designer failed to include de-icing equipment,

VOLTAGE AMPLIFIERS in CONTROL CIRCUITS

By RONALD L. IVES

MORE than one owner of an all-wave or communications receiver has wanted to operate auxiliary equipment with the band-switch, but has been stymied by the lack of room for an additional switch wafer. Some have tried to operate a.c. relays in parallel with the band-indicator lights, only to find that the heater winding which supplies the lights had insufficient spare capacity, or that the leads from the lamp circuit to the relay introduced hum into the system.

Zero-drain a.c. relays are in about the same category as d.c. transformers, so some other method is needed if we are going to operate from the band-indicator light system. It should draw negligible current and introduce no hum. The method of Fig. 1 meets these specifications and (with voltage-multiplying circuits where necessary) will operate satisfactorily in a number of applications where it is necessary to actuate a relay from a low-voltage, low-current source. A triode with a suitable relay in its plate circuit controls the external auxiliary equipment. The plate relay can be any convenient standard type, such as a 10,000-ohm Potter and Brumfield LM-11 or equivalent.

Rectifier circuits shunted across the band-indicator lights are shown in Fig. 2. Commonly called voltage multipliers, they are actually voltage multipliers, with a theoretical output of approximately 1.4 times the line voltage times the number of sections employed. Because of circuit losses the voltage obtainable is always less than the theoretical value; and voltage gain per section declines as the number of sections is increased, all other factors remaining the same. Voltages shown in Fig. 2 are those actually obtained in a 60-cycle circuit.

For circuit simplicity, these control circuits are designed to cut off the relay tube when the circuit is "live." This

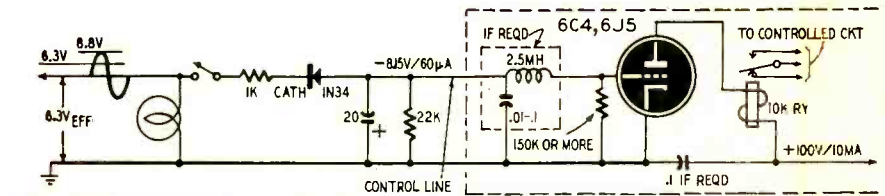


Fig. 1—Remote-control circuit uses low-voltage d.c. obtained from 6.3-volt band-indicator-lamp circuit.

also—in many instances—equalizes the power drain on the supply of the auxiliary device. Reverse operation, so that the relay pulls in when the control circuit is live, is entirely practicable, but usually requires more complicated relay-tube circuitry.

When the same device must be operated from more than one band-indicator light, the rectifier can be fed from the center tap of a high-resistance jumper between the hot terminals of the lights, as in Fig. 3. Output voltage will be approximately half that of the same rectifier fed from a single light. The same principle can be extended to any number of lights, with a corresponding reduction in output voltage.

Additional filtering is usually not necessary, but when needed must be isolated from the voltage multiplier by a high impedance. A large capacitor directly across the output of a tripler, for example, acts as an a.c. shunt, as shown in Fig. 4, and reduces the output voltage greatly. Because of low current drain, isolation with a high resistance is entirely satisfactory.

Circuit constants of rectifiers of this general type are not critical, and components have a long service life. Two triplers have been in service for more than 2,000 hours with no component failures. Rectifier bulk is small, a tripler with standard components occupying about as much space as a pack of cigarettes. All components need not be in the same place, provided they are kept away from low-level audio circuits. END

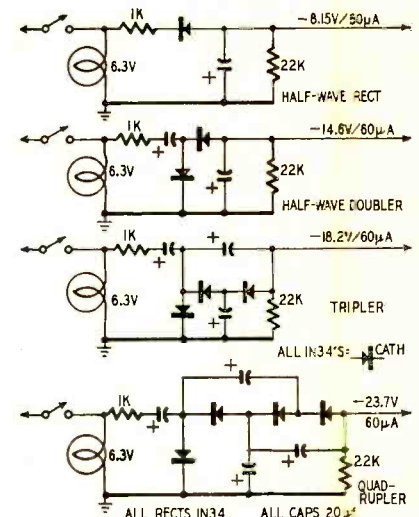


Fig. 2—Basic circuit and multipliers.

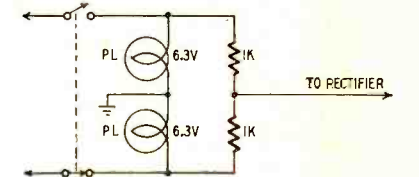


Fig. 3—Circuit for two-band control.

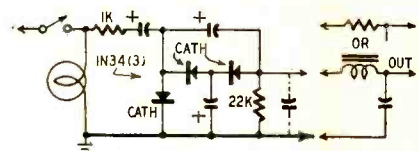


Fig. 4—Extra filter capacitance must be isolated as shown to reduce loading.

and the first sleet storm put the station off the air. (Apparently there is a considerable difference in winter weather conditions between Wilkes-Barre and York, although these two cities are only about 100 miles apart. The Wilkes-Barre antenna is about 2,000 feet above sea level, and much more subject to freezing.)

Still more troubles had developed in the microwave pickup units. WBRE-TV has been able to bypass these successfully when necessary with the aid of a v.h.f. standby receiver and a super-duper rhombic antenna beamed at New York, and picking up signals directly from the Empire State Building.


Receivers and their troubles

The chief problem has been oscillator radiation from u.h.f. converters. When one of the units goes on the air (literally) it can blank out v.h.f. reception over an entire neighborhood.

Since there are no tubes available commercially at the present time which can amplify effectively over the frequency range 470-890 mc, these converters have no r.f. stage between mixer and antenna. As a result, a large part of the oscillator output goes up the flue—and spreads a pall of interference over a wide area when the converter oscillator operates in the v.h.f. TV band.

As an illustration: The oscillator in a u.h.f. converter with output on channel 6 will tune from about 97 mc to about 200 mc in covering the entire u.h.f. band. (The fourth harmonic of the oscillator—roughly 388 to 800 mc—beats with the incoming signal to produce the channel-6 difference frequency.) At the low end of the u.h.f. band the second harmonic of the oscillator (194 mc and up) falls right on v.h.f. channels 10 to 13. At the high end of the u.h.f. band the oscillator's fundamental will do the same thing on v.h.f. channels 7 to 10. Some one-channel converters and turret-tuner u.h.f. strips cause similar troubles. END

LONG DISTANCE FM RECEIVER

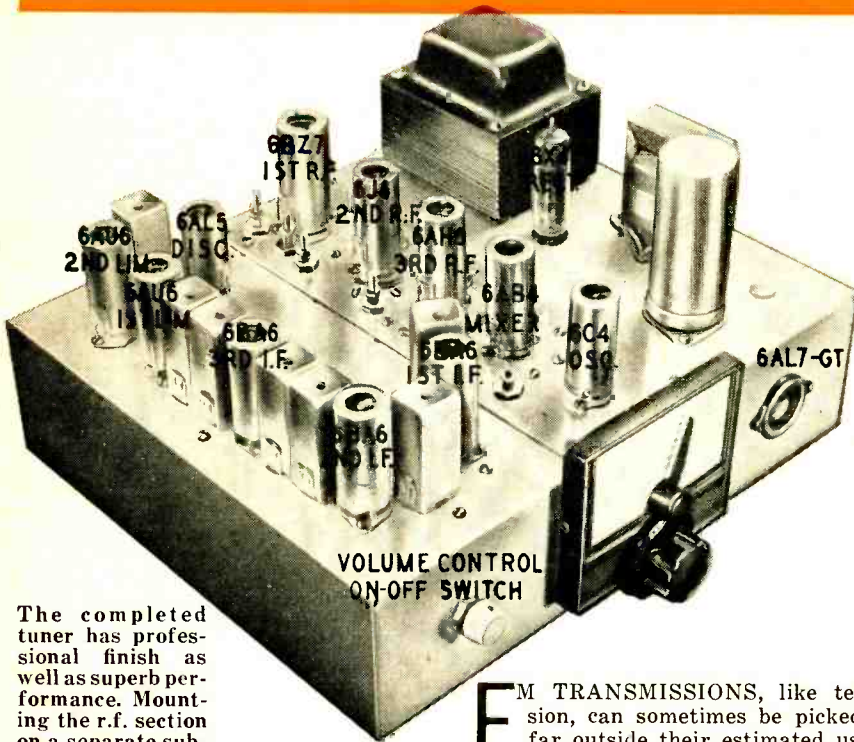

The completed tuner has professional finish as well as superb performance. Mounting the r.f. section on a separate sub-chassis simplifies construction and makes future modifications easy.


FM TRANSMISSIONS, like television, can sometimes be picked up far outside their estimated useful service areas. Today, thanks to recent developments widely used in television receivers, it is possible to build an FM receiver which has the high sensitivity and extremely low noise level necessary to give consistent, satisfactory reception over long distances.


Three low-noise r.f. stages and bandpass-coupled i.f.'s solve a receiving problem

By **WILLIAM H. KUMM**


These advances are the cascode circuit, the neutralized push-pull-triode r.f. amplifier, and the "elevator" transformer. By incorporating these in the front end—plus an unusual band-pass-coupled i.f. amplifier—the receiver gain and selectivity can be raised to such a high level that a station 85 miles away can be brought in day after day without the slightest interference from either of two "local" stations on adjacent channels.

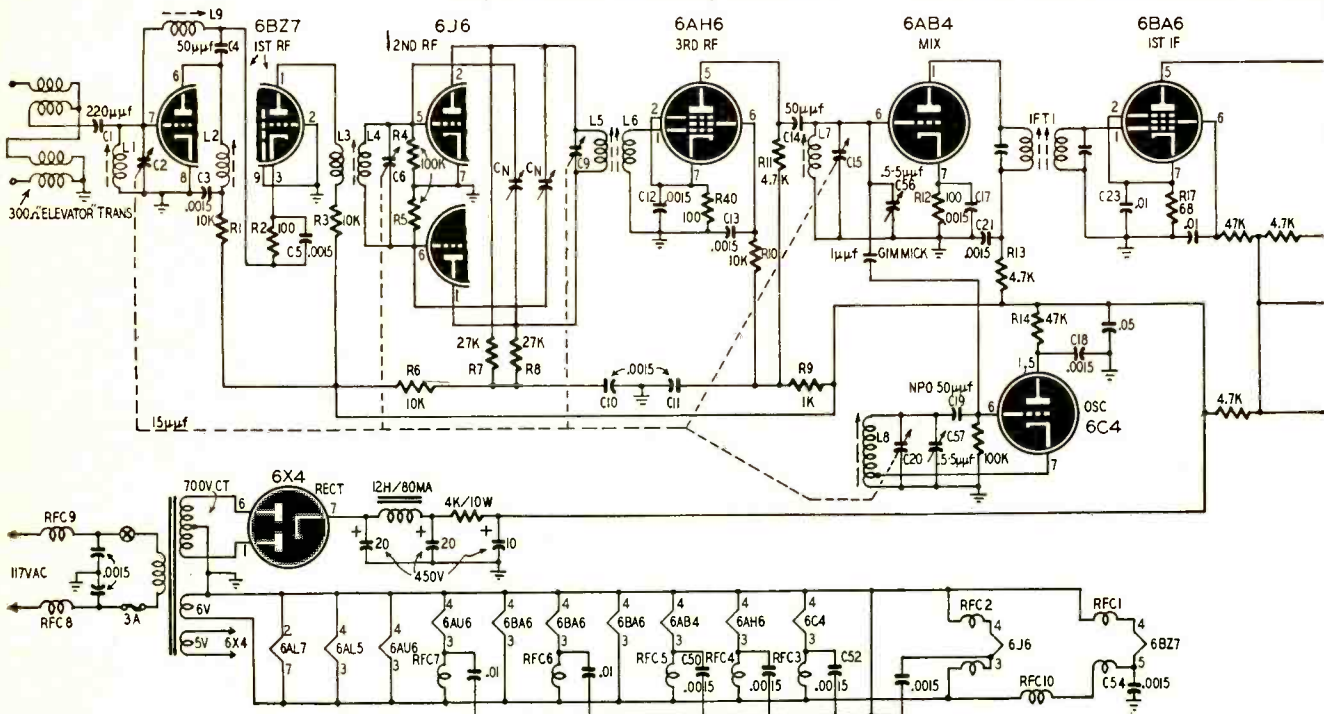Receiving conditions at Amherst, Mass., will illustrate the problem and show how—after much experiment—very satisfactory results were obtained. The desired transmission on 95.9 mc originates in Woburn, Mass. (just outside of Boston), almost due east of Amherst. The power output is 5,000



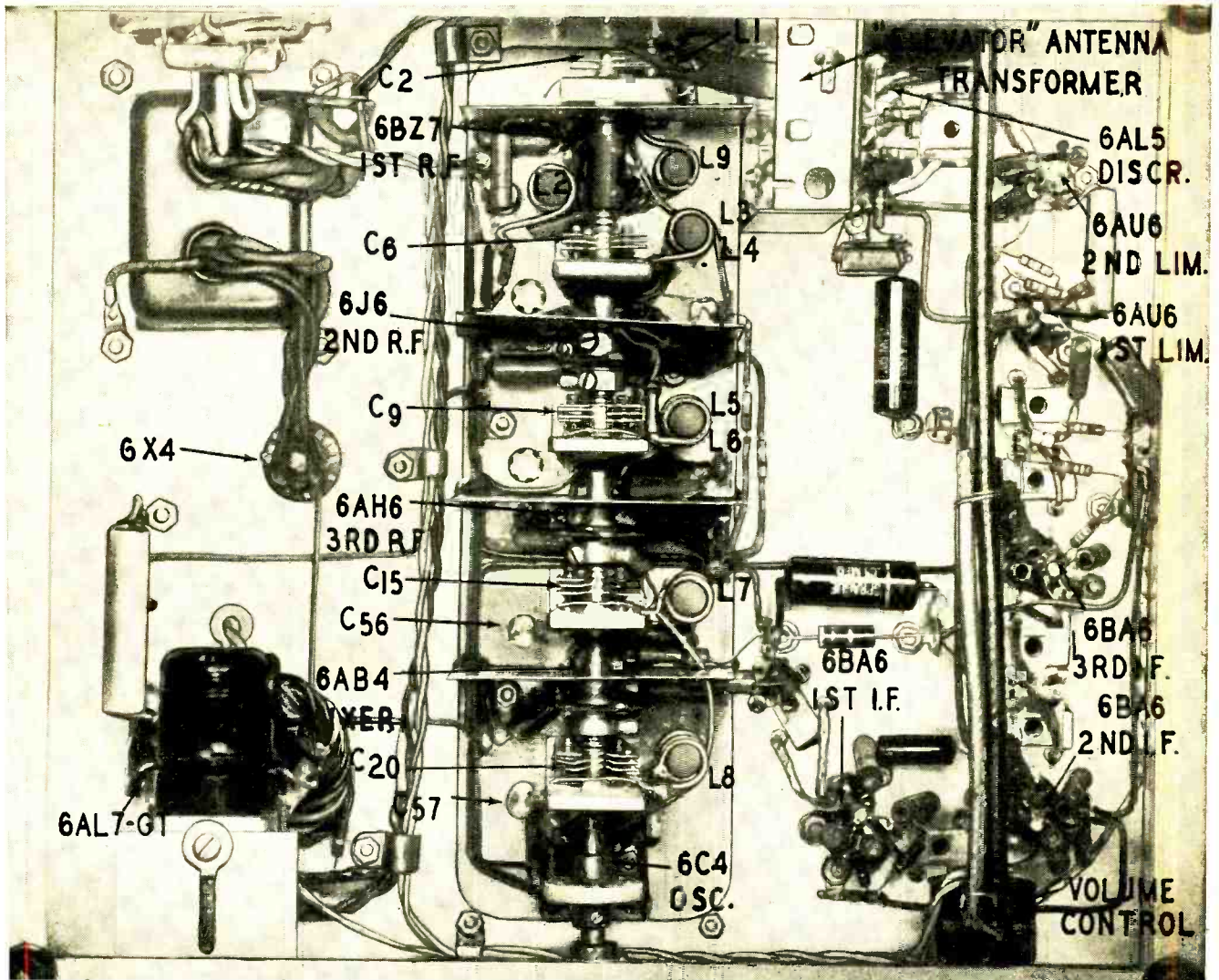

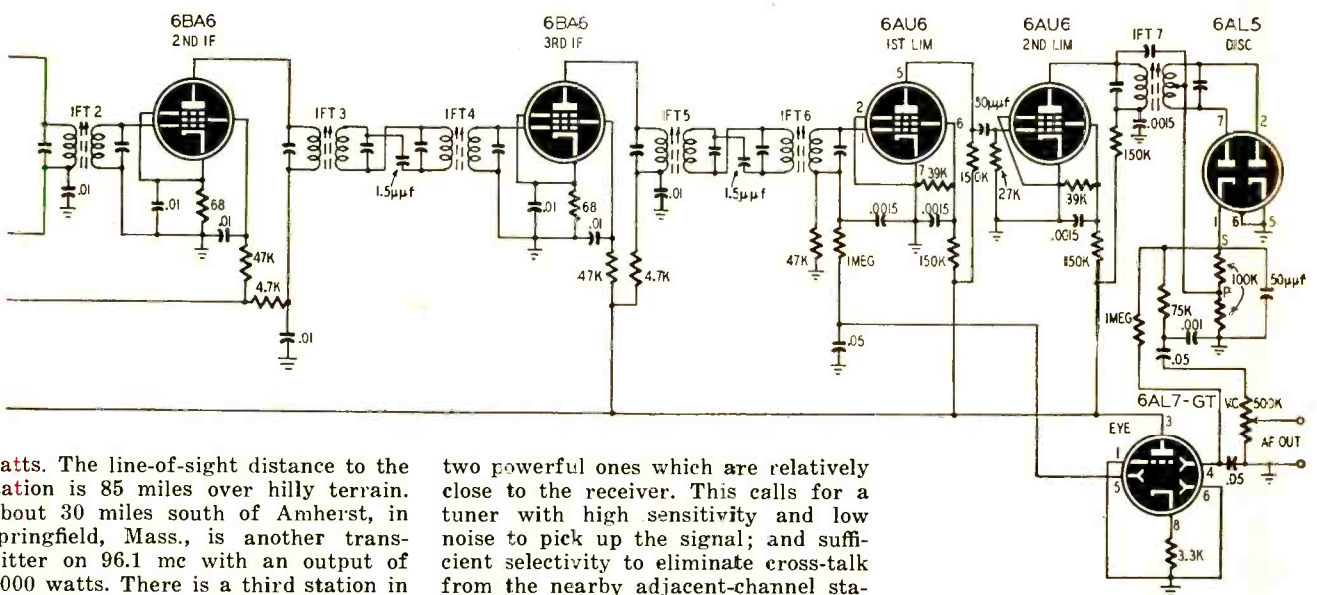Tube and component layout under the tuner chassis. Note the copper interstage shields installed directly across the r.f.-amplifier and mixer sockets. Placement and wiring in the front end should follow the original as closely as possible.



watts. The line-of-sight distance to the station is 85 miles over hilly terrain. About 30 miles south of Amherst, in Springfield, Mass., is another transmitter on 96.1 mc with an output of 1,000 watts. There is a third station in Hartford, Conn., about 60 miles south of Amherst. This one is on 95.7 mc, and has an output of 50 kw.

The problem is that the weak, distant, desired signal is directly between

two powerful ones which are relatively close to the receiver. This calls for a tuner with high sensitivity and low noise to pick up the signal; and sufficient selectivity to eliminate cross-talk from the nearby adjacent-channel stations.

The tuner described in this article is the third of a series of tuners built in an effort to solve the problem.

The first tuner had two pentode r.f.

Fig. 1—Circuit diagram of the high-sensitivity, low-noise FM tuner. Exceptional selectivity without clipping of two modulation peaks is provided by two dual-transformer-coupled i.f. stages.

stages—a 6AH6 followed by a 6AK5—and a 6AK5 pentode converter with a 6C4 oscillator. There were two 6BA6 i.f. stages, two 6AU6 limiters, and a 6AL5 discriminator. It had pretty good sensitivity, but the noise level with the pentode r.f. stages and the pentode converter was too high, so the entire front end was rebuilt. The second model had two 6AB4 grounded-grid-triode r.f. amplifiers followed by a 6AH6 pentode r.f. stage; a 6AB4 triode converter; and a 6C4 oscillator. The i.f. system was the same one used in the original model. This set had a low noise level, by virtue of the grounded-grid-triode r.f. stages and the triode converter; but it lacked the sensitivity of the first tuner, so it was scrapped too.

The present set is the result of an attempt to combine sensitivity with low noise level and a higher degree of selectivity than previously.

Circuit analysis

Fig. 1 is the schematic of the final model. The tuner has 13 tubes which perform the following functions: First radio frequency amplifier, a 6BZ7 double triode in a cascode circuit. Following this is a neutralized 6J6 push-pull-triode r.f. stage. The third r.f. stage is a 6AH6 pentode. The converter is a 6AB4 triode, and the local oscillator is a 6C4 triode. Following the converter are three 6BA6 i.f. stages operating at 10.7 mc, with dual-transformer band-pass coupling. Two 6AU6 limiters in cascade are next, and the discriminator is a 6AL5 double diode. There is a 6AL7 tuning eye operating from the a.v.c. line, and the power-supply rectifier is a 6X4.

A convenient and efficient coupling method for matching 300-ohm lead-in to the input grid was borrowed from TV practice. One of the so-called "elevator coils" gives us relatively light input loading, which allows us to tune the input grid circuit with one section of the five-gang tuning capacitor. The plate circuit of the first triode (half of the 6BZ7) is not tuned because it is not critical at all. The grounded-grid half of the 6BZ7 has a slug-tuned neutralizing coil (L9) to the grid of the

first triode through which the cathode current of the second triode passes. Its plate circuit (L3) has untuned link coupling to the 6J6 push-pull grid circuit. Both the grid circuit (L4) and the plate circuit (L5) of this push-pull stage are tuned by sections of the gang. A link from the 6J6 output goes into the untuned grid of the 6AH6 third r.f. amplifier (L6), whose plate circuit is impedance-coupled to the grid of the 6AB4 mixer (L7). This is also tuned by one of the ganged capacitors. The oscillator is a 6C4 in a conventional Hartley circuit, tuned by the fifth gang of the tuning capacitor.

The plates of the converter and all r.f. tubes operate at about 150 volts, and the oscillator has about 100 volts on its plate.

Two of the 3 i.f. stages are band-pass-coupled by "back-to-back" i.f. transformers. This arrangement steepens the sides of the i.f. response curve, to give the desired selectivity. The i.f. stages are operated at relatively low voltages—approximately 90 on the plates and 60 on the screens—to reduce any tendency to regenerate. The cascaded 6AU6 limiters operate at even lower voltages than the i.f. stages. They have about 40 volts on the plates and 30 volts on the screens for good limiting even on extremely weak signals.

The 6AL5 discriminator circuit has a 75-microsecond de-emphasis filter in its output. This feeds the volume control, which also incorporates the power switch for the tuner.

Bifilar-wound r.f. chokes were inserted in the filaments of the first two r.f. stages, with single chokes in the hot sides of the remaining r.f. tube filaments, and in the filaments of alternate i.f. and limiter tubes. The slug-tuned interstage coils in the r.f., mixer, and oscillator stages are all self-supporting. They were tuned with iron cores taken from National XR50 coil forms, but any high-frequency iron cores available may be used. The five-gang tuning capacitor was made up of National UM-15 15- μmf miniature sections linked with insulated couplings.

Tubular trimmer capacitors were used in the converter grid circuit and

the oscillator grid circuit, but the other tuned circuits tracked satisfactorily with the slugs only. The number of turns given in the table for each coil is only approximate, and it is advisable to use a grid-dip meter to find the correct number of turns for each coil. The tuner covers 86 to 110 mc, which takes in TV-channel 6 sound at one end and aircraft signals at the other.

The 6J6 push-pull triodes are cross-neutralized by two $\frac{1}{16}$ -inch inside diameter copper tubes about $\frac{1}{2}$ inch long (C_N). These are soldered to the terminals of the plate tuning capacitor and an insulated wire from the opposite grid terminal of the 6J6 is inserted in each tube. This is a very handy way of neutralizing, takes up little space, and fits the physical layout very well. One of these neutralizing tubes can be seen in the underchassis photo at the right of tuning capacitor C9.

Construction

Parts placement, orientation of tube sockets, and lead dress are highly critical, especially in the r.f.-mixer-oscillator section. To reduce the possibility of regeneration, and to insure satisfactory alignment, follow the layout given in Fig. 2 as closely as possible—especially the socket keying.

Copper shields were mounted across the converter socket and all r.f. tube sockets to isolate their grid circuits from their plate circuits as much as possible. These shields are drilled to pass the tuning shaft.

There is a bit of backlash in the last section of the tuning gang. For this reason, the antenna circuit, which is not critical at all, is placed at this end; the highly critical oscillator circuit is closest to the dial, where there is minimum backlash.

The bandpass coupling in the i.f. stages very definitely helps to narrow the bandwidth, but it does reduce the gain. Where the tuner is to be used for long-distance reception with no selectivity problems, single-transformer coupling is preferable.

The 6AL7-GT twin-beam tuning eye is an added refinement and operates off the discriminator output and the grid

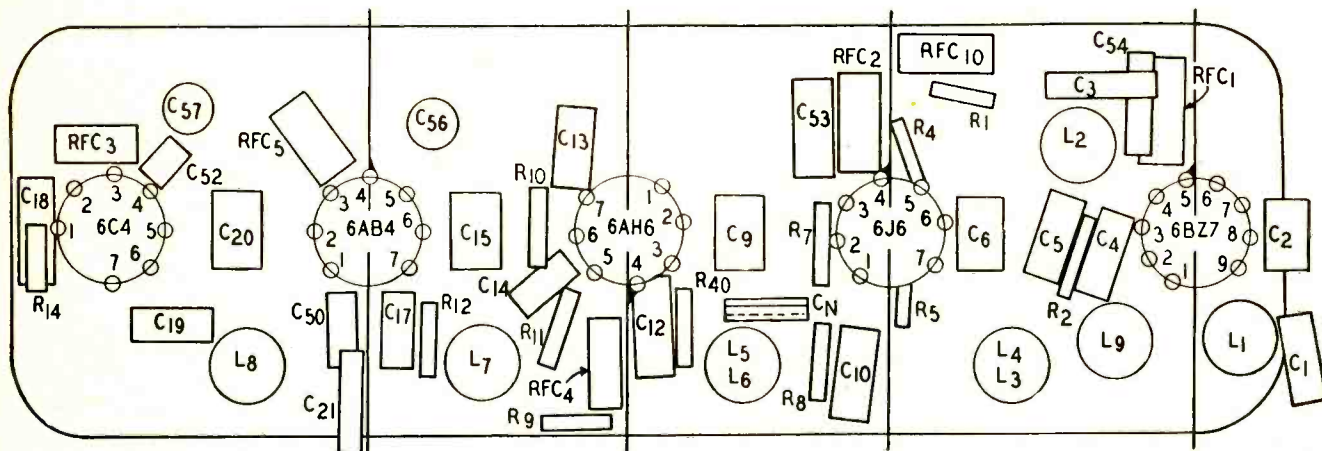


Fig. 2—Layout diagram of r.f., mixer, and oscillator stages. Component numbers refer to circuit elements shown in Fig. 1. Note the positions of the terminals on the tube sockets, and the connections between interstage shields and heater pins.

circuit of the first limiter. A microammeter in series with the first limiter grid return would give a more accurate indication of signal strength, but is a good deal more expensive.

Alignment and tracking

For i.f. alignment, connect a vacuum-tube voltmeter from pin 5 of the tuning-eye socket to ground. Remove the 6C4 oscillator tube from its socket so there will be no conversion of unwanted signals. With a 10.7-mc signal fed into the converter grid tune the i.f. transformers for maximum reading on the lowest voltage scale of the v.t.v.m. If the transformers are very far out of alignment it may be necessary to introduce a strong signal at the first-limiter grid and work back stage by stage to the converter grid, introducing the signal in the stage just ahead of the one being aligned.

In aligning the quadruple-tuned band-pass circuits for optimum bandwidth connect an oscilloscope to the plate of the first limiter and feed the output of a sweep-signal generator to the converter grid. Set the generator for a total sweep width of 450 kc with 10.7 as the center frequency. Adjust the various i.f.-transformer slugs to give a tall, flat-topped response curve with sides as steep as possible. With single-transformer i.f. coupling the oscilloscope and sweep-generator alignment is unnecessary; v.t.v.m. maximum readings on 10.7 mc are sufficient.

The discriminator primary is adjusted for a *maximum* reading with the v.t.v.m. connected between the load center-point (F) and ground. The secondary is then adjusted for *zero* voltage reading with the v.t.v.m. between point S and ground. Now plug the oscillator tube back in.

To align the front end, connect the v.t.v.m. between pin 5 of the 6AL7-GT socket and ground, as in the i.f. alignment procedure. The oscillator should be aligned first just above the high end of the FM band—at approximately 109 mc—by opening the main tuning gang all the way, running the oscillator-coil (L8) slug *halfway* in, and adjusting trimmer capacitor C57 for maximum output. To track the oscillator at the low end of the band, set the generator at 87 mc, close the main tuning capacitor completely, and adjust the oscillator-coil slug for maximum output.

Adjust the mixer grid circuit (C56 and L7) next in exactly the same way. The interstage r.f. coils are peaked at the high end of the band by stretching or compressing the windings with the slugs *halfway* in. Then the low end is peaked by adjusting the slugs for maximum output. If desired, the second r.f. stage can be peaked in the middle of the FM band instead of at the ends, for more uniform over-all response.

Neutralizing procedure

The r.f. stages are neutralized after they have been aligned. The v.t.v.m. is left in the position for r.f. alignment.

Disconnect one side of the 6J6 heater and feed a signal to the antenna terminals at the high end of the tuning range. Adjust the neutralizing capacitors (C_N) in equal steps for *minimum* reading on the v.t.v.m.

Reconnect the 6J6 heater and disconnect one of the heater leads on the 6BZ7. With the same high-end signal fed in at the antenna terminals, adjust

Materials for tuner

Resistors: 2—1 megohm, 4—150,000 ohms, 5—100,000 ohms, 1—75,000 ohms, 5—47,000 ohms, 2—39,000 ohms, 3—27,000 ohms, 4—10,000 ohms, 5—4,700 ohms, 1—3,300 ohms, 1—1,000 ohms, 3—100 ohms, 3—68 ohms, 1/2 watt; 1—4,700 ohms, 1 watt; 1—4,000 ohms, 10 watts; 1—500,000-ohm audio-taper potentiometer.
Capacitors: (Electrolytic) 2—20, 1—10 μ f, 450 v. (Paper) 4—.05 μ f, 600 v. (Ceramic) 1—.01, 20—.0015 μ f, 1—220, 4—50 μ uf. (Zero temp. coeff. ceramic), 1—50 μ uf 500 v. (Mica) 1—.001 μ f, 500 v. (Silver mica) 2—1.5 μ uf, 500 v. (Variable) 5—15 μ uf (National type UM 15 or equiv.); 2—.5—5- μ uf ceramic tubular trimmers (Erie type 532 or equiv.); 2 neutralizing capacitors (see text); 1—1- μ uf gimmick.
Transformers: 1 power transformer, 700 v./c.t., at 200 ma, 6.3 v. at 6 amp, 5 v. at 3 amp (Thoradson type T22R07 or equiv.); 6—10.7-mc i.f. transformers, (Miller type 1463 or equiv.); 1—10.7-mc discriminator (Miller type 1464 or equiv.); 1—antenna matching transformer (Philco No. 324432-1, RCA No. 73591, or equiv.); 1—150-200-ma filter choke.
Miscellaneous: 1—6BZ7, 1—6J6, 1—6AH6, 1—6AB4, 1—6C4, 3—6BA6, 2—6AU6, 1—6AL5, 1—6X4, 1—6AL7-GT; 1—9-pin miniature, 1—7-pin miniature, 1 octal sockets; 5—insulated flexible couplings; 1 dial (Millen type 10039 or equiv.); 7 h.f. powdered-iron tuning slugs (see text); 1—s.p.s.t. on-off switch; chassis; socket shield; 3-amp fuse and holder; terminals; hardware; wire; solder.

the slug in the neutralizing coil (L9) for *minimum* output. L9 may have to be stretched or compressed to obtain this minimum.

With the antenna terminals open, an interesting way of indicating the benefit of low-noise neutralized triodes can be tried. When the 6J6 and 6BZ7 are properly neutralized, the noise level will *decrease* if they are plugged in after the rest of the set has warmed up. The noise level will *increase* when the 6AH6 is plugged in and warms up because it is a pentode and hence noisy.

The "elevator-transformer" antenna-input system is not absolutely necessary, but if one can be obtained or home-wound it will decrease the input grid loading and allow us to gang-tune this circuit.

When the tuner was completed it was compared with one of the better table-model commercial sets. The results were conclusive. With the commercial receiver, the desired signal could barely be made out in the cross-talk of the nearby stations. There was no entertainment value here. The tuner, by comparison, gave a strong, relatively hiss-free signal with no cross-talk. Over almost two years it has given fairly consistent daytime and evening reception of New York City and Philadelphia stations, from the Amherst receiver location. The distances to these two cities are about 170 and 225 air miles respectively. Troy, N. Y.; Binghamton, N. Y.; Providence, R. I.; Lawrence, Mass.—in fact nearly every FM broad-

COIL TABLE

L1, 2, 4, 5, 7	3 1/2 turns No. 16 bare tinned wire, 3/8 inch dia., 3/4 inch long.
L3	2 1/2 turns No. 20 insulated wire interwound with L4.
L6	2 1/2 turns No. 20 insulated wire interwound with L5.
L8	3 1/2 turns No. 16 bare tinned wire, 3/8 inch dia., 1 inch long; tapped 1 turn from ground.
L9	Approx. 12 turns No. 20 enameled copper wire, 3/8 inch dia., 3/4 inch long. Number of turns adjusted to neutralize 6BZ7 (see text).
RFC1, 2	Bifilar winding—15 turns No. 26 enameled wire close-wound on 1/4-inch diameter form.
RFC3, 4, 5, 6, 7, 8, 9, 10.	20 turns No. 26 enameled wire close-wound on 47,000-ohm or higher, 1-watt insulated resistor form.

cast station within 200 miles—has been heard at least once. The antenna is a folded dipole with reflector and director mounted about 10 feet above the roof of the house and rotated manually by a homemade mechanism.

Long-distance FM reception is fascinating, especially when freak conditions occur. In the summer of 1951 the receiver was taken to the White Mountains of New Hampshire. In one evening 18 stations were heard, ranging from Ohio to as far west as Minnesota, over distances of as much as 1,100 miles. END



Suggested by N. Radicone, Brooklyn, N. Y.
 "Howdy Doody heck! I'm the repair man. This set isn't fixed yet!"

AMPLIFYING

the REED ORGAN

By B. FRANKLYN SHINN

Great improvement results with little labor and expense.

THE writer, who has been a church organist for many years, recently had occasion to play one of the reed-type organs that are still found in many churches. Finding that the instrument was not adequate for the size and acoustics of the building, I decided to experiment with electrical amplification. The results were so far above expectation that the solution may provide a new source of revenue for service technicians in designing and setting up similar installations.

In "reed" organs the tones are generated by brass reeds vibrated by air drawn past them by a foot-operated bellows or a motor-driven blower. The tones generated by the reeds are rich in harmonic content but rather weak. Efforts to reinforce the output by di-

rect microphone pickup and amplification were not very successful. At high output levels the sound was unpleasant and the problems of acoustic feedback were not easy to solve. The speakers must be placed so that the organist can hear the result, but the microphone can "hear" it too! In seeking a solution I reasoned that the top of the reed chest would in all probability vibrate as a sounding board, and would reproduce the tones of the reeds. I mounted a contact microphone at the center of the reed chest on the SWELL organ. The result was so good that I decided to carry the experiment further.

The instrument was a two-manual and pedal-clavier organ with 20 stops. As each manual had distinctive tone characteristics which I wanted to main-

tain, I decided to use a separate pickup for each manual. The pedal-clavier tones could not be picked up without excessive background noise, but in any case the bass response was more than adequate, since enough of the pedal tones reached the two pickups provided for the manuals without the complication of a separate input. Each pickup had to be provided with a foot-operated volume-control, and as the leads involved were very long, the problem of hum had to be kept in mind. It was decided to try to develop low impedance devices for the purpose.

Two contact mikes were made from a pair of war-surplus 50-ohm dynamic headphones. I carefully loosened the cap from one headphone and cut a circular hole about one-half inch in



Fig. 2—The completed contact microphone, with four rubber support blocks mounted on the face of the earpiece cover.

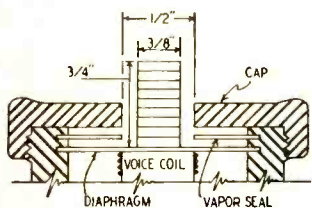


Fig. 1—Section through a modified dynamic headphone, showing the cork contact pile at the center of the diaphragm.

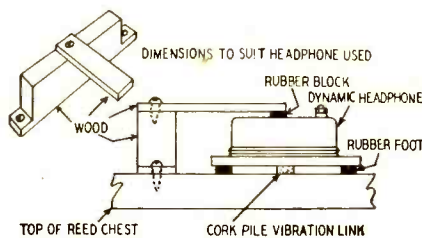


Fig. 3—Microphone clamping method.

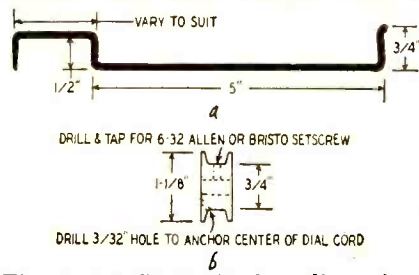


Fig. 4—(a) Steel-wire bow dimensions. (b) Driving pulley for volume control.

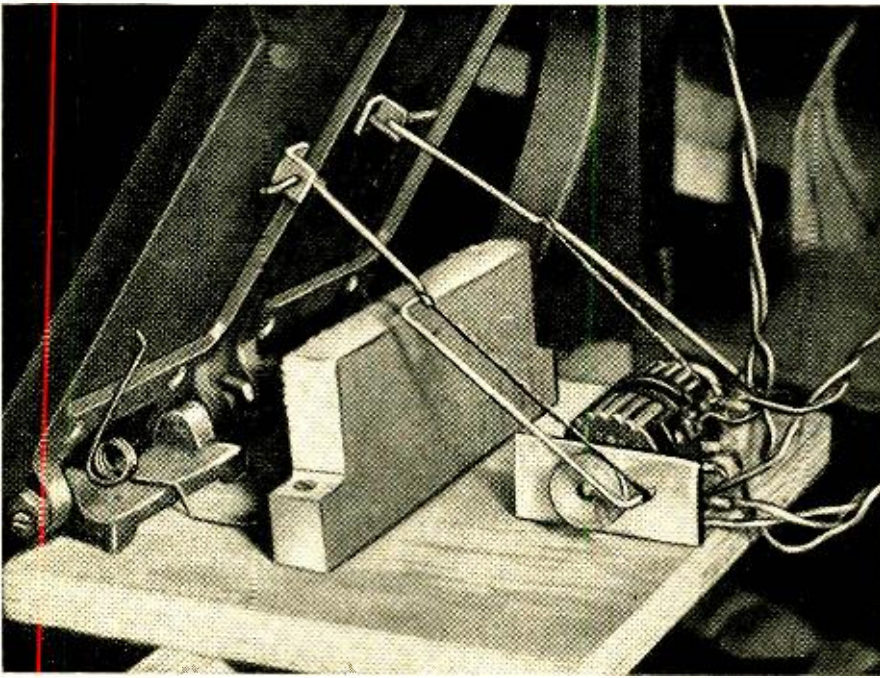


Fig. 5—Foot-operated gain-control assembly. Vertical block is pedal stop.

diameter through the center of the cap, and also through the oiled-silk moisture seal that covers the conical diaphragm. With a card punch I cut enough discs— $\frac{3}{8}$ -inch in diameter—from cork gasket material to make a stack about $\frac{3}{8}$ inch high. I cemented these together with Glyptal, and cemented the entire stack to the center of the diaphragm so that it projected through the hole in the oiled-silk vapor seal. Then I replaced the cap. See Fig. 1. As the next step I cut eight sections about $\frac{3}{8}$ -inch square by $\frac{1}{4}$ inch thick from a rubber eraser, and cemented these to the face of the cap as shown in Fig. 2. The tip of the cork pillar protrudes just far enough that when the rubber feet are held firmly against a flat surface, the end of the cork pillar rests squarely on the same surface.

The microphone was then clamped to the soundboard of the organ at the desired point by screwing a block of wood to the soundboard, and providing a small clamping piece projecting over the body of the mike. Another block of rubber between the body of the microphone and the clamping piece assures that the vibrations of the soundboard will be transmitted to the diaphragm through the cork pillar, but flexible mounting of the heavier body of the microphone will damp out trans-

mission through the mounting blocks.

A pair of 175-ohm, heavy-duty wire-wound potentiometers—also war surplus—made effective gain controls for the microphones, and they stand vigorous and continuous operation much better than ordinary radio-type controls. A method of mounting and operating these by foot then had to be devised.

The instrument had a pair of pedals that had originally operated the bellows. With the installation of an electric blower, these pedals were no longer needed, and they were taken over for the job.

To convert the reciprocating motion of the pedals into rotary motion for the controls in the simplest way possible, we went back through ancient history to what was probably the earliest system known to man: winding the string of a bow around a shaft, and making the shaft revolve by sawing back and forth with the bow. Angle brackets were fastened to the backs of the pedals to serve as bearings for the bows. The bows were bent from steel wire to the dimensions given in Fig. 4. (This steel wire can be taken from an ordinary coat hanger.)

The controls were mounted back-to-back on a U-shaped chassis with the vertical sides of the U in line with the

bow-bearing brackets on the backs of the pedals. The controls were wired so that the ground side of the one control is nearest the pedals, and the ground side of the other is away from the pedals, because one pedal will produce clockwise rotation and the other counterclockwise rotation. See Fig. 5.

With the pivots for the bows about $4\frac{1}{2}$ inches above the pedal hinges, the bows will have a straight-line travel of approximately 2 inches. To convert this into an equivalent rotation, turn a couple of drums out of brass or other suitable material to a diameter of $\frac{3}{4}$ inch at the bottom of the groove. See Fig. 4-b. Drill the centers for the volume control shafts ($\frac{1}{4}$ inch) and drill and tap the drums for No. 6-32 Allen or Bristo setscrews. Also drill a hole at an angle through the rim of the drum to provide an anchor for the bowstring.

Use only the best grade of dial cord. Anchor the center of the cord to the drum. Fasten the drum to the volume-control shaft and turn the control to the OFF position. Tie one end of the cord to the pedal as shown in Fig. 5, holding the pedal in the raised position. Wrap one complete turn of the cord around the drum and tie the other end to the tip of the bow. Any service technician who can thread up a dial can do this with his teeth while his helper holds his hands behind his back!

It may be desirable to provide stiffness in the hinges of the pedals so that they will remain in any desired position. We took over the pedals from an old player piano whose hinges were of the pin-ended shaft operating in a socket-ended screw. Tightening the screws was sufficient to provide the desired feel for the writer. The vertical block of wood between the pedals and the controls prevents the pedals from being depressed too far.

The mixer circuit is given in Fig. 6. An electronic engineer could no doubt improve it, but it worked. The main amplifier was a 6C5 feeding a 6SL7 phase-inverter driving push-pull 6V6's with negative feedback around the final stages.

Experiment to find the best speaker location. It goes without saying that the largest speaker obtainable should be used, and that adequate baffling must be provided. Tweeters were tried, but added nothing to the output. The use of at least two speakers is recommended, as the final tone frequently resembles a pipe organ to a surprising degree, and the essence of such tone is that it seems diverse and not located at a single source. Direct the speakers at a plaster wall, or better yet, at the corners of several plaster walls.

Experiment to find the best locations for the pickups too. The center of the back of the wind-chest is probably the best location, as far as possible from outside or internal supports so that it is free to vibrate. It may be desirable to try a location toward the treble end of the instrument to balance the result. Consult the organist.

END

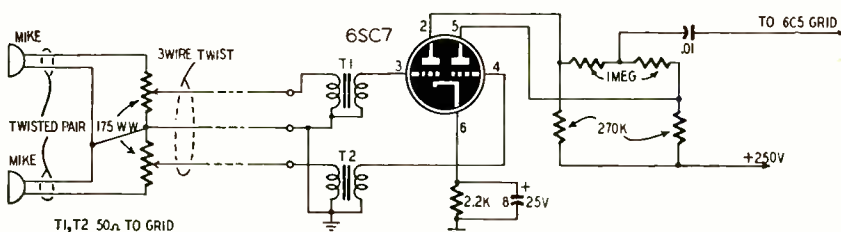


Fig. 6—Inputs are mixed through a simple and effective circuit using one 6SC7.

How practical filter sections differ from the mathematicians' loss-free ideal

By NORMAN H. CROWHURST

FROM correspondence I have received since the publication of "Loudspeaker Crossover Design" in the July, 1952, issue of RADIO-ELECTRONICS, it is evident that many—even engineers—have more vague ideas about filters than might have been expected. Articles have appeared from time to time, giving various details of filter design, complete with circuits and values, or with charts or formulas from which values can be calculated to suit individual applications. This information has included idealized response characteristics, and a general impression seems to exist that filters are special circuits possessed of some magical properties which can be achieved simply by applying the charts or formulas.

Mathematicians may be more fortunate than the rest of us in being able to understand the *derivation* of the wonderful circuits presented in textbooks, but whether or not they understand fully the practical implications of their handiwork, they generally fail to convey this information in terms the

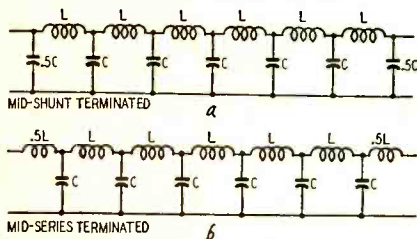


Fig. 1—Artificial lines built up from two types of low-pass filter sections.

technician who is not a mathematical genius can understand. The truth is that, even to the mathematician, complete analysis of circuits containing a number of reactance elements is highly involved. Even our mathematical friends look for short cuts. As anyone who has tried taking a short cut knows, it can be very useful *when it can be certain that the short cut really does lead to the same place as the regular route.*

Travelling up the line

Most filter designs are based on transmission-line theory. To understand this let us first look at the properties of transmission lines. They consist essentially of two conductors spaced apart by dielectric material. The conductors may be similar or different, concentric or parallel wire—in all cases the conductors possess resistance and inductance distributed uniformly along their length, and the dielectric between them will introduce capacitance and in-

duction leakage (conductance) also distributed uniformly along the length of the line.

The theory of transmission lines deduces that attenuation along the line is due to conductor resistance and insulation conductance. Time delay and other effects are created by inductance and capacitance. When these four quantities are in a simple proportional relationship the line is "distortionless"; this means uniform attenuation and time delay for all frequencies. As all frequencies suffer the same *time* delay, this means the *phase* delay of individual frequencies will be proportional to frequency. Such a distortionless line does not occur naturally; insulation conductance is usually too low (or insulation resistance too high), to satisfy the proportional relationship required. Increasing insulation conductance by deliberately making the line more leaky is obviously undesirable because this will increase the attenuation along the line.

Long lines are usually loaded to make them distortionless. This consists of artificially increasing inductance so that correct proportional relationship is obtained. There are two kinds of loading: distributed and lumped. Distributed loading is introduced by inserting magnetic material along the conductors to increase the inductance uniformly all along the line. Lumped loading is achieved by inserting chokes—or *loading coils*—at regular intervals along the line, so the average inductance value satisfies the proportional relationship required.

Theoretical analysis of lines with distributed loading is quite simple, but the mathematics for lumped loading become formidable, and approximations have to be made to obtain workable formulas. These apply only over a limited range of frequencies; beyond this range the approximations are not good enough. It is obvious that a line with lumped loading cannot achieve the distortionless condition in the same way as one using distributed loading; but it does produce an approximation to the distortionless condition nearer than the unloaded line, within the range of frequencies for which it is designed.

... and back again

But we did not start out to discuss transmission lines—the real subject of this article is *filters*. The transmission line is merely a short cut to conventional filter design. Enough has been said to show that a distortionless transmission line is somewhat a "castle in

the air". Filter design is based on another approximation in transmission-line theory, called the "loss-free line." In this approach, conductor resistance and insulation conductance are both assumed to be zero, so the line possesses only inductance and capacitance.

Characteristic impedance

A loss-free line would be distortionless, and would possess what is called a *characteristic impedance*. If the line is terminated with a resistance equal to the characteristic impedance, the voltage and current in this terminating resistance will naturally follow the usual Ohm's law relationship; but the signal voltage and current at any point along the line will be identical in value with that in the terminating resistance. Progressive phase delay takes place along the line, but this will not affect either the values of voltage and current or the phase relationship between them at any one point.

Now suppose the line is terminated, not by a resistance equal to its characteristic impedance, but by some other value—either a different resistance, or a reactance. The usual explanation of what happens states that when the line is terminated by its characteristic resistance all the energy transmitted along the line is dissipated in this termination; but when some different value is used, some of the energy arriving at the termination is reflected back along the line. The varying phase relations between the reflected components of voltage and current and the original forward-going components, cause the effective impedance of the line measured at different points to vary. The net re-

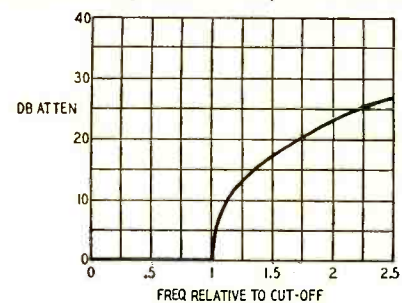


Fig. 2—Attenuation curve of a typical low-pass filter section that is terminated in its image impedance. See text.

sult: with wrong resistance termination, the impedance varies above and below the characteristic value, having maximum values at half-wave intervals, and minimum values also at half-wave intervals, but spaced mid-way between the maximum values; with re-

FILTERS

actance termination the impedance of the line varies so as to produce alternately positive and negative reactance components at similar half-wave intervals.

This brief consideration shows that even the comparatively simple loss-free line, wholly theoretical as it is, can produce some quite complicated results if the operating conditions are not exactly as planned, especially when it is remembered that the wavelengths of different signals along the same line will vary in inverse proportion to frequency; so the impedance at the sending end of a line mismatched at the receiving end will vary in a very complicated way over a wide frequency band. However, in our short cut to filter theory, lines are always assumed to be correctly terminated to avoid these complications.

The simplest form of filter derived directly from this imaginary loss-free line is the low-pass type. A number of sections of this type of filter are called an artificial line. Fig. 1 shows such an artificial line. (A high-pass filter merely has the positions of L and C reversed.) The basic difference from the theoretical loss-free line is that the inductance and capacitance of the line are uniformly distributed along its length, so each little bit of inductance is between two little bits of capacitance, so finely divided that a true equivalent would contain an infinite number of both inductances and capacitances. The artificial line has a restricted, or finite, number of elements.

Image impedance

The practical effect of this fact is that the artificial line has a definite cutoff frequency (it may be "high-pass" or "low-pass"). The loss-free line had no cutoff frequency, remember (provided we do not take into consideration the effect of transverse propagation between conductors. This enters the picture only when we get to waveguides). The term *image impedance* is used to

replace what was called *characteristic impedance* for the transmission line; it signifies that if this image impedance is applied as termination to the output end, the impedance measured at the input will be identical. What is often overlooked about the artificial line is that, besides having a cutoff frequency, its image impedance also has a frequency characteristic. *Image impedance* is thus quite different from the *characteristic impedance* of the loss-free transmission line.

If the artificial line is terminated at what are termed mid-shunt points, represented at Fig. 1-a, the theoretical image impedance rises to infinity (or open circuit) at the cutoff frequency. Below cutoff this image impedance is resistive and starts from a value identical with the characteristic impedance of the equivalent transmission line. Above the cutoff frequency the theoretical image impedance becomes reactive.

If the artificial line is terminated at a mid-series point, as represented at Fig. 1-b, the image impedance at cutoff falls to zero (short-circuit). Below cutoff the image impedance is always a resistance and likewise starts from the characteristic impedance of the equivalent transmission line. Above cutoff, the image impedance again becomes a reactance.

The usual way of showing the transmission (or attenuation) characteristic of such an artificial line is represented in Fig. 2. Note that the attenuation is zero right up to the cutoff frequency, and from there it suddenly starts to rise steeply. In curves of this kind the filter is assumed to be terminated by its image impedance, something which is not always clearly stated.

Before considering the implications of this fact on practical circuits, let us turn to the next stage in filter derivation—what are called *m*-derived filters.

The idea is that one of the elements, series or shunt, in a basic section of the artificial line, is modified by a factor *m* (modification) and then the other one is also modified and another element (of opposite kind of reactance) is introduced in such a way that the image impedance in the pass range, i.e. well away from cutoff frequency, retains its original value. In practice, the factor *m* is a fraction of 1.

Fig. 3 shows basic mid-series and mid-shunt sections of artificial line together with the *m*-derived filter obtained from each. Fig. 4 shows the attenuation characteristic for one of these *m*-derived filters. Comparing this with Fig. 2, the advantages gained are that

the cutoff slope is much steeper, and at one frequency beyond the pass range (indicated by the dotted line) the attenuation becomes theoretically infinite. (In practice this attenuation is limited by losses). This attenuation characteristic is also plotted on the assumption that the filter is terminated by its image impedance.

What an image!

Now to see what this assumption of image impedance termination really means. Fig. 5 shows how mid-series image impedance varies with frequency for a low-pass filter or artificial line of the simple type (given by $m = 1$), and for different values of *m* in series *m*-derived types. Books on filters recommend using, as termination for a com-

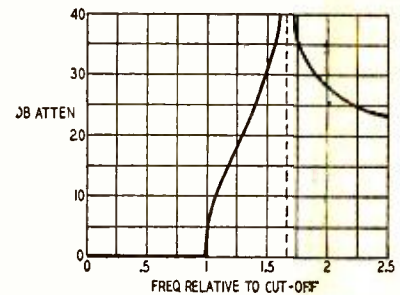


Fig. 4—Attenuation of *m*-derived low-pass filter. In this example $m = 0.8$.

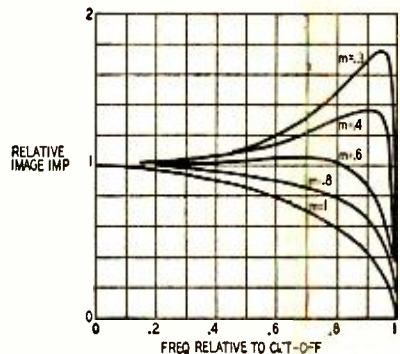


Fig. 5—How image impedance of low-pass filters varies with different *m* values.

posite filter, an *m*-derived section with a value of $m = 0.6$, because this value of *m* gives an image impedance that adheres most closely to characteristic impedance up to cutoff frequency. But, even then, to get the idealized performance characteristic given in Figs. 2 and 4, the output load (loudspeaker) impedance must look like one of the curves of Fig. 5. Even if, and when, the speaker manufacturer obliges, who wants to load the amplifier with such an impedance—since it will also "appear" at the input terminals? Every type of filter has an image impedance that either rises to open circuit or falls to short circuit at cutoff frequency: but the practical terminating impedance never does this.

However, it is possible to design "constant resistance" types which approach very closely to the idealized characteristic. The second and concluding installment of this article will describe such filters and their design.

(TO BE CONTINUED)

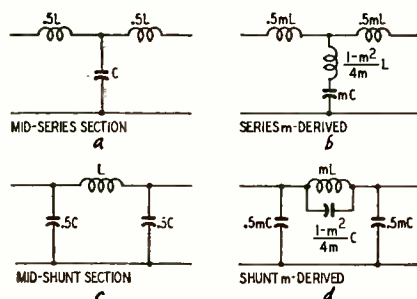


Fig. 3—Basic low-pass filter sections, with corresponding *m*-derived types.

ELECTROSTATIC SPEAKER

An old type of speaker starts out a new life under better auspices

By WERNER W. DIEFENBACH

PRACTICALLY every home radio now sold in Western Germany is equipped to receive FM broadcasting in the 87.5-100-mc band (RADIO-ELECTRONICS, March, 1953, P. 63). The majority of German listeners attach great importance to high-quality reproduction, and insist on good audio response from 40 to 12,000 cycles, and even higher. Their demands have compelled German radio manufacturers to develop low-cost wide-range speaker systems. One of the most interesting features of these new systems is the trend to electrostatic speakers for the high-frequency units.

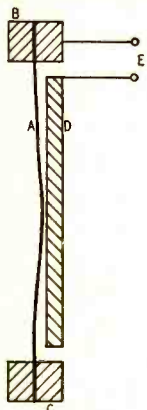


Fig. 1—Cross-section through an electrostatic speaker. The d.c. polarizing voltage E prevents "doubling" due to inertia of diaphragm. See text.

Electrostatic speakers in themselves are not new. A number of types have been designed and manufactured in the past for general use, but their large size and the high polarizing voltages required prevented them from being very successful. (Older readers will remember the *Kylectron*, sold in the United States in the late '20's.—*Editor*) However, the electrostatic speaker has distinct advantages as the h.f. element in a two- or three-way system, where its size and voltage requirements are both small. It costs much less to manufacture than the dynamic type, and has no pronounced resonant peaks between 7 kc and 20 kc.

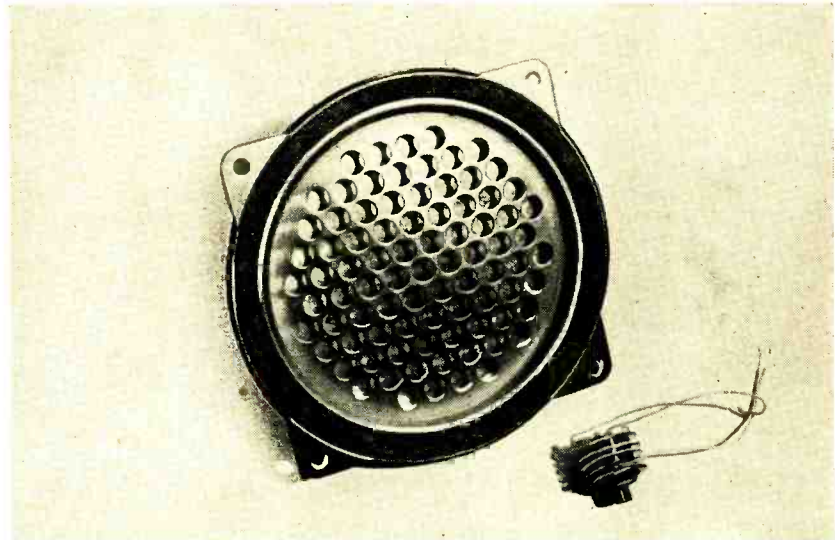


Fig. 2—Isophon electrostatic tweeter. Coil is part of the high-pass filter.

In principle, the electrostatic speaker is nothing but a two-plate capacitor (see Fig. 1). The diaphragm A—usually made of thin metal or metallized plastic foil—forms one of the plates, and is clamped at the edges (B and C). The heavy back plate D, representing the other plate of the capacitor, is spaced a small distance from diaphragm A. A d.c. polarizing voltage applied between A and D creates an electrostatic attraction which tends to pull the plates together. Since only A is flexible enough to move, it bends in at the center, but is prevented from actually touching D by the mechanical design of the speaker.

Now, if an a.c. signal is superimposed on the d.c., diaphragm A will move in and out in accordance with the a.c. variations. (Without the d.c. bias pulling it toward D, the diaphragm would swing almost *twice as far* in the opposite direction on the second half-cycle—its inertia alone would carry it an equal distance back past the original position, and the driving force of the second half-cycle of the signal would be added to this movement. This is known as "doubling," and is the reason why the d.c. polarizing voltage is essential.) Good efficiency requires high d.c. bias voltage or very small normal clearance between A and D.

Fig. 2 shows a typical modern electrostatic tweeter (Isophon). The diaphragm is $3\frac{1}{16}$ inches in diameter, and the speaker is only $\frac{3}{4}$ inch deep overall. The coil at the right is part of the high-pass filter that prevents the tweeter from being damaged by low frequencies. The circuit for feeding the tweeter is given in Fig. 3.

In this arrangement the speaker is fed with about 250 volts polarizing bias through R1. C1 and L1 form a high-pass filter between the impedance-matching tap on the output transformer and the speaker. The low-frequency cutoff (turnover) of the filter can be varied by adjusting the powdered-iron core of the coil. L1 has a maximum inductance of about 40 mh and a d.c. resistance of about 125 ohms. Higher values of inductance develop excessive voltage at the turnover frequency.

The filter is adjusted for a turnover

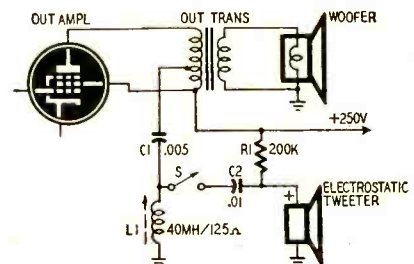



Fig. 3—Schematic of two-way speaker system with Isophon electrostatic unit.

between 7 and 8 kc. The remarkably flat acoustic-pressure curve between 7 kc and 20 kc is shown in Fig. 4.

The speaker is coupled to the filter network through C2, and can be disconnected from the circuit if desired by opening switch S.

Directivity

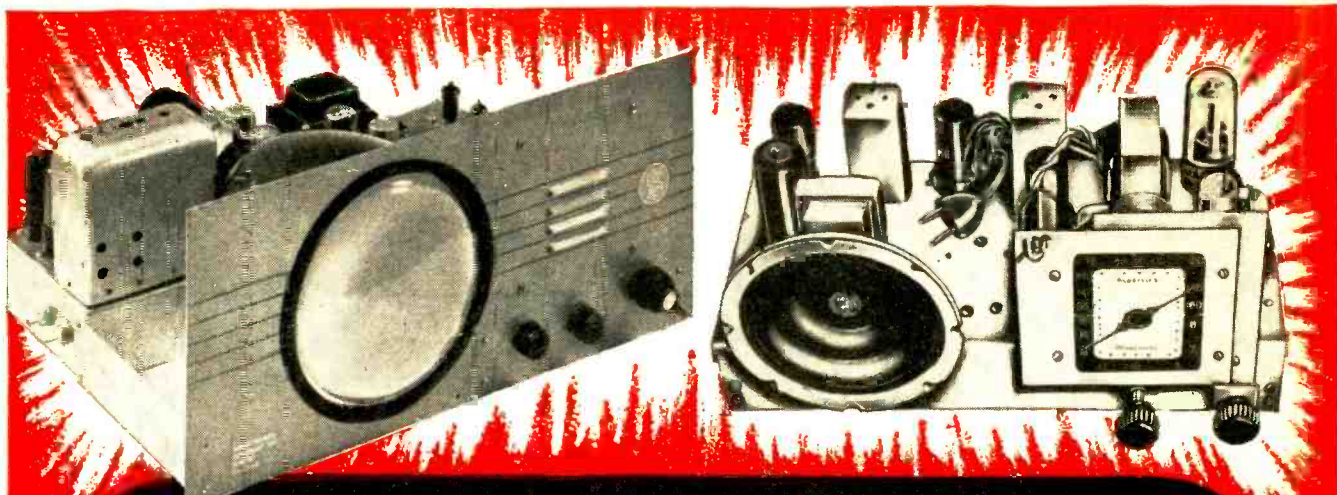High-frequency speakers are notoriously directive, so that listeners sitting off the main axis of a tweeter without



**TRAIN *FASTER* — TRAIN *BETTER* — TRAIN *EASIER*
 IN 10 MONTHS — OR LESS — FOR
RADIO-TELEVISION**

Our 21st Year Training Men for Greater Incomes and Security in Radio-Television

**I SEND YOU
 18 BIG KITS**

of Radio-Television parts and equipment. Much of your training will be actual construction and experimentation . . . the kind of truly PRACTICAL instruction that prepares you for your Radio-Television career.



Frank L. Sprayberry
 President
 Sprayberry Academy
 of Radio

NEW! NO OBLIGATION PLAN

**You Have No Monthly Payment Contract to Sign
 Pay For Your Training as You Earn and Learn**

You can get into Radio-Television, today's fastest growing big money opportunity field, in *months* instead of years! My completely new "package unit" training plan prepares you in as little as 10 months or even less! *No monthly payment contract to sign—thus NO RISK to you!* This is America's finest, most complete, practical training—gets you ready to handle any practical job in the booming Radio-Television industry. Start your own profitable Radio-Television shop . . . or accept a good paying job. I have trained hundreds of successful Radio-Television technicians during the past 21 years—and stand ready to train you, even if you have no previous experience! Mail coupon, and get all the facts—FREE!



**Valuable Equipment Included
 With Training**

The new Sprayberry "package" plan includes many big kits of genuine, professional Radio-Television equipment. You perform over 300 demonstrations, experiments and construction projects. You build a powerful 6-tube 2-band radio set, multi-range test meter, signal generator, signal tracer, many other projects. All equipment and lessons are yours to keep . . . you have practically everything you need to set up your own profitable Radio-Television service shop.

Earn Extra Money While You Learn!

All your 10 months of training is IN YOUR HOME in spare hours. Keep on with your present job and income while learning. With each training "package" unit, you receive extra plans and "Business Builder" ideas for spare time Radio-Television jobs. Near television stations everywhere, open vast new opportunities for trained Radio-Television Technicians—and those in training. If you expect to be in the armed forces later, there is no better preparation than practical Sprayberry Radio-Television training.

YOU BUILD the Television set and the powerful superheterodyne radio receiver shown above IN ADDITION to the other test units shown here (many are not shown because of lack of space). All equipment I send you is YOURS TO KEEP.

Approved for Veterans under the G. I. Bill

**SPRAYBERRY ACADEMY OF RADIO 111 NORTH CANAL ST.
 Dept. 20-V, Chicago 6, Ill.**

**MAIL COUPON
 TODAY!
 NO OBLIGATION**

**SPRAYBERRY ACADEMY OF RADIO, Dept. 20-V,
 111 North Canal St., Chicago 6, Ill.**

Please rush to me all information on your 10-MONTH Radio-Television Training Plan. I understand this does not obligate me and that no salesman will call upon me. Be sure to include 3 books FREE.

Name..... Age.....
 Address.....
 City..... Zone..... State.....

I invite you to get all the facts—
**FREE TO YOU 3 BIG
 RADIO-TELEVISION BOOKS**

I want you to have ALL the facts about my new 10-MONTH Radio-Television Training—without cost! Rush coupon for my three big Radio-Television books: "How to Make Money in Radio-Television," PLUS my new illustrated Television Bulletin PLUS an actual sample Sprayberry Lesson—ALL FREE. No obligation and no salesman will call. Mail coupon NOW!



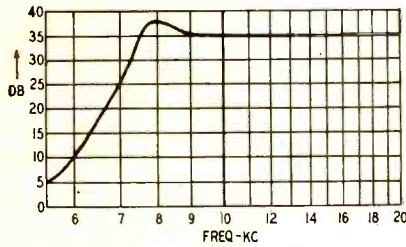


Fig. 4—Response of *Isophon* tweeter is remarkably flat above turnover.

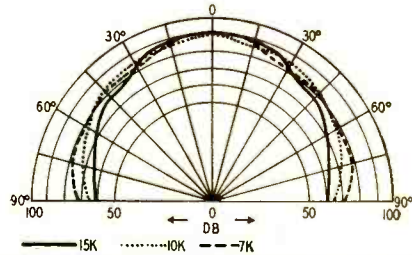


Fig. 6—Horizontal distribution pattern of the *Koerting* electrostatic tweeter.

a special wide-angle distribution horn may not hear much of the high-fre-

quency radiation. This disadvantage is overcome in one electrostatic tweeter

(Koerting) by giving the diaphragm and back plate an outward curvature. See Fig. 5. The success of this design can be seen in the horizontal-distribution pattern of the Koerting tweeter (Fig. 6).

A three-way speaker system made by Koerting for high-quality receivers is shown in Fig. 7. The characteristics and mounting of the individual speakers are designed to distribute all frequencies uniformly throughout the room. Extensive tests indicate that these units have good service life as well as excellent frequency response, even at high relative humidity. END

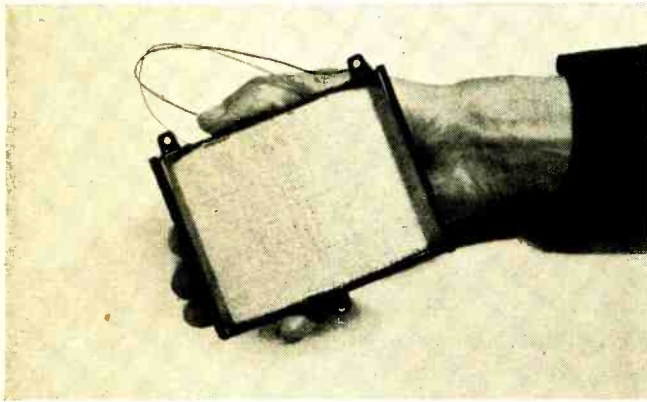


Fig. 5—*Koerting* curved-plate electrostatic tweeter has wide-angle distribution.

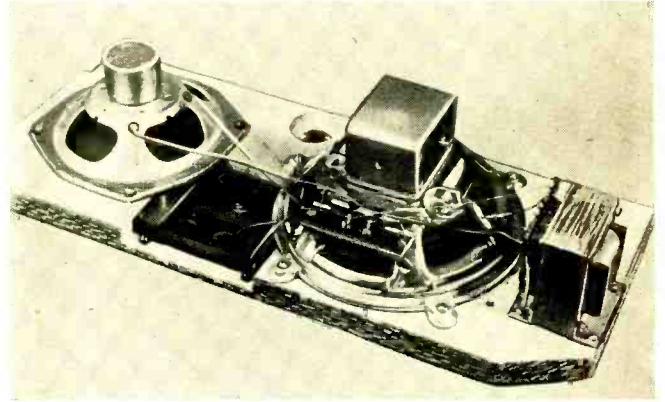


Fig. 7—Three-way speaker system used in high-quality German radios. The electrostatic unit is in the center.

RELIABLE WIDE-RANGE AUDIO OSCILLATOR

WIDE-RANGE audio oscillators featuring low distortion and a high degree of stability are rapidly becoming a necessity. This capacitance-tuned Wien bridge audio oscillator is described through the courtesy of Cornell-Dubilier.

The unit covers from 20 to 20,000 cycles in three ranges. The lowest range tunes from 20 to 200 cycles when the 20-megohm resistors are in the bridge. The bands are tuned with a standard 2-section, 365- μ f tuning capacitor (C2 and C3) instead of the 4-section, 500- μ f unit often specified for use in these instruments. C1, C4, and C5 are 50- μ f APC-type air trimmers. C1 compensates for the stray capacitance across C3. C4 and C5 raise the capacitance range to 40-400 μ f. The tuning capacitor is mounted on a plastic plate supported above the chassis on standoff insulators. The portion of the chassis immediately below the tuning capacitor is cut out to minimize stray capacitance. An insulated shaft connects the shaft to the tuning dial.

The resistors used in the bridge should be accurate to 1%, so we recommend precision resistors unless you select them on an accurate bridge from a supply of 1/2-watt units. The range switch is a 2-pole, 3-position rotary type with ceramic insulation.

The power supply is mounted below the chassis with a partition shield to isolate it from the hum-sensitive parts

of the circuit. Heater leads are twisted and dressed close to the chassis. All grounds for the 12AT7 return to one point on the chassis.

Use the following procedure in preparing the oscillator for calibration:


1. Set the slider on the 10,000-ohm bleeder resistor about one-fourth the way up from the grounded end.
2. Set the range switch to $\times 1$.
3. Set the OSCILLATION CONTROL to maximum resistance, connect a pair of high-resistance phones to the low-impedance output jack, then set the OUTPUT CONTROL to the middle of its range.
4. Set C1, C4, and C5 to about three-fourths of maximum capacitance and

set the tuning capacitor C2-C3 to maximum capacitance (fully closed).

5. Turn on the power and let the tubes warm up. Listen for a tone in the phones. If you don't hear one, advance the OUTPUT CONTROL and turn the tuning capacitor to minimum-capacitance position. Advance the OSCILLATION CONTROL until a tone is heard.

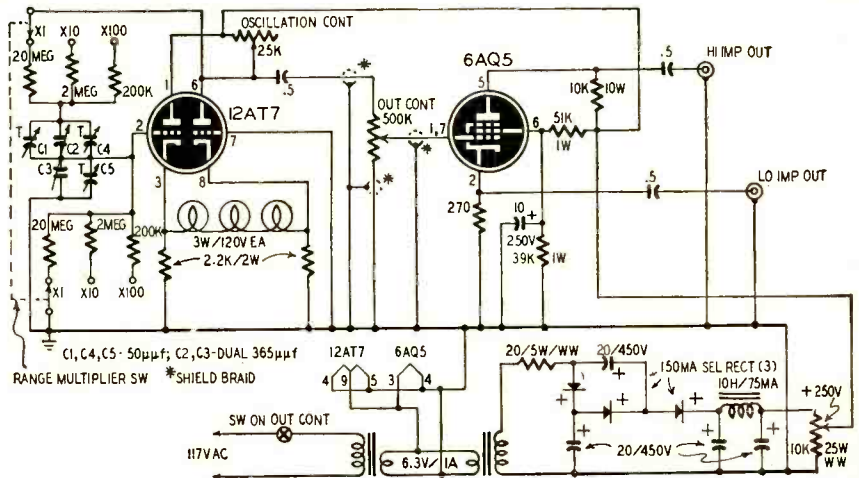6. Use a high-resistance voltmeter to set the slider on the voltage divider to exactly 250 volts, then repeat step 5.

The instrument is now ready for calibration. Follow the procedure outlined in the article "Calibrating Audio Oscillators" in the October, 1948, issue of RADIO-ELECTRONICS. END




Heathkit SUPERHETERODYNE RECEIVER KITS

- High gain dual iron core tuned type IF transformers
- AC transformer operation for safety
- Continuously variable tone control
- Sturdy punched and plated steel chassis
- Ideal for custom installation
- Full AVC action
- Inverse feedback for improved frequency response
- Kit supplied with all necessary construction material except speaker and cabinet. (Available separately if desired).

6 tube all wave circuit.
3 ranges, continuous coverage 550 kc to over 20 megacycles, shipping wt. 11 lbs.


Model AR-1

\$23.50

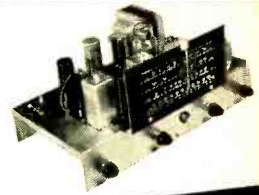

5 tube broadcast band 550 to 1600 kc coverage, shipping wt. 11 lbs.

Model BR-1
\$19.50

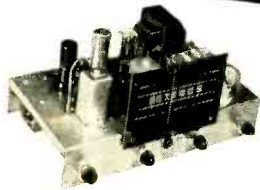

Two excellent radio receiver kits featuring clean design and open layout for simplified construction. Satisfy that urge to build your own radio receiver and select the model which meets your requirements. Both receivers feature continuously variable tone control, a radio phono switch and phono input and an AC receptacle for the phono motor. A six inch calibrated slide rule type dial with a 9 to 1 ratio vernier dial drive insures easy tuning.

SHIPPING INFORMATION

ON PARCEL POST ORDERS include postage for weight shown and insurance. (We insure all shipments.) Don't worry about sending more than the correct amount — if you send us too much, every extra cent will be promptly returned.

ON EXPRESS ORDERS do not include transportation charges. They will be collected by Express Agency on delivery.

ORDERS FROM CANADA must include full remittance for merchandise.

Orders processed on the same day received. Customers notified of unavoidable delay.

U. S. postal or express money orders, bank drafts or checks are acceptable. Do not send loose coins or stamps.

ALL PRICES SUBJECT TO CHANGE WITHOUT NOTICE

EXPORT AGENT
ROCKE INTERNATIONAL CORP.
13 E. 40th ST.
NEW YORK CITY (16)
CALL: AR48-N.Y.

The HEATH COMPANY

... BENTON HARBOR 20, MICHIGAN

ORDER BLANK

MAIL YOUR ORDER TODAY TO THE
HEATH COMPANY
BENTON HARBOR 20,
MICHIGAN



From

SHIP VIA


- Parcel Post
- Express
- Freight
- Best Way

(PLEASE PRINT)

QUANTITY	ITEM	PRICE	QUANTITY	ITEM	PRICE
	Heathkit Oscilloscope Kit—Model O-8 (29 lbs.)	\$43.50		Heathkit Square Wave Gen. Kit—Model SQ-1 (14 lbs.)	\$29.50
	Heathkit Intensifier Kit (O-8 only) No. 339 (1 lb.)	7.50		Heathkit AC VTVM Kit—Model AV-2 (5 lbs.)	29.50
	Heathkit Voltage Calibrator Kit—Model VC-1 (5 lbs.)	9.50		Heathkit Intermodulation Analyzer Kit—Model IM-1 (18 lbs.)	39.50
	Heathkit Electronic Switch Kit—Model S-2 (11 lbs.)	19.50		Heathkit Regulated Power Supply Kit—Model PS-2 (20 lbs.)	29.50
	Heathkit Scope Demodulator Probe Kit No. 337 (1 lb.)	4.50		Heathkit Handitester Kit—Model M-1 (3 lbs.)	13.50
	Heathkit T.V. Alignment Generator Kit—Model TS-2 (20 lbs.)	39.50		Heathkit Decade Resistance Kit—Model DR-1 (4 lbs.)	19.50
	Heathkit Q Meter Kit—Model QM-1 (12 lbs.)	39.50		Heathkit Decade Condenser Kit—Model DC-1 (4 lbs.)	16.50
	Heathkit Grid Dip Meter Kit—Model GD-1 (4 lbs.)	19.50		Heathkit Impedance Bridge Kit—Model IB-1B (15 lbs.)	69.50
	Heathkit VTVM Kit—Model V-6 (7 lbs.)	24.50		Heathkit Battery Tester Kit—Model BT-1 (3 lbs.)	7.50
	Heathkit RF Probe Kit No. 309 (1 lb.)	5.50		Heathkit Resistance Substitution Box Kit—Model RS-1 (3 lbs.)	5.50
	Heathkit HV Probe Kit No. 336 (2 lbs.)	5.50		Heathkit F.M. Tuner Kit—Model FM-2 (9 lbs.)	22.50
	Heathkit Peak-to-Peak Volt. Probe Kit No. 338 (2 lbs.)	6.50		Heathkit Broadcast Receiver Kit—Model BR-1 (11 lbs.)	19.50
	Heathkit Visual-Aural Signal Tracer Kit—Model T-3 (8 lbs.)	22.50		Heathkit Three Band Receiver Kit—Model AR-1 (11 lbs.)	23.50
	Heathkit Condenser Checker Kit—Model C-3 (7 lbs.)	19.50		Heathkit Amplifier Kit—Model A-7 (10 lbs.)	14.50
	Heathkit RF Signal Generator Kit—Model SG-7 (7 lbs.)	19.50		Heathkit Amplifier Kit—Model A-7A (10 lbs.)	16.50
	Heathkit Tube Checker Kit—Model TC-1 (12 lbs.)	29.50		Heathkit Amplifier Kit—Model A-8 (19 lbs.)	33.50
	Heathkit T.V. Tube Adapter No. 355 (1 lb.)	4.50		Heathkit Amplifier Kit—Model A-8A (19 lbs.)	35.50
	Heathkit Battery Eliminator Kit—Model BE-3 (20 lbs.)	24.50		Williamson Type Amplifier Kit (Type:)	
	Heathkit Vibrator Tester Kit—Model VT-1 (7 lbs.)	14.50		Shipped express only	
	Heathkit Audio Generator Kit—Model AG-8 (16 lbs.)	29.50		WA-P1 Preampifier Kit (7 lbs.) (Shipped exp. or p.p.)	19.75
	Heathkit Audio Oscillator Kit—Model AO-1 (14 lbs.)	24.50			
	Heathkit Audio Frequency Meter Kit—Model AF-1 (15 lbs.)	34.50			

*Please ship C.O.D. Postage enclosed for _____ lbs. Enclosed find Check Money Order for _____

THE LOW DOWN ON THE BC-442-A

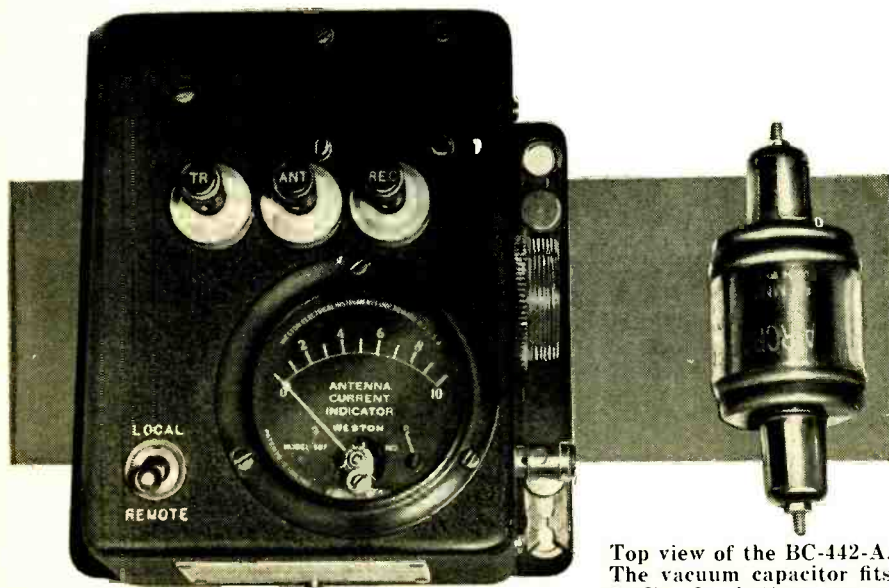

Top view of the BC-442-A. The vacuum capacitor fits cavity in bottom cover.

Piece-by-piece or "as is"—this antenna relay unit is a real surplus goldmine for transmitting amateurs

By JOHN T. FRYE

THE supply of worth-while war surplus electronic equipment has virtually disappeared from the market. Faced with this hard fact, we should re-examine the equipment we have already bought and "stashed" away against some vague possible future need. The antenna relay unit for the 274-N and ARC-5 command transmitters, known variously as the BC-442-A or by the Navy model number CBY-29125, was purchased by thousands of amateurs and experimenters; but many who bought these compact little units still do not realize what a treasure they have. The aim of this article is to tell them. The diagram of the BC-442-A is shown in Fig. 1. The LOCAL-REMOTE switch and the connections shown in dashed lines were provided in earlier models of the BC-442-A. Lead A is omitted in units using the LOCAL-REMOTE switch.

The 2-inch G-E or Weston antenna current indicator has specially shaped pole pieces which produce a nonlinear d.c. characteristic which partially compensates for the nonlinearity of the r.f. thermocouple used with it. The dial scale is calibrated from 0 to 10 in purely arbitrary linear units. Table I shows the current *versus* scale readings of the meter.

The unusually low resistance of the movement (3 ohms \pm 20%) makes the instrument very voltage sensitive. To demonstrate this fact, I constructed a simple voltaic cell by placing a quarter and a copper penny on opposite sides of

a piece of note paper that had been moistened with the tongue. This cell deflected the meter pointer a full two divisions. You will note that while the full-scale current is around 5 ma, 1 ma drives the pointer to half-scale. This makes the meter very useful in any application where a substantial indication of very low current is desired and yet where considerable peaks of current—peaks that would damage a microammeter—must be anticipated. A typical use is contained in the article "S-Meter From Surplus" on page 47 of the June, 1952, issue of RADIO-ELECTRONICS.

The meter is designed, however, to be used with the thermocouple located inside the case of the BC-442-A. This thermocouple develops its rated 19.5 mv of d.c. across the meter terminals when approximately 0.75 amperes of r.f. current flows through the LINE terminals located at the ends of the unit. Table II shows the relationship between r.f. current through the thermocouple and the scale reading of the meter. The improved linearity shown by the indications listed in Table II is the result of using the special meter pole pieces mentioned previously.

You will note that a substantial meter indication is had with as low as 100 ma of r.f. current. The sensitivity cannot be further increased by substituting a microammeter for the meter in the unit. A thermocouple is a very low-impedance limited-voltage-generating device, and it cannot push any significant amount of current through the


high resistance—usually several hundred ohms—of a microammeter coil.

Applications

The amateur or experimenter can find dozens of important uses for this sensitive r.f. thermocouple and meter. For example, when very short leads were used to connect the LINE terminals of the thermocouple between the bottom of a center-loaded 75-meter whip antenna and the car body, shock excitation from a BC-696-A transmitter running 40 watts input and feeding an antenna several feet from the car was sufficient to produce a half-scale reading on the meter. You can easily tune a whip antenna by tuning the transmitter to the desired frequency and then trimming the loading coil for maximum shock-excited current.

The man who likes to experiment with antennas can place the thermocouple directly across the center of a receiving dipole cut to the frequency and placed several wavelengths away from the transmitting antenna. A twisted pair or shielded leads can be run from the thermocouple back to the meter at the operating position. Varying the spacing or length of elements in the transmitting antenna, will result in a change in current of the receiving dipole.

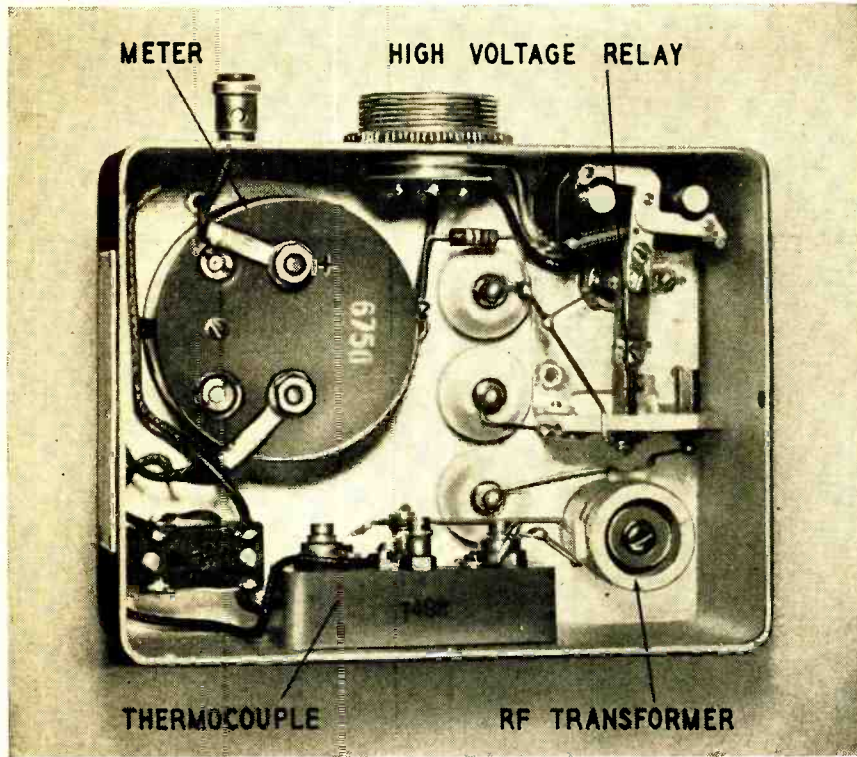If it is desired to measure the antenna current produced by any except the smallest transmitters, the .75-ampere maximum reading of the thermocouple-and-meter combination will not



Underside of the antenna relay unit, with cover removed to show components. The resistor between ground and the REC terminal is not used in all models.

be adequate. However, if the built-in r.f. transformer is used ahead of the thermocouple, the current-measuring capacity is roughly increased by a multiplier of 10 to a maximum capacity of 7.5 amperes of r.f. current. This special transformer can be seen in the picture and is shown in the wiring diagram of Fig. 1. If it is to be used, the parts should be left mounted in the case exactly as they are, for changing the lead lengths from the transformer to the thermocouple will change the readings.

The spring carrying the moving contact points of the high-voltage relay can be shifted so that instead of pressing against the inside of the fixed contact point farthest from the end of the case it presses against the outside of the fixed contact nearest the side of the case. Then, if the switch is thrown to the LOCAL position, the r.f. current can be read when applied to the TR and ANT terminals.

Table III shows the relation between measured r.f. current applied to these terminals and the meter reading. The last two figures on this chart were esti-

mated because the r.f. meter used for calibrating went only to 5 amp.

The relay is a nice little item. It consists of a set of s.p.d.t. contacts with excellent high-voltage insulation and exceptional spacing that provide very low capacitance and good arc-stopping characteristics. In addition, there is another pair of s.p.s.t. normally-open contacts. As can be seen from the bottom-view photo, the action of the relay armature is a torque affair instead of the usual straight up-and-down pull. Two coils connected in series produce this torque. Each has a resistance of 90 ohms, making a total of 180 ohms. The relay was designed to work on 28 volts d.c. with a current of 155 ma. A 30-volt stepdown transformer, a 200-ma selenium rectifier, and a 50- μ f filter capacitor can be used to make a power supply (see Fig. 2) for operating this and other 24-28-volt relays.

This particular relay can be used for send-receive switching of single-wire antennas. The extra set of contacts can be employed to ground the receiver antenna lead-in while transmitting, just

as was done in the original setup. The relay can also be used for switching r.f. inside the transmitter or for switching connections carrying very high voltages. You need not worry about the relay wearing out. It originally operated with each closing of the key on the 274-N transmitters!

The final valuable item of the unit is the 50- μ mf, 5,000-volt vacuum capacitor originally mounted beneath the tuning unit but pictured beside it in the top-view photograph. It features a high voltage rating, excellent stability, and low inductance. The first and third features make it very useful in eliminating TVI. When connected between the plate and filament or grid and filament of a transmitter final amplifier, it provides a low-impedance bypass for high-frequency harmonics that otherwise would have to return through the tank circuit and so could reach the antenna and be radiated. Phil Rand, in his booklet on TVI prevention, gives excellent

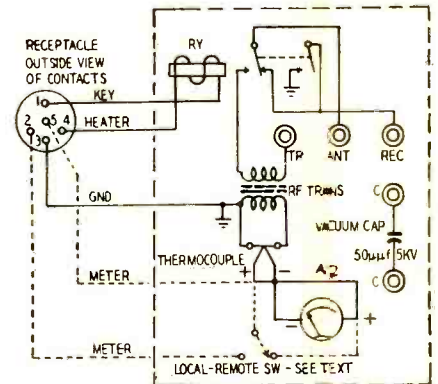


Fig. 1—Diagram of the BC-412-A unit.

suggestions on how this identical capacitor can be used to good advantage. It can also be used to pad a high-frequency final tank circuit for operating on a lower band.

The stability and low inductance of the capacitor also make it an excellent one to be used with a grid-dip meter for measuring the inductance of small coils. The coil is connected directly across the capacitor with very short, heavy leads, and then the resonant fre-



Fig. 2—Diagram of an inexpensive 28-volt d.c. supply for surplus relays.

quency is determined with the grid-dip meter. The inductance of the coil in microhenries equals

$$\frac{25,330}{C \times f^2}$$

where C is the capacitance in μ mf (50 in this case) and f is the resonant frequency in megacycles.

It is obviously impossible to point out all of the various uses of the BC-442-A and its components. It is hoped, though, that this discussion of the characteristics of these several items will enable you to use them more intelligently and confidently than you otherwise could have done. END

TABLE I (Meter alone)		TABLE II (Thermocouple and Meter)		TABLE III (Using r.f. transformer)	
D.C. ma.	Scale	R.F. amps.	Scale	R.F. amps	Scale
.1	.5	.1	1	1	.5
.2	1	.2	2	1.5	1.25
.3	1.75	.3	4	2	2.5
.4	2.5	.4	5.5	2.5	3
1	5.2	.6	8.25	3	4
2	7.5	.75	10	6 (Approx.)	8
3	9			7.5 (Approx.)	10
4	9.6				
5	10.2				

for the
new 12 volt
auto circuit

RADIART

announces its
6300 series...

an addition
to the full line of



Seal-Vent

RED SEAL VIBRATORS

Faster Starting

The exclusive RADIART design permits the briefest possible "Warm-up" period, thereby making the RADIART vibrators practically instantaneous starting. This added feature means greater performance.

Longer Life

There's more for your money in every RADIART vibrator—they last longer! Precision manufacture, using only the finest materials, assures long lasting, trouble-free performance.

Complete Replacement Line

RADIART has a CORRECT replacement vibrator for every original equipment vibrator. 12 Radiart vibrator types serve over 89% of all popular replacements. NOW..THE NEW 6300 SERIES IS READY FOR THE NEW '53 car MODELS with radios having 12 volt circuits.

Seal-Vented

Sealed at the factory to prevent the formation of an insulating film on the points while the vibrator is on the shelf...the sealed vent automatically opens when put in use to allow the vibrator to "breathe".



SUBSIDIARY OF



preferred by Servicemen Everywhere

THE RADIART CORPORATION CLEVELAND 13, OHIO

VIBRATORS • AUTO AERIALS • TV ANTENNAS • ROTORS • POWER SUPPLIES

CBS-HYTRON TRANSISTORS

CBS-HYTRON PT-2A




ACTUAL SIZE



CBS-HYTRON PT-2S

- Moisture-resistant
- Plug-in or solder-in
- Sturdy triangular basing
- Polarized base connections
- Auto-electronically formed
- Thoroughly stabilized
- Operate up to 55° C

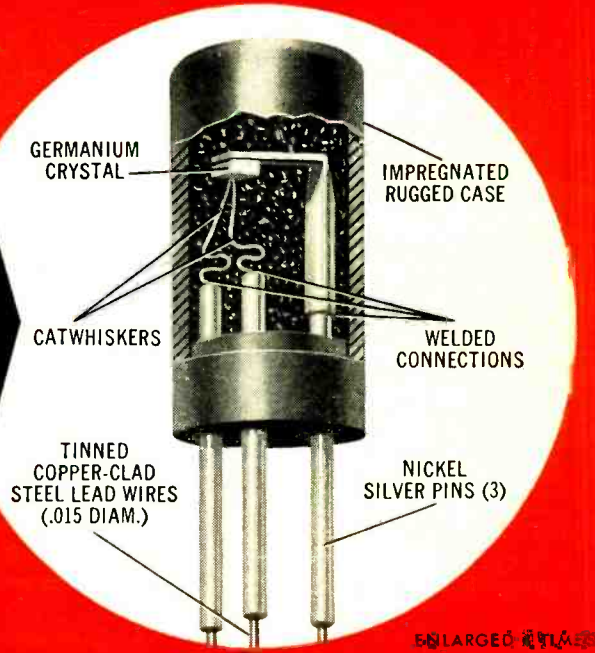

ENLARGED 10X

AND YOU CAN BUY THEM NOW!


Already a major producer of germanium diodes, CBS-Hytron now offers you prompt delivery of transistors: Point-contact CBS-Hytron PT-2A (for amplifying) and PT-2S (for switching). Both have stable characteristics and are guaranteed moisture-resistant. Note flexible leads welded to base pins. You may solder flexible leads into circuit. Or snip them to use stiff base pins in CBS-Hytron type T-2 socket.

Triangular arrangement of base pins is stronger . . . avoids bent pins. Easy-to-remember basing layout simulates basing symbol (see diagram). Polarization makes socket connections foolproof. You are assured of uniformly optimum characteristics by electronic control of pulse forming. Thorough aging achieves maximum stability. You may operate these transistors up to 55° C. And you can order both CBS-Hytron PT-2A and PT-2S for immediate delivery.




MECHANICAL FEATURES

1. Single-ended construction gives maximum mechanical stability.
2. Rugged triangular basing design resists shock and vibration.
3. Dual-purpose connections permit use of flexible leads or stiff plug-in base pins.
4. Direct soldering of germanium wafer to base support guarantees positive contact, avoids flaking.
5. Glass-filled plastic case and high-temperature impregnating wax assure moisture-resistant, trouble-free operation.

BASING AND SOCKET

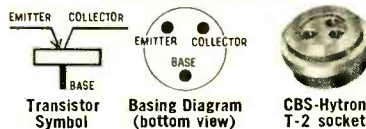

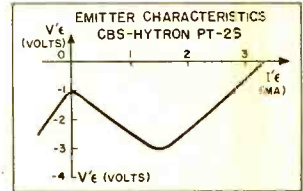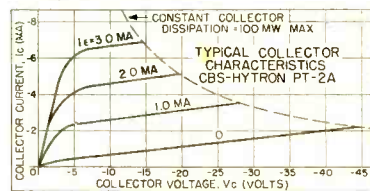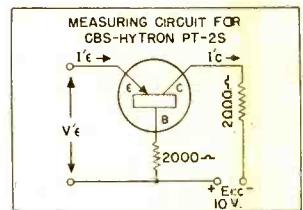Note similarity of pin layout to that of transistor symbol. CBS-Hytron type T-2 transistor socket features groove to guide pins into socket. Also anti-burn-out design to insure that base connection of transistor will always be made first.



MANUFACTURERS OF RECEIVING TUBES SINCE 1921
HYTRON RADIO AND ELECTRONICS CO.

A Division of Columbia Broadcasting System, Inc.
Main Office: Danvers, Massachusetts


WRITE FOR DATA. Complete free data on CBS-Hytron PT-2A and PT-2S . . . and the T-2 socket . . . are yours for the asking.

RECEIVING . . . TRANSMITTING . . . SPECIAL-PURPOSE AND TV PICTURE TUBES • GERMANIUM DIODES AND TRANSISTORS


ELECTRONIC INTERVAL TIMER

By JOHN L. HARNED

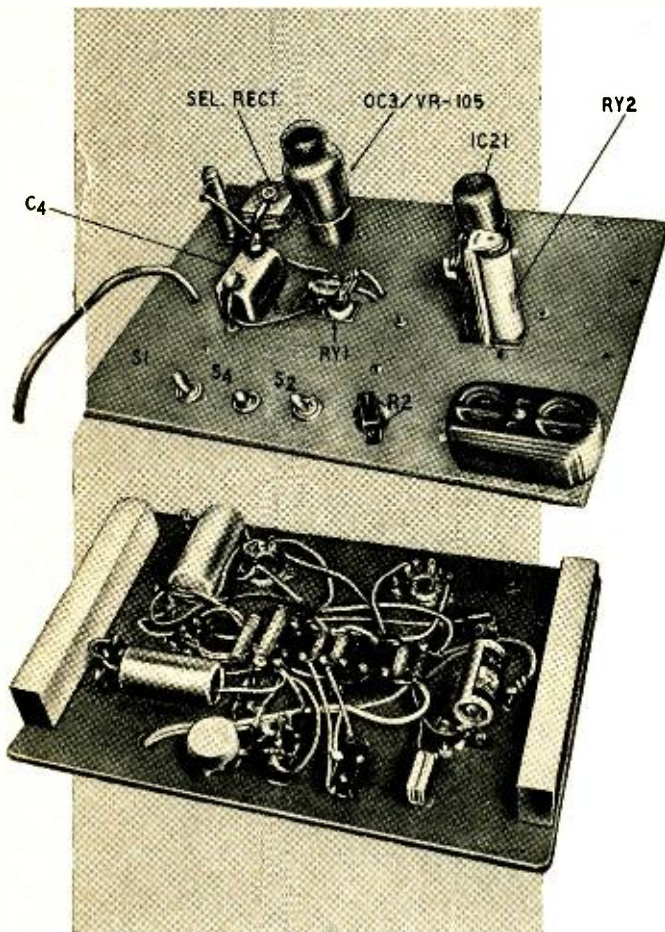Turns equipment on or off after any time period from 6 seconds to 15 hours or more



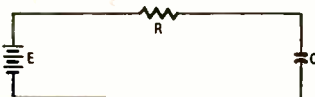(Above) Timer layout and wiring. Fig. 1 (below)—Basic time-constant circuit. Fig. 2 (right)—Schematic of the timer. Type 1C21 is a cold-cathode thyratron triode.



IT IS often convenient and sometimes necessary to have a means of turning various types of electrical equipment on or off automatically, after a predetermined time interval. This electronic interval timer does just that, and combines versatility, dependability, and ease of operation with low cost, simple construction, and minimum operating power.


The design of the electronic interval timer is based on the characteristics of an R-C circuit when connected to a d.c. voltage supply. See Fig. 1. The time the capacitor will take to charge to the applied voltage E can be computed from the circuit constants. Such time *t* is represented by the formula

$$t = -RC \left(\log_e \frac{EC - q}{EC} \right)$$

where R is the resistance in ohms, C is the capacitance in farads, \log_e is the natural logarithm, E is the supply voltage, q is the required charge in coulombs, and t is the time required in seconds. The charge is equal to the product of the capacitance in farads and the voltage across the capacitor. Thus the time it takes for the voltage across a capacitor to build up to a predetermined value is directly proportional to the resistance in series with the capacitor. Any time desired to bring the capacitor up to a certain charge q can be obtained by changing R while maintaining C and E constant. The design of the electronic interval timer has been based on this relationship.

Circuit operation

The operation of the timer circuit (Fig. 2) is relatively simple. When the power switch S1 and the timer switch S2 are closed, C1 begins to charge through R1 and R2. When C1 has charged to the breakdown potential of V1, V1 conducts and energizes relay RY1. This closes RY1's relay contacts which in turn causes C2 to charge through R3 or R4, depending on the position of S4. When V1 conducts, C1 discharges rapidly through the low resistance of RY1 and V1 until the extinguishing potential of V1 is reached. When this happens relay RY1 is de-energized and RY1's contacts open again.

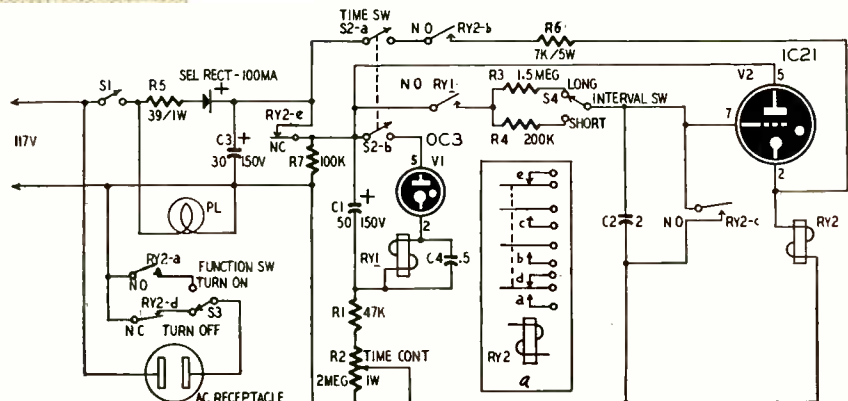

You can build a better Auto Radio Repair Business!



Yes, you can build a better car radio repair business with the help of Delco Radio and here is why: fully one-half the cars that pass your door are Delco Radio-equipped; Delco Radio alone can supply you with Delco Radio original equipment replacement parts plus universal replacement parts; Delco alone can supply you with a complete and comprehensive Delco Radio Service Manual plus monthly issues of "Testing Tips," a bulletin giving the very latest factory information on testing and repairing Delco car radios—even the sensational new "Favorite Station" Signal-Seeking model! To get this start toward a better car radio repair business you need only be on the Delco Radio team—you need only get together with your nearest United Motors Electronics Distributor. Don't delay . . . act today!

DELCO RADIO

DIVISION OF GENERAL MOTORS CORPORATION, KOKOMO, INDIANA

A GENERAL MOTORS PRODUCT  A UNITED MOTORS LINE

DISTRIBUTED BY ELECTRONICS WHOLESALERS EVERYWHERE





**That's Why Top Service Men
Install PERMA-TUBE
the Mast that's UP TO STAY**


Television set owners aren't happy when the set goes out on a big night and the antenna is ruined because an inferior mast failed from inside corrosion or high winds during a storm.

That's why more and more smart service men are protecting their reputations for good work by installing J&L Perma-tube TV masts. They've found that—1. PERMA-TUBE is made of special high-strength J&L steel that stays up in storms that flatten masts of conduit or other types of tubing. 2. PERMA-TUBE is pretreated with vinsynite and then coated inside and out with a metallic vinyl resin base. The result—corrosion proof masting that doesn't weaken or cause ugly rust streaks on the customer's home. 3. PERMA-TUBE is easy and economical to install—the only mast with both ends of the joint machine fitted.

You can get PERMA-TUBE in standard lengths, diameters and wall thicknesses. Write today for complete information and the name of your nearest distributor.

HERE'S INSIDE INFORMATION ON WHAT CORROSION DOES

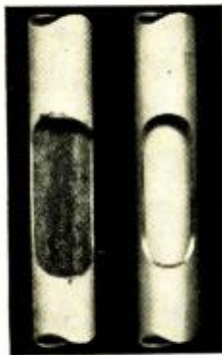Section of ordinary conduit tubing used for TV masts after 96 hours in a salt spray test (A.S.T.M. Designation B-117-49T) to accelerate corrosion. Extensive rust inside the mast has reduced strength—caused rusty water to drain onto the owner's home.



Section of PERMA-TUBE after 500 hours salt spray test shows no evidence of corrosion. Strength has been retained and the chance of rust streaks on owner's home are eliminated. Note sturdier wall thickness of Perma-tube sample.

FOR COMPLETE INFORMATION MAIL THIS COUPON TODAY



Jones & Laughlin Steel Corporation
496 Gateway Center
Pittsburgh 30, Pa.

Without charge, please send me: Name of nearest distributor
 Complete information on Perma-tube

Name _____
Company _____
Address _____

This cycle repeats itself until the charge on C2 reaches the potential necessary to break down V2. When V2 conducts, the control relay RY2 is energized; this closes contacts RY2-a, RY2-b, and RY2-c, and opens contacts RY2-d and RY2-e. RY2-a can turn on an external electrical appliance; RY2-d can turn off an external electrical appliance; RY2-e turns off the timing circuit when relay RY2 is energized; contacts RY2-b are holding contacts to keep relay RY2 energized; and contacts RY2-c discharge C2 after relay RY2 has been energized.

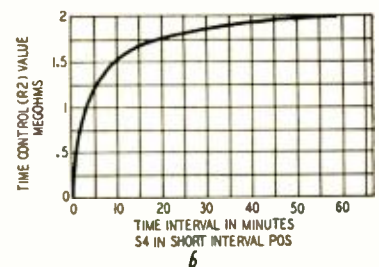
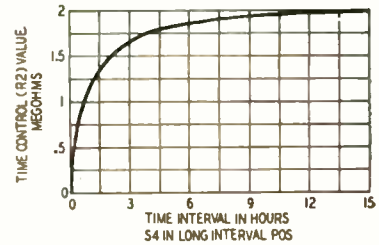


Fig. 3—Approximate long- and short-interval calibration curves for use with a linear timing-control potentiometer.

Resistors R3, R4, and the potentiometer R2 determine the time interval before relay RY2 is energized after the timer switch S2 has been closed. R2 determines the time it takes to charge C1 to the breakdown voltage of V1 and resistors R3 and R4 determine the number of times relay RY1 must energize before C2 charges to the breakdown potential of V2. (R3 is for long intervals and R4 is for short intervals.)

Since C1 is an electrolytic capacitor, there is some leakage through it, which causes the time required to charge C1 to a predetermined voltage to vary nonuniformly with uniform changes in the resistance of R2. This leakage is generally constant as long as the capacitor does not deteriorate, and thus does not affect the operation of the circuit. R1 is the critical resistance needed to make the circuit operate.

R5 and R6 are current-limiting resistors and R7 is a bleeder. C3 is the filter capacitor. C4 smooths out the current pulses passing through RY1. The pilot lamp PL was added to the circuit to provide a constant light source for V1. Gas-filled V-R tubes can be partially ionized by light, and this lamp helps maintain the breakdown potential of V1 at a constant value.

Using the timer



To operate the electronic interval timer, plug the timer line cord into any convenient a.c. outlet. Plug the electrical appliance to be controlled into the a.c. receptacle on the timer. Throw control switch S3 to the position desired

RCA VoltOhmysts*

*outsell all other
VTVM'S*

RCA WV-97A
SENIOR VoltOhmyst
\$67.50 Suggested
User Price

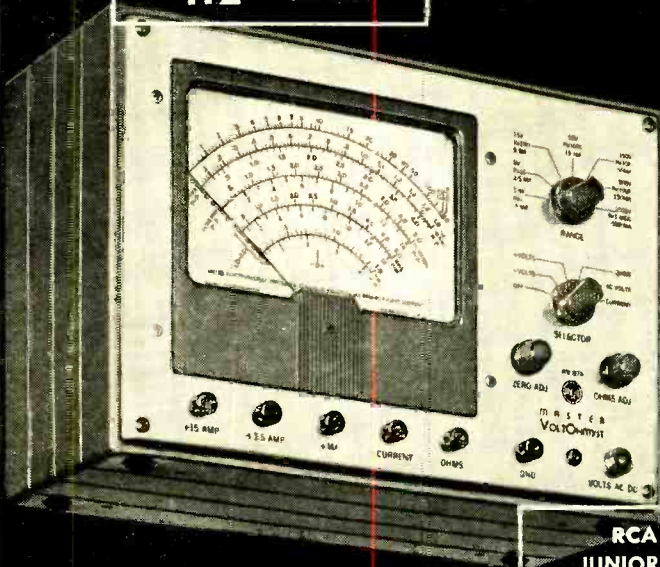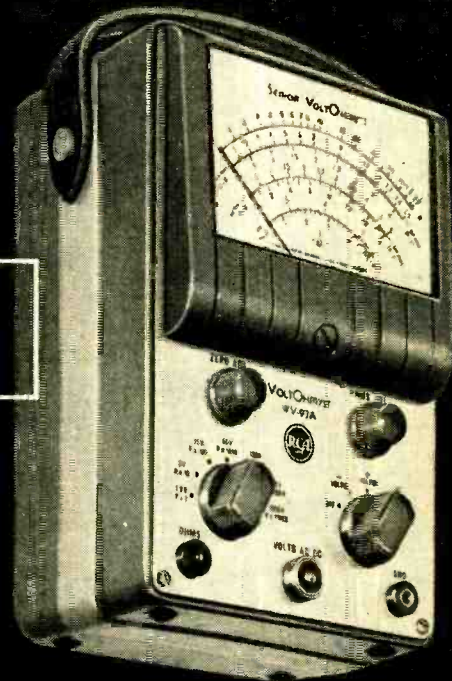RCA WV-87A
MASTER VoltOhmyst
\$112.50 Suggested
User Price



RCA WV-77A
JUNIOR VoltOhmyst
\$47.50 Suggested
User Price



Because they're factory-calibrated under laboratory conditions... incorporate more features... have unusual accuracy and stability... in short, offer you more for your money—RCA VoltOhmysts outsell all other makes of vacuum-tube voltmeters.

All RCA VoltOhmysts employ a degenerative bridge circuit to compensate for line-voltage changes... a sturdy 200-microampere meter movement electronically protected against burn-out... large,

easy-to-read scales... metal shielding against external fields... and have an input resistance of 11 megohms on all dc ranges.

Before you buy a vacuum-tube voltmeter, be sure to get the full details on the RCA VoltOhmyst best suited to your needs. See your RCA Test Equipment Distributor today... or write RCA, Commercial Engineering, Section 67CX, Harrison, N. J.

*Tmk®




RADIO CORPORATION of AMERICA
TEST EQUIPMENT

HARRISON, N. J.

the latest!

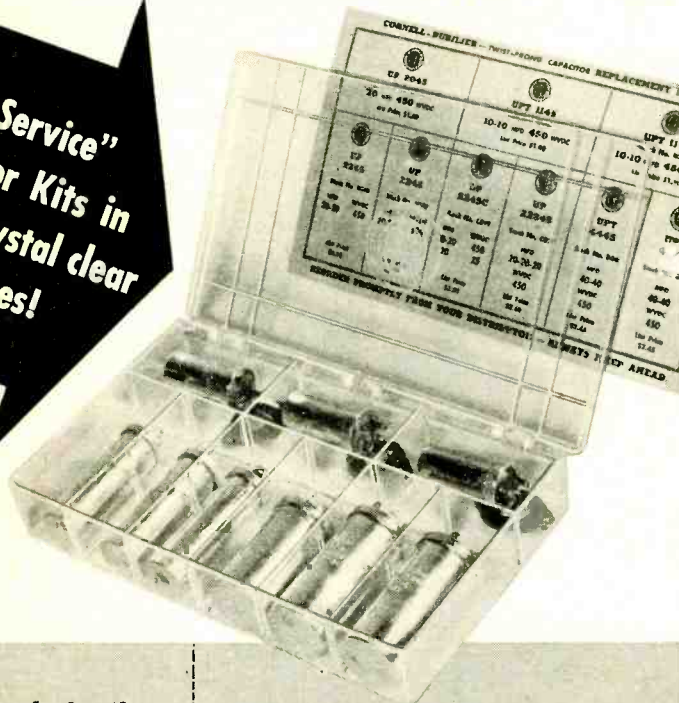"Quick Service"
Capacitor Kits in
handy crystal clear
plastic cases!



And you pay *only* for the capacitors. Case costs you nothing.

6 kits for practically every possible twist-prong electrolytic capacitor replacement. Designed to service most TV sets.

See this new packaging of dependable Cornell-Dubilier electrolytics at your jobber today. Cornell-Dubilier Electric Corp., So. Plainfield, N. J.

- KIT #1 — UNIVERSAL
- KIT #2 — FOR RCA SETS
- KIT #3 — FOR PHILCO SETS
- KIT #4 — FOR MOTOROLA SETS
- KIT #5 — FOR GENERAL ELECTRIC SETS
- KIT #6 — FOR ADMIRAL SETS

A service of

CORNELL-DUBILIER

world's largest maker of capacitors

PLANTS IN SO. PLAINFIELD, N. J. • NEW BEDFORD, WORCESTER AND CAMBRIDGE, MASSACHUSETTS • PROVIDENCE, R. I. • INDIANAPOLIS, INDIANA • FUQUAYS SPRINGS, NORTH CAROLINA • SUBSIDIARY, RADIART CORP., CLEVELAND, OHIO

(TURN ON OR TURN OFF). Then set the timing control R2 for minimum time, turn on the switch S1 and allow a warmup period of 30 seconds. After this, set the time control R2 and the interval switch S4 for the time interval desired. The timer can then be thrown into operation at any time by simply throwing S2 to its ON position.

The time intervals for which the timer can be set cover a large range. The shortest interval is 6 seconds and the longest is 15.5 hours. However, the longest time interval can be increased easily to cover a period of several days by replacing R3 with a larger resistor (20 to 40 megohms).

Materials for Timer:

Resistors: 1—7,500 ohms, 5 watts; 1—39 ohms, 1 watt; 1—1.5 megohms, 1—200,000 ohms, 1—100,000 ohms, 1—47,000 ohms, 1/2 watt; 1—2-megohm, 1-watt potentiometer, linear or logarithmic taper (see text).
Capacitors: (Electrolytic) 1—50 μ f, 150 volts, (Paper) 1—2 μ f, 1—0.5 μ f, 600 volts, oil-filled.
Miscellaneous: 1—OC3/VR-105, 1—IC21; 1—100-ma selenium rectifier; 1—s.p.s.t. relay (normally-open contacts), coil resistance 1,280 ohms, Leach type P-3 or equivalent; 1—5-pole, s.t. relay (three contacts normally open; 2 contacts normally closed), coil resistance 350 ohms; 2 octal sockets; 1—117-volt pilot lamp and socket (see text); 1 s.p.s.t. toggle switch; 2 s.p.d.t. toggle switches; 1 d.p.s.t. toggle switch; 1 dual power-outlet receptacle; line cord and plug; terminals, hardware, wire, solder.

Applications

The electronic interval timer can be put to many uses. Around the home it can turn the radio or TV set off at night, or turn it on in the morning; turn a washing machine off after a certain time interval; or turn various lights on or off.

Usefulness can be greatly increased by using two timers at once. This makes it possible to turn an electrical appliance on after a predetermined time interval and off after another interval.

Construction details

Surplus parts were used throughout the electronic interval timer so that the total cost was less than \$10. A transformerless circuit was used, to reduce cost, weight, and size. Relays RY1 and RY2 were purchased from surplus stores for 25 cents each. Relay RY1 requires 12 ma to energize it and relay RY2 requires 23 ma. This relay may have four double-throw switch sections or it may have one set of s.p.d.t. contacts, two s.p.s.t. normally open contacts, and one s.p.s.t. normally closed contact. A schematic of RY2 is shown in Fig. 2-a. The lamp PL, used to illuminate V1, is not critical. Any small 117-volt lamp will do.

In installing relay RY2 it is very important to make sure that contact RY2-b close *before* contact RY2-c, otherwise sparking will occur when the relay is energized. The original time-control potentiometer R4 was a good-quality volume control with a linear taper. Since the time interval does not vary uniformly with the time-control setting, you can get better adjustment and a more linear calibration scale by using a control with a *logarithmic* taper. The graphs in Fig. 3 provide approximate calibration curves as a starting point. END

RADIO-ELECTRONICS

EASY TO LEARN CODE

It is easy to learn or increase speed with an Instructograph Code Teacher. Affords the quickest and most practical method yet developed. For beginners or advanced students. Available tapes for beginner's alphabet to typical messages on all subjects. Speed range 5 to 40 WPM. Always ready—no QRM.



ENDORSED BY THOUSANDS!

The Instructograph Code Teacher literally takes the place of an operator-instructor and enables anyone to learn and master code without further assistance. Thousands of successful operators have "acquired the code" with the Instructograph System. Write today for convenient rental and purchase plans.

INSTRUCTOGRAPH COMPANY

4701 Sheridan Rd., Dept. RC, Chicago, 40, ILL.

WANTED

WE NEED YOUR SURPLUS ELECTRONIC EQUIPMENT

WE PAY TOP \$\$\$ FOR:

- ★ RADIO RECEIVERS
- ★ TRANSMITTERS
- ★ ARC-1
- ★ ARC-3
- ★ ART-13
- ★ CONTROL BOXES
- ★ INDICATORS
- ★ CLAMPS
- ★ PLUGS
- ★ CORDS
- ★ RELAYS
- ★ TELEPHONE MATERIALS
- ★ AN CONNECTORS
- ★ WE BUY ANYTHING!

Write, Wire today! Tell us what you have.

TALLEN CO., Inc., Dept. RE
159 Carlton Ave., Brooklyn 5, N. Y.

FAR BETTER RECEPTION

IN EVERY LOCATION

with Sensational New

TRIO ZIG-ZAG

Patent Pending

TV ANTENNAS




SUBURBAN MODELS

Models ZZ4A and ZZ6A give you all-channel (2 thru 13) reception in ONE SINGLE BAY ANTENNA. The Model ZZ4A has excellent gain and is designed for suburban areas. Model ZZ6A has even greater gain and provides excellent all-channel reception in near fringe areas.




NEAR FRINGE MODELS

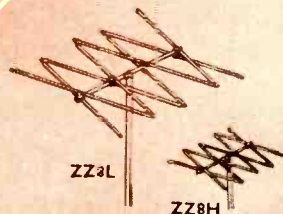For near fringe area reception, the Models ZZ6L and ZZ6H are recommended. Model ZZ6L covers Channels 2 thru 6, Model ZZ6H is for Channels 7 thru 13. Both antennas offer high gain with patterns and front-to-back ratios similar to cut-to-channel yagis.




FRINGE MODELS

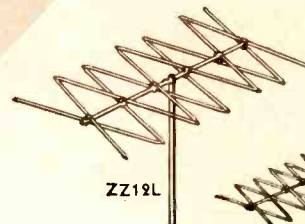Models ZZ8L and ZZ8H were designed for normal fringe area reception and provide clear, snow-free pictures. Forward lobe patterns and front-to-back ratios are similar to a good single channel, multi-element yagi.




ULTRA FRINGE MODELS

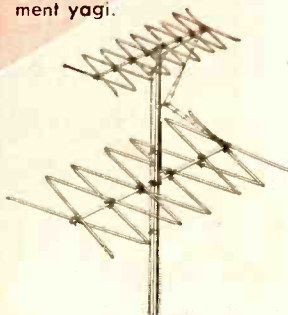The extremely high gains of the ZZ12L and the ZZ16H models provide unequalled reception in ultra-fringe areas. Model ZZ12L covers Channels 2 thru 6 and Model ZZ16H, Channels 7 thru 13. These two models when stacked, are fed with only one 300 ohm line and provide ALL VHF CHANNEL RECEPTION. Line match is excellent and front-to-back ratios are unusually high.



ZZ12L and ZZ16H are stacked for all VHF Channel Reception

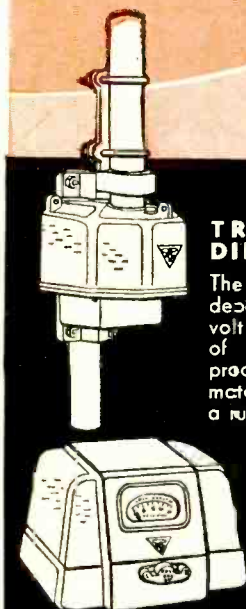* To provide even greater strength, TRIO Antennas now have stamped steel element clamps.



TRIO ROTATOR AND DIRECTION INDICATOR

The TRIO Rotator is America's most dependable — has two powerful 24 volt motors — one for each direction of rotation. Absolutely weather-proof, permanently lubricated. All motors, shafts and gears mounted on a rugged, one-piece casting for true alignment, strength and longer life. Every TRIO Rotator fully guaranteed for two years! Beautiful Direction Indicator has "finger tip" control — no need to hold knob for rotation. A touch of the finger starts it — a touch stops it!



TRIO

TRIO MANUFACTURING COMPANY

GRIGGSVILLE, ILLINOIS

New! Up-to-date!



TELEVISION SERVICING

by **Walter H. Buchsbaum**

Get this brand new, complete handbook for sure-fire working knowledge of TV installation, maintenance and troubleshooting. Tells you step-by-step procedures for audio IF alignment, video IF alignment, aligning RF amplifiers, mixers, oscillators, etc. All possible defects classified for ready reference, thoroughly analyzed to show what is wrong and why . . . and what to do to correct the defect. No mathematical knowledge needed! Practical, authoritative, up-to-the minute, the perfect handbook for set owners, trainees, and repairmen.



Symptoms of defective operation easily recognized, quickly corrected by illustrations, diagrams and how-to-do-it facts in this new book.

USE IT 10 DAYS FREE

Coupon below brings you "Television Servicing" on FREE trial for 10 days, without obligation. Mail it NOW.

PRENTICE-HALL, INC., Dept. M-RE-453A
70 Fifth Ave., New York 11, N. Y.

Send me, for 10 DAYS' FREE TRIAL, "Television Servicing." I will return it in ten days and pay nothing—or keep it and send \$1.35 down (plus postage) and \$2 monthly for 2 months.

NAME.....
 ADDRESS.....
 CITY..... ZONE..... STATE.....

SAVE! Send \$5.35 with this coupon, and we'll pay postage and packing.



HAVING TROUBLE GETTING FAR AWAY TELEVISION STATIONS UP TO 125 MILES AWAY—OR MORE?


If you're in **FRINGE** area— not right next door or fairly close to the television stations you want to get, you need the **DAVIS VHF SUPER-VISION ALL-CHANNEL ANTENNA**. For ALL CHANNELS.

The **DAVIS SUPER-VISION** is one of the three basic elements necessary for **FINE RECEPTION**. It's actually as important as a fine television receiving set. So, when you buy, **BUY RIGHT—all the way through: Set, Antenna and Leadline**. And the services of a competent television technician to make the installation. If you miss on one, you'll miss what you're really buying: **AMERICA'S FINEST TELEVISION RECEPTION**.

The **DAVIS STORY** is a **BIG STORY**— in performance. *Get all the facts.* Aside from distance and **DX** reception, know about the "other ten" important features.

PRICED RIGHT for such fine reception. List only \$34.95. Worth every cent of its cost with "the price forgotten long after fine reception remains."

WHAT'S YOUR ANSWER TO THIS QUESTION?

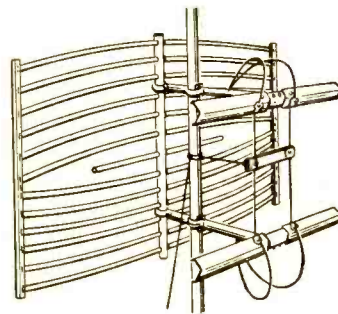

DAVIS SUPER-VISION FOR FRINGE AREA & DX

"The Original Antenna Sold With A Money-Back Guarantee"

Built By America's Fastest Growing Antenna Manufacturer


AT YOUR JOBBERS, or MAIL COUPON TO:

DAVIS ELECTRONICS 1-30
 4313 West Magnolia Blvd., Burbank, California
SIRS: RUSH INFORMATION TO ME AS CHECKED BELOW:

Send Free Technical Data on new **SUPER-VISION ANTENNA**.
 Send Name and Address of **NEAREST JOBBER**.
 Name.....
 Street.....
 City..... State.....

ELECTRONIC'S LATEST TROUBLE-SHOOTER

A compact—complete—circuit analyzer

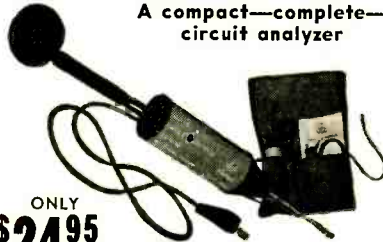

ONLY \$24.95

Model E-C (Pat. Pending)

THE AMAZING TV SERVISSET

A precision engineered professional quality electronic test instrument. Ideal for field or bench servicing of Radio, Television, Radar, Communications gear, etc. Now—Quickly—Conveniently—At Low Cost
CHECKS: sync, sweep, video, audio circuits, TV high voltage supplies (DC, RF, or Pulse), low voltage supplies, coils, condensers, resistors, tubes, transformers, speakers, etc. Will localize trouble to a particular stage, determine defective component and can actually be clamped in circuit to restore circuit operation temporarily in 80% of component or tube defects. Ideal for locating and confirming intermittents.

SPECIFICATIONS:

RF & AF Signal Tracer, RF & AF Signal Injector, AC & DC Voltage Indicator 0-50, 550/20,000, Dc Polarity Indicator 60/550/20,000 volts, Lo ohms 0-5, Hi ohms 0-500k-20 megohms, Tests Condensers, .00025-12 mfd., Tests Resistors 2 ohms—20 megohms, 2 Capacitance Sub ranges, .01-1 & 4-40 mfd., 3 Resistance Sub ranges 50-500 ohms, 5k-25k, 100k-1 meg.

Will complement your existing equipment and will outperform other testers costing many times more.

A MUST FOR THE MODERN TV AND ELECTRONICS SERVICE ENGINEER.


Comes in handy cloth pouch, complete with all accessories including ALNICO phone, TV high voltage adapter, phone extension cord, test lead, Klipson adapter and complete detailed instruction Manual, disclosing latest TV trouble-shooting techniques.

See Serviset at your distributor today. If he can't supply, order direct from factory, \$24.95 postpaid.



LEE ELECTRONIC LABS., INC.

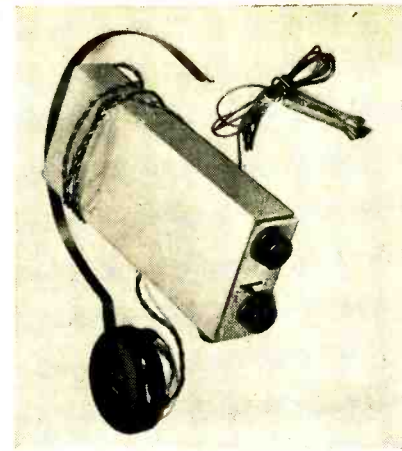Dept. RE-4, 233 Dudley Street
 Boston 19, Mass.



Appearance of the vest-pocket receiver.

TWO-TUBE POCKET SET USES FAMOUS CIRCUIT

By **NICHOLAS A. TAX**

It was my ambition to build for myself a true vest-pocket radio set—one that would tune in all the local stations with good selectivity. Much time and many experiments resulted in the one described below.

The circuit I use is the old "three-circuit tuner," which dates back to the beginning of radio itself. Years ago it was considered highly sensitive and capable of reaching great distances, but was a bulky thing. The "vario-coupler" itself was about 3 inches in diameter and 4 inches long, and the set required a good antenna and ground.


The tuned circuit

What I did here was to re-create the variocoupler in miniature and in a different form. The antenna and grid coils are wound on a rectangular plastic form $2\frac{1}{4} \times 4\frac{1}{16} \times \frac{3}{4}$ inches. This form is actually part of the tiny chassis. The antenna winding, L2, consists of 7 feet of No. 26 enameled wire. The grid winding, L3, has 25 feet 6 inches of the same wire. The two coils are spaced about $\frac{3}{16}$ -inch apart. This spacing allows a shaft to run through to L1, the tickler coil. I worked with this coil for about two months, trying to figure a way to control regeneration without enlarging the size of the set. Finally I hit on the idea of winding the tickler coil on a tiny triangular form fitted in one corner of the grid coil. When its windings are brought parallel to the grid coil, regeneration is at its highest point. This worked beautifully. The tickler coil is 18 feet of Belden 5-44 Litz wire, wound on a triangular form $\frac{3}{8} \times 1\frac{1}{4} \times 1\frac{1}{4}$ inches. This form is made from cardboard dipped in liquid plastic. The shaft was made from an

Accurate CAPACITANCE METER

Combined With a True VTVM

Measures Capacitance directly on a large 6½ inch scale . . .
As low as 0.5 mmf . . . As high as 1000 mf . . . In 7 ranges . . .

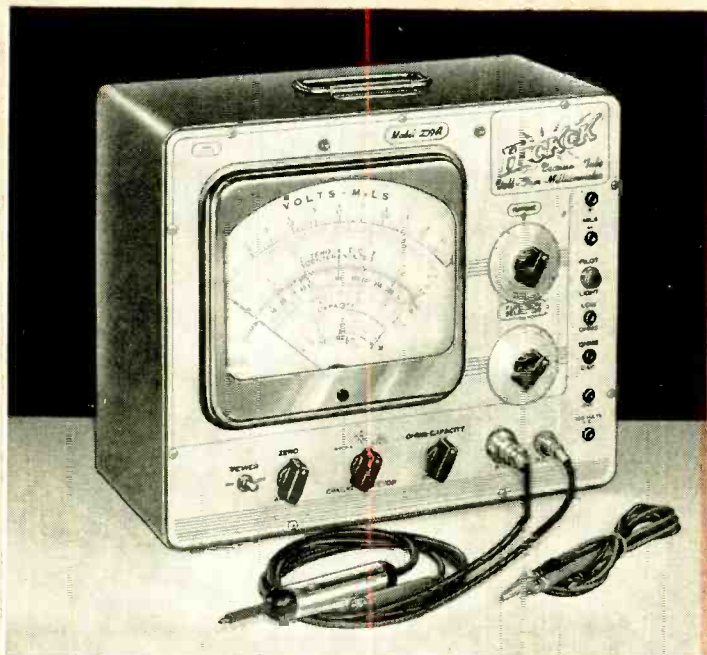


Model 209A

In addition to being an accurate capacitance meter, the 209A furnishes the following readings on a large, 9-inch colored scale:

- DC Volts, 0-1200 in 6 ranges
- AC, RMS Volts, 0-1200 in 6 ranges.
- AC, Peak to Peak Volts, 0-1200 in 6 ranges.
- AF, IF and RF voltages from 10 cycles to 300 megacycles.
- 0.1 ohm to 10,000 megohms in 7 ranges.
- 50 mh to 100 henries.
- DC Mils, 0-1200 in 6 ranges.
- DC Zero-center scales, 0 to ±1200 volts.
- Decibels -20 to +25 in 3 ranges.
- AC input impedance: 8 mmf, shunted by 12 megohms.
- DC input impedance: Approximately 12 megohms.
- Built-in power supply permits high accuracy even with wide line-voltage fluctuation.

This HICKOK Model 209A is years-proven in the most demanding field and laboratory use. It is, without a doubt, the most dependable and accurate instrument of its kind. These 209A's seem never to fail in service, cause trouble, or wear out . . . And don't forget, the high frequency probe and leads are included. Also a high voltage probe is available to extend DC range to 30,000 volts.

ACTUAL
SIZE

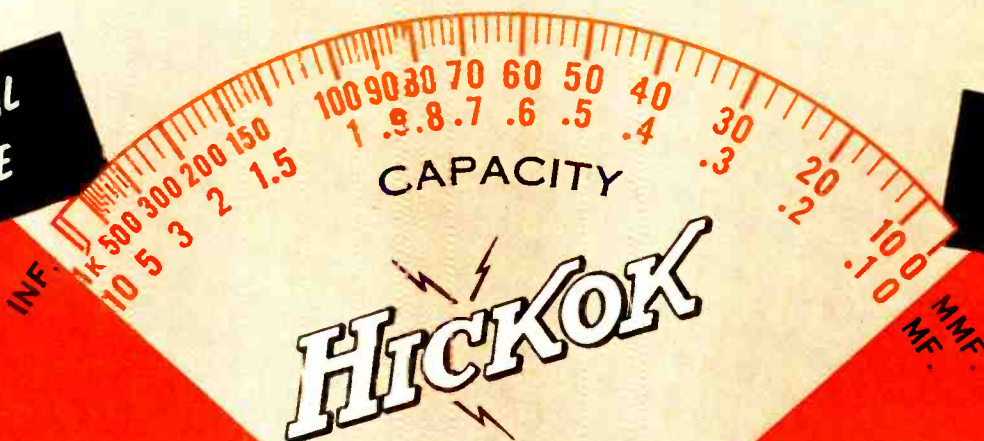


EASY TO
READ

THE HICKOK ELECTRICAL INSTRUMENT COMPANY

10531 Dupont Avenue

Cleveland 8, Ohio

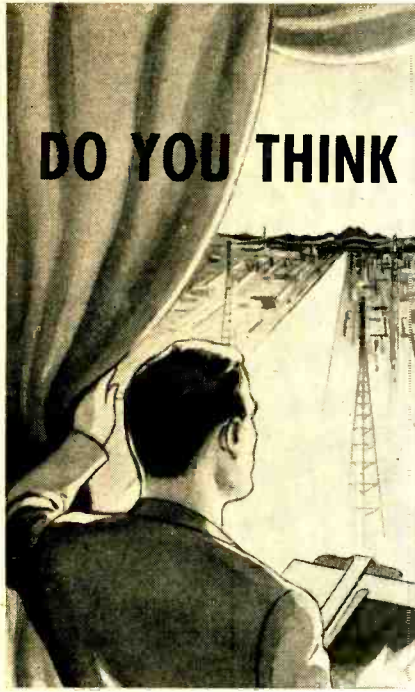Ask for a demonstration of the HICKOK Model 209A at your Jobber's today!



**DO YOU THINK
CREATIVELY
in
ELECTRONICS
PHYSICS
MECHANICS**

We are seeking several men with *creative* minds—men able to think, beyond today's realities. You should have a well-rounded background in electronics or an allied field.

We offer *freedom* not only to envision your ideas but also to carry them to completion. You will work on the problems of color television, radar, radio with the most advanced equipment, and as a member of one of industry's foremost engineering teams. To the right man we offer a lifetime career opportunity.

Write to us in full confidence. We want an opportunity to explain to you the many benefits of working and creating with this organization.

All the members of our staff know of this advertisement.

Write to Box S4-53

c/o **RADIO-ELECTRONICS**
25 WEST BROADWAY
NEW YORK 7, N. Y.

8-penny nail. One end was ground down to about $\frac{1}{16}$ inch diameter and forced through the bottom of the form. A small piece of brass shim stock was soldered to the nail and clipped into the cardboard to strengthen it. Just above the shaft the fine wire was wound in three layers, one on top of the other, approximately 6 feet to the layer, with hot paraffin wax between each layer. This was done to prevent the following layer from displacing the other.

The tuning capacitor will be of special interest. I made a frame from 1-inch angle iron (dressed down considerably) and bent down a third side. To this I fitted a 100-580- μmf trimmer capacitor, removed the set-screw, placed a small block of brass on the blade, and made a shaft with an eccentric that moves the brass block, thus opening and closing the blade of the trimmer capacitor. There is less than a 180° turn with the knob which covers from 740 to 1600 kc. I tried various amounts of wire in the grid coil trying to get it to tune down to 550 kc, but gave up. Evidently a bigger trimmer capacitor is needed to do this. I did try a 45-380- μmf trimmer capacitor but had no luck.

The end of the tuning capacitor shaft is ground flat to prevent the knob from slipping.

Hand-made components


The switch was made from brass shim stock, as were the battery clips. The shim stock I was using was brittle and it was necessary to anneal it with a blowtorch so that it could be bent without breaking. All brass and metal parts were tinned with solder to give them a nice appearance and to prevent corrosion.

The plastic chassis was made from a refrigerator dish. Pieces were cut from it and cemented together with liquid plastic. It looks almost as if it had been molded in one piece.

Thin-head rivets were not available, so I used galvanized screen-wire tacks with the heads ground down almost paper thin.

To prevent the heat of the soldering iron from melting the plastic chassis under small brass parts, wires were soldered to them before they were riveted in place. This may not have been necessary, as I soldered one connection (A plus on battery clip) and immediately applied a damp cloth to it, with no harm to the chassis.

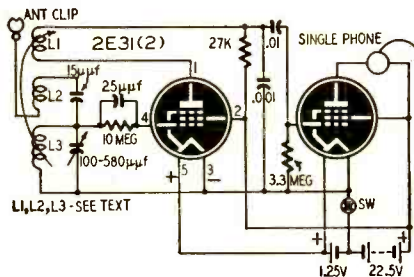
The set uses two 2E31 subminiature tubes, a hearing aid A cell, a 22½-volt B battery, small ceramic capacitors, and ½-watt resistors.



The vest-pocket receiver uses the ancient but excellent 3-circuit tuner.

**Here's how to
SAVE MONEY ON
INSTRUMENTS!**

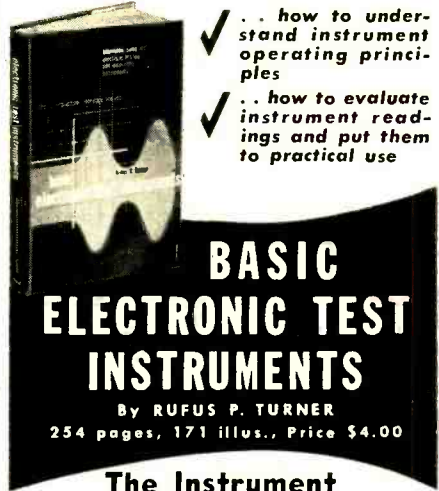- ✓ ... how to do faster, better testing with fewer instruments
- ✓ ... how to increase the usefulness of your present instruments
- ✓ ... how to choose the right instrument for each job



- ✓ ... how to understand instrument operating principles
- ✓ ... how to evaluate instrument readings and put them to practical use

**The Instrument
Book Written Especially for
SERVICEMEN • AMATEURS
• EXPERIMENTERS**

★ HERE'S a brand new book that can save you money on instruments and help you use your present instruments lots more efficiently!

Over 60 instruments—from the most modern TV pattern generators to special-purpose bridges—are carefully described. Their uses are fully explained and valuable work-saving short cuts outlined.

Included are complete details on simple meters for current and voltage; ohmmeters and V-O-M's; V-T voltmeters; power meters; impedance meters; capacitor checkers; inductance checkers; special-purpose bridges; oscilloscopes (this material alone is worth the entire price of the book to busy servicemen!); r-f test oscillators and signal generators; audio test oscillators; radio frequency and audio frequency measuring devices; audio-amplifier testing devices; r-f signal tracers and tube testers.

Among other things, BASIC ELECTRIC TEST INSTRUMENTS is a complete training course in the latest instruments including grid-dip oscillators, TV sweep and marker generators; TV linearity pattern generators, square-wave generators, distortion meters and others.

SEE WHAT IT CAN DO!

You are shown new uses for VOM's, scopes, signal generators and other old standbys. You learn how easy it is to extend the range of many old instruments; how power drain measurements can be used for fast TV troubleshooting; how a useful and accurate bridge can be built from a combination of familiar general-purpose instruments; how to calculate shunts and multipliers; how to measure r-f impedance with a simple T-network; how to measure inductance and capacitance with a grid-dip oscillator and scores of other money-saving "tricks".

Just off the press! Read BASIC ELECTRIC TEST INSTRUMENTS for 10 days at our risk!

10-DAY FREE EXAMINATION


Dept. RE-43, Rinehart Books, Inc., Technical Division, 232 Madison Ave., New York 16, N. Y.

Send Turner's BASIC ELECTRIC TEST INSTRUMENTS for 10-day FREE EXAMINATION. If I decide to keep book, I will then remit \$4.00 plus postage. Otherwise I will return book post-paid promptly and owe you nothing.

Name _____
Address _____
City, Zone, State _____

Employers Name and Address _____
OUTSIDE U.S.A.—Price \$4.50, cash only. Money back if book is returned postpaid in 10 days.

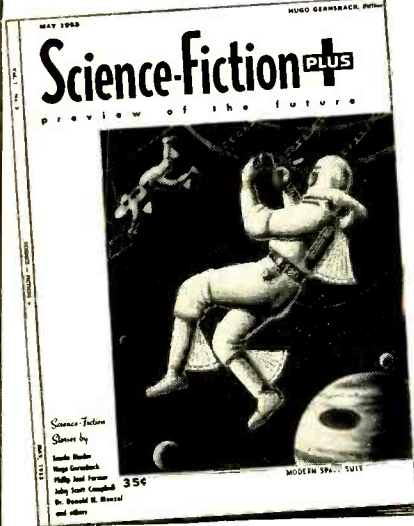Watch for this
NEW
GERNSBACK MAGAZINE
Instructive • Entertaining



ON SALE APRIL 10


Reserve a copy at your favorite newsstand now.

The New Model 670-A

SUPER-METER

a combination

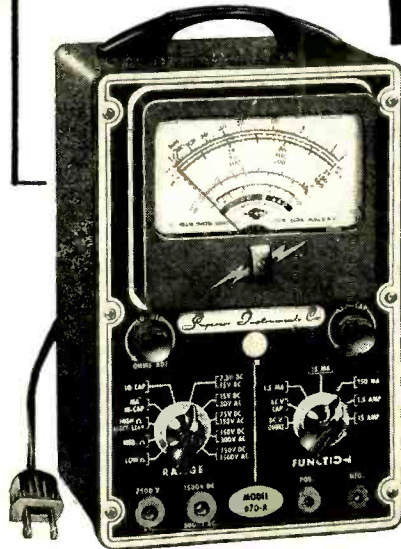VOLT-OHM MILLIAMMETER plus
CAPACITY REACTANCE, INDUCTANCE
and DECIBEL MEASUREMENTS



SPECIFICATIONS:

- D.C. VOLTS: 0 to 7.5/15/75/150/750/1,500/7,500 Volts
- A.C. VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
- OUTPUT VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
- D.C. CURRENT: 0 to 1.5/15/150 Ma. 0 to 1.5/15 Amperes
- RESISTANCE: 0 to 1,000/100,000 Ohms 0 to 10 Megohms
- CAPACITY: .001 to 1 Mfd. 1 to 50 Mfd. (Quality test for electrolytics)
- REACTANCE: 20 to 2,500 Ohms 2,500 Ohms to 2.5 Megohms
- INDUCTANCE: .15 to 7 Henries 7 to 7,000 Henries
- DECIBELS: -6 to +18 +14 to +38 +34 to +58

The Model 670-A comes housed in a rugged crackle-finished steel cabinet complete with test leads and operating instructions. Size 6 1/4" x 9 1/2" x 4 1/2"

\$28⁴⁰
NET

ADDED FEATURE

The Model 670-A includes a special GOOD-BAD scale for checking the quality of electrolytic condensers at a test potential of 150 Volts.

AT YOUR RADIO PARTS JOBBER

Write Dept. RC-4 for complete catalog.

Manufactured and Guaranteed by

SUPERIOR INSTRUMENTS CO.
227 Fulton Street • New York 7, N. Y.


Get This Valuable Book

Just for Examining COYNE'S New 6-Volume Set

FREE



"Applied Practical Radio-Television"

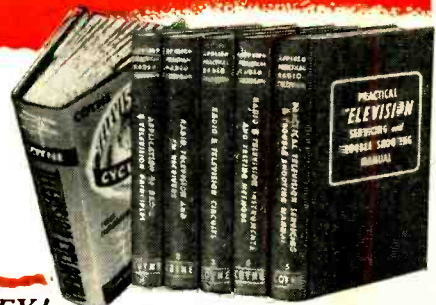

Yes, you get this big, brand new book, "150 Radio-Television Picture Patterns and Diagrams Explained", absolutely FREE! Just off the press! Gives complete wiring circuits and diagrams on the latest Radio and Television Sets. Easy-to-read, large 8 1/2 x 11" pages, with full instructions on how to read and use the diagrams. A "must" in every Radio and Television service-man's repair kit. You get this valuable book as a FREE Gift for asking to see Coyne's great new 6-book set, "Applied Practical Radio-Television"!

Here's "Know-How" That Makes You Worth More!

Coyne's great new 6-volume set gives you all the answers to servicing problems—quickly! For basic "know-how" that is easy to understand, you'll find everything you want in volumes 1 to 5 which contain over 5000 practical facts and data. They cover every step from principles to installing, servicing, trouble-shooting and aligning all types of radio and TV sets. So up-to-date it includes COLOR TV and UHF, adaptors and converters. Also covers very latest information on TRANSISTORS.

762-Page Television Cyclopeda Included

And then, for speedy on-the-job use, you get volume 6—the famous Coyne TELEVISION CYCLOPEDIA. It answers today's television problems on servicing, alignment, installation and others. In easy-to-find AEC order, cross indexed. Use this 6 volume TV-RADIO LIBRARY free for 7 days; get the valuable Servicing Book ABSOLUTELY FREE!

ON 7 DAY
FREE TRIAL!

SEND NO MONEY! Just mail coupon for 6-volume set on 7 days free trial. We'll include book of 150 TV-Radio Patterns & Diagrams. If you keep the set, pay \$3 in 7 days and \$3 per month until \$22.50 plus postage is paid. (Cash price \$29.95). Or you can return the library at our expense in 7 days and owe nothing. **YOU BE THE JUDGE. Either way, the book of TV-Radio Patterns is yours FREE to keep!** Offer is limited. Act NOW!

FREE BOOK—FREE TRIAL COUPON!

COYNE ELECTRICAL & TELEVISION-RADIO SCHOOL, Dept. 43-T1
500 S. Paulina St., Chicago 12, Ill.

YES! Send 6-volume "Applied Practical Radio-Television" for 7 days FREE TRIAL per your offer. Include TV-Radio Patterns & Diagram Book FREE.

Name.....Age.....

Address.....

City.....Zone.....State.....

Where Employed.....
() Check here if you want library sent COD. You pay postman \$20.95 plus COD postage on delivery. 7-day money-back guarantee.

COYNE ELECTRICAL & TELEVISION-RADIO SCHOOL
500 S. Paulina St., Dept. 43-T1 Chicago 12, Ill.

RIDER TEK- FILE*

packaged
tv
service
information—
factory-
authorized
factory-
approved
for easy
tv servicing...
tailor-made
for over
2800
receivers...
only
\$2 per pack

(at your jobbers)

*dependable replacement parts listing beginning with Pack 57

JOHN F. RIDER

Publisher, Inc.

480 Canal Street
New York 13, N. Y.


The audio is delivered by *one* head-phone from a standard, inexpensive 2,000-ohm pair of phones. A small metal head-band was cut from galvanized metal and fitted to the phone.

The two tubes were mounted in rubber, cemented to the chassis to prevent damage from shock and also to secure them nicely.

Very small terminal strips were used as tie-points. These were riveted in place on the chassis.

The case that houses the little set was made from cardboard and then given three coats of liquid plastic and two coats of enamel. The plastic gives it a smooth finish and stiffens it, rendering it unbreakable.

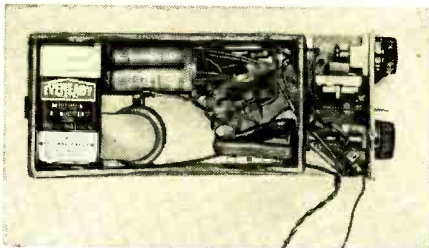As you will note on the circuit, I have a 15- μ f ceramic capacitor at the start of the antenna winding. This was installed after much experimenting and completely eliminates the use of a ground wire which is almost always necessary with the old variocoupler. Also note that the antenna lead is con-



Triangle at lower right is the tickler; the other coils are wound on the case.

nected to the end of the winding nearest the grid coil. This gave the best results, and greater distance was obtained.

This little set requires fine adjustment with both knobs to bring in distant stations, and with such adjustment, they can be brought in clear and loud. I find the best way to tune is to place the set in your shirt pocket so that your hands are free to adjust both knobs at the same time. I have brought in stations 1,300 miles away at night when conditions are good.

The finger-stop on a dial telephone seems to serve very well for the antenna, for local stations, also metal parts of table or floor lamps.

Materials for vest-pocket receiver

Resistors: 1—10 megohms, 1—3.3 megohms; 1—27,000 ohms, 1/2 watt.

Capacitors: 1—15, 1—25, 1—100- μ f, ceramic or mica; 1—.01 μ f, paper; 1—100-580- μ f trimmer (see text).

Tubes: 2—2E31

Miscellaneous: 1 s.p.s.t. miniature switch, 1 single phone, A and B batteries, case, wiring, coils, hardware, etc. Many of these items are described in the text.

To give this set a fair test it should be tried in a wood-frame building. I have had very little luck in steel structures. It may work differently in other localities.

The cost of the set was about \$8.50, including batteries, tubes, and head-phone. This does not include all the small parts made by hand. These would probably run the cost up pretty high, as I spent six months of my spare time building it. (I enjoyed every minute of it.)

END

Standard Brand Radio & T.V.

TUBES

Convince yourself. Send TODAY for our bi-weekly Bulletin of Excellent Tube Values. Dept. "C"

RMA Guarantee
Current Datings

MANNFRED
Electronics Corporation

Buickley 7-6555 6584

EFFECTIVE IMMEDIATELY: ALL TUBES INDIVIDUALLY BOXED IN ATTRACTIVE TWO COLOR BOXES AT NO EXTRA CHARGE!

136 LIBERTY STREET N. Y.

ANOTHER OUTSTANDING JOBBER

HURON SUPPLY CO. Inc.

119 W. Huron Street
Buffalo 1, N. Y.

HAS THE
SENSATIONAL NEW
TEICO 470-K 7"
SCOPE KIT
IN STOCK!

\$79.95

RADIO ENGINEERING 27 MONTHS
DEGREE IN 27 MONTHS

Inclusive, specialized course including strong basis in mathematics and electrical engineering, advanced radio theory and design, television, Modern lab. Low tuition. Self-help opportunities. Also B.S. degree in 27 months in Aeronautical, Chemical, Civil, Electrical, and Mechanical Engineering. G.I. Gov't approved. Enter June, September, December, March. Catalog.

INDIANA TECHNICAL COLLEGE
154 E. Washington Blvd., Fort Wayne 2, Indiana

EVERY RADIOMAN
Can Use These SERVICE HINTS!
Valuable Manual Yours—FREE!

Every page of "How to Simplify Radio Repairs" is packed with on-the-spot, practical ideas. Contains photos, charts, diagrams—no fluff—no vague theory. In plain every-day language it gives you priceless suggestions—new servicing ideas. You'll use and benefit from the experience of experts. Partial list of contents: How to Localize Trouble; How to Service Amplifiers; How to Test for Distortion; How to Test Audio Circuits; How to Test Speakers; How to Find Faults in Oscillators; How to Test Radio Parts—and it's all yours—FREE! No obligation.

FEILER SEND COUPON OR GOVERNMENT POSTCARD FOR YOUR FREE COPY TODAY!

FEILER ENGINEERING CO., Dept. 4RC3
8026 N. Monticello Ave.,
Skokie, Ill. (Suburb of Chicago)
Please return my FREE copy of "How to Simplify Radio Repairs."

Name.....
Address.....
City..... Zone..... State.....

BUY TEST EQUIPMENT ON THIS RADICALLY NEW TIME PAYMENT PLAN

NO INTEREST!! - NO CARRYING CHARGES!!

USE CONVENIENT TIME PAYMENT ORDER BLANK BELOW

Superior's New Model 770

VOLT-OHM MILLIAMMETER

Sensitivity—1000 ohms per volt

Uses latest design 2% accurate 1 Mil. D'Arsonval type meter. • Same zero adjustment holds for both resistance ranges. It is not necessary to readjust when switching from one resistance range to another. This is an important time-saving feature never before included in a V.O.M. in this price range. • Housed in round-cornered, molded case. • Beautiful black etched panel. Depressed letters filled with permanent white. Insures long-life even with constant use.

SPECIFICATIONS:

- 6 A.C. VOLTAGE RANGES: 0-15/30/150/300/1500/3000 Volts.
- 6 D.C. VOLTAGE RANGES: 0-7.5/15/75/150/750/1500 Volts.
- 4 D.C. CURRENT RANGES: 0-1.5/15/150 MA. 0-1.5 AMPS.
- 2 RESISTANCE RANGES: 0-500 Ohms 0-1 Megohm.



Model 770 is an accurate pocket-size V.O.M. Measures only 3 1/8" x 5 3/8" x 2 1/4".

\$14.90
NET

The Model 770 comes complete with self-contained batteries, test leads and all operating instructions.

Superior's New Model TV-11

TUBE TESTER



Operates on 105-130 Volt 60 Cycles A.C. Hand-rubbed oak cabinet complete with portable cover

\$47.50
NET

• Uses the new self-cleaning Level-Action Switches for individual element testing. Because all elements are numbered according to pin number in the RMA base numbering system, the user can instantly identify which element is under test. Tubes having tapped filaments and tubes with filaments terminating in more than one pin are truly tested with the Model TV-11 as any of the pins may be placed in the neutral position when necessary. • Uses no combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible to damage a tube by inserting it in the wrong socket. • Free-moving built-in roll chart provides complete data for all tubes. • Phone jack on front panel for plugging in either phones or external amplifier detects microphonic tubes or noise due to faulty elements and loose external connections.


Superior's New Model 670-A

SUPER-METER

A combination volt-ohm milliammeter plus capacity reactance inductance and decibel measurements

SPECIFICATIONS:

- D.C. VOLTS: 0 to 7.5/15/75/150/750/1,500/7,000 Volts
- A.C. VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
- OUTPUT VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
- D.C. CURRENT: 0 to 1.5/15/150 Ma. 0 to 1.5/15 Amperes
- RESISTANCE: 0 to 1,000/100,000 Ohms 0 to 10 Megohms
- CAPACITY: .001 to 1 Mfd. 1 to 50 Mfd. (Quality test for electrolytics)
- REACTANCE: 50 to 2,500 Ohms 2,500 Ohms to 2.5 Megohms
- INDUCTANCE: .15 to 7 Henries 7 to 7,000 Henries
- DECIBELS: -6 to +18 +11 to +38 +31 to +58

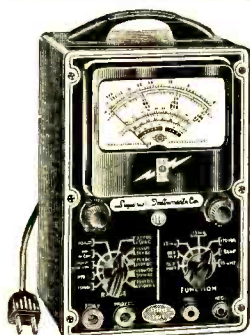

Comes housed in rugged, crackle-finished steel cabinet complete with test leads and operating instructions. Size 6 1/4" x 9 1/2" x 4 1/2".

\$28.40
NET

ADDED FEATURE
The Model 670-A includes a special GOOD-BAD scale for checking the quality of electrolytic condensers at a test potential of 150 Volts.

Superior's New

TV BAR GENERATOR

THROWS AN ACTUAL BAR PATTERN ON ANY TV RECEIVER SCREEN!!



TV Bar Generator comes complete with shielded leads and detailed operating instructions. Only

\$39.95
NET

**CONNECTS DIRECT TO ANTENNA POST
NO CONNECTION INSIDE RECEIVER**

Features—


Can be used when no stations are on the air. • Provides linear patterns to adjust vertical and horizontal linearity. • Provides vertical and horizontal sweep signals. • Provides signal for testing video amplifiers.

Superior's Model 660-A—A NEW A.C. OPERATED

SIGNAL GENERATOR

Provides Complete Coverage for A.M.—F.M. and TV Alignment

• Generates Radio Frequencies from 100 Kilocycles to 60 Megacycles on fundamentals and from 60 Megacycles to 220 Megacycles on powerful harmonics. • Accuracy and stability are assured by the use of permeability trimmed Hi-Q coils. • R. F. available separately or modulated by the internal audio oscillator. Built in 400 cycle sine wave audio oscillator used to modulate the R. F. signal also available separately for audio testing of receivers, amplifiers, hard of hearing aids, etc. • R. F. Oscillator Circuit: A high transconductance heptode is used as an R. F. oscillator, mixer and amplifier. Modulation is effected by electron coupling in the mixer section thus isolating the oscillator from load changes and affording high stability. • A. F. Oscillator Circuit: A high-mu triode is used as an audio oscillator in a high-C Colpitts Circuit. The output (over 1 Volt) is nearly pure sine wave. • Attenuator: A 5 step ladder type of attenuator is used.

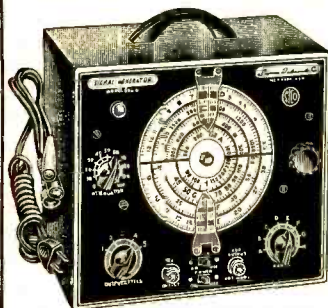

• Tubes used: 1—6BE6 as R. F. Oscillator, mixer and amplifier. 1—6BE6 as Audio Oscillator. 1—6HG as Power Rectifier.

The Model 660-A comes complete with coaxial cable, test lead and instructions

\$42.95
NET

NEW TIME PAYMENT PLAN

ORDER BLANK

MOSS ELECTRONIC DISTRIBUTING CO., INC.
Dept. B-54, 38 Murray Street, New York 7, N. Y.

Please send me the units checked below. I am enclosing the down payment with order and agree to pay the monthly balance as shown. It is understood there will be no carrying, interest or any other charges, provided I send my monthly payments when due. If it is further understood that should I fail to make payment when due, the full unpaid balance shall become immediately due and payable.

- MODEL 770 Total Price \$14.90
\$2.90 down payment. Balance \$2.00 monthly for 6 months.
- MODEL TV-11 Total Price \$47.50
\$11.50 down payment. Balance \$6.00 monthly for 6 months.
- MODEL 670-A Total Price \$28.40
\$7.40 down payment. Balance \$3.50 monthly for 6 months.
- TELEVISION BAR GENERATOR Total Price \$39.95
\$9.95 down payment. Balance \$5.00 monthly for 6 months.
- MODEL 660-A Total Price \$42.95
\$12.95 down payment. Balance \$5.00 monthly for 6 months.

I enclose \$_____ as down payment.
 Ship C.O.D. for the down payment.

Signature _____

Name _____

Address _____

City _____ Zone _____ State _____

ENGINEERS
AND
PHYSICISTS

attending the
NATIONAL
CONFERENCE
on
AIRBORNE
ELECTRONICS
Dayton, Ohio
May 11-13

INQUIRIES
ARE INVITED
REGARDING
OPENINGS ON
OUR STAFF

Radar Laboratories
Microwave Laboratories
Guided Missile Laboratories
Advanced Electronics Laboratories
Electron Tube Laboratories
Field Engineering Department

For the convenience of
those attending the Conference,
members of the Hughes
Laboratories Staff will be
available for interviews at
the Convention hotel.

HUGHES

RESEARCH AND
DEVELOPMENT LABORATORIES
Scientific and Engineering Staff
CULVER CITY, LOS ANGELES
COUNTY, CALIFORNIA

Assurance is required that relocation
of the applicant will not cause dis-
ruption of an urgent military project.

BRIDGED-T NETWORK MAKES IDEAL PHASE SHIFTER

THE bridged-T network, familiar as an audio attenuator and oscillator feedback circuit, has found another important application. It can be used as an effective phase shifter at a.f. or at r.f., while maintaining constant attenuation. Phase shifters are used to control servos and test networks, and for circuit measurements. The bridged-T phase shifter can vary phase angle over a wide range; it has a common input and output ground; it is relatively easy to construct and operate.

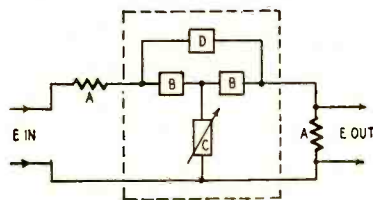


Fig. 1—Basic bridged-T filter network.

The new circuit is described by Myron G. Pawley in the *Journal of Research of the National Bureau of Standards*, Sept., 1950, page 193. Mr. Pawley has also obtained a patent* which covers several practical forms of his idea.

Fig. 1 is the basic bridged-T. Input and output load impedances are designated A. (These may be equivalent impedances reflected by transformer windings.) The network is shown within dotted lines, C being the variable shunt element. When correctly designed, this network provides constant attenuation, but the phase of the output signal will be shifted as C varies.

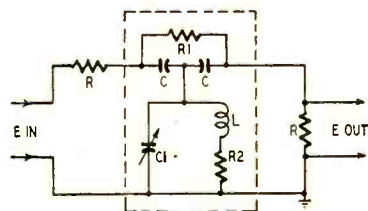


Fig. 2—Pawley bridged-T phase shifter.

One form of the invention appears in Fig. 2. The shunt element is shown here as a combination of resistance, capacitance, and inductance. The capacitor is the variable element. The following relationships must be maintained.

$$R_1 = 2R + 8R_2;$$

$$X_L = \frac{X_C}{2};$$

X_C must be much greater than R_1 ; X_{C1} must be much greater than X_L , which gives C_1 a value of about 100 μf at 4.17 kc, and about 2 μf at 29.1 mc.

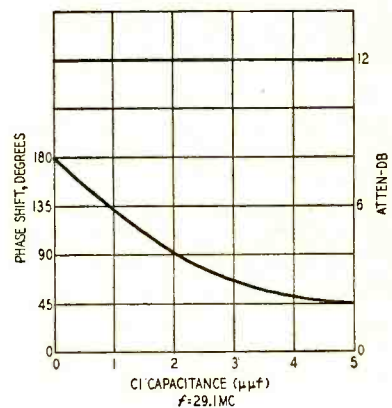
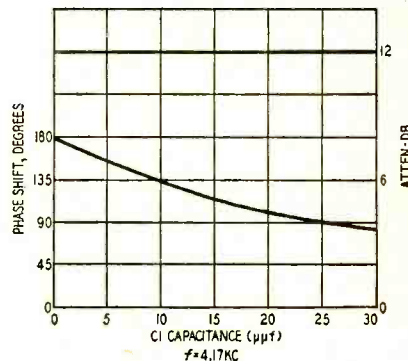


Fig. 3—Phase-shift versus capacitance curves for Pawley bridged-T networks at frequencies of 4.17 kc and 29.1 mc.

Typical circuit constants are listed in Table I for a frequency of 4.17 kc. Table II shows values for 29.1 mc. The corresponding graphs appear above in Fig. 3. In each case the attenuation remains constant at 12 db.

Another circuit for operation at 4.17 kc is shown in Fig. 4. Here a variable

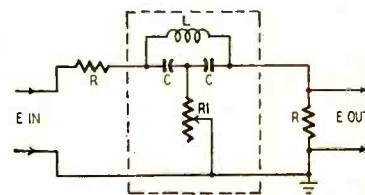


Fig. 4—Resistance controlled shifter.


resistor R_1 controls the phase shift. For this circuit, the Q of L must be much greater than unity, and X_C must be much greater than

$$\frac{R}{2}$$

In addition we must choose $X_L = 4X_C$. These requirements are met by the circuit values listed in Table III. END

Table I		Table II		Table III	
R	1,000 ohms	R	50 ohms	R1	1,000 ohms
R1	5,120 ohms	R1	114 ohms	C	.004 μf
R2	390 ohms	R2	1.75 ohms	L	1.4 h
C	520 μf	C	10.5 μf	Q of L	94
L	1.4 h	L	1.44 μh		

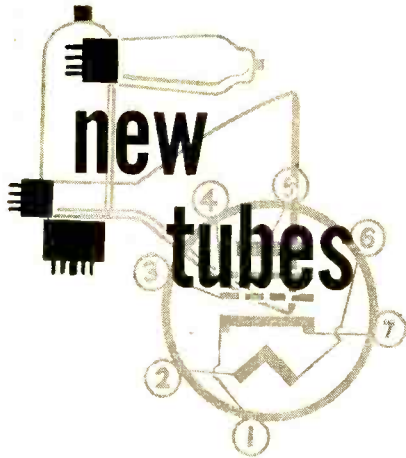*Pat. No. 2,606,966 assigned to the United States Government.



THE trend in large-screen picture tubes seems to be toward reviving the spherical faceplate—apparently to increase the effective picture area. Rauland has announced two new 21-inch rectangular all-glass tubes of this type, with an effective screen area of 252 square inches, compared with 245 square inches for 21-inch rectangulars with cylindrical faceplates.

Type 21YP4 has low-voltage electrostatic focus and magnetic deflection; type 21ZP4 has both magnetic focus and deflection. Both tubes have gray filter faceplates, external conductive coatings, and the Rauland indicator-type ion trap, which glows when the ion-trap magnet is not positioned correctly.

New cathode-ray tubes

A British-made 1-inch all-glass cathode-ray tube is now available on the American market.



The *Cossor* 1CP1 has a standard Loktal base, electrostatic deflection, and fixed electrostatic focus, all of which simplify its application to compact test and monitoring equipment.

The 1CP1 operates at anode voltages of 500 to 800 (maximum), with spot diameter ranging from 0.3 mm (.012 inch) at the lower voltage, to 0.2 mm (.008 inch) at 800 volts.

At maximum anode voltage the deflection sensitivity of the plates nearest the anode is approximately 72 volts per inch; the plates farthest from the anode have a sensitivity of 88 volts per inch. The heater-cathode insulation will withstand a voltage difference of 250 volts maximum.

Bias for the 1CP1 can be obtained from a 10,000-ohm cathode resistor. The maximum circuit resistance between control grid and cathode is 1 megohm; maximum resistance between any deflecting plate and anode is 5 megohms.

The electrical characteristics and the application of the 1CP1 are similar to those of the 1-inch metal-shell RCA cathode-ray tube, type 913.

APRIL, 1953

A yellow banner featuring the 'ATR' logo in a black oval. Below the logo, the text reads 'for A.C. current ANYWHERE!'. The banner is framed by a black dashed line and contains a line-art illustration of a cityscape with buildings, a car, and a house.

A photograph of a black, rectangular ATR inverter unit. The front panel features a control panel with a power switch, a 'TEST' button, and a 'POWER' knob. A power cord is attached to the side. The unit is set against a background of a dashed black circle.

STANDARD and HEAVY DUTY INVERTERS

For Inverting D. C. to A.C. ... Specially Designed for operating A. C. Radios, Television Sets, Amplifiers, Address Systems, and Radio Test Equipment from D. C. Voltages in Vehicles, Ships, Trains, Planes and in D. C. Districts.

The bottom section of the advertisement features the 'ATR' logo in a yellow oval. To the left, it says 'See your jobber or write factory'. To the right, there is a list of features: 'NEW MODELS', 'NEW DESIGNS', and 'NEW LITERATURE'. Below this, the text reads: 'A" Battery Eliminators, DC-AC Inverters, Auto Radio Vibrators', 'AMERICAN TELEVISION & RADIO Co.', 'Quality Products Since 1931', and 'SAINT PAUL 1, MINNESOTA—U. S. A.'. The background includes illustrations of a train, a bus, and a ship.

MONEY-SAVING OFFER

**ON THE TWO LATEST AND GREATEST
GHIRARDI RADIO-TV SERVICE TRAINING BOOKS**

**... only \$12 for the 2-book set
... 4 months to pay
... 10-day examination privilege**

**THE
BASIC
"KNOW-HOW"
OF MODERN
CIRCUITS**

**RADIO AND
TELEVISION
RECEIVER**



CIRCUITRY & OPERATION

Learn circuits fully—and watch service "headaches" disappear!

IT'S lots easier to repair any radio or TV set when you know all about its circuits; how they work and their peculiarities! You locate troubles faster. You work more efficiently. What's more, the basic knowledge of circuitry contained in Ghirardi's *Radio & TV Receiver Circuitry and Operation* is ideal to help fit you for dozens of other radio-TV-electronic jobs.

CUT TESTING TIME IN HALF!

Actually, there are only a few basic circuits—but each of these has many variations. You learn to recognize each of them instantly. You learn how to locate troubles in far less time and with a lot less testing.

SPEEDS UP YOUR WORK ON TOUGH JOBS!

Here's what this great new book covers:—1-Amblytone Modulation; 2-Frequency Modulation; 3-RF Amplifiers and TRF Receivers; 4-AM Superhets; 5-AM Detectors and AVC systems; 6-Push Button Tuning and AFC systems; 7-AP Amplifiers; 8-Loudspeakers; 9-Radio Power Supplies; 10-Television Receivers; 11-Phono Pickups and Record Players; 12-Automatic Record Changers; 13-Mechanical Construction of Receivers, etc. Contains 688 pages. Jam-packed with helpful servicing data. 417 illustrations help make circuits easy to learn. Price separately \$6.00.

See for yourself how much this book can help you! Use coupon for 10-day trial examination!



When you buy . . .

a Ghirardi technical training book, you KNOW you're getting the best—at the lowest possible cost. For over 20 years, Ghirardi books have been more widely used in schools, colleges, for military and naval radio training and for more home study than any other books of their kind!

**COMPLETE
TRAINING IN
PROFESSIONAL
SERVICE
METHODS**

**RADIO AND
TELEVISION
RECEIVER**



TROUBLESHOOTING AND REPAIR

The book that paves your way to better-paying service jobs!

FOR beginners, Ghirardi's NEW *Radio & TV Receiver TROUBLESHOOTING AND REPAIR* makes every phase of the work easy to understand. For experienced servicemen, it is a splendid way to "brush up" on specific types of work; to develop better troubleshooting techniques; or to find fast answers to problems.

Of particular importance, you learn all about MODERN test methods. Starting with quick analysis of common troubles, you then progress rapidly to "static" tests and "dynamic" signal tracing and signal injection techniques. Special problems in hard-to-fix sets are clearly explained. Step by step charts demonstrate professional servicing procedures almost at a glance.

THE HOW-TO-DO-IT GUIDE TO MODERN SERVICING

Receiver alignment is made easier than you might have thought possible. Tuning problems, speaker troubles, components and their repair or replacement and dozens of other subjects are covered fully.

You learn to analyze TV patterns accurately; how to handle TV fading and propagation troubles; what to do about intermittent troubles—in short, everything the modern serviceman needs to know. Contains 820 pages, 419 illus.

Start training NOW for greater service efficiency, better jobs and higher profits!

Use coupon. Read this big book for 10 days before you decide whether or not to buy!

10-DAY TRIAL EXAMINATION OFFER!

Dept. RE-43, Rinehart Books, Inc., Technical Division,
232 Madison Ave., New York 16, New York

Send books checked below for 10-day examination. In 10 days, I will either remit price indicated in full or return books in good condition.

- Radio & TV Receiver
Circuitry & Operation
Price \$6.00
- Radio & TV Receiver
Troubleshooting & Repair
Price \$6.75

COMBINATION OFFER—both books only \$12

(Regular price \$12.75—you save 75¢)
(Payable at the rate of \$3 after 10 days if you decide to keep books, and \$3 a month thereafter until total of \$12 is paid.)

Name

Address

City..... Zone..... State.....

Employer.....
OUTSIDE U.S.A.—\$7.25 for TROUBLESHOOTING & REPAIR; \$6.50 for CIRCUITRY & OPERATION; \$13.00 for BOTH books. Cash Only. Money refunded if you return books in 10 days.

NEW DESIGN


Du Mont has announced two new electrostatic focus and deflection cathode-ray tubes for oscilloscope use. They have exceptionally high deflection sensitivity, obtained by using extra-long deflection plates and limiting the useful display area to less than the full screen diameter. The right-angle relation between horizontal and vertical traces is accurate to 1°.

Type 3WP- is a 3-inch tube with an accelerator (ultor) rating of 2,500 volts maximum. Representative operating conditions for the 3WP- are: Accelerator voltage—1,500; focusing voltage—247 to 465; grid 1 voltage for visual extinction of undeflected spot—minus 45 to minus 75; grid-circuit resistance—1.5 megohms max.; grid 1 modulating voltage—50 volts max.; line width—.026 inch max.; light output (P1 phosphor) 7 foot lamberts minimum; deflection factors: D1-D2—62-76 volts per inch; D3-D4—43-52 volts per inch; useful scan: D1-D2—2.5 inches; D3-D4—2.25 inches.

Du Mont type 5ADP- is a 5-inch tube with similar high deflection-sensitivity characteristics, and the addition of a post-accelerator anode with a 6,000-volt maximum rating. With 3,000 volts on the post-accelerator, and 1,500 volts on the accelerator anode, the 5ADP- has a deflection sensitivity of 40-50 volts per inch for D1 and D2, and 31.5-38.5 volts per inch for D3 and D4.

Two other new Du Mont cathode-ray tubes are designed for observing high-frequency phenomena. These are the 5XP-A and 5XP-AM. Both types have electrostatic focus and deflection, and are equipped with post-accelerator anodes that may be operated as high as 25,500 volts. The 5XP-AM has a metal-backed screen which provides twice the light output of the 5XP-A. Vertical-deflection sensitivity is down only 10% at 200 mc. END

A NEW FORM OF PARASITIC

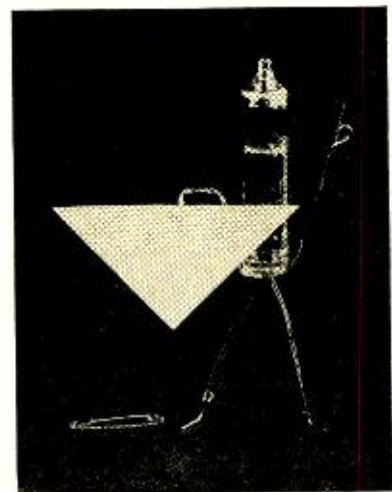

Workers at Sylvania's Emporium, Penna., plant create new tube types that speak for themselves. Here a campaign orator offers us a three-point program.

RADIO-ELECTRONICS

ciation, according to George Morton, chairman of the policy committee, is a city ordinance to license and bond TV service technicians. Meetings have already been arranged with the city's mayor and electrical inspector, for the purpose of drawing up such an ordinance.

NATESA MEETS IN KANSAS CITY

NATESA's Spring Convention—its first national convention for TV-service dealers, managers, and technicians—will be held Friday through Sunday, April 10, 11, and 12, in Kansas City. Television Service Engineers, Inc. of Greater Kansas City will play host to the more than 500 member guests expected to attend from all parts of the United States.

Exhibits of about 50 manufacturers

—with emphasis on u.h.f. TV equipment—will fill 1½ floors in the Continental Hotel.

The convention will open Friday afternoon with registration and a cocktail party. Business sessions will be held Saturday, with addresses by NATESA President Frank Moch and manufacturers' representatives. These will be followed by a banquet and floor show, and the presentation of awards.

The Sunday session will feature an optional ranch-style breakfast and round-table discussions.

FRSAP ELECTS NEW OFFICERS

Milan S. Krupa, of the Associated Radio Servicemen of Luzerne County, was elected president of the Federation of Radio Servicemen's Associations of Pennsylvania. He succeeds Dave Krantz,

who, after 6 years of continuous service, declined to continue as president of FRSAP. Mr. Krantz will head a new advisory council to be made up of the heads of all member chapters.

Other officers elected for one-year terms were Bertram Bregenzer, of the Radio Servicemen's Association of Pittsburgh, vice president; Fred Schmidt, of the Mid-State Radio Servicemen's Association (Harrisburg), treasurer; and Leon Helk, Lackawanna County Radio Servicemen's Association (Scranton), secretary.

A special committee under vice-president Bregenzer will aid the formation of new chapters. Requests for membership in FRSAP have already been received from servicemen's groups in Lancaster, Butler, Johnstown, Erie, and Sunbury. END




CUSTOM-BUILT TV CABINETS

Direct from MANUFACTURER to YOU!

Be Alert—be smart! Don't be misled by other offerings of cabinets similar to these original TeleSound creations, at lower prices. They are NOT the same quality. When you buy from TeleSound, you buy from the MANUFACTURER—at the lowest possible prices consistent with the high quality of these cabinets.

Be price and quality conscious! TeleSound wholesale prices enable you to sell more, make a BETTER PROFIT for yourself, with greater satisfaction to your customers. Compare price and quality—then—buy with confidence from TeleSound. Our factory-to-you shipments, and lowest wholesale prices, are your guarantee of satisfaction!

GUARANTEED QUALITY & VALUE!

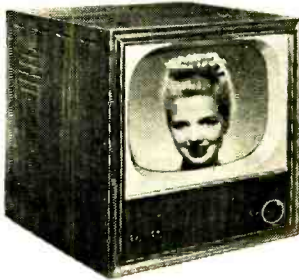

H:25", D:21½", W:25" Wgt: 50 Lbs.
TABLE MODEL 500 **\$42.00**



H:40¼", D:22½", W:25¼" Wgt: 60 lbs.
CONSOLE MODEL 200 **\$47.50**

As above, for 24" Picture Tube
H:31", D:24", W:27" Wgt: 60 lbs. **\$55.80**



H:41¼", D:23¾", W:34", Wgt: 100 lbs.
CONSOLE MODEL 1000 **\$82.50**

All TeleSound cabinets illustrated are available in Ribbon Stripe Mahogany. Model 200 also available in Walnut. All cabinets can be had in Blonde Korina at 10% additional. These cabinets are custom built and drilled to fit standard 630 type chassis. We can supply them with undrilled panel to fit any other chassis you specify. Complete cabinet catalog available on request. All prices subject to change without notice.

Terrific!
VIDEO SUPER-POWERED TV CHASSIS
MODEL 530-DX
\$139.50 Less Pix Tube



Highest sensitivity of any TV receiver known today! Designed for excellent performance in both fringe and strong signal areas.
VIDEO 630 TV Chassis \$149.50
VIDEO 630-DX TV Chassis \$159.50

TECHMASTER

Model C-30 TV Chassis \$149.50
Model 1930 TV Chassis \$179.50
Model 2431-P TV Chassis \$199.50
Prices above include all receiving tubes, less pix tube.

SHELDON TV PICTURE TUBES

Full ONE YEAR Guarantee.
17" 17BP4 \$28.90
20" 20CP4A \$38.05
21" 21EP4A \$40.25
21" 21BP4 \$76.00
27" 27GP4 (Electro-magnetic) \$90.00

FAMOUS TELESOUND PACKAGE DEAL Save money! Order the TeleSound cabinet of your choice in combination with famous Video 530-DX TV Chassis, 12" speaker, and your choice of picture tube. ADD: for Video 630, \$10; Video 630-DX, \$20; Techmaster C-30, \$10; 1930, \$40; 2431-P, \$60.


CABINET STYLE	Combined with Video 530-DX Chassis, 12" Speaker, and		
	17" CRT	20" CRT	21" CRT
200	\$209.50	\$218.25	\$220.50
500	\$204.00	\$212.95	\$215.00
1000	-	\$252.25	\$254.25
			24" CRT
			\$249.75
			\$289.00
			27" CRT
			\$302.50

Please include 25% deposit with orders, balance C.O.D. All shipments F.O.B., NYC "Designers & Manufacturers of Custom TV and Radio Furniture"



421 West 28th Street
New York 1, N.Y.
Phone: WI 7-0719

Completely NEW—
scientifically designed

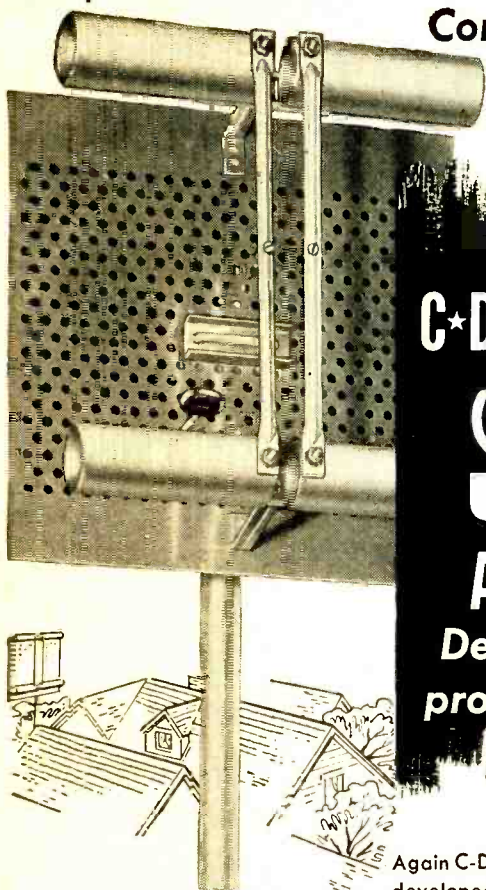

C-D Model U-4
Skyhawk
UHF-TV
ANTENNA
Definitely Superior—
proven by Field Test

Again C-D's pioneering engineers anticipated and developed THE antenna specifically for UHF reception—the C-D SKYHAWK is ready NOW for the fast growing UHF market. Completely "bug" proof. Thoroughly performance-tested. Completely dependable. Broad-band coverage with uniform gain over the entire UHF spectrum and factory PRE-ASSEMBLED for speedy installation. Make every UHF installation the best—use the C-D SKYHAWK Model U-4.

- ★ Uniform Gain With Low Vertical Radiation (No Ghosts)
- ★ Uniform Gain . . . Low Standing Wave Ratio
- ★ 300 OHM Terminal Impedance
- ★ May Be Stacked . . . Measures 12 x 12 x 5 inches

YOUR C-D DISTRIBUTOR IS READY TO SERVE YOU



CONSISTENTLY DEPENDABLE

CORNELL-DUBILIER

SOUTH PLAINFIELD, NEW JERSEY



- CAPACITORS
- ANTENNAS
- ROTORS
- VIBRATORS
- CONVERTERS



- 1220 pages
- 80,000 items
- 8,000 illustrations
- 8" x 11" — 5 lbs.

Publisher's price \$6.50—your price through your regular parts distributor **\$1.95**

The right part when you need it, for service

This permanent, hard cover Official Buying Guide of the electronic-TV parts and equipment industry with its comprehensive detailed index, eliminates the need for maintaining files of small catalogs and manufacturers' literature. RADIO'S MASTER catalogs 90% of TV and electronic equipment. Not merely part number listings—complete descriptions, specifications and illustrations written and compiled by each manufacturer. Enables you to make comparisons or substitutions right now!



UNITED CATALOG PUBLISHERS, INC.
110 Lafayette St., New York 13


U.H.F. OSCILLATOR TUNING

Patent No. 2,618,705

John E. Allen, Lansdale, Pa.

(Assigned to Philco Corporation, Phila. Pa.)

This device overcomes the difficulty of u.h.f. switching. It generates two distinct frequencies from a single oscillator. One of these frequencies is fixed; the other is adjustable over a narrow range. A push-button switches from one to the other. The fixed frequency is suitable to control a transmitter. The other frequency may be the local oscillation for receiving. Both are stable because they are cavity-controlled.

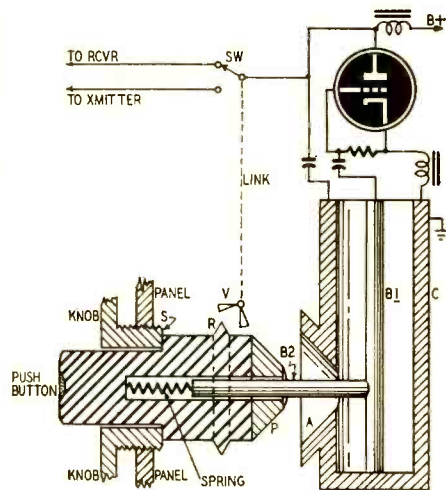

The figure shows a coaxial-line cavity. C is the grounded outer conductor. B1 is the inner line which has an extended portion B2 passing through a flared aperture in C. A metallic, tapered plug P fits snugly into this aperture A, when the push-button is depressed. When desired, a catch (not shown) is set to hold the plug in this position. When P is inserted into A, the oscillator frequency is the natural frequency of the cavity.

When its catch is released, P is forcibly withdrawn from A by a spring. The plug comes to rest against the stop S. Due to capacitance between C and P, the frequency is now changed. This second frequency is adjustable by turning the threaded knob shown. Rotating it clockwise, for example, moves it deeper behind the panel so P cannot come out of A quite so far.

Note the annular ring R around the push-button. When the button is depressed, R acts against the pivoted vane V. V is moved counterclockwise. A mechanical link forces switch SW to its lower contact. Therefore the fixed frequency is fed to the transmitting circuits. When the button is released, V is moved clockwise by R. SW is now forced upward and makes contact with the receiver lead.


IMPROVED BROADSIDE ARRAY

Patent No. 2,622,198

Richard G. Clapp, Haverford, and Samuel H. Colodny and Bernard Wise, Philadelphia, Pa. (Assigned to Philco Corporation, Phila. Pa.)

A simple dipole radiates in only two directions. As the antenna is lengthened, minor lobes appear in its directional pattern. These undesirable lobes can be eliminated by proper control of the radiation. The antenna should radiate maximum power from its center. Radiation should fall off progressively as we pass to the ends. This principle is applied to a broadside array in this invention.

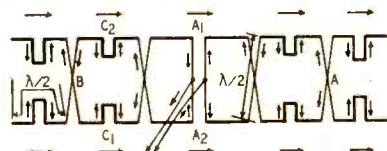The diagram shows a 10-element array. It has 5 elements in each of 2 rows. Arrows show the instantaneous direction of current flow. By transposing the elements, current flows in the same direction in each horizontal element. Therefore the radiation is strengthened. The vertical elements cannot radiate. This is because each such pair carries opposing currents which cancel the radiation.



EXPERIMENTERS SPECIALS




1 RPM MOTOR
115 volts, 60 cycles. Syn-chron model 600. Use for timing devices, models, displays, gadgets, etc.
Stock No. RE-5
Price **\$2.95** each



AMPERE DEMAND METER
Stewart Warner-748A. Indicates up to 20 Amperes long time average current drain. High time lag—follows heating effect of supply transformers. Use to check motor and line overload as well as peak average demand. Indicating average and average peak recorder pointers.
Stock No. RE-119
Special @ **\$3.95** each



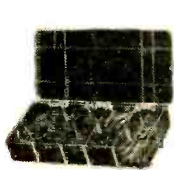Redmond 6 Volt DC Motor
—An ideal small dc motor for the experimenter. Operates from 6 volts dc at 3000 rpm. Requires 1.75 amperes for 1/100 horsepower.
Stock No. R-137
Special **\$2.95** each



RESISTOR KIT
A miracle of value, 99 carbon-on-ceramic deposited resistors. German made. 10% tolerance. 11 popular values 100 ohms to 100 K. Assorted 1/4, 1/2 and 1 watt. 9 compartment hinged covered clear plastic box.
Stock No. RE-1002
Special at only **\$1.98**


Tachometers—Stewart Warner—2000 rpm. \$5.95 each
Tachometers—Stewart Warner—4000 rpm. \$6.95 each
Mercury Switch—Tilt to activate—1 Amp. .4 for \$2.00
CIB Thyratrons—1 Ampere rating. Special. \$4.25 each

Write for free catalogue of Electronic, Aircraft, Hydraulic and other equipment. See March Radio-Electronics for our Meter Advertisement.

Minimum order \$2.00. F.O.B. Paterson, N. J.

ELECTRO DEVICES, INC.
4-6 Godwin Ave. Paterson, N. J.

CH. 7 THRU CH. 13 INCLUSIVE

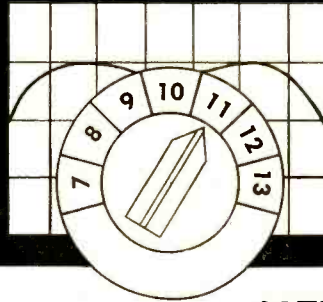

—ALL SEVEN CHANNELS

with the **NEW Silver Streak BAZOOKA**
cat. no. 1860

Outstanding performer for fringe area installations where several high-band channels are operating. Eliminates individual high-gain antennas, matching networks, and switching devices.

- ★ One forward lobe — 13½ db front-to-back ratio.
- ★ 9 db gain across all seven channels.
- ★ Bazooka factory-tuned. Simple installation.
- ★ Exclusive Taco Click-Rig — no screws to tighten.
- ★ Mechanically balanced — ideal for use with rotor.




TECHNICAL APPLIANCE CORPORATION, SHERBURNE, N. Y.

A NATIONWIDE NETWORK OF TOP DISTRIBUTORS CARRY TACO ANTENNAS

In Canada: Hackbusch Electronics Ltd., Toronto 4, Ont.

Just Out

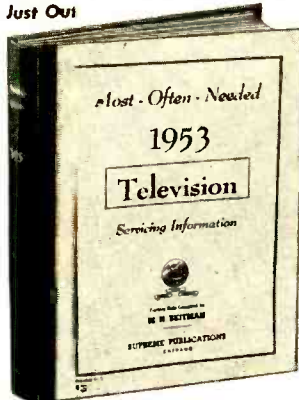

This newest giant volume of the Supreme TV series covers 1953 factory data on all popular television sets of all makes. There are explanations of new circuits, 192 pages of alignment procedure, test patterns, response curves, pages of waveforms, voltage charts, service hints, production changes, and dozens of double-spread circuit diagrams. Manual-style binding (opens flat). Special price, only... **\$3**

New SUPREME 1953 TV Manual


GET IT AT YOUR RADIO JOBBER OR SEND COUPON

COVERS ALL POPULAR SETS

This new Supreme 1953 TV manual has all the required service material on every popular television set of every important manufacturer. Here is helpful, practical, factory-prepared data that will really make TV servicing and adjustment easy for you. Benefit and save with this amazing manual scoop. This new giant TV manual, as well as the previous volumes for other years, has complete circuits, alignment facts, test patterns, response curves, service hints, recommended changes, voltage charts, waveforms, and many double-page diagram blueprints. Here is your TV service material to help you do more expert work quicker; and priced at only \$3 and \$2 per manual covering a whole year of material. See coupon below for the complete list of all seven TV volumes, from 1947 to 1953. Order at our risk for a 10-day trial.

AMAZING BARGAIN OFFER

The new 1953 TV manual is the most remarkable value offered by Supreme Publications in their 19 years of business. This mammoth television servicing manual at only \$3, or the TV manuals for previous years for only \$3 and \$2 each, are amazing bargains and defy competition. There is nothing else like them. Each manual is a virtual treatise on practical television repairs. By normal standards, each such large manual packed as it is with practical facts, hundreds of illustrations, diagrams, charts, photographs, and expensive extra-large blueprints, should sell for \$10—but as SUPREME special values they are priced at \$3 and \$2 each. Only a publisher who sold over one million TV and radio manuals can offer such bargains based on tremendous volume-sales. Be ready to repair any TV set by having in your shop all seven Television Manuals listed in coupon. Or try the new 1953 TV manual to see what an amazing bargain you get for only \$3. Send no-risk trial coupon.

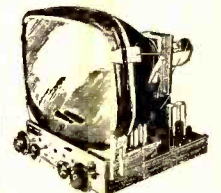

The repair of any television set is really easy with Supreme TV service manuals. Every set is covered in a practical manner that will simplify troubleshooting and repair. This is the help you need to find toughest faults in a jiffy. Each \$3 volume covers a whole year of material. Be wise, buy Supreme Manuals only once each year instead of spending dollars every week for not needed data.



RADIO DIAGRAMS

Here is your complete source of all needed RADIO diagrams and service data. Covers everything from most recent radios to pre-war old-timers; home radios, auto sets, combinations, changers, and portables. Sensational values. Still sold at pre-Korean prices. Only \$2 for most volumes. Every Radio manual contains large schematics, all needed alignment facts, parts lists, voltage values, trimmers, dial stringing, and helpful service hints. Volumes are large in size, 8½ x 11 inches, about 192 pages. See coupon at right for a complete list of these low-priced manuals.

NO-RISK TRIAL ORDER COUPON

SUPREME PUBLICATIONS, 3727 W. 13th St., Chicago 23, ILL.

- Radio Diagram Manuals**
- New 1952 Manual, \$2.50
 - 1951 Radio
 - 1950 Manual
 - 1949 Radio
 - 1948
 - 1947
 - 1946
 - 1942
 - 1941
 - 1940
 - 1939
 - 1926-1938 Manual, \$2.50
- PRICED AT ONLY \$2 EACH**

Send TV and Radio manuals checked below and at left. Satisfaction guaranteed or money back.

New 1953 Television Servicing Manual, \$3.
 1952 Television Manual, \$3. 1951 TV, \$3.
 1950 Television Manual, \$3. 1949 TV, \$3.
 1948 TV, \$3. 1947 TV & FM, only \$2.

I am enclosing \$..... Send postpaid.
 Send C.O.D. I am enclosing \$..... deposit.

Name:
 Address:

Supreme Publications
Available from Leading Radio Jobbers

PRICE REDUCTIONS

ON STANCOR YOKES and FLYBACKS

It's our way of saying, "Thanks for your confidence." Yes, thanks to you, the sale of these Stancor TV components has increased tremendously... our costs are lower... and we are passing these savings on to you.

These components are the same high quality, triple-tested units you have always received and come to expect from Stancor. At these new, low prices they are even better values than before.

DEFLECTION YOKES

PART NO.	OLD LIST PRICE	NEW LIST PRICE
DY-8	10.75	9.80
DY-8A	11.00	10.00
DY-9	10.75	9.80
DY-9A	11.00	10.00
DY-10	10.75	9.80
DY-10A	11.00	10.00
DY-11A	*	10.00
DY-12A	*	10.00

FLYBACKS

PART NO.	OLD LIST PRICE	NEW LIST PRICE
A-8128	10.50	10.00
A-8129	11.00	10.50
A-8130	11.00	10.00
A-8131	7.00	6.50
A-8132	*	10.50
A-8133	11.00	10.50
A-8134	11.00	10.50

STANDARD TRANSFORMER CORPORATION

3592 ELSTON AVENUE
CHICAGO 18, ILLINOIS




*New items: DY-11A is used in 172 models of 15 manufacturers. DY-12 is used in 160 models of 8 manufacturers. A-8132 is an exact replacement for Muntz TO-0031, used in over 300,000 sets. Ask your Stancor distributor for Bulletin No. 461 listing applications of these units, or write Stancor direct for your free copy.

Stancor Transformers are listed in Photofact Folders, Tek-Files and Counterfacts.

Export Sales: Roburn Agencies, 39 Warren Street, New York 7, N. Y.

OVER 50,000
TECHNICIANS
HAVE LEARNED

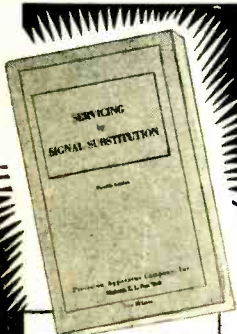

**'SERVICING BY
SIGNAL SUBSTITUTION'**
A BEST SELLER FOR OVER 12 YEARS!
(NEW, UP-TO-DATE, 12TH EDITION)

HOW TO GET
THE MOST OUT
OF BASIC TEST
EQUIPMENT

ONLY **40¢**

103 pages. Invaluable information that will help you re-double the value of your basic test equipment.

The Modern, Simplified, Dynamic Approach to Receiver Adjustment & Alignment Problems.

- ★ Nothing complicated to learn
- ★ No extra equipment to purchase
- ★ Universal... non-obsolescent
- ★ Employs only Basic Test Instruments

Ask for "S.S.S." at your local Radio Parts Jobber or remit 40¢ in small stamps or coin directly to factory.

PRECISION APPARATUS COMPANY, INC.
92-27 HORACE HARDING BLVD., ELMHURST 4, N. Y.

for A.M. - F.M. - TV

NEW PATENTS

To reduce minor lobes, folds are introduced in some of the elements. These folds cannot radiate because the re-entrant parts carry opposite currents. However, these folds decrease the effective lengths of the horizontal radiators in the figure, the end elements have the greatest folds so they have least radiation. The next adjacent elements are folded to a lesser extent so they have greater radiation. The center elements have no folded stubs. Their radiation is maximum as desired. This variation in folding is the feature that is patented.

For maximum efficiency, the elements should radiate in accordance with the binomial expansion, a mathematical formula. For a 5-element row (as in this array) the horizontal elements should radiate in the following proportion: 1, 4, 6, 4, 1.


FM RADIOSONDE SYSTEM

Patent 2,613,347

William Todd, Neptune City, N. J.
(Assigned to United States of America as represented by the Secretary of War)

Generally speaking, FM communication requires an elaborate receiver and a simple transmitter. Therefore FM is suitable for radiosonde systems where the transmitter must be light and compact. This inventor points out other FM advantages and suggests its use in radiosonde work.

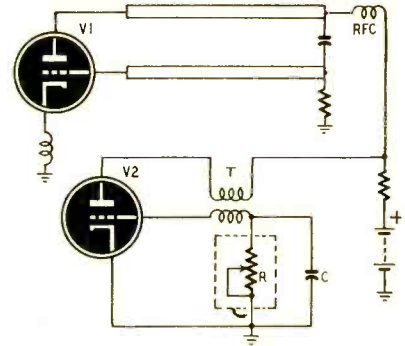The figure shows the transmitter circuit. V1 is an oscillator tuned to about 400 mc. V2 is the modulator which conducts intermittently. When current flows, feedback impresses a large negative pulse on its grid. Then the tube is blocked



until C can discharge its negative voltage through R. This resistor is shown as a variable element. If, for example, it is reduced, the blocked interval becomes less. Then the average current through V2 is increased. Since V1 and V2 are coupled through a common dropping resistor, the r.f. tube gets less plate potential. As in any self-excited oscillator this means a change in carrier frequency.

Actually, R may be a thermistor or other element whose resistance depends upon temperature, humidity, pressure, etc. Any change in the resistance of R makes a corresponding variation in carrier frequency, which is interpreted at the receiver.

In FM, the carrier amplitude remains constant. This makes it easier to track the radiosonde transmitter. Also, a small change in frequency can be detected easier than a small change in amplitude.

END




"I'm afraid my set is troubled with Flop-Over!"

RADIO-ELECTRONICS

AMPLIFIER CALIBRATION

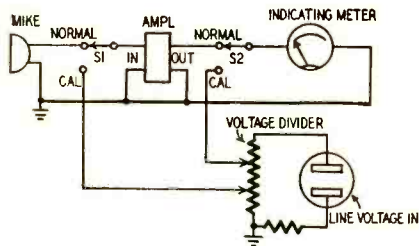Most radio and PA amplifiers do not need extra high stability. A slight change in amplifier gain from time to time does not matter. On the other hand, if the amplifier is part of a precision instrument, constant gain is of the utmost importance. For this reason, the General Radio sound-level meter includes an internal checking circuit. A gain test may be made quickly and at any time.




With switches S1 and S2 in positions shown, the amplifier is ready for normal use. To test its gain, S2 is thrown to CAL. The meter measures a relatively high voltage from the line voltage divider. This reading is noted. Now S2 is returned to NORMAL and S1 is switched to CAL. This feeds a small a.c. signal to the amplifier. If the amplifier gain is correct, the meter will show the same reading as before.

This is how the calibration circuit operates. Before leaving the factory, the voltage divider taps are adjusted and fixed so the voltage ratio between taps equals the amplifier gain. When the calibration is checked, the attenuation of the potentiometer is balanced by the amplifier gain. Since these are equal, the meter will give identical readings as described above. The actual meter deflection is not important.

AUDIO PREAMPLIFIER

Most modern audio amplifiers use some form of microphone or phono pre-amplifier to amplify the low-level signal to a point where it can be fed into the main amplifier. The input signal is usually very low so preamplifier designers try all sorts of tricks to minimize noise and hum.

I suppose that you would call this a cascade amplifier, but it differs from the cascade in that the grid of the second triode is not grounded at the signal frequency and some of the output signal from the second triode section is fed back into the grid through the 470,000-ohm resistor. The grid is 60 volts positive. I varied the positive grid voltage but it works better with the value shown. From ordinary observations, it would appear that this circuit is impossible but such is not the case.

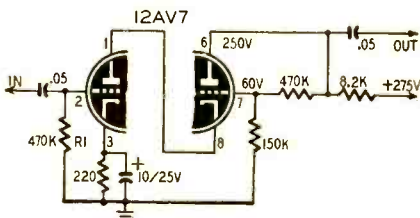


EDLIE says **"Save with confidence"**

Special! Custom Built AUTOMOBILE RADIOS


For 1949, 1950, 1951, 1952 & 1953 Models, Made by Automatic Radio

Every auto radio is powerfully built, 6-tube superhet. With RF stage and 3-gang condenser for sensitive, long distance reception. Latest miniature tubes used with beam-power output and oversized Alnico V speaker, offering plenty of volume with excellent tone. Includes Automatic Volume Control and has extra low battery drain. Each model is Custom-Built, designed for the individual automobile and can be mounted within 4 minutes without cables or brackets. No holes to drill. *Indicate make and year of automobile when ordering.*

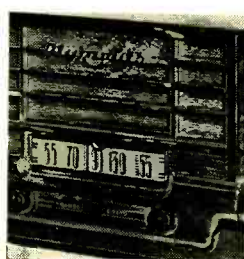

Electro-Touch Tuning

A mere touch of the finger and your radio's electronically tuned to a station with absolute precision... and not to just a few pre-set stations. Your eyes never have to leave the road for tuning is completely automatic. Ideal performance is yours with this custom-built, 7-tube, 3-gang radio. Assures top reception wherever you go. Superhet. circuit with a rectifier, operates on a 6-V. storage battery. Includes Automatic Volume control, permanent magnet dynamic speaker and gives 8-tube performance. Beautifully finished to match

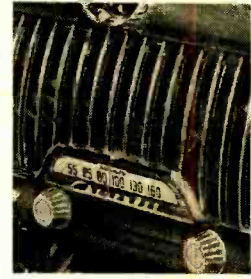

your car, can be easily installed in a few minutes. No holes to drill.

For: Ford, Mercury, Dodge, Plymouth, Chevrolet, Hudson, Studebaker and Henry J.

Write for our Special Prices!

For: Ford, Chevrolet and Dodge. Be sure to mention make and year of car when ordering.

VHF-UHF BOOSTER-CONVERTER

Made by Sutco—Just out


This great new Booster-Converter enables all TV receivers now being made to receive UHF signals and also have the booster which is necessary for VHF in fringe areas. It employs its own power, a crystal mixer, and two tubes: a 6AF4, and a 6J6. Operates on 110-115 V. A.C. The 6J6 is used in a balanced push-pull amplifier circuit and in the converter IF. The converted signal is then boosted and fed to the TV receiver. The booster is slug tuned and has a 75-300 ohm input and output. Provision for built-in UHF antenna. *Easy to install.*

Now only

\$3570




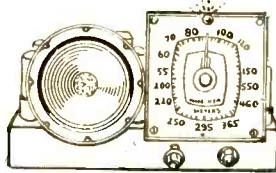Edlie Cuts Prices on these **QUALITY KITS**



6-TUBE RADIO KIT

Kit #2—A low-priced 6 TUBE KIT designed for high sensitivity, excellent selectivity and good tone quality. Uses 25L6, 25Z6, 6SQ7, 6SA7, 6SK7, 6SK7 in an easily constructed circuit. The 6 Tube Kit is shipped with all parts, including punched chassis, resistors, condensers, coils, sockets, PM Speaker, hardware, etc.
And at a closeout price of only (less tubes and cabinet) **\$6.95**
Matched set of six tubes **\$3.25** for kit

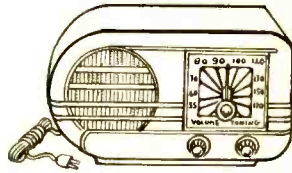

5 TUBE AC-DC SUPERHET KIT

Kit #1—Five Tube superheterodyne kit, A.C.-D.C. contains all components required to construct this latest design, highly sensitive superheterodyne broadcast receiver, complete with black bakelite cabinet (excludes with black wire and solder) ... Only **\$7.95**
Kit of 5 tubes (12AT6, 12BA6, 12BE6, 35WA, 50C5). Only \$3.25.

Electronic Code Practice Oscillator & Blinker Kit

AC/DC or Battery Operated!
Kit #3—One of the most practical Code Practice Oscillators ever designed. Yet one of the simplest to build and operate.
Can be used with any number of headphones. Adjustable Pitch Control—Any type of headphone can be used.
No warmup time—ready to operate instantly. Simple and safe to operate.
Operates anywhere—with AC or DC power, or from a 90 volt Miniature Battery.
Learn Blinker Code with flashing light. Blinker can be used as signaling device.
International Morse Code included.
Kit \$1.95 Assembled 2.95 each

3-TUBE PHONO AMPLIFIER

Not a Kit!

An assembled unit ready for installation using tone and volume control and six feet of rubber (not including Tubes) **\$2.95**
With Complete Set of Tubes... **\$3.95**

PHONO OSCILLATOR

Not a Kit!

Wireless phono oscillator transmits recording for crystal pickups or voice from carbon mike through radio without wires. Can also be used as an intercomm by using P.M. speaker as mike. Price (excluding tubes) **\$2.95**
With Complete Set of Tubes... **\$3.95**

Terms: All merchandise shipped F.O.B. New York City, prices are subject to change without notice. Include 10% deposit for C.O.D.'s.
WRITE FOR NEW CATALOG—Free!








EDLIE Electronics

154 Greenwich St. DI 9-3143
New York 6, N. Y.



Famed Across the Nation

FOR QUICK, EASY INSTALLATION!

						
Model EZ-2 2 Sec. 49" List \$3.45	Model CO-3A 3 Sec. 57" List \$5.15	Model MH-3 3 Sec. 57" List \$5.65	Model FD-3 3 Sec. 4"-55" List \$7.45	RAD-3 \$5.15 3 Sec. 70" RAD-4 \$6.25 4 Sec. 92" RAD-5 \$7.25 5 Sec. 112"	Model CS-3 3 Sec. 60" List \$3.85	COMMUNICATION BASE and SPRING MB-2 \$7.25 STEEL MAST MM-72 72" List \$5.75

SEE YOUR PARTS JOBBER NOW FOR THOSE Easy-to-Install RADELCO Antennas!

No matter what your installation needs may be, you'll find exactly the aerials you want at your nearest Radelco jobber... and at prices that will please you! You'll like the high quality and fine workmanship found in every Radelco antenna. You'll like their smart styling and handsome finish... but best of all you'll like their speed and ease of installation. If you want more for your money when you buy antennas make it a point to say "Radelco!"

RADELCO
MANUFACTURING CO.

7580 GARFIELD BLVD.
CLEVELAND 25, OHIO



VTVM

FACTORY ASSEMBLED AND CALIBRATED MODEL 940 VACUUM TUBE VOLTMETER

SPECIFICATIONS:

- 6-AC VOLT RANGES 0-3, 15, 30, 150, 300, 1500. Frequency response from 25 to 100,000 cycles
- 6-DC VOLT RANGES 0-3, 15, 30, 150, 300, 1500. Up to 30,000 volts with accessory probe
- 5-RESISTANCE RANGES 1,000-10,000—1 Meg-10 Megohm, 1,000 megohms, 10 megohms center on 1,000 megohm scale
- 5-DECIBEL RANGES -24 to -1.5, -8 to -15, +12 to +35, +21.5 to 44.5, +32 55

The Model 940 comes complete with test leads and operating instructions in a round cornered bakelite case. Factory assembled & calibrated.

10 DAY MONEY BACK GUARANTEE

Write for FREE CATALOGUE

ELLIOT LABORATORIES, Dept. RE-4

54-34 201 Street

Bayside 62, N. Y.



FEATURES

- Due to the high input resistance of 16.5 megohms, the circuit under test will not be loaded down.
- All functions and ranges are electronics, therefore no danger of meter being burned out.

\$29.95
NET

The preamplifier was used to drive a 6F6 output tube with a radio and low output phono pickup and as far as I can determine with any other test, it has excellent low- and high-frequency

Materials for audio preamplifier


Resistors: 2—470,000, 1—150,000, 1—8,200, 1—220 ohms, 1/2 watt.
Capacitors: 2—.05 μ f, 600 volts, paper; 1—10 μ f, 25 volts, electrolytic.
Miscellaneous: 1—12AV7 tube; 1—nine-contact miniature socket. Chassis, hook-up wire, terminal lugs, hardware.

response. The combined gain of both sections is just about equal to a 6J5 but the audio quality is far better. I had no difficulty with any hum even though no part of the circuit was shielded. A 500,000-ohm volume control can be used in place of R1, if desired.—Wilbur J. Hantz.

PHASE INVERTER CIRCUIT

I don't recall when or where I saw this phase inverter described, but I do feel that you will like its performance in your favorite amplifier. I've used it for several years in a 25-watt amplifier and do not hesitate to recommend it to others.

If we disregard the presence of C2 and R1 and make R2 equal to R3, we have the popular hot-cathode or kangaroo inverter, which has a gain of about 0.9 from its grid to the grid of one of the push-pull tubes. The total gain is about 1.8. This low gain is the result of 50% negative feedback developed across the cathode load resistor, in series with the signal voltage applied to the phase inverter grid.

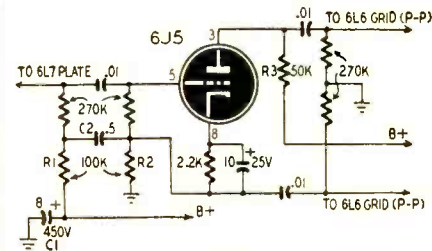


Adding R1 and C2 to the circuit increases the gain tremendously. (See pages 98 and 100, January, 1953, for the theory of this circuit.—Editor) The reactances of C1 and C2 are so low at audio frequencies that R1 and R2 are effectively in parallel. For balanced output from both halves of the inverter, the effective resistance of R1 and R2 in parallel should equal the resistance of R3. So we make R1 and R2 each twice the value of R3.

This inverter should be used with a pentode or other multigridd tube with a high plate resistance. I use a 6L7 with a plate resistance of about 800,000 ohms.—G. R. Anglado

SIMPLE SIGNAL GENERATOR

With low-cost r.f. type signal generators generally available, many service technicians and experimenters overlook the multivibrator as a signal generator suitable for accurate alignment of receiver r.f. and i.f. circuits. The average owner of a multivibrator-type signal generator uses it only for shooting trouble in sets that are dead or badly out of alignment. The major disadvantage of the usual multivibrator signal

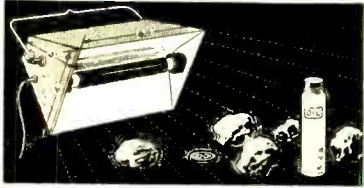
BLAK-RAY SELF-FILTERING ULTRA VIOLET LAMP



BLAK-RAY 4-watt lamp, model X-4, complete with U-V tube. This lamp gives long-wave ultra-violet radiation having a wave-length of 3654 to 4000 angstrom units. Some of the substances made to fluoresce visibly when illuminated by U-V light are certain woods, oils, minerals, milkstone, cloth, paints, plastics, yarn, drugs, crayons, etc. This lamp is self-filtering and the invisible U-V rays are harmless to the eyes and skin. Equipped with spectral-finish aluminum reflector. Consumes only 4 watts and can be plugged into any 110 volt 50-60 cycle A.C. outlet. Will give 2000 to 3000 hours of service. It weighs but 1 $\frac{3}{4}$ lbs. Approved by the Underwriters Laboratories and has a built-in transformer so that it may be safely used for long periods when necessary. Extra U-V tubes are available.

Ship wt. 4 lbs.
ITEM NO. 125
UNUSUAL BUY \$14.75

POWERFUL ALL PURPOSE MOTOR

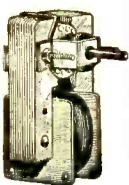

Sturdy shaded pole A.C. induction motor. 15 watts, 3000 rpm. 3"x2"x1 $\frac{3}{4}$ "; 4 mounting studs; $\frac{7}{8}$ " shaft, $\frac{3}{16}$ " diameter; 110-120 volts, 50-60 cycles. A.C. only. When geared down, this unit can operate an 18" turntable with a 200 lb. dead weight. Use it for fans, displays, timers and other purposes. Ship wt. 2 lbs.

ITEM NO. 147
UNUSUAL BUY \$2.45

WATTHOUR METER

Leading makes—reconditioned. Ideal for trailer parks. 100-110 volts, 60 cycles, 2-wire A.C. 5 amp. Heavy metal case $8\frac{1}{2}$ " x $6\frac{1}{4}$ " x 5". Easy to install. Ship wt. 14 lbs.



ITEM NO. 33
NOW ONLY \$4.50

WESTERN ELECTRIC BREAST MIKE



Lightweight 1 lb. carbon microphone. Aircraft type. Breastplate mounting, adjustable 2-way swivel. Easily fastened straps. For home broadcasts, communications etc. Complete with 6 foot cord, hard rubber plug. Serrated plate, non-rusting finish. Ship wt. 2 lbs.

ITEM NO. 152
NEW LOW PRICE \$1.75

AMAZING BLACK LIGHT



250-watt ultra-violet light source. Makes fluorescent articles glow in the dark. Fits any lamp socket. For experimenting, entertaining, unusual lighting effects. Ship wt. 2 lbs.

ITEM NO. 87
A SAVING AT \$2.45

250 POWER TELESCOPE LENS KIT

Make your own high powered 6 ft. telescope! Kit contains 2" diam., 75" focal length, ground and polished objective lens and necessary eye pieces. Magnifies 50x to 250x. Full instructions. Ship wt. 1 lb.

ITEM NO. 123
YOU SAVE AT \$2.95

HUDSON SPECIALTIES CO.
25 West Broadway, Dept. RE-4-53
New York 7, N. Y.


I am enclosing full remittance for items circled below. (Be sure to include shipping charges.)
OR, my deposit of \$..... Ship balance C.O.D.
MINIMUM C.O.D. ORDER \$5.00.
C.O.D. ORDERS ACCEPTED ONLY WITH 20% DEPOSIT
INCLUDE SHIPPING CHARGES.

Circle Items Wanted
87 147 33 152 125 123

Name Please Print Clearly
Address
City Zone State

generator is that its output signal is too broad for accurate alignment of i.f. circuits. This obstacle was overcome in a battery-operated multivibrator type signal generator described in *Radio and Electronics* (Wellington, New Zealand).

The diagram shows a pair of triode-connected 3S4's in a 400-cycle multivibrator circuit. When the output switch is in the I.F. position, the 400-cycle signal is applied to the tuned winding of a 455-ke i.f. transformer. This circuit is shocked into damped oscillations at a rate of 400 times per second. This, in effect, produces a 455-ke signal modulated by a rough 400-cycle note. With the switch in the R.F. position, the harmonics of the multivibrator fundamental blanket the spectrum up to about 30 mc.

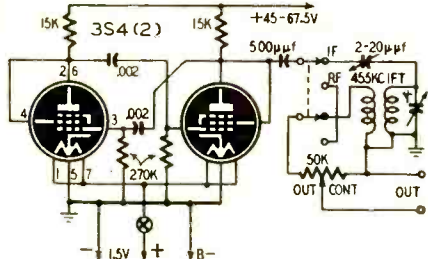

The author describes the use of the unit for aligning superhets. Connect the output of the generator to the mixer circuit and peak the i.f. transformer trimmers for maximum output. Tune the set to the high-frequency end of the band, adjust the oscillator trimmer to about two-thirds capacitance, and feed the i.f. output of the generator to the antenna terminals of the set. Peak the antenna and r.f. trimmers for maximum output. Tune the set to the low end of the band and adjust the oscillator padder for maximum output.

Disconnect the generator, connect an antenna, and tune in a station on the high end of the band. Identify the station and check its frequency against the dial setting. If the dial setting is incorrect, set the dial correctly and retune the station with the oscillator trimmer. Use the generator to peak the antenna and r.f. trimmers. Tune in a station on the low end of the band and recheck the dial calibration. Readjust the oscillator padder to bring in the station at the correct dial setting. Repeat the process several times. Touch up the oscillator trimmer on the high end of the band and the padder at the low end so the dial calibration is correct at both ends of the dial. This procedure is particularly useful in lining up a newly constructed receiver.

(Before you sneer at the idea of using a battery-powered signal generator, just stop and think how handy it will be for touching-up the alignment of auto radios and for simple servicing jobs at summer camps and in areas where a.c. is not available.—Editor)

Parts for signal generator

Resistors: 2—15,000, 2—270,000 ohms, $\frac{1}{2}$ watt; 1—50,000-ohm potentiometer.
Capacitors: (Mica): 2—0.02 µf, 1—500 µf; 1—2-20-µf mica or ceramic trimmer.
Miscellaneous: 2—7-pin miniature sockets; 2—354 tubes; 1—s.p.s.t., 1—d.p.d.t. toggle or rotary switch; 1—455-ke i.f. transformer. Batteries, hardware, hookup wire.


END

GROMMES AMPLIFIERS



A high fidelity single unit amplifier with unusual performance. Power output, 10 watts, 20 watts peak. Distortion at 10 watts, 1% harmonic and 2% intermodulation. Frequency response ± 5DB: 20 to 20,000 CPS (± 1 DB, 30 to 20,000 CPS at 10 watt level).
Model 50 PG \$55.00

Model 215BA 15 Watt

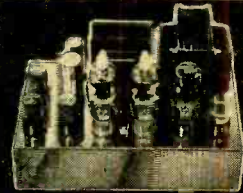

ALL TRIODE BASIC AMPLIFIER

Response 80 to 100,000-CPS. Peak power 2-watts. Distortions at 8 watts, 87% H. and 2% I.M. 25 DB feedback from 2 loops, 2 direct coupled stages, cathode follower drivers.
\$99.50


WRITE FOR CATALOG



PRECISION ELECTRONICS, Inc.
9101 King Avenue, Franklin Park, Ill.

HI-GAIN TUNER-BOOSTER

LESS TUBES WITH DIAL

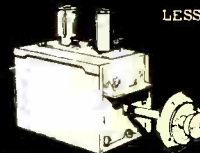

\$4.75

COMPLETE WITH TUBES
\$6.00

Solve poor T.V. reception with a Hi-Gain Booster. Banish weak fringe areas, reduce snow. This unit comes to you as a highly serviceable High-Gain Tuner. Uses 6J6 Tubes in very efficient Hi-Q Circuit. Has 8 tuned circuits using pure silver inductances and individual compensation providing high gain on all channels. Built in 5:1 Vernier Drive. This is a complete departure from ordinary tuners.

All necessary parts and instructions are included to convert this unit in a few minutes to one of the highest gain boosters on the market regardless of price.

100 ASSORTED RESISTORS

Carbon insulated. New in current RMA Values 5%, 10% and 20% in $\frac{1}{2}$, 1 and 2 watt. \$2.00

Shipments sent postpaid when full payment is enclosed with order. 25% deposit on C.O.D. shipments. Open account privileges to rated firms. Send for our new bulletin listing many T.V. Components at terrific price reductions.

FRANK W. DECRAY & ASSOCIATES

11842 W. Jefferson Boulevard Culver City, California

ANOTHER OUTSTANDING JOBBER PENINSULA TELEVISION & RADIO SUPPLY

42 West Gibson St. Salinas, Calif.

HAS THE SENSATIONAL NEW **TEICO** 473-K 7" SCOPE KIT **IN STOCK!**



\$79.95

5% higher on West Coast

YOUR HIGH-PAYING
interesting career in
TELEVISION
starts here!

HOME STUDY COURSE



with one of America's
LARGEST schools

There's a place for YOU in the tremendous, billion-dollar Television, Radio & Electronics industry! It's so easy to get started with the famous CRESCENT SCHOOL course. Learn in your spare time . . . illustrated, simplified lessons and kits to practice on. No previous training needed. Send for FREE sample lesson . . . make this day the day you started on your way to a brilliant career!

APPROVED FOR KOREAN VETS
Also Day & Eve. Classes
Trained at Our School



CRESCENT SCHOOL
"One of the Largest of its kind"

SEND COUPON TODAY!

CRESCENT SCHOOL Dept. E4
500 Pacific Street, Bklyn. 17, N.Y.

Sirs: Rush your FREE sample lesson and full details about the CRESCENT SCHOOL Course—at no obligation to me!

Home Study Course Residential Course

NAME _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____

PRES-PROBE CONDENSER TESTER



Finds Intermittent Condensers Instantly
NET

Pres-probe's sliding tip with variable resistance prevents condenser heating. Tests with power on. Requires no adjustment. Stops guesswork. Saves time. Convenient probe size (7 1/2" long). Satisfaction guaranteed.



See Your Dist. or Order Direct

PRES-PROBE CO.
4034 N. Sixth St., Milwaukee 12, Wisc.

NEW
These two TV-radio books show you over 900 ways to save time and money!

From the publishers of
RADIO - ELECTRONICS



112 Pages \$1.00
132 Illustrations


RADIO & TV HINTS—No. 47

No matter what phase of electronics you're in—TV, radio, audio or amateur—you can work faster, better, and easier when you know the tricks of the trade. Here's a new and different kind of book which gives you over 300 hints, kinks and short cuts worked out by the experts and passed along to you for only a dollar. It would take you a lifetime to gather all the inside information which is handed to you here this easy way. Order your copy today.

RADIO & TV HINTS presents over 300 practical short cuts on just about every phase of electronics. Conveniently grouped in sections on Test Instruments, Tools, Television, Radio Servicing, Audio, Amateur and Miscellaneous.

TELEVISION TECHNOTES—No. 46

When you're servicing a TV set—time is money and too much of both are wasted in routine trouble-shooting. Here's a book that will cut that kind of time-wasting, nerve-wracking work to the bone. Lists over 600 actual troubles which have cropped up in scores of sets made by 27 leading manufacturers. Tells you what they look like, how they sound and how to put your finger on them and correct them quickly and painlessly. If you're in servicing, you need this book—Get a copy today.

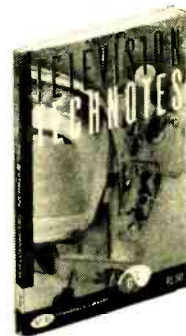

Helps you solve troubles like these: Sync Buzz • Hum • Poor Contrast • Horizontal Wiggle • Microphonics • Arcing • Vertical Jitter • Audio Buzz • Intermittent Picture Tubes • Ineffective A.G.C. • No Vertical Sweep • Blooming Picture • Noise in Picture • Vertical Roll • And many, many others.

128 Pages \$1.50
58 Illustrations

Other GERNSBACK LIBRARY BOOKS
You'll find helpful!

- Radio Tube Fundamentals • Bk. 45 \$1.00
- Basic Radio Course • Bk. 44 \$2.25
- Model Control by Radio • Bk. 43 \$1.00
- High-Fidelity Techniques • Bk. 42 \$1.00
- Public-Address Guide • Bk. 41 75¢
- The Cathode-Ray Oscilloscope • Bk. 40 75¢
- Practical Disc Recording • Bk. 39 75¢

See your distributor—or mail this coupon

GERNSBACK PUBLICATIONS, INC. Dept. 43
25 West Broadway
New York 7, N. Y.

Enclosed is my remittance of \$ _____
Please send me, postpaid, the books checked below.

47—RADIO & TV HINTS
 46—TELEVISION TECHNOTES
 45 44 43 42 41 40 39

Name _____
(Please print clearly.)

Street _____
City _____ Zone _____ State _____

RADIO-ELECTRONICS

DRILL SIZE REMINDER

The average radio service technician uses wood, machine, and sheet-metal screws so rarely that he usually has to waste a lot of time looking up data on the drill size for the holes. One way of having the desired data on hand when needed is to write it on the cover of the screw container.

For sheet-metal screws, record the size of the drill used for the pilot hole. On wood screws, write the drill size and depth of the starter hole. For machine screws, write the size of the smallest drill which will allow the screw to pass without binding or damaging the threads. Recording this data on the screw containers takes only a few moments and will save lots more time before a box of screws is exhausted.—*Ken Maxwell*

OSCILLOSCOPE BLANKING

Many TV sweep generators do not provide a means for blanking out the retrace curve on the scope when sweeping an i.f. or discriminator response curve. Since the sweep is a 60-cycle sine wave, it is possible to blank out the return trace by connecting one side of the scope's 6.3-volt heater winding to the intensity-modulation input terminal in the scope. With this connection, the single trace is easier to read and inspect.—*Bedrich Hrachovina*

SOLDERING TIPS


Before screwing in a new soldering iron tip, apply a coating of graphite to its threads. This prevents freezing and makes the tip easy to remove when it has worn out.—*Leonard Pfeiffer*

TV FOCUSING TRICK


Here is a trick to facilitate focusing a TV set: I use a strong reading glass to magnify the scanning lines. Then I adjust the focus control until the scanning lines are as sharp and distinct as possible.—*John A. Comstock*

QUICK IRON HEATER

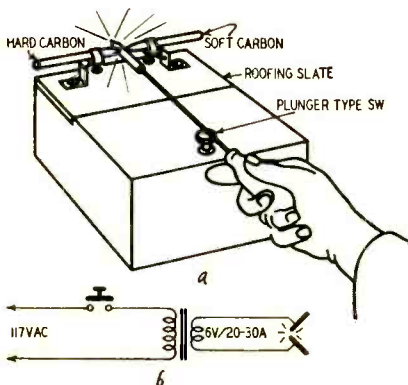This type of soldering-iron heater is rugged, safe, dependable, and unusually fast heating. The iron is heated by placing its tip in an arc between two carbon rods connected across the secondary of a 6-volt, 20-30-ampere filament transformer. The construction of the unit is shown in the illustration at *a*. The schematic is shown at *b*.



APRIL, 1953

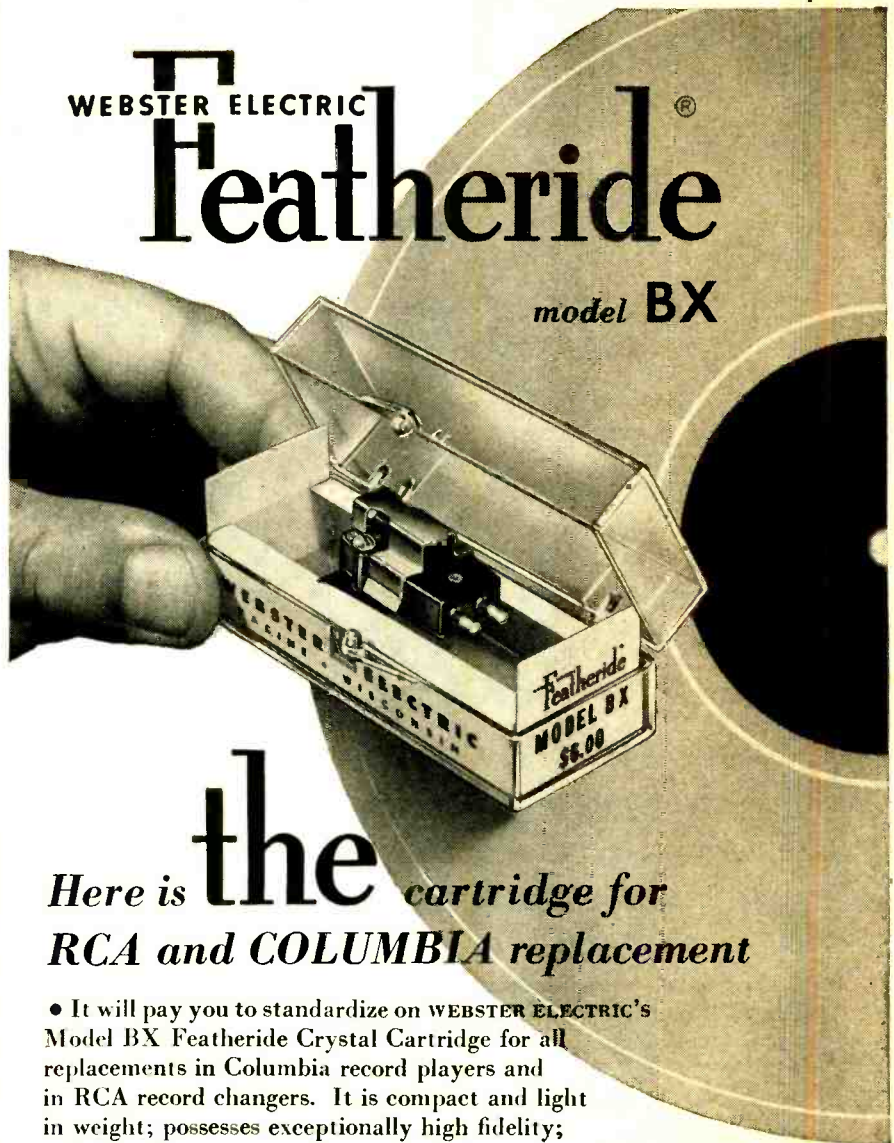

Here is **the** cartridge for **RCA and COLUMBIA** replacement

- It will pay you to standardize on WEBSTER ELECTRIC'S Model BX Featheride Crystal Cartridge for all replacements in Columbia record players and in RCA record changers. It is compact and light in weight; possesses exceptionally high fidelity; and (like all WEBSTER ELECTRIC replacement cartridges) has the famous Dri-seal protection against moisture and humidity.

- Individually packed in a handsome, useful plastic "jewel case," the Model BX is furnished with 1-mil needle, bracket and spring for installing in RCS series RP168 and 190 changers, also spacer nut for installing in series 193-1 changers. Simply remove bracket and spring to install in Columbia or other 1/2" mounting arms. Write us for Catalog Sheet RC189.

specifications and data

Application: 33 1/3 and 45 RPM records	Construction: Moulded plastic half-shells
Output (1000 CPS): .5-.75 volts	Mounting: Universal for RCA record changers and Columbia record players
Tracking Pressure: 7 grams	Terminals: Pin Type
Cut-off Frequency: 7000 CPS	Needle: Osmium tipped, replaceable
Weight: 10 grams	Webster Electric Co., Racine, Wisconsin • Established 1909

Webster Electric Company, Clark and DeKoven Streets, Dept. RE-4 Racine, Wis.
Please send me Catalog Sheet RC189 on Featheride Pick-up Cartridges for replacement use.

Name _____ (Please Print)
Address _____
City _____ State _____ Zone _____
Jobber Service Technician Other

WEBSTER ELECTRIC
RACINE • WISCONSIN

"Where Quality is a Responsibility and Fair Dealing an Obligation"

NEW IT'S TERRIFIC! EICO 7 MODEL 470 -INCH PUSH-PULL SCOPE



KIT
\$79.95
Factory Wired
\$129.50

- HIGHLIGHT FEATURES:**
- Boosted Vert. Sensitivity: 10 mv rms/in.
 - Extended flat freq. response: 10 cps—1 MC (± 2 db).
 - 3-step freq.-compensated attenuator; cathode follower input.
 - Internal voltage calibrator; dir. cal. screen.
 - Extended sweep range: 15 cps—100 kc.
 - Int. pos. or neg., ext. & line sync.
 - On front panel: sawtooth, 60 cps outputs; intensity mod. & ext. sync inputs.
 - Var. phasing of int. 60 cps sweep.
 - Direct connection to CRT plates.

ORDER NOW!

For full specifications on Model 470 and the complete EICO line, write for latest catalog.

ALLIED RADIO

833 W. JACKSON BLVD., CHICAGO 7, ILL.



"Mrs. O'Toole, may I have that kit of JENSEN NEEDLES on the chair, please?"

TV Receiver Sensitivity Measurements made Simple with

The New "SensiMeter"*

... a "must" in fringe areas



Net \$129.50
*Pat. Applied For

Approved by leading television manufacturers!

- * Takes the guesswork out of TV service
- * Checks receiver from antenna terminals to picture tube
- * Microvolt scale is divided into 3 sections as a guide for the servicemen
- * Sensitivity testing is accepted by servicemen as the best method of determining the cause of bad pictures

Consult your jobber or write for further information

SI SERVICE INSTRUMENTS COMPANY
422 South Dearborn Street, Chicago 5, Illinois

TRY THIS ONE


The heater is turned on by a micro-switch mounted inside the box with its plunger protruding on the outside. The hard carbon rod is the type used in arc lamps and movie projectors. The other is a soft type which may be taken from a discarded flashlight cell. Clamps for holding the carbons can be made from sheet metal or can be purchased from electrical supply dealers.

I find that this is the fastest practical method of heating large soldering irons. Long ice-picks (or lengths of drill rod) can be threaded and fitted into small, specially shaped copper tips used for getting into those tight places.

This heater develops a very high heat, so it takes a little practice to get the iron to the right temperature without burning it. A clock or watch with a sweep second hand is useful in timing the heating operation until you get the hang of it.—*J. Perkinson, Jr.*

NOVEL TONE CONTROL

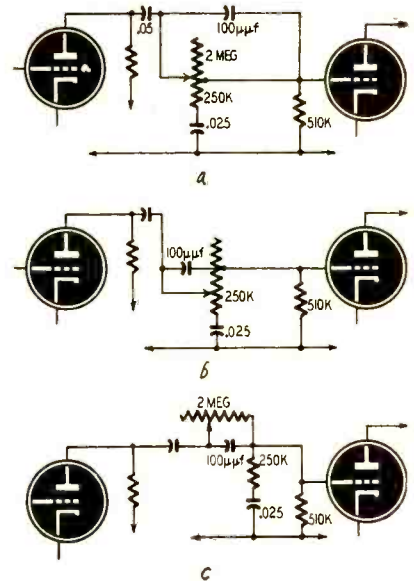While rebuilding a phono amplifier I found myself with just enough space on the control panel for one tone control while I wanted two separate controls for bass and treble boost. I considered using concentric controls, but abandoned the idea in favor of this single-control circuit which provides normal response or bass or treble cut, simply by turning the control toward opposite ends of its range.



The control circuit consists of a 2.5-megohm potentiometer tapped at 250,000 ohms and two capacitors. The control network is used between two high-mu triodes.

Response is normal when the arm of the control is opposite the tapped point as in drawing *a* in the illustration. The arm of the control is moved toward the low-resistance end for bass boost and toward the open end to boost the highs. Diagrams *b* and *c* show the equivalent circuits for treble and bass cut, respectively.—*Dr. Leon Greenberg.*

END

REMOTE FM TUNER

? *Is there any way to adapt an FM tuner for remote control? Push-button tuning is desirable, but if this is not feasible, can the dial and control portion of the tuner be mounted at a distance from the rest of the tuner?—E. E. W., Burlingame, Calif.*

A. For push-button tuning, replace each section of the tuning-capacitor gang with a multiposition rotary switch and small ceramic trimmer capacitors. The switch must have as many sections as there are tuning capacitor sections. There should be one capacitor and one switch position for each FM channel that you wish to receive. Wire the switch so it switches a different capacitor across the coil in each position. Adjust the capacitors—4-30- μ f units—for proper tuning of each channel.

If the distance between the tuning head and the main chassis of the tuner is limited to a few feet, you may be able to use flexible control shafts like those used in some automobile radios and military communications equipment. Cables longer than three or four feet are likely to cause backlash which will make tuning difficult. If the tuner has a.f.c., it will compensate for a small amount of backlash.

Another method of providing remote control for the FM tuner is to separate the tuning control, dial, and the r.f. amplifier, converter, and oscillator circuits from the i.f. circuits. The latter may be on the remote chassis with the power supply. The remainder of the components would then be installed on a small chassis to be placed at the operating position. The first i.f. transformer would be on the chassis with the i.f. strip and connected to the mixer plate through low-capacitance coaxial cable.

The capacitance of the cable will shunt the transformer primary, making it difficult to resonate the i.f. input circuit. If the transformer is slug-tuned, you may have to replace the fixed tuning capacitor with a smaller one or remove it entirely. If the circuit still doesn't tune to the i.f., try replacing the powdered-iron slug with a brass one.


IMPEDANCE MEASUREMENTS

? *How can I measure the impedance of ribbon-type transmission lines without using involved formulas? I want to spot-check the impedance of ribbon line as it is being extruded in a plastics plant.—M. D., Brooklyn, N. Y.*

A. We would suggest using an r.f. impedance bridge or a standing-wave ratio indicator and a grid-dip oscillator or any convenient source of low-power r.f. voltage. Take a sample of the line and terminate it in a noninductive resistor having a resistance equal to the nominal characteristic impedance of the line. Feed in the r.f. signal and measure the standing-wave ratio on the bridge. When the impedance of the line equals the resistance of the load, the

Best! for UHF Fringes!

TEL-A-RAY Fringemaster

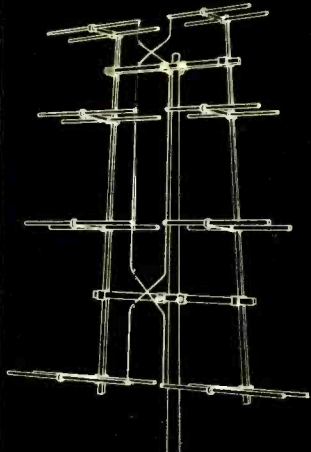


Looking for good UHF reception in the fringe areas? Try the Fringemaster, Tel-a-Ray's new collinear-type, cut to channel array built from noncorrosive Dural. Effectively covers 20 channels.

The Fringemaster's all-grounded construction gives positive lightning protection, reduces noise and permits a high front-to-back ratio. Also, there is no insulator loss!

List prices: No. 800 (not assembled) \$10.95; No. 800A (completely assembled ready for mounting on mast) \$12.95; No. 800D (two-bay array not assembled) \$24.95; No. 800DA (two-bay array completely assembled) \$27.50.

Write today for information on the complete line of Tel-a-Ray UHF antennas. Tel-a-Ray has a UHF antenna for every installation problem.



TRADE MARK

Tel-a-Ray
ENTERPRISES INCORPORATED
 BOX 332E · HENDERSON · KENTUCKY

Now! HANDLE UP TO 90% OF TV TROUBLES



by the easy
PICTURE ANALYSIS METHOD!

Cut hours of tedious TV trouble-shooting to minutes! Make repairs twice as fast! Operation of Ghirardi's new PIX-O-FIX TV TROUBLE FINDER GUIDE is simplicity itself. Covers all TV receivers.

PIX-O-FIX TV TROUBLE FINDER GUIDE

By Ghirard. & Middleton

Only \$1.

Covers 24 common troubles identified by actual screen photos

- • • 190 possible causes of these troubles localized to receiver stage or section where they are most likely to occur.
- • • 253 step-by-step remedies for these troubles
- • • 4,500 words in CAUSE AND REMEDY section to show exactly what to do.

WHAT TO DO—HOW TO DO IT

Step-by-step repair instructions follow. Components likely to be faulty are specified. Quick tests are outlined. PIX-O-FIX guides you every step of the way! Remember! PIX-O-FIX is NOT a "fix-it-yourself" gadget for consumers. It is a truly professional device for servicemen, apprentices and students—prepared by two of the nation's foremost service instructors—A. A. Ghirardi and R. G. Middleton.

MONEY BACK IF YOU'RE NOT SATISFIED!

Simply pin a \$1 bill to this ad. Mail with your name and address to the publisher. If not satisfactory, return PIX-O-FIX in 10 days and your \$1 will be refunded promptly. (Price outside U.S.A. \$1.25 same money-back guarantee).

Dept. RE-43, RINEHART BOOKS, Inc., Technical Div., 232 Madison Ave., New York 32, New York

V E E GOT IT!

Check these tube prices against your last purchase order. We're positive you can't beat these prices for branded tubes, fully guaranteed and individually boxed.

0Z4A .. .68	6AV6 .. .41	6W1 .. .49
1B3 .. .68	6BA6 .. .48	6X4 .. .39
1R5 .. .61	6BC5 .. .56	6X5 .. .38
1S5 .. .52	6BG6 ..1.40	12AT7 .. .73
1T4 .. .61	6BE6 .. .49	12AU6 .. .48
1U1 .. .60	6BQ6 .. .90	12A07 .. .57
1X2 .. .68	6C1 .. .40	12BA6 .. .48
3Q1 .. .65	6CB6 .. .56	12BF6 .. .48
3Q5 .. .70	6CD6 ..1.79	12SA7 .. .57
3S1 .. .60	6D5 .. .40	12SK7 .. .55
5U4 .. .45	6E .. .71	12SN7 .. .57
5Y3 .. .35	6K6 .. .48	12SQ7 .. .47
6AC7 .. .80	6S1 .. .51	19BG6 ..1.44
6AG5 .. .56	6SA7 .. .57	25BQ6 .. .90
6AK5 ..1.15	6SK7 .. .55	25L6 .. .50
6AL5 .. .45	6SQ7 .. .47	35W4 .. .34
6AQ5 .. .51	6SN7 .. .57	3Z5 .. .40
6AT6 .. .41	6T8 .. .83	50B5 .. .53
6AU6 .. .45	6V6 .. .51	50L6 .. .53


Jobber Inquiries Invited

All prices F.O.B., N.Y. Min. order \$5.00. C.O.D.'s, of course. 25% deposit with order. Pre-paid shipments if check in full with order.

V E E Dept. E-1
 Box 134,
 Queens Village 29, N.Y.

PERSONAL MUSIC

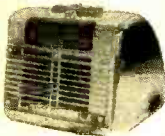CHROME MUSIC BOX containing 5" Speaker and Coin Timer Motor. Can be used for remote speaker in Home, Car, Shop, Boat, Office, etc. Timer Motor operates from 24 Volt 60 cycle. Prices:



With 5" Dynamic Speaker \$3.55
With 5" PM Speaker \$4.95
TRANSFORMER—24 Volt to operate Timer \$1.50
Motor from 110 V. 60 cycle

RECEIVER & TRANSMITTER

RECEIVER BC-229—TRF Receiver with 3 Plug in Coils to cover Freq. Range 201 to 398, 2500-4700, 4150-7700 KC. With 6 Tubes: 1/37 - 1/38 - 3/39 Power Supply required 6 or 12 Volt & 250 Volts. Size: 16" x 8" x 7". Schematic included \$8.95
TRANSMITTER BC-230—Voice modulated Trans. with 5 Plug in Coils to cover Freq. Range 2500 to 7700 KC with 4 Tubes: 2/10y - 2/45 & RF Meter 0-1.5 Amps. Power Supply required 6 or 12 Volt and 350 Volts. Size: 13" x 8" x 7". Schematic included \$8.95

SPECIAL BUY—FOR BOTH ABOVE RECEIVER & TRANSMITTER: \$15.00

PE-101C DYNAMOTOR

(Reprints of original CQ conversion articles, Oct. and Dec., 1952 issues, furnished.)
2 OR 12 VOLT
This is the Dynamotor the Hams have been talking about. Easily adapted to supply 625 V. @ 150 MA. and 325 V. 125 MA. at 12 V.—or 300 V. 90 MA. and 160 V. 110 MA. at 6 V. (Illustration shows modified) NEW: \$4.95



BATTERY SWITCHING UNIT & METER
Used to switch load from one battery to another, or 6 to 12 Volts. Contains Weston 2" Meter, 0-15 Volt DC Scale for reading battery voltage, 20 Amp DPDT Switch & Indicator. Case size: 4" x 6 1/4" x 2 3/4". NEW: \$2.95

JUST WHAT YOU NEED . . .

- Standard Test Leads, 4" x 1 1/2" Prads. Pair 39¢
3 for \$1.00
Phone Plug—Nickel Plated, Screw Terminals. Each: 39¢ — 3 for \$1.00
Instrument Knobs—Bar, Octagon, Round, Set Screw, Skirts—Ass't. 10 for \$1.00
Line Cord—Brown Rubber 7 Ft., Molded Rubber Plug Each: 29¢ — 4 for \$1.00
Line Cord—Black Rubber 6 Ft. Angle Molded Plug Each: 39¢ — 3 for \$1.00
Resistors Carbon—Ass't. 1/4, 1/2, 1 and 2 Watt 100 for \$2.95
Resistors—Wire Wound—Ass't. 5 to 100 Watt 25 for \$2.95
Mica Condensers—Ass't. Values & Voltages—50 for \$2.95

ATTN.: TELEVISION FRINGE AREAS
AIRCRAFT GUY CABLE—1/2" 7 x 7 Strand, Weatherproofed, Galvanized, Preformed—920 lb. Test. This cable has been tested and proven in many fringe areas over many years—millions of feet in use. PRICES: 4 1/2¢ per Ft.—1000 Ft. @ 4¢ per Ft.—5000 Ft. @ 3 1/2¢ per Ft.

REVERSIBLE MOTOR

Motor Reversible—3.7 RPM. 40 lb. torque. 24 Volts DC or AC. Motor size: 5 1/2" x 4 1/2" x 3 1/16". Shaft size: 2 1/32" x 5/16". Philco No. 441-1008 NEW: \$5.95
110 Volt AC TRANSFORMER to operate above motor NEW: \$4.95

AERIAL WIRE—Phosphorus Bronze #16 Stranded, 200 lb. test. Weatherproof, 150 Feet on Reel. RL-3 with Clips \$1.50
Telephone Wire—3 Cond. copper & steel, 525 Ft. \$4.75

TRANSFORMERS—110 V. 60 CYCLE PRIMARIES:

6.3 V. 1 Amp \$1.25 24 V. 1 Amp \$1.95
24 V. 1/2 Amp \$1.50 24 V. 6.5 Amp \$5.95
6—24—or 30 Volt, 8 Amp \$5.95
Two 12 V. 4 Amp Windings—gives 12 V. 8 Amp or 24 V. 4 Amp \$5.95
325-0-325 V. 50 MA.—6.3 V. 2.5 Amp; 6.3 Volt 6 Amp (Rect. 6x5) Half Shell—2 3/8" x 3 3/8" No. T-23-28 \$2.75
175-0-175 V. 40 MA.—6.3 V. @ 2.4 A.; 6.3 V. @ 6 A.; Halfshell: 2 5/8" x 2 3/16" x 2 3/8", No. T-23-40 \$1.75
350-0-350 V. 90 MA.—6.3 V. @ 3 A.; 5 V. @ 3 A.; Upright—3 1/8" x 3 1/8" x 3 1/8" \$3.25

Address Dept. RE • Minimum Order \$5.00
Prices F.O.B., Lima, O. 25% Deposit on C.O.D. Orders

FAIR RADIO SALES
132 SOUTH MAIN ST. • LIMA, OHIO

load absorbs all the power and there are no standing waves on the line. This indicates that the load resistance and line impedance are equal.

These measurements can be made with the Antennascope made by Eldico of New York, Inc., 44-31 Douglaston Parkway, Douglaston, N. Y., and the Micro-Match made by The M. C. Jones Electronics Co. of Bristol, Conn.

2-TUBE, 360-WATT RIG

? About 10 years ago, one of the tube manufacturers published details on the construction of a 2-tube, 3-band, 360-watt transmitter for 160, 80, and 40 meters. It used a 6V6 crystal oscillator and an 813 final amplifier. The screen of the 813 was in series with the cathode return of the oscillator. If you are familiar with this transmitter, I would appreciate having its circuit printed in an early issue. I want to use the rig for c.w. traffic nets—R. O. W., Camden, N. J.

A. We hope that this diagram is the one you want. It appeared originally in data supplied by RCA. The 6V6-GT oscillator operates straight through with 160-, 80-, and 40-meter crystals. The plate-cathode resistance of the oscillator tube is used as a part of the voltage divider supplying the 813 screen grid. A glass (G or GT) tube must be used in this application. If a metal tube should be used, its shell would be 400 volts above ground and would present a serious shock hazard.

The tapped, untuned oscillator coil, L1, consists of 155 turns of No. 28 enameled wire close-wound on a 1 1/8-inch form. Taps for 40 and 80 meters are placed at 21 and 65 turns respectively. If the inductance of L1 or the position of the taps is just right, minimum r.f. crystal current will occur simultaneously with maximum oscillator output. Crystal current is indicated by a glow in the 60-ma pilot lamp in series with the crystal. Oscillator output is indicated by the 813 grid current. Slight variations in wire and coil diameter may cause excessive crystal current or sluggish oscillation, and make it necessary to adjust the position of the taps. If crystal current


causes the lamp to light, the inductance of the part of the coil in use is probably too large. If the crystal is hard to start, not enough coil is being used. The final tank coils are 500-watt units for 160, 80, and 40 meters.

Preliminary oscillator adjustments should be made with the 813 plate lead disconnected and the supply voltage reduced to about 1,000 by inserting a 50,000-100,000-ohm resistor in series with R1. The oscillator should supply 3 to 7 ma of grid current to the 813 without the crystal pilot lamp showing any color. If the circuit performs satisfactorily, connect the 813 plate, tune the output tank to resonance, and raise the supply voltage to 2,000. The 813 can then be loaded to 180 ma for c.w. operation. Grid current will be 7 to 10 ma; power output will be approximately 275 watts. If the supply voltage is 1,600 or less, R2 should be disconnected so the 813 will have correct screen voltage.

Plate modulation may be employed by reducing the supply voltage to 1,600 and disconnecting R2. Approximately 135 watts of audio is required for 100% modulation. This can be supplied by class-B 809's operating from a separate 1,000-volt supply or by class-B 811's with 1,500 volts on the plates. The 811's and the 813 can be operated from a common 1,500-volt supply.

(The 811 has recently been superseded by the 811-A, which has the same electrical characteristics with improved internal construction. At 1,500 volts—the maximum for intermittent service—the 811-A's draw a peak-signal plate current of 313 ma, with a recommended plate-to-plate load of 12,400 ohms.—Editor)

The 813 plate-current jack and the rotor of the final tuning capacitor are hot. To minimize the danger of shock, the jack should be mounted on a bakelite strip recessed about 1 1/2 inch behind the front chassis apron, and the tuning capacitor shaft should be fitted with an insulated coupling and extension shaft. Plate spacing of the final tank capacitor should be .07 inch or more for c.w. and .084 inch for phone operation. END

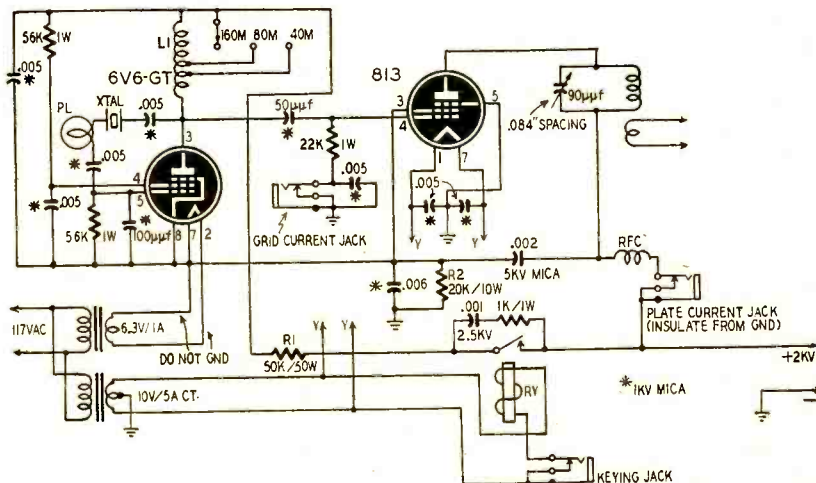

PHILCO 8-200

This set had a 60-cycle hum on all stations when the volume was turned up. It was found to be originating in the 14C6 circuit. All components checked good. The trouble was cleared up by resoldering all connections on the 14C6 socket.—*Manuel Silva*

BELMONT 12AX26 TV SET

In this model, sound bars may appear in the picture when the set is jarred or when the volume control is advanced. This trouble is usually caused by a microphonic tube in the i.f. strip.

To determine which tube is causing the trouble, gently tap each of the i.f. tubes while watching the picture. The bad tube will produce sound bars when you tap it. Replacing the tube will eliminate the difficulty.—*John A. Comstock*

ADMIRAL 20X1, 20Y1, 20Z1

Field reports and laboratory tests indicate that about 80% of the complaints of vertical foldover with high line voltage can be cleared up by replacing the 12AU7 vertical output tube. Try several 12AU7 tubes of brands other than Sylvania before replacing the vertical output transformer.—*Admiral Service Bulletin*

ZENITH 5-S-127

The complaint was severe motorboating. The trouble was caused by a short between the B plus lead from the second i.f. transformer and one end of the white a.v.c. resistor.

The set was restored to normal operation by replacing the B plus lead with one having heavier insulation.—*Gordon V. Weeks*

SPARTON TV RECEIVERS

Insufficient width in Sparton rectangular-tube TV receivers may be caused by variations in the characteristics of the 6BQ6-GT horizontal output tubes. A 30,000-ohm resistor may be added across R110 and R111 (33,000 and 39,000 ohms, respectively) in series with the screen voltage and provides greater width.

If the 30,000-ohm resistor is already in the circuit and width is greater than necessary, the screen voltage and width may be reduced by removing the resistor.—*Sparton Service Division Bulletin*

TELE-KING 516M TV SETS

These models and others using the TVC chassis may have complaints of a constant buzzing in the audio with the volume turned down. If realigning the sound i.f.'s does not cure the trouble, shield the lead between the plate of the 6T8 (triode section) and the control grid of the 6AQ5 audio output tube. This lead is very long (about 18 inches) and picks up radiation from the vertical output transformer.—*Dock B. Gerald*

WESTINGHOUSE H-210, H-211

Sticking dial pointer is cured by lubricating two dial pulleys and increasing cord tension.—*Westinghouse Service Hints*




SKY-Hi MASTS

- HYDRAULIC
- PNEUMATIC
- TELESCOPIC

For Radar, Microwave or Television

- Steel or Aluminum Constructed
- Special Masts any Height Required to 200 feet
- Standard Masts - 40, 60, 80 or 100 foot
- Raised to desired height by Oil, Water or Air
- Fluid Control Valves and Latches for proper sequence in Raising and Lowering (Pat. Pending)
- Most Versatile Mast on the Market

Used with all types of antennas!

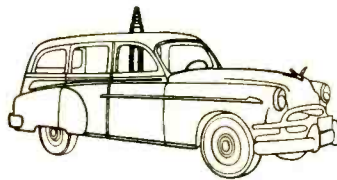

Mobile units for Trucks, Trailers and Station Wagons. Cannot be equaled for Signal Probing. Excellent for UHF Survey Work. Pinpoints strongest signal height. WRITE FOR DETAILS

• Used extensively by government and commercial agencies

WE INVITE COMPARISON

THOMAS MOLD & DIE COMPANY

BOX 126 - WOOSTER, OHIO

Windsor RADIO & TV RECEIVING TUBES

Peak Performance TESTED*—and GUARANTEED

TYPE	PRICE	TYPE	PRICE	TYPE	PRICE	TYPE	PRICE
1A7GT	\$.61	6AQ5	\$.46	6K6GT	\$.41	12AK7	\$.61
1B3GT	.63	6AR5	.38	6L6CA	.50	12BA6	.65
1L4	.57	6AS5	.50	6Q7GT	.50	12BH7	.63
1N5GT	.57	6AT6	.38	6SA	.46	12SA7GT	.52
1R5	.56	6AU6	.43	6SBGT	.52	12SK7GT	.50
1S4	.61	6AV6	.37	6SA7GT	.52	12SL7GT	.61
1S5	.47	6BA6	.96	6SH7GT	.47	12SN7GT	.54
1Q8	.56	6BE6	.45	6SK7GT	.50	12SQ7GT	.62
1T4	.71	6BA7	.60	6SL7GT	.62	12SQT	.62
1T5GT	.46	6BC5	.53	6SN7GT	.54	19B6G	1.39
1U4	.55	6BD5GT	.89	6S7GT	.42	25BQ6GT	.69
1U5	.46	6BE6GT	.46	6T8	.77	25LGT	.48
1X2A	.67	6BE6	.46	6U8	.78	25W4GT	.48
2X2	1.50	6BF5	.60	6V6GT	.46	25Z6GT	.42
3V4	.56	6BF6	.39	6W4GT	.45	35B5	.48
3Q5GT	.65	6BG6G	1.34	6W6GT	.57	35C5	.48
3S4	.55	6BH6	.57	6X4	.34	35L6GT	.47
3V4	.56	6BJ6	.48	6Y6G	.58	35W4	.30
5R4GV	.91	6BK7	.88	12AT6	.48	3Z5GT	.10
SU4G	.40	6BQ6GT	.89	12AT7	.68	50A5	.68
5Y4G	.29	6BQ7	.84	12AU6	.43	50B5	.47
5Y4G	.39	6C4	.37	12AU7	.53	50C5	.47
6AB4	.46	6CB6	.53	12AV6	.37	50L6GT	.47
6AC5	.54	6CD6G	1.85	12AV7	.79	117Z3GT	.39
6AK5	.95	6J5GT	.40				
6AL5	.40	6J6	.62				
		OAZ	.88	5654	1.50		

* To merit your confidence—to insure your satisfaction—Every tube we ship has been tested in a radio or TV set for PEAK PERFORMANCE. Each tube is attractively packaged in individual carton—and, Each WINDSOR Tube you buy carries the full RTMA GUARANTEE!

25% Deposit with Order. All Merchandise F.O.B. New York City. For orders less than \$10, add \$1 handling cost. Deduct 2% if full remittance accompanies order. All merchandise subject to prior sale and price change without notice.



Windsor ELECTRONIC TUBE CO. Dept. C-4 1515 SHEEPSHEAD BAY ROAD BROOKLYN 35, N. Y.

ANOTHER OUTSTANDING JOBBER
VAN SICKLE RADIO SUPPLY CO.
 1320 S. Calhoun St.
 Ft. Wayne, Indiana


HAS THE SENSATIONAL NEW
TEICO 470-K 7" SCOPE KIT
 IN STOCK!
 \$79.95

PEN-OSCIL-LITE
 Extremely convenient test oscillator for all radio servicing; alignment • Small as a pen • Self powered • Range from 700 cycles audio to over 600 megacycles u.h.f. • Output from zero to 125 v. • Low in cost • Used by Signal Corps

• Write for information.
GENERAL TEST EQUIPMENT
 38 Argyle Ave. Buffalo 9, N. Y.

... to servicemen who really want to learn to use the OSCILLOSCOPE fully and accurately!

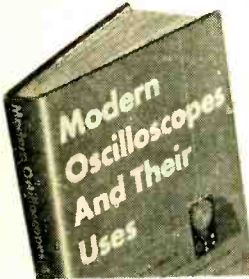A complete guide to using the handiest service instrument of all... On all kinds of jobs!... Written so you can really understand it



MODERN OSCILLOSCOPES AND THEIR USES

By JACOB H. RUITER, Jr.
of Allen B. DuMont Laboratories, Inc.
326 pages, 370 illustrations, \$6.00



Like most servicemen, you've probably read a lot about oscilloscopes—but still don't know how to use them as well as you'd like to.

If so, here's the book you've been looking for! In MODERN OSCILLOSCOPES AND THEIR USES, Mr. Ruiter starts right at the beginning. He shows how oscilloscopes are designed and how they work. Then he explains exactly how, why and where to use them. No involved mathematics. No puzzling theoretical discussions. Instead, this world famous authority gets right down to earth in answering the questions that have probably kept you from taking full advantage of the money-making service possibilities in oscilloscopes.

HOW TO HANDLE TOUGH JOBS EASIER AND FASTER



From routine troubleshooting to handling the toughest realigning and adjusting jobs, each operation is carefully explained. These include determining where and how to use the oscilloscope; how to make connections; how to adjust circuit components; how to set the controls—AND, ABOVE ALL, HOW TO ANALYZE PATTERNS. From dozens of pattern photos you see and learn to recognize patterns that are wrong, nearly right and exactly right!

SAVE HUNDREDS OF DOLLARS IN AM-FM-TV SERVICE TIME!



Busy servicemen have told us that the television service section of MODERN OSCILLOSCOPES alone is worth the entire price of the book. Here you get exact procedures for aligning the I-F stages; aligning V-F tuned circuits in the mixer stage; checking gain sweep circuits... and dozens of other jobs. Similar big sections cover use of the oscilloscope in AM and FM radio servicing and other electronic uses.

No other type of specific service training can mean so much to you in terms of increasing your efficiency and earning power. Use coupon today!

READ IT 10 DAYS at our risk!

Dept. RE-43, RINEHART BOOKS, Inc.
Technical Division
232 Madison Avenue, New York 16, New York

Send MODERN OSCILLOSCOPES AND THEIR USES for 10-DAY FREE EXAMINATION. If book is satisfactory, I will then send you \$6.00 promptly in full payment. If not, I will return book postpaid in good condition and owe you nothing.

Name.....
Address.....
City, Zone, State.....
Employers' Name and Address.....
Price outside U.S.A. \$6.50, cash only. Money back if you return book within 10 days.

UNUSUAL BRIGHTNESS PROBLEM

An Emerson model 585 was brought in with the complaint that the brightness control did not function properly. It was impossible to get uniform darkness over the screen.

When the brightness control was backed down, dark bars appeared at the sides of the screen. Continued rotation of the control resulted in the bars widening until they met in the center to black out the screen.

A Du Mont RA-112 came in with the same complaint. However, in this case, the picture got black on only one side.

In both cases the trouble was caused by an open filter capacitor on the B plus line to the first anode of the picture tube.—J. V. Caraseno

60-CYCLE HUM IN RCA KCS38 CHASSIS

Complaints of 60-cycle hum in extremely strong signal areas can be cleared up by referring to Figs. 1 and 2 and making the following modifications:

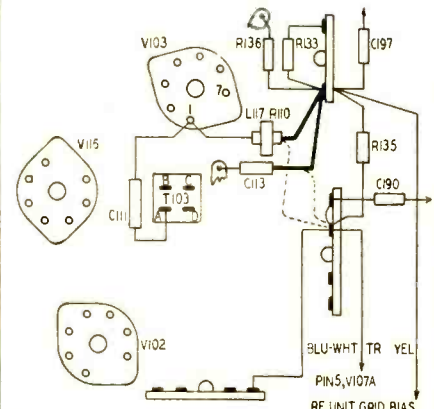


Fig. 1—Wiring changes in RCA KCS38.

Disconnect R110-L117 and C113 from their present tie-point at the junction of R135 and C190 and reconnect them to the adjacent tie-point at the junction of C197, R135, R136, and R133. The original wiring which is removed is shown in dashed lines on the pictorial diagram in Fig. 1 and on the schematic in Fig. 2.

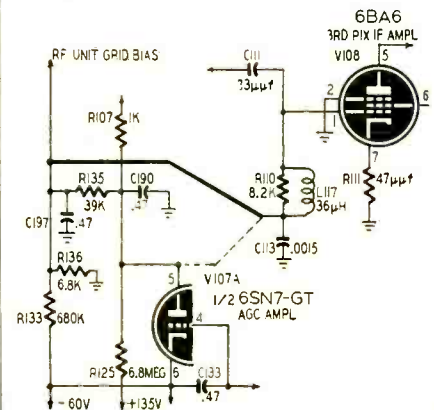


Fig. 2—Schematic of circuit changes.

The heavy lines indicate new wiring. These changes, which produce a greater a.g.c. voltage at the r.f. stage and first picture i.f. amplifier, have been made in late production models of the KCS38 chassis.—RCA Radio Phono TV Tips

STAN-BURN E-D-A-R-K-E

★ CATHODE RAY TUBE SPECIALS ★

Standard Brands—Unconditionally Guaranteed	Price	Price	
GENERAL ELECTRIC 21EP4A	\$7.35		
STP4	\$43.55	24AP4A \$8.75	
7JP4	18.15	10BP4A SHELTON \$14.30	
10BP4A	18.35	12LP4A	17.80
10FP4A	24.40	14CP4	20.35
12KP4A	27.50	15DP4	22.55
12LP4A	21.40	16FP4	24.85
12UP4B	27.10	16EP4A	24.85
14CP4	20.60	16DP4A	24.85
16AP4A	29.10	16FP4A	24.85
16DP4A	26.65	16LP4A	24.85
16GP4	27.85	16KP4A	24.85
16HP4	25.25	17BP4	26.05
17BP4A	23.90	19DP4	28.50
17CP4	33.90	19AP4	28.50
19AP4A	34.80	20CP4	30.80
20CP4	35.45	21EP4	32.45
20LP4	36.95	16EP4A Rautand	42.00

★ ANTENNAE SPECIALS ★

Price	Price	Price
DOUBLE V 3/8"	1.11	12 or more \$2.98
DOUBLE V 3/8" Dowel	2.45	
10 Element Conical 3/8"	3.95	2.95
Folded Hi Straight Low Quick Rig	3.55	2.55
WINDOW CONICALS	4.25	3.25
	4.95	3.75

★ MASTS ★

5 FOOT SWEDGED	.79	.69
10 FOOT PLAIN	1.39	1.29

★ TV WIRE ★

42 Mil.	\$9.95 M Ft.
55 Mil. 300 OHM	14.95 M Ft.
72 OHM COAXIAL	45.00 M Ft.

★ CHASSIS 630 REGAL with Cascade Tuner \$149.50

★ OPEN FACE CABINET 39.00

★ WIRE RECORDERS IN STOCK

WILCOX GAY—Model 2410	\$ 89.97
PENTRON—Model 9T3C—2-speed Tape Recorder	Net 134.50
RADIO CRAFTSMAN Model C400—Hi Fi Amplifier	Net 42.90
Model C10—AM—FM Tuner	Net 131.50
Model CS00—Williamson Amplifier	Net 99.50

We also carry MASCO—BOGEN—PILOT, etc. Amplifiers—Pre-Amps, FM Tuners and WEBSTER Tape Recorders.

★ Audio Devices, Discs and Scotch Tape in Stock

Audio Plastic Red Oxide Plastic tape—\$3.30

Half-hour spool...\$2.30 One-hour spool...\$3.30

★ AUTHORIZED DISTRIBUTORS for: General Electric, Kenrad, Tung-Sol, National Union, De Wald, Regal, Automatic and General Motors.

★ We carry a complete stock of HI-FIDELITY and SOUND EQUIPMENT. Send us your requests. We also carry a complete line of popular makes of Radio and TV tubes, at 50% discount. Also many other special purpose and transmitting types, and all electronic parts and equipment at lowest prices. Send us a list of your requirements for prompt quotations.

★ Terms: 20% with order. Balance COD. All prices FOB. NEW YORK Warehouse. Minimum order \$5.00.

★ Write for our latest price list to Dept. RE-4

★ **STAN-BURN RADIO and ELECTRONICS CO.**
(C.B.S. THEATRE BLDG.)
1697 BROADWAY • NEW YORK 19 N.Y.

★ **STAN-BURN RADIO and ELECTRONICS CO.**
(C.B.S. THEATRE BLDG.)
1697 BROADWAY • NEW YORK 19 N.Y.

Holds the Screw! Drives it too!

Unconditionally Guaranteed

Quick-Wedge SCREW-HOLDING SCREWDRIVER

Ask for it at your Dealer
Kedman Co., 233 S. 5 W., Salt Lake City, Utah

A. G. Cudahy, Kenosha, Wisc.	10.00
Dave's Radio & TV Service, St. Paul, Minn.	5.00
Harry L. Gormley, Philadelphia, Pa.	5.00
Morris Klein, Glassport, Pa.	5.00
Jim Schaller, Van Nuys, Calif.	1.00
Ship's Company and students of FAETULANT Detachment #2, U. S. Naval Air Station, Jacksonville, Fla.	38.37
Carl C. Shirley, St. Petersburg, Fla.	2.00
C. O. Sims, Pitman, New Jersey	10.00
Mr. & Mrs. R. E. Slight, Massillon, Ohio	5.00
Albert Steinberg, Phila., Pa.	15.00
Ruth & Lois Vandebree, Noank, Conn.	1.00

RADIO-ELECTRONICS Contributions as of February 19, 1953 \$9,949.59
 FAMILY CIRCLE Contributions .. 584.50

TOTAL Contributions as of February 19, 1953 \$10,534.09

So Simple

"A child could fix a TV set,"
 They tell us, as we work and sweat.

"A child could do it," we reply,
 "But *children* are too smart to try."
 —JEANNE DEGOOD

CORRECTION

Clear Beam Television Antennas, Burbank, California, was omitted from our annual Antenna Directory (January) because of difficulties in mail service. The company manufactures v.h.f., u.h.f., and special u.h.f. lead-in, antennas and accessories.

Radio Thirty-Five Years Ago
 In Gernsback Publications

HUGO GERNSBACK Founder	
Modern Electrics	1908
Wireless Association of America	1908
Electrical Experimenter	1913
Radio News	1919
Science & Invention	1920
Television	1927
Radio-Craft	1929
Short-Wave Craft	1930
Television News	1931

Some of the larger libraries still have copies of ELECTRICAL EXPERIMENTER on file for interested readers.

APRIL 1919

ELECTRICAL EXPERIMENTER

- Grand Opera in Your Home, by H. Gernsback.
- Guiding Airships with the "Radio Barrage", by Lee de Forest.
- The Moon's Rotation, by Nikola Tesla.
- How to Make a Direct-Reading Wave-meter and Decremeter, by H. Winfield Secor.
- German Radio Apparatus Used at Metz.
- Radiotelephony to Airplanes a Great Success. END

APRIL, 1953

NOW!

TEST, SERVICE

12v. AUTO RADIOS

New Electro


DC Power Supply

Model C-12

0-16 Volts for 0-8

Amperes Continuous Output. Up

to 12 Amperes Intermittently.

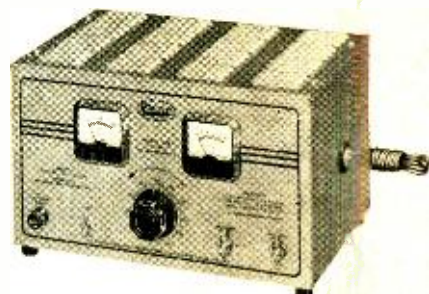

Ripple Only 3% at Full Load

Completely variable output makes it possible to test equipment under any voltage input condition. Provides filtered adjustable DC voltage for testing and servicing 12 volt and 6 volt auto radios from AC lines. Operates electronic equipment used on trucks, tanks and other mobile units and low voltage devices. Utilizes Superior Powerstat Voltage Control (Model 10) for extremely fine voltage adjustments.

Another Better-Than-Rated EPL Product!

Write for Free Bulletin!

ELECTRO PRODUCTS LABORATORIES

4501-Rc North Ravenswood Ave., Chicago 40, Ill.
 CANADA: ATLAS RADIO CORP., LTD., Toronto, Ont.



-to Gratify Your Wish for Excellence

BOGEN R-701 FM-AM TUNER

• SUPERB REPRODUCTION

• TECHNICAL SUPERIORITY

• HANDSOME STYLING

• OUTSTANDING PERFORMANCE

• EVERY OPERATING CONVENIENCE

The Model R-701 is a truly superb FM-AM radio receiver designed expressly for the discriminating listener. It provides a quality of performance so brilliantly real and so vastly superior to standard mass produced receivers that it must be heard to be believed. Handsomely styled for custom installation, it is easily adaptable to any wall or cabinet closure. Six position function selector switch, volume control, and separate bass and treble correctors centralize all operation on one panel ... permit remote location of the audio amplifier.

MODEL HO10 — A superb all triode amplifier providing minimum distortion (less than 0.3% at 10 watts), maximum response (flat to 50,000 cycles), tremendous dynamic range and overall balance. Ideal for use with the R701 Tuner.

MODEL DO10 — New popular priced Hi-Fi custom Amplifier, designed for use with the new R701 Tuner. Can be mounted directly behind the tuner in most installations. Ten watts output at less than 1% distortion. Response flat 20-20,000 cps.

WRITE FOR LITERATURE TO DESK RE-4

DAVID BOGEN CO., INC.

29 NINTH AVE., NEW YORK 14, N. Y.

A Quarter Century of Electronic Equipment Specialization

Depend on Mallory
for
Approved Precision Quality



“Better Than Ever”

“I put a Mallory Vibrator in it. Used ’em for years on all my service work and haven’t had a call-back yet.”

That is the main reason you’ll find 5 out of 6 service men using Mallory Vibrators for all their service work. When you put a Mallory Vibrator in a set, the job stays sold . . . no call-backs . . . no wasted time to run up costs.



The patented, tuned mechanism in Mallory Vibrators is the secret of their dependability and long life . . . the reason they are more widely used as original equipment than all other makes combined.

These exclusive performance features give you better vibrators, available in a complete line, meeting or exceeding original equipment specifications . . .

Slow contact make . . . for less wear

High contact pressure . . . for low resistance

Fast clean break . . . for reduced arcing

Next time you order vibrators . . . ask for Mallory. It is a sure way to beat the call-back problem . . . be sure all your service jobs stay “sold”.

P. R. MALLORY & CO. Inc.
MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
RECTIFIERS • POWER SUPPLIES • FILTERS • MERCURY BATTERIES

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA

Portrait of a serviceman

...building a reputation

This could be you . . . making a name for yourself in your own community . . .

To you, fixing a television set is a routine job . . . but to your customer, it's an important event . . . and she expects to get her money's worth.

Once she's seen the familiar RCA trademark on those tube cartons, you have her complete confidence. She's sure now that her set is in good hands.

And it is . . . because you've learned from experience, that the superior quality of RCA Tubes and Kinescopes is your best measure of protection against the costliness and inconvenience of premature tube failures. It's good to know you can fix a receiver and forget about call-backs.

Helping you to safeguard your reputation is a vital, everyday service of RCA Tubes. And that protection is yours at no extra cost.



DYNAMIC NEW PROMOTION PLAN TO HELP YOU BUILD YOUR BUSINESS

Ask your RCA Tube Distributor for your copy of the colorful, 16-page booklet "A Magic Pass-Key to Customer Confidence."

FREE



A brand-new campaign is outlined, illustrated, and described in full detail. Be sure to get your copy. It's free!



RADIO CORPORATION of AMERICA

ELECTRON TUBES

HARRISON, N. J.

ADV Plans, LLC

Copyright Notice:

The entire contents of this CD/DVD are copyright 2014 by ADV Plans, LLC. All Rights Reserved.

Reproduction or distribution of this disk, either free or for a fee is strictly prohibited. We actively monitor and remove listings on eBay thru Vero.

You are free to copy or use individual images in your own projects, magazines, brochures or other school projects.

Only the sellers listed here are authorized distributors of this collection:
www.theclassicarchives.com/authorizedsuppliers

Please view our other products at
www.theclassicarchives.com,
or our ebay stores:

[TheClassicArchives](#)
[ADVPlans](#)
[SuperShedPlans](#)

