

NOVEMBER 1954

RADIO - ELECTRONICS

TELEVISION • SERVICING • HIGH FIDELITY

HUGO GERNSBACH, Editor

In this issue:

Servicing "Dog"
TV Receivers



Save Time With
Test Equipment



A Low-Cost
Crossover
Network



A.F.C. For Your
FM Receiver



35¢

U. S. and
CANADA

Repairing TV antennas
a quarter-mile above
New York's sidewalks
(see page 4)



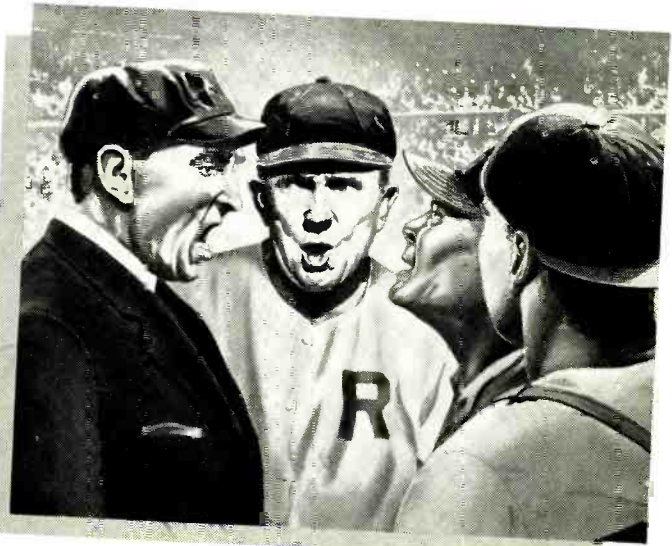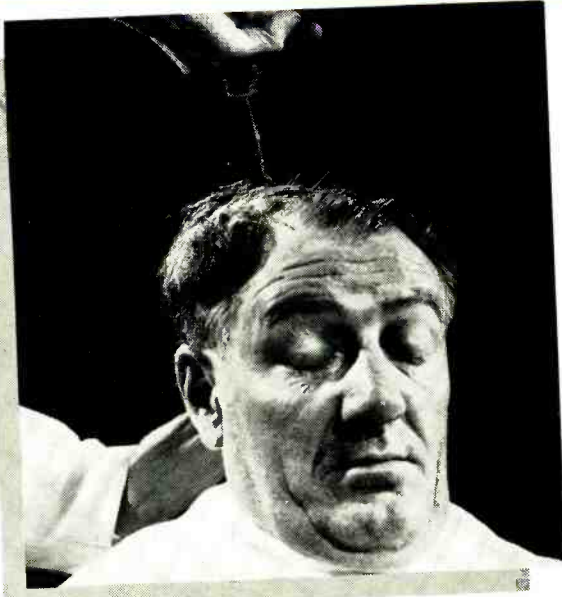=SERIOUS SERVICEMEN= DRAW A BEAD ON QUALITY,=



=OFFER PROFESSIONAL TREATMENT AND AVOID RHUBARBS.=

They combine dependable
products with skilled workmanship.
They know they can depend
on Du Mont Teletrons
to do more for their service.

Replacement Sales, Cathode-ray Tube Division,
Allen B. Du Mont Laboratories, Inc., Clifton, N. J. *T.M.



An Invitation...

To men who want to "go places" in TV SERVICING

Find out about this NEW,
ALL-PRACTICE WAY
of becoming a Professional
TV SERVICEMAN

If you have some Radio or Television experience, or if you know basic Radio-Television principles but lack experience—NRI's new Professional Television Servicing course can train you to go places in TV servicing. This advertisement is your personal invitation to get a free copy of our booklet describing this training in detail.

Learn-by-Doing "All the Way"

This is 100% learn-by-doing, practical training. We supply all components, all tubes, including a 17-inch picture tube, and comprehensive manuals covering a thorough program of practice. You learn how experts diagnose TV defects quickly. You see how various defects affect receiver performance—picture and sound; learn causes of defects, accurately, easily, and how to fix them. You do more than just build circuits. You get practice recognizing, isolating, and fixing innumerable troubles.

You get actual experience aligning TV receivers, diagnosing the causes of complaints from scope patterns, eliminating interference, using germanium crystals to rectify the TV picture signal, obtaining maximum brightness and definition by properly adjusting the ion trap and centering magnets, etc. There isn't room on this or even several pages of this magazine to list all the servicing experience you get.

UHF & COLOR TV Making New Boom

Installing front-end channel selector strips in modern UHF-VHF Television receivers and learning UHF servicing problems and their solution is part of the practice you get. To cash in on the coming color TV boom you'll need the kind of foundation in knowledge and experience this training gives.

Get Details of New Course Free

Once again—if you want to go places in TV servicing, we invite you to find out what you get, what you practice, what you learn from NRI's new course in Professional Television Servicing. See pictures of equipment supplied, read what you practice. Judge for yourself whether this training will further your ambition to reach the top in TV servicing. We believe it will. We believe many of tomorrow's top TV servicemen will be graduates of this training. Mailing the coupon involves no obligation.



Train at home easily, quickly, for TV's top servicing jobs. NRI's Professional Television Servicing course includes a 17-inch picture tube and all other tubes and components to build a complete TV Receiver, Oscilloscope, Signal Generator, H.F. Probe. Complete training, including all equipment, available now for a low introductory price—under \$200 on easy terms.



National Radio Institute, Dept. 4MFT
16th and U Sts., N.W., Washington 9, D. C.

Please send my FREE copy of "How to Reach the Top in TV Servicing." I understand no salesman will call.

Name.....Age.....

Address.....

City.....Zone....State.....

RADIO - ELECTRONICS

Formerly RADIO CRAFT • Incorporating SHORT WAVE CRAFT • TELEVISION NEWS • RADIO & TELEVISION*

Hugo Gernsback
Editor and Publisher
M. Harvey Gernsback,
Editorial Director
Fred Shunaman
Managing Editor
Robert F. Scott
W2PWG, Technical Editor
Jerome Kass
Associate Editor
I. Queen
Editorial Associate
Matthew Mandl
Television Consultant
Angie Pascale
Editorial Production
Wm. Lyon McLaughlin
Tech. Illustration Director
Sol Ehrlich
Art Director

Lee Robinson
General Manager
John J. Lamson
Sales Manager
G. Aliquo
Circulation Manager
Adam J. Smith
Director, Newsstand Sales
Robert Fallath
Promotion Manager
Seymour Schwartz
Advertising Production

Gernsback Publications, Inc.
Hugo Gernsback
Chairman of the Board
M. Harvey Gernsback
President
G. Aliquo
Secretary



Member
Magazine Publishers
Association

ON THE COVER

Maintenance work high up on the Empire State Building's television antenna tower. The picture was rendered by a novel process by Martin J. Weber from an ordinary black-and-white photo by Ed Clarity, which was separated photographically into the four line originals from which the plates for printing the cover were prepared.



CONTENTS

NOVEMBER 1954

Editorial (Page 31)	
Hot Electrons—or Cold?.....	by Hugo Gernsback 31
Television (Pages 32-45)	
Unusual TV Circuits.....	by Robert F. Scott 32
Servicing Dog Receivers.....	by Robert G. Middleton 34
Zero-Reference and Alignment.....	by Engineering Staff, Scala Radio Co. 36
Element Sizes for U.H.F. Antennas.....	by Matthew Mandl 38
Color TV Circuits, Part VI—The three-gun picture tube and its control circuitry.....	by Ken Kleidon and Phil Steinberg 40
Mechanical Bugs Are Deadliest.....	by Milton Lowens 41
Television—it's a cinch (Thirteenth conversation, second half: Parasitic capacitance; value of load resistors; high-frequency compensation circuits).....	by E. Aisberg 42
TV Service Clinic.....	by Jerome Kass 44
Test Instruments (Pages 46-57)	
Sine-wave Square-wave Generator.....	by Frank J. Di Elsi 46
Save Time with Test Equipment.....	by Edward M. Noll 48
VR Tube Tester.....	by Joseph Sodaro 51
Compensated Headphone Circuit.....	by George D. Philpott 52
Signal Generator.....	by A. J. Galofre 53
Neon-Lamp Test Set.....	54
Square Waves: \$1.00.....	by Don Ketchum 55
Radio (Pages 56-62)	
Electronic Headphone.....	by John A. Irwin and I. Queen 56
Swinging Chokes and Power Supply Regulation.....	by N. H. Crowhurst 58
Adding A.F.C. to your FM Tuner.....	by A. Ringel and E. R. Gunny 61
Punch Press Control Circuit.....	by Walter T. Stevenson 62
Audio—High Fidelity (Pages 63-92)	
A Low-Cost Crossover Network.....	by James P. Rogers 63
Servicing High-Fidelity Equipment, Part IX—Equalization and Frequency Response.....	by Joseph Marshall 66
High-Quality Audio, Part XV—Tape Recorders: Mechanical and Electrical Characteristics.....	by Richard H. Dorf 79
For Golden Ears Only.....	by Monitor 86
Electronics (Pages 94-106)	
Now—Diodes Amplify!.....	by Eric Leslie 94
The Photo transistor.....	by Harry Mileaf 96
The Magnetic Amplifier.....	by Leo G. Sands 103
DEPARTMENTS	
The Radio Month.....	6
Correspondence.....	14
Technicians' News.....	108
New Tubes and Transistors.....	110
Technotes.....	117
Patents.....	119
Radio-Electronic Circuits.....	125
Try This One.....	128
New Devices.....	131
Question Box.....	138
Business.....	142
People.....	146
Technical Literature.....	149
Books.....	152

MEMBER Audit Bureau of Circulation

Vol. XXV, No. 11

Average Paid Circulation over 180,000

RADIO-ELECTRONICS, November 1954, Vol. XXV, No. 11. Published monthly at Mt. Morris, Illinois, by Gernsback Publications, Inc. Entered as Second Class matter June 23, 1954, at the Post Office at Mt. Morris, Ill. Copyright 1954 by Gernsback Publications, Inc. Text and illustrations must not be reproduced without permission of copyright owners. EXECUTIVE, EDITORIAL AND ADVERTISING OFFICES: Gernsback Publications, Inc., 25 West Broadway, New York 7, N. Y. Telephone REctor 2-8630. Hugo Gernsback, Chairman of the Board; M. Harvey Gernsback, President; G. Aliquo, Secretary.

SUBSCRIPTIONS: Address correspondence to Radio-Electronics, Subscription Dept., 404 N. Wesley Ave., Mt. Morris, Ill., or 25 West Broadway, New York 7, N. Y. When ordering a change please furnish an address stencil impression from a recent wrapper. Allow one month for change of address. SUBSCRIPTION RATES: In U. S. and Canada, and in U. S. possessions, \$3.50 for one year; \$6.00 for two years; \$8.00 for three years; single copies 35c. All other foreign countries \$4.50 a year; \$8.00 for two years; \$11.00 for three years.

BRANCH ADVERTISING OFFICES: Chicago: 7522 North Sheridan Road, Tel. ROckers Park 4-8000. Los Angeles: Ralph W. Harker and Associates, 600 South New Hampshire, Tel. MArtilson 6-1271. San Francisco: Ralph W. Harker and Associates, 582 Market St., Tel. GARfield 1-2481. FOREIGN AGENTS: Great Britain: Atlas Publishing and Distributing Co., Ltd., London E.C. 4. Australia: McGill's Agency, Melbourne. France: Brenano's, Paris 2e. Belgium: Agence et Messageries de la Presse, Brussels. Holland: Trilecton, Heemstede. Greece: International Book & News Agency, Athens. So. Africa: Central News Agency Ltd., Johannesburg; Capetown, Natal, Universal Book Agency, Johannesburg. Middle East: Steimatzky Middle East Agency, Jerusalem. India: Broadway News Centre, Dadar, Bombay #14. Pakistan: Paradise Book Stall, Karachi 3. POSTMASTER: If undeliverable send form 3578 to: RADIO-ELECTRONICS, 25 West Broadway, New York 7, N. Y. *Trademark registered U.S. Patent Office.



National Schools brings you a new dimension in training for TELEVISION-RADIO-ELECTRONICS

YOU CAN LEARN BY HOME STUDY, IF—

- you are ambitious to increase your earning power.
- you want to broaden your knowledge and skill.
- you choose the school with the most complete training and service.

50 Years of Successful Training

National Schools has been training men for success since 1905. Our graduates are located around the globe, in good-paying jobs in servicing, installation and manufacturing... in public and private industry, or in their own businesses. All this experience and background are your assurance of success.

What This New Dimension in Home Study Means to You

As a National Schools student, with Shop Method Home Training, you master *all phases* of the industry—TV, Radio, Electronics—theory and practice. You learn HOW and WHY, in one complete course at one low tuition.

Because National Schools' world headquarters are in Los Angeles—"capital city" of TV-Radio-Electronics—our staff is in close touch with industry. Our lessons and manuals are constantly revised to keep you up-to-the-minute on latest developments. We show you how to make spare time earnings as you learn, and we give you free placement assistance upon graduation. National Schools is approved for G. I. Training. Both Resident and Home Study courses are offered. If you are of draft age, our training helps you achieve specialized ratings and higher pay grades.

This *new dimension* enables us to train you as you should be trained at home, regardless of your age or previous education.

Your Course Includes Valuable Units

We send you important equipment, including a commercial, pro-

fessional Multitester... plus parts to build Receivers, Oscillators, Signal Generator, Continuity Checker, other units, and Short Wave and Standard Broadcast Superhet Receiver.

Mail Coupon for Complete Information

Get these two free books about this new dimension in Home Training. A comprehensive, illustrated fact-book and a sample National Schools lesson. No obligation, so mail coupon today.

NATIONAL SCHOOLS
TECHNICAL TRADE TRAINING SINCE 1905
Los Angeles 37, Calif. • Chicago: 323 W. Polk St.
In Canada: 811 W. Hastings St., Vancouver, B. C.



MAIL NOW TO OFFICE NEAREST YOU!

(mail in envelope or paste on postal card)

NATIONAL SCHOOLS, Dept. RG-114

4000 S. FIGUEROA STREET OR **323 W. POLK STREET**
LOS ANGELES 37, CALIF., OR **CHICAGO 7, ILL.**

Rush FREE BOOK, "Your Future in Radio-TV-Electronics," and FREE LESSON. No obligation, no salesman will call.

NAME _____ BIRTHDAY _____ 19__


ADDRESS _____

CITY _____ ZONE _____ STATE _____

Check if interested ONLY in Resident Training at Los Angeles.

VETERANS: Give date of discharge.

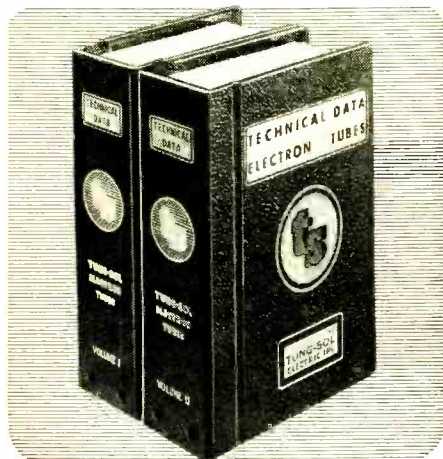TUNG-SOL TECHNICAL DATA PAYS OFF IN SERVICE!



T-58 700 pages—600 tube types



NEW! 1954 Edition! T-70 200 pages of data on CR tubes, receiving and special tubes, dial lamps



T-31 300 blueprint base diagrams for 1100 tube types

Here's the most practical set of tube reference books in the industry—all the information you need for everyday jobs! They're easy to read—easy to use (always lie flat when open). You'll get work done faster with Tung-Sol Technical Data Books. Ask your tube supplier about them.

TUNG-SOL ELECTRIC INC., Newark 4, N. J.
Sales Offices: Atlanta, Chicago, Columbus, Culver City (Los Angeles), Dallas, Denver, Detroit, Newark, Seattle.



TUNG-SOL® easy reference TECHNICAL DATA

Tung-Sol makes All-Glass Sealed Beam Lamps, Miniature Lamps, Signal Flashers, Picture Tubes, Radio, TV and Special Purpose Electron Tubes and Semiconductor Products.



TELEVISION TELEPHONE was recently demonstrated at the Western Electronic Show in Los Angeles. When the telephone receiver is lifted from its hook, the caller's image appears simultaneously on one half of his screen and half the screen of the telephone at the other end of the circuit. Upon answering, the image of the called party is shown on the remaining half of each screen.

A simple adjustment enables either

party to make the entire screen area available for a variety of uses, such as viewing signatures, documents, and miscellaneous articles.


When the set is not in use as a TV telephone, the screen can be used for monitoring an industrial closed-loop television system, for receiving subscription television, or for taking programs from the air in the same manner as a standard television receiver. The system is made by Kay Lab, San Diego.



RATE-GROWN TRANSISTORS are scheduled for mass production by G.-E. Dr. W. R. G. Baker, G-E vice-president, said that the rate-grown process is the only one showing promise of large-scale transistor production at prices competitive with vacuum tubes. Present plans call for a multimillion volume of these transistor units within the next two

years. Their availability and low price should result in widespread use.

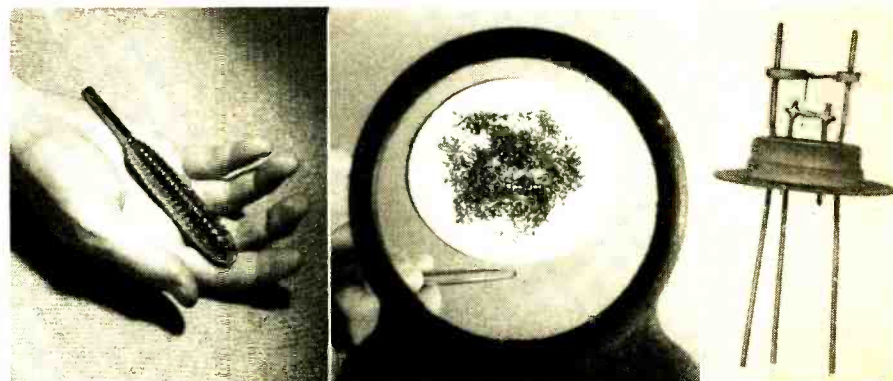The rate-grown process involves introducing special impurities and varying the heat controls during the crystal growing process. By this method, in only two hours, a large ingot is formed (see photo, left) containing as many
(Continued on page 10)



Now IN YOUR OWN HOME Learn

TELEVISION

RADIO-ELECTRONICS

the Amazingly Effective

D. T. I. WAY

—with the aid of BOTH HOME EQUIPMENT and HOME MOVIES



NO PREVIOUS EXPERIENCE NEEDED

NOW... get

EVERYTHING YOU NEED

for real Laboratory-type training AT HOME

Above: Work over 300 fascinating experiments with this equipment



5 INCH "SCOPE"

Oscilloscope



Multi-Meter



21 INCH

Build and keep this BIG DTI Engineered TV set—easily converted to B.H.F. (DTI offers another home training, but without the TV set.)

1. Build over 300 fascinating experiments from 16 BIG SHIPMENTS of Electronic-Radio parts which you KEEP.
2. Build valuable commercial-type test equipment—as shown to the left—which you KEEP. This includes a quality 5 INCH oscilloscope and jewel bearing Multi-Meter—both highly useful for Television work.
3. Build and keep a big 21 INCH TV Set. (D.T.I. offers another home training in Television-Radio-Electronics, but without the TV set.)
4. Use a 16 mm. movie projector and new series of highly instructive movies—a wonderful aid to help you grasp important fundamentals faster... easier... better.
5. Enjoy well-illustrated, easy-to-read lessons with handy FOLD-OUT diagrams.
6. Get an honest-to-goodness EMPLOYMENT SERVICE to help you get a good job after graduating—or assistance in starting your OWN SALES AND SERVICE BUSINESS. Mail coupon today for the complete details.

D.T.I.'s Training is available in Canada



89 WAYS TO EARN MONEY IN TELEVISION RADIO-ELECTRONICS

Get this information-packed publication

FREE!

Mail Coupon Today

What will mailing the coupon below do for YOU? Just this! You'll find out about one of today's most remarkable... practical ways to prepare to get into America's amazing billion dollar opportunity field of TELEVISION-RADIO-ELECTRONICS. You'll see how to get into fascinating work that pays well... that offers one of America's most promising futures... that enables you to start your own business almost "on a shoe string," if you prefer this to a job opportunity.

And above all, you'll get some GOOD NEWS especially welcomed by men anxious to earn REAL MONEY in this thrilling field. For you'll see that NOW you can get the kind of practical, laboratory-type training so desirable for making real progress in Television-Radio-Electronics AND WITHOUT LEAVING HOME.

You'll see that DeVry Technical Institute sends everything needed to set up your own HOME LABORATORY.

You get and keep the same type of basic electronic equipment used in our modern Chicago Training Laboratories. You get home training that includes the knowledge and experience gained from training thousands of students first hand in Chicago.

And to top it all, you use DTI's amazingly effective and exclusive home training aid—INSTRUCTIVE MOVIES. But why not get the complete story? Mail coupon today for information-packed literature.


MODERN LABORATORIES

If you prefer, get all your preparation in our new Chicago Training Laboratories—one of the finest of its kind. Ample instructors, modern equipment. Write for details!

MILITARY SERVICE!

If you're subject to military service, the information we have for you should prove very helpful. Mail coupon today.

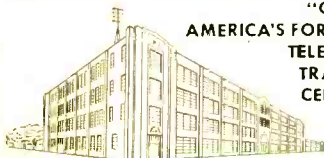"ONE OF AMERICA'S FOREMOST TELEVISION TRAINING CENTERS"



DEVRY TECHNICAL INSTITUTE

AFFILIATED WITH
DEFOREST'S TRAINING, INC.
 CHICAGO 41, ILLINOIS

DEVRY TECHNICAL INSTITUTE

4141 BELMONT AVE., CHICAGO 41, ILL. Dept. RE-11-K

I would like your valuable information-packed publication showing how I can get started toward a good job or my own business in Television-Radio-Electronics.

Name.....Age.....


Street.....Apt.....

City.....Zone.....State.....

Pickering Audio Components...

SYNONYMOUS WITH HIGHEST QUALITY


Design... Manufacture... Performance

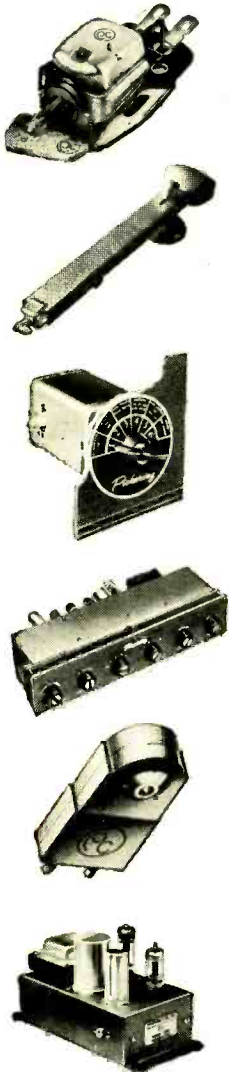

In every field of endeavor . . . manufacturing,
the theatre, concert or contest . . .
there is always one standout.






In HI-FI equipment the standout is Pickering . . .
pioneer in this field, responsible
for the development and introduction of outstanding
components for highest quality performance;
every product bearing the Pickering name

is engineered to conquer the challenge of
optimum performance . . . in their manufacture
the most stringent quality controls are
exercised to assure and maintain the "Ne Plus Ultra"
reputation for products featured by the  emblem.



It's with good reason that professionals use
Pickering Audio Components . . . they know
the values built into Pickering equipment.
INVESTIGATE and you too will use Pickering
components for your HI-FI system. . . .
You'll thrill to new listening experiences . . .
you'll have the same high quality performance
as leading FM/AM good music stations, network
and recording studios . . . REMEMBER, leading
record companies use Pickering Components
for quality control.

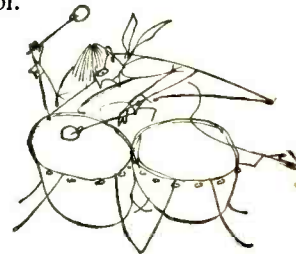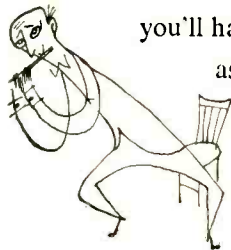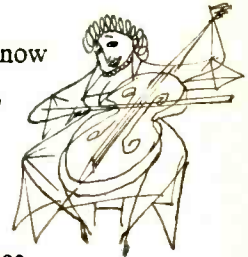

PICKERING and company incorporated •

PICKERING PROFESSIONAL AUDIO EQUIPMENT

Oceanside, L. I., New York

"For those who can hear the difference"

. . . Demonstrated and sold by Leading Radio Parts Distributors everywhere.

For the one nearest you and for detailed literature, write Dept. P-6.

FREE

TELLS HOW -

WE GUARANTEE

TO TRAIN AND COACH YOU AT HOME IN SPARE TIME UNTIL YOU GET

YOUR FCC LICENSE

If you have had any practical experience—Amateur, Army, Navy, radio, repair, or experimenting.

Here is your guarantee

If you fail to pass your Commercial License exam after completing our course, we guarantee to continue your training without additional cost of any kind, until you successfully obtain your Commercial license, provided you first sit for this examination within 90 days after completing your course.

TELLS HOW -

OUR AMAZINGLY EFFECTIVE JOB-FINDING SERVICE HELPS CIRE STUDENTS GET BETTER JOBS. HERE ARE JUST A FEW RECENT EXAMPLES OF JOB-FINDING RESULTS:

GETS CIVIL SERVICE JOB

"Thanks to your course I obtained my 2nd phone license, and am now employed by Civil Service at Great Lakes Naval Training Station as an Equipment Specialist."

Kenneth R. Leiser, Fair Oaks, Md., Del., McHenry, Ill.

GETS STATE POLICE JOB

"I have obtained my 1st class ticket (thanks to your school) and since receiving same I have held good jobs at all times. I am now Chief Radio Operator with the Kentucky State Police."

Edwin Healy, 264 E. 3rd St., London, Ky.

GETS BROADCAST JOB

"I wish to thank your Job-Finding Service for the help in securing for me the position of transmitter operator here at WCAE, in Pittsburgh."

Walter Koschik, 1442 Ridge Ave., N. Braddock, Pa.

GETS AIRLINES JOB

"Due to your Job-Finding Service, I have been getting many offers from all over the country, and I have taken a job with Capital Airlines in Chicago, as a Radio Mechanic."

Harry Clare, 4537 S. Drexel Blvd., Chicago, Ill.

HERE'S PROOF FCC LICENSES ARE OFTEN SECURED IN A FEW HOURS OF STUDY WITH OUR COACHING AT HOME IN SPARE TIME:

Name and Address	License	Lessons
Lee Worthy, 2210 1/2 Wilshire St., Bakersfield, Cal.	2nd Phone	16
Clifford E. Vogt, Box 1016, Dania, Fla.	1st Phone	20
Francis X. Foerch, 38 Beucler Pl., Bergenfield, N. J.	1st Phone	38
S/Sgt. Ben H. Davis, 317 North Roosevelt, Lebanon, Ill.	1st Phone	23
Albert Schoell, 110 West 11th St., Escondido, Cal.	2nd Phone	23

CARL E. SMITH, E.E. Consulting Engineer, President

CLEVELAND INSTITUTE OF RADIO ELECTRONICS
Desk RE-70, 4900 Euclid Bldg., Cleveland 3, Ohio

MONEY MAKING
FCC
Commercial Radio Operator
LICENSE
INFORMATION

TV Engineering

INCLUDED IN OUR TRAINING AND COACHING

TELLS HOW -

EMPLOYERS MAKE JOB OFFERS LIKE THESE TO OUR GRADUATES EVERY MONTH!

Letter from nationally-known Airlines. "We would also appreciate if you would place the following additional advertisement in your bulletin—Wanted—Superintendent of Communications . . . Salary \$866.66 per month."

Letter from nationally known airplane manufacturer. "We need men with electronic training or experience in radar maintenance to perform operational check-out of radar and other electronics systems . . . Starting salary . . . amounting to \$329.33 per month."

Letter from nationally-known Airlines. "We are contemplating placing . . . an Airline Ground Radio Engineer." Starting salary \$385 per month.

These are just a few of the examples of the job offers that come to our office periodically. Some licensed radioman filled each of these jobs; it might have been you!

Ours is the only home study course which supplies FCC-type examinations with all lessons and final tests.

ACT NOW!

Get ALL 3 FREE

Your FCC Ticket is recognized by most employers in the electronic field as proof of your technical ability.



MAIL COUPON NOW!

Cleveland Institute of Radio Electronics
Desk RE-70—4900 Euclid Bldg., Cleveland 3, Ohio
(Address to Desk No. to avoid delay)


I want to know how I can get my FCC Ticket in a minimum of time. Send me your FREE booklet, "How to Pass FCC License Examinations" (does not cover exams for Amateur License), as well as a sample FCC-type exam and the amazing new booklet, "Money-Making FCC License information."

Be sure to tell me about your Television Engineering Course.

Name _____
Address _____
City _____ Zone _____ State _____

FOR PROMPT RESULTS, SEND AIR MAIL
Special tuition rates to member of the U.S. Armed Forces

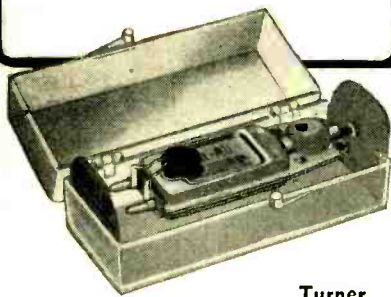REPLACE 95% OF ALL 78 RPM'S WITH 1 CARTRIDGE



Turner
Model AU

You don't have to stock a variety of replacement cartridges with Turner's Model AU. Turner engineering has created this one dual voltage, universal cartridge to replace 95% of all 78 rpm cartridges.

The secret is an externally mounted condenser — leave it on for 2.0 volts or lower output — simply slip it off for outputs over 2.0 volts.

And you can count on Turner quality throughout. The Model AU crystal cartridge tracks perfectly for excellent reproduction without needle hum or hiss. You can't buy a better replacement cartridge than Turner's Model AU.

Model AU
Universal Replacement Cartridge
priced right only \$4.95



Model A High Voltage
Same cartridge as Model AU
but furnished without condenser.
List Price \$4.45

Write today for complete details.

THE TURNER CO.

933 17th
Street NE



Cedar Rapids,
Iowa

IN CANADA, Canadian Marconi Company,
Toronto, Ontario and Branches.
EXPORT: Ad. Auriema, Inc., 89 Broad Street,
New York 4, N. Y.

as 100 wafer-thin layers of specially treated germanium. The ingot is then diced into thousands of very small bars (center). Each bar with leads attached becomes a transistor (right).

A feature of this process is that germanium growth can be varied so that transistors with optimum operating characteristics can be obtained at will.

TEN NEW TV STATIONS have gone on the air since our last report. These are:

KOVR	Stockton, Calif.	13
WJNO-TV	Palm Beach, Fla.	5
WINT	Waterloo—Ft. Wayne, Ind.	15
WTWO	Bangor, Me.	2
WMTW	Poland Spring, Me.	8
KSWM-TV	Joplin, Mo.	12
WCMB-TV	Harrisburg, Pa.	27
WUSN-TV	Charleston, S.C.	2
WMVT	Montpelier, Vt.	3
WCHS-TV	Charleston, W. Va.	8

One station, KTHE, Los Angeles, Calif., channel 28, has gone off the air. CKLW-TV, Windsor, Ont., Canada, channel 9, has gone on the air.

The deletion of KMBC-TV, Kansas City, Mo., channel 9, from the TV station list in the September, 1954, issue was an error. KMBC-TV shared time with WHB-TV. WHB-TV ended operation. KMBC-TV is still on the air.

A SCHOLARSHIP, to be awarded annually to an engineering student who has demonstrated outstanding ability and potentialities in the field of radio-electronics, has been established by Hugo Gernsback, editor and publisher of RADIO-ELECTRONICS. The scholarship has been established at New York University, for students who have completed the junior year in the University's College of Engineering.

The scholarship fund will provide \$1,000 annually to defray the tuition costs of the selected student.



Hugo Gernsback and Lawrence Wechsler


The scholarship fund is the outgrowth of an award made to Mr. Gernsback himself in 1953, when leaders of the electronics industry presented him with a handsome silver trophy in recognition of his "fifty years of devoted effort and contributions to the radio-electronic art." At that time he expressed a wish to establish a Hugo Gernsback

TV SERVICEMEN: here's the help you need

NEW

"TV SERVICE DATA BOOK"

by MILTON S. KIVER

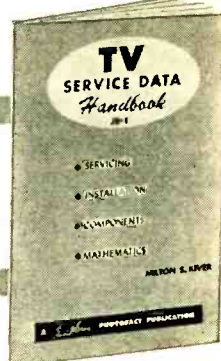

Packed with
facts you'll
use every
single day

**GET IT
TODAY**

**all the data you need
in one handy guide—**

- saves valuable time
- helps you earn more

Instant TV Servicing and Installation Reference: Have at your finger-tips all of the most frequently needed charts, tables and formulas you require in Television servicing and installation. Includes charts on fuses, color codes, attenuator pads, monochrome signal specifications, guy wire lengths, etc.—all the data you'll ever want in your daily work. Save valuable time on calculations by quick reference to the tables of mathematical constants and electrical formulas. Speeds your work for greater earnings.

Trouble-Shooting Guide: Includes section on TV trouble-shooting. Lists common trouble symptoms and tells how to locate defective components. Recommends most effective methods for use of test probes and other accessory equipment. You'll want to keep it handy in your tube caddy for quick reference at the bench or in the field. It pays for itself in a single day's work. Over 100 pages. 5 1/2" x 8 1/2".

ORDER JB-1. \$1.50
Only

**ORDER
TODAY**

HOWARD W. SAMS & CO., INC.

Order from your Parts Jobber today, or write to Howard W. Sams & Co., Inc., 2205 East 46th St., Indianapolis 5, Ind.



My (check) (money order) for \$..... enclosed. Send..... copy (ies) of "TV Service Data Book" (JB-1, \$1.50).

Name.....

Address.....

City..... Zone..... State.....
(outside U.S.A. priced slightly higher)

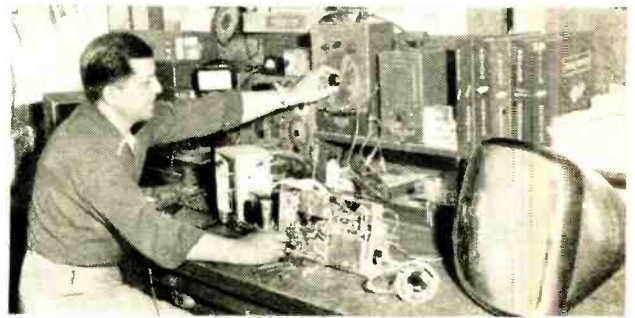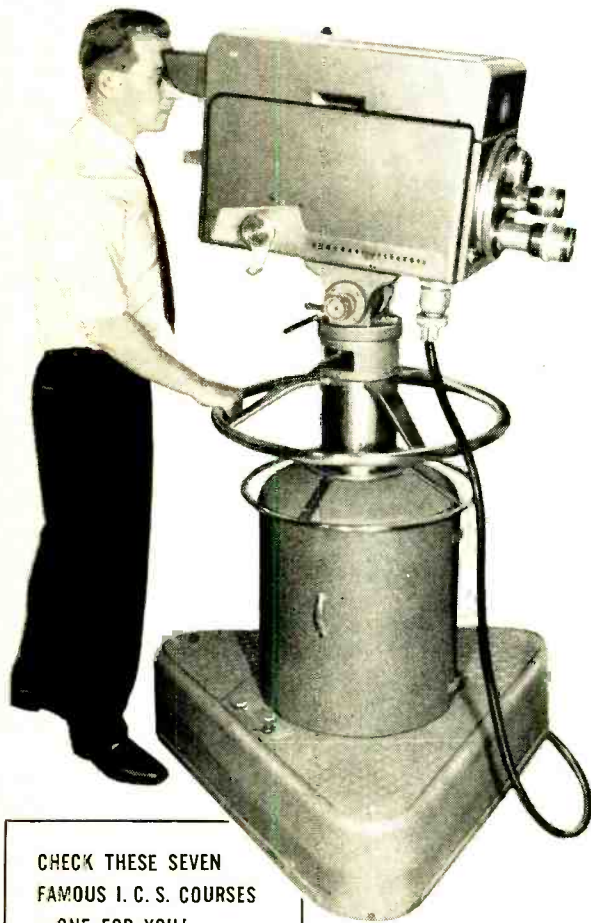Get yourself on the beam to the BIG MONEY in RADIO and TV



That's the way to become an expert Radio or Television service man. Study the bedrock theories and principles. These are vitally important. Nothing can take their place.

No royal road to learning

Listen to what radioman R. G. Hamlin of Bay City, Michigan, says: "There's no royal road to learning. I am convinced more than ever after examining the lessons of friends who were lured by short-cut methods . . . 'understandability' and 'rememberability' are of utmost importance and I.C.S. lessons qualify on both counts."

New I.C.S. Courses

I.C.S. offers you two new courses in radio and television servicing—one for beginners, the other for the more experienced. Also courses in Industrial Electronics, Television Technician, Practical Radio-Television Engineering.

All are sound, practical, extremely thorough. You learn by doing—the world-famous I.C.S. way. Completely modern. Success proved. Endorsed by employers. Low in cost. And no interference with business and social life.

Send for 2 FREE Books

Mark and mail the coupon. It brings you by return mail the 36-page gold-mine of tips on "How to Succeed." Also the 1954 catalog outlining the opportunities in the field you check—whether it's Radio-Television or one of the other 276 I.C.S. Courses. Absolutely no obligation!

CHECK THESE SEVEN FAMOUS I. C. S. COURSES—ONE FOR YOU!

- PRACTICAL RADIO-TELEVISION ENGINEERING**—Foundation course for radio-television career. Basic principles plus advanced training. Radio, Sound, TV.
- TELEVISION TECHNICIAN**—To qualify you for high level technical positions in television. Camera, studio, transmitter techniques. Manufacture, sale and installation of TV equipment.
- TELEVISION RECEIVER SERVICING**—Installation, servicing, conversion. Dealership. For the man who knows about radio and wants TV training.
- RADIO & TELEVISION SERVICING**—Designed to start you repairing, installing and servicing radio and television receivers soon after starting the course.
- RADIO & TELEVISION SERVICING WITH TRAINING EQUIPMENT**—Same as above but with addition of high-grade radio servicing equipment and tools.
- RADIO OPERATING COURSE**—Special course to help you pass the Government examination for operator's licenses. Code, TV, FM, Radio regulations.
- INDUSTRIAL ELECTRONICS**—Broad, solid background course devoted to the electron tube and to its many applications.

For Real Job Security—Get I.C.S. Training!

I.C.S., Scranton 9, Penna.

INTERNATIONAL CORRESPONDENCE SCHOOLS




2881-L, SCRANTON 9, PENNA.

Without cost or obligation, send me "HOW TO SUCCEED" and the booklet about the course BEFORE which I have marked X:

- | | | | | |
|---|--|---|---|--|
| <p>ART</p> <ul style="list-style-type: none"> <input type="checkbox"/> Commercial Art <input type="checkbox"/> Magazine Illustrating <input type="checkbox"/> Fashion Illustrating <input type="checkbox"/> Cartooning <input type="checkbox"/> Sketching and Painting <input type="checkbox"/> Show Card and Sign Lettering <p>AUTOMOTIVE</p> <ul style="list-style-type: none"> <input type="checkbox"/> Automobile Mechanic <input type="checkbox"/> Auto Elec. Technician <input type="checkbox"/> Auto Body Rebuilding and Refinishing <input type="checkbox"/> Diesel—Gas Engines <p>AVIATION</p> <ul style="list-style-type: none"> <input type="checkbox"/> Aeronautical Engineering Jr. <input type="checkbox"/> Aircraft Engine Mechanic <input type="checkbox"/> Airplane Drafting <p>BUILDING</p> <ul style="list-style-type: none"> <input type="checkbox"/> Architecture <input type="checkbox"/> Arch. Drafting <input type="checkbox"/> Building Contractor <input type="checkbox"/> Estimating <input type="checkbox"/> Carpenter and Mill Work <input type="checkbox"/> Carpenter Foreman <input type="checkbox"/> Reading Blueprints <input type="checkbox"/> House Planning <input type="checkbox"/> Plumbing | <ul style="list-style-type: none"> <input type="checkbox"/> Heating <input type="checkbox"/> Painting Contractor <input type="checkbox"/> Air Conditioning <input type="checkbox"/> Electrician <p>BUSINESS</p> <ul style="list-style-type: none"> <input type="checkbox"/> Business Administration <input type="checkbox"/> Certified Public Accountant <input type="checkbox"/> Bookkeeping and Accounting <input type="checkbox"/> Office Management <input type="checkbox"/> Stenography and Typing <input type="checkbox"/> Secretarial <input type="checkbox"/> Federal Tax <input type="checkbox"/> Business Correspondence <input type="checkbox"/> Letter-writing Improvement <input type="checkbox"/> Personnel and Labor Relations <input type="checkbox"/> Advertising <input type="checkbox"/> Retail Business Management <input type="checkbox"/> Sales Management <input type="checkbox"/> Short Story Writing <input type="checkbox"/> Creative Salesmanship <input type="checkbox"/> Traffic Management <p>CHEMISTRY</p> <ul style="list-style-type: none"> <input type="checkbox"/> Chemical Engineering <input type="checkbox"/> Chemistry <input type="checkbox"/> Analytical Chemistry | <ul style="list-style-type: none"> <input type="checkbox"/> Petroleum—Nat'l Gas <input type="checkbox"/> Pulp and Paper Making <input type="checkbox"/> Plastics <p>CIVIL, STRUCTURAL ENGINEERING</p> <ul style="list-style-type: none"> <input type="checkbox"/> Civil Engineering <input type="checkbox"/> Structural Engineering <input type="checkbox"/> Surveying and Mapping <input type="checkbox"/> Structural Drafting <input type="checkbox"/> Mechanical Engineering <input type="checkbox"/> Reading Blueprints <input type="checkbox"/> Construction Engineering <input type="checkbox"/> Sanitary Engineering <p>DRAFTING</p> <ul style="list-style-type: none"> <input type="checkbox"/> Aircraft Drafting <input type="checkbox"/> Architectural Drafting <input type="checkbox"/> Electrical Drafting <input type="checkbox"/> Highway Engineering <input type="checkbox"/> Structural Drafting <input type="checkbox"/> Sheet Metal Drafting <input type="checkbox"/> Ship Drafting <input type="checkbox"/> Mine Surveying and Drafting <p>ELECTRICAL</p> <ul style="list-style-type: none"> <input type="checkbox"/> Electrical Engineering <input type="checkbox"/> Electrician <input type="checkbox"/> Electrical Maintenance | <ul style="list-style-type: none"> <input type="checkbox"/> Electrical Drafting <input type="checkbox"/> Electric Power and Light <input type="checkbox"/> Lineman <p>HIGH SCHOOL</p> <ul style="list-style-type: none"> <input type="checkbox"/> High School Subjects <input type="checkbox"/> Mathematics <input type="checkbox"/> Commercial <input type="checkbox"/> Good English <p>MECHANICAL AND SHOP</p> <ul style="list-style-type: none"> <input type="checkbox"/> Mechanical Engineering <input type="checkbox"/> Industrial Engineering <input type="checkbox"/> Industrial Supervision <input type="checkbox"/> Foremanship <input type="checkbox"/> Mechanical Drafting <input type="checkbox"/> Machine Design-Drafting <input type="checkbox"/> Machine Shop Practice <input type="checkbox"/> Tool Design <input type="checkbox"/> Industrial Instrumentation <input type="checkbox"/> Machine Shop Inspection <input type="checkbox"/> Reading Blueprints <input type="checkbox"/> Toolmaking <input type="checkbox"/> Gas—Electric Welding <input type="checkbox"/> Heat Treatment—Metallurgy <input type="checkbox"/> Sheet Metal Work <input type="checkbox"/> Sheet Metal Pattern Drafting <input type="checkbox"/> Refrigeration | <p>POWER</p> <ul style="list-style-type: none"> <input type="checkbox"/> Combustion Engineering <input type="checkbox"/> Diesel—Electric <input type="checkbox"/> Electric Light and Power <input type="checkbox"/> Stationary Steam Engineering <input type="checkbox"/> Stationary Fireman <p>RADIO, TELEVISION COMMUNICATIONS</p> <ul style="list-style-type: none"> <input type="checkbox"/> Practical Radio—TV Engineering <input type="checkbox"/> Radio Operating <input type="checkbox"/> Radio and TV Servicing <input type="checkbox"/> Television—Technician <input type="checkbox"/> Electronics <input type="checkbox"/> Telephone Work <p>RAILROAD</p> <ul style="list-style-type: none"> <input type="checkbox"/> Locomotive Engineer <input type="checkbox"/> Diesel Locomotive <input type="checkbox"/> Air Brakes <input type="checkbox"/> Cat Inspector <input type="checkbox"/> Railroad Administration <input type="checkbox"/> Telephone Work <p>TEXTILE</p> <ul style="list-style-type: none"> <input type="checkbox"/> Textile Engineering <input type="checkbox"/> Cotton, Rayon, Woolen Mfg. <input type="checkbox"/> Carding and Spinning <input type="checkbox"/> Warming and Weaving <input type="checkbox"/> Loom Fixing <input type="checkbox"/> Throwing <input type="checkbox"/> Finishing and Dyeing <input type="checkbox"/> Textile Designing |
|---|--|---|---|--|

Name _____ Age _____ Home Address _____
 City _____ Zone _____ State _____ Working Hours _____ A.M. to P.M. _____
 Occupation _____ Canadian residents send coupon to International Correspondence Schools Canadian, Ltd., Montreal, Canada. . . . Special tuition rates to members of the U. S. Armed Forces.

take a look
INSIDE

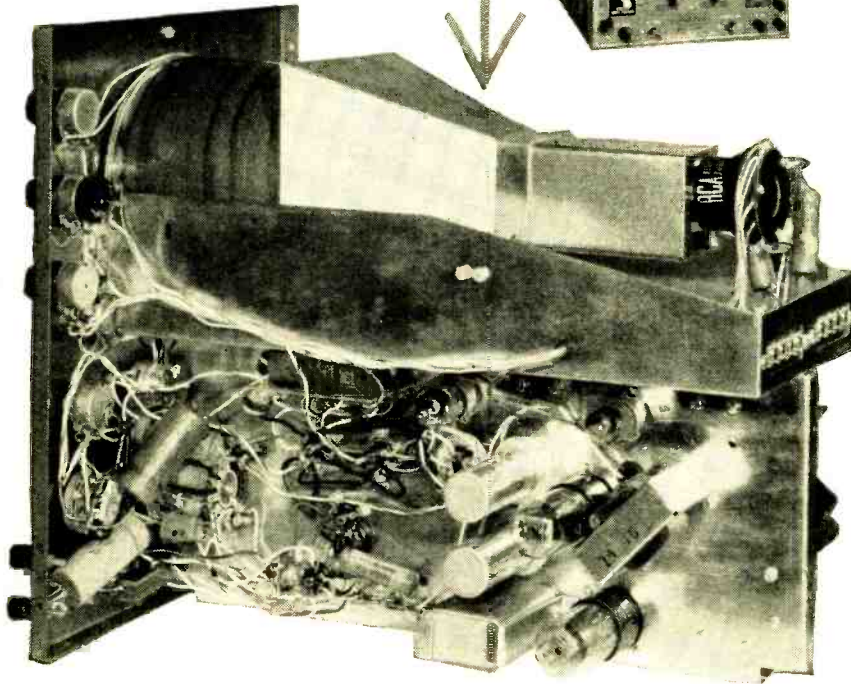

Any careful buyer of test equipment would want to examine inside construction before he buys. And, yet, this is rarely convenient or practical.

That's why we're showing the picture above. It tells its own story of what's on the inside of a Jackson CRO-2 Oscilloscope. We'll let the picture speak for itself—with only this one comment—It's typical of the construction of all Jackson equipment.

This kind of careful layout, and neat, point-to-point wiring is an important part of Jackson "Service-Engineering." For Jackson instruments are built to perform their service operations year after year, under the most trying of service conditions.

Next time you're in the market for test equipment, look at Jackson—outside or inside. You'll find an instrument you will want to own.

"Service Engineered"
Test Equipment



16-18 S. Patterson Blvd., Dayton 2, Ohio, In Canada: The Canadian Marconi Co.


trophy as an annual award to the man making the year's outstanding contribution to the electronics industry.

Recognizing the crying need for top engineering talent in electronics today, Mr. Gernsback revised his original intention and decided instead to create a living trophy, dedicated to furthering the education of engineering students who have demonstrated potentialities of scientific leadership in the field of electronics.

The first award of this scholarship—for the academic year 1954-55—has been made to Lawrence Wechsler, of 110-45 71st Road, Forest Hills, N.Y. Selection of students will be made by a committee appointed by the University.

U.H.F. TRANSISTOR recently developed by Bell Labs operates at 440 mc, higher in frequency than any transistor yet known. The unit, called an "intrinsic-barrier" transistor, has a power gain of approximately 1,000 and operates effectively as a u.h.f. oscillator.

An intrinsically pure layer is added

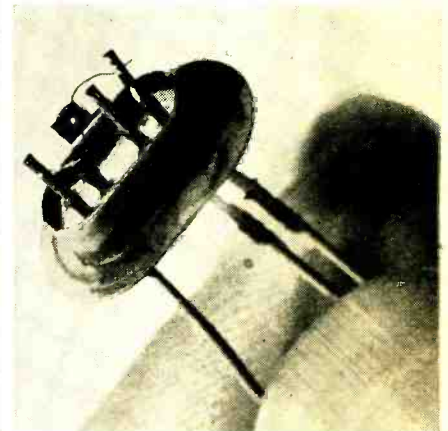

to a basic p-n-p wafer, which acts as a "shock absorber" for high-voltage electrical charges. This chemically pure part of the germanium crystal remains neutral, while the three adjoining sections receive plus or minus charges.

The "intrinsic" region in the middle of the transistor permits the faster movement of positive charges, isolates the input and output areas, and reduces the stored energy to make functioning at the high frequencies possible.

FCC JURISDICTION over community TV was requested by the Fairmont Broadcasting Co., permit holder of station WJPB-TV, channel 35, Fairmont, W. Va. The request concerned specifically community TV distribution systems operating for a profit.


The company charged that many community systems are in direct competition to TV stations, inserting commercial advertisements in network programs picked up off the air, with or without the consent of stations. In other areas, systems are preparing to telecast live, local, sponsored programs over their closed circuits. These, it is claimed, will "constitute a serious economic threat to allocated and established TV stations." END

**DANGER!
CURVES**

Don't let any Antenna Manufacturer
pitch curves to you!

new WINEGARD

INTERCEPTOR

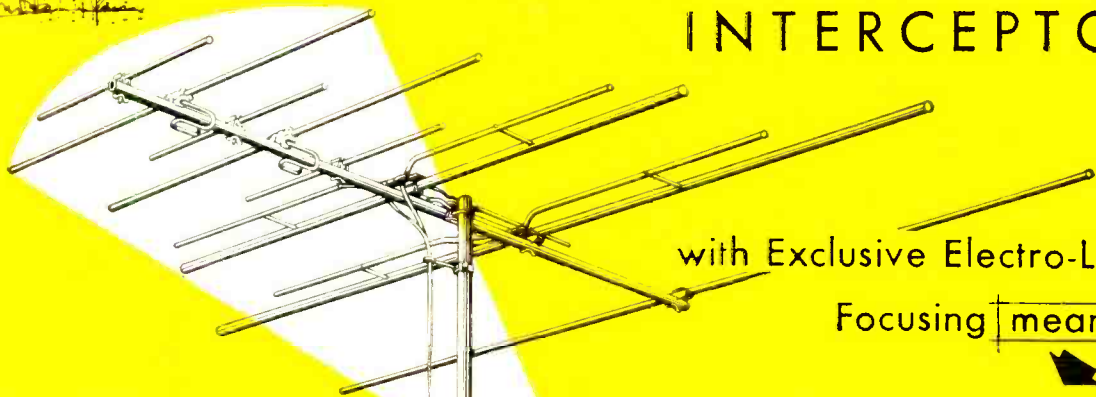

with Exclusive Electro-Lens*
Focusing means...

Don't be misled by any manufacturer's "homemade" charts on antenna performance. We can show you how to plot curves that will "prove" that a busted steel guitar on an 8-ft. flagpole outperforms any antenna you can name—even our own superb *Winegard INTERCEPTOR*.


No—all that counts is, PERFORMANCE IN ACTUAL USE. Therefore, DO THIS: Use a *single* INTERCEPTOR on your next installation where you'd ordinarily stack two bays. See if *one* INTERCEPTOR doesn't give better results than any stacked installation you have made nearby. Once in a blue moon, a second bay is necessary even with our INTERCEPTOR. But rarely. So we say to you, "Why use *two* when ONE will do?"

Order an INTERCEPTOR today. Let it tell its own story in the only place it counts—on one of your own installations. If it doesn't far surpass any other antenna you've ever used, fire it back to us! We'll return your money—and we'll still be friends! So . . . order NOW!


**A FAR BETTER PICTURE
OR YOUR MONEY BACK!**

Antenna No.	Winegard Trade Name	List Price
L-4	INTERCEPTOR	\$24.95 a bay
L-5	PIXIE	\$14.95 a bay

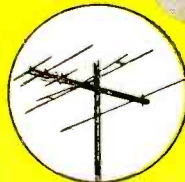Shipped, one L-4 to a carton (stacking bars available)
Shipped, two L-5's to a carton with stacking bars.



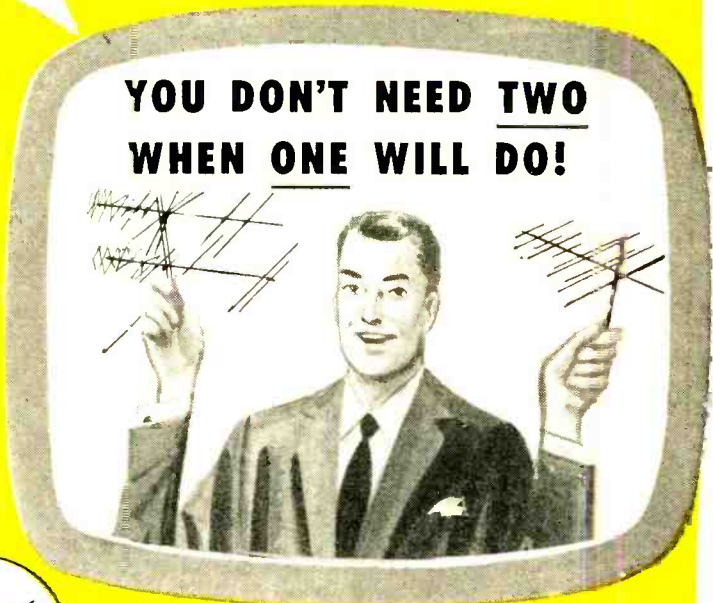WINEGARD PIXIE
A quality all VHF channel antenna for top performance at a low price.



*Patent Pending

THE INTERCEPTOR gives the clearest, sharpest pictures obtainable . . . not just on one or two channels . . . but on all 12 VHF channels.


See your jobber now or write us for complete information.



WINEGARD COMPANY

3000 Scotten Boulevard, Burlington, Iowa

NEW!

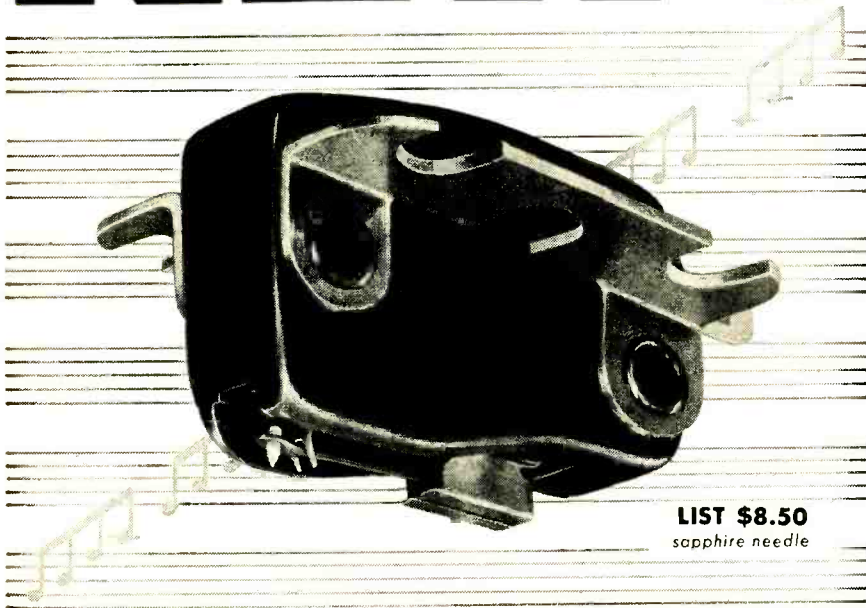

LIST \$8.50
sapphire needle

...another first from

SONOTONE

wide-range
high-compliance
single-needle ceramic cartridge



Here at last is a high fidelity cartridge at a moderate price,
available in either of two needle sizes —
one for 45 and 33 $\frac{1}{3}$ rpm, the other for 78 rpm.

Performance is at the same high level as the world-famous
Sonotone "Turnover."

Send coupon for free bulletin showing the exceptional specifications
of this new cartridge.

ELECTRONIC APPLICATIONS DIVISION

SONOTONE CORPORATION

Elmsford, New York

SONOTONE CORPORATION, DEPT. E
ELMSFORD, N. Y.

Please send me free bulletin describing your new IP Cartridge.

NAME _____

ADDRESS _____ APT. _____

CITY _____ STATE _____



QUESTION BOX

Dear Editor:

Let me say that from my viewpoint you definitely should continue the Question Box.

Being behind the typewriter you have no way of knowing how it is being received on the reading end except by the number of questions that come in. Believe me, this is not a good basis. The questions you receive represent a cross-section of what every technician is thinking. And when you receive one question, your answer will benefit thousands of readers.

Your answer to the question concerning the modification of the Eico 425 scope was utilized by thousands of Eico users. You may have received only one letter but your reply to that one question answered innumerable unwritten ones.

No, you can't stop the Question Box, for it plays a very important part in the electronics field.

STEWART BABBITT, W6QHR
Bellflower, Calif.

ANOTHER IDEA

Dear Editor:

This is in reply to the article "A Superunusual Case" that appeared in the September issue of RADIO-ELECTRONICS. Not agreeing with Mr. Gnessin I suppose a guess of my own is in order, so here is what I think happened.

The picture became normal when the 6SN7 was first removed and would go out when the tube was reinstalled. Then, after all components in this stage were changed with a .05- μ f capacitor inserted by mistake, the set worked with the tube in but not when the tube was removed.

This I would say was the normal condition. I do not believe it would have made any difference whether a .05- or .005- μ f capacitor had been installed. It would have worked just the same.


Before the components were changed, I believe there was either excessive leakage across some terminal connections or coupling by some adjacent wiring or component that was not apparent to the eye. This condition was corrected subconsciously when all the components were replaced.

ALBERT J. PAUKSTITUS
Transmitter engineer
WWDC and WWDC-FM
Silver Spring, Md.

free

1955 VALUE PACKED ALLIED

308-PAGE CATALOG

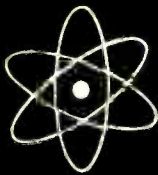


the only COMPLETE
catalog for Everything
in TV, Radio and
Industrial Electronics

SEND FOR IT TODAY


Get ALLIED'S 1955 Catalog—308 pages packed with the world's largest selection of quality electronic equipment at lowest, money-saving prices. Select from the latest in High Fidelity systems and components; custom TV chassis, TV antennas and accessories; AM and FM receiving equipment; P.A. Systems and accessories; recorders and supplies; Amateur receivers, transmitters and station gear; specialized industrial electronic equipment; test instruments; builders' kits; huge listings of parts, tubes, tools, books—the world's *most complete* stocks of quality equipment. ALLIED gives you *every* buying advantage: fastest shipment, expert personal help, lowest prices, assured satisfaction. Get the big 1955 ALLIED Catalog. Keep it handy—save time and money on *everything in* Electronics. Send for your FREE copy today.

World's largest Stocks

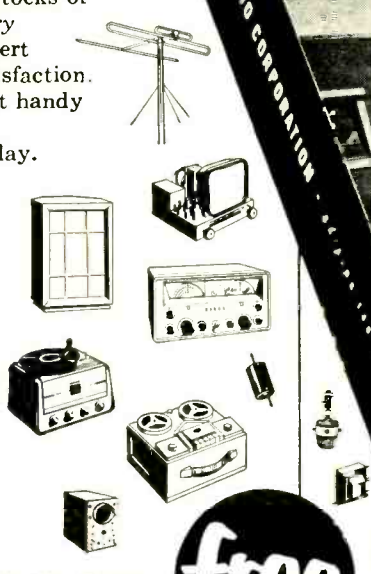- All TV and Radio Parts
- All Electron Tube Types
- Test and Lab Instruments
- High Fidelity Equipment
- Custom TV Chassis
- AM, FM Receiving Equipment
- Recorders and Supplies
- P. A. Systems, Accessories
- Amateur Station Gear
- Builders' Kits & Supplies
- Equipment for Industry



free

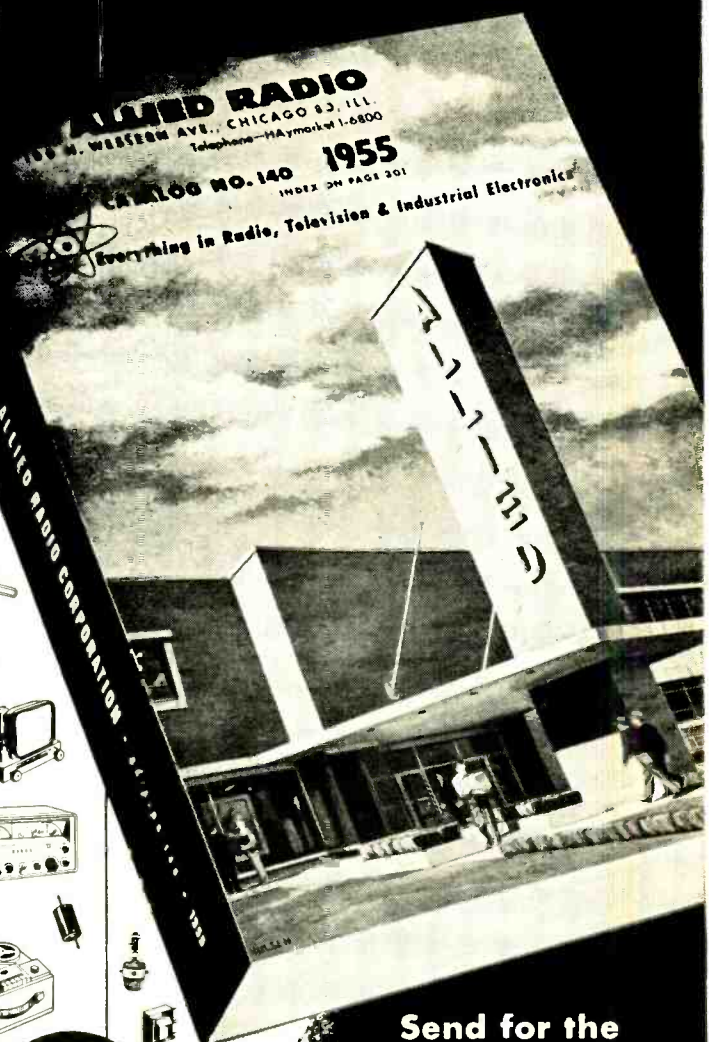

Send for the
leading Electronic
Supply Guide

ALLIED RADIO

World's Largest Electronic Supply House

EASY-PAY TERMS

Use ALLIED'S liberal Easy Payment Plan—only 10% down, 12 months to pay—no carrying charges if you pay in 60 days. Available on Hi-Fi and P. A. units, recorders, TV chassis, test instruments, Amateur gear, etc.

HI-FI SPECIALISTS

To keep up with the latest and best in High Fidelity, look to ALLIED. Count on us for *all* the latest releases and largest stocks of Hi-Fi equipment. We specialize, too, in TV supply—and are foremost in the field of Builders' Kits.

ultra-modern facilities for the FASTEST SERVICE IN ELECTRONIC SUPPLY



ALLIED RADIO CORP., Dept. 2-L-4
100 N. Western Ave., Chicago 80, Illinois

Send FREE 308-Page 1955 ALLIED Catalog


Name.....

Address.....

City.....Zone.....State.....

Simpson

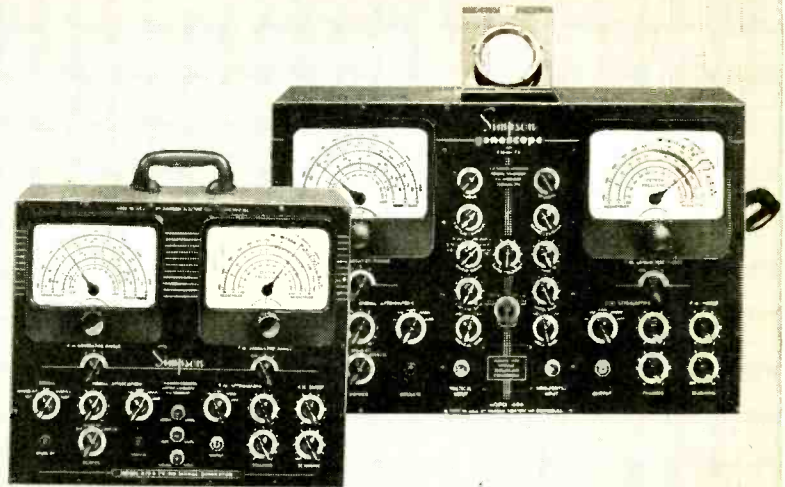**MODEL 480
GENESCOPE***
and
**MODEL 479
TV-FM SIGNAL GENERATOR**



NOW..

ready for color!

**ENDORSED BY THESE
NATIONALLY KNOWN
SERVICE
MANAGERS . . .**



**NEW MODEL 406
CHROMATIC AMPLIFIER***
\$24.95



**NEW
CHROMATIC PROBE***
\$9.95

In just 15 seconds—you can convert your Simpson Model 480 Genescope or Model 479 TV-FM Signal Generator for the alignment of color TV! Two new Simpson accessories make this possible . . . the new **Chromatic Probe** and the new **Model 406 Chromatic Amplifier**. No internal changes or connections are necessary.

In conjunction with either the Simpson Genescope or TV-FM Signal Generator, the new Chromatic Probe can align and test the chroma channel, I and Q channels, and color video amplifier in color TV receivers. What's more, it gives you two new black-and-white applications — direct video amplifier testing and stage-by-stage testing.

The new Simpson Chromatic Probe also has the widest frequency range of any equipment on the market—8kc to 4.5 mc.

The new Simpson Chromatic Amplifier permits testing of low-gain video amplifiers in color television receivers, as well as other tests where a low-gain scope is being used.

With these low-cost accessories, the Simpson test equipment you bought for black-and-white TV will also meet your color requirements. Once again—in spite of rapid technological changes—your investment in Simpson equipment is protected.

Four years ago, the Service Managers of these companies endorsed the Simpson 480 Genescope for black-and-white TV. Now, they endorse it for color—proof that your investment in a 480 is protected.

M. J. SCHINKE
Admiral



A. R. DAMBRAUSKAS
hallicrafters



TIM ALEXANDER
Motorola



FRANK LOASBY
RAYTHEON



ASK YOUR JOBBER OR WRITE . . .

Simpson ELECTRIC COMPANY

WORLD'S LARGEST MANUFACTURER OF ELECTRONIC TEST EQUIPMENT
5200 W. Kinzie St., Chicago 44, Ill. Telephone EStbrook 9-1121
In Canada: Bach-Simpson, Ltd., London, Ontario

* Trademark



*Prepare now for
the great opportunity
field of...*

*You Can Quickly
be doing interesting
profitable work
like this!*

TELEVISION

RADIO-ELECTRONICS

*In spare time
at home!*

A fascinating field! A great future! A good job or independence in a business of your own! TV is growing by leaps and bounds—1227 new communities, 1845 new stations have been given the "go-ahead". Trained men are worth their weight in gold!

MODERN TRAINING BY COYNE RIGHT IN YOUR OWN HOME

Here is modern, up-to-the-minute Home Training in Television and Radio designed to meet the standards that have made the Coyne School famous for many years. You get personal supervision by members of Coyne instruction staff—men who know TELEVISION AND RADIO AND KNOW HOW

B. W. COOKE, President

COYNE SCHOOL

A TECHNICAL TRADE INSTITUTE
CHARTERED NOT FOR PROFIT
Established 1899

500 S. Paulina Dept. 84-HR4 Chicago 12,

TELEVISION ★ RADIO ★ ELECTRICITY ★ REFRIGERATION ★ ELECTRONICS

TO TEACH IT—men who have helped train thousands of men and young men, Service men and Veterans.

LEARN TO EARN IN SPARE TIME

COYNE offers a most practical, down-to-earth Home Television Training. Simple, easy to follow step-by-step instructions, fully illustrated. So practical, you can quickly be earning money in Television and Radio and keep your present job while training.

Let us show you that this is not only the newest, most up-to-the-minute Training in Television-Radio-Electronics—but also it **costs you much less than you'd expect to pay**. Send coupon today for details including Easy Payment Plan.

B. W. COOKE, President
COYNE SCHOOL
500 S. Paulina St., Chicago 12
Dept. 84-HR4

Send details of your offer on training checked below. This does not obligate me and no salesman will call. I am interested in:

- Television-Radio Home Training
- Electricity in Coyne Shops
- Television-Radio in Coyne Shops

Name

Address

City State

YOU CAN ALSO TRAIN FOR


TELEVISION-RADIO OF ELECTRICITY
IN THE GREAT SHOPS
OF COYNE AT CHICAGO



Coyne, of course, also offers practical resident training in the Coyne Training Shops here in Chicago in the fields of TELEVISION-RADIO and ELECTRICITY. If you prefer to get information about our resident courses in either or both of these fields, then check on the coupon accordingly and mail it to us. Our fully illustrated 48 page Guide To Careers in Television-Radio and Electricity and complete details about our resident training will be sent you by return mail. No cost or obligation to you, of course, and no salesman will call on you.

MAIL COUPON FOR INFORMATION

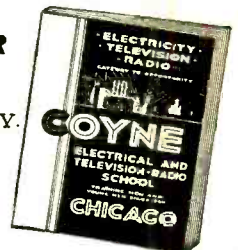Fill in and mail coupon TODAY. Paste it on a postcard if you wish. Complete details will come by return mail. No cost—no obligation and no salesman will call.





GET LONGER . . . TROUBLE-FREE LIFE
AT NO EXTRA COST WITH CBS-HYTRON

CTS-RATED* 6CU6

Why the CTS-Rated* 6CU6? The 6CU6 horizontal amplifier is rated the same as the 6BQ6GT . . . is electrically interchangeable with it. *But . . .* because the 6CU6 is rated for continuous television service, it will *live* under 6BQ6GT maximum ratings.

The 6BQ6GT is a good tube. (Heck, CBS-Hytron originated it.) But, it was designed for 10- and 12-inch TV sets. Today it carries the load in 21-inch sets. Furthermore, it must combat the accumulated dissipation caused by: 1. Line-voltage variations. 2. Faulty receiver adjustments. 3. Shifting values of components due to age

and overload. Result: The 6BQ6GT is often operated above maximum ratings.


Obviously, a brand-new design . . . not just an improved 6BQ6GT . . . was needed. The husky CBS-Hytron 6CU6 (See Mechanical Features) is the answer: a premium-performance tube *at no extra cost*. CTS-Rated, it offers generous safety margins for plate dissipation . . . high-voltage insulation . . . and high-line protection. Note also the bar graph showing much larger plate and envelope areas of CBS-Hytron 6CU6.

In the 6CU6 . . . another CBS-Hytron first . . . high voltage and heat meet their match. You forget run-away plate current, high-voltage arc-overs, and shrinking TV pictures. You gain by longer life . . . minimized service . . . happier customers. Try the CBS-Hytron 6CU6 today.

FLASH!
NEW CTS-RATED 12CU6-25CU6
... with all the 6CU6's
features ... at no extra cost
... now available for
series-string operation.
Combined data sheet for
6CU6, 12CU6, and 25CU6
free on request.

MECHANICAL FEATURES OF 6CU6

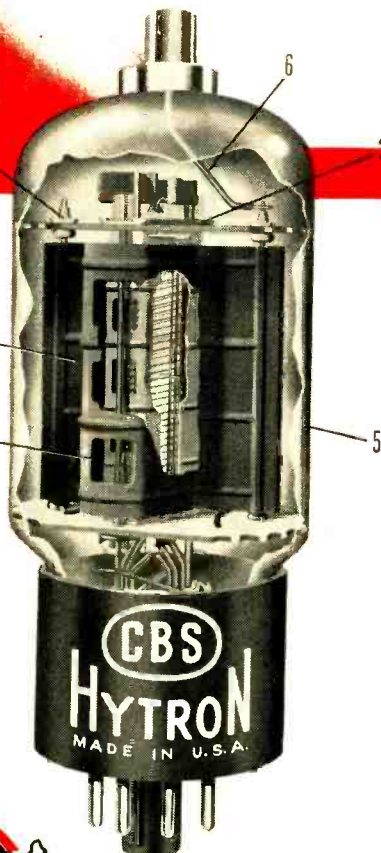1. Heavier-gauge plate with large radiating fins.
2. Vents in beam plates and plate aligned for maximum radiation of heat from grids.
3. Anti-arc rings for uniform distribution of electrostatic field.
4. Anti-arc mica eyelets.
5. T-12 transmitting-type bulb.
6. Plate connection "hard-soldered" and positioned to reduce heat conduction and arcing.



*Rated for Continuous
Television Service

6CU6 OFFERS GREATER DISSIPATION RESERVES

6BQ6GT

6CU6

WITH 48.5% MORE BULB AREA

6BQ6GT

6CU6

WITH 31.5% MORE PLATE AREA



Manufacturers of
Receiving Tubes Since 1921

CBS-HYTRON Main Office: Danvers, Massachusetts

A Division of Columbia Broadcasting System, Inc.

A MEMBER OF THE CBS FAMILY: CBS Radio • CBS Television • Columbia Records, Inc.
CBS Laboratories • CBS-Columbia • CBS International • and CBS-Hytron

RECEIVING • TRANSMITTING • SPECIAL-PURPOSE • TV PICTURE TUBES • CRYSTAL DIODES AND TRANSISTORS
20 RADIO-ELECTRONICS



L. C. Lane, B.S., M.A.
President, Radio-Television
Training Association
Executive Director, Pierce
School of Radio & Television

VETERANS!

NON-VETERANS!

MY FREE LESSON

MAY CHANGE YOUR ENTIRE LIFE

THREE COURSES TO TRAIN YOU FOR THE JOB YOU WANT

RADIO-FM-TELEVISION TECHNICIAN COURSE

— No previous experience necessary. You learn by practicing with the professional equipment I send you. Many of my graduates now have good paying technician jobs with such firms as RCA, NBC-TV, Dumont TV and numerous other TV Studios and plants.

FM-TV TECHNICIAN COURSE

— Previous training or experience in radio required. You can save months of time if you have previous Armed Forces or civilian radio experience! Train at home with kits of parts, plus equipment to build BIG SCREEN TV RECEIVER. ALL FURNISHED AT NO EXTRA COST!

EXTRA TRAINING IN NEW YORK CITY AT NO ADDITIONAL COST

— After you finish your home study training in either of these two courses, you get two weeks, 50 hours, of intensive Laboratory work on modern electronic equipment at our associate school in New York City, Pierce School of Radio & Television. THIS EXTRA TRAINING IS YOURS AT NO EXTRA COST WHATSOEVER. My courses are complete without this extra training, but it gives you added opportunity for review and practice.

TV CAMERAMAN AND STUDIO TECHNICIAN COURSE

— Advanced training for men with radio or TV training or experience. I train you at home for an exciting high pay job as the man behind the TV camera.

VETERANS

My school fully approved to train Veterans under New Korean G. I. Bill. Available only to Veterans discharged after August 20, 1951. If eligible, CHECK COUPON!

EARN WHILE YOU LEARN

— Almost from the very start you can earn extra money while learning by repairing Radio-TV sets for friends and neighbors. Many of my students earn up to \$25 a week . . . pay for their entire training from spare time earnings . . . start their own profitable service business.

FREE FCC COACHING COURSE

— Important for BETTER PAY JOBS requiring FCC License. You get this training AT NO EXTRA COST. Top TV jobs go to FCC-licensed technicians.

ENOUGH EQUIPMENT TO SET UP YOUR OWN HOME LABORATORY

With the equipment I send you as part of your course you BUILD and KEEP a professional GIANT SCREEN TV RECEIVER complete with big picture tube (takes any size up to 21-inch) . . . also a Super-Het Radio Receiver, AF-RF Signal Generator, Combination Voltmeter-Ammeter-Ohmmeter, C-W Telephone Transmitter, Public Address System, AC-DC Power Supply. Everything supplied, including all tubes. My practical, easy-to-understand lessons have brought success to hundreds of men. You, too, can train for a better-paying job or set up a business of your own if you act NOW!



Radio Television Training Association

52 EAST 19th STREET • NEW YORK 3, N. Y.

Licensed by the State of New York • Approved for Veteran Training

NOVEMBER, 1954

Just by clipping the coupon below and sending it to me today, you can open up a whole new future for yourself in America's fastest-growing field — Radio-Television-Electronics.

The very day I receive your coupon I will send to you Free a Sample Lesson and my New 36-page Book showing you "How to Make Money in Television, Radio, Electronics" by STUDYING AT HOME IN YOUR SPARE TIME.

At absolutely no cost or obligation you can see for yourself how you can begin now to prepare yourself for a better-paying career as a TV repairman, studio technician, cameraman or any one of the many promising jobs in the field that is bringing success and security to hundreds of men — many of them with no more than grammar school education and no experience whatsoever.

If you think I was exaggerating when I said, "My Free Lesson May Change Your Entire Life," just see what some of my graduates say about my training —

"RTTA training gave me the skill and know-how to do the work I love best and enjoy better things in life."
Harold Gimlen
Flint, Michigan

"If it had not been for you, your instructors and the school, I never would have had this opportunity."
J. A. Irwin
Radio-TV Repairman
Coburg, Ont., Canada

"I know I would not have achieved this progress if it weren't for the help and guidance from RTTA."
Edward Brault
Chief Radar Operator
National Guard
Central Falls, R. I.

These letters and many more like them are in my files. The TV Boom that brought good opportunities to these RTTA graduates is still on with no sign of letting up. Don't let opportunity pass you by. Write today for your Sample Lesson, new 36-page book, TV Job Opportunities List, and 48-state list of future TV stations — ALL FREE!

MAIL THIS COUPON TODAY!

Public Address System Dept. R-11

Mr. Leonard C. Lane, President
RADIO-TELEVISION TRAINING ASSOCIATION
52 East 19th Street, New York 3, N. Y.

Dear Mr. Lane: Mail me your NEW FREE BOOK, FREE SAMPLE LESSON, and FREE aids that will show me how I can make BIG MONEY IN TELEVISION. I understand I am under no obligation and no salesman will call.

(PLEASE PRINT PLAINLY)

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

I AM INTERESTED IN:

Radio-FM-TV Technician Course
 FM-TV Technician Course
 TV Cameraman & Studio Technician Course

VETERANS!
Check here
for Training under NEW
G.I. Bill.

NO SALESMAN WILL CALL!


NEW

PHILCO

Super Performance

TV

ANTENNAS

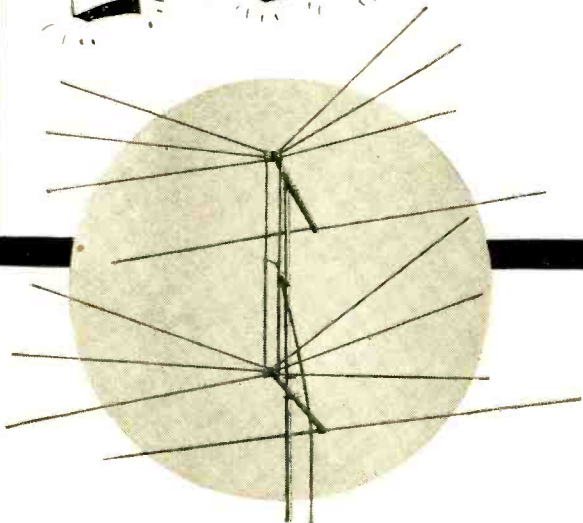

PHILCO TWO-BAY SUPER CONICAL


Strong signal pick-up on all VHF-UHF channels. Ideal for fringe area reception... aluminum construction with dowelled elements: Part No. 45-3096-2. Single bay design: Part No. 45-3096.

BUILD CUSTOMER CONFIDENCE... MORE SALES FOR YOU!

Designed to outperform any equivalent antenna in its class, each Philco Super Performance TV Antenna provides the finest picture possible... long life and ease of installation. Powerful Conical... all-aluminum VHF Yagis, engineered for quick rigging... light weight. Stacked versions provide top-quality fringe area reception. Only six UHF Yagis cover the entire UHF spectrum. Here's powerful reception on all channels... the kind that builds customer confidence... more sales for you!

GET YOUR "PHILCO FREE RIDE"

That's right! Ride any way you like it... or earn all of them! They're yours FREE with PHILCO FREE RIDE TICKETS... and there's no waiting! Collect your selected "ride" as soon as you have the necessary number of tickets. You can enjoy Rollfast Roller Skates; Radio Flyer Coaster Wagon; Rollfast Bicycle; BMC Juvenile Tractor; Airplane Trip for Two; 1/2 Ton Panel Dodge Truck; Plymouth Plaza Sedan. Concentrate your parts and accessories purchases on PHILCO and make double profits... profits through the great ready-made PHILCO market of PHILCO owners and PLUS

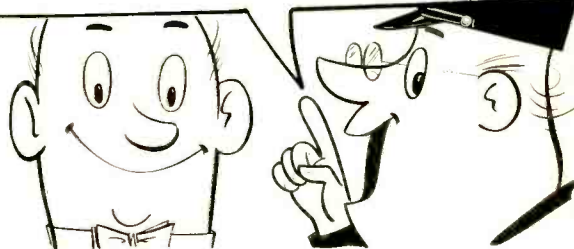

PROFITS with these great FREE RIDES... all at no extra cost to you. Don't wait... register NOW! Get started on your FREE RIDE with PHILCO!


SEE YOUR PHILCO DISTRIBUTOR FOR DETAILS



PHILCO CORPORATION

ACCESSORY DIVISION

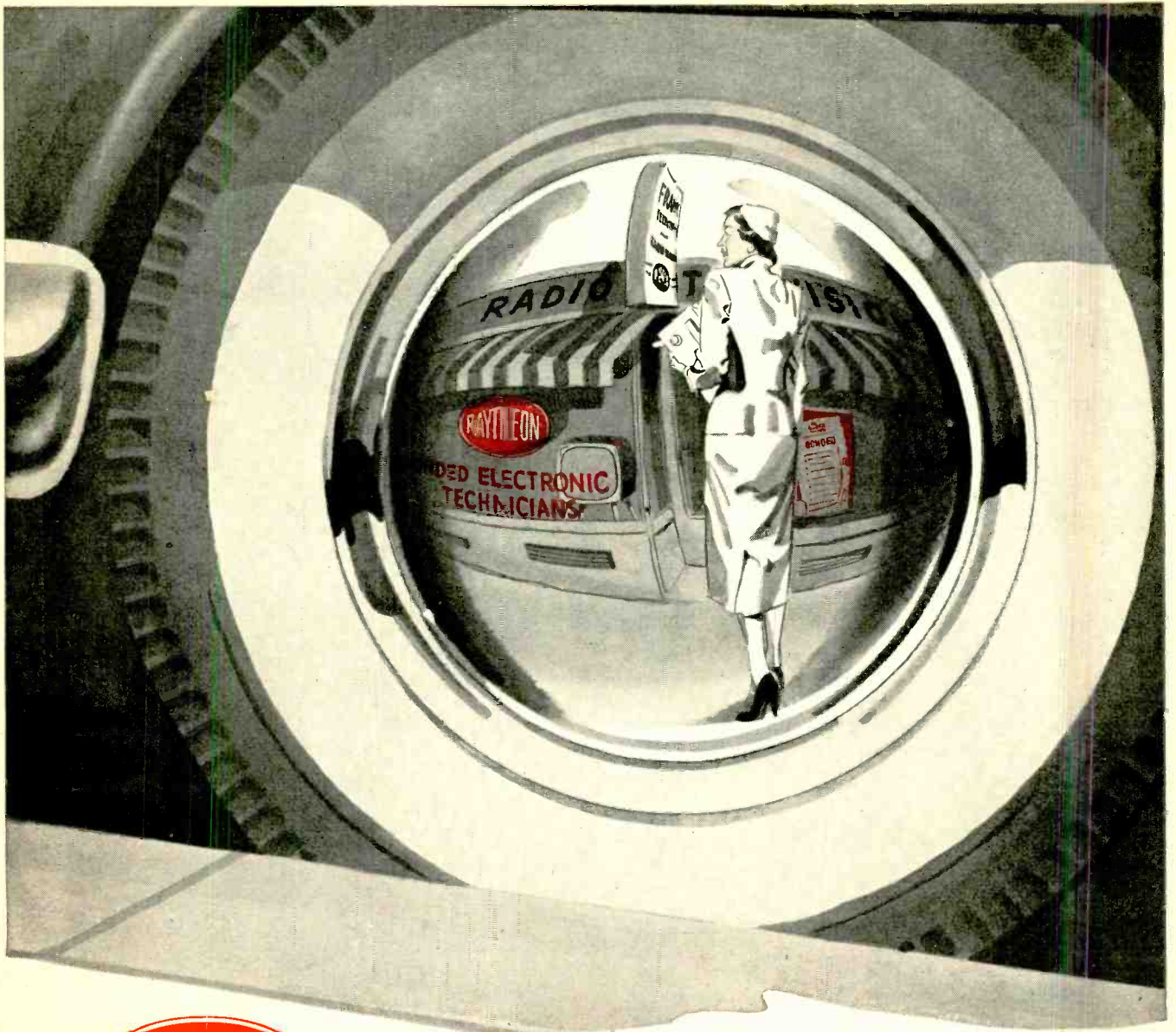"A" AND ALLEGHENY AVE., PHILADELPHIA 34, PA.



The **RAYTHEON** BONDED Electronic Technician PROGRAM
 will reflect more business and profits in your shop, too!



Customers have confidence in Raytheon Bonded Dealers for two important reasons: (1) they value the security of the Raytheon Bond and (2) they appreciate the fairness and good sense of the Raytheon "Code of Ethics" to which these dealers adhere. And this confidence is reflected in more volume and profit for the Raytheon Bonded Dealer.

If you can qualify for this exclusive business builder you'll find it will inspire greater customer confidence in your shop and result in more profitable business for you. Ask your Raytheon Tube Distributor about it, today.



RAYTHEON MANUFACTURING COMPANY

Receiving and Cathode Ray Tube Operations
 Newton, Mass., Chicago, Ill., Atlanta, Ga., Los Angeles, Calif.


Excellence in Electronics

RAYTHEON MAKES ALL THESE:

RECEIVING AND PICTURE TUBES • RELIABLE SUBMINIATURE AND MINIATURE TUBES • SEMICONDUCTOR DIODES AND TRANSISTORS • NUCLEONIC TUBES • HIGHWAVE TUBES

The BUY of a Lifetime!

1 **craftsmen**
C800A
DELUXE AM-FM TUNER

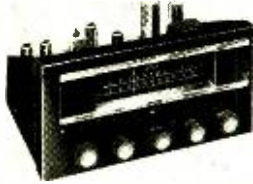

Latest production with higher sensitivity and improved tone balance. Incorporates Craftsmen's famous AFC, Phono Pre-Amp and Record Compensator. Net \$159.50

2 **craftsmen**
C500A
ULTRA FIDELITY AMPLIFIER



Featuring the famous Williamson Circuit with superior KT66 Output Tubes. Full 15 watts 20 to 20,000 cps within 1/10 of 1 db. Distortion so low it can hardly be measured. Net \$99.50

3 **GARRARD**
"TRIUMPH" RC80 AUTOMATIC
3-SPEED RECORD CHANGER



The standard of excellence the world over. Plays all records, 33 1/3, 45, 78 rpm records in 7", 10" and 12" sizes. Quiet, smooth-running 4-pole motor, weighted turntable. Automatic shut-off after last record. Muting switch cuts out sound during change cycle. Net \$49.50
SPECIAL '45' SPINDLE for Garrard "Triumph" Changer Net \$3.50

4 **Electro-Voice**
12 TRXB TRIAXIAL SPEAKER



Advance design full range easy to mount 12" TRIAXIAL 3-WAY SPEAKER SYSTEM. Electro-Voice laboratory research has combined Woofer, Middler and Tweeter into a near-perfect instrument for sound reproduction. Clearly, and realistically reproduces all tones and overtones with unexcelled balance. Net \$59.70



5 **GENERAL ELECTRIC**
RPX-050 TRIPLE-PLAY
VARIABLE RELUCTANCE
MAGNETIC PICKUP



For finest phono reproduction of all types of records. Considered by many engineers and music lovers the finest pickup at any price! Furnished mounted in changer ready for use. Supplied with genuine General Electric Double Sapphire Needle. Net \$8.20


TERMINAL'S *Sensational* "5-STAR" Hi-Fi BUY!

Complete, Matched PHONO-RADIO SYSTEM

ALL BRAND NEW famous name components • ALL current models and production • ALL Fully Guaranteed • Supplied with ALL TUBES • Warranty Cards • Instructions • Indoor Antenna • GE Dual Sapphire Needle • ALL Cables and Plugs • Your '5-STAR' System consisting of ALL ITEMS ILLUSTRATED and DESCRIBED ABOVE... comes ready to plug together and play!

OUR BIG BUY YOUR BIG SAVING!

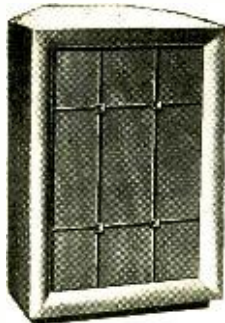This Complete System for
Only \$259. f.o.b. our store
Total Regular Net \$379.90



Electro-Voice
KLIPSCH
MATCHED
COMPANION CABINETS
for '5-STAR' SYSTEM



ELECTRO-VOICE ARISTOCRAT SPEAKER CABINET WITH KLIPSCH LICENSED FOLDED HORN
Companion Speaker Cabinet for the PEERAGE Equipment Console. Corner enclosure designed to match the characteristics of the Electro-Voice 12TRXB Speaker. The patented KLIPSCH principle provides a full octave of added bass without boominess and greater speaker power handling capacity. 29 1/2" high, 19" wide, 16 1/2" deep.
In MAHOGANY Net \$66.00 • In BLONDE Net \$72.00

ELECTRO-VOICE PEERAGE EQUIPMENT CONSOLE
Fashioned by furniture craftsmen. In Beautiful Blonde Korina or Tropical Mahogany Veneer, hand-rubbed finish. Supplied all cut out to house C800A Tuner, C500A Amplifier and RC-80 Changer. Tilting tuner compartment opens to easy-to-operate angle. Record changer mounts in drawer directly below tuner panel on roller slides for smooth operation. 29 1/4" high, 20 1/2" wide, 18 3/4" deep.
In MAHOGANY Net \$96.00 • In BLONDE Net \$102.00

All Items Available Separately at Individual Net Prices

"5-STAR" Hi-Fi SYSTEM

Complete with Both PEERAGE and ARISTOCRAT Matched Cabinets

(As Shown Here)

Available from Terminal

ATTRACTIVELY PRICED

When Ordered at One Time

Price on Request — Write Today!

MAIL ORDERS FILLED WITHIN 48 HOURS

If you cannot come to our store for this sensational value, order by mail. Send full remittance or \$25.00 on account. Balance C. O. D. Every item FULLY GUARANTEED.

DON'T DELAY — ORDER TODAY!

WE RESERVE THE RIGHT TO LIMIT QUANTITIES




Terminal Radio CORP.

83 CORTLANDT STREET, NEW YORK 7, N. Y. • WOrth 4-3311

© COPYRIGHT 1954 TERMINAL RADIO CORP.

RADIO-ELECTRONICS

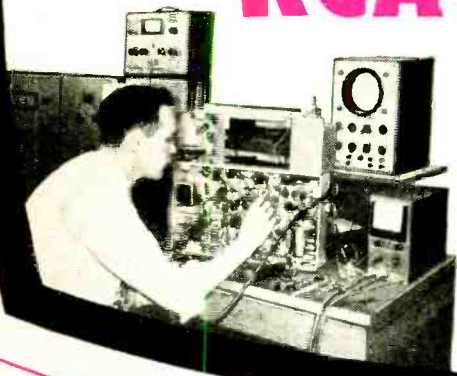Home Study Courses in TELEVISION SERVICING offered by RCA INSTITUTES



Study Television Servicing—from the very source of the latest up-to-the-minute TV and Color TV developments. Train under the direction of men who are experts in this field. Take advantage of this opportunity to place yourself on the road to success in television. RCA Institutes, Inc. (A Service of Radio Corporation of America), thoroughly trains you in the "why" as well as the "how" of servicing television receivers.

FIRST HOME STUDY COURSE IN COLOR TV SERVICING

Now you can train yourself to take advantage of the big future in Color TV. RCA Institutes Home Study Course covers all phases of Color TV Servicing. It is a practical down-to-earth course in basic color theory as well as how-to-do-it servicing techniques.

This color television course was planned and developed through the combined efforts of instructors of RCA Institutes, engineers of RCA Laboratories, and training specialists of RCA Service Company. You get the benefit of years of RCA research and development in color television.


Because of its highly specialized nature, this course is offered only to those already experienced in radio-television servicing. Color TV Servicing will open the door to the big opportunity you've always hoped for. Find out how easy it is to cash in on Color TV. *Mail coupon today.*

SEND FOR FREE BOOKLET

Mail coupon in envelope or paste on postal card. Check course you are interested in. We will send you a booklet that gives you complete information. *No salesman will call.*



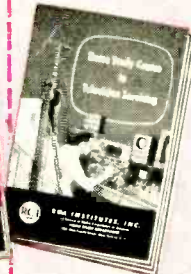RCA INSTITUTES, INC.
A SERVICE OF RADIO CORPORATION OF AMERICA
350 WEST FOURTH STREET, NEW YORK 14, N. Y.



HOME STUDY COURSE IN BLACK-AND-WHITE TV SERVICING

Thousands of men in the radio-electronics industry have successfully trained themselves as qualified specialists for a good job or a business of their own—servicing television receivers. You can do this too.

This RCA Institutes TV Servicing course gives you up-to-the-minute training and information on the very latest developments in black-and-white television.

As you study at home, in your spare time, you progress rapidly. Hundreds of pictures and diagrams, easy-to-understand lessons help you to quickly become a qualified TV serviceman.

There are ample opportunities in TV, for radio servicemen who have expert training. Mail coupon today. Start on the road to success in TV Servicing.

MAIL COUPON NOW


RCA INSTITUTES, INC.
Home Study Dept. RE-1154
350 West Fourth Street, New York 14, N. Y.
Without obligation on my part, please send me copy of booklet on:

- Home Study Course in TELEVISION SERVICING.
 Home Study Course in COLOR TV SERVICING.

Name _____ (please print)

Address _____

City _____ Zone _____ State _____

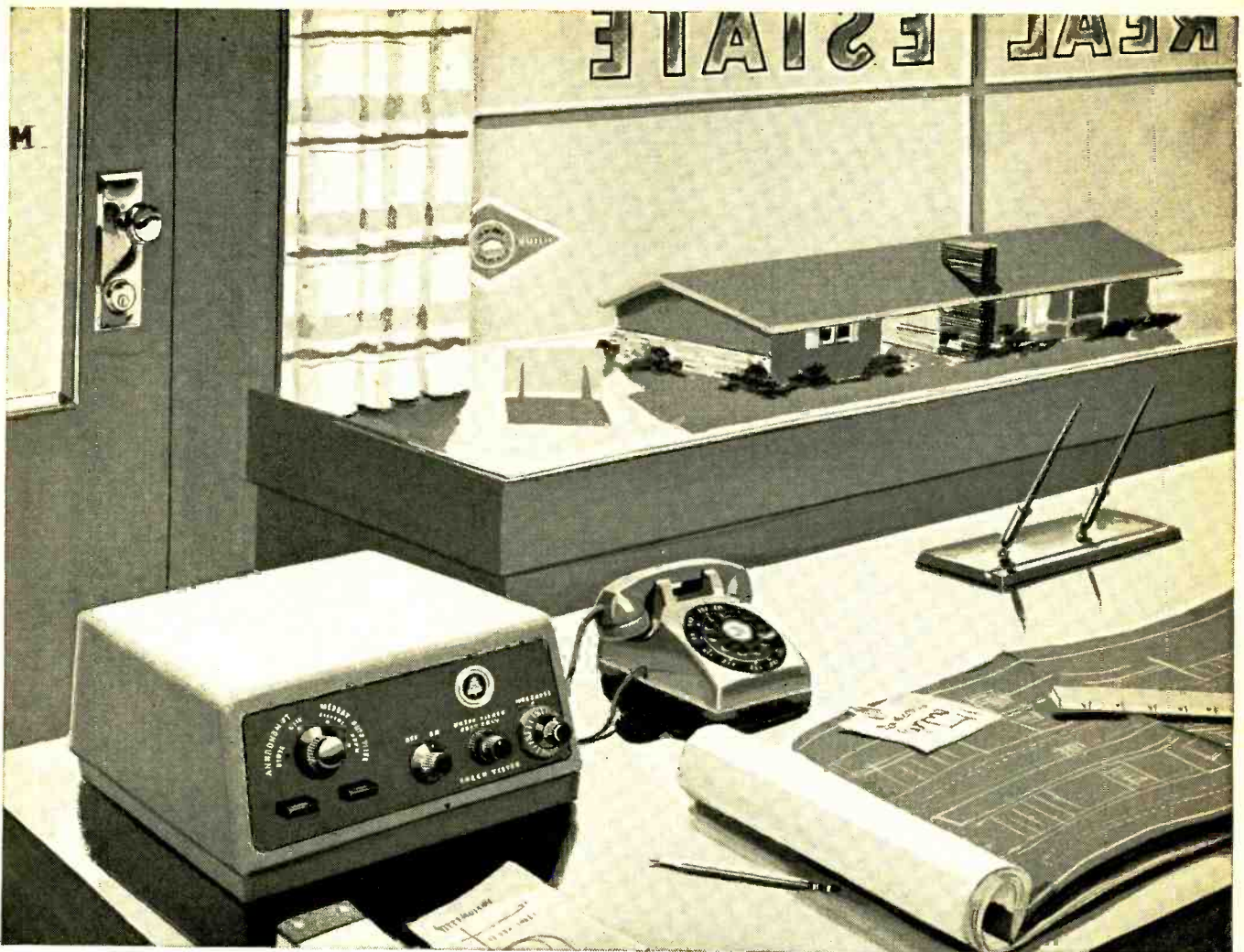

Bell's new Telephone Answering Set. In use, the machine tells the caller when to start talking, and when his time—thirty seconds—is up.

He's out... but he's answering his telephone!

This newly designed Bell Telephone Answering Set makes it possible for you to go out—but leave your voice behind.

Before you leave you twist a knob, dictate a message into your telephone, then switch the machine to "Automatic Answer." When somebody calls, the machine starts up and the caller hears your voice telling who you are, requesting his name and telephone number, repeating whatever you have said. The reply is recorded too. On your return you play back all the calls that have come in, as often as you please.

The new machine features "talking rubber," a Laboratories-developed recording medium made of rubber-like plastic and iron oxide which can be used over and over again millions of times. It is another example of how Bell Laboratories research works to help your local Bell Telephone Company serve you.

**Bell Telephone
Laboratories**



*Improving telephone service for America provides
careers for men in scientific and technical fields*

BREAK THRU THE FRINGE BARRIERS IN ALL DIRECTIONS

200 MILES VHF

30 MILES UHF
COLOR and BLACK-WHITE
ALL CHANNELS 2-83
WITHOUT ANY
ROTORMOTOR

The *Riviera*

NEW PATENTED RADAR ANTENNA

53 CLAIMS GRANTED IN 5 U. S. PATENTS — #2,585,670 — #2,609,503 — #2,625,655 — #2,644,091 — #2,661,423

OPENS NEW HORIZONS TO TV VIEWERS

These are the reasons why the "Riviera" is by far the most powerful VHF antenna on the market today!

1. Utilizes 16 elements 60" long, 1/2" diameter.
2. Utilizes a specially designed, extra low loss four conductor air-dielectric POLYMICALENE transmission line which has up to 50% less loss when wet than the finest conventional transmission lines.
3. The "Riviera" encompasses an electro-magnetic capture volume of well over 650 cubic feet, many times more than conventional antennas.
4. The antenna works on the revolutionary principle that the approaching wave front is elliptically rather than horizontally polarized.
5. The new specially designed 9 position electronic orientation switch, aside from changing directivity, maintains a consistently better impedance match over the entire UHF-VHF spectrum.
6. The above features combine to give the "Riviera" antenna greater usable gain at the TV set antenna terminals than the best of any competitive antennas using rotor motors.

This new wonder antenna, called the "Riviera", is already making history. Beyond any question of a doubt, and on an unconditional money back guarantee, it will positively outperform in the field under actual installation conditions, any and all competitive antennas on the VHF channels, with or without rotor motors.

POLAR PATTERNS



only
\$49⁵⁰
LIST PRICE

Price includes:
Complete Stacked
Array • Stacking
Bars • 9 Position
Switch • Switch-
to-set Coupler •
2 Stand-offs, 7 1/2" •
Complete instructions

The polar directivity response patterns show the major lobes of the "Riviera" antenna on VHF. It shows the fullness of coverage in all directions of this remarkable, patented antenna as it is turned through each of the nine switch positions. Each degree of shading constitutes a different switch position. This excellent directivity response, which can be switched at will, plus the extremely high gains, clearly indicate why the Riviera is such a superior performer.

ALL CHANNEL ANTENNA CORP.

47-39 49th STREET, WOODSIDE 77, N. Y.

EXETER 2-1336

IN UHF-VHF DISTRICTS . . . USE

The **NEW Super 60**

100 MILES VHF • 60 MILES UHF

**FREE 1955
EICO CATALOG!**
Tells you how to **SAVE 50%** on
your test equipment costs!

EICO
THE LARGEST MANUFACTURER OF ITS KIND IN THE WORLD


**KITS
INSTRUMENTS**

THE INDUSTRY'S MOST COMPLETE LINE OF KITS & INSTRUMENTS
1/3 MILLION EICO INSTRUMENTS IN USE THE WORLD OVER —
SAVE 50% — BUILD 'EM IN ONE EVENING... THEY LAST A LIFETIME.


The Exclusive **EICO** Make-Good
GUARANTEE

Each EICO Kit and Instrument is **thoroughly** guaranteed by EICO and your
jobber to contain only selected quality components. EICO guarantees to
replace any component which might become defective in normal use at
no charge to the customer within 90 days of purchase.
EICO guarantees all Kits assembled according to EICO's amplified
instructions will operate as specified therein.
EICO guarantees service and calibration of every EICO Kit and Instru-
ment at the nominal charge as stated in the instructions.

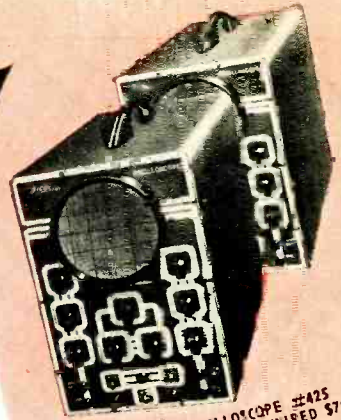ELECTRONIC INSTRUMENT CO., INC.
Test Equipment Manufacturers
84 WITHERS STREET, BROOKLYN 11, N. Y.



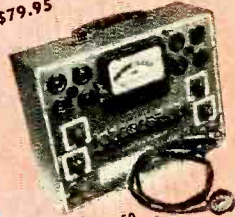5" PUSH-PULL OSCILLOSCOPE #475
KIT \$44.95 WIRE \$79.95
NEW! #470 7" PUSH-PULL OSCILLOSCOPE
KIT \$79.95 WIRE \$129.50



CRA... \$4.50
TUBE TESTER #525
KIT \$34.95 WIRE \$49.95




20,000 Ohms/Volt
MULTIMETER #565
KIT \$24.95
WIRE \$29.95



1,000 Ohms/Volt
MULTIMETER #566
KIT \$12.90
WIRE \$14.90



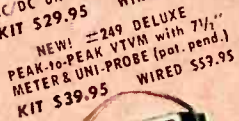NEW! #232 PEAK-TO-PEAK
VTVM with DUAL-PURPOSE
AC/DC UNI-PROBE (pat. pend.)
KIT \$29.95 WIRE \$49.95



NEW! #249 DELUXE
PEAK-TO-PEAK VTVM with 7 1/2"
METER & UNI-PROBE (pat. pend.)
KIT \$39.95 WIRE \$59.95




VACUUM TUBE VOLTMETER #221
KIT \$25.95 WIRE \$39.95
DELUXE VTVM (with 7 1/2" METER) #214
KIT \$34.95 WIRE \$54.95




R-C BRIDGE & R-C-L
COMPARATOR #950B
KIT \$19.95 WIRE \$29.95



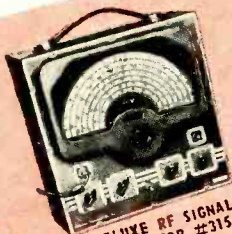MULTI-SIGNAL
TRACER #145
KIT \$19.95 WIRE \$28.95



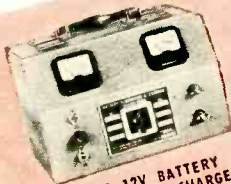DELUXE RF SIGNAL
GENERATOR #315
KIT \$39.95 WIRE \$59.95



6V & 12V BATTERY
ELIMINATOR & CHARGER
#1050
KIT \$29.95 WIRE \$38.95



NEW! #944 FLYBACK
TRANSFORMER & YOKE
TESTER
KIT \$23.95 WIRE \$34.95




RF SIGNAL GENERATOR #320
KIT \$19.95 WIRE \$29.95



TV/FM SWEEP GENERATOR #360
KIT \$34.95 WIRE \$49.95

SMC—4.5MC CRYSTAL
\$3.95 ea.

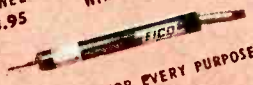

A PROBE FOR EVERY PURPOSE

EICO

See the famous EICO Line at your jobber today
SEND FOR FREE CATALOG C11
ELECTRONIC INSTRUMENT CO., Inc.
84 Withers Street • Brooklyn 11, N. Y.
Prices 5% higher on West Coast

HOT ELECTRONS—OR COLD?

.... *New Means of Liberating Electrons in the Future*

THE science of electronics began with a *released electron flow*, when Edison first noted an important phenomenon now known as the Edison effect. This revolutionary discovery occurred in 1883. Sealing a separate wire or plate into an electric light bulb, Edison noted that when the bulb was lit, an electrical current could be made to flow from the hot filament to the sealed-in cold plate. This despite the fact that there was no connection between the filament and the plate.

It was some years before scientists understood that what went on in the tube was a stream, or flow, of hot electrons from the filament to the cold plate, bridging the vacuum as if it were a good conductor.

Practically our entire science of radioelectronics—up to very recently—was built upon the hot-filament-to-cold-plate flow of *heat-generated* electrons. No practical electron tube for *general* radioelectronic purposes has been perfected that works in a cold state (Exceptions: specialized tubes such as certain rectifiers, photoelectric and multiplier tubes, etc.).

In the early days of wireless we used crystal detectors which worked quite well in the cold state without *heat-released* electrons. We may thus call them *cold quasi autoelectrons*, because they are practically self-releasing. Nevertheless, they require *some* energy to make them flow, even if the energy is exceedingly minute—as, for instance, radio-frequency currents collected from an aerial. Now the crystal detector becomes a rectifier and current flows through the earphones, bringing the distant broadcast music to us in the form of sound.

The modern, metamorphosed crystal—now known as a semiconductor and called a transistor—has caused a revolution in electronics, partly because it can oscillate just as can a vacuum tube, but more importantly, because it is an amplifier. Amplification is something the crystal diode never could achieve practically, though apparently it is about to make its debut as an amplifier. (page 94)

The transistor, in its many designs and types, functions with cold quasi autoelectrons and an exceedingly low energy input.

But marvelous device that it is, the transistor nevertheless is not the final word in electronics, for it still requires outside power to function.

The day is not too far distant when the atom will power the transistor and similar devices, *making them independent of outside energy in supplying current for the transformers, loudspeaker, picture tube, etc.*

As long ago as our October, 1945, issue, the writer, speaking of the future harnessing of the atom, said editorially: "From this it appears that such tiny, but powerful, generators will not contain moving parts in order to generate electricity." This idea was scoffed at for many years, but last September it was accepted as a coming reality by no less an authority than Eugene M. Zuckert, former chairman of the Atomic Energy Com-

mission. In a talk in Boston before the Savings Bank Association of Massachusetts, he assured his listeners that conversion of atomic energy *directly* into electricity was no longer a dream.

For that matter, the atomic battery, recently demonstrated and fully described in these pages, proves that the generation of electrical power in small quantities, directly from the atom, can no longer be called visionary.

It is thus certain that in the foreseeable future the atom in some manner will be coupled to the transistor to power it. *Indeed, the radioactive element will be integrated into the transistor, making it a single component.* Incidentally, laboratory samples of such devices are already in existence—not perfected, but an excellent blueprint of what will be done in the future.

These *autotransistors*, atom-powered, require no batteries, no electric light circuits, indeed no outside source of current whatever. *The atom furnishes whatever electric energy is required.* Such an autotransistor becomes in effect a true autoelectric generator, liberating in itself any desired flow of electrons, within reason.


The cost of such an atom-powered autotransistor will be quite reasonable—cheaper, in due time, than the present-day vacuum tube. Vast research during the past few years, particularly in atomic by-products, assures this. Even today, a large list of atomic radioactive isotopes can be bought at reasonable cost, chiefly because so very little is required. To atom-power an autotransistor will require only a minute quantity of a particular radioactive isotope. Moreover, the half-life of many such promising isotopes runs from five to hundreds of years, hence the life of the average autotransistor will be measured in decades.

Will it not be dangerous to work with such atomic transistors? Can they be handled safely? Would they not endanger owners of future atom-powered radio and television receivers? The answer must be a reassuring "no." We already mentioned that only minute amounts of radioactive substances will be used. All such atomic components will be safely sealed in lead or other shielding devices, allowing no leakage of dangerous radiation. The service technician of the future will carry a Geiger counter, or its equivalent, routinely. He will periodically test all atomic components for leaks, eliminating those that are defective.

By eliminating a large number of present-day components, the circuitry of future receivers will be greatly reduced, too. The manufacture of such sets, using printed circuits and many printed components, will be much simplified. Automation of receivers will make their building cost low, too. Hence, servicing the future sets will be easier also, and far less costly than today. Utopia? No—merely good and intelligent applied science.

H.G.

Unusual

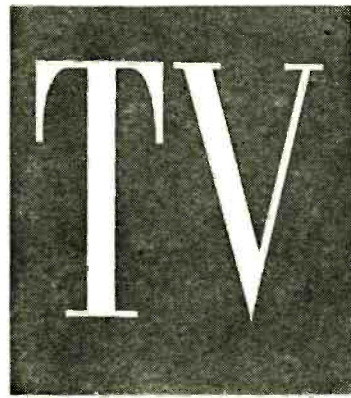

Circuits

By ROBERT F. SCOTT
TECHNICAL EDITOR

*Recent developments,
circuit tricks, and
modifications for
improving TV performance*

SOME of the latest TV receivers use triodes such as the 6C4 or half of a dual triode instead of a diode in the video detector and a.g.c. circuits. Fig. 1 shows the circuit used in the Arvin TE331 chassis. The video i.f. signal from the fourth picture i.f. amplifier is fed to the cathode of a triode (one half of a 12AU7). The grid acts as the anode of a diode detector.

The detected video signal appears across detector load L1, R1, and L2 and is capacitance-coupled to the 6AC7 video amplifier. The grid and cathode are returned to a 2.4-volt point on voltage divider R5, R6.

The 12AU7 plate is the anode of the a.g.c. detector diode. The rectified voltage across R2, R3, and R4 is used as a.g.c. voltage. The portion of it that appears across R3 and R4 is applied to the first three video i.f. amplifier stages. Two levels of a.g.c. for the tuner are available at the LOCAL-DISTANCE switch.

The plate of the triode returns directly to ground through R2, R3, and R4

while the cathode is biased 2.4 volts positive. This bias prevents the a.g.c. detector from conducting until the i.f. signal voltage equals or exceeds 2.4.

The delay bias does not affect the operation of the video detector because the detector anode (the control grid) is also biased 2.4 volts positive.

The RCA video detector

At first glance the video detector circuit in the RCA KCS72D-1 and KCS72D-2 (Fig. 2) appears very similar to the circuit in Fig. 1. However, there is a decided difference between the two circuits. The video detector uses one half of a 12AU7 twin triode. The other half is the vertical sync separator. The video detector and sync separator halves of the tube must be shielded from each other to prevent interaction. Shielding can be obtained by grounding the plate of the detector. However,

grounding the plate loads the detector circuit and reduces its efficiency.

RCA has worked out a novel scheme for isolating the two halves of the 12AU7 without loading the video detector. The plate of the video detector is grounded through a .01- μ f capacitor (C1) and is connected to a negative voltage (the grid of the 6BQ6-GT horizontal output tube). The negative voltage prevents the plate from drawing current as it would if grounded directly. The 2.2-megohm resistor and .01- μ f capacitor filter out the horizontal sweep voltage and prevent it from affecting the video and sync circuits.

Another unusual circuit feature of the RCA KCS72D chassis is in the low-voltage rectifier circuit (Fig. 3). A 5Y3-GT and 5U4-G are connected in parallel as full-wave rectifiers. The impedances of the two tubes are such that the current divides between them

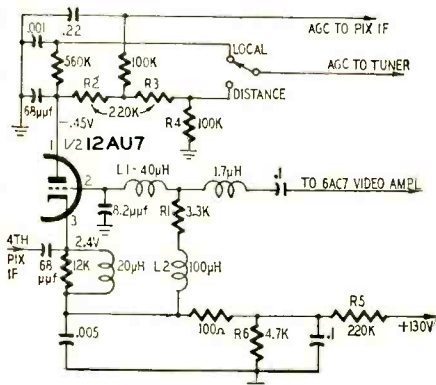


Fig. 1—Schematic of video detector and a.g.c. circuits in Arvin TE331.

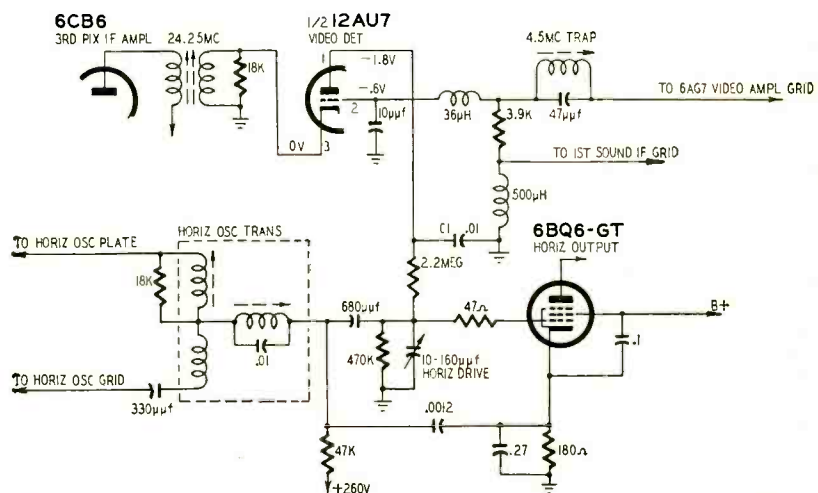


Fig. 2—Video detector and associated circuits in the RCA KCS72D-1,2.

with approximately two-thirds being carried by the 5U4-G and one-third by the 5Y3-GT.

Horizontal a.f.c. clamp

TV receivers that use Synchro-lock type a.f.c. circuits sometimes develop a hook at the top of the picture. This is often caused by vertical sync pulses leaking into the horizontal sync circuit and causing instantaneous changes in the error voltage developed by the horizontal discriminator. In the Video Products 630DX, K24C, and similar models, the diodes in the 6AT6 first a.f. amplifier are used to clamp the error voltage on the sync discriminator cathodes as shown in Fig. 4. Any increase in the error voltage due to vertical sync pulses causes the diodes to conduct and act to level out that voltage.

The 22,000-ohm resistor and 0.1- μ f capacitor have a time constant that effectively smoothes out transient variations in the voltage on the discriminator cathodes.

Olympic video detector and a.g.c.

The video detector and first sound i.f. amplifier circuit in the Olympic TL-20 and TK-17 chassis (Fig. 5) is similar to that used in the Magnavox series 105 described in this column in the July, 1952, issue.

In both circuits, the grid and cathode of the 6BA6 act as a diode video detector. Unlike the Magnavox, which uses a keyed a.g.c. circuit, the Olympic system uses the d.c. component of the rectified video i.f. signal as a source of a.g.c. voltage. The d.c. voltage is tapped off the 5,600-ohm detector load resistor and fed to the a.g.c. line supplying the tuner and first and second video i.f. stages. The filter network for the a.g.c. line consists of a 1-megohm series resistor and a 0.1- μ f smoothing capacitor connected from the a.g.c. line to ground.

Two-tube TV sound strip

The sound strip of the average TV set contains five separate tubes—some sets have seven or eight. The Westinghouse V-2227-1 TV chassis is unusual in that there are only two tubes in the sound circuit. A 6BK5 video amplifier (Fig. 6) is driven by direct coupling from the video detector. The sound take-off point is at the plate of the 6BK5 video amplifier. The 4.5-mc sound i.f. signal is fed from this point to the grid of the 6BN6 gated-beam FM detector. The output of the 6BN6 drives the 6BK5 a.f. output stage.

Hallcrafters' a.g.c. delay

Various methods of grading and delaying the application of a.g.c. voltage to cascode-type tuners were discussed in the July, 1953, and December, 1953, issues. Fig. 7 shows a somewhat different solution to the problem of supplying a.g.c. to cascode tuners. This is the circuit used in the Hallcrafters A1100D.

A 6AL5 is used as the video detector and a.g.c. rectifier. Diode V1-a is the video detector. The signal is fed to its cathode and the video signal is developed across the 3,300-ohm detector load resistor. The a.c. component of this signal is fed to the grid of the 6CB6 video output stage and the d.c. component is filtered and used as a.g.c. voltage for the first and second picture i.f. amplifiers. The negative voltage on the plate of V1-a averages only about 0.2 volt so this section of the 6AL5 conducts on all i.f. signals exceeding 0.2 volt peak.

A.g.c. voltage for the cascode tuner is developed by V1-b. This a.g.c. voltage is developed across R1 and is filtered by R2, R3, C1, and C2. With no signal input and all controls set for normal operation, there is a cutoff bias of approximately 5.6 volts between the plate and cathode of V1-b. This section does not conduct and develop tuner a.g.c. voltage until the picture i.f. signal exceeds the bias voltage. A positive voltage for the cathode of V1-b is obtained from a B plus voltage divider consisting of a 47,000-ohm resistor and the contrast control connected in series between the 125-volt line and ground.

When the contrast control is advanced for a weak signal, R4 is shorted out and positive bias is increased on the cathode. This increases the delay in production of tuner a.g.c. voltage and permits the tuner to operate at maximum gain.

On strong signals, the contrast control is rotated so that its arm moves toward ground. This action decreases the tuner a.g.c. delay bias on the cathode of V1-b and reduces the gain of the video amplifier by placing a larger portion of the contrast control in parallel with R4.

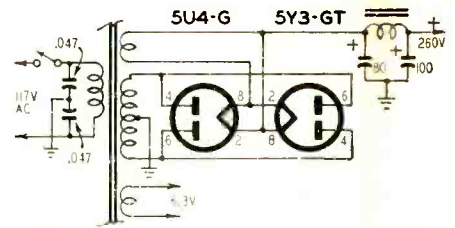


Fig. 3—RCA KCS72D power supply.

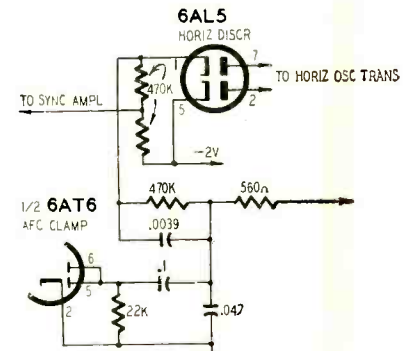


Fig. 4—Video Products' a.f.c. clamp.

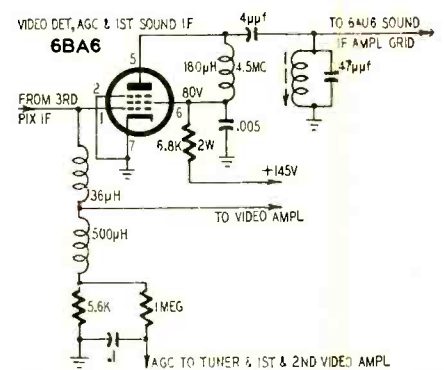


Fig. 5—Video detector and first audio amplifier in Olympic TL-20, TK-17.

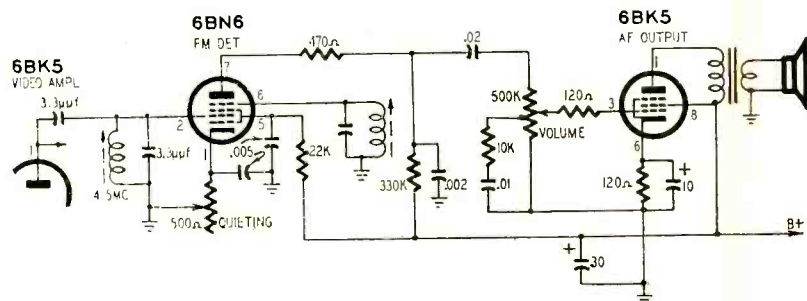


Fig. 6—Diagram of the audio section of the Westinghouse V-2227-1 chassis.


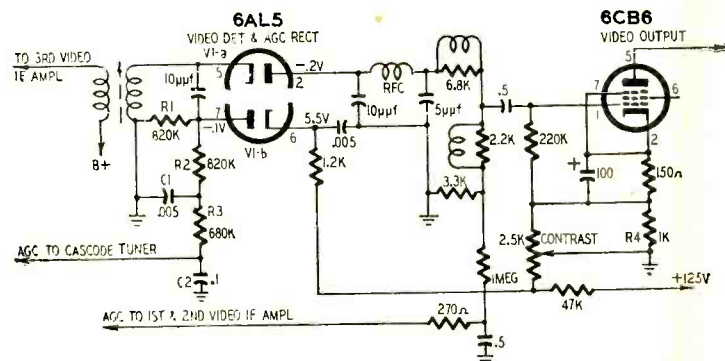


Fig. 7—Video detector and a.g.c. rectifier in the Hallcrafters A1100D.

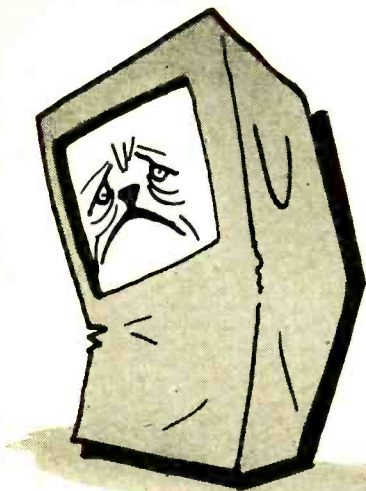

SERVICING DOG RECEIVERS

Special techniques are required for trouble-shooting those really tough ones

By ROBERT G. MIDDLETON*

TELEVISION receivers that have been tackled and given up by several shops are called by various and often unprintable names. They finally acquire the title of *dog* after no one in the community has been able to restore the receiver to satisfactory operation. Some shops in metropolitan areas specialize in "dog" work; these shops, in general, are much better equipped than the usual service shop.

A dog job must be undertaken very seriously: there is a good chance that the technician will be stumped even when provided with more and better instruments than the shop which let out the job. The first step is to obtain a complete history of the trouble, since important clues are sometimes so obtained. For example, if the defect has developed gradually and is slowly becoming worse, the experienced technician may suspect a failing electrolytic capacitor in an out-of-the-way portion of the circuit because these often depreciate slowly.

For example, a receiver was brought in with a dark vertical bar down the center of the screen. It was reported that the trouble had developed gradually and was slowly getting worse. The service technician suspected that some electrolytic capacitor might be failing. Since the dark band appeared vertically on the screen, the spurious voltage causing the trouble must be originating in horizontal circuits. All d.c. voltages and resistances checked O.K.; the picture tube and yoke had already been replaced.

*Field engineer, Simpson Electric Co.

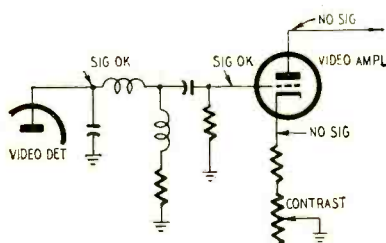


Fig. 1—Test points in video circuit.

The picture tube was grid-driven, and the cathode operated in the brightness circuit, powered from the booster circuit. After several false starts, a scope check was made at the cathode of the picture tube. The trouble became apparent as a substantial a.c. voltage at the horizontal frequency superimposed upon the d.c. voltage in the brightness circuit. Shunting a bypass capacitor from cathode to chassis removed the vertical bar. This, of course, was not a repair, but only a confirmation of the scope analysis.

The next step was to trace the spurious a.c. voltage with the scope back to its source, which proved to be a faulty electrolytic capacitor in the booster-decoupling circuit. Thus the preliminary theory, based on the history of the complaint, was correct. And served to make short work of what could have been a very difficult job, as the faulty capacitor was located in a somewhat inconspicuous part of the circuit. This job also served to emphasize the value of a scope to supplement the information provided by d.c. voltage and resistance measurements.

Of course, the history of the complaint often sheds no light on the trouble, and permits no theories to be formed. In such a case, work starts with a careful analysis of the symptoms. For example, a receiver was brought in with the complaint that the picture had suddenly disappeared, while the sound remained. No tube noise appeared on the screen of the picture tube when the contrast control was wide open, which indicated video-amplifier trouble, since the sound was taken off the picture-detector output. New tubes had been tried, and d.c. voltage and resistance measurements checked correctly.

To check the video-amplifier operation, a scope and low-capacitance probe were applied, starting with the output circuit of the picture detector (Fig. 1), at which point the video signal appeared normally. The video signal was present through the series peaking coil to the grid terminal of the video-amplifier

tube socket. However, it stopped there; no signal could be found at the plate of the video amplifier or at the cathode (across the contrast control). This was a very unusual situation, and the first thought was that the heater was not energized. However, a check showed that the heater was operating normally. Another tube was tried, because occasionally even a new tube will be found defective. This was another bad guess.

After wasting a lot of time in idle speculation, it finally occurred to the service technician that a signal being present at the grid terminal of the socket was no assurance that the signal was also present at the grid terminal of the tube base. A scope check showed the suspicion to be correct—the socket was defective, and a new tube socket cleared up the trouble. This job also emphasized the value of a scope.

Correct measurement

The service technician must always "use his bean," and be on the alert for incorrectly made measurements. For example, a receiver was brought in with poor picture quality. The d.c. voltage measurements in the i.f. amplifier did not all check correctly. The service data called for 135 volts at the plate and 145 volts at the screen of an i.f. tube. The voltmeter indicated 145 volts at both plate and screen.

A look at the circuit arrangement (Fig. 2) made this situation a real puzzler, since the plate and screen were tied together through the coupling coil which had a very low resistance. Investigation revealed that the service data was wrong! The technician who compiled the service data had used a

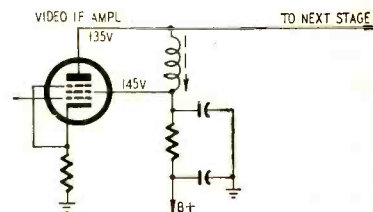


Fig. 2—Video i.f. amplifier stage.

20,000-ohms-per-volt meter to make these measurements. Lead resonance had caused the circuit to oscillate when making the plate-voltage measurements, reflecting circuit disturbances which worked out as a lower plate resistance in the tube and a lower apparent plate voltage. A v.t.v.m. avoids such difficulties, because the 1-megohm isolating resistor in the d.c. probe decouples the leads from the circuit.

Another practical example of incorrect measurement (or interpretation) occurred when servicing a receiver brought in with the complaint that the picture was too narrow. In a case like this, it is good practice to check first the drive at the grid of the horizontal-output tube. The drive was only 60% of the peak-to-peak voltage specified for the receiver, and the conclusion was drawn immediately that the trouble was probably in the horizontal-oscillator circuit and not in the horizontal sweep circuit. The d.c. voltage measurements showed low plate voltage at the horizontal oscillator. Some time was wasted checking the low-voltage power supply before discovering that the plate voltage was obtained from the booster circuit. Substitution of normal plate voltage to the horizontal oscillator by a pair of test leads from another chassis showed that the conclusion was true,

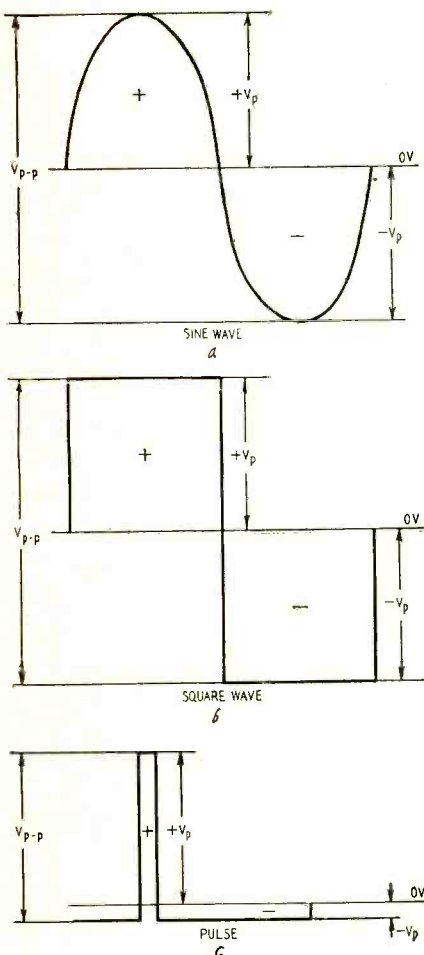


Fig. 3—Peak-to-peak calculations of frequently used television waveforms.

and that the trouble was actually in the booster circuit. Replacement of a faulty booster capacitor restored normal operation.

Interconnected circuits of this type complicate servicing. Merely setting the receiver controls to the positions specified by the service data for voltage measurements may not be sufficient. It still may be impossible to make a correct measurement until the influence of other receiver sections, possibly faulty, is removed from the circuit.

Measurements may be made incorrectly for other reasons; for example, reading peak-to-peak voltages is sometimes confusing. Occasionally it is incorrectly assumed that a peak-to-peak voltage is equal to twice the peak voltage. That this is not true may be seen from Fig. 3. Unless symmetrical waveforms, such as sine waves (a), or square waves (b) are under measurement, the positive-peak voltage is not equal to the negative-peak voltage (c).

To obtain a clear understanding of such measurements, the following points must be learned:

1. A sine wave is the element or "atom" of a.c. electricity—all non-sinusoidal waves can be broken down into a certain number of sine waves of various voltages, frequencies, and phases.
2. A sine wave has a positive-peak value which is equal to its negative-peak value, since the sine wave is a symmetrical waveform.
3. A sine wave has a definite relation to a d.c. voltage of the same value; this is called the r.m.s. or root-mean-square, or effective, value of the sine wave.
4. Before an r.m.s. voltage can be used to calibrate a scope, the r.m.s. value must be converted to the corresponding peak-to-peak value by multiplying by 2.83.
5. The multiplying factor of 2.83 applies only to sine waves; it does not apply to square waves, sawtooth waves, pulses, or rectifier waveforms.
6. Once a scope has been calibrated in terms of a peak-to-peak voltage on a sine-wave basis, the peak-to-peak calibration will apply to any waveform whatever.
7. The resting position of the scope beam indicates the zero-volt level. Positive-peak voltages are measured by counting squares of deflection above the zero-volt level; negative-peak voltages are measured by counting squares of deflection below the zero-volt level. The same calibration serves for peak voltage measurements as well as for peak-to-peak voltage measurements.
8. When a d.c. voltage is used for scope calibration, the d.c. value is equivalent to a peak-to-peak value. However, d.c. voltages are not indicated by an a.c. scope.
9. Unsymmetrical waveforms do not have equal positive and negative

deflections with respect to the zero-volt line; however, the positive area of any waveform is always exactly equal to the negative area of the waveform, since there is just as much positive electricity in a waveform as there is negative electricity.

10. A d.c. scope is converted into an a.c. scope by a series blocking capacitor in the input circuit; a d.c. scope shows the d.c. voltage component value in addition to the a.c. waveform values.

Measuring Instruments

Peak-to-peak voltages are best measured with a scope and low-capacitance probe. The probe (usually of the 10-to-1 variety) minimizes circuit loading and permits accurate measurements in sensitive circuits. When the scope provides for internal calibration, the 10-to-1 attenuation of the probe must be taken into account, and the nominal calibrating voltage must be divided by 0.1 in making the calibration. For example, if the scope is calibrated from a 6.3-volt r.m.s. sine-wave source, the 6.3 volts is first multiplied by 2.83 to obtain its peak-to-peak value of 17 volts. But if a 10-to-1 probe is used in making receiver tests, this 17 volts peak-to-peak is regarded as 1.7 volts peak-to-peak in calibrating the scope, thus taking into account the signal attenuation in the probe.

Standard voltmeters with peak-reading a.c. scales must not be used in making peak-to-peak measurements, since, as shown in Fig. 3, many waveforms do not provide equal values of positive and negative peaks. Likewise, a voltmeter with a half-wave rectifier probe cannot have a peak-to-peak scale, because full peak-to-peak information is not obtained by the probe. A suitable voltmeter must provide a voltage-doubler type probe (or built-in) rectifier, with a peak-to-peak indicating scale. Since the circuit loading of such an arrangement is much greater than that of a 10-to-1 scope probe, most service technicians prefer the use of the scope and probe.

It is sometimes supposed that a peak-to-peak measurement can be made by taking two measurements with a half-wave instrument, reversing the test leads for the second measurement, and adding (supposedly) the positive and negative peak values. Unfortunately, one of the measurements is almost certain to be in serious error because this method causes the "ground" terminal of the instrument to be applied to the "hot" side of the circuit for one of the measurements. As a result, the "hot" side of the circuit is partially shorted-out by the "ground" side of the instrument. On the other hand, a voltage-doubler type probe obtains both positive and negative peak voltages with the "hot" side of the instrument applied to the "hot" side of the circuit, and the peak-to-peak measurement can be made correctly.

END

ZERO-REFERENCE and

*Various problems involved
in servicing with an
oscilloscope*



By The Engineering Staff, Scala Radio Co.

WHEN a response curve is displayed on the screen of a d.c. scope, the base line level is always "locked" at a position on the screen set by the operator. By adjusting the vertical centering control (vertical positioning control) of the scope, the operator chooses the zero-volt reference position. As tuned circuits are adjusted, the response curve will change in form, but the zero-volt reference level remains fixed on the scope screen.

Fig. 1 shows that, as a ratio-discriminator transformer is adjusted, the S curve may appear completely above or completely below the zero-volt level when the circuits are detuned; but when the circuits are in proper adjustment,

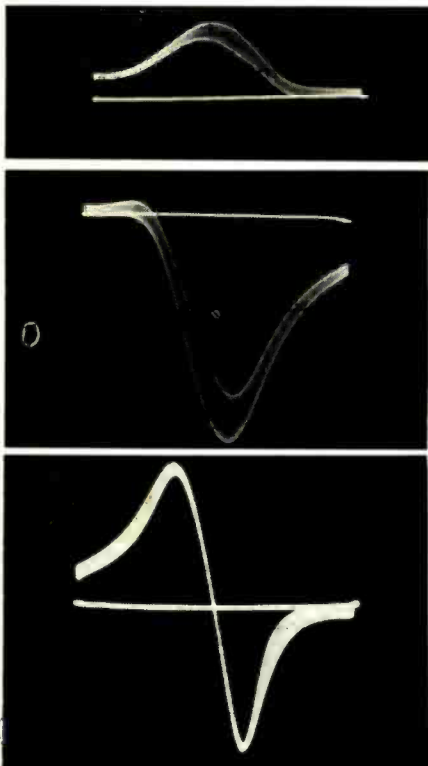


Fig. 1—S-curve variations as the ratio-discriminator transformer is adjusted.

the S curve appears symmetrical with respect to the zero-volt level. And if a d.c. scope is used in the alignment procedure, this zero-volt level does not shift on the screen as the adjustments are made to the ratio-discriminator transformer.

However, when the zero-volt reference level is developed by a suitable blanking network in the sweep-generator circuits, the zero-volt level does not remain fixed in position on the scope screen—it will move up or down the screen as the tuned circuits are adjusted, and the shape of the response curve changes.

A clear distinction must be made between the zero-volt reference level on an a.c. scope and the resting position of the beam when no signal is applied. Unlike a d.c. scope, an a.c. scope displays the zero-volt reference level and the resting positions at different heights on the screen. Fig. 2 shows an i.f. response curve, with a zero-volt reference base line developed by the sweep generator, and the resting position of the beam, as displayed on the screen of an a.c. scope. The zero-volt reference level appears below the resting level of the trace. This is the essential distinction between displays on a.c. scopes and d.c. scopes.

The zero-volt reference level can be developed by the sweep generator in

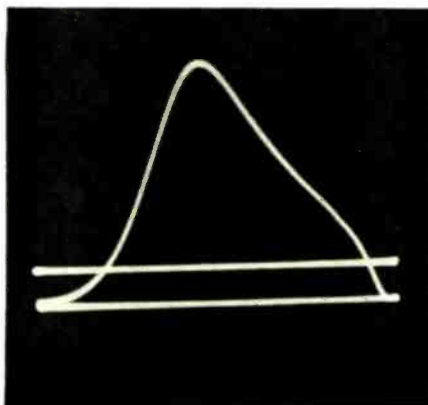


Fig. 2—No-signal position at different level than zero-volt reference line.

various ways. One of the simplest means of developing a zero-volt reference level is shown in Fig. 3. A pair of contacts in an automobile-radio vibrator rapidly short the input terminals of the scope during operation.

Shorting out the input signal to the scope at rapid intervals makes the beam fall to the zero-volt level many times during the forward sweep. The action is similar to that of an electronic switch, except that in this case the action is that of a mechanical switch.

When the zero-reference function is built into a sweep generator at the factory, a mechanical switch is not used—it is more convenient to design an electronic switch. The electronic switch is in fact a keying bias (square-wave voltage), that is applied to the grid of the swept oscillator in the generator. The keying bias changes from maximum to minimum voltage 60 times a second, to synchronize with the horizontal sweep rate in the scope. However, synchronism is not essential to satisfactory keying, so the random switching of the auto-radio vibrator will provide an entirely satisfactory display.

Landmarks

The technician should learn to look for various "landmarks" as soon as the receiver chassis is placed on the bench. Some of these are the peaking coils in the video-detector circuit, which are suitable points for scope connection in

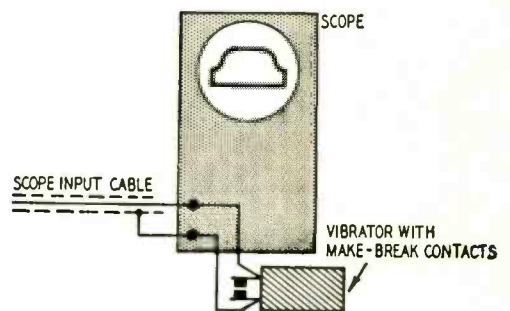


Fig. 3—Developing a zero-volt reference line for use with an a.c. scope.

i.f. alignment; and the mixer tube, a suitable point for capacitive injection of the sweep signal into the i.f. input circuit.

The a.g.c. bus, to which the d.c. returns are made from the grid circuits of the i.f. amplifier tubes, usually can be located without using a circuit diagram for the receiver. Most of the present-day tubes used in i.f. amplifiers have pin 1 as the control grid, and unless unfamiliar i.f. transformers are used in the receiver under test, it is easy to pick out the return point of the grid circuit, which identifies the a.g.c. bus. Fixed d.c. bias should be applied between the a.g.c. bus and chassis ground to stabilize i.f. amplifier operation during alignment and to set the gain at a suitable point.

When the front end is of a familiar type, the local-oscillator tube can be quickly located. In the majority of cases, the technician will reach for a dummy oscillator-mixer tube which he has made up.

The output of the video amplifier is usually easy to locate, also; it consists of the final pair of peaking coils in the signal-circuit line-up, and the output from this set of coils is fed to either the grid (green lead) or to the cathode (yellow lead) of the picture tube. Although the video amplifier is not always checked during an alignment job, complaints of poor picture quality are sometimes traced to this section.

Override bias battery

Receiver manufacturers usually state that override bias should be applied to the i.f. amplifier to stabilize the output and control the gain during alignment. This override bias is essential in the case of keyed a.g.c. systems, because the keyed a.g.c. circuit is normally operated by horizontal sync pulses having a frequency of 15,750 cycles. When a

60-cycle alignment voltage is applied, the a.g.c. circuit becomes unstable and the forward trace usually has a different shape from the return trace. However, when override bias from flashlight cells is applied to the grids of the i.f. amplifier tubes, the a.g.c. circuit is stabilized, and trace and retrace have the same shape.

Many technicians open the a.g.c. bus from its driving circuit for application of the override bias. This can be done, if desired, but it represents a waste of time, because the stabilization is not affected by opening or closing the circuit. The a.g.c. circuit has a high impedance, and when a low-impedance voltage source, such as flashlight cells, is shunted between the a.g.c. bus and chassis ground, the low-impedance source fixes the voltage in the circuit. Hence, disconnection of the a.g.c. bus is not required.

About -3 volts is generally used for override bias application, but, as will be discussed in future articles, special alignment jobs arise where a greater or a lesser value of override bias may be more suitable.

Transformer, or transformerless?

Some receivers are of the transformerless type. They may or may not have a hot chassis. The hot chassis types have one side connected to the power line. The possibility of having hot-chassis sets to work on makes a line-isolation transformer at the service bench essential, to avoid the possibility of shock, due to the operator touching the chassis while standing on a damp floor, touching a conduit, pipe, or other ground path.

Using a line-isolation transformer also protects the test equipment. Instrument cases are usually grounded to avoid minor shocks to the operator when he touches the metal portions of the equipment. Minor shocks result from the use of shunt capacitors in the line filters of the test instruments; these line-filter capacitors conduct a small current, sometimes sufficient to be felt by the operator. Hence it is common practice to ground the instrument cases.

Since instrument cases are grounded, connecting the instruments to a hot-chassis circuit can result either in blown fuses, or in burned-out components in the instruments. The line-isolation transformer prevents such damage.

Standing-wave distortion

Standing-wave distortion is a most troublesome alignment bug, especially when the technician is unaware of its basic cause. Standing-wave distortion shows up as a change in the shape of the response curve due to body capacitance in the vicinity of the instruments or the TV chassis, and appears as shown in Fig. 4.

There are at least two types of standing-wave distortion. One occurs *inside* the sweep-output cable, the other occurs *outside* the sweep-output cable. Stand-

ing waves are generated inside the sweep-output cable when the cable is improperly terminated. The sweep-output cable is usually connected to a light load, such as a floating tube shield over the mixer tube. This floating tube shield represents a very light capacitive load at the end of the sweep-output cable, and does not provide the required termination (impedance match).

To terminate a sweep-output cable properly, it is usually necessary to shunt a 75-ohm carbon resistor across the end of the cable. The termination is sometimes provided by the manufacturer of the instrument. It is essential to use a carbon resistor for termination, because a wirewound resistor will have high inductive reactance at intermediate alignment frequencies, and will fail to provide a proper termination.

When a sweep-output cable is not terminated in its own characteristic impedance (usually 75 ohms), a peculiar situation results. Not all of the electric energy flowing down the cable is absorbed by the load. Some of the downcoming energy is reflected back up the cable again. This reflected energy interferes with the incoming energy at half-wave points, and as the generator sweeps through the frequency band, these interferences, sometimes called "hot" spots and "cold" spots, oscillate along the cable, back and forth, at a 60-cycle rate. The generator will then deliver a higher voltage to the load at one frequency, and a lower voltage at another.

The response curve is distorted by the abnormal voltages. But there is a distinguishing characteristic which is very important to the working technician—the curve shape changes when a terminating resistor is shunted across the end of the output cable, but the curve shape does not change when the technician moves about or touches the test instruments.

If the curve shape changes when a dial or cable is touched, standing-wave distortion is present as a result of sweep voltage on the outside of the instruments and cables. In some cases sweep voltage spreads out over the outside of the cable because of improper termination, but more often the sweep voltage spreads along the outside of the cable from the generator end. Faulty connectors, for example, are often responsible for sweep voltage leaking from the generator to the outside of the cable.

One of the standard methods for minimizing trouble from standing-wave voltages of this type is to ground all the test instruments together. A business-like way is to mount all the instruments in a rack-and-panel assembly, which can in turn be grounded to a water pipe. More often than not a water pipe will not be close at hand. In such an event use a heavy copper strap to connect all instrument cases and run the strap to a water pipe or a copper rod driven into the earth. Where possible, solder the copper strap to the instrument cases and, of course, to the grounded rod. END

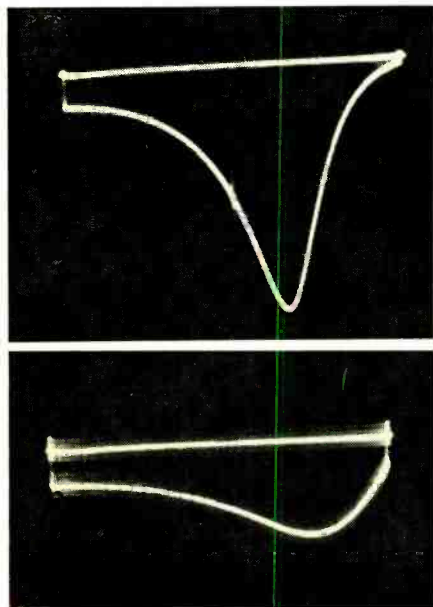


Fig. 4-a—Normal response curve. 4-b—Curve changes shape when sweep-generator tuning dial is touched.

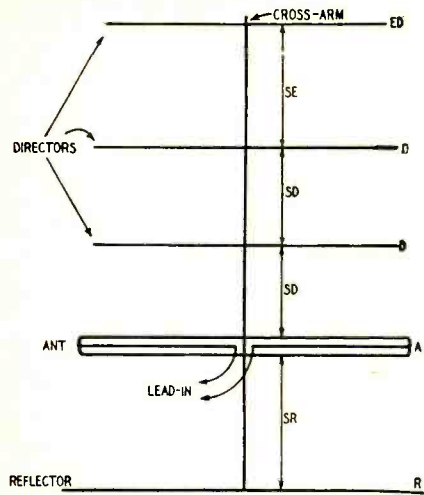


Fig. 1—A five-element Yagi antenna showing length of reflector and directors, and spacing between them.

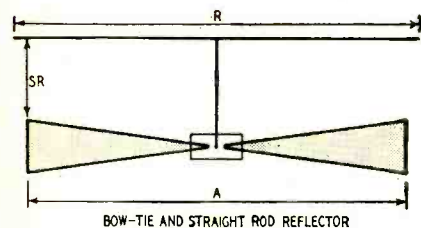
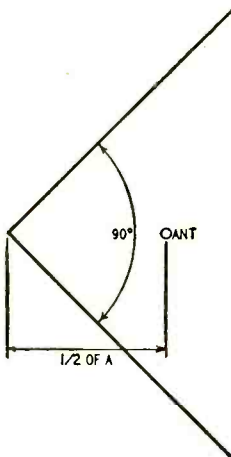
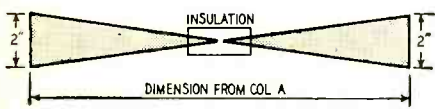
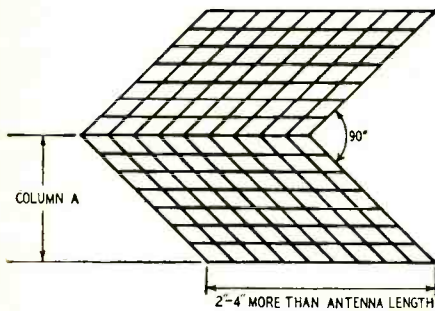


Fig. 2—Diagram indicates all dimensions of the bowtie antenna and screen and straight-rod reflectors.

ELEMENT SIZES for UHF ANTENNAS

By MATTHEW MANDL

THE antenna dimensions given in Table I can be used in constructing u.h.f. antennas such as the Yagi, the bowtie with reflector, and the bowtie with a flat screen or corner reflector. Since antennas have a slightly broader response at the ultra-high frequencies, and differences in element lengths are small, the table has been prepared in quarter-inch steps for the antenna elements. Thus the unnecessary fraction-of-an-inch measurements are minimized. In a number of instances a set of dimensions covers from two to five channels. As shown in Fig. 1, the lengths given in Table I apply to the total length of the antenna, director, reflectors, and spacings between.

Yagi antennas have high gain, and the 4- or 5-element types can be used over several adjacent channels. If greater gain is desired, 6- or 10-element Yagi antennas can be constructed. Generally, these will be useful only for the particular channel for which they are cut, and orientation will be very critical. The table can also be used for construction of broad-band u.h.f. Yagi antennas. The broad-band types, however, have less gain than a Yagi designed for a specific channel. (See "Broadband Yagi Antennas," page 45 of the September, 1953, issue of RADIO-ELECTRONICS.)

When constructing the u.h.f. Yagi, all directors except the last one should have the dimension shown in column D. Thus, if a Yagi has six directors, the first five (from the antenna) have the dimension given in column D for the channel desired, while the last director has the length given in column ED. The end director (ED) is also spaced from the last director by a greater distance than the others, as given in column SE.

For v.h.f., maximum gain is obtained when reflectors are spaced 0.15 wavelength from the antenna, while directors are spaced 0.1 wavelength. Since the same diameter elements are used for u.h.f. (one-quarter to one-half-inch stock), spacings given in Table I are somewhat greater to minimize capacitance effects between elements, and aid in keeping the antenna impedance up. An ordinary folded dipole will result in a greater impedance drop than the double-folded dipole shown in Fig. 1.

Thus, the double-folded dipole is recommended, plus the use of one-quarter-inch diameter aluminum or copper tubing. Space the folded-dipole sections no farther apart than the diameter of the tubing used. The crossarm should be metal; it should interconnect the reflector, all directors, and the unbroken elements of the antenna. Make sure the elements are mounted directly at their center, within a quarter inch.

The bowtie antenna can pick up any u.h.f. channel if it is cut for the lowest channel to be received. Thus, a bowtie designed for channel 14 can pick up all the other channels if the signal strength of the stations is sufficient and the antenna is oriented correctly. The bowtie however does not have the gain of the Yagi. Dimensions given in Table I are used for the illustrations in Fig. 2. The bowtie can be mounted on an insulator, while the folded-dipole element of Fig. 1 is usually very rigid and an insulator is unnecessary. (Air is the best insulator, and does not accumulate the dirt, grit, and moisture which affect u.h.f. reception so much.)

When antennas are double-stacked, gain is increased approximately 3 db. Thus, a 4-element u.h.f. Yagi with a gain of 8 db can be stacked to give a gain of 11 db. If four such types are stacked, the gain will be 14 db. An 8-bay stack has a gain of 17 db. You must double the number of elements (bays) in an array to increase the gain 3 db. Stack the antennas at a distance equal to the antenna length (Column A).

Two Examples

We wish to construct a 6-element Yagi as shown in Fig. 1, with an additional director, to be used on channel 28. Table I indicates that the dimensions given for channels 27, 28, and 29 apply. Thus, the reflector is 10.5 inches, the radiator (A) is 10 inches, and the next three directors are 9.5 inches each. The last director is 8.5 inches. Spacing between the reflector and antenna is 4.75 inches, and between the first three directors, 4 inches. The spacing between the last two directors is 5.5 inches.

We wish to construct a bowtie with corner reflector, to cover channels 14, 26, and 30. The antenna is cut for the lowest channel and is 12 inches wide. Two screens are used to form the cor-

ner reflector, each 12 by 16 inches wide. The bowtie is spaced 6 inches from the center of the screen.

TABLE I

Dimension in inches

Channel Numbers	R	A	D	ED	SR	SD	SE
14	12.5	12.0	11.5	11.0	6.0	5.0	7.0
15	12.25	11.75	11.25	10.25	5.75	4.75	6.75
16-17	12.0	11.5	11.0	10.0	5.5	4.5	6.5
18	11.75	11.25	10.75	9.75	5.25	4.5	6.25
19, 20	11.5	11.0	10.5	9.5	5.0	4.5	6.0
21, 22	11.25	10.75	10.25	9.25	5.0	4.5	6.0
23, 24, 25	11.0	10.5	10.0	9.0	5.0	4.0	6.0
26	10.75	10.25	9.75	8.75	5.0	4.0	6.0
27, 28, 29	10.5	10.0	9.5	8.5	4.75	4.0	5.5
30, 31	10.25	9.75	9.25	8.25	4.75	3.75	5.5
32, 33, 34	10.0	9.5	9.0	8.0	4.75	3.5	5.5
35, 36, 37	9.75	9.25	8.75	7.75	4.5	3.5	5.25
38, 39, 40	9.5	9.0	8.5	7.5	4.5	3.5	5.25
41, 42, 43	9.25	8.75	8.5	7.5	4.25	3.25	4.75
44, 45, 46	9.0	8.5	8.25	7.5	4.25	3.25	4.75
47, 48	8.75	8.25	8.0	7.25	4.0	3.25	4.5
49 to 53	8.5	8.0	7.75	7.25	4.0	3.0	4.5
54, 55, 56	8.25	7.75	7.5	7.0	3.5	3.0	4.0
57 to 61	8.0	7.5	7.25	6.75	3.5	3.0	4.0
62, 63, 64	7.75	7.25	7.0	6.5	3.5	2.75	4.0
65 to 70	7.25	7.0	6.75	6.25	3.5	2.75	4.0
71 to 75	7.25	6.75	6.5	6.25	3.25	2.5	3.75
76 to 81	7.0	6.5	6.25	6.0	3.25	2.5	3.75
82, 83	6.75	6.25	6.0	6.0	3.0	2.5	3.5

U.h.f. installation factors

1. Mount antenna at least six feet away from tin roofs, metal rain gutters, or other metallic objects.

2. Use high-grade, low-loss standoff insulators. Never tape the lead-in directly to the mast.

3. Use high-grade transmission line, such as the tubular two-wire line or the new u.h.f. open-wire line. Space well away from parallel-running rain pipes or metal conduit.

4. Use a short lead-in from the antenna to the receiver, and leave only enough slack behind the receiver so it can be moved for cleaning. Never leave a coil of lead-in lying behind the receiver.

5. If possible, explore the antenna mounting site by moving the antenna around to find an area where u.h.f. signals are highest.

6. If a tubular line is used, seal up the top to keep water out, and punch a few drain holes in the line where it enters the home.

7. If the station is over 25 miles away and is transmitting with low power, or if your converter or receiver is faulty, u.h.f. reception will suffer. Check these facts before condemning the antenna system.

8. Orient antenna carefully for best signal strength. This is particularly important with Yagi antennas.

9. For lasting results, the application of a clear plastic spray on the antenna and insulators will assure good performance.

10. In hilly terrain a slight upward tilt of Yagi or stacked antennas may increase signal strength.

11. Try a section of tin foil or aluminum foil 8 inches long, wrapped around the transmission line near the converter or receiver. This helps tune some frequencies better than others when slid up and down. (Not applicable to open-wire line.)

12. If u.h.f. stations seem to drift, check the crystal mixer in the converter, or check the local oscillator tube in the receiver.

END

NEW TV REMOTE CONTROL

A new and low-cost approach to the problem of tuning a television receiver from a distance is the *Controlmaster*, which uses the stepping-relay principle. A ratchet-paw solenoid mounted on the tuner operates the cam ratchet usually located at the center of the tuner drum. The present model—made by the Mercury Marine Electric Co., San Francisco—is adapted to the widely used Standard Coil tuner.


Pressing the remote solenoid control button energizes the solenoid armature and moves the channel selector one

notch.

The *Controlmaster* is mounted on the rear of the tuner where the dust cover is usually located—a new cover is furnished to replace it.

Besides the ratchet-paw assembly, the control unit includes 25 feet of 8-conduit cable and a remote-control assembly consisting of an on-off switch, volume control, contrast button, and solenoid control button.

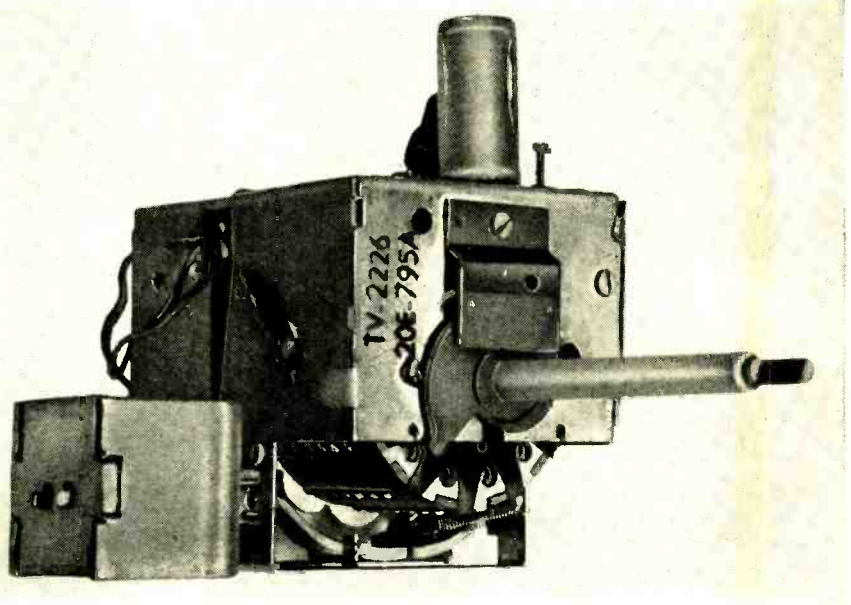The new control is remarkably simple in design and apparently equally positive in operation.



THE CORE OF THE MATTER

In Buenos Aires (see photo) we have our servicing headaches as anywhere else. I recently went out on a routine service call involving a Zenith model 19K20. The owner complained that the horizontal sync was completely out.

The horizontal sweep circuit of this receiver uses the Gruen a.f.c. system which I have found to be extremely stable. The only control requiring adjustment is the iron core of the oscillator coil in the front of the set. It has a control knob with a stop that permits

only one rotation of the core. If you take off the knob, the core can be rotated through several turns. This is done in cases where it is necessary to compensate for some change in operating conditions.

When I inspected the set the a.f.c. was working properly but the horizontal oscillator was away off its normal frequency.

I changed the 6NS7 horizontal oscillator and the 6AQ7 a.f.c. tube—no luck. I then pulled the chassis to check for a possible defective capacitor in the oscillator tank. I changed the suspected capacitors—still no luck. After making all the usual measurements without finding the trouble source, I was ready to tell the customer that it would be necessary to take the set to the shop for a more extensive checkover.

In moving the chassis, I saw a piece of iron core—a part of the horizontal coil's core that had broken off and fallen out. The remainder of the core was unable to bring the oscillator to its correct frequency. A drop of cement applied to the core fixed everything.

—Egon Strauss



COLOR TV CIRCUITS

Part VI—The three-gun picture tube and its control circuitry

By KEN KLEIDON* and PHIL STEINBERG*

THE first five articles of this series covered circuitry of color receivers using the three-gun color picture tube. It was pointed out that the majority of these circuits would also be found in the single-gun (Lawrence) tube receiver. A later installment will cover circuits required specifically for the single-gun tube receiver. This article will deal with the operation of a three-gun type picture tube.

To understand the operation of a three-gun color picture tube consider the tube as three separate picture tubes in one glass envelope. Each of the three separate picture tubes has an individual filament, cathode, control grid, accelerating anode (screen grid), focus anode, and phosphor-dot screen identical to a monochrome or black-and-white picture tube. The only difference between the three separate picture tubes is the color of the screen. One has a red phosphor-dot screen; the other two colors are blue and green, which comprise the three primary colors necessary to produce a color picture. The filaments are connected in parallel and the focus electrodes are tied together internally. Fig. 1 shows the essential elements and base connections of a three-gun picture tube.

Two components in a three-gun picture tube not found in a black-and-white tube are a shadow mask and a convergence electrode. These are required for mechanical reasons and to assure that the proper electron beam strikes the correct phosphor dot at the right time.

Most black-and-white picture tubes require an ion-trap magnet. It must sometimes be adjusted during installation. A color picture tube does not

*Raytheon Manufacturing Company, Television and Radio Division.

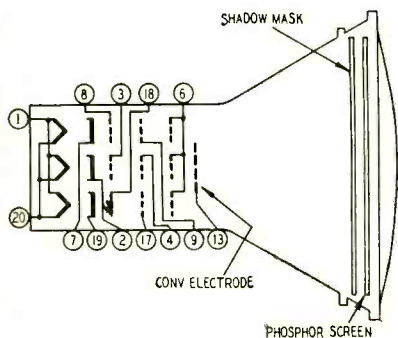


Fig. 1—The three-gun picture tube.

require an ion-trap magnet. Instead, it has a purity coil which must also be adjusted. The purity coil is located behind the deflection yoke (Fig. 2). Its function is to align the three electron guns by an electromagnetic field so that the beam from each gun strikes only its own phosphor dots. A pure red field is desired when only the red gun is operating and pure blue only when the blue gun is operating. The electron beam from the red gun must strike only red phosphor dots, electrons from the green gun must strike only green dots, and blue phosphor dots must be illuminated only by the electron stream from the blue gun.

The deflection yoke on a color picture tube performs the same function as on a black-and-white tube. The only other new components for a color tube are the convergence magnets. Three are provided (one for each gun). Their action is to deflect their respective beams so they converge at the same hole in the shadow mask. Then each beam strikes only its own proper phosphor dot at the correct time, thus preventing color fringing. (See Fig. 3.)

Only one brightness control is necessary for a black-and-white picture tube. A three-gun color tube has an individual brightness control for the blue and green guns and a master brightness control which affects the brightness of all three guns. This is shown in Fig. 4-a. An individual red brightness control is not needed as the red phosphor is the least efficient of the three. The blue and green brightness controls are adjusted to obtain a balance using red as a reference.

In black-and-white receiver design the accelerating anode or screen grid voltage is fixed at a predetermined level. Due to nonuniformities and varying cutoff characteristics of each gun, individual screen controls are necessary for a three-gun picture tube. Also required are a high-potential focus and convergence electrode voltage. Cor-

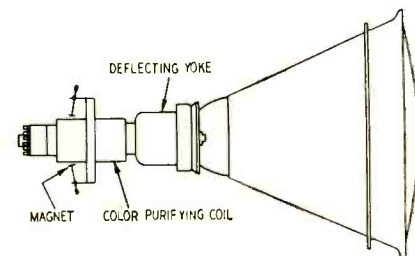


Fig. 2—Location of the purity coil.

responding controls are provided. These controls are shown in Figs. 4-b and 4-c, respectively.

Since the face plate on which the red, blue, and green phosphor dots are deposited is flat (in the RCA 15-inch tube, for example), the distance that the three electron beams travel to reach the center or an edge of the tube varies. If there was no compensation for this variation, both the focus and convergence would change and present an unsatisfactory color picture. For this reason both the focus and convergence potentials are varied by a parabolic waveform obtained from the horizontal and vertical deflection circuits to compensate for the distance changes in electron beam travel. The parabolic waveforms vary the focus and converge potentials so as to provide correct convergence and focus over the entire viewing screen.

Figs. 5-a and 5-b illustrate the parabolic waveforms usually obtained from the cathodes of the horizontal and vertical output tubes after they are applied to wave-shaping networks and amplifiers. Fig. 5-c shows the combined waveforms which are applied to the focus and convergence electrodes. Amplitude, phasing, and wave-shaping controls are provided to adjust the parabolic waveforms to the proper size and shape to correct for mechanical deficiencies of the three-gun color picture tube. The d.c. convergence and focus controls are usually referred to as static controls and the controls which affect the parabolic waveforms are referred to as dynamic controls.

The set-up or installation adjustments of a color picture tube are identical to a black-and-white tube in that the same controls must be adjusted in basically the same manner. The vertical size, linearity and centering, horizontal size, drive, linearity and centering as well as the hold controls, etc., must be properly adjusted before the controls

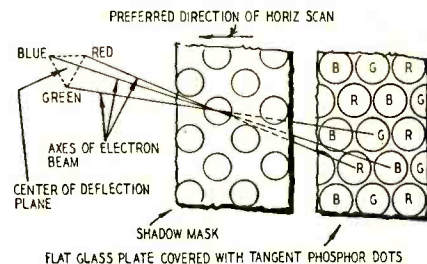


Fig. 3—Proper convergence action.

MECHANICAL BUGS ARE DEADLIEST

By MILTON LOWENS

PROBABLY it could never happen again but...

I remember the set well—it was a Du Mont RA-110A—not only because of its weight, which was considerable, but because of the trouble it gave me. The complaint was routine: no pix, no sound, raster O.K. I considered the facts on my way over and wondered how long it would take to fix the set. I made a small bet with myself that I would hit the bad tube in the tuner on the first try. It couldn't be the r.f. amplifier (some sound usually gets through), so it would be either the mixer or the oscillator. I hoped it would be the mixer—the list price of the 6AK5 is higher than that of the 6AB4 and I could use the money.

I lost my bet. I didn't hit the tube on the first try, nor the second, nor the third. The set was lively enough. Auto ignition noise came roaring through. Scraping the antenna leads on their terminals gave plenty of noise and flashes on the picture tube. Tuner trouble, I decided. That's when I found out the weight of the chassis. The nice old widow looked sympathetic as I staggered out.

I should have used my signal generator once I got the set on the bench, but I was sure I knew what the trouble was—one of the sliders was not touching the ends of one of the coils—or the trolley was off the wire. I had heard of these Inductuner troubles although I never had tried to fix one. I was not so sure I could. Unpleasant visions arose involving a big bill for a replacement tuner and the sad face of the nice old widow who obviously was not too well fixed.

First thing to do though was to see just what had failed. This meant removing the aluminum cover over the coils. Why is it that so many otherwise well-engineered sets make things so tough for the service technician? Did you ever try to get one of these covers off without taking the whole tuner out of the chassis? Well, I did what I had seen plenty of evidence of others having done: I removed the accessible top screws and pried the cover high enough to peek in.

Everything looked fine. All voltages, measured from above with the tubes out of the sockets, were normal. In disgust I twirled the tuning knob to hear the sound of the many gears in the special dial. Everything turned nicely except the concealed shaft in the tuner on which the coils were mounted. The trouble? Both Allen-head setscrews on the dial drive collar were loose and the coils stopped at a dead spot!

I happily tightened the setscrews and returned the receiver to its original condition. I had learned a lesson—a television set is an electrical device but it is made of mechanical parts. END

typical of a color tube are attempted. Then the first step would be to adjust for color purity.

Purity Adjustments

1. Turn contrast control to minimum.
2. Turn blue and green screen controls to minimum. Turn red screen control to maximum.
3. Adjust master brightness control for average brightness.
4. Position yoke for small red field raster in center of screen.
5. Adjust purity coil positioning and current control for pure red field.
6. Repeat steps 4 and 5.
7. Check purity of blue and green fields and compromise the settings of the purity adjustment, if necessary, to secure best red, blue, and green fields.

Convergence Adjustments

1. Connect dot generator to receiver.
2. Turn horizontal and vertical convergence amplitude controls to minimum.
3. Turn d.c. convergence control to minimum.
4. Adjust screen controls for equal size color dots.
5. Adjust convergence magnets for equal spacing between color dots at center of tube. Must form an equilateral triangle.
6. Adjust d.c. convergence control until color dots at center of tube

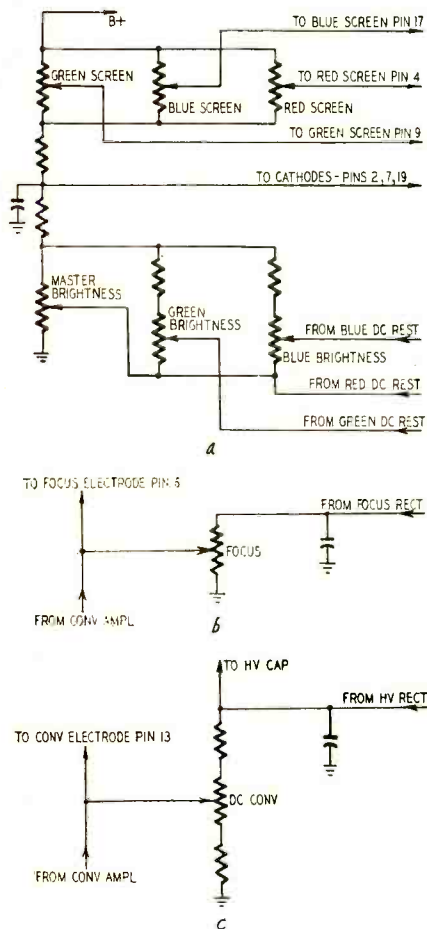


Fig. 4—Various circuits necessary for three-gun color tube operation.

come together and form a white dot. Readjust convergence magnets if necessary.

7. Adjust horizontal convergence phase and amplitude controls until center horizontal line converges.
8. Adjust vertical convergence shaping and amplitude controls until center vertical line converges.
9. Repeat steps 6, 7, and 8 until only white dots appear over entire face of tube.

The dot generator recommended for the convergence adjustment is not an absolute requirement as a cross-bar generator will serve equally as well.

Color Balance

1. Turn the chroma and contrast controls to minimum.
2. Adjust master brightness control for high brightness.
3. Adjust red, blue, and green screen controls for a light gray or a low-brightness white picture.
4. Turn contrast control to its center adjustment position.
5. Adjust the blue and green video gain controls for a satisfactory black-and-white picture.
6. Adjust master brightness control for a low-brightness-level picture.
7. Adjust blue and green brightness controls for a satisfactory picture.
8. Turn master brightness and contrast controls from maximum to minimum and observe picture. If a change of picture color is noticed, repeat procedure.

The above adjustment procedures are not presented to be used as a step-by-step adjustment method but only as a general outline to give service technicians who are unfamiliar with or who have never attempted color picture tube adjustments an idea of the procedure to be followed. The manufacturer's service literature should be consulted, the specified equipment used, and the procedures outlined should be carefully followed. See also RADIO-ELECTRONICS, May 1954 issue on P. 35.

TO BE CONTINUED

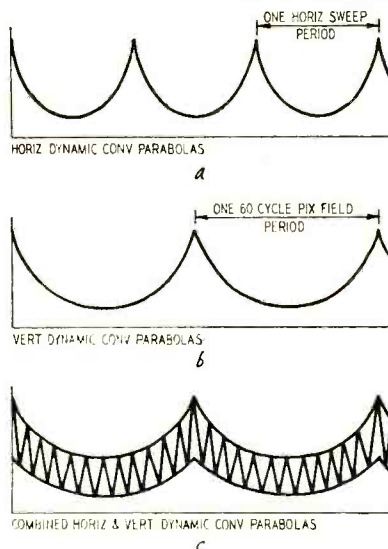


Fig. 5—Waveforms that are applied to the focus and convergence electrodes.

TELEVISION... it's a cinch

From the original "La Télévision . . . Mais c'est très simple!" Translated from the French by Fred Shunaman. All North American rights reserved. No extract may be printed without the permission of RADIO-ELECTRONICS and the author.

By E. AISBERG

*Thirteenth conversation, second half:
Parasitic capacitances; value of load
resistors; high-frequency compensation.*

Video is not audio

WILL—Now that we've finally got our video frequency clear of its carrier, all we have to do is amplify it. That shouldn't be too much different from amplifying the audio frequencies in a radio receiver, except for the wider frequency band you have to amplify. And with the frequencies 'way up in the megacycles, I suppose you have to be pretty careful of stray wiring capacitances?

KEN—That's for sure! But that's not the only difference between a.f. and v.f. Fortunately, some of the differences are in our favor and make our problems easier instead of harder. For instance, we need only a *voltage* to control the picture tube's electron beam at the output of our amplifier, rather than *power* to operate a speaker.

WILL—So we have to put out volts instead of watts? Fine—voltages are easier to calculate! And what are the other differences between a.f. and v.f.?

KEN—Another important difference is that we don't need nearly as much gain as the average audio amplifier. To vary the brilliance of the spot from a good white to a good black needs only 20 to 30 volts. You usually get about a volt at the detector output. Therefore—in spite of the things that tend to cut down the gain in a video amplifier—one stage is enough in most cases. A few models do have two video stages, though.

WILL—And the "things that tend to cut down the gain" are tied up with the high frequencies and problems of stray capacitances?

KEN—You've guessed it! The video amplifier uses the old reliable resistance-coupling system. And—right across the coupling resistor, which is R in this diagram—you have a capacitance that may run up to 30 μf .


WILL—I see. And that capacitance is made up—I suppose—from the capacitance between the plate and the various other electrodes in the tube, plus the wiring capacitances?

KEN—Pretty good! All you've left out is the input capacitance of the following tube—between the grid and cathode of the picture tube, or (if you are feeding into the second of two video stages) the grid and cathode of the following amplifier.

WILL—H'm-m, with all these parasitic capacitances, the reactance at 4 mc would be less than a couple of thousand ohms. That means if we use a 100,000-ohm load resistor, same as in radio—all the higher frequencies would be shorted around it, and the high-frequency gain would be zero. So we lose all the highs—I mean detail—on our image.

KEN—Fine. You've analyzed the causes of the trouble, so you shouldn't have much trouble supplying a remedy?

WILL—Well, I suppose we'll just have to throw away some more efficiency. So, we'll have to cut the load resistor down to a value that's comparable to the reactance of C at the highest frequencies the amplifier will have to handle. But—if we cut R down to 2,000 ohms or so the gain will be pretty low. With such a low resistance, we're going to need a lot of plate current to get any gain at all! So our tube will have to be a pretty powerful one. . . .

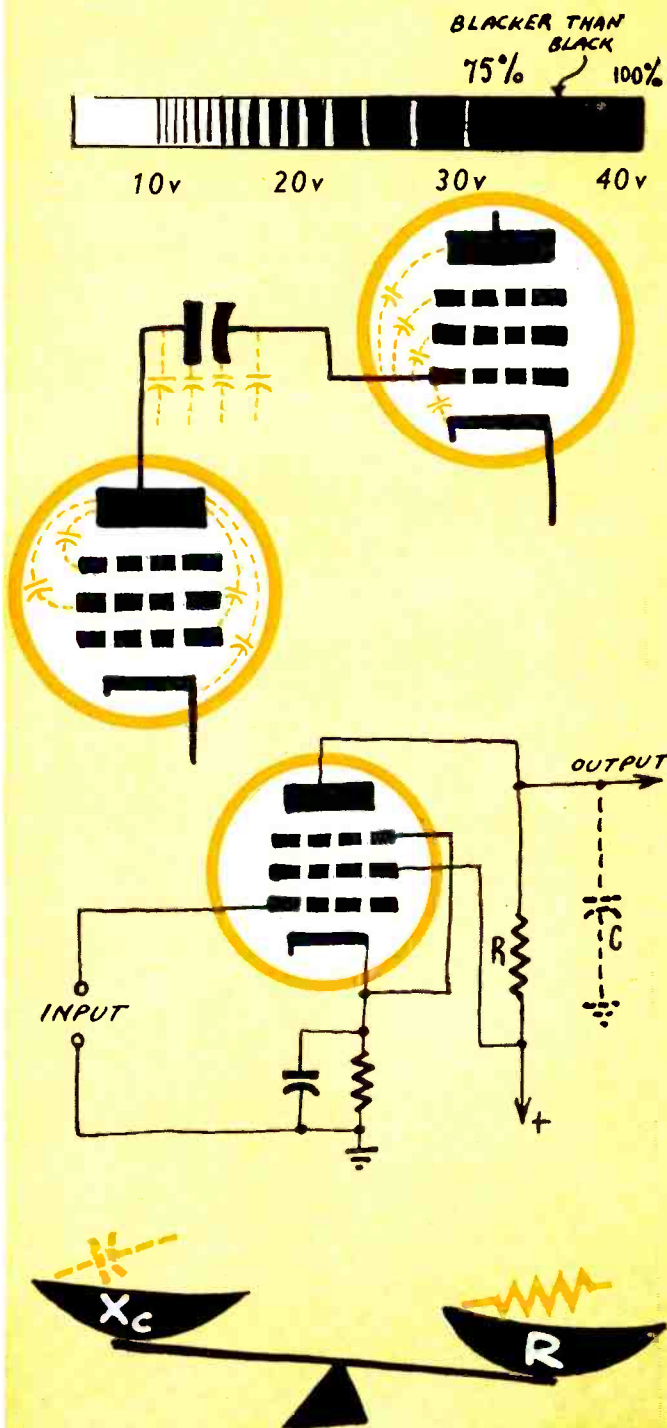

KEN—You're right all the way! As with the r.f. and i.f. amplifiers, we need a tube with high transconductance. The gain is—under these conditions—practically equal to the product of the transconductance and output impedance of the amplifier.

WILL—Then TV is based on waste all the way down the line! We invent remarkable special tubes, then use them at a fraction of their possible amplification, damp our tuned circuits, cut down our load resistors . . . ! What a life! !

KEN—Don't worry, Will. The main thing is to get enough signal at the output. In spite of all the inefficiency and low gain we usually manage to do that.

Improving the response curve

WILL—I'm thinking along radio lines, as usual. So I wonder why we can't help out our high-frequency response with some kind of "treble boost" that will accentuate the higher frequencies?

KEN—A good question! And the answer is—they *do* use such a "boost" on all receivers. The job is done with small inductors, placed either in series or parallel with the parasitic capacitance, or in both positions. In *parallel* compensation, the winding L1 is placed in series with the load resistor R, as you see. When the value is correct, the response in the high-frequency direction is considerably improved.

WILL—I suppose L1—together with the stray, or parasitic, capacitance—is tuned to the high frequencies you want to reinforce. Then its impedance increases a lot at those frequencies and is added to load resistance R, so the apparent plate load (and therefore the stage gain) will be higher over a small range of frequencies in the upper video range?

KEN—That's just about it. In fact, it's even a bit better, for L1 neutralizes the effect of the parasitic capacitance and to some extent therefore increases the plate load over the whole range of frequencies. And we can get the same result—or even a little better one—by *series peaking*. A winding L2 is placed in the output circuit of the stage in such a way as to divide into two parts (C2 and C3) the parasitic capacitance. In some cases L2 may be shunted across the resistor of the same order of resistance as R. The coil is often wound right on the resistor.

WILL—The circuit looks like a low-pass filter.

KEN—That's just what it is, but it has a very high cutoff point. But to be really valuable as a filter, the capacitances C2 and C3 should be in a certain ratio. And of course—with these wild capacitances—it's pretty hard to be sure of anything. . . .



WILL—Didn't you say a while ago that we could combine both types of compensating circuits in a single video amplifier stage?

KEN—I did. And a combination of series and parallel peaking really does do the work! It gives you an excellent response curve, and permits an increase of gain by further increasing the value of R. But all the elements must be carefully calculated and precisely adjusted.

WILL—Effective, eh? Can you use these circuits on two-stage video amplifiers, too?

KEN—Of course. But isn't it getting a bit late? Suppose we continue our studies some other time.

TO BE CONTINUED

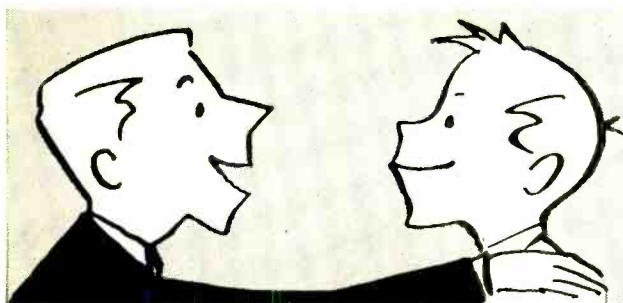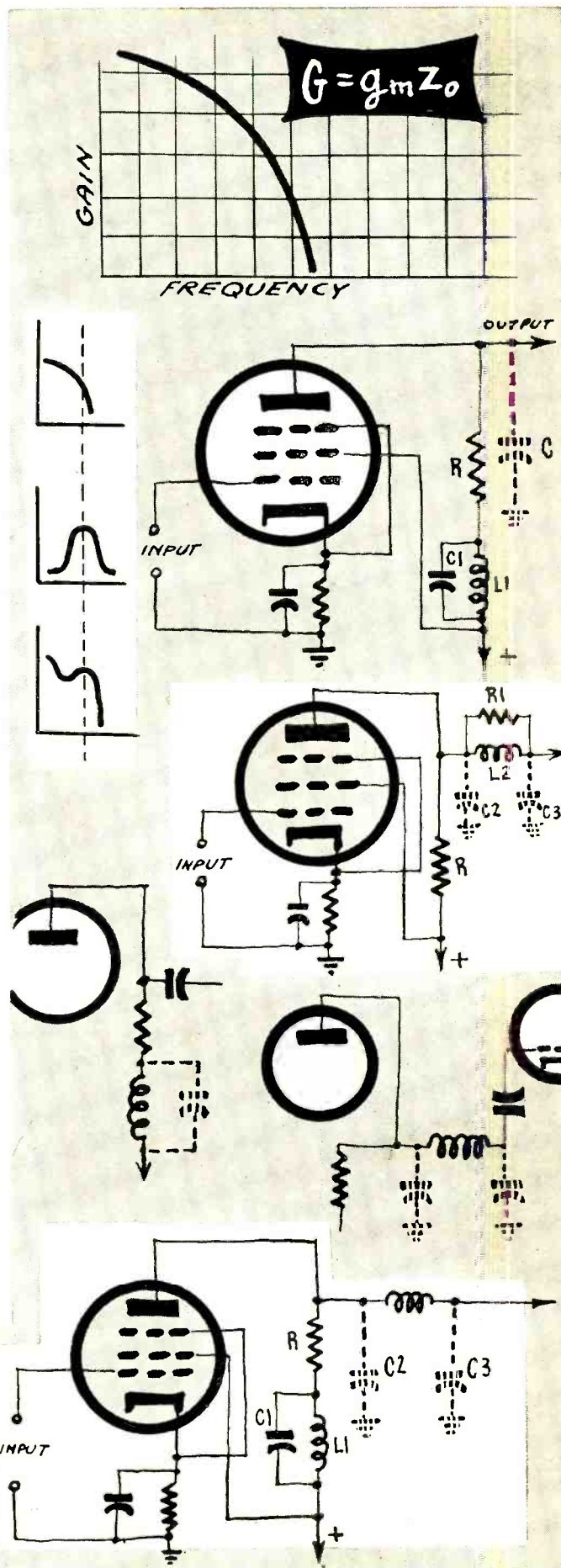

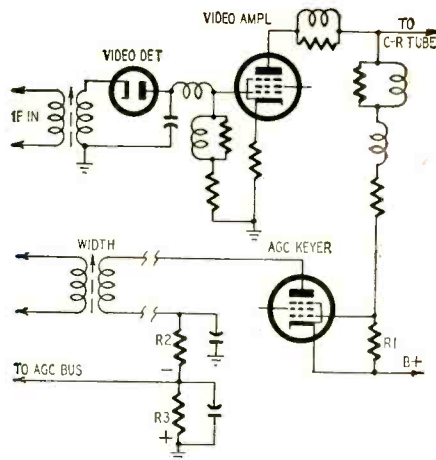
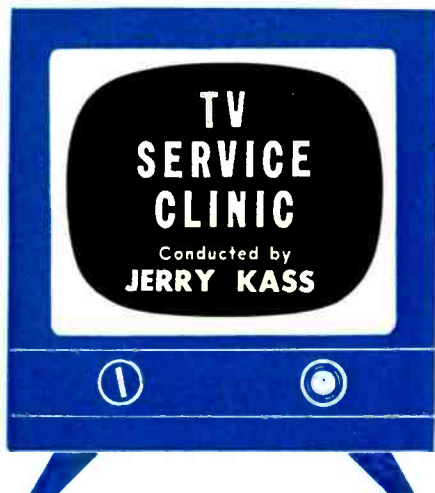


Fig. 1—Basic keyed a.g.c. circuit.

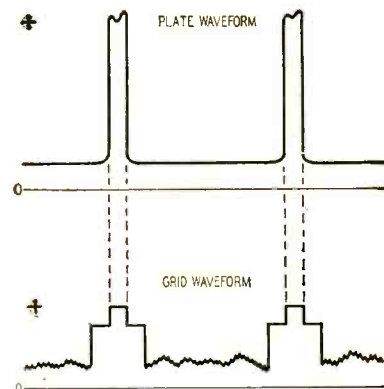


Fig. 2—Waveforms on the a.g.c. keyer.

THE purpose of a.g.c. in a TV receiver is to vary the gain of the r.f. and video i.f. amplifiers to maintain a constant signal level at the input to the video amplifier. By feeding the rectified i.f. signal into a special circuit that develops a negative bias voltage in proportion to the strength of the signal, and then feeding this negative voltage to the grids of the r.f. and video i.f. amplifiers, a constant-amplitude signal can be obtained.

Under normal conditions, a simple a.g.c. circuit will provide satisfactory operation—under difficult conditions, it falls short. The standard a.g.c. circuit is a slow-moving affair. It must rectify the video i.f. signal and filter it to obtain a d.c. voltage. Because of the relatively long vertical pulses, the a.g.c. filter must be capable of smoothing out signal components as low as 60 cycles. Such a circuit would obviously not follow a signal rapidly varying in strength.

The principal enemy of the simple a.g.c. circuit is noise—especially in areas where the signal-to-noise ratio is low. Noise usually appears as sharply peaked impulses that are amplified and rectified along with the signal. A prolonged noise condition acts the same to a simple a.g.c. circuit as an increase in signal strength and will therefore increase the negative a.g.c. bias and further weaken a usually already weak signal. Another troublemaker is airplane flutter, a series of increases and decreases in signal strength caused by signal reflections from an airplane in flight. Since this can occur at a frequency of over 100 cycles, most simple a.g.c. circuits cannot smooth out this variation and the result is a continuous overload and fading on the picture screen.

The solution might seem to be faster-acting a.g.c. filter circuits. However, among other problems, a fast-acting filter circuit could not filter out the broad vertical pulse—the pulse would appear as an increase in signal strength, increasing the a.g.c. bias and decreasing the amplitude of the sync pulse, making synchronization difficult.

The solution to these problems lies in a fast-acting a.g.c. circuit known as keyed a.g.c. In this system the a.g.c. bias will be determined not by the entire signal, but only by the horizontal sync pulses in the complete video signal. Any noise occurring between pulses will have no effect on the a.g.c. bias, and noise occurring during the pulse will have little effect because the pulse represents the maximum transmitter signal strength. The a.g.c. action can be made very fast because the vertical pulse will not appear as a wide pulse to the keyed tube. Fig. 1 shows a basic keyed a.g.c. circuit.

Keyed a.g.c.

Most commonly, a pentode such as the 6AU6 is used as the keyer tube. Its control grid is fed the composite video signal with positive-going sync from the video amplifier. In addition, to maintain the d.c. component of the signal, the control grid is direct-coupled to the plate of the video amplifier. The cathode is connected to some point slightly more positive than the control grid to make the grid slightly negative with respect to the cathode. This is frequently done simply by connecting these elements across part of the video amplifier plate-load resistance. The voltage drop across this resistor (R1) is such that the tube is held at cutoff except when a positive horizontal sync pulse appears at the grid.

The plate is at ground potential except at those times (15,750 cycles per second) when it is fed a positive pulse of approximately 300 to 500 volts from the horizontal output circuit—usually from a winding on the width coil. Since the plate-voltage pulses on the keyer tube are in sync with the positive-going horizontal sync pulses on the control grid, they appear simultaneously (Fig. 2) and the keyer tube conducts (is "keyed"). The plate current flow of the keyer develops a negative voltage across load resistors R2 and R3. This voltage, directly proportional to the sync-pulse amplitude, is fed to the a.g.c. controlled r.f. and i.f. stages.

Only the 15,750-cycle horizontal frequency need be filtered so the a.g.c. can have a much shorter time constant than simpler types. This fast action permits the circuit to follow and compensate for rapid changes in signal strength.


The value of the plate keying pulse is not critical. Since a pentode is used as the keyed a.g.c. tube, a great amount of amplification is obtained. And as in all pentodes, plate current being fairly independent of plate voltage, the a.g.c. bias is controlled entirely by the peak amplitude of the horizontal sync pulses applied to the control grid of the keyer tube. The sync pulse is used for this purpose because, whereas the video modulation continually varies, the sync pulses are transmitted at a constant amplitude. Only a change in signal strength would vary the amplitude of the sync pulses.

Trouble-shooting

The complexity of servicing a keyed a.g.c. circuit can be seen from the number of other circuits involved. Aside from the keyer circuit, there is the video amplifier feeding the grid-cathode circuit, the horizontal output circuit feeding the keyer plate, and the various r.f. and i.f. circuits being fed a negative bias from the keyer output.

As an example, it might seem that one of the essentials of proper keyed a.g.c. action, that of simultaneous positive grid and plate voltages, would be automatic. Yet, if the horizontal oscillator is out of sync, the horizontal plate pulse will not occur at the right time, and proper a.g.c. voltage will not be developed. The same trouble can occur with a poorly operating a.f.c. circuit, since this circuit has considerable control over the horizontal oscillator.

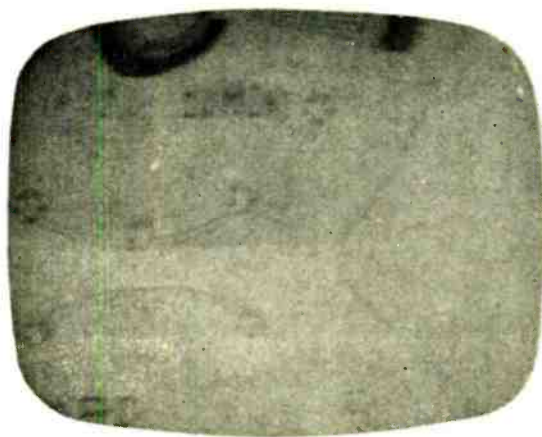As a rule, a poorly operating keyed a.g.c. circuit will produce too much or not enough a.g.c. voltage. As a result, the following defects are most commonly seen: excessive, insufficient, or varying contrast; snow; airplane flutter; poor horizontal and vertical hold; poor noise immunity, and picture overload.



Courtesy Du Mont
 Fig. 3—Poor contrast, snow, and poor sync may result from excessive bias.

A common cause of overload is keyer-tube failure. The heater may be open, cathode emission low, the a.g.c. winding on the width coil open, or some other defect may lower the a.g.c. voltage. This will frequently cause the overloading of an i.f. or video amplifier tube and cause the screen to go blank or a negative picture to appear. If the overload takes place before the sync take-off, it will also result in poor horizontal and vertical synchronization. When replacing a width coil be careful of the polarity of the windings—incorrect polarity will also cause a negative picture.

Another cause of overload is the improper adjustment of the a.g.c. control. If readjustment does not help, place a potentiometer across a 9-volt battery, connect the center arm to the a.g.c. line, and use this as the negative a.g.c. bias. Some receivers have convenient test points, others require that the a.g.c. line be opened and still others that the keyer tube be removed. Set the potentiometer for the manufacturer's recommended bias voltage and observe receiver operation under proper bias voltage. If a scope can be used to observe the keyer grid, plate, and filter waveforms, troubleshooting will be that much quicker. If the trouble is due to a circuit defect in the a.g.c. line, setting the proper bias voltage should clear the picture. If trouble persists despite normal a.g.c. bias, it is usually safe to turn your attention to another circuit. Before applying battery bias, be sure the a.g.c. line is not short-circuited to ground.

Much the same procedure can be used to check excessive bias that causes snow and poor contrast, and poor sync stability. (See Fig. 3.) This could be caused by a decrease in the keyer bias causing excessive plate current flow in the keyer. This is often caused by a low-emission video amplifier resulting in too small a voltage drop across the keyer input resistor R1. This resistor is a critical factor in proper a.g.c. action. If it varies in value, it will cause considerable changes in bias volt-

age. Equally critical is the plate current flow through this resistor. Both should be checked carefully.

The keyed a.g.c. circuit is a frequent cause of poor interlace. A defective filtering component will allow horizontal sync pulses to appear on the a.g.c. line where there should be only d.c. This upsets normal vertical synchronization and destroys proper interlace. Trouble of this nature can usually be checked by placing a scope on the a.g.c. line.

In cases of fading, always check for components that are varying in value.

Tuner alignment

I was recently called upon to service a General Electric receiver having a model U.H.F.-70 tuner. Besides a position for continuous tuning, this unit has two fixed u.h.f. positions. I tried to adjust these positions without success. According to the manufacturer's instructions it is necessary to turn the oscillator and r.f. cores a given number of turns from some starting point. Since other technicians had previously adjusted this tuner, I have no idea of what position the cores are in and therefore cannot adjust them. The continuous tuning on this u.h.f. unit works perfectly, so I am sure that the only thing wrong is the fixed-channel adjustments. Is there any way I can correct this condition?—G. L. C., Springfield, Ill.

Although the original "count" has been lost there is an alternate procedure for aligning this unit. Set the u.h.f. selector to one of the fixed positions and turn the u.h.f. oscillator tuning core counterclockwise until the slotted end of the core is flush with the first turn of the coil.

Be sure the core is flush with the first turn and not the coil form. If the core is unscrewed too far, it will be difficult to start into the coil again without cross-threading.

From this starting point, slowly turn the oscillator tuning core clockwise into the coil until a u.h.f. picture and sound signal are received. While turning the oscillator core clockwise into the coil

several minor responses as well as two strong picture responses will be noticed. Use the first strong response received while turning the core clockwise from its starting point. While turning, be careful not to exert heavy pressure on the core—the coil damages easily.

Now adjust the r.f. tuning core for maximum picture signal. Then readjust the oscillator core so that the fine-tuning control on the TV receiver will permit tuning in audio bars. Be sure you can tune away from any adjacent-channel interference.

Picture and sound loss

I am servicing a Meck receiver that apparently has a bad tuner. I get a raster but no picture or sound. I would like information on replacing the existing tuner with the Standard cascode tuner. There is no model number on this receiver, but the circuit checks with the Meck XQA.—H. S., Cleveland, Ohio

You mention that the tuner is bad but do not state how you came to this conclusion. If this receiver is similar to the XQA model, it is an intercarrier receiver and the sound take-off is at the video amplifier. The lack of picture and sound (with the raster present) could be caused by a defective tube or circuit in the tuner, the video i.f. amplifiers, the video detector or the video amplifier. Thus, your idea of replacing the tuner to correct this trouble may not be the solution. If a defective tube or part exists in the video i.f. stages or the detector or video amplifier, the new tuner would be of no help.

The Standard Coil cascode tuner is supplied with complete schematic and installation instructions. You can find additional information on cascode tuners in previous issues of RADIO-ELECTRONICS: January, 1953, page 49; September, 1953, page 58; and January, 1954, page 43.

Arcing in picture tube


I recently got a brand new Stromberg-Carlson TV receiver. During the first week or so of operation there was considerable arcing in the neck of the picture tube, a 21FP4A. The receiver is model 421. I checked all voltages applied to the tube and found them to be of proper value. The odd thing about the arcing was that it interfered very little with the picture. I carefully checked all components in the various circuits feeding the picture tube elements and found them all in good condition. Now after a couple of weeks, the arcing has stopped. The picture is fine but I wonder if anything has been damaged that will show up at some later date.—S. M., Buffalo, N.Y.

The arcing in the 21FP4A during the first week of operation is due to the presence of loose particles in the neck of the tube. They work their way into the gun structure and cause the arcing. When these particles are burned out, the arcing stops. This will rarely cause permanent damage. END


sine-wave square-wave generator

Instrument features a wide frequency range and extremely stable output

By FRANK J. DiELSI

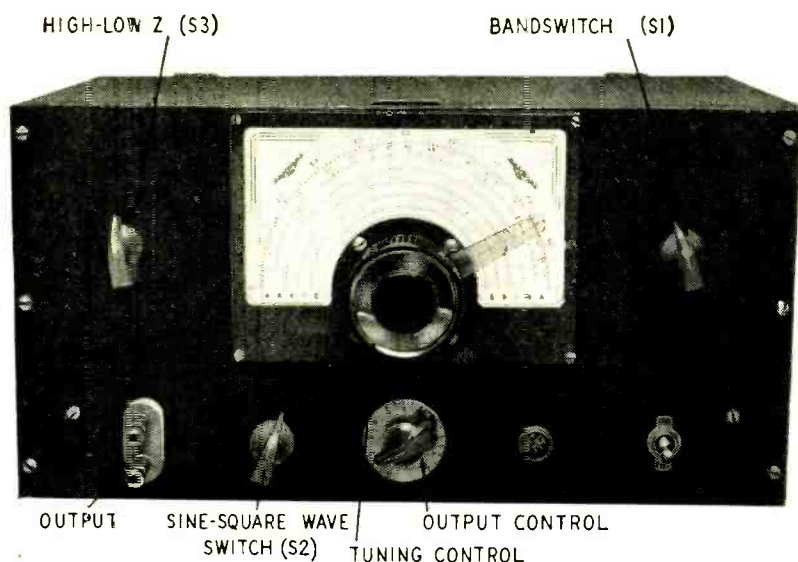

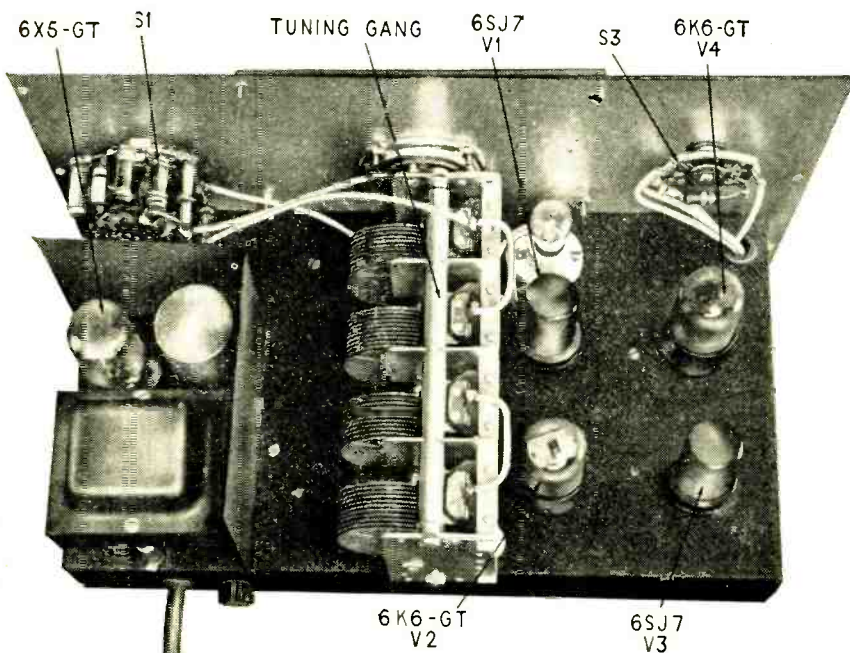This instrument produces both sine and square waves, and has a frequency range from 20 to 200,000 cycles.



Top view of the sine-wave and square-wave generator. The frequency-determining resistors are on bandswitch.


THE generator described in this article is a versatile and dependable instrument that can be used for testing audio amplifiers, video amplifiers and sweep circuits as well as in many other applications. Although compact and inexpensive, it has a stable output within ± 0.43 db over its wide range with sine- and square-wave output at either low or high impedance. The sine-wave output—in four bands of 20-200, 200-2,000, 2,000-20,000 and 20,000-200,000 cycles—has less than 0.8% distortion. The low-impedance sine-wave output is 5 volts; the high-impedance 21 volts. The square wave has a rise time of less than 2 microseconds in the three ranges of 20-200, 200-2,000 and 2,000-20,000 cycles. The peak-to-peak square-wave amplitude is 23 volts at low impedance and 92 volts at high impedance.

Circuit

The oscillator is a two-stage wide-band amplifier using a 6SJ7 (V1) and a 6K6-GT (V2) with the output coupled through a modified Wein bridge to the input. The frequency-determining arms of the bridge (in band 1 position) consist of R2 in series with two of the parallel sections of a 4-gang tuning capacitor, and R1 shunted across the other two sections. A 4-gang broadcast tuning capacitor with 440 μf per section is used to get 880 μf in each variable arm of the bridge, thus obtaining plenty of overlap on all bands.

To prevent distortion and unstable output the oscillation amplitude is controlled by the negative feedback arms of the bridge consisting of R3 and the 3-watt 120-volt lamp. This lamp in the cathode return of V1 serves as a bias resistance that increases very rapidly with a small increase in oscillation amplitude, thus increasing the inverse feedback and maintaining the output essentially constant.

The output of the oscillator is coupled to a two-stage amplifier consisting of a 6SJ7 (V3) and a triode-connected 6K6-GT (V4). This amplifier isolates the oscillator section from the load. For square-wave output, S2 removes the inverse feedback to V3 and also shorts out its cathode bias resistor, causing it to clip the sine wave of the oscillator section and produce a very steep-sided and flat-topped square

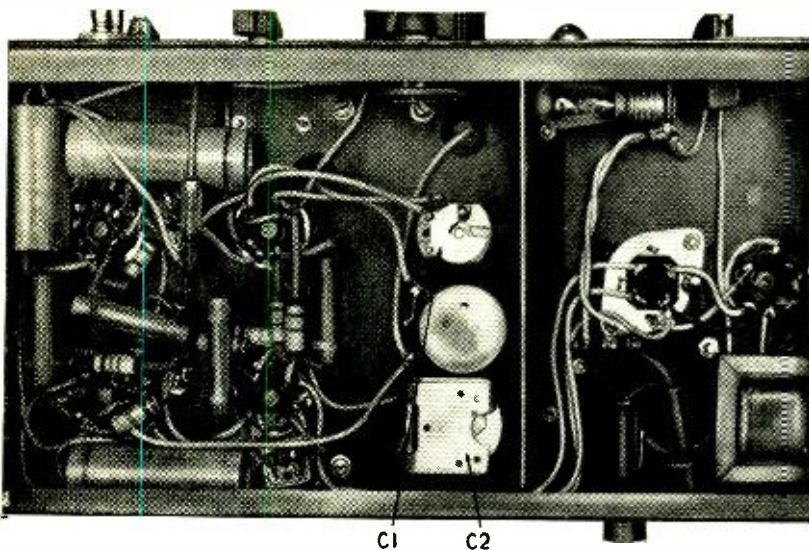

Underchassis view. Note shield between the power supply and signal circuits.

wave. The response of V3 is greatly improved by omitting the screen bypass capacitor.

A high- or low-impedance output may be selected with S3. The high-impedance output is taken across the 2,500-ohm plate load resistor of V4. For low-impedance output V4 is used as a cathode follower, with an output impedance of 340 ohms. When used as a cathode follower, the plate load resistor of V4 is not shunted-out since this would remove the inverse feedback to V3 and cause overloading and excessive distortion of the sine-wave output. Resistor R4 is included in the circuit to reduce the sudden surge of charging current of C4 when switching from low to high impedance with square-wave output. A 500- μ f cathode capacitor (C3) with a reactance of only 15 ohms at 20 cycles and a 40- μ f plate coupling capacitor with a reactance of 190 ohms at 20 cycles are used to pass the low frequencies.

Construction

The instrument is enclosed in a 7 x 12 x 8-inch cabinet. The layout of the

components can be seen in the photographs and is not too critical except that the power supply—including the a.c. switch, fuse, pilot light, and filament wiring—should be shielded. The 4-gang tuning capacitor must be insulated from the chassis and panel.

The band-determining resistors are mounted directly on the lugs of the 2-pole 4-position bandswitch.

Parts for generator

Resistors: 2—10,000, 2—100,000, 2—510,000, 2—1 megohm, 2—10 megohms, 1/2 watt; 2—510, 1—3,300, 1—4,700, 1—10,000, 2—51,000, 1watt; 1—4,700, 2—10,000, 1—27,000, 2—51,000, 2—100,000, 2 watts; 1—2,500, 1—10,000, 10 watts; 1—5,000, 1—10,000, potentiometer.

Capacitors: 1—50 μ f, 1—.002 μ f, mica or ceramic; 2—0.5 μ f, paper, 400 volts; 1—20-20-20 μ f, 2—40 μ f, 450 volts, electrolytic; 1—500 μ f, 25 volts, electrolytic; 1—100 μ f, 1—400 μ f, 1—4-gang 440- μ f-per-section, variable.

Miscellaneous: 2—6SJ7, 2—6K6-GT, 1—6X5-GT, tubes; 1—power transformer, 600 volts ct @ 30 ma, 6.3 volts @ 2 amps; 1—filter choke, 30 h @ 30 ma; 1—3-watt 120-volt G-E lamp (type S-6); 1—socket for lamp; 5—sockets for tubes; 1—pilot light and holder; 1—1-amp fuse and holder; 1—2-pole 4-position switch; 1—s.p.d.t. switch; 1—d.p.d.t. switch; 1—s.p.s.t. switch; 1—line cord; 1—output jack; 1—chassis; 1—cabinet; 1—dial face (National SCN or equivalent).

On the front panel a National type SCN dial is used for the tuning control. In the lower left corner of the panel next to the output terminals is sine-square switch S2. Output control R5 is directly below the tuning knob. Output impedance switch S3 is to the left of the main dial and bandswitch S1 is at the right.

Calibration


The instrument should be enclosed in the cabinet before attempting any adjustment because the large frame of the tuning capacitor is at grid potential and will pick up any stray fields in the room.

If the band-determining resistors are selected within 1% accuracy, the dial needs to be calibrated on only one band since all the other bands have the same 10-1 ratio frequency calibration. If extreme accuracy is not essential, the exact resistances are less important than matching the corresponding pairs such as R1 and R2. The resistors may be selected from 10% tolerance stock and matched with a good ohmmeter.


Adjust trimmer C1 for uniform output over the 20-200-cycle band with feedback control R3 set as low as possible without causing loss of oscillation. If R3 is set too high, excessive sine-wave distortion will result. Trimmer C1 is used to balance out the frame-to-ground capacitance of the tuning capacitor which is across the other arm of the bridge. If constant output cannot be obtained, another 3-watt 120-volt lamp should be tried.

Variable screen bypass capacitor C2 can usually be set at approximately half capacitance (200 μ f). If difficulty is experienced with the dial-calibration tracking of the higher-frequency bands 3 and 4 as against 1 and 2, C2 can be adjusted to make bands 3 and 4 fall in line. This capacitor compensates for the high-frequency phase shift caused by tube and stray capacitances. After C1 and C2 have been adjusted, the generator may be calibrated by comparing its frequency with the power-line frequency or other standards on an oscilloscope.

END


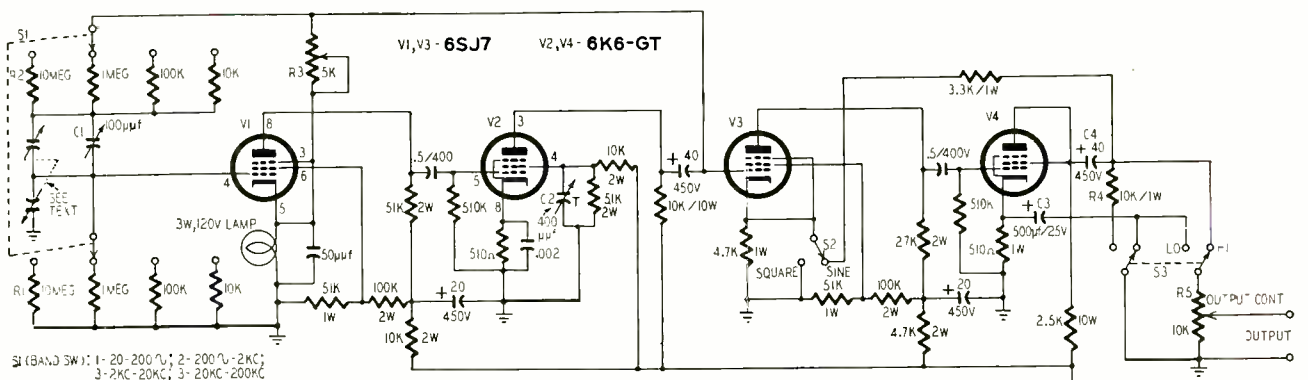


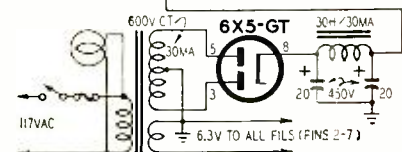As the schematic above shows, the sine-wave square-wave generator is a reasonably simple wiring job.



SAVE TIME with TEST EQUIPMENT

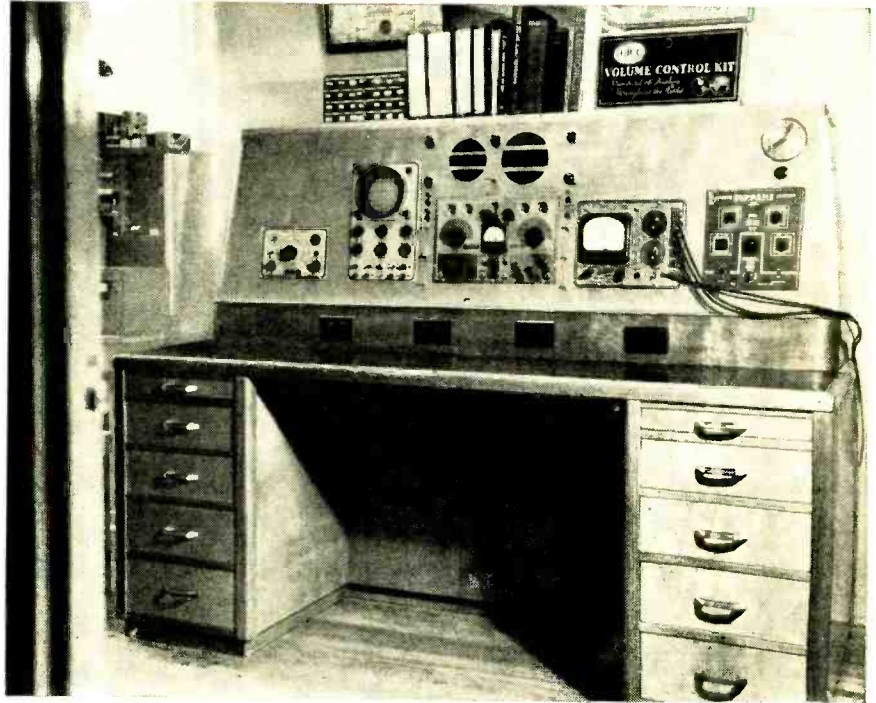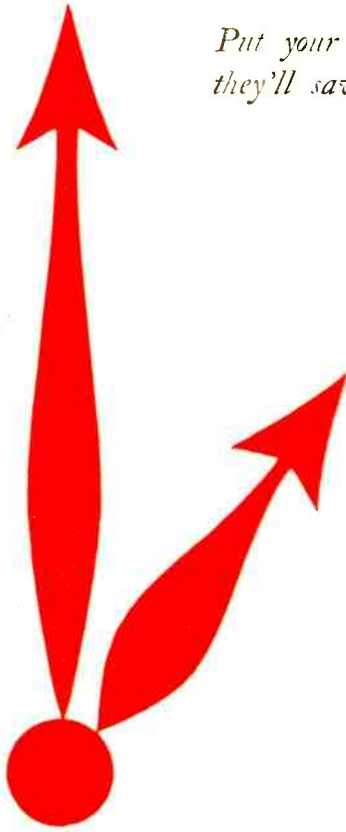*Put your instruments to work—
they'll save you time and money*



By EDWARD M. NOLL

A well planned service bench assists the technician in the use of equipment.

MANY a technician has learned to manipulate oscilloscope controls with great skill the first day the unit was placed in front of him, but one year later he knows no more about how to use this scope than he did the first day. At the same time an apparently awkward beginner who perhaps required days before he could adjust a scope properly has become a marvel by continuous practice.

All of us feel awkward, slow, and at times skeptical when we put a new piece of test equipment into operation. We do not always recognize that skill, speed and effectiveness grow with time and practice. Like a beginner on skates, you are slow and wobbly—but that doesn't mean you can't become a fast, successful operator. In any technical field, it isn't how quickly you learn that matters, but how persistently you grow into the skill, care and speed that marks the master.

Let us assume that to acquire skill we must try to make extensive use of our test equipment. Locate the equipment properly because *how often you apply test equipment depends on how convenient it is to use*. Certainly, if the test unit is hidden in a closet or on a

shelf a few feet overhead, it will not be used frequently.

The bench arrangement should be such that all equipment is close at hand without interfering with work on a chassis. It should be placed at the rear or side of the bench work area so that the leads are always convenient for speedy attachment to a chassis. The equipment should not, of course, be so positioned that it can get in the way and make the actual bench work awkward. No matter what the arrangement, it must be so planned as to keep the test equipment out of the way but still convenient to use.

A common complaint of the technician regarding the use of test equipment is that it takes so long to connect and disconnect. This is not the fault of the equipment *but the fault of the bench arrangement*. A bench should be planned so that within 5 minutes after placing a chassis on it, the equipment can be connected and ready to use. If it requires 15 to 30 minutes to put your test equipment into operation, your arrangement is inefficient.

Applications

There are applications for test equipment in every section of a television re-

ceiver. It is our responsibility to learn these applications and how we can use the equipment to speed adjustment, alignment and repair work, and thus render a better caliber of service.

Successful use of test equipment is a function of three factors—what can be done with test equipment, how to do it, and what precautions to take in doing it.

Of the many uses for test equipment in the repair and adjustment of a tuner, the three basic ones are:

1. Measurement of supply voltage points.
2. Measurement of local oscillator grid voltage, and test for mixer grid injection.
3. Response curve of tuner.

In most tuners it is simple to locate the supply voltage sources. When the tuner remains inoperative after tube substitutions, check all supply voltage points with a v.t.v.m. The next step, if these voltages are normal, is to connect the v.t.v.m. to the grid of the local oscillator to see if proper negative voltage is developed, indicating oscillation. In some cases the oscillator is functioning but no excitation reaches the mixer, so the v.t.v.m. can also be attached to the mixer grid to determine

if proper oscillator injection exists.

The response curve of a tuner tells all about its operation. The effect of tube replacement in terms of sensitivity and frequency response can be easily seen. If the bench arrangement has been planned properly it should require only a few minutes to obtain the tuner response curve. Once the curve can be seen, the choice of tube replacement becomes definite. For example, if the local oscillator is weak on the high band and a new tube is substituted, there will be an immediate increase in the amplitude of the tuner response curve. Likewise, the replacement of the r.f. amplifier or mixer tube will influence the response curve and show up a weak tube—with more certainty than any tube checker or picture observation.

Watching the response curve during tube replacement not only indicates the tuner sensitivity but also any change in bandwidth and its influence on frequency response and interference rejection. The response curve on each channel should be watched carefully as tuner changes are made. This applies particularly in a fringe area where there is adjacent-channel interference or impulse noise disturbances because the response curve shows the tuner's ability to reject interference without affecting the resolution of the picture.

The TV tuner is a compromise device because it must function on so many channels spread over a wide frequency range. Consequently, we do not obtain an ideal response on each channel and there are certain departures from the ideal pattern (Fig. 1). In observing the response pattern on any given

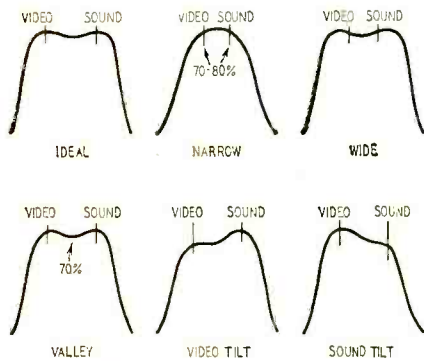


Fig. 1—TV tuner response limits. The curves are drawn to different scales, the distance between the two vertical markers being 4.5 mc in all the cases.

channel, be certain that the response departures do not exceed the specified limits of the tuner. In fact, slight touch-up of the alignment adjustments on the tuner can help to favor a particular channel. When the signal is weak or accompanied by a great deal of interference, it is advisable to use as narrow a pattern as possible without disturbing the frequency response.

Test equipment precautions

It is necessary to consider two factors very carefully, if test equipment is to be of any use to you. First—is the align-

ment equipment functioning properly, and second—is it connected correctly? If these two points are overlooked, use of the equipment may be a waste of time, or worse.

To obtain the response pattern indicated as typical by the manufacturer of a given receiver it is, in most all cases, necessary to connect the alignment equipment and tuner in exactly the manner recommended in the service notes. Failure to do so may cause the equipment setup itself to distort the pattern. If an attempt is made to obtain a correct pattern, it will be impossible to do so or a poor alignment will result that can hurt receiver performance.

The sweep signal generator should be linear in two ways to obtain a good response pattern—the amplitude of the output over the swept range and the frequency deviation on each of the given channels. This linearity should exist over the entire range of output levels from strong signal to weak signal. Oscilloscope sensitivity should be such that when a sweep signal output comparable in strength to a received TV signal is applied, a usable deflection is obtained. Signal level and a.g.c. bias affect tuner performance, and it is always preferable to align a tuner at the approximate signal levels of your area.

A most important consideration in sweep alignment, and one taken far too lightly, is marker accuracy. Although it is possible to obtain a response pattern with the shape and amplitude indicated by the manufacturer, it is to no avail if it is shifted in frequency even a small amount. In fact, just a slight shift in the channel 3 response pattern (Fig. 2) because of inaccurate picture and sound carrier markers can cause the pattern to shift into the channel 2 or channel 4 spectrum. For example, if the pattern shift is on the high side of correct frequency, it means that we emphasize adjacent-channel interference from the picture carrier of the next highest channel and, at the same time, reduce the sensitivity of the tuner to the desired picture carrier frequency. An error of just half a megacycle could be detrimental. Thus for tuner alignment in fringe areas and areas troubled by adjacent-channel interference it is important to have accurate markers—either crystal-controlled markers or a marker generator that is calibrated with a crystal source.

U.h.f. devices

There are a number of applications for test equipment in the adjustment or repair of u.h.f. converters. In the newer u.h.f. units special test points are often included to permit attachment of a v.t.v.m. or sensitive current meter.

Key considerations in the efficient operation of a u.h.f. converter are proper local oscillator strength, proper crystal current, and proper oscillator injection. These three conditions can be checked with a v.t.v.m. For example,

with the v.t.v.m. connected at the crystal-current test point, the operation of the converter can be predicted

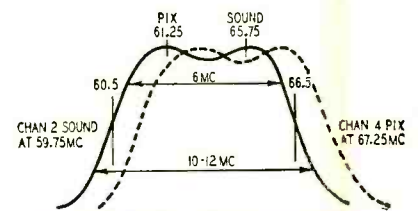


Fig. 2—Shift in the tuner response.

and the results of any changes observed. The crystal current is a function of the three factors mentioned—a low crystal current indicates a defective crystal, a weak local oscillator tube, or improper local oscillator injection. With the meter connected to the test point the crystal mixer can be replaced to check if normal crystal current returns. If the current reading is still low, the local oscillator tube should be replaced to check if it is weak. With the crystal current still low make certain that the crystal injection control, if present, has been set properly. When low crystal current still persists, there may be a defect in the local oscillator circuit. To check the local oscillator tube, connect the v.t.v.m. to the grid of the oscillator (to check strength of oscillation) and other supply voltage points to locate a possible defect.

Another consideration in a continuous tuning type u.h.f. converter is proper tracking over the entire u.h.f. band. Often tracking has to be adjusted when the local oscillator tube or crystal mixer is replaced. A simple method of checking the tracking of a u.h.f. converter is to connect a signal source to the input of the converter and a conventional v.h.f. field-intensity meter to the output circuit (Fig. 3). The v.h.f. field-intensity meter serves as a very sensitive output indicator and can be used to measure the weak u.h.f. harmonics of a standard v.h.f. signal source.

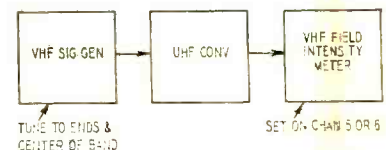


Fig. 3—Checking converter tracking.

If the v.h.f. fundamental signal source is set exactly on 175 mc, it produces a third harmonic at 525 mc, a fourth harmonic on exactly 700 mc, and a fifth harmonic on 875 mc. This fundamental frequency, therefore, produces a harmonic signal at the high-, center-, and low-frequency portions of the band (channels 23, 52, and 81). Make certain that the field-intensity meter reading is not the result of a harmonic of the v.h.f. local oscillator of the field-intensity meter itself. If the field-intensity meter is actually recording one of the harmonics of the v.h.f. signal source, the meter reading will fall away

TEST INSTRUMENTS

when the signal source is switched off temporarily.

Some manufacturers have been presenting sweep alignment data for their u.h.f. units. At present, service-type u.h.f. test equipment is not available but in a short time it is likely to become plentiful. There are a number of restrictions imposed on test equipment for u.h.f. alignment. The crystal mixer of the usual u.h.f. unit has a loss instead of a gain as compared to a vacuum-tube mixer. Thus the actual sweep indication is rather weak when the applied sweep signal is made comparable to a received signal amplitude-wise. As a result, the scope sensitivity must be high, and it is highly possible a special preamplifier will be constructed in the form of a probe to permit a good visual indication from

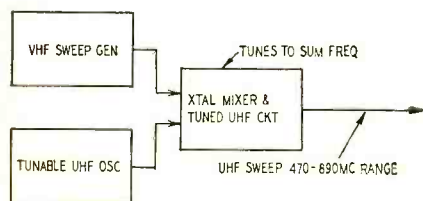


Fig. 4—Indirect u.h.f. sweep generator.

the very weak sweep signal that must be rectified to obtain the response pattern.

A recent method of u.h.f. sweep generation uses an indirect approach (Fig. 4). In this system the actual frequency deviation occurs in the v.h.f. range (can be a present v.h.f. sweep oscillator) and is mixed with a single-frequency, tunable oscillator set in the u.h.f. range. The sum frequency is utilized at the output of the mixer (generally a crystal mixer) to produce the u.h.f. sweep signal. Thus a single-frequency, but variable u.h.f. oscillator plus a crystal mixer stage can be constructed into a unit that operates in conjunction with a present v.h.f. sweep generator to form a u.h.f. sweep signal at its output.

Video i.f. response

There are four important reasons for using sweep alignment equipment when making any changes in the i.f. system of a television receiver:

1. A proper video i.f. response curve is necessary to minimize intercarrier disturbances.
2. With many new v.h.f. stations, higher-powered transmitters, and more sensitive receivers, adjacent-channel interference has become a problem in many areas. A proper video i.f. response curve is necessary to have maximum rejection at the adjacent-channel picture and sound carrier frequencies.
3. Circuit changes and even tube replacements can influence the video response curve and alter the picture quality in terms of resolution and development of i.f. transients.
4. The presence of color television receivers will impose stricter requirements

on alignment and all of us must become familiar with critical alignment techniques and future refinements. Slight departure in i.f. response can cause phase shift over the video-frequency spectrum that would go unnoticed on monochrome but will have a decided influence on the color picture. In fact, special circuits are planned for the video amplifier of a color receiver to correct for any departures in phase between various frequency components of the video signal. However, the correction can restore proper response for limited departures only in earlier stages. Likewise an improper response can cause the loss of color information and the color synchronization signal because they are positioned at the high-frequency end of the video range.

A set in the shop should always be checked in terms of the response of the tuner and video i.f. section. If the picture on a particular model appears a bit smeary, do not always jump to the conclusion that it is a matter of design. Often it is just a slight defect in alignment because of resonant-circuit drift or a tube has degraded in performance enough to hurt picture resolution without giving the customer any indication of loss in sensitivity (because of a.g.c. action). Remember it is a credit to your organization if you can take a receiver back to a customer and have him remark, "I've never seen the picture so clear before."

For video i.f. alignment, too, the need for accurate markers is becoming increasingly important. The video i.f. range is approximately twice as high in frequency as in earlier receivers and,

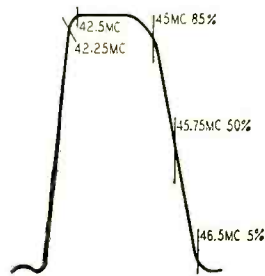


Fig. 5—Calibrated response curve.

consequently, the calibration of a marker generator is a more trying problem for the test equipment manufacturer. In the first place it is a higher frequency and more difficult to obtain even with the same percentage drift. In addition, the absolute permissible drift is the same as for the previously much lower i.f. Thus to maintain this absolute limit on drift the actual percentage of drift is less at the higher frequency.

Some method of crystal calibration of your marker generator is almost a necessity if you are to align and check alignment with accuracy. The importance of accurate alignment megacycle-wise is apparent from the actual response curves and their calibration as recommended by manufacturers (Fig.

5). The location of the picture carrier on the response curve has much to do with the resolution (particularly low-frequency response) and the stability of the picture in fringe areas or under severe noise conditions. The proper location of the sound carrier on the response curve determines how free of intercarrier buzz you can hold the receiver. The location of the adjacent-channel picture and the sound i.f. is important so receivers can be least sensitive to adjacent-channel interference. The over-all smoothness (freedom from humps and ridges) and the over-all bandwidth of the curve determines the resolution and freedom from transients.

In the usual stagger-tuned i.f. amplifier the individual resonant circuits are peaked using a v.t.v.m. at the video detector and a single-frequency generator at the input circuit. In a typical receiver (an RCA receiver's response curves are shown in Fig. 5) it is necessary to set the single-frequency generator on these various frequencies: 39.25, 41.25, 47.25, 43.7, 45.5, and 41.8 mc.

Tell me, can you set your signal generator dial on 43.7 mc accurately? Do you feel certain that if you can set it there that you obtain this frequency instead of 44 or 43 mc? *Crystal checkpoints should be a part of all marker generators.*

Sound i.f. section

A sweep generator, oscilloscope, and 4.5-mc crystal marker source are preferred alignment and repair equipment for the sound i.f. section. Again, this method presents conclusive evidence of sound-strip performance in terms of gain, frequency response, noise rejection, and intercarrier buzz rejection. The trend toward higher-fidelity audio systems in the television receiver places increasing importance on sound-drift performance in avoiding raspy sound and high background levels.


Though at times not as effective, a signal generator and v.t.v.m. can also be used to adjust the sound i.f. section. If other than a crystal-controlled 4.5-mc signal source is used, be certain to set the frequency as close to 4.5 mc as possible. Once set, do not move off this frequency until alignment is complete. For peak signal and minimum background noise the frequency demodulator, limiter, and i.f. amplifier center frequencies must be the same. This means there is highest gain and maximum noise rejection about the center frequency of the FM signal applied to the frequency demodulator.

Many receivers now in operation and many that have been repaired are not operating with the very best picture and maximum interference rejection. It is the use of test equipment that permits service far above average and, with an efficient bench arrangement, you will spend no more time per set than using a less critical repair technique. END

Something new and different in the way of tube checkers

VR TUBE TESTER

By JOSEPH F. SODARO

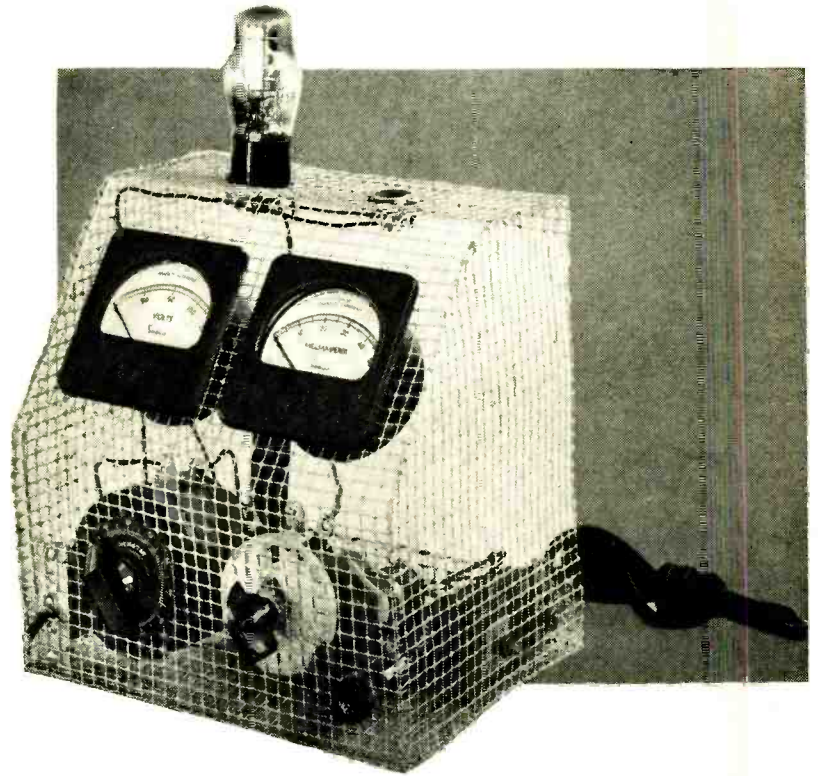

For illustrative purposes, the VR tester is built on hardware cloth.

It is often necessary to measure the operating conditions of a voltage regulator tube, especially when a circuit defect has caused excessive

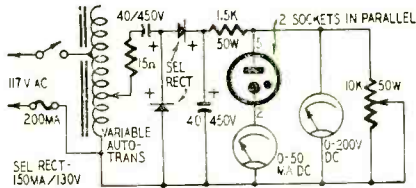


Fig. 1—Schematic of VR tube tester.

current flow through it. These measurements include determination of the striking or starting voltage as well as operating voltage across the tube, within the control current range.

The electrical characteristics of interest for the six popular types of VR tubes are listed in the table. The starting voltage is the voltage required to cause the tube to ionize. If this value is higher than normal, the source voltage may fail to reach the required value.

As a result, the tube will not ionize, and the voltage source will not be regulated.

Once ionized, the tube will pass more

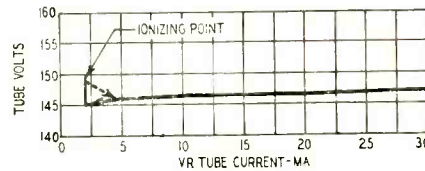


Fig. 2—Action of VR tube current.

or less current as the input voltage is increased or decreased, but the voltage across it remains constant. Similarly, tube voltage is constant as load current is increased or decreased. The VR tube current changes to accommodate load current change. Under normal operation a VR tube will regulate from the minimum to the maximum of its current rating, providing a wide range of voltage stabilization.

The VR tube tester is designed to

measure starting voltage and current, operating voltage, the current range over which the operating voltage is constant, and extinguishing current.

Manufacturers' data indicate that the supply voltage to the VR tube should be at least 30 volts higher than the average d.c. starting voltage to insure reliable starting throughout the normal tube life. Failure of a VR tube to regulate may be caused by too low a supply voltage, too much series resistance, or excessive load current.

Circuit of the checker

The tester circuit shown in Fig. 1 provides a variable source voltage for the tube under test to simulate line-voltage changes. It also provides a variable load to simulate load changes. Input voltage is adjusted by a small variable autotransformer, the output of which is rectified and filtered in a voltage-doubler circuit using selenium rectifiers. The variable load is a 50-watt rheostat capable of handling 70 milliamperes. The voltmeter and milliammeter have an accuracy of 2%.

A voltage doubler is used instead of

ELECTRICAL CHARACTERISTICS OF VR TUBES

Tube	Approx. starting volts D.C.	Min. Tube ma	Max. Tube ma	Approx. oper. volts	socket
0A3/VR75	100	5	40	75	Octal
0B3/VR90	125	10	30	90	Octal
0C3/VR105	115-135	5	40	105-108	Octal
0B2	115	5	30	105-108	Min.
0A2	155-156	5	30	150-151	Min.
0D3/VR150	160-180	5	40	150-153	Octal

Parts for VR tube tester

1—15-ohm, 1/2-watt, resistor; 1—1,500-ohm, 50-watt, resistor; 1—10,000-ohm, 50-watt, rheostat; 1—variable autotransformer, 165 volt-amperes (Powerstat, Superior Electric type 10 or equivalent); 2—40- μ f, 450-volt, capacitors (electrolytic); 2—selenium rectifiers, 150 ma, 130 volts; 1—200-ma fuse, and holder; 1—milliammeter, 0-50 d.c.; 1—voltmeter, 0-200 d.c.; 1—s.p.s.t. switch; 1—octal tube socket; 1—miniature tube socket; 1—chassis (see text).

TEST INSTRUMENTS

a simpler half-wave circuit, to provide for testing 150-volt tubes. At a load current of 150 milliamperes—the current limit for the rectifiers—the output from this supply exceeds 200 volts. The circuit is fused for 200 milliamperes. The maximum load current obtainable when the load is short-circuited is 150 milliamperes for normal a.c. line voltage. Tube sockets to accommodate the VR tubes are wired in parallel, but of course only one tube can be tested at a time.

Construction details

Hardware-cloth chassis construction was used for simplicity and to show internal construction of the prototype. Dimensions of the prototype are: 8 inches wide, 6 inches deep at the base, 8 inches high at the rear and 3 inches deep on top. The lower portion of the front panel is 4 inches high, and the slanting panel is 5 inches in length.

The line switch, fuse holder, Powerstat (autotransformer), and load resistor are mounted on the lower front panel. Both meters are mounted on the slanting panel. The tube sockets, located on the top are octal and 7-pin miniature types.

The rectifiers are all mounted on the right side of the chassis, and the

filter capacitors are mounted on the bottom. The a.c. line enters from the rear and is brought to the fuse holder and a tie-point.

Operation

To operate the VR tube tester turn the autotransformer control to zero and the load rheostat to maximum resistance. Put the VR tube to be tested in the socket, and turn the power on. Slowly advance the autotransformer control while observing the voltage and current to the tube. The striking voltage for a good tube is reached at a value higher than the operating voltage shown in the table. At this point the tube ionizes, voltage drops to the operating value, and tube current increases to approximately 5 ma.

Continue to increase input voltage until maximum tube current is reached. Throughout this input voltage change, the tube voltage must remain constant to indicate satisfactory operation. The operating voltages in the table are approximate. As a result, this measurement may vary from tube to tube. In most applications the operating voltage is not critical provided the voltage is constant both for input and for load changes.

Next, increase load current by de-

creasing the rheostat resistance. As the load takes current from the tube, output voltage should remain constant until the minimum ionization current for the tube is reached. The tube will lose control as ionization ceases and the tube voltage will decrease. The data from the test of an 0D3/VR150 is shown in Fig. 2. As the supply voltage was increased to 146 volts, the tube current rose to 2 ma and remained constant until the voltage increased to 149 volts. At this point the tube ionized completely, the tube voltage dropped to 146 volts and tube current increased to 4.5 milliamperes. This portion of the curve is shown dashed because the changes occurred instantaneously, and data could not be taken between these points. From 4.5 to 30 milliamperes the tube voltage increased gradually to 147 volts.

As load current increased, tube current decreased along the same curve with tube voltage decreasing to 146 volts at 4.5 milliamperes. A further increase in load current caused the tube voltage to decrease gradually as the tube was extinguished. This action is shown by the lower left-hand portion of the curve.

This VR tube tester will be of great value to the technician working with regulated power-supply circuits. END

Compensated Headphone Circuit

By GEORGE D. PHILPOTT

WHEN connecting a headphone jack to the secondary of an output transformer, it is common to load the transformer with a resistor across the terminals of the jack. By connecting a moving-coil load to the jack, in place of the resistor, headphone fidelity can be improved.

A speaker voice coil when moving and cutting lines of force reflects counter-e.m.f. back to the transformer—and to any reactive unit (headphones) on the line.

To visualize this counter-e.m.f., consider negative feedback such as exists when a voltage is fed to a point 180° out of phase with it. In effect, this is just about what goes on in the output

circuit of an audio amplifier when voice-coil movement—and counter movement—reflects self-generated currents back to the output stage. The “damping factor” of the amplifier output tube enters the counter-e.m.f. picture—with regard to harmonic and subharmonic tendencies of the stage. Voice-coil counter-e.m.f. affects a changing plate impedance by varying the primary inductance of the output transformer, giving a hint of why a nonlinear plate load might offer better harmonic cancellation than a linear (resistor) load.

In other words, a moving-coil impedance used across the terminals of low-impedance headphones, such as Signal Corps HS-33, or Army-Navy type ANB-H-1's, tends to bring out the lows, lowers harmonic distortion by improving the damping factor of the output tube, and in general allows for more pleasing tone reproduction.

As shown in Fig. 1, a small PM speaker that has been replaced because of a defective cone, but which has magnet and voice coil intact, can be used for constructing a moving-coil load for your headphone hookup.

Remove the damaged cone, using speaker solvent or a razor blade. Leave the small strips of cone supporting the voice-coil leads. With tinsnips, cut off the outer cone support, as shown. This leaves you the voice coil, magnet, and spider (centering) assembly. Make sure that the voice coil is in good shape—not rubbing the pole piece, open, or

with the windings loose. Mount the assembly, preferably inside the receiver cabinet, and run leads from there directly to the headphone jack (Mallory A-3-A or equivalent), connecting as shown in Fig. 2.

High-impedance headphones may be used across the low-impedance secondary of the output transformer, but more satisfactory results are obtained when they are connected in place of the output transformer's primary winding or across it.

When connecting *any* headphone on the plate side of the output stage, it is advisable to change the plate bypass capacitor, or at least make sure that

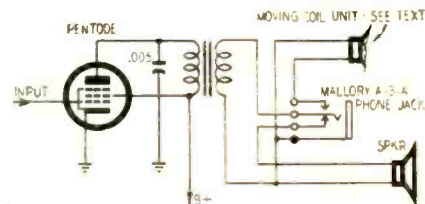


Fig. 2—How the circuit is hooked up.

it can withstand a voltage surge of 600 or higher. These capacitors were not calculated to stand the unusual peak voltage imposed on them by circuit making and breaking. They have a nasty habit of shorting out soon after the initial jack installation—usually when phones are being plugged in or withdrawn from the jack. A 1,600-volt capacitor did a beautiful job. END


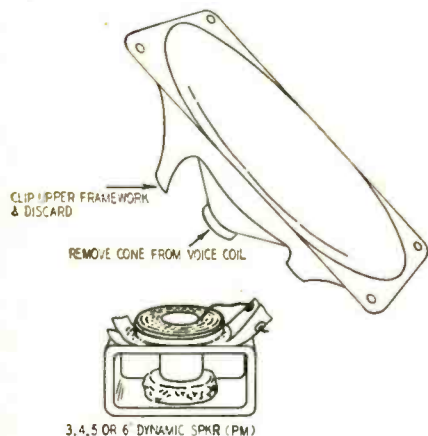


Fig. 1—Mechanical details of the unit.

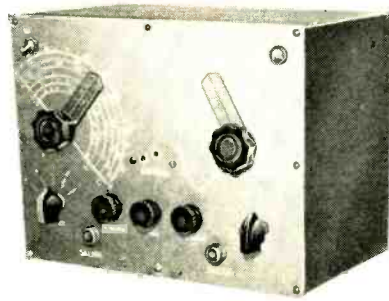
*Inexpensive
instrument
has many
applications*



At left—The finished generator. Decals and lacquer give it a professional appearance. Below—Top view of the equipment gives a good idea of the layout.

SIGNAL GENERATOR

By A. J. GALOFRE

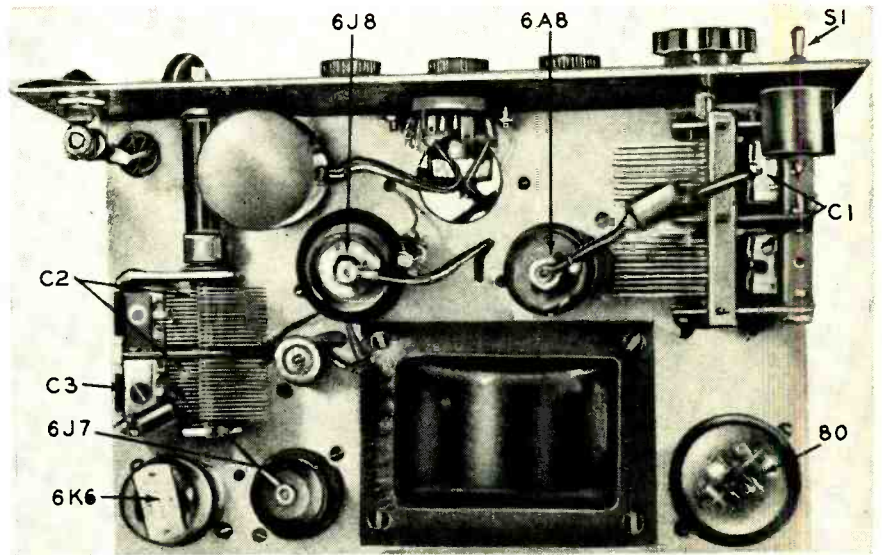

CONSIDERING the many applications of this multipurpose signal generator, its components are simple and its cost is indeed low. Its value also lies in the combining of many test functions in one instrument, which saves both space and time.

The signal generator was primarily designed for the alignment of stagger-tuned video i.f. amplifiers where closely separated signals are needed (the 630 requires 21.8, 25.3, 22.5, 25.2, and 23.4 mc).

Instruments sufficiently accurate to provide these small frequency differences are usually beyond the average technician's pocketbook. In this multipurpose signal generator the r.f. and crystal oscillator signals are mixed and provide a continuous tone with crystal accuracy.

A block diagram of the a.f.-r.f. signal generator is shown in Fig. 1. An interesting circuit feature is found in the 6J8 where a common grid connects the crystal oscillator with the 6A8 oscillator circuit. The complete schematic dia-

gram is shown in Fig. 2. Switches S1 and S2 control the functioning of r.f. and a.f. oscillators. Removing the crystal will of course prevent the crystal oscillator from functioning.

The r.f. signal generator uses a 6A8 operating as a transitron oscillator. It furnishes a stable frequency at high output. A single set of coils are all that is needed, and bands are changed with

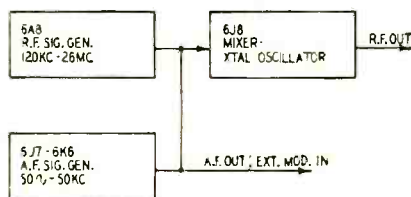


Fig. 1—Block diagram of the generator.

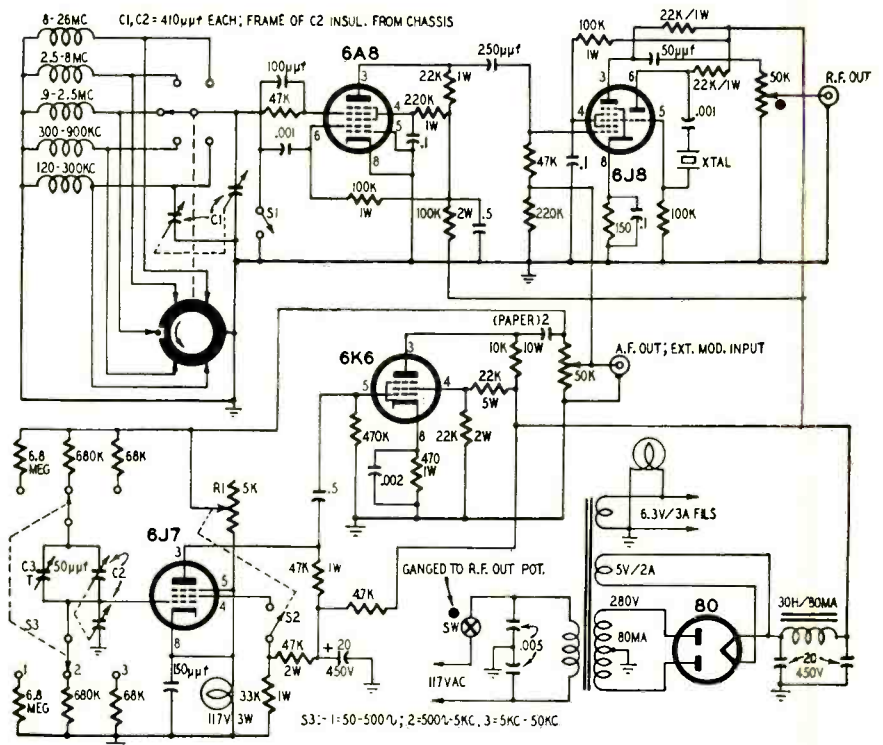


Fig. 2—Schematic diagram of the multipurpose a.f.-r.f. signal generator.

TEST INSTRUMENTS

a 1-gang, 5-position selector switch.

When the crystal is removed from its socket the 6A8 r.f. signal is fed to the r.f. output terminal, with or without modulation, and the instrument is used as a standard signal generator.

The crystal oscillator uses a Pierce type circuit and works as well with crystals of 7 and 14 mc. I have not tried it at other frequencies, but I believe it is flexible enough to cover a wide range of frequencies. Closing switch S1 permits the instrument to operate as an independent crystal oscillator, with or without modulation.

The a.f. signal generator provides three bands: 50 to 500 cycles, 500 to 5,000 cycles, and 5,000 to 50,000 cycles. The three bands provide a sufficient range for radio and TV servicing. As a TV bar generator the instrument will supply frequencies of 600 and 157,500 cycles, providing 10 horizontal and vertical bars. Resistor R1 is variable from the front panel and is used to control the a.f. wave shape. For stable oscillation, R1 is adjusted for maximum feedback.

Operation

The r.f. and crystal signals are used together to obtain highly accurate signals for the alignment of video i.f. amplifiers. To illustrate, suppose we

want to obtain a signal of 23.4 mc. We make the following adjustments:

Crystal oscillator	14.0 mc
R.f. generator	9.4 mc

Sum	23.4 mc
-----	---------

Assuming the crystal frequency to be highly accurate, any possible error is limited to a deviation of the 9.4 mc signal. Any error is bound to be less than if the r.f. generator was tuned directly to 23.4 mc.

If greater accuracy is desired, the following combination might be used:

Crystal oscillator	14.0 mc
R.f. generator	2.3 mc

Difference	11.7 mc
Second harmonic	23.4 mc

In this case, we may assume the 23.4 mc to be completely accurate. Let us suppose that the error in the 2.3 mc is 2% or .046 mc. Multiplying this by 2 because we are dealing with the second harmonic, we obtain .092 mc, an error of only .004% of the desired frequency, 23.4 mc.

Occasionally it is difficult to pick out the desired harmonic. To solve this problem, the i.f. amplifier to be used should first be roughly adjusted with the i.f. signal taken directly from the r.f. oscillator with the crystal out of the circuit. The instrument also will

supply markers for sweep-generator alignment.

I constructed this instrument, as much as possible, out of spare parts in my workshop. It is built in a 6 x 9 x 11-inch case. This proved to be a little small, so I advise using a case at least 20% larger. I used decals for the panel

Parts for signal generator

Resistors: 1—150, 1—4,700, 2—47,000, 2—68,000, 1—100,000, 1—220,000, 1—470,000, 2—680,000, 2—6.8 megohms, 1/2 watt; 1—470, 2—22,000, 1—33,000, 1—47,000, 2—100,000, 1—220,000, 1 watt; 1—22,000, 1—47,000, 1—100,000, 2 watt; 1—22,000, 5 watt; 1—10,000, 10 watt; 1—5,000 (with on-off switch), 1—50,000, 1—50,000 (with on-off switch), potentiometers.

Capacitors: 1—50 μ f, 1—100 μ f, 1—150 μ f, 1—250 μ f, 500 volts, ceramic; 2—0.001 μ f, 1—0.002 μ f, 2—0.005 μ f, 3—0.1 μ f, 2—0.5 μ f, 1—2.0 μ f, 400 volts, paper; 1—20-20-20 μ f, 450 volts, electrolytic; 1—50 μ f, trimmer; 2—15 to 467 μ f, 2-gang variable (1 with insulated rotors).

Miscellaneous: 1—6A8-GT, 1—6J8-G, 1—6J7, 1—6K6-GT, 180, tubes; 1—power transformer, 560 volts c.t. at 80 ma, 6.3 volts at 3 amps, 5 volts at 2 amps; 1—filter choke, 30 henries at 80 ma; crystals; 1—lamp, 117 volts, 3 watts; 1—chassis and cabinet; coils covering 120 kc to 26 mc; sockets for tubes and crystal; 1—s.p.s.t. switch; 1—pilot light and assembly; 1—1-gang, 5-position switch.

printing, and added a thick layer of transparent lacquer to get a commercial appearance. I have used this signal generator for some time, and am highly satisfied with it. END

NEON-LAMP TEST SET

THE neon lamp is versatile and inexpensive. It can regulate and indicate voltages, it can oscillate and can show the presence of light, X-rays, and other radiations. This circuit (Fig. 1 from U.S. Patent No. 2,682,636 issued to Jerome Brewer of Kansas City, Mo.) combines many useful functions of a neon lamp into a single instrument, simple enough to be used as a classroom demonstrator of electronic principles.

The line voltage (d.c. or a.c.) is applied as shown. This voltage is stabilized by a pair of 150,000-ohm resistors and neon lamp LM1. The regulated output is available at the VOLTAGE OUTPUT terminals.

Lamp LM2 is fed by two voltages in series. One is the drop across R2. This should be approximately 50-60 volts and is insufficient to ignite the lamp. This

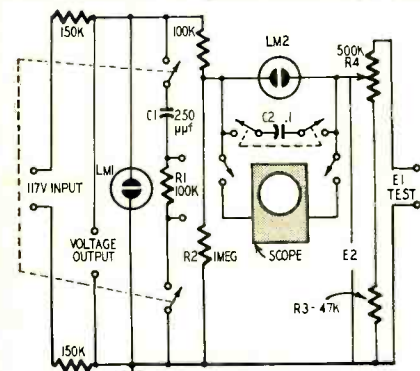


Fig. 1—Versatile neon lamp circuit.

constant voltage should be measured with a v.t.v.m. as it must be known accurately. The other voltage is E2. As R4 is increased, a point is reached at which LM2 ignites. (On a.c., both plates of the lamp glow; on d.c. only one.) At this instant the voltage across LM2 is approximately 65 volts a.c. or 80 volts d.c., the ignition potential of a neon lamp. (For highest accuracy, the exact ignition value for LM2 may be measured.) If the drop across R2 is known, so is E2.

Potentiometer R4 can be calibrated to indicate values of E1 at the TEST terminals for any setting at which LM2 begins to glow. This can be done by applying known values for E1, adjusting R4, and watching LM2 for glow.

This voltage measurement consumes no power from E1, because LM2 passes no current until the correct setting of R4 is reached. After this, LM2 glows and conducts—this does not matter. The measurement has been completed.

If E1 is a.c. and has the same frequency as the line, it should be connected in phase with the line. Thus the two

voltages add across LM2. In any case, when LM2 flashes, it indicates the peak sum of these voltages.

The circuit becomes an oscillator when 100 volts d.c. is applied at E1, the line disconnected, and C2 is switched in. A sawtooth wave is generated. The frequency depends upon values of C2, R2, and R3, as well as the lower portion of R4 which varies the frequency. The wave may be inspected, or the frequency measured, by switching in an oscilloscope.

With the power line connected as shown and 30 volts d.c. fed in at E1, radiation may be detected. If R4 is set so that LM2 is just below the ignition point, when light, X-rays or radioactive excitation falls on LM2, it breaks down.

The circuit in Fig. 2 illustrates an invention (patent No. 2,682,637) that is a division of the patent previously described, and is based on it. Line voltage E1 is regulated by LM1. A fraction of it (E2) is delivered by the potentiometer. If E2 is in phase with unknown voltage E3, these will add across the neon lamps.

To measure an unknown voltage between 10 and 80 (E3), only one neon lamp is needed—LM3 and LM4 are shorted out. When LM2 glows, the voltage across it is 65 volts a.c. or 80 volts d.c. If E2 is known (from the potentiometer calibration), so is E3.

To measure higher voltage, other lamps are switched in. Each lamp represents an additional 65 volts a.c. or 80 volts d.c. END


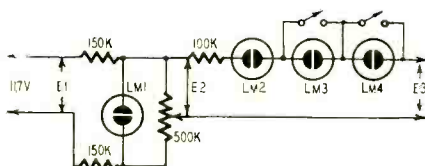


Fig. 2—Adaptation of Fig. 1 patent.

By DON KETCHUM*

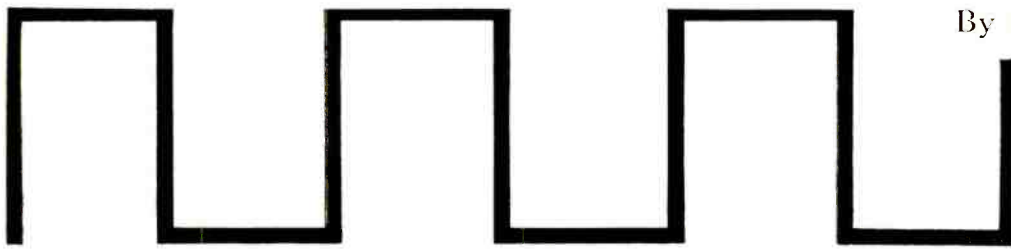

SQUARE WAVES : \$1.00

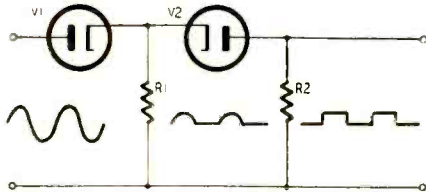


Fig. 1—Basic diode clipper circuit.

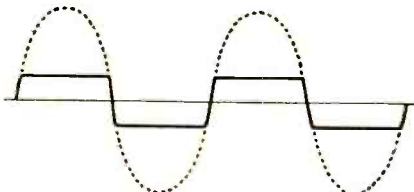


Fig. 2—Output waveform of Fig. 1.

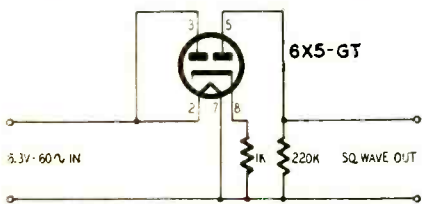


Fig. 3—Generator circuit using 6X5-GT.

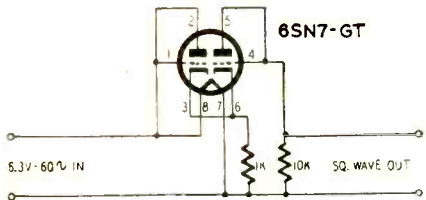


Fig. 4—Generator circuit using 6SN7-GT.

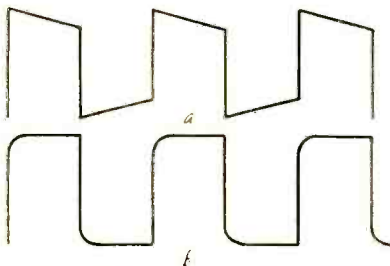


Fig. 5-a—Poor low-frequency response; 5-b—poor high-frequency response.

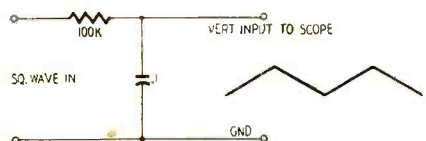


Fig. 6—Basic integrating network.

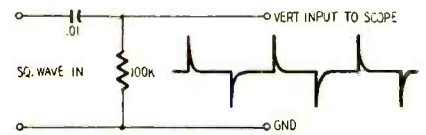


Fig. 7—Basic differentiating network.

FEW service shops have a square-wave generator, possibly because of its high cost and infrequent use. Yet a simple square-wave generator may be built very cheaply—for \$1.00 or so if the junk box contributes. It is good enough not only to demonstrate some basic concepts of circuit theory but also may be valuable for checking the frequency and phase response of amplifiers.

This particular device is really not a generator at all, but a dual clipper. It consists of two diodes that clip off the positive and negative peaks of a sine wave, leaving a remarkably true square wave. As shown in Fig. 1, a sine wave applied across the input terminals will allow V1 to conduct on positive half-cycles, resulting in the waveform shown across R1, the negative half-cycle being cut off. This waveform is then applied to V2 which will conduct only on the negative half-cycle, cutting off the positive portion of the sine wave. At first thought it may appear that if both half-cycles were cut off, the output would be zero or just a straight line; but a diode will conduct slightly with zero volt on the plate. (By actual measurement on a 6X5-GT a current of about 0.4 ma was observed.) This means that not quite all of each half-cycle was cut off; the result, the square wave shown in Fig. 2 appears across R2. (We didn't believe this either, but it works!—*Editor*)

With 6.3 volts r.m.s. input (about 18 volts peak-to-peak) a square wave measuring about 0.3 volt peak-to-peak is obtained. This means that about 59/60 of each half-cycle is cut off, leaving a square wave with almost vertical sides.

The actual circuit of our 60-cycle square-wave generator is shown in Fig. 3. It uses a 6X5-GT. A 6SN7-GT may be used as shown in Fig. 4. Both work equally well. All that is needed is a 6.3-volt 60-cycle source that furnishes both the heater power and the sine wave.

Using square waves

Square waves have a distinct advantage over sine waves in testing amplifiers for phase and frequency response. To pass a square wave with very little distortion the amplifier must have constant gain over a band of frequencies

from less than 1/10th of to over 21 times the square-wave frequency. Both audio and video amplifiers can be checked by using square waves of the proper frequencies. If the amplifier has poor low-frequency response, the flat tops of the square wave will be tilted (Fig. 5-a). If the high-frequency response is poor, the leading corners of the square wave will be rounded (Fig. 5-b). This can be demonstrated by connecting the output of a square-wave generator to the vertical input of an oscilloscope. With the square wave appearing on the oscilloscope, connect a .05- μ f capacitor across the output of the square-wave generator, and the waveform will appear as in Fig. 5-b, showing loss of high frequencies. To obtain the waveform of Fig. 5-a, remove the shunt capacitor and connect a .005- μ f capacitor in series with the lead from the square-wave generator to the vertical input of the oscilloscope. This results in low-frequency loss.

TV sync circuits

Sync pulses in television work are forms of square or rectangular waves. The horizontal and vertical pulses are separated by resistor-capacitor networks called differentiating and integrating circuits. The principles involved can be demonstrated easily. The circuit shown in Fig. 6 is an integrating network and responds to the horizontal or flat portion of a square wave—the part where the voltage is constant. This circuit gives a triangular wave shape.

If a square wave is applied to a differentiating network (Fig. 7), the output consists of short pulses produced by a change in voltage. The pulses are the vertical sides of the square wave. The polarity of the pulses depends on whether they are formed by a leading or lagging edge of the square wave.

Many electronic circuits operate on the principle of resistor-capacitor response to voltage changes. A better understanding of these principles can be obtained by building the simple circuits shown and observing the waveforms that can be produced.

References


- TV Troubleshooting and Repair Guidebook, Volume 2 by Robert G. Middleton, Chapter 3.
- Heathkit Technical Application Bulletin No. 1-C, 5-A, and 5-B by Louis E. Garner, Jr.
- Basic Electronic Test Instruments by Rufus P. Turner. Pages 219-222.

*Instructor, American TV Labs of California, Hollywood, Calif.

ELECTRONIC HEADPHONE

Baby tending and actor cueing are but two of many uses for this vest-pocket transistor receiver and midget transmitter


By JOHN A. IRWIN and I. QUEEN

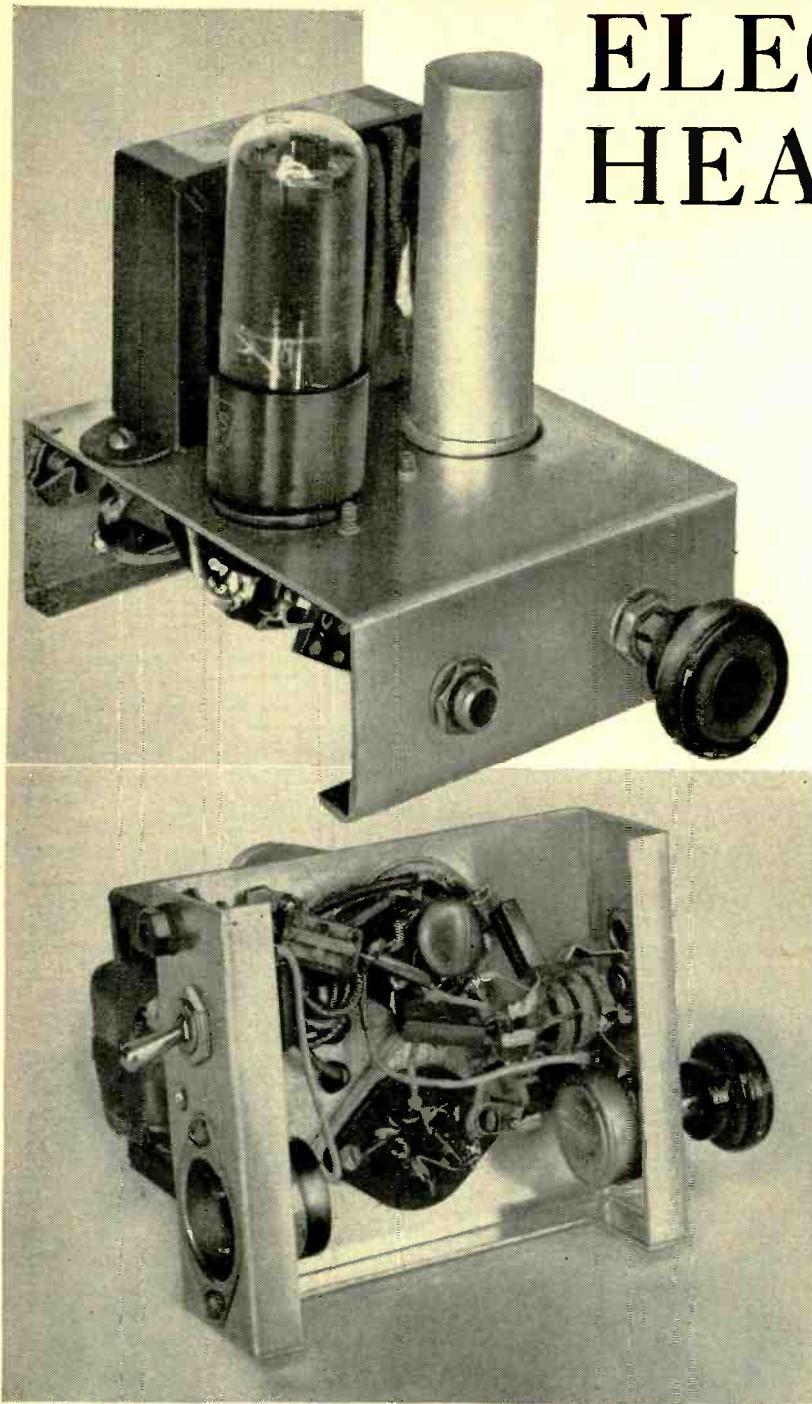

Top, the one-tube transmitter—unit tunes between 1.5 and 1.8 mc. Center, underchassis view of transmitter. A single 117L7 is used. Right, the receiver, containing a single audio frequency stage.

THERE are times when some way of transmitting a radio signal a short distance to a small or inconspicuous receiver may be very useful. The first application that comes to mind is a cueing or prompting device for actors. Such apparatus (which can be very costly) is often used by magicians or "mentalists."

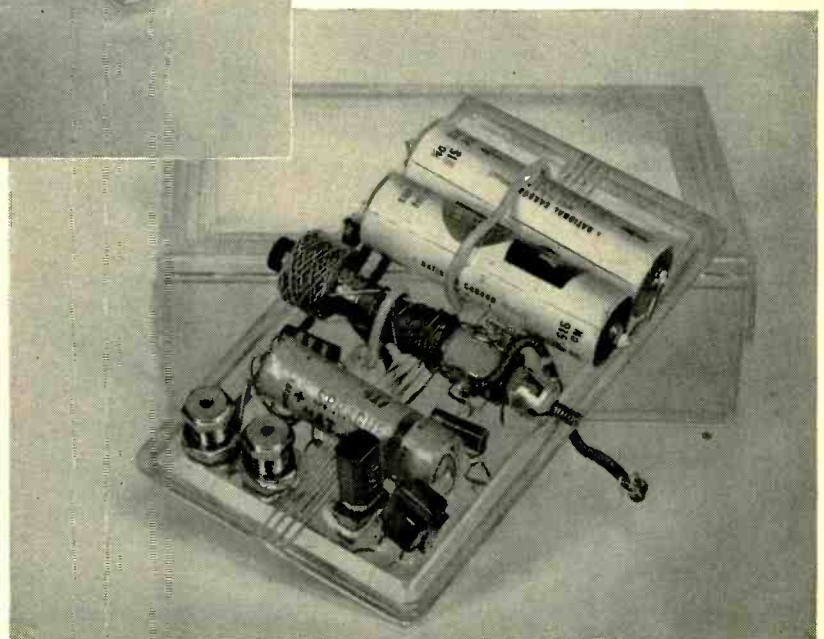In the home such equipment may be used to hear radio or phonograph music without disturbing other persons in a room. (True, the listener could wear headphones, but they would limit his movements and the long leads would be



a safety hazard.) In some cases this transmitter-receiver combination might even be used as a radio "nurse," with the advantage that the mother could move from room to room without getting out of the "nurse's" range.

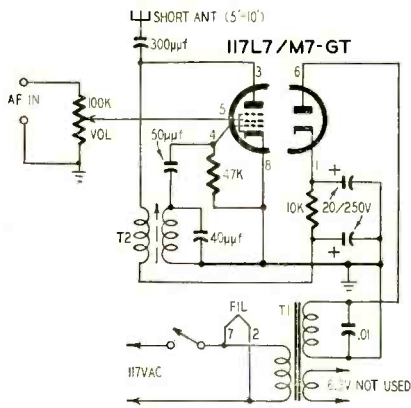


Fig. 1—One-tube transmitter. Isolation transformer reduces shock hazard.

A 117L7 tube (actually called a 117L7/M7-GT) makes a fine oscillator for the transmitting end. Its filament requires 117 volts which may be supplied directly from the line, avoiding the need for a 6.3-volt transformer. This tube has, in one envelope, a diode and a pentode. The diode is used as line rectifier (Fig. 1). The pentode is the oscillator tuned to the high end of the broadcast band or slightly above. The oscillator will work without isolation transformer T1, but its use is definitely recommended. It prevents a shock hazard when the chassis (or any other normally grounded point) is touched. The transformer may be any small unit delivering up to 150 volts at a few milliamperes.

The pentode screen is not returned to B plus as might be expected, but to ground. It is varied about 1 volt above and below ground potential by the modulation input.

Typical modulation sources are: speaker voice coil (working out of a radio, phono, or tape machine amplifier), FM or AM tuner, crystal pickup, high output mike. In any case the signal amplitude should be about 1 volt or more.

The oscillator tunes between 1.5 and 1.8 mc. The iron core of oscillator coil T2 controls the frequency. Adjust it while listening in on a near-by broadcast or all-wave receiver. Any unoccupied channel is recommended. Use as short an antenna as possible for the receiver used. If the antenna is too long, you may create radio interference over a wide area. With a 5-foot antenna on an ordinary home-type radio receiver, you should be able to hear the oscillator signal 20 or 30 feet away.

A simple portable receiver is shown in Fig. 2. It is a crystal set followed by an audio-frequency stage. The detector is a CK707; it was found more efficient than the usual 1N34. The amplifier uses a CK722 junction tran-

sistor, although a CK721 provides still more gain. Two penlight cells power the transistor.

With this receiver, signals are audible several feet from the oscillator. Thus if the "transmitting antenna" is strung across the ceiling of a small room, the signals will be heard over most of it. A small antenna, perhaps a foot or two, may be added at the receiver if necessary. Of course the *Superloop* (at the receiver) should be tuned to the same frequency as the oscillator. Adjust the iron core of the *Superloop* for maximum output.

The receiver uses such tiny components that the chief problem is mounting them. In the photo shown, parts are mounted on a plastic sheet. Leads are passed through small holes drilled in the plastic. Thus the parts are held in place by their own leads. All soldering is done under the plastic sheet. If desired, each part may be held in place with polystyrene cement. When completed, the plastic subchassis is put inside a plastic box to protect it. This may be a cigarette case, for example, which can be carried in a shirt pocket.

The *Superloop* is an antenna coil now available in most radio stores. It has an adjustable iron core. The tap is not used here. The coupling transformer is manufactured by Gramer. It is a tiny unit only 11/32 x 3/8 x 3/8 inch and weighs only a fraction of an ounce.

If your oscillator uses an antenna from 5 to 8 feet long, this receiver will pick up its signals 3 or 4 feet away. With an antenna 15 feet long, the effective range is nearly doubled,

and so on. The length of antenna you

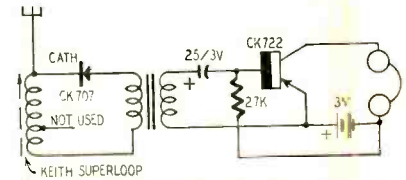


Fig. 2—Schematic of the receiver.

may use depends upon your location. If you live in an apartment house, your antenna must be a very short wire. Otherwise you may hear from your neighbors or even the FCC.

Parts list for transmitter

1—10,000 ohm, 1—47,000 ohm, 1/2 watt, resistor; 1—100,000-ohm potentiometer; 1—40 µf, 1—50 µf, 1—300 µf, mica, 400 volts, capacitor; 1—.01 µf, paper or ceramic, capacitor; 1—20-20 µf, 250 volts, electrolytic; 1—117L7-GT tube; 1—octal socket; 1—slug-tuned broadcast oscillator transformer; 1—power transformer, 150-volt secondary @ 15 ma (or more); 1—s.p.s.t. switch; 1—phone jack; 1—pin jack.


Parts list for receiver

1—27,000-ohm, 1/2 watt, resistor; 1—25 µf, 3 volts, electrolytic; 1—Keith *Superloop* antenna coil; 1—CK707 crystal; 1—a.f. coupling transformer, 20,000 to 1,000 ohms (Gramer); 1—CK722 transistor and socket; 2—penlight cells; 1—plastic sheet and box; 2—jacks for phones.

If a more powerful receiver is needed, try a superhet tuner. (See "A More Compact Battery Portable," September, 1954, page 90). The speaker and output transformer are not needed here, and one audio stage may be sufficient.

Such a portable set may be built within a space 3 x 3 x 2 inches or less. It will pick up signals from the oscillator up to 20 feet away when a short transmitter antenna is used. END



FINNEY ANTENNA-SCOPE

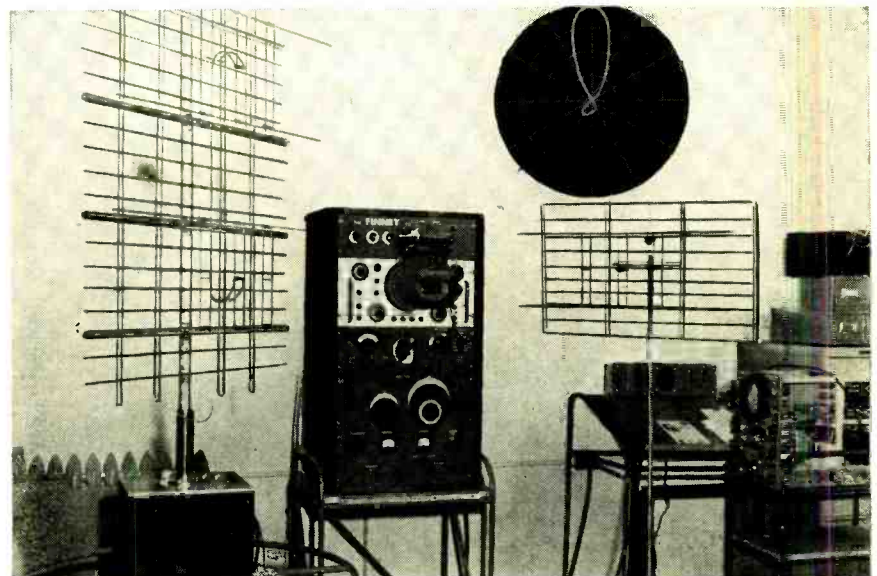

To speed up the time-consuming point-by-point method of plotting an antenna pattern, an antenna-pattern plotting and gain measurement instrument, the *Antenna-Scope*, has been designed by the Finney Co.

The *Antenna-Scope* displays on the screen of a polar oscilloscope the true voltage field pattern of any antenna being tested. The speed at which this pattern is traced is limited only by the antenna rotation rate. Antenna speeds of 30 to 60 r.p.m. are used and a complete field pattern is plotted in 1 to 2 seconds. The *Antenna-Scope* provides full coverage through the 50- to 1,000-mc range.

RADIO

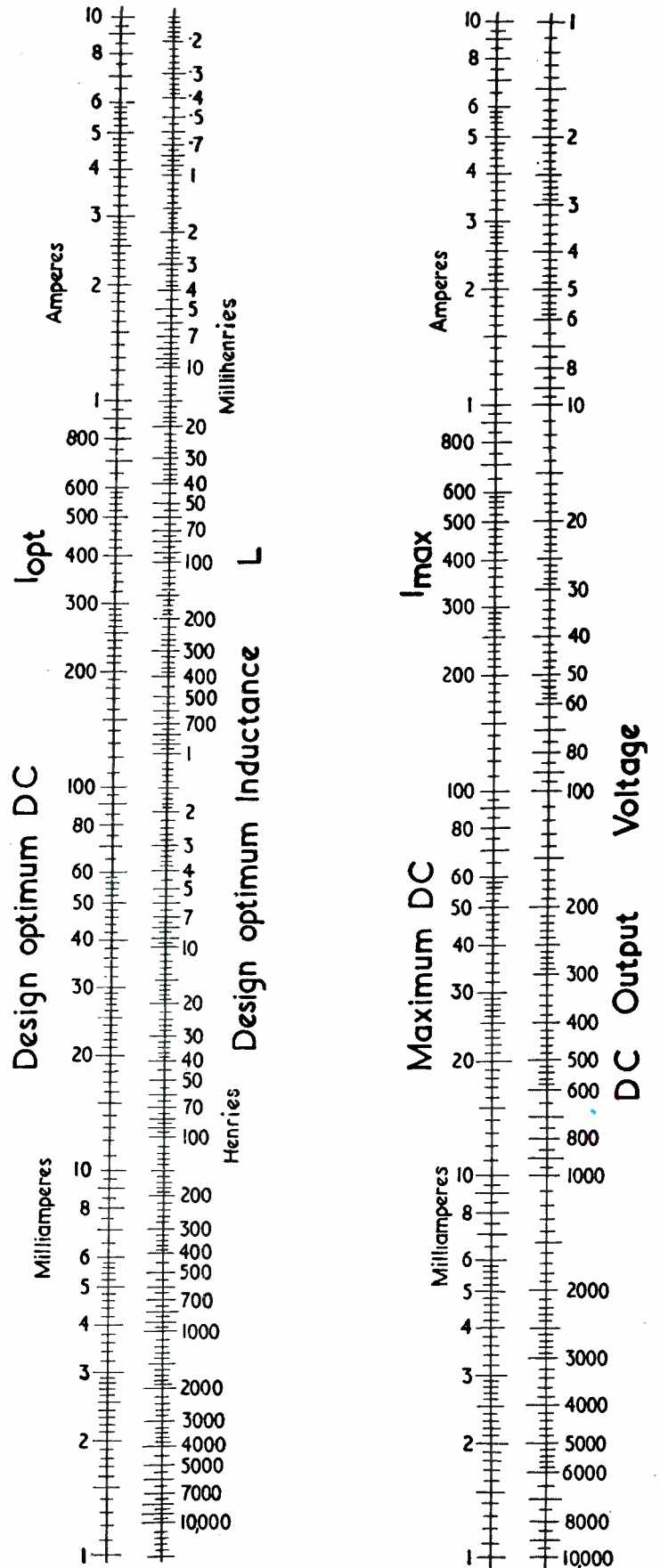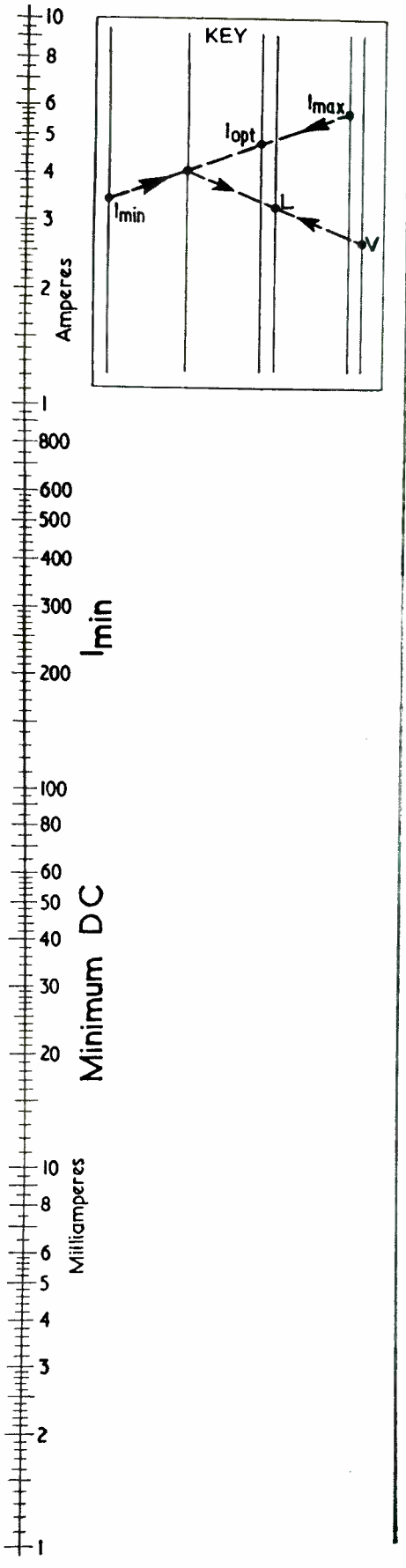

Design chart for calculating the optimum value of a swinging choke for a given range of B supply current swing.

SWINGING CHOKES AND POWER-SUPPLY REGULATION

Long used in transmitting circuits, the swinging choke is valuable in some types of audio power supplies. Fundamentals and design factors are discussed here

By NORMAN H. CROWHURST

MANY modern audio output circuits are operated class AB, causing large fluctuations in plate current. Two 6V6 tubes operated under recommended push-pull conditions, for example, swing from a total cathode current of 73 ma at zero signal to 105 ma at full output, a rise of over 40%. In normal power supply circuits such a rise in load current would result in an appreciable drop in d.c. supply voltage. This drop would reduce the available maximum output, and possibly introduce distortion (the bias becomes incorrect for the changed B voltage). So it is obviously desirable that the power supply be well regulated.

Some output-stage designs using transmitter type triodes or large output pentodes connected as triodes, biased for class-B operation, demand even greater relative changes in current between zero-signal and full-output conditions.

The voltage drop as the load current is increased is due to two effects: the voltage drop in transformer windings,

chokes, and across the rectifier, and the inherent characteristic of the filter circuit that follows the rectifier.

The latter factor is not always appreciated. Fig. 1 includes a typical curve for the d.c. output voltage with a capacitor input (reservoir) type filter and an assumed loss, due to the various voltage drops listed above, of zero. However generous are the proportions of the transformer, rectifier and choke, the voltage characteristic of such a circuit cannot be better than this curve.

To offset these various sources of voltage drop as load current is increased, the swinging-choke type of filter is sometimes used when the current taken by the output tubes varies with signal. Fig. 2 shows a simple rectifier, choke, and filter capacitor arrangement for this circuit. Fig. 3 shows how the waveforms change to produce a rising output voltage characteristic in a theoretical resistanceless circuit designed for this purpose.

In Fig. 3-a the inductance of the choke is large enough to smooth out fluctuations in the output current from the rectifier to a considerable extent; so the choke current has a steady value with a slight ripple imposed on it. The output voltage from the choke has very little ripple at all due to the further smoothing effect of the filter capacitor. As the rectifier is conducting all the time, the output voltage is the average value of the voltage at the input to the choke, neglecting the effect of resistance drops. So the output voltage from a choke filter is 0.637 times the peak value of input voltage (or 0.9 times the

r.m.s. value of the peak input voltage).

Fig. 3-b shows the waveforms as saturation begins. The positive current swing becomes very peaky due to saturation; the negative excursion becomes flatter, making the waveform asymmetrical. The effect on the output voltage is a tendency to rise to a higher point on the input waveform, as the positive-going pulses begin to make the filter capacitor act as a true reservoir. (The vertical lines in the current waveforms indicate the points where the current in the choke changes over from one plate of the rectifier to the other. At no point, however, does the current actually fall to zero during this time—it merely changes rapidly from one plate to the other.)

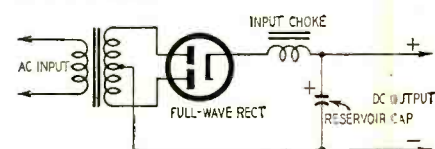


Fig. 2—Choke-input full-wave rectifier.

Fig. 3-c shows the same arrangement with saturation further advanced. The process can be compared to a change-over from choke input at low currents to capacitor input at high currents. The similarity at high current can be seen by comparison with the waveforms of a capacitor-input circuit, shown in Fig. 2-d. From this comparison, Fig. 1 shows how a swinging choke can produce a region of constant voltage output from the power supply. A filter using a non-saturating, resistanceless choke (assuming no losses elsewhere) would pro-

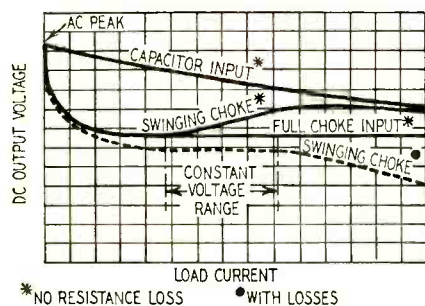


Fig. 1—Power supply characteristics.

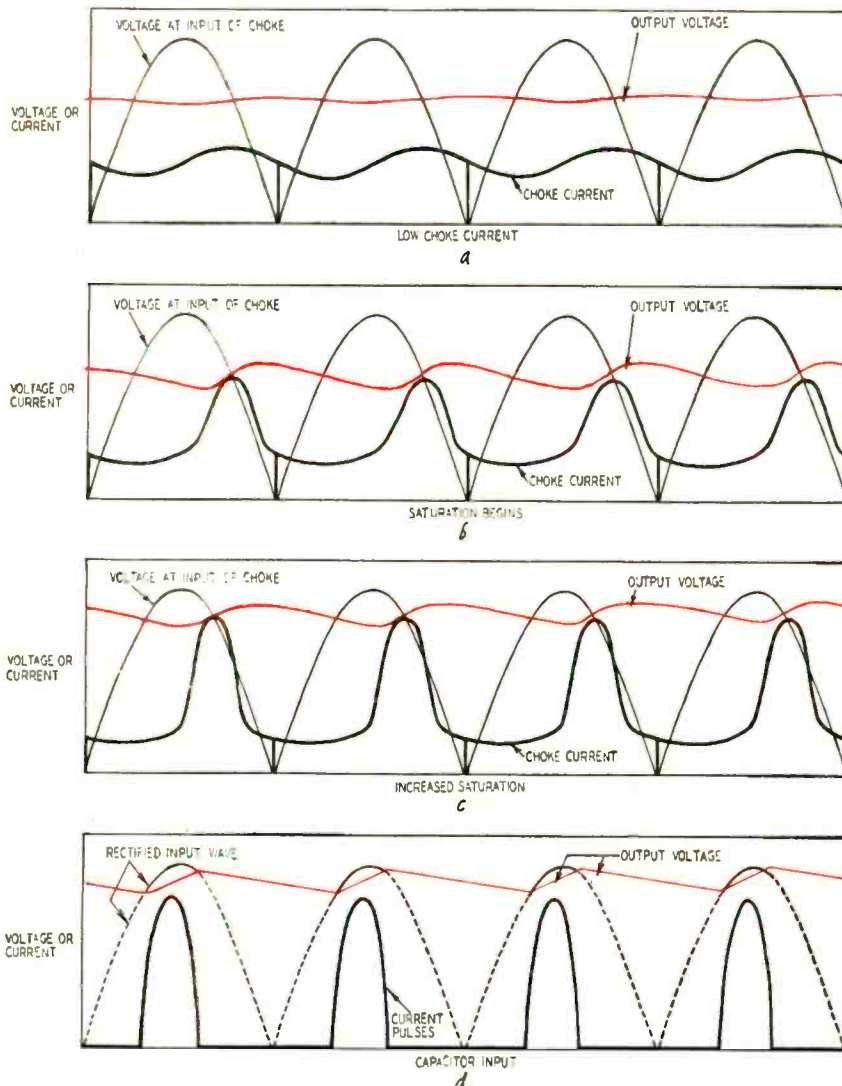


Fig. 3—Waveforms of swinging-choke operation at various load currents.

duce a level output at 0.637 of the peak a.c. input, for current values above the point where the inductance is large enough to prevent the filter capacitor from acting partially as a reservoir. (The reservoir action accounts for the upward sweep of the curve toward zero current.)

A swinging choke with no resistance losses would produce a characteristic following the full choke curve up to the point where saturation begins to set in. At this point it will begin to rise toward the capacitor input characteristic (if the same capacitor value is used in both cases). The dotted curve in Fig. 1 shows the final result when the effects of losses due to resistance in the plate transformer, choke, and rectifier are taken into account. These losses produce a voltage drop from the ideal curve directly proportional to current, but one in which the d.c. output voltage becomes virtually constant over a certain range, as shown.

The whole action is rather complicated, and a completely satisfactory mathematical analysis of its behavior has never been published. At one time it was assumed that the inductance of the choke had a constant value through-

out each rectification cycle. The output voltage of such an arrangement was then analyzed as the inductance was varied. The curves of Fig. 3 show that the assumption of constant inductance during a cycle is not strictly true. Using

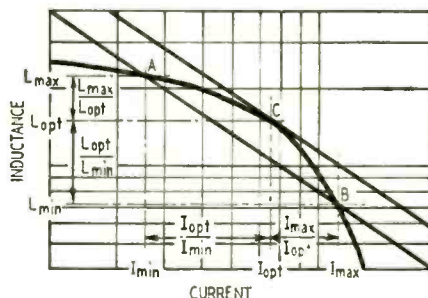


Fig. 4—Choke inductance-current characteristics drawn on log-log scale.

this principle as a basis, an ideal swinging choke would have an inductance that reduced in inverse proportion to increasing load current, as represented by the straight line joining AB in Fig. 4.

Investigation of a variety of iron-cored inductances with direct current flowing showed that the curve of in-

ductance against current, as represented by ACB in Fig. 4, has inherent relations that never depart very far from the proportions shown. A logarithmic scale is used, so the distance between two points on the curve represents the ratio between the currents or inductances at those points, rather than the difference between them.

The inherent ratio of these proportions is incorporated into the design chart, so the optimum inductance value at a current, represented by point C, that bears a definite relationship to the minimum and maximum currents, represented by points A and B, can always be calculated from knowledge of the circuit requirements.

In practice, although the theory remains somewhat doubtful, this method of calculation has proved useful in preparing a chart for finding a choke with the right characteristic for a job. The quantities required for the chart are the maximum and minimum currents and the d.c. output voltage, using full-wave rectification at a supply frequency of 50 or 60 cycles. Using a straightedge as shown in the key on the chart gives us the inductance and current rating for a choke, having its optimum value at the current rating specified.

To give an example of the chart's use, suppose that the two 6V6's mentioned at the beginning of this article are used in an amplifier where the total B supply current consumption at zero signal is 100 ma, rising to 135 ma at full output. The chart shows that the design figure should be a little over 120 ma, and with a supply voltage of 285, as recommended by the tube manufacturers, the inductance required is about 3.8 h. In practice a 4-h 120-ma choke would serve this purpose well.

A small practical point for amplifiers using choke-input filters: a ticky kind of hum, similar to static hum, is sometimes heard. This is due to the sudden current change-over in the rectifier circuit, referred to earlier, which can produce by induction extremely sharp pulses in various parts of the circuit. To overcome this, a simple method is to use a small capacitor at the input end of the swinging choke (Fig. 5). Its value must be small enough not to interfere with the choke action appreciably at low currents, but large enough

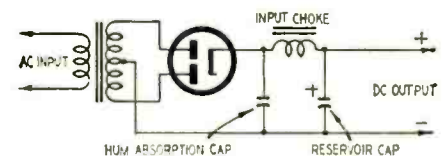


Fig. 5—Adding a small input capacitor.

to smooth off the sharp negative-going points of the voltage waveform at the input to the choke. This avoids the suddenness of transition from one plate to the other in the rectifier. Suitable values for this input capacitor are from 0.1 to 0.5 μ f, depending upon its application. It should have a generous voltage rating because of the relatively large ripple current it will carry. END

ADDING AFC TO YOUR FM TUNER

By A. RINGEL* and E. R. GUNNY*

A DRAWBACK of the average FM home receiver is drift during the warmup period. Even though, percentagewise, the change is remarkably small for a commercial receiver, it is great enough to cause most users to condemn the unit as unsatisfactory because the sound

frequencies. We shall call this the tuning error. When the oscillator drifts above the correct frequency, the d.c. voltage at the discriminator swings from zero volt to some positive value. Below the correct frequency, the d.c. voltage is negative. When the set is correctly tuned, the discriminator voltage is zero.

Control resistor R. can be the plate resistance of a triode shown in Fig. 2, the resistance of which varies as a function of the grid voltage. When the grid becomes more positive, the plate resistance of the triode decreases. The lower resistance increases the shunting effect of C., lowering the oscillator frequency. The operation is reversed when the grid becomes negative, raising the oscillator frequency. The control voltage available at the discriminator is of the proper polarity to be used directly on the grid of the tube.

To correct for oscillator drift and to make tuning less critical, means must be provided to vary electrically the oscillator frequency in response to the d.c. voltage of the discriminator.

Fig. 1 shows the equivalent a.f.c. circuit. By varying R., a control resistance, effective capacitance of the main tuning capacitor and auxiliary capacitor C. can be changed. This results in a change in oscillator frequency.

When any change occurs that tends to increase frequency, a positive voltage is produced. It lowers the plate resistance of the triode, which adds capacitance and lowers the oscillator fre-

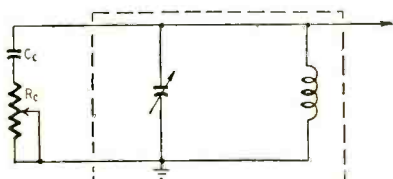


Fig. 1—The equivalent a.f.c. circuit.


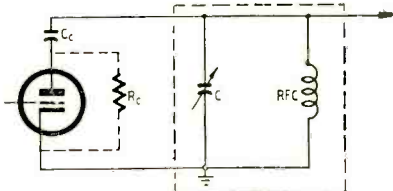


Fig. 2—Resistor is replaced by tube.

becomes mushy in a short time after being set on a station. Some receivers are available with automatic frequency control. This feature eliminates the usual tuning difficulties, but makes the FM receiver too expensive ever to become as popular as the a.c.-d.c. table radios.

This article describes a simple but effective a.f.c. circuit that can be added to any FM receiver with a few parts and without any need for special test equipment.

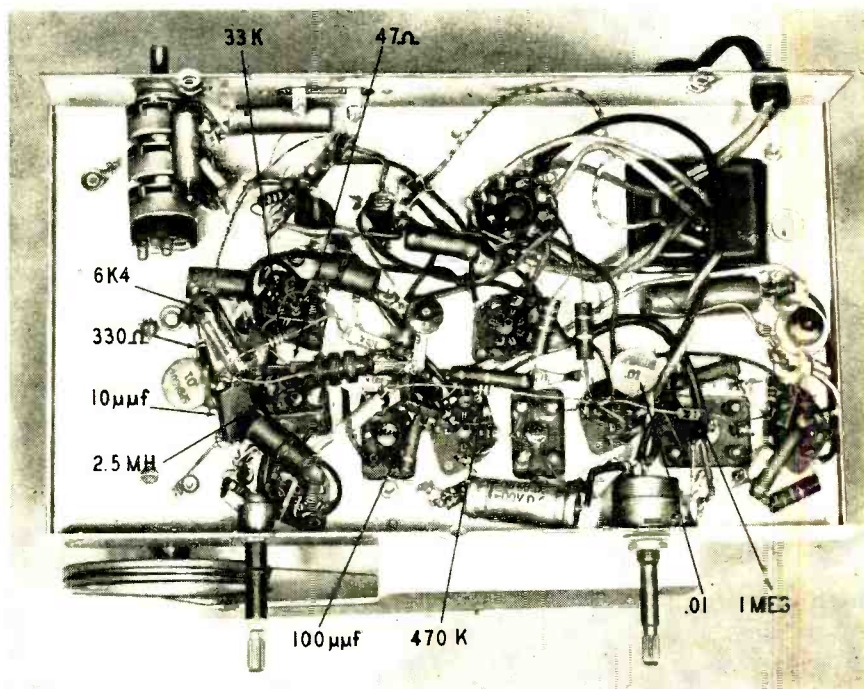Any FM receiver, whether it uses a discriminator or ratio detector, produces at the audio end a d.c. voltage proportional in amplitude and phase to differences in frequency between the desired and the actual center fre-



Underchassis view of tuner showing components added for a.f.c. operation.

*HUGHES AIRCRAFT COMPANY
Culver City, Calif.

quency until the discriminator voltage is zero. The effectiveness of this circuit is determined solely by the transconductance of the control tube used. The higher the transconductance, the better

Parts for a.f.c. circuit

Resistors: 1—47, 1—330, 1—33,000, 1—470,000, 1—1 megohm, 1/2 watt.
Capacitors: 1—10 μf, 1—100 μf, 200 volts, mica; 1—0.1 μf, 200 volts, mica.
Miscellaneous: 1—choke, 2.5 mh; 1—6K4 subminiature tube and socket.

the control. Some satisfactory control tubes are the 6C4, 1/2 12AT7, 1/2 12AU7, 1/2 6J6, and subminiature type 6K4, used in the unit in Fig. 3-a. The diagrams at *b* and *c* in Fig. 3 show the d.c. take-off points in typical ratio-detector and discriminator circuits.

The choke maintains the plate at an appropriate r.f. high impedance above B plus, which is equivalent to r.f. ground. The resistors and capacitors in the grid circuit serve as a low-pass filter. Mount the tube as close as possible to the oscillator tube socket. Plate and cathode leads should be short and direct. While the grid wiring of the 6K4 is not critical, it should be run so as to avoid hum pickup from the 60-cycle line.

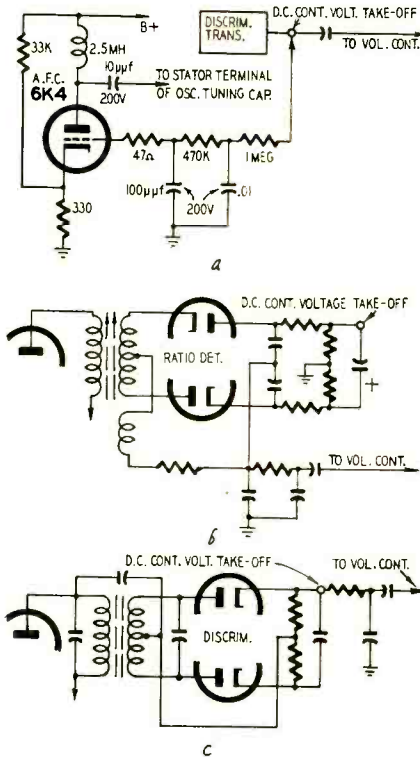


Fig. 3-a—Schematic of a.f.c. circuit; 3-b, c—typical circuit applications.

After completing the wiring, tune the receiver to a strong station. When the tubes have warmed up, reduce the oscillator trimmer until the station can be tuned in at exactly the dial setting at which it had been received before the a.f.c. was added. Adding a switch to disconnect the a.f.c. line from the d.c. take-off and connecting it to ground (Fig. 3-a) will simplify tuning in weak stations close to strong ones.

In a.c.-d.c. FM receivers with the filaments in series, another tube can usually be added. In sets having a 50-volt output tube, it can be replaced by a 35-volt tube. A 150-ma, 12-volt triode or control tube can be added in the filament string without any further changes. Some receivers already use a 35-volt output tube and usually have a resistor in series with the filaments. Whatever the value of this resistor, it must be reduced by 84 ohms, so that another 12-volt tube may be added to the string.

While a.f.c. may seem an unnecessary refinement to some, it is subconsciously annoying to all of us to have to retune after warmup, and persons unfamiliar with radio may attribute the effects of drift to FM in general, and abandon it for the more familiar and comfortable AM band. **END**

PUNCH PRESS CONTROL CIRCUIT

By WALTER T. STEVENSON

MANY of the older punch presses in use today are activated by a positive-action sliding-pin clutch controlled by a hand lever or a foot treadle. If the treadle is held down a trifle too long the punch makes more than one stroke and damages the dies or material and also may endanger the operator.

Double strokes and their damaging and hazardous effects can be prevented by disconnecting the mechanical linkage between the treadle and the clutch dog and by operating the clutch dog with a solenoid coupled to an electronic control circuit. Closing the control switch instantly engages the clutch and automatically releases it after the time interval required for safe and efficient operation of the press.

The operation of the electronic circuit is based on the time constant of a resistance and capacitance in series as in Fig. 1. When the switch is closed, the capacitor begins to charge through the relay coil. The charging current is limited only by the d.c. resistance of the coil and the back e.m.f. induced

in it. The charging current flowing through the relay coil closes the contacts and holds them closed until the capacitor has charged.

Fig. 2 shows the complete circuit of the punch press control unit. When

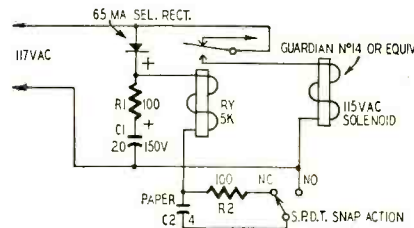


Fig. 2—The completed circuit. Relay at right operates the press mechanism.

the s.p.d.t. switch is closed, C2 begins to charge and pulls in the relay contacts. The contacts open when the charging current drops below the hold-in level of the relay. The time that the contacts remain closed is determined by the capacitance of C2 and the resistance of the relay coil. Adjust the value of C2 so the relay contacts open to de-energize the solenoid and release the clutch dog at the correct instant. A 4-μf capacitor is satisfactory for C2 in most applications.

When the switch is released, C2

discharges through R2 so the punch will be free to operate the next time the switch is pressed.

C1 is the filter or storage capacitor and R1 is a protective resistor to limit the charging current to prevent damaging the selenium rectifier. It and R2, which slows down the discharge of C2 and thus prevents burning out the switch contact, may be 1/2-watt units, since they are on intermittent duty. C2 should be a paper type. It may be built up of smaller units and varied in capacitance till it provides sufficient "dwell" for proper solenoid operation. C1 is an ordinary electrolytic capacitor.

To hook up the device, remove the mechanical linkage between the clutch dog and the treadle. Mount the solenoid as close as practical to the clutch dog and couple to it. Adjust spring tension, stroke, and linkage for proper operation. The lower the mechanical mass of the setup, the more precise will be the action. Each press has its own peculiarities and must be treated as an individual problem.

The control switch, a snap-action type, should be fitted with a cord and polarized plug and may be mounted for either treadle or knee operation. The parts layout is not important but you must take care to avoid all grounds, because all lines are hot to ground. **END**


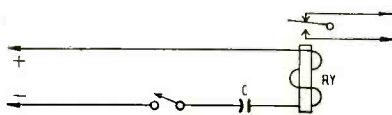


Fig. 1—The fundamental circuit. The relay coil serves as the resistance.

Crossover network—breadboard style.

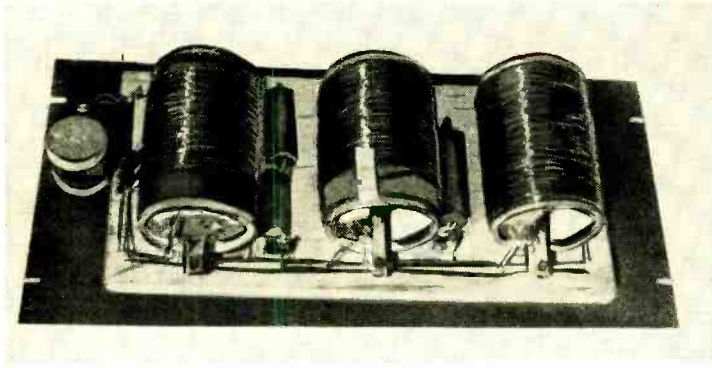

By JAMES P. ROGERS*

*A few simple components
and a little work will
improve the quality of
any good audio amplifier*

A LOW-COST CROSSOVER NETWORK

THIS entire crossover network can be built for about \$6—even less if some of the parts come from the experimenter's junk box.

The purpose of a crossover network is to separate the bass and treble notes and feed them to individual speakers whose resonance falls within that band of frequencies. Even in my own rig, which uses identical speakers, the improvement is tremendous because neither speaker is required to respond to the entire audio range. Design a filter circuit that rapidly attenuates all frequencies above a certain point, and another that attenuates all frequencies below a certain point. Plot their characteristics on a graph. There will be a point at which the two curves coincide. This point is the crossover frequency. In my home-built network 1,000 cycles was arbitrarily chosen as a base from which to begin calculations.

By combining two filter circuits as shown in Fig. 1, a network¹ can be produced to perform to the satisfaction of even the most critical listener.

In calculating the values of L and C, you must know the impedance of the speakers, the crossover frequency desired, and the size of the coil forms you wish to use.

In the following calculations speakers are 8 ohms each, and cleanser cans of the Bab-O or Kitchen Kleanser type were used for coil forms.

Calculations

For the purpose of explaining the calculations we will assume you will use the same values and materials as in my original model. Later the information will be translated into terms of wire

turns. For now, let us consider the formulas for the values of L and C:

$$L1 = \frac{R_o}{6.28 f_c} \quad C1 = \frac{1}{6.28 f_c R_o}$$

$$L3 = \frac{R_o}{12.56 f_c} \quad C2 = \frac{2}{6.28 f_c R_o}$$

$$L4 = (1+m) \frac{R_o}{6.28 f_c}$$

$$C5 = \left(\frac{1}{1+m} \right) \left(\frac{1}{6.28 f_c R_o} \right)$$

where L is in henries, C is in farads, R_o is speaker impedance, f_c is crossover frequency, and m is the design constant equal to 0.6. (The numbering of coils and capacitors follows Terman—cited above—and is used here for the convenience of readers who are able to refer to the *Radio Engineer's Handbook*.)

By substituting the given values of crossover frequency, speaker impedance, and design constant for the unknowns it is possible to find the exact values of inductance and capacitance needed.

$$L1 = \frac{8}{6.28 \times 1,000} \quad L1 = \frac{8}{6,280}$$

$$L1 = 0.00127 \text{ henry}$$

or
1,270 microhenries

$$L3 = \frac{8}{12,560}$$

$$L3 = 0.000637 \text{ henry}$$

or
637 microhenries

$$L4 = (1+0.6) \frac{8}{6,280}$$

$$L4 = \left(\frac{1.6}{1} \right) \left(\frac{8}{6,280} \right)$$

$$L4 = \frac{12.8}{6,280}$$

$$L4 = 0.002038 \text{ henry}$$

or
2,038 microhenries

$$C1 = \frac{1}{6,280 \times 8} \quad C1 = \frac{1}{50,240}$$

$$C1 = 0.0000199 \text{ farad}$$

or
19.9 microfarads

$$C2 = \frac{2}{6,280 \times 8} \quad C2 = \frac{2}{50,240}$$

$$C2 = 0.0000398 \text{ farad}$$

or
39.8 microfarads

$$C5 = \left(\frac{1}{1.6} \right) \left(\frac{1}{50,240} \right) \quad C5 = \frac{1}{80,384}$$

$$C5 = 0.0000124 \text{ farad}$$

or
12.4 microfarads

Having found the values of L and C for the network, it is next necessary to determine the number of turns of wire that will produce the required inductance. The formula² for this is:

$$N = \sqrt{\frac{3a+9b}{0.2a^2}} \times L$$

where N is the number of turns of wire, a is the diameter of the winding in inches, b is the length of the winding in inches, and L is the inductance in microhenries.

I chose cleanser cans as coil forms because they were available and inexpensive. These dimensions provide the values for a and b in the formula—a is equal to 3, and b to 5. Note that since the formula calls for the inductance in microhenries, the values in henries arrived at earlier must be converted.

This crossover network is much larger than commercially available units and could no doubt be reworked for greater compactness.

It performed so well, however, that no modifications were deemed necessary. Space was not considered important although wire size was—to reduce losses—so No. 18 wire was used. This seemed especially important since the amplifier that the network is used with employs a pair of 807's with a plate voltage of 450.

*Engineering Dept. WLW-A, Atlanta, Ga.

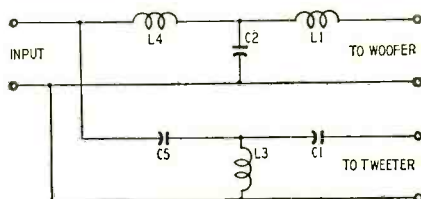


Fig. 1—A simple two-filter network.

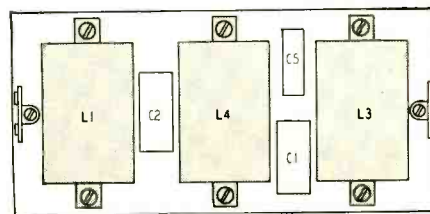


Fig. 2—Arrangements of components.

AUDIO—HIGH FIDELITY

From the information we now have we can compute the required number of wire turns for our coils.

$$N = \sqrt{\frac{L1}{1.8} \times 1,270} \quad N = 195$$

$$N = \sqrt{\frac{L3}{1.8} \times 637} \quad N = 138$$

$$N = \sqrt{\frac{L4}{1.8} \times 2,038} \quad N = 247$$

Construction

Drive a nail through a piece of wood, and drop the wire spool over the nail. Wind the wire by hand from the spool onto the cleanser can. In starting the winding, pierce a small hole in the fiber side at the end of the can containing the pouring perforations. Pass 6 or 8 inches of the wire through the hole in the fiber. Then feed it through one of the perforations in the metal end.

As the first layer of the winding is completed, carefully wind a layer of friction tape around the coil. This provides insulation between the layers and also holds the first layer in place while the second is being wound.

(Note that the inductance formula is not entirely correct for a bank winding. However, it worked out approximately for the author, who checked his crossover point with an audio oscillator—a frequency record could be used—and a vacuum-tube voltmeter. Variation in the inductance would result in slight differences in the crossover point and impedance, neither of which are particularly critical.—*Editor*)

When the required number of turns is reached, pierce a second hole in the fiber side of the cleanser can and feed another 6 or 8 inches of the wire through the fiber and then through another perforation in the metal end. Solder a 2-connector terminal strip to the metal end and cut the two protruding wires to the correct length for securing to the terminals. Before the wires are soldered, slip a piece of spaghetti over each to protect it from the sharp edges of the metal top.

After the coil is complete give it a good coating of varnish or coil dope to protect the insulation and prevent loosening of the turns. (Removing the metal ends of the can in no way changed the characteristics of the network.)

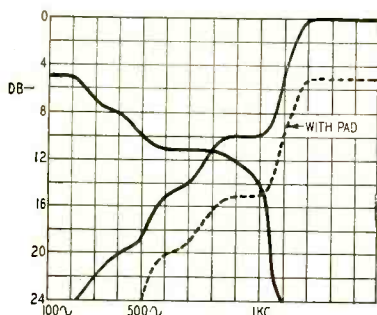


Fig. 3—Characteristics of the network with and without attenuating pad.

The network is laid out breadboard fashion with the components arranged as in Fig. 2. The base is a piece of 5-ply wood measuring 7 x 14½ x ¾ inches. Each coil is fastened to the base by ½ x ½-inch wood strips 6⅝ inches long. The strips are passed through the coil form from end to end and held in place by wood screws.

The three capacitors are mounted between the coils, using single-connector terminal strips. A 2-connector terminal is used at one end of the base for the input and a 3-connector terminal at the other end as the output.

All that remains is to connect the various components with suitable hook-up wire.

There are two optional features. The unit may be mounted on a standard panel for rack mounting, as I did, or it may be placed inside the speaker cabinet. The second feature is a pad at the output of the high-frequency network. Because of the extremely low reactance of the low-frequency speaker voice coil from 10 cycles to roll-off, there is a 5-db loss, causing an unbalance between the highs and lows. The result is a crossover at about 800 rather than the calculated 1,000 cycles. To counteract this a 500-ohm

Parts for crossover network

1—12 µf, 1—20 µf, 1—40 µf, 450 volts, electrolytic capacitors; 3—cleanser cans; 4—2-connector terminal strip; 5—1-connector terminal strip; 1—3-connector terminal strip; 2½ pounds—No. 18 enamel wire; 1—7 x 14½ x ¾-inch board; 6—1½-inch wood screws; 7—¼-inch wood screws; hook up wire.

T-pad was inserted between the output of the high-frequency section and its speaker, and the highs attenuated 5 db. Crossover then occurs at 1,000 cycles. Theoretically, I suppose a 4-ohm pad should have been used, but I did not have one, and the high resistance did not seem to disturb anything. (Still another use for the pad is to compensate for different room acoustics and listener preferences.)


Fig. 3 shows graphically—if you'll pardon the expression—the characteristics of the network both with and without the attenuating pad.

With or without the pad this economical network will improve the performance of any sound system and can be constructed in a spare evening. END

References

- ¹Radio Engineer's Handbook, Terman, page 249.
- ²The Radio Amateur's Handbook, 30th Edition, page 27.


CIRCULAR EXPONENTIAL HORN

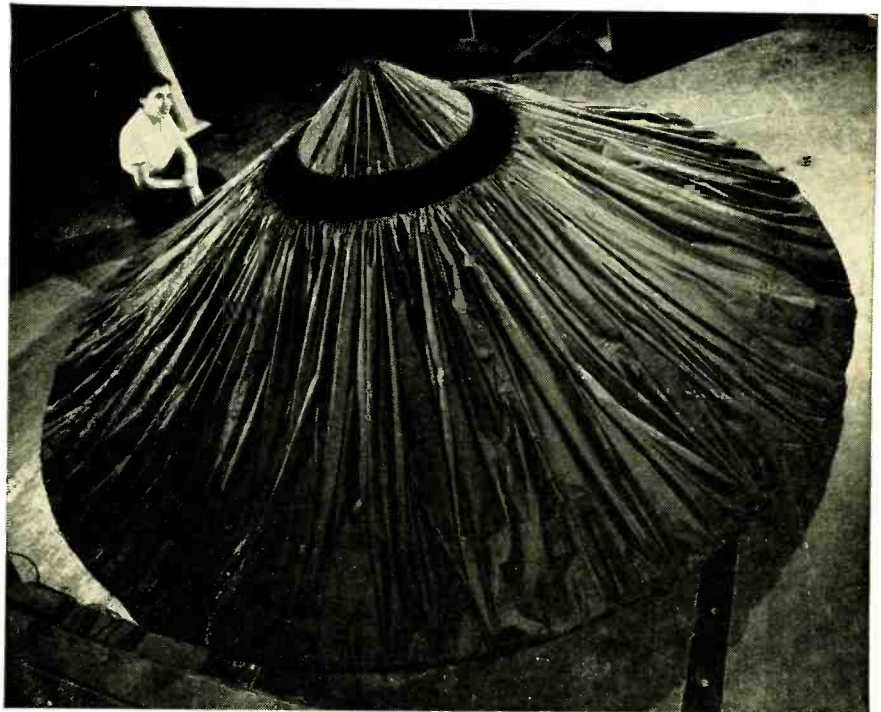



A new sound reproducing system, the Radial Exponential Transducer, has been demonstrated at the Buhl Planetarium, Pittsburgh. Designed by engineer Anthony Doschek, the system is primarily intended for high-fidelity speech and music reproduction in commercial and industrial applications.

The acoustical principle involved is similar to that of the exponential horn except that transformation of the acoustic energy takes place via an exponentially expanding, ring-shaped air load rather than the conventional columnar load. The exponential curve is generated by a very rigid circular structure, critically spaced and bolted to the plane of either a floor, wall or ceiling. The "mouth" of the transducer is actually a slot turned back on itself through a full circle of rotation, thereby radiating sound uniformly over the entire listening area. Five speakers are used to achieve smooth response from below 20 cycles to beyond the limit of audibility.

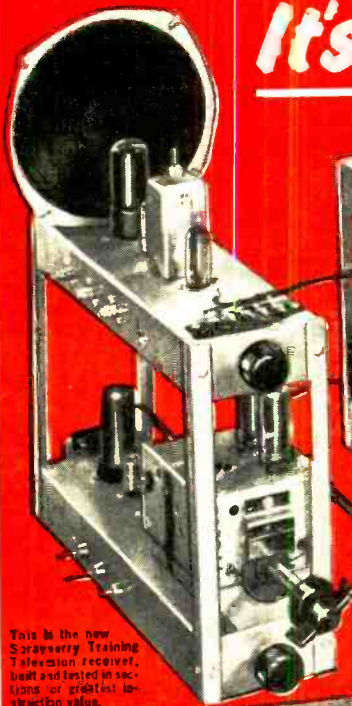**It's New! 3 Years in Development
-NOW READY FOR YOU!**



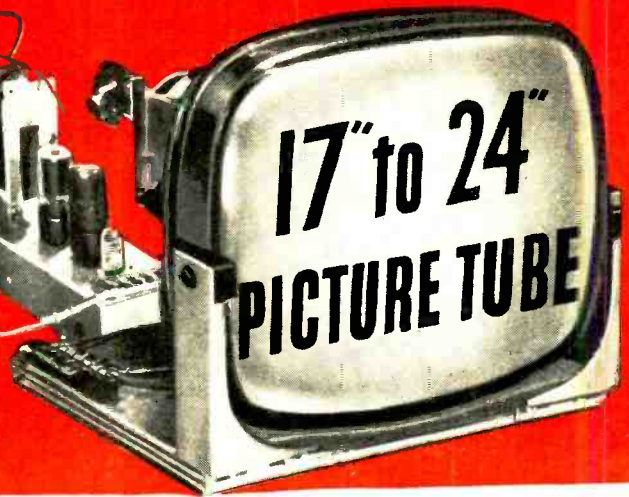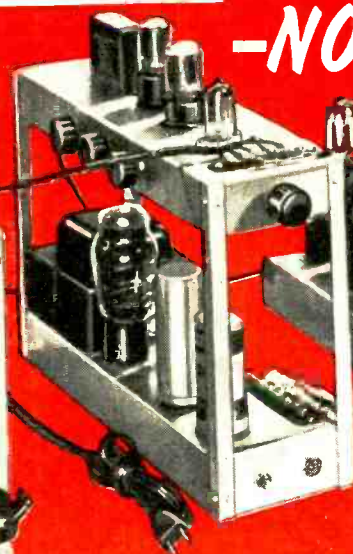This is the new Sprayberry Training Television receiver, built and tested in sections of greatest instructional value.



New Equipment! New Lessons! Enlarged Course!
SPRAYBERRY PRACTICAL TRAINING IN
RADIO-TELEVISION


3 NO OBLIGATION TRAINING PLANS

**You have NO MONTHLY PAYMENT CONTRACT to sign
... pay for this outstanding training as you learn!**




Frank L. Sprayberry
President, Sprayberry
Academy of Radio

The complete facts are so big and so important to any man seeking training in Radio-Television that I urge you to mail the coupon below at once for my big all-new 56 page **FREE CATALOG** and **FREE Sample Lesson**. Get the full story of this remarkable new and up-to-the-second Training Plan. You'll read about my 3 **NO OBLIGATION PLANS** or "packaged unit" instruction for both beginners and the experienced man. You'll learn how I can now prepare you in as little as **10 MONTHS** to take your place in this fast moving big money industry as a **Trained Radio-Television Technician**. You'll see that you take no risk in enrolling for my Training because you **DO NOT SIGN A BINDING TIME PAYMENT CONTRACT**. I have been training successful Radio-TV technicians for 22 years... I can prepare you, too, to get into your own profitable Service Shop or a good paying job, even if you have no knowledge of Radio-Television. Mail the coupon... I rush full information **FREE** and without obligation. (No salesman will call.)

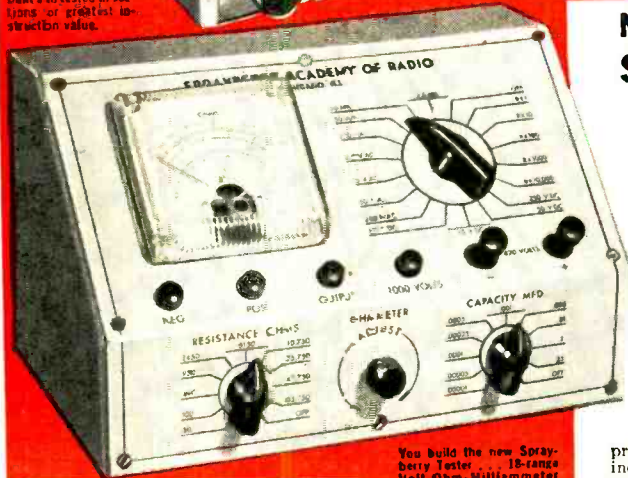

These photos show only a small part of the training equipment I send my students.

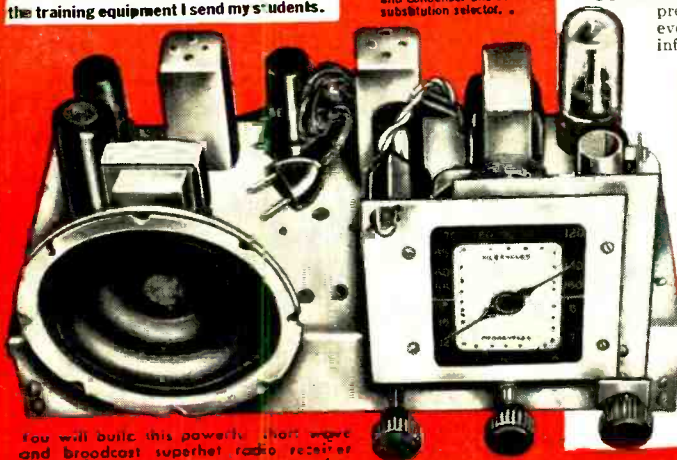You build the new Sprayberry Tester... 18-range Volt-Ohm-Milliammeter readings plus output meter and condenser and resistor substitution selector.



You will build this powerful short wave and broadcast superhet radio receiver for valuable shop instruction practice.

NEWEST DEVELOPMENTS

Your training covers
**U H F, Color
Television, F M,
Oscilloscope
Servicing, High
Fidelity Sound
and Transistors.**

**PRACTICE AND TRAIN AT HOME
WITH 25 NEW KITS OF EQUIPMENT**

You get valuable practical experience in construction, testing and shop practice. You build a powerful 2 band superhet radio, the all-new 18 range Sprayberry multimeter, the new Sprayberry Training Television receiver, signal generator, signal tracer and many other projects. All equipment is yours to use and keep... and you have practically everything needed to set up a Radio-Television Service Shop.

All your training is **IN YOUR HOME** in spare hours. Keep on with your present job and income while learning. I help you earn extra spare time money while you learn. If you expect to be in the armed forces later, there is no better preparation than practical Sprayberry Radio-Television training. Rush coupon below for all the facts—**FREE!**

SPRAYBERRY ACADEMY OF RADIO
111 NORTH CANAL STREET, DEPT. 20-R, CHICAGO 6, ILLINOIS

HOW TO MAKE MONEY IN
Radio-Television
TRAINING PLAN

GETTING YOUR
START IN RADIO-
TELEVISION

**FREE CATALOG AND
SAMPLE LESSON**

Rush coupon for my catalog "How to Make Money in Radio-Television". **PLUS** an actual sample Sprayberry Lesson without obligation—**ALL FREE**. Mail coupon **NOW!**

SPRAYBERRY ACADEMY OF RADIO MAIL THIS COUPON FOR FREE
Dept. 20-R, 111 N. Canal St., Chicago 6, Ill. FACTS AND SAMPLE LESSON

Please rush all information on your ALL-NEW Radio-Television Training Plan. I understand this does not obligate me and that no salesman will call upon me. Include New Catalog and Sample Lesson **FREE**.

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

SERVICING

HIGH-FIDELITY

Part IX—Equalization and frequency response

EQUIPMENT

By JOSEPH MARSHALL

THE playback equalization of a hi-fi system may change with time and correction may become necessary. The simplest and most frequent cause of a shift in playback characteristics is a worn stylus. The translation loss at high frequencies increases rapidly as flats are formed on the needle. Long before a needle becomes dangerous to records, its ability to trace the frequencies above 7,000 cycles deteriorates enough to reduce output above this region by as much as 6 db. The simplest and best check for this is the translation-loss test on the Cook series 10LP record.

The simplest and quickest way to check equalization is with the Clarkstan 102M sweep-frequency test record and a scope. This disc is recorded with LP pre-emphasis. Played back with a good LP equalizer it will produce a reasonably flat trace. Played back with old AES, new RIAA standard, or other equalizers, the trace will show variations from flatness on both ends. The rise at the high-frequency end for the new RIAA standard will be about 2 or 3 db, and for the old AES about 4 or 5 db at 10,000 cycles.

If you have any difficulty obtaining or maintaining synchronization with the sweep record, it is an almost certain

sign that wow is excessive. While using the sweep record, watch for signs of distortion, resonances, and poor transient response. If your scope is sensitive enough, it is best to connect it directly to the output of the preamp so that troubles caused by following portions of the system are eliminated. Distortion is evidenced by a doubling of the trace at the high-frequency end and by a sharpening of the wave shape at low frequencies into a triangular, rather than sine-wave, form. Resonances are indicated by bulges at the resonant frequencies or band of frequencies. Transient response can be checked by watching the very beginning of the trace. If the system reacts to the synchronizing pulse by producing echoes or hang-over, the initial portion of the trace will be followed by a weaving curve rather than a smooth one. Some of these effects are indicated in the drawings of Fig. 1.

If a scope has a sweep magnifying circuit, it is possible to examine the trace minutely from beginning to end and the exact point at which any distortion occurs—as well as its nature—is much more easily determined. A study of the leaflet which comes with the Clarkstan record, and some experience, will soon make you familiar with

the various patterns and their significance.

A more exact, though more tedious, method of checking equalization is using a steady-state test-frequency record and an output indicator. When the budget for test records is limited, the Cook series 10 is probably the most useful single record because it permits the greatest variety of tests. It is also the only one which covers the complete audio range from 20 to 20,000 cycles and is, therefore, the only one which offers a measure of the response of those very high quality pickups which go beyond 10 or 12 kc. A useful procedure with this record is this:

1. Play side B with the equalizer set for the LP curve. Watch the output indicator or wattmeter. The reading should be almost the same (say within 2 or 3 db at most) for all the test tones in band 1. Listen for a change in pitch on each tone; such a change will indicate wow.

2. Measure the intermodulation at the beginning and end of each of the two IM bands. When the record is new, the IM should run from about 3 or 3½% with the finest pickups to 5% with average pickups on the outermost band, and should not rise to more than 5 to 8% on the innermost one. If the rise

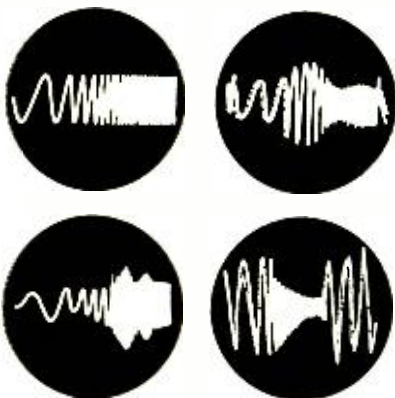


Fig. 1—Various response patterns.

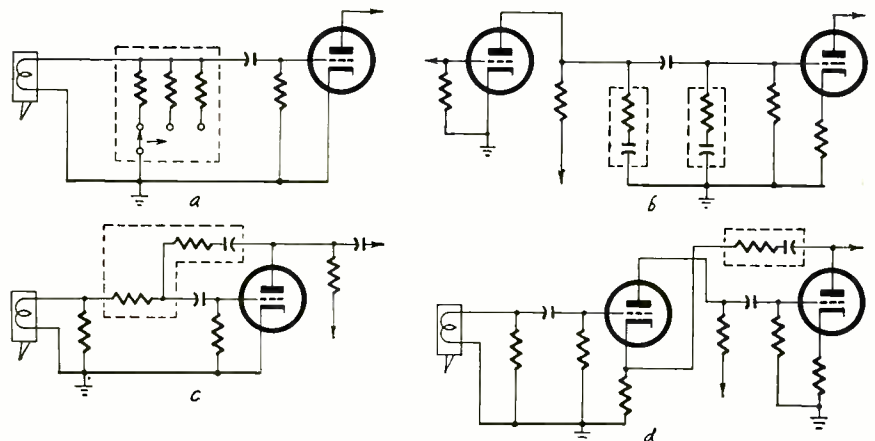


Fig. 2—Types of equalizer circuits.


NEW 1955

Heathkit

Engineering Features


New PRINTED CIRCUITS

One of the many tremendous improvements in the new 1955 Heathkits is the use of an etched metal process printed circuit board. Printed circuits will be used in Heathkits whenever they will affect construction simplification, performance stabilization, and lend themselves to instrument design. Now for the first time a kit instrument company offers the advantages of modern printed circuit instrument construction technique. For the first time consideration has been given toward reducing kit assembly time. Also this is the first time that printed circuit boards have been hand soldered on a volume basis. Offered only by Heathkit, the pioneer and leader in kit instrument design.

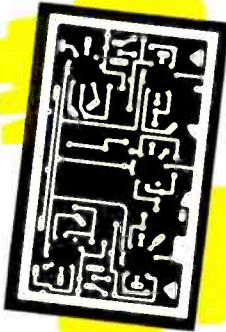

New PEAK-TO-PEAK VTVM CIRCUIT

New 6AL5 full wave rectifier in AC input circuit permits full scale peak-to-peak measurements. Seven ranges — upper limits 4000 volts peak-to-peak. Just the thing you TV servicemen have needed in making TV circuit voltage checks. Precision resistor voltage divider limits AC RMS level to 150 volts. Prevents overloading the rectifier — extends upper limit AC RMS ranges to 1500 volts — further protects meter and circuitry against AC flash-over or arcing. Another definite example of continuing Heathkit design leadership in the kit instrument field.

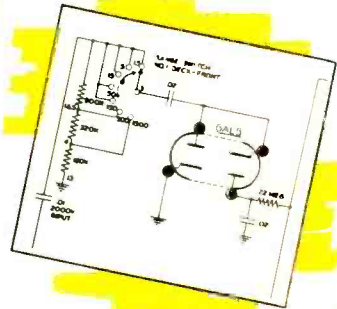

New HIGH READABILITY PANELS

New 1955 Heathkits feature complete panel redesign. Sharp white lettering applied to the beautiful charcoal gray panels, provide a new high in readability. Lettering is easy-to-read open style and panel calibrations are vividly clear against the pleasing soft gray background. New knobs of exclusive Heathkit design.



New 3" UTILITY SCOPE

The new 3" Scope is a "natural" for the well rounded line of Heathkit instruments. Small in size, 11 3/4" deep, 6 1/2" wide, 9 1/2" high, yet big in performance. Just think of the value, an Oscilloscope for \$29.50. Brilliant intensity, sharp focusing, wide positioning range. An ideal portable Scope for the TV serviceman — a second shop scope — modulation monitor for you hams (deflection plate terminals in rear of cabinet). Performance to spare for all general scope applications. See specifications on following page.




New STYLING New COLOR

New styling and coloring is responsible for tremendous improvement in Heathkit appearance. The new instrument panel color combination is high definition white lettering in a soft charcoal gray panel. Cabinet color is a lighter leather gray. The satin gold baked enamel cabinet for the WA-12 Pre-amplifier is further indicative of the modern pre-setting trend in Heathkit styling.



New SCOPE SWEEP CIRCUIT 10 CYCLES — 500 KC

New 1955 Heathkit Model 0-10 Scope features a new wide frequency range sweep generator covering 10 cycles to 500,000 cycles. This coverage is available in virtually decade five sweep ranges and is five times greater than the sweep frequency range usually available. Excellent retrace time characteristics, actually less than 20% at 500 KC. Use of the free running Heath circuit provides a larger margin of stability and a new high in Heathkit Scope performance.

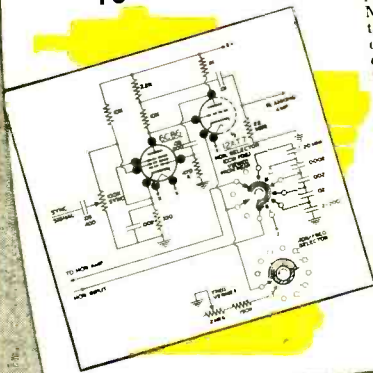

Continuing PROGRESS FUTURE LINE EXPANSION

The outstanding improvements featured in the 1955 Heathkit line are representative of the progress characterized by Heath Company operation. Long range planning will provide a continuing succession of new kit releases to further expand the Heathkit line which already represents the world's greatest selection of electronic kits. The innovations in the 1955 line, are representative of additional new models scheduled for release for the coming years.



SEE THE INSTRUMENTS
ON THE FOLLOWING PAGES

HEATH COMPANY • Benton Harbor 20, Mich.

Heathkit ELECTRONIC SWITCH KIT

The basic function of the Heathkit Electronic Switch Kit is to permit simultaneous oscilloscope observation of two separate traces which can be either separated or superimposed for individual study. This is accomplished through the use of two individually controlled inputs working through amplifier, multi-vibrator, and blocking stages. The output of the Electronic Switch is connected directly to the vertical input of the Oscilloscope. A typical example of usefulness would be simultaneous observation of a signal or waveform as it appears at both the input and output stages of an amplifier.

APPLICATIONS


An Electronic Switch has many applications to increase the over-all operating versatility of your oscilloscope. It can be used to check amplifier distortion—audio crossover networks—phase inverter circuits—to measure phase shift—special waveform study, etc. The instrument can also be conveniently used as a square wave generator over the range of switching frequencies, often providing the necessary wave form response information without incurring the expense of an additional instrument. Ownership of this instrument will reveal many entirely new fields of oscilloscope application and will quickly justify the modest cost of the Electronic Switch Kit.

Tube complement:
2—6X4, 2—6SN7,
1—6X5.

Continuously variable
switching rates in three
ranges from less than 10
CPS to over 2000 CPS.

Individual input
gain controls, position
control, coarse frequency
control, and fine
frequency control

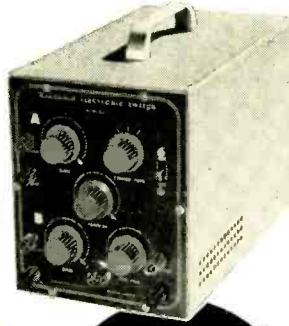Transformer operated for
safety when used in con-
junction with other equip-
ment.



MODEL S-2

\$23.50

Shpg. Wt.
8 lbs.

Heathkit VOLTAGE CALIBRATOR KIT



MODEL VC-2

\$11.50

Shpg. Wt. 4 lbs.

Another useful oscilloscope accessory particularly in circuit development work and in TV and radio service work. The Voltage Calibrator provides a convenient method for making peak-to-peak voltage measurements with an oscilloscope, by establishing a relationship on a comparison basis between the amplitude of an unknown wave shape and a known output of the voltage calibrator. Peak-to-peak voltage values are read directly from a calibrated panel scale without recourse to involved calculations.

FEATURES:

To off-set line voltage supply irregularities, the instrument features a voltage regulator tube. A convenient "signal" position on the panel switch by-passes the calibrator completely and the signal is applied through the oscilloscope vertical input, thereby eliminating the necessity for constantly transferring test leads.

RANGES:

With the Heathkit Voltage Calibrator it is possible to measure all types of complex waveforms within a voltage range of .01 to 100 volts peak-to-peak. Build this instrument in a few hours and enjoy the added benefits offered only through combination use of test equipment.

Heathkit LOW CAPACITY PROBE KIT



No. 342

\$3.50

Shpg. Wt. 1 lb.

An oscilloscope accessory, the 342 Low Capacity Probe permits observation of complex TV waveforms without distortion. An adjustable trimmer provides proper matching to any conventional scope input circuit. Excellent for high frequency, high impedance, or broad bandwidth circuits. The attenuation ratio can be varied to meet individual requirements.

Heathkit SCOPE DEMODULATOR PROBE KIT



No. 337-C

\$3.50

Shpg. Wt. 1 lb.

Extend the usefulness of your oscilloscope by observing modulation envelopes of RF or IF carriers found in TV and radio receivers. The Heathkit Demodulator Probe will be helpful in alignment work, as a gain analyzer and a signal tracer. Easy construction with the new modern printed circuit board. Voltage limits are 30 volts RMS and 500 volts D.C.

HEATH company

BENTON HARBOR 20,
MICHIGAN

AUDIO—HIGH FIDELITY

does exceed 2 or 3%, check the needle, alignment, and tracking. If you do not have an IM analyzer, it is possible that you can detect a rise in IM by ear. It takes a very critical ear to discern a rise from 3 to 5%; but if you do perceive a rise from the outermost to the innermost grooves, the chances are you have at least that much rise and probably a good deal more.

3. Band 3 of side B sweeps the low end of the spectrum down to 20 cycles. The output meter should give a uniform response (with the LP equalizer) at least down to 50 cycles and preferably all the way down to 20 cycles. Listen carefully through this band for it will reveal arm and cartridge resonances, speaker resonance, and tracking and compliance troubles. Resonance is indicated by a sudden rise in output at some portion of the sweep band. Poor tracking or compliance will be evidenced by a buzzing or a fuzzy tone. This is also an excellent band for checking frequency doubling in loudspeakers. Since very few systems are capable of reproducing fundamentals below 40 cycles, listen very carefully as the tone sweeps below that point. On a speaker with no distortion, you should get a sudden, very marked reduction or complete cutoff at some point below 40 cycles. Most speakers, however, do produce frequency doubling and so they will continue to emit sound; but this sound will suddenly rise about an octave in pitch.

4. Turn the record over to side A and change the equalizer to the flat position of treble. This side will play back flat only with an equalizer which does not de-emphasize the highs. Amplifiers which do not provide a flat position will show a slope at the high-frequency end, and the slope at 10,000 cycles gives a good check of equalization. I suggest that you play the 1,000-cycle band to adjust the output level, and then move the pick up to the sixth band, the 10-ke band—unless the pickup is one of the very wide range type. I suggest this because the bands above 10 ke are subject to rapid wear and should be reserved for use when they are really needed.

If the amplifier in question does not have a flat position, this series of bands can be played back with an LP equalization. The bulletin which comes with the records gives a table showing the readings for an LP curve. If this portion gives a reasonably flat response, the chances are it will provide good equalization in all equalizer positions.

5. Note the reading on the 10,000-cycle band as compared with the refer-

CURVE RESPONSE

(1 volt at 1 kc)

Curve	Reading at 10 kc
LP	—15 db or 0.15 to 0.20 volt
New RIAA	—14 db or 0.20 to 0.25 volt
Old AES	—12 db or 0.25 to 0.33 volt

ence reading on the initial 1,000-cycle band. This is necessary for the transla-


NEW *Heathkit* 5" PUSH-PULL OSCILLOSCOPE KIT FOR COLOR TV

BRAND NEW DESIGN: The new Heathkit Model O-10 Oscilloscope would be something special at any price, but is almost unbelievable at \$69.50. Completely re-designed scope has broadband amplifiers for color TV work and offers brilliant overall performance. Vertical frequency response within 5 db from 5 cps to 5 mc. Even more astounding, the response is down less than 1½ db at 3.58 mc. the color TV sync burst frequency. It is essential that scopes for color work have these broadband characteristics.


PRINTED CIRCUITS: Two printed circuit boards used in this fine instrument to insure stable, consistent performance. Problems solved by pre-engineering of boards, and their use guarantees completed unit that will have same characteristics as lab development model. Printed circuits simplify construction and save labor.

NEW SWEEP CIRCUIT: Sweep circuit operates with exceptionally good linearity from 20 cps to over 500,000 cps. 5 times the usual range for scopes in this price range. An entirely new circuit introduced for the first time in any Heathkit.

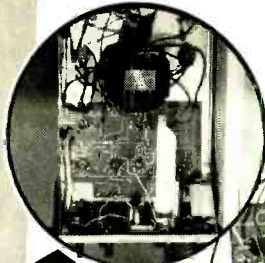Simplified, standardized construction technique of vertical and horizontal amplifier construction made possible through the use of a single printed circuit board.



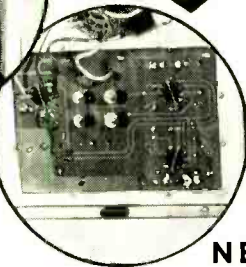Clean, open, under chassis construction and wiring. Possible only through use of pre-cabled wiring harness, and simplified printed circuit boards.



FEATURES: Other outstanding characteristics of this professional oscilloscope are: Built-in 1V peak-to-peak reference for calibration of plastic CRT face-plate; 5" 5UP1 CRT; push-pull hor. and vert. deflection amplifiers; hor. trace width expandable to 3 times diameter of CRT tube to allow inspection of any small portion of the signal; deflection sensitivity, .025 volts per inch; wiring harness pre-formed and cabled to save construction time and insure professional appearance and operation. Incorporates efficient retrace blanking. Frequency compensated step attenuator at the vertical input. Entire tube face useable. No rollover on vertical over-load. Performance obtainable only in much more expensive laboratory models.


Uses 5UP1, 6AB4, 6B07, 12BH7, 6CB6, 12AT7, 2-12AU7, 6X4, 1V2, and 6C4. Quality components used throughout so that outstanding performance characteristics may be maintained for years to come. Plastic molded condensers are used in all coupling and by-pass applications. The "new-look" in Heathkit styling produces professional appearance in keeping with the professional performance of this instrument.

First color television service Oscilloscope with necessary high sensitivity and full 5 megacycle bandwidth.

New printed circuit construction, all components all mounted on high insulation surface resulting in uniformly low circuit capacities.

New type wide frequency range Heath sweep generator, 10 cycles to 500,000

New 5UP1 CR tube

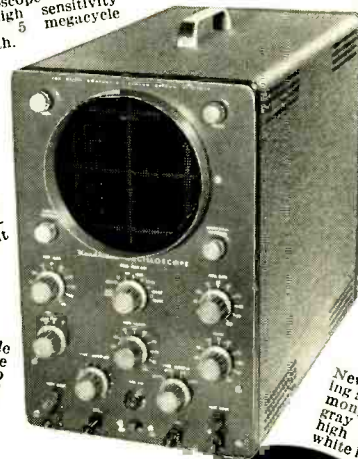

New cabinet styling and color harmony—charcoal gray panel with high readability white lettering.

MODEL O-10

\$69.50

Shpg. Wt. 27 lbs.

NEW *Heathkit* 3" PRINTED CIRCUIT

OSCILLOSCOPE KIT

MODEL OL-1

\$29.50

Shpg. Wt. 15 lbs.

New easy-to-build printed circuit board with high insulation factor.

New Heathkit instrument styling—charcoal gray panel with high readability white lettering.

New Heath twin triode sweep generator 15-100,000 cycle sweep.

New compact utility Scope—light-weight—portable for service work.

Deflection plate terminals—ideal for ham transmitter modulation monitoring.

EXCEPTIONAL VALUE: The brand new Model OL-1 Utility Oscilloscope is designed especially for portable applications so that outside servicemen or persons performing field tests can have the advantages of a scope available. Then too, it is ideal for home workshop, the ham-shack, or as an "extra" scope for the service shop. It is compact, light in weight, and surprisingly versatile in operation. An outstanding instrument for the price.

Front panel controls are "bench-tested" for ease of operation and convenience. Printed circuit board used for constant circuit performance. Assembly time cut in half!

SPECIFICATIONS: Vertical amplifiers feature frequency response within 1 db from 10 cps to 100 kc. and within 5 db from 5 cps to 500 kc. Vertical sensitivity .2 volts per inch at 1 ke. with input impedance of 12 mufd shunting 10 megohms.

Horizontal response within 1 db from 10 cps to 200 kc. and within 5 db from 5 cps to 500 kc. Hor. sensitivity .25 volts per inch at 1 ke, input impedance of 15 mufd shunting 10 megohms. Sweep generator covers 10 cps to 100,000 cps with stable positive lock-in circuit. Cathode follower input in both vert. and hor. amplifiers; push-pull vertical and horizontal deflection amplifiers; 3" CRT; electronic positioning controls for wide range of vertical and horizontal spot deflection; provision for internal and external sync; 60 cycle line sweep. New modern color styling and unusual performance make this instrument an outstanding value.

NEW *Heathkit* 5" PRINTED CIRCUIT

OSCILLOSCOPE KIT

MODEL OM-1

\$39.50

Shpg. Wt. 24 lbs.

VERSATILE INSTRUMENT: The new Model OM-1 general purpose Oscilloscope represents an outstanding dollar value in reliable test equipment. Full 5 inch CRT. Printed circuit boards for ease of assembly, constant circuit characteristics, and rugged component mounting. Includes all the design features necessary for servicemen, students, experimenters, radio amateurs, etc. Frequency response of amplifiers flat within 1 db from 10 cps to 100 kc, and down only 7 db from 10 cps to 500 kc. Sweep generator range from 20 cps to 100,000 cps. Also features new Heathkit color styling with charcoal gray panel and high definition white lettering for readability even under subdued lighting conditions.

DESIGN FEATURES: A full-size, versatile oscilloscope at a price you can afford. Other features are: adjustable spot shape control; BF connections to deflection plates; direct coupled centering controls; external and internal sweep and sync; 60 cycle line sync; built in 1 volt peak-to-peak panel terminal reference voltage; professional appearance of cabinet, panel, and knob styling.

5BP1 CR TUBE



HEATH company

BENTON HARBOR 20,
MICHIGAN

Heathkit MULTIMETER KIT

20,000 ohms per volt
sensitivity DC;
5,000 ohms per
volt AC.

Polarity reversal
switch eliminates
transferring of
test leads.

All 1% Precision
multiplier
resistors—sensitive 50
microamp 4 1/2
Simpson meter.

Total of 35 meter
ranges on two
color scale.



New modern cabinet
styling—attractive
appearance.

MODEL MM-1

\$26.50

Shpg. Wt. 6 lbs.

The new Heathkit Multimeter is a "must" to complete the instrument lineup of any well equipped service shop. Here is an instrument packed with every desirable service feature, many of which are not found in other Multimeters. All of the measurement ranges you need or want. High sensitivity 20,000 ohms per volt DC; 5,000 ohms per volt AC.

★ ADVANTAGES

Complete portability through freedom from AC line power operation—provides service ranges of direct current measurements from 150 microamps up to 15 amperes—can be safely operated in RF fields without impairing accuracy of measurement.

★ RANGES

Full scale AC and DC voltage ranges are 0-1.5, 5, 50, 150, 500, 1500 and 5,000 volts. Direct current ranges are 150 microamps, 15, 150 and 500 milliamperes and 15 amperes. Resistances are measured from .2 ohms to 20 megohms in 3 ranges and db range from -10 to +65 db.

★ CONSTRUCTION

The Heathkit MM-1 features a unique resistor ring switch mounting assembly procedure. With this method of assembly the precision resistors are wired to the rings and range switch before actual mounting of the switch to the instrument panel. This procedure affords the advantage of simpler construction yet complete accessibility of precision resistors in event replacement is ever required. Ohmmeter batteries were selected for convenience of replacement and only standard commercially available types are used. Batteries consist of 1 type C flashlight cell and 4 Penlite cells. All batteries and necessary test leads are furnished with the kit.

Heathkit HANDITESTER KIT



MODEL M-1

\$14.50

Shpg. Wt. 3 lbs.

The Heathkit Model M-1 Handitester readily fulfills major requirements for

a compact, portable volt-ohm milliammeter. The small size of the smooth gleaming molded bakelite case permits the instrument to be tucked into your coat pocket, toolbox or glove compartment of your car. Always the "Handitester" for those simple repair jobs.

RANGES:

Despite its compact size, the Handitester is packed with every desirable feature required in an instrument of this type. AC or DC voltage ranges, full scale, 10, 30, 300, 1,000 and 5,000 volts. 2 convenient ohmmeter ranges 0-3,000 ohms and 0-300,000 ohms. 2 DC milliammeter ranges 0-10 milliamperes and 0-100 milliamperes.

CONSTRUCTION

The instrument uses a 400 microampere meter movement which is shunted with resistors to provide a uniform 1 milliampere load in both AC and DC ranges. This design allows the use of but 1 set of 1% precision divider resistors on both AC and DC and provides a simplicity of switching. A small hearing aid type ohms adjust control provides the necessary zero adjust function on the ohmmeter range. The AC rectifier circuit uses a high quality Bradley rectifier and a dual half wave hookup. Necessary test leads and battery are included in the price of this popular kit.

Heathkit RESISTANCE SUBSTITUTION BOX KIT

MODEL RS-1

\$5.50



Shpg. Wt.
2 lbs.

36 standard RTMA 1 watt resistor values between 15 ohms and 10 megohms with an accuracy of 10% are at your fingertips in the Model RS-1 Resistance Substitution Box kit. This sturdy and attractive accessory will easily prove its worth many times over as a time saving device. Order several today.

Heathkit CONDENSER SUBSTITUTION BOX KIT

MODEL
CS-1



\$5.50

Shpg. Wt.
2 lbs.

18 standard RTMA values are available from .0001 mfd to .22 mfd. An 18 position switch set in the panel of an attractive bakelite case allows quick changes without touching the test leads. Invest a few minutes of your time now and save hours of work later on.

HEATH company

BENTON HARBOR 20,
MICHIGAN

AUDIO—HIGH FIDELITY

tion-loss test to come. It also gives a pretty good check of equalization. The table gives the approximate readings at 10,000 cycles for the several commonly used curves when the 1,000-cycle tone is set for 1 volt. The New RIAA Standard is identical with both the new AES and the ortho curves.

Don't expect exact readings. A variation within the range given will be generally indistinguishable to the listener.

6. When you get to the innermost band, reset your volume control to get the same reading for the 1,000-cycle tone as at the beginning.

Now take a careful reading of the level of the following 10,000-cycle tone. Compare this with the reading noted in step 4. If the reading in step 6 is from one-third to one-half that in step 4, the needle is still O.K.; if it is less than one-third, the needle (or alignment) is poor. I would check the alignment first, correct it if necessary, and run another check. If this reading comes within tolerance, the needle is all right. In that case, repeat the IM measurement on side B; chances are it, too, has been improved.

If the outfit is not producing a reasonably flat response curve, the equalization is off. If the departure is entirely above 5 or 7 kc, check the translation loss as in step 6. If it is too high, chances are very good that the needle alone is at fault. Change the needle and try again. If you still are off on the high-frequency end, check to see if you get about the same variation, or at least in the same direction, on all equalization positions. If the curve is off in the same direction at all positions, it is almost certainly due to either high-frequency losses in the cable from pickup to equalizer or improper loading of the pickup, or both.

Every cartridge, whether magnetic or piezoelectric, must work into an optimum load to provide a flat curve. In magnetic pickups variations in the resistive load produce variations in high-frequency response; in piezoelectric pickups, the variation is in the low-frequency response. In either case, as the resistance of the load is increased so is the response at the affected end. This principle is very often employed in equalizers to produce desired high-frequency equalization, as in *a* of Fig. 2. Check the diagram or circuit to see if that is true in this instance.

But before doing anything at all about it, first determine if the equalizer was designed for the cartridge in use. The Pickering requires a load about half that of the G-E and will produce a rising response at high frequencies with a G-E load; a G-E on the other hand, when used with a Pickering load, will produce a falling response. Many of today's amplifiers and preamplifiers have a switch which changes the load resistance for different pickups. Check to see if that is the case with your equipment.

In many equalizers the load remains

NEW Heathkit VACUUM TUBE VOLTMETER KIT PRINTED CIRCUIT DESIGN

New charcoal gray baked enamel panel with high readability white lettering. Soft feather gray cabinet, subdued pilot light indicator.

New printed circuit board for faster, easier construction—exact duplication of Lab development model.



Another outstanding example of continuing Heath Company pioneering and leadership in the kit instrument field. A new printed circuit VTVM. New peak-to-peak circuit—new styling and new panel design. A prewired, prefabricated printed circuit board eliminates chassis wiring, cuts assembly time in half, assures duplication of Engineering pilot model specifications, and virtually eliminates possibility of construction error.

CIRCUIT:

A 6AL5 tube operated as a full wave AC input rectifier permits seven peak-to-peak voltage ranges with upper limits of 4000 volts P-P. Just the ticket for you TV servicemen. Voltage divider in the 6AL5 input circuit limits applied AC input to a safe level. This circuitry and the isolation of the meter in the cathode of the 12AU7 bridge circuit affords a high degree of protection to the sensitive 200 microampere meter.

RANGES:

Seven voltage ranges. 1.5, 5, 15, 50, 150, 500 and 1,500 volts DC and AC RMS. Peak-to-peak ranges 4, 14, 40, 140, 400, 1400, 4000. Ohmmeter ranges X1, X10, X100, X1000, X10K, X100K, X1 meg. Additional features are a db scale, a center scale zero position, and a polarity reversal switch.

IMPORTANT FEATURES:



High impedance 11 megohm input—transformer operated—1% precision resistors. 6AL5 and 12AU7 tube—selenium power rectifier—individual AC and DC calibrations—smoother improved zero adjust control action—new panel styling and color—new placement of pilot light—new positive contact battery mounting—new knobs—test leads included.

The new V-7 also sets the pace as a kit instrument style leader. Smart, good-looking charcoal gray panel and soft feather gray cabinet. High readability panel with sharply contrasting white calibrations. The pleasing, eye catching, modern styling is in harmonious balance with the outstanding circuit design improvements. Easily the best buy in kit instruments.

New easy-to-read open panel layout. Off-on switch now incorporated in the selector switch.


MODEL V-7
\$24⁵⁰
Shpg. Wt. 7 lbs.

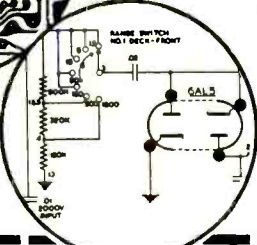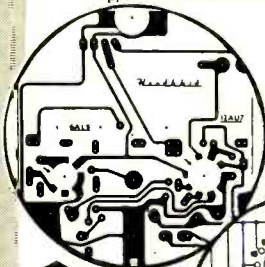New peak-to-peak meter scale—new color harmony—new knobs.



The first kit instrument to offer a labor-saving, error-free printed circuit board. Your instrument an exact wiring replica of Engineering development model.

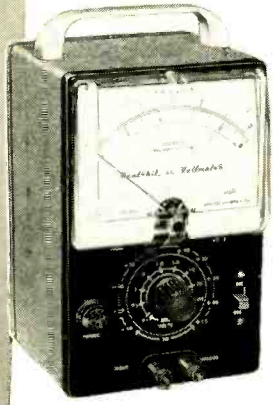Heathkit AC VACUUM TUBE VOLTMETER KIT MODEL AV-2



\$29⁵⁰ Shpg. Wt. 5 lbs.

Extreme sensitivity has been emphasized in the design of the Heathkit AC VTVM. Ten full scale RMS ranges are .01, .03, .1, .3, 1, 3, 10, 30, 100, and 300 volts. Frequency response is substantially flat from 10 cycles per second to 50 KC with input impedance of 1 megohm at 1 KC. Will accurately measure as low as 1 millivolt at high impedance. Total db range is -52 db to +52 db. An excellent kit for measuring

the output of phono cartridges and the gain of amplifier stages. Use it also to check power supply ripple, as a sensitive null detector, and for compiling frequency response data. Features one knob operation, 200 microampere Simpson meter and precision resistors.

Heathkit AUDIO WATTMETER KIT



MODEL AW-1
\$29⁵⁰
Shpg. Wt. 6 lbs.

Read audio power output directly without using external load resistors with the new Heathkit Audio Wattmeter. Built-in non-inductive load resistors provide impedances of 4, 3, 16, and 600 ohms. Flat response from 10 CPS to 250 KC. Full scale power ranges are 0-5 MW, 0-50 MW, 0-500 MW, 0-5 W and 0-50 W. Model AW-1 will operate continuously at 25 watts and has a duty cycle of 3 minutes at 50 watts. Total db range in five positions is -50 db to +48 db, using the standard 1 milliwatt 600 ohms.

Heathkit 30,000 VOLTS DC PROBE KIT

Measure up to 30,000 volts DC with the Heathkit VTVM and the 336 high voltage Probe. Precision resistor provides multiplication factor of 100. Can be used with any 11 megohm input VTVM. Housed in a Polystyrene two color sleek plastic probe body for safety of operation.



**Heathkit PEAK-TO-PEAK
PROBE KIT**



No. 338-C
\$5⁵⁰
Shpg. Wt. 2 lbs.

Peak-to-peak values not exceeding 80 volts at a DC level of not more than 600 volts, can now be read directly by using 338-C Probe with previous model Heathkit VTVM's or any VTVM with 11 megohm input resistance. Probe construction features a modern printed circuit board for easy assembly. Frequency range 5 KC to 5 MC.

Heathkit RF PROBE KIT

The Heathkit RF Probe will permit the measurement of RF voltages up to 250 MC with an accuracy of ±10%. The limits are 30 volts AC and a DC level of 500 volts. Designed for any 11 megohm input VTVM. Modern styling, Polystyrene aluminum housing, Polystyrene insulation, and printed circuit board for easy assembly.



No. 309-C
\$3⁵⁰ Shpg. Wt. 1 lb.

HEATH company
BENTON HARBOR 20,
MICHIGAN

Heathkit 6-12 VOLT BATTERY ELIMINATOR KIT

Here is the new 12 volt Heathkit Battery Eliminator so necessary for modern up-to-date operation of your Service Shop. Furnishes either 6 or 12 volt output which can be selected at the flick of a panel switch. Use the BE-4 to service all of the new 12 volt car radios in addition to the conventional 6 volt models.

RANGES:

This new Battery Eliminator provides two continuously variable output voltage ranges. 0-6 volts D.C. at 10 amperes continuously or 15 amperes maximum intermittent and 0-12 volts D.C. at 5 amperes continuously or 7.5 amperes maximum intermittent. The output voltage is clean and well filtered, as the circuit uses two 10,000 mfd condensers.

The continuously variable voltage output feature is of definite aid in determining the starting point of vibrators, the voltage operating range of oscillator circuits, etc.

OTHER USES:

The controllable low voltage DC supply has many other applications besides primary use in car radio service work. Can be nicely used as a battery charger, or low voltage DC supply for electric trains. Has applications in high gain audio work requiring clean DC filament supply. Can be used for low power electro-plating or as a power supply for battery powered intercommunication systems.

Automatic overload relay—self resetting—fuse protected.

New 18 plate split filter unit.

Continuously variable output voltage, either 6 or 12 volt operation.

Constant ammeter and voltmeter monitoring.

MODEL BE-4

\$31⁵⁰

Shpg. Wt. 17 lbs.



Heathkit VIBRATOR TESTER KIT

MODEL VT-1

\$14⁵⁰

Shpg. Wt. 6 lbs.



This time-saving device will quickly pay for itself in your auto radio service shop. 6 volt vibrators can be checked instantly on the Good-Bad type meter scale. Operation requires only a variable DC voltage from 4 to 6 volts at 4 amperes. Model BE-4 Battery Eliminator is recommended for this application.

Five test sockets provide for the testing of hundreds of interrupter and self-rectifier types. Proper starting voltage is determined easily and accurately. Over-all quality is then unmistakably indicated on the panel mounted meter.

Heathkit IMPEDANCE BRIDGE KIT

MODEL IB-2

\$59⁵⁰ Shpg. Wt. 12 lbs.



The new Heathkit Impedance Bridge features built-in adjustable phase shift oscillator and amplifier. This instrument actually represents four instruments in one compact unit. The Wheatstone bridge for resistance measurements, the Capacity Comparison bridge for capacity measurements, Maxwell bridge for low Q, and Hay bridge for high Q measurements.

DESIGN:

Panel provisions for external generator use. A new two section CRL dial, provides ten separate "units." Ten separate units switch settings and fractions of units are read on a continuously variable calibrated control. A special minimum capacity shielded and balanced impedance matching transformer between the generator and bridge circuit is automatically switched to provide correct load operation of the generator circuit. The instrument uses 1/2% precision resistors and condensers in all measurements circuits.

Heathkit VARIABLE VOLTAGE ISOLATION TRANSFORMER KIT

Variable output voltage between 90 and 130 volts AC. Rated at 100 volt-amperes continuously and 200 volt-amperes intermittently. The principle function of the Heathkit Isolation Transformer is to isolate the circuit being tested from line interference being caused by motors, appliances, etc. It works backward too by isolating such devices from the line.

Many other uses, especially with AC-DC type circuits. Do not confuse the Heathkit Isolation Transformer with the hazardous auto transformer type line voltage boosters.

MODEL IT-1

\$16⁵⁰

Shpg. Wt. 10 lbs.



HEATH company
BENTON HARBOR 20,
MICHIGAN

AUDIO—HIGH FIDELITY

constant (Fig. 3-a) and the equalization is obtained either in a feedback loop as in *c* and *d* of Fig. 2 or by an interstage bypass as in *b* of Fig. 2, If you get a constant variation in response at 10,000 cycles in the same direction on all equalizer positions, you can probably correct the slope by adjusting the load. If the response rises at high frequencies on all positions, you can shunt the preamp input with a resistor (Fig. 3-b). The best thing to do is to connect a 250,000-ohm potentiometer across the preamp input or cartridge output, and adjust it to obtain the flattest possible response in all equalizer positions at 10 kc. When you have found the right position, replace it with a fixed resistor.

If, on the other hand, the variation is downward, put the potentiometer in series with the load resistor (Fig. 3-c) and again adjust for the flattest possible response. If you can't achieve com-

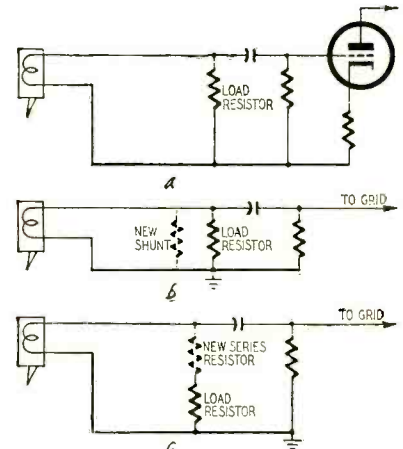


Fig. 3—Circuits for loading pickup.

plete equalization with a change in load, shorten the pickup cable or replace it with one of lower capacitance.

When the departure is only on one curve, check the values of the resistors and capacitors and check for opens or shorts. Resistors should be within 10% of the specified value.

The Dubbings Company has met the need for a test record suitable for rapid testing of phono conditions with its D-100 and D-101 records. The former offers a frequency band with flat treble equalization and a 6-db-per-octave slope below 500 cycles; it also has bands for testing rumble, hum, wow and flutter, as well as stylus compliance and tracking. The D-101 is unique in offering test runs for the four American curves: LP, RIAA, old NARTB, and old AES.

The D-100 will test all aspects of a phono system except needle condition and intermodulation—though the tracking bands offer some clue of needle condition. The first 13 bands are frequencies from 30 to 12,000 cycles. The next band is unmodulated for checking hum and rumble. The following band has a tone suitable for checking wow and flutter. The four innermost bands are

NEW *Heathkit* TV ALIGNMENT GENERATOR KIT

Here is the most radically improved Sweep Generator in the history of the TV service industry. The basic design follows latest high frequency techniques which result in a combination of performance features not found in any other sweep generator.

SWEEP:

Sweep action is obtained electronically through the use of a newly developed controllable inductor, thereby eliminating all moving parts with their resultant hum, vibration, fatigue, etc. Frequency coverage entirely on fundamentals, is continuous from 4 MC to 220 MC at an output level well over a measurable .1 volt.

Triple marker system, 4.5 MC crystal controlled marker—continuously variable marker—provisions for external marker.

MARKER:

The same instrument incorporates a triple marker system with a crystal controlled reference. A variable marker provides accurate coverage from 19 to 60 MC on fundamentals, and 57 to 180 MC on calibrated harmonics. A separate fixed crystal controlled 4.5 MC marker can be used for checking IF, band-pass, calibration, reference, etc. Provisions are also made for external marker use. A 4.5 MC crystal is supplied with the kit.

POWER SUPPLY:

The transformer operated Power Supply features voltage regulation for stable oscillator operation. Three sets of shielded cables are furnished with the kit. Sweep range is completely and smoothly controllable from zero up to a maximum of 50 MC, depending upon base frequency.

Here is a TV Sweep Generator that truly no serviceman can afford to be without for rapid, accurate, TV alignment work.

Controllable inductor sweep oscillator with output entirely on fundamentals.

Triple marker system; 4.5 MC crystal controlled—3 sets of low loss, low capacity shielded cables included.


Electronically operated, smooth, continuous, variable sweep circuit. No vibration, hum or noise.

Frequency coverage: 4 MC—220 MC continuous including FM spectrum. RF output well over .1 volt.


MODEL TS-3

\$44.50

Shpg. Wt. 18 lbs.

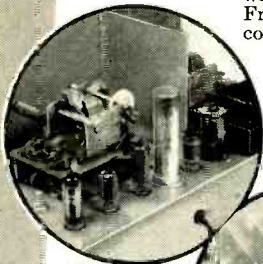

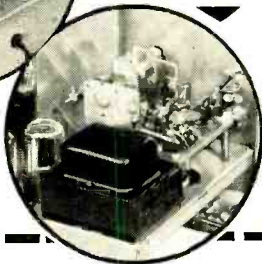Automatic amplitude control circuit—constant output voltage regulated power supply.



NEW *Heathkit* SIGNAL GENERATOR KIT

MODEL SG-8

\$19.50 Shpg. Wt. 8 lbs.

The new Heathkit service type Signal Generator, Model SG-8 incorporates many design features not usually found in this instrument price range. Frequency coverage is from 160 KC to 110 MC in five ranges, all on fundamentals, with useful calibrated harmonics up to 220 MC. The RF output level is well in excess of 100,000 microvolts throughout the frequency range. The oscillator circuit consists of a twin triode tube, one-half used as a Colpitts oscillator, and the other half as a cathode follower output which acts as a buffer between the oscillator and external load, thereby eliminating oscillator frequency shift usually caused by external loading.

All coils are factory wound and adjusted, thereby completely eliminating the need for individual calibration and the use of additional calibrating equipment. The stable, low impedance output, features step and variable attenuation for complete control of RF level. A separate 6C4 triode acts as a 400 cycle sine wave oscillator, and a panel mounted switching system permits choice of either external or internal modulation.

Heathkit LABORATORY GENERATOR KIT

The new Heathkit Laboratory type Signal Generator definitely establishes a new performance standard for a kit instrument. An outstanding feature involves the use of a panel mounted 200 microampere meter calibrated both in microvolts and percent modulation, thereby providing a definite reference level for using the Signal Generator in design work, gain measurements, selectivity, frequency response checks.

DESIGN:

Additional design features are copper plated shield enclosure for oscillator and buffer stages resulting in effective double shielding. Fibre panel control shaft extensions in RF carrying circuits, thorough AC line filtering, careful shielding of the attenuator network, voltage regulated B plus supply, selenium rectifier, etc.

RANGES:

Frequency coverage from 150 KC to 30 MC all on fundamentals in five separate ranges. Output voltage .1 volt with provisions for metered external or internal modulation. Output impedance termination 50 ohms. Transformer operated power supply.

Investigate the many dollar stretching features offered by the LG-1 before investing in any generator for Laboratory or Service work.




MODEL LG-1

\$39.50

Shpg. Wt. 16 lbs.

NEW *Heathkit* BAR GENERATOR KIT

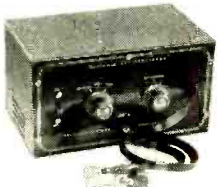

MODEL
BG-1

\$14.50 Shpg. Wt. 4 lbs.

The Heathkit BG-1 produces a series of horizontal or vertical bars on a TV screen. Since these bars are equally spaced, they will quickly indicate picture linearity of the receiver under test without waiting for transmitted test patterns. Panel switch provides "standby—horizontal and vertical position." The oscillator unit uses a 12AT7 twin triode for the RF oscillator and video carrier frequencies. A neon relaxation oscillator provides low frequency for vertical linearity tests. The instrument will also provide an indication of horizontal and vertical sync circuit stability as well as overall picture size. Operation is simple and merely requires connection to the TV receiver antenna terminal. Transformer operated for safety.

HEATH company
BENTON HARBOR 20,
MICHIGAN

Heathkit VISUAL-AURAL SIGNAL-TRACER KIT

The new Heathkit Visual-Aural Signal Tracer features a special high gain RF input channel used in conjunction with a newly designed wide frequency range demodulator probe. High RF sensitivity permits signal tracing from the receiver antenna input. Separate low gain channel and probe available for audio circuit exploration. Both input channels are constantly monitored by an electron ray beam indicator so that visual as well as aural indications may be obtained.

NOISE LOCATOR:

A decidedly unusual feature is a noise locator circuit used in conjunction with the audio probe. With this system, a DC potential is applied to a suspected circuit component and the action of the voltage in the component can be seen as well as heard. Invaluable for ferreting out noisy or intermittent condensers, noisy resistors, controls, IF and power transformers, etc.

WATTMETER:

Built-in calibrated wattmeter circuit will prove useful for quick preliminary check of total wattage consumption of equipment under test. Separate panel terminals provide external use of the speaker or output transformer for substitution purposes. Saves valuable service time by eliminating the necessity for speaker removal on every service job. The same panel terminals also provide easy access to a well filtered B plus supply for external use. Don't overlook the many interesting service possibilities provided through the use of this instrument, and let the Signal Tracer work for you by saving time and money.

Substitution test speaker—utility amplifier.

Noise locator circuit—calibrated wattmeter.


RF and audio probes supplied along with necessary test leads.

Visual and aural signal tracing.

MODEL T-3
\$23⁵⁰

Shpg. Wt. 9 lbs.

Heathkit CONDENSER CHECKER KIT

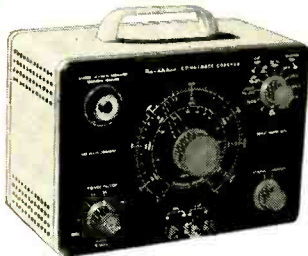

MODEL C-3


\$19⁵⁰ Shpg. Wt. 7 lbs.

Here is a handy test instrument for any Service Shop. Unknown values of capacity and resistance are quickly determined on the direct reading condenser checker dial. Capacity is measured in four ranges from .001 mfd to 1000 mfd. Resistance in the range from 100 ohms to 5 megohms.

DC polarizing voltages of 25, 150, 250, 350, and 450 volts are available for leakage tests on all types of condensers. For electrolytics, a power factor control is provided to balance out inherent leakage and to indicate directly the power factor of a condenser under test. Proper balancing of the AC bridge is reflected in the degree of closure of an electron beam indicator tube.

Model C-3 uses a transformer operated power supply, spring return leakage test switch, and a convenient combination of panel scales for all readings. Test leads are furnished in addition to precision components for calibrating purposes. Quick and easy to operate, the Heathkit Condenser Checker will save valuable time and increase your Shop efficiency.

Heathkit "Q" METER KIT

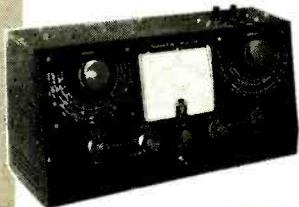

MODEL QM-1

\$44⁵⁰

Shpg. Wt. 14 lbs.

The Heathkit QM-1 represents the first practical popular priced Q meter available within the price range of schools, laboratories, TV service men, and experimenters. This instrument will enable the operator to simulate conditions encountered in practical circuits and to measure the performance of coils or condensers at the operating frequencies actually encountered. All indications of value are read directly on the 4 1/2" 50 microampere Simpson calibrated meter scale. Measures Q of condensers, RF resistance, and the distributed capacity of coils. Oscillator section supplies RF frequencies 150 KC to 18 MC in four ranges. Calibrate capacity with range of 40 MMF to 450 MMF with vernier of ±3 MMF. Investigate the many services this instrument can perform for you.

Heathkit AUDIO OSCILLATOR KIT



MODEL AO-1

\$24⁵⁰

Shpg. Wt. 10 lbs.

The Heathkit Audio Oscillator will produce both sine and square waves within the frequency range from 20 CPS to 20 KC in three ranges. Thermistor controlled linearity results in a variation of no more than ±1 db in a 10 volt (no load) variable output level. There will be less than .6% distortion from 100 CPS throughout the audible range. Low impedance 600 ohm output. Precision 1% resistors, used in the range multiplier circuits to provide accurate calibration.

HEATH company
BENTON HARBOR 20,
MICHIGAN

AUDIO—HIGH FIDELITY

unique in that they offer a simple test for compliance tracking ability. These bands are modulated with a 400-cycle tone whose amplitude increases by 4 db from band to band, so that the innermost band is 12 db higher than the outermost. Poor compliance or tracking is indicated by a buzzing or a fuzziness of tone. Only the highest quality professional pickups and arms will track all four bands perfectly; good home systems, however, should track at least the first two perfectly.


D-101 is a most useful record which tests equalization for the four American curves. Do not expect complete flatness. Few equalizers provide exact equalization for all curves. As long as the variation does not exceed 2 or 3 db, for any curve, reproduction will be considered satisfactory.

TO BE CONTINUED

MILLIONTH TRANSISTOR



A milestone in transistor history was reached on June 15 when Raytheon produced its one-millionth transistor. The company, which states that it has produced three times as many transistors as all other manufacturers combined, made point-contact transistors available in 1948. In late 1952 it began production on germanium junction units, which comprise the large majority of all transistors made to date. So far, most of Raytheon's transistor output has gone to the hearing aid industry. The photo shows Charles R. Adams, Jr. (left), president of the Raytheon Manufacturing Co., presenting the one-millionth transistor to Massachusetts Governor C. A. Herter.

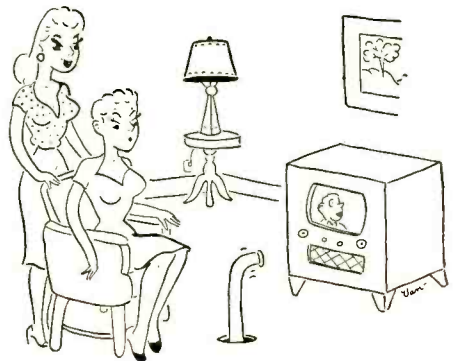

"Even while in his workshop, he can't stand to miss his programs."

Heathkit TUBE CHECKER KIT

The Heathkit TC-2 Tube Checker was primarily designed for the convenience of radio and TV servicemen and will check the operating quality of tubes commonly encountered in this type of work. Test set-up procedure is simplified, rapid, and flexible. Panel sockets accommodate 4, 5, 6, and 7 pin tubes, octal and loctal, 7 and 9 pin miniatures, 5 pin Hytron, and a blank socket for new tubes. Built-in neon short indicator, individual 3-position lever switch for each tube element, spring return test switch, 14 filament voltage ranges, and line-set control to compensate for supply voltage variations, all represent features of the TC-2.

Illuminated for easy reading and quick identification of chart reference.

Simplified construction—new harness type wiring—closer tolerance resistors

Smart, professional appearance—a valuable in counter or portable models.

Improved smooth running roll chart mechanical action.



Three color Good B.A.D. 1 1/2" plastic cased meter.

MODEL TC-2

\$29.50


Shpg. Wt. 12 lbs.

Heathkit PORTABLE TUBE CHECKER KIT

The portable model is supplied with a strikingly attractive two-tone cabinet finished in rich maroon proxylin impregnated fabric covering with a contrasting gray on the inside of the detachable cover.


MODEL TC-2P
\$34.50

Shpg. Wt. 15 lbs.

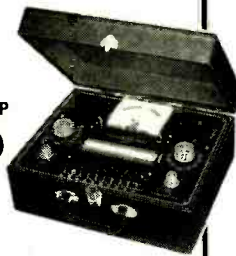

Results of tube tests are read directly from the large 4 1/2" Simpson 3-color meter. Checks emission, shorted elements, open elements, and continuity. Wiring procedure has been simplified through the use of multi-wired color coded cable providing a harness type installation between tube sockets and lever switches. This procedure insures standard assembly and imparts a "factory built" appearance to the instrument. New Construction Manual furnishes detailed information regarding tube set-up procedure for testing of new or unlisted tube types. No delay necessary for release of factory data.

Heathkit REGULATED POWER SUPPLY KIT

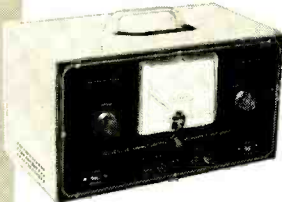

MODEL PS-2
\$33.50 Shpg. Wt. 15 lbs.

Here is a source of regulated D.C. voltage for circuit development work. Power supply voltage and current drain to the circuit under test are constantly monitored by the 4 1/2" panel mounted meter. Separate 6.3 volt at 4 ampere A.C. filament source available. The regulated and variable output voltage will be constant over wide load variations, and hum ripple will not exceed .012% at 250 volts under a 50 MA load. Completely isolated circuit, standby switch, and other desirable features, make the Model PS-2 extremely useful in a wide variety of applications.

Heathkit TV PICTURE TUBE TEST ADAPTER

The Heathkit TV Picture Tube Test Adapter used with the Heathkit Tube Checker Kit, will quickly check picture tubes for emission, shorts, etc. and determine tube quality. Consists of standard 12-pin TV tube socket, four feet of cable, octal socket connector, and data sheet.



No. 355

\$4.50 Shpg. Wt. 1 lb.

Heathkit DECADE RESISTANCE KIT



MODEL DR-1
\$19.50
Shpg. Wt. 4 lbs.

Twenty 1% resistors are decade in 1 ohm steps to provide any value between 1 ohm and 99,999 ohms. Sturdy ceramic switches with silver plated contacts insure reliable service. Use the Decade Resistance in bridge circuits, meter multipliers, calibrations, or any application requiring a wide range of precision resistance values.

Heathkit AUDIO GENERATOR KIT

Here is an Audio Generator with features generally found only in the most expensive instruments. Sine wave coverage from 20 cycles to 1 Megacycle—response flat ± 1 db from 20 cycles to 400 Kc—continuously variable and step attenuated output. Because the output voltage is relatively constant over wide frequency ranges, the AG-8 is ideal for running frequency response curves in audio circuits. Once set by means of the attenuator, this voltage may be relied upon for accuracy within ± 1 db. Instrument features low impedance 600 ohm output circuit and distortion less than .4 of 1% from 100 CPS through audible range.



MODEL AG-8
\$29.50

Shpg. Wt. 11 lbs.

Heathkit DECADE CONDENSER KIT

The Heathkit Decade Condenser provides a ready source of capacity values from 100 mmf to .111 mfd inclusive in capacity steps of 100 mmf. Silver plated contacts on husky ceramic switches, assure positive contact for each switch position. Precision silver mica condensers $\pm 1\%$ accuracy for close tolerance accurate work.

MODEL DC-1
\$16.50
Shpg. Wt. 3 lbs.



HEATH company

BENTON HARBOR 20,
MICHIGAN

NEW *Heathkit* HIGH FIDELITY PREAMPLIFIER KIT

Here is the exciting new Heathkit Preamplifier with all of the features you audiophiles have asked for and at a down-to-earth price level. Beautiful satin gold baked enamel finish, striking control knobs and arrangement, attractive custom appearance and entirely functional design.

DESIGN:

Uses three twin triode tubes in a shock mounted chassis, 2-12AX7 and 1-12AU7. Features tube shielding, plastic sealed color coded capacitors, smooth acting controls, good filtering, excellent decoupling, low hum and noise level, and all aluminum cabinet. Special balancing control for absolute minimum hum level. Cathode follower, low impedance output circuit for complete installation flexibility.

SPECIFICATIONS:

Provides five switch selected inputs, 3 high level, and two low level, each with individual level controls—4 position LP, RIAA, AES, and early 78 equalization switch—4 position roll-off switch, 8, 12, 16 with one flat position. Separate tone controls, bass 18 db boost and 12 db cut at 50 CPS, treble 15 db boost, and 20 db cut at 15,000 CPS. Power re-

Equalization for LP, RIAA, AES, and early 78.

Separate bass and treble tone controls—special hum control.



Cathode follower low impedance output circuit.

Beautiful, modern appearance, blends with any interior or color scheme.

Five switch selected inputs with individual level controls.

Requirements from Heathkit Williamson Type Amplifier power supply 6.3 volts AC at 1 ampere, and 300 volts DC at 10 MA. Over-all dimensions 12 1/8" wide x 5 1/4" deep x 3 3/8" high.

APPLICATION:

The new Heathkit WA-P2 Preamplifier has been designed to operate with any of the Heathkit Williamson Type Amplifiers and is directly interchangeable with the previous Model WA-P1 Preamplifier unit. Order your kit today and enjoy completely smooth control over the operation of your Hi-Fi system. Obtain the exact tonal balance of bass and treble with the precise degree of equalization you want. Note that the design of the WA-P2 accommodates the newly established RIAA curve.

MODEL WA-P2

\$19.75

Shpg. Wt. 7 lbs.

HAM EQUIPMENT

Single knob band switching—pre-wound coils.



Crystal or VFO excitation—metered operation. 52 Ohm coaxial output—built-in power supply.

MODEL AT-1

\$29.50

Shpg. Wt. 16 lbs.

filter, good shielding and a 52 ohm coaxial output. The 425 volt, 100 milliamper power supply and 5U4 rectifier are more than adequate for the 6AG7 oscillator multiplier and 6L6 amplifier doubler.

Heathkit
AMATEUR

TRANSMITTER KIT

The Heathkit AT-1 Transmitter has established a high reputation and has been enthusiastically accepted by hundreds of experienced operators as well as beginners. Power input up to 35 watts for the novice and suitable as a standby exciter for your higher powered rig later on.

Model AT-1 can be crystal or VFO excited and operates on 80, 40, 20, 15, 11 and 10 meters. The pre-wound coils with the oscillator and amplifier are switched simultaneously by the rugged band switch. Meter switch allows a reading of the final grid and plate current on the panel mounted meter. Modulator input and VFO power sockets are provided as well as a key jack for CW operation. Other features include a crystal socket, standby switch, key click filter, AC line

Brand
NEW

Smooth acting illuminated and precalibrated dial.

HEATHKIT VFO KIT

The new Heathkit VFO is the perfect companion to the Heathkit Model AT-1 Transmitter and it has sufficient output to drive any multi-stage transmitter of modern design. Good mechanical and electrical design insures operating stability. Coils are wound on stable, heavy duty, ceramic forms using Litz or double cellulose wire coated with Polystyrene cement and baked for humidity protection. Variable capacitor of differential type construction, especially designed for maximum bandspread. Kit is furnished with a carefully precalibrated scale which provides well over two feet of scale length. Smooth acting vernier reduction drive and illuminated dial provides easy tuning and zero beating.

Power requirements 6.3 volts AC at .45 amperes, and 250 volts DC at 15 mls. Just plug it into the power receptacle provided on the rear of the AT-1 Transmitter. Seven band coverage 160 through 10 meters with 10 volt average RF output. Uses 6AU6 electron coupled Clapp oscillator and OA2 voltage regulator.

Copper plated chassis—aluminum cabinet—easy to build.



Seven band coverage 160 through 10 meters at 10 volt RF output.

6AU6 electron coupled Clapp oscillator and OA2 voltage regulator.

MODEL VF-1

\$19.50

Shpg. Wt. 7 lbs.

Heathkit

GRID DIP METER KIT

The invaluable instrument for Hams, servicemen and experimenters. Useful in TV service work, for alignment of traps, filters, IF stages, peaking compensation networks, etc. Locates spurious oscillation, provides a relative indication of power in transmitter stages. Use it for neutralization, locating parasites, correcting TVI, measuring CL and Q of components, and determining RF circuit resonant frequencies. The variable meter sensitivity control, headphone jack, 500 microampere Simpson meter, continuous frequency coverage from 2 MC to 250 MC. Pre-wound coil kit and rack included.

LOW FREQUENCY COILS:

Low frequency range extended to 355 KC by the use of two additional coils. Complete with dial correlation curves. Set 341-A for GD-1B and set 341 for GD-1A. Shpg. wt. 1 lb. Price \$3.00



MODEL GD-1B

\$19.50

Shpg. Wt. 4 lbs.

Heathkit ANTENNA

IMPEDANCE METER KIT



MODEL AM-1

\$14.50

Shpg. Wt. 2 lbs.

Determine antenna resonance and resistance, transmission line surge impedance, and receiver input impedance. Works with one-half and one-quarter wave lines, half wave and folded dipoles, harmonic mobile and beam antennas. Resistance type SWR bridge—100 microampere meter—frequency range 0-150 MC—impedance range 0-600 ohms.



MODEL AC-1

\$14.50

Shpg. Wt. 4 lbs.

Heathkit

ANTENNA COUPLER KIT

For the Heathkit AT-1 Transmitter or any comparable Amateur Transmitter. Will handle power up to 75 watts at its 52 ohm coaxial input. Matches a wide range of antenna impedances with its L type tuning network and neon indicator. A tapped inductance provides coarse adjustment and a transmitting type variable condenser sets it "right on the nose." Will operate on the 10 through 80 meter bands.

HEATH company

BENTON HARBOR 20,
MICHIGAN

New LOW PRICED HEATHKIT SINGLE UNIT Williamson Type High Fidelity AMPLIFIER KIT

Here is the newest Heathkit Hi-Fi Amplifier at the lowest price ever quoted for a complete Williamson Type Amplifier circuit. The W-4 Model has been designed for single chassis construction, and only for the new Chicago Transformer Company Model BO-13 "super range" high fidelity output transformer. This transformer, a new development in the Hi-Fi field, is being offered at substantial saving over transformers of comparable quality. It is outstanding in performance and on the basis of our tests, we find it equal in every respect to transformers used in the W-2 and W-3 Heathkit series.

LOW PRICES:

Through utilization of a single chassis with resultant economy obtained through elimination of duplicate sheet metal fabrication, connecting cables, plugs, sockets, and a new Chicago "super range" output transformer, a 20% price reduction has been made possible without sacrificing kit quality.


COMPONENTS:

The new Heathkit W-4 uses the same heavy duty power transformer and choke. It has all of the features of previous models including individual jacks and a wire wound control to balance the output tubes—plastic high quality capacitors and the exact circuitry previously utilized in Williamson Type Amplifiers. Intermodulation distortion and harmonic distortion are both at the same low level as in the W-2 and W-3 models.

CONSTRUCTION:

Here is the opportunity for even the economy minded Hi-Fi enthusiast to enjoy all of the advantages offered through Hi-Fi reproduction of fine recorded music. Simplified step-by-step Construction Manual completely eliminates necessity of electronic knowledge or special equipment. Assemble this Amplifier in a few pleasant hours.

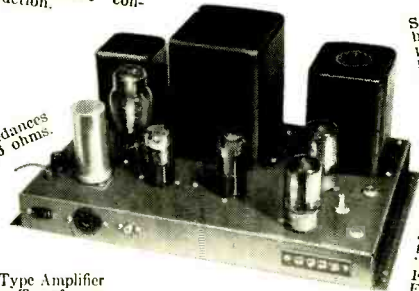Rugged, heavy duty,
single chassis con-
struction.
Output impedances
4, 8, and 16 ohms.



Standard
brand com-
ponents used,
no sacrifice of
quality.

Lowest price high quality
Williamson Type Ampli-
fier ever offered.


Send for
free booklet
"High
Fidelity
Especially
For You."

COMBINATIONS AVAILABLE

W-4M with Chicago "super-range" trans-
former only. Single chassis main amplifier
and power supply. Shipping **\$39.75**
weight 28 lbs. Express only

COMBINATION W-4 with Chicago
"super-range" transformer only includes
single chassis main amplifier and power sup-
ply with WA-P2 preamplifier **\$59.50**
kit. Shpg. wt. 35 lbs. Express only

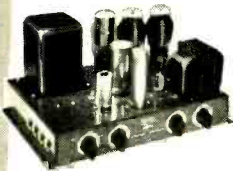NEW Heathkit 20 WATT High Fidelity AMPLIFIER KIT



MODEL A-9B

\$35⁵⁰

Shpg. Wt. 24 lbs.

In keeping with the progressive policy of the Heath Company, further improvement has been made in the already famous Heathkit High Fidelity 20 Watt Amplifier. Additional reserve power has been obtained by using a heavier power transformer. A new output transformer designed and manufactured especially for the Heath Company, now provides output impedances of 4, 8, 16 and 500 ohms. The harmonic distortion level will not exceed 1% at the rated output.

FEATURES:

Outstanding features of the Heathkit 20 watt Amplifier include frequency response of ± 1 db from 20 CPS to 20 KC. Separate (boost and cut) bass and treble tone controls. Four switch selected input jacks and a special hum balancing control. Flexibility is emphasized in the in-

put circuits and proper equalization for all input devices is incorporated.

TUBE LINEUP:

12AX7 magnetic preamplifier and first audio amplifier. 12AU7 two stage amplifier with tone controls. 12AU7 voltage amplifier and phase splitter. Two 6L6 push-pull beam power output and 5U4G rectifier. The Heathkit Model A-9B is excellent for custom installation and is designed for outstanding service at a very reasonable cost.

Heathkit SIX WATT AMPLIFIER KIT



MODEL A-7B

\$15⁵⁰

Shpg. Wt. 10 lbs.

An outstanding value, this economically priced 5 watt Amplifier is capable of performance expected only in much more expensive units. Only 2 or 3 watts output will ever be used in normal home applications and Model A-7B will be more than adequate for this purpose.

SPECIFICATIONS:

Two switch selected inputs are available for crystal and ceramic phono pickups, tuner, TV audio, tape recorder, and carbon type microphone. Model A-7B features separate bass and treble tone controls, push-pull balanced output stages, output impedances of 4, 8, and 15 ohms, and extremely wide frequency range $\pm 1\frac{1}{2}$ db from 20 CPS to 20 KC. Not just a souped up AC-DC job. Full wave rectification, transformer operated power supply and good filtering, result in exceptionally low hum level.

MODEL A-7C

Provides a preamplifier stage and proper compensation for the variable reluctance cartridge and low level microphone. \$17.50

Heathkit WILLIAMSON TYPE AMPLIFIER KIT

Here is the famous kit form Williamson Type high fidelity Amplifier that has deservedly earned highest praise from every strata of Hi-Fi music lovers. Virtually distortionless, clean musical reproduction, full range frequency response, and more than adequate power reserve.

OUTPUT TRANSFORMERS:

This outstanding Williamson Type Hi-Fidelity Amplifier is supplied with the famous Aerosound TO-300 output transformer. This quality transformer features the popular "ultra-linear" output circuit for clean maximum power level. Separate chassis for amplifier and power supply.

SPECIFICATIONS:

Frequency response within 1 db from 10 cycles to 100,000 cycles. Harmonic distortion at 5 watt output less than .5% between 20 cycles and 20,000 cycles. 1M distortion at 5 watts equivalent output, .5% using 60 and 3,000 cycles. Output impedances of 4, 8, or 16 ohms. Overall dimensions for each unit 7" high x 5 $\frac{1}{2}$ " wide x 11 $\frac{1}{2}$ " long.


CONSTRUCTION MANUAL:

This fine kit is supplied with a completely detailed step-by-step Construction Manual and the only effort required is the assembly and wiring of the pre-engineered kit. Even the complete novice can successfully construct this Amplifier and have fun building it.

COMBINATIONS AVAILABLE:

W-3 Amplifier Kit (Includes Main Amplifier with Aerosound Output Transformer, Power Supply and WA-P2 Preamplifier.) Shipping weight 37 lbs. Shipped express only **\$69.50**

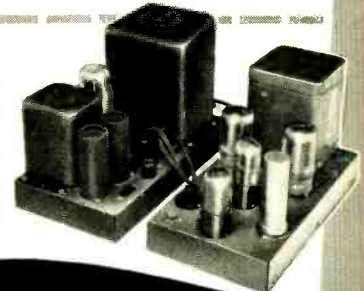W-3M Amplifier Kit (Includes Main Amplifier with Aerosound Output Transformer and Power Supply.) Shipping **\$49.75** weight 29 lbs. Express only



HEATH company

BENTON HARBOR 20,
MICHIGAN

Separate BFO oscillator tube and circuit.

Continuous coverage 550 KC—35 MC on 4 Bands.



MODEL AR-2
\$25.50
 (Less Cabinet)
 Shpg. Wt. 12 lbs.

Phone—standby—CW panel switch.

RF gain control with AGC on-off switch.

Electrical band-spread tuning with logging scales.

Heathkit COMMUNICATIONS RECEIVER KIT

An excellent example of typical Heath Company ability to produce top quality kit merchandise at ridiculously low prices, is the AR-2 Communications Receiver. Here is a transformer operated all-wave receiver with all of the desired features and none of the disadvantages commonly encountered in so-called "economy sets."

Receiver employs high gain miniature tubes and IF transformers, chassis mounted 5½" PM speaker, headphone jack, slide rule dial with Ham Bands plainly identified, and easy tuning with direct planetary drive. Continuous frequency coverage from 550 KC to 35 MC on 4 Bands, with electrical bandspread tuning and logging scales. Other features are RF gain control with AGC on-off switch—phone-standby-CW panel switch—prewound coils in a shielded turret assembly and copper plated chassis and shielding.


Uses 12BE6 mixer-oscillator, 12BA6 IF amplifier, 12AV6 detector-first audio, 12A6 beam power output, 12BA6 BFO oscillator, and 5Y3 rectifier. A lettered control plate is provided for the cabinet of your choice or you can order the optional Heathkit cabinet featuring the full size aluminum panel.

RECEIVER CABINETS

Proxylon impregnated fabric covered plywood cabinet available for BR-2 and AR-2 receivers. Includes aluminum panel, flocked reinforced speaker grill and protective rubber feet.

- For BR-2 Receiver, Cabinet 91-9 \$4.50
Shipping weight 5 lbs.
- AR-2 Receiver, Cabinet 91-10 \$4.50
Shipping weight 5 lbs.

Heathkit FM TUNER KIT

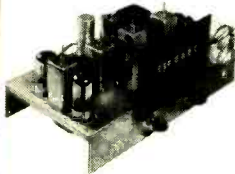

MODEL FM-2
\$22.50

Shpg. Wt. 8 lbs.

Here is an FM Tuner that can be operated with your Hi-Fi Amplifier or through the "phono" section of the ordinary radio. Completely AC operated to eliminate problems usually encountered in "economy type" AC-DC tuner circuits. Features 8 tube circuit with separate mixer and oscillator, 3 double tuned IF stages followed by a limiter discriminator providing maximum sensitivity and selectivity across the full FM frequency band of 88 MC to 108 MC. The tuning unit is factory assembled and adjusted, thus eliminating tedious critical "front end" alignment problems. The attractive slide rule dial and vernier tuning combine to make the Heathkit FM-2 Tuner simple to operate.

Heathkit BROADCAST BAND RECEIVER KIT



MODEL BR-2
\$17.50

(Less Cabinet)
 Shpg. Wt. 10 lbs.

The Model BR-2 Broadcast Band Receiver is designed especially for the beginner without any sacrifice of quality. This receiver features a transformer operated power supply, high gain miniature tubes, sharply tuned IF transformers, new rod type built-in antenna, and a trouble-free planetary tuning system. Exceptional performance with unusually high sensitivity, good selectivity, and excellent tone quality from the 5½" PM chassis mounted speaker. Can be used either as a receiver, tuner, or phono amplifier. Uses 12BE6 mixer-oscillator, 12BA6 IF amplifier, 12AV6 detector, 12A6 beam power output, and 5Y3 rectifier.

HEATH COMPANY • Benton Harbor 20, Mich.

ORDER BLANK



MAIL YOUR ORDER TODAY TO THE
HEATH COMPANY
 BENTON HARBOR 20,
 MICHIGAN

WALNUT 5-1175

From _____

SHIP VIA

- Parcel Post
- Express
- Freight
- Best Way

QUANTITY	ITEM	MODEL NO.	PRICE

Enclosed find () check () money order for _____
 Please ship C.O.D. () postage enclosed for _____ pounds.

On Express orders do not include transportation charges—they will be collected by the express agency at time of delivery.

ON PARCEL POST ORDERS insure postage for weight shown. ORDERS FROM CANADA and APO's must include full remittance.

HIGH-QUALITY AUDIO

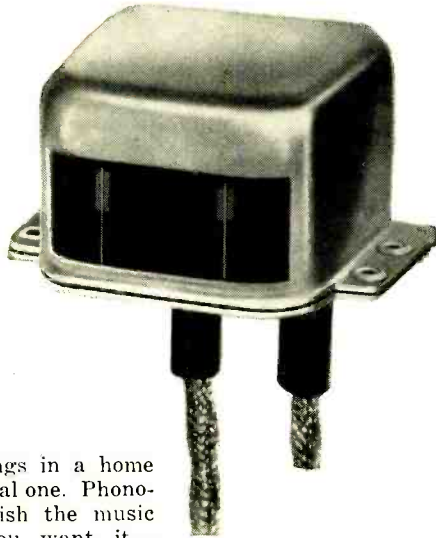


Fig. 1—Shure recording - playback head.

THE role of recordings in a home music system is a vital one. Phonograph records furnish the music you want when you want it—assuming, of course, the music you want has been recorded and you can afford to buy it. And home recording has recently assumed a very much different meaning from the one it had when tape was not available and when high fidelity was an experimental hobby of a few instead of the religion of millions.

Tape recorders are plentiful today and simple to operate. A great many music system owners use them as part and parcel of their equipment to supplement the music supply and to have just plain fun. But because tape machines are easy to get and use, it does not mean they are ideal for every purpose. Nor does it mean that the serious music enthusiast need know nothing about them. There is the matter of selection of an appropriate recorder, of how to “build” it into the system, and of how to use and maintain it to best advantage.

The basic idea of tape recording is extremely simple. The tape is a paper or plastic material coated with fine particles of iron oxide in an adhesive binder. The tape passes over an electromagnet, the field strength of which is varied by the incoming audio program. The tape is thus magnetized at varying strengths along its length, the comparative strengths being a record of each audio wave in turn. In playback, the tape is passed over a similar electromagnet whose coil is connected to the input of an amplifier. The moving magnetic lines of force from the tape are picked up by the electromagnet core and cut the wires of the coil, inducing in them voltages of varying amplitude. These are amplified and the audio is thus re-created.

The electromagnet in recording is

Part XV—Tape recorders—mechanical and electrical characteristics

By RICHARD H. DORF*

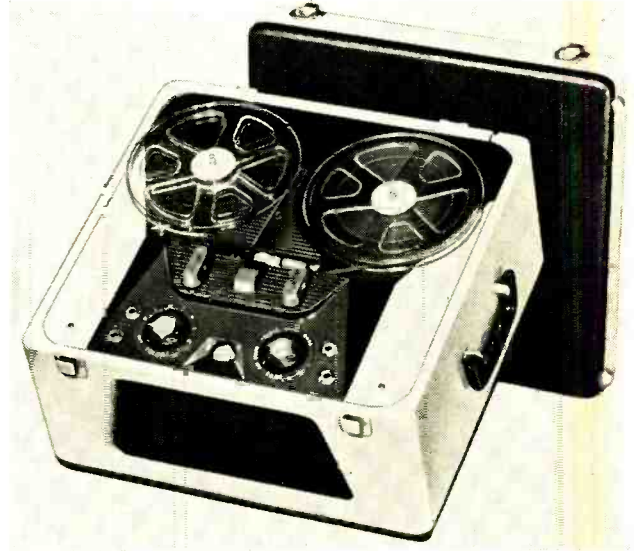


Fig. 2—The Pen-tron tape recorder.



Fig. 3—Concertone tape recorder.

*Audio Consultant, New York City

ELECTRICAL
ENGINEERS
or
PHYSICS
GRADUATES

with experience in
RADAR
or
ELECTRONICS
or those desiring to enter
these areas...

The time was never
more opportune than
now for becoming
associated with the field
of advanced electronics.
Because of military
emphasis this is the most
rapidly growing and
promising sphere
of endeavor for the
young electrical
engineer or physicist.

Since 1948 Hughes Research and Development Laboratories have been engaged in an expanding program for design, development and manufacture of highly complex radar fire control systems for fighter and interceptor aircraft. This requires Hughes technical advisors in the field to serve companies and military agencies employing the equipment.

As one of these field engineers you will become familiar with the entire systems involved, including the most advanced electronic computers. With this advantage you will be ideally situated to broaden your experience and learning more quickly for future application to advanced electronics activity.

Positions are available in the continental United States for married and single men under 35 years of age. Overseas assignments are open to single men only.

Scientific and Engineering Staff

RESEARCH AND
DEVELOPMENT
LABORATORIES

Culver City,
Los Angeles County,
California

Assurance is required that relocation of the applicant will not cause disruption of an urgent military project.

HUGHES

AUDIO—HIGH FIDELITY

the recording head and the other electromagnet mentioned is the playback head. They are so much alike in requirements (though not necessarily identical) that a single head is often used for both purposes with appropriate circuit switching. The Shure type 815 head (Fig. 1) is an example. Such heads are used in all of the less expensive nonprofessional machines, such as the Pentron shown in Fig. 2. Professional recorders such as the Concertone (Fig. 3) have separate heads. This has a dual advantage. First, each head can be designed for particular application. Second, with separate heads for recording and playback, the recording can be monitored from the tape during the recording process.

Fig. 4 is a diagram of one kind of recording or playback head, viewed from the edge of the tape. The core

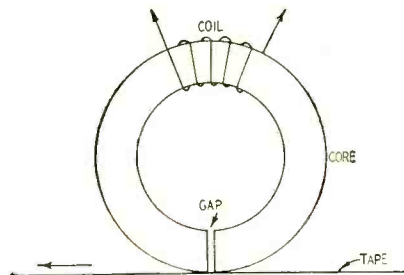


Fig. 4—Construction of recording head.

is a ring of magnetically "soft" material with high permeability. Such a material is very easily magnetized but does not retain appreciable magnetism when the current is removed from the coil. A typical substance is mu-metal.

The iron-oxide coating of the tape is magnetically "hard"; that is, once magnetized, it retains much of its magnetism for a long period. The tape moves continuously over the small gap in the core. When magnetic lines of force pass through the core they find the reluctance, or magnetic resistance of air (or whatever other material may fill the gap) is comparatively high. These lines pass more easily through the tape coating, and in doing so they magnetize the coating within the gap. Since the strength of the field varies with the audio, each successive small area of tape coating that passes the gap is magnetized to a somewhat different field strength.

In playback, the tape may again be passed over the same head. This time the coil is connected to an amplifier input. As each little magnetized section of tape passes the gap, its magnetic field causes lines of force to pass through the core and cut the coil. The induced voltage is then amplified.

The first complication comes through magnetic hysteresis. When an unmagnetized tape is subjected to a magnetic field of certain strength, it is magnetized to a corresponding strength (over a certain range). However, when the magnetic field is removed (the section of tape leaves the head), the tape magnetism falls to a certain lesser

Save time—Step up efficiency in ELECTRONICS DESIGN

Here's a wealth of technical help for efficiently handling electronics design problems—help that gives you answers already worked out by the country's top electronics men!—help that can save you hours of research and experimentation!

You'll find electronics mathematics and theory in concise form—design practices for hundreds of pieces of electronics equipment—and even the results of advanced electronic experiments. Radio, television, facsimile, sound, and scores of other phases of electronics are covered—and it's all condensed, classified, and indexed for quick, easy use.

The McGraw-Hill

ELECTRONICS DESIGN LIBRARY

Edited by John Markus and Vin Zeluff
Associate Editors, ELECTRONICS
Four volumes, 2151 pages, 9 x 12,
3534 charts, diagrams,
and illustrations, \$33.00
Easy terms—low price
saves you \$6.00

This Library contains 1083 articles culled from recent issues of ELECTRONICS Magazine the cream of the information essential to those working with or concerned with the design of electronics equipment. For instance, you'll find

—4 Big Volumes—

Electronics for
Engineers

Handbook of Industrial Electronic Circuits

Electronics Manual for Radio Engineers

Electronics for Communication Engineers

233 diagrams of industrial circuits, measurement methods for television picture tubes, factors in permanent magnet design, and specific help for reading industrial circuits and redesigning them for your own uses.

Every step, method, practice, and procedure is explained in the simplest possible terms, with literally thousands of charts and diagrams to make clear the text.

Included are not only the measuring and operating techniques used by radio designers and technicians, but also a wealth of engineering aids for parts and equipment design of television, radar, and other vacuum tube apparatus.

Special price
saves you \$6.00

See books 10 days free before you start easy payments. If bought separately, books would cost \$39—under this plan you pay just \$8 at the end of 10 days and \$5 a month until low price of \$33 is paid—a \$6 saving!

—Production help—

Included too is information for electronics production men—data on quality control, inspection procedures, test equipment, and other factors in manufacturing electronics equipment.

10 DAYS FREE EXAMINATION

McGraw-Hill Book Co., Inc., Dept. RE-11
330 West 42nd St., New York 36, N. Y.

Send me for 10 days' examination the ELECTRONICS DESIGN LIBRARY. In 10 days I will remit \$8.00, plus low cents delivery, then \$5.00 a month until \$33.00 is paid. If not satisfied, I will return books postpaid. (We pay delivery if you remit with this coupon; same return privilege)

(PRINT)

Name

Address

City Zone State

Company

Position

This offer applies to U. S. only

RE-11

AUDIO—HIGH FIDELITY

value. The lesser values vary with the inducing field over only a very small range—not going down to zero. As a result, a sine wave recorded on tape is distorted (Fig. 5). This distortion is removed by ultrasonic bias—a signal of between 30 and 60 kc is superimposed on the audio fed to the head. The signal for bias is generated by an

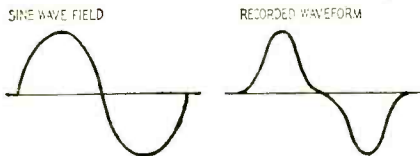


Fig. 5—Sine-wave field is distorted.

oscillator. How it works to remove distortion is too involved for this article—those interested can refer to "What Is Supersonic Bias?," RADIO-ELECTRONICS, January, 1949.

Frequency response

While head inductance causes a change in head reactance as frequency varies, this is usually countered by feeding the head from a constant-current source such as a pentode tube. Since the magnetic field depends on coil current, the recorded magnetism on the tape is fairly constant from low frequencies up to some midrange frequency. Above this point, however, core losses and gap effect reduce the treble. In playback, there is reduction in output between the midrange and the bass, as well as from midrange to treble. Fig. 6 shows the general shape of the output curve of a playback head from a tape recorded without equalization. The lower part of the curve is due to the induced voltage, depending on the speed at which the lines do the cutting. At lower frequencies the velocity is obviously lower; therefore, so is the output.

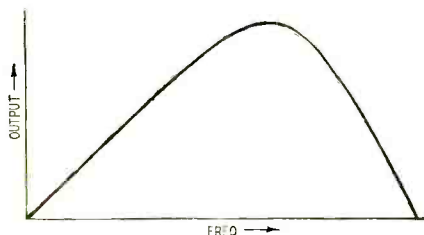


Fig. 6—Output of a playback head.

An additional loss occurs in the treble, due largely to gap effect. In Fig. 4, note that the length of tape played back at any one instant is equal to the gap length. If the gap is very small with respect to a wavelength, say 1/20 wavelength, then it scans only 1/20 of the wave at a time and the output voltage will show a good representation of the wave. Suppose, however, that an entire wavelength fits under the gap at one time. The wavelength contains all values of magnetism from zero to maximum in both directions, the sum total of which—and therefore the head output—is zero. It follows that there is a loss of output as soon as the wave-

8 MASTERPIECES

LONG-PLAYING 33 1/3 R.P.M. HIGH-FIDELITY

COMPLETE TO THE LAST NOTE!

NO STRINGS ATTACHED!

\$1.00

Without obligating yourself to buy another record, you can enjoy all advantages of trial membership.

Long
Playing

NOW YOU can get a real start on a complete record collection. You get ALL EIGHT masterpieces—complete to the last note—for only \$1.00. NOT \$1 each, but \$1 for ALL EIGHT!

Of course, this price bears no relation to the value of the recordings. Even for TWENTY times that amount, you could not buy these masterpieces in recordings of equal quality.

Why We Make This Amazing Offer

We were FORCED to make this "give-away" offer . . . for only by putting our recordings in your hands can we convince you how extraordinary their tonal quality is. Performed by internationally-renowned orchestras, conductors, and soloists. Custom-pressed on the purest vinyl plastic. Reproduced with a fidelity of tone which encompasses the entire range of human hearing . . . 50 to 15,000 cycles!

HOW CLUB OPERATES: As a trial member, you are not obligated to ever buy another record from us. You do, however, have the right to try—free of charge—any of the Society's monthly selections which interest you. You receive prior notice of these. You pay nothing in advance. And you are not obligated to keep those you try . . . even after you have played them and read the interesting music notes which accompany each selection. You pay only for those which—after having tried them—you decide you really want to own. And for these, you pay only the low member's price of \$1.50 per long-playing disc, embodying on the average about 40 minutes of music by the great masters. A saving of about 2/3 off the usual retail price!

Think how much beauty and serenity these recordings will add to your life—at a trifling cost. Think what a cultural advantage your children will gain by having great music as an everyday inspiration.

Mail Coupon Now

We obviously cannot keep "handing out" such magnificent long-playing recordings indefinitely. Production capacity limits the membership rolls; once filled the offer has to be withdrawn. So avoid disappointment. Rush coupon with a dollar today. *The Musical Masterpiece Society, Inc., Dept. 5211, 43 West 61st Street, New York 23, N. Y.*

Not \$1 each, but \$1 for all 8!

SCHUBERT

Symphony No. 8
(The "Unfinished"),
Zurich Tonhalle Orch.,
Otto Ackermann, Conducting

BETHOVEN

The Ruins of Athens
(March and Choir),
Netherlands Philharmonic
Choir and Orch.,
Walter Goehr, Conducting

BRAHMS

Academic Festival Overture,
Utrecht Symphony,
Paul Huppers, Conducting

MOZART

Piano Concerto in E Flat, K 107
Artur Balsam, piano,
Winterthur Symphony Orch.,
Otto Ackermann, Conducting

BACH

Tocatta and Fugue in D Minor,
A. Schreiner, Organ of the
Tabernacle, Salt Lake City

WAGNER

Die Meistersinger, Prelude, Act 1,
Zurich Tonhalle Orch.,
Otto Ackermann, Conducting

DUKAS

Sorcerer's Apprentice,
Utrecht Symphony,
Paul Huppers, Conducting

MOUSSORGSKY

Night on Bald Mountain,
Netherlands Philharmonic
Walter Goehr, Conducting

FREE "Music in Your Home" by Olin Downes

Mail coupon at once to receive, FREE, fascinating brochure by dean of American music critics. A guide to the valuable program notes and musical annotations which come free with every selection.



The Musical Masterpiece Society, Inc. Dept. 5211
43 West 61st Street, New York 23, N. Y.

ALL 8 MASTERPIECES—\$1.00

Here is my dollar in complete payment; please send me ALL 8 of the masterpieces listed above and enroll me as a trial member. Send me notice of future selections which I may try for 5 days without cost or obligation. For those future l.p. discs I decide to keep after I have tried them, I will pay only the special member's price of \$1.50 each, plus few cents shipping. I may cancel my trial membership at any time.

Name.....

Address.....

City..... State..... 5211

In Canada address: 686 Bathurst St., Toronto 4, Ont.

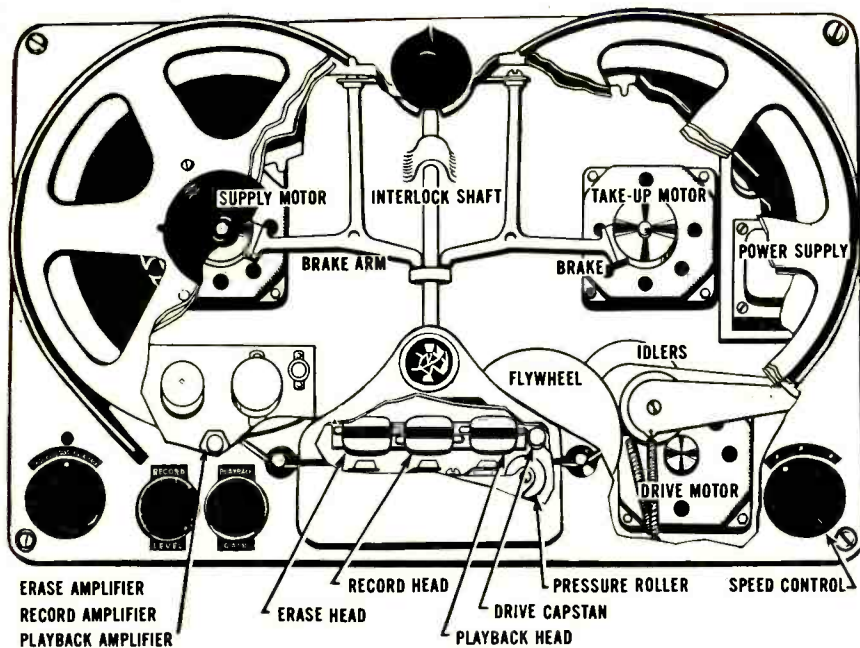


Fig. 7—Concertone mechanical system.



Fig. 8—Presto 6-N recording assembly.

length of recorded sound on the tape begins to approach the length of the gap, and that there is total loss when the wavelength and gap are equal. The losses are rather easy to calculate and the results show that loss is 6 db when the gap is 0.6 wavelength, about 13 db when it is 0.8 wavelength, and so on. This largely accounts for the rather sharp dropoff of highs in the curve of Fig. 6.

There are two ways of extending the high-frequency response before it is necessary to equalize electrically for the rest. They are important, because equalization causes loss of gain, increased noise, and is seldom obtained with real precision. First, the gap should be made as small as possible. Second, the length of waves can be increased by making the tape run

faster; this spreads out each wave over a longer bit of tape.

Let us take a numerical example. Suppose the gap is 1 mil (.001 inch) long, and the tape is running at 7.5 i.p.s. (inches per second). In the 7.5 inches of tape running past the head each second there are 7,500 segments, each 1 mil long. If, therefore, we record 7,500 cycles, each wave will be as long as the gap, and output at this frequency will be zero, no matter how hard we try to equalize.

Now suppose we halve the gap length. Wavelength becomes twice the gap length and the output droop due to gap effect is only about 4 db. (It is actually a good deal more, due to core losses in both recording and playback heads.) Or suppose we leave the gap at 1 mil and run the tape twice as fast—at 15

i.p.s. The result is the same. In actual practice, manufacturers try to keep effective gap width to around 0.5 mil. This makes reproduction to 15,000 cycles impossible, but, with equalization, satisfactory response is possible to around 10,000 and output can easily be linear to 7,500 cycles, at 7.5 i.p.s. Raising the speed to 15 i.p.s. gives full linear 15,000-cycle response, necessary for high fidelity. A few manufacturers have succeeded in reducing core losses and controlling gap length effectively enough to make possible responses more extended than these.

While you are unlikely to design or manufacture tape recorders from the above information, it does show a couple of important points to remember when buying and using a machine. The 3.75-i.p.s. speed with which most inexpensive recorders are equipped simply does not do for good sound. It is usable only for speech—and even then it is suitable only for record purposes, not when the speaker's voice must sound with faithfulness. The 7.5-i.p.s. speed is also—except on a very few machines—unacceptable for high fidelity since its results will be much below those obtained from your tuner and records.

Mechanical system

This part of a tape recorder is as important as the electrical characteristics. Fig. 7 is a cutaway drawing giving some idea of the mechanical system of the Concertone shown in Fig. 3.

There are three motors. The principal one is the drive motor which is coupled to a capstan. Between the capstan and a pressure roller, the tape is pinched. Constant tape speed depends on this drive system. In less expensive models the drive motor is a 4-shaded-pole unit. These being subject to speed changes with load changes, a better model is available with a motor synchronized by the 60-cycle power frequency and almost completely free of speed changes. This is extremely important, because speed changes cause variations, slow and fast, of music pitch, a more annoying defect than perhaps anything else.

The take-up motor drives the take-up reel. During recording and playback its power is reduced with a series lamp so that it is just strong enough to make sure the tape winds up tight, but not strong enough to affect the speed of the drive capstan. The supply motor is similar. During recording and playback it is off entirely; during rewind it is on full. A better system, utilized in other machines, supplies a small amount of power so that the supply reel cannot spill tape even if it is not braked. In this model a mechanical brake stops the reels when the drive capstan is not pulling tape.

In using recorders, it is essential that power not be removed from the motors while the mechanical system is engaged; that is why mechanical con-

NOW!

THESE FAMOUS ORIGINAL EQUIPMENT FAVORITES

available through selected
local distributors

for SERVICE • EXPERIMENTAL • INDUSTRIAL • *and* MILITARY uses

For over 25 years, these Stackpole components have been sold only direct from the factory in huge production quantities to the world's leading equipment manufacturers.

Now, for the first time, you can get them in lots of up to 1,000 through selected parts distributors . . . fast and economically.


Every Stackpole component is produced under full quality control that extends from raw materials to final tests. And each type is fully proved through years of field service in the most exacting applications—military, service replacement, and commercial.

Write for bulletin on any type and name of nearest distributor.


STACKPOLE




Iron Cores

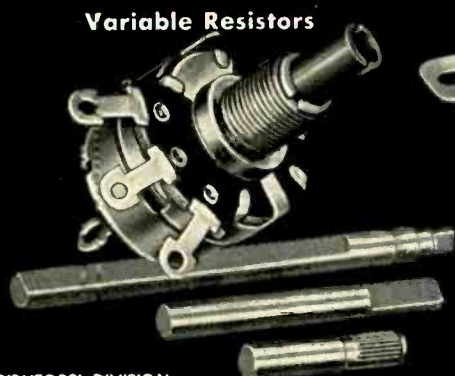

Variable Resistors

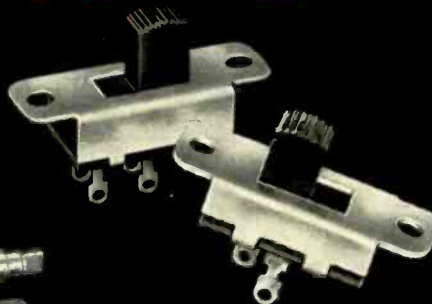

Low Cost Slide Switches

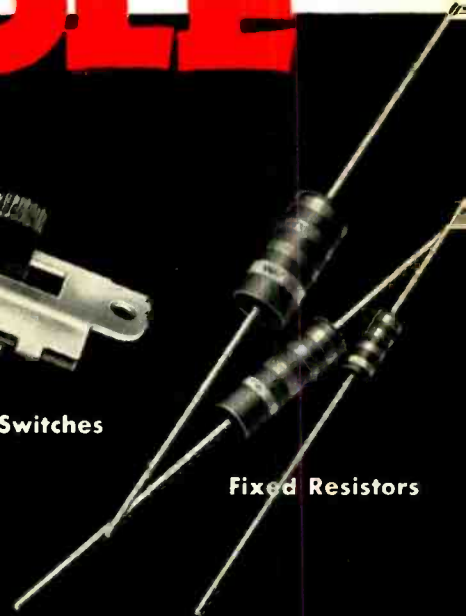

Fixed Resistors

DISTRIBUTORS' DIVISION

STACKPOLE CARBON COMPANY

26 Rittenhouse Place, Ardmore, Pa.

(Branches in St. Marys and Kane, Pa.)

*more
Cannon lines
now available
at jobbers'
shelves!*

get the full story...

Write for ICC
and RJC catalogs TODAY!



Twenty pages of information on 14 different lines of Cannon connectors, including list prices on more than 850 individual items. 130 illustrations.

Audio, military, general industrial.
Get your copies... NOW!

AN3108B Plug AN3102A receptacle

"AN" (Air Force-Navy) Series Connectors

Proved in military service. World-wide standard. Lightweight. Uniform in quality. Interchangeable inserts. Threaded coupling nut. Rapid and easy disconnect. Cable clamps and other accessories.

typical lines newly offered...

K-21C Plug K-32S receptacle

Cannon "K" Series

All-purpose... Adapted to a variety of general electrical and electronic applications. Special Acme thread. Rugged. 220 contact layouts available.

When you write for our catalogs... Please refer to this magazine or Dept. 144

CANNON PLUGS



CANNON ELECTRIC COMPANY
3209 Humboldt St., Los Angeles 31, California
Factories in Los Angeles; East Haven; Toronto, Canada; London, England. Representatives and distributors in all principal cities.

The DE-SNOWER Line

... for TV RECEPTION where boosters have failed!

Here, for home use, is the same high quality antenna-mounted Preamplifier used in hundreds of community TV systems serving as many as 5000 receivers from a single antenna.

The De-Snower Preamplifier's maintenance-free cascode circuit combines a whopping 25 db gain with exceptionally low noise—only 6 db—to give the best TV reception attainable even with long lead-ins.

Available in two models—Channels 2-6, or 2-13. *Flat response for color.*

... for profitable MULTIPLE INSTALLATIONS

Make extra sales by providing clubs, motels, and apartments with small-size Jerrold community TV systems of their own. The De-Snower all-channel Distribution Amplifier provides 15 db gain to each of its 8 outlets—like having a preamp at each receiver. Extremely low noise cascode circuit using 3-6BQ7-A's, 1-6AK5, & 1-6CB6 tubes handles 72 or 300 ohm inputs from one all-band antenna, separate hi-lo arrays, or from De-Snower Preamplifier. Distributes clear, snow-free signals to remotely located sets.

JERROLD ELECTRONICS CORP.

26th & Dickinson Sts.
Philadelphia 46, Pa.

JERROLD

AUDIO—HIGH FIDELITY

trols are always provided. Any of the rubber rollers resting against something will develop a flat, and the flat will cause small speed variations called flutter.

The flywheel in Fig. 7 illustrates another advantage of recording at higher speed. The drive motor has any small variations ironed out to some extent by the flywheel. At high speeds any flywheel has greater effective inertia and wows or flutter in the recording are less.

Off-the-air recording

While there is great satisfaction in taping good air performances and adding them to the recorded library, there are drawbacks. Tape is expensive—just how expensive depending (in addition to the tape quality) on recording speed. For high-quality recording at 15 i.p.s., a 7-inch (1,200-foot) reel will record only 15 minutes; even dual-track machines make the tape good only for 30 minutes—and then with a break for turning over the tape. This is almost as expensive as buying a complete LP record with a maximum of 50 minutes of recording time. Even at 7.5 i.p.s., costs are comparable. Machines such as the Concertone which take 10-inch reels will record for a continuous half-hour at 15 i.p.s. For a full hour with dual-track, costs are considerably more than for an LP record which will record the same symphony, quartet, or other piece of music.

Tape storage takes more space than record storage. But even more important, it is impossible to take the same spur-of-the-moment pleasure in threading a tape as in throwing a platter on a turntable, to say nothing of having to rewind it again. On all counts, therefore, it seems that the best way to carry music in the library is to put in on discs.

Disc recording has been available to amateurs for many years, but principally through cheap assemblies incapable of making records of any quality. Most of these were dropped in favor of the easier and quicker tape process.

However, a really serious music enthusiast who is located where good FM concerts are heard has a great advantage if he procures a good professional disc-making assembly. My record library includes a great many very fine discs made on a Presto 6-N assembly like that of Fig. 8. The ideal process is to make off-the-air recordings on a good tape machine first, since timing is usually unknown and the tape (if it is on 10-inch, 2,400-foot reels) lasts long enough to take care of most things, especially at 7.5 i.p.s. Later, then, the tape is scanned and selected music is put on a disc. The disc becomes part of the record library, while the tape is used again.

In the next and final article of this series, we shall discuss selecting the components of a disc-recording system.

TO BE CONTINUED

See the De-Snower Line at Leading Distributors or write direct for copies of illustrated brochure.

WAR DECLARED ON DEALER CALL-BACKS!



NEW TUBE TYPES FROM SYLVANIA SPEARHEAD ATTACK!

The most important step in a concentrated campaign to eliminate dealer call-backs has been taken by Sylvania with the release of a group of new tube types. Sylvania's new 5U4GB leads the group.

The 5U4GB attacks the call-back enemy on many different fronts:

1. The tube has been re-designed. Now, plates are longer and heavier with twin wings for better heat dissipation, Sylvania's 5U4GB carries increased ratings of 275 ma at 44 volts drop with 1.0 amp peak plate current.
2. Wafer Stem Construction—originally developed by Sylvania for the lock-in tube—has been adapted to the 5U4GB. The wafer stem eliminates electrolysis, provides stronger mount construction, permits better spacing.
3. A new T-12 bulb provides greater heat dissipation, gives added strength, more rigidity because of its straight construction.
4. Bottom mica has been added to make the tube stronger, improve filament alignment and eliminate arcing.

Other Sylvania types are vastly improved, too! All have Sylvania's famous wafer stem construction, plus these additional design features:

- Better Lead Spacing
- Stronger Mount Supports
- Stronger Micas
- Firmer Filament and Plates
- Greater Protection Against Shock and Vibration
- Better Heat Dissipation
- No Glass Electrolysis
- Fewer Burnouts
- Stronger, More Rugged Overall Construction

NO MINOR SKIRMISH

The Sylvania war on dealer call-backs is not a minor skirmish. It will continue until dealer call-backs on these and other receiving tube types are completely eliminated. The dealer's

biggest profit-robbing enemy can look forward only to an incessant, continuing effort on the part of Sylvania to make his existence a thing of the past. These quality tubes are now at your Sylvania distributor's.

TO IDENTIFY SYLVANIA'S NEW RECEIVING TUBES LOOK FOR THE NEW CARTON!



This new tube carton identifies Sylvania's new high quality, improved receiving tubes. It's assurance to dealers of the finest receiving tubes made—unsurpassed for quality and performance. For further information write to Dept. 4R-3811 at Sylvania.

SYLVANIA

Sylvania Electric Products Inc. 1740 Broadway, New York 19, N. Y.

In Canada: Sylvania Electric (Canada) Ltd., University Tower Bldg., St. Catherine Street, Montreal, P. Q.

LIGHTING • RADIO • ELECTRONICS • TELEVISION

FOR GOLDEN EARS ONLY

A review of the latest in audio components and recordings of interest to the hi-fi enthusiast

By **MONITOR**

NOW that high fidelity is spreading beyond the great metropolitan centers and "good music" stations are to be found all over the country, the item most needed by many audiophiles is an FM tuner capable of real high-fidelity performance in the remote fringe areas. The Fisher model 70-RT fills the bill very nicely. It appears to live up to the claim of 1.5- to 3-microvolt sensitivity for 20 db of quieting. The quality of the audio it delivers is excellent; it is convenient and simple to use; the built-in phono equalizer and tone-control circuits are versatile and equal to those of many independent control units, and it is well engineered to make it adaptable to various combinations of record players, amplifiers, and speakers.

To give an idea of possible performance let me describe my situation. The nearest city is 40 airline miles away and has one educational FM station, radiating about 3 kw, that provides hi-fi programs in the evening. A much larger city 140 airline miles away has three FM stations offering hi-fi programs but none of the three radiates over 10 kw. Taking elevation into account, my antenna is still some 30 miles beyond line of sight. However, I have a large horn antenna for TV and FM that delivers around 14 db of gain throughout the FM band and feeds the receiver remarkably steady signals from the three hi-fi stations varying from 1 to 5 microvolts in value. The average receiver with a sensitivity of 10 to 25 microvolts will not bring these stations in and most will show no trace of them whatever.

The 70-RT brings in two of them with complete quieting more than 99% of the time; the third is slightly in the noise, but a homemade cascode booster helps. The tuner doubles or triples the number of stations receivable regularly from all directions and on a good night you can find a station on almost every channel despite the fact that most are more than 100 miles away.

Granting that both my situation and

antenna are unusual, the question is: "What can you expect of the 70-RT with a commercial antenna?" I would say that if the average receiver shows a steady trace of the desired signal but it is not strong enough to produce complete quieting, the 70-RT would almost certainly bring it up to completely satisfactory quality. The chances are very good, too, that you would hear many stations you do not hear at all now. It is very risky to generalize but I believe that, given an antenna with an honest 8 to 10 db of gain, the 70-RT ought to provide reliable reception of stations 75 miles away; in locations with a low noise level up to 100 miles.

Aside from excellent sensitivity, the 70-RT has several other commendable features. The bandwidth is 200 kc at 6 db down, and around 180 kc at 3 db down; that means very low distortion especially on hi-fi programs with a lot of pre-emphasized highs. The a.f.c. (see diagram) is both adjustable and removable—a fine idea. A control on the back of the chassis can be adjusted to set the range within which the a.f.c. will operate; as near as I can determine it can be set so the a.f.c. takes over when a signal is as much as 500 kc off resonance or as little as 150 kc. Moreover, the selector switch on the panel permits choice of reception with or without a.f.c. However, I foresee little use for the shut-off switch; I was able to use the a.f.c. with no trouble whatever on a weak distant station only 200 kc removed from a very strong local 10 miles away.

The AM portion is also excellent. The small loop antenna which comes with the receiver will suffice almost anywhere to bring in all the stations one wants. Two bandwidths are provided and the wide one produces an audio curve flat to 5,000 cycles and down about 5 db at 8,000 cycles. There is a whistle filter and the combination provides acceptable quality with very low interference from interchannel whistles, monkey-chatter, etc. This is as good fidelity as is usable except in the one or two metropolitan

centers having wide-range AM stations. A magic-eye tuning indicator makes both AM and FM tuning simple enough for the most unskilled member of the family.

The audio control unit is about as good and flexible as most independent-control units. Besides the AM and FM inputs, two others are provided. One is for a magnetic pickup and is loaded with 220,000 ohms. This will yield a flat or rising high-frequency response with the G-E, Audak, and Ferranti pickups; pickups that require a lower load can be loaded very simply with a ½-watt resistor at the cartridge terminals. Another input for a crystal pickup, TV set, tape player, or what have you, has a 500,000-ohm input load.

Two outputs are also provided. One is ahead of the tone-control circuits for use with tape recorders, etc.; the other follows the tone-control circuits for use with amplifier and speakers. Incidentally, although the unequalized output is labeled DETECTOR OUTPUT, it also includes the phono and TV channels. Both outputs are through cathode followers so that long cables can be used, and both can be used simultaneously.

There is a good loudness control that can be switched on and off. A nice refinement is that the loudness control and the switch disabling it are mounted coaxially with a double knob. The loudness control can be switched on and off, to suit the need, without moving the hand from the one set of knobs. The tone-control circuit is adequate though the bass boost may not be as high as many people would like it to be. There are two a.c. receptacles on the chassis so that the power amplifier, turntable, tape recorder, or whatever, can be controlled with the on-off switch of the tuner. Up to 500 watts, in addition to the drain of the 70-RT, is permissible.

The phono equalizer provides four equalizations—AES, LP, ORTHO and NARTB. Actually there are only two treble and three bass slopes, but the results are acceptable. A run with the Dubbings D-101 test record showed a

INCREDIBLE

is the only way to describe the new JFD

JET-HELIX

a radical new flat plane helical concept for VHF-UHF




it's "the
RAINBOW
antenna"

INCREDIBLE FEATURES!

- delivers highest gain!
- outstanding front to back ratio!
- sharpest picture clarity!
- greatest fidelity color reception!
- finest snow-free, trouble-free performance!

INCREDIBLE FACTS!

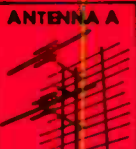IT ALL ADDS UP TO A NEW HIGH IN S/N RATING



S/N FIGURE OF MERIT *		
JFD JET-HELIX—57.85%		
ANTENNA A	ANTENNA B	ANTENNA C
		
43.15%	31.85%	38.5%

*The S/N Figure of Merit sums up the major individual characteristics of an antenna in one concise value. Write for S/N Figures of Merit engineering folder No. 299 for complete details.

THE JET-HELIX IS BETTER BY AN AVERAGE OF 44.5%

- The Microwave Helix design delivers record-shattering power and performance—highest signal magnitude on all channels with the least possible amplified noise!
- Only the Jet-Helix has been exhaustively pre-tested in the field by JFD engineers!
- Only the JFD Jet-Helix comes to you backed by the greatest consumer advertising support in antenna history—literally pre-selling the Jet-Helix for you!
- Yes, compare its Alcoa Aluminum construction, compare its pre-assembled convenience—compare the JFD Jet-Helix by any standards known—and you must agree—here is the New Star of Antennas—the JFD Jet-Helix!

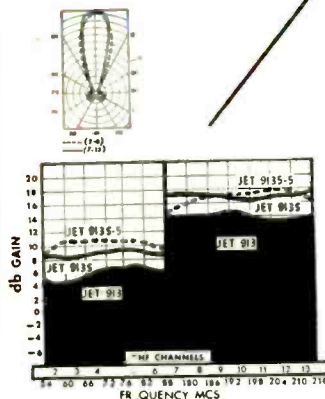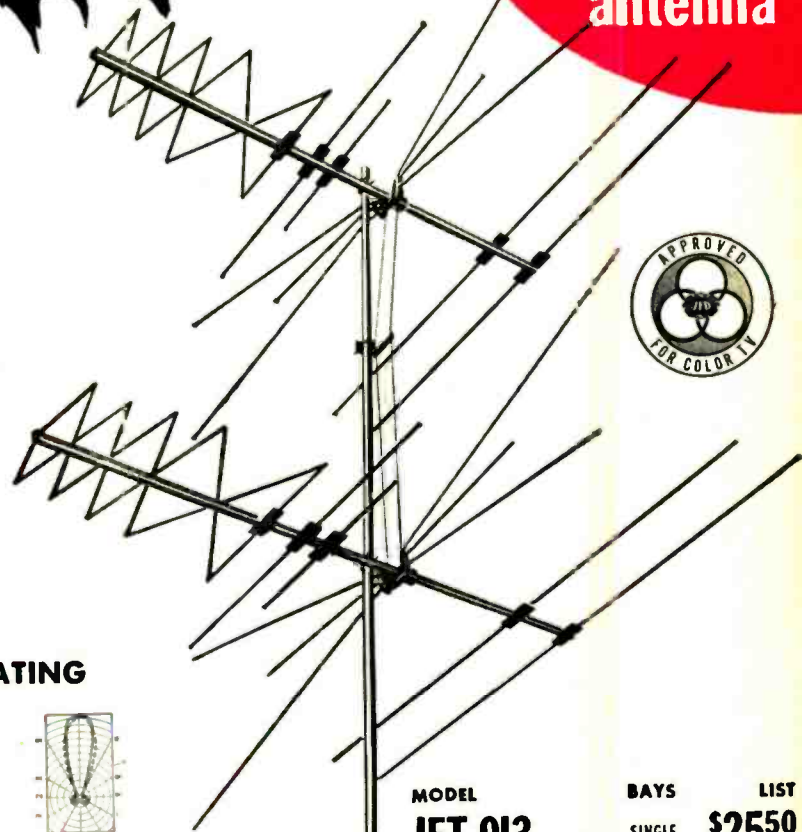THE JET-HELIX IS THE ONE ANTENNA THAT OUTPERFORMS ALL OTHERS IN FRINGE AREAS ON BOTH VHF-UHF



MODEL	BAYS	LIST PRICE
JET 913	SINGLE	\$2550
JET 913 S	STACKED	\$5250
JET 913 S-5	HALF WAVE STACKED	\$5500


DO NOT CONFUSE WITH OTHER SIMILAR ARRAYS!
THIS ANTENNA IS RADICALLY NEW!



JFD MFG. CO., INC.
BROOKLYN 4, NEW YORK

INTERNATIONAL DIVISION
15 MOORE STREET NEW YORK CITY

AUDIO—HIGH FIDELITY

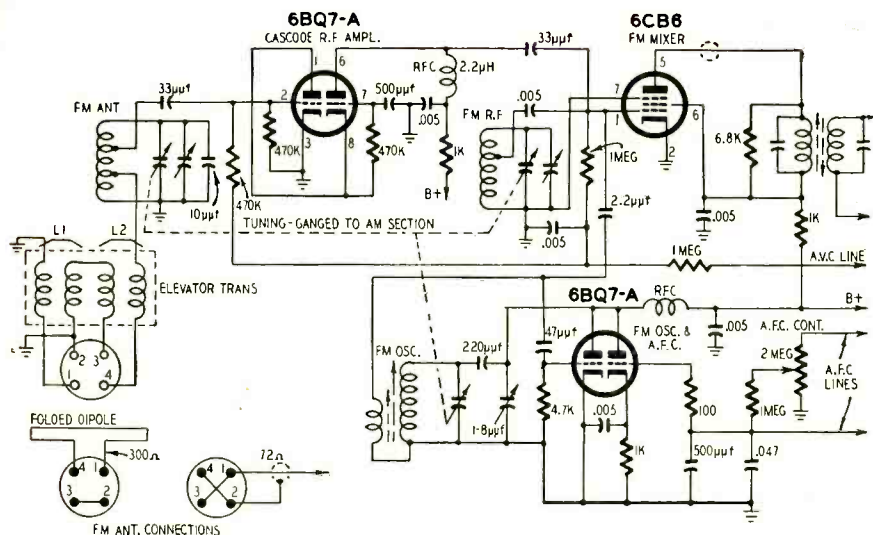

The Fisher 70-RT's front-end with cascode r.f. amplifier and optional a.f.c.

response (with the Ferranti) flat within plus or minus 2 db—mostly within 1 db—at almost all points of all four curves. The NARTB and ORTHO curves showed a bass boost of between 5 and 8 db below 50 cycles but I don't consider this a disadvantage, provided a low rumble and hum turntable is used. Almost all speaker systems can use at least that much boost in that region.

The 70-RT will provide very high quality reception with very simple antennas in normal station areas; it is capable of bringing noise-free hi-fi reception to fringe areas where less sensitive receivers are inadequate.

New Records

HOFFMAN: *Mandolin Concerto*

Gerd Lindner-Bonelli and Symphony Orchestra of Radio Leipzig

DITERSDORF: *Harp Concerto*

Irmgard Helmis and Chamber Orchestra of Radio Berlin

Urania URLP 7910

MOZART: *A Musical Joke* (K522)

Chamber Orchestra of Radio Berlin.

MEHUL: *Symphony No. 1*

Symphony Orchestra of Radio Berlin.

Urania URLP 7109

All this music dates from the Mozartian or post-Mozartian era and will be enjoyed by everyone who likes Mozart's music—and who doesn't? The connoisseur will welcome acquaintance with some obscure and almost never heard music and composers of the period, while the hi-fi man will find here some interesting listening.

The *Mandolin Concerto* dates to around 1800 when the mandolin (in a more complex form than the modern counterpart) was popular in Vienna. Since this instrument is seldom heard in serious music, the collector will want to latch onto this recording as an excellent example of the quality of the instrument. The recording produces marked "presence." Indeed, one sometimes gets the feeling the mandolin is right on one's lap. This, I presume, is

due to close-up miking of the solo instrument that makes many of the incidental noises of fingering and plucking audible. At any rate you have the odd effect of listening to this music *not* as it would sound to a member of the audience, but rather more as it would sound to the soloist. This makes for an interestingly intimate realism on a good hi-fi system and very superior show-off or demonstration material. The transients of the plucked strings are very well reproduced and should be fine test material for this, too.

The *Harp Concerto* was written for the cembalo—a keyed dulcimer or early type of piano—and in consequence the harp sounds very different from its usual self. Here it is "played with two hands," like a harpsichord, and you hear a much greater interplay of the familiar mid and top registers with the less often heard low register. The effect, I suppose, is a cross between that of a harpsichord and a rather ill-tempered piano, which, possibly, is what a cembalo sounded like. Anyhow this is charming music. If you listen carefully, you'll hear an occasional vibrato as the low

harp notes decay, changing pitch as they do. The two sides provide an interesting contrast in plucked strings—the mandolin highly damped, the harp resonantly undamped. The recording is excellent.

The Mozart piece, heard occasionally at children's concerts, is a satire on the musical clichés and performances of his day, and good fun. It is noteworthy for the very clean and vibrant double bass in spots. Played back with NAB or AES bass compensation, it will vibrate the floors very gratifyingly.

I'm not ashamed to say that I had never heard of Etienne Henri Mehul before this or, if I did, he slipped my mind. The way portions of it remind me of various better known symphonies suggests that Mehul's music didn't slip the minds of some of his illustrious successors. If he wrote any more stuff as good as this, I hope Urania will dig it up. The recording is not remarkable in any single respect from a hi-fi point of view but it is well balanced, fairly clean, and up to the excellent standards of Urania's 50- to 15,000-cycle series of which it is an example. You can also hear, in several spots, a very mightily blown piccolo.

By the way, Urania is now using on these discs the ORTHO curve, although they sound better to me with an NAB bass and the ORTHO treble.

STRAVINSKY: *Pulcinella Suite and Apollon Musagètes*

Vienna Chamber Orchestra

Vox PL8270

STRAVINSKY: *Histoire du Soldat*

Instrumental Ensemble under Ferdinand Oubradous

Vox PL7960

RAVEL: *Bolero, Spanish Rhapsody, Alborada Del Graciosa, La Valse, Pavanne for a Dead Princess*


Symphony Orchestra of Radio Paris

Vox PL8150


LISZT: *Piano Concertos Nos. 1 and 2*
Orazio Frugoni and Pro Musica Symphony

Vox PL8390

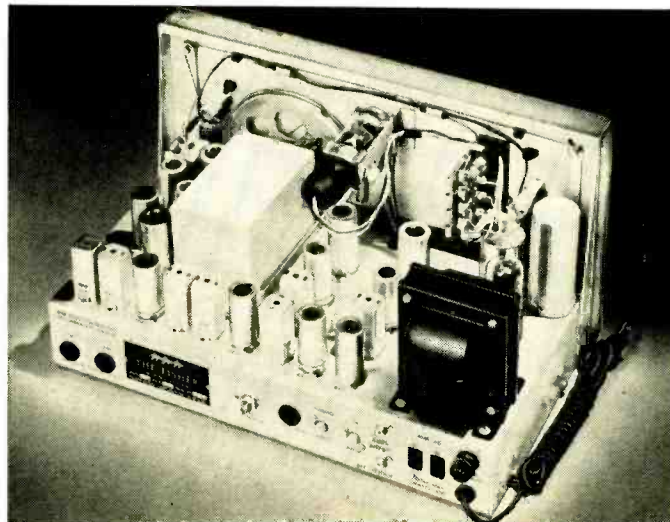All except the *Histoire du Soldat* (Story of a Soldier), are in the new ultra-high-fidelity series of Vox records and very good they are, especially in



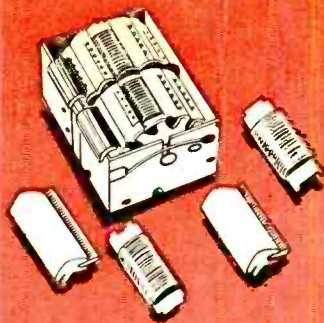The Fisher 70-RT, an AM and FM tuner with phono preamplifier-equalizer.




G-C TUNER-KLEEM'R For every Standard Coil tuner. Cleans both stationary and rotary contacts at every twist of the channel selector. Easy to install, means extra profit, better reception.
No. 9132.....Net \$1.00




Poof!
THERE GOES NOISE!

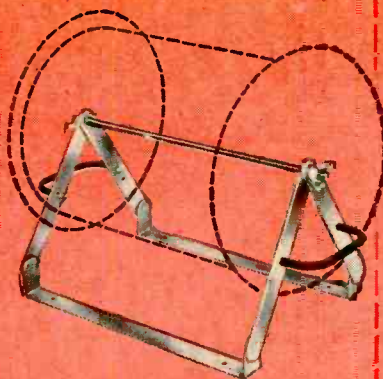G-C SPRAKLEEN The original power spray electrical contact cleaner and lubricant. Eliminates noises in TV tuners, contacts, controls, relays and switches. No waste, no need to remove parts.
No. 8666 6 oz. can.....Net \$1.00



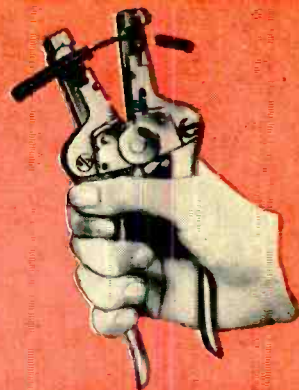G-C PORTABLE WIRE REEL New, convenient way to handle wire coiled on spools. Just slip spool onto reel and pull out what you need. No more twisted or tangled wire when you go out on a job!
No. 9111.....Net \$2.40




G-C SPEEDEX WIRE STRIPPERS New automatic "766" series has delayed return action to prevent crushing of fine stranded wires. Easy to use, with easy-grip handles for easy operation. Interchangeable blades. Specify wire size.
Series 766 (12 models).....Net \$4.95

Save time... Save money... Speed up your service work!



with
SERVICE AIDS


AT LEADING PARTS DISTRIBUTORS EVERYWHERE

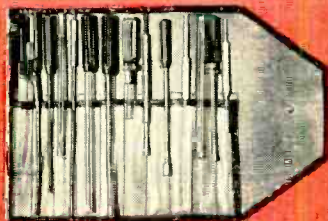

G-C DELUXE ALIGNMENT TOOL KIT Handy roll type case with 16 most-used tools. Tool tips are extra thin, of best grade hardened spring steel for long useful service. Value of tools sold separately \$15.00.
No. 8280.....Net \$7.74



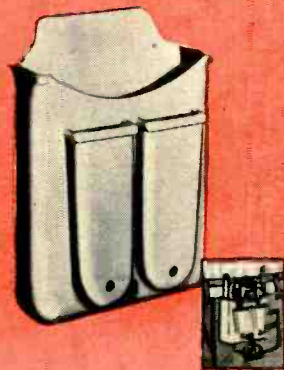G-C GENERAL SKRATCH STIK Easy to use, in handy carry-with-you case. Removes scratches on walnut, mahogany, oak—all shades and colors. Avoid embarrassment on the job... wipe Skcratch Stik on that accidental scratch!
No. 909.....Net \$0.30



G-C "TUX" TOOL KIT Made of remarkable new "Alathon" polyethylene. Flexible, tough, will not lose shape. Keep your tools with you, your tape on a chain. Lightweight.
No. 8943.....Net \$2.37



G-C ILLUMINATED INSPECTION MIRROR Penlight batteries make this tool independent of cords or connections. Adjustable 1" hinged mirror mounted to 6" transparent lucite rod. No shock. On-off switch. Length 12 1/4". Bulb, less batteries.
No. 8725.....Net \$1.95



G-C COMBINATION LEAD-IN TUBE AND LIGHTNING ARRESTOR Simplest feed-thru idea you ever saw. Drill 3/4" hole, any wall up to 16" and insert. Arrestor on outside, wall plug inside. A new G-C exclusive!
No. 8641.....Net \$2.37


FREE Your copy of the big, illustrated G-C catalog. Send postcard today!



GENERAL CEMENT MFG. CO.
910 TAYLOR AVENUE
ROCKFORD, ILL.



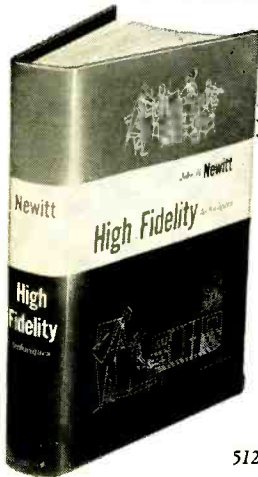Cash in! on HIGH FIDELITY SERVICE AND CUSTOM BUILDING OPPORTUNITIES!



HIGH FIDELITY TECHNIQUES

by John H. Newitt

The complete guide to hi-fi methods, equipment, circuits, building and service

512 pages; 203 illus.

Price \$7.50

TOPS FOR HI-FI FANS

Here, at last, is a complete, fully authentic book that enables you to say "goodbye!" to hi-fi guesswork... helps you get topnotch reproduction at lowest possible cost.

Endorsed by leading experts.

"A much needed book is here" says High Fidelity magazine.

circuits and ideas that are debated wherever high fidelity enthusiasts and experts gather.

From custom building and service techniques and ideas to how to suppress noise... from woofer-tweeters to bass reflex problems... from records and recording to getting the best loud-speaker arrangement... from output transformers to crossover frequencies... from volume expansion to overhang and hundreds of others, HIGH FIDELITY TECHNIQUES covers its subjects completely.

Read from the beginning, this great book can help you be an expert in this fast-growing field.

Used as reference, it will help you solve problems in a jiffy.

Best of all, you don't risk a cent. Read it 10 days at our risk... before you decide!

10-DAY FREE EXAMINATION

Dept. RE-114, RINEHART & CO., INC.
232 Madison Ave., New York 16, N.Y.

Sure! Send HIGH FIDELITY TECHNIQUES for 10-day FREE EXAMINATION. If I like book, I will then promptly send \$7.50 (plus a few cents postage) in full payment. Otherwise, I will return book postpaid and owe you nothing!

Name _____

Address _____

City, Zone, State _____

OUTSIDE U.S.A.—Price \$8.00 cash with order.
Money back if book is returned in 10 days.

AUDIO—HIGH FIDELITY

the bass end. Cook, Mercury, and Capital have been doing a good job recently with drums, but the double basses and piano bass on these discs are tops for me so far. In places they will almost vibrate the dust out of your rugs. Moreover, this is a clean vibrant bass, not a mere rumble or boom. Practically guaranteed to pop the buttons off the vests of owners of good horns and other enclosures capable of doing a good bass full justice.

The highs are also good and I for one did not miss the incessant tinkling of triangles in the background like flocks of belled cows. These are well-balanced recordings, and give an excellent illusion of presence, whatever the miking.

The Pulcinella Suite is a top-drawer test and demonstration record. It is possible I'm slightly prejudiced because this is one of my favorite pieces of music. Stravinsky's free-wheeling rendition of some old tunes of Pergolesi hits me in both my musical weak spots—the polyphony of them good old days, and the remarkable though not always pleasant tonal inventions of the moderns. But aside from being delightful music, this recording offers excellent material for taking the measure of a sound system. I have already mentioned the really big bass often heavily underlining solo instruments and offering an excellent measure of intermodulation. There is, in addition, the interplay of many instruments, winds and strings, enriched by Stravinsky's characteristic coloring. It rises to one of the most wonderful polyphonic crescendos I know of in the *Duetto* about an inch from the end, in which brasses and double basses play around each other at high levels—offering as good a measure of definition in a different way as the opening fanfare of the Final Movement of Copland's Third Symphony. Also the solo instruments, or rather voices of polyphony, include the flute, oboe, bassoon, trumpet, and trombone; and there is a string orchestra behind them. There is plenty of opportunity to judge the naturalness of all, and to compare the differences between them.


The Apollo ballet on the other side is not particularly remarkable, but it is an excellent recording of strings with an exceptional definition in the choirs.

The Story of a Soldier would be a fine addition to a Stravinsky collection if the narration were in English instead of the original French, for the voices are natural and the music good and not without some hi-fi interest. But since the voices occupy so large a portion of the disc, it will be of interest primarily to fans of Stravinsky, particularly those who can follow spoken French.

The very well recorded Ravel record is a fine show-off disc and, with nearly an hour on both sides, represents a lot of music for the money. It is, moreover, music which most people will enjoy. The Bolero, for instance, reveals the fine



Our Newest Catalog is Now Available

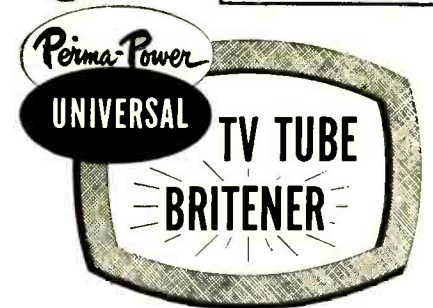

Here is Engineering at its Peak!

IT'S PARALLEL!
IT'S SERIES!
IT'S ISOLATION!
IT'S ELECTROSTATIC!
IT'S UNIVERSAL!

List Price \$4.45


Sold Through Better Jobbers



Export: Scheel International 4237 N. Lincoln, Chicago 13, Ill.

Field Tested and Proven

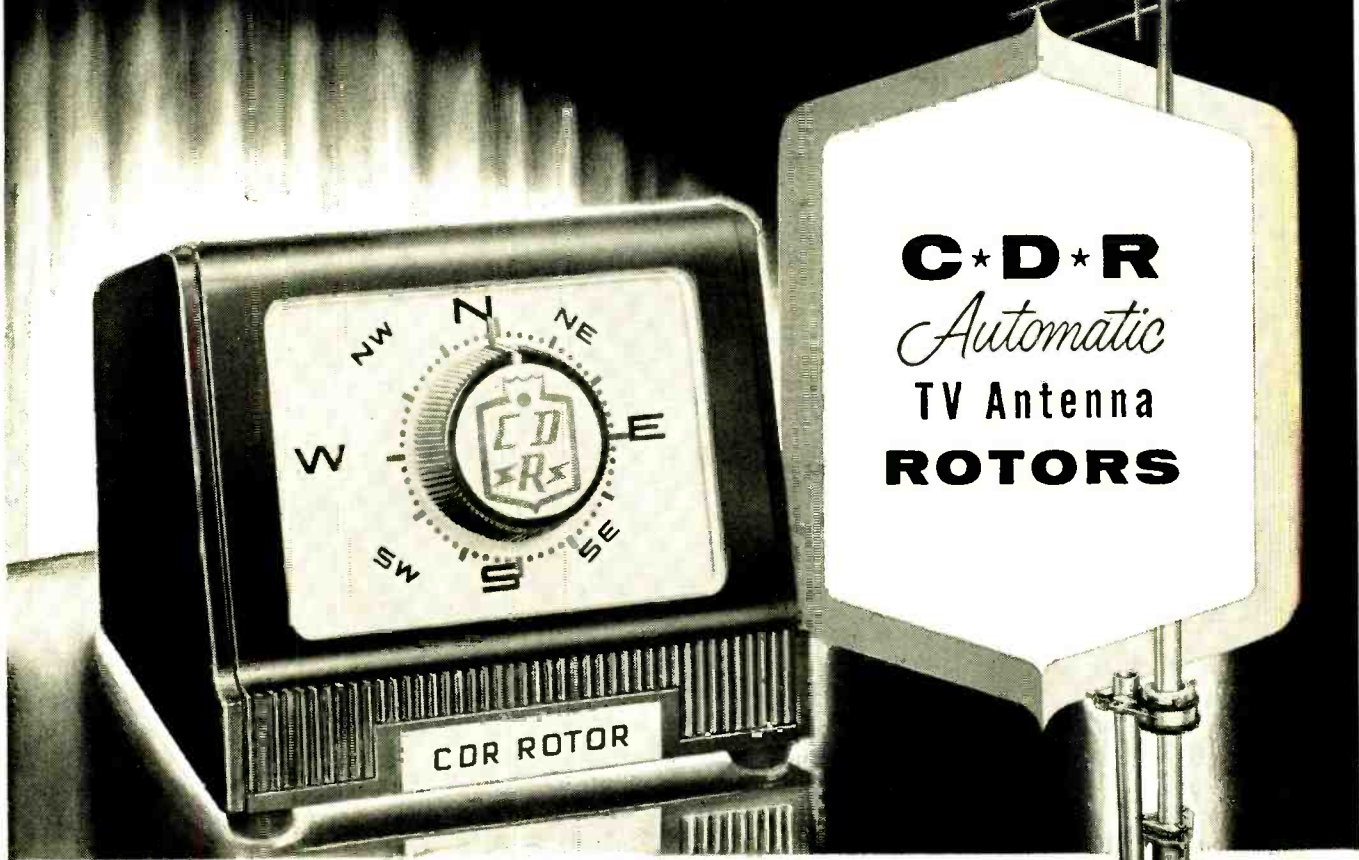by Hundreds of Thousands of Satisfied Users



model AR-2 . . . complete AUTOMATIC rotor with thrust bearing . . . and handsome modern design cabinet, uses 4 wire cable


model AR-1 . . . same as AR-2 without thrust bearing

model TR-12

A special combination value consisting of complete rotor including thrust bearing. Handsome modern cabinet with meter control dial, uses 4 wire cable .

model TR-11

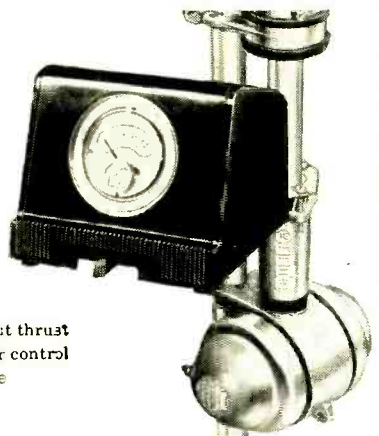The same as the TR-12 without thrust bearing, complete with meter control dial cabinet, uses 4 wire cable




model TR-2

The heavy-duty rotor with plastic cabinet featuring "Compass Control", illuminated "perfect pattern" dial, uses 8 wire cable

model TR-4

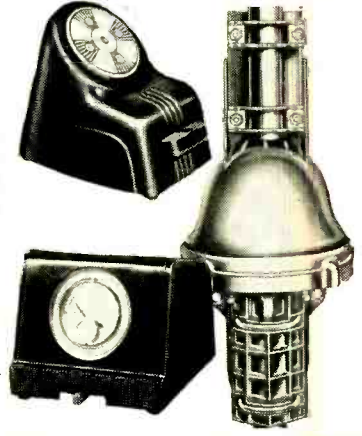The heavy-duty rotor complete with handsome, modern design cabinet with meter control dial, uses 4 wire cable .



CORNELL-DUBILIER
SOUTH PLAINFIELD, N. J.



THE RADIART CORP.
CLEVELAND 13, OHIO

AUTHENTIC KLIPSCH DESIGNS...

 **by Cabinart**


From the drawing boards of Paul KLIPSCH, world-famous designer of high fidelity speaker enclosures, come revolutionary new designs which are produced for you by CABINART. Mr. Klipsch is renowned as the developer of the Klipsch corner horn design... an innovation which effectively extends and enhances the bass range of all program material by utilizing the walls of the room in which the unit is placed. Complete freedom from boom and distortion, crispness and clarity of sound reproduction, and smartly styled appearance are some of the qualities which have combined to make Klipsch designs by Cabinart the most truly desired speaker enclosures in the high fidelity sphere.



KR-5

Only 20" high, this compact speaker enclosure embodies all of the Klipsch-Quality performance within its miniature size. It can be wall-mounted, corner-hung, placed on a table, a bench, a shelf, anywhere in the home! For versatility... plus performance... plus price... there's nothing like it in the world.

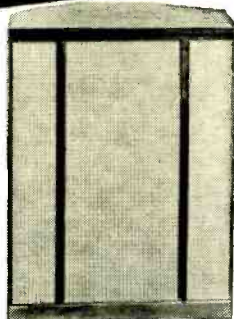Finished **\$48.00** net
Utility (unfinished) **\$33.00** net



KR-4

Approved by popular acceptance. Introduced in the Fall of 1953, the KR-4 received the immediate acclaim of critics and music lovers alike. Here is system performance in a Klipsch corner horn speaker enclosure so flexible in design as to provide the widest latitudes in determining your listening requirements.

12" model	{	Finished \$69.00 net
		Kit form \$36.00 net
15" model	{	Finished \$87.00 net
		Kit form \$42.00 net



KR-3

Surpassed in performance only by the Klipschorn, the KR-3, based upon the same proven principles, is engineered for loudspeakers up to and including 15" in diameter, coaxial or separate, 2 or 3 way systems. Outstanding versatility unmatched at such low cost.

Finished **\$126.00** net
Utility (unfinished) **\$84.00** net

All three of the Klipsch models are available in a variety of beautiful finishes: Honey Walnut on Walnut, French Mahogany on Mahogany, Korina (Blonde Mahogany), and Ebony (black Lacquer). The KR-5 is also available in a portable leatherette model.

See the Klipsch Models at your local jobber, or write for complete information to Dept. 16-L

G & H WOOD PRODUCTS CO., 75 North 11th St., Brooklyn 11, N. Y.

AUDIO—HIGH FIDELITY

nuances of Ravel's clever composition—such as blending two dissimilar instruments, an octave or more apart, in close unison to produce a sound which at first hearing appears to be that of a single, novel instrument. Both Valse and Rhapsody provide spectacular effects.

The Liszt Concertos are noteworthy for dynamic range, volume and depth of the piano bass. This is very big piano. If your system can be thrown into motorboating, portions of this are likely to do it. Listen especially for the reverberations produced when the left hand hits those chords as hard as Liszt intended them to be hit.

The only marring notes on these records are an occasional, very slight, trace of very low rumble in the Pulcinella Suite that will be audible only when a rumble-free turntable is used, and an occasional distortion in the highs of the Ravel.

Listen to the Band. Vox Concert Band
Vox VX590

Marches. Deutchmeister Band


Westminster WL 3003

One kind of music pleases practically everybody and usually provides good material for showing off both highs and lows and definition—good old-fashioned band music of the kind they used to play in the town square on a Sunday afternoon. These two records are capable of transporting you the 20, 30 or more years back to your home town and such a Sunday afternoon. Well recorded, they present relatively small bands, playing the conventional rather corny band style. The Vox has the more familiar music with, curiously enough, the big drums on one side and the triangles and tubas on the other. The drums are not as big as in some other records I know of and the highs not so striking either. But they do create that "you are there" feeling.

The Westminster has more of a small-band sound and a kind of beery playing style which is amusing. Connoisseurs of band music will like the less familiar works on these two sides. Highly recommended, if for no other reason than to give the whole crew a lift just before quitting time. END



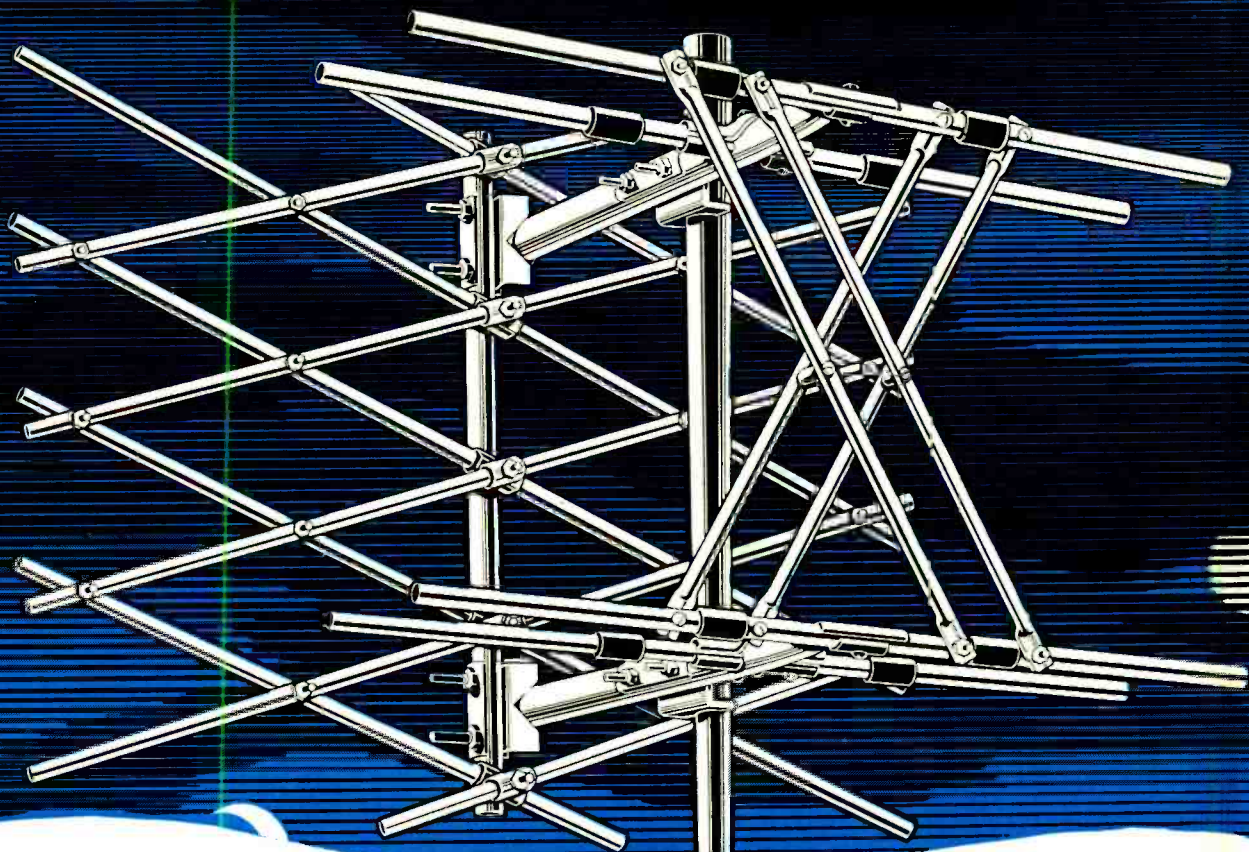"I think it's interference from my wife's reducing machine"



Here's the ideal "a l-channel" antenna
for fringe and far fringe reception

THE NEW RADELCO

DRAGNET*

MODEL DN2 FOR VHF • UHF

*with the Sensational
Diamond-Back Reflector*

- ★ Completely rejects interference from both back and sides.
- ★ Eliminates co-channel interference.
- ★ Front to back ratio far surpasses any other antenna on the market.
- ★ Superior a l-channel gain.
- ★ Completely pre-assembled.

\$34⁹⁵
LIST

*Trade Mark
Registered
Pat. Pending

**The Dragnet
Has Been
Thoroughly
Field Tested**

After several years of development and field testing in all sections of the country, Radelco now gives you an antenna that definitely solves the reception problem in areas where reception has been found most difficult.


RADELCO MANUFACTURING CO.
CLEVELAND 25, OHIO



Dragnets are now being shipped to distributors throughout the nation. Place your order now with your favorite parts jobber.

Handle Tough Service Jobs

AS "SLICK" AS YOU DO THE EASY ONES!

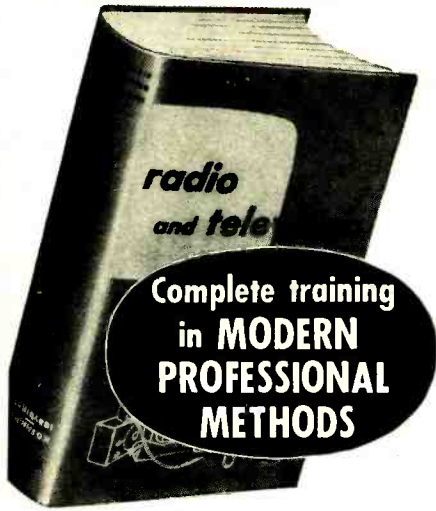

FIX ANY RADIO OR TV SET EVER MADE . . .

Easier . . . Better . . . Faster

How to troubleshoot the professional way

AM, FM and TV readjustment made easy

Testing tips and ideas

A complete guide to TV service

Component problems and how to solve them

Special problems in Battery Sets, Communications Receivers, Recorders, etc.

Servicing, tuning and switching mechanisms.

. . . and dozens of other subjects

Owning this big, up-to-the-minute book is like having two of the world's greatest electronic experts standing by your side on every job . . . telling you just what to do, exactly how to do it!

Written by Ghirardi and Johnson, **RADIO & TELEVISION TROUBLESHOOTING AND REPAIR** is a complete guide to modern professional methods . . . the kind that pay off big.

Step by step, it takes you through service procedures . . . from locating troubles fast and with less testing to making repairs accurately and promptly.

For beginners, this giant book is a complete service training course . . . at only a fraction of the price you might expect. For experienced servicemen, it is the ideal way to "brush up" on specific jobs; to develop better methods and shortcuts; and to find quick answers to problems that will enable you to handle tough jobs as fast and accurately as you now handle the easy ones.

Contains 820 big pages. Over 400 pictures, diagrams and charts make things doubly clear.

Remember! More men now in good servicing jobs get their training from Ghirardi books than any others of their type . . . and this new book is the latest and greatest of them all! Practice from it for 10 full days AT OUR RISK!

EXAMINE IT FREE!

Dept. RE-114, RINEHART & CO., Inc.
232 Madison Ave., New York 16, N. Y.

Send Ghirardi's new Radio & TV TROUBLESHOOTING AND REPAIR book for 10-day FREE EXAMINATION. If I decide to keep book, will then promptly remit \$6.75 (plus a few cents postage) in full payment. If not, I will return book postpaid and owe you nothing.

Name

Address

City, Zone, State

OUTSIDE U.S.A.—Price \$7.25 each with order. Money back if book is returned within 10 days.

ELECTRONICS

Now—Diodes Amplify!

THE crystal diode is now an amplifier. Indeed, in new circuits designed by A. W. Holt of the Bureau of Standards, the ordinary germanium or silicon crystal not only amplifies but oscillates. Power gains up to 10 per stage have been obtained with the diode amplifier, and it is believed that future improvements in diode manufacture may make these amplifiers useful even up to microwave frequencies.

The principle on which the new amplifier works has long been known, but has been considered a weakness in diode rectifiers. It is the reverse current flow which occurs when a diode is switched from the conducting to the nonconducting state. When voltage is applied to a crystal so that the anode is more positive than the cathode (a of Fig. 1), its conductivity is high. The applied voltage creates a steady stream of carriers. These are the "holes" or electrons of transistor terminology. (This article is written in terms of holes, with current flowing from positive to negative.)

If the voltage is applied in the opposite direction (b of Fig. 1), no carriers are injected, the impedance of the diode remains high, and current flow is negligible.

But this drop in current is not instantaneous. The carriers already in the crystal are swept out by the back voltage, creating a large reverse current for a short time. This reverse current is used to make the crystal amplify.

A transistor example

The diode amplifier action resembles that of a transistor, which can be thought of as two diodes with a common semiconductor element. One diode—the emitter—has voltage applied in the conductive or "forward" direction which causes large numbers of carriers to

flow through the crystal. The other diode—the collector—is connected in the reverse direction, and a large voltage applied to it causes very small currents to flow. The current which does flow in the collector circuit depends on the number of carriers injected by the emitter. If the emitter voltage is raised or lowered, causing more or less emitter current flow, the collector current also becomes greater or smaller.

In some junction transistors, the variations in collector current almost equal those in emitter current, and we can think of the action as transferring current from the emitter to the collector circuit. But the collector circuit is one with higher voltage and a higher load resistance, so a given change in current in that circuit represents a much greater amount of power than in the emitter circuit ($P=IR$). "Power gain in the transistor is obtained by a transfer of current from one circuit of low impedance to another circuit of high impedance."

If alternating current is applied to a crystal diode, it acts like an emitter during half the cycle; like a collector during the other half. The diode amplifier must be supplied with power from an r.f. source whose frequency is at least as high as that of the modulating signal frequency. In the examples described here, a square waveform at 1 mc, entirely positive-going (point A in Fig. 2 varies from 0 to 20 volts positive to ground), is used. The power supply is also called the clock, because it controls the time during which the crystal is in the conductive or the high-impedance state. The diode amplifier is therefore in a class with magnetic and dielectric amplifiers in that it requires an alternating power supply, as opposed to tubes. Like the magnetic amplifier, too, it has so far been used for pulse amplification and control applications, though experiments indicate that it might be used for audio amplification, should there be any reason for so doing.

Signals are applied at point B in Fig. 2, through a rectifier shown here as a vacuum-tube diode, which prevents back-action into the signal circuit.

When there is no input at point B, there is no current in the circuit A-C-R_L-ground. The diode passes no current during one alternation of the power supply because the voltage is zero, and none during the other because it is in the high-impedance direction of

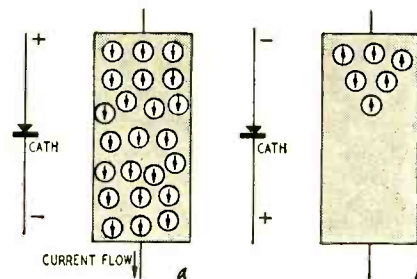


Fig. 1—How the crystal is filled with carriers on the forward alternation and emptied during the reverse cycle.

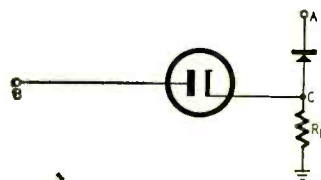


Fig. 2—The simplest diode amplifier.

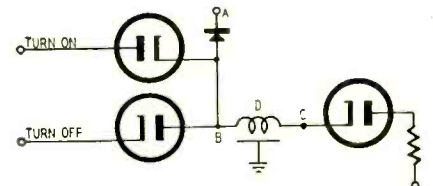


Fig. 3—This flip-flop circuit runs until turned off by a negative pulse.

ELECTRONICS

the diode. A small spike—due to the diode capacitance—appears in the output, but can be reduced if desired by shunting R_L with a capacitor.

If point B is raised to about 2 volts while the clock is at zero, carriers are injected into the crystal, current flowing in the direction B-C-A. When the voltage again rises at A, these carriers are swept back out of the crystal, and a current flows through R_L , creating a voltage across it. Transfer of current from a low-impedance to a high-impedance circuit results in power gain.

To increase the amount of current gain for application to another stage, the voltage gain across R_L must be changed to current gain. This is done with a stepdown transformer, and various circuits have been worked out to compensate for the complications introduced by the transformer inductance.

Flip-flops and current doublers

A number of special circuits—for pulse amplification and for use in electronic computers—have already been designed by Bureau of Standards scientists. One of the most interesting is a flip-flop circuit in which the diode oscillates. A 2-volt positive pulse is injected through the TURN ON gate (Fig. 3) while the clock (power supply) is at zero volt. When point A raises to 20 volts, a surge of current goes down delay line D. The line is an open circuit for a positive pulse, so the surge is reflected and arrives at point B (if the delay-line's time constant is correct) just in time to inject carriers into the crystal, and the cycle is repeated. (The diode beyond point C is to absorb a negative pulse reflected from point B due to mismatch between delay line and crystal.) The circuit continues to oscillate till a negative pulse is applied through the TURN OFF gate.

Another interesting circuit is a "current multiplier" which uses capacitors in a manner reminiscent of a vacuum-tube voltage multiplier. When point B of Fig. 4 is more positive than point E, electron flow (more convenient to consider in this circuit than positive "carriers") in the direction E-D-C-B charges the capacitors in series. Diodes 1 and 3 do not conduct. With the voltage reversed (or cut to zero), diode 2 cuts off and the capacitors discharge in parallel (B-C-E and B-D-E). This circuit has been used with a germanium diode amplifier to make a flip-flop whose frequency can be carried over a very wide range. END


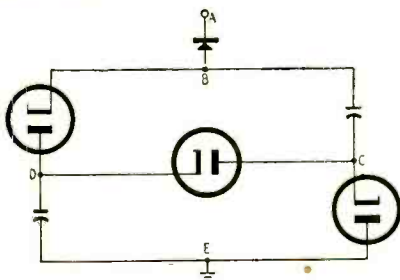


Fig. 4—Diode current-doubler circuit.

NOVEMBER, 1954

a "HOT TIP" for better soldering!

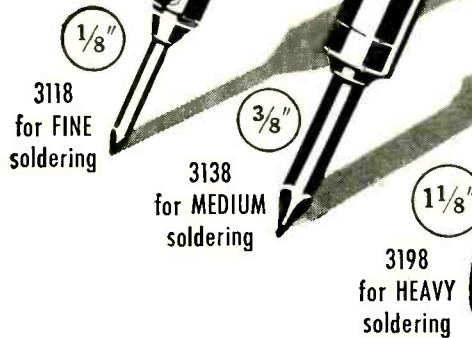

use American Beauty ELECTRIC SOLDERING IRONS

The Tip . . . That's where American Beauty Electric Soldering Irons "pay off" in economy, dependability, efficiency—on all your soldering jobs.

Made of commercially-pure copper rod, heavily nicked to resist corrosion and oxidation, there are American Beauty tips in many special shapes and sizes available to fit particular requirements.

All 12 models of American Beauty Electric Soldering Irons feature tip lengths proportioned to size to permit full insertion into the element core and maximum soldering length.

American Beauty Electric Soldering Irons are available in Tip Sizes from $\frac{1}{8}$ " to $1\frac{1}{8}$ " and in wattages from 25 to 550.

Write For Descriptive Literature

AMERICAN ELECTRICAL HEATER COMPANY



No. 143-H

DETROIT 2, MICHIGAN

YEARS YOUNG 1894-1954

ENGINEERING INSTITUTE

An Accredited Technical Institute • Founded in 1927

3224 16th Street, N.W.

Washington 10, D. C.

NOVEMBER, 1954

CHECK FIELD OF GREATEST INTEREST Broadcast Radio Engineering (AM, FM, TV) Practical Television Engineering TV, FM & Advanced AM Servicing

Name _____

Street _____

City _____

Zone _____ State _____

Check Residence School Veteran

THE PHOTOTRANSISTOR

POWERS • FLYBACKS • YOKES • WIDTH
STANCOR
 YOUR MOST COMPLETE SOURCE OF
**EXACT REPLACEMENT
 TV TRANSFORMERS**
 LINEARITY CONTROLS • VERTICAL OUTPUTS •
 BLOCKING-OSCILLATORS

● Designed from original manufacturers specifications, STANCOR exact replacement transformers faithfully duplicate the ratings and mounting styles of the original unit.

There is no skimping on wire, insulation or laminations. They will equal or better the performance and quality of the original and every STANCOR transformer is individually tested before packaging.



NEW... and typical of STANCOR exact replacements is the DY-13A Deflection Yoke, exact replacement for all Muntz 24" and 27" sets. There are no leads to solder—the DY-13A plugs into the set. Bulletin 495 listing models using this yoke is available from your distributor or from STANCOR.

Stancor transformers are listed in:
 Photofact Folders
 Counterfacts
 Radio's Master
 File-O-Matic



CHICAGO STANDARD TRANSFORMER CORPORATION

3592 ELSTON AVENUE • CHICAGO 18, ILLINOIS

EXPORT SALES: Roburn Agencies, Inc., 431 Greenwich Street, New York 13, N. Y.

OVER 97,000 TECHNICIANS HAVE LEARNED
 HOW TO GET THE MOST OUT OF
 BASIC TEST EQUIPMENT


'Servicing by Signal Substitution'

A BEST SELLER FOR OVER 13 YEARS!
 (NEW, UP-TO-DATE, 14th EDITION)

The Modern, Simplified, Dynamic Approach to
 all Receiver Adjustment & Alignment Problems

- ★ Nothing complicated to learn
- ★ No extra equipment to purchase
- ★ Universal . . . non-obsolete
- ★ Employs only Basic Test Instruments

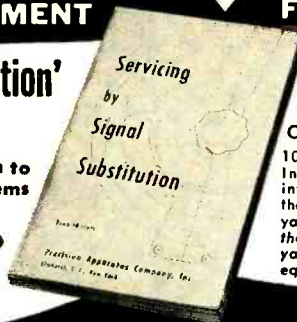Ask for "S.S.S." at your local Radio
 Parts jobber or remit 40¢ in small
 stamps or coin directly to factory.



ONLY 40¢
 103 pages.
 Invaluable
 information
 that will help
 you redouble
 the value of
 your basic test
 equipment.

PRECISION APPARATUS COMPANY, INC.
 92-27 HORACE HARDING BLVD., ELMHURST 4, N. Y.

ELECTRONICS

veloped the first piece of phototransistor commercial equipment for Bell Telephone. This was a card translator (Fig. 1) installed in 1952 as part of a complex nation-wide telephone switching system, and resulted in a great saving of space and power.

Like the ordinary transistor, the phototransistor can be made as a point-contact or junction type. The one shown in Fig. 2 is a coaxial point-contact phototransistor. There isn't too much difference between this point-contact phototransistor and the point-contact transistor; their basic construction is the same except that the emitter contact has been removed so that the photosensitive emitter surface can be used to its fullest extent. Therefore, this phototransistor has only two contacts whereas a comparable transistor has three.

During the early manufacturing stages, when the transistor is not yet photosensitive, it has all three contacts. However, after power has been applied to the emitter contact, and the emitter surface has become photosensitive, the contact is removed (Fig. 3). The photosensitive surface at the emitter is usually only .01 inch in dimensions. Because of this a lens is used to focus the light source on the sensitive area.

The phototransistor operates on the same principle as an ordinary transistor. The two are compared in Fig. 4. In the ordinary transistor, the resistance of the collector-base circuit is determined by the electron flow in the emitter-base circuit. When a positive signal is applied to the emitter, as shown in *a* of Fig. 4, the emitter electron flow increases, causing a corresponding drop in collector-base resistance and an increase in collector current.

In the phototransistor, the resistance to the flow of collector current also depends upon the status of the electrons in the emitter. However, since there is no complete circuit to provide for emitter current flow, the collector-base resistance is dependent on electron agitation in the photosensitive emitter area. Thus, when a light beam strikes the photosensitive emitter (*b* of Fig. 4), the resultant agitation of the electrons in the emitter reduces the collector-base

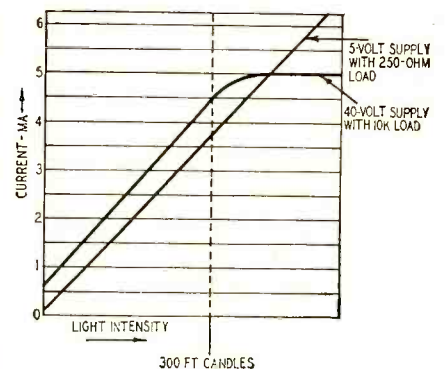


Fig. 5—Diagram shows characteristics of an n-p-n junction phototransistor.



When you want FP Capacitors . . .
specify Mallory. Why accept imitations
when the genuine FP's cost no more?

100% of all FP Capacitors are MALLORY

There is only one FP Capacitor . . . and that
is the Mallory FP.

Designed by Mallory . . . introduced by Mallory
. . . available *only* from Mallory . . . FP Capa-
citors have a combination of features that are
exclusively Mallory—

- 85°C construction
- Ability to handle high ripple currents
- Well suited for voltage doubler circuits
- Ideal for use with selenium rectifiers
- Genuine fabricated plate anode
- Corrosive impurities held to less than
7 parts in 10 million
- Long shelf life
- Long service life
- Fast, twist prong mounting
- Standardized can size

P. R. MALLORY & CO Inc
MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
RECTIFIERS • POWER SUPPLIES • CONVERTERS • MERCURY BATTERIES

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

In ONE compact unit, the

TRANSMISSION

TV Component Tester

PROVIDES **6** VITAL
SERVICING FUNCTIONS

It's terrific as a

- PICTURE TUBE TESTER
- FLYBACK & YOKE TESTER
- SELENIUM RECTIFIER TEST.
- CONDENSER TESTER
- CONTINUITY TESTER
- PIC. TUBE REACTIVATOR



You get \$176 worth of Testing and Repair Instrumentation in 1 compact unit for the amazing low price of only...

\$49⁹⁵

HERE'S HOW: if you bought 6 separate instruments to do the 6 jobs listed above, your cost would be \$176, as follows:

- | | |
|--------------------------------------|--------|
| 1. PICTURE TUBE TESTER, value..... | \$ 39. |
| 2. FLYBACK & YOKE TESTER, value..... | 39. |
| 3. SELENIUM REC. TESTER, value..... | 29. |
| 4. CONDENSER TESTER, value..... | 39. |
| 5. CONTINUITY TESTER, value..... | 15. |
| 6. PIC. TUBE REACTIVATOR, value..... | 15. |

Total Instrumentation, value.....\$176.

You get all 6 in 1 Transvision TV Component Tester, for only **\$49.95**

10 DAY TRIAL: Try this Transvision TV COMPONENT TESTER for 10 days. Then, if you are not 100% satisfied, you may return it. Your purchase price, less 10% (our cost of handling and repacking) will be promptly refunded.

TRANSMISSION, INC.
NEW ROCHELLE, N. Y.

TRANSMISSION, INC., New Rochelle, N. Y. Dept. RE-11

() Send TV COMPONENT TESTERS @ \$49.95

() Enclosed find \$ deposit. Balance C.O.D.

() Enclosed find \$ in full.

I accept your 10 Day Trial terms.

Name _____

Address _____

City _____ State _____

My Jobber is _____

JOBBER INQUIRIES INVITED.

ELECTRONICS

resistance. Then the collector current increases.

Another form of phototransistor is the n-p-n junction type (described on p. 120, RADIO-ELECTRONICS, November, 1953), a Bell Telephone development. This type of phototransistor is being manufactured by Transistor Products Inc., of Boston, Mass. They describe it as a light-sensitive device with an incorporated amplifier. The X-25, as it is called, uses the base rather than the emitter, as the photosensitive area. As the chart in Fig. 5 shows, this phototransistor is capable of operating a relay directly; it can supply an increase of 4 milliamperes or more when light is applied. Of course, sensitive relays that can be energized by these small currents must be used. Examples of some relays that can be used with the phototransistor are the Advance type 1200 and Potter and Bromfield's LM and SS series. These relays have sensitivities of 1 to 9 ma and vary in resistance from 2,200 to 40,000 ohms. The load resistance of the relay is an important item to consider because of its limiting effect on the current flow. Thus, it is advisable to use higher supply voltages with higher relay resistances. The load lines given in Fig. 5 are typical examples; intermediate supplies and load resistances can be used. The X-25 has a maximum rating of 60 milliwatts, and can be used within the range shown in Fig. 6.

Although the phototransistor has not yet been perfected, and is relatively high priced, various manufacturers are trying to adapt it to their particular products. Even though it is a high-priced item, the phototransistor will still reduce the cost of equipment using it, because it does not require sensitive amplifiers. Another point to consider is that maintenance costs will be reduced. An example of the various circuit requirements of the phototransistor as compared to the phototube is shown in Fig. 7, a basic automatic control circuit for opening doors. The phototube circuit (a) is set up so that the current flow from the phototube—caused by the light beam—produces a high negative bias at the grid of the amplifier tube. This bias limits the plate current of the


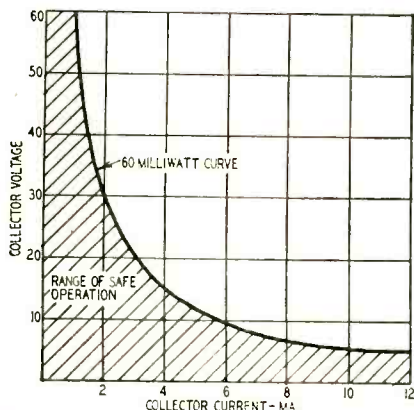


Fig. 6—Operating range of the X-25. The unit has maximum rating of 60 mw.

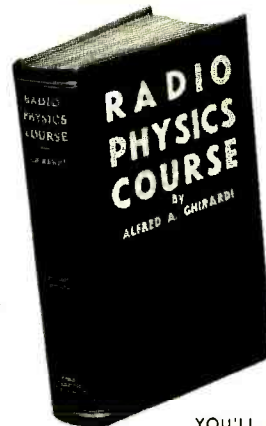HERE'S HOW TO GET STARTED IN RADIO-ELECTRONICS



A. A. Ghirardi

The World's
Most Famous
Book for
Beginners

The simplest,
most complete basic
training ever
offered

RADIO PHYSICS COURSE

by Ghirardi

972 pages,
508 illus.

856 self-test
review
questions

Over 300 pages on
Basic Electricity

36 courses
in one

Covers all
phases of
Theory,

Components,
Capacitance,
Inductance,
Circuits,
Broadcasting,
Receiving,
Tubes,
Amplification,
Radiation
... and dozens of
other subjects.

YOU'LL quickly understand every word of Ghirardi's RADIO PHYSICS COURSE book without previous training! And you'll be pleasantly surprised how quickly it enables you to master subjects that other books and courses make seem very complicated.

This world-famous book is the oldest basic text on the market. It's still a "best seller" BECAUSE it is so outstandingly complete... and BECAUSE it makes things so amazingly clear.

You can buy newer and far costlier training... but you can't beat this famous "old timer" for really learning what you want to know. Hundreds of thousands of copies are in use throughout the world. More men now in Radio-TV-Electronics got their start from RADIO PHYSICS COURSE than any other book or course—and still endorse it as the best, quickest and most complete training for beginners.

NO LESSONS TO WAIT FOR!

LEARN FAST... AND RIGHT
Everything is complete in this one giant, 972-page book... at only \$6.50.

It starts you right at the beginning... with Basic Electricity. Then you progress logically and clearly through the entire field of radio-electronics—from components and circuits showing basic functions to their final uses in modern equipment. On completion of RADIO PHYSICS COURSE, you're equipped with the complete basic "know how" that is essential for any kind of specialization in radio, television or general electronics! Use coupon. Study from it 10 days at our risk.

STUDY 10 DAYS FREE.

Dept. RE-114, RINEHART BOOKS, INC.,
232 Madison Ave., New York 16, N. Y.

Send Ghirardi's 972-page RADIO PHYSICS COURSE book for 10 day free examination. If I decide to keep it I will then promptly remit \$6.50 (plus postage). If not, I will return book postpaid and owe you nothing.

Name _____

Address _____

City, Zone, State _____

OUTSIDE U.S.A.—Price \$7.00 cash with order. Same return privilege with money refunded.

ELECTRONICS

the diode. A small spike—due to the diode capacitance—appears in the output, but can be reduced if desired by shunting R_1 with a capacitor.

If point B is raised to about 2 volts while the clock is at zero, carriers are injected into the crystal, current flowing in the direction B-C-A. When the voltage again rises at A, these carriers are swept back out of the crystal, and a current flows through R_1 , creating a voltage across it. Transfer of current from a low-impedance to a high-impedance circuit results in power gain.

To increase the amount of current gain for application to another stage, the voltage gain across R_1 must be changed to current gain. This is done with a stepdown transformer, and various circuits have been worked out to compensate for the complications introduced by the transformer inductance.

Flip-flops and current doublers

A number of special circuits—for pulse amplification and for use in electronic computers—have already been designed by Bureau of Standards scientists. One of the most interesting is a flip-flop circuit in which the diode oscillates. A 2-volt positive pulse is injected through the TURN ON gate (Fig. 3) while the clock (power supply) is at zero volt. When point A raises to 20 volts, a surge of current goes down delay line D. The line is an open circuit for a positive pulse, so the surge is reflected and arrives at point B (if the delay-line's time constant is correct) just in time to inject carriers into the crystal, and the cycle is repeated. (The diode beyond point C is to absorb a negative pulse reflected from point B due to mismatch between delay line and crystal.) The circuit continues to oscillate till a negative pulse is applied through the TURN OFF gate.

Another interesting circuit is a "current multiplier" which uses capacitors in a manner reminiscent of a vacuum-tube voltage multiplier. When point B of Fig. 4 is more positive than point E, electron flow (more convenient to consider in this circuit than positive "carriers") in the direction E-D-C-B charges the capacitors in series. Diodes 1 and 3 do not conduct. With the voltage reversed (or cut to zero), diode 2 cuts off and the capacitors discharge in parallel (B-C-E and B-D-E). This circuit has been used with a germanium diode amplifier to make a flip-flop whose frequency can be carried over a very wide range. END

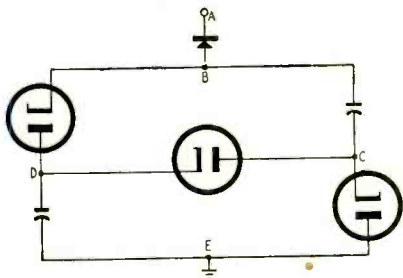


Fig. 4—Diode current-doubler circuit.

a "HOT TIP" for better soldering!

1/8"
3118
for FINE
soldering

3/8"
3138
for MEDIUM
soldering

1 1/8"
3198
for HEAVY
soldering

use American Beauty

ELECTRIC SOLDERING IRONS

The Tip . . . That's where American Beauty Electric Soldering Irons "pay off" in economy, dependability, efficiency—on all your soldering jobs.

Made of commercially-pure copper rod, heavily nicked to resist corrosion and oxidation, there are American Beauty tips in many special shapes and sizes available to fit particular requirements.

All 12 models of American Beauty Electric Soldering Irons feature tip lengths proportioned to size to permit full insertion into the element core and maximum soldering length.

American Beauty Electric Soldering Irons are available in Tip Sizes from 1/8" to 1 1/8" and in wattages from 25 to 550.

Write For Descriptive Literature

AMERICAN ELECTRICAL HEATER COMPANY

American Beauty
ELECTRIC IRONS

No. 143-H

DETROIT 2, MICHIGAN

60
YEARS YOUNG
1894 1954

THE PHOTOTRANSISTOR

By HARRY MILEAF *An outgrowth of transistor research, this unit is remarkably photosensitive and widely applicable*

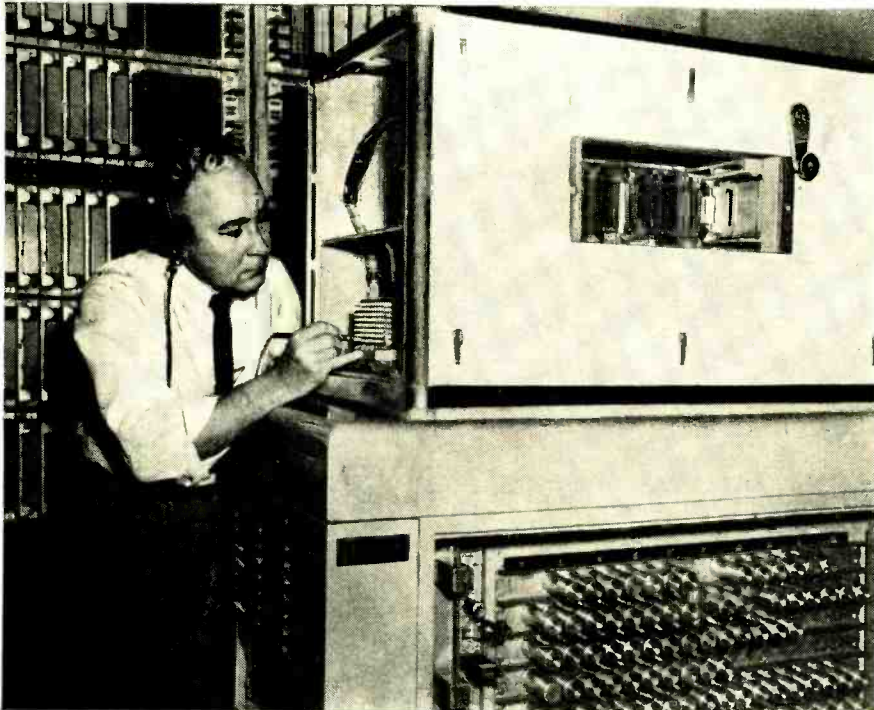


Fig. 1—First application of the phototransistor—card translator equipment.

Courtesy Bell Labs.

THE amazing transistor has invaded the realm of the vacuum tube and, in a short span of time, shown that it will soon become the most important factor in electronics. In radio, television, computers, counters, and many other phases of electronics, it has brought us promise of space conservation, power efficiency, and design simplicity.

An important adaptation of the transistor, the phototransistor, shows even more immediate promise of being used in the industrial field. Besides having all of the advantages of the transistor, it is the most photosensitive device produced because of its current-amplifying characteristics.

Photosensitivity has been an impor-

tant part of automatic equipment for many years. It has been used extensively in automatic "on-off" devices such as automatic door openers, counters, keyers, light dimmers, and other applications. Up to now, the ordinary phototube has enjoyed a monopoly in photosensitive equipment. But it has the disadvantage of supplying only small amounts of photosensitive current. Amplifiers have to build up these small variations to a high enough value to operate the automatic equipment. The phototransistor, on the other hand, can supply enough current to operate a relay directly. (Phototubes deliver microamperes; phototransistors deliver milliamperes.) Because of this characteristic, the phototransistor requires

less complementary equipment and is more efficient.

The phototransistor is not exactly new, in the strictest sense of the word. Some companies have spent the last couple of years constantly improving the phototransistor. Western Electric, pioneers in transistor construction, de-

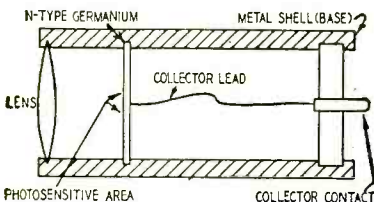


Fig. 2—A coaxial phototransistor—similar to a point-contact transistor.

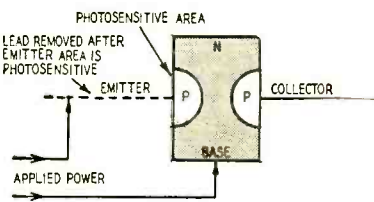


Fig. 3—In processing transistor, power is applied between base and emitter.

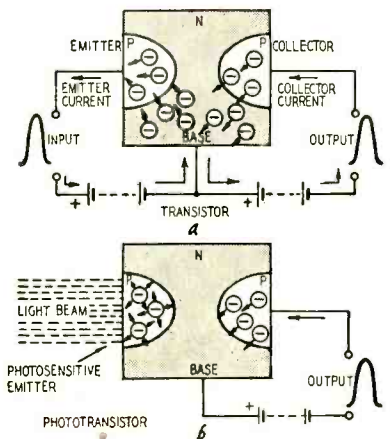


Fig. 4—Diagrams show comparison of transistor and phototransistor theory.

CREI prepares you quickly for success in

The future is in your hands!

The signs are plain as to the future of the trained men in the electronics industry. It is a tremendous industry, and—at the *present time* there are more jobs than there are trained men to fill them. But—when there's a choice between a trained and untrained applicant, the trained man will get the job. Your biggest problem is to decide on—and begin the best possible training program.

**CREI Home Study . . .
The Quick Way to Get There.**



Since 1927, CREI has given thousands of ambitious young men the technical knowledge that leads to more money and security. The time-tested CREI procedure can help *you*, too—if you really want to be helped. CREI lessons are prepared by experts in easy-to-understand form. There is a course of instruction geared to the field in which you want to specialize. You study at *your* convenience, at *your* rate of speed. Your CREI instructors guide you carefully through the material, and grade your written work personally (not by machine).

**Industry Recognizes
CREI Training.**

CREI courses are prepared, and taught with an eye to the needs and demands of industry, so your CREI diploma can open many doors for you. Countless CREI graduates now enjoy important,

good-paying positions with America's most important companies. Many famous organizations have arranged CREI group training for their radio-electronics-television personnel. To name a few: All America Cables and Radio, Inc.; Canadian Aviation Electronics, Ltd.; Canadian Broadcasting Corporation; Columbia Broadcasting System; Canadian Marconi Company; Hoffman Radio Corporation; Machlett Laboratories; Glenn L. Martin Company; Magnavox Company; Pan American Airways, Atlantic Division; Radio Corporation of America, RCA Victor Division; Technical Appliance Corporation; Trans-Canada Air Lines; United Air Lines. Their choice for training of their own personnel is a good cue for *your* choice of a school.



**Benefits Felt
Right Away.**

Almost immediately, you feel the benefits of CREI training. Your employer, when informed of your step toward advancement (only at your request), is certain to take new interest in you and in your future. What you learn in CREI Home Study can start helping you do a better job immediately.

- BROADCASTING
- TELEVISION
- MANUFACTURING
- COMMUNICATIONS
- SERVICING
- AERONAUTICAL ELECTRONICS



**CREI also offers
Resident Instruction**

at the same high technical level—day or night, in Washington, D. C. New classes start once a month. If this instruction meets your requirements, check the coupon for Residence School catalog.

INFORMATION FOR VETERANS

If you were discharged after June 27, 1950—let the new G. I. Bill of Rights help you obtain resident instruction. Check the coupon for full information.

**Get this fact-packed booklet
today. It's free.**

Called "Your Future in the New World of Electronics," this free illustrated booklet gives you the latest picture of the growth and future of the gigantic electronics world. It includes a complete outline of the courses CREI offers (except Television and FM Servicing) together with all the facts you need to judge and compare. Take 2 minutes to send for this booklet right now. We'll promptly send your copy. The rest—your future—is up to you.

CAPITOL RADIO ENGINEERING INSTITUTE

An Accredited Technical Institute • Founded in 1927

3224 16th Street, N.W.

Washington 10, D. C.

MAIL COUPON FOR FREE BOOKLET

CAPITOL RADIO ENGINEERING INSTITUTE

Accredited Technical Institute Curricula. Founded in 1927
Dept. 1411A, 3224 16th St., N.W., Washington 10, D. C.
Send booklet "Your Future in the New World of Electronics" and course outline.
CHECK Practical Radio Engineering Aeronautical Radio Engineering
FIELD OF Broadcast Radio Engineering (AM, FM, TV)
GREATEST Practical Television Engineering
INTEREST TV, FM & Advanced AM Servicing

Name _____
Street _____
City _____ Zone _____ State _____
Check Residence School Veteran

POWERS • FLYBACKS • YOKES • WIDTH
STANCOR
 YOUR MOST COMPLETE SOURCE OF
**EXACT REPLACEMENT
 TV TRANSFORMERS**
 LINEARITY CONTROLS • VERTICAL OUTPUTS •
 BLOCKING-OSCILLATORS



NEW... and typical of STANCOR exact replacements is the DY-13A Deflection Yoke, exact replacement for all Muntz 24" and 27" sets. There are no leads to solder—the DY-13A plugs into the set. Bulletin 495 listing models using this yoke is available from your distributor or from STANCOR.

Stancor transformers are listed in:
Photofact Folders
Counterfacts
Radio's Master
File-O-Matic



CHICAGO STANDARD TRANSFORMER CORPORATION

3592 ELSTON AVENUE • CHICAGO 18, ILLINOIS
 EXPORT SALES: Roburn Agencies, Inc., 431 Greenwich Street, New York 13, N. Y.

OVER 97,000 TECHNICIANS HAVE LEARNED

HOW TO GET THE MOST OUT OF BASIC TEST EQUIPMENT for AM FM-TV


'Servicing by Signal Substitution'

A BEST SELLER FOR OVER 13 YEARS!
 (NEW, UP-TO-DATE, 14th EDITION)

The Modern, Simplified, Dynamic Approach to all Receiver Adjustment & Alignment Problems

- ★ Nothing complicated to learn
- ★ No extra equipment to purchase
- ★ Universal... non-obsolete
- ★ Employs only Basic Test Instruments

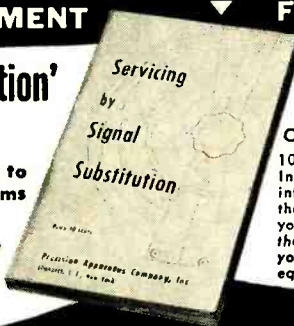Ask for "S.S.S." at your local Radio Parts jobber or remit 40¢ in small stamps or coin directly to factory.



ONLY 40¢
 103 pages. Invaluable information that will help you redouble the value of your basic test equipment.

PRECISION APPARATUS COMPANY, INC.
 92-27 HORACE HARDING BLVD., ELMHURST 4, N. Y.

ELECTRONICS

veloped the first piece of phototransistor commercial equipment for Bell Telephone. This was a card translator (Fig. 1) installed in 1952 as part of a complex nation-wide telephone switching system, and resulted in a great saving of space and power.

Like the ordinary transistor, the phototransistor can be made as a point-contact or junction type. The one shown in Fig. 2 is a coaxial point-contact phototransistor. There isn't too much difference between this point-contact phototransistor and the point-contact transistor; their basic construction is the same except that the emitter contact has been removed so that the photosensitive emitter surface can be used to its fullest extent. Therefore, this phototransistor has only two contacts whereas a comparable transistor has three.

During the early manufacturing stages, when the transistor is not yet photosensitive, it has all three contacts. However, after power has been applied to the emitter contact, and the emitter surface has become photosensitive, the contact is removed (Fig. 3). The photosensitive surface at the emitter is usually only .01 inch in dimensions. Because of this a lens is used to focus the light source on the sensitive area.

The phototransistor operates on the same principle as an ordinary transistor. The two are compared in Fig. 4. In the ordinary transistor, the resistance of the collector-base circuit is determined by the electron flow in the emitter-base circuit. When a positive signal is applied to the emitter, as shown in *a* of Fig. 4, the emitter electron flow increases, causing a corresponding drop in collector-base resistance and an increase in collector current.

In the phototransistor, the resistance to the flow of collector current also depends upon the status of the electrons in the emitter. However, since there is no complete circuit to provide for emitter current flow, the collector-base resistance is dependent on electron agitation in the photosensitive emitter area. Thus, when a light beam strikes the photosensitive emitter (*b* of Fig. 4), the resultant agitation of the electrons in the emitter reduces the collector-base

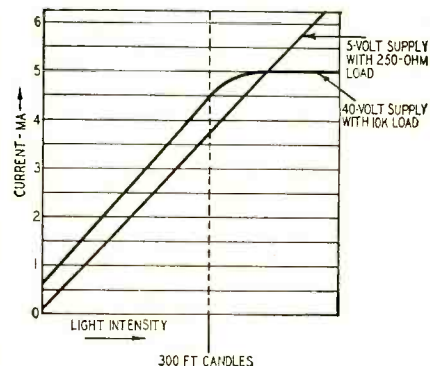


Fig. 5—Diagram shows characteristics of an n-p-n junction phototransistor.



When you want FP Capacitors . . .
specify Mallory. Why accept imitations
when the genuine FP's cost no more?

100% of all FP Capacitors are MALLORY

There is only one FP Capacitor . . . and that
is the Mallory FP.

Designed by Mallory . . . introduced by Mallory
. . . available *only* from Mallory . . . FP Capa-
citors have a combination of features that are
exclusively Mallory—

- 85°C construction
- Ability to handle high ripple currents
- Well suited for voltage doubler circuits
- Ideal for use with selenium rectifiers
- Genuine fabricated plate anode
- Corrosive impurities held to less than
7 parts in 10 million
- Long shelf life
- Long service life
- Fast, twist prong mounting
- Standardized can size

P. R. MALLORY & CO. Inc.
MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
RECTIFIERS • POWER SUPPLIES • CONVERTERS • MERCURY BATTERIES

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

In ONE compact unit, the

TRANSVISION

TV Component Tester

PROVIDES **6** VITAL
SERVICING FUNCTIONS

It's terrific as a

- PICTURE TUBE TESTER
- FLYBACK & YOKE TESTER
- SELENIUM RECTIFIER TEST.
- CONDENSER TESTER
- CONTINUITY TESTER
- PIC. TUBE REACTIVATOR



You get \$176 worth of Testing and Repair Instrumentation in 1 compact unit for the amazing low price of only . . .

\$49⁹⁵

HERE'S HOW: if you bought 6 separate instruments to do the 6 jobs listed above, your cost would be \$176, as follows:

- | | |
|--------------------------------------|--------|
| 1. PICTURE TUBE TESTER, value..... | \$ 39. |
| 2. FLYBACK & YOKE TESTER, value..... | 39. |
| 3. SELENIUM REC. TESTER, value..... | 29. |
| 4. CONDENSER TESTER, value..... | 39. |
| 5. CONTINUITY TESTER, value..... | 15. |
| 6. PIC. TUBE REACTIVATOR, value..... | 15. |

Total Instrumentation, value.....\$176.

You get all 6 in 1 Transvision TV Component Tester, for only.....**\$49.95**

10 DAY TRIAL: Try this Transvision TV COMPONENT TESTER for 10 days. Then, if you are not 100% satisfied, you may return it. Your purchase price, less 10% (our cost of handling and repacking) will be promptly refunded.

TRANSVISION, INC.
NEW ROCHELLE, N. Y.

TRANSVISION, INC., New Rochelle, N. Y. Dept. RE-11

() Send TV COMPONENT TESTERS @ \$49.95

() Enclosed find \$ deposit. Balance C.O.D.

() Enclosed find \$ in full.

I accept your 10 Day Trial terms.

Name.....

Address.....

City..... State.....

My Jobber is.....

JOBBER INQUIRIES INVITED.

ELECTRONICS

resistance. Then the collector current increases.

Another form of phototransistor is the n-p-n junction type (described on p. 120, RADIO-ELECTRONICS, November, 1953), a Bell Telephone development. This type of phototransistor is being manufactured by Transistor Products Inc., of Boston, Mass. They describe it as a light-sensitive device with an incorporated amplifier. The X-25, as it is called, uses the base rather than the emitter, as the photosensitive area. As the chart in Fig. 5 shows, this phototransistor is capable of operating a relay directly; it can supply an increase of 4 milliamperes or more when light is applied. Of course, sensitive relays that can be energized by these small currents must be used. Examples of some relays that can be used with the phototransistor are the Advance type 1200 and Potter and Bromfield's LM and SS series. These relays have sensitivities of 1 to 9 ma and vary in resistance from 2,200 to 40,000 ohms. The load resistance of the relay is an important item to consider because of its limiting effect on the current flow. Thus, it is advisable to use higher supply voltages with higher relay resistances. The load lines given in Fig. 5 are typical examples; intermediate supplies and load resistances can be used. The X-25 has a maximum rating of 60 milliwatts, and can be used within the range shown in Fig. 6.

Although the phototransistor has not yet been perfected, and is relatively high priced, various manufacturers are trying to adapt it to their particular products. Even though it is a high-priced item, the phototransistor will still reduce the cost of equipment using it, because it does not require sensitive amplifiers. Another point to consider is that maintenance costs will be reduced. An example of the various circuit requirements of the phototransistor as compared to the phototube is shown in Fig. 7, a basic automatic control circuit for opening doors. The phototube circuit (a) is set up so that the current flow from the phototube—caused by the light beam—produces a high negative bias at the grid of the amplifier tube. This bias limits the plate current of the


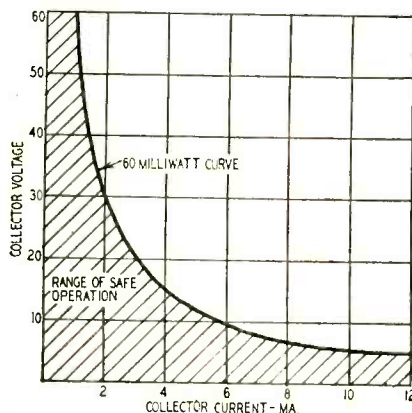


Fig. 6—Operating range of the X-25. The unit has maximum rating of 60 mw.

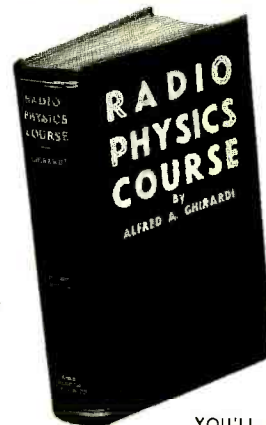HERE'S HOW TO GET STARTED IN RADIO-ELECTRONICS



A. A. Ghirardi

The World's
Most Famous
Book for
Beginners

The simplest,
most com-
plete basic
training ever
offered

RADIO PHYSICS COURSE

by Ghirardi

972 pages,

508 illus.

856 self-test

review

questions

Over 300 pages on
Basic Electricity

36 courses
in one

Covers all
phases of
Theory,

Components,
Capacitance,
Inductance,
Circuits,
Broadcasting,
Receiving,
Tubes,
Amplification,
Radiation
... and dozens of
other subjects.

YOU'LL quickly understand every word of Ghirardi's RADIO PHYSICS COURSE book without previous training! And you'll be pleasantly surprised how quickly it enables you to master subjects that other books and courses make seem very complicated.

This world-famous book is the oldest basic text on the market. It's still a "best seller" BECAUSE it is so outstandingly complete . . . and BECAUSE it makes things so amazingly clear.

You can buy newer and far costlier training . . . but you can't beat this famous "old timer" for really learning what you want to know. Hundreds of thousands of copies are in use throughout the world. More men now in Radio-TV-Electronics got their start from RADIO PHYSICS COURSE than any other book or course—and still endorse it as the best, quickest and most complete training for beginners.

NO LESSONS TO WAIT FOR!

LEARN FAST . . . AND RIGHT

Everything is complete in this one giant, 972-page book . . . at only \$6.50.

It starts you right at the beginning . . . with Basic Electricity. Then you progress logically and clearly through the entire field of radio-electronics—from components and circuits showing basic functions to their final uses in modern equipment. On completion of RADIO PHYSICS COURSE, you're equipped with the complete basic "know how" that is essential for any kind of specialization in radio, television or general electronics! Use coupon. Study from it 10 days at our risk.

STUDY 10 DAYS FREE

Dept. RE-114, RINEHART BOOKS, INC.,
232 Madison Ave., New York 16, N. Y.

Send Ghirardi's 972-page RADIO PHYSICS COURSE book for 10 day free examination. If I decide to keep it I will then promptly remit \$6.50 (plus postage). If not, I will return book postpaid and owe you nothing.

Name.....


Address.....

City, Zone, State.....

OUTSIDE U.S.A.—Price \$7.00 cash with order.
Some return privilege with money refunded.

WE ARE SHARING the success of our products WITH YOU

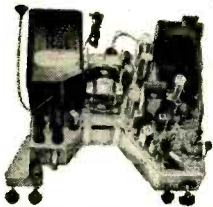as a CUSTOMER'S DIVIDEND in the most SENSATIONAL PRICE SLASHING EVER!



Build your own
SUPER DE LUXE
31-TUBE
#630 TV CHASSIS

#630 SUPER DE LUXE 31-TUBE TV KIT

Engineered in strict adherence to the genuine RCA #630 plus added features. • OPERATES 16" to 24" PICTURE TUBES • CASCADE TUNER • COSINE YOKE • LARGER POWER TRANSFORMER • KEYED AGC • 12" SPEAKER • CONDENSERS and RESISTORS at rated capacities and tolerances. You receive a COMPLETE SET OF PARTS AND TUBES, everything needed is included. You will enjoy building it with "LIFE-SIZE" easy to follow step-by-step ASSEMBLING INSTRUCTIONS" included with each KIT.

slashed to **\$99.99** Less CRT

#630 SUPER TV CHASSIS DE LUXE

LICENSED UNDER RCA PATENTS
COMPLETE READY TO PLUG IN AND PLAY—
Similar in characteristics and features to the TV KIT at left • Manufactured especially for us by nationally known manufacturers • No efforts or expense have been spared in workmanship or materials, to make this #630 SUPER DE LUXE TV CHASSIS the best obtainable for fringe areas, clarity and all-around performance. Customers report reception better than 200 miles. Each set is factory aligned and air-tested • All parts carry the RMA three month guarantee • Our mass volume of business on this CHASSIS (numbering thousands of pleased customers) now makes it possible for us to reduce the price.

slashed to **\$142.27** Less CRT

We Also Sell The Complete Line of TECH-MASTER #630 TV CHASSIS. Catalog mailed on request.

OVER 100 BARGAINS!

SELENIUM RECTIFIER 65ma	\$.44
SELENIUM RECTIFIER 75ma	.56
SELENIUM RECTIFIER 100ma	.69
SELENIUM RECTIFIER 150ma	.74
SELENIUM RECTIFIER 300ma	1.28
SELENIUM RECTIFIER 350ma	1.61
SELENIUM RECTIFIER 400ma	1.77
SELENIUM RECTIFIER 450ma	1.89
SELENIUM RECTIFIER 500ma	1.98

4" PM SPEAKER, alnico #5, 1 oz. magnet	1.12
5" PM SPEAKER, alnico #5 1 oz. magnet	1.19
6" PM SPEAKER, alnico #5 1 oz. magnet	1.38
AUDIO OUTPUT TRANSFORMER (50L5)	.29
AUDIO OUTPUT TRANSFORMER (6K5)	.49
AUDIO OUTPUT TRANS. (universal any tube)	.79
VOLUME CONTROL, L/S 1/4, 1/2, 1 or 2 meg.	.22
VOLUME CONTROL, W/S 1/4, 1/2, 1 or 2 meg.	.42
VARI-LOOPSTICK ANTENNA	.39
I.F. TRANSFORMER COIL, 456kc	.28
I.F. TRANSFORMER COIL, FM 10.7mc	.28
VARIABLE CONDENSER, 2 gang super	.39
6-FOOT LINE CORD WITH MOLDED PLUG	.14

SAPPHIRE PHONOGRAPH NEEDLE	.49
PHONO MOTOR 78 rpm, complete with f.t.	2.62
PHONO MOTOR 3 speed, complete with f.t.	4.47
PHONO AMPLIFIER, incl. 3 tubes	4.68
FAMOUS MAKE CRYSTAL PICKUP	2.42
CRYSTAL PICKUP, 33, 45 & 78 rpm	3.99
1 Lb. ROSIN CORE SOLDER 40/60	.78

TV POWER TRANSFORMER, 250ma	3.98
TV BACK CUP, for recessing CRT	.39
I2-ASST. TV HANDY BRACKETIS	.95
I2-ASST. TV COILS	.59
TV STATIONARY HV CAGE	.79
RCA FLYBACK TRANSFORMER, doubler type	1.17
GEN. ELECTRIC AGC WIDTH COIL	.19
TV CONVERTER COILS	.39
TV VERTICAL OUTPUT TRANSFORMER 10 to 1	.97
TV WIRE WOUND RESISTOR 5300/2-500 ohms	.12
QUARTER AMP. FUSE	.02
TV ELECTROLYTIC SUB CHASSIS	.17
TV CONICAL ROOF ANTENNA	2.69
TV CONICAL ROOF ANTENNA, double	4.88
TV FLYBACK TRANS. single I83	2.54
COAXIAL CABLE, RG59/U, 1,000 feet	37.96
COAXIAL CABLE, RG-11/U, 1,000 feet	87.50
TV 90° deflection yokes	5.98
TV FLYBACK TRANS. for 90° TV Chassis	4.42
LUCITE TV SUB CHASSIS, for HV section	2.26
ELECTROLYTIC CONDENSER, 8mf-450v	.22
TV ELECTROLYTIC CONDENSER 1000/250v-fd	.24
TV PICTURE TUBE BRIGHTENER, complete	.99
TV FOCUS COILS, 250 ohms	.99

5-TUBE TABLE MODEL RADIO, complete	13.89
#630 CHASSIS PAN, with sockets on	5.94

UHF STRIPS—F, 22, 25, 26, 27, 28, 33, 34, 35	3.99
UHF STRIPS—F, 39, 40, 41, 45, 46, 48, 49, 54	3.99
UHF STRIPS—F, 55, 59, 67, 71, 73, 78	3.99
UHF STRIPS—K, 17, 24, 34, 39, 45, 48, 57, 73	3.99
UHF STRIPS—Q, 36, 39, 45, 46, 55, 61, 66, 69	3.99
VHF STRIPS—F, 6, 8, 10, 12 osc. or antenna	.49
VHF STRIPS—Q, 6, 8, 10, 12 osc. or antenna	.49

100—SMALL PEANUT TUBE CART. 1 1/2" x 2 1/2"	.79
100—LARGE PEANUT TUBE CART. 1 1/2" x 2 3/4"	.94
100—GT TYPE TUBE CART. 1 1/4" x 1/2" x 3 3/8"	1.04
100—SMALL G TUBE CART. 1 1/2" x 1 1/2" x 4 1/2"	1.29
100—LARGE G TUBE CARTONS 2" x 2" x 5"	1.59
100—EXTRA LARGE TUB. CART. 2 1/4" x 2 1/4" x 6 1/2"	2.67


RADIO TUBULAR CONDENSER .25-600v	.12
RADIO TUBULAR CONDENSER 5-600v	.19
RADIO TUBULAR CONDENSER 20/20-150v	.37
RADIO TUBULAR CONDENSER 50/30-150v	.39
RADIO TUBULAR CONDENSER 16/16-450v	.59
RADIO TUBULAR CONDENSER 40-450v	.64

Closing out excess stock of New Guaranteed Receiving Tubes in Standard Brands:

IH5—56, IQ5—49, ILE3—64, ILD5—49, ILB4—49, IT5—49, ILC6—49, ILH4—49, 6AK5—69, 6C5—52, 6AB7—54, 6H6—39, 6C4—52, 6F5—39, 6Q7—49, 6J7—49, 6A7—49, 6A8—52, 6SD7—49, 6SF7—49, 6SF5—45, 6SJ7—49, 6AV6—54, 6SA7—49, 6BE6—49, 7F8—49, 7F7—49, 7Y4—44, 7V7—47, 7E7—49, 7A8—57, 7A6—48, 12AL5—49, 12SL7—45, 12SK7—49, 12SA7—54, 12SR7—42, 12SL7—39, 12SG7—52, 14A7—49, 25L6—52, 25A6—49, 35A5—56, 37—07, 39/44—07, 1B3—74, 5U4—49, 6AT6—42, 6AL5—44, 6AG5—59, 6J6—59, 6AU6—57, 6AC7—99, 6SN7—72, 6SH7—48, 6SK7—49, 6J5—36, 6BG7—1.87, 5V4—1.19, 6K6—59.

CUSTOM-BUILT CABINETS FOR #630 AND ALL OTHER TV SETS

The VOGUE

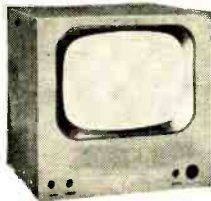

H-25", W-26", D-22"

\$35.91

The FUTURAMIC




H-37", W-28", D-24 1/4"

\$79.34

From Factory to You

4 LEADING STYLES in genuine mahogany or walnut (blond 10% extra) • Ready drilled for any # 630 TV chassis and cutout for any 14", 17", 19", 20" or 21" picture tube at no extra in price • Also supplied with undrilled knob panel for any other TV set • EVERYTHING NECESSARY for an easy perfect assembly is included • Each cabinet is delivered complete as pictured with mask, safety glass, mounting brackets, backboard, backup, hardware and assembling instructions • Each cabinet is shipped in an air cushioned carton from FACTORY to YOU!

The MAYFAIR

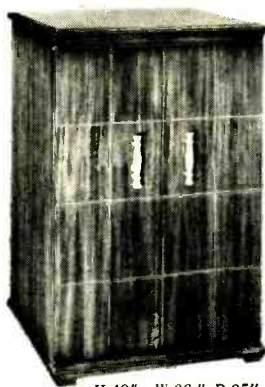

H-40", W-26", D-25"

\$88.70

The MANHATTAN



H-41", W-25", D-23"

\$53.43

NATIONALLY KNOWN BRAND PICTURE TUBES

BRAND NEW in Factory Sealed Cartons—With a Full Year Guarantee

17" #17BP4A **\$26.66** | 21" #21EP1B Aluminized **\$39.21** | 24" #24CP4A Aluminized **\$59.99** | 27" #27EP4A Aluminized **\$74.31**

Brooks LIFE-SIZE Edition
#630 TV KIT BUILDER-SET OF INSTRUCTIONS
BUILDING YOUR OWN #630 TV CHASSIS is now simplified with this COMPLETE SET OF BUILDING & WIRING INSTRUCTIONS. Covers all #630's, from the RCA 10" SET to the latest SUPER DE LUXE 31-tube 16" to 24" RECEIVER. EVERYTHING AT A GLANCE—LAYOUT CHARTS show chassis and components in actual LIFE-SIZE with instructions alongside the illustrations.
only **\$1.25** postpaid

Brooks CASCADE MANUAL
how to install tuner in any TV SET with easy to follow step-by-step instructions
25¢ postpaid
● HINTS FOR BETTER PICTURES ON 630TV
● 630TV DIAGRAM WITH MODIFICATIONS
● ILLUSTRATED TV CONVERSION MANUAL
● PULSE KEYED AGC CIRCUIT DIAGRAM
● RMA RESISTOR & MICA CODE CHARTS
All for **50¢** postpaid

BROOKS RADIO & TV CORP., 84 Vesey St., Dept. A, New York 7, N.Y. TELEPHONE: COrtland 7-2359



Hot Off The Press!

NEW
SANGAMO
twist-tab
DRY ELECTROLYTIC
CAPACITOR
REPLACEMENT
GUIDE

FILL IN AND
 MAIL THIS COUPON
 TO DEPT. SP

the little Indian says: SEND FOR YOUR FREE COPY TODAY



PLEASE SEND ME A FREE COPY OF YOUR NEW TWIST-TAB REPLACEMENT GUIDE

NAME _____

FIRM _____

ADDRESS _____

CITY _____ STATE _____

SC54-15

SANGAMO ELECTRIC COMPANY • MARION, ILL.

ELECTRONICS

amplifier tube so that the relay cannot be energized. However, when an object blocks the beam of light, the phototube current drops off and the bias at the amplifier tube decreases. The plate current then increases and actuates the relay. Its contacts close and the door-opening mechanism operates.

The phototransistor control circuit (b) does not require an amplifier. The beam of light on the photosensitive base supplies enough current to actuate the relay. The relay in this circuit is connected so that the contact points are open when it is energized. Therefore, when the light source is cut off, the current decreases and the relay is de-energized. This causes the contact points to close and energize the door-opening mechanism.

Fig. 7 shows the simplicity of the phototransistor circuit. In the phototube circuit only one amplifier was used because plenty of light change was available. But, if the circuit had to react to smaller changes of light intensity, the phototube would require much more amplification as compared to the phototransistor. Of course, a photomultiplier tube could be used in such a case, but the amount of noise that would be developed would limit its usefulness with critical circuits. The circuit shown in Fig. 7 is also similar to those used for counting.

One of the latest developments in phototransistors is that associated with the phototransistor control unit, described on p. 118, RADIO-ELECTRONICS, November, 1953, another Bell patent. This circuit uses an n-p-n junction phototransistor with two photosensitive surfaces (emitter and collector) that can be set up in a bridge circuit so that changes can be more accurately measured. It can be used to maintain brilliancy in photographic exposure processes, stage light intensity, and infra-red baking processes (the phototransistor is sensitive to infra-red). END


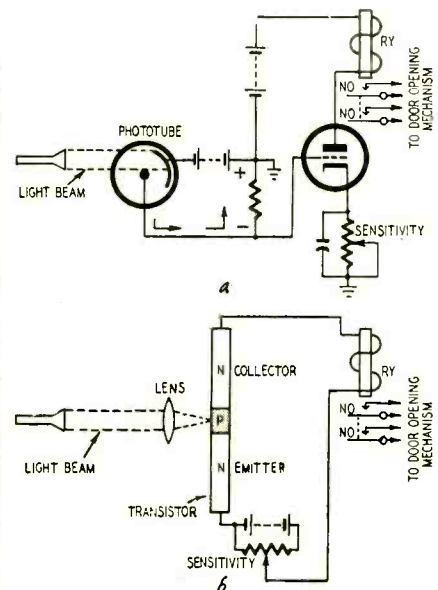


Fig. 7—Comparison diagrams of basic photosensitive control circuits.

the magnetic AMPLIFIER

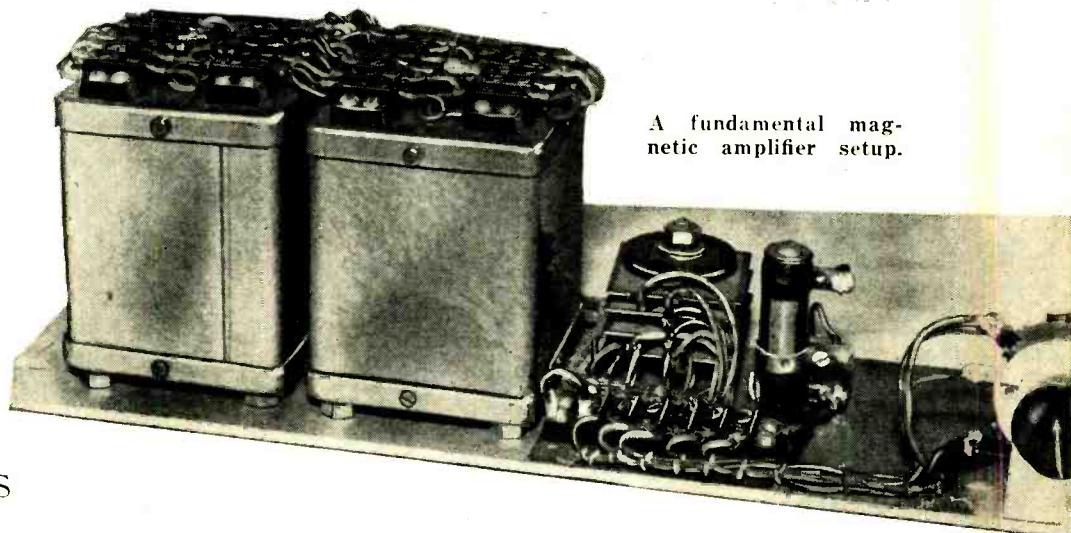*Voltage gain,
high-speed
switching, or
automatic control
are all possible
with this
durable device*



A fundamental magnetic amplifier setup.

Photos Courtesy Bogac Railway Equipment Division

By LEO G. SANDS

THE transistor, the electrostatic amplifier, and the magnetic amplifier are competitors, but not necessarily successors to the vacuum tube. Only seven years ago, the transistor was invented at the Bell Telephone Laboratories. Since that time it has been the subject of much discussion and is now finding its place in practice.

The magnetic amplifier, on the other hand, is not new and has been used for many years. But it was not generally known by the name magnetic amplifier. Many radio technicians will remember an early Majestic radio receiver in which the dial light dimmed when the receiver was tuned to resonance with an incoming signal. This is a form of magnetic amplifier.

It has been widely stated that the Germans invented the magnetic amplifier. Records indicate that it is an American invention used as far back as 1885 for the control of electrical machinery.

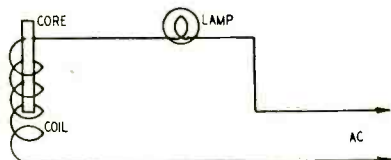


Fig. 1—A magnetic a.c. light dimmer.

The Germans, however, should be credited with reviving interest in magnetic amplifiers and developing them into practical forms for a wide variety of applications. They applied magnetic amplifiers to many tasks formerly assigned to vacuum tubes, such as in servo systems, regulators, fire control, frequency control, and computer circuits.

Statistics indicate that the great majority of electronic equipment failures

are caused by vacuum tubes. If tubes are the weakest link, it seems logical that the tubes themselves should be improved or, whenever possible, replaced by devices which do not wear out as readily. Ruggedized vacuum tubes have been made available, with the result that failures and replacements are reduced. The vacuum tube is, in reality, a very reliable device, but its applications are limited by its fragility and the fact that it wears out in a short time.

A magnetic amplifier is a static device which will perform many of the functions of vacuum tubes. Its applications in its present stage of development are limited, but the many jobs it is capable of doing, it can do well and with greater reliability than can vacuum tubes.

A few examples

The basic principles of operation of the magnetic amplifier may be more easily understood by studying the circuit of a coil and lamp in series as indicated in Fig. 1. When a core of magnetic materials is inserted in the coil, the lamp glows dimly because the coil's impedance increases. When the core is removed, the current increases and the lamp glows more brightly. By adjusting the position of the core, the brilliance of the lamp may be varied by degrees.

The radio tuning indicator system shown in Fig. 2 illustrates the principle of electrical control with a saturable reactor. The decrease in plate current flowing through the coil because of a.v.c. action when the receiver is tuned to resonance increases its inductance, and therefore its impedance to the flow of current through the lamp. The principle can be further demonstrated by connecting a transformer of suitable characteristics in the manner shown in

Fig. 3. Varying the amount of d.c. flowing through L1 changes the impedance of L2 to the flow of current through the lamp.

In Fig. 4 the circuit is modified to include a rectifier in series with the load. This is a basic simple form of magnetic amplifier. The pulsating d.c. which now flows in the secondary L2

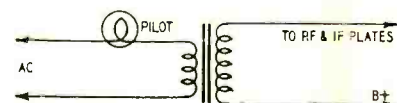


Fig. 2—Circuit of a tuning indicator based on magnetic amplifier principles.

aids the primary L1 or control winding to cause saturation of the core. As this circuit requires less power for control than the device which is to be controlled, we now have a true amplifier.

A practical magnetic amplifier is not as simple to design and build as the foregoing might infer. The saturable coil, transformer, or "transductor," as it is called by the magnetic amplifier

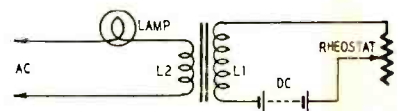


Fig. 3—A rough experimental hookup.

engineer, is the most important element. The transductor is a special type of transformer using *core materials that are easily saturated*. A great variety of core materials are used to meet the requirements of specific applications. So if the experimenter hooks up the circuit of Fig. 3 or Fig. 4, he is likely to get results which may demonstrate the principles of magnetic amplification, but should not be surprised if his control power is as great as that being

ELECTRONICS

controlled. That is because of the core material of the ordinary transformers,

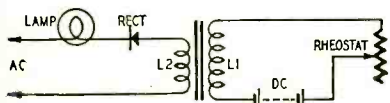


Fig. 4—This circuit really amplifies.

which is much harder to saturate than cores in magnetic amplifier equipment.

Practical magnetic amplifiers

A typical transductor consists of control coils and load coils wound opposed to neutralize any transformer effect into the control winding. A practical magnetic amplifier is shown in Fig. 5. Here the transductor is provided with control windings and two opposed load windings. The selenium rectifiers permit flow of current through one of the load coils during one half of a cycle only and through the other load coil during the other half of the cycle. Varying the current flow in the control windings causes a wide change in the impedance of the load coils.

The circuit of Fig. 5 may be modified to permit control of a d.c. load by adding a bridge rectifier as shown in Fig. 6.

To increase the gain of a magnetic amplifier, positive feedback has been used to realize gains up to several million per stage. In practical applications, gain in the order of several thousand times is common. Fig. 7 illustrates a circuit employing such feedback. Neg-

ative feedback is also used to increase linearity.

The development of the magnetic amplifier did not get a real push forward until selenium rectifiers with extremely high forward-to-reverse current ratios become available. Run-of-the-mill selenium rectifiers intended for power applications usually are not suitable.

The availability of satisfactory rectifiers in sufficient volume became so acute that Bogue set up its own selenium rectifier manufacturing facilities to build rectifiers with suitable characteristics. Belcon rectifiers are being manufactured by Bogue with forward-to-reverse current ratios in the order of 1,500 to 1.

Some applications

New applications for magnetic amplifiers are being discovered continuously. They have been made to operate at frequencies higher than 1 megacycle, although it is not economically feasible to build radio receivers or public-address amplifiers using magnetic amplifiers instead of vacuum tubes.

The armed forces and many industrial and educational organizations are probing further into the development and applications of magnetic amplifiers. Electronic equipment is being redesigned to substitute magnetic amplifiers for vacuum tubes. New military and industrial electronic devices with few or no vacuum tubes are being developed.

Magnetic amplifiers are being used to operate motors and relays directly from photocells, strain gauges and thermo-

couples. They are also being used to replace mechanical relays by utilizing the flip-flop characteristics of magnetic amplifiers. As contacts and moving

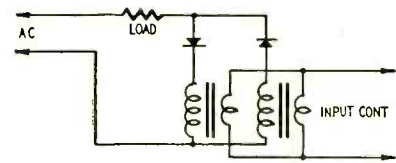


Fig. 5—A practical magnetic amplifier.

parts are eliminated, greater reliability under all kinds of weather and moisture conditions can be achieved. Furthermore, they are explosion-proof.

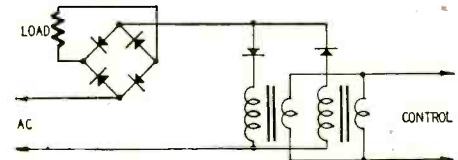


Fig. 6—How a d.c. load is controlled.

A very popular application of the magnetic amplifier is in automatic regulation of the output voltage of electrical generators. The Bogue 400-cycle motor-generator power-supply systems use magnetic amplifier voltage regulators which maintain output voltage to plus or minus 1/2% or better, no load to full load, with frequency remaining at 400 cycles no load to full load.

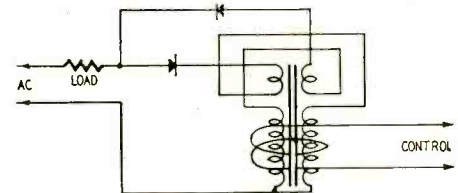


Fig. 7—Feedback increases sensitivity.


The speed of a motor may be controlled within very close limits with magnetic-amplifier regulators, and a large number of motors may be kept in step with each other. The speed may be adjustable with magnetic amplifiers holding the speed to the desired value.

Servo systems using magnetic amplifiers instead of vacuum tubes are inherently more reliable because there are no tubes to wear out or filaments to burn out. A typical magnetic amplifier servo system is the Bogue ship-steering servo. This particular servo system causes the ship's rudder to track automatically with the steering wheel to an accuracy of a quarter of a degree.

The life of a magnetic amplifier is not easy to predict. The transductor is a form of transformer. If well designed, its life is a great many years. Selenium rectifiers operated within their ratings have a service life estimated conservatively at more than 50,000 hours, which is many times more than the life expectancy of a vacuum tube. END

References

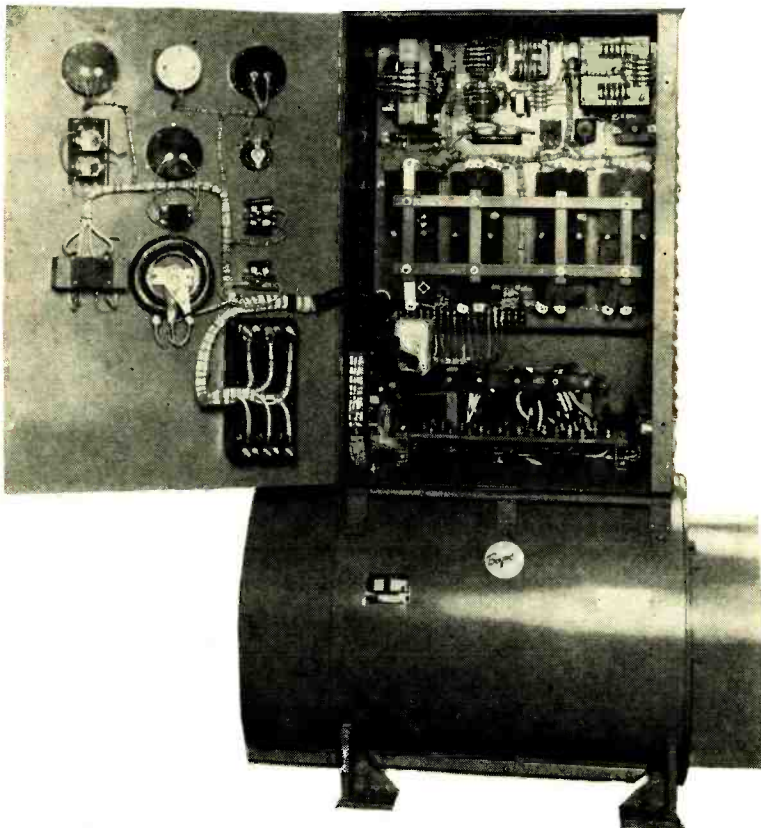- "The Magnetic Amplifier," by A. A. Bosschart, RADIO-ELECTRONICS, September, 1951.
- "Simple Magnetic Amplifier," by Erwin Levey, RADIO-ELECTRONICS, June, 1952.



A magnetic amplifier control used with 400-cycle motor-generator equipment.

SELLING OUT!

COMPLETE STOCK

of Nationally Advertised Radio & Television Testing Equipment, Parts, and Electrical Appliances to be sold regardless of cost.

This is the opportunity of a lifetime!

TEST-CRAFT Model TC-10

Quality Multitester


AC and DC Voltage Ranges: 0-5/15/150/1500/3000 Volts. DC Current Ranges: 0-5/50 ma. 0-1.5 Amps. Resistance Ranges: 0-100 ohms, 0-100 K. Size: 6"x3 1/2"x2. Complete with batteries and full instructions.

Only **\$9.85**

Reg. \$14.85

Model 999 Combination F. M., A. M. and Television Signal Generator A.C. Operated

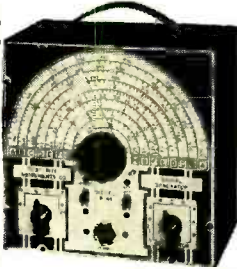Generates R.F. frequencies from 150 kilocycles to 50 megacycles. Positive action attenuator provides effective output control at all times. R.F. is obtainable separately or modulated by the Audio Frequency.



Complete with test leads and full instructions.

Only **\$19.50**

Reg. \$39.50

TEST CRAFT Model TC-50 Tube and Set Tester

tests all tubes up-to-date incl. 4, 5, 6, 7L, octals, loctals, television, magic eye, thyrotors, single ended, floating filament, mercury vapor, new miniatures, etc.

Multimeter Specifications: AC and DC Voltage Ranges: 0-1-100-1000-5000. DC Current Ranges: 0-10/100/1 Amp. Low Resistance Range: 0-10,000 Ohms. Medium Resistance Range: 0-100,000 Ohms. High Resistance Range: 0-1 megohm.

Complete with test leads and full instructions.

Only **\$29.50**

Reg. \$49.50

TEST CRAFT Model TC-75 Combination Test Speaker and Signal Tracer

Combination Test Speaker and Signal Tracer



plus speaker substitution
plus resistor tester
plus condenser tester
plus output indicator
plus field substitutor
plus voice coil substitution
Complete with full instructions

Reg. \$39.50

Only **\$24.50**

PRICES REDUCED UP TO 80%

Below mentioned units are not kits, but all factory wired and brand new. Some models have been discontinued by the manufacturer, but every one is factory sealed and carries a one year, factory guarantee.

		Dealers Net Price	Our Selling-Out Price
SUPERIOR	Model 1553 Multitester	\$ 29.25	\$ 14.50
"	PB-100 Multitester	28.40	15.00
"	680-5000 Ohms per volt Multitester	27.65	14.50
"	670 Supermeter	28.40	22.75
"	TV-11 Tube Tester	47.50	37.95
"	660 Signal Generator	42.95	34.50
"	CA-11 Signal Tracer	18.75	9.95
"	Television Bar Generator	39.95	32.50
METROPOLITAN	111, A.C.-D.C. Multitester	21.50	11.50
"	999, A.M.-F.M. & Television Signal Generator A.C. Operated	39.50	19.50
TEST CRAFT	TC-10, A.C.-D.C. Multitester	14.85	9.85
"	TC-50, Combin. Tube and Set Tester	49.50	29.50
"	TC-75, Combin. Test Speaker and Signal Tracer	39.50	24.50
SUPREME	543-S, Multitester	24.50	14.50
RADIO CITY PRODUCTS	322, Tube Tester	41.50	29.50
"	461, A.P. Multitester	39.50	19.95
"	668, Electronic Multitester	74.50	39.50
"	665, A.C.-D.C. V.T. Volt-Ohm Capacity	95.40	59.50
GENERAL ELECTRONICS	200, A.M.-F.M. & Television Signal Generator, A.C. operated	39.50	24.50
MONITOR	200, Crystal operated Signal Generator	59.50	29.50
WESTON	689-IF, Ohmmeter, incl. leather case	36.50	19.85
SHALLCROSS	630, Wheatstone Resistance Bridge	145.00	75.00
"	637, Kelvine Wheatstone Res. Bridge	185.00	100.00
REINER ELECTRONICS	333, D.C. Volt-Ohm Milliammeter	26.95	14.50
ELECTRONIC MEASUREMENTS CORP.	102, Volometer	14.90	11.90
"	205, Tube Tester	47.50	37.50
"	206, Mutual Conductance Tube Tester	83.50	67.50
"	600, Oscilloscope	99.50	79.50
GRUEN	2 1/2" D.C., D'Arsonval Type, 1 Milliammeter, Meter	9.95	2.95
WESTON	606, 1 Milliam. Meter	12.95	3.95
"	507, F.S.-1.2 Milliam. Meter	12.95	3.95
TRIPLETT	331-JP 30 Amperes, Meter	12.95	4.95
MARION	3" D'Arsonval Type 1 Milliam. with calibrated Volt-Ohm Current Scale, Meter	12.95	3.95
ACRO	Radio & Phonograph Chassis Cradles	6.95	2.95
PHILCO	6 1/2" Paper Recording Discs, sold only in cartons of 100	.15 each	.03
DUOTONE	8" Glass Recording Discs, sold only in cartons of 24	.75 each	.15
"	12" Metal Recording Discs, sold only in cartons of 50	1.50 each	.30
HOLYOKE	180 ohm resistance line cords, 6 feet with plug, No. 22, stranded, finned, copper push-back wire on 500" spools	1.25 each 5.00	.35 2.50
SUPREME	3 speed recordplayers, with life-time needle, portable case, speaker & amplifier	reduced to	14.95
DUOSONIC	Capri, 3 speed recordplayers, cartridge with double-needle, plastic case, speaker and amplifier reduced to		19.95
MAGUIRE	Recordchanger	37.50 each	9.95
CAPITOL	Automatic Pop Up Toaster, fully guaranteed	19.95 each	9.95
NELSON	Model 441, double, twin-sized electric Waffle Maker	14.95 each	7.95
"	Electrical Waffle maker	reduced to	3.95
"	Electrical Mixer	reduced to	4.95
CUCKOO CLOCK	Genuine, imported Black Forest, hand-carved, cuckoos every 15 minutes	reduced to	7.95
GLO	Electronic, oscillating massager with infra-red heat combined	8.95 each	3.95
ROTO-BROIL 400 MODEL IMPERIAL DELUXE	Fully Automatic Rotisserie and Broiler Com- bination, 7-way, with time clock, 3 heat element, double powered	69.50	29.95

All prices are f.o.b. New York, 20% deposit with order, balance C.O.D., or full remittance with order

WRITE, PHONE OR WIRE YOUR ORDER FOR IMMEDIATE DELIVERY. QUANTITIES ARE LIMITED.

METROPOLITAN ELECTRONICS & INSTRUMENT CO.

106 Fifth Ave., New York 11, N. Y.


Telephone: OREGON 5-1707
Cable Address: METRONICS

ROHN *the Foremost Name* in TV Towers...

PRESENTS
2 new additions

the "PACKAGE" TOWER

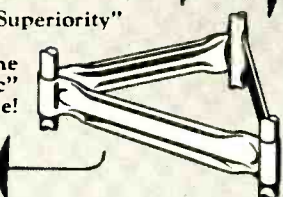The "Superiority" secret is in the "magic" triangle!



The answer to your storage space dreams — reduced freight rates give you the edge on competition!

PAT. PENDING

Both towers are self-supporting and have all the Rohn "Superior Design" features that make the Rohn line truly proved in performance and nationally accepted!

the NO. 6 TOWER

Built to fill 75% of your requirements — structurally as sound as the Rohn Standard No. 10 Tower — yet costs less!

These new Rohn Towers continue to feature the famous triangular design, the self-supporting features and the simplicity of design which gives extraordinary ruggedness and durability! New, advanced Rohn designing utilizes mass production machinery to greatly lower cost — yet actually produce a tower structurally sturdier than before! Get full facts today on Rohn Towers that are loaded with "Sales Appeal" . . . so far advanced in design and engineering to be truly years ahead!

See your authorized Rohn Representative or Distributor for catalog sheets and complete details. Or . . . write, phone or wire . . .



ROHN MANUFACTURING CO.
DEPT. RE 116 LIMESTONE BELLEVUE
PEORIA, ILL.

"Pioneer designers and manufacturers of towers of all kinds sold with assurance and satisfaction coast-to-coast!"

FASTER TROUBLE SHOOTING!

NEW TV DYNATRACER THE 3-IN-1 TEST TOOL

REQUIRES NO ADDITIONAL EQUIPMENT
SIGNAL TRACER · VOLTAGE TRACER · COMPONENT CHECKER

SPECIFICATIONS—The self contained DYNATRACER isolates trouble to a stage or component . . . tracing signals through any Video, Sound Sync, ACF, Horizontal or Vertical Sweep Circuit.

WHAT'S MORE, this remarkable instrument traces voltages (50/500V AC/DC) and then instantly locates open, shorted, intermittent or leaky (up to 20 megohms) condensers, resistors, coils, transformers, etc.

Save Time—Save Labor—Save Money—With The DYNATRACER
—Your Most Indispensable TV Repair Tool—

Complete Trouble Shooting Manual Enclosed FREE

See your local distributor—or if he can't supply you clip a \$5.00 bill, check or money order to this advertisement. 100% absolute satisfaction guaranteed or money back within ten days.

Send Your Order Today to

Century ELECTRONICS CO.
211-04 99th Ave., Dept. 119
Queens Village, N. Y.

10,000 Servicemen
Users of DYNA-
TRACER Can't Be
Wrong!

\$4.95
POSTPAID



TEA CLINIC AND FAIR

The Texas Electronics Association, sponsor of the Radio and Television Service Clinic and Electronics Fair, reports the program was highly successful. The event was held in Dallas, Tex., and was the second annual affair.

The program featured a broad series of technical and business topics with emphasis on color television. The subjects covered color TV lectures, service cost analysis, public relations and advertising, credits and collections, legal aspects, TVI causes and cures, color test equipment, transistors, and merchandising. Each was discussed by a specialist recognized in his field.

The distaff side was treated to a sight-seeing tour, Cinerama and an ice revue.

NETSDA ELECTS HEAD

At a meeting of the National Electronic Technicians and Service Dealers Associations held in New York, Max Liebowitz of New York City was elected president. Other officers elected at the meeting were Dave Van Nest of Trenton, N.J., vice-president; John A. Wheaton of Mineola, L.I., secretary, and T. L. Clarkson of Harrisburg, Pa., treasurer.

Provision was made for incorporation as a nonprofit organization and plans were formulated for rotating meetings in different states and more particularly at local meeting halls of member associations. Group directors are being set up on a state-wide basis to coordinate local and state activities of national interest to radio and TV technicians and dealers.

ALL WORK AND NO PAY

Members of the Television Association of Battle Creek offered to clean the picture tube and cover glass of TV sets free during a 3-day period. The operation was aimed at boosting service business by promoting the goodwill of television users.

The members who took part in the experiment cleaned about 100 sets; few reported any increase in service business. It seems that most of those who asked for the free cleaning service were old customers whose sets were operating perfectly.

FRSAP MEETING

Completed reports concerning an educational program, price survey, and investigation of unethical service advertising were represented at the monthly meeting of the Federation of Radio Servicemen's Associations of Pennsyl-

vania in Altoona, Pa. Upon complete reports from each chapter, the federation plans to make up a questionnaire for distribution to all member chapters throughout the state concerning the charges involved in radio-TV servicing. A standard price-rate sheet based on the answers received will be prepared.

The group's educational committee supplied all delegates with an outline of a service course to be followed by member chapters for the purpose of aiding technicians in each chapter. A copy of the federation's anti-bait advertising bill was also submitted to delegates for possible action by local civic officials in their areas.

COLOR TV SEMINAR

In preparation for color TV in the Miami area a symposium was held in that city, sponsored by the Radio and Television Technicians Guild of Florida, Inc.

A capacity crowd turned out to hear Dr. T. T. Goldsmith, Jr., vice president of Du Mont, speak on the history of color TV and its future as well as various technical subjects. Other speakers also discussed the many phases of this subject of interest to service technicians.

ECTRA ETHICS

A streamlined code of ethics has been outlined by P. O. Ferrera, president of the Erie County Television Radio Association. Reduced to five points, it pledges ECTRA members to:

1. Guarantee radio and TV work for 90 days from date performed and replacement parts for 90 days from date installed.
2. Use only parts of recognized quality.
3. Charge no more than list price for parts.
4. Keep charges for labor fair and reasonable.
5. Perform only such repair work as is necessary or authorized.

GUILD STARTS PRP

The Radio Television Guild of Long Island has released the August issue of their publication, *The Guild News*. It features an editorial on a new venture called PRP (Public Relations Program).

The purpose of this program is to elevate the standards of the service industry to the level of a recognized profession. A business group will be set up within the guild, composed of members who are shop owners or self-employed service technicians. This group will embark on an extensive public relations program.

To be eligible to participate in this program, members will have to meet certain minimum requirements, such as full-time employment in the service industry, and good reputation. Excluded are shops that offer free service, free estimates, dollar service or the various other gimmicks used in bait advertisement.

the **ENCYCLOPEDIA** of **SWEEP CIRCUIT**

SERVICING AND REPLACEMENT

RAM

TELEVISION COMPONENTS SERVICE MANUAL
1955 EDITION
ORIGINAL SERVICE REPLACEMENTS

- 64 pages, 37 "Pix-A-Faults", 67 schematics, 34 "Trouble-Facts" — no other Manual comes anywhere near such completeness!
- Shows you how to find and replace faulty flybacks, yokes, vertical output transformers, vertical blocking oscillators, linearity and width coils — of every type and brand — fast and accurately.
- Latest field-gathered experience — saves you oacs of time, money, labor.

Write for it now.
Ask for Ram Manual RE-11.

RAM ELECTRONICS SALES CO.

Irvington-on-Hudson, New York

Compare! Lowest Prices Anywhere!

FREE BONUS

of tubes with every order.
Cash in on this sensational gift offer!

all TUBES

- Individually boxed
- Guaranteed for 1 Year

0B3 VR90S.75	3E5	.46	6AV6	.37	6F5GT	.39	6U4	.60	12BD6	.45	25W4	.56	
1A5GT	.46	30A	.48	6AX4	.53	6F6	.37	6U5	.44	12BE6	.39	26	.45
1A6	.59	30S5GT	.49	6B6G	.64	6G6G	.52	6U6	.63	12BF6	.39	27	.39
1A7GT	.47	35A	.46	6B5	.64	6H6GT	.41	6U8	.61	12BH7	.63	35B5	.40
1AB5	.59	3V4	.47	6BA6	.39	6J5GT	.37	6V3	.93	12J5GT	.42	35C5	.39
1B3	.65	5U4G	.41	6BA7	.57	6J6	.52	6V6GT	.39	12Q7G	.39	35L6GT	.41
1B5	.59	5V4	.73	6BC5	.41	6K6GT	.37	6W4GT	.44	12S8	.70	35W4	.37
1B7GT	.59	5X4	.40	6BC7	.71	6J7G	.43	6W6GT	.44	12SA7GT	.44	35Z4	.39
1C5GT	.43	5W4	.50	6BD5GT	.59	6J8	.69	6X4	.37	12S7GT	.52	35Z5GT	.37
1E7	.29	5V3G	.32	6BD6	.45	6K5	.47	6X5GT	.37	12S7J	.44	36	.60
1H4G	.48	5V3GT	.32	6BE6	.39	6K7	.44	6Y6G	.48	12SK7GT	.48	42	.42
1H5GT	.40	5V4G	.35	6BF5	.61	6L6	.63	7A4	.47	12SL7GT	.47	43	.55
1G5	.60	5Z3	.46	6BF6	.37	6Q7	.45	7AF7	.53	12SN7GT	.52	45	.55
1L4	.46	6A3	.59	6BG6G	1.19	6S4	.38	7E7	.44	12S07	.42	50B5	.35
1LCS	.51	6A7	.59	6BH6	.46	6S8	.53	7G6	.40	12SR7	.49	50C5	.39
1N5	.46	6A8	.62	6BJ6	.39	6SA7GT	.43	7E8	.49	14AF7	.50	50D6	.59
1P5	.57	6AB4	.44	6BK7	.59	6SD7GT	.41	7F7	.59	14A7	.60	50L6GT	.40
1Q5	.58	6AG5	.43	6BL7	.59	6SF5GT	.46	7X7	.70	14J7	.60	50Y6	.48
1R5	.45	6AJ5	.70	6BD6GT	.65	6SH7	.73	12AL5	.37	14M7	.48	58B6GT	.37
1S5	.39	6AK5	.72	6B5	.65	6SG7GT	.41	12AT2	.37	19B6G	.95	50Y7	.59
1T4	.45	6AL5	.38	6BQ7	.90	6S7GT	.41	12AU5	.38	19C8	.70	70L7GT	1.09
1T5	.53	6AQ5	.39	6BZ7	.90	6SK7GT	.41	12AU7	.43	19T8	.79	75	.41
1U4	.45	6AQ6	.37	6C4	.37	6SL7GT	.48	12AV5	.39	19V8	.89	76	.44
1U5	.39	6AR5	.37	6C5GT	.39	6SN7GT	.49	12AV7	.59	25AV5	.83	78	.47
1X2	.60	6AS5	.50	6C6	.44	6SQ7GT	.37	12AX4	.48	25B6GT	.62	80	.35
2A3	.70	6AT6	.37	6CD6G	1.23	6SR7GT	.60	12AX7	.48	25L6	.39	117Z3	.37
2X2	1.50	6AU6	.38	6D6	.45	6SS7	.60	12AZ7	.69	25Z5	.40	117L7	.39
3A4	.45	6AV5	.83	6E5	.43	6T8	.56	12BA6	.38	25Z6GT	.37	807	1.20

TERMS: A 25% deposit must accompany order, balance C.O.D. Shipments F.O.B. Irvington, N.J. Orders under \$10.00: \$1.00 handling charge. Merchandise subject to prior sale.

HI-LITE

ELECTRONIC SALES CO.

837A 18th Avenue • Irvington 11, N. J.

LEARN COLOR TV THIS EASY WAY!

Just off the Press!

ABC OF COLOR TV



H. G. Cisin's remarkable book takes the mystery out of Color TV. The only book which explains this fascinating new TV development in a simple down-to-earth manner. It actually translates the highly technical descriptions of research scientists into plain everyday language.

Covers basic color principles, compatible color TV system, the color signal, color TV reception, plus practical pointers on color mix tubes, tests, etc. Just the info TV servicemen must have to cash in on this rapidly expanding new field. Profusely illustrated.

Only \$1

NEW! 1955 TV DOCTOR ATTENTION: NOVICE SERVICEMEN!



The new TV DOCTOR was written expressly for you by H. G. Cisin, noted TV educator and author. Mr. Cisin has trained thousands of TV technicians, many of them now holding important positions in television. His years of experience are embodied in this valuable book!

TV DOCTOR contains just the info you need to start in TV servicing. No theory, math or formulas—but full of practical information. Copyrighted Trouble Shooting Guide pin-points hundreds of TV troubles, enabling you to diagnose faults without previous experience. Method applies to all TV sets, old and new. Special chips on COLOR TV and U.H.F. Useful data about TV sets, tuners, antennas, lead-ins, interference, safety suggestions. Many clear illustrations.

Only \$1

FAMOUS "TV CONSULTANT" TV Serviceman's Silent Partner



New, easy-to-use way to solve toughest TV troubles. UHF sec. includes conversions, installations and servicing. Modern alignment methods shown by pictures, diagrams and simple directions, tell exactly what to do and how to do it. Practical pointers on use of all TV Test Instruments. Over 300 pix. raster and sound symptoms. Detailed directions tell where and how to find faulty parts.

Over 135 RAPID CHECKS many using pix tube as trouble locator. 125 illustr. of scope wave forms, diagrams, station patterns, show various defects—take mystery out of TV servicing. NO THEORY—NO MATH—NO FORMULAS—just practical service info. covering all types of TV sets.

Only \$2

NEW! 1954 TV TUBE LOCATOR

TROUBLE INDICATING TUBE LOCATION GUIDES for over 3000 most popular models from Admiral to Zenith plus PIX TUBES used in each model! 1947 to 1953 models. A storehouse of valuable TV servicing info. priced very low for large volume sales.

Only \$1

NEW! Trouble Shooting PIX GUIDE incl. TV TERMS Explained

Sec. 1 is a fully illustrated GUIDE to oft-recurring pix faults. Causes and cures explained. Copyrighted. Trouble indicating Illustrated chart tells where troubles start in typical TV set—illustrations show resulting faulty TV pictures. Sec. 2 explains hundreds of TV terms in non-technical language.

Only \$1

NEW! TV TROUBLE TRACER

Each vol. contains different copyrighted "Trouble indicating TUBE LOCATION GUIDES" of over 500 most popular TV models. Vol. 1 has older sets, vol. 3 newest 1954 models. 40 common picture troubles illustrated, traced to source and cured.

Vols. 1, 2 & 3—Only 50c ea.

H. G. CISIN, PUBLISHER

Order from your Jobber today, or if not stocked, write to

Harry G. Cisin, Dept. E-29
Amagansett, New York

Enclosed find \$..... Send

- | | |
|--|--|
| <input type="checkbox"/> Color TV | <input type="checkbox"/> TV Pix Guide |
| <input type="checkbox"/> TV Doctor | <input type="checkbox"/> TV Tracer, Vol. 1 |
| <input type="checkbox"/> TV Consultant | <input type="checkbox"/> TV Tracer, Vol. 2 |
| <input type="checkbox"/> TV Tube Locator | <input type="checkbox"/> TV Tracer, Vol. 3 |

Name.....

Address.....


City..... Zone..... State.....

new Tubes & Transistors



NEWS of the season was expected to be the 21-inch RCA color tube unveiled by that company at the David Sarnoff Research Laboratories, Princeton, N.J., September 15 in connection with the advance announcement of RCA's new 28-tube color receiver. The new tube uses the conventional three-gun shadow-mask principle, with a curved mask like that of the CBS Colortron. The new tube is a 70°-deflection round metal type, 25 $\frac{3}{8}$ inches long, with picture area of 250 square inches, and a special color equalizer which takes the place of the coil formerly used to neutralize the effect of the earth's field. This consists of a large polepiece in the form of a double ring which goes around the tube just behind the face. On this polepiece are mounted a number of short bar magnets which may be turned to vary the field at any point around the circumference of the tube. The new color equalizer not only gives more effective neutralization of the earth's field, RCA spokesmen pointed out, but cuts manufacturing costs. The ulti voltage of the new tube is 25,000, and the focusing voltage in the order of 4,500, with other element voltages in proportion. The basing diagram was not released, but would probably follow the 19-inch tube. Price to manufacturers was \$175, and tubes were to be available in November.

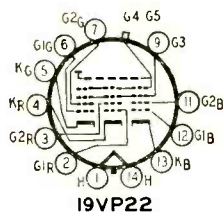The CBS-Colortron 205 (briefly described in September) marked a significant advance in color tube development. The tube has a 6.3-volt filament, drawing 1.8 amperes. It uses electrostatic focusing, electromagnetic convergence




and deflection, and has a deflection angle of 62°. Length is 26 $\frac{1}{2}$ inches. The tube screen is a metal-backed, tricolor, phosphor-dot type.

Under typical operating conditions, the anode voltage is 25,000; the No. 3 grid (focus) voltage is 6,500 to 8,000; with 200 volts on the No. 2 grids, the grid No. 1 voltage, for visual extinction of the raster, is -45 to -100; with -75 volts on the No. 1 grids, the grid No. 2 voltage is 150 to 330.

NEW! ATLAS CJ-30 COBRA-JECTOR

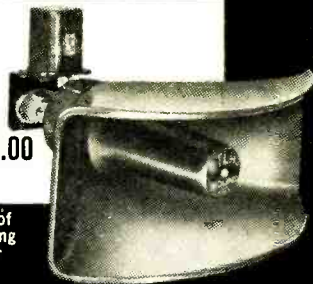INDESTRUCTIBLE FIBER-GLASS
ALL WEATHER
WIDE ANGLE DISPERSION



List \$40.00
NET \$24.00

Complete with Driver.

Weatherproof Line Matching Transformer as shown, Net \$5.10.

New versatile all-purpose projector—excellent for paging & talk-back, intercom, marine, and industrial voice & music systems. Penetrating articulation assures wide angle intelligible coverage even under adverse sound conditions. "ALNICO-V-PLUS" magnetic assembly. Double-sealed against all weather. Omni-directional mounting bracket. Quick, easy installation. An amazing "power package"—Specify the CJ-30 for the "tough" jobs!

Input Power (continuous).....15 watts
Input Impedance.....8 ohms
Response.....250-9000 cps
Dispersion.....120° x 60°
Dimensions:.....Opening, 14" x 6"
Overall Length 14"



WRITE FOR COMPLETE CATALOG

ATLAS SOUND CORP.

1443—39 St., Bklyn. 18, N. Y.

In Canada: Atlas Radio Corp., Ltd., Toronto, Ont.

FRANKLIN Announces New VACUUM TUBE VOLTMETER KIT



Engineered by Electronic Craftsmen with over 30 Years Experience

Model FV-1

\$24.50

5 lbs. ship. wt.

Quality parts—Finest on the market.

Recessed handle—Sinks into case to permit stacking.

Large 4 $\frac{1}{2}$ " meter—Easier to read than others.

Etched panel—Smooth etched rubproof panel keeps wording legible.

Low price—In spite of better grade parts, Model FV-1 sells for bargain price.

Equal to, or better than competitive makes! Fast measurements with greater accuracy on 1 $\frac{1}{2}$ volt low scale give more than 2 $\frac{1}{2}$ -inch scale length per volt. AC-DC ranges 0-1.5-5-15-50-150-500-1500 volts (1000 volt max. on AC). Ohmmeter range from X1 to X100K and X1 meg. Measures .1 ohm to 1000 megohms. Many other features.

Kit includes tubes, assembly material, test leads, manual for assembly. (Wired—\$35.50)

MAIL ORDER for MODEL FV-1 TODAY!

FRANKLIN ELECTRONICS

King St., Franklin Park, Ill.

Enclosed find check, money order. Ship C.O.D. C.O.D. postage. Money back guarantee.

Name.....


Address.....

City..... Zone..... State.....

Now!

telrex

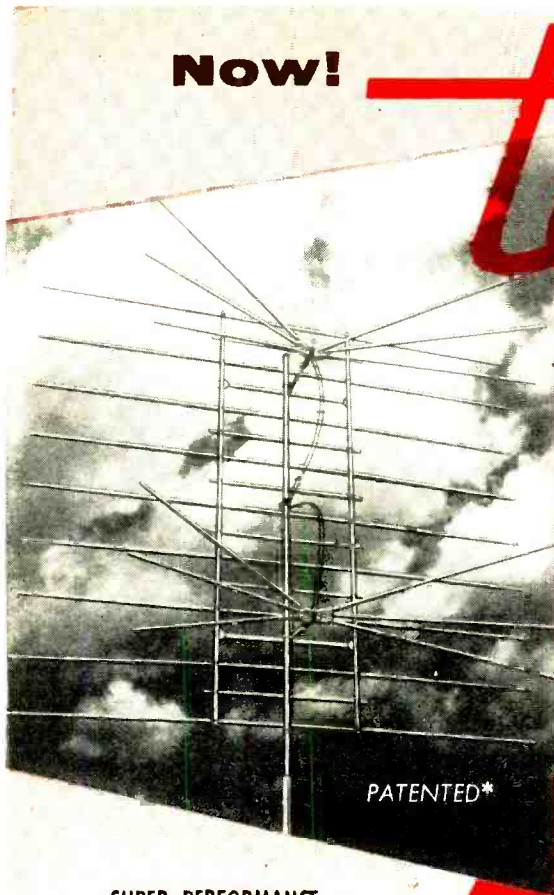**gives you the most
TECHNICALLY
PERFECTED
TV ARRAY
in the entire world!**



**SUPER PERFORMANCE
ON VHF — EXCELLENT
PERFORMANCE ON UHF**

**"CONICAL-V-BEAM" DIPOLES
FOR BEST AND MOST UNIFORM
MATCH TO 300 OR 200 OHM
LINE ACROSS ENTIRE BAND**

**FULLY PRE-ASSEMBLED —
INSTALLS QUICKLY AND
PERMANENTLY**

**NO PHASING (PHASE SHIFT)
TRANSFORMERS ATTACH TO
OHM LINE OR 200 OHM
LOW LOSS LINE**

**ALL ALUMINUM CONSTRUCTION
LIGHTWEIGHT — DURABLE
NO RIVETS TO WORK LOOSE
AND BECOME NOISY!**

LIST PRICES:

**Model 201 (Single Bay) \$26⁵⁰
Model 202 (2 Bays Stacked) \$57⁰⁰
Model 204 (4 Bays Stacked) \$124⁰⁰**

**AMERICA'S
OUTSTANDING
TELEVISION
BEAM**

THE NEW
VHF
**KING
PIN!**

**— designed to obsolete all
existing TV arrays, provides maximum
gain, maximum F/B ratio, minimum
spurious lobes, no phase shift
— best for B&W or Color TV**

The best S/W/R, S/N/R and H-E plane pattern TV Array ever devised. Utilizes the Patented "Conical-V-Beam" theory to perfection. "Conical-V-Beam" dipoles provide true broad-band characteristics with maximum gain and signal to noise ratio with NO PHASE SHIFT. New transmission line and spline back provide the perfect pattern on all channels. If you've tried the rest — Now! Try the best!

telrex **INC.**

"CONICAL-V-BEAMS"®

**ASBURY PARK 9
NEW JERSEY**

**"Conical-V-Beams" are produced under U. S. Patent No. 23,346, Canadian Patent No. 500,436 and British Patent No. 691,485 — other patents pending. Sold only through authorized distributors.*

It's new!
and only your
Centralab
distributor
has it

The **completely insulated**
ceramic disc capacitor
that took 4 years to build

**Centralab
Type MD
Molded Disc**

Available in
53 values
Pkg. of **5—**
only \$1.50
suggested list price

Better-than-ever insulation —
2500 V.D.C. breakdown to ground.
You can place next to a chassis
or high-voltage leads without flash-
over or breakdown.

Higher-than-ever lead strength —
greater than the tensile strength of
the wire itself. Leads can't pull out.

These are only two of many
reasons why the Centralab Type MD
Disc is in a class by itself — why
you can count on getting premium
performance. Get all the facts
from Centralab Catalog No. 29.
Send coupon for your free copy.

Better still, give Centralab MD's
a trial as replacements on your
next jobs.

Centralab

Tear out coupon and mail today!


CENTRALAB,
A Division of Globe-Union Inc.
922K E. Keefe Avenue
Milwaukee 1, Wisconsin

Send me Centralab Catalog No 29.

Name.....
Company.....
Address.....
City..... Zone..... State.....

D-4454

Master the scope

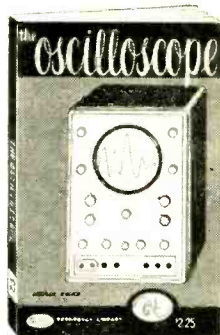

THE OSCILLOSCOPE. By George
Zwick. Gernsback Library Book No.
52. 192 Pages. Over 100 illustrations.
Only \$2.25.

THE OSCILLOSCOPE is first of
all a practical instruction book on
how to use the scope properly. Of
course, the author tells you what
goes on behind the cathode-ray
tube, but when you've got that
down, he really rolls up his sleeves
and gives you full details on how
to use the scope to best advantage
in all types of servicing and how
to understand everything you read
on the face of the tube. Moreover,
he warns you about the pitfalls of
using the scope improperly and
tells you how to avoid them.

WRITTEN FOR ON-THE-BENCH USE

This isn't a book you'll read, dig-
est and forget about. The author
—a teacher and engineer, gives you
the kind of tips you need when
working on some of the "dogs"
likely to cross your bench today.
This is a book you'll keep open on
the bench as you work along with
the set and the scope—and the more
you use it and read it, the more
you'll profit from it. THE OSCIL-
LOSCOPE is the biggest Gernsback
Library Book yet published. Look
at this partial list of contents.
Check all the information it packs
into its 192 pages. Where else could
you get so much information on
oscilloscopes for such a low price!
This book belongs on every service
technician's work bench. Order
your copy today and start now to
cash in on the added knowledge
this book will bring you.

When you really understand how the
oscilloscope works and all the things
it can do, you'll get lots more use out
of it. It will help you do a better job
faster—and in the long run, earn more
money. This big new **GERNSBACK
LIBRARY BOOK** is a practical guide
on how to get the most out of the
scope.

Partial List of Contents of THE OSCILLOSCOPE

CHAPTER 1 WAVE- FORMS

Direct current • alter-
nating current • Al-
ternating current
cycle • Sine waves •
The sawtooth •
Square waves • Trap-
ezoidal waves •
Comparison between
waveforms.

CHAPTER 2—THE CATHODE-RAY TUBE

Structure • The elec-
tron gun • Grids •
Anodes • Cross-over
point • Deflection
system • Time bases
• Linear and non-
linear sweep • The
fluorescent screen •
The phosphor.

CHAPTER 3—SWEEP SYSTEMS

Flyback time • hori-
zontal deflection vol-
tage • Sawtooth gen-
erators • Relaxation
oscillator • Firing
voltage • Sawtooth
frequency • Fre-
quency control • Syn-
chronization • Mark-
er signals • Retrace
blanking.

CHAPTER 4—TYPICAL OSCILLOSCOPES

Circuit analysis of
the Du Mont 208B
and the RCA WO-
56A.

CHAPTER 5—ALIGN- MENT

Meaning of Bandpass
• Alignment of peak-
tuned i.f. system •
Broad-band align-
ment • The FM dis-
criminator • The ratio
detector • Video i.f.
channels • I.f. align-
ment procedure •

Quick alignment
check • TV sound i.f.
channels • Front-end
alignment • Oscil-
lator alignment using
stations • Video-out-
put response.

CHAPTER 6— OSCILLOSCOPE TECHNIQUES

Matching pad bal-
anced to ground •
Scope probes • The
r.f. probe • Isolation
of instrument from
equipment under test
• Coupling to the
front end • Measur-
ing low input vol-
tages • A.g.c. bias
substitute • Calibra-
tion of scope as a
voltmeter • Plotting
curves • Scope pre-
cautions.

CHAPTER 7—TESTS AND MEASUREMENTS

Audio-gain measure-
ments • Audio re-
sponse • Phase shift
• Hum • Video flutter
• Measurement of
current waveshapes
• Auto-radio vibrator
supplies • Selenium
rectifiers • Checking
filter operation •
Measuring ripple.

CHAPTER 8—EXPERI- MENTS USING THE OSCILLOSCOPE

Adjustment of con-
trols • Direct and
amplified signals •
Lissajous figures •
Audio distortion •
Modulation envelope
• Square wave test-
ing • Meter behavior
on pulse voltages •
Capacitor leakage
measurements.

Other Gernsback Library Books you'll want to read.

- Transistors — Theory and Practice.** No. 51—\$2.00
TV Repair Techniques. No. 50—\$1.50
Radio & TV Test Instruments. No. 49—\$1.50
High-Fidelity—Design, Construction, Measurements. No. 48—\$1.50
Radio & TV Hints. No. 47—\$1.00
Television Techniques. No. 46—\$1.50
Radio Tube Fundamentals. No. 45—\$1.00
Basic Radio Course. No. 44 (Cloth Bound)—\$2.25
Model Control By Radio. No. 43—\$1.00
High-Fidelity Techniques. No. 42—\$1.00
Public-Address Guide. No. 41—75c
Practical Disc Recording. No. 39—75c

From the publishers of
RADIO-ELECTRONICS

See your distributor—or mail this coupon

GERNSBACK PUBLICATIONS, INC., Dept. 114
25 West Broadway
New York 7, N.Y.

Enclosed is my remittance of \$.....
Please send me the following books postpaid.

- 52 THE OSCILLOSCOPE \$2.25
 39 41 42 43 44 45
 46 47 48 49 50 51


Name.....
(Please print clearly)

Street.....

City..... Zone..... State.....

Having broken the "electron barrier" that once limited radar performance, a giant electronic tube (see photo) produced by Sperry Gyroscope Co. makes its way into this column. Known as a megawatt klystron, the tube is 8 feet tall and produces 4,000,000 watts, more than 250 times the wattage developed in the radar that beamed pulses to the moon and back in 1946. More important, the frequency of this power can be held 20 to 200 times closer than the frequency limits of radio and TV transmitters in the United States.

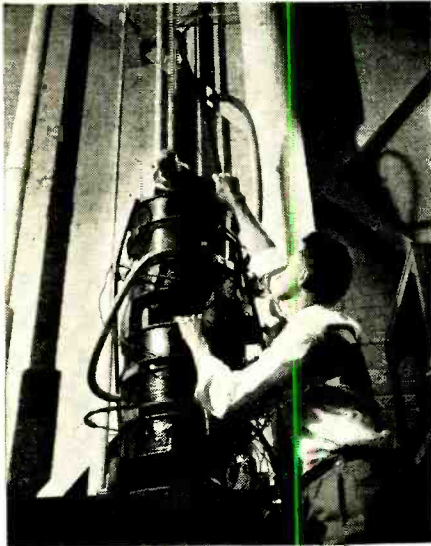
Westinghouse has announced a new 17-inch picture tube having a deflection



The 4-megawatt klystron is installed. angle of 90°. The 17ATP4 and its aluminized counterpart, the 17ATP4-A, use electrostatic focusing and magnetic deflection. They are of all-glass, rectangular construction.

Two new 21-inch, aluminized, all-glass, rectangular television picture tubes, with a deflection angle of 72°, has been announced by Sylvania. The new tubes have gray, filter-glass, spherical face-plates with 265 square inches of useful picture area.

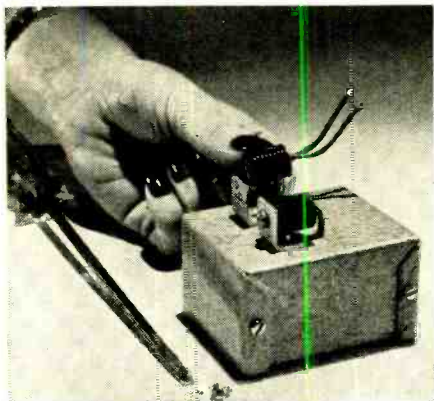The electrostatically focused 21AVP4-A and the magnetically focused 21AWP4 use a single-field ion-trap magnet. These tubes are designed for magnetic deflection and are supplied with an external conductive coating.



New Westinghouse power transistors.


THIS IS THE NEW IMPORTED *Fen-tone* Hi-Fi Audio Line:



Created by craftsmen whose love for music inspired the finest phonograph instrument made.

Featuring:


- ★ The only truly automatic and foolproof changer (patented), playing ten intermixed records, without pre-setting, in any odd size between 6" and 12".
- ★ Precision built: free from rumble and acoustic feedback.
- ★ Automatic muting switch. Automatic shut-off. Built in 3-stage tone filter. Spring mounted chassis.
- ★ Famous P5000 magnetic cartridge, with freedom from distortion over the whole frequency range of 30 to 18,000 cycles, giving "true-to-nature" reproduction of exceptional brilliance.

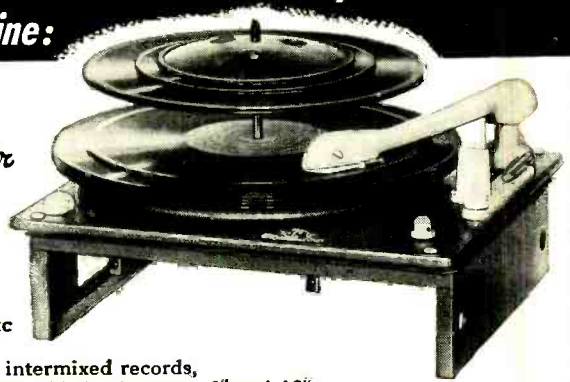

VORTEXION PROFESSIONAL QUALITY TAPE RECORDER

Featuring:

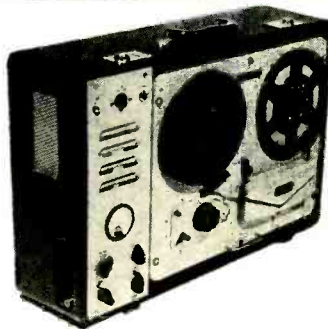- ★ Three individual motors.
- ★ Speed: 7½ and 3¼ I.P.S., dual tracks.
- ★ WOW and FLUTTER less than .2%. Frequency 50—12,000 C.P.S.
- ★ Accommodates 1750' reels (8").




MOTEK TAPE TRANSPORT MECHANISM

(Without Amplifier)



Featuring:

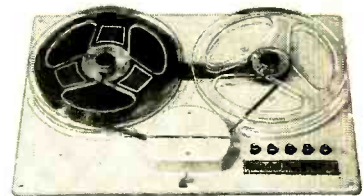- ★ Three individual motors.
- ★ Speed: 7½ I.P.S., dual tracks.
- ★ Hi-Fi record/playback and erase heads.
- ★ Push button control.
- ★ Frequency response better than 50—10,000 C.P.S.
- ★ WOW and FLUTTER less than .3%.
- ★ Accommodates 1200' reels (7").



Ask for descriptive literature


SOLD THROUGH MANUFACTURERS AND JOBBERS

FENTON COMPANY, 15 MOORE ST., N. Y. 4, N. Y.

CONCORD'S BUY OF THE MONTH

Convert to UHF for only...
New WESTINGHOUSE UHF Tuner

It's Fabulous!! The opportunity of a lifetime. Now you can convert to UHF for only \$3.95. Sensational Westinghouse UHF Tuners are designed to operate in conjunction with your present VHF tuner to give you complete ALL-CHANNEL coverage. Tunes 450 to 870 Mc. Output 43 Mc. Regular 300 ohm input. The ideal basic element for building tuner, converter, booster or for experimenting on UHF. Convenient size for installation in TV chassis. (5 x 2½ x 5") Complete with 6AF4 and 6AN1, and easy-to-follow schematic. Shpg. wt. 2 lbs.
Stock No. 99-G-V11390... Worth \$24.95

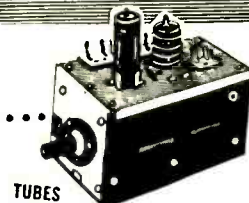

\$3.95

Worth \$24.95
Complete with Tubes and Easy to-follow Schematic.

TUBES ALONE WORTH \$3.50

CONCORD RADIO Dept. C11 54 Vesey St., N. Y. 7
20% deposit with C.O.D. MINIMUM ORDER \$5.00
 Please send NEW 1955 CONCORD Catalog!

NAME _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____


CONCORD RADIO • 54 VESEY ST. NEW YORK 7, N. Y. • DIgby 9-1132

precise

says: Ask ANY
Engineer or Serviceman,
"WHAT'S THE TOUGHEST
TEST OF ALL?"

YOUR test . . . the way the equipment works in actual use . . . under actual conditions. PRECISE test equipment has passed that test countless times . . . every instrument fully proven. That is why YOU and thousands like you have made PRECISE the fastest growing line of test instruments in America today!

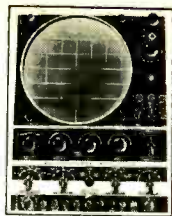Remember, too, PRECISE uses no surplus. See the complete line of PRECISE quality instruments at your jobber now—and save!



EXCLUSIVE PRECISE 8½" OSCILLOSCOPE
#308K kit form \$129.50
#308W factory wired \$229.50


PRECISE 7" OSCILLOSCOPE
#300K kit form \$94.95
#300W factory wired \$199.50

ise ★ precise ★



EXCLUSIVE PRECISE VOLT. REG. V.T.V.M.
#9071K kit form \$35.95
#9071W factory wired \$49.95

ise ★ precise ★ prec

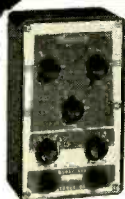

PRECISE RESISTANCE
DECADE BOX
#468K kit form \$18.95
#468W factory wired \$24.95
PRECISE CAPACITY DECADE BOX
#478K kit form \$18.95
#478W factory wired \$24.95



NEW PRECISE VOLTAGE REG. POWER SUPPLY
#760K kit form \$39.95
#760W factory wired \$59.95

precise ★ precise ★ precise ★ precise ★ prec



PRECISE HIGH VOLTAGE PROBE
#999 wired only \$6.98
PRECISE RF PROBE
#912 wired only \$4.25
PRECISE CAPACITY ATTENUATOR PROBE
#960 wired only \$5.95



PRECISE RF-AF-TV & MARKER GENERATOR
#630K kit form \$33.95
#630KA pre-assembled head \$38.95
#630W factory wired \$53.95



NEW PRECISE Em. & MUT. CONO. TUBE TESTER
#111K kit form \$39.95
#111W factory wired \$139.95

★ precise ★ precise ★ precise ★ precise ★ pr



PRECISE UNIV. AF SINE, SQ. & PULSE GEN.
#635K kit form \$33.50
#635W factory wired \$52.50




PRECISE RF SIGNAL GENERATOR
#610K kit form \$23.95
#610KA pre-assembled head \$28.95
#610W factory wired \$39.95



NEW PRECISE VACUUM TUBE VOLTMETER
#909K kit form \$25.98
#909W factory wired \$37.50

precise ★ prec

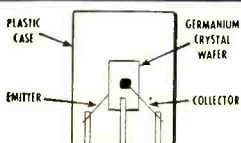

PRECISE NEW T1 TRANSISTOR KIT
PRECISE offers a simple and direct approach to the understanding of transistors. The instruction book covers the physics and practical applications in simple and non-mathematical terms. Two transistors, one germanium diode, transformer, electrolytics, coils, resistors, condensers, chassis, etc. are supplied.
Model T1 kit only \$17.95

precise

DEVELOPMENT CORP.
OCEANSIDE, NEW YORK

Prices slightly higher in the West. Prices and specifications subject to change without notice.

SEND FOR NEWEST PRECISE CATALOG—DEPT. MB-2

NEW TUBES

(Continued)

A series of 13 hydrogen thyratron tubes has been announced by Kuthe Laboratories, Inc., of Newark, N.J. Designed for a wide variety of applications in industrial and military equipment, they range from the type 1528, a miniature tube rated at a peak output of 10 kw at an average power level of 25 watts, to the type 1257, a giant rated at 38,000 kw peak, 45 kw average.

Two new pentodes, designed especially for high-fidelity audio sound systems, have been announced by Amperex. The pentodes, types 6CA7 and EL84, are capable of high plate dissipation. The 6CA7 (25 watts) and the EL84 (12 watts) deliver high power without drawing control-grid current.

Through a combination of special mounting and physical design (see photo), Westinghouse has produced a new germanium power transistor having a 1-watt rating. The black-ribbed mounting provides the cooling necessary for the high collector dissipation.

The p-n-p transistor, type 2N71, can be used in any low-frequency circuit, such as class-A amplifiers, where output power is desired.

CORRECTIONS

A .0015- μ f capacitor should be connected between pins 8 and 3 of the 6H6 in the diagram at the bottom of page 96 in the July, 1954, issue. The omission of this capacitor results in a short across the 24-mc coil.

We thank G. P. Oberto of Richmond, Va., for calling our attention to this omission.

In the article "Tracking Down Horizontal Instability," September, 1954, page 62, a statement is made in the third column, 23rd line: "If a.g.c. tube change does not eliminate pulling, place 0.5- μ f paper capacitor (if keyed a.g.c. is used, 4 μ f) from a a.g.c. bus to ground."

It should read "(if keyed a.g.c. is used; otherwise 4 μ f)."

We thank the author of the article, Mr. Cyrus Glickstein, for calling this error to our attention.

There is an error in Fig. 3 of the article "Color TV Circuits" in the August, 1954, issue. The connections to the screen and controls are reversed. The primary (right-hand) winding of T3 is shown connected between the plate and control grid. The primary winding should be between the plate and screen.

Our thanks to H. T. Fuller of San Bernardino, Calif., for this correction.

A typographical error destroys the meaning of Will's first statement on page 48 of "Television . . . it's a cinch" in the October issue. Will's statement should read: Then, with cathode injection, we'd use negative-polarity detection for one stage and positive for two.

Lafayette GREAT BARGAIN SALE!


3 TUBE
CIRCUIT

alliance

CASCAMATIC
the NEW automatic
TV BOOSTER

SMASH PRICE! ~~29.95~~

6.45 ea. IN LOTS OF 3
singly, ea. 6.95

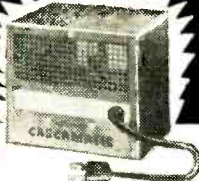


The Alliance Cascamatic TV booster is the latest accessory which combines all the advantages of television boosters in a single unit. Fully automatic — requires no further tuning — no manual control. Automatically turns on and off with set. Completely hidden from view — mounted in back of the set. Instantly installed — requires no further attention. Improves quality of both picture and sound signals. Eliminates noise — improves signal-to-noise ratio. Features famous "California" circuit with three tubes. Works on all VHF channels. Uses two 6J6 tubes and one 6BK7. Attractive metal cabinet 4" x 5 1/2" x 4 1/2". 110-125 volts, 60 cycles AC. Complete with tubes and instructions. Shpg. 1/2 lb.

CASCAMATIC TV BOOSTER.
List \$29.95 In Lots of 3, ea. 6.45
Singly, ea. 6.95

NEW POCKET AC-DC VOM MULTITESTER

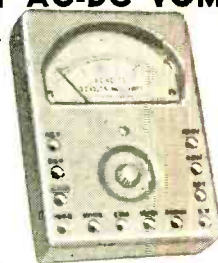9.95

This instrument is one of the best buys that Lafayette has ever offered in a Wide Range AC-DC MULTITESTER. An ideal portable unit that meets the need for a compact, yet rugged test instrument. Has ease of operation usually FOUND ONLY IN MORE EXPENSIVE INSTRUMENTS. Has 1000 ohms/volt sensitivity on both AC or DC. Uses full 3 1/2" rectangular meter with large, easy to read scale. Uses 1% precision resistors. Jeweled D'Arsonval microamp meter movement. Ranges: AC-DC and output volts 0-25, 0-250, 0-1000V; DC current 0-1, 0-10, 0-100. Resistance 0-10K and 0-100K ohms. In handsome sturdy bakelite case. Size 3 1/2" x 3 1/4" x 1 3/8". Supplied complete with test leads and batteries. A Must for every serviceman, shop, laboratory or experimenter—and at Lafayette's Price you can afford to own one. Shpg. Wt. 2 1/2 lbs.



MODEL RW-27C—Complete..... in Lots of 3 **9.45**
Singly, ea. **9.95**

Lafayette Greatest Tape Buy Ever!


1200 FT. REEL
Genuine Plastic Base
RECORDING TAPE

\$1.89 per roll plus postage (C.O.D.'s accepted)

LAFAYETTE made a terrific deal with one of the leading manufacturers of recording tape to supply us with their regular tape which sells for almost twice our price. **WE GUARANTEE ABSOLUTE SATISFACTION OR YOUR MONEY BACK.** The finest, professional-quality recording tape obtainable. Highest performance for thousands of playings. Red Oxide Base in a smooth, uniform coating; greater signal strength; with maximum fidelity; uniform frequency response from 40-15,000 cps.

3 LENS TURRET MICROSCOPE

100X-200X-300X

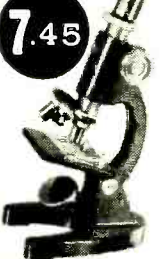

Precision built for accuracy and long lasting service. Triple position turret holds 3 achromatic color-corrected objectives for magnification at 100X, 200X and 300X power! Heavy base and stand—inclines through 90°. Dual knob focusing by rack and pinion. Adjustable plano sub-stage mirror. High-grade microoptics used throughout! Complete with fitted wooden carrying case and slides. Shpg. Wt. 4 1/2 lbs.

F-10 **NET 7.45**

MAP MEASURER & COMPASS

- Not a gadget—a real instrument!
- Measures curved or irregular shapes!
- Use on any size map.

Ideal for motorist—camper—hunter—boating enthusiast! Just trace along route and read distance from dial! Built-in Magnetic compass fully calibrated.

F-47..... **Net 1.69**

4 x 40 FIELD GLASS

- Imported from Germany.
- Built-in Magnetic Compass.
- Smooth Center Focusing.

Magnifies objects 4 times! Not a "drugstore toy". Contain fine optically ground and polished lenses. 40 mm objective lenses for maximum light gathering power. Complete with neck strap.

F-39—Tax Included..... **Net 3.99**

PRECISION DRAFTING SET

11 Pieces—Fitted Felt-Lined Case Made in Germany, of heavy brass, nickel plated and polished. Instruments include 5 1/2" Compass with pencil and pen points and lengthening bar. 5 1/2" Divider, three 3 1/2" sidewheel bow dividers with needle point, pen point and pencil point. 5" Ruling pen, extra handle for pen or pencil, capsule with extra leads. Interchangeability of these many parts makes this an exceptionally versatile set. Your money back—if this set is not worth twice our price!

F-13..... **Net 2.75**

3-SPEED PHONO MOTOR WITH TURNTABLE

Plays 33 1/3, 45 and 78 RPM records. Quiet dependable operation assured by rubber shock-mounted friction type motor. Speed change control permits instantaneous meshing of proper idler for desired speed. Shpg. Wt. 3 1/2 lbs. List Price \$10.95.

Stock No. ML-13..... **Net 4.95**

LAFAYETTE MICROPHONE

3.95

- Western Electric Magnetic Head
- UTC Ouncer Transformer




A terrific value! High impedance mike with —55 db output level. Compact, modern, slim styling. Contains W.E. 253A magnetic head and UTC ouncer. Silver plastic casing with detachable desk stand. Lightweight—only 11 ounces. Complete with 6 ft. cable.

PA-23..... **Net 3.95**

YACHT STYLE BAROMETER

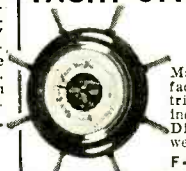- Made in Germany.
- Hardwood Polished Case.
- Solid Brass Spokes.



May be used on wall or desk. Open face porcelainized scale reveals intricate mechanism. Reads 26 to 32 inches. Polished brass bezel. 3 1/4" in Diameter by 1 1/2" deep. Forecasts weather 12 to 24 hours in advance.

F-51..... **Net 5.75**

12" COAXIAL SPEAKER

12-inch Alnico V PM with 1 inch voice coil and heavy one piece cone. Specially designed 3-inch Alnico V PM tweeter completes this combination speaker, range 40 to 17,000 cps. Built-in high pass filter. Installs same as regular PM speaker only two wires to connect. Impedance 8 ohm. Wt. 8 lbs.

STOCK NO. SK-22..... **11.97**



A REAL BARGAIN IN CRESCENT, 3 SPEED AUTOMATIC "INTERMIX" RECORD CHANGER

ONLY 19.95



WITH TURNOVER CRYSTAL CARTRIDGE

Famous make latest design, fully automatic changer at record low price! This peerless performer plays all 7", 10" and 12" records in any sequence. "Free-Floating" featherweight tone arm has Webster turn-over cartridge and dual needles for 33 1/3, 45 and 78 rpm, balanced for excellent tonal reproduction. Automatic shut-off after last record. Direct rim drive turntable action and constant speed motor for "wow"-free operation. Easily installed. Will not jam. 13" x 11 1/2" with 5 1/2" clearance required above and 2 1/2" below mtg. board. Complete with Phono and AC Cords. Fresh stock. Quantity limited at this low price. Wt. 10 lbs. No. A501..... **19.95**

SPEEDWAY 1/4" DRILL



Powerful, lightweight drill, for home or shop. Capacity: 1/4" in steel. 1/2" in hard wood. Speed at full load: 1,500 r.p.m. Heavy duty trigger switch with "lock" and instant release. With Jacobs geared key chuck. For 115 volts AC-DC. Shpg. Wt. 4 lbs. HD-108 Speedway 1/4" Drill..... **Net 14.29**

Phono Cartridges

3.5 volt output

Guaranteed high quality exact duplicates for direct replacement of all standard cartridges such as L70, L82, L92, W60B, N10, and many others. Pin plug connectors for all 78 r.p.m.

LIST PRICE \$5.50

STOCK NO. PK-11—Single, each..... **1.99**

FREE BARGAIN CATALOG

Microscopes, Binoculars, Barometers, Compasses, Timers, Hearing Aids, Tools, Car Radios, Record Players, Tape Recorders, TV Boosters, Antennas, Intercoms, Hi Fidelity Equipment, P.A. Systems, All Radio, TV & HAM SUPPLIES. Check full of buys at great savings. Write today for your free copy.



Top Quality CRYSTAL MIKE

\$5.75

- —52 db output level
- Range 30 - 10,000 cps



A really fine microphone by a manufacturer known the world over. Use for amateur broadcasting, public address and home recording. Can be used with floor stand. Shpg. Wt. 2 1/2 lbs.

PA-21..... **5.75**

SELENIUM RECTIFIER

Stock No.	Mil	Lots of 10	
		Each	Each
RE-12	65 MA	.57	.55
RE-14	75 MA	.67	.64
RE-10	100 MA	.80	.75
RE-15	150 MA	.92	.85
RE-16	200 MA	1.19	1.08
RE-11	250 MA	1.29	1.19
RE-17	300 MA	1.39	1.29
RE-18	350 MA	1.57	1.50
RE-13	400 MA	1.75	1.68
RE-19	450 MA	1.77	1.70



WESTERN ELECTRIC HEARING AID

Reg. price **\$185.00** Our price **\$14.95**

Brand new, in original Western Electric's jeweler's case. Supplied with receiver, receiver cord, battery cord and plug (less batteries). Money back guaranteed. Act now while they last! Uses Burgess JX30E and 8R batteries at \$1.55 per set.



SONOTONE 9980-S

TURNOVER CERAMIC PHONO CARTRIDGE WITH DUAL SAPPHIRE NEEDLES REPLACEMENT FOR COLUMBIA 360—VM—WEBSTER AND CRESCENT RECORD CHANGERS



SPECIFY STOCK NO. PK-40 In lots of 5, each..... **3.50** Singly, each..... **3.98**

BATTERY ELIMINATOR AND CHARGER

WAS 36.75

SPECIAL 17.45



Typical Lafayette Value. Made by leading manufacturer. Operates from 110 VAC and supplies 6 volt DC up to 10 amps continuous, 15 amps intermittent. 9-Position switch adjusts output for any drain from 1/4 amp up. As battery charger delivers approx. 8 amps tapering to 2.5 amps; lower rates obtained from other taps. Has separate voltmeter and ammeter. Size 8 1/4 x 7 1/4 x 7". Metal Cabinet. Shpg. Wt. 16 lbs.

Lafayette Radio
NEW YORK, N.Y. 100 Sixth Ave.
BRONX, N.Y. 542 E. Fordham Rd.
NEWARK, N.J. 24 Central Ave.
PLAINFIELD, N.J. 139 West 2nd St.
BOSTON, MASS. 110 Federal St.
DEPT. JK
Include postage with order.

select
RCP...
for best
test
performance

modern
designs
to
maintain
modern
circuits



Unequalled Performance and Appearance Achieved with New RCP Design.

Universal MULTITESTER—MODEL 480
Only \$14.85 Net

Based on the world famous RCP model 447 Multitester, the model 480 sets an all-time high in value for an economical, rugged, universal tester that is a must for every laboratory, shop and serviceman's kit.


3" meter 800 microampere D'Arsonval movement gives 1,000 ohms per volt sensitivity. Battery for ohmmeter readily removable—no soldering necessary. Flush molded in jacks.

Only because of enormous production is this unusually low price possible. Here is a better, yet lower cost, instrument than any similar unit on the market.

See your local parts distributor or WRITE RE-11 FOR LATEST RCP CATALOG
RADIO CITY PRODUCTS COMPANY
EASTON, PENNSYLVANIA



HEATHKIT OWNERS

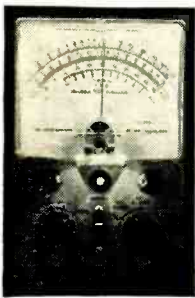

MODERNIZE YOUR VTVM

Illuminate the meter and panel, and improve the looks of your VTVM by installing a STETLIGHT.

The STETLIGHT is a new and different type of panel lamp with a "Plexiglas" prism*, chrome light shield*, and miniature indicating lens*.

Send for free brochure or order a STETLIGHT for your Heathkit today. Other models available for regular panel illumination.

NET PRICE **\$1.00** Postpaid

Mail Check or Money Order To

STETLIGHT

BOX 24 MAYNARD, MASS.

MONEY BACK GUARANTEE

* Patent Applied For

TELEVISION

Big demand for graduates

B.S. DEGREE IN 27 MONTHS in radio including TV engineering—VHF, UHF, AM and FM. Students use over \$100,000 worth of equipment including 2 large commercial type transmitters in new TV lab. Intense specialized course includes strong basis in mathematics, science and advanced design in radio and TV.

Hundreds of young men each year are earning engineering degrees in this recognized institution. Start any quarter. Many earn a major part of expense in this industrial center. Low tuition. Competent instruction. Thorough, intense, practical program. Also **B.S. DEGREE IN 27 MO.** in Aeronautical, Chemical, Civil, Electrical and Mechanical Engineering. G.I. Gov't approved. Enter Dec., March, June, Sept. Free catalog. **ENROLL NOW.**

INDIANA TECHNICAL COLLEGE
1711 E. Washington Blvd., Fort Wayne 2, Indiana

New VU Magnemite*



**Spring-Motor
Battery-Operated
Magnetic Tape Recorder**

Now you can consistently make professional recordings under the most grueling field conditions. Tapes will faultlessly play back on all professional and home recorders. Ruggedly designed for maximum dependability and top-notch efficiency. Combines unlimited versatility of performance with extreme simplicity of operation. Choice of fourteen models available for every conceivable application

Incorporates a multi-purpose VU monitoring meter for precise setting of recording level without earphone monitoring. Meter also accurately indicates condition of "A" and "B" batteries. Five single speeds as well as two, three and 4-speed models available. Units weigh only 19 lbs. with batteries and measure 6½" x 9½" x 14¼". Higher speed models meet NARTB standards. All recorders are guaranteed for One Full Year.


Write for complete technical specifications and direct factory prices to Dept. RE

AMPLIFIER CORP. of AMERICA

398 Broadway, N. Y. 13, N. Y.

* U.S. Pat. Reg. U.S. Pat. Off.

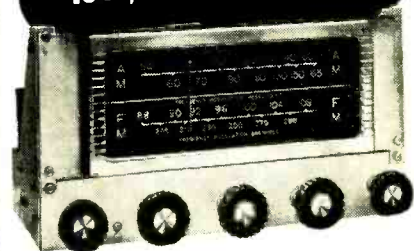Here is the finest
Tuner-Amplifier
at an unbelievably
low, low price!



Hi-Fidelity AM-FM Tuner

with built-in 10 Watt Amplifier

Here's a superb tuner and amplifier integrated as a single unit and featuring extreme sensitivity, selectivity, low distortion. Plug it into any custom music system you're planning and you'll be amazed when you compare its outstanding performance with its price. Shock mounted, it comes complete with 10 tubes for high efficiency, push-pull audio output, full range bass and treble control, large illuminated slide rule dial, tuner and chassis, built-in FM antenna, provision for phonograph input. 10" Hi-Fi Speaker. FM band 88 to 108 MC.

Only
\$52.49

List Price \$139.50

Pre-amplifier \$7.50 additional

Write Dept. RE-11 for latest FREE catalog.

STEVE-EL Electronics Corp.

61 Reade St.

New York 7, N. Y.

RADIO-ELECTRONICS

Technotes



RCA 3-HES-5 (RS-146)


Cases of hard-to-locate hum have been experienced in this record player. This trouble has been traced to an electrostatic condition that causes an accumulation of dust and minute cuttings between the chassis apron and the terminals of the loudness control. This causes a partial short that produces the hum. The difficulty can be eliminated by cleaning the space with an air blast or a soft brush.

Later production models have a coating of black insulating paint at this point.—RCA Service Co.

IGNITION INTERFERENCE

Try checking the continuity of the spark-plug leads when stubborn cases of ignition noise do not respond to the usual treatment. Use an ohmmeter or continuity checker consisting of a battery and small bulb. You may find an open lead between the distributor and a spark plug.

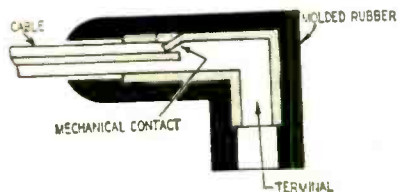Check first the spark plug end of the cable. When the lead end and terminal are molded in rubber, the terminal is probably not soldered to the conductor. The connection will be purely mechanical. Use pliers to squeeze the rubber housing at the cable end of the terminal. If continuity is restored,




the connection is probably satisfactory. If the contact is intermittent, the quickest remedy is to open the rubber housing and solder the lead to the terminal. Reinsulate the terminal to prevent corrosion. The drawing shows the cross section of a typical ignition terminal.

If you decide to replace the open lead, be sure to check continuity in the new lead. Open leads may be satisfactory from an ignition standpoint; they are unsatisfactory for interference-free radio reception.—Motorola Newsgram

ADMIRAL 24D1

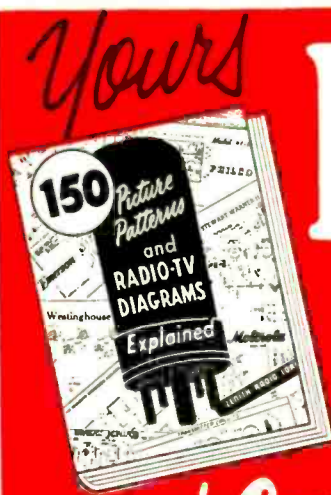The complaint was flickering, with a 2-inch wide bar moving vertically across the screen. The trouble was difficult to localize because any movement or tapping anywhere on the chassis caused interference in the picture. It proved to be intermittent grounding of



Yours FREE!

"Applied Practical Radio-Television"

This Big Valuable Book Given
Just For Examining
Coyne's New 6-Volume Set

ON 7 DAY
FREE TRIAL!



Yes, you get this big, new 1954 book, "150 Radio-Television Picture Patterns and Diagrams Explained", absolutely FREE! Just off the press! Gives complete 11 x 22" Schematic Diagrams on leading models Radio and Television Sets. Easy-to-read, large 8½ x 11" pages, with full instructions on how to read and use the diagrams. A "must" in every Radio and Television serviceman's repair kit. You get this valuable book as a FREE Gift for asking to see Coyne's great new 6-book set, "Applied-Practical Radio-Television"!

At Last! Money-Making "Know-How" on Transistors, Color TV and Servicing

Coyne's great new 6-volume set gives you all the answers to servicing problems—quickly! For basic "know-how" that is easy to understand, you'll find everything you want in volumes 1 to 5 which contains over 5000 practical facts and data. They cover every step from principles to installing, servicing, troubleshooting and aligning all types of radio and TV sets. So up-to-date it includes COLOR TV and UHF, adapters, converters. Also covers latest data on TRANSISTORS.

Extra! 802-Page Television Cyclopedic Included

And then, for speedy on-the-job use, you get Volume 6—the famous COYNE TELEVISION CYCLOPEDIA. It answers today's television problems on servicing, alignment, installation and others. In easy-to-find ABC order, cross indexed. Use this 6-Volume TV-RADIO LIBRARY free for 7 days; get valuable Servicing Book ABSOLUTELY FREE!

SEND NO MONEY!

Just mail coupon for 6-volume set on 7 days free trial. We'll include book of 150 TV-Radio Patterns & Diagrams. If you keep the set, pay \$2 in 7 days and \$2 per month until \$22.50 plus postage is paid. (Cash price \$20.95.) Or you can return the library at our expense in 7 days and owe nothing. YOU BE THE JUDGE. Either way, the book of TV-Radio Patterns is yours FREE to keep! Offer is limited. Act NOW!

OVER 2500 PAGES OF RADIO & TELEVISION FACTS

Vol. 1—Application of Television-Radio Principles; 300 pages—resonance, tuning, amplifiers, oscillators, etc.

Vol. 2—Radio, Television & FM Receivers; 403 pages—rectifiers, high frequency, short wave, FM, antennas.

Vol. 3—Radio-Television Circuits; 386 pages—power tubes, decoupling, distortion, photo-tubes, phase inverters, etc.

Vol. 4—Latest Instruments For Servicing; 343 pages—all types of testing instruments; their use in service work.

Vol. 5—TV Servicing & Trouble Shooting Manual; 400 pages—servicing of all TV sets, UHF, boosters, color TV printed in 4 colors, transistors, etc.

PLUS TV CYCLOPEDIA

Quick answers to all TV problems in A-B-C order, 802 pages, illustrated; hundreds of facts on servicing UHF, transistors, installation, alignment, much more.

FREE BOOK—FREE TRIAL COUPON!

Educational Book Publishing Division
COYNE ELECTRICAL SCHOOL, Dept. B4-T1
500 S. Paulina St., Chicago 12, Ill.

YES! Send 6-volume "Applied Practical Radio-Television" for 7 days FREE TRIAL per your offer. Include TV-Radio Patterns & Diagram Book FREE.

Name _____ Age _____
Address _____
City _____ Zone _____ State _____

Where Employed _____
 Check here if you want library sent COD. You pay postman \$20.95 plus COD postage on delivery. 7-day money-back guarantee.

COYNE ELECTRICAL SCHOOL

(Educational Book Publ. Div.)
500 So. Paulina Street
Dept. B4-T1, Chicago 12, Ill.

5
CORES
OF
ERSIN
FLUX

in **ERSIN**
Multicore
**WORLD'S FINEST
CORED SOLDER
ON WOODEN SPOOL**

ASK FOR
NEW
50c
**SERVICE
PAK**

Ready Now
ON YOUR
JOBBER'S
COUNTER

EXTRA VALUE! Unlike other low cost, haphazard solder packages, the MULTICORE SERVICE PAK features a convenient wooden spool, and—important to you—length of wire, alloy and gauge is clearly marked on every 50c SERVICE PAK!

Also available in 1 lb. cartons and 7 lb. reels.

MULTICORE SALES CORPORATION, 164 Duane St., New York 13, N. Y.

STOP!
TV INTERFERENCE

Eliminates interference caused by Short Wave... F.M. Hams... Diathermy... Atmospheric disturbances, etc.

With a **TELEMATIC**
Full Range FILTER KIT

SIMPLE — SPEEDY — EFFICIENT

- Eliminates antenna-fed interference!
- Covers full-range both I.F. and R.F. Sharper, steadier picture!
- Fewer service recalls!
- Any filter in kit replaceable separately!

FILTER KIT
contains 2 Hi-Pass Filters, 4 WAVE TRAPS covering full range of interference signals.

Send for **FREE** Booklet on "TV-INTERFERENCE"

TELEMATIC
16 Howard Ave. Brooklyn 21, N.Y.

CRYSTAL MIKE (O.D. 2 1/4" x 5 3/4") Hi-impedance. Use as LABEL or HAND MIKE. Moulded black bakelite case; 12 ft. shielded cable. \$3.98

ORNAMENTAL METAL GRILLE . . . Bright brass finish, diamond 1 3/4" x 1 3/4" — 12" x 12" — 99c; 12" x 18" — \$1.49; 16" x 16" — \$1.59; 16" x 20" — \$1.98; 18" x 24" — \$2.75. (ANY SIZE CUT TO ORDER UP TO 48" sq. ft. — \$1.00 sq. ft.)
PLASTIC "SARAN" GRILLE CLOTH. Beautiful Gold or Mahogany weave. Sizes to 72" wide—per sq. ft. 50c.
1 1/2" FIBRE-GLASS ACOUSTICAL CABINET LINING for all sound-absorption purposes. 36" wide—\$1.15 running ft.
Ideal intercom sub-station. (Size: 5 3/4" x 1 1/4" x 3 1/2") \$1.29

!! ALNICO MAGNETS !!



Just a few of the many types always in stock!

Polished Bar . . . 9/16" x 7/32" x 3/4" . . . \$1.00; 100/\$7.50
"U" Type . . . 3/4" x 3/8" x 1/2" . . . 49c; 12/\$5.00
Large "U" Type . . . 2 1/2" x 1 1/4" x 3/4" ea. \$1.39; 6/\$5.95
Ring Type . . . 2 1/2" dia. 1 1/4" thick ea. \$2.59
1 1/2" dia. 1 1/4" thick ea. \$2.59
Alnico "Chip" Magnets . . . Small, ferric shapes, approx. 90 pcs./oz. 15c/oz.; \$1.50 lb.
Alnico Magnet Kit . . . Powerful Bar, Block, "U", Rod, etc. Kit of 10 assorted. \$2.98
(WRITE FOR LATEST ALNICO SUPPLEMENT)

RM-38A CONTROL UNIT Loaded with: Lever Switches, Resistors, Terminal Jacks, Cables, Plugs, etc. \$2.95

!! SCOPE PARTS !! . . . 3" CR TUBE (3BP1, etc.) \$1.29
5" CR TUBE FRONT BEZEL 98
5" CR TUBE SPONGE RUBBER FRONT GASKET . . . 69
5" SCOPE VISOR—moulded vinyl 98
5 1/4" CLEAR CONVEX GLASS LENS, rad. 39c; 6/1.98
ANR-II-1 PHONE UNITS . . . 300 ohm . . . ea. . . 98
RADIO-TV BUILDERS LIBRARY for Hams, Servicemen, Students, 25 inside; Photofacts, Riders & other TV and Radio schematics—set . . . 98
RADIO HARDWARE TREASURE . . . FULL LB. CAN. of: Nuts, Screws, Washers, Etc. . . . 89c; 3 lbs. \$2.49

Jumbo Radio-Electronics Parts Kit!!!!
OVER 10,000 ALREADY SOLD!
WHY PAY MORE FOR PARTS? Here's a "GOLD-MINE" of new & surplus inventory odds & ends at a fraction of original cost. 15 FULL LBS. OF CONTROLS, SOCKETS, CAPACITORS, RESISTORS, WIRES, COILS, PHOTOFACTS, TV & RADIO DIAGRAMS, SWITCHES, CHASSIS, PLUS DOZENS OF OTHER ITEMS! (Ship. wt. 20 lbs.) \$3.95
ALL FOR
"DIRECT FACTORY SPEAKER REPAIRS SINCE 1927"
Min. Order \$3.00; 25% discount on all C.O.D.'s. Full remittance with foreign orders. Please add sufficient postage—excess refunded.

LEOTONE RADIO CORP.
67 Dey Street
New York 7, N. Y.

TECHNOTES (Continued)

the top tuning slug in the ratio detector transformer.

Originally the slug was fixed in place with wax. In time, the wax melted from the heat and left a thin film between the slug screw and the ground clip. Vibration from the speaker or any other source caused intermittent contact.

The remedy is to clean the slug screw with contact cleaner and then rotate the screw back and forth while pinching the clip to the screw with the fingers. Wrap a rubber band around the shaft and clip to hold the final adjustment. Rewaxing is an invitation for the trouble to return.—*Elmer M. Woods*


STROMBERG-CARLSON TV

If you have trouble with poor interlace in Stromberg-Carlson TV sets, check the circuit for a 10,000-ohm resistor (R48 in most sets) connected in series with a capacitor between ground and the B plus end of the vertical oscillator transformer.

Removing this capacitor will probably cure the interlace troubles.—*Carl Hennig*

A.C.-D.C. SETS

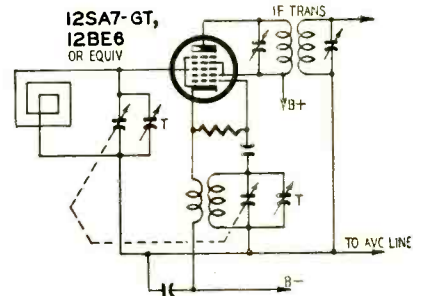When poor sensitivity in a.c.-d.c. sets is not due to low voltages, weak tubes, and other usual causes, use a v.t.v.m. to check for a high negative voltage on the signal grid of the converter tube. A high negative voltage is usually caused by a leaky oscillator grid coup-



ling capacitor in sets using the circuit shown. Any leakage in the oscillator grid capacitor couples the oscillator's d.c. bias voltage to the a.v.c. line and causes loss of sensitivity. Replacing the capacitor restores the original performance quality of the receiver. This defect is troublesome because usual servicing procedures do not lead to suspicion of the grid-leak circuit.

This trouble occurs often in sets with the tuning capacitor rotor and both coils returned to the a.v.c. line as in the diagram.—*Ralph S. Thompson*

G-E MODEL L-573

A flickering pilot lamp accompanied by hum is often caused by an intermittent short or high leakage in the pilot lamp socket. Replace the socket with a new one.

The same symptoms may occur in other a.c.-d.c. sets that have a tapped heater for the pilot lamp.—*John C. Chepla*

END

ONLY
Grommes
HI-FI AMPLIFIERS
offers SO MUCH
for SO LITTLE

Performance and quality
comparable to costlier amplifiers



\$59.50
net
Model 55-PG

Sensational new 12 watt successor to the famous Grommes 50-PG series. Advanced design features: 4-position record compensator, rumble switch, loudness switch, feedback phone equalization and cathode coupled calibrated bass and treble controls.

Power output—12 watts; 20 watts peak.
Distortion—1% harmonic and 2% intermodulation at 12 watts.
Frequency response—± .5 DB. 20 to 50,000 CPS.
Power response—± 1. DB. 30 to 20,000 CPS at 10 watts.
Outputs—includes high impedance jack for tape recorder.
Removable etched control panel; many other features.

BIGGEST VALUE
IN 10 WATT AMPLIFIERS



\$42.75
net
GROMMES Model LJ-3

New Grommes Model LJ-3 offers the most value in 10 watt amplifiers in the low-priced field. Features 4-position record compensator, 3 inputs, bass and treble controls and increased negative feedback.

Power output—10 watts; 18 watts peak.
Distortion—2% harmonic and 3% intermodulation at 10 watts.
Frequency response—± 1. DB. 20 to 20,000 CPS. 2 AC outlets; fuse; many other features.

See Nearest HI-FI Jobber or Send Coupon



Grommes

DIVISION of PRECISION ELECTRONICS, INC.
9101 Etj King St., Franklin Park, Ill.

Rush FREE New Bulletin

Name _____

Address _____

City _____ Zone _____ State _____

Patents



EFFICIENT TV RECEIVER

Patent No. 2,683,805

George W. Fyler, Lombard, Ill.

(Assigned to Motorola, Inc., Chicago)

A TV receiver consumes considerable power. Most of it is necessary for proper operation of the set, but a significant fraction represents useless heat loss. This is because certain TV tubes operate at only 150 volts. Some require 250 volts for maximum efficiency, while still others need higher voltage, approximately 400. With a single power supply, the lower-voltage tubes must be supplied through voltage dividers or dropping resistors. These generate plenty of heat that raises the electric bill. They also complicate the circuit.

This invention cuts power loss in a receiver by connecting tubes in series. A voltage doubler supplies 400 volts to the set. A lower string of six tubes includes low-voltage types. They are supplied with 150 volts. An upper string comprises 250-volt tubes. Their plates are connected to the 400-volt line, but their cathodes are tied to the 150-volt bus. In other words, the tubes themselves divide the higher voltage.

Tubes requiring a full 400 volts are connected from the 400-volt line to the negative bus. Three others—the horizontal output, vertical oscillator and vertical output tubes—are fed from the boosted (500-volt) supply.

The plate voltage of the a.c. tubes in the lower string tends to fluctuate with signal strength. To prevent this, the audio output tube is placed in the upper string. This tube passes considerable plate current which loads and stabilizes the 150-volt bus.

One problem remains. The audio output tube is usually a high gm type. A slight change in grid bias results in a large variation of plate current. This might affect the voltage on the tubes in the lower string. To prevent this a large cathode resistor is connected in series with the first audio tube. This stabilizes its plate current. Then the audio output tube is *directly coupled* to the plate of the previous tube, assuring a constant plate current from the output tube and, in turn, a constant potential at the 150-volt line.

TRANSISTOR BIAS CIRCUIT

Patent No. 2,680,160

Robert E. Yaeger, Califon, N.J.

(Assigned to Bell Telephone Labs., Inc.)

Base current of a junction transistor varies considerably with temperature. Therefore constant bias cannot be obtained from a resistor in the base lead. This invention uses a resistor in the emitter circuit. It stabilizes the flow into the emitter as well as the collector current.

The diagram shows an n-p-n transistor using a single battery of about 4.5 volts. Resistors R₁ and R₂ divide this voltage so that about 0.5 volt is impressed at the base. R₃ is chosen for approximately the same voltage to the emitter. Thus the potential difference between base and emitter is near zero. For an n-p-n crystal, the emitter should be slightly negative.

If the base current is kept small, the emitter current is nearly constant and equal to:

$$I_e = E \frac{R_1}{R_3 (R_1 + R_2)}$$

This also gives the value of collector current.

“SHALL I
BUY A
TURNTABLE
OR A
RECORD
CHANGER?”



GET THE FACTS

from one of America's leading manufacturers of professional recording and playback equipment. Plus a FREE Strobe Disc for checking Turntable Speeds. Write today.

REK-O-KUT COMPANY, Dept. PL-13
38-01 Queens Blvd., Long Island City 1, N. Y.

Please send me the facts on turntables and record changers... plus the Free Strobe Disc.

Name _____

Address _____

City _____ Zone _____ State _____

My Dealer is _____

Engineering

WRITERS

ENGINEERS, E. E. or PHYSICS GRADUATES, for preparation of technical manuals...

HUGHES RESEARCH AND DEVELOPMENT LABORATORIES' expanding program for production of radar, electronic digital computers, guided missiles and other military advanced electronic systems and devices requires the following:

1 ELECTRICAL ENGINEERING AND PHYSICS GRADUATES to prepare operating, servicing and overhauling instructions for complex electronic equipment. Those with previous maintenance experience on military equipment preferred. Writers will participate in a three-month program in our technical training school to become familiar with the latest Hughes equipment prior to writing assignments.

2 ENGINEERS EXPERIENCED in the writing and preparation of maintenance manuals for electronic equipment or guided missiles. These specialists will work step-by-step with the people designing, developing and manufacturing the products involved. Experience in the writing of engineering reports is of value.

HOW TO APPLY

Write full details of your qualifications to

HUGHES

Research and Development Laboratories

SCIENTIFIC AND ENGINEERING STAFF


Culver City, Los Angeles County California

Assurance is required that relocation of the applicant will not cause disruption of an urgent military project.

PATENTS

(Continued)

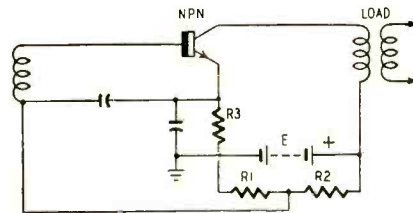Temperature effects are minimized by this circuit. A power amplifier may be designed for optimum output without fear that a rise in ambient temperature will damage the crystal.



TV RECORDING

Patent No. 2,682,572

George K. Graham, Oceanside, N.Y.

[Assigned to Radio Corp. of America]

TV broadcasters record their programs on 16-mm motion picture film. A film camera is mounted in front of a special kinescope and the pictures are photographed. A kinescope recording—or more briefly, "kinescope"—does not have the best quality since it is photographed from a scanned TV image. This new invention permits improved quality by using a film camera alongside each TV studio camera. As the director switches from one TV camera to another, he automatically energizes the corresponding film camera.

At the beginning of each scene, the camera number is "fogged" on the film for identification. A relay system also marks on the film the number of the camera that took the previous scene. Thus the separate strips of negative may be spliced in correct order, no matter how many cameras are used for a particular program.

One important matter is the lag between the instant a film camera is energized and the time it reaches synchronous speed. A line is fogged on the film to indicate the exact frame at which the camera reached proper speed. In addition, the camera shooting the previous scene must continue to operate until the succeeding one reaches correct speed.

The sound track is no problem. No matter how many cameras are in use, a single strip of film can record the sound of the entire program.

VOLTAGE MULTIPLIER


Patent No. 2,682,002

Van R. Gibson, Jr., North Syracuse, N.Y.

[Assigned to General Electric Co.]

No tapped transformers or voltage dividers are found in this circuit, yet it provides for several stepped-up voltages. Each of the available outputs is a multiple of the input.

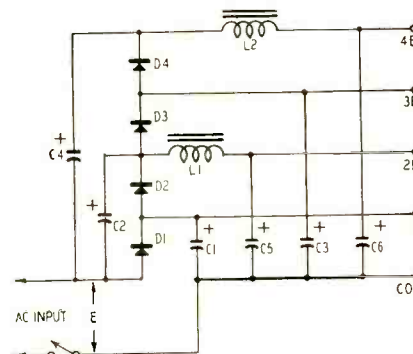A quadrupler is shown in the diagram. During the first (positive) input half-cycle, C1 charges to the peak value (E) of the input through D1. During the next negative alternation, D1 blocks, but C1 is in series with the line. Therefore C2 charges to 2E volts through




D2. During the next half-cycle, the line is positive again and acts in series with C2. Therefore C3 is charged to 3E volts through D3. During the fourth alternation, C4 charges to 4E volts through D4. More rectifiers could be added for still greater voltage multiplication.

(Continued on page 124)

SAVE!

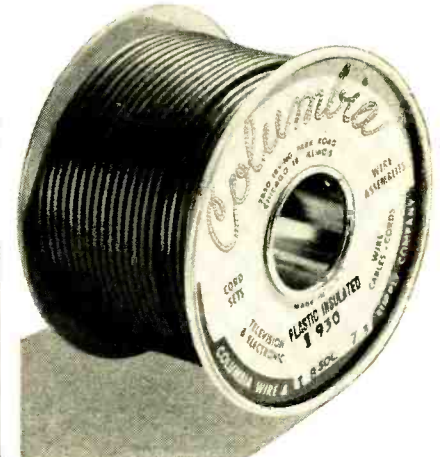with
Columbia
**PLASTIC INSULATED
HOOKUP WIRE**



SAVE!

Save time by conveniently having the hookup wire you need on service calls. Buy this hookup wire at one cost per spool no matter what gauge or type.

SAVE!

Obtain attractive, re-usable, durable metal spools at no cost. Spools can be utilized after wire on spool is used up.

SAVE!


Minimize service problems by carrying the hookup wire with ten different colors for each gauge... easier to find, easier to use, better to work with.

ORDER FROM YOUR JOBBER TODAY! Illustrated catalog is available. Write today.

Watch for Columbia's new packaging of Television Cable!


Columbia
WIRE & SUPPLY CO.
2850 Irving Park Road • Chicago 18, Ill.
"America's Most Complete Wire Line"

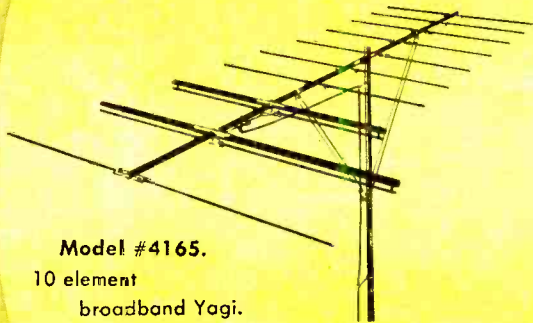A new standard in
 electrical and mechanical
 perfection in all **32**
 new YAGI antennas




Model #4165.
 10 element
 broadband Yagi.

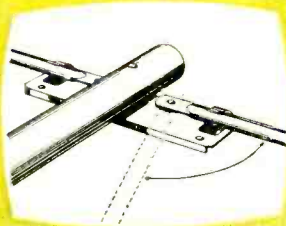Walsco's exclusive
 "umbrella" snap-out
 design provides perfect
 element alignment
 instantly.




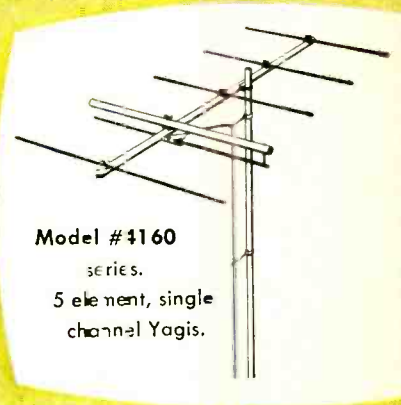Featuring the new
 WALSCO "Octopus"
 Model #4110.
 A combination
 Yagi-conical for
 superlative all-channel
 reception.



Model #4160
 series.
 5 element, single
 channel Yagis.

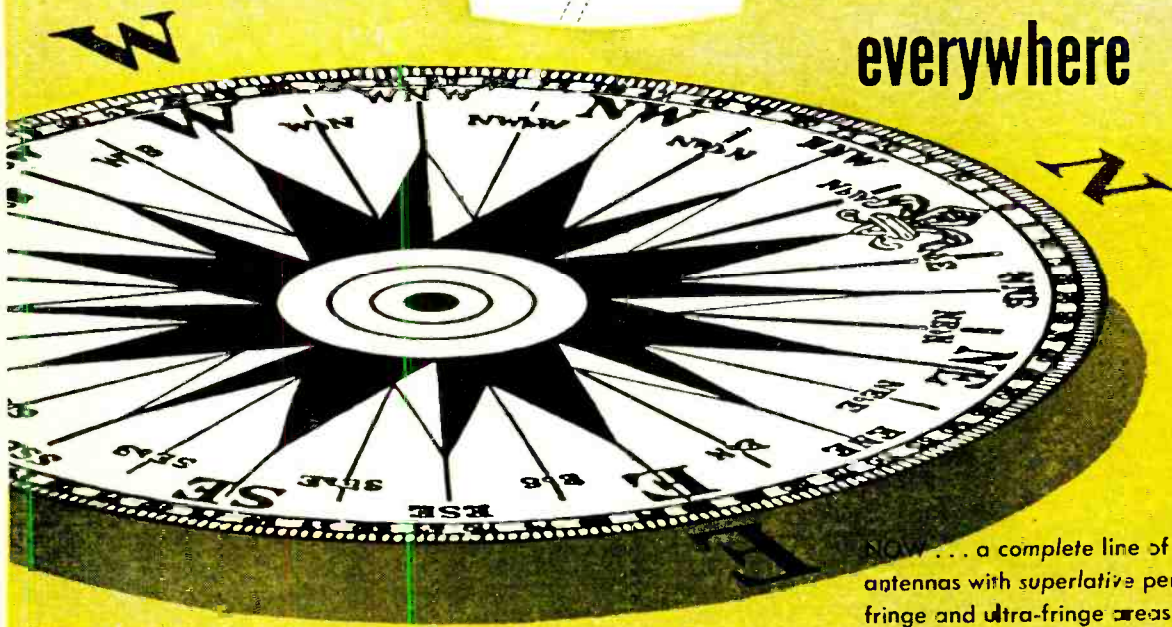WALSCO "futurized" YAGIS reach everywhere



NOW... a complete line of 32 "futurized" Yagi antennas with *superlative* performance... for fringe and ultra-fringe areas; for black and white and color on all present and future channels. No loose hardware... completely pre-assembled using Walsco's exclusive "umbrella" snap-out design. Nothing compares at any price!

Write for complete information
 on all 32 "futurized" Yagi models




ELECTRONICS CORPORATION

3602 Crenshaw Blvd. • Los Angeles 16, California

Overseas Distributor:

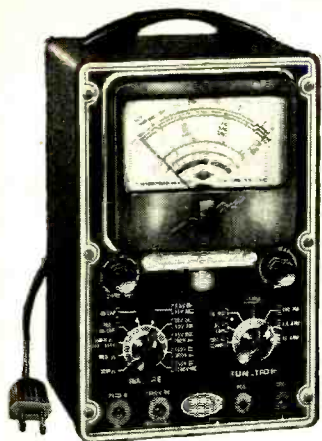Ad Auriema, Inc. • 89 Broad St., New York 4, N.Y.



Measures 6 1/4" x 9 1/2" x 4 1/2"

Superior's new
Model 670-A

SUPER METER

A COMBINATION VOLT-OHM MILLIAMMETER PLUS
CAPACITY REACTANCE INDUCTANCE AND DECIBEL MEASUREMENTS

SPECIFICATIONS:

D.C. VOLTS: 0 to 7.5/15/75/150/750/1,500/7,500 Volts
 A.C. VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
 OUTPUT VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
 D.C. CURRENT: 0 to 1.5/15/150 Ma. 0 to 1.5/15 Amperes
 RESISTANCE: 0 to 1,000/100,000 Ohms 0 to 10 Megohms
 CAPACITY: .001 to 1 Mfd. 1 to 50 Mfd. (Good-Bad scale for checking quality of electrolytic condensers.)
 REACTANCE: 50 to 2,500 Ohms 2,500 Ohms to 2.5 Megohms
 INDUCTANCE: .15 to 7 Henries 7 to 7,000 Henries
 DECIBELS: -6 to +18 +14 to +38 +34 to +58

ADDED FEATURE:

Built-in ISOLATION TRANSFORMER
reduces possibility of burning out
meter through misuse.

The Model 670-A comes housed, in a rugged crackle-finished steel cabinet complete with test leads and operating instructions.

\$2840
NET



Superior's new
Model TV-11

TUBE TESTER

SPECIFICATIONS:

- ★ Tests all tubes including 4, 5, 6, 7, Octal, Lock-in, Peanut, Bantam, Hearing Aid, Thyatron Miniatures, Sub-miniatures, Novals, Sub-minars, Proximity fuse types, etc.
- ★ Uses the new self-cleaning Lever Action Switches for individual element testing. Because all elements are numbered according to pin-number in the RMA base numbering system, the user can instantly identify which element is under test. Tubes having tapped filaments and tubes with filaments terminating in more than one pin are truly tested with the Model TV-11 as any of the pins may be placed in the neutral position when necessary.
- ★ The Model TV-11 does not use any combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible

to damage a tube by inserting it in the wrong socket.

- ★ Free-moving built-in roll chart provides complete data for all tubes.
- ★ Newly designed Line Voltage Control compensates for variation of any Line Voltage between 105 Volts and 130 Volts.
- ★ NOISE TEST: Phono-jack on front panel for plugging in either phones or external amplifier will detect microphonic tubes or noise due to faulty elements and loose internal connections.

The model TV-11 operates on 105-130 Volt 60 Cycles A.C. Comes housed in a beautiful hand-rubbed oak cabinet complete with portable cover

\$4750
NET

EXTRA SERVICE—The Model TV-11 may be used as an extremely sensitive Condenser Leakage Checker. A relaxation

type oscillator incorporated in this model will detect leakages even when the frequency is one per minute.

SUPERIOR'S NEW MODEL TV-40

C.R.T. TUBE TESTER

A complete picture tube tester
★ for little more than the price of a "make-shift" adapter!!

★ Tests all magnetically deflected tubes . . . in the set . . . out of the set . . . in the carton!!



The Model TV-40 is absolutely complete! Self-contained, including built-in power supply, it tests picture tubes in the only practical way to efficiently test such tubes; that is by the use of a separate instrument which is designed exclusively to test the ever increasing number of picture tubes!

EASY TO USE:

Simply insert line cord into any 110 volt A.C. outlet, then attach tester socket to tube base (Ion Trap Need Not Be on Tube). Throw switch up for quality test . . . read direct on Good-Bad scale. Throw switch down for all leakage tests.

SPECIFICATIONS:

- Tests ALL magnetically deflected picture tubes from 7 inch to 30 inch types.
- Tests for quality by the well established emission method. All readings on "Good-Bad" scale.
- Tests for inter-element shorts and leakages up to 5 megohms.
- Tests for open elements.

Model TV-40 C.R.T. Tube Tester comes absolutely complete—nothing else to buy. Housed in round cornered, molded bakelite case. Only

\$1585
NET

**SHIPPED ON APPROVAL
NO MONEY WITH ORDER — NO C.O.D.**

Try any of the above instruments for 10 days before you buy. If completely satisfied then send down payment and pay balance as indicated on coupon. No Interest or Carrying Charges Added! If not completely satisfied return unit to us, no explanation necessary.

MOSS ELECTRONIC DISTRIBUTING CO., INC.
Dept. D-76, 3849 Tenth Ave., New York 34, N.Y.

Please send me the units checked. I agree to pay down payment within 10 days and to pay the monthly balance as shown. It is understood there will be no carrying, interest or any other charges, provided I send my monthly payments when due. It is further understood that should I fail to make payment when due, the full unpaid balance shall become immediately due and payable.

Model 670-A.....Total Price \$28.40 \$7.40 within 10 days. Balance \$3.50 monthly for 6 months. Model TV-11.....Total Price \$47.50 \$11.50 within 10 days. Balance \$6.00 monthly for 6 months. Model TV-40.....Total Price \$15.85 \$3.95 within 10 days. Balance \$4.00 monthly for 3 months.

Name
Address
City..... Zone..... State.....

The Model
TV-50

GENOMETER

A versatile all-inclusive GENERATOR which provides ALL the outputs for servicing:


A. M. Radio

F. M. Radio

Amplifiers

Black and White TV

Color TV

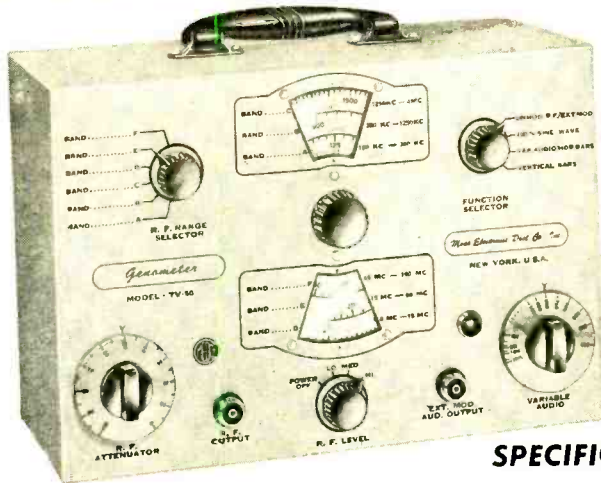

7 Signal Generators in One!

- ✓ R. F. Signal Generator for A.M.
- ✓ R. F. Signal Generator for F.M.
- ✓ Audio Frequency Generator
- ✓ Bar Generator
- ✓ Cross Hatch Generator
- ✓ Color Dot Pattern Generator
- ✓ Marker Generator

SPECIFICATIONS:

R. F. SIGNAL GENERATOR:

The Model TV-50 Genometer provides *complete* coverage for A.M. and F.M. alignment. Generates Radio Frequencies from 100 Kilocycles to 60 Megacycles on fundamentals and from 60 Megacycles to 180 Megacycles on powerful harmonics. Accuracy and stability are assured by use of permeability trimmed Hi-Q coils. R.F. is available *separately*, modulated by the fixed 400 cycle sine-wave audio or modulated by the variable 300 cycle to 20,000 cycle variable audio. Provision has also been made for injection of any external modulating source.

VARIABLE AUDIO FREQUENCY GENERATOR:

In addition to a fixed 400 cycle sine-wave audio, the Model TV-50 Genometer provides a variable 300 cycle to 20,000 cycle peaked wave audio signal. This service is used for checking distortion in amplifiers, measuring amplifier gain, trouble shooting hearing aids, etc.

BAR GENERATOR:

This feature of the Model TV-50 Genometer will permit you to throw an actual Bar Pattern on any TV Receiver Screen. Pattern will consist of 4 to 16 horizontal bars or 7 to 20 vertical bars. A Bar Generator is acknowledged to provide the quickest and most efficient way of adjusting TV linearity controls. The Model TV-50 employs a recently improved Bar Generator circuit which assures stable never-shifting vertical and horizontal bars.

CROSS HATCH GENERATOR:

The Model TV-50 Genometer will project a cross-hatch pattern on any TV picture tube. The pattern will consist of non-shifting, horizontal and vertical lines *interlaced* to provide a stable cross-hatch effect. This service is used primarily for correct ion trap positioning and for adjustment of linearity.

DOT PATTERN GENERATOR (For Color TV)

Although you will be able to use most of your regular standard equipment for servicing Color TV, the one addition which is a "must" is a Dot Pattern Generator. The Dot Pattern projected on any color TV Receiver tube by the Model TV-50 will enable you to adjust for *proper color convergence*. When all controls and circuits are in proper alignment, the resulting pattern will consist of a sharp white dot pattern on a black background. One or more circuit or control deviations will result in a dot pattern out of convergence, with the blue, red and green dots in overlapping dot patterns.

MARKER GENERATOR:

The Model TV-50 includes *all* the most frequently needed marker points. Because of the ever-changing and ever-increasing number of such points required, we decided against using crystal holders. We instead adjust each marker point against precise laboratory standards. The following markers are provided: 189 Kc., 262.5 Kc., 456 Kc., 600 Kc., 1000 Kc., 1400 Kc., 1600 Kc., 2000 Kc., 2500 Kc., 3579 Kc., 4.5 Mc., 5 Mc., 10.7 Mc. (3579 Kc. is the color burst frequency.)

The Model TV-50 comes absolutely complete with shielded leads and operating instructions. Only

\$47⁵⁰
NET

SHIPPED ON APPROVAL

NO MONEY WITH ORDER — NO C. O. D.

Try it for 10 days before you buy. If completely satisfied *then* send \$11.50 and pay balance at rate of \$6.00 per month for 6 months. No Interest or Carrying Charges Added! If not completely satisfied return unit to us, no explanation necessary.

MOSS ELECTRONIC DISTRIBUTING CO., INC.
Dept. D-76, 3849 Tenth Ave., New York 34, N. Y.

Please rush one Model TV-50. I agree to pay \$11.50 within 10 days and to pay \$6.00 per month thereafter. It is understood there will be no carrying, interest or any other charges, provided I send my monthly payments when due. It is further understood that should I fail to make payment when due, the full unpaid balance shall become immediately due and payable.

Name

Address

City

Zone


State

NEW

AGAIN, FIRST
WITH THE
LATEST!

What's a
reputation worth?

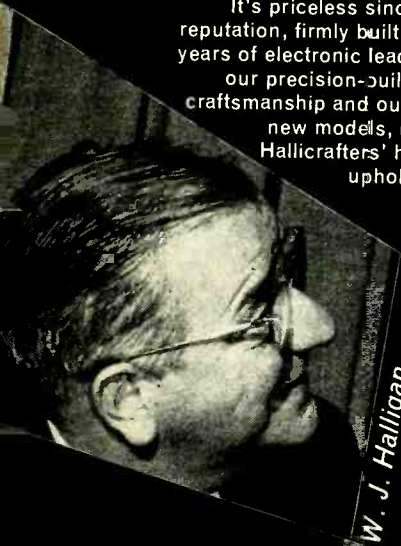It's priceless since Hallicrafters' reputation, firmly built on over twenty years of electronic leadership reflects our precision-built products, our craftsmanship and our future. These new models, in keeping with Hallicrafters' high standards, uphold this tradition of quality.



W. J. Halligan

Low cost unit with high priced performance over Broadcast Band 540-1650 kc plus three short-wave bands from 1650 kc-32 Mc. Electrical band-spread operates over large easy-to-read dial. Headphone tip jacks on rear and powerful built-in PM speaker. Oscillator for reception of code signals. Four tubes plus rectifier. 105/125 V. 50/60 cycle AC/DC \$49.95



Bill Halligan, Jr.



Model S-38D

These two new Civic Patrol receivers are over 10 times as sensitive as previous models, greater increased audio power output and built-in relay squelch system. Perfect for monitoring, police, fire, taxicab, telephone-mobile, forestry, Civil Defense. The S-94 covers 30-50 Mc and the S-95 150-173 Mc. Built-in speaker and provisions for headphones. Eight tubes plus rectifier. 105/125 V. 50/60 cycle AC/DC \$59.95

Write for complete specifications.



Model S-94 (S-95)

hallicrafters

CHICAGO 24, ILLINOIS

NEW PATENTS

(Continued)


Note that the line in series with C2 carries a pulsating voltage. For example, when E is positive, the total is 3E volts. When it is negative, the resultant is only E volts. The a.c. component would charge and discharge C5 at line frequency, if it were not for L1. Similarly, L2 blocks a.c. from passing through C6.

ELECTRONIC STOP-WATCH

Patent No. 2,673,956

Joseph G. Beard, Haddonfield, N.J.
(Assigned to Radio Corp. of America)

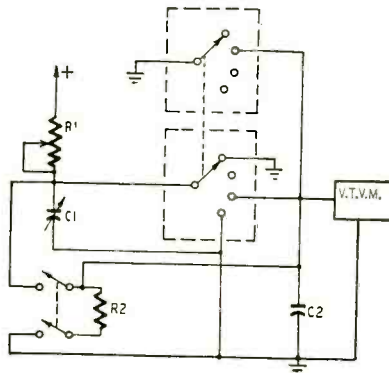This timer can measure successive intervals without error. A mechanical stop-watch cannot be used in this way because it must be reset to zero each time. In this circuit the time indication is stored while the next interval is being measured.




In the position shown in the diagram, C1 is shorted out by the switch. To begin the timing, the switch is moved to its next position, discharging C2, a storage capacitor, while C1 begins to charge through R1 from a d.c. source. At the end of the period the switch is moved another step. This puts C1 across C2 so that part of the charge on the first capacitor is transferred to the second. The voltage across C2 is measured on a v.t.v.m. The indication remains on the meter for a long time because there is no leakage path.

In practice, the ganged switch should remain on the third contact for a very-short predetermined time before moving to the fourth. For quick readings, the v.t.v.m. may be calibrated in terms of seconds, although it actually measures the charge accumulated in a given time.


R2 is a calibrating resistor. When switched across C2 it forms a voltage divider which delivers a known voltage across the v.t.v.m. Thus the voltmeter may be adjusted to its proper setting, for example, full scale.

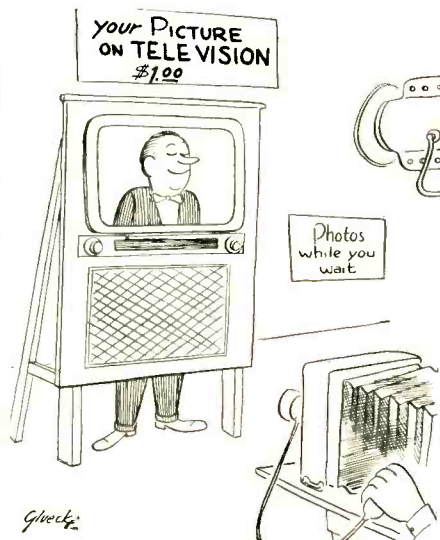This electronic stop-watch may find a great deal of use in industrial applications such as time study involving stop-and-go manufacturing processes. END



SH!

LIKE
NEW!

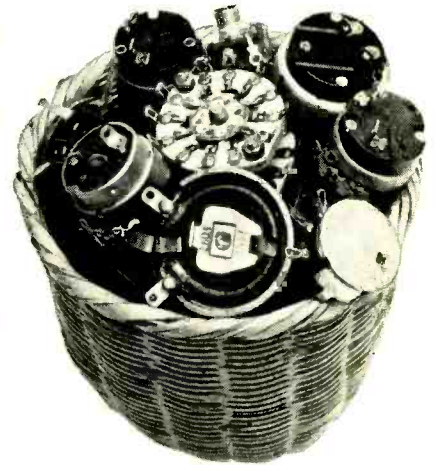

QUIETROLE

Reg. U. S. Pat. Off.

The ORIGINAL
NON-INFLAMMABLE
NON-CONDUCTIVE
LUBRICANT CLEANER

CONTROLS & SWITCHES like new by the BASKETFUL for only a few PENNIES . . . that's what QUIETROLE can do for you, and only QUIETROLE will give that long lasting smooth, quiet operation . . . even



new controls last longer and operate quieter when treated with QUIETROLE . . . the original and most reliable product of its kind.

THE CHOICE OF
BETTER SERVICEMEN
"EVERYWHERE!"

Supplied in 2; 4; and 8 oz. sizes. Ask for it at your distributor.



manufactured by

QUIETROLE COMPANY

Spartanburg, South Carolina

INTERNATIONAL RECTIFIER CORP.

Brings You A Chance to Win A
FREE FORD V-8
Plus 49 Other Big Prizes
• • • • •
Selenium Diode

Application Contest

INTERNATIONAL RECTIFIER CORPORATION'S Selenium Diode Application Contest is open to you. Here is a chance to cash in on your ability and ingenuity.

Just illustrate and explain a new application for International Rectifier Corporation's SELENIUM DIODES.

Pick up an official entry blank from your Parts Distributor. He has one or will be glad to get one for you. Have the entry blank countersigned by your Distributor's Salesman and send it to us before January 1, 1955. The entry blank will give you all the rules and information.

Our Judges

DR. LEE de FOREST
United Engineering Labs, L. A.
J. T. CATALDO
Int'l. Rectifier Corp, El Segundo
F. W. PARRISH
Int'l. Rectifier Corp, El Segundo

For Entry Blanks

See Your

PARTS DISTRIBUTOR

Your Ability and "Know-How"
Can Win A

FREE FORD FOR YOU!

**GET YOUR ENTRY BLANK
TODAY!**

**CONTEST ENDS
JANUARY 1, 1955**

INTERNATIONAL RECTIFIER



E. SEGUNDO


CALIFORNIA

radio-electronic Circuits



CONTINUITY CHECKER

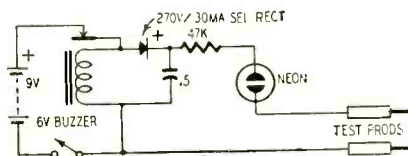Simple and inexpensive continuity checkers have been made from time immemorial by connecting a small pilot lamp or flashlight bulb and a low-voltage battery in series with a pair of test prods. These devices, suitable for locating shorts and tracing continuity when circuit resistance is low, are not usable when the circuit resistance drops the voltage to the point where the indicator



lamp will not light.

In *The Radio Constructor* (London, England), G. A. French describes a combination continuity and capacitor tester that operates from a 6-9-volt dry battery and checks leakage and continuity up to about 10 megohms. High voltage for the neon-lamp indicator is obtained from a vibrator-type supply using a standard 6-volt buzzer as shown in the diagram.

When the circuit is broken by the vibrator, the quick collapse of the magnetic field induces in the coil a voltage many times higher than the battery voltage. This voltage is rectified and filtered and then applied to the neon tester. The brightness of the glow in the tube is determined by the resistance between the test prods.

Paper and mica capacitors can be tested for leakage, opens, and shorts by observing the action of the neon lamp. A good capacitor with very high leakage causes the lamp to flash once when the prods are touched to it. Fairly high leakage resistance causes the lamp to flash continuously at a low rate. Compare the flash rate of the capacitor under test with a good capacitor of the same value to determine its quality. Leakage high enough to make the capacitor unusable is indicated when the indicator glows faintly but does not flash. A shorted capacitor causes a bright continuous glow.

A selenium rectifier rated at approximately 270 volts r.m.s. at about 30 ma is recommended for this application. Rectifiers of this type are made by several firms but may not be readily available at radio supply houses. You can substitute two standard 130-volt rectifiers connected in series. The neon lamp

HICKOK

LABORATORY SIZE VACUUM TUBE Volt Ohm Milliammeter



MODEL
209A

- ★ Large 9" Meter Scale
- ★ Zero-Center DC Scale
- ★ Polarity Reversing Switch

RANGES

Volts, AC-DC and mils DC: 0-1200 in 6 ranges.

Volts, AC, Peak-to-Peak: 0-300 in 5 ranges.

Resistance: 0.1 ohm to 10,000 meg. in 8 ranges.

Capacity: 1 mmf to 1000 mf in 7 ranges.

Current, DC: 5 microamps to 1200 milliamps.

Input Impedance: AC, 3 meg. on 1200 VAC scale. 1200 meg. (shunted by 6 mmf). DC, 12 megohms.

Inductance: 50 mh to 100 henries.

Frequency: 30 cps to 300 megacycles.

Decibels: -20 to +25, in 3 ranges.

13 1/4" H. x 16 1/4" W. x 7" D. 18 1/2 lbs. net wgt.

The versatile Model 209A is a laboratory instrument of highest quality, accuracy and dependability. Ideal for the radio-television manufacturer or service engineer. Designed to meet the large number of applications in the electronic or industrial laboratory. Provides the sensitivity and range for quick and accurate measurements of sine or complex waves of TV or industrial devices. Write today for complete information, or see your nearest HICKOK jobber.

THE HICKOK ELECTRICAL INSTRUMENT CO.
10531 Dupont Ave. • Cleveland 8, O.

BALLOT

Hallicrafters

ON THE LATEST BALLOT:

119 Geophysical laboratories

41 Automotive field experimentation groups

4 Nuclear laboratories

73 Chemical research installations

208 Electronic research laboratories

382 Colleges and universities (various departments cooperating with industry)

72 Meteorological groups

Use Hallicrafters communications equipment in testing, research and in the field. Are you familiar with the complete line of Hallicrafters communications equipment for use in industry?

hallicrafters

4401 West 5th Avenue
Chicago 24, Illinois

Please send full information on Hallicrafters line.

Name _____

Title _____

Company name _____

Address _____

RADIO-ELECTRONIC CIRCUITS



(Continued)

should strike at about 80 volts d.c. Try an NE-2 or NE-7.

A miniature battery and buzzer will enable you to tuck this instrument into a pocket-size cigarette case.

BLOCKING OSCILLATOR

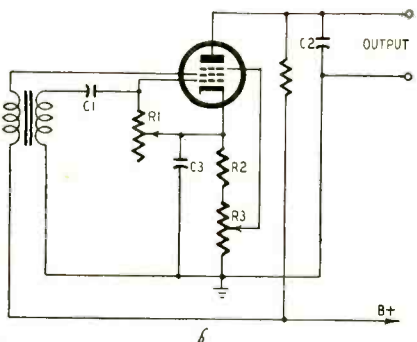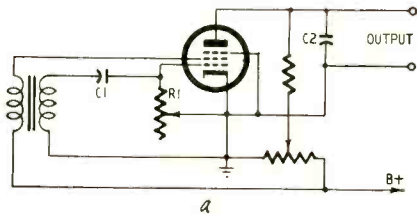When a pentode tube is used as a blocking oscillator as at *a* in the illustration, the transformer is usually connected so oscillation occurs between the control grid and the screen grid while the plate controls the action of discharge capacitor C2. In these circuits, the amplitude of the output wave-



form is usually controlled by varying the plate-supply voltage with a potentiometer. The frequency of oscillation is controlled by the time constant of R1-C1 (the setting of R1). When the suppressor grid is at or near ground potential, the amplitude of the output signal varies with the setting of R1.

The diagram at *b* shows a circuit modification that makes amplitude independent of frequency. In this circuit, described in *Electronic Engineering* (London, England), the amplitude is controlled by varying a bias voltage on the suppressor grid. The bias is developed across R2 and R3. R2 prevents the suppressor from being brought too close to zero bias.



BE Sure with **CORNISH**

Wires

Identified with QUALITY since the swaddling days of Radio. The era of Television finds them, more than ever, the Serviceman's Friend.

- TV LEAD-IN CABLES
- ANTENNA CONTROL CABLES
- INTERCOMMUNICATION CABLES
- COAXIAL CABLES
- MICROPHONE CABLES
- SHIELDED CABLES
- TEST LEAD WIRES
- HOOK-UP WIRES
- PORTABLE CORDS
- REPLACEMENT CORD SETS

CORNISH WIRE COMPANY, INC.
50 Church Street, New York 7, N. Y.

NEW EICO PROBES*

SCOPE PROBES



SCOPE DEMODULATOR PROBE
KIT \$3.75 WIRED \$5.75

LOW CAPACITY PROBE
KIT \$3.75 WIRED \$5.75

DIRECT PROBE
KIT \$2.75 WIRED \$3.95

SPECIAL . . . All 3 Scope Probes
KIT \$9.95 WIRED \$14.95

VTVM PROBES

VTVM RF PROBES
KIT \$3.75 WIRED \$4.95

PEAK-TO-PEAK PROBES
KIT \$4.95 WIRED \$6.95



Sensational High Voltage Probe

Model HVP-2 . . . ONLY \$4.95

© 54 Extends range of VTVMs & VOMs to 30 KV *pat. pend.

EICO


Write for FREE Catalog CP-11

ELECTRONIC INSTRUMENT CO., INC.
84 Withers Street • Brooklyn 11, N. Y.

(Continued)

MOBILE PLAYER

Here is a neat little mobile record player that can be used for picnics and for advertising purposes where a microphone is not required. A spring-wound

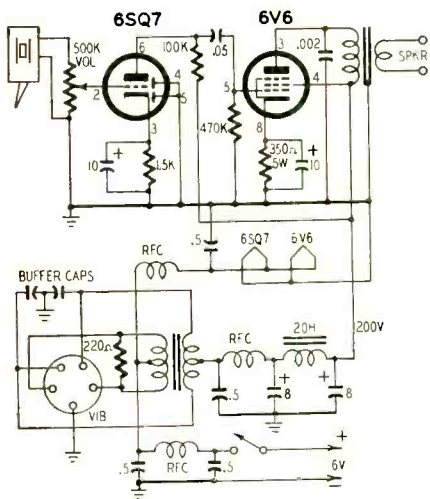


or 6-volt turntable is used. The power transformer and synchronous vibrator may be salvaged from an old auto radio.

The chokes in the 6-volt circuit consist of 30 turns of No. 18 wire on a 1/2-inch form. Wind two layers on the form—30 turns for each choke. The choke in the B plus lead is a winding from a 455-ke i.f. transformer. These chokes, plus adequate shielding, will minimize vibrator hash and hum.

The system works best with a horn-type speaker.—*Carl Hennig*

V.T.V.M. FOR ANTENNA TUNING

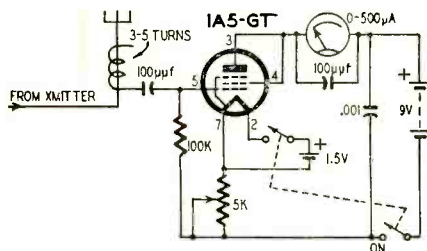Long-wire antennas and low-powered transmitters are generally used during field-day contests and emergency radio drills. Under these circumstances, it is often difficult to tune the transmitter and match it properly to the antenna. Pilot lamps and r.f. ammeters in the antenna lead often require more current for a usable indication than there is in the lead at the point of insertion.



The solution to this problem is to use a simple battery-operated v.t.v.m. like that described by John Pickard in *Radio Constructor* (London, England).

The unit consists of a triode-connected 1A5-GT with a meter in its plate circuit as shown. The grid is coupled to the antenna lead-in with 3 to 5 turns of insulated wire. The 5,000-ohm bias resistor is adjusted for a deflection of 50-100 µa, then the transmitter is keyed and its tuning controls adjusted for maximum deflection on the meter.

"The jack of all trades is master of none . . ."

That's why

QUAM

Adjust-a-Cone

REPLACEMENT SPEAKERS

are **EXACT REPLACEMENTS**

Each one is designed to do a specific job—and to do it as well—or better—than the original speaker.

QUAM speakers are built for quality—not compromise. They are exact replacements—every one of them—with the right magnet, the right power handling capacity, and the right size to do the job you—and your customers—want them to do.

FREE The QUAM catalog listing over 100 exact replacement speakers.

ask for QUAM the quality line for all your speaker needs

QUAM-NICHOLS COMPANY

236 East Marquette Road • Chicago 37, Illinois

When answering advertisements please mention
RADIO-ELECTRONICS

TV GLO-TEST

Replaces \$279 in TESTING EQUIPMENT

This sensational new all-purpose tester does the work of equipment costing nearly 12½ times as much. Recently featured in RADIO-ELECTRONICS and other publications, the GLO-TEST has been bought and used enthusiastically by hundreds of TV and Radio Servicemen, Sound Technicians, Amateurs, Experimenters and Electricians.

More than 50 uses: Pixtube Tester—AC-DC; Measures Voltage to 50 KV; Signal Generator; Signal Tracer; Tube Tester; Resistor and Capacitor Measurements; Checks Distortion, Linearity. Accuracy is comparable to VTVM. GLO-TEST complete with test leads and instruction booklet, postpaid only \$14.50

Send check or money order. Satisfaction guaranteed. Free literature on request. Dealer Inquiries Invited.



V. A. ENTERPRISES, Dept. AA, 608 E. Rosecrans Blvd., Compton, Calif.

FULLY GUARANTEED

*W9WJV beats
last year's
Field Day record
with hallicrafters*




Lawrence T. Fadner, team captain in Chicago's 1954 North Suburban Ham Club ARRL 40 meter CW Field Day bettered the club's last year record by nearly 30%.



and Hallicrafters SX88 is hot news too. More hams are telling each other about this new receiver than about any equipment in years.

*Used by 33 governments,
sold in 89 countries*

hallicrafters
CHICAGO 24, ILLINOIS

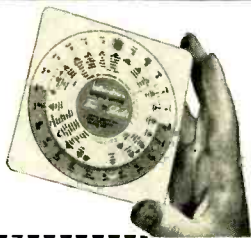

MAIL THIS COUPON

FREE—Send me World-wide Time Conversion Dial Calculator and all band frequency allocation chart plus a fund of other handy data.

Name _____

Address _____

City _____ State _____

Ham (call letters _____) Listener

Occupation _____

Hallicrafter equipment I would like to know about:




EMERGENCY CAPACITOR

While visiting a friend I was asked to see if I could repair a small portable radio so we could use it on a fishing trip. I found an open coupling capacitor between the arm of the volume control and the grid of the first a.f. stage. A replacement capacitor was not available so I made a coupling gimmick by winding about 3 feet of hookup wire tightly around the lead to the arm of the volume control and connecting the other end to the grid of the tube. The gimmick provided sufficient coupling to restore the volume to a level high enough for use on the trip.—*Bill Kelly*

(When the defective coupling capacitor is from a diode detector it can be bridged to make a temporary repair of the simpler circuits. Do not bridge the capacitor when fixed bias is used on the following grid.—*Editor*)

T-3 SIGNAL TRACER

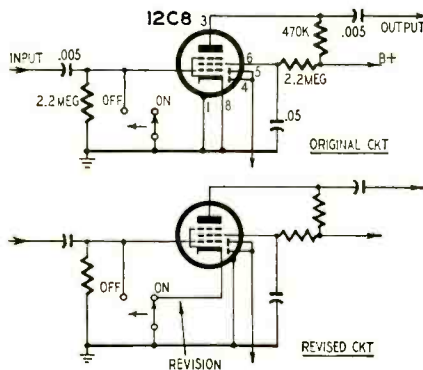Hum was objectionable when using my Heathkit T-3 signal tracer to trace audio circuits. Various methods of hum elimination were tried without success. In this kit the pentode section of a 12C8 amplifies the output of the r.f. probe. When the tracer was used for audio work, a switch was closed to short the grid to ground. Hum disappeared when this tube was removed from the circuit.



The HIGH GAIN switch in my particular kit has an extra lug which connects to ground in the ON position and is removed from ground in the OFF position. By connecting the cathode to this lug as shown in the revised schematic, I was able to eliminate the hum. The metal envelope of the tube (pin 1) must remain connected to ground, as this reduces the possibility of the tube

GREAT SAVINGS | Fall Specials

TV PICTURE TUBES ONE YEAR GUARANTEE

10BP4 .. \$10.95	17BP4 .. \$16.95
12LP4 .. 11.95	17CP4 .. 17.95
12LP4A .. 12.95	17GP4 .. 18.95
12QP4 .. 12.95	17HP4 .. 18.95
12JP4 .. 12.95	19AP4 .. 19.95
14BP4 .. 13.95	19BP4 .. 18.95
16RP4 .. 15.95	19DP4 .. 18.95
16AP4 .. 16.95	20CP4 .. 19.95
16CP4 .. 16.95	21AP4 .. 22.95
16GP4 .. 16.95	21EP4 .. 21.95
16DP4 .. 15.95	21FP4 .. 22.95

All Prices With Old Tube
Add \$5.00 deposit to tube price. Deposit is fully returned upon receipt of your old tube.

630-DX TECH-MASTER CHASSIS, \$145.50 with Cascode Tuner..... now

UHF CONVERTER Mfd. by Tech-Master for 630-DX or any 630 Chassis. (Fits into well of chassis) \$32.50

TV Wire, 300 ohm, 55 mil... 100 ft. \$1.00

DEFLECTION YOKES
60° Yokes... 69c ea.
70° Yokes... \$1.95 ea.
New CASCODE Tuners Complete, \$14.95 factory aligned ea.

FP CONDENSERS with 20/150V., 3-20/20V. 25c ea.
Metal Plates, 4-Sections 20/150V., 150/150V., 100/150V., 100/30V. 39c ea.
10 for \$1.95 ea. 10 for \$3.49 ea.

Special! VARIABLE CONDENSERS
2 gang super het 29c ea.
3 gang AM/FM 89c ea.
2 gang mini. type 89c ea.
Small single gang 98c ea.

CONTROLS
2 meg. IRC..... 39c ea.
Sw. for above. 9c ea.
25K, Type J, AB... 6/89c
180K Type J, AB... 6/89c
CRYSTAL MIKES
Removed from new equipment, 69c ea. hearing aid type
All perfect! 3 for \$1.89
Miniature Chokes 29c ea. 3 leads, 3K ohms hearing aid type, 4 for \$1.

WRITE FOR FREE NEW CIRCULAR. Terms: 25% dep. with order, bal. C.O.D. F.O.B. New York City. Prices subject to change without notice.

ROSE ELECTRONICS, Inc.
76 Vesey St., New York 7, N.Y. | CO. 7-6195

RADIO-TV SERVICE IS TWICE AS EASY



when you really know circuits!

Learn circuits fully... and watch service "head-aches" disappear! Locate troubles quicker, with less testing. Repair them faster, better, more profitably.

Radio & TV CIRCUITRY AND OPERATION
Chirardi & Johnson
669 pages
Price \$6.50

Teaches you how to recognize them fast... how they work... how to know what to look for... how to avoid guesswork and useless testing. Easy to understand. Fully indexed so you can find what you want in a jiffy. Throughout, this big book brings you the above-average training that paves the way for topnotch, good-pay jobs.

MAIL NOW FOR FREE TRIAL

Dept. RE-114, RINEHART & CO., INC.
232 Madison Ave., New York 16, N. Y.

Send Radio & TV Receiver Circuitry and Operation for 10 day free examination. I will then either return book to you promptly or send \$6.50 (plus postage) in full payment.

Name _____

Address _____

City, Zone, State _____

OUTSIDE U.S.A.—Price \$7.25, cash only.
Money back if book is returned in 10 days.

AMERICA'S MOST DEPENDABLE ROTATOR

THE TRIO "ARISTOCRAT"



NOW...

*America's
most
beautiful!*

The sleek, modern, low silhouette of the new TRIO rotator control case marks a new high in styling.

Beauty, here, is more than skin deep since its low center of gravity makes it tip-proof! Note, too, that there are NO unsightly control knobs or switches to spoil its beauty. These are located at top rear of case — where your hand naturally rests in operation of rotator!

There is no obscuring the easily-read lighted dial. Available in either blonde or mahogany, the unit with its graceful flowing lines blends perfectly with any decor.

Yes, America's most dependable rotator is now America's most beautiful as well!

Switch and directional controls are located at top rear of case for most convenient manual operation. Lighted dial permits operation in darkened room and also indicates when rotator is on. When on, pointer always shows exact position of antenna.



✓ Only Rotator With Two Motors

✓ Only Rotator With Two-Year Guarantee



THE TRIO
"ARISTOCRAT"

...CULMINATION OF
SIX YEARS RESEARCH
AND PRODUCTION



TRIO


Manufacturing Co.

GRIGGSVILLE, ILLINOIS

Leading a brand new line...

1000°

OF CALIBRATED BANDSPREAD!

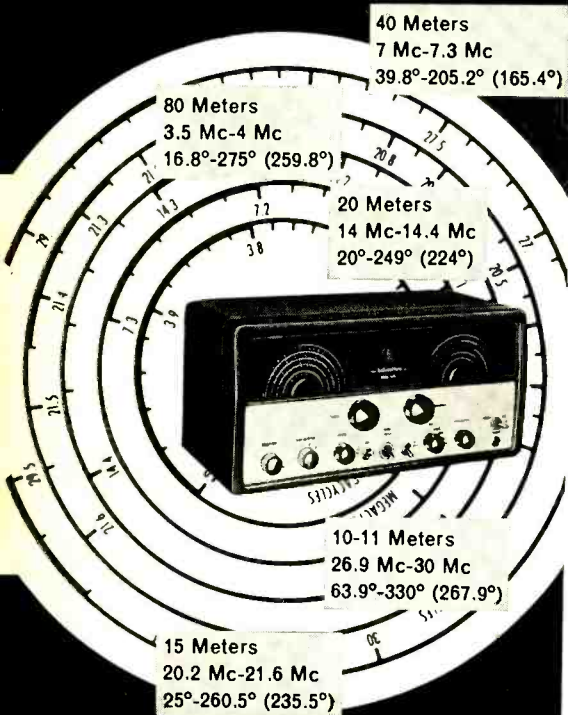

MODEL S85

S-85 Receiver (AC)
S-86 Receiver (AC-DC)
105/125 V. 50/60 cycle
Either \$119.95

We here at Hallicrafters are proud of our new communications line, especially the new S-85 receiver with over 1000° of calibrated bandspread. Broadcast band 540-1680 Kc and three short-wave bands 1680 Kc-34 Mc on large easy to read dial. Separate bandspread tuning condenser and built-in speaker. Seven tubes plus rectifier. Coupon below brings complete specifications.

*Used by 33 governments,
Sold in 89 countries.*

hallicrafters
Chicago 24, Illinois



MAIL THIS COUPON

FREE World-wide time converter
Specification sheet S-85(S-86)
 S-95(S-94) S-38D
Name _____
Address _____
City _____ Zone _____ State _____
 Ham (call letters _____) Listener
Occupation _____

TRY THIS ONE (Continued)
picking up stray noises while the cathode circuit is open.

On some kits a replacement switch may have to be used, but this should not be difficult to locate in the inevitable box of spare parts around any shop. The improved performance will more than justify the small amount of time and effort expended.—Francis J. Stifter

CALIBRATING A V.T.V.M.

After assembling my v.t.v.m. kit I found that I could not expect better than 5% accuracy on the a.c. range because of possible variations in the line voltage applied to the transformer used to deliver calibration voltages. To combat this, I made an octal plug and obtained my test voltages from a tube tester with the line voltage control adjusted to set the meter to the calibrate point. The d.c. scale was calibrated with two new dry cells connected in series to read 3.1 volts on the 5-volt scale.

This idea is also useful for recalibrating the v.t.v.m. after replacing critical tubes.—E. F. Sharp

IMPROVED MIKE STAND

Often when the microphone is removed from an adjustable stand, the inner tube slides down and damages the connector or slips all the way down into the outer tube. Drill a 1/16-inch diameter hole about 2 inches below the threaded part of the inner tube and screw in a No. 6 self-tapping screw. The screw is small enough to be inconspicuous and large enough to prevent the inner tube from sliding down too far.—Hart Webber

NUTS IN SMALL CHASSIS

Do you have trouble starting small nuts in crowded or inaccessible parts of a chassis? If so, try this method: Put a drop of service cement on the tip of your forefinger and let it set a few seconds, then place the nut in it. The cement holds the nut securely enough for you to start it on the screw.—H. C. Harris

HANDY WIRE STRIPPER

A large alligator clip makes an efficient and economical wire stripper for plastic-covered wire. Fasten the clip to your workbench with one jaw flat against the top and the stripper is ready for use. Open the jaws and feed the wire into the "snout." Allow the jaws to close; if the spring is not strong enough, press down on upper jaw with finger. Pull wire straight out, and insulation will be stripped off.—Clarence C. Lewis

"REALIGNMENT SOLVENT"

To keep i.f. transformers from detuning many manufacturers seal the slug with glyptal or some type of cement. When realignment is necessary, a few drops of solvent must be used to loosen the glyptal. I have found that lacquer thinner or amyl acetate (banana oil) does the job nicely.—J. Kane

END

**STAN-BURN
ELECTRONICS**

*** CATHODE RAY TUBE SPECIALS ***
ONE YEAR GUARANTEE

G.E.		STAN-BURN	
10BP4A	\$14.95	10BP4	\$10.20
12KP4A	21.10	12LP4	11.90
12LP4A	24.45	12MP4	13.95
12QP4A	18.75	12OP4	11.90
Dumont B1014	21.00	12PP4	11.90
12UP4B	28.75	14CP4	15.60
15DP4	24.50	15DP4	17.50
Dumont	23.75	16CP4 or A	17.50
16AP4A	30.95	16JP4 or A	17.50
16BP4A (N.U.)	25.25	16OP4 or A	17.50
16GP4 or B	31.25	16FP4	17.50
16KP4, 16RP4	24.20	16WP4	17.50
(Aluminum)	28.35	16AP4	17.50
16JP4A (N.U.)	25.25	16FP4A	23.00
16LP4A	28.50	16EP4	19.00
16WP4A	26.50	16CP4A	23.50
16GP4B	31.25	16GP4 or A	21.00
17BP4B	24.25	17BP4	25.50
17CP4B	30.30	17CP4A	24.50
17CP4	34.00	17CP4B	22.60
(Aluminum)	38.50	19FP4	23.00
19AP4A	41.50	19AP4	24.00
20CP4	30.00	19AP4A	23.90
20LP4	37.50	19AP4A	24.90
21AP4	42.00	20CP4	23.95
21EP4A	32.80	21EP4A	25.50
21EP4A	37.35	21AP4	26.50
24AP4	78.50	24AP4	49.00

QUANTITY CRT USERS

We will give you DUD allowances if you ship them to us Prepaid. 10 CRT's minimum shipment. WRITE FOR DETAILS.

AUTHORIZED DISTRIBUTORS for: General Electric, Kenrad, Tung-Sol, National Union, De Wald, Regal, Automatic and General Motors.

AUTOMATIC CUSTOM-BUILT RADIOS for Plymouth, Ford, Chevrolet and many others, always in stock. We carry a complete stock of **QUALITY and SOUND EQUIPMENT.** Send us your requests. We also carry a complete line of popular makes of Radio tubes at 50-100% discount. Also many other special purpose and transmitting types, and all electronic parts and equipment at lowest prices. Send us a list of your requirements for prompt quotations. Terms: 20% with order. Balance C.O.D. All prices FOB. NEW YORK Warehouse. Minimum order \$5.00. Write for our latest price list and Hi-Fi Catalog to Dept. RE-11.

STAN-BURN RADIO and ELECTRONICS CO.
1497 BROADWAY • NEW YORK 19, N.Y.

OSCIL-O-PEN

Extremely convenient test oscillator for all radio servicing; alignment • Small as a pen • Self-powered • Range from 700 cycles audio to over 600 megacycles u.h.f. • Output from zero to 125 v. • Low in cost • Used by Signal Corps. • Write for information.

GENERAL TEST EQUIPMENT
38 Argyle Ave. Buffalo 9, N. Y.

Just Out! PRACTICAL REFERENCE BOOK ON TRANSISTORS

Every Radio-TV Serviceman and Technician Needs It! Includes complete "how-to-do-it" wiring data on the use of Transistors in TV, Radio, Photo Cell Relays, Hearing Aids, Amplifiers, Oscillators. You learn how to install, test and service transistorized equipment. Contains the latest, practical information about this revolutionary new electronic development!



SEND NO MONEY! Just mail coupon. On delivery pay postman introductory price of just \$1.50 plus C.O.D. fee and postage. Or save postage by sending \$1.50 with coupon now. Sold on 7-day money-back guarantee. Be first with the latest "know-how". Order your Transistor book TODAY!

RUSH THIS INTRODUCTORY OFFER COUPON


COYNE ELECTRICAL SCHOOL
500 S. Paulina St., Dept. B4-T2, Chicago 12, Ill.
YES! Rush your new book: "TRANSISTORS & THEIR APPLICATIONS", at \$1.50 plus C.O.D. and postage, on 7-day trial.
Name _____
Address _____
City _____ State _____
 Check here if you are enclosing \$1.50. We pay postage. 7-Day Money Back Guarantee.

new Devices



DECADE V.T.V.M.

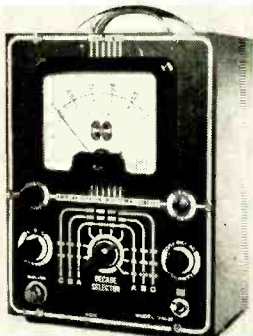American Scientific Development Co., 334-336 So. Main St., Fort Atkinson, Wis., is producing its new model VM-30 *Deca-Meter*, a v.t.v.m. with 30 cascaded ranges in 10-volt steps to 100 volts, 50-volt steps to 500 volts, and 100-volt steps to 1,000 volts. Assuming that the range selector is set for 10-volt steps and




the decade switch is set to 90 volts, an input of 90 volts will read zero on the meter. Voltages between 90 and 100 are spread across the scale. The voltage indicated on the meter must be added to the voltage setting of the decade selector to get the true value of voltage.

The instrument has an 11-megohm input resistance, a polarity reversal switch, and a full-wave 6AL5 rectifier for r.m.s. measurements. The circuits are voltage-regulated to minimize drift and the effects of line-voltage fluctuations.

SWEEP GENERATOR

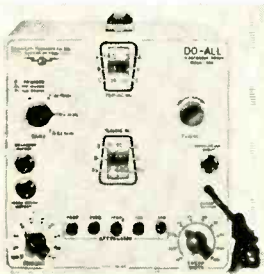Radio City Products Co., Inc., Easton, Pa., has introduced a new all-electronic sweep generator which is designed for both color and black-and-white television. The unit, model 780, can also be used in servicing FM, AM, and communications equipment. Its range is from 3.2 to 900 mc.



TUBE CHECKER

Television Engineers, Inc., 311 E. 79th St., Chicago 19, Ill., has introduced a *Vis-U-All* tube checker designed for testing over



300 television and radio tubes, including battery tubes. It weighs 10 pounds, measures 15 x 12 x 6 inches, and is built into a brown leatherette carrying case. In addition to checking the individual sections of multisectional tubes, the checker tests separately for grid-to-cathode and heater-to-cathode shorts, as well as providing a gassy short test.

NEW V.T.V.M.

Electronic Instrument Co., Inc., 84 Withers St., Brooklyn 11, N. Y., has announced a new peak-to-peak vacuum-tube voltmeter, model 249, with a 7½-inch meter. It is available in both kit and wired form.

The instrument reads peak-to-peak voltage of complex and sine waves, d.c. voltage, and resist-




ance. It provides for center-scale zero adjustment for TV and FM alignment and for calibration from outside the cabinet.

The d.c. voltmeter ranges are: 0-1.5, 5, 15, 50, 150, 1,500 volts. The a.c. voltmeter ranges are r.m.s. values and are the same as the peak-to-peak readings of sine and complex waves are: 0-4, 14, 42, 140, 420, 1,400, 4,200 volts. There is a separate scale for 0-1.5 volts r.m.s. and corresponding 0-4-volt peak-to-peak ranges. The frequency response is 30 cycles to 3 mc, and the ohmmeter measures 0 to 1,000 megohms in seven ranges.

OSCILLOSCOPE CALIBRATOR


Service Instruments Co., 422 Dearborn Street, Chicago, Ill., is now manufacturing an oscilloscope calibrator for measuring peak-to-peak voltages. The

Compare... prove EMC superiority

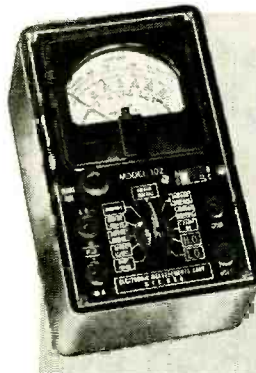

model 102

(1000 ohms per volt meter) • 3" SQUARE METER • 3 AC CURRENT RANGES (0-30/150/600 ma.) • Same zero adjustment for both resistance ranges (0-1000 ohms, 0-1 megohms) • 5 DC & 5 AC Voltage Ranges to 3,000 volts • Also 4 DC Current Ranges **\$14.90**

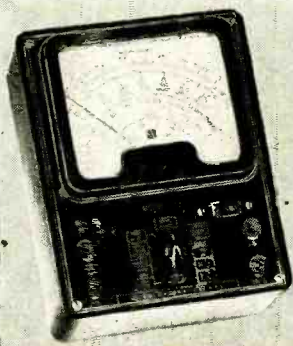

model 103

(1000 ohms per volt meter) • 4½" SQUARE METER • 3 AC CURRENT RANGES (0-30/150/600 ma.) • Same zero adjustment for both resistance ranges (0-1000 ohms, 0-1 megohms) • Same Range: cs Model 102 • Also 5 DB Ranges **\$18.75**
Model 103-S with plastic carrying strap..... **\$19.25**



model 104

(20,000 ohms per volt meter) • 4½" SQUARE METER (50 micro-amperes-Alnico magnet) • Includes carrying strap • 5 DC Voltage Ranges at 20,000 ohms volt to 3,000 V. • 5 AC Voltage Ranges to 3,000 V. • 3 Resistance Ranges to 20 megs • Also 3 AC & DC Current Ranges • 5 DB Ranges **\$26.95**
HVT 30,000 Volt Probe for Model 104 **\$7.95**

EMC

Write Dept. RE-11 for Free Complete Catalogue of these and other Instruments.

ELECTRONIC MEASUREMENTS CORPORATION
280 LAFAYETTE STREET • NEW YORK 12, N. Y.

EXPORT DEPARTMENT 136 LIBERTY STREET, N. Y. 10038, N. Y.

NEW AMPHENOL TWIN-LEAD

Extra-Quality—Extra-Strength



NEW 300 ohm CENTURY line is a superior twin-lead with a full web thickness of 100 mil that provides extra strength for long runs on tv installations.



NEW 300 ohm HEAVY DUTY line is a superior lead-in featuring lower db loss as well as a thick 185 mil web and heavy 7/26 copper conductors. This remarkably tough line will perform equally well as a tv lead-in or as an amateur transmitting line.



Reinstated! 300 ohm AIR-CORE KW Transmitting Twin-Lead is similar in construction to AMPHENOL's patented 14-271 Tubular Twin-Lead and offers the same low-loss features. Rated at 1 KW, this line also makes a very deluxe receiving lead-in for fringe VHF or UHF television areas.



Reinstated! Four Conductor Rotator Cable is ideal for remote control applications. Ribbed polyethylene dielectric makes separation of the four conductors easy—one conductor is tinned for faster identification on the job.

Receiving, transmitting, four conductor rotator cable—the extensive line of AMPHENOL twin-leads includes everything needed for any tv, fm or amateur application! Made only of the best materials, under strict quality control through every phase of manufacture, AMPHENOL twin-leads are guaranteed to be free of defects and will perform with utmost efficiency.

AMERICAN PHENOLIC CORPORATION
chicago 50, illinois
In Canada: AMPHENOL CANADA, LIMITED



Send for your copy of the new AMPHENOL Vest-Pocket Guide to Twin-Leads. Most extensive compilation of twin-lead information ever offered!



NEW DEVICES

(Continued)


system employed is a comparative method by which the line voltage is calibrated and compared in amplitude to the unknown waveform on the scope.



Two mounting bars are provided so that the meter can be permanently connected to the scope. When the meter is turned off, the input is connected "straight through," and the unknown waveform is applied directly to the scope input.

AUTO RADIO TESTERS

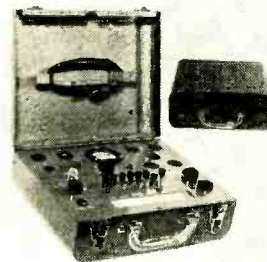D. W. Thomas Engineering, Inc., 1820 W. 54th St., Los Angeles, Calif., has announced a new tube and vibrator tester, model 1402, for automobile radio servicing which operates from either 6 or 12 volts d.c., and a novel battery eliminator, model 1400. Although the two are designed to operate as a single



unit, the tube tester may be used independently. It works directly from the power supply of an automobile through a plug inserted into the cigarette-lighter socket.

The battery eliminator is powered by 115 volts 60 cycles per second and is used for bench testing of all types of automobile radios and contains a variable transformer so that the voltage output is continuously variable from 0 to 15, at 10 amperes.


27-INCH CHASSIS

Transvision, Inc., 460 North Ave., New Rochelle, N. Y., is now marketing a 27-inch chassis with aluminized tube, containing remote-control and dual sound systems. Special alignment procedures insure 4-mc bandwidth, and the keyed a.g.c. circuit minimizes interference from outside noise. An 18,000-volt second-anode supply insures optimum picture brightness.



NEW ANTENNA

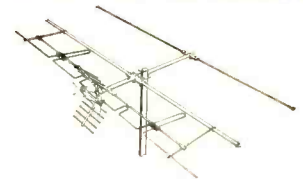
Alliance Manufacturing Co., Lake Park Blvd., Alliance, Ohio, has introduced the *Monolober*



antenna, available in single or double bay. A feature of this unit permits the gain of a v.h.f. antenna to be added to that of a u.h.f. antenna.

ANTENNAS

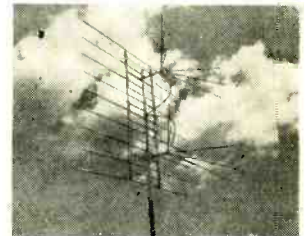
Telrex, Inc., Asbury, N. J., has announced the new *King Pin* Conical-V-Beam single-bay and two-bay screen arrays—models 201 and 202.



The two-bay array was designed for fringe area reception. Its gain is 7½ to 8½ db on the low v.h.f. channels; 15 to 17 db on the upper v.h.f. channels. Through the use of Conical-V-Beam dipoles, a uniform match is obtained to 300-ohm standard or 200-ohm low-loss line over the entire band over which the antenna operates.

AUTOMATIC ROTOR

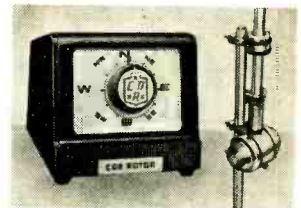Cornell-Dubilier Electric Corp., South Plainfield, N. J., and their subsidiary, Radiart




Corp., 3455 Vega Ave., Cleveland, Ohio, have put out an automatic rotor using 4-wire cable. It is housed in a plastic cabinet. Model AR-2 includes a thrust bearing, and model AR-1 is for ordinary installations without a thrust bearing.

Both of the above models have a mechanical brake that is released magnetically.

ANTENNA ROTATOR

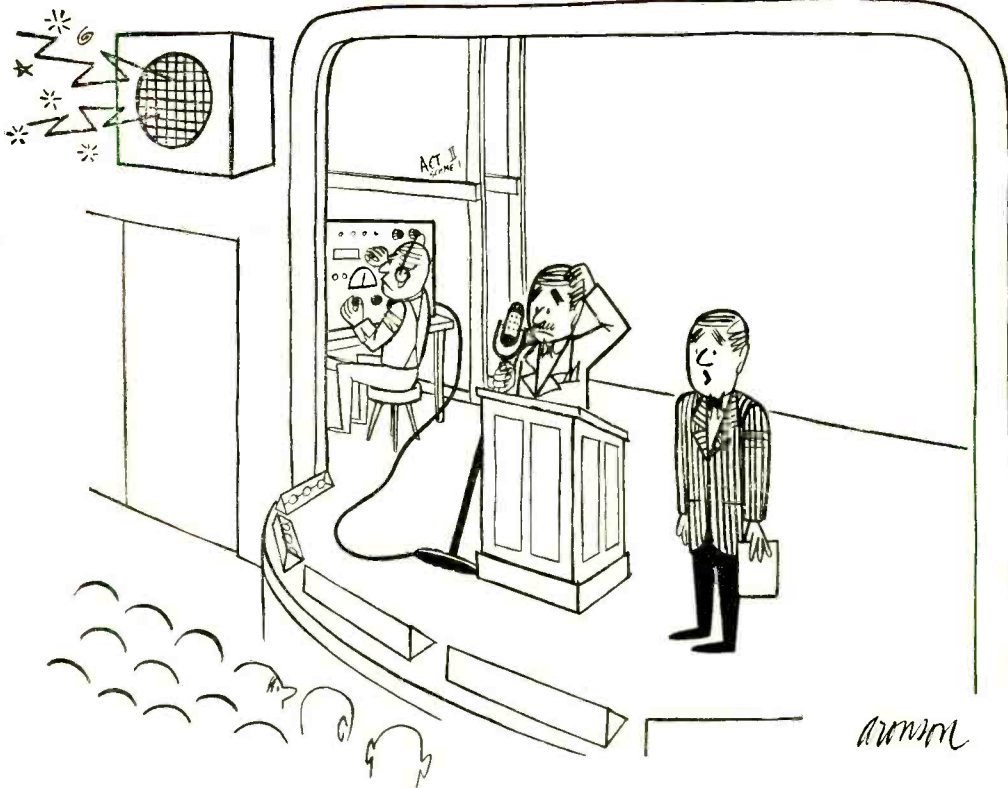
Leader Electronics, Inc., 2927 E. 55th St., Cleveland, Ohio, has announced a new antenna rotator, model 500, with an automatically illuminated dial. The






IS THERE A SPRAGUE CAPACITOR
IN THE HOUSE?

Don't Be Vague... Insist on SPRAGUE

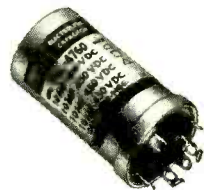


Insist on Sprague
TWIST-LOK[☆] 'LYTICS

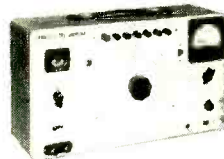Sprague TVL's fill the top performance bill in the toughest TV circuits. High temperatures, surge voltages, ripple currents won't faze them. Like all Sprague capacitors, Twist-Lok 'Lytics are your first line of defense against expensive call-backs.



Insist on Sprague
TEL-OHMIKE[®]

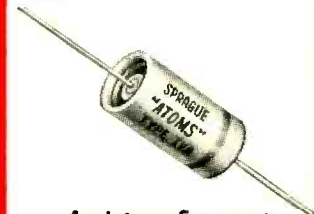This capacitor-resistor analyzer is the handiest instrument you can buy! Moderately priced for radio and TV repair shops, the Model TO-4 Tel-Ohmike offers top quality and accuracy for every service need. Priced so you can afford it at **\$73.50**
NET



Insist on Sprague
ATOMS[®]

The smallest TV 'lytics made—and the only small ones for 85°C (185°F) up to 450 volts d-c. Guaranteed for low leakage and long shelf life, they withstand high temperatures, high ripple currents, high surge voltages. From crowded TV chassis to jam-packed portables, Sprague Atoms fit 'em all.

Accept no substitutes. There is a Sprague Distributor in every sales area in the United States. Write for the name of your nearest source of supply today.

☆ Trademark

SPRAGUE

Get your copy of Sprague's latest radio and TV service catalog C-670. Write Sprague Products Company*, 105 Marshall St., North Adams, Mass.

*Distributors' Division of Sprague Electric Company

**WORLD'S LARGEST
CAPACITOR MANUFACTURER**

A Star Is Born...

Only EICO #232 Peak-to-Peak VTVM has all these Advanced Features ★

**NEW
PEAK-to-PEAK
VTVM
AT LOWEST COST**

With Exclusive
Uni-Probe

★ FOR THE FIRST TIME ALL CALIBRATION IS DONE WITH INSTRUMENT IN CABINET.

★ 7 non-skip ranges on every function — DC/RMS sine volts: 0-1.5, 5, 15, 50, 150, 500, 1500. (To 30 kv with HVP probe.) Res.: 0.2 ohms to 1000 megohms.—Uniform 3 to 1 scale ratio assures extreme wide-range accuracy.

★ Flat freq. response 30 cps to 3 mc.

★ Measures directly peak-to-peak voltage of complex & sine waves: 0-4, 14, 42, 140, 420, 1400, 4200. Vital for TV servicing. Saves the cost of separate Peak-to-Peak Probe.

★ Terrific time and trouble-saver! One probe for all functions—in a "twist of the wrist" it selects DC or AC (Peak-to-Peak & RMS/OHMS)

★ No annoying lead tangle, no back-and-forth prod changing. Positive-action, super-rugged!

★ Modern styling, etched panel; compact, easily portable. Size: 8½" x 5" x 5".

KIT \$29.95
Factory Wired \$49.95

Complete with UNI-PROBE at no extra cost



Excellent for your bench
Model 249 Peak-to-Peak VTVM with Giant 7½" Meter
KIT \$39.95 **Wired \$59.95**
Complete with UNI-PROBE


See this amazing engineering achievement at your jobber today. Write now for FREE latest catalog **CV-11**

EICO

ELECTRONIC INSTRUMENT CO., INC.
84 Withers Street
Brooklyn 11, N. Y.

Prices 5% higher on West Coast. ©54

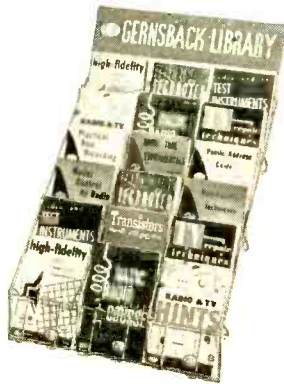It will pay you to get to know the Gernsback Library Books



See these books at your parts distributor or use coupon on page 112.

The Oscilloscope — No. 52. How to use the scope to best advantage in servicing. 192 Pages. \$2.25.

Transistors—Theory and Practice—No. 51. Rufus Turner explains transistors for the benefit of the practical man. \$2.00

TV Repair Techniques—No. 50. The experts tell you how to solve tough servicing problems. \$1.50

Radio & TV Test Instruments—No. 49. Build your own servicing instruments. \$1.50

High-Fidelity — Design, Construction, Measurements. No. 48. New 3-way approach by 21 top hi-fi experts. \$1.50

Radio & TV Hints—No. 47. Over 300 sure-fire hints, gimmicks, and short cuts. \$1.00

Television Technotes — No. 46. How to save trouble-shooting time. \$1.50

Radio Tube Fundamentals—No. 45. Theory for the practical man. \$1.00

Basic Radio Course — No. 44. John T. Frye gives the technician the low-down on theory. Cloth bound \$2.25.

Model Control By Radio —No. 43. Theory and construction for beginner and expert alike. \$1.00

High-Fidelity Techniques —No. 42. James R. Langham's off-beat classic for hi-fi fans. \$1.00

Public-Address Guide—No. 41. Only 75c
Practical Disc Recording—No. 39. Only 75c

Gernsback Publications, Inc. 25 W. Broadway, New York 7, N.Y.,
Publishers of RADIO-ELECTRONICS

face lights when the rotator is in operation and shuts off when the tuning has been completed. A new control box features vernier precision tuning.

The top 6 inches is shaped to fit all rotators.

This aluminum mast is one-third the weight of steel masts, making it easier to handle and install.

NEW TOWER

Rohn Manufacturing Co., 116 Limestone, Bellevue, Peoria, Ill., announces a new No. 6 tower suitable for home TV installation and other communication requirements. This tower is self-supporting to 50 feet in height or guyed to 150 feet. It features a 12½-inch triangular design with heavy-duty corrugated cross bracing which utilizes mass production machinery.

U.H.F. CONVERTER

Fenton Co., 15 Moore St., New York 4, N. Y., is now distributing the new *Fen-tone* model Cl u.h.f. converter for continuous tuning of channels 14 through 83. The unit uses a high-pass filter input circuit, a germanium diode mixer, and a 6AF4 oscillator tuned by silver-



plated parallel lines. The input and output impedances are 300 ohms. The converter is factory-set for 82-mc output on channels 5 and 6 but any vacant channel can be used by shifting the tuning knob the difference between 82 mc and the frequency of the channel selected as the i.f.

The 9 x 5¼ x 5¼-inch metal cabinet is topped by an illuminated 7¼ x 7¼ x 3¼-inch glass brick that can be used as a lamp, plant vase, or illuminated aquarium. Power consumption from 110-125-volt, 60-cycle lines is 5 watts for the converter alone and 7.5 watts for the lamp.

NEW ANTENNA MAST


JFD Manufacturing Co., 6101 16th Ave., Brooklyn, N. Y., has announced a new telescoping television antenna mast, *Alu-zoom*. The top section has an outside diameter of 1½ inches. The wall thickness is .056 inch.



U.H.F. ANTENNA

Technical Appliance Corp., has announced a new u.h.f. antenna, *Super 12*, that comprises 12 open bowtie driven elements plus a large screen reflector. Driven elements are connected in parallel to a common terminal panel, while the individual 4-bay arrays are driven in series-parallel for perfect polarization. The reflector screen is made in one piece folded at the center.

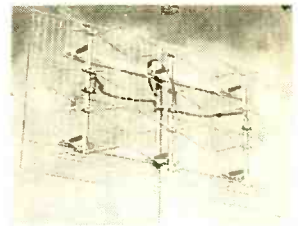The *Super 12* shows a voltage gain of approximately 18 db over the v.h.f. spectrum. Directivity is sharp, varying between 5° to 10°, depending upon frequency of operation. Front-to-back ratio is high.



NEW FLYBACKS

The Stancor Division of the Chicago Standard Transformer Corp., Addison and Elston, Chicago, Ill., has announced the addition of six new flybacks for Muntz, RCA, Airline, and Sentinel—A-8242, A-8243, A-8244, A-8245, A-8246, and A-8247.

NEW AMPLIFIER

Newcomb Audio Products Co., 6824 Lexington Ave., Hollywood 38, Calif., has announced a new *Compact 12* amplifier. It combines a 12-watt amplifier, pre-amplifier, and control unit. Separate bass crossover and treble roll-off controls provide up to 36 basic playback curves.

Distortion in the *Compact 12* is below 1% at 12 watts, and frequency response is within ±1 db from 20 to 20,000 cycles. Seven inputs include radio, microphone, high-output magnetic pickup, low-output magnetic pickup, crystal pickup, tape input and auxiliary or TV. A new tape output jack allows recording while listening. A six-position selector offers the choice of various recording curves.



AUDIO CONTROL CENTER

Brociner Electronics Laboratory, 344 E. 32nd St., New York 36, N.Y., has announced the Mark 30C audio control center. It is a self-powered preamplifier that provides complete facilities for selection of radio, TV, tape, or phonograph inputs, separate turnover and roll-off controls for record compensation; continuously adjustable bass and


treble controls providing boost and cut, and a loudness control. Either of two phonograph inputs may be used. One is provided with a sharp-cutoff, high-pass filter of the feedback type for rumble suppression. An adjustable rear-panel control permits correct termination of any phono pickup. A tape take-off jack is mounted on the rear apron.

Negative feedback circuits reduce IM distortion to less than 0.1% for outputs as high as 4 volts. The output stage is a feedback type and has the low-impedance feature of the conventional cathode follower, but with marked improvement in distortion figures.



JENSEN CABINETS

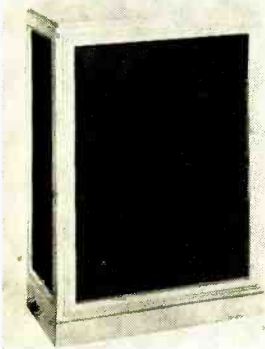Jensen Manufacturing Co., 6601 So. Laramie Ave., Chicago, Ill., is making two back-loading cabinets for 12-inch (model BL-220) and 15-inch (model BL-250) speakers. The cabinets have been designed with an eye to




flexibility in mounting coaxial or triaxial speakers, mid- and high-frequency units and woofers, tweeters or supertweeters in any desired combination without changes to the cabinets.

They may be fitted into a corner or placed against a wall.

These units were erroneously described under incorrect model numbers—one of them of a superseded model—in our September issue.

MICROPHONE

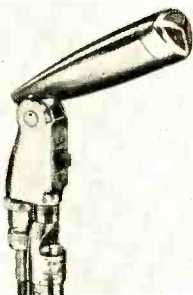Electro-Voice, Inc., Buchanan, Mich., has introduced a new model 623 slim-design general-




purpose dynamic microphone. It can be used indoors and outdoors for public address, home recording, paging, and radio amateur communications.

The 623 can be used on a stand or in the hand. Its frequency response is 60 to 11,000 cycles, and its output level is -55 db.

RECTIFIER CHASSIS

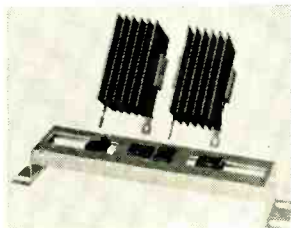Sarkes Tarzian, Inc., 415 No. College Ave., Bloomington, Ind., is now making available to distributors a simple conversion unit that when installed on a chassis will permit the use of the firm's plug-in selenium rectifiers. This simplifies replacement of rectifiers and eliminates removing the chassis and soldering.



FOUR-WAY TUBE TOOL

General Cement Manufacturing Co., Rockford, Ill., has announced a 4-in-1 Tube Gadget made of plastic and rubber. This unbreakable tool has four functions—pin straightening for 7- and 9-pin tubes, tube pulling, and tube tapping.



TUBE BRIGHTENER

C-B-C Electronic Co., Inc., 1310 Callowhill St., Philadelphia 23, Pa., has announced a new Picboost television picture-tube brightener model UB.

This unit will restore brightness to dim picture tubes in any television receiver, whether series or parallel wired, a slide switch on the cap of the unit giving the technician the type of heater connection he needs. The transformer is a heavy-duty type drawing negligible current.



REPLACEMENT SYSTEM

Centralab, a division of Globe-Union Inc., 900 E. Keefe Ave., Milwaukee 1, Wis., has introduced a new Fastatch system of dual concentric-control replacements which eliminates the problems of finding a special control. The rear unit, complete with inner shaft, has been sep-

MAIL TODAY

BUILD 15 RADIOS

AT HOME

With the New Improved 1955

\$19⁹⁵

Progressive Radio "EDU-KIT"

NOW INCLUDES

HIGH FIDELITY,

SIGNAL TRACER, and

CODE OSCILLATOR

BUILD 15 RADIOS AT HOME WITH THE PROGRESSIVE RADIO "EDU-KIT"

- ATTRACTIVELY GIFT PACKED
- FREE SOLDERING IRON
- NO ADDITIONAL PARTS NEEDED
- EXCELLENT BACKGROUND FOR TV
- 10 DAY MONEY-BACK GUARANTEE
- SCHOOL INQUIRIES INVITED
- ABSOLUTELY NO KNOWLEDGE OF RADIO NECESSARY

WHAT THE PROGRESSIVE RADIO "EDU-KIT" OFFERS YOU

The Progressive Radio "Edu-Kit" offers you a home study course at a rock bottom price. Our Kit is designed to train Radio Technicians, with the basic facts of Radio Theory and Construction Practice expressed simply and clearly. You will gain a knowledge of basic Radio Principles involved in Radio Reception, Radio Transmission and Audio Amplification.

You will learn how to identify Radio Symbols and Diagrams; how to build radios, using regular radio circuit schematics; how to mount various radio parts; how to wire and solder in a professional manner. You will learn how to operate Receivers, Transmitters, and Audio Amplifiers. You will learn how to service and trouble-shoot radios. You will learn code. You will receive training for F.C.C. license. You will learn High Fidelity.

In brief, you will receive a practical basic education in Radio, worth many times the small price you pay.

THE KIT FOR EVERYONE

The Progressive Radio "Edu-Kit" was specifically prepared for any person who has a desire to learn Radio. The Kit has been used successfully by young and old in all parts of the world. It is not necessary that you have even the slightest background in science or radio.

The Progressive Radio "Edu-Kit" is used by many Radio Schools and Clubs in this country and abroad. It is used for training and rehabilitation of Armed Forces Personnel and Veterans throughout the world.

The Progressive Radio "Edu-Kit" requires no instructor. All instructions are included, all parts are individually boxed, and identified by name, photograph and diagram. Every step involved in building these sets is carefully explained. You cannot make a mistake.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" comes complete with instructions. These instructions are arranged in a clear, simple and progressive manner. The theory of Radio Transmission, Radio Reception, Audio Amplification, and servicing by Signal Tracing is clearly explained. Every part is identified by photograph and diagram. You will learn the function and theory of every part used.

The Progressive Radio "Edu-Kit" uses the principle of "Learn by Doing". Therefore you will build radios, perform jobs, and conduct experiments to illustrate the principles which you learn. These radios are designed in a modern manner according to the best principles of present-day educational practice. You begin by building a simple radio. The next set that you build is slightly more advanced. Gradually, in a progressive manner, you will find yourself constructing still more advanced multi-tube radio sets, and doing work like a professional Radio Technician. Altogether you will build fifteen radios, including Receivers, Transmitters, Amplifiers, Code Oscillator and Signal Tracer. These sets operate on 105-125 V. AC/DC. An Adaptor for 210-250 V. AC/DC operation is available.

THE PROGRESSIVE RADIO "EDU-KIT" IS COMPLETE

You will receive every part necessary to build 15 different radio sets. Our kits contain tubes, tube sockets, chassis, variable condensers, electrolytic condensers, mica condensers, paper condensers, resistors, fine cords, selenium rectifiers, tie strips, coils, hardware, tubing, etc.

Every part that you need is included. These parts are individually packaged, so that you can easily identify every item. A soldering iron is included, as well as an Electrical and Radio Tester. Complete, easy-to-follow instructions are provided. In addition, the "Edu-Kit" now contains lessons for servicing with the Progressive Signal Tracer, F.C.C. instructions, quizzes, high fidelity instructions. The "Edu-Kit" is a complete radio course, down to the smallest detail.

TROUBLE-SHOOTING LESSONS

Trouble-shooting and servicing are included. You will be taught to recognize and repair troubles. You will build and learn to operate a professional Signal Tracer. You receive an Electrical and Radio Tester, and learn to use it for radio repairs. While you are learning in this practical way, you will be able to do many a repair job for your neighbors and friends, and charge fees which will far exceed the cost of the "Edu-Kit". Here is your opportunity to learn radio quickly and easily, and have others pay for it. Our Consultation Service will help you with any technical problems which you may have.

FREE EXTRAS

- ELECTRICAL & RADIO TESTER ● ELECTRIC SOLDERING IRON ● TV BOOK ● RADIO TROUBLE-SHOOTING GUIDE ● CONSULTATION SERVICE ● QUIZZES ● F.C.C. TRAINING

Progressive "Edu-Kits" Inc., 497 Union Ave., Dept. RE-98, Brooklyn 11, N.Y.

MAIL TODAY—Order shipped same day received.

10-Day Money-Back Guarantee. Include ALL FREE EXTRAS

Send "Edu-Kit" Postpaid. I enclose full payment of \$19.95 (U.S.A. only).

Send "Edu-Kit" Postpaid. I enclose full payment of \$20.95 (Outside U.S.A.).

210-250 V. Adapter for "Edu-Kit"—\$2.50.

Send "Edu-Kit" C.O.D. I will pay \$19.95 plus postage (U.S.A. only).

I wish additional information describing "Edu-Kit". No Obligation.

Send me FREE Radio-TV Servicing Literature. No Obligation.

Name.....

Address.....

PROGRESSIVE "EDU-KITS" INC.

497 UNION AVE., Dept. RE-98, Brooklyn 11, N. Y.

arated from the front unit, complete with the outer shaft, so that the shafts can be cut to the proper length. Then the units snap together.

The number of controls in the new system is limited to the differences in resistance and taper—a total of 61 fronts and 65 rears instead of more than 500 custom units. These 126 controls, making 4,000 possible combinations, will handle any carbon dual replacement in TV now and the great majority of future units including color.



INSULATING COMPOUND

Insl-X Sales Co., 26 Rittenhouse Square, Ardmore, Pa., has announced a new dielectric, abrasion-resistant insulating compound for tools and equipment.

Designated E-33, the new compound is chemically inert, will not corrode or injure any equipment to which it is applied, nor will it be damaged by exposure



to oils, greases, ordinary acids or alkalis.

Items to be protected with E-33 need only to be dipped into the compound, permitted to drain and dry—a 15-minute operation. Three coats an hour apart are recommended for 110-220-volt exposure. The dielectric strength (dry) is 1,200 to 1,500 volts per mil, the approximate thickness of one dip coat.

TUBE TESTER

Boland & Boyce, Inc., 236 Washington Ave., Belleville 9, N.J., has announced a new picture-tube and TV-receiver tester that checks all magnetically deflected black-and-white or color tubes under actual receiving conditions. The model 701 picture-tube tester is available in kit form or factory-wired. The

complete assembly, including a 4½-inch, 100-microampere Simpson meter, is housed in a steel carrying case 9 x 6 x 5 inches.


In operation, the socket is disconnected from the base of the picture tube and inserted into the tester by a cabled adapter cord. A second adapter cord connects between meter and picture tube. With the receiver turned on, accurate measurements are rapidly made of the current and voltages applied to any tube element. Quantitative and qualitative tests include: grid to cathode, heater to cathode, and grid to screen leakage; grid-cathode voltage from receiver; receiver d.c. screen and video-signal output voltages.



FLYBACK TESTER

TeleTest, Inc., 30-01 Linden Place, Flushing, L.I., N.Y., has introduced a new portable and compact flyback tester which tells exactly what condition any flyback is in, testing good flybacks as well as showing if one bad. It also checks yokes, with

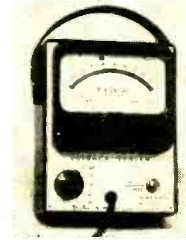coils, and linearity coils for shorted turns.




TV CHASSIS

Walsco Electronics Corp., 3225 Exposition Place, Los Angeles 18, Calif., has introduced a new printed-circuit TV chassis, model PC-9, containing 25 tubes. Using nine circuit units printed on removable plastic strips, the usual 2,900 hand-soldered connections have been reduced to only 56.

The motor-driven remote control automatically finds the channel and locks in the best balanced picture and sound.

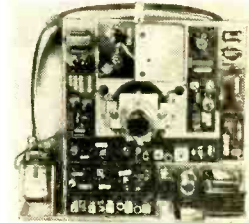Only the volume and channel knobs are exposed. END



IDEAS that will help you to MOVE AHEAD and MAKE MORE MONEY in

RADIO-ELECTRONICS

A FEW OF THE FEATURES you won't want to miss in next month's issue and the issues ahead:

- **PICTURE TUBES—SAINTS OR SINNERS**
Is it the picture tube that is defective? And if so, what can be done about it?
- **EMPLOYMENT IN ELECTRONICS**
Where the jobs are, what they require—and roughly, what they pay.
- **RELAY COMPUTER**
A description of a simple electric brain which the reader can construct—if he likes.
- **DECIBEL MEASUREMENTS**
How you can check input and output with simple equipment.
- **SERVICING DOG RECEIVERS**
A series of articles by engineer-writer Bob Middleton on the TV technician's most troublesome problem.
- **WHAT! NO HIGH VOLTAGE?**
Causes of and cures for high-voltage failures in TV receivers.
- **PLUS**
Many other top notch features on servicing, TV, radio and audio-high fidelity by some of the best technician-writers in the field.



● FREE! VALUABLE COLOR TV SERVICING GUIDE

... yours as a gift with your subscription to RADIO-ELECTRONICS if you send payment NOW!

YOUR NO RISK GUARANTEE

If at any time you do not feel that RADIO-ELECTRONICS is a real help to you, just tell us so and we will promptly refund the unused portion of your subscription. You may keep the TV service guide as a gift. Fair enough? We want you to be the sole judge.

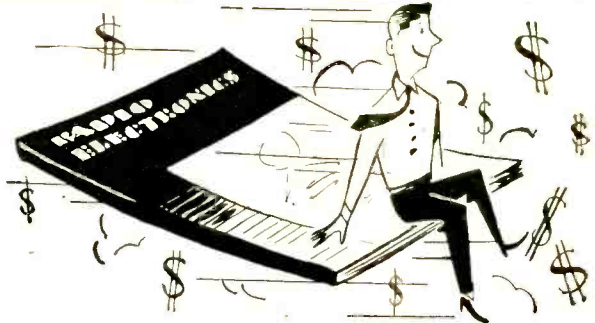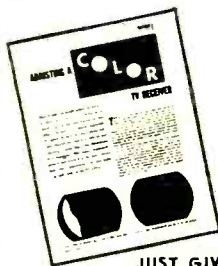DON'T MISS A SINGLE ISSUE—subscribe today and SAVE MONEY. JUST GIVE THIS COUPON to your magazine agent or mail it direct to us. →



YES—I want to MOVE AHEAD AND MAKE MORE MONEY

Please enter my subscription to RADIO-ELECTRONICS as checked below under your NO RISK offer and send me as a free gift the COLOR TV SERVICING GUIDE.

PLEASE CHECK:

- One Year—12 big issues—\$3.50**
(SAVING ME 85c over the single copy price)
- Or you may prefer:
- 3 Years—36 big issues—\$8.00**
(SAVING ME \$5.05 over the single copy price)
- 2 Years—24 big issues—\$6.00**
(SAVING ME \$2.70 over the single copy price)
- I enclose \$..... Please bill me.

NAME (Please Print Clearly)

ADDRESS

CITY ZONE STATE 114

MAIL TODAY TO: RADIO-ELECTRONICS
25 West Broadway, New York 7, N.Y.

LEARN MORE ABOUT Sound and Servicing WITH RIDER BOOKS

SOUND

GUIDE TO AUDIO REPRODUCTION

by D. Fidelman

A to Z explanation of the reproduction of sound design, construction, assembly and testing of sound systems and their components. Valuable for service technicians, engineers, amateurs. Over 250 (5 1/2 x 8 1/2") pages. **ONLY \$3.50**

HIGH FIDELITY SIMPLIFIED

by H. D. Weiler

Story of high fidelity clearly told, easily understood. Tells what to buy and what to do. **HIGH FIDELITY MAGAZINE** said of this book, "fulfills its title." Chapters include: Sound; Acoustics; Simple Loudspeaker; Hi-Fi Loudspeaker; Basic Amplifier; Record Player; The Tuner; and a list of hi-fi component manufacturers! **208 (5 1/2 x 8 1/2") pages. ONLY \$2.50**

HOW TO SERVICE TAPE RECORDERS

by C. A. Tutbill

The complete tape recorder story... practical, easy to understand! Covers operation of recording heads and drive mechanisms used by various manufacturers. Electronic circuits diagrammed and explained. Trouble shooting techniques illustrated. Also tells how to set up a tape recorder repair shop. **5 1/2 x 8 1/2". Soft cover. ONLY \$2.90**

SERVICING

TV FIELD SERVICE MANUALS—

Vols. 1 & 2

edited by Harold Alsborg

Finest practical data for in-the-home servicing. Tube layouts; picture tube adjustments; front and rear controls; tube comment; tuner and horizontal oscillator adjustments; key voltages; dial stringing; trouble symptoms. Spiral binding; books lie flat.

VOL. 2 covers Bendix, Capehart, CBS Columbia, Crosley, DuMont, 160 (5 1/2 x 8 1/2") pages, illus. Soft cover. **ONLY \$2.40**

VOL. 1 covers Admiral, Affiliated Retailers (Artone), Ameco (AMC), Air King, Air Marshall, Allied Purchasing, Andra, Arvin and Automatic, 128 (5 1/2 x 8 1/2") pages. Soft cover. **ONLY \$2.10**

PICTURE BOOK OF TV TROUBLES—

Vol. 1

by John F. Rider Laboratory Staff

First of new "TV Case History" series on how to diagnose TV receiver troubles by means of picture and waveform observations. All material is the result of actual troubleshooting done in the Rider lab! Over 65 "faulty" picture tube pattern illustrations over 150 waveforms (normal and abnormal). Chapters include: Pulse-width Type Synchoguide; Phase Detector—Stabilized Multivibrator; Phase Discriminator—sine wave oscillator (Synchrolock); Phase Detector—sine wave oscillator. **Approx. 80 (5 1/2 x 8 1/2") pages. ONLY \$1.35**

HOW TO USE TEST PROBES

by A. A. Ghirardi and R. G. Middleton

Only book of its kind! Written by two of the country's leading electronics experts! Covers all types of test probes used with VOM's, VTVM's, and scopes. Tells which probe to use, where to use it, how to use it! Chapters include: Resistive; High-Voltage D-C Probe; Capacitance-Divider; High-Voltage A-C Probe; Test Cable; Shielding and Test-Circuit Loading; Fundamentals; Resistive; Circuit-Isolation Probe ("D-C Probe"); Compensated R-C ("Low Capacitance") and Cathode Follower Circuit-Isolation Probe; Rectifying Probes for the VTVM; Demodulator Probes; Index. **Approx. 176 (5 1/2 x 8 1/2") pages. ONLY \$2.90**

OBTAINING AND INTERPRETING TEST SCOPE TRACES

by John F. Rider

At last! The key to successful use of the oscilloscope! Covers radio, audio, television, transmitters—everything about the meaning of scope traces. More than 800 waveforms! Typical Chapters: Interpretation of Test Scope Traces; Sine & Complex Waveforms; Square Waveforms; Rectangular Waveforms; Saw-Tooth & Trapezoidal Waveforms; Differential & Integrated Waveforms; Modulated Waveforms; Response and S Curves; Scope Controls; Phase & Frequency Scope Traces; Test Set-Ups. **192 (5 1/2 x 8 1/2") pages, illus. Soft cover. ONLY \$2.40**

In Canada, all prices approximately 5% higher


Buy these books from your jobber or bookstore NOW. If not available thru these sources, write

JOHN F. RIDER PUBLISHER, INC.
480 Canal Street, New York 13, N. Y.
In Canada: Charles W. Pointon & Alicia Ave., Dept. 7, Toronto, Ontario
East Agent: Reburn Agencies, Inc. 39 Warren Street New York 7, New York
West Coast Office: 4216-20 W. Jefferson Blvd., Los Angeles, California
Cable Address: Reburnage N. Y.

CO-TRAP gives highest FRONT TO BACK RATIO of 5 major competitors!

introducing the all channel
SKYLINE IMPERIAL with Co-Trap




AMAZING FRONT TO BACK RATIO TEST DATA

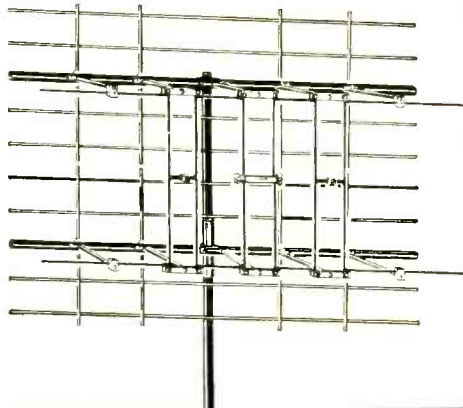

FREQUENCY (Mc)	RELATIVE VOLTAGE -DB	
	2-bay Model 701 Without "Co-Trap" Screen	Skyline Imperial Model 701-CT With "Co-Trap" Screen
50	9.12	10.1
60	9.4	18.1
70	9.4	14.
80	6.8	14.8
90	7.4	14.8
170	3.5	12.9
180	5.1	14.
190	6.4	21.9
200	4.7	16.9
210	4.1	14.
216	3.5	20

Independently tested by the Research Division of Mark Products Co. of Chicago, Edward F. Harris, Chief Engineer

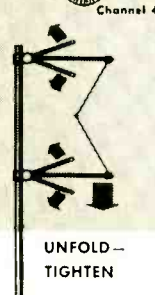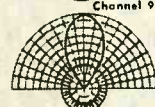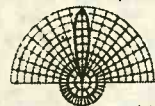Patented
CHARACTERISTIC VHF
BAND PATTERNS
with "Co-Trap"



3000 WITNESSES AT GRAND DEBUT WATCH THE "IMPERIAL" OUTPERFORM 4 MAJOR COMPETITORS!

Side-by-side comparison test proves "Imperial" far superior at rejecting co-channel interference!

Two competitors failed completely—pictures entirely blotted out.

Another two showed inferior pictures and much interference.

Coming through with flying colors, the "Imperial" gave a clear picture free of interference.

Full size 5000 square inch screen.

All aluminum—extra heavy throughout.

Completely pre-assembled.

MODEL No. 701-CT
(2-bay, with "Co-Trap" screen)

LIST
\$27.50

MODEL No. 700-CT (4-bay, with "Co-Trap" screen) also available—\$37 list

SKYLINE MFG. CO. 1652 Rockwell Ave., Cleveland 14, Ohio

NEW! WRIST RADIO

Amazingly powerful! Plays while you wear it. 400 mile reception using just its own antenna. No connections needed to ground, aerial, lamp, telephone, etc. Times full broadcast band with sharp selectivity. Plans, kits, complete sets. Details FREE.

HUCKERT ELECTRONICS, Box 7400, Washington 4, D.C.

ENJOY 3 COLOR TELEVISION FILTER SCREEN NOW

Changes dull eye-straining black and white pictures into beautiful color tones. Seconds to attach. No tools used. Helps eliminate glare and snow in fringe areas. Order direct. Send \$1 for screen size up to 16". \$1.25 size 17". \$1.50 size 20". \$2 size 21". \$2.50 size 24". \$3 size 27". We pay postage except on C.O.D. orders. Satisfaction guaranteed. Inquiries from dealers also welcomed.
Zingo Products, Johnstown 13, New York

EASY TO LEARN CODE

It is easy to learn or increase speed with an Instructograph Code Teacher. Affords the quickest and most practical method yet developed. For beginners or advanced students. Available tapes from beginner's alphabet to typical messages on all subjects. Speed range 5 to 40 WPM. Always ready—no QRM.



ENDORSED BY THOUSANDS!

The Instructograph Code Teacher literally takes the place of an operator-instructor and enables anyone to learn and master code without further assistance. Thousands of successful operators have "acquired the code" with the Instructograph System. Write today for convenient rental and purchase plans.

INSTRUCTOGRAPH COMPANY

4701 Sheridan Rd., Dept. RC, Chicago 40, Ill.

Have You Spent \$2,000.00 On Instruments?



Basic Electronic Test Instruments

by
Rufus P. Turner
254 pages
171 illus.
Price \$4.00

THE BOOK THAT HELPS YOU

- ... save money on instruments
- ... do better work with fewer instruments.
- ... put old instruments to new uses
- ... modernize old instruments

GOODBYE TO INSTRUMENT GUESSWORK!

Here are just a few of the instruments covered: Current & Voltage Meters; Ohmmeters; V-O-M's; V-T Voltmeters; Power Meters; Impedance Meters; Capacitor Checkers; Inductance Checkers; Grid-dip Oscillators; Special-purpose Bridges; Oscilloscopes; R-F Test Oscillators; Signal Generators; Audio Oscillators; R-F and A-F Measuring Devices; Signal Tracers; Tube Testers; TV Sweep & Marker Generators; Linearity Pattern Generators; Distortion Meters; Square-Wave Generators... and dozens more. Use coupon.




10-DAY FREE EXAMINATION

Dept. RE-114. RINEHART & CO., INC.
232 Madison Ave., New York 16, N. Y.

Sure, I'm interested in saving on instruments, so send Turner's BASIC ELECTRONICS TEST INSTRUMENTS on 10-day approval. In 10 days I will either send you \$4.00 plus postage or return book postpaid and owe nothing.

Name
Address
City, Zone, State

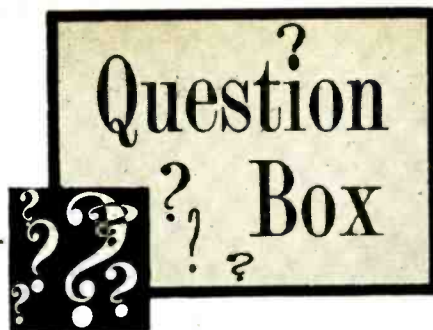OT TRIDE U.S.A.—Price \$5.50, cash with order. Money refunded if book is returned in 10 days.




A.F. LEVEL INDICATOR

I would like to have the circuit of a 6E5 or similar tube as an output level indicator for audio amplifiers and different types of recorders.—E. W. S., Central Islip, N. Y.

The circuit of a simple level indicator is shown. A portion of the signal voltage in the plate circuit of the output stage is rectified and used as negative bias on the indicator tube. The rectifier may be a germanium diode or any convenient vacuum tube.

Coupling capacitor C should have a

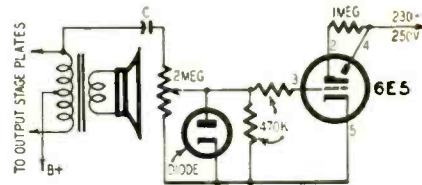rating of at least 600, preferably 1,000 or 1,500 volts. Use the largest value of capacitance that you can without



noticeably reducing high-frequency response.

QUICK-HEATING INTERCOM


I want to construct an intercom using battery type tubes so it can be turned off until needed and yet be ready for operation as soon as a switch is thrown. I would like to use a 1H5-GT and push-pull 305-GT's or equivalents and want the remote station to be able to signal or preferably originate a call to the master.—F. G. M., Billings, Mont.

This circuit is a modification of one that appeared in the September, 1948, issue, now out of print. With it the remote station originates a call by pressing a push-button or normally open lever switch. This switch operates a 6-volt d.c. relay whose contacts connect one side of the line to the filament and


plate supply rectifier.

A 3S4 and 3Q4 are used in push-pull to simplify the problem of supplying bias. The grid bias is the voltage difference between the control grid and the negative end of the filament (pin 1). Pin 1 of the 3S4 is about 7.5 volts above ground and pin 1 of the 3Q4 is about 4.5 volts above ground, so both have correct bias.

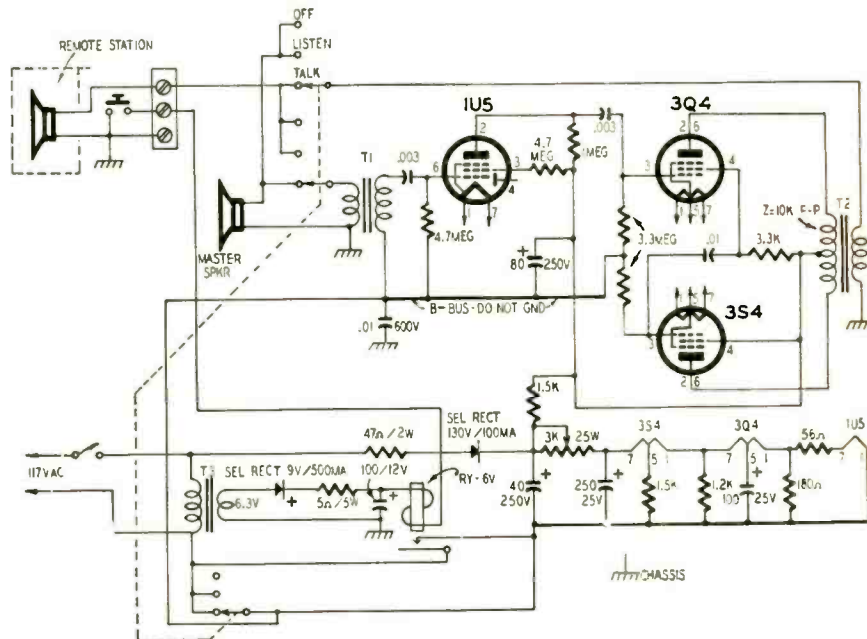There is a slight difference in the optimum plate load impedances of the 3S4 and 3Q4 but this should not affect the quality or output. Signal voltage for the grid of the 3S4 is obtained from the screen circuit of the 3Q4. For optimum performance you can vary the value of the 3Q4 screen resistor for



6 VOLT BATTERY SOLDERING IRON AND WELDER

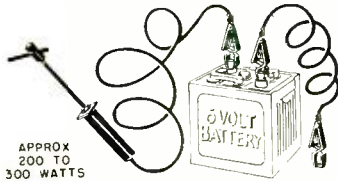

APPROX
200 TO
300 WATTS

U.S. Army release. Brand New—Never Used. Fully Guaranteed. This soldering iron can be used to solder or weld when connected to any six-volt storage battery. Uses approximately 200 to 300 watts. The high intensity arc created between the metal to be soldered and the carbon electrode (carbons supplied free with iron) can be used to heat tin or aluminum solder. Suitable also for light brazing and spot welding. Arc can be used for melting metals, cutting holes and soldering seams in chassis. Also useful for analyzing metals and minerals.

Battery soldering iron outfit includes 2 carbons, 3 heavy duty spring clips, 2 pieces 5 ft. heavy duty wire cable. (Battery not included.) Ideal for use where current is not available. Ship wt. 4 lbs.

\$1.95

ITEM NO. 126
UNUSUAL BUY (Shp. Chgs. 40¢)

POWERFUL ALL PURPOSE MOTOR



Sturdy shaded pole A.C. induction motor. 15 watts, 3000 rpm. 3"x2"x1 3/4"; 4 mounting studs; 7/8" shaft, 3/16" diameter; 110-120 volts, 50-60 cycles. A.C. only. When geared down, this unit can operate an 18" turntable with a 200 lb. dead weight. Use it for fans, displays, timers and other purposes. Ship wt. 2 lbs.

\$2.45

ITEM NO. 147
UNUSUAL BUY (Shp. Chgs. 35¢)

WATTHOUR METER

Leading makes—reconditioned. Ideal for trailer parks, 100-110 volts, 60 cycles, 2-wire A.C. 5 amp. Heavy metal case 8 1/2" x 6 1/4" x 5". Easy to install. Ship. wt. 14 lbs.



ITEM NO. 33
NOW ONLY **\$4.50**

(Shp. Chgs. \$1.25)

WESTERN ELECTRIC BREAST MIKE



Lightweight 1 lb. carbon microphone. Aircraft type. Breastplate mounting, adjustable 2-way swivel. Easily fastened straps. For home broadcasts, communications etc. Complete with 6 foot cord, hard rubber plug. Sheradized plate, non-rusting finish. Ship. wt. 2 lbs.

\$1.98

ITEM NO. 152
NEW LOW PRICE (Shp. Chgs. 32¢)

AMAZING BLACK LIGHT



250-watt ultra-violet light source. Makes fluorescent articles glow in the dark. Fits any lamp socket. For experimenting, entertaining, unusual lighting effects. Ship. wt. 2 lbs.

\$2.45

ITEM NO. 87
A SAVING AT (Shp. Chgs. 35¢)

250 POWER TELESCOPE LENS KIT

Make your own high powered 6 ft. telescope! Kit contains 2" diam., 75" focal length, ground and polished objective lens and necessary eye pieces. Magnifies 50x to 250x. Full instructions. Ship. wt. 1 lb.

\$2.95

ITEM NO. 123
YOU SAVE AT (Shp. Chgs. 10¢)

HUDSON SPECIALTIES CO.
25 West Broadway, Dept. RE-11-54
New York 7, N. Y.

I am enclosing full remittance for items circled below. (Be sure to include shipping charges.)
OR, my deposit of \$... Ship balance C.O.D.
MINIMUM C.O.D. ORDER \$5.00.
C.O.D. ORDERS ACCEPTED ONLY WITH 20% DEPOSIT
INCLUDE SHIPPING CHARGES.

Circle Items Wanted

87 147 33 152 126 123

Name Please Print Clearly

Address

City Zone State



GOODLINE
is Virgin
POLYETHYLENE

Now—SILICONE "WETPRUF"® PROCESSED, ANOTHER GOODLINE FIRST, Extends useful wet service life as much as 400%.

ALL GOODLINE Low Loss Television Transmission Lines are now especially SILICONE PROCESSED to repel moisture AT NO INCREASE IN COST TO YOU.

Your distributor has these SILICONE PROCESSED, WATER REPELLENT GOODLINE TRANSMISSION LINES in stock now — ready for you...

Ask for them by name. Insist on these genuine GOODLINE "WETPRUF" TELEVISION LINES.

**GOODLINE AIRLEAD — 733 GA & 737 GA GOODLINE HOLO — 801 GH
GOODLINE SHEATHLEED — 812 GS & 823 GS GOODLINE TELEAD**

ALSO THE ECONOMY NON-SILICONE GOODLINE ANGELUS

*IT'S EASY TO TELL IF IT'S "GENUINE GOODLINE" All Don Good Television Leadlines are Quickly Identified By The Blue and Yellow Reel.

ALL GOODLINE TELEVISION TRANSMISSION LINES ARE PURE VIRGIN POLYETHYLENE ESPECIALLY COMPOUNDED FOR LONG SERVICE LIFE.

Don Good INC.

**SOLD BY LEADING
JOBBER & DEALERS**

**Send coupon NOW!
Get samples "in your hands"
—you'll realize why
Don Good Products make
the finest television
reception possible.**

DON GOOD, INC. 1-20
1014 Fair Oaks Ave., So. Pasadena, Calif.
Please rush Samples and Complete Information covering Don Good Products.

Name _____
Street _____
City _____ State _____

**Floritone EXTENSION SPEAKER
"CONTROL AT YOUR FINGERTIPS"**

The extra "personal" speaker for your TV—a "must" for the "hard of hearing" and the utmost in luxurious listening pleasure for every TV or radio owner. 4 in 1 switch controls either speaker—both speakers—or shuts off sound. Easily installed and lists for only \$14.95.



SAMPLE
\$10.00
(Dept. R.E.)

Dealers and distributors, write for liberal discount information.

SOOTIN'S, INC.

321 NW 3rd Ave., Miami 36, Fla.

UHF COIL BOARDS

(Standard Coil Product)

\$2.50 per set
Postage prepaid

- Small lot orders OK (Minimum order—12 sets)
- Servicemen—a real buy while they last!

CHANNELS (Types Q, K, F/G)

18	23	27	46
20	21	29	56
21	25	34	

- Enclose check with order. No C.O.D.'s

Send to: **Pacific Mercury Sales Corp.**
8345 Hoyvenhurst Ave.
Sepulveda, Calif.

INVALUABLE GUIDES FOR Specialized Servicing



be an
expert on
**AUTO
RADIOS**



NEW VOLUME 4

Covers 50 chassis (62 models) produced during 1953. Complete coverage includes schematics, chassis photo views, replacement parts data, service hints, etc. 288 pages. 8½ x 11".

Order AR-4. Only.....\$3.00

Vol. 3. Covers 47 chassis (80 models) produced in 1950, 1951, 1952. 288 pages. 8½ x 11". Order AR-3. Only.....\$3.00

Vol. 2. Covers 60 chassis (90 models) produced in 1948, 1949, 1950. 288 pages. Order AR-2. Only.....\$3.00

Vol. 1. Covers 100 models made from 1946 to 1949. 396 pages. Order AR-1. Only.....\$4.95

be an expert on **AUDIO AMPLIFIERS**



NEW VOLUME 5

Covers 37 amplifiers, 12 preamplifiers and 14 tuners made in 1952, 1953. Complete analysis based on lab study: circuit diagrams, chassis photo views, parts data, full coverage. 352 pages, 8½ x 11".

Order AA-5. Only.....\$3.95

Vol. 4. Covers 75 amplifiers and tuners made in 1951, 1952. 352 pages; 8½ x 11". Order AA-4. Only.....\$3.95

Vol. 3. Covers 50 amplifiers and 22 tuners made in 1950. 352 pages, 8½ x 11".

Order AA-3. Only.....\$3.95

Vol. 2. Covers 104 amplifiers and 12 tuners made in 1949. 368 pages, 8½ x 11".

Order AA-2. Only.....\$3.95

ORDER
TODAY

HOWARD W. SAMS & CO., INC.

Order from your Parts Jobber today, or write to Howard W. Sams & Co., Inc., 2205 East 46th St., Indianapolis 5, Ind.

\$.....enclosed. Send following books:

AR-4 AR-2 AA-5 AA-3
 AR-3 AR-1 AA-4 AA-2

Name.....

Address.....

City.....Zone.....State.....
(outside U.S.A. priced slightly higher)

QUESTION BOX

(Continued)

equal signal voltages on the control grids.

When putting the unit into operation for the first time, set the 3,000-ohm, 25-watt resistor so its full resistance is in the circuit. Then gradually reduce the resistance until there is 9.8 volts between pin 7 of the 3S4 and the B-minus bus.

If the stations are reasonably close together, you can use standard 3-5-ohm PM speakers. T1 may be a 25,000-ohm plate-to-voice-coil transformer with the primary in the grid circuit and T2 a standard output transformer to match the speakers to a plate-to-plate impedance of about 25,000 ohms. If the run between stations is fairly long, use 40-50-ohm speakers and output and input transformers to match. T3 is a 6.3-volt filament transformer.

AMPLIFIER CONVERSION

I like the performance of the low-cost amplifier in the Question Box of the February, 1954, issue, so I'd like to construct another using push-pull power amplifiers for more output. Please show the necessary circuit changes.—R. B. D., Tacloban, Leyte, P. I.

Push-pull power amplifiers with three different methods of phase inversion are shown. The diagram at *a* is self-explanatory. It shows the tone controls and a vacuum-tube phase inverter.

The circuits at *b* and *c* use tubeless phase inversion. The tone controls are not shown. Point A is a common refer-

Interest in the Question Box, as indicated by letters received, is not high, and the question has arisen as to whether the space might not be better devoted to other subjects. What do our readers think? Should we: (1) continue the Question Box as is; (2) discontinue it; or (3) substitute some other material, and if so, what? Please mail your vote to Question Box, Radio-Electronics, 25 West Broadway, New York 7, N.Y.

ence on the three diagrams. In circuit *b*, the input signal is fed directly to the grid V1. Its screen current varies about 7 ma between zero input and full-signal input and produces an out-of-phase audio voltage across the 1,800-ohm screen resistor. This voltage is tapped off and fed to the control grid of V2. For best results, adjust the value of the screen resistor for equal signal voltages on the control grids.

The circuit at *c* produces phase inversion by autotransformer action. The signal on the grid of V1 flows to ground through the upper half of the audio choke and produces an out-of-phase voltage of equal amplitude in the lower half to drive V2.

The choke should be a center-tapped type with an inductance of at least 10 henries. You can use the primary of a push-pull output transformer that is designed to work with a plate-to-plate load of about 14,000 ohms.

The power-supply requirements are

arkay kits

world's finest radio, phono, TV, and test kits

hifi ac/dc amplifier kit

arkay kit model A-5: A high-fidelity AC/DC amplifier kit featuring a new, improved push-pull output circuit plus a specially designed output transformer utilizing 2 speakers for the new 3d-dimensional qualities of audio reproduction. New engineering developments give you hi-fi at the lowest possible price. Kit is complete, except for speakers.

Hi-Fi at Lowest Price

\$9.95

ac/dc radio kit



arkay kit model S-5E: New, 5-tube superhet. kit designed for radio students and hobbyists. Includes new 3D color instruction book, 550-1600 kc, complete with glistening walnut bakelite cabinet. Fun to assemble.

Build this Quality Radio Yourself **\$14.95**

hi-fi pre-amp kit

arkay kit model PA-3: Complete compensation for LP, NARTB, AES and early 78 RPM records. Kit also may be used as a control unit for custom hi-fi installations. Includes bass and treble control and contains 5 turnover and roll-off switch positions; 3 dual triode tubes are used to give maximum performance always.



\$16.95

10 watt hi-fi amplifier kit



arkay kit model A-10: Complete with built-in pre-amplifier for magnetic cartridge, mike, crystal phono or radio tuner. Frequency response ± 1 db., 20 to 20,000 cps. with wide response bass and treble controls. Speaker output inductance:

4, 8, 16 ohms; negative feedback; hum: 70 db below rated output. Complete with tubes!

\$21.95

hi-fi amplifier with built-in pre-amp

arkay kit model FL-10: A striking new design with physical dimensions and style for use on a shelf or corner without elaborate or expensive enclosures. Specifications: same as model A-10 (above).






Stylized Unit that needs No Cabinet **\$27.95**

Write today for new catalog including complete arkay line of radio, TV, phonograph, amplifier and test equipment kits.

the world's finest kits

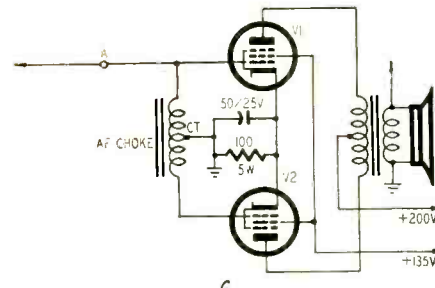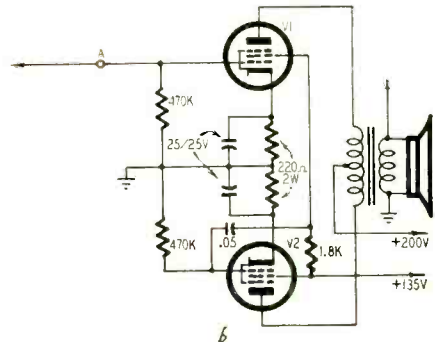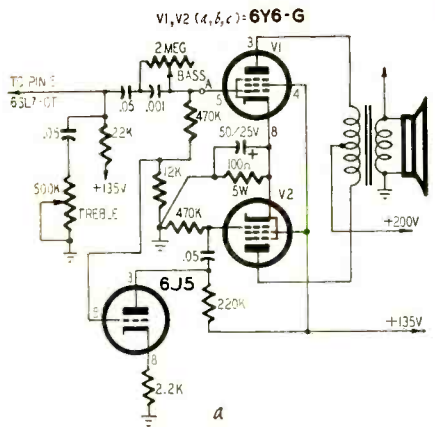arkay RADIO KITS, INC.
120 Cedar Street
New York 6, N. Y.
BEekman 3-6686



nearly doubled by the addition of the second 6Y6-G, so the power transformer should be able to supply at least 160 ma. END

Radio Thirty-Five Years Ago
In Gernsback Publications

HUGO GERNSBACK Founder	
Modern Electrics	1908
Wireless Association of America	1908
Electrical Experimenter	1913
Radio News	1919
Science & Invention	1920
Television	1927
Radio-Craft	1929
Short-Wave Craft	1930
Television News	1931

Some of the larger libraries still have copies of ELECTRICAL EXPERIMENTER on file for interested readers.

In November, 1920 Science and Invention (formerly Electrical Experimenter)

The Belin System of Telephotography 300-K.V.A. Transmitter at Bolinas, Calif. by Allan C. Forbes, Assoc. I.R.E.

The Audion in a New Rôle Simplest Long Wave Receiver (Part II). by Elliott A. White

New Radio License Rules at New York

your customers want the BEST!...the "ORIGINAL"


MOSLEY

Wall


Thru

To Get The ORIGINAL, Ask For It By Name!

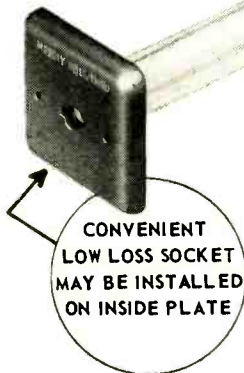TAKES ALL POPULAR LINES! RUBBER GROMMET SEALS OUT MOISTURE!



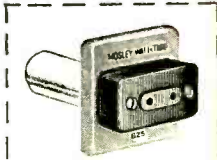POLYSTYRENE THRU-OUT! FULL 1/8" THICK WALL - BEST FOR UHF, VHF, COLOR



Cat. No. 625 MOSLEY WALL-THRU, in brown or ivory. List Price \$1.95

Cat. No. 625-PK WALL-THRU, with Universal TV Socket & mating Plug. List Price \$3.00

Write for free copy of MOSLEY Condensed Catalog, Form D-1. Tells - How To Make More Installation Profits!

Mosley Electronics, Inc.
8622 ST. CHARLES ROCK ROAD
ST. LOUIS 14, MISSOURI

A Word Of Caution!

Because there are numerous imitations, similar in appearance to the popular Wall-Thru, the TV installer is cautioned to ask for the Original MOSLEY Wall-Thru - by name!

For Quality, Value, Practical Design - insist upon the MOSLEY Wall-Thru . . . Another PREMIUM QUALITY MOSLEY Accessory for Better, More Profitable TV Installations!



"Our stock of JENSEN NEEDLES"

GET INTO THE HI-FI PROFIT PICTURE



with **N**ationally-advertised
Easy-to-sell
Wonderfully designed
Competitively priced
Operationally-advanced
Merchandised to the hilt
Brilliantly engineered
SERIES D AMPLIFIERS


Please send me full details of Newcomb's new sales policy.
 Also send me Public Address System Catalog.

name _____
address _____
city _____ state _____
name of distributor _____

NEWCOMB AUDIO PRODUCTS CO.
6824 Lexington Ave., Hollywood 38, California

A New Champion!

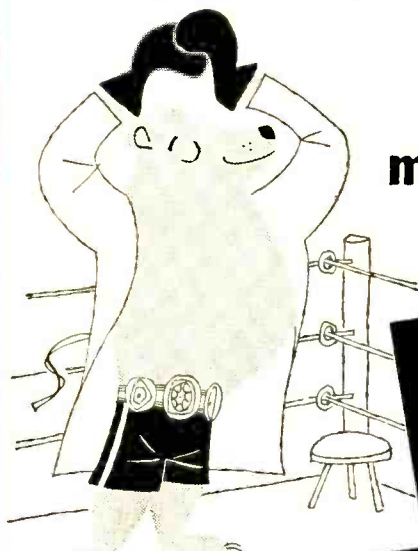tops in the
field of
molded tubular
capacitors



**C-D's
Cub**



- * Outperforms all other molded tubulars in humidity tests!
- * Stands up under temperatures up to 100°C.
- * You get more for your dollar with this premium tubular designed and built especially for replacement needs, with "better-than-the-original" performance!
- * Ask your C-D jobber about the special "Cub-Kit"!

For the name of your C-D distributor, see the yellow pages of your classified phone book. Write for Catalog to: Dept. RC-114, Cornell-Dubilier Electric Corp., South Plainfield, N. J.

CONSISTENTLY DEPENDABLE
CORNELL-DUBILIER

There are more C-D capacitors in use today than any other make.

PLANTS IN SOUTH PLAINFIELD, NEW JERSEY; NEW BEDFORD, WORCESTER AND CAMBRIDGE, MASSACHUSETTS; PROVIDENCE AND HOPE VALLEY, RHODE ISLAND; INDIANAPOLIS, INDIANA; SANFORD AND FUYQUAY SPRINGS, NORTH CAROLINA. SUBSIDIARY RADIART CORPORATION, CLEVELAND, OHIO



Business



Merchandising and Promotion

General Cement Manufacturing Co., Rockford, Ill., is planning to launch a stepped-up advertising and promotional campaign next year in celebration



Art director D. Rice points out artwork details to General Cement executives.

of its 25th anniversary which occurs January 6, 1955. Paul J. Steffen Co., Chicago, the company's advertising agency, is working out the details of the campaign.

Pyramid Electric Co., North Bergen, N. J., developed a new 6-month inventory record and interchangeability chart for distributors who handle its capacitors. The chart gives Pyramid's equivalent for capacitors manufactured by other companies as well.

Radio City Products, Easton, Pa., designed a new point-of-sale display to aid distributors in promoting the sale of its recently issued model 480 universal multimeter.

JFD Manufacturing Co., Brooklyn, N. Y., is now packaging its Tune-A-Scope v.h.f./u.h.f. indoor TV antenna in a colorful new container. The company also announced that its chief antenna engineer, Doug Carpenter, had traveled 87,000 miles during the past year conducting antenna tests and lectures


**BUY DIRECT
MANUFACTURER TO DEALER**
ANTENNAS-INSTALLATION
HARDWARE AND ACCESSORIES
WRITE FOR CATALOG

Skysweeper inc.
P. O. BOX 68
McHENRY, ILL.

**RADIO CONTROLLED
Garage Door
Operating Mechanism \$24.50**
Write for Information
P. E. HAWKINS CO.
631 Prospect Kansas City 24, Mo.

THE BOOSTER BUY OF THE YEAR
Famous Masco TVB
"Cascadian" Booster
formerly \$42.50 now \$19.50.
Dealer discount available

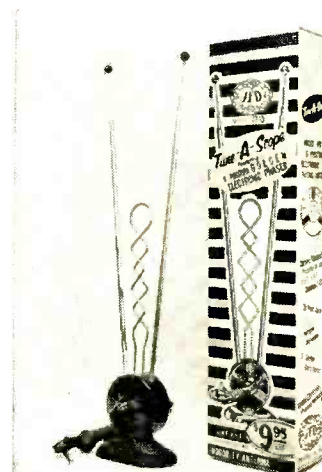ELCRAFT ELECTRONICS
32-28 49 St., L.I.C. 3, N.Y.



BUSINESS (continued)
 throughout the U. S. and Canada. JFD will continue this informative program to aid distributors and dealers in selling its products.

RCA Tube Division, Harrison, N.J., announced a new parts inventory plan for service technicians to aid in the promotion of the use of replacement parts for its 45-r.p.m. Victrola phonographs.

Calendar of Events

Polytechnic Institute of Brooklyn Symposium on Modern Advances in Microwave Techniques. November 8-10, Auditorium of the Engineering Societies Building, New York, N. Y.
Audio Fair, Los Angeles. February 10-12, Alexandria Hotel, Los Angeles, Calif.

Business Briefs

... Alliance Manufacturing Co., Alliance, Ohio, manufacturer of the *Tenna Rotor* antenna rotor and *Lift-A-Door* automatic garage door operator, entered a new field with the introduction of its *Triceptor* line of all-channel antennas. John Bentia, Alliance executive vice-president, stated that the company is presently featuring its *Monolober* model in single or double bay.

Sylvania Electric Products, New York City, launched a new promotional program for West Coast distributors of its renewal tubes. The campaign, intended to help service technicians cut down on call backs, includes the introduction among new tube types of Sylvania's 5U4-GB and 6BQ6-GTA tubes.

Raytheon's Receiving and Cathode Ray Division has announced to its industrial tube distributors a price reduction on its popular type CK722 transistor, according to F. E. Anderson, distributor sales manager. Effective September 1, 1954, users may purchase this popular Raytheon type transistor for \$3.50.

New Plants and Expansions

Ward Products Corp., Cleveland, Ohio, established a new antenna research laboratory in Ashtabula, Ohio, for the design and testing of TV and automobile antennas.

RCA Tube Division, Harrison, N. J., has set up ten new warehouses strategically located throughout the U. S. for the distribution of its radio and industrial batteries. Batteries were formerly warehoused with other RCA products. The new program will speed delivery to battery distributors.

Erie Resistor Corp., Erie, Pa., announced that two of its subsidiaries had opened new enlarged plants: Erie Resistor Ltd. of Canada, in Trenton, Ontario, Canada, and Fryling Electric Products in Holly Springs, Miss.

Lowell Manufacturing Co., St. Louis, Mo., opened an additional plant directly east of its present plant. The company manufactures low-level sound equipment.

Blonder-Tongue Laboratories, West-

"BIG SAVINGS FOR YOU"

EDLIE Just Out!
says First Time Anywhere
Larrel's

E-Z TV REPAIR GUIDE

The only Fix-It-Yourself guide made expressly for YOUR TV SET!
 Save costly TV repairs with this new, simplified method which includes all necessary data for just your set. No confusing, unimportant information applicable to hundreds of different makes. Simplifies detection of faulty tubes in your TV receiver. It's a great idea—it's a great guide. Order today and have your set back in perfect condition at once. Send us make and model of your set when ordering. Only **50¢**

NEW KIT SUPERSENSITIVE 2 STATION INTERCOMMUNICATIONS SYSTEM—Kit \$12.95



Factory Wired **\$16.95**

This fine unit is suitable for use in home, office, factory, nursery, or sick room. So sensitive it will pick up baby's whimper. Operates from 115 V. AC/DC. Both stations housed in compact, handsome plastic cabinets; 6" x 6" x 3 1/2". Requires only 2 wires to connect for quick installation. Complete with 50 ft. of twin conductor wire.

E-Z TV REPAIR GUIDE

Save costly TV repairs... FIX IT YOURSELF

This simplified method of repairing your own TV set... **50¢**

PREPARED EXPRESSLY FOR YOUR SET

No confusing, complicated information applicable to hundreds of different makes.

50¢

This Guide Has Been Prepared Only For Your Set

Larrel Electronics Inc.

Newest Flashlight

BROW-LITE

Frees Both Hands for repair work.



Just out! Brow-Lite gives you the third-hand you've always wished for when using a flashlight. Indispensable to servicemen—excellent for night work. Safe and quicker than flashlight. Fits easily on your head like a pair of glasses yet can be worn comfortably with or without glasses. Adjustable to any angle.

WORLD'S MOST USEFUL FLASHLIGHT. Uses standard penlite batteries & bulb.

Complete with battery & bulb

\$1.98

Electronic CODE OSCILLATOR KIT
 AC-DC or Battery Operated!
 Kit #2—One of the most practical Code Practice Oscillators ever designed, yet one of the simplest to build and operate. Can be used with any number of headphones. Adjustable Pitch Control—Any type of headphone can be used. No warmup time—ready to operate instantly. Simple and safe to operate. Operates anywhere—with AC or DC power, or from a 90 volt Miniature Battery. Learn Blinker Code with flashing light. Blinker can be used as signaling device. International Morse Code included.
KIT each \$1.95 Assembled \$2.95


Phono Oscillator
NEW SAVINGS!
NOT A KIT!

Wireless phono oscillator transmits recording for crystal pickups of voice from carbon mike through radio without wires. Can also be used as an intercom by using PM speaker as \$2.95 mike (less tubes)
With complete set \$3.95 of tubes.

3 TUBE PHONO AMPLIFIER
NOT A KIT

An assembled unit ready for installation using tone and volume control and 6 ft. tube-her cord. (less tubes) \$2.95
Lowest Price!
With complete set of tubes \$4.45

TERRIFIC VALUE!

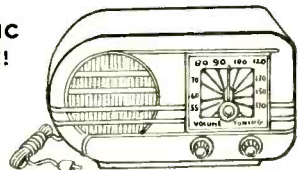


5 TUBE AC/DC Superhet Kit

Kit #1: 5 tube superhet kit. AC/DC includes all quality components required to construct this latest design, highly sensitive superhet broadcast receiver, complete with black, glistering bakelite cabinet (exclusive wire & solder). Kit of 5 tubes. 12AT6, 2/12BA6, 12BE6, 35W4, 50L5.
\$7.95
Price, Less Tubes..... \$3.25

Extra for Tubes..... **\$3.25**

3-Way Portable RADIO KIT
AC/DC Batteries



NEW, compact, lightweight portable radio kit with the very latest supersensitive superhet circuit. Wonderful reception from either batteries or 115 V., 50-60 cycle AC or DC. Includes all complete parts (except wire & solder) necessary to build a great sounding radio. Also includes circuit diagrams and simplified, complete step-by-step instruction folder which makes assembling easy. Housed in a beautifully hinged, glossed Catalin cabinet in two delightful colors and distinctive color: maroon or alabaster (ivory). Size: 5 1/2" x 5 3/8" x 4 1/2". Includes tubes! **\$13.95**

BATTERY KIT: add..... \$2.59

PRECISION RESISTOR KIT

Consists of 50—1% Wilkor carbon film resistors of 50 different ohmages, housed in a transparent plastic box. May be combined in series or parallel to produce almost any desired ohmage. Each resistor retails for about 85¢.
Terrific Cash Saver!
Kit of 50..... only \$2.45

PRECISION WIRE WOUND RESISTOR KIT

Includes 20 resistors, WW3, WW4 and WW5 of 1% tolerance in assorted ohmages... with plastic box. **\$2.95 Complete**

SELENIUM RECTIFIERS
 Standard high grade makes (Federal, Sarkes-Tarjian etc.) at great savings.
 65 Ma. \$.54 300 Ma. \$1.19
 100 Ma. \$.68 350 Ma. \$ 1.35
 250 Ma. \$ 1.19 400 Ma. \$ 1.52
DEDUCT 10% on orders of 25 or more —may be assorted.

Great Savings!
6-TUBE RADIO KIT

Kit #2: Low priced 6-tube kit designed for extra high sensitivity, excellent selectivity and good, rich tone quality. Uses 25L6, 25Z6, 6X4, 6SA7, 2/6SK7 in an easily constructed circuit. Includes all parts: paneled chassis, resistors, condensers, coils, sockets, PM speaker, hardware, etc. **\$6.95**
Special closeout price, (Less tubes & cabinet), Matched set of 6 tubes \$3.25 for kit

Special Savings CRYSTAL DIODES

IN34	\$.55	IN48	\$.45
IN3A65	IN6445
IN47W.E.	1.25		

TERMS: All mdse shipped FOB New York City, prices subject to change without notice. Include 20% deposit for COD's. **WRITE TODAY FOR NEW FREE CATALOG!**

EDLIE Electronics

154 Greenwich St.
 DI 9-3143
 New York 6, N. Y.

HERSHEL RADIO CO. BIGGEST BUYS!

FIL. TRANSFORMER

PRI. 117V. 60 cycle
 Sec.,
 6.4v 12amp.
 6.4v 10amp.
 5v 3amp.
 5v 3amp.
 2.5v 1.75amp.
\$4.95
 SIZE: 5 1/16" x 5 1/16" x 5 1/4" H.

RCA OUTPUT

TRANSFORMER
 P.P. 616'S 25 watt
 PRI 5000 Ohms
 output, Sec. #1
 500 Ohms. Sec.
 #2 600 Ohms.
 Sidetone 15 to
 15,000 cy. flat.
\$1.95

NOVEMBER SPECIALS

A-Ignition Coil Pri. 3 V. Sec.
 15,000 V. Ideal for Photo-
 flash \$1.29
 B-Full Wave Meter Rectifier.
 For use with 0-1 Ma. Meter
 95c
 C-Willard Battery, 2 Volt
 20 AH \$2.50
 D-Headset Adapter MC 385-A.
 High to low use with HS-93
 or HS-38 \$95c

HI-LO ANTENNAS

Outdoor improved Model
 K 1/2" Aluminum-Seamless
 Tubing with 1 1/4"-5 Foot
 Mast and Roof Mount.
 Buy Now and Save.
 Complete **\$5.95** Ea.

OIL COND.

MFD	VDC	PRICE
.05	3000	\$1.95
.05	7500	2.29
.1	4000	1.29
.1	7000	1.75
.1	7500	2.49
.5	2500	1.75
2 x .5	8000	1.49
1	3000	2.49
1	3600	2.95
1	5000	4.95
2	600	.49
2	1000	.95
2	3000	4.95
4	1000	1.95
6	600	1.29
7	600	1.39
8	600	1.75
8	1000	2.49
10	600	2.49
10	1500	4.95

DUAL 4-1000

2x4 600 3.95
 13.5 220 vac. 1.95
 6 330 vac. .95

PAPER CAN

MFD	VDC	PRICE
250	10	\$.39
500	12	.49
1000	3	.69
1000	13	.95
1000	25	1.29
1200	10	.95
1600	15	1.29
24000	3	1.49
117	110 vac.	1.45

PHOTO-FLASH SPECIAL!

MFD	VDC	PRICE
525	450	\$9.95

1 KW ANT. CHANGEOVER

RELAY
 110 VAC
 60 Cycle
 15 Amp
 2500 Volt
 D.P.D.T.
\$9.95

BUTTERFLY CONDENSERS

TYPE A-106-330 MC-
 Antenna Type
 TYPE B-300-1000 MC-
 Uses 368AS tube
 TYPE C-300-1000 MC-
 Clip for Xtol Det.
 TYPE D-135-485 MC
YOUR CHOICE \$4.95

CHOKE SPECIALS!

DUAL 4.5 120MA	\$ 1.95
4.5 70MA	
DUAL 1H 400MA	\$2.95
4.2H 75MA	
15H 80MA 385 OHM	\$ 1.95
2-7H. Swinging 550MA	\$ 5.95

MODULATION and DRIVER TRANSFORMERS

\$4.95 for Both
 Modulation
 trans. 815 Class
 AB2 56 Watt
 DRIVER, 65N7
 to Modulator.

VIBRATOR SUPPLIES

PE 117C **YOUR CHOICE \$9.95**
 Input 6 or 12V DC. To Sup-
 ply Fil. and Plate Power.
 Used with 6C 659.
 PE 204C
 Input 12V DC. Supply Fil.
 and Plate Supply. Used
 with 6E99.

PLATE TRANS. only

\$9.95
 PRI. 90 v
 60 cy.
 3 amp. Sec. 640 v
 1 amp. 654 x
 5 1/4 x 6 1/4 H.

TELEGRAPH SOUNDER

\$7.95
 Main Line 150
 ohms. Attn. C.A.P.

HERSHEL RADIO CO.

5245 GRAND RIVER
 Detroit 8, Michigan
 Phone TYler 8-9400

TERMS: Cash with order or 25%
 DOWN—BALANCE C.O.D. NET
 10 DAYS RATED ACCOUNTS
 ALL PRICES NET F.O.B. DETROIT
 Merchandise Subject to Prior Sale

AGENTS TV-RADIO SERVICE LIBRARY

HERE IS LATE INFORMATION IN A HANDY FORM FOR RADIO AND TELEVISION REPAIRMEN, SERVICEMEN AND STUDENTS



2 VOL. \$6 COMPLETE \$1 A MO. PAY ONLY 1 MO.
 AUDELS T.V. RADIO SERVICE LIBRARY—Highly Endorsed—1001 Facts—Over 1552 Pages—625 Illustrations, Diagrams of Parts, Presents Important Subjects of Modern Radio, Television, Industrial Electronics, F.M., Public Address Systems, Auto, Marine & Aircraft Radio, Phonograph Pick-Ups, etc.

IT PAYS TO KNOW!
 The Basic Principles—Construction—Installation—Operation—Repairs—Trouble Shooting. Shows How to get Sharp, Clear T.V. Pictures. Install Aerials—How to Test, Explains Color Systems, Methods of Conversion, Terms, etc. Includes Ultra High Frequency (U.H.F.)—Valuable for Quick Ready Reference & Home Study. Tells How to Solve T.V. & Radio Troubles—Answers Your Questions.

Get this information for yourself. 7 DAY TEST—ASK TO SEE IT!

MAIL ORDER

AUDELS Publishers, 49 W. 23 St., N.Y. 10, N.Y.
 Mail AUDELS T.V. RADIO SERVICE LIBRARY 2 Vols. \$6 on 7 days free trial. If O. K. I will remit \$1 in 7 days and \$1 monthly until \$6 is paid. Otherwise I will return them.

Name _____
 Address _____
 Occupation _____
 Employed by _____ RE

NEW! Electro completely assembled 6 and 12 VOLT DC POWER SUPPLY



Model D-612
ONLY \$39.95
 at a comparable KIT PRICE
 0 to 8, 0 to 16v. completely variable; 0 to 10 amps. at 12v. continuous. Operates all auto radios. For relays, low voltage devices, battery charging, etc. Less than 5% ripple over rated ranges. Withstands high voltages.

MODEL "B" FILTERED DC POWER SUPPLY

For testing, servicing, operating low power 2-way mobile auto radios. 1 Model "B" delivers 6v. at 20 amps. 2 Model "B's" in parallel deliver 6v. at 20 amps. **\$49.80**

MODEL "S" Converts Battery Radios to AC ALL-Electric

Assures hum-free reception from any 1 1/2v., 4 to 6-tube battery radio using 115-volt, 50-60 cycle source. Fits battery space. Guaranteed three years. **\$11.10**
 Write for details or ask EPL representative

ELECTRO PRODUCTS LABORATORIES
 4501-Ra N. Ravenswood Ave., Chicago 40, Ill.
 Canada: Atlas Radio Corp., Ltd., Toronto

BUSINESS

(continued)

field, N. J., has expanded its production facilities with the opening of a second plant. Production Manager Arthur Janus heads factory operations. The company also announced an increase in its personnel.

Raytheon Manufacturing Co. moved its New York offices to larger quarters at 589 Fifth Ave., New York. The office conducts sales functions of the company's international operations, equipment sales, and receiving and special tube sales.

Permoflux Corp., Chicago, moved its Distributor Division to new quarters at 2835 No. Kedzie Ave. The move concentrates the division's various functions in one building to permit better and faster service to its distributors.

General Electric plans to establish a new electron tube development laboratory on Stanford University land in Palo Alto, Calif. The new laboratory will concentrate on developing and exploring the application of microwave electron tubes. It will be under the direction of H. R. Oldfield, Jr., former manager of the G-E Advanced Electronics Center at Cornell University.

National Co., Malden and Melrose, Mass., established a New Products Department which will be managed by Robert J. Caldwell, formerly of High Voltage Engineering Corp. The company also revealed plans to double its research and engineering facilities.

Fanon Electric Co. moved to 150-09 South Road, Jamaica, N. Y.

Telematic Industries is now located in larger quarters at 16 Howard Ave., Brooklyn, N. Y.

Business briefs

... Admiral Corp., Chicago, is using "automation"—the use of high-speed robot machines—to assemble automatically part of the chassis in its new line of TV sets.

... NEDA held a banquet and its annual general membership meeting in conjunction with the regional educational seminar for parts distributors at the Baker Hotel in Dallas.

... Gramer-Halldorson Transformer Corp., Chicago, recently held a sales meeting via a 20-station nationwide telephone hookup during which J. M. Blackledge, president of the corporation, addressed his entire sales force in all sections of the country. C. A. Hansen, Distributor Division sales manager, also addressed the reps.

... JFD Manufacturing Co., Brooklyn, N. Y., was issued a U. S. design patent for its Pal line of standoff insulators.

... Capitol Radio Engineering Institute, Washington, D. C., was authorized by the District of Columbia Board of Education to confer the degree of Associate in Applied Science to resident school graduates who complete a specialized course now being offered. **END**

VIDEO TUBES

ELECTRIC COMPANY

AT WHOLESALE

★ 100% GUARANTEED ★

BRANDED! ★ SAME DAY SERVICE!

1A4P29	6BD559	7F859
1A749	6BE639	7J759
1B359	6BG699	7K759
1B4P79	6BH649	7U549
1C629	6BJ649	7Z439
1C729	6BK769	12AL539
1E7GT39	6BL769	12AT639
1F5G29	6BN699	12AT769
1H549	6BQ679	12AU639
1L449	6BQ779	12AU759
1L659	6BY5G59	12AV639
1LA639	6BZ779	12AV769
1LC539	6C439	12AX759
1LC639	6CB649	12BA639
1N549	6CD699	12BA759
1R549	6CU6GT99	12BE639
1S539	6F639	12BH759
1T449	6F769	12SA749
1T5GT69	6J659	12SK749
1U449	6J879	12SN759
1U539	6K639	12SL759
1X259	6L669	12SQ739
2A329	6N669	14S779
2A729	6S439	19BG699
3A799	6S859	19T869
3Q449	6SA749	25BQ679
3Q559	6SD749	25L6GT39
3S449	6SK749	25W4GT39
3V449	6SL759	25Z639
5U439	6SN759	35B539
5V449	6SQ739	35C539
5Y329	6SR749	35W429
5Y449	6T869	35Z329
5Z329	6U869	35Z529
6AB439	6V649	35/5129
6AG549	6W4GT39	3629
6AJ569	6X429	3729
6AK569	6X529	39/4429
6AL539	7A4 XXL39	4929
6AQ549	7A649	50B549
6AS549	7A749	50C549
6AT639	7A849	50L649
6AU639	7AK779	7529
6AV639	7B449	7629
6B779	7B549	7729
6BA649	7B649	8029
6BA759	7B749	117L7GT99
6BC549	7F759	117Z329

Surprise Package of Radio & TV Parts

3 lbs. of parts including resistors, controls, coils, IF cans, etc. Easily worth \$10.00

\$1.95

FREE! with every order of \$20 or more—famous "Oxwall" magnetic screw driver kit. Includes all sizes—Phillips head, long handles to get in those tight spots, etc. 7 screwdrivers in all. May be purchased outright. List value \$4.89 \$1.99 each; 3 for \$5.50.


MINIMUM ORDER \$7.00

25% deposit with order. Balance COD. If full remittance is sent, please include postage. Excess money will be refunded. We have more than 250 types in stock at all times. Order your other needs at similar savings or write for quotations. Quantity users—write for special discounts!

VIDEO ELECTRIC COMPANY
79 CLINTON PLACE
NEWARK, N. J.

ERIE

Complete line of
DISC CERAMICONS

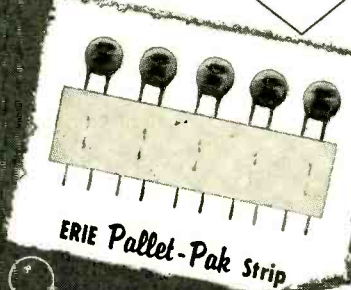

ERIE Pallet-Pak Strip

Initially, limited values and styles of Hi-K By-Pass and Coupling Disc Ceramicons will be offered in the ERIE Pallet-Pak. Further values and styles and High-Stability General Purpose Disc Ceramicons will soon be included in this new packaging. The Pallet-Pak strip will be standard for bulk orders, therefore need not be specified.

Pallet-Pak
... ERIE's new method of packaging popular values of Disc Ceramicons in bulk. Five discs are stapled between the lead wires to hold them between strips of cardboard, keeping the leads straight and holding the capacitors firmly in place. No mixed mass of tangled leads — but orderly, easily handled and identified bulk quantities of identical high quality Generals of ERIE's Ceramicons. Bulk quantities will be supplied with this new packaging at no change in price.

STANDARD STOCK CLASSES

ERIE Disc Ceramicons are available to Distributors in four classes as standard stock: — High Stability General Purpose Ceramicons in a wide range of values, (5 mmf to 1500 mmf) with 10% capacity tolerance, — Hi-K By-Pass and Coupling Ceramicons from 470 mmf to .02 mfd GMV, — Hi-K Dual at 1500, 3000, and 6000 Volts, DC. Working. Characteristic of all classes is smallness of size graduating with increase in capacity value. For complete listing of styles and values available write for D-54 Catalog which includes all ERIE Distributor products.

ERIE components are stocked by leading electronic distributors everywhere.


ERIE
RESISTOR CORP.

ELECTRONICS DISTRIBUTOR DIVISION

ERIE RESISTOR CORPORATION

Main Offices: ERIE, PA.

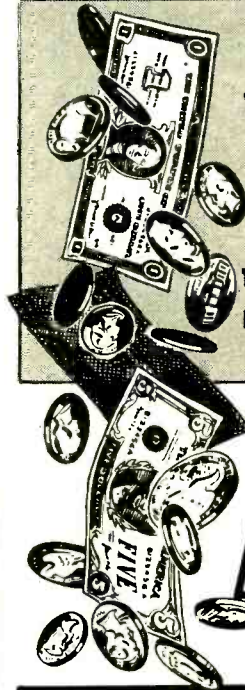Factories: ERIE, PA. • LONDON, ENGLAND • TRENTON, ONTARIO




IT'S LIKE \$\$\$ IN YOUR POCKET
WHEN YOU HAVE OUR BIG 1955

FREE CATALOG!

164 VALUE-LOADED PAGES OF EVERYTHING
IN RADIO, TELEVISION AND ELECTRONICS

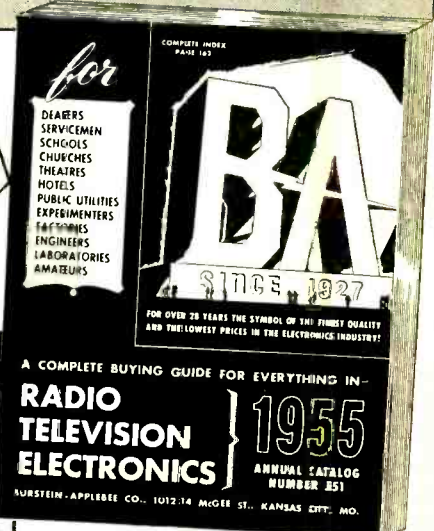FOR 28 YEARS
THE OUTSTANDING
DOLLAR-
SAVING
BUYING GUIDE
IN THE ENTIRE
ELECTRONICS
INDUSTRY!



BURSTEIN-APPLEBEE CO.

BURSTEIN-APPLEBEE CO. Dept. 5,
1012-14 McGee St., Kansas City 6, Mo.

Send Free B-A Catalog No. 551.

Name.....

Address.....

City..... State.....

A COMPLETE BUYING GUIDE FOR EVERYTHING IN
RADIO TELEVISION ELECTRONICS } **1955**
ANNUAL CATALOG
NUMBER 351

BURSTEIN-APPLEBEE CO., 1012-14 MCGEE ST., KANSAS CITY, MO.

SEND FOR IT TODAY!

Color Servicing

IS NOW IN THE FAMOUS
Mandl's TV Servicing


**A MASTER HANDBOOK
FOR ANY SERVICE JOB
A COMPLETE COURSE
IN TV SERVICING**



The new section on color servicing and color circuits gives you the same clear how-to-do-it instruction that has made this book a favorite with servicemen everywhere. You'll be FULLY prepared to service any set, do the best job of installation or trouble shooting in minimum time, either for color or for black and white.

Make your Math EASY!

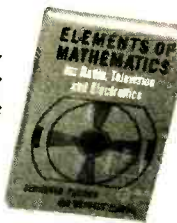You'll find those time-saving equations easy to use, easy to solve with the aid of



Elements of Mathematics for Radio, TV & Electronics

By Bernhard Fischer & Herbert Jacobs

If you've ever hesitated to use a time-saving equation because you were not quite sure how to set it up, or had moments of doubt about decimals or percentages, or wanted a quick check on your figuring—THIS IS THE BOOK FOR YOU. It makes crystal clear each step in the reasoning and each procedure in the arithmetic, geometry, and algebra needed by radio and TV technicians. You'll find it EASY to work out frequency resolutions, voltage drops, inductive reactances, decibels and the many other radio and TV problems in which accurate use of math is essential. Hundreds of sample problems, with answers, give you thorough practice.

10-day FREE TRIAL

The Macmillan Co., 60 Fifth Ave., New York 11

Please send me the books checked below. I will remit full price plus small delivery charge, or return books in 10 days. (Save: Send check or money order and we pay delivery charge)

Mandl's TV Servicing \$5.75 Elements of Mathematics for Radio & TV \$7.20

Signed _____

Address _____

This offer good only within continental limits of U.S.A.

People

Douglas Y. Smith was appointed vice-president and general manager of the Tube Division of R.C.A. He was general marketing manager of the Tube Division since October, 1953.



Charles W. Hosterman was promoted to the newly created position of assistant general manager of Sylvania Electronics Division with headquarters in Woburn, Mass. He was formerly manager of the Sylvania Radio Tube Division's plant in Shawnee, Okla.



John D. van der Veer was appointed assistant general sales manager of Tung-Sol Electric Co., Newark, N. J. He had been manager of initial equipment electron tube sales.



Carl Goudy and Herbert Brown, co-founders of Technical Appliance Corp., Sherburne, N. Y., were presented with



Carl Goudy, board chairman of Taco, receives presentation from A. C. Les-carboursa.

tokens of appreciation by company personnel at a clambake and field day held on the company's 20th anniversary.

Newton Cook was appointed jobber sales manager of Chicago Standard Transformer Corp., Chicago. He is a 20-year veteran in the electronic industry and has spent many years with Chicago Standard. In his new position, he will direct the activities of the Chicago and Stancor Jobber Sales Divisions.



5 NEW TRIAD *CORRECT REPLACEMENT FLYBACKS

These new flybacks are mechanically correct and electrically correct ruggedized versions of manufacturer's items — precisely engineered by TRIAD for specific makes and models — to give exceptionally high performance and long, trouble-free service.

D-40 List Price \$10.25 —
Correct replacement for
Admiral #79C30-2,
79C30-4, 79C38-1,
79038-1.



D-41 List Price \$10.25
Correct replacement for
Admiral #79C30-1 and
79C30-3.



D-42 List Price \$10.25
Correct replacement for
Admiral #79D41-1,
79D41-2, Sheraton
EL-112A, EL-119,
EL-119B and others.



D-43 List Price \$10.25
Correct replacement for
Emerson #738067,
738068, 738069, 738073,
738074, 738075, 738082,
738083, 738085, 738086.



D-44 List Price \$10.25
Correct replacement for
Emerson #738079 and
738084.



WRITE FOR FREE LITERATURE

Triad Transformers are listed in Sam's Photofact folders & Counter-Facts and Riders Replacement Parts List.



4055 Redwood Ave., Venice, Calif.

PEOPLE

(Continued)

Richard T. Orth joined Westinghouse Electric Corp., as vice-president in charge of the Electronic Tube Division, succeeding E. W. Ritter, who continues with the company as a consultant. Orth was formerly a vice-president with RCA and general manager of its tube division.



Julian K. Sprague, president of Sprague Electric Co., North Adams, Mass., was named chairman of the Advisory Group on Electronic Parts of the Department of Defense.

Walter E. Sutter was appointed manager of sales for instruments and industrial electronic products of the Commercial Equipment Department of the General Electric Co., with headquarters at Electronics Park, Syracuse, N. Y. He has been associated with G-E since 1946.

Everett E. Leedom joined Electro-Voice Inc., Buchanan, Mich., as advertising manager. He was formerly with Acme Steel Co. and Warner Press.



Obituary:

Albert M. Margolis, vice-president and treasurer of Almo Radio Co., Philadelphia distributors, and well known throughout the parts industry, passed away recently at the age of 52.

Personnel Notes

... Dr. W. R. G. Baker, General Electric vice-president, was reappointed chairman of the RETMA Television Committee. Robert Sprague, Jr., Sprague Electric Co., was named chairman of the association's Industrial Relations Committee.


... Leon B. Ungar, Ungar Electric Tools Inc., was elected president of the Radio Parts and Electronic Equipment Shows, Inc., sponsors of the annual Electronic Parts Show. Other officers include Elliott Wilkinson, Wilkinson Bros., vice-president; Karl Jensen, Jensen Industries, secretary, and Bernard L. Cahn, Insuline Corp., re-elected treasurer. The 1955 Electronic Parts Show will be held in Chicago, May 16-19.

... Mrs. Helen B. Anderson joined Pyramid Electric, North Bergen, N. J., as a sales engineer. She was previously associated with General Electric as an engineer and technical writer.

... Dr. Donald L. Benedict was named director of physical sciences research of Stanford Research Institute, Stanford, Calif. He was formerly assistant director of the Engineering Division and had served as a consultant to Raytheon Manufacturing Co. **END**


OUTSTANDING for HIGH FIDELITY!
BUY DIRECT AND SAVE
'PRE-FAB' COLLINS TUNERS and RECEIVERS
AUDIO PRODUCTS CO.
NOW!
 with AFC

Each Collins Tuner Kit is complete with punched chassis, tubes, power transformer, power supply components, hardware, dial assembly, tuning eye, knobs, wire, etc., as well as the completed sub-assemblies: FM tuning units, AM tuning units, IF amplifiers, etc., where applicable. All sub-assemblies wired, tested and aligned at the factory make Collins Pre-Fab Kits easy to assemble even without technical knowledge. The end result is a fine, high quality, high fidelity instrument at often less than half the cost—because you helped make it and bought it direct from the factory.

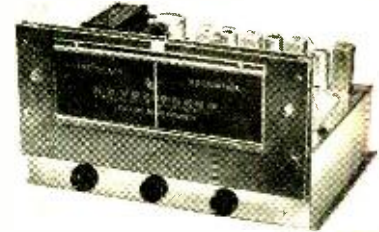

FM Tuner Kit
\$55
 with AFC \$58.50


The FM-11 tuner is available in kit form with the IF Amplifier mounted in the chassis, wired and tested by us. You mount the completed RF Tuning Unit and power supply, then after some simple wiring, it's all set to operate. 11 tubes: 6J6 RF amp, 6AG5 converter, 6C4 oscillator, 6BA6 1st IF, (2) 6AU6 2nd and 3rd IF, (2) 6AU6 limiters, 6AL5 discriminator, 6AL7-GT double tuning eye, 5Y3-GT rectifier. Sensitivity 6 to 10 microvolts, less than 1/2 of 1% distortion, 20 to 20,000 cycle response with 2DB variation. Chassis dimensions: 12 1/2" wide, 8" deep, 7" high. Illustrated manual supplied. Shipping weight 14 lbs.

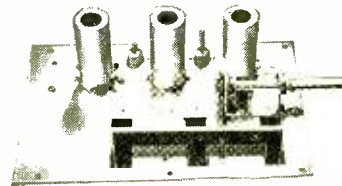

FMF-3 Tuning Unit
\$15.25
 with AFC \$18.75

The best for FM. The most sensitive and most selective type of "front end" on the market. 6 to 10 microvolts sensitivity. Image ratio 500 to 1. 6J6 tuned RF stage, 6AG5 converter, 6C4 oscillator. Permeability tuned, stable and drift-free. Chassis plate measures 6 1/2" x 4 1/2". In combination with the IF-6 amplifier, the highest order of sensitivity on FM can be attained. Tubes included as well as schematic and instructions. Draws 30 ma. Shipping weight FMF-3: 2 1/2 lbs. Dial available @ \$3.85.

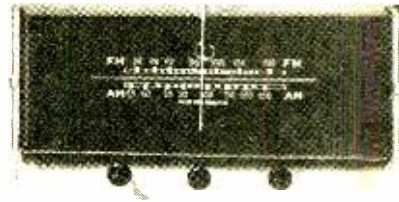IF-6 Amplifier
\$19.75
 6 Tubes, Shipping Wgt. 3 lbs.



FM/AM Tuner Kit
\$77.50
 with AFC \$81.00

The original 15 tube deluxe FM/AM pre-fab kit redesigned on a smaller chassis. The tuner now measures 14" wide by 12" deep by 7 1/2" high. This attractive new front and dial assembly opens up new applications where space is at a premium. Kit includes everything necessary to put it into operation—punched chassis, tubes, wired and aligned components, power supply, hardware, etc. Kit comprises FMF-3 tuning unit, IF-6 amplifier, AM-4 AM tuning unit, magic eye assembly and complete instructions. All tubes included. Shipping weight 19 lbs.



AM-4 Tuning Unit
\$24.50

Tops in AM superhet performance! A 3-gang tuning condenser gives 3 tuned stages with high sensitivity and selectivity. Assembly is completely wired, tested and aligned ready for immediate use. Frequency coverage 540 KC to 1650 KC at a sensitivity of 5 microvolts. Tubes 6BA6 RF amplifier; 6BE6 converter; 6BA6 IF amplifier and 6AT6 detector. Draws 30 ma @ 220 volts. Mounts on a chassis plate measuring 4" x 7 3/8". Shipping weight 2 1/2 lbs. Dial available at \$3.85.

FOR USERS OF COLLINS TUNERS:

Receive \$5.00 credit toward the new FMF-3A front end! Mail us your old front end with \$13.75 and we will send you the new, improved FMF-3A with AFC, or, remit the full amount of \$18.75 and when we receive your old unit in return a check will be mailed you for \$5.00.



To: Collins Audio Products Co. Inc. RE-11
 P.O. Box 348, Westfield, N. J.
 Tel. Westfield 2-4290

FM Tuner Kit FM/AM Tuner Kit FMF-3 Tuning Unit
 with AFC with AFC with AFC

IF-6 Amplifier AM-4 Tuning Unit

NAME

ADDRESS

CITY STATE

Amount for Kit \$ See weights, add shipping cost \$

Total amount enclosed \$ Check Money Order

WHEN YOU THINK OF TUNERS, THINK OF COLLINS AUDIO PRODUCTS

The Finest UHF Converter Ever Designed



Ultravert OUTPERFORMS ALL OTHERS IN THE FIELD

\$39.95

LIST

- ✓ Precise Impedance Match
- ✓ Higher Gain
- ✓ Lower Noise Factor
- ✓ Automatic 'on/off'
- ✓ Dual Speed Tuning

Check with your supplier today.
Also ask about the Model '99'
at \$19.95 . . . or write Dept. WL-3

B-LONDER-TONGUE LABORATORIES, INC.
Westfield, New Jersey

TOP QUALITY TUBES ONE YEAR GUARANTEE BELOW MFRS' PRICES!

A WORD TO THE WISE: "JUNK is the MOST EXPENSIVE Thing You Can Buy!"
Junk is NEVER a Bargain. . . . Price alone is not enough . . . a REAL Bargain is a combination of Price AND Quality: LOW Price and HIGH Quality! On the basis of QUALITY and DEPENDABILITY, Electron Tube Wholesalers offer the LOWEST TUBE PRICES on the market today!

Type	Price
0A2	.89
0A2 VR75	.99
0B2	.79
0B3 VR90	.95
0C3 VR105	.98
0D3 VR150	.89
0Z4	.54
1A5GT	.43
1A7	.53
1A8S	.39
1AX2	.59
1B3	.69
10BGT	.77
1G6GT	.54
1M5GT	.43
1J6G	.49
1L4	.49
1LA4	.59
1LA6	.79
1LB4	.79
1LC5	.59
1LC6	.79
1LDS	.59
1LE3	.78
1LG5	.77
1LH4	.78
1LN5	.57
1NS	.61
1P8GT	.56
1Q5GT	.57
1R5	.54
1S4	.58
1S5	.45
1S6	.48
1T4	.53
1U4	.53
1U5	.39
IV	.69
1V2	.50
1X2A	.59
2A3	.95
2A4G	.99
2A6	.49
2A7	.84
2B7	.64
2X2	.39
2X2A	1.85
3A5	.42
3A5	.90
3A8	.60
3B6	.39
3D6	.39
3LF4	.79
3Q4	.55

Type	Price
3Q5GT	.69
3S4	.56
3V4	.58
5T4	1.28
5U4G	.55
5V4	.82
5Y3GT	.39
5Z3	.44
6A3	.89
6A5	.51
6A7	.67
6A8	.51
6AB4	.75
6AC5GT	.99
6AC7	.89
6AF4	.89
6AF6	.75
6AG5	.56
6AG7	.95
6AM6	.89
6AJ5	.89
6AK5	.79
6AL5	.41
6AL7	.89
6AM8	.69
6AQ5	.49
6AR5	.45
6A55	.48
6AT6	.41
6AU6	.46
6AV5	.79
6AV6	.34
6AX4GT	.59
6B7	.95
6B8G	.82
6B8	.99
6BAG	.49
6BA7	.56
6BC7	.54
6BD6	.49
6BE6	.36
6B6G	1.24
6BM6	.48
6BZ6	.49
6BK7A	.96
6BL7GT	.89
6BN6	.79
6BQ6	.95
6BQ7A	.92
6BZ7	.92
6C5	.41
6CS	.39
6CG6	.57

Type	Price
6C8G	.85
6CB6	.57
6CD6	1.49
6E4	.64
6CS6	.59
6D6	.69
6D8G	.98
6E2	.48
6F5	.39
6F6	.45
6F7	.95
6FR6	.69
6G6G	.65
6H6	.32

Type	Price
6H7GT	.50
6J6	.50
6K7	.49
6L7GT	.59
6M7GT	.59
6Q7	.45
6R7	.45
6S7	.60
6T7	.45
6U7	.95
6V7	.79
6W7	.79
6X7	.45
6Y7	.45
6Z7	.62
7A7	.65
7B7	.75
7C7	.85
7D7	.85
7E7	.85
7F7	.85
7G7	.85
7H7	.85
7J7	.85
7K7	.85
7L7	.85
7M7	.85
7N7	.85
7O7	.85
7P7	.85
7Q7	.85
7R7	.85
7S7	.85
7T7	.85
7U7	.85
7V7	.85
7W7	.85

Type	Price
7C5	.49
7C7	.65
7E5	.59
7E7	.59
7F7	.65
7F8	.65
7F9	.65
7G7	.75
7H7	.75
7J7	.75
7K7	.75
7L7	.75
7M7	.75
7N7	.75
7O7	.75
7P7	.75
7Q7	.75
7R7	.75
7S7	.75
7T7	.75
7U7	.75
7V7	.75
7W7	.75

Type	Price
12BA6	.49
12B6	.39
12BH7	.59
12B7	.69
12B8	.65
12C8	.58
12C7	.58
12D7	.58
12E6	.45
12E7	.45
12F6	.45
12F7	.45
12G6	.45
12G7	.45
12H6	.45
12H7	.45
12J6	.45
12J7	.45
12K6	.45
12K7	.45
12L6	.45
12L7	.45
12M6	.45
12M7	.45
12N6	.45
12N7	.45
12O6	.45
12O7	.45
12P6	.45
12P7	.45
12Q6	.45
12Q7	.45
12R6	.45
12R7	.45
12S6	.45
12S7	.45
12T6	.45
12T7	.45
12U6	.45
12U7	.45
12V6	.45
12V7	.45
12W6	.45
12W7	.45
12X6	.45
12X7	.45
12Y6	.45
12Y7	.45
12Z6	.45
12Z7	.45

THIS MONTH'S SPECIALS

Our new policy brings you greater tube savings than you thought possible! As a GOODWILL offering, we are giving, each month, a number of popular tube types (listed in extra bold) AT PRICES BELOW OUR OWN COST! Look for these terrific offers of different types each month, in industry-wide publications.

Type	Price	Type	Price
6A55	.48	6V3	1.02
6A76	.41	6V4	.70
6B16	.46	6V6GT	.47
6B27	.49	6V7A	.45
6B36	.49	6V7B	.45
6B47	.49	6V7C	.45
6B57	.49	6V7D	.45
6B67	.49	6V7E	.45
6B77	.49	6V7F	.45
6B87	.49	6V7G	.45
6B97	.49	6V7H	.45
6C07	.49	6V7I	.45
6C17	.49	6V7J	.45
6C27	.49	6V7K	.45
6C37	.49	6V7L	.45
6C47	.49	6V7M	.45
6C57	.49	6V7N	.45
6C67	.49	6V7O	.45
6C77	.49	6V7P	.45
6C87	.49	6V7Q	.45
6C97	.49	6V7R	.45
6D07	.49	6V7S	.45
6D17	.49	6V7T	.45
6D27	.49	6V7U	.45
6D37	.49	6V7V	.45
6D47	.49	6V7W	.45
6D57	.49	6V7X	.45
6D67	.49	6V7Y	.45
6D77	.49	6V7Z	.45
6D87	.49	6V8	.45
6D97	.49	6V9	.45
6E07	.49	6V10	.45
6E17	.49	6V11	.45
6E27	.49	6V12	.45
6E37	.49	6V13	.45
6E47	.49	6V14	.45
6E57	.49	6V15	.45
6E67	.49	6V16	.45
6E77	.49	6V17	.45
6E87	.49	6V18	.45
6E97	.49	6V19	.45
6F07	.49	6V20	.45
6F17	.49	6V21	.45
6F27	.49	6V22	.45
6F37	.49	6V23	.45
6F47	.49	6V24	.45
6F57	.49	6V25	.45
6F67	.49	6V26	.45
6F77	.49	6V27	.45
6F87	.49	6V28	.45
6F97	.49	6V29	.45
6G07	.49	6V30	.45
6G17	.49	6V31	.45
6G27	.49	6V32	.45
6G37	.49	6V33	.45
6G47	.49	6V34	.45
6G57	.49	6V35	.45
6G67	.49	6V36	.45
6G77	.49	6V37	.45
6G87	.49	6V38	.45
6G97	.49	6V39	.45
6H07	.49	6V40	.45

EXPORT INQUIRIES INVITED!
New Complete Listing—Send For Free Copy!

ELECTRON TUBE WHOLESALERS, INC.
140 DUANE STREET • NEW YORK 13, N. Y. • Phone: Barclay 7-7616

Minimum order \$40. Prices include 25% deposit with order. All prices F.O.B. our warehouse, N.Y.C. WRITE FOR TYPES NOT LISTED

OPPORTUNITY ADLETS

Rates—45¢ per word (including name, address and initials). Minimum ad 10 words. Cash must accompany all ads except those placed by accredited agencies. Discount, 10% for 12 consecutive issues. Misleading or objectionable ads not accepted. Copy for Jan. issue must reach us before Nov. 15, 1964.

Radio-Electronics
25 W. Broadway, New York 7, N. Y.

SPEAKER REPAIRS ON ALL MAKES. 8" & 12" HI-FI speakers for sale. Amprite Speaker Service, 70 Vesey St., New York 7, N.Y.

ALL MAKES TEST EQUIPMENT REPAIRED—bits constructed. Free information. Buelow Electronics, Pioneer Road, Beulah, Michigan.

SPEAKER RECONING: Guaranteed workmanship. C&M Recone Co., 255 Tioga St., Trenton 9, N.J.

OCTO-TENNA. Most efficient antenna made. \$4.95. Guaranteed. Derr, 1018 Taylor, Vallejo, California.

DIAGRAMS FOR REPAIRING RADIOS \$1.00, Record Changers \$1.50, Television \$2.00, Give Make, Model. Diagram Service, 672-RE, Hartford 1, Conn.

TEST EQUIPMENT Repaired by Factory Staff. All makes, Hickok, Simpson, Triplett, Heath, etc. Prompt service at low factory prices. Our nineteenth year. Free estimate. Douglas Instrument Laboratory, 1764 Norfolk Avenue, Boston 19, Mass.

NOW AT LAST. A pocket F.M. radio self-contained tunes 87.5 to 108.5 MC, plays \$1.00 self-addressed envelope, 6000 mile range subminiature set, 355 kc to 16 meters plans 50c and self-addressed envelope. Beginners broadcast kit with subminiature tube, less batteries and phone. \$5.95 postpaid, P.S. Only 25¢ deposit on all C.O.D. orders. Ekeradio, 646 N. Fair Oaks Ave., Pasadena, California.

HI FI BARGAINS COLLARD 3-822 INTERMIX 45 Spindle-dual ceramic cartridge-mounting board—\$36.95 PREPAID. CRESCENT TRIMOMATIC dual cartridge-automatic shut-off-mounting board \$24.95 PREPAID. LOW PRICES—Cartridges, tuners, etc. WRITE TODAY. FIDELITY UNLIMITED, 63-03 39 Ave., Woodside, N.Y.

MAKE MONEY, buy a 25 cents coin operated meter and install on a TV, washer, dryer, etc. Complete \$69.00 with instructions. Send money to GARRY TV, 11 Atlantic Ave., Brooklyn, N.Y.

TUBES—TV, RADIO, TRANSMITTING, AND SPECIAL PURPOSE TYPES BOUGHT, SOLD AND EXCHANGED. Send details to B. N. Gensler W2LNI, 136 Liberty, N. Y. 6, N. Y.

ALL MAKES OF ELECTRICAL INSTRUMENTS AND TESTING equipment repaired. Write for free catalogue on new and used instruments at a savings. Hazleton Instrument Co., 128 Liberty Street, New York, N. Y.

BUILD YOUR OWN ELECTRONIC ORGAN. Sample Circuit 25¢. Jim Kirk, W6JJK, 1552 Church Street, San Francisco 14, Calif.

"RADIOBUILDERS" Magazine for Experimenters, beginners. 12 issues \$1.50. Copy 15¢. Unusual Catalog free. Laboratories, 328-B Fuller, Redwood City, Calif.

WANTED: AN/APR-4, other "APR", "TS-", "IE-", ARC-1, ARC-2, AHT-13, B-248, etc. Microwave Equipment. Everything Surplus. Special tubes. Test Manuals. Lab Quality Equipment, Meters, Fast Action, Fair Treatment. Top Dollar! Littell, Fairhills Box 26, Dayton 9, Ohio.

BUY WHOLESALE—25,000 items—Catalog 25¢. Matthews, 1472-P2 Broadway, NYC 36.

SPEAKER RECONING: 25 years experience, Michigan Speaker Reconing Service, 930 Metropolis, Marine City, Michigan.

TEST EQUIPMENT FOR SALE. Slightly used, perfect condition: Heath V-4A VTVM \$18.00, Elco 320 Signal Generator \$15.00, Elco 425 Oscilloscope \$32.00, Robert Moore, K2AMH, 51-09 Parsons Blvd., Flushing 55, N.Y.

Power Transformers Rebuilt: all makes, Victor Re-2—\$12.95, Red Arrow Radio, 924 Metropolis, Marine City, Michigan.

ALUMINUM TUBING. Angle and Channel, Plain and Perforated Sheet, Willard Radcliff, Fostoria, Ohio.


25-50% DISCOUNT, guaranteed Factory Fresh LP records; 63c and up; pre-recorded tapes. Send 20c for catalogue. SOUTHWEST RECORDS, 4710 Caroline, Houston 4, Texas.

TELEVISION RECEIVERS \$30 UP. WAJPI, 1420 South Randolph, Arlington 4, Virginia.

Code practice electronic oscillators, new, guaranteed \$4.00. Keys \$2.00 Postpaid, Details free. C. Stout, 2241 E. Broadway, Muskegon, Michigan.

TV FM ANTENNAS, ALL TYPES INCLUDING UHF. Mounts, accessories. Lowest prices. Wholesale Supply Co., Lunenburg 2, Mass.

technical Literature

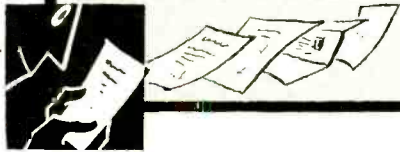

INTERFERENCE MEASUREMENT

Empire Devices has issued a 6-page catalog which describes noise meters, distortion analyzers, impulse generators, attenuators, and crystal mixers.

Included are engineering specifications on noise and field-intensity meter models NF-105 and NF-114. The catalog also gives technical data on noise and distortion analyzer ND-110. Additional

Any or all of these catalogs, bulletins, or periodicals are available to you on request direct to the manufacturers, whose addresses are listed at the end of each item. Use your letterhead—do not use postcards. To facilitate identification, mention the issue and page of RADIO-ELECTRONICS on which the item appears. UNLESS OTHERWISE STATED, ALL ITEMS ARE GRATIS. ALL LITERATURE OFFERS ARE VOID AFTER SIX MONTHS.

items covered in the catalog are step attenuators, u.h.f. attenuators, and a broad-band crystal mixer.

Empire Devices Products Corp., 58-15 Bell Blvd., Bayside 61, N. Y.

HOUSE ORGAN

EICO is now putting out a house organ called "The EICO News Bulletin," a bimonthly publication that describes sales and technical facts. Humor, Dale Carnegie philosophy, and general human-interest material are also included.

Electronic Instrument Co., Inc., 84 Withers St., Brooklyn 11, N. Y.

SERVICE PARTS DIRECTORY

A 36-page service parts directory, SP-1021, offers basic service and parts-replacement data for all 1952-model RCA home television receivers. It contains schematic and wiring diagrams, parts lists, and top and bottom chassis views for 27 different table models and console receivers. The television receivers are indexed by model name and number for quick identification and location. Also included is a special cross-reference which identifies by model name and number all RCA receivers produced between 1946 and 1952, and indicates previously issued service parts directories in which they are described. The SP-1021 features spread-out easy-to-read schematics.

RCA electronic parts distributors or Commercial Engineering Dept., RCA Tube Division, Harrison, N. J. 50 cents.

TRANSFORMERS

Chicago Standard Transformer has issued a new transformer catalog, CT-554. This 32-page book contains detailed descriptions of over 500 stock transformers for military, new equipment, general replacement, and power and control circuit applications. A simplified classification system makes it easy to locate any particular unit, and

SAVE MONEY... MAKE MONEY...

LEARN TV

the practical way--

17", 21" and 27"

ASSEMBLE A
TRANSVISION TV KIT

Pay as You Wire \$ **39**

Down Payment

WE WILL HELP YOU to start learning TV the practical way -- by assembling a TRANSVISION TV KIT in EASY STAGES. For only \$39 you get PACKAGE #1 (standard first pkg. for all of our kits). This package gives you the BASIC CHASSIS and over 450 TV COMPONENTS with complete instructions, drawings, photos, and Service Booklet. When ready, you order the next stage (pkg. #2), etc. Low prices make your complete kit a terrific buy.



Low prices make your complete kit a terrific buy.

Shows 6 Great TV Kits:

EXCLUSIVE: Only Transvision TV Kits are adaptable to UHF. Ideal for FRINGE AREAS. No Previous Technical Knowledge required. Write now!

FREE CATALOG

TRANSVISION
THE OLDEST NAME IN TV

NEW ROCHELLE, N. Y.

MAIL THIS COUPON TODAY

Educational Director

TRANSVISION, INC., NEW ROCHELLE, N. Y. Dept. FE-11

I'm enclosing \$_____ deposit. Send standard kit PACKAGE #1, with all Instruction Material. Balance C.O.D.

Send FREE copy of your new TV Kit Catalog.

Name _____

Address _____

City _____ State _____


WATCH FOR OUR ANNUAL INDEX

in the December Issue

A genuine *Regency* 12 watt combination amplifier and pre-amplifier for high fidelity at moderate cost.

Model HF 150 • \$99.50 net from your dealer.

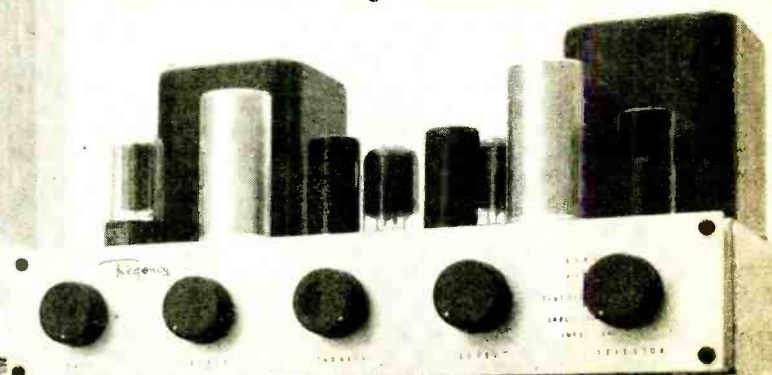Regency makes a complete line of high fidelity amplifiers and tuners from one thousand dollars to about seventy dollars.



Mr. Serviceman
check these
items for...
Value!



See your local
Parts Jobber



Align-o-Pak
ONLY all elec-
tronic isolated bias
supply
Model BE2
Eliminates TV
Alignment Bias
Batteries. Provides
voltages recom-
mended by all TV
manufacturers.
Quickly diagnoses
AGC trouble.

\$7.85

UHF HI-PASS FILTER



Model HP2

Passes UHF, rejects
VHF up to 50 DB
without tuning.
Eliminates FM,
Airport, Taxi cab
interference, etc.

\$2.37



Up-Down
VOLTAGE
BOOSTER

Model LB2

Adds or subtracts
10 volts line vol-
tage with heavy,
safe toggle switches
for any TV set. Line
restored to normal
when turned off.

YOUR COST... \$5.97
Model—LB2-N—with
protective new NEON
INDICATOR which
glows at 126 volts
—\$7.17.

PEAK-TO-PEAK Comparison Meter



Add peak-to-peak measurements to
your scope for only **\$8.75**
Handy for servicing gated AGC, gated
sync separator, and essential for color.

Write for Additional Information

SERVICE INSTRUMENTS CO.
422 So. Dearborn—Chicago 5

TECHNICAL LITERATURE (Continued)

the dimensions of all cased units are shown.

Almost 100 new transformers are listed, including many not previously available as stock units. These include military, standard transformers, hermetically sealed 400-cycle transformers, and molded toroidal inductors. High-fidelity transformers, miniature audio transformers, and ultra-miniature transistor transformers are some of the other new units listed.

Chicago Standard Transformer Corp.,
3501 Addison St., Chicago 18, Ill.

CAPACITORS

Folder AB-19A contains technical data and operating characteristics of Astron *Hy-Met* high-temperature metal-ite metalized paper capacitors. It provides information on the types of *Hy-Met* available and gives their capacitance stability, voltage rating and de-rating, and other characteristics.

Folder AB-18A contains all pertinent information on *Meteor* capacitors. Also shown are accessories, mounting hardware, and constructional variations available to meet individual requirements.

Folder AB-20B gives technical information on the *Blue Point* type of molded plastic paper capacitors.

Astron Corporation, 255 Grant Ave.,
East Newark, N. J.

DISC RESISTORS

Bulletin T-1 on resistance strips and concentric disc resistors gives data on construction, tolerances, resistance values, power and voltage ratings, dimensions, machining techniques, temperature coefficients, and voltage coefficients. It contains charts and graphs.

International Resistance Co., 401 No.
Broad St., Philadelphia 8, Pa.

AUDIO EQUIPMENT

Catalog 55 describes microphones, accessories, magnetic recording heads, and phono pickup cartridges. It also contains cartridge and recording-head replacement charts. Catalog 33 describes the new *Concert-Line 333* studio microphone.

Shure Brothers, 225 W. Huron St.,
Chicago, Ill.

TV ANTENNAS

A catalog, "Ward Antenna Rama," illustrates and describes v.h.f. and u.h.f. TV antennas. *Tele-Vane*, *Dymon-Vane*, and *Circle-Vane* Yagi antennas are also described.

Available to distributors and dealers from Ward Products Corp., Division of the Gabriel Co., 1148 Euclid Ave., Cleveland, Ohio.

ELECTRIC PLANT

A 16-page booklet with many photographs, entitled "Power Points Digest," describes how Onan electric plants are used as emergency standby units, for contractors' portable power needs, as magnet chargers for cranes and trucks, and for primary power for a display coach.

D. W. Onan & Sons Inc., Minneapolis,
Minn. **END**

METERS:




WESTON AC AMMETER
(Pictured) in portable leather case,
with Test Leads, 2 1/2" x 3 1/2" x 2 1/2"
0-15 AC & 0-3 AC Scale **\$9.95**
DC AMMETER HOYT—
in portable metal case, with Test
Leads, 4 1/2" Fan, Mir-
rored Scale 0-15 ADC. **\$4.95**

0-500 MICROAMMETER TRIPLET, 2 1/2" Sq. **\$4.95**
0-5 MA DC WESTINGHOUSE, 2 1/2" Sq. **\$3.95**
D-B METER—10 to Plus 6, G.E., 3 1/2" Rd. **\$4.95**
TS-291/V VOLTOHMETER—Meter 3" square, 1000
ohms per volt, D'Arsonval Movement—0/300/600 VDC
Scale and 0-1 Meg. Case size: 3 1/2" x 5 1/2" x 2 1/4"
W/Test Leads 17/0 1-56 Test Set **NEW: \$7.95**

SOUND POWERED HEAD AND CHEST SET—Navy Type—No batteries re-
quired—Ideal for TV antenna
installations and many other uses. 20 Ft. Cord.
Used—Tested **\$3.95 Ea.**

AERIAL WIRE—Phosphor Bronze #16 Strand-
ed, 200 lb. test. Weatherproof, 150
Feet on Reel. RL-3 with Clips **\$1.50**

TG-34A KEYS

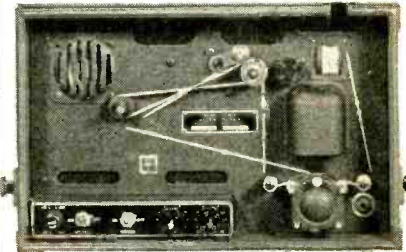

PORTABLE—115 or 230 V. @ 50 to 60 cycles—
KEYER TG-34A is an automatic unit for re-
producing audible code practice signals previously
recorded in ink on paper tape. By use of the
self contained speaker, the unit will provide
code practice signals to one or more people
or provide a keying oscillator for use with a
hand key. The unit is compact, in portable
carrying case, and complete with tubes, photo
cell, and operating manual. Size: 10 1/8" x 10 1/2"
x 15 1/8". Shipping weight: 45 lbs. **PRICES:**
BRAND NEW: \$22.95 • USED: \$14.95

TG-10 KEYS: Same function as TG-34A,
only larger, using 2/6N7—2/6L6—2/6SJ7—1/5U4G
Tubes and 1/923 Photo Cell. Housed in standard
Metal Cabinet, can be removed for 19" rack mts.
Size 11" H x 24" W x 18 1/2" D.

— USED, TESTED: \$19.95

Address Dept. RE • Minimum Order \$5.00
Prices F. O. B. Lima, O. 25% Deposit on C. O. D. Orders

FAIR RADIO SALES
132 SOUTH MAIN ST. • LIMA, OHIO

SUBSCRIBERS

If you're moving, please
don't forget to send us your
address as it appears on the
copy of the magazine, includ-
ing the numbers shown be-
side your name, as well as
your new address.

If we receive this informa-
tion before the 20th of the
month, you will continue get-
ting the magazine without
interruption.

Your cooperation will be
most helpful and greatly ap-
preciated.

RADIO SCHOOL DIRECTORY

MORE JOBS than graduates

Demand for our engineering graduates exceeds supply. *Effective placement.* Study in this world-famed college established 1884. Quarters start January, March, June, September. *Approved for Korean Vets.*

Bach. Sc. degree in 27 months
Complete Radio Eng. courses . . . TV, UHF and FM. Also Mech., Civil, Elec., Chem., Aero. and Adm. Eng.; Bus. Adm., Acct. Small classes. Well-equipped labs. Modest costs. Prep. courses. Write *Jean McCarthy, Director of Admissions, for Catalog and Campus View Book.*



TRI-STATE COLLEGE

2414 College Avenue, Angola, Indiana

TELEVISION

PREPARE FOR A GOOD JOB!

BROADCAST ENGINEER
ELECTRONICS
RADIO SERVICING

Television Servicing

(Approved for Veterans)

SEND FOR FREE LITERATURE

BALTIMORE TECHNICAL INSTITUTE
1425 EUTAW PLACE, BALTIMORE 17, MD.

GET INTO ELECTRONICS

You can enter this uncrowded, interesting field. Defense expansion, new developments demand trained specialists. Study all phases radio & electronics theory and practice: TV, FM, broadcasting, servicing, aviation, marine, police radio. 18-month course. Graduates in demand by major companies. H.S. or equivalent required. Begin Jan., March, June, Sept. Campus life. Write for catalog.
VALPARAISO TECHNICAL INSTITUTE
Dept. C Valparaiso, Ind.



TV REPAIRMEN EARN TOP MONEY!

IN JUST 12 MONTHS, COMPLETE TV SERVICE TRAINING, INCLUDING COLOR TV. Stream-lined course gives you all essentials for a good job as service technician. Graduates in great demand; jobs are plentiful in this growing field. Other electronic courses in radio operation and maintenance. Day or evening classes. Opportunity for employment in local industry. Approved for Korean veterans.

Write for Catalog 111 Today

INDIANAPOLIS ELECTRONIC SCHOOL
312 E. Washington, Indianapolis 4, Ind.

RADIO ENGINEERING DEGREE IN 27 MONTHS

Intensive, specialized course including strong basis in mathematics and electrical engineering, advanced radio theory and design, television. Modern lab. Low tuition. Self-help opportunities. Also B.S. degree in 27 months in Aeronautical, Chemical, Civil, Electrical, and Mechanical Engineering. G.I. Gov't approved. Enter December, March, June, September. Catalog.

INDIANA TECHNICAL COLLEGE

1511 E. Washington Blvd., Fort Wayne 2, Indiana

Watch for the
December Issue of
RADIO-ELECTRONICS
on Sale Nov. 23

Electronic Engineers
Excellent opportunity for professional growth and advancement in interesting and important work.

Get Your F.C.C. LICENSE Quickly!

Correspondence or residence preparation for F.C.C. examinations. Results guaranteed.

An FCC commercial operator license means greater opportunities and higher pay. We are specialists in preparing you, in a MINIMUM OF TIME, to pass FCC examinations for all classes of licenses. Beginners get 2nd class license in 5 weeks and 1st class in 3 additional weeks. Write for free booklet.

GRANTHAM School of Electronics

Dept. 101, 6064 Hollywood Blvd., Hollywood 28, Calif.

**CODE SENDING
RECEIVING SPEED**

Be a "key" man. Learn how to send and receive messages in code by telegraph and radio. Commerce needs thousands of men for jobs. Good pay, adventure, interesting work. Learn at home quickly through famous Candler System. Quality for Amateur or Commercial License. Write for FREE BOOK.
CANDLER SYSTEM CO.
Dept. 3-M, Box 928, Denver 1, Colo., U.S.A.



RCA INSTITUTES, INC.

A service of Radio Corporation of America
350 West 4th St., New York 14, N. Y.

OFFERS COURSES IN
ALL TECHNICAL PHASES OF
RADIO, TELEVISION, ELECTRONICS

Approved for Veterans
Write Dept. RE-54 for Catalog

**EARN MORE MONEY—
BE A PROFESSIONAL
TELEVISION
SERVICE
TECHNICIAN**

HOW TO BE A SUCCESSFUL TELEVISION TECHNICIAN

STEP INTO THE TOP PAY
\$5,000—\$10,000 A YEAR
CLASS. 8 MONTHS' SHOP
TRAINING QUALIFIES YOU.

If you want to reach your goal as a Successful Service Technician you will need plenty of "KNOW HOW" to qualify for the better servicing jobs or profitable shop ownership.

SEND FOR
FREE
BOOK TODAY!

WESTERN TV offers real experience on live equipment in our BIG SHOPS AND LABORATORIES in the shortest practical time under expert instructors. Graduates are in big demand because they have the "field experience" necessary for immediate "bench" or supervisory positions. You learn every phase of Radio and TV servicing (AM, FM, VHF, UHF). WTI men win fast promotion . . . can demand better pay . . . develop highly profitable businesses of their own with the latest and most PRACTICAL PERSONALIZED TRAINING BEHIND THEM. You concentrate all your time on being a PROFESSIONAL TV SERVICE TECHNICIAN — non-essential math and engineering theory omitted. YOU CAN EARN WHILE YOU LEARN. Special Finance Plan.

APPROVED FOR VETERANS. Find out how you can get into the TOP PAY GROUP — Send for this fact-packed book NOW!

WESTERN TELEVISION INSTITUTE


America's Leading
Television
Servicing School

Western Television Institute Dept. E-12-4
341 W. 18th St., Los Angeles 15, Calif.
Without obligation, please send FREE fully illustrated booklet. (No salesman will call.)

NAME _____ AGE _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____

Become an

ELECTRICAL ENGINEER

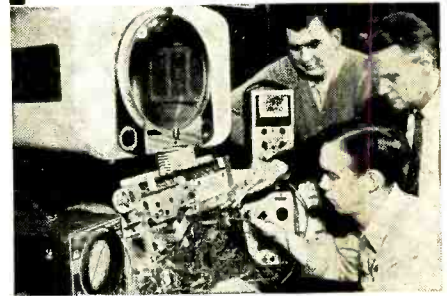

Major in Electronics or Power BS Degree in 36 months

Prepare now for a career as an electrical engineer or engineering technician — and take advantage of the many opportunities in these expanding fields.

You can save a year by optional year round study. Previous military, academic, or practical training may be evaluated for advanced credit.

Enter Radio and Television — courses 12 to 18 months

You can be a radio technician in 12 months. In an additional 6-months you can become a radio-television technician with Associate in Applied Science degree. Color television instruction is included in this program.

These technician courses may form the first third of the program leading to a degree in Electrical Engineering. Twenty-one subjects in electronics, electronic engineering and electronic design are included in these courses.

Courses also offered: radio-television service (12 mos.); electrical service (6 mos.); general preparatory (3 mos.).

Terms — January, April, July, September

Faculty of specialists. 50,000 former students—annual enrollment from 48 states, 23 foreign countries. Non-profit institution. 51st year. Courses approved for veterans. Residence courses only.

MS-6A



MILWAUKEE SCHOOL OF ENGINEERING

MILWAUKEE SCHOOL OF ENGINEERING
Dept. RE-1154, 1025 N. Milwaukee Street
Milwaukee 1, Wisconsin

Send FREE illustrated booklets
 Career in Electrical Engineering.
 Career in Radio-Television.

I am interested in _____ (name of course)

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

If veteran, indicate date of discharge _____

NEW STOCK OF FIRST QUALITY TELTRON TUBES

GUARANTEED! . . . LOWEST PRICES EVER!

All tubes individually boxed . . . unconditionally guaranteed for one year!

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
1A7GT	.53	5Z3	.42	6BA7	.58	6F5GT	.44	6X8	.80	12SL7GT	.60
1H5GT	.51	6A8	.40	6BC5	.48	6H6	.50	7F8	.49	12SN7GT	.56
1L4	.51	6K7	.40	6BE6	.46	6J6	.61	7N7	.49	19B6G	1.18
1L6	.51	6AB4	.40	6BF5	.48	6J5GT	.49	12AL5	.43	19T8	.71
1LC6	.49	6Q7	.40	6BF6	.48	6K6GT	.39	12AT6	.37	25B6GT	.82
1N5GT	.51	6AC7	.65	6BG6G	1.18	6L6	.78	12AU6	.43	25L6GT	.41
1R5	.51	6AF4	1.02	6BK5	.75	6S4	.31	12AU7	.58	25Z5	.55
1T4	.51	6AG5	.52	6BJ6	.51	6S8GT	.65	12AV6	.42	25Z6GT	.36
1U4	.51	6AH4GT	.65	6BH6	.51	6SA7GT	.45	12AV7	.73	35B5	.48
1U5	.43	6AJ5	.46	6BK7	.78	6SK7GT	.45	12AX4GT	.60	35C5	.48
1X2	.65	6AK5	.96	6BL7GT	.78	6SL7GT	.60	12AX7	.61	35W4	.33
2A3	.35	6AL5	.43	6BN6	.90	6SN7	.60	12AZ7	.65	35Y4	.42
2A7	.35	6AQ5	.48	6BQ7	.85	6SQ7GT	.38	12B1	.72	35Z5GT	.33
3Q1	.53	6AR5	.48	6BY5G	.60	6T8	.71	12BA6	.46	50A5	.49
3Q5GT	.61	6AT6	.37	6BZ7	.95	6U8	.76	12BA7	.58	50B5	.48
3S4	.48	6AUSGT	.60	6C1	.41	6V3	.80	12BE6	.46	50C5	.48
3V4	.48	6AV5GT	.60	6CB7	.51	6V6GT	.46	12BH7	.61	TYPE 80	.40
5Y3G	.49	6AV6	.60	6CD6G	1.63	6W6GT	.53	12BZ7	.63	117Z3	.33
5Y3GT	.30	6AX3GT	.60	6CU6	.95	6X1	.37	12K7	.40	117Z6GT	.65
5Y4G	.40	6AX5GT	.60	6F6	.42	6X5GT	.38				

GIFT OFFER!
One 6BG6G tube will be shipped FREE with any order accompanying this ad.

FREE \$7.20 list value Bonus Box of three 6SN7 tubes and 25 assorted resistors with each order of \$25 or more.

SAME DAY SERVICE

48 Hour Postal Delivery To West Coast

TERMS: Save all freight and postage charges. All orders accompanied by full remittance will be shipped POSTAGE PAID anywhere in the continental U.S.A.

25% deposit required on C.O.D.'s. Minimum order \$10.00. Open accounts to rated firms only.

Send for Free complete tube listing and monthly specials! Get on our mailing list.

TELTRON ELECTRIC COMPANY

428 Harrison Ave.,

Dept. RE-11

Harrison, N. J.


Phone HUmboldt 4-9848

SPECIAL!—till DEC. 1

Type	Price	Type	Price
1B3GT	.35	6T8	.57
5U3G	.40	6W4GT	.35
6AC7	.65	12AT7	.53
6AG5	.44	12AU7	.47
6AL5	.28	12BA6	.36
6AU6	.35	12BE6	.40
6AV6	.34	12BY7	.62
6BA6	.38	12SA7	.43
6BK7	.78	12SK7	.43
6BQ6GT	.75	12SL7GT	.45
6BZ7	.80	12SQ7	.35
6J6	.48	25L6GT	.35
6SN7GT	.48	50L6GT	.49

By popular demand we are repeating the August Specials . . . good until December 1st.

Books

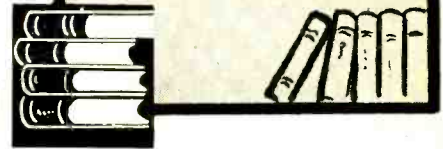

THE MAGIC OF ELECTRONICS, by Edward J. Bukstein. Frederick Ungar Publishing Co., 105 E. 24 St., New York City. 6x9 inches, 256 pages. \$3.95.

In this day of increasingly complex circuitry and equipment it is refreshing to read a technical book written at the layman's level. It also reminds us that there is more to electronics than much-publicized radar and television.

Of the more than 60 "chapters" in the book, Bukstein spends only three discussing fundamentals of electronics. From there—in the straightforward easy-to-read style familiar to RADIO-ELECTRONICS readers—the electronic curtain is pulled aside, and a fabulous assortment of electronic applications is put on display.

Given a thorough review is such diverse equipment as the pyrometer, that regulates both the temperature of furnaces and the constancy of color patterns in textiles; the chromalizer, that teaches deaf children to speak; the radio knife, that makes possible bloodless surgery; equipment that surface-hardens metal parts without flame, and numerous other devices in the fields of medicine, industry, and aviation.

No attempt has been made at an exhaustive analysis—rather, it is the author's intent to give the reader a general idea of the underlying principles in the various applications of electronics.—JK

WORLD RADIO-TELEVISION HANDBOOK (eighth edition). Edited and published by O. Lund Johansen, Lindforsalle 1, Hellerup, Copenhagen, Denmark. Distributed in the United States by Ben E. Wilbur, 47 Mounthaven Drive, Livingstone, N.J. 6½x8½ inches, 136 pages. \$1.50.

The eighth edition of the shortwave listeners' bible has added a television section, containing what appears to be the most complete list of TV stations published to date, together with addresses of their administrative offices.

The shortwave section has been increased in size—due apparently to an increase in broadcasting activity—and indicates the frequency, power, and operating periods of the high-frequency broadcast stations of the world, as well as the medium- and low-frequency stations of most countries.

A table in the front of the book informs the listener of the best frequencies for various times of the day and year, and the information under "Services" of the various countries also gives him hints as to where and when best reception can be expected. The

NEW! All Channel VHF-UHF TV RECEPTION IN ALL DIRECTIONS


SUPER POWERFUL

Only \$23.50

Model AX-524

ROCKET DIRECTRONIC MOTORLESS TV ANTENNA
360° ELECTRONICALLY SWITCHED BEAM

In the fringe or ultra-fringe, the NEW 1954 Motorless Directronic will outperform any ordinary antenna. This sensational new 360° VHF-UHF TV Antenna offers "around the compass" reception WITH-OUT Rotors. Provides superb ghost-free picture clarity. Model AX-524 "Servoless" Array contains 11-Peg Molded Insulator of Extreme tensile strength, 21 hi-tensile aluminum elements, including 6 Multi-purpose Reflector-directors, 1 set matched tie rods, Universal Mast Clamps, Opposition Beam Selector Switch, 75' Low-loss UHF-VHF Tubular TR-X Cable.

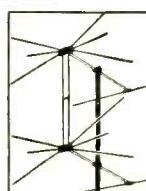

2 BAY 16 ELEMENT CONICAL ARRAY

\$4.99 EACH IN Single Lots
LOTS OF 3 \$5.30 Each

Hi-gain 16-element conical with sturdy 3/8" hi-tensile aluminum elements. For fringe use. Complete coverage of Ch. 2 thru 13. Packed in cartons of three 16-element arrays, per carton, with tie rods, at \$14.95 per carton. Single 16-element array \$ 5.30 no tie rods.


1 carton 6 arrays . . . 13.50
4 bay stacking assembly . . . 1.95
No. 4B

Supreme in the Fringe

NEW ROCKET ULTRA-POWERED FRINGE KING

- Super Broad-band Reception
- Synchronized for Color or Black and White
- Super Front-to-Back Ratio
- Gain: 8 db Low-Band 11 db Hi-band
- Minimum co-channel interference

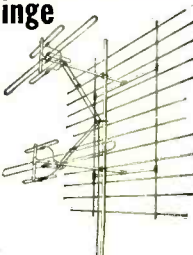The Rocket Fringe King provides a new improved super broad band reception in fringe and deep fringe areas that measurably increases reception pleasure. New design greatly increases uniform antenna response, with very good LIF primary and sub-primary receptivity. Front-to-back ratio higher than multi-channel vags. When installed, we guarantee you can "see" the difference.



Model FK-232 \$23.95 ea.

ALL PRICES F.O.B. CLEVELAND, OHIO
Do not return more than complete purchase price. Pay shipping charges on receipt of goods. 25% deposit on all C.O.D. orders, please. Money-back guarantee. Prices subject to Change Without Notice

National Electronics
OF CLEVELAND
THE HOUSE OF TV VALUES
211 Delco Bldg. Cleveland 3, Ohio

FAMOUS ROCKET ZOOM-UP TOWERS

• Sturdy • Reliable • Easiest Installation
Economize with Rocket Zoom-up Towers. Offers quickest, easiest way to make an installation up to 50'. Each section telescopes inside the other—to erect, simply slide out each section in its turn—insert bolt thru section below—tighten to keep mast from turning. Each tower complete with guy rings, bolts, and mounting base suitable for peak or flat roof. Handsome and sturdy. Rocket Zoom-ups offer you economy and long life. Order by size.

20' \$ 9.95 30' \$15.95
40' 19.95 50' 29.95
(Deduct 10% discount in lots of 3)

NEW LOW PRICE!

RADIART TELEROTOR

Radiart's famous TR-2 at new money-saving price. Powerful, rugged, weather-proof—handles installations up to 150 lbs. Control box light indicates orientation of antenna. Factory lubricated for life. Truly a good buy at our new price. Base 8-round wire, 8 conductor wire \$0.08 Ft.

MODEL TR-2 \$26.97

FOR Fast Alignment AND AGC Troubleshooting




**BOLAND
& BOYCE
MODEL 704
BIAS BOX**

0-17 volts d-c
Only 2 1/4" by
2 1/4" by 4"

Here's the fast, easy way to tackle automatic gain or automatic control circuit troubleshooting and tough re-alignment jobs. The B & B Bias Box supplies steady, accurately adjustable bias voltages from 0 to 17 volts d-c to substitute for the receiver's own AGC circuit. Just clip it to the chassis apron, attach one lead to nearest 6.3 volt heater terminal and the other in place of the usual AGC supply. No external power needed! Includes detailed instructions, all parts, and clips. KIT—Only \$9.95. FACTORY WIRED AND TESTED—\$12.95.

TEST C-R TUBES and RECEIVER CIRCUITS

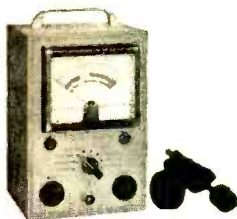

The B & B TV Picture Tube & Receiver Tester connects between C-R Tube and receiver. Measures both C-R tube and receiver performance dynamically in one all-inclusive test. Tells at a glance whether tube or set is at fault.

8-position switch tests: grid-cathode, heater-cathode, & grid-screen leakage; grid-cathode voltages; receiver screen and video output voltages; beam current at HV anode; grid control of beam; effect of brightness and contrast controls; and much more.

Separate 115 v. a-c operated plug-in power supply available for testing tubes while still in their cartons. Prices include 2 cabled leads and detailed instruction manual. KIT—\$29.95. FACTORY WIRED & TESTED—\$39.95.

USE ONE HV PROBE for all meters, all ranges

This B&B Universal High-Voltage Probe accurately extends the range of any VTVM, multimeter, or voltmeter having sensitivities of 10,000 ohms-per-volt or more. Complete with 4 plug-in precision resistors and instructions for matching any meter, any range—10KV, 30KV, 60KV, and many others. With shielded cable and Amphenol connectors. B&B MODEL 702 HV PROBE—\$11.95.



At Leading Distributors Everywhere

Write for Brochure Describing all B&B Products

BOLAND & BOYCE, Inc.

Dept. RE-114, 236 Washington Avenue
Belleville 9, N. J.

BOOKS (Continued)
world station list by frequencies still appears—a great convenience to dx seekers—as well as the station listings under countries.—FS

WORLD RADIO VALVE HANDBOOK, edited and published by O. Lund Johansen, Copenhagen, Denmark. Distributed in the United States by Ben E. Wilbur, Livingstone, N.J. 136 pages. \$1.75.

The subtitle *Receiving Valves of the World, Their Data, Uses, and Interchangeability* sums up the aim and scope of this book. Tubes are listed in alphabetical and numerical order in a type index that refers the reader to a table including all tubes that are equivalents or near-equivalents. Differences in characteristics are covered by footnotes. A second index classifies tubes according to circuit function and construction.

SPECIALIZED AUTO RADIO MANUAL. John F. Rider Publisher, Inc., 480 Canal St., New York, N.Y. Volume 3-A: 123 pages, \$1.80. Volume 5-A: 204 pages, \$3.00.

These are two of a series of volumes of diagrams and servicing data covering all makes and models of radios in 1950-54 automobiles and trucks. Volume 3-A covers receivers in Chevrolet and Pontiac cars and GMC and Chevrolet trucks. Volume 5-C includes Henry J, Hudson, Kaiser-Frazer, Nash, Packard, Studebaker, and Willys products.

TABLES OF LAGRANGIAN COEFFICIENTS FOR SEXAGESIMAL INTERPOLATION (National Bureau of Standards Applied Mathematics Series 35). U. S. Government Printing Office, Washington 25, D.C. 157 pages. \$2.00.

The most common Lagrangian tables used in astronomy, geodesy, ballistics, engineering, and geography provide decimal subdivision of the argument so no cumbersome interpolations are required to find the required coefficients. This table simplifies the problem by providing arguments in sexagesimal measure (angles or time in units of degrees, hours, minutes, and seconds).

MOST-OFTEN-NEEDED 1954 RADIO DIAGRAMS AND SERVICING INFORMATION, compiled by M. N. Beitman. Supreme Publications, 1760 Balsam Road, Highland Park, Ill. 160 pages. \$2.50.

This is the latest addition in the continued series of volumes of diagrams and service data on modern home, auto, and portable radios.

The volume consists of reprints of data and diagrams on approximately 560 models made by 32 receiver manufacturers.

To simplify these rather complex tables, several pages are devoted to the scope of the material and illustrations of the use of the coefficients. Special explanations are given for use of coefficients near the beginning and end of a table, and in tables having differences. Prior to the tables is a chapter devoted to the methods of making computations.

END

Fix TV Sets Twice as Fast!



**CUT TIME
IN HALF
on 2 jobs
out of 3!**



**PIX-O-FIX
TV TROUBLE FINDERS**
by Ghirardi and Middleton

Now! Handle television receiver troubles by easy picture analysis. Let these famous PIX-O-FIX Guides tell you what is wrong . . . then show exactly how to fix it fast, easy and r-i-g-h-t! No lost time! No needless testing!

Remember! PIX-O-FIX TV Trouble Finder Guides are NOT gadgets. They're practical, professional servicing devices by two of America's best-known service authorities . . . and you buy them on a money-back guarantee.

Just turn the PIX-O-FIX dial until the picture in its window shows the same trouble symptoms (wavy lines, snow, no raster, "squeezing" distortion, etc., etc.) as the picture on the TV set you're repairing. PIX-O-FIX then tells the possible causes of this trouble and gives step-by-step repair instructions. It's as easy as that!

The two PIX-O-FIX Guides cover 47 different kinds of TV troubles . . . just about anything you're called on to fix. Try them!

**SPECIAL!
Get both
for only \$2
use coupon**

PIX-O-FIX No. 1 Makes it easy to identify 24 common TV troubles by looking at the picture. Gives 194 causes and 253 remedies with step by step instructions for these troubles. Price separately: \$1.25.

PIX-O-FIX No. 2 Covers 23 additional TV troubles with easy-to-understand repair instructions. Together, these two PIX-O-FIX Guides are a practical guide to fast picture analysis servicing of any TV set! Price separately: \$1.25.

10-DAY MONEY-BACK GUARANTEE

Dept. RE-114, Rinehart & Co., Inc.
232 Madison Ave., New York 16, N. Y.

Enclosed is \$_____ for which please rush:

- PIX-O-FIX No. 1 (\$1.25)
 PIX-O-FIX No. 2 (\$1.25)


SPECIAL OFFER: Both PIX-O-FIX No. 1 and No. 2 at only \$2.00 for the two.

If not satisfactory, I will return PIX-O-FIX postpaid in 10 days and you guarantee to refund my money.

Name _____

Street _____

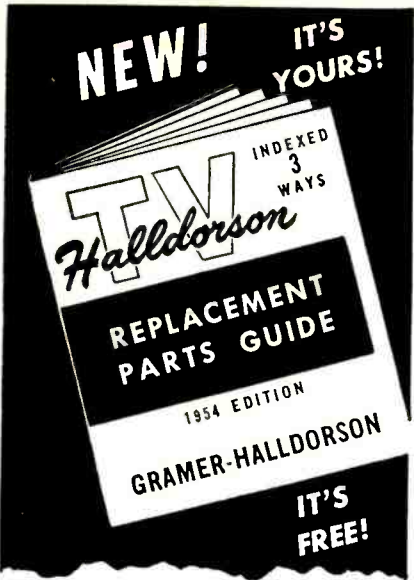City, Zone, State _____
OUTSIDE U.S.A. \$1.50 each, \$2.50 for both. Same money-back return privilege.




The Only T-V Parts Guide

CROSS-INDEXED THREE WAYS:

- PARTS EASY TO FIND**
- 1. by Model Number**
 - 2. by Chassis Number**
 - 3. by Part Number**

This New Guide makes available the very **NEWEST T-V REPLACEMENT PARTS** in addition to the complete Gramer-Halldorsen line. It is obtainable at your dealer without cost. If he cannot supply you write direct c/o Dept. R. E.

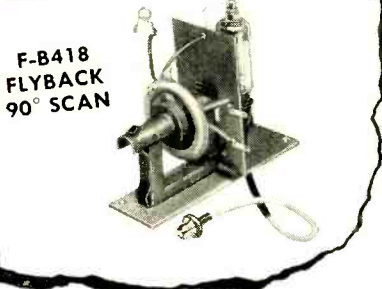A Splendid Example of the Many New Items Available:



TRANSFORMERS

Power - Audio - Filament - Output
Input - Flyback - All Types!

The **NEW GRAMER HALLDORSON DEFLECTION YOKE**
Write FOR FULL DETAILS



Address: Dept. R. E.

GRAMER Halldorsen
TRANSFORMER CORPORATION

2734 N. PULASKI ROAD, CHICAGO 39, ILLINOIS

ADVERTISING INDEX

Radio-Electronics does not assume responsibility for any errors appearing in the index below.

All Channel Antenna Corp.	29
Allied Radio Corp.	15
American Electrical Heater Mfg. Co.	95
American Phenolic Corp.	132
Amplifier Corporation of America	116
Arday Radio Kits, Inc.	140
Atlas Sound Corp.	110
Audiol Publishers	144
Barry Electronics Corp.	154
Bell Telephone Labs.	26
Blonder Tongue Labs.	148
Boland & Boyce, Inc.	153
Brooks Radio & TV Corp.	101
Burstein Applebee Co.	145
CBS Hytron (Div. of Columbia Broadcastng System)	20
Cannon Electric Co.	84
Capitol Radio Engineering Institute	97
Centralab Division of Globe-Union	112
Century Electronics Co.	108
Channo Master Corp.	18, 19
Chicago Standard Transformer Corp.	110
Cisin, H. G.	9
Cleveland Institute of Radio-Electronics	19
Collins Audio Products Co., Inc.	47
Columbia Wire & Supply Co.	120
Concord Radio	113
Cornell Dubilier Electric Corp.	142
Cornish Wire Co.	126
Coyne Electrical & TV Radio School	17, 117, 130
DeVry Technical Institute	7
DuMont Labs. Allen B.	Inside Front Cover
Edie Electronics	143
Elecraft Electronics	142
Electronic Instrument Co., (EICO)	30, 126, 134
Electro Products	144
Electro-Voice, Inc.	Inside Back Cover
Electron Tube Wholesalers, Inc.	148
Electronic Measurements Corp.	131
Erie Resistor Corp.	145
Fair Radio Sales	149
Fenton Co.	113
Franklin Electronics	110
G. & H. Wood Products Co.	92
General Cement Mfg. Co.	89
General Test Equipment	130
Good, Inc.	144
Grammer-Halldorsen Transformer Co.	154
Hallcrafters Co.	124, 126, 128, 130
Hawkins, P. E., Co.	142
Heath Co.	67-78
Hershel Radio	144
Hickok Electrical Instrument Co.	125
Hi-Lite Electronic Sales Co.	109
Hockett Electronics	137
IV	95
Hudson Specialist Co.	139
Hughes Research & Development Labs.	80, 120
Indiana Technical College	116
Instructograph Co.	137
International Correspondence Schools	114
International Rectifier Corp.	124
JFD Mfg. Co., Inc.	87
Jackson Electrical Instrument Co.	12
Jensen Industries	141
Jerrid Electronics Corp.	84
Kay-Townes Antenna Corp.	104, 105
Lafayette Radio Corp.	115
Leotard Radio Corp.	98
Macmillan Co., The	146
Mailory & Co., Inc. P. R.	141
McGraw Hill Book Co.	80
Metropolitan Electronics & Instrument Co.	107
Mosley Electronics	141
Moss Electronic Distributing Co.	122, 123
Multicore Sales Corp.	118
Musical Masterpiece Society, The	81
National Electronics of Cleveland	152
National Radio Institute	3, 27, 28
National Schools	5
Newcomb Audio Products Co.	141
Opportunity Adlets	148
Pacific Mercury Sales Corp.	139
Perma-Power Co.	90
Philoco Corp.	22
Pickering Co.	8
Precision Development Corp.	114
Precision Apparatus Co., Inc.	147
Precision Electronics	119
Progressive "Edu-Kits," Inc.	135
Quam-Nichols Co.	127
Quietrol Co.	124
RCA Institutes, Inc.	25
RCA Victor Division (Rad o Corp. of America)	Back Cover
Rad-Tel Tube Co.	155
Radcel Mfg. Co.	93
Radiart Corp.	91
Radio City Products	116
Radio Television Training Institute	21
Baltimore Technical Institute	109
Candler System Co.	109
Grantham School of Electronics	149
Indiana Technical College	119
Indianapolis Electronic School	137
Milwaukee School of Engineering	153
RCA Institutes, Inc.	108
Tri-State College	128
Valparaiso Technical Institute	142
Western Television Institute	128
RCA Institutes, Inc.	25
RCA Victor Division (Rad o Corp. of America)	Back Cover
Rad-Tel Tube Co.	155
Radcel Mfg. Co.	93
Radiart Corp.	91
Radio City Products	116
Radio Television Training Institute	21
Baltimore Technical Institute	109
Candler System Co.	109
Grantham School of Electronics	149
Indiana Technical College	119
Indianapolis Electronic School	137
Milwaukee School of Engineering	153
RCA Institutes, Inc.	108
Tri-State College	128
Valparaiso Technical Institute	142
Western Television Institute	128
Radio City Products	116
Radio Television Training Institute	21
Baltimore Technical Institute	109
Candler System Co.	109
Grantham School of Electronics	149
Indiana Technical College	119
Indianapolis Electronic School	137
Milwaukee School of Engineering	153
RCA Institutes, Inc.	108
Tri-State College	128
Valparaiso Technical Institute	142
Western Television Institute	128
Radio City Products	116
Radio Television Training Institute	21
Baltimore Technical Institute	109
Candler System Co.	109
Grantham School of Electronics	149
Indiana Technical College	119
Indianapolis Electronic School	137
Milwaukee School of Engineering	153
RCA Institutes, Inc.	108
Tri-State College	128
Valparaiso Technical Institute	142
Western Television Institute	128
Radio City Products	116
Radio Television Training Institute	21
Baltimore Technical Institute	109
Candler System Co.	109
Grantham School of Electronics	149
Indiana Technical College	119
Indianapolis Electronic School	137
Milwaukee School of Engineering	153
RCA Institutes, Inc.	108
Tri-State College	128
Valparaiso Technical Institute	142
Western Television Institute	128

RADIO SCHOOL DIRECTORY PAGE 151

Baltimore Technical Institute	109
Candler System Co.	109
Grantham School of Electronics	149
Indiana Technical College	119
Indianapolis Electronic School	137
Milwaukee School of Engineering	153
RCA Institutes, Inc.	108
Tri-State College	128
Valparaiso Technical Institute	142
Western Television Institute	128
Radio City Products	116
Radio Television Training Institute	21
Baltimore Technical Institute	109
Candler System Co.	109
Grantham School of Electronics	149
Indiana Technical College	119
Indianapolis Electronic School	137
Milwaukee School of Engineering	153
RCA Institutes, Inc.	108
Tri-State College	128
Valparaiso Technical Institute	142
Western Television Institute	128
Radio City Products	116
Radio Television Training Institute	21
Baltimore Technical Institute	109
Candler System Co.	109
Grantham School of Electronics	149
Indiana Technical College	119
Indianapolis Electronic School	137
Milwaukee School of Engineering	153
RCA Institutes, Inc.	108
Tri-State College	128
Valparaiso Technical Institute	142
Western Television Institute	128
Radio City Products	116
Radio Television Training Institute	21
Baltimore Technical Institute	109
Candler System Co.	109
Grantham School of Electronics	149
Indiana Technical College	119
Indianapolis Electronic School	137
Milwaukee School of Engineering	153
RCA Institutes, Inc.	108
Tri-State College	128
Valparaiso Technical Institute	142
Western Television Institute	128
Radio City Products	116
Radio Television Training Institute	21
Baltimore Technical Institute	109
Candler System Co.	109
Grantham School of Electronics	149
Indiana Technical College	119
Indianapolis Electronic School	137
Milwaukee School of Engineering	153
RCA Institutes, Inc.	108
Tri-State College	128
Valparaiso Technical Institute	142
Western Television Institute	128

NEW LOW Prices on STANDARD BRAND TUBES

From the 5 Leading Manufacturers

- Individually boxed.
- Only 1st quality
- Latest Dating—
- No private label, electrical or mechanical rejects.
- No rebrands or reworked "bargains."

AUTHORIZED DISTRIBUTORS
CBS-HYTRON—EIMAC—WESTINGHOUSE
AND OTHERS

Tube Orders Over \$25.00, with full
remittance, PREPAID to you in U.S.A.

Type	Net	Type	Net	Type	Net
0Z4	-.50	6BF5	.85	7N7	.95
1A5GT	.80	6BF6	.70	7Q7	1.00
1A7GT	1.00	6BG6G	1.80	7R7	1.30
1B3GT	.85	6BH5	.80	7S7	1.25
1H5GT	.75	6BJ6	.70	7V7	1.30
1L4	.85	6BK5	.90	7W7	1.30
1L6	1.00	6BK7A	1.20	7Z4	.85
1LA4	1.00	6BL7GT	1.15	7X7	1.00
1LA6	1.00				

For QUALITY - PERFORMANCE - DEPENDABILITY

Rad-Tel Tubes Guaranteed 1 FULL YEAR



**70% to 90%
OFF**

- Same Day Service
- All Tubes Individually Boxed
- 300 Types Always in Stock

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
OA2	.74	3E5	.46	6BA7	.57	6S8GT	.53	7F7	.79	12Q7	.59	26	.45
OA4	.68	3LF4	.69	6BC5	.54	6SA7GT	.55	7F8	.79	12S8GT	.62	27	.39
OB2	.81	3Q4	.48	6BD5	.59	6SD7GT	.41	7G7	.89	12SA7GT	.65	32L7	.89
OC3	.72	3Q5GT	.69	6BD6	.45	6SF5GT	.46	7H7	.59	12SC7M	.63	35	.58
OD3	.70	3S4	.58	6BE6	.51	6SG7GT	.41	7J7	.79	12SF5	.50	35A5	.58
OZ4M	.65	3V4	.58	6BF5	.41	6SH7GT	.49	7K7	.69	12SG7	.51	35B5	.52
1A5	.49	5AZ4	.59	6BF6	.37	6SJ7GT	.41	7L7	.59	12SJ7M	.67	35C5	.51
1A7GT	.47	5T4	.79	6BG6G	1.25	6SK7GT	.53	7N7	.69	12SK7GT	.63	35L6GT	.51
1AX2	.62	5U4G	.55	6BH6	.53	6SL7GT	.48	7Q7	.66	12SL7GT	.57	35W4	.47
1B3GT	.73	5W4GT	.50	6BJ6	.49	6SN7GT	.59	7R7	.89	12SN7GT	.52	35Y4	.54
1C5	.43	5Y3GT	.37	6BK5	.80	6SQ7GT	.46	7S7	.79	12SQ7GT	.56	35Z8	.59
1E7	.29	5Y4	.51	6BK7	.80	6SR7GT	.45	7V7	.89	12SR7M	.49	35Z4	.47
1G6	.24	5Z3	.45	6BL7GT	.83	6SS7GT	.42	7X6	.54	12V6GT	.46	35Z5GT	.47
1H4	.30	6A6	.51	6BN6	.59	6T4	.99	7X7	.70	12X4	.38	36	.39
1H5GT	.49	6A7	.69	6BQ6GT	.98	6T8	.80	7Y4	.69	14A4	.69	45	.55
1L4	.46	6A8	.62	6BQ7	.90	6U5	.57	7Z4	.59	14A5	.59	45Z5	.49
1LA4	.59	6AB4	.44	6BZ7	.90	6U6	.59	12A6	.54	14A7	.63	46	.69
1LA6	.69	6AC5	.69	6C4	.40	6U8	.78	12A8GT	.61	14AF7	.59	50A5	.55
1LB4	.69	6AC7M	.86	6C5	.39	6V6GT	.50	12AL5	.37	14B6	.63	50B5	.52
1LC5	.59	6AF4	.90	6C6	.58	6W4GT	.47	12AQ5	.52	14B8	.63	50C5	.51
1LC6	.79	6AG5	.56	6CB6	.54	6W6GT	.57	12AT6	.41	14C5	.79	50L5GT	.61
1LD5	.59	6AG7M	.99	6CD6	1.11	6X4	.37	12AT7	.72	14C7	.79	50X6	.49
1LE3	.59	6AH4	.57	6CF6	.64	6X5GT	.37	12AU6	.46	14E6	.75	50Y6	.49
1LG5	.69	6AH6	.73	6CS6	.51	6X8	.75	12AU7	.60	14E7	.88	50Y7	.50
1LH4	.69	6AJ5	.65	6D6	.59	6Y6G	.48	12AV6	.39	14F7	.65	55	.49
1LN5	.59	6AK5	.55	6E5	.48	7A4	.47	12AV7	.73	14F8	.69	56	.49
1N5GT	.67	6AK6	.59	6F5GT	.39	7A5	.59	12AX4	.67	14H7	.59	57	.58
1P5GT	.57	6AL5	.42	6F6	.59	7A6	.69	12AX7	.63	14J7	.30	58	.60
1Q5GT	.58	6AM8	.78	6G6	.42	7A7	.69	12AY7	.69	14N7	.84	70L7	.97
1R5	.62	6AQ5	.50	6H6GT	.41	7A8	.68	12AZ7	.59	14R7	.79	75	.49
1S4	.59	6AQ6	.37	6J5GT	.43	7AD7	.79	12B4	.60	14S7	.89	76	.44
1S5	.51	6AQ7	.70	6J6	.52	7AF7	.53	12BA6	.49	14W7	.30	77	.57
1T4	.58	6AR5	.45	6J7	.43	7AG7	.69	12BA7	.60	14X7	.69	78	.47
1T5	.59	6AS5	.50	6K5	.47	7AH7	.79	12BD6	.45	14Y7	.62	80	.43
1U4	.57	6AS6	1.49	6K6GT	.45	7B4	.44	12BE6	.51	19BG6	1.39	83V	.68
1U5	.50	6AT6	.41	6K7	.44	7B5	.45	12BF6	.39	19T8	.59	84/6Z4	.46
1V	.43	6AU4GT	.68	6L6	.64	7B6	.69	12BH7	.63	19V8	.79	85	.59
1X2A	.63	6AU5GT	.82	6L7M	.68	7B7	.49	12BY7	.65	24A	.39	117L7	.99
2A3	.30	6AU6	.46	6N7M	.63	7C4	.59	12BZ7	.65	25AV5GT	.83	117F7	.99
2W3	.38	6AV5GT	.83	6Q7	.45	7C5	.69	12C8M	.34	25BQ6GT	.98	117Z3	.37
2X2	.49	6AV6	.40	6R7	.69	7C6	.59	12H6	.56	25L6GT	.51	117Z6	.69
3A4	.45	6AX4GT	.65	6S4	.48	7E5	.59	12J5	.42	25W4GT	.59	807	.99
3B7	.27	6B4	.54	6S7M	.79	7E6	.30	12J7	.49	25Z5	.66	865A	1.39
3D6	.27	6BA6	.49	6S78	1.90	7E7	.59	12K8	.59	25Z6	.49	1274	.30

TERMS: A 25% deposit must accompany all orders—balance C.O.D. All shipments F.O.B. Irvington warehouse. ORDERS UNDER \$10—\$1.00 HANDLING CHARGE. . . Subject to prior sale.


PLEASE: Send full remittance . . . allow for postage and save C.O.D. charges! We refund all unused money! Dept. RE-11.

Phone: Essex 5-2947

Tubes in Bold Type Cover 90% of Demand

Rad-Tel TUBE CO.

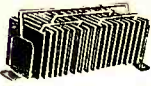'Integrity Is Our Chief Asset'
115 COIT ST., IRVINGTON II, N. J.



NEW SELENIUM RECTIFIERS

We specialize in Rectifiers, Power supplies, Full wave bridges.

Table with columns: Curr. Cont., Volts, and various current/voltage ratings for selenium rectifiers.

New Rectifier & Transformer

Table listing transformer and rectifier specifications, including current and voltage ratings and prices.

NEW HIGH CURRENT PWR SUPPLIES LTD*

Table listing power supply specifications, including current and voltage ratings and prices.

NEW RECTIFIER XFMRs

Table listing transformer specifications, including current and voltage ratings and prices.

NEW RECTIFIER CHOKES

Table listing choke specifications, including current and voltage ratings and prices.

TAB THAT'S A BUY

NEW BATTERY CHARGER RECTIFIER

13-0-13V (CT) 100 Amp full cooled or 13-0-13V (CT) 100 Amp full cooled or 13-0-13V (CT) 100 Amp full cooled...

TV & COAX CABLE

Table listing TV and coax cable specifications and prices.

RG8U 52 Ohm 100 ft. \$11; 1000 Ft. \$98; RG11 75 Ohm 100 ft. \$11; 1000 Ft. \$98...

TRANSFORMER SPECIAL

6.3 VOLT 3/4 AMP CONTINUOUS DTY. 115VAC Input. SIZE 2.5 16H 2L 1 1/2" W. MTG CNTR 23# MFGRS...

OIL CONDENSERS

Table listing oil condenser specifications and prices.

PRECISION POTENTIOMETERS

Heliplot 100 Ohm 0.5% Tol. 10 Turn \$7.98; Heliplot 2000 Ohm 0.5% Tol. 10 Turn \$7.98...

NEWLY IMPORTED LATEST MODEL POCKET VOLT METER 12C

\$10.99 Plus U.S.C.

1000-OHM Per/V

Reads AC & DC. Volts: 0 to 5, 25, 250 & 1000 Volts. DC: 0 to 50, 500 & 1000 Volts. 100MA OHMS; 1 to 10K & 100K HI-impedance - 170 Ohms...

METER SALE

Table listing meter sale items and prices, including various models and brands.

HI-FI SPEAKERS

All 8 ohm, 1/4" C.C. Amino V Magnets. Full Range. 25 watt/2500 Ohm. Wires needed for HF & LF Response. Famous Hi-Fi Speakers Mfg. 15" Coaxial PM & 5" Tweeter...

AUDIO COMPONENTS

Electronic triplay cart. \$1.98; GE RPX041 Hi-Fi Goldtone \$5.25; GE RPX050 GE Orange Box \$6.69...

HIGH FIDELITY AUDIO

You are there! Hear Carnegie Hall in your living room through the NEW TAB HI-FI Linear Amplifier. Check these outstanding features: Response...

TUBES

*From This Special List We Ship \$10.00 and Up Tube Orders At Our Expense (Postpaid) Within Continental Limits of U.S.A.

Large table listing various vacuum tube models, types, and prices.

TEST CORDS

8 FT Test Leads, Heavy Duty. 25 Strand W/Alligator Clips. 15 FT Extension 51 Conductor, 100 V. Rubber Insul. \$1.00...

TROUBLE LIGHTS (As Shown)

Table listing trouble light specifications and prices.

TRANSFORMERS

Table listing transformer specifications and prices.

BATTERY 106 WATT/SCDS

Same specs, only batteries. \$36.98; \$25MFD 450V/53w secs condensers; low leakage 231A 50V/500uF \$2.17...

PHOTOFLASH KIT

Includes transf condensers 50x52MFD/450V/Total 1.04MFD; 50V/500uF; capacitors, rectifier, flash tube in indicating flash gun, ready to go on Kodachrome 25 \$39.98

CIRCUIT BREAKER FUSES

PUSH TO RESET. Am. 27ct \$3-\$15-\$20; Ea. 27ct for \$1.00, 100 \$15; Circuit Breaker Fuse with 20 Minute Time 39c...

VARIABLE DC POWER SUPPLY

Full Wave rectification, 6000Mfd filter, Condensers, fused, R.3V or 12.6V at 2 amp, operates 115V/60Cz. Model 2DCP... \$12.98

FILAMENT TRANS.

Table listing filament transformer specifications and prices.

866A KIT and XFORMER

(2) 866A Tubes & Sockets, Transformer Rated PR115V 60Cz. Sec. 2 5VCT 110V 10A. Volt Insulation & 498

TOGGLE SWITCHES

Table listing toggle switch specifications and prices.

YOU PICK THEM WHILE THEY LAST

LOTS OF 10. Your selection of 10 at 39c each or smaller quantity at indicated prices.

ELECTROLYTIC CONDENSER FRESH STOCK

Table listing electrolytic condenser specifications and prices.

PRECISION RESISTORS

Four Million in Stock. All 1% Accuracy Gtd. ORD. ANY VALUE WE HAVE IT. REGULARLY SOLD FOR 60c AND UP

THAT'S A BUY

Dept. 11RE 111 Liberty Street, New York 6, N.Y., U.S.A.

TELEVISION ANTENNA

VELOCAL. Full range response, all channel, power foldable POLE Hi & low antennas, all channel, construction, \$4.95

TV CONICAL ANTENNA

8 elements conical, all channel, sturdy construction, \$4.95

DOUBLE-V ANT.

8 elements, all channel, sturdy construction, \$4.99

5 FOOT INTERLOCKING

Match, rustproof. \$2 for \$1.49; 10 for \$7

Money Back Guaranteed

(Cost of Mds. Only) \$5 Min. Order F.O.B. N.Y.C. Add Shpg. Charges or 25% Dep. Tubes Gtd. via R-Exp. only. Prices subject to Change Without Notice. Phone Reactor 2-6245.

CABLE: "TABPARTS"

CABLE: "TABPARTS"

NEW PACESETTER in today's Most Complete line of GENERAL-PURPOSE

DYNAMIC MICROPHONES



NEW "623"

SLIM DYNAMIC

Size 7½" x 1-5/16".
Net wt. 15 ozs. List \$49.50

You get advanced styling...plus E-V quality...in this new pacesetter! Proved E-V features guarantee dependable operation indoors and outdoors...for public address, paging, recording and communications.

The "623" can be used on a stand or in the hand. Omnidirectional. Response 60-11,000 cps. Output -55 db. Acoustalloy diaphragm. Pressure cast case finished in Satin Chromium. Tilttable head. Built-in cable connector. 5/8"-27 thread. "On-Off" switch. Choice of Hi-Z or Low-Z by changing one wire in cable connector. 18 ft. cable. *Get full details now.*



Model 647 Lavalier

Small, rugged PA dynamic for chest, desk or hand use. Supplied with neck cord, support clips and 18 ft. cord. Omnidirectional. Response 60-13,000 cps at -57 db level. 150 ohms or Hi-Z. Acoustalloy diaphragm. Black anodized finish. Size 5" x 1". List \$80.00

Model 636 Slimair

Exceptionally fine dynamic for PA, recording and general use. Response 60-13,000 cps. Output -55 db. Acoustalloy diaphragm. Pop-proof head. Omnidirectional. Wide pick-up range. Tilttable head. "On-Off" switch. Satin Chromium finish. 18 ft. cable. 1-1/16" diam. Use for Hi-Z or Low-Z. List \$70.00

Model 611 Mercury

Smartly styled dynamic. Response 50-8000 cps. Output -55 db. Omnidirectional. Acoustalloy diaphragm. Tilttable head. "On-Off" switch. Satin Chromium finish. Available in 50, 150 or 250 ohms, or Hi-Z. With 6 ft. or 18 ft. cable.

Model 611-8. List \$35.50
Model 611-20. List \$37.50

Model 630

High fidelity, high output dynamic. Response 60-13,000 cps. Output -55 db. Use on stand or in hand. Acoustalloy diaphragm. Omnidirectional. Tilttable head. "On-Off" switch. Satin Chromium finish. Compact, rugged, versatile. 18 ft. cable. Available in 50, 250 ohms or Hi-Z. List \$47.00

Model 605

Durable dynamic. Response 65-7500 cps. Output -55 db. Omnidirectional. Acoustalloy diaphragm. Head at 22° fixed tilt. Satin Chromium finish. Choice of 50, 250 ohms or Hi-Z. Models with 6 ft. and 18 ft. cable.

Model 605-8. List \$27.50
Model 605-20. List \$29.50

Cardyne Cardioid

Provides wide-angle front pick-up—dead at rear. Reduces feedback and reverberation pick-up. High-Low impedance selector. Tilttable head. "On-Off" switch. Satin Chromium finish. 18 ft. cable.

Model 726. Response 50-8000 cps. Output -55 db. List \$75
Model 731. Response 40-10,000 cps. Output -52 db. Dual-type external shock mount. List \$95

No Finer Choice Than

Electro-Voice

In addition to the models shown here, the complete E-V line includes famous TV and BC Microphones, hand-held Mobile-Mikes, Differential Noise Cancelling Microphones, and others. Write for helpful information on any application.

ELECTRO-VOICE, INC., BUCHANAN, MICH. Export: 13 E. 40th St., N.Y. 16, U.S.A. Cables: Arlab

NEW EDITION!

Now ready, the RC-17...the 1954 edition of the RCA RECEIVING TUBE MANUAL

Revised and up-to-date, this "standard reference tool" for radio-tv service technicians, engineers, and experimenters covers the complete line of RCA receiving tubes and picture tubes for home-entertainment use. It includes basic tube theory, installation and operation data, and features application information, comprehensive resistance-coupled amplifier charts, *plus* new circuits for hi-fi amplifiers.

Get your copies of the RC-17 Receiving Tube Manual from your local RCA Tube Distributor, from your technical bookshop, or from RCA Commercial Engineering Section K39x, Harrison, N. J. At only 60 cents* per copy, you'll want one of these manuals for every serviceman in your shop.



ONLY
60*
¢

*SUGGESTED
LIST PRICE

RCA receiving tube

RCA

receiving
tube
manual



RADIO CORPORATION of AMERICA
ELECTRON TUBES

HARRISON, N. J.

ADV Plans, LLC

Copyright Notice:

The entire contents of this CD/DVD are copyright 2014 by ADV Plans, LLC. All Rights Reserved.

Reproduction or distribution of this disk, either free or for a fee is strictly prohibited. We actively monitor and remove listings on eBay thru Vero.

You are free to copy or use individual images in your own projects, magazines, brochures or other school projects.

Only the sellers listed here are authorized distributors of this collection:
www.theclassicarchives.com/authorizedsuppliers

Please view our other products at
www.theclassicarchives.com,
or our ebay stores:

[TheClassicArchives](#)
[ADVPlans](#)
[SuperShedPlans](#)

