

FEBRUARY 1960

# Radio-Electronics

ONE-CONTROL MULTIMETER

HUGO GERNSBACK, Editor

Electronic Voltage Regulator  
For Your Car

Motors Balanced  
By Electronics

New Circuit Kills  
P-A Howl

See page 4

50c

W P SMITH 9-61  
2905 VICTOR ST  
ST LOUIS 4 MISSOURI

... the smartest move you can make

# is to TRIPLETT VOMs

... the world's most complete line of VOMs for every purpose!

**TRIPLET**

Quality...  
First to last



**Model 639-N Case \$9.50.** Handsome, black cowhide leather. Center-cover flaps snap back for full view of scales and complete access to instrument without removal from case.

**Model Pt. T-225-A-33 Tester Stand \$0.50.** Metal, holds tester in approximately 45° angle; facilitates easy reading.

**Probe for High Voltage Testing \$14.50.** For models 630, 630-A, 630-PL, 630-APL, and 631. Completely insulated polystyrene; guard-type handle. 11 1/4" long; 48" hi-voltage wire lead with banana plug at tester end. Available in 0-12,000 AC or DC volts, and 0-30,000 AC or DC volts.

**Model 630-T \$54.50.** Specially designed for telephone maintenance. 2% accuracy on DC. Fused protected circuit protects resistors and meter in ohms ranges. Special neck strap holds instrument, freeing both hands. Banana jack connectors eliminate all shock hazard. Completely insulated case protects from ground.

**Model 666-R Pocket VOM \$29.50.** Hand size, ideal for electrical maintenance. With recessed range knob it fits easily into case. AC rectifier pre-calibrated unit for easy replacement. Banana jacks at panel top prevent leads falling over meter dial. Single king-size selector switch minimizes incorrect settings, burnouts. 20 ranges. Molded case streamlined, fully insulated.

**Model 666-HH Pocket VOM \$27.50.** Compact, hand-size; 3" meter integral with panel, adjusted to 400 microamperes at 250 millivolts. Only 3 jacks necessary for all ranges. 19 ranges.

**Model 625-NA \$54.50.** Dual sensitivity for extra ranges; large mirror scale for super readability. 3-color meter scale 5" long. 6" instrument, 0-50 microamp. AC volts at 10,000 O/V for checking many audio and high imped-

ance AC circuits usually requiring VTVM. 38 ranges. Molded insulated case.

**Interior View** showing advanced engineering features of all Triplet VOMs. Molded mounting for resistors and shunts allows direct connections without cabling. Eliminates shorts. Longer life.

**Model 630 \$44.50.** Popular, streamlined; long meter scales for easy reading. Outstanding line ohm scale; low reading .1 ohm, high 100 megs. Single king-size selector-switch minimizes incorrect settings, burnouts. High sensitivity: 20,000 ohms per volt DC; 5,000 AC. Molded, fully insulated case.

**Model 630-A \$54.50.** Laboratory type; 1/2% resistors for greater accuracy. Long mirrored scale eliminates parallax. Banana jacks, low resistance connections; high flux magnet increases ruggedness. Single king-size selector switch minimizes incorrect settings, burnouts. Molded fully insulated case.

**Model 630-PL \$44.50.** Instant-vision, wider spread scales; streamlined case; handsome modern design. Unbreakable window. Outstanding linear ohm scale; low reading .1 ohm; high to 100 megs. Single king-size selector switch minimizes incorrect settings, burnouts. 5 to 500,000 cps frequency response in AC measurements. DC Polarity Reversing switch. High sensitivity: 5,000 ohms per volt AC; 20,000 ohms per volt DC.

**Model 10 Clamp-On Adapter \$14.50.** Checks line loads with model 310 (can also be used with 6 other models). Instant, accurate, safe. No circuit breaking or work interruption. Easy range switching. Available in 6 AC Ammeter ranges: 0-6-12-30-60-120-300. Clips around single wire to read AC. Amperes direct. Use with adapter 101 to instantly divide 2-conductor cords. Molded case fully insulated, black plastic with engraved white markings.

**Model 630-APL \$54.50.** Laboratory type with 1/2% resistors, more accurate movement. Long mirrored scales eliminate parallax. Unbreakable window. Single king-size switch minimizes incorrect settings, burnouts. 5 to 500,000 cps frequency response in AC measurements. DC Polarity Reversing switch. High sensitivity: 5,000 ohms per volt AC; 20,000 ohms per volt DC. Molded case fully insulated.


**Model 630-NA \$74.50.** Super DeLuxe with 70 ranges—nearly double conventional types. Frequency compensated from 35 cps to 20 kc. Temperature compensated. Accurate within 1 1/2% full scale reading on DC. Large open front meter easy to read. Unbreakable window. Mirrored scale. Meter protection against overloads. Molded fully insulated case.

**Model 631 Combination VOM and VTVM \$64.50.** Two fundamental units at the price of a single tester. The No. 1 instrument for all electronic men. Battery operation assures VTVM stability and long life. Sensitivity PLUS. 1.2 volt (VTVM) range is equal to more than nine million ohms per volt. Large easy to read meter with unbreakable face. Single king-size selector switch minimizes incorrect settings, burnouts. Molded case fully insulated.

**Model 310 \$34.50.** The only complete miniature VOM with 20,000 ohms per volt and selector range switch. Self-shielded against strong magnetic field. Rugged, high torque, barring instrument. Unbreakable plastic meter window. Converts to common probe—frees one hand—by fitting interchangeable test prod into top. Standard sensitivity 20,000 ohms per volt DC, and 5,000 ohms per volt AC. Accuracy 3% DC. Molded fully insulated case.

**TRIPLET**  
Quality...  
First to last

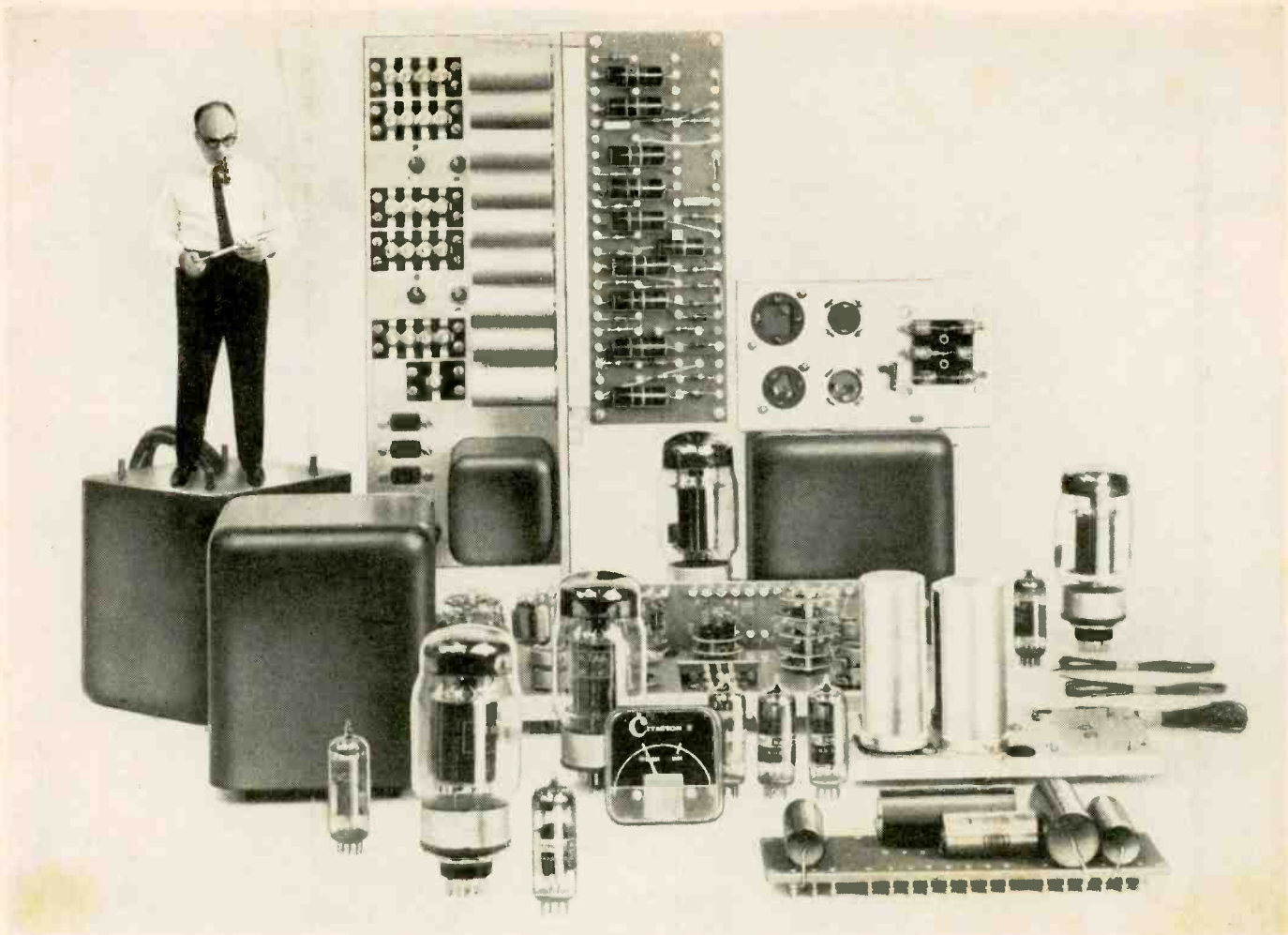TRIPLET ELECTRICAL INSTRUMENT COMPANY  
BLUFFTON, OHIO



## We don't pack an engineer into each new Citation Kit but...

... the engineering built into each kit is so precise that the unit constructed in the home will be the equal of the factory-produced instrument.

It is far more difficult to design a kit than to produce a completely manufactured product. In the plant the engineer can control his design from the moment of inception until the final packaging. The kit builder has only his tools, his ingenuity and little, if any, test equipment.

Therefore, the complex process of in-plant production and control which guarantees the fine finished product must somehow be *embedded* in the kit design. The Citation engineering group at Harman-Kardon, headed by Stewart Hegeman, has succeeded in doing just this in the design of the new Citation I, Stereophonic Preamplifier Control Center and Citation II, 120 Watt Stereophonic Power Amplifier.

Only heavy duty components, operating at tight tolerances, have been selected for the Citation Kits. As a result, even if every component is operated at its limit — remote as this possibility is — the instruments will perform well within their specifications.

Rigid terminal boards are provided for mounting resistors and condensers. Once mounted, these components are suspended tightly between turret lugs. Lead length is sharply defined. The uniform spacing of components and uniform lead length insure the overall stability of the unit.

Improper routing of leads, particularly long leads, can result in unstable performance. To prevent this, the Citation II is equipped with a template to construct a Cable Harness. The result: each wire is just the right length and in just the right place to achieve perfect performance.

These truly remarkable achievements in Control Engineering are only a few of the many exciting new developments in kit design from the Citation Division of Harman-Kardon.

**THE CITATION I, Stereophonic Preamplifier Control Center**, is a brilliantly designed instrument, reflecting engineering advances found only in the best professional equipment. The control over program material offered by the new Citation I enables the user to perfectly re-create every characteristic of the original performance. (The Citation I — \$139.95; Factory-Wired — \$239.95; Walnut Enclosure, WW-1 — \$29.95.)

**THE CITATION II, 120 Watt Stereophonic Power Amplifier**, has a peak power output of 260 Watts! This remarkable instrument will reproduce frequencies as low as 5 cycles virtually without phase shift, and frequencies as high as 100,000 cycles without any evidence of instability or ringing. At normal listening levels, the only measurable distortion in this unit comes from the laboratory testing equipment. (The Citation II — \$159.95; Factory-Wired — \$219.95; Charcoal Brown Enclosure, AC-2 — \$7.95.) All prices slightly higher in the West.

Harman-Kardon has prepared a free detailed report on both of these remarkable new instruments which we will be pleased to send to you. Simply write to Dept. RE-2, Citation Kit Division, Harman-Kardon, Inc., Westbury, L. I.



Citation I

Build the Very Best **CITATION KITS** by **harman kardon**



FEBRUARY, 1960

# Radio-Electronics

Formerly RADIO-CRAFT ■ Incorporating SHORT WAVE CRAFT ■ TELEVISION NEWS ■ RADIO & TELEVISION

## EDITORIAL

33 Microelectronics—Hugo Gernsback

## TEST INSTRUMENTS

- 34 Single-Control Multimeter—Albert Stratmoen
- 37 Portable Power Supply—I. Queen
- 38 Transistor Substitution Box—Leonard J. D'Airo
- 39 Clamp Type Ac Microammeter

## AUDIO-HIGH FIDELITY

- 40 Stop Feedback in Public-Address Systems (Cover Feature)—M. R. Schroeder
- 43 Tape Recorder Word Puzzle—John A. Comstock
- 44 RCA's Two-Way Stereo Amplifier—Robert F. Scott
- 47 Design Your Own Preamp, Part II—Norman H. Crowhurst
- 50 New Discs and Tapes—Reviewed by Chester Santon

## INDUSTRIAL ELECTRONICS

- 51 ITV Lens and Lighting Systems—Edward M. Noll
- 54 Photoelectric Register Controls . . . How They Work, Part II—Allan Lytel
- 58 Electronic Balancing for Better Motors—J. W. Essex

## WHAT'S NEW

- 61 Pictorial Report of New Developments

## TELEVISION

- 62 Servicing Chroma Demodulators—Robert G. Middleton
- 74 Spotting Video If Oscillation—Warren J. Smith
- 77 TV Service Clinic—Conducted by Jack Darr
- 83 FM-TV Dx in 1959, Part II—Robert B. Cooper
- 88 TV Minus Rf—L. M. Dilley

## ELECTRONICS

- 96 Micromodules . . . Today and Tomorrow—Jordan McQuay
- 101 Mouse Transmits Own Temperature—Richard S. Griffith, W7MPQ
- 107 All-Transistor Voltage Regulator for Your Car—Daniel Meyer

## RADIO

- 115 Electronic Alarms in Clock Radios—Henry O. Maxwell
  - 116 No-Band-Switching Preselector—Robert Abbatecola, W2YIZ
  - 118 Rapid Cabinet Repair—Edwin Bohr
  - 125 A Tough Dog!—James A. Fred
  - 128 Economy Code Oscillator—James Martin
- |                         |                                  |
|-------------------------|----------------------------------|
| 150 Business and People | 142 New Tubes and Semiconductors |
| 22 Correspondence       | 6 News Briefs                    |
| 154 New Books           | 148 Noteworthy Circuits          |
| 152 New Literature      | 130 Technicians' News            |
| 136 New Patents         | 133 Technotes                    |
| 138 New Products        | 145 Try This One                 |
|                         | 149 50 Years Ago                 |

## ON THE COVER

(Story on page 40)

Dr. M. R. Schroeder of Bell Telephone Laboratories demonstrates the action of his signal-shifting acoustic feedback preventer. Top trace on scope shows signal build-up without shifting; bottom trace is same signal with shifting.

**Hugo Gernsback**  
.....Editor and Publisher

**M. Harvey Gernsback**  
.....Editorial Director

**Fred Shunaman**  
.....Managing Editor

**Robert F. Scott**  
.....W2PWG, Technical Editor

**Larry Steckler**  
.....Associate Editor

**Charles B. Graham**  
.....Associate Editor

**I. Queen**  
.....Editorial Associate

**Elizabeth Stalcup**  
.....Production Manager

**Wm. Lyon McLaughlin**  
.....Tech. Illustration Director

**Sol Ehrlich**  
.....Art Director

**Fred Neinast**  
.....Staff Artist

**Lee Robinson**  
.....Director, Advertising Sales

**John J. Lamson**  
.....Eastern Sales Manager

**G. Aliquo**  
.....Circulation Manager

**Adam J. Smith**  
.....Director, Newsstand Sales

**Robert Fallath**  
.....Promotion Manager



Average Paid Circulation Over 187,000



RADIO-ELECTRONICS is indexed in *Applied Science & Technology Index* (Formerly *Industrial Arts Index*)

RADIO-ELECTRONICS, February, 1960, Vol. XXXI, No. 2. Published monthly at Mt. Morris, Ill., by Gernsback Publications, Inc. Second-class postage paid at Mt. Morris, Ill. Copyright 1959 by Gernsback Publications, Inc. All rights reserved under Universal, International and Pan-American Copyright Conventions.

**SUBSCRIPTION RATES:** U.S., U.S. possessions and Canada, \$4.00 for one year; \$7.00 for two years; \$10.00 for three years. Pan-American countries \$5.00 for one year; \$9.00 for two years; \$13.00 for three years. All other countries \$5.50 a year; \$10.00 for two years; \$14.50 for three years.

**SUBSCRIPTIONS:** Address correspondence to Radio-Electronics, Subscription Dept., 154 West 14th St., New York 11, N.Y. When requesting a change of address, please furnish an address label from a recent issue. Allow one month for change of address.

**GERNSBACK PUBLICATIONS, INC.** Executive, Editorial and Advertising Offices, 154 West 14th St., New York 11, N.Y. Telephone ALgonquin 5-7755. Hugo Gernsback, Chairman of the Board; M. Harvey Gernsback, President; G. Aliquo, Secretary.

**BRANCH ADVERTISING OFFICES and FOREIGN AGENTS** listed on page 159.

**POSTMASTER:** If undeliverable, send Form 3579 to: RADIO-ELECTRONICS, 154 West 14th St., New York 11, N.Y.

\*Trademark registered U. S. Pat. Office.

RADIO-ELECTRONICS

**NOW!**  
at a price  
you can afford!

# MAKE MORE MONEY in TELEVISION RADIO-ELECTRONICS

**BETTER...MORE COMPLETE...LOWER COST...  
WITH NATIONAL SCHOOLS SHOP-METHOD  
HOME TRAINING!**

**BETTER...** Training that is proved and tested in Resident School shops and laboratories, by a School that is the **OLDEST** and **LARGEST** of its kind in the world.

**MORE COMPLETE...** You learn **ALL PHASES** of *Television-Radio-Electronics*.

**LOWER COST...** Other schools make several courses out of the material in our **ONE MASTER COURSE** . . . and you pay more for less training than you get in *our course* at **ONE LOW TUITION!**



**These two FREE books will show you how!**

You get all information by mail . . . You make your own decision . . . at home! **NO SALESMAN WILL CALL**

## TOP PAY... UNLIMITED OPPORTUNITIES LIFETIME SECURITY CAN BE YOURS!

You are needed in the Television, Radio, and Electronics industry! Trained technicians are in growing demand at excellent pay—in **ALL PHASES**, including Servicing, Manufacturing, Broadcasting and Communications, Automation, Radar, Government Missile Projects.

**NATIONAL SCHOOLS SHOP-METHOD HOME TRAINING**, with newly added lessons and equipment, trains you in your spare time at home, for these unlimited opportunities, including many technical jobs leading to supervisory positions.

**YOU LEARN BY BUILDING EQUIPMENT WITH KITS AND PARTS WE SEND YOU.** Your National Schools course includes thorough *Practical* training—**YOU LEARN BY DOING!** We send you complete standard equipment of professional quality for building various experimental and test units. You advance step by step, perform more than 100 experiments, and you build a complete TV set from the ground up, that is yours to keep! A big, new TV picture tube is included at no extra charge.

**EARN AS YOU LEARN.** We'll show you how to earn extra money right from the start. Many of our students pay for their course—and more—while studying. So can you!

### RESIDENT TRAINING AT LOS ANGELES

If you wish to take your training in our Resident School at Los Angeles, the world's TV capital, start **NOW** in our big, modern Shops, Labs and Radio-TV Studios. Here you work with latest Electronic equipment - - professionally installed - - finest, most complete facilities offered by any school. Expert, friendly instructors. Personal attention. Graduate Employment Service. Help in finding home near school - - and part time job while you learn. Check box in coupon for full information.

**LESSONS AND INSTRUCTION MATERIAL ARE UP-TO-DATE, PRACTICAL, INTERESTING.** Every National Schools Shop-Method lesson is made easy to understand by numerous illustrations and diagrams. All instruction material has been developed and tested in our own Resident School Shops, Laboratories and Studios.

**SEND FOR INFORMATION TODAY . . .** it can mean the difference between **SUCCESS** and failure for you! Send for your **FREE BOOK** "Your Future in Television-Radio-Electronics" and **FREE Sample Lesson**. Do it **TODAY**, while you are thinking about your future. It doesn't cost you anything to investigate!

### GET THE BENEFITS OF OUR OVER 50 YEARS EXPERIENCE

Approved for  
GI Training



**NATIONAL SCHOOLS**

Los Angeles 37, Calif.

## YOU GET...

- 19 Big Kits—**YOURS TO KEEP!**
- Friendly Instruction and Guidance
- Job Placement Service
- Unlimited Consultation
- Diploma—Recognized by Industry
- **EVERYTHING YOU NEED FOR SUCCESS!**

### SHOP-METHOD HOME TRAINING COVERS ALL PHASES OF INDUSTRY

1. Television, including Color TV
2. Radio AM & FM
3. Electronics for Guided Missiles
4. Sound Recording and Hi-Fidelity
5. FCC License
6. Automation and Computers
7. Radar & Micro-Waves
8. Broadcasting and Communications

## NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1905

**MAIL NOW TO**  
**NATIONAL SCHOOLS, Dept RG-20**

4000 S. FIGUEROA ST. LOS ANGELES 37, CALIF.

Rush free TV-Radio "Opportunity" Book and sample lesson. No salesman will call.

NAME \_\_\_\_\_ AGE \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_  
 Check if interested **ONLY** in Resident School training at Los Angeles.  
VETERANS: Give date of Discharge \_\_\_\_\_

# News Briefs

**ELECTRONICS AND JETS** may combine to revolutionize distribution of high-value low-bulk merchandise if a new concept in distribution pioneered by Raytheon spreads to distribution of other similar merchandise.

The Raytheon plan includes data-processing machines for receiving and dispatching orders, controlling inventories and keeping accounts, and deliveries largely by jet cargo planes which make the entire country "5 hours wide and 3 hours deep," according to American Airlines, who cooperated in setting up the system.

Special punch-card equipment designed and installed by Western Union can accept a typical order in 17 minutes, fill it in 90 minutes and deliver it to a jet plane at the airport in 45 minutes, making it possible to fill orders anywhere in the United States within 24 hours after the order is placed.

Tel-O-Riginator equipment will be installed first in the 25 district offices of Raytheon's Distributor Products Div., and eventually in the offices of all major distributors of Raytheon products.

**NO MORE WOOFERS & TWEETERS?** So goes the suggestion of Dr. Amar G. Bose, MIT professor who recently patented a speaker system which uses a one-eighth segment of a sphere covered with 22 identical small cones, placed in a corner of the room. Effectively, the whole spherical surface moves in unison

to make those bass notes boom right. Somewhat similar systems, not usually in corners, have been in private use for several years.

**MARS TECHNICAL NET** schedule for February: Feb. 3, "Quartz Crystals in SSB Filters," W. E. Benton; Feb. 10, "Design Philosophy of a Modern SSB Transceiver," Chick Carny; Feb. 17, "Distortion in High-Fidelity Amplifiers," Milton Snitzer; Feb. 24, "High-Power Transmitter Stations," Herbert Hawkins.

Sessions will continue each Wednesday at 9 p.m. EST, 4030 kc, upper sideband, with discussion via net radio following each talk.

**FM STATION** was given away in New York. WBAI-FM, good music station belonging to Louis Schweitzer, chemical engineer and industrialist, was presented by him to nonprofit Pacifica Foundation, to become a listener-sponsored, no-advertising station.

The station will broadcast classical music, with jazz, folk music, children's shows and public affairs programs also aired. Listeners will be asked (but not pressed) to send in \$12 a year to sponsor the station.

A similar operation has been run by Pacifica in Berkeley, Calif., since 1949. KPFA-FM is now nearly self-supporting, with 7,500 paying listeners. Pacifica opened a second station, KPFK-FM, in Los Angeles in mid-1959 and

has almost 5,000 paid subscribers to date.

**FIRST BROADCAST** of opera made by Lee de Forest from the Metropolitan Opera House in New York City Jan. 13, 1910, was celebrated through the month of January with a special exhibit by the New York Public Library. Exhibit included all collectable memorabilia on the historic event.


**TRANSISTOR TELEVISION** set by Emerson was scheduled to go into production this winter. Size of screen was not definitely decided but officials said it would be a full-size picture tube, not a small optically enlarged one like Philco's 2-inch tube-with-lens. The price was expected to be near that of Philco's portable set, \$250. Emerson said its transistors would be American-made.

**IRE WILL HONOR** Dr. Harry Nyquist, authority on feedback analysis, along with Haraden Pratt, J. A. Rajchman, J. W. Gewartowski, K. A. Norton, and E. J. Nalos. Dr. Nyquist will receive the society's 1960 Medal of Honor "for fundamental contributions to a quantitative understanding of thermal noise, data transmission, and negative feedback." Mr. Pratt will get the Founder's Award, the Institute's second highest award, which is bestowed only on special occasions. Seventy-six engineers will be elevated to the rank of Fellow. Among them is William Sichak of ITT, whose picture appeared on our February, 1959, cover.

New officers of the IRE for 1960 include Ronald McFarlan, consultant to Datamatic and Raytheon, president; J. N. Dyer, Airborne Instruments, vice president; and J. A. Ratcliffe, Cavendish Labs (England), vice president.

**ANECHOIC RF TEST RANGE**, in effect, is the antenna test setup at Technical Appliance Corp. between two hilltops in Sherbourne, N. Y., where a 3,000-foot valley between transmitter and receiver location provides near-free-field conditions for checking new antenna designs. Towers installed can handle antennas up to 60 feet in diameter.

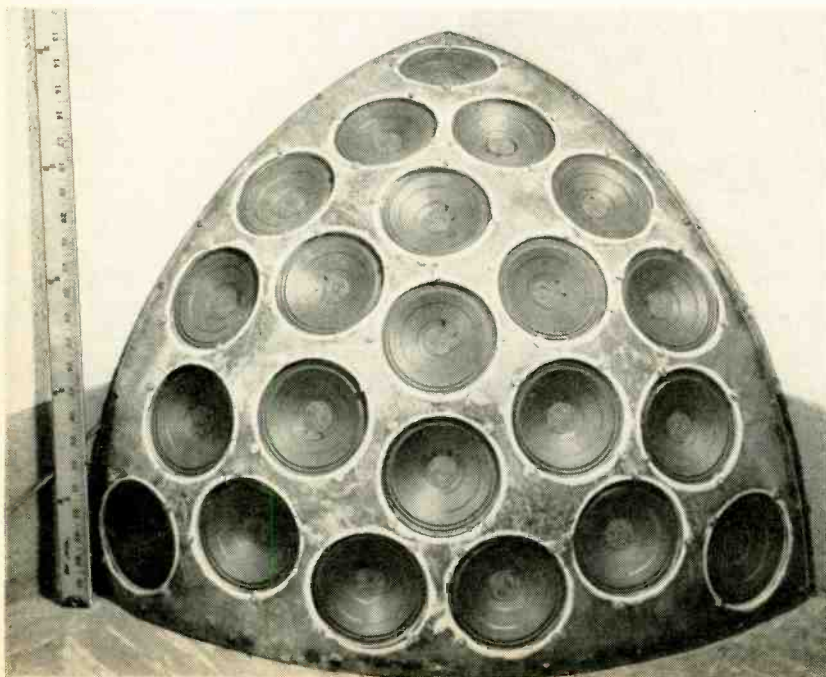**MEDICAL ELECTRONICS** took another step forward with the introduction of an optical probe consisting of thousands of minute spun-glass fibers bound together, with a small lens focusing on their ends. Each of the fibers picks up light from a minute section of the surface ahead of it and transmits it to the other end. The mosaic of spots of light  
(Continued on page 10)




In Spare Time at Home—Prepare for a Better Job—or  
Your Own Business in One of the Many Branches of

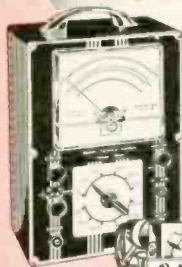
# ELECTRONICS



You build and keep this valuable Vacuum Tube **VOLTMETER**



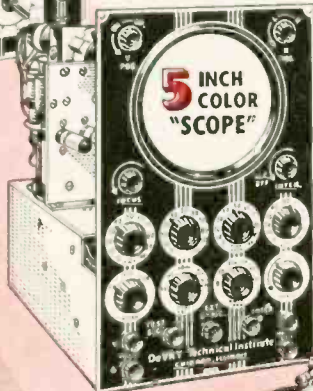You build and keep this 5-inch **COLOR OSCILLOSCOPE**—almost a "must" for TV servicing.



## RADIO - TELEVISION - RADAR

If you are seeking a better job or a business of your own, the appealing field of Television-Radio-Electronics offers **REAL PROMISE!**

In this fast-growing field, trained Electronic technicians find many good-paying, interesting jobs in manufacturing, installing, operating, servicing. Equally important is the fact that these are **GOOD JOBS**—offering the kind of a future that an untrained man often dreams about.

No previous technical experience or advanced education needed. Prepare for this profitable field in your spare time at home, or in our modern Chicago or Toronto Laboratories. Nothing else like it! Send for **FREE** details.




## COLOR TV

DeVry Tech's program also includes training in Color Television

... make important points crystal clear. Speeds your learning. It's almost like having an instructor at your side!

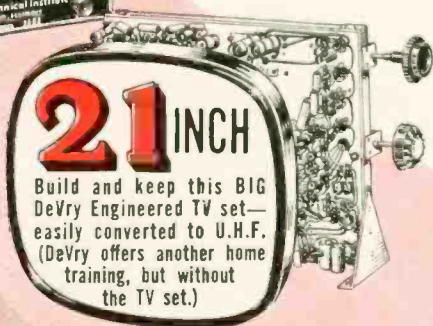If you are subject to military service, the information we have should prove very helpful. Mail coupon to-day.



**21 INCH**

Build and keep this **BIG DeVry Engineered TV set**—easily converted to U.H.F. (DeVry offers another home training, but without the TV set.)

## EARN WHILE YOU LEARN

After you get part of DeVry Tech's training with equipment at home, you may then in your spare time, begin to earn real money servicing Radio and Television sets.

## Your GUIDE

### to Profitable Job Opportunities

TV-Radio Broadcast Technician  
Color Television Specialist  
Radar Operator • Laboratory Technician  
Airline Radio Man • Computer Specialist  
Quality Control Manager  
Your Own Sales & Service Shop

... **PLUS MANY OTHERS**

### YOU GET THE SAME **EMPLOYMENT SERVICE**

that has helped thousands of our graduates toward fine careers in Electronics.



You work over **300** Learn-By-Doing projects



Build over 300 practical projects from many shipments of Radio-Electronic parts. You build and operate TV-Radio circuits... wireless microphone... and many other major projects—all designed to provide outstanding practical experience at home.

Send for **FREE BOOKLET TODAY!**

Accredited Member of National Home Study Council

"One of North America's Foremost Electronics Training Centers"



# DeVRY TECHNICAL INSTITUTE

CHICAGO 41, ILLINOIS

**ACT NOW!** Get information-packed publication **FREE!** Mail coupon today.

### DeVRY TECHNICAL INSTITUTE

4141 Belmont Ave., Chicago 41, Ill., Dept. RE-2-Q

Please give me your **FREE** booklet, "Electronics in Space Travel," and tell me how I may prepare to enter one or more branches of Electronics.

Name \_\_\_\_\_ Age \_\_\_\_\_

Street \_\_\_\_\_ PLEASE PRINT Apt. \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

Canadian residents address DeVry Tech of Canada, Ltd.  
2044 626 Roselawn Ave., Toronto 12, Ontario

*Exclusive 3-way switching puts the*

# TURNER MODEL 250 "LIFT-SWITCH"

*in a class by itself*



microphone

Offers more versatility, convenience and ease of operation than any other

Here's a mike you can sell to meet the needs of any customer. It's ideal for dispatch, paging, P.A., control tower and amateur use. Wired to operate both relay and mike circuits at a touch. The Model 250 "Lift-Switch" is a high impedance dynamic mike with a smooth response from 60 to 10,000 c.p.s., and an output level of -52 db. List price is \$49.50.

*For complete information on the Model 250 and specifications for the 6 other crystal and dynamic models, write today to:*



**THE TURNER MICROPHONE COMPANY**

933 17th St. N.E., Cedar Rapids, Iowa

IN CANADA: CANADIAN MARCONI CO.,  
TORONTO, ONTARIO AND BRANCHES

EXPORT: AD AURIEMA, INC.  
85 BROAD ST., NEW YORK 4, N.Y.

*Exclusive 3-way switching  
arrangement — — —*



**LIFT THE MIKE, IT'S LIVE.** Additional slide lock switch in base deactivates lift switch when necessary.



**DEPRESS THE FRONT BAR** for push-to-talk. Gives "inter-com" convenience in a microphone.



**MOVE THE LEVER-LOCK SWITCH** forward. The mike is live. Both hands are free for work.



# Now

**FOR THE FIRST *time***



*2 year*  
**GUARANTEE**



**2 year guarantee  
on ASTRON  
"Twist-Prong" and  
"Minimite"  
electrolytic  
capacitors**

**BUILD YOUR REPUTATION** with the  
only capacitor line that offers a full  
**TWO** year performance guarantee

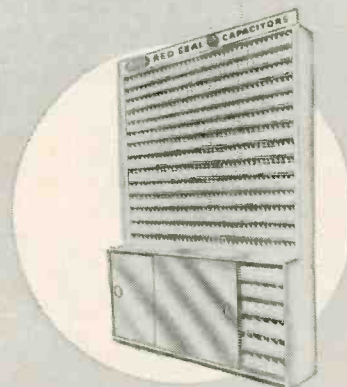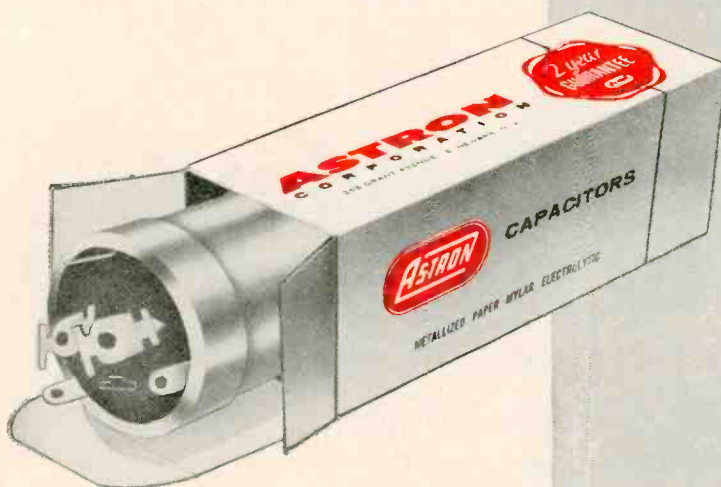The Red Seal is your guide to quality and  
economy. Astron Guaranteed Twist Prong  
Capacitors are available through all better  
distributors now displaying the Red Seal.



Look for the Red Seal  
Capacitor Display Cabinet  
at your "DISTRIBUTOR"



# **ASTRON**

C O R P O R A T I O N  
255 GRANT AVENUE • EAST NEWARK, NEW JERSEY

SEND IMMEDIATELY FOR OUR NEW ALL INCLUSIVE REPLACEMENT CATALOG.

is scanned, then displayed up to 35 times life-size on TV monitors.

Dental and surgical work previously unavailable for observation can now be examined by doctors or classes while operations are in progress.

#### Calendar of Events

**ISA Instrument-Automation Conference and Exhibit**, Feb. 2-4, Sam Houston Coliseum, Houston, Tex.

**Winter Convention on Military Electronics**, Feb. 3-5, Ambassador Hotel, Los Angeles, Calif.

**Solid State Circuits Conference**, Feb. 10-12, University of Pennsylvania, Philadelphia, Pa.

**Cleveland Electronics Conference**, Feb. 11-12, Engineering and Scientific Center, Cleveland, Ohio.

**ERA National Convention**, Feb. 11-13, Drake Hotel, Chicago, Ill.

**EP&EM Educational Seminar**, Feb. 16, Niles, Ill.

**ERA Southern California Chapter Distributor - Representative - Manufacturer Conference**, Feb. 18-20, Palm Springs, Calif.

**Distributor - Representative - Manufacturer Conference**, Feb. 18-21, El Mirador Hotel, Palm Springs, Calif.

**International Electronic Parts Show**, Feb. 19-23, Parc des Expositions, Porte de Versailles, Paris, France.

**Annual EIA Industrial Relations Conference**, Feb. 24-26, Hollywood Beach Hotel, Hollywood, Fla.

**Scintillation Counter Symposium**, Feb. 25-26, Washington, D. C.

**EIA Spring Conference**, Mar. 16-18, Hotel Statler, Washington, D.C.

**IRE National Convention**, Mar. 21-24, Coliseum & Waldorf Astoria Hotel, New York, N.Y.

#### Hi-Fi Show

**IHFH Hi-Fi Show**, Mar. 25-27, National Guard Armory, Washington, D.C.

Details on all events supplied by sponsoring organizations.

**FRAUD IN TV REPAIR** was charged against Fairfax County, Virginia, service dealer T. M. Lowery for charging \$36.30 for repairs he didn't make. Found guilty by Judge J. N. Groves, Lowery was given 15 days in jail, plus a suspended sentence for a year. A detective testified at the trial that all Lowery actually did was replace two small tubes, one unnecessarily, although his bill included such items as "reworking" a sound circuit, reworking the video circuit, restoring high voltage and adjusting the channel selector.

**MICROMINIATURE CIRCUITS** that cost no more than the same ones built with standard components were demonstrated at a press conference by Aero-vox's Hi-Q division at their Olean, N.Y., plant. The photo shows a complete adder circuit designed for use in a ballistic missile computer. It is 50 times smaller than conventional units, measures only  $\frac{1}{2} \times \frac{1}{2} \times 1$  inch and contains 85 components. These units are not the smallest that can be made, but are the smallest ones that can be made at a

(Continued on page 14)

# How to Get

## An FCC License can be

## Get Your FCC License

**We Guarantee**  
to train you until you receive  
**Your FCC License**  
— or your money back

The Master Course in Electronics will provide you with the mental tools of the electronics technician and prepare you for a First Class FCC License (Commercial) with a radar endorsement. When you successfully complete the Master Course, if you fail to pass the FCC examination, you will receive a full refund of all tuition payments.

**Cleveland Institute Training Results in success with commercial FCC examinations . . . easily . . . and quickly.**

# Free!

**FIND OUT HOW:**

1. The new electronic devices can be handled by you
2. To solve the problems that will stump your fellow technicians
3. Training is Job Insurance when employment is tough to find . . . and more money for you when times are good

**Mail Coupon NOW . . .**

(Commercial)

# an FCC License

## your Guarantee of Success in Electronics

### in a Minimum of Time

mail  
coupon  
NOW!


### here's proof of good jobs

Irving Laing:

"Your lessons are helping me a lot in my Navy work. You cover topics that were not presented by the Navy at the E.T. School. . . . Your course has helped greatly to get my 2nd class FCC ticket. I am now a radio and T.V. engineer at WTVS and WDTR in Detroit, Michigan."

*Irving I. Laing,  
15887 Robson,  
Detroit 27, Michigan*

## Get all 3 FREE

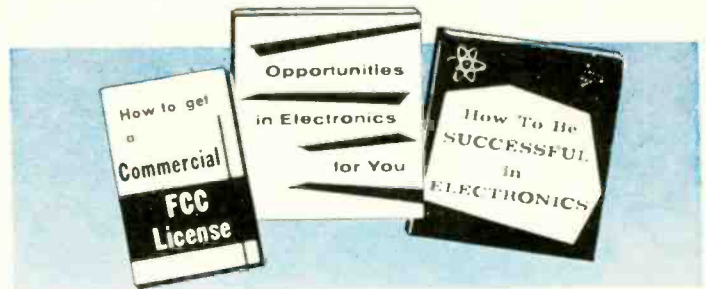

Accredited by The National Home Study Council

**Cleveland Institute of Electronics**

Desk RE 38B, 4900 Euclid Ave., Cleveland 3, Ohio



Please send FREE Booklets prepared to help me get ahead in Electronics. I have had training or experience in Electronics as indicated below:

- |   |   |
|---|---|
| <input type="checkbox"/> Military           | <input type="checkbox"/> Broadcasting       |
| <input type="checkbox"/> Radio-TV Servicing | <input type="checkbox"/> Home Experimenting |
| <input type="checkbox"/> Manufacturing      | <input type="checkbox"/> Telephone Company  |
| <input type="checkbox"/> Amateur Radio      | <input type="checkbox"/> Other.....         |

In what kind of work are you now engaged?.....

In what branch of Electronics are you interested?.....

Name..... Age.....

Address.....

City..... Zone..... State.....

Desk RE 38B

## Receive All These Booklets FREE!




My new plates  
 behave like plates...  
 not filaments

**(FORGET YOUR  
 LOW-VOLTAGE  
 RECTIFIER PROBLEMS)**

**HOW BACK EMISSION  
 IS ELIMINATED**

Back emission from overheated plate to filament causes most rectifier failures. Reverse current mounts... filament is stripped... overheats... burns out.

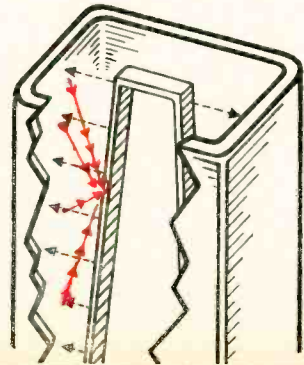That's why the new CBS 5U4GB plates are of non-emissive material, are larger, and run cooler. These and many other advance engineered features make the new CBS 5U4GB the best you can buy. Here's typical proof. Dynamic "blast" tests brutally cycle the tube between 4 and 6.8 volts with 800 volts plate potential. Yet back emission is just measurable... less than one milliamper!



"My new plates don't heat up and start acting like filaments. They can't because my plate material is designed not to emit wrong-way electrons. So back emission can't build up and burn out my filament. And you aren't pestered with premature failures."

That is right. The new CBS 5U4GB offers you *total reliability*... proved in performance by leading TV and radio set manufacturers. You, too, can profit from the *total reliability* of CBS tubes. Just replace with CBS... always.

**TOTAL RELIABILITY...**  
 proved in performance



*Receiving, industrial  
 and picture tubes  
 transistors and diodes  
 audio components  
 and phonographs*

**CBS ELECTRONICS**

Danvers, Massachusetts  
 A Division of Columbia Broadcasting System, Inc.

**COLUMBIA RECORD CLUB offers with pride**  
**the greatest musical achievement since the introduction of stereo records**

The first complete recordings of the  
**9 SYMPHONIES**  
of  
**BEETHOVEN**  
conducted by  
**BRUNO WALTER**


reproduced in glorious

**STEREO**

ALL **\$5.98**  
FOR ONLY

REGULAR RETAIL  
VALUE, \$41.98

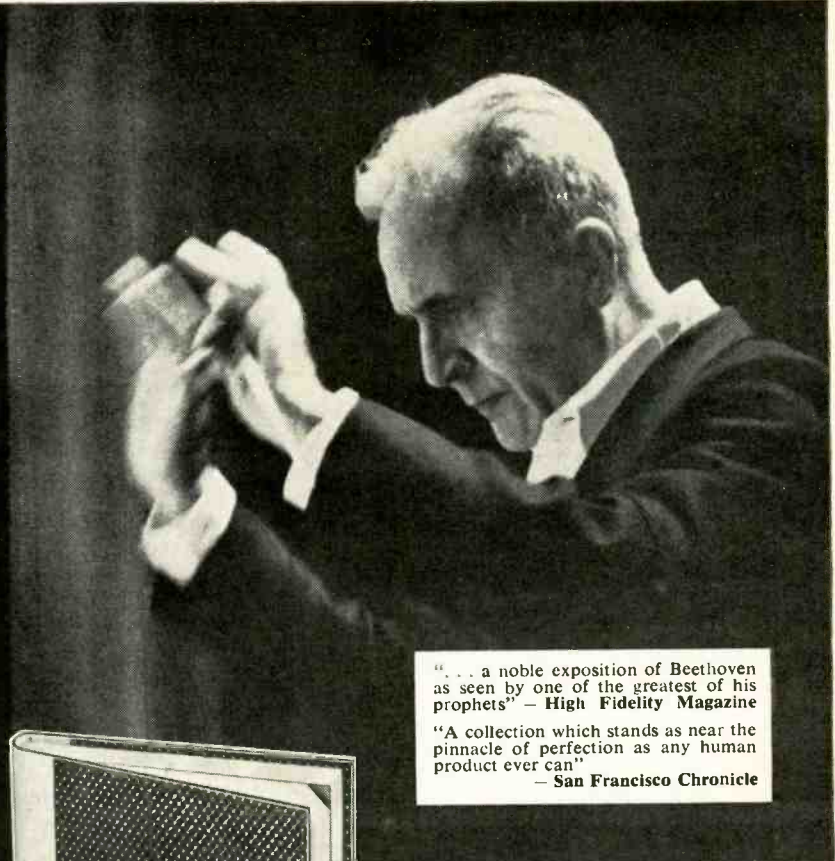if you join the Club now and agree to purchase  
as few as six selections from the more than 150  
to be made available during the coming 12 months



"... a noble exposition of Beethoven as seen by one of the greatest of his prophets" — High Fidelity Magazine  
"A collection which stands as near the pinnacle of perfection as any human product ever can" — San Francisco Chronicle



**NOTE: Stereo records must be played only on a stereo phonograph**

**DELUXE PACKAGE**

Seven 12" Columbia stereo records in a luxurious box, covered with white leather-like Fabrikoid and lustrous black-and-gold cloth. Also includes 48-page booklet with previously unpublished photographs; program notes; anecdotes and reviews by Beethoven's contemporaries and present day critics.

**THE CORNERSTONE OF ANY STEREO LIBRARY...**

If you now own a stereo phonograph, or plan to purchase one soon, here is a unique opportunity to obtain — for only \$5.98 — this magnificent Columbia 7-Record Set containing all nine Beethoven Symphonies... in glowing performances by one of his greatest interpreters, Dr. Bruno Walter... and reproduced with amazingly realistic "concert hall" fidelity through the miracle of stereophonic sound!

**TO RECEIVE YOUR BEETHOVEN SET FOR ONLY \$5.98** — simply fill in and mail the coupon now. Be sure to indicate which one of the Club's two Divisions you wish to join: Stereo Classical or Stereo Popular — whichever one best suits your musical taste.

**HOW THE CLUB OPERATES:** Each month the Club's staff of music experts selects outstanding recordings from every field of music. These selections are described in the Club Magazine, which you receive free each month.

You may accept the monthly selection for your Division... take any of the other records offered (Classical or popular)... or take NO record in any particular month.

Your only membership obligation is to purchase six selections from the more than 150

Columbia and Epic records to be offered in the coming 12 months. You may discontinue your membership at any time thereafter.

The records you want are mailed and billed to you at the regular list price of \$4.98 (Classical and Original Cast selections, \$5.98), plus a small mailing and handling charge.

**FREE BONUS RECORDS GIVEN REGULARLY:** If you wish to continue as a member after purchasing six records, you will receive a Columbia or Epic stereo Bonus record of your choice free for every two selections you buy.

**MAIL THE COUPON TODAY!** Since the number of Beethoven Sets we can distribute on this special offer is limited — we sincerely urge you to mail the coupon at once.

**ALSO AVAILABLE IN REGULAR HIGH FIDELITY!**

If you have a standard phonograph, you may receive the regular high-fidelity version of this Deluxe Beethoven Set for only \$5.98. The plan is exactly the same as outlined above — except that you join any one of the Club's four regular musical Divisions, and you pay only \$3.98 (Popular) or \$4.98 (Classical and Original Cast selections) for the regular high-fidelity records you accept. Check appropriate box in coupon.

**SEND NO MONEY — Mail this coupon now to receive the 9 Beethoven Symphonies for only \$5.98**

**COLUMBIA RECORD CLUB, Dept. 210-9**  
**Terre Haute, Indiana**

Please send me, at once, the Deluxe 7-Record Stereo Set of Beethoven Symphonies, for which I am to be billed only \$5.98, plus a small mailing and handling charge. Enroll me in the following Division of the Club:

(check one box only)

Stereo Classical      Stereo Popular

I agree to purchase six selections from the more than 150 records to be offered during the coming 12 months, at regular list price plus small mailing and handling charge. If I decide to continue my membership, I am to receive a 12" Columbia or Epic stereo Bonus record of my choice FREE for every two additional selections I buy.

If you wish to receive your Beethoven Set in regular high-fidelity, check below the musical Division of your choice. You agree to purchase 6 selections from more than 150 regular high-fidelity records to be offered in the next 12 months.

Classical     Popular     Show Music     Jazz

Name.....  
(Please Print)

Address.....

City..... ZONE..... State.....

*ALASKA and HAWAII: write for special membership plan*  
*CANADA: address 1111 Leslie St., Don Mills, Ontario*


If you want this membership credited to an established Columbia or Epic record dealer, authorized to accept subscriptions, fill in below:

Dealer's Name  
and Address.....

B5-DA (STER)    B5-DG (REG)    59

© Columbia, © Epic, © Marcas Reg. © Columbia Records Sales Corp., 1960

# Mullard TUBES CIRCUITS for STEREO

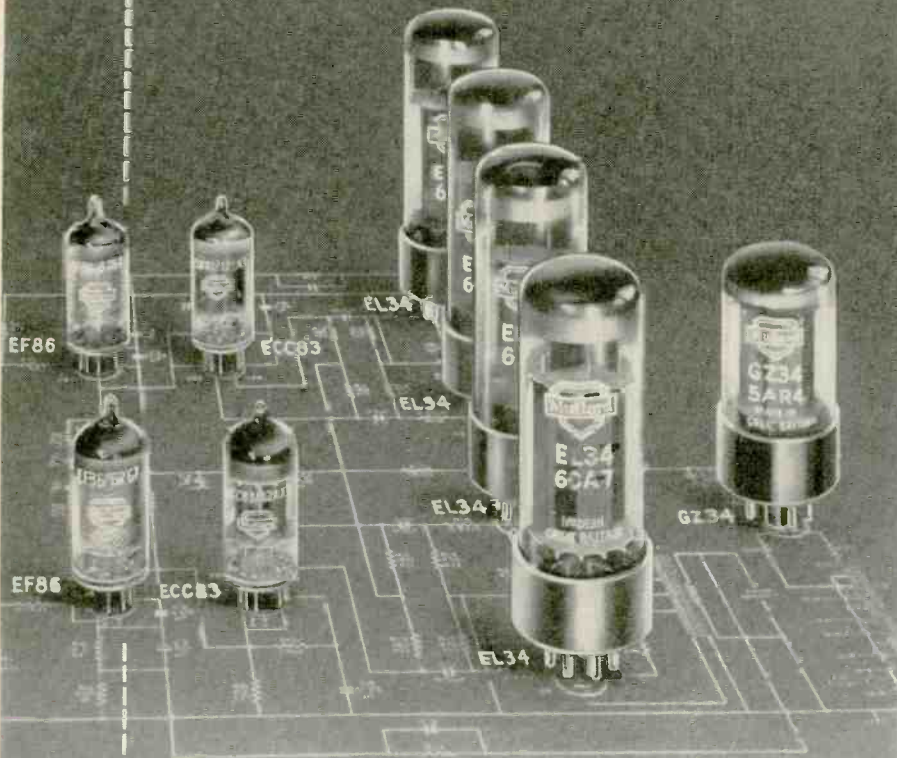

MULLARD tubes and circuits, already acclaimed throughout the world for their advanced engineering and reliability, are in great demand for today's stereo amplifiers.

Heading the preferred list for power output tubes is the MULLARD EL-34/6CA7. This extremely linear output pentode which is capable of 60 watts push-pull in Class AB<sub>1</sub> (60 watts per channel stereo—120 watts monophonic) gives a special superiority even to the finest components. This linearity coupled with a uniformity that is already well known make the MULLARD EL-34/6CA7 the first choice for superb sound reproduction.

Design and build your stereo equipment around MULLARD. Circuit and interchangeability data for all MULLARD Electron Tubes are available at your distributor or write to Technical Services Division.


"Circuits for Audio Amplifiers" is a new MULLARD publication in which the wide range of MULLARD high quality audio circuits is presented conveniently in one book. Four introductory chapters are devoted to theoretical and practical considerations of high quality sound reproduction with monophonic equipment or with stereophonic systems. The rest of the book comprises circuit descriptions, constructional details, and some performance figures of 12 MULLARD circuits. These circuits include well-known MULLARD designs, some modifications and improvements to these circuits, and a number of completely new ones. Only \$2.50 from your dealer or by mail from our Technical Services Division.

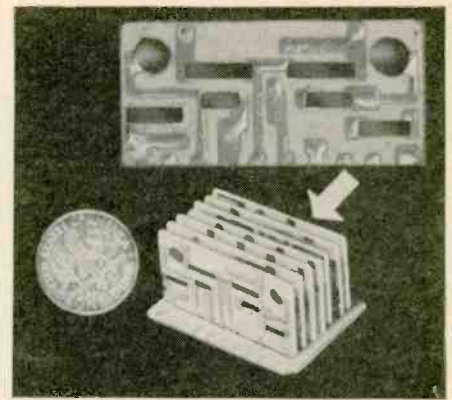**Mullard**

Trade Mark  
Mullard Ltd.



**INTERNATIONAL ELECTRONICS CORP.**  
81 SPRING ST., NEW YORK 12, N. Y.



price comparable with standard versions.

Two advanced types of capacitors now in production—Cerafil and Cerol—were also shown. Both are ceramics and are made in a way that makes great size reduction possible.

To make a Cerafil capacitor, Aerovox starts off with a ceramic tube about 1/32 inch in diameter. The tube's outer surface is metallized, and the metallized layer acts as one of the electrodes. Over the metallized surface, a thin film of ceramic dielectric is formed and over the dielectric goes another metallized layer for the other electrode. A single finished tube or a parallel combination makes up the finished unit, depending on its capacitance. Leads, protective coating and color coding are the final steps.

The Cerafil line covers values from 10  $\mu\text{f}$  to 0.1  $\mu\text{f}$ . Up through the .001- $\mu\text{f}$  units, they measure .090 inch in diameter and 0.320 inch long. The 0.1- $\mu\text{f}$  units are 0.310-inch diameter and 0.750 inch long.

As it is not practical to make Cerafil capacitors larger than 0.1  $\mu\text{f}$  at this time, Aerovox has developed a rolled type ceramic-dielectric capacitor for the larger capacitance values of 0.1  $\mu\text{f}$ –2  $\mu\text{f}$ . The 0.1- $\mu\text{f}$  capacitors are 0.210 inch in diameter and 0.690 inch in length, and the 2- $\mu\text{f}$  units are 0.400 inch in diameter and 1.44 inches long. All Cerafil and Cerol units are rated at 100 volts at 85°C.

USSR SPACE TIMETABLE may be far ahead of ours, Dr. Eberhardt Rehtin, telecommunications chief of the Jet Propulsion Laboratory, said in a speech in which he also declared that continuing space programs at their present level is largely a waste of money.

According to Dr. Rehtin, Soviet space scientists have presented a plan under which a Soviet satellite carrying two men will, within the next few months, orbit the earth for 2 weeks, and shortly afterward two men with a television camera will make a round trip to the moon. This may be followed by another rocket in which two men and two women will make a trip around the moon lasting a half-year. In 1961, Soviet scientists expect to send rockets to Mars and Venus.

(Continued on page 18)

# F.C.C. COMMERCIAL OPERATOR LICENSE

## Training... for Jobs in Electronics

### F.C.C. LICENSE—THE KEY TO BETTER JOBS

An F.C.C. *commercial* (not amateur) license is your ticket to higher pay and more interesting employment. This license is Federal Government evidence of your qualifications in electronics. Employers are eager to hire *licensed* technicians.

### WHICH LICENSE FOR WHICH JOB?

The **THIRD CLASS** radiotelephone license is of value primarily in that it qualifies you to take the second class examination. The scope of authority covered by a third class license is extremely limited.

The **SECOND CLASS** radiotelephone license qualifies you to install, maintain and operate most all radiotelephone equipment except commercial broadcast station equipment.

The **FIRST CLASS** radiotelephone license qualifies you to install, maintain and operate every type of radiotelephone equipment (except amateur) including all radio and television stations in the United States, its territories and possessions. This is the highest class of radiotelephone license available.

### GRANTHAM TRAINING PREPARES YOU

The Grantham Communications Electronics Course prepares you for a **FIRST CLASS** F.C.C. license, and it does this by **TEACHING** you electronics. Each point is covered simply and in detail, with emphasis on making the subject easy to understand. The organization of the subject matter is such that you progress, step-by-step, to your specific objective—a first class F.C.C. license.

### CORRESPONDENCE OR RESIDENCE CLASSES

Grantham training is offered by correspondence or in resident classes. Either way, we train you quickly and thoroughly—teach you a great deal of electronics and prepare you to pass the F.C.C. examination for a *first class* license. Your first class F.C.C. license is the quick, easy way to prove to your employer that you are worth more money.

Our training (either in resident classes or by correspondence) prepares you for a first class F.C.C. license in as little as 12 weeks. Most of our *correspondence* students take longer than 12 weeks to finish the course and get their first class licenses, but most of our full-time *resident* students get their first class licenses in 12 weeks or less. If you are a beginner in electronics, this F.C.C. license plus the electronic theory we teach you will qualify you for certain types of employment, and you can improve your practical ability while on the job earning a salary. On the other hand, if you already have practical experience, the Grantham course can add a thorough knowledge of theory and an F.C.C. license to that practical experience—a most important step in qualifying you for higher pay and greater job security.

Our free booklet gives details of how you can prepare quickly for a better job in the rapidly expanding electronics industry. Clip the coupon below and mail it to the Grantham School nearest you.

**FOUR COMPLETE SCHOOLS:** *To better serve our many students throughout the entire country, Grantham School of Electronics maintains four complete Divisions—located in Hollywood, Calif., Seattle, Wash., Kansas City, Mo., and Washington, D.C. All Divisions of Grantham School of Electronics offer the same rapid courses in F.C.C. license preparation, either by home study or in resident classes.*

Get your First Class Commercial F.C.C. License in 12 weeks by training at

# Grantham School OF ELECTRONICS

HOLLYWOOD  
CALIF.

1505 N. Western Ave.  
Hollywood 27, Calif.  
(Phone: HO 7-7727)

SEATTLE  
WASH.

408 Marion Street  
Seattle 4, Wash.  
(Phone: MA 2-7227)

KANSAS CITY  
MO.

3123 Gillham Road  
Kansas City 9, Mo.  
(Phone: JE 1-6320)

WASHINGTON  
D. C.

821-19th Street, N. W.  
Washington 6, D. C.  
(Phone: ST 3-3614)

for **FREE** Booklet **CLIP COUPON** and mail  
in envelope or paste on postal card.



To: **GRANTHAM SCHOOL OF ELECTRONICS**

1505 N. Western • 408 Marion • 3123 Gillham Rd. • 821-19th, NW  
Hollywood • Seattle • Kansas City • Washington

Please send me your free booklet telling how I can get my commercial F. C. C. license quickly. I understand there is no obligation and no salesman will call.

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

I am interested in:  Home Study,  Resident Classes

04-B

MAIL COUPON NOW

# WINEGARD Antenna Dealers to Make 1960



**PAUL HARVEY**  
Sells Winegard Gold  
Color'Ceptor Antennas  
on National ABC Radio Network

*"I'll be telling your customers why the Winegard Gold Color'Ceptor TV antenna is America's best antenna buy. I suggest you stock up on Color'Ceptors now to take advantage of Winegard's advertising and make more profit in 1960."*


Tune in Paul Harvey News, ABC Network, Monday through Friday 5:55 E.S.T., starting January 18. (Check local listings for time and station.)

## Profit with the Antenna Dealers have learned to trust

*Winegard dealers make more money for  
three important reasons—*

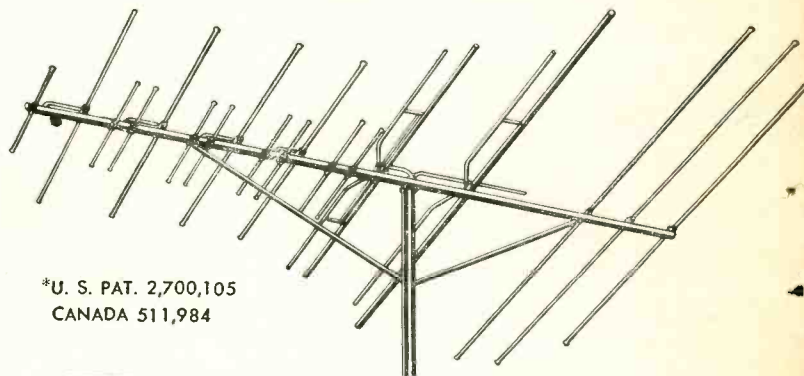1. They have the best performing, easiest to install, best constructed and neatest looking antenna on the market in the Winegard Gold Color'Ceptor.
2. They have the only *written* Performance Guarantee in the industry that guarantees 100% customer satisfaction or full list price of antenna refunded by Winegard—and the dealer still keeps his profit.
3. They get the antenna industry's biggest advertising backing.

Three Color'Ceptor models meet all needs: CL-4, \$29.95; SCL-4, \$38.95; CL-4X (with power pack) \$44.90



\*U. S. PAT. 2,700,105  
CANADA 511,984

### **Winegard Gold Anodizing**

Winegard's special 7 cycle bright gold anodizing inside and out (not a cheap flash finish) hardens the antenna surface, seals out corrosion and weathering, exceeds U.S. Gov't specifications in salt spray tests.

Winegard performance is protected by U.S. patents, confirmed by leading consumer researchers, by millions of happy users, by prospering dealers everywhere. First with the advancements the public wants and sales-minded dealers can sell! Feature the leader and be one!



# Get Biggest Ad Backing Biggest Profit Year Ever!

**NOT here today and gone tomorrow... but ALL YEAR LONG!**

Big Winegard Gold Color'Ceptor ads in the biggest consumer magazines... Paul Harvey on Network Radio... The Antenna Industry's biggest and most helpful advertising keeps hammering away, stronger and better than ever!



**YOUR NAME HERE**



Giant 6-ft. 3-color metal road sign... with your name on it.



Balloons—With Winegard selling message—

## DEALER SALES HELPS

to connect Winegard's ad powerhouse to your cash register. To use in your store, outside your store, and out where the sales begin. Get these sales helps (delivery prepaid) with FREE "PROMOTION BUCKS". One "Buck" goes with each Color'Ceptor you order. Use your "Bucks" to get the sales helps that will do you the most good.



Illuminated window and counter sign.



Gold anodized telescopic antenna display mast.



Truck decals, pressure-sensitive. No water.



Metal outdoor store sign with hanger.

# Winegard

ANTENNA  SYSTEMS

WINEGARD CO. 3009-1 Scotten, Burlington, Iowa

### WINEGARD CO.

3013-2 Scotten, Burlington, Iowa

- RUSH full color brochure showing Winegard's new antenna dealer sales aids... and tell me how I can get them free!
- Send literature on Winegard's complete line of FM and TV antennas.

NAME \_\_\_\_\_

POSITION \_\_\_\_\_ FIRM \_\_\_\_\_

ADDRESS \_\_\_\_\_

# What's the latest score on cartridges?

✓	<b>1<sup>ST</sup></b>	ceramic cartridge was invented by Sonotone...
✓	<b>13</b>	years ago. Today, over...
✓	<b>65</b>	different manufacturers have specified Sonotone for...
✓	<b>662</b>	models of high-quality phonographs. Altogether over...
✓	<b>9,000,000</b>	Sonotone Ceramic Cartridges have been used for original and replacement purposes. ('Nuff said!)

**Sonotone** CORP.

Electronic Applications Division, Dept. C2-20

**ELMSFORD, NEW YORK**

In Canada, contact Atlas Radio Corp., Ltd., Toronto

Leading makers of fine ceramic cartridges, speakers, microphones, electronic tubes.

## NEWS BRIEFS (Continued from page 14)

A more hopeful note was struck by Noah Dietrich, head of the Houston Fearless Corp., who stated that America has shaken off its complacency because of recent Russian advances. He predicted that we will now entirely eclipse Russian advances in missiles and space.

**JACK BINNS**, famed as the radio operator who sent the first radio distress signal to save a ship at sea (1909), died December 8, 1959, at the age of 75.

His CQD summoned aid to the sinking ship *Republic*, with the result that all 1,600 passengers and the crew were taken off the ship before it sunk.

Mr. Binns was born in England and



worked for the Marconi Co. as a wireless operator for 7 years. He later was a reporter for the *New York American* and then worked on the staff of the *New York Tribune*. Joining the Hazeltine Corp. in 1924, he became president in 1942, chairman of the board in 1952 and, at the time of his death, was honorary chairman of the board.

**ELECTRONIC LUNGS, HEART** and other vital organs were seen by Gen. David Sarnoff in his crystal ball as replacements for damaged body parts. "Miniaturized electronic components," he thought, might eventually be developed "to serve as long-time replacement for organs that become defective through injury or age." He also predicted an electronic "dashboard"—a home device like the bathroom scale, which would "register heartbeats, blood pressure, pulse, with an alarm system," warning when to call the doctor.

**FM CAR RADIO** is now in production by Motorola. Designed for under-dash mounting in all 12-volt automobiles, the model FM-900 uses seven tubes, three transistors. Output is 15 watts push-pull. It works off regular AM car antenna, and includes afe.



FM car radios will also be offered by other makers, according to predictions by Standard Coil President J. O. Burke, "the industry is near a breakthrough on practical use of FM radios in automobiles." And Radio Condenser Corp. officials say that at least 6 manufacturers are considering production of FM car sets.

**DR. OLIVER E. BUCKLEY.** Bell Labs president and board chairman until his retirement in 1952, died Dec. 14 at the age of 72. Dr. Buckley was an outstanding scientist and administrator who also had served the US in numerous advisory capacities.

His early work included production and testing of power tubes for the first



trans-Atlantic voice radio contact (1915) and research leading to laying of transoceanic phone cables to Europe, Hawaii and Alaska. He held 43 patents.

Among other honors he received were the Edison Medal of the American Institute of Electrical Engineers and this nation's highest civilian award, the Medal of Merit.

**19-INCH TV TUBE** with square corners, which will join its big brother 23-inch picture tube this year, is seen likely to replace a large share of the 17-inch market. The 19-inch screen will appear in portables, will also replace some lower-priced 21-inch sets using 114° deflection, it can work in 110° circuits.

Added to set makers producing 23-inch sets were RCA, Zenith and Motorola. Previously using 23-inchers were Westinghouse, Admiral, Sylvania, Hoffman and others.

**INTERNATIONAL** Telecommunications Union (ITU) elected G. C. Gross of the US to be secretary general for next 3 years as it adjourned its once-every-10-years meeting which deals with radio spectrum allocations.

Prior to service with the ITU, Mr. Gross headed the FCC's International Technical Div.

**NEW SEMICONDUCTOR** material is gallium phosphide, which can operate at temperatures up to seven times as high as can silicon. The Signal Corps has made working diodes of the material which promises to solve some of the severe high-heat problems of guided missiles and space electronics. **END**

# 3 NEW STEREO AMPLIFIERS

FROM




# H. H. SCOTT



**299**  
**40 Watt**  
**Stereo Amplifier**  
**\$199.95\***

**Third Channel Output, Separate Tone Controls Make These The Most Versatile Amplifiers You Can Buy!**

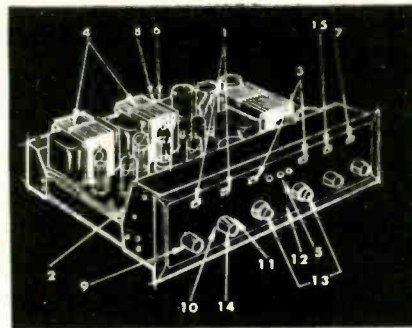H. H. Scott's 299 Stereo Amplifier has been acclaimed "world's most versatile" by editors of all leading hi fi magazines. Like all H. H. Scott stereo amplifiers, it includes a third channel to give optimum realism in stereo playback and a signal for driving extension speak systems. Other advanced features include special balancing facilities and *separate* tone controls on each channel to let you adjust for tonal differences in speakers and room acoustics.



1. Provision for connecting two phono cartridges.
  2. D.C. Filament supply to virtually eliminate hum.
  3. Separate record scratch and rumble filters.
  4. Dual 20 watt power stages. 5. Visual signal light panel. 6. Stereo tape recorder output. 7. Phase reverse switch. 8. Third channel output. 9. Compensation for direct connection of tape playback heads. 10. Special switching to use your stereo pickup on monophonic records. 11. Play a monophonic source through both channels simultaneously. 12. Can be used as an electronic crossover. 13. Completely separate Bass and Treble controls on each channel. 14. Special balancing circuit. 15. Loudness compensation.
- Specifications: Distortion (first order difference tone) less than 0.3%. Frequency Response: 20 cps to 30,000 cps. Harmonic Distortion: 0.8% at full power output. Noise and Hum: Hum better than 80db below full power output; noise equivalent to 10 microvolts on low level input.

### 222 24 Watt Stereo Amplifier

This budget priced stereo amplifier has such features as Third Channel Output and separate tone controls usually found only in much more expensive equipment. It is backed by H. H. Scott's reputation for quality and engineering leadership. \$159.95\*



### 130 Stereo Preamplifier

All the features of the 299 plus many more. Used where it is desired to separate heat producing power amplifiers from control location or where higher power is required than available in integrated amplifiers. \$169.95\*



\*Slightly higher West of Rockies. Accessory case extra.

**H. H. SCOTT**

H. H. Scott, Inc. 111 Powdermill Road, Dept. RE-2 Maynard, Mass.

Rush me new catalog and complete technical specifications on all new H. H. Scott components.

Name.....

Address.....

City..... State.....

Export: Telesco International, 36 W. 40th St., N.Y.C.

HEAR THE FABULOUS LONDON-SCOTT INTEGRATED STEREO ARM AND CARTRIDGE



## A Valuable Service for Industrial Servicemen—Free

If you're a serviceman planning a career in industrial electronics, you can't afford to miss out on this opportunity to get *Tung-Sol Tips* regularly and without cost. Every issue of Tung-Sol's monthly feature is crammed-full of vital technical information aimed at giving you a broad understanding of industrial components and equipment. Everything from theory of operation to application, installation and maintenance.

Coming up soon are wide-ranging articles on:

- ▶ D.C. Amplifiers and Choppers
- ▶ Mobile Communications with a special issue devoted to single-side band operation.
- ▶ Induction Heating Systems.
- ▶ Temperature Control Systems.
- ▶ Weight Control and Batching.
- ▶ Closed Circuit Television.

And these are just a few of the many topics to be discussed in Tung-Sol's highly informative series.

With every issue you'll be building your own valuable storehouse of information designed specifically to give you the facts you need for your job. Write today asking to be put on the *Tung-Sol Tips* mailing list. Tung-Sol Electric Inc., Newark 4, New Jersey.

### Back Issues

You can still get back issues of Tung-Sol Tips which you might have missed, including: (1) Semiconductor Rectifiers; (2) Gas-Filled Rectifiers; (3) Theory of Thyatron Operation; (4) Practical Applications of Thyatrons; (5) Photo-Electric Theory and Operations; (6) A. C. Amplifiers. Write and specify which you would like to receive.

**ts TUNG-SOL®**  
ELECTRON TUBES • SEMICONDUCTORS

## Correspondence



### WANTS INDUSTRIAL TECHNICIANS

Dear Editor:

Regarding Lester Berry's letter on servicing industrial electronic equipment, our company is presently looking for qualified service organizations throughout the country to service our equipment.

We would like very much to hear from technicians and get their views and opinions on this sort of service.

We hope that you will continue your articles on industrial electronics equipment. These articles may stimulate service organizations into doing this kind of work.

RONALD WAGNER

Jordan Controls Co., Inc.  
3235 W. Hampton Ave.  
Milwaukee 9, Wis.

### MICRO-INCH, NOT MICRON!

Dear Editor:

I have noticed that tape recorder manufacturers and magazines such as your own have been describing tape head gap widths in terms of "micron" when they mean micro-inch. For example, "90 microns" instead of .000090 inch, or 90 millionths of an inch.

A micron is a unit in the metric system, a millionth of a meter. Thus 90 microns equals 0.0035 inch; 120 microns would be .0047 inch—very sizable gaps! In other words, a micron is almost 40 times as big as a micro-inch!

All scientific work and measurements are based on the metric system, of which the micron is a part. Think what confusion would be wrought by the unthinking introduction of a new meaning for the term "micron"! Micro-inch is after all an economical term, and it does mean a millionth of an inch, which micron does not.

PHILIP N. BRIDGES

Rockville, Md.

### INDUSTRIAL SERVICING

Dear Editor:

Lester Berry's letter in your December issue in regard to industrial service requires an answer.

There is no doubt that manufacturers of industrial electronic equipment sometimes shun the radio-TV service technician who inquires about servicing its equipment or asks for technical information.

The typical manufacturer of industrial electronic equipment is desperately looking for independent service operators to service the equipment he sells. However, because the public relations

aren't all they should be (for the TV service industry) many of these manufacturers are afraid to turn over their customers to a TV service shop. It isn't that the fully informed feel that way, but the bad press the industry has received causes manufacturers to use extreme caution.

It has been established that manufacturers of industrial electronic equipment need independent service organizations, and that many TV service shop proprietors are interested in industrial business. The two must get together. The problem is a matter of adequate communication and lack of salesmanship. The manufacturer must be sold on the idea of a TV service shop being able to handle industrial servicing.

The service technician, looking for industrial service business, should put on a better front. Unfortunately, the manufacturer looks upon him as a tradesman in whitecoats with no finesse in handling industrial customers. The service technician must wear his salesman's hat and sell the manufacturer on depending upon him so the manufacturer can in turn sell him to the customer with complete confidence.

There is no easy answer. But, the fact remains that the service technician and the equipment manufacturer need each other.

LEO G. SANDS

Ridgewood, N. J.

### RESEARCH INFORMATION CENTERS

Dear Editor:

I read your editorial "Millions of Electronic Facts" (December, 1959, page 27) with interest and would like to add to it. For 14 years I have applied considerable study and research to the problem of information centers.

The principal factor preventing establishment of centers such as you advocate is that there is a considerable amount of time and expense required in setting up such a program, during which no benefits can be expected. Management in general has therefore turned thumbs down on these projects. This may seem short-sighted, but since the program would not bolster profits during its initial stages, this attitude is justified from a practical viewpoint.

The crux of the development has been an automated cross-reference indexing system. As an individual worker in the field, I have found the most frustrating factor to be the lack of funds to demonstrate the complete system.

An example of the advances to be expected with this system:

Just 3 typist-operators could process 1,780 cross-referenced abstracts a day. Present systems require 24 typists, plus several file clerks. This would take care of the roughly 240 important electronic English-language journals presently published monthly. Such cross-referenced abstracts would be in form to be filed by machine or by any other method.

I believe that this is one of the more  
(Continued on page 26)


**WE'RE MAKING IT EASIER THAN EVER TO BECOME A WELL PAID  
RADIO-TELEVISION SERVICE TECHNICIAN**

**NOW - Just \$6 Starts You Training in  
RADIO-TELEVISION**

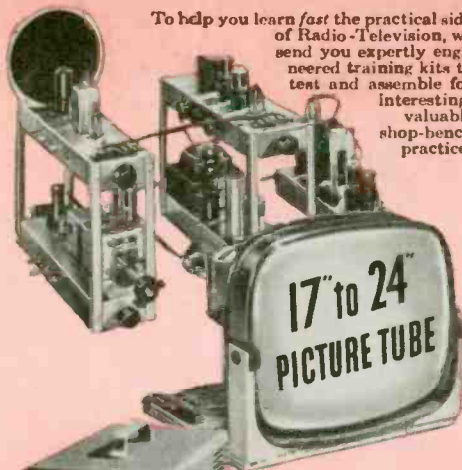**the SPRAYBERRY "Learn-by-Doing" Way . . .**

**25 BIG, COMPLETE KITS  
of PARTS & EQUIPMENT**


To help you learn *fast* the practical side of Radio-Television, we send you expertly engineered training kits to test and assemble for interesting, valuable shop-bench practice!




• The new Sprayberry Training Television Receiver, built and tested in 5 sections.

• Now offered . . . this fine modern oscilloscope.

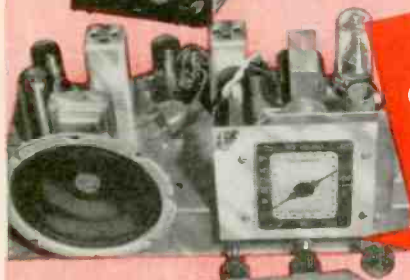• You build this powerful two-band superheterodyne radio receiver.



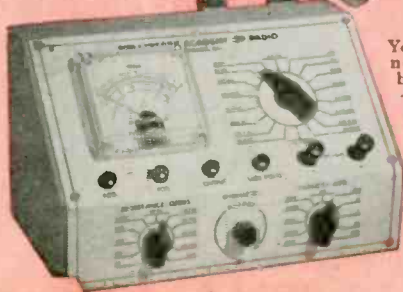**Big New  
CATALOG  
AND  
Sample Lesson  
FREE!**



You build the new Sprayberry tester—a complete 18-range Volt-Ohm-Milliammeter test meter.



★ ★ ★ ★ This great industry is begging for trained men . . . to step into good paying jobs or a profitable business of their own! Our new plan opens the doors of Radio-Television wide to every ambitious man who is ready to act at once!

Men by the thousands . . . trained Radio-Television Service Technicians . . . are needed at once! Perhaps you've thought about entering this interesting, top paying field, but lack of ready money held you back. Now—just \$6 enrolls you for America's finest, most up to date home study training in Radio-Television! Unbelievable? No, the explanation is simple! We believe Radio-Television *must* have the additional men it needs as quickly as possible. We are willing to do our part by making Sprayberry Training available for less money down and on easier terms than ever before. This is your big opportunity to get the training you need . . . to step into a fine job or your own Radio-Television Service Business.

**Complete Facts Free—Act Now; Offer Limited**

Only a limited number of students may be accepted on this liberal and unusual basis. We urge you to act at once . . . mail the coupon below and get complete details plus our big new catalog and an actual sample lesson—all free. No obligation . . . no salesman will bother you.

**HOME STUDY TRAINING IN SPARE TIME**

Under world-famous 27-year old Sprayberry Plan, you learn entirely at home in spare time. You keep on with your present job and income. You train as fast or as slowly as you wish. You get valuable kits of parts and equipment for priceless shop-bench practice. And everything you receive, lessons and equipment alike, is all yours to keep.

**LET US PROVE HOW EASILY YOU CAN LEARN!**

Radio-Television needs YOU! And Sprayberry is ready to train you on better, easier terms, that any ambitious man can afford. Just \$6 starts you! Mail coupon today . . . let the facts speak for themselves. You have everything to gain. Let us prove the kind of opportunity that's in store for you!

**SPRAYBERRY Academy of Radio-Television**  
1512 Jarvis Avenue, Dept. 20-G, Chicago 26, Illinois

**Mail This Coupon Now—No Salesman Will Call**


**Sprayberry Academy of Radio-Television**  
Dept. 20-G, 1512 W. Jarvis Ave., Chicago 26, Ill.

Please rush all information on your ALL-NEW Radio-Television Training Plan. I understand this does not obligate me and that no salesman will call upon me. Include New Catalog and Sample Lesson FREE.


NAME . . . . . Age . . . . .

ADDRESS . . . . .

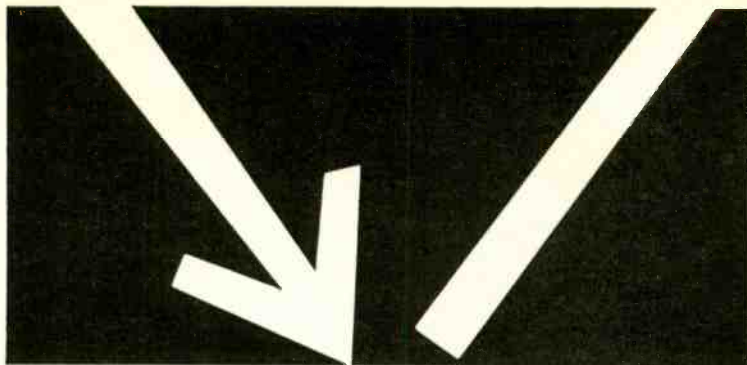CITY . . . . . ZONE . . . . . STATE . . . . .


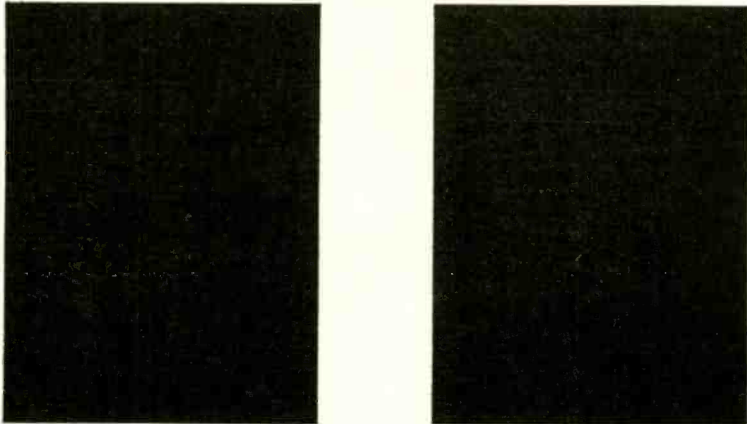
## HOW MUCH DO YOU KNOW ABOUT TRANSISTORS ?



Attend the

**Delco Electronics—One Week  
—Advanced Training School** No tuition charge  
No laboratory fees  
Textbooks supplied

Bring yourself up to date on transistors and other modern electronic equipment with personalized instruction at the Delco Electronic training school to be held soon at a General Motors Training Center near you. Classes are conducted by graduate engineers with special training in your field.

The Delco Radio diploma, awarded only to those who successfully complete the courses, will mean a great deal to you—and to your customers.

The Delco Electronics—One Week—Advanced Training Schools will be conducted in the General Motors Training Centers indicated below. One of them is near you. Register now through your local Delco Electronic Parts Distributor or write directly to Delco Radio Division, General Motors Corporation, Kokomo, Indiana, Attention: Service Manager.

### COURSES OF STUDY OFFERED AT NO COST TO YOU:

- ① Transistor Fundamentals—complete coverage of transistor theory without the use of mathematics.
- ② Transistor Circuit Trouble-shooting—lecture and lab work analyzing defects in transistor circuits.
- ③ Hybrid-type Automobile Radios—low voltage tube and output transistor circuits. Lecture and lab.
- ④ Trouble-shooting procedures for dead or weak low voltage auto radios—factory developed techniques that are foolproof.
- ⑤ Lecture and lab practice on "Signal Seeker" and "Wonder Bar" auto radio tuners and trigger circuits.
- ⑥ Guide-Matic Headlamp Control (Autronic Eye)—lecture and lab.
- ⑦ Twilight Sentinel Automatic Headlight Switch—lecture and lab.
- ⑧ Garage Door Operators—lecture and lab work including the new Delco Radio all-transistor control units.
- ⑨ Auto Portable Radios—lectures on circuitry of both 1959 and 1960 auto portable radios.

**DELCO**  
DEPENDABILITY  
**RADIO**  
RELIABILITY

DELCO ELECTRONICS TRAINING SCHOOL SCHEDULE						
DATE	REGION 1	REGION 2	REGION 3	REGION 4	REGION 5	REGION 6
1-11	Philadelphia	New Orleans	Chicago			
1-18				St. Louis	Dallas	Salt Lake City
1-25		Atlanta	Detroit			
2-1	Union			Omaha	Memphis	
2-8						Los Angeles
2-15	Pittsburgh	Jacksonville				
2-22	Pittsburgh		Cincinnati			
2-29				Kansas City		
3-7	Tarrytown	Charlotte		Kansas City	Dallas	Portland
3-14			Cleveland			
3-21				Omaha	El Paso	
3-28	Boston	Atlanta				Los Angeles
4-4	Boston		Chicago	Minneapolis		
4-11				Minneapolis	Houston	
4-18	Union	Washington	Milwaukee		Houston	San Francisco
4-25		Washington				
5-2			Cincinnati	Omaha		Portland
5-9	Buffalo				Okla. City	
5-16		Atlanta	Detroit	St. Louis		
5-23						Los Angeles
6-6	Tarrytown		Chicago		Dallas	
6-13		New Orleans				San Francisco
6-20	Philadelphia			Denver		
6-27			Cleveland		Memphis	Salt Lake City

why  
the most  
advanced  
professional  
cartridge...



**Electro-Voice**® NEW MAGNERAMIC \* 31 MD7

has ceramic  
elements!

For more than 35 years, Electro-Voice has been a leader in the development and manufacture of dynamic microphones and loudspeakers. Why then, with this extensive experience in designing and producing electro-magnetic devices, is Electro-Voice introducing the new Magneramic 31 Series stereo cartridge using ceramic elements?

The reason is that Electro-Voice is genuinely convinced that a precision ceramic cartridge is the finest type that can be made today . . . definitely superior to the magnetic type. The superiority of the Magneramic 31 is demonstrated in these three areas.

**GREATER FLEXIBILITY** — The 31 Series cartridge will operate perfectly at any stylus pressure from 2 to 20 grams. The same stylus assembly can be used for operation on both turntable and record changers; performance need not be compromised by using a special, stiff stylus assembly for record changers. Record wear is the only criterion in setting stylus pressure — cartridge operation is not affected. Thus, when converting from a changer to a turntable, or vice versa, replacement of the stylus assembly is not necessary when using the Magneramic 31.

**HIGHER OUTPUT** — Along with the trend toward less efficient speaker systems, more amplifier power has become a necessity. While most stereo amplifiers are now designed with input sensitivities to match the typical 5-millivolt output of magnetic stereo cartridges, nearly all monaural amplifiers were designed for at least 8-millivolt input. These cannot be driven to full output with a magnetic stereo cartridge. The Magneramic 31 develops a full 8-millivolt output and couples directly into any "magnetic" preamp unit. This higher output should especially be considered by those planning conversion to stereo utilizing existent monaural amplifiers.

**FREEDOM FROM HUM** — The increased amplifier gain required to satisfactorily drive low-efficiency speakers coupled with decreased cartridge output has significantly increased system hum problems. Also, conventional methods of hum elimination used in monaural magnetic cartridges become difficult or impossible to apply to stereo magnetics. The Magneramic 31 completely eliminates these problems — it is non-inductive and has adequate output.

The Electro-Voice Magneramic 31 MD7 cartridge directly replaces any monophonic or stereophonic magnetic cartridge now on the market. It feeds into the preamp input-jack specified for magnetic cartridges and does not require adaptors or circuit modifications.

**SPECIFICATIONS — MAGNERAMIC 31 MD7**

*Response Range:* 20 to 15,000 cps  $\pm$  2 db  
*Compliance, Vertical:*  $3.5 \times 10^{-6}$  cm/dyne  
*Compliance, Lateral:*  $3.5 \times 10^{-6}$  cm/dyne  
*Isolation:* 28 db @ 1000 cycles  
*Tracking Force:* 2 to 4 grams in transcription arms  
4 to 6 grams in changer arms  
*Styli:* .7 mil diamond  
*Output:* 8 millivolts  
*Recommended Load:* 22,000 to 47,000 ohms  
(Magnetic phono inputs)  
*Elements:* 2, Lead Zirconium Titanate (Ceramic)  
*Weight:* 8 grams  
*Terminals:* 4, standard .050" connectors  
*Mounting Centers:*  $\frac{1}{2}$ " and  $\frac{3}{16}$ " fits both  
*Audiophile Net:* \$24.00

Want more information? Write to Dept. 20E for the booklet entitled, "FACTS ABOUT THE ELECTRO-VOICE MAGNERAMIC CARTRIDGE"


**Electro-Voice**® INC.

BUCHANAN, MICHIGAN

# WEATHERS STEREO COMPONENTS

combine HIGH QUALITY REPRODUCTION and

# low record wear

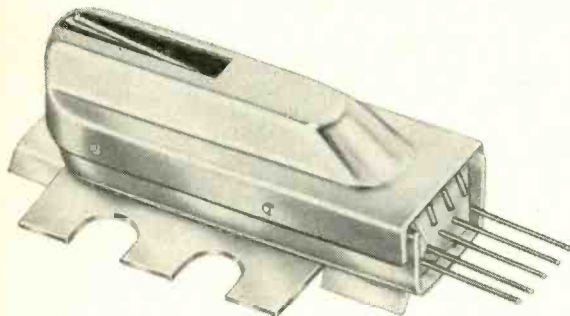

## WEATHERS StereoRamic Cartridge C-501

### SPECIFICATIONS

Frequency Response ..... 20-30,000 cps  
 Compliance .....  $10 \times 10^{-6}$  cm/dyne  
 Dynamic Moving Mass ..... 1.0 milligrams  
 Tracking Force . . . 1-2 grams—Professional arms  
                           2-6 grams—Changers and other type arms  
 Stylus ..... 0.7 mil diamond or sapphire  
 Separation ..... 25 db  
 Signal-to-noise Ratio ..... -60 db  
 Output per channel  
                           15 millivolts into magnetic input

*Audiophile Net*  
 C-501-D—Diamond  
 C-501-S—Sapphire

**\$17.50**  
**\$ 9.75**

A new achievement in ceramic cartridge performance . . . advance-designed for use in changers and other tonearms. Weathers ceramic cartridge does not fight with record grooves. Its effortless, smooth-treading performance means less wear for your records. There is a complete lack of needle talk and chatter, made possible through the use of Weathers Ring Filter Technique—the most efficient means of securing separation between channels . . . better than 25 db. Shielded, too, against hum. Weathers StereoRamic Cartridge comes fully wired and ready for use.

# balance

*Weathers Tonearm MT-5  
 is balanced perfectly . . .  
 so accurate that  
 turntable leveling  
 is unnecessary!*

The Weathers Micro-Touch Stereo Tonearm is designed exclusively for Weathers StereoRamic Cartridge and is an exact duplicate of the arm created for the famous FM 1-gram system. This 1-gram tracking force assures low record wear. Shock mounting isolates the tonearm resonance down to 15 cps. Superbly constructed for cueing ease. Made of the finest basswood which gives maximum strength with minimum weight. Comes complete with stereo leads.



### SPECIFICATIONS

Arm Bearing System ..... Viscous Damping  
 Tracking Force ..... Easily adjusted 1 to 8 grams  
 Finish ..... Ebony with gold trim  
 Overall length ..... 13 inches  
 Pivot to Stylus Tip Length ..... 9 3/4 inches  
 Recommended Overhang ..... 1/2 inch

*Audiophile Net* **\$38.50**

Ask your dealer for a FREE HOME DEMONSTRATION of Weathers components, or write today for illustrated booklet, Dept. RE-2

*"Weathers Technical Magic Is Sound"*

## WEATHERS INDUSTRIES

DIVISION OF ADVANCE INDUSTRIES, INC.

66 E. Gloucester Pike, Barrington, N. J.

Export: Joseph Plasencia, Inc., 401 Broadway, New York 13, N. Y.

CORRESPONDENCE (Continued from p. 22)

important advances available to research engineering. It is not being utilized, and does not appear likely to be adopted in our lifetime.

C. A. PRITCHARD

Arlington, Va.

## INDUSTRIAL ELECTRONICS CIRCUITS

*Dear Editor:*

I am very glad to see an industrial section in RADIO-ELECTRONICS Magazine, especially the article on relays by Alvin G. Sydnor ("Relays in Industry," November, 1959, page 52).

There is a very great need for a magazine on industrial circuits of all kinds.

HAROLD MALE

*New Westminster  
 British Columbia*

## INDUSTRIAL INFORMATION

*Dear Editor:*

I am interested to see you are starting an industrial electronics section. Two years ago I saw an article on how to build a color organ which used thyratrons to operate lights corresponding to treble, mid-range and bass. Later I improved on this, with an experimental unit of 8 channels, which I expanded to 10, then 20 and finally 30. When I went into stereo, I divided the channels into 15 per speaker, so I now have a stereo color organ.

What I am working up to is that I knew little about thyratrons and had to study up on them. I got very little information. I found books that gave circuits for arc welders, etc., but seldom went into lighting circuits, especially theater lighting and dimming, which depend on this principle. I also noticed references to magnetic amplifiers and, though the principles were explained, it seems that no practical circuits with practical values are given. For example, I can imagine an article on building a theater switchboard would be of interest to people working in little-theater groups throughout the country.

DON F. HILL

*Los Angeles, Calif.*

(It is very definitely our intention to describe actual equipment rather than abstract circuitry in our industrial electronics articles.—*Editor*)

## FAN MAIL

*Dear Editor:*

For a long time I have been buying your magazine at newsstands every time I saw an interesting article.

RADIO-ELECTRONICS has been so interesting the last three issues that I have decided to be one of your permanent subscribers, and I will, if you continue to keep the magazine loaded with up-to-date information on new gadgets and developments in the electronics field.

Best wishes for continued success.

JESUS M. MALDONADO

*Bradenton, Fla.*

END




# FREE


# ALLIED'S 1960

## ELECTRONIC SUPPLY CATALOG

*value-packed...send for it!*

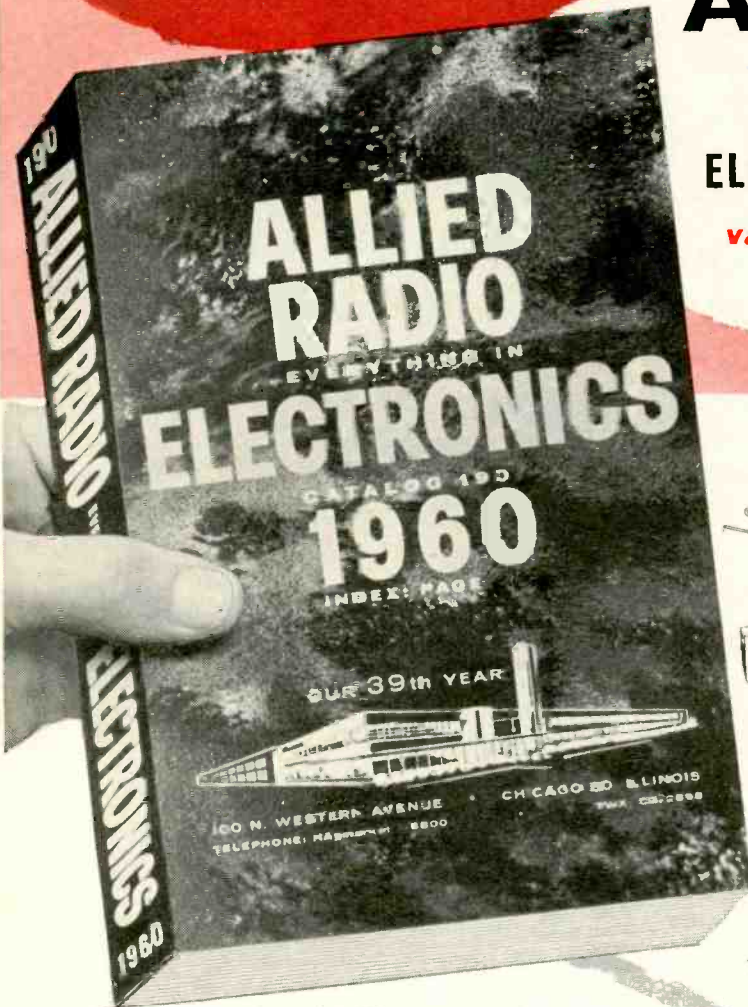

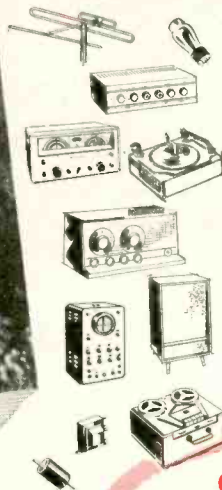your complete money-saving guide to  
**EVERYTHING IN ELECTRONICS**



- Latest Stereo Hi-Fi Systems— Everything in Hi-Fi Components
- Money-Saving, Build-Your-Own KNIGHT-KITS® for Every Need
- Values in Recorders and Supplies
- Latest Public Address Systems, Paging and Intercom Equipment
- Amateur Receivers, Transmitters and Station Gear
- Test and Laboratory Instruments
- TV Tubes, Antennas, Accessories
- Huge Listings of Parts, Tubes, Transistors, Tools, Books

### ALLIED exclusives:

**MONEY-SAVING KNIGHT-KITS®**—the very best in build-your-own electronic equipment—designed to save you up to 50%. "Convenience Engineered" for easiest assembly; the only kits covered by Money-Back Guarantee. Complete selection of Stereo hi-fi kits, Hobbyist kits, Test Instrument and Amateur kits. KNIGHT-KITS are an exclusive ALLIED product.

**KNIGHT® STEREO HI-FI**—truly the best for less—the finest you can buy, yet far lower in cost. Select super-value KNIGHT components or complete systems and save most. Also see the world's largest selection of famous-name hi-fi components and money-saving ALLIED-recommended complete hi-fi systems.

### ONLY \$2 DOWN

on orders up to \$50; only \$5 down on orders up to \$200; only \$10 down over \$200. Up to 24 months to pay.

Get every buying advantage at ALLIED: lowest money-saving prices, fastest shipment, expert personal help, guaranteed satisfaction.

send for the leading  
electronic supply guide

# FREE

## ALLIED RADIO



World's Largest Electronic Supply House

ALLIED RADIO CORP., Dept. 2-8  
100 N. Western Ave., Chicago 80, Ill.

Send FREE 1960 ALLIED Catalog.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_



## How far can you go in electronics . . .

**Two years ago, Field Engineer William G. Miles was asked to outline his thinking on how far he could go in electronics at IBM . . . without a degree. Now, he reviews the progress he's since made. His present position: Group Manager, responsible for keeping one of America's largest electronic computers in top operating condition. Here's his story.**

**HURDLING THE DEGREE BARRIER.** "A few years ago," recalls Bill Miles, "I felt that I'd gone about as far as a technician could without a degree. I just couldn't hurdle that education barrier. Now, thanks to IBM, I have a solid electronics education. I'm a Group Manager on the SAGE project, responsible for 20 field engineers. My future looks brighter than it ever did. I don't know of another company where a technician can go farther or receive more recognition, without a degree, than at IBM."

**UTILIZING HIS NAVAL TRAINING.** Bill Miles spent three years as a Naval Aviation Radar Technician. After discharge from service, he worked as a TV serviceman, at the same time pursuing an engineering education at night. "I knew there were good career opportunities around somewhere, but I couldn't find them," Bill Miles says. "I investigated several big companies. They were impressed with my ability, but my lack of a degree kept me from the kind of a career I wanted. Then I answered an ad similar to this."

**EXTENSIVE ELECTRONICS SCHOOLING.** In May, 1955, he joined IBM and began an extended training course. "The teaching was as technically advanced as I could ask for. Each day, I gained

a deeper knowledge of electronics and added to my professional stature. IBM shows real interest in you as an individual: what your goals are, what plans you've made to reach your goals, how the company can help speed you toward them or even higher goals."

**ASSIGNED TO SAGE SITE.** After his training, Bill Miles was assigned to a SAGE site. SAGE is an important link in America's air defense, and the heart of SAGE is a real-time computer made by IBM. The SAGE computer analyzes radar data with uncanny accuracy, checks it against available air traffic information, and presents visual displays to assist the Air Force in identifying flying objects as friend or foe.

**UPGRADING TECHNICIANS.** "The job of IBM field engineers is to keep SAGE computers running," he explains. "This involves maintaining, testing, and checking computer units. It means anticipating trouble before it occurs. The work turned out to be exactly what I was looking for. I had a chance to do work ordinarily done by graduate engineers . . . work usually denied to men without a degree. Of all the companies I know, IBM appears to be one of the few which upgrades technicians to levels of engineering responsibility . . . levels dictated not by your formal education but by your native talents."

**MANY EDUCATIONAL OPPORTUNITIES.** "SAGE field engineers have many opportunities for education beyond the 'basic' training, which lasts 20 weeks," says Bill Miles. "After a year or two in the field, they may be selected for further training to learn how the complete SAGE electronic computer system works. To



Bill Miles reviews two-year-old article about his IBM career.

## without a degree?

Keep up with the most advanced electronic developments, they may also attend classes during working hours."

**RAPID ADVANCE TO GROUP MANAGER.** In his four years with IBM, Bill Miles has received several promotions. He is now Group Manager at a SAGE site. "My advancement is an example of IBM's policy of promoting from within," he says. "The company is quick to recognize a man's contributions and quick to reward him. This means lots of opportunities for new men who show potential for advancement along clearly defined routes—both in the technical and managerial areas. There are no limits set on your future. Everything IBM has ever promised about advancement in field engineering, I've seen happen—either to me or to someone I know."

\* \* \*

If you have a minimum of 3 years' technical schooling after high school—or equivalent experience—you may be eligible for 20 weeks' training as a Computer Units Field Engineer. Starting salaries are based on your education and experience. While training you will also receive a living allowance.

From then on, you can go as far as your abilities and ambition will take you. And, as you may already know, at IBM you receive company-paid benefits that set standards for industry today.

**WRITE TODAY TO:** Mr. N. H. Heyer  
Dept. 649N  
Federal Systems Division  
IBM Corp., Kingston, N. Y.

You'll receive a prompt reply. Personal interviews arranged in all areas of the United States.

FEBRUARY, 1960




Discussing counseling methods with personnel management.

Demonstrating how SAGE operating console works.
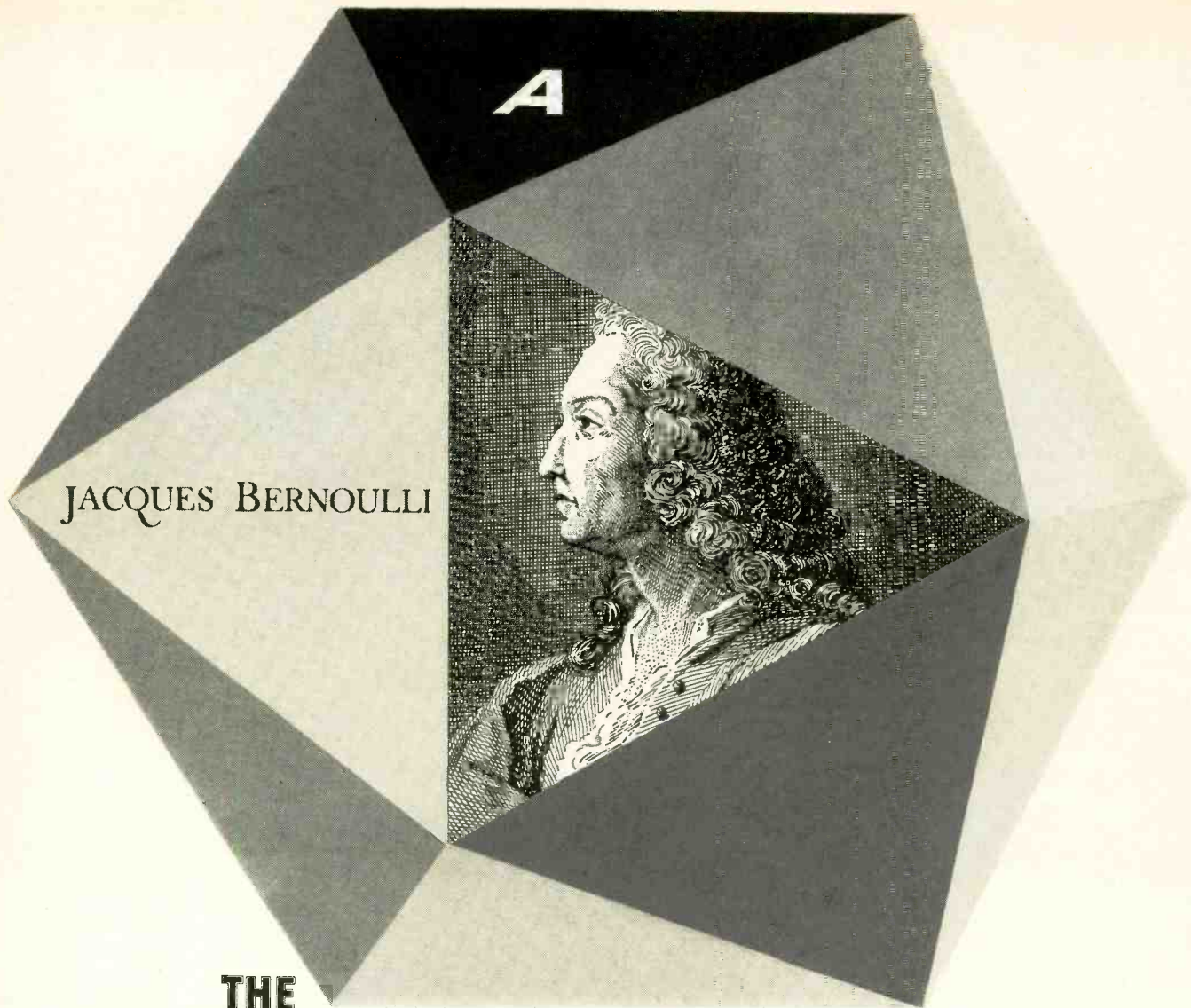
# IBM®

INTERNATIONAL BUSINESS MACHINES CORPORATION



JACQUES BERNOULLI

# THE WIZARD OF ODDS

*He solved a telephone traffic problem two centuries ago*

Jacques Bernoulli, the great Swiss mathematician, pondered a question early in the 18th century. Can you mathematically predict what will happen when events of chance take place, as in throwing dice?

His answer was the classical Bernoulli binomial distribution—a basic formula in the mathematics of probability (published in 1713). The laws of probability say, for instance, that if you roll 150 icosahedrons (the 20-faced solid shown above), 15 or more of them will come to rest with side “A” on top only about once in a hundred times.

Identical laws of probability govern the calls coming into your local Bell Telephone exchange. Suppose you are one of a group of 150 telephone subscribers, each of whom makes a three-minute call during the busiest hour of the day. Since three minutes is one-twentieth of an hour, the

probability that you or any other subscriber will be busy is 1 in 20, the same as the probability that side “A” of an icosahedron will be on top. The odds against 15 or more of you talking at once are again about 100 to 1. Thus it would be extravagant to supply your group with 150 trunk circuits when 15 are sufficient for good service.

Telephone engineers discovered at the turn of the century that telephone users obey Bernoulli’s formula. At Bell Telephone Laboratories, mathematicians have developed the mathematics of probability into a tool of tremendous economic value. All over the Bell System, the mathematical approach helps provide the world’s finest telephone service using the least possible equipment. The achievements of these mathematicians again illustrate how Bell Laboratories works to improve your telephone service.



**BELL TELEPHONE LABORATORIES**

*World center of communications research and development*

In **STEREO**  
**STEREO**


and Mono Hi-Fi... the experts say  
your best buy is

**EICO**

"The overall design of the HF-81 is conservative, honest and functional. It is a good value considered purely on its own merits, and a better one when its price is considered as well."

— Hirsch-Houck Labs (HIGH FIDELITY Magazine)

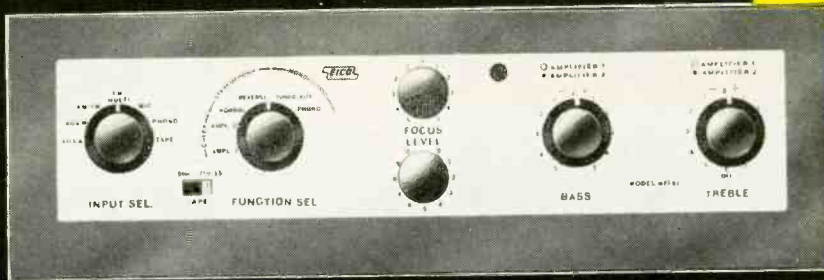- Advanced engineering • Finest quality components
- "Beginner-Tested," easy step-by-step instructions
- LIFETIME service & calibration guarantee at nominal cost
- IN STOCK — compare, then take home any EICO equipment — right "off the shelf" — from 1500 neighborhood EICO dealers.



Stereo Amplifier-Preamp HF81

**HF81 Stereo Amplifier-Preamp** selects, amplifies, controls any stereo source & feeds it thru self-contained dual 14W amplifiers to a pair of speakers. Provides 28W monophonically. Ganged level controls, separate balance control, independent bass & treble controls for each channel. Identical Williamson-type, push-pull EL84 power amplifiers. "Excellent" — SATURDAY REVIEW; HI-FI MUSIC AT HOME. "Outstanding quality... extremely versatile." — ELECTRONICS WORLD LAB-TESTED. Kit \$69.95. Wired \$109.95. Includes cover.

**HF85 Stereo Preamp** is a complete, master stereo preamp-control unit, self-powered for flexibility & to avoid power-supply problems. Distortion borders on unmeasurable even at high output levels. Level, bass, & treble controls independent for each channel or ganged for both channels. Inputs for phono, tape head, mike, AM, FM, & FM-multiplex. One each auxiliary A & B input in each channel. Switched-in loudness compensator. "Extreme flexibility... a bargain." — HI-FI REVIEW. Kit \$39.95. Wired \$64.95. Includes cover.

**New HF87 70-Watt Stereo Power Amplifier:** Dual 35W power amplifiers of the highest quality. Uses top-quality output transformers for undistorted response across the entire audio range at full power to provide utmost clarity on full orchestra & organ. IM distortion 1% at 70W, harmonic distortion less than 1% from 20 to 20,000 cps within 1 db of 70W. Ultra-linear connected EL34 output stages & surgeistor-protected silicon diode rectifier power supply. Selector switch chooses mono or stereo service; 4, 8, 16, and 32 ohm speaker taps, input level controls; basic sensitivity 0.38 volts. Without exaggeration, one of the very finest stereo amplifiers available regardless of price. Use with self-powered stereo preamp-control unit (HF85 recommended). Kit \$74.95. Wired \$114.95.

**HF86 28W Stereo Power Amplifier Kit \$43.95. Wired \$74.95.**

**FM Tuner HFT90:** Prewired, prealigned, temperature-compensated "front end" is drift-free. Prewired exclusive precision eye-tronic® traveling tuning indicator. Sensitivity: 1.5 uv for 20 db quieting; 2.5 uv for 30 db quieting, full limiting

from 25 uv. IF bandwidth 260 kc at 6 db points. Both cathode follower & FM-multiplex stereo outputs, prevent obsolescence. Very low distortion. "One of the best buys in high fidelity kits." — AUDIOCRAFT. Kit \$39.95\*. Wired \$65.95\*. Cover \$3.95. \*Less cover, F.E.T. Incl.

**New AM Tuner HFT94.** Matches HFT90. Selects "hi-fi" wide (20c-9kc @ -3 db) or weak-station narrow (20c-5kc @ -3 db) bandpass. Tuned RF stage for high selectivity & sensitivity; precision eye-tronic® tuning. Kit \$39.95. Wired \$65.95. Incl. Cover & F.E.T.

**New FM/AM tuner HFT92** combines the renowned EICO HFT90 tuner with excellent AM tuning facilities. Kit \$59.95. Wired \$94.95. Includes covers and F.E.T.

**New AF-4 Stereo Amplifier** provides clean 4W per channel or 8W total output. Inputs for ceramic/crystal stereo pick-ups, AM-FM stereo, FM-multi stereo. 6-position stereo/mono selector. Clutch-concentric level & tone controls. Use with a pair of HFS-5 Speaker Systems for good quality, low-cost stereo. Kit \$38.95. Wired \$64.95.

**HF12 Mono Integrated Amplifier** provides complete "front-end" facilities and true high fidelity performance. Inputs for phono, tape head, TV, tuner and crystal/ceramic cartridge. Preferred variable crossover, feedback type tone control circuit. Highly stable Williamson-type power amplifier circuit. Power output: 12W continuous, 25W peak. Kit \$34.95. Wired \$57.95. Includes cover.

**New HFS3 3-Way Speaker System Semi-Kit** complete with factory-built 3/4" veneered plywood (4 sides) cabinet. Bellows-suspension, full-inch excursion 12" woofer (22 cps res.), 8" mid-range speaker with high internal damping cone for smooth response, 3 1/2" cone tweeter, 2 1/4 cu. ft. ducted-port enclosure. System Q of 1/2 for smoothest frequency & best transient response. 32-14,000 cps clean, useful response. 16 ohms impedance. HWD: 26 1/2", 13 7/8", 14 3/8". Unfinished birch \$72.50. Walnut, mahogany or teak \$87.50.

**New HFS5 2-Way Speaker System Semi-Kit** complete with factory-built 3/4" veneered plywood (4 sides) cabinet. Bellows-suspension, 5/8" excursion



Stereo Preamp HF85



70W Stereo Power Amplifier HF87  
28W Stereo Power Amplifier HF86



FM Tuner HFT90 AM Tuner HFT94 FM/AM Tuner HFT92



Stereo Integrated Amplifier AF4



12W Mono Integrated Amplifier HF12  
Other Mono Integrated Ampifiers:  
50, 30, & 20W (use 2 for stereo)



2-Way Bookshelf Speaker System HFS1  
3-Way Speaker System HFS3  
2-Way Speaker System HFS5

tion, 8" woofer (45 cps res.), & 3 1/2" cone tweeter. 1 1/4 cu. ft. ducted-port enclosure. System Q of 1/2 for smoothest frequency & best transient response. 45-14,000 cps clean, useful response. HWD: 24", 12 1/2", 10 1/2". Unfinished birch \$47.50. Walnut, mahogany or teak \$59.50. **HFS1 Bookshelf Speaker System** complete with factory-built cabinet. Jensen 8" woofer, matching Jensen compression-driver exponential horn tweeter. Smooth clean bass; crisp extended highs. 70-12,000 cps range. 8 ohms. HWD: 23" x 11" x 9". Price \$39.95.

**HFS2 Omni-Directional Speaker System** (not illus.) HWD: 36", 15 1/4", 11 1/2". "Eminently musical!" — HIGH FIDELITY. "Fine for stereo" — MODERN HI-FI. Completely factory-built. Mahogany or walnut \$139.95. Blond \$144.95.

**IMPORTANT NOTE:** All EICO kits built according to our instructions, and all EICO factory-assembled equipment, conform to the high standards and specifications as published in EICO literature and advertisements. All EICO factory-assembled equipment is completely and meticulously hand-wired throughout — no printed circuitry; each factory-assembled unit is 100% final-tested throughout for each feature and function — no "spot" or "partial" checking. In EICO's final-test techniques, nothing is left to chance.

Fill out coupon on other side for FREE CATALOG. Ask your dealer about EICO'S exclusive Stereo Records Bonus.




Over 1 MILLION EICO instruments in use throughout the world.

Add 5% in the West. Copyright 1960 by Electronic Instr. Co., Inc., 33-00 N. Blvd. L. I. C. I. N. Y.

The specs prove it...your best buy is



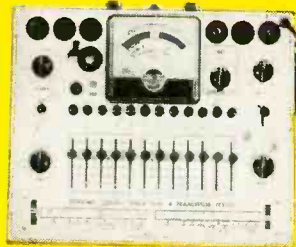**TV-FM SWEEP GENERATOR AND MARKER #368**  
KIT \$69.95 WIRED \$119.95



**A**  
**DYNAMIC CONDUCTANCE TUBE & TRANSISTOR TESTER #666**  
KIT \$69.95 WIRED \$109.95  
Complete with steel cover & handle

**RF SIGNAL GENERATOR #324**  
KIT \$26.95 WIRED \$39.95



**D**  
**PEAK-TO-PEAK VTVM #232 & UNIPROBE (pat. pend)**  
KIT \$29.95  
WIRED \$49.95



**C**  
**5" OSCILLOSCOPE #460**  
KIT \$79.95 WIRED \$129.50  
**E**  
**5" PUSH-PULL Oscilloscope #425:**  
Kit \$44.95 Wired \$79.95

**A** Tests all receiving tubes (picture tubes with adapter), n-p-n and p-n-p transistors. Composite indication of Gm, Gp & peak emission. Simultaneous selection of any one of 4 combinations of 3 plate voltages, 3 screen voltages, 3 ranges of continuously variable grid voltage (with 5% accurate pot.). Sensitive 200 ua meter. 10 six-position lever switches: freepoint connection of each tube pin. 10 pushbuttons: rapid insert of any tube element in leakage test circuit. Direct reading of inter-element leakage in ohms. New gear-driven rollchart. **CRA Adapter \$4.50.**

**B** Entirely electronic sweep circuit with accurately-biased inductor for excellent linearity. Extremely flat RF output. Exceptional tuning accuracy. Hum and leakage eliminated. 5 fund. sweep ranges: 3-216 mc. Variable marker range: 2-75 mc

in 3 fund. bands, 60-225 mc on harmonic band. 4.5 xtal marker osc., xtal supplied. Ext. marker provision. Attenuators: Marker Size, RF Fine, RF Coarse (4-step decade). Narrow range phasing control for accurate alignment.

**C** 150 kc to 435 mc with ONE generator in 6 fund. bands and 1 harmonic band!  $\pm 1.5\%$  freq. accuracy. Colpitts RF osc. directly plate-modulated by K-follower for improved mod. Variable depth of int. mod. 0-50% by 400 cps Colpitts osc. Variable gain ext. mod. amplifier: only 3.0 v needed for 30% mod. Turret-mounted, slug-tuned coils for max. accuracy. Fine and Coarse (3-step) RF attenuators. RF output 100,000 uv, AF output to 10 v.

**D** Uni-Probe — exclusive with EICO — only 1 probe performs all functions: half-turn of probe tip selects DC or AC-Ohms. Calibration without re-

moving from cabinet. Measure directly p-p voltage of complex & sine waves: 0-4, 14, 42, 140, 420, 1400, 4200. DC/RMS sine volts: 0-1.5, 5, 15, 50, 150, 500, 1500 (up to 30,000 v. with HVP probe, & 250 mc with PRF probe). Ohms: 0.2 ohms to 1000 megs.  $4\frac{1}{2}$ " meter, can't-burn-out circuit. 7 non-skip ranges on every function. Zero center.

**E** Features DC amplifiers! Flat from DC to 4.5 mc, usable to 10 mc. Vert. Sens.: 25 mv/in.; input Z 3 megs; direct-coupled & push-pull throughout. 4-step freq.-compensated attenuator up to 1000:1. Sweep: perfectly linear 10 cps — 100 kc (ext. cap. for range to 1 cps). Pre-set TV V & H positions. Auto sync. lim. & ampl. Direct or cap. coupling; bal. or unbal. inputs; edge-lit engraved lucite screen with dimmer control; plus many more outstanding features.

**FREE CATALOG shows you HOW TO SAVE 50% on 65 models of top quality professional test equipment. MAIL COUPON NOW!**



**New Transistor Portable Radio RA-6**  
Kit \$29.95  
Wired \$49.95  
Incl. F. E. T.; less 9V batt. Prealigned RF, IF xfmrs; push-pull audio; 8" spkr.

\*PAT. PEND.



**NEW Power & Bias Supply for Transistorized Eqpt. #1020 \***  
Kit \$19.95  
Wired \$27.95



**NEW Tube & CRT Fil. Tester #612**  
Kit \$3.95  
Wired \$5.95  
Fast-checks radio/TV tubes, pilot lamps, etc.




**Series/Parallel R-C Combination Box #1140**  
Kit \$13.95  
Wired \$19.95



**Tube Tester #625**  
Kit \$34.95  
Wired \$49.95  
• tests 600 mil series string type tubes  
• illuminated roll-chart  
**Pix Tube Test Adapter..... \$4.50**



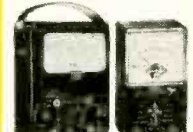**6V & 12V Battery Eliminator and Charger #1050**  
Kit \$29.95  
Wired \$38.95  
Extra-filtered for transistor equip.  
#1060 Kit \$38.95  
Wired \$47.95



**20,000 Ohms/Volt V-O-M #565**  
Kit \$24.95  
Wired \$29.95  
**1000 Ohms/Volt V-O-M #536**  
Kit \$12.90  
Wired \$14.90



33-00 Northern Blvd. L. I. C. 1, N. Y.

Add 5% in the West. © 1959

TURN PAGE FOR MORE EICO VALUES



**R-C Bridge & R-C-L Comparator #950B**  
Kit \$19.95  
Wired \$29.95  
Reads 0.5 ohms-500 megs, 10 mmfd-5000 mfd, power factor



VTVM Probes	Kit	Wired
Peak-to-Peak	\$4.95	\$6.95
RF	\$3.75	\$4.95
High Voltage Probe-1		\$6.95
High Voltage Probe-2		\$4.95
Scope Probes		
Demodulator	\$3.75	\$5.75
Direct	\$2.75	\$3.95
Low Capacity	\$3.75	\$5.75

**EICO**  
33-00 Northern Blvd.  
L. I. C. 1, N. Y.

Show me HOW TO SAVE 50% on  Test Instruments  
 Hi-Fi  Ham Gear.  Send free Stereo Hi-Fi Guide. Send me FREE Catalog, name of neighborhood dealer.

Name.....  
Address.....  
City..... Zone..... State.....

# MICROELECTRONICS

... *A Major Revolution in Electronics Is Shaping* ...

**E**VER since the beginning of radio, and later the electronic art, components have steadily shrunk. We have reported its progress on this page at regular intervals.\*

During the past few years, the shrinking of practically all electronic parts has accelerated at an unprecedented rate, so rapidly, in fact, that at this moment the art already has moved into *molecular electronics*—termed by some research laboratories *molelectronics*.

RCA, General Electric, Westinghouse, Bell Laboratories, IBM, Texas Instruments are only a few of the pioneering researchers who are now deeply in *microelectronics*, a development that presages a revolution far greater than even the advent of the transistor.

To grasp this new advance fully, let us report that already the laboratories have components so small that they cannot be seen by the naked eye—they are truly of microscopic size! Nor do they look at all like the usual units. In fact, if the scientist who demonstrates the item to you did not assure you that the little speck you glimpsed under the microscope was a transistor or a capacitor or a resistor, you probably would not believe it. Yet such microcomponents are already facts today in the laboratory. By the mid-1960's, they will probably be for sale in civilian items, such as hearing aids, bio-electronic medical appliances and others. *Microradios*, considerably less than 1 inch square, will most likely appear by 1965 or earlier.

Why this frantic reduction in size? There are excellent reasons for it. First, economics—a huge shrinking in materials, in weight and, consequently, in cost, becomes possible. Second, and more important, in the coming microelectronics art, *practically all—if not all—soldering will have disappeared*, as an anachronism and technical barbarism. Hence, there will be little of the ancient disease of miscontacts or even worse, "intermittents" that have plagued manufacturers and service technicians for generations.

Third, and of vast importance: Military and coming space requirements are so stringent and so vital that large size and failures of components are matters of continuous threat to life. Hence they cannot be tolerated—there just cannot be a failure in future electronic gear.

In microelectronics, the reduction of size and weight, as well as other advantages—for instance, practically indestructible components that never wear out—will usher in a new age for the art.

What really is microelectronics? Stripped of most scientific and technical terms, it is the production and adaptation of microfilms so thin that they measure only one molecule thick.

We know the molecule is the smallest particle of matter that can exist by itself and still retain all the properties of the original element. That we really have to do with microscopic dimensions will be better appreciated when we realize that it takes nearly 1,000,000 films the thickness of one molecule to measure 1 inch thick!†

\* See "Midget Radio Sets," January, 1931; "Shrinking Radio," January, 1944; "Miniature Radios," September, 1944; "Microtubes," November, 1947; "Miniradios," November, 1953; "Minitellevision," August, 1956—and many others.

†The figure was based on the molecule of ordinary water (H<sub>2</sub>O). Atoms

Yet, unlikely as it sounds, it is possible to fashion capacitors, resistors and even transistors of single or multiple molecules, that behave exactly as their big brothers. It even becomes possible to build amplifiers and switching devices for computers that are so tiny that they can be seen only under a high-power microscope.

The microfilms that make this revolutionary art possible today are fashioned from either silicon or germanium, but it is certain that in the future other materials will be used as well. At present, there are various techniques—all more or less experimental—for fashioning the various components. Normally, the raw materials are sprayed, sputtered or evaporated in a high vacuum under considerable heat, as the first step. An insulating film, one or two molecules thick, may then be sprayed on; then the first step may be repeated. A few such steps will result in a workable micro-capacitor. Resistors and transistors are created in similar fashion.

One may start with a metallic or insulating base, then build the component on top of it. The next required component can go right on top of the first one, depending upon the desired circuit. Or, if necessary, another component can be fashioned alongside the first one, and so forth.

The various components can readily be insulated from each other by spraying various amounts of oxygen, which then forms an oxide film on them. By proper manipulation, the components, whenever required, will be connected electrically with each other, either by direct contact or by sprayed metal film. Hence such sophisticated "micro-wiring" will no longer be the bothersome factor our present-day crude wiring or even printed circuits are.

It can be seen that in using these and other more refined techniques it becomes feasible to build complete radio chassis so tiny that hundreds of them can be placed in a single thimble!

It becomes clear now why such micro-assemblies are so rugged that they will be practically indestructible. Their minuscule size, and micro-weight, safeguards the structure against shock and mechanical stress. This is of utmost importance for military and space applications.

While such microelectronic assemblies can readily be connected and interconnected to other assemblies, they can also be electrically connected to their respective power supply.

Although batteries for portable electronic gear have steadily shrunk in size, chemical type dry cells probably will not be able to contract down to molecular size in the foreseeable future. And if they could, their power output would be so microscopic that they would never be able to drive even the smallest speaker for more than a few seconds.

Yet microbatteries with a serviceable electrical output are an early and foreseeable possibility. We speak of atomic batteries here. There is no difficulty in building them down to molecular size. Atomic batteries predicted by us in 1945 are a reality today. They are certain to be incorporated along with other components into self-powered microelectronic assemblies during the next 10 years.—H.G.

of silicon and germanium have diameters in the order of one ten-millionth inch, and therefore would form much thinner films.

# SINGLE CONTROL MULTIMETER

A unit without a zero control made possible by mercury batteries

By ALBERT STRATMOEN

THE volt-ohm-milliammeter is the most universally used electronic test instrument. It is usually purchased ready-made or in kit form because the time involved in designing and constructing one is great enough to make it impractical. However, if one can get a meter movement for which the proper scales and design have been worked out, the project becomes practical.


This article describes the features and construction of a vom that should appeal to both the experienced man and the beginner. It has three features not found in commercial models:

- ▶ No zero-adjust control for the ohms section

- ▶ Maximum current in the ohms section limited to 500  $\mu$ a

- ▶ The same linear scale for ac and dc ranges

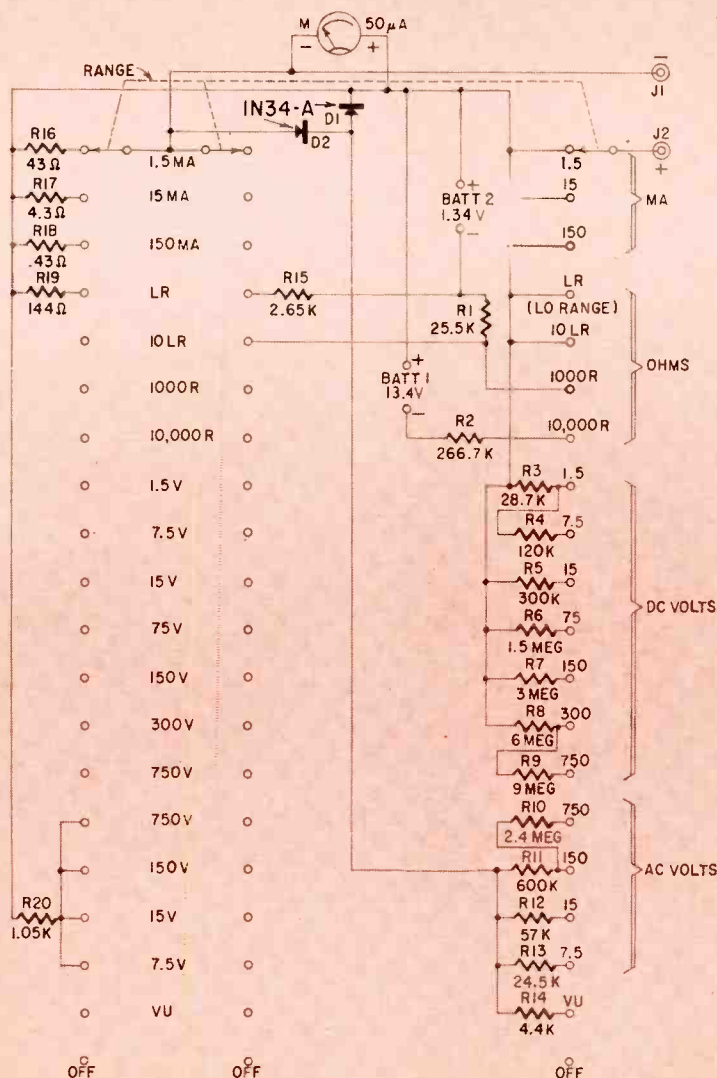Zero-adjust controls are needed in the ohms section of conventional instruments because the dry cells (carbon-zinc type) used as power sources are



- R1—25,500 ohms
- R2—266,700 ohms
- R3—28,700 ohms
- R4—120,000 ohms, deposited carbon
- R5—300,000 ohms, deposited carbon
- R6—1.5 megohms, deposited carbon
- R7—3 megohms, deposited carbon
- R8—6 megohms, deposited carbon
- R9—9 megohms, deposited carbon
- R10—2.4 megohms, deposited carbon
- R11—600,000 ohms, deposited carbon
- R12—57,000 ohms
- R13—24,500 ohms
- R14—4,400 ohms
- R15—2,650 ohms
- R16—43 ohms
- R17—4.3 ohms, wirewound
- R18—0.43 ohms, wirewound
- R19—144 ohms
- R20—1,050 ohms

All resistors  $\frac{1}{2}$  watt—10% units are selected with ohmmeter or resistance bridge to within 1% or better except for deposited-carbon and wirewound units  
 BATT 1—13.4 volts (Two Mallory TR-136R's in series with 1 cell removed from each)  
 BATT 2—1.34 volts (1 cell of Mallory TR-136R—removed from BATT 1)  
 D1, 2—IN34-A  
 J1, 2—insulated banana jacks  
 M—meter, 50  $\mu$ a,  $\frac{1}{2}$ -inch scale (Precise Development M-50 or equivalent)  
 S—3-deck 3-pole 20-position nonshorting rotary (JBT MS-20-3 or equivalent)  
 Case, bakelite 6  $\frac{13}{16}$  x 5  $\frac{9}{16}$  x 2  $\frac{5}{16}$ " with panel (Allied Radio 86P287 and 86P289 or equivalent)  
 Miscellaneous hardware

Circuit of the I-control unit




not constant-voltage sources. Their output varies from almost 1.6 (when new) to about 1.3 volts during their useful lifetime. Therefore, a variable resistor is needed to compensate for the variation. In addition, low resistances are measured by passing high current—up to 50 ma on the lowest range—through the unknown resistance. When the battery is new, it doesn't matter. However, as it ages its internal resistance increases and the output voltage drops on the ranges using more current, making it necessary to adjust the zero control constantly when changing ranges.

Mercury batteries are far superior for this purpose as their 1.34 volts per cell remains constant during their useful lifetime. Therefore, the main reason for having an ohms-adjust control does not apply when mercury cells are used as a power source. The 50-ma drain for the low ohms range of most meters is pretty heavy for mercury batteries, but, by using a backup circuit for the two lowest ranges, current is limited to 500  $\mu$ a. The backup circuit passes full-scale current through the meter and shunts the meter with the unknown resistance. So, when no resistance is connected to the test leads, the meter indicates full scale (infinite resistance). The reading drops as the resistance shunted across the meter is decreased. When the external resistance is equal to the meter's internal resistance, the pointer will be at exactly half scale—in this instrument, 1,300 ohms.

To read lower resistance values than would be possible with this value of half-scale indication, the meter is shunted on the low-resistance range to 500  $\mu$ a, making 130 ohms the half-scale value for this range. The lowest resistance that can be read on this range is 1 ohm. For reading very low resistance values, I recommend a separate instrument such as the one described in the August, 1953, issue of RADIO-ELECTRONICS. This reads as low as .01 ohm with a maximum current of 50 ma. It also measures direct current from 50 ma to 10 amps. As I brought out in this earlier article, 50- $\mu$ a movements are fine for measuring voltage and high values of resistance but aren't suited for low resistance and current. That is why I have only three current ranges and use the saved switch positions for voltage and resistance.

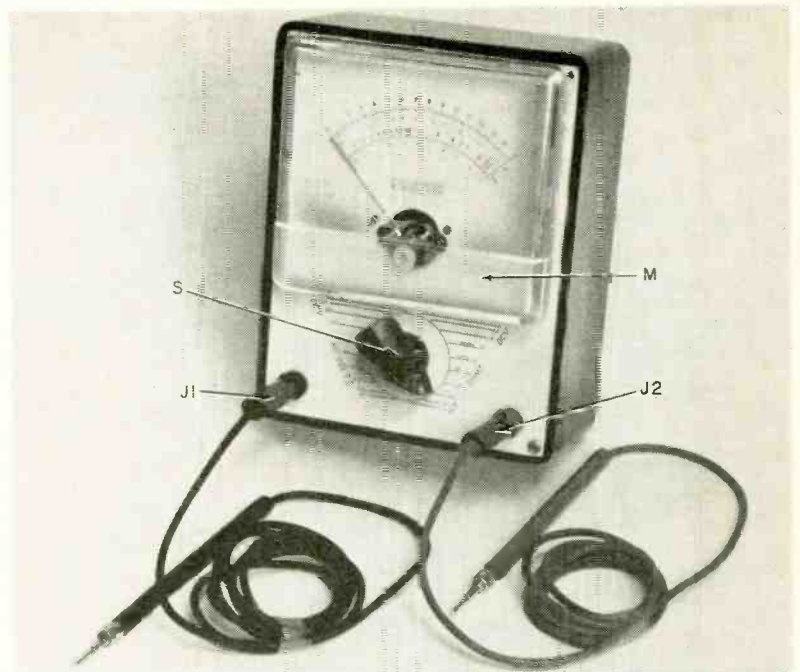
**Building the vom**

The first step in constructing the instrument is to mount the parts on the panel. This panel is in two layers. One is the bakelite panel that comes with the case, and the other is a plexiglas sheet of the same size. The range dial is sandwiched between these and is a photographic reduction. It isn't difficult to draw one of the proper size. If you can engrave bakelite, you will not need the plexiglas or the paper drawing. I mounted the two large mercury batteries by taping them to strips of plexiglas and fastening the strips with meter




(Above) Neat-looking instrument covers ac and dc volts, ohms, dc ma and db.

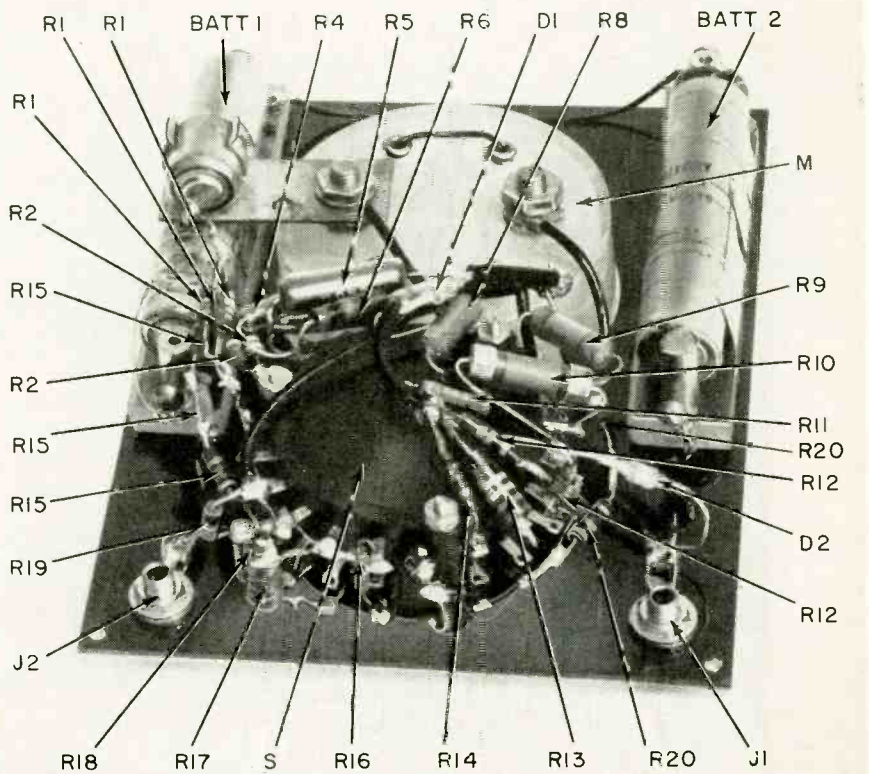(Below) A three-gang switch and associated wiring fills the meter's bakelite case. Each component of resistors built up from several units is marked with the resistor number.



Tests conducted by a member of the staff of RADIO-ELECTRONICS showed that the author's unit is an excellent multimeter. Accuracy, checked against an EICO vohm at assorted ac and dc voltages, was within 2%. On low resistance ranges the meter did not go to exactly full scale, but when checked by measuring various 1% precision resistors accuracy is within 2%. The meter scales as shown are hard to read. They can be made clearer by adding calibrations for the 7.5-, 75-, and 750-volt ranges.

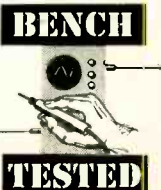

## TEST INSTRUMENTS

mounting bolts. I used brass pillars with a crosswise hole that was tapped for 6-32 bolts instead of nuts. These contact the ends of the batteries and form convenient terminal posts.

One cell is removed from each battery, cutting them down to a total of ten cells. Remove this cell from the positive end of each battery and you will have a tab on the center electrode you can solder to. One of these cells is used for the three low ranges and the other becomes a spare. As shown in the photo, the single cell is mounted in a fuse clip that has been soldered to a piece of brass.


Next, mount the range switch and its knob and the banana jacks. To have as much room for these as possible, mount the meter as high on the panel as you can. The meter scale can be cemented in place either before or after you mount the meter on the panel. It is wise to make a new aluminum backing for the scale as the original is punched for slide-in scales. Before pasting in the scale, remove the 700-ohm resistor in series with the meter coil. Evidently it brings the meter resistance up to an even 2,000 ohms, but the backup circuit works best with low resistances, so the scale has been calibrated for a 1,300-ohm movement and is accurate for only this value. If you are using another make meter and it has a lower resistance, you could add some series resistance to bring it up to 1,300 ohms. Be sure to get one with a lance or knife-edge pointer. The arc is 90°.

### Wiring details

All other components can now be soldered in place. Note that except for the deposited-carbon resistors all are of nonstandard values. You will have to borrow a good ohmmeter or resistance bridge and select them from a stock of common carbon resistors. The wire-wound resistors are made up from No. 30 copper wire wound on forms made of high-value radial-lead carbon resistors.


Starting with the ohms section, install R19, the 500- $\mu$ a shunt. You may find a nominal 150-ohm carbon resistor that is just right or you can use some series or parallel arrangement to get the exact value.

The multipliers for the dc ranges (R3 to R9) are mostly deposited carbon. R3 is an odd value to compensate for the meter resistance. Only two of the ac multipliers (R10 and R11) are standard values. Two factors to consider for ac are rectifier efficiency and linearity. Install R10 and R11 and set the range switch to 150 volts ac. Connect a 10,000-ohm variable resistor as a temporary R20 and set it to minimum. Touch the test leads to the ac line and adjust the pot until the meter gives the same reading as your standard voltmeter. Then replace the variable control with a fixed resistor of the same value. It should be approximately 1,050 ohms. If you have a really accurate ac voltmeter, you could improve accuracy on the 15, 7.5 and VU range by adjust-

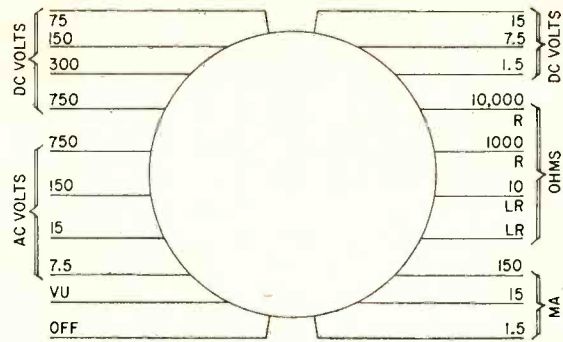

Range scale shown  
actual size.

Meter face shown  
actual size.

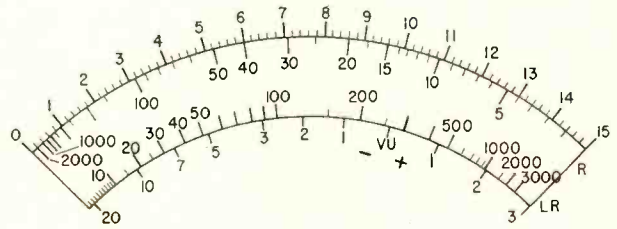

E	7.5	15	150	750
DB	+16	+22	+42	+54

ing R12, R13, R14 until the readings agree with your standard. But if you have done a good job on the ohms section and have measured these resistors accurately, you should be within the usual 5% accuracy for ac meters.

### Design factors

You will notice that I do not use a separate meter scale for ac. This is a big advantage, but it requires paying attention to rectifier linearity. The extra diode that shorts the meter and rectifier during the undesired half-cycle helps improve linearity as no current leaks through during this period. However, when dealing with currents of 5  $\mu$ a or less, diodes increase in forward resistance and decrease in back resistance, therefore losing their efficiency. Even silicon diodes that may have a back resistance of 10,000,000 ohms for larger currents act this way. Their back resistance may drop to 20,000 ohms near zero current. I found that 1N34's are as good as any for this purpose.

If we try to make the ac ranges as sensitive as possible, we run into linearity problems. The 5- $\mu$ a point below which the rectifiers act more like resistors than rectifiers represents a considerable part of the arc. But if we decrease the sensitivity by shunting the meter, this effect becomes less important. I found that 4,000 ohms per volt is the greatest sensitivity that will give reasonable linearity. True, 2,000 ohms per volt would be better, but it would load some circuits excessively.

The VU range is not shunted as linearity isn't as important and I wanted to approximate the standard VU meters. There are quite a few problems when one tries to have a VU range on a multimeter. This is mainly because of meter movements' characteristics.

VU types are more lively due to less damping and possibly more torque. For audio work, 0 db is 1 mw in a 600-ohm line or 0.775 volt. Standard VU meters do not indicate zero at this level but at 6 db down from 10-mw. However, I had to use 0.775 volt as zero to use the higher ranges for decibels, so this meter will indicate zero VU when the level is 1 milliwatt. This applies only for steady tones; for male speech the readings will be very close to a standard VU meter because of the more sluggish movement. For steady tones you can match a standard VU meter by adding 7,500 ohms in series with the test leads. For the higher ranges, add the appropriate number of decibels shown in the box on the meter scale.

The shunt resistors for dc are difficult to measure accurately, especially R17 and R18. For best results check them against a good standard by passing current through both meters in series.

I would like to give my reasons for selecting the voltage ranges by indicating the uses for each:

#### Dc ranges

- 1.5—dry cells, mercury cells, filaments of 1.4-volt tubes
- 7.5—6-volt storage batteries
- 15—12-volt storage batteries, 9-volt transistor supplies
- 75—multiple of 15, bias of output tubes
- 150—transformerless plate voltages
- 300—transformer type plate voltages
- 750—multiple of 150

#### Ac ranges



- VU—telephone and low-level audio
- 7.5—6.3-volt heaters
- 15—12.6-volt heaters
- 150—ac line, heaters of higher-voltage tubes
- 750—multiple of 150, input to rectifiers

END

# PORTABLE POWER SUPPLY

By I. QUEEN  
EDITORIAL ASSOCIATE

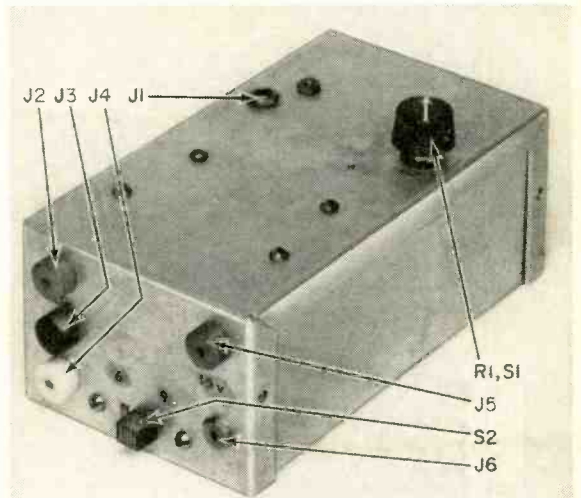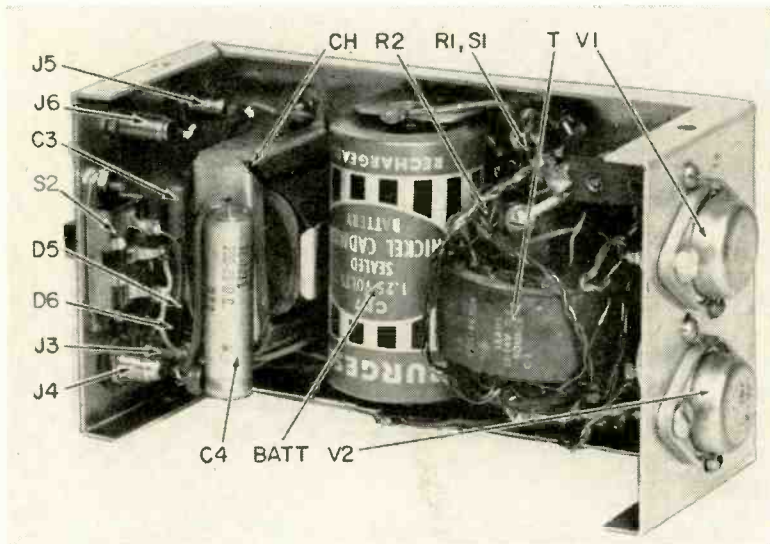1.5, 6.2 and 9.1 volts regulated and about 20 volts semiregulated dc are the outputs of this 5 x 3 x 2-inch device



The finished unit is small enough to fit in the palm of your hand.

The case looks crowded, but there is plenty of room for all the parts. Note the power transistors mounted on the rear of the case.

**T**HIS supply is suitable for transistor circuits. It provides 1.5, 6.2 and 9.1 volts with excellent regulation. There is also a semiregulated output of about 20 volts. The power source is a size-D flashlight cell which energizes a transistor oscillator. The voltage is stepped up, rectified and then regulated by a Zener diode.


Potentiometer R1 controls the input to the oscillator. Its resistance is set as high as possible for the amount of power needed, to save battery power. You can measure the drain by plugging a meter into jack J1.

Four inexpensive diodes make up the bridge rectifier. Each one can handle up to 200 volts peak at high temperature. The choke's resistance must be low. Since ripple frequency is quite high, even a low inductance filters effectively.

There is no direct connection between the 1.5 volts from the D-cell and any of the stepped-up voltages. Thus the 1.5 volts may be combined with any of the others. For example, 6.2 volts minus 1.5 gives 4.7 volts.

The power box measures 5 x 3 x 2 inches. Transistors are mounted at one end, using a Motorola mounting kit available for this purpose. Correct polarity of the transformer is important. Base and collector windings are labeled B1, B2, C1, C2. B1 and C1 must connect to the same transistor.

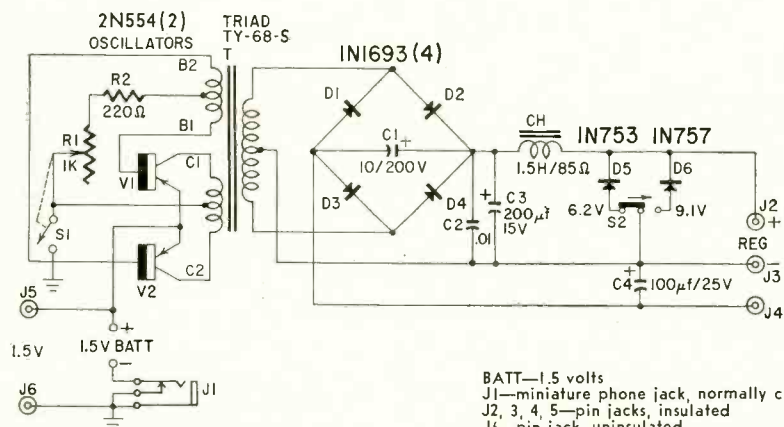Here are some of the advantages of this power source. It replaces expensive batteries and needs only a common flashlight cell. A maximum of about 20



- R1—pot, 1,000 ohms with spst switch
- R2—220 ohms, 1/2 watt
- C1—10 μf, 200 volts, electrolytic, miniature
- C2—0.01 μf, 500 volts, disc ceramic
- C3—200 μf, 15 volts, electrolytic, miniature
- C4—100 μf, 25 volts, electrolytic, miniature
- CH—1.5 henries, 85 ohms
- D1, 2, 3, 4—IN1693
- D5—IN753
- D6—IN757

- BATT—1.5 volts
- J1—miniature phone jack, normally closed
- J2, 3, 4, 5—pin jacks, insulated
- J6—pin jack, uninsulated
- S1—spst on R1
- S2—spdt slide
- T—transistor power supply transformer, 12 volt dc input, 250 volts, 65 ma from rectifier (Triad TY-68S or equivalent)
- V1, 2—2N554
- Mounting kit for transistor
- Holder for battery
- Case, 5 x 3 x 2 inches
- Miscellaneous hardware

Circuit of the simple portable power supply.

ma is available from the regulated voltages. An aging D-cell lowers this maximum, but cannot affect the voltage set by a Zener diode. Contrast this with direct battery operation where the battery voltage begins to drop as soon as it is put to use. Like a TV flyback circuit, this one puts out a limited amount of power, so it has built-in safety. If more than 20 ma is taken from one of the regulated voltage taps, the output drops sharply. The short-circuit current is only about 1 ma. This means

greater safety for the power supply itself and for the transistors you energize. At full drain, the D-cell will deliver nearly 250 ma. At light loads, the drain will be about 60 to 100 ma, which extends cell life to 30 hours or more.

If this power supply will be used often and at moderate drains, your best bet is to use one of the new rechargeable nickel-cadmium cells. I find a Burgess CD-7 very satisfactory for this application. At 250-ma drain it lasts 10 hours before recharging is needed. **END**

## TEST INSTRUMENTS

10 transistors at your fingertips.  
Just flip a switch to select the one  
you want

# TRANSISTOR SUBSTITUTION BOX

By **LEONARD J. D'AIRO\***

**T**HIS transistor substitution box has proved to be a pretty valuable piece of equipment on a number of occasions when transistor circuits were being checked out. It has taken a rightful place in my workshop, alongside the resistance, capacitance and inductance substitution boxes.

In this unit, there are substitutes for 10 transistors. Included are general-purpose, small-signal audio, large-signal audio, power and rf types. Selection is for useful characteristics and any combination may be used.

The combination shown in the schematic covers most practical applications. These transistors are:

- General purpose 2N107, 2N170
- Small-signal audio 2N132, 2N214
- Large-signal audio 2N217, 2N213
- Power 2N256
- Rf CK768, 2N484, 2N147


Note that in the first three groups, one transistor is a p-n-p and the other is an n-p-n, while the power transistor is a p-n-p (since most applications use a p-n-p unit). In the rf group, two transistors are p-n-p's and one is an n-p-n.

A transistor substitution box is, of course, much more expensive than the more usual capacitor or resistor substitute array, at first sight so much so as to appear impractical. But until we get a great deal more familiar with transistor receivers and can spot a bad transistor more easily, the positive answers it gives save enough servicing time to pay for it very quickly.

The transistors suggested in the parts list represent the average units used in transistor radios, amplifiers and related equipment. The types that are finally chosen and used should match the particular requirements of the user.


A cigar box or aluminum chassis box can be used to mount the selector switch and transistors. All wiring must be quite rigid and as short as possible. The power transistor must be mounted on a heat sink and kept as far as possible from other transistors. **END**

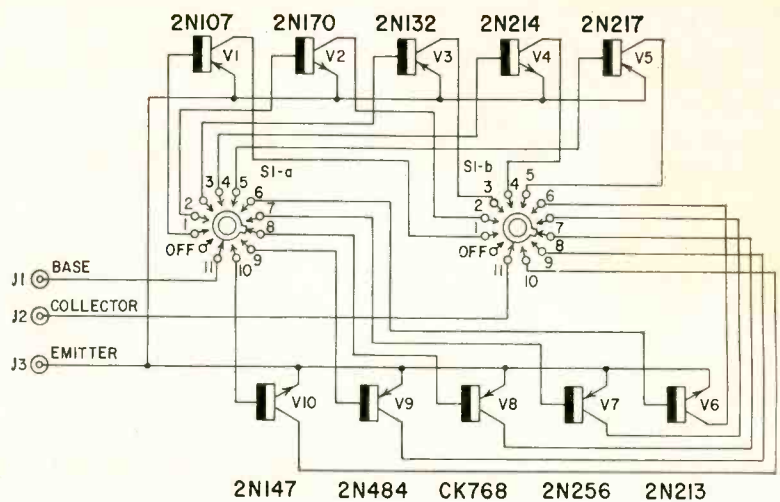\*Author *Servicing Transistor Radios*, Gernsback Library.




- |   |                        |
|---|------------------------|
| J1, 2, 3—3-way binding posts or tip jacks | V6—2N213               |
| S1—2-pole 12-position rotary, nonshorting | V7—2N256               |
| V1—2N107                                  | V8—CK768               |
| V2—2N170                                  | V9—2N484               |
| V3—2N132                                  | V10—2N147              |
| V4—2N214                                  | Chassis box to suit    |
| V5—2N217                                  | Miscellaneous hardware |


Circuit of the substituter.

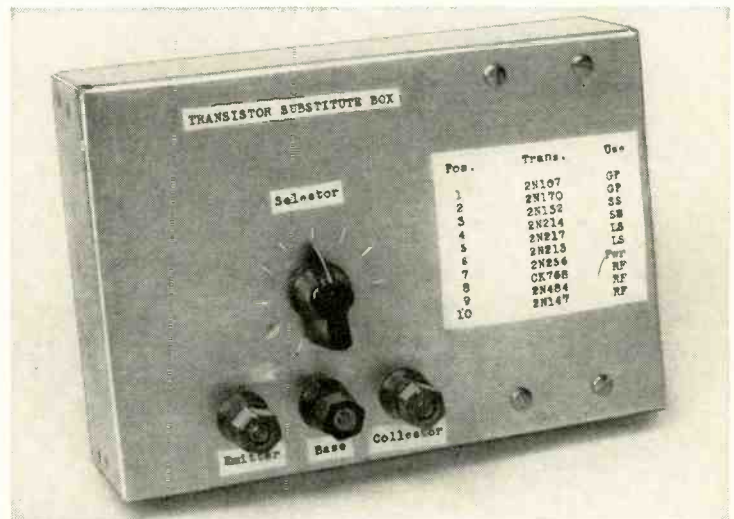

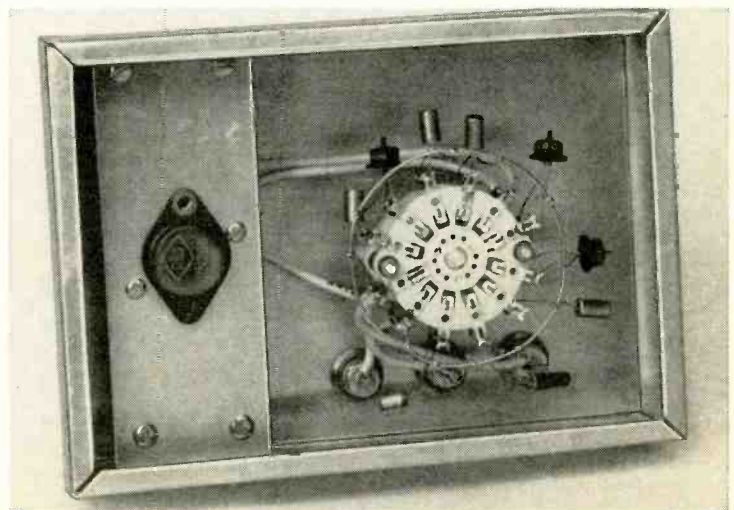Front panel of the transistor substitution box. Chart at right shows which transistor is in use.



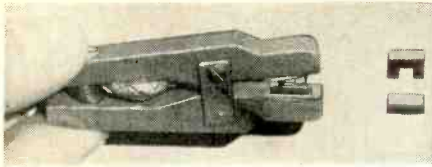Inside the substitution box. Author used transistors other than those in the schematic and listed on the box's front panel to match his own special requirements.



# CLAMP TYPE AC MICROAMMETER

**T**HE circuit shows a portable battery-powered ac microammeter developed by the National Bureau of Standards. It will measure currents between 200  $\mu$ a and 200 ma over a frequency range of 50 to 100,000 cycles.

The jaws of the probe contain the most difficult part of the unit—a pickup transformer. It is built as shown in Fig. 1. The core consists of C and I sections of 0.014-inch silicon-steel laminations with dimensions as in Fig. 1-b. Each winding consists of 250 turns of No. 44

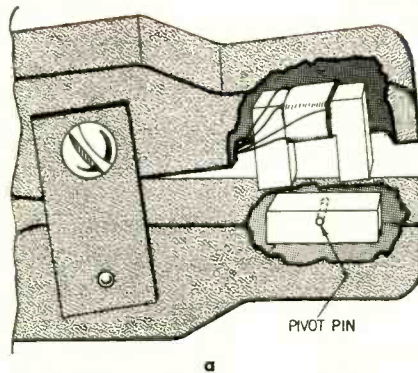


Fig. 1—Construction and mounting details of the pickup transformer.

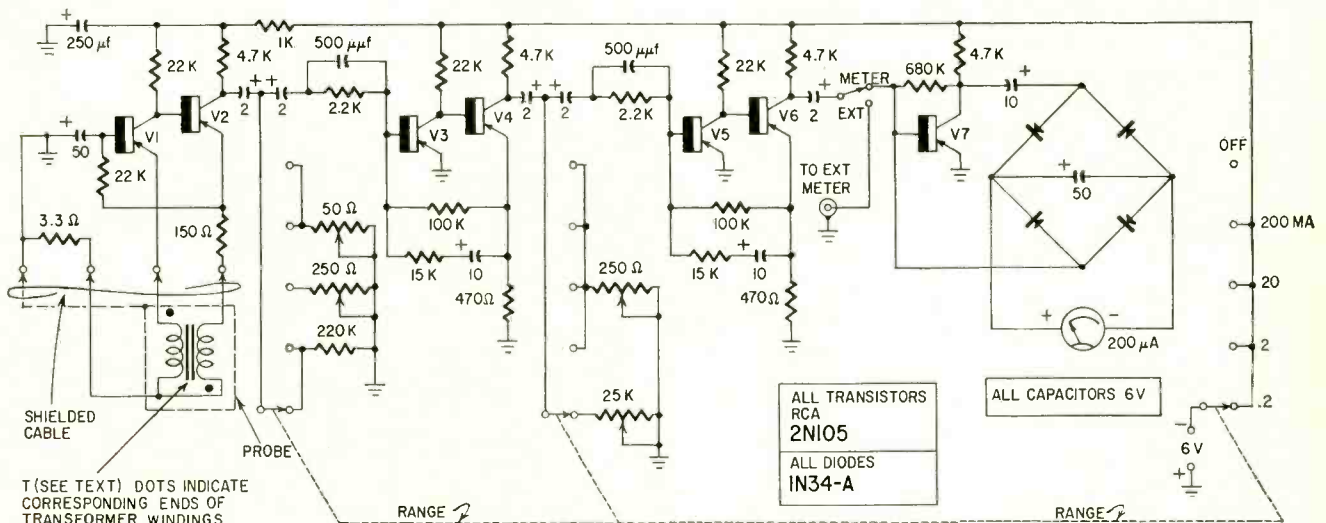
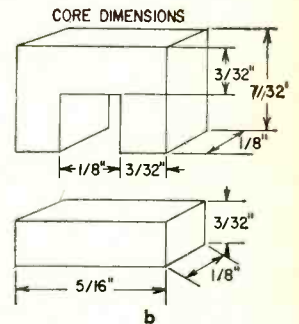


Fig. 2—Circuits of the all transistor meter.


enameled wire. Both are wound on the C-shaped section of the core. One winding of transformer T is the secondary and picks up the actual current. The transformer's primary is, of course, the conductor carrying the current to be measured. The other winding, the tertiary, forms part of a feedback circuit which provides frequency equalization. This winding makes the transformer's output between 100 and 100,000 cycles linear for a particular primary current.

The transformer's output is fed to the first part of the meter's circuitry (see Fig. 2), a two-transistor preamp. Gain in this stage is cut down by feedback which provides frequency stabilization and reduces phase shift at the higher frequencies. Two intermediate stages, each using two direct-coupled transistor amplifiers deliver the needed gain—about 20 db per stage. A 200  $\mu$ a dc meter is the indicator and is driven through a full-wave bridge.

The transformer core is mounted in a spring-loaded bakelite clamp, about

the size and shape of an ordinary clothespin (Fig. 1-a and head photo). The legs of the C project downward from the upper jaw of the clamp, while the I is contained in the lower jaw. A pin passes through the center of the I, providing rotary movement in the plane

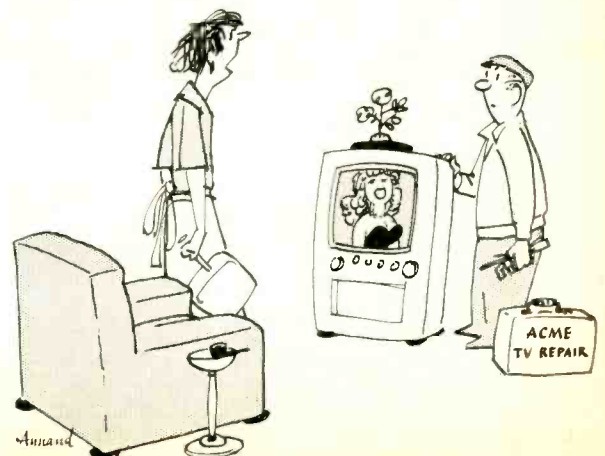of the jaws, so that the I will seat itself properly on the projecting legs of the C and close the gap as the clamp closes. The matching faces of these parts are ground. Shielding with Mumetal minimizes sensitivity to external magnetic fields. END



# STOP FEEDBACK



*The inventor of a completely new system of acoustic feedback elimination tells how it works in a story prepared especially for this magazine*

## L in PUBLIC ADDRESS SYSTEMS

By M. R. SCHROEDER \*

**F**EEDBACK is one of the fundamental facts of life. Without it we couldn't live and our machines wouldn't run. Basically, feedback means that the output of a something acts on itself, thus forming a feedback loop. The something can be a machine, a human being, a group of people, a plant—almost anything one might imagine. The action can be either inhibiting (negative feedback) or stimulating (positive feedback). A guest at a cocktail party who feels the effect of a drink and decides to reduce his further intake is an example of negative feedback. Negative feedback generally leads to a stable situation.

Not so, usually, positive feedback. Imagine another guest at the same party who feels stimulated in proportion to his previous consumption. This is a clear example of positive feedback leading to complete instability in the original mechanical sense of the word. Another example of positive feedback leading to instability is a burning house. Once the fire has started, the hotter it gets, the faster the rest of the house will burn down—unless the firefighters arrive in time. And that's what this story is concerned with: fire-fighting the instability resulting from positive feedback in a public-address system.

### Feedback in PA systems

While feedback is desirable and even essential in many instances, in public-address (PA) systems it certainly is not. It leads to the well-known "singing" and often outright "howling," rendering the system not only useless as far as amplifying the speaker's voice is concerned but actually annoying from the listener's standpoint.

Why does it happen? The answer to this question is simple: the sound from the loudspeaker(s) gets back into the microphone—either directly or after

bouncing off the walls of the room and other obstacles. If the total sound amplitude reaching the microphone from the speaker exceeds what went into the microphone in the first place and if this feedback sound is in phase with (reinforcing) the original input, we have positive feedback leading to instability which shows up as audible howling.

The next question is: what can one do about it? Again, the answer seems to be simple: turn the amplifier gain down! Here, however, we are running counter to the very purpose of PA systems—to amplify sound, not to attenuate it. In other words, there is competition between two basic requirements of a PA system: sufficient amplification on one side and stability on the other side.

Of course, one could sidestep the whole feedback problem by putting the orator in a glass-walled isolation booth. However, apart from the considerable cost involved, this does not look like a very popular proposal. (Also, the speaker might fear that the credibility of what he has to say is impaired by speaking from an isolation booth!)

Thus, the basic task of somehow reconciling sufficient amplification with stability when loudspeakers and microphones operate in the same sound field is still to be solved. Several proposals to improve this situation have been made in the past and are successfully used in existing PA systems. We shall discuss these first.

Imagine a PA system plagued with predominantly direct sound feedback. This happens when loudspeaker and microphone are fairly close to each other. Suppose further that the speaker has a strong response peak (a resonance) at some frequency. Then the maximum permissible gain for stable operation is given by the height of that response peak. If it sticks out 10 db above the otherwise flat response of the loop path of microphone-amplifier-loudspeaker-air-microphone, maximum

permissible amplifier gain is 10 db less than what it would be without that resonance peak. The loudness, on the other hand, is not increased by the narrow response peak, except at frequencies close to the resonance. So this time the loudness-stability compromise can be improved by equalizing the response peak of the speaker. It can be done by incorporating an adjustable anti-resonance in the system's preamplifier or power amplifier. Commercial amplifiers that use this principle have been on the market for some time and we need not concern ourselves with this case any more except to remember two things:

- ▶ Peaked responses are poison for PA systems.
- ▶ Equalizing such response peaks allows greater stable sound amplification.

Another powerful antidote for acoustic feedback is the use of directional microphones and speakers. This method is used extensively, and almost instinctively, in the field. Usually, loudspeakers and microphones have some degree of directionality and people place them so that as little sound as possible radiates directly from the speaker into the microphone. Nobody who has any feeling for the principles involved would place the microphone right in front of the loudspeaker.

Unfortunately, eliminating the *direct* sound feedback does not get rid of *all* feedback. There is still the indirect sound, reflected from the walls, ceiling, floor, audience, etc.—what room acousticians call the reverberant sound. To understand its effect and to minimize it, we must learn a little about room acoustics.

Luckily, all we need to know about room acoustics are some of the characteristics of steady-state frequency responses of rooms. One obtains the steady-state frequency response between two points in a room by putting a loudspeaker at one point, a microphone at the other, supplying the speaker with a tone of slowly varying

\* Bell Telephone Laboratories, Inc., Murray Hill, N. J.

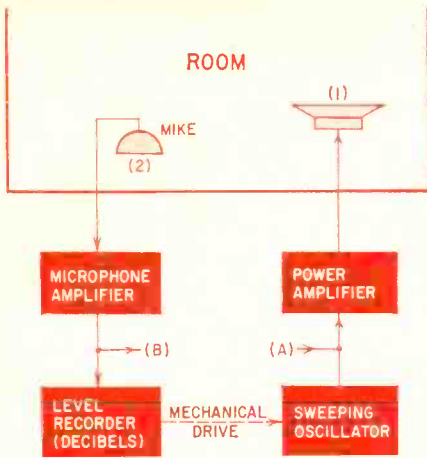


Fig. 1—How to get the steady-state frequency response between two points in a room.

frequency and recording the output of the microphone with a level (decibel) recorder. This is shown in Fig. 1. Such an experiment was performed by E. C. Wente<sup>1</sup> at Bell Telephone Laboratories in 1935. Dr. Wente was very much surprised at what he saw when he looked at the response records. A small section of such a frequency is reproduced in Fig. 2. In Dr. Wente's own words: "Within this small range of frequency, there are a large number of peaks and valleys and the variations in level are as much as 40 db. Any communications engineer looking at this transmission curve would classify the corresponding transmission system as a very poor one, perhaps incapable of transmitting intelligible speech."

Nevertheless, this is the kind of response a PA system operating in a room has to cope with and, as we pointed out above, it is just poison. The amplification or loudness of the PA system plus the room is given by the average level,  $g_{average}$ , indicated by a dashed line in Fig. 2. The maximum permissible stable gain is limited by the highest response peak, indicated by  $g_{max}$ . If rooms had flat responses (the dashed line in Fig. 2) or if they could be flattened by some trick, the gain could be raised by an amount equal to the difference between  $g_{max}$  and  $g_{average}$ , 12.5 db in the example of Fig. 2.

However, while it is not too difficult to equalize a single peak, a loudspeaker's resonance for instance, it becomes completely impossible in the case of the myriad peaks of a room. Typically, a room has several thousand such peaks in the audio range.<sup>2</sup> To make things worse, these peaks are not fixed. They move about as the location of the person speaking, the microphone, the loudspeaker or the audience is varied. In other words, the response of a room cannot be equalized. We just have to live with it.

The frequency-shifting idea

If we cannot do anything about the room, perhaps we can do something

about the signal radiated by the loudspeaker. More specifically, we may ask whether we can modify the signal so it no longer cares how jagged the room response is or, to put it differently, so its feedback stability is determined not by the peaks of the response but by the average level. Furthermore, is there such a modification that is at the same time imperceptible to the audience? This sounds like asking too much. But, fortunately, the answer to both these questions is yes.

The trick is to shift all frequency components of the signal by a small but constant amount. The frequency-shift apparatus may be inserted between the microphone amplifier and the power amplifier, as shown in Fig. 3, or incorporated in either one.

Telephone engineers have found that small frequency shifts of speech signals, a few cycles per second, are

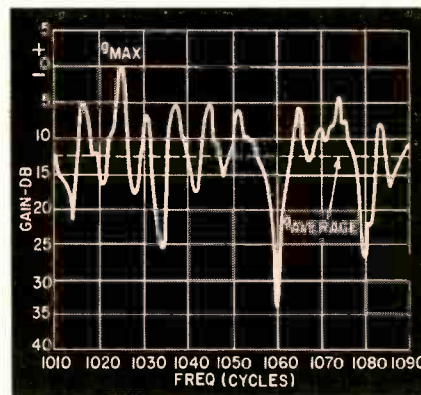


Fig. 2—Over an 80-cycle spread, amplifier gain may show a variation of more than 30 db.

nearly imperceptible and that frequency shifts as large as 20 cycles are still tolerable.<sup>3</sup> In fact, involuntary frequency shifts occur all the time in single-sideband telephony. Every time we make a long-distance call, our voice arrives at its destination shifted by a few cycles in frequency.

Now that we know that frequency shifting does not hurt us, the next question is, "Does it help?" To answer it, we refer again to Fig. 2. As the signal we assume a simple 1,025-cycle sine wave. The gain for this frequency is  $g_{max}$ . If in Fig. 1 the input of the power amplifier (A) is connected to the output of the microphone amplifier (B) to form a PA system and if the gain is raised by a slight amount, our sine wave will continuously grow in amplitude for every trip around the feedback loop.†

With frequency shifting (see Fig. 3), the picture is completely changed because, for every trip around the feedback loop, the frequency of our signal is shifted by, say, +5 cycles. Thus, on the second trip around, the signal frequency is 1,030 cycles for which the

† In addition to the loop gain exceeding zero db, a certain phase condition<sup>4</sup> has to be fulfilled. However, among the thousands of peaks of a room, one can always find several for which this condition is fulfilled if the maximum loop gain exceeds zero db by a small amount.

loop gain, according to Fig. 2, is about -10 db. On the third trip around the feedback loop, the signal frequency is again shifted by +5 cycles and is now 1,035 cycles. The gain for 1,035 cycles is again about -10 db. And so forth. In short, the cumulative amplification of a signal as it goes round and round the feedback loop is no longer determined by the possibly very high gain at its original frequency but by the average gain of the room response. Thus, while the room response is actually unchanged, from the feedback point of view it is as if the peaks of the response had disappeared and been used to fill up the valleys of the response curve. Frequency shifting does the seemingly impossible. No matter how jagged the response is, it completely flattens it, at least as far as feedback stability is concerned. And that is what we are interested in.

An approximate theoretical formula<sup>5</sup> has been derived for the difference between the maximum and the average gain—the extra stable gain to be expected from frequency shifting:

$$g_{max} - g_{average} = 10 \log_{10} [\log_e TW] + 2.5 \text{ db}$$

Here T is the average reverberation time of the room and W is the bandwidth of the PA system. And  $e = 2.718$ —the base of the natural logarithms. Because of the double logarithm, the result depends little on T and W. For example, if  $W = 5,000$  cycles and  $T = 1$  sec,  $g_{max} - g_{average} = 11.8$  db. For  $T = 2$  sec,  $g_{max} - g_{average} = 12.1$  db.

Thus, one may say that from a stability point of view, the permissible increase in gain when using frequency

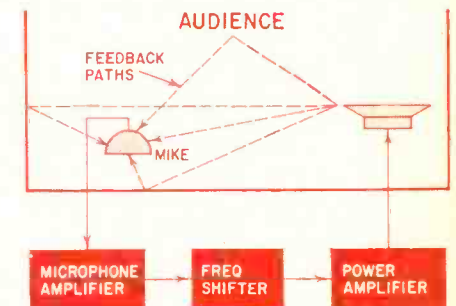


Fig. 3—The frequency shifter is inserted between the microphone amplifier and the power amplifier.

shifting is about 12 db. This theoretical prediction is borne out by the measurements (Fig. 4).

From a subjective point of view, the performance has to be evaluated differently. Without frequency shifting, the loop gain must remain below approximately -3 db for the "singing" to be tolerable. With frequency shifting, the gain can be raised to +3 db, for similar subjective acceptability. For gains in excess of +3 db, the performance of the PA system, while still stable, becomes less and less pleasing. Thus, from a subjective point of view, frequency shifting is worth about 6 db of in-

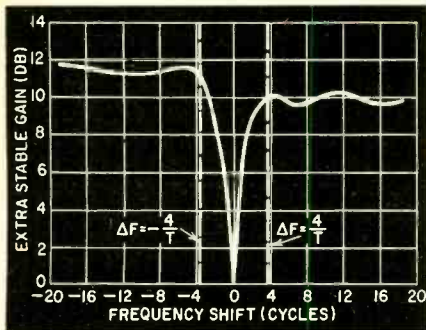


Fig. 4—From the viewpoint of stability, phase shift permits about a 12-db increase in gain.

creased gain plus several decibels of additional margin against howling.

Optimum frequency shift

Now that we know that frequency shifting is so helpful, the question naturally arises as to whether there is an optimum value for the amount of shift. Here again a look at Fig. 2 provides the answer. Obviously, if we are shifting only a minute amount, say 1 cycle, it will take the signal many trips around the feedback loop (Fig. 3) before it is shifted enough in frequency to reach the next valley—a point of low amplification. In the meantime, the signal may have built up to a very large amplitude. An optimum or, in any case, a good value for the frequency shift is the average distance between the peaks and valleys. In this manner, a frequency component that starts out at a point of high gain reaches a point of low gain as quickly as possible, namely after one trip around the feedback loop.

The distance between the response peaks and adjacent valleys of a room is roughly 4 divided by the reverberation time.<sup>6</sup> Since most rooms have reverberation times of about 1 second, a good value for the frequency shift is 4 or 5 cycles. This prediction is confirmed by our measurements in various auditoriums and rooms. Fig. 4 shows the extra stable gain that can be realized by frequency shifting as a function of the amount of the shift. These measurements were made in the Bell Telephone Laboratories Auditorium at Murray Hill, N. J. The average reverbera-

tion time, T, in this auditorium is very close to 1 second. Thus, the theoretically required shift is 4 cycles. Fig. 4 shows that a shift of this magnitude is indeed sufficient. For larger shifts, the extra stable gain remains between 9.5 and 12 db. This means that the actual shift is not very critical as long as it is more than 4/T cycles. The fact that negative shifts give somewhat better results than positive shifts has no general significance. It is advisable to use frequency shifters which can shift both upward and downward and to decide in each case which direction of the shift is preferable.

Single-sideband frequency shifting

A convenient method of effecting a constant-frequency shift is single-sideband modulation as shown in Fig. 5. The signal is first amplitude-modulated upon a carrier frequency of, say, 20 kc. A bandpass filter with a sharp lower cutoff (SSB FILTER 20KC-30KC) removes the lower sideband. The upper sideband is then demodulated by a carrier of, say, 19.995 kc. The resulting signal has all its frequency components shifted by +5 cycles. The only technical problem is to keep the difference frequency between the two carriers close to the desired amount—5 cycles in our example. This can be done with crystal-controlled oscillators, negative feedback control, or by deriving the second carrier frequency from the first one and a 5-cycle sine wave by "quadrature modulation" as illustrated in Fig. 5. Note that the 20-kc oscillators are made up from a 40-kc oscillator and frequency-dividing flip-flops. A circuit of this kind, using 29 transistors, was used in our experiments and demonstrations. We are now building a frequency shifter with crystal controlled oscillators. This promises much simpler, more reliable and less critical equipment. The improved frequency shifter will be described in detail in a forthcoming publication.

A word of caution

Frequency shifting offers a powerful protection against howling caused by acoustic feedback. Because of the extremely widespread use of public-address systems, the method described here could be of benefit to many people

—audiences and speakers alike. However, like any invention, it should be used intelligently. In particular, one should not exploit the additional stable gain exclusively for greater amplification (loudness). Rather, one should reserve a certain portion of the extra stable gain as an additional insurance against accidental increases in feedback that may be caused by heating up of amplifiers, changes in the audience or of the speaker's location. Such intelligent use could be enforced by providing access to the volume control only when the frequency shifter is inoperative. In this manner the gain would never be adjusted to a value above the singing point (except by deaf people). After setting the gain potentiometer and switching in the frequency shifting, the system would have a safety margin of about 10 db against instability and a 3-6-db margin against undesirable subjective effects. In addition, there is a considerable increase in loudness because a PA system without frequency shifting has to be operated several decibels below the singing point.

Acknowledgements

I am grateful to Dr. Erwin Meyer, my professor at Goettingen University, for bringing me into contact with the interesting problems of steady-state sound transmission in rooms, the solution of which formed the basis of the present invention. I am also indebted to Drs. J. R. Pierce and E. E. David, Jr., at Bell Telephone Laboratories, for drawing my attention to the acoustic feedback problem. Mr. H. W. Hines assisted me in the construction of the frequency-shift apparatus, and Mr. J. E. West helped me with the measurements. END

References

- <sup>1</sup>E. C. Wente, *J. Acoust. Soc. Am.*, Vol. 7 (1935), p. 123.
- <sup>2</sup>H. Kuttruff and R. Thiele, *Acustica*, Vol. 4 (1954), p. 614 (Beiheft 2).
- <sup>3</sup>H. Fletcher, *Speech and Hearing in Communication*, D. Van Nostrand Co., New York (1953), p. 352.
- <sup>4</sup>H. Nyquist, *Bell Syst. Tech. J.*, Vol. 11 (1932), p. 126.
- <sup>5</sup>M. R. Schroeder, *Proceedings of Third International Congress on Acoustics*, Elsevier Publishing Co., Amsterdam (1960) (to be published).
- <sup>6</sup>M. R. Schroeder, *Acustica*, Vol. 4 (1954), p. 594 (Beiheft 2).

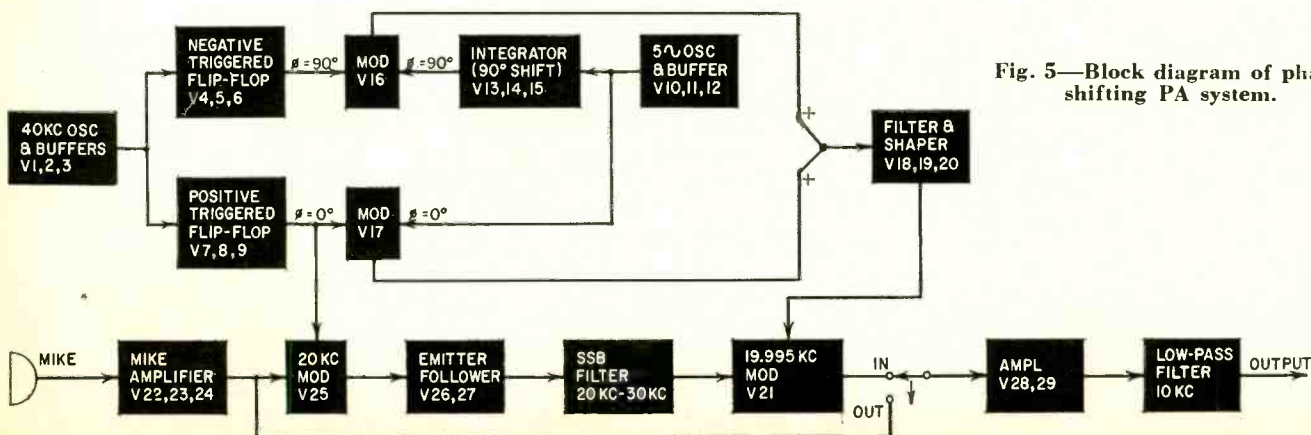


Fig. 5—Block diagram of phase-shifting PA system.



# TAPE RECORDER WORD PUZZLE

By JOHN A. COMSTOCK


HERE is a sound-on-tape puzzle for you to work that is made up entirely of tape-recording words and terminology. If tape recording is your hobby or interest, you will find this puzzle fun to do, and a challenge, too! (Answer on page 132)

**ACROSS**

1. Iron-oxide-coated plastic or paper ribbon.
3. The metallic oxide on recording tape.
4. A playback head with a narrow --- provides better high-frequency response than a head with a wide one.
5. A tape recorder with fast ----- saves one's patience in waiting to hear the playback.
6. Material which serves as a base for most recording tapes.
9. A type of plastic which serves as a base for some recording tapes.
11. Many recorders have two speeds. They are called ---- speed units.
12. The tape recorder part that places magnetic variations on tape.
14. A recorder which is capable of giving a three-dimensional sound effect.
15. A microphone (slang).
17. The spools on which tape is wound.
19. A slow unsteadiness of sound volume and pitch caused by variations in the tape's speed as it travels by the record or playback head.
21. Type of tape added at the beginning of a reel. Often used for indexing.
22. To put intelligence on tape.
23. When the stop button is depressed, the ----- stop both reels simultaneously.

**DOWN**

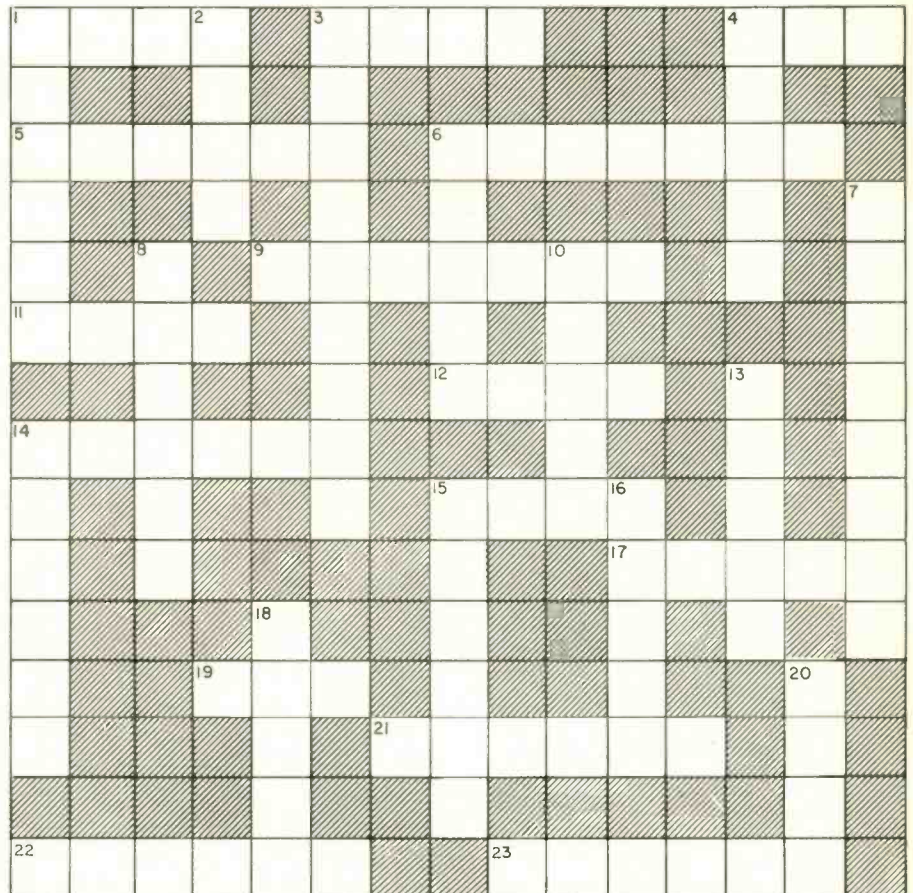1. In selecting a tape recorder, one should choose a recorder that is easy to -----.
2. To cut out portions of tape and eliminate unwanted material.
3. Some recorders have a VU meter as a record level ----- while others have a tuning eye or neon lamp that serves the same function.
4. Some recorders have a tape ----- or roller around which the tape passes to keep it correctly positioned.
6. Jumper cord used to record from radio, TV or record player.
7. If music is to be recorded, it is advisable to select a faster tape speed to improve frequency -----.
8. The reel on which tape is wound



10. Most recorders are dual -----.
13. When recording, you must watch the record ----- indicator to prevent distortion due to overmodulation.
14. Join two pieces of recording material.
15. A ----- passed over a tape will remove the recorded intelligence.
16. Tape may be used almost indefinitely because it is possible to ----- the tape and use it over again almost any number of times.
18. The electromechanical device which provides power to turn the reels and move the recording tape.
20. The current which flows through the recording head and sets up a varying magnetic field. **END**

## High-Fidelity AM Broadcast Station

WLW in Cincinnati has rebuilt its equipment completely for hi-fi sound an attempt to parallel on AM what some FM broadcasters have been doing. After the reworking job, which cost \$300,000, the 50-kw station claimed it is "the highest-fidelity station in the world." The statement also carried these details: "within ±1 db from 17 to 21,500 cycles, with distortion less than 0.3%."

Frank McIntosh, head of McIntosh Laboratories, prominent high-fidelity equipment maker, and inventor of the McIntosh "unity-coupled" audio out-

put circuit, made measurements and tests on the rebuilt equipment and the broadcast signal. He said that the station is providing as high-quality transmission to its listeners as any station on the air.

WLW has changed its programming from the top 40 tunes and rock'n'roll to one of standard tunes, show music and classical selections. The business manager says they've increased the number of regular listeners appreciably, and are selling more commercial time than before the changeover. Apparently high fidelity *can* be profitable.

RCA's

2

# -WAY STEREO AMPLIFIER

*Unique circuit lets the customer add a speaker and flip a switch to change his single-channel push-pull amplifier into a dual single-ended job for stereo reproduction*

By **ROBERT F. SCOTT**  
TECHNICAL EDITOR

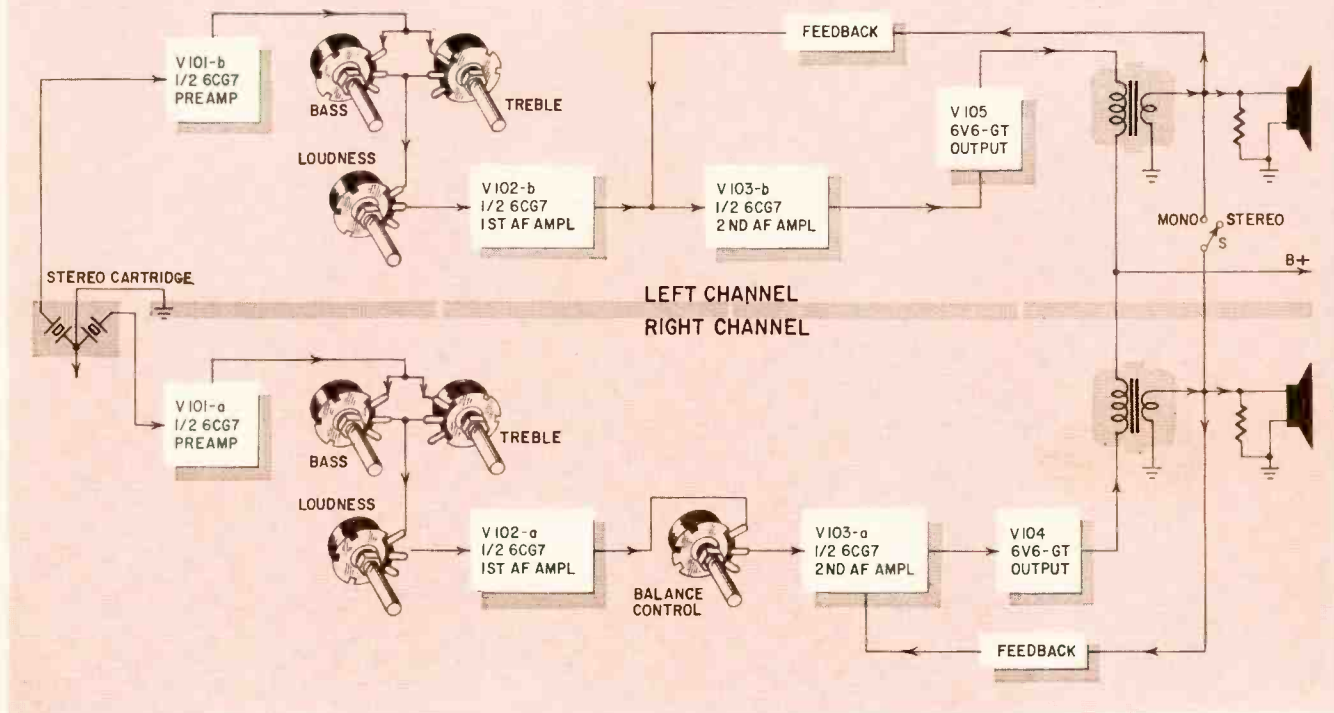


Fig. 1—Basic diagram of the RCA circuit.

**D**URING a year that stereophonic records and tapes have been widely available at reasonable prices, reproducing equipment has generally consisted of two complete monophonic amplifiers on the same or separate chassis. In single-chassis models, the cost has been slightly greater than that of a monophonic amplifier with equivalent frequency response and total power output. Two new circuits have been devised to eliminate the amplifier for the second channel and thus greatly reduce the cost of stereo equipment for the audiophile. All he needs is a second speaker to convert from monophonic to stereo reproduction.

The circuit developed by CBS-Columbia accepts stereo input signals and reproduces one channel with the output tubes working in parallel and

the other channel with the tubes effectively in parallel. This circuit is described in "Two-Way Stereo Amplifier," by Bauer, Bachman and Hollywood, in the December, 1958, issue.

The second circuit is the RCA development described here. Basically, it consists of two single-ended amplifiers operating independently for stereo and as a single push-pull amplifier for monophonic reproduction. This system is used in some recent Victrolas and AM-FM phonograph combinations. These units can be converted to stereo simply by adding another speaker. The block diagram of the RCA two-way stereo amplifier is shown in Fig. 1.

#### Basic circuit

The cartridge used with the amplifier is phased to deliver equal and out-of-phase signal voltages from stereo and

monophonic records. These signals are fed to the grids of preamplifiers V101-a and V101-b. They are amplified by V102 and V103 and appear out of phase at the plates of power amplifiers V104 and V105.

Speakers must operate in phase for satisfactory stereo or monophonic playback so the phase of the output signals in one of the channels is inverted by reversing the primary connections to one of the output transformers. Thus, in-phase speaker operation is obtained from two identical amplifiers with out-of-phase inputs.

Switch S is a part of the function-selector switch connected to corresponding taps on the secondaries of the output transformers. During stereo playback, S is open and the two amplifiers are entirely separate and independent. When S is closed, the trans-

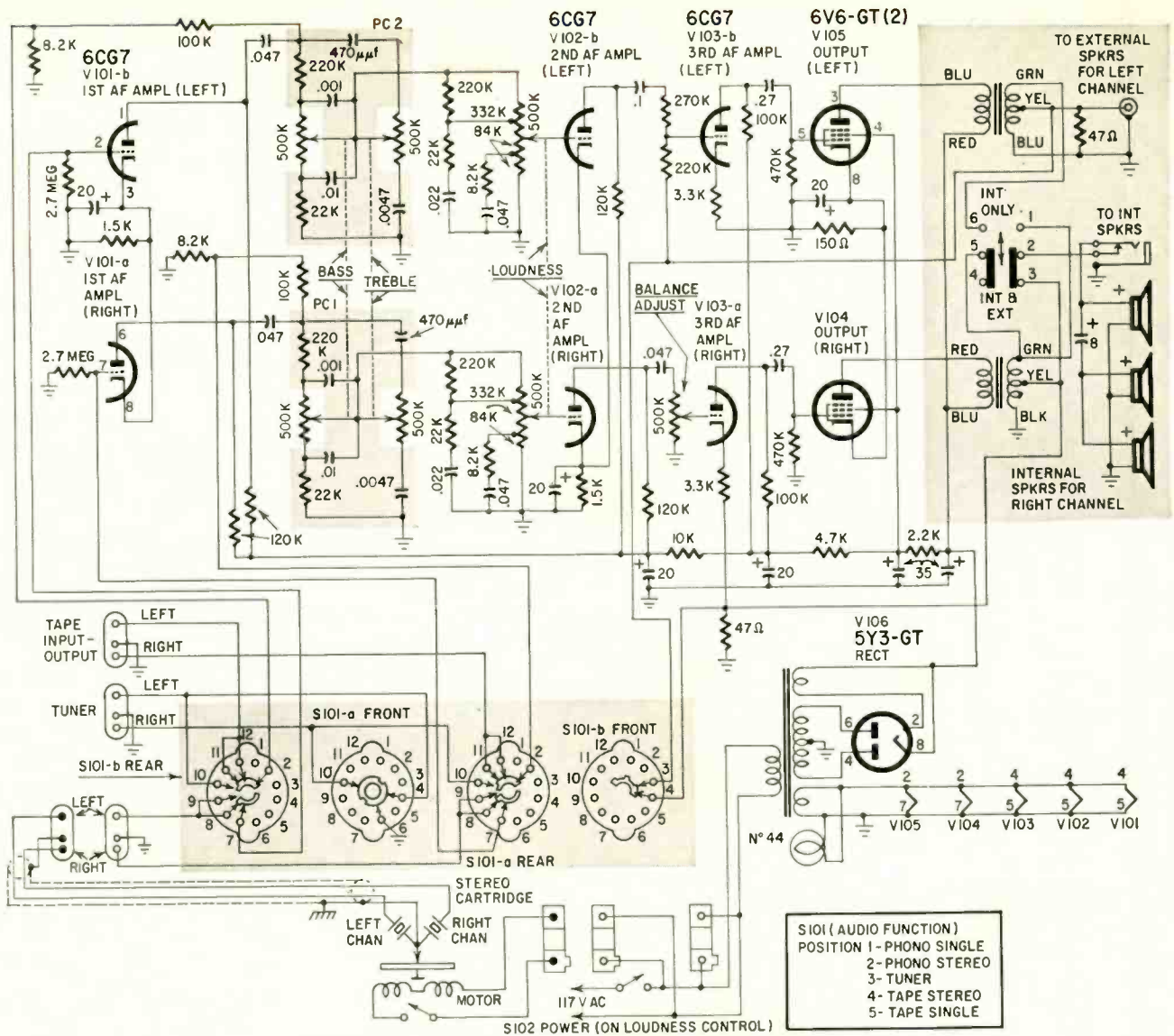


Fig. 2—Schematic of the dual-channel amplifier.

former secondaries and speaker voice coils are connected in parallel for monophonic operation. Since the signals at the output plates are out of phase and those at the speakers are in phase, circuit action is essentially the same as for normal push-pull operation with phase inversion taking place in the output transformer instead of some low-level point in the amplifier.

**Schematic analysis**

The circuit of the unique RS-171 amplifier used in the SHC-8 and SHC-9 stereophonic combinations is shown in Fig. 2. Inputs from the tuner, tape recorder and phonograph cartridge are connected to individual input terminals. The five-position AUDIO FUNCTION switch (S101) selects the desired input and mode of operation. In the PHONO and TUNER positions, the TAPE jacks are connected to the preamp plates and can deliver stereophonic signals to a stereo tape recorder.

The AM-FM tuner included in the RCA combinations cannot be used for AM-FM stereocasts. An AM-FM selector switch on the tuner chassis selects either the AM or FM output and feeds it to the amplifier's TUNER input terminals. The selected direct output from the detector is fed to the amplifier's right channel and to the input of a zero-gain phase inverter. (See Fig. 3.) The phase inverter's output is fed into the left-channel input terminal. Thus equal and out-of-phase monophonic signals are applied to the right- and left-channel inputs.

Bass, treble and loudness controls are conventional. Corresponding controls for each channel are ganged, using especially selected potentiometers to insure good tracking. In the left channel, the grid of the second af amplifier (V103-b) is fed approximately half the voltage developed across a voltage divider consisting of 270,000- and 220,000-ohm resistors in series. The corresponding stage (V103-a) in

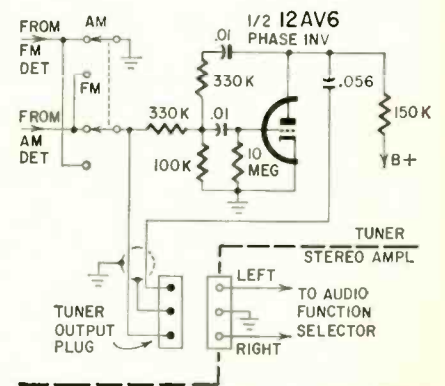


Fig. 3—Simplified diagram of the input switching arrangement.

the right channel is fed from the arm of the 500,000-ohm BALANCE control so the outputs of the two channels can be balanced no matter which one is weaker.

Approximately 15 db of negative feedback is applied around the last two

# AUDIO—HIGH FIDELITY

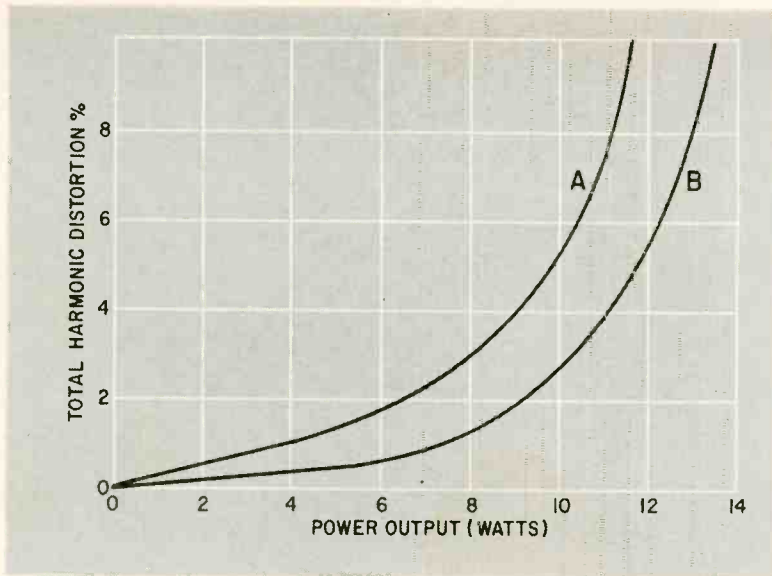


Fig. 4—Comparative distortion curves for dual single-ended amplifiers vs push-pull version.

stages in each amplifier. The voltage developed across the 4-ohm voice-coil taps is 180° out of phase with the signal input to V103-b, so feedback is applied in series with its grid. In the right channel, the feedback voltage and input to V103-a are in phase so the feedback is applied in series with the cathode.


The plates of the output tubes are supplied directly from the rectifier output. Residual ac ripple is high at this point but, since it is injected inside the feedback loop, hum is degenerated by the feedback factor. Furthermore, because hum is in phase on the output plates, it cancels—through phase inversion—in the voice-coil circuit. Thus hum is reduced to a level approaching the result of cancellation in a well-balanced conventional push-pull output stage.

Even-order harmonics generated in the two channels are in phase throughout the amplifiers so they cancel when the voice-coil circuits are paralleled for monophonic operation. Curve A in Fig. 4 shows the power-distortion characteristics for stereo and B shows monophonic (push-pull) performance.


The Victrolas and RCA combinations have internal speakers connected to the right-channel amplifier. A jack is connected across the secondary of the left-channel output transformer for adding the second speaker required for stereo and often desired for monophonic playback. See Fig. 2 for a look at the switching circuit.

When the switch is in the INT ONLY position and no speaker is used in the left channel, both amplifiers are paralleled across and properly matched to the internal speakers. The parallel connection insures that the amplifiers are effectively in push-pull regardless of the position of the input selector.

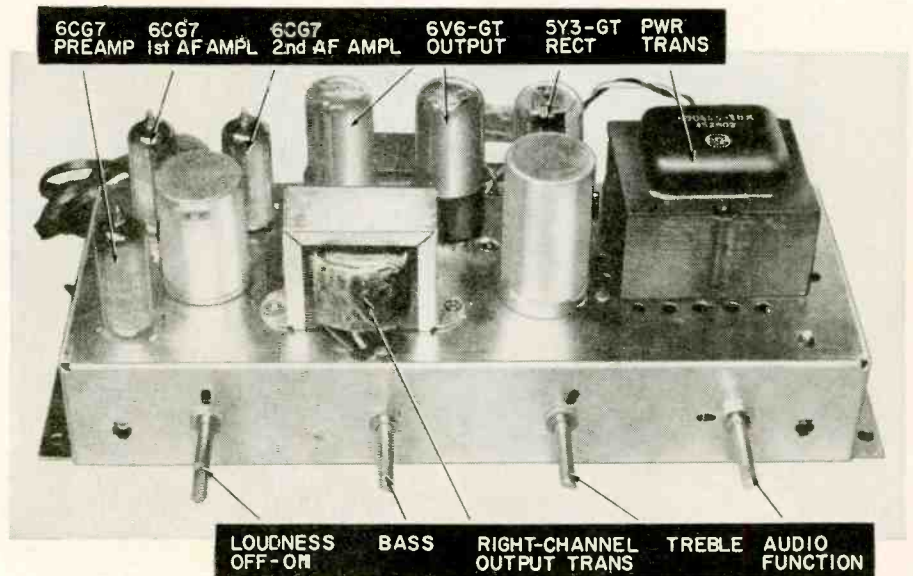In the INT & EXT position, the left channel feeds the external speakers. The amplifiers are operated single-ended for stereo and in push-pull—by paralleling the transformer secondaries—for monophonic reproduction. END



RCA uses 6 tubes in their stereo unit.

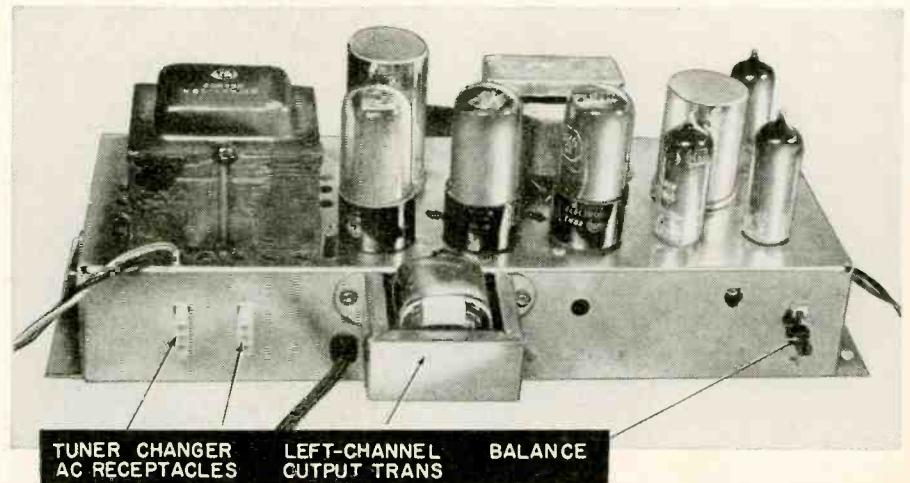

The balance control and the left-channel output transformer are mounted on the rear of the chassis.

# DESIGN

Part II—Tone controls, how they work and how to make them give the results you want

# YOUR OWN PREAMP

By NORMAN H. CROWHURST\*

At one time tone controls were used for a wider variety of purposes than nowadays, including, for example, compensation for deficiencies in the equalization characteristic. But modern preamps have equalization characteristics which accurately restore the original flat frequency response applied to the recording amplifier in making the recording. Of course this does not mean that the recording and reproduction chain is now perfect.

At the studio end, the system's balance is adjusted according to the judg-

ment of the people responsible for making the recording.

This means that a good preamp permits adjusting the comparative response to lower and higher frequencies independent of the equalization characteristic. The first thing to decide is how you want to vary the response at the low and high ends.

### High-frequency tone controls

Without going into peaking circuits, there are two ways of varying the response. As referred to the high end, these are illustrated in Fig. 1. At Fig. 1-a, a certain frequency is used as a

starting point (500 cycles) and the response may be pushed up or down, from this frequency upward, to a varying degree which is set by the treble control. The other type of adjustment raises or lowers the frequency at which accentuation or rolloff begins (Fig. 1-b).

shown in Fig. 1-a. At the lower end of the spectrum, attenuation in the network is determined by the purely resistive voltage divider, R1 and R2. At the upper end of the frequency response, the reactance of the capacitors brings the potentiometer in parallel with the fixed resistance arrangement and modifies attenuation according to the potentiometer's setting. The frequency at which the change in level begins to have effect is determined by the relation of the reactances of the capacitors to the resistances in the circuit.

To design this circuit we must pick an attenuation that fixes the maximum high-frequency boost we can get. Assume we decide to provide a maximum of 14-db boost. This means the attenuation must be 14 db, or the tapping point on the fixed resistance divider must be one-fifth of the total resistance. So resistor R1 must be four times R2.

So that overall response is level when the pot's slider is one-fifth of the way from the bottom end, the capacitors' reactances should be in the same proportion. C1 should have four times the reactance of C2; or, in capacitance, C2 should be four times C1.

The lower turnover point—the sort of "swivel" point in Fig. 1-a, where maximum boost is 3 db and maximum rolloff 3 db—comes out where the reactance of R1 is equal to the reactance of C1 and the reactance of C2 equals R2's resistance.

Different fixed positions, giving responses similar to those in Fig. 1-b, can be produced by the circuit shown

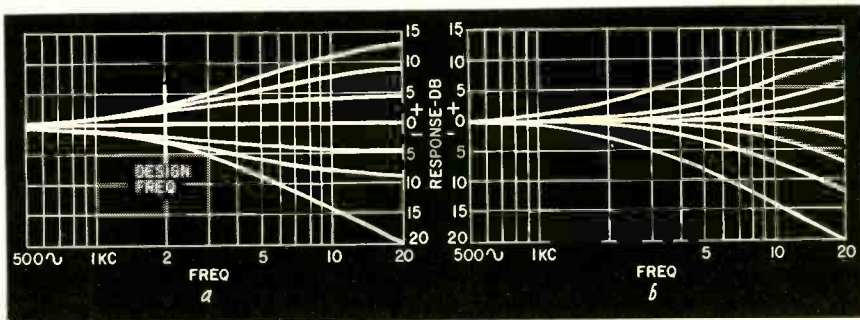


Fig. 1—Two basic methods of altering response with a treble tone control: a—a variable amount of boost or rolloff is applied, beginning at the same frequency; b—the point where boost or rolloff starts is shifted.

ment of the people responsible for making the recording. The recording studio or auditorium may have excessive brilliance in its reverberation characteristic, causing overemphasis at the high end. It may also produce peculiar effects at the low end, or at any other frequency in the band. Some efforts are made during recording to give satisfactory balance in the recorded program.

However, when this program is reproduced in a living room, the best judgment of balance may not always agree with that determined by the people making the recording. All these things are at best a compromise and the living room in which you reproduce the sound adds further reverberation or acoustic characteristics to the reproduction. This may modify the best compromise for any particular piece of

starting point (500 cycles) and the response may be pushed up or down, from this frequency upward, to a varying degree which is set by the treble control. The other type of adjustment raises or lowers the frequency at which accentuation or rolloff begins (Fig. 1-b).

Fig. 2-a shows a basic circuit designed to give the response variation

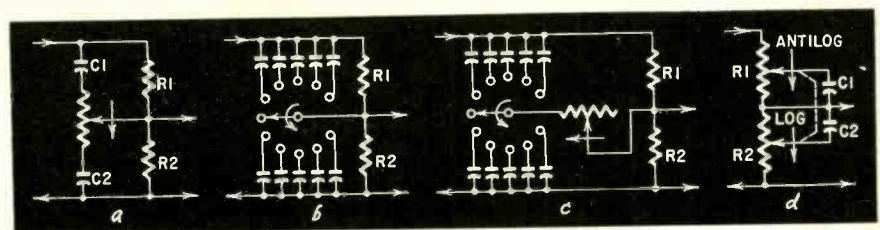


Fig. 2—Basic circuits for high-frequency tone control: a—continuously variable, results like Fig. 1-a; b—fixed steps, results like Fig. 1-b; c—results are combination of Fig. 1-a and Fig. 1-b; d—continuously variable combination of results of Fig. 1-a and Fig. 1-b. Arrows on pots and switches indicate rotation from maximum boost to maximum rolloff.

\*Author: High-Fidelity Circuit Design (Gernsback Library).

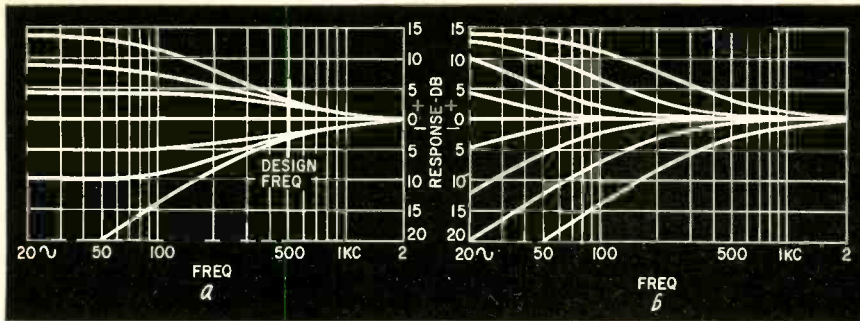


Fig. 3—Two basic methods of varying low-frequency response produce these results.

in Fig. 2-b. It switches a series of capacitors across R1 to produce 14-db boost (using the same values as for Fig. 2-a) starting at different frequencies, or across R2 to produce a rolloff, also starting at different frequencies.

For simplicity, Fig. 2-b shows a single-pole switch with a number of capacitors that connect to either the top or bottom of the R1, R2 combination. Economizing in capacitors by using a 2-pole switch (one pole to select the appropriate capacitor and the other to determine whether the capacitor is connected across R1 or R2) does not work. It is not possible to halve the number of capacitors, because different ranges of values are required for shunting R1 and R2 to get the same range of turnover frequencies for boost and rolloff.

A refinement to this method calls for including a variable resistance in series with the capacitor—or more conveniently in series with the switch arm so that the amount of boost or rolloff can be determined too. This is shown in Fig. 2-c. In effect the circuit combines the responses of Figs. 1-a and 1-b.

A circuit that provides continuously variable boost and rolloff in respect to the frequency at which it starts and the amount is shown in Fig. 2-d. This requires a two-gang potentiometer in which the value of the two resistance elements is in the same ratio as the maximum amount of required boost—say 4 to 1 for a 14-db maximum boost.

For this circuit to operate most effectively, resistance tapers should be complementary. Both can be linear or, preferably, R2 should have a log taper while R1 should have the so-called antilog taper. Under these conditions, when both potentiometers are set to their middle position, response is flat and the capacitors are shunting only about one-tenth of their respective resistance. This makes the frequency range of this kind of control much greater than one using linear potentiometers.

Low-frequency tone controls

Turning to bass compensation, we can produce a similar family of curves by corresponding circuit arrangements. The two possibilities for curves are shown in Fig. 3, and the circuits in Fig. 4. Resistors R1 and R2 provide

the basic attenuation for the upper end of the range this time. In Fig. 4-a, C1 and C2 control the turnover frequency and R3 varies the bass boost or rolloff.

R3 should be large compared to R1 or R2. Bass boost or rolloff begins at the frequency where C1's reactance equals R1, and C2's reactance equals R2. The response is, of course, level when the slider is the same fraction up resistor R3 that R2 is of the total R1 + R2. This produces a response variation of the pattern shown at Fig. 3-a.

Fig. 4-b produces a number of fixed responses similar to those shown in Fig. 3-b. Fixed resistors R1 and R2 determine the maximum amount of boost while the 2-pole switch determines which side the capacitors are in and what value capacitor is used.

It is not readily possible, without using inductors instead of capacitors, to produce a circuit corresponding to Fig. 2-d for the low-frequency response. Fig. 4-c shows the nearest approximation that can be made with capacitors. This is because the arrangement that varies the rolloff frequency, rather than the amount, requires a variable resistance in series with the capacitors instead of in shunt as in Fig. 2-d. This means that attenuation is fixed at the extreme low-frequency end, but variable according to the setting of the control (R1, R2) through the larger part of the low-frequency region, which is what controls how loud the program sounds. Obviously, this is undesirable, but can be offset by introducing a third potentiometer

(R3) to produce further attenuation in reciprocal fashion. Now, when the boost-or-rolloff control is set for minimum attenuation (R1, R2, R3), representing maximum rolloff, the additional control (R3) is set for maximum attenuation, and vice versa. To make this work, the range of control must be limited by "bottom-end" resistors or the program would go off at each end position.

The circuit is not altogether satisfactory, because it relies on all of the potentiometers having the right taper for maintaining constant gain over the greater portion of the low-frequency region. The best tapers to use are the semi-log tapers direct and reverse.

Practical composites

Having discussed the various possible controls for a versatile variation of response, the next question is how to incorporate them into practical circuits. As with fixed equalizer networks, they may be inserted between stages of an amplifier or be used as part of a feedback network over a section of an amplifier. From the design standpoint, the forward method is simpler.

The basis for design has already been mentioned as each type was discussed. We will just take a simple design of a composite tone control circuit as an example of how to apply it in an actual circuit. Design can be made ideally simple by feeding the tone control circuit from a cathode follower to give a very low source resistance.

As any tone control causes a loss of gain for the same reason an equalizer does (to provide "headroom" for the boost), additional stages are necessary to make up for the lost amplification. So in this design we'll assume we do not try to use a cathode follower. Using a 12AU7 tube with a 250-volt plate supply, a 47,000-ohm plate coupling resistor, and an 1,800-ohm cathode bias resistor, we get a gain of 14 with a 14,000-ohm effective plate resistance (Fig. 5). This information is obtained from the curves shown in Fig. 6. Assume we have set ourselves a minimum bass and treble boost of 14 db.

The treble boost is cut down, com-

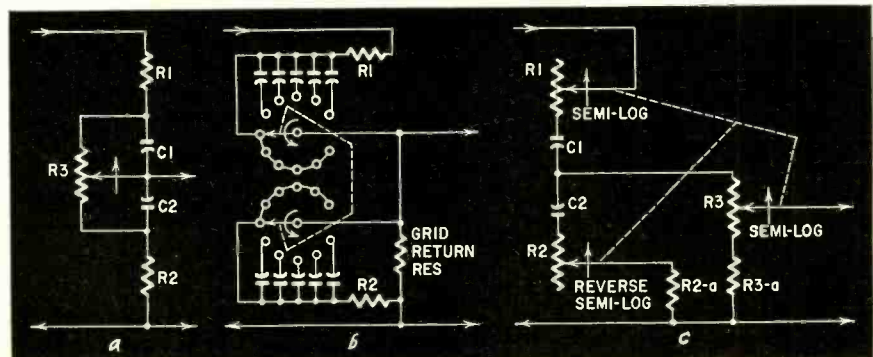


Fig. 4—Some basic circuits for low-frequency tone control: a—continuously variable, results in Fig. 3-a; b—fixed steps, results in Fig. 3-b; c—continuously variable combination of Fig. 3-a and Fig. 3-b, but can only approximate constant mid-band gain and requires three potentiometers.

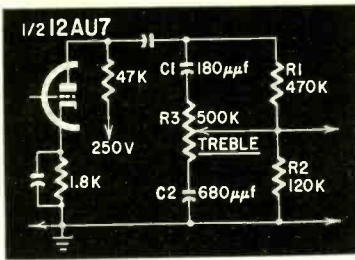


Fig. 5—First part of the design for a composite tone control, showing the values for high-frequency control.

pared with the theoretical value, by the source resistance. This means that the effective value of R2 (Fig. 5) for treble boost must include the source resistance, which consists of 14,000 ohms in parallel with 47,000 ohms, about 11,000 ohms. Assume we make R1 470,000 ohms. Then the combination of R2 with the source resistance must be one-fourth of this, or about 120,000 ohms. Deducting the source resistance means that R2 will be satisfactory at 100,000 ohms. But if we use a 500,000-ohm pot for the treble control (R3) it will be effectively in parallel with R2 at maximum boost, so the combination with the 500,000 ohms in parallel should be 100,000 ohms. Well, this brings us back to a value of 120,000 ohms for R2.

Assume that we decide to make the high-frequency turnover point, which will be 3 db up or down, according to whether we use boost or rolloff, at 2,000 cycles. Then C1 will need to have a reactance of 470,000 ohms at 2,000 cycles. A 180-µf capacitor is the nearest convenient value for this purpose. C2 should have 120,000 ohms of reactance at 2,000 cycles—680 µf serves well for this position. We have now designed in the values of Fig. 5 for the high-frequency boost and rolloff controls.

What we now need is some provision for low-frequency boost and rolloff (Fig. 7). For the main part of the response, the series resistance of the attenuation circuit consists of R1 plus the source resistance which adds up to 480,000 ohms, while the shunt resistance consists of just R2, which is 120,000 ohms. This produces a 5-to-1 attenuation as required. The boost will occur when R4's slider is at the top end.

To keep most of the full 14-db attenuation, R4 should be the highest value obtainable, because it will deteriorate the maximum boost. Suppose R4 is made 2 megohms. Then the minimum attenuation, at the extreme bottom end of the range, will be produced by 480,000 ohms in series and 2.12 megohms in shunt, which will give almost 2-db loss. This means that the ultimate boost will be 2 db short of the desired 14 db. If you use a 5-megohm pot, this loss will be reduced to less than 1 db. So from this point of view R4 should be the highest value obtainable.

Assuming we want the 3-db boost

point to appear at 500 cycles, C4 should have a reactance of 120,000 ohms at 500 cycles. This requires a .0025-µf capacitor. To get a rolloff of 3 db at the same point, C3 must be about 500,000 ohms at 500 cycles, for which a 620-µf capacitor will serve.

ear at the low-frequency end. A smaller difference in level makes a bigger difference in apparent loudness.

This procedure illustrates a typical design approach to a tone control for a preamplifier. Some prefer to use variations of combined control of fre-


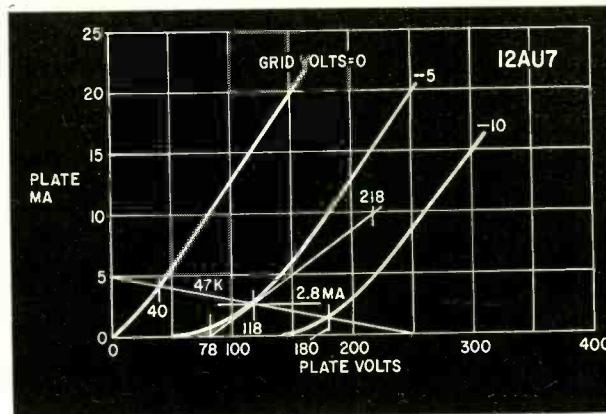


Fig. 6—Part of the curves for a 12AU7, to show the construction on which the figures in the text are based.

Fig. 7—The circuit of Fig. 5 extended to take care of low-frequency control. The values are calculated in the text.

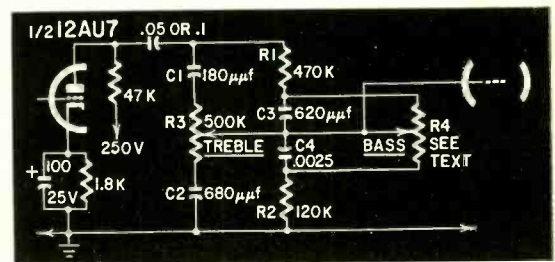

The complete schematic is shown in Fig. 7. It has to include the coupling capacitor, which should be in the region of .05 or 0.1 µf—this is not critical.

But there is another factor to consider—it may be wise to settle for a value lower than 5 megohms for R4, because when maximum bass boost is used, the grid return for the following stage is 5 megohms, but when minimum bass is used it is only 120,000 ohms. For this reason, it may be wise to settle for the lower amount of boost given by 1 or 2 megohms in this position.


This will not be as serious a loss as may be thought, because bass boost sounds much more effective than a corresponding amount of treble boost, due to the convergence of the sensitivity (Fletcher-Munson) curves of the

quency response in the forward amplifier and feedback response control. Theoretically, one could place the network of Fig. 7 in the feedback network and have the control working exactly in reverse—the ends that provide boost in the forward circuit would provide rolloff in the feedback circuit and vice versa.


But there are complications in trying to do this because of phase-shift problems if more than one stage is used. And if only one stage is used, the problem is getting workable resistance values that will not load the stage gain down.

The next step in tone controls is a study of the feedback types. As this is a rather more complex subject it will be treated in an article of its own at a later date.

TO BE CONTINUED

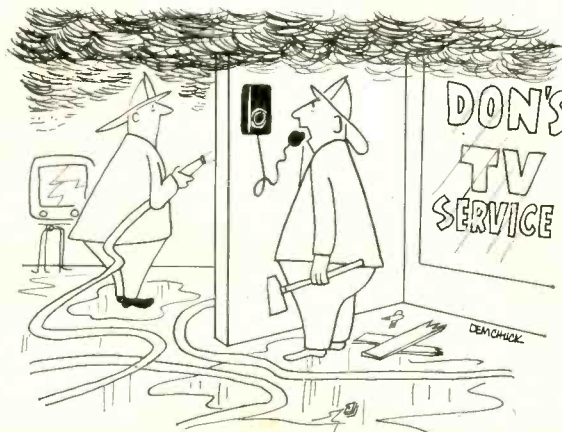

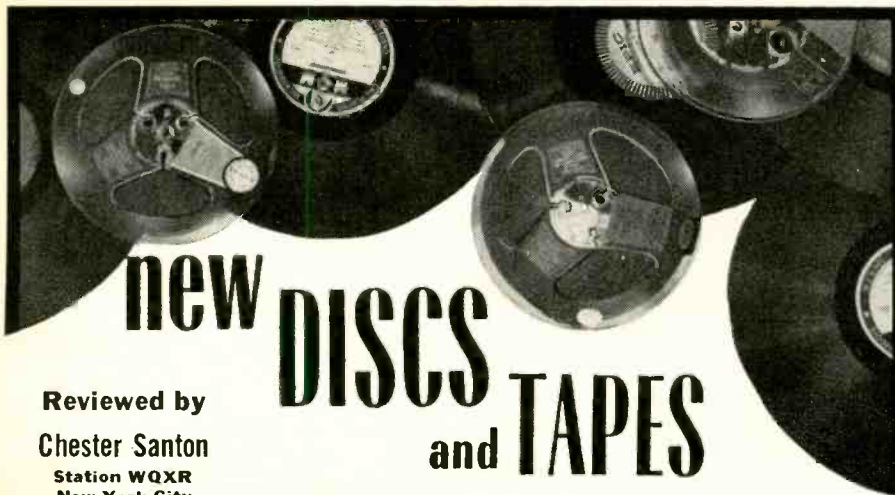"No, this isn't Don. Your set is smoking . . ."



# new DISCS and TAPES

Reviewed by  
**Chester Santon**  
Station WQXR  
New York City

STEREO and MONO

THE roster of companies releasing recorded tapes now boasts an interesting new entry. Material from the huge London Records catalog will now be available on four-track open-reel tapes. London thereby becomes the first influential record firm to throw its support behind the 7.5-ips quarter-track format. The audiophile should soon be able to find any popular recording he chooses in either the disc or tape stereo medium.

**High Spirits**  
Audiotape Special Offer (2-track, 7.5 ips)  
(7-inch; playing time, 28 min.)  
Technical Rating: EXCELLENT

The latest bonus reel issued by Audio Devices, Inc. is aimed at the three present forms of open-reel playback in the home. A 1-hour version of this recording is available on both dual-track mono and four-track stereo. This two-track stereo reel offers ½ hour of music. I tried the two-track stereo version first because their last promotional effort reviewed a few months ago was two-track. There is a perceptible improvement in the sound of *High Spirits* with a cleaner bite whenever the wave gets steep. Response is smoother throughout the frequency range. Following the example of the previous tape (*Blood and Thunder*), no attempt has been made to saturate the recording surface with a level of the highest-possible decibel count. Some outfits have been known to resort to this to mask the tape hiss that followed the use of inferior tape stock or carelessness in the dubbing process. The *High Spirits* theme of this collection comes from careful selection of music of an optimistic nature. A seldom-heard Johann Strauss march sets the mood. Then follows lilting music from the same composer's *Die Fledermaus*. The final movement of Beethoven's first (and lightest) symphony and sections of Tchaikovsky's *Capriccio Italian* and Bizet's *Suite from Carmen* take us to the reel's climax—the blazing *Rakoczy March* by Berlioz. The hour-long version of this recording retains the same first and last selections, but offers more extended samplings of the remaining works heard on this reel. I was surprised to discover that the four-track version stands up very well in the company of the two-track stereo. Signal-to-noise ratio is quite similar. The difference in background was spotted at only one area, soft passages in the Beethoven symphony. The noise level there was a shade higher than that on the two-track. Lows are about equal on both reels and the four-track has enough upward tilt at the high end to bring it in line with the two-track job. The familiar advantages of tape in locating the instruments is equally evident in each reel.

**Guitarra de Venezuela**  
Alirio Diaz, guitar  
Hi Fi Stereo Record R 812  
Technical Rating: ?

Two years after the introduction of the stereo disc, the problem of phase still awaits solution on some labels. This particular record sounds better with the stereo preamp phase-reversal switch in the position opposite to that used for normal, correctly phased stereo material. Some variables are present in playback, but in the

case of this solo guitar record most listeners will find their suspicions aroused when they first hear it on two channels that are in phase. On such a system, the guitar may appear to have a ludicrously wide source of sound. At any rate, I discovered that a flick of the phase-reversal switch into opposite position focused the sound to a reasonable area between speakers, improved the clarity and helped the lower register of the instrument. Only then was I ready to enjoy an excellent recital for classical guitar as played by Señor Diaz.

**HANDEL: Messiah**  
Sir Thomas Beecham conducting Soloists, Royal Philharmonic Orchestra and Chorus  
RCA Victor Stereo Records (4) LDS-6409  
Technical Rating: EXCELLENT

For many months RCA Victor has been preparing a special series of recordings under the supervision of Dario Soria, who established Angel Records in this country before joining RCA. The highlight of the first release in the Soria series is a new version of Handel's choral drama *Messiah* conducted by Sir Thomas Beecham. I haven't heard the other recent stereo versions of Handel's greatest oratorio, but this album is one of the most impressive recording jobs I've encountered in my years of listening. Anyone considering the purchase of this recording for playback on a good system is hereby warned that most choral stereo discs in his collection will sound either tinny or tame after this one. In his highly personalized treatment of the score, Beecham stresses the color and excitement in the sound of the orchestra. The depth and liveness of the stereo illusion lifted me out of my chair when chorus and orchestra reached the first full-volume moment in the intense dynamic range.

**TCHAIKOVSKY: Symphony No. 6 in B Minor**  
Vladimir Golschmann conducting Vienna State Opera Orchestra  
Vanguard Demonstration Stereo Disc SRV-1125D  
Technical Rating: EXCELLENT

In the past, Vanguard's Stereolab demo records have offered virtually all the technical re-



finements of their full-price line. No exception to the rule, this version of the Tchaikovsky sixth, priced at \$2.98, enjoys considerable advantage over earlier recordings of the *Pathétique*. The latest cutters are capable of cleaner sound, and stereo directionality is far more pronounced. Other orchestras may have more power in the way they play this score, but Vanguard has a whale of a record at an irresistible price.

**The Dukes at Carnegie Hall**  
Audio Fidelity Stereo Record AFSD-5918  
Technical Rating: GOOD

The Dukes of Dixieland chalk up their tenth release for Audio Fidelity on the stage of Carnegie Hall. This recording of the affair opens with an instrumental warmup on *Royal Garden Blues*. Then the audience in the hall has a chance to be heard. As each member of the band is introduced, he identifies himself with a few measures on his individual instrument while acknowledging the applause of the crowd. Although the Duke's familiar brand of Dixieland enjoys greater freedom on stage than it has under studio conditions, the job of the engineering staff was not made easier. Control of sound is adequate. In addition to reliables such as *Mush-rat Ramble* and *Sweet Georgia Brown*, the bill of fare highlights the trombone in *Slide Frog Slide* and *76 Trombones*.

**Giant Wurlitzer Pipe Organ, Vol. 6**  
Leon Berry  
Audio Fidelity Stereo Disc AFSD-5904  
Technical Rating: EXCELLENT

Here's another signpost of technical progress in the stereo disc. Leon Berry fans familiar with the ultra-close miking pickup used in his monophonic releases may be interested to learn that this technique has now been successfully transferred to dual-channel discs. The playing still has a lumbering style, but the sound is clean-cut. Most of the tunes are old standbys such as *Avalon*, *Moonlight and Roses* and *Darktown Strutter's Ball*.

**Swingin' Round the World**  
Jonah Jones Quartet  
Capitol Stereo Record ST-1237  
Technical Rating: EXCELLENT

With the audacious trumpet of Jonah Jones blazing the trail, the traveling is light in this musical tour of the globe. Muted or full, Jonah's horn takes his group into each country with nonchalant ease. The tunes, however, seldom depart from the Tin Pan Alley level.

**Take Me Along (Original Cast Recording)**  
RCA Victor Stereo Record LSO-1050  
Technical Rating: FAIR

This new Broadway musical based on Eugene O'Neill's play "Ah Wilderness" stars Jackie Gleason, Walter Pidgeon and Eileen Herlie. With the aid of Robert Merrill's music and lyrics, they translate into sound the starched-collar atmosphere of a small Connecticut town in the year 1906. Unfortunately, the acoustics jolt the listener into the present. Someone decided that the studio sound wasn't live enough to carry out the illusion of stage presence on a portable phonograph. The dosage of artificial reverberation introduced is too much for my equipment under normal playback curve. Much of the boominess, however, can be melted with sufficient rolloff in the bass end.

**Note: Following record is a 12-inch mono LP and plays back with RIAA curve.**  
**British Band Classics, Vol. 2**  
Frederick Fennell conducting Eastman Wind Ensemble  
Mercury MG 50197  
Technical Rating: EXCELLENT

Admirers of Mercury's first album of band classics from England are already aware of the foundation-shaking possibilities of this series. Vol. 2 will not disappoint them. In Walton's *Crown Imperial March*, the large pipe organ of the Eastman Theater lends its voice to the thunderous sonorities of winds and percussion. Gordon Jacob's setting of 16th century tunes by William Byrd, recorded for the first time, may prove a bit esoteric to some band enthusiasts, but this early music does lend a fresh flavor to Fennell's smart wind group. If your system loafers along at its full output, this one's a jimdandy to play. END

Name and address of any manufacturer of records mentioned in this column may be obtained by writing Records, RADIO-ELECTRONICS, 154 West 14 St., New York 11, N.Y.



the preset value or base speed. Actual motor speed is usually lower or higher than its base value so two-way operation is possible without reversing the motor.

Material is normally fed into the machine at a speed slightly higher than required. Then the proper rate of speed is set by selecting the base speed of the motor so it reduces overfeed until the material and the cutter are in register.

The system corrects continuously for any deviation in position between the material and the cutter by either increasing or decreasing motor speed from its base value, thus feeding the material slower or faster to keep it and the cutter synchronized.

The selector switch, which is geared to the cutter, produces a signal which indicates the cutter's position. This switch contains two phototubes, an amplifier tube and a light-source lamp. A disk that rotates inside the selector switch contains six pairs of slots. These slots permit light to strike the phototubes as they pass in front of them. This produces the cutter-position signals (leading and lagging), which are amplified and sent to the control panel. The control will operate for web speeds of 20 to 750 feet per minute and with one to six register marks per cut.

While the control can detect errors as small as .005 inch, the accuracy of the cut depends upon such other factors

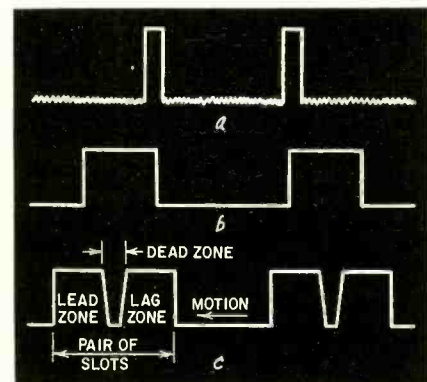


Fig. 4—Waveforms from: a—web scanner; b—selector switch leading or lagging zones; c—selector switch.

as register-mark spacing, backlash in the gearing, loose couplings, tension control of the web, etc. With an average machine, accuracies of  $\pm 1/32$  inch are expected, provided the register marks are equally spaced and web tension is reasonably controlled. With an exceptionally good machine and close control over the other variables, accuracies of  $\pm 1/64$  inch can be obtained.

**Register-mark scanner**

This unit looks at the register marks printed on the material. The phototube observes the material as it passes a focused spot of light. When a mark passes the light spot, a change of intensity is noted by the phototube, then amplified and sent to the main panel. In this way the position of the material is noted. The scanner operates on either light increase (light mark on dark back-

ground) or light decrease (dark mark on light background) simply by setting a toggle switch on the scanner. The output waveform is shown in Fig. 4-a.

**Selector switch**

The position of the knife or other device working on the material is registered by the selector switch. Two signals are developed: one before the knife cuts (leading zone), and one after the knife cuts (trailing zone). This is done by gearing the unit to the knife so a slotted disk inside the unit revolves with the cutter. On one side of the disk are two phototubes. On the other side is a light source. The slots are arranged so light strikes first one and then the other phototube, thus creating two signals which are amplified and sent to the control panel. An adjustment inside the unit allows the two zones to overlap (light falls on the trailing phototube before leaving the leading phototube) or to have a dead zone (light falls on neither phototube).

Selector waveforms are shown in Fig. 4-b as the signal from either the leading or lagging zone. Fig. 4-c shows selector waveforms and indicates the lead and lag zones.

**Register mark indicator**

Going back to the schematic, V2, a 6E5 indicator, mounted at the top of the panel, indicates incoming register-mark signals. By observing V2, one can see when a register mark is detected by the sudden widening of the shaded area.

**Dc bridge**

A network of resistors placed between the positive and negative dc buses supplies various voltages necessary for the operation of the panel. These voltages are adjusted by setting slides on the resistors.

**Discriminator**

In this circuit the positions of the knife and paper are compared. V3 and V4 have two controlling grids; one takes its signal from the register-mark scanner and the other receives its signal from the selector switch. Two tubes are required because there are two selector switch signals, one for the leading zone and one for the trailing zone. The two grids in each tube are normally operated so that no current flows unless a positive signal appears on both grids at once. When the material is in register, both discriminator tubes produce signals or both remain cut off, depending on the adjustment of the dead zone in the selector switch. When the material is out of register, only one tube produces a signal.

**Error detection**

This stage detects the difference between the precise setting of the cutter knife and the position of the register marks.

**Motor control**

The normal running speed of the correction motor for a particular machine speed is controlled by the base-speed potentiometer. If the material is in register, correction-motor speed is nor-

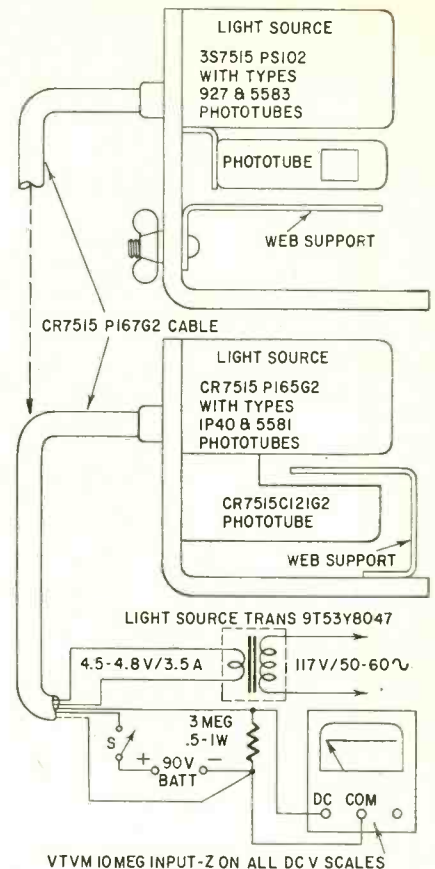


Fig. 5—Register sample tester.

mal. However, if there is an error, the correction motor runs either faster or slower, depending on the signal coming from the stability network.

Current through the generator field is regulated. When in register, current is at a value determined by the base speed setting. When an error is detected, field current is varied to correct motor speed. There are advance and retard pushbuttons for changing register while the machine is running.

**Servicing techniques**

**Cutoff register controls**

A sample tester, shown in Fig. 5, tests samples of register marks on a


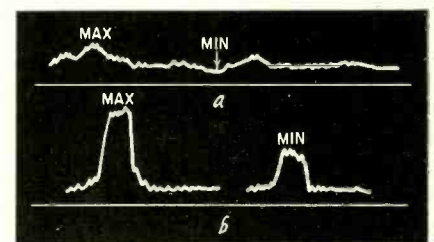


Fig. 6—Characteristics of web (a) and register-mark (b) variations. Register marks must have at least 20 times the amplitude of web variations.

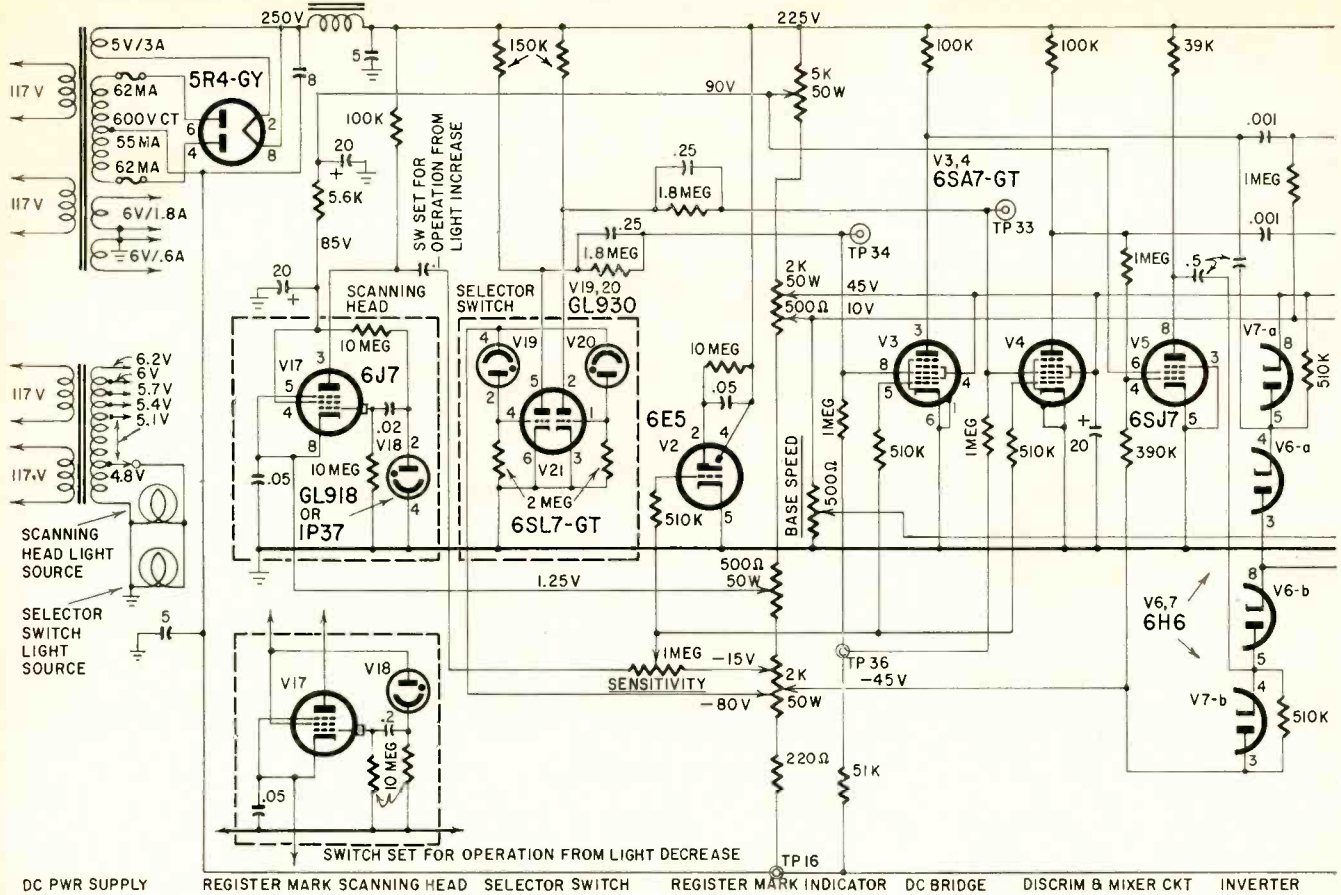web to determine the output signals from the motor control. Two register controls are shown. The samples are set up so that the operating conditions are as close to actual use as possible. A light-source transformer with a 4.5- to 4.8-volt output is required.



A 3-megohm load, a 90-volt dc source and a vtvm or an oscilloscope are used for testing. When the web is moved so light passes over the register mark, a signal voltage change of at least 0.5 volt is needed to assure normal operation of the controls.

A second important characteristic is shown in Fig. 6. Two conditions are shown, the variations in the web material as in Fig 6-a and the variations in register marks as in Fig. 6-b. In this example a positive signal is shown from the register mark. There are wide variations in some web materials. Both extremes, maximum and minimum, are shown for the web alone and the register marks. For best operation the register-mark minimum should be at least 20 times greater than maximum web variation.

**Maintenance**

A check of all tubes, except the neon tubes and the phototubes, is desirable whenever the control is serviced. A standard tube checker will do, although it does not guarantee that the tube will work satisfactorily. Some tube difficulties cannot be detected on a standard checker. Keep a full complement of spare tubes on hand at all times and if any tube is questionable, replace it! The tubes and their corresponding sockets should be marked as the tubes must be replaced in the same sockets after checking to insure proper operation. The phototubes have a long life and should not cause trouble

unless they are mechanically damaged.

The lenses in the scanning head, its light source and selector switch must be cleaned regularly to maintain reliable operation. The scanning head and the exterior light-source lens must be replaced with the flat side toward the material. The inner light-source lens must be replaced with the flat side toward the lamp.

The rest of the components need no attention unless mechanically damaged. For this reason the unit should be mounted where it is protected against damage from passing vehicles, etc.

**Servicing**

When trouble crops up, its approximate location and nature can often be determined by the circumstances under which it began. In cases where this approach fails, observational checks should isolate the trouble to a particular section of the control. When the difficulty is isolated, a routine check of circuits and components will indicate the fault.

When troubleshooting, first make sure that the panel is receiving power. This may be checked readily by observing the indicating-eye tube (for green color) and the scanning head and selector switch lamps (for light). If the lamps are lit but the indicating-eye tube is out, check the small panel fuses. If all of these indications are negative, the incoming power lines, including fuses and switches, should be checked. If the lamp in either light source is

out but the panel above is getting power, the lamp is burned out and must be replaced.

If the neon tubes flash but the generator field current does not kick, check the detector diode tubes and replace them if necessary. When the diodes are not defective but there is still no generator field current change, check the components in the stabilizing circuit.

Signals from the selector switch may be checked with either a vtvm or an oscilloscope. A 20,000-ohms-per-volt voltmeter will also give a satisfactory check.


When light falls on phototube V19, a voltmeter connected at TP34 should change from about -30 to +10 volts. This also holds true for V20 and TP33.

It is important that these potentials be as indicated. If this change is not indicated, the amplifier in the selector switch may be bad.

If both tests are positive, place a jumper between the test point and ground and rotate the selector switch by hand. This gives the effect of a continuous register-mark signal. As the disk in the selector switch rotates, first one and then the other neon tube should flash and the generator field-current meter should kick first in one direction and then in the other, but its average value should not change appreciably from its base-speed value.

When the control seems to hold register but does not hold it accurately, check the dead-zone adjustment on the selector switch.

If faulty operation has been traced

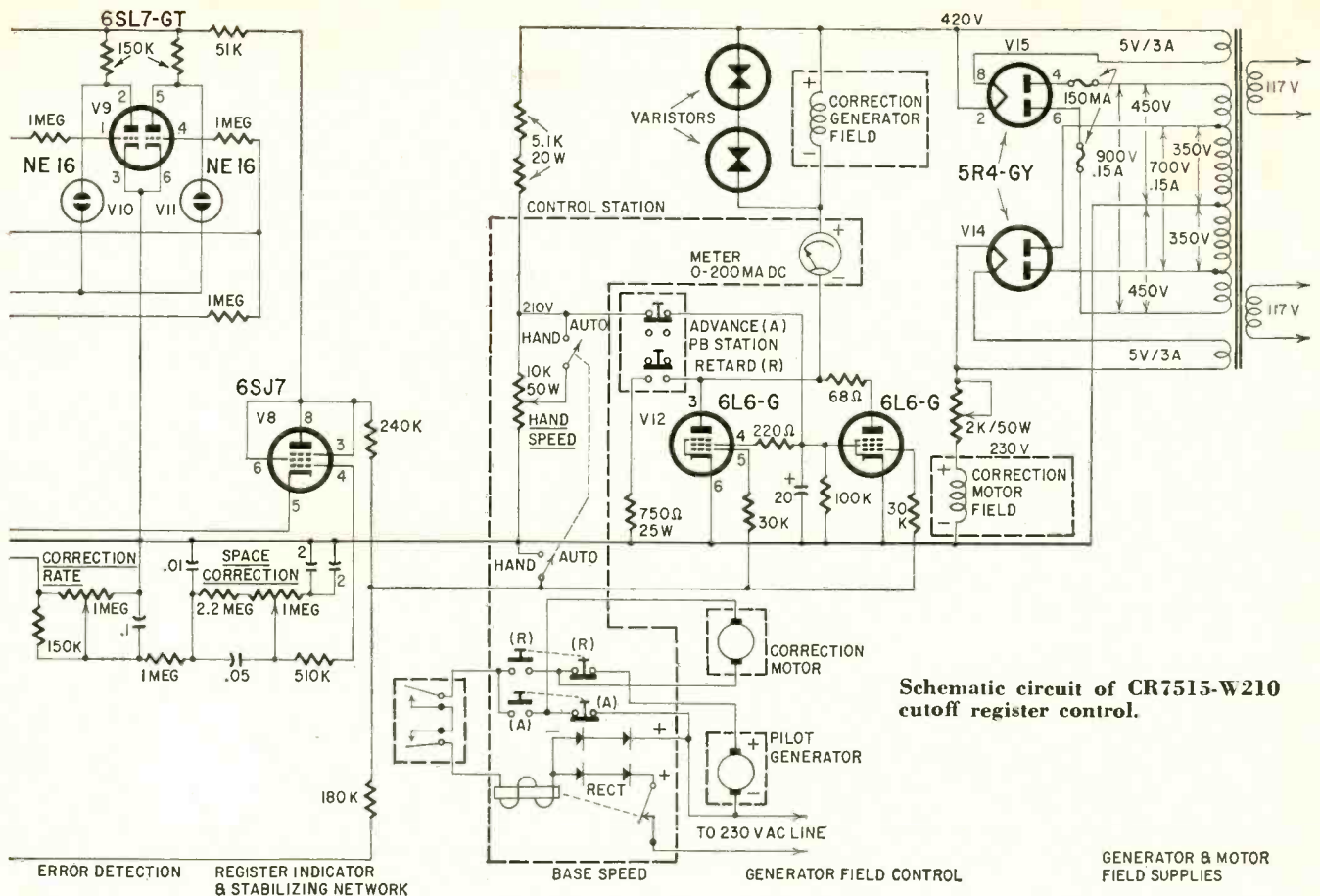

Schematic circuit of CR7515-W210 cutoff register control.

to the control, voltages should be checked. A vtvm or a 20,000-ohms-per-volt voltmeter should be used and all measurements made between ground and the point listed, with the common lead being connected to ground. These readings should be made with the machine stopped.

At times it is desirable to run the machine when trouble has been traced to the control. If the machine will not be damaged by being run without material, functions of the control can be observed and checked under these simulated operating conditions.

An oscilloscope simplifies troubleshooting, since the signals from the scanner and selector switch may be followed through the control and the exact spot where these signals are lost can be located.

With an understanding of how the circuit works the trouble may be located readily with an oscilloscope, if it is electrical and not mechanical. With or without an oscilloscope, however, there is no substitute for a thorough understanding of the circuit when troubleshooting.

**General**

Signals seen on a scope will vary, depending upon the differences in the web material and the register marks. The characteristics of each web material and the register marks must be determined for proper servicing. Fig 7, for example, shows several signal levels


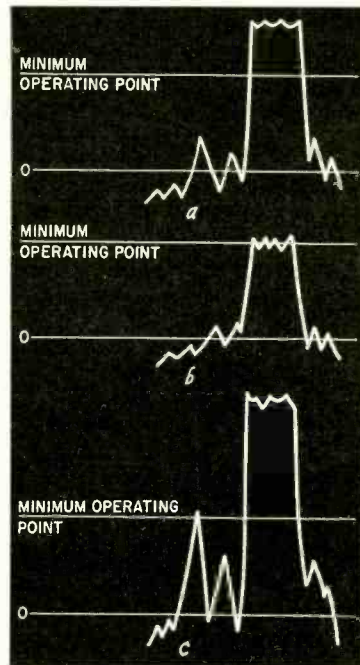


Fig. 7—Effect of signal-level adjustment on register-mark signal: a—correct setting; b—too low; c—too high.

Fig. 8—Pulse formed as register mark passes by (a) increased light falling on phototube; (b) decreased light falling on phototube.

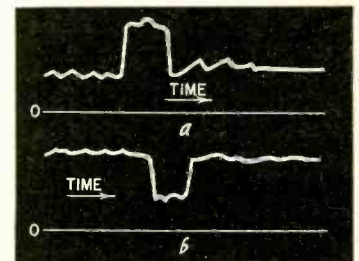


improper operation. Only the condition shown in Fig. 7-a is desirable.

Both negative and positive pulses are possible, depending upon the type of phototube circuit and the number of amplifiers. In Fig. 8 a pulse for light increase is shown in Fig. 8-a and for light decrease in Fig. 8-b.

The following list of servicing checks is suggested as a way to prevent trouble.

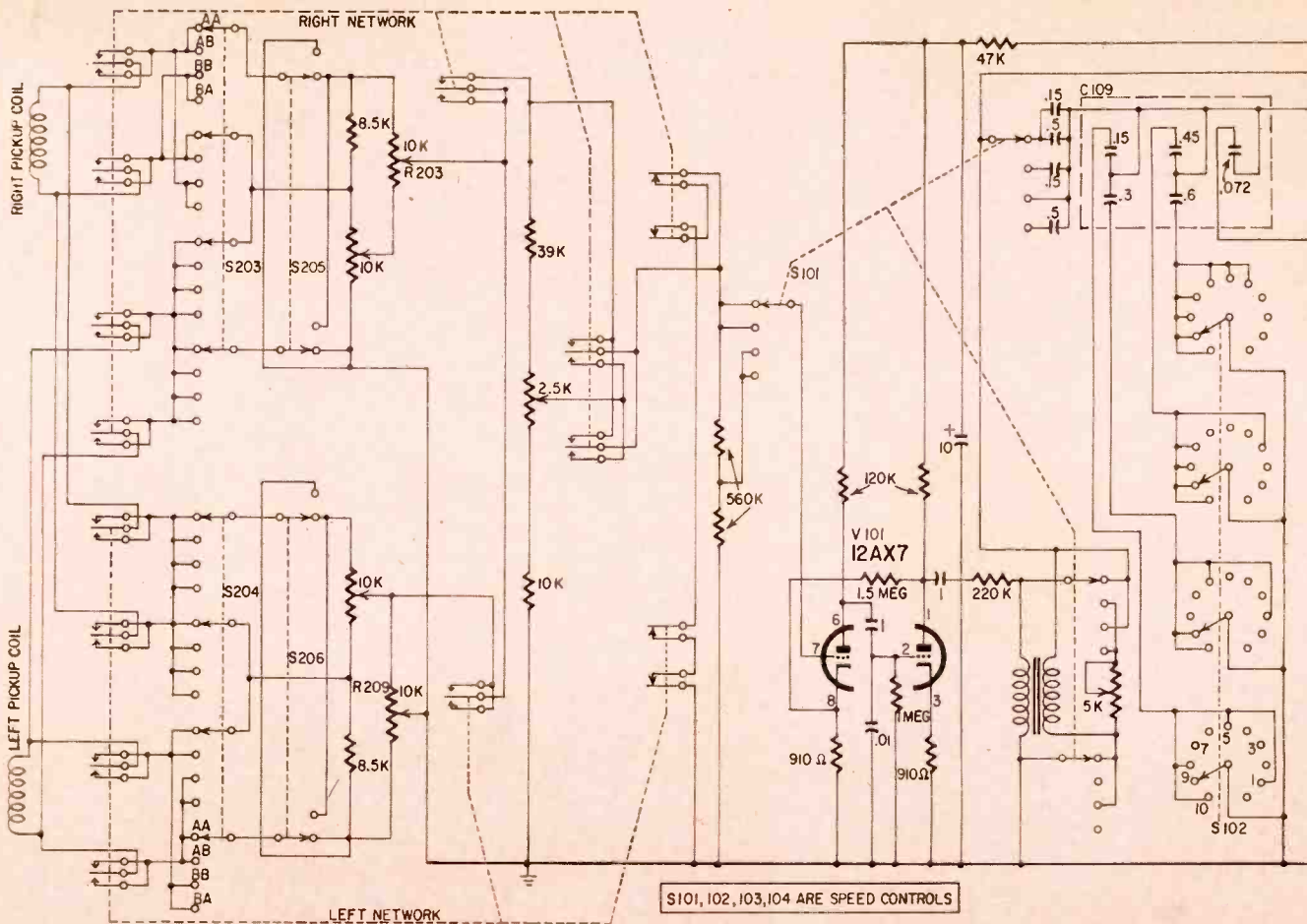1. Check light source for bright, steady light. Lenses must be clean.
  2. Check alignment and focus of scanner. Direct interference from other light sources should be kept from the phototube and the register marks.
  3. Check signal amplitude and variation.
  4. Check line-voltage variations and common grounding.
- END



# ELECTRONIC BALANCING for BETTER MOTORS

*Balance the rotor of a fractional-horsepower motor and you increase efficiency, and reduce wear and vibration. One way to do this is with an electronic dynamic balancer*

By J. W. ESSEX\*

**S**MALL electric motors are in constant use wherever you turn—phonographs, drills, saws, typewriters and mixers. The heart of these fractional horsepower motors is the rotor, which turns at speeds as high as 3,400 rpm. If the rotor is balanced, there are no problems; if it isn't, the motor will be noisy and vibrate. It will also wear excessively and be inefficient. Such vibration can even make a motor shake itself to pieces—holding nuts work loose, tie rods fall out and the whole works comes apart.

How are rotors balanced? The old method called for taking the completed rotor and placing it on a set of two steel rails. If unbalanced it would roll along the track until the heavier weight of one side would bring it to rest. Then the operator would remove the rotor and place it in a drill press. After drilling out some of the mass from the heavy side, the rotor would go back to the rails for another check, and so on until it was balanced properly.


The process works well, but is too slow. Using this method, two men could run off only 150 rotors a day, far short of a desired target of 700 a day. Also, static balancing does not reveal dynamic unbalance caused by two equal weights at equal distance from the rotational axis and located on opposite ends of the rotating part (Fig. 1).

## Electronic balancing

The solution to the problem came in the form of an electronic balancing machine. It has proved itself by turning out more, better-balanced rotors per day. The result is

\*Former inspector, quality control, Small Motor Div., Canadian Westinghouse, Hamilton, Canada.

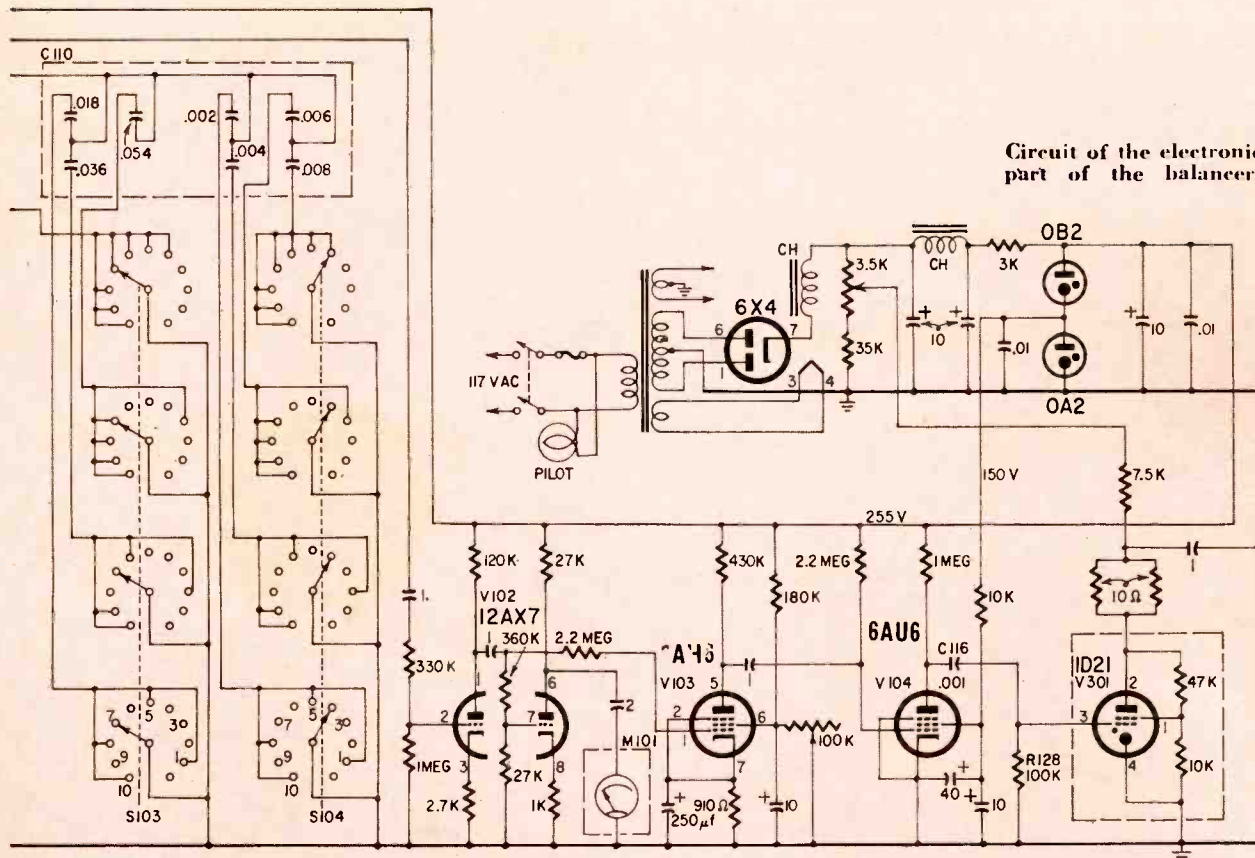Circuit of the electronic part of the balancer.



higher quality at lower cost, a survival prerequisite in this mechanical age.

The time-consuming part of rotor balancing is in finding the unbalance point and the amount of mass that must be removed to balance the rotor. Here's how this problem is handled by the Gisholt Dynetric balancer, a machine with which the author is familiar.

The rotor to be balanced is placed on the Dynetric balancer as shown in Fig. 2. A numbered reference ring is attached around the rotor and a belt drive placed around the center of the rotor. When the balancer is turned on, the rotor is spun at about 800 rpm. If it is unbalanced, it will vibrate in its cradle, move a couple of coils in a magnetic field, producing a sine-wave output. The output is amplified and shaped to produce pulses that fire a strobe light. The vibrations appear at the same time during each revolution, so the light flashes at the same time each revolution. The operator notes the reference number that appears in the strobe light over the reference pointer. This identifies the off-balance point. The meter tells the operator how much weight must be taken off or added. (The more common practice is to drill out the necessary material.) After this is done, another check is made and if the rotor passes, the job is done.

#### Balance a rotor

Now let's take a closer look at the electronics side of the operation. How is the vibration picked up and changed to a pulse that triggers the strobe light?

A rotor to be balanced is placed in a cradle (Fig. 3) that

consists of two supports attached to coils which move in strong magnetic fields. The more the coils move in the magnetic fields the greater their voltage output. The coils' outputs are fed to a common meter which indicates a voltage when either end of the rotor moves up and down.

When the rotor is unbalanced, represented by weight  $W$  on the right side, and is rotated, it vibrates between lines  $Y$ - $Y$  and  $Z$ - $Z$ . As the right side swings more than the left side, the voltage induced in coil  $A$  is greater than that in coil  $B$ . The coils are arranged so the voltages fed to the meter buck each other and the meter reads only the difference.

By adjusting coil  $A$ 's output with the potentiometer, the meter can be zeroed. In this way the effect of weight  $W$  in the right plane is balanced out. If a weight is placed on the left end of the rotor, the meter would measure the unbalance in the left plane. This is how the two planes of the rotor are separated for balancing.

In use, the pickup vibrations are followed by somewhat complicated networks and level or volume controls. They can be seen in the main diagram at the head of this article, the complete electronic circuit of the Gisholt balancer.

Of course, the weak vibrations set up by the rotor must be amplified before they can be used, and this is where electronics comes in. The amplifier uses four tubes (in addition to the strobotron, rectifier and voltage regulators) to provide amplification in the order of 1,600,000 times. The output from the coils is fed to a 12AX7 (V101) for impedance matching and early amplification. The signal then goes to V102, another 12AX7 used as a resistance-coupled ampli-

## INDUSTRIAL ELECTRONICS

fier to drive meter M101, which indicates the amount of unbalance. The filter network between V101 and V102 cuts down extraneous vibrations which could cause false readings. They are tuned filters that eliminate all vibrations except at the frequency at which the rotor is turning (usually 800 cycles). To trigger the 1D21 strobo-

tron two additional amplifiers are used. (The signal amplitude that triggers the strobe light is 15 times greater than that fed to the meter.) These pentodes (6AH6 and 6AU6) square the pickup voltage before they are differentiated by C116 and R128 and fed to the strobe tube.

The gas-filled strobe tube flashes

each time a pulse reaches its grid. The flashing light makes the rotor appear to stand still, and the numbered reference ring identifies the spot. The same lamp, reference pointer and numbered ring are used in locating the point of correction in each of the two correction planes.

At these points a small amount of mass is drilled out. The necessary amount is shown on a chart that lists the size of the drill bit and depth to use.

### Set up the balancer

The balancer is only as good as the man setting it up. The trick is to get a good minimum in each plane, using a test rotor and adding modeling clay to each side in turn. This gives a zero standard to set the machine for. It also insures that any unbalance in the right plane will not affect unbalance in the left plane and vice versa.

Let's run through a sample setup to show how this is done. First we want to balance out any unbalance in the right plane in relation to the left plane. To do this we place a rotor in the cradle and add weight in the form of modeling clay in the right plane. The control box left/right switches are set for the left plane. The rotor is set spinning and a reading is taken from the meter, which is set for coarse measurements. Once it is taken, a small amount of clay is added and the rotor is spun once again. If this causes an increase in the meter reading, reverse the input switch before continuing. As the operator proceeds, adjusting controls as he goes along, the meter reading drops each time clay is added. As the readings get low, the operator switches to the fine reading and continues adding clay and rechecking. When readings get low once again, the operator keeps adding clay and checks the settings of switches S204 and S206 and potentiometer R209 (only one combination of these controls will give a zero reading). This continues until a zero reading is obtained. Now that the left side is balanced the operator sets the left/right switch to right and repeats the process, this time adding clay to the left side of the rotor. When doing final balancing on this side, switches S203, S205 and potentiometer R203 are adjusted.

Once established, settings are recorded so that for successive rotors of the same type approximate settings can be made without all the preliminaries given here. In our plant we eventually got a list of figures for all the rotors we make. It simplifies the job considerably when switching from one rotor to another.

Now the angle/amount switch is set to angle and the strobe light flashes, indicating the point of the unbalance. In this way electronics gives us a machine that makes low-cost, high-quality fractional-horsepower motors possible.

END

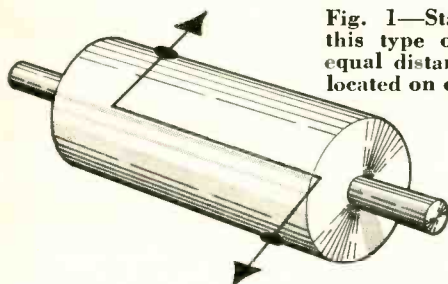


Fig. 1—Static balancing will not disclose this type of misbalance—equal weights at equal distance from the rotational axis and located on opposite ends of the rotating part.

Fig. 2—Gisholt Dynetric balancer in operation.


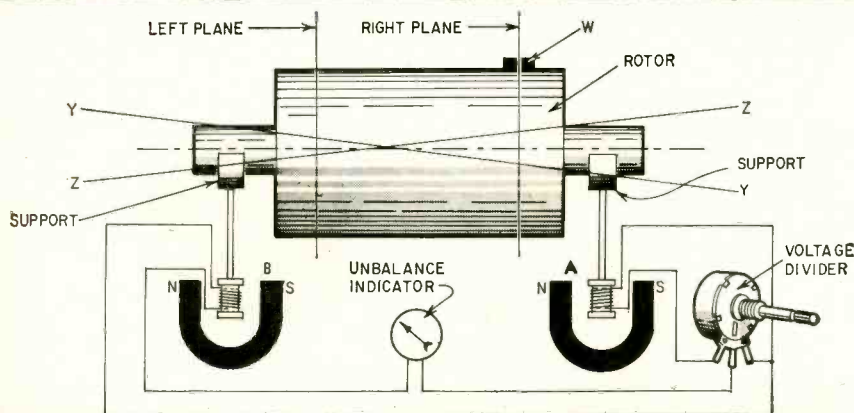
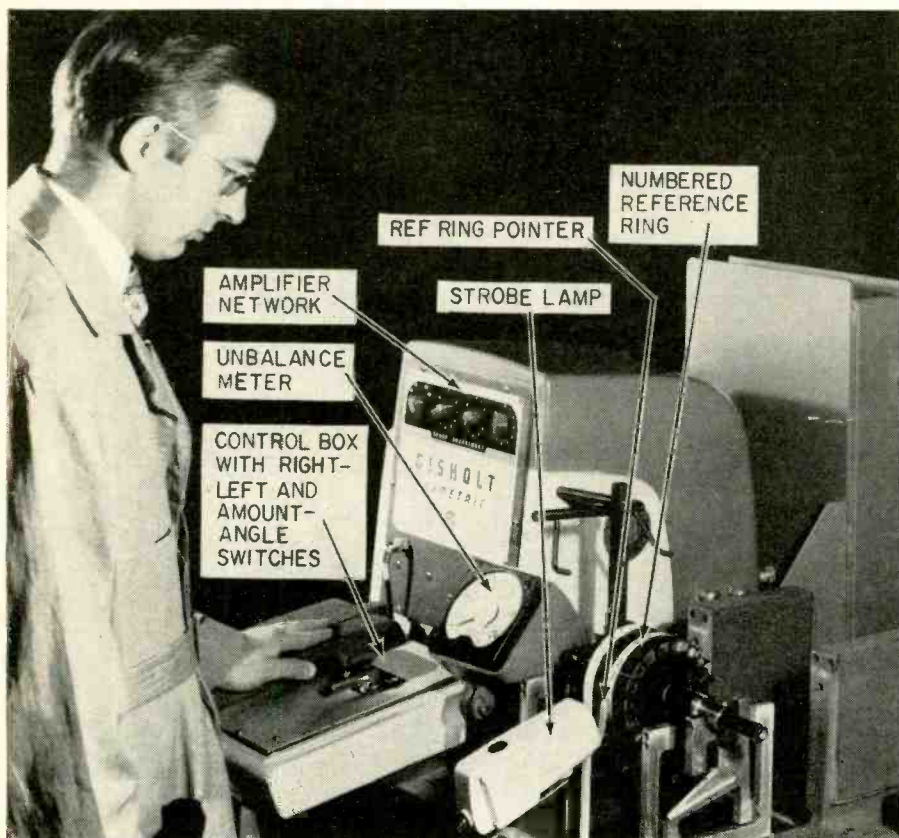


Fig. 3—How rotor vibration is transformed into an electronic signal.


what's

new


?

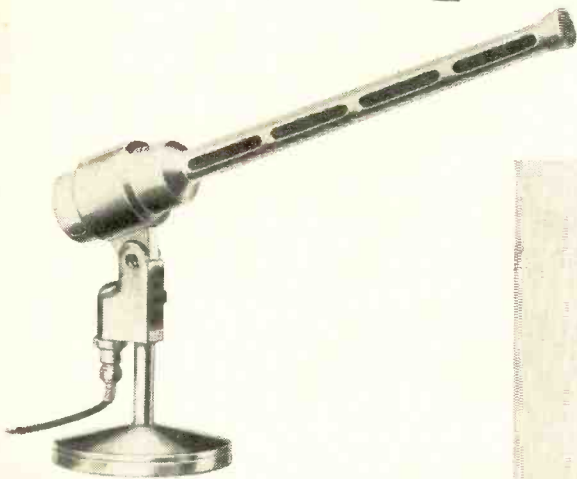

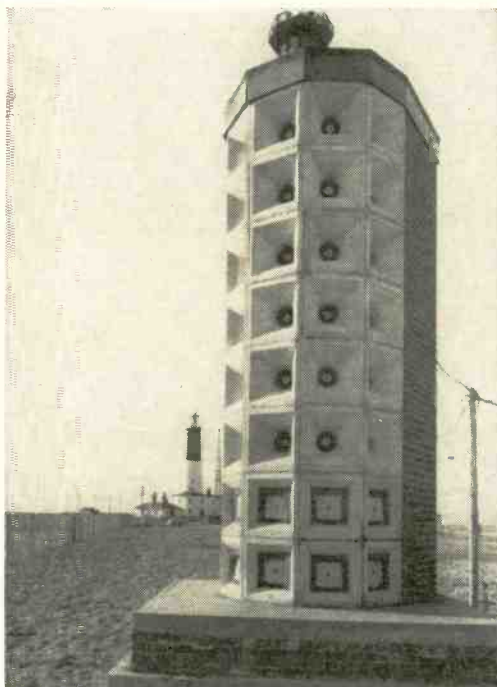
**MICROPHONE** maintains proper response three times normal distance from the sound source, cancels noise from rear and sides. Known as the Electro-Voice 644 Sound Spot, it uses a cardioid unit and the interesting distributed front opening shown to accept sound 45° each side of center, reduce sound from unwanted directions more than 20 db. Response: 40-12,000 cycles.



**LOUDSPEAKING LIGHTHOUSE** at Dungeness, Kent, England, will have 60 big cone speakers, beaming 3 kw of audio out to sea, in place of the old-fashioned foghorn. The stack of speakers, set up for testing in the photo, will be mounted in the upper portion of the lighthouse. An automatic photocell fog detector will turn the horn on when needed. (More information on the lighthouse was printed in **RADIO-ELECTRONICS**, December, 1959, on page 16.)

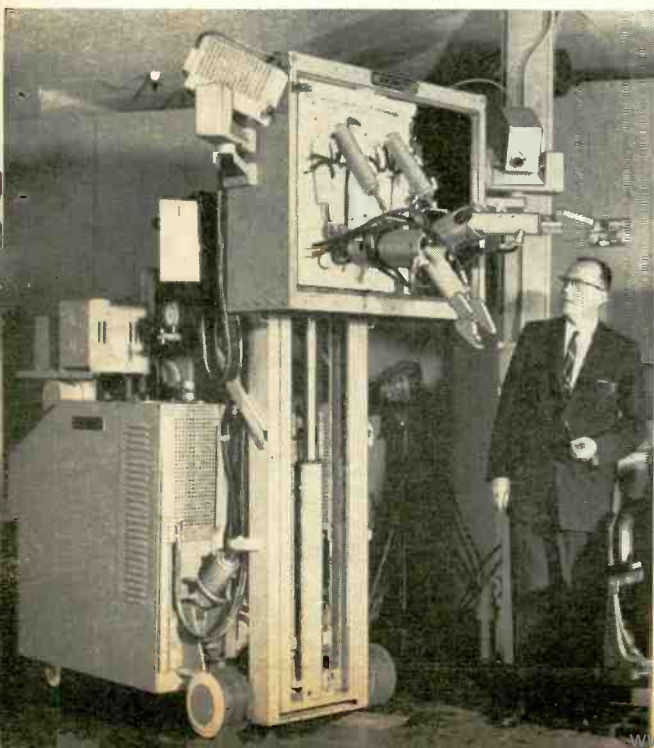

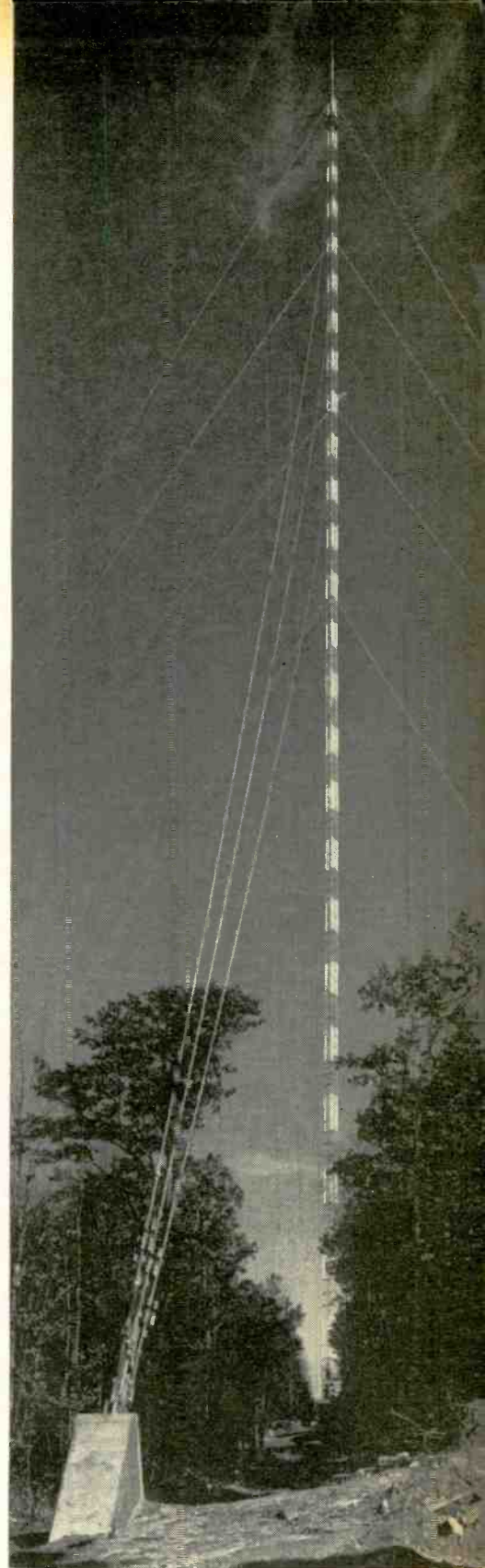**MOBOT MARK I**, mobile replacement for man in dangerous areas, is completely remote-controlled. Lifts, moves, places, takes apart units up to 1,500 lb. Hears all, sees all, uses wrenches, screwdrivers, hammers, shears. Operating range limited to 200 feet by length of control cable. Hughes Aircraft developed Mobot for AEC contractor Sandia Corp.



**TALLEST STRUCTURE** ever erected by man is the tower of station WGAN-TV, Portland, Me. A third of a mile high (1,619 feet), almost twice the height of the Eiffel Tower, 154 feet more than Empire State Building, the tower sways up to 6 feet in high winds, can stand 150-mile-per-hour gales. Built by Kline Iron & Steel, Columbia, S. C.

# SERVICING CHROMA DEMODULATORS

*Do the people on the color TV screen have blue faces? If they do, this article may help you locate the trouble*

**By ROBERT G. MIDDLETON**  
RADIO-ELECTRONICS TELEVISION CONSULTANT


COLOR pictures are incorrectly reproduced when something goes wrong in the chroma demodulator (chroma detector) circuits. Several types of chroma demodulator circuits are used in modern color TV receivers. These are: (R - Y)(B - Y) circuits; (R - Y)(G - Y) circuits; bootstrap circuit; XZ circuit.

Formerly, the IQ demodulator circuit was extensively used. An (R - Y)Q circuit was used prior to the XZ circuit.

Some types of servicing procedures are the same for all chroma demodulator systems. Other servicing methods differ for each type of circuit.



We will consider these in order. The basic plan of the (R - Y)(B - Y) system is shown in Fig. 1. Some receivers use diode demodulators, as in Fig. 2. Let us review the servicing procedures for this configuration.

A preliminary test for demodulator trouble can be made with a vtvm, as

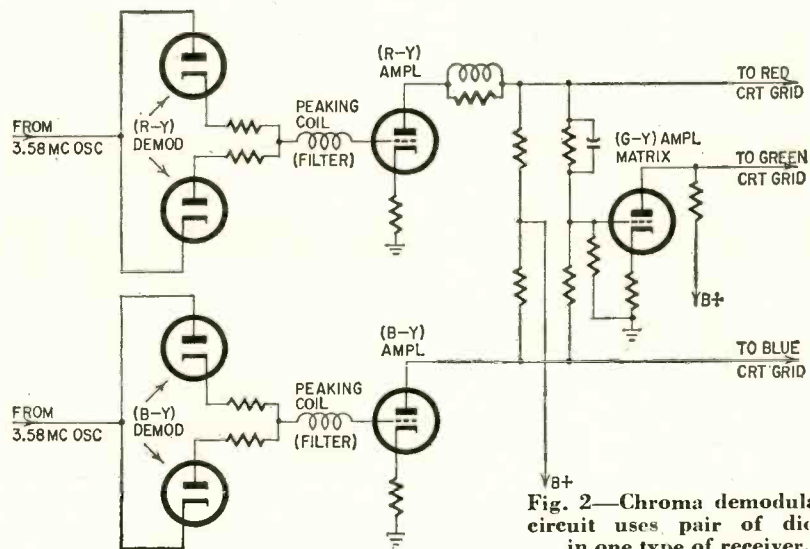

**Fig. 2—Chroma demodulator circuit uses pair of diodes in one type of receiver.**

**Fig. 1—Basic plan of the (R - Y)(B - Y) chroma demodulator system.**

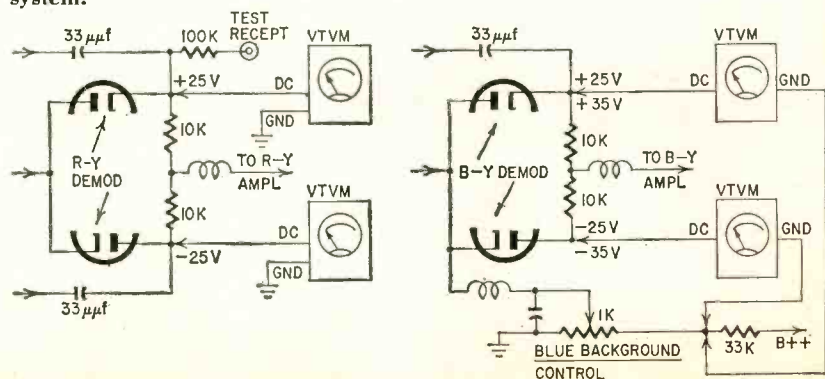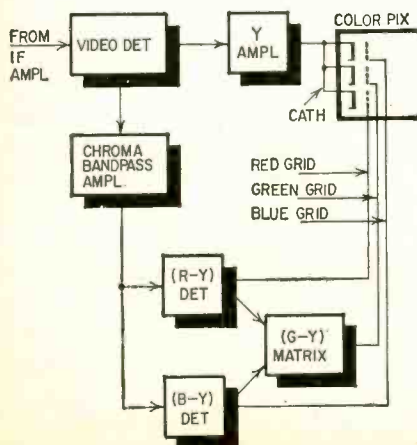

**Fig. 3—Vtvm tests of diode-type (R - Y)(B - Y) chroma demodulators.**



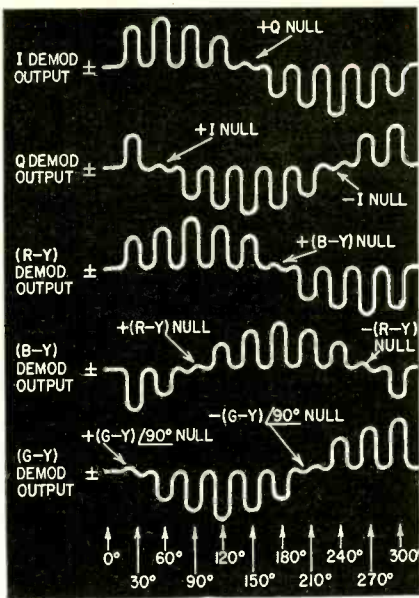


Fig. 4—Correct null points for chroma demodulators, using a keyed rainbow test signal.

in Fig. 3. No signal input is applied to the receiver. Equal values of dc voltages must be found at the test points indicated. Note the 1,000-ohm pot in the B - Y demodulator circuit. This is a blue-background control. The exact voltage measured at a B - Y demodulator test point will vary, depending on this control's setting. Nevertheless, equal values are found at the two B - Y test points if the circuit is operating properly. Note that a positive voltage appears at one tube, and a negative voltage at the other.

The voltage measured with the vtvm comes from the subcarrier oscillator. If it is weak, look for trouble in the subcarrier oscillator circuit. If it is unbalanced, look for faulty resistors in the demodulator circuit.

Chroma demodulators normally measure from 25 to 35 dc volts in this type of test. In this circuit, it is important to have adequate subcarrier voltage.

Another useful test can be made with a keyed rainbow signal. If such a signal is applied to the receiver and a scope is connected at a chroma demodulator output, patterns like those shown in Fig. 4 are seen. The output must go to zero (null) on certain "pips." Fig. 4 shows the required nulls for I, Q, R - Y, B - Y, and G - Y demodulators.

If you don't get the required null, try adjusting the color phasing control. If it is out of range, adjust the master color phasing control. This is a capacitor or a slug-tuned coil in the burst amplifier section, and can be located from the receiver's service data.

Having obtained a correct null from the R - Y demodulator, check the B - Y demodulator next. If the B - Y null is incorrect, try adjusting the quadrature transformer. The quadrature transformer is located between the subcarrier oscillator and the chroma demodulators.

It is usually possible to get correct nulls on both the R - Y and B - Y demodulators by adjusting the quadrature transformer. However, if you cannot get correct nulls from both demodulators, there is a fault in the demodulator circuits, or the quadrature transformer is defective.

The easiest way to adjust the quadrature transformer is to connect the output from the R - Y demodulator to the scope's vertical input terminals, and output from the B - Y demodulator to the scope's horizontal input terminals. A circular pattern on the scope screen, as illustrated in Fig. 5, indicates correct adjustment.

You will note a wedge-shaped sector in the circular pattern. This is caused by the burst blanking action. The wedge revolves around the circle as you adjust the color phasing control.

The wedge also revolves when you adjust the slugs in the quadrature

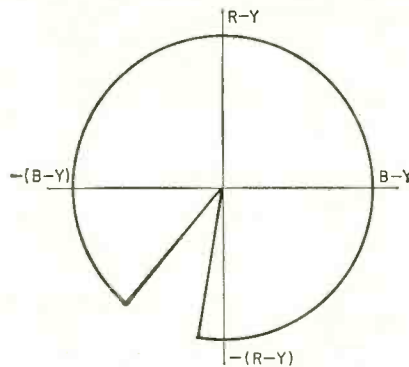


Fig. 5—When the quadrature transformer is properly adjusted we can get a circular pattern on the scope screen. Otherwise we can only get a tilted ellipse.

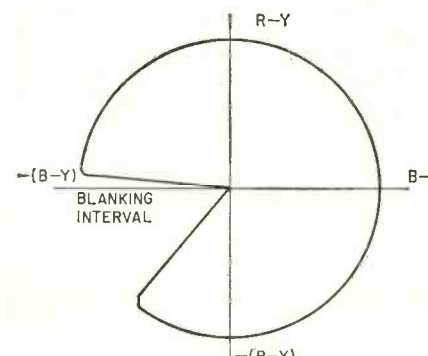


Fig. 6—Normal wedge position for (R - Y) (B - Y) chroma demodulators.

transformer. The normal position for the wedge depends on the type of demodulator system. The correct position for the (R - Y) (B - Y) system is shown in Fig. 6.

We set the color phasing control to the mid-point of its range, and then adjust the quadrature transformer to make the wedge appear as in Fig. 6. Otherwise, the control will be off range when we check for the nulls in Fig. 4.

Perhaps you prefer to use the NTSC type of generator in making demodulator tests. These generators have indi-

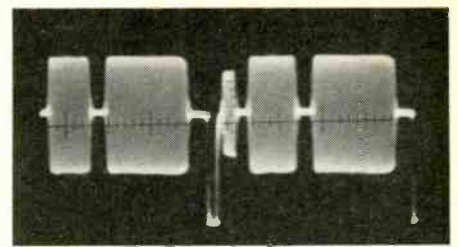


Fig. 7—A display of an R - Y bar and a B - Y bar from a color bar generator as seen on the screen of a wide-band scope. The difference between the two signals cannot be seen in this type of pattern, since they differ in phase only.

vidual R - Y and B - Y test signals. They appear on a wide-band scope screen as in Fig. 7. The R - Y bar is narrower than the B - Y bar. This provides bar identification in the signal-tracing tests described later.

When this type of test signal is used, proper operation of the R - Y and B - Y demodulators gives patterns like those in Fig. 8. A scope connected at the R - Y demodulator output shows a square wave on the R - Y signal, but a null on the B - Y signal. Likewise, at the B - Y demodulator output, a square wave is obtained on the B - Y signal, but a null on the R - Y signal.

If we use a 100% saturated NTSC color bar test signal, we observe crankshaft patterns at the chroma demodulator outputs. Patterns for correct operation of the R - Y and B - Y demodulators, as well as the Y channel, are shown in Fig. 9.

Pentode chroma demodulators

Quite a few (R - Y) (B - Y) chroma demodulators use pentode tubes, instead of duo-diodes. A typical pentode demodulator is shown in Fig. 10. The chroma signal is applied to the control grid. The subcarrier oscillator signal is applied to the suppressor grid. Demodulated output is taken from the plate circuit.

The tests described previously for duo-diode chroma demodulators are used in the pentode configuration too, with the exception of the vtvm test. The

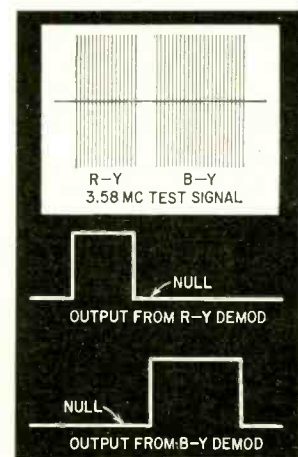


Fig. 8—R - Y and B - Y test signal and scope patterns found at the chroma demodulator outputs.

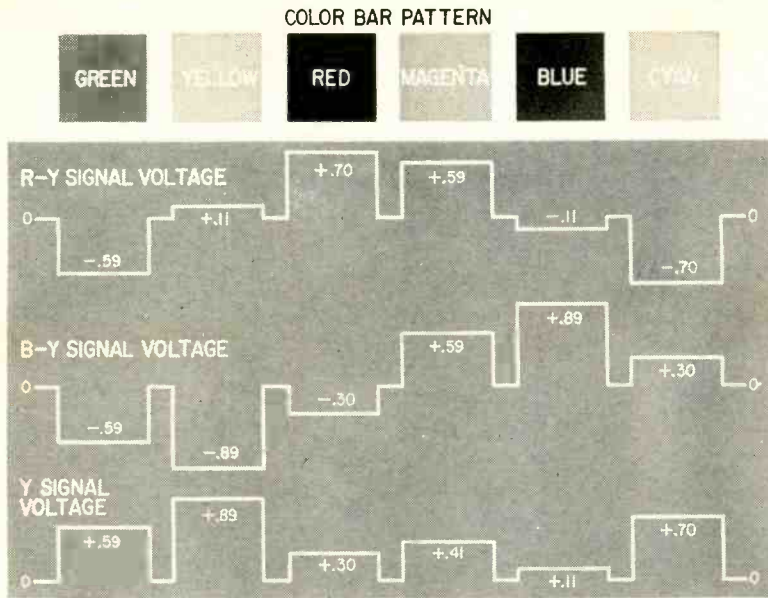


Fig. 9—Correct crankshaft scope patterns for normal operation of the R-Y and B-Y demodulators. Y crankshaft pattern is also shown.

pentode provides amplification. Its gain is about 10. A gain test is made with a scope and low-capacitance probe.

When an R - Y test signal is applied to the grid, a scope test should show 10 times more deflection at the plate than at the grid. If not, look for circuit faults. Also check the subcarrier voltage at the suppressor grid. There should be at least 20 volts peak to peak, in normal operation.

Peaking coils are used in the plate circuit, as in Fig. 10. Sometimes one of the coils has an adjustable slug. In other receivers, fixed peaking coils are used. The coils must have correct inductance values. Otherwise, the demodulator's bandpass is incorrect and color reproduction suffers.

The best way to test the peaking coils is to use a sweep generator and

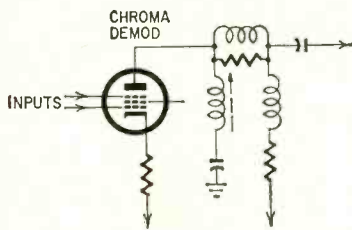


Fig. 10—A pentode chroma demodulator.

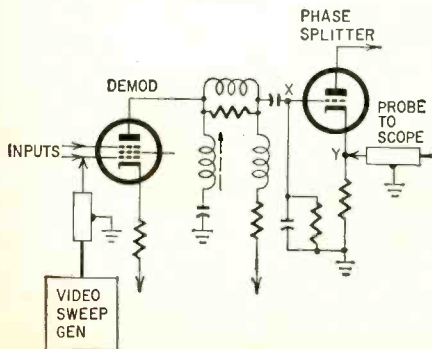


Fig. 11—Checking frequency response of a chroma demodulator.

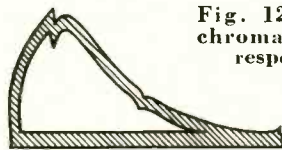


Fig. 12—A typical chroma demodulator response curve.

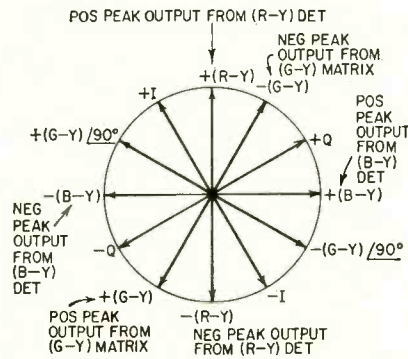


Fig. 13—G-Y is not in quadrature to either R-Y or B-Y. It is in quadrature only to (G-Y)/90°.

scope. Apply a video sweep signal to the grid of the demodulator tube, as in Fig. 11. Use a demodulator probe at a low-impedance point in the output circuit—the cathode of a phase splitter is suitable, as in Fig. 11. Do not apply the probe at a high-impedance point, or the curve will be distorted. If the probe is connected at X in Fig. 11, you run into distortion. However, the probe can be properly applied at Y. A typical curve is shown in Fig. 12. It has absorption markers at 0.5 and 1.5 mc. However, be sure to consult the service data for the particular chassis you are working on.

If the response curve is incorrect, look for defective or incorrectly tuned peaking coils. Off-value load resistors also cause curve distortion.

(R - Y)(G - Y) demodulators

Quite a few modern color receivers

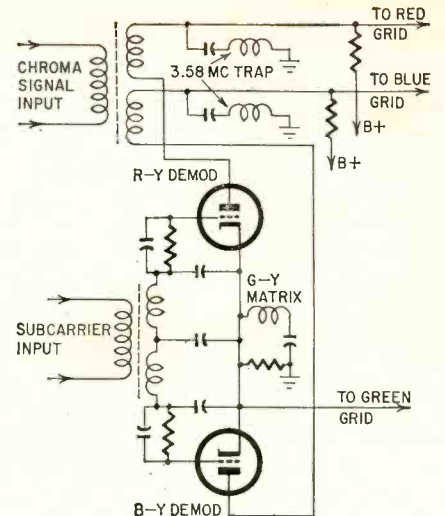


Fig. 14—The bootstrap demodulator matrixes G-Y in its common cathode circuit.

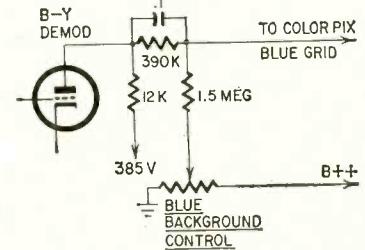


Fig. 15—Blue background control varies the dc bias on the blue grid.

interchange the positions of the B - Y demodulators and the G - Y matrix. That is, G - Y is developed in a chroma demodulator. B - Y is then obtained by matrixing G - Y with R - Y. This method gives a somewhat better signal-to-noise ratio.

This is not a quadrature demodulation system, as seen from Fig. 13. R - Y and G - Y are not separated 90°, as are R - Y and B - Y. Chroma demodulators can be operated along any pair of axes.

Servicing (R - Y)(G - Y) demodu-

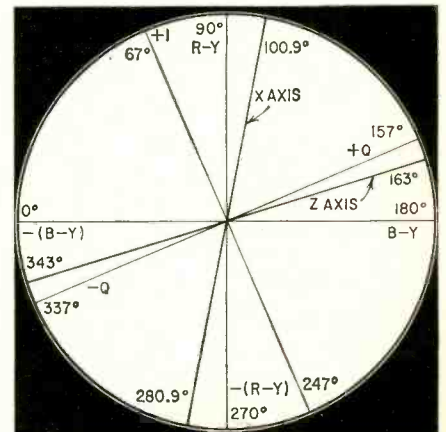


Fig. 16—An XZ chroma demodulator operates on subcarrier phases which are in the vicinity of the R - Y and Q axes.

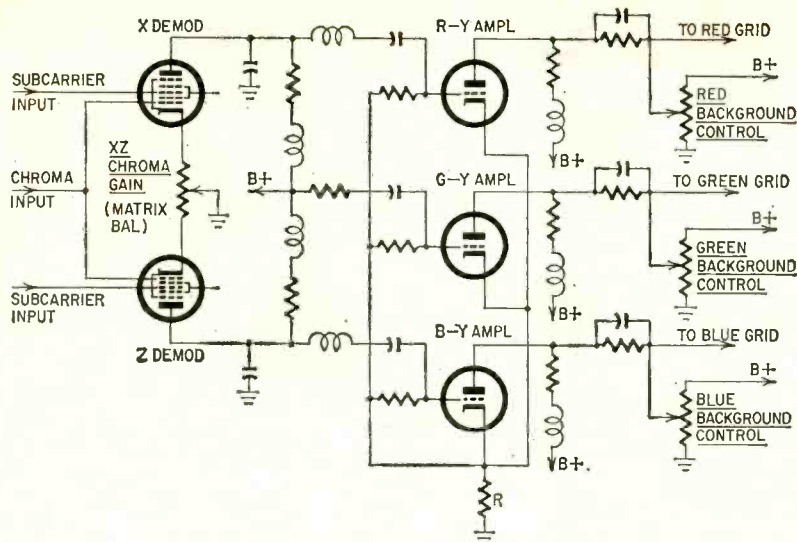


Fig. 17—The three color-difference amplifiers have common-cathode circuit. X and Z signals are thereby converted into R-Y, B-Y and G-Y.

lator circuits is very similar to servicing (R-Y)(B-Y) circuits; the same principles apply throughout. A G-Y demodulator must have sufficient 3.58-mc subcarrier oscillator voltage, just as the R-Y and B-Y demodulators discussed earlier. It nulls on the quadrature (G-Y)  $/90^\circ$  signal, if operating properly. Frequency response can be checked with a sweep generator, demodulator probe and scope.

#### Bootstrap demodulators

The chroma demodulators we discussed are low-level circuits. They are followed by amplifiers, before their signal is applied to the color picture tube.

On the other hand, the bootstrap demodulator illustrated in Fig. 14 is a high-level circuit. The outputs are applied directly to the picture-tube grids. It is an economy design, widely used in present-day color receivers.

Faults in a bootstrap demodulator are often more difficult to spot by picture analysis than in other demodulator configurations. This is because the bootstrap circuit branches interact. However, the test principles discussed earlier still apply. That is, if we apply an R-Y test signal to the receiver, the B-Y channel normally nulls. The R-Y channel normally nulls on a B-Y signal. The G-Y channel normally nulls on a (G-Y)  $/90^\circ$  signal.

Note that the output from the bootstrap demodulator is dc-coupled to the picture-tube grids. Dc coupling is also used in the Fig. 2 configuration.

Nearly all modern color receivers have dc-coupled chroma channels. This eliminates the need for dc restorer circuits. Dc coupling results in raster tinting when circuit trouble occurs. Note that the plate voltages for the triodes in Fig. 14 are also bias voltages for the picture-tube grids. For this reason, trouble in such circuits causes a red, green or blue raster, even in black-and-white reception.

Grid bias is varied with a background control, often connected as in Fig. 15. It controls grid bias through the required range. The grid bias is obtained from both the background control and the demodulator plate.

#### The XZ demodulator circuit

Some present-day color receivers use the XZ system of chroma demodulation, shown in Fig. 16. The XZ configuration is comparable to the (R-Y)(G-Y) arrangement, in that it is not a quadrature demodulation system. The axes of demodulation are in the region of the R-Y and Q axes. (See Fig. 16.)

R-Y, B-Y and G-Y outputs are obtained from the amplifier tubes shown in Fig. 17. These are also matrixes. Note that resistor R is common to the three cathodes of the color-difference amplifiers. The R-Y and B-Y amplifiers are grid-driven. The G-Y amplifier is cathode-driven.

A chroma gain control is provided in the X and Z demodulator-tube cathode circuits. It is adjusted to obtain standard nulls from the R-Y, B-Y and G-Y channels.

Hence, servicing the XZ demodulator system is basically similar to the procedures described for other chroma demodulator circuits. If correct nulls are not obtained on the three quadrature test signals, we check the phasing transformer between the color-subcarrier oscillator and the XZ demodulators, check the setting of the XZ gain control and the subcarrier injection voltage to the demodulators (this should be about 20 volts peak to peak).

If these checks do not give correct nulls, dc voltage checks in the demodulator circuits come next, and the voltages measured are compared with those specified in the receiver's service data. A scope and low-capacitance probe help localize ac signal distortion and incorrect peak-to-peak voltages. These checks assist in localizing a faulty component in a demodulator circuit. END

# NEXT MONTH

## How Good Are Speaker Response Curves?

Design engineers and high-fidelity listeners alike know that the response curves of a speaker or speaker system cannot be depended on to give an idea of its performance in a given living room. This story tells some of the reasons.

## Audio Aid for the Industrial Technician

A one-transistor oscillator for use on location on industrial jobs, for adjusting motion picture sound equipment and as a signal source for ordinary signal tracing.

## Licking the Intermittents

How to conquer the worst of all the technician's troubles—the defect that disappears as you approach the set. All the old methods—and a few you may not have heard of.

## Solar Cells

One of the men who were instrumental in developing the original Bell solar cells tells how the experimenter or student can roll his own.

# New Transistor Clock Radio Kit

**HEATHKIT**



## EVERYTHING A CLOCK-RADIO CAN OFFER ... AND PORTABLE TOO!

- Completely portable, all-transistor circuit
- Runs up to 500 hours on standard batteries
- Deluxe features at half the cost
- Easy to assemble

HEATHKIT TCR-1  
**\$45<sup>95</sup>**

### "YOUR CUE" TRANSISTOR CLOCK RADIO KIT (TCR-1)

Take all the deluxe features found in the most expensive clock-radios, add the convenience of complete portability, plus a modern 6-transistor battery operated circuit . . . then slash the price at least in half, and you have the new Heathkit "Your Cue" Transistor Portable Clock Radio.

Packing every modern clock-radio feature into a compact, beautifully styled turquoise and ivory plastic cabinet, "Your Cue" lulls you to sleep, wakes you up, gives you the correct time and provides top quality radio entertainment in and out-of-doors. It can also be used with the Heathkit Transistor Intercom system, opposite page, to provide music or a "selective alarm" system for one or more rooms covered by the intercom system.

An "Alarm-set" hand, hour hand, minute hand and sweep second hand grace the easy-to-read clock dial. All controls are conveniently located and simple to operate. The "lull-to-sleep" control sets the radio for up to an hour's playing time, automatically shutting off the receiver when you are deep in slumber. Other controls set "Your Cue" to wake you to soft music, or conventional "buzzer" alarm. A special earphone jack is provided for private listening or connection to your intercom or music system. At all times crystal-clear portable radio entertainment is yours at the flick of a switch.

The modern 6-transistor circuit features prealigned IF's for ease of assembly. A tuned RF stage and double tuned input to the IF stage assure top performance. The built-in rod-type antenna pulls in far-off stations with outstanding clarity while a large 4" x 6" speaker provides tonal reproduction of unusual quality.

Six easily obtainable penlight-size mercury batteries power the radio receiver up to 500 hours, while the clock operates up to 5 months from a single battery of the same type. Ordinary penlight cells may also be used with reduced battery life.

The handsome two-tone cabinet, measuring only 3½" H. x 8" W. x 7½" D. fits neatly into the optional carrying case for beach use, boating, sporting events, hunting, hiking, or camping.

Wherever you are, you'll find "Your Cue" your constant companion. Shpg. Wt. 5 lbs.

### LEATHER CARRYING CASE


HEATHKIT  
NO. 63-3

**\$4<sup>95</sup>**

Shpg. Wt. 2 lbs.



**HEATH COMPANY** / Benton Harbor, Mich.

 a subsidiary of Daystrom, Inc.

# New Transistor Intercom Kit

## TALK WITH ANY OR ALL FIVE STATIONS WITH YOUR OWN INTERCOM SYSTEM

- Battery Power Permits Placement Anywhere
- Versatile Unit has Many Important Uses
- Complete Privacy of Conversations Assured

### TRANSISTOR INTERCOM KIT (XI-1 and XIR-1)

A flexible, versatile transistor intercom, has been developed by Heath engineers to enable you to set up your own communications system at an unbelievably low price.

Consisting of a master unit (XI-1) and up to five remote stations (XIR-1), the system is designed for any remote unit to call the master, for any remote station to call any other remote station, or for the master unit to call any single remote unit or any combination of remote units. Complete privacy is assured, since a call to a remote station cannot be interrupted or listened to while the remote unit is in operation unless switched in by the master unit. Used with clock-radio, opposite page, it can serve as a music or "selective alarm" system.

Transistor circuitry means long life, instant operation and minimum battery drain. Eight ordinary, inexpensive "C" flashlight batteries will run a unit for up to 300 hours of normal "on" time. Circuitry is especially designed for crisp, clear intelligible communication and the instant operation feature allows tuning of the units off between calls, extending battery life. Use of battery power does away with power cords, allowing each unit to be placed where most convenient. Only two wires are required between the master unit and each remote station. Beautifully styled, the Heathkit Intercom presents a new approach in design. Both master and remote stations have two-piece cases in ivory and turquoise for a rich, quality appearance. Batteries not included. Shpg. Wt. 6 lbs.

### AC POWER SUPPLY (XP-1)

A permanent power supply for 24-hour operation of the XI-1 Intercom on household current. Converts 110 V. AC to well filtered 12-volt DC output, eliminating the need for batteries. Power supply is small, compact and fits in space normally occupied by batteries.

HEATHKIT XP-1.....\$9.95

## NEW IMPROVED DESIGN

### STEREO-MONO PREAMP KIT (SP-2A, SP-1A)

Get the SP-2A Stereo Preamp kit now, or the SP-1A monophonic version which you can easily convert to stereo whenever you choose by assembling the second channel (C-SP-1A) and plugging it into your SP-1A.

The SP-2A permits stereo, two channel mixing, or either channel monophonic use, and includes a remote balance control.

Six inputs (12 in the stereo version) accommodate tape, magnetic phono and microphone, plus three separate high level inputs. Level controls provided on "mag. phono" and high level inputs. Switch selects NARTB equalization for tape head input, and RIAA, LP or 78 RPM compensation for mag. phono input

HEATHKIT SP-1A (monophonic) Shpg. Wt. 13 lbs.....\$37.95  
HEATHKIT C-SP-1A (not shown) (converts SP-1A to SP-2A) Shpg. Wt. 4 lbs.....\$21.95

## THE WORLD'S BIGGEST BARGAIN IN A HI-FI AMPLIFIER

### 55 WATT HI-FI AMPLIFIER KIT (W-7A)

Utilizing advanced design in components and tubes to achieve unprecedented performance with fewer parts, Heathkit has produced the world's first and only "dollar-a-watt" genuine high fidelity amplifier. Meeting full 55-watt hi-fi rating and 50-watt professional standards, the new improved W-7A provides a comfortable margin of distortion-free power for any high fidelity application.


The sleek, modern styling of this unit allows unobtrusive installation anywhere in the home. The clean, open layout of chassis and precut, cabled wiring harness makes the W-7A extremely easy to assemble. Shpg. Wt. 28 lbs.

**SPECIFICATIONS**—Power output: Hi-Fi rating, 55 watts; Professional rating, 50 watts. Power response: ±1 db from 20 cps to 20 kc at 55 watts output. Total harmonic distortion: Less than 2% from 30 cps to 15 kc at 55 watts output. Intermodulation distortion: Less than 1% at 62 watts output using 60 cps and 6 kc signal mixed 4:1. Hum and noise: 80 db below 55 watts, unweighted. Damping factor: Switch on front panel for selecting either maximum (20:1) or unity (1:1). Output impedances: 4, 8 and 16 ohms and 70-volt line. Power requirements: 117 volts, 50/60 cycles, 90-160 watts. Dimensions: 8 1/2" D. x 6 1/2" H. x 15" W.



HEATHKIT XI-1 (Master)

**\$27<sup>95</sup>**

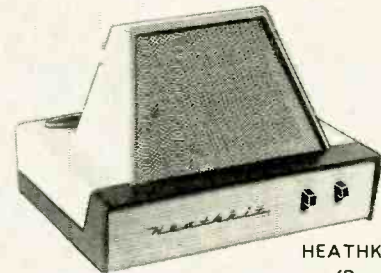

HEATHKIT XIR-1 (Remote)

**\$6<sup>95</sup>**

Shpg. Wt. 4 lbs.

**New**

HEATHKIT SP-2A (stereo)  
Shpg. Wt. 15 lbs.

**\$56<sup>95</sup>**

\$5.70 down. \$6.00 mo.



**New**



HEATHKIT W-7A

**\$54<sup>95</sup>**

New



HEATHKIT SA-2

**\$52<sup>95</sup>**

# Stereo Amplifiers

**YOUR BEST DOLLAR VALUE  
IN STEREO...**

## 14/14 WATT STEREO AMPLIFIER KIT (SA-2)

Complete control is at your fingertips with this versatile Stereo Amplifier-Preamplifier. Providing 14 watts per stereo channel, or 28 watts total monophonic, the SA-2 offers every modern feature in a master stereo control center at a price to please the budget minded. The unit offers selection of dual channel stereo operation, monophonic operation using both channels simultaneously, or using either channel for monophonic program material independent of the other channel. A 4-position input selector switch provides choice of mag. phono, crystal phono, tuner, and high level auxiliary input for tape recorder, TV, etc. Other features include RIAA equalization on mag. phono, channel reversing function, clutched volume control, ganged dual tone controls, speaker phase reversal switch and two AC outlets. Handsomely styled black and gold vinyl-clad steel cabinet. Shpg. Wt. 23 lbs.

**SPECIFICATIONS**—Power output: 14 watts per channel, "hi-fi"; 12 watts per channel, "professional"; 16 watts per channel, "utility". Power response:  $\pm 1$  db from 20 cps to 20 kc at 14 watts output. Total harmonic distortion: less than 2%, 30 cps to 15 kc at 14 watts output. Intermodulation distortion: less than 1% at 10 watts output using 60 cps and 6 kc signal mixed 4:1. Hum and noise: mag. phono input, 47 db below 14 watts; tuner and crystal phono, 63 db below 14 watts. Controls: dual clutched volume; ganged bass, ganged treble; 4-position selector; speaker phasing switch. AC receptacle: 1 switched, 1 normal. Inputs: 4 stereo or 8 monophonic. Outputs: 4, 8 and 16 ohms. Dimensions: 4 $\frac{1}{2}$ " H. x 15" W. x 8" D. Power requirements: 117 volts, 50/60 cycle, AC, 150 watts (fused).

New



HEATHKIT SA-3

**\$29<sup>95</sup>**

## ECONOMY STEREO AMPLIFIER KIT (SA-3)


This amazing performer delivers more than enough power for pure, undistorted room-filling stereophonic sound at the lowest possible cost. Featuring 3 watts per stereo channel and 6 watts as a monophonic amplifier, the SA-3 has been proven by exhaustive tests to be more than adequate in volume for every listening taste.

You will find its ease of assembly another plus feature. Heathkit construction manuals, world famous for their clarity and thoroughness, lead you a simple step at a time to successful completion of the kit. Larger than life-size diagrams show you exactly what each part looks like, where it goes, and how it is installed.

The amplifier is tastefully styled in black with gold trimmed control knobs and gold screened front and rear panel. A tremendous buy at this low Heathkit price! Shpg. Wt. 13 lbs.

**SPECIFICATIONS**—Power output: 3 watts per channel. Power response:  $\pm 1$  db from 50 cps, 20 kc at 3 watts out. Total harmonic distortion: less than 3%; 60 cps, 20 kc. Intermodulation distortion: less than 2% @ 3 watts output using 60 cycle & 6 kc signal mixed 4:1. Hum and noise: 65 db below full output. Controls: dual clutched volume; ganged treble, ganged bass; 7-position selector; speaker phasing switch; on-off switch. Inputs (each channel): tuner, crystal or ceramic phono. Outputs (each channel): 4, 8, 16 ohms. Finish: black with gold trim. Dimensions: 12 $\frac{1}{4}$ " W. x 6 $\frac{1}{2}$ " D. x 3 $\frac{1}{2}$ " H.

New

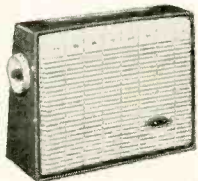

HEATHKIT XR-2P  
(6 lbs.)

**\$29<sup>95</sup>**



HEATHKIT XR-2L  
(7 lbs.) **\$34.95**

## 6-TRANSISTOR PORTABLE RADIOS (XR-2P and XR-2L)

New, improved styling, new vernier tuning, up to 1,000 hours on flashlight batteries . . . are just a few of the plus features you get with these new transistor portables. Carry them with you wherever you go; to the beach, on trips, boating, etc. These new, improved models bring you the outstanding performance of the preceding models plus brand new styling and the additional convenience of vernier tuning for smooth, effortless station selection. The XR-2P features a mocha and beige high-impact plastic case. The XR-2L has a sun-tan color leather case with an identical beige plastic front. Six Texas Instrument transistors are used for high sensitivity and selectivity. A large 4" x 6" PM speaker with heavy magnet provides excellent tone quality. The roomy chassis makes it unnecessary to crowd components, adding greatly to ease of construction. The six standard size "D" flashlight batteries used for power provide extremely long battery life and can be purchased anywhere. Fun to build, and fun to use . . . order one today!

New



HEATHKIT DS-1  
**\$69<sup>95</sup>**

\$7.00 DN., \$7.00 MO.

- Indicates Depth and Type of Bottom From 0 to 100 Feet
- Detects Submerged Objects (fish, logs, etc.) and Their Depth
- Completely Transistorized . . . Operates From Flashlight Batteries

## TRANSISTOR DEPTH SOUNDER (DS-1)

Weekend boatsman or professional . . . fisherman or skindiver . . . here's the depth sounder for you. Depth is indicated by a flashing neon lamp rotating behind a transparent circle in the molded black plastic dial face. A large hood around the dial enables the viewer to easily read the indicator in bright light or sunshine. The transducer uses a barium titanate element mounted in a faired, molded epoxy resin housing with solid brass through-hull fitting and mounting hardware. While designed for permanent mounting on the bottom of the boat, temporary outboard mounting of the transducer is also possible. The completely transistorized circuit operates from 6 flashlight cells and one long-life battery. Comes complete with splash-proof cabinet, hardware and gimbal-type mounting bracket. Shpg. Wt. 10 lbs.

# New Amplifiers & Tuners

## A NEW AMPLIFIER AND PREAMP UNIT PRICED WELL WITHIN ANY BUDGET

### 14-WATT HI-FI AMPLIFIER KIT (EA-3)

This thrilling successor to the famous Heathkit EA-2 is one of the finest investments anyone can make in top quality high fidelity equipment. It delivers a full 14 watts of hi-fi rated power and easily meets professional standards as a 12-watt amplifier.

Rich, full range sound reproduction and low noise and distortion are achieved through careful design using the latest developments in the audio science. Miniature tubes are used throughout, including EL-84 output tubes in a push-pull output circuit with a special-design output transformer. The built-in preamplifier has three separate switch-selected inputs for magnetic phono, crystal phono or tape, and AM-FM tuner. RIAA equalization is featured on the magnetic phono input. Shpg. Wt. 15 lbs.

**NOTE THESE OUTSTANDING SPECIFICATIONS—Power output:** 14 watts, Hi-Fi; 12 watts, Professional; 16 watts, Utility. **Power response:**  $\pm 1$  db from 20 cps to 20 kc at 14 watts output. **Total harmonic distortion:** less than 2%, 30 cps to 15 kc at 14 watts output. **Intermodulation distortion:** less than 1% at 16 watts output using 60 cps and 6 kc signal mixed 4:1. **Hum and noise:** mag. phono input, 47 db below 14 watts; tuner and crystal phono, 63 db below 14 watts. **Output impedances:** 4, 8 and 16 ohms.



HEATHKIT EA-3  
**\$29<sup>95</sup>**

## NEVER BEFORE HAS ANY HI-FI AMPLIFIER OFFERED SO MUCH AT SO LOW A PRICE

### "UNIVERSAL" 14-WATT HI-FI AMPLIFIER KIT (UA-2)

Meeting 14-watt "hi-fi" and 12-watt "professional" standards, the UA-2 lives up to its title "universal" performing with equal brilliance in the most demanding monophonic or stereophonic high fidelity systems. Its high quality, remarkable economy and ease of assembly make it one of the finest values in high fidelity equipment. Buy two for stereo. Shpg. Wt. 13 lbs.

**SPECIFICATIONS—Power output:** Hi-Fi rating, 14 watts; Professional rating, 12 watts. **Power response:**  $\pm 1$  db from 20 cps to 20 kc at 14 watts output. **Total harmonic distortion:** Less than 2% from 20 cps to 20 kc at 14 watts output. **Intermodulation distortion:** Less than 1% at 14 watts output using 60 cps and 6 kc signal mixed 4:1. **Hum and noise:** 73 db below 14 watts. **Output impedances:** 4, 8 and 16 ohms. **Damping factor:** Switched for unity or maximum; maximum damping factor 15:1. **Input voltage for 14 watt output:** .7 volts. **Power requirements:** 117 volts 50/60 cycles, 55 watts. **Dimensions:** 10" W. x 6 $\frac{1}{2}$ " D. x 4 $\frac{3}{4}$ " H.



HEATHKIT UA-2  
**\$22<sup>95</sup>**

## MORE STATIONS AND TRUE FM QUALITY ARE YOURS WITH THIS FINE TUNER KIT

### HIGH FIDELITY FM TUNER KIT (FM-4)


This handsomely styled FM tuner features better than 2.5 microvolt sensitivity, automatic frequency control (AFC) with on-off switch, flywheel tuning and prewired, prealigned and pretested tuning unit. Clean chassis layout, prealigned intermediate stage transformers and assembled tuning unit makes construction simple—guarantees top performance. Flywheel tuning and new soft, evenly-lighted dial scale provide smooth, effortless operation. Vinyl-covered case has black, simulated-leather texture with gold design and trim. Multiplex adapter output also provided. Shpg. Wt. 8 lbs.

**SPECIFICATIONS—Tuning range:** 88 to 108 mc. **Quieting sensitivity:** 2.5 uv for 20 db of quieting. **IF frequency:** 10.7 mc. **Image ratio:** 45 db. **AFC correction factor:** 75 kc per volt. **AM suppression:** 25 db. **Frequency response:**  $\pm 2$  db 20 to 20,000 cps. **Harmonic distortion:** Less than 1.5%, 1100 uv, 400 cycles 100% modulation. **Intermodulation distortion:** Less than 1%, 60 cycles and 6 kc mixed 4:1 1100 uv, 30% modulation. **Antenna:** 300 ohms unbalanced. **Output impedance:** 600 ohms (cathode follower). **Output voltage:** nominal .5 volt (with 30% modulation, 20 uv signal). **Power requirements:** 105-125 volts 50/60 cycle AC at 25 watts. **Overall dimensions:** 4 $\frac{1}{2}$ " H. x 13 $\frac{1}{4}$ " W. x 5 $\frac{1}{2}$ " D.



HEATHKIT FM-4  
**\$34<sup>95</sup>**

**HEATH COMPANY** / Benton Harbor, Mich.

 a subsidiary of Daystrom, Inc.

# New



# Tape Recorders



- Choice of 3 Outstanding Models
- Compare With \$350-\$400 Machines
- Preassembled Tape Mechanism
- Choice of Monophonic or Stereo models
- Complete versatility
- Easy to assemble, easy to use

## PROFESSIONAL QUALITY TAPE RECORDER KITS (TR-1 Series)

Enjoy the incomparable performance of these professional quality tape recorders at less than half the usual cost. These outstanding kits offer a combination of features found only in much higher priced professional equipment, generally selling for \$350 to \$400. Not the least of these special features is the handsome styling which characterizes the kits... a semi-gloss black panel is set off by a plastic escutcheon in soft gold, which is matched by black control knobs with gold inserts. The mechanical assembly, with fast forward and rewind functions, comes to you completely assembled and adjusted; you build only the tape amplifier. And, you'll find this very easy to accomplish, since the two circuit boards eliminate much of the wiring. Separate record and playback heads and amplifiers allow monitoring from tape while recording and a "pause" control permits instant starting and stopping of tape for accurate cueing and tape editing. A digit counter is provided for convenient selection of any particular recording. Push-pull knob provides instant selection of 3 3/4" or 7 1/2" IPS tape speed. Safety interlock on record switch reduces possibility of accidental erasure of recorded tapes. Shpg. Wt. 30 lbs.

**SPECIFICATIONS—Tape speed:** 7.5" and 3.75" per second. **Maximum reel size:** 7". **Frequency response (record-playback):** ±2.5 db. 30 to 12,000 cps at 7.5 IPS; ±2.5 db, 30 to 6,500 cps at 3.75 IPS. **Harmonic distortion:** 1% or less at normal recording level; 3% or less at peak recording level. **Signal-to-noise ratio:** 50 db or better, referred to normal recording level. **Flutter and wow:** 0.3% RMS at 7.5 IPS; 0.35% RMS at 3.75 IPS. **Heads (3):** erase, record, and in-line stereo playback (TR-1C, monophonic playback). **Playback equalization:** NARTB curve, within ±2 db. **Inputs (2):** microphone and line. **Input impedance:** 1 megohm. **Model TR-1D & TR-1E outputs (2):** A and B stereo channels. **Model TR-1C output (1):** monophonic. **Output levels:** approximately 2 volts maximum. **Output impedance:** approximately 600 ohm (cathode followers). **Recording level indicator:** professional type dc meter. **Bias erase frequency:** 60 kc. **Timing accuracy:** ±2%. **Power requirements:** 105-125 volts AC, 60 cycles, 35 watts. **Dimensions:** 15 1/2" W. x 13 1/2" D. Total height 10 1/2". **Mounting:** requires minimum of 8 1/2" below and 1 1/2" above mounting surface. May be operated in either horizontal or vertical position.

- MODEL TR-1C Monophonic Tape Deck:** \$159.95 \$16.00 DWN. Monophonic Record and Playback. \$14.00 MO.
- MODEL TR-1D Two Track Stereo Tape Deck:** Monophonic Record and Playback, plus Playback of 2-track \$169.95 \$17.00 DWN. Pre-recorded Stereo Tapes (stacked). \$15.00 MO.
- MODEL TR-1E Four Track Stereo Tape Deck:** Monophonic Record and Playback, plus Playback of 4-track \$169.95 \$17.00 DWN. Pre-recorded Stereo Tapes (stacked). \$15.00 MO.
- MODEL C-TR-1C Conversion Kit:** Converts TR-1C to TR-1D (see TR-1D description above). Shpg. Wt. 2 lbs. .... \$19.95
- MODEL C-TR-1D Conversion Kit:** Converts TR-1D to TR-1E (see TR-1E description above). Shpg. Wt. 2 lbs. .... \$14.95
- MODEL C-TR-1CQ Conversion Kit:** Converts TR-1C to TR-1E (see TR-1E description above). Shpg. Wt. 2 lbs. .... \$19.95

**NOTE:** To convert TR-1C to TR-1E, purchase both C-TR-1C and C-TR-1D conversion kits.

## STEREO-MONO TAPE RECORDER KITS (TR-1A Series)

Here are the tape recorders the avid hi-fi fan will find most appealing! Their complete flexibility in installation and many functions make them our most versatile tape recorder kits. This outstanding tape recorder now can be purchased in any one of three versions. You can buy the new two-track (TR-1AH) or four-track (TR-1AQ) versions which record and play back both stereo and monophonic programming, or the two-track monophonic record-playback version (TR-1A) and later convert to either two-track or four-track stereo record-playback models by purchasing the MK-4 or MK-5 conversion kits. The tape deck mechanism is extremely simple to assemble. Long, faithful service is assured by precision bearings and close machining tolerances that hold flutter and wow to less than 0.35%. Power is provided by a four-pole, fan-cooled induction motor. One lever controls all tape handling functions of forward, fast-forward or rewind modes of operation. The deck handles up to 7" tape reels at 7.5 or 3.75 IPS as determined by belt position. The TR-1A series decks may be mounted in either a vertical or horizontal position (mounting brackets included). The TE-1 Tape Electronics kits supplied feature NARTB equalization, separate record and playback gain controls and a safety interlock. Provision is made for mike or line inputs and recording level is indicated on a 6E5 "magic eye" tube. Two circuit boards simplify assembly.

**MODEL TR-1A:** Monophonic two-track record/playback with fast forward and rewind functions. Includes one \$99.95 \$10.00 DWN. TE-4 Tape Electronics kit. Shpg. Wt. 24 lbs. \$9.00 MO.

**TR-1A SPECIFICATIONS—Frequency response:** 7.5 IPS ±3 db 50 to 12,000 cps; 3.75 IPS ±3 db 50 to 7,000 cps. **Signal-to-noise ratio:** better than 45 db below full output of 1.25 volts/channel. **Harmonic distortion:** less than 2% at full output. **Bias erase frequency:** 60 kc (push-pull oscillator).


**MODEL TR-1AH:** Two-track monophonic and stereo record/playback with fast forward and rewind functions. Two \$149.95 \$15.00 DWN. TE-4 Tape Electronics kits. Shpg. Wt. 36 lbs. \$13.00 MO.

**TR-1AH SPECIFICATIONS—Frequency response:** 7.5 IPS ±3 db 40 to 15,000 cps; 3.75 IPS ±3 db 40 to 10,000 cps. **Signal-to-noise ratio:** 45 db below full output of 1 volt/channel. **Harmonic distortion:** less than 2% at full output. **Bias erase frequency:** 60 kc (push-pull oscillator).

**MODEL TR-1AQ:** Four-track monophonic and stereo record/playback with fast forward and rewind functions. Two \$149.95 \$15.00 DWN. TE-4 Tape Electronics kits. Shpg. Wt. 36 lbs. \$13.00 MO.


**TR-1AQ SPECIFICATIONS—Frequency response:** 7.5 IPS ±3 db 40 to 15,000 cps; 3.75 IPS ±3 db 40 to 10,000 cps. **Signal-to-noise ratio:** 40 db below full output of .75 volts/channel. **Harmonic distortion:** less than 2% at full output. **Bias erase:** 60 kc (push-pull oscillator).

**HEATH COMPANY/Benton Harbor, Mich.**

 a subsidiary of Daystrom, Inc.


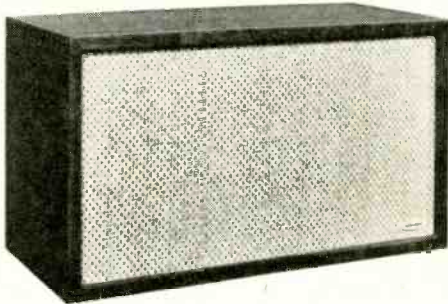
# New "Acoustic Suspension" Hi-Fi Speaker System Kit



HEATHKIT AS-2U (unfinished)

**\$69<sup>95</sup>**

HEATHKIT AS-2M (mahogany) **\$79.95**  
HEATHKIT AS-2B (birch) **EACH**

**NOW—FOR THE FIRST TIME  
—EXCLUSIVELY FROM HEATH**

## ACOUSTIC SUSPENSION HI-FI SPEAKER SYSTEM KIT (AS-2)

A revolutionary principle in speaker design, the Acoustic Research speaker has been universally accepted as one of the most praiseworthy speaker systems in the world of high fidelity sound reproduction. Heathkit is proud to be the sole kit licensee of this Acoustic Suspension principle from AR, Inc., and now offers for the first time this remarkable speaker system in money-saving, easy-to-build kit form.

The 10" Acoustic Suspension woofer delivers clean, clear extended-range bass response and outstanding high frequency distribution is provided by the specially designed "cross-fired" two-speaker tweeter assembly.

Another first in the Heathkit line is the availability of preassembled and prefinished cabinets. Cabinets are available in prefinished birch (blond) or mahogany, or in unfinished birch suitable for the finish of your choice. Kit assembly consists merely of mounting the speakers, wiring the simple cross-over network and filling the cabinet with the fiberglass included. Shpg. Wt. 32 lbs.

**SPECIFICATIONS—Frequency response (at 10 watts input):**  $\pm 5$  db, 42 to 14,000 cps; 10 db down at 30 and 16,000 cps. **Harmonic distortion:** below 2% down to 50 cps; below 3% down to 40 cps at 10 watts input in corner room location. **Impedance:** 8 ohms. **Suggested amplifier power:** 20 watts minimum. **Suggested damping factor:** high (5:1 or greater). **Efficiency:** about 2%. **Distribution angle:** 90° in horizontal plane. **Dimensions:** 24" W. x 13 $\frac{1}{2}$ " H. x 11 $\frac{1}{2}$ " D.

## New Test Equipment




HEATHKIT FMO-1 Price to be announced

## AN INSTRUMENT LONG-AWAITED BY SERVICE TECHNICIANS EVERYWHERE!
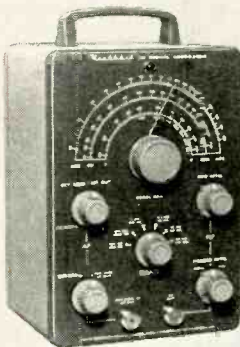
### HEATHKIT FM TEST OSCILLATOR KIT (FMO-1)

Here in one compact, easy-to-use instrument are provided all the test signals and sweep frequencies required for fast, easy alignment and troubleshooting of RF, IF and detector sections of FM tuners and receivers. An instrument unique in the test equipment field . . . being the only one of its type designed especially for FM service work.

**SPECIFICATIONS—Output frequencies:** for RF alignment, 90 mc (FM band low end), 100 mc (FM band middle range), 107 mc (FM band high end). **Modulation:** 400-cycle incidental FM. **IF and detector alignment:** 10.7 mc sweep. **Sweep width markers:** 200 kc to over 1 mc, variable, 10.7 mc (crystal), 100 kc sub-markers. **Modulation:** 400-cycle AM. **For other applications:** 10.0 mc (crystal) and harmonics, 100 kc, 400-cycle audio. **Controls:** main frequency selector, modulation switch/concentric level control, marker oscillator switch/concentric level control, sweep width—power switch, output control, AF-RF (source impedance) switch. **Power supply:** transformer, selenium rectifier. **Power requirements:** 105-125 V, 50/60 cycles, 12 watts. **Cabinet size:** 7 $\frac{3}{4}$ " H. x 4 $\frac{3}{4}$ " W. x 4 $\frac{3}{4}$ " D.



HEATHKIT RF-1

**\$27<sup>95</sup>**

## PREASSEMBLED AND ALIGNED BANDSWITCH/COIL ASSEMBLY

### RF SIGNAL GENERATOR KIT (RF-1)

Moderately priced, and capable of precision performance the RF-1 provides highly accurate and stable RF signals for trouble-shooting and aligning RF and IF circuits of all kinds. Modulated or unmodulated RF output of at least 100,000 microvolts is available, controlled by both fixed-step and continuously variable controls. A built-in 400 cycle audio generator with 10-volt output provides internal modulation of RF signal and is available separately for audio tests. A preassembled bandswitch and coil assembly, aligned to factory precision standards, eliminates the need for special alignment equipment. Shpg. Wt. 7 lbs.

**SPECIFICATIONS—Frequency range:** Band A, 100 kc to 320 kc; Band B, 310 kc to 1.1 mc; Band C, 1 mc to 3.2 mc; Band D, 3.1 mc to 11 mc; Band E, 10 mc to 32 mc; Band F, 32 mc to 110 mc. **Calibrated harmonics:** 110 mc to 220 mc. **Accuracy:** 2%. **Output:** impedance, 50 ohms; voltage, in excess of 100,000  $\mu$ v on all bands. **Modulation:** internal, 400 cycles approx. 30% depth; external, approx. 3 V across 50 k ohm for 30%. **400 cycles audio output:** approx. 10 V open circuit. **Tube complement:** V1 12AT7 RF oscillator, V2 6AN8 modulator and output. **Power requirements:** 105-125 V 50/60 cycles AC, 15 watts. **Aluminum cabinet dimensions:** 6 $\frac{1}{2}$ " W. x 9 $\frac{1}{2}$ " H. x 5" D.

New



HEATHKIT KS-1

**\$169<sup>95</sup>**



HEATHKIT KL-1

**\$415<sup>00</sup>**



HEATHKIT XC-2

**\$36<sup>95</sup>**



HEATHKIT UT-1

**\$28<sup>95</sup>**

# Ham Radio Gear

## TOP POWER WITH ECONOMY AND SAFETY

### KILOWATT POWER SUPPLY KIT (KS-1)

The KS-1 is designed as a companion to the "Chippewa" Linear Amplifier and is also suitable for supplying plate power to most other RF amplifiers in the medium to high power class. The KS-1 features an oil-filled, hermetically sealed plate transformer to minimize corona, a swinging choke in the filter circuit for good regulation, and a 60-second time delay relay to permit adequate heating of the mercury vapor rectifiers before application of plate voltage. All components are conservatively rated and well insulated for long life and dependable service. Shpg. Wt. 105 lbs.

**SPECIFICATIONS**—Maximum DC power output: 1500 watts. Nominal DC voltage output: 3000 or 1500 volts. Maximum DC current output: Average 500 ma, peak 1000 ma. Regulation: 180 to 600 ma (typical linear amplifier), 8%; 0 to 300 ma (typical class C amplifier), 10%; 0 to 500 ma, 15%. Ripple: Less than 1%. Tube complement: (2) 866A mercury vapor rectifiers. Recommended ambient temperature: 50 to 100 degrees F. Circuit: Two half-wave mercury vapor rectifiers in a full wave, single-phase configuration with swinging choke input filtering. Line power requirements: 115 V, 50/60 cycles, 20 amperes; 230 V, 50/60 cycles, 10 amperes. Chassis size: 17½" W. x 12" H. x 13" D.

## MOVE TO THE TOP IN TRANSMITTING POWER

### "CHIPPEWA" KILOWATT LINEAR AMPLIFIER KIT (KL-1)

The KL-1 operates at maximum legal amateur power inputs in SSB, CW or AM service using any of the popular CW, SSB and AM exciters as a driver. Premium tubes (4—400's) push the "Chippewa" to top performance levels while a centrifugal blower provides more than adequate cooling. Shpg. Wt. 70 lbs.

**SPECIFICATIONS**—RF section: Driving power required (10 meters): Class AB1 (tuned grid) 10 watts peak; Class C (tuned grid) 40 watts; Class AB1 (swamped grid) 60 watts peak. Power input: Class AB1 (SSB-voice modulation) 2000 watts PEP; Class AB1 (SSB-two tone test) 1300 watts; Class AB1 (AM linear) 1000 watts; Class C (CW) 1000 watts. Power output (20 meters): Class AB1 (SSB-voice modulation) 900 watts PEP; Class AB1 (SSB-two tone test) 550 watts; Class AB1 (AM linear) 300 watts; Class C (CW) 750 watts. Output impedance: 50 to 72 ohms (unbalanced). Input impedance: 50 to 72 ohms (unbalanced). Band coverage: 80, 40, 20, 15 and 10 meters. Panel metering: 0 to 50 ma. grid current; 0 to 100 ma screen current; 0 to 5000 volt plate voltage; 0 to 1000 ma plate current. Tube complement: Final tubes. (2) 4-400A; clamp tube, (1) 6DQ6; voltage regulators, (4) OD3, (2) OC3. Power requirements: AC (power supply primary circuit), 250 watts, 115 volt, 50/60 cycles; DC, 3000 to 4000 volts, 450 ma. Cabinet size: 19½" W. x 11¼" H. x 16" D.

### 2-METER CONVERTER KIT (XC-2)

Extends coverage of the Heathkit "Mohawk" Receiver to the 2-meter band. May also be used with receivers tuning a 4 mc segment between the frequencies of 22 and 35 mc when appropriate crystal is used. Shpg. Wt. 7 lbs.

**SPECIFICATIONS**—Noise figure: 4.5 db; 1 uv signal provides 20 db thermal noise quieting. Sensitivity: approx. .1 uv input will provide a signal better than 6 db over noise level. Gain: approx. 40 db. Pass band: essentially flat 144 to 148 mc; approx. 35 db down at 143 and 149 mc. Image rejection: better than 100 db (tunable). Output impedance: 50 to 75 ohms. Input impedance: 50 to 75 ohms. Frequency: input, 144 to 148 mc; output, 22 to 28 mc with crystal supplied. Tubes: 6AM4, 6BS8, 6EA8, 12AT7. Crystal: .005% 3rd overtone. Power requirements: 150 volts DC at 50 ma (dropping resistor supplied for 210 VDC RX-1 operation) 6.3 volts AC/DC at 1.375 amps. Size: 9" W. x 5½" H. x 4¾" D.

### "BEST BUY" UTILITY POWER SUPPLY KIT (UT-1)

This power supply is ideal for converting the Heathkit "Cheyenne" and "Comanche" mobile transmitter and receiver to fixed station operation; or may be used to provide necessary filament and plate voltage for a wide variety of amateur equipment. Features silicon diode rectifiers, high capacity filters for superior dynamic regulation, and line filtering to minimize TVI and reduce receiver line noise. On ICAS basis, provides 150 watts DC plus filament power for 6.3 volt or 12.6 volt filament applications (6.3 VAC., 8 amps. or 12.6 VAC., 4 amps.; 600 VCD., 250 ma or 600 VDC., 200 ma and 300 VDC., 100 ma). Less than 1% ripple; excellent regulation. Housed in attractive green and gray-green cabinet measuring 9" long, 4¾" wide, 6" high. Shpg. Wt. 15 lbs.





FOR  
THE  
CRITICAL  
CUSTOMER

the world's most  
trouble-free cartridges..

**SHURE**

*Stereo Dynetic*

**H I F I P H O N O C A R T R I D G E S**  
Shure High Fidelity Stereo Dynetic phono cartridges are designed to satisfy the most critical requirements. Made under custom laboratory conditions, each unit is checked electrically, mechanically and acoustically to insure trouble-free performance.




**PROFESSIONAL**  
**MODEL M3D**  
AT \$45.00\*

\*audiophile net.  
with 0.7 mil diamond

Incomparable quality—the overwhelming choice of independent critics and experts. Floats at only 3 grams in transcription tone arms. Distortion-free response from 20 to 15,000 cps. Superbly designed and built to perfectionist tolerances.

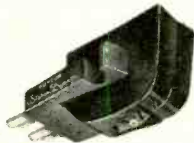**CUSTOM**  
**MODEL M7D**  
AT \$24.00\*



\*audiophile net.  
with 0.7 mil diamond

Outclasses every cartridge except the Shure M3D—by actual listening tests! Tracks perfectly at minimum pressure available in record changer arms. Smooth from 40 to 15,000 cps.

Use Only Shure Replacement Styli that carry the certification "Precision Manufactured by Shure." Inferior imitations can seriously degrade the performance of the cartridge.

Literature available:

**SHURE BROTHERS, INC.**  
222 Hartrey Avenue, Evanston, Illinois

**TELEVISION**

**SPOTTING  
VIDEO  
IF  
OSCILLATION**


By **WARREN J. SMITH**

**O**SCILLATIONS in the video if strip possibly produce more inferiority and self-distrust among service technicians than any other fault of TV receivers. Methods of troubleshooting this type of oscillation are usually involved and often time-consuming. This simplified method saves much of the time and most of the worry.

The first question is: When should video if oscillation be suspected? When the audio is normal and the video information is present but not entirely legible. The raster may be streaked with long white lines or have a spotted appearance unaffected by changes in the contrast control setting. The presence of oscillations can be quickly verified by connecting a vacuum-tube voltmeter across the detector load resistor as indicated in the figure. Normal voltage readings at this point, with no input signal, vary from 0.5 to 1, due to the space charge of the detector tube and the small amount of rectified voltage caused by normal disturbances such as noise. Oscillation increases the voltage to some high value. In extreme cases it may read as high as 35 volts.


The exact cause of oscillation is often difficult to determine, but it can usually be attributed to one of two things: misalignment or a defective component in the if strip. It is comparatively easy to correct a misaligned if strip. Oscillations are usually caused by two or more if transformers being tuned too close to the same frequency. The method recommended here is to locate the if transformer that is tuned to the highest frequency and turn the tuning slug all the way out. Next, the transformer that corresponds with the lowest frequency is located and its tuning slug turned all the way in. If one transformer is normally tuned to the center frequency of the bandpass, its tuning slug is approximately centered. Any other if transformers should be adjusted either to a quarter- or halfway position between the others, depending upon their frequency. This will result in an

**WE'VE  
GOT  
A  
SECRET!**

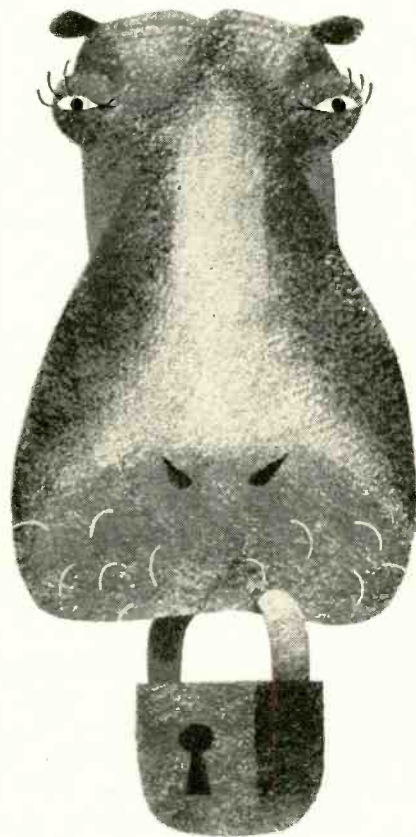

Our lips are locked . . . but not for long. You will soon learn about the new Standard Coil Products tuner program. Watch for it. It means better service for your customers—greater profits for you.

## TELEVISION

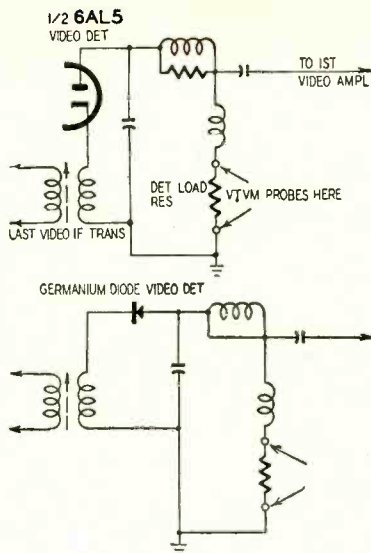

Basic schematic of typical tube and diode TV detector circuits, showing probe placement.

extremely wide response but eliminates any tendency toward oscillation. The alignment can now be finished by following the manufacturer's alignment table for that particular model.

Suppose that after going through the procedure above, oscillation still remains. The voltmeter again indicates an excessive amount of voltage across the detector load resistor as one of the if slugs is adjusted to its normal setting. Then oscillation is attributable to a defective component, a trouble that is often difficult to isolate. A change in value of a loading resistor across an if transformer, a leaky coupling capacitor, an increase in value of plate or grid load resistors are all sources of oscillations. A leaky coupling capacitor permits a portion of the high positive plate voltage to leak over to the grid of the following stage. This positive voltage on the grid reduces the normal bias on the tube and results in excessive gain in the stage, allowing oscillations to develop. An increase in value of grid or plate load resistors permits the Q of the stage to rise above normal, and again excessive gain causes oscillation.

A method for quickly locating the stage in which the oscillations are originating is to bypass the grid of each video if tube with a .001- $\mu$ f capacitor to ground. The capacitors eliminate the tendency of oscillations to build up and, by removing them one by one (starting at the stage preceding the detector) while observing the voltmeter for an increase of voltage across the detector load resistor, it can be determined exactly in which stage they are being developed. For this purpose several capacitors with short leads and clips should be made up, to save time.

To find the exact cause of the trouble once the stage in which it originates is isolated, measure and compare with the manufacturer's information the plate, grid and cathode voltages of the

## Here's where to buy your HEATHKIT® locally...

... through any of the carefully selected Heathkit Dealers listed below. This service has been established in answer to hundreds of requests, and we think that you, too, will welcome the availability of convenient "over-the-counter" delivery.

Although you will find your local dealers' price somewhat higher than the advertised direct mail

price, we're sure you'll agree that this increase is justified... as your dealer has absorbed all transportation costs, provides a reliable source for parts and service, offers local display and demonstration facilities, stands ready to counsel or advise you on any problems that might arise... and, of course, carries a complete stock of kits for immediate delivery.

- |   |  |  |   |
|---|--|--|---|
| <p><b>CALIFORNIA</b></p> <p>BERKELEY, CALIF. ZACKIT Corp.</p> <p>CHICO, CALIF. Dunlap Radio &amp; TV Supply Co.</p> <p>EL CAJON, CALIF. Tetrad Electronics</p> <p>FRESNO, CALIF. Dunlap Radio &amp; TV Supply Co.</p> <p>LOS ANGELES, CALIF. Kierulff Sound Corp.</p> <p>LOS ANGELES (WEST), CALIF. Kierulff Sound Corp.</p> <p>LONG BEACH, CALIF. Kierulff Sound Corp.</p> <p>MARYSVILLE, CALIF. Dunlap Radio &amp; TV Supply Co.</p> <p>MERCED, CALIF. Dunlap Radio &amp; TV Supply Co.</p> <p>MODESTO, CALIF. Dunlap Radio &amp; TV Supply Co.</p> <p>PALO ALTO, CALIF. Zack Electronics</p> <p>PASADENA, CALIF. Kierulff Sound Corporation</p> <p>RIVERSIDE, CALIF. Kierulff Sound Corp.</p> <p>SACRAMENTO, CALIF. Dunlap Radio &amp; TV Supply Co.</p> <p>SAN DIEGO, CALIF. Tetrad Electronics</p> <p>SAN FERNANDO VALLEY Kierulff Sound Corp.</p> <p>SAN FRANCISCO, CALIF. Zack Electronics</p> <p>SANTA ANA-ORANGE, CALIF. Kierulff Sound Corp.</p> <p>SANTA BARBARA, CALIF. ZACKIT Corp.</p> <p>STOCKTON, CALIF. Dunlap Radio &amp; TV Supply Co.</p> <p>VISALIA, CALIF. Dunlap Radio &amp; TV Supply Co.</p> <p><b>COLORADO</b></p> <p>DENVER Radio Products Sales Corp.</p> <p><b>DELAWARE</b></p> <p>WILMINGTON, DELAWARE Radio Electric Service Co.</p> <p><b>HAWAII</b></p> <p>HILO, HAWAII Radio-Television Corp., Ltd.</p> <p>HONOLULU, HAWAII Radio-Television Corp., Ltd.</p> <p><b>ILLINOIS</b></p> <p>ALTON, ILLINOIS Radonics-Alton, Inc.</p> <p><b>INDIANA</b></p> <p>FT. WAYNE, INDIANA Ft. Wayne Electronic Supply, Inc.</p> <p>INDIANAPOLIS, INDIANA Graham Electronic Supply, Inc.</p> <p>LAFAYETTE, INDIANA Lafayette Radio Supply, Inc.</p> <p>MUNCIE, INDIANA Muncie Electronic Supply, Inc.</p> <p><b>IOWA</b></p> <p>DES MOINES, IOWA Radio Trade Supply Co.</p> <p>FT. DODGE, IOWA Radio Trade Supply Co.</p> <p>MARSHALLTOWN, IOWA Radio Trade Supply Co.</p> <p>WATERLOO, IOWA Radio Trade Supply Co.</p> <p><b>LOUISIANA</b></p> <p>HOUMA, LOUISIANA Crescent Electronic Supply</p> <p>LAFAYETTE, LOUISIANA Sterling Electronics, Inc.</p> <p>NEW ORLEANS, LOUISIANA Crescent Electronic Supply</p> <p>NEW ORLEANS, LOUISIANA Hi-Fi, Inc.</p> | <p><b>MARYLAND</b></p> <p>BALTIMORE, MARYLAND American Distributing Company (2 locations)</p> <p>The Hi-Fi Shop</p> <p><b>MASSACHUSETTS</b></p> <p>BOSTON, MASS. Audionics, Inc.</p> <p><b>MICHIGAN</b></p> <p>ALLEN PARK, MICHIGAN Volta Electronics</p> <p>DETROIT, MICHIGAN High Fidelity Workshop</p> <p>PONTIAC, MICHIGAN High Fidelity Workshop</p> <p><b>MINNESOTA</b></p> <p>DULUTH, MINN. Lew Bonn Company</p> <p>MINNEAPOLIS, MINN. Lew Bonn Company</p> <p>ST. PAUL, MINN. Lew Bonn Company</p> <p>Hi-Fi Sound</p> <p><b>MISSISSIPPI</b></p> <p>GULFPORT, MISS. Crescent Electronic Supply</p> <p><b>MISSOURI</b></p> <p>KANSAS CITY BA High Fidelity (2 locations)</p> <p>Burnstein-Appelbee Co. (2 locations)</p> <p>ST. LOUIS, MO. Radonics—Easton</p> <p>Radonics—Jefferson</p> <p>Radonics—West, Inc.</p> <p>Radonics—Gravois, Inc.</p> <p><b>NEW JERSEY</b></p> <p>ATLANTIC CITY, N.J. Radio Electric Service Co.</p> <p>CAMDEN, N.J. Radio Electric Service Co.</p> <p>MOUNTAINSIDE, N.J. Federated Purchaser, Inc.</p> <p>NEWARK, N.J. Federated Purchaser, Inc.</p> <p><b>NEW YORK</b></p> <p>ALBANY, NEW YORK Ft. Orange Radio Distributing Co.</p> <p>BATH, NEW YORK Rochester Radio Supply Co., Inc.</p> <p>BELLEROSE, NEW YORK Cross Island Electronics, Inc.</p> <p>BINGHAMTON, NEW YORK Stack Electronics, Inc.</p> <p>BROOKLYN, NEW YORK Acme Electronics, Inc.</p> <p>ELMIRA, NEW YORK Stack Electronics, Inc.</p> <p>FARMINGDALE, NEW YORK Gem Electronics Dist., Inc.</p> <p>FOREST HILLS, NEW YORK Beam Electronics, Inc.</p> <p>GENEVA, NEW YORK Rochester Radio Supply Co., Inc.</p> <p>HERKIMER, NEW YORK Herkimer Electronics Co., Inc.</p> <p>HICKSVILLE, NEW YORK Gem Electronics Dist., Inc.</p> <p>MINEOLA, NEW YORK Arrow Electronics, Inc.</p> <p>MT. VERNON, NEW YORK Davis Radio Distributing Co.</p> <p>NEW YORK, NEW YORK Arrow Electronics, Inc.</p> <p>Harvey Radio Company, Inc.</p> <p>ROCHESTER, NEW YORK Rochester Radio Supply Co., Inc.</p> | <p><b>NEW YORK (Cont.)</b></p> <p>SYRACUSE, NEW YORK Syracuse Radio Supply Co., Inc.</p> <p>UTICA, NEW YORK Genesee Electronics Company</p> <p>VALLEY STREAM, NEW YORK Elm Electronics, Inc.</p> <p>WATERTOWN, NEW YORK Watertown Electronics, Inc.</p> <p><b>NORTH CAROLINA</b></p> <p>CHARLOTTE, NORTH CAROLINA Southeastern Radio Supply Co.</p> <p>FAYETTEVILLE, NORTH CAROLINA Southeastern Radio Supply Co.</p> <p>GREENSBORO, NORTH CAROLINA Southeastern Radio Supply Co.</p> <p>KINSTON, NORTH CAROLINA Southeastern Radio Supply Co.</p> <p>RALEIGH, NORTH CAROLINA Southeastern Radio Supply Co.</p> <p><b>OHIO</b></p> <p>AKRON, OHIO Sun Radio Company</p> <p>CHILLICOTHE, OHIO Buckeye Electronics Dist., Inc.</p> <p>CLEVELAND, OHIO Pioneer Electronic Supply Co. (2 locations)</p> <p>COLUMBUS, OHIO Buckeye Electronics Dist., Inc.</p> <p>DAYTON, OHIO Sreppo, Inc.</p> <p>Ham'n Hi Fi, Inc.</p> <p>LORAIN, OHIO Pioneer Electronic Supply Co.</p> <p>MAPLE HEIGHTS, OHIO Pioneer Electronic Supply Co.</p> <p>NEWARK, OHIO Buckeye Electronics Dist., Inc.</p> <p>SANDUSKY, OHIO Pioneer Electronic Supply Co.</p> <p>SPRINGFIELD, OHIO Standard Radio-Springfield, Inc.</p> <p>TOLEDO, OHIO Lifetime Electronics</p> <p>YOUNGSTOWN, OHIO Radio &amp; TV Parts Company</p> <p>ZANESVILLE, OHIO Buckeye Electronics Dist., Inc.</p> <p><b>OREGON</b></p> <p>MEDFORD, OREGON Ver'l G. Walker Company</p> <p>PORTLAND, OREGON Eccles Electric Co.</p> <p>SALEM, OREGON Cecil Farnes Co.</p> <p><b>PENNSYLVANIA</b></p> <p>ALLENTOWN, PA. Federated Purchaser, Inc.</p> <p>EASTON, PA. Federated Purchaser, Inc.</p> <p>ERIE, PA. J. V. Duncombe Co. (2 locations)</p> <p>PHILADELPHIA, PA. Austin Electronics, Inc.</p> <p>Radio Electric Service Co. (3 locations)</p> <p>PITTSBURGH, PA. House of Audio</p> <p>WILLOW GROVE, PA. Radio Electric Service Co.</p> <p>YORK, PA. Radio Electric Service Co.</p> <p><b>RHODE ISLAND</b></p> <p>PROVIDENCE, R. I. Audionics, Inc.</p> | <p><b>SOUTH CAROLINA</b></p> <p>ANDERSON, S.C. Dixie Radio Supply Co. of Greenville</p> <p>CHARLESTON, S.C. Radio Laboratories</p> <p>COLUMBIA, S.C. Dixie Radio Supply Co. of Columbia</p> <p>FLORENCE, S.C. Dixie Radio Supply Co. of Florence</p> <p>GREENVILLE, S.C. Dixie Radio Supply Co. of Greenville</p> <p>SPARTANBURG, S.C. Dixie Radio Supply Co. of Greenville</p> <p>SUMTER, S.C. Dixie Radio Supply Co. of Columbia</p> <p><b>TENNESSEE</b></p> <p>JOHNSON CITY, TENNESSEE Chemistry Electronic Distributors</p> <p>KINGSFORD, TENNESSEE Chemistry Electronic Distributors</p> <p>KNOXVILLE, TENNESSEE Chemistry Electronic Distributors</p> <p><b>TEXAS</b></p> <p>BEAUMONT, TEXAS Sterling Electronics, Inc.</p> <p>BRYAN, TEXAS Sterling Electronics, Inc.</p> <p>DALLAS, TEXAS Hillcrest Records &amp; Hi Fi</p> <p>HOUSTON, TEXAS Sound Equipment, Inc.</p> <p>Sterling Electronics, Inc.</p> <p>LUFKIN, TEXAS Sterling Electronics, Inc.</p> <p><b>VIRGINIA</b></p> <p>ARLINGTON, VIRGINIA Key Electronics, Inc.</p> <p>NEWPORT NEWS, VIRGINIA Cain Electronics Co., Inc.</p> <p>NORFOLK, VIRGINIA Cain Electronics Co., Inc. (2 locations)</p> <p>PORTSMOUTH, VIRGINIA Cain Electronics Co., Inc.</p> <p>RICHMOND, VA. Meridian Electronics, Inc.</p> <p>ROANOKE, VA. McKnight Electronics, Inc.</p> <p><b>WASHINGTON</b></p> <p>SEATTLE, WASHINGTON Seattle Radio Supply, Inc.</p> <p>SPOKANE, WASHINGTON Northwest Electronics, Inc.</p> <p><b>WEST VIRGINIA</b></p> <p>BECKLEY, W. VA. Chemistry Electronic Distributors</p> <p>BLUEFIELD, W. VA. Meyers Electronics</p> <p>CHARLESTON, W. VA. Chemistry Electronic Distributors</p> <p>POINT PLEASANT, W. VA. Chemistry Electronic Distributors</p> <p><b>WISCONSIN</b></p> <p>LA CROSSE, WIS. Lew Bonn Company</p> <p>MADISON, WIS. Hi-Fi Corner</p> <p>Satterfield Electronics, Inc.</p> <p>MILWAUKEE, WIS. Hi-Fi Center</p> <p>PORTAGE, WIS. Satterfield Electronics, Inc.</p> <p>WISCONSIN RAPIDS, WIS. Satterfield Electronics, Inc.</p> |
|---|--|--|---|

New York Service Representative  
Empire State Electronic Serv., Inc.


180-14 Union Turnpike, Flushing 66, Long Island, New York



HEATH COMPANY / Benton Harbor, Mich.

a subsidiary of Daystrom, Inc.

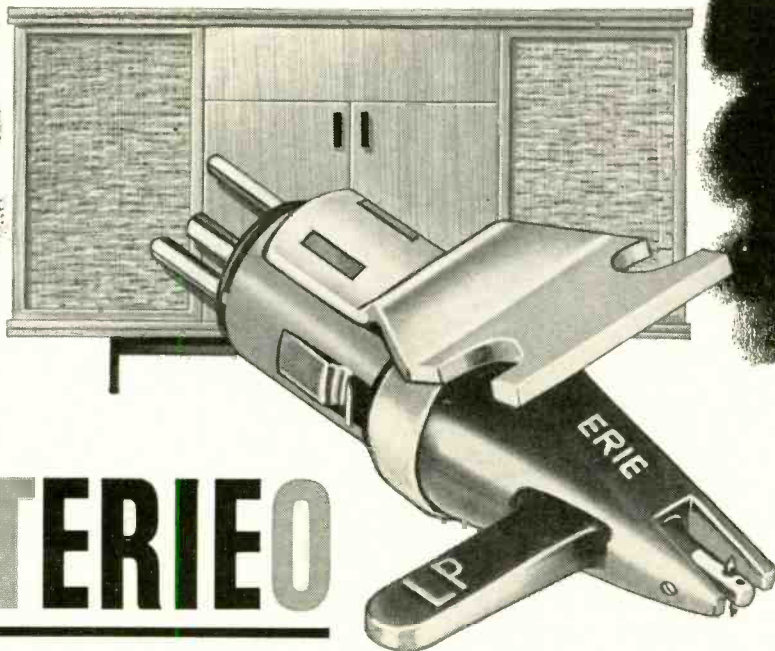Now used as original equipment  
by leading manufacturers



**STERIEO**

single-element **STEREO** cartridge

Take a tip from the audio engineers who design packaged stereo sets. For your stereo work or stereo fun—replacement or conversion, specify the STERIEO ceramic cartridge.

There are good reasons why STERIEO is supplied as original equipment on the sets of several leading manufacturers. Balanced channel outputs are inherent in STERIEO's single-element design, and highly effective channel separation is assured by its unique insulator-conductor construction.

In engineering tests STERIEO's full frequency response delivers the full dimensional sound so important to a fine stereophonic system.

Ask for STERIEO at your electronic or audio parts store. Replacement unit as low as \$6.95 list, and conversion kit as low as \$8.95 list. (Dual stylus—sapphire/sapphire; diamond stylus slightly higher.)

For where-to-buy information write to:

**ERIE Electronics Distributor Division**  
**ERIE RESISTOR CORPORATION**  
Erie, Pennsylvania

## TELEVISION

tube. If the grid voltage measures less negative than normal, a leaky capacitor or gassy tube is indicated. Measure the voltage at either end of the grid load resistor. It should read the same at both points with respect to ground. If not, keep the voltmeter connected to the grid of the tube and remove the tubes on either side of the coupling network. If the bias voltage on the grid still remains less negative than normal, the coupling capacitor is defective and should be replaced. If the voltmeter gives a normal reading after the tubes have been removed, check for a gassy tube by replacing it with one known to be good. If, after replacing the tube, the bias still remains at an abnormal value, resistance tests must be made. Turn off the receiver and allow sufficient time for the tubes to cool off. Then measure the plate, screen, grid and decoupling resistors for a change in value. A deviation up to 10% of the manufacturer's stated values is considered normal. Other possible causes of oscillation are open heater or screen bypass capacitors or an open decoupling capacitor in the plate or grid circuits. Also be sure to check the lead dress—some receivers are very critical. The plate and grid leads must be kept as far apart as possible to prevent undesirable feedback.

The source of trouble is usually found to be a leaky, open or shorted capacitor or a resistor that has changed in value. If none of these defects appear, measure the resistance from grid to ground. It should correspond to the value of the grid load resistor. If it doesn't, remove the leads from the grid terminal and measure the resistance from the terminal to ground. The resistance meter should give an infinite resistance reading—if not, the socket must be replaced, preferably with a low-loss unit. The author has run into this heart-breaking TV oddity several times. It's a real puzzler to the service technician who is unaware of its possibility.

Fortunately, oscillation in video if circuits is not too common a problem. When it does occur, the troubleshooting procedure outlined here may help the service technician to correct the trouble quickly and efficiently. **END**



**W**IDE-BAND TV service oscilloscopes have frequency-compensated step attenuators (Fig. 1). Unless the compensating trimmer capacitors C1, C2 and C3 are properly adjusted, waveform displays will be distorted.

The simplest method of checking the compensating adjustments is shown in Fig. 2. A 20-kc sawtooth voltage is tapped off at a point of suitable level in the scope's horizontal amplifier and fed to the vertical input terminal.

A diagonal-line pattern appears on the scope screen, as seen in Fig. 3-a. The trimmer capacitor on each step of the attenuator is adjusted to display a straight line. Too high a value of compensating capacitance produces the pattern shown in Fig. 3-b. The effect of too little is shown in Fig. 3-c.

Avoid overload. As Fig. 3-d shows vertical amplifier overload will produce kinks at the ends of the line. For this reason, the tapoff point in the horizontal amplifier must be properly chosen.

The same method can be used to adjust the trimmer capacitor in a 10-to-1 low-capacitance probe (Fig. 4). The trimmer is adjusted to display a straight diagonal line on the screen.

Accuracy of this method depends upon freedom from distortion in the scope amplifiers. If the amplifiers distort, different waveforms are applied to the vertical and horizontal plates of the CRT.

Amplitude distortion is plainly evident. On the other hand, frequency distortion is trickier. The sawtooth sweep rate, in any case, should not be increased past the point that waveform displays may show horizontal non-linearity, as illustrated in Fig. 5.

**Lead-in cables**


*We are installing a three-outlet antenna system in a new home constructed of adobe, with cement-slab*

*floors. The contractor has recommended putting 300-ohm ribbon in a plastic tube and laying it in the cement floors. We are in a fringe area, and our signal levels run from 50 to 100  $\mu$ v. However,*


*if we could do this, it would certainly simplify the installation. What results could we expect from it?—E. L. P., Escondido, Calif.*

You can run the lead-in cable through the cement floors if you wish, but I'm afraid that your losses would be quite prohibitive with standard 300-ohm twin-lead, even encased in plastic tubing. I assume this to mean standard electrical conduit, made of plastic. I believe you will have to use coaxial cable for this, which must still be run through the plastic (or metal, in this case) conduit.


You can get a very neat installation if you run the conduit up through the walls to the point where the tapoff is to be located, and terminate it (the conduit) in a standard electrical outlet box. As the coax is 72-ohm, impedance-matching transformers will have to be used. Jerrold, Blonder-Tongue and many others make 72-300-ohm matching transformers designed to fit standard electrical outlet boxes complete with plastic covers in any color de-

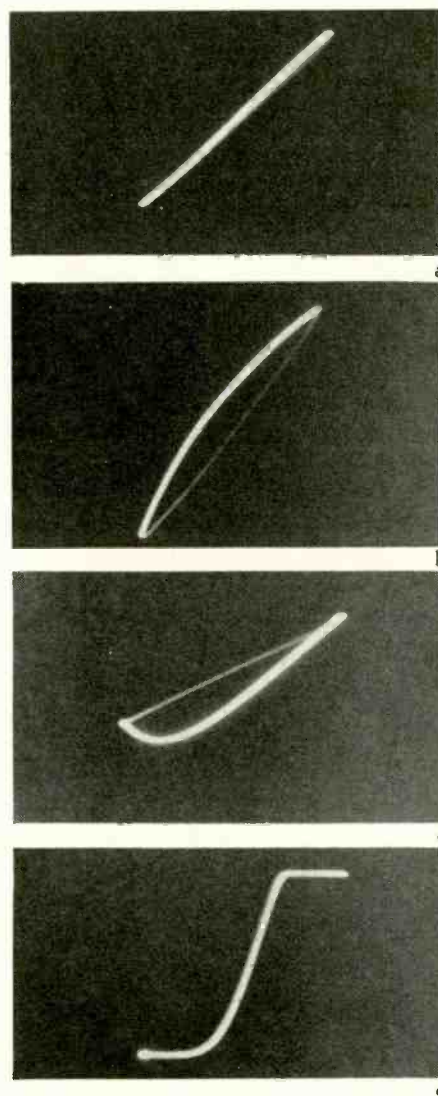


**Fig. 3—**Waveforms seen on scope screen indicate compensation of step attenuator: a—correct compensation; b—too much compensating capacitance; c—too little compensating capacitance; d—vertical amplifier overloaded, too much input voltage.

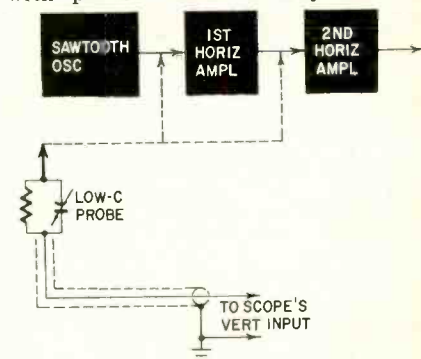


**Fig. 4—**A low capacitance probe can be adjusted with the help of a sawtooth voltage.

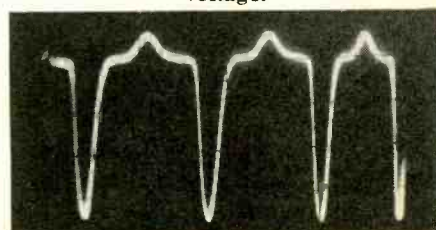

**Fig. 5—**Waveform display showing horizontal nonlinearity.

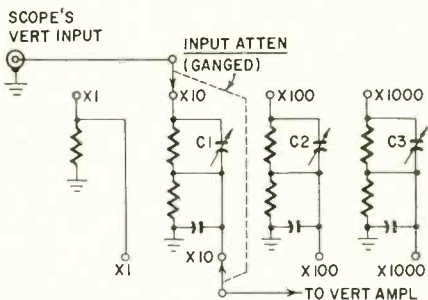

**Fig. 1—**Typical compensated step attenuator for a wide-band scope.

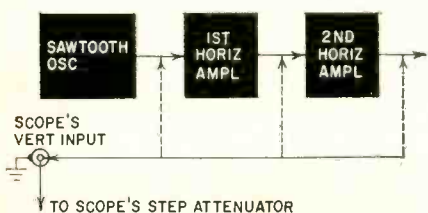

**Fig. 2—**Sawtooth voltage of suitable value is tapped off scope's sawtooth oscillator and fed to its vertical input.

# Build This Superb *Schober* Organ From Simple Kits and SAVE OVER 50%!



LET US SEND YOU FREE DETAILS HOW TO ASSEMBLE A *Schober* ELECTRONIC ORGAN IN SPARE TIME!

The Beautiful *Schober* CONSOLETTA — the only small organ with two full 61-note keyboards and 22 stops. Requires only 2' x 3'2" floor space! Commercial value approximately \$1600 or more — yet you save over 50% when you build this thrilling instrument!

Give Your Family A Lifetime of Musical Joy With A Magnificent Schober ELECTRONIC Organ!

Now you can build the brilliant, full-range Schober CONSOLETTA or the larger CONCERT MODEL with simple hand tools. No skills are necessary to construct an instrument with one of the finest reputations among electronic organs. No woodworking necessary — consoles come completely assembled and finished. All you do is assemble clearly marked electronic parts guided by clear illustrations and detailed step-by-step instructions. Even teen-agers can assemble the Schober! You build from kits, as fast or as slowly as you please... at home, in spare time — with a small table serving as your entire work shop!

Send For Complete Details On Schober Organs and For Hi-Fi Demonstration Record The coupon will bring you a handsome 16-page booklet in full color describing Schober organs in detail, plus articles on how easy and rewarding it is to build your own organ and how pleasant and quick it is to learn to play the organ. In addition, we have prepared an exciting 10" hi-fi LP record demonstrating the full range of tones and voices available on the Schober, which you may have for only \$2.00 (refunded when you order a kit). Literature on the Schober is FREE! There is no obligation; no salesman will call.

THE GREAT CONCERT MODEL meets specifications of American Guild of Organists

Pay As You Build Your Organ; Start With As Little As \$18.94! You may start building your Schober at once with an investment of as little as \$18.94. The musical instrument you assemble is as fine, and technically perfect, as a commercial organ built in a factory — yet you save over 50% on top-quality electronic parts, on high-priced labor, on usual retail store mark-up! In your own home, with your own hands you build an organ with *genuine pipe organ tones* in an infinite variety of tone colors to bring into your home the full grandeur of the Emperor of Instruments. You may build the CONSOLETTA for your home, or you may want to build the great CONCERT MODEL for home, church, school or theatre. You save 50% and more in either case.



Mail This Coupon For FREE Literature and Hi-Fi Record Today!

The Schober Organ Corp., Dept. RE-3, 2248 Broadway, New York 24, N. Y.

Please send me FREE full-color booklet and other literature on the Schober organs.

Please send me the 10" hi-fi Schober demonstration record. I enclose \$2.00 (refundable on receipt of my first kit order).

Name.....

Address.....

City..... Zone..... State.....

## TELEVISION

sired and a plug-in connection for the lead-in to the set.

With the signal level you mention, a booster amplifier will be needed near the antenna to raise the signal to a snow-free level, and to make up for the small additional loss incurred by the use of the coax. However, there are distribution amplifiers, such as the Blonder-Tongue DA8-B, which are built specifically for just such applications. This amplifier has a gain of about 10 db, and can supply as many as 8 outlets from a single input. The DA8-B has both 300- and 75-ohm outputs.

For the cable, probably RG59U would be the best and easiest to handle. This cable has a nominal impedance of 73 ohms, and an outside diameter of only 1/4 inch. It can be fished through standard 1/2-inch electrical conduit with ease. If there is insufficient gain, an antenna booster, like the Jerrold DeSnower or Blonder-Tongue AB-1, with about 26-db gain over all vhf channels will help out greatly.

With careful workmanship, this should make a very neat installation.

## Voltage and current waveforms

Why is a voltage waveform different from a current waveform? The book I have on scopes doesn't explain this.— A. M., Windsor, Ont.

A voltage waveform is not different from a current waveform when working with sine waves. On the other hand, when working with complex waves, voltage and current waveforms will always differ in reactive circuits (Fig. 6).

The square wave is a complex wave. It contains a large number of sine waves. In the R-C circuit, each harmonic in the square wave flows as if it alone were present. The high-frequency harmonics are practically short-circuited by the capacitor. Their voltage is accordingly impressed across the resistor. On the other hand, the low-frequency harmonics are practically blocked by the capacitor, and their voltage is impressed across the capacitor. Thus, the waveform across the resistor is the sum of the higher-frequency harmonics in the square wave. The waveform across the capacitor is

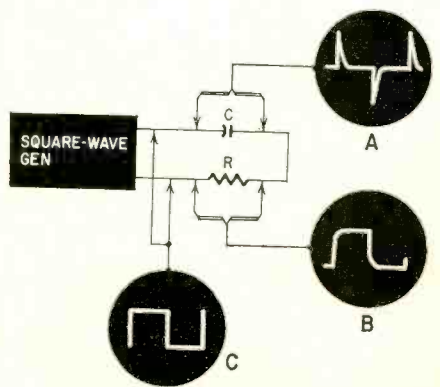


Fig. 6—A is a voltage waveform and B is a current waveform. If we add them, we get the square wave C.




## TELEVISION

the sum of the lower-frequency harmonics. If you add the waveforms across capacitor and resistor, you recover the original square wave. Any attempt to break the law (Kirchhoff's) will fail. In other words, we could have fallen back on Kirchhoff's law to deduce the complementary shapes of waveforms across resistor and capacitor. Let us look at the circuit again, from the standpoint of voltage and current. The waveform across the resistor shows the current flowing into and out of the capacitor. The waveform across the capacitor shows the voltage drop across it. Current and voltage waveforms accordingly differ in the reactive circuit driven by a complex voltage.

### Burning resistors

*I am servicing a Packard-Bell 2301 in which the voltage-doubler resistors burn out after several hours of operation. Voltages are OK in the flyback circuit. Higher wattage resistors have been tried.—A. R. S., Seattle, Wash.*

There is evidently excessive current drain through the 1-meg resistors (Fig.

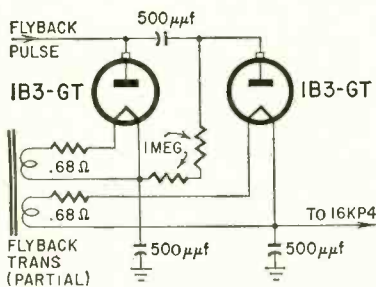

**Fig. 7—**The 1-meg voltage-doubler resistors will overheat if excessive current is drawn from the high-voltage power supply.

7). Check operation with the high-voltage lead disconnected from the 16KP4. The tube may be drawing excessive current. However, if the resistors still burn out, the 500- $\mu$ f capacitors should be checked for leakage. A rough check can be made by disconnecting each capacitor in turn. If the resistors still overheat, check the insulation resistance between the 1B3-GT filament windings and the transformer assembly.

### Transient oscillation

*We've an RCA KCS-68C chassis which was worked on for a complaint of no high voltage. Replacing a small capacitor in the horizontal oscillator circuit restored the high voltage and the set was delivered. In about a week it was back in the shop. The customer said the picture suddenly pulled in about 4 inches on each side. We've checked all parts in the horizontal sweep and oscillator circuit and all voltage readings seem OK. A puzzling thing to us: if we touch the cap of the 6CD6 with a screwdriver picture width returns to normal! The picture is good, except for the width.—W. S., Detroit, Mich.*

Your clue is that touching the hori-

1500  
servicemen  
told us\*



Perma-Power

VU-BRITES

BRIGHTEN  
THE BUSINESS  
PICTURE, TOO!

1500 servicemen recently gave us their good *business* reasons for choosing Perma-Power Vu-Brites. You and your colleagues told us that your customers invariably had confidence in the neat-looking product and the attractive package . . . and were pleasantly surprised by the low price (\$9.95 the dozen, net). Result: no sales resistance—a happy satisfied customer who is sure to call back next time—virtually guaranteeing you a highly profitable picture tube sale.

Of course, you have a lot of other good reasons for choosing Perma-Power Vu-Brites. One outstanding reason is that you've never found a defective one. That's because Perma-Power Vu-Brites are engineered for quality, and 100% tested. They instantly restore brilliance and clarity to fading TV pictures. You can use them on either electro-static or electro-magnetic picture tubes, Model C-401 in Series sets, Model C-402 in Parallel sets.

Perma-Power also makes a full line of special purpose briteners, tube restorers, and accessories, all described in our latest catalog, available free from your distributor, or by writing direct to us. Don't say "brightener," say "Perma-Power" . . . the standard of all comparison.

\* on their entry blanks in Perma-Power's Las Vegas contest.

Perma-Power COMPANY

3100 N. ELSTON AVENUE • CHICAGO 18, ILL.

ALWAYS INSIST  
ON PROVED  
BRAND NAMES

Ask By Name For  
GENUINE

"NOISE"

PRODUCTS

BEWARE OF  
CHEAP  
SUBSTITUTES

NO-NOISE

TUNER-TONIC

With PERMA-FILM

- Economical—a little does a lot.
- Cleans, lubricates, restores all tuners, including wafer type.
- Non-toxic, non-inflammable.
- Use for TV, radio and FM.

6 Oz. Aerosol Can

\$3.25

NET to Servicemen



NO-NOISE  
VOLUME CONTROL  
and  
CONTACT RESTORER

• Cleans • Lubricates • Protects  
NOT A CARBON TET  
SOLUTION

2 Oz. Bottle \$1.00

6 Oz. Spray Can \$2.25

NET to Servicemen

NOW AVAILABLE

FREE

AT YOUR JOBBERS

5" PLASTIC  
EXTENDER



With Push  
Button  
Assembly  
For Pin-  
Point Ap-  
plications


Does Not  
Cause  
Shorts

ELECTRONIC CHEMICAL CORP.

813 Communipaw Avenue Jersey City 4, N. J.

These men are getting practical training in...

# ELECTRICITY ELECTRONICS

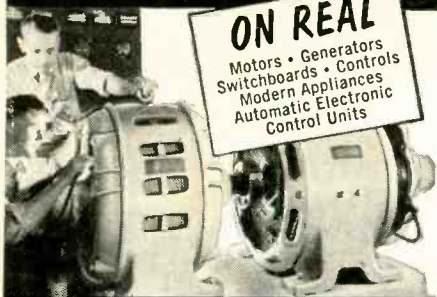

# TELEVISION RADIO ELECTRONICS



## Train in NEW Shop-Labs of COYNE

in Chicago—Electrical and Electronic Center of the World. Prepare for a better job and a successful future in a TOP OPPORTUNITY FIELD. Train on real full size equipment at COYNE where thousands of successful men have trained for 60 years—largest, oldest, best equipped school of its kind. Professional and experienced instructors show you how, then do practical jobs yourself on more than a quarter of a million dollars worth of equipment. No previous experience or advanced education needed. Employment Service to Graduates.

Start Now—Pay Later—Liberal Finance and Payment Plans. Pay most of tuition after graduation. Part-time employment help for students. Choose from nine yearly Starting Dates.

Mail Coupon or Write to Address Below for Free Book—"Guide to Careers." Whether you prefer ELECTRICITY, TELEVISION-RADIO or COMBINED ELECTRONICS, which includes both fields, this book describes all training offered.

Information comes by mail. No obligation and NO SALESMAN WILL CALL.

B. W. Cooke, Jr., Pres. Founded 1899  
**COYNE ELECTRICAL SCHOOL**  
 Chartered as an Educational Institution Not For Profit  
 1501 W. Congress Pkwy., Chicago 7, Ill., Dept. 20-5c

**MAIL COUPON** OR WRITE TO ADDRESS BELOW

COYNE ELECTRICAL SCHOOL  
 New Coyne Building Dept. 20-5C  
 1501 W. Congress Pkwy., Chicago 7, Ill.

Send BIG FREE book and details of all the training you offer. I am especially interested in,

Electricity  Television  Both Fields

Name.....  
 Address.....  
 City..... State.....  
 (I understand no Salesman will call)

## TELEVISION

zontal output tube plate cap with the screwdriver brings back the width. It looks as if you have a case of parasitic oscillation in the 6CD6 plate circuit. Touching the cap is adding enough capacitance to damp out these oscillations. This circuit includes a very small capacitor, a 33- $\mu\text{f}$  unit connected across two terminals on the flyback. Since this is inside the high-voltage housing on this set, did you check it? You might try taking scope waveforms around the high-voltage circuit, using either a very low-capacitance probe or very loose coupling to the horizontal output tube plate lead to see if you can detect any unusual waveforms.

I believe that replacing the 33- $\mu\text{f}$  capacitor on the flyback will stop your trouble. If not, try adding 100-ohm resistors in the plate and screen grid leads of the 6CD6. You might also check the width link on the back of the chassis. We have found several cases where the link had corroded and was not making good connections. Clean it up and check the 180- $\mu\text{f}$  capacitor the link connects across the width coil. You might also try adding about 150-200  $\mu\text{f}$  across this capacitor. Also try adding a 100- $\mu\text{f}$  capacitor, rated at least 5 kv, from terminal 2 on the flyback to the chassis.

### First and second detectors

What is the difference in operation between the first detector and the second detector? Both act as nonlinear devices, as both produce beat frequencies. The second detector also cuts off the negative portion of the video if signal. Hence, the first detector also cuts off the negative swing of the if signal. Why detect the if signal, when it has already passed through the first detector?—O. T., Los Angeles, Calif.

The first detector (mixer) and the second detector (picture detector) are both nonlinear resistances. It is helpful

through the video amplifier, the 23-mc (or 45-mc) if signal must be rectified in the picture detector. The output from the picture detector is a low-pass filter, with a response from dc to 4.5 mc (Fig. 8).

### Double trouble

I have a couple of questions. A Philco 51T 2130 TV I am working on comes on with a Christmas-tree effect for a few seconds, then the picture snaps into sync. Also, after it has been on for about 5 minutes, it begins to pull horizontally, tearing the picture at times. Then the vertical pulls down slowly out of sync. When I put a .004- $\mu\text{f}$  capacitor on pin 6 of the video amplifier (12AV7) or pin 6 of the 12AU7 second sync separator, the picture locks in perfectly. What is the reason for this?—E. J. S., St. Louis, Mo.

Here we are again concerned with the correct adjustment of the horizontal oscillator. Your Philco uses a stabilized multivibrator. The effect has several names: Christmas-treering, mode-hopping, squegging, etc., but it is all the same thing. The horizontal oscillator is trying to operate (momentarily) at the wrong frequency and the correction circuit is yanking it back on frequency bodily! This is happening several times per second, causing the peculiar effect. I would suggest running a complete realignment of the horizontal oscillator circuit. If this chassis has the extra horizontal oscillator centering control (some runs in this series did, others did not) adjust it so the oscillator will run and lock a picture in with the ringing coil shorted out. Then adjust the ringing coil for a stable picture.

The other trouble is obviously sync. From the symptoms, it seems that video is leaking into the sync. Replace the 12AV7 sync amplifier no matter how it tests on a tube tester! These tubes are very critical in the circuit used here.

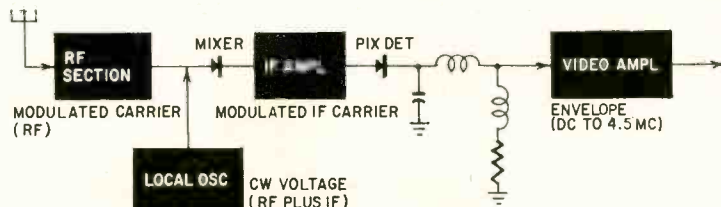


Fig. 8—Both the mixer and the pix detector are rectifiers. However, the mixer passes a difference beat frequency to the if amplifier, while the pix detector passes the modulation envelope to the video amplifier.

to regard the mixer from the standpoint of generating a difference frequency (the difference between the rf and the local-oscillator frequency). This is a frequency translation. The fact that rectification occurs in the mixer is beside the point. The if amplifier is tuned to the difference frequency (23 or 45 mc), and the video-frequency component is rejected. Of course, we can see this video-frequency component if we connect a scope to the "looker point" on the tuner. Now, the if signal is still a high-frequency modulated carrier. Before the modulation envelope can be passed

Also, check the plate load resistors for each stage—sync and video amplifier—and the small coupling capacitors between each stage. If any of these has even the slightest leakage, it will change the bias on the sync separators and really fix things up for you!



In some versions of this circuit, a small capacitor was installed between the 12AV7 input grid and the chassis. It bypassed some of the signal's high-frequency video component and improved sync action. If it gives a permanent improvement, put a small capacitor there and leave it. Try several

# SAVE $\frac{1}{2}$ THE TIME
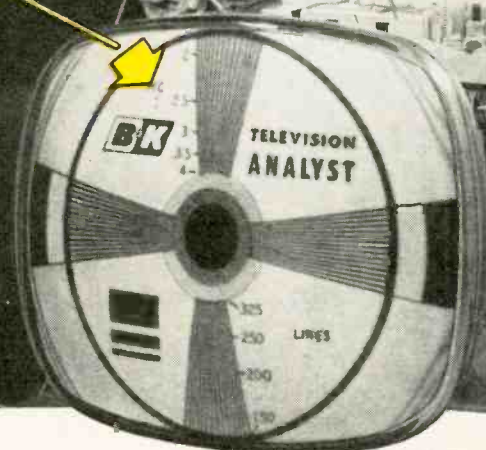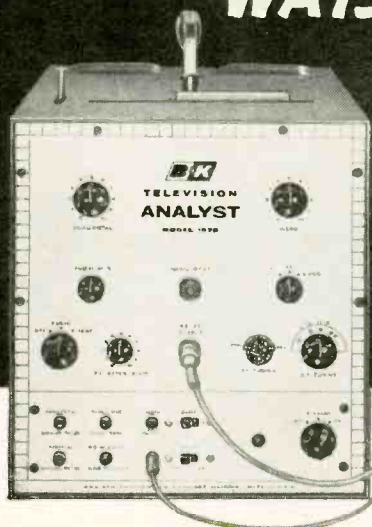
## Make Twice The Profit!

in TV  
Trouble-Shooting

**THIS EASY**  
SIGNAL INJECTION  
POINT-TO-POINT  
DIRECT VIEWING  
**WAY**



## MODEL 1075 TELEVISION ANALYST

Solve Rough Sweep Output Problems



### NEW Model A107 DYNA-SWEEP CIRCUIT ANALYZER

Solves many hours of service work. Provides vertical and horizontal sync and driving pulses that enable you more easily and quickly to check out every stage in the sync and sweep sections of a television receiver.

Tracks down troubles in the horizontal and vertical output circuit including defective output transformer and yoke; checks for shorted turns, leakage, opens, short circuits, and continuity. Includes unique high-voltage indication. Eliminates trial and error replacements.

**Model A107 Dyna-Sweep.** Companion unit for use only with B&K Model 1075 Television Analyst for driving source.

Net, \$49.95

**Model 1070 Dyna-Sweep.** Same as Model A107 but has its own horizontal and vertical driving pulse, and is used independently of the Model 1075.

Net, \$69.95

### New Technique Makes TV Servicing Easier, Faster, More Profitable

Thousands of service technicians already save thousands of hours every day with the amazing B&K TELEVISION ANALYST. Enables you to inject your own TV signal at any point and watch the resulting test pattern on the picture tube itself. Makes it quick and easy to isolate, pin-point, and correct TV trouble in any stage throughout the video, audio, r.f., i.f., sync, and sweep sections of black & white and color television sets—including intermittents. Makes external scope or wave-form interpretation unnecessary. Enables any serviceman to cut servicing time in half, service more TV sets in less time, really satisfy more customers, and make more money. Color generator provides both rainbow pattern and color bars.

**MODEL 1075 TELEVISION ANALYST.** Complete with standard test pattern, white dot, white line, and color-bar slide transparencies, and one clear acetate. Net, **\$259<sup>95</sup>**

See your B&K Distributor or Write for Bulletin ST24-E




**B & K MANUFACTURING CO.**

1801 W. BELLE PLAINE AVE • CHICAGO 13, ILL.

Canada: Atlas Radio Corp., 50 Wingold, Toronto 10, Ont.  
Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.



NEW HIGH FIDELITY DRIVERS  
of great importance to technicians

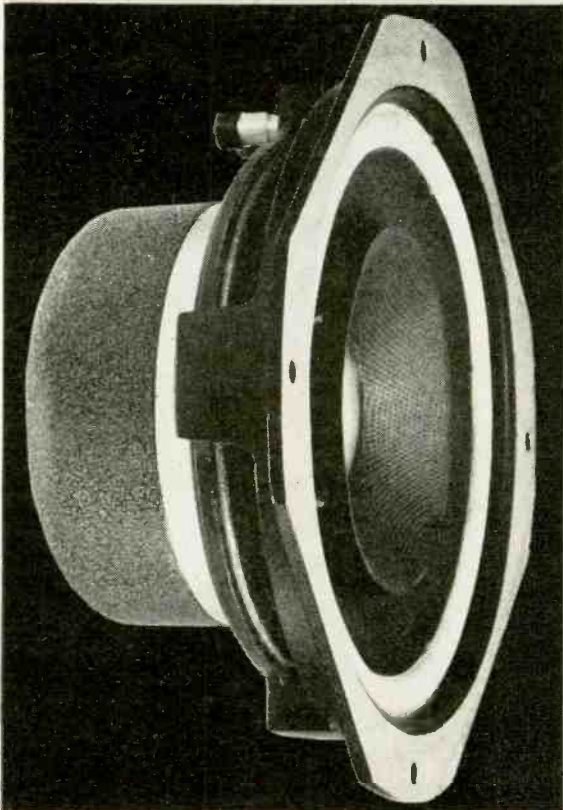**JBL**  
LINEAR-EFFICIENCY  
PRECISION LOUDSPEAKERS



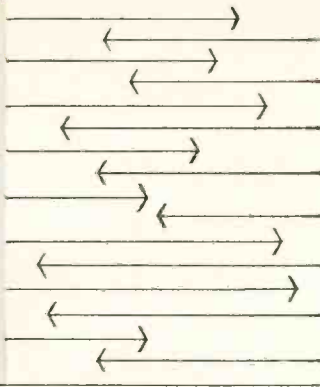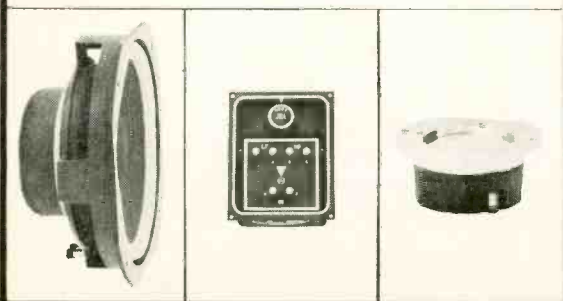**TWO-WAY LINEAR-EFFICIENCY SYSTEM KIT**

JBL MODEL S5 includes a super 10" JBL MODEL LE10 Low Frequency Driver with free air cone resonance of 15 c.p.s.; JBL MODEL LX3 Dividing Network for crossover at 1,000 c.p.s.; JBL MODEL LE30 High Frequency Driver, a 5 1/2 octave direct radiator. These three units form an integrated, perfectly matched, electro-acoustical system; they must be used with each other.



The new JBL Linear-Efficiency transducer, combining long linear excursion with relatively high efficiency, is engineered for sealed enclosure or infinite baffle installation. It is a development of great significance to the electronic technician because:

... it is an ideal replacement speaker;  
... it can be readily mounted in a wall;

... it gives true precision reproduction in the small space frequently required in stereo installations;

... it does not require excessive power for full-range reproduction.

Sound from any existing system, except those employing the very best loudspeakers, can be greatly improved, easily, with the JBL Linear-Efficiency speaker because enclosure dimensions are not critical, and acoustical requirements can be readily met. The mounting flange is designed so that the speaker can be mounted from the front, or the rear, of the baffle—wall or enclosure. An enclosed volume of only two cubic feet, or more, is recommended.

The efficiency of the LE drivers is such that 20 watts is more than sufficient power for home use. However, the dynamic range of these long-throw speakers permits the use of much more powerful amplifiers.

Super 8" JBL MODEL LE8 (illustrated left) shows a flatness of response from 30 to 15,000 c.p.s. that is without precedent in a unit of this size. Impedance: 16 ohms. Flux: 223,500 Maxwells. Power capacity: 20 watts continuous program. Free air cone resonance: 37 c.p.s. Frame: rigid cast aluminum. Baffle hole diameter (front mounting): 7 1/8". Shipping weight: 11 lbs.

Write for free technical bulletins



JAMES B. LANSING SOUND, INC.  
3249 Casitas Avenue  
Los Angeles 39, California

**TELEVISION**

values, around 100–500  $\mu\text{f}$ , and use the one that gives the best sync locking.

**Anti-ringing capacitor**

Why does a 56- $\mu\text{f}$  capacitor across the high side of the horizontal deflection coils minimize ringing bars?—H. B., Palisade Park, N. J.

During flyback, a 10- $\mu\text{sec}$  pulse of several hundred volts is applied to the horizontal yoke windings. The pulse waveform has a high harmonic content.

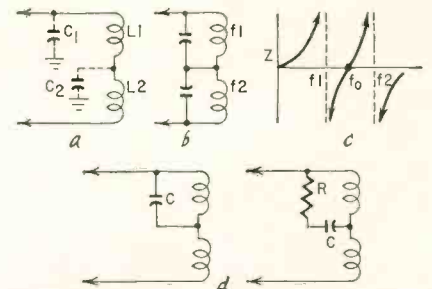


Fig. 9—Yoke ringing: a—Yoke windings L1 and L2 are tuned to parallel resonance by stray capacitances C1 and C2; b—equivalent yoke circuit is that of two parallel-resonant circuits connected in series; c—Whenever two parallel-resonant circuits (having different resonant frequencies) are connected in series, there is a series-resonant frequency  $f_0$  between parallel-resonant frequencies  $f_1$  and  $f_2$ ; d—Small capacitor C (left) or capacitor and resistor (C and R) (right) are used to tune the higher-frequency coil to the same resonant frequency as other coil. R is damping resistor which makes adjustment less critical.

The horizontal windings (L1 and L2 in Fig. 9) are tuned by stray capacitances C1 and C2. The windings are loosely coupled, and form a pair of parallel-resonant circuits, connected in series with each other. That is, we have the equivalent circuit shown in Fig. 9-b, resonant at two slightly different frequencies,  $f_1$  and  $f_2$ . Whenever two such circuits are connected in series, the impedance curve shows a series-resonant frequency  $f_0$ , between  $f_1$  and  $f_2$ , as indicated in Fig. 9-c. When pulsed, strong ringing occurs at the series-resonant frequency—Z is low and this harmonic frequency causes a strong current flow at  $f_0$ . As shown in Fig. 9-d, we use a small capacitor, or capacitor and resistor, to tune both windings to the same frequency, and eliminate  $f_0$ .

**16- to 21-inch screen**

I would like to convert a Sentinel 1U416.416 and an Arvin 3160 to a 17- or 21-inch picture tube. The Sentinel now has a 16GP4, and the Arvin is using a 16AP4.—H. K. L., Chicago, Ill.

A 21EP4 can be swept satisfactorily by the Sentinel chassis. No component changes are required, although the picture will be a bit dimmer on the larger screen. Converting the Arvin chassis may require a change of flyback and yoke, depending upon whether adequate high voltage is available, and whether the present yoke is a 70° type. END

# fm tv dx

Part II

## in 1959

By ROBERT B. COOPER, Jr.

**F**M dxer Bruce Elving still maintains his comfortable lead in the run for top honors in the FM dxing ranks with a whopping total of 346 FM stations heard in Duluth, Minn. But even with this tremendous total, Elving managed to log 14 new dx hauls in one short 26-hour period—Aug. 18–19. Elving found many Ohio, Michigan, New York and Pennsylvania FM stations rolling into his Duluth location—600–800 miles.

Wayne Baer, Meyersville, Pa., is another ardent FM dxer, and a pretty good hand with weak signals in the video range, too. Baer's report of WHAD-FM, Delafield, Wis., on Sept. 11 is one of several FM dx hauls noted during the year in which one or two FM stations in the 400–700-mile range snuck in while no other signs of FM dx were present. WHAD-FM is 575 miles from dxer Baer.

And TV dxer David Beal of Tucson

uses a 1947 model FM tuner to do his dxing. His list of 24 FM calls includes 20 E-skip stations logged during the last 6 weeks of the TV dx skip season this summer.

Oct. 9–10, 1959

Followers of the regular TV and FM Dx column will remember the excitement passed on from this desk to dxers regarding the expected potential of the Oct. 9–10 period as a very unusual meteor shower date. It was scheduled for the reappearance of the Giacobinids meteor shower, associated with the 13-year orbital pattern of the Draconid comet. During the comet's last pass close to earth in 1946, astronomers recorded a very vivid meteor display. Therefore, astronomers and ionospheric physicists assumed this year's scheduled return of the 13-year comet would bring a recurrence of the 1946 display.

But sadly, nothing or very little, if

anything, occurred. The shower was not only poor, it was almost nonexistent as showers go.

But despite all the lost sleep, at least one dxer considered his efforts well rewarding. John Cody, dxing from Middletown, Conn., did see a few good bursts. Cody, like so many others, felt the high-band channels deserved the most watching, and watch he did. First from 6 am to 4 pm EST on the 9th and then, after a rest, back at the dials from 1:30 am until 9 am on the 10th—17.5 hours of dial twisting and blank screen watching which netted him a new station and much experience.

Even with the burst count running below an average shower count, but slightly above normal, Cody nabbed high-bander WLOF-TV, channel 9, Orlando, Fla., 1,150 miles. WLOF-TV was logged on two bursts, the first at 3:43 am, the second at 3:55 am. And we emphasize that this was done during a time segment when burst counts (the number of meteor bursts per minute) were only average.

WLOF-TV was helping those observing the expected shower by staying on with test pattern and tone (dx tests like this, and others, will be one of the many regular features of the new hobby magazine, *TV-FM Dxing Horizons*). Although 17.5 hours may seem like a lot of hours to watch for two short bursts from one new station, to dxer Cody and hundreds like him it is

# IT'S THE NEW MARK II FROM WESTON:



an advanced new design for the  
WORLD'S FINEST PORTABLE ANALYZER

Here's an all-new version of the famous WESTON MODEL 980 Volt-Ohm-Milliammeter . . . engineered to offer you

- **INCREASED RANGE.** High-voltage range has been extended to 4000 volts.
- **INCREASED SENSITIVITY.** D-C sensitivity of 20,000 ohms/volt; accuracy within 2% of full scale.
- **IMPROVED SHIELDING.** Cormag® mechanism assures positive magnetic shielding; housing shields against electrostatic interference.
- **GREATER RUGGEDNESS.** Spring-backed jewel movement resists shock, vibration; case is impact-resistant. Ohm-ranges are fuse-protected.
- **SIMPLIFIED CONTROL.** Single dial control for range and function switching.
- **NEW COMPACTNESS.** Size and weight are reduced for maximum convenience and portability.

## WESTON

*Instruments*


WORLD LEADER IN MEASUREMENT AND CONTROL

Order from your local Weston distributor. For information, write to Daystrom-Weston, Sales Division, Newark 12, N. J. In Canada: Daystrom, Ltd., 840 Caledonia Rd., Toronto 19, Ont. Export: Daystrom Int'l., 100 Empire St., Newark 12, N. J.



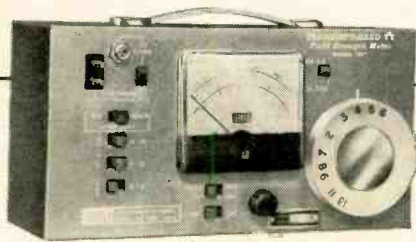**Now!**

**Checking Signal Strength *Anywhere*  
... IS AN EASY ONE-MAN JOB!**



**JERROLD**

**MODEL  
TMT**

**Direct Reading**

**TRANSISTORIZED  
FIELD STRENGTH METER**

*only \$135. net weatherprotecting leather carrying case, \$12.95 net*

Now you can measure *exactly* how much signal is in the area, coming off the antenna, coming off the down lead and is at the set! Just 4½ pounds of rugged instrument, the radically new Jerrold TMT responds only to the TV sync signal to which it is tuned and is therefore immune to noise . . . carries its own power supply (4 simple "c" batteries). Tailor-made for the professional television serviceman and systems technician, the TMT:

- provides accurate ( $\pm 3$  db) signal strength readings
- reads *directly*, not relatively in microvolts (100 to 2,000,000) in 8 switchable ranges
- for probing and orienting antenna signals and measuring distribution systems
- checks horizontal synchronizing frequencies in TV receivers

**JERROLD** ELECTRONICS CORPORATION, Distributor Sales Division  
 PD 188 The Jerrold Building, Philadelphia 32, Pa.  
 Jerrold Electronics (Canada) Limited, Toronto  
 Export Representative: CBS International, New York 22, N.Y.

**TELEVISION**

time well spent for such a rare catch.

**TV dxer of the year**

In last year's tabulated standings of the members of the Over 50 TV Dx Club, dxer John Cody was 9th with 165 calls to his credit. At that time, Cody was fast approaching the point where additional new loggings would come slowly, especially from a location where he sits with his back virtually to the Atlantic, and only 180° of horizon available for dxing purposes. So Cody turned to meteor scatter, watching the high band almost exclusively when the low band was jumping with burst signals from stations 700 to 1,200 miles distant, and his high-

**1959-60 OVER 50 DX CLUB**

Number of Stations	Dxer	Location
282	Barney Rauch	Peoria, Ill.
249	David Janiowak	Milwaukee, Wis.
218	John Cody	Middletown, Conn.
201	Bill Eckberg	Walnut, Ill.
185	Gary Ehresman	South Bend, Ind.
172	Bob Cooper	Modesto-Fresno, Calif.
161	James Gould	Kokomo, Ind.
160	Jim Himes	Joes, Colo.
159	R. H. Gordon	Harrisburg, Pa.
152	Gary Olson	Barrington, Ill.
142	Walter Owen, Jr.	Springfield, Ohio
136	John T. Sowders	Richmond, Ky.
133	Donald Ruland	Holly Hill, Fla.
132	Stanley J. Penc	Utica, N. Y.
130	Frank Wheeler	Erie, Pa.
129	Dibrell Ingram, Jr.	Conway, Ark.
124	Ed Prond	Dolton, Ill.
123	Gary Rahn	Owen Sound, Ont., Canada
118	Jack Collier	Arlington, Va.
111	Franklin G. Brown	Easley, S. C.
109	David Beal	Tucson, Ariz.
107	Wayne Baer	Meyersville, Pa.
105	Paul Petosky	Trout Lake, Mich.
103	Bill McCarl	Moline, Ill.
103	Ronald Boyd	Truro, N.S., Canada
101	Leon Elliston	Dallas, Tex.
100	James Buchmann	La Crosse, Wis.
100	Rod Luoma	Detroit, Mich.
98	Roger Brown	East Lansing, Mich.
96	Ron Pugh	Fort Bragg, Calif.
92	J. M. Majdak, Jr.	Brattleboro, Vt.
85	Dave Novick	Wauwatosa, Wis.
83	Morris Foote	Middleton, Idaho
83	Jim Dillon	Regina, Sask., Canada
83	Chris Carlisle	Watertown, N. Y.
80	M. L. Whitson, Jr.	Los Alamos, N. M.
78	David Hanson	Washburn, Wis.
76	Russell Cain	Reno, Nev.
74	A. Coro Jr.	Marianao, Cuba
72	Merwyn Dowden	Chester, Va.
69	Bryan Rawlings	Montreal, Que., Canada
69	David S. Roberts	Royal Oak, Mich.
69	Doyle C. Warren	Little Rock, Ark.
67	Richard Bergen, 3rd	La Grange, Ky.
67	Lawrence Molish	Winnipeg, Manitoba, Canada
65	Bert Nuber	Ft. Lauderdale, Fla.
64	Harley Hurlburt	Bennington, Vt.
64	D. W. Parsons	Port Allen, La.
61	Julius Boosi	South Bend, Ind.
59	John Dranchak	Bridgeport, Conn.
57	Richard Zwirko	New Haven, Conn.
56	Thomas Rathke	Clintonville, Wis.
54	Bill Hauser	Oklahoma City, Okla.
53	H. Korb	North Bay, Ont., Canada
53	David Webb	Springfield, Mass.
51	Peter J. Layne	Las Cruces, N. M.
51	Barton Cronin	Ontario, Ore.
<b>FM Dx Listing</b>		
330	Bruce Elving	Duluth, Minn.
114	Wayne Baer	Meyersdale, Pa.
103	Bill Finn	Milwaukee, Wis.
65	Harold Moensterman	Evansville, Ind.
55	Dale Chute	Toronto, Ont., Canada
41	D. G. Bennie	Kinston, N. C.
40	John Ebeling	Minneapolis, Minn.
21	David Beal	Tucson, Ariz.

## TELEVISION

band results have been very interesting.

During the Perseids meteor shower in mid-August, he parlayed a single burst on channel 7 into two separate station identifications, at 9:30 EST on Aug. 12. The first was from KHQA-TV, 979 miles in Missouri; the second from KWWL-TV, 914 miles away in Iowa. Two new stations on channel 7, by meteor burst, were both logged on a single burst. It has not been uncommon to log two, perhaps even three, stations on a single burst on the lower channels (2 to 6), but to the best of our knowledge this is the first case of such skill on the high band (channels 7-13).

During a special dx test on Aug. 17, Cody nabbed channel 12, WRDW-TV, Augusta, Ga., a neat 757-mile haul via bursts on long-haul ground wave.

On Aug. 21, Cody watched ground wave extend south first into Virginia, then farther, into North Carolina and, finally, South Carolina! South Carolina high-bander WIS-TV, channel 10, Columbia, at 691 miles was followed by WBTW, channel 8, Florence, 640 miles. Many dxers would consider a high-band haul of 320 miles good dx, but Cody's log for Aug. 25 shows the notation, "WBAL-TV, channel 11, Baltimore, 320 miles overridden by WTVD, 11, Durham, N. Car., 520 miles!" Cody concludes his August report with the comment, "Best month I have ever seen for TV dxing" and, with 11 new stations to his credit in August, many of them high-banders at that, his end-of-August total of 217 was impressive indeed. TV dx is where you find it, and dxer Cody has certainly found it on the plains of New England!

## Dxing Horizons

As stated in the January issue, this is the last appearance of this column in RADIO-ELECTRONICS. Realizing for some time that eventually the TV-FM dxing clan would have to strike out on its own, the groundwork for a magazine exclusively for dx has been laid and the first issue of *TV-FM Dxing Horizons* scheduled for January, 1960. It is devoted in its entirety to long-range TV and FM reception, concerning itself with construction articles, feature stories and columns of reports on the many varied dxing activities. This is your opportunity to get behind a magazine devoted to your hobby; it has grown to the point where it must support itself or sink from view. If you have not received your January issue, send for a sample copy of *TV-FM Dxing Horizons*. (820 Tully Road, Modesto, Calif.)

Speaking once again for the hobby of FM and TV dx reception, I would like to express the thanks of thousands of dxers who through the years have found in the RADIO-ELECTRONICS column information simply not available in any other major circulation magazine. To RADIO-ELECTRONICS, thanks for this regular space and for the assist in getting this hobby launched. **END**

FEBRUARY, 1960

# With DYNAKIT you KNOW you have the BEST!

*The finest high fidelity you can buy at any price*

## DESIGNED FOR STEREO



PAS-2 \$59.95



Stereo 70 \$99.95

- New stereo control preamp with complete flexibility, fastest construction, and simplest operation
- Only 8 hours to build
- Truly unmeasurable distortion—below 0.05%
- Two outstanding 35 watt channels (160 watts peak) to power any speaker
- Unequaled transient response
- Absolute stability with every loudspeaker without restriction of bandwidth

## STEREO IN EASY STEPS

*Start with a superb monophonic system*



PAM-1 \$34.95



Mark IV \$59.95

- History-making "no-distortion" pre-amplifier which has never been equalled
- 6 hour assembly
- Either the renowned 60 watt Mark III or its new little brother, the 40 watt Mark IV
- 3 hours to build

*Expand to matchless Stereo*



Add the  
DSC-1 \$12.95



Two Mark III's  
\$79.95 each

- Every stereo function at your fingertips
- Unsurpassed flexibility
- Unitized panel or cabinet mount available as an accessory
- Just add the second Mark III or Mark IV and you can have the most highly recommended, most desired stereo amplifier ensemble for less than 20 hours of your time

*See and hear Dynakits at your local dealer*

A post card will bring complete specifications

**DYNACO, INC. 3916 Powelton Ave. Phila. 4, Pa.**

**CABLE ADDRESS: DYNACO, PHILA.**

# RCA KITS

FOR VALUE, QUALITY AND PERFORMANCE!



## RCA WV-38A (K) VOLT-OHM-MILLIAMMETER

only **\$29.95\*** (includes batteries, probe and cable with slip-on alligator clip, ground lead and clip, assembly and operating instructions) (available factory-wired and calibrated—only \$43.95\*)

Exclusive features make this RCA VOM kit the buy of a lifetime! Extra 1-volt and 0.25 volt (250 mv) ranges for wider usage in transistor servicing—new handle clip accommodates probes and test leads for extra carrying convenience. Assembles in a breeze!

**FEATURING:** ohms-divider network fuse-protected • easier-to-read scales • extra-large 5/4 inch meter • polarity reversal switch • excellent frequency response • full-wave bridge rectifier • low circuit loading • standard dbm ranges.

**SPECIFICATIONS:** Input Resistance—20,000 ohms per volt on DC; 5,000 ohms per volt on AC • Accuracy—± 3% DC, ± 5% AC (full scale) • Regular Scales—2.5, 10, 50, 250, 1000, 5000 volts, AC and DC; 50  $\mu$ a 1, 10, 100, 500 ma, 10 amps (DC) • Extra Scales—250 mv. and 1 volt (dc) • Frequency Response—AC-flat from 10 cycles to 50 Kc (usable response at 500 Kc) • Ohms—3 ranges: Rx1—(0-2,000 ohms); Rx100 (0-200,000 ohms); Rx10,000 (0-20,000,000 ohms) • Dimensions—W. 5 1/4", H. 6 7/8", D. 3 1/8"

## RCA WO-33A (K) 3-INCH OSCILLOSCOPE

only **\$79.95\*** (complete with Low-Cap, Direct Input Probe and Cable) (also available factory-wired and calibrated—only \$129.95\*)

The first 'scope kit with "get-up-and-go!" Use it for practically everything—video servicing, audio and ultrasonic equipment, low level audio servicing of pickups, mikes, pre-amps, radios and amplifiers, troubleshooting ham radio, hi-fi equipment, etc.—and you can take it with you, on the job, anywhere!

**FEATURING:** voltage-calibrated frequency-compensated, 3 to 1 step attenuator • scaled graph screen and calibrating voltage source for direct reading of peak-to-peak voltages • "plus-minus" internal sync... holds sync up to 4.5 Mc • shielded input cable with low capacitance probe included • weighs only 14 pounds • includes built in bracket to hold power cord and cables.

**SPECIFICATIONS:** Vertical Amplifier (Narrow Band Position)—Sensitivity, 3 rms mv/inch; Bandwidth, within -3 db, 20 cps to 150 Kc • Vertical Amplifier (Wide Band Position)—Sensitivity, 100 rms mv/inch; Bandwidth, within -3db, 5.5 cps to 5.5 Mc • Vertical Input Impedance—At Low-Cap cable input... 10 megohms, 10  $\mu$ f (approx.); At Direct-cable input... 1 megohm, 90  $\mu$ f (approx.) • Sweep Circuit—Sawtooth Range, 15 cps to 75 Kc; Sync, external,  $\pm$  internal; Line Sweep, 160° adjustable phase.




## RCA WV-77E (K) VOLTOHMYST®

only **\$29.95\*** (also available factory-wired and calibrated only \$49.95\*)

Think of it—an RCA VoltOhmyst Kit at this low, low price! You get famous RCA accuracy and dependability, plus the easiest to assemble kit you've ever seen!

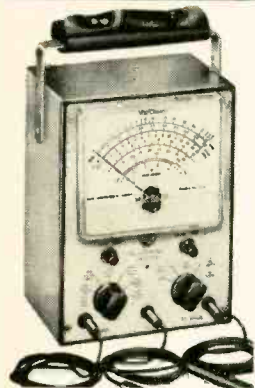**FEATURING:** ohms-divider network protected by fuse • ultra-slim probes and flexible leads • sleeve attachment on handle stores probes, leads, power cord • separate 1 1/2 volts rms and 4 volts peak-to-peak scales for accuracy on low ac measurements • front-panel lettering acid-etched.



**SPECIFICATIONS:** Measures: DC Volts—0.02 volt to 1500 volts in 7 overlapping ranges; AC Volts (RMS)—0.1 volt to 1500 volts in 7 overlapping ranges; AC Volts (peak-to-peak)—0.2 volt to 4000 volts in 7 overlapping ranges; Resistance—from 0.2 ohm to 1000 megohms in 7 overlapping ranges. Zero-center indication for discriminator alignment • Accuracy—± 3% of full scale on dc ranges; ± 5% of full scale on ac ranges • Frequency Response—flat within ± 5%, from 40 cycles to 5 Mc on the 1.5, 5, and 15-volt rms ranges and the 4, 14, and 40-volt peak-to-peak ranges • DC Input Resistance—standard 11 megohms (1 megohm resistor in probe).

\*User Price (Optional)

See them all at your local RCA Test Equipment Distributor!



**RADIO CORPORATION OF AMERICA**  
ELECTRON TUBE DIVISION HARRISON, N. J.

## TELEVISION

# TV Minus Rf

By L. M. DILLEY

HOW to repair a television set without tools, test equipment, parts or tubes—this was my dilemma on a recent stormy winter evening while visiting friends in the country.

I arrived to find a mood of gloom among the small fry of the household. The TV had "gone dead." I consented to look at the set—a 17-inch Zenith table model. It was showing a bright raster and the usual slight hiss was audible from the speaker.

I removed the back and chassis with a nail file and a rusty pair of gas pliers. A visual inspection revealed no glow in the second video if, a 6CB6—the type tube used in all three if stages and in two sockets of the turret tuner.

To check the apparently dead if tube, I substituted a 6CB6 from the rf section. A faint picture appeared, accompanied by a fair amount of sound. This gave me an idea.

I asked my host for a short piece of small-diameter wire and he produced a length of rusty soft-iron stovepipe wire. I cut two 4-inch lengths, scraping one end of each with the nail file. One length of the wire was then wrapped with one thickness of cellophane tape, the wires laid parallel and tightly twisted together to form a capacitor. I separated the two cleaned ends slightly and inserted them into the socket holes normally occupied by pin No. 1 (grid) and pin No. 5 (plate) of the 6CB6 in the rf stage.

That did it! The sound came up with a boom, and the picture became sharp and contrasty with very little snow. The set gave good pictures on all three available channels. In fact, the owner claimed that performance on channel 8 was as good as it had ever been.

The payoff occurred the following week when a local technician was called to replace the missing tube. He was surprised how well the set performed without it. After removing the gimmicked stove-wire capacitor, he came up with this learned pronouncement: "The reason your friend used iron wire was because it's magnetic. This caused it to work nearly as well as a tube." END

## EASING FOCUS ADJUSTMENTS

To adjust a TV's focus controls for hair-line scanning lines, hold a magnifying shaving mirror near the screen of the set while focus adjustments are being made. The size of each individual scanning line will be greatly magnified, making it easier to pinpoint them quickly and accurately.—J. A. Compton



*New Products and Developments Provide  
More TV Signal Power Anywhere—On Any Number of Sets*

## **BLONDER-TONGUE** World's Most Complete Line of TV Signal Amplifiers

### **New Product**




#### **ALL-CHANNEL TV-FM AMPLIFIER MODEL HAB**

**Applications:** Better TV and FM Reception on 1 to 29 TV sets.

**Features:** FG\* input • High gain . . . 22 db (12.5 times) on low TV and FM bands • 24 db (16 times) on high TV band • NS† terminals and solderless 75 ohm cable connector • Input and Output . . . 75 or 300 ohms • 0.7 volts RF and 1.4 volts RF maximum output at 75 and 300 ohms respectively. List \$62.50

### **New Product**

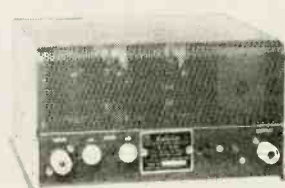

#### **BROADBAND AMPLIFIER MODEL MLA-b**

**Applications:** For Better VHF TV Reception on 30 to 150 TV sets.

**Features:** FG\* input • High gain . . . 40 db (100 times) • 1.7 volts RF maximum output • Frequency response  $\pm 1$  db, on both bands,  $\pm 0.5$  db for any TV channel, each band • Variable gain and tilt controls for each band • Solderless 75 ohm radiation-proof coax fittings. List \$142.50

### **New Product**



#### **ALL-CHANNEL MASTER TV AUTOMATIC GAIN CONTROL AMPLIFIER, MODEL MAC**

**Applications:** Better TV Reception In Large Master TV Systems.


**Features:** Less than 1 db output variation for 10 db change in input,  $\pm 0.5$  db for any TV channel. Compensates for signal and system variations • Controlled variable insertion gain  $\pm 10$  db • For use with amplifier with over 16 db gain and output voltage of 0.6 to 2.5 volts RF (such as MLA-b).


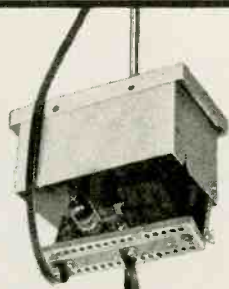
#### **ALL-CHANNEL DISTRIBUTION AMPLIFIER, MODEL DA8-B**

**Applications:** Better TV Reception on 3 to 8 sets.

**Features:** 8 isolated 75 ohm or 300 ohm TV outlets from a single 75 ohm or 300 ohm input • 10 db gain on all channels at each outlet • 22 db isolation • Low noise, all triode circuitry • Variable 20 db gain control prevents system overload. List \$94.50




#### **VHF ANTENNA BOOSTER, MODEL AB-2**

**Applications:** Home and other small installations. Mast-mounted amplifier.

**Features:** FG\* inputs • Gain . . . 10 db on all TV channels • Weather-protected "swing-down" chassis • NS† terminals • Boosts signal before line loss develops • Remote power supply • Single transmission line handles AC and signal power. List \$53.95
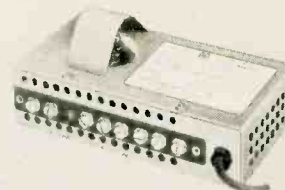
#### **FM ANTENNA BOOSTER, MODEL AB-FM**

Same as Model AB-2 except improves FM reception in all signal areas. 16 db gain over entire 88 to 108 mc band. List \$53.95



#### **TWO-SET POW-R BOOSTER MODEL B-24**

**Applications:** Home and small TV installations — 1 to 4 sets.

**Features:** FG\* input • 10 db gain on low band and 7 db on high band for 1 set operation, 3 to 5 db for 2 sets, and "No-Loss" for 4 set hook-up with BT A-104, four set coupler • NS† terminals • On/Off switch • Built-in power supply • No tuning required. List \$24.95

\*FG Latest premium type frame-grid input circuit provides highest possible signal-to-noise ratio

†NS'NO-STRIP'-Exclusive B-T 300 ohm No-Strip terminals for speedy, secure positive installation.



Available at parts distributors. For further information write Dept. RE-2.  
**BLONDER-TONGUE LABORATORIES INC.**

9 Alling Street, Newark 2, New Jersey

In Canada: Telequipment Mfg. Co. Ltd., London, Ont. Export: Morhan Export Corp., New York 13, N. Y.

hi-fi components • UHF converters • master TV systems • industrial TV cameras • FM-AM radios



# HOW TO BUILD A STEREO CONSOLE THAT REPRODUCES MUSIC AS FAITHFULLY AS SEPARATELY MOUNTED COMPONENTS

For many years, serious music lovers have searched for a way to enclose high quality high-fidelity equipment in a cabinet that would match their finest furniture.

Until now, there was no practical solution. You had to compromise. You had to sacrifice the best possible music reproduction if you wanted a good looking cabinet. If you insisted on high quality reproduction, you chose components, some of which may not have been quite so appealing to the eye.

If you dislike compromise, Stromberg-Carlson's new kind of console will interest you. We call them Integrity Series Component Ensembles—and to an uncompromising music lover each word in that name will be significant.

At the start, we faced the same problem that every console manufacturer has tried to overcome: when full-range speakers were rigidly mounted in the same console as high quality components, there was a serious loss of sound quality.

This loss—most often recognized as muddy or boomy noise—is caused by “feedback.” It occurs because sensitive components can detect the speaker vibrations which are fed back through the body of the cabinet. These vibrations are amplified with the music and reproduced as noise.

If you own a console now, but do not hear these noises, it is not because your ears are insensitive.

You do not hear them because we and every other console manufacturer had to eliminate them by compromising the musical reproduction of your console. You do not hear them because the sound you hear is not complete.


## HOW TO BUILD A CONSOLE THAT ELIMINATES FEEDBACK NOISES

As we analyzed the problem, we realized there were seven projects that we had to accomplish before

we could bring you this new kind of console.

**PROJECT #1** The first consideration was given to our components. They had to have high quality reproduction. The standards we set for them can be most simply described by the phrase “Integrity in Music Reproduction.” If you are familiar with Stromberg-Carlson stereo tuners, amplifiers, turntables and speakers, we believe you will agree they earn this description.

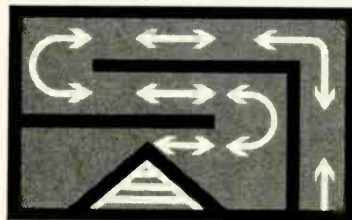
**PROJECT #2** Speaker systems were the next important project. For our new kind of stereo console we needed two speaker systems of unquestionable quality. We were fortunate here, because we



had already developed a system that met the quality requirements, the well-regarded Acoustical Labyrinth® Speaker System. Its quarter

wavelength duct enclosure, properly coupled to a low-frequency radiator, achieved a system resonance lower than the un baffled free air cone resonance of the radiator itself. This is the kind of quality we knew you wanted.

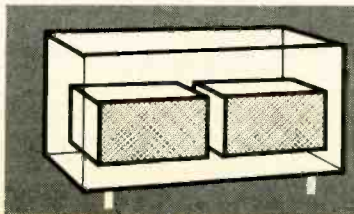**PROJECT #3** To reduce the size of high quality speaker systems so that they would fit into a stereo console of reasonable dimensions. We were certain that component-quality sound in a console could only be achieved with speaker systems that




did not depend on the console cabinet for their enclosure. This meant that we had to reduce the size of the Acoustical Labyrinth enclosure.

sure so that we could fit two separate speaker enclosures within a cabinet that had reasonable dimensions. It was not easy, but we did it. After many, many trials and tests we achieved the correct size without sacrificing one iota of the extremely linear and extended response of the system.
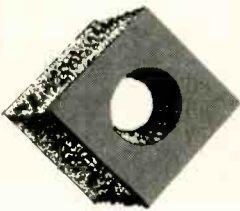
## NOW THE MOST DIFFICULT PROBLEM HAD TO BE FACED

**PROJECT #4** To effectively eliminate feedback by effectively eliminating the mechanical coupling that allows it to occur. Instead of treating the symptoms, we treated the cause. We developed a method of effectively isolating the speaker systems from the sensitive components. (As a result, Stromberg-Carlson Integrity Series Ensembles are the first successful uncompromised ensembles.)

The key development is what we call ISO-COUSTIC SPEAKER SYSTEM MOUNTING. This mounting, in which the resistance and compliance to vertical and horizontal pressures have been carefully engineered, has solved the problem. It allows Stromberg-Carlson to create a cabinet-within-cabinet suspension system which prevents transmission of speaker vibrations to the sensitive components. If you component owners could put your equipment into a cabinet whose speaker systems have our ISO-COUSTIC Mounting, the quality of the sound you'd hear would be as good as your component system is now. In fact, the components we use are the same ones you would choose for your separately mounted component system. They are interchangeable.



## INTEGRITY SERIES WILL NEVER BECOME OBSOLETE

**PROJECT #5** To assure the purchaser of an Integrity Ensemble that his choice would never be obsolete, we designed the units in accordance with a modular concept. All of the components are completely interchangeable. You can replace any component in the ensemble to keep pace with new developments—without ever replacing your fine cabinetry.



## CABINETRY HAD TO BE EXCEPTIONAL, TOO


**PROJECT #6** To design cabinets with the permanent beauty of fine furniture. Federico responded to the challenge by creating cabinetry in Traditional, Contemporary, Early American, Italian Provincial, French Provincial and Oriental

styling. You choose from 16 basic models in these styles, in a choice of finishes. These cabinets, like a fine painting, best describe themselves. They must be seen.

**PROJECT #7** To give you maximum flexibility in your enjoyment of an Integrity Series Ensemble. Every ensemble provides for your listening tastes and room acoustics by including the Stereo Choice Switch for precise regulation of stereo separation, with or without separate matching speaker systems. All ensembles provide space for adding a tape deck.

You may select your own Stromberg-Carlson stereo components or choose a recommended component complement—in any case Stromberg-Carlson components are always interchangeable.

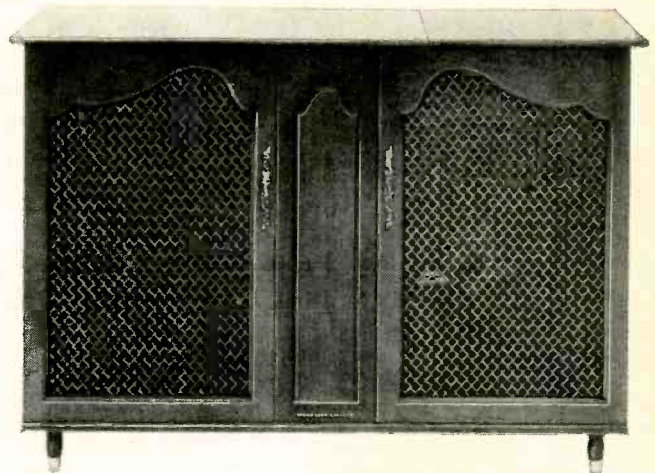If you now own a console or components, we invite you to exercise your critical judgment by listening to an Integrity Series Ensemble. (You will find that the better component shops—as well as the better department and music stores—have chosen to feature this new kind of stereo console.) Listen carefully. Look closely. Ask questions. Then accept not our judgment, but your own.



## INTEGRITY SERIES COMPONENT ENSEMBLES

—three hundred and fifty dollars to about six thousand dollars. You may choose from 16 models in Traditional, Contemporary and Period stylings, each tastefully designed by Federico. You may select your own Stromberg-Carlson components or choose a recommended Stromberg-Carlson component complement—in any case Stromberg-Carlson components are always interchangeable.

For a complete color catalog of Integrity Series Component Ensembles and components write STROMBERG-CARLSON, Special Products Division, 1478 N. Goodman St., Rochester 3, New York.

*“There is nothing finer than a Stromberg-Carlson”*

**STROMBERG-CARLSON**  
A DIVISION OF **GENERAL DYNAMICS**

*For integrity in music...*

# A NEW STROMBERG-CARLSON SINGLE-SPEED TURNTABLE

*...in component systems*

*...in Integrity Series Ensembles*



PR-500

**PR-500 SINGLE SPEED** Here is a revolutionary concept in turntable design: a dual-drive system consisting of two hysteresis-synchronous motors operating one belt drive.

The motors are spaced exactly 180° apart. Any variation of speed is automatically corrected by the interaction of the motors and the impregnated belt. Rumble and noise are virtually eliminated by the belt drive and a unique suspension system in which the tone arm and table, as a unit, are isolated from the mounting board.

Single, 33 $\frac{1}{3}$  speed. Includes tone arm. PR-500, black and brushed chrome ..... \$69.95\*

**PR-499 "PERFECTEMPO" ALL SPEEDS** The "Perfectempo" incorporates every valid, time-proven design principle: belt drive; continuously variable cone drive (14 to 80 rpm); stroboscopic speed indicator; dynamically balanced, weighted table; precision motor; plus Stromberg-Carlson's original double-acting motor and table suspension system that effectively eliminates unwanted noise. Performance proves it: Wow 0.14% rms; Flutter 0.09% rms; Rumble -55 db re 20 cm/sec at 1 kc. PR-499, morocco red with aluminum trim ..... \$99.95\*



PR-499


**RA-498 TONE ARM** The Stromberg-Carlson Tone Arm uses the most valid engineering concepts of tone arm design. Single pivot point suspension, true viscous damping and high moment of inertia result in extremely low resonance and consequently yield flat response below the limits of audibility. A calibrated counterweight is adjustable to provide any needle point force. For stereo operation, complete with mounting base, viscous fluid, rest, and cartridge clip. Fits all standard turntables. RA-498 ..... \$24.95\*



RA-498

\*Prices audiophile net, turntables less bases.

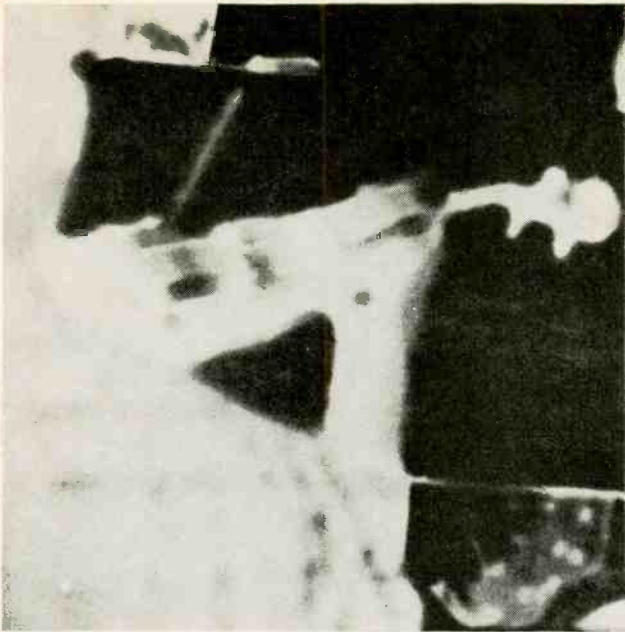**"THERE IS NOTHING FINER THAN A STROMBERG-CARLSON"**



*For integrity in music...*


## THREE NEW STROMBERG-CARLSON TUNERS

*...in component systems*


*...in Integrity Series Ensembles*

**SR-445 AM-FM STEREO TUNER** The SR-445 is actually two separate and complete units which have been placed together for convenience of mounting and use. They have individual circuitry in which no duplicate use of tubes or circuits is involved. Operate as an AM tuner, an FM tuner or together as an AM-FM stereo tuner. The SR-445 combines the separate AM and FM tuners described below. The specifications are exactly the same as listed for these two units. SR-445 . . . . \$129.95\*

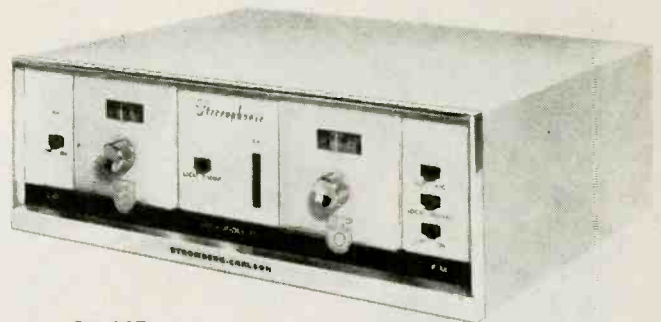*All three tuners are available in gold and white or black and brushed chrome. Top cover in white, black, tan or red available at extra cost.*




SR-445

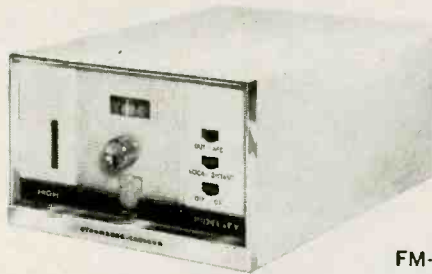

FM-443

**FM-443 FM TUNER** Exceptionally sensitive, low noise reception due to the wide peak-to-peak separation (475 kc) and long, linear slope (350 kc) of the balanced ratio detector, and the grounded grid cascode front end. Sensitivity is 2 uv for 20 db quieting, 4 uv for 30 db quieting (300 ohm). Local-Distant Switch results in 2 uv for 40 db quieting on local stations. Dial station selector and "hair-trigger" tuning eye. Temperature controlled circuits eliminate drift. Includes switched AFC circuit. Tuning Range: 88-108 mc. Bandwidth: 200 kc. Frequency Response: 20-20,000 cps. Self-powered with auxiliary power for AM-441 tuner. Provision for multiplex adapter. FM-443 . . . . . \$79.95\*

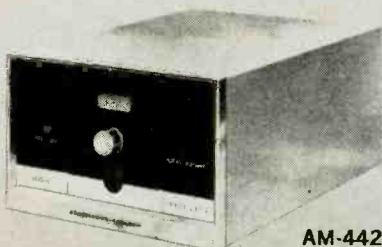

AM-442/AM-441

**AM-442 AM TUNER** For exceptional AM reception, this tuner has a frequency response of 20-7,000 cps, down 7 db at 7,000 cps. It features a tuned RF stage and 3-gang variable tuning condenser. Its tuning range is 540 to 1,600 kc; Bandwidth is 9 kc. Local-Distant Switch adds 20 db quieting on local stations. Adjustable ferrite loop and external antenna. AM-442 . . . . . \$59.95\*  
**AM-441 AM TUNER** Same as above, but without its own power supply . . . . . \$49.95\*

*\*Prices audiophile net, zone 1, less cover*


**STROMBERG-CARLSON**  
A DIVISION OF **GENERAL DYNAMICS**

*For integrity in music...*

# STROMBERG-CARLSON STEREO CONTROL AMPLIFIERS

*...for component systems*

*...for Integrity Series Ensembles*

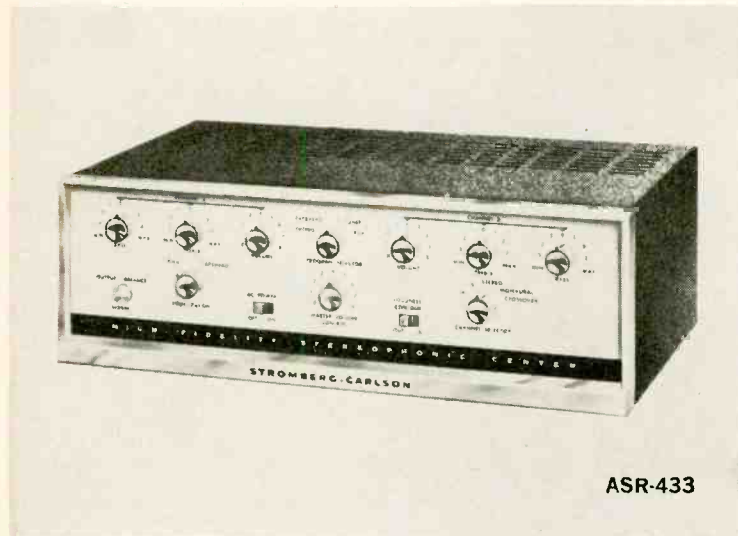


**ASR-433**

**ASR-433 STEREO "24" CONTROL AMPLIFIER** A dual channel amplifier with excellent performance and control features. Each channel provides 12 watts of exceptionally clean, balanced power. The exclusive "Stereo Tone Balance" signal permits you to adjust the two channels by a single tone.


The deliberately conservative specifications include: frequency response 20-20,000 cps; harmonic distortion less than 1% at full output; IM distortion less than 1% at program level; hum and noise 63 db down. Inputs: magnetic and ceramic phono; tuner; tapehead; auxiliary/tape. Available in gold and white or black and brushed chrome. ASR-433 .. \$129.95\*

**ASR-444 STEREO "60" CONTROL AMPLIFIER** offers all desirable controls, plus high power. Each channel provides 30 watts of balanced power. It features separate bass, treble and volume controls for each channel, a master gain and loudness control, and the "Stereo Tone Balance" signal. Specifications: frequency response 20-20,000 cps; harmonic distortion less than 0.7% at full output, IM distortion less than 1% at program level. Same inputs as ASR-433. In gold and white or black and brushed chrome. ASR-444 ..... \$169.95\*

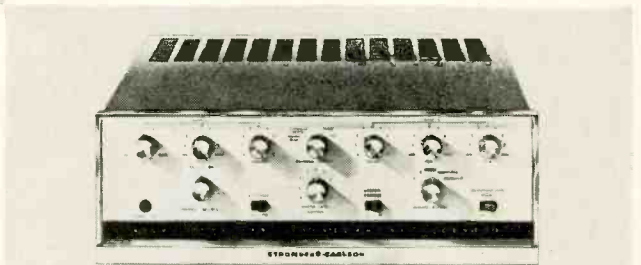

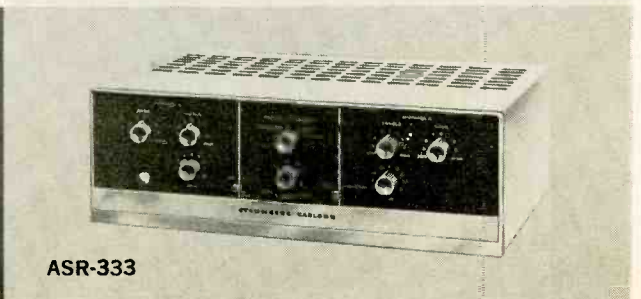**ASR-444**


**ASR-333 STEREO CONTROL AMPLIFIER**, and a fine ceramic cartridge, give you quality performance at a low price. This amplifier—with 12 watts per channel—was designed for optimum reproduction with ceramic cartridges. It features tone and volume controls for each channel, plus a loudness control. Frequency response, noise level, distortion, same as ASR-433. Inputs: ceramic phono, tuner, tape/auxiliary. In black and brushed chrome. ASR-333 ..... \$99.95\*



**ASR-333**

\*Prices Audiophile net, Zone 1, less top covers, which are available in white, black, tan or red.

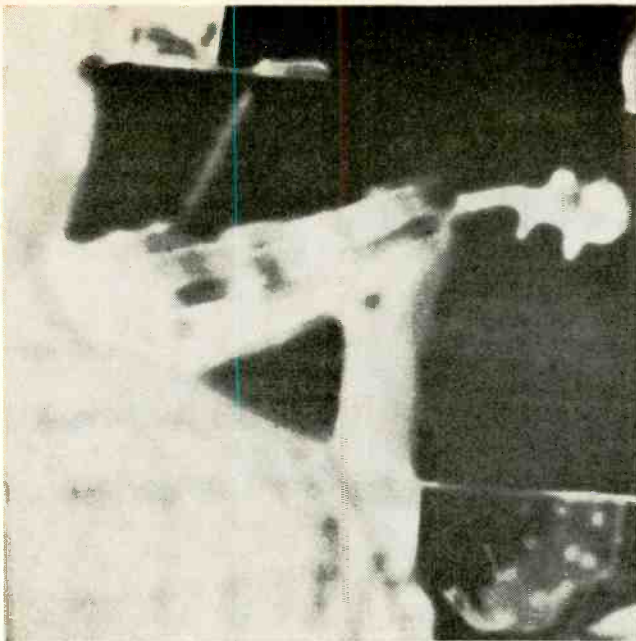**"THERE IS NOTHING FINER THAN A STROMBERG-CARLSON"**




*For integrity in music...*

## STROMBERG-CARLSON SPEAKERS AND SYSTEMS

*...for component systems*


*...for Integrity Series Ensembles*

Stromberg-Carlson manufactures a full line of speakers and the famous Acoustical Labyrinth® Speaker System. This system enclosure achieves a system resonance that is lower than the un-baffled free air cone resonance of the low frequency radiator. It utilizes mass loading and frictional damping as acoustical devices to extend the low frequency range of the system with extreme flatness of response. Five new complete speaker systems with a variety of decorator housings are now available. We suggest that you compare the quality of their performance with similar equipment. You be the judge.

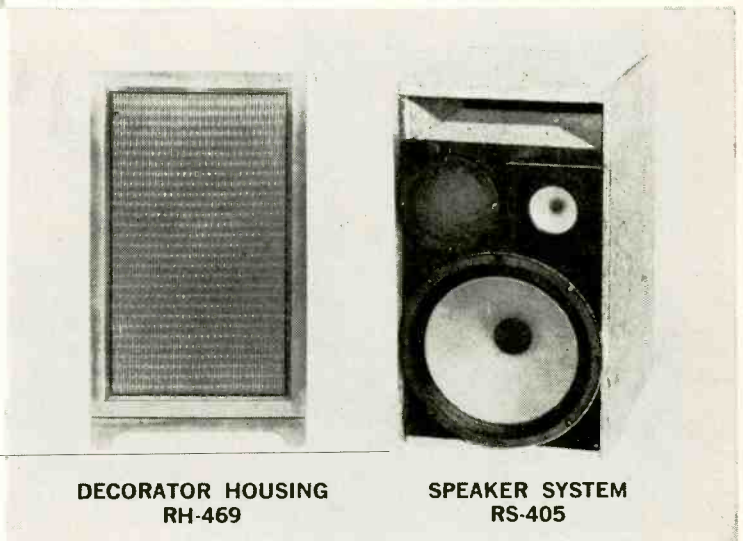

**DECORATOR HOUSING  
RH-469**

**SPEAKER SYSTEM  
RS-405**

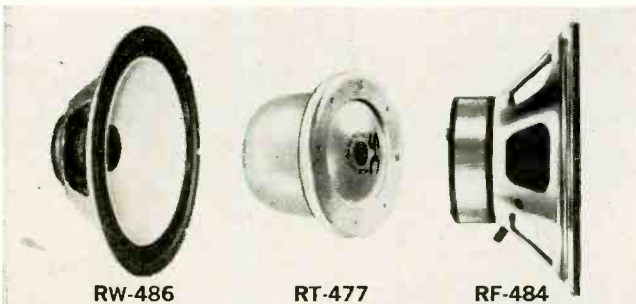


**RW-486**

**RT-477**

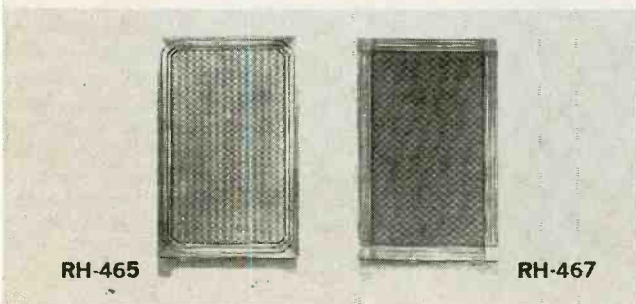**RF-484**

**SPEAKERS** Stromberg-Carlson loudspeakers include tweeters, woofers, coaxials and mid-range transducers. They are available in all popular sizes and price ranges.

The unusual Stromberg-Carlson "Slimline" feature allows maximum versatility in installation, and is made possible by another feature: the new "Barite" ceramic magnet, which is used to insure excellent transient response over the full effective frequency range.



**RH-465**

**RH-467**

**ENCLOSURE KITS** Acoustical Labyrinth enclosures are now available as unassembled kits. All pieces are precision-cut to size, ready to assemble. Nails, glue, complete instructions—everything you need is included. Enclosures are available for 8", 12" and 15" systems. The same decorator housings available for factory assembled systems may be used. Write for full details on speakers and housings available.

For full details on Stromberg-Carlson components, write Stromberg-Carlson, a Division of General Dynamics, 1478 N. Goodman St., Rochester 3, N. Y.

# STROMBERG-CARLSON

A DIVISION OF **GENERAL DYNAMICS**

FEBRUARY, 1960

95

## ELECTRONICS

A new concept of circuitry; a new dimension in electronics

# micro modules...

## today and tomorrow

By JORDAN McQUAY

**T**HERE'S something new, radically new, in electronics: *micromodules*.

These tiny, precision devices—each smaller than a cube of sugar but are 10 times smaller and lighter than conventional electronic equipment.

More than a new idea, the micromodule is a completely different and revolutionary concept of electronics design and construction. It's a unique concept—utilizing *microminiaturization* and other advanced techniques. It's a dramatic concept—providing tremendous potentialities wherever size, bulk and weight of equipment are critical.

The notion of micromodules was spawned from critical military requirements for lighter-weight smaller com-

munications and electronics equipment, for use aboard satellites and space vehicles of today and tomorrow.

Over a year ago, the Army Signal Corps initiated a major research and development program for micromodules, but leaned heavily on the communications-electronics industry for help. A \$5-million development contract was awarded to RCA. Subsequently, a dozen other companies have joined the program—which will continue for several years.

Although the concept of micromodules has immediate military value, it will be applied, to some degree, to all kinds of communications and electronics equipment and systems.

The joint military-industry program has progressed with amazing speed. The first results can now be described, some of them for the first time in a national magazine.

### Characteristics

A micromodule (Fig. 1) consists of a number of waferlike *micro-elements*, which are stacked and interconnected. All micro-elements have the same shape and size— $3/10$  inch square—and represent the ultimate in microminiaturization to date. A micro-element may consist of a resistor, capacitor, inductor, transistor, diode or other element—or it may be a combination of several such circuit elements.

Appropriate micro-elements are arranged according to the desired circuit—for an oscillator, amplifier or other stage—and are encased permanently, thus losing their individual identity. The result is a small, cube-shaped solid—a micromodule—which is actually a complete aggregate, ready to function as an oscillator, filter, counter, amplifier or other electronic stage.

Equipped with tiny leads, a number of micromodules can be connected in combinations to provide a variety of circuits for radio transmitters and receivers, audio amplifiers, pulse devices, data computers and many other kinds of electronic equipment (Fig. 2). In every such application, micromodularized equipment will be about





Fig. 1 (top left)—A typical micromodule.

Fig. 2 (left)—Complete circuit of a 7-stage micromodule superhet receiver—and a lump of sugar

Fig. 3 (bottom left)—Conventional components (left) and equivalent micro-elements (right). Top bottom: diode, capacitor, resistor, inductor, capacitor.

Fig. 4 (below)—Ceramic wafer upon which every micro-element is constructed.

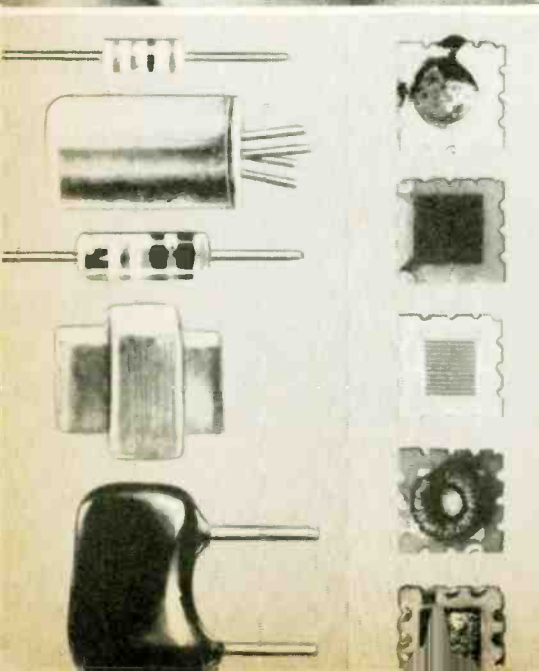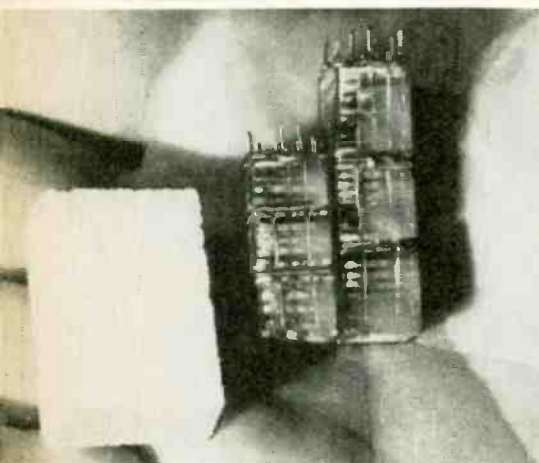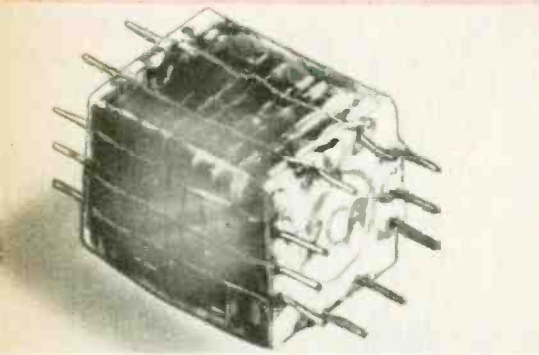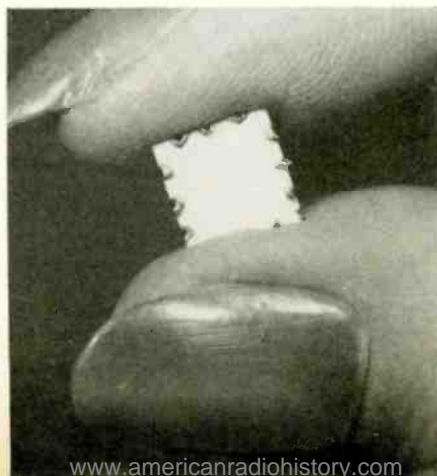Figs. 1, 3 RCA photos. Figs. 2, 4 Army Signal Corps





## ELECTRONICS

one-tenth the size and weight of conventional equipment.

With the plug-in method of connecting micromodules, maintenance and repair is greatly simplified. Individual micromodules can be removed and analyzed separately with automatic test equipment currently under development. Faulty modules can simply be replaced without repair. Ultimate cost of a micromodule will be so low that it will be more economical to replace a defective one than try to repair it.

Entirely new manufacturing processes will develop with universal acceptance of micromodules. With the introduction of automation in their manufacture, there will be a substantial increase in dependability. And mass production will lower the cost of these devices far below that of



Army Signal Corps

Fig. 5—Ceramic capacitor as a micro-element.

similar equipment of conventional manufacture.

This is the broad program—the basic concept of micromodules—a revolutionary development and a new dimension in electronics.

Many certain advances of the future are still on designers' drawing boards and many developments will require much additional research and engineering. But astounding advances have been made during only the first year of concerted military-industry effort. This is particularly true of the research, design and fabrication of the first micro-elements—the foundation blocks of every micromodule.

### Micro-elements

Over a dozen basic types of micro-elements have been perfected. These families include resistors, ceramic and electrolytic capacitors, inductors, transformers, diodes and crystals (Fig. 3). Many others are under development. Within a few years there will be at least 35 families, representing about 135 design types.

Every micro-element is constructed on or within a single ceramic wafer 3/10 inch square and 1/100 inch thick (Fig. 4). Each tiny slab of insulating material is precision-cut, with 12 notches around its outer edge. These notches are for terminals to facilitate assembly and construction.

Micro-element resistors range in value from 10 ohms to 1 megohm. There are two types. In one, a vacuum deposit

A QUARTER-CENTURY OF **PRECISION** KNOW-HOW IS YOURS IN

# P A C O

## QUALITY ELECTRONIC EQUIPMENT IN KIT FORM

FOR:

electronic hobbyists and amateur radio

hi-fi custom building and service

science education and technical schools

industrial testing and quality control

PACO is the only line of test instrument kits engineered and produced under the auspices of a leading test equipment and meter manufacturer.

and, you pay nothing extra for the convenience of buying PACO kits directly from your own local parts distributor.

COMPARE PACO against any other kits for performance, appearance, ruggedness, ease of operation and simplicity of assembly and wiring.

COMPARE PACO's superbly detailed, step-by-step instruction manuals and giant size wiring diagrams, against any you have ever seen.

SEE HOW PACO sets an entirely new standard in electronic instrument kit design and kit assembly instruction.

■ Available and on display at leading electronic parts distributors.

■ Write for latest, complete catalog.

# P A C O

Electronics Co., Inc.,

70-31 84th St., Glendale 27, L. I., N. Y.

Export: 458 B'way, N. Y. 13, U.S.A.,

Canada: Atlas Radio Corp., Toronto 19.

A DIVISION OF

**PRECISION APPARATUS CO., INC.**

 <p><b>MODEL B-10</b> Battery Eliminator Kit • less than 0.3% ripple output • no external filters required Kit Net Price: .....\$41.95 Factory Wired: .....\$49.50</p>	 <p><b>MODEL S-55</b> Wideband 5" Oscilloscope • response DC to 5 Mc • push-pull V and H amplifiers Kit Net Price: .....\$87.50 Factory Wired: .....\$139.50</p>
 <p><b>MODEL C-20</b> Res-Cap-Ratio Bridge Kit • 10 mmfd to 2000 mfd • 1/2 ohm to 200 megs Kit Net Price: .....\$20.95 Factory Wired: .....\$31.50</p>	 <p><b>MODEL T-60</b> Tube Checker Kit • full free-point lever selector system • built-in roll chart Kit Net Price: .....\$38.75 Factory Wired: .....\$54.50</p>
 <p><b>MODEL G-30</b> RF Signal Generator Kit • 160 Kc to 240 Mc in 8 bands • 120 Mc fundamental output Kit Net Price: .....\$28.50 Factory Wired: .....\$39.95</p>	 <p><b>MODEL T-65</b> Transistor and Crystal Diode Tester Kit • tests I<sub>cb0</sub>, gain, leakage, etc. • tests both p-n-p and n-p-n types Kit Net Price: .....\$39.95 Factory Wired: .....\$59.50</p>
 <p><b>MODEL M-40</b> High Sensitivity V-O-M Kit • 20,000 ohms/volt DC • 10,000 ohms/volt AC Kit Net Price: .....\$31.50 Factory Wired: .....\$37.50</p>	 <p><b>MODEL V-70</b> Vacuum Tube Voltmeter Kit • wide-range • peak-to-peak Kit Net Price: .....\$31.50 Factory Wired: .....\$47.50</p>
 <p><b>MODEL S-50</b> 5" Cathode Ray Oscilloscope Kit • push-pull vertical and horizontal amplifiers Kit Net Price: .....\$49.50 Factory Wired: .....\$84.50</p>	 <p><b>MODEL Z-80</b> RF-AF Signal Tracer Kit • high gain RF and AF amplifier • visual and audible indicator Kit Net Price: .....\$29.50 Factory Wired: .....\$42.50</p>
 <p><b>MODEL SA-40</b> 40-Watt Stereo Preamp-Amplifier • silicon diode, low impedance power supply • 14 controls for optimum flexibility Kit Net Price: .....\$ 79.95 Factory Wired: .....\$129.95</p>	<p><b>COMING SOON!</b></p> <p><b>MODEL ST-45</b> AM/FM Stereo Tuner Kit Matching companion for the SA-40</p>

# P A C O

# COMPLETE TRAINING FOR BETTER RADIO-TV SERVICE JOBS



Let these two world-famous Ghirardi training books teach you to handle all types of AM, FM and TV service jobs by approved professional methods—and watch your efficiency and earnings soar!

Completely modern, profusely illustrated and written so you can easily understand every word, these books pave the way to fast, accurate service on any type of home radio-TV-electronic equipment ever made. Each book contains the latest data on the latest methods and equipment—NOT a relish of old, out-of-date material. Each is co-authored by A. A. Ghirardi whose famous RADIO PHYSICS COURSE and MODERN RADIO SERVICE were, for 20 years, more widely used for military, school and study training than any other books of their type.

## THE NEW Ghirardi RADIO-TV SERVICE LIBRARY

Almost 1500 pages and over 800 clear illustrations show step-by-step how to handle every phase of modern trouble-shooting and servicing.

### 1—Radio and Television Receiver TROUBLESHOOTING & REPAIR

A complete guide to professional service methods. For the novice, it is a comprehensive training course. For the experienced serviceman, it is a quick way to "brush up" on specific jobs, to develop improved techniques or to find fast answers to puzzling service problems. Includes invaluable "step-by-step" service charts. 820 pages, 417 illus., price \$7.50 separately. See combination offer!

### 2—Radio and Television Receiver CIRCUITRY AND OPERATION

This 669-page volume is the ideal guide for servicemen who realize it pays to know what really makes modern radio-TV receivers "tick" and why. Gives a complete understanding of basic circuits and circuit variations; how to recognize them at a glance; how to eliminate guesswork and useless testing in servicing them. 417 illus., price separately \$6.75.

### New low price . . . You Save \$1.25!

If broken into lesson form and sent to you as a "course," you'd regard these two great books as a bargain at \$50 or more! Together, they form a complete modern servicing library to help you work faster, more efficiently and more profitably. Under this offer you buy them both for only \$13.00. You save \$1.25 on the price of the two books—and have the privilege of paying in easy installments while you use them.

### 10-DAY FREE TRIAL

Dept. RE-20, RINEHART & CO., Inc.  
232 Madison Ave., New York 16, N.Y.

Send books below for 10-day FREE EXAMINATION. In 10 days, I will either remit price indicated (plus postage) or return books postpaid and owe you nothing. (Save! Send cash with order and we pay postage. Same return privilege with money refunded.)

Radio & TV Receiver TROUBLESHOOTING & REPAIR. (Price \$7.50 separately)

Radio & TV Receiver CIRCUITRY & OPERATION (Price \$6.75 separately)

Check here for MONEY-SAVING COMBINATION OFFER . . . Save \$1.25.

Send both of above big books at special price of only \$13.00 for the two (regular price \$14.25) . . . you save \$1.25. Payable at rate of \$4 (plus postage) after 10 days if you decide to keep books and \$3 a month thereafter until \$13 has been paid.

Name.....


Address.....

City, Zone, State.....

Outside U.S.A.—\$8 for TROUBLESHOOTING & REPAIR; \$7.25 for CIRCUITRY & OPERATION; \$14 for both. Cash with order only, but same 10-day return privilege.
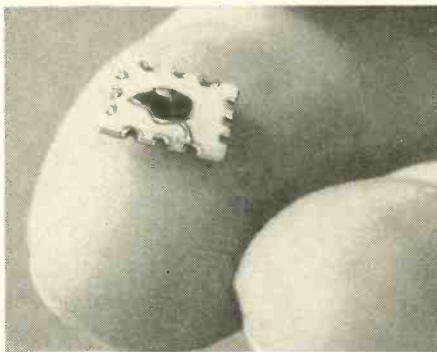
## ELECTRONICS

of metal film is first placed on the surface of a wafer, and then the desired resistor pattern is mechanically scribed to any precise value. In the second type, a tin oxide resistance film



Army Signal Corps

Fig. 6—A diode as a micro-element.

is deposited as a series of lines which can be terminated in various ways to provide different values of resistance. In either type, as many as four resistors of diverse value can be accommodated on a single wafer.

Unlike conventional capacitors which assume a variety of shapes and sizes, all micro-element capacitors are the size of a standardized wafer. General-purpose units, having values up to 0.2  $\mu$ f, are formed by a coating of conventional high-K dielectric ceramics (Fig. 5). Higher values of capacitance are obtained with multi-layer coatings of film-thin ceramics. Tiny electrolytic structures with solid electrolyte are used for micro-element capacitors to provide values from 0.1 to 10  $\mu$ f. Precision capacitors, having values up to several thousand  $\mu$ mf, are constructed with dielectric materials of conventional, precision, temperature-compensating ceramics.

Micro-element inductors and transformers consist of toroidal windings on ferromagnetic cores attached to an insulating wafer. They range in value from a few microhenries to as high as 10 mh. The success of these devices is due to the development of ferrite cores with very-low-temperature coefficients. Inductor performance is determined almost entirely by the characteristics of the ferrite core on which the inductor is wound.

Semiconductors, such as transistors and diodes, are essentially commercial units which have been adapted to micro-element form.

There are presently four kinds of transistors, equivalent to types 2N109, 2N404, 2N140 and 2N384. Each transistor is hermetically sealed within the cavity of a specially recessed wafer.

There are three kinds of micro-element diodes (Fig. 6), equivalent to the 1N277, 1N643 and a Zener type. Each diode is assembled by soldering the commercial semiconductor directly to the wafer.

Micro-element crystals operate in the range of 7 to 70 mc. Three wafers are required to house each crystal. The quartz crystal is mounted in the



RADIOTELEPHONE LICENSE MANUAL \$5.00

In one convenient volume, complete study-guide questions with clear, concise answers for preparation for all USA commercial radiotelephone operator's license examinations.

RADIO HANDBOOK, GIANT 15th EDITION. A one-volume library of radio information, with extensive, simplified theory. Detailed how-to-build-it data on dozens of items of practical radio equipment ..... \$7.50\*

WORLD'S RADIO TUBES (Brans' Radio Tubes Vade Mecum) World's most authoritative tube book..... \$5.00\*

WORLD'S EQUIVALENT TUBES (Brans' Equivalent Tubes Vade Mecum) Over 32,900 comparisons ..... \$5.00\*


SURPLUS RADIO CONVERSION MANUAL. VOL. I. Practical conversions. Write for list of contents. \$2.50\*

SURPLUS RADIO CONVERSION MANUAL. VOL. II. Companion to Volume I. \$2.50\*



BUY FROM YOUR DISTRIBUTOR  
Add 10% on direct mail orders to  
EDITORS and ENGINEERS, Ltd.  
Summerland California

## STYLUS PRESSURE GAUGE

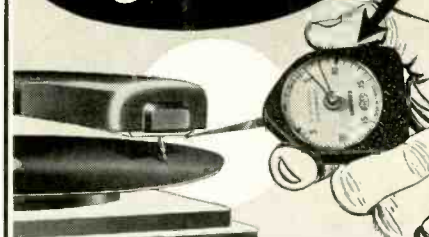

Precision stylus pressure gauges are available in 10 models ranging in calibration from .5 to 5 gram range up to 200 to 2000 gram range.

Cat. No. 6385, shown above, with 2-15 gram range or 3/32 to 1/2 oz. range **\$11.65**

The extra indicator "hand" will remain at the maximum reading of the device until reset by a knob on the dial face.

CORRECT STYLUS PRESSURE NOT ONLY GUARANTEES MINIMUM STYLUS AND RECORD WEAR, BUT ASSURES SOUND PICK-UP AT MINIMUM DISTORTION.

For Complete Information request our 96 Page Catalog—Contact any of our 4 "Coast to Coast" Locations or your nearest Local Distributor.



**SCHERR-TUMICO**  
PRECISION MEASURING TOOLS AND INSTRUMENTS

WAREHOUSE STOCK, SHOWROOMS & SALES OFFICES AT  
NEW YORK: 200 Lafayette Street, New York 12, N. Y.  
ST. JAMES: St. James, Minnesota  
LOS ANGELES: 3337 West Olympic Blvd., Los Angeles 19, Cal.  
CHICAGO: 5045 W. Harrison, Chicago 44, Ill.

When writing to any of the above locations, refer to DEPT FF-2

RADIO-ELECTRONICS

## ELECTRONICS


center hole of a special kind of wafer, covered on each side by two conventional solid wafers, and then hermetically sealed.

To save space, two or three micro-elements are sometimes assembled on a single wafer. This also increases reliability, since the number of soldered connections is reduced. Such multiple types of micro-elements include R-C networks, L-C filters and other combinations.

Still to be developed are the micro-elements for thermistors, thyristers, magnetic devices, solid-state switches and variable circuit elements.
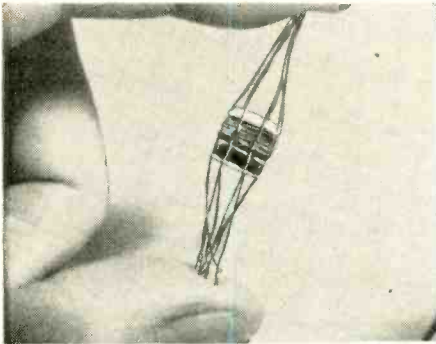
### Kinds of micromodules

A complete micromodule consists of a number of micro-elements arranged so the combination constitutes a desired electronic circuit—oscillator, amplifier or other complete stage. Connecting leads usually pass through the notches in the wafer of each micro-element. Additional riser leads are used to dissipate heat generated within the micromodule during operation. A terminal wafer is placed over the end of the stack, internal connectors are soldered



*Army Signal Corps*

**Fig. 7—Complete, encased micromodule ready for use.**

and the entire assembly is permanently encased (Fig. 7). Only leads for external connections protrude.

In operation, a micromodule is basically an integrated electronic stage that provides a specific, complete circuit function. For such operation, it requires a source of power and appropriate input, output and other connections.

To date, nearly 20 distinct kinds of micromodules have been developed, fabricated and used successfully as part of the military-industry program.

Representing a wide range of circuit functions, some of the principal kinds that demonstrate the potential capabilities of micromodules in rf, if, audio and digital circuitry are:


► An rf amplifier (Fig. 8) provides 10 db gain at 48 mc as the input stage of a portable military radio receiver. The micromodule includes a type 2N384 transistor, and a microminiature transformer with an rf ferrite core.

► For the same military receiver, an if amplifier (Fig. 9) has a gain of 20 db at a frequency of 4.3 mc with a bandwidth of about 200 kc. The stage includes a 2N384 transistor.

# Solve Rough Sweep Output Problems

## IN MINUTES

## INSTEAD OF HOURS!

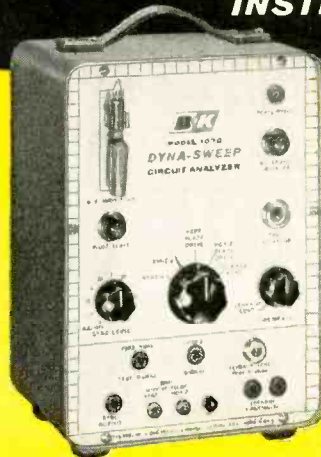

## NEW **B&K** DYNA-SWEEP CIRCUIT ANALYZER

1. Provides composite synchronizing signals (negative or positive) to inject directly in each sync stage.
2. Provides plate drive signal to check complete vertical output circuit, including V.O. transformer.
3. Provides vertical yoke test signal to determine if vertical yoke windings are defective.
4. Provides horizontal plate driving signal to directly drive TV horizontal output transformer circuit.
5. Provides B+ boost indicator.
6. Provides unique high-voltage indicator.
7. Provides sensitive tests for each of the horizontal output components, including H.O. transformer and yoke. Immediately reveals their true condition, good or bad.

Quickly solves tough output servicing problems that have always plagued the TV serviceman. Provides horizontal and vertical sync and driving pulses that make it easy to check out every stage in the sync and sweep sections of a television receiver. Tracks down troubles in the horizontal and vertical output circuit, including defective output transformer and yoke. Checks for shorted turns, leakage, opens, short circuits, and continuity. Gives unique high-voltage indication. Eliminates trial and error replacements. Saves many hours of service work! Pays for itself over and over again.

Model 1070 Dyna-Sweep. Net, \$69.95



**MODEL A107 DYNA-SWEEP CIRCUIT ANALYZER**  
for use with B&K Model 1075 Television Analyst

Functions like the Model 1070 above, but is designed as a companion unit for use only with B&K Model 1075 Television Analyst for driving source. Makes your Television Analyst more useful and valuable than ever. Net, \$49.95

See your B&K Distributor or Write for Bulletin ST24 E

**B & K MANUFACTURING CO.**  
1801 W. BELLE PLAINE AVE • CHICAGO 13, ILL.



Canada: Atlas Radio Corp., 50 Wingold, Toronto 10, Ont. • Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.

## SERVICEMEN KNOW!

Here they pay less and get the best

### HUSH®

**Chemically-Electronically, engineered for Tuners and Switching Mechanisms.**

When New HUSH is applied it will wash-away that dirt, leaving clean and positive contacts protected by a lasting lubricant. New HUSH is made from the finest solvents and it contains Electro-Silicone oils.

Also available—2 oz., 6 oz. Spray can \$2.25 net  
8 oz., 32 oz. containers

### EVER-QUIET®

Since 1949

**VOLUME CONTROL AND CONTACT RESTORER**


EVER-QUIET is a free-flowing liquid that leaves no powder residue. Scientifically designed to seep around the shaft and penetrate the control or potentiometer, cleaning the contacts and leaving a safe protecting film. Harmless to metals, wire or carbon.

Also available— 6 oz. Spray can \$1.59 net  
32 oz. containers

2 oz. Bottle & dispenser 79c net




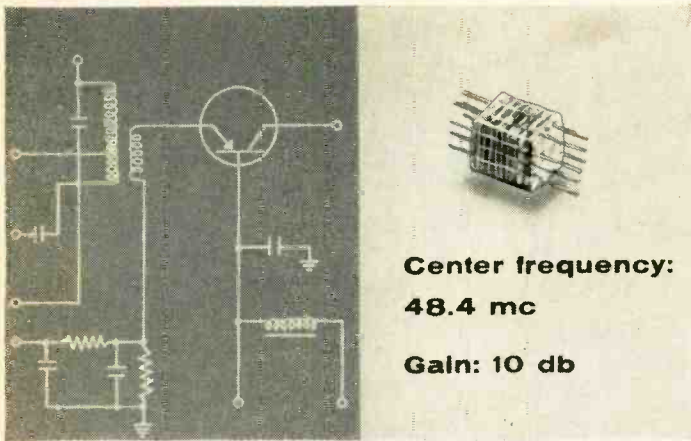**CHEMICAL ELECTRONIC ENGINEERING, INC. Matawan, New Jersey**




**Center frequency:**  
48.4 mc  
**Gain:** 10 db

Fig. 8—Rf amplifier circuit and equivalent micromodule used in military radio receiver.

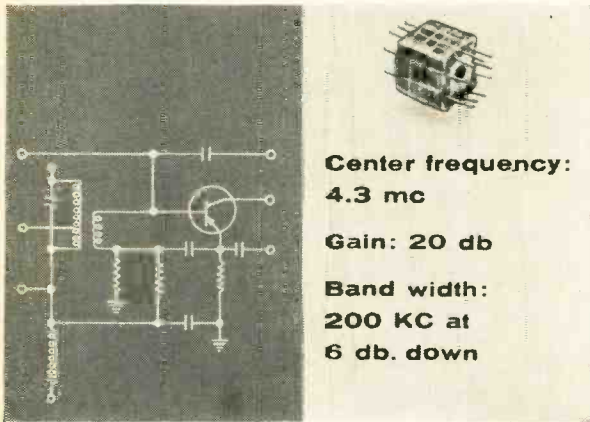

**Center frequency:**  
4.3 mc  
**Gain:** 20 db  
**Band width:**  
200 KC at  
6 db. down


Fig. 9—If amplifier circuit and equivalent micromodule.

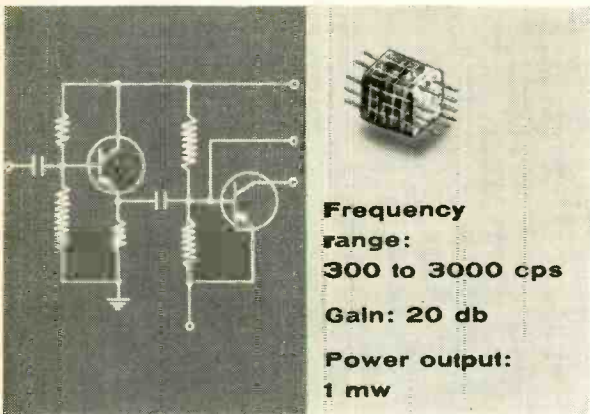

**Frequency range:**  
300 to 3000 cps  
**Gain:** 20 db  
**Power output:**  
1 mw

Fig. 10—Audio amplifier circuit and the micromodule it represents.

Fig. 11—Pulse generator as a micromodule.

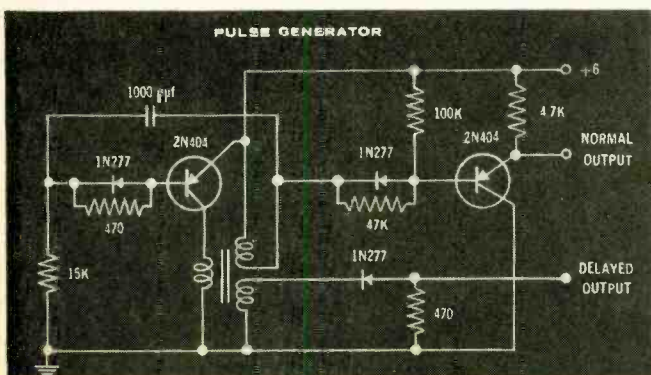

▶ An audio amplifier (Fig. 10) for the same receiver has 20 db gain, with a frequency range from 300 to 3,000 cycles. The micromodule includes two 2N269 transistors, the first of which functions as an emitter follower in place of the usual audio input transformer.

▶ A variety of digital type micro-miniature devices have also been developed. These include binary dividers, gates, clippers, pulse generators, sawtooth generators, output amplifiers and others—each constructed in the form of a single micromodule.

▶ Typical of these is the pulse generator stage (Fig. 11), which includes two type 2N404 transistors, three type 1N277 diodes and a 1:1:1 microminiature pulse transformer.

### Combining modules

When a number of appropriate micromodules are connected together, the complete circuitry for an electronics device can be provided in micro-miniaturized form.

For example, a seven-stage transistor superheterodyne radio receiver is so small it can be held in a spoon. This combination consists of seven interconnected micromodules that include an rf amplifier, if amplifiers and an audio amplifier. The only additional parts needed to put the unit into operation are an antenna, a source of power and some type of reproducing device.

Another assembly of micromodules built into a fountain-pen case, forms a five-stage transistor radio receiver. The case also contains an antenna, tuning controls and a small battery. In strong signal areas, it receives local reception broadcast-band stations excellently.

Future applications of the micro-modular concept are almost unlimited, particularly where critical size and weight limitations affect the design of communications and electronics equipment. Even though some systems—such as certain types of automatic data-processing equipment—become increasingly complex, micromodules will help minimize size and weight and will simplify repair and maintenance.

Much further research, design and development are necessary—not only to improve initial accomplishments but also to extend the micromodular concept into new areas.

One of these areas is semiconductors. There'll be more extensive use of semiconductors as the active circuit elements of micromodules, because the vast majority of existing electronics circuits can be transistorized.

Virtually all future equipment operating at low or medium power levels will use transistors and other semiconductor devices. At the same time, advances in solid-state physics can be used directly in developing new types of micromodules. Thus, the micro-modular idea becomes the logical stepping stone to multi-function solid-state devices of the future.

END




# MOUSE transmits own temperature


*Weighing less than 3.5 grams, this little transmitter reads the temperature of laboratory animals without disturbing them*



By RICHARD S. GRIFFITH, W7MPQ

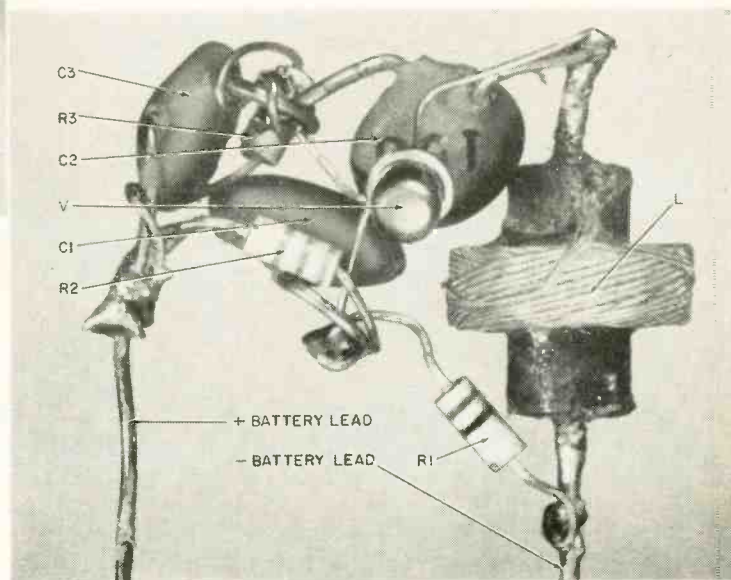

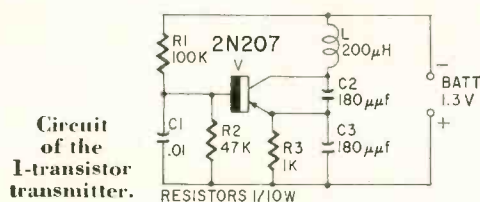Closeup view of the subminiature transmitter.



R1—100,000 ohms, 1/10 watt  
R2—47,000 ohms, 1/10 watt  
R3—1,000 ohms, 1/10 watt  
C1—0.01 µf, ceramic  
C2, 3—180 µf, ceramic  
BATT—mercury cell, 1.3 volts (Eveready E400 or equivalent)  
L—200 µh, peaking coil (Miller 6154 or equivalent)  
V—2N207

ARE you man or mouse?" This time the radio transmitter is operated by a mouse. Yes, our white mice transmit and so do our rabbits.

The College of Pharmacy at the University of Arizona needed a device that would give a constant indication of body-temperature changes of laboratory animals. These readings would be recorded while the effect of various drugs on the animals was being tested.

The final results of the drug tests were important, but knowing what was happening to body temperature all through the testing was just as vital. Body temperature of animals (including man) is a great controlling factor in their life functions.

Normally, a rectal thermometer is used to measure the temperature of laboratory animals. But there is a catch to this method—when an animal is handled in any manner, its temperature goes up almost immediately. So even though the thermometer may be a highly accurate instrument, readings are not necessarily true indications.

The College of Pharmacy needed an

instrument which would indicate body-temperature changes without disturbing the animal. It would have to give a continuous reading so rate of temperature change as well as the relative amount of change could be seen. If it could be calibrated to show the actual temperature too, the instrument would be doubly valuable.

Size and weight were important. After all, a 15-gram white mouse couldn't be expected to carry around a load equal to its own weight. Transistors and other miniature parts were vital, and this meant a subminiature power source as well.

### First attempts

On this basis, the work started, Read C. Easton (W1NAO/7) and myself being handed the job by Richard F. Childs of the college faculty.

It was obvious that the transmitted

signal would be extremely low power. But what signal would be used? An oscillator was tried first. A thermistor varied its frequency in proportion to temperature changes. Such a unit seemed to give favorable results, but we had to get a rather large mouse to carry the load. Transmitter weight was about 18 grams, and the animal could barely straighten his hind legs.


Next, a much smaller thermistor was used. And the entire unit was powered by a section sliced off a penlight cell. A few tests revealed that the thermistor was unnecessary—a small resistor (R2) could be substituted. The oscillator was very sensitive to heat variations, causing the desired frequency variations without a thermistor. (See diagram for a look at the circuit.) It operates on 750 kc at 25°C. The oscillator was encapsulated in plastic.

The first real test was made on a rabbit, in a laboratory class supervised by Dr. Albert L. Piccioni. The animal had been given a drug that would raise its body temperature.

A random length of wire coiled loosely  
(Continued on page 106)



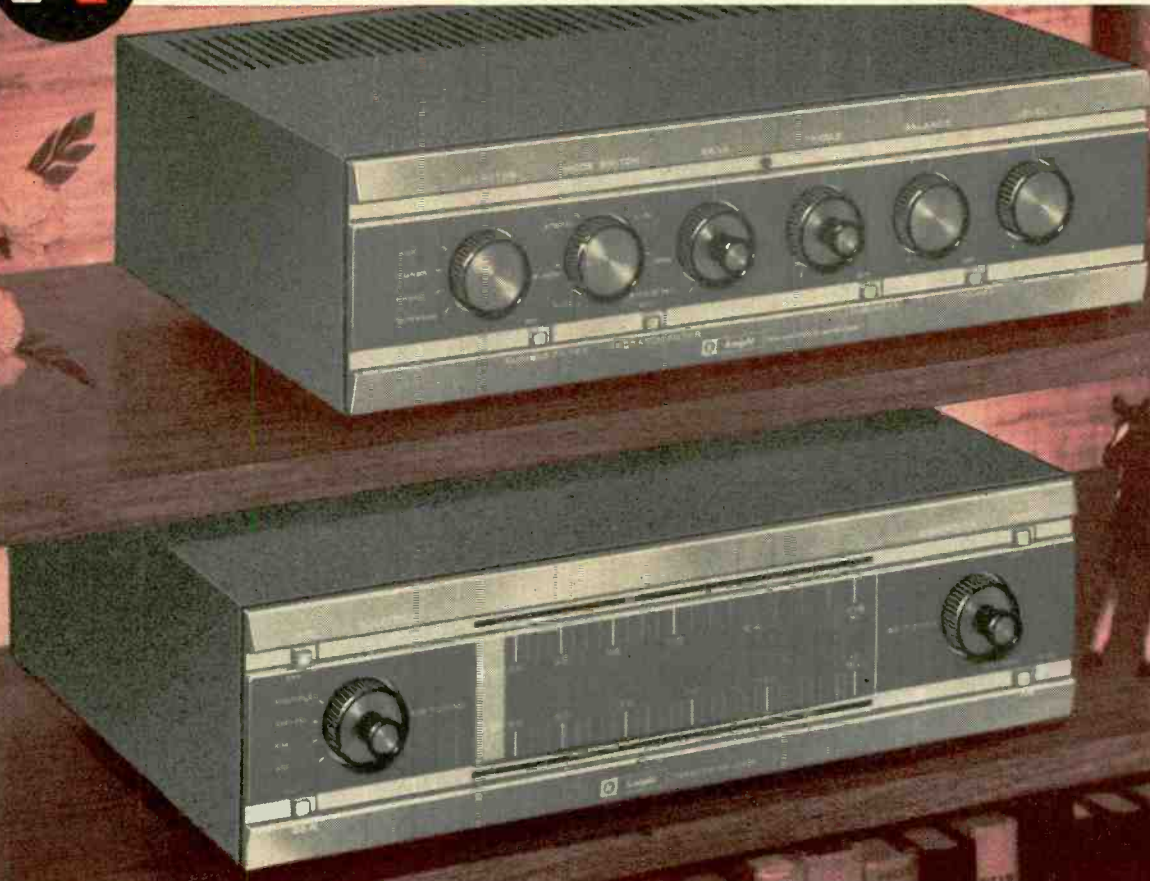newest **knight-kits** <sup>®</sup> ... years-ahead  
A PRODUCT OF ALLIED RADIO



incomparable **knight-kit** stereo hi-fi saves you up to 50%

**DELUXE 40-WATT STEREO AMPLIFIER KIT**

Y-774D

**\$79<sup>50</sup>**

**\$5 Down**

Finest hi-fi stereo amplifier you can buy in money-saving kit form. Features special full-frequency range, extra center-channel output for 3-speaker systems. Dual built-in equalized preamps accommodate every existing sound source; exceptional control versatility, including single knob channel balance and separate dual concentric tone controls for each channel. Outputs for stereo tape recording. Exclusive printed circuit switches and plug-in units for easy assembly. Custom-styled in Cordovan gray vinyl plastic bonded to steel; Desert Beige and Sand Gold extruded solid aluminum escutcheon; 4 1/8 x 15 1/2 x 11 1/4". Shpg. wt. 24 lbs.

**\$5**

**DOWN**

Model Y-774D. 40-Watt Stereo Amplifier Kit.

**DELUXE STEREO FM-AM TUNER KIT**

Y-731D

**\$87<sup>50</sup>**

**\$5 Down**


Distinguished for quality and styling, years-ahead in features. Has completely independent FM and AM sections, each with moving-bar "magic eye" tuning indicator. Only tuner kit with Dynamic Sideband Regulation (DSR) on FM for purest, distortion-free reception. Sectionalized construction permits easy addition of "built-in" multiplex. Has 2 1/2 μV sensitivity. Double limiter-discriminator FM circuits—adjustable AFC. Separate cathode-follower outputs on FM and AM with level set controls. Precisely aligned RF and IF transformers in FM section. Printed circuit boards for fastest, easiest assembly. Styling matches the 40-watt amplifier; 4 1/8 x 15 1/2 x 12". Shpg. wt., 18 lbs.

**\$5**

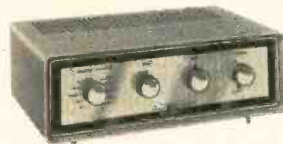**DOWN**

Model Y-731D. Stereo FM-AM Tuner Kit.

there is a money-saving **knight-kit** for every hi-fi need




**SEE THEM ALL**  
 See the impressive selection of Hi-Fi Knight-Kits (including speaker systems) in the money-saving 1960 ALLIED Catalog. If you haven't a copy, send for it today.

**20-Watt Stereo Amplifier**  
 Truly a super-value. Built-in equalized preamps; single-knob selector switch for control convenience; dual concentric, clutch-type level control. 17 lbs.  
 Y-773D. \$2 Down. Only **\$44<sup>50</sup>**

**FM-AM Hi-Fi Tuner Kit**  
 Amazing buy, featuring: Tuned RF stage; high sensitivity; AFC; flywheel tuning; pre-aligned IF and RF coils; cathode follower output. Truly great value. 14 lbs.  
 Y-787D. \$2 Down. Only **\$49<sup>95</sup>**

**18-Watt Hi-Fi Amplifier Kit**  
 A brilliant performer at unbelievable savings. 18 watts at only 0.5% distortion; RCA 6973 audio output tubes; 8 inputs; 7 record equalization settings. 15 lbs.  
 Y-797D. \$2 Down. Only **\$39<sup>95</sup>**


**FREE**

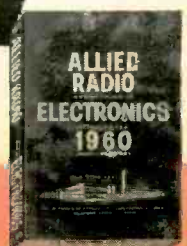

**ONLY \$5 DOWN (OR LESS)** on orders up to \$200; up to 24 months to pay. Fast handling—no red tape—take advantage of these easiest-pay terms...

[www.americanradiohistory.com](http://www.americanradiohistory.com)

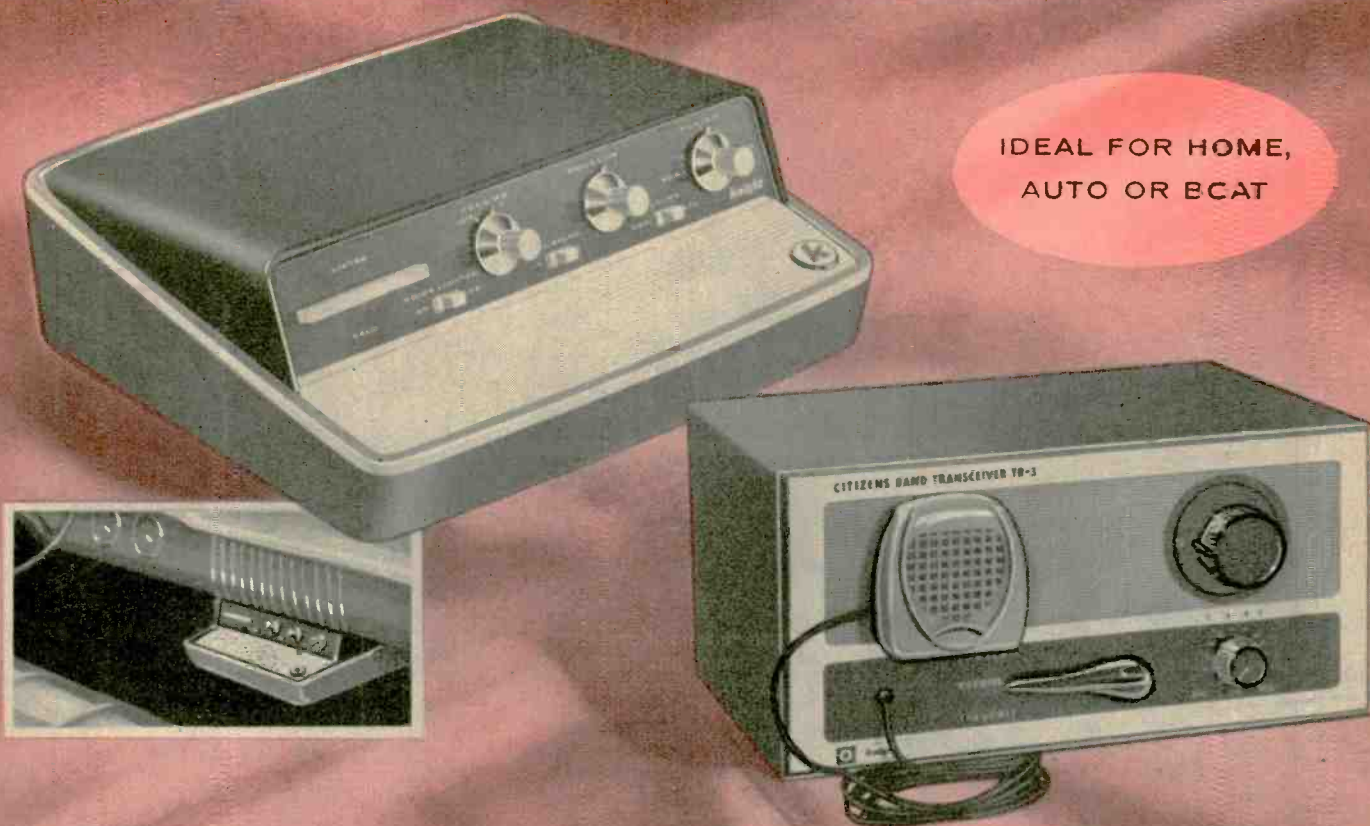for you who want to build the very best for less...



IDEAL FOR HOME,  
AUTO OR BCAT

all-new *knight-kit* citizens band transceivers... 2-way radio everyone can afford

**CITIZENS BAND SUPERHET TRANSCEIVER KIT**

Y-712D  
**\$79<sup>95</sup>**  
\$5 Down

A high-sensitivity do-it-yourself transceiver for efficient, economical 2-way radiotelephone communication. Any citizen, 18 or older, can get a license—no exam required. For mobile or stationary use. Covers up to 20 miles, depending on antenna height and terrain. Works just like an intercom, with talk-listen operation. Receiver is sensi-

tive superhet; tunes all channels continuously. 5-watt transmitter section. Built-in AC power supply. With transmitting crystal (available for any channel from 1 to 22—specify preference) and doublet antenna. Extras available: Y-723, 6-12 v. DC power supply, \$10.95; Y-729 vertical antenna, \$6.50; Y-714 mobile mounting bracket, \$5.35. Distinctive high-impact styrene case; 5 x 12 x 12". Shpg. wt., 20 lbs.

Model Y-712D. Superhet Transceiver Kit.

**\$5**  
DOWN

**CITIZENS BAND TRANSCEIVER KIT**

Y-713D  
**\$39<sup>95</sup>**  
\$2 Down

Low-cost super-regenerative receiver and 5-watt transmitter kit. Readily fits car, boat or desk. Simple, one-switch operation permits talk or listen. Receiver tunes all 22 channels continuously. Built-in AC power supply. With mike, transmitting crystal—

specify channel (1 to 22) if you have a preference—and doublet antenna. Handsomely styled case; 6 x 10 x 8". Designed for easy assembly and dependable operation. Available extras: Y-723, 6-12 v. DC power supply, \$10.95; Y-729 vertical antenna, \$6.50; Y-724 mobile mounting bracket, \$5.35. Shpg. wt., 10 lbs.

Model Y-713D. Transceiver Kit.

**\$2**  
DOWN

dozens of exciting hobbyist kits available



**"Span Master" 4-Band Radio Kit**

Famous for world-wide short-wave and broadcast reception. True band-switching; continuous 4-band coverage from Broadcast to 30 mc. Sensitive regenerative circuit; 4" PM speaker. With cabinet. 8 lbs.

Y-258D. \$2 Down. Only..... **\$25<sup>95</sup>**

**"Ranger" Clock-Radio Kit**

Easiest superhet of all to build—plug-in modules and printed circuit board eliminate small parts assembly. Excellent AM broadcast reception. Telechron clock has "sleep" switch. With appliance outlet. 6 lbs.

Y-737D. \$2 Down. Only..... **\$24<sup>95</sup>**




**5-Transistor Portable Radio Kit**

Popular, low-cost personal portable. Fun to build; superhet circuit; only 22 ounces; big 3 1/2" speaker; built-in ferrite loopstick; phone jack. (Less battery, \$1.30.) 2 lbs.

Y-771D. \$2 Down. Only..... **\$25<sup>95</sup>**

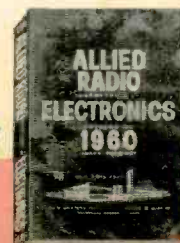**SEE THEM ALL:** Knight-Kits offer the most exciting hobbyist kits available. See the complete selection in the 1960 ALLIED Catalog. Write for it now—use coupon on page following.



**FREE**

manufactured and sold exclusively by

**ALLIED RADIO**

100 N. WESTERN AVE., CHICAGO 80, ILL.

www.americanradiohistory.com



newest **knight-kits**® ... years-ahead  
A PRODUCT OF ALLIED RADIO



**knight-kits** break through the professional instrument price barrier

**5" LAB DC SCOPE KIT WITH IVA**

**Y-611D**  
**\$285<sup>00</sup>**  
(less preamps)

For the first time in easy-to-build kit form—a triggered sweep DC precision quality lab scope with plug-in interchangeable vertical amplifiers (IVA). Brilliantly engineered with an impressive array of professional features, including: crystal-controlled timing markers; DC amplifiers in both horizontal and vertical channels; electronically regulated power supply; sweep timing adjustable to 1%; built-in voltage regulated peak-to-peak calibrator. Three interchangeable vertical preamplifiers are available: high-gain differential, \$35.95; wide-band (to 10 mc), \$24.95; dual-trace, \$48.95. **There is no other instrument like this in kit form**—here is laboratory precision quality and reliability at far less than the cost of any comparable factory-built unit. Shpg. wt. 50 lbs.

**Model Y-611D.** Lab DC Scope Kit.

**\$10**  
**DOWN**

Available in March—reserve yours now

**LAB AUTOMATIC AC VTVM KIT**

**Y-608D**  
**\$99<sup>50</sup>**  
**\$5 Down**

A major achievement in instrumentation! This all-new AC VTVM features **automatic range selection**—by means of an electronically-actuated self-seeking mechanism which **automatically** selects the proper range when you touch probes to the circuit under examination. Simultaneously, a front panel light indicates the range in use. Covers 11 ranges from 3 millivolts to 300 volts full scale; frequency response to 2.5 mc. Reads as low as 100  $\mu$ v. Highly stable 3-stage amplifier has cathode follower output; ideal for use as preamp for other test equipment or for connection to scope for simultaneous wave form observation. Includes precise trigger circuits; regulated power supply; latest printed circuitry for easy assembly and quality performance. An exclusive Knight-Kit development—there is no other instrument like it on the market, in any form or at any cost.

Shpg. wt. 13½ lbs.

**Model Y-608D.** AC VTVM Kit.

**\$5**  
**DOWN**

save on every instrument need with **knight-kits** ... best by design



**Famous-Value VTVM Kit**  
Measures DC voltage (11 meg. input) and resistance; AC voltage, rms and peak-to-peak. 4½" meter. Push-pull balanced bridge circuit. 7 lbs.

**Y-125D.** \$2 Down. Only **\$25<sup>75</sup>**



**Deluxe Tube Checker Kit**  
Checks over 700 receiving type tubes. 16 filament voltages. Tests cathode emission as well as shorts, open elements, etc. 15 lbs.

**Y-143D.** \$2 Down. Only **\$32<sup>95</sup>**



**5" Wide-Band Scope Kit**  
Top versatility. 5 mc bandwidth; DC coupled p-p output amplifiers; 25 mv/inch vertical amplifier sensitivity. Outstanding value. 29 lbs.

**Y-144D.** \$5 Down. Only **\$65<sup>75</sup>**

**SEE THEM ALL**

You'll find dozens of other fine quality Knight-Kit instrument values fully described in the 1960 **ALLIED Catalog**. If you haven't a copy, write for it now—use coupon on opposite page.

**FREE**

send for the value-packed 1960 **ALLIED CATALOG**





electronic achievements at half the factory-built cost



years-ahead **knight-kit** amateur gear

**T-400 AMATEUR 400-WATT TRANSMITTER KIT**

Y-716D  
**\$395<sup>00</sup>**  
 400-Watt CW  
 Transmitter


Truly the "dream" transmitter—has what it takes to punch out a QRM-busting SSB, AM, or CW signal. 600 watts F.E.P. input on SSB; 400 watts on AM and CW. Covers 80, 40, 20, 10, and 15 or 6 meter bands. Start with the basic CW kit— then add AM and SSB accessory units and other "add-ins" whenever you wish. Has heterodyne VFO to assure a signal which "stays put." Tremendous 14" dial is precision-calibrated for all bands, 80 through 6 meters. SSB features: front panel controls—VOX, anti-trip and adjustable speech compression. Smooth, chirpless screen-clamp keying, plus VFO keying for complete CW break-in. Has 7034/4X150A final—coasts along well within its CCS ratings; silicon rectifier power supply runs cool. Dozens of advanced features put this job in a class all its own. Shpg. wt. 140 lbs.

Model Y-716D. T-400 CW Transmitter Kit.

Available in March—reserve yours now

"Add-in" Accessories: SSB Generator Kit, \$69.95 • AM Modulator Kit, \$24.95 • Speech Amplifier Kit, \$9.95 • Monitor Scope Kit, \$37.95 • 6-Meter Conversion Kit, \$7.50.

**\$10**  
 DOWN

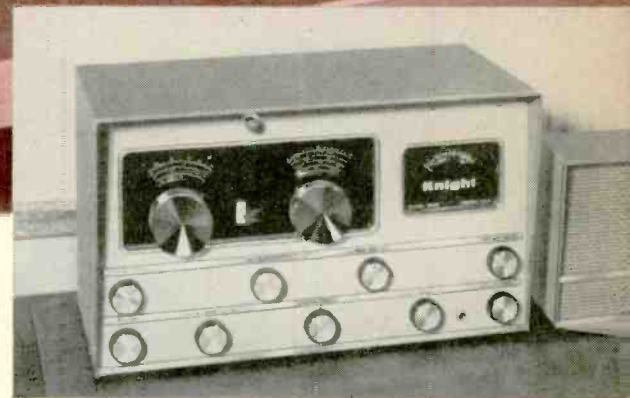

**R-100 AMATEUR RECEIVER KIT**

Y-726D  
**\$104<sup>50</sup>**  
 \$5 Down

Incomparable receiver kit with all the features, selectivity and sensitivity of high-priced commercial units. Tunes 540 kc to 30 mc in 4 bands; calibrated bandspread on all Ham bands; 300 cps to 4.5 kc selectivity; exclusive printed-circuit bandswitch; built-in Q-multiplier; constant-running HFO—dozens of other professional features. Truly superior kit value. 30 lbs.

Model Y-726D. R-100 Receiver Kit. **\$5** DOWN

Y-727D. S-Meter Kit for above, only..... \$10.75  
 Y-728D. 4" Matching Speaker, only..... 7.50


**FREE** Send for the 1960  
**ALLIED CATALOG**

Describes the complete KNIGHT-KIT line in detail—the leading Buying Guide for everything in Electronics. Send for your FREE copy. Use coupon at right.

**ALLIED  
 RADIO**

pioneers in quality electronic kit development

OUR 39th YEAR

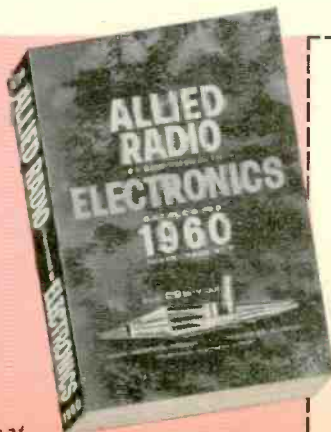

**ALLIED RADIO CORP., Dept. 132-B**  
 100 N. Western Ave., Chicago 80, Ill.

Ship me the following KNIGHT-KITS:

Quantity	Description	Model No.	Price

\$..... enclosed. (For parcel post include postage; express shipped collect)

**Send FREE 1960 ALLIED CATALOG**

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

## Precision cutting... a simple job

with the new

# Centralab

## SK-2

## SHAFT-KUT

## TOOL



Now you can cut controls and control the cut . . . precisely and exactly.

CENTRALAB's Shaft-Kut Tool is a precision instrument, *guaranteed* to make a really simple job of cutting shafts to the exact size you need.

With this tool you can cut any single or dual control . . . or switch shaft, and get cuts that are accurate to  $\frac{1}{64}$ th of an inch! The tool and calibrated jig are made of case hardened tool steel, designed to last a lifetime.

You can't make a wrong cut with the CENTRALAB Shaft-Kut Tool! And the price is less than half what you'd expect to pay for a precision device of this kind . . . a low \$4.95 dealer net. Ask your distributor to show you how easy it is to use this new tool.

# Centralab

B-5931

ELECTRONICS DIVISION OF GLOBE-UNION INC.  
900A E. KEEFE AVE. • MILWAUKEE 1, WIS.  
IN CANADA: 669 Bayview Ave., Toronto 17, Ont.

CONTROLS • ROTARY SWITCHES • CERAMIC CAPACITORS  
PACKAGED ELECTRONIC CIRCUITS • ENGINEERED CERAMICS

## ELECTRONICS

(Continued from page 101)

on the table formed the receiving antenna. A piece of plastic about 3 feet square was placed over it and the animal rested on the plastic sheet. The transmitter was attached to the rabbit's belly with adhesive tape (the hair was clipped from that area).

A short antenna from a BC-221 frequency meter was coupled loosely to the receiving antenna, and frequency recordings were made every 2 minutes.

After testing had continued for about 15 minutes, the animal's temperature was taken with a rectal thermometer. Then the rabbit was given a drug which lowered its body temperature rather slowly. Frequency readings every 2 minutes were continued, and temperatures were recorded with the thermometer every  $\frac{1}{2}$  hour. The entire test took 3 hours.

Results were most encouraging. They showed definitely that every time the animal was excited by being handled its temperature went up and after handling promptly dropped back and continued to decrease. It showed the rate and amount of temperature decrease, and the effects of excitement.

### Make it smaller

The transmitter was still too large for the average white mouse. So while university researchers continued their tests with the first transmitter, which was dubbed "Mousenik I," work began on a smaller unit. Resistors of 1/10 watt had been used, and the ceramic capacitors and coil were about as tiny as we could find. It became a matter of using the shortest possible leads, careful soldering, a tiny mercury battery, and only enough plastic to hold the unit together.

"Mousenik II" was completed and tipped the scales at 6 grams, complete with plastic and battery. It was only one-third the weight of the first unit. But with more clipping and use of clear Krylon in place of the plastic (several coats were sprayed on), "Mousenik III" was completed and weighed in at 3.3 grams, with battery!

Now the white mice are about to have a new role in life. The present tiny unit does not even seem to be an inconvenience to the transmitting mouse.


The unit has a range of about 1 foot without any antenna. With an antenna, and a carbon microphone in series with a 3-volt battery to the coil, the unit was voice-modulated and a readable signal received at about 40 or 50 feet.

No attempt has been made to measure the unit's power output. The input is 0.3 ma at 1.3 volts, which means of course that the mercury battery will not need frequent replacement.

The white mice, rabbits and guinea pigs in the University of Arizona laboratories can now broadcast to all who will listen, and can give a message of vital importance to researchers. All of which means that medical research will profit indirectly by amateur radio —hams have again served. **END**

# ALL-TRANSISTOR VOLTAGE REGULATOR FOR YOUR CAR

By DANIEL MEYER\*

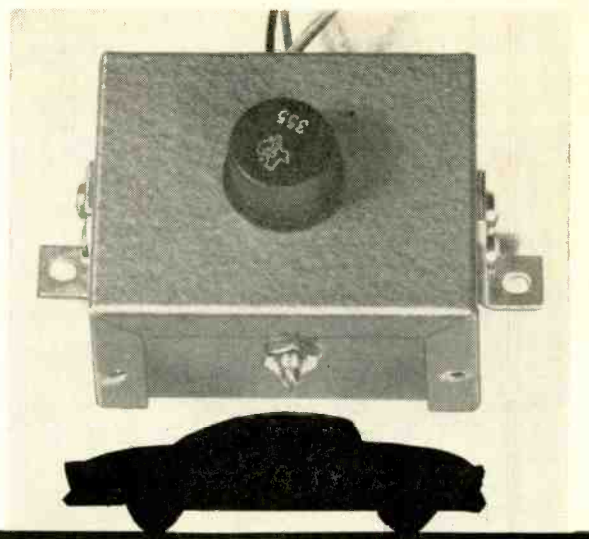

*Four-transistor circuit replaces the tricky vibrating contact in your car's voltage regulator*

If the battery in your car has ever boiled over and run dry, or slowly lost its charge, I am sure that you realize the importance of your generator's voltage regulator. This device keeps the generator's output voltage constant under all load and speed conditions encountered during normal driving.

A dc generator's output is usually regulated by controlling the amount of current flowing in the field winding. More field current increases the intensity of the magnetic field in the pole pieces. The armature cuts more lines of magnetic flux per revolution, and the output voltage goes up. This is all true if the speed of rotation is constant. Below a certain speed the generator does not deliver more than a few volts no matter how much field current flows in the field windings. At higher speeds less field current is needed to produce the same output voltage because the armature cuts the lines of flux faster.

Desirable characteristics for a regulator are:

- ▶ Good regulation under all load and speed conditions
- ▶ No radio interference
- ▶ Reliability and long service life
- ▶ Easy adjustment
- ▶ Low cost

Which quality is the most important

\*Research engineer, Southwest Research Institute.

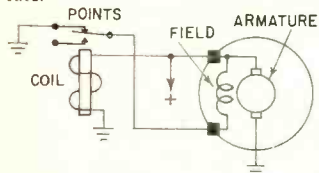



Fig. 1—This type voltage regulator is found in cars, small boats and most light aircraft.

Fig. 2—The carbon-pile type regulator is used in most military aircraft.

depends on the application. Cars, small boats and most light aircraft use the vibrating-point type regulator. This regulator (Fig. 1) works reasonably well and is very cheap to produce. The relay coil is connected to the generator's output, and the normally closed contact points are in series with the field winding. The contact points and the relay's sensitivity are set so the points will open at the output voltage desired from the generator. This results in a very rapid opening and closing of the points as the voltage rises and falls about the operating points. The arc created at the points helps smooth the regulating action and cannot be suppressed with a capacitor if proper operation is expected.

This type of regulator is difficult to adjust and doesn't hold an adjustment too well. The arc at the points causes radio noise. This is especially objectionable on sensitive mobile radios used by hams. There is no way to change the setting on this regulator except by varying the point gap or relay armature tension.

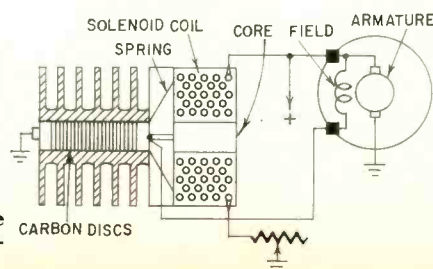A better regulator is the carbon-pile type. It is used in most military aircraft. Its construction is shown in Fig. 2. The amount of spring pressure on the stack of carbon discs controls the resistance of the stack. The stack is in series with the generator's field winding. Varying its resistance controls the field current and thus the output volt-




age, which is fed to a solenoid whose core is connected to the compression spring. Changes in the output voltage move the core and spring in or out, depending on whether the voltage goes up or down.

The regulating action of this type of regulator is smoother than the vibrating-point kind and it does not generate radio noise, but it does have moving parts that wear out. The carbon discs burn and pit with use and must be replaced periodically. The output voltage can be adjusted over a limited range with a potentiometer in series with the solenoid winding. Initial adjustments must be made by a trained person with special equipment. Incorrect adjustment can destroy the carbon discs, and make it necessary to replace the stack again. This regulator also costs much more than the simple point type.

## All-transistor regulator

By using a power transistor as the resistance in series with the field (Fig. 3), most of the disadvantages of the previously discussed regulators are overcome. Basically the output voltage is sensed and compared with a reference voltage. The difference between the two is amplified and drives the transistor's base. Any change in the output voltage is instantly corrected for by a change in the transistor's emitter-collector resistance. Regulation is very close because of the high amplification of the transistor circuit. Output voltage can be adjusted after the regulator is installed. The reliability and service life of the unit are limited only by the quality of the transistors and components used. Heat drift of the transistor characteristics is no problem unless it is extreme. Drift in the reference diode could cause variations in output, but this is not likely in a properly designed circuit.

Let's see how the regulator works.

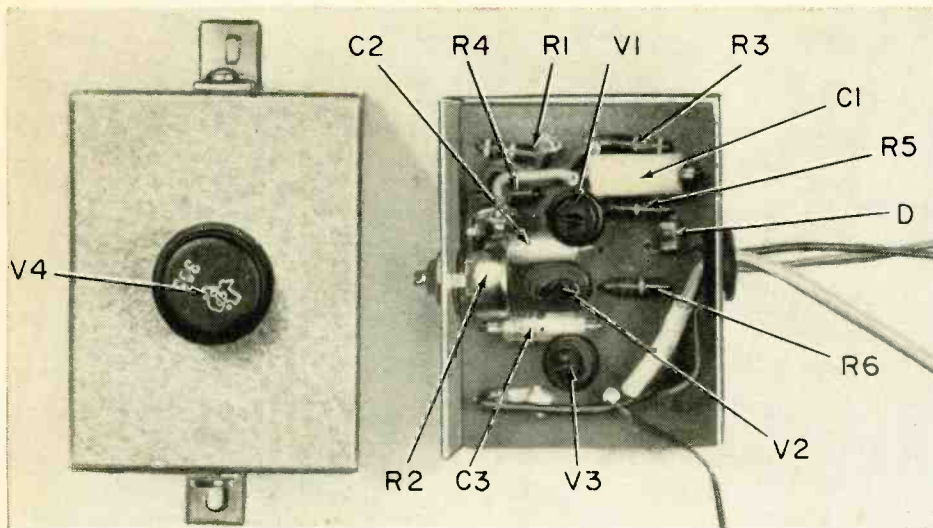

A few parts easily fit into the miniature case. Resistor R7 is not called out as it was added to the regulator circuit after the photographs were taken.


A few leads, a transistor and a potentiometer are the only components that extend outside the regulator case.

The generator's output voltage is dropped across resistors R1, R3 and potentiometer R2. Transistor V1's base is connected to the arm on the potentiometer, and its voltage will vary with the output of the generator and the potentiometer setting. V1's emitter voltage is clamped at a predetermined level by reference diode D. This diode is similar in action to a voltage-regulator glow tube, but operates at a much lower level. It keeps V1's emitter at a constant voltage level while the base voltage is varying in proportion to the generator's output.


This produces a signal that is amplified by V1 and direct-coupled to V2's base. The signal is amplified by V2 and fed to V3's base. Transistor V3 is connected as an emitter follower. The circuit has some current gain, but its main purpose is to couple the high impedance of V2's collector circuit to the low impedance of V4's base circuit. A higher output voltage will make V1 conduct more current, raising V2's emitter-to-base voltage so V2 also passes more current in its collector circuit. This reduces V3's emitter-to-base voltage so less current flows in its collector circuit, and also in V4's base circuit. V4's emitter-collector resistance rises, reducing the field current, and output voltage returns to normal.

Lower output voltage does just the opposite and increases field current. Capacitors C1, C2 and C3 prevent hunting and any tendency to oscillate.

Other transistors can be substituted for the types specified as long as voltage or current ratings are not exceeded. The power transistor (V4) must have a reasonably high beta, since the operating voltage for its collector drops as more current flows in the field winding. If an inefficient transistor is used here, there might be difficulty in getting enough drive to produce full generator output under full-load conditions. (The

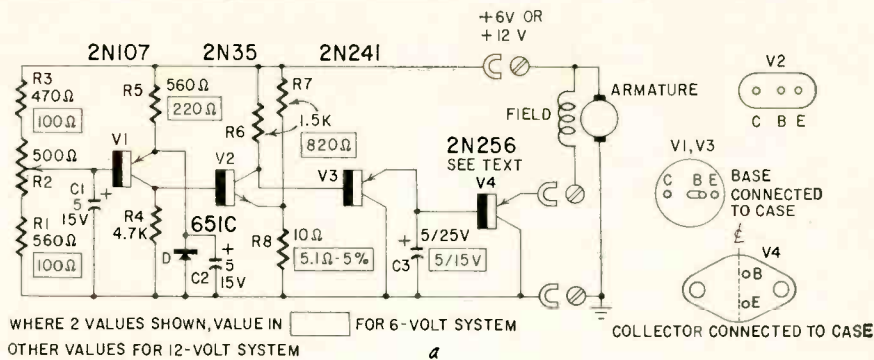

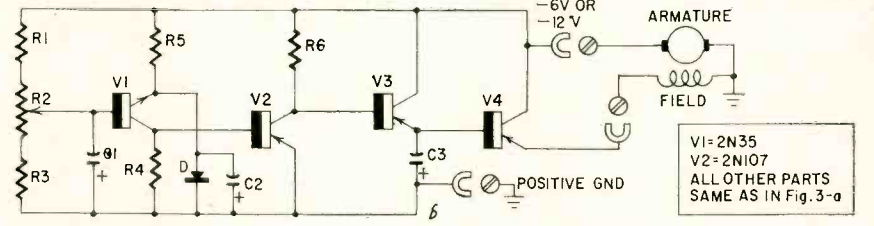WHERE 2 VALUES SHOWN, VALUE IN [ ] FOR 6-VOLT SYSTEM  
OTHER VALUES FOR 12-VOLT SYSTEM



- R1—560 ohms \*100 ohms
- R2—pot, 500 ohms
- R3—470 ohms \*100 ohms
- R4—4,700 ohms
- R5—560 ohms \*220 ohms
- R6—1,500 ohms \*820 ohms
- R7—1,500 ohms \*820 ohms
- R8—10 ohms \*5.1 ohms, 5%
- C1, 2—5  $\mu$ f, 15 volts, electrolytic
- C3—5  $\mu$ f, 25 volts, electrolytic
- \*5  $\mu$ f, 15 volts, electrolytic
- D—reference diode (Texas Instruments 651C)
- V1—2N107
- V2—2N35
- V3—2N241
- V4—2N256 (see text)
- Case, 2 1/8 x 2 3/4 x 1 1/8 inches
- Miscellaneous hardware
- \*Indicates values to use for regulator for 6-volt systems.

author informs us that more suitable transistors have been developed since the article was written, and suggests that a 2N364 could well be used in the V2 position, and a Delco DS-501 used for V4.—Editor)


Before building the regulator you have to know which of the four variations of generator system circuitry is in your car. The generator field may be internally grounded, or it may be connected to the armature terminal. In addition there are both positive- and negative-ground systems.

To determine which system your car uses, connect an ammeter in series with the field circuit on the present regulator. Since the system's polarity can be determined by checking the connections

at the battery you can find out which way the generator field is connected by observing which way the ammeter must be connected to read in the right direction.

For example, if the battery's positive terminal is connected to the engine block or chassis, and the ammeter reads up scale when its negative lead is connected to the generator and its positive lead to the regulator—the field is connected to the armature terminal. If the ammeter connections have to be reversed, the field is grounded internally.

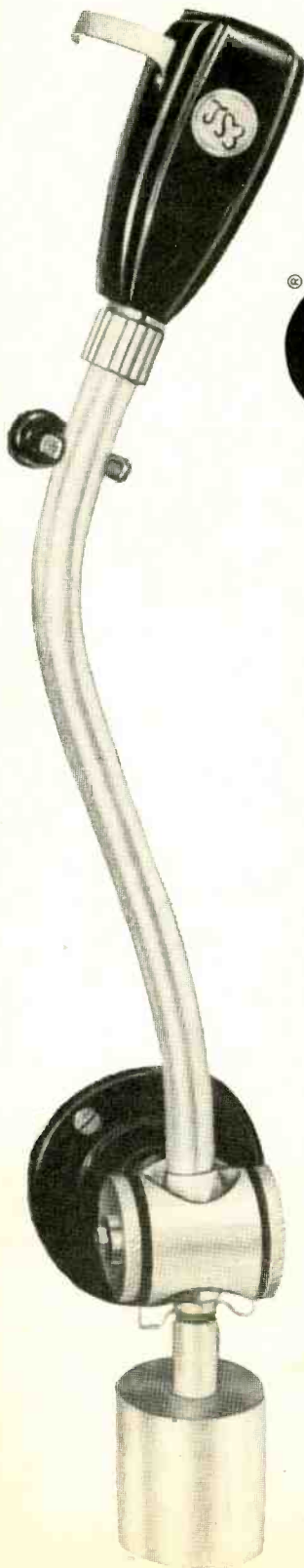The schematics shown (Figs. 3-a and 3-b) are for either negative ground, field connected to the armature, or positive ground, field-grounded generator circuits. If the system on the




**"The ESL arm will permit any cartridge to sound its best and at the same time reduce record wear to a minimum. One couldn't ask more of a tone arm."**



**FOR LISTENING AT ITS BEST**  
**Electro-Sonic Laboratories, Inc.**  
 Dept. E • 35-54 Thirty-sixth Street • Long Island City 1, N. Y.

—Equipment Audit test report by MODERN HI-FI magazine

## ELECTRONICS

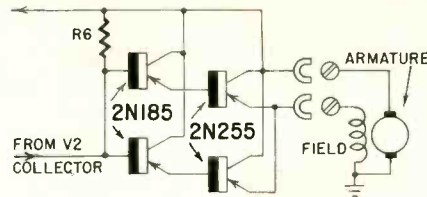

**Fig. 4—If total power drain is 1.8 amps or higher use this output circuit for the regulator.**

car is one of the other two types, the field connection inside the generator must be changed before this regulator can be used. The power transistor's collector must be insulated from the case in the positive ground circuit. This is done with a mica washer.

After the ammeter, used to check the field connections, is properly connected, leave it in the circuit and check the maximum field current. To do this start the engine and turn on all electrical units on the car—lights, heater blower, radio, etc. Now slowly speed up the engine and note the reading on the ammeter when a click is heard from the regulator box on the car. This is the reverse-current relay cutting in. If the reading is 1.8 amps or more, the dual-driver power transistor circuit shown in Fig. 4 must be used.

### Construction kinks

The unit shown was built into a 2 1/8 x 2 3/4 x 1 5/8-inch case which also acts as a heat sink for the power transistor. All parts except the power transistor are mounted on a phenolic board in the model shown in the photographs. The small transistors were soldered directly in place to protect them against vibration. Sockets can be used if desired. Parts placement is not critical, and any convenient construction method will do just as well as the printed board used in my version. The connections to the emitter and base pins of the power transistor are made with single pins broken out of a miniature seven-pin tube socket. Put spaghetti over the pins to insure that no shorts develop when the box is assembled. All parts must be firmly in place since this unit will be subjected to rather violent motion at times.

When wiring the potentiometer, make sure that full counterclockwise rotation places the wiper tap closest to the positive line. This will give an increase in generator voltage when the potentiometer is turned clockwise on the completed unit. The photographs show a type 355 transistor in the power stage. This type is obsolete, but can be replaced by a 2N256. If a 355 is available or on hand it can be used on a 12-volt regulator, but would be worked too close to its maximum current ratings if it were used on a 6-volt unit. Any of the transistors listed in the parts list will work well on either 6- or 12-volt units.

(Continued on page 114)


## 3 POPULAR **SECO** TESTERS

...Top Choice of  
 Service Technicians  
**EVERYWHERE**



### COMPLETE, PORTABLE TUBE TESTER

**MODEL  
 107**

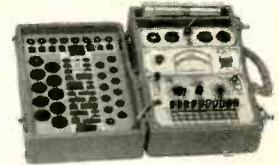


Provides 3 important tests: amplifier types tested for gain by Dynamic Mutual Conductance method—power types tested for cathode current by Cathode Emission method—all types tested for shorts and grid error by Grid Circuit Test developed and patented by Seco. Dynamic Mutual Conductance Test pre-wired for fast set-up. Cathode Emission Test done by free point pin-selector method—will not be obsolete. Self-contained in portable case.

MODEL 107—Wired and factory tested . . . . . \$139.50 NET

### NEW! LOW-COST GRID CIRCUIT AND TUBE MERIT TESTER

**MODEL  
 78**

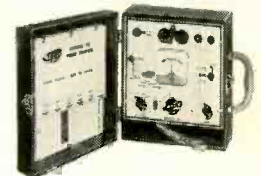


Designed expressly for TV servicing—easy to set-up and simple to use, a highly accurate professional tester! Complete coverage of all modern TV tube types as well as all heater type radio tubes including hybrid types, using only 5 sockets. Incorporates patented Seco Grid Circuit Test plus reliable Cathode Emission test also checks filament continuity and provides open element test. One easy-to-read meter. Two-stage DC amplifier isolates meter from tube under test to protect meter—provides a wide range of load currents and test conditions. Complete in a portable carrying case, with pin straighteners, and index-chart for quick set-up data.

MODEL 78—Wired and factory tested . . . . . \$69.50 NET

### NEW! DYNAMIC TRANSISTOR CHECKER

**MODEL  
 100**

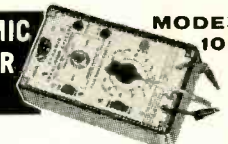

This low-cost transistor checker safely tests PNP and NPN transistors either "in or out" of circuit. Covers wide range of types: small signal including "drift" types, medium power; and power types. Provides positive check for "opens," shorts, and gain—condition indicated by means of a visual indicator plus jacks for meter or scope. Also provides GO-NO-GO test at practical currents—and permits matching of similar types. Will not be obsolete—no set-up or roll charts required! Compact, lightweight, complete, and ready-to-use.

MODEL 100—Wired and factory tested . . . . . \$19.95 NET

Sold only  
 through **Electronic  
 Parts Distributors**

Write today for  
**FULL DETAILS**



**SECO MANUFACTURING**  
 5015 Penn Avenue South, Minneapolis, Minnesota

NAME \_\_\_\_\_  
 ADDRESS \_\_\_\_\_  
 CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

East Canada: Daveco Agencies, Ltd., Montreal, Quebec  
 West Canada: Ron Merritt Co., Vancouver 1, British Columbia

# Plain Facts about ELECTRONICS and CREI

*—why you need advanced  
electronics education*


*—how you can get it without  
quitting your present job*

**N**O DOUBT you know what is happening in electronics. You know that the electronics industry is growing with extraordinary rapidity. You know that regardless of the ups and downs of the business cycle, openings are always found for men with solid, advanced electronics education.

You know that every computer needs installation and maintenance. You know that every missile carries the end result of years of electronics planning and development. You know that every piece of radar equipment, every servo-mechanism, every astronomical device, requires not only electronics designers and builders but also electronics maintenance personnel as well. You know that our new awareness of outer space is founded on the inner workings of satellites. Rockets make them possible and elec-

tronics guides them and makes them intelligible.

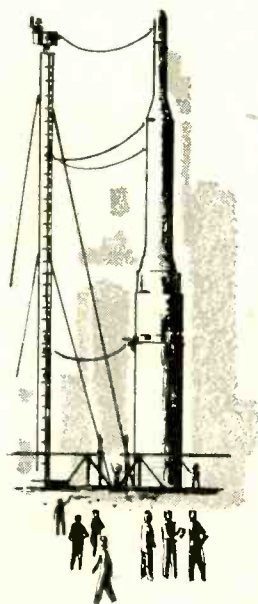And you know that the day of the mediocre electronics man is done. Added responsibilities and salary increases go to men with both **theoretical and practical** knowledge.



CREI home study courses make you eligible for positions which require **advanced** electronics education. You need not quit your present job. You can meet your family responsibilities while gaining knowledge of electronics engineering technology so essential for career advancement.

#### **CREI'S QUALIFICATIONS**

We are now in our 34th year. 1958 marked the start of CREI Atomics, a division of CREI devised to meet the need for advanced home study education in nu-

clear engineering technology. 1958 also marked the opening of our European Division, bringing advanced professional electronic education to Western Europe.

Since 1927 we have directed the technical education of thousands—as individuals and in groups—in electronics engineering technology. We developed the first civilian pilot course for radio mechanics for the Army Signal Corps in 1941, supplied 300,000 texts to the U. S. Navy in a special course for radio technicians in the South Pacific in 1943, trained hundreds of technicians during World War II for the Signal Corps. We co-founded the National Council of Technical Schools, which first established scholastic and business standards for the technical school field. We were among the first three technical institutes whose curricula were accredited by the Engineers' Council for Professional Development. In 1946 we instituted the group training programs now used by companies which represent the cream of the electronics

and aviation industries. In 1957 we initiated a plan which permits direct personal supervision for home study final exams.

What does this record of achievement mean to you as a CREI student?

It means that industry and the Armed Services alike respect CREI men. It means that your CREI diploma is a door opener.

Significantly, Help Wanted ads often specify "CREI education or equivalent required." Our Placement Bureau, which helps graduates and advanced students find more desirable positions, is always available to CREI men. While no placement guarantees will be made by CREI or any other reputable institution, for many years the demand for CREI graduates and advanced students has far exceeded the supply.

Paul S. Lewis, Jr., a research assistant in an AEC-sponsored nuclear physics research program—and a CREI student—writes, "Like most large-scale physics projects, this machine (a proton accelerator) is largely electronics. The need for electronics technicians on basic scientific research projects will no doubt continue to grow."

Charles E. Lawson, another CREI student, brings out another point: "The fact that I am enrolled with CREI was met with enthusiasm on the part of my employer, Wright Airborne Electronics. A former student of CREI is now chief engineer for the company."



### CREI HOME STUDY ADVANTAGES

Technical education is accomplished on your own time, during hours chosen by you. You waste no time in travel. You have plenty of time to do your best. Your work is under the supervision of a regular staff instructor who guides your progress step by step. Courses are prepared by experts, presented in easy-to-understand form, kept up to date by periodic revision. Experience in more than three decades of home-study teaching, during which



time we have corrected and commented on many hundreds of thousands of examinations, enables us to avoid difficult-to-understand text matter in our lessons.

### CREI STUDENTS

Our active home study roster today numbers more than 20,400 professional electronics engineers and technicians, all over the world and in every phase of electronics, about one-third military, the rest civilian. Their median age is 28. In 1958 they devoted approximately 1,572,465 hours to 104,831 lesson texts, answered (and were individually graded upon) 1,048,310 searching questions and engineering problems. They studied electronics engineering technology—transistors, microwaves, forward scatter, computers, servomechanisms, radar, electronic navigational devices, and the entire field of modern electronics. New students enrolled during the year

are on the missile ranges of Vandenburg AF Base and Cape Canaveral. They are at Alamogordo and China Lake, at SAC bases around the world. They are in the research laboratories and manufacturing plants where the latest electronic equipment is designed and produced. They maintain electronic equipment for United Air Lines and Trans-Canada Air Lines. They share in electronics at All-America Cables and Radio, Inc., and The Martin Co. They work for U.S.I.A. (Voice of America) and Columbia Broadcasting System, for Gates Radio and Federal Electric, to name but a few. All of the firms mentioned offer their personnel CREI technical education under company plans. CREI men are found by the hundreds among field engineers of major electronic manufacturers. They're across the world—and across the street. They are the men you must compete with to hold your place in the electronics profession. Wouldn't you like to be as well qualified?

### QUALIFICATIONS FOR CREI

College degree is not essential. If you have had basic electronic education, practical experience in electronics, and a high school education, you can probably qualify. A good way to find out: Use the postage-paid card. It will bring you the free book which has launched thousands on their advanced careers: "Insurance For Your




Future in the New World of Electronics." Please fill out the card carefully, checking appropriate items and providing essential data. Tuition is reasonable and may

be paid monthly. It takes just one \$10-a-week raise to repay your investment in CREI education and leave you a substantial bonus the first year. Available to veterans under GI bill.
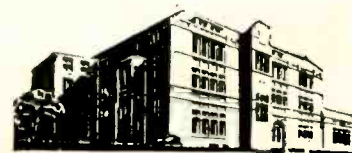
### LATEST CREI COURSE

Automation and Industrial Electronics Engineering Technology. Complete course, covering all electronic phases of automation. Special emphasis on theory, functioning and applications of servomechanisms and computers. Also noteworthy—lessons on machine control, instrumentation, data processing and telemetry.




### RESIDENCE SCHOOL

For those who can attend classes, CREI operates residence programs in Washington, D. C. Day and evening classes start at regular intervals. Qualified graduates earn AAS degree in 27 months. Electronics experience not required for admission.
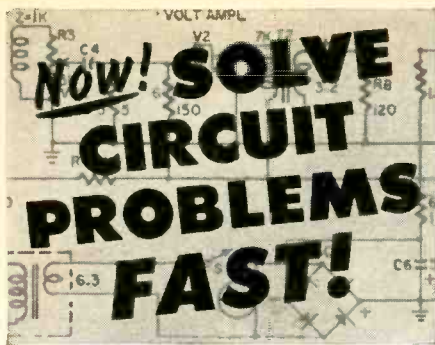
### CAPITOL RADIO ENGINEERING INSTITUTE


Founded 1927  
ECPD Accredited Technical Institute Curricula  
Dept. 1402 G1 BB  
3224 16th St., N.W.  
Washington 10, D. C.



Goodbye to trial-and-error methods. Every circuit calculation you need can now be done accurately with
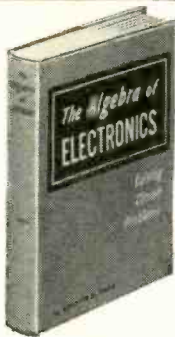
### THE ALGEBRA OF ELECTRONICS

YOU'LL BE AMAZED at how easy it is to figure resistances, load inductances, impedances, etc. for ANY part of ANY electronic circuit. With this new book, THE ALGEBRA OF ELECTRONICS, you will quickly gain the tools, techniques and shortcuts needed.



#### Three Great Books in One!

First, it's a textbook. All practical mathematical techniques explained clearly step-by-step; easy to follow by those with no more math training than high-school algebra and simple differential calculus.

Second, it's a handbook. Graphs and tables answer common electronic problems for those not wishing to work out complex derivations themselves.

Third, it's a review. Every equation is discussed, along with its practical on-the-job applications. 100 problems are shown with methods and answers provided.

THE ALGEBRA OF ELECTRONICS was written by Chester H. Page, Consultant to the Director of the National Bureau of Standards. Dr. Page discusses basic laws and fundamental principles, practical methods of solving simultaneous equations. He develops elementary Fourier wave-form analysis, shows effects of frequency selectivity, modulation, and analyzes tubes, transistors and power supplies.

Try It FREE for 10 Days

Whether you're a repairman, technician, or engineer, you'll find THE ALGEBRA OF ELECTRONICS both profitable and interesting. Send coupon for a FREE 10-DAY EXAMINATION. No obligation — unless you want to keep the book. Mail coupon today to

Van Nostrand  
Dept. 182, Princeton, N.J.  
Established 1848

- 127 TOPICS**  
340 Pages  
252 Illustrations
- Nonlinear Resistance
  - Network Topology
  - Mesh Currents
  - Kirchoff's Law
  - Voltage Variables
  - Triangularization
  - Simultaneous Equations
  - Kramer's Rule
  - Thevenin's Theorem
  - Wheatstone Bridge
  - Conjugacy
  - Black-Box Variables
  - Image Impedances
  - Attenuators
  - Capacitance
  - Dielectrics
  - Sinusoidal Voltage
  - Energy Storage
  - Series-Tuned Circuits
  - Series Resonance
  - Complex Phasors
  - Mutual Inductance
  - Transformers
  - Critical Coupling
  - F-M Discriminator
  - Impedance Matching
  - Hyperbolic Functions
  - Diodes
  - Amplifiers
  - Transistors
  - Thermal Noise
  - Demodulation — many more

## ELECTRONICS

(Continued from page 109)

Installing the generator regulator on your car is easy. First remove the wire connected to the terminal marked FLD on the regulator in the car. Connect this wire to the wire coming from the emitter of the power transistor. Now connect the positive wire to the terminal marked ARM on the old regulator. Make sure the Minibox is grounded, or better yet, connect a wire from the ground on the circuit board to the case of the old regulator. Note that the old regulator is not removed. This is because the reverse-current relay

and the current-regulator coil are also in the same box.


Setting the regulator requires a multimeter and a screwdriver. Connect the meter to the ARM terminal, and start the engine. Run the engine fast enough to get a steady reading on the meter. Now turn the potentiometer on the regulator until the desired output voltage is reached, and lock the adjustment. If a locking type potentiometer is not used, seal it with Glyptol or corona dope. The generator on a 6-volt system is usually set to 7.25 volts, and to 14.4 volts for a 12-volt system. END

## MODEL TRAIN CONTROL

Very realistic starting, coasting and braking effects are obtained in a model train system by this automatic R-C time-delay control composed of the 150- $\mu$ f capacitor and the various resistors. The voltage applied to the track changes smoothly between any of the switch positions. When entering "stop" position (7), the stop obtained is a realistic coasting stop. Faster braking

is obtained in positions 8 and 9.

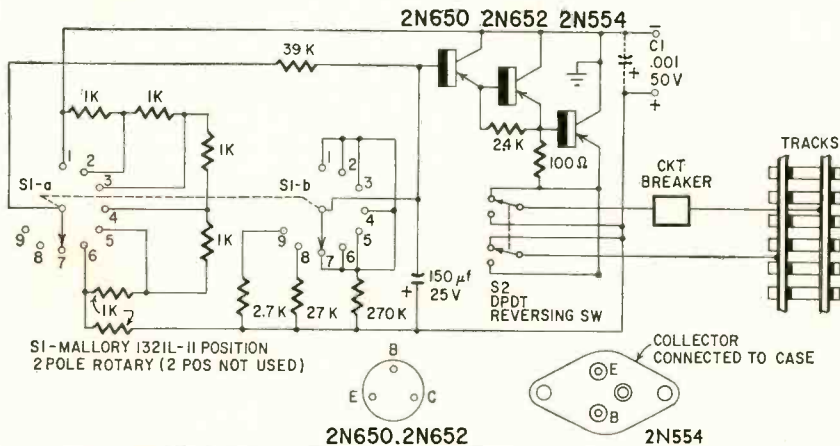The power supply should be well filtered. However, you can get satisfactory results with unfiltered supplies by including capacitor C1. Values of R1, R2 and R3 can be changed to obtain different braking speeds. The 2N554 transistor should be fastened to the aluminum chassis for proper heat sinking.—Motorola Semiconductors



**\$11.90** Buys You an Acoustic-Designed 12" Bookshelf Enclosure Kit

14" H  
21" W  
11 3/4" D  
20 lbs.

If the need is for something bigger try the Model Two. Its 4 1/2 feet of baffle area gives you quality reproduction in combination with a 12" speaker. Brass-ferruled legs give it a clean, modern appearance. Meets the highest Home-wood standards.

29" H (with legs), 20" W, 12 1/2" D. 25 lbs.  
Price: 17.95 in birch

All you need to build is a Hammer-Screwdriver—and 30 minutes! That's how easy it is with a Homewood design.

Satisfaction Guaranteed or your money back in ten days. Send check or money order (no COD's). Freight collect.

D. VAN NOSTRAND COMPANY, INC.,  
Dept. 182, PRINCETON, N. J.  
(In Canada: 25 Hollinger Rd., Toronto 16)

Send for free examination—THE ALGEBRA OF ELECTRONICS. If I don't feel it can make electronic calculations clearer, easier, and faster, I may return it within 10 days; owe nothing. Otherwise, I will pay \$2.75 down, plus small delivery cost, and \$3 per month for 2 months.

Name ..... (Please Print Plainly)  
Address .....  
City ..... Zone ..... State .....

SAVE! Enclose \$8.75 WITH coupon and we will pay ALL shipping costs. Same ten-day money-back privilege.

Model One: Acoustically correct bass-reflex baffle for 12" or 8" speaker at a come-and-get-it price. Use it for a second speaker in your stereo system; for an extension speaker; for top sound reproduction from a first speaker. 3/4" plywood with natural veneer finish on four sides eliminates unwanted resonance and provides an attractive appearance in horizontal or vertical use. Easily assembled, custom-designed to leave no end-plies visible.

Price: 11.90 in birch 15.90 in walnut

Complete finishing kit guaranteed to give a beautiful, durable luster to every kind of unfinished furniture. Contains two cans of varnish, sealer, brush, sandpaper, oil stain, and precise, easy-to-follow instructions. Available in Mahogany, Walnut, Blonde, Blonde Oak, Fruitwood, Maple, Cherry and Ebony. Specify when ordering. Price: \$3.98


**HOMWOOD INDUSTRIES** Inc.

26 Court Street, Brooklyn 1, N. Y.

Please send me:  Fin. Kit.....  
 Model One Bookshelf Enclosure (Birch  Walnut   
 Model Two Enclosure  Homewood Catalog  
My check  or money-order  for..... is enclosed.

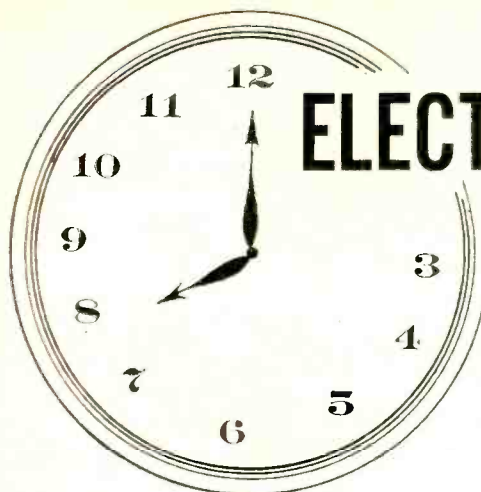Name.....  
Address.....  
City..... Zone..... State.....





# ELECTRONIC ALARMS in CLOCK RADIOS

*The buzzer is out. In both vacuum tube and transistor sets, audio oscillators are making that early morning awakening signal*

By HENRY O. MAXWELL

THE new line of Westinghouse clock radios feature audio oscillators instead of the conventional buzzer type alarms. Fig. 1 shows the audio and alarm circuits of the V-2239-6 chassis used in the H-677T4 and similar models. When you wish to be awakened by the alarm instead of the radio, turn the set off with the ON-OFF-AUTO switch and turn the volume control fully counterclockwise. This opens S2-a and S2-b.

In the morning, when it's time to get up, the clock mechanism turns on the

radio by connecting the B-minus bus and the heater-string return to one side of the ac line. Since S2-a is open, the plate of the 50C5 output tube is connected to the grid of the 12AV6 audio amplifier through C8 and C6.

Any minor disturbance in the 50C5 plate circuit is amplified by the 12AV6 and fed to the grid of the 50C5 in proper phase to sustain oscillations at around 800 cycles.

The NE-2A neon lamp is connected as an 8-cycle relaxation oscillator between the feedback line and ground.

Each time the NE-2A fires, it short-circuits the feedback loop and keys the 800-cycle note on and off at an 8-cycle rate. The keying or interruption rate is determined by the values of R4, C7 and R5. Resistor R6 reduces the amplitude of the alarm signal to a comfortable level. The alarm is turned off and the radio on by advancing the volume control. This closes S2-a to short out R6 and S2-b to ground the feedback line.

### Transistor version

Fig. 2 shows the audio and alarm circuits of the Westinghouse Chantecler 8-transistor battery-operated model H-685P8 clock radios using the V-2396-1 chassis. When the volume control is turned to the extreme left, S1-a and S1-b open and the audio section of the receiver now functions as a 250-cycle oscillator. When S1-a is open, an in-phase signal is fed from one side of the push-pull output transformer through R27 to the base of the driver transistor to sustain oscillations. S1-b inserts R23 in the collector supply lead to the driver transistor. This reduces the collector voltage and drops the alarm volume to a pleasing level.

Advancing the volume control closes S1. S1-a grounds the feedback loop to kill the oscillations and S1-b shorts out R27 to restore normal collector voltage to the driver. END

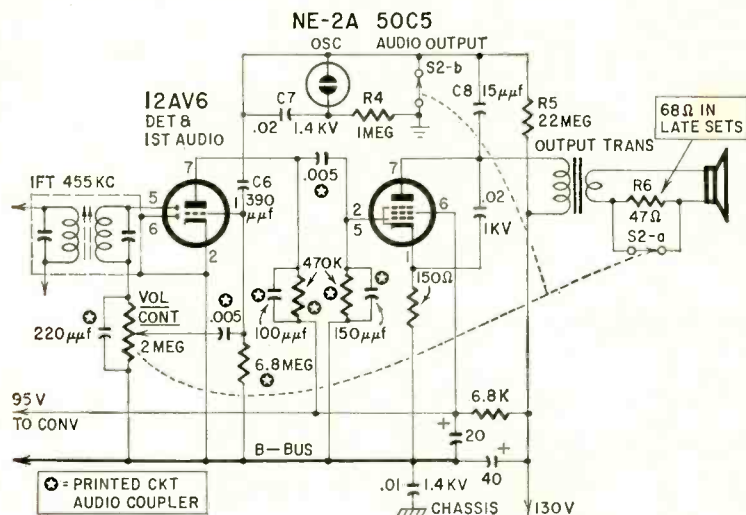


Fig. 1—Audio and alarm circuits of the Westinghouse V-2239-6 chassis.


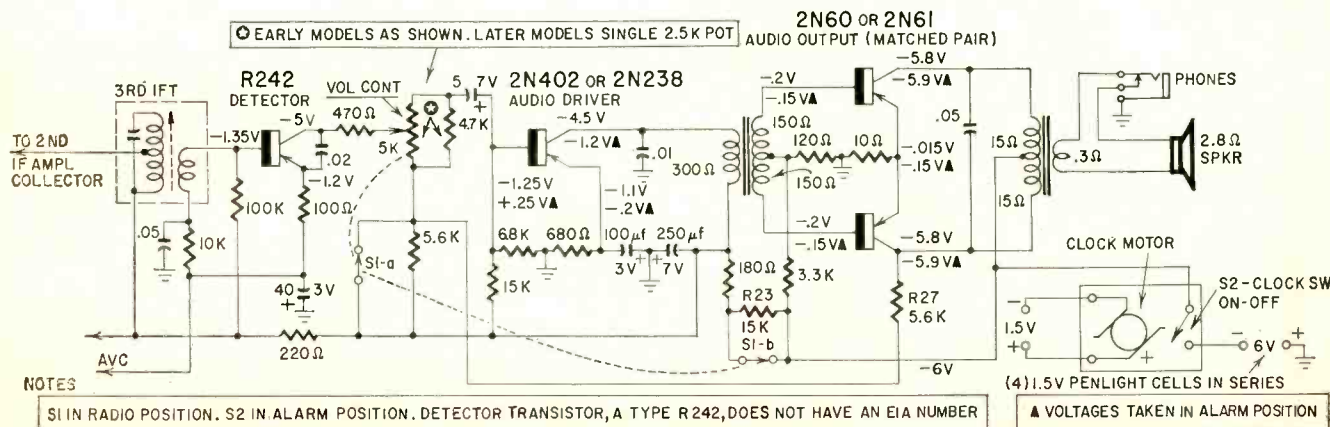


Fig. 2—The setup in a transistor set, the Westinghouse model H-685P8.

# No-Band-Switching PRESELECTOR

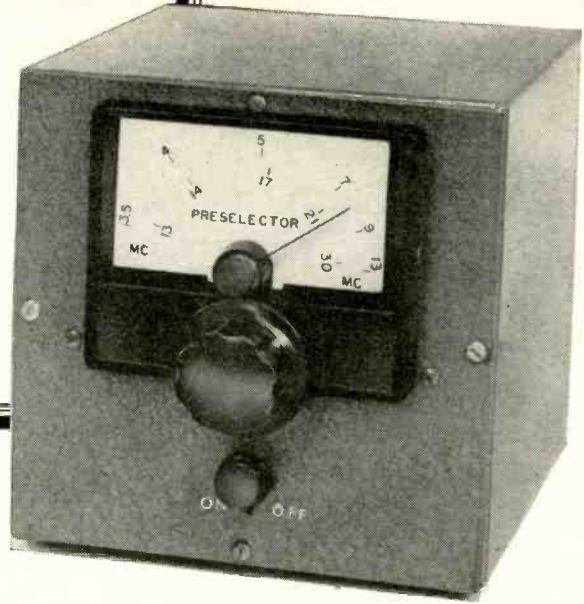

Rf amplifier covers 3.5-30 mc without switching. Boosts receiver gain 6 to 9 S units

By ROBERT ABBATECOLA, W2YIZ

**W**ANT a preselector to cover all frequencies from 3.5 to 30 mc without any band switching? It can be done by using one of the single-ended multi-band tuner circuits, employing the tapped-coil circuit. As shown in the schematic, the larger capacitance, C1-a and C11-a, of the dual capacitors is connected across the full coil and tunes from 3.5 to 13 mc. The smaller section, C1-b and C11-b, is connected to the tap on the coil and tunes from 13 to 30 mc. As you will note, at any particular capacitor setting there are two tuned frequencies. The section in use depends on the frequency to which the receiver is tuned. Therefore, all frequencies within the 3.5-30-mc range are amplified without any band switching.

The one switch on the preselector's panel does two things:

▶ In the off position, ac power is removed from the preselector and the antenna lead-in is connected to the receiver's input.

▶ In the on position, ac power is applied to the preselector, the antenna is connected to its input and the preselector's output is connected to the receiver's input.

Running tests on my receiver at various amateur band frequencies, I got the following increase in S units:

mc	S-units
3.5	8
7.0	9
14.0	8
21.0	6
29.0	7


Consequently, with the preselector hooked up, there is a substantial increase in gain and signal-to-noise ratio, and the image frequency response is reduced at the higher frequencies.

Mount the input coil and variable capacitors on the top of the chassis and the output coil and variable capacitors under the chassis. Also, install a small

copper shield 1 3/4 inches high across the 6CB6 socket, connecting pin 3 and the socket's little round center shield to ground. Both steps are needed to shield the input signal from the output signal.

In putting a circuit of this type together, be careful when mounting and placing parts since both input (grid

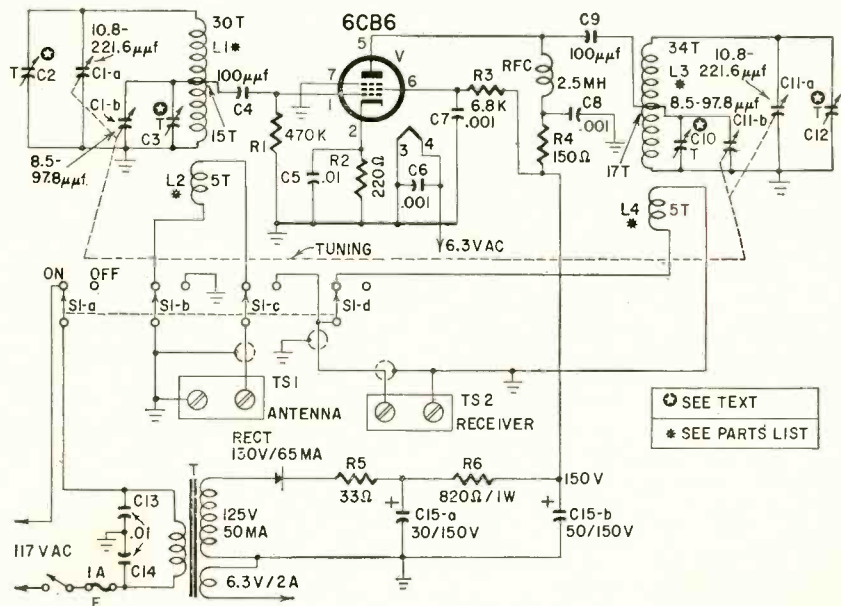circuit) and output (plate circuit) are tuned to the same frequency. All component leads to the tube socket pins and ground should be as short as possible. Input circuit components must be kept as far from the output circuit as possible to prevent oscillation. And don't forget to use short lengths of coax cable




- R1—470,000 ohms
- R2—220 ohms
- R3—6,800 ohms
- R4—150 ohms
- R5—33 ohms
- R6—820 ohms, 1 watt

- All resistors 1/2-watt 10% unless noted
- C1, 11—variable capacitors, dual section, 10.8 to 221.6 μmf and 8.5 to 97.8 μmf (Allied Radio No. 61 H011 or equivalent)
- C2, 3, 10, 12—trimmers on C1 and C11 (see text)
- C4, 9—100 μmf ceramic
- C5, 13, 14—.01 μf, 600 volts, disc ceramic
- C6, 7, 8—.001 μf, 600 volts, disc ceramic
- C15—30-50 μf, 150 volts, electrolytic
- F—1 amp
- L1—30 turns Barker & Williamson, coil No. 3012 tapped at 15 turns from ground side

- L2—5 turns No. 22 cotton-covered wound over ground end of L1
- L3—34 turns Barker & Williamson coil No. 3012 tapped at 17 turns from ground side
- L4—5 turns No. 22 cotton-covered wound over ground end of L3
- RECT—130 volts, 65 ma, selenium
- RFC—2.5 mh
- SI—4-pole 2-position rotary, ceramic
- T—power transformer: primary 117 volts; secondary, 125 volts, 50 ma; 6.3 volts, 2 amps (Stancor PS-8421 or equivalent)
- TS1, 2—2-lug terminal strips
- V—6CB6
- Fuse holder
- Socket, 7-pin miniature
- Chassis to suit
- Cabinet to suit
- Miscellaneous hardware

Circuit of the 1-tube preselector.

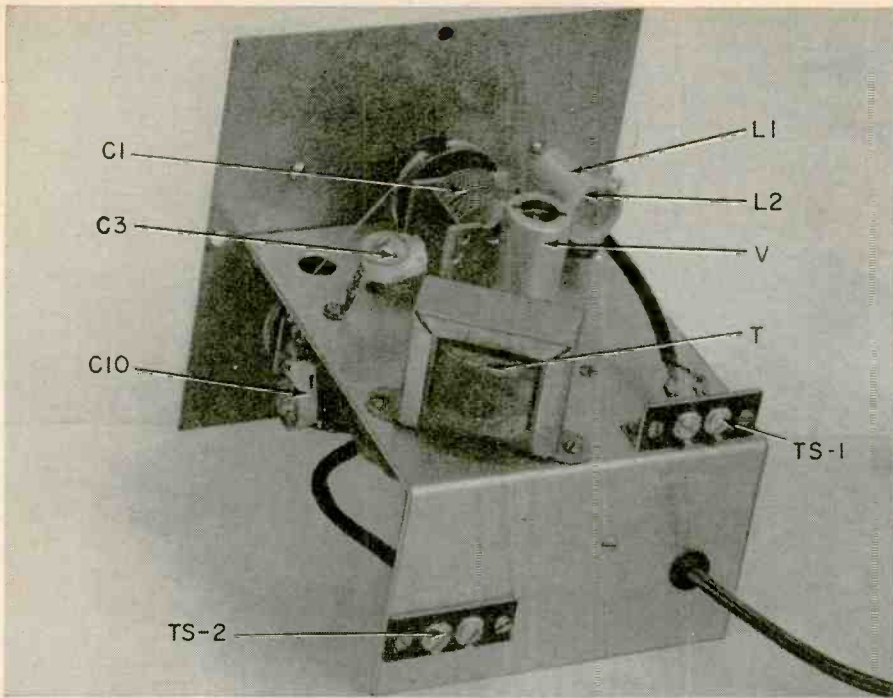

Antenna and receiver terminals are on the back of the preselector's chassis.

between the antenna input to and the output from switch S1.

When making the tap on the Barker & Williamson No. 3012 coil, you will find it helpful to push the winding you intend to tap in toward the center of the coil and solder it by putting the iron through the top of the coil. This makes it easier to make the solder connection for the tap lead, which is covered with spaghetti, without getting solder on adjoining coil turns. The couplings or link coils are wound over the ground side of the main coils. One Barker & Williamson coil No. 3012 is turned into two main coils by cutting it in half.

A standard power supply is used. However, since the current requirements are very modest—6.3 volts ac at 0.3 amp and 150 volts dc at 10 ma—power could also be taken from the receiver to which the preselector is attached, provided it is a power transformer type.

In the photographs, you can see just how the tuning capacitors are ganged. Two small dial drums (one on each shaft) are connected with a length of dial cord. A small spring is attached to one of the drums and the dial cable to keep the cable taut. A Millen vernier dial facilitates tuning. The cabinet is a 6 x 6 x 6-inch utility box.


**Align before using**

Alignment is comparatively simple. Connect a short length of coax cable from the preselector's output to the receiver's antenna input to help eliminate any tendency toward oscillation. Then, turn on the preselector. Feed a modulated 13-mc signal from a signal generator into the preselector's input and tune the receiver to the same frequency. Set the preselector so its variable capa-

citors are at minimum capacitance, fully opened position. Adjust trimmers C2 and C12 for maximum signal to the receiver, using the smallest input possible. Use the receiver's S meter as an indicator. If the receiver does not have one, connect an ac output meter to the speaker's voice coil and use it instead. With the preselector tuning capacitors left in the same position, switch the signal generator to 30 mc and tune the receiver to that frequency also. Then follow the same procedure you used on C2 and C12 for C3 and C10.

If a signal generator is not handy, use steady signals received at approximately 13 and 30 mc to align the preselector. In my unit the variable capacitors did not have trimmers, so I mounted 1.5-7- $\mu\mu\text{f}$  ceramic trimmers across the variable capacitors.

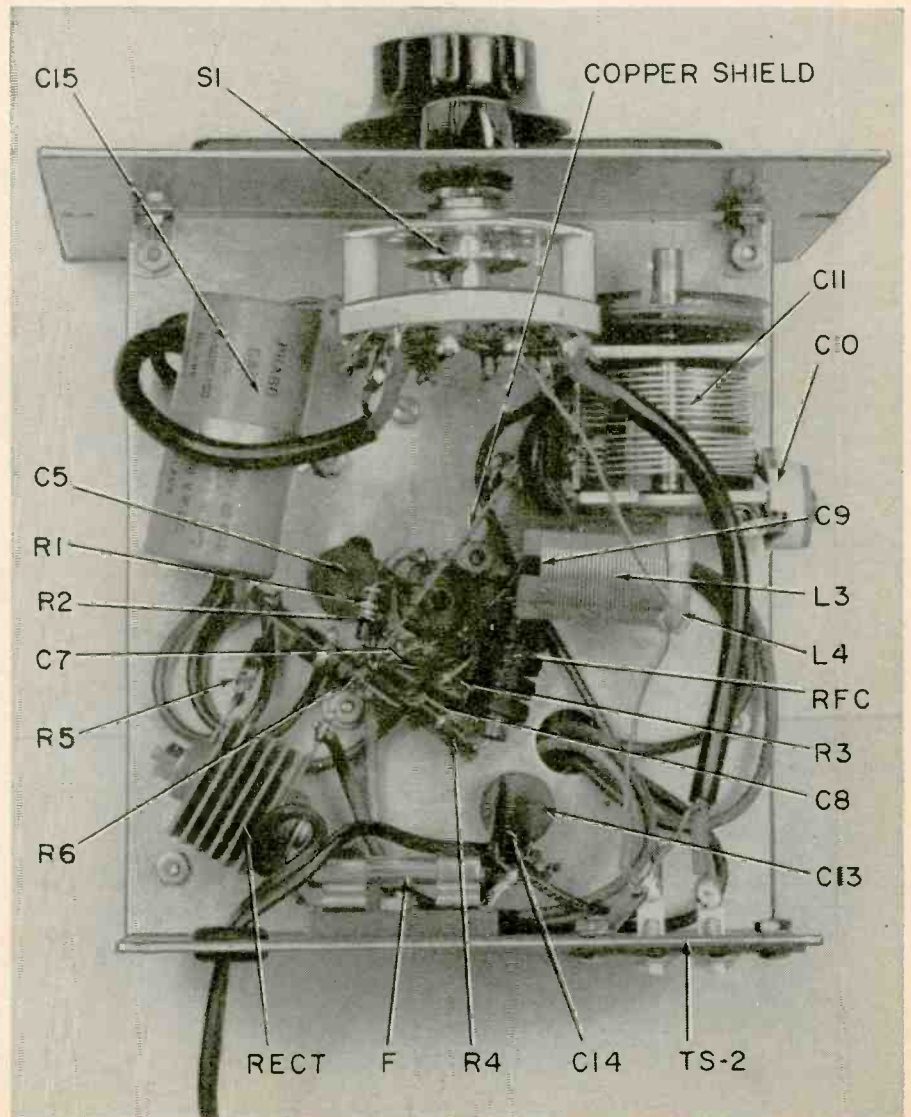To use the preselector, hook up the antenna (any kind will work), tune the receiver to the frequency desired and then the preselector until a maximum signal is indicated. END



Underchassis view showing a suggested parts layout.


# RAPID



# REPAIR

*20 minutes and some plastic resin rebuilds a broken radio or TV cabinet.*

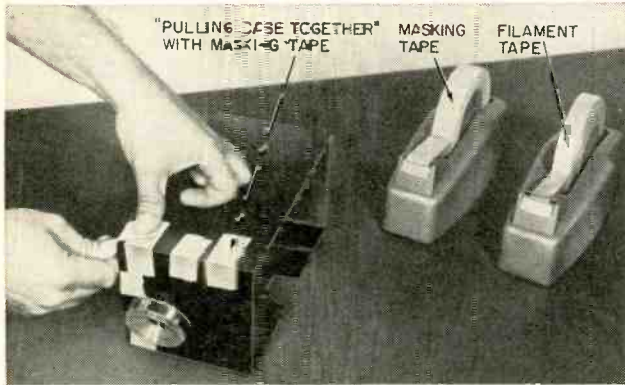By **EDWIN BOHR**

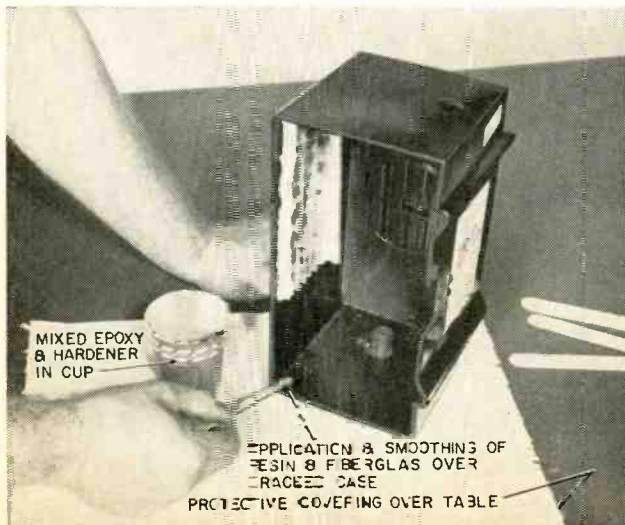


**Fig. 1**—The first step is to fasten the pieces of the case together with masking tape or filament-reinforced tape.



**Fig. 2**—Equipment and materials for mixing the resin.

**Fig. 3**—All resin is applied to inside surfaces of the cabinet.



**N**OT a week passes in an active repair shop without running into a customer with a cracked or broken TV or radio cabinet. And none of them wants to wait—sometimes several months—for a replacement cabinet.

If the job can be done quickly and without a patched-up look, the best solution is a cabinet repair. Plastic resins now available make such repairs attractive, easy, quick and profitable. The cost of material is negligible.

No special talents with woodworking, plastics or metals are required, and the resin works equally well on any of these materials. Just use reasonable care in mixing and applying them.

The completed cabinet repair will be almost invisible and the original cracks should be noticeable only on close inspection. The broken sections will bond to greater strength than the original cabinet.

Readers will be skeptical of these statements. We have all seen "cabinet repairs" smeared with speaker cement, plastered with adhesive tape, or melted and streaked from the action of powerful solvents. Give any of them a strong push and they fall apart.

The resins we are going to describe, are quite unlike any of the cements, adhesives or gunks used for electronic service applications. (Nearly all of these depend upon an evaporating solvent or vehicle.) They are liquid and remain liquid (even in an open container) until mixed with a hardener or catalyst. Mixed with the hardener, the resin gels and cures to a hard plastic within a matter of hours.

Because they are not glues, furniture clamps or great pressures are unnecessary while the resin solidifies.

They have high adhesive qualities, mechanical strength is good (compared with extremely poor for most service cements) and shrinkage is low. They adhere to both metals and nonmetals.

To make the resins even stronger, Fiberglas cloth, filaments or fluff may be added as reinforcement, producing a material stronger than steel in some respects.

Two classes of resin are readily available, the polyester and epoxy. The epoxy types have higher tensile strength, greater adhesion to metals and, in some instances, are easier

*(Continued on page 122)*

NUMBER **2** OF A SERIES  
OF **CD**

50TH ANNIVERSARY  
PROMOTIONS!

**SUB-MINIATURIZED  
ALUMINUM-FOIL**

CD

**ELECTROLYTICS**

**30%**  
SMALLER

**30%**  
MORE RELIABLE

Cornell-Dubilier aims a 30-30 promotion at you for a big birthday bull's eye—and hits the mark with “Electomites”®—the sub-miniature, *metal-cased* electrolytic capacitors that are *30% smaller* and *30% more reliable* than conventional electrolytics. Fabricated from selected highest-purity aluminum foil and unsurpassed in performance, “Electomite” tubulars also have a “short”-preventing plastic sleeve which makes them perfect for those close-fitting coupling, bypass and filter applications you come across every day in low-voltage, transistorized and printed circuitry.

**HERE'S THE PROMOTION:**

Quantity	Type No.	Capacitance (mfd.) Tolerance: -10%, +150%	Voltage
4	NLW 40-3	40	3
4	NLW 10-15	10	15
3	NLW 50-15	50	15
3	NLW 100-15	100	15

**ALL 14 for \$8.67**

This 30-30 promotion is good for 60 days. So get the full story—and the promotion—from your Cornell-Dubilier Distributor today! Also ask about C-D's complete, special capacitor line for industrial electronic maintenance.



**CORNELL-DUBILIER ELECTRIC CORPORATION**

AFFILIATED WITH FEDERAL PACIFIC ELECTRIC COMPANY

# NOW YOU CAN HAVE YOUR CHOICE OF CENTURY'S UNIQUE Peak-to-Peak VACUUM TUBE VOLT METERS

Model VT-10  
LINE OPERATED



Model VT-10  
**\$58.50**  
Net

TERMS: \$14.50 within 10 days. Balance \$11 monthly for 4 months.

## FEATURES OF VT-1 and VT-10

- New advanced pentode amplifier circuit
- Large 6" 100-microampere meter, many times more sensitive than meters used in most V.T.V.M.s
- Simplified multi-color easy-to-read 4-scale meter
- No heat operation assures stability and accuracy
- Amplifier rectifier circuit with frequency compensated attenuator — a feature found only in costly laboratory instruments
- Meter completely isolated
- Hand-crafted circuitry eliminates the headaches of printed circuitry
- 1% resistors used for permanent accuracy
- Rugged gray hammertone steel case provides necessary shielding and eliminates plastic case drawbacks of cracking or melting
- Deep brushed long lasting etched aluminum panel
- Matching cover protects instrument face — snaps on and off instantly.

WITH LARGE EASY-TO-READ 6" METER

featuring the sensational new  
**MULTI-PROBE** (Patent Pending)

No extra probes to buy! The versatile  
MULTI-PROBE does the work of 4 probes

- 1 DC Probe
- 2 AC-Ohms Probe
- 3 Lo-Cap Probe
- 4 RF Probe

No longer do you have to cart around a maze of entangled cables, lose time alternating cables or hunting for a misplaced probe. With just a twist of the MULTI-PROBE tip you can set it to function as either a DC Probe, AC-Ohms Probe, Lo-Cap Probe or RF Probe.

### LINE OPERATED

Ideal for use on the test bench. Designed to run cool even under continuous operation . . . Line isolated.

### BATTERY OPERATED

Completely portable . . . Invaluable wherever line connection is undesirable or unavailable . . . Unique circuitry assures low battery drain.

## FUNCTIONS OF VT-1 and VT-10

**DC VOLTMETER** . . . Will measure D.C. down to 1.5 volts full scale with minimum circuit loading, and give accurate readings of scale divisions as low as .025 volts . . . Will measure low AGC and oscillator bias voltages from .1 volts or less up to 1500 volts with consistent laboratory accuracy on all ranges . . . Zero center provided for all balancing measurements such as discriminator, ratio detector alignment and hi-fi amplifier balancing.

**AC VOLTMETER** . . . True Peak-to-Peak measurements as low as 3 volts of any wave form including TV sync, deflection voltages, video pulses, distortion in hi-fi amplifiers, AGC and color TV gating pulses . . . Scale divisions are easily read down to .1 volts . . . Measures RMS at 1/20th the circuit loading of a V.D.M. . . . Unlike most other V.T.V.M.'s there is no loss in accuracy on the lowest AC range.

**ELECTRONIC OHMETER** . . . Measures from 0 to 1000 megohms . . . Scale divisions are easily read down to .2 ohms . . . Will measure resistance values from .2 ohms to one billion ohms . . . Will detect high resistance leakage in electrolytic and by-pass condensers.

**RF and LO-CAP MEASUREMENTS** . . . With these extra VT-1 functions you can measure voltages in extremely high-impedance circuits such as sync and AGC pulses, driving saw tooth voltages, color TV gating pulses, mixer output levels, I.F. stage-by-stage gain and detector inputs.

Model VT-1  
BATTERY OPERATED



Model VT-1  
**\$58.50**  
Net

TERMS: \$14.50 within 10 days. Balance \$11 monthly for 4 months.

## SPECIFICATIONS OF VT-1 and VT-10

- DC Volts — 0 to 1.5/6/30/150/300/600/1500 volts
- AC Volts (RMS and Peak-to-Peak) — 0 to 3/12/60/300/1200 volts
- Ohms — to a billion ohms, 10 ohms center scale — RX1/10/100/1K/10K/100K/1M
- RF — Peak reading demodulator supplied for use on all DC ranges
- Zero Center — available on all DC volt ranges with zero at mid-scale
- Decibels — from -10 Db to +10/22/36/50/62 based on the Dbm unit: ODB-1MW in 600 ohms
- Impedance — 11 megohms DC, 1 megohm AC, 10 megohms Lo-Cap
- Input Capacity — 130 mmfd. RMS, 250 mmfd. Peak-to-Peak, 25 mmfd. Lo-Cap

Model CT-1

# IN-CIRCUIT CONDENSER TESTER

Here is an IN-CIRCUIT CONDENSER that DOES THE WHOLE JOB! The CT-1 actually steps in and takes over where all other in-circuit condensers fail. The ingenious application of a dual bridge principle gives the CT-1 a tremendous range of operation . . . and makes it an absolute 'must' for every serviceman.

### in-circuit checks:


- ✓ Quality of condensers even with circuit shunt resistance . . . (This includes leakage, shorts, opens, intermittents)
- ✓ Value of all condensers from 200 mmfd. to .5 mfd.
- ✓ Quality of all electrolytic condensers (the ability to hold a charge)
- ✓ Transformer, socket and wiring leakage capacity

### out-of-circuit checks:

- ✓ Quality of condensers . . . (This includes leakage, shorts, opens and intermittents)
- ✓ Value of all condensers from 50 mmfd. to .5 mfd.
- ✓ Quality of all electrolytic condensers (the ability to hold a charge)
- ✓ High resistance leakage up to 300 megohms
- ✓ New or unknown condensers . . . transformer, socket, component and wiring leakage capacity
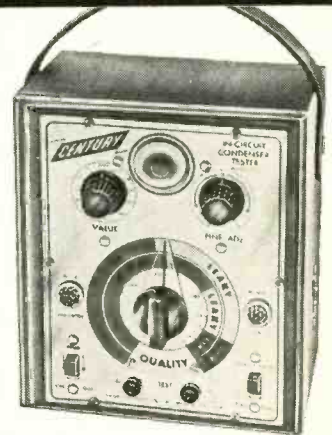
### OUTSTANDING FEATURES

- Ultra-sensitive 2 tube drift-free circuitry
- Multi-color direct scale readings for both quality and value . . . in-circuit or out-of-circuit
- Simultaneous readings of circuit capacity and circuit resistance
- Built-in hi-leakage indicator sensitive to over 300 megohms
- Cannot damage circuit components
- Electronic eye balance indicator for even greater accuracy
- Isolated power line
- Deep brushed long lasting etched aluminum panel
- Housed in sturdy gray hammertone finish steel case . . . comes complete with test leads



Model CT-1  
**\$34.50**  
Net

TERMS: \$9.50 within 10 days. Balance \$5 monthly for 5 months.

# 10 DAY FREE TRIAL ON CENTURY INSTRUMENTS OF YOUR CHOICE

See for yourself at no risk why thousands of servicemen all over the country selected CENTURY test equipment above all others. Send for instruments of your choice without obligation . . . try them for 10 days before you buy . . . only then, if satisfied, pay in easy-to-buy monthly installments — without any financing or carrying charges added.



Model  
CRT-2

# CRT TESTER-REACTIVATOR

## TESTS, REPAIRS and REACTIVATES

- **ALL BLACK AND WHITE PICTURE TUBES** (including 110° tubes) . . . from 8" to 30", whether 12 pin base, 8 pin base, 14 pin base . . . and the very latest 7 pin base.
- **ALL COLOR PICTURE TUBES** . . . Each of the red, green and blue color guns is handled separately.

### CHECK THESE EXCLUSIVE FEATURES

- ✓ **THE MULTI-HEAD** (Patent Pending) . . . **A SINGLE PLUG IN CABLE AND UNIQUE TEST HEAD** — A tremendous advance over the maze of cables and adapters generally found with other testers.
- ✓ **WATCH IT REACTIVATE THE PICTURE TUBE** — You actually see and control the reactivation directly on the meter as it takes place. This allows you for the first time to properly control the reactivation voltage and eliminates the danger of stripping the cathode of the oxide coating. It also enables you to see whether the build-up is lasting.
- ✓ **CONTROLLED "SHOT" WITH HIGHER VOLTAGE FOR BETTER REACTIVATION** — Stronger than any found in other testers — high enough to really do the job — yet controlled to avoid damage to the picture tube.
- ✓ **UNIQUE HIGH VOLTAGE PULSE CIRCUIT** — Will burn out inter-element shorts and weld open circuits with complete safety to the picture tube.

Housed in hand-rubbed oak carrying case — complete with **MULTI-HEAD**

Model CRT-2


**\$57.50**  
Net

TERMS: \$13.50 within 10 days. Balance \$11 monthly for 4 months.

THE CRT-2 DOES ALL THIS RIGHT IN THE CARTON, OUT OF THE CARTON OR IN THE SET

- |            |  |
|------------|--|
| TEST       | } • For quality of every black and white and color picture tube, employing the time proven dynamic cathode emission test principle.<br>• For inter-element shorts and leakage up to one megohm. Separate short test provided for each element in the picture tube.<br>• For life expectancy. |
| REPAIR     |  |
| REACTIVATE |  |
- Will clear inter-element shorts and leakage.
  - Will weld open elements.
  - The "SHOT" (high voltage controlled pulse) method of reactivation provided by the CRT-2 will restore picture tube to new life in instances where it was not possible before. The high voltage is applied without danger of stripping the cathode as you always have perfect control of the high voltage pulse.
  - The "BOOST" method of reactivation also provided by the CRT-2 is used effectively on tubes with a superficially good picture but with poor emission and short life expectancy. It will also improve definition, contrast and focus greatly and add longer life to the picture tube.

- ✓ **VISUAL LIFE TEST** — Enables both you and your customer to see the life-expectancy of any picture tube right on the meter . . . helps eliminate resistance to picture tube replacement when necessary.
- ✓ **SPECIAL LOW SCREEN VOLTAGE TUBES** — Will handle new type picture tubes with special low voltage of approximately 50 volts.
- ✓ **SEPARATE FILAMENT VOLTAGES** — including the very latest 2.35 volt and 8.4 volt types as well as the older 6.3 volt types.
- ✓ **NEW 'SF' PICTURE TUBES** — Accommodates the different base pin connections of this new type picture tube.

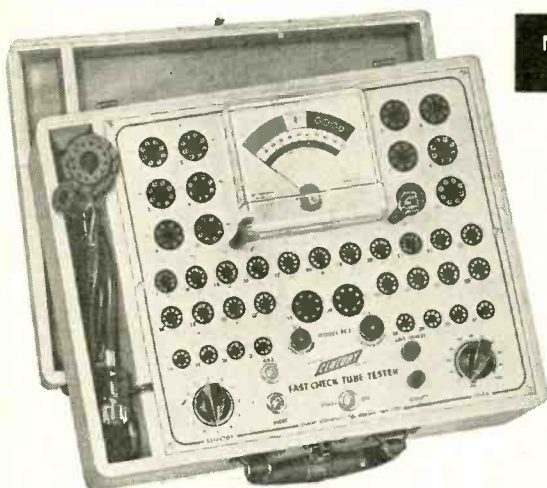

Model  
FC-2

# FAST-CHECK TUBE TESTER

Simply set two controls . . . insert tube . . . and press quality button to test any of over 900 tube types completely, accurately . . . IN JUST SECONDS!

The FAST-CHECK enables you to cut servicing time way down, eliminate unprofitable call-backs and increase your dollar earnings by selling more tubes with very little effort on your part. You make every call pay extra dividends by merely showing your customer the actual condition and life expectancy of the tube. The extra tubes you will sell each day will pay for the FAST-CHECK in a very short time.

### PICTURE TUBE TEST ADAPTER INCLUDED WITH FAST-CHECK

Enables you to check all picture tubes (including the new short-neck 110 degree type) for cathode emission, shorts and life expectancy . . . also to rejuvenate weak picture tubes.

### RANGE OF OPERATION

- ✓ Checks quality of over 900 tubes types, employing the time proven dynamic cathode emission test. This covers more than 99% of all tubes in use today, including the newest series-string TV tubes, auto 12 plate-volt tubes, OZ4s, magic eye tubes, gas regulators, special purpose hi-fi tubes and even foreign tubes.
- ✓ Checks for inter-element shorts and leakage.
- ✓ Checks for gas content.
- ✓ Checks for life-expectancy.

### SPECIFICATIONS

- No time consuming multiple switching . . . only two settings are required instead of banks of switches on conventional testers
- No annoying roll chart checking . . . tube chart listing over 900 tube types is located inside cover. New listings are added without costly roll chart replacement
- Checks each section of multi-section tubes and if only one section is defective the tube will read "Bad" on the meter scale
- 41 phosphor bronze beryllium tube sockets never need replacement
- 7-pin and 9-pin straighteners mounted on panel
- Large 4 1/2" D'Arsonval type meter is the most sensitive available, yet rugged — fully protected against accidental burn-out
- Special scale on meter for low current tubes
- Compensation for line voltage variation
- 12 filament positions
- Separate gas and short jewel indicators
- Line isolated — no shock hazards
- Deep brushed long lasting etched aluminum panel.

**NOTE:** The Fast-Check positively cannot become obsolete . . . circuitry is engineered to accommodate all future tube types as they come out. New tube listings are furnished periodically at no cost.

Housed in hand-rubbed oak carrying case complete with CRT ADAPTER

Model FC-2

**\$69.50**  
Net

TERMS: \$14.50 within 10 days. Balance \$11 monthly for 5 months.

**MAIL  
FREE  
TRIAL  
COUPON  
TODAY!**

## CENTURY ELECTRONICS CO., INC.

111 Roosevelt Ave., Dept. 102, Mineola, N. Y.

- |                          |  |         |
|--------------------------|--|---------|
| <input type="checkbox"/> | Model VT-10 Vacuum Tube Volt Meter . . . . .               | \$58.50 |
|                          | \$14.50 within 10 days. Balance \$11 monthly for 4 months. |         |
| <input type="checkbox"/> | Model VT-1 Battery Vacuum Tube Volt Meter . . . . .        | \$58.50 |
|                          | \$14.50 within 10 days. Balance \$11 monthly for 4 months. |         |
| <input type="checkbox"/> | Model CT-1 In-Circuit Condenser Tester . . . . .           | \$34.50 |
|                          | \$9.50 within 10 days. Balance \$5 monthly for 5 months.   |         |
| <input type="checkbox"/> | Model CRT-2 CRT Tester-Reactivator . . . . .               | \$57.50 |
|                          | \$13.50 within 10 days. Balance \$11 monthly for 4 months. |         |
| <input type="checkbox"/> | Model FC-2 Fast-Check Tube Tester . . . . .                | \$69.50 |
|                          | \$14.50 within 10 days. Balance \$11 monthly for 5 months. |         |

Prices Net F.O.B. Mineola, N. Y.

Yes, I want to take advantage of your 10 day FREE try-before-you-buy offer. Ship on approval the instruments I have checked. After I have tried the equipment for 10 full days I will either send you the down payment and agree to pay the balance in the monthly payments shown, or I will return the units and owe nothing.

Name  Please print clearly

Address

City  State

ALL TUBES INDIVIDUALLY BOXED . . . UNCONDITIONALLY GUARANTEED ONE YEAR SEND FOR FREE COMPLETE TUBE LIST & ORDER BLANK INQUIRY PUTS YOU ON MAIL-LIST

# TELTRON SMASHES PRICES ON TUBES for '60!

**GIFT OFFER**  
ONE 6B6G tube will be shipped FREE with any \$10.00 or more order accompanying this ad.

**FREE**  
\$7.50 list value. Bonus box includes 3 6SN7 tubes & 25 assorted resistors & condensers with each order of \$25.00 or more of receiving tubes and special purpose tubes only.



## MOST OFTEN USED TUBES

OZ4	.45	6B8C	.49	9U8	.49
1B3GT	.52	6B8E	.48	10DE7	.79
1R5	.51	6B8C8	.48	12AB5	.44
174	.43	6BE6	.46	12AT7	.44
1U4	.51	6B8E	.46	12AT7	.44
1U5	.51	6B8E	.46	12AT7	.44
1X2	.75	6B8E	.46	12AT7	.44
2AF4	.62	6B8E	.46	12AT7	.44
2BN4	1.02	6B8E	.46	12AT7	.44
3A6	.43	6B8E	.46	12AT7	.44
3B5	.43	6B8E	.46	12AT7	.44
3BN6	.58	6B8E	.46	12AT7	.44
3BZ6	.45	6B8E	.46	12AT7	.44
3C8E	.90	6B8E	.46	12AT7	.44
3OT6	.51	6B8E	.46	12AT7	.44
3V4	.51	6B8E	.46	12AT7	.44
4B2B	.48	6B8E	.46	12AT7	.44
4B7	.69	6B8E	.46	12AT7	.44
4C86	.75	6B8E	.46	12AT7	.44
4NB	.51	6B8E	.46	12AT7	.44
5A8	.59	6B8E	.46	12AT7	.44
5A78	.64	6B8E	.46	12AT7	.44
5B7	.64	6B8E	.46	12AT7	.44
5B8K7	.58	6B8E	.46	12AT7	.44
5J6	.64	6B8E	.46	12AT7	.44
5T8	.59	6B8E	.46	12AT7	.44
5U4G	.43	6B8E	.46	12AT7	.44
5U4GA	.43	6B8E	.46	12AT7	.44
5U4GB	.43	6B8E	.46	12AT7	.44
5U4G	.43	6B8E	.46	12AT7	.44
5V4	.59	6B8E	.46	12AT7	.44
5X8	.49	6B8E	.46	12AT7	.44
5Y8	.47	6B8E	.46	12AT7	.44
6A4	.30	6B8E	.46	12AT7	.44
6A7	.43	6B8E	.46	12AT7	.44
6AF4	1.02	6B8E	.46	12AT7	.44
6AS	.47	6B8E	.46	12AT7	.44
6AM6	.52	6B8E	.46	12AT7	.44
6AL5	.43	6B8E	.46	12AT7	.44
6AM8	.59	6B8E	.46	12AT7	.44
6S07	.60	6B8E	.46	12AT7	.44
6S07	.36	6B8E	.46	12AT7	.44
6S07	.48	6B8E	.46	12AT7	.44

## NEW AND HARD TO GET TYPES PROMPT DELIVERY

1DN5	.60
1C3GT/1B3	.70
2CY5	.50
3AF4	1.02
4DE6	.55
4DT6	.59
5CQ8	.59
6B8J	.64
6B8D5	.74
6C08	.59
6CX8	.64
6D55	.69
6A8	1.02
6C8X	.70
11CY7	.74
8AW8	.59
17AX4GT	.50
17D4.50 50EH5	.59

## APPROX. COST ANY TYPE TUBE CESS REPAIRED

1A6	.93	7B4	.44
1C5GT	.57	7B5	.41
1C7G	.39	7B8	.47
1F5	.39	7C5	.44
1H4G	.39	7F8	.77
1LA6	.66	7H7	.51
1L8	.56	7N7	.44
1LM4	.66	7V7	.82
1LN5	.66	7Y4	.35
1L8	.56	7Z4	.44
1M4	.66	7Z7	.82
1N5	.66	7Z8	.44
6A7	.59	12K7GT	.48
6B7	.40	12Q7GT	.48
6B87	.40	12R7	.48
6B87	.40	12S7	.48
1A53	.60	14A7	.43
6A07GT	.60	14B6	.36
6F6	.42	35Y4	.52
6D6	.59	27	.45
6F5GT	.44	35A5	.48
6F6	.42	35Y4	.52
6S7	.89	37	.59
6S87Y	.50	39/44	.39
6S87	.43	45	.55
6U5	.54	50A5	.48
6U7G	.40	50X6	.53
6V4	.47	50Z6	.44
6V6	.47	71A	.65
6V7	.47	75	.44
6V8	.42	80	.40

Obsolete, seldom used tubes. Immed. delivery.

## Semiconductors for immediate delivery.

1N34	.49
1N38	.95
1N60	.34
1N66	.49
1N82A	1.00
1N253	4.25
1N256	19.95
1N295	.30
1N460A	4.00
1N1096	9.00
2N63	3.75
2N130A	2.00
2N329A	40.00
2N484	1.75
2N622	30.00
2N633	1.35

## Special-purpose, transmitting and industrial Tubes for immediate delivery.

0A2	.70	807	1.00
2A4G	.75	811A	3.25
2D21	.65	813	9.25
2E26	2.50	833A	40.00
2X2	.75	826	1.00
5R4GY1.00	20.50	.85	
6J4	1.00	5675	12.25
12A6	.60	5879	3.00
FG27	8.50	6146	3.85
HY69	1.75	6161	34.50

## NEW PRICE SCHEDULE OF TELEVISION PICTURE TUBES

PICTURE GUARANTEED FOR ONE (1) YEAR			
8DP4	17E4	913.25	21AVP4 519.25
10AP4	17CP4	17.25	21AWP4 18.75
10BP4	17GP4	17.95	21BFP4 19.25
12LP4	17HP4	16.49	21MP4 21.25
14BP4	17JP4	16.49	21PP4 17.25
14CP4	17KP4	17.45	21RFP4 18.75
14QP4	17LP4	13.25	21SFP4 18.75
14RP4	17MP4	16.49	21TFP4 17.25
16CP4	17NP4	16.49	21VFP4 17.25
16DP4	17OP4	15.75	21WFP4 27.25
16EP4	17PP4	15.75	21XFP4 27.25
16FP4	17QP4	17.75	21YFP4 27.25
16GP4	17RP4	17.75	21ZFP4 27.25
16HP4	17SP4	17.75	21AFP4 27.25
16IP4	17TP4	17.75	21BFP4 27.25
16JP4	17UP4	17.75	21CFP4 27.25
16KP4	17VP4	17.75	21DFP4 27.25
16LP4	17WP4	17.75	21EFP4 27.25
16MP4	17XP4	17.75	21FFP4 27.25
16NP4	17YP4	17.75	21GFP4 27.25
16OP4	17ZP4	17.75	21HFP4 27.25
16PP4	17AP4	19.25	21IFP4 27.25
16QP4	17BP4	19.25	21JFP4 27.25
16RP4	17CP4	19.25	21KFP4 27.25
16SP4	17DP4	19.25	21LFP4 27.25
16TP4	17EP4	19.25	21MFP4 27.25
16UP4	17FP4	19.25	21NFP4 27.25
16VP4	17GP4	19.25	21OP4 27.25
16WP4	17HP4	19.25	21PP4 27.25
16XP4	17IP4	19.25	21QFP4 27.25
16YP4	17JP4	19.25	21RFP4 27.25
16ZP4	17KP4	19.25	21SFP4 27.25
17AP4	17LP4	19.25	21TFP4 27.25
17BP4	17MP4	19.25	21VFP4 27.25
17CP4	17NP4	19.25	21WFP4 27.25
17DP4	17OP4	19.25	21XFP4 27.25
17EP4	17PP4	19.25	21YFP4 27.25
17FP4	17QP4	19.25	21ZFP4 27.25
17GP4	17RP4	19.25	21AFP4 27.25
17HP4	17SP4	19.25	21BFP4 27.25
17IP4	17TP4	19.25	21CFP4 27.25
17JP4	17UP4	19.25	21DFP4 27.25
17KP4	17VP4	19.25	21EFP4 27.25
17LP4	17WP4	19.25	21FFP4 27.25
17MP4	17XP4	19.25	21GFP4 27.25
17NP4	17YP4	19.25	21HFP4 27.25
17OP4	17ZP4	19.25	21IFP4 27.25
17PP4	17AP4	19.25	21JFP4 27.25
17QP4	17BP4	19.25	21KFP4 27.25
17RP4	17CP4	19.25	21LFP4 27.25
17SP4	17DP4	19.25	21MFP4 27.25
17TP4	17EP4	19.25	21NFP4 27.25
17UP4	17FP4	19.25	21OP4 27.25
17VP4	17GP4	19.25	21PP4 27.25
17WP4	17HP4	19.25	21QFP4 27.25
17XP4	17IP4	19.25	21RFP4 27.25
17YP4	17JP4	19.25	21SFP4 27.25
17ZP4	17KP4	19.25	21TFP4 27.25
18AP4	17LP4	19.25	21VFP4 27.25
18BP4	17MP4	19.25	21WFP4 27.25
18CP4	17NP4	19.25	21XFP4 27.25
18DP4	17OP4	19.25	21YFP4 27.25
18EP4	17PP4	19.25	21ZFP4 27.25
18FP4	17QP4	19.25	21AFP4 27.25
18GP4	17RP4	19.25	21BFP4 27.25
18HP4	17SP4	19.25	21CFP4 27.25
18IP4	17TP4	19.25	21DFP4 27.25
18JP4	17UP4	19.25	21EFP4 27.25
18KP4	17VP4	19.25	21FFP4 27.25
18LP4	17WP4	19.25	21GFP4 27.25
18MP4	17XP4	19.25	21HFP4 27.25
18NP4	17YP4	19.25	21IFP4 27.25
18OP4	17ZP4	19.25	21JFP4 27.25
18PP4	18AP4	19.25	21KFP4 27.25
18QP4	18BP4	19.25	21LFP4 27.25
18RP4	18CP4	19.25	21MFP4 27.25
18SP4	18DP4	19.25	21NFP4 27.25
18TP4	18EP4	19.25	21OP4 27.25
18UP4	18FP4	19.25	21PP4 27.25
18VP4	18GP4	19.25	21QFP4 27.25
18WP4	18HP4	19.25	21RFP4 27.25
18XP4	18IP4	19.25	21SFP4 27.25
18YP4	18JP4	19.25	21TFP4 27.25
18ZP4	18KP4	19.25	21VFP4 27.25
19AP4	18LP4	19.25	21WFP4 27.25
19BP4	18MP4	19.25	21XFP4 27.25
19CP4	18NP4	19.25	21YFP4 27.25
19DP4	18OP4	19.25	21ZFP4 27.25
19EP4	18PP4	19.25	21AFP4 27.25
19FP4	18QP4	19.25	21BFP4 27.25
19GP4	18RP4	19.25	21CFP4 27.25
19HP4	18SP4	19.25	21DFP4 27.25
19IP4	18TP4	19.25	21EFP4 27.25
19JP4	18UP4	19.25	21FFP4 27.25
19KP4	18VP4	19.25	21GFP4 27.25
19LP4	18WP4	19.25	21HFP4 27.25
19MP4	18XP4	19.25	21IFP4 27.25
19NP4	18YP4	19.25	21JFP4 27.25
19OP4	18ZP4	19.25	21KFP4 27.25
19PP4	19AP4	19.25	21LFP4 27.25
19QP4	19BP4	19.25	21MFP4 27.25
19RP4	19CP4	19.25	21NFP4 27.25
19SP4	19DP4	19.25	21OP4 27.25
19TP4	19EP4	19.25	21PP4 27.25
19UP4	19FP4	19.25	21QFP4 27.25
19VP4	19GP4	19.25	21RFP4 27.25
19WP4	19HP4	19.25	21SFP4 27.25
19XP4	19IP4	19.25	21TFP4 27.25
19YP4	19JP4	19.25	21VFP4 27.25
19ZP4	19KP4	19.25	21WFP4 27.25
20AP4	19LP4	19.25	21XFP4 27.25
20BP4	19MP4	19.25	21YFP4 27.25
20CP4	19NP4	19.25	21ZFP4 27.25
20DP4	19OP4	19.25	21AFP4 27.25
20EP4	19PP4	19.25	21BFP4 27.25
20FP4	19QP4	19.25	21CFP4 27.25
20GP4	19RP4	19.25	21DFP4 27.25
20HP4	19SP4	19.25	21EFP4 27.25
20IP4	19TP4	19.25	21FFP4 27.25
20JP4	19UP4	19.25	21GFP4 27.25
20KP4	19VP4	19.25	21HFP4 27.25
20LP4	19WP4	19.25	21IFP4 27.25
20MP4	19XP4	19.25	21JFP4 27.25
20NP4	19YP4	19.25	21KFP4 27.25
20OP4	19ZP4	19.25	21LFP4 27.25
20PP4	20AP4	19.25	21MFP4 27.25
20QP4	20BP4	19.25	21NFP4 27.25
20RP4	20CP4	19.25	21OP4 27.25
20SP4	20DP4	19.25	21PP4 27.25
20TP4	20EP4	19.25	21QFP4 27.25
20UP4	20FP4	19.25	21RFP4 27.25
20VP4	20GP4	19.25	21SFP4 27.25
20WP4	20HP4	19.25	21TFP4 27.25
20XP4	20IP4	19.25	21VFP4 27.25
20YP4	20JP4	19.25	21WFP4 27.25
20ZP4	20KP4	19.25	21XFP4 27.25
21AP4	20LP4	19.25	21YFP4 27.25
21BP4	20MP4	19.25	21ZFP4 27.25
21CP4	20NP4	19.25	21



## RADIO

spilled resin from the workbench.

Place a cup on the left side of the balance and make sure the sliding weight is completely to the left. Now balance the weight of the empty cup, placing weight on the right side of the balance. Bits of solder or small hardware will do.

Then place additional calibrated weights on the right, equal to the desired amount of resin, and add resin until the scale is again balanced.

As the last weighing step, slide the adjustable weight to the right—an amount equal to the required weight of the catalyst. Next, add catalyst to the resin until the scale balances. Around 5 or 6 grams of resin will be enough to repair the cabinet in the photographs.

### Weights and measures

The gram is a very convenient unit of weight, based on the metric system. Approximately 28 grams equal 1 ounce.

Ordinary coins make convenient gram weights. A nickel weighs 5 grams. (This should be easy to remember!) A dime weighs 2.5 grams, a quarter 6.25 grams, and a fifty-cent piece weighs 12.5 grams.

Follow the directions on the resin container closely. Do not guess at the proportions or amounts.

To a very small extent, we shall violate this warning and suggest that 10% additional catalyst be used when mixing less than 10 grams. This compensates for catalyst that will be lost as a film on the mixing container and not mixed with the resin.

Whenever you see an unmixed drop of catalyst on the side of the cup, gather some resin on the mixing stick and smear it into the catalyst. Then push this into the central pool of resin and continue to stir. Never stir even a very small batch of plastic less than 2 minutes. Thorough mixing is important.

Most readers will not wish to invest in a balance scale. As a substitute, glue or tape two paper cups—one at each end of a foot ruler. Then pivot the ruler at exactly the 6-inch mark on a round pencil. Tape the pencil to the table so it will not roll. Now add bits of wire or solder until the cups balance or, just as good, almost balance.

This simple arrangement will tilt from one side to the other with less than 1/20 gram. This is even more sensitive than the photographic scale. However, it is not as convenient.

Use coins for weights of 2.5 grams or more. For smaller weights, cut a length of solder equal to 5 grams and divide it into five equal lengths. These will serve as gram weights. Divide them further for even smaller weights.

### After mixing

When the resin and catalyst are mixed, immediately spread the mixture over the crack and 1/2 inch either side of the break. *Do this only on the inside of the cabinet.* See Fig. 3.

# FIRST TIME . . . a versatile

# DUAL

# HEAT

## SOLDERING GUN

FOR ONLY  
**\$7<sup>95</sup>**  
LIST  
Model 8200K



...and best of all,  
it's a new

# Weller®

Here from Weller, long time leader in the soldering field, is the newest and finest soldering gun value on the market.

**WELLER DUAL HEAT FEATURE** saves time, gives greater convenience and greatly increases tip life. A touch of your finger on the Triggermatic control switches heat to high (125 watts) or low (90 watts) as your job requires. It adapts instantly to varying needs, and you use high heat only when necessary.

**HIGH EFFICIENCY WELLERTIP** utilizes copper for superior heat transfer and soldering efficiency, plus iron plating for durability. Flat cross-section design gives added strength and rigidity.

**NEWEST DESIGN** with sturdy plastic housing that resists hard knocks. Compact "feel" and comfortable balance aid precision soldering. Like all other Weller guns, this new model features instant heat, and a spotlight illuminates your work.



### KIT INCLUDED

In addition to the Dual Heat Soldering Gun you get:


- Nylon Flux Brush
- Soldering Aid for opening old joints, twisting wires
- All-purpose Solder

On sale now at your  
Electronic Parts Distributor

WELLER ELECTRIC CORP. • 601 Stone's Crossing Rd., Easton, Pa.
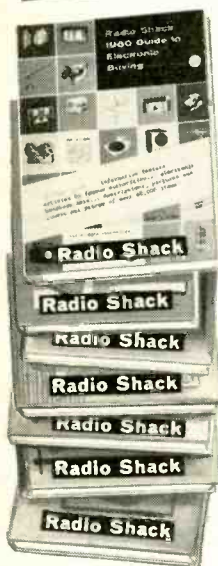
# RADIO SHACK flash!

Send Coupon for Latest  
**FREE**  
ELECTRONICS Catalog  
plus every new issue for 1960



Act today! See the newest, the best, the most complete line of electronic equipment in America—stereo, hi-fi, ham radio, LP records, tapes, optical goods and scores of others. Over 100,000 items—everything for the amateur, the pro, the devotee or just the interested.

Mail the coupon now! We will send you immediately, Free and Postpaid, not only our latest 312 page Electronics Catalog but every new issue for the next 12 months—a full year's Free sub-

scription to the finest in electronics and associated products all at famous money-saving Radio Shack prices. Satisfaction guaranteed on every order or your money back. Invest in the best—and save money too—shop at Radio Shack.

Just one of thousands of RADIO SHACK buys

Transistor Battery Radio  
19.95 Value  
only

**\$9.95**



Exclusive Radio Shack transistor battery radio. Only 2 3/4 x 4 x 1 1/4 inches in size. Weighs less than 10 ounces. Built-in speaker and ferrite antenna. Conelrad markings, handsome molded case.

## RADIO SHACK CORPORATION DEPT. 2E

730 Commonwealth Ave. • Boston 17, Massachusetts

Radio Shack Corporation Dept. 2E  
730 Commonwealth Ave.  
Boston 17, Massachusetts

Please send me, FREE and POSTPAID, your latest Electronics Catalog. Also send me every new issue for the next 12 months—a full year's subscription FREE.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
Postoffice or City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

## RADIO

Now spread Fiberglas filaments or fluff over the resin and work them into it with the wooden stick. Use enough Fiberglas to make a puttylike consistency. As necessary, smooth a slight amount of additional resin over the surface and the job is completed.

To get the Fiberglas filaments, cut coarse Fiberglas cloth (supplied with the kits) into small strips with scissors. The woven structure easily pulls apart, yielding large bundles of filaments.

Besides reinforcement, the Fiberglas keeps the resin from running or dripping while it is still liquid.

Through capillary action, the hairline crack fills flush to the outside surface. The crack is too small, however, for the resin to run out and mar the exterior.

Clear resin is suitable for repairing any color cabinet. Since the resin reduces the discontinuity at the surface, a clear resin-filled hairline crack is hardly noticeable.

If colored resins are attempted, any mismatch in color will cause the crack to stand out in contrast. Green, blue, red and white pigments are available for coloring the resin and possibly can be of some use in special applications.

The resin will usually reach full hardness within 24 hours. Placing the cabinet in a warm part of the room hastens the hardening. But, under no circumstances, place a plastic cabinet

near a heater. This is a direct invitation for a distorted (or even melted) cabinet.


Remove the masking tape, give the case a quick polish and the job is done.

Try patching a junked cabinet at leisure, to sharpen your technique before jumping into a rush customer job. Then, perhaps, you would like to repair the multimeter case that fell from the truck months ago and is now bandaged together with electrical tape?


For a case broken into three or more parts, join two pieces at a time, let the resin harden, and then join the resulting larger pieces. Even large TV cabinets may be handled this way without too much trouble.

Once you get the hang of it, a cabinet can be repaired in 20 minutes, including getting everything together and mixing the resin. The work can easily be handled by a helper or even the distaff section of the shop.

END

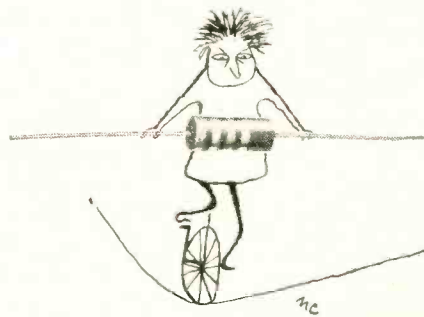
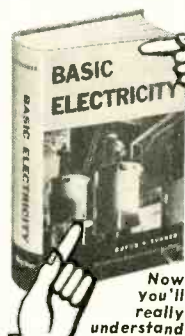
## HERE'S HOW TO GET YOUR START in Radio-Electronics!



The most important training of all!

No matter what you want to do in radio-electronics, this big 396-page BASIC ELECTRICITY manual brings you the kind of down-to-earth training you absolutely must have. Backed with it, you'll read technical articles with new understanding. You'll know what's what about circuits, components, and equipment. Every detail of electric-electronic procedure and operation will be far clearer to you than ever before.

Now you'll really understand circuits—components—equipment!

BASIC ELECTRICITY covers the entire field—from circuits and currents to polyphase and phone principles . . . from tubes to transistors . . . from batteries, instruments and measurements to motors, generators, transformers and all the rest. More than 300 pictures and set-up diagrams make things doubly clear. Then, to top off your basic training, it includes an easily understood 61-page INTRODUCTION TO ELECTRONICS. Read it for 10 days at our risk!


### 10-DAY FREE EXAMINATION

Dept. RE-20, RINEHART & CO., Inc.  
232 Madison Ave., New York 16, N.Y.

Send BASIC ELECTRICITY training manual for 10-day free examination. If I like book, I will then send you \$6.50 (plus postage) in full payment. Otherwise I will return book and owe you nothing. (Save! Send \$6.50 with order and we pay postage. 10-day money-back guarantee.)

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City, Zone, State \_\_\_\_\_  
OUTSIDE U.S.A. \$7.00 cash. 10-day money-back guarantee
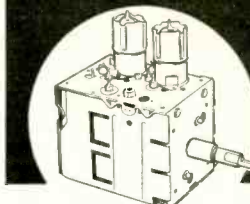
## TARZIAN Offers 48-Hour, Direct Factory Service on Tuner Repairs



only  
**\$8.50**

Price Effective Jan. 1, 1960

That's right. Net, \$8.50 per unit and \$15 for UV combinations, including ALL replacement parts. 90-day warranty against defective workmanship and parts failure. Tuners repaired on approved, open accounts. Replacements offered at these prices\* on tuners not repairable:

- VHF 12 position tuner . . . . . \$22.00
- VHF 13 or 16 position . . . . . 23.00
- VHF/UHF combination . . . . . 25.00
- UHF only . . . . . 15.50

\*Subject to change



Tarzian-made tuners are easily identified by this stamping on the unit. When inquiring about service or replacements for other than Tarzian-made tuners, always give tube complement . . . shaft length . . . filament voltage . . . series or shunt heater . . . IF frequency, chassis identification and allow a little more time for service. Use this address for fast, 48-hour service:

## SARKES TARZIAN, Inc.

Att.: Service Mgr., Tuner Division  
East Hillside Drive  
Bloomington, Indiana


**RADIO**

# A Tough Dog!

By **JAMES A. FRED**

A RECENT radio repair job on an RCA model 8X71 turned out to be a tough dog. An AM/FM table model, it had a bad case of hum modulation—hum that comes in only when a signal is tuned in. The set had been in another service shop before I got it.

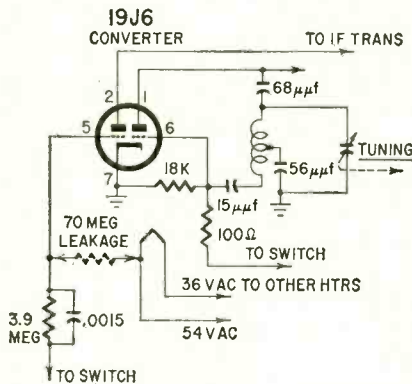Whenever I get a set that has been worked on like this one, I always get a circuit diagram and check it over before I start to work. I soon found



that an electrolytic and two ceramic capacitors were missing from the FM discriminator circuit. I replaced these two parts plus a 35W4 that had been misplaced and found that the hum was still there.

I removed the tubes from the set and tested them on a mutual-conductance tube checker. All tested good.

When a visual examination failed to reveal anything wrong, I resorted to the old trick of listening for hum with a pair of headphones. I connected a .05-µf capacitor in series with one headphone lead and grounded the other. I then touched each pin of the 19J6 converter tube with the unconnected end of the capacitor while I listened for hum. I first tried pins 3 and 4 and naturally got a loud hum since these were the heater pins. I then went through the rest of them in order and heard a hum on pins 5 and 2, with the loudest hum on pin 2. This seemed to indicate that there was something wrong with the 19J6 so I took it out of the socket and checked for leakage with the highest resistance range of my vtm. Between the heater and pin 5 there was a resistance reading of 70 megohms. Between all the other pins, the resistance reading was infinity. This leakage resistance allowed a small portion of the voltage on the heater string to leak through to the grid, where it modulated the incoming signal. The set now worked on AM, but was still dead on FM. I started another wire-by-wire check and found that a bypass capacitor had been soldered from grid to ground instead of from cathode to ground on the socket of the FM if amplifier. Rewiring one lead restored normal operation. **END**



# YOU NEED THIS...

## FREE GIANT ALL NEW 1960 BA CATALOG

*A Complete Buying Guide for Everything in*

# RADIO TV ELECTRONICS

ANNUAL CATALOG 601

**BA**

SINCE 1927

**204 KING-SIZED PAGES**

**EVERYTHING IN RADIO TV AND ELECTRONICS**

**100'S OF NEW ITEMS LISTED HERE FOR 1st TIME**

**21 PAGES OF BARGAINS NOT IN ANY OTHER CATALOG**

**RUSH COUPON TODAY!**

**BURSTEIN-APPLEBEE CO.**

**BURSTEIN-APPLEBEE CO. Dept. M,  
1012-14 McGee St., Kansas City 6, Mo.**

Send Free 1960 B-A Catalog No. 601.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_

Say you saw it in  
**RADIO-ELECTRONICS**  
when answering ads!

## TAPE RECORDERS

**HI-FI COMPONENTS SLEEP LEARN KITS**

**MERITAPE**  
Low cost, high quality recording  
tape, in boxes or cans.

**UNUSUAL VALUES FREE**  
1960 CATALOG

**DRESSNER, 69-02RE 174 St., Flushing 65, N.Y.**

**MAIL ORDER HI-FI**

You can now purchase all your HI-FI from one reliable source and be assured of perfect delivery. Carston makes delivery from NY stock on most HI-FI, Recorders and tape within 24 hours. SEND US A LIST OF YOUR HI-FI REQUIREMENTS FOR OUR WHOLESALE QUOTATION and our FREE wholesale catalogue.

**CARSTON STUDIOS** 125-RD E. 88 St. New York 28, N. Y.

## ENGINEERING

**B. S. DEGREE IN 27 MONTHS**

Prepare for unlimited opportunities of the Electronic Age! Students study engineering under accelerated program leading to B.S. degree in 27 mo.; or standard 4-yr. program leading to B.E. degree in 36 mo. B.S. degree (36 mo.) in Math., Chem., Physics. Year-round classes. Comprehensive training in electronics, television, advanced radio theory and design, math., nuclear physics and elec. eng. Also prep courses. Low rate. Earn board. G.I. approved. Enter March, June, Sept., Dec. Catalog.

**INDIANA TECHNICAL COLLEGE**  
1720 E. Washington Blvd., Fort Wayne 2, Indiana

Please send me free information on B.S. ENGINEERING DEGREE IN 27 MONTHS as checked.

Electronics  Chemical  Aeronautical  Electrical

Civil  Mechanical  Electrical

B.E. DEGREE IN 36 MO. in:  Electrical (Power or Electronics)


Aeronautical  Chemical  Electronics

Civil  Mechanical  Metallurgical

B.S. DEGREE IN 36 MO. in: Math.  Chem.  Physics

Name \_\_\_\_\_

Address \_\_\_\_\_

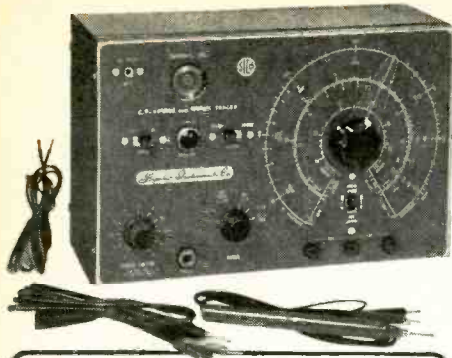

For the first time ever: **ONE TESTER PROVIDES ALL THE SERVICES LISTED BELOW!**

**SUPERIOR'S  
NEW  
MODEL 76**

# ALL PURPOSE BRIDGE

IT'S A **CONDENSER BRIDGE**  
IT'S A **SIGNAL TRACER**

IT'S A **RESISTANCE BRIDGE**  
IT'S A **TV ANTENNA TESTER**

**SPECIFICATIONS:**

in the antenna, so why not check the TV antenna first? 2 Ranges: 2' to 200' for 72 ohm coax and 2' to 250' for 300 ohm ribbon.

**SIGNAL TRACER SECTION**

With the use of the R.F. and A.F. Probes included with the Model 76, you can make stage gain measurements, locate signal loss in R.F. and Audio stages, localize faulty stages, locate distortion and hum, etc. Provision has been made for use of phones and meter if desired.

Model 76 comes complete with all accessories including R.F. and A.F. Probes; Test Leads and operating instructions. Nothing else to buy. Only.....

**\$26<sup>95</sup>  
NET**

**Model 76 BRIDGE . . . Total Price \$26.95—**  
Terms: \$6.95 after 10 day trial, then \$5.00 monthly for 4 months if satisfactory. Otherwise return, no explanation necessary!



**SUPERIOR'S NEW  
MODEL 79**

# SUPER-METER

**WITH NEW 6" FULL-VIEW METER**

*A Combination*

**VOLT-OHM MILLIAMMETER.**

*Plus* **CAPACITY, REACTANCE, INDUCTANCE and DECIBEL MEASUREMENTS.**

*Also Tests* **SELENIUM and SILICON RECTIFIERS, SILICON and GERMANIUM DIODES.**

The Model 79 represents 20 years of continuous experience in the design and production of SUPER-METERS, an exclusive SICO development.

In 1938 Superior Instruments Co. designed its first SUPER-METER, Model 1150. In 1940 it followed with Model 1250 and in succeeding years with others including Models 670 and 670-A. All were basically V.O.M.'s with extra services provided to meet changing requirements.

Now, Model 79, the latest SUPER-METER includes not only every circuit improvement perfected in 20 years of specialization, but in addition includes those services which are "musts" for properly servicing the ever increasing num-

ber of new components used in all phases of today's electronic production. For example with the Model 79 SUPER-METER you can measure the quality of selenium and silicon rectifiers and all types of diodes—components which have come into common use only within the past five years, and because this latest SUPER-METER necessarily required extra meter scale, SICO used its new full-view 6-inch meter.

**Specifications**

D.C. VOLTS: 0 to 7.5/15/75/150/750/1,500.  
A.C. VOLTS: 0 to 15/30/150/300/1,500/3,000.  
D.C. CURRENT: 0 to 1.5/15/150 Ma. 0 to 1.5/15 Amperes.

RESISTANCE: 0 to 1,000/100,000 Ohms. 0 to 10 Megohms.  
CAPACITY: .001 to 1 Mfd. 1 to 50 Mfd.  
REACTANCE: 50 to 2,500 Ohms. 2,500 Ohms to 2.5 Megohms.

INDUCTANCE: .15 to 7 Henries. 7 to 7,000 Henries.  
DECIBELS: -8 to +18, +14 to +38, +34 to +58.


The following components are all tested for QUALITY at appropriate test potentials. Two separate BAD-GOOD scales on the meter are used for direct readings.

All Electrolytic Condensers from 1 MFD to 1000 MFD.  
All Selenium Rectifiers. All Germanium Diodes,  
All Silicon Rectifiers. All Silicon Diodes.

Model 79 comes complete with operating instructions and test leads. Use it on the bench—use it on calls. A streamlined carrying case included at no extra charge accommodates the tester, instruction book and test leads. Only.....

**\$38<sup>50</sup>  
NET**

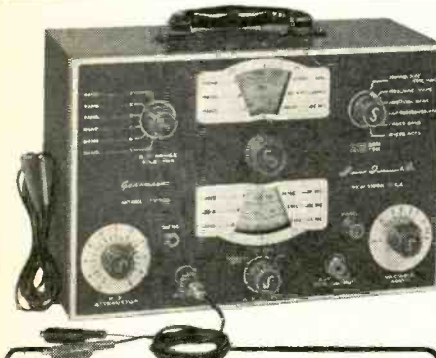**Model 79 — SUPER-METER . . . Total Price \$38.50 —** Terms: \$8.50 after 10 day trial, then \$6.00 per month for 5 months if satisfactory. Otherwise return, no explanation necessary!



# GENOMETER

## 7 Signal Generators in One!

- ✓ R.F. Signal Generator for A.M.
- ✓ R.F. Signal Generator for F.M.
- ✓ Audio Frequency Generator
- ✓ Bar Generator
- ✓ Cross Hatch Generator
- ✓ Color Dot Pattern Generator
- ✓ Marker Generator

A versatile all-inclusive GENERATOR which provides ALL the outputs for servicing:

**A.M. Radio • F.M. Radio • Amplifiers • Black and White TV • Color TV**

**R. F. SIGNAL GENERATOR:** The Model TV-50A Genometer provides complete coverage for A.M. and F.M. alignment. Generates Radio Frequencies from 100 Kilocycles to 60 Megacycles on fundamentals and from 60 Megacycles to 180 Megacycles on powerful harmonics.

**VARIABLE AUDIO FREQUENCY GENERATOR:** In addition to a fixed 400 cycle sine-wave audio, the Model TV-50A Genometer provides a variable 300 cycle to 20,000 cycle peak wave audio signal.

**BAR GENERATOR:** The Model TV-50A projects an actual Bar Pattern on any TV Receiver Screen. Pattern will consist of 4 to 16 horizontal bars or 7 to 20 vertical bars.

THE MODEL TV-50A comes absolutely complete with shielded leads and operating instructions.

**Model TV-50A—Genometer. Total price—\$47.50—** Terms: \$11.50 after 10 day trial, then \$6.00 monthly for 6 months if satisfactory. Otherwise return, no explanation necessary!

**CROSS HATCH GENERATOR:** The Model TV-50A Genometer will project a cross-hatch pattern on any TV picture tube. The pattern will consist of non-shifting, horizontal and vertical lines interlaced to provide a stable cross-hatch effect.

**DOT PATTERN GENERATOR (FOR COLOR TV)** Although you will be able to use most of your regular standard equipment for servicing Color TV, the one addition which is a "must" is a Dot Pattern Generator. The Dot Pattern projected on any color TV Receiver tube by the Model TV-50A will enable you to adjust for proper color convergence.

**MARKER GENERATOR:** The Model TV-50A includes all the most frequently needed marker points. The following markers are provided: 189 Kc., 262.5 Kc., 456 Kc., 600 Kc., 1000 Kc., 1400 Kc., 1600 Kc., 2000 Kc., 2500 Kc., 3579 Kc., 4.5 Mc., 5 Mc., 10.7 Mc. (3579 Kc. is the color burst frequency).

**\$47<sup>50</sup>  
NET**

**EXAMINE BEFORE YOU BUY!**  
**USE APPROVAL FORM ON NEXT PAGE**



SUPERIOR'S NEW MODEL TW-11

STANDARD PROFESSIONAL

# TUBE TESTER

★ Tests all tubes, including 4, 5, 6, 7, Octal, Lock-in, Hearing Aid, Thyatron, Miniatures, Sub-miniatures, Novals, Subminars, Proximity fuse types, etc.

★ Uses the new self-cleaning Lever Action Switches for individual element testing. Because all elements are numbered according to pin-number in the RMA base numbering system, the user can instantly identify which element is under test. Tubes having tapped filaments and tubes with filaments terminating in more than one pin are truly tested with the Model TW-11 as any of the pins may be placed in the neutral position when necessary.

★ The Model TW-11 does not use any combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible to damage a tube by inserting it in the wrong socket.

★ Free-moving built-in roll chart provides complete data for all tubes. All tube listings printed in large easy-to-read type.

**NOISE TEST:** Phono-jack on front panel for plugging in either phones or external amplifier will detect microphonic tubes or noise due to faulty elements and loose internal connections.

### EXTRAORDINARY FEATURE

**SEPARATE SCALE FOR LOW-CURRENT TUBES:** Previously, on emission-type tube testers, it has been standard practice to use one scale for all tubes. As a result, the calibration for low-current types has been restricted to a small portion of the scale. The extra scale used here greatly simplifies testing of low-current types.

Model TW-11—Tube Tester  
Total Price .....\$47.50  
Terms: \$11.50 after 10 day trial, then \$6.00 monthly for 6 months if satisfactory. Otherwise return, no explanation necessary.

The Model TW-11 operates on 105-130 Volt 60 Cycles A.C. Comes housed in a handsome portable saddle-stitched Texon Case. Only

**\$47<sup>50</sup>**

SUPERIOR'S NEW MODEL 82A

Multi-Socket Type

# TUBE TESTER



**TEST ANY TUBE IN 10 SECONDS FLAT!**

- 1 Turn the filament selector switch to position specified.
- 2 Insert tube into a numbered socket as designated on our chart (over 600 types included).
- 3 Press down the quality button—

**THAT'S ALL! Read emission quality direct on bad-good meter scale.**

### SPECIFICATIONS

- Tests over 600 tube types
- Tests OZ4 and other gas-filled tubes
- Employs new 4" meter with sealed air-damping chamber resulting in accurate vibrationless readings
- Use of 22 sockets permits testing all popular tube types and prevents possible obsolescence
- Dual Scale meter permits testing of low current tubes
- 7 and 9 pin straighteners mounted on panel
- All sections of multi-element tubes tested simultaneously
- Ultra-sensitive leakage test circuit will indicate leakage up to 5 megohms

Production of this Model was delayed a full year pending careful study by Superior's engineering staff of this new method of testing tubes. Don't let the low price mislead you! We claim Model 82A will outperform similar looking units which sell for much more — and as proof, we offer to ship it on our examine before you buy policy.

To test any tube, you simply insert it into a numbered socket as designated, turn the filament switch and press down the quality switch — THAT'S ALL! Read quality on meter. Inter-element leakage if any indicates automatically.

Model 82A—Tube Tester  
Total Price .....\$36.50  
Terms: \$6.50 after 10 day trial, then \$6.00 monthly for 5 months if satisfactory. Otherwise return, no explanation necessary.

Model 82A comes housed in handsome, portable Saddle-Stitched Texon case. Only

**\$36<sup>50</sup>**

SUPERIOR'S NEW MODEL 83

# C. R. T. TESTER

TESTS AND REJUVENATES ALL PICTURE TUBES

**ALL BLACK AND WHITE TUBES**

From 50 degree to 110 degree types —from 8" to 30" types.

**ALL COLOR TUBES**

Test ALL picture tubes—in the carton—out of the carton—in the set!



Model 83—C.R.T. Tube Tester  
Total Price .....\$38.50  
Terms: \$8.50 after 10 day trial, then \$6.00 monthly for 5 months if satisfactory. Otherwise return, no explanation necessary.

• Model 83 is not simply a rehased black and white C.R.T. Tester with a color adapter added. Model 83 employs a new improved circuit designed specifically to test the older type black and white tubes, the newer type black and white tubes and all color picture tubes.

• Model 83 provides separate filament operating voltages for the older 6.3 types and the newer 8.4 types.

• Model 83 employs a 4" air-damped meter with quality and calibrated scales.

• Model 83 properly tests the red, green and blue sections of color tubes individually—for each section of a color tube contains its own filament, plate, grid and cathode.

• Model 83 will detect tubes which are apparently good but require rejuvenation. Such tubes will provide a picture seemingly good but lacking in proper definition, contrast and focus. To test for such malfunction, you simply press the rej. switch of Model 83. If the tube is weakening, the meter reading will indicate the condition.

• Rejuvenation of picture tubes is not simply a matter of applying a high voltage to the filament. Such voltages improperly applied can strip the cathode of the oxide coating essential for proper emission. The Model 83 applies a selective low voltage uniformly to assure increased life with no danger of cathode damage.

Model 83 comes housed in handsome portable Saddle-Stitched Texon case—complete with sockets for all black and white tubes and all color tubes. Only

**\$38<sup>50</sup>**

# SHIPPED ON APPROVAL NO MONEY WITH ORDER — NO C. O. D.

Try any of the instruments on this or the facing page for 10 days before you buy. If completely satisfied then send down payment and pay balance as indicated on coupon. **No Interest or Finance Charges Added!** If not completely satisfied return unit to us, no explanation necessary.

MOSS ELECTRONIC, INC.

Dept. D-713, 3849 Tenth Ave., New York 34, N. Y.

Please send me the units checked on approval. If completely satisfied I will pay on the terms specified with no interest or finance charges added. Otherwise, I will return after a 10 day trial positively cancelling all further obligations.

- |  |   |
|--|---|
| <input type="checkbox"/> Model 78.....Total Price \$26.95<br>\$6.95 within 10 days. Balance \$5.00<br>monthly for 4 months.      | <input type="checkbox"/> Model TW-11.....Total Price \$47.50<br>\$11.50 within 10 days. Balance \$6.00<br>monthly for 6 months. |
| <input type="checkbox"/> Model 79.....Total Price \$38.50<br>\$8.50 within 10 days. Balance \$6.00<br>monthly for 5 months.      | <input type="checkbox"/> Model 82A.....Total Price \$36.50<br>\$6.50 within 10 days. Balance \$6.00<br>monthly for 5 months.    |
| <input type="checkbox"/> Model TV-50A.....Total Price \$47.50<br>\$11.50 within 10 days. Balance \$6.00<br>monthly for 6 months. | <input type="checkbox"/> Model 83.....Total Price \$38.50<br>\$8.50 within 10 days. Balance \$6.00<br>monthly for 5 months.     |

Name.....

Address.....

City.....Zone.....State.....

All prices net, F.O.B., N. Y. C.

# Transpace — 6 channel Citizens' Band radiophone



You get every top feature in a TRANSPACE — the set that gives you the full possibilities of Class "D."

**Six-channel operation.** Choose up to 6 channels, by means of an illuminated front panel selector. The dial is direct reading — no interpolation needed.

**Three-way power supply** — operates from 115 volts ac, 6 and 12 volts dc. Only one Transpace Model for car or home.

**Maximum legal power** — a full 3 watts RF output.

**One-microvolt sensitivity** for maximum reception... 37 db selectivity.

**Full 100% modulation**, plus automatic squelch and automatic noise limiter.

**No retuning** — the Transpace maintains full sensitivity and power output when you switch channels.

**Rugged construction**—withstands the roughest mobile use. Super-tough vinyl finish.

**Immediate delivery from stock.** Write for literature and name of local dealer.



12902 Foothill Boulevard • San Fernando, California

## RESIST-O-CHEST

ends  
"cigar box  
confusion"  
COMPACT  
ALL-METAL  
HINGED-LID



Order from  
your IRC  
Distributor



FREE!


with any of 10 Handy-Pak  
Carbon Resistor Assortments  
34 to 77 Values

**\$24<sup>48</sup>** to **\$110<sup>88</sup>** Dealer Net

INTERNATIONAL RESISTANCE COMPANY  
DISTRIBUTOR SALES DIVISION  
414 N. 13th STREET • PHILADELPHIA 6, PA.

**VIS-U-ALL**  
BUSINESS BUILDING TEST EQUIPMENT FOR SERVICE DEALERS

here's  
**MONEY MAKING  
CONVENIENCE**

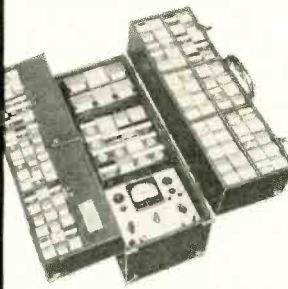

tubes, tools and built-in  
tube tester... all in one  
handy case!

THE V100 **DYNAMIC  
CADDY-TESTER**

Built-in tester checks over 800  
TV-radio tubes dynamically;  
also tests picture tubes and  
selenium rectifiers. On house  
calls, you test all tubes in a  
set... sell more, make more!  
Only 4 sockets and exclusive  
Master Switch test all receiv-  
ing tubes, past, present and  
future. Never obsolete. Well  
built, professional caddy holds  
150 tubes.

ONLY \$109.00

Write  
for  
Details

**VIS-U-ALL**  
PRODUCTS CO.  
645 EASTERN, S. E.  
GRAND RAPIDS 6,  
MICHIGAN


RADIO

# ECONOMY CODE OSCILLATOR


By JAMES MARTIN

If economy is important to you when constructing a code-practice oscillator, this one is for you. It consists of five inexpensive components, a low-priced transistor, a standard earphone, two small capacitors and a 1.5-volt flashlight battery.

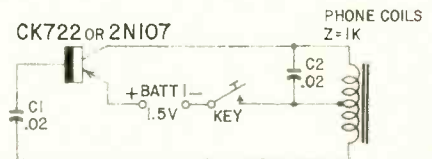The unusual part of the circuit is that the earphone is used as a tapped choke to provide feedback. This eliminates the expensive transformer or tapped choke.



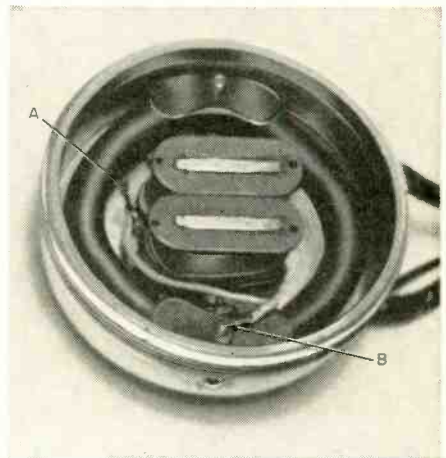As the diagram shows, the tap is made at the connection between the two coils. Most phones contain two coils, and the connection between them is usually easy to get at. A short length of wire is



soldered to this connection (point A in photo) and neatly led around and soldered to one of the screws that hold the magnet down (point B in photo). A wire, the length of the phone cord, is also secured to the screw. It is taped securely to the phone cord at 4- or 5-inch intervals.

The circuit is fairly simple. The feedback that maintains oscillation is obtained from the phone coil and fed back to the transistor's floating base.

## RADIO

The operating frequency is determined chiefly by the values of capacitor C2 and the inductance of the phone coil that C2 is connected across. Current drain runs from about 100 to 200  $\mu$ a, depending on the particular transistor used.

Construction is no problem. The oscillator can easily be assembled in a small




plastic box. I used a miniature jack and plug to connect the key to the oscillator, but this is optional and the wires may be connected directly to the key.

With most transistors, volume will be extremely high, and, in all probability, a resistor will have to be placed in series with the key to hold the volume down to a more comfortable level. The value of this resistor will depend on the volume desired. Of course a potentiometer could be inserted to give variable control of volume. END
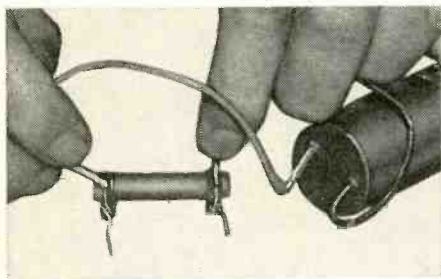
## DISCHARGING ELECTROLYTICS

The common practice is to discharge electrolytic capacitors by shorting their terminals together or by placing a metallic tool across the terminals. This practice is satisfactory for small-value capacitors but may damage larger



units such as the photographic flash types and those over 40  $\mu$ f used in radio and television. The strain on the large dielectric area is too sudden and may cause a puncture of the dielectric film, producing leakage or a short circuit thereafter.

Large capacitors should be discharged through a resistor (see photo). After the initial surge the terminals may then be short-circuited.—A. R. Clawson.



**.. CUT TEST TIME IN HALF!**

**.. DON'T WASTE MONEY on instruments you don't need!**

# Down-to-earth training in MODERN TEST INSTRUMENTS and how to use them fast and right!



Probably the most important factor in TV-radio or industrial electronic service is a complete working knowledge of instruments—which ones you really ought to have—which ones to use for specific jobs—how to substitute one for another—and how to use instruments properly in following professional time-saving procedures every step of the way. And that's exactly the kind of practical, easy-to-understand training these Rinehart manuals bring you! 570 pages and over 360 clear pictures provide above-average instrument training that equips you for better, faster work and higher earnings.

## A COMPLETE MANUAL OF MODERN INSTRUMENTS A money-saving guide to every type in common use!

This 254-page Basic Electronic TEST INSTRUMENTS is a complete working guide to practically every instrument in common use. Teaches you the advantages and disadvantages of various types; helps you get more for your instrument dollars and avoid buying those you don't really

need; outlines instrument construction and operation; explains instrument features and the particular applications for each; tells how to calibrate and care for them, and how to select the ones most suitable for your particular needs. Price separately \$4.95.

## MANUAL OF TIME-SAVING TEST PROCEDURES How to troubleshoot better, faster and more accurately!

This big manual brings the kind of "brass tacks" training that helps you locate troubles in a jiffy by teaching you exactly what instruments to use and exactly how, where and why to use them; how to substitute one instrument for another and how to develop time—and money-saving test methods all along the line. Basic Electronic TEST PROCEDURES covers: Current Checks; making measurements of Power, Capacitance,

Inductance Resistance, AF, RF, Phase, Distortion and Modulation; Checking Sensitivity, RF Gain, Fidelity, AVC Voltage, Operating Voltages, etc. Includes visual alignment techniques—even transmitter and industrial electronic test procedures. 316 pages, 190 how-to-do-it pictures and dozens of step-by-step troubleshooting procedures. Price \$6.50 separately.

### PRACTICE 10 DAYS FREE!

Dept. RE-20, RINEHART & CO., INC.  
232 Madison Ave., New York 16, N.Y.

Send books indicated below for 10-day FREE examination. In 10 days I will either remit price shown (plus postage) or return books postpaid and owe you nothing.

- Basic Electronic TEST INSTRUMENTS, \$4.95 separately
- Basic Electronic TEST PROCEDURES, \$6.50 separately

Check here for **MONEY-SAVING COMBINATION OFFER**. Send both manuals at special price of only \$10.00 for the two (regular price \$11.45... you save \$1.45.) Payable at rate of \$4.00 plus postage after 10 days if you decide to keep books and \$3.00 a month for 2 months until \$10.00 has been paid. (**EXTRA SAVING!** Send \$10 with order and Rinehart pays postage. 10-day return privilege with money refunded.)

Name.....

Address.....

City, Zone, State.....

**OUTSIDE U.S.A.—\$5.45 for TEST INSTRUMENTS; \$7.00 for TEST PROCEDURES; \$11.00 for both. Cash only but money refunded if you return books in 10 days.**

**SAVE \$1.45**

on this complete 2 vol. instrument library!

YOU'LL LIKE Rinehart books for two BIG reasons: They're fully complete and they make even the most complicated procedures easy to understand!

# ATTENTION

- Service Technicians' Associations
- Club Members
- Student Groups


Special subscription rates to RADIO-ELECTRONICS are available to associations, clubs, schools, employee groups, etc. For information write— G. Aliquo

**Radio-Electronics** 154 West 14th St., New York 11, N. Y.

# Service Technicians! YOU EARN MORE... YOU RATE with the public when you own the **PHOTOFACT**® service data library!

"Sams PHOTOFACTS are as important to my shop as the instruments I use. Sams are a must in an up-to-date service department."

—Louis Michael  
Aliquippa, Penna.

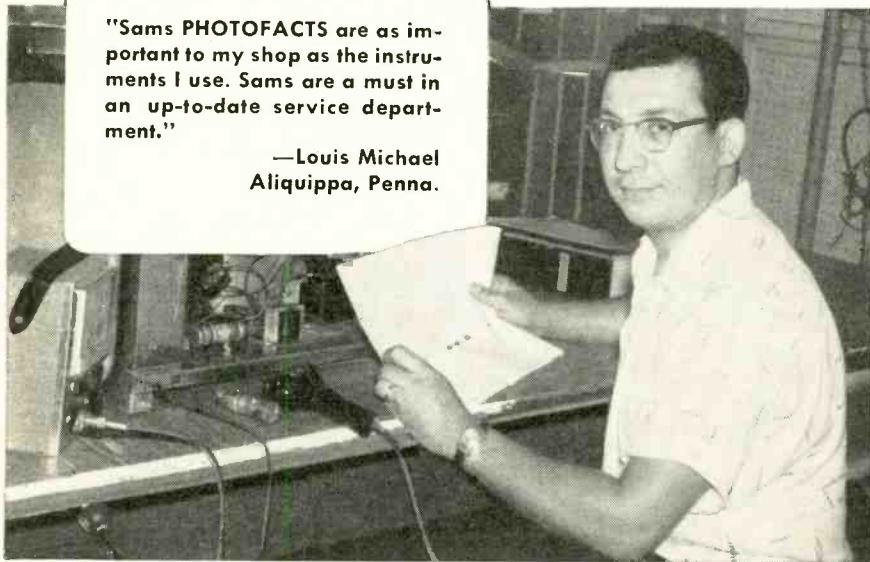

YES, if you are one of the thousands of owners of a complete PHOTOFACT Service Data Library, you are enjoying maximum earnings. It's inevitable, because no matter how expert you are, you can always *save more time on any job, get more jobs done daily—EARN MORE, DAY IN AND DAY OUT...*

Moreover—as the owner of a complete PHOTOFACT Library, *you know your customers' sets best. You can actually show each customer you have the PHOTOFACT Folder covering his very own set. Result: You command public respect and acceptance which paves the way to more business and earnings for you...*

## HOW TO STAY AHEAD...

Today, the truly successful Service Technicians are those who own the complete PHOTOFACT Library, who can meet and solve any repair problem—faster and more profitably. And these men *keep ahead* because they're on a Standing Order Subscription with their Distributors to receive all new PHOTOFACTS as they are released monthly.

For PHOTOFACT Library Easy-Buy Plan details and Standing Order Subscription, see your Sams Distributor today, or write to Howard W. Sams...



If you now own a PHOTOFACT Library, you can apply for membership in the powerful new "PEET" program, designed to build prestige and business for the Service Technician who qualifies. Ask your Sams Distributor for the "PEET" details, or mail coupon today!

**HOWARD W. SAMS & CO., INC.**  
1726 E. 38th St., Indianapolis 6, Ind.

- Send me full details on the new "PEET" Program. Include full information on the Easy-Buy Plan and Free File Cabinet deal.
- I'm a Service Technician:  full-time;  part-time

My Distributor is: \_\_\_\_\_

Shop Name \_\_\_\_\_

Attn: \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

TECHNICIANS'

**NEWS**

## N. C. CERTIFIES TECHS

The certification of TV technicians as "journeyman TV technician" or as "television technician," based upon examinations or successful completion of state-sponsored courses is proceeding in North Carolina.

In the photograph, State legislator Ed Kemp (right) is presenting to J. L.



Warren, president of the High Point (N. C.) Radio & TV Technician's Association, a card identifying him as a certified technician.

The program was established by the state's Vocational Education Division with the help of the North Carolina Federation of Electronic Technicians (NCFEA) and is now being offered at 13 centers throughout North Carolina.

Interested technicians may contact L. L. Leathers, president of the NCFEA, at 221 Sutherland St., Durham, or their local Director of Vocational Education.

## MICHIGAN SERVICE COSTS

TSA (Michigan) sponsored a business training course starting in October, 1959, with representatives from RCA, G-E, Bell Telephone and others participating. Brought out in panel discussions at the first meeting were these interesting figures for the 50 members of TSA at the session.

Average labor charges were from \$7.95 to \$9.50 for a 1-hour home call.

Average for shop repairs was from \$24.50 to \$35.

Average pickup and delivery charges ran from \$9 to two full call charges.

The clinics which continue at one per month (2½ hour sessions), were scheduled through March. They're strictly on business; nothing technical.

## DEL. VALLEY GROUP HITS RETAILING WHOLESALE

An editorial in the *TSA News* (Delaware Valley) headed "Loose Distribution Deserves Just Retribution" discusses wholesale parts distributors who sell to retail customers. Recommending



**ARE YOU ON THE LIST?**

Radio-Electronics is publishing a detailed list of the known television service associations in North America. If you belong to an association that isn't on our list or want to get the name and address of the one closest to you, drop a postcard to: Association Editor, Radio-Electronics, 154 West 14 Street, New York 11, N.Y.

**CALIFORNIA STATE ELECTRONICS ASS'N.**  
1111 Weldon Ave.  
Fresno 4, Calif.  
Keith Kirstein, President

**LOS CERRITOS CHAPTER, RTA**  
16733 Bellflower Blvd.  
Bellflower, Calif.  
Harry J. Mackey, President

**SOCIETY OF RADIO & TV TECHNICIANS, INC.**

Box 4012, Burbank-Glendale Chapter  
Glendale, Calif.  
Gene Sheppard, Secretary  
Van Nuys Chapter  
Box 126  
Van Nuys, Calif.  
Arnold Meyer, President

**PASADENA CHAPTER, RTA**  
Box 1142, Main Post Office  
Pasadena, Calif.  
Wayne Hartwell, President

**RADIO TV TECHNICIANS ASS'N. OF CALIF., INC.**

4729 E. Gage Ave.  
Bell, Calif.  
Victor L. Bangle, Executive Director

**POMONA CHAPTER, RTA**  
522 West Holl St.  
Ontario, Calif.  
R. J. McCoskrie, President

**ALAMEDA COUNTY TV AND RADIO ASS'N.**

6609 Chabot Rd.  
Oakland 18, Calif.  
Philip Fisher, Executive Secretary

**RIVERSIDE CHAPTER, RTA**  
Box 74  
Arlington, Calif.  
Howard Bogue, President

**HIGH DESERT CHAPTER, RTA**

Box 963  
Apple Valley, Calif.  
Earl J. Cusack, President

**SAN ANTONIO CHAPTER, RTA**  
Box 626  
South Gate, Calif.  
Harry Midkiff, President

**INDEPENDENT TV SERVICE DEALERS ASS'N.**

213 S. Coronado St.  
Los Angeles 57, California  
Hugh W. Wilkins, president

**SAN BERNARDINO CHAPTER, RTA**  
277 E. Baseline  
San Bernardino, Calif.  
Orville Deardorff, President

**LONG BEACH CHAPTER, RTA**

Box 4085  
Long Beach, Calif.  
John Whittaker, President

**SAN DIEGO CHAPTER, RTA**  
Box 4325  
San Diego, Calif.  
Grayson Lovell, President

**SOUTH BAY CHAPTER, RTA**  
438 Buckhorn St.  
Inglewood, Calif.  
G. P. R. Christensen, President

that members of TSA-Delaware Valley patronize jobbers who refuse to sell at retail, *TSA News* points out that possession and use of a state sales-tax number in these sales is a good guidepost to a jobber who wants to sell only to dealers.

**TECHNICIAN SHORTAGE IN CALIFORNIA**

There is a shortage of good TV technicians, says IPET, organ of the Society of Radio & Television Technicians, Van Nuys, Calif., in an editorial. "The fact remains that today the shortage of good trained technicians is more acute than at any time in electronics' short history. Every day more technicians leave for greener fields because they can make more money with less grief and less work. Hardly a day goes by that some shop doesn't call asking for a good outside man or a top bench man.

"Still the top wages offered to these men is nowhere near what they can get at any local factory or manufacturer. Why does this condition exist? Why can't the local TV shop meet the prices paid by industry in general? Here again we must face facts. Shops that are still charging 1949 prices simply can't pay 1959 labor costs . . . Until the industry raises its standards and its prices I'm afraid good technicians are going to be hard to find . . ."

**OPPOSES LICENSING**

*TEAM News* (Mo.) says: A license . . . will give dignity to the shop that cannot hold a customer now because of a lack of ethics . . . it will produce a new field for the people who grow fat on 'payoffs' and will introduce the evils of the bribe, pressure and outside control to this industry, which has managed to maintain its integrity and independence despite the efforts of some opportunists inside and outside of the industry.

"It is ridiculous to try to put teeth in existing laws to cover one industry and bypass all others. What good does it do to protect the public from the unscrupulous TV man when some unscrupulous doctor, lawyer, real estate agent, insurance man, plumber, electrician, mechanic, clothing salesman, furniture salesman, undertaker, interior decorator, tree surgeon, butcher, baker and candlestick maker is waiting to get the hook into him? And most of them with a big fat license to back up the action?"

**FLORIDA TECHS TO ASK LICENSING**

TESA (Miami) announced plans to ask the Dade County (Florida) Board of Commissioners to license and regulate radio-TV service technicians through an ordinance. TESA plans included an apprentice training program, made provision for already practicing technicians who are paying municipal taxes properly through a "grandfather" clause.

One reason licensing was needed, TESA stated, was that over half a dozen people in Dade County had been killed by improperly installed electronic devices during 1959.

**TEXAS LAW WORKING**

In the *NATESA Scope* president Mac Metoyer writes, "It is interesting to note . . . that most letters crossing my desk refer to shops everywhere having good business. Oren Wunsch of Beaumont, Texas even called long distance trying to locate service technicians.

"He explained that with the new Texas state sales tax law, part-time TV 'fixit' men have virtually gone out of the field. The Texas law requires a consumer to pay sales tax to the vendor. The vendor must have a tax collection permit, and must post a bond in favor of the State of Texas to insure payment. The bonding companies require definite proof of one being in business before

**NEW FROM HOWARD W. SAMS**

**"From Tinfoil to Stereo"**  
The Evolution of the Phonograph



by Oliver Read & Walter L. Welch

Here is the most complete history of the phonograph ever written—from the use of tinfoil to the revolutionary stereo record—the whole exciting story of the men and events responsible for the development of the phonograph!

You'll be fascinated by this masterful account of the evolution of the phonograph. Covers everything: man's earliest dreams of imitating sound; the Edison tinfoil phonograph and the development of the earliest prototypes; the patent struggles; the development of cylinders and discs; the coin-slot phonograph; the introduction of the internal horn; the beginnings of radio and its contribution to recording and reproduction; sound pictures and the phonograph; the war of the record speeds; growth of component systems; tape vs. discs—right down to today. Includes dozens of rare photographs. A wonderful book for every hi-fi enthusiast and phonograph connoisseur. 576 pages, 6 x 9", fully illustrated. Only . . . . . \$9.95

**MORE NEW SAMS BOOKS**

**"101 Ways to Use Your Ham Test Equipment"**



by Bob Middleton

A practical "how-to-do-it" book for amateur radio operators and service technicians who specialize in the repair of ham radio equipment. Gives concise applications for grid dip meters, antenna impedance meters, oscilloscopes, bridges, simple noise generators and reflected power meters. Each use is clearly described, with full data on connections required, proper test procedures and evaluation of results. 168 pages; 5½ x 8½"; illustrated. Only . . . . . \$2.00

**"Servicing Hi-Fi and FM in the Customer's Home"**



by Milton S. Kiver

Describes a wide range of quick, easy test methods for hi-fi amplifiers, AM-FM receivers, record changers, turntables and tape recorders. Includes several unusual new methods, such as the use of an AM detector probe to trace FM circuits. Methods are selected for their quick, practical application and their ability to locate actual and potential trouble spots in hi-fi equipment. Indispensable to anyone interested in servicing hi-fi. 160 pages; 5½ x 8½"; illustrated. Only . . . . . \$2.95

**HOWARD W. SAMS & CO., INC.**

Order from your Sams Distributor today, or mail to Howard W. Sams & Co., Inc., Dept. 13-20 1720 E. 38th St., Indianapolis 6, Ind.

- Send me the following books:
- "From Tinfoil to Stereo" (EPR-1)
  - "101 Ways to Use Your Ham Test Equip." (TEM-6)
  - "Servicing Hi-Fi in the Customer's Home" (SHK-1)
- \$ . . . . . enclosed.  Send Free Book List

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

(outside U.S.A. priced slightly higher)

they will bond the firm. This means a place of business and a minimum investment. To sell retail (to the consumer) without a tax permit is a felony.

"Even though this new law includes all businesses, it has been a great aid to the established electronic service firms."

**ESFETA SECRETARY RESIGNS**

George Carlson, secretary of the Empire State Federation of Electronic Technicians Associations, and Eastern secretary of the National Alliance of TV & Electronic Service Associations, has resigned from his ESFETA post to devote his full time to NATESA duties. Carlson is also active in his local group, Electronic Technician's Association, Jamestown, N. Y.

**ST. LOUIS TECHNICIANS GIVE SETS TO NEEDY**

As part of their expression of the Christmas spirit the members of TESA—St. Louis voted to repair radio sets and give them to the Volunteer Bureau of the Health & Welfare Council of St. Louis, Mo. Most members of the group indicated they had at least one old receiver around the shop, and would repair it for the cause. A local parts distributor, Crown Electronics, generously volunteered to supply needed parts to service dealers participating in this Christmas program.

**TUBE-CADDY THIEVES MOVE TO BURGLARY**

Miami service technicians, plagued by a series of thefts of tube caddies from their trucks and cars while out on calls, have nothing on parts jobber Vance Baldwin, Inc., of 7700 N.W. 7th Ave., Miami, who recently lost 8,000 tubes, a tube tester, tape recorder and an amplifier to thieves. The robbers broke into the store at night.

**ARTSNY RAISES DUES**

The Associated Radio & Television Technicians of New York City increased their dues to \$35 a year from a former figure of \$18. On a show of hands, only two members were not in favor of the proposed increase.

END

**Locate:**  
THAT DEFECTIVE CIRCUIT QUICKLY

**new BUZIT**  
TRANSISTORIZED SIGNAL TRACER

**NO CLIPS OR WIRES TO MESS WITH**

Available at your favorite jobber

**W MODEL BZI**

**SIMPLY PRESS SWITCH**  
to on position &..... begin signal tracing;... by probing into circuit.

**SUITABLE FOR VIDEO TRACING**  
Buzit transmits many harmonics from AUDIO TO VIDEO RANGE.

• FITS THE POCKET LIKE A PEN  
• OPERATES ON TWO PEN LIGHT BATTERIES

Used for trouble shooting  
AF CIRCUITS IF CIRCUITS RF CIRCUITS  
VIDEO CONTINUITY CHECKS  
SPEAKERS -ETC

ONLY \$8.10 DLR. NET

WORKMAN TV Products, Inc.  
SARASOTA, FLORIDA

**MORE! FOR THE**



**DIFFERENCE**



\*FLUXVALVE. \*\*V-GUARD. \*\*\*V-GUARD. UNIPOISE PAC (TM)

Royal System Wall Cabinets designed by Poul Cadavus.

Here is more for the best of everything in quality record reproduction—the more that makes the difference! more output!... more channel separation!... more response... more record life! In short—more to enjoy because there's more quality for more listening pleasure. Without question, Pickering's Collectors' Series 380 is the finest—with more features and more flexibility than any other stereo pickup in the world.

For example, the 380 is fully encapsulated in radiation-proof precious mu-metal for absolutely hum-free performance in any record player regardless of type—make—model. The only true way to judge a high fidelity component is to compare it with another... measure its performance with the most vital instrument of all... the ear. For—those who can hear the difference choose PICKERING\*.

**COLLECTORS' SERIES 380.**

OUTPUT: 15 mv per channel, CHANNEL SEPARATION: 30:35 db.  
FREQUENCY RESPONSE: + 2 db 20,000 cycles. SIGNAL TO NOISE RATIO: -65 db below reference. TRACKING FORCE: "A" type stylus—2.5 grams; "C" type stylus—3-7 grams.

Model 380E Collectors' Ensemble includes the Stanton Stereo FLUXVALVE with 3 "V-GUARD" styli for stereo, microgroove and 78 rpm records. . . . . \$60.00

Model 380A includes Stanton Stereo FLUXVALVE with D3807A "V-GUARD" stylus for transcription arms. . . . . \$34.50

Model 380C includes Stanton Stereo FLUXVALVE with D3807C "V-GUARD" stylus for auto-changer arms. . . . . \$29.85

\*PICKERING—for more than a decade—the world's most experienced manufacturer of high fidelity pickups



Only the Stanton Stereo FLUXVALVE features the safe, comfortable, easily replaceable stylus assembly.

FOR THOSE WHO CAN HEAR THE DIFFERENCE



PICKERING & CO., INC., PLAINVIEW, NEW YORK

**Answer to Tape Recorder Word Puzzle on page 43**

T	A	P	E	S	I	R	O	N			G	A	P
H		D		N								U	
R	E	W	I	N	D	P	L	A	S	T	I	C	
E		T	I	A							D	R	
A	T	A	C	E	T	A	T	E	E	E			
D	U	A	L	A	C	A	R				S		
S	K		T	H	E	A	D	L	P				
S	T	E	R	E	O	C	E	E	O				
P	U		R	M	I	K	E	V	N				
L	P			A	R	E	E	L	S				
I			M		G	A	L	L	E				
C		W	O	W	N	S	B						
E		T	L	E	A	D	E	R	I				
			O	T					A				
R	E	C	O	R	D		B	R	A	K	E	S	



### WESTINGHOUSE H21T104

On humid days the receiver would overload on strong signals. The set would behave satisfactorily when relative humidity was low.

The condition was simulated in the shop with a squirt from a perfume atomizer. A gentle spray on the wiring side of the printed chassis board near the keyed age tube section (half of a 5BT8, pentode section) produced the symptom.

The wiring board around the socket was carefully cleaned. This did away with a leakage path between lugs 7 and 8. The leakage reduced the age by reducing the video signal applied to the grid, pin 8. The area was sprayed with high-voltage dope after it was cleaned.—*E. A. Chung*

### STEWART WARNER 21T9300A

The set developed extremely critical and unstable sync. Low-amplitude sync pulses were evident when the waveform at the integrator's output was examined.



Resistance checking revealed a trifle low tolerance on the grid resistor of the

gated sync clipper, a 6BE6. Replacing the resistor, R97, solved the problem.—*Mark Wilson*
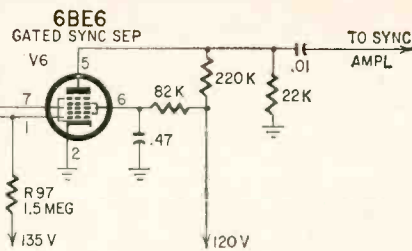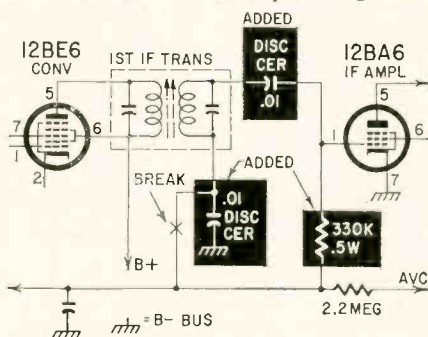
### LEAKY IF TRANSFORMER

Rather than replace or repair a leaky miniature if transformer, I find it quicker and cheaper to block the secondary winding against the leaking plate voltage with a couple of .01- $\mu$ f ceramic disc capacitors.

In the G-E model 572 used as an illustration, the leak kept the grid of




the 12BA6 at 0.5 volt dc, regardless of any age action which still managed to come through on strong local stations. The increased plate current in the 12BA6 lowered plate and screen voltages in the set from the 95 called for in the schematic to 85. Voltage returned to normal after the repair.

Typically, the leakage resistance between the two windings of the if transformer could not be measured with the ohmmeter section of my vtvm.—*E. T. Thiersch*

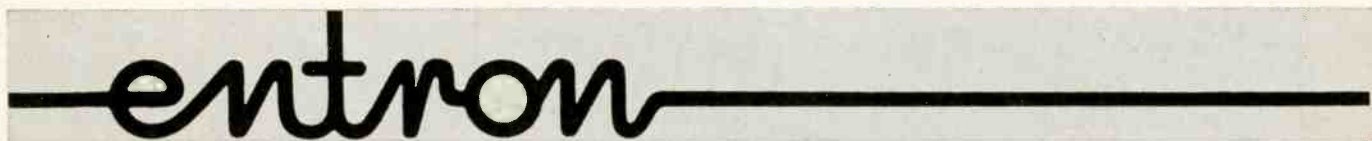
### MODEL BK 414 SOUNDMIRROR

Distortion of the sound that appears as a sort of gurgling or gargling of the voice and music is caused by too little bias on the amplifier tubes. The case in point had a leaky capacitor coupling the first amplifier (6J7) to the second amplifier, a 6SJ7. The value of this capacitor is .005  $\mu$ f. It should be replaced with a 600-volt molded-paper unit.—*Lawrence Shaw* END


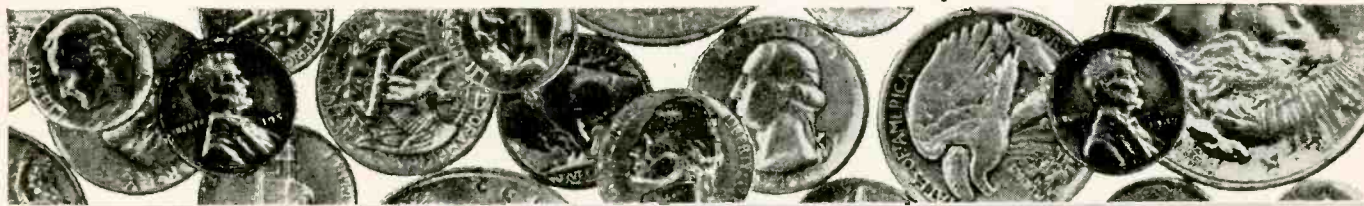
## SPELLS GREATER PROFITS FOR YOU

with the New Master Television Antenna System Line!



**E**quipment with the skill built in — precision designed for easier installation, longer life, better performance.

**N**o large inventories with the New Entron line. Fewer components do the job better!

**T**echnical information, catalogues, brochures, and installation information, all free dealer helps from Entron!

**R**eap the benefits of Entron's national advertising. Over 100,000 service men each month see Entron ads in selected publications keyed to the TV service market.

**O**nly selected dealers in each area are chosen to handle the

**N**ew Entron Master Television Antenna System equipment line.

**THE SKILL'S BUILT IN**

Write today for further information on how Entron can solve your profit puzzles!



P. O. Box 287 Bladensburg, Md.

APpleton 7-9585

GET THAT SYLVANIA SIGN UP TODAY!

# ARTHUR GODFREY IS SELLING YOU!

Now sponsored by Sylvania Silver Screen 85 picture tubes, Arthur Godfrey is telling America about you, selling America on you – the independent TV service dealer!

He's spreading the word to millions – on the CBS Radio network – 196 stations coast-to-coast – that you are the man to see for the finest TV service. Millions more are reading about you in the pages of *The Saturday Evening Post*. When Arthur Godfrey tells his audience to look for the “. . . Sylvania decal in the window of your local independent TV service dealer's shop,” are you with it?

See your Sylvania distributor for Sylvania Silver Screen 85 picture tubes and Sylvania quality receiving tubes. Get your display kit of colorful window streamers and posters. Get that Sylvania sign up today!

*Electronic Tubes Division, 1740 Broadway, New York 19, N. Y.*


See your local paper for time and station

“IT'S **ARTHUR GODFREY TIME**” . . . brought to you by

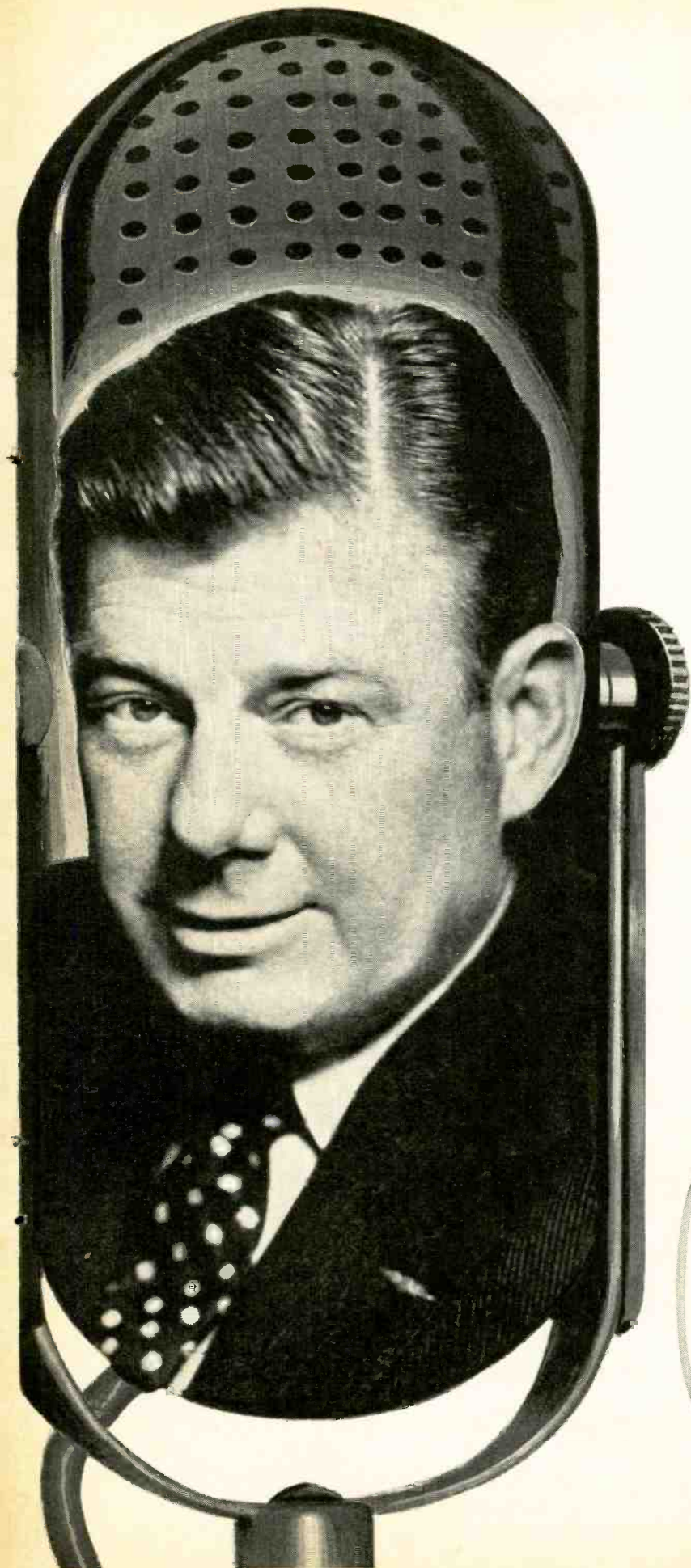 **SYLVANIA**

Subsidiary of **GENERAL TELEPHONE & ELECTRONICS** 





**SYLVANIA SILVER SCREEN 85**

**4 WAYS BETTER**

- \* Sharper focus*
- \* Clearer picture*
- \* Greater contrast*
- \* More light output*

**SYLVANIA  
"SILVER SCREEN  
85"**

# new PATENTS

## BEAM REGISTRATION CIRCUIT

Patent No. 2,885,594

Arnold Lesti, Kensington, Md. (Assigned to Andromeda, Inc., Kensington, Md.)

This patent deals with color kinescopes whose targets are coated with phosphor strips. As a strip is scanned, it emits a primary color. The phosphors exist in groups of three—red, blue and green. Each blue phosphor is processed so it also emits a short-persistence violet light which is transmitted through a filter onto a photocell.

The tube's gun emits a trio of closely spaced beams which scan the corresponding phosphors as a unit (Fig. 1). The incoming TV signal controls the intensity of each beam and thus determines whether red, blue, green, or any

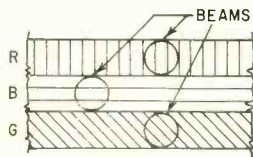


Fig. 1

combination thereof, becomes visible at a given time and point. This invention solves the problem of beam alignment so the proper phosphor is scanned by the correct beam.

Fig. 2 shows chrominance signals at the grids of the kinescope. The luminance (-Y) signal is applied at all cathodes. A pilot frequency modulates the upper and lower cathodes as shown, thus superimposing a high frequency on them.

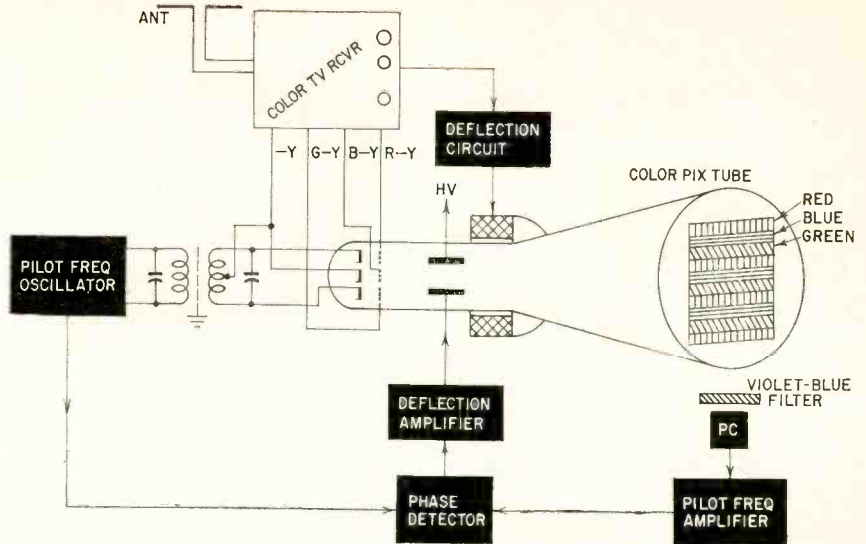


Fig. 2

Consider what happens when the beams are out of alignment. If the triple beam is too low, the beam corresponding to red will fall (at least partly) on the blue phosphor. Since the red (upper) cathode is modulated at pilot frequency, the photocell will receive an hf-modulated violet light. On the other hand, if the beam is too high, the green beam will modulate the blue phosphor. Again the photocell will deliver output, this time of opposite phase (because the upper cathode is out of phase with the lower, with respect to the pilot frequency).

A phase detector receives the pilot frequency signal and generates dc which may be positive or negative.

The output is fed back (through smoothing and corrective networks, not shown) to auxiliary deflection plates. They raise or lower the beam as required for accurate registration.

## BATTERY-LESS RADIO

Patent No. 2,813,242

Lloyd R. Crump, Silver Spring, Md. (May be used by US Government without payment of royalties)

Transistors require so little power that broadcast radiation may be sufficient. Several such circuits have been described in this magazine: April 1957, page 85; April 1955, page 96.

This radio uses a full-wave rectifier to extract maximum radiation power from an antenna. Coil L1 is tuned to the desired signal, which is detected by diode D1, then amplified by transistor V.

Coils L2 and L3 are tuned to the strongest local transmitter, not necessarily the same as the desired signal. One circuit delivers positive voltage to C1, the other charges C2 negatively.

# YOU CAN ALSO DO THE BIG JOBS WITH WIZARDS



HOME - 7 Outlets - One Antenna - No Amplification: Residence of Bob Barker, MC of the popular daytime NBC show Truth Or Consequences.



HOTEL - 120 Outlets - One Antenna - One Amplifier: The Montecito - 6650 Franklin, Hollywood, California.



## THE WIZARD 300\*

ELECTRO-MAGNETIC COUPLER FOR ALL SINGLE ANTENNA MULTIPLE-OUTLET SYSTEMS IN TV FLAT LINE

\*Pat. Pend

**\$1.95**  
LIST PRICE

The high electrical efficiency of the Wizard 300 is proven in many installations where more than thirty receivers are being operated from a single antenna without amplification.

Information on any of the above jobs and a brochure covering Wizard System installations is available. Write Dept. RE-129.

**CHARLES ENGINEERING, INC.**  
6053 Melrose Avenue • Los Angeles, California




HOUSING PROJECT - 2,549 Wizards Installed To Date: L.A. Housing Authority, Los Angeles, California.



APARTMENT - 39 Outlets - One Antenna - No Amplification: The Del Rio - 10236 Old River School Road, Downey, Calif.



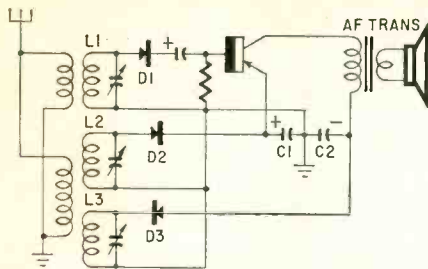APARTMENT - 48 Outlets - Two Antennas (24 Outlets each) - No Amplification: The Paramount Riviera - 12447 Paramount Blvd., Downey, California.



These capacitors energize V with correct polarity. The inventor finds that with indoor antenna pickup from a 5-kw transmitter 5 miles away, he generates up to 3 volts at 250  $\mu$ .

**DIODE PULSE AMPLIFIER**  
 Patent No. 2,892,979

William A. Ogleree, Southampton, Pa. (Assigned to Burroughs Corp., Detroit, Mich.)

This pulse amplifier works on the principle that a conducting diode cannot immediately be switched to nonconduction. Its back resistance remains low for a few microseconds, depending upon the prior forward flow. Here a 1N91

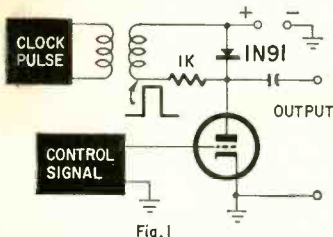


Fig. 1

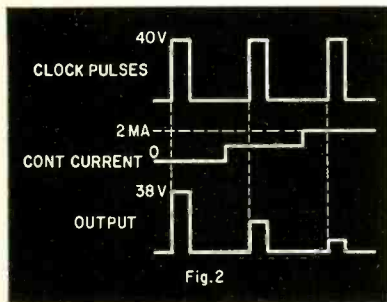



Fig. 2

diode is blocked periodically by a clock pulse of 0.1- $\mu$ sec duration and 40-volt amplitude. Forward flow is provided by plate current which can vary from zero to 2 ma (see Fig. 1).

When blocked by a reverse clock pulse, the 1N91 back resistance may vary from several hundred thousand ohms (no prior flow) to a few ohms (2-ma prior flow). Since the diode shunts the output terminals, it controls the output. Fig. 2 shows how the output pulse depends upon the control current. Note that output pulses occur only during a clock pulse. END



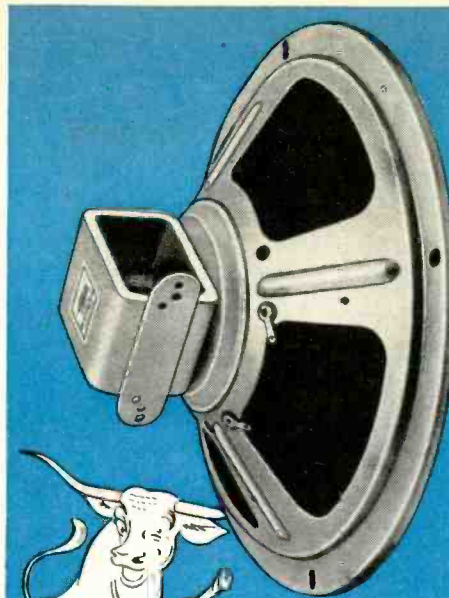"Now, lady, who's been feeding you a line?"



**OXFORD SPEAKERS**  
 Preferred for original equipment.  
 Proven for replacement.

Our catalog is available upon request.



**OXFORD**  
 -the  
*Leader*

Largest exclusive  
**SPEAKER** manufacturer  
 in the world  
 6 factories located  
 throughout the U.S.A.

ONCE MORE UNTO THE BREACH, DEAR FRIENDS! When you are looking for replacement speakers on a par with original equipment, the prime source is Oxford. Oxford is the foremost name in original equipment speakers specified by manufacturers. We can supply you with exact replacement speakers which will be of the same high quality as that originally supplied. Oxford has a complete line for any and every application.

**OXFORD Components,**  
 A Division of Oxford Electric Corp.  
 556 West Monroe St., Chicago 6, Illinois

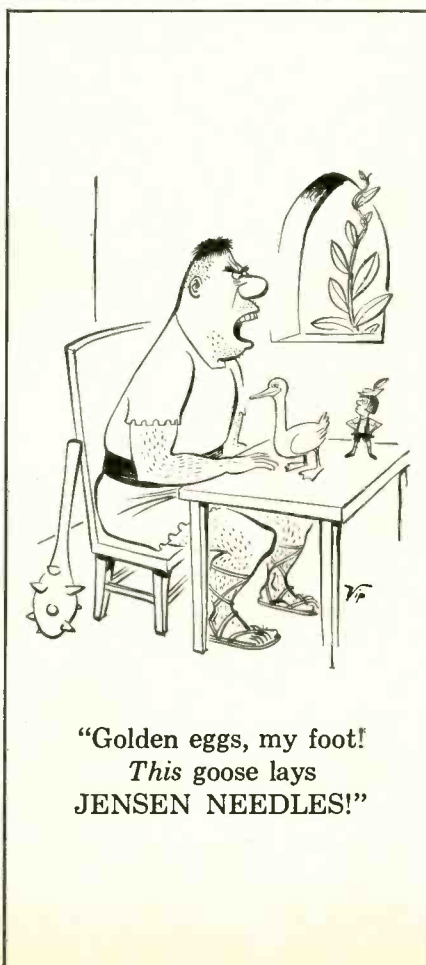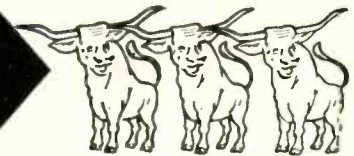Oxford Speakers are available from recognized electronic parts distributors.



"Golden eggs, my foot!  
 This goose lays  
**JENSEN NEEDLES!**"

**DON'T GUESS ...**

KNOW THE TEMPERATURE OF YOUR SOLDERING GUN BEFORE TOUCHING PRINTED CIRCUITS AND LAMINATED WIRING BOARDS!



**ESICO GUNCHOKE®**

REDUCES TEMPERATURE OF YOUR SOLDERING GUN TO TWO CONSTANT HEATS - 500° OR 600°

- Assures correct temperature for soldering printed circuits and laminated wiring boards.
- No need to wait for a slow-heating iron — and still have doubtful temperature.
- Just plug into GUNCHOKE and GUNCHOKE into outlet.
- Small, compact, to fit in your tool kit.

FOR ALL WIDELY USED GUNS  
 Get GUNCHOKE from your distributor



**LUGER GUN**

Perfect balance permits delicate touch for most intricate work. Transformer built in handle eliminates tip heaviness. Long, thin tips simplify soldering connections inaccessible with other guns. LUGER is 150-watt capacity.

**ELECTRIC SOLDERING IRON CO., INC.**  
 760 W. Elm Street DEEP RIVER, CONN.

**BECOME A RADIO TECHNICIAN**  
for only \$22.95

# BUILD 16 RADIO

CIRCUITS AT HOME

with the New Progressive

RADIO "EDU-KIT"<sup>®</sup>

All Guaranteed to Work!

PRACTICAL only  
HOME RADIO COURSE \$22.95



Reg. U.S.  
Pat. Off.

NOW INCLUDES

- ★ 12 RECEIVERS
- ★ TRANSMITTER
- ★ SIGNAL TRACER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR

- ★ No Knowledge of Radio Necessary
- ★ No Additional Parts or Tools needed
- ★ Excellent Background for TV
- ★ School Inquiries Invited
- ★ Attractively Gift Packed

## FREE EXTRAS

- SET OF TOOLS • RADIO & ELECTRONICS TESTER • ELECTRIC SOLDERING IRON • TESTER INSTRUCTION MANUAL • MEMBERSHIP IN RADIO-TV CLUB: CONSULTATION SERVICE • HI-FI GUIDE • QUIZZES • TV BOOK • FCC AMATEUR LICENSE TRAINING • RADIO BOOK • PRINTED CIRCUITRY • PLIERS-CUTTERS • ALIGNMENT TOOL • WRENCH SET • CERTIFICATE OF MERIT • VALUABLE DISCOUNT CARD

### WHAT THE "EDU-KIT" OFFERS YOU

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction, servicing, basic Hi-Fi and TV repairs, code, FCC amateur license requirements.

You will learn how to identify radio symbols, how to read and interpret schematics, how to mount and layout radio parts, how to wire and solder, how to operate electronic equipment, how to build radios. Today it is no longer necessary to spend hundreds of dollars for a radio course. You will receive a basic education in radio, worth many times the small price you pay, only \$22.95 complete.

### THE KIT FOR EVERYONE

The Progressive Radio "Edu-Kit" was specifically prepared for any person who has a desire to learn Radio. The "Edu-Kit" has been used successfully by young and old in all parts of the world, by many Radio Schools and Clubs in this country and abroad. It is used for training and rehabilitation of Armed Forces Personnel and Veterans throughout the world.

The Progressive Radio "Edu-Kit" requires no instructor. All instructions are included. Every step is carefully explained. You cannot make a mistake.

### PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore, you must construct radio circuits, perform jobs and conduct experiments to illustrate the principles which you learn.

You begin by examining the various radio parts included in the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set, you will enjoy listening to regular broadcast stations, learn theory, practice testing and troubleshooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will learn yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician.

Included in the "Edu-Kit" course are sixteen Receiver, Transmitter, Code Oscillator, Signal Tracer and Signal Injector circuits. These are not unprofessional "breadboard" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

In order to provide a thorough, well-integrated and easily-learned radio course, the "Edu-Kit" includes practical work as well as theory; troubleshooting in addition to construction; training for all, whether your purpose in learning radio be for hobby, business or job; progressively-arranged material, ranging from simple circuits to well-advanced topics in Hi-Fi and TV. Your studies will be further aided by Quiz materials and our well-known FREE Consultation Service.

### THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build 16 different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable, electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, hookup wire, solder, etc.

In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional electric soldering iron, and a self-powered Dynamic Radio & Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator, in addition to the F.C.C.-type Questions and Answers for Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, and a High Fidelity Guide and Quiz Book. Everything is yours to keep.

J. Statais, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The "Edu-Kit" paid for itself, I was ready to spend \$240 for a course, but I found your ad and sent for your Kit."

### UNCONDITIONAL MONEY-BACK GUARANTEE

The Progressive Radio "Edu-Kit" has been sold to many thousands of individuals, schools and organizations, public and private, throughout the world. It is recognized internationally as the ideal radio course.

By popular demand the Progressive Radio "Edu-Kit" is now available in Spanish as well as English.

It is understood and agreed that should the Progressive Radio "Edu-Kit" be returned to Progressive "Edu-Kits" Inc., for any reason whatever, the purchase price will be refunded in full, without quibble or question, and without delay.

The high recognition which Progressive "Edu-Kits" Inc. has earned through its many years of service to the public is due to its unconditional insistence upon the maintenance of perfect engineering, the highest instructional standards, and 100% adherence to its Unconditional Money-Back Guarantee. As a result, we do not have a single dissatisfied customer throughout the entire world.

ORDER FROM AD—RECEIVE FREE BONUS RESISTOR AND CONDENSER KITS WORTH \$7.00

- Send "Edu-Kit" Postpaid. I enclose full payment of \$22.95.
- Send "Edu-Kit" C.O.D. I will pay \$22.95 plus postage.
- Send me FREE additional information describing "Edu-Kit."

Name.....  
Address.....

**Progressive "EDU-KITS" Inc.**

1186 Broadway, Dept. 161G  
Hewlett, N. Y.

# new PRODUCTS




**TV AMPLIFIER model MLA-B.** Gain 40 db, output 1.7 volts on separate high- and low-band outputs. Response within 1 db overall, within 1/2 db on any channel. Separate gain and 6-



db tilt controls each band.—Blonder-Tongue Laboratories, Inc., 9 Alling St., Newark 2, N.J.

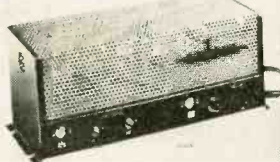**TV MASTER AMPLIFIER model SA-23** 38-db gain, 2 bands, channels 2-6 and 7-13. Tilt and



gain controls for each band. 6 lbs, 12 x 4 1/2 x 5 in.—Entron, Inc., Box 287, Bladensburg, Md.

**LOW-COST MASTING** (aluminum) equal in price to steel tubing. Weighs 66% less than steel, has nonslip fitted joints.



Sections 5, 7 1/2 and 10 ft. 1 1/4-in dia No. 19 gauge. Natural silver or gold-anodized.—JFD Electronics Corp., 6101 16th Ave., Brooklyn 4, N. Y.


**SOLDERING GUN model 8100 B.** Single heat unit, 100 watts, prefocused spotlight. High-efficiency iron-plated copper tip.—Weller Electric Corp., 601 Stone's Crossing Road, Easton, Pa.

**HIGH-VOLTAGE INSULATION.** No-Arc fluid paints on horizontal output transformers and yokes, hardens quickly, insulates up to 20,000 volts. 2-ounce bottle comes with brush applicator.—Chemtronics, Inc., 122 Montgomery St., Brooklyn 25, N. Y.

**AUTO ANTENNAS, series Spring-Magic.** 2- and 3-section telescoping styles with heavy-duty steel spring inside base.

Spring allows rod to push back out of way when obstructions strike, stand back up when clear.—Telco Electronics Mfg. Co., (Div. of GC-Telextron Inc.) 400 S. Wyman St., Rockford, Ill.

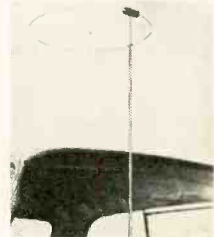**FM AUTO ANTENNA model Halo** fits over standard AM car



antennas, eliminating hole drilling. Aluminum loop. Improves AM reception.—Clear Beam Antenna Corp., 21341 Roscoe Blvd., Canoga Park, Calif.

**PHONE ADAPTER model SW-144** includes speaker disable



switch, level control for phones. Takes 2 sets phones. Complete with 20-foot flat cable.—Olson Radio Corp., 260 S. Forge St., Akron, Ohio.

**EARPHONE** for transistor radios. Model R201 fits 90% of all sets. Includes connector cord.



Snap-on ear holder bends to fit individual wearer.—Rye Sound Corp., Box 210, Mamaroneck, N. Y.

**CITIZENS BAND** tranceiver models W-CB-1 (wired) and CB-1 (kit). Receiver tunes all 23 channels. For 117 v ac; 6- and 12-volt vibrator supplies



# DX-16 Super Deluxe TV KIT

70° or 90° — operating all 17", 21", 24" and 27" PICTURE TUBES



Dimensions 17 1/2" W x 16" D  
Shipping weight 40 lbs.


- ★ Produces a 16-Tube Chassis with 30-Tube performance.
- ★ Latest Intercarrier Circuitry and Multi-section Tubes.
- ★ Standard Neutrode Tuner for Selectivity & Fine Definition.
- ★ All Video and I.F. Coils factory pre-aligned and tuned.
- ★ Large 250ma Power Transformer for dependable service.
- ★ 12" Speaker or Twin-cone 6" x 9" Speaker.

Includes LIFE-SIZE step-by-step Building Instructions  
Most Up-To-Date and Practical Course in Television
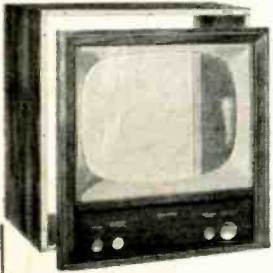
## COMPLETE KIT

with SET OF WESTINGHOUSE TUBES \$93.49  
4-6CB6, 6U8, 6T8, 6C4, 12BH7, 6SN7, 6H06, 6W4, 6K6,  
1X2B, 5U4, 6BN4, 6GC8, incl. in the Tuner (less CRT)

Also sold on EASY-PAYMENT-PLAN Buy LIFE-SIZE Instructions—\$2.49—and buy Parts as you build.



17" TV Cabinet Kit . . \$24.97 24" or 27" TV Cabinet Kit . . \$38.47 24" or 27" Front Panel Assembly . . \$24.97

## BUILD YOUR OWN CABINET FOR TV CHASSIS

Comparable to the type that Top Mfrs. use on high priced TV sets.

CABINET KIT with 90% of the job done, includes—

FRONT SECTION in Solid Mahogany, Walnut or Blond Korina. TOP, SIDES, BACK, MASK, SAFETY GLASS, ETC.

And EASY-TO-FOLLOW ASSEMBLY INSTRUCTIONS

Front, Top and Sides supplied in a beautiful Piano Finish • Knob panel undrilled • For matching Mask specify type or number of CRT used. Same price—Mahogany, Walnut or Blond. (Shipping weight 36 lbs.)

21" CABINET KIT \$26.97

## TECH-MASTER for 1960 ★ "GOLD MEDAL" #2430-N

WORLD'S MOST POWERFUL TV CHASSIS

Latest #630 Type Advanced Circuitry, using 30 Tubes. Available in 90° or 110°. \$175.00  
COMPLETE ready to operate including all Tubes, CRT Brackets, 12" Speaker, Knobs, Etc. (less CRT) . . . \$175.00

Brochure mailed on request

- |  |  |
|--|--|
| VM CHANGER 4-speed incl. Stereo Cartridge. . . \$26.94 | 90° TV CONVERSION KIT all Essential Parts. . . 15.98 |
| RC-121 STEREO GARRARD CHANGER 4-speed 29.97            | 70° TV CONVERSION KIT all Essential Parts. . . 13.97 |
| RC-88 STEREO GARRARD CHANGER 4-speed .44.62            | AGC KIT complete w/6AU6 and instructions . . . 4.59  |
| RC-98 STEREO GARRARD CHANGER 4-speed 53.24             | UNIVERSAL 70° FLYBACK TRANSFORMER 4.86               |
| G.E. STEREO DIAMOND CARTRIDGE #GC7. 11.97              | UNIVERSAL 90° FLYBACK TRANSFORMER 5.24               |
| RONETTE or SONOTONE STEREO CART. . . 3.49              | 17" TV MASK Gray 13 3/4" x 17 1/4" . . . . . 1.49    |
| RECORD CHANGER BASE, any type, any finish 3.41         | 21" TV MASK gray 18" x 22 1/2" . . . . . 2.38        |
| S16 NORELCO 8" HI-FI SPEAKER #3800 . . . 6.94          | 21" TV SAFETY GLASS 18" x 22 1/2" . . . . . 4.93     |
| 12" UNIVERSAL TWIN-CONE SPKR. 6.8 magnet 5.97          | 24" or 27" TV MASK gray 21" x 26" . . . . . 4.13     |
| PHONO MOTOR 4-speed complete with T.T. etc. 4.61       | 24" or 27" TV SAFETY GLASS 21" x 26" . . . . . 5.87  |
| PHONO ARM complete with 4-speed Cartridge . . 3.38     | AC-DC PHONO AMPLIFIER incl 12AT6, 50C5, 35W4 5.98    |
| TWO-STATION INTERCOM, complete with tubes 15.38        | S27 4-SPEED PORTABLE PHONO, complete. . . 13.78      |

Literature on CONVERSION & AGC KITS—Free on request. Stereo Changers and Cartridges we supply, play all records.

**TUBULAR CONDENSERS—85°C TOP QUALITY—Equally as good for Radio or TV work**  
.0047-400v, .01-400v, .02-400v, .047-400v, .001-600v, .0047-600v, .01-600v, .02-600v, .03-600v 5¢ ea.  
.1-400v, .25-400v, .47-400v, .047-600v, .1-600v, .25-600v, .001-1000v, .0047-1000v, .01-1000v, 8¢ ea.  
.035-1000v, .047-1000v, .1-1000v, .007-1600v, .001-1600v, .005-1600v, .001-6000v, .001-6000v, 14¢ ea.

**ELECTROLYTIC CONDENSERS—85°C** 1-50v, 1-150v, 2-450v, 8-150v, 10-150v 19¢ ea.  
20/20-150v, 50/30-150v, 40-150v, 10-450v, 20-450v, 30-450v, 40-450v, 60-450v, 80-450v, . . . . . 34¢ ea.

**CARBON RESISTORS—Regular factory stock in Stackpole, Speer, etc.**  
1/2 WATT 10% 10, 39, 47, 100, 120, 150, 270, 330, 390, 470, 560, 680, 820, 1k, 1800Ω . . . . . 2¢ ea.  
1/2 WATT 10% 2700, 3300, 3900, 4700, 5600, 6800, 8200, 10k, 15k, 18k, 22k, 27k, 33kΩ . . . . . 2¢ ea.  
1/2 WATT 10% 39k, 47k, 50k, 56k, 68k, 82k, 100k, 120k, 150k, 180k, 220k, 270k, 330kΩ . . . . . 2¢ ea.  
1/2 WATT 10% 390k, 470k, 560k, 680k, 820kΩ 1, 1.2, 1.5, 2.2, 6.8, 10, 15 MEGΩ . . . . . 2¢ ea.  
1 WATT 10% 3.3, 10, 39, 100, 120, 150, 330, 470, 560, 680, 820, 1k, 1800, 2700, 4700Ω . . . . . 3¢ ea.  
1 WATT 10% 6800, 10k, 15k, 18k, 22k, 27k, 33k, 39k, 47k, 68k, 82k, 100k, 150k, 470k, 680kΩ . . . . . 3¢ ea.  
2 WATT 10% 18, 22, 82, 100, 180, 2200, 3900, 4700, 6800, 8200, 18k, 22k, 100k, 470kΩ . . . . . 4¢ ea.

**WIREWOUND RESISTORS** 5-5w, 16-10w, 20-10w, 47-5w, 100-5w, 140-5w, 220-5w. 16¢ ea.  
280-10w, 390-5w, 470-5w, 600-10w, 680-10w, 820-5w, 1K-5w, 1K-10w, 1500-5w, 2K-10w. . . . . 16¢ ea.  
2500-5w, 3K-10w, 4700-5w, 5K-10w, 6K-10w, 7K-10w, 8200-5w, 10K-5w, 15K-5w, 22.5K-10w. . . . . 16¢ ea.  
**CERAMIC CONDENSERS** 1, 2, 3, 5, 6.8, 10, 22, 25, 47, 50, 51, 56, 82, 100, 120, 150 mmmf . . . . . 3¢ ea.  
**CERAMIC CONDENSERS** 220, 250, 270, 330, 470, 1k, 1200, 1500, 2k, 5k, 6800, 10k mmmf . . . . . 3¢ ea.  
**MICA CONDENSERS** 5, 10, 25, 50, 56, 68, 75, 100, 120, 150, 220, 270, 330, 470, 510 mmmf . . . . . 3¢ ea.  
**MICA CONDENSERS** 560, 680, 820, 1k, 1500, 2k, 2500, 3300, 4700, 6k, 6800, 8k, 10k mmmf . . . . . 3¢ ea.

- |  |  |   |   |
|--|--|---|---|
| <input type="checkbox"/> 200-SELF TAPPING SCREWS #8 x 1/2" \$1       | <input type="checkbox"/> 1-SELENIUM RECTIFIER 450ma \$1          | <input type="checkbox"/> 25'-INSULATED SHIELDED WIRE \$1              | <input type="checkbox"/> \$15-'JACKPOT' TELEVISION PARTS \$1  |
| <input type="checkbox"/> 50-WING NUTS 8/32 chrome plated \$1         | <input type="checkbox"/> 1-LB. SPOOL ROSIN CORE SOLDER 40/60 \$1 | <input type="checkbox"/> 32'-TEST PROD WIRE deluxe (red or black) \$1 | <input type="checkbox"/> 600-ASST. HDWARE screws, nuts, riv. etc. \$1   |
| <input type="checkbox"/> 1-SILICON RECTIFIER 750 ma 500v \$1         | <input type="checkbox"/> 3-TV ALIGNMENT TOOLS assortment #1 \$1  | <input type="checkbox"/> 100'-FINEST NYLON DIAL CORD best size \$1    | <input type="checkbox"/> 8-ASST. LUCITE CASES handy for parts \$1   |
| <input type="checkbox"/> 5-DIODE CRYSTALS 2-1N21 2-1N22 1-1N64 \$1   | <input type="checkbox"/> 3-TV ALIGNMENT TOOLS assortment #2 \$1  | <input type="checkbox"/> 1-57 INDOOR TV ANT. hi-gain 3 sec. \$1       | <input type="checkbox"/> 2-KENRAD 65M7 TUBES \$1  |
| <input type="checkbox"/> 3-DIODE CRYSTALS 1-1N60, 1-1N64, 1-1N89 \$1 | <input type="checkbox"/> 3-TV ALIGNMENT TOOLS assortment #3 \$1  | <input type="checkbox"/> 1-RCA 70° FLYBACK TRANS. 75240 \$1           | <input type="checkbox"/> 3-RCA 6C4 TUBES \$1  |
| <input type="checkbox"/> 2-SELENIUM RECT. 1-65 ma & 1-250ma \$1      | <input type="checkbox"/> 3-TV ALIGNMENT TOOLS assortment #4 \$1  | <input type="checkbox"/> 1-90° FLYBACK TRANS incl. schematic \$1      | <input type="checkbox"/> 2-GENERAL ELEC. 35W4 TUBES \$1   |
| <input type="checkbox"/> 2-SELENIUM RECT. 1-75ma & 1-150 ma \$1      | <input type="checkbox"/> 3-TV ALIGNMENT TOOLS assortment #5 \$1  | <input type="checkbox"/> 2-ELECTRIC MOTORS 1 1/2 volt. 1001 uses \$1  | <input type="checkbox"/> TOP BRAND TUBES-183, 1X2B, 024, 5U4, 6SN7, 6CB6, 6U8, 6J6, 6V6, 6K6, 6X8, 6AX4, 12AU7 EACH . . . . . \$1 |

EACH ALIGNMENT TOOL is different & valued at over \$1

# "ONE DOLLAR" Buys

As much as \$24 worth — Everything Brand New and sold to you with a money back guarantee.

**DEDUCT 10% ON ANY ORDER OF \$10 OR OVER (ON DOLLAR BUYS)**

Plus a FREE SURPRISE PACKAGE

## 10-TUBES #104.. \$1

Brand New, Mfd. by TUNG-SOL, Regular list price \$2.40 ea. Also serves as a 1T4, 40,000 to go, without limit or reserve. First come first served. 10% off on orders over \$10 applies.

- |   |   |
|---|---|
| <input type="checkbox"/> 1-3" PM SPEAKER alnico #5 magnet \$1         | <input type="checkbox"/> 100-ASST. 1/2 WATT RESISTORS some 50% \$1                      |
| <input type="checkbox"/> 1-4" PM SPEAKER alnico #5 magnet \$1         | <input type="checkbox"/> 70-ASST'ED 1WATT RESISTORS some 50% \$1                        |
| <input type="checkbox"/> 1-5" PM SPEAKER alnico #5 magnet \$1         | <input type="checkbox"/> 35-ASST'ED 2WATT RESISTORS some 50% \$1                        |
| <input type="checkbox"/> 1-2 1/2" WEEBEE SPEAKER for HI-FI \$1        | <input type="checkbox"/> 1-25WATT PRINTED CIRCUIT SOCKETS \$1                           |
| <input type="checkbox"/> 3-AUDIO OUTPUT TRANS. 50L8 type \$1          | <input type="checkbox"/> 50-ASST. TUBULAR CONDENSERS \$1                                |
| <input type="checkbox"/> 3-AUDIO OUTPUT TRANS. 6K6 or 6V6 \$1         | <input type="checkbox"/> 20-TUBULAR CONDENSERS .047-800v \$1                            |
| <input type="checkbox"/> 2-AUDIO OUTPUT TRANS. 6K6 push-pull \$1      | <input type="checkbox"/> 15-TUBULAR CONDENSERS .47-600v \$1                             |
| <input type="checkbox"/> 15-ASST. TV COILS sync, peaking, width \$1   | <input type="checkbox"/> 20-ASST. TUBULAR CONDENSERS .001-1000v \$1                     |
| <input type="checkbox"/> 3-1.F. COIL TRANSFORMERS 456 kc \$1          | <input type="checkbox"/> 20-TUBULAR CONDENSERS .005-800v \$1                            |
| <input type="checkbox"/> 3-1.F. COIL TRANSFORMERS 10.7 mc FM \$1      | <input type="checkbox"/> 20-TUBULAR CONDENSERS .01-800v \$1                             |
| <input type="checkbox"/> 3-1.F. COIL TRANSFORMERS 10.7 mc (auto) \$1  | <input type="checkbox"/> 15-TUBULAR CONDENSERS .25-800v \$1                             |
| <input type="checkbox"/> 4-OVAL LOOP ANTENNAS ass't hi-gain \$1       | <input type="checkbox"/> 10-HV TUB. CONDENSERS .007-1500v \$1                           |
| <input type="checkbox"/> 3-LOOPSTICK ANT. new ferrite adjustable \$1  | <input type="checkbox"/> 10-ASST. RADIO ELECTROLYTIC COND. \$1                          |
| <input type="checkbox"/> 3-VARIABLE COND. super 420/182 mfd \$1       | <input type="checkbox"/> 5-ASST. TV ELECTROLYTIC COND. \$1                              |
| <input type="checkbox"/> 4-ASST. SIZES R.A. DIO CHASSIS PANS \$1      | <input type="checkbox"/> 2-ELECTROLYTIC COND. 40-400-450v \$1                           |
| <input type="checkbox"/> 12-RADIO OSCILLATOR COILS 456 kc \$1         | <input type="checkbox"/> 3-ELECTROLYTIC COND. 80-450v \$1                               |
| <input type="checkbox"/> 3-1/2 MEG. VOLUME CONTROLS w/switch \$1      | <input type="checkbox"/> 3-ELECTROLYTIC COND. 50/30-150v. \$1                           |
| <input type="checkbox"/> 5-50K VOLUME CONTROLS less switch \$1        | <input type="checkbox"/> 30-FP CONDENSER MOUNTING WAFERS \$1                            |
| <input type="checkbox"/> 3-ASST. WATT WIREWOUND CONTROLS \$1          | <input type="checkbox"/> 50-ASST. MICA CONDENSERS .007-1500v \$1                        |
| <input type="checkbox"/> 10-ASST. VOLUME CONTROLS less switch \$1     | <input type="checkbox"/> 50-ASST. CERAMIC COND. some in 5% \$1                          |
| <input type="checkbox"/> 5-ASST. VOLUME CONTROLS w/switch \$1         | <input type="checkbox"/> 50-ASSORTED FUSES popular sizes \$1                            |
| <input type="checkbox"/> 100-VOLUME CONTROL w/switch \$1              | <input type="checkbox"/> 25' SPONGE RUBBER 1 1/4"x1/4" many uses \$1                    |
| <input type="checkbox"/> 10-SURE GRIP ALLIGATOR CLIPS \$1             | <input type="checkbox"/> 50-SOCKETS 1/2 WATT \$1  |
| <input type="checkbox"/> 1-GOLD GRILLE CLOTH 14x14or 12x18 \$1        | <input type="checkbox"/> 50-470K(1/2) WATT RESISTORS 10% \$1                            |
| <input type="checkbox"/> 5-SETS SPEAKER PLUGS wired \$1               | <input type="checkbox"/> 50-2.2 MEGΩ 1/2 W. RESISTORS 10% \$1                           |
| <input type="checkbox"/> 10-SETS PHONO PLUGS and WAXES \$1            | <input type="checkbox"/> 10-ASST. WIREWOUND RES. 5, 10, 25, 50, 100, 250, 500, 1000 \$1 |
| <input type="checkbox"/> 2-52.50 SAPPHIRE NEEDLES 5000 plays \$1      | <input type="checkbox"/> 40-ASSORTED RESISTORS best sizes \$1                           |
| <input type="checkbox"/> 20-ASST. PILOT LIGHTS popular types \$1      | <input type="checkbox"/> 35-ASST. DISC CERAMICS best numbers \$1                        |
| <input type="checkbox"/> 10-PILOT LT. SKTS. bayonet type, wired \$1   | <input type="checkbox"/> 35-DISC CERAMICS 5000 mmmf \$1                                 |
| <input type="checkbox"/> 50-ASST. TERMINAL STRIPS 1, 2, 3, 4 lug \$1  | <input type="checkbox"/> 25-ASSORTED MICA TRIMMER Conds. \$1                            |
| <input type="checkbox"/> 3-SELENIUM RECTIFIERS 65ma \$1               | <input type="checkbox"/> 10-6' ELECTRIC LINE CORDS w/plugs \$1                          |
| <input type="checkbox"/> 35-ASST. RADIO KNOBS. scr. & push. \$1       | <input type="checkbox"/> 5-TV CHEATER CORDS w/both plugs \$1                            |
| <input type="checkbox"/> 75-KNOB SPRINGS standard 3/8" 1/2" \$1       | <input type="checkbox"/> 4-50' SPOOLS HOOK-UP WIRE 4 colors \$1                         |
| <input type="checkbox"/> 100-ASSORTED KNOB SET-SCREWS \$1             | <input type="checkbox"/> 50-STRIP ASST. SPAGHETTI best sizes \$1                        |
| <input type="checkbox"/> 25-ASST. RADIO DIAL POINTERS \$1             | <input type="checkbox"/> 100-ASST. RUBBER GROMMETS best sizes \$1                       |
| <input type="checkbox"/> 25-ASST'ED CLOCK RADIO KNOBS \$1             | <input type="checkbox"/> 100'-TWIN LEAD-IN WIRE 3000' heav. duty \$1                    |
| <input type="checkbox"/> 15-ASST. ROTARY SWITCHES 8 worth \$1         | <input type="checkbox"/> 50'-FLAT 4-COND. WIRE many purposes \$1                        |
| <input type="checkbox"/> 3-TOGGLE SWITCHES 85 spst. dpdt. etc. \$1    | <input type="checkbox"/> 35-MICA COND. 20-5mmf & 15-25 mmf \$1                          |
| <input type="checkbox"/> 6-SLIDE SWITCHES spst. dpdt. etc. \$1        | <input type="checkbox"/> 35-MICA COND. 20-50 mmmf & 15-68mmf \$1                        |
| <input type="checkbox"/> 4-BAKELITE KNIFE SWITCHES 650v \$1           | <input type="checkbox"/> 35-MICA COND. 20-100mmf, 15-270mmf \$1                         |
| <input type="checkbox"/> 35-ASST. SOCKETS octal, nov. & miniature \$1 | <input type="checkbox"/> 35-MICA COND. 20-470mmf, 15-680mmf \$1                         |
| <input type="checkbox"/> 5-TV CRT. SOCKETS with 18" leads \$1         | <input type="checkbox"/> 35-MICA COND. 20-820mmf, 15-1000mmf \$1                        |
| <input type="checkbox"/> 3-TV CARTWHEEL CONDENSERS 20 kv \$1          | <input type="checkbox"/> 35-MICA COND. 20-2200, 15-2400mmf \$1                          |
| <input type="checkbox"/> 1-T. CARTWHEEL CONDENSERS 30kv \$1           | <input type="checkbox"/> 35-MICA COND. 20-3300, 15-4700mmf \$1                          |
| <input type="checkbox"/> 3-HV RECTIFIER SOCKETS 1B3 m'nt'd \$1        | <input type="checkbox"/> 35-MICA COND. 20-6800, 15-10,000mmf \$1                        |
| <input type="checkbox"/> 3-HV RECTIFIER SOCKETS 1X2 m'nt'd \$1        | <input type="checkbox"/> 35-CERAMIC COND. 20-3mmf, 15-10mmf \$1                         |
| <input type="checkbox"/> 20-ASST. TV KNOBS, SWITCHES, etc. \$1        | <input type="checkbox"/> 35-CERAMIC COND. 20-25mmf, 15-47mmf \$1                        |
| <input type="checkbox"/> 25-ASST. PEAKING COILS popular types \$1     | <input type="checkbox"/> 35-CERAMIC COND. 20-200mmf, 15-5000mmf \$1                     |
| <input type="checkbox"/> 1-RCA SYNCHROGUIDE COIL #205R1 \$1           | <input type="checkbox"/> 35-CERAMIC COND. 20-100, 15-150mmf \$1                         |
| <input type="checkbox"/> 1-RCA SYNCHROLOC COIL #20B78 \$1             | <input type="checkbox"/> 35-CERAMIC COND. 20-2070, 15-470mmf \$1                        |
| <input type="checkbox"/> 1-RATIO DETECTOR COIL 4.5 mc \$1             | <input type="checkbox"/> 35-CERAMIC COND. 20-1000, 15-1500mmf \$1                       |
| <input type="checkbox"/> 1-RATIO DETECTOR COIL 10.7 mc \$1            | <input type="checkbox"/> 35-CERAMIC COND. 20-2000, 15-5000mmf \$1                       |

HANDY WAY TO ORDER—Simply tear out advertisement and pencil mark items wanted (X in square is sufficient); enclose with money order or check. You will receive a new copy of this ad for re-orders.

ON SMALL ORDERS—Include stamps for postage, excess will be refunded. Larger orders shipped express collect.

# BROOKS RADIO & TV CORP., 84 Vesey St., Dept. A, New York 7, N. Y. TELEPHONE Corland 7-2359

# H.G. CISIN'S TUBE REPLACEMENT GUIDE

1960 EXPANDED EDITION

EVERYONE who uses vacuum tubes NEEDS this new 1960 Expanded Edition TUBE REPLACEMENT GUIDE!



Contains over 2700 substitutes for over 1500 tubes, including radio & TV receiving tubes, tubes used in Hi-Fi & Stereo, foreign tubes and TV picture tubes.

All tubes suggested for substitution have characteristics similar to those they are to replace, FIT INTO SAME SOCKET & NEED NO WIRING CHANGE.

Two chapters cover complete listing of TV PIX TUBE replacements including newest 110° tubes.

Substitutes given for over 225 foreign tubes. Last chapter lists transistor substitutes. The only complete substitution guide featuring all receiving tube SUBSTITUTIONS WITHOUT SOCKET CHANGES OR REWIRING.

This valuable book will save you TIME & MONEY and permit operation even though original tubes are unavailable.

**Order From Your Parts Jobber or Rush Coupon Below Now!**

**LEARN MORE! EARN MORE!**  
WITH H. G. CISIN'S TV SERVICE BOOKS

Check books desired in spaces at right.

TUBE REPLACEMENT GUIDE See above	\$1.00
TV CONSULTANT—Serviceman's Silent Partner	2.00
SHOOT TV & RADIO TROUBLES FAST	1.50
HOW & WHY OF HI-FI & STEREO—Newest & Best	1.00
ABC OF COLOR TV—Learn this easy way	1.00
TELEVISION DOCTOR—Beginner's Best Buy	1.00
TV TUBE LOCATOR—Vol. 1 '47-'54 Models	1.00
TV TUBE LOCATOR—Vol. 2 '55-'57 Models	1.50
PIX GUIDE WITH TV TERMS	1.00
RAPID TV TROUBLE SHOOTING METHOD	1.00
RCA TV TUBE LOCATION GUIDES—'47 to '55 Models	1.00
ADMIRAL TV TUBE LOCATION GUIDES—'47-'56 Models	1.00
TV TROUBLE TRACER—Vol. 1—Older sets	0.50
TV TROUBLE TRACER—Vol. 2—'52 to '53 Models	0.50
TV TROUBLE TRACER—Vol. 3—'53-'54 Models	0.50
TV TROUBLE TRACER—Vol. 4—'54-'55 Models	0.50
TV TROUBLE TRACER—Vol. 5—'55-'56 Models	0.50
TV TROUBLE TRACER—Vol. 6—'56-'57 Models	0.50
TV TROUBLE TRACER—Vol. 7—1958 Models	0.50
GUIDE TO BASIC ELECTRICITY—Vol. 1	0.50
GUIDE TO BASIC ELECTRICITY—Vol. 2	0.50
GUIDE TO BASIC ELECTRICITY—Vol. 3	0.50
STROBOSCOPE DISC—3-SPEEDS	0.15
TV-RADIO TUBE SUBST. GUIDE—Condensed Edition	0.50
TROUBLE TRACER CHART—Pix Guide	0.35

HARRY G. CISIN, Publisher  
Amagansett, N.Y.

Dept. E-54

Enclosed find \$..... Rush books checked above.

Name.....

Address.....

City..... Zone..... State.....

Minimum Order accepted \$1.00. Sorry, No C.O.D.

## NEW PRODUCTS (Continued)



available for battery operation. Various antennas available. Supplied either as kit or factory-wired.—Heath Co., Benton Harbor, Mich.

CITIZENS BAND tranceiver model G-12. Four crystal-controlled channels. Operates on 12 volts dc or house ac. Push-to-talk




button on microphone. Transmitter 5 watts. Receiver 2.5 watts audio, adjustable squelch.—Gonset Div., Young Spring & Wire Corp., 801 S. Main St., Burbank, Calif.

STEREO TUNER model 330-D. 2 tuners on one chassis. FM sensitivity 2.5  $\mu$ v by IHFM stand-



ard. AM wide-range detector; 3-position AM pass-band switch. Tuning meter switches to FM or AM. Wood case optional.—H. H. Scott, Inc., 111 Powdermill Road, Maynard, Mass.

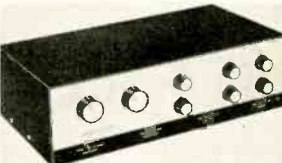STEREO PREAMP KIT PAS-2 includes tape-head channels and extra-low-level channel for user to wire for microphone, extra tape head, second set of



magnetic pickups, etc. Built-in power supply provides dc heater power. Distortion under 0.5% at normal levels, noise 74 db down. Response within 0.5 db 10–40,000 cycles. Also available factory-wired.—Dynaco, Inc., 3916 Powelton Ave., Philadelphia 4, Pa.

STEREO AMPLIFIER. Economy model KN-520 has dual 10-watt units separate bass and treble controls each channel. Response  $\pm 1$  db from 40–15,000 cycles. Distortion 1.5% at 50 cycles, 0.5% at 20 kc. Hum and noise 40 db below rated output at magnetic phono input. Complete with



metal case.—Allied Radio Corp., 100 N. Western Ave., Chicago 80, Ill.

STEREO AMPLIFIER deluxe model KN-760 has dual 30-watt units. Concentric clutch type tone controls, continuously vari-



able stereo separation—blend control, 3-position loudness compensation switch. Stereo channel outputs mixed for third (center) channel speaker. Response 25 to 20,000 cycles within  $\pm 0.5$  db. IM distortion under 2% at rated output. Hum, noise 54 db down at phono inputs, 47 db down at tape-head input. Silicon rectifier supply.—Allied Radio Corp., 100 N. Western Ave., Chicago 80, Ill.

CROSSOVER NETWORK economy model CN-8 high-pass filter for 8- or 16-ohm speak-



ers.—Vidaire Electronics Mfg. Corp., 44 Church St., Baldwin, N. Y.

BULK ERASER for magnetic sound film and tape handles reels



up to 10½-in diameter. Taperaser draws 500 watts from 117 volts ac.—Audiotex Mfg. Co., 400 S. Wyman St., Rockford, Ill.


WIDE-RANGE SPEAKER model 1201B is a 12-inch single-



cone 25-watt unit. Response 48–13,000 cycles. Magnet Alnico 5, 14.5 oz.—General Electric Co., 1285 Boston Ave., Bridgeport, Conn.

LIFETIME STYLUS guaranteed "against wear anytime during the life of the owner" is being made in wide variety of models for most pickups.—Jensen Industries, 7333 W. Harrison St., Forest Park, Ill.

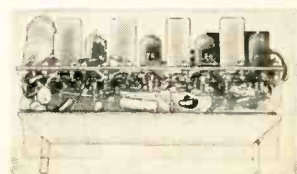BASIC FM TUNER includes rf stage, mixer, ifs, limiters and



discriminator. 6 tubes, pre-wired. Requires power supply. Afc with defeat, cathode-follower output. Sensitivity 1  $\mu$ v for 20-db quiet-

NEW PRODUCTS (Continued)


ing. Selectivity 200 kc at 6 db down. Distortion under 0.5% at 2 volts output.—J. W. Miller Co., 5917 S. Main St., Los Angeles 3, Calif.

**ECONOMY TONE SWITCH** series 200 for original equipment manufacturers. Up to 250 ma at 115 volts ac; 2 or 3 positions;



3, 4, 6 or 9 (shown) contacts. Breakdown 1,000 volts rms.—Centralab, Div. of Globe-Union, Inc., 900 E. Keefe Ave., Milwaukee 1, Wis.

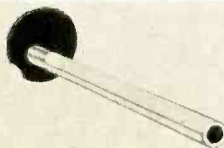**FINE-TUNING SHAFT** replacement No. TS4 extra long length, replaces most TV fine



tuning shafts on sets ranging from Admiral to Zenith. Rotates 360° without stop. Aluminum shaft saws readily.—Eastern Jewel Corp., Rego Park 74, N. Y.

**MICA CAPACITOR KIT. MK-1 Sampler.** 40 silvered micas in 7 most popular ratings from 100 μf to .001 μf, 5% tolerance. 500 volts dc.—Sprague Electric Co., 125 Marshall St., North Adams, Mass.

**SUBMINIATURE ELECTROLYTICS.** Electomite aluminum-foil capacitors. Low leakage, welded terminals.—20 to +85°C.



1-450 μf at 3 volts, 1-18 μf at 150 volts, other values at 3-150 volts. 3/16 x 1/2 in to 3/8 x 1 1/2 in.—Cornell-Dubilier Electric Corp., South Plainfield, N. J.

**TEMP-STABLE CAPACITORS.** Type 820-UB polystyrene



dielectric, low capacitance change with temperature. Temperature-coefficient less than 125 parts per million per degree C. Low dielectric absorption, low dissipation factor. .001 to 0.68 μf; 100, 200, 400, 600 volts.—Good-All Electric Mfg. Co., Ogallala, Nebr.


**RESISTOR LINE.** Bathtub units ceramic-encased, water-proof. 5-watt size, 5-6,000 ohms; 10-watt, 5-15,000 ohms. 4-, 7-,



15- and 20-watt sizes on special order.—Milwaukee Resistor Co., 700 W. Virginia St., Milwaukee 4, Wis.

**1% RESISTORS.** Hot-Coat deposited-carbon, 1/8 and 1/4 watts, high temperature rating, nonreactive coating. Meet MIL-R-10509B specs.—Clarostat Mfg. Co., Inc., Dover, N. H.

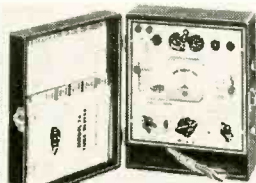**TUBE TESTER** model 78 includes cathode emission and grid-



circuit tests. A 2-stage dc amplifier isolates meter against damage.—Seco Mfg. Co., 5015 Penn Ave., S., Minneapolis, Minn.

**SIGNAL GENERATOR** model RF-1. 100 kc to 110 mc on fundamentals, 220 mc on harmonics.



Rf modulated by built-in 400-cycle generator or external source. 400-cycle audio up to 10

volts available at separate output. Rf output up to 100,000 μv adjustable by attenuator. Frequency calibration within 2%. Preassembled bandswitch and coil factory-aligned.—Heath Co., Benton Harbor, Mich.

**ELECTRON-TUBE ANALYZER** model ETA-100B enables positive evaluation and matching of tubes. Measures true plate, screen current, transconductance at precise voltages.



Gas and leakage test continuously variable to 10 megohms. Determines firing point of thyratrons, regulation of gas-tube regulators, forward and reverse current of small dry-disc rectifiers and diodes. Supplies continuously variable dc voltage for outside circuits 0-100 volts. 50 ma; 0-450 volts 300 ma. Two negative sources from 0-100 volts at 50 ma.—American Scientific Development, Box 404, Janesville, Wis. END

All specifications on these pages are from manufacturers' data.

Get This Valuable Book

**FREE**



Yes, you get this big, brand new book, "150 Radio-Television Picture Patterns and Diagrams Explained", absolutely FREE! Complete 11x22" Schematic Diagrams on leading models Radio and TV Sets help cut your servicing time. Easy-to-read, large 8 1/2 x 11" pages, with full instructions on how to use the diagrams. A "must" in every repair kit. You get this book as a FREE Gift for asking to see Coyne's new 7-book set, "Applied Practical Radio-Television"!

**At Last! Money-Making "Know-How" On Transistors, Color TV and Servicing** Coyne's great 7-volume set gives you all the answers to servicing problems—quickly! For basic "know-how" that's easy to understand you'll find everything you want in Volumes 1 to 5 on over 5000 practical facts and data. Every step from fundamentals to installing, servicing and trouble-shooting all types of radio and TV sets. So up-to-date it includes the latest on COLOR TV and UHF. All this plus Volume 7—TRANSISTOR CIRCUITS—the most complete book ever published on the applications of transistors in electronics. New! Set has colorful design, washable covers.

**EXTRA! 868-Page TV Cyclopeda Included!** For speedy on-the-job use, you also get Vol. 6—famous Coyne CYCLOPEDIA. Answers problems on servicing, alignment, installation, etc. In easy ARC order. Use this 7-volume TV-RADIO LIBRARY FREE for 7 days; get the Servicing Book FREE!

**FREE!**

5 Years Of Valuable Supplements



With your set you also get Coyne's annual Supplement Service FREE for 5 years. Keeps your set up-to-date on everything that will be new in radio, television, electronics and electricity.

Just For Examining COYNE'S New Set

"Applied Practical Radio-Television"

on 7 DAY FREE TRIAL!

**NOW!**  
**7 BIG BOOKS**  
**IN ONE GREAT SET!**



**SEND NO MONEY!** Just mail coupon for 7-volume set on 7 days free trial. We'll include book of 150 TV-Radio Patterns & Diagrams. If you keep the set, pay \$3 in 7 days and \$3 per month until \$27.25 plus postage is paid. (Cash price, only \$24.95). Or you can return the library at our expense in 7 days and owe nothing. **YOU BE THE JUDGE.** Either way, the book of TV-Radio Patterns is yours FREE to keep! Offer is limited. Act NOW!

**FREE BOOK—FREE TRIAL COUPON!**

Educational Book Publishing Division  
COYNE ELECTRICAL SCHOOL, Dept. 20-T1  
1501 W. Congress Pkwy., Chicago 7, Ill.

YES! Send 7-Volume "Applied Practical Radio-Television" for 7 days FREE TRIAL per your offer. Include TV-Radio Patterns & Diagram Book FREE.

Name ..... Age .....

Address .....

City ..... Zone ..... State .....

Where Employed .....

Check here if you want library sent C.O.D. You pay postman \$24.95 plus C.O.D. postage on delivery. 7-day money-back guaranteed.

Educational Book Publishing Division  
**COYNE ELECTRICAL SCHOOL**  
1501 W. Congress Pkwy., Dept. 20-T1, Chicago 7, Ill.

**"TAB" Tubes Tested, Inspected, Boxed**  
Six Months Guarantee!! No Rejects!  
**NEW & Used Gov't & Mfgs. Surplus!**

Orders \$10 or more, Receiving types only ypd, 48 states

0A2	.80	6B16	.69	12AT6	.59	18S1	1.00
0B2	.65	6BK7	.99	12AT7	.84	117Z6	1.10
0C3	.89	6BL7	1.25	12AU6	.69	4-65A	16.00
0D3	.59	6BN6	.98	12B7	.89	2D23	2.75
0Z4	.59	6BQ6	1.19	12AX7	.79	3D23	3.85
1A7	.89	6BZ7	1.25	12BA6	.65	717A	5/81
1B3	.73	6CA7	.43	12BB7	.69	4-125	3/81
1R5	.78	6C5	.69	12BD6	.59	4-250	35.00
1S4	.78	6CB6	.80	12BE6	.59	4E27	7.00
1T4	.78	6CD6	1.19	12BF6	.59	4PR60	29.50

Send \$1 for Catalog!

1U4	3/81	6HG6	3/81	12BH7	.99	4X150	5.00
1K5	.73	6J5	.52	12BY7	.98	4X250	35.00
1X2A	.98	6J6	.48	12C27	.69	4X500	37.81
3Q4	.68	6K6	.59	12CU6	1.45	5BP1	4.98
3Q5	.86	6K7	.74	12SA7	.94	5BP4	4.98
3S4	.68	6L6	1.19	12SQ7	.89	5T	4.00
3V4	.83	6S4	.59	12SM7	.59	100T	7.00
5F4	.98	6S8	.99	12SJ7	.75	316A	5/81
5U4	.99	6S7	.99	12SQ7	.94	28B	3/81
5V4	.89	6SB7	1.19	12SQ7	.89	418B	16.00

Wanted Surplus Electronics from schools & U

5Y3	.59	6SC7	.89	198G6	2.15	450T	42.00
6AB4	.59	6SC7	.79	19T8	1.16	80T	1.00
6AC7	1.70	25BQ6	.69	25BQ6	1.39	409	39.00
6AG7	.89	85J7	.69	25L6	.69	811A	4.40
6AH6	.89	6SK7	.72	25W4	.77	812	3.00
6AK5	.69	6SL7	.89	25Z5	.89	813	9.00
6AL5	2/81	6SN7	2/81	25Z6	.75	814	3.45
6AQ5	.63	85Q7	.74	EL34	3.49	815	2.75
6AS7	3.00	6SR7	3.00	EL37	2.49	817	12.00
6AT6	.49	6T8	.98	35L6	.69	829B	8.00

Wanted 904 (1 tube) Top \$ \$ \$ Paid

6AU4	1.10	6U8	.98	35W4	.49	832A	7.00
6AU5	1.19	6V6GT	.77	35W4	.69	865A	2.75
6AU6	.89	6W4	.79	35Z5	.69	1625	5/81
6AX4	.79	6W6	.89	50A5	.69	6146	4.00
6BA6	.59	6X4	2/81	50B5	.69	5879	.98
6BA7	1.09	6X5	.49	50L6	.89	5881	2.75
6BD6	.89	6Y6	.97	50L6	.69	6550	3.90
6BE6	.59	7N7	.89	K766	3.29	5654	1.00
6BG6	1.30	12AL5	.59	75L6	.89	5894	\$27
6BH6	.72	12AQ5	.75	80	.59	7193	10/\$1

**TUBES WANTED! WE BUY! SELL & TRADE!**

**TRANSISTORIZED DC POWER!**  
HI-EFFICIENCY, DC TO DC TO 450 VDC  
"TABSTAT" KIT or BUILT!  
Output 450 & TAP 250VDC at up to 150 MA/Up to 70 Watts 80% efficiency, ripple 0.2%, low idle current one amp silicon rectifiers, oil condensers, toroid transf. fused & short circuit proof. Regulation 5% at 20 to 100% load! Small in size! Quiet! Light wt! Low priced gtd "TABSTAT" TR1245CB built \$35. Pre-Assembled U-build kit TR1245CK Only \$30. Six V Inpt. TR845CB \$35 or Kit TR845CK \$30. "TABSTAT" 250VDC @ 100MA/1V in TR1245CB \$27. Kit TR1225CK \$24, 6V inpt TR8125CB \$27, Kit TR625CK \$24.



**KITS! "TAB" THE BEST KITS!**  
All Kits Contain Most Popular Values & Sizes

- |                            |                            |
|----------------------------|----------------------------|
| Kit 2 Eng. Parallel Rules  | Kit 5 Sub-Min Tubes        |
| Kit 35 Precision Resistors | Kit 40 Standoff Insulators |
| Kit 10 Switches            | Kit 35 Power Resistors     |
| Kit 75 Resistors 1/2 1/2W  | Kit 75 Mic. Condens.       |
| Kit 150 Carbon Resistors   | Kit 5 Crystal Diodes       |
| Kit 25 Panel Lamp          | Kit 100 Fuses, Assorted    |
| Kit 12 Electrolytic Cond's | Kit 100 Ceramic Cond's.    |
| Kit 56 Tube Sockets        | Kit 10 Germanium Diodes    |
| Kit 65 Tubular Cond's      | Kit 5 FT243 Xtal Holders   |
| Kit 500 Lugs & Eyelets     | Kit 8 Silicon Diodes       |
| Kit 10 Bathtub Oil Cond's  | Kit 5 Microswitches        |
| Kit 5 lbs. Surprise Pckg.  | Kit 4 Ass'd Rectifiers     |
| Kit 10 Xmtrr Mica Cond's.  | Kit 2 PNP Transistors      |
| Kit 3 Phone/Patch Xfmrs.   | Kit 4x50 Ft Hookup Wire    |
| Kit 3 Searchlights         | Kit 2 Veeder Counters      |
| Kit Circular Slide Rule    | Kit 2-Computer Toroids     |
| Kit 12 Algitr Clip Ass'd.  | Kit High Gain XTAL Mike    |

**BUY 10 KITS—GET ONE FREE/EACH KIT 99¢**

**LOW PRICED NEW SILICON 500MA RECTIFIERS GTD!**  
Input Working Range RMS/ACV Res. or Cap.


rms/piv 35/50	rms/piv 70/100	rms/piv 140/200	rms/piv 210/300
39¢	45¢	56¢	65¢
rms/piv 280/400	rms/piv 350/500	rms/piv 420/600	rms/piv 490/700
78¢	\$1.00	\$1.26	\$1.50
rms/piv 560/800	rms/piv 770/1100	rms/piv 770/1100	rms/piv 770/1100
\$1.59	\$1.89	\$2.58	\$3.12

Use in Bridge or C.T. up to 750ma dc  
General Purpose 400PIV @ 250Ma Spt 2 for \$1; 25 for \$10.

\*Postpaid 48 states TopHats only!

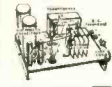**NEW DC POWER for TRANSISTORS!!**

New low-cost 25 volt one amp filtered 10% Ripple Power Supply. Same as specified in Transistor Manuals G.E., RCA, CBS. Ideal for power transistor circuits, rugged & small in size! Preassembled kit U-build B25VIACK \$10, or assembled B25VIACB \$12.



**"TAB" BARGAINS—YOUR BEST BUY!**

- |  |         |
|--|---------|
| BC696/3 to 4 Mc's Xmtrr Good Condition.....  | \$5.95  |
| AN-ARR2/Rcvr As Is Good for Parts.....   | \$1.59  |
| RDX/USN 200-400 Mc's Rcvr less Tubes.....  | \$25.00 |
| RAX/Rcvr covers 4 Bands 1.5 to 9 Mc's Super-Het 8 tubes, has BFO Vernier Ltr Qty!..... | \$24.00 |
| BC653/100 to 200W Xmtrr Phone or CW 2 to 4.5 Mc's includes 12V Dymtrr 5 Channels.....  | \$39.00 |
| "Irish" Tape 1200' HI QTY Gtd \$1.59 @ 6 for \$9                                       |         |
| "Irish" Tape Mylar 2400' ft Best QTY \$4.49, 3/\$12                                    |         |
| Snoopercope Tube 2 \$5 @ 2/\$9   |         |
| 2N277 \$4.50; 2N278 \$5.50; 2N441 \$3; 2N442 \$5                                       |         |

**NEW "TEKSEL" SELENIUM RECTIFIERS**

FULL WAVE BRIDGE RECTIFIERS. ONE YEAR GTD!				
AMP.	18VDC	36VAC	72VAC	144VAC
CONT.	14VDC	28VDC	56VDC	112VDC
1AMP	\$ 1.30	\$ 2.00	\$ 4.90	\$ 9.45
2AMP	2.15	3.00	6.25	12.30
3AMP	3.00	4.00	8.00	15.00
6AMP	4.15	8.00	18.75	36.15
10AMP	6.10	12.15	26.30	48.90
15AMP	9.50	19.00	40.00	86.60
24AMP	15.00	29.45	57.50	108.45


**NEW Selenium Radio & TV Rectifiers! GTD.**  
65Ma 45c. @ 6 for \$2; 100Ma 45c @ 12/\$5; 250Ma 65c @ 10/\$6; 300Ma 85c @ 10/\$8; 500Ma \$1 @ 10/\$8; 25/\$18  
Orders of \$10 or More. Postpaid 48 states! This Item only.

**"TAB"** TERMS: Money Back Guaranteed Our 15th year. \$2 min. order F.O.B. N.Y.C. Add shpg charges or for C.O.D. 25% Dep. Prices shown subject to change.  
111GA LIBERTY ST., N.Y. 6, N.Y.  
Send 25c PHONE: RECTOR 2-6245 for Catalog

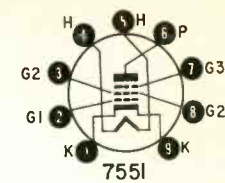**NEW TUBES and SEMI-CONDUCTORS**

**VACUUM** tubes dominate the field this month. There is a vhf TV rf amplifier, a frame-grid amplifier for TV if stages and a beam power tube for mobile communications equipment.

**7551**  
A beam power tube in a 9-pin miniature envelope, the 7551 is designed for reliable service in mobile communications equipment operating from a 12-volt battery system. The 7551 is particularly useful as a class-C rf amplifier, oscillator, or frequency multiplier, at frequencies up to 175 mc. It can also be used in modulator and audio power amplifier applications.




Typical operating characteristics of the RCA 7551 as an rf amplifier at 175 mc are:

	CCS*	ICAS†
Vp	250	300
G3	300	300
connected to cathode		
Vg2	200	200
Vg1	-40	-42
Vg1 (peak rf)	47	52
Ip (ma)	60	70
Ig2 (ma)	3.7	3.7
Ig1 (ma) (approx)	1.5	2.1
Pdriver (watts) (approx)	1	1
Poutput (watts) (approx)	6.5	8.5
		10

\*Continuous Commercial Service  
†Intermittent Commercial and Amateur Service

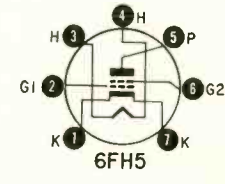**6FH5**  
A semi-remote cutoff tetrode of the 7-pin miniature type intended for use—triode connected—in grounded-cath-



ode rf amplifier circuits of vhf TV tuners. Grid 2, primarily intended as a shield, provides low capacitance be-

**PROFESSIONAL technicians use Dave Rice's OFFICIAL ORDER BOOKS for every TV-RADIO service call**



This is the businesslike approach to service record keeping. Triuplicate forms serve as order form, invoice and office record, with spaces for complete information on every job. Separate listings for receiving tubes, pix tube, parts, serial numbers, labor and tax charges, signatures, etc. 75c a book, \$6.50 for dust-proof box of 10. In stock at your distributor. Write for your free folder describing Dave Rice's OFFICIAL ORDER BOOKS, including an actual size sample copy of the handy order form.

For customer's prices on every replacement part, plus flat rate and hourly service charge data, regional and national, Dave Rice's OFFICIAL PRICING DIGEST, listing over 63,000 items. \$2.50.

**HEART DISEASE Enemy #1 HEART FUND Defense #1**

**GIVE**

**ELECTRONIC PUBLISHING CO., INC.**  
180 N. WACKER DRIVE  
CHICAGO 6, ILLINOIS


tween grid 1 and plate to facilitate neutralization and reduce oscillator radiation. When connected as a triode, the RCA 6FH5 features high transconductance at low plate voltage to provide high gain.

Characteristics of the 6FH5 in Class-A1 amplifier service with its cathode connected to grid 2 are:

$V_p$	135
$V_{G1}$	-1
$R_p$	5,600
$g_m$ ( $\mu$ mhos)	9,000
$\mu$	50
$I_p$ (ma)	11
$V_{G1}$ for	
$I_p=100 \mu a$	-5.5
$V_{htr}$	6.3
$I_{htr}$ (ma)	200

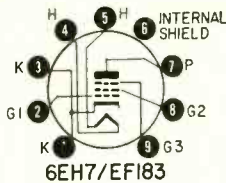**6EH7/EF183**

A frame-grid remote-cutoff pentode designed for use as an amplifier in TV receivers. Its high transconductance, low interelectrode and feedback capacitances make possible the construction of simplified broad-band amplifiers with high stability.




Typical operating characteristics of the Amperex 6EH7/EF183 are:

$V_p$	200
$V_{G2}$ supply	200
$V_{G1}$	0
$R_{G2}$ (series) (ohms)	27,000
$V_{G1}$	-2
$g_m$ ( $\mu$ mhos)	12,500
$I_p$ (ma)	12
$I_{G2}$ (ma)	4.5
$R_p$ (ohms)	500,000
$R_{input}$ (ohms)	11,000

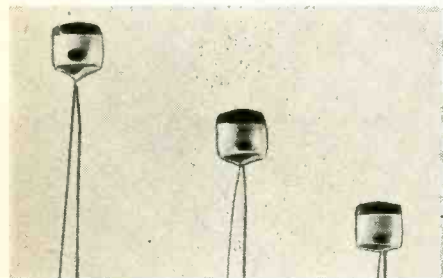**Selenium diodes**

These subminiature plastic-encapsulated units have been developed by Radio Receptor. Capable of operating in temperatures between  $-50^{\circ}C$  and  $100^{\circ}C$  without derating, the diodes come in eight types with peak-inverse-



voltage ranges of 50-400 at 12.5 ma. Maximum case length is only 0.380 inch with widths ranging from 0.340 to 0.480 inch. Applications cover computers, business machines, arc suppressors, power supplies, radios, TV sets, hearing aids and electric games.

**7558**

A beam-power tube in a 9-pin miniature envelope designed for use in fixed-

# Transistor Radio Servicing CAN be Highly Profitable




**The ONLY Complete Transistor Radio Service Lab**  
Everything you need for less than \$50



**Check Transistors, Diodes, Rectifiers . . .**

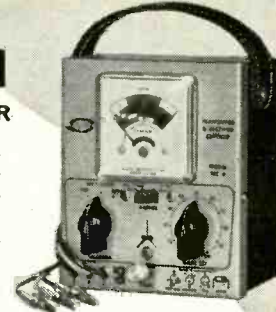**SENCORE TRC4 TRANSISTOR CHECKER**


Accurately checks all transistors in hearing aids, radios and power transistors in auto radios. Tests for opens, shorts, leakage, current gain. Measures forward-reverse current ratio on all crystal diodes. Measures forward and reverse currents on selenium rectifiers. With set-up chart for accurate checking of each transistor. Size,  $5x4\frac{1}{2}x2\frac{1}{2}$ ". With batteries. DEALER NET..... **17<sup>95</sup>**



**Replace Batteries During Repair . . .**

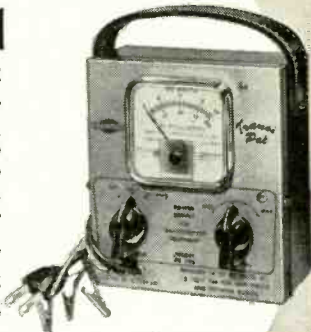**SENCORE PS103 BATTERY ELIMINATOR**

All-new "Transi-Pak," twin to TRC4 Checker above. Provides variable DC voltage to 24 volts; 1.5-volt biasing tap (a "must" for servicing Philco and Sylvania radios). Metered current output, to 100 ma. Handles 200-ma peaks. Two 200-mfd electrolytics provide proper filtering and low output impedance. No hum or feedback problems. Ideal for alignment using station signal; adjust IF slugs for max. current, also ideal for charging nickel-cadmium batteries. Size,  $5x4\frac{1}{2}x2\frac{1}{2}$ ". DEALER NET..... **17<sup>95</sup>**



**Find Defective Stage in a Minute . . .**

**SENCORE HG104 HARMONIC GENERATOR**

New signal generator designed primarily for fast signal-tracing of transistor radio circuits. No need to unsolder all transistors. Provides RF, IF and audio signals *simultaneously*, drastically cutting service time. Traces from speaker to antenna. Clear 1000 cycle note signal is heard in speaker from all good stages. Signal weakens or stops at defective stage. Equally as effective for testing TV, hi-fi and other audio circuits also. Size,  $3\frac{1}{2}x4\frac{1}{2}x1\frac{3}{4}$ ". With batteries. DEALER NET..... **9<sup>95</sup>**



Turn page for other



See your Parts Distributor NOW!

# SENCORE

ADDISON 2, ILLINOIS

**OPPORTUNITY ADLETS**

Rates—50c per word (including name, address and initials). Minimum ad 10 words. Cash must accompany all ads except those placed by accredited agencies. Discount, 10% for 12 consecutive issues. Misleading or objectionable ads not accepted. Copy for March issue must reach us before Jan. 15, 1959.

**RADIO-ELECTRONICS**

154 West 14 St., New York 11, N. Y.

PRINTING PRESSES, type, supplies. Lists 4c. TURN-BAUGH SERVICE, Mechanicsburg, Pa.

LEARN CIVIL and criminal investigation at home. Earn steady, good pay. INSTITUTE APPLIED SCIENCE, 1920 Sunnyside, Dept. 262, Chicago 40, Ill.

RADIO & TV TUBES at Manufacturers' Prices! 100% Guaranteed! Brand New! No re-brands or pulls! UNITED RADIO, Box 1000, Newark, N.J.

STEREO TAPE RENTALS. For the very best at lowest prices. Write CALIFORNIA TAPED MUSIC ASSN., 763 El Camino Real, Redwood City, Calif.

CASH PAID! Sell your surplus electronic tubes. Want unused, clean radio and TV receiving, transmitting, special-purpose, Magnetrons, Klystrons, broadcast types, etc. Want military & commercial lab/test and communications equipment such as G.R., H.F., AN/UJM prehs. Also want commercial receivers and transmitters. For a fair deal write BARRY, 512 Broadway, New York 12, N. Y. WALKER 5-7000.

Hi-Fi, Recorders, Tapes. FREE Wholesale Catalogue. CARSTON, 215-T East 88th St., New York 28, N. Y.

DISCOUNTS UP TO 50% on Hi-Fi amplifiers, tuners, speakers, tape recorders, individual quotations only, no catalogs. CLASSIFIED HI-FI EXCHANGE, 2375 East 65th Street, Brooklyn 34, N. Y.

CAMERA Repairmen greatly needed! You can learn manufacturers' service methods at home, in your spare time! Free, big illustrated book tells how! Write today. NATIONAL CAMERA REPAIR SCHOOL, Dept. RE-2, Englewood, Colorado.

SONGPOEMS and LYRICS WANTED! Mail to: TIN PAN ALLEY, INC. 1650 Broadway, New York 19, N. Y.

PRINTED CIRCUIT BOARDS designed, manufactured. Custom PC kits. Brochure. Electronic Aids, Box 137, Stamford, Conn.

TELE-VUE Troubleshooter is the answer to all your servicing problems. Waste no time on book theory. Eliminate guesswork. Spots faults in minutes. 3 years advanced research developing this complete repair guide. Get FREE FACTS. Write Dept. RE, National Technical Research Labs., 1118 W. Hadley St., Whittier, Calif.

PROFESSIONAL electronic projects — Organs, Timers, Computers, etc.—\$1 each. List Free. PARKS, Box 1665, Seattle 55, Wash.

(Continued on p. 145)

why your next speaker system should be

# THE NEW AUDAX PARAFLEX

- Only Audax incorporates the Patented Paraflex Foam Suspension to give longer travel to the cone, resulting in honest bass without boom or hangover. You get bass with real bottom!

- New Styrofoam Radial Strut-Bracing reinforces cone, assures rigid piston action, preventing cone break-up. Eliminates distortion, provides clean reproduction up to the full-rated power output. Needs as little as 10 watts output. You get greater amplifier economy in stereo installations.

- New Oriented Grain-Processed Magnet gives 20% more efficiency than standard Alnico V.

- New Ducted-Slot Enclosure specifically designed to enhance the depth and striking realism of the Paraflex high-compliance speaker units. Speakers are located symmetrically on each side of the ducted slot, resulting in clean bass without trace of boom or unnatural heaviness.


- New, dramatic enclosure styling by George Nelson—featuring... new, three-dimensional Dynel "Acoustiscreen" grille, removable for cleaning!

- Audax Paraflex Speakers are lab-tested and a performance seal on each unit indicates its resonant frequency  $\pm 1$  cycle.

Model CA-80 12" x 12" x 24" with two full range speakers—\$99.95

Model CA-100 15" x 12" x 25" with two 10" full range speakers and 2 matching cone tweeters—\$139.95

Also full line of component speakers

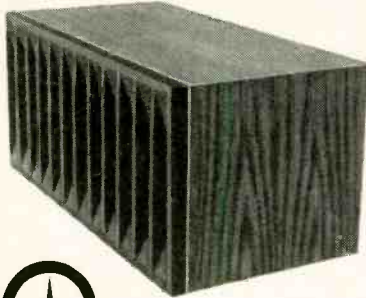


Write for free catalog and specifications, to: AUDAX Division of the Rek-O-Kut Co., Inc. Dept. RE-2, 38-19 108th St., Corona 68, N. Y.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_

Export: Morhan Exporting Corp., 458 Broadway, New York 13  
Canada: Atlas Radio Corp., 50 Wingold Ave., Toronto 19, Ont.

## NEW TUBES & SEMICONDUCTORS (Cont'd)

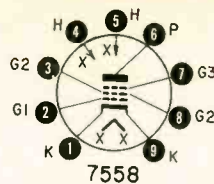

station communications equipment. The 7558 is particularly useful in class-C rf amplifier, oscillator and frequency-multiplier service up to 175 mc. It can also be used in modulator and audio-frequency power amplifiers.

Maximum ratings of the RCA 7558 as an rf power amplifier and oscillator (class-C Telegraphy) and rf power amplifier (class-C FM Telephony) are:

	CCS*	ICAS†
$V_P$	300	300
$V_{G3}$	connected to cathode	
$V_{G2}$	250	250
$V_{G1}$	-125	-125
$I_P$ (ma)	70	80
$I_{G2}$ (ma)	15	15
$I_{G1}$ (ma)	5	5
Plate input (watts)	21	24
$G2$ input (watts)	2	2
$P_P$ (watts)	10	12

\*Continuous Commercial Service

†Intermittent Commercial and Amateur Service

Maximum characteristics are:

gm ( $\mu$ mhos) 6,400

### Miscellaneous

Image orthicon unveiled by G-E—type GL-7929—produces pictures of usable black-and-white quality at 1-foot-

candle illumination compared to the 10 foot-candles required by standard camera tubes. The tube is electrically interchangeable with standard camera tubes. Extreme sensitivity results mainly from a high-gain thin-film target of magnesium oxide.

Spruce Pine Mica Co. is offering a line of 23 mica transistor washers. All are .002 inch thick and will insulate transistors from a chassis without reducing heat-sink characteristics appreciably.

Motorola is turning out three kinds of transistor mounting kits so power transistors can be mounted electrically isolated from a chassis or heat sink while excellent heat-transfer characteristics are maintained. Kits mount all power transistors in the TO-3 and TO-5 packages.

Style 33 silicon rectifier produced by Syntron is rated at 37.5 amps at 25°C



on a 5 x 5 x 1/2-inch copper heat sink. Piv ranges from 50-400 volts in 50-volt steps.

END



D-612T

\$49.95

serviceman's net



## FIRST 3 in 1 POWER SUPPLY

1. powers transistor personal radios
2. powers transistor auto radios
3. powers 12/6 volt tube/transistor auto radios

Outservices, outlasts all others in its price class. Reserve power to handle all servicing. Low AC ripple: less than 0.5% up to 5 amperes. 2% at 10 amperes. Best regulation to operate solenoid tuning controls. Two ranges: 0-8 and 0-16 volts continuously variable. 10 amperes at 12 volts continuous duty. 20 amperes intermittent. Patented conduction cooling lengthens rectifier life and increases capacity.

Compare the difference at your distributor or request Bulletin D-612T

ELECTRO PRODUCTS LABORATORIES 4501-R Ravenswood, Chicago 41  
Canada: Atlas Radio Corporation Ltd., Toronto



# FIRST TO POWER ALL THREE!



**TRY THIS ONE**

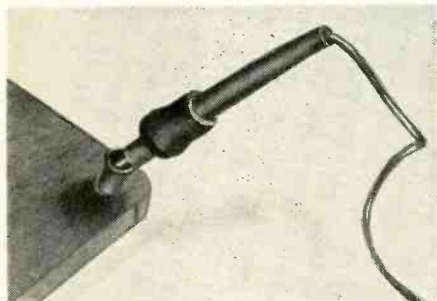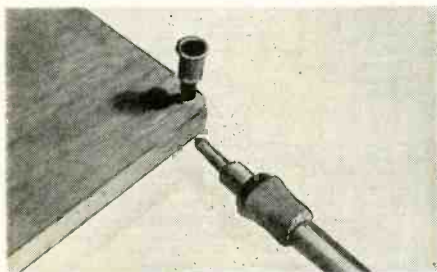**PENCIL-IRON REST**

Sometimes the correct place to put a pencil iron on the bench is hard to find. One excellent solution is to use a discarded 1B3 tube. Break away the glass envelope from the metal cap and skirt.



Then drill a hole in the bench large enough for the cap to be inserted in and you have a permanent iron holder that will never be in the way. With the tip of the iron inserted as the heating element, it can also be used as a miniature solder pot for multiple tinning operations, etc.—*J. Burton Burnett*

**FOIL FOILS INTERMITTENTS**


Does that thermal intermittent have you baffled because it has jumped back into its hiding place now that you have removed the chassis from its cabinet? Here may be the answer to your problem. Wrap all suspected tubes with aluminum foil, and set the chassis on a sheet of foil tacked to the bench. The aluminum foil will reflect dissipated heat, hasten set warmup and help ferret out the defective component.

This kink often works where soldering iron, heat lamp and hair dryers fail.—*James C. Conrad*

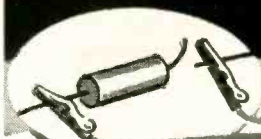**IMPROVE RELAY SENSITIVITY**

Many factors affect the sensitivity of a relay, and most cannot readily be altered without major rebuilding. To get a great improvement, try adjusting the relay armature and contacts.

*Servicemen!* **SAVE TIME...SUBSTITUTE THE SENCORE WAY**



**The Fastest, Surest Method Known!**

**Substitute for Capacitors, Resistors**

**SENCORE H-36—THE "HANDY 36"**

36 most-often-needed resistors and capacitors, for fast, easy, direct substitution in all circuits. • Eliminates searching for replacement components for test purposes. • Avoids unnecessary unsoldering and soldering—no more solder mess. • Pays for itself the first month in time saved. • Flick of a switch instantly selects any one of...

- 24 RESISTORS from 10 ohms to 5.6 megohms
  - 10 CAPACITORS from 100 mmfd to .5 mfd
  - 2 ELECTROLYTICS, 10 mfd and 40 mfd
- DEALER NET..... **1275**

**Substitute for Electrolytic Capacitors**

**SENCORE ES102 ELECTRO-SUB**

Usable from 2 to 450 volts, D.C.

Contains 10 electrolytics from 4 to 350 mfd. Select the correct value with the flick of a switch. Features automatic discharge, surge protector circuit. Prevents accidental "healing" of capacitor being bridged. Completely safe—no arc or spark when connecting or disconnecting. DEALER NET..... **1595**

**Substitute for Fuse Resistors During Repair**

**SENCORE FS3 "FUSE-SAFE" CIRCUIT TESTER**

Instantly tells you whether or not it is safe to replace fuse resistors, fuses, or circuit breakers. Separate red and green scale for each commercially available fuse resistor used in radio and TV. Eliminates guesswork and wasted time. Also handy for wattage checks up to 1100 watts. DEALER NET..... **895**


**Substitute for Bias Batteries During Repair**

**SENCORE BE3 "ALIGN-O-PAK"**

Completely isolated DC supply, with less than 0.1% ripple. Eliminates messy batteries in TV service work. Handy for alignment, AGC trouble-shooting, or checking gated sync circuits. Just dial the voltage you need, 0-18 volts, positive or negative. Covers all voltages recommended by TV set manufacturers. Size, 3½x4½x1¼". For 110-120 volts, 60 cycle AC. DEALER NET..... **785**

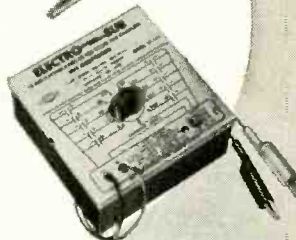**UNIVERSAL TV JUMPER CORD**

Fits any set from back to chassis. Box has male and female plugs for additional power source, soldering, etc. DEALER NET **195**



Turn page for other



See your Parts Distributor Now!

**SENCORE**

ADDISON 2, ILLINOIS

**OPPORTUNITY ADLETS (Continued from p. 143)**

TRADE-IN TV \$6 up; also color. Write JUSTIS, Newport, Del.

LEARN WHILE ASLEEP. Hypnotize with your recorder, phonograph or amazing new Electronic Educator endless tape recorder. Catalog, details free. SLEEP-LEARNING ASSOCIATION, Box 24-RD, Olympia, Wash.

RENT STEREO TAPES. Over 900 different, all major labels. Free catalog. Stereo-Part, 1608-K Centinela Ave., Inglewood 3, Calif.

HI-FI DOCTOR—will solve your hi-fi problems on the spot. Acoustic, Audio, Radio Engineer. Stereo Designing. Professional visits, day evening, New York area. WILLIAM BOHN, Plaza 7-8569, weekdays.

DIAGRAMS FOR REPAIRING RADIOS \$1. Television \$2. Give make, Model. DIAGRAM SERVICE, Box 627-RE, Hartford 1, Conn.

ALL MAKES OF ELECTRICAL INSTRUMENTS AND TESTING equipment repaired. HAZELTON INSTRUMENT CO., 128 Liberty Street, New York, N.Y.

SPECIAL! RUBBER STAMP with pad—Three lines \$1.00. IDEAL RUBBER STAMPS, Box 21, Camden, Tenn.

5-INCH TV Test CRT. Complete with adapter \$3.95 post paid. CRYSTAL ELECTRONICS, 9507 101st Ave., Ozone Park, N.Y. HI 1-0700.

LITERATURE THAT WILL place you in a position to pass FCC commercial phone exams. Not a course. Write Postcard for free details. WALLACE COOK, Box 10634M, Jackson 9, Miss.

*Looking?*

You stand a better chance of finding what you want if you advertise in RADIO-ELECTRONICS Opportunity Adlets. See details on page 143.

**NEW FOR 1960! EXCLUSIVE OFFER**  
**FREE!** CHOOSE ANY 2  
**PAKETTES**  
 WITH EVERY 12 PAKETTE ORDERS

6 PAKETTE ORDERS—CHOOSE 1 PAKETTE FREE

- 6 SUBMINIATURE DIODES  
Germanium, silicon, etc.  
Only 1/4" long. Excellent for transistor circuits. Color coded. Equivalent to 1N34A, 1N43, 1N56, 1N38A, 1N60. Some \$1 worth \$2 ea.
- TRANSISTOR RADIO BASIC  
Incl. transistor & socket, diode, loop, stick. In handy packets. \$1
- 2 POWER TRANSISTORS  
Handles 10 watts. For cars, etc. Worth \$10 \$1
- 2 SILICON RECTIFIERS  
500 mil. Axial leads. Size of 1W resist. Reg. \$3 ea. \$1
- 8-PC. NUTDRIVER SET  
Molded, lucite handle. Steel socket, wrenches. 3/16, 7/32, 1/4, 3/16, 11/32, 7/16". In carry case. \$1
- 10 PANEL SWITCHES  
115 VAC, micro, slide, etc. Some worth \$1 \$1.50 ea. \$1
- 4 OUTPUT XFMRs  
50L6, 6V6, 6K6, etc. Open frame types. Some worth \$2.50 ea. \$1
- 2 FLEA POWER MOTORS  
1 1/2 VDC. Powerful. 100's of control uses. \$1
- 40 TUBE SOCKETS  
4, 5, 6, 7, 8, 9 pins. Octals, mini types. Some shield, some ceramic. Reg. \$10. \$1
- 40 DISC CONDENSERS  
Incl. world's finest; only 1/4" x 10mm! to 1000 VDC. \$1
- 30 "SEALED" CIRCUITS  
Built-in resistor coupling networks. Reg. \$20. \$1
- 40 MOLDED CONDENSERS  
0.001 to 1 to 1000 VDC. Oils, porcelain, black beauties. Reg. \$3 \$3.00
- 65 RESISTOR SPECIAL  
W.W., & carbon, prect. min. power, variable. mini types too. 1/2W to 50W. Reg. \$17. \$1
- 40 POWER RESISTORS  
5 to 50W to 10,000 ohms. Reg. \$15. \$1
- 50 TRANSISTOR COND.  
Mini condensers. 0.00025 to 0.1 mf. In 100's of trans. sets. Reg. \$7. \$1
- 100 HALF WATTERS  
Resistors, carbon, 10 ohms to 2 meg. 10% tol. Pop'l'r makers. Reg. \$1 \$10.
- 15 "GRAIN-O-WHEAT"  
Lamps: by G-E, 1.5 VDC. For mini. \$1 worth. Worth 25¢. \$1
- 70 MICA CONDENSERS  
0.00025 to .01 to 1000 VDC. "Silvers" too. 20 values. Reg. \$1 \$13.
- 35 TWO WATTERS  
10 radio & TV values; 100 ohms to 500k. 5¢ too. Reg. \$8. \$1
- 15 ROTARY SWITCHES  
1, 2, 3 gang; long shafts. Pop'l'r types. Reg. \$15. \$1
- 15 VOLUME CONTROLS  
Long & useable shafts. Up to 1 meg. Singles, duals, switch types. Reg. \$20. \$1
- 2 SOLAR BATTERIES  
Generates power from Sun & "bulb" light. 100's of projects. Reg. \$4. \$1
- 20 TWIST DRILLS  
1/16 thru 1/4" with calibrated case. For electric drills. Reg. \$1 \$2.50.
- 24 ARTISTS BRUSHES  
1 to 8 sizes. 100% pure camel hair \$1
- 40 HI Q CONDENSERS  
NPO's, standoff types too. 20 values. Finest prec. quality. \$1 Reg. \$9.

**NEW! 20-in-1 PAKETTE**

Introductory Special! Carbons, wirewounds, volume control, precision condensers, electros, ceramics, mica, paper discs, hi-G, molybdenum oils, diodes, wire, switches, transistor diodes, sockets, tie strips, coils; in handy PAKETTE. Satisfaction **\$2.00** guaranteed.


- FREE! WRITE FOR GIANT BARGAIN CATALOG
- Minimum Order \$2.00
- Include check or M.O. with sufficient postage; excess returned.
- C.O.D. orders, 25% down; rated, net 30 days. INCLUDE POSTAL ZONE in address. (Canada postage, 48¢ 1lb.; 28¢ ea. additional lb.)

- My FREE PAKETTES are:
- Check each item wanted
  - Return ad with order
  - Avg. 1 lb. per Pakette.
  - Each Pakette Guaranteed

**LEKTRON**  
 131 Everett Ave.  
 CHELSEA 50, MASS.

TRY THIS ONE (Continued)

The spring tension on the relay armature has an appreciable affect on sensitivity. Tension should be adjusted to the absolute minimum required to operate the relay. Spring tension is usually adjusted by bending the metal tab to which it is anchored. Sometimes the original spring has to be replaced by a lighter one that has less tension. The spacing of the relay contacts also affects its sensitivity. They should be set to the absolute minimum clearance, in the open position, that prevents arcing. Much more current is required to close a relay than to keep it closed because the magnetic flux is denser near the coil core. To increase sensitivity further, the clearance between the armature and the coil core, in the closed position, should be the absolute minimum that keeps them from touching. After these adjustments are made, the relay will be as sensitive as possible without changing the coil and core design.—Albert J. Krukowski

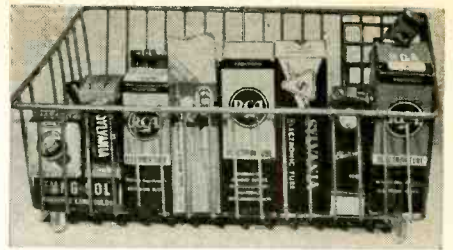


pick one up at the five and dime.—Harry Leeper

**STRIPPING SHORT HARNESSSED WIRES**

Here's how to use automatic wire strippers to strip short lengths of wiring harness. Simply loop a piece of scrap wire around the cable and grip this scrap with one set of jaws and the short lead with the stripping jaws. —Hugh Lineback

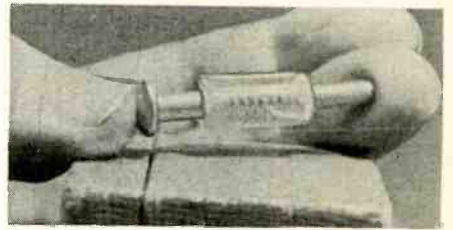**USE A BALLPOINT PEN**

Technicians will have frequent need for the handy items that can be made from the sleeve of a plastic (or metal)




**TUBE HOLDER**

Most technicians have a stock of bench tubes that are used exclusively for testing. When a bad tube is returned to its carton and a new tube from the technician's stock is installed in the set. To keep these bench tubes on hand and not all over the bench, try using an ordinary dish drainer—you can

**EASIER TO BUILD LAYER BUILT COLOR GUIDE**

**Grommes DE LUXE HI-FIDELITY KITS**

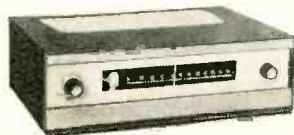

101GTK FM TUNER

Finest tuner kit offered! "Standard Coil" tuning unit is pre-wired, pre-aligned and can be tuned-in as soon as completed, without professional adjustments. Better reception than tuners costing 2 or 3 times as much. Latest circuits, matched crystal diode detector, Foster Seeley Discriminator, AFC, Electronic Tuning Eye, Quiet, drift-free. Simply and successfully assembled by anyone with screwdriver, pliers and soldering iron. Step-by-step Instructions. Model 101GTK, only \$59.50



20 WATT STEREO AMP.  
De Luxe stereo at half the cost! Two 10 watt channels with 2 pre-amplifiers, 40 watts peak. Fre. Res. ±0.5dB. 20-20,000 CPS. Complete controls. 20LJK ..... \$59.50



10 WATT AMPLIFIER  
With built-in pre-amp. 20 watts peak. Fre. Res. ±1DB. 20-20,000 CPS. 4 inputs. Output: 4, 8, 16 ohms. Automatic Loudness Control. 1J6K ..... \$24.95

Many other kits available—  
 At dealers or sent prepaid with check or M.O.

**FREE!**

GROMMES Div. of Precision Electronics, Inc.  
 9101-N King Ave., Franklin Park, Ill.  
 Please rush details on Grommes Kit Line.

Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_ State \_\_\_\_\_  
 Your Dealer's Name \_\_\_\_\_

**TV PICTURE TUBES**

At Lowest Prices

10BP4	7.95	17BP4	9.95	21AMP4	15.75
12LP4	8.50	17CP4	17.00	21ATP4	15.75
14B/CP4	9.95	17GP4	17.60	21AUP4	15.75
16DP4	12.00	17HP4	12.50	21EP4	13.50
16EP4	12.75	17LP4	11.50	21FP4	14.50
16GP4	14.50	17QP4	9.95	21WP4	14.00
16KP4	9.95	17TP4	17.00	21YP4	14.50
16LP4	10.95	19AP4	16.00	21ZP4	13.50
16RP4	9.95	20CP4	13.50	24CP4	23.50
16WP4	12.00	20HP4	14.50	24DP4	24.50
16PT4	9.95	21AP4	22.10	27EP4	39.95
17AVP4	12.50	21ALP4	15.75	27RP4	39.95

1 year warranty

Aluminized Tubes \$5.00 more than above prices. Prices include the return of an acceptable similar tube under vacuum. These tubes are manufactured from reprocessed used glass bulbs. All parts and materials including the electron gun are brand new.

ALL PRICES FOR CHICAGO, ILLINOIS. Deposit required, when old tube is not returned, refundable at time of return. 25% deposit required on C.O.D. shipments. Old tubes must be returned prepaid. Tubes shipped Rail Express.

WRITE FOR COMPLETE LIST.

**PICTURE TUBE OUTLET**

3032 Milwaukee Ave., Chicago 18, Ill.  
 Dickens 2-2048

Please mention  
**RADIO-ELECTRONICS**  
 when answering ads


**WHY PAY MORE?**

BONAFIDE now offers the biggest discounts on all famous HI-FI & Stereo components or kits of your choice.

**BIG TRADE-IN ALLOWANCES**  
 We can give you the best deal & expert advice but also guarantee everything sold. Write for our special price quotations on package deals. No sale too small.

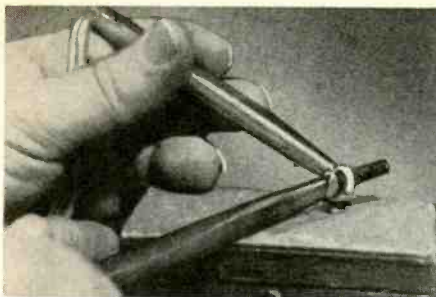
**BONAFIDE ELECTRONICS**  
 Dept. RE2, 89 1/2 Cortland St., N.Y. 7, N.Y.





ballpoint pen. An insulating sleeve of any length up to 5 inches can be made from the sleeve of a discarded plastic pen. Insulators for electrical testing prods are another possibility.

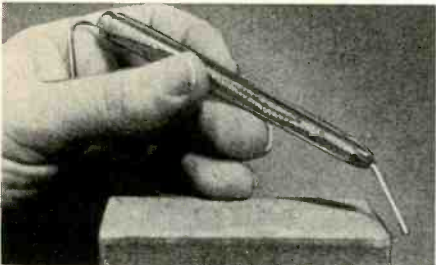Run the ends of a length of string through a ballpoint-pen sleeve, and the resulting loop at one end of the barrel will make a holder for a screw or bolt that must be inserted into an almost inaccessible hole on a TV chassis. For somewhat similar use, insert a straight-



ened-out paper clip in such a sleeve and use it to get a drop or two of light oil to a normally inaccessible spot.

Convenient-size bushings and insulated feet for any lightweight chassis are other items that can be made in a minute from these handy sleeves. For insulating feet, thread the inside of the sleeve for a proper-size screw.—*Glen F. Stillwell*

### INVERTED CARTONS MARK EMPTIES

To tell which tube cartons in our caddy are empty, we always put the empty cartons back so that the writing on the end flap is upside down. This makes it a much easier job when the caddy is refilled, and eliminates the possibility of cartons being carried around empty.—*John C. Alexander*

### VIALS HOLD BATTERIES

I have found that small plastic vials that are used as containers for five and dime store items can be made into ideal battery holders for compact transistor circuits. The vials are a perfect fit for penlight batteries and are very easily fitted with screw contacts at either end for voltage pickup.

If exhausted batteries are accidentally left in the plastic holders, there's no danger of acid leakage ruining the holder. This is an advantage over metal types that are soon destroyed by acid.

The screw terminals at either end can be tightened to hold the batteries very securely in the case, thus assuring positive contact at all times.—*John C. Abram*

# Check TUBES, VIBRATORS THE SENCORE WAY




America's Most Popular Tube Tester  
more than 25,000 now in use
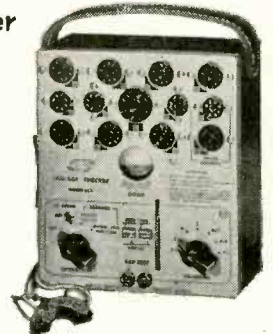
## SENCORE LC3 LEAKAGE CHECKER

Whips those "tough dog" tube troubles . . .

Ask any serviceman who owns one . . . or try one for just one day of servicing in your shop. You'll see for yourself how much time the LC3 can save *you*. Checks for leakage between all elements, whether caused by gas, grid emission or foreign particles. Also checks leakage on all capacitors with voltage applied—including electrolytics. Provides instant filament checks in "Fil-Check" position—no need for a second filament checker. One spare pre-heating socket and new roll chart prevent obsolescence. New charts provided—no charge. Leakage sensitivity; 100 megohms, control grid to all other elements; 50,000 ohms, heater to cathode. Size, 7x6x3½". Wt., 3 lbs. For 110-120 volts, 60 cycle AC. DEALER NET **28<sup>95</sup>**



**NOW . . . checks 172 tube types—more than any other checker of this type.**

**NEW . . . replaceable Roll Chart prevents obsolescence.**

Check Filaments of All Receiving Tubes and Picture Tubes



### FC4 FILAMENT CHECKER

For fast, easy checking of all tube filaments, without pulling chassis. Neon light goes out if tube filament is good. Also acts as continuity and voltage tester. Neon lamp glows when 115 v. AC is applied by cheater cord, providing a check on power to TV set. Size, 3½x4x1". **2<sup>95</sup>** With leads. DEALER NET . . . . .

Check 3- and 4-Prong Vibrators . . . Faster, Easier



### VB2 "VIBRA-DAPTOR"

Plugs into any tube checker; ideal for use with LC3 above. To check 6-v. vibrators, set for 6AX4 or 6SN7; for 12-v. vibrators, set for 12AX4 or 12SN7. Two No. 51 lamps indicate whether vibrator needs replacing. Instructions on front panel. Steel case. Size, 1½x1½x3". **2<sup>75</sup>** DEALER NET . . . . .

See your Parts Distributor NOW!

Turn page for other  
**SENCORE**  
Time Savers

# SENCORE

ADDISON 2, ILLINOIS

### SUPER MAGNET SUPER SAVING!

Buy this Little Giant magnet, most powerful made, a sensational bargain! The low price of \$1.95 is less than 50% of what you'd pay for this magnet. Experimenters, hobbyists will find hundreds of uses for this powerful 4 oz. Alnico permanent magnet. LIFTS 5 lbs. EASILY. Limited quantity. Order several today. Measures 1¾ x 1½". Item No. 86 **\$1.95**  
Special Bargain (Shp. Chgs. 10c)



### 250 POWER TELESCOPE LENS KIT

Make your own high powered 6 ft. telescope! Kit contains 2" diam., 75" focal length, ground and polished objective lens and necessary eye pieces. Magnifies 50x to 250x. Full instructions.

ITEM NO. 123  
**\$3.45**  
(Shp. Chgs. 10c)



### AMAZING BLACK LIGHT

250-watt ultra-violet light source. Makes fluorescent articles glow in the dark. Fits any lamp socket. For experimenting, entertaining, unusual lighting effects.



Shp. wt. 2 lbs. ITEM NO. 87 **\$3.45**  
(P. P. & Hdg. Chgs. 35c)



### WATHOUR METER

Leading makes—reconditioned. Ideal for trailer parks. 100-110 volts, 60 cycles. 2-wire A.C. 5 amp. Heavy metal case 8½" x 6¼" x 5". Easy to install. Shp. wt. 14 lbs.

ITEM NO. 33 **\$4.95**  
NOW ONLY  
(P.P. & Hdg. Chgs. \$1.25)

HUDSON SPECIALTIES CO., 160 W. 14th St. Dept. RE-2-60, New York 7, N.Y.  
I am enclosing full remittance for items circled below. (Be sure to include shipping charges.)  
87 33 86 123

Name ..... Please Print Clearly  
Address .....  
City ..... Zone.....State.....



Fill in coupon for a FREE One Year Subscription to OLSON RADIO'S Fantastic Bargain Packed Catalog — Unheard of LOW, LOW, WHOLESALE PRICES on Brand Name Speakers, Changers, Tubes, Tools, Hi-Fi's, Stereo Amps, Tuners and thousands of other Electronic Bargains.

NAME \_\_\_\_\_  
 ADDRESS \_\_\_\_\_  
 CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

If you have a friend interested in electronics send his name and address for a FREE subscription also.

**OLSON RADIO CORPORATION**  
 704 S. Forge St., Akron 8, Ohio




## HOW TO LOOK AT A SPEAKER BY wigo

PRONOUNCE IT WEEGO

Like this connoisseur, judge a speaker by its sound, not by its looks. With Wigo, you get sound performance...because Wigo puts the quality and value on the inside where you may not see it, but you sure can hear it! For literature, write...




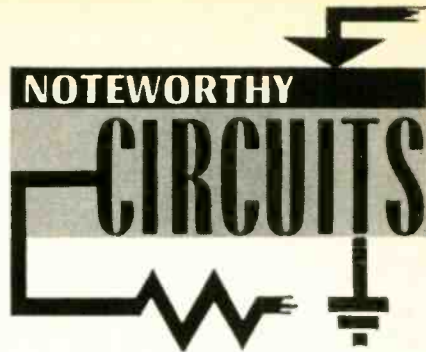
PRODUCTS OF DISTINCTION  
 202-4 East 19th St., N.Y.3, N.Y.



## NOTEWORTHY CIRCUITS
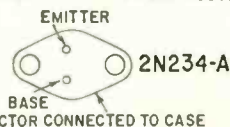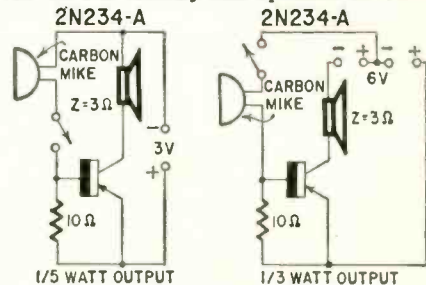
### TWO MEGAPHONES


These 1-transistor megaphones put out a surprising amount of power, considering the simplicity of their circuits. Mount the battery and speaker in a box



with the microphone on a long wire away from the box to prevent feedback and oscillation. A spring return push-to-talk switch will conserve battery life. —Bendix Semiconductors
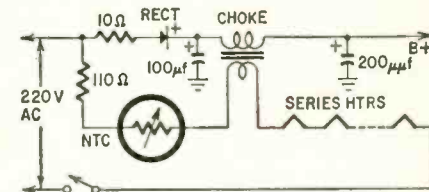
### HUM-CANCELING CIRCUIT

This arrangement is found in some German Union television receivers. The supply is an ac-dc type and fed from the standard German 220-volt line. A series heater string is used, and heater



current also flows through a small additional winding on the filter choke. Correctly connecting this winding introduces hum, opposite in phase to hum from the half-wave rectifier. Complete cancellation is impossible because of the nonsinusoidal rectified waveform, but the improvement is marked and economical to get.—A. V. J. Martin

### HEADPHONES FOR TV LISTENING

An interesting method of adding headphones to a TV set was shown in the January, 1960, issue of RADIO-ELECTRONICS, page 56. Since then, I have come up with a variation of this system that might be preferred by some readers.

This time crystal phones are connected to the output of the audio output tube through a blocking capacitor,

**LOOK**  
 no further . . . If you're searching for hi-fi savings. Write us your requirements now.  
 Key Electronics Company  
 120-A Liberty St., N.Y. 6, N.Y.  
 Cloverdale 8-4288

**FREE!** CATALOG OF HI-FI, RADIO, TV PARTS & ACCESSORIES — yours for the asking!  
**Vidaire** ELECTRONICS MFG. CORP.  
 44 CHURCH ST. • BALDWIN, N. Y.

# ELECTRONICS ENGINEERING-TECHNICIANS



AT HEALD'S YOU LEARN BY ACTUAL PRACTICE IN MODERN LABORATORIES . . . AND GET TOP PAY JOBS.

**HEALD'S ENGINEERING COLLEGE**  
 Established 1863  
 Van Ness at Post, RE  
 San Francisco, Calif.

Bachelor of Science Degree, 30 Months  
 Save Two Years' Time


- Radio-TV Technician including Color TV (12 Months)
- Electronics Technician (12 Months)
- Industrial Electronics Technician (12 Months)
- Electronics Engineering (B.S. Degree)
- Electrical Engineering (B.S. Degree)
- Mechanical Engineering (B.S. Degree)
- Civil Engineering (B.S. Degree)
- Architecture (B.S. Degree)

Heald College ranks FIRST West of the Mississippi in "Who's Who in America"


Approved for Veterans DAY AND EVENING CLASSES  
 Write for Catalog and Registration Application.  
 New Term Starting Soon.

Your Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_  
 State \_\_\_\_\_

NOTEWORTHY CIRCUITS (Continued)

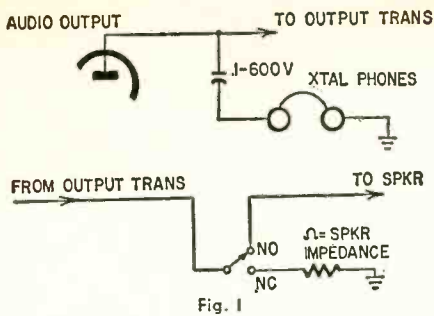

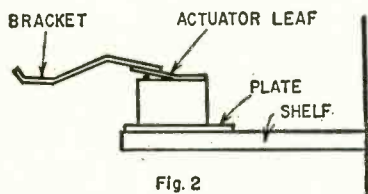0.1  $\mu$ f 600 volts (see Fig. 1). The phones are on all the time, only the speaker is switched on and off—lifting the earphones off their rack turns the speaker off; replacing them turns the speaker on once again. A spdt Micro-switch built into the earphone bracket handles the switching (see Fig. 2). You



can also use the switch arrangement shown in the January issue.

The main drawback to this system is in connecting the capacitor to the output tube's plate. A technician can wire it in directly, but the do-it-yourselfer might not care for the job. To avoid pulling the chassis, use a test adapter or make one yourself. Then simply connect the takeoff capacitor to the adapter. Now pull the output tube, insert the adapter, reinsert the tube and you're in business.—William B. Rasmussen

50 Years Ago  
In Gernsback Publications


HUGO GERNSBACK, Founder

Modern Electrics	1908
Wireless Association of America	1908
Electrical Experimenter	1913
Radio News	1919
Science & Invention	1920
Television	1927
Radio-Craft	1929
Short-Wave Craft	1930
Television News	1931

Some larger libraries still have copies of Modern Electrics on file for interested readers.

In February, 1910, Modern Electrics

- Dr. de Forest's New Radio Telephone. Portable Receiving Set, by Edward Featherstone.
- The New Rossi Detector, by A. C. Marlowe.
- Pocket Wireless, by the Brussels Correspondent.
- Electrolytic Detector Operates Relay. Duplex Wireless.
- A Tuning Transformer, by Richard H. Foster.
- Apartment Aerial Pole, by Robert D. Skelly.
- An Efficient Sending Condenser, by Maurice Friedman.
- Selective Detector Board, by R. Fulton Adams.
- Variable Sending Condenser, by Fred Wadsworth.

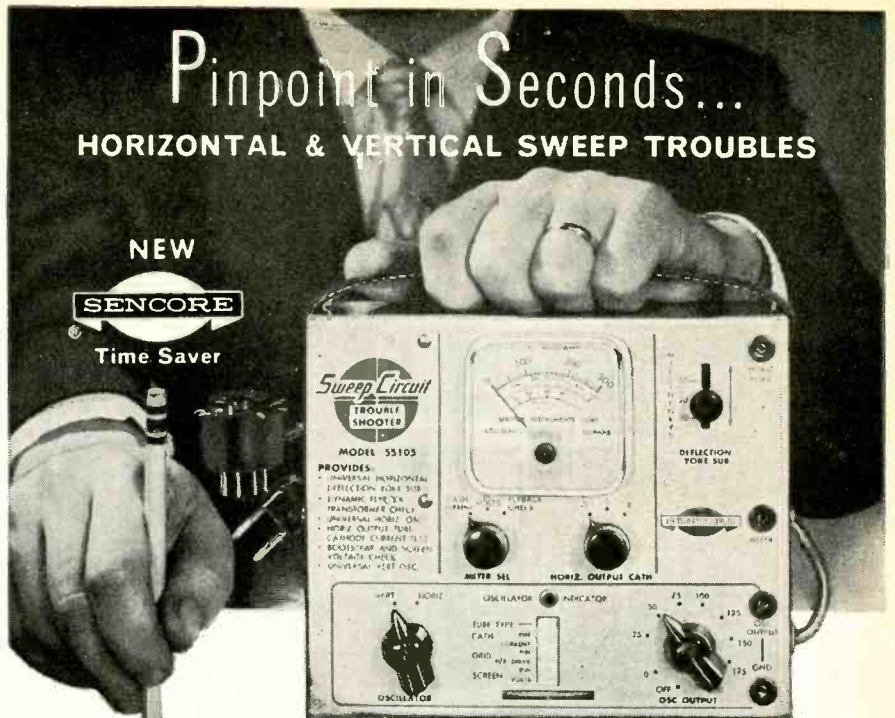

SENCORE SS105 SWEEP CIRCUIT TROUBLE SHOOTER

IT'S A... **UNIVERSAL HORIZONTAL OSCILLATOR.** For direct substitution. No wires to disconnect in most cases. Traces trouble right down to the defective component. Variable output from 0-200 volts, peak-to-peak.

**HORIZONTAL OUTPUT CATHODE CURRENT CHECKER.** A proven method that quickly checks the condition of the horizontal output tube and associated components. Adaptor socket prevents breaking wires. Easily replaceable Roll Chart gives all necessary pin, current and voltage data.

**UNIVERSAL DEFLECTION YOKE.** A new, simple way to determine yoke failure accurately—without removing yoke from picture tube. Merely disconnect one yoke lead and substitute. If high voltage (also bright vertical line) is restored, TV yoke is defective.

**DYNAMIC FLYBACK TRANSFORMER CHECKER.** Merely flip switch to "Flyback Check" and meter will indicate condition of flyback transformer, in degrees of horizontal deflection. Extremely sensitive and accurate; even shows up one shorted turn on flyback.

**VOLTMETER.** For testing bootstrap, screen and other voltages. Direct-reading voltmeter, 0-1000 volts.

**UNIVERSAL VERTICAL OSCILLATOR.** Checks oscillator, output transformer and yoke. Merely touch lead to component and check picture on screen.

Size, 7x6x3 1/2". Wt. 4 lbs.  
For 110-120 volts, 60 cycle AC.

DEALER NET 39<sup>50</sup>



HORIZ. OSC.	VERT. OSC.
HORIZ. O.P. STAGE	VERT. O.P. STAGE
HORIZ. FLYBACK XFORMER	VERT. O.P. XFORMER
HORIZ. DEFLEC. YOKE	VERT. DEFLEC. YOKE

See Your Parts Distributor NOW!

SENCORE

ADDISON 2, ILLINOIS

ADD TO YOUR INCOME

Learn at Home to Fix APPLIANCES

FREE SAMPLE LESSON

Tester Furnished—No Extra Charge. National Radio Institute trains you at home. Every service customer is worth more when you can fix his electrical appliances. Mail coupon for Lesson and Catalog.

National Radio Inst., Dept. F80, Washington 16, D.C.  
Please send me Electrical Appliance Sample Lesson and Catalog FREE (No salesman will call).  
Name.....Age.....  
Address.....  
City.....Zone.....State.....  
ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL

FOR CEREBRAL PALSY

JOB TRAINING

JOIN

the 53 Minute March  
United Cerebral Palsy



**COYNE offers**  
**LOW COST**  
**TELEVISION**  
Training in  
Spare Time **AT HOME**

The future is **YOURS** in  
**TELEVISION—RADIO**  
**COLOR TV!**

A fabulous field—good pay—fascinating work—a prosperous future! Good jobs, or independence in your own business!



Coyne brings you **MODERN—QUALITY** Television Home Training; training designed to meet Coyne standards. Includes **RADIO, UHF and COLOR TV**. No previous experience needed. Practical Job Guides to show you how to do actual servicing jobs—make money early in course. You pay only for your training, no costly “put together kits.”

Send coupon or write to address below for **FREE Book**

and full details including easy Payment Plan. No obligation, no salesman will call.



B. W. Cooke, Jr., President

Coyne — the Institution behind this training... the largest, oldest, best equipped residential school of its kind now in its new home pictured here... Founded 1899.

**COYNE**  
**ELECTRICAL SCHOOL**

1501 W. Congress Pkwy., Chicago, Dept. 20-H5  
Chartered as an Educational Institution  
Not For Profit

COYNE Television, Home Training Division  
Dept. 20-H5 —New Coyne Building  
1501 W. Congress Pkwy., Chicago 7, Ill.  
Send Free Book and details on how I can get Coyne Quality Television Home Training at low cost and easy terms.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

(It is understood no salesman will call)

**BUSINESS and**  
**PEOPLE**

Einar G. Carlson has been elected director and secretary of Hickok Electrical Instrument Co., Cleveland, Ohio. He is a partner in the law firm of Pennell, Carlson & Rees, the company's counsel. Henry Packard White, chief engineer and owner of H. P. White Laboratory, and E. G. Perkins, president of Supreme Electronics Corp., a Hickok subsidiary, were also named to the board of directors.



Thomas S. Knight Jr. (left), was named sales manager, General Electric receiving and TV picture tubes and hi-fi components in the Owensboro, Ky., plant. Since 1955 he has been distributor sales manager, serving franchised parts distributors in Florida and southern



Georgia. Charles J. Coward has been named general manager of the newly formed audio products section of General Electric, Housewares & Radio Receiver Div., Bridgeport, Conn. He had been serving as a consultant in the marketing services division before this appointment.

Howard D. Vann was appointed director of advertising and public relations for Globe Electronics, a recently acquired division of Textron Electronics, Inc. He was formerly director of community relations for Mutual and United of Omaha.



Warren E. Dalbke was appointed Midwest regional manager, equipment sales, for CBS Electronics, Danvers, Mass. He had been district manager, equipment sales.



Frank A. Comerci joined Audio Devices, Inc., New York, as senior project engineer in the Stamford, Conn., lab.

For the past 12 years he had been in charge of the Communications & Acoustics Section at the New York Naval Shipyard, Brooklyn, N. Y.

John Pacconi, Jr., is now associated with Glaser-Steers Corp., Newark, N. J., as customer service manager. He was previously with Lafayette Radio.



Ken Burton is the new sales manager for Duotone Co., Keyport, N. J. He has been active in the needle business for the past 6 years.



William N. Latshaw joined Heath Co., Benton Harbor, Mich., in the newly created position of advertising production manager, assisting Clifford M. Edwards, director of advertising. He comes to Heath from MacFarland, Aveyard Advertising Agency in Chicago.



Winegard Co., Burlington, Iowa, is sponsoring a “Paul Harvey News” program over 210 local ABC radio stations to promote its Color-Ceptor antennas. A special cooperative advertising program is available to dealers. Winegard's



advertising campaign in national magazines and its dealer sales aids will be continued. Paul Harvey (left), is shown in a recent tour of the Winegard plant with John R. Winegard, company president.

Ben Braun joined I. H. Manufacturing Co., New York, a subsidiary of Industrial Hardware Corp., as director of sales. He had been director of marketing for Telematic Co.

Ernest F. Tonsmeire was named controller of Raytheon Co., Receiving Tube Div., Quincy, Mass. He joined the company from Sylvania's Home Electronics Div., where he was controller of branch operations.

Edward Manville was appointed sales manager of the Communications Products Div. of Vocaline Co., Old Saybrook, Conn., and Ralph Routsong was named marketing manager.

Sylvania Electronic Tubes, division of



Sylvania Electric Products, Inc., was presented the NATESA Friends of Service Management plaque for the ninth consecutive year. Matthew D. Burns (third from left), Sylvania Electronic Tubes president, is shown accepting the award from Mac Metoyer, NATESA president, as other NATESA and Sylvania executives look on.

**Electro-Voice, Inc.,** Buchanan, Mich., has expanded its product line to include replacement needles, according to a statement by Larry LeKashman, vice president of marketing. The new replacement line will meet requirements for 97% of needles now in use.



**Haskel Blair** was elected president of University Loudspeakers, Inc., White Plains, N. Y., a subsidiary of Ling-Altec Electronics, Inc. He succeeds Sidney Levy who will continue as executive vice president and director of engineering. Blair has been active in electronics since 1923, most recently as a manufacturer's rep.

**EIA PRODUCTION & SALES**

(10 months)	1959	1958
TV picture-tube factory sales	7,864,893	6,814,166
Receiving-tube factory sales	358,477,000	333,258,000
TV set production	5,195,440	4,067,606
Radio production	12,722,970	8,904,772
FM radio production	430,763	235,647
TV retail sales	4,448,901	3,991,530
Radio retail sales	6,125,790*	5,241,629*

\*Excluding auto radios.

END



**SIGNAL TRACER**

Checks all stages from Antenna to Speaker or Picture Tube. Tests microphones, appliances, pickups, transformers, speakers, resistors, condensers, etc.

Model 202 (with AF Probe)...Net \$37.50

Model A Probe (RF Demodulator) .....Net 4.50

Model B Probe (RF Demodulator, Amplifier) .....Net 7.50



**VTVM KIT**

Easily assembled! Solves numerous problems. Sensitive voltage measurements with negligible circuit loading. Accurate AC voltage ranges for checking line voltages, amplifier power output, frequency response. Positive and negative DC voltage ranges. Checks resistance. Radio, TV servicing; maintenance of electronic equipment; many other uses. Net \$27.95.

**PRECISION ELECTRONICS, INC.**

9101-N King Ave., Franklin Park, Illinois

**UPPER STRATA STRATEGY!**

Friend of ours who always attends the sessions in the lecture halls, starts on the Fourth Floor with Production Items . . . and works his way down to Components on the First Floor. Says his feet tell him it's easier to come down than to go up! And he never misses a trick this way. Sounds like good engineering logic. Why don't you join him this year . . . and see if it doesn't work for you!

*Will Copp*  
Show Manager

**1959 IRE SHOW REGISTRATION: 60,052** . . . . . and we're set to handle even more of you in 1960 looking for **NEW IDEAS in RADIO-ELECTRONICS!**



Yes, the IRE NATIONAL CONVENTION and RADIO ENGINEERING SHOW is growing bigger every year, and drawing more people—950 exhibitors representing 80% of the productive capacity of your industry—60,052 registrants last year! Yet, it's one of the most well planned, well executed gatherings you'll ever see!

There's room to move around, room to see all you want to see because the IRE takes over all 4 floors of the giant Coliseum in New York City to show what your huge, fast moving radio-electronics industry is coming up with. First and second floors for components; third for instruments and systems; and fourth for production items. Follow the engineers to the Coliseum for NEW IDEAS IN RADIO-ELECTRONICS, 1960!

**The IRE NATIONAL CONVENTION**  
Waldorf-Astoria Hotel  
and **The RADIO ENGINEERING SHOW**  
Coliseum, New York City


**MARCH 21, 22, 23, 24**

**The Institute of Radio Engineers**  
1 East 79th St., New York 21, N. Y.

**KNIGHT**  
A PRODUCT OF ALLIED RADIO

the superior speaker buy  
in every price range

unconditionally guaranteed for one full year

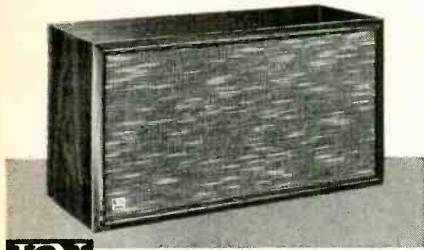


**KN 280**  
high-compliance  
2-way speaker system

\$59.95

\$5 down

Features: 8" long-excursion low-frequency driver; balanced, adjustable tweeter; quality cabinet, lustrously finished on four sides. 12½ x 24 x 10½". 28½ lbs.

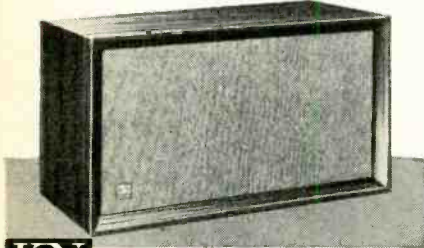


**KN 2000**  
high-compliance  
3-way speaker system

\$84.50

\$5 down

Features: 12" free-edge woofer; matched 8" mid-range driver; compression HF unit; sealed, acoustically damped system, finished on four sides. 13¾ x 26¾ x 12¾". 45 lbs.

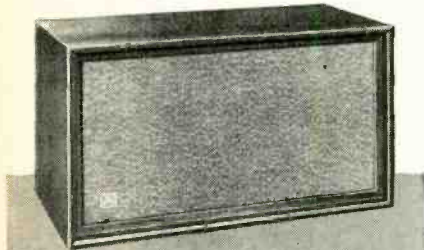

**KN 3000**  
high-compliance system with  
2 built-in electrostatic tweeters

\$129.50

\$5 down

Features: Electrostatic Arthur Janszen radiators; special high-compliance weighted-cone 12" woofer. Enclosure sealed, hand-finished on four sides. 14 x 26½ x 13". 50 lbs.

Moneyback Guarantee—  
15-Day Trial Privilege  
order from

**ALLIED RADIO**

ALLIED RADIO, Dept. 189-B  
100 N. Western Ave., Chicago 80, Ill.

Ship:  KN-280.  KN-2000.  KN-3000.

Mahog.  Oak.  Wal. \$\_\_\_\_\_encl.

SEND FREE 1960 CATALOG. I am interested in saving money on everything in Hi-Fi.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

FREE  
catalog



# new LITERATURE

Any or all of these catalogs, bulletins, or periodicals are available to you on request direct to the manufacturers, whose addresses are listed at the end of each item. Use your letter-head—do not use postcards. To facilitate identification, mention the issue and page of RADIO-ELECTRONICS on which the item appears. UNLESS OTHERWISE STATED, ALL ITEMS ARE GRATIS. ALL LITERATURE OFFERS ARE VOID AFTER SIX MONTHS.

**CONDUCTIVE MICROPAINTS** are explained and typical applications outlined in this 8-page brochure. Paints for shielding, resistance, long-wear protection are detailed and prices given.—Micro-Circuits Co., New Buffalo, Mich.

**REUSABLE BATTERIES** are illustrated in this 8-page book. It describes all electrical and physical characteristics, gives applications data and compares this line with ordinary batteries.—

Yardney Electric Corp., 40-50 Leonard St., New York, N. Y.

**NICKEL-CADMIUM** rechargeable batteries are examined thoroughly in 19 pages of this book, *Battery Engineering Bulletin No. 8*. Rectangular, cylindrical and button types are included. Discharge curves and methods of calculating capacity and charge rate are here too.—Union Carbide Consumer Products Co., 30 E. 42 St., New York 17, N. Y.

**TANTALUM CAPACITORS**—solid electrolytics *type SCM*—are listed in 14-page booklet complete enough for engineers, clear enough for beginners.—Texas Instruments Inc., Box 312, Dallas, Tex.

**SERVICING TRANSISTOR EQUIPMENT** is No. 6 in the *Tech Tips* series for technicians. It's a 4-page bulletin full of practical information.—CBS Electronics, 100 Endicott St., Danvers, Mass.

**TRANSISTOR CHOPPERS** are the subject of the September '59 issue of *TI Application Notes*. The 4-page bulletin discusses design using equivalent circuits.—Texas Instruments, Inc., Box 312, Dallas, Tex.

**REGULATED SUPPLIES**, frequency changers, inverters, electrostatic generators are briefly described in a 6-page short-form catalog.—Sorensen & Co., Inc., Richards Ave., S. Norwalk, Conn.

**SOLDERING IRONS** are described and tip construction is explained. Complete

Choose ...

**XCELITE**

Hand Tools ... the Professionals do!

You need the BEST TOOLS to do the BEST JOB . . .




Your Radio, TV and Electronic  
Parts Distributor has them!

Check the "SEIZER"

Provides the necessary  
"third hand" in so many  
tricky situations!

No. 42H

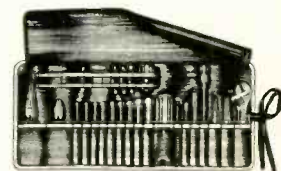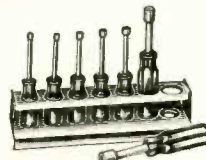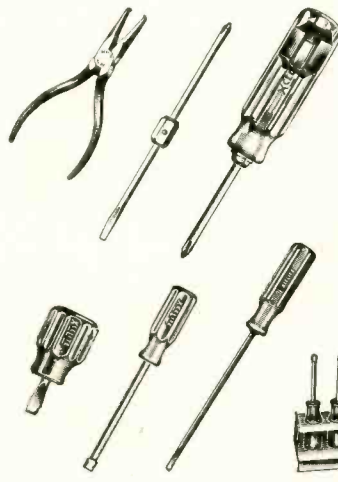- Clamps on as a Heat Sink.
- Holds wires etc. while soldering.
- Holds dial cords when stringing them.
- Retrieves small items from awkward places.
- Out-reaches and out-holds needle nose pliers.



Select from the Complete Line of Quality Tools and Handy Kits . . .

**XCELITE, INCORPORATED**  
ORCHARD PARK, NEW YORK  
Canada: Charles W. Pointon, Ltd., Toronto

**XCELITE**  
Quality Hand Tools  
PREFERRED BY THE EXPERTS

line of irons are shown. *Publication GED-3553*.—General Electric distributors, or General Electric Co., Schenectady 5, N. Y.

**COIL FORM CHART** for wall display, 21 x 27 inches, shows ceramic and phenolic coil forms, dimensions, terminal arrangements and other information useful in designing coils.—*Cambridge Thermionic Corp.*, 445 Concord Ave., Cambridge 38, Mass.

**SPECIAL KNOBS** for instruments and receivers are shown in six styles, five sizes. Dimensions are also given in 4-page *Bulletin 59-3*.—*National Radio Co.*, Melrose, Mass.

**TIME-DELAY RELAYS** including transistor timing module are described in accuracies from 10% to 0.01% in *Engineering Bulletin 5903*, 8 pages.—*Tempo Instrument Inc.*, Box 338, Hicksville, N. Y.

**CHART RECORDERS** are shown in *Bulletin GEA-6933*, 12 pages. Dimensions, recording speed, accuracies, are included.—*General Electric Co.*, Schenectady 5, N. Y.

**HOOK-ON AMMETERS**, pocket size for testing ac voltages are described with specifications and construction details, ranges, applications and accuracy in 4-page bulletin *GEA-6292C*.—*General Electric Co.*, Schenectady 5, N. Y.

**DIELECTRIC MATERIALS** at microwave frequencies are listed with temperature

ratings, dielectric constants, dissipation factors, weight, on large (22 x 37 inches) wall chart.—*Emerson & Cumming, Inc.*, Canton, Mass.

**PULSE TRANSFORMERS**, their design and use, are discussed with equivalent circuits, applications and typical design and manufacturing considerations. 18 pages.—*PCA Electronics, Inc.*, 16799 Schoenborn St., Sepulveda, Calif.

**COMMUNICATIONS ANTENNAS** are shown and described electrically and mechanically in 45 pages. Base station and vehicular antennas are included along with mounting accessories. *Catalog No. 59*.—*Communication Products Co., Inc.*, Marlboro, N. J. END



"Wife comes in and snoops around sometimes!"

**DON'T BLOW YOUR TOP!**

A happier solution is **EMC TEST EQUIPMENT** . . . finest precision instruments at the lowest possible prices!

**Model 102 Voltmeter**  
Features a 3 1/2" x 2" accurate—800 microamperes D'Arsonval-type plastic front meter with 3 AC current ranges, and the same zero adjustment for both resistance ranges. Specifications . . . AC Voltage—5 Ranges: 0 to 12-120-600-1200-3000 volts. DC Voltage—5 Ranges: 0 to 6-60-300-600-3000 volts. AC Current—3 Ranges: 0 to 30-150-600 ma. DC Current—4 Ranges: 0 to 6-30-130 ma. 0 to 1.2 amps. Two Resistance Ranges: 0 to 1000 ohms, 0 to 1 megohms. Model 102, Wt. 1 lb. 5 oz. Size: 3 3/4" x 6 3/4" x 2". \$14.90; Kit, \$12.50.

**Model 204 Tube-Battery-Ohm Capacity Tester**  
Emission tube tester. Completely flexible switching arrangement. Checks batteries under rated load on "reject-good" scale. Checks condenser leakage to 1 meg. Checks resistance up to 4 megs. Checks capacity from .01 to 1 mfd. Model 204P, illustrated, \$55.90. Model CRA, Cathode ray tube adaptor, \$4.50.

**Model 700 RF-AF Crystal Marker TV Bar-Generator**  
Complete coverage from 18 cycles to 108 megacycles on fundamentals. Bar generator for TV adjustment with a variable number of bars available for horizontal or vertical alignment. Square wave generator to 20 kilocycles. Wien Bridge AF oscillator with sine wave output from 18 cycles to 300 kilocycles. Crystal marker and amplitude control. Individually tuned coils. Constant RF output impedance. Stepped RF attenuator. Variable percentage of modulation. Model 700 \$55.90


**Model 205 Tube Tester**  
Uses standard emission test. Tests all tubes including Noval and subminiatures. Completely flexible switching arrangement. Checks for shorts, leakages and opens. Model 205P, Hand rubbed oak carrying case, \$47.50 (illustrated); Kit, \$36.20. Model CRA, Cathode ray tube adaptor, \$4.50.

**Model 104 Voltmeter**  
Features a 4 1/2" x 50 microampere meter, with 3 AC current ranges and 3 resistance ranges to 20 megohms. Specifications . . . DC Voltage: 5 ranges (20,000 ohms per volt). 0 to 6-60-300-600-3000 volts. AC Voltage: 5 ranges (1,000 ohms per volt). 0 to 6-60-300-600-3000 volts. DC Current—3 Ranges: 0 to 6-60-600 ma. AC Current—3 Ranges: 0 to 30-300 ma. 0 to 3 amps. 3 Resistance Ranges: 0 to 20K, 0 to 200K, 0 to 20 megs. 5 DB Ranges: —4 to +67 DB. Model 104, with carrying strap; Wt. 2 lbs. 5 oz. Size: 5 1/4" x 6 3/4" x 2 1/4". \$26.95; Kit, \$19.95. Model HVT, 30,000 volt probe for Model 104, \$7.95.

Yes, tell me more, send me FREE—a detailed catalog of the complete EMC line. RE-26

NAME \_\_\_\_\_  
STREET \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_

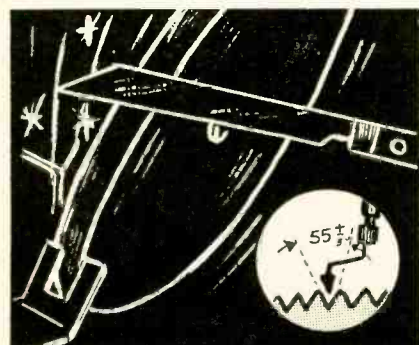**EMC** Electronic Measurements Corp.  
625 B'way, New York 12, N. Y.  
Ex. Dept. 431 Greenwich St., New York 13, N. Y.



**AYE, THERE'S THE RUB . . .**

It's become a classic . . . what hand polishing of the diamond radius in the Duotone Needle can do for hi-fi and stereo. Smooth to ±.0001 tolerance whereas ordinary needles produced by automation seldom do better than ±.0007. Often the latter have no polish at all, leading to excessive record wear. Aye, but there's the rub! Other classic features in the Duotone Diamond Needle: 1. A guaranteed whole diamond (not a welded chip that can break off). 2. 55° (±5) for the stylus angle every time (others varying to 85° often skip in the groove). 3. Quality controlled by 500 power microscopic inspection.

**DUOTONE**  
DIAMOND NEEDLE

Keyport, New Jersey  
In Canada: Chas. W. Pointon, Ltd., Toronto

**THANK YOU!**  
... for all our friends who entered our "Chance of a Lifetime" Contest, we extend our thanks and sincere appreciation for your wonderful entries and fine patronage of our products.



Victor J. Goss I. G. Tracy

**WINNING SLOGAN:**  
"Workman Outstanding Repair parts Keep Man-hours At New Low"

Submitted by Mr. I. G. Tracy, I. G. Tracy Television Service, Tulsa, Oklahoma. First Prize. New Volkswagen equipped with Jackson Test Equipment.

S&S Radio Supply, Tulsa, Oklahoma (distributor for Tracy Television Service). Second Prize. New Volkswagen.

Victor J. Goss, Counterman at S&S Radio Supply whose name appeared on Mr. Tracy's entry: Third Prize, \$250 U. S. Savings Bond.

**WORKMAN TV PRODUCTS, Inc.**  
Sarasota, Florida

# new BOOKS

**PHYSICS OF ELECTRICITY AND MAGNETISM** by William Taussig Scott. John Wiley & Sons, Inc., 440 Fourth Ave., N. Y. 16, N. Y. 5 3/4 x 9 in. 635 pp. \$8.75.

This one is for upper-class students and graduates. It discusses the very latest in mathematical theories, using vectors and calculus. It is slanted towards the physicist.

Basic concepts are studied first: charge, field, potential. Then follow electric currents, magnetism, radiation. Topics include batteries, magnetic material, circuits, meters, waveguides.

**ELECTRONIC COMPONENTS HANDBOOK (VOL. 3)**, edited by Keith Henny, Craig Walsh and Harry Mileaf. McGraw-Hill Book Co., 330 W. 42 St., New York, N. Y. 8 1/2 x 11 in. 180 pp. \$10.

Vol. 3 completes the series prepared to help designers of military and commercial equipment in selecting components for maximum reliability. It provides data on transformers, inductors, magnetic amplifiers, saturable reactors, connectors, wire and cables, terminals and terminal boards, tube shields and hardware. The effects of altitude, humidity, shock, vibration and other unfavorable conditions are discussed.

**TRANSISTOR CIRCUITS**, by K. W. Cattermole. MacMillan Co., 60 Fifth Ave., N. Y. 11, N. Y. 5 1/2 x 8 1/2 in. 442 pp. \$14.

This book is for readers familiar with tube circuits and math. It begins with the theory and manufacture of semiconductors. Amplifiers, binary circuits, wave generators, modulators, etc. are analyzed, and equations derived for them. Mathematical design data appears in several appendices.

**R-L-C COMPONENTS HANDBOOK**, by David Mark. John F. Rider, Publisher, Inc., 116 W. 14 St., N. Y. 11, N. Y. 5 1/2 x 8 1/2 in. 146 pp. \$3.50.

Some technicians believe that a capacitor is just a capacitor. But there are many different kinds, and for any given application one kind is best. The same holds for resistors and inductors. This book describes the characteristics and applications of R, L and C components, including thermistors and transformers. Temperature effects, tolerance and color codes are discussed. This book will help you make the correct replacement in every circuit.—IQ

**ELECTRICAL ENGINEERING, Second Edition**, by William H. Erickson and Nelson H. Bryant. John Wiley & Sons, Inc., 440 Fourth Ave., New York 16, N.Y. 5 3/4 x 9 in. 614 pp. \$8.

These authors have written about circuits, electronics and machines especially for engineering students majoring in subjects other than electricity. They discuss and analyze transformers, motors, control equipment, tubes and

(Continued on page 158)



## THE G/L HI-FI BOOK CLUB HELPS YOU UNDERSTAND HI-FI BETTER... ENJOY IT MORE!



Here's a complete book club just for the hi-fi fan. Whether you're selecting your first system — or have already been through years of juggling amplifiers, speakers, enclosures and

other components in your never-ending search for the ultimate, this club can help you get more out of your hi-fi system. The Library tells you everything from how to select a system, choose components, get rid of hum, improve response — even how to get a system to look like it belongs in a living room. Books range from the remarkable non-technical guide *Hi-Fi Made Easy* to H. A. Hartley's *Audio Design Handbook* for the advanced audiophile. Each book is beautifully printed — handsomely bound — a joy to behold in any living room or library. They retail for \$5.00 each — but to G/L Club Members only they're just \$3.75. And you RISK NO MONEY. You receive each book on approval. You keep only the books you like — pay only for those you keep. Join this remarkable club today — see how much more you'll enjoy hi-fi. Start at the beginning with *Hi-Fi Made Easy* — in no time at all you'll be the recognized hi-fi expert in your circle.

### HOW TO JOIN THE G/L AUDIO-HI FI BOOK CLUB

- Select one book from those listed on the coupon.
- SEND NO MONEY — we will send you the book on approval and we'll pay the postage. If you like it send your remittance for the special club price of \$3.75.
- New books are released about every three months. You receive these automatically on the same no-risk plan.
- You may cancel any time after you have accepted four books — no time limit.

**JOIN NOW — Select the book you want from these books already published**  
**HI-FI MADE EASY** — By Norman H. Crowhurst. A hi-fi book for the "man in the street". A non-technical classic by one of the giants of high fidelity. He tells you what hi-fi is, what each component does. Weighs package vs. component systems, explains systems, circuits, stereo — all without a single schematic, mathematical formula or word of engineering jargon. Illustrated with light-hearted but instructive cartoons. A treasury of hi-fi information and a delight to read.

**STEREO—HOW IT WORKS** — By Herman Burstein. All about stereo — what it is, what it can do, what it can't do. Warns about pitfalls. Covers everything — from fundamentals to installation and advanced techniques and applications.  
**H. A. HARTLEY'S AUDIO DESIGN HANDBOOK** — This expert explains design principles so the non-engineering hi-fi fan can design his own equipment.

**AUDIO MEASUREMENTS** — By Norman H. Crowhurst. Covers audio measurements from service shop to laboratory level. Shows how to make tests, what instruments to use, how to interpret results.  
**DESIGNING AND BUILDING HI-FI FURNITURE** — By Jeff Markell. How to have a hi-fi system that looks as good as it sounds. Covers everything from what woods to use to room arrangement.

**ELEMENTS OF TAPE RECORDER CIRCUITS** — By Herman Burstein and Henry C. Pollak. Answers all your questions about the electronic aspects of a tape recorder. What to look for when you buy.  
**MAINTAINING HI-FI EQUIPMENT** — By Joseph Marshall. Covers the specialized techniques necessary to repair hi-fi equipment. Includes acoustical, mechanical and electronic faults.

**UNDERSTANDING HI-FI CIRCUITS** — By Norman H. Crowhurst. Now have the system best suited to your tastes — and budget. Tells you which phase inverter is best, weighs fixed vs. self bias, triode vs. pentode, answers hundreds of other questions.  
**BASIC AUDIO COURSE** — By Donald C. Hoefler. Explains everything about audio from the theory of sound to disc and tape recording techniques.

### MAIL THIS COUPON NOW

Gernsback Library, Inc., Dept. 208  
 154 West 14th Street, New York 11, N. Y.

Enroll me in the G/L  
 AUDIO-HI FI BOOK CLUB.

Send me the book checked on approval.  
 (Please check one only)

- Hi-Fi Made Easy
- Stereo—How it Works
- Designing and Building Hi-Fi Furniture
- Audio Measurements
- Audio Design Handbook
- Elements of Tape Recorder Circuits
- Maintaining Hi-Fi Equipment
- Understanding Hi-Fi Circuits
- Basic Audio Course

Name.....  
 Street.....  
 City..... Zone..... State.....

please print



# SCHOOL DIRECTORY

## ELECTRONICS ENGINEERING DEGREE IN 27 MONTHS

Prepare for unlimited opportunities in electronics!

U.S. Engineering degree (27 mo.): Mathematics, Electrical Engineering, TV, advanced Radio Theory and Design. U.E. (36 mo.): Aeronautical, Chemical, Civil, Electrical, Mechanical, Metallurgical Eng. B.S. (36 mo.): Math., Chem., Physics. Also preparatory courses. Earn board. G.I. approved. 20 bldgs., dorms, gym. Enter March, June, Sept., Dec. Catalog. Keeping pace with progress.

**INDIANA TECHNICAL COLLEGE**  
1520 E. Washington Boulevard, Fort Wayne 2, Indiana



**CODE SENDING RECEIVING SPEED**

Be a "key" man. Learn how to send and receive messages in International Morse code. Communicate with operators around the globe. Learn at home quickly through famous Candler System. Used by best operators. Qualify for Amateur or Commercial License. Write for FREE BOOK.

**CANDLER SYSTEM CO.**  
Dept. 3-B, Box 9226, Denver 20, Colo. USA

### ENGINEERING COURSES

E.E.  
Option Electronics or Power Mechanical, Civil & Physics Also in Liberal Arts & Business Administration presented through

**HOME STUDY**  
Resident Classes Also Available If Desired

**PACIFIC INTERNATIONAL COLLEGE OF ARTS & SCIENCES**  
Primarily a correspondence school

5719-N Santa Monica Blvd. Hollywood 38, Calif.

### GET INTO ELECTRONICS

V.T.I. training leads to success as technicians, field engineers, specialists in communications, guided missiles, computers, radar and automation. Basic and advanced courses in theory and laboratory. Assoc. degree in electronics in 28 mos. B.S. in electronic engineering obtainable. ECPD accredited. G.I. approved. Graduates in all branches of electronics with major companies. Start February, September. Dorms, campus. High School graduate or equivalent. Catalog.

**VALPARAISO TECHNICAL INSTITUTE**  
Dept. C Valparaiso, Indiana



### FREE! ELECTRONICS BOOKS

I.C.S. will send you FREE 3 valuable booklets that tell you where the big-pay jobs are in Radio-TV Electronics... who are the industry's most-wanted men... how you can "cash-in" in a big way on your future. There's no obligation. Don't delay. Mail the coupon now!

**INTERNATIONAL CORRESPONDENCE SCHOOLS**  
Dept. 40683A, Scranton 15, Penna.

Please send free success book, sample lesson, and catalog checked.

General Electronics  Radio-TV Serv'g  Practical Electrician  
 Industrial Electronics  Sound Equipmt. Serv'g  Profess'l Eng. (Elec.)  
 Radio-TV Eng'g  Electrical Eng'g's  Electrical Drafting  
 Electronic Servicing  Electrical Tech.  Other \_\_\_\_\_

Name \_\_\_\_\_ Age \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_

## ELECTRONICS

**PREPARE FOR A GOOD JOB!**  
**BROADCAST ENGINEER**  
**RADIO SERVICING AUTOMATION**

**TELEVISION SERVICING**  
**BLACK & WHITE—COLOR**

APPROVED FOR VETERANS AND SURVIVORS OF VETERANS BUILDING AIR CONDITIONED SEND FOR FREE LITERATURE

**BALTIMORE TECHNICAL INSTITUTE**  
1425 EUTAW PLACE, BALTIMORE 17, MD.

### engineering degree in 27 months

Grasp your chance for a better life. Rapid advancement. Better income. **BACHELOR OF SCIENCE DEGREE IN 27 MONTHS** in Elect. (Electronics or Power major), Mech., Civil, Aero., Chem., Engineering. **IN 36 MONTHS** in Business Administration (General Business, Acctg., Motor Transport Mgt. majors). Small classes. More professional class hours. Well-equipped labs. Campus. Dorms. Modest costs. Year-round operation. Founded 1884. Enter Mar., June, Sept., Jan. Write J. G. McCarthy, Director of Admissions, for Catalog and "Your Career in Engineering and Commerce" Book.

**TRI-STATE COLLEGE** 2420 College Ave. Angola, Indiana

## ENGINEERING HOME STUDY COURSES

Courses written by world authorities in all branches of engineering and science and proved successful by thousands of our graduates. One hour each day in your spare time will start you off to higher pay, security and prestige. Personalized instruction methods ensure rapid progress. Fill in the coupon and indicate the course of interest. We will send you a complete outline of the course and a booklet describing the Institute and our advanced teaching methods.

RADIO  
ELECTRONICS  
TELEVISION  
CIRCUIT  
MATHEMATICS  
ELECTRICAL ENG.  
TELEPHONY  
CIVIL ENG.  
SURVEYING  
ARCHITECTURE  
FORESTRY  
MINING  
STRUCTURAL  
MECHANICAL ENG.  
INDUSTRIAL ENG.  
& MANAGEMENT  
REFRIGERATION  
DRAFTING  
PLASTICS  
AERONAUTICAL  
ENG.  
HIGH SCHOOL  
CHEMICAL  
MATHEMATICS  
JOURNALISM  
ACCOUNTING

**MAIL THIS COUPON TODAY**


CANADIAN INSTITUTE OF SCIENCE & TECHNOLOGY LIMITED  
730 Century Bldg., 412, 5th St. N.W., Wash., D.C.

NAME.....  
ADDRESS.....  
CITY.....STATE.....

COURSE OF INTEREST.....  
Canadians: Send to C.I.S.T., 740, Garden Bldg., 263 Adelaide St. West, Toronto, Ontario.

**C. I. S. T.**

## FREE CAREER BOOKLET

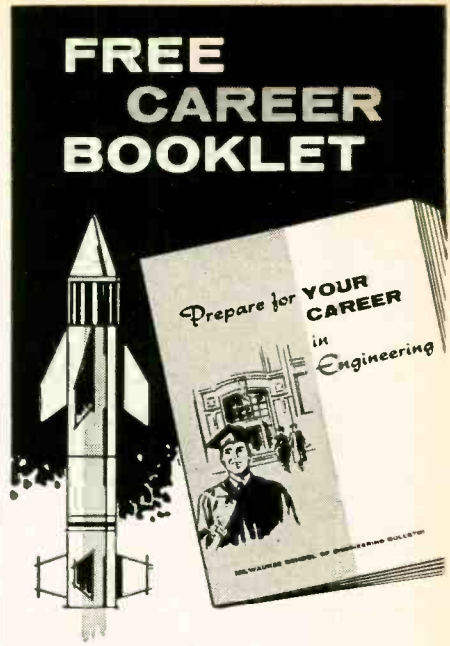

to guide you to a successful future in

## ELECTRONICS RADIO-TV COMPUTERS ELECTRICAL ENGINEERING

This interesting pictorial booklet tells you how you can prepare for a dynamic career as an Electrical Engineer or Engineering Technician in many exciting, growing fields:

**MISSILES • RADAR • RESEARCH**  
**ELECTRICAL POWER • ROCKETRY**  
**AUTOMATION • AVIONICS**  
**SALES • DEVELOPMENT**

Get all the facts about job opportunities, length of study, courses offered, degrees you can earn, scholarships, part-time work — as well as pictures of the Milwaukee School of Engineering's educational and recreational facilities. No obligation — it's yours free.

**MILWAUKEE SCHOOL OF ENGINEERING**

**MAIL COUPON TODAY!**

**MILWAUKEE SCHOOL OF ENGINEERING**  
Dept. RE 260, 1025 N. Milwaukee St.  
Milwaukee, Wisconsin MS-113


Please send FREE "Your Career" booklet I'm interested in  Electronics  Radio-TV  Computers  Electrical Engineering  Mechanical Engineering (PLEASE PRINT)

Name..... Age.....  
Address.....  
City..... Zone..... State.....  
 I'm eligible for veterans education benefits.  
Discharge date.....

# Lafayette Superior Quality HI-FI KITS!

The *FINEST* . . . through research . . . engineered by LAFAYETTE!

## KT-250

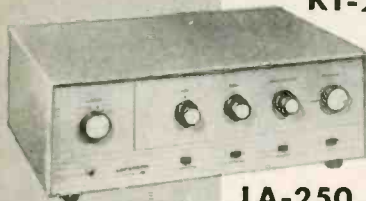

IN KIT  
FORM

64.50

LA-250 89.50  
COMPLETELY WIRED


## 50 WATT INTEGRATED STEREO AMPLIFIER

- RESPONSE 17-21,000 CPS  $\pm$  1 DB (at normal listening level)
- UNIQUE "BLEND" CONTROL
- PREMIUM EL86 OUTPUT TUBES
- 50 WATTS MONAURAL—25 WATTS EACH STEREO CHANNEL
- CLUTCH-OPERATED VOLUME CONTROL
- SEPARATE BASS & TREBLE CONTROLS

A completely new stereo high fidelity amplifier with a high quality of reproduction, remarkable versatility and new distinctive styling. Full range of controls include a unique "blend" control for continuously variable channel separation—from full monaural to full stereo, 4-position Selector, Mode, Loudness and Phasing switches plus outputs for 4, 8 or 16 ohm speakers. Harmonic distortion less than 0.25%, IM distortion less than 1%. Hum and Noise 74 db below full output. Assembly is simple—no special skills or tools required. Complete with deluxe cabinet and legs, all parts, tubes and detailed instruction manual. Shpg. wt., 26 lbs.

KT-250 WX Stereo Amplifier Kit ..... 5.00 Down ..... Net 64.50  
LA-250 WX Stereo Amplifier, wired & tested ..... 5.00 Down ..... Net 89.50

## KT-600

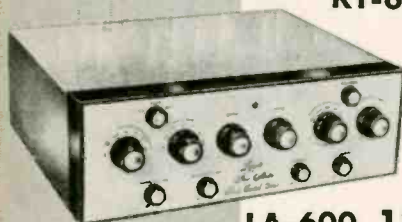

IN KIT  
FORM

79.50

LA-600 134.50  
COMPLETELY WIRED


## PROFESSIONAL STEREO CONTROL CENTER

- RESPONSE 5-40,000 CPS  $\pm$  1 DB
- UNIQUE STEREO & MONAURAL CONTROL FEATURES
- PRECISE "NULL" BALANCING SYSTEM
- CONCENTRIC INPUT LEVEL CONTROLS

A truly professional stereo preamplifier and master audio control center—solves every stereo/monaural control problem. Features unique Bridge Control for variable cross-channel feed for elimination of exaggerated channel separation effects—plus controlled 3rd channel output. Has all-concentric controls—including clutch-operated Volume Balance control. Provides complete and advanced facilities for accepting, controlling and providing undistorted gain for any and all program sources. Sensitivity 2.2 mv for 1 volt out (low level inputs). Dual low impedance "plate follower" outputs 1500 ohms. Response 5-40,000 cps  $\pm$  1 db. Less than .03% IM distortion. Less than .1% harmonic distortion. Hum and noise 80 db below 2 volts (high level inputs). Uses 7 new 7025 low-noise dual triodes. Size: 14" x 4 1/2" x 10 3/8". Shpg. wt., 16 lbs. Complete with all parts, tubes, deluxe cabinet and detailed instruction manual.

KT-600 WX Stereo Preamplifier Kit ..... 5.00 Down ..... Net 79.50  
LA-600 WX Stereo Preamplifier, wired and tested ..... 5.00 Down ..... Net 134.50

## KT-310

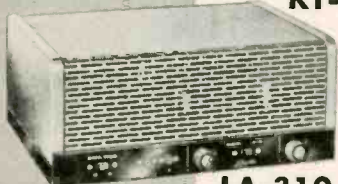

IN KIT  
FORM

47.50

LA-310 72.50  
COMPLETELY WIRED

## STEREO/MONAURAL POWER AMPLIFIER KIT

- 36 WATT STEREO AMPLIFIER—18 WATTS EACH CHANNEL
- EMPLOYS 4 PREMIUM-TYPE 7189 TUBES
- 2 PRINTED CIRCUIT BOARDS FOR SIMPLIFIED WIRING
- RESPONSE BETTER THAN 35-30,000 CPS  $\pm$  1/2 DB AT 18 WATTS
- LESS THAN 1% HARMONIC OR IM DISTORTION

A superb basic stereo amplifier in easy-to-build kit form. Unit may be used with a stereo preamplifier to provide two 18 watt stereo channels or, at the flick of a switch, as a fine 36 watt monaural amplifier. Controls include 2 input volume controls, Channel Reverse switch and Monaural-Stereo switch. Dual outputs for 4, 8, 16 or 32 ohm speakers. Input sensitivity .45 volts per channel for full output. Tubes are 2-6AN8, 4-7189, GZ-34 rectifier. Size 10-9/16" d x 5 1/4" h x 13 1/4" w. Complete kit with cage, all parts, tubes and detailed instruction manual. Shpg. wt., 22 lbs.

KT-310 WX Stereo Power Amplifier Kit ..... 2.00 Down ..... Net 47.50  
LA-310 WX Stereo Power Amplifier, wired and tested ..... 5.00 Down ..... Net 72.50

## KT-500



IN KIT  
FORM

74.50

LT-50 124.50  
COMPLETELY WIRED

## FM-AM STEREO TUNER KIT

- 11 Tubes (4 dual-purpose) + Tuning Eye + Selenium rectifier provide 17 tube performance
- Multiplex Output for new Stereo FM
- Armstrong Circuit with Dual Limiters and Foster-Seeley Discriminator
- Extreme Sensitivity and Wide Frequency Response

A precision engineered, highly stable tuner—perfect for lifelike stereo FM-AM broadcast reception, FM reception and/or AM reception. Features separate tuning and volume controls for AM and FM. Magic eye on AM and FM, plus automatic frequency control on FM for accurate tuning—stations are "locked" in. Other deluxe features include cathode follower outputs and 5-position Function Selector. Efficient, broadband circuitry on AM with built-in antenna. FM section features include 2 microvolts sensitivity for 30 db quieting, frequency response 20-20,000 cps  $\pm$  1/2 db and full 200 KC bandwidth. Two printed circuit boards make wiring simple—even for such a complex unit. Complete kit includes all parts, deluxe cabinet and detailed instruction manual. Size is 13 3/4" W x 10 3/4" D x 4 1/2" H. Shpg. wt., 22 lbs.

KT-500 WX FM-AM Stereo Tuner Kit ..... 5.00 Down ..... Net 74.50  
LT-50 WX Same as above, wired & tested ..... 5.00 Down ..... Net 124.50

**NEW!**



IN KIT  
FORM

52.50

KT-236 52.50

## LAFAYETTE 36-WATT INTEGRATED STEREO AMPLIFIER KIT

- 36-WATTS MONAURALLY—18 WATTS PER CHANNEL
- FREQUENCY RESPONSE 15-30,000 CPS  $\pm$  1 DB
- UNIQUE "BLEND" CONTROL
- CONCENTRIC CLUTCH-OPERATED VOLUME CONTROL
- DUAL CONCENTRIC BASS AND TREBLE CONTROLS
- 4-EL84 TUBES IN PUSH PULL

This exciting new amplifier kit combines dual preamplifiers and dual 18 watt power amplifiers on one compact chassis. Instant selection from monophonic to stereophonic is provided by the turn of a switch. An amazing new "Blend" control gives continuously variable channel separation from full monophonic to full stereo. The concentric clutch-operated volume control offers independent or simultaneous level adjustments of both channels. Dual concentric bass and treble controls furnish 4 independent tonal adjustments. Harmonic distortion less than 0.15% at normal listening level. I.M. distortion is less than .3%. Hum and noise 70 db below rated output. Complete with cage, legs and detailed instructions. Shpg. Wt., 24 lbs.

KT 236 WX Stereo Amplifier Kit ..... 5.00 Down ..... Net 52.50

**LAFAYETTE RADIO**

165-08 LIBERTY AVE., JAMAICA 33, N. Y.  
AXtrel 1-7000

NEW YORK, N. Y.  
100 6th Ave.  
Worth 6-5300

BOSTON, MASS.  
110 Federal St.  
Hubbard 2-7850

BRONX, N. Y.  
542 E. Fordham Rd.  
Fordham 7-8813

NEWARK, N. J.  
24 Central Ave.  
Market 2-1661

PLAINFIELD, N. J.  
139 W. 2nd St.  
Plainfield 6-4718

# NEW! Lafayette 50 Watt Complete Stereo Phono System



## COMPONENTS

LAFAYETTE LA-250 50-WATT STEREO AMPLIFIER	89.50
GARRARD RC121/11 STEREO CHANGER	41.65
NEW GE VR-22 (.7 MIL) DIAMOND STEREO CARTRIDGE	24.45
LAFAYETTE PK-111 WOOD CHANGER BASE	3.95
2-LAFAYETTE SK-58 FAMOUS FREE EDGE	
12" COAXIAL SPEAKERS at 29.50	59.00
Regular Catalog Price	<del>218.55</del>

## COMPLETE STEREO SYSTEM

# 174.50

YOUR GUARANTEED BEST STEREO SYSTEM BUY!

YOU SAVE 44.05


This superb system will add a new dimension in living to your home with all the excitement and realism of a live concert. The new Lafayette LA-250, 50-watt stereo amplifier (25 watts each channel) forms the heart of this outstanding stereo hi-fi phonograph music system—the features, versatility and advanced circuitry of this unit are second to none. Also included is the famous Garrard RC121/11 intermix 4-speed automatic record changer with full manual or automatic operation supplied with your choice of stereo cartridges—the new GE VR-22 (.7 Mil) diamond stereo cartridge, Pickering 371-7D (.7 Mil) diamond stereo cartridge, Shure M7D (.7 Mil) diamond stereo cartridge or the new Electro-Voice 31 MD7 (.7 Mil) diamond stereo cartridge. Supplied with the Lafayette wood base cut for the RC121 in your choice of finishes. These outstanding components are coupled

with the 2 famous free edge Lafayette SK-58 12" Coaxial speakers with built-in crossover network and brilliance level control. System supplied with plugs, cables and simple instructions. Shpg. wt., 67 lbs.

**HF-681WX** Hi-Fi STEREO PHONO SYSTEM with choice of cartridge and mahogany, walnut or blond changer base (please specify) 5.00 Down **Net 174.50**

**HF-683WX** Same as HF-681, but with 2 Lafayette Eliptoflex Series Bookshelf Enclosures (please specify finish). Shpg. wt., 143 lbs. 10.00 Down **Net 229.95**

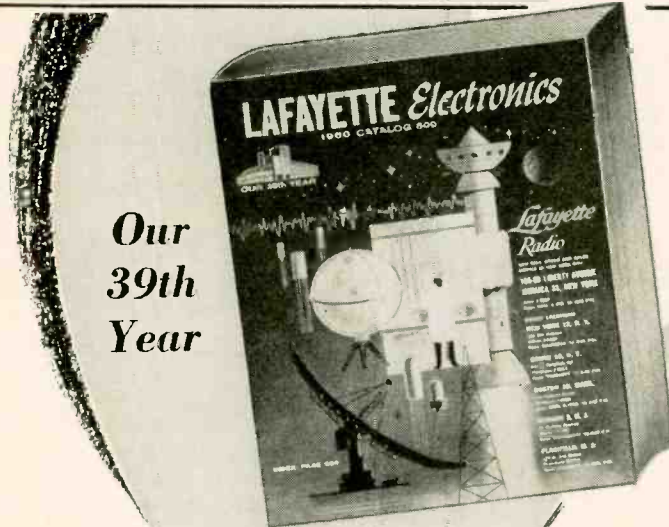**HF-682WX** Stereo AM-FM-Phono System. Same as HF-681 but including the Lafayette LT-50 stereo tuner. Shpg. wt., 85 lbs. 28.75 Down, 10.00 Down **Net 287.50**



Our  
39th  
Year

## Leaders in Hi-Fi

The most complete selection and largest stocks of hi-fi components and systems—available for immediate delivery at the lowest possible prices. Save even more on Lafayette endorsed "best-buy" complete systems.

# Lafayette Radio

"Everything in Electronics"

# FREE! 1960 CATALOG 308 GIANT SIZED PAGES

The Complete Catalog Featuring  
"The Best Buys In The Business"

FOR THE NEWEST AND FINEST IN  
STEREOPHONIC HI-FI EQUIPMENT AND SYSTEMS

- TAPE RECORDERS ● PUBLIC ADDRESS SYSTEMS
- AMATEUR EQUIPMENT ● INDUSTRIAL SUPPLIES
- MINIATURE COMPONENTS ● RADIO & TV TUBES AND PARTS
- EXCLUSIVE LAFAYETTE TRANSISTOR & HI-FI KITS

Send for Lafayette's FREE Catalog—the most complete, up-to-the-minute electronic supply catalog crammed full of everything in electronics at our customary down-to-earth money-saving prices.

A "must" for the economy-minded hi-fi enthusiast, experimenter, hobbyist, engineer, technician, student, serviceman and dealer.

**FREE** LAFAYETTE RADIO, Dept. JB6  
P.O. Box 222, Jamaica 31, N. Y.  
308 GIANT SIZED PAGES — FREE

Name

Address

City  State

# CITIZENS BAND RADIO at it's VERY BEST!




## NEW Arkay SQ-9 'SKY-VOX' Citizens' 2-Way Radio

Completely Wired and Aligned Front End Makes  
It The Easiest Kit to Assemble

Magnificently engineered for outstanding performance, ease of assembly and operation, the Sky-Vox offers high sensitivity, selectivity, stability and fidelity of sound. The finest in citizens' band communication for business, pleasure, auto, farm, home, industry, etc.

Advanced design features include: Completely assembled front end with 3 channels aligned ready to install in main chassis • Up-to-the-minute circuitry with 8 tubes and 5 diodes • Supersensitive crystal controlled superhet receiving circuit • Crystal controlled oscillator Pentode RF amplifier transmitting circuit • Front Panel controls include 3 position channel selector • Receive-Transmit switch • Volume control • Squelch control • Mike input • Noise balance control in rear chassis.

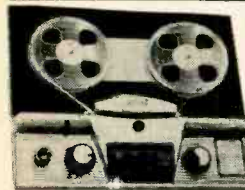Power Requirements: 117 Volts 60 cycles AC or 12 Volts DC. Sensitivity: 1  $\mu$ V, 400 cy. at 27.015 Mc. for full output (2.5 Watts); Signal/Noise Better than 35 DB • Image 30 DB • IF Bandwidth 5 KC • Complete with 2 cables, microphone and set of crystals. Attractive metal case. Size: 5" Hx8 1/2" Dx11" W. **\$79.95**  
Wired and Tested \$119.95 • Easy-to-build Kit



## the Arkay MS-5 STEREO Record TAPE DECK

Professional quality  
at a popular price!

A supreme achievement in tape deck design and performance, the ARKAY records your favorite music with the same superb performance of tape recorders costing many times more. No other tape deck, regardless of price—offers so many important features. Here's just a few:

- Combination Head for 2 or 4 Track Stereo-Two Speeds
- 30-16,000 cps  $\pm$  2 db.
- Flutter and wow: 1/4 of 1%
- Five-button operation
- -55 db. S/N
- All-metal tape fingers
- Drop-in Loading
- All-metal tape guards
- Large (1/2" diam.) capstan
- Size: 12 3/16" x 14 1/2" x 6 1/4"

2 Track Only \$129.95 • 4 Track Slightly Higher



## ARKAY CS-28 Stereo Amp/Pre-Amp Complete Control Center

Full 28 watts stereo of monaural, 60 watts peak • 14 watts each channel • reverse stereo • balance control • two channel gain control • full range bass and treble controls • 1% distortion, 4:2 to 1 • harmonic distortion, 1% 30-20,000 cps • dual pre-amp 2V output jacks • speaker outputs, 4, 8, 16, 32 ohms • response, 20-20,000 cps • push-pull EL84 Williamson circuit. Wired and tested \$99.95 • Easy-to-build Kit **\$64.95**



## ARKAY ST-11 AM-FM STEREO TUNER

Here, for the first time, is an AM-FM STEREO Tuner with the reach of every audiophile. Unmatched by units costing twice the price, the ST-11 is two distinct receivers in one featuring 4  $\mu$ V. for 20 db quieting. Variable AFC. Single front panel switch controls AM, FM or STEREO selection. Wired and tested \$74.50 Easy-to-build Kit **\$49.95**

SPA-55 STEREO AMP 55 watts stereo-monaural, 27 1/2 watts each channel. Wired \$79.95 Kit **\$64.95**



## ARKAY VT-10 6-INCH MULTI-PURPOSE VACUUM TUBE VOLTMETER

Advanced design and precision features make the Arkay VT-10 a truly sensational buy. Unmatched at this price. You get exclusive larger 6-100  $\mu$ A meter movement, within 2% accuracy, and edge-lighted for easier reading. 1% precision multiplier resistors are used throughout the range switch. There are 7 AC (RMS) and DC ranges, 7 AC (peak-to-peak) ranges. Resistance, db and other essential ranges. Durable plastic case. **\$25.95**  
Wired and tested \$47.95. Easy-to-build Kit

See and hear ARKAY Kits at your dealer.  
FREE! Stereo booklet and catalog. Write Dept. RE  
All prices 5% higher west of Mississippi



## NEW BOOKS (Continued from p. 154)

transistors, meters and amplifiers, both theoretically and as found in use.

The book is clear and complete. It includes problems with answers at the end of each chapter.

**MAGNETIC-AMPLIFIER CIRCUITS**, by William A. Geyger. McGraw-Hill Book Co., 330 W. 42 St., N. Y. 36, N. Y. 6 x 9 in. 394 pp. \$7

**MAGNETIC AMPLIFIER ENGINEERING**, by George M. Attura. McGraw-Hill Book Co., 330 W. 42 St., N. Y. 36, N. Y. 6 x 9 in. 220 pp. \$7.50

*Magnetic Amplifier Circuits* is a practical and comprehensive book for circuit designers. It uses a minimum of math, but relies heavily on diagrams and curves. The book discusses basic and complex circuits including non-feedback, feedback and self-balancing types, and analyzes them in clear fashion. The author aids clarity by his listings of advantages, modes of operation, characteristics and measurements where applicable. An extensive bibliography (including patents) follows each chapter.

*Magnetic Amplifier Engineering* is for engineers and deals with theory and principles. It starts with magnetic and reactor theory, then discusses core material and measurements, saturable reactors and rectifiers. The second half of the book discusses basic amplifiers, controls and output circuits.

The author compares the magnetic amplifier with other types, and includes new material on hybrid amplifiers. The method of analysis used here is basic and can be applied to any magnetic amplifier, however complex.

**101 WAYS TO USE YOUR OSCILLOSCOPE**, by Robert G. Middleton. Howard W. Sams & Co., Inc., Indianapolis 6, Ind. 5 1/2 x 8 1/2 in. 180 pp. \$2.50.

This working handbook shows how to use your scope in many new ways. The 101 applications deal particularly with TV receivers and include waveform measurement, signal tracing, circuit adjustments, balancing indication, etc.

Tests are grouped under headings like video amplifier, sync circuit, chroma, rf and if. Diagrams show how to set up the equipment for test, and photos show the resultant pattern. This book will reduce your servicing time and effort.—JQ

**GASEOUS CONDUCTORS**, by James Dillon Cobine. Dover Publications, Inc., 180 Varick St., New York, N. Y. 5 1/4 x 8 in. 606 pp. \$2.75.

This text for the specialist and graduate engineer requires a knowledge of at least calculus. It begins with basic theory and general laws of gases and goes on to discuss space charge, emission, glow, corona and arc discharges. Finally, it deals with applications like rectifiers, glow and fluorescent lamps, circuit breakers, lightning arresters, welding and voltage regulation.

The author seems to have covered the field very well. The book ends with problems, math tables and selected experiments. **END**

# PURCHASING A HI-FI SYSTEM?

Send Us  
Your  
List Of  
Components  
For A  
Package  
Quotation

WE WON'T BE  
UNDERSOLD!

All merchandise  
is brand new, fac-  
tory fresh & guar-  
anteed.

Free Hi Fi Catalog  
Available on Request.

# AIREX RADIO

CORPORATION

64-RE Cortlandt St., N.Y. 7, CO 7-2137

## PARTIAL LIST OF BRANDS IN STOCK

Altec Lansing  
Electrovoice  
Jensen • Stephens  
Hartley  
University  
Acoustic Research  
Janszen  
Wharfedale  
Karlsen Cabinets  
Viking  
Concertone  
Bell • G.E.  
Weathers  
Harman-Kardon  
Eico • Pilot  
Sherwood  
Acrosound  
Fisher • Dual  
Changer  
Bogen • Leak  
Dynakit  
H. H. Scott  
Ferrograph  
Tanberg  
Pentron  
Ampex • De Wald  
Revere  
Challenger  
Wollensak  
Garrard  
Miracord  
Glaser-Steers  
Rek-O-Kut  
Components  
Norelco  
Fairchild  
Pickering • Gray  
Audio Tape  
Conrac  
Wellcor Cabinets

The March issue of  
**RADIO-ELECTRONICS**  
on Sale Feb. 25

## BEST IN HI-FI VALUES!

NO  
DELAY  
SERVICE

All orders rushed to you  
in factory-sealed cartons.

Write for free catalog.

audion

25-E Oxford Road  
Massapequa, New York

## LEARN THE SHORT-CUTS

# Professional TELEVISION All-Practice TRAINING

Jump your earnings fixing black-and-white and color sets. Get into the top-pay bracket. NRI's concentrated spare time, low-cost training can do it for you. You'll fix sets faster, easier. Special course for Radio and TV servicemen — not for beginners. Full information free. Mail coupon now: **NATIONAL RADIO INSTITUTE, Dept. OBFT, Wash. 16, D.C.**

NATIONAL RADIO INSTITUTE  
Dept. OBFT, Washington 16, D.C.

Without cost or obligation send me facts about your  
Professional All-Practice TV Course.

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL

## ADVERTISING INDEX

Radio-Electronics does not assume responsibility for any errors appearing in the index below.

<table border="0" style="width: 100%;"> <tr><td>Alex Radio Corp.</td><td>158</td></tr> <tr><td>Allied Radio Corp.</td><td>27, 102-105, 158</td></tr> <tr><td>Arkay International Inc.</td><td>158</td></tr> <tr><td>Astac Corp.</td><td>Inside Back Cover</td></tr> <tr><td>Astron Corp.</td><td>9</td></tr> <tr><td>Audax, Div. of Rek-O-Kut.</td><td>144</td></tr> <tr><td>Audion</td><td>158</td></tr> <tr><td colspan="2"> </td></tr> <tr><td>B &amp; K Mfg. Co.</td><td>81, 99</td></tr> <tr><td>Barry Electronics Corp.</td><td>159</td></tr> <tr><td>Bell Telephone Labs</td><td>30</td></tr> <tr><td>Blonder-Tongue Labs</td><td>89</td></tr> <tr><td>Bonalide Radio</td><td>148</td></tr> <tr><td>Brooks Radio &amp; TV Corp.</td><td>159</td></tr> <tr><td>Burstein-Applebe Co.</td><td>125</td></tr> <tr><td colspan="2"> </td></tr> <tr><td>CRS Electronics</td><td>12</td></tr> <tr><td>Capitol Radio Engineering Inst.</td><td>110-113</td></tr> <tr><td>Carson Studios</td><td>125</td></tr> <tr><td>Castle TV Tuner Service</td><td>159</td></tr> <tr><td>Centralab Div. of Globe Union</td><td>106</td></tr> <tr><td>Century Electronics Co., Inc.</td><td>120-121</td></tr> <tr><td>Charles Engineering Co.</td><td>136</td></tr> <tr><td>Chemical Electronic Engineering</td><td>99</td></tr> <tr><td>Cisin (H. G.) Publisher</td><td>140</td></tr> <tr><td>Cleveland Inst. of Radio Electronics</td><td>10-11</td></tr> <tr><td>Colordaptor</td><td>122</td></tr> <tr><td>Columbia Record Club</td><td>13</td></tr> <tr><td>Cornell-Dubilier Electric Corp.</td><td>119</td></tr> <tr><td>Coyne Electrical School</td><td>80, 141, 150</td></tr> <tr><td colspan="2"> </td></tr> <tr><td>Delco Radio Div. of General Motors</td><td>24</td></tr> <tr><td>DeVry Technical Inst.</td><td>7</td></tr> <tr><td>Dressner</td><td>125</td></tr> <tr><td>Duotone Co., Inc.</td><td>153</td></tr> <tr><td>Dynaco Inc.</td><td>87</td></tr> <tr><td colspan="2"> </td></tr> <tr><td>Editors &amp; Engineers</td><td>98</td></tr> <tr><td>Electric Soldering Iron Co.</td><td>137</td></tr> <tr><td>Electro Products Labs</td><td>144</td></tr> <tr><td>Electro-Sonic Labs</td><td>109</td></tr> <tr><td>Electronic Chemical Corp.</td><td>79</td></tr> <tr><td>Electronic Instrument Co. (EICO)</td><td>30, 31</td></tr> <tr><td>Electronic Measurement Corp.</td><td>153</td></tr> <tr><td>Electronic Publishing Co.</td><td>142</td></tr> <tr><td>Electro-Voice Inc.</td><td>25</td></tr> <tr><td>Entron Co.</td><td>133</td></tr> <tr><td>Ernie Resistor Corp.</td><td>76</td></tr> <tr><td colspan="2"> </td></tr> <tr><td>Gernsback Library, Inc.</td><td>154</td></tr> <tr><td>Grantham School of Electronics</td><td>15</td></tr> <tr><td colspan="2"> </td></tr> <tr><td>Harmon-Kardon</td><td>3</td></tr> <tr><td>Heald Engineering College</td><td>148</td></tr> <tr><td>Heath Co.</td><td>66-73, 75</td></tr> <tr><td>Hi Fidelity Centre</td><td>122</td></tr> <tr><td>Homegood Products</td><td>114</td></tr> <tr><td>Hulston Specialties Co.</td><td>147</td></tr> <tr><td colspan="2"> </td></tr> <tr><td>Indiana Technical College</td><td>125</td></tr> <tr><td>Institute of Radio Engineers</td><td>151</td></tr> <tr><td>International Business Machines</td><td>28-29</td></tr> <tr><td>International Electronics Corp.</td><td>14</td></tr> <tr><td>International Resistance Corp.</td><td>128</td></tr> <tr><td colspan="2"> </td></tr> <tr><td>Jensen Industries</td><td>137</td></tr> <tr><td>Jerrold Electronics Co.</td><td>84</td></tr> <tr><td colspan="2"> </td></tr> <tr><td>Key Electronics Co.</td><td>148</td></tr> <tr><td colspan="2"> </td></tr> <tr><td>Lafayette Radio</td><td>156-157</td></tr> <tr><td>James B. Lansing Sound, Inc.</td><td>82</td></tr> <tr><td>Lektron Inc.</td><td>146</td></tr> <tr><td colspan="2"> </td></tr> <tr><td>Moss Electronics Inc.</td><td>126-127</td></tr> </table>	Alex Radio Corp.	158	Allied Radio Corp.	27, 102-105, 158	Arkay International Inc.	158	Astac Corp.	Inside Back Cover	Astron Corp.	9	Audax, Div. of Rek-O-Kut.	144	Audion	158			B & K Mfg. Co.	81, 99	Barry Electronics Corp.	159	Bell Telephone Labs	30	Blonder-Tongue Labs	89	Bonalide Radio	148	Brooks Radio & TV Corp.	159	Burstein-Applebe Co.	125			CRS Electronics	12	Capitol Radio Engineering Inst.	110-113	Carson Studios	125	Castle TV Tuner Service	159	Centralab Div. of Globe Union	106	Century Electronics Co., Inc.	120-121	Charles Engineering Co.	136	Chemical Electronic Engineering	99	Cisin (H. G.) Publisher	140	Cleveland Inst. of Radio Electronics	10-11	Colordaptor	122	Columbia Record Club	13	Cornell-Dubilier Electric Corp.	119	Coyne Electrical School	80, 141, 150			Delco Radio Div. of General Motors	24	DeVry Technical Inst.	7	Dressner	125	Duotone Co., Inc.	153	Dynaco Inc.	87			Editors & Engineers	98	Electric Soldering Iron Co.	137	Electro Products Labs	144	Electro-Sonic Labs	109	Electronic Chemical Corp.	79	Electronic Instrument Co. (EICO)	30, 31	Electronic Measurement Corp.	153	Electronic Publishing Co.	142	Electro-Voice Inc.	25	Entron Co.	133	Ernie Resistor Corp.	76			Gernsback Library, Inc.	154	Grantham School of Electronics	15			Harmon-Kardon	3	Heald Engineering College	148	Heath Co.	66-73, 75	Hi Fidelity Centre	122	Homegood Products	114	Hulston Specialties Co.	147			Indiana Technical College	125	Institute of Radio Engineers	151	International Business Machines	28-29	International Electronics Corp.	14	International Resistance Corp.	128			Jensen Industries	137	Jerrold Electronics Co.	84			Key Electronics Co.	148			Lafayette Radio	156-157	James B. Lansing Sound, Inc.	82	Lektron Inc.	146			Moss Electronics Inc.	126-127	<table border="0" style="width: 100%;"> <tr><td>National Radio Institute</td><td>19-20, 149, 158</td></tr> <tr><td>National Schools</td><td>5</td></tr> <tr><td colspan="2"> </td></tr> <tr><td>Olson Radio Corp.</td><td>148</td></tr> <tr><td>Opportunity Adults</td><td>143, 145</td></tr> <tr><td>Oxford Components, Inc.</td><td>137</td></tr> <tr><td colspan="2"> </td></tr> <tr><td>Paco Electronics Co., Inc.</td><td>97</td></tr> <tr><td>Perma-Power Co.</td><td>79</td></tr> <tr><td>Philco Technip Div.</td><td>160</td></tr> <tr><td>Pickering &amp; Co., Inc.</td><td>132</td></tr> <tr><td>Picture Tube Outlet</td><td>146</td></tr> <tr><td>Precision Electronics, Inc. (Grommes Kits)</td><td>146</td></tr> <tr><td>Princeton Electronics, Inc. (Test Equip.)</td><td>151</td></tr> <tr><td>Progressive "Edu-Kits" Inc.</td><td>138</td></tr> <tr><td colspan="2"> </td></tr> <tr><td>RCA Electron Tube Div.</td><td>Back Cover</td></tr> <tr><td>RCA Institutes</td><td>85-86</td></tr> <tr><td>RCA (Test Equipment)</td><td>88</td></tr> <tr><td>Radio Shack Corp.</td><td>124</td></tr> <tr><td>Rek-O-Kut</td><td>144</td></tr> <tr><td>Rinehart &amp; Co., Inc.</td><td>98, 124, 129</td></tr> <tr><td colspan="2"> </td></tr> <tr><td>Sams (Howard W.) &amp; Co., Inc.</td><td>130-131</td></tr> <tr><td>Scherr-Tunico Co.</td><td>98</td></tr> <tr><td>Schober Organ Co.</td><td>78</td></tr> <tr><td>Scott Inc.</td><td>21</td></tr> <tr><td>Seco Mfg. Co.</td><td>109</td></tr> <tr><td>Sencore</td><td>143, 145, 147, 149</td></tr> <tr><td>Shure Brothers, Inc.</td><td>74</td></tr> <tr><td>Sonotone Corp.</td><td>18</td></tr> <tr><td>Sprayberry Academy of Radio TV</td><td>23</td></tr> <tr><td>Standard Coil Products Co. Inc.</td><td>90-95</td></tr> <tr><td>Sylvania Electric Products, Inc.</td><td>134-135</td></tr> <tr><td colspan="2"> </td></tr> <tr><td>TAB</td><td>142</td></tr> <tr><td>Tarzon, (Sarkes) Inc.</td><td>124</td></tr> <tr><td>Teltron Electrical Co.</td><td>122</td></tr> <tr><td>Transpace</td><td>128</td></tr> <tr><td>Triplet Electrical Instrument Co.</td><td>Inside Front Cover</td></tr> <tr><td>Tung-Sol Electric Co.</td><td>22</td></tr> <tr><td>Turner Co.</td><td>8</td></tr> <tr><td colspan="2"> </td></tr> <tr><td>United Audio Products</td><td>148</td></tr> <tr><td colspan="2"> </td></tr> <tr><td>D. Van Nostrand Co., Inc.</td><td>114</td></tr> <tr><td>Vidair Electronics Mfg. Corp.</td><td>148</td></tr> <tr><td>Vis-U-All Products Co.</td><td>128</td></tr> <tr><td colspan="2"> </td></tr> <tr><td>Weathers Industries</td><td>26</td></tr> <tr><td>Weller Electric Corp.</td><td>123</td></tr> <tr><td>Weston Electrical Instrument Corp.</td><td>83</td></tr> <tr><td>Winegard Co.</td><td>16-17</td></tr> <tr><td>Workman TV</td><td>132, 153</td></tr> <tr><td colspan="2"> </td></tr> <tr><td>Xcelite</td><td>152</td></tr> </table>	National Radio Institute	19-20, 149, 158	National Schools	5			Olson Radio Corp.	148	Opportunity Adults	143, 145	Oxford Components, Inc.	137			Paco Electronics Co., Inc.	97	Perma-Power Co.	79	Philco Technip Div.	160	Pickering & Co., Inc.	132	Picture Tube Outlet	146	Precision Electronics, Inc. (Grommes Kits)	146	Princeton Electronics, Inc. (Test Equip.)	151	Progressive "Edu-Kits" Inc.	138			RCA Electron Tube Div.	Back Cover	RCA Institutes	85-86	RCA (Test Equipment)	88	Radio Shack Corp.	124	Rek-O-Kut	144	Rinehart & Co., Inc.	98, 124, 129			Sams (Howard W.) & Co., Inc.	130-131	Scherr-Tunico Co.	98	Schober Organ Co.	78	Scott Inc.	21	Seco Mfg. Co.	109	Sencore	143, 145, 147, 149	Shure Brothers, Inc.	74	Sonotone Corp.	18	Sprayberry Academy of Radio TV	23	Standard Coil Products Co. Inc.	90-95	Sylvania Electric Products, Inc.	134-135			TAB	142	Tarzon, (Sarkes) Inc.	124	Teltron Electrical Co.	122	Transpace	128	Triplet Electrical Instrument Co.	Inside Front Cover	Tung-Sol Electric Co.	22	Turner Co.	8			United Audio Products	148			D. Van Nostrand Co., Inc.	114	Vidair Electronics Mfg. Corp.	148	Vis-U-All Products Co.	128			Weathers Industries	26	Weller Electric Corp.	123	Weston Electrical Instrument Corp.	83	Winegard Co.	16-17	Workman TV	132, 153			Xcelite	152
Alex Radio Corp.	158																																																																																																																																																																																																																																																																						
Allied Radio Corp.	27, 102-105, 158																																																																																																																																																																																																																																																																						
Arkay International Inc.	158																																																																																																																																																																																																																																																																						
Astac Corp.	Inside Back Cover																																																																																																																																																																																																																																																																						
Astron Corp.	9																																																																																																																																																																																																																																																																						
Audax, Div. of Rek-O-Kut.	144																																																																																																																																																																																																																																																																						
Audion	158																																																																																																																																																																																																																																																																						
B & K Mfg. Co.	81, 99																																																																																																																																																																																																																																																																						
Barry Electronics Corp.	159																																																																																																																																																																																																																																																																						
Bell Telephone Labs	30																																																																																																																																																																																																																																																																						
Blonder-Tongue Labs	89																																																																																																																																																																																																																																																																						
Bonalide Radio	148																																																																																																																																																																																																																																																																						
Brooks Radio & TV Corp.	159																																																																																																																																																																																																																																																																						
Burstein-Applebe Co.	125																																																																																																																																																																																																																																																																						
CRS Electronics	12																																																																																																																																																																																																																																																																						
Capitol Radio Engineering Inst.	110-113																																																																																																																																																																																																																																																																						
Carson Studios	125																																																																																																																																																																																																																																																																						
Castle TV Tuner Service	159																																																																																																																																																																																																																																																																						
Centralab Div. of Globe Union	106																																																																																																																																																																																																																																																																						
Century Electronics Co., Inc.	120-121																																																																																																																																																																																																																																																																						
Charles Engineering Co.	136																																																																																																																																																																																																																																																																						
Chemical Electronic Engineering	99																																																																																																																																																																																																																																																																						
Cisin (H. G.) Publisher	140																																																																																																																																																																																																																																																																						
Cleveland Inst. of Radio Electronics	10-11																																																																																																																																																																																																																																																																						
Colordaptor	122																																																																																																																																																																																																																																																																						
Columbia Record Club	13																																																																																																																																																																																																																																																																						
Cornell-Dubilier Electric Corp.	119																																																																																																																																																																																																																																																																						
Coyne Electrical School	80, 141, 150																																																																																																																																																																																																																																																																						
Delco Radio Div. of General Motors	24																																																																																																																																																																																																																																																																						
DeVry Technical Inst.	7																																																																																																																																																																																																																																																																						
Dressner	125																																																																																																																																																																																																																																																																						
Duotone Co., Inc.	153																																																																																																																																																																																																																																																																						
Dynaco Inc.	87																																																																																																																																																																																																																																																																						
Editors & Engineers	98																																																																																																																																																																																																																																																																						
Electric Soldering Iron Co.	137																																																																																																																																																																																																																																																																						
Electro Products Labs	144																																																																																																																																																																																																																																																																						
Electro-Sonic Labs	109																																																																																																																																																																																																																																																																						
Electronic Chemical Corp.	79																																																																																																																																																																																																																																																																						
Electronic Instrument Co. (EICO)	30, 31																																																																																																																																																																																																																																																																						
Electronic Measurement Corp.	153																																																																																																																																																																																																																																																																						
Electronic Publishing Co.	142																																																																																																																																																																																																																																																																						
Electro-Voice Inc.	25																																																																																																																																																																																																																																																																						
Entron Co.	133																																																																																																																																																																																																																																																																						
Ernie Resistor Corp.	76																																																																																																																																																																																																																																																																						
Gernsback Library, Inc.	154																																																																																																																																																																																																																																																																						
Grantham School of Electronics	15																																																																																																																																																																																																																																																																						
Harmon-Kardon	3																																																																																																																																																																																																																																																																						
Heald Engineering College	148																																																																																																																																																																																																																																																																						
Heath Co.	66-73, 75																																																																																																																																																																																																																																																																						
Hi Fidelity Centre	122																																																																																																																																																																																																																																																																						
Homegood Products	114																																																																																																																																																																																																																																																																						
Hulston Specialties Co.	147																																																																																																																																																																																																																																																																						
Indiana Technical College	125																																																																																																																																																																																																																																																																						
Institute of Radio Engineers	151																																																																																																																																																																																																																																																																						
International Business Machines	28-29																																																																																																																																																																																																																																																																						
International Electronics Corp.	14																																																																																																																																																																																																																																																																						
International Resistance Corp.	128																																																																																																																																																																																																																																																																						
Jensen Industries	137																																																																																																																																																																																																																																																																						
Jerrold Electronics Co.	84																																																																																																																																																																																																																																																																						
Key Electronics Co.	148																																																																																																																																																																																																																																																																						
Lafayette Radio	156-157																																																																																																																																																																																																																																																																						
James B. Lansing Sound, Inc.	82																																																																																																																																																																																																																																																																						
Lektron Inc.	146																																																																																																																																																																																																																																																																						
Moss Electronics Inc.	126-127																																																																																																																																																																																																																																																																						
National Radio Institute	19-20, 149, 158																																																																																																																																																																																																																																																																						
National Schools	5																																																																																																																																																																																																																																																																						
Olson Radio Corp.	148																																																																																																																																																																																																																																																																						
Opportunity Adults	143, 145																																																																																																																																																																																																																																																																						
Oxford Components, Inc.	137																																																																																																																																																																																																																																																																						
Paco Electronics Co., Inc.	97																																																																																																																																																																																																																																																																						
Perma-Power Co.	79																																																																																																																																																																																																																																																																						
Philco Technip Div.	160																																																																																																																																																																																																																																																																						
Pickering & Co., Inc.	132																																																																																																																																																																																																																																																																						
Picture Tube Outlet	146																																																																																																																																																																																																																																																																						
Precision Electronics, Inc. (Grommes Kits)	146																																																																																																																																																																																																																																																																						
Princeton Electronics, Inc. (Test Equip.)	151																																																																																																																																																																																																																																																																						
Progressive "Edu-Kits" Inc.	138																																																																																																																																																																																																																																																																						
RCA Electron Tube Div.	Back Cover																																																																																																																																																																																																																																																																						
RCA Institutes	85-86																																																																																																																																																																																																																																																																						
RCA (Test Equipment)	88																																																																																																																																																																																																																																																																						
Radio Shack Corp.	124																																																																																																																																																																																																																																																																						
Rek-O-Kut	144																																																																																																																																																																																																																																																																						
Rinehart & Co., Inc.	98, 124, 129																																																																																																																																																																																																																																																																						
Sams (Howard W.) & Co., Inc.	130-131																																																																																																																																																																																																																																																																						
Scherr-Tunico Co.	98																																																																																																																																																																																																																																																																						
Schober Organ Co.	78																																																																																																																																																																																																																																																																						
Scott Inc.	21																																																																																																																																																																																																																																																																						
Seco Mfg. Co.	109																																																																																																																																																																																																																																																																						
Sencore	143, 145, 147, 149																																																																																																																																																																																																																																																																						
Shure Brothers, Inc.	74																																																																																																																																																																																																																																																																						
Sonotone Corp.	18																																																																																																																																																																																																																																																																						
Sprayberry Academy of Radio TV	23																																																																																																																																																																																																																																																																						
Standard Coil Products Co. Inc.	90-95																																																																																																																																																																																																																																																																						
Sylvania Electric Products, Inc.	134-135																																																																																																																																																																																																																																																																						
TAB	142																																																																																																																																																																																																																																																																						
Tarzon, (Sarkes) Inc.	124																																																																																																																																																																																																																																																																						
Teltron Electrical Co.	122																																																																																																																																																																																																																																																																						
Transpace	128																																																																																																																																																																																																																																																																						
Triplet Electrical Instrument Co.	Inside Front Cover																																																																																																																																																																																																																																																																						
Tung-Sol Electric Co.	22																																																																																																																																																																																																																																																																						
Turner Co.	8																																																																																																																																																																																																																																																																						
United Audio Products	148																																																																																																																																																																																																																																																																						
D. Van Nostrand Co., Inc.	114																																																																																																																																																																																																																																																																						
Vidair Electronics Mfg. Corp.	148																																																																																																																																																																																																																																																																						
Vis-U-All Products Co.	128																																																																																																																																																																																																																																																																						
Weathers Industries	26																																																																																																																																																																																																																																																																						
Weller Electric Corp.	123																																																																																																																																																																																																																																																																						
Weston Electrical Instrument Corp.	83																																																																																																																																																																																																																																																																						
Winegard Co.	16-17																																																																																																																																																																																																																																																																						
Workman TV	132, 153																																																																																																																																																																																																																																																																						
Xcelite	152																																																																																																																																																																																																																																																																						

### SCHOOL DIRECTORY PAGE 155

Baltimore Technical Institute  
 Canadian Institute of Science & Technology  
 Candler System Co.  
 Indiana Technical College  
 International Correspondence School  
 Milwaukee School of Engineering  
 Pacific International College of Arts & Sciences  
 Tri-State College  
 Valparaiso Technical Institute

BRANCH ADVERTISING OFFICES: Chicago: 5500 N. Menard Ave., Chicago, Ill., Spring 4-1444. Los Angeles: Husted-Coughlin, 600 South New Hampshire, Tel. DUm-kirk 7-2328. San Francisco: Husted-Coughlin, 444 Market St., Tel. GArlend 1-2481.  
 FOREIGN AGENTS: Great Britain: Atlas Publishing and Distributing Co., Ltd., 18 Bride Lane, London E.C. 4.  
 Printed in the United States of America

## BARRY SPECIALS

- **Deluxe Thermador Choke**. 4 Hy @ 900 Ma. Sealed. Beautiful construction. (Ltd. Qty) \$8.95.
- **Amperite Delay Relay Type 115N060T**. 60 Second delay. Operates on 115 VAC @ 60 CPS. Fits miniature tube socket. Special 90¢.
- **Socket for 5D21, 715A/B/C, etc.** Ceramic. 50¢ ea. (10 for \$4.00).
- **G. E. Pyranol Capacitor**. 1.0 Mfd @ 6000 VDC. New. Boxed \$4.95 ea.
- **BC-603 Power Supply**. Completely wired. Ready to operate the popular BC603 Receivers. Has exact connector used on BC603 Revr. 115 VAC @ 60 CPS operation. \$9.95.
- **UHF Transmitter**—Compact. Near 1 1/4 meter band. Converts easily to 2 meters. Uses two 6201's into single Amperex 6360 twin triode. Size: 4" x 4" x 11". Antenna is 10 1/2". New. (Most beautiful rig. Finest parts we have seen in yrs.) A real gem, complete with tubes, antenna and case (no book). \$19.95. Schematic furnished.
- **Battery for above xmfr** furnishes 300 VDC plate and 6.3 VDC filament \$4.95.
- **New — Sonotone Rechargeable Battery**. Plug in any AC outlet to recharge. Use 100's of times. Orig. jobber boxed. \$7.95.
- **Hi-Fi Special Western Electric 300B Output Tubes**. Special \$5.50 each (2 for \$10.00).
- **Mallory Inductance**. Unused. This famous device is an excellent UHF front-end tuner suitable for TV, UHF, Ham/Comm'l revrs, etc. Brand new, unused. \$2.95.
- **Double-Spaced Variable Capacitor**. 14 Min. to 64 Max. Mmf. Will handle up to 100 watts AM. Ceramic insulation. \$1.00.
- **Choke**. .35 Hy @ 2 Amps. DC resistance: 2.2 Ohms. Herm. sid. \$4.25. Open Frame: \$3.50.
- **RCA Remote TV Control** For use in 1955 and many earlier RCA TV sets (write for list of sets unit will accommodate). Controls picture & audio. Convenient, practical @ \$18.95 (with 28 page manual).
- **Electrolytic Condensers**. 4 x 20 Mfd @ 450 VDC. Sprague. Stock #CO4X20. 69¢ each.
- **Jennings Fixed Vacuum Capacitors Type JCS-25** Mmf @ 10,000 V. Peak. Cat. #JCS25; 50 Mmf @ 10,000 V. Peak. Cat. #JCS50) .....\$3.75 ea.
- **Oil Capacitor 2 Mfd @ 6000 VDC**. New. Mfd. by Illinois Condenser Corp. \$8.95.
- **Oil Capacitor 2 Mfd @ 7500 VDC**. New. Mfd by G.E. \$22.50.
- **Crystal Oven**. 12 VAC or DC Oven for 10 Crystal type CR 18/U, or similar crystals. Heater & thermostat enc. Cat. #CFT40148A. \$2.50.

### FOLLOWING ITEMS ARE REMOVED FROM NEW EQUIPMENT. ALL IN PERFECT CLEAN CONDITION. LIMITED QUANTITIES:


- **Adjustable Time Delay Relay**. SPST. 5 Amps. (N.O.) 115 VAC Coil. Adjust from 2 to 30 sec. \$5.95.
- **Overload Relay**. Adj. from .5 to 2 Amps DC. Westinghouse Glass enc. \$7.50.
- **CD 2 Mfd. @ 6000 VDC Oil Capacitor**. \$8.00.
- **Sangamo Mica Capacitor** .002Mfd @ 12,500 volts. \$4.95.
- **Filter Choke**. 11 Hy @ 300 Ma. Herm. sid. \$3.95.
- **Swinging Choke**. 6 to 19 Hy @ 300 to 30 Ma. Herm. sid. \$4.95.

**SPECIAL TRANSMITTING & SPECIAL PURPOSE TUBES:** 3B28 @ \$3.00; 4-125A @ \$29.00; 4-250A @ \$38.00; 4X150A @ \$7.00; 4X250B @ \$35.00; RKR-72 @ .15¢; HF-100 @ \$8.00; 204A @ \$12.00; 300B @ \$5.50; 404A/5847 @ \$6.00; 807 @ \$1.15; 811 @ \$3.25; 830B @ .50¢; 837 @ \$1.00; 838 @ \$1.00; 884 @ .90¢; 5654 @ \$1.75; 8013 @ \$3.00. Many others. Largest diversified tube stock in country. Write for Special purpose & xmtg tube catalog (free).

Coming out soon 1960 Green Sheet .25c—Write. Hqs for tubes, semiconductors, tube cartons. All at sensible prices with Barry guarantee (cost of mds only). \$5.00 minimum order. Mds. subject to prior sale.

**INDUSTRIAL INQUIRIES INVITED.**  
 Factory authorized distributors for Westinghouse. CBS tubes and semiconductors.

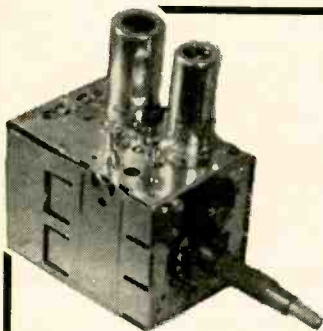**BARRY ELECTRONICS CORP.**  
 Dept. RE-2, 512 Broadway  
 (near Spring St.)  
 New York 12, N.Y. Walker 5-7000



# TV TUNERS OVERHAULED

**ALL MAKES AND MODELS VHF OR UHF**

**ALIGNED TO ORIGINAL STANDARDS FAST SERVICE PRESENT DELIVERY IS 48 HRS. ON MANY TYPES**

**90 Days Warranty**

**VHF OR UHF TUNER OVERHAULED \$ 9.95 NET**  
**UHF/VHF COMBINATION OVERHAULED \$19.90 NET**

Prices include labor and minor parts only, defective tubes and damaged major parts are extra at net prices.


Forward defective tuner complete with tubes, shield cover and any damaged parts. Quote make and model, and describe fault. We will ship C.O.D.—F.O.B. Chicago or Toronto.

**Castle TV Tuner Service**

Suppliers of rebuilt TV Tuners to leading manufacturers, technicians & service dealers, coast to coast. Original and Only Complete TV Tuner Service covering the North American Continent.

5710 N. Western Ave.  
 Chicago 45, Illinois  
 In Canada:—136 Main St.,  
 Toronto 13, Ont.
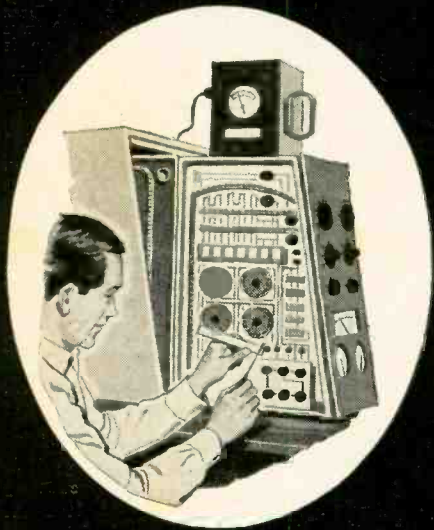
# Learn TRANSISTOR, COMPUTER OR RADAR TECHNOLOGY at home



Prepare now for advancement...and for a secure and profitable career in one of these growing fields of electronics

## CHOOSE FROM 7 PROVEN COURSES

1. **SEMICONDUCTORS**—Transistor Principles and Practices. Learn Theory, construction, application of all types of transistors.
2. **PRINCIPLES OF RADAR CIRCUITS AND EQUIPMENT**—Introduction to, and detailed study of radar fundamentals.
3. **RADAR SYSTEMS PRINCIPLES AND PRACTICES (Advanced Level)**—Applications of radar components, systems, design... performance measurement.
4. **INTRODUCTION TO ANALOG COMPUTERS**—Covers theories and fundamentals of all makes of analog computers.
5. **ANALOG COMPUTER SYSTEMS (Advanced Level)**—Covers the analog system concepts and methods.
6. **AUTOMATIC DIGITAL COMPUTERS**—Digital computer theory, maintenance, installation, basic programming.
7. **PROGRAMMING FOR DIGITAL COMPUTERS**—Covers encoding, set-up and operation.

## MAIL COUPON TODAY FOR FREE INFORMATION

PHILCO TECHNOLOGICAL CENTER

"C" and Ontario Streets, P.O., Box 4730, Phila. 34, Pa.

TCR-4

Please send full information on subjects checked below. (No obligation)

- |   |   |
|---|---|
| <input type="checkbox"/> 1. Semiconductors                    | <input type="checkbox"/> 4. Intro. to Analog Comp.  |
| <input type="checkbox"/> 2. Principles of Radar               | <input type="checkbox"/> 5. Analog Comp. Systems    |
| <input type="checkbox"/> 3. Radar Systems                     | <input type="checkbox"/> 6. Automatic Digital Comp. |
| <input type="checkbox"/> 7. Programming for Digital Computers |   |

NAME \_\_\_\_\_  
 COMPANY \_\_\_\_\_ POSITION \_\_\_\_\_  
 ADDRESS \_\_\_\_\_  
 CITY \_\_\_\_\_ STATE \_\_\_\_\_

Expand your knowledge in one of these rapidly advancing fields of electronics and you'll be set for a secure and profitable future. Transistor technology is becoming one of the biggest fields in electronics. The use of automatic computers in automated factories, business offices and military systems is outpacing the technical manpower needed to build and maintain them. New developments in radar have given new life to this dynamic field. Electronics men are in demand, but it takes specialists to land the big jobs. Now's the time to prepare... advance and prosper in this new era.

**Learn with proven home study courses from the Philco Technological Center.** Get a practical, working knowledge with proven courses developed by specialists in electronics and training... men who know the kind of knowledge you need. Philco Technological Center is a department of Philco TechRep Division, one of the world's leading field engineering organizations.

**NOW READY**—A special computer programming course that covers all important techniques of encoding and operation... ideal for maintenance men, or those who wish to become Programmers. Send for full details. No salesman will call.





HERE'S A **COMPACT** DESIGN

that's preferred among  
all modern designs!

IT'S THE SLIM, TRIM NEW  
330 MICROPHONE SERIES  
Dynamic, Ceramic and Crystal Models

BY **ASTATIC**

ACTUAL  
SIZE



never before such quality of performance and  
versatility of application at such low price

Yes, here's a classic design in modern, compact microphones—small, slender, unobtrusive, a beauty in simplicity. But the greatest achievement is in the magnificent performance quality of the Series among a great host of applications.

The Dynamic Models 335H (high impedance) and 335L (low impedance) operate with highest quality characteristics in TV and radio broadcast usage, in professional or home recording, public address, almost unlimited other lavalier, hand or stand applications.

The Ceramic Model 331 is a voice range unit specifically engineered for excellence in communications applications, 27 megacycle citizens' band use, and paging.

Ceramic Model 333 is a wide-range microphone offering a similarly high new level of perfection for tape recording, P. A. Systems, etc.

Crystal Model 332, with satin chrome body and cap, black grille, is already famous through widespread use. Performance throughout the series is of the highest order. **THUS, THE GREATEST NEWS OF ALL CONCERNING THESE NEW ASTATIC UNITS IS THEIR AMAZINGLY LOW COST!** Check out these new Astatic Microphones at your first opportunity.

Model	Type	Output	Frequency Range	Impedance	Finish	List Price
331	Ceramic	-56 db	300-5,000	High	Black Body and Grille, Chrome Cap	\$17.90
333	Ceramic	-58 db	30-12,000	High		17.90
335H	Dynamic	-56 db	50-12,000	High	TV Grey Body, Chrome Cap and Grille	26.50
335L	Dynamic	-57 db	50-12,000	Low		23.50

**NOTE:** Model 331 has momentary-on, spring-return switch, is furnished with hang-up bracket. Cable provides for audio and relay connections. All other models have slide switch with "lock-on" position, are complete with lavalier and stand adaptor with 5/8"-27 thread.

**THE Astatic CORPORATION, CONNEAUT, OHIO**  
KNOWN THE WORLD OVER



In Canada: Canadian Astatic Limited, Toronto, Ontario  
Export Sales: Roburn Agencies, Inc., 431 Greenwich St., N. Y. 13, N. Y., U. S. A.

GO BY BRAND . .  
GO BUY ASTATIC

# REDUCE DAMPER TUBE CALLBACKS



## Here are some important facts about damper circuits

In the transformer-coupled circuit, Figure 1, the damper cathode is connected to the "low" (Boost) side of the sweep-output circuit. The voltage difference between cathode and ground is usually less than about 600 volts.

In the direct-drive circuit, Figure 2, and in the auto-transformer circuits, Figures 3 and 4, the damper cathode is connected to a "high" point in the sweep-output circuit. The peak voltage difference between cathode and ground may be several thousand volts.

Because the damper cathode is "above ground" by several hundred to several thousand volts, care must be taken to prevent voltage breakdown between heater and cathode in the

damper tube. Two basic methods are used:

In one method, shown in Figures 1, 2, and 3, heater is connected to cathode. This connection eliminates voltage difference between heater and cathode, but it also makes the damper tube heater circuit "hot" with respect to ground. For this reason it is necessary to use a separate secondary winding on the power transformer just for the damper heater. This winding, and its connecting leads, must be insulated to withstand the peak voltage difference between cathode and ground.

In the circuits of Figures 1, 2, and 3, if the damper heater winding becomes grounded, or arcs to ground, high current will flow from B+ to ground through the damper tube, and the fuse will blow. Correction of this trouble usually requires costly and time-consuming replacement of the power transformer.

The second method, shown in Figure 4, takes advantage of the fact that modern damper tubes, such as the RCA-6AX4-GTA, 6AU4-GTA, and 6DE4, are designed to withstand high-amplitude positive pulse voltages between heater and cathode. These RCA

tubes make it possible to ground the damper heater circuit, and for this reason, the damper heater may be connected to the regular 6.3-volt-ac grounded-heater circuit, thus eliminating the need for an additional high-voltage-insulated secondary on the power transformer.

From a servicing viewpoint, the second method has definite advantages:

In the circuit of Figure 4, if the insulation between heater and cathode should break down, high current will flow from B+ to ground through the damper tube, and the fuse will blow, but the trouble can be corrected easily, quickly, and inexpensively by installing a new RCA damper tube. This is a lot easier and cheaper than installing a new power transformer!

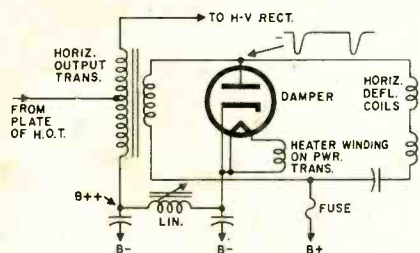


Figure 1. Transformer-coupled horizontal-output circuit. Note that the damper tube heater is connected to the cathode.

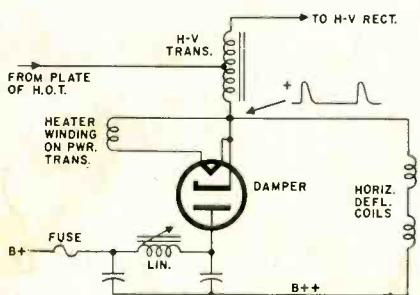


Figure 2. Direct-drive circuit. In some variations of this circuit, a capacitor is connected between heater and cathode in place of the direct connection. The capacitor serves to reduce the pulse-voltage difference between heater and cathode.

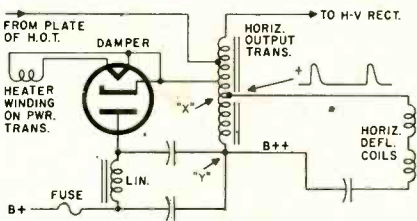


Figure 3. Auto-transformer circuit in which the damper tube heater is connected to the cathode. In some variations of this circuit, the heater is connected to a lower-voltage tap, "X" or "Y", in order to make the heater negative with respect to the cathode, and to reduce the shunting effect of the heater-circuit capacitance.


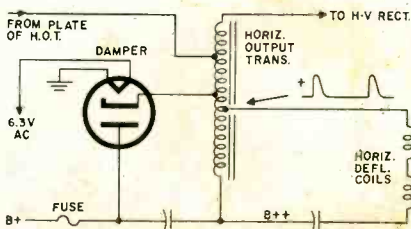


Figure 4. Modern auto-transformer circuit in which the damper tube heater is grounded. Tubes such as the RCA-6AX4-GTA, 6AU4-GTA, and 6DE4, which are designed to withstand high peak pulse voltage between heater and cathode, are required in this circuit.

Momentary arcing, or flashover, in a horizontal output tube or damper tube may be "self-correcting", that is, the flashover may not occur again. But the momentary flashover results in a heavy surge of current which will blow the conventional type of fuse. You can eliminate such unnecessary fuse failure by using RCA "chemical" fuses in the horizontal-output circuit. Three varieties, RCA Stock Nos. 104295, 105041, 105042, are available at your RCA distributor.

RCA damper tubes are designed to give long, dependable service—eliminate costly callbacks—prevent loss of your time and profits. Take for example the RCA-6DE4 and RCA-17DE4. These tubes can supply a peak plate current of 1100 milliampères and withstand a heater-to-cathode potential of 5000 volts—with a 900-volt dc component! Assure your customers of this kind of performance by asking your distributor for RCA damper tubes.

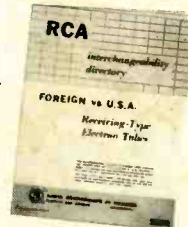

Get your copy of RCA's Foreign-vs-U.S.A. Receiving Tube-Interchangeability Directory (ICE-197) from your authorized RCA Tube Distributor.



ANOTHER WAY RCA HELPS YOU IMPROVE YOUR BUSINESS

**RADIO CORPORATION OF AMERICA**

Electron Tube Division

Harrison, N. J.