

Radio-Electronics

MARCH 1960
IND




Radiophones for Small Boats

**Electronics Controls
Melting Glass**

**Make Your Own
Solar Cells**


**How Good Are Speaker
Response Curves?**

HUGO G. VEBACK, Editor

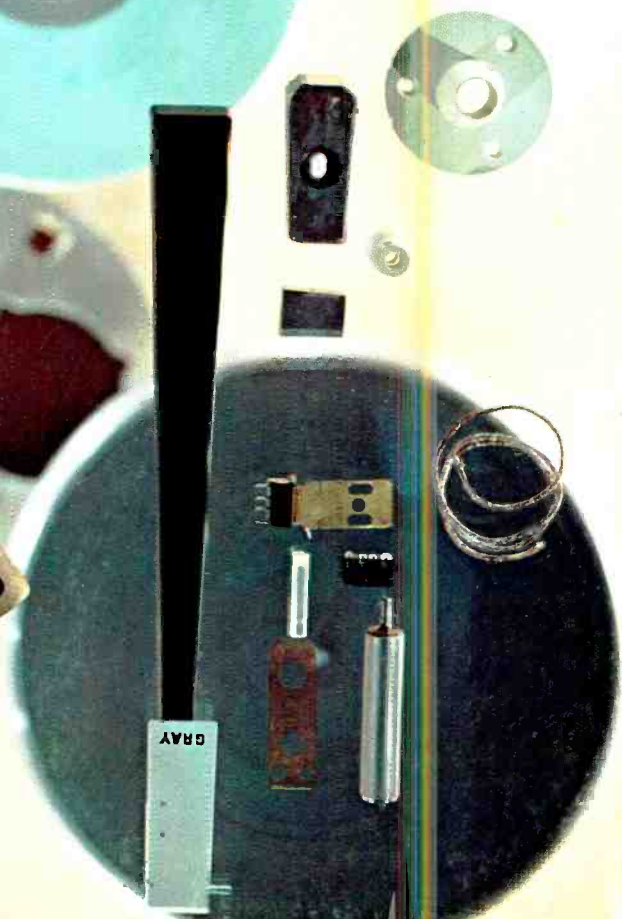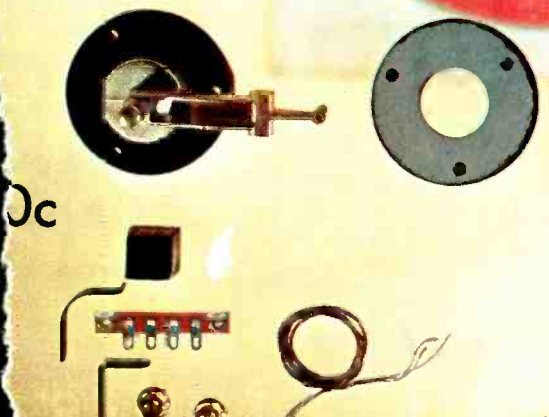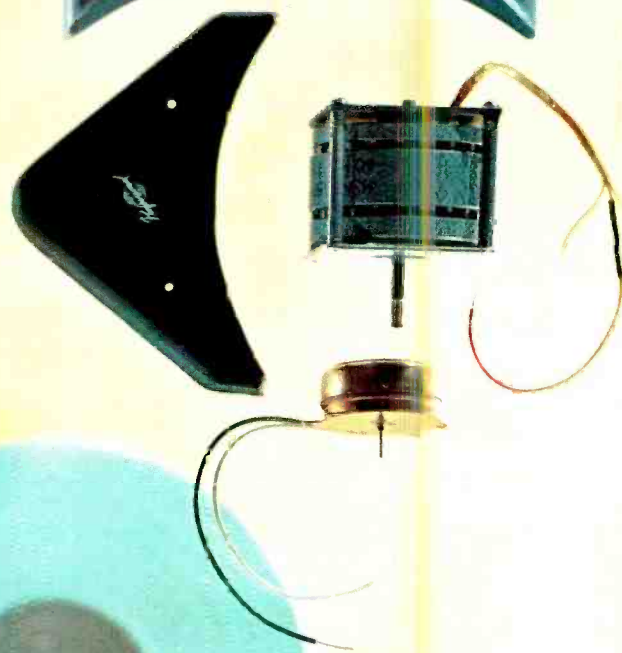


**KITS FOR
TURNTABLES
AND ARMS**

See page 44

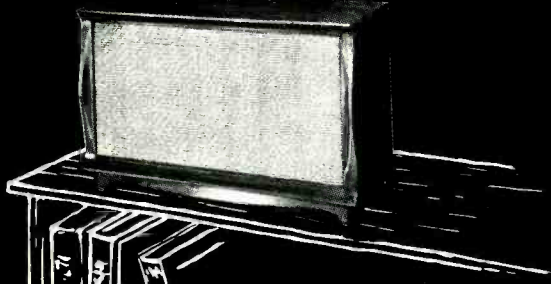

TR-10 TRI-ETTE 3-Way Speaker System.

Compare the Jensen TRI-ETTE with any bookshelf speaker and let your own ears tell you the reason for its rocketing popularity . . . *it sounds better!* It's what you'd expect from advanced Jensen engineering that begins where others leave off. Efficient too . . . needs only a 10-watt amplifier. Handsome in graceful contemporary design with fine woods in choice of Walnut, Mahogany or Tawny Ash. Get a TRI-ETTE speaker system for superb mono hi-fi . . . add another for the finest stereo reproduction in small space at only \$119.50 each. Table Base (extra) . . . \$5.45. Matching Floor Stand 14" high (extra) . . . \$12.95

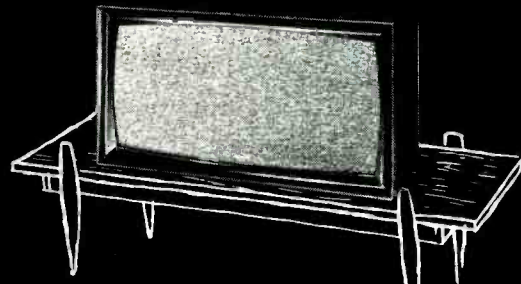


DF-1 DUETTE 2-Way Speaker System.

A new high in loudspeaker value . . . a high quality, economically priced 2-way "bookshelf" system made possible by an entirely new and different high compliance 8" FLEXAIR* woofer by Jensen . . . capable of movement *more than twice as far* as previously available units . . . with low distortion bass down to 36 cycles in tube-vented BASS-SUPERFLEX* enclosure. Fine furniture crafted of 3/4" selected veneer in choice of Walnut, Mahogany or Tawny Ash finished on four sides for horizontal or vertical placement. Only \$79.50. Table Base (extra) . . . \$5.45. Floor Stand for vertical placement (extra) . . . \$7.50

You should know there is something better!

Jensen "BOOKSHELF" LOUDSPEAKERS AND KITS

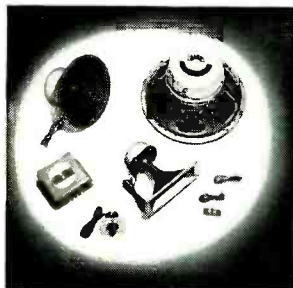SPEAKER SYSTEMS IN FINE FURNITURE OR KITS FOR STEREO AND MONO HI-FI




KT-33
3-WAY
SPEAKER
SYSTEM
KIT

BASIC
ENCLOSURE
DATA

USE THESE KITS IN YOUR OWN CABINETRY OR BUILT-IN SYSTEM


For outstanding TRI-ETTE performance in your own enclosure or custom built-in system, the KT-33 Kit is the answer. Includes P12-NF 12-inch FLEXAIR woofer, P8-UM 8-inch midchannel, RP-103A compression driver tweeter, H-F control, crossover network, wiring

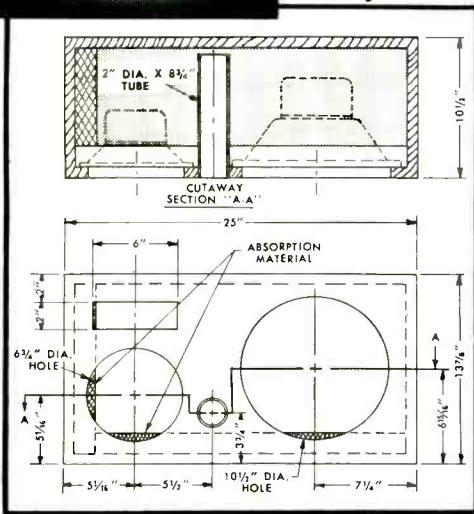and full instructions for enclosure construction and installation. (Enclosure vent-tube 46MP06 must be ordered separately. Price 50c postpaid, direct from factory.) **KT-33 Speaker Kit.** Net only \$80.00. **KT-233 TWINKIT*** Two matched systems for stereo. Net Only \$160.00.




KDF-1 2-WAY SPEAKER SYSTEM KIT

For fine sound at minimum cost, Jensen's KDF-1 DUETTE Speaker Kit gives you complete 2-way system performance. When you make your own cabinet or built-in speaker system and install the KDF-1 Kit you'll save and get the same fine performance of the DF-1 DUETTE furniture model. Includes P8-QF 8-inch FLEXAIR woofer, enclosure vent-tube, P35-VAH tweeter, coupling element, terminal panel, H-F control, wiring material and complete instructions for building enclosure. Net only \$29.75.

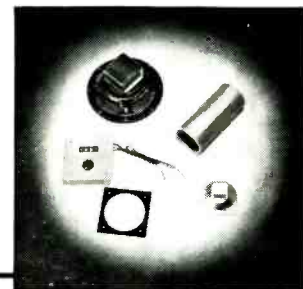

BASIC
ENCLOSURE
DATA

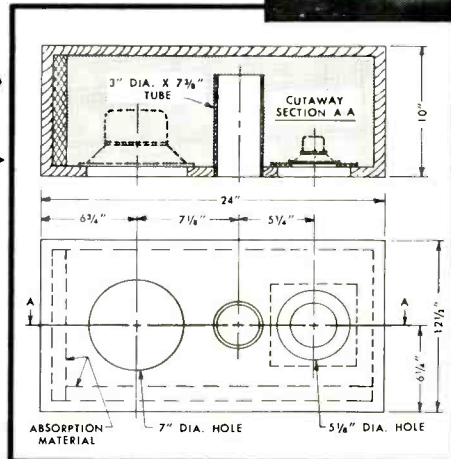ALL JOINTS MUST BE AIR TIGHT
USE 3/4" PLYWOOD THROUGHOUT



Jensen MANUFACTURING COMPANY

Division of The Muter Company

6601 S. Laramie Avenue • Chicago 38, Illinois
In Canada: Renfrew Electric Co., Ltd., Toronto
In Mexico: Radios Y Television, S.A., Mexico, D.F.

*T.M.



TD-124
Turntable **\$99.75 net.**
(Base only \$9.00)

A pleasure to buy...

Thorens has thought of many ways to make buying a Thorens TD-124 a distinct pleasure. A Thorens franchised dealer is a man of broad knowledge and ability, can command your immediate respect, That's why there aren't too many of them. The service *after* you buy is just as important as the initial sale. You get an almost unheard of full one year guarantee. All this in addition to "music as it's meant to be heard." See your Thorens dealer tomorrow . . . you're in for a real treat.



THORENS

Guaranteed for one full year. Sold only through carefully selected franchised dealers.

SWISS MADE PRODUCTS HI-FI COMPONENTS • MUSIC BOXES
SPRING-POWERED SHAVERS • LIGHTERS • New Hyde Park, New York

MARCH, 1960

a continuing pleasure to own!

No other turntable combines all these features. The Thorens TD-124 gives you . . .

- 4 speeds—plays any record you have or can buy.
- Easy-to-use illuminated strobe lets you set exact record speed for best musical reproduction while record is playing.
- Extra heavy table (11½ lbs.) for extra smooth running . . . includes light-weight aluminum cueing table.
- Built-in level with easy-to-get-at fingertip control.
- Easy arm installation or change.
- Motor operates on 50/60 cps, any voltage from 100 to 250.

This isn't all . . . when you see it, you'll agree that this is the turntable you've been waiting for.

0.1



MARCH, 1960

Radio-Electronics

Formerly RADIO-CRAFT ■ Incorporating SHORT WAVE CRAFT ■ TELEVISION NEWS ■ RADIO & TELEVISION*

EDITORIAL

- 33 Brain an Electric Computer—David Stafford-Clark

RADIO

- ✓ 34 Small-Boat Radiotelephones—Elbert Robberson
- 38 Miniature Front End for FM Receivers—E. D. Lucas, Jr.
- 39 FM Sensitivity Switches
- ✓ 40 Build This Transistor Auto Radio—A. V. J. Martin

WHAT'S NEW

- 43 Pictorial Reports of New Developments

AUDIO-HIGH FIDELITY

- 44 Turntables and Pickup Arms Built from Kits—Charles B. Graham
- 46 Cityrama—Multilingual Tourist Bus
- 47 New Developments in Audio Circuits—Robert F. Scott
- 49 Lows Are Directional Too
- ✓ 50 How Valid Are Speaker Response Curves—George L. Augspurger
- 54 Design Your Own Preamp, Part III—Norman H. Crowhurst
- 56 Feed TV Audio Into Hi-Fi Systems—George B. Leonard
- 57 New Discs and Tapes, Stereo and Mono—Reviewed by Chester L. Santon

INDUSTRIAL ELECTRONICS

- ✓ 58 Electronics Controls Level of Molten Glass—Murray Barlowe
- 59 How Leak Detectors Work
- 60 Audio Generator for Industrial Service Jobs—William F. Kernin
- 62 Photoelectric Control Made Easy—R. L. Winklepleck

TEST INSTRUMENTS

- 63 Universal 2-Terminal Oscillator—Paul S. Lederer
- 64 That Versatile Electron-Ray Tube—John Potter Shields
- 66 Mini-capacitance Test Set—David Stone
- 71 Handy Cable Checker—Warren J. Smith

ELECTRONICS

- 72 Electronic Flare Flashes Warning Signals—Edwin N. Kaufman
- 74 What's With Characteristic Impedance—Robert G. Middleton
- 76 Electronics in the Classroom—Sol D. Prensky
- ✓ 89 How To Make Solar Cells—D. M. Chapin

TELEVISION

- 95 Licking the Intermittents—Lyman E. Greenlee
- 109 How to Retouch, Repair, Refinish Cabinets—Jeff Markell
- 114 TV Service Clinic—Conducted by Jack Darr

- 140 Business and People
- 18 Correspondence
- 146 New Books
- 144 New Literature
- 128 New Patents
- 119 New Products
- 130 New Tubes and Semiconductors
- 6 News Briefs
- 136 Noteworthy Circuits
- 124 Technicians' News
- 142 Technotes
- 133 Try This One
- 132 50 Years Ago

RADIO-ELECTRONICS is indexed in *Applied Science & Technology Index* (Formerly *Industrial Arts Index*)

RADIO-ELECTRONICS, March, 1960, Vol. XXXI, No. 3. Published monthly at Mt. Morris, Ill., by Gernsback Publications, Inc. Second-class postage paid at Mt. Morris, Ill. Copyright 1960 by Gernsback Publications, Inc. All rights reserved under Universal, International and Pan-American Copyright Conventions.

SUBSCRIPTION RATES: U.S., U.S. possessions and Canada, \$4.00 for one year; \$7.00 for two years; \$10.00 for three years. Pan-American countries \$5.00 for one year; \$9.00 for two years; \$13.00 for three years. All other countries \$5.50 a year; \$10.00 for two years; \$14.50 for three years.

SUBSCRIPTIONS: Address correspondence to Radio-Electronics, Subscription Dept., 154 West 14th St., New York 11, N.Y. When requesting a change of address, please furnish an address label from a recent issue. Allow one month for change of address.

GERNSBACK PUBLICATIONS, INC. Executive, Editorial and Advertising Offices, 154 West 14th St., New York 11, N.Y. Telephone ALgonquin 5-7755. Hugo Gernsback, Chairman of the Board; M. Harvey Gernsback, President; G. Aliquo, Secretary.

BRANCH ADVERTISING OFFICES and FOREIGN AGENTS listed on page 149.

POSTMASTER: If undeliverable, send Form 3579 to: RADIO-ELECTRONICS, 154 West 14th St., New York 11, N.Y.

ON THE COVER

(Story on page 44)

Parts of ten kit arms and turntables arranged by Art Director Ehrlich into an interesting abstraction. Components arm is center; Audax left; Gray right. Upper right motor used in Gray, Rek-O-Kut tables; motor below it is Weathers.

Color original by Habershaw Studios

- Hugo Gernsback Editor and Publisher
- M. Harvey Gernsback Editorial Director
- Fred Shunaman Managing Editor
- Robert F. Scott W2PWG, Technical Editor
- Larry Steckler Associate Editor
- Charles B. Graham Associate Editor
- I. Queen Editorial Associate
- Elizabeth Stalcup Production Manager
- Wm. Lyon McLaughlin Tech. Illustration Director
- Sol Ehrlich Art Director
- Fred Neimast Staff Artist
- Lee Robinson Director, Advertising Sales
- John J. Lamson Eastern Sales Manager
- G. Aliquo Circulation Manager
- Adam J. Smith Director, Newsstand Sales
- Robert Fallath Promotion Manager



Average Paid Circulation
Over 187,000



*Trademark registered U. S. Pat. Office.

RADIO-ELECTRONICS

NOW!
at a price
you can afford!

MAKE MORE MONEY in TELEVISION RADIO-ELECTRONICS

**BETTER...MORE COMPLETE...LOWER COST...
WITH NATIONAL SCHOOLS' SHOP-METHOD
HOME TRAINING!**

BETTER... Training that is proved and tested in Resident School shops and laboratories, by a School that is the **OLDEST** and **LARGEST** of its kind in the world.

MORE COMPLETE... You learn **ALL PHASES** of *Television-Radio-Electronics*.

LOWER COST... Other schools make several courses out of the material in our **ONE MASTER COURSE** . . . and you pay more for less training than you get in *our course* at **ONE LOW TUITION!**



These two **FREE** books will show you how!

You get all information by mail . . . You make your own decision . . . at home! **NO SALESMAN WILL CALL**

TOP PAY... UNLIMITED OPPORTUNITIES LIFETIME SECURITY CAN BE YOURS!

You are needed in the Television, Radio, and Electronics industry! Trained technicians are in growing demand at excellent pay—in **ALL PHASES**, including Servicing, Manufacturing, Broadcasting and Communications, Automation, Radar, Government Missile Projects.

NATIONAL SCHOOLS SHOP-METHOD HOME TRAINING, with newly added lessons and equipment, trains you in your spare time at home, for these unlimited opportunities, including many technical jobs leading to supervisory positions.

YOU LEARN BY BUILDING EQUIPMENT WITH KITS AND PARTS WE SEND YOU. Your National Schools course includes thorough *Practical* training—**YOU LEARN BY DOING!** We send you complete standard equipment of professional quality for building various experimental and test units. You advance step by step, perform more than 100 experiments, and you build a complete TV set from the ground up, that is yours to keep! A big, new TV picture tube is included at no extra charge.

EARN AS YOU LEARN. We'll show you how to earn extra money right from the start. Many of our students pay for their course—and more—while studying. So can you!

LESSONS AND INSTRUCTION MATERIAL ARE **UP-TO-DATE, PRACTICAL, INTERESTING.** Every National Schools Shop-Method lesson is made easy to understand by numerous illustrations and diagrams. All instruction material has been developed and tested in our own Resident School Shops, Laboratories and Studios.

SEND FOR INFORMATION TODAY . . . it can mean the difference between **SUCCESS** and failure for you! Send for your **FREE BOOK** "Your Future in Television-Radio-Electronics" and **FREE Sample Lesson.** Do it **TODAY**, while you are thinking about your future. It doesn't cost you anything to investigate!

GET THE BENEFITS OF OUR OVER 50 YEARS EXPERIENCE

Approved for
GI Training



NATIONAL SCHOOLS

Los Angeles 37, Calif.

YOU GET...

- 19 Big Kits—**YOURS TO KEEP!**
- Friendly Instruction and Guidance
- Job Placement Service
- Unlimited Consultation
- Diploma—Recognized by Industry
- **EVERYTHING YOU NEED FOR SUCCESS!**

SHOP-METHOD HOME TRAINING COVERS ALL PHASES OF INDUSTRY

1. Television, including Color TV
2. Radio AM & FM
3. Electronics for Guided Missiles
4. Sound Recording and Hi-Fidelity
5. FCC License
6. Automation and Computers
7. Radar & Micro-Waves
8. Broadcasting and Communications

RESIDENT TRAINING AT LOS ANGELES

If you wish to take your training in our Resident School at Los Angeles, the world's TV capital, start **NOW** in our big, modern Shops, Labs and Radio-TV Studios. Here you work with latest Electronic equipment - - professionally installed - - finest, most complete facilities offered by any school. Expert, friendly instructors. Personal attention. Graduate Employment Service. Help in finding home near school - - and part time job while you learn. Check box in coupon for full information.

NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1905

MAIL NOW TO
NATIONAL TECHNICAL SCHOOLS, Dept. R5-30
4000 S. FIGUEROA ST. LOS ANGELES 37, CALIF.
Rush free TV-Radio "Opportunity" Book and sample lesson. No salesman will call.

NAME _____ AGE _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____
 Check if interested **ONLY** in Resident School training at Los Angeles.
VETERANS Give date of Discharge _____

News Briefs

Machine Talks Back

A computer at the University of Toronto conversed about the weather with a human after being fed a 300-word vocabulary and 350 "frame" sentences, each with spaces left for key word fill-ins.

After being told at the beginning of the conversation that it was cloudy, the machine was later told by the man that it was a clear day. The IBM 650 computer answered at that point, "Let me have no lying. It becomes none but tradesmen. How can overcast weather and the clear day you mention coexist?"

[*Pravda* speaking?—Editor]

Experts predict that within 10 years these machines will be so skilled in conversation that no outsider will be able to detect whether a machine or a human is composing the answers.

Thermoplastic Recording

A revolutionary recording method developed by G-E scientist W. E. Glenn combines some advantages of film with the instantaneous playback and reusability of magnetic tape. G-E showed a system recording TV pictures from a standard TV set and played them back through



a device similar to a 16-mm movie projector.

The recording medium is a tape that looks a lot like movie film. It has three layers, an ordinary base on which has been deposited a very thin metallic conducting layer (transparent), and over that a thermoplastic film which melts at relatively low temperatures. This surface is "written on" by an electron gun which scans it horizontally, depositing negative electric charges in accordance with the signal. Film movement, 5 or 10 inches per second, provides vertical scan.

After the tape passes under the electron gun the top layer of the tape is softened instantaneously by an rf heater. The attraction of the negative charges for the grounded or positive conducting layer below now creates ridges and valleys as the negative charges on the surface try to move closer to the opposite charge below. The stronger the charge at any given point the deeper the valley. The plastic hardens quickly, freezing the signal deformations.

The whole recording process takes about 1/100 second, and playback through an optical diffraction grating system is instantaneous. One commercial drawback is that the recording system operates in a vacuum.

Playback may also use a photocell to give an electrical output. With light on the film at the right angle, the recording becomes visible to the eye. A specimen is shown in the photograph here, with a paper clip for scale.

The information-carrying density of the new method is said to be about 100 times as great as that of

equivalent area of magnetic tape.

While G-E officials said, "Considerable work must be still done before commercially practical equipment can be made available for commercial markets," others guessed it would be at least 2 to 5 years before anything practical could be seen.

Boating Electronics Up

If the recent Boat Show at the New York Coliseum is any indication, the well-equipped weekend boatsman will have at least one piece of electronic gear on board this summer. For the small boat with outboard there are portable radiotelephones, all-transistor depth finders (100-foot depth range lets the fisherman find the fish before he drops anchor), radio-direction finders, and Citizens-band radio gear.

The owner of the larger boat has even more to choose from. As well as larger versions of the portable gear for the small boat there are fuel-vapor detection units, rudder-position indicators, converters, battery chargers and electronic automatic pilots.

This upswing in electronic equipment for the boat owner obviously means more service business for the electronic technician.

Transoceanic "Waveguide"?


An elevated atmospheric duct which may carry TV frequencies with little distortion and at low loss has been found to exist at about 5,000 feet over the South Atlantic ocean, according to Air Force and Navy scientists.

Meteorological studies had predicted that such semipermanent atmospheric ducts existed, and results of first experiments not only prove there is one between South America and Africa, but that there are probably others between California and Hawaii, Cape Verde (Africa) and Puerto Rico, and Australia and the Philippines.

Satellite Relay

Balloon satellite try will be made with cooperation of the French Committee for Space Research in an attempt to use a US-launched 100-foot balloon as a reflector to beam high-frequency signals between US and France. It is now anticipated that this first attempt will place the artificial satellite about 600 miles above the earth. (See also RADIO-ELECTRONICS, December, 1959, pages

(Continued on page 10)

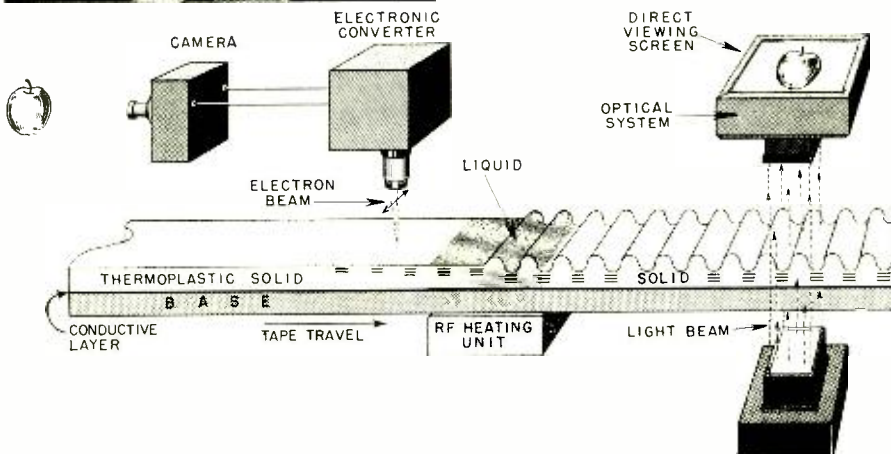



**The Man
who works with
His Hands..**

MEN 17-55



Has a Real Advantage When Preparing for
MONEY! EXCITEMENT! JOBS!
in
Electronics

**FROM RADAR-TV . . . TO GUIDED
MISSILE CONTROL
ETC.**



Machine Operator



Gas Station Attendant



Stock Clerk



Soda Clerk



Laborer



Farmer

IS YOUR PRESENT JOB LIKE THESE?

You may have just the skill needed to train for a real job in Electronics!

"One of North America's Foremost Electronics Training Centers"
Accredited Member of National Home Study Council



EMPLOYMENT SERVICE
Helps graduates get started toward a good job or their own service shop.

DeVRY TECHNICAL INSTITUTE
CHICAGO • TORONTO

You run a punch press, drive a tractor, work at a gas station. Or, maybe you can make home repairs, wire an electric appliance, or tune your car. You work with your hands. So did Thomas Edison and many other famous men. Artists, engineers, surgeons—all "work with their hands"—and so do Electronics Technicians! So, by all means, be proud of your "hand skills!"

DeVry Tech readily prepares men who use their hands for good-paying careers in the fast-growing Electronics field by sending 16 shipments of quality parts for building their own valuable test equipment. They work over 300 projects with these parts while they learn important basic theory. They learn in spare time at home, or in our well-equipped training centers in Chicago or Toronto. Many earn money part time repairing TV and radio sets while still training! When they finish, we help them get started.

NO ADVANCED EDUCATION NEEDED!

DeVry Covers What You'll Need to Know

2 FREE Booklets

Send coupon TODAY!



If you can understand clearly-written instructions, work with equipment, run training movies in your home, you surely can train for a profitable future in Electronics. ACT NOW to find out. Send for two fact-filled booklets that have helped so many men get started toward the kind of careers they wanted.

DeVRY TECHNICAL INSTITUTE
4141 Belmont Ave., Chicago 41, Ill., Dept. EE-1Q

Please give me your two FREE booklets, "Pocket Guide to Real Earnings" and "Electronics in Space Travel." Also, include details on how to prepare for a career in one or more branches of Electronics.

Name _____ Age _____

Street _____ Apt. _____

City _____ Zone _____ State _____

Check here if you face military service.

Canadian residents write DeVry Tech of Canada, Ltd.,
2072 626 Roselawn Ave., Toronto 12, Ont.

GET THAT SYLVANIA SIGN UP TODAY!

ARTHUR GODFREY IS SELLING YOU!

Now sponsored by Sylvania Silver Screen 85 picture tubes, Arthur Godfrey is selling America on you – the independent TV service dealer!

He's telling millions – on the CBS Radio network – coast-to-coast – that you are the man to see for the finest TV service. Millions more are reading about you in *The Saturday Evening Post*. When Arthur Godfrey tells folks to “look for the Sylvania decal in the window of your local independent TV service dealer’s shop,” make sure you’re with it.

See your Sylvania distributor for Sylvania Silver Screen 85 picture tubes and Sylvania quality receiving tubes. Get your display kit of window streamers and posters. Get that sign up today!

*Electronic Tubes Division, Sylvania Electric Products Inc.,
1740 Broadway, N. Y. 19, N. Y.*



**SYLVANIA
SILVER SCREEN 85
4 WAYS BETTER**

- * Sharper focus
- * Clearer picture
- * Greater contrast
- * More light output



See your local paper for time and station

“IT’S ARTHUR GODFREY TIME” – brought to you by

 **SYLVANIA**

Subsidiary of **GENERAL TELEPHONE & ELECTRONICS** 

“I Teach MATH a Funny Way”

— says DR. AARON BAKST, distinguished mathematician and lecturer at New York University.

An Amazing New Way To Master Every Phase of Mathematics—The Key To a Better Job, Higher Pay, Security In Today's Technical Age

THE NEW YORK TIMES says of Dr. Bakst's method: "A rich dish, well-stocked with parlor tricks and ingenious problems ... a new trend toward the humanization of mathematics."

PARTIAL CONTENTS of this 791-Page Book

Short Turns in Long Division
Fractions Without Denominators
The Game of 999
Properties of Numbers
Repeated-Digit Bafflers
The Other Side of Zero
Secret Codes with Numbers
The Great Pyramid Mystery
Simple Calculating Devices
A Home-Made Abacus
Multiplication Made Painless
Remember that Phone Number
The Number Magician's Secret
Algebra Magic
Why the Rich Get Richer
Arithmetic Sequences for Rabbits
Logarithm Declares a Dividend
Streamlining Everyday Computations
How to Figure the Odds
Unsquaring the Square
The Triangle —
 Servant and Master
Measuring Heights with a Mirror
The Secret of the Sphinx
Trig without Tables
Squashing the Rectangle
How to Wrap a Circle
Cutting Corners From a Triangle
The Shortest Route on Earth
Cork-screw Geometry
Mathematics on the Rifle Range
Systems of Numeration
Number Giants
The Gogolplex
Sherlock Holmes Arithmetic
The Math-Minded Mother-in-Law
Algebra and Common Sense
How to Buy on Installments
Fun with Lady Luck
Passport for Geometric Figures
200 Men and an Egg
Math — Key to the Universe
Math and Magic

DR. BAKST'S "funny way to teach math" cuts out the learning and memorizing of rules and formulas. In 791 fascinating pages his book *Mathematics: Its Magic and Mastery*, uses entertaining puzzles, games and tricks to simplify and humanize math for the average person.

Even if you never finished high school math, you'll find this book easy to follow. It explains every basic step in mathematics; shows how to solve all sorts of problems, from adding up everyday bills to short-cut ways of operating giant electronic calculators. And even Einstein's theory of relativity is explained so simply that any layman can readily understand it.

**Unsquaring the Square;
How to Figure the Odds;
The Great Pyramid Mystery;
The Game of 999**

These and scores of other intriguing solutions to problems (see partial table of contents at left) quickly give you a good grasp of advanced arithmetic, algebra, geometry, and trigonometry.

You learn by *doing*, not by studying. And what you do is made so absorbing that you'll thoroughly enjoy each single "treasure hunt" episode with this

gifted mathematician and writer.

Today's Stress on Math

In today's world of science, automation, engineering, and automatic computing, a good knowledge of all phases of mathematics will help *anyone* to advance himself faster and farther. In fact, it is an absolute essential in many fields, for reaching the top positions.

Dr. Bakst's book assures that your new knowledge of math will be of *practical* value to you — because he applies its principles to home life, insurance, business, finance, scientific and managerial problems.

**SEND NO MONEY
Examine it FREE for 10 days**

There is no need to send any money now. The coupon will bring you this 791-page book for 10 days' free trial. If not convinced that it brings you an interesting and practical way to gain a knowledge of mathematics which will be of great value to you, return it and owe nothing. Otherwise you may keep it by sending us only \$1.50 down and the balance in easy payments. Mail the coupon NOW.

**D. Van Nostrand Company, Inc.,
Dept. 183A, Princeton, N. J.
(Established 1848)**

FREE EXAMINATION COUPON

**D. VAN NOSTRAND COMPANY, INC., DEPT. 183A,
120 ALEXANDER STREET, PRINCETON, N. J.**


Please send—for ten days free examination Dr. Aaron Bakst's MATHEMATICS: ITS MAGIC AND MASTERY. Within ten days I will either return the book or send you \$1.50 as first payment and only \$2.00 per month for three months until the total price of \$7.50, plus a small shipping cost, is paid.

PRINT NAME.....

ADDRESS.....

CITY.....ZONE.....STATE.....

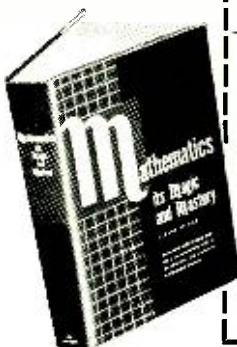SAVE: Check here if you are enclosing \$7.50 WITH this coupon. Then WE will pay all shipping costs. Same return privilege; refund guaranteed.
(In Canada: Address 25 Hollinger Road, Toronto 16, Canada. Price slightly higher.)



**A WHOLE LIBRARY IN ONE
GIANT 791-PAGE VOLUME**

10, 54, and March, 1958, pages 33, 125.)

Figures Camera Angles

TV bloopers can be eliminated for under a third of a million dollars (in case you own a TV station) by installing three videotape recorders altered to incorporate a time-delay scheme similar in many respects to the tape loop used in some setups to produce audio echoes.

An electrical engineer, H. H. Hume, of Brooklyn, N. Y., has patented a system which would record views from two or three cameras on videotapes, give the TV directors several seconds in which to choose the best camera angle to present to viewers or, if necessary, cut the program off the air before objectionable material is transmitted.

Mr. Hume worked out the scheme because he was a Dodger baseball fan (when the team was in Brooklyn, anyhow) who was annoyed at missing the fast throw to third when the TV cameraman thought it was going to first!

Educational Stratovision

Stratovision plan got official FCC approval to operate from a base at Purdue University, Indiana, for the school year 1960-61, with experimental TV transmissions via airplane relay. Described in RADIO-ELECTRONICS, December, 1959, and October, 1945, the plan calls for beaming programs to a circling plane on unused TV channels, for rebroadcasting to a ground area with a radius of about 150-200 miles.

Two simultaneous transmissions of the educational programs will be made to compare the results using a 6-mc bandwidth with 3 mc. Ten schools will be set up with regular and narrow-band receivers for the 1-year test period. Transmitters on the ground and in the DC-7 will use peak power of 12 kw.


New Voice for America

Almost 5 megawatts will be the total transmitter power for the Voice of America's consolidated East Coast facilities to be started near Greenville, N. C., soon. Two mammoth transmitter installations and a receiving station will be spaced around an 18-mile triangle to eliminate mutual interference.

Several presently scattered VOA installations will be concentrated at Greenville to beam programs overseas with six 500-kw, six 250-kw and 10 lesser-powered transmitters. They'll use almost a hundred rhombic, curtain and log periodic antennas requiring 400 towers from 50 to 375 feet high.

Electronics Goes Fishing

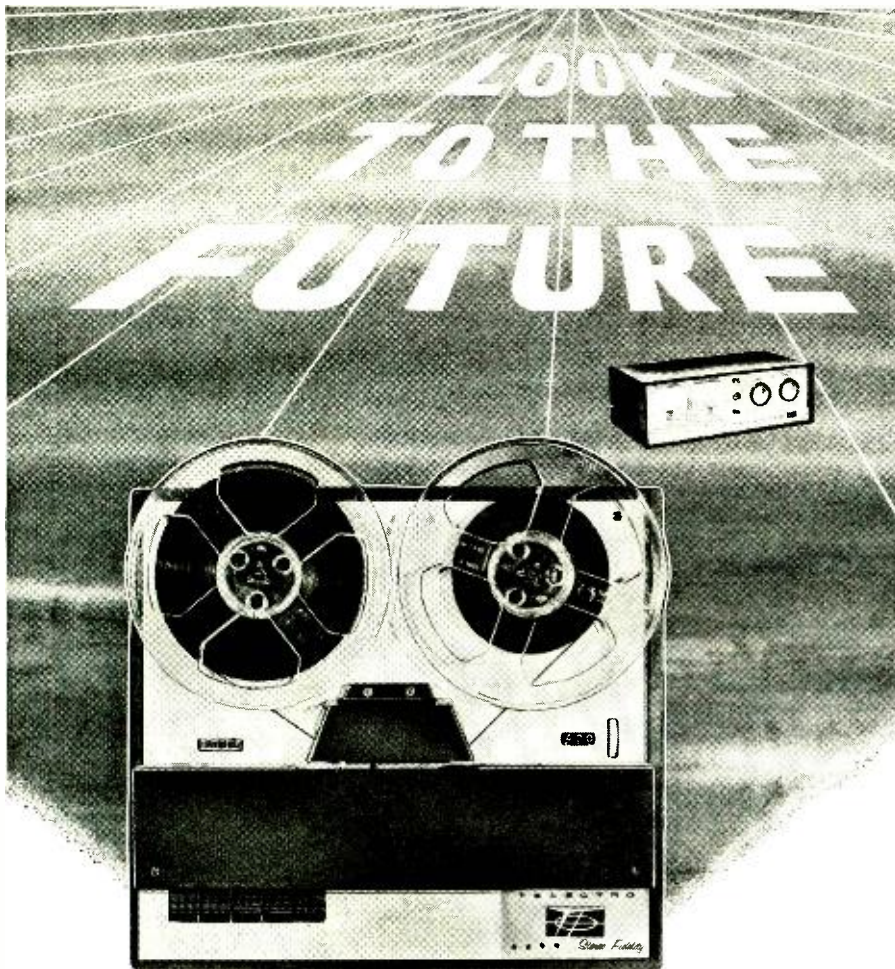Going fishing will be even less work in the future, due to electronics which attract fish into a large tube



Experts agree that repeated playings will soon deteriorate the total quality of a disc recording. Yet, fifteen, fifty, five hundred playings from now, you can still enjoy the same sweet, clean highs, the same rich velvety lows that you cherished in your recordings today.

How? By recording your favorite music on a

TELECTRO SERIES 900 STEREO TAPE DECK

Telectro's low, low price . . . as low as **\$89.95** . . . makes tape recording your most economical as well as your most satisfactory program source. Yet, in spite of its low price, a Telectro tape deck offers the quality and versatility demanded by the finest monaural and stereophonic high fidelity systems.

CHECK THESE TOP QUALITY FEATURES

- 4-track head for all stereo and monaural tapes • Interchangeable head assemblies
- Stereo and monaural record/playback • Unique pushbutton controls • 3 speed versatility: 7½ ips, 3¾ ips, and the extra convenience of ultra long-play 1½ ips • Solenoid-operated automatic shutoff
- Digital tape counter • Rotary speed selector for easy speed choice • Unique brake design permits easy reel rotation • Fast wind—fast rewind, with no spillage or breakage
- Pushbutton interlocks fulfill professional requirements.

Make your high fidelity system complete with a stereo tape deck by

TELECTRO



a product of **TELECTROSONIC CORPORATION**
35-18 37th St., Long Island City 1, N. Y.

Ask to see the five great TELECTRO tape decks and the complete line of Telectro design-mated tape preamplifiers at your high fidelity dealer, or write for full information Dept.



FREE

tells how

Get your FCC Commercial License —or your money back

The Master Course in Electronics will provide you with the mental tools of the electronics technician and prepare you for a First Class FCC License (Commercial) with a radar endorsement. When you successfully complete the Master Course if you fail to pass the FCC examination, you will receive a full refund of all tuition payments.

EFFECTIVE
JOB FINDING
SERVICE HELPS CIRE
TRAINEES GET
BETTER JOBS

"License and \$25 raise due to Cleveland Institute Training"

"I sat for and passed the FCC exam for my second class license. This meant a promotion to Senior Radio Technician with the Wyoming Highway Department, a \$25 a month raise and a District of my own for all maintenance on the State's two-way communication system. I wish to sincerely thank you and the school for the wonderful radio knowledge you have passed on to me. I highly recommend the school to all acquaintances who might possibly be interested in radio. I am truly convinced I could never have passed the FCC exam without your wonderful help and consideration for anyone wishing to help themselves."

CHARLES C. ROBERSON
Cheyenne, Wyoming

HERE'S PROOF
FCC LICENSES
ARE OFTEN SECURED
IN A FEW HOURS
WITH OUR
COACHING

Name and Address	License	Time
John H. Johnson, Boise City, Okla.	1st	20 weeks
Prentice Harrison, Lewes, Delaware	1st	27 weeks
Herbert W. Clay, Phoenix, Arizona	2nd	22 weeks
Thomas J. Bingham, Finley, North Dakota	2nd	9 weeks
William F. Masterson, Key West, Fla.	2nd	24 weeks

EMPLOYERS
MAKE JOB OFFERS
LIKE THESE TO OUR
GRADUATES EVERY
MONTH

Employers Make Job Offers Like These To Our Graduates Every Month

Broadcast Station in Illinois: "We are in need of an engineer with a first class phone license, preferably a student of Cleveland Institute of Radio Electronics; 40 hour week plus 8 hours overtime."

West Coast Manufacturer: "We are currently in need of men with electronics training or experience in radar maintenance. We would appreciate your referral of interested persons to us."

Cleveland Institute of Electronics
RE 39 B, 4900 Euclid Bldg., Cleveland 3, Ohio

Your FCC Ticket is recognized by employers as proof of your technical ability.

Accredited by
National Home Study
Council



Please send Free Booklets prepared to help me get ahead in Electronics. I have had training or experience in Electronics as indicated below:

Military Amateur Radio Telephone Company
 Radio-TV Servicing Broadcasting Other
 Manufacturing Home Experimenting


In what kind of work are you now engaged?

In what branch of Electronics are you interested?

Name Age Address

City Zone State

RE 39B

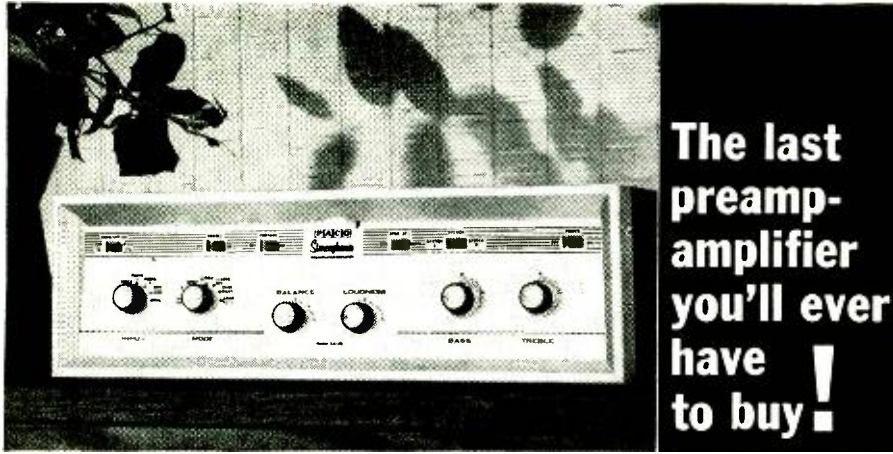

**The last
preamp-
amplifier
you'll ever
have
to buy!**

*A new
40-watt
stereo
preamp-amplifier
in kit form
for only
\$79.95
by
PACO*

*also
available
factory wired
for \$129.95*

*Ask your own
Audio-Radio-TV
Serviceman about
PACO and PRECISION
products. He'll tell you that
they always live up to their
specs. That's why we can
say that the PACO SA-40
is the last preamp-amplifier
you'll ever have to buy*

*Available at leading electronic
parts distributors and
wherever good sound is sold.*

*For complete information
write to:*

PACO

*Electronics Co., Inc.
70-31 84th Street
Glendale 27, L. I., N. Y.*

*A Division of
PRECISION
Apparatus Company, Inc.*

*Export:
Morhan Exporting Corp.
458 Broadway
N. Y. 13, N. Y., U.S.A.*

*Canada:
Atlas Radio Corp., Ltd.
50 Wingold Ave.
Toronto 19, Ontario*

PACO is the kit division of **PRECISION** Apparatus Co., Inc., world famous manufacturers of laboratory electronic instruments for over a quarter century. The new Model SA-40 is the first of a series of component high fidelity kits from PACO...engineered for utmost performance and lasting value—designed for maximum eye-appeal.

Whether you're an experienced audiophile or a newcomer to the thrill of high fidelity, the factors you must consider in choosing the amplifier you need are: **POWER, DISTORTION, FLEXIBILITY and VALUE.**

The PACO SA-40 offers you greater reserve power capacity than any other preamp-amplifier in its category. Its exceptional circuit design assures highly stable performance with extremely low distortion. Step-by-step assembly instructions and giant-size wiring diagrams are so clearly detailed and simple that the technical difference between expert and novice disappears. And...the SA-40 provides maximum flexibility in any stereophonic high fidelity system...present or contemplated.

For those interested in engineering details, some of the more important technical specifications are listed below:

POWER OUTPUT:

Steady State Power Output: 20 watts per channel, 40 watts total.

Music Waveform Power Output: 25 watts per channel, 50 watts total.

Peak Power Output: 40 watts per channel, 80 watts total.

RESPONSE: 30 cps to 90 Kc, ± 1.0 db.

DISTORTION:

Harmonic: Less than .2% at 20 watts per channel output. Less than .1% at 10 watts per channel output.

Intermodulation: Less than 1% at full rated output.

FRONT PANEL CONTROLS AND SWITCHES: 14 controls including separate bass and treble controls for complete flexibility with any monophonic or stereo program source.

INPUTS: 14 total; 3 dual high-level and 4 dual low-level.

OUTPUTS: Dual tape outputs, separate preamp output as well as standard dual speaker outputs.

HUM AND NOISE LEVEL:

High Level Input: 80 db below rated output.

Low Level Input: 70 db below rated output.

Tape Input: 65 db below rated output.

SPEAKER CONNECTIONS: 4, 8, 16, 32 ohms.

SENSITIVITY FOR RATED OUTPUT:

Aux Input: .75 V Phono 1: (Magnetic) 5 Mv.

Tuner: .75 V Phono 2: (Magnetic) 5 Mv. or Ceramic. 3V

INVERSE FEEDBACK: 25 db

DAMPING FACTOR: 22

BASS TONE CONTROL RANGE: ± 15 db at 50 cps.

TREBLE TONE CONTROL RANGE: ± 15 db at 10 Kc.

RUMBLE FILTER: 6 db per octave below 50 cps.

EQUALIZATION: Phono: "RIAA"; "EUR";

Tape: 3/4 and 7/8 ips, NARTB

TAPE OUTPUT LEVEL: 2 volts per channel.

POWER SUPPLY: Silicon diode, low impedance for minimum distortion on extended high level passages.

EXTERNAL DESIGN: Gold and satin black hooded case, with panel illumination and satin gold panel.

DIMENSIONS: 15 1/2" wide x 11 3/4" deep x 5 3/8" high

Model SA-40: Complete with case and step-by-step assembly-operating manual **Kit Net Price \$ 79.95**

Model SA-40W: Factory Wired **Net Price \$129.95**

**NOW AVAILABLE—MODEL ST-45
AM/FM STEREO TUNER KIT
matching companion
for the SA-40**



lowered into the water. A few kilowatts of current are pulsed periodically, pulling in all fish within a 10-yard radius. A light is used to attract them from greater distance.

So far, herring and sardines have been caught with the equipment on trawlers in the North Sea. It's been found that different kinds of fish respond to different voltages. Work was done by Herr J. Dethloff, director of the International Electronics Laboratories, Hamburg, Germany.

New Radar Has Long Reach

Long range radar MADRE uses *M*agnetic *D*rum *R*eceiving *E*quipment to preserve transmitted pulses, compare them with returning pulses to extend radar range out to 500 to 2,600 miles, depending on atmospheric conditions.

Low frequencies (3-30 mc) and relatively low powers averaging only 100 kw are beamed by huge fixed antennas, a typical one being 330 feet long and 150 feet high.

Mars Technical Net

Schedule for March will present "Transistorized Test Equipment for the Amateur Station," Bob Gundersen, W2JIO, Braille Technical Press—March 2; "Fundamental Requirements for Military SSB Receiver Design," Dudley Kahn, Signal Corps—March 9; "Low Noise Preampifiers," Dr. James W. Meyer, MIT Lincoln Labs—March 16; "Fundamentals of Single Sideband and Some Commercial Practice," S. Edwin Piller, Radio Engineering Labs—March 30.

The First Army MARS (Military Affiliate Radio System) SSB Network passed its second birthday in January this year. The net operates in the northeastern part of the United States.

Two TV Starters

Two new TV stations started with the new year:

KDSJ-TV, Deadwood, S. D..... 5

KNBS, Walla Walla, Wash.....22

KDSJ-TV is a satellite of KRSD-TV, Rapid City, S. D., channel 7.

There were two changes in call letters:

KCPX-TV, Salt Lake City,

Utah 4

(formerly KTVT)

KVER-TV, Clovis, N. M.....12

(formerly KICA)

The US tally of operating stations is up to 567, including 474 vhf and 93 uhf. The noncommercial figure remains 43.

Canada has opened its third French-language outlet:

CBAFT, Moncton, N. B.....11

Its total thus moves up to 59.

Improved Radar

River radar requirements have produced improved short-range radars with seven graduated ranges,



1. Also: Let It Rain, Stairway to the Sea, Flame of Love, etc.

STEREO RECORDS
for every musical taste!



5. A Night on Bald Mountain, Steppes of Central Asia, etc.



6. Bess, You Is My Woman Now; It Ain't Necessarily So; etc.



17. Over the Rainbow, Night and Day, Easy to Love, 9 more



34. "...the music is all extraordinary" — Boston Daily Record



33. This brilliant musical painting is an American classic




10. A brilliant new performance of this popular concerto



13. But Not for Me, Fascinating Rhythm, Man I Love, 9 more



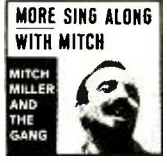2. 1001 hi-fi delights. "...top-notch sound" — Billboard



9. Sweet Adeline, For Me and My Gal, Pretty Baby, 13 more



15. An exciting array of 16 classical and popular selections



18. Rain in Spain, I Could Have Danced All Night, etc.

COLUMBIA RECORD CLUB offers new members


ANY SIX

of these 12" long-playing STEREO records

FOR ONLY \$4.98

Retail Value up to \$35.88.

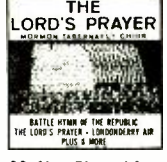
if you join the Club now and agree to purchase as few as 5 selections from the more than 150 to be made available during the coming 12 months



11. Also: Blessed Are They That Mourn, Come Ye Saints, etc.



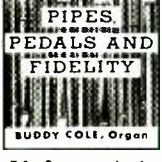24. "Musical excitement that's hard to beat" — Variety




56. Serenade in Blue, Willow Weep for Me, 9 others



3. Stella by Starlight, Pacific Sunset, Yes-terdays, 9 others



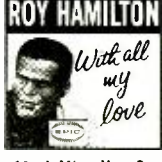25. Superbly played by one of Europe's finest orchestras




40. I Miss You So, Speak Low, Time After Time, 9 more



36. A musical landscape. "...spacious, noble" — High Fidelity



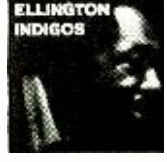26. Blue Moon, Fools Rush In, Don't Worry 'bout Me, 9 more



47. Solitude, Where or When, Dancing in the Dark, 5 more



49. One of the most melodically beautiful of all symphonies



30. Alexander's Ragtime Band, Cheek to Cheek, Always, etc.



19. Tales from the Vienna Woods, Blue Danube, 8 others



12. Londonderry Air, Shenandoah, 11 more folksong favorites




22. "Enormous talent and technique" — Chicago News



4. Wild Man Blues, Fine and Mellow, I Left My Baby, 5 more



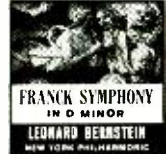37. "Most exciting recording of this work" — Time



14. "No symphony like it... incomparable" — Olin Downes



7. One Kiss, Will You Remember, Song of Love, 9 more



29. Three of the Master's favorite chamber works



31. You've Changed, Body and Soul, I Got It Bad, 9 others



35. "One of the great, great albums" — San Francisco Examiner



50. Come to Me, That Old Feeling, Long Ago, 9 more



8. "Beautiful...lingering brilliance" — Chicago Tribune



39. Tico Tico, My Shaw, Besame Mucho, 9 others

AN EXCITING NEW OFFER FROM THE WORLD'S LARGEST RECORD CLUB

If you now own a stereo phonograph, or plan to purchase one in the near future—here is a unique opportunity to obtain ANY SIX of these brand-new stereo records for only \$4.98!

TO RECEIVE 6 STEREO RECORDS FOR \$4.98—fill in and mail the coupon now. Be sure to indicate which one of the Club's two musical Divisions you wish to join: Stereo Classical or Stereo Popular.

HOW THE CLUB OPERATES: Each month the Club's staff of music experts selects outstanding recordings from every field of music. These selections are described in the Club's entertaining Music Magazine, which you receive free each month.

You may accept the monthly selection for your Division, take any other records offered (classical or popular), or take NO record in any particular month.

Your only obligation as a member is to purchase five selections from the more than 150 Columbia and Epic records to be offered in the coming 12 months... and you may discontinue your membership at any time thereafter.

FREE BONUS RECORDS GIVEN REGULARLY: If you wish to continue as a member after purchasing five records, you will receive a Columbia or Epic stereo Bonus record of your choice free for every two selections you buy—a 50% dividend.

The records you want are mailed and billed to you at the regular list price of \$4.98 (Classical and Original Cast selections, \$5.98), plus a small mailing and handling charge.

MAIL THE COUPON TODAY!

NOTE: Stereo records must be played only on a stereo phonograph

SEND NO MONEY — Mail coupon to receive 6 stereo records for \$4.98

COLUMBIA RECORD CLUB, Dept. 212-8
Stereophonic Section, Terre Haute, Indiana

I accept your offer and have circled at the right the numbers of the six records I wish to receive for \$4.98, plus small mailing and handling charge. Enroll me in the following Division of the Club.

(check one box only)

Stereo Classical Stereo Popular

I agree to purchase five selections from the more than 150 records to be offered during the coming 12 months, at regular list price plus small mailing and handling charge. For every two additional selections I accept, I am to receive a 12" Columbia or Epic stereo Bonus record of my choice FREE.

Name..... (Please Print)
Address.....
City..... ZONE..... State.....

ALASKA and HAWAII: write for special membership plan
CANADA: address 1111 Leslie St., Don Mills, Ontario

If you want this membership credited to an established Columbia or Epic record dealer, authorized to accept subscriptions, fill in below:

Dealer's Name.....
Dealer's Address.....

21

© "Columbia," © "Epic," © Marcus Reg. © Columbia Records Sales Corp., 1960

CIRCLE 6 NUMBERS:	
1	31
2	33
3	34
4	35
5	36
6	37
7	39
8	40
9	47
10	49
11	50
12	56

one
word
more
about
the

Amperex®
6CA7/EL34

OUTPUT
PENTODE



NOW ITS RATED POWER OUTPUT IS

60
WATTS
(Class AB₁)

We are pleased to announce that as a result of the further exploration of the 6CA7's capabilities... its power output rating has been raised to 60 watts in a distributed load circuit. This was achieved by increasing the screen grid voltage to 500V. The screen voltage rating now equals the plate voltage rating, thus greatly simplifying the design of power supplies.

Class AB₁ Audio Amplifier Distributed Load Connection Typical Operation
(Fixed Bias—Two Tubes Push Pull)

Plate Supply Voltage.....500 V	Harmonic Distortion2.5%
Grid No. 2 Supply Voltage.....(See Note) 500 V	Plate and Grid No. 2 Current (Max. Signal).....2x112 mA
Grid No. 1 Bias.....(approx.)—44.5 V	Input Signal Voltage (rms)......32 V
Plate to Plate Load Resistance....7000 Ω	Plate and Grid No. 2 Current (Zero Signal)......2x57 mA
Power Output60 W	

NOTE: Screen voltage is obtained from taps located at 43% of the plate winding turns. An unbypassed resistor of 1KΩ in series with each screen grid is necessary to prevent screen overload.




ask **Amperex**

ask your Amperex distributor
about Amperex voltage ampli-
fier, rectifier and output tubes
for hi-fi circuits.

AMPEREX ELECTRONIC CORP.
230 Duffy Avenue, Hicksville, L. I., N. Y.

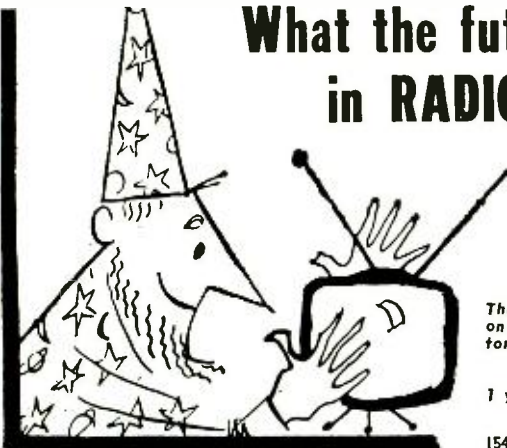What the future holds for you in RADIO-ELECTRONICS



- All Transistor FM Portable
- Photoflash uses Transistors
- Improving the Twin-Coupled Amplifier
- Servicing Horizontal Sweep Circuits
- Simple Pulse Generator
- Adding Sound to 35-mm Slides

The APRIL issue of RADIO-ELECTRONICS goes on sale March 29 at all better parts distributors and newsstands.

SUBSCRIPTION RATES

1 year \$4.00 2 years \$7.00 3 years \$10.00

RADIO-ELECTRONICS

154 West 14th Street New York 11, N. Y.

NEWS BRIEFS (Continued)

the closest of which covers objects at 440 yards. The new Decca radar also has a variable focus control which enables sharpening the picture, or eliminating unwanted "echoes."

Chicago Receiver Meeting

Papers on TV and broadcast receivers are being solicited for the Chicago Spring Conference on Broadcast and Television Receivers, sponsored by the IRE, June 20 and 21. For further information, contact Jack Bridges, Papers Chairman, c/o Warwick Mfg. Co., 7300 N. LeHigh Ave., Chicago 48, Ill.

Calendar of Events

- EIA Spring Conference, Mar. 16-18, Hotel Statler, Washington, D. C.
- IRE National Convention, Mar. 21-24, Coliseum & Waldorf Astoria Hotel, New York, N. Y.
- Nuclear Congress, April 3-8, New York Coliseum, New York, N. Y.
- Conference on Automatic Techniques, April 18-19, Sheraton Cleveland Hotel, Cleveland, Ohio.
- Symposium on Active Networks and Feedback Systems, April 19-21, Auditorium of Engineering Societies Bldg., New York, N. Y.
- Southwest IRE Regional Conference and Electronics Show, April 20-22, Shamrock-Hilton Hotel, Houston, Tex.
- PACE Annual Meeting, April 29-May 1, Nevele Hotel & Country Club, Ellen-ville, N. Y.

Details on all events supplied
by sponsoring organizations.

Breaks 'em up

In merrie England, a TV viewer, John L. McNally of Canterbury, fed up with 2 years of his set acting up constantly took a sledge hammer to the shop where he'd bought his receiver and smashed every set in sight. The judge agreed that he had provocation, but gave him 6 months to cool off anyhow.

John Reinartz Honored

In recognition of more than half a century as an amateur radio pioneer, followed by distinguished contributions to military and commercial communications, a testimonial banquet was tendered to John Reinartz (1QP, 1XAM and K6BJ) on Feb. 1. The testimonial coincided with Reinartz' retirement as manager of the Amateur Service Department of Eitel-McCullough, who sponsored the banquet.

Reinartz, probably one of the greatest American amateurs of all time, was known to millions in the '20's as the inventor of the almost universally used Reinartz shortwave receiver circuit. He was one of the earlier experimenters in high-frequency propagation, and with Leon Dely of France pioneered trans-Atlantic two-way transmissions at 100 meters (3000 kc).

Learn Electronics

PREPARE FOR YOUR F. C. C. LICENSE—YOUR TICKET TO A BETTER JOB AND HIGHER PAY!

F. C. C. LICENSE—THE KEY TO BETTER JOBS

An F.C.C. *commercial* (not amateur) license is your ticket to higher pay and more interesting employment. This license is Federal Government evidence of your qualifications in electronics. Employers are eager to hire *licensed* technicians.

WHICH LICENSE FOR WHICH JOB?

The **THIRD CLASS** radiotelephone license is of value primarily in that it qualifies you to take the second class examination. The scope of authority covered by a third class license is extremely limited.

The **SECOND CLASS** radiotelephone license qualifies you to install, maintain and operate most all radiotelephone equipment except commercial broadcast station equipment.

The **FIRST CLASS** radiotelephone license qualifies you to install, maintain and operate every type of radiotelephone equipment (except amateur) including all radio and television stations in the United States, its territories and possessions. This is the highest class of radiotelephone license available.

GRANTHAM TRAINING PREPARES YOU

The Grantham Communications Electronics Course prepares you for a **FIRST CLASS** F.C.C. license, and it does this by **TEACHING** you electronics. Each point is covered simply and in detail, with emphasis on making the subject easy to understand. The organization of the subject matter is such that you progress, step-by-step, to your specific objective—a first class F.C.C. license.


CORRESPONDENCE OR RESIDENCE CLASSES

Grantham training is available by correspondence or in resident classes. Either way (residence or correspondence), we train you quickly and well—no previous training required. Even a beginner may qualify for his first class license in a relatively short time.

FOUR COMPLETE SCHOOLS: *To better serve our many students throughout the entire country, Grantham School of Electronics maintains four complete Divisions—located in Hollywood, Calif., Seattle, Wash., Kansas City, Mo., and Washington, D.C. All Divisions of Grantham School of Electronics offer the same rapid courses in F.C.C. license preparation, either by home study or in resident classes.*

This booklet

FREE!

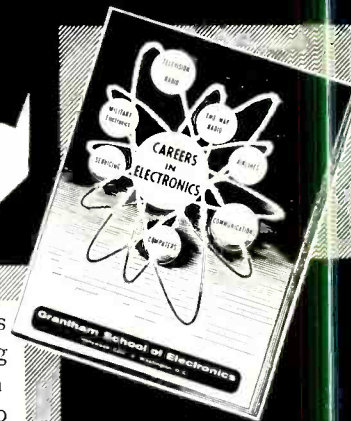

This free booklet gives details of our training and explains what an F.C.C. license can do for your future.

Upgrade Your Income with a First Class F. C. C. LICENSE

HERE'S PROOF...

that Grantham students prepare for F.C.C. examination in a minimum of time. Here is a list of a few of our recent graduates, the class of license they got, and how long it took them:

	License	Weeks
Donald E. Mason, 2659 Centinella, Santa Monica, Calif.....	1st	12
Everett T. Bozard, 411 N. Wash. St., Alexandria, Va.....	1st	12
Henry M. Best, 1003 Vermont St., Fremont, N. C.....	1st	11
Harold V. Jones, P. O. Box 705, Alamogordo, N. M.....	1st	13
Michael F. Aperio, 916 Townsend St., Chester, Pa.....	1st	12
Earl A. Stewart, 3918 Modesto Dr., San Bernardino, Calif.....	1st	14
Donald L. Leebug, Box 1075, Anchorage, Alaska.....	1st	12
J. Milton Condit, 1312 N. 78th Street, Seattle, Wash.....	1st	8
John R. Bahrs, 72 Hazelton St., Ridgefield Park, N. J.....	1st	12
Richard Baden, 4226 - 37th St., N.W., Washington, D. C.....	1st	12
James F. Stewart, 2618½ Prospect Ave., La Crescenta, Calif....	1st	12
Norman R. Cook, 130 Olive Street, Neodeska, Kans.....	1st	12

GRANTHAM SCHOOL OF ELECTRONICS

HOLLYWOOD CALIF.

1505 N. Western Ave. (HO 7-7727)
Hollywood, Calif.

SEATTLE WASH.

408 Marion Street (MA 2-7227)
Seattle, Wash.

KANSAS CITY MO.

3123 Gillham Road (JE 1-6320)
Kansas City, Mo.

WASHINGTON D. C.

821 - 19th Street, N. W. (ST 3-3614)
Washington, D. C.

MAIL COUPON TO SCHOOL NEAREST YOU

(Mail in envelope or paste on postal card)

TO: GRANTHAM SCHOOL OF ELECTRONICS

1505 N. Western • 408 Marion • 3123 Gillham Rd. • 821 19th, NW
Hollywood • Seattle • Kansas City • Washington



Gentlemen:

Please send me your free booklet telling how I can get my commercial F.C.C. license quickly. I understand there is no obligation and no salesman will call.

Name _____ Age _____

Address _____

City _____ State _____

I am interested in: Home Study, Resident Classes 14-C

Centralab has the answer

to your ~~dual~~ control problems

Dual

FASTATCH Dual Radiohms®



No need to fence with dual concentric replacements . . . your problems are solved with CENTRALAB Model F and R controls. Just match front and rear units with proper resistance and taper—cut shafts to length (it's easy with the CENTRALAB SK-2 precision Shaft-Kut Tool)—snap together, and *ouche*, you're ready to go.

You won't be foiled by switch problems, either. Just parry them by snapping on a Fastatch KR line switch if needed.

Fastatch Radiohms enable you to meet the demand for an immense variety of dual concentrics with a minimum of components. (The handy FDK-100 Kit provides coverage of 90% of your dual control requirements.) Ask your distributor for full information about CENTRALAB Model F & R controls.

CENTRALAB products are listed in PHOTOFACETS, COUNTERFACTS, and THE RADIO-ELECTRONIC MASTER.

Centralab

B 6002 CRL

ELECTRONICS DIVISION OF GLOBE-UNION INC.
900A E. KEEFE AVE. • MILWAUKEE 1, WIS.
IN CANADA: 669 Bayview Ave., Toronto 17, Ont.

CONTROLS • ROTARY SWITCHES • CERAMIC CAPACITORS
PACKAGED ELECTRONIC CIRCUITS • ENGINEERED CERAMICS

Ion Engine

A new potential source of power for space and other engines has been developed and demonstrated by NASA (National Aeronautics and Space Administration). This experimental engine uses the rare metal cesium as a propellant. The metal is vaporized and placed near tungsten strips where the reaction separates ions from the cesium. Tantalum or stainless steel electrodes near the rear of the motor then attract the freed ions, and they shoot out the rear of the engine, providing thrust.

The amount of thrust which can be developed in this way is relatively small, but NASA believes an ion engine could provide adequate thrust to propel vehicles once outside gravitational fields.

AM SSB Stereo Broadcasting

Four foreign radio stations will initiate compatible AM stereo broadcasting using the Kahn Research system soon.

The system develops two separate sidebands, one for each stereo channel, at the transmitter. Then two standard AM sets are tuned, one to the lower sideband, one to the upper. Full monophonic reception is available by simply tuning to the center of the carrier.

The stations which will use the system are in Canada, Mexico and Venezuela.

Automatic Industrial Control on the Way

An industrial computer has been running almost continually for 6 months in a severe test of industrial control equipment reliability which points toward total control of industrial operations through computer automation.

A general-purpose digital computer and associated equipment at Sterlington, La. monitors 350 temperature, pressure and flow points at a public-utility electric plant, continuously scanning them in sequence. Using the scanned information, it computes a number of variables, setting off an alarm if measured or computed values go outside preset limits. In such cases, it pinpoints the trouble spot.


This Daystrom data logger and computer uses 4,000 transistors and 7,500 diodes. Its high reliability is said to be the result of solid-state design whose operational rate is *relatively* slow, only 50 kc. Its accuracy is 1 part in 1,000,000. The next step will be a fully automated digital computer control system to be installed by Daystrom at Little Gypsy, La., where it will run a 230,000-kw utility station. It will continuously monitor 1,226 check points and automatically start, operate, shut down the generating station. END

FREE


ALLIED'S 1960

ELECTRONIC SUPPLY CATALOG

value-packed...send for it!

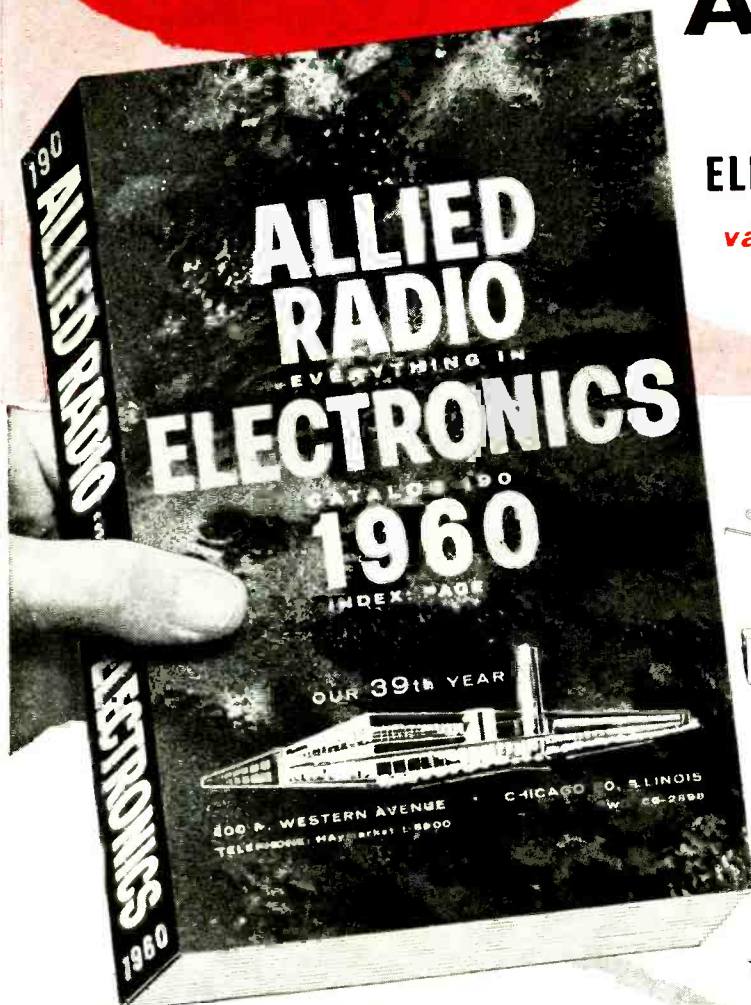

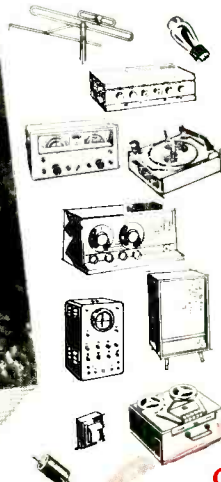your complete money-saving guide to
EVERYTHING IN ELECTRONICS



- Latest Stereo Hi-Fi Systems — Everything in Hi-Fi Components
- Money-Saving, Build-Your-Own KNIGHT-KITS® for Every Need
- Values in Recorders and Supplies
- Latest Public Address Systems, Paging and Intercom Equipment
- Amateur Receivers, Transmitters and Station Gear
- Test and Laboratory Instruments
- TV Tubes, Antennas, Accessories
- Huge Listings of Parts, Tubes, Transistors, Tools, Books

ONLY \$2 DOWN

on orders up to \$50; only \$5 down on orders up to \$200; only \$10 down over \$200. Up to 24 months to pay.

ALLIED exclusives:

MONEY-SAVING KNIGHT-KITS®—the very best in build-your-own electronic equipment—designed to save you up to 50%. "Convenience Engineered" for easiest assembly; the only kits covered by Money-Back Guarantee. Complete selection of Stereo hi-fi kits, Hobbyist kits, Test Instrument and Amateur kits. KNIGHT-KITS are an exclusive ALLIED product.

KNIGHT® STEREO HI-FI—truly the best for less—the finest you can buy, yet far lower in cost. Select super-value KNIGHT components or complete systems and save most. Also see the world's largest selection of famous-name hi-fi components and money-saving ALLIED-recommended complete hi-fi systems.

Get every buying advantage at ALLIED: lowest money-saving prices, fastest shipment, expert personal help, guaranteed satisfaction.

send for the leading
electronic supply guide

FREE

ALLIED RADIO



World's Largest Electronic Supply House


ALLIED RADIO CORP., Dept. 2-C
100 N. Western Ave., Chicago 80, Ill.

Send FREE 1960 ALLIED Catalog.

Name _____

Address _____

City _____ Zone _____ State _____

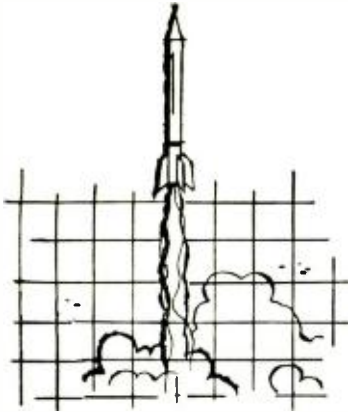

*Technicians—
you can
be a
computer
specialist
with*
Burroughs


The dynamic field of integrated Data Processing for Military Weapons Systems at BURROUGHS Military Field Service Division offers you that fine career which will challenge your full potential...will advance you to engineering status through work on important long-range ATLAS and SAGE programs...give you recognition and reward in the field of the future: Digital Computation.

Qualified applicants will receive: 1) 8 to 22 weeks' classroom training in Data Processing Systems. 2) Starting salary commensurate with experience and ability. 3) Full salary while training. 4) Excellent fringe benefits including educational assistance program. Current field assignments include far-West and Western areas after your training is completed.

If you are a graduate of an accredited Technical School and/or have military training in radar or communications equipment, plus at least 2 years' experience in electronics, you are invited to address your inquiries to Mr. R. F. Johnson, Department 2451, Military Field Service Division, Burroughs Drive, Radnor, Penna. (A suburb of Philadelphia).



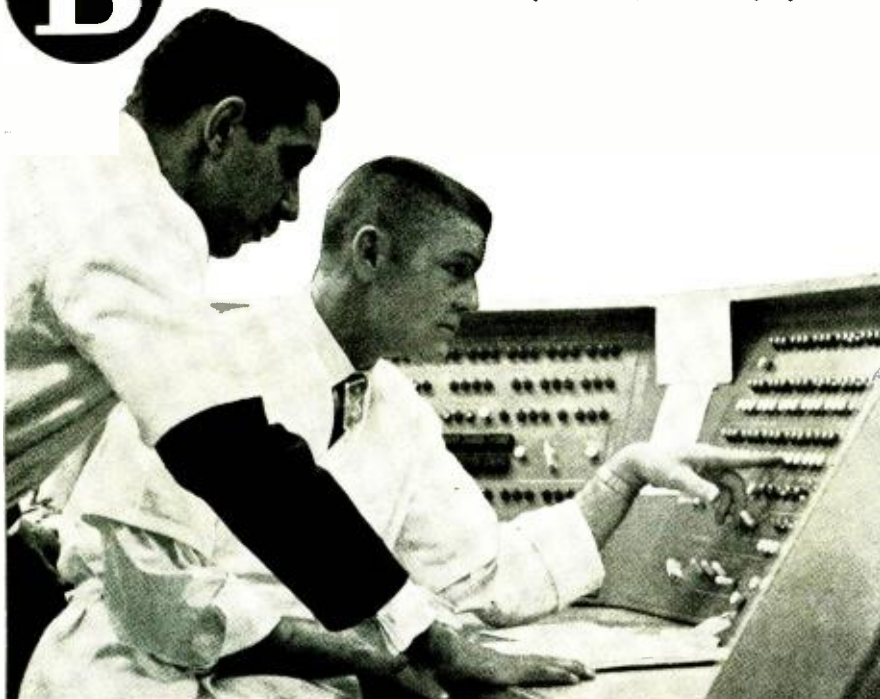Burroughs Corporation
"NEW DIMENSIONS/in computation for military systems"



Correspondence



MORE ON 7-TRANSISTOR POCKET RADIO

Dear Editor:

We have received several inquiries as to the availability of the RCA 239S1 speaker I specified in my article "7-Transistor Pocket Radio" (November 1959, page 32-34). Unfortunately, this speaker has been discontinued. However, several imported 2-inch speakers are available through many of the larger parts distributors which should prove satisfactory. Some variation in speaker impedance can be tolerated.

Not shown on the diagram was the interlead shield (lead 3) of the 2N247 transistors. These and the shields of the if transformers should go to ground.

Due to normal production variations in other components, R4 (330,000 ohms) may have to be increased or decreased to obtain the maximum if gain commensurate with stable operation.

This table shows the terminal connections for the Miller transformers (numbers are shown on the Miller units):

<i>T1</i>	<i>T2</i>
1—gnd	1—not used
2—T2	2—ave
3—V1 coll.	3—V2 base
4—C1	4—T1
5—C5	5—B minus
<i>T3</i>	<i>T4</i>
1—not used	1—not used
2—ave	2—gnd
3—V3 base	3—D
4—V2 coll.	4—V3 coll.
5—R6	5—B minus

HAL WITTLINGER

*RCA Tube Div.
Harrison, N. J.*

COMMERCIAL SERVICE— ANOTHER VIEW

Dear Editor:

In the December 1959 issue of RADIO-ELECTRONICS Mr. Lester Berry stated that he would refuse to do commercial equipment service jobs in the future because of lack of cooperation from manufacturers.

I too, like Mr. Berry, have tried in vain to get parts for a NATCO 3030-1 16-mm sound projector. However, this is not a good example of lack of cooperation—the company has been out of business for a number of years.

I have been trying to get two fiber gears for this machine for over 6 months. Though this job was not very profitable, it will not cause me to quit this interesting and profitable field of service work.

I have enjoyed your articles on industrial electronics and this is one of the
(Continued on page 22)




LET RCA TRAIN YOU IN ELECTRONICS

RCA Institutes, one of the world's leading electronic technical schools, offers a Home Study Course in . . .

ELECTRONICS FOR AUTOMATION

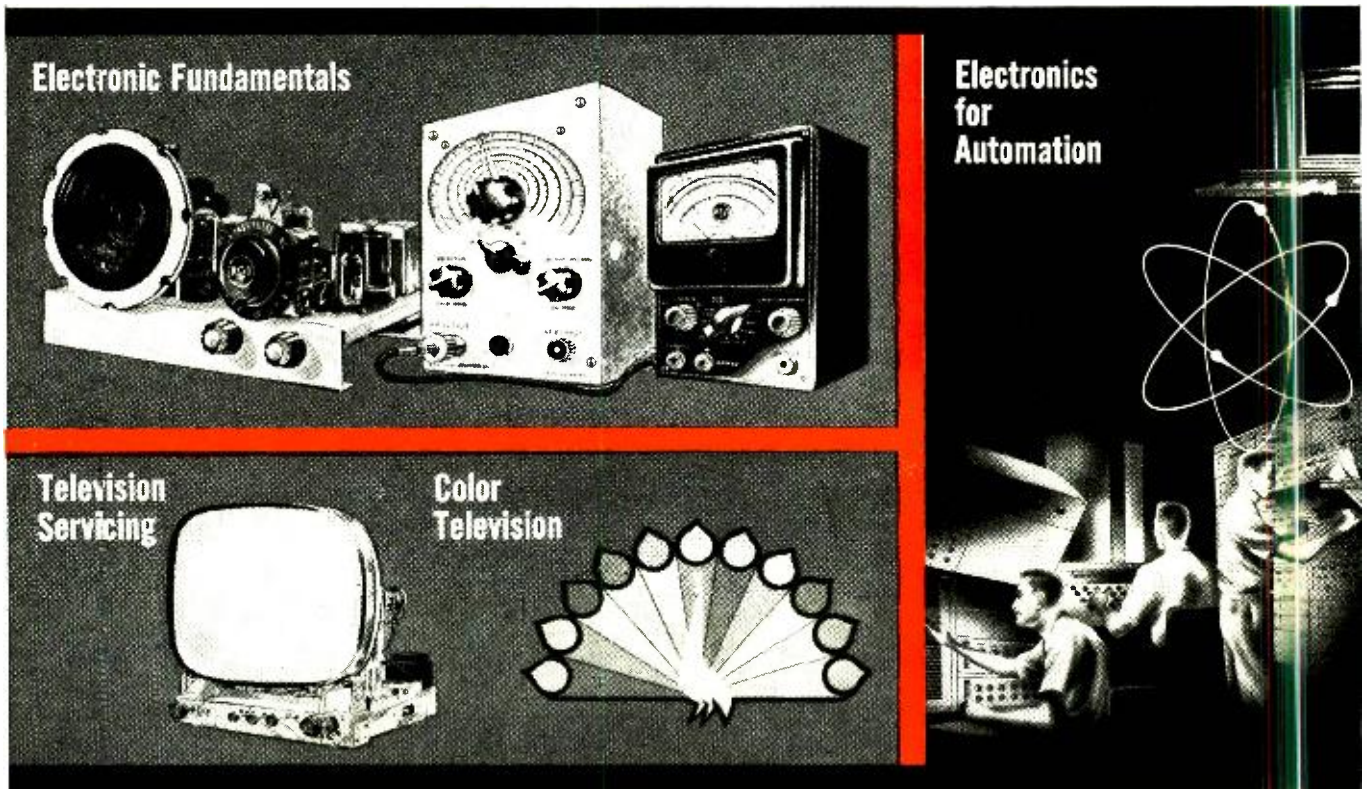. . . Now you have *four* comprehensive courses for your electronic training . . . from basic electronic theory to the more advanced principles of color TV and Automation.



Send for our
64 page Home
Study Catalog

FREE!

RESIDENT SCHOOLS in New York City and Los Angeles offer Technical Institute and Vocational School Courses in Electronics. Day and Evening classes start 4 times each year. Resident School Catalog sent free on request.

ANOTHER WAY RCA SERVES EDUCATION THROUGH ELECTRONICS



Practical work with the very first lesson. Pay-as-you-learn. You need pay for only one study group at a time.

RCA INSTITUTES, Inc. Home Study School, Dept. ZRE-30

A Service of Radio Corporation of America
350 West Fourth Street, New York 14, N. Y.

Please rush me your FREE illustrated 64-page book "Your Career in Electronics," describing your home training programs. No obligation. No salesman will call.

Name Age
Please print

Address

City Zone State

Veterans: Enter discharge date

CANADIANS — Take advantage of these same RCA courses at no additional cost. No postage, no customs, no delay. Send coupon to: RCA Victor Company, Ltd., 5001 Cote de Liesse Rd., Montreal 9, Quebec
To save time, paste coupon on postcard.



RADIO & TV SERVICE
PORTLAND - EUGENE - LONGVIEW - YAKIMA

200 N. W. 4th Ave.
Portland 5, Oregon
September 27, 1959

Westinghouse Electric Corp.
600 St. Paul Ave.
Los Angeles 17, California

Gentlemen:

We are constantly seeking improved products to recommend and sell to our customers, and we are pleased to inform you that Westinghouse receiving tubes and picture tubes fall into that category.

We changed over exclusively to Westinghouse tubes approximately January 1st, of this year. Since it was a new product to us, we kept complete records of tube failures and customer call backs. Our call backs due directly to tube failures were reduced by over 90 per cent.

It is with complete confidence that we recommend and sell your quality Gold Star picture tubes. The picture quality is excellent, and the tubes are exceeding our greatest expectations. In the past nine months, we have used approximately 500 picture tubes, and as of now have only replaced three. Two of which were defective out of the carton, and only one failed in actual use. In fact, we are so confident in the life of the picture tube, that we are now guaranteeing our picture tube replacements for three years.

We have gained two things by the use of your tubes. Greater customer satisfaction, and more net dollars for us due to the very minimal amount of tube failures.

Please thank your Engineers and Quality Control Department for the fine product that they are putting in our hands to sell to the consumers.

Sincerely yours,

ACE RADIO & TV SERVICE

Philip Blank
Philip Blank

PH:jd

"call backs
reduced by
over 50%! "

"It is with complete confidence that we recommend and sell your quality Gold Star picture tubes."

"We are so confident in the life of the picture tube that we are now guaranteeing our picture tube replacements for three years."

"We have gained...greater customer satisfaction, and more net dollars for us due to the very minimum amount of tube failures."

We can't think of a thing to add. Except, perhaps, that your local Westinghouse electronic tube distributor will be happy to introduce you to the line. If your distributor doesn't carry them yet, give us his name. We'll send someone over to enlighten the poor fellow.

YOU CAN BE SURE...IF IT'S **Westinghouse**

Westinghouse Electronic Tube Division, Elmira, N.Y.

CITIZENS BAND RADIO
at it's VERY BEST!



NEW Arkay SQ-9 'SKY-VOX'
Citizens' 2-Way Radio

Superhet Receiver—Crystal Controlled Transmitter

Magnificently engineered for outstanding performance, ease of assembly and operation, the Sky-Vox offers high sensitivity, selectivity, stability and fidelity of sound.—The finest in citizens' band communication for business, pleasure, auto, farm, home, industry, etc.

Completely Wired & Aligned Front End for Easy Assembly

Advanced design features include: Completely assembled front end with 3 channels aligned ready to install in main chassis • Up-to-the-minute circuitry with 8 tubes and 5 diodes • Supersensitive crystal controlled superhet receiving circuit • Crystal controlled oscillator Pentode RF amplifier transmitting circuit • Front Panel controls include 3 position channel selector • Receive-Transmit switch • Volume control • Squelch control • Mike input • Noise balance control in rear chassis

Power Requirements: 117 Volts 60 cycles AC or 12 Volts DC. Sensitivity: 1 u/v, 400 cy. at 27.015 Mc. for full output 12.5 watts; Signal Noise Better than 35 dB • Image 30 dB • IF Bandwidth 5 KC • Complete with 2 cables, microphone and set of crystals. Attractive metal case, size 3 1/2" H x 2 1/2" D x 11 1/2" W.

Wired and Tested \$119.95 • Easy-to-build Kit \$79.95



the Arkay MS-5
STEREO Playback
TAPE DECK

Professional quality at a popular price!

A supreme achievement in tape deck design and performance, the ARKAY records your favorite music with the same superb performance of tape recorders costing many times more. No other tape deck—regardless of price—offers so many important features. Here's just a few:

- Combination Head for 2 or 4 Track Stereo-Two Speeds
- 30-18,000 cps ± 2 db.
- Flutter and wow: 1/4 of 1%
- Five-button operation
- -55 db. S/N
- All-metal tape fingers
- Drop-In Loading
- All-metal tape guards
- Large (1/2" diam.) capstan
- Size: 12-3/16" x 14 1/2" x 6 1/4"

2 Track Only \$129.95 • 4 Track Slightly Higher



ARKAY CS-28
Stereo Amp/Pre-Amp
Complete
Control Center

Full 28 watts stereo of monoaural, 60 watts peak

- 14 watts each channel reverse stereo
- Balance control • two-channel gain control • full range bass and treble controls • 18 distortion, 1% to 2% harmonic distortion, 1.2% 30-20,000 cps • dual pre-amp 2V output jacks • speaker outputs, 4, 8, 16, 32 ohms • response, 20-20,000 cps • push-pull EL84 Williamson circuit

Wired and tested \$99.95 • Easy-to-build Kit \$64.95



ARKAY ST-11 AM-FM
STEREO TUNER

Here, for the first time, is an AM-FM STEREO Tuner within the reach of every audiophile. Unmatched by units costing twice the price, the ST-11 is two distinct receivers in one featuring 4 uV. for 20 db quieting, Variable AFC, Single front panel switch controls AM, FM or STEREO selection.

Wired and tested \$74.50 • Easy-to-build Kit \$49.95



SPA-55 STEREO AMP 55 watts stereo-monoaural, 27 1/2 watts each channel. **Wired \$79.95 Kit \$64.95**



ARKAY VT-10 6-INCH
MULTI-PURPOSE
VACUUM TUBE VOLTMETER

Advanced design and precision features make the Arkay VT-10 a truly sensational buy, unmatched at this price. You get exclusive larger 6-1/4" 100 ua meter movement, within 2% accuracy, and edge-lighted for easier reading. 10% precision multiplier resistors are used throughout the range switch. There are 7 AC (RMS) and DC ranges, 7 AC (peak-to-peak) ranges, Resonance, db and other essential ranges. Durable plastic case.

Wired and tested \$47.95. Easy-to-build Kit \$25.95

See and hear ARKAY Kits at your dealer. **FREE!** Stereo booklet and catalog. Write Dept. RE

All prices 5% higher west of Mississippi



CORRESPONDENCE (Continued from p. 18)

reasons I have just renewed my subscription to your fine magazine for another 3 years.

How about an article on sound projectors? **JAMES L. STELZIG**
St. Cloud, Minn.

SPEAKERS IN TRUCKS

Dear Editor:

I found the article "Hints on Installing Mobile Radio Equipment" by R. J. Hendrick (Dec., 1959, p. 58) very interesting and comprehensive.

An additional solution to the common speaker installation problem may be helpful to your readers. Practically all late model cars and trucks have speaker grilles built into the dashboard for standard 5 x 7 or 6 x 9 speakers. Since most fleet vehicles don't use broadcast receivers, this spot can be used for the mobile radio speaker. The speaker supplied is replaced with a 5 x 7 or 6 x 9 oval.

The slight additional expense will be more than repaid by the esthetic and acoustic improvement.

CHARLES E. COHN
Chicago, Ill.

DEFENDS PART-TIMERS

Dear Editor:

RADIO-ELECTRONICS seems to be becoming a crying towel for some of these so-called technicians who cannot compete with honest part-timers! A good service organization has nothing to fear from part-timers. If a part-timer does not do good work, he'll go the way of many others who have tried the same thing.

Has licensing helped the medical profession? Doctors still can't cure the common cold. But if a physician loses a patient, he still presents his bill . . . and a lawyer collects even if his client goes to jail!

Many part-timers repair sets that some bigger shop has worked on and failed to repair satisfactorily. Most part-timers at least guarantee their work, and back it up!

I am for licensing, if a test goes along with licensing. That way we can eliminate these cry-babies!

AL HART

ADMIRE TESLA


Dear Editor:

Some day I hope to visit you to see the bronze bust of the death mask of Nikola Tesla. I consider Tesla one of the greatest minds ever to come to earth. It is too bad more people do not revere this great man. We are all so indebted to him.

MAC STURM
Philadelphia, Pa.
(Nikola Tesla, 1857-1943, inventor of the induction motor, was the holder of over 700 patents. His early experiments foreshadowed remote radio control, tuning and wireless transmission of power. More and more people are coming to recognize this lonely visionary genius as a true giant of radio, "possibly the greatest inventor who ever lived."—Editor) **END**

FOR P. A.
OR TAPE

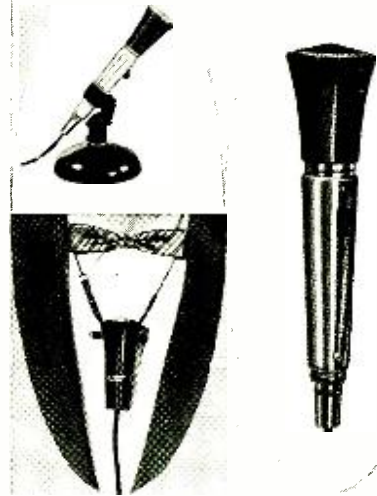*unlimited versatility . . .
exceptional performance . . .
long service life . . .
nominal cost . . .*



controlled magnetic microphone by

SHURE

Striking, streamlined unit delivers fine voice and music reproduction in dozens of public address and home recording applications. Whether used indoors or out, in-the-hand, or on a desk or floor stand, you'll be impressed by its fine response, high output, ruggedness and beauty of design. The Commando offers you such important features as dual impedance, on-off switch, and cable connector. Patented controlled magnetic construction is unaffected by extremes of temperature and humidity, can be depended on to maintain high level of quality through tough, sustained usage, year after year.

the Commando is available in three models:

DELUXE Model "430"
A dual-impedance unit with A25 swivel adapter, on-off switch, cable connector
list price \$3850

LAVALIER Model "420"
A dual-impedance unit with lavalier cord and clip assembly
list price \$3000

STANDARD Model "415"
A high impedance unit with A25 swivel adapter
list price \$2750



write for free literature:
SHURE BROTHERS INC.
222 Hartrey Ave.
Evanston, Ill., Dept. 12-I
Manufacturers of world-famous Shure High-Fidelity Stereo Dynetic Phono Cartridges.

IMPORTANT: For the men who wants to make big money in Radio-Television!

ONLY SPRAYBERRY TRAINING IN RADIO and TELEVISION

offers you all of these vital new advantages to help you earn more money from the start!

NEW

Business Builders

... through these practical proven plans and ideas we help you make plenty of extra money in spare time while training!

NEW

Training Equipment

... the famous Sprayberry Training kits have been newly engineered by our staff to offer you the latest in Radio-TV Service Techniques!

NEW

Transistor Course

... literally millions of new transistor radios are being used. We show you how to make money fixing them!

NEW

High Fidelity

... there's big money to be made installing and servicing Hi-Fi units. Your Sprayberry training now offers you this valuable and profitable preparation!

TRAIN AT HOME—SPARE TIME


WITH THESE **25 BIG COMPLETE KITS of PARTS & EQUIPMENT**



You learn Radio-TV Servicing the best way... the practical way... testing and assembling these modern kits of equipment.


◀ The new Sprayberry Training Television Receiver, built and tested in 5 sections.

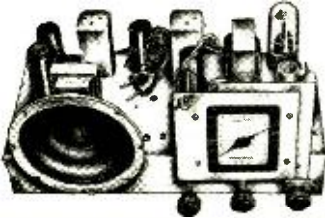Now offered... this fine modern oscilloscope.



◀ You build this powerful two-band superheterodyne radio receiver.

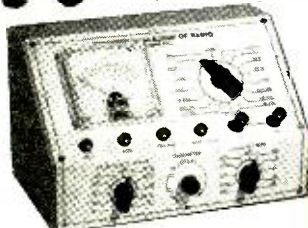You build the new Sprayberry tester—a complete 18-range Volt-Ohm-Mill ammeter test meter.



FREE These two big new books are yours free! Find out what Radio-Television offers you... and let us show you how easily you can learn, even without previous experience of any kind. Rush COUPON today!

The field of Radio-Television Servicing is such a fast moving industry that the best jobs and biggest incomes always go first to the man with the most modern, complete and up-to-date training. Thanks to constant revision and improvement... Sprayberry Training helps you earn more from the start... and keeps you earning more in the months and years ahead!

Make no mistake! All radio-television training is *not* alike. The basic purpose behind Sprayberry Training is to prepare you as rapidly and as surely as possible... to make top money servicing Radio and Television sets and equipment. This is where the big money has been for years... and will continue to be in the years ahead.

It's important for you to know that for over 30 years... Sprayberry Training has been preparing ambitious men for success in this interesting and profitable kind of work. Our school has helped hundreds to qualify for the best jobs... or to get started in profitable businesses of their own. Today our student rolls are the largest in our school's history... because the need and demand for Radio-Television Service Technicians has never been more urgent.

Just \$6.00 Starts You

To encourage more men to enter Radio-Television at once... to help fill the great need for trained men... we're making it easier than ever before to start training. Just \$6.00 enrolls you. This liberal offer is naturally limited. Get the facts now

and consider enrollment while these favorable terms are available to you.


KEEP YOUR JOB... while learning

Under the Sprayberry Plan you train entirely at home in spare time. You combine the most modern lesson training with fascinating and invaluable practical work with 25 big kits of parts and equipment that we supply. You get the equivalent of years of shop practice... and you can train as fast or as slowly as you wish. We help you make excellent spare time money while learning... and everything you receive—lessons, books, manuals, equipment—all yours to keep!

This is the Radio-Television industry's most modern and up-to-the-minute training. Sprayberry is the *one* school that gives you personalized attention and takes a real interest in your progress. Remember... just \$6 starts you! Mail the coupon today. Let the facts speak for themselves. Let us send you our new catalog and sample lesson... and *prove* the kind of opportunity that Sprayberry training can open up for you.

SPRAYBERRY ACADEMY OF RADIO-TELEVISION

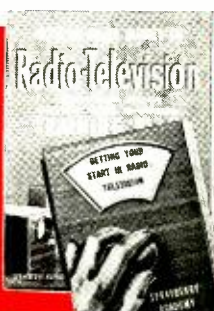Dept. 20-H, 1512 West Jarvis Ave., Chicago 26, Ill.



MAIL COUPON—No Salesman Will Call

SPRAYBERRY ACADEMY OF RADIO-TELEVISION
DEPT. 20-H, 1512 W. JARVIS AVE., CHICAGO 26, ILL.
Please rush all information on your ALL-NEW Radio-Television Training Plan. I understand this does not obligate me and that no salesman will call upon me. Include New Catalog and Sample Lesson FREE.

NAME.....AGE.....
ADDRESS.....
CITY.....ZONE.....STATE.....

YOU'RE AS SUCCESSFUL GENERAL ELECTRIC'S



AS YOU WANT TO BE WITH NEW PSM* METHOD!

*PROFITABLE SERVICE MANAGEMENT

Earn the good things of life for yourself and your family by following the Profit signposts on every page of General Electric's PSM* Method! The engraved Certificate which says you have completed this instruction program, will mean new success for you as a TV technician.

Says Dr. John K. Pfahl of Ohio State University, under whose direction the new General Electric program was prepared: "The electronic service dealer must be, at the same time, a technician, good businessman, and sales manager." You learn step-by-step how to realize these aims, by following General Electric's Profitable Service Management Method. You are shown how to assure a satisfactory profit margin, not merely

hope for it—how to increase business by methods others have found unfailingly effective.

In the LP record "Sounds of Success" you will hear from the lips of experienced TV technicians just how they have built greater incomes. After completing the two volumes of instruction that make up the study course, a questionnaire is available to check your acquired knowledge, prior to receiving your Certificate.

All come handsomely packaged for your bookshelf. Check the highlights of General Electric's PSM* Method given below! Then see your G-E tube distributor! *Distributor Sales, Electronic Components Division, General Electric Company, Owensboro, Kentucky.*

HERE ARE SOME OF THE MANY SUBJECTS YOU WILL STUDY:

BOOK NO. 1. "SOUND BUSINESS PRACTICES"

BUSINESS FOR PROFIT: Your reasons for owning a business...How much money should you make?...How to make your business profitable.

PLANNING YOUR BUSINESS: Planning expansion...Cash planning...Shop planning.

ORGANIZING YOUR BUSINESS: Overhead costs...Pricing...What it costs you to make a service call...What it costs you to make a shop repair...Inventory control...Credit organization...Choosing a form of organization.

CONTROLLING YOUR BUSINESS: Why use records?...What records are needed...Taxation...Use an accountant.

BOOK NO. 2. "SELLING ELECTRONIC SERVICE"

ARE YOU ATTRACTING NEW CUSTOMERS?: Attracting new business...Businesslike appearance...Effective selling...Good identification...Basic market research.


PROMOTING YOUR BUSINESS: Advertising technique...Advertising campaign planning...Special offers...Seasonal planning...Customer contact.

KEEPING YOUR CUSTOMERS SATISFIED: Customer relations...Customer grievances...Guaranteeing repairs...Building new customers.



Progress Is Our Most Important Product


GENERAL  ELECTRIC

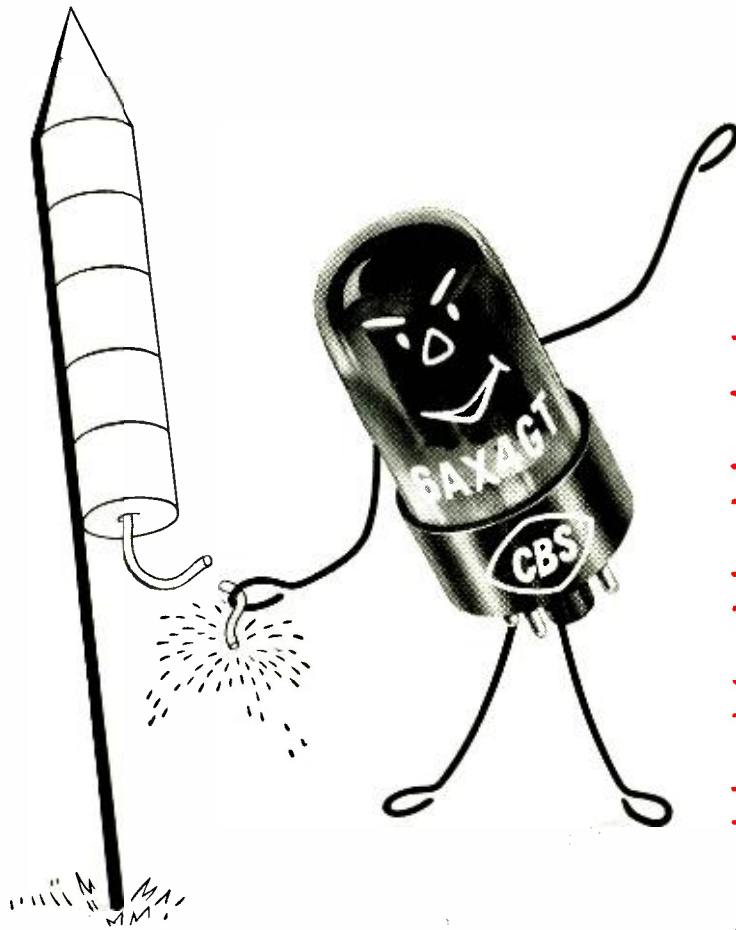

No
more
fireworks
for
me!

**(NO MORE DAMPER
ARCING FOR YOU)**

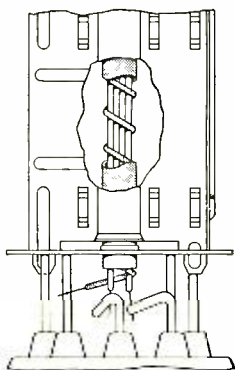Typical of the many design features of CBS dampers is this new anchored heater-cathode insulator. Actually a tungsten coil coated with insulating material, it is mechanically anchored to prevent any movement that might lead to heater-cathode shorts. As a secondary precaution, the coil has fewer turns to minimize cathode-to-insulator contact, yet maintain perfect heater-cathode spacing.



"Damper diodes are prone to fireworks. Not me. I've been arc-proofed from heater to cathode to plate . . . and I'm blast-tested to insure it. That goes for my whole family of CBS damper tubes. Use us and relax."

It's true. CBS damper diodes have been completely redesigned to offer you *total reliability* . . . proved in performance by leading TV and radio set manufacturers. You, too, can profit more from the *total reliability* of CBS tubes. To prove it . . . just replace with CBS.

TOTAL RELIABILITY...
proved in performance



*Receiving, industrial
and picture tubes
transistors and diodes
audio components
and phonographs.*

CBS ELECTRONICS

Danvers, Massachusetts

A Division of Columbia Broadcasting System, Inc.



Here is the new Standard Coil Tuner Replacement and Repair Program that enables you to offer better service to your customers at greater profit. Now Standard Coil Products provides the tools that will enable you to cash in on the profitable tuner repair and replacement market.

TUNER REPLACEMENT LISTING IN SAMS PHOTOFACT

Starting in January, Standard Coil tuner replacement listings will appear in all Sams TV Photofact. Tuner replacement information will be right at your finger tips. Standard Coil is the *only* manufacturer ever to provide this service.

NEW TV TUNER REPLACEMENT GUIDE

Lists original equipment TV tuners with the Standard Coil equivalent replacement for each. Also includes major mechanical replacement parts for all Standard Coil Tuners—those used in original equipment as well as the universal replacement. Eliminates all guesswork—minimizes your tuner repair and replacement problems.

48 HOUR FACTORY GUARANTEED REPAIR SERVICE

Standard Coil's special service department set-up assures factory guaranteed repairs—*on a 48 hour in-plant cycle!* All repaired tuners carry a *six month warranty* on defective workmanship and parts failure (excluding tubes). Gives you more time for additional service calls—promptly returns your customer's set to like new operating condition.

DEFECTIVE TUNER TRADE-IN ALLOWANCE

Tuners which can *not* be repaired can be traded in against a new replacement tuner which carries a *full twelve month factory guarantee*. See your Standard Coil Distributor for complete details on how trade-ins can increase your tuner sales and profits—create greater customer satisfaction.

JUMP ON THE STANDARD COIL PROFIT WAGON TODAY!

For additional details, see your authorized Standard Coil Distributor or write to:

Standard

Coil Products Co., Inc.

2085 North Hawthorne Avenue, Melrose Park, Illinois

make your first move to **ROHN**




You Have the Greatest Sales Potential by Far With America's MOST COMPLETE LINE OF

TOWERS—MASTS ROOF TOWERS Installation Accessories

ROHN TV TOWERS

ROHN makes the finest towers available for television reception! Illustrated is the No. 25 with amazing "zig-zag" cross bracing design. The entire tower is rated 33% stronger than other similar sized towers. Yes, sell and install the No. 25 up to 50 feet self-supporting or, properly guyed, up to 360 feet!

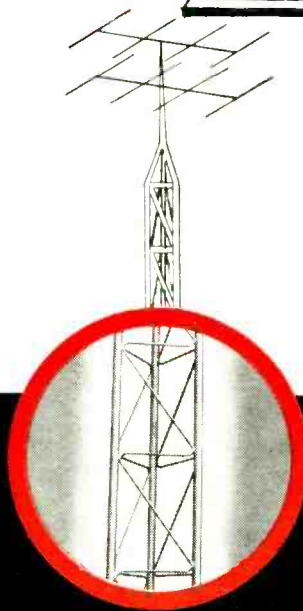
Or if you prefer, sell the popular ROHN No. 6 tower with the famous "Magic Triangle" cross-bracing. Both are fully HOT DIPPED GALVANIZED AFTER FABRICATION! Sections in easy-to-handle 10 ft. lengths.



From every standpoint, ROHN Towers offer you MORE . . . more quality, more variety, more advanced design, more sales features, more service, more total sales and more PROFITS! Move forward with these ROHN items!



ROHN COMMUNICATION TOWERS

Here you have FIVE complete lines of heavy-duty, FULLY ENGINEERED communication towers to fulfill any communications requirement. Shown is the ROHN "SS" tower which is self-supporting up to 130 feet. Other models — (30-40-50-60) are available in heights up to 630 feet when guyed! Handle these towers for the demand in your area. There's a complete NEW catalog on this line. Get a copy so you'll have it on hand.

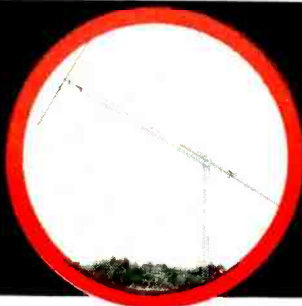


AMATEUR "FOLD-OVER" TOWERS

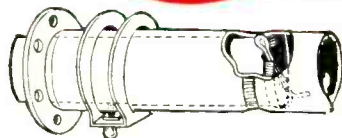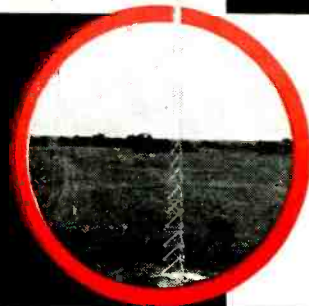Specially designed "fold-over" towers are the best ever designed for amateur radio and experimentation. They are the most desired because they "fold-over" completely so you work on the ground for ease and safety. Three sizes, including heavy-duty type to handle any needs. All hot dipped galvanized.




TELESCOPING MASTS

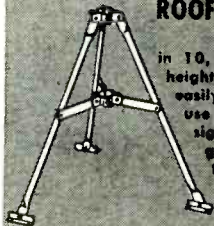Unexcelled in design, structural strength, and sales appeal. All popular sizes, heights, and weights available. Also, mast tubing in exact specifications that's demanded today.



ROOF TOWERS . . .

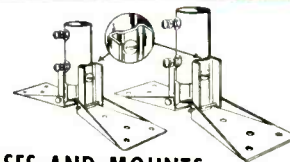in 10, 5, 3, and 2½ feet heights — very popular — easily shipped — ideal in use — the best ever designed — in hot-dipped galvanized finish — truly a big profit item for you!



BASES AND MOUNTS

Wide variety of bases and mounts. Special features include "locking" device — also cast aluminum roof mounts — and a host of other installation items . . . get full details.



TV SERVICE-TABLE

For holding TV sets while servicing, or storing, or for mobile use of set in such places as motels, hospitals, etc. Ideal for dozens of uses — thousands sold. Large casters — a real work-saver.

ROHN

Manufacturing
Company

116 Limestone, Bellevue
Peoria, Illinois

Get complete catalog from your ROHN representative or jobber or MAIL THIS COUPON!

Gentlemen: Please send me literature on ROHN Towers and Accessories.

Firm _____

Name _____ Title _____

Address _____

City _____ State _____

Over 2 MILLION EICO instruments in use throughout the world. Add 5% in the West.



IF YOU LOVE TO CREATE... BUILD EICO KITS

In **STEREO** and

**Mono Hi-Fi...
the experts say
your Best Buy
is EICO**



Stereo Amplifier-Preamp HF81t



Stereo Preamp HF85t†



**FM Tuner HFT90t†
AM Tuner HFT94t†
FM, AM Tuner HFT92t†**



**100W Stereo Power Amplifier HF89
70W Stereo Power Amplifier HF87
28W Stereo Power Amplifier HF86**



Stereo Integrated Amplifier AF4t†



**3-Way Speaker System HFS3
2-Way Bookshelf Speaker Systems
HFS5 and HFS1**



**NEW!
Stereo Automatic Changer/
Player 1007**



- Exclusive advanced systematized engineering
 - Latest and finest quality parts
 - Exclusive "Beginner-Tested" easy step-by-step instructions
 - Exclusive TRIPLE quality control
 - Exclusive 1 FETIME guarantee at nominal cost
- IN STOCK** — Compare, then take home any EICO equipment — right "off the shelf" — from 1500 neighborhood EICO dealers throughout the U.S. and Canada.

HF81 Stereo Amplifier-Preamp selects, amplifies, controls any stereo source & feeds it thru self-contained dual 14W amplifiers to a pair of speakers. Provides 28W monophonically. Ganged level controls, separate balance control, independent bass and treble controls for each channel. Identical Williamson-type, push-pull EL84 power amplifiers. "Excellent" — SATURDAY REVIEW. "Out-standing... extremely versatile." — ELECTRONICS WORLD. Kit \$69.95. Wired \$109.95. Incl. cover.

HF85 Stereo Preamp: Complete master stereo preamp/control unit, self-powered. Distortion borders on unmeasurable. Level, bass, & treble controls independent for each channel or ganged for both channels. Inputs for phono, tape head, mike, AM, FM, & FM-multiplex. One each auxiliary A & B input in each channel. "Extreme flexibility... a bargain." — HI-FI REVIEW. Kit \$39.95. Wired \$64.95. Incl. cover.

New HF89 100-Watt Stereo Power Amplifier: Dual 50W highest quality power amplifiers. 200W peak power output. Uses superlative ultra-linear connected output transformers for undistorted response across the entire audio range at full power, assuring utmost clarity on full orchestra & organ. 60 db channel separation. IM distortion 0.5% at 100W harmonic distortion less than 1% from 20-20,000 cps within 1 db of 100W. Kit \$99.50. Wired \$129.50.

HF87 70-Watt Stereo Power Amplifier. Dual 35W power amplifiers identical circuit-wise to the superb HF89, differing only in rating of the output transformers. IM distortion 1% at 70W; harmonic distortion less than 1% from 20-20,000 cps within 1 db of 70W. Kit \$74.95. Wired \$114.95.

HF86 28-Watt Stereo Power Amp. Flawless reproduction at modest price. Kit \$43.95. Wired \$74.95.

FM Tuner HFT90 Pre-wired, prealigned, temperature-compensated "front end" is drift-free. Pre-wired exclusive precision eye-tronic® traveling tuning indicator. Sensitivity: 1.5 uv for 20 db quieting; 2.5 uv for 30 db quieting, full limiting from 25 uv. IF bandwidth 260 kc at 6 db points. Both cathode follower & FM-multiplex stereo outputs, prevent obsolescence. Very low distortion. "One of the best buys in high fidelity kits." — AUDIOCRAFT Kit \$39.95. Wired \$65.95. Cover \$3.95. *Less cover, F.E.T. incl.

AM Tuner HFT94: Matches HFT 90. Selects "hi-fi" wide (20-9000 cps @ -3 db) or weak-station narrow (20-5000 cps @ -3 db) bandpass. Tuned RF stage for high selectivity & sensitivity. Precision eye-tronic® tuning. "One of the best available." — HI-FI SYSTEMS. Kit \$39.95. Wired \$65.95. Incl. cover & F.E.T.

New FM/AM Tuner HFT92 combines renowned EICO HFT90 FM Tuner with excellent AM tuning facilities. Kit \$59.95. Wired \$94.95. Incl. cover & F.E.T.

New AF-4 Economy Stereo Integrated Amplifier provides clean 4W per channel or 8W total output. Kit \$38.95. Wired \$64.95. Incl. cover & F.E.T.

HF12 Mono Integrated Amplifier (not illus.): Complete "front end" facilities & true hi-fi performance. 12W continuous, 25W peak. Kit \$34.95. Wired \$57.95. Incl. cover.

New HFS3 3-Way Speaker System Semi-Kit complete with factory-built 3/4" veneered plywood (4 sides) cabinet. Bellows-suspension, full-inch excursion 12" woofer (22 cps res.) 8" mid-range speaker with high internal damping cone for smooth response, 3 1/2" cone tweeter, 2 1/4 cu. ft. ducted-port enclosure. System Q of 1/2 for smoothest frequency & best transient response. 32-14,000 cps clean, useful response. 16 ohms impedance. HWD: 26 1/2", 13 1/8", 14 3/8". Unfinished birch \$22.50. Walnut, mahogany or teak \$87.50.

New HFS5 2-Way Speaker System Semi-Kit complete with factory-built 3/4" veneered plywood (4 sides) cabinet. Bellows-suspension, 3/8" excursion, 8" woofer (45 cps. res.), & 3 1/2" cone tweeter, 1 1/4 cu. ft. ducted-port enclosure. System Q of 1/2 for smoothest freq. & best transient resp. 45-14,000 cps clean, useful resp. 16 ohms.

See Eico at IRE Booth 3505

HWD: 24", 12 1/2", 10 1/2". Unfinished birch \$47.50. Walnut, mahogany or teak \$59.50.

HFS1 Bookshelf Speaker System complete with factory-built cabinet. Jensen 8" woofer, matching Jensen compression-driver exponential horn tweeter. Smooth clean bass; crisp extended highs. 70-12,000 cps range, 8 ohms. HWD: 23" x 11" x 9". Price \$39.95.

HFS2 Omni-Directional Speaker System (not illus.) HWD: 36", 15 1/4", 11 1/2". "Fine for stereo" — MODERN HI-FI. Completely factory-built. Mahogany or walnut \$139.95. Blond \$144.95.

New Stereo Automatic Changer/Player: The first & only LUXURY unit at a popular price! New unique engineering advances no other unit can offer regardless of price: overall integrated design, published frequency response stylus pressure precision-adjusted by factory, advanced design cartridge. Compact: 10 3/4" x 13". Model 1007D: 0.7 mil diamond, 3 mil sapphire dual stylus — \$59.75. Model 1007S: 0.7 mil & 3 mil sapphire — \$49.75. Includes F.E.T.

†Shown in optional Furniture Wood Cabinet WE71: Unfinished Birch, \$9.95; Walnut or Mahogany, \$13.95.

††Shown in optional Furniture Wood Cabinet WE70: Unfinished Birch, \$8.95; Walnut or Mahogany, \$12.50.

EICO, 33-00 N. Blvd., L.I.C. 1, N. Y.

Show me how to SAVE 50% on easy-to-build top-quality Hi-Fi. Send FREE catalog, Stereo Hi-Fi Guide plus name of neighborhood EICO dealer.

Name.....


Address.....

City..... Zone..... State.....

Listen to the EICO Hour, WABC-FM, N.Y., 5.5 MC, Mon. to Fri. 7:15-8 P.M., Sat. 11-12 P.M. Ask dealer about EICO's Stereo Records Bonuses.

© 1960 by EICO, 33-00 N. Blvd., L.I.C. 1, N.Y.

The specs prove it...your best buy is

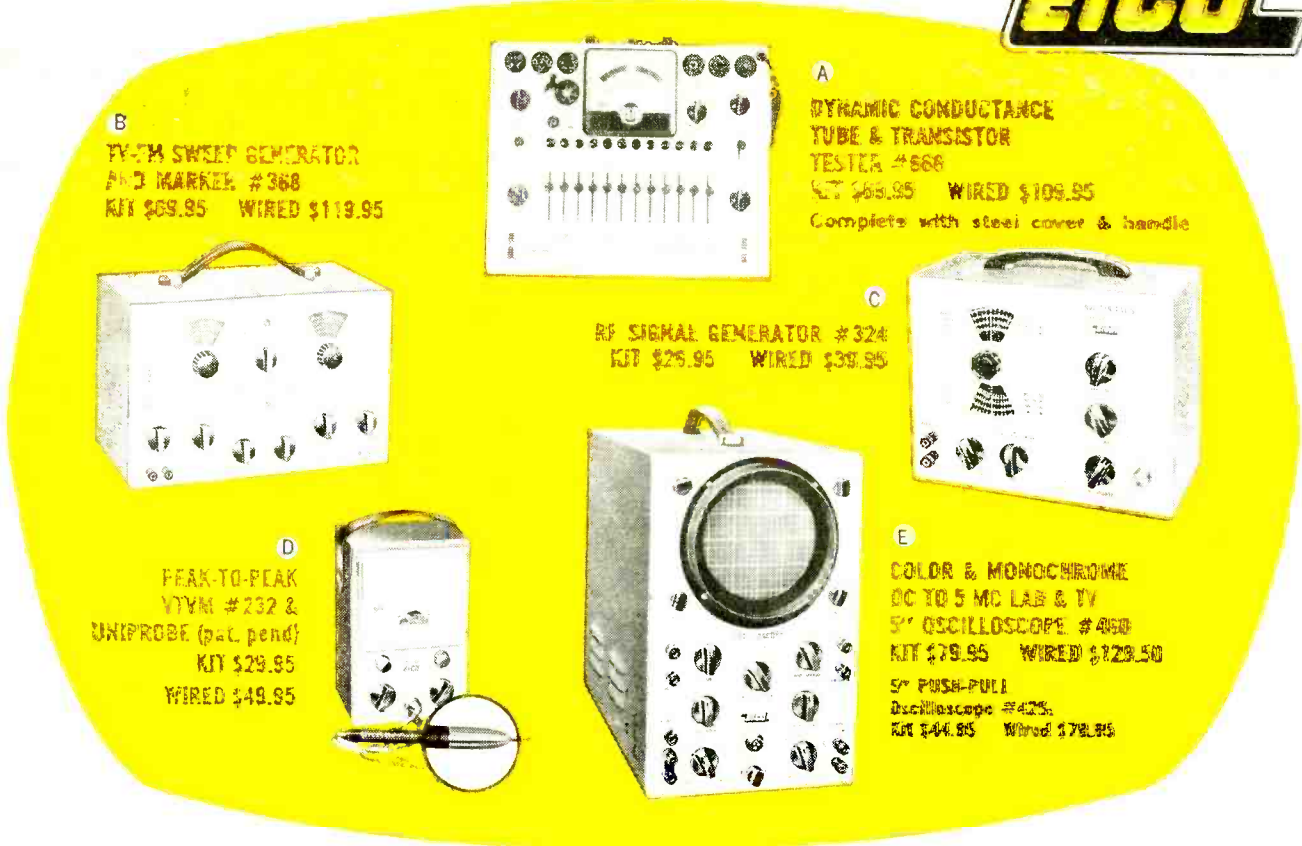

B
VY-PM SWEEP GENERATOR
AND MARKER #368
KIT \$69.95 WIRED \$119.95

A
DYNAMIC CONDUCTANCE
TUBE & TRANSISTOR
TESTER #668
KIT \$65.95 WIRED \$109.95
 Complets with steel cover & handle

RF SIGNAL GENERATOR #324
KIT \$25.95 WIRED \$39.95

D
PEAK-TO-PEAK
VYVM #232 &
UNI-PROBE (pat. pend)
KIT \$29.95
WIRED \$49.95

E
COLOR & MONOCHROME
DC TO 5 MC LAB & TV
5" OSCILLOSCOPE #460
KIT \$79.95 WIRED \$129.50
5" PUSH-PULL
Oscilloscope #425
KIT \$44.95 WIRED \$79.95

A Tests all receiving tubes (picture tubes with adapter), n-p-n and p-n-p transistors. Composite indication of Gm, Gp & peak emission. Simultaneous selection of any one of 4 combinations of 3 plate voltages, 3 screen voltages, 3 ranges of continuously variable grid voltage (with 5% accurate pot.). Sensitive 200 ua meter. 10 six-position lever switches: freepoint connection of each tube pin, 10 pushbuttons: rapid insert of any tube element in leakage test circuit. Direct reading of inter-element leakage in ohms. New gear-driven rollchart. **CRA Adapter \$4.50.**

E Entirely electronic sweep circuit with accurately-biased inductor for excellent linearity. Extremely flat RF output. Exceptional tuning accuracy. Hum and leakage eliminated. 5 fund. sweep ranges: 3-216 mc. Variable marker range: 2-75 mc

in 3 fund. bands, 60-225 mc on harmonic band. 4.5 xtal marker osc., xtal supplied. Ext. marker provision. Attenuators: Marker Size, RF Fine, RF Coarse (4-step decade). Narrow range phasing control for accurate alignment.

F 150 kc to 435 mc with ONE generator in 6 fund. bands and 1 harmonic band! $\pm 1.5\%$ freq. accuracy. Colpitts RF osc. directly plate-modulated by K-follower for improved mod. Variable depth of int. mod. 0-50% by 400 cps Colpitts osc. Variable gain ext. mod. amplifier: only 3.0 v needed for 30% mod. Turret-mounted, slug-tuned coils for max. accuracy. Fine and Coarse (3-step) RF attenuators. RF output 100,000 uv, AF output to 10 v.

G Uni-Probe -- exclusive with EICO -- only 1 probe performs all functions: half-turn of probe tip selects DC or AC-Ohms. Calibration without re-

moving from cabinet. Measure directly p-p voltage of complex & sine waves: 0-4, 14, 42, 140, 420, 1400, 4200. DC/RMS sine volts: 0-1.5, 5, 15, 50, 150, 500, 1500 (up to 30,000 v. with HVP probe, & 250 mc with PRF probe). Ohms: 0.2 ohms to 1000 megohms. 4 1/2" meter, can't-burn-out circuit. 7 non-skip ranges on every function. Zero center.

H Features DC amplifiers! Flat from DC to 4.5 mc, usable to 10 mc. Vert. Sens.: 25 mv/in.; input Z 3 megohms; direct-coupled & push-pull throughout. 4-step freq.-compensated attenuator up to 1000:1. Sweep: perfectly linear 10 cps - 100 kc (ext. cap. for range to 1 cps). Pre-set TV V & H positions. Auto sync. lim. & ampl. Direct or cap. coupling; bal. or unbal. inputs; edge-lit engraved lucite screen with dimmer control; plus many more outstanding features.

FREE CATALOG shows you HOW TO SAVE 50% on 65 models of top quality professional test equipment. MAIL COUPON NOW!

***PAT. PEND.**

New Transistor Portable Radio RA-6
 Kit \$29.95
 Wired \$49.95
 Incl. F.E.T.; less 9V batt. Preamplified RF, IF xfmrs, push-pull audio; 6" spkr.

NEW Power & Bias Supply for Transistorized Eqp. = 1020 *
 Kit \$19.95
 Wired \$27.95

NEW Tube & CRT Fil. Tester = 612
 Kit \$3.95
 Wired \$5.95
 Fast-checks radio/TV tubes, pilot lamps, etc.

Series/Parallel R-C Combination Box = 1140
 Kit \$13.95
 Wired \$19.95

Tube Tester = 625
 Kit \$34.95
 Wired \$49.95
 • tests 600 mil series string type tubes
 • illuminated roll-chart
 Pix Tube Test Adapter \$4.50

6V & 12V Battery Eliminator & Charger = 1050
 Kit \$29.95
 Wired \$38.95
 Extra-filtered for transistor eqpt. = 1060 Kit \$38.95
 Wired \$47.95

20,000 Ohms/Volt V-O-M = 565
 Kit \$24.95
 Wired \$29.95
1000 Ohms/Volt V-O-M = 536
 Kit \$12.90
 Wired \$14.90

33-00 Northern Blvd. L.I.C. 1, N.Y.
 Add 5% in the West. © 1959

TURN PAGE FOR MORE EICO VALUES

R-C Bridge & R-C-L Comparator = 950B
 Kit \$19.95
 Wired \$29.95
 Reads 0.5 ohms-500 megohms, 10 mmfd-5000 mfd, power factor

VTVM Probes

	Kit	Wired
Peak-to-Peak	\$4.95	\$6.95
RF	\$3.75	\$4.95
High Voltage Probe-1		\$6.95
High Voltage Probe-2		\$4.95
Scope Probes		
Demodulator	\$3.75	\$5.75
Direct	\$2.75	\$3.95
Low Capacity	\$3.75	\$5.75

EICO
 23-00 Northern Blvd.
 L.I.C. 1, N.Y.

Show me HOW TO SAVE 50% on Test Instruments Hi-Fi Ham Gear. Send free Stereo Hi-Fi Guide. Send me FREE Catalog, name of neighborhood dealer.

Name _____
 Address _____
 City _____ Zone _____ State _____

BRAIN AN ELECTRIC COMPUTER

By DAVID STAFFORD-CLARK*

The following is part of an address delivered to the Annual General Meeting of the Mental Health Research Fund given in London early in 1959. In view of the great interest in electronic computers and their vast impact on our current thinking and research, we have arranged with Dr. Stafford-Clark, an eminent thinker in his field, to bring to our readers the latest thoughts on biological vs. electronic computers. —H.G.

It is perhaps in the study of man's conscious and unconscious reaction with his environment in its widest sense that the method of psychological inquiry has still its greatest single contribution to make. Man has been called a communicating animal; and certainly he conveys and experiences his loves and hates, his hopes and fears, his values and principles, and the greatest discoveries of his mind, through a communications system which is the most complicated and yet most flexible known to exist. The mathematical theory of communications, which can be related to psychological methods of inquiry and concentrated in the dedicated study of man's mind by man himself, may provide ultimately one of the keys by which all our interlocking processes of human existence, and particularly of practical psychiatric knowledge, can be opened for our fuller understanding.

There is a good deal to be said for using the working analogy of an electronic computer to convey something of the way in which the brain works in this sense. But the brain is an electronic computer with fifteen thousand million separate cells, of possibly immeasurable complexity, which provides for its remarkable flexibility and wonderful precision. We have already seen that the electroencephalogram, crude though its information must yet remain, at least supports the view that it is in its electrical function that we must seek the practical key to the work of the brain. Its communication is by electrical signals, and their transmission from neurone to neurone through synapses is probably the way in which patterns of activity are regulated and controlled. It has indeed proved possible to use the mathematical theory of communications to draw some tentative conclusions about this aspect of the work of the brain (Ashby, 1952).

But all models which have so far been constructed to give working analogies of brain function have taken the source of their electrical power for granted. Such power has in fact been piped in from the local main supply in the laboratory, or stored in accumulators [batteries] hitched on to the working model. *I am sure that in all our research we must never forget that the brain is the only electronic computer which manufactures its own electricity biochemically as it goes along.* In studying the functions of the brain, therefore, we have to remember that we are at least two removes from the subjective experiences, and from the output in terms of behavior, which we seek to explain. At one remove there is the electrical network, in

all its wonderful complexity and beautiful intricacy; and at the second remove there is the biochemical process, also wonderfully intricate and many-sided, whereby the brain continues to live, to breathe, to gain its nourishment and to make its power. It is in the biochemical aspects of brain function in health and illness that we see those changes which may affect both conductivity and availability of electrical power within the system. And it is the ultimate translation of this power into electrical signals, which are themselves the only measurable accompaniment to thought and feeling, which presumably alone makes these processes possible.

Our relative technical proficiency in measuring biochemical changes must never blind us to the fact that these are of ultimate importance only in their effect upon the patterns of electrical activity, conduction, communication and control in the final functioning of the brain; and as clinicians we must never forget that communication remains the ultimate key to the treatment of schizophrenia, or indeed of any other kind of illness. In one sense the cardinal features of schizophrenia may perhaps be regarded as respectively: (1) A failure to make the usual interpretation of external or internal events; for example, to understand what is going on in the world outside, or indeed what might be going on in one's own body. (2) A failure to communicate in the usual way with other people. (3) A failure to integrate interpretation and communication, within one's self or with others, in a way which will allow even the first two difficulties to become apparent in their full nature to any but the trained observer.

There is, in fact, so far as brain function is concerned, a failure of communication and control. Clinically it is this failure of communication and control which brings the schizophrenic to the doctor. However skilful and appropriate our physical treatment of schizophrenia may become as the result of refinement in our knowledge and understanding, both of the biochemical processes which may underlie it and the electrophysiological processes whose secondary disturbances ultimately bring about the illness. It remains true that we can treat patients successfully, and restore them to true health and happiness, only if we gain contact with them at a human and personal level, and give them thereby the bridge over which they may cross back to normal harmony and understanding with their fellows. This is the ultimate aim in every aspect of clinical research in psychiatry; and indeed it is the ultimate aim of all forms of research directed toward the understanding or relief of mental illness.

END

*MD, FRCP, DPM. Physician-in-charge, Department of Psychological Medicine, and director of the York Clinic, Guy's Hospital, London; consultant physician, Bethlem Royal and Maudsley Hospitals, and Institute of Psychiatry, University of London

Repairing and installing marine radiotelephones can increase your shop's income

SMALL BOAT RADIOTELEPHONES



A Raytheon RAY-12 radiotelephone in use.

By **ELBERT ROBERSON**

TODAY any owner of a small boat can carry a two-way radiotelephone aboard. The equipment takes up little space, and the owner need not take a license test or even know the difference between a transistor and a quenched gap. And the recent development of outboard cruisers with electric starting motors, generators and 6- or 12-volt batteries means that marine radiotelephone activity should grow all over the country. Now is a good time to get acquainted.

The primary purpose of marine radiotelephony is to promote safety. Equipment is designed to be as simple and foolproof as possible, and to be compact in size as well as easy on the batteries. The standard frequency range is from 2 to 3 megacycles, and transmitter power runs from 15 to 150 watts. The transmitter and receiver must operate on a number of preset channels, with all critical controls behind the

panel, available only to the service technician, who must have a commercial Second-Class or higher FCC license.

Operator controls are limited to the bare essentials. The simplest phones have only a receiver on-off switch and volume control, a channel-selector ganged-wafer switch that controls the operating frequency of both the transmitter and receiver, and a transmitter on-off switch. A push-to-talk button on the microphone or telephone handset, or a panel switch, disables the receiver, switches the antenna and puts the transmitter on the air for talk periods. More elaborate equipment has such extras as a receiver tuning control for the standard-broadcast band, automatic noise limiter and squelch controls, transmitting antenna tuning trimmer, and loudspeaker-handset switch for receiver audio output.

Receiver circuits

To keep battery current drain to a minimum, as few tubes as will provide the essential receiver functions are used. The superhet circuit is employed exclusively, with the oscillator frequency controlled by a quartz crystal for each communication channel. The mixer-input circuit usually is tuned by one inductor and separate trimmer capacitors for each channel, the channel being automatically selected by the channel switch. Sometimes, however, separate slug-tuned coils are used. A ganged variable capacitor and separate mixer input and self-excited oscillator

coils are used to cover the broadcast band.

Many sets have an old familiar line-up of tubes—6K8 mixer; 6SK7 if amplifier; 6SQ7 second detector, AVC and first audio, and a 6V6 audio power amplifier.

While larger phones may have more modern tubes, with an rf stage before the mixer and, perhaps, an additional if amplifier, automatic-noise-limiter diode and a squelch tube, there is nothing tricky about the circuits. One feature, however, which differs from any other simple multi-band receiver design is the crystal oscillator. The most common circuit is a form of Pierce oscillator—a simplified version is shown in Fig. 1, with the crystal effectively between the grid and plate of the oscillator section of the mixer tube, providing positive feedback at the crystal's resonant frequency. On the broadcast band, a coil and variable capacitor are switched in, resulting in a form of the familiar Hartley circuit. One of the several crystals for the different channels (ground to frequencies 455 kc removed from signal frequency) or the broadcast-band oscillator coil is selected by the channel switch for frequency changing.

Boat receivers are particularly sensitive to interference from the engine ignition system, since there is ordinarily no shielding around the engine and spark pulses are transmitted directly to the telephone antenna. To minimize this sharp-peaked noise, simple noise

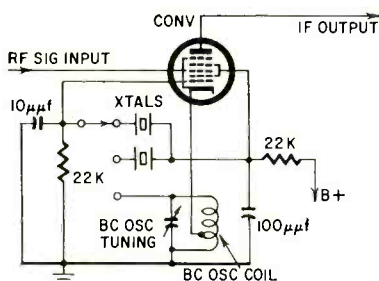


Fig. 1—Simplified Pierce oscillator used in radiotelephone receivers.



Radiotelephones are available for the smallest boats. Here a Sonar portable is being hooked up.



Transmitting frequencies must be measured periodically.

Trivoli Radio & Marine

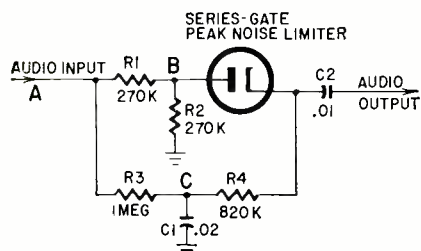


Fig. 2—Noise limiter found in the Bendix model 42A radiotelephone.

limiters are common. Fig. 2 shows one such arrangement, used in the Bendix model 42A radiotelephone.

An unmodulated signal carrier establishes a negative dc potential at point A, which is divided across the two 270,000-ohm resistors (R1 and R2), which form the load for the second detector. Therefore, half of the detector's output voltage is impressed on the noise limiter's anode. The constants of the filter (R3, R4 and C1) are such that point C is held to the average level of signal. Normally, point B is positive with respect to point C, so the diode conducts, passing the signal. However, on receipt of a noise pulse, point B shoots sharply negative (while C remains at the average level), cutting off the diode and interrupting the audio circuit.

Because the receivers have avc, sensitivity jumps up to maximum between received signals, resulting in an annoying amount of noise. Accordingly, a squelch circuit is often used. Many

variations are found, but the principle is illustrated by the Bendix 42A which employs the circuit shown in Fig. 3.

The between-signals noise level establishes a certain negative avc potential across the squelch control (R1) which is set so the squelch tube conducts. This pulls the grid of the af amplifier in the negative direction to cut-off. A signal causes the avc negative-voltage increase to cut off the squelch tube. When this happens, the grid of the audio amplifier swings toward

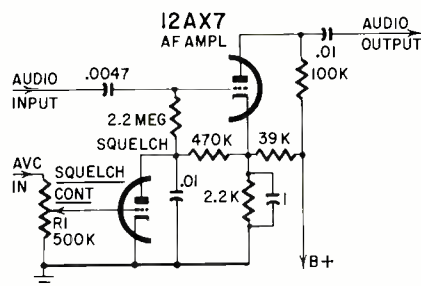


Fig. 3—This squelch circuit is used by Bendix in their model 42A.

positive, the tube conducts, and the signal goes on through.

Transmitter circuits

Because electrical power on a small boat is limited, transmitters are designed to get a signal on the air with the fewest number of tubes. The rf section, accordingly, consists of the minimum legal lineup: a crystal-controlled oscillator and one rf amplifier

stage, operating straight through on the crystal's fundamental frequency. Two amplifier tubes are used in parallel when more than one tube's worth of power is needed.

For simplicity, the oscillator uses either some form of Pierce circuit or a modified Colpitts. Because neither circuit contains tuned elements, channel changing is just a matter of switching from one crystal to another. An example of the Colpitts-derived oscillator is used in the Kaar TR249, shown in Fig. 4. In this oscillator, the tube cathode is isolated above ground by rf choke RFC1, and positive feedback from the output to the grid circuit is provided by capacitors C1 and C2.

In the rf amplifier, extreme care is necessary to suppress harmonics, since many of the second harmonics, easily radiated by the short antennas used on boats, fall on critical aircraft frequencies. Therefore, grid drive and bias are carefully set and tuned plate circuits are high-C to give maximum operating Q.

The FCC requirement that a fre-

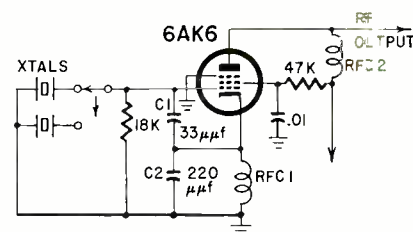


Fig. 4—Colpitts-derived oscillator used in the Kaar TR249.



The Bendix 42A radiotelephone with its transistor power supply.

quency-governing adjustments be preset by a licensed technician could be met in a number of ways. One, of course, would be to have separate tank tuning capacitors in the rf amplifier plate circuit, each pretuned to the desired frequency and selected by the channel switch. But this would add to the transmitter's bulk and cost. Since space and economic considerations are very important in this field, separate inductor taps for each channel are often used instead. Mechanically, this is done by using clip leads tapped onto the plate coil and brought to the channel switch. To keep plate voltage out of the tank coil, which, of course, must be handled during the tuning operation, parallel plate feed is the rule.

To attenuate harmonic output, Hudson American Corp. transmitters have a Faraday shield between the rf amplifier plate coil and the antenna coupling coil. However, most transmitters have pi-network—or low-pass filter—rf output. A representative circuit is shown in Fig. 5.

The tube is most commonly a 6L6 or 807, capacitively coupled to the oscillator. Rectified drive current develops grid-bias voltage across R1, which may be supplemented somewhat through the use of a bypassed cathode resistor. This latter feature also tends to limit off-resonance plate current to a safe value. A jack in the cathode circuit permits metering while the equipment is being tuned.

Voltage from the modulated B-plus source is supplied to the screen and is grounded for rf by C1, whose value is chosen to act as an rf ground without being high enough to soak up any serious amount of audio voltage. Careful layout (and sometimes parasitic suppressor resistors in plate, screen or grid circuit) keep the amplifier "cool," without need for neutralization.

Although a fixed value of plate tuning capacitance is shown (C3, Fig. 5), two or more additional capacitors are used when a wide spread of frequencies must be covered, to keep tank Q at the optimum value. Such capacitors are cut in on channels where they are required by another wafer on the channel switch. Small trimmers are also sometimes used at this point to fine-tune the tank, although this is not ordinarily essential, because of the broadening out of amplifier tuning

Hudson-American's Nautilus I has a 135-watt output.



APELCO AE-75M has a plate current meter on the panel.



RCA makes this 20-watt radiotelephone. It is their ET-8059 Golden Sentry. The booster control is the transmitter's antenna tuning trimmer.

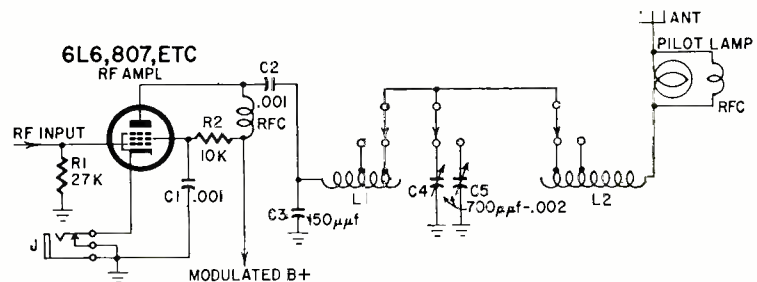
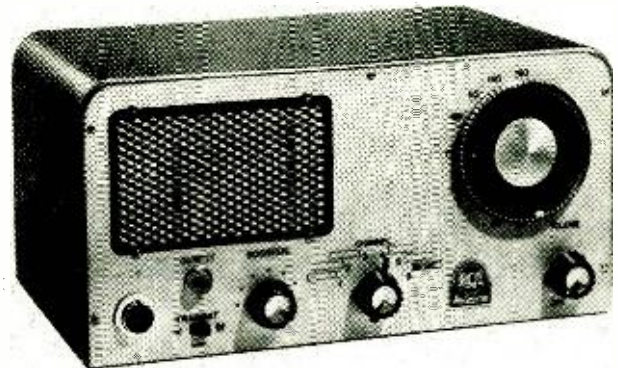


Fig. 5—Low-pass filter between rf amplifier output and antenna attenuates harmonic output of transmitter.

when the antenna load resistance is coupled in. The main plate tuning is accomplished by fastening the taps to the proper turns on the coil.

Coupling to the antenna is provided by C4, C5 and additional capacitors in broad-frequency-range transmitters. Ordinarily, two values are enough for covering the two sets of normal marine-band frequencies—one around 2.1 mc and the other around 2.6. Jumpers on the channel switch connect in the capacitor required for the family of frequencies in use.

On all except the largest vessels (such as lofty-masted sailboats), the antenna is very much less than one-quarter wavelength long, so it must be loaded inductively. The antenna is tuned with clip leads, and relative output is indicated by a pilot lamp shunted by a very small coil to prevent filament burnout or introducing lamp resistance directly into the antenna circuit.

Some telephones also incorporate a variable inductor (not shown on the diagram) in series with the antenna loading circuit so the operator can touch up antenna tuning when necessary to compensate for unpredictable detuning caused by movement of the boat's rigging, etc.

Modulators

Some very small radiotelephones use the receiver's af power amplifier as a transmitter modulator. Usual practice is, however, to have a separate modulator. The simplest arrangement, and one which has been very popular, is shown in Fig. 6. Because the carbon microphone has a high gain, no speech amplifier is necessary, the modulator-tube grid being driven directly by the microphone transformer. Microphone current is obtained from the tube cathode, although it is sometimes taken from the B-plus line through a resistor. The FCC requirement that bandwidth be limited to frequencies required for the transmission of speech is met by using a microphone of limited bandpass, with rapid cutoff above 3,000 cycles. Overmodulation is prevented by limiting average modulation levels to about 75%.

A sensitive carbon microphone is used directly in some equipment to drive a pair of modulators as large as 807's. In others, a speech amplifier stage is used, with the carbon microphone in the cathode circuit.

An example of the latest practice employs a crystal microphone with a resistance-coupled speech amplifier the output of which is fed through a 12AX7 speech clipper and an audio filter into a pair of paralleled 6L6's in a single-ended modulator. Usual practice, however, is to use push-pull when more than one modulator tube is required to produce the necessary audio power. Diode peak-limiting circuits are also used to eliminate overmodulating the transmitter.

Power supplies

Tube heaters are energized in series,

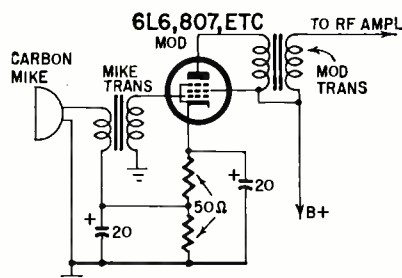


Fig. 6—A popular radiotelephone modulator circuit.

parallel and series-parallel arrangements directly from the boat's battery of 6, 12 or 32 volts. Plate power is supplied by dynamotors, vibrator power supplies or most recently, by transistor power supplies. Designs are the same as are common in other mobile equipment. Small units have only one plate power supply. Its output is transferred from receiver to transmitter and vice versa as required. This would be uneconomical in the larger units, so they use a small power supply for the receiver and control circuits, with a high-voltage dynamotor for transmitter power.

A few units are built to operate from 117 volts ac, supplied either by an engine-driven alternator or a converter fed from the boat's dc lines. These are used rarely, and only on the largest craft.

Installation and maintenance

In a boat, a solid and well-thought-out installation is essential. Equipment should be placed where it will be convenient to operate, but also with consideration to short antenna and ground leads, as well as power input lines. Because there isn't much voltage to begin with on a small boat, extra-heavy wiring is standard to minimize voltage drop, especially for transmitting when comparatively heavy current is being drawn.

Radiotelephone equipment should be connected to the battery, switchboard or accessory power outlet by cables which are not used for another load. The lines should be fused at the power end, but in the hot lead only. A fuse or circuit breaker should never be installed in the ground lead of a power feeder.

Manufactured antennas available from radiotelephone manufacturers are used on most powerboats. They are supplied with hardware for mounting alongside a cabin or on deck. The main thing is to provide enough mechanical strength in the supporting members to withstand the strain when the boat is rolling or pitching violently. A great many carelessly installed antennas have either broken or pitched overboard through lack of care in installation. Another important point is to be extra careful of the insulation in mounting and lead-in insulators—a small amount of leakage caused by a film of salt spray on an inadequate insulator can seriously affect transmitter range. On sailboats, a wire is secured to

the mast or hung from a point aloft, or a span of the boat's standing rigging, such as a backstay or a shroud, is isolated by splicing in insulators. The important thing is to choose a location for the antenna wire where it will be as much in the clear as possible.

A radiotelephone will perform, after a fashion, with the boat's engine as a ground. However, for maximum transmitting range, the ground-connection area should be as great as the construction of the boat will allow. A ground consisting of a sheet of copper with an area of not less than 12 square feet is considered the minimum for satisfactory service. Such ground plates are screw-fastened to a flat area on the bottom of the hull or keel and connection made by a bolt through the hull. Plates are sometimes installed inside the bottom of small high-speed boats. In this case, there is no direct connection to the ground, the capacitance of the plate to ground serving instead.

Small-boat radiotelephones develop trouble more from inactivity or misuse than from wearing out. The main factors in routine maintenance are to make sure that the equipment is kept clean and dry, relay and switch contacts are bright and components such as vibrators and tubes are up to par. A large part of the service technician's difficulties arise from "operator trouble,"—the layman owner either does not work the buttons in the right manner or he does not understand some special circumstance that arises. In this category are such "defects" as strong static common in summer thundersqualls; excessive interference from other stations on a channel common over weekends and holidays during the boating season, or just plain ordinary being out of transmitting range for the amount of power on board.

So one of the important parts of installing and maintaining this gear is that of making sure the owner understands the limitations of the equipment, as well as how to operate his gear.

Receiver servicing is just the same as in any equipment you find ashore. And, with their simplicity, the transmitters seldom present any problems that cannot be solved with a visual rf probe—an ordinary neon bulb, that is.


Become acquainted with their little peculiarities, and marine radiotelephones offer an interesting field in which to work. END

VAIN HOPE

By Phyllis Barlow

My goal is that customers
All will agree
My service is strictly
"Hi-Fi" not "Hi-Fee"!

MINIATURE FRONT END for FM RECEIVERS

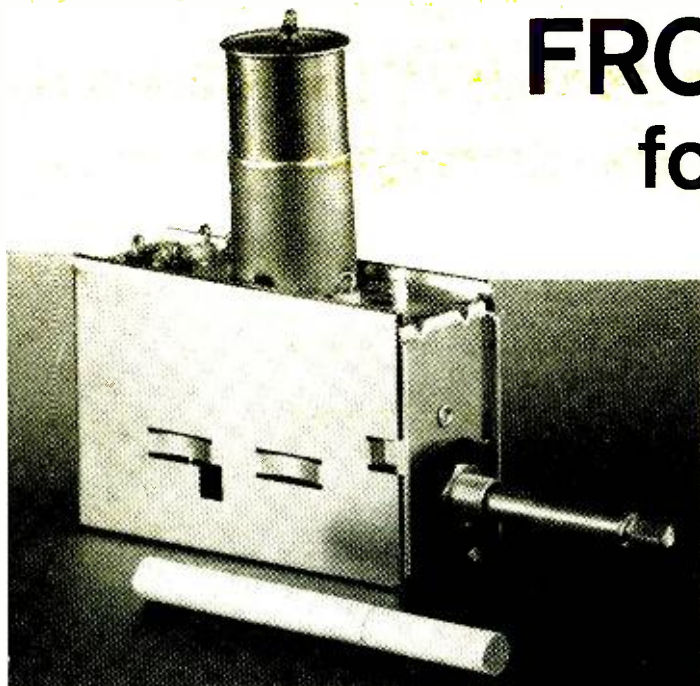

By following TV tuner techniques, the manufacturer has come up with an FM tuner that measures only 4 1/4 x 1 1/4 x 3 1/4 inches—including the tube

By E. D. LUCAS, JR.

A MINIATURE FM tuner—rf amplifier and mixer-oscillator—that employs only one tube is now being supplied by Standard Coil Products to some eight manufacturers of hi-fi receivers. A modified version may be made available to auto radio manufacturers in the near future. The tiny unit, which takes up less than 15 cubic inches, depends on a printed-circuit board to keep its size down.

As shown in Fig. 1, the input from the antenna is fed through feedthrough capacitor C16 and a bandpass filter (C15, L7, L8) to the cathode of a grounded grid amplifier (triode section of a 6AQ8 or a 6DT8). The second stage, the other triode section of the tube, is an autodyne oscillator-mixer that has controlled regeneration.

The unit is tuned by varying the inductances of L1 and L2 with brass slugs on a lead screw. The lead screw is coupled to the main tuning shaft with a sliding coupling. The slugs in L1 and L2 are individually adjusted at the factory so the frequency of the tuned circuits is correctly set for the high end of the FM band. L10 and L9 are shorted loops that enable the manufacturer to adjust the low end of the band. Tickler coil L4 is 1 1/2 turns wound around L2, and linked to it by mutual inductance. It is adjusted for enough feedback to start the oscillator.

To improve the tuner's gain, an additional regenerative circuit provides if

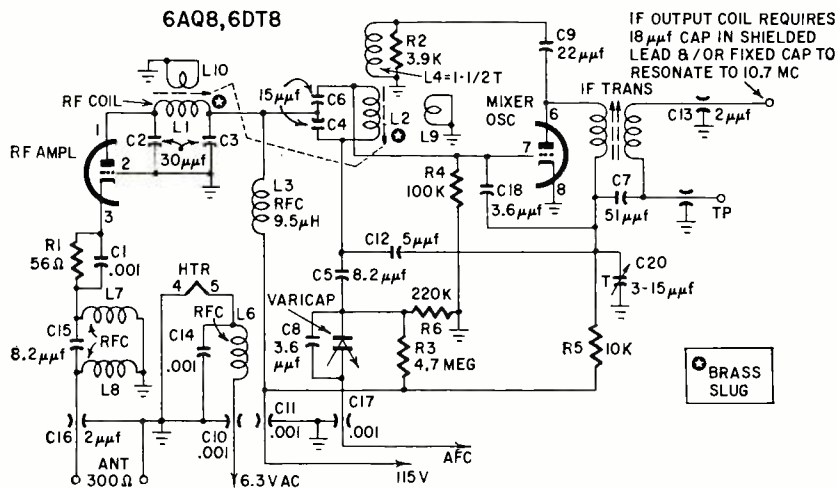


Fig. 1—Circuit of the single-tube FM front end.

feedback through C18 and C12 to the tuned tank circuit of the grid. Trimmer C20 adjusts the amount of regeneration, making it possible to compensate for variations in components. Without C20, capacitors and resistors would have to have tighter tolerances, which would increase the tuner's cost.

Another interesting design point (Fig. 2) is that the oscillator tank circuit contains a capacitor bridge, with C4 and C6 "split" to furnish a cold point—effectively zero for oscillator voltage—at their junction. The other arms of this bridge contain the grid capacitance of the oscillator and a composite afc capacitance consisting

of the combined capacitances of C5, C12, C8 and the Varicap.

One reason the capacitor bridge is designed with such a cold point is to keep oscillator radiation to a minimum. Another is that by maintaining this point at zero for oscillator voltage, it is possible to connect the associated rf amplifier circuit without changing the oscillator frequency. The cold point eliminates interference between the rf and oscillator tuned circuits. Should a measurable amount of oscillator voltage ever appear at this cold point, it would flow through the rf circuit. Since this circuit is tuned to a different frequency, such a flow would tend to pull

FM SENSITIVITY SWITCHES

Two sensitivity circuits in modern FM tuners

the oscillator, resulting in mistracking.

Automatic frequency control (afc) is accomplished by a change in the capacitive reactance of a Varicap. It is so selected that a variation in back bias will vary its capacitive reactance. Thanks to this characteristic, an error signal indicating off-frequency operation can be fed back from the FM receiver's discriminator or ratio detector for automatic oscillator-frequency correction. Capacitors C5, C12 and C8 are interdependent from both an if feedback standpoint (as previously described in connection with the capacitor bridge) and from the standpoint of afc sensitivity. The design in Fig. 1 will provide an oscillator frequency variation of 100 kc per volt applied to the afc terminal. Without regard to the interdependence just noted, a reduction in C8's value or an increase in C5's value or both will increase afc sensi-

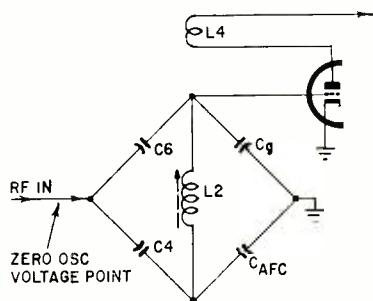


Fig. 2 — Bridge circuit is in the oscillator grid.

tivity. If such a modification is made, the autodyne circuit must be rebalanced, both as regards the cold point and the if feedback.

The voltage divider formed by R5, R3, and R6 provides the necessary positive voltage to back-bias the Varicap so the afc voltage can swing positively as well as negatively without causing current to flow in the Varicap.

The tuner's output is conventional through a double-tuned if transformer whose secondary feeds directly into the grid of the first if amplifier. The tuner output transformer's secondary requires approximately 18 μf of capacitance in the shielded lead to the first if stage, or sufficient additional capacitance in the form of a fixed capacitor to bring the total value up to about 18 μf , so the circuit will resonate at 10.7 mc.

Standard Coil is manufacturing two principal versions of this tuner, differing only mechanically, in the shaft arrangement. One version, used in receivers having a slide rule type of dial, has no gear-reduction unit connected to the tuning shaft, and 5½ complete rotations of this shaft are required for tuning over the full FM band. The other version has a gear-reduction unit which drives an outer shaft coaxial with the tuning shaft. This outer shaft can be used to drive a pointer directly. This pointer, normally used with a circular dial, will indicate complete coverage of the FM band through an arc of 254°. **END**

IN the early days of radio, before the advent of variable-mu tubes, many sets had local-distant switches to control a set's gain or signal input. After being practically extinct for a great many years, these sensitivity controls are beginning to show up again—particularly in high-quality FM tuners.

Fig. 1 is the front-end and age circuit in the Scott 310-C FM tuner. The FM if signal is tapped off the grid of the first limiter and rectified to produce an age voltage across load resistor R20. This voltage is filtered and fed to the grid of the input section of the cascode rf amplifier. When the NORMAL-DISTANT switch is in the DISTANT position, the bias on the rf amplifier is reduced and it operates at maximum gain.

It is not desirable to operate the cascode at maximum gain at all times because its linearity is not as good as when operating with a somewhat higher bias. The less linear an amplifier, the more sensitive it is to overloading. Its response to spurious signals also increases. The NORMAL position of the switch applies optimum age bias to the tube, increasing its linearity and ability to handle high signal levels with minimum distortion.

Fig. 2 shows the rf amplifier and SENSITIVITY switch in the Sherwood S-3000 FM tuner. When the switch is

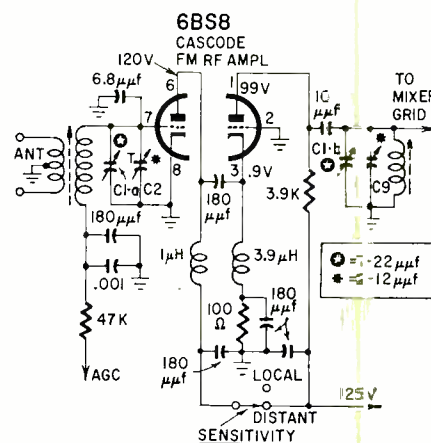


Fig. 2—The Sherwood S-3000 uses this circuit.

thrown to LOCAL, B-plus voltage is removed from the first half of the cascode amplifier. Strong local signals are fed—without amplification—to the grid of the second half of the cascode through the inter-electrode capacitance of the input section of the stage. Switching to DISTANT places B-plus voltage on the input section so the cascode operates with its normal gain determined by the age voltage applied to the grid of the input section. **END**


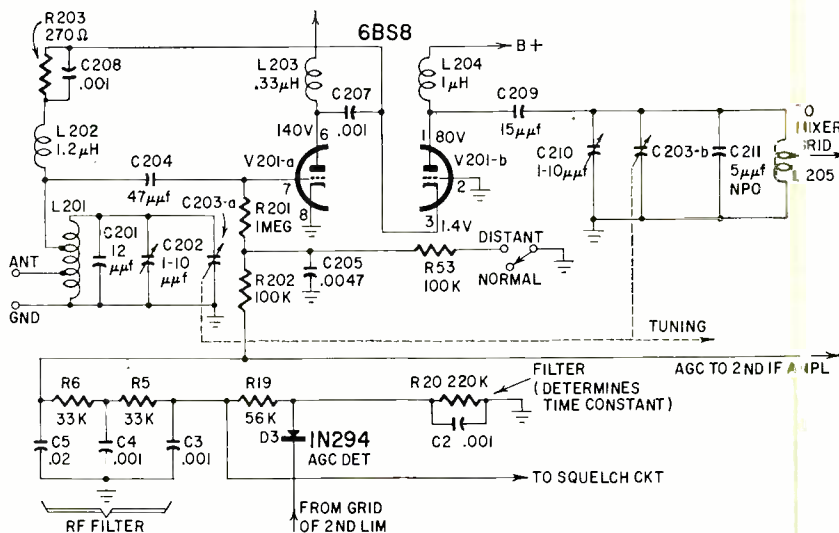


Fig. 1—Sensitivity circuit in the Scott 310-C FM tuner.

BUILD THIS TRANSISTOR AUTO RADIO

...it has signal seeker

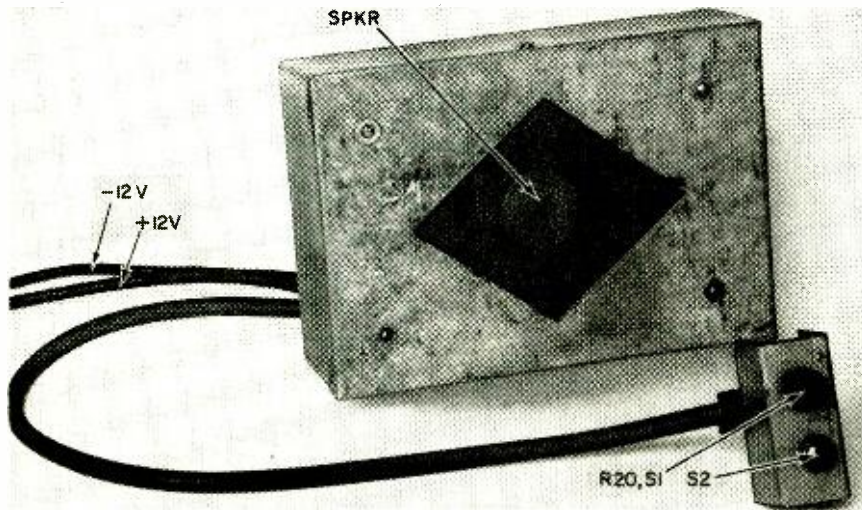

Search-and-tune receiver is controlled by one knob and one pushbutton on the car's dash. The rest of the set is tucked into some out-of-the-way spot

By A. V. J. MARTIN

HAVE a gripe with a sports car. Said gripe is the radio or rather the lack of one. Now adding a radio to a car is a rather simple matter, but I have some qualifications:

- ▶ I don't like conspicuous dials and knobs on the dash.
- ▶ I am partial to transistor equipment.
- ▶ I strongly favor automatic tuning.
- ▶ I am hopelessly limited in the amount of green stuff.
- ▶ I am too individualistic to be satisfied with a radio that is like everybody else's.

As a result, I had to build a radio to my own specifications. It is all-transistor and not limited to 0.25-watt output; I want to hear it when I have the top down. Also, it has to be heard, but not seen; I mounted it behind the dash, well out of the way. It has automatic tuning and a minimum of controls; in the final design there is only a search pushbutton and a combination volume control and on-off switch. Both are miniature types and quite unobstructive. They can be mounted on the dash or on a small angle bracket bolted under the dash.

My final design uses eight transistors and delivers several watts output. It has good sensitivity, automatic tuning

and fits into a 8 x 5½ x 3-inch box.

Receiver circuit

Since the standard auto whip antenna is comparatively short and not very sensitive, the receiver (Fig. 1) has an rf amplifier, using a 2N140, to increase sensitivity. The rf stage's input is untuned and its output feeds the rf tuned circuit through a tap on L1. The coil we used had no secondary, so we made one by winding six turns of wire around the existing winding. Small-gauge hook-up wire was used, but most wire will work just as well.

The mixer, another 2N140, also works as an oscillator through emitter-to-collector coupling. The collector side of this coupling is connected in series with the first if transformer's primary. In the two if stages 2N140's are used. No neutralization was needed.

The last if amplifier drives a 1N295 crystal detector providing the audio signal and the avc voltage. The avc output is filtered and applied directly to the base of the first if amplifier. At the same time, the emitter voltage of this controlled transistor follows the variations of the avc signal and is used as the avc voltage for the mixer and the second if amplifier with suitable decoupling. The collector supply to the

first if amplifier also contains a decoupling circuit for stability.

The audio signal appears across the 5,000-ohm volume control. The af signal is applied through an R-C coupling to the first audio amplifier, a 2N109.

A transformer-coupled driver feeds the 2N301 power amplifier. The recommended operating point for this transistor is at 400-ma collector current. But, with limited space, it is impossible to use a heat sink large enough to cool the transistor efficiently. The solution was a temperature-sensitive resistance—in its inexpensive version—two bulbs from a Weller soldering gun (2.2 volts, 250 ma each). They are connected in series between the power transistor's emitter and ground. With the values given for the voltage divider in the base circuit, these two bulbs just glow. If they do not, reduce the value of the resistance between the base and the -12-volt line.

At this point the resistance of the bulbs increases rapidly with current, and the output stage is stabilized and shows no tendency to run away. This corresponds to approximately 300-ma collector current.

A 6-watt output transformer is used in the receiver. For best matching, only half of its center-tapped primary is used.

AST signal-seeking system

The Automatic Search and Tune system in the receiver is the result of a lot of experimenting and head scratching. The heart of the system is a surplus motor measuring 3 inches in length and 1¼ inches in diameter. Its label



A member of the staff of RADIO-ELECTRONICS checked the unit. He reports: "Ideal for the modern car. Unit plays immediately and works well. Search and tune circuit works effectively. Sound reproduction not as good as that of a standard auto radio, but to some extent may be due to the built-in speaker. Unit is especially good for small sports cars and many of the imported models. In these models, the radio can be mounted under the hood, the speaker under the dash, and the controls—volume and pushbutton tuning—on the dash."

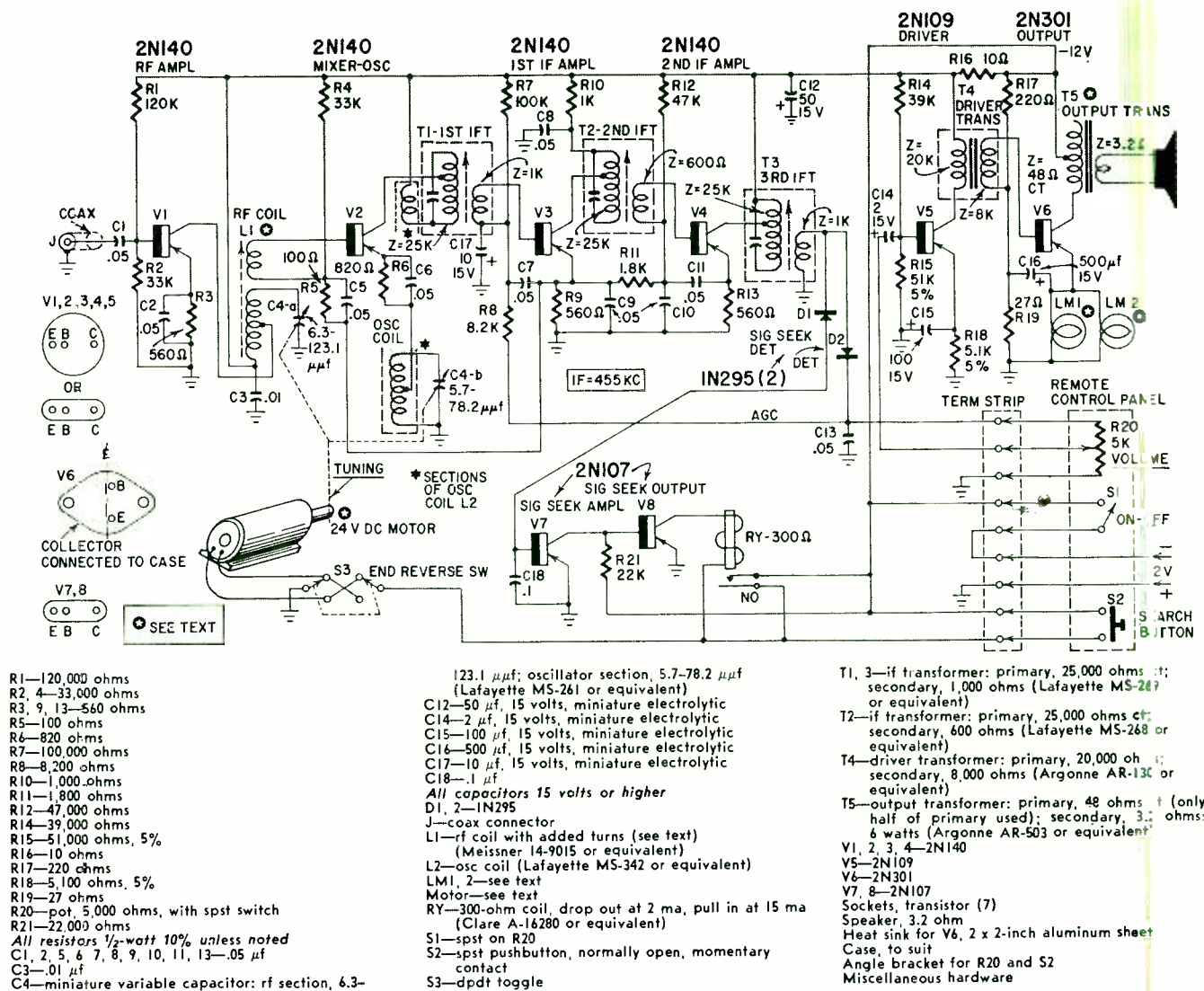


Fig. 1—Circuit of the 8-transistor receiver.

says "Delco Appliance, 145 rpm, 24 volts dc." The motor includes a reduction gear and is available in surplus houses. If you buy it there, get the gear wheel it drives at the same time. Other motors with about the same specifications can be obtained from C&H Sales Co., 2176 E. Colorado St., Pasadena 8, Calif.

The motor runs in both directions on 12 volts dc by reversing the polarity. Enlarge the center hole of the driven gear wheel to fit the variable-capacitor shaft. The threaded holes in the gear wheel are used to attach two angle pieces which flip the reverse direction switch. Once you get them adjusted properly, solder the angle pieces to the gear wheel. This way, the motor drives the variable capacitor in one direction until it reaches the end of its allowable rotation. At this point, one angle piece flips the reverse switch over and the capacitor is rotated in the other direction, and so on (Fig. 2).

The electronic part of the AST system stops the motor when a station tunes in. To do so, the if signal developed across the last if tuned circuit drives a separate 1N295 detector. The


detected dc voltage controls a two-transistor dc amplifier. If the received signal is strong enough, the stop relay in the collector circuit opens and cuts off the AST circuit and the motor. The circuit is designed so that total fading of a station (when going through a tunnel) will not actuate the system. Tuning will not change until the search button is pressed. This starts the motor running, detunes the receiver and

cancels the voltage holding the second AST transistor cut off so the relay is excited and stays closed until a station is received that is powerful enough to open the relay again.


Note that in this design the output AST transistor draws current only during the short search period—a maximum of 4 seconds for end-to-end rotation.

An AST sensitivity control could be


Fig. 2—Detail of the end-reverse switch assembly.

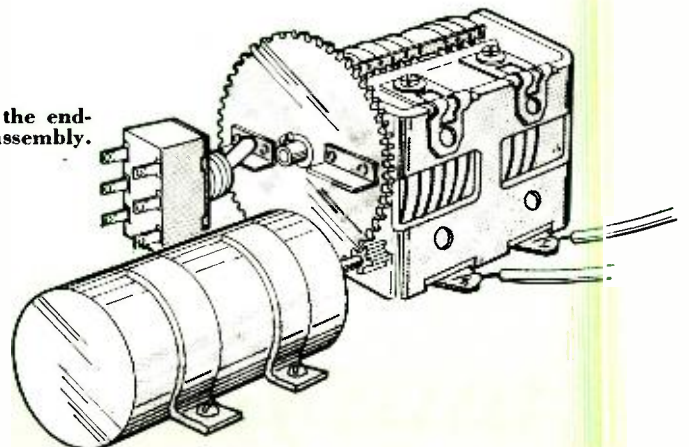

RADIO

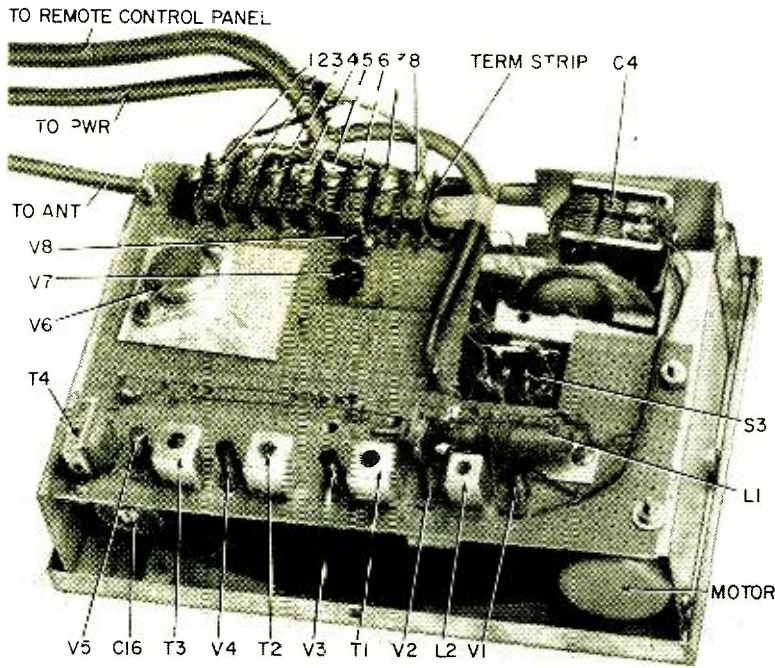

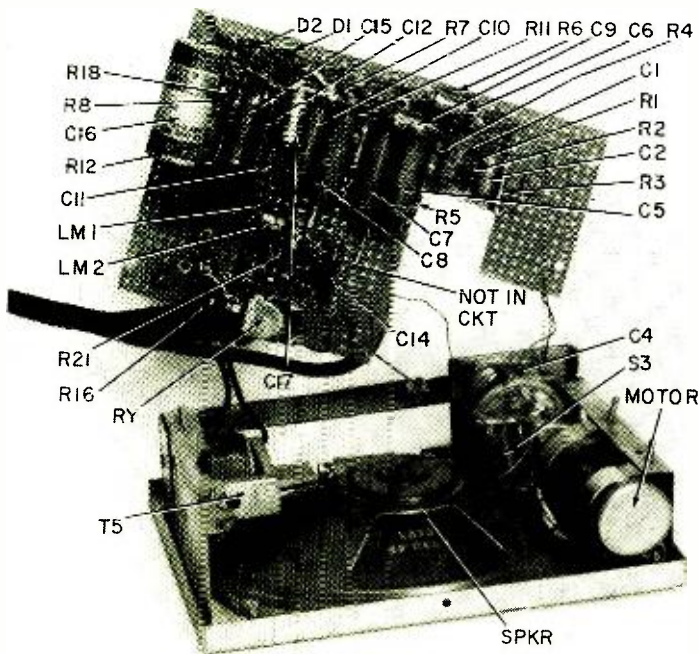Top view of the auto radio's chassis. Note cut-out section of chassis board to make room for the end-reverse switch and tuning capacitor.



With the chassis tilted clear. Parts layout on its underside is revealed as is the motor and its mounts.

added (switching or varying a base to ground resistance in the AST input). I felt it unnecessary along with a silencing circuit to keep the receiver cut off while searching. The AST circuit delivers 18-ma no-station current and 1- or 2-ma on-station current. Any relay operating between these values will work. I used the one specified in the parts list, a Clare A-16280 available from Relay Sales Inc., Box 186, West Chicago, Ill., or Clare distributors.

Assembly and alignment

I used an elliptical 5 x 7-inch Audax speaker because it has an inverted magnet—the magnet is mounted in front of the cone—making the speaking thinner. Of course, standard speakers can also be used, just use a larger case. The photos show the way I arranged the parts. Note that the phenolic chassis is cut away to make room for the variable capacitor and the reverse switch.

A seven-conductor cable runs from the set to the control panel—two leads to the search switch, two leads to the on-off switch, and three leads to the volume control. Two other leads connect the receiver to the car's battery circuit. Heavy wiring is not needed as total power consumption is only about 350 ma. You might fuse the positive supply line with a 3/4- or 1-amp fuse.

Alignment is straightforward. First set up the if circuits for 455 kc. Then, with the variable capacitor fully closed, adjust the oscillator coil slug to receive 550 kc, and tune the antenna coil slug for maximum sensitivity. Next, with the tuning capacitor fully open, adjust the oscillator trimmer for 1,550 kc and peak sensitivity with the antenna trimmer. Then start at the beginning and repeat all steps. Twice around is usually enough.

There are no other adjustments. However, you may have to suppress parasitic noise caused by your car. Resistor type spark plugs and capacitors across the generator and other motors—fans, blowers, etc., should do. Use a standard antenna and connecting cable.

Afc system

As designed, the set does not stop exactly on tune, but actually at the point where the detected dc voltage opens the stop relay. This tuning, though not exact, is good enough for practical purposes thanks to the receiver's high selectivity and energetic avc system.

From a purely technical point of view this isn't right. So I designed an afc circuit, using two crystal diodes and a voltage-sensitive diode to shift the oscillator frequency. While the system works better, it has not been included since no suitable if transformer is available. For those who want to make their own, the circuit is shown in Fig. 3. It replaces the last if transformer and detector of Fig. 1.

With the nominal 12-volt supply, current consumption is 350 ma. If the supply voltage goes up to 16, current drain goes up to 500 ma and operation is still satisfactory. If supply voltage goes down, power output decreases, but the receiver operates down to 5 volts, when total current is 100 ma.

CAUTION: Be sure to connect the power supply with the right polarity. The set shown is designed for use with a positive ground. To use with a negative ground system connections must be modified and the tuning capacitor insulated from the chassis. END


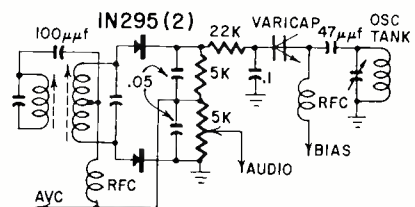


Fig. 3—Optional afc system will make station tuning exact.

what's

new ?

WORLD'S LARGEST RADIO TELESCOPE under construction near Sugar Grove, W. Va. The facility will be known as Naval Radio Research Station. Covering 7 acres, the mechanism will rotate and elevate a 600-foot-diameter aluminum-mesh reflector dish, which will probe into space for a distance 19 times the range of the 200-inch telescope at Mt. Palomar. A baby 60-foot dish remotely located will probe for interference sources. Scheduled for 1960 completion.

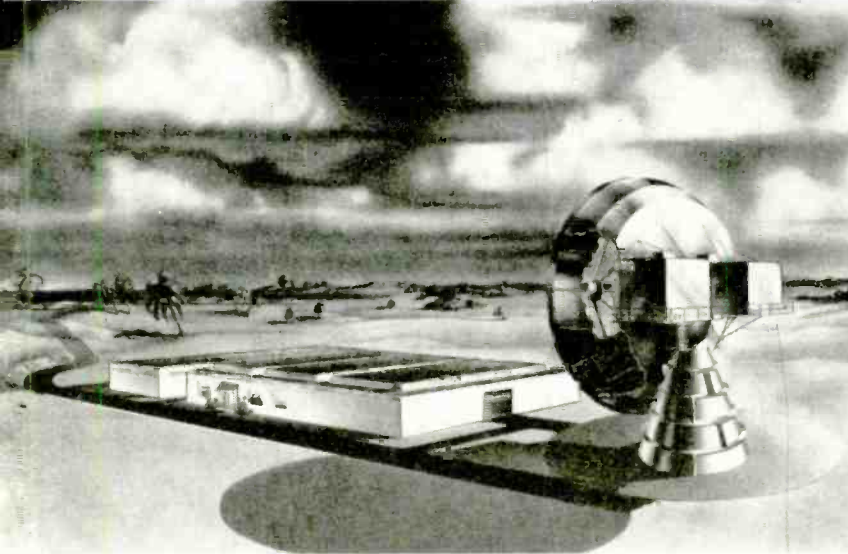

MISSILE DEFENSE of the future will include five-story-high Pincushion radar tracking antenna. System will use 12 or more narrow beams to fix on, follow and identify intercontinental ballistic missiles thousands of miles away. Important part of this radar will be super-power Amplitron tube (RADIO-ELECTRONICS, page 6, July, 1959; page 54, August, 1959). The 80-ton antenna is part of development by Raytheon for the Advanced Research Projects Agency.



ELECTRONIC LIFEGUARD works under water, sounds alarm if a child or pet falls into or enters unattended swimming pool. Submerged microphone picks up vibrations, sends them to remotely located relay control amplifier. Minneapolis-Honeywell.

MODERN-DESIGN entertainment center, *Fantasia*, has upswept wing, swiveling TV—stereo speaker section atop stereo disc, tape, radio, amplifier section. Front door (open here) closes when not in use. Arkay International.




TURNTABLES and PICKUP ARMS

built from KITS

Ten kits are on the market. All go together quickly and easily

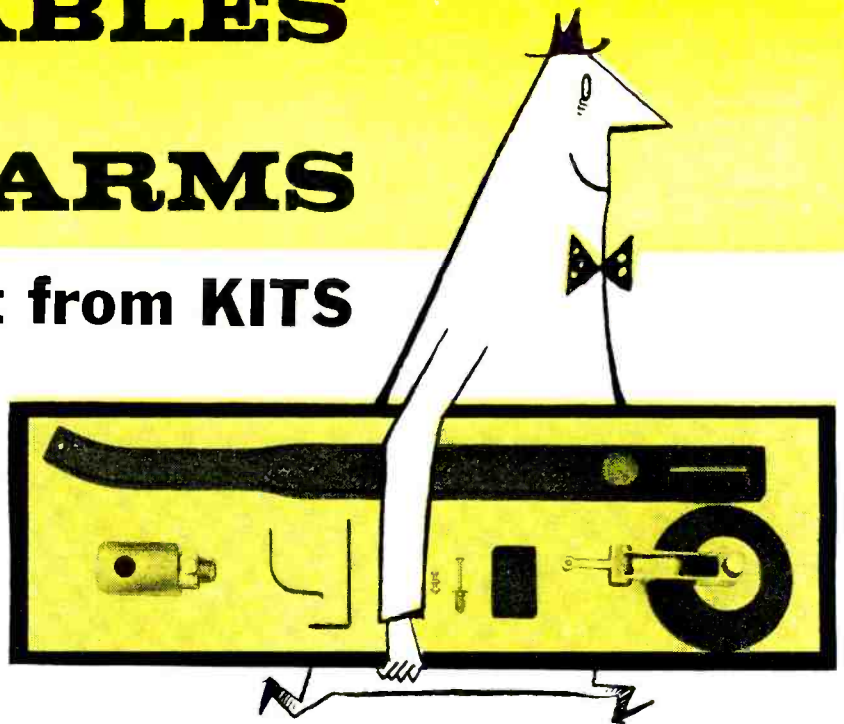By **CHARLES B. GRAHAM**
ASSOCIATE EDITOR



Audax KT-16 arm kit before assembly.

In the past few years, while high fidelity has grown from a basement experimenter's art to its present state, another even bigger movement has been growing—do-it-yourselfism. As it has grown, it has overlapped into the high-fidelity movement. Merging of the two has created a demand for a large number of kits for putting together various parts of a high-fidelity music system.

A few years ago there were kits only for audio amplifiers. Then came kits for other electronic components—FM tuners, AM tuners, and combination FM-AM units. Kits for assembling loudspeaker enclosures were a natural development. And now we have kits for the other electromechanical parts of the playback system—tape recorders (two), record changer (one) and pickup arms and turntables.

The last are particularly to be recommended to the person just starting out who may be afraid of soldering wires and small parts. Arms and turntables are almost as easy to assemble as speaker kits, and can provide an excellent introduction to kit building for the man or boy who says, "I can't put things together at all; I'm all thumbs." These kits are also fine for saving money and getting the satisfaction that comes from putting one's own system together.

There are 10 arm and turntable kits on the market now (6 turntables, 4 arms). Any one can be assembled in much less time than any electronic kit

—30 minutes to an hour approximately.

We assembled most of the kits listed in the two charts just to see how they went together. Most of them could be assembled even without the carefully written and clearly illustrated instructions supplied. Only a screwdriver is required in most cases. Even a soldering iron is unnecessary with the turntable kits, since electricians' "wire nuts" are used for ac power connections between line cord, motor, switch and click-suppressing capacitor (supplied with five of the six turntable kits).

Turntable kits

There has been a strong trend toward belt drive in transcription turntables in the last year or two. This is especially evident in the design of the kits, where we find five of the six using belts. This has two advantages. First, the belt isolates the motor, major source of turntable noise, from the frame or motorboard on which the pickup is mounted. Second, assembly of a belt drive is much easier and more reliable than precision gears and idler fitting or positioning.

Because belt drive is such a simple system, the five turntables using it have a strong resemblance to each other. Each has about a dozen parts, plus miscellaneous tiny components and a few small nuts, screws and springs. The major parts they all have are the turntable, a machined well to take the turntable's shaft, the motor, an assembly to shock-mount and partially isolate

the motor, a metal motor board to hold the motor and turntable shaft well, and a belt to transfer power from motor to turntable. Each also has a click-suppressing capacitor, a switch and a line cord.

The only kit which doesn't use belt drive is the Weathers. It has a small soft-rubber wheel mounted on the motor shaft. Its rim drives the turntable directly. It uses a light turntable and a small 12-pole synchronous motor.

All six turntable kits are single-speed (33½ rpm), although the Thorens kit, like its factory-assembled older brothers, has a control knob allowing variation of the standard LP speed from about 30 to 36 rpm. The Rek-O-Kut K-33 has a belt-tension adjusting screw which may be employed to make similar minor adjustments in the turntable's rpm, although the primary purpose of this adjustment, which is ordinarily concealed under the decorative cover, is to allow precise adjustment of the turntable to exactly 33½ rpm when it is installed. Rek-O-Kut and Thorens have thoughtfully provided a stroboscope disc right on the turntable.

Each of the belt-driven kits has a turntable whose effective mass has been made as high as economics permit. The Rek-O-Kut, Gray and Thorens turntables are machined metal with as much weight as possible concentrated at the outside. The Components turntable is cast from what appears to be a special ceramic material, very heavy, which rings almost like metal when struck.

Components Corp. arm as shipped in block of Polyfoam.



The 10 major pieces of Rek-O-Kut K-33 kit spread out on its mounting board prior to assembly.

Two of the units employ hysteresis synchronous motors. Each of these kits cost \$10 to \$20 more than the other models. In earlier years, one always tried to purchase a turntable with a hysteresis synchronous motor, if finances permitted. Today many experts agree that the design and mounting of the turntable can and often does lower rumble more than simply upgrading it by substituting a synchronous motor for a four-pole induction motor.


The hysteresis synchronous motors used in the Gray and the Rek-O-Kut (K-33H only) kits are both of the outside-rotor type, and may be driven with electronic power supplies to get any speed from below 33 rpm to over 78.

Because turntable manufacturers purchase the wood bases and motor boards in fairly small quantities (in terms of furniture quantities), the price

TURNTABLE KITS
(all 33 $\frac{1}{3}$ rpm)

Make and Model	Speed Adjustment	No. pieces, excluding nuts, screws, etc.	Sync motor	Price of base	Kit Price
Components Corp.	no	9	no	\$7.50	\$29.50
Gray HSK-33	no†	14	yes	\$17.95*	\$49.50
Rek-O-Kut K-33	slightly	10	no	\$8.95*	\$39.95
Rek-O-Kut K-33H	no†	11	yes	\$8.95*	\$49.95
Thorens TDK-101	yes	12	no	\$9.00	\$47.50
Weathers	no†	6	yes	\$5.95	\$49.95

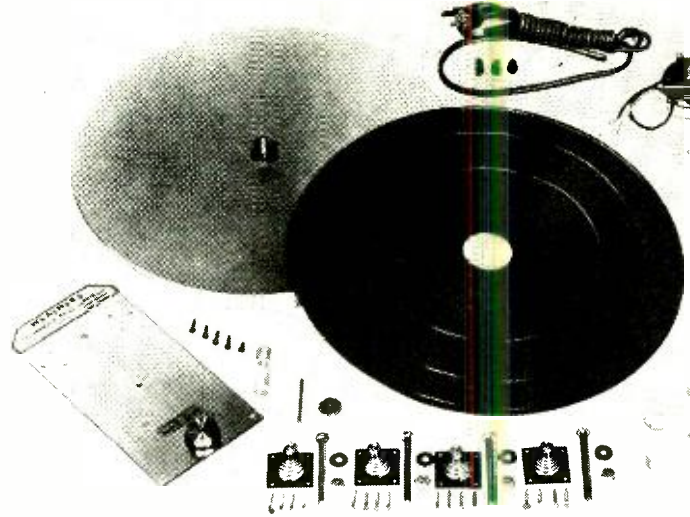
*Company can supply flat motorboard for mounting turntable at less than \$5.00.
†Complete range of speed available with variable frequency electronic power supply.



All parts of the Weathers low-mass turntable spread out prior to assembly.




All parts of Components Corp. turntable.

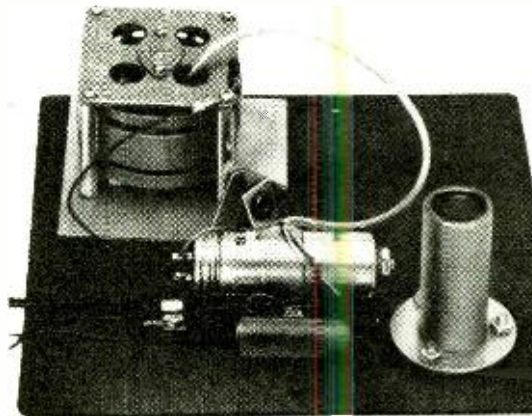

Underside of Gray turntable kit after assembly.



Thorens TDK-101 kit.

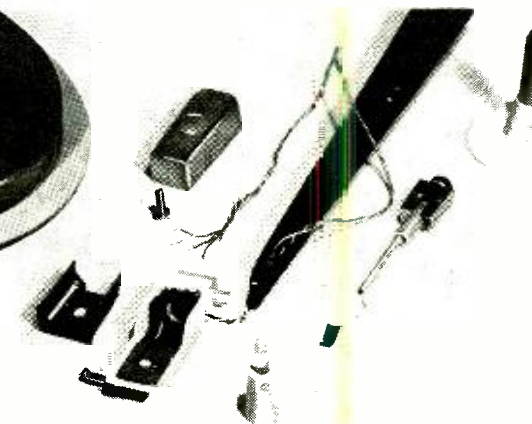

Gray viscous-damped arm had most parts of any arm kit.

PHONOGRAPH ARM KITS

Make and Model	Construction	Interchangeable heads or slides	Number of pieces	Price
Audax KT-12	inertially balanced	yes @ \$3.95	8	\$15.50
Audax KT-16	inertially balanced	yes @ \$3.95	8	\$16.50
Components "Pro"	inertially balanced	1 screw, 3 or 4 terminal clips @ \$2.00	13	\$ 9.50
Gray SAK-12	viscous damped	yes @ \$4.60	16	\$23.95

AUDIO—HIGH FIDELITY

of these bases are often a large proportion of the total price of the turntable. They become even more expensive, proportionately, when mounting a turntable kit.

Fortunately, turntable-kit makers provide full-size paper templates for cutting one's own mounting board or base. It may be reasonably assumed that most people who buy a turntable kit will seriously consider cutting (or having the local lumberyard cut) at least a motor board, since complete mounting bases run as much as \$17.95.

Phono arm kits

Although the arms, in general, have no more parts than the turntables, and are smaller and cost less, they went together no more easily than the turntables. One touchy part was stringing the leads and soldering the cartridge terminal clips to them.

Three of the kit arms are of the type which is balanced without using springs. They employ a sliding weight near the rear end for adjusting the vertical tracking force. All the kits are supplied with arm rests.

The only kit of the lot which needs tools beyond screwdriver, soldering iron and pliers was the one for the Components arm. We needed a hammer to secure the main pivot to the body of the arm. Although the maker didn't supply a hammer, he did supply a large ball for the hammer to drive against the pivot in securing it!

Most technicians are aware that positioning the tone arm correctly in relation to the turntable is important. It is even more important for stereo than in reproduction of monophonic discs. In playing back stereo records, improper positioning cannot only produce distortion and extra record (and stylus) wear, as in mono playback, but can often introduce a serious loss in the separation between stereo channels.

The arm makers furnish full-size paper layouts for precise arm positioning on the wooden motor board or base. They should be followed religiously to minimize tracking error. END

HUM REDUCTION

Dc heater supplies are undoubtedly the best way to eliminate ac hum. However, for small home amplifiers such a heater supply with its several large capacitors can turn out to be larger than the amplifier, and extremely expensive. An excellent substitute is to wire the heaters with shielded cable. At ordinary room volume, this reduces hum to inaudible levels.

For the best possible results, insulate the shield from the chassis at all but one point. Here a good ground connection is made. However, except for the finicky, this is not really necessary.

Of course, shielding the heater wiring is of no help when hum is introduced from some other source, so follow all good wiring practices as usual.—R. C. Sandison

CITYRAMA . . .



multilingual tourist bus

An electronic announcer describes points of interest to passengers in this Paris sightseeing bus in any of 8 languages

The big Citroen bus is fitted with a special 8-track tape recorder. The 8 languages are recorded on the 35-mm wide tape, which is started by the driver as the bus approaches points of interest. After a talk of a minute or two, it is switched to background music.

The bus carries 8 amplifiers and 8 preamplifiers with the wide 8-track tape seen here. A 470-ampere-hour, 24-volt battery supplies 110 volts ac through a rotary converter to power the setup. Tape machines for background music are also seen, as well as drawers for extra tapes, filed by language.

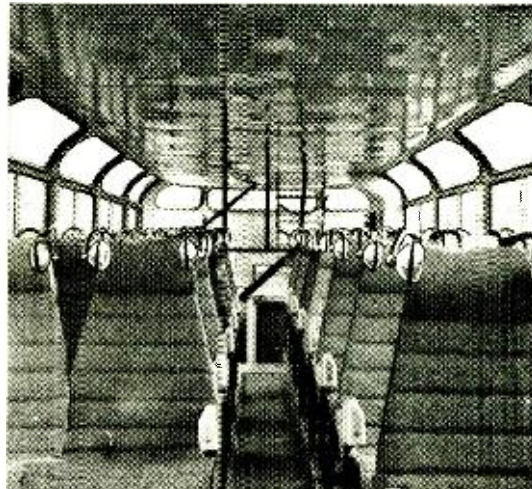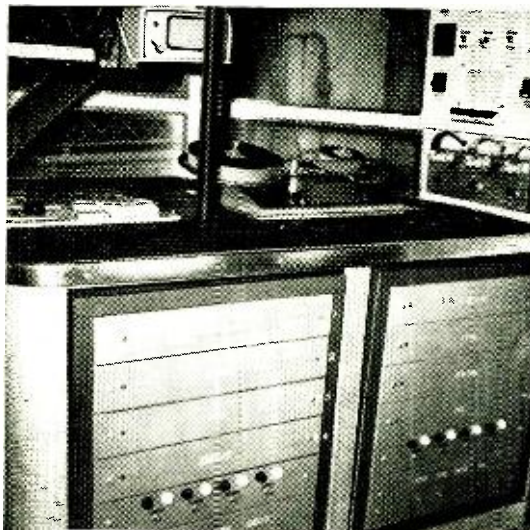To avoid confusion, the speakers are placed in the seat head rests, so they can operate at a low level. A control box on the arm rest permits the listener to vary the volume within limits, and to select the desired language. Special announcements can be made by the hostess, seated at the front of the bus, who can switch in her microphone and override the recordings.



new developments in

Three interesting circuits: one reduces distortion caused by overmodulation and low signal strength; another is a phase inverter with exceptional gain, and the third is a TV video amplifier that doubles as a phono preamp

By **ROBERT F. SCOTT**
TECHNICAL EDITOR

THE current crop of radio and audio equipment is chock full of new and unusual circuits of interest to the technician. Those described here include a new circuit for reducing distortion caused by overmodulation and low signal strength in FM tuners, a low-distortion phase inverter with exceptionally high gain and a TV video amplifier that doubles as a phonograph preamp.

FM distortion eliminator

Critical FM listeners have often been annoyed by distortion that is noticed all too frequently on strong local stations and on those weak fringe-area stations that are invariably the favorites of many hi-fi fans. Distortion on strong signals is generally caused by overmodulation at the transmitter. When the FM transmitter overmodulates, the carrier swing exceeds the FCC maximum of ± 75 kc and the resulting FM if carrier exceeds the linear portion of the discriminator curve.

Fig. 1-a shows a carrier with less than 100% modulation falling within the linear (150-kc) portion of the discriminator's response curve. Compare this with Fig. 1-b where we have a carrier with more than 100% modulation. The carrier now spills over onto the back slopes of the response curve and distorts the discriminator output as shown.

Fig. 2 compares weak (a) and strong (b) FM signals in the receiver's if bandpass. In Fig. 2-a, only those signals falling between 10.675 and 10.725 mc exceed the threshold of limiting and saturate the limiter(s). Those audio frequencies whose amplitude makes the FM carrier swing below 10.675 mc and above 10.725 mc will be distorted in the discriminator's output.

The DSR (Dynamic Sideband Regulation) circuit in the Knight KN-120 stereo tuner is designed to minimize the types of distortion just discussed. A portion of the discriminator's audio output is applied to the grid of the tuner's afc tube so the high-frequency oscillator is modulated in phase with the incoming audio. This reduces the frequency swing of the FM if signal by

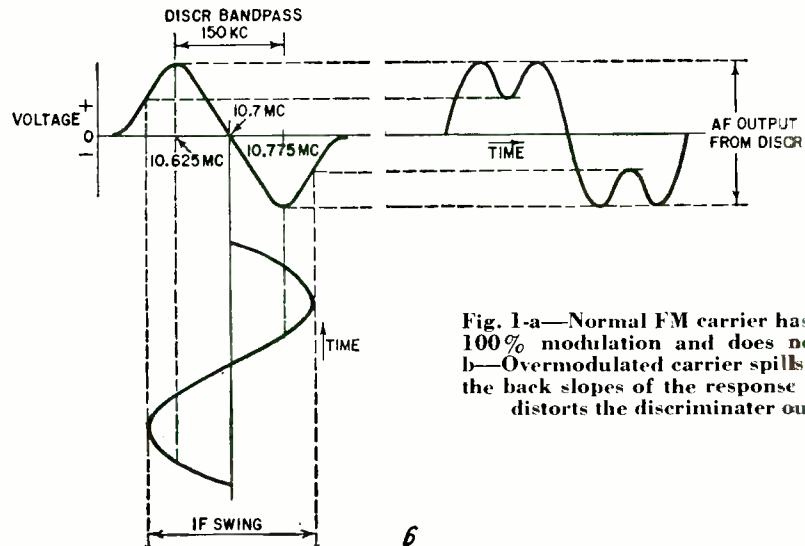
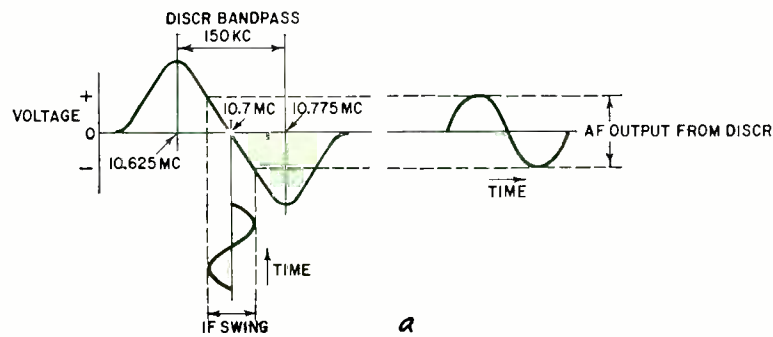
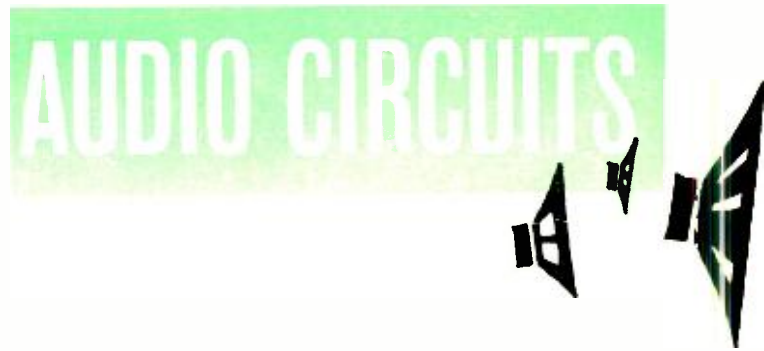


Fig. 1-a—Normal FM carrier has less than 100% modulation and does not distort. b—Overmodulated carrier spills over onto the back slopes of the response curve and distorts the discriminator output.

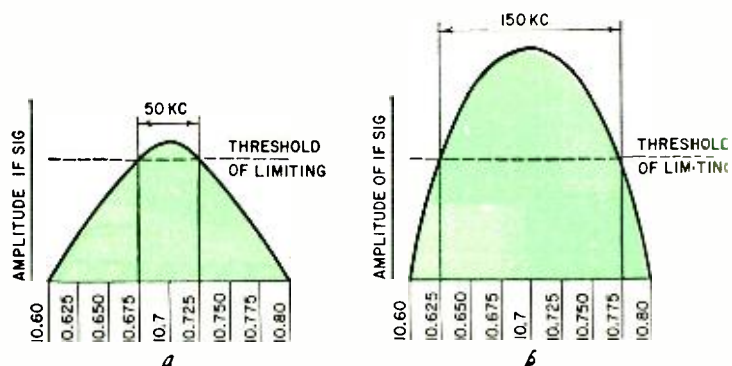


Fig. 2—Weak and strong signals in the FM receiver's if bandpass: a—only signals between 10.675 and 10.725 mc saturate limiter(s); b—with higher amplitude, signals between 10.625 and 10.775 mc saturate the limiter(s).

AUDIO—HIGH FIDELITY

reducing the instantaneous difference between the oscillator and the incoming FM signal.

For example, consider a 98-mc FM carrier modulated by audio producing a swing of ± 75 kc (from 97.925 to 98.075 mc). With the receiver's oscillator fixed at 10.7 mc above the carrier (at 108.7 mc), the if swings plus and minus 75 kc (from 10.625 to 10.775 mc). In a tuner without DSR or with the DSR turned off, the rf and if carrier deviations are equal.

Now, let's see what happens when we modulate the oscillator so its frequency swings in phase with the incoming FM signal. Assume that the instantaneous audio extracted from the discriminator swings the oscillator ± 10 kc. Now, the oscillator frequency is 108.690 mc when the incoming signal hits 97.925 mc and rises to 108.710 mc when the FM signal

modulator's grid (afc tube) through a filter network composed of a .01- μ f capacitor and 3.3-megohm and 470,000-ohm resistors. The discriminator's af output is fed to a cathode follower

locked so afc cannot be turned off while DSR is on.

Dynamic sideband regulation tends to provide the distortion-free performance of the wideband discriminator under varying signal and modulation levels while having the advantage of being less affected by sideband clipping in the if circuits.


High-gain phase inverter

Audio design engineers are constantly seeking new types of phase inverters that will provide higher gain and lower distortion than existing types. High gain means that fewer voltage amplifiers are required when the amplifier is to be driven by low-level signals. With fewer stages, phase shift is reduced and heavier negative feedback can be used while maintaining a high margin of stability.

Some designers use a high-gain inverter with comparatively high distortion and then reduce distortion with negative feedback. Others prefer a low-distortion inverter, even if its gain is very low. Typical examples of these two schools of thought are the various forms of paraphase and long-tail inverters frequently used in high-quality amplifiers. A typical floating paraphase inverter with an ECC83/12AX7 has a gain of 58 to 62 with distortion ranging from 3.5 to 5.5%. A long-tail pair with the same tube and range of plate voltages has a gain of 25-27 with 1.8% distortion.

Design engineers at Amperex Electronic Corp. have developed a new form of split-load inverter in which a weird combination of positive and negative feedback is used to obtain exceptionally high gain with reasonably low distortion. The circuit in Fig. 4 provides gains up to 800 with considerable attenuation of frequencies in the upper end of the audio range. High-frequency losses are reduced in practical circuits when gain is reduced to 200-300.

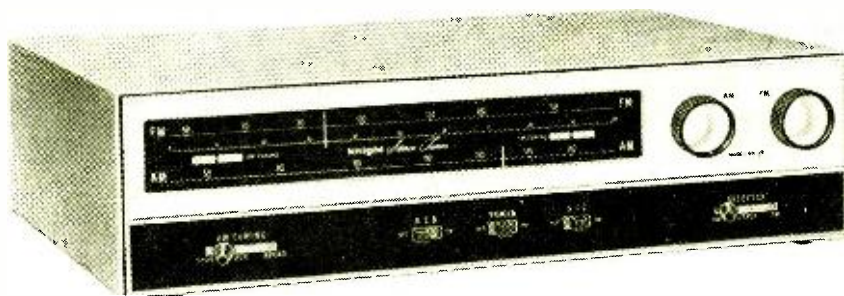In Fig. 4, the plate of V1-a is fed through R3 from V1-b's cathode. Negative feedback is applied to V1-a by R2 the unbypassed cathode resistor. The low-potential end of cathode resistor R5 is returned to V1-a's cathode and develops a positive feedback voltage across R2. The positive feedback voltage across R2 exceeds the negative



The Knight KN-120 stereo tuner incorporates a DSR circuit in its design.

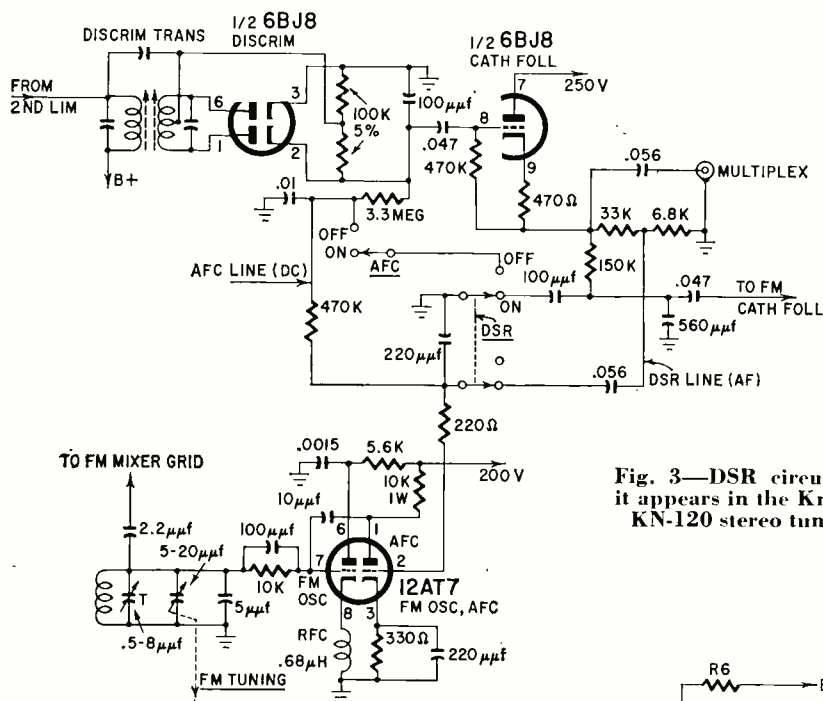


Fig. 3—DSR circuit as it appears in the Knight KN-120 stereo tuner.

swings to 98.075. Thus the DSR has reduced the if swing from 150 to 130 kc. Reducing the if swing has the same effect as reducing the transmitter's deviation or modulation by turning down the af gain control at the studio.

Thus with DSR, an overmodulated signal like that in Fig. 1-b would be compressed to fit within the linear portion of the discriminator's passband and distortion would be prevented. Similarly, the full swing of a weak signal (Fig. 2-a) can be compressed so it falls within the portion of the if response curve extending above the threshold of limiting so all distortion-producing residual amplitude modulation will be removed.

DSR circuit analysis

The circuit of the DSR is shown in Fig. 3. The discriminator's dc output is tapped off and fed to the reactance

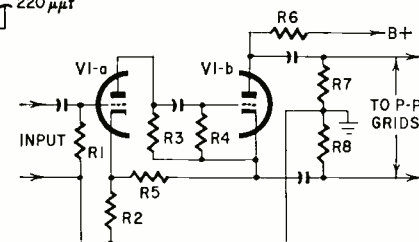


Fig. 4—This circuit provides gains up to 800 with attenuation of high frequencies. High-frequency losses are reduced when gain is lowered to 200-300.

where a small portion is tapped off and fed to the afc grid through the .056- μ f capacitor. This makes the oscillator swing in phase with the audio signal. To provide optimum performance with the DSR on, the 100- μ f capacitor is switched into the circuit to change the time constant of the de-emphasis network.

Since the oscillator must be tuned on the nose for proper DSR operation, the afc and DSR switches are inter-

LOWS ARE DIRECTIONAL TOO

TWO General Electric engineers have rescued the low-frequency part of the audio spectrum from the charge of non-directionality so often made by stereo specialists. The listener will breathe a sigh of relief, for not only does this confirm the (occasional) evidence of his senses, but marks a reversal in the trend toward whittling away the stereo frequencies.

Resigned to the idea that "nothing under 200 cycles is directional," he has been willing to accept without argument the extension of that area up to 300 cycles. But with one West Coast stereo system basing itself on "experimental proof" that the frequencies above 2,500 cycles contribute little or nothing to stereo, the enthusiast had reason to fear his band might shrink to a point frequency. Now the tide has turned, and the stereo spectrum is increasing rather than decreasing.

The two engineers, W. H. Beaubien and H. B. Moore, conducted carefully controlled tests with 29 listeners to see if they could tell from which speaker the low notes came. They made an elaborate setup to (a) pass full stereo information through two wide-range speaker systems separated about 10 feet, and (b) to pass full audio information through the same speakers after combining it through special circuitry to eliminate directionality.

They also used high-pass filters to emphasize the lows. Directional perception among the 29 people tested, using musical material below 100 cycles, was 80%. This appeared to indicate a high degree of directional perception at the low frequencies, in contrast to previous tests made with continuous sine waves.

The room in which the experiments were conducted was similar in size to a large living room, with a high ceiling (12 feet). Speakers were placed along the sides, pointing toward the center of one end. The listeners were positioned near that end, 10 feet from either speaker.

The two men delivered a paper on their experiments at the Audio Engineering Society (AES) convention. END

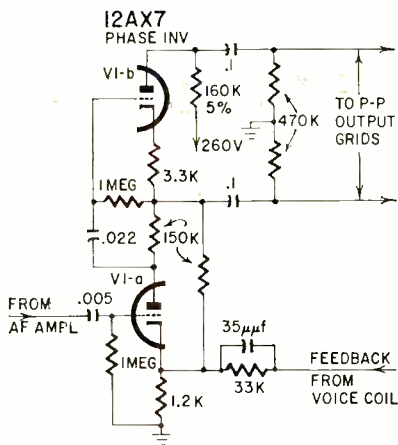


Fig. 5—High-gain phase inverter as used in Admiral's 5T4-A amplifier.

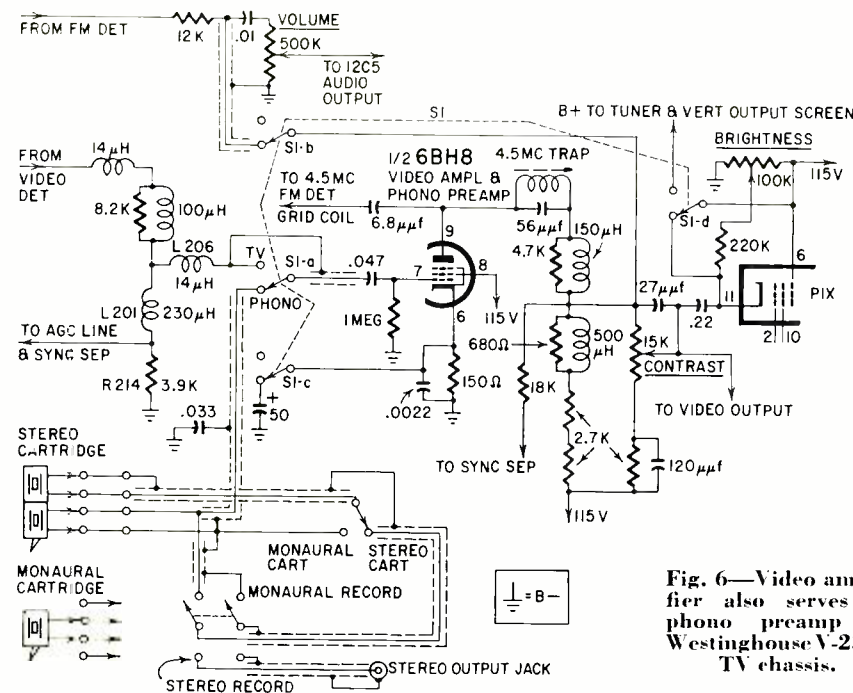


Fig. 6—Video amplifier also serves as phono preamp in Westinghouse V-2365 TV chassis.

feedback voltage and V1-a would tend to be unstable if its plate load resistor (R3) were not connected to V1-b's cathode. However, since R3 returns to V1-b's cathode and V1-a's plate and V1-b's cathode are in phase, enough negative feedback is applied to give the circuit complete stability.

Fig. 5 is the circuit—including schematic layout—as used in Admiral's 5T4-A amplifier chassis. Gain is around 200. The circuit is further stabilized and its response widened by applying negative feedback to V1-a's cathode from the output transformer's secondary.

Audio-video amplifier


The Westinghouse V-2365 TV chassis is designed so its audio system can be used as one channel of a stereo system. However, since the 12C5 output tube is fed directly from the FM detector, it was necessary to provide a phono pre-amplifier. It was done by using the video amplifier, as shown in Fig. 6.

When switching to PHONO, section

tube. Removing B plus from the tuner prevents rf signals from being picked up and possibly feeding into the audio circuit through stray inductive or capacitive coupling. Connecting 115 volts to the cathode of the picture tube cuts it off and prevents flashes of light from appearing on the screen when the set is turned on or off with S1 in the PHONO position.

A remaining section of S1 (not shown) breaks the 135-volt line feeding the vertical output and damper plates and the screen grid of the horizontal output circuits. Cutting off the horizontal amplifier removes the boosted B-plus voltage source that supplies the horizontal and vertical oscillators and the FM detector. With the deflection circuits fully disabled, there is no possibility of 60- and 15,750-cycle sweep signals causing audio interference.

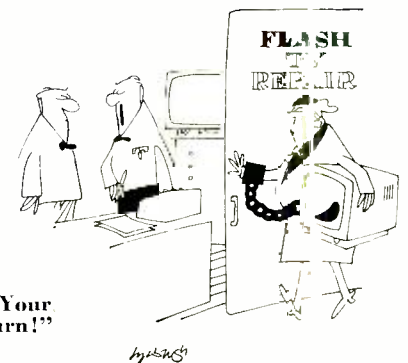The TV-phono combination is supplied with a monophonic cartridge but can be readily adapted for stereo by adding a stereo cartridge and an auxiliary amplifier-speaker unit. END



"Your turn!"

HOW VALID ARE SPEAKER RESPONSE CURVES

Do they really mean something or are they just a heap of meaningless confusion intended to sell speakers?

By **GEORGE L. AUGSPURGER**

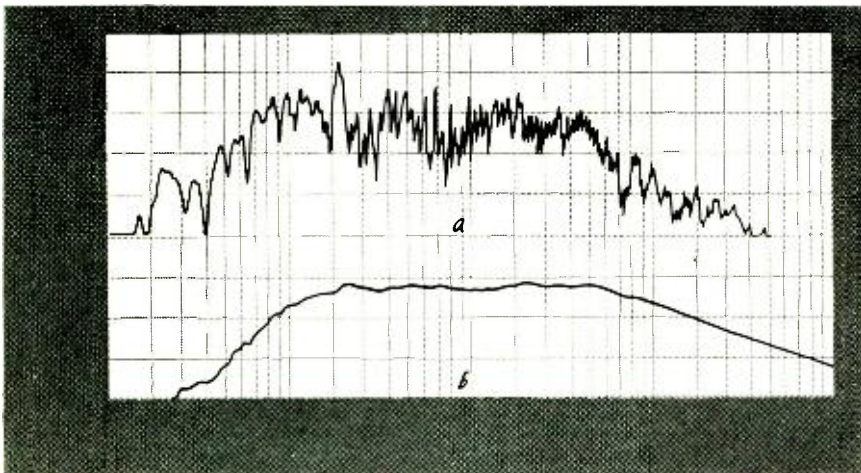


Fig. 1—Both curves are run under identical conditions, but with different chart and pen speeds. Note how the higher speed smooths out the curve.

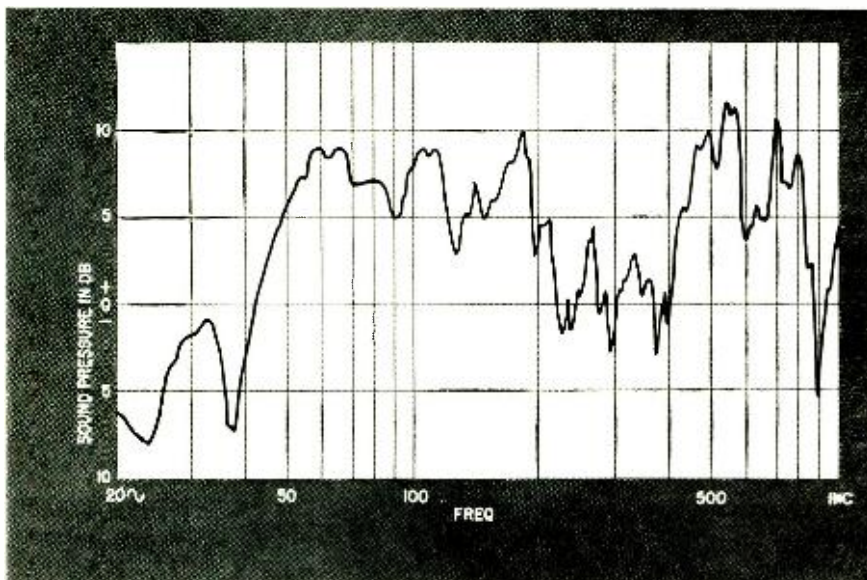


Fig. 2—Sine-wave response of a front-loaded folded horn. The microphone pickup was placed 3 feet from the horn mouth and on its axis.

THE myth that high-fidelity reproduction is directly related to frequency response is an article of faith the audiophile seems unwilling to give up. Irresponsible statements in hi-fi primers and consumer publications haven't helped. The truth is that most of the time "frequency response" is an almost meaningless term, and at best is just one of the many factors that relate to what we call realistic sound reproduction.

Those who have suffered most from the emphasis on response curves are speaker manufacturers. Talking about a speaker's frequency response just isn't the same as going over a power amplifier. Nevertheless, when Joe Decibel hears the new Stereonic Triple Piston speaker system at the audio show, his first reaction is, "Sounds great! What's its frequency response?"

The person in charge generally sighs and assumes the question is pure noise from a semantics standpoint—something like "How do you do?" And the answer is simply another part of the ritual, "20 to 20,000." No speaker manufacturer at an audio show has the slightest hope of persuading the audiophile that there is really no truthful, yet simple, answer to his question.

However, a verbal white lie is not the same as publishing an impressive chart with lots of squiggly lines and the notation "machine-run frequency response curve." How valid are such curves? Can they be used as a basis for comparing and selecting speakers?

Standards for measuring speaker frequency response do exist and the measurements made are, within reasonable limits, repeatable. Mr. Villchur has been hammering at this for several years and publishing quite honest curves complete with details on how they were made.

But, even if we had such data available—measured under identical conditions—for every speaker on the market,

there is still no assurance that this mass of material would agree with listening tests made in the customer's home. In the first place, frequency response by itself is not enough. Beranek states that frequency response is only one of seven characteristics which are required to describe the performance of a loudspeaker.¹

He further warns, "The use of a pressure microphone has the disadvantage that it is a 'monaural' (one-ear) device, whereas we ordinarily listen to sound 'binaurally' (two ears). . . . We must expect, therefore, that our 'monaurally' measured response curve will not bear an exact relationship to what a listener would perceive if he were in the same location as the microphone."²

Even charting a response curve is not cut and dried. All sorts of things affect the way such a curve turns out.

Making response curves

Loudspeaker response curves are generally run by feeding a sine wave to the speaker, picking up the sound with a calibrated microphone, and feeding the signal to some sort of measuring device. We can connect the mike to a VU meter and laboriously plot a curve point by point, or we can use a graphic recorder to do the job automatically. The photo shows a very elaborate version of such a machine.

That the characteristics of this device will affect the final curve just as much as the speaker under test is seldom mentioned. The relationship of the speed at which the curve is run to the rapidity with which the pen can follow abrupt changes determines how much peaks and dips in the response are averaged out during the course of the test.


There is always some degree of smoothing, and this is all right so long as we know it is present, but we must also know how much. For example, Fig. 1 shows two curves run on the same speaker under the same physical conditions on the same machine. They are both legitimate curves if we know how the machine was set. But what is too often done is to say nothing about the method other than it is "automatic," and simply publish the better curve.

Acoustic surroundings

Speaker tests are usually run in free-field conditions—acoustic reflections are eliminated so far as possible to get an honest indication of the speaker's performance. But is such a curve really honest? How many of us listen to hi-fi in an anechoic chamber?

The purist will say this is a childish objection. If the speaker won't perform well in open space, it certainly won't be any better in an average room and, after all, free-field testing is the only way we can get a standard of comparison. The opposing position is that this may be the only standard we have, but from the consumer's point of view it is a pretty poor one.

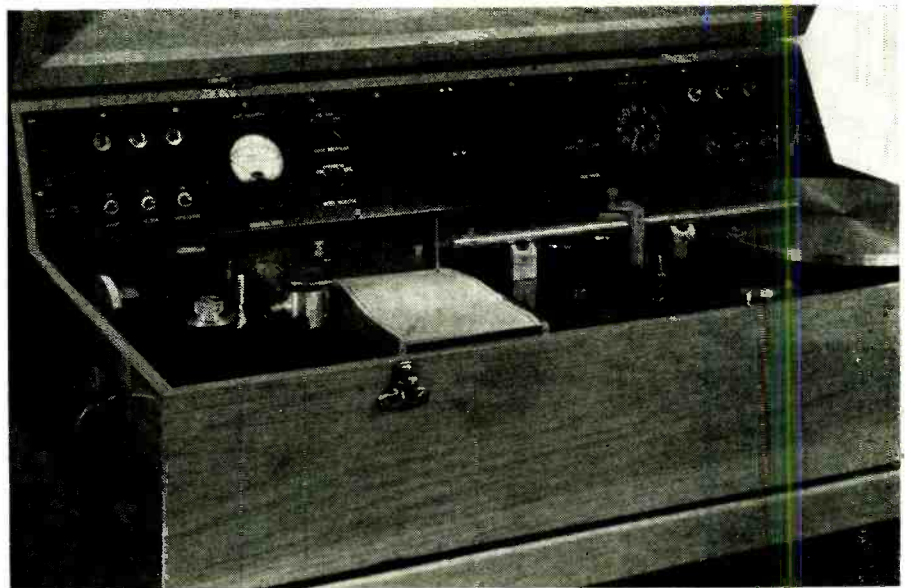The basis for my viewpoint is that different speaker systems behave dif-



An automatic loudspeaker-response chart recorder. This unit has three speeds.

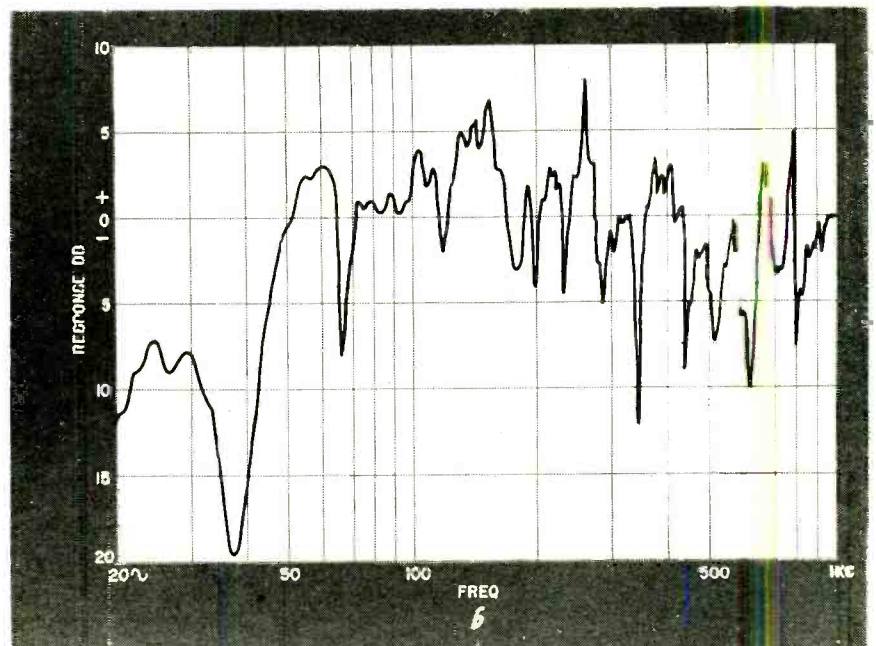
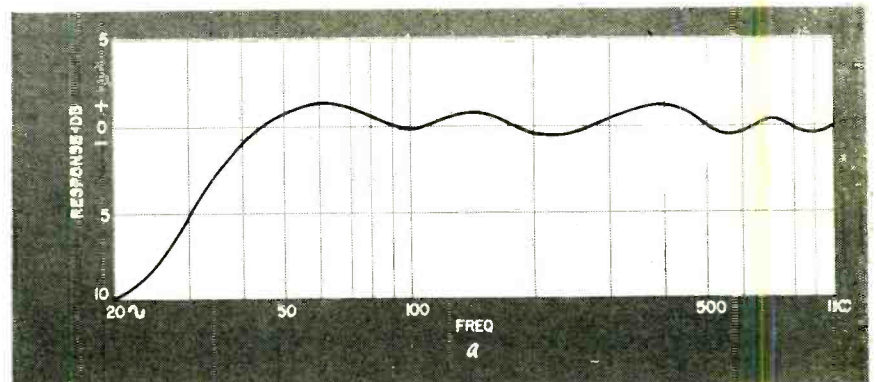


Fig. 3—Comparison of sine-wave response curves: a—Free-field curve published by speaker manufacturer; b—curve run with speaker in corner of listening room. The microphone pickup was placed 3 feet from the speaker on its axis.

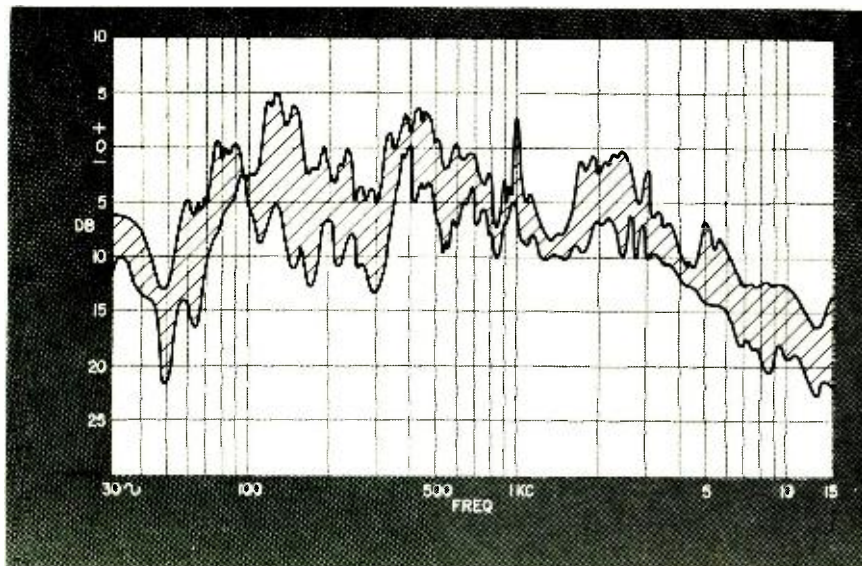


Fig. 4—Variation of pressure response of an 8-inch speaker in a small baffle. Unit was set up in a listening room at floor level. Shaded area shows maximum variations in sine-wave pressure response curves at five microphone positions.

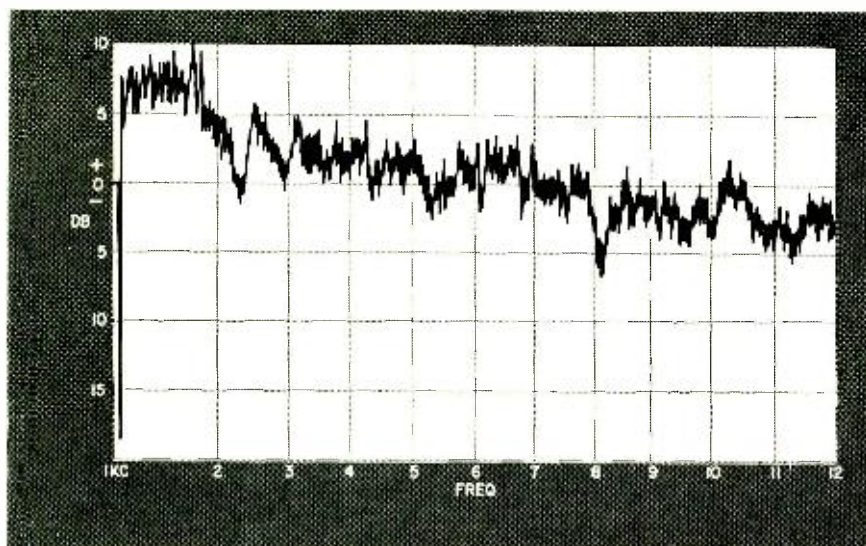


Fig. 5—Response curve run with white-noise input and wave analyzer.

ferently when moved from an anechoic chamber to a listening room. For one thing, it is not generally realized that standing waves not only affect what a listener hears (depending on where he is sitting), but actually influence the physical motion of the speaker cone.

Some designs are what might be called socially adaptable—if they run into a strong standing wave at some frequency, they obligingly change their intensity. Others (usually the more efficient horn-loaded designs) are rugged individualists who maintain their output regardless of acoustic environment.³

A second consideration is that a system which has a large sound source is generally less affected by room acoustics than a small one. A large corner-horn or multiple-woofer array will often give better results in a small listening room than a more compact unit of comparable

quality, even though common sense suggests that the opposite should be true.

A third factor is that the corner horn is designed as an integral part of a room and cannot be measured under conditions equivalent to free space. So it is easy to see why a comparison of response curves for these two kinds of systems is bound to be more a guessing game than a scientific analysis.

The pitfalls of such comparisons are illustrated in Figs. 2 and 3. Fig. 2 is the sine-wave response curve of a folded corner horn measured in a 15 x 27-foot listening room. Compare it to Fig. 3-a—the published response of a sealed “acoustic-suspension” system measured in free air (radiating into a 180° solid angle). In this instance, there is no reason to doubt the honesty of the published curve since the manufacturer specified the exact conditions under which it was run.

Any normal audiophile, shown these two curves, would not hesitate an instant to pick the sealed box as the “better” of the two speaker systems.

But now let us move the small box indoors and measure it under the same conditions which give us the curve for the corner horn. The miserable affair of Fig. 3-b is the result! The reason for this surprising change of behavior is a combination of the three factors just discussed.

True, the small system can be used in a variety of room locations, while the horn is restricted to corner placement. But a number of tests indicate that no matter where the small speaker is placed in this particular room, its measured curve is never significantly smoother than that shown.

Mr. Paul Klipsch would probably say this experiment shows why a corner horn is better than a direct radiator. Mr. Villehur can undoubtedly argue the opposite. (My own feeling is that either system can be very, very good under proper conditions.) But the only important point here is that comparing these two designs on the basis of published sine-wave response curves is grossly unfair.

Sometimes, rather complex methods are used to measure a speaker in a room, yet to average out room effects so that the resultant curve corresponds with listener evaluation. Jensen loudspeaker engineers sometimes use five microphones placed at various locations. The outputs from these are averaged automatically and fed to the chart recorder.

Another method is to plot several curves at various mike locations, and then graph maximum and minimum output at all frequencies. Such a graph is shown in Fig. 4. The shaded area indicates maximum variations between five microphone positions for a single 8-inch speaker in a very small enclosure.

One final remark on acoustic surroundings. Even elaborate anechoic chambers can be made to yield different curves with a little juggling. Two laboratory technicians for a highly reputable firm once spent a full week trying every conceivable location of microphone and loudspeaker in their anechoic chamber to get the smoothest possible curve for publication.

Source material

So far, we have assumed that the speaker was being fed pure sine waves at various frequencies. This is standard procedure, but not the only standard method. Warble tones or white noise are often used to show up characteristics not measurable by sine-wave tests.

The white-noise method is particularly interesting. The speaker is connected to a source of white noise covering the entire audio spectrum at a substantial power level. This means that the unit is trying to reproduce random bursts of every frequency simultaneously—a more difficult requirement than even the most dissonant modern music.

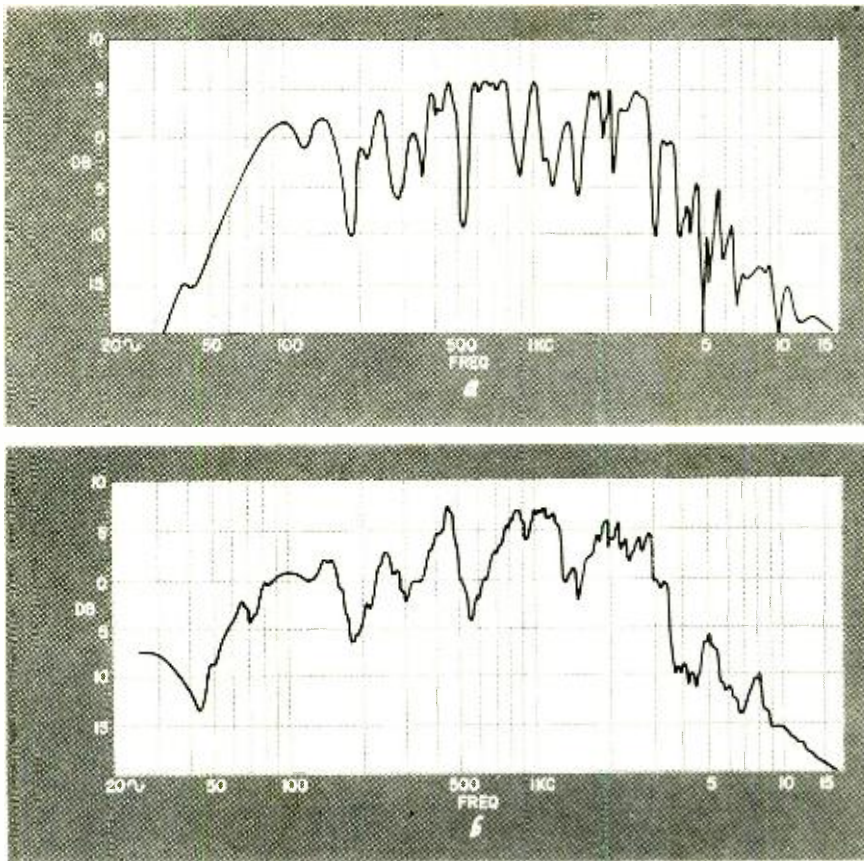


Fig. 6—Sine-wave vs white-noise response of 8-inch speaker in small cabinet in corner of listening room at floor level. Microphone pickup is placed 3 feet from the speaker on its axis: a—white-noise input; b—sine wave input.

The noise thus produced is picked up by a microphone and fed to a narrow-band variable wave analyzer. This is an expensive filter having a bandpass of only a few cycles, and continuously variable over the band of audible frequencies. While the speaker is struggling to reproduce everything at once, we measure what it actually is producing at each frequency.

Fig. 5 is a white-noise curve run on a high-quality tweeter. The continuous ups and downs of about 2 db are caused by random fluctuations of the source rather than any characteristic of the unit under test. Notice that the frequency scale is not logarithmic, and that the curve must be replotted for normal comparison purposes.

Fig. 6-a is such a curve redrawn from a white-noise and wave-analyzer recording. The unit under test was a cheap 8-inch speaker in a very small enclosure. Fig. 6-b is a standard sine-wave curve run on the same unit under identical physical conditions. Both methods supposedly measure the same thing, yet there is little similarity between the two curves!

Engineers who work with white-noise testing find that a speaker which has the same curve with white-noise as with sine-wave input usually sounds considerably better than one which may have a smoother sine-wave curve, but displays different characteristics when reproducing white noise.

The various methods described are

some of the tests used to determine the frequency response of a loudspeaker. They are all in common use and are all valid, yet they may give significantly different results. Other characteristics are measured by other equally complicated methods. The goal of all this



testing is to be able to correlate measurable response with listening evaluation so specific factors can be isolated for design and development work.

Consequently, we must admit that speaker response curves are valid—for the engineer who made them. Such tests are a valuable tool in improving loudspeaker design.

But it seems silly for the consumer to study test results which admittedly only approximate final listening evaluation. The audiophile isn't interested in building a speaker, he wants to buy one. And the only valid way to judge a speaker for music reproduction is to listen to it reproduce music.

Beware of the dealer who demonstrates with an audio oscillator, and who is eager to point out the unit which has *more* bass and *more* treble. This is like judging orchestras on the basis of which has more violins or louder kettle-drums. Instead, listen to music you like in a relaxed atmosphere, and listen for the system which sounds most natural.

Once you own such a system, you can bask in perfect confidence when your jealous friends say, "Well, it sounds all right, but what's the frequency response?"

Like the Rolls-Royce owner, you calmly reply, "Adequate." ENT

¹Leo L. Beranek, *Acoustic Measurements*, Wiley, 1949, page 661.

²*Ibid.*, page 666.

³A. L. Thurau, "Loudspeakers and Microphones for Auditory Perspective," *Bell Laboratories Record*, Vol. 12, No. 7, March 1934.

Reprinted in *Audio*, October, 1957.

"The problem then is to select an internal (amplifier) impedance such that variations of power output with load impedance shall be minimum. . . . The load impedance will vary accordingly as the outgoing waves are met by aiding or opposing pressure from the returning waves. . . . Hence rather large variations in sound output would have to be tolerated were it not for the smoothing effect of properly chosen electrical impedance. . . . An essential condition for this is the high efficiency of the low-frequency loudspeaker."

WHEN IT COMES TO YOUR PROTECTION . . .

Radio-Electronics is just as fast on the draw as Matt Dillon, Wyatt Earp or any of real, reel, or TV marshals on the Old West. For instance—for the last 51 issues (since January 1956) we have refused all mail-order tube advertising which did not state specifically that the tubes advertised were new and unused, or seconds, rejects or otherwise sub-standard if that were the case. Pardner, that has cost us plenty of pesos in lost advertising space—but we think it was straight shooting—and as long as it has protected you, it's been worth it.

DESIGN

YOUR OWN PREAMP

By **NORMAN H. CROWHURST***

FEEDBACK can be applied in a variety of ways to produce tone-control effects. The simplest, as we discussed last month, is the single-stage arrangement, with the normal passive network “inverted” in the feedback connection. But proper use of feedback can produce effects not possible with simple passive circuits. Fig. 1 shows one example.

By choosing the right parameters, the circuit gives an accentuated rolloff below the bass-boost frequency. This can help eliminate rumble—a feature that bass boost is apt to emphasize! Also this circuit permits maximum boost to work with a progressively sharper slope, considerably exceeding that possible with passive circuits (Fig. 2). First we'll explain how the circuit works, then how the values are

*Author: *High-Fidelity Circuit Design* (Gernsback Library).

calculated to get the required response.

How it works

Mid-frequency gain is held very nearly constant by the overall feedback resistors R9, R10 with R3, R11. But there is also an internal loop, using R5 from the slider of R7. Varying this internal loop with R7 effectively varies the gain of the pentode stage. As R7 is varied, the amount of feedback produced by the outer loop changes, to keep the overall gain constant. This change in amount of feedback alters the interaction effects, so the response can be made to vary between bass boost and bass cut. More of that in a moment.

For high-frequency control, the conventional “inverted” arrangement is applied, using C4 to give boost by reducing high-frequency feedback, and C6 to give cut, by increasing the high-frequency feedback. Now we'll go

construction or the tabulation in a tube manual—whichever is convenient.)

Feeding the audio output from the triode section through R4 to the pentode grid attenuates some of this gain. (R4 is needed to isolate the stages so the internal feedback loop gives satisfactory control and does not make the triode stage distort.) The net gain, from the triode's grid to the grid of the pentode, without any feedback, works out to about 16.

The pentode section, with a 10,000-ohm plate resistor, 22,000-ohm screen feed resistor (well decoupled with 10 μf, to avoid affecting the feedback response) and 120 ohms bias (also well bypassed with 500 μf) gives a gain of 70. Feedback resistors R9 and R10 act as an ac load for this plate, reducing its no-feedback gain to about 56. So the maximum no-feedback gain of the two stages comes out to 16 times 56, or almost 900.

With R7's slider at the top, there is no internal-loop feedback, and 900 is the gain before the outer-loop feedback cuts it down. With R7's slider at the bottom end, internal-loop feedback is maximum. C2 is large enough not to affect the response within the active range. The voltage fed back to the pentode grid, via R5 in series and R4 and R6 as parallel termination, is half the audio voltage at the pentode plate. This now limits the pentode's effective gain to 2, or the two stages to 32.

Turning potentiometer R7 changes the internal gain from 32 to 900. The outer-loop feedback uses R9, R10 and R3, R11. The first two parallel to 43,000 ohms, while the last two parallel to 2,700 ohms, giving a feedback fraction of $\frac{2.7}{43 + 2.7}$, or about 1/17. So the net outer-loop gain varies from $\frac{32}{17}$, or about 1.9, to $\frac{900}{17}$, or about 53. This is the variation of Aβ. The feedback factor is (1 + Aβ), so it will vary from 2.9 to 54. In db, this is 9.2 to 34.6.

Selecting circuit values

To see what can be done with this, we need the chart of Fig. 3. The response shaping depends on the amount of feed-

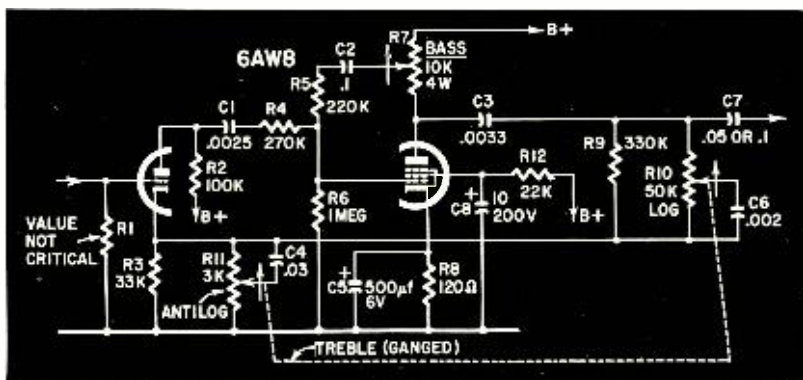


Fig. 1—Circuit of feedback tone control discussed in this article.

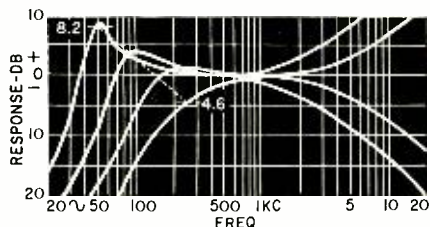


Fig. 2—Response variation covered by the circuit in Fig. 1.

through the calculations that get everything happening at the right place.

The triode section of the 6AW8 has a 100,000-ohm dc load resistor and is coupled to R4, R5 and R6, for ac load, which parallel to look like about 470,000 ohms. The bias resistor is 33,000 ohms in parallel with 3,000 ohms, which is about 2,700 ohms. This produces a gain in the triode section of about 40. (This can be determined from load-line con-

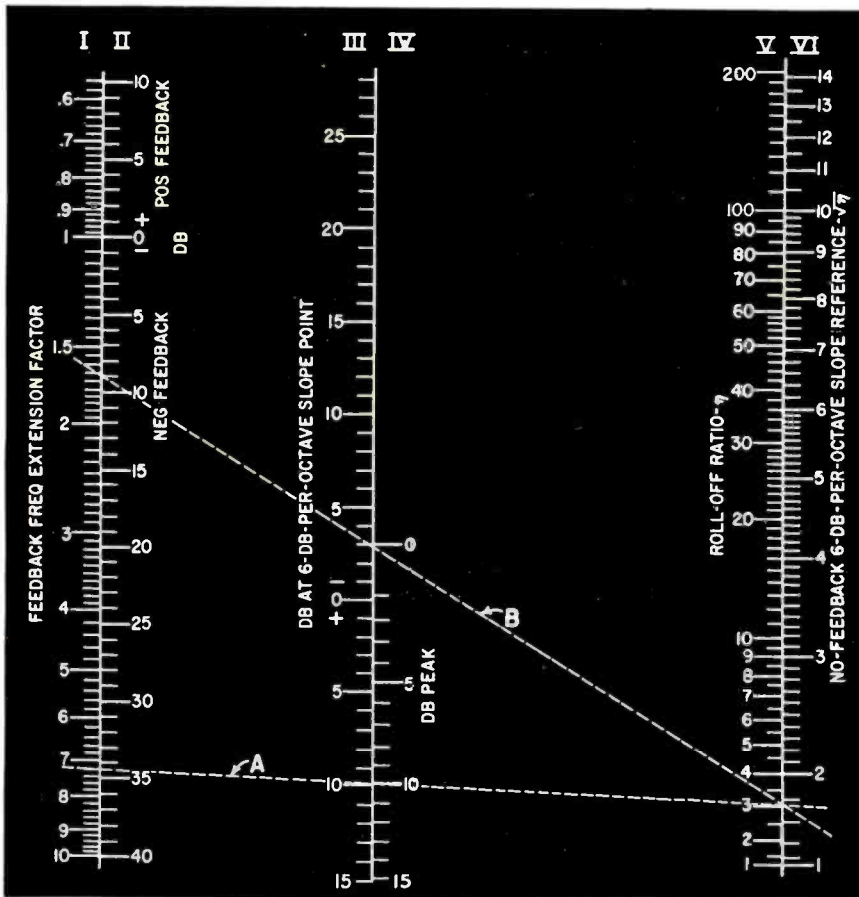


Fig. 3—Nomograph used to calculate the feedback parameters for this type of tone control circuit.

back and the ratio between the internal rolloff frequencies (in this case set by C1 and C3). The db response at a reference frequency (to be explained below) is given on the center scale when a straightedge is laid between the values of feedback at the left and rolloff ratio at the right.

Let's assume we want a maximum boost of 10 db. This occurs with maximum feedback (34.6 db). Using the chart, we line up our straightedge with 34.6 on scale II (the amount of negative feedback) and 10 on scale III (the desired boost at the unity-slope reference frequency) and where this line

(A) cuts scale V we read the rolloff ratio to be 3. Now, using the same rolloff ratio (3), and 9.2 db of feedback instead of 34.6 to plot line B on the chart, we find that we are 3 db down at the unity slope reference frequency. As this means only the minimum position will avoid peaking at all, let's try again.

Choosing a rolloff ratio of 6, the 9.2-db feedback gives 4.6 db down at unity slope reference frequency, while 34.6-db feedback gives 8.2 db up at the reference frequency. But don't conclude that this is all the variation you get—from +8.2 db to -4.6 db at the same point.

That reference frequency

That's not all there is to it. Changing the feedback shifts the reference frequency as well as changing the response shape. Let's see what this reference frequency is and how it is arrived at.

Without feedback, the two couplings have rolloffs related by a predetermined ratio—we have tentatively set for 6. Without feedback, the unity slope reference frequency is at the geometric mean between these rolloffs (Fig. 4). At this frequency, the slope is exactly 6 db per octave. The spacing between each rolloff frequency and the reference frequency is $\sqrt{6}$, or about 2.45.

Now feedback is added, which extends the reference frequency outward. With low-frequency rolloffs it goes downward. The left-hand side of the left scale of Fig. 3 tells how much (the ratio). With 9.2-db feedback, the shift is a factor of 1.7. With 34.6-db feedback, it is 7.3.

Assume now we settle for an 8.2-db boost at 50 cycles. This means 50 cycles is the no-feedback reference frequency divided by 7.3. Or the no-feedback reference frequency is 7.3 times 50 cycles—365 cycles. Going to the other

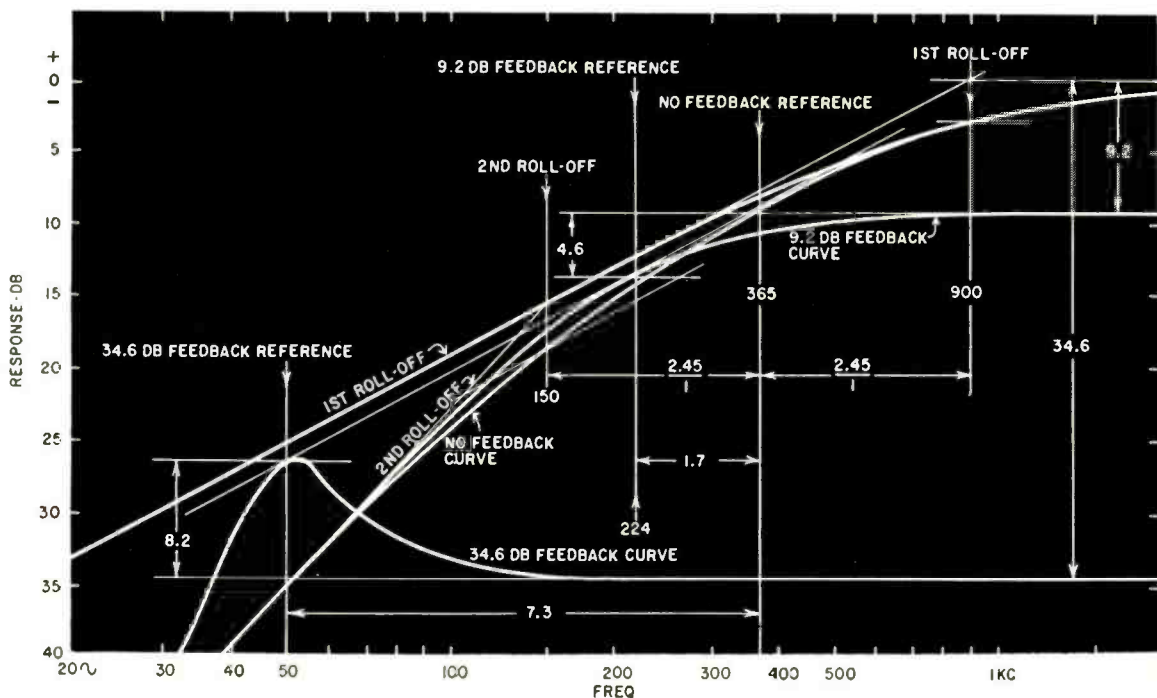


Fig. 4 -- Construction evaluated with aid of Fig. 3. Vertical dimensions are db; horizontal ones are ratio between the frequencies indicated, in accordance with data on nomograph of Fig. 3.

ELECTRONICS CONTROLS LEVEL OF

A lucky break (carefully prepared for in advance) offered the opportunity; electronic knowledge solved the problem

MOLTEN GLASS

By MURRAY BARLOWE *

MANY people have asked me how I, a radio-TV service shop operator, got into industrial electronics servicing. I usually tell them, "It's like getting into anything else—if you want to badly enough, and think about it enough, and plan and prepare long enough, you'll find a break that will make it possible. That's the way it happened to me."

Some time ago I was called by a Mrs. Yahnkers who told me her husband had been having difficulty with their television set. She asked me to come over at lunch time to meet him so he could show me just what the set was doing wrong. I knew that Mr. Yahnkers was the plant manager at the local glass factory, so I made a date with him for the next day.

It turned out that the switch contacts on his tuner were causing intermittents on several channels. I explained it to him, got his OK on a replacement and took the set to the shop.

When I returned it he was there to check it out and, as I learned, to check me out too. I'd been talking up repairing electronics other than home entertainment devices to all my customers, and apparently something I'd said or maybe the way I'd repaired his TV set, had impressed Mr. Yahnkers. Whatever the reason, he asked me if I'd take a look at a problem at his plant, a local manufacturing branch of the Pittsburgh Plate Glass Co., in Hicksville, N. Y.

They were having trouble maintaining the level of molten glass in their furnaces. I suggested that it might be solved electronically. Mr. Yahnkers was interested and told me to see what I could come up with.

The process of manufacturing fiber glass consists of drawing glass fibers from a melting furnace and winding them on a rapidly rotating drum. Broken glass is dropped into the furnace

through an opening in the top, and glass fibers are drawn through openings in a bushing plate on the bottom. Variations in the level of molten glass affect its temperature, thus varying its viscosity. This in turn varies the diameter and causes the drawn glass fibers to break.

The feeding of glass from the hopper was electrically controlled. A circuit was closed at regular timed intervals, dropping a predetermined amount of glass into the furnace. The level of the glass was monitored visually by operators checking 48 furnaces! As the level changed, the rate of feed was adjusted by changing the timer interval. Obviously, what was needed was a sensing de-

a simple control unit attached. This worked for a day, and then became erratic. Investigation showed that, not only was the glass conductive at this high temperature, but so was the burning gas above it. I noticed that the resistance of the gas was higher than the glass so I added a sensitivity control to the unit in an attempt to differentiate between glass and gas resistance. Operation was improved but was still not dependable. The resistance of gas and glass varied so that it was impossible to find a stable setting for the sensitivity control. Further investigation revealed that, even though the resistance of the gas and glass varied all over the lot, the ratio of their resistances was always at least 3 to 1.

This was something that you could hang your hat on. So the next step was to develop a circuit that could sense this 3-to-1 relationship. By using a three-probe arrangement (Fig. 1), I was able to compare the resistance between probe 1 and 3 to the resistance between 2 and 3. Probe 1 is always in the glass and senses glass resistance at all times. Probe 2 is in gas or glass,

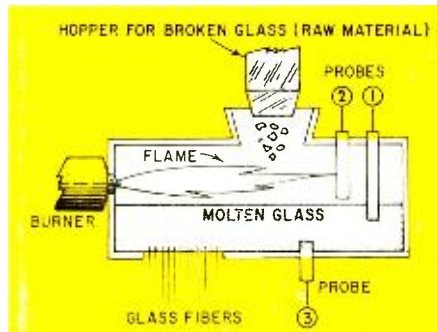


Fig. 1—Probe setup in glass furnace.

vice to check the glass level. It would complete an automatic control loop and eliminate the need for manual monitoring.

First steps

I found out that molten glass is a conductor. So we put a pair of high-temperature metal probes into the furnace, one through the bottom into the glass, the other through the top with its tip set at the desired level. These probes are about the size of long pencils, and are used purely to make electrical contact with the molten glass. The resistance of the glass was measured and

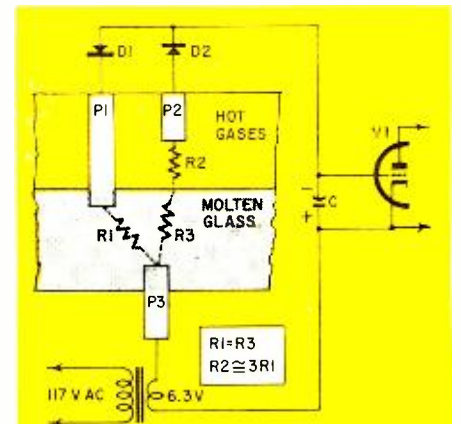


Fig. 2—Simplified diagram showing probe arrangement and how it works.

* Barlowe TV, Bethpage, N. Y.

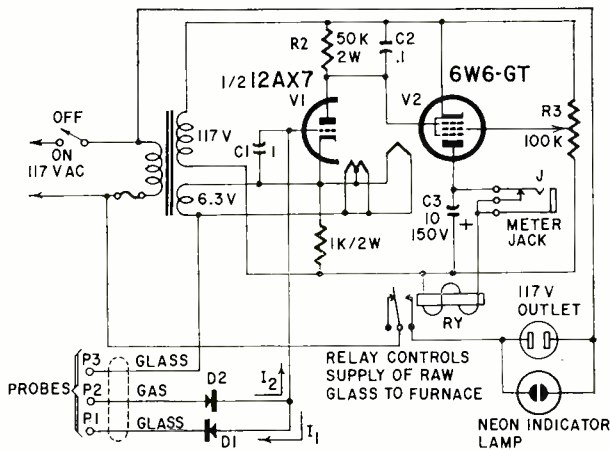


Fig 3—Circuit of complete level-detector unit, less probes

depending on the glass level. The ratio of resistance between 1 and 3 and 2 and 3 indicates positively whether probe 2 is in gas or glass. A small rectified ac voltage is passed through these probe circuits by D1 and D2 (Fig. 2), and the resultant control voltage is applied to the grid of a vacuum tube.

Resistances R1 and R2 represent the resistance of the glass or the gas. When the level is high, both probes are in the glass, the resistances are equal. The currents from the ac source through the diodes are equal and in opposite directions. When the level drops, probe 2 is in gas, resistance goes up at least three times and current through D1 is three times as great as through D2. Capacitor C charges in the polarity indicated and the tube is cut off, causing a relay to close which allows a supply of raw broken glass to drop into a hopper which feeds the charge to the furnace.

We built a prototype unit on this principle and tested it. It operated so well that Pittsburgh flew in a patent

attorney from their home office to evaluate the device. This resulted in US Patent No. 2,868,396, filed March 12, 1956, and granted Jan. 13, 1959. We subsequently manufactured 60 of these automatic control units (48 installed on the furnaces and 12 standby units). We also did the actual wiring and installation of the units.

How it works

Looking at Fig. 3, here's how the unit works:

P1 is the reference probe which always remains in the molten glass. A fixed amount of current flows from the filament transformer through P3 and the glass to P1, through D1, charging capacitor C1 a few volts negative. This is enough to bias V1 beyond cutoff.

If the glass level reaches P2 (gas probe), it eliminates the resistance of the gas. An equal amount of current now flows through both diodes, but in opposite directions. This current flow charges C1 to an equal potential in the opposite direction, exactly cancelling

out the initial negative voltage. This removes the cutoff bias from V1 making it conduct heavily. If the glass level drops, the resistance of the gas is added in series with the resistance of the glass, cutting down the amount of current through diode D2. I₁ is now greater than I₂, charging C1 and biasing V1 beyond cutoff.

If V1 is biased beyond cutoff, its plate voltage goes up. This positive voltage is direct-coupled to V2's grid, increasing its plate current which energizes the relay and closes the circuit to the output socket. This makes glass feed into the hopper. As soon as the glass gets up to the proper level, equal currents zero the voltage across C1, V1 conducts, its plate voltage drops, bias on V2 goes strongly negative (almost to cutoff). The relay then opens, cutting off the feed of raw glass to the hopper that supplies the furnace.

Note that there is no dc power supply—it isn't needed. Raw ac is applied to the tubes, which conduct on each half cycle. Capacitor C2 filters the pulsating dc developed across R2, and C3 filters the voltage across the relay coil, eliminating relay chatter.

R3 sets V2's operating point. J is a metering jack which is normally closed. It is used to measure the relay current when setting R3. The neon indicator lamp shows when the control is calling for glass.

A test set simulates the conditions in the furnace for setting units up in the shop and checking them out without having to use an operating furnace.

The test set consists of three resistors, which simulate the resistances of the gas and the glass, and a switch, which simulates raising or lowering of the glass level to contact probe P2. END

HOW LEAK DETECTORS WORK

LEAK detectors are extremely sensitive instruments which locate and indicate the size of very small leaks by measuring the rate of flow of a rare gas, usually helium, through the leaks. The sensing element is a mass spectrometer tube which responds to the presence of minute quantities of helium, providing an electrical signal proportional to the amount of the gas present. Leak detectors are used for production testing of practically anything which must be hermetically sealed when it is in use.

The object to be leak-tested is exhausted to a high vacuum, then sprayed with helium while its empty insides are connected to the leak detector. Another method requires that the object be filled with helium under pressure, and the leak detector then searches the surface of the object.


The mass spectrometer tube detects the presence of helium in microscopic quantities by connecting to the vacuum system so that the tube is in series with the test object and the vacuum pumping system. As gas molecules enter

the spectrometer tube, they are bombarded (Fig. 1) by electrons emitted from the hot heater. When a bombarding electron strikes a molecule, an electron is knocked off the molecule, leaving it positively charged, or ionized. These positive ions are pushed out of the chamber, or "ion gun," by an ion repeller grid.

Other electrodes appropriately charged direct the ions into a beam, which is passed between the poles of an external permanent magnet. The magnetic field deflects each ion, the lighter ions being deflected more than the heavier ones. The spectrometer tube is tuned so that the helium ions are the only ones deflected through exactly the correct angle to hit the target. All other ions are stopped by the baffle plates.

The flow of helium ions to the target constitutes a small electrical current which is amplified by an electrometer tube and then built up by a very stable amplifier which drives a meter or produces an audio tone. Since only the helium ions reach the collector, spurious

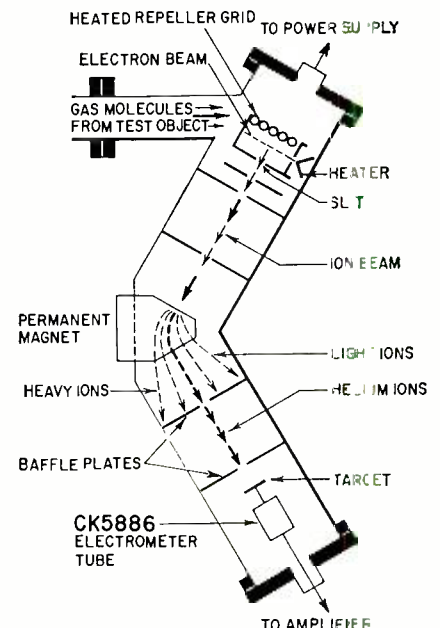signals from other ions are therefore eliminated. END



AUDIO GENERATOR

for Industrial Service Jobs

For field-service work, the industrial technician needs a portable audio generator. Here is a fixed-tone 1-transistor unit that is hard to beat

By WILLIAM F. KERNIN

A PIECE of test gear is usually designed to fit the type of equipment to be serviced and the conditions that may be encountered on location. This seems especially true in industrial electronics. One example is a field-service audio oscillator designed for the industrial electronics technician.

It is a single-frequency instrument with a variable-amplitude output. Completely self-contained, the one-transistor unit does not require external power connections.

In setting up and adjusting industrial motion-picture sound-recording equipment, a 3,000-cycle tone is often recommended. Also, 3,000 cycles falls within the band of frequencies to which the average ear is most sensitive—particularly at low amplitude. So the oscillator is designed for a 3,000-cycle output. This becomes very valuable when servicing equipment in locations with a high background-noise level. Typical examples include production areas, computer rooms and dispatch and control areas.


Stability is another design factor. Not so much frequency stability, but rather the ability to provide a clean sine wave into a wide variety of loads.

Finally, for economy and ease of repair, the test oscillator has to be simple and built from the same types of components used in companion pieces of test gear, if possible.

Circuit details

The diagram shows the circuit. A Colpitts oscillator proved more stable under adverse loading conditions than other forms of transistor audio oscillator circuits tried. The output remains a clean 3,000-cycle sine wave with 2% total measurable distortion for loads down to 5 ohms.

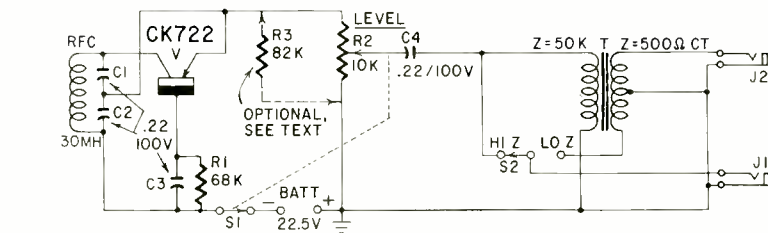A CK722 was used with a 22.5-volt supply to conform with parts used in companion equipment. The tank circuit—C1, C2, and RFC—determines the operating frequency and supplies the necessary feedback to sustain oscillations. Resistor R1 provides the proper operating bias on the transistor. Potentiometer R2 acts as the emitter load in addition to controlling output ampli-



R1—68,000 ohms, 1/2 watt
 R2—pot, 10,000 ohms, linear taper, with spst switch
 R3—see text (optional)
 C1, 2, 3, 4—0.22 μf, 100 volts, paper
 BATT—22.5 volts (Burgess U-15, Mallory RM-412R or equivalent)
 J1, 2—phone jacks
 RFC—30 mh (Miller 692 or equivalent)

S1—spst on R2
 S2—spdt toggle
 T—output transformer: primary 50,000 ohms; secondary, 500 ohms ct (UTC H-1 or equivalent)
 V—CK722
 Case—4 x 4 x 2 inches
 Miscellaneous hardware

tude. Capacitor C4 and transformer T match the oscillator's output to a variety of loads.

A pair of phone jacks (J1 and J2) and switch S2 provide three types of output.

With S2 in the LO Z position, J1 and J2 provide a 500-ohm balanced line output. These jacks are mounted to match the duplex phone plug used for patch cords in broadcast and communications work. If a low-impedance, single-ended output is desired, one jack is used with ground. Such an output can be used for loads down to 5 ohms.

With S2 in the HI Z position, J1 is across T1's high-impedance primary. This provides maximum output into high-impedance loads ranging from 1,000 ohms up.

Output for the HI Z position can be set for a maximum of 1 volt rms into a 50,000-ohm load. This corresponds to a 100-mv output from the balanced-line jacks into a 500-ohm load with S2 in the LO Z position. As the loading increases, output voltage drops. However, the output will remain a pure sine wave with 2% overall distortion down to a 5-ohm load.

The maximum output voltage is determined primarily by the value of the bias resistor (R1) and, to a lesser degree, by R2. The values shown produce a maximum HI Z output of approximately 0.9 volt—90 mv for the LO Z balanced output. Resultant total current drain on the battery—1.8 ma. For the full 1-volt output, insert resistor R3 and adjust about the typical value shown to obtain the exact voltage, if desired.

A 4 x 4 x 2-inch black crackle utility box forms the basic package for the unit. Physical parts layout can be seen from the photographs. A Burgess U-15 battery—22.5 volts—is the power source.

Wiring and parts placement are not critical. The transistor is soldered into the circuit for ruggedness. A proper

heat sink on the leads should be used when soldering the transistor into the circuit. This prevents damaging the unit with excessive heat. Finally, correct battery polarity must be observed.

Put it to work


As an audio source for normal signal tracing, the transistor audio oscillator serves quite well. Requiring no external power, it is ideal for checking remote microphone and communications lines. An audio signal is fed into the line using either the HI Z or balanced 500-ohm output—depending on the characteristics of the line. This signal can be readily checked at the other end with a pair of headphones or the existing audio equipment.

A variation of this procedure can be used to check and identify multi-conductor lines such as those used in intercom and multiplex control systems.


The unit lends itself to servicing professional audio and tape recording equipment. Since its output is a clean 3,000-cycle sine wave, it is heard as a pure tone through appropriate reproducing equipment. To check tape recording gear, record the 3,000-cycle signal on the tape at a suitable level. When played back, it should still be a pure 3,000-cycle tone.

Any irregularities can be quickly detected by ear. Things such as sticky or dirty heads, variations in motor speed, roughness and irregularities in a tape flywheel drum, incorrect head positioning and other mechanical defects show up as variations in the reproduced tone. To check the reproduce electronics or system alone, use a pre-recorded tape of the 3,000-cycle tone. This procedure also applies to checking audio gear for excessive distortion and overload.

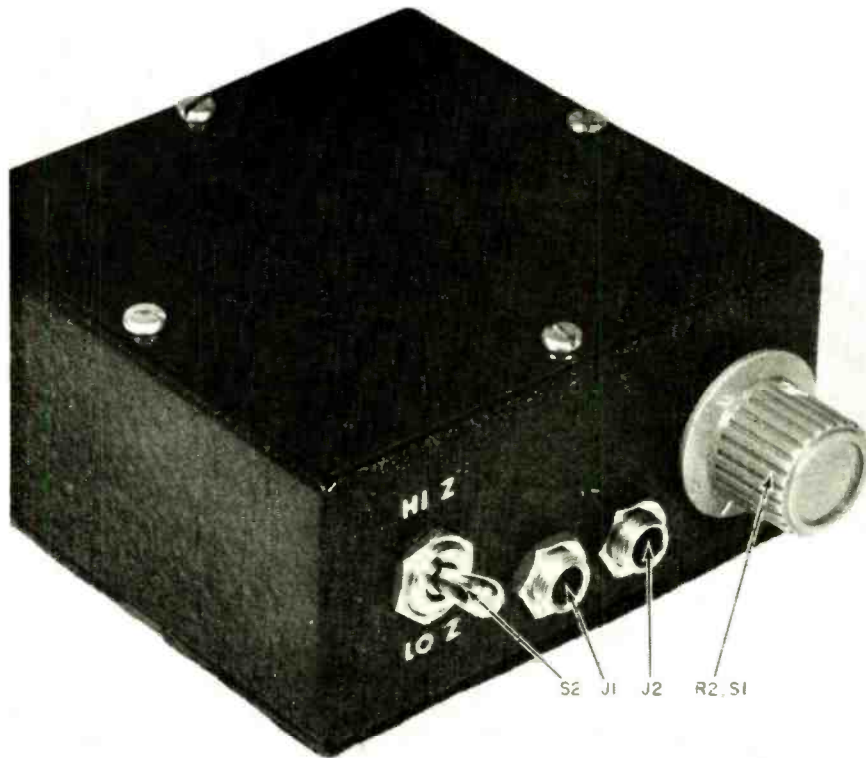These are a few of the many jobs the transistor audio oscillator can do and do well. It was designed for a specific type of service but is readily adaptable to many other tasks. END



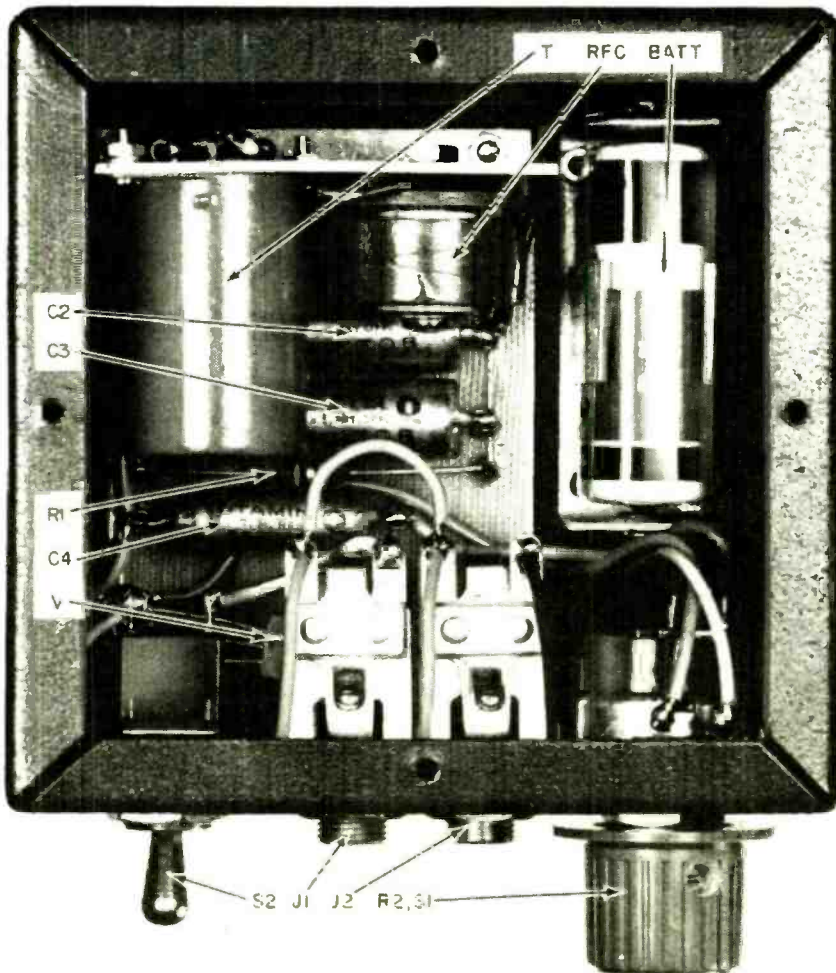Completed unit in its 4 x 4 x 2-inch case.



All components are solidly mounted to avoid damage from rough handling.

NEXT MONTH

All-Transistor FM Receiver

Circuit analysis of a popular imported transistor FM portable. A working knowledge of its circuits will stand you in good stead when domestic models hit the market.

Servicing Horizontal Sweep Circuits

Too many technicians short-change themselves by not making systematic and exhaustive tests when troubleshooting sweep circuits. Follow the author's step-by-step guide to quicker sweep-circuit repairs.

Transistorized Photoflash

Constant light output, long battery life, fast recycling and light weight are but a few of the features of this electronic photoflash unit. Ordinary flashlight cells deliver about 80 flashes.

VTVM Switches to Powerless Voltmeter with Simple Conversion

A vtvm is useless away from ac power lines. A switch and a couple of resistors will convert it to a full-range dc voltmeter useful for servicing when power is not available.


Putting Audio Transformers to Work

Audio transformers are much more complex than they seem and their performance can be tricky in some circuits. A well-known authority explains how to use them and modify their response to meet your needs.

PHOTOELECTRIC CONTROL MADE EASY

It takes only five components and a case to build what is one of the simplest photoelectric controls

By R. L. WINKLEPLECK

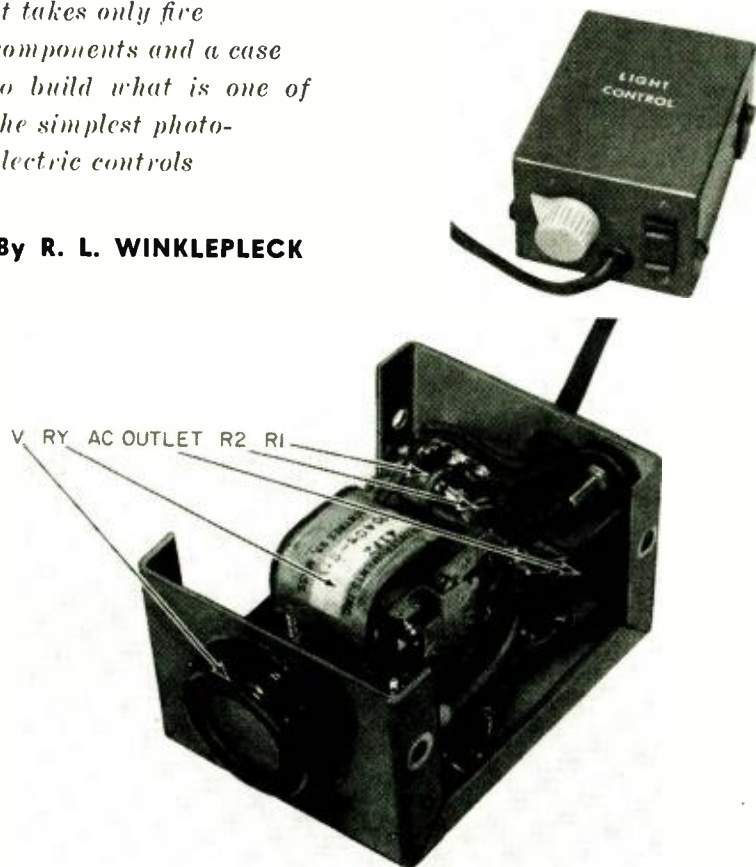

(Top right) Completed light control. Sensitivity control and ac outlet for controlled device are on front panel.


(Above) Two resistors, photocell and relay are vital parts of the light control.

THE many very real needs for control devices which respond to variations in light intensity have resulted in a number of commercial control units and many designs for home construction. Applications seem almost without limit and more are being found every day. There are automatic door openers, street-light controls, home and industrial controls for automatically turning on lights in the evening, liquid-level indicators, industrial counters, safety interlocks, burglar alarms, etc.

Convenient as such devices are, even around the home, they're not inexpensive since most of them depend on an amplifying system which builds up the comparatively weak signal of the light-sensing tube or cell to a level great enough to actuate a relay. But this cost picture has changed with the appearance of a photoconductive cell which combines good sensitivity with improved power-handling ability and low price. It is now possible to build

a light-actuated control in which the photocell *directly* drives a moderately sensitive relay, and doesn't require direct sunlight to do so. Thus, a power source, a relay and the new photocell make up the complete control.

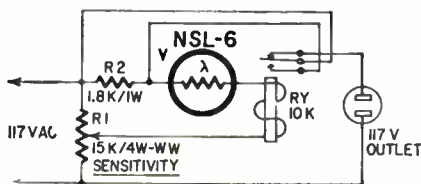The diagram and photos show a control unit specifically designed to turn on lights automatically and un-



- R1—pot, 15,000 ohms, 4 watts, wirewound
- R2—1,800 ohms, 1 watt
- RY—spdt relay, 10,000 ohms (Sigma 41-FZ-10000-ACS-SIL or equivalent)
- V—photoconductive cell (NSL-6, see text)
- 117-volt outlet
- Case, 2 3/4 x 2 1/8 x 1 1/8 inches
- Miscellaneous hardware

Circuit of the uncomplicated device.

attended as nighttime approaches. It has only four major components. Wirewound potentiometer R1 is a voltage divider that acts as a sensitivity control. Cadmium sulphide photoconductive cell V is a light-sensitive resistor whose resistance varies inversely with light intensity. It is hermetically sealed in a 1 1/4-inch diameter metal disk with a 0.62-inch window. It has a 1-watt power dissipation rating. The cell used is a National Semiconductors type NSL-6 available in this country through Harvey Radio, 103 W. 13rd St., New York 36, N. Y. Price \$2.45.

The relay is a fairly sensitive ac unit. Resistor R2 isn't absolutely essential, but does contribute to smooth operation for an application where light intensity varies slowly. Frequently, under such conditions, there is a tendency for relay chatter at the point where it is just ready to pull in or drop out. In this circuit, the relay shunts R2 on pull in and restores it to the circuit on release. This effectively swings total circuit resistance rapidly across the critical point and minimizes relay chatter.

Construction is obviously simple. All components are easily assembled in a 2 3/4 x 2 1/8 x 1 1/8-inch case. Leads are short and their placement is non-critical. It's a very short one-evening project.

Warning: do not make any connections to the unit's case or you will have a hot-chassis hazard in the making. As an added precaution, it might be wise to place the unit in some out-of-the-way spot when it is in use.


In use, the unit is plugged into a convenient outlet and placed close to a window. A lamp is plugged into the outlet on the unit. The SENSITIVITY control is adjusted so the lamp goes on when outside light fades to the desired level. The only precaution is to be sure the light from the lamp does not strike, directly or by reflection, the sensitive area of the photocell. A black cardboard tube over the cell might be helpful. For outside use, it can be pointed at northern sky and a small shelter rigged up to protect it both from weather and any interfering lights.

Only slight modifications are necessary to adapt this basic unit to other applications. If it's to be used to open garage doors when illuminated by the auto headlights, R2 may be omitted and the door operator connected to the normally open contacts on the relay so the operator is actuated when light strikes the photocell. Protect the light cell from daylight with a long black tube aimed so the cell is directly illuminated by the auto headlights as the car approaches the garage.


This unit has an advantage in addition to sensitivity, simplicity, dependability and construction economy: it doesn't cost much to operate. Many applications require such a control to be in constant operation. This unit uses less than 1 watt in darkness and less than 2 watts when illuminated. END

UNIVERSAL 2-TERMINAL OSCILLATOR

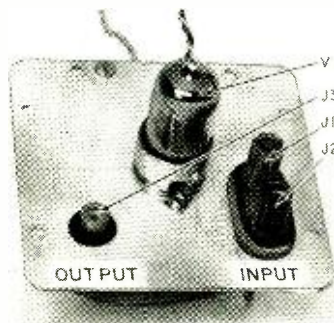Connect a resonant circuit across the two input terminals and the output frequency is the test circuit's resonant frequency



By PAUL S. LEDERER

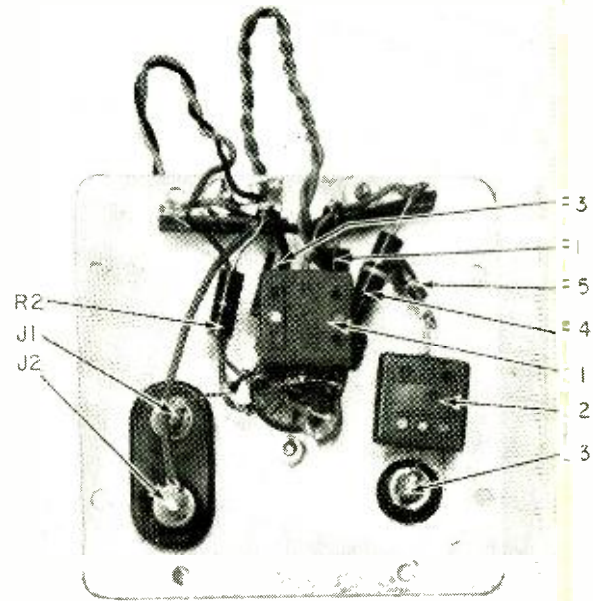

Under the chassis are the few resistors and capacitors that form the guts of the 2-terminal oscillator.

On top of the chassis only the tube and output and input terminals show.

WHILE experimenting with circuits involving a number of parallel-resonant networks, I needed a quick and convenient way of locating the resonant frequency or for tuning the network to resonate at a desired frequency.

The circuit that developed is a two-terminal oscillator that consists of a cathode-follower direct-coupled to a grounded-grid voltage amplifier. Part of the signal at the grounded-grid amplifier's plate is fed back to the cathode-follower's grid through a resistor and blocking capacitor. This positive feedback makes the circuit operate as a multivibrator as long as there is no resonant circuit across the input terminals. When a resonant circuit is connected, the system oscillates at the parallel-resonant frequency.


Experiments indicate that the oscillator works best when the inductances are between 1 and 100 mh. Inductances tested included if transformers, toroidal coils and pie-wound rf chokes. Tuning capacitances were varied over a wide range and showed that the oscillator works well up to about 500 kc.

A series of tests were made using various combinations of inductances and capacitances and comparing the resonant frequencies obtained with the

two-terminal oscillators and those obtained by feeding the tuned circuit from a constant-current audio oscillator and noting the oscillator frequency that gave maximum voltage across the tuned circuit. Variations did not exceed 3% except when self-resonant frequencies were measured. In these cases, frequency variations up to 10% are probably caused by variations in the capacitance of leads and instruments.

Tests to determine self-resonant frequencies of rf chokes with no external tuning capacitance across the choke indicated that the oscillator circuit presents a capacitance of about 30 μmf across the input terminals. This tends to make a self-resonant frequency measured in this manner a little lower than the correct one.

While it was not possible to find minimum Q values required for satisfactory operation, it appeared that the circuit would function properly as long as the parallel impedance of the tuned circuit exceeded 300 ohms. Thus, for example, a 1-mh pie-wound rf choke in parallel with a .01- μf capacitor (about 320 ohms parallel impedance) makes a 51-kc oscillator frequency (the computed value). Raising the capacitance to .02 μf (parallel impedance about 220 ohms) stops oscillations.

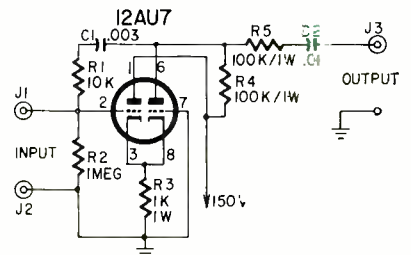


- R1—10,000 ohms, 1/2 watt
- R2—1 megohm, 1/2 watt
- R3—1,000 ohms, 1 watt
- R4, R5—100,000 ohms, 1 watt
- C1—.003 μf , mica
- C2—.01 μf , mica
- J1, J2—dual 5-way binding posts
- J3—pin jack
- V—12AU7
- Socket, 9-pin miniature
- Chassis
- Miscellaneous hardware

Circuit of the 1-tube unit.

Similarly, a 100-mh precision inductor shunted by 0.32 μf (parallel impedance about 500 ohms) produces oscillations at 890 cycles. Raising the capacitance to 2.0 μf (parallel impedance about 200 ohms) stops oscillations.

A 12AU7 double triode is used in the oscillator circuit. About 6 ma at 150 volts is required for the plate supply. The output voltage delivered by the circuit through a 100,000-ohm resistor and .01- μf capacitor (to reduce loading of the circuit) ranges from about 25 volts rms at the low frequencies to about 0.5 rms near 500 kc. It varies somewhat with the type of inductance used, but is generally high enough for oscilloscope display (Lissajous patterns for frequency determination) or in industrial or research use, for feeding direct reading electronic counters. END


BENCH

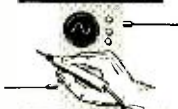

TESTED

Tests conducted by a member of the staff of RADIO-ELECTRONICS show that the oscillator operates substantially as the author indicates. However, it is useful up into the lower megacycle range and is not limited to 500 kc. Accuracy, as checked with a scope, is better than 3%. Parallel impedance of tuned circuit must be more than 300 ohms for the circuit to operate properly. Without any external components connected to the input terminals, the circuit becomes a free-running oscillator.

That Versatile ELECTRON- RAY TUBE

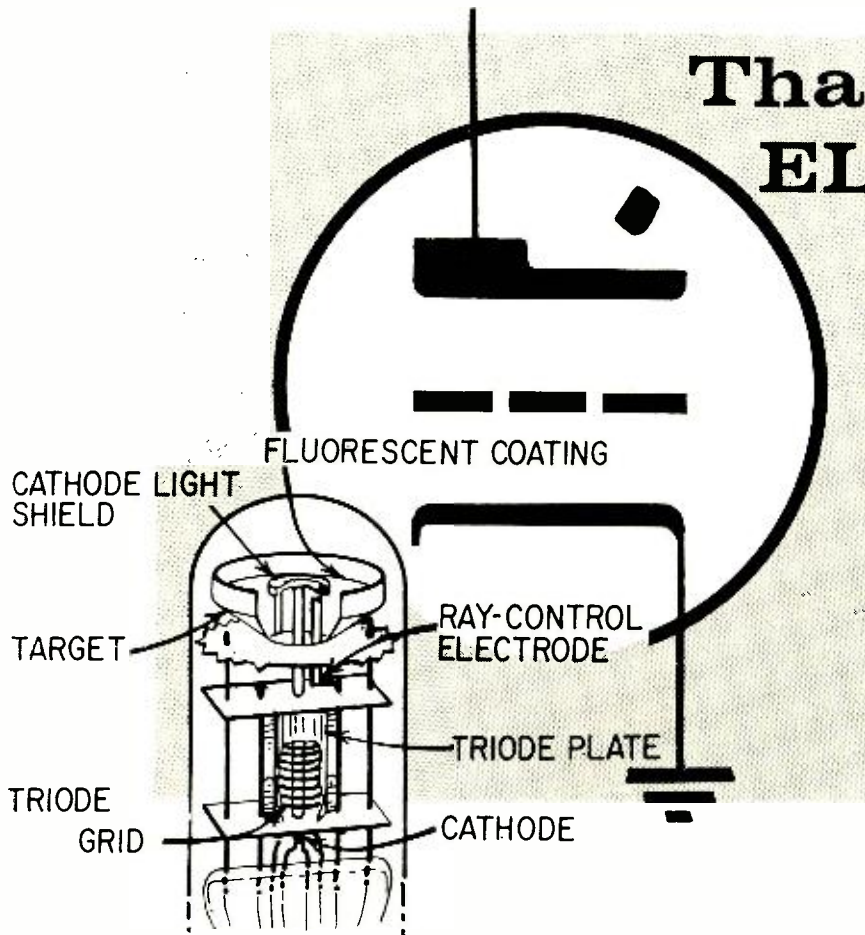

Some interesting and useful test instruments can be built around it. Four such devices are described here—a volt-ohmmeter; picture-tube circuit tester; grid-dip meter, and a capacitor tester

By JOHN POTTER SHIELDS

THE electron ray tube, more popularly known as a "magic eye tube," was developed in the mid '30's for use as a visual tuning indicator in radio receivers. Construction of such a tube is shown above.

The most common type of electron-ray tube has two sections. The first, a triode, operates as a dc amplifier and the second is the actual electron-ray indicator. In operation, the heated cathode emits electrons which are attracted by the positively charged target of the electron-ray section. This target is

controlled by the ray-control electrode. The ray-control electrode is proportional to the voltage at the triode section's grid. The triode plate current through load resistor R (Fig. 1) produces a voltage drop which determines the voltage applied to the ray-control electrode, since it is directly coupled to the triode plate. Therefore, increasing the negative voltage at the triode's grid causes a corresponding decrease in target shadow angle and vice versa.

This description applies to 6E5 and 6U5 tubes. The 6E5 contains a sharp-cutoff triode while the 6U5 contains a remote-cutoff one. The 6AF6 operates on a similar principle, but contains two independent ray-control electrodes and no triode control section. (There is also

a type 6AL7 electron-ray tube which was designed for use as a tuning indicator in FM receivers.)

Now that we have seen how this tube works, let's see what we can use it for besides a tuning indicator.

Volt-ohmmeter

The multimeter circuit of Fig. 2 uses an inexpensive 6E5 to take the place of a sensitive meter movement. It measures positive or negative dc voltages, ac voltages and resistance. It has the standard high input impedance of a true vtvm and four voltage and resistance ranges. Resistor values for the string can be calculated to suit, or picked up from any article on making


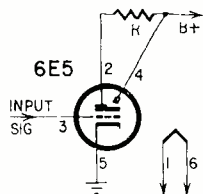


Fig. 1—Basic indicator circuit using a 6E5.

coated with a phosphor which fluoresces when struck by a stream of electrons.

An element known as a ray-control electrode is mounted between the cathode and target. When this electrode is more negative than the target, electrons headed toward the target space behind the ray-control electrode are repelled. This causes that portion of the target to remain unlit, casting a shadow. As the ray-control electrode becomes less negative, the shadow angle decreases.

The voltage applied to the ray-con-

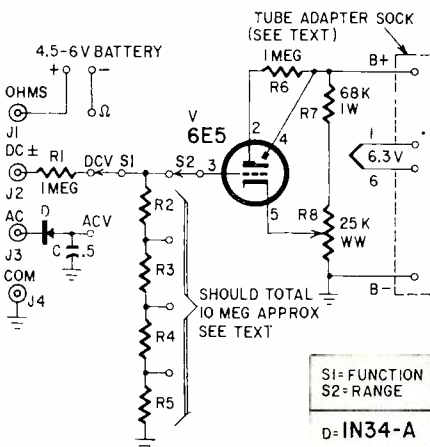

- R1—1 megohm
- R2, 3, 4, 5—select to give desired ranges (total resistance should be approximately 10 megohms)
- R6—1 megohm
- R7—68,000 ohms, 1 watt
- R8—pot, 25,000 ohms, wirewound
- All resistors 1/2-watt 10% unless noted
- C—0.5 μ f, 600 volts
- D—IN34-A
- J1, 2, 3, 4—pin or tip jacks
- S1—single-pole 3-position rotary
- S2—single-pole 4-position rotary
- V—6E5
- Battery, 6 volts
- Socket, 6-pin for V
- Test adapter socket (see text)
- Chassis to suit
- Miscellaneous hardware

Fig. 2—A 6E5 takes the place of sensitive meter in this vom circuit. Unit has the same high impedance as a vtvm.

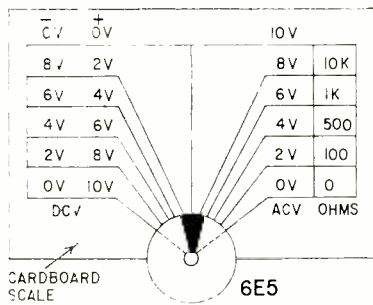


Fig. 3—Dial scale used with the electron-ray vom.

a vtvm. Because of its extremely high input impedance, it will not load the circuit under test. This is especially valuable when measuring oscillator grid and avc voltages. The standard multimeter, with its rather low input impedance, may draw excessive current from such a circuit, causing it to function improperly and giving false reading. This little meter is rugged and compact and practically burnout-proof. There is no delicate meter movement to be damaged.

Another unusual feature of the meter is its power supply. All operating voltages are derived from the device under test. A tube adapter socket is used to tap off operating voltages. Since almost all radios, amplifiers and TV sets use a power-amplifier pentode somewhere in the circuit, you only have to remove this tube, insert the adapter and reinsert the tube in the top of the adapter. The tube must be inserted in the adapter or operating voltages in the device being tested may be upset. A miniature adapter can be used if desired or a small power supply can be built into the meter.

The meter scale (Fig. 3) is self-explanatory. Calibration is simple, requiring only a variable ac and dc voltage supply and a calibrated meter. The ohms scale is calibrated, using a decade resistance box and a small battery.

An unusual trick is used in the meter. A tuning eye gives a shadow-angle decrease only with a corresponding increase in *negative* grid-to-cathode potential and normally would be useless for measuring positive input voltages. This problem is solved by connecting a potentiometer between B-plus and ground. The cathode of the 6E5 is connected to the movable arm

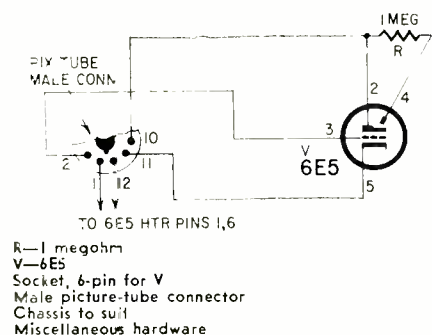


Fig. 4—A few easy-to-get parts go together to form a picture-tube circuit tester.


of the pot. Thus, the pot can be adjusted to make the cathode more positive than the grid, which is the same as making the grid negative with respect to the cathode. The arm of the pot is adjusted so that the 6E5 shadow just closes. Now, a positive potential applied to the input of the meter increases the shadow angle from zero with an increase in *positive* input voltage. Since the positive voltage required for a given increase in shadow angle is identical with a given negative voltage for the same decrease, no separate calibration is required for positive and negative scales. The crystal diode in the ac circuit must be polarized to provide a negative output.

Picture-tube circuit checker

Fig. 4 shows another very handy little tester. This unit helps check the operation of a TV receiver. The CRT socket is removed from the set's picture tube and plugged into our gadget. If heater voltage is being applied the 6E5's heater will light. If first anode voltage is reaching the picture tube, the 6E5 will show its familiar greenish target glow. If video information is reaching the cathode or grid of the picture tube (as the case may be), the 6E5 shadow will have a hazy, fluctuating appearance. This gadget is easy to build and its use can save the service technician a lot of time and trouble.

Grid-dip meter

Fig. 5 shows our electron-ray tube

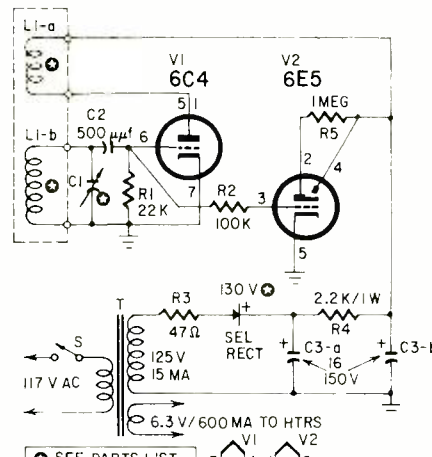


- R1—22,000 ohms
- R2—100,000 ohms
- R3—47 ohms
- R4—2,200 ohms, 1 watt
- R5—1 megohm
- All resistors 1/2-watt 10% unless noted
- C1—variable capacitor, value to match plug-in coils
- C2—500 μ f
- C3—16-16 μ f, 150 volts, electrolytic
- L1—set of plug-in coils to give desired frequency range
- RECT—selenium, 130 volts, 20 ma
- S—spst toggle
- T—power transformer: primary 117 volts; secondary, 125 volts, 15 ma; 6.3 volts, 600 ma (Stancor PS-8415 or equivalent)
- V1—6C4
- V2—6E5
- Socket, 6-pin for V2
- Socket, 4-pin for L
- Chassis to suit
- Miscellaneous hardware

Fig. 5—A grid-dip meter is another instrument in which an electron-ray tube can be used.

used in a grid-dip meter. Here the electron-ray tube, a 6E5, takes the place of a 0-1-ma meter. The 6E5 is inexpensive and much more rugged than the meter movement. A tickler feedback circuit employing four-prong plug-in coils is used. The 6E5 grid is connected through an isolating resistor to the grid of the 6C4 oscillator. When the grid-dip oscillator (gdo) is tuned to resonance with an external circuit, the 6C4 grid voltage drops, causing a drop in the 6E5's negative grid voltage. This, in turn, decreases the 6E5's shadow angle. In using this or any other gdo, do not couple it too near the circuit under test. Too close coupling broadens the eye-shadow dip, giving less accurate readings.

Checking capacitors

A capacitor checker is another use for the 6E5. The circuit in Fig. 6 is such a device. When switch S2 is in position A, the capacitor under test is charged by the dc power supply. If the capacitor is shorted or very leaky, the neon lamp in series with it lights. If the capacitor is intermittent, the neon lamp flashes erratically. When switch S2 is thrown to position B and if the capacitor is OK, the 6E5 shadow first closes completely and then gradually opens to its normal angle. If the capacitor is open, the shadow angle remains unchanged. The time it takes the shadow angle to return to normal after it has closed depends mainly upon the capacitance of the capacitor being tested. However, by familiarizing oneself with the action of this device with known good capacitors, one can make a good check of the quality of a suspected unit. For a given value of capacitance, the time it takes the shadow angle to return to normal will be longer with a higher quality capacitor—less leakage.

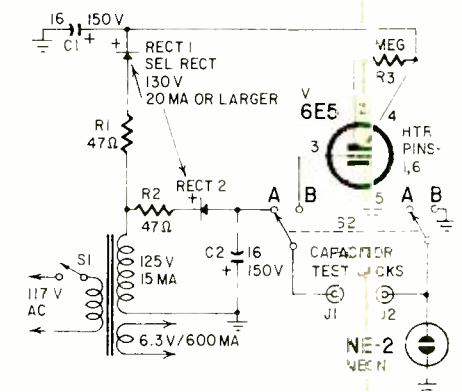

- R1, 2—47 ohms, 1/2 watt, 10%
- R3—1 megohm, 1/2 watt, 10%
- C1, 2—16 μ f, 150 volts, electrolytics
- J1, 2—pin or tip jacks
- RECT 1, 2—selenium, 130 volts, 20 ma or larger
- S1—spst toggle
- S2—dpdt toggle
- T—power transformer: primary 117 volts; secondary, 125 volts, 15 ma; 6.3 volts, 600 ma (Stancor PS-8415 or equivalent)
- V—6E5
- Socket, 6-pin for V
- Neon lamp, NE-2
- Chassis to suit
- Miscellaneous hardware


Fig. 6—This simple capacitor checker can be built in an evening.

mini-capacitance

TEST SET

Handy instrument measures capacitances between 1 and 5,000 $\mu\mu\text{f}$

By DAVID STONE

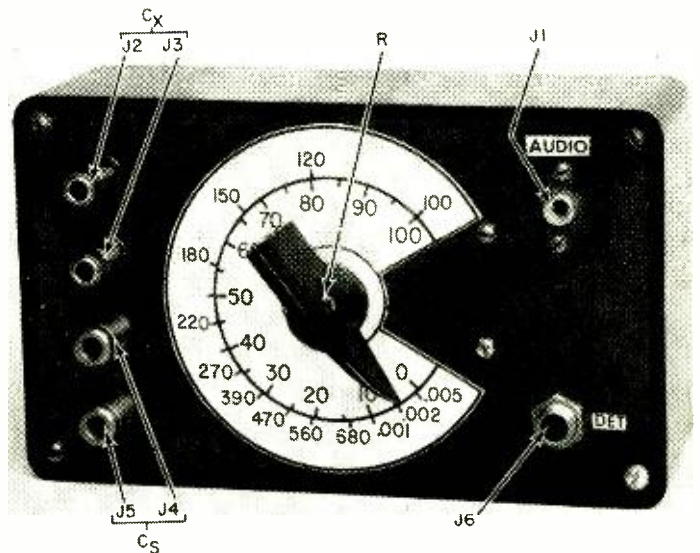

ANY electronic experimenter or technician will find lots of use for this instrument. It is specially designed for capacitances from about 5,000 $\mu\mu\text{f}$ down to 1 $\mu\mu\text{f}$ or less. Thus it can measure short transmission lines, interelectrode capacitance, unknown micas and ceramics, etc. Another important application: use it to set variables and trimmers to required values. Easy to assemble and

operate, when accurately calibrated, it is capable of very high precision.

The basic circuit (Fig. 1) consists of a transformer, standard capacitor and calibrated potentiometer. An external audio generator feeds the primary of transformer T. It also sends current through capacitor C_x , the unknown. The transformer's secondary feeds capacitor C through a voltage-dividing network. Note that the windings must

be connected out of phase, so detector currents will oppose.

The current through the unknown is $E_1 \times C_x$ (if we ignore detector impedance). Through C it is $E_2 \times C_s$. When these are equal (and opposite), no sound is heard or measured at the detector jack. Therefore at balance $E_1 C_x = E_2 C_s$. Since C_s is known, it is easy


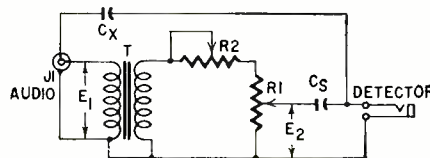


Fig. 1—Basic circuit of the mini-capacitance checker.

to calculate C_x if the voltage ratio is known. Thus, R1 can be calibrated in terms of voltage ratio. Then, at null, it is easy to calculate C_x from the dial setting. Still better, R1 may be calibrated directly in terms of C_x for any given C_s . This is the method used here and it will be described.

Fig. 2 is a more practical form of the instrument. All components are mounted on a bakelite panel made for a box measuring 6 x 3 3/4 x 2 inches. Transformer T is a subminiature transistor unit available from Lafayette Radio (Argonne AR-113). Any other similar transformer would also work well. For example, an interstage transformer with a 500-ohm primary and a 5,000-ohm center-tapped secondary is

(Continued on page 70)

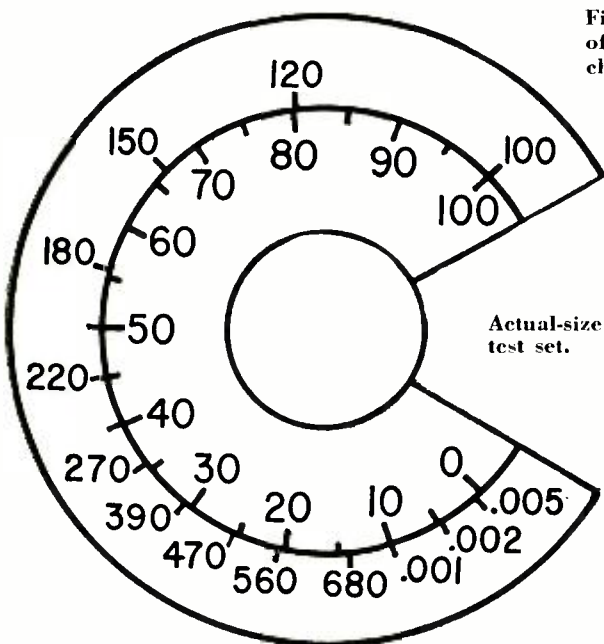

Actual-size dial for the test set.

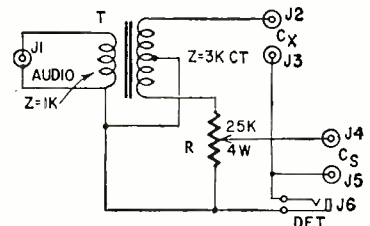


Fig. 2—Complete circuit of the test set.

R—25,000 ohms, 4 watts, linear taper
T—see text
J1—phono jack
J6—phone jack
J2, 3, 4, 5—binding posts
Bakelite box 6 x 3 3/4 x 2 inches

**FROM
HEATHKIT®
... 12 NEW
AND
WONDERFUL
STEREO,
MARINE,
AMATEUR
& TEST
GEAR
ITEMS!**



HEATHKIT AA-50 \$79.95

**New hi-fi stereo features!
25/25 watt stereo amplifier kit**

In one handsome package, you get both stereo power and control, with a host of deluxe features. B-f rated at 25 watts per stereo channel (50 watts mono) this new Heathkit design includes channel separation control; new mixed center speaker output; stereo reverse and balance controls; separate tone controls for each channel with ganged volume controls, and five switch-selected inputs for each channel. Ease of assembly is assured by two circuit boards, minimizing the possibility of wiring errors. Adjustment of individual channel controls gives a pseudo-stereo effect to even monophonic program material. 30 lbs.



HEATHKIT DF-3 \$99.95

**Now is the time to build marine equipment
and Heath brings you a new
3-band direction finder kit**

Featuring a nine-transistor circuit . . . flashlight battery power supply . . . preassembled, prealigned tuning section . . . three bands (beacon and aeronautical broadcast, and marine-telephone) . . . and a new "sense" antenna system that eliminates 180° ambiguity in bearings . . . this beautifully styled, splash-resistant, rugged instrument is an incomparable value at its low Heathkit price. 13 lbs.

MONEY-BACK GUARANTEE

Heath Company unconditionally guarantees that each Heathkit® product assembled in accordance with our easy-to-understand instruction manual must meet our published specifications for performance or your purchase price will be cheerfully refunded.

Build now for summer fun & enjoyment

HEATHKIT® GIVES YOU MORE IN THESE TEN WAYS:

- 1. Building a Heathkit is easy**—Check-by-step instruction manuals make it virtually impossible for you to fail.
- 2. Building a Heathkit is quick**—No complicated, technical jargon for you to decipher; at most, a Heathkit takes only a few evenings to assemble.
- 3. Building a Heathkit is economical**—Mass production and purchasing economies are passed directly along to you, our customers.
- 4. Building a Heathkit is educational**—As you build, you learn . . . more about electronics, more about the component units and when and where to add them.
- 5. Building a Heathkit is fun**—Nothing quite equals the sense of achievement you receive when you successfully complete a Heathkit unit and "tune-in" for the first time.
- 6. Your Heathkit is Guaranteed**—Every Heathkit unit is guaranteed to meet advertised performance specifications . . . or your money will be cheerfully refunded.
- 7. Your Heathkit is available on Convenient Credit**—Our time payment plan makes it possible for you to order now . . . pay later.
- 8. Your Heathkit is Tops in Quality**—The very finest in electronic equipment comes to you in kit form from the Heath Company.
- 9. Heathkit Dealers can Serve you Locally**—Carefully selected Heathkit representatives are available in most localities.
- 10. Heathkit Service is Customer Service**—Our staff of technical experts is always ready to answer your questions or help you if you have any difficulty.




HEATHKIT DS-1
\$69.95



For boatsman, fisherman or skindiver a new, low-cost, depth sounder kit

Completely transistorized, this invaluable marine accessory enables you to detect submerged objects and their depth as well as to gauge the depth of the water and the nature of the bottom from 0 to 100 feet. Self-contained power supply uses 6 standard flashlight cells and 1 long-life 9 V. battery. Attractively styled, two-tone marine-green cabinet uses "tongue and groove" joints for splash protection; all metal parts treated to resist corrosion. Transducer may be mounted permanently through hull or temporarily outboard. 10 lbs.

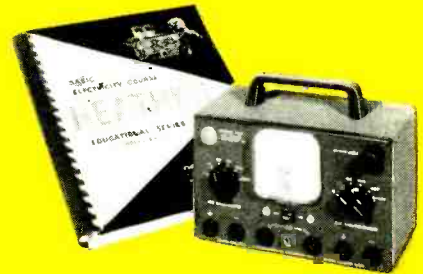

HEATHKIT EK-1 \$19.95



HEATHKIT HW-19 \$39.95
(Ten Meter)
HEATHKIT HW-29 \$39.95
(Six Meter)

A wonderful addition to the "ham shack" two new 6 and 10 meter transceiver kits


They're combination transmitters, designed for crystal control, and variable tuned receivers operating on the 6 and 10 meter amateur bands (50 to 54 mc from HW-29 and 28 to 29.7 mc for HW-19) in either fixed or mobile installations. Highly sensitive superregenerative receivers pull in signals as low as 1 microvolt; low power output is more than adequate for "local" net operation. Other features include: built-in RF trap on 10 meter version to minimize TVI; adjustable link coupling on 6 meter version; built-in amplifier metering jack and "press-to-talk" switch with "transmit" and "hold" positions. Can be used in ham shack or as compact mobile rigs. Not for Citizens Band use. 10 lbs.



HEATHKIT AD-10 \$33.95



HEATHKIT AA-20 \$34.95

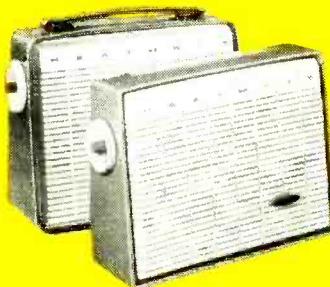

HEATHKIT XR-2L \$34.95
HEATHKIT XR-2P \$29.95

Wherever you are . . . wherever you go you can carry your music with you 6-transistor portable radio kit

Assembled in only a few hours, both of these models incorporate superior design features that will give you portable listening enjoyment day after day. Vernier tuning control gives smooth, easily-separated station tuning. Large 4" x 6" PM speaker with heavy magnet provides "big set" richness of tone. Operates on standard size "D" flashlight batteries. Six Texas Instrument transistors.

XR-2L (simulated leather and plastic) 7 lbs.
XR-2P (high-impact plastic) 6 lbs.



HEATHKIT AA-30 \$45.95

ORDERING INSTRUCTIONS

Fill out the order blank below, giving us your name and address in the space provided at right. Include charges for parcel post according to weights shown. Express orders are shipped delivery charges collect. All prices F.O.B. Benton Harbor, Mich. A 20% deposit is required on all C.O.D. orders. Prices subject to change without notice.



FREE CATALOG!

Over 150 items of stereo, marine, amateur and test equipment are illustrated and described in the complete Heathkit Catalog.



Quantity	Item	Model No.	Price

Ship via. Parcel Post Express C.O.D. Best Way

HEATH COMPANY Benton Harbor 20, Mich.

Please send my free copy of your complete catalog.


Name _____

Address _____

City _____ Zone _____ State _____

Learn more about the wonderful world of electronics! Educational kit

Teaches, as you build, the basic "yardsticks" of electronics—opens up many fascinating areas of study for youngsters and adults alike. At less than the cost of a few textbooks on the subject, here's a complete basic electricity course resulting in a volt-ohm-milliammeter of a thousand-and-one uses. See the practical results of what you are learning—the EK-1 is first in a series of educational kits prepared by Heath. 4 lbs.

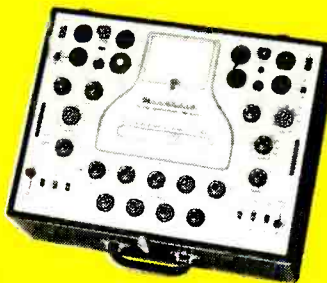

HEATHKIT TT-1

\$134.95

Outstanding professional quality . . . mutual conduction tube tester kit

An impressive list of electronic and mechanical features make this tube tester one of the finest values in the industry. Tests Gm (amplifiers) from 0-24,000 micromhos, Emission, Leakage, Grid current ($\frac{1}{4}$ microampere sensitivity), Voltage regulators (Built-in Variable DC Power Supply), low power thyatron and eye tubes. Features 300, 450 and 600 ma constant current heater supplies, Life test, Hybrid tube test, built-in switch operated calibration circuit. Large easy-to-read meter, constant tension free rolling roll chart mechanism. Includes 7 wiring harnesses. Assembly skill of technician or higher recommended. Assembly time, 40 hours average. Black leatherette case with white trim, nylon feet, removable top. (27 lbs.)

Here it is! A new manual stereo record player kit

Made by famous Garrard of England, the AD-10 is a compact 4-speed player designed to provide trouble-free performance with low rumble, flutter and wow figures. Rubber matted heavy turntable is shock-mounted, and idler wheels retract, when turned off, to prevent flat spots. Powered by line-filtered, four-pole induction motor at 16, 33 $\frac{1}{2}$, 45 and 78 rpm. Supplied with Sonotone STA4-SD ceramic stereo turnover cartridge with .7 mil diamond and 3 mil sapphire styli. 10 lbs.



HEATHKIT TCR-1

\$46.95

Start the day . . . spend the day . . . with "your cue" transistor clock-radio kit

Completely portable . . . superb modern styling in high impact plastic . . . powerful 6-transistor circuit operating from long-life mercury batteries or ordinary pen-light cells. Does everything you expect from a clock-radio—and costs you so little! Handsome cabinet measures only 3 $\frac{1}{2}$ " H. x 8" W. x 7 $\frac{1}{2}$ " D. for ease of placement anywhere in the home. Batteries not included. 5 lbs.

It's easy and economical to go stereo with these two Heathkit "compatibles"—stereo preamp kit (AA-20)

Made for each other, either of these components can be incorporated with your present stereo system. The preamplifier (AA-20) features 4 inputs in each stereo channel and gives you a choice of 6 functions. It will accommodate a magnetic phonograph (RIAA equalized), a crystal or ceramic phonograph, and 2 auxiliary sources (AM-FM tuners, TV, tape recorders, etc.), and is completely self-powered. 8 lbs.

Hi-fi rated 14/14 watt stereo power amplifier kit (AA-30)

Two 14-watt high fidelity amplifiers, one for each stereo channel, are packaged in this single, compact, handsomely styled amplifier (AA-30). Ideal for use with the AA-20, any stereo preamp or with a pair of monophonic preamps, it features individual amplifier gain controls and speaker phase reversal switch. Output terminals accommodate 4, 8 and 16 ohm speakers. 21 lbs.



HEATHKIT GC-1

\$99.95

New, all transistor "Mohican" general coverage receiver kit

The "Mohican" is the first all transistor communications-type receiver in kit form and first to use ceramic IF transformers. Covers 550 kc to 30 mc on five bands, with five separately calibrated bands to cover amateur frequencies (including 11 meter citizens band). Powered by 8 standard size "C" flashlight cells. Built-in 54" whip antenna, flywheel tuning, tuning meter, and headphone jack. Truly an outstanding receiver! Batteries not included. 20 lbs.

HEATH COMPANY Benton Harbor, Michigan

Operate your...

- tape recorder
- P. A. system
- portable TV set
- hand tools

FROM YOUR CAR, Boat or Plane!

with

ATR

INVERTERS



for changing your storage battery current to A.C. HOUSEHOLD ELECTRICITY Anywhere... in your own car!

OPERATES
PORTABLE TV SET
directly from your car!

OPERATES


- RADIOS
 - RECORD PLAYERS
 - MIXMASTERS, ETC.
- directly from your car!

MAKE YOUR CAR, BOAT OR PLANE
"A ROLLING OFFICE!"



OPERATES

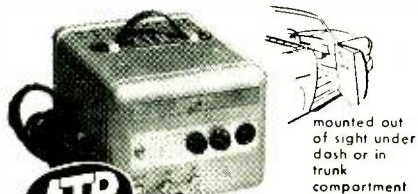- TAPE RECORDERS
 - DICTATING MACHINES
 - PUBLIC ADDRESS SYSTEMS
 - ELECTRIC SHAVERS
- directly from your car!



mounted out of sight under dash or in trunk compartment

ATR
UNIVERSAL INVERTERS

Especially designed to change 6 or 12 volt D.C. to 110 volt A.C. 60 cycles. for...

- EXECUTIVES
- POLICEMEN
- SALESMEN
- REPORTERS
- OUTDOOR MEN
- FIREMEN
- PUBLIC OFFICIALS

MODELS 6U-RHG (6 volts) 125 to 150 watts. Shipping weight 27 lbs. List price... \$99.50

DEALER NET PRICE... \$66.34

12U-RHG (12 volts) 150 to 175 watts. Shipping weight 27 lbs. List price... \$99.50

DEALER NET PRICE... \$66.34

Write for literature on other Sizes and Models of ATR INVERTERS, priced as low as \$11.95 list.


SEE YOUR JOBBER OR WRITE FACTORY

- ✓ NEW Models ✓ NEW DESIGNS ✓ NEW LITERATURE
- "A" Battery Eliminators • DC-AC Inverters • Auto Radio Vibrators

ATR

AMERICAN TELEVISION & RADIO CO.
Quality Products Since 1931
SAINT PAUL 1, MINNESOTA, U. S. A.

TEST INSTRUMENTS

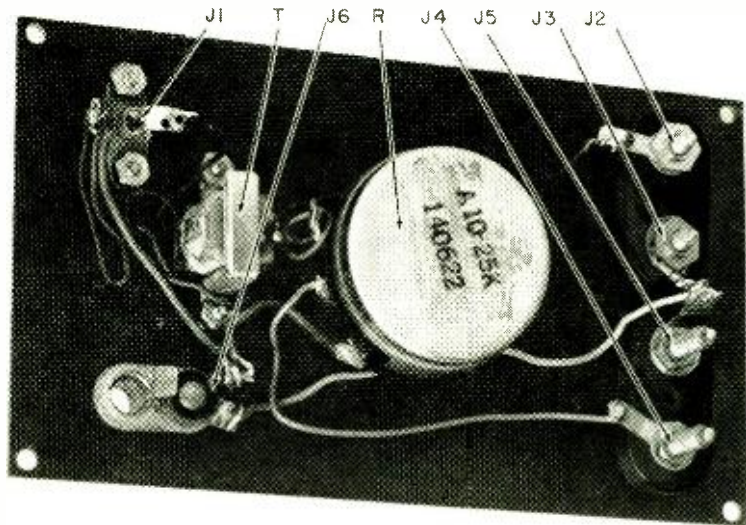

The limited number of parts makes construction fast and simple

(Continued from page 66)
suitable. (The difference impedance-wise has negligible effect.) For even greater accuracy, one of the many surplus shielded transformers could be used.

Potentiometer R is a 4-watt unit that has a linear taper. It is chosen not for its power-handling capacity but because it has a relatively large diameter and can provide higher accuracy. As shown in the photo, it is controlled by a large arrow knob moving over a hand-prepared calibration scale. For convenience, a headphone set is used to detect balance. A signal of approximately 850 cycles has been found suitable. The audio input amplitude may be between 5 and 10 volts.

From Fig. 2 it is obvious that C₁ must be equal to or smaller than C₂ to obtain a null. When R's arm is at the top, equal and opposite voltages are being applied to both capacitors, and null is obtained when they are equal. At any other setting, R reduces the voltage and requires a smaller C₁ to produce a null. For example, at R's mid-scale, balance requires that C₁ be one-half of C₂, and so on. This shows that R may be calibrated in terms of angle rotation and the divisions should be uniform. For maximum accuracy, however, it is better to calibrate directly from known capacitors.

Obtain four capacitors: 100μf (two of them), 25 μf and 50 μf. Use a 100-μf as the standard, and the second 100-μf as the unknown. Set R to balance and mark off the null position as 100. For a check, transpose the capacitors and see if the same point is determined at balance. If not, divide the difference and mark off a point midway between the two null positions. Now with the 100-μf as C₁, connect the 50-μf at C₂, balance and mark off 50 at the appropriate point. With 25 μf at C₁, mark the point 25.

It pays to use good standards for this instrument. Centralab type TCZ is excellent. They are 2% tolerance units with zero temperature coefficient, avail-

able in values from 12 to 100 μf.

After determining the major divisions (0, 25, 50, 75, 100), fill in with smaller, equally spaced markings. Five small divisions for each major one should be adequate and will enable measurements *directly* in multiples of 5 μf. Because the variation is uniform, you can easily interpolate between the smaller divisions.

An obvious method of extending range is to use different standard values. If you use .001 μf, you can measure unknowns 10 times *greater* than your original calibration. On the other hand, with a 10-μf standard you can measure 10 times *smaller*.

A different method is used here to extend measurements above 100 μf. Transpose the capacitors by connecting the standard at C₁ and the unknown at C₂. Now you can measure conveniently from 100 μf (with a 100-μf standard) up to .001 μf. The new calibration is found by calculating from 10,000 where

D

D is the original calibration. Thus, 400 μf on the high range corresponds to the 25-μf point on the low range, etc. The list shows corresponding points.

Low Range	High Range
10	.001
20	500
25	400
30	333
35	286
40	250
45	222
50	200
55	182
60	165
65	154
70	143
75	133
80	125
85	118
90	111
100	100


Note that the high range is not a linear one, so be careful when interpolating between marked divisions.

With both ranges on a single scale you have a wide-band, accurate bridge requiring but a single standard. END

TEST INSTRUMENTS

HANDY CABLE CHECKER

BECAUSE of the large number of cables used with our PA equipment, we found it convenient to construct a simple cable checker as an aid to periodic cable testing. The cable connectors are plugged into the matching connectors on the checker and the rotary switch turned through its various positions while observing an ohmmeter which serves as a short-open indicator. Although the connectors on our equipment have been standardized to suit our own requirements (P1, P4, J1, J3—Amph-

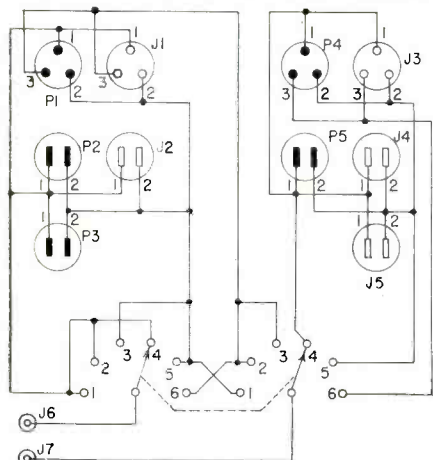

nol mike connectors; P2, P5, J2, J4—Jones cable connectors; P3, J5—ac power connectors), other types may be accommodated by wiring additional connectors in parallel. Ohmmeter indications for the six switch positions are:

Switch Position	Ohmmeter Indication
1	Infinite, or leads 1 and 2 are shorted
2	Infinite, or leads 1 and 3 are shorted
3	Infinite, or leads 2 and 3 are shorted
4	Finite, or lead 1 is open
5	Finite, or lead 2 is open
6	Finite, or lead 3 is open

—Warren J. Smith



"I'm almost finished with your set, m'am."

MARCH, 1960

Now Completely SELF-CONTAINED

For Testing & Rejuvenating
BLACK AND WHITE and COLOR including 110° TUBES

NEW CRT 440



TESTS AND REJUVENATES

all black & white and color picture tubes at correct filament voltage from 1 to 12 V.

TESTS AND REJUVENATES

110° tubes with 2.34, 2.68, 6.3 and 8.4 volt filaments.

TESTS AND REJUVENATES

color picture tubes. Checks each color gun separately same as black & white tubes.

Used by Thousands of Professional Servicemen
MAKES NEW PICTURE TUBE SALES EASIER

Gives you more value than ever—all-in-one. Quickly checks and corrects most TV picture tube troubles in a few minutes right in the home without removing tube from set. Gives new useful life to weak or inoperative tubes. Checks leakage. Restores emission and brightness. Repairs inter-element shorts and open circuits. Life test checks gas content and predicts remaining useful life of picture tube. Completely self-contained in leatherette-covered carrying case. Net, \$69.50

ACCESSORIES for USE ONLY with FORMER B&K Models 400 and 350 CRT



Model C40 Adapter. For use only with all previous B&K Model 400 and 350 CRT's. Tests and rejuvenates TV color picture tubes and 6.3 volt 110° picture tubes. Net, \$9.95



Model CR48 Adapter. For use only with all previous B&K Model 400 and 350 CRT's. Tests and rejuvenates 110° picture tubes with 2.34, 2.68, and 8.4 volt filaments. Net, \$4.95



See your B&K Distributor
or Send now for Bulletin ST24-E

B & K MANUFACTURING CO.
3726 N. Southport Ave. • Chicago 13, Illinois
Canada: Atlas Radio Corp., 50 Wingold, Toronto 14, Ont.
Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.

NEW!



RESIST-O-RACK

FREE! with any 4
Handy-Pak Carbon Resistor
Assortments • 77 Values

\$55⁴⁴ to \$110⁸⁸ Dealer Net

All-metal • Can also be wall mounted



Order from
your IRC
Distributor

INTERNATIONAL RESISTANCE COMPANY
DISTRIBUTOR SALES DIVISION
414 N. 13th STREET • PHILADELPHIA 8, PA.

Electronic Flare Flashes Warning Signals

By EDWIN N. KAUFMAN *


At one time or another we have all seen the flashing lights used on the tops of street barricades guarding excavations or detours. Many times I have been asked about the possibility of packaging this type of unit for automobile use as a portable electronic flare. It would be used as a warning signal when changing a tire at night, etc.

For some time my answer to such questions was "much too unreliable," as the majority of these lamps are electromechanically operated. Transistors have shed new light on the scene.

Types of flashers


Today, there are two ways to use transistors to produce light flashes. Both use a metronome type circuit in which one transistor pulses a second which is biased to cutoff. One such circuit uses two germanium transistors (one n-p-n and one p-n-p) with a small tungsten lamp in the collector lead as the light source. This setup requires either a 3- or 6-volt battery. The circuit offers simplicity, few parts and good battery life. However, a study of tungsten lamps indicates that on-off cycling is a decided factor leading to short and unreliable bulb life. For commercial uses where many multiple units are installed on a barricade, this

* Chief engineer, Rho Engineering Co.

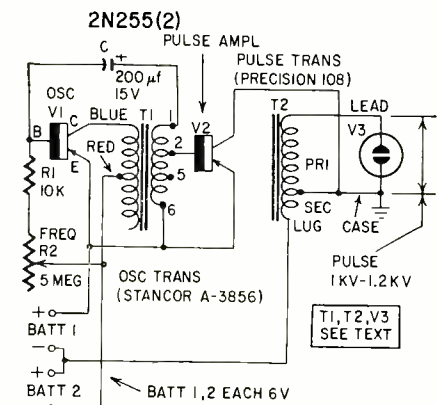

- R1—10,000 ohms, 1/2 watt
- R2—pot, 5 megohms, linear taper
- C—200 μ f, 15 volts, electrolytic
- BATT 1, 2—6 volts (RCA VS009 or equivalent)
- T1—universal output transformer, single or push-pull plates (4,000-14,000 ohms) to voice coil (Stancor A-3856 or equivalent)
- T2—see text (Precision Transformer model 108, Stancor P-4026, or P-8190 or equivalent)
- V1, 2—2N255
- V3—gas tube (see text)
- Chassis board
- Reflector
- Miscellaneous hardware

Circuit of 2-transistor flare.

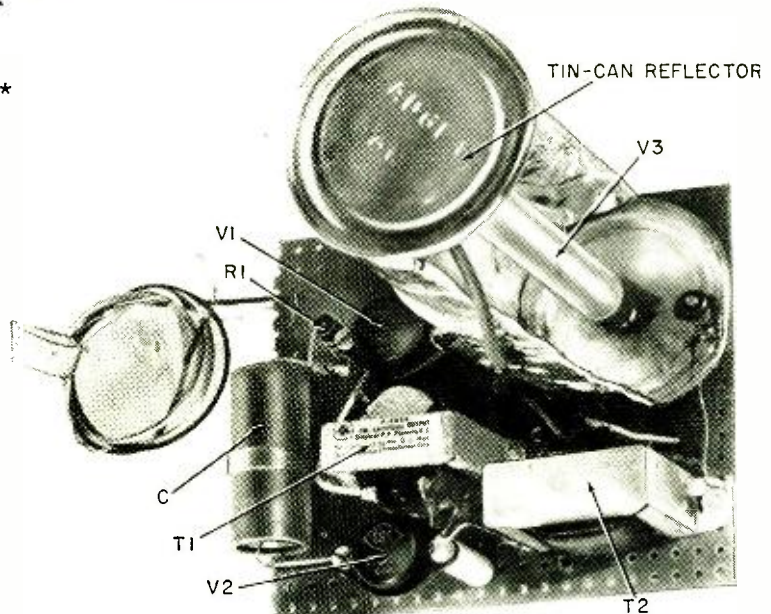

BENCH



TESTED

Checked out by one of the magazine's staff, this little unit blinked regularly and apparently reliably during the period it was watched. It was clearly visible about two blocks away. This would make it useful for most warning signals, but might not be adequate for "changing a tire at night" as the author suggests, on a high-speed highway, especially if confused with the glare of opposing headlights. For such purposes the conventional red flare is still supreme.

may not be serious. But for reliable operation it is not acceptable.

The second and most reliable method uses a gas tube for the light flash. Again a metronome type circuit is used (see diagram). Transistor V1 generates pulses over a range of about 60 to 120 a minute. The optimum pulse rate is 90 flashes per minute. The unit shown in the photos is set at this pulse rate by using a single fixed resistor in place of the series R1-R2 combination. Transformer T1 provides a low-impedance path between V2's base and emitter and supplies low-voltage high-current pulses. The circuit operates from 3 to 6 months on one set of batteries.

Capacitor C's value is not critical and can be varied over a wide range—100-500 μ f—and remain in a usable flashing range. Two low-cost 2N255 power transistors are used. No heat sink is needed. A lug is installed under the head of the screw holding the transistor down and is used as the collector connection. Connections to the base and emitter are soldered directly to the ends of the pins.

Almost any output transformer can be used for T1. Select the output impedance tap that gives the best performance. Again, this is not critical.

The most critical components in the circuit are output transformer T2 and the gas tube. I used the transformer

from a Precision Radiation Co. model 108 Geiger counter (model 108 transformer). This unit can be had from the firm, 4223 W. Jefferson Blvd., Los Angeles, Calif., as long as its supply lasts, or the units in the parts list can be substituted. Connect the substitute units—they are filament transformers—as autotransformers and use just like the 108.

The flash tube

For the gas tube you can use a short piece (6-8 inches) of neon tubing, made up by a local neon sign shop (preferably neon tubing), or, much cheaper, a 4- or 6-watt fluorescent lamp.

For best results use a reflector behind the lamp. You can make one from a tin can lined with aluminum foil. By using colored cellophane around the lamp, either red or amber flashes can be obtained. During the day, light output will seem rather dismal, but at night it is more than ample.

The major source of trouble with this type unit is pulse-transformer breakdown. The high-voltage spikes from the transformer reach much higher values than the actual firing voltage of the gas tube. If transformer insulation is at all weak, it will break down. If this happens, get a transformer with better insulation or a gas tube with a lower firing voltage. END




Winegard's

"K" SERIES, NEW, PLAIN-ALUMINUM ANTENNA LINE

Now, Winegard introduces a complete new series of plain aluminum antennas in addition to Winegard's incomparable line of GOLD ANODIZED TV and FM antennas. Winegard "K" Series antennas are priced so you can meet any competitive situation . . . at the same time, you can give your customers

a much better antenna for the money.

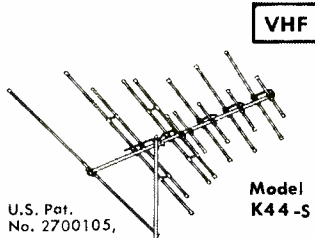
Compare "K" Series antennas with plain aluminum models offered by others. See for yourself how *much more* you get from Winegard. You'll find a "K" Series model for every reception requirement. Ask your Winegard distributor or send in the coupon below.



U.S. Pat. No. 2700105, Model K44-S

POWERCEPTOR

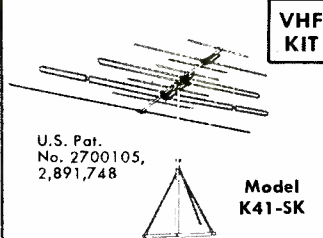
Four 9 and 11-element models with fold-out driven elements. Electro-Lens director system. All-channels 2-13. List \$19.50 and \$21.50.



U.S. Pat. No. 2700105, 2,891,748 Model K41-SK

SUPER POWERBEAM

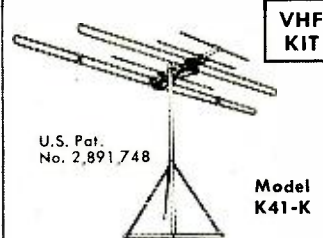
Three complete fringe area kits. Patented tripod roof mount, Chimney mount, Mast and guy wire mount. All channels 2-13. List: \$26.20, \$29.35, \$36.70.



U.S. Pat. No. 2,891,748 Model K41-K

POWERBEAM

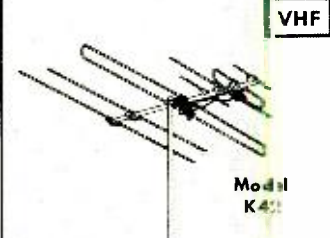
Complete kit including patented universal tripod roof mount. Excellent for primary and near-fringe areas. All ch. 2-13. List, \$14.95.



Model K41-K

POWER PIX

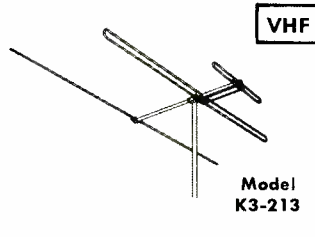
Ideal replacement for old style "Con Yagis". Full-power gain on all channels 2-13. Stacking increases power 34%. List, \$13.00.



Model K3-213

INLINE

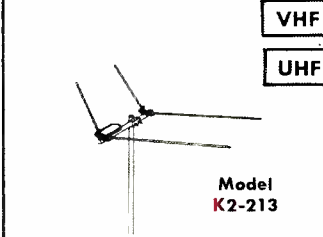
Well-built standard inline for all (VHF) channel coverage in primary areas. Dual moisture-barrier insulators. List, \$6.00.



Model K2-213

VEE

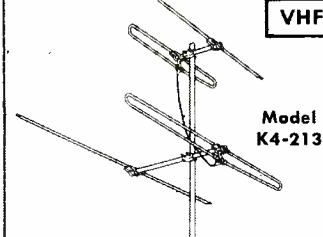
Improved version of the popular "Vee". Reflector has inductance loading coil for more uniform gain and frequency response. List, \$5.55.



Model K4-213

HI-LO

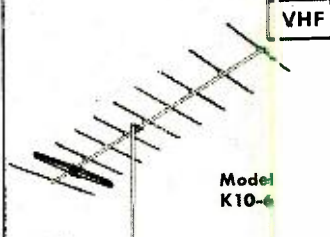
For use in city and suburban areas. List, \$7.90. HI only, List \$2.60. LO only, List \$5.05. Includes one-piece, wrap-around mast clamp.



Model K10-6

CUT-TO-CHANNEL

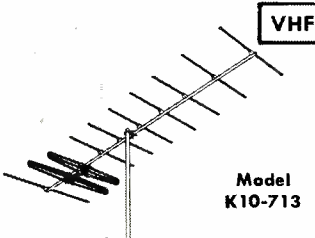
Complete series of wide-spaced 5-element and 10-element cut-to-channel yagis. Center bar of driven element snaps out for stacking. List, \$4.90 up.



Model K10-713

BROAD-BAND

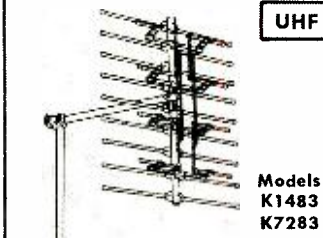
Complete series of wide-spaced 5-element and 10-element broad-band yagis. Center bars of driven elements snap out for stacking. List, \$7.20 up.



Models K1483 K7283

UHF COLINEAR

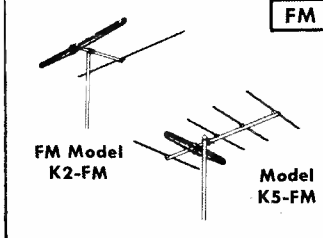High gain antenna with exclusive offset mount. Stacks horizontally for greatest efficiency. Regular UHF or Translator UHF model, List \$9.80.



FM Model K2-FM

Model K5-FM

FM

Two-element and 5-element wide-spaced FM yagis for improved reception on 88-108 mc. Directive, high-gain design. K2-FM, List \$5.05. K5-FM, List \$13.80.

GET THE DETAILS

The Winegard Company
3013-3 Scotten Blvd.
Burlington, Iowa

Please send technical bulletins on the following "K" Series models:

Name _____

Address _____

What's With CHARACTERISTIC IMPEDANCE?

By ROBERT G. MIDDLETON

CHARACTERISTIC impedance sounds like one of the higher confusions, but it is really very simple. The only reason it seems difficult is that it has been explained mostly by college professors who are trying to show how smart they are. You know, BS, followed by MS and then by PhD. Everybody knows about BS, etc. But take a look at Fig. 1.

By forming a chain of resistors and checking with an ohmmeter as we make the chain longer and longer, we find that the input resistance is coming to a *limiting value of 300 ohms*.

And, if we do as shown in Fig. 2 and terminate *any* length of chain with a 300-ohm resistor, the input resistance is *always* 300 ohms.

But you better buy the resistors wholesale. That way, they are cheap at half the price.

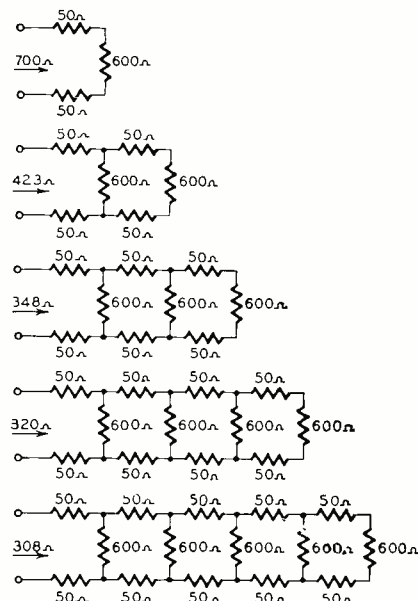


Fig. 1—Simple experiment with handful of resistors and an ohmmeter proves a resistor chain rapidly approaches a limiting or constant value of input resistance.

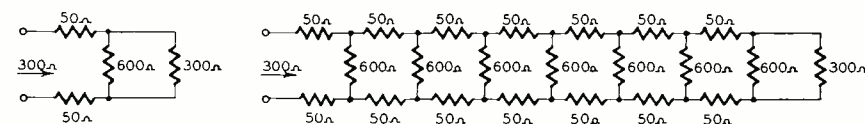


Fig. 2—Take any number of sections in a chain, and terminate them with the characteristic resistance, and the input resistance is the same.

Sometimes it's difficult for us to look at the chains in Fig. 1 and believe that the input resistance is settling down to 300 ohms. We seem to feel that, if we go on adding shunt resistors, the input resistance must keep going lower and lower. *But it doesn't*. It settles down to a limiting value, and this is the *characteristic resistance* of the chain—300 ohms, no more, no less.

A settled-down chain is pretty long, like a giraffe's neck.

You remember about the local yokel who went to the circus, took a look at a giraffe and said, "There ain't no such animal."

Hold your hats, boys—this one almost nobody is going to believe.

Enter Professor Egghead

Let's make like Professor Egghead, BS, MS, PhD. (MS means more of the same.)

Eggy says that we ought to do it the hard way, using the quadratic equation. That way, almost *nobody* knows what we are talking about, and that's good according to Eggy. Oh yes, PhD means Piled high and Deep.

Well, anyhow, according to Eggy, you take a section of the resistor chain and terminate it with R, as shown in Fig. 3. We don't know what R is, but we will say it is the characteristic resistance of the chain. So, that would make the input resistance of the chain equal to R also.

All we got to do now is find R! To do it the hard way, we have to use the quadratic formula that says $Y = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$. Who said where's the DDT?

So when we put in the 50's and the 600's ($R = 50 + 50 + \frac{600R}{600 + R}$) and solve the dad-blamed equation, we come out all right—we get 300 ohms, just as we would if we had good sense and used an ohmmeter.

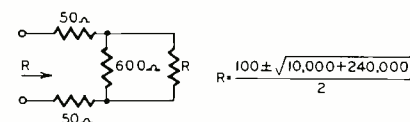


Fig. 3—Eggy says to do it the hard way, like this. What we find in the quadratic equation shouldn't happen to a dog, but it does.

But not so fast, Eggy. You have thrown out the baby with the bathwater. Honest.

Here's how you done it. That quadratic formula gave us *two* answers. It gave us a +300 ohms, and a -200 ohms. We threw out the -200 ohms because that's the sloppy way we do things in the ivory tower.

The quadratic formula was trying to tell us something, and we wouldn't listen.

Bend an ear. If we terminate our resistor chain with -200 ohms, it works out. The input resistance is -200 ohms! The solution is a *negative* resistance. What is a negative resistance? Well, it is the resistance that you have in a dynatron or transitron or electric arc. It is as real as positive resistance that we have in composition resistors, lamp filaments or what have you.

So we come to the "Ain't no such animal" again, only this time its neck is out a mile. A resistor chain can be terminated with proper values of *either* positive or negative resistance, and the input resistance will be the same as the terminating resistance.

Believe it or not, we can make up a resistor chain a mile long and, if we terminate the chain with its negative characteristic resistance, that negative resistance will be reflected back, section by section, the whole mile, to make the input resistance the same value of negative resistance. Ho hum.

Why don't you tell us these things, Eggy?

Going back to Fig. 1, we don't have to use 50- and 600-ohm resistors. These happen to give us a characteristic resistance of 300 ohms.

But actually, we can select *any* values we want to, and we will always

ELECTRONICS

have a characteristic resistance. It won't be 300 ohms. It might be 75 or 600 ohms. But *any* resistor chain like Fig. 1 always has a characteristic resistance.

In fact, it always has *two* characteristic resistances. It will have a positive characteristic resistance and a negative characteristic resistance.

It's just like the definition of a filter—"a filter is any combination of coils and capacitors." I like definitions of this sort, even if Eggy don't. They help to make life more simple. But they don't cut much ice in the ivory tower, seems like.

Coils and capacitors

Let's fiddle around with coils and capacitors a little, instead of resistors.

If we make up a chain of 13- μmf capacitors and 1.17- μh coils, we have the same thing as in Fig. 1, only

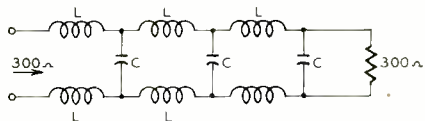


Fig. 1—Any chain of L and C has some characteristic impedance. When $C = 13\text{-}\mu\text{mf}$ per foot and $L = 1.17\text{-}\mu\text{h}$ per foot, characteristic line impedance is 300 ohms.

different. But it is the same difference. If we terminate the chain with a 300-ohm resistor, an ohmmeter shows 300 ohms at the input of the line.

And now, we can use either an ac or dc ohmmeter. And the input resistance is still 300 ohms for ac or for dc.

Take a couple of parallel wires with a wire diameter to give 1.17 μh per foot, and space them to give a capacitance of 13 μmf per foot. We will then

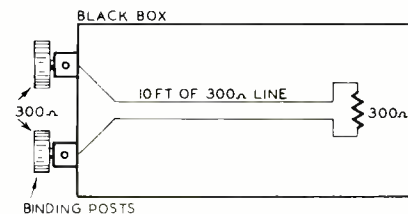


Fig. 5—If 10 feet of 300-ohm line is in a black box and terminated with 300-ohm resistor, there is no way of telling the box contains anything but a 300-ohm resistor.

find a characteristic resistance of 300 ohms for this line.

Take the deal in Fig. 4. All the L and all the C cancel out at *all* frequencies. The same thing on a 300-ohm ribbon line. If you terminate the line with a 300-ohm resistor, you wouldn't know that there was any inductance or capacitance.

To show what we mean, look at Fig. 5. If we have 10 feet (or 100 feet) of terminated 300-ohm line in a black box, no tests at the terminals are possible which will show anything but a 300-ohm resistor in the box.

In other words, the input impedance of the line is purely resistive.

Time for a short beer.

END


MARCH, 1960

you get so much more in

KNIGHT[®]


A PRODUCT OF ALLIED RADIO

hi-fi speakers

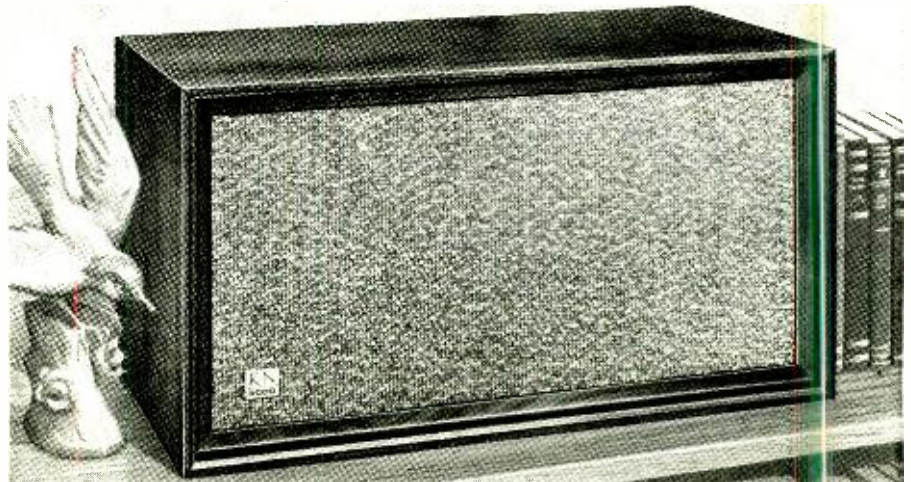

high-compliance speaker system with two built-in Arthur Janszen electrostatic tweeters

Allied's own hi-fi speaker value extraordinary. Features patented Arthur Janszen design dual electrostatic tweeters right in the cabinet—no clumsy "add-ons" needed. High compliance woofer is all-new controlled-mass design. The results are phenomenal: Distortion is held to a mere 0.5% at full 50 watts input. Response is clean and level, 30-25,000 cps. Meets the most critical professional requirements—transparent high frequencies beyond audible limits—smooth, honest bass. (Ask for impartial lab performance report.) Impedance, 8 ohms. The attractive, acoustically-sealed enclosure is hand-finished on four sides; 4 x 26½ x 13"; available in mahogany, limed oak or walnut. U.L. Approved. Unconditionally guaranteed for one full year. Sugg. wt., 50 lbs... **Only \$129.50. \$5 down.**

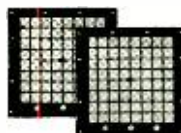


Built-In Arthur Janszen design patented dual electrostatic radiators—rated the best again and again. Built-in power supply; certified response to beyond 25,000 cps.

New High-Compliance 12" woofer, featuring weighted cone in solid cast-aluminum alloy frame... provides extremely solid, very low bass performance.



15-Day Trial & Moneyback Guarantee: Try the KN-3000 Speaker System under your own operating conditions for 15 days; if you are not completely satisfied, your purchase price will be refunded by Allied upon return of equipment.

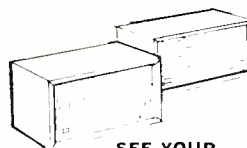New Easy Terms: **Only \$5 down** (or less) on orders up to \$200. Up to 24 months to pay



SEE YOUR FREE 1960 ALLIED CATALOG

for the largest selection of money-saving hi-fi speakers and speaker systems (true high compliance shelf speaker systems begin as low as \$59.95). See hundreds of top buys on everything in Hi-Fi in the 1960 Allied Catalog. Write for your FREE copy today.

order from

ALLIED RADIO

ALLIED RADIO, Dept. 201-C
100 N. Western Ave., Chicago 80, Ill.

Ship me _____ KN-3000 Speaker System(s).
 Mahog. Oak. Wal.
\$ _____ encl. (Shipped F.O.B. Chicago)


SEND FREE 1960 CATALOG. I am interested in saving money on everything in Hi-Fi.

Send impartial Lab Report on KN-3000 Speaker.

Name _____

Address _____

City _____ Zone _____ State _____

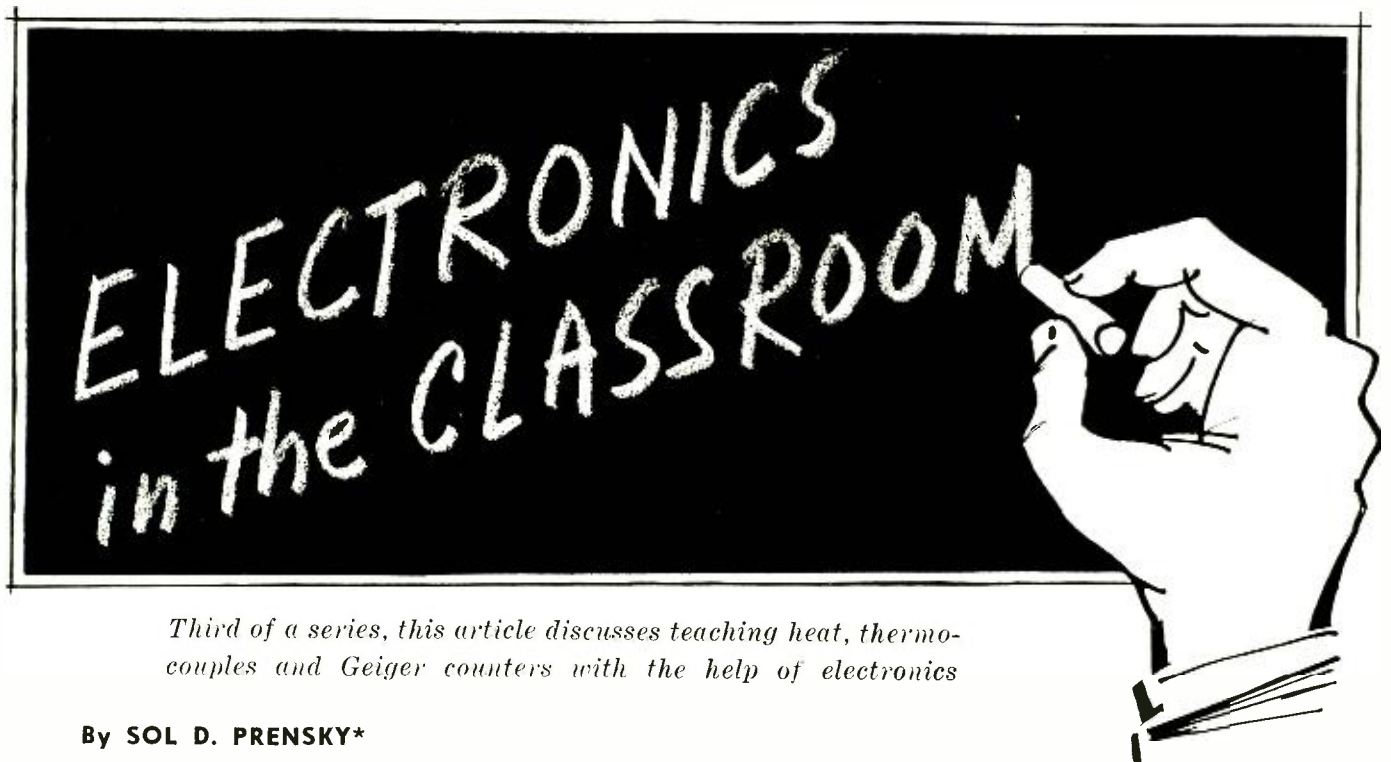

Third of a series, this article discusses teaching heat, thermocouples and Geiger counters with the help of electronics

By SOL D. PRENSKY*

THE first two articles in this series (February, 1959, page 46 and May, 1959, page 44) clearly showed how modern electronic equipment can be used in the science classroom to provide clear and interesting demonstrations of physical properties.

The principles of heat can also be demonstrated in an equally interesting fashion.

Electricity from heat

Thermo-elements for converting heat into electricity have been very much in the news—the possibility of obtaining usable quantities of electricity directly from the heat of a nuclear reactor and the remote indication of critical temperatures in space vehicles have been widely publicized.

Both functions are possible because an emf is produced by raising the temperature of a junction of two dissimilar metals. Although this effect was discovered by Seebeck more than 100 years ago—in 1826—recent research into solid-state physics has uncovered exciting new possibilities for much improved thermo-electric materials. For example, a report from Dr. Raymond Bowers of the Solid-State Physics Dept. of the Westinghouse Research Laboratories indicates developments in thermo-elements that point toward sizable amounts of electrical power produced from very-high-temperature sources.¹ There is also a real possibility of utilizing the reverse action (the Peltier effect, 1834) where cooling is produced by forcing an electric current through a similar thermo-electric junction in the reverse direction.

Leaving the newer possibilities (many of which are classified as to their details) for future development, we will concentrate on the conventional thermo-elements presently available to illustrate the basic thermo-electric property of producing a measurable electrical output by applying heat. It is important at the outset to realize that a single thermocouple produces very little electrical power when heated by a laboratory burner, so even the detection of this electrical output on an ordinary meter is not very easy to show.

Taking an ordinary thermocouple (iron-constantan) as an example, the generated voltage may be expected to be in the order of around $50 \mu\text{v}$ per degree Centigrade, and is fairly linear with temperature rise. So for a rise of 100°C , an output voltage of around 5 mv may be expected. This small output is very difficult to detect with the general-purpose type of meter ordinarily found in the laboratory. On the familiar 0-1-ma meter range for example, the nominal short-circuit current reading at 100°C would be limited by the internal resistance of the meter (around 100 ohms), and therefore would show an approximate deflection of only 5 mv divided by 100 ohms, or .05 ma, which would be barely readable. It would not help to try switching to a more sensitive current range since the meter's internal resistance would increase correspondingly and the meter deflection would still be disappointingly small.

The difficulty in obtaining a direct reading of thermocouple output on an ordinary current-operated meter

(whether ammeter or voltmeter) can be overcome by using more sensitive indicators (electronic galvanometers, millivoltmeters or null-reading potentiometers) or a combination of thermocouples to get a larger electrical output. The latter method will be used here in the form of a commercial thermopile, which consists of a large number of individual thermocouples in series.

The thermopile used in the first demonstration (Minneapolis-Honeywell Powerpile model CS 82) is particularly effective. When heated by a flame, it can supply up to about 500 mv (0.5 volt) on open circuit, and around 100 ma on short circuit. The current shown on a milliammeter in series with it will, of course, be decreased by the internal resistance of the indicating meter, but will still be more than enough to produce a good deflection on the demonstration meter. The same thermopile can also be employed as the sole source of energy for a transistor amplifier circuit, as is shown in a subsequent demonstration.

The simple arrangement for measuring the current output of the thermopile (as would be done in temperature measurement by pyrometer) is shown in Fig. 1. The source of heat can be any flame (even from a match) but preferably from a Bunsen or alcohol burner. The large-size demonstration multimeter (Hickok 209A) should be set on its 120-ma range, and a substantial deflection should be obtained after the thermopile has been heated for 2 or 3 minutes. (Note that the flame should be directed at the edge of thermopile opposite the one where the leads come out.) With a suitable calibrating source,

(Continued on page 80)

*Prof. E. E. Dept., Fairleigh Dickinson University, Teaneck, N.J.

¹News Briefs, RADIO-ELECTRONICS, June, 1959, page 6.

EXCITING NEWS FROM RCA!

Announcing a new plan
to give your store

THE SUCCESSFUL LOOK

FIND OUT
HOW THIS PLAN CAN HELP YOU:

- Attract new customers
- Display and merchandise your products and service more effectively
- Utilize your present floor space to far better advantage
- Increase the efficiency of your service operation

SEE NEXT PAGE FOR
IMPORTANT DETAILS.

Your Store...Key to Successful Sales

with the new **RCA**

STORE IMPROVEMENT PLAN

Your skill, experience and integrity are the basic qualities that help you sell your service to the public. The appearance of your store can impress them with these facts—invite them inside to call on you with confidence.

The components shown here—and many more—are all available from your Authorized RCA Tube Distributor under the new RCA Store Improvement Plan. With minimum effort on your part, they will help you give your store *the successful look* inside and out. *No expensive store renovation is required.* No fancy, impractical blueprints are offered. Instead you are provided with carefully thought-out components that increase the business potential of any shop—big or small, old or new.

THE SUCCESSFUL LOOK—OUTSIDE

STORE FRONT



PROFESSIONALLY INSTALLED
WINDOW DISPLAYS—
CHANGED EVERY SEASON

With this plan, your store window becomes a strong invitation to new customers. It will be decorated and fitted with attractive seasonal displays—prepared by RCA—without any fuss or bother on your part.



RCA ILLUMINATED WINDOW VALANCES—ALSO USED AS
IN-STORE MODULAR DISPLAY PANELS

Here's a brand new idea that can be used to decorate your store window—or the interior of your shop as shown in the "Sales Area" photograph on opposite page. A choice of two- or four-foot lithographed panels, in gold-finished satin steel, gives you complete flexibility in designing your own customized illuminated window valance. Complete with hanging hardware and fluorescent lighting.




A good looking store front is your first opportunity to convert a passerby to a customer. The RCA Store Improvement Program offers you the elements to make your store front a working partner in your business.

Talk to your Authorized RCA Tube Distributor about this exciting plan right away. Ask him for your copy of RCA's new Store Improvement Guide (4F257), with a complete list of the components available and the order forms to secure them. Find out how easily and quickly you can add those few extra touches to your store to give it that Successful Look for 1960.

SALES AREA

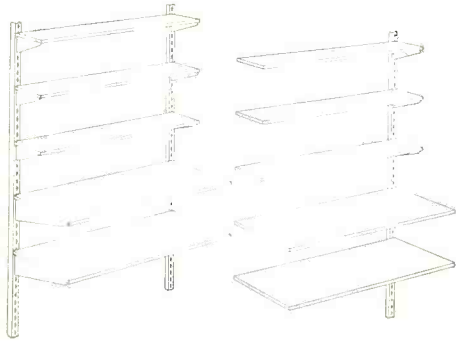The interior of your shop should be an important sales aid. Here, good first impressions can be reinforced, to make it easier for you to sell your products and services.



RCA DISPLAY AND STORAGE SHELVING UNITS

Attractive, sturdy shelving helps you display your merchandise more effectively for added sales. The RCA Plan offers basic four-foot shelving units, with add-on units to fit every need. Units may be set up in a variety of arrangements—and are easily disassembled and re-arranged.



THE SUCCESSFUL LOOK—INSIDE

SERVICE AREA

An efficient service area, providing faster, better organized work flow, is an important key to profits.



SHOP BENCH UNITS

These sturdy benches mount on shelving units to provide additional storage and work space, efficient work flow, better use of floor space. They save you time and money.

ADDITIONAL SALES AIDS— TO HELP BRIGHTEN YOUR PROFIT PICTURE

Eye catching sales accessories can draw attention to the services you offer. Sales-boosting accessories include illuminated clocks, signs, product display units, door bars, streamers, decals, service auto lights—even uniforms.



RADIO CORPORATION OF AMERICA

Electron Tube Division

Harrison, N. J.

TUBE PROBLEM:

An amplifier manufacturer was plagued by noise, microphonics and hum that developed in the high gain stages of his amplifiers. Sonotone engineers were consulted on the problem.

SONOTONE SOLVES IT:

Sonotone engineers discovered that they could correct *all three* complaints by redesigning just *one* tube.

RESULTS:

The heater element was changed to a coil heater, eliminating the hum. And rigid controls on the mount structure and processing reduced microphonics and noise. This resulted in the Sonotone reliable type 7025. It's now available for initial equipment and replacement purposes.

Let Sonotone help solve *your* tube problem, too.

Sonotone SOLE

Electronic Applications Division, Dept. T2-30

ELMSFORD, NEW YORK

Leading makers of fine ceramic cartridges, speakers, microphones, tape heads, electron tubes.

In Canada, contact Atlas Radio Corp., Ltd., Toronto

ELECTRONICS

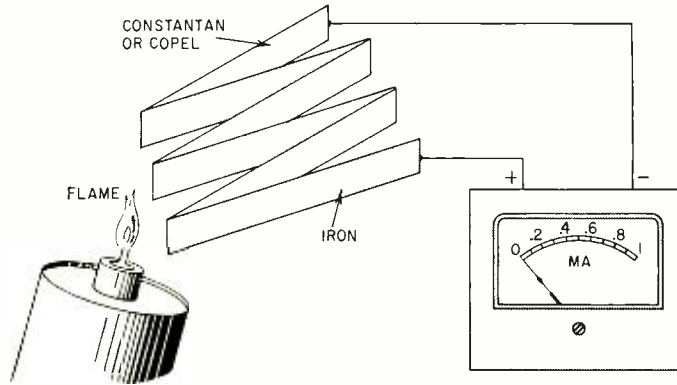


Fig. 1—Measuring the current output of thermocouples connected in series to form a thermopile.

(Continued from page 76)

the meter could then be marked off as a remote temperature indicator.

Heat-powered electrical devices

The fascinating possibilities that are opening up as a result of advances in thermo-electric conversion can be demonstrated with the same thermopile. Although the newer arrangements for high-efficiency conversion (such as cesium-plasma couples) are still in the experimental stage, the thermo-elements that are commercially available can power flea-power circuits, which the undemanding transistor has made possible. Miniature hearing aids, audio oscillators and radio receivers using headphones are a few examples.

The circuit used here is that of a simple transistor audio oscillator which will produce an audible tone from a loudspeaker, using either an alcohol flame or cigarette lighter as the only power source.

For classroom demonstration, we want the sound to come from a loudspeaker rather than headphones, and this arrangement using a Bunsen burner or alcohol lamp is discussed first. (The do-it-yourself version using

a match or cigarette lighter is covered later.) The overall appearance of the sound-from-heat class demonstration unit is shown in Fig. 2, and the circuit of the transistor oscillator in Fig. 3. A medium-power 2N186-A transistor is connected in a positive-feedback circuit. Variations in collector current flowing in the upper half of the transformer primary are fed back to the base through the lower half of the primary winding, supplying positive feedback for oscillation. Base bias current is regulated by the 10,000-ohm variable resistance of R2 in series with fixed resistor R1, and bypassed for ac by capacitor C1. The resulting audio oscillations are fed to the 45-ohm speaker by the voice-coil winding. Using the 45-ohm intercom type speaker requires a smaller stepdown ratio in the transformer, thus conserving as much as possible of the small voltage (and relatively large current) delivered by the thermopile. The setup will also work with a conventional 4-ohm speaker and output transformer if the primary's dc resistance is kept low. The pitch of the resulting tone is initially set by C2's value, and can be varied slightly with R2. No switch is used; the unit

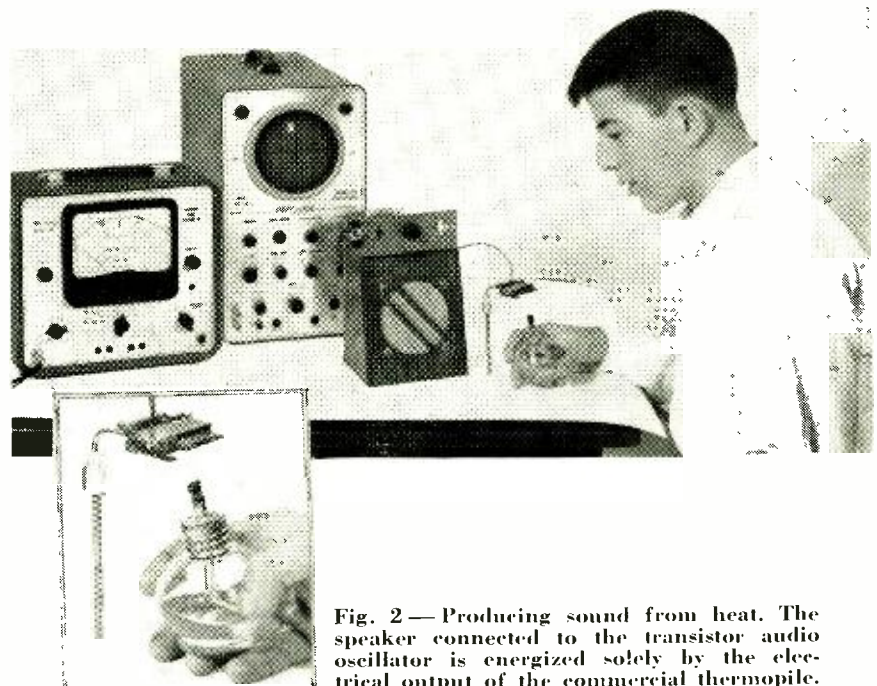


Fig. 2—Producing sound from heat. The speaker connected to the transistor audio oscillator is energized solely by the electrical output of the commercial thermopile.

ELECTRONICS

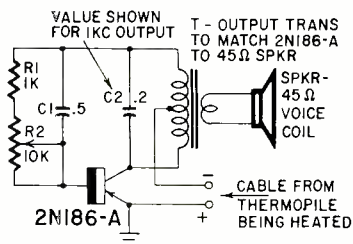


Fig. 3—Schematic of transistor audio oscillator that can be powered by thermopile's output.

simply starts up when the business end of the thermopile has become hot enough (in 2 or 3 minutes), and stops by itself when the thermopile cools off. The thermopile is commercially available as a pilot control for gas burners (Minneapolis-Honeywell Powerpile CS82A1X-32X15, list price \$9.30).

The do-it-yourselfer can make his own thermocouples and thermopiles from the raw materials in the form of metal strips or ribbons. He can then build electronic devices that can be powered by these home-built thermoelements. The metallic raw material can be purchased from scientific supply houses, generally in spools. For kit builders (some call themselves thermo-electronicists), a complete line of parts, kits and literature is available for making thermal batteries of the "zig-zag" and disc types, some having a 2-volt output.² A very simple kit for an electronic device that requires little supply power is the Knight-Kit headphone code oscillator circuit shown in Fig. 4.

Temperature-sensitive resistor

The change in resistance of a conducting material with temperature is used to make another form of temperature-sensitive transducer. This type is widely used to measure small temperature changes in an electrical form for remote indication or telemetering, as from a space vehicle. In its older form, where the positive temperature coefficient of the resistance of a pure metal was used, the method was fairly insensitive. Platinum wire, for example, is typical of the pure metals, with a temperature coefficient (α) of approximately $+ .004$. When a length of platinum wire that has a resistance of 100 ohms is heated to 25°C above room

²Thermo-electronicist kit supplier is Hermon E. Cotter, 15766 Blackstone, Detroit 23, Mich.

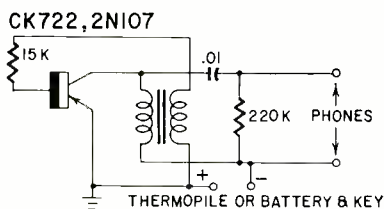


Fig. 4—Headphone type of code-practice oscillator suitable for operation from modest output of a home-made thermopile.

COMPARE

QUAM SPEAKERS

feature
for
feature

then decide
for yourself which brand
gives you the best value and the best
performance in every speaker installation

	QUAM	BRAND A	BRAND B
ADJUST-A-CONE SUSPENSION to assure precise voice coil centering and alignment	YES	NO	NO
U-SHAPED POT to give you lowest possible energy loss and accurate magnet alignment	YES	NO	NO
ALNICO V MAGNETS	YES	YES	YES
HUMI-GARD CONE for greater heat and humidity protection in outdoor speakers	YES	NO	NO
AVAILABLE WITH SPECIAL VOICE COILS, SPECIAL FIELDS	YES	NO	NO
ADVERTISED TO THE PUBLIC	NO	YES	NO
LISTINGS IN PHOTOFACTS AND COUNTERFACTS to save you time, assure correct replacements	YES	NO	NO
THIRTY YEARS OF EXPERIENCE in engineering and manufacturing quality loudspeakers under same ownership	YES	NO	NO

Write

for your free copy of the QUAM General Catalog, listing the full line of QUAM speakers for radio-tv replacement, public address, and high fidelity. QUAM speakers are completely manufactured in the United States of America.

QUAM-NICHOLS COMPANY

238 East Marquette Road • Chicago 37, Illinois

ALWAYS INSIST ON PROVED BRAND NAMES Ask By Name For GENUINE "NO NOISE" PRODUCTS BEWARE OF CHEAP SUBSTITUTES

NO-NOISE TUNER-TONIC

With PERMA-FILM

- Economical—a little does a lot.
- Cleans, lubricates, restores all tuners, including water type.
- Non-toxic, non-inflammable.
- Use for TV, radio and FM.

6 Oz. Aerosol Can

\$3.25

NET to Servicemen



NO-NOISE VOLUME CONTROL and CONTACT RESTORER

- Cleans
- Lubricates
- Protects
- NOT A CARBON TET SOLUTION

2 Oz. Bottle \$1.00
6 Oz. Spray Can \$2.25
NET to Servicemen

NOW AVAILABLE

FREE AT YOUR JOBBERS 5" PLASTIC EXTENDER



With Push Button Assembly For Pin-Point Applications Does Not Cause Short

ELECTRONIC CHEMICAL CORP. 813 Communipaw Avenue Jersey City 4, N. J.

ELECTRONICS

temperature, its resistance goes up to 110 ohms. By comparison, the new semiconductor materials are much more sensitive. Their temperature coefficient is negative and of the order of $-.04$. Because this change with temperature is much faster than that of a metal (and in the opposite direction), a ratio based on absolute temperature is used to plot the unit's resistance.³ Such a table for a 100-ohm thermistor (Glennite 21TE1) shows that the new resistance at 25°C above room temperature would be 40.6 ohms. So for the same 25°C change in temperature, the resistance of the platinum increases by about 10%, while that of the semiconductor thermistor decreases by about 60%. This substantial change in thermistor resistance with small change in temperature can easily be detected and displayed on an electrical instrument.

Detecting temperature changes

A circuit using a thermistor as one arm of a Wheatstone bridge is shown in Fig. 5. The thermistor (Glennite 31CB1) has a nominal resistance of 1,000 ohms at room temperature (25°C). The bridge is arranged with equal arms of 1,000 ohms for R1 and R2. Potentiometer R3 in series with the 220-ohm fixed resistor R4 allows this arm to produce a balance when the total resistance of R3 plus R4 is set to

³See table in thermistor bulletin of Gulton Industries, Glennite Thermistor Div., Metuchen, N.J.

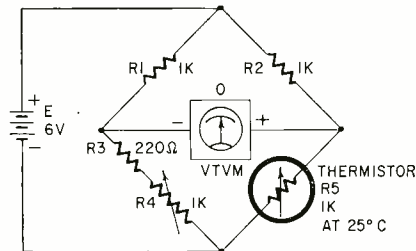


Fig. 5—Wheatstone bridge used to measure temperature changes.

equal the actual thermistor (R5) resistance. R4 allows for enough variation of its arm to restore balance when the thermistor responds to a change in its surrounding (ambient) temperature.

The indicator is a large-size vtvm previously used in Parts I and II as a demonstration meter. This time it is used on its zero-center 1.5-0-1.5 volts dc range. When used in this manner, a change of 5°C in the temperature of the thermistor (coefficient -3.9%) will cause its resistance to change to 830 ohms (or about five-sixths of its original value). The corresponding unbalance voltage (ΔE) can then be expected to be around $\frac{1}{4}$ volt, a value easily read on the demonstration meter.⁴

As an alternative method of indicat-

⁴ ΔE can be predicted from the equal-arm bridge expression:

$$\Delta E = E \left[\frac{1 - \alpha}{2(1 + \alpha)} \right]$$

where α is the ratio of the new thermistor resistance to the old ($5/6$ in this case).

ing the change in resistance, potentiometer R4 could be marked off to read the temperature directly from the amount of resistance required to restore the bridge balance. Either way, the bridge method for indicating the change in resistance offers an important advantage over simpler ohmmeter methods in that negligible current is taken by the de vtvm indicator at balance. When used with refinements that take into account such matters as resistance of the leads, the heating effect of the current through the thermistor, and high galvanometer sensitivity, this bridge method can detect a temperature change as small as .0005°C, or about one part in a million at room temperature. (See Partridge reference.)

Radioactivity

The subject of radiations from radioactive material is very broad. The present discussion of the demonstration of the detection of radioactivity and indicating its relative intensity is, of necessity, limited in its scope and restricted to that portion of the field that concerns only one common method of indicating the relative intensity of any radioactivity present. This type of survey meter employs a Geiger-Muller tube in a Geiger counter arrangement. With the understanding that this demonstration must be regarded merely as an introduction to this highly important topic, a bit of background on the various

NOW take another look at

NEW  MODEL 644

SOUND SPOT MICROPHONE • LIST \$110.00

If you are in the commercial sound business, you have had your share of . . . "they couldn't be done" . . . jobs at one time or another in your business life. These jobs could not be solved because general purpose microphones just couldn't do the job. That, fortunately, is past history. E-V's new Model 644 ushers in a new era in the concept of microphone pick-up. So take another look and see how many of those "tough" jobs the 644 reclassifies to "simple and easy". Your local E-V distributor has all the details on the Model 644. Why not call him today or write Dept. 30E for our new Commercial Sound Catalog No. 132.

Electro-Voice®

types of radiation makes a good starting point.

Most of us are familiar with the term radiation, as applied to the naturally radioactive substances uranium or thorium (and their byproduct, radium). We also recognize the primary radiations that constantly emanate from them in three forms:

▶ **Alpha particle (α)**—the positively charged nucleus of a helium atom.

Composition: 2 protons, 2 neutrons, giving it a charge of +2 and a weight about 4 times the hydrogen atom.

Range: Travels about 1 inch in air, and is stopped by a piece of paper or, to all practical purposes, by the skin.

▶ **Beta Particle (β)**—an elementary charge of electricity.

Composition: 1 electron, giving it a charge of -1, and a weight about 1/1,850 that of the hydrogen atom (or about 7,500 times lighter than an alpha particle).

Range: Travels a few feet in air and is stopped by an inch of wood.

▶ **Gamma ray (γ)**—radiant energy. *Composition:* Very high-frequency photon having no charge or weight.

Range: Great distance through air and correspondingly smaller distances through concrete or lead. (The greatest danger to living cells is from these highly penetrating rays.)

To the three radiations from the naturally radioactive material must be

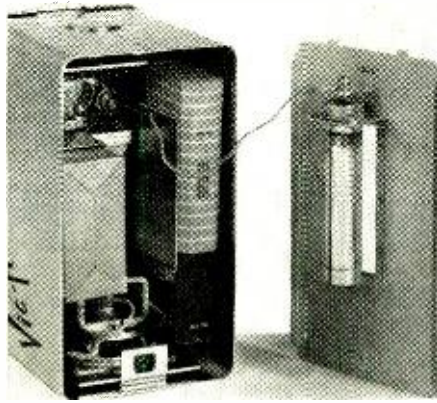


Fig. 6—Bottom (left) and top (right) views of the Vico-Tic portable Geiger counter. The Geiger-Muller tube is mounted behind the window in the instrument's bottom.

added the radiations possible from man-made radioactive materials—the radioactive isotopes which are being produced in ever-increasing quantity. This is not the place to discuss the protons, neutrons and other elementary-particle manifestations in nuclear reactions. Suffice it to say that they are fundamentally important to all of us. Knowing that these radiations cannot be seen, heard, smelled, tasted or felt, we should also all know how they can be detected.

The various methods of counting radioactive radiations are based chiefly on the ionizing properties of the radia-


tions. This is true for all of the three most commonly used methods:

▶ The simplest—the photographic film method. Blackening of the photographic plate is caused by the ionizing effects of the radiations on the silver compounds in the film emulsion

▶ The most sensitive—the scintillation counter. Ionizing particles cause a phosphorescent screen to produce flashes of light, which are seen and greatly amplified by a photomultiplier tube, and then counted.

▶ The most commonly used—the Gei-


(Continued on page 88)

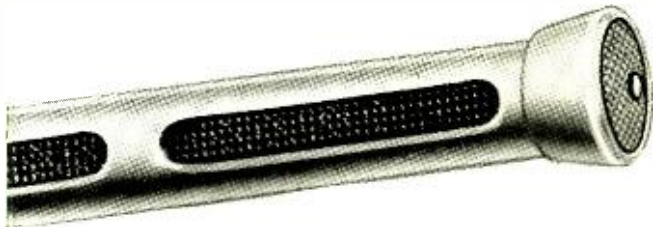


those "impossible" sound jobs!

compare polar patterns yourself


NON-DIRECTIONAL

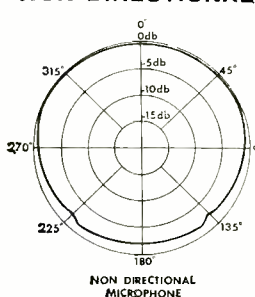

CARDIOID

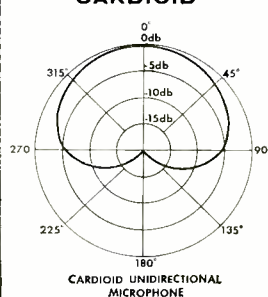

SOUND SPOT

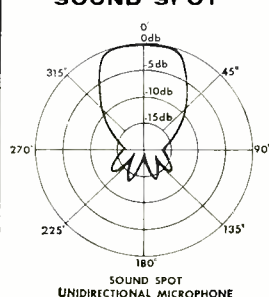

- Four times greater working distance than the best cardioids, depending on acoustics
- Greatly reduces feedback
- Retains "on-mike" presence despite extended working distance
- Excellent outdoors . . . less wind noise
- Priced low to fit most budgets
- Lasts a lifetime

Another better product for better sound from . . .

ELECTRO-VOICE, INC.

Commercial Products Division • Loudspeakers-Microphones

BUCHANAN, MICHIGAN





A Home Study Program for Engineering Technicians and Professional Engineers Comparable in Technological Content to College-Level Electronics Residence Courses.

CREI's Extension Division offers combinations of courses in advanced electronics engineering technology to meet present or future employment requirements, and step up your earning power.

A CREI program, the product of 33 years experience, is neither short-cut nor magic formula. It is an accredited home study curriculum which may take as little as 18 months, or as much as 3 years, depending upon the course selected and amount of stick-to-itiveness brought to bear. The program is designed specifically for men employed in a technical capacity in the electronics industry, where a shortage of manpower with advanced technical education not only exists, but shows every likelihood of increasing.

Now fifth in volume among American industries, the elec-

tronics industry offers almost unlimited employment and advancement opportunities. Applications of new electronic developments in automation, instrumentation, industrial electronics, aeronautical electronics, guided missiles, servomechanisms, computers, astronautics and telemetering create new jobs every day. Yet, paradoxically, industry growth does not always mean individual growth. Companies actively seeking men with modern, advanced technological knowledge are simultaneously firing mediocre men who lack this knowledge.

CREI students (more than

20,400 are currently enrolled) keep pace with the needs of the ever-advancing electronics industry and are eagerly sought by employers who offer solid opportunities for rapid promotion.

Since 1927 we have directed the technical education of students in advanced electronics engineering technology. We developed the prototype civilian electronics course for the Army Signal Corps in 1941, supplied 300,000 texts to the U. S. Navy in a special course for radio technicians in the South Pacific in 1943, trained hundreds of technicians during World War II for the Signal Corps. We co-founded

RADIO-ELECTRONICS

the National Council of Technical Schools, which first established scholastic and business standards for the technical school field. We were among the first three technical institutes whose curricula were accredited by the Engineers' Council for Professional Development. In 1946 we instituted the group training programs used by companies representing the cream of the electronics and aviation industries. CREI courses are widely employed today in company-sponsored educational plans by companies throughout the U. S. and Canada.

What does this record of achievement mean to you as a CREI student? It means that industry and the Armed Services alike respect CREI men. It means that your CREI diploma is a door-opener. Significantly, Help Wanted ads often specify "CREI education or equivalent required." Our Placement Bureau, which helps graduates and advanced students find more desirable positions, is always available to CREI men. While no placement guarantees will be made by CREI or any other reputable institution, for many years the demand for CREI graduates and advanced students has far exceeded the supply.




CREI HOME STUDY ADVANTAGES.

This advanced technical education is accomplished on your own time, during hours chosen by you. You waste no time in travel. You have plenty of time to do your best. Your work is under the supervision of a regular staff instructor who guides your progress step by step. Courses are prepared and taught by men experienced both in teaching and in electronics, presented in easy-to-understand form, kept up to date by periodic revision. Experience in more than three decades of home-study teaching, during which time we have corrected and commented on many hundreds of thousands of examinations, en-

ables us to anticipate questions in our lesson material.

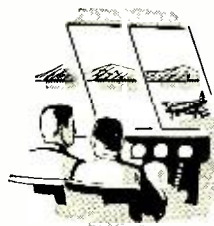CREI STUDENTS are professional electronics engineers and technicians, all over the world and in every phase of electronics, about one-third military, the rest civilian. Their median age is 28. In 1958 they devoted approximately 1,572,400 hours to 104,831



lesson texts, answered and were individually graded upon 1,048,310 searching questions and engineering problems. They studied advanced electronics engineering technology associated with transistors, microwaves, forward scatter, computers, servomechanisms, radar, electronic navigational devices and the entire field of modern electronics. New students enrolled during the year are on the missile ranges of

Vandenburg AF Base and Cape Canaveral. They are at Alamogordo and China Lake, at SAC bases around the world. They are in the research laboratories and manufacturing plants where the latest electronic equipment is designed and produced. They maintain electronic equipment for United Air Lines, and Trans-Canada Air Lines. They share in electronics at All America Cables and Radio, Inc., and The Martin Co. They work for USIA (Voice of America) and Columbia Broadcasting System, for Gates Radio and Federal Electric, to name but a few. All of the firms mentioned offer their personnel CREI education under company sponsorship. CREI men are found by the hundreds among field engineers of major electronic manufacturers. They're across the world and across the street. They're men you'll compete with—to gain or hold your place in the electronics profession.



If ambition is part of your make-up—if you

want to convert interest and energy into dollars of income—if you want to convert your spare evening hours into material benefit and the personal satisfaction that comes with advancement and respect of your associates—then CREI's home study education assures you of:

1. A solid foundation of college-level, advanced technical electronic engineering knowledge.

2. A means of keeping abreast of the complex developments in electronics.

3. The ability to communicate intelligently with your engineering associates and superiors.

4. The best preparation for professional advancement in electronics as the industry demands more qualified personnel.

QUALIFICATIONS FOR CREI. College degree is not essential. If you have had basic electronic education, practical experience in electronics and a high school education, you can probably qualify. A good way to find out: Use the postage-paid card. It will bring you the free 54-page book which has launched thousands on their advanced careers: "Insurance for Your Future in the New World of Electronics." Tuition is reasonable and may be paid monthly. It takes just one \$10-a-week raise to repay your investment in CREI education and leave you a substantial bonus the first year. Available to veterans under GI bill.



RESIDENCE SCHOOL in Washington, D. C. for those who can attend classes. Day and evening classes start at regular intervals. Qualified graduates earn AAS degree in approximately 27 months. Electronics experience not required for admission.

CAPITOL RADIO ENGINEERING INSTITUTE

ECPD Accredited Technical Institute Curricula. Founded 1927

Dept. 1403-GI
3224 16TH ST., N.W.
WASHINGTON 10, D. C.

EE

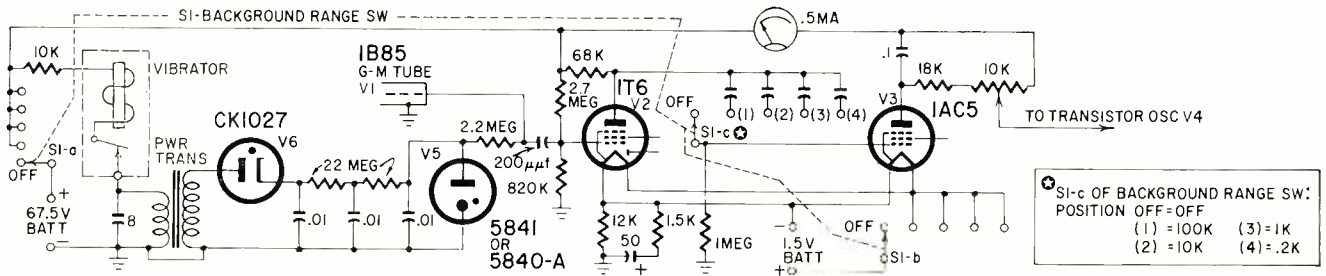


Fig. 7—Functional circuit of Geiger-counter type of radiation detector.

(Continued from page 83)

ger counter. A pulse of ionization resulting from the passage of a single ionizing particle through the gas of the G-M tube is amplified and counted.

The last method is selected for use here because the Geiger detector responds to all types of radioactive radiations, regardless of whether the ionization results directly from a primary source, such as an alpha or beta particle, or indirectly from a secondary source, such as a photo-electron produced in the gas by the passage of a gamma ray. (This method may also be extended to neutrons, which produce no ionization directly, but do eject ionizing protons from suitable materials. The protons in turn ionize the gas in proportion to the number of neutrons that produced them.) As a result of the ionization, produced either directly or by secondary radiation in the G-M tube, the count of the ionizing events provides a measure of the overall intensity of the radiation.

Geiger-counter demonstration

The appearance of reasonably priced portable Geiger counters, popular for survey purposes, as a radiation-danger monitor, and also in amateur uranium prospecting, is shown in Fig. 6. The rear view shows the silvered surface of the Geiger tube behind the window in the base of the case. The tube itself consists of a central wire conductor in a thin-walled metallic envelope that encloses the low-pressure gas within the tube. The walls of the window and tube are kept thin to allow the passage of energetic beta rays in addition to gamma rays. In operation, about 900 volts dc is applied to the inner conductor so the tube operates in its "plateau" region. (This is the sensitive voltage region at which the gas is well below its glow-discharge level, but is responsive to any radiation that produces an ionizing event and gives an electrical pulse as an output.) The top view shows the indicating meter and the sensitivity selector switch (left) as the main control. (The right-hand knob simply controls speaker volume.)

A simplified functional schematic circuit of the Geiger counter is shown in Fig. 7. Two batteries form its power supply—a 1.5-volt unit for the amplifying tube filaments and a 67.5-volt unit, both for the plate supply of the amplifying tube and for the vibrator producing the 900-volt potential applied to the Geiger tube.

Starting with the 900-volt high-voltage arrangement, the 67.5-volt battery feeds the vibrator. The vibrator's interrupter action induces high-voltage inductive kicks in the transformer's secondary which are rectified by rectifier V6, filtered by the R-C combination and stabilized by the 900-volt 5840 glow-tube (V5). The positive side of this high voltage is applied to the central conductor of the 1B85 Geiger tube (V1).

With the Geiger tube energized, we can trace the arrival of an ionizing event, such as a cosmic ray, which is a natural phenomenon constantly occurring at random. The electrical pulse resulting from the ionization by the cosmic ray is fed to the input of the two-stage amplifier, which charges the integrating capacitor in the plate circuit of the first stage and which produces a proportionate current pulse in the meter in the plate circuit of the second stage. A transistor oscillator is also connected to the output of the second stage so each pulse can be heard as a separate chirp in the speaker if the counts come slowly enough. This is the situation when the selector switch is set to its most sensitive position. Since these random pulses come too slowly for the meter to assume a steady average position, the background count is made by counting the chirps for a few minutes, and getting an average.

After the background count has been established (the position of the instrument, whether horizontal or vertical, is not significant for this count), a standardizing radioactive sample (provided with the instrument) is held against the instrument's base. The chirps quickly merge into a tone (indicating

counts too rapid to count) and the meter needle tends to go off scale. The selector switch is now placed to a less-sensitive range position and the reading of the meter is taken, 375 counts per minute. Subtracting the background count of about 35 gives 340 counts per minute as an indication of the activity of this particular sample, which corresponds (for this quantity of sample) roughly to ore containing around 0.5% of uranium.

For comparing other radioactive sources, the radium-coated dial of a wristwatch will provide a good example (see Fig. 8). When held against the base, the reading obtained was about 4,000 counts per minute, indicating radiation activity around 10 times greater than the sample of ore. (This is not surprising—the radium used on the dial face has been greatly refined.)

There are many varieties of Geiger type survey meters on the market, with various probes and refinements. Further experiments, such as testing different shielding material in varying thicknesses, use of special probes for discriminating between types of radiations and determination of the half-life of a radio isotope, must be left for later consideration. With this introduction, it is hoped that a good intelligent start can be made toward a better presentation and understanding of this important area of vital knowledge. END

References

Gordon R. Partridge, *Principles of Electronic Instruments*, Prentice-Hall, 1958
 Batcher & Moulie, *The Electronic Control Handbook*, Instruments Publishing Co., 1946
 US Atomic Energy Commission, *The New Force of Atomic Energy*, Office of Public Education, Savannah River Operations Office, PO Box A, Aiken, S.C.


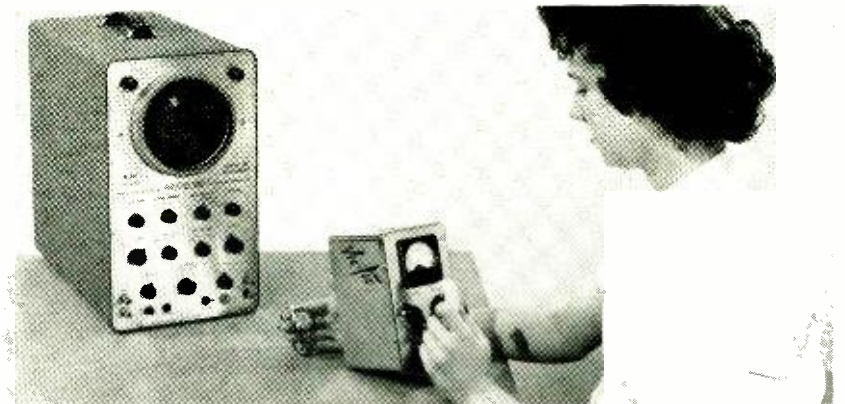


Fig. 8—Using a Geiger counter to measure and hear the radiation given off by the luminous dial of a wrist watch. The oscilloscope is optional and used if a simultaneous visual display is desired.

how to make

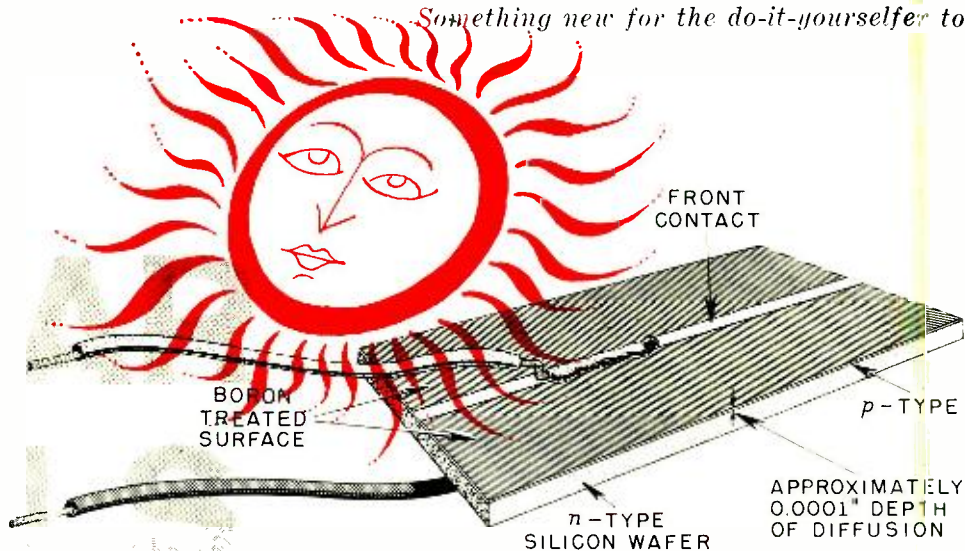Something new for the do-it-yourselfer to try



Makeup of finished home-made solar cell.

By D. M. CHAPIN*

SINCE the silicon solar cell (Bell solar battery) was announced in April, 1954, there has been keen interest in making and using solar cells. Unfortunately, the process was exacting, and required materials and equipment not available in most high school or college laboratories. Anyone who asked how he could make a solar cell was politely told he would be unable to do so and was advised to buy finished cells.

This situation has always been distasteful to several workers at Bell Laboratories, and when I was asked to lecture to a group of science teachers, I resolved to simplify the process so that anyone could use it in any high school lab. It may still be more practical to buy finished cells, but anyone who can handle hydrofluoric and nitric acids can make a solar cell. Probably its efficiency will be less than 10% (maybe 5% or 6%) but the open-circuit voltage even in dim light can be quite good. With reasonable skill in the operation, the finished cell will be reasonably rugged and have permanent soldered leads.

Since this is a how-to-do-it article, theory will be limited to that necessary to understand what is being done. For complete coverage of theory, the reader is directed to the references at the end of the article. For the present, it is sufficient to know that electric current is generated in a silicon crystal (also germanium and others) when light of the proper wavelength (color) is absorbed at the interface between n-type and p-type regions. The types of silicon are produced by minute amounts of impurities. For our purpose, we will start with n-type silicon wafers and change the surface type by diffusing boron into the surface. The depth of diffusion is so small that light can penetrate to the junction between the diffused layer and the original material and produce an electric current. The cell is completed by making contact to the diffused surface and to the original material. (For more information on the whys of this action, consult the references.)

The outline below gives an overall picture of the process and will be followed by a more detailed description.

1. The silicon wafers, obtainable from International Rectifier Corp., are lap-ground with 280 mesh carborundum.
2. The cells are lightly etched in a mixture of HNO_3 (nitric acid) and HF (hydrofluoric acid).
3. One surface is painted with a solution of boric acid, boric oxide or commercial grade borax.

4. To diffuse the boron into the surface, wafers are heated in air for about 10 minutes at about $1,050^\circ\text{C}$ and cooled to room temperature.
5. The untreated side is again lap-ground with carborundum.
6. The cells are treated with HF to remove oxides.
7. Part of the diffused surface is covered with acid-resisting tape.
8. Exposed surfaces are electroplated in electroless nickel-plating solution. (The formula and summary of the process appear later in the article.)
9. Plated surfaces are tinned with solder, and leads are attached.
10. The edges of the wafer are ground with carborundum.
11. HF and HNO_3 etchant is applied to the edges to complete the separation of p- and n-areas.

The operation in detail

1. As previously stated, this process starts with n-type silicon wafers purchased for the purpose. Maybe some day the amateur can start with sand, but refining silicon and preparing wafers is still "beyond the scope—." International Rectifier Corp., (1521 E. Grand Avenue, El Segundo, Calif.), has supplied wafers for educational purposes to high schools and other institutions at \$1.25 per wafer. The quotation was for 20 wafers and may be slightly different for smaller amounts. The wafers are 1 x 2 cm and are designated "solar-grade n-type silicon wafers." Very good cells have been made from them.

Lap-grinding the wafers removes surface stairs and provides a good surface for electroplating. Use carborundum powder (about 280 mesh) and water on a flat piece of glass, grinding by hand for a minute or two. Slight pressure of the fingers on their tops is sufficient to move the wafers over the glass and cause grinding. Only the surface to be diffused with boron needs to be lapped at this time. The "back" surface will be treated later.

2. Even a very fine grinding produces strains of its own. These can be removed with acid. The effect desired is a compromise between a roughened surface to take the electroplate and a strain-free surface. Before starting, note that HF and HNO_3 are dangerous acids and the fumes should not be breathed! HF is particularly dangerous as its effects are not immediately evident but persist with considerable pain for

(Continued on page 92)

*Bell Telephone Laboratories, Murray Hill, N. J.

SUPERIOR'S NEW MODEL 77

VACUUM TUBE VOLTMETER

WITH NEW 6" FULL-VIEW METER

Compare it to any peak-to-peak V. T. V. M. made by any other manufacturer at any price

SPECIFICATIONS

• DC VOLTS — 0 to 3/15/75/150/300/750/1,500 volts at 11 megohms input resistance. • AC VOLTS (RMS) — 0 to 3/15/75/150/300/750/1,500 volts. • AC VOLTS (Peak to Peak) — 0 to 6/40/200/400/800/2,000 volts. • ELECTRONIC OHMMETER — 0 to 1,000 ohms/10,000 ohms/100,000 ohms/1 megohm/10 megohms/100 megohms/1,000 megohms. • DECIBELS — 10 db to + 18 db, + 10 db to + 38 db, + 30 db to - 58 db. All based on 0 db = .006 watts (6 mw) into a 500 ohm line (1.73v). • ZERO CENTER METER — For discriminator alignment with full scale range of 0 to 1.5/7.5/37.5/75/150/375/750 volts at 11 megohms input resistance.

Complete with operating instructions, probe, leads, and case, 110-120 volt 60 cycle. Only.....

\$42⁵⁰
NET



Model 77—Vacuum Tube Voltmeter
Total Price \$42.50
Terms: \$12.50 after 10 day trial, then \$6.00 monthly for 5 months if satisfactory. Otherwise return, no explanation necessary.

• Uses new improved SICO printed circuitry. • Employs a 12AU7 as D.C. amplifier and two 9006's as peak-to-peak voltage rectifiers to assure maximum stability. • Meter is isolated from the measuring circuit by a balanced push-pull amplifier. • Uses selected 1% zero temperature coefficient resistors as multipliers.

AS A DC VOLTMETER: The Model 77 is indispensable in HI-FI Amplifier servicing and a must for Black and White and color TV Receiver servicing where circuit loading cannot be tolerated.

AS AN ELECTRONIC OHMMETER: Because of its wide range of measurement leaky capacitors show up glaringly. Because of its sensitivity and low loading, intermittents are easily found, isolated and repaired.

AS AN AC VOLTMETER: Measures RMS value of sine wave, and peak-to-peak value of complex wave. Pedestal voltages that determine the "black" level in TV receivers are easily read.

SUPERIOR'S NEW MODEL 79

SUPER-METER

WITH NEW 6" FULL-VIEW METER

A Combination

VOLT-OHM MILLIAMMETER.

Plus CAPACITY, REACTANCE, INDUCTANCE and DECIBEL MEASUREMENTS.

Also Tests SELENIUM and SILICON RECTIFIERS, SILICON and GERMANIUM DIODES.

ber of new components used in all phases of today's electronic production. For example with the Model 79 SUPER-METER you can measure the quality of selenium and silicon rectifiers and all types of diodes—components which have come into common use only within the past five years, and because this latest SUPER-METER necessarily required extra meter scale, SICO used its new full-view 6-inch meter.

Specifications

D.C. VOLTS: 0 to 7.5/15/75/150 750 1,500.
A.C. VOLTS: 0 to 15/30 150/300/1,500 3,000.
D.C. CURRENT: 0 to 1.5/15 150 Ma. 0 to 1.5/15 Amperes.
RESISTANCE: 0 to 1,000 100,000 Ohms. 0 to 10 Megohms.
CAPACITY: .001 to 1 Mfd. 1 to 50 Mfd.
REACTANCE: 50 to 2,500 Ohms. 2,500 Ohms to 2.5 Megohms.
INDUCTANCE: .15 to 7 H-tries. 7 to 7,000 Henries.
DECIBELS: -6 to +18, +14 to +38, +31 to +58.

The following components are all tested for QUALITY at appropriate test potentials. Two separate BAD-GOOD scales on the meter are used for direct readings.

All Electrolytic Condensers from 1 MFD to 1000 MFD.
All Selenium Rectifiers. All Germanium Diodes.
All Silicon Rectifiers. All Silicon Diodes.

Model 79 comes complete with operating instructions and test leads. Use it on the bench—use it on call. A streamlined carrying case included at no extra charge accommodates the tester, instruction book and test leads.
Only

\$38⁵⁰
NET



Model 79 — SUPER-METER . . . Total Price \$38.50 — Terms: \$8.50 after 10 day trial, then \$6.00 per month for 5 months if satisfactory. Otherwise return, no explanation necessary!

The Model 79 represents 20 years of continuous experience in the design and production of SUPER-METERS, an exclusive SICO development.

In 1938 Superior Instruments Co. designed its first SUPER-METER, Model 1150. In 1940 it followed with Model 1250 and in succeeding years with others including Models 670 and 670-A. All were basically V.O.M.'s with extra services provided to meet changing requirements.

Now, Model 79, the latest SUPER-METER includes not only every circuit improvement perfected in 20 years of specialization, but in addition includes those services which are "musts" for properly servicing the ever increasing num-

GENOMETER

7 Signal Generators in One!

- ✓ R.F. Signal Generator for A.M.
- ✓ R.F. Signal Generator for F.M.
- ✓ Audio Frequency Generator
- ✓ Bar Generator
- ✓ Cross Hatch Generator
- ✓ Color Dot Pattern Generator
- ✓ Marker Generator

A versatile all-inclusive GENERATOR which provides ALL the outputs for servicing:
A.M. Radio • F.M. Radio • Amplifiers • Black and White TV • Color TV
R. F. SIGNAL GENERATOR: The Model TV-50A Genometer provides complete coverage for A.M. and F.M. alignment. Generates Radio Frequencies from 100 Kilocycles to 60 Megacycles on fundamentals and from 60 Megacycles to 180 Megacycles on powerful harmonics.
VARIABLE AUDIO FREQUENCY GENERATOR: In addition to a fixed 400 cycle sine-wave audio, the Model TV-50A Genometer provides a variable 300 cycle to 20,000 cycle peak wave audio signal.
BAR GENERATOR: The Model TV-50A projects an actual Bar Pattern on any TV Receiver Screen. Pattern will consist of 4 to 16 horizontal bars or 7 to 20 vertical bars.

THE MODEL TV-50A comes absolutely complete with shielded leads and operating instructions.

\$47⁵⁰
NET



Model TV-50A—Genometer. Total price—\$47.50—Terms: \$11.50 after 10 day trial, then \$6.00 monthly for 6 months if satisfactory. Otherwise return, no explanation necessary!

CROSS HATCH GENERATOR: The Model TV-50A Genometer will project a cross-hatch pattern on any TV picture tube. The pattern will consist of non-shifting, horizontal and vertical lines interlaced to provide a stable cross-hatch effect.

DOT PATTERN GENERATOR (FOR COLOR TV) Although you will be able to use most of your regular standard equipment for servicing Color TV, the one addition which is a "must" is a Dot Pattern Generator. The Dot Pattern projected on any color TV Receiver tube by the Model TV-50A will enable you to adjust for proper color convergence.

MARKER GENERATOR: The Model TV-50A includes all the most frequently needed marker points. The following markers are provided: 189 Kc., 262.5 Kc., 456 Kc., 600 Kc., 1000 Kc., 1400 Kc., 1600 Kc., 2000 Kc., 2500 Kc., 3579 Kc., 4.5 Mc., 5 Mc., 10.7 Mc. (3579 Kc. is the color burst frequency).

EXAMINE BEFORE YOU BUY!
USE APPROVAL FORM ON NEXT PAGE

SUPERIOR'S NEW MODEL TW-11

STANDARD PROFESSIONAL

TUBE TESTER



Model TW-11—Tube Tester
Total Price \$47.50

Terms: \$11.50 after 10 day trial, then \$6.00 monthly for 6 months if satisfactory. Otherwise return, no explanation necessary.

★ Tests all tubes, including 4, 5, 6, 7, Octal, Lock-in, Hearing Aid, Thyatron, Miniatures, Sub-miniatures, Novals, Subminars, Proximity fuse types, etc.

★ Uses the new self-cleaning Lever Action Switches for individual element testing. Because all elements are numbered according to pin-number in the RMA base numbering system, the user can instantly identify which element is under test. Tubes having tapped filaments and tubes with filaments terminating in more than one pin are truly tested with the Model TW-11 as any of the pins may be placed in the neutral position when necessary.

★ The Model TW-11 does not use any combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible to damage a tube by inserting it in the wrong socket.

★ Free-moving built-in roll chart provides complete data for all tubes. All tube listings printed in large easy-to-read type.

NOISE TEST: Phono-jack on front panel for plugging in either phones or external amplifier will detect micro-phonics tubes or noise due to faulty elements and loose internal connections.

EXTRAORDINARY FEATURES

SEPARATE SCALE FOR LOW-CURRENT TUBES: Previously, on emission-type tube testers, it has been standard practice to use one scale for all tubes. As a result, the calibration for low-current types has been restricted to a small portion of the scale. The extra scale used here greatly simplifies testing of low-current types.

The Model TW-11 operates on 105-130 Volt 60 Cycles A.C. Comes housed in a handsome portable saddle-stitched Texon Case. Only

\$47⁵⁰

SUPERIOR'S NEW MODEL 82A

Multi-Socket Type

TUBE TESTER



Model 82A—Tube Tester
Total Price \$36.50

Terms: \$6.50 after 10 day trial, then \$6.00 monthly for 5 months if satisfactory. Otherwise return, no explanation necessary.

TEST ANY TUBE IN 10 SECONDS FLAT!

- ① Turn the filament selector switch to position specified.
- ② Insert tube into a numbered socket as designated on our chart (over 600 types included).
- ③ Press down the quality button—

THAT'S ALL! Read emission quality direct on bad-good meter scale.

SPECIFICATIONS

- Tests over 600 tube types
- Tests OZ4 and other gas-filled tubes
- Employs new 4" meter with sealed air-damping chamber resulting in accurate vibrationless readings
- Use of 22 sockets permits testing all popular tube types and prevents possible obsolescence
- Dual Scale meter permits testing of low current tubes
- 7 and 9 pin straighteners mounted on panel
- All sections of multi-element tubes tested simultaneously
- Ultra-sensitive leakage test circuit will indicate leakage up to 5 megohms

Production of this Model was delayed a full year pending careful study by Superior's engineering staff of this new method of testing tubes. Don't let the low price mislead you! We claim Model 82A will outperform similar looking units which sell for much more — and as proof we offer to ship it on our examine before you buy policy.

To test any tube, you simply insert it into a numbered socket as designated, turn the filament switch and press down the quality switch—THAT'S ALL! Read quality on meter. Inter-element leakage if any indicates automatically.

Model 82A comes housed in handsome, portable Saddle-Stitched Texon case. Only

\$36⁵⁰

SUPERIOR'S NEW MODEL 83

C.R.T. TESTER

TESTS AND REJUVENATES ALL PICTURE TUBES

ALL BLACK AND WHITE TUBES

From 50 degree to 110 degree types —from 8" to 30" types.

ALL COLOR TUBES

Test ALL picture tubes—in the carton—out of the carton—in the set!



Model 83—C.R.T. Tube Tester
Total Price \$38.50

Terms: \$8.50 after 10 day trial, then \$6.00 monthly for 5 months if satisfactory. Otherwise return, no explanation necessary.

● Model 83 is not simply a rehashed black and white C.R.T. Tester with a color adapter added. Model 83 employs a new improved circuit designed specifically to test the older type black and white tubes, the newer type black and white tubes and all color picture tubes.

● Model 83 provides separate filament operating voltages for the older 6.3 types and the newer 8.4 types.

● Model 83 employs a 4" air-damped meter with quality and calibrated scales.

● Model 83 properly tests the red, green and blue sections of color tubes individually—for each section of a color tube contains its own filament, plate, grid and cathode.

● Model 83 will detect tubes which are apparently good but require rejuvenation. Such tubes will provide a picture seemingly good but lacking in proper definition, contrast and focus. To test for such malfunction, you simply press the rej. switch of Model 83. If the tube is weakening, the meter reading will indicate the condition.

● Rejuvenation of picture tubes is not simply a matter of applying a high voltage to the filament. Such voltages improperly applied can strip the cathode of the oxide coating essential for proper emission. The Model 83 applies a selective low voltage uniformly to assure increased life with no danger of cathode damage.

Model 83 comes housed in handsome portable Saddle Stitched Texon case—complete with sockets for all black and white tubes and all color tubes. Only

\$38⁵⁰

SHIPPED ON APPROVAL NO MONEY WITH ORDER — NO C.O.D.

Try any of the instruments on this or the facing page for 10 days before you buy. If completely satisfied then send down payment and pay balance as indicated on coupon. **No Interest or Finance Charges Added!** If not completely satisfied return unit to us, no explanation necessary.

MOSS ELECTRONIC, INC.

Dept. D-729, 3849 Tenth Ave., New York 34, N. Y.

Please send me the units checked out approval. If completely satisfied I will pay on the terms specified with no interest or finance charges added. Otherwise, I will return after a 10 day trial positively cancelling all further obligations.


- | | |
|--|---|
| <input type="checkbox"/> Model 77 Total Price \$42.50
\$12.50 within 10 days. Balance \$6.00
monthly for 5 months. | <input type="checkbox"/> Model TW-11 Total Price \$47.50
\$11.50 within 10 days. Balance \$6.00
monthly for 6 months. |
| <input type="checkbox"/> Model 79 Total Price \$38.50
\$8.50 within 10 days. Balance \$6.00
monthly for 5 months. | <input type="checkbox"/> Model 82A Total Price \$36.50
\$6.50 within 10 days. Balance \$6.00
monthly for 5 months. |
| <input type="checkbox"/> Model TV-50A Total Price \$47.50
\$11.50 within 10 days. Balance \$6.00
monthly for 6 months. | <input type="checkbox"/> Model 83 Total Price \$38.50
\$8.50 within 10 days. Balance \$6.00
monthly for 5 months. |

Name.....

Address

City..... Zone State

All prices net, F.O.B., N. Y. C.

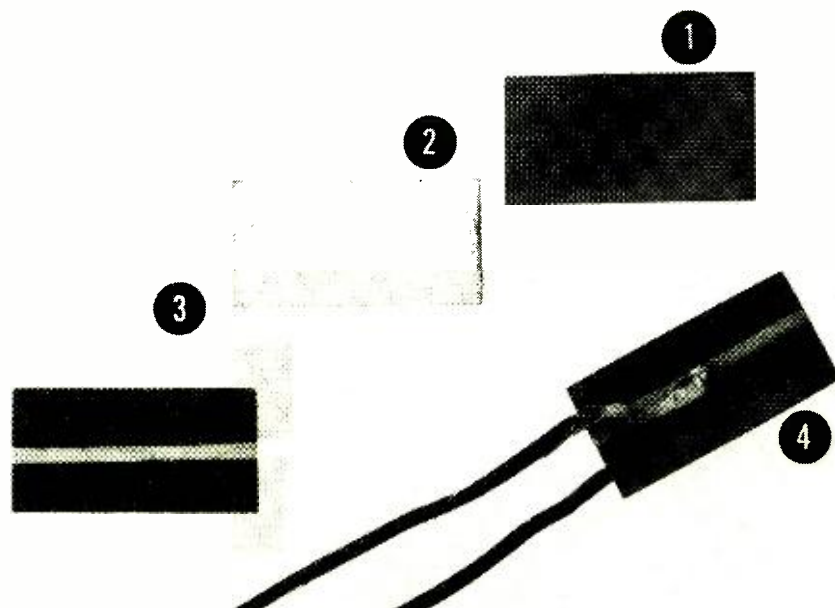

The solar cell at various stages: (1) the raw silicon element; (2) after diffusion—step 4; (3) after plating—step 8; (4) the completed unit.

(Continued from page 89)

hours or days. The area around the nails is especially vulnerable. Rubber gloves or careful handling with frequent washing in fresh water is necessary. A slurry of MgO in glycerine should be applied immediately to any suspected areas of contact. A fume hood is desirable, but careful handling in a well ventilated room proved quite satisfactory in a recent demonstration. Be sure you know how to handle acids before attempting this process.

In one respect these acids are easy to handle. Concentrated HNO_3 and HF can be mixed freely in any proportion with each other and with water without danger of overheating and violent eruption.

Plastic trays cut from empty HF bottles make excellent containers for etching. Glass and metal containers will be attacked by the acids. Cover the wafer to be etched with concentrated HNO_3 . Add small amounts of concentrated HF, stirring by tipping the tray until bubbles start. Action can be stopped by flooding with HNO_3 . After about $\frac{1}{2}$ minute of etching, flood with HNO_3 , pour off the acids and rinse several times with pure water. A shiny surface indicates too much etching, which will give a good p-n layer but will make attaching contacts very difficult.

3. Almost any compound of boron appears to be effective, and several solvents, including water and alcohol, have been used in related processes. The particular combination used in the present process was boric acid and methyl-cellosolve. To this was added fine alundum powder which acts as a binder, prevents sticking if several wafers are stacked, and serves to identify the treated surface. It is not essential to the process.

The proportions of this mixture are not critical. I used about equal parts of boric acid and alundum powder with enough methyl-cellosolve to make a thin paste.

Paint the mixture on the lapped surface of the wafer. Drying of the surface is desirable, although it appears not essential. Alundum containers or fragments of quartz tubing make good holders for the wafers.

4. Almost any ceramic oven, stove or furnace will reach $1,050^\circ\text{C}$.

A temperature of $1,100^\circ\text{C}$ gives faster diffusion. However, the best cells made recently were heated only to $1,000^\circ\text{C}$. For these, the time was increased to a half hour. Cells have been made at 950°C .

Diffusion in air has been shown to be quite satisfactory. There may be some virtue in protecting against contamina-

tion from the furnace by enclosing the wafer in a quartz tube open at one or both ends. In a recent demonstration, the simplest furnace imaginable was used. The photo shows the parts for such a furnace and an assembled furnace. The heating element is an Eagle straight Glocoil No. 415 made by Eagle Electric Manufacturing Co. and is available in many hardware stores. The hole in the center of the ceramic core serves as a heating chamber. The coil is mounted horizontally in a hole bored through a magnesia brick. A few pieces of firebrick around the coil would serve almost as well. Even moderately insulated, this unit will get too hot and burn out on normal house voltage. A Variac (variable autotransformer) to control the temperature is very useful. A bank of ordinary lamps in series with the furnace can be used as a rheostat to control the power to the furnace. To increase furnace temperature, use more lamps or higher wattage ones. Lacking these, temperature can be controlled by moving the brick insulation away from the heater coil.

Too long a diffusion time at high temperature will give a barrier beyond the reach of incoming light and will produce a cell of low current. Too little diffusion gives a surface easily damaged, a p-n junction too near the surface to absorb radiation and too high a surface resistance. Both voltage and current will be degraded.

At the end of the heating period (about 10 minutes for $1,050^\circ\text{C}$, 30 minutes for $1,000^\circ\text{C}$), remove the wafer in its quartz boat and let it cool rapidly in air. You now have a p-n barrier near the top surface. The remaining steps are to clean it up and to make appropriate contacts.

5. The untreated side is again lap-ground with carborundum. The treated side has a coating of oxide on it and is not easily damaged at this point. The grinding is to remove any p-type layer from the back surface and expose clean n-type material. It is done in the same manner as before.

6. In the polyethylene tray, cover the wafer with HF and let stand for a minute or two. HF will remove the oxide but not damage the silicon. Be sure that all traces of HNO_3 have been removed or the p-layer will be etched off. There should not be any visible evidence of chemical action except that the alundum powder will wash off the treated surface. Rinse carefully in clean water and handle only with filter paper. At this stage, keep fingers off!

7. A good acid-resisting tape is Minnesota Mining & Manufacturing Co. tape No. 549. Cut two strips of this tape and press on the active surface, leaving a narrow strip $\frac{1}{16}$ inch wide down the center. Press the tape down well

ELECTRONICS

to insure bonding. A little tape extending beyond the end and edges is useful for handling without touching the wafer.

8. Put the wafer in electroless (see formula and summary of process below) nickel-plating solution heated to just below boiling. Cover the container to keep out light. Without this precaution, voltages formed by the barrier prevent proper plating to the p-layer. About 10 minutes in the solution gives a good coverage. When the cell comes out of this bath, it should have a mat silver coating on the narrow strip and on the back. The coating should be tightly bonded and not easily rubbed off. Rinse well with water.

Electroplating is largely an art. If you did not get a well bonded electroplate, try putting in a little more ammonia. Sometimes it appears to help to drop in a small piece of freshly polished silicon or metal as a starter. If the electroplate peels off the top surface, maybe the cell was dirty from handling or perhaps the cell was etched too much in step 2. Either start all over or skip step 9 and be satisfied with pressure contacts and low current. A good voltage should result on open circuit and this will be reassuring and show that the diffusion was done correctly.

9. Remove the masking tape and tin all plated surfaces with a good grade of acid core solder (or radio solder with acid paste). Acid flux is useful here and should give a well tinned surface. Be a little careful on the treated surface not to scratch through the p-n layer. Solder flexible copper leads to top and bottom, staying away from the extreme edges to facilitate step 11. Rinse off all acid flux. You now should have a good cell with firmly soldered leads but completely self-shorted.


10. Grind edges all around to separate the top surface from the bottom electrodes. Use carborundum powder on glass as before. Rinse and dry well.

11. Mix a small amount of equal parts of HF and HNO₃. Holding the cell by its leads and using a splinter of wood (for example, a large toothpick), paint the acid mixture on all the edges. This provides a separation not possible with grinding alone. After a minute or two, wash well in a flood of water to prevent etching where not wanted. If it is necessary to repeat this etch, be sure to dry the cell well before painting on more acid.

Recently, solar cells have been made omitting steps 2 and 11 (etching with acids). The results were satisfactory. So the beginner is urged to eliminate these steps for his first cell. If someone then finds a simpler method to remove the oxide formed during the diffusion (step 6), both the HNO₃ and HF can be eliminated and the process will be quite safe.

Testing the cell

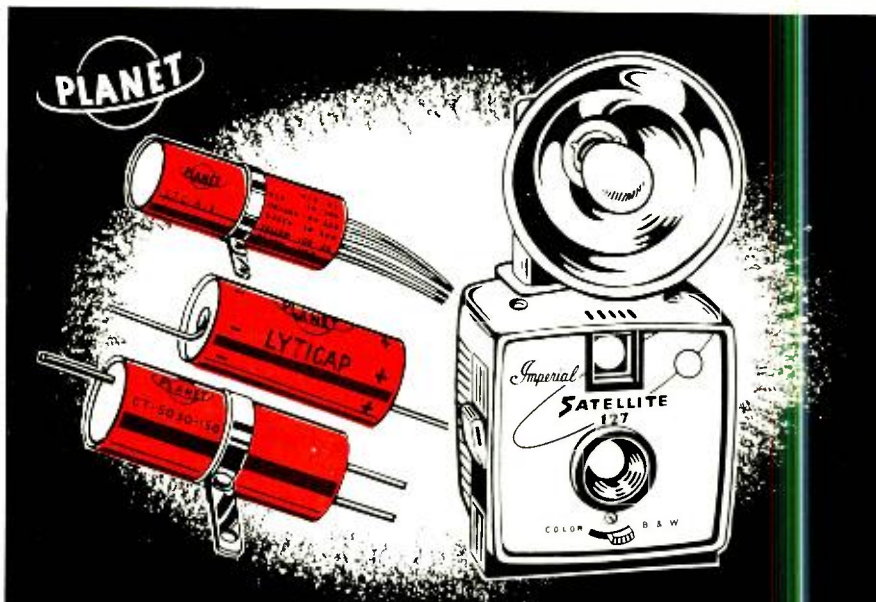Do not expect a 10% cell from this process, although you may approach



BUY 35 CONDENSERS and GET CAMERA FREE

IMPERIAL SATELLITE 3-WAY FLASH CAMERA FREE with the purchase of 35 PLANET capacitors . . . takes color snaps, color slides or black and white . . . easy to operate . . . even a child can take excellent pictures . . . attractively packaged with free film offer enabling user to have film developed and processed and receive a new roll of film for \$1.00 . . . MAKES A WONDERFUL GIFT.

Limited time offer . . . call your PLANET Distributor now . . . ask for Assortment CA-35.

PLANET SALES CORPORATION
225 Belleville Avenue Bloomfield, New Jersey

HIGH FIDELITY—buy, sell, find out. You'll get good results if you advertise in

RADIO-ELECTRONICS Opportunity Adlets
154 West 14th Street New York 11, N. Y.



LOOK
no further . . . if you're searching for hi-fi savings. Write us your requirements now.
Key Electronics Company
120-A Liberty St., 4.Y. 6, N.Y.
Clovevdate 8-4288

MAIL ORDER HI-FI

You can now purchase all your HI-FI from one reliable source and be assured of perfect delivery. Carston makes delivery from NY stock on most HI-FI. Records and tape within 24 hours. SEND US A LIST OF YOUR HI-FI REQUIREMENTS FOR OUR WHOLESALE QUOTATION and our FREE wholesale catalogue.

CARSTON STUDIOS 125-RD E 88 St. New York 3, N. Y.



It's smart to get the BEST and keep the rest of your PROFITS! . . . with EMC TEST EQUIPMENT . . . the finest quality line of precision instruments at the lowest possible prices.





Model 102 Volometer

Features a 3 1/2" . 2% accurate—800 microamperes D'Arsonval-type plastic front meter with 3 AC current ranges; and the same zero adjustment for both resistance ranges. Specifications . . . AC Voltage—5 Ranges: 0 to 12, 120-600, 1200-3000 volts. DC Voltage—5 Ranges: 0 to 6-60-300-600-3000 volts. AC Current—3 Ranges: 0 to 30-150-600 ma. DC Current—4 Ranges: 0 to 6-30-130 ma. 0 to 1.2 amps. Two Resistance Ranges: 0 to 1000 ohms. 0 to 1 megohms. Model 102. Wt 1 lb 5 oz. Size. 3 3/4" x 6 1/4" x 2". \$14.90. Kit, \$12.50.

Model 204 Tube-Battery-Ohm Capacity Tester

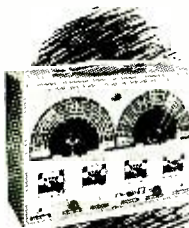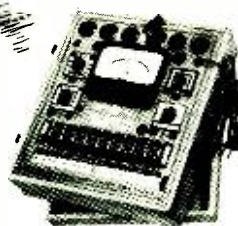Emission tube tester. Completely flexible switching arrangement. Checks batteries under rated load on "reject-good" scale. Checks condenser leakage to 1 meg. Checks resistance up to 4 megs. Checks capacity from .01 to 1 mfd. Model 204P, illustrated. \$55.90. Model CRA, Cathode ray tube adaptor. \$4.50.



Model 700 RF-AF Crystal Marker TV Bar-Generator

Complete coverage from 18 cycles to 108 megacycles on fundamentals. Bar generator for TV adjustment with a variable number of bars, available for horizontal or vertical alignment. Square wave generator to 26 kilocycles. Wien Bridge AF oscillator with sine wave output from 18 cycles to 300 kilocycles. Crystal marker and amplitude control. Individually tuned coils. Constant RF output impedance. Stepped RF attenuator. Variable percentage of modulation. Model 700 . . . \$55.90

Model 205 Tube Tester


Uses standard emission test. Tests all tubes including Noval and subminiatures. Completely flexible switching arrangement. Checks for shorts, leakages and opens. Model 205P, Hand rubbed oak carrying case. \$47.50 (illustrated). Kit, \$36.20. Model CRA, Cathode ray tube adaptor, \$4.50.




Model 104 Volometer

Features a 4 1/2" . 50 microampere meter, with 3 AC current ranges and 3 resistance ranges to 20 megohms. Specifications . . . DC Voltage: 5 ranges (20,000 ohms per volt): 0 to 6-60-300-600-3000 volts. AC Voltage: 5 ranges (1,000 ohms per volt): 0 to 6-60-300-600-3000 volts. DC Current—3 Ranges: 0 to 6-60-600 ma. AC Current—3 Ranges: 0 to 30-300 ma 0 to 3 amps. 3 Resistance Ranges: 0 to 20K, 0 to 200K, 0 to 20 megs. 5 0B Ranges. —4 to —67 dB. Model 104, with carrying strap. Wt 2 lbs. 5 oz. Size 5 1/4" x 6 1/4" x 2 1/8". \$26.95. Kit, \$19.95. Model HVT, 30,000 volt probe for Model 104, \$7.95

ELECTRONICS

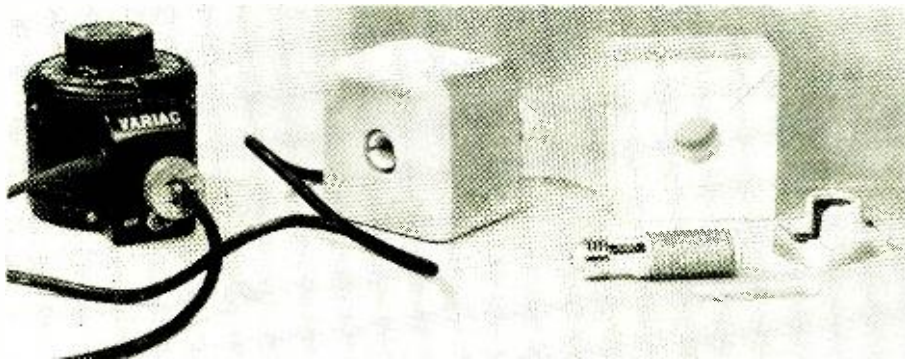

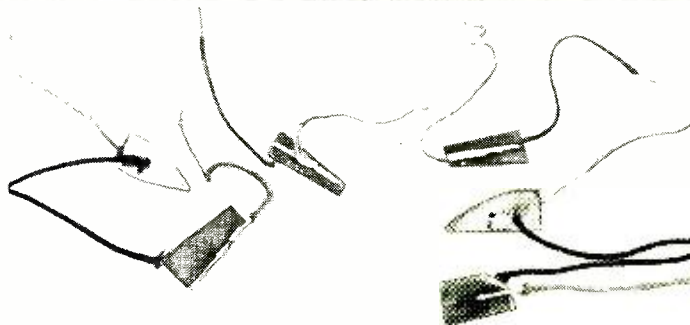(Above) Simple furnace is made from magnesia brick and a standard heating element.



(Right) Assortment of home-made solar cells.

this value. You can get a good idea of how well you have done by the following rough tests. The treated surface will be the positive terminal. In a well lighted room but not in direct sunlight nor directly under a lamp, a reading of 0.3 volt on a good voltmeter is good, 0.2 volt is acceptable and anything near 0.4 volt is excellent. A good reading here indicates that your barrier is good and that the cell is not shorted. If you get much less than 0.2 volt under this condition, try etching the edges again, or maybe repeat both grinding and etching.

Now increase the light to full sunlight or what can be obtained close to a 100-watt lamp. Before the cell gets hot, a reading of 0.50 volt is good, 0.40 volt is passable and 0.55 volt puts you with the experts.

The voltage test tells if the barrier is good and not shorted. Now connect to an ammeter to test the contacts and the depth of the barrier. Under a strong spotlight, current up to 0.2 ampere is possible. In full sunlight .030 ampere short-circuit is good and .040 is excellent. The theoretical limit for 1 x 2-cm wafers is about .090 ampere in full sunlight.

Cells can be connected in series to produce more voltage or in parallel to increase the current. In planning your finished battery, allow about 0.3 volt per cell for best power output.

Formula for electroless nickel

1. Nickel chloride—30 grams
 2. Sodium hypophosphite—10 grams
 3. Ammonium citrate—65 grams
 4. Ammonium chloride—50 grams
- Add water to make 1,000 cc. Filter the solution. Add ammonium hydroxide (household ammonia) until the solution turns from green to blue. The pH should be between 8 and 10. Bring the solution to just under boiling and drop

in the parts to be plated. Ten minutes is normal plating time. Plate light-sensitive material in the dark. Keep surfaces free from grease. Do not handle surfaces to be plated. END.

References

D. M. Chapin, C. S. Fuller and G. L. Pearson: "A New Silicon P-n Junction Photocell for Converting Solar Radiation into Electrical Power," *J. Appl. Phys.* Vol. 25, page 676; May, 1954.

Chapin, Fuller and Pearson: "The Bell Solar Battery," *Bell Telephone Record*, July, 1955.

G. Raisbeck: "The Bell Solar Battery," *Scientific American*, December, 1955.

Transactions of the Conference on the Use of Solar Energy, The Scientific Basis, Vol. V, Electrical Processes, sponsored by Association for Applied Solar Energy, Phoenix, Ariz., 1955.

Proceedings of the World Symposium on Applied Solar Energy, Association for Applied Solar Energy, Phoenix, Arizona, 1955.

M. B. Prince: *J. Appl. Physics*, Vol. 26, page 534; 1955.

W. Shockley: *Holes and Electrons*, D. Van Nostrand, 1950.

Bridges, Scaff and Shive: *Transistor Technology*, D. Van Nostrand, January, 1958.

London, Chapman and Hall: *Photosensors, A Treatise on Photoelectric Devices and Their Application to Industry*.

Photoconductivity of Germanium—Submitted for the Master's Thesis, Purdue University, Dept. of Physics, August, 1952.

The Sun at Work, Newsletter of Association for Applied Solar Energy, Phoenix, Ariz.

Solar Energy, Journal of Solar Energy Science and Engineering, Association for Applied Solar Energy, 3424 N. Central Avenue, Phoenix, Ariz.

D. C. Reynolds and G. M. Leies: *Electrical Engr.*, Vol. 73, page 734; 1954.

R. L. Cumberow: *Phys. Rev.*, Vol. 95, page 16; 1954.

E. S. Rittner: *Phys. Rev.*, Vol. 96, page 1708; 1954.

An Introduction to Solar Energy, Edited by A. M. Zarem, to be published by McGraw-Hill.

P. Rappaport: *Phys. Rev.*, Vol. 93, page 16; 1954.

R. S. Ohl and E. F. Kingsbury: "Photoelectric Properties of Ionically Bombarded Silicon," *Bell Technical Journal*, Vol. 31, No. 4, pp. 802-15; July, 1952.

R. S. Ohl: "Properties of Ionically Bombarded Silicon," *Bell Technical Journal*, Vol. 31, No. 1; January, 1952.

D. A. Jenny, J. J. Loferski and P. Rappaport: "Photovoltaic Effect in Ga As P-n Junctions and Solar Energy Conversion," *Phys. Rev.* Vol. 101, No. 3; Feb. 1, 1956.

R. E. Halsted: "Temperature Consideration in Solar Battery Development," *J. Appl. Phys.* Vol. 18, No. 10; page 1131; October, 1957.

U. F. Gianola: "Photovoltaic Noise in Silicon Broad Area P-n Junctions," *J. Appl. Phys.*, Vol. 27, pp. 51-54; January, 1956.

Yes, tell me more, send me FREE—a detailed catalog of the complete EMC line. RE-36

NAME _____

STREET _____


CITY _____ STATE _____

EMC Electronic Measurements Corp.
625 B'way, New York 12, N. Y.
Ex. Dept. 431 Greenwich St., New York 13, N. Y.

LICKING THE i-n-t-e-r-m-i-t-t-e-n-t-s

Techniques for tracking down these most difficult of troubles

By **LYMAN E. GREENLEE**

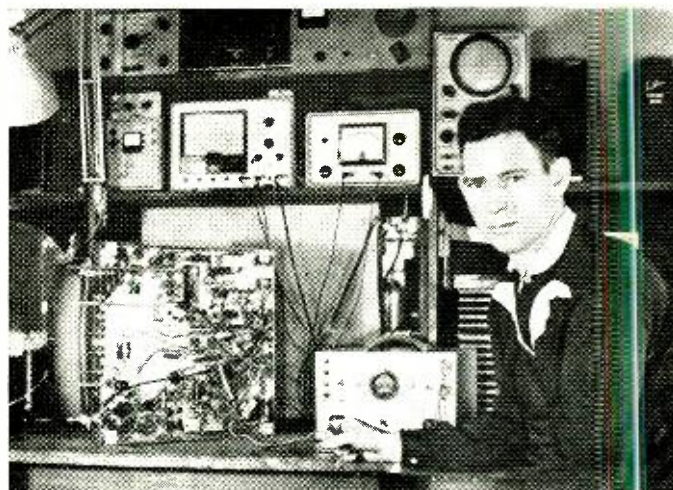

Technician using the surge supply for testing intermittent in a television receiver.

INTERMITTENTS! Please, don't mention that nasty word around the shop. They may make life interesting for the technician but they certainly do not add to his income unless he is equipped to handle them with speed, and too many of such time-consuming toughies can put a technician out of the service business for good.

One cannot delve into a tough electronic mystery with only bare hands and horse sense. These things help, but good equipment is also required. Unfortunately, many technicians are limited as to funds for purchase of all the equipment they may need. The equipment essential for working with intermittents with any degree of success is:

Tube checker While a mutual conductance checker is preferred, a simple emission job is useful and costs less. Since the best tester we can buy will not reveal some tube defects and we must as a last resort try substitution, most any simple checker will do. For field service, its speed of operation, ruggedness and portability are the most important considerations.

Volt-ohm-milliammeter This instrument should be accurate, portable, rugged and dependable. Many good ones are now on the market at reasonable prices.

Variable-voltage isolation transformer This piece of equipment should vary the line voltage between 0-150 volts. The transformer should handle at least 7.5 amps continuously. If a voltmeter is not built in, provide one externally for monitoring the output.

Vacuum-tube voltmeter

Oscilloscope

Signal generator One that will cover

the operating frequencies of the equipment under test. For most checking on intermittents, tests are made using the regular channels rather than the output from the signal generator.

Source of variable dc voltage For making surge tests and breakdown tests on capacitors, resistors and transformers. This piece of equipment (see "Surge Supply for Intermittents," December, 1956, page 58) can be made out of junkbox parts.

Resistance-capacitance bridge This piece of equipment is highly recommended because of the excellent leakage checks provided that will reveal hidden sources of trouble. Since capacitors are among the worst offenders when it comes to causing intermittent operation, checking them accurately is important. And to avoid trouble with repair jobs, every replacement should be carefully checked before it is put into use.

Heat lamp This unit should be portable and have an aluminum reflector.

A heat bulb may be inserted in a photographic reflector equipped with a hand clamp. The lamp is used to raise the working temperature of suspected parts. Heat must always be applied carefully to avoid damage.

Hot box for cooking a chassis The box is simply four pieces of plywood $\frac{3}{8}$ inch thick and about 30 inches square. It can be assembled over the chassis to form a box with the bottom and front open. The boards may be held together with small pieces of angle iron and some wood screws so that the assembly may be dismantled and folded flat for easy storage when not in use. The plywood should be covered on one side with sheet asbestos which may be attached with ordinary wallpaper paste. Cover the front with a piece of canvas or an old blanket. Mount a thermometer through a hole in the top board to show the inside temperature and you are ready for business. Because of fire hazard, a chassis must be watched constantly while cooking. Always keep a fire extinguisher handy.

A bar generator, audio oscillator, grid dip meter, resistance and capacitance substitution boxes, picture-tube reactivator and checker, and a signal tracer are all useful in checking intermittents. Several potentiometers mounted on a board with test leads attached are also useful. Equipment built from kits is adequate for most jobs. The saving in cost is certainly worth while.

A large percentage of service calls involve only tube replacement. Ordinary tube troubles like shorts, open filaments or heaters, weak emission, gas and breakage show up immediately.

(Continued on page 100)





newest knight-kits[®] . . . years-ahead
A PRODUCT OF ALLIED RADIO



incomparable **knight-kit** stereo hi-fi saves you up to 50%

DELUXE 40-WATT STEREO AMPLIFIER KIT

Y-774D

\$79⁵⁰

\$5 Down

Finest hi-fi stereo amplifier you can buy in money-saving kit form. Features special full-frequency range, extra center-channel output for 3-speaker systems. Dual built-in equalized preamps accommodate every existing sound source; exceptional control versatility, including single knob channel balance and separate dual concentric tone controls for each channel. Outputs for stereo tape recording. Exclusive printed circuit switches and plug-in units for easy assembly. Custom-styled in Cordovan gray vinyl plastic bonded to steel; Desert Beige and Sand Gold extruded solid aluminum escutcheon; 4 1/8 x 15 1/2 x 11 1/4". Shpg. wt. 24 lbs.

Model Y-774D. 40-Watt Stereo Amplifier Kit.

**\$5
DOWN**

DELUXE STEREO FM-AM TUNER KIT

Y-731D

\$87⁵⁰


\$5 Down

Distinguished for quality and styling, years-ahead in features. Has completely independent FM and AM sections, each with moving-bar "magic eye" tuning indicator. Only tuner kit with Dynamic Sideband Regulation (DSR) on FM for purest, distortion-free reception. Sectionalized construction permits easy addition of "built-in" multiplex. Has 2 1/2 μV sensitivity. Double limiter-discriminator FM circuits—adjustable AFC. Separate cathode-follower outputs on FM and AM with level set controls. Precisely aligned RF and IF transformers in FM section. Printed circuit boards for fastest, easiest assembly. Styling matches the 40-watt amplifier; 4 1/8 x 15 1/2 x 12". Shpg. wt., 18 lbs.

Model Y-731D. Stereo FM-AM Tuner Kit.

**\$5
DOWN**

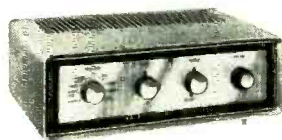
there is a money-saving **knight-kit** for every hi-fi need



20-Watt Stereo Amplifier

Truly a super-value. Built-in equalized preamps; single-knob selector switch for control convenience; dual concentric, clutch-type level control. 17 lbs.

Y-773D. \$2 Down. Only **\$44⁵⁰**

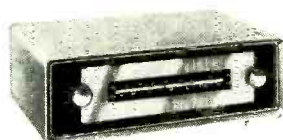

FM-AM Hi-Fi Tuner Kit

Amazing buy, featuring: Tuned RF stage; high sensitivity; AFC; flywheel tuning; pre-aligned IF and RF coils; cathode follower output. Truly great value. 14 lbs.

Y-787D. \$2 Down. Only **\$49⁹⁵**



18-Watt Hi-Fi Amplifier Kit

A brilliant performer at unbelievable savings. 18 watts at only 0.5% distortion; RCA 6973 audio output tubes; 8 inputs; 7 record equalization settings. 15 lbs.

Y-797D. \$2 Down. Only **\$39⁹⁵**

SEE THEM ALL
 See the impressive selection of Hi-Fi Knight-Kits (including speaker systems) in the money-saving 1960 ALLIED Catalog. If you haven't a copy, send for it today.

FREE



ONLY \$5 DOWN (OR LESS) on orders up to \$200; up to 24 months to pay. Fast handling—no red tape—take advantage of these easiest-pay terms...

for you who want to build the very best for less...



IDEAL FOR HOME,
AUTO OR BOAT



all-new *knight-kit* citizens band transceivers... 2-way radio everyone can afford

CITIZENS BAND SUPERHET TRANSCEIVER KIT

Y-712D
\$79⁹⁵
 \$5 Down

A high-sensitivity do-it-yourself transceiver for efficient, economical 2-way radiotelephone communication. Any citizen, 18 or older, can get a license—no exam required. For mobile or stationary use. Covers up to 20 miles, depending on antenna height and terrain. Works just like an intercom, with talk-listen operation. Receiver is sensitive superhet; tunes all channels continuously. 5-watt transmitter section. Built-in AC power supply. With transmitting crystal (available for any channel from 1 to 22—specify preference) and doublet antenna. Extras available: Y-723, 6-12 v. DC power supply, \$10.95; Y-729 vertical antenna, \$6.50; Y-714 mobile mounting bracket, \$5.35. Distinctive high-impact styrene case; 5 x 12 x 12". Shpg. wt., 20 lbs.

Model Y-712D. Superhet Transceiver Kit.

**\$5
DOWN**

CITIZENS BAND TRANSCEIVER KIT

Y-713D
\$39⁹⁵
 \$2 Down

Low-cost super-regenerative receiver and 5-watt transmitter kit. Readily fits car, boat or desk. Simple, one-switch operation permits talk or listen. Receiver tunes all 22 channels continuously. Built-in AC power supply. With mike, transmitting crystal—specify channel (1 to 22) if you have a preference—and doublet antenna. Handsomely styled case; 6 x 10 x 8". Designed for easy assembly and dependable operation. Available extras: Y-723, 6-12 v. DC power supply, \$10.95; Y-729 vertical antenna, \$6.50; Y-724 mobile mounting bracket, \$5.35. Shpg. wt., 10 lbs.

Model Y-713D. Transceiver Kit.


**\$2
DOWN**

dozens of exciting hobbyist kits available




"Span Master" 4-Band Radio Kit
 Famous for world-wide short-wave and broadcast reception. True band-switching; continuous 4-band coverage from Broadcast to 30 mc. Sensitive regenerative circuit; 4" PM speaker. With cabinet. 8 lbs.

Y-258D. \$2 Down. Only..... **\$25⁹⁵**

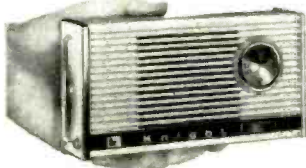

5-Transistor Portable Radio Kit
 Popular, low-cost personal portable. Fun to build; superhet circuit; only 22 ounces; big 3 1/2" speaker; built-in ferrite loopstick; phone jack. (Less battery, \$1.30.) 2 lbs.


Y-771D. \$2 Down. Only..... **\$25⁹⁵**

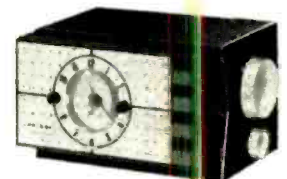

"Ranger" Clock-Radio Kit
 Easiest superhet of all to build—plug-in modules and printed circuit board eliminate small parts assembly. Excellent AM broadcast reception. Telechron clock has "sleep" switch. With appliance outlet. 6 lbs.

Y-737D. \$2 Down. Only..... **\$24⁹⁵**

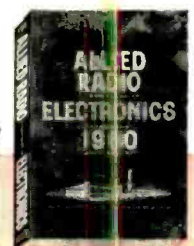SEE THEM ALL: Knight-Kits offer the most exciting hobbyist kits available. See the complete selection in the 1960 ALLIED Catalog. Write for it now—use coupon on page following.



FREE

manufactured and sold exclusively by **ALLIED RADIO** 100 N. WESTERN AVE., CHICAGO 80, ILL.

www.americanradiohistory.com



newest knight-kits® ... years-ahead
A PRODUCT OF ALLIED RADIO



knight-kits break through the professional instrument price barrier

5" LAB DC SCOPE KIT WITH IVA

Y-611D For the first time in easy-to-build kit form—a triggered sweep DC precision quality lab scope with plug-in **interchangeable vertical amplifiers (IVA)**. Brilliantly engineered with an impressive array of professional features, including: crystal-controlled timing markers; DC amplifiers in both horizontal and vertical channels; electronically regulated power supply; sweep timing adjustable to 1%; built-in voltage regulated peak-to-peak calibrator. Three interchangeable vertical preamplifiers are available: high-gain differential, \$35.95; wide-band (to 10 mc), \$24.95; dual-trace, \$48.95. **There is no other instrument like this in kit form**—here is laboratory precision quality and reliability at far less than the cost of any comparable factory-built unit. Shpg. wt. 50 lbs.

Model Y-611D. Lab DC Scope Kit.

\$285⁰⁰
(less preamps)

\$10
DOWN

LAB AUTOMATIC AC VTVM KIT

Y-608D A major achievement in instrumentation! This all-new AC VTVM features **automatic range selection**—by means of an electronically-actuated self-seeking mechanism which **automatically** selects the proper range when you touch probes to the circuit under examination. Simultaneously, a front panel light indicates the range in use. Covers 11 ranges from 3 millivolts to 300 volts full scale; frequency response to 2.5 mc. Reads as low as 100 μ v. Highly stable 3-stage amplifier has cathode follower output; ideal for use as preamp for other test equipment or for connection to scope for simultaneous wave form observation. Includes precise trigger circuits; regulated power supply; latest printed circuitry for easy assembly and quality performance. An exclusive Knight-Kit development—there is no other instrument like it on the market, in any form or at any cost.

Shpg. wt. 13½ lbs.
Model Y-608D. AC VTVM Kit.


\$99⁵⁰
\$5 Down

\$5
DOWN

save on every instrument need with **knight-kits** ... best by design



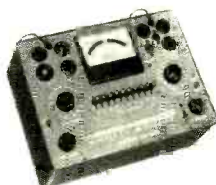Famous-Value VTVM Kit
Measures DC voltage (11 meg. input) and resistance; AC voltage, rms and peak-to-peak. 4½" meter. Push-pull balanced bridge circuit. 7 lbs.
Y-125D. \$2 Down. Only **\$25⁷⁵**



Deluxe Tube Checker Kit
Checks over 700 receiving type tubes. 16 filament voltages. Tests cathode emission as well as shorts, open elements, etc. 15 lbs.
Y-143D. \$2 Down. Only **\$32⁹⁵**



5" Wide-Band Scope Kit
Top versatility. 5 mc bandwidth; DC coupled p-p output amplifiers; 25 mv/inch vertical amplifier sensitivity. Outstanding value. 29 lbs.
Y-144D. \$5 Down. Only **\$65⁷⁵**

SEE THEM ALL
You'll find dozens of other fine quality Knight-Kit instrument values fully described in the 1960 ALLIED Catalog. If you haven't a copy, write for it now—use coupon on opposite page.

FREE send for the value-packed 1960 ALLIED CATALOG

www.americanradiohistory.com



electronic achievements at half the factory-built cost



years-ahead *knight-kit* amateur gear

T-400 AMATEUR 400-WATT TRANSMITTER KIT


Y-716D
\$395⁰⁰
 400-Watt CW
 Transmitter

Truly the "dream" transmitter—has what it takes to punch out a QRM-busting SSB, AM, or CW signal. 600 watts P.E.P. input on SSB; 400 watts on AM and CW. Covers 80, 40, 20, 10, and 15 or 6 meter bands. Start with the basic CW kit— then add AM and SSB accessory units and other "add-ins" whenever you wish. Has heterodyne VFO to assure a signal which "stays put." Tremendous 14" dial is precision-calibrated for all bands, 80 through 6 meters. SSB features: front panel controls—VOX, anti-trip and adjustable speech compression. Smooth, chirpless screen-clamp keying, plus VFO keying for complete CW break-in. Has 7034/4X150A final—coasts along well within its CCS ratings; silicon rectifier power supply runs cool. Dozens of advanced features put this job in a class all its own. Shpg. wt. 140 lbs.

Model Y-715D. T-400 CW Transmitter Kit.

\$10
 DOWN

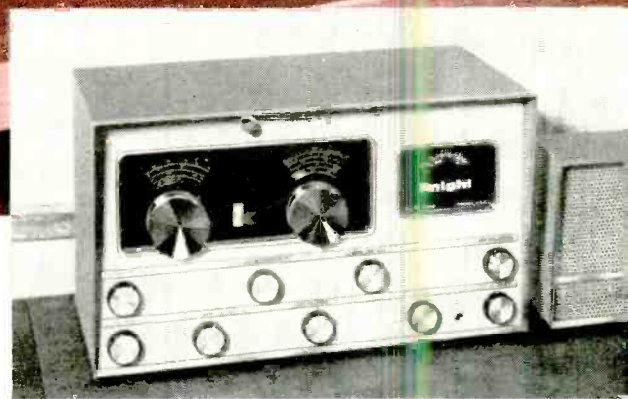"Add-In" Accessories: SSB Generator Kit, \$69.95 • AM Modulator Kit, \$24.95 • Speech Amplifier Kit, \$9.95 • Monitor Scope Kit, \$37.95 • 6-Meter Conversion Kit, \$7.50.



R-100 AMATEUR RECEIVER KIT

Y-726D
\$104⁵⁰
 \$5 Down

Incomparable receiver kit with all the features, selectivity and sensitivity of high-priced commercial units. Tunes 540 kc to 30 mc in 4 bands; calibrated bandspread on all Ham bands; 300 cps to 4.5 kc selectivity; exclusive printed-circuit bandswitch; built-in Q-multiplier; constant-running HFO—dozens of other professional features. Truly superior kit value. 30 lbs.

Model Y-726D. R-100 Receiver Kit. **\$5** DOWN


Y-727D. S-Meter Kit for above, only..... \$10.75
 Y-728D. 4" Matching Speaker, only..... 7.50

FREE Send for the 1960
ALLIED CATALOG

Describes the complete KNIGHT-KIT line in detail—the leading Buying Guide for everything in Electronics. Send for your FREE copy. Use coupon at right.

**ALLIED
 RADIO**

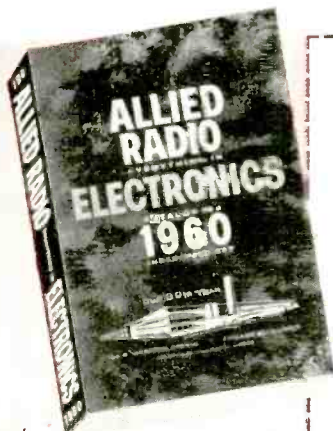pioneers in quality electronic kit development
 OUR 39th YEAR



ALLIED RADIO CORP., Dept. 132-C
 100 N. Western Ave., Chicago 80, Ill.

Ship me the following KNIGHT-KITS:

Quantity	Description	Model No.	Price


\$..... enclosed. (For parcel post include postage, express shipped collect)

Send **FREE 1960 ALLIED CATALOG**

Name.....

Address.....

City..... Zone..... State.....

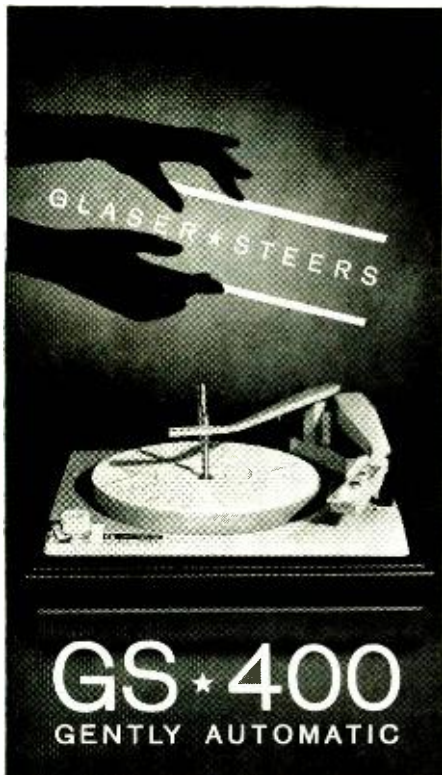

YOUR HIGH FIDELITY DEALER
IS NOW SHOWING THE NEW
GLASER-STEERS GS-400
THE GENTLY AUTOMATIC CHANGER
THAT PAMPERS
YOUR PRECIOUS RECORDS

Gently automatic, the new GS-400 handles your treasured records with utmost care preserving the brilliance of their original performance for many additional playings.

Gently automatic, it combines the finest record playing features with all the automatic conveniences of a record changer. The GS-400 draws upon the major engineering advances developed in the famous GS-77 to provide precise tracking of stereo and monophonic records and trouble-free operation for optimum performance.

The GS-400 in your high fidelity system, brings out the best in the other components and, at the same time, keeps the cost of the system in a moderate range. Attractive Holiday Grey changer with silver trim, white turntable pad. Less cartridge and base..... only \$47.50

GLASER-STEERS GS-77, World's only record changer with "Turntable Pause" and now the distinguished companion of the GS-400. Less cartridge and base..... only \$59.50 See and hear the GS-400 and GS-77 at your dealer today. For details write:

GLASER-STEERS CORPORATION
155 Oraton St., Newark 4, N. J.


GS-400 FEATURES — 4-speed automatic and manual operation: 16, 33, 45, 78 rpm • rumble, wow and flutter virtually inaudible • counter balanced, die-cast aluminum arm • damped acoustically isolated arm—shock suspension prevents mechanical feedback through arm pivot. Resonance is negligible • 4-pole, hum-shielded motor for smooth constant speed • full provision for 2, 3, or 4 terminal, stereo and mono cartridges • single-knob control sets all operations • double-channel muting switch and RC network maintains silence for both stereo channels • quick-change cartridge holder.

TELEVISION

(Continued from page 95)

The old tubes are thrown away and new ones installed—the customer is happy. The fun starts when the customer calls 2 hours later to inform us that we did not fix her set, we just made it worse. By the time we get back to look the situation over, everything is working like a charm. We turn the set off and it refuses to come back on again. That's the way it goes!

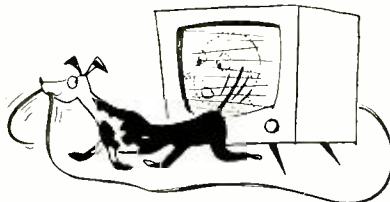Often a new rectifier tube will pep up plate voltages enough to cause a coupling capacitor to let go, and once the cycle has started there is no cure short of actually tracking down the defective part and replacing it. Meanwhile, the owner is unhappy about the whole deal and often unwilling to pay for any



extra labor or materials. Tact and a lot of careful explaining are necessary at this point, and here is where knowledge, experience and equipment will pay off.

The set is taken to the shop, and the tubes check OK. But are they really all good? No tube checker can give a final answer because there are some defects that do not show up on the best of tube checkers. The applied voltages and loads are different from those in the chassis. Pounding on the tubes while they are being checked often indicates loose elements; it can also break good tubes. And we may still overlook an intermittent. The fastest way to eliminate tubes completely as a source of trouble is to replace the whole set at one time, and then give the equipment a thorough check. If the trouble shows up after the usual waiting time, we can forget about tubes and start looking elsewhere.

A complete set of good used tubes should be kept on a rack above the workbench for use in checking doubtful sets. These tubes should be set-tested and all above reproach as far as noise, emission and overall performance can be determined. A very important point to remember when working with intermittents is: *never do anything haphazardly*. Always keep a record of every move so things can always be returned to the starting point in case the trouble has not been found.

External causes of trouble

Before pulling a chassis make sure that the trouble is not external. Many hours have been wasted slaving over a perfectly good chassis only to find later on that it was the antenna that was bad or the line voltage was way off. This check list may help to eliminate the external causes of trouble:

Antenna system

1. Check for loose elements, corrosion,

ONE CENT SALE

BUY ONE AT OUR REGULAR LOW PRICE
AND GET THE SECOND FOR ONLY 1¢ MORE

CITIZENS BAND TRANSMITTER (27 MC) chassis complete with crystal. \$12.49 each, two for \$12.50.

TRANSMITTER similar to above but with 5 watt RF stage instead of 1 watt. \$14.99 each, two for \$15.00.

CITIZENS BAND RECEIVER chassis turnable through all 22 channels. Complete with audio amplifier. \$9.99 ea., two for \$10.00.

AMATEUR BAND TRANSCIEVER (144-148 MC) chassis with dual VHF triodes for walkie-talkie radiophone. \$9.99 ea., two for \$10.00.

TRANSCIEVER TRANSFORMER: Mike to grid input and plate to low impedance headphone output. Good for telephone handsets. \$1.99 pair, two for \$2.00.

TELEPHONE HANDSETS with push-to-talk switch. \$5.99 each, two pair for \$6.00.

MICROPHONE High output 200 ohm carbon with terminal lugs. \$1.49 ea., two for \$1.50.

COILED CORD 4 conductor 11' telephone cord. Extends to over 4 ft. .99 ea., two for \$1.

KIT OF PARTS for AM-FM VHF radio receiver. Tunable from 80-200 mc, which includes U. S. satellite frequencies. \$6.99 ea., two for \$7.00.

TRANSISTOR AUDIO AMPLIFIER gives 50X voltage gain on low level signals. Operates on 1½ volts. \$3.99 ea., two for \$4.00.

CONVERTER (Crystal controlled) for 27 MC Citizens Band. Adapts any standard broadcast radio to 27 MC band. Tunes all 22 channels. Complete with tubes and crystal. \$14.99 each, 2 for \$15.00.


TRANSMITTER CRYSTALS in holders. Assorted frequencies for experimenters. Bag of 10 only \$1.49—two bags for \$1.50.

ALL MERCHANDISE GUARANTEED

LIMITED QUANTITY—
NO LITERATURE OR CATALOG

Remit in full. Include sufficient postage.
No C.O.D.'s.

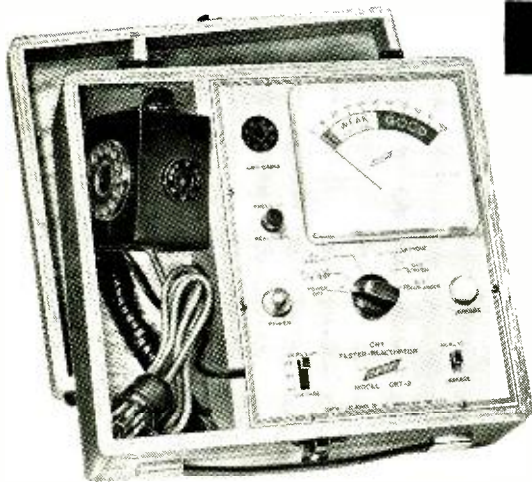VANGUARD ELECTRONIC LABS.
Box 12 RE-3 Hollis 23, N.Y.



Model
CRT-2

CRT TESTER-REACTIVATOR

TESTS, REPAIRS and REACTIVATES

- **ALL BLACK AND WHITE PICTURE TUBES** (including 110° tubes) . . . from 8" to 30", whether 12 pin base, 8 pin base, 14 pin base . . . and the very latest 7 pin base.
- **ALL COLOR PICTURE TUBES** . . . Each of the red, green and blue color guns is handled separately.

CHECK THESE EXCLUSIVE FEATURES

- ✓ **THE MULTI-HEAD** (Patent Pending) . . . A SINGLE PLUG IN CABLE AND UNIQUE TEST HEAD — A tremendous advance over the maze of cables and adapters generally found with other testers.
- ✓ **WATCH IT REACTIVATE THE PICTURE TUBE** — You actually see and control the reactivation directly on the meter as it takes place. This allows you for the first time to properly control the reactivation voltage and eliminates the danger of stripping the cathode of the oxide coating. It also enables you to see whether the build-up is lasting.
- ✓ **CONTROLLED "SHOT" WITH HIGHER VOLTAGE FOR BETTER REACTIVATION** — Stronger than any found in other testers — high enough to really do the job — yet controlled to avoid damage to the picture tube.
- ✓ **UNIQUE HIGH VOLTAGE PULSE CIRCUIT** — Will burn out inter-element shorts and weld open circuits with complete safety to the picture tube.

Housed in hand-rubbed oak carrying case — complete with MULTI-HEAD


Model CRT-2
\$57.50
Net

TERMS: \$13.50 within 10 days. Balance \$11 monthly for 4 months.

THE CRT-2 DOES ALL THIS RIGHT IN THE CARTON, OUT OF THE CARTON OR IN THE SET

- | | | |
|------------|---|--|
| TEST | } | • For quality of every black and white and color picture tube, employing the time proven dynamic cathode emission test principle. |
| | | • For inter-element shorts and leakage up to one megohm. Separate short test provided for each element in the picture tube. |
| | | • For life expectancy. |
| REPAIR | } | • Will clear inter-element shorts and leakage. |
| | | • Will weld open elements. |
| REACTIVATE | } | • The "SHOT" (high voltage controlled pulse) method of reactivation provided by the CRT-2 will restore picture tube to new life in instances where it was not possible before. The high voltage is applied without danger of stripping the cathode as you always have perfect control of the high voltage pulse. |
| | | • The "BOOST" method of reactivation also provided by the CRT-2 is used effectively on tubes with a superficially good picture but with poor emission and short life expectancy. It will also improve definition, contrast and focus greatly and add longer life to the picture tube. |
| | | |

- ✓ **VISUAL LIFE TEST** — Enables both you and your customer to see the life-expectancy of any picture tube right on the meter . . . helps eliminate resistance to picture tube replacement when necessary.
- ✓ **SPECIAL LOW SCREEN VOLTAGE TUBES** — Will handle new type picture tubes with special low voltage of approximately 50 volts.
- ✓ **SEPARATE FILAMENT VOLTAGES** — including the very latest 2.35 volt and 8.4 volt types as well as the older 6.3 volt types.
- ✓ **NEW '5F' PICTURE TUBES** — Accommodates the different base pin connections of this new type picture tube.

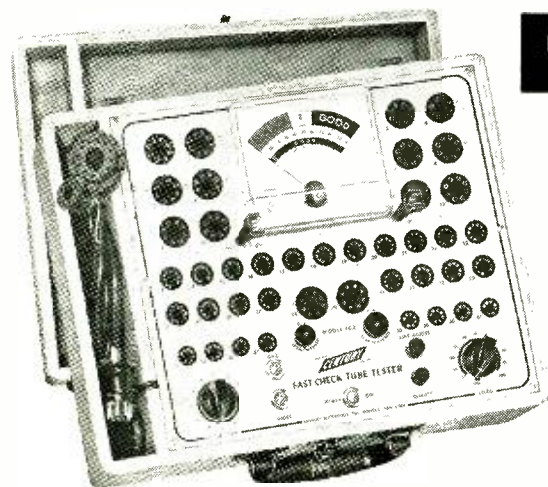

Model
FC-2

FAST-CHECK TUBE TESTER

Simply set two controls . . . insert tube . . . and press quality button to test any of over 900 tube types completely, accurately . . . IN JUST SECONDS!

The FAST-CHECK enables you to cut servicing time way down, eliminate unprofitable call-backs and increase your dollar earnings by selling more tubes with very little effort on your part. You make every call pay extra dividends by merely showing your customer the actual condition and life expectancy of the tube. The extra tubes you will sell each day will pay for the FAST-CHECK in a very short time.

PICTURE TUBE TEST ADAPTER INCLUDED WITH FAST-CHECK

Enables you to check all picture tubes (including the new short-neck 110 degree type) for cathode emission, shorts and life expectancy . . . also to rejuvenate weak picture tubes.

RANGE OF OPERATION

- ✓ Checks quality of over 900 tube types, employing the time proven dynamic cathode emission test. This covers more than 99% of all tubes in use today, including the newest series-string TV tubes, auto 12 plate-volt tubes, O24s, magic eye tubes, gas regulators, special purpose hi-fi tubes and even foreign tubes.
- ✓ Checks for inter-element shorts and leakage.
- ✓ Checks for gas content.
- ✓ Checks for life-expectancy.

SPECIFICATIONS

- No time consuming multiple switching . . . only two settings are required instead of banks of switches on conventional testers
- No annoying roll chart checking . . . tube chart listing over 900 tube types is located inside cover. New listings are added without costly roll chart replacement
- Checks each section of multi-section tubes and if only one section is defective the tube will read "Bad" on the meter scale
- 41 phosphor bronze beryllium tube sockets never need replacement
- 7-pin and 9-pin straighteners mounted on panel
- Large 4 1/2" D'Arsonval type meter is the most sensitive available, yet rugged — fully protected against accidental burn-out
- Special scale on meter for low current tubes
- Compensation for line voltage variation
- 12 filament positions
- Separate gas and short jewel indicators
- Line isolated — no shock hazards
- Deep brushed long lasting etched aluminum panel.

NOTE: The Fast-Check positively cannot become obsolete . . . circuitry is engineered to accommodate all future tube types as they come out. New tube listings are furnished periodically at no cost.

Housed in hand-rubbed oak carrying case complete with CRT ADAPTER

Model FC-2
\$69.50
Net

TERMS: \$14.50 within 10 days. Balance \$11 monthly for 5 months.

**MAIL
FREE
TRIAL
COUPON
TODAY!**

CENTURY ELECTRONICS CO., INC.

111 Roosevelt Ave., Dept. 103, Mineola, N. Y.

- | | | |
|--------------------------|--|---------|
| <input type="checkbox"/> | Model VT-10 Vacuum Tube Volt Meter | \$58.50 |
| | \$14.50 within 10 days. Balance \$11 monthly for 4 months. | |
| <input type="checkbox"/> | Model VT-1 Battery Vacuum Tube Volt Meter | \$58.50 |
| | \$14.50 within 10 days. Balance \$11 monthly for 4 months. | |
| <input type="checkbox"/> | Model CT-1 In-Circuit Condenser Tester | \$34.50 |
| | \$9.50 within 10 days. Balance \$5 monthly for 5 months. | |
| <input type="checkbox"/> | Model CRT-2 CRT Tester-Reactivator | \$57.50 |
| | \$13.50 within 10 days. Balance \$11 monthly for 4 months. | |
| <input type="checkbox"/> | Model FC-2 Fast-Check Tube Tester | \$69.50 |
| | \$14.50 within 10 days. Balance \$11 monthly for 5 months. | |
- Prices Net F.O.B. Mineola, N. Y.

Yes, I want to take advantage of your 10 day FREE try-before-you-buy offer. Ship on approval the instruments I have checked. After I have tried the equipment for 10 full days I will either send you the down payment and agree to pay the balance in the monthly payments shown, or I will return the units and owe nothing.

Name
Please print clearly
Address
City State

TELEVISION

(Continued from page 101)

- Cockroaches are an annoying source of trouble. They eat the insulation from wiring, remove the labels from parts and have been known literally to fill if transformer cans where they are electrocuted and can cause intermittent arcing. Since we do not want the things running loose in the shop, the chassis should be placed in a cardboard box and fumigated with a bug bomb. Close up the box for about 30-minutes after a thorough spraying.

Miscellaneous

- Excessive carbon (soot) in the air from a defective heating plant can cause intermittent arcing in the high-voltage section. The remedy is a thorough cleaning with solvent, and spraying with anticorona dope. Cleansing must be thorough to remove every trace of carbon. Dope must be allowed to dry thoroughly before the set is turned on, otherwise fire may occur. Excessive dust, tobacco smoke, lint or dirt can cause a similar condition.
- Check for acid fumes in air. A small radio was ruined because it was installed on a shelf over a battery charger and string of storage batteries. An unusual condition of this type should be noted and pointed out to the owner before any work is started. Damage from acids may be

impossible to correct, so usually the equipment must be junked. Fortunately, such locations are rare.

Internal troubles

Having climinated tubes and external causes as trouble sources, we may safely assume the trouble is confined to the chassis. An attempt should be made to classify and isolate the trouble. Intermittents can be classified according to the type of trouble, nature and duration of the cycle (if a definite time cycle is involved) and may be divided into two general groups:



- The group in which overall operation continues at approximately the normal level, but there is intermittent interference with picture or sound. The interference originates within the chassis and may consist of hash, noisy sound, lines in picture, pulling, distortion of either picture or sound, etc.

- The group in which operation of some portion of the circuit ceases momentarily and may be restored in any one of several ways. This group may be divided into two general classes:

- Those in which overall operation ceases.
- Those in which only one section goes dead. This may be: picture dead, sound dead, won't hold, etc.

Regardless of the nature of the intermittent, the routine checking procedure is pretty much the same. Obtain a manual covering the specific chassis involved and a wiring diagram. Checking without the circuit diagram is slower and more difficult.

Chassis check list

Overall mechanical check. Look for:

- Loose wires, poor insulation, broken wires.
- Rosin solder joints.
- Defective tube sockets.
- Broken or loose controls.
- Worn-out tuner mechanism.
- Loose parts.
- Burned resistors.
- Overheated transformers or chokes. (Check electrolytics for excessive current drain.)
- Fluid leakage from capacitors. (Disregard seepage or oil drippings; these are normal.)
- Signs of overheating, like blistered paint.
- Bad selenium rectifiers—check by sight and smell, and twist with the fingers to see if plates are loose.

Go over every inch of the chassis, literally, using a pair of long-nose pliers to move wires and parts around as the checking progresses. Many technicians fail on intermittents because they overlook the obvious. The trouble is probably literally staring you in the face—look in the right place and read the signs of burned paint and blackened resistors.


If a thorough mechanical check reveals nothing, proceed with an electrical check.

Overall electrical check

- Using the variable-voltage isolation transformer, check the lowest voltage at which operation is possible. Gradually raise the voltage, noting any effect on the intermittent condition. Allow the chassis to operate for some time at high line voltage to see if anything breaks down. During this period connect the oscilloscope to the point of greatest suspicion of trouble and look for any changes in waveform as input voltage is varied.
- If voltage changes seem to have little effect, assemble the hot box and allow the chassis to cook for an hour or so at a high temperature.
- Check chassis voltages from the data given in the service manual, using the vacuum-tube voltmeter.

Overloading and heat checks have to be made carefully to avoid damaging

THE EVOLUTION OF A FAMOUS TAPE RECORDER

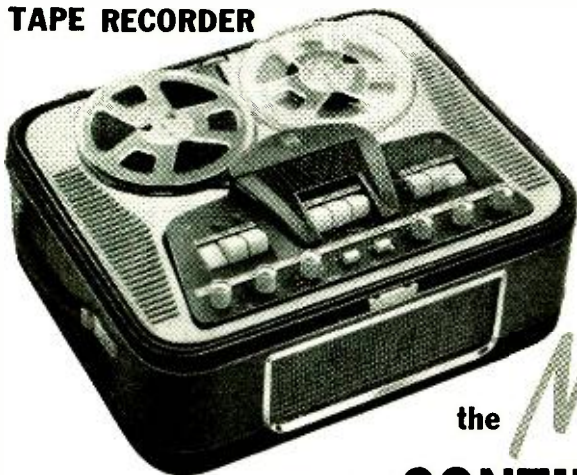

(MODEL EL 3536)
SPECIFICATIONS

- ◆ Four-track stereophonic or monophonic recording and playback
- ◆ Three tape speeds — 1 $\frac{1}{8}$, 3 $\frac{3}{4}$ and 7 $\frac{1}{2}$ ips
- ◆ Completely self-contained, including dual recording and playback preamplifiers, dual power amplifiers, two Norelco wide-range loudspeakers (second in lid) and stereo dynamic microphone (dual elements)
- ◆ Can also be used as a quality stereo hi-fi system with tuner or record player.

the *Norelco*[®]
CONTINENTAL
"400" a new
**4-track stereo-record/
stereo-playback
tape recorder**
guild-crafted for you by
Philips of the Netherlands

For additional descriptive literature write to:
North American Philips Co., Inc.
High Fidelity Products Division
230 Duffy Avenue
Hicksville, L. I., N. Y.



One Quality-One Line-THE BEST!

G-C Electronic Chemicals



G-C MAKES ALL THESE PRODUCTS FOR YOU! Not one special purpose item—or two or three . . . but a COMPLETE selection of thousands of products for the service trade. That's the G-C line, first choice with radio and TV servicemen for over 30 years. Always ask for G-C . . . the line you can always trust for quality, variety, economy.

G-C ZERO-MIST SPRA-KOAT No. 8667 Cools circuits instantly, saves hours locating intermittently defective components including capacitors, resistors and transistors. 16 oz. spray can.

Dealer Net \$2.17

NEW G-C RED-X HIGH VOLTAGE CORONA DOPE No. 50-2 Prevent corona shorts on high voltage circuits in TV sets. Used by many of the leading TV set manufacturers. Excellent high voltage insulating qualities. Easy to apply, air drying. 2 oz. bottle.

Dealer Net \$0.72

NEW



G-C RED-X HIGH VOLTAGE CORONA DOPE

Regular 99¢ Value
FREE!



6 oz. SPRA-KLEEN FREE!

When You Buy **ZERO-MIST**

Spra-Kleen . . . the finest TV Tuner Cleaner on the market made by the original manufacturers of electronic chemicals. Eliminates dust, dirt and corrosion the easy way.

FREE... DE-OX-ID
When You Buy
RED-X CORONA DOPE

De-Ox-Id . . . the miracle cleaner that prevents contact oxidation. A dependable and superior cleaner for all electronic contacts.



Regular 66¢ Value
FREE!



G-C ELECTRONICS CO.

Division of Textron Inc.

West Plant: Los Angeles 18, California • Main Plant: ROCKFORD, ILLINOIS, U.S.A.

GET THE FACTS ON ALL G-C

Chemicals and Cements, Alignment Tools, Service Aids, Hardware and all the rest. Send postcard for this free G-C Catalog!



ACT TODAY! CUT OUT AND TAKE TO YOUR JOBBER FOR FREE OFFER . . .

FREE G-C ELECTRONICS COUPON

YOU BUY 1 G-C Zero-Mist Spra-Koat No. 8667
Dealer Net \$2.17

YOU GET FREE 1 G-C Spra-Kleen Cleaner No. 8656 Worth 99¢
Finest TV Tuner Cleaner on the Market.

Coupon void if taxed, prohibited or restricted by law.
Cash value: 1/20th of 1¢. Offer Expires April 30, 1960.

G-C ELECTRONICS CO., Division of Textron Inc.
Los Angeles 18, California • Rockford, Illinois

FREE G-C ELECTRONICS COUPON

YOU BUY 1 G-C Red-X TV High Voltage
Corona Dope No. 50-2—Dealer Net \$0.72

YOU GET FREE 1 G-C De-Ox-Id No. 19-1 Worth 66¢

The Miracle Cleaner that prevents Contact Oxidation.

Coupon void if taxed, prohibited or restricted by law.
Cash value: 1/20th of 1¢. Offer Expires April 30, 1960.

G-C ELECTRONICS CO., Division of Textron Inc.
Los Angeles 18, California • Rockford, Illinois

ATLAS PAGING SPEAKER STYLED FOR MODERN DÉCORS


The New Atlas DU-12 Perfect for the Most Discriminating Applications. For the first time here's a loudspeaker that doesn't look like one. Modeled along the sleek, straight lines of a modern lighting fixture, and finished in brushed satin aluminum, the Atlas DU-12 is styled to harmonize and enhance the most ultra of modern décors.

Acoustically, the Atlas DU-12 offers high intelligibility, efficiency and directivity — features that mark it as a fine quality loudspeaker. The frequency response of the DU-12 is "tailored" to reproduce speech with clean, crisp articulation. Its horn type construction and universal mounting bracket provide complete directional control, confining the sound coverage to the required service areas. And, there's no wiring exposed to mar its appearance because all connections and line matching transformer are completely hidden behind the mounting canopy. Canopy is equipped with adapter strap for mounting on any flat surface or for use on standard electrical outlet box. In commercial installations where both décor and true acoustical quality are important, the Atlas DU-12 is the only answer. Investigate the profit opportunities for yourself. Write for information on the complete line of Atlas P.A. speakers, mike stands and accessories.



Décor-Projector DU-12

List \$35.00
Net \$21.00

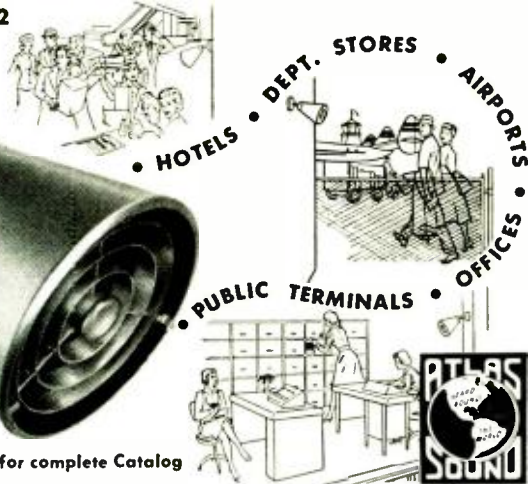

Write for complete Catalog

ATLAS Sound Corp.

Dept. RE3, 1449 39th Street, Brooklyn 18, N. Y.
In Canada: Atlas Radio Corp., Ltd., Toronto, Ont.

At Last!

The book with YOU in mind

FUNDAMENTALS OF ELECTRONICS

By E. NORMAN LURCH

State University of New York,
Farmingdale

Here's a brand new book aimed straight at you, if you're interested in all of electronics. Not just radio, not just TV, not just computers, but the whole vast field is covered. Armed with this material you're equipped to tackle any branch of electronics.

For instance, it covers tubes and transistors equally—they're both vital today. Tough ones like the decibel question get extra space. And there are many home study problems to help you along. Neither high school stuff nor heavy engineering, this book is paced just right for the man with a technician's know-how.

Published 1960, 631 pages, \$8.25

Check it out for 10 days—
FREE! WRITE

JOHN WILEY & SONS, Inc.
440 PARK AVE. SOUTH, NEW YORK 16, N.Y.



"I once took a JENSEN
NEEDLE out of his paw."

TELEVISION

good components. Generally speaking, if the chassis is either voltage or temperature sensitive, the effect can be spotted without going to extremes that would damage good parts. This is somewhat like pounding tubes with the screwdriver; they can be broken!

If overloading, high-temperature and voltage checks reveal nothing, other means must be used. If we can by this time pinpoint it to specific circuitry, well and good. Usually, this is difficult, and often impossible if the intermittent condition lasts only a few minutes at a time followed by hours of normal operation.

The really rough ones are often the cases where an oscillator refuses to start without an external shock and where the trouble is due to a case of stable circuitry so balanced that the oscillator does not get the initial "push" to start it off. Any disturbance such as touching the chassis, flipping the power switch rapidly, disconnecting the antenna or even flipping on a room light will start things going. No hard and fast rules can be set for repairing such cases and it may be a matter of trial-and-error substitution. Here is where the potentiometers with test leads attached come in handy. Circuit values can be shifted around until a point of reliable operation is found, and then the values can be measured and replaced with fixed resistors. *Changing circuit values is not for the beginner.* If you find it necessary to alter circuit values, make a little diagram showing what was changed and why the alterations were made. Attach it permanently to the chassis with tape.

Basic causes of intermittents

Tubes We can easily eliminate by substitution all the tubes at once as a source of trouble. There are of course many reasons why tubes cause an intermittent condition—poor welds, loose elements, parts almost touching internally, loose bases, defective heaters, etc. All these are sources of trouble we may not be able to check on a tube tester. *Substitution is the answer.*


Capacitors Capacitors may be either shorted, open or develop internal leakage which will unbalance other circuits. The basic function of a capacitor is to store an electrical charge. If the charge leaks off, the capacitor is like a bucket with a hole in the bottom.

Capacitors are used for filtering, coupling and time-delay networks. All of them show some leakage. If this condition increases with age they must be replaced. These conditions are often hard to check because of other circuit components which make checks for leakage impossible unless the capacitor is removed or special equipment used. Sometimes, it is quicker to discard the suspected ones than it is to try to salvage them by removal, checking and replacement. New replacements should be carefully tested for leakage and capacitance before being used. Surge

NEW

ORANGE-DROP®

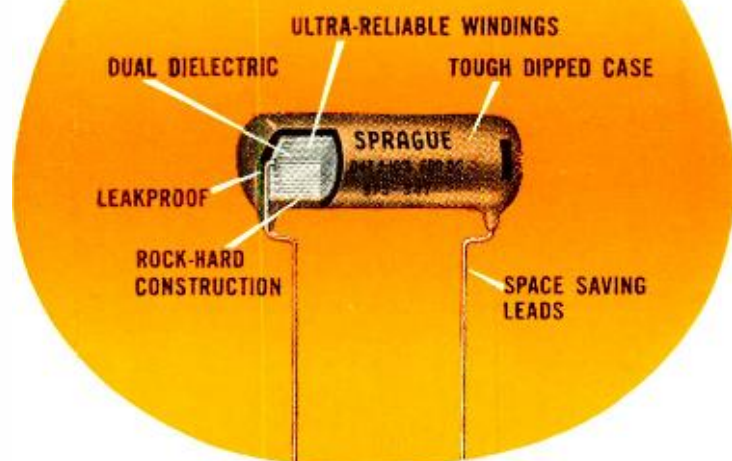DIPPED DIFILM® CAPACITORS FOR EXACT ORIGINAL REPLACEMENT



THIS NEW . . . MINIATURE . . . DIFILM
CAPACITOR OUTPERFORMS ALL
OTHER DIPPED TUBULAR CAPACITORS!

SPRAGUE DIFILM *does it again!* First to give you at regular prices the finest molded tubular capacitor made—the DIFILM BLACK BEAUTY . . . and now the newest DIFILM capacitor—the ORANGE-DROP dipped capacitor.

● SPRAGUE ORANGE-DROP CAPACITORS are especially made for easy installation in tight spots . . . where only an exact replacement will fit. They are the exact same dipped capacitors used by leading manufacturers in many TV sets.

WHY ORANGE-DROPS BEAT HEAT AND HUMIDITY

Sprague Orange-Drop Mylar-Paper Dipped Capacitors combine the proven long life of paper capacitors with the effective moisture resistance of film capacitors. Their duplex dielectric of kraft paper and polyester film is impregnated with HCX®, Sprague's exclusive hydrocarbon material which saturates the paper and fills voids and pinholes in the film before the HCX polymerizes. The result is a solid, rock-hard capacitor section which is then double-dipped in bright orange epoxy resin for moisture protection. Leads are neatly crimped for easy installation on printed wiring boards.

● SPRAGUE ORANGE-DROP CAPACITORS are a natural teammate for the molded Difilm Black Beauty®. Black Beauties, born out of engineering to tough missile standards, are still far and away the best replacement capacitors—better than any other molded or dipped . . . paper, film, or film-paper combination . . . capacitor made for entertainment electronics.

● Where a dipped capacitor is called for, no other dipped unit can match the ORANGE-DROP. Your distributor is stocked with all popular ratings in 200, 400, 600, and 1000 volts in handy Sprague Kleeer-Paks. Order some today.

*Du Pont Trademark


don't be vague—insist on

SPRAGUE® the mark of reliability

ANOTHER TESTED RELIABLE PRODUCT BY THE WORLD'S
LARGEST CAPACITOR MANUFACTURER

HANDLE THE TOUGH SERVICE JOBS

AS SLICK AS YOU DO THE EASY ONES...

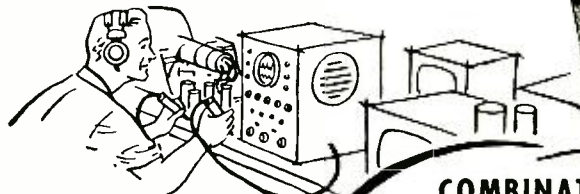

This famous Ghirardi Service Library shows you how to

HANDLE ANY JOB EASIER, BETTER and lots faster.



COMBINATION OFFER SAVE \$1.25

Almost 1500 pages of modern service training for only \$13.00
3 MONTHS TO PAY

These two giant how-to-do-it Ghirardi manuals make it easy for you to be an expert on all types of Radio-TV receiver service... at only a fraction of the price you might expect to pay. From tough realignment jobs to tracking down "intermittents"... from analyzing response curves to "static" and "dynamic" test procedures, these books explain every step clearly as A-B-C. They point out time-saving short cuts and help you work better, more profitably! Use coupon. Practice from them 10 days AT OUR RISK!

1 COMPLETE Professional TRAINING IN MODERN SERVICE METHODS

Radio and Television TROUBLESHOOTING AND REPAIR gets right down to earth in guiding you through each service procedure... from locating troubles quickly to fixing them fast and right.

For beginners, this famous 822-page book is an absolutely complete training course in professional methods. For experienced servicemen, it is the ideal way to develop better troubleshooting methods and shortcuts, to find quick answers to puzzling problems and to handle tough jobs faster.

Block diagrams, oscilloscope patterns, response curves and other features speed your work... make each step doubly clear. Handy troubleshoot-

ing charts cover practically every type of job from troubleshooting television to AM and FM realignment. IF and Detector sections, car radios and many more.

Here are a few of the subjects covered in Radio and TV Troubleshooting and Repair: Component Troubles; Basic Troubleshooting Methods; Shortcuts, Tips and Ideas; Complete Guide to TV Service; Realignment Made Easy; FM, Communications Receivers, Record Players, etc.; Auto Radios; Loudspeakers; Tuner and Switching Mechanisms; and dozens more. 417 clear illustrations. Price only \$7.50 separately. See MONEY-SAVING OFFER in coupon.

2 Learn all about circuits... AND WATCH SERVICE HEADACHES DISAPPEAR!

You can repair any radio or TV set... even special electronic equipment far better and faster when you know all about its circuits! That's where this 669-page Radio & TV CIRCUITRY AND OPERATION is worth its weight in gold.

You locate troubles in far less time... because circuitry "know-how" teaches you exactly what to look for and where. You make repairs better and faster... because you eliminate useless testing and guesswork.

Radio & TV CIRCUITRY AND OPERATION deals fully with practically every circuit and circuit variation used in modern receivers. It teaches you their peculiarities and likely trouble spots.

Over 110 pages explain Television... from scanning to signal to every circuit detail of each of the receiver sections.

Includes: AM... FM... R-F Amplifiers and TRF... AM Superhets... AM Detector and AVC Systems... A-F Amplifiers... Speakers... Power Supplies... Television... Antenna Systems... Pickups and Record Players... Changers... Mechanical Construction of Receivers... and lots more.

Throughout, this great book equips you with the kind of above-average service training that really pays off! Price only \$6.75... or see MONEY-SAVING OFFER in coupon.

PRACTICE 10 DAYS FREE!

Dept. RE-30, RINEHART AND COMPANY, 232 Madison Ave., NEW YORK 16, N. Y. Send books checked for 10-DAY FREE EXAMINATION. In 10 days, I will either remit price indicated (plus postage) or return books postpaid and owe you nothing. (NOTE: Send cash with order and we pay postage. Same 10-day return privilege with money promptly refunded.)

MONEY-SAVING COMBINATION

Both books only \$13.00... you save \$1.25. Payable at rate of \$4 (plus postage) after 10 days and \$3 a month thereafter until \$13.00 has been paid.

- Radio & TV Troubleshooting and Repair (\$7.50)
- Radio & TV Circuitry and Operation (\$6.75)

Name _____

Address _____

City, Zone, State _____

OUTSIDE U.S.A.—\$8.00 for TROUBLESHOOTING AND REPAIR; \$7.25 for CIRCUITRY AND OPERATION; \$14.00 for both. Cash with order only. Money refunded if you return books in 10 days.

TELEVISION

checking often reveals defects that would otherwise never show up.

Resistors They may be open or they may change in value with age or temperature. They may increase in value rapidly under load. Unless they are temperature-sensitive Global resistors we want them to remain constant in value. Permanent changes in value can be checked, but the intermittents may check OK cold and open up under load. Some technicians like to check them by temporary overloading. A resistor may be safely overloaded to the point where the paint just starts to blister, but if carried too far such overloading can cause permanent damage. If a resistor is consistently running too warm in a circuit, either it is too small in wattage or some tube or capacitor is passing an excessive amount of current and this is overloading the resistor.

Transformers, chokes, yoke The usual troubles are open or shorted windings. Turns may be intermittently shorted, and this condition is hard to detect. There is an obvious tendency to replace a transformer only as a last resort. Substitution is often the only final answer, but surge checking will frequently show up defects impossible to locate otherwise. To apply a voltage surge, we need only a charged capacitor which is discharged through the transformer winding. Capacitor size and charging voltage depend on the size and type of coil being tested, and the amount of overload that can be safely applied. For small outputs—if, and if coils—about 2 μ f provides a sufficient surge to detect intermittents without danger of damage to the windings. For power transformers, chokes and deflection coils, use a 16- μ f capacitor or larger and charge to 300 volts or more. Chokes can be overloaded to the point where the wax starts to melt, provided the overload is removed before the wax actually runs out. Usually an increase of 50% in operating voltage will provide sufficient overload to cause the most obstinate intermittent condition to break down. Additional overloading will only damage good components.

The wise technician will use every method and means at his disposal when tracking down an intermittent. Overloading, heat, pounding, tube substitution, surge checking, careful inspection and a little horsesense are all of value. A final hint for quick and accurate circuit tracing: Using the wiring diagram, take a red or blue pencil and draw a line through each circuit as it is checked or make a check mark at the symbol of each component as it is tested on the chassis. Get a bottle of colored lacquer and a small brush. A nail polish bottle is most convenient. Mark each part as it is tested with a little daub of paint. You can tell when the job is finished, and you will not only save time involved in haphazardly checking some parts two or three times, but will also avoid overlooking the one part that is causing all the trouble. **END**



How to RETOUCH REPAIR REFINISH



*Part I—Burns,
scratches, gouges and
other imperfections
in the finish of a
cabinet can be
removed or hidden.
And the work is
profitable*

By JEFF MARKELL*

PERHAPS you have a good old TV, radio or hi-fi cabinet that you'd like to hang on to. But time has taken its toll and the finish has become rather shabby. Or perhaps you are in the servicing field and get requests from customers to touch up battered cabinets while the insides are in for repair. In either case, you can do a great deal to brighten up a dull, beatup cabinet.

If you are in the servicing business, you doubtless already know what a boon to customer relations even a coat of polish on a cabinet can be. If you haven't tried this simple approach, try it for a while to see if it isn't worth instituting as a standard procedure.

You can give it a fancy name and call it applied psychology if you please, but when a customer gets back a unit that looks better than when she sent it out for repairs, she is likely to think that it plays a great deal better too. And you then have a customer who swears by your work for reasons that have nothing to do with electronics.

If cabinet work goes beyond a routine rubdown and polish, you should charge the customer for it and the matter should be taken up with her before you start. If you see obvious defects or injuries that can be repaired, point them out to the customer when the job first comes in. Suggest that they be attended to while the unit is in for repair. In this way, you can add dollars to your repair billings and build customer satisfaction with the lady of the house at the same time.

If you are tied up with strictly elec-

tronic work and can't spare the time for cabinet repairs, make a deal with a local cabinetmaker. In return for the steady volume of business you can provide, he should be willing to give you prices that will let you make a dollar or two on the cabinet work. And you can guarantee professional quality.

Whether you collaborate with a cabinet man or do the work yourself, you still have to know what to look for and what can be done to deal with your customer intelligently. Let's investigate the kinds of defects most often encountered and what can be done about them.

It helps to break down the common types of cabinet defects into two categories. The first consists of various types of injuries resulting from use, wear and tear or transit damage. While such injuries are occasionally serious enough to warrant discarding the entire cabinet, they are usually relatively minor and rather simple to correct. The second category of defects is made up of breakdowns or failures in the cabinet resulting either from old age or construction or finishing methods that were not what they might have been from the start. These will be detailed next month.

Burns are easy

One of the commonest cabinet injuries is burns. About 99% appear on the cabinet tops, and about 98% are cigarette burns. The ones along the edges of the tops are the result of someone's parking a lighted cigarette. The ones in the middle of the top are spots where a lighted cigarette fell off an ashtray.

Burns are easy to detect. They pretty much shout at you. Their size ranges from a very small discolored spot to a large blackened area a couple of inches long and half an inch wide. The size is your tip to how difficult it will be to repair. A large-area burn is generally a deep one. Though it may appear to be superficial, wait until you start scraping away the charred material. You may have to go a lot deeper than you thought to get all the scorched wood out.

There are two ways to treat a burn, but for either one the first step is the same—scraping. All charred material, both finish and wood, must be removed. Do the rough work with a sharp knife—a paring knife with a curved blade, a jack knife or a curved Exacto knife is good.

When you have removed all the burned finish and scraped out all the blackened wood, smooth off the spot

A word of caution to those who have never before attempted to repair or retouch furniture finishes. This type of work is not arduous or heavy labor, but it does require a bit of skill or, if you will, "feel" that can be acquired only with practice. For example, it takes a few tries before you'll get the feel of how much pressure to apply when French polishing or how long to heat the knife when burning-in. Therefore, before you try your first job for bacon, you ought to practice on an old discarded cabinet or table to get used to the materials and methods. The chances are that your first solder joint wasn't perfect either.

*Markell Associates, Cabinet Design and Construction.

TELEVISION

with very fine sandpaper, 2/0 to 4/0, and stain it to match the surrounding area.

French polishing

Now you have to decide which way to retouch, the decision depends on how deep a hole you have in the surface after scraping. If the depth of the scraped-out spot is $\frac{1}{8}$ inch or less, use a method known as French polishing. Make a small pad of cheesecloth or gauze about $1\frac{1}{2}$ inches square and about 20 layers thick. Wet the pad with white shellac and squeeze out the excess so the pad is soggy but not dripping. Then pull up the four corners in your fingers to make a round ended pad, and apply 3 or 4 drops of linseed oil to the rounded portion. With a brisk motion, rub the shellac into the affected area. At first, apply very little pressure. After a few seconds, the shellac will start to harden and you can apply more pressure—about what you would use to polish hard wax. Keep repeating this process, working shellac into the burned area and around the edges until you have built it up level with the rest of the top. When you are finished, the spot you have been doctoring will be glossy. If the rest of the piece is satin finished, dull the repaired spot down with extremely fine steel wool, 4/0 sandpaper or pumice.


Burning in

French polishing is fine for a shallow burn, but what do you do if you have a deep one? More than $\frac{1}{8}$ inch. Again it's easy. After the burned area has been scraped out, sanded and stained to match the surrounding color, you use a technique called burning in. For this you need an alcohol lamp, a small flexible spatula (a light, springy artist's palette knife is excellent) and a shellac stick either transparent or a color that matches the piece being repaired.

Heat the palette knife over the alcohol lamp. Touch the heated knife to the shellac stick and melt a small amount of material from it. Place it in the hole to be filled. Repeat the process, filling the hole a little at a time until it is level with the surrounding area. Do not overheat the knife or the shellac will burn, creating carbon that will smudge the repair. You need only enough heat to melt a little of the shellac stick at a time. When the hole is filled, use the heated knife to smooth the surface around the edges. Again be careful not to overheat the knife or it will blister the surrounding finish. Complete your smoothing operation by sanding lightly with the finest possible paper, about 4/0, and top off with French polish or rub with steel wool or pumice, to make the repair conform with the surrounding texture.

Water and beverage stains

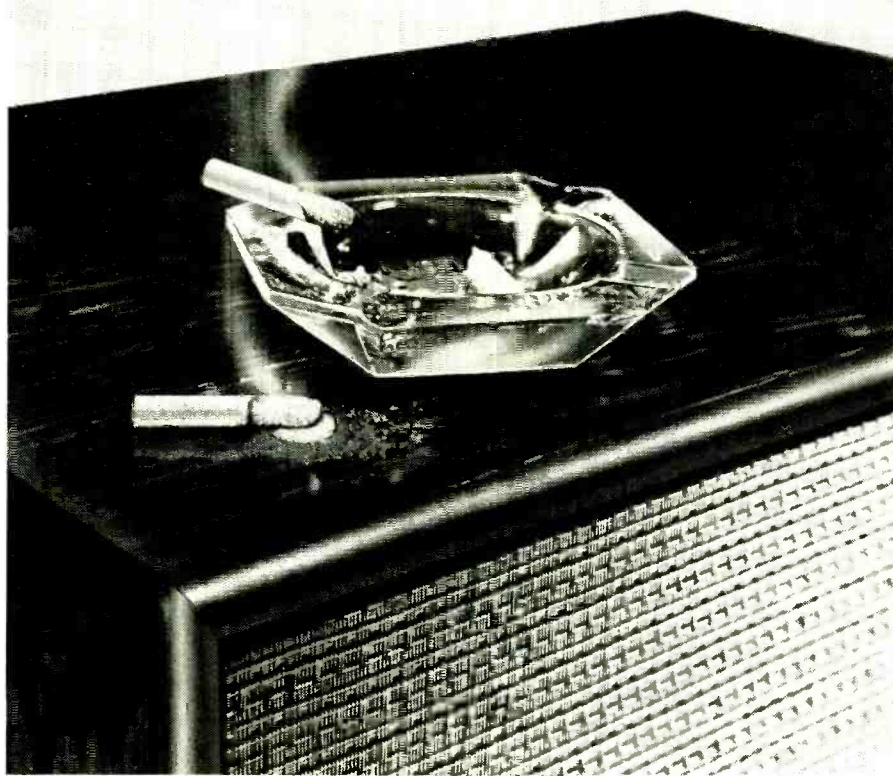Opaque or semi-opaque milky areas on cabinet tops are usually water or beverage stains. They may be in the



Cigarette burns are the most common type of cabinet damage.

Illustrations Gernsback Library

The ring left by glass standing on the top of a cabinet is easy to remove—if you know how.




form of rings left by the bottoms of wet glasses, or irregularly shaped areas caused by spilled beverages that were allowed to stand.

There are two ways to remove these annoying white spots. One is by rubbing them out, and the other is by chemical

action. Since such spots do not generally penetrate clear through the finish, try rubbing them out first.

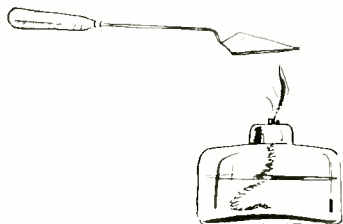On a dull finish, use very fine steel wool and oil. On a semi-gloss finish, use pumice; on a high-gloss finish, rottenstone. Merely rub the spot with the



For burning-in, you will need an alcohol lamp and a spatula as well as some shellac sticks.

appropriate abrasive until it disappears.

If rubbing doesn't seem to affect the spot much, switch to a chemical treatment, since you've apparently got a spot that goes fairly deep. The trouble with chemical methods is that if the chemicals are too strong or are left on too long they'll take the finish off the area entirely, so you have to be very careful.

One method is to use ammonia. Dampen a soft rag or cheesecloth with ammonia, then wring the pad out as hard as you can. Now, very gently, quickly and lightly, brush the ammonia across the white spot. For bad white spots on lacquer finishes, do the same thing with lacquer thinner. I cannot caution you too strongly to work quickly and lightly, lest you take all the finish off along with the spot. If this happens, you've a job of French polishing on your hands.

Scratches

Little ones, big ones or both, you will find scratches on every used piece of furniture. The primary trouble with the appearance of an old cabinet is often a myriad of little scratches which give it a terribly dull, defeated-looking appearance. Most of them can be compounded out both easily and rapidly. This is where you might get a life-long customer by expending just a little effort.

Most scratches can be removed by rubbing with 4/0 steel wool, pumice, rottenstone and oil, furniture rubbing compound, or even automobile rubbing compound, depending on the amount of gloss desired in the final result.

When you do a routine good-will type of polishing job, don't try to get all the scratches out. You'll get most of them out with a brief rubdown with the proper abrasive, and this way you get the effect you want—appreciably brightening the appearance of the cabinet without going to a lot of work and expense.

For a dull satin finish, use the steel wool. On a semi-gloss, use pumice and oil or pumice and water. For a high gloss finish, use furniture rubbing compound. If you can't find any, use automobile rubbing compound. It's just about the same. In the unlikely event that you cannot find either one locally, use rottenstone and oil. The high gloss is, of course, the most exacting finish

to clean up because it shows finer scratches than either of the others. When you are through rubbing out the scratches, go over the whole piece with a good furniture polish to complete the job properly.

You'll often find that by rubbing only the top and applying furniture polish to the entire cabinet you will get the desired effect, since the largest proportion of scratches will be on the top.

Where you really want to get out all the scratches, and there are some deep or stubborn ones that do not respond to rubbing alone, try French polish and then rub out.

Nicks and gouges

There are dozens of ways in which a cabinet can be hit or scraped, nicked or gouged, either in transit or around the house. The simplest nicks require more labor to repair than scratches, and they can be big and deep enough to be impossible to repair completely. If they are really big, you can reduce the unsightliness considerably, but don't give anyone the idea that you are going to make them disappear entirely.

All deep depressions require the same treatment. The first step is to clear away all loose splinters and chipped finish in and around the area. Stain where restoration of color is required, and burn in with alcohol lamp, spatula and shellac stick as described previous-

IT'S THE NEW MARK II FROM WESTON:



an advanced new design for the
WORLD'S FINEST PORTABLE ANALYZER

Here's an all-new version of the famous WESTON MODEL 980 Volt-Ohm-Milliammeter . . . engineered to offer you

- **INCREASED RANGE.** High-voltage range has been extended to 4000 volts.
- **INCREASED SENSITIVITY.** D-C sensitivity of 20,000 ohms/volt; accuracy within 2% of full scale.
- **IMPROVED SHIELDING.** Cormag® mechanism assures positive magnetic shielding; housing shields against electrostatic interference.
- **GREATER RUGGEDNESS.** Spring-backed jewel movement resists shock, vibration; case is impact-resistant. Ohm-ranges are fuse-protected.
- **SIMPLIFIED CONTROL.** Single dial control for range and function switching.
- **NEW COMPACTNESS.** Size and weight are reduced for maximum convenience and portability.

Order from your local Weston distributor. For information, write to Daystrom-Weston, Sales Division, Newark 12, N. J. In Canada: Daystrom, Ltd., 840 Caledonia Rd., Toronto 19, Ont. Export: Daystrom Int'l., 100 Empire St., Newark 12, N. J.

WESTON

Instruments

WORLD LEADER IN MEASUREMENT AND CONTROL

MARCH, 1960


111

biggest sound

you ever heard from a bookshelf speaker

AUDAX CA-60

\$59.95 only **9" x 10 1/2" x 18"**

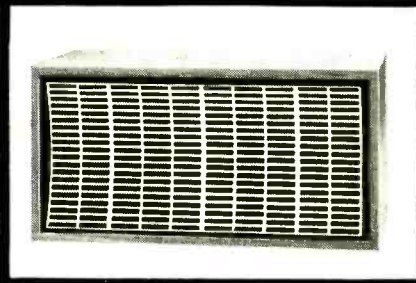

Among many individuals, there is a need to minimize on the space to be devoted to a component stereo system. A rash of "bookshelf" types have appeared in an attempt to meet this need. In practice, however, they seem neither fish nor fowl...either too large for compactly spaced bookshelves or too small for use as free-standing units.

The AUDAX CA-60 is a true bookshelf speaker system, measuring only 9" high by 10 1/2" deep by 18" wide. It houses a 6" woofer and separate tweeter in a ducted-slot enclosure constructed of 3/4" thick wood, finished in oiled, hand-rubbed walnut on four sides. The grille is shaped in an attractive parabolic contour, giving the unit a character which blends with a variety of surroundings.

A real powerhouse... handles 20 watts in integrated program material! Hear it at your dealer's.

DO YOU KNOW ABOUT THE FULL LINE OF AUDAX-ENGINEERED REPLACEMENT SPEAKERS AND COMPLETE SPEAKER SYSTEMS?

AUDAX-Division of Rek-O-Kut Co., Inc. Dept. RE-3, 38-19 108th St., Corona 68, N. Y.

- Please send full information on:
- Model CA-60 And Other Systems
 - Audax Replacement Speakers
 - Enclosed is 25¢ for book of 6 plans "How to Build Your Own Audax Enclosure"

Name _____
 Address _____
 City _____ Zone _____ State _____
 Morhan Export Corp., 458 Broadway, N. Y. 13
 Atlas Radio Corp., 50 Wingold Ave., Toronto.

TELEVISION

filled in with shellac

Burn holes can be filled with shellac.

ly. I prefer using transparent shellac sticks for burning in since the transparent type allows grain and color to show through, making a better match with the surrounding area than is usually possible with opaque, colored shellac sticks. After burning in, finish off by smoothing out and polishing as with other types of injuries.

Crushed edges and corners

When a cabinet is dropped during transit, the usual result is a crushed corner or edge. Like deep nicks and gouges, this type of damage can be vastly improved, but cannot always be repaired 100%. One word of caution: before you even think of doing anything about a crushed corner, examine the joint alongside it and all other joints, particularly the one diagonally across from the damaged one. Check for joints that are sprung and have started to split open. If the joints have started to go, the structural integrity of the entire cabinet is in serious trouble. In severe cases, the cabinet may have to be discarded.

Crushed corners or edges are another form of damage you would treat with a shellac stick and burn-in. When repairing a crushed corner, use your judgment as to how far to try to rebuild it. It is usually inadvisable to try to build up a badly crushed corner to its full original shape. The new corner would be very fragile — it is made only of shellac. Build up bad crushes say 1/4 inch or a bit more and stop. The damage won't be completely hidden, but it will be a great deal less obvious, and the repair will be more likely to stay in place.

Loose or broken hardware

Hinges that are wobbly because of loose screws, hinges bent out of shape, bent lid supports that won't open or won't support, door catches that won't catch, drawer slides that won't slide, all fall under the head of loose or broken hardware. A lot of the trouble caused by such problems is secondary — scratching and scarring caused by continued use of the cabinet after the hardware has gone west.

As a general rule, the best thing to do with bent or broken hardware is to take it off and replace it. A bent or broken hinge, catch or lid support will never be quite right if you try to fix it. On an antique piece with antique hardware that cannot be replaced, you have no choice but to try and repair it. Otherwise, don't waste your time.

One of the most common troubles with hardware is not that the hardware itself is damaged, but merely that the screws holding it in position have stripped their threads in the wood and

PURCHASING A HI-FI SYSTEM?

Send Us Your List Of Components For A Package Quotation

WE WON'T BE UNDERSOLD!

All merchandise is brand new, factory fresh & guaranteed.

Free Hi-Fi Catalog Available on Request.

AIREX RADIO

CORPORATION

64-RE Cortlandt St., N.Y. 7, CO 7-2137

PARTIAL LIST OF BRANDS IN STOCK

- Altec Lansing
- Electrovoice
- Jensen • Stephens
- Hartley
- University
- Acoustic Research
- Janszen
- Wharfedale
- Karlson Cabinets
- Viking
- Concertone
- Bell • G.E.
- Weather's
- Harman-Kardon
- Eico • Pilot
- Sherwood
- Acousound
- Fisher • Dual
- Changer
- Bogen • Leak
- Dynakit
- H. H. Scott
- Ferrograph
- Tandberg
- Pentron • Revere
- Ampex • De Wald
- Karg Ampli & Spkrs
- Challenger • Quad
- Wollensak
- Garrard
- Miracord
- Glaser-Steers
- Rek-O-Kut
- Components
- Norelco
- Fairchild
- Pickering • Gray
- Audio Tape
- Conrac
- Wellcor Cabinets

NEW!

ALCO 20,000 ohms per volt

VOLT-OHM-MILLIAMMETER MODEL TS-60H



- High sensitivity — 20,000Ω per volt
- Modern design
- Exceptionally wide scale arc
- Compares with 4 1/2" meters
- Measures 3/4" wide x 4 1/2" x 1 1/4"
- Compact, black bakelite cabinet

D.C. Volt Ranges—5, 25, 250, 500 and 2500 @ 20,000Ω per volt

A.C. Volt Ranges—10, 50, 100, 500 and 1000 @ 10,000Ω per volt

D.C. Current—50μa, 2.5ma, 250ma

Resistance—0-60,000 ohms, 0-6 megohms

Capacity—.001 mfd.-1 mfd (w/10 VAC supply) .00001 mfd.-.001 mfd (w/100 VAC supply)

\$16.95

Decibel— -20db to +22db complete

ORDER DIRECT OR FROM YOUR NEAREST DISTRIBUTOR

ALCO ELECTRONIC PRODUCTS, INC. Dept. E-3, 3 Wolcott Ave., Lawrence, Mass.

TELEVISION

loosened. Rather than replace them with larger screws that may not fit the hardware, remove the screws, fill the holes with plastic wood and while the plastic wood is still soft, redrive the screws. Caution! Drive only until the screw heads are flush—any more and you'll pull the plastic wood right back out. Give the plastic wood time to set, and you'll find the hardware is tight again.

This completes our discussion of the more common cabinet injuries. Deterioration due to age or construction failures in a cabinet result in other symptoms and treatments. Next month we treat some of the harder-to-handle troubles. We start off with cracked, glazed or alligatored finishes, continue on to open joints, work over some loose legs and molding and finish up with refinishing. TO BE CONTINUED

CURE DISCOVERED FOR TV TUBES!

A Texas scientist, noted for his extensive research in the field of aniline dyes and the pre-natal dying of wool, which has gained him world-wide recognition as the world's foremost lamb dyer, has at long last isolated a heretofore unsuspected valve in receiving tubes which seriously limits the tube's capability and useful life. It has long been felt in engineering circles that tubes would pass both mc's and kc's. It has now been shown that acidic atmospheres in vacuum tubes cause a little door to close over the valve and prevent the free passage of mc's, which all will recognize as fatal.


Five New York doctors verified these findings and report that their sets work better when the tubes are treated with XL-9, a secret formula prepared by the Texas Institute.

XL-9, containing a slight trace of lanolin extracted from pre-natal lamb's wool together with three other as yet unspecified ingredients, when applied to the outside of receiving tubes has the property of easing internal stresses and allows the free passage of mc's and kc's.

Leading tube engineers say that the discovery of the hidden valve is a complete surprise to them and that their quality-control sections have never listed this on their reports. Both CGS and Rayvania have ordered large shipments of new formula XL-9, which they promise will coat each tube leaving their plants in the future.

Service technicians all over the country hail this discovery as the greatest boon to set owners of all time, and are making plans to award a plaque to the Texas Institute in recognition of its great contribution to mankind.—*Reprinted from TESA (of Seattle) News.*

1551 pages

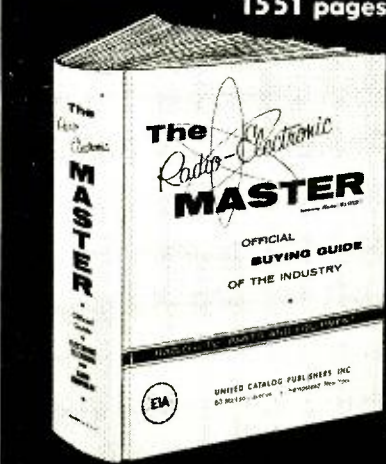

World's LARGEST Electronic Catalog

\$3.50
at parts distributors \$4.50 in Canada

1960 RADIO-ELECTRONIC MASTER

now available at your distributor

NEW...STREAMLINED...28 EASY-TO-USE PRODUCT SECTIONS COVER ALL LATEST PRODUCTS

• Printed circuit components • Stereo equipment • Miniature and sub-miniature components • Silicon rectifiers • New transistor types • Citizen's band, SSB and new mobile ham gear • Components and equipment for microwave and telemetering.... Plus every new electronic product for servicing, experimenting, design, industrial and military applications.

GREATER INCOME...SPEDIER DESIGN & PURCHASING...MORE HOBBY FUN

SERVICE TECHNICIANS
More profitable operation. Covers all items necessary for Radio-TV-audio servicing. Offers thousands of products for extra income in hi-fi, sound and industrial servicing. You can buy, sell and bill direct from The MASTER...it shows list prices!

ENGINEERS & P.A.'s
Save time. Quickest way to get current factory-accurate data on all the products needed for research, design and production. Systematically organized in 28 product sections for rapid product comparison. Minute details so necessary for specifying.


HAMS, HOBBYISTS, EXPERIMENTERS
Get the right product to do the job because you shop in the electronic supermarket — The MASTER. Specifications, descriptions, prices of receivers, transmitters, hi-fi gear, cabinets and hard-to-locate items not found in smaller catalogs.

No matter what product or component you require...

YOU'LL FIND IT FASTER IN THE

1960 MASTER

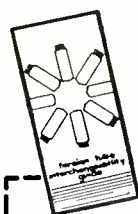RADIO ELECTRONIC MASTER, 58 Madison Ave., Hempstead, N.Y.



FREE...FROM YOUR DISTRIBUTOR

24-page Foreign Tube Interchangeability Guide or write direct enclosing 25¢ for handling

ADD TO YOUR INCOME

Learn at Home to Fix APPLIANCES


FREE SAMPLE LESSON

Tester Furnished—No Extra Charge.
National Radio Institute trains you at home. Every service customer is worth more when you can fix his electrical appliances. Mail coupon for Lesson and Catalog.

National Radio Inst., Dept. FCO, Washington 16, D.C.
Please send me Electrical Appliance Sample Lesson and Catalog FREE (No salesman will call).

Name.....Age.....
Address.....
City.....Zone.....State.....
ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL

CONVERT TO COLOR TV

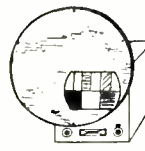

COLORDAPTOR—A simple 10-tube circuit and rotating color wheel converts any size B & W TV to receive compatible color TV.

COLORDAPTOR—Easily attached to any TV set does not affect normal operation, often built from parts experimenters have on hand. **BRELLIANT COLOR!**

ONLY \$1.95

Complete booklet—gives theory of operation, all construction details, schematic, and sample color filters.

Essential Parts Kit—All Special Parts—Coils, Delay Line, Crystal, Color Filters

Up to 16" **\$19.95** 17" and **\$20.95**
Sets—**Larger**

Other Kits, Wired Chassis, Motors Available

COLORDAPTOR
1798 Santa Cruz,
Menlo Park, Calif.

I'll show you how to make real money during the boom in F-M

Comeback of F-M Radio can mean plenty of extra money if you're in business now or plan to start full or part-time repair shop. Here's how to get the expert know-how you need to cash in:

Famous "Quick-Way" F-M Manual Now Ready in 3rd Edition - Newly Revised, Completely Rewritten and Up-to-Date. Latest Circuitry, Components; Servicing Data and Methods.

N. Y. Times reports F-M radio has "bounced back with vibrant life" . . . that over 800 FM stations are already transmitting or being rushed to completion.

You can easily tap this new source of servicing profits, says noted radio-TV authority Milton Kiver, because you already have the skills you need. It's just a matter of applying them to F-M's different circuitry and components. His new 3rd Edition of *F-M Simplified* shows you exactly how to do that—for it's a complete "course" in everything you need to know about what goes on in an F-M receiver or transmitter, and how to fix it fast.

Covers A-M/F-M Receivers, Hi-Fi Tuners, Mobile and Fixed-Base Units!

You start right out with a clear, easy-to-understand explanation of how F-M differs from A-M. Then, section by section, with big illustrations guiding you, Kiver explains what each component does . . . phase modulation . . . antennas . . . tuners . . . H.F. oscillators . . . amplifiers . . . limiters . . . receiver alignment.

Scores of simplified servicing procedures are laid out for you step-by-step. Over 300 typical problems enable you to check your new knowledge and methods as you master the 16 information-filled chapters. Soon you're ready to tackle any F-M repair.

Practice with Book 10 Days Free!

To prove how profitable F-M *Simplified* can be for you, we'll send it 10 days FREE. Try its methods on next F-M job that comes in. If you're not overwhelmed with its practical dollars-and-cents value, just return it. No obligation. Mail coupon for free-examination copy today to:



D. Van Nostrand Company, Inc., Dept. 183, Princeton, N.J. (Established 1848)

Send No Money

D. VAN NOSTRAND COMPANY, INC.
Dept. 183, Princeton, N.J.
In Canada: 25 Hollinger Rd., Toronto 16

Send me the new 3rd Edition of Kiver's F-M SIMPLIFIED for FREE examination. If I don't feel it will give me quick, easy command of F-M servicing, I'll return it within 10 days, owe nothing. Otherwise I'll pay \$2.50 down, plus small delivery cost, and \$2.50 per month for 2 months as payment in full.

Name (please PRINT)

Address

City Zone State

SAVE! Enclose \$7.50 WITH coupon and WE PAY all shipping costs. 10-day money-back guarantee.



conducted by
JACK DARR

WE'VE had a lot of inquiries lately about yokes—testing, substituting and so on. Several readers have asked for a brief discussion of this, so here goes.

Beside the standard symptom of yoke trouble, which is a trapezoidal raster, there are several other reliable indications. The best of these is the absence of boost voltage—your damper tube will have only B-plus on both cathode and plate. A good rule for boost-voltage value is that it should be at least 100 volts above the B-plus. So if the raster is dim or nonexistent and the boost is gone, look for trouble in or around the yoke.

There are several ways. The quickest is a regular flyback-yoke tester. The suspected component is connected across this. If it has any shorted turns or other defects, they will show up on the meter reading. Actually, this tunes the yoke or flyback to resonance and reads the output. A short will lower the winding's Q so far that the meter reading will be much lower.

A good home-made test is the substitution of a yoke with duplicate characteristics. Note that in this test we're not interested in getting a complete yoke with the exact characteristics needed. All we need is a yoke that is within about 20% of the inductance value of the original, so that we can be certain that the original is defective.

Most of us have at least two or three new yokes in stock. One of them should come close enough for test purposes. If not, a yoke from another TV set may be used. Disconnect the horizontal windings of the original and connect the test yoke. Now, measure high voltage, boost, etc., to see if it comes back to normal. If so, the original yoke is defective. Before discarding it though, take a good look at wiring, the balancing network and the connecting leads. Many yoke troubles come from minor wiring shorts or loose connections.

There is a certain amount of tolerance in yoke inductance, but not too much—15% to 20% according to various authorities. Fortunately, there are only about 10 inductance values in common use in horizontal yokes, and 5 in the vertical sections. There are a

TABLE I
Inductances of Deflection Yokes

Horizontal (mh)	Vertical (mh)
8.3	3.5
10.3	11.5
12.5	12.3
13.5	40.0
18.5	42.0
19.0	48.0
25.0	50.0
30.0	


large number of combinations of these values, of course. Table I shows the range of inductance to be expected in each section.

Some typical symptoms of yoke trouble are trapezoidal pictures, ringing in the raster causing wrinkles and bright lines at the left side (look for the telltale bending of the scanning lines that denote raster instead of video troubles), insufficient height or width. Either of the last two may be found with or without the trapezoidal shape. A very good indication is a loss or lowering of boost voltage. Watch out for troubles which seem to be in the yoke but aren't. Typical of these are open boost filter capacitors which can cause a wrinkled and slightly trapezoidal raster. This usually happens in sets which draw vertical output current from the boost. A tipoff to this is found in the vertical linearity control which will act as a brightness, width and high-voltage control all in one! The brightness control will also change the shape of the raster.

If you lack information about the yoke, a rough guess can be made from the dc resistance. Table II gives the approximate resistance values for the

TABLE II
Inductance vs Resistance of Deflection Yokes

Horizontal	
Inductance (mh)	Resistance (ohms)
8-10	13-15
12-14	18-20
18-21	30
24-25	38-40
30	50
Vertical	
3.3	3.6
40	40-45
45	50-55
48	55-65

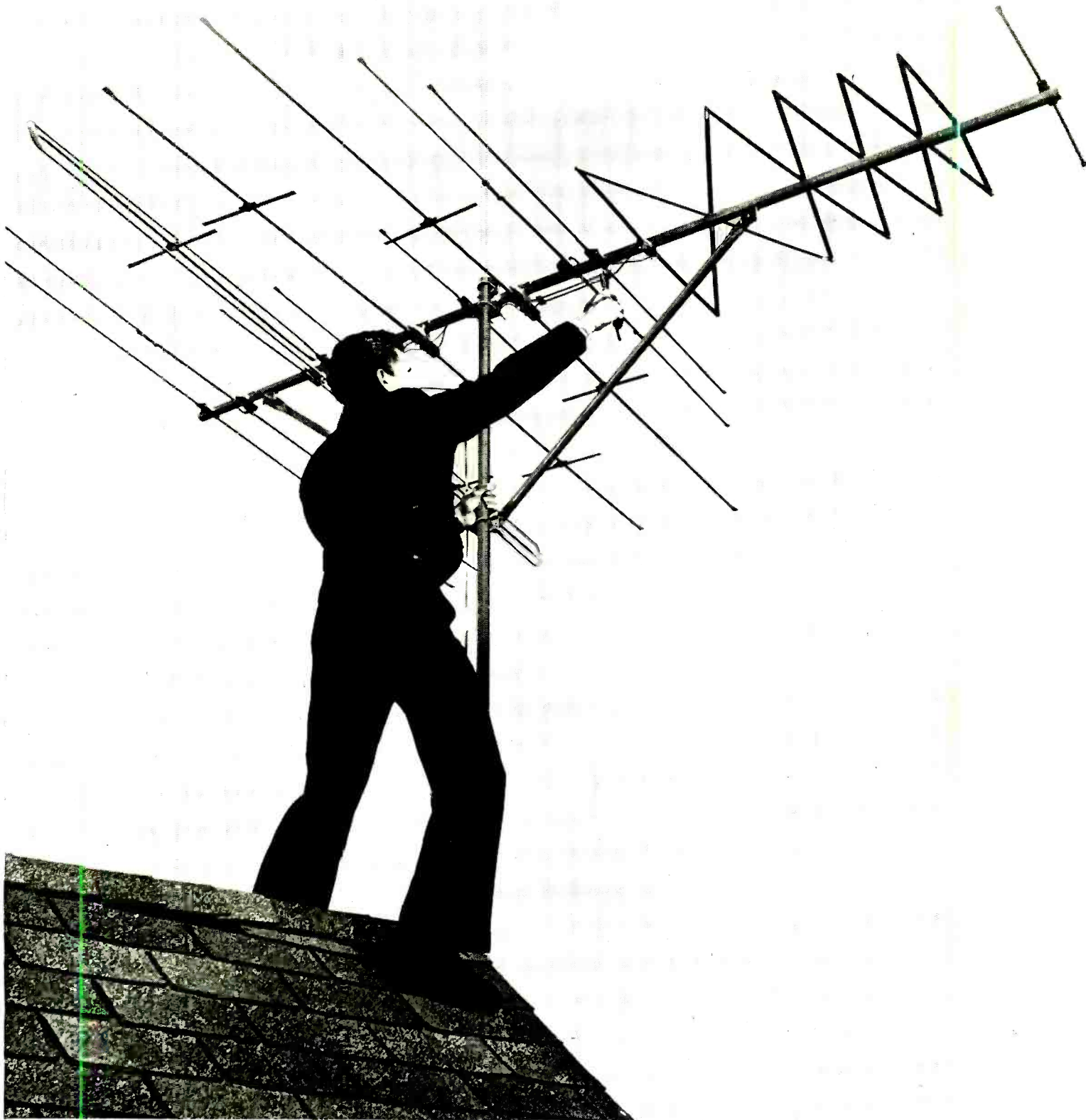

The Businessman in the Service-Technician Suit knows that the service-dealer leaders of tomorrow install JFD Hi-Fi Helix Colortennas today. He relies on JFD for uncompromising performance...quality...durability to build confidence and insure complete customer satisfaction.

www.americanradiohistory.com

THE BRAND THAT PUTS YOU
IN COMMAND OF THE MARKET

JFD

JFD ELECTRONICS CORPORATION
BROOKLYN 4, NEW YORK



TV TUNERS OVERHAULED

ALL MAKES AND MODELS **VHF OR UHF**

90 Days Warranty

FAST SERVICE

PRESENT DELIVERY IS 48 HRS. ON MANY TYPES

VHF OR UHF TUNER OVERHAULED

\$ 9.95 NET

Prices include labor and minor parts only, defective tubes and damaged major parts are extra at net prices.

UHF/VHF COMBINATION OVERHAULED

\$19.90 NET

Forward defective tuner complete with tubes, shield cover and any damaged parts. Quote make and model, and describe fault. We will ship C.O.D.—F.O.B. Chicago or Toronto.

Castle TV Tuner Service

5710 N. Western Ave.
Chicago 45, Illinois

Suppliers of rebuilt TV Tuners to leading manufacturers, technicians & service dealers, coast to coast. Original and Only Complete TV Tuner Service covering the North American Continent.

In Canada:—136 Main St.,
Toronto 13, Ont.

The April issue of
RADIO-ELECTRONICS
will be on sale March 29.

Reserve your copy now at your newsdealers.



TRAIN QUICKLY! OLDEST, BEST EQUIPPED SCHOOL of ITS KIND in U.S.

Get practical training in New Shop-Labs of Coyne. Prepare for a better job and a successful future in a top opportunity field. Advanced education or previous experience not needed. Employment service to graduates.

Enroll NOW—Pay Later

Finance Plan and Easy Payment Plan. Also Part Time Employment help for students.

FREE BOOK Clip coupon or write to address below for Free Illustrated Book—"Guide to Careers"—Describes all training offered. No obligation and No Salesman Will Call. Act NOW.

B. W. Cooke, Jr., President
COYNE CHARTERED NOT FOR PROFIT ELECTRICAL SCHOOL Established 1899
1501 W. Congress Pkwy. Chicago, Dept. 30-5C

COYNE Electrical School
1501 W. Congress Pkwy., Chicago 7, Ill.
Dept. 30-5C


Send FREE book "Guide to Careers" and details of all training you offer. However, I am especially interested in:

ELECTRICITY TELEVISION BOTH FIELDS

NAME.....

ADDRESS.....

CITY.....STATE.....

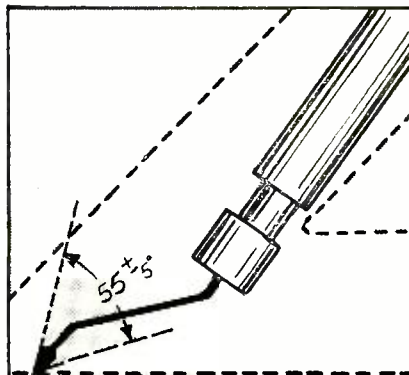

what's the angle?

55 (±5) degrees—a whole diamond—hand polished

Why 55 (±5) degrees? To fit standards set by record manufacturers. Styli ground mechanically may have angles up to 85 degrees. The Duotone stylus is hand ground and polished as close to record-groove requirements as possible. A whole diamond, 2/3 embedded in the stylus, that can't break off like a welded chip—guaranteed—and the protection of a microscopic inspection for ±.0001 tolerance in its radius—that's the angle.

DUOTONE

DIAMOND NEEDLE

Keypoint, New Jersey

In Canada: Chas. W. Pointon, Ltd., Toronto

TELEVISION

various yoke windings. This should be used for substitution tests only, unless no service information at all is available, a situation seldom found today. Service literature from manufacturers, service-data publications and yoke manufacturer's catalogues, all have very comprehensive lists of almost all sets made within the last several years. If half of a yoke winding is burned up, resistance measurements can be made by reading the undamaged half, then doubling the reading. When replacing the yoke, be sure to duplicate the R-C network originally used, for the best matching and elimination of ringing in the raster.

Picture smear

How can picture smear in an Admiral 14YP3 be prevented when the picture-tube leads are extended approximately 2½ feet?—D. M. K., Davenport, Wash.

The picture smear is caused by excessive shunt capacitance at the video amplifier output, caused by the extended leads to the picture tube. You won't have to use a cathode follower if the stray capacitance of the video signal lead is held to a low value. The lead should be suspended in free space and not run close to metal surfaces.

Zero reference levels

What is the meaning of ac and dc zero-reference levels on scope screens, for which I cannot find answers in any text?—O. T., Los Angeles, Calif.

The ac and dc zero-reference levels are given by the beam resting position on the scope screen, with no input signal. A dc scope provides a dc zero-reference level. An ac scope provides an ac zero-reference level. Consider a power supply having a ripple voltage.

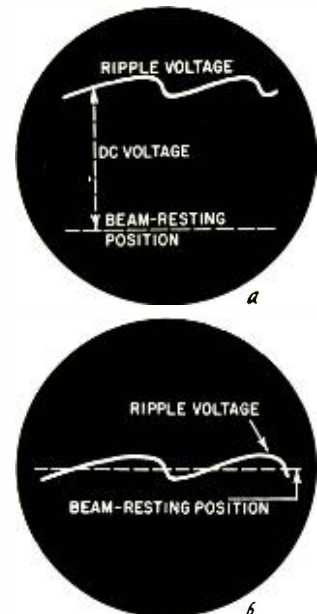


Fig. 1-a—Beam resting position of trace in a dc scope is the dc zero-reference level; b—beam resting position of trace in an ac scope is the ac zero-reference level.

TELEVISION

Both ac and dc output are present. We sometimes call the output a pulsating dc voltage. As shown in Fig. 1-a, a dc scope displays both the ac and dc voltage components with respect to the beam resting position. The ripple pattern rises above the dc zero level by a distance proportional to the dc component. The percentage of ripple (ac) is given by its peak-to-peak voltage with respect to the dc voltage deflection. On the other hand, an ac scope shows only the ac component, as indicated in Fig. 1-b. The ripple waveform is centered on the beam resting (zero ac) level.

Hole in the raster

A Crosley G21TOWH chassis has developed what we call "hole-in-the-raster" trouble! From 30 minutes to 3 hours after it is turned on, a small notch in the upper right-hand corner of the screen blacks out. It grows until it has blacked out about 6 square inches of the picture. There is very little or no foldover around the edges. The hole moves with the raster or picture when the vertical hold is moved, its position staying fixed relative to the raster. We have substituted several parts, including the yoke, flyback, picture tube and a complete low-voltage power supply with filters. An external horizontal

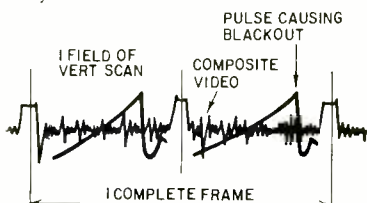


Fig. 2—Hole in the raster can be caused by a spurious pulse in the field scan.

drive has been used for the output.—*J. M., Tupelo, Miss.*

This is indeed an unusual trouble! The fact that the hole moves with the raster when the vertical hold control is moved rules out my first thought—stray magnetic fields developing within the cabinet or yoke, etc. or a defective dag coating on the picture tube (causing a negative electrostatic field to develop inside the bulb). The clue here is that the hole rolls with the vertical scan. Its origin must then be in the vertical output stage since it is synchronized with its output. To black out the tube in any place, the CRT must receive a pulse of voltage of the proper polarity on its grid or cathode. Therefore, we now have two facts—a pulse of voltage is getting into the video channel (either into the video amplifier or CRT circuits themselves) and this pulse is originating in the vertical output circuit (the most likely, since the highest pulse voltages are present there).

Take careful measurements with a scope on the video input to the picture tube, also in the video amplifier stage. Pull the video amplifier tube or disable it to see whether the trouble is originating before or after the video amplifier grid. You'll probably find a pulse volt-



*Spring Special!
Limited time
Only!*

**SAVE
\$3.20**

Get a 1 year subscription to both of these magazines
with purchase of any one of these

Weller POWER TOOLS



Popular Homecraft and Home Craftsman are the leading magazines in the do-it-yourself field. Both are full of ideas for fixing and making things. They feature home workshop projects with photographs, plans and blueprints—and a host of money-saving tips on home improvement. Regular subscription price, \$3.20 a year. Subscription cards included in tool cartons. Special offer expires June 15, 1960.

PROFESSIONAL SOLDERING GUN—The same heavy duty, 250-watt gun used by electronic servicemen the world over. Just pull the trigger—tip heats instantly and twin spotlights flick on to illuminate your work. Tip has long reach and can be bent to get into difficult places. MODEL 8250A **\$12.95**
Both magazine subscriptions included

POWER SANDER—Big 25 sq. in. sanding surface and 14,400 strokes a minute get jobs done fast and easy. Straight-line action never bucks, twists or scars the surface. Goes all the way into corners and under low places. Assorted sandpaper and polishing cloth included. MODEL 700 **\$16.95**
Both magazine subscriptions included

SABRE SAW—A portable saw that makes every kind of cut through plywood, composition board, plastics, aluminum, etc. Even makes its own starting hole for inside cuts—no need to drill. Exclusive strain-relief feature prevents breakage. 3 different blades included. MODEL 800 **\$19.95**
Both magazine subscriptions included

AT YOUR ELECTRONIC PARTS DISTRIBUTOR Weller Electric Corp. Easton, Pa.

CARTOONS

RADIO-ELECTRONICS pays \$3.00 for good cartoon ideas and \$15 and up for finished work

RADIO-ELECTRONICS 154 West 14th St. New York, 11 N.Y.

FREE! CATALOG OF
HI-FI, RADIO, TV
PARTS & ACCESSORIES —
yours for the asking!
Vidair ELECTRONICS MFG. CORP.
44 CHURCH ST. • BALDWIN, N. Y.

WHY PAY MORE?
BONAFIDE now offers the biggest discounts on all famous HI-FI & Stereo components or HI's of your choice.
BIG TRADE-IN ALLOWANCES
We can give you the best deal & expert advice and also guarantee everything sold. Write for our special price quotations on package deals. No sale-too small.
BONAFIDE ELECTRONICS
Dept. RE3, 89½ Cortland St., N.Y. 7, N.Y.

TELEVISION

age in the field scan. It would have to be shaped roughly like the one shown in Fig. 2 to cause the effect noted.

Check or replace the 5- μ f capacitor between the brightness control and the 260-volt line, and the 20- μ f unit between the vertical linearity control and B-minus. They have been known to cause some very unusual symptoms in this chassis. There is also the possibility of interelement leakage in the multiple electrolytics.

Alignment problem

I am working on a Mattison 630 and am having difficulty with alignment. On an if sweep check, the 27.75-mc trap after-response shows up normally. But when sweeping at rf through the antenna input terminals, the response slopes off and the after-response disappears. I do not get clear image outlines on channel 2. Edges show grain or wavy lines. Is this caused by a picture carrier too low on the curve, or by regeneration?—G. L. S., Mercer, Pa.

The after-response may not show up on an overall sweep check for two reasons: First, the rf response may be attenuated in this region. A separate rf tuner alignment check should be made. Second, you may have limited rf sweep output from your generator, so insufficient signal is applied at rf to provide a true comparison with the if sweep response. There is also the possibility of

mixer regeneration. This can be checked by turning the channel-selector switch while sweeping the if amplifier—use a floating tube shield over the mixer tube. If the if curve changes substantially in this test, the tuner needs attention or replacement. The grain is caused by inadequate rejection of the sound carrier. Check settings of the sound traps with an accurate marker generator. Waving lines at the edges of objects can be attributed to several causes in a weak-signal area. Without a more definite and detailed description, it would be difficult to tie this down.

Sync buzz

Can you recommend an FM detector and driver circuit to replace a slope discriminator in a Hyde Park 172? I am interested in minimizing sync buzz.—J. B. E., Jr., So. Plainfield, N. J.


A limiter ahead of the FM detector is most effective in eliminating sync buzz. In view of the circuit now in use, I would suggest elaborating along the lines of the Tele-Tone TV-316. The present 25L6 can be used.

Critical horizontal oscillator

I have been having difficulty with the horizontal oscillator circuits in CBS 1621 chassis, which are made in Canada. The last one required critical selection of 6SN7 and 6DQ6 tubes. A 6CU6 taken from another set because of pie-crust operates satisfactorily in

place of the specified 6DQ6-A. Can you suggest the cause of the trouble?—R. A. W., Port Severn, Ont.

The need for selecting 6SN7's can be correlated with their cutoff characteristics. Various tube manufacturers have quality-control procedures to weed out 6SN7's with remote cutoff. A few tube testers will check cutoff. The difficulty with the 6DQ6's has a familiar ring. It is very likely that the tubes that give unsatisfactory oscillation are being "bugged" by parasitic oscillation. Try inserting 47-ohm resistors in series with the grid, plate and screen-grid leads, at the socket terminals. Standard heater chokes in series with the heater leads may also help. END

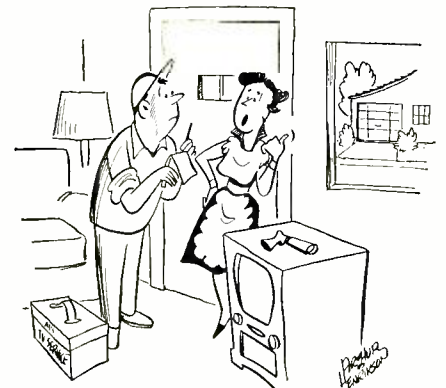

"The television's OK—but our neighbor's garage door opens when I use the remote control!"

FROM TURNER...QUALITY MICROPHONES FOR EVERY APPLICATION




Model 58

FOR TV, BROADCAST AND HI-FI RECORDING

Model 58, a dynamic miniature with high fidelity, meets TV, broadcasting, recording, PA requirements of performance, durability, compactness. Model 58 has the sensitive Turner Dynaflex diaphragm which resists shock, temperature extremes, moisture. Response; 60 - 13,000 c.p.s. Level; -57 db at high impedance. Model 58 wired for quick selection of high or low impedance. Model 58A for quick selection of 50 or 200 ohms impedance. List price \$57.00.


FOR DISPATCH, PAGING, P.A., CONTROL TOWER AND AMATEUR USE

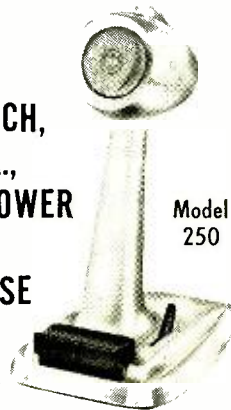

Model 250

The Turner "Lift-Switch" Model 250 dynamic offers you more versatility, convenience and ease of operation than any other microphone. Wired to operate both relay and mike circuits at a touch. Has Turner's exclusive 3-way switching. 1) Lift the mike, it's live; 2) depress the front bar for push-to-talk; 3) move the lever-lock forward. The mike is live and stays live. The model 250 is a high impedance microphone. Response; 60 - 10,000 c.p.s. Level; -52 db. Complete with single unit die-cast case and 20 ft., three conductor (one shielded) cable. Furnished in satin chrome. List \$49.50.

GENERAL PURPOSE

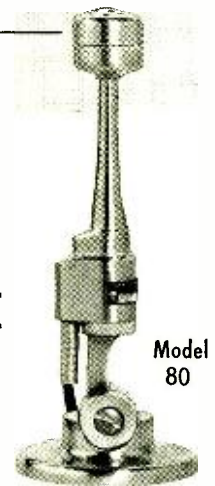

Model 80

A slender, compact and graceful crystal microphone. Highly versatile. Can be adapted for hand, stand or desk uses. Total weight only five oz. Response; 80 - 7,000 c.p.s. Level; -54 db. Equipped with 7 ft. single conductor shielded cable. List price \$15.95 (Less C-4 stand illustrated).

Write for free catalog



THE TURNER MICROPHONE COMPANY

933 17th St. N.E., Cedar Rapids, Iowa
IN CANADA: Canadian Marconi Co.,
Toronto, Ontario and Branches
EXPORT: Ad Auriema, inc.,
85 Broad St., New York 4, N.Y.

new PRODUCTS



DIRECTION FINDER KIT model DF-3 tunes aircraft, marine telephone, standard broadcast bands. 9 transistors operate from 6 standard flashlight



cells. Balanced-loop rotating antenna and collapsible whip antenna used together to eliminate 180° ambiguity. Front end preassembled and prealigned.—Heath Co., Benton Harbor, Mich.

DEPTH-SOUNDER KIT model DS-1 indicates depth and nature of bottom up to 100 feet, detects fish, logs and other sub-



merged objects. Operates on one 9-volt battery and standard flashlight cells. Depth read directly in feet on circular scale inside light hood. Transducer mounts permanently or used outboard in temporary installations. Metal parts treated to resist corrosion.—Heath Co., Benton Harbor, Mich.

CITIZENS' BAND transceiver model BS-27 includes tunable superregenerative receiver, also covers amateur 10-meter band. Receiver sensitivity 1 mv or better. Transmitter input to fi-



nal rf amplifier 5 watts. Includes under-dash mounting bracket.—Kay-Townes Antenna Co., Box 593, Rome, Ga.


CITIZENS' BAND transceiver model HE-15 powered by house ac, 6 or 12 volts dc with accessory power supply. Receiver tunable to any channel; transmitter switches to any of up to 5 channels. Crystals replaceable in front panel. Side-mounting brackets for installation in car, truck, boat, etc. 3-position func-



tion switch: talk, receive, talk-with-spring-return.—Lafayette Radio Electronics Corp., 165-08 Liberty Ave., Jamaica 33, N. Y.

CITIZENS' BAND SET model C-27A provides choice of 6 channels via front-panel switching. Adjacent-channel interference 37 db down. Receiver sensitivity 1 μ v, adjustable squelch, noise limiter, 3-watts sound output. Ceramic microphone push-to-

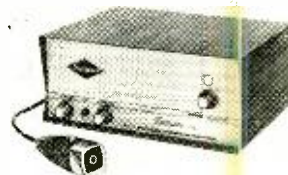talk switch. Power supply uses 117 v ac, 6 or 12 v dc by chang-



ing power cord.—Transpace, Inc., 12902 Foothill Blvd., San Fernando, Calif.

SSB COMMUNICATIONS RECEIVER model HQ-180 350 kc to 30 mc in 6 ranges. 18-tube superhet, noise limiter, adjustable crystal filter, adjustable sidebands, 7-position if selectivity, 4-position avc switch, built-in crystal calibrator. Signal-to-noise ratio 20 db with 0.5- μ v CW input. Rack-mount-




ing or in cabinet.—Hammarlund Mfg. Co., Inc. 460 W. 34 St., N. Y. 1, N. Y.

MOBILE TRANSISTOR AMPLIFIER model TP20M, 20-watts output, low current requirement: 3½ amps at 12 volts at full output, ½ to ¼ amp with no input. Output impedance

Get This Valuable Book

FREE

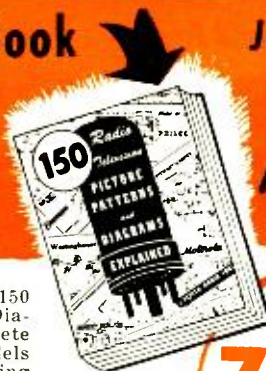

Just For Examining COYNE'S New Set
"Applied Practical Radio-Television"
on 7 DAY FREE TRIAL!

Yes, you get this big, brand new book, "150 Radio-Television Picture Patterns and Diagrams Explained", absolutely FREE! Complete 11x22" Schematic Diagrams on leading models Radio and TV Sets help cut your servicing time Easy-to-read, large 8½x11" pages, with full instructions on how to use the diagrams. A "must" in every repair kit. You get this book as a FREE Gift for asking to see Coyne's new 7-book set, "Applied Practical Radio-Television"!

At Last! Money-Making "Know-How" On Transistors, Color TV and Servicing

Coyne's great 7-volume set gives you all the answers to servicing problems—quickly! For basic "know-how" that's easy to understand you'll find everything you want in Volumes 1 to 5 on over 5000 practical facts and data. Every step from fundamentals to installing, servicing and trouble-shooting all types of radio and TV sets. So up-to-date it includes the latest on COLOR TV and UHF. All this plus Volume 7—TRANSISTOR CIRCUITS—the most complete book ever published on the applications of transistors in electronics. *New!* Set has colorful design, washable covers.

EXTRA! 868-Page TV Cyclopeda Included!

For speedy on-the-job use, you also get Vol. 6—famous Coyne CYCLOPEDIA. Answers problems on servicing, alignment, installation, etc. in easy ABC order. Use this 7-volume TV-RADIO LIBRARY FREE for 7 days; get the Servicing Book FREE!

FREE!

5 Years Of Valuable Supplements



With your set you also get Coyne's annual Supplement Service FREE for 5 years. Keeps your set up-to-date on everything that will be new in radio, television, electronics and electricity.

NOW!
7 BIG BOOKS
IN ONE GREAT SET!



SEND NO MONEY! Just mail coupon for 7-volume set on 7 days free trial. We'll include book of 150 TV-Radio Patterns & Diagrams. If you keep the set, pay \$3 in 7 days and \$3 per month until \$27.25 plus postage is paid. (Cash price, only \$24.95). Or you can return the library at our expense in 7 days and owe nothing. **YOU BE THE JUDGE.** Either way, the book of TV-Radio Patterns is yours FREE to keep! Offer is limited. Act NOW!

FREE BOOK—FREE TRIAL COUPON!

Educational Book Publishing Division
COYNE ELECTRICAL SCHOOL, Dept. 30-T1
1501 W. Congress Pkwy., Chicago 7, Ill.

YES! Send 7-Volume "Applied Practical Radio-Television" for 7 days FREE TRIAL per your offer. Include TV-Radio Patterns & Diagram Book FREE.

Name Age

Address

City Zone State

Where Employed

Check here if you want library sent C.O.D. You pay postman \$24.95 plus C.O.D. postage on delivery. 7-day money-back guarantee.

Educational Book Publishing Division
COYNE ELECTRICAL SCHOOL
1501 W. Congress Pkwy., Dept. 30-T1, Chicago 7, Ill.



Opportunities

FIELD ENGINEERS for UNIVAC MISSILE-GUIDANCE COMPUTERS

A limited group of qualified applicants are being selected for special training as field engineers for maintenance assignments on ultra-reliable Univac missile-guidance computers and other military electronic data processing systems.

Openings involve maintenance of the Univac ICBM guidance computer, the first computer of its size to be completely transistorized and a system which has established the highest record of reliability in its class.

This computer incorporates many concepts which are being used in the development of advanced computers, both military and commercial.

Applicants should have at least two years of formal education in Electronics with three or more years experience in maintenance or maintenance-instruction. This experience should be associated with complex electronic equipment such as TV, radar, sonar, or digital computing systems.

Prior to assignment, field engineers will receive two to six months training at full pay in our St. Paul, Minnesota, laboratories. Benefits include company paid life insurance, hospitalization, medical and surgical benefits, relocation expenses, and living allowances at field sites.

This is an unsurpassed opportunity to learn and progress in the field of computer technology.

We also have openings for qualified instructors with backgrounds similar to the above.

Send complete resume of education and experience to:


Remington Rand Univac
DIVISION OF SPERRY RAND CORPORATION

R. K. PATTERSON
Department Q-3

2750 West Seventh St., St. Paul 16, Minnesota




NEW PRODUCTS (Continued)

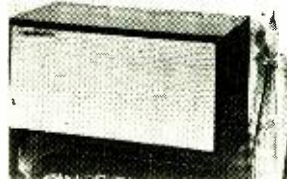


dispersion. Soft - suspension woofer. L-C crossover network. High efficiency, fully driven by amplifiers from 10 watts up. Response 35-17,500 cycles. Fits any 12-inch bookshelf.—**Alecort, Inc.**, Green & Tioga Sts., Ithaca, N. Y.

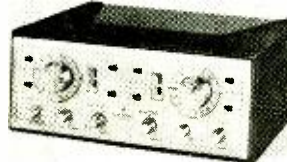STEREO RECEIVER model 399 combines 2 power amplifiers 2 preamps, FM and AM tuners, and complete stereo controls on one chassis. Output 20 watts




per channel, connections provided for third channel output to drive mid-channel speaker. Includes all features of Scott 299 stereo amplifier and 330D AM-FM stereo tuner. Highly flexible controls include phase reverse.—**H. H. Scott, Inc.**, 111 Powdermill Road, Maynard, Mass.

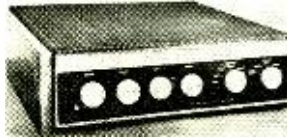TRANSISTOR STEREO AMPLIFIER model S-25. Integrated stereo amplifier, preamp-control unit, 25 watts per channel, response ± 1 db 20-20,000 cycles




at full output. Distortion under 0.8%. Hum 100 db down. Tape head, low-level microphone inputs. Flexible controls provide all stereo switching functions. Powered by 117 volts ac or 12 volts dc.—**Transis-Tronics, Inc.**, 1650 21 St., Santa Monica, Calif.

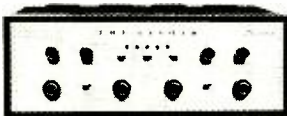STEREO AMPLIFIER model X-205 complete control center, dual 25-watt (music-power rating) power amplifiers on one chassis. Distortion 0.8% at 25 watts. Controls include output



to drive center-channel power amplifier, blend and balance, scratch and rumble filters. Accepts company's remote-control accessory. Indicator lights show operating mode.—**Fisher Radio Corp.**, 21-21 44th Drive, Long Island City 1, N. Y.

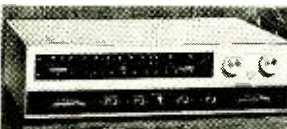STEREO TUNER Knight KN-125, 2 complete tuners on a chassis. FM sensitivity 1.2 μ v, 20-db quieting, includes afc and



adjustable dynamic sideband regulation and 50-ohm shielded antenna input. AM tuned rf stage, 3-position bandwidth switch, 10-ke whistle filter, sensitivity 4 μ v for 20-db signal-to-noise ratio.—**Allied Radio Corp.**, 100 N. Western Ave., Chicago 80, Ill.

STEREO TUNER-PREAMPS models SR-7000 (shown) and SR-8000 combine FM, AM tun-



ers, preamp and control units on one chassis. Separate tuning indicators for FM and AM, switches control FM afc, AM bandwidth, loudness - volume control, output phase. Other conventional controls included.—**Sargent-Raymont Co.**, 4926 E. 12 St., Oakland, Calif.

STEREO RECORDER model 970 similar to model 960 with addition of two 5-watt monitoring amplifiers, two 7-inch



oval speakers. Sound from speakers beamed by adjustable sound-directing panels at each end of long portable case. Monitoring off tape during recording available through totally separate record and playback amplifiers and heads. Plays back mono, 2- or 4-track stereo, records mono or 2-track stereo. Jacks for headphones or external speakers disable internal speakers. 2 high-impedance line inputs, 2 high-impedance microphone inputs separate level controls for each. Dynamic range 55 db at 7 1/2 ips. Head gap 90 millionths inch.—**Ampex Audio, Inc.**, 1020 Kifer Road, Sunnyvale, Calif.

STEREO PLAYBACK TAPE machine model 692 records mono, plays back 2-track, 4-track



tapes without head adjustment or switching. 2-speed unit has pushbuttons, two power amplifiers, two 5 x 7-in speakers. Response 70 to 12,000 cycles. Compartment in case accommodates optional radio tuner.—**Recordio Corp.**, Charlotte, Mich.


STEREO DISC CHANGER model GS-400. Low-priced phonograph player handles all sizes discs mixed in any sequence. Plays manually or automatically. Arm may be held during

NEW PRODUCTS (Continued)



change cycles without damage. Muting switch during cycle. Quick-change cartridge holder. 2 separate shielded 2-conductor cables from cartridge minimize hum loops. Vernier stylus pressure adjustment. Precut bases available.—**Glaser-Steers Corp.**, 155 Oraton St., Newark 4, N.J.

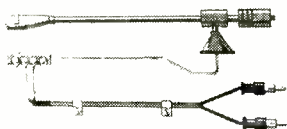STEREO CONNECTING CABLE model *KK-1*, with spade terminals at one end connecting screw terminal strip from



stereo tone arm to phono inputs of amplifier. Designed for company's tone arms, works with other arms as well.—**Rek-O-Kut Co., Inc.**, 38-19 108 St., Corona 98, N.Y.

MINIATURE CAPACITORS type *MTWK*. Metalized paper-plastic film units for industrial, military and similar equipment. Temperature range -55 to +125°C, without voltage derating. Hermetically sealed tu-

bular metal cases with glass-to-metal end seals in various



mounting styles (photo). Full range of capacitances in 200-, 400-, 600-volt sizes.—**Cornell-Dubilier Electric Corp.**, South Plainfield, N.J.


MICROMETER FREQUENCY METER model *105-B* (see) with any station WWV receiver and



modified model *111* Measurements Corp. crystal calibrator measures transmitter frequency from 50 to 500 mc with accuracy better than one part per million (.0001%). *PPM* package includes modified crystal calibrator.—**Lampkin Laboratories, Inc.**, Bradenton, Fla.


TUBE-CHECKER KIT model *400*. Compact unit checks 400

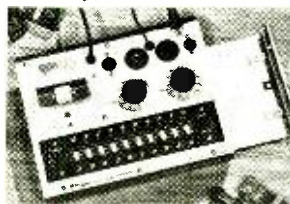types of tubes. Shows filament continuity, shorted elements,



cathode emission on 7-pin, 9-pin, octal and loctal tubes. Scales marked in red and green bands "Replace-Good." Special diode-checking scale.—**Allied Radio Corp.**, 100 N. Western Ave., Chicago 80, Ill.

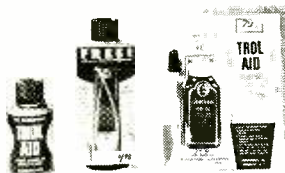CONTACT-CONTROL CLEANER "*Trol-Aid*" non-toxic volume control and contact lubricant-cleaner contains no carbon tetrachloride, doesn't affect electrical properties or insulation. 8-, 3-, 2-oz. sizes. Large size includes wall mount



and nonbreakable, pliable spray aid for pin-point applications and difficult places.—**Chemtronics, Inc.**, 122 Montgomery St., Brooklyn, N.Y.

MINIATURE TOGGLE SWITCH handles up to 100% overload beyond rated 5 amps.

115 volts ac. Designed for use with microminiature components, measures 1/2 x 1/8 x 1/4 in.



Life-cycle rating 100,000 operations, contact resistance 30 microhms, insulation test 100,000 megohms, breakdown voltage 1,000 volts ac. Spdt and dpdt models.—**Alco Electronics**, 3 Wolcott Ave., Lawrence, Mass.

PICTURE-TUBE TESTER model *TV X 759* reads tube beam current, not just cathode emission. Meter indicates 0-100 µa in red, 400-600 µa in yellow. Shorts and leaks 1 meg-ohm down are indicated. All standard pie-



ture tubes handled, including 110" types (with adapter).—**Imperial Electronic Sales, Inc.**, 250 Montgomery St., Shreveport, La. END

All specifications on these pages from Manufacturers' data.

YOU CAN ALSO DO THE BIG JOBS WITH WIZARDS



HOME - 7 Outlets - One Antenna - No Amplification: Residence of Bob Barker, MC of the popular daytime NBC show *Truth Or Consequences*.



HOTEL - 120 Outlets - One Antenna - One Amplifier: The Montecito - 6650 Franklin, Hollywood, California.



THE WIZARD 300*

ELECTRO-MAGNETIC COUPLER FOR ALL SINGLE ANTENNA MULTIPLE-OUTLET SYSTEMS IN TV FLAT LINE

*Pat. Pend.

\$1.95
LIST PRICE

The high electrical efficiency of the Wizard 300 is proven in many installations where more than thirty receivers are being operated from a single antenna without amplification.

Information on any of the above jobs and a brochure covering Wizard System installations is available. Write Dept. RE-129.

CHARLES ENGINEERING, INC.
6053 Melrose Avenue • Los Angeles, California



HOUSING PROJECT - 2,549 Wizards Installed To Date: L.A. Housing Authority, Los Angeles, California.



APARTMENT - 39 Outlets - One Antenna - No Amplification: The Del Rio - 10236 Old River School Road, Downey, Calif




APARTMENT - 48 Outlets - Two Antennas (24 Outlets each) - No Amplification: The Paramount Riviera - 12447 Paramount Blvd., Downey, California.

Service Technicians! YOU EARN MORE... YOU RATE with the public when you own the PHOTOFACT® service data library!

"PHOTOFACTS are
the single most important
addition to good service.
They save lots of time."

—George A. Petzold
Baltimore, Maryland

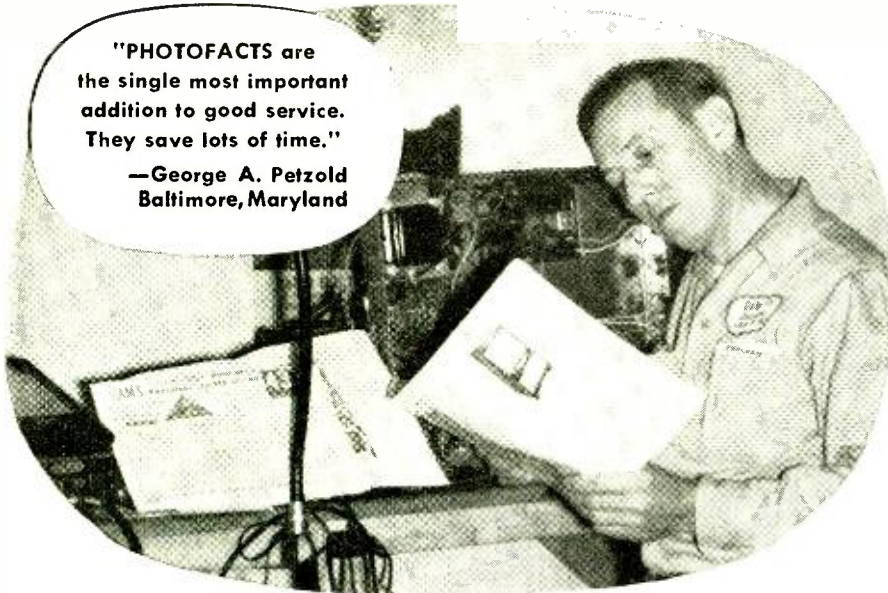

You enjoy maximum earnings as the owner of a complete PHOTOFACT Service Data Library! It's inevitable, because no matter how expert you are, you can always *save more time on any job, get more jobs done daily*—EARN MORE, DAY IN AND DAY OUT...

What's more—as the owner of a complete PHOTOFACT Library, you know your customers' sets *best*. You can actually show each customer you have the PHOTOFACT Folder covering his very own set. Result: You command public respect and acceptance which paves the way to more business and earnings for you.

HOW TO STAY AHEAD...

Yes, the truly successful Service Technicians are those who own the complete PHOTOFACT Library, who can meet and solve any repair problem—faster and more profitably. And these men *keep ahead* because they're on a Standing Order Subscription with their Distributors to receive all new PHOTOFACTS as they are released monthly. (They're eligible for the benefits of membership in PEET, too—see below!)

For PHOTOFACT Library Easy-Buy Plan details and Standing Order Subscription, see your Sams Distributor today, or write to Howard W. Sams...



If you now own a PHOTOFACT Library, you can apply for membership in the powerful new "PEET" program, designed to build prestige and business for the Service Technician who qualifies. Ask your Sams Distributor for the "PEET" details, or mail coupon today!

HOWARD W. SAMS & CO., INC.
1726 E. 38th St., Indianapolis 6, Ind.

Send me full details on the new "PEET" Program. Include full information on the Easy-Buy Plan and Free File Cabinet deal.

I'm a Service Technician full-time; part-time

My distributor is _____

Shop Name _____

Attn: _____

Address _____

City _____ Zone _____ State _____

TECHNICIANS'

NEWS

CALIF. GROUP INSURANCE PLAN

CSEA (California State Electronics Association) continues past the 30-member mark. A major factor appears to be its growing insurance package for members. Already set is a health insurance plan which pays \$500 hospital expenses (\$50 deductible), 80% over \$500, and 80% of medical expenses. Also included are \$1,000 life insurance and \$1,000 accidental death benefits.

Business manager James Wakefield said that workmen's compensation would be the next part of the CSEA-sponsored insurance setup.

ARE YOU ON THE LIST?

Radio-Electronics is publishing a detailed list of the known television service associations in North America. If you belong to an association that isn't on our list or want to get the name and address of the one closest to you, drop a postcard to: Association Editor, Radio-Electronics, 154 West 14 Street, New York 11, N.Y.

RADIO-ELECTRONICS TECHNICIANS ASS'N OF ONTARIO (RTA)

40 Westminster Ave.
Hamilton

Gerald F. Leeks, Secretary

BELLEVILLE CHAPTER
89 Second St.
Campbellford
Morgan Ames, Secretary

NIAGARA FALLS
CHAPTER
23 Alberta St.
Niagara Falls
R. Peckham, Secretary

HAMILTON CHAPTER
741 Gage Ave., S.
Hamilton
Don Napper, President

PETERBOROUGH
CHAPTER
482 Cordash Crescent
Peterborough

KINGSTON CHAPTER
511 Albert St.
Kingston
M. Andriesky, Secretary

SUDBURY CHAPTER
27 Lisgar St.
Sudbury
Paul Ross, Secretary

KITCHENER CHAPTER
88 Grohn St.
Kitchener

TORONTO CHAPTER
197 Avenue Rd.
Toronto
R. Humphries, Secretary

LONDON, ST. THOMAS
CHAPTER
33 Simcoe St.
St. Thomas

WINDSOR CHAPTER
3001 Raddison Ave.
Windsor, N.W.
Otto Alemann, Secretary

FALSE ADS KEEP SHOP OUT

The TV Service Newsletter of the Independent TV Service Dealers Association of Los Angeles County, Inc. reports that an application for membership was recently voted down because advertising run by the service dealer was considered undesirable. "The membership application submitted by _____ TV Service was rejected and the treasurer ordered to return the initiation fee submitted.

RADIO-ELECTRONICS

"While this applicant had a clean record with the BBB and the Los Angeles Police Department's Bunco Squad, his advertising was of such a nature that his membership is not considered desirable. Our secretary discussed the matter with the applicant, who refused to make the changes [in his advertising] suggested.

"It is not the policy of the ITVSDA to try to destroy the individuality of any ethical method of operation by a shop, but limits must be drawn somewhere. In this case it was the opinion of the board that the applicant could not possibly fulfill the claims and/or offer made in his ad, and therefore his advertising was not ethical."

TESA-MILWAUKEE LOOKS AT APPRENTICE PROGRAM

TESA-Milwaukee is considering some sort of apprenticeship plan which would take students or graduates from the local Milwaukee Vocational School and give them on-the-job training. TESA News pointed out that "the TV service industry is in need of good technicians; students who have had 2 years of day school training or 4 years of night school training would make ideal material. Such students have a good theoretical background and generally need only the experience of the shop and field service to make them into well rounded TV service technicians...."

TV TECH ACQUITTED

A San Bernadino TV technician was acquitted in Municipal Court there after being charged with fraud in the repair of a TV set. Two similar cases against other men were dismissed.

The Radio-TV Technicians Association collected information on the basis of repairs allegedly made on "gimmicked" sets. The city then charged the three men. The judge released them because he was "impressed" when one of the technicians performed a repair in court which two expert electronic instructors had told him could not be done.—Scott Radio Supply Radiogram, Long Beach, Calif.

LICENSING ALTERNATIVE

W. C. Pecht, editor of TEAM (Mo.) News, writes, "Now that I've said I'm agin it (licensing), it behooves me to offer an alternative to it. . . . So here are a few:

"Stop knocking your competitor; make competition, don't just meet it; improve your technical ability and your management methods; improve your public relations by recognizing the fact that the customer pays the bills, treat him as such; strengthen the associations by increased membership and attendance at meetings; adopt an advertising code of ethics and protect it; seek a method of voluntary certification, publicize it and the code of ethics; support and cooperate with local distributors; dress and act like a reputable technician and business man;

protect the name of your competitor as though it were your own.

"Just as a license itself cannot cure every ill of the industry, the alternative cannot be a thing in itself; it must be many things. . . ."

MONEY-MAKING MAN

From the TESA Milwaukee News: "How can I make a better living in TV service? If your shop is average, you have about \$600 invested in technical literature and less than \$5 in books on business management. . . . Any boy can be a technician; it takes a man to make money doing it. . . . TESA meetings provide you with an opportunity to learn successful business techniques. There probably is no other place you can learn so much so quickly.

"I would like to cite John Lukich, of Lukich TV, as an example of those who learn at our meetings. John has been a member for only a year. But has doubled his income in that year. John is willing to share this information with anybody. Call him for the best testimonial on what he learned."

KC REPLY TO TEAM SUIT

The City of Kansas City, its Mayor, the Chief of Police and the Commissioner of Revenue denied that the recently enacted technician-licensing ordinance violates either the Federal or State constitution. This was in answer to a suit against the city and its officials by two members of TEAM (The Electronic Association of Missouri) seeking to invalidate the law.

TSA-Kansas City, NATESA affiliate, entered the case as a friend of the court to support the ordinance.

CERTIFICATION IN B.C.

First step toward certification of service technicians in British Columbia is a voluntary written and bench examination; successful technicians get a certificate showing they've passed. Before taking the exam, a man must prove he's been active in the trade for 4 years.


The Provincial Department of Labour in Vancouver, B. C., writes, "We have just finished administering the examination to a small group and so it is too soon for anyone to analyze the benefits or limitations of the project..."

The department set the program up at the request of technicians' groups seeking increased recognition and improved technical standards.

TOO MANY TV TECHS?

From the Mo-Kan News comes this provocative discussion, ". . . how is it that you can't hire a good bench man at the drop of a hat? Why can't you hire them at the snap of your finger if there is an oversupply? Some shop owners say there is a definite shortage of good men. The question is what constitutes a good man?"

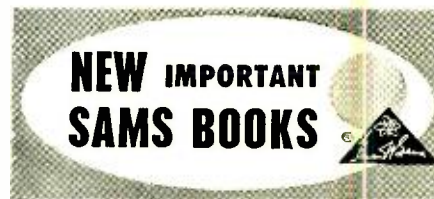". . . in 1948 there were only 200,000 TV sets in the whole country. It is hard to say how many technicians there



"TV Servicing Shortcuts"

by Milton S. Kivier



ALL-NEW EDITION! Famous best-seller, completely revised, more valuable than ever. Helps the technician sharpen his service techniques by use of the case-history method. Shows through 69 case histories how to quickly solve commonly recurring TV service problems. Outlines trouble symptoms; gives step-by-step explanation of how to track down, localize and solve the trouble in any TV set. Includes a number of transistor and printed-board servicing problems. A truly invaluable trouble-shooting guide. 104 pages; 5½ x 8½". Only..... \$150

"ABC's of Ham Radio"

(How to get your novice license)

by Howard S. Pyle



Here's all you need to know to qualify for the radio amateur novice license. Written by an expert, formerly a government License Examiner, and teacher of a course on the subject. Includes typical questions from novice exams to illustrate points. Chapters include: About the Exam; The Radio Telegraph Code; Basic Electricity; Radio Power Supplies; Electrical Measurements; The Radio Transmitter; Legal Aspects of Operation; Examination Procedure; You're On the Air; etc. Best book of its kind—written so everyone can understand it. 112 pages; 5½ x 8½". Only..... \$750

MORE NEW BOOKS

"Two-Way Mobile Radio Handbook"

Author Jack Helmi presents the first really comprehensive treatment of the subject of mobile radio. Ten complete chapters cover: basic systems; types of receivers available; transmitters; control systems; antenna systems; power; servicing of mobile radios; etc. Written especially for those who service, install and maintain mobile equipment. 240 pages; 5½ x 8½". Only..... \$3.95

"Servicing TV Video Systems"

The third volume in Jesse Dines' series of comprehensive TV circuit coverages. Discusses operation of the video-IF amplifier, video-detector, video-amplifier, and the picture-tube stages of a TV receiver. Includes data on color sets and recent changes in video systems. Really helps you master the modern video system; gives you trouble-shooting know-how, helpful servicing hints, methods for improving fringe area reception, and picture tube substitution data. Owners of Dines' previous books ("Servicing TV Sync Circuits" and "Servicing TV Sweep Systems" will want to add this valuable book to their library. 264 pages; 5½ x 8½". Only..... \$3.95

HOWARD W. SAMS & CO., INC.

Order from your Sams Distributor today, or mail to Howard W. Sams & Co., Inc. Dept. C-20 1720 E. 38th St., Indianapolis 6, Ind.

- Send me the following books:
- "TV Servicing Shortcuts" (TK-2)
 - "ABC's of Ham Radio" (HAP-1)
 - "Two-Way Mobile Radio Handbook" (MR-1)
 - "Servicing TV Video Systems" (VID-1)

\$.....enclosed. Send FREE Book List

Name.....

Address.....

City.....Zone.....State.....

(Outside U.S.A. priced slightly higher)

"TAB" Tubes Tested, Inspected, Boxed

Six Months Guarantee!! No Rejects!

NEW & Used Gov't & Mfrs. Surplus!

Orders \$10 or more. Receiving tapes only ppd. 48 states

0A2	.80	6B16	.69	12A7E	.59	18S1	1.00
0B2	.65	6BK7	.59	12AT7	.89	11Z76	1.10
0C3	.59	6BL7	1.25	12AU6	.69	4-65A	16.00
0D3	.55	6BM7	.98	12AU7	.69	20D1	2.78
0Z4	.59	6BQ6	1.19	12AX7	.79	30D3	3.85
1A7	.89	6BZ7	1.25	12BA6	.65	717A	5.81
1B3	.74	6B4	.74	12BF7	.69	4-250	35.00
1R5	.78	6C5	.69	12BD6	.59	4-250	35.00
1S4	.78	6C8B	.80	12BE6	.59	4E27	7.00
1T4	.78	6CDB	1.49	12BF6	.59	4PR60	29.50

Sold by "Buyout"

1U4	3/81	6H6	3/81	12BH7	.99	4X150G	\$15
1U2A	.73	6J5	.53	12BY7	.98	4X250	35.00
1X2A	.98	6J6	.38	12BZ7	.98	4X500	38.00
3Q4	.68	6K6	.59	12CU6	1.45	5B1P	4.98
3Q5	.86	6K7	.74	12SA7	.94	5B4	4.98
3S4	.68	6L6	1.19	12SQ7	.89	5T	4.00
3V4	.83	6S4	.59	12SH7	.75	100T	7.00
3V4	.98	6S8	.69	12SJ7	.75	316A	5.81
5U4	.99	6SA7	.69	12SK7	.64	388A	3/81
5V4	.80	6S7	1.19	12SQ7	.89	515B	16.00

Wanted Surplus Electronics from schools & I.

5Y3	.59	6SC7	.79	19B6	2.15	450T	12.00
6B4	.59	6SQ7	.79	19T8	1.16	807	1.00
6C7	.74	6SH7	.69	25Z5	1.19	809	9.00
6A6	.89	6SJ7	.69	25L6	.69	811A	4.40
6AG7	.99	6SK7	.72	25W4	.77	812	3.00
6AK5	.99	6SL7	.89	25Z5	.69	813	9.00
6AL5	2/81	6SN7	2/81	25Z6	.75	814	3.45
6A5	.63	6SQ7	.74	EL34	3.49	815	2.75
6A57	3/81	6S7	3/81	6S7	2.49	826	2.50
6AT6	.49	6T8	.98	35L6	.69	829B	8.00

Wanted 504 U tubes! Top \$ \$ Paid

6AU4	1.10	6U8	.98	35W4	.49	832A	7.00
6AU5	1.19	6V6GT	.70	35Y4	.69	866A	2.75
6AU6	.89	6W4	.79	35Z5	.69	812S	9.00
6AX4	.79	6W6	.80	50A5	.69	6146	4.00
6BA6	.59	6X4	2/81	50B5	.69	5879	.98
6B7	1.00	6X5	.69	50C5	.69	6123	9.00
6DD6	.69	6Y6	.97	50L6	.69	6550	3.90
6EE6	.59	7N7	.80	K766	3.29	5654	1.00
6EG6	1.39	12AL5	.59	815	.59	894	12.00
6BH6	.72	12AQ5	.73	80	.59	7193	10/81

TUBES WANTED! WE BUY! SELL & TRADE!

NEW "TEKSEL" SELENIUM RECTIFIERS

FULL WAVE BRIDGE RECTIFIERS. ONE YEAR GTD!

AMP. 18VAC 36VAC 72VAC 144VAC

CMT. 14WV 27 49 56V 256V 116 809

1AMP	\$ 1.30	\$ 2.00	\$ 4.90	\$ 9.45
2AMP	2.15	3.00	6.25	12.30
3AMP	2.90	4.00	8.60	16.75
4AMP	4.15	5.00	11.00	20.90
10AMP	6.10	8.00	18.30	36.15
15AMP	9.90	19.00	40.00	66.60
24AMP	15.00	29.45	57.50	108.45

NEW SILICON 500MA RECTIFIERS LO PRICED GTD!
Input Working Range RMS/ACV Res. or Cap.

rms/piv	35/50	rms/piv	70/100	rms/piv	140/200	rms/piv	210/300
280/400	78c	350/500	\$1.00	420/600	\$1.26	490/700	\$1.50
560/800	\$1.59	630/900	\$1.89	700/1000	\$2.58	770/1100	\$3.12

Use in Bridge or C.T. up to 750ma dc
General Purpose 400PIV @ 250ma Special 2 for \$1;
25 for \$10. *Ppd. 48 states TopHats only!

YOUR BEST BUY! "TAB" FOR BARGAINS

2N277 \$1.50; 2N278 \$3.50; 2N441 \$3; 2N442 \$3;
"BRUSH" TAPE 1200' BEST GRADE \$150 @ 4 for \$9;
"BRUSH" TAPE 2400' FL. MYLAR BEST GRADE \$1.10;
3 for \$8; 18150 Hitachi CHEMICO 18150 MIB \$7 @ 2;
2 for \$9; 18150 Hitachi CHEMICO 18150 MIB \$7 @ 2;
18150 NEW ORIG. SIG CORPS RECALIB & RECON-
DITIONED OSEAS PKCD NEW CALIBRATION BOOK
MINT CONDIN \$1.10; NEW RC1336 29.90 @ 36.90
MCA TRANS-IVER WITH 6A12V SUPPLY & SPARES
OSEAS PKCD \$89; 1012-USA 200-100M's RCRV Less
Tubes \$25; AN-MIR2 RCRV 6000 (CRD) less tubes
\$1.50. SEND FOR NEW CATALOG 25c.

DC POWER SUPPLIES FOR TRANSISTORS!

New low-cost filtered 0.5% Ripple Power Supply. Same as specified in Transistor Manual G-E. Ideal for Powering transistor circuits, small in size!

12 VDC at 150 Ma-T12V150M..... \$ 8
25 VDC at 150 Ma-T25V150M..... \$10
40 VDC at 1 Amp-T10V1A..... \$19

TRANSISTORIZED DC POWER! HI-EFFICIENCY DC TO DC 450 VDC "TABSTAT" KIT or BUILT!

Output 450 & TAP 250VDC at up to 150 MA/Up to 70 Watts 80% efficiency; Ripple 0.25% low idle current one amp silicon rectifiers, oil condensers, toroid transformer, fused & short circuit proof. Regulation 5% at 20 to 100% load! Small in Size! Quiet! Light wgt! Lo-priced etc! "TABSTAT" TR1215CB built \$38. Pre-Assembled U-Built kit TR1245CK only \$33. "TAB-STAT" 450VDC @ 100MA/12V in TR1225CB \$30. Kit TR1225CK \$27. 6V impt TR6125CB \$30. Kit TR625CK \$27.

KITS "TAB" THE BEST KITS!

- All Kits Come with Popular Line of 100+ Tubes
- Kit 2 Eng. Parallel Resistors
- Kit 35 Precision Resistors
- Kit 10 Switches
- Kit 75 Resistors 1/2 1/4W
- Kit 150 Carbon Resistors
- Kit 25 Panel Lamps
- Kit 12 Electrolytic Cond's
- Kit 56 Tube Sockets
- Kit 65 Tubular Cond's
- Kit 500 Lug's & Eyelets
- Kit 10 Bathub Oil Cond's
- Kit 5 lbs. Surprise Pkg.
- Kit 10 Xmtrr Mica Cond's
- Kit 3 Phone/Patch Xfms
- Kit 3 Searchlights
- Kit Circular Slide Rule
- Kit 12 Algrt Clrp Ass't'd.
- Kit 5 Sub-Min Tubes
- Kit 40 Standoff Insulators
- Kit 35 Power Resistors
- Kit 75 Mica Condensers
- Kit 5 Crystal Diodes
- Kit 100 Fuses, Assorted
- Kit 100 Ceramic Cond's
- Kit 10 Germanium Diodes
- Kit 5 FT243 Xtal Holders
- Kit 5 Silicon Diodes
- Kit 5 Microswitches
- Kit 4 Ass'd Rectifiers
- Kit 2 PNP Transistors
- Kit 450 Ft. Pickup Wire
- Kit 2 Veeder Counters
- Kit 2-Computer Toroids
- Kit High Gain XTA Mike

BUY 10 KITS—GET ONE FREE! EACH KIT 99c

"TAB" TERMS: Money Back Guarantee! Our 15th year. \$2 min. order F.O.B. N.Y.C. Add shpg charges or for C.O.D. 2-50¢. Prices shown subject to change.

111-GF LIBERTY ST., N.Y. 6, N.Y.
Send 25c PHONE: RECTOR 2-6245 for Catalog

TECHNICIANS' NEWS (Continued)

were, but 1 year later there were five times as many sets. Were there five times as many technicians? By 1950, we had four times as many sets as in 1949, and 20 times as many as in 1948. We don't know if there were 20 times as many technicians in 1950 as 2 years before, but we doubt it. By the end of 1958, there were over 200 times as many TV receivers in use as in 1948. Were there 200 technicians by then for every single one only 10 years earlier?

"In 1948 there were no transistor radios and the record player business was only a fraction of what it is today. Many of our customers today have two or more TV sets. Hospitals, hotels and motels have them in abundance.

"Whether there are too many service technicians is certainly a controversial question. However, most people admit there is a need for good men..."

SENDING BOYS TO DO MEN'S...

Shortage of TV technicians is causing Los Angeles service dealers to recruit high school students as repair technicians, according to a report in *Home Furnishings Daily*.

Milton Aller, of Tops TV & Hi-Fi, said that TV technicians were being drained off by industry. Another prominent service dealer, Murray Gibin, Universal TV Co., Inc., said the trouble stemmed from manufacturers who educate the public to expect troublefree

sets. As a result, retailers cannot include service charges in sales prices, the customer is unhappy about service costs and the service dealer has to try to get whatever service personnel he can.

ESFETA ELECTS

Empire State Federation of Electronic Technicians Associations, Inc. elected new officers and voted to accept a new association from St. Lawrence County, increasing its membership to 15 associations.

Incoming officers are Irving Toner, president; Robert Henderson, vice president; O. Capitelli, secretary; Mel Cohen, corresponding secretary.

KNOXVILLE TECHS FORM GROUP

More than 30 TV service dealers have applied for membership in a newly formed service association which hopes to "eliminate misrepresentation by marginal service companies."

The BBB (Better Business Bureau) cooperated with radio-TV people in the formation of the group, which elected Lonnie Dispennette, of the local Sears Roebuck TV service department, president.

DON'T DO-IT-YOURSELF!

A parts jobber in Detroit, Mich., takes local ads saying, in part, "Open Letter To TV Set Owners—You



FIX OLD RADIOS IN A JIFFY!

Fix 'em good as new... without lost time or needless testing

Often, it takes more time than it's worth to fix old radios... but NOT when you own this 3 1/2-pound, 744-page RADIO TROUBLESHOOTER'S HANDBOOK! Just look up the old make and model. Handbook tells exactly what is likely to be wrong—shows exactly how to fix it. No wasted time. No needless testing. Gives common trouble symptoms for over 4,800 old home receiver models, auto radios, and record changers made from 1925 to 1942 by 202 manufacturers. Includes old tube and component data no longer available from any other source.

CUT SERVICE TIME IN HALF!

Even beginners can repair old sets which might otherwise be thrown away because service data is lacking! Handbook more than pays for itself first time you use it! Covers old sets made by Airline, Apex, Arvin, Atwater-Kent, Belmont, Bosch, Brunswick, Clarion, Crosley, Emerson, Fada, G-E, Kolster, Majestic, Motorola, Philco, Pilot, RCA, Silvertone, Spartan, Stromberg and dozens more. The only service guide of its kind still in print.

10 DAY FREE EXAMINATION

Dept. RE-30, RINEHART & CO., Inc.
232 Madison Ave., New York 16, N. Y.

Send RADIO TROUBLESHOOTER'S HANDBOOK for 10-day examination. If I decide to keep book, I will then send \$6.95 plus postage. Otherwise, I will return book promptly and owe you nothing.
(SAVE! Send \$6.95 with order and we pay postage. Same 10-day return privilege with money refunded.)

Name _____
Address _____
City, Zone, State _____
OUTSIDE U. S. A.—Price \$7.45 cash with order only. Money back if you return book in 10 days.

THE BATTERY THAT'S USED IN GUIDED MISSILES NOW RELEASED AS GOVERNMENT SURPLUS



For Photography, Aircraft, Models, Searchlights, Radios, etc.
\$1.95 EA. Postpaid

Sintered-plate Nickel-Cadmium alkaline storage batteries designed for "NIKE" Missile and now surplus due to design change. A lifetime battery with no known limit on service over 5000 recharges on test without loss of capacity. Other features: Virtually indestructible, compact & lightweight, withstands heavy shock and vibration. Flat voltage curve during discharge retains charge year or more. High discharge rate up to 50 amps for this cell, no corrosive fumes to harm clothing or equipment, spill-proof construction, discharge in any position. Indefinite storage without deterioration, operates in temperatures —60°F to +200°F. Each cell is approx. 6 ampere hour capacity. Nominal voltage per cell is 1.2 volts. (A 6 V. battery requires 5 cells.) Cell size 6 7/8" H. x 2 1/2" W. x 1 1/2" T. Wt. 6 oz. Contains Potassium-hydroxide (30%) electrolyte. Negligible loss during lifetime service. Add only distilled water once a year. A fraction of Government cost.

Used Test Cells \$1.95 ea. Postpaid
Brand New Cells 2.95 ea. Postpaid
24 V. Battery. (20 cells in metal case) used \$40. new \$60.

ALL CELLS GUARANTEED TO YOUR SATISFACTION OR MONEY REFUNDED (LESS POSTAGE). Plastic battery cases may have slight cracks. Repaired easily with household cement. Or you may add 25¢ to price of each to insure uncracked case.

ESSE RADIO COMPANY, Dept. M-6
42 W. South Street Indianapolis 25, Indiana

Please mention RADIO-ELECTRONICS when answering ads.

BEST IN HI-FI VALUES!

NO DELAY SERVICE All orders rushed to you in factory-sealed cartons. Write for free catalog.

audion 25-E Oxford Road Massapequa, New York

wouldn't take a doctor's prescription to a hardware or grocery store—yet many people take their TV tubes to such places in the mistaken belief that they can find their troubles. . . This practice is costing the general public thousands of dollars annually in replacement of tubes that may not need replacing."

WANTS JOBBERS CLOSED ON SATURDAY

TESA—St. Louis reports a letter saying, "A lot of dealers want the parts distributors to close Saturdays. The dealers say that having them open on the weekend lets too many tube sales and other items go to the distributors when they should go to dealers.

"I for one would like to see them close on Saturdays. How about all dealers getting together and asking the distributors to close on Saturdays?"

ANTENNA FOULS POWER LINE

In Carbondale, Pa., an improperly installed TV antenna fell onto public-utility power lines, disabling electrical power service in 450 homes for several hours. All lights and refrigerators were out of use during the mishap. The power lines fell down on a dairy truck, but no one was injured.

Subsequently FRTSAP (Pennsylvania Federation of Radio & TV Service Associations) voted to present standards of antenna installation and main-

tenance to the state and to utility companies. The group is pressing to incorporate the standards into the technician licensing law. They'd also like to see antenna installations inspected by an Underwriters group.

NATESA URGES SELECTIVE BUYING


The National Alliance of Television & Electronic Service Associations called on its members, during its Chicago convention to buy parts only from manufacturers who do not compete with the independent service technician. NATESA delegates also resolved to recognize only the standard 90-day warranty on parts and tubes and 1 year on picture tubes. No factory labor warranty is to be recognized. Finally, the group asked manufacturers to register all TV sets by number and issue numbered registration certificates to owners. Comment from set makers held out little hope of accomplishing this last request.

TEXAS TECHNICIANS' PAY

The US Department of Labor has released a survey dealing with the pay structure in TV service shops in Dallas, Tex. It found that the average gross pay for bench technicians was \$81.50, for outside men \$75.50. The highest-paid group included the men who worked both at the bench and outside. They averaged \$92 a week. END

ORDER YOUR ENCLOSURE KITS FROM HOMEWOOD

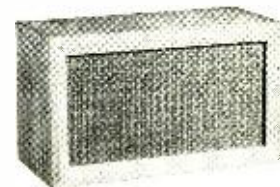Bring out the best in your speakers... save dollars in assembly and finishing costs... get the fun of "doing-it-yourself"!



ONLY \$11.95


MODEL 6

Factory assembled, ready for finishing. Makes your 8" speaker sound like a million! Made of 1/2" hardwood ply, beautifully grained and smoothly sanded. 10" h. x 16" w. x 9" d. 9 lbs. Order two for matched stereo performance.



MODEL 1

4 1/2 cubic feet of baffle space assures you crispest, cleanest bass response from any 12" speaker system. Full-grained white birch ply, with pre-attached bracing cleats for easy assembly. Kit includes everything you need for assembly. 29" h. x 20" w. x 21 1/2" d. (5" legs). 25 lbs. \$18.95

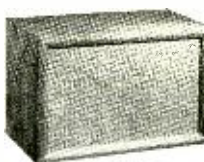

MODEL 2

Clear-grained on four sides for bookshelf or floor use. Acoustically accurate for 12" systems, with adapter board for 8" speakers. Sturdy, 3/4" ply eliminates unwanted resonances, improves bass response. 14" h. x 21" w. x 11 3/4" d. 20 lbs.

In Birch \$14.50
In Walnut \$19.95

MODEL 13. Finishing kit; includes generous quantities of everything you need to do a professional, long-lasting finishing job, plus brush, sandpaper and easy-to-follow instructions. Specify: Mahogany, Walnut, Blonde, Oak, Fruitwood, Maple, Cherry, Ebony, Natural. \$3.88

Ten-day money-back guarantee. All items shipped freight collect. Please send check or M.O. (No COD's)

HOMWOOD INDUSTRIES, Inc.
26Y Court Street, Brooklyn 1, N.Y.

Please send me:
() Model 6 () Model 1 () Model 2 (Birch/Walnut)
() Model 13
() Homewood catalog

I enclose remittance in the amount of \$ _____

Name _____

Address _____

City _____ Zone _____ State _____

**GRIPS THE SCREW!
DRIVES IT TOO!**

QUICK-WEDGE SCREW-HOLDING SCREW DRIVER

2" to 14" blades, 4 bit sizes. Available with shock-proof plastic covered tubing.

Ask For It At Your Dealer

KEDMAN CO., 233 S. 5th W., Salt Lake City, Ut.

"LESS WORK HOURS — MORE MONEY with E-Z-HOOK!"
Jed Motz
Audio Engineer, Cincinnati, Ohio

"In my business of designing and building Hi-fi equipment, I've saved many hours of work using E-Z-Hook Test Connectors. NO MORE SOLDERING or unsoldering wires when I use E-Z-Hook Sub Connectors to connect component parts in experimental setups and bread-boarding. They connect and disconnect so easily and I'm always sure of quick, positive connections. WHEN CHECKING out circuits, I save lots more time, too, with E-Z-Hook Tips and Clips. Hooking up the Scope, Meters, Speakers, etc., with these self-holding connections, leaves my hands free. And, since they can't pull off, I don't have delays and aggravations caused by loose intermittent test connections that used to jump off and short. Believe me, the hours I saved put dollars in my pockets."

EXCLUSIVE E-Z-HOOK DESIGN!

EASY TO USE! GUARANTEED!
The self-adjusting stainless steel hook and nylon insulator clamps firmly in even hard-to-reach places. Eliminates loose intermittent connections and adjacent shorts.

AT YOUR FAVORITE PARTS DISTRIBUTOR
From 49¢ up

ORDER THROUGH YOUR PARTS DISTRIBUTOR
E-Z-HOOK TEST PRODUCTS
Dept. G3, 1536 Woodburn Ave.
Covington, Ky.

Canadian Rep. Len Finkler Ltd., Toronto, Ont.

LOOKING?—you stand a better chance of finding what you want if you advertise in

RADIO-ELECTRONICS Opportunity Adlets.

See details on Page 135

GERNSBACK LIBRARY

Low-cost, paper-covered books on all phases of TV, radio, audio-high fidelity and practical electronics

ON SALE AT ALL BETTER PARTS DISTRIBUTORS

PRECISION PERFORMERS



carbon-deposited RESISTORS

When the application calls for accuracy and stability you'll find Aerovox Precision ($\pm 1\%$) Carbon-Deposited Resistors fill the bill perfectly. Manufactured under exacting quality control specifications to assure excellent performance even under adverse operating conditions.

CARBOFILM RESISTORS . . . for wide use in circuits where accuracy and economy are factors. Units are protected by a specially formulated Aerovox coating against environmental conditions. Stocked in 300 values in following ratings:

Type	Sizes	Min. Ohms	Max. Meg-ohms
CPS- $\frac{1}{2}$ watt	0.162D x $\frac{1}{2}$ L	7	2
CP- $\frac{1}{2}$ watt	0.230D x $\frac{1}{2}$ L	3	5
CPL- $\frac{1}{2}$ watt	0.230D x $\frac{1}{2}$ L	5,100,000	7.5
CP-1 watt	0.293D x $\frac{1}{2}$ L	10	15
CP-2 watt	0.293D x $2\frac{1}{2}$ L	50	100

CARBOMOLD RESISTORS . . . encapsulated in a strong reinforced moisture and heat resistant plastic these units offer new standards of reliability. Over 500 standard values available from stock as follows:

Type	Sizes	Std. Min. Ohms	Std. Max. Meg.
CPM- $\frac{1}{2}$	$\frac{1}{2}$ x .735	10	2.49
CPM-1	$\frac{1}{2}$ x $1\frac{3}{4}$	10	5.11
CPM-2	$\frac{1}{2}$ x $2\frac{1}{4}$	30	10

All units marked with type number, RN Number, value and tolerance. Available for "off-the-shelf" delivery from your local Aerovox Distributor.

AEROVOX CORPORATION
DISTRIBUTOR DIVISION
NEW BEDFORD, MASS.

Trademark

new PATENTS


REDUCING RECOVERY TIME

Patent No. 2,894,152

Richard L. Anderson, Syracuse, N. Y. (Assigned to IBM, New York, N. Y.)


Recovery time is the interval required before a conducting diode can be made to block. It is a disadvantage which limits a diode's high-frequency response.

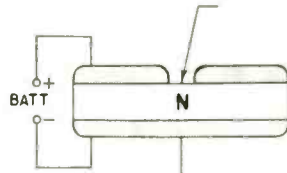Here a metallic surface is coated or soldered



to the diode (Fig. 1), leaving only a small opening for the point contact. A dc bias is im-

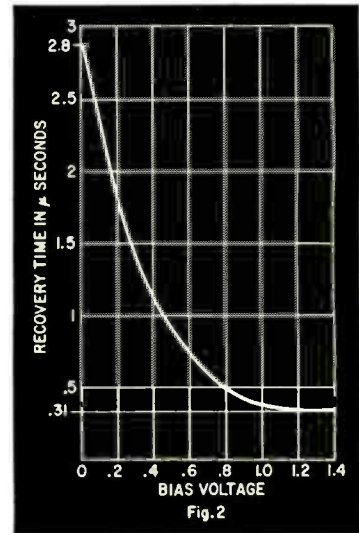pressed across the diode to remove positive carriers from the semiconductor. This leaves



few charges to carry a flow when blocking bias is applied.

In a typical diode, 2.5 mm square and 0.75 mm thick, a 1.4-volt bias reduced recovery time from 2.8 to 0.31 μsec (see Fig. 2).


CAMERA-RADIO-TELESCOPE

Patent No. 2,899,879

Rena Lopez, New York, N. Y.

A single box carries all three of these items: camera, radio and telescope, making it ideal for picnics, vacations, sports. The radio and camera

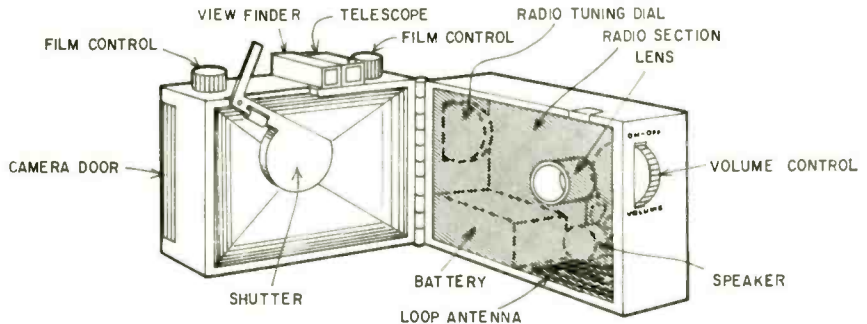film. When the handle is swung sideways, it opens an aperture and allows light to pass through the lens to expose the film.



lens are mounted in the right-hand section of the hinged box (see diagram). The left portion carries the camera and telescope. When the box is closed, the lens fits into place in front of the

A hinged door permits access to the film compartment when necessary. The telescope is mounted alongside the camera viewfinder next to the film control.


AUDIENCE SURVEY SYSTEM

Patent No. 2,903,508

J. L. Hathaway, Manhasset, N. Y. (Assigned to RCA)

This invention makes it possible to find out the channel to which a TV receiver is tuned, without ringing doorbells or phoning. A mobile unit moves past the house, and meters indicate

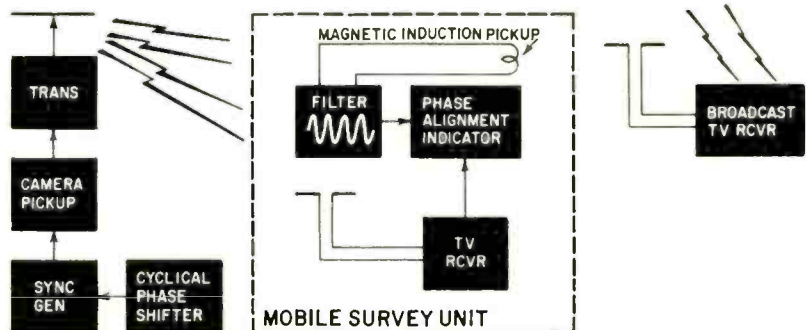set (15.75 kc and harmonics). The respective pulses are clipped, broadened and combined in a phase comparator. Maximum output occurs only when the pulses are exactly in step.



what the occupants are viewing. It works on the fact that when a receiving set is properly tuned, the phase of its horizontal sync frequency is synchronized with that of the transmitter.

The mobile unit tunes in the broadcast transmitter and also picks up radiation from the TV

Transmitters in the same area are generally synchronized with a common power source so to assure that each transmitter in the area has a distinct phase of its own, each should include some means for continuous phase shift at a slow rate.


END

GET *more!* DO *more!* MAKE *more!*

PROFIT PROFESSIONALLY ON EVERY CALL WITH

NEW **B&K**

**LOW-COST PROFESSIONAL
Model 550 DYNA-QUIK
DYNAMIC MUTUAL CONDUCTANCE TUBE TESTER**

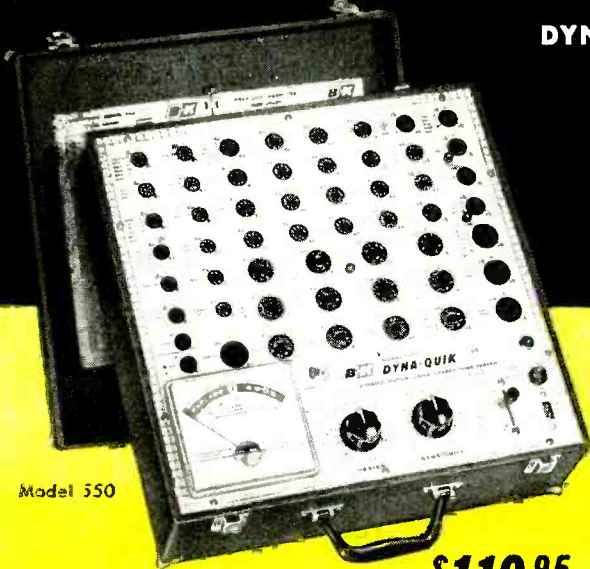

Model 550

NET **\$119⁹⁵**

Every service-technician now can easily check tubes the B&K professional way! Only with a *genuine dynamic mutual conductance tube tester* can you make a complete and accurate test under the actual dynamic operating conditions of the TV set. The compact new "550" is not just an emission checker. *It completely checks more tubes faster—with laboratory accuracy.* And the cost is so amazingly low, it pays its way over and over again! Take a tip from thousands of professional servicemen—*use B&K Dyna-Quik.* There is nothing like it.



Get More for Your Money
—IN SPEED, ACCURACY, AND VALUE



Save Customers
—SAVE CALL-BACKS, SAVE COST



Sell More Tubes
—MAKE MORE MONEY PER CALL

MODEL 550 DYNA-QUIK TUBE TESTER


Tests Each Section of Dual-Section Tubes Separately

Great new value in professional quick-check at small cost. Provides **more** tube sockets to test **more** tubes faster. Accurately checks most of the TV and radio tubes usually encountered in everyday service work. Tests each section of dual-section tubes separately. **Measures true dynamic mutual conductance.** Checks tubes for shorts, grid emission, gas content, and leakage. Completely tests each tube in seconds, checks average TV set in a few minutes, in home or shop. One switch tests everything. Fast, convenient reference listings on socket panel. Patented circuit provides automatic line voltage compensation. 7-pin and 9-pin straighteners on panel. Handsome, luggage-type carrying case. Net, **\$119⁹⁵**

MODEL 650 DELUXE DYNA-QUIK

Today's Finest Portable Tube and Transistor Tester

Accurately checks over 99% of the tubes most widely used in television receivers, plus popular home and portable radio tubes. Tests over 600 tube types. Lists over 125 most popular tube types, with settings, on socket panels for maximum operating speed. Complete listing in fast, index-type selector. **Measures true dynamic mutual conductance.** Tests each section of multiple tubes separately for GM, Shorts, Grid Emission, Gas Content and Life. Includes 16 spare sockets and ample filament voltages for future new tube types. **Transistor Section** checks transistors, diodes, and selenium rectifiers. Luggage-type carrying case. Net, **\$169⁹⁵**

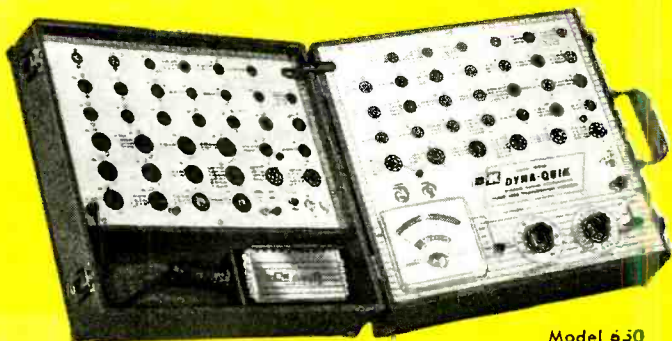

Model 650

B&K

B & K MANUFACTURING CO.
1801 W. BELLE PLAINE AVE • CHICAGO 13, ILL.

Canada: Atlas Radio Corp., 50 Wingold, Toronto 10, Ont.
Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.


See Your Distributor or Send Now for Bulletin ST24-E

NEW TUBES and SEMI-CONDUCTORS

TUBES and semiconductors are about equally represented this month. We start off with two tetrode transistors, go on to a couple of TV tubes, touch on a solar cell and silicon-controlled rectifiers and close with another TV tube and a quartet of silicon transistors.

3N36, 3N37

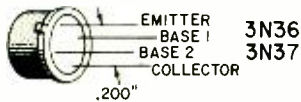Two germanium meltback n-p-n tetrode transistors designed for high-



frequency use as an amplifier, oscillator or mixer. The 3N36 is recommended for use in the frequency range from


30-100 mc; the 3N37 for 100-200 mc. Both make good wide-band video amplifiers from low frequency to 10 mc.

Absolute maximum ratings of these General Electric tetrode transistors at 25°C. are:

V_{CB} (either base)	7
V_{EB} (either base)	2
V_{CE}	6
I_C (ma)	20
I_E (ma)	20
I_{B2} (ma)	2
P_{Total} (mw)	30

6EV7

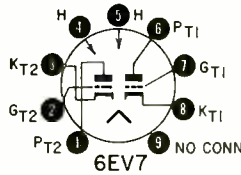A high- μ twin triode in a 9-pin miniature envelope designed for use as



a relay-control tube in remote-control tuning units of TV receivers.

The tube is processed for long periods of operation under standby (plate-current cut off) conditions. It features slotted micas to assure low interelectrode leakage, special cathode sleeve material to minimize cathode interface resistance and interelectrode leakage and a separate base pin for each cathode.

Maximum ratings of the RCA 6EV7

in relay control service (each section) are:


V_P	300
V_G (pos bias value)	0
I_K (ma)	20
P_P (watts when on time exceeds 30 seconds in any 2-minute interval)	2.5
(watts when on time does not exceed 30 seconds in any 2-minute interval)	4.5

In class-A1 amplifier service, the tube has a transconductance of 5,200 μ mhos and an amplification factor of 60 (plate voltage, 250; plate current 9.2 ma.).

6GM6

A semi-remote-cutoff pentode in a 7-pin miniature envelope, designed for use as an if amplifier in gain-controlled picture if stages of TV receivers. The 6GM6 has separate base pins for grid 3 and the cathode. This permits the use of an unbypassed cathode resistor to minimize changes in input conductance and input capacitance with bias.

Characteristics of the RCA 6GM6

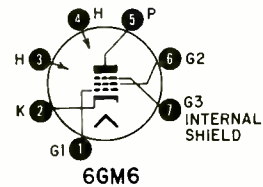

UPPER STRATA STRATEGY!

Friend of ours who always attends the sessions in the lecture halls, starts on the Fourth Floor with Production Items . . . and works his way down to Components on the First Floor. Says his feet tell him it's easier to come down than to go up! And he never misses a trick this way. Sounds like good engineering logic. Why don't you join him this year . . . and see if it doesn't work for you!

Will Copp
Show Manager

COME TO THE COLISEUM...

the place to look for
NEW IDEAS IN RADIO-ELECTRONICS

1960!

Here, in New York City's Coliseum, is where you'll find the very latest information about the giant, radio-electronics industry's plans for the future.


Here, you'll rub shoulders with over 60,000 of your fellow radio-electronics engineers. Here, you'll see 950 exhibits, representative of 80% of your industry's productive capacity, covering equipment, component parts, instruments and production. Here, you'll hear your choice of more than 200 papers to be given during the CONVENTION.

Yes, here — and only here — is your once-a-year chance to see and profit by all the NEW IDEAS IN RADIO-ELECTRONICS, 1960 gathered in one place. Attend the IRE NATIONAL CONVENTION AND RADIO ENGINEERING SHOW. Come to the Coliseum!

The IRE NATIONAL CONVENTION
Waldorf-Astoria Hotel
and The RADIO ENGINEERING SHOW
Coliseum, New York City

MARCH 21, 22, 23, 24

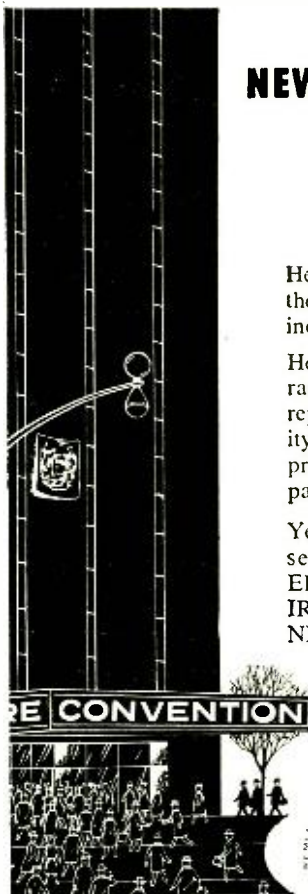The Institute of Radio Engineers
1 East 79th St., New York 21, N. Y.




when used as a class-A1 amplifier are

V_p	125
G3 connected to cathode	
V_{G2}	125
R_k (ohms)	56
R_p (k ohms)	200
gm (μ mhos)	13,000
I_p (ma)	14
I_{G2} (ma)	3.4

N2009

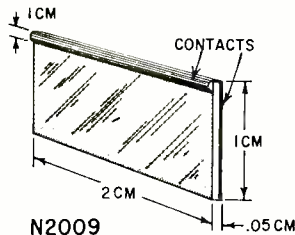Silicon solar cells with 9% efficiency available as single cells or in ruggedized shingle arrays for space vehicles, missiles and industrial applications. The diffused-junction cells measure




N2009

1 x 2 x .05 cm. The Texas Instruments N2009 will deliver up to 22.5 mw at 56.5 ma and 0.4 volt per cell when operated under sunlight levels found in near space. All cells have a silicon monoxide coating to reduce reflection losses. Glass covers can be provided to give increased emissivity in the 4-14-micron range. Cells have alloyed contacts for fabrication into multiple arrays.

X16RC2—X16RC20

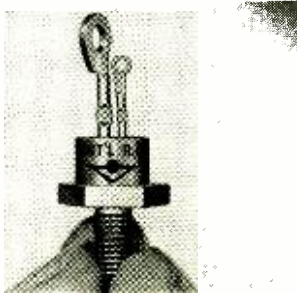Silicon-controlled rectifiers (thyrodes) for applications requiring load currents up to 16 amps and blocking voltages from 20-200, made by International Rectifier. This new series is capable



of controlling 16 amps of current in static switching, dc motor control, variable and regulated dc power supplies, welding control, ignition firing and similar switching applications.

The three-junction semiconductor unit switches rapidly to a conducting state when a signal is applied to its third (gate) terminal, or when its critical breakover voltage is exceeded.

6GN8, 8GN8

A high- μ triode and a sharp-cutoff pentode in the same 9-pin envelope. The triode section is designed for use as a voltage amplifier or sync separator. The pentode section features a controlled plate knee characteristic and is designed for video amplifier service. The 8GN8 has an 8-volt 600-ma heater with controlled warmup for series-string heater circuits.

Transistor Radio Servicing CAN be Highly Profitable



The ONLY Complete Transistor Radio Service Lab
Everything you need for less than \$50



Check Transistors, Diodes, Rectifiers . . .

SENCORE TRC4 TRANSISTOR CHECKER

Accurately checks all transistors in hearing aids, radios and power transistors in auto radios. Tests for opens, shorts, leakage, current gain. Measures forward-reverse current ratio on all crystal diodes. Measures forward and reverse currents on selenium rectifiers. With set-up chart for accurate checking of each transistor. Size, 5x4 1/2 x 2 1/2". With batteries. DEALER NET..... **17⁹⁵**



Replace Batteries During Repair . . .

SENCORE PS103 BATTERY ELIMINATOR

All-new "Transi-Pak," twin to TRC4 Checker above. Provides variable DC voltage to 24 volts; 1.5-volt biasing tap (a "must" for servicing Philco and Sylvania radios). Metered current output, to 100 ma. Handles 200-ma peaks. Two 200-mfd electrolytics provide proper filtering and low output impedance. No hum or feedback problems. Ideal for alignment using station signal; adjust IF slugs for max. current, also ideal for charging nickel-cadmium batteries. Size, 5x4 1/2 x 2 1/2". DEALER NET..... **17⁹⁵**



Find Defective Stage in a Minute . . .

SENCORE HG104 HARMONIC GENERATOR

New signal generator designed primarily for fast signal-tracing of transistor radio circuits. No need to unsolder all transistors. Provides RF, IF and audio signals *simultaneously*, drastically cutting service time. Traces from speaker to antenna. Clear 1000 cycle note signal is heard in speaker from all good stages. Signal weakens or stops at defective stage. Equally as effective for testing TV, hi-fi and other audio circuits also. Size, 3 1/2 x 4 1/2 x 1 3/4". With batteries. DEALER NET..... **9⁹⁵**



Turn page for other
SENCORE
Time Savers

See your Parts
Distributor
NOW!


SENCORE

ADDISON 2, ILLINOIS

Please mention **RADIO-ELECTRONICS** when answering ads.

ENGINEERING

B. S. DEGREE IN 27 MONTHS

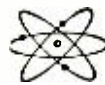

Prepare for unlimited opportunities of the Electronic Age! Students study engineering under accelerated program leading to B.S. degree in 27 mo.; or standard 4-yr. program leading to B.E. degree in 36 mo. B.S. degree (36 mo.) in Math., Chem., Physics. Year-round classes. Comprehensive training in electronics, television, advanced radio theory and design, math., nuclear physics and elec. eng. Also prep courses. Low rate. Earn board. G.I. approved. Enter March, June, Sept., Dec. Catalog.

INDIANA TECHNICAL COLLEGE

1730 E. Washington Blvd., Fort Wayne 2, Indiana

Please send me free information on B.S. ENGINEERING DEGREE IN 27 MONTHS as checked.

- Electronics Chemical Aeronautical
- Civil Mechanical Electrical
- B.E. DEGREE IN 36 MO. in:** Electrical (Power or Electronics)
- Aeronautical Chemical Electrical
- Civil Mechanical Metallurgical
- B.S. DEGREE IN 36 MO. in:** Math. Chem. Physics

Name.....
Address.....

HI-FI RECORDING TAPE

Free Response 99-12 KC.—10 day money back guarantee. *Made by Minn. Min. & Mfg. Co.

	3	10	25
*1200' Acetate ea.	\$1.55	\$1.39	\$1.29
*1800' "	1.95	1.75	1.65
*1800' Mylar "	2.39	2.15	1.99
2400' "	3.29	2.99	2.75

Any assortment permitted for quantity discount. Add postage 15¢ per spool—25¢ or over 10¢.

In Stock—HI-FI under mfgs. franchise—A. R., Bell, Bogen, Dynaco, E. V., Eleo, ESL, Fisher, Garrard, Har-Kar., Norelco, Pilot, Rek-O-Kut, Shure, Thorens, Univ., Wollensack & many many other components & Tape recorders. Send for low, low return mail quotation. *We Guarantee to Save You Money. Wholesale catalog free.

HI-FIDELITY CENTER

1799-N 1st Ave. New York 28, N.Y.




DOUBLE PROFITS

with these two ILLINOIS "HOT" LINES

You really make extra profits with ILLINOIS UMP Twist Prong Capacitors which are especially designed for TV replacement. Each capacitor is fully guaranteed for one year . . . and is needed and in demand for replacement use NOW!

UMP

ELECTROMITE

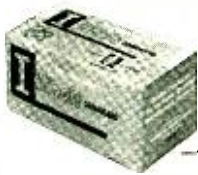

Here are popular, fast moving capacitors which mean repeat business for you. They withstand extreme moisture and temperature conditions. Made of highest quality and unconditionally guaranteed for one year, these attractively-priced capacitors are packaged in eye-appealing boxes.

ILLINOIS "UMP" and "ELECTROMITE" Capacitors are available from leading electronic parts distributors.

Write for our complete catalog.

ILLINOIS


CONDENSER COMPANY

1616 NORTH THROOP STREET
CHICAGO 22, ILL. EV 4-1300


Export Department: 15 Moore Street, New York 4, New York



Time Tested Quality

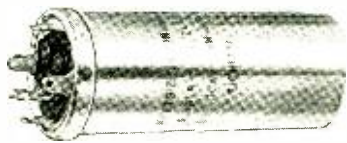

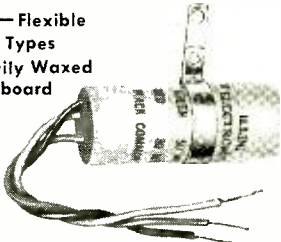
INTE—Flexible Lead Types
Heavily Waxed Cardboard Case



IHCE—Tubular Types
Aluminum Case



NEW TUBES & SEMICONDUCTORS (Contd.)

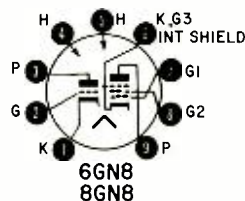


Typical operating characteristics of the Sylvania 6GN8 and 8GN8 are:

	Triode	Pentode
V_p	250	200
V_{G2}	—	150
V_{G1}	-2	—
$R_{k \text{ bias}}$ (ohms)	—	100
I_{G2} (ma)	—	5.5
I_p (ma)	2	25
gm (μ mhos)	2,700	11,500
μ	100	—
R_p (k ohms)	37	60

2N1276, -77, -78, -79

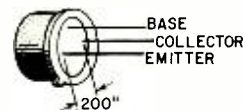A group of n-p-n silicon transistors for amplifier applications in the audio- and radio-frequency range and for general-purpose switching circuits. All



2N1276
2N1277
2N1278
2N1279

are grown-junction units with a diffused base.

Maximum ratings of these G-E units at 25°C are:

V_{CB}	40
V_{CE}	30
V_{EB}	1
I_C (ma)	25
P_C (mw)	150

Typical characteristics of these units are:

H_{fe}	2N1276/-77/-78/-79			
$(V_{CB}=5, I_E=1 \text{ ma})$	14	33	66	101
$f = 1 \text{ kc}$	22	18	15	15
NF (db)				
G_o (pwr gain db)				
$(V_{CE}=5, I_C=1 \text{ ma}, f=1 \text{ kc})$	37	39	44	45
f_{cb} (cutoff freq mc)				
$(V_{CB}=20, I_E=1 \text{ ma})$	30	30	30	34

END

50 Years Ago

In Gernsback Publications

HUGO GERNSBACK, Founder

Modern Electrics	1908
Wireless Association of America	1908
Electrical Experimenter	1913
Radio News	1919
Science & Invention	1920
Television	1927
Radio-Craft	1929
Short-Wave Craft	1930
Television News	1931

Some larger libraries still have copies of Modern Electrics on file for interested readers.

In March, 1910, Modern Electrics

Condensers for the Production of Electric Oscillations, by William E. Smith. Duplex Wireless Receptive System, by George F. Worts.

German Wave-Control Device, by the Berlin Correspondent.

The Peukert (High Frequency) Generator.


Pancake Tuner, by A. C. Marlowe.

Precaution Against "Kickbacks", by Cyril C. Lotz.

Helps for the Amateur. Simplified Aerial Switch.

PUT YOUR OSCILLOSCOPE TO WORK!

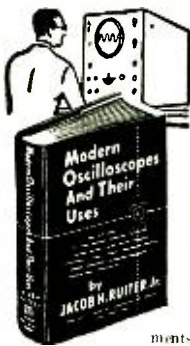Learn to use the handiest service instrument of all!



The book that really shows you how!

Dust off that oscilloscope of yours! Put it to work fully on the dozens of jobs it can do better than any other service instrument.

Handle jobs twice as fast—and lots more profitably!

This big book, MODERN OSCILLOSCOPES AND THEIR USES shows you how . . . in a way you can really understand. Clearly and simply, it explains exactly where and how to use your "scope on all types of AM, FM, and TV service . . . from trouble-shooting to set realigning and everything in between. No fancy theory. You quickly learn how to make connections; how to adjust circuit components; how to set the controls; and how to analyze patterns fast and right! New section even covers quantitative measurements—the slickest method of locating many color TV troubles and aligning sets properly. Has 326 pages and 370 clear pictures including many pattern photos.

Practice from it 10 days . . . at our risk!

10-DAY FREE EXAMINATION!

Dept. RE-30, RINEHART & CO., Inc.
232 Madison Ave., New York 16, N. Y.

Send MODERN OSCILLOSCOPES AND THEIR USES for 10-day FREE EXAMINATION. If I decide to keep book, I will then send you \$8.50 plus a few cents postage in full payment. If not, I will return book postpaid and owe you nothing. **SAVE!** Send cash with order and we pay postage. Same return privilege with money refunded.)

Name

Address

City, Zone, State

OUTSIDE U.S.A.—Cash with order only. Price \$7.00. Money back if book is returned in 10 days.

TAPE RECORDERS
*Recording Tape 1200 foot acetate (plastic) \$1.29. 1800 foot acetate (plastic) \$1.79. 1800 foot MYLAR (Polyester) \$2.39. 2400 foot MYLAR (polyester) \$3.49 (Studios, large users even lower).
*Oxide guaranteed not to rub off or streak—or money back. Compare ours with other "bargain" tape. You'll find it's more than just "price" when you deal with us. We are original pioneers in the tape recorder business and our reputation means everything to us. Send for Free Catalog. COMMIS- SIONED ELECTRONICS CO., 1776 Colum- bia Road, Washington, D. C.

Order your copy of the April issue of **RADIO-ELECTRONICS** now. On sale March 29.

TV PICTURE TUBES

At Lowest Prices

10BP4	\$ 7.95	17BP4	\$ 9.95	21AMP4	\$15.75
12LP4	8.50	17CP4	17.00	21ATP4	15.75
13B/CP4	9.95	17GP4	17.60	21AUP4	15.75
16DP4	12.00	17HP4	12.50	21EP4	13.50
16EP4	12.75	17LP4	11.50	21FP4	14.50
16GP4	14.50	17QP4	9.95	21WP4	14.00
16KP4	9.95	17TP4	17.00	21YP4	14.50
16LP4	10.95	19AP4	16.00	21ZP4	13.50
16RP4	9.95	20CP4	13.50	24CP4	23.50
16WP4	12.00	20HP4	14.50	24DP4	24.50
16TP4	9.95	21AP4	22.10	27EP4	39.95
17AVP4	12.50	21ALP4	15.75	27RP4	39.95

1 year warranty

Aluminized Tubes \$5.00 more than above prices. Prices include the return of an acceptable similar tube under vacuum. These tubes are manufactured from reprocessed used glass bulbs. All parts and materials including the electron gun are brand new.

ALL PRICES FOB CHICAGO, ILLINOIS. Deposit required when old tube is not returned, refundable at time of return. 25% deposit required on COD shipments. Old tubes must be returned prepaid. Tubes shipped Rail Express.

WRITE FOR COMPLETE LIST.

—PICTURE TUBE OUTLET—
3032 Milwaukee Ave., Chicago 18, Ill.
Dickens 2-2048




REPLACING SELENIUM RECTIFIERS

A good percentage of portable radio servicing entails replacing selenium rectifiers. The majority are 75-ma units which are operated close to their maximum current ratings. Many technicians would like to use 100-ma replacements to get a safety margin, but because of their larger physical size this cannot be done. I solved this problem by using 150-ma silicon diodes as replacements. These units can be installed as easily as a resistor. By stocking these 150-ma silicon diodes I have eliminated the necessity of stocking an assortment of selenium rectifiers for portable radios.—*Albert J. Krukowski*

TAPE-SPLICER CLEANING

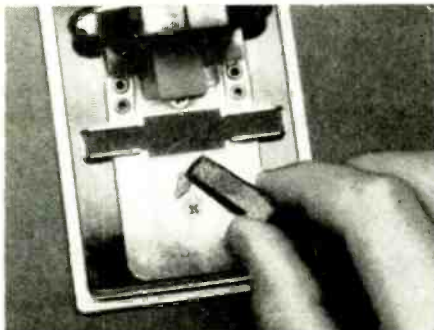One of the hardest cleanup jobs the tape-recording fan runs into is that of removing the tiny bits of magnetic tape that get stuck in the hinge of the splicer where they are likely to be caught in the splicing tape. The solution to the



problem is simple. Just use a small magnet (I salvaged mine from an ion trap) to pick the scraps of tape out of the splicer. The tape, of course, is magnetic and is attracted to the magnet. A word of caution: Demagnetize the splicer occasionally to avoid damaging valuable recordings.—*Ronald S. Newbower*

BOOST FRINGE RECEPTION

The small five-tube receiver in fringe areas needs a little boost for good reception. The schematic shows how to supply it. Very little cost or time is involved. The only parts needed are some hookup wire and a small variable capacitor. I took the variable capacitor from the rf stage of an old Army receiver. The plates on this little variable capacitor are the size of a dime.

Connect the little trimmer to the antenna section trimmer of the receiver's

Servicemen! SAVE TIME...SUBSTITUTE THE SENCORE WAY

The Fastest, Surest Method Known!

Substitute for Capacitors, Resistors

SENCORE H-36—THE "HANDY 36"

36 most-often-needed resistors and capacitors, for fast, easy, direct substitution in all circuits. • Eliminates searching for replacement components for test purposes. • Avoids unnecessary unsoldering and soldering—no more solder mess. • Pays for itself the first month in time saved. • Flick of a switch instantly selects any one of...

- 24 RESISTORS from 10 ohms to 5.6 megohms
 - 10 CAPACITORS from 100 mmfd to .5 mfd
 - 2 ELECTROLYTICS, 10 mfd and 40 mfd
- DEALER NET..... **12⁹⁵**

Substitute for Electrolytic Capacitors

SENCORE ES102 ELECTRO-SUB

Usable from 2 to 450 volts, D.C. Contains 10 electrolytics from 4 to 350 mfd. Select the correct value with the flick of a switch. Features automatic discharge, surge protector circuit. Prevents accidental "healing" of capacitor being bridged. Completely safe—no arc or spark when connecting or disconnecting. DEALER NET..... **15⁹⁵**

Substitute for Fuse Resistors During Repair

SENCORE FS3 "FUSE-SAFE" CIRCUIT TESTER

Instantly tells you whether or not it is safe to replace fuse resistors, fuses, or circuit breakers. Separate red and green scale for each commercially available fuse resistor used in radio and TV. Eliminates guesswork and wasted time. Also handy for wattage checks up to 1100 watts. DEALER NET..... **8⁹⁵**

Substitute for Bias Batteries During Repair

SENCORE BE3 "ALIGN-O-PAK"

Completely isolated DC supply, with less than 0.1% ripple. Eliminates messy batteries in TV service work. Handy for alignment, AGC trouble-shooting, or checking gated sync circuits. Just dial the voltage you need. 0-18 volts, positive or negative. Covers all voltages recommended by TV set manufacturers. Size, 3 1/2 x 4 1/2 x 1 1/4". For 110-120 volts, 60 cycle AC. DEALER NET..... **7⁸⁵**

UNIVERSAL TV JUMPER CORD



Fits any set from back to chassis. Box has male and female plugs for additional power source, soldering, etc. DEALER NET **1⁹⁵**



Turn page for other
SENCORE
Time Savers

See your Parts Distributor Now!


SENCORE

ADDISON 2, ILLINOIS

SUPER POWERED SINGLE CHANNEL AMPLIFIER

Minimum 20V—5 Watts on All Channels

This all new super powered unit has the highest output of any TV channel amplifier with sufficient power to cover large communities with ample signal voltage and deliver a strong signal thru many miles of cable. The unit was designed specifically for community television and is the only unit of its kind that does not produce power in fractions of a watt. For full rated output a high-powered commercial transmitting tube is used.

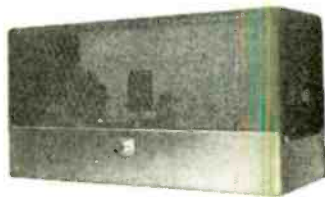

- C. C. S. Service
- Channels 2-13 as specified
- Co-axial input and output connectors for 75 OHM Line
- Linear class A operation
- 26 db min. gain
- 6-8 mcs. band width
- Requires only 1 V input
- Low Power Drain (1 Amp.)

MCDEL SPA
\$350

Write for details today.

SEG Electronics • 1778-A Flatbush Ave., Brooklyn 10, New York

HOTTEST ITEM Ever Offered!


CITIZENS-BAND 11-METER CLASS "D" TRANSCEIVER KIT—by Philmore

Only \$39.95

2-Way Communication
OFFICE—HOME—AUTO
BOATS—FARMS—ETC.

ANYONE CAN GET LICENSE

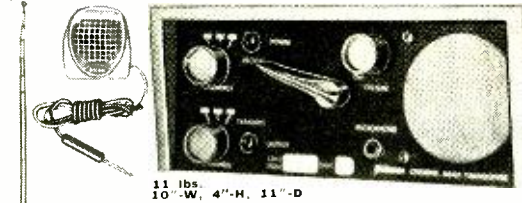License available to all Citizens. No tests, no skill required. Just fill out FCC FORM (enclosed with Philmore Kit) and mail to Federal Communications Commission.



11 lbs.
10"-W, 4"-H, 11"-D

Philmore—The Leader in mfg. the famous #630 TV CHASSIS—Now takes the lead in TRANSCEIVERS—bringing you this SENSATIONAL INSTRUMENT with Features, Quality and Performance better than in Other Makes selling at many times the Price.

- ★ Selected Components, matched to make up a Completed Unit for proper operation conforming to all FCC specifications on all of the 22 authorized Channels.
- ★ Sensitive Superregenerative Detector is virtually drift-free. Will pick up signals from the furthest limits of transmitter range, as far as 10 miles.
- ★ Transmitter delivers maximum allowable 5 watts plate power.
- ★ Any 3 Channels may be automatically switch-selected, insuring interference-free communication at all times. Both Receiver and Transmitter are individually tuned to pre-arranged frequencies. Transmitter is Crystal controlled with accuracy of .005%.

Philmore has designed this KIT so that anyone (without any special knowledge) can build it. The step-by-step Instructions . . . LIFE-SIZE PICTORIAL DIAGRAMS . . . and Selected matched Components—assure you success and pleasure in building it.

Complete with Cabinet, 5 Tubes, Microphone, Crystal and all parts necessary to build it.

- TC-11 TRANSCEIVER KIT for 115 volts A.C. \$39.95
- TC-612 TRANSCEIVER KIT for 6 & 12 volts (auto or boat) 44.49
- TC-15 MATCHED ANTENNA 7 section (illustrated at left) 4.50

BROOKS RADIO & TV CORP., 84 Vesey St., New York 7, N.Y.

Please mention

RADIO-ELECTRONICS
When answering ads

RADIO SHACK FLASH!

Send Coupon for Latest
FREE
ELECTRONICS CATALOG
plus every new issue for 1960



For the newest and best in electronics equipment—stereo, hi-fi, ham radio, tapes—mail coupon today for Radio Shack's latest FREE 312 page catalog. Also get every new edition for next 12 months, Free. Satisfaction guaranteed or your money back. Mail coupon now.

Just one of thousands of RADIO SHACK buys


Transistor Battery Radio
19.95 Value
only
\$9.95



Exclusive Radio Shack transistor battery radio. Only 2 1/2 x 4 x 1 1/4 inches in size. Weighs less than 10 ounces. Built-in speaker and ferrite antenna. Conrad markings, handsome molded case.

Radio Shack Corp., 730 Commonwealth Ave., Boston 17, Mass. Dept. 60C10
Send FREE Electronics Catalog—Also every new issue for 12 months, a full year's subscription Free.
Name _____
Address _____
Postoffice _____
or City _____ Zone _____ State _____

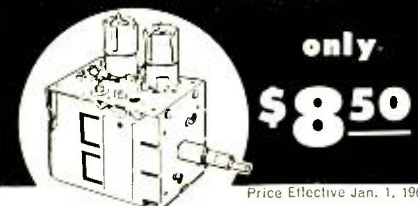TARZIAN Offers 48-Hour, Direct Factory Service on Tuner Repairs



only
\$8.50

Price Effective Jan. 1, 1960

That's right. Net, \$8.50 per unit and \$15 for UV combinations, including ALL replacement parts. 90-day warranty against defective workmanship and parts failure. Tuners repaired on approved, open accounts. Replacements offered at these prices* on tuners not repairable:

- VHF 12 position tuner \$22.00
- VHF 13 or 16 position 23.00
- VHF/UHF combination 25.00
- UHF only 15.50

*Subject to change



Tarzian-made tuners are easily identified by this stamping on the unit. When inquiring about service or replacements for other than Tarzian-made tuners, always give tube complement . . . shaft length . . . filament voltage . . . series or shunt heater . . . IF frequency, chassis identification and allow a little more time for service. Use this address for fast, 48-hour service:


SARKES TARZIAN, Inc.
Att.: Service Mgr., Tuner Division
East Hillside Drive
Bloomington, Indiana

NOTEWORTHY CIRCUITS

LATCHING CIRCUIT USES STANDARD RELAY

Here is a circuit that uses a standard relay to obtain a latching or memory action. The relay must have an extra set of normally open contacts which are not needed in the control application, but a dpst relay will do for most uses.

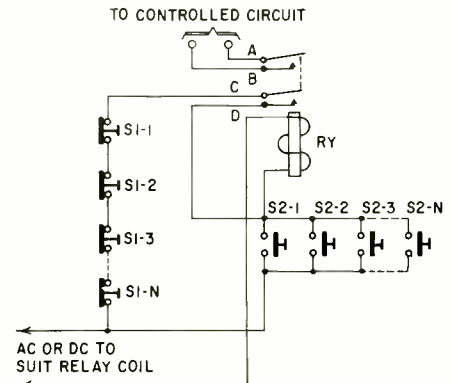The latching action requires only a momentary operation of a pushbutton to latch, and another push to reset or




unlatch. An added advantage of this hookup is that only three wires need be run for the installation of as many control positions as may be required or desired.

Here's how the circuit works: When S2 is closed momentarily, the relay coil is energized and contacts A-B and C-D close. Since S1 is normally closed, the closing of contacts C-D bridges S1 and the relay coil remains energized when S2 opens. A momentary operation of S1 now de-energizes the relay coil, opening C-D and unlatching the circuit.—Robert E. Monroe

SUN-POWERED OSCILLATOR

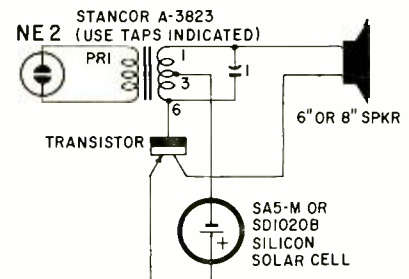This one-transistor 400-cycle oscillator is powered by a single solar cell. Almost any transistor will work in this



circuit. The arrangement shown is for p-n-p types. For n-p-n transistors, reverse the solar cell.


A neon lamp is connected so it will

glow whenever the transistor oscillates. This makes the circuit a transistor checker. Plug in a good transistor and the lamp lights. Plug in a bad one and nothing happens.

By using a 100-watt lamp as the light source, you can get a rough approximation of the transistor's gain. A very good transistor will oscillate when the lamp is 30 inches from the solar cell. Less sensitive units will not oscillate until the lamp is brought closer to the solar cell and voltage increases.—*G. L. Garvin*

FASTER BREAK-IN

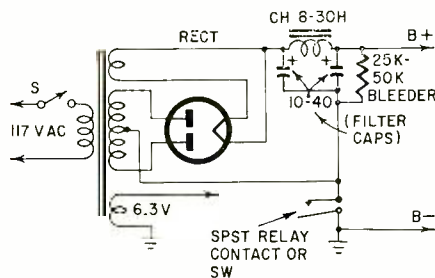Both the receiver and transmitter in many ham or Citizens-band setups have a slow recovery time from receive to transmit and vice versa. Lots of receivers and transmitters are wired so that the center tap of the power transformer is broken, and the filter capacitors and bleeder resistor are left in the circuit




to drain off through the B-plus line. The transmitter vfo and some crystal oscillators use this type of circuit.

By breaking the center tap with the minus side of the filter capacitors and the bleeder resistor connected direct to the center tap, this condition is improved from 75% to 100% in all cases tried. A spst relay contact or switch is used to break this connection.—*George P. Obero, K4GRY*

LIGHT BLINKER

This simple circuit is a blinker whose time interval is adjustable. As it works off 6- or 12-volt batteries, it could be set up as a warning device for your car. Should you get stuck at night, just plug it into the cigarette lighter and set it up on the road behind your car.

When switch S is closed, turning the

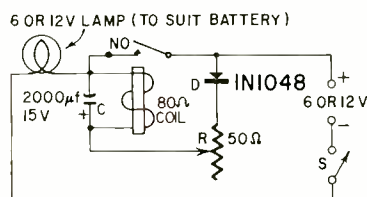

unit on, the capacitor charges and closes the relay, lighting the lamp. The diode keeps the capacitor from being shorted by the relay contacts and the light remains lit until the capacitor discharges through potentiometer R and the relay coil. Then the relay opens, the light goes out and the whole sequence repeats itself.—*L. George* END

Pinpoint in Seconds...

HORIZONTAL & VERTICAL SWEEP TROUBLES

NEW

SENCORE

Time Saver

Superg Circuit

TROUBLE SHOOTER

MODEL SS105

PROVIDES

The missing link in TV service ...

SENCORE SS105 SWEEP CIRCUIT TROUBLE SHOOTER

IT'S A ...

UNIVERSAL HORIZONTAL OSCILLATOR.

For direct substitution. No wires to disconnect in most cases. Traces trouble right down to the defective component. Variable output from 0-200 volts, peak-to-peak.

HORIZONTAL OUTPUT CATHODE CURRENT CHECKER.

A proven method that quickly checks the condition of the horizontal output tube and associated components. Adaptor socket prevents breaking wires. Easily replaceable Roll Chart gives all necessary pin, current and voltage data.

UNIVERSAL DEFLECTION YOKE.

A new, simple way to determine yoke failure accurately—without removing yoke from picture tube. Merely disconnect one yoke lead and substitute. If high voltage (also bright vertical line) is restored, TV yoke is defective.

DYNAMIC FLYBACK TRANSFORMER CHECKER.

Merely flip switch to "Flyback Check" and meter will indicate condition of flyback transformer, in degrees of horizontal deflection. Extremely sensitive and accurate; even shows up one shorted turn on flyback.

VOLTMETER.

For testing bootstrap, screen and other voltages. Direct-reading voltmeter, 0-1000 volts.

UNIVERSAL VERTICAL OSCILLATOR.

Checks oscillator, output transformer and yoke. Merely touch lead to component and check picture on screen.

Size, 7x6x3½". Wt. 4 lbs.
For 110-120 volts, 60 cycle AC. DEALER NET 42⁹⁵

SENCORE

ADDISON 2, ILLINOIS

See Your Parts Distributor NOW!

OPPORTUNITY ADLETS (Continued from p. 135)

SONGPOEMS and LYRICS WANTED! Mail to: TIN PAN ALLEY, INC. 1650 Broadway, New York 19, N. Y.

LEARN WHILE ASLEEP. Hypnotize with your recorder, phonograph or amazing new Electronic Educator endless tape recorder. Catalog, details free. SLEEP-LEARNING ASSOCIATION, Box 24-RD, Olympia, Wash.

RADIO & TV TUBES at Manufacturers' Prices! 100% Guaranteed! Brand New! No re-brands or pulls! UNITED RADIO, Box 1000, Newark, N.J.

LOW QUOTES on everything HIFI & Stereo Tapes. Bargain List: HIFI, Roslyn 5, Pa.

FRESH 9V radio batteries .55 each, 10 for \$4.50 Flar type 066P. JETCO, 919 Robacca, McKeesport, Pa.

TUBES, TOP Nationally Advertised Brands. New tubes, no factory rejects. Manufacturer's Boxes, 1st quality, fully guaranteed, condensers, speakers, rectifiers, etc. Terrific Discounts. Write to TELETYPE SUPPLY CO. 139 Western Promenade, Cranston, Rhode Island.

BOOK—200 Electric Struts \$1. De Cutting, 875 Arastradero, Palo Alto, Calif.

NEW ANTENNAS 10' loop, 150 to 1753.4 to 7 mc. Rotating type MN 20 C by Bendix \$3.95. ANTENNAS Box 416, Edna, Texas.

LEARN CIVIL and criminal investigation at home. Earn steady, good pay. INSTITUTE APPLIED SCIENCE, 1920 Sunnyside, Dept. 263, Chicago 40, Ill.

PRINTED CIRCUIT BOARDS designed, manufactured. Custom PC kits. Brochure, Electronic Aids, Box 137, Stamford, Conn.

TELE-VUE Troubleshooter is the answer to all your servicing problems. Waste no time on book theory. Eliminate guesswork. Spots faults in minutes. 3 years advanced research developing this complete repair guide. Get FREE FACTS. Write Dept. RE, NATIONAL TECHNICAL RESEARCH LABS., 1118 W. Hadley St., Whitefish, Calif.

CASH PAID! Sell your surplus electronic tubes. Want unused, clean radio and TV receiving, transmitting, special-purpose, Magnetrons, Klystrons, broadbeam types, etc. Want military & commercial lab/test and communications equipment such as G.R., H.P., AN-UPM prefix. Also want commercial receivers and transmitters. For a fair deal write BARRY, 512 Broadway, New York 12, N. Y. Walker 3-7000.

HIFI, Recorders, Tapes. FREE Wholesale Catalogue. CARSTON, 215-T East 88th St., New York 58, N. Y.

EXPERIENCED TECHNICIAN

Service 2-Way FM Radio Equipment

First or Second Class Phone License Necessary
Salary: \$7,000 a year
Fringe Benefits, Hospitalization Group Insurance
Send complete resume to:

Communications Associates Inc.

PO Box 8, Grove Hall Station, Boston 21, Mass.

Learn TRANSISTOR, COMPUTER OR RADAR TECHNOLOGY at home



Prepare now for advancement... and for a secure and profitable career in one of these growing fields of electronics

CHOOSE FROM 7 PROVEN COURSES

1. **SEMICONDUCTORS**—Transistor Principles and Practices. Learn Theory, construction, application of all types of transistors.
2. **PRINCIPLES OF RADAR CIRCUITS AND EQUIPMENT**—Introduction to, and detailed study of radar fundamentals.
3. **RADAR SYSTEMS PRINCIPLES AND PRACTICES (Advanced Level)**—Applications of radar components, systems, design . . . performance measurement.
4. **INTRODUCTION TO ANALOG COMPUTERS**—Covers theories and fundamentals of all makes of analog computers.
5. **ANALOG COMPUTER SYSTEMS (Advanced Level)**—Covers the analog system concepts and methods.
6. **AUTOMATIC DIGITAL COMPUTERS**—Digital computer theory, maintenance, installation, basic programming.
7. **PROGRAMMING FOR DIGITAL COMPUTERS**—Covers encoding, set-up and operation.

MAIL COUPON TODAY FOR FREE INFORMATION

PHILCO TECHNOLOGICAL CENTER TCR-5
 "C" and Ontario Streets, P.O., Box 4730, Phila. 34, Pa.
 Please send full information on subjects checked below. (No obligation)

<input type="checkbox"/> 1. Semiconductors	<input type="checkbox"/> 4. Intro. to Analog Comp.
<input type="checkbox"/> 2. Principles of Radar	<input type="checkbox"/> 5. Analog Comp. Systems
<input type="checkbox"/> 3. Radar Systems	<input type="checkbox"/> 6. Automatic Digital Comp.
<input type="checkbox"/> 7. Programming for Digital Computers	



NAME _____
 COMPANY _____ POSITION _____
 ADDRESS _____
 CITY _____ STATE _____

Expand your knowledge in one of these rapidly advancing fields of electronics and you'll be set for a secure and profitable future. Transistor technology is becoming one of the biggest fields in electronics. The use of automatic computers in automated factories, business offices and military systems is outpacing the technical manpower needed to build and maintain them. New developments in radar have given new life to this dynamic field. Electronics men are in demand, but it takes specialists to land the big jobs. Now's the time to prepare . . . advance and prosper in this new era.

Learn with proven home study courses from the Philco Technological Center. Get a practical, working knowledge with proven courses developed by specialists in electronics and training . . . men who know the kind of knowledge you need. Philco Technological Center is a department of Philco TechRep Division, one of the world's leading field engineering organizations.

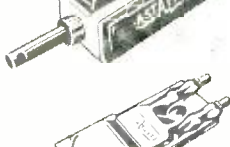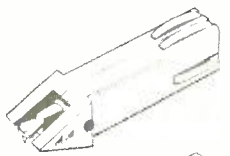NOW READY—A special computer programming course that covers all important techniques of encoding and operation . . . ideal for maintenance men, or those who wish to become Programmers. Send for full details. No salesman will call.





GO BY BRAND ...
GO BUY ASTATIC

YOU WOULDN'T GO
AFTER THE "BIG ONES"
WITH

"Bent Pin"

FISHING TACKLE



... and you can't go after big cartridge business without

ASTATIC

THE ONLY, REPEAT ONLY, COMPLETE PHONO CARTRIDGE LINE

Whether you sell, install or use phono cartridges, you're ahead with the one dominant name in the industry — ASTATIC. Only Astatic can give you, on every single replacement, the ORIGINAL or DIRECT REPLACEMENT cartridge that exactly matches the other components of the player.

AND VERY OFTEN THE PRICE IS BELOW THAT OF SUBSTITUTES. This is the one sure way to best results, to fullest quality and fidelity of sound reproduction. THIS IS THE ONE SOURCE OF MAXIMUM SALES AND PROFITS FOR YOU.

IT'S BETTER BUSINESS TO SELL ASTATIC
LEADER WITH ORIGINALS — FIRST WITH REPLACEMENTS

ASTATIC CERAMIC AND CRYSTAL PHONO CARTRIDGES: STEREO AND MONAURAL, PLUG-IN AND CONVENTIONAL, WITH DIAMOND OR SAPPHIRE STYLI



CORPORATION, CONNEAUT, OHIO

KNOWN THE WORLD OVER



IN CANADA: CANADIAN ASTATIC, LIMITED, TORONTO, ONTARIO
EXPORT SALES: ROBURN AGENCIES, INC., 431 GREENWICH ST.
N. Y. 13, N. Y., U. S. A.

FIRST NAME IN PHONO CARTRIDGES, NEEDLES, MICROPHONES

*Straight facts
on
replacement
picture tubes...*



RCA Monogram is second only to RCA Silverama

1. MONOGRAM is RCA's economy line of brand-name replacement picture tubes—equal in performance to any so-called “first-quality” picture-tube lines that also contain used materials.
2. RCA Monogram is surpassed only by the *guaranteed all-new* RCA Silverama—the picture tube that commands premium price and profits.
3. Only RCA, of the three largest-selling brands of replacement TV picture tubes, offers you this double line for two distinct sales needs: RCA Monogram for the budget-minded...and premium RCA Silverama for those customers who demand the very best.
4. Most important, there are big new profit possibilities for dealers on the Monogram Picture Tube line. Get the exciting facts from your RCA distributor today!



RADIO CORPORATION OF AMERICA
Electron Tube Division

Harrison, N. J.

© Silverama