

Radio-Electronics


MASTER 60c ■ DEC. 1968

TELEVISION · SERVICING · HIGH FIDELITY

GERNSBACK PUBLICATION

It's easy to fix Solid-State TV

*INDEX
p. 68*

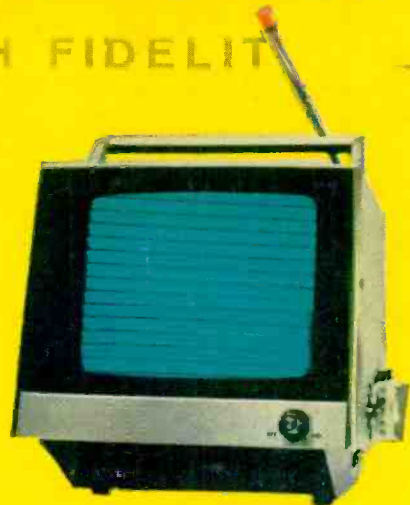


~IP 77

BUILD: Stereo headset Control center

X 66-69




ABC's of Transistors

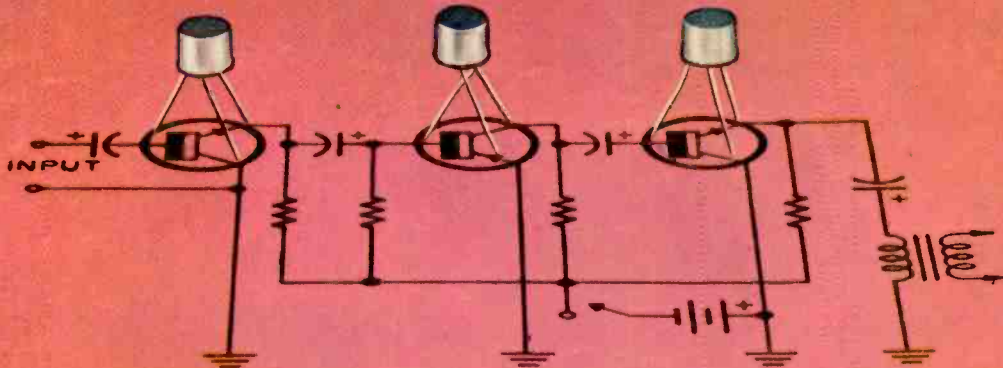

\$44,000,000

WILL BUY 1,000,000 TRIPLETT 310 VOM'S BUT YOU ONLY NEED ONE... AT \$44⁰⁰ THAT'S A BARGAIN

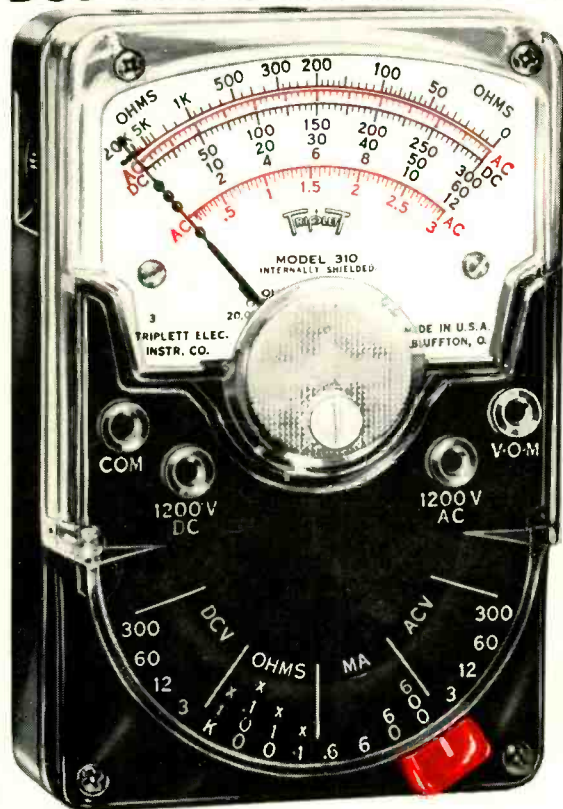

MODEL 310
World's Largest Selling
Volt-Ohm-Milliammeter
(SHOWN ACTUAL SIZE)



MODEL 310-C
Volt-Ohm-Milliammeter

- 1** HAND SIZE V-O-M WITH PROVISION FOR ATTACHING AC CLAMP-ON AMMETER.
- 2** 20,000 OHMS PER VOLT DC SENSITIVITY; 5,000 AC.
- 3** ONE SELECTOR SWITCH MINIMIZES CHANCE OF INCORRECT SETTINGS AND BURNOUTS.

310-C PLUS FEATURES

- 1** Hand size V-O-M with provision for attaching AC Clamp-on Ammeter.
- 2** 15,000 OHMS per volt AC sensitivity; (20,000 DC same as 310).
- 3** Single fully enclosed Lever Range Switch, plus DC Polarity Reversing.

MODELS 100 AND 100-C

Comprehensive test sets. Model 100 includes: Model 310 V-O-M, Model 10 Clamp-on Ammeter Adapter; Model 101 Line Separator; Model 379 Leather Case; Model 311 leads. (\$83.20 Value Separate Unit Purchase Price.)

MODEL 100 — U.S.A. User Net.....\$78.00
MODEL 100-C — Same as above, but with Model 310-C. Net.....\$88.00



SELF-SHIELDED Bar-Ring instrument; permits checking in strong magnetic fields. FITTING INTERCHANGEABLE test prod tip into top of tester makes it the common probe, thereby freeing one hand. UNBREAKABLE plastic meter window. BANANA-TYPE JACKS—positive connection and long life.

Model 310—\$44.00 Model 310-C—\$56.00 Model 369 Leather Case—\$4.20
All Prices are Suggested U.S.A. User Net, Subject to Change

THE WORLD'S MOST COMPLETE LINE OF V-O-M's • AVAILABLE FROM YOUR TRIPLETT DISTRIBUTOR'S STOCK



TRIPLETT ELECTRICAL INSTRUMENT COMPANY, BLUFFTON, OHIO 45817

DON'T FORGET TO ASK 'EM "WHAT ELSE NEEDS FIXING?"

Circle 7 on reader's service card

What Does electronics Mean To You?

This is the "electronics age." Advancements in electronics are coming, one on top of another, so rapidly that the *average technician* cannot stay abreast of the changes. But *some* technicians — those who thoroughly understand fundamental principles — *are* able to stay up with these changes, and they make top pay because of their special ability.

Is *your* electronics knowledge obsolescent? If so, nothing can make you obsolete so quickly as to neglect the study of basic concepts and fundamental principles.

Upgrade Your Knowledge and Earn Your Degree

Grantham's strong-foundation educational program in electronics leads to non-obsolescent skills — to skills based more on reasoning than on merely doing — and leads first to the Associate and then to the Bachelor of Science Degree.

The Grantham Engineering Degree Program in electronics places heavy stress on fundamental concepts of logic and mathematics rather than on superficial manipulative skills. Since these fundamental ideas are largely unfamiliar to many electronics technicians, it is necessary to develop them in a systematic manner.

Get Your FCC License Along The Way

You have heard and read, over and over again, about how important an FCC license is to your success in electronics. It is certainly true that an FCC license is important — sometimes essential — but it's not enough! Without further education, you can't make it to the top. Get your FCC license without fail, but don't stop there. To prepare for the best jobs, continue your electronics education and get your degree.

This kind of thinking makes good common sense to those who want to make more money in electronics. It also makes good common sense to prepare for your FCC license with the School that gives degree credit for your license training — and with the School that can then take you from the FCC license level to the DEGREE level. The first *two semesters* of the 7-semester Grantham degree curriculum prepare you for the first class FCC license and radar endorsement.

Grantham School of Electronics

1505 N. Western Ave. 818 18th Street, N.W.
Hollywood, Calif. 90027 or Washington, D.C. 20006

Telephone:
(213) 469-7878

Telephone:
(202) 298-7460

Accreditation, and G.I. Bill Approval

Grantham School of Electronics was established in Hollywood, California in 1951, and the Eastern Division of the School was opened in Washington, D.C. in 1955.

The School is *approved* in California by the California State Department of Education, is *approved* in the District of Columbia by the D.C. Board of Education, is *approved* under the "Cold War G.I. Bill" to offer resident courses in Hollywood and Washington and correspondence courses from Hollywood, is *accredited* by the Accrediting Commission of the National Home Study Council, and is *authorized* under the laws of the State of California to grant academic degrees.

The Grantham Engineering Program

The entire Grantham Electronics Engineering Curriculum consists of seven semesters (or sections), as listed below. The first six semesters lead to the Associate in Science Degree, and Semester 7 (together with transfer credits in "the humanities") lead to the Bachelor of Science Degree.

Semester 1 — Basic Electronics Technology
(80 lessons, by correspondence or in residence)

Semester 2 — Communications Circuits and Systems
(80 lessons, by correspondence or in residence)

Semester 3 — Electronics Laboratory
(16 weeks, in residence in Hollywood or Washington — or credit may be given for at least one year of practical experience)

Semester 4 — Physics, Engineering Analysis, & Computers
(80 lessons, by correspondence)

Semester 5 — Analytic Geometry and Calculus
(80 lessons, by correspondence)

Semester 6 — Solidstate Physics, Circuit Design, and Technical Writing
(80 lessons, by correspondence)

Review & Exam — Review and Comprehensive Examination on Semesters 1 thru 6, for the Associate in Science Degree
(two-week resident class, meeting in Hollywood)

Semester 7 — Advanced Electronics Engineering
(16-week resident class, meeting in Hollywood)

Transfer Credits — Certain credits in English, Social Studies, etc., in addition to Grantham Semesters 1 thru 7, are required for the *Bachelor of Science Degree in Electronics Engineering*.

Mail the coupon below for our free Bulletin.

Grantham School of Electronics RE-12-68
1505 N. Western Ave., Hollywood, Calif. 90027

Please mail me your free Bulletin, which explains how the Grantham educational program can prepare me for my FCC License, my Associate in Science Degree, and my Bachelor of Science Degree in Electronics Engineering. I understand no salesman or counselor will call.

Name _____ Age _____

Address _____

City _____ State _____ Zip _____

Circle 8 on reader's service card

LOOKING AHEAD

By DAVID LACHENBRUCH
CONTRIBUTING EDITOR

Mike with ears

The gadget in the photo may look a bit eerie, but it's described by its developers as the next step after stereo. Called Environ-Ears, it's basically a two-



microphone assembly with an "integrated acoustical labyrinth that duplicates the localization and noise-reducing functions of the human ear." Developed by Listening, Inc., Arlington, Mass., and used in Navy-backed research, Environ-Ears resembles two human ears mounted at opposite ends of a rod.

It is claimed to be ideally suited for recreating the actual sounds at the original recording session—for everything from business conferences to symphonies—since it simulates in playback the actual physical positions of the sounds recorded. Used with a conventional stereo recorder, its developers say it permits the listener to differentiate between sounds from below, in front of, or behind the microphone, and eliminates reverberation and extraneous environmental noises, much as human ears do. It's currently priced at a rather steep \$950, but lower-priced versions could be forthcoming.

FM on the rise

There's no let up in sight for the groundswell in the popularity of FM radio. In the first half of this year, 44 percent of the table, portable and clock radios purchased in the US contained FM, as compared with only 35 percent one year earlier. It now seems entirely possible that the majority of radios sold in the coming year will contain FM tuners.

Interestingly, the overwhelming majority of FM radios sold here—more than 86 percent in the first six months of 1968—were imported, mostly from Japan. Even FM radios carrying the trademarks of American radio manufacturers have a better than 50-50 chance of coming from abroad.

In the automotive market, FM is moving more slowly. For January through June 1968, a little less than 10 percent of all car radios sold as original equipment or after-market "hang-ons" could tune the FM band. This represents a small increase over FM's 8.4 percent penetration of the car radio field in the first half of 1967.

Cassettes—how hi the fi?

Can a high-fidelity enthusiast find happiness with a tape that moves at 1 7/8 inches per second? Apparently some of the major component audio equipment manufacturers think he can and will, in the latest chapter of the amazing saga of the tiny, Dutch-born two-reel cassette. Although its original acceptance came in a battery-operated, voice-recorder format, such audio-

phile manufacturers as Ampex, Fisher, Harman-Kardon and H. H. Scott have now embraced the cassette recorder.


Unquestionably, there's a trade off between fidelity and convenience in the use of the cassette, whose response is around 20-12,000 Hz. But many manufacturers feel this won't always be the case. The very success of the cassette is spurring an all out effort to extend its characteristics into the high fidelity range, while improving on its convenience as a music playback medium. Cassettes using high-density tape, such as DuPont's Crolyn, will soon be available. High-quality precision recorder mechanisms have already been developed to reduce flutter by maintaining very constant speed. One manufacturer, TEAC of Japan, soon will offer a two-speed cassette recorder, which will include a double-fast 3 3/4 ips for high-fidelity recording.

For greater convenience in music playback, several manufacturers are developing automatic-reverse cassette recorders and players. And there's a race on for an endless-loop cassette that never has to be rewound. Philips of Holland and Sony and TDK of Japan are among the leading entries in this effort.

Mail by phone

The increasing availability of low-cost facsimile systems which can send graphic material over regular telephone lines without the need for special treated paper or other supplies is giving birth to a new public "mail-by-phone" industry.

At least four "networks" of public facsimile stations are now in operation, under the names of Docu-Trans, Insta-Fax, Transceiver Corporation and Tele-Trans. They have set up shop in major US cities to offer long-distance document transmission facilities to the general public. Charges generally are around \$2.50 to \$3.00 per standard 8 1/2-by-11-inch page—plus the regular long-distance telephone charge for the 6 minutes required to send a page of copy.

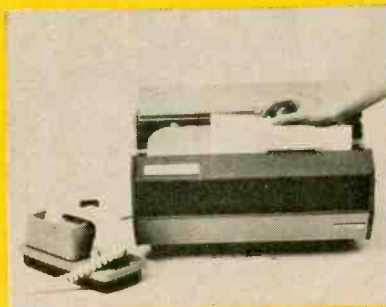

All of the networks currently use a facsimile system developed by the Magnavox Company (photo), which is available on lease from the Xerox Corporation under the name of Xerox Telecopier or from Magnavox under the Magnafax name. A single machine is used for both transmission and reception. For transmission, the material to be sent is affixed to a revolving drum and the telephone handset placed in a special cradle. A photocell scanner converts the light and dark material on the page into audible signals. At the receiving end, a standard carbon-paper set (a sheet of carbon attached to a piece of manifold paper) is placed on the drum, and a stylus recreates the original copy. R-E

Radio-Electronics

December 1968 • Over 60 Years of Electronics Publishing

CAREERS

- Computer Lingo—Today's New Machine Languages** **32** ... Matthew Mandl
The programmer is the middleman
- Jobs For Electronic Testers** **52** L. L. Farkas
What's the technician doing today
- Computer Schools** **89**

BUILD ONE OF THESE

- Stereo Headset Control Center** **35** ... Wayne Lemons
Add a stereo phono for a complete stereo system
- 50-Watt Portable AC Outlet** **38** Jack Jaques
It goes anywhere your car goes
- Stereo Tape/Slide Controller** **47** Earl T. Hansen
Don't waste a channel for triggering
- Dancing Christmas Lights** **50** R. W. Fox
Decorate the outside of your house this year

TELEVISION

- In The Shop ... With Jack** **22** Jack Darr
Signal tracing color TV
- It's Easy To Fix Solid-State TV** **41** ... Matthew Mandl
Ins and outs of transistor TV circuits
- Service Clinic** **88**


GENERAL ELECTRONICS

- Looking Ahead** **2** David Lachenbruch
Current happenings with future overtones
- ABC's of Transistors** **44**
See how they work
- For The Experimenter**
9 Digital-Readout IC Instruments **57** Ralph Genter
Digital instruments you'll want to build
- Equipment Report:** **72** ... Fred Shunaman
Heathkit Band Box Playmate

DEPARTMENTS


- | | | |
|--------------------------------|--|------------------------------------|
| Correspondence 14 | New Products 77 | Noteworthy Circuit 92 |
| New Books 98 | New Tubes and Semiconductors 90 | Readers Service 76 |
| New Literature 83 | News Briefs 4 | Technotes 70 |

INDEX p. 68

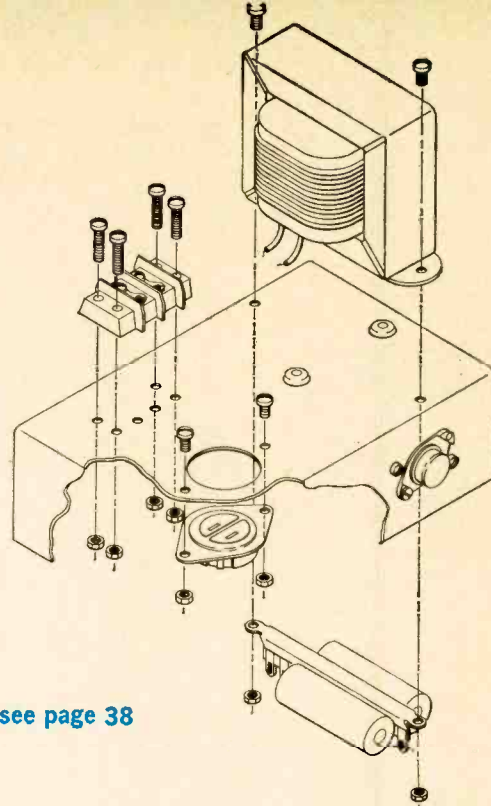


see page 38

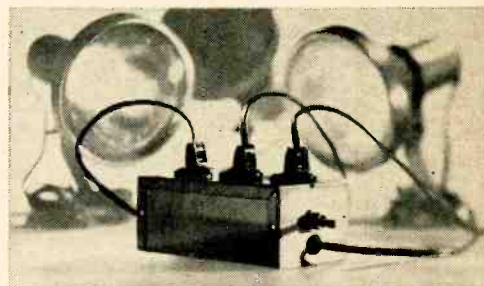Portable ac outlet delivers up to 50 watts. Just hook it up to a 12-volt battery. Simplified exploded diagrams make it easy to build.



Dancing lights this Christmas? It's a cinch with this tricky SCR circuit to automatically vary the intensity of outdoor lighting.

see page 50

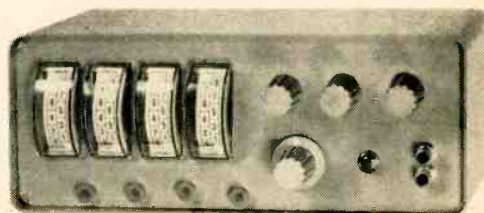

You can make 9 digital instruments. A large assortment of equipment and the necessary building techniques are shown.

see page 57

RADIO-ELECTRONICS, DECEMBER 1968, Volume XXXIX, No. 12
Published monthly by Gernsback Publications, Inc., at Ferry St., Concord, N. H. 03302
Editorial, Advertising, and Executive offices: 200 Park Ave. S., New York, N.Y. 10003. Subscription Service: Boulder, Colo. 80302.
Second-class postage paid at Concord, N. H. Printed in U.S.A. One-year subscription rate: U.S. and possessions, Canada, \$6.
Pan-American countries, \$7. Other countries, \$7.50. Single copies: 60¢. ©1968, by Gernsback Publications, Inc. All rights reserved.
POSTMASTER: Notices of undelivered copies (Form 3579) to Boulder, Colo. 80302.



Member,
Institute of High Fidelity.
Radio-Electronics is indexed in
Applied Science & Technology Index (formerly *Industrial Arts Index*)

NEWS BRIEFS


NEW ARM WORKS WITH THOUGHT SIGNALS



Artificial arm is willed into operation, producing natural arm-like movements.

A new electronically controlled artificial arm that promises greatly increased dexterity for amputees has been developed. The system uses a solid-state, sensor-amplifier package and a unique feedback circuit that enables operators to sense how much weight they are supporting.

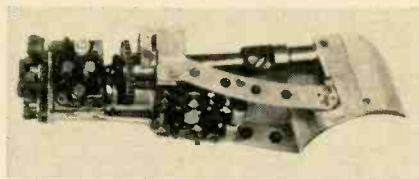Amputees, by willing a non-existent arm into action, contract



Amplifier circuits and the drive motor.

stump muscles that generate millivolt-level signals. Sensors in the system detect and amplify these signals, and the operator can apply varying degrees of force by "thinking" the amount of effort needed.

Developers believe that with a little experience amputees can use the new arm with no more conscious thought than is needed for a normal one. Similar systems under consideration may aid some 7000 Thalidomide children with above-elbow stumps.

The 2-lb arm is powered by a battery that can be worn around the waist. Although it is not available for general use, the arm could be mass-produced for less than \$1000 each. The mechanism was developed in a joint project by MIT, Harvard, Massachusetts General Hospital and Liberty Mutual Insurance.

DIM LIGHT TV CAMERAS

Two highly sensitive TV-camera tubes have been developed independently by Bell Telephone Labs and

Westinghouse. The new devices have potential applications for see-in-the-dark surveillance TV and Picturephones that permit people to see each other as they talk. The Westinghouse system is an offshoot of similar devices used in military and space applications ("Starlight Scope Sees in the Dark," August 1968). The camera tube uses the principle of secondary electron conduction, which "amplifies" light by accelerating electrons from a photocathode onto a sensitive target. The camera system shown here weighs only 12 lbs, draws 17 watts and can provide clear TV pictures under moonlight conditions.

Bell revealed a camera tube they plan to use in their Picturephone. A

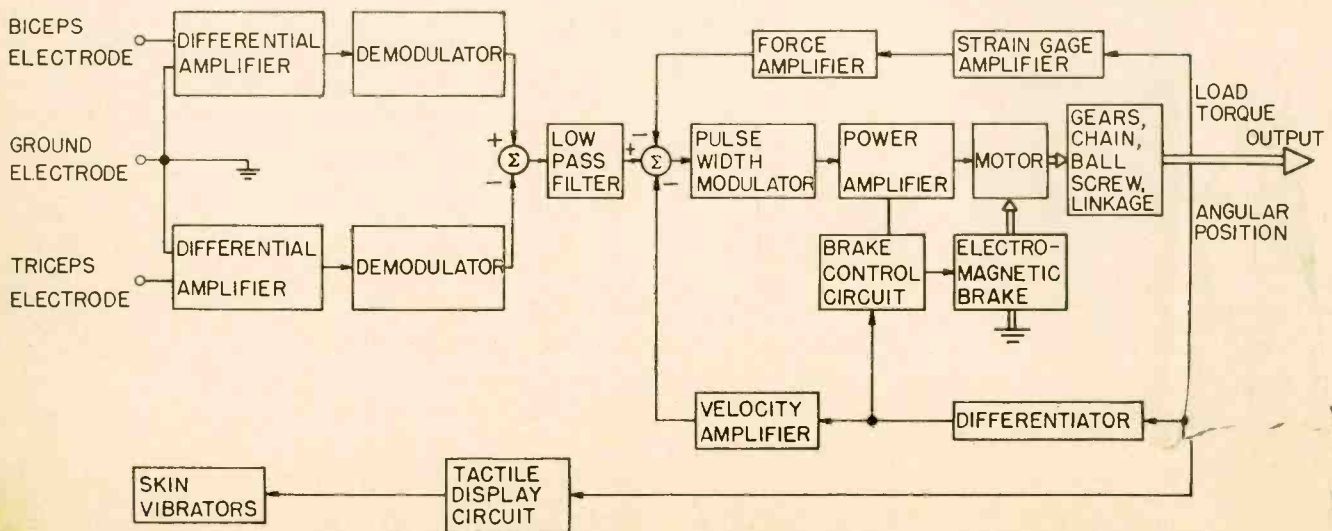


Diagram shows how signals are detected by sensors and amplified to operate motors.

The call-back killers...

Genuine RCA replacement parts.

They're famous for silencing customer complaints and wiping out costly call-backs.


That's because they're specially designed and fabricated... every electronic valve, every material, every mechanical dimension... for particular applications in specific RCA home-instruments.

In effect, they're original parts. They restore original performance and original customer satisfaction.

You can spread that satisfaction around by using many of them for universal application, too. They're great for upgrading performance wherever you use them.

Call your RCA distributor. He'll set you up with a supply of the fastest moving ones today.

Parts and Accessories, Deptford, N.J.

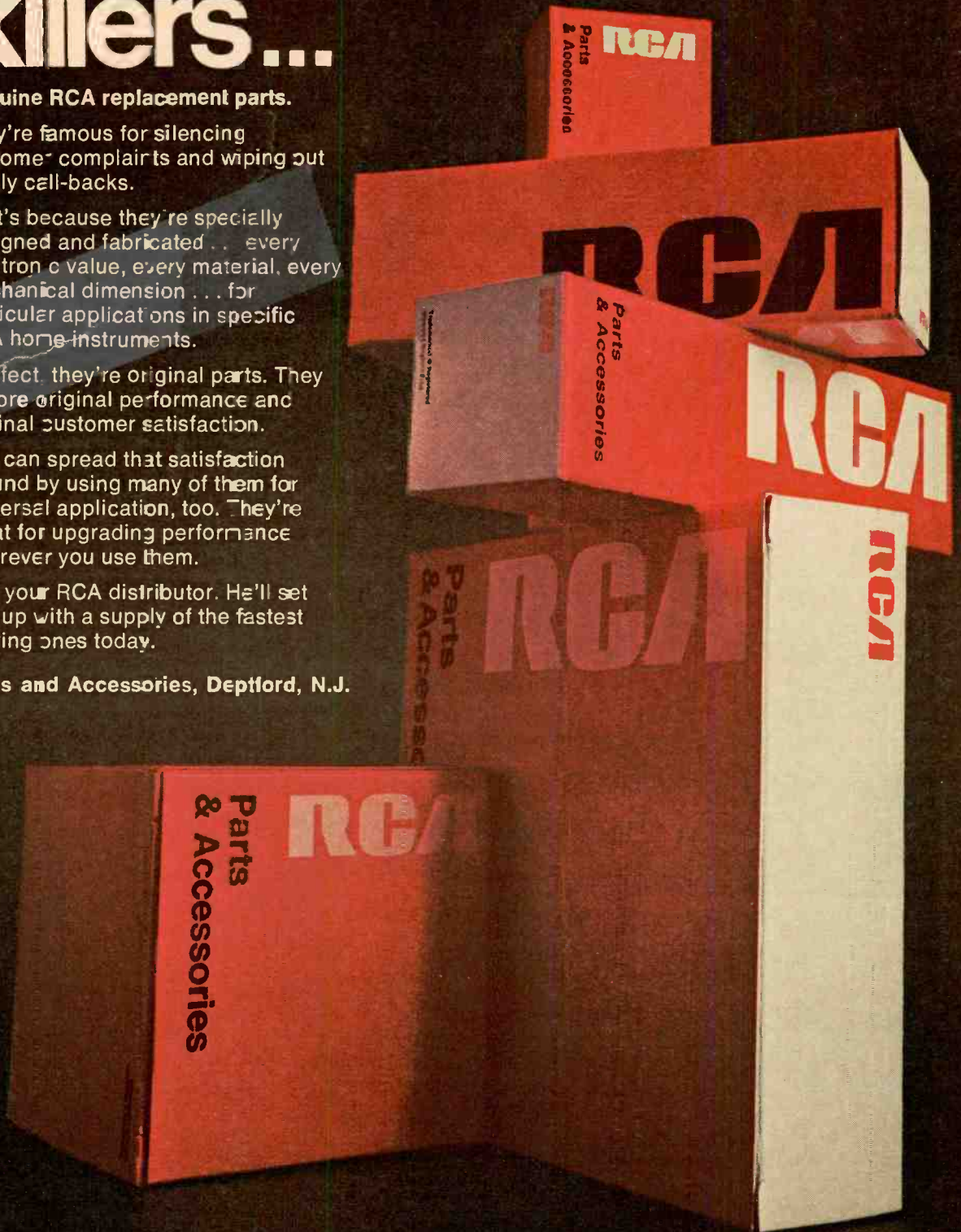

**There's no substitute
for SUCCESS...**



JAMES WONG--Research Engineer
Heald Engineering College Graduate

or IN-CLASS INSTRUCTION!

In electronics, it's the training that makes the difference. Employers require well-trained men and the first thing checked is where you gained your knowledge.

HEALD GRADUATES have many job offers with starting salaries often in excess of \$10,000 per year. AND advancement is rapid.

GET STARTED NOW. Be a
DRAFTSMAN---12 months
TECHNICIAN---15 months
ENGINEER (B.S. Deg.)---30 months
ARCHITECT (B.S. Deg.)---36 months

YOU are eligible for HEALD ENGINEERING COLLEGE if you have a high school education or the equivalent.

Increased income starts with success--- success starts with your move to Heald. Send now for FREE brochures with more information on Heald in San Francisco and your future in Engineering.

FREE LIFETIME PLACEMENT SERVICE
VETERAN APPROVED



WRITE TODAY FOR DETAILS

HEALD Engineering College

1215 Van Ness Ave., San Francisco, California 94109

Please send me information about:

- ARCHITECTURE
 - ENGINEERING: Civil Electrical
Electronic Mechanical
 - TECHNOLOGY: Electronic Engineering Technician (FCC)
Radio-Television Technician (FCC)
 - DRAFTING: Mechanical Electrical
Structural
- I am interested in Day Evening courses
Also send an application.

NAME _____ AGE _____
ADDRESS _____
CITY _____
STATE _____
ZIP _____ PHONE _____

Circle 10 on reader's service card

penny-size, silicon-water target enables the tube to produce images without illuminating the subject with floodlights. Light energy is converted into electrical energy by some 500,000 photodiodes on one side of the wafer. The new tube is the same size as standard vidicon tubes (1" in diameter, 7" long), but Bell predicts a lifetime of 20 years compared to the vidicon's few thousand hours.

MIXING 'MEMORY' CRYSTALS

Two different types of liquid crystal material are combined by an RCA scientist to form a quasi-emulsion that can "memorize" its reflective "on" condition after power is removed. The clear solution becomes



reflectively opaque when subjected to an electric field. ("Liquid Crystal Displays," News Briefs, August 1968). A storage cell in the "on" state is in the foreground. The novel mixture, when placed between transparent flat "windows", is expected to be useful for graphic displays that are changed only periodically.

SPACE GUN READIED



Earth will be "zapped" with a gun from outer space this year if all goes according to plan. The "attack," however, will be friendly and planned
(continued on page 12)

Radio - Electronics

HUGO GERNSBACK (1884-1967)
founder

M. HARVEY GERNSBACK,
editor and publisher

LARRY STECKLER, managing editor

Robert F. Scott, W2PWG
senior technical editor

John R. Free, associate editor

Jack Darr, service editor

I. Queen, editorial associate

Matthew Mandl, contributing editor

David Lachenbruch, contributing editor

Carrie Ng, editorial assistant

Bruce Ward, production manager

Elizabeth Shincel, production assistant

G. Aliquo, circulation manager

Cover by Harry Schlack

RADIO-ELECTRONICS is published by Gernsback Publications, Inc.
200 Park Ave. South
New York, N.Y. 10003
(212) 777-6400

President: M. Harvey Gernsback
Vice President-Secretary: G. Aliquo

ADVERTISING REPRESENTATIVES

EAST
John J. Lamson, Eastern Sales Manager

MIDWEST/N.&S. Car., Ga., Tenn.
Robert Pattis, the Bill Pattis Co., 4761 West Touhy Ave., Lincolnwood, Ill. 60466
(312) 679-1100

W. COAST/Texas/Arkansas/Oklahoma
J. E. Publishers Representative Co., 8380 Melrose Ave., Los Angeles, Calif. 90069,
(213) 653-5841; 420 Market St. San Francisco, Calif. 94111, (415) 981-4527

UNITED KINGDOM
Publishing & Distributing Co., Ltd., Mitre House, 177 Regent St., London W.1, England

SUBSCRIPTION SERVICE: Send all subscription correspondence and orders to RADIO-ELECTRONICS, Subscription Department, Boulder, Colo. 80302. For change of address, allow six weeks, furnishing both the old and new addresses and if possible enclosing label from a recent issue.

MOVING? Or writing about subscription? Be sure to fill out form below.

For FASTEST service on address change, missing copies, etc., attach old mailing label in first space below. Otherwise please print clearly your address as we now have it.

OLD ADDRESS (Attach old label if available)

Name

Address

City State

Zip Code

NEW ADDRESS


Name

Address

City State

Zip Code

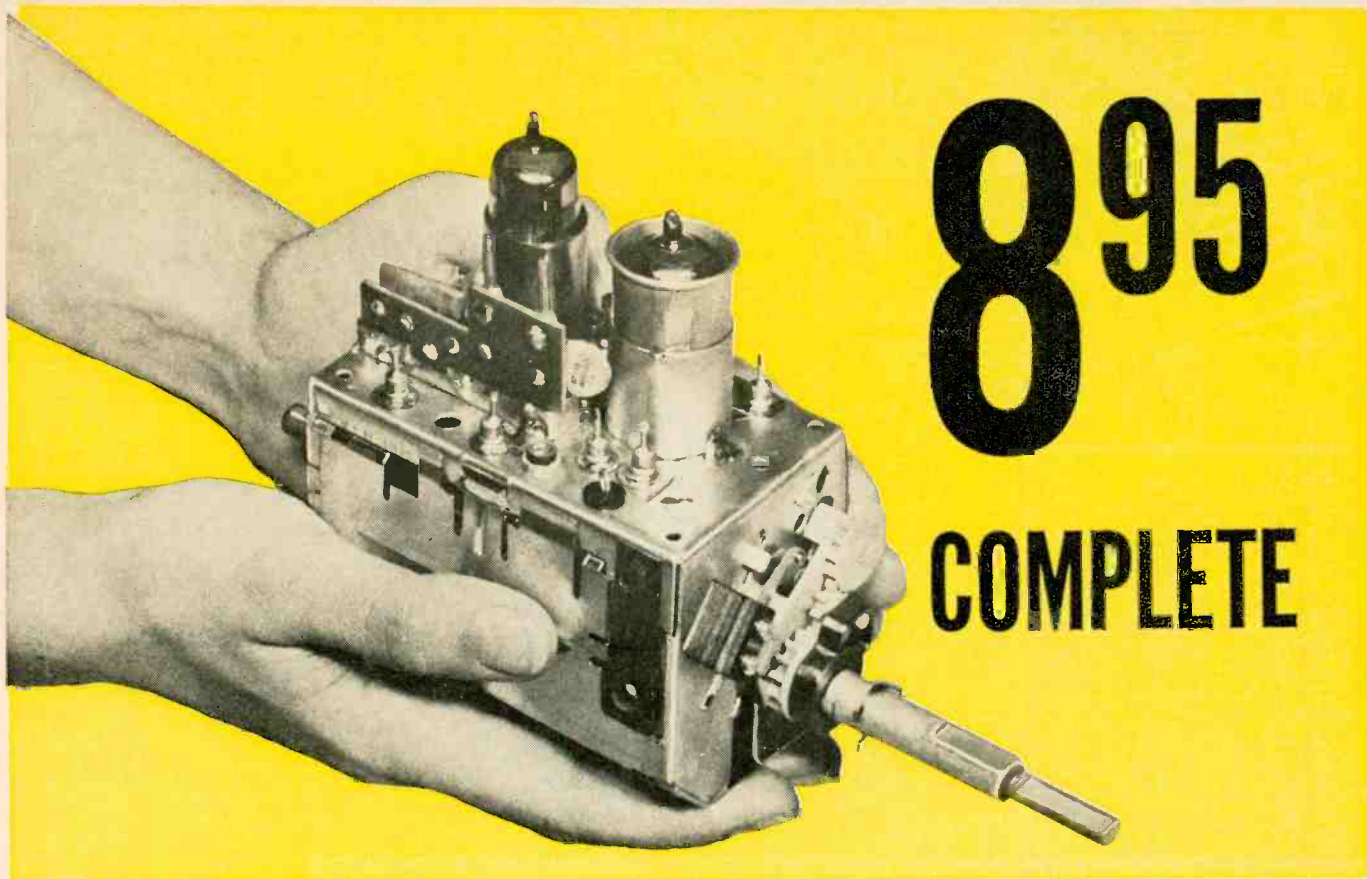Mail to: **RADIO-ELECTRONICS**
Subscription Dept. Boulder, Colo. 80302



895 COMPLETE

Castle, the pioneer of television tuner overhauling, offers the following services to solve ALL your television tuner problems.

● **OVERHAUL SERVICE** — All makes and models.

- VHF or UHF tuner \$9.95
- UHF-VHF combination (one piece chassis) \$9.95
- TRANSISTOR tuner \$9.95
- COLOR tuner \$9.95
(Guaranteed color alignment . . . no additional charge)

Overhaul includes parts, except tubes and transistors.

Simply send us the defective tuner complete; include tubes, shield cover and any damaged parts with model number and complaint. Your tuner will be expertly overhauled and returned promptly, performance restored, aligned to original standards and warranted for 90 days.

UV combination tuner must be single chassis type; dismantle tandem UHF and VHF tuners and send in the defective unit only.

And remember—for over a decade Castle has been the leader in this specialized field . . . your assurance of the best in TV tuner overhauling.

● **CUSTOM REPLACEMENTS**

Exact replacements are available for tuners that our inspection reveals are unfit for overhaul. As low as \$12.95 exchange. (Replacements are new or rebuilt.)

● **UNIVERSAL REPLACEMENTS**

Prefer to do it yourself?

Castle universal replacement tuners are available with the following specifications.

STOCK No.	HEATERS	SHAFT		I.F. OUTPUT		PRICE
		Min.*	Max.*	Snd.	Pic.	
CR6P	Parallel 6.3v	1¾"	3"	41.25	45.75	8.95
CR7S	Series 600mA	1¾"	3"	41.25	45.75	9.50
CR9S	Series 450mA	1¾"	3"	41.25	45.75	9.50
CR6XL	Parallel 6.3v	2½"	12"	41.25	45.75	10.45
CR7XL	Series 600mA	2½"	12"	41.25	45.75	11.00
CR9XL	Series 450mA	2½"	12"	41.25	45.75	11.00

*Selector shaft length measured from tuner front apron to extreme tip of shaft.

These Castle replacement tuners are all equipped with memory fine tuning, UHF position with plug input for UHF tuner, rear shaft extension and switch for remote control motor drive . . . they come complete with hardware and component kit to adapt for use in thousands of popular TV receivers.

Order universal replacements out of Main Plant (Chicago) only.



CASTLE TV TUNER SERVICE, INC.

MAIN PLANT: 5715 N. Western Ave., Chicago, Illinois 60645
EAST: 41-96 Vernon Blvd., Long Island City, N.Y. 11101

Circle 11 on reader's service card

Discover the ease and excitement of learning Electronics with programmed equipment NRI sends you

When you train at home with NRI, you train with your hands as well as your head. You learn the WHY of Electronics, Communications, TV-Radio the NRI pioneering "3-Dimensional" way. NRI training is the result of more than half a century of simplifying, organizing, dramatizing subject matter, and providing personal services unique for a home study school. You get the kind of technical training that gives you priceless confidence as you gain experience equal to many, many months of training on the job.



NRI—The 53 Year Leader in Electronics Training

APPROVED UNDER NEW GI BILL

If you served since January 31, 1955, or are in service, check GI line in postage-free card.



*Earn \$5 or more an hour
spare or full time in*

TV-RADIO SERVICING

Color Television has arrived. Sales are soaring, along with the continuing popularity of other home entertainment equipment like portable radios, tape recorders, hi-fi sets, phonographs and auto radios. TV-Radio servicing is one of your best routes to spare-time earnings, a good paying job or a business of your own. NRI not only trains you quickly and expertly, but also shows you how to get started in Servicing soon after you enroll, earning as you learn. NRI trains you in today's methods of installing and repairing all Electronic equipment for the home—including booming Color TV. You even build, experiment with and keep to enjoy your own solid-state radio and your choice of black-and-white or Color TV receiver. Like thousands of others, you can be earning \$5 or more an hour extra in spare time starting soon.

*There's money and
success awaiting you in*

BROADCASTING — COMMUNICATIONS


The experience you gain from intensely practical NRI training in Complete Communications equals as much as two years of training on the job. With NRI, you can train for a choice of careers ranging from mobile, marine and aviation radio to TV broadcasting and space communications. You learn how to install, maintain and operate today's remarkable transmitting and receiving equipment by actually *doing* it. You build and experiment with test equipment, like a VTVM you keep. You build and operate amplifier circuits, transmission line and antenna systems, even build and use a phone-cw transmitter suitable for transmission on the 80-meter amateur band. Whichever of five NRI Communications courses you choose, you prepare for your FCC License exams, and *you must pass your FCC exams or NRI refunds your tuition in full.*

*Move ahead in America's
fast growing industry as*

ELECTRONICS TECHNICIAN

Electronics touches everyone's lives. This vast field of opportunity is open to you with NRI training. Industrial/Military Electronics training—like all NRI courses—prepares you quickly, thoroughly the practical "hands on" way. You build with, and learn to understand the functions of, today's miracle solid-state components like printed circuits, diodes and transistors. You build and experiment with Electronic circuitry used in automation, data processing, ultrasonics, telemetry. Whatever your interest in Electronics, NRI training can fill your needs. Prove to yourself what nearly a million NRI students could tell you . . . that you get more for your money from NRI. Check the postage-free card and mail it today for your FREE NRI Color Catalog. No salesman will call. NATIONAL RADIO INSTITUTE, Electronics Division, Washington, D.C. 20016.

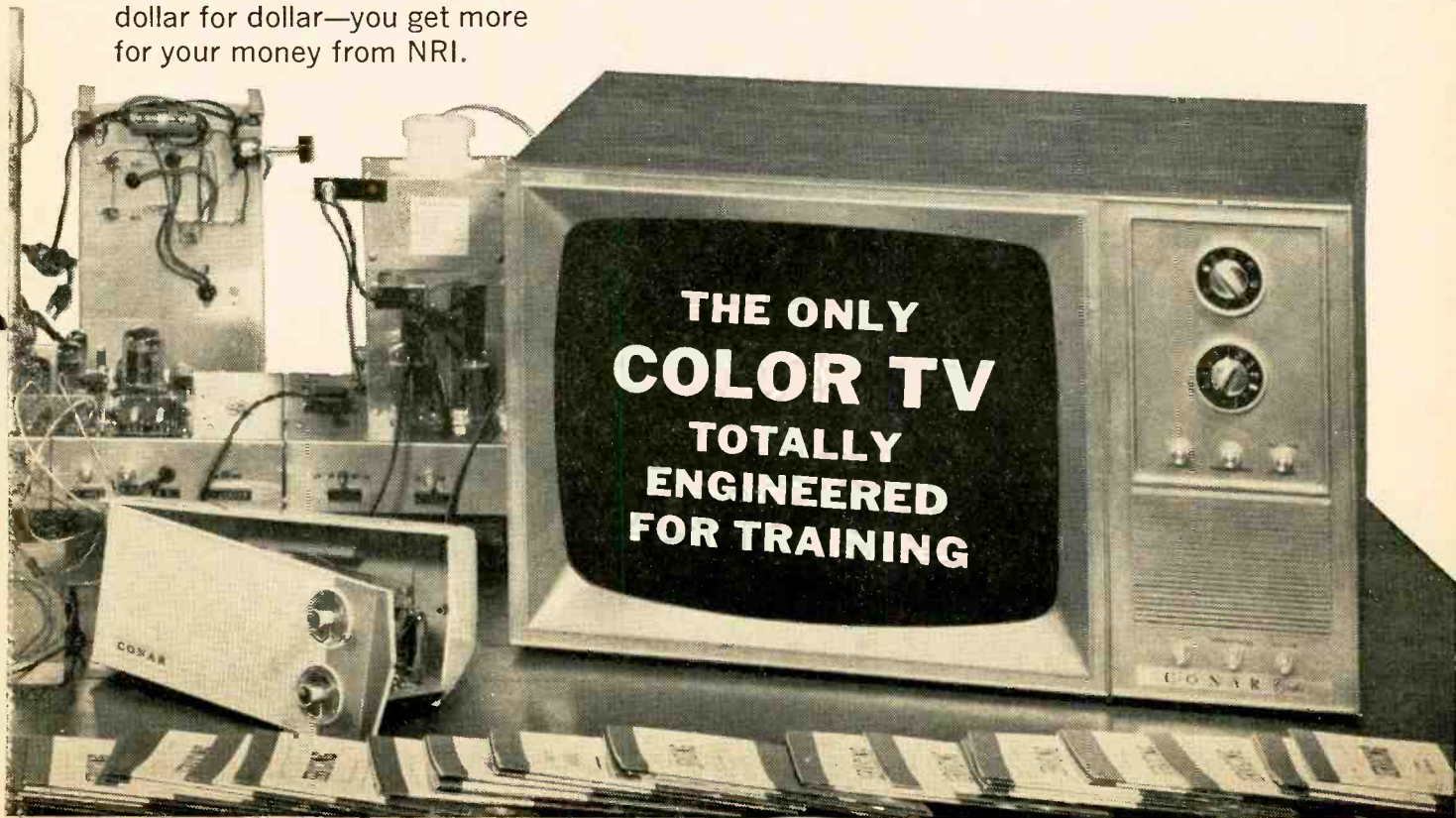YOU GET MORE FOR YOUR MONEY FROM NRI — Build, test, explore, discover. Everything you see here is included in one NRI course—including Color TV. Other courses equally complete. And you'll be surprised at the low tuition costs. Text for text, kit for kit, dollar for dollar—you get more for your money from NRI.



The TRUE electronic solution to a major problem of engine operation!

DELTA'S FABULOUS MARK TEN®



Only \$44.95 ppd.
In easy-to-build Deltakit®
Only \$29.95 ppd.

CAPACITIVE DISCHARGE IGNITION SYSTEM

You've read about The Mark Ten in *Mechanix Illustrated*, *Popular Mechanics*, *Electronics* and other publications!

Now discover for yourself the dramatic improvement in performance of your car, camper, jeep, truck, boat — any vehicle! Delta's remarkable electronic achievement saves on gas, promotes better acceleration, gives your car that zip you've always wanted. Find out why even Detroit has finally come around. In four years of proven reliability, Delta's Mark Ten has set new records of ignition benefits. No re-wiring! Works on literally any type of gasoline engine.

Why settle for less when you can buy the original DELTA Mark Ten, never excelled and so unique that a U.S. Patent has been granted.

READY FOR THESE BENEFITS?

- ▲ Dramatic Increase in Performance and in Fast Acceleration
- ▲ Promotes more Complete Combustion
- ▲ Points and Plugs last 3 to 10 Times Longer
- ▲ Up to 20% Mileage Increase (saves gas)

LITERATURE SENT BY RETURN MAIL
BETTER YET — ORDER TODAY!



DELTA PRODUCTS, INC. DP 7-17

P.O. Box 1147 RE • Grand Junction, Colo. 81501

Enclosed is \$ _____ Ship ppd. Ship C.O.D.

Please send:

- Mark Tens (Deltakit®) @ \$29.95
(12 VOLT POSITIVE OR NEGATIVE GROUND ONLY)
- Mark Tens (Assembled) @ \$44.95
- 6 Volt: Negative Ground only.
- 12 Volt: Specify Positive Ground Negative Ground

Car Year _____ Make _____

Name _____

Address _____

City/State _____ Zip _____

Circle 13 on reader's service card


NEWS BRIEFS

(continued from page 6)

by NASA scientists to determine if man can create artificial aurora light formations in the atmosphere. This electron accelerator system will be carried 120–180 miles into space by an Aerobee rocket to fire a stream of charged particles toward the atmosphere. The gun's reed-switching mechanism, which fits an 8"-deep gun platform assembly, is in the foreground. Device was built by Ion Physics Corp.

'FLIPPED' CRYSTAL DELAY LINE

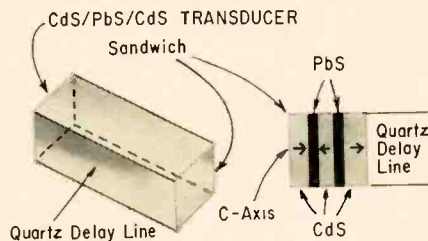A technique of "flipping" alternate layers of thin-film piezoelectric transducers makes possible acoustic delay lines with four times the power range and twice the frequency range of earlier transducer crystals. The devices convert electrical signals into



CdS = Cadmium Sulfide, PbS = Lead Sulfide.

sound waves for an interval, then convert the signal back into electricity. The transducer sandwiches consist of up to five layers of crystalline piezoelectric cadmium sulfide separated by extremely thin crystalline layers of lead sulphide. The PbS layers, Westinghouse scientist Dr. John de Klerk discovered, reverse the transduction direction of successive CdS layers. When an electric field is applied across the crystal, the reversed layers assure correct acoustical phasing.

TELEVISION FROM SPACE

India is planning a pilot project for 1971 in which TV broadcasts from a satellite will be received directly by 10,000 community receivers and rebroadcast to three times as many sets by vhf stations. Plans call for eventually broadcasting directly to all of the country's villages and cities. NASA is cooperating with the Indian Government, and will provide communication channels for Indian use aboard a synchronous satellite to be orbited above the Indian Ocean in 1971. R-E

12

RADIO-ELECTRONICS

new SAMS books

Television Service Training Manual, 2nd Edition

by Edward F. Rice. Updated and expanded to include new servicing short cuts and tests, this book is the key to quick and profitable TV repair for both beginners and experienced technicians. Through the use of skillfully chosen circuit test points, and text keyed to the schematics, troubles are quickly isolated to specific components. Thorough treatment of all sections of the TV receiver, and wide use of schematics, charts, and drawings provide you with rapid, sure-fire analysis and repair procedures. 240 pages.
Order 20628, only\$4.95

101 Questions & Answers About Auto Tape Units

by Leo G. Sands. The answers to your questions about the increasingly popular automobile tape playing units are presented in easy-to-understand question and answer form. The information you want is contained in six sections dealing with tape cartridges and cassettes, cartridge and cassette players, circuitry, installation procedures, troubleshooting, and maintenance. 72 pages.
Order 20671, only\$1.75

101 Easy Test Instrument Projects

by Robert M. Brown & Tom Kneitel. If you are interested in the fun and challenge of building your own money-saving test equipment, this book is for you. Most of the projects in this book cost less than \$5 to build and can be put together in a single evening. Projects range in complexity from a simple continuity tester to a sound level meter or a radiation finder; also includes power supplies, signal tracers and injectors, meters, generators, transistor testers, picture tube rejuvenators, metal locators, flashlight cell chargers, and many others. 128 pages.
Order 20678, only\$3.25

Electronics in Photography

by Byron G. Wels. Whether you are a photography fan or an electronics man, you will enjoy this informal, clear explanation of how electronic photographic equipment works. Practical theory covers converting electricity into light (lights, lamps, and flash units) and the reverse (photocells); discusses timing and timing devices, controls, electronic cameras, and synchronization of sound and film. Also includes chapters on wiring the darkroom and making repairs. 128 pages.
Order 20672, only\$3.50

FET Principles, Experiments, and Projects

by Edward M. Noll. Covers the operating principles of FET's (field effect transistors) for the audio enthusiast, radio amateur, short-wave listener, CB'er, and experimenter. Theory coverage is basic, with emphasis on practical mathematics used in the featured experiments and projects. Inserting proper component values for favorable circuit operation is taught by use of pegboard or simple chassis mounting arrangements. Includes chapter on FET mathematics. 272 pages.
Order 20594, only\$4.95

These and over 300 other SAMS books are available from your Electronic Parts Distributor

Howard W. Sams & Co., Inc.

Order from your Sams Distributor today, or mail to Howard W. Sams & Co., Inc., Dept. RE-12, 4300 W. 62nd Street, Indianapolis, Ind. 46268

Send me the following books:

- 20628 20673 20594
- 20671 20672

\$ _____ enclosed

Name _____


Address _____

City _____

State _____ Zip _____

My Distributor is _____

Circle 14 on reader's service card

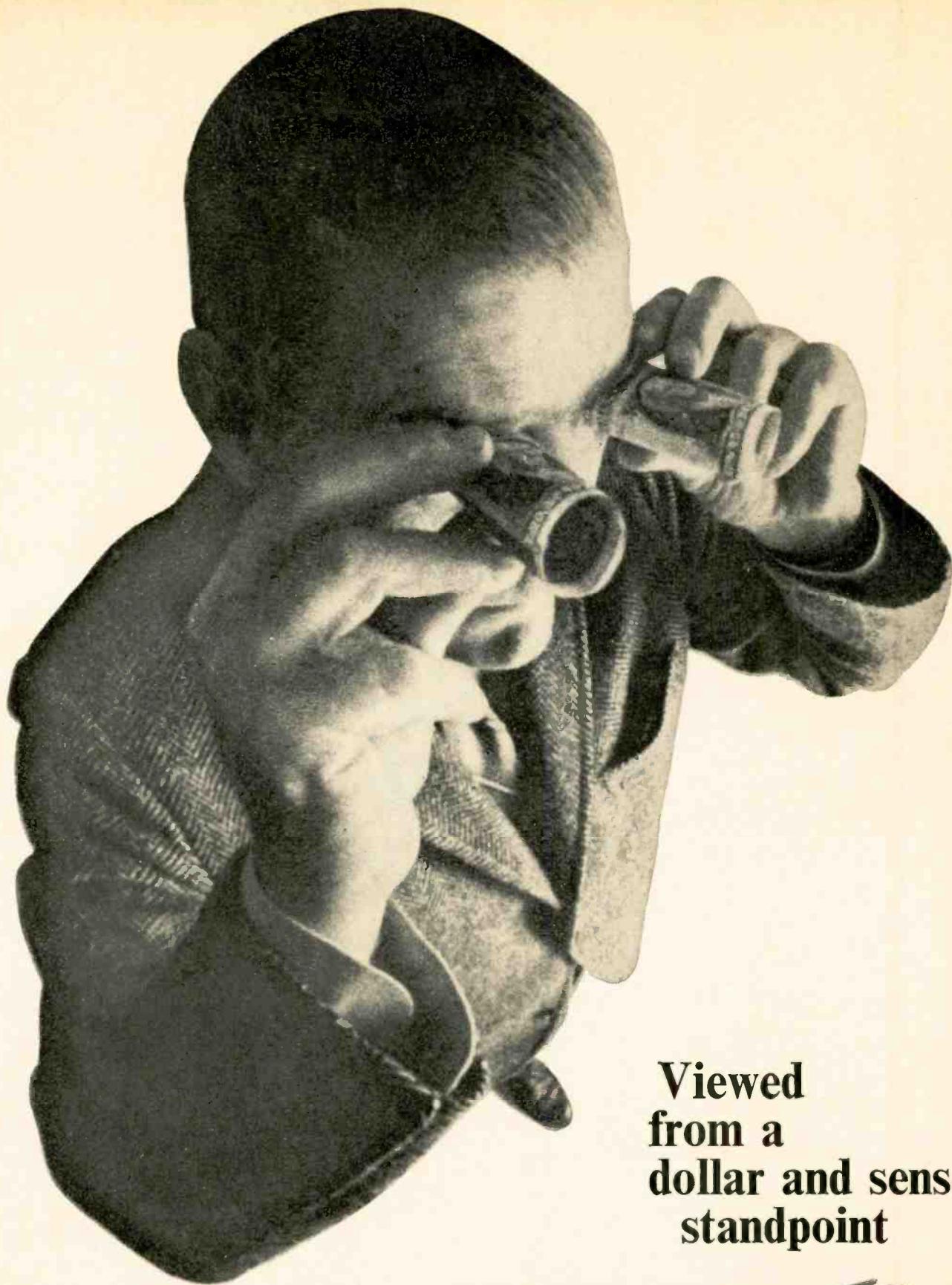

Viewed from a dollar and sense standpoint

You can't get a better buy for your hi-fi system than a Shure cartridge, whether it's the renowned "Super Track" V-15 Type II at \$67.50 or the new M91E Easy-Mount "Hi-Track" at \$49.95, made in the tradition of all fine Shure cartridges. If you're new to hi-fi, benefit from the published opinions of experts the world over: the **Shure V-15 Type II Super Track** makes a decidedly hearable difference. If you want to spend less, the M91E is right for you. You can always "trade-up" to a V-15 Type II at a later date. Shure Brothers, Inc., 222 Hartrey Avenue, Evanston, Illinois 60204.


NEW! M91E Hi-Track Elliptical Cartridge with optimized design parameters for trackability second only to the incomparable V-15 Type II. Bi-radial .0002" x .0007" diamond stylus. 20-20,000 Hz. Channel Separation: more than 25 db @ 1 KHz. Tracking force range 3/4 to 1 1/2 grams. Trackability specifications @ 1 gram: 20 cm/sec @ 400 Hz.; 28 cm/sec @ 1 KHz.; 25 cm/sec @ 5 KHz.; 18 cm/sec @ 10 KHz. \$49.95.

Circle 15 on reader's service card



© 1968 SHURE BROTHERS, INC.

C Correspondence

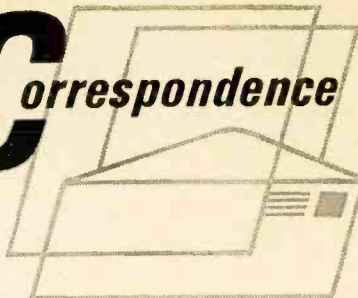

I WANT AN INDEX

Just looked at the December 1967 index and from what I saw, I would very much like you to continue with your annual indexes.

In earlier indexes (1950's) the big problem was that you had to look under almost all the headings to find what you were after and even then you might only get part of what was covered in that year since the Correspondence, Noteworthy Circuits, and Try This One columns usually weren't listed.

One idea which I would like to see you incorporate is to publish the yearly index and also an index covering a period of five or ten years.

KEITH MUDDLE
Stratford, Ont., Canada

We'll compromise. There will be an index in the December 1968 issue. But it will be shortened somewhat. It will list all articles and monthly columns. However, it will not break down each department in detail. The space we save will be used to present you with an extra article.

NEW RESISTANCE BRIDGE

Recently the United States Patent Office granted me a patent on a new resistance measuring bridge.

To measure the resistance of an ordinary carbon resistor, we normally use an ohmmeter. But an ohmmeter is unreliable when measuring the resistance of a 1/2% wirewound resistor. To measure the resistance of such precision wirewound resistors we use a Wheatstone bridge.

But resistance can be measured to a remarkable degree of perfection. Many instruments have been made that depend on resistance change to measure temperature, chemical composition, strain, etc. To measure the temperature from the planet Mars requires something more accurate than a Wheatstone bridge. The Bucher bridge, my invention will do it.

The Bucher bridge will measure as accurately one mile from the unknown resistor as it will three inches

conversation piece.

Just look at the Pace Base! Forget for a second that it's the complete CB two way radio that needs no extras. What makes it more unusual is how it looks. So attractive, so decorative. With wood grained cabinet and elegant over-all appearance, even the lady of the house likes to have it around. The Pace Base Station is neat—and complete. Included in one unit are standing wave ratio meter, power meter, S meter and variable output control mike. All for \$330.00.

See your electronic dealer or write us.

((P)) PACE COMMUNICATIONS CORP.
a NOVA-TECH company

24049 S. Frampton Avenue, Harbor City, California 90710
ENGINEERED WITH THE ENGINEER IN MIND


Circle 16 on reader's service card

for
her...



2 FREE PAIRS
of famous
KAYSER[®]
gloves!

for
him...

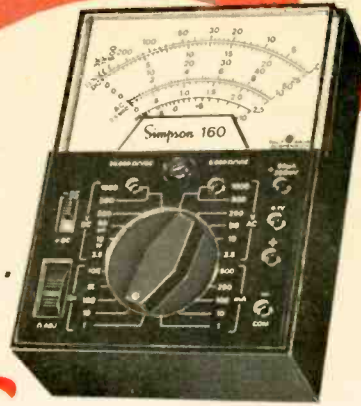

Simpson's
160 Handi-VOM[®]



Wouldn't you like your wife to give you a 160 VOM this Christmas?

Right now at participating Simpson distributors . . . the 160 Christmas package. Your wife buys the 160 Handi-VOM[®] for you—and receives a bonus for herself. Two *free* pairs of famous Kayser gloves!

Kayser, as your wife knows, is the quality fashion glove sold in fine stores. She'll receive a black and a white pair, in stretch nylon, free with the Simpson 160.

And you will get the one hand-size VOM with full-size VOM accuracy and sensitivity. Its virtually friction-free Taut Band movement is protected by a varistor from even 200,000% overloads. The five resistance ranges, combined with low millivolt and microvolt ranges, are just what's needed for work on today's solid-state circuits.

Your Simpson distributor has been allotted only a limited supply of special 160 Christmas packages—so hurry!



Look for the special
Simpson 160 Christmas
Package at your local
Electronic Parts Distributor

160 Handi-VOM[®] complete
with batteries, test leads, and
operator's manual. . . . \$53.00


SIMPSON ELECTRIC COMPANY

5200 W. Kinzie Street, Chicago, Illinois 60644 • Phone (312) 379-1121

DECEMBER 1968

15

BREAKTHROUGH

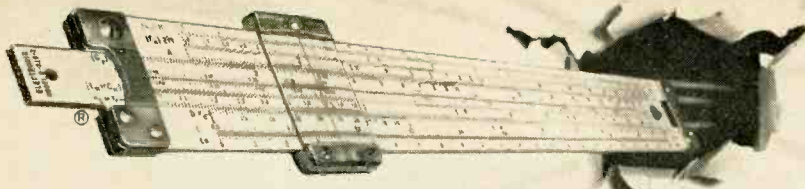

IN ELECTRONICS CALCULATING

Still plodding through math and electronics problems the slow pencil-and-paper way? Smash the paperwork barrier with this new Electronics Slide Rule.

Even if you've never used a slide rule before, you can whiz through resonant frequency calculations and inductive or capacitive reactance problems. You can find reciprocals for resistance formulas instantly. You can even locate tricky decimal points in a jiffy.

You can also work regular math problems in a flash: multiplication, division, square roots, logarithms, trigonometry.

Anyone can use this sturdy 12-inch, all-metal slide rule. We show you how with our complete 4-lesson instruction course. Slide rule, course, and handsome leather carrying case deliberately priced low as our way of making friends with men in Electronics. FREE booklet gives full details. Mail coupon below today.

MAIL THIS COUPON FOR FREE BOOKLET

CIE Cleveland Institute of Electronics
1776 E. 17th St., Cleveland, Ohio 44114

Please send me, without charge or obligation, your booklet describing the Electronics Slide Rule and 4-lesson instruction course. Also FREE if I act at once—a handy, pocket-sized Electronics Data Guide.



Name _____ (please print)

Address _____

City _____ State _____ Zip _____

Accredited Member National Home Study Council • A Leader in Electronics Training... Since 1934 **RE-159**

Circle 17 on reader's service card

Build this pipelike Schober Recital Organ for only \$1725!*



*Includes finished walnut console. (Only \$1361 if you build your own console.) Amplifier, speaker system, optional accessories extra.

You couldn't touch an organ like this in a store for less than \$4,000—and there never has been an electronic instrument with this vast variety of genuine pipe-organ voices that you can add to and change any time you like! All four families of formal pipe tones are present in variety to delight players of classic and religious music. Yet you can change the entire organ for popular and theatrical sounds, or plug in special voices for baroque, romantic, or modern repertoires. If you've dreamed of the sound of a large pipe organ in your own home, if you're looking for an organ for your church, you'll be more thrilled and happy with a Schober Recital Organ than you could possibly imagine—kit or no kit.

You can learn to play it—and a full-size, full-facility instrument is easier to learn on than any cut-down "home" model. And you can build it, from Schober Kits, world famous for ease of assembly without the slightest knowledge of electronics or music, for design and parts quality from the ground up, and—above all—for the highest praise from musicians everywhere.

Send right now for the full-color Schober catalog, containing specifications of all five Schober Organ models, beginning at \$599.50. No charge, no obligation. If you like music, you owe yourself a Schober Organ!

The Schober Organ Corp., Dept. RE-61
43 West 61st Street, New York, N.Y. 10023

- Please send me Schober Organ Catalog and free 7-inch "sample" record.
- Enclosed please find \$1.00 for 12-inch L.P. record of Schober Organ music.

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

Circle 18 on reader's service card

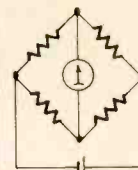


Fig. 1

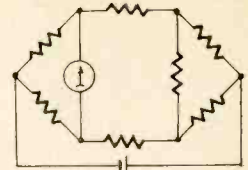


Fig. 2

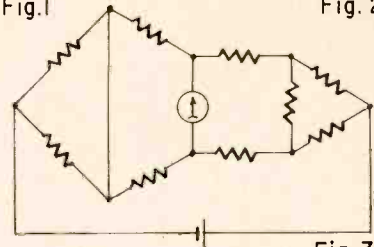


Fig. 3

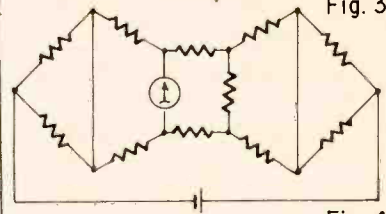


Fig. 4

from the same unknown resistor.

Fig. 1 shows a conventional Wheatstone bridge. Figs. 2, 3 and 4 are forms of the Bucher bridge. Fig. 2 is the hexagon bridge. Fig. 3 is the octagon bridge. Fig. 4 is the decagon bridge.

DR. J. F. BUCHER
2980 River Road
Eugene, Ore.

Hate to say it, Doctor, but you're a tease. You've got to tell us more. How does the bridge work? What's your patent number? How do you make those long-distance measurements? Put it all together and you may end up with an article R-E readers would find fascinating.

EAVESDROPPING DROPOUT

Len Buckwalter's article, "Eavesdrop on Aircraft, Fire & Police" was interesting (August 1968). But like all other articles on the subject, he neglected the 450-470-MHz band.


In Fig. 1 the band is listed and that's about it. Not a word is mentioned about converters or receivers.

A few converters are available for the uhf band. They are not easy to locate, but do exist. The Ameco model CUT is probably the best on the market. Olsen sells one called the Clark 450. And the Electra Corp. makes two units called the Little Tiger and the Eavesdropper Jr.

KEN GREENBERG
Chicago, Ill.

Ok, Ken, you've filled that gap yourself. Thanks for the comments. But until 450-470-MHz gear is readily available at reasonable prices, many readers cannot get it.

R-E

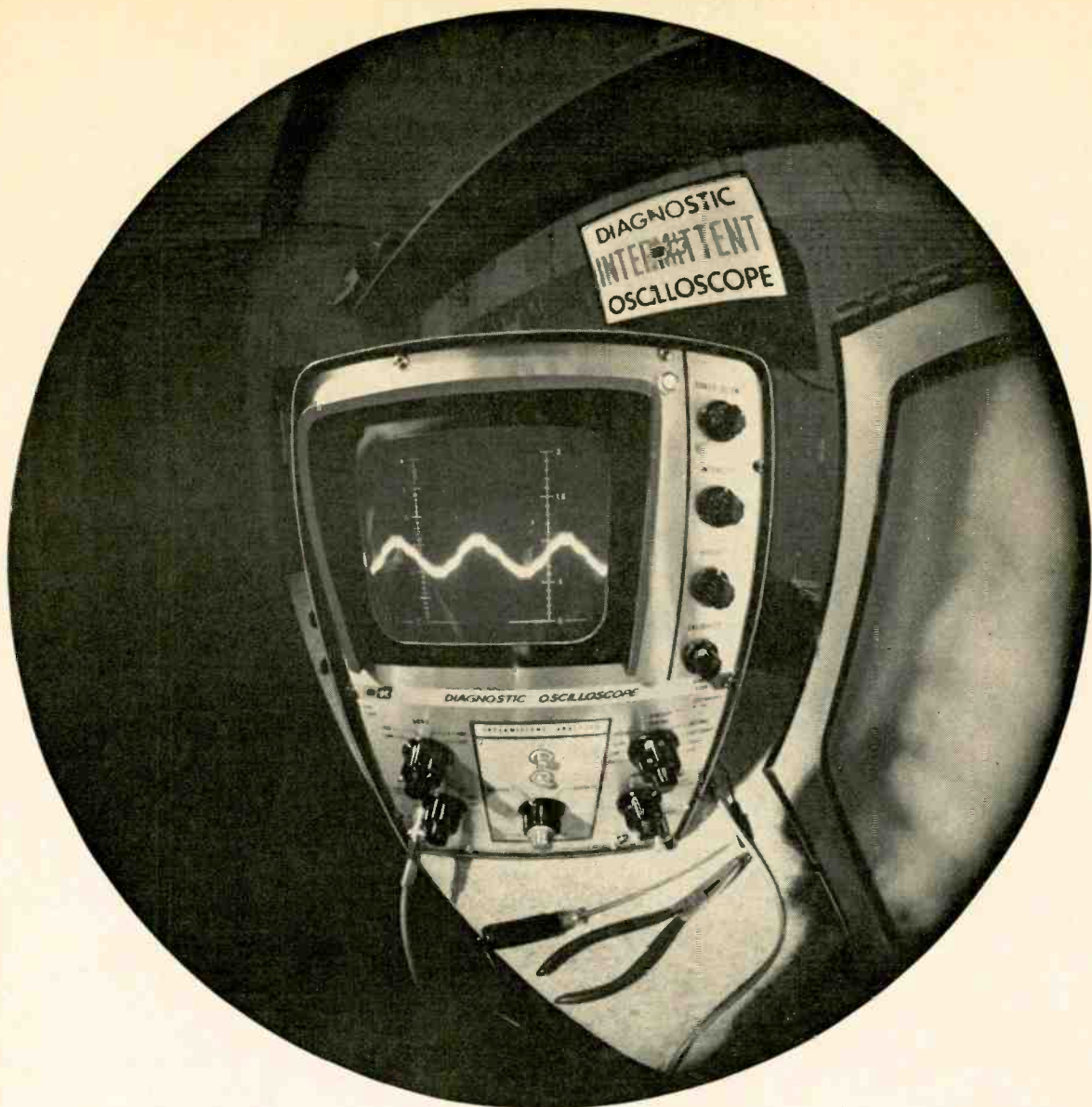

Another benchwarmer?

Not this one. Our new B&K Diagnostic Oscilloscope is more than re-engineering of an old model to keep pace with TV technology. It is instead a basic departure from all other oscilloscopes. A departure that has simplified a complex instrument to make it easier for you to use. But there's something else.



What this oscilloscope has is exclusive. An Intermittent Analyzer with electronic memory—and optional remote Audio/Visual Alarm.

With it, the elusive intermittent conditions that make so many TV sets tough dogs can now be detected and identified in your absence. Preset one control.

When the faulty stage is detected, you'll know about it as soon as you come back from service calls. Then run the scope overnight to check another set for an intermittent condition.

All this adds up to greater shop efficiency, more time for profit-making service calls and a lot more mileage out of a very fine diagnostic oscilloscope.


An oscilloscope that shows vector patterns exactly as specified by color TV manufacturers. (All vectorscope inputs and controls are conveniently located on the front panel.) Also allows you to read peak-to-peak voltages in all ranges on a double-scale calibrated screen—just by turning a switch. (As the range is selected, the appropriate scale lights automatically.)

Circle 19 on reader's service card

Automatic synchronization locks in all patterns at any signal level or frequency. There are also fewer controls and these are positioned for easier operation.

Give our Diagnostic Oscilloscope some thought. It's worth it not to be sidelined with a benchwarmer. See your B&K Distributor or drop us a note for detailed literature on Model 1450 and our full-line test equipment catalog, AP-24.

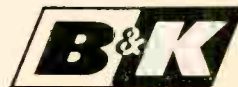DIAGNOSTIC OSCILLOSCOPE
Model 1450, Net: \$279⁹⁵



B & K Division of DYNASCAN CORPORATION
1801 W. Belle Plaine - Chicago, Illinois 60613
Where electronic innovation is a way of life.

Two more examples of how RCA Institutes provides up-to-the-minute Home Training in all phases of electronics:


NEW CATV LESSONS

The demand is heavy for technicians in the booming field of CATV (Community Antenna Television Systems).

CATV was initially used to make it possible for large numbers of television receiver users to get good reception in remote areas through the use of a common antenna. It now brings to more people more programs than are available from local stations. It also improves reception where multipath signal transmission exists.

RCA Institutes includes two comprehensive lessons, covering the practical phases of CATV systems and servicing in Television Servicing and Communications courses and programs at no additional total tuition cost. Get in on the ground floor of this rewarding and expanding field. Send for full information today!

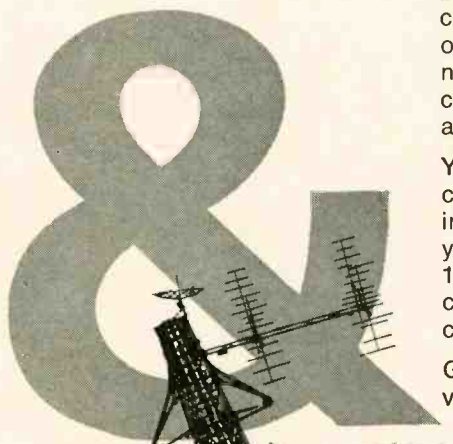Prepare yourself for a career in the expanding field of CATV.



NEW COLOR TV KIT


To make courses even more practical and to better prepare you for a more rewarding future, RCA Institutes now includes an exciting Color TV Kit in both the beginner's program and the advanced course in color TV servicing. The cost of the kit is included in the tuition—nothing extra to pay. You also get five construction/experiment manuals plus a comprehensive service manual.

You'll receive all the materials and components to perform over 50 information-packed experiments. When you finish you'll have constructed an 18" (measured diagonally) high quality, color TV set, complete with rich cabinet in wood grain design.

Get all the details on RCA Institutes' valuable new Color TV Kit!

SEND THE ATTACHED CARD TODAY!

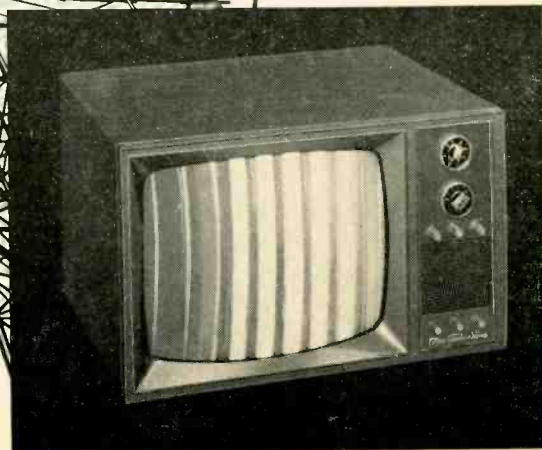This is the high quality color TV set you'll construct, complete with rich cabinet in wood grain design.



Learn electronics at home faster, easier, almost automatically—with RCA AUTOTEXT

Are you just a beginner with an interest in the exciting field of electronics? Or, are you already earning a living in electronics and want to brush-up or expand your knowledge in a more rewarding field of electronics? In either case, AUTOTEXT, RCA Institutes' own method of Home Training will help you learn electronics more quickly and with less effort, even if you've had trouble with conventional learning methods in the past.

THOUSANDS OF WELL PAID JOBS ARE OPEN NOW TO MEN SKILLED IN ELECTRONICS!

Thousands of well paid jobs in electronics go unfilled every year because not enough men have taken the opportunity to train themselves for these openings. RCA Institutes has done something positive to help men with an aptitude and interest in electronics to qualify for these jobs.

HOME STUDY CAN TRAIN YOU FOR REWARDING CAREER OPPORTUNITIES

To help fill the "manpower gap" in the electronics field, RCA Institutes has developed a broad scope of Home Training courses, all designed to lead to a well paying career in electronics in the least possible time. You also have the opportunity to enroll in an RCA "Career Program" exclusively created to train you quickly for the job you want! Each "Career Program" starts with the amazing AUTOTEXT Programmed Instruction Method. And, all along the way, your program is supervised by RCA Institutes experts who become personally involved in your training and help you over any "rough spots" that may develop.

VARIETY OF KITS ARE YOURS TO KEEP

To give practical application to your studies, a variety of valuable RCA Institutes engineered kits are included in your program. Each kit is complete in itself, and yours to keep at no extra cost. You get the new Programmed Electronics Breadboard for limitless experiments, including building a working signal generator, multimeter, and a fully transistorized superheterodyne AM receiver.

ONLY FROM RCA INSTITUTES— TRANSISTORIZED TV KIT— VALUABLE OSCILLOSCOPE

All students receive a valuable oscilloscope. Those enrolled in the Television program receive the all-new transistorized TV Kit. Both at no extra cost and only from RCA Institutes.

CHOOSE THE "CAREER PROGRAM" THAT APPEALS MOST TO YOU

Start today on the electronics career of your choice. Pick the one that suits you best and mark it off on the attached card.

- Television Servicing
- Telecommunications
- FCC License Preparation
- Automation Electronics
- Automatic Controls
- Digital Techniques
- Industrial Electronics
- Nuclear Instrumentation
- Solid State Electronics
- Electronics Drafting

ADVANCED TRAINING

For those already working in electronics, RCA Institutes offers advanced courses. You can start on a higher level without wasting time on work you already know.

2 CONVENIENT PAYMENT PLANS

RCA Institutes offers a unique tuition plan that lets you progress at your own pace. You only pay for lessons as you order them. You don't sign a contract obligating you to continue the course.

There's no large down-payment to lose if you decide not to continue.

However, if you desire, RCA Institutes also offers a convenient monthly payment plan.

CLASSROOM TRAINING ALSO AVAILABLE

If you prefer, you can attend classes at RCA Institutes Resident School, one of the largest of its kind in New York City. Coeducational classroom and laboratory training, day and evening sessions, start four times a year. Simply check "Classroom Training" on the attached card for full information.

JOB PLACEMENT SERVICE, TOO!

Companies like IBM, Bell Telephone Labs, GE, RCA, Xerox, Honeywell, Grumman, Westinghouse, and major Radio and TV Networks have regularly employed graduates through RCA Institutes' own placement service.

SEND ATTACHED POSTAGE PAID CARD TODAY. FREE DESCRIPTIVE BOOK YOURS WITHOUT OBLIGATION. NO SALESMAN WILL CALL.

All RCA Institutes courses and programs are approved for veterans under the new G.I. Bill.

Accredited Member
National Home Study Council

IF REPLY CARD IS DETACHED—SEND THIS COUPON TODAY
RCA INSTITUTES, Inc., Dept. REQ-D8
320 West 31st Street, N.Y., N.Y. 10001

Please rush me FREE illustrated catalog. I understand that I am under no obligation, and that no salesman will call.

Name _____ Age _____
(please print)

Address _____

City _____

State _____ Zip _____

now... a dozen tools
for dozens of jobs
in a hip pocket set!



No. 99PS-50

Really compact, this new nutdriver/screwdriver set features 12 interchangeable blades and an amber plastic (UL) handle. All are contained in a slim, trim, see-thru plastic case which easily fits hip pocket. Broad, flat base permits case to be used as a bench stand. Ideal for assembly and service work.

7 NUTDRIVERS:

3/16", 7/32", 1/4",
9/32", 5/16", 11/32",
3/8" hex openings.

**2 SLOTTED
SCREWDRIVERS:**

3/16" and 9/32" tips.

**2 PHILLIPS
SCREWDRIVERS:**

#1 and #2 sizes.

EXTENSION BLADE:

Adds 4" reach to
driving blades.

HANDLE:

Shockproof, breakproof. Exclusive, positive locking device holds blades firmly for turning, permits easy removal.



WRITE FOR
CATALOG 162



XCELITE, INC., 12 BANK ST., ORCHARD PARK, N. Y.
Canada: Charles W. Pointon, Ltd., Toronto, Ont.

Circle 21 on reader's service card

In the Shop . . . With Jack

By JACK DARR
SERVICE EDITOR

SIGNAL TRACING COLOR TV

THERE ARE A COUPLE OF COLOR TV circuits that we ought to get straightened out. It'll make things easier, when you run into color trouble—all colors or any one color that isn't what it ought to be.

Check the picture tube first, of course, and try new tubes in the demodulators and bandpass amplifiers. After that, if you've still got the same trouble, try signal tracing.

The signal to check comes from the bandpass amplifier and goes through the three demodulators to the picture-tube grids. Put a color-bar signal into the set and follow it with—you guessed it—a scope. Incidentally, a wide-band scope is not absolutely essential for this, though it's nice. You can use a narrow-band scope, but a low-capacitance probe is necessary. What you follow is practically an *audio* waveform. The 10 color bars are basically a waveform with a fundamental of about 160 kHz. (Each "bar" is a pulse at 157.5 kHz.)

Take the red signal, for instance. Look at it on the grid of the red (R-Y) amplifier (Fig. 1). This odd-looking pattern means that the red gun *conducts* whenever the peaks of the "bar" signal drop *below* the imaginary center line of the waveform. Each pip is one bar. On that basis, the third bar from the left should be the brightest—pure red. If you kill the

This column is for your service problems—TV, radio, audio or general and industrial electronics. We answer all questions individually by mail, free of charge, and the more interesting ones will be printed here.

If you're really stuck, write us. We'll do our best to help you. Don't forget to enclose a stamped, self-addressed envelope. Write: Service Editor, Radio-Electronics, 200 Park Ave. South, New York 10003.

blue and green guns, that's what you'd see.

You're on the grid, so the *negative* signal peaks make the tube's plate current drop and the plate voltage rise. You get a *positive* voltage peak on the plate. Since this is dc-coupled to the red CRT grid, it makes that gun conduct more, causing a *brighter* red bar.

The plate waveform should look exactly like the grid waveform but inverted (Fig. 2). Gain? Easy to check. First read the p-p amplitude of the *grid* signal. Then read the plate waveform the same way. The normal p-p amplitudes are usually on the schematic, but even if they aren't, you can tell from the *ratio* between the two.

In a Motorola 908 chassis, for instance, there's about 13 volts p-p on

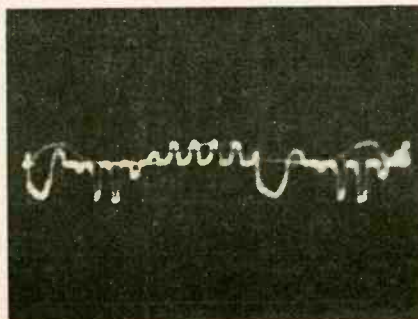


Fig. 1—Color-bar signal on R-Y grid. Each pip is one color generator bar.

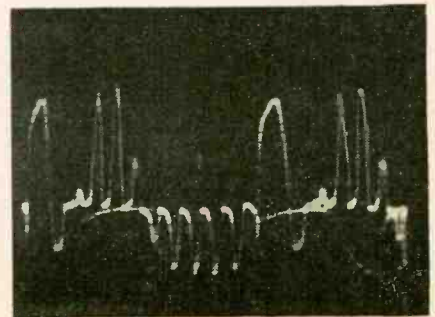


Fig. 2—Inverted plate waveform. Check gain by comparing with the grid signal.

Scott's new LR-88 receiver takes the



out of kit building

Building a kit used to be something you couldn't do with ladies and children present, but Scott's new LR-88 AM/FM stereo receiver kit has changed all that. First, there's the instruction manual. In clear and simple language, it leads you, step-by-step, through every stage of the assembly process. And each stage is illustrated . . . full-size, full-color. Next, there's Scott's ingenious new Kit-Pak®. The parts for each assembly stage are in individual compartments, keyed to the instructions. All wires are color-coded, and pre-cut and pre-stripped to the proper sizes. Difficult or critical sections are pre-wired, pre-aligned, pre-tested, and factory-mounted on printed circuit boards. Is soldering your bugaboo? Scott has provided push-on solderless connectors for the hard-to-get-at spots.

About thirty painless hours after you've started, you've completed one great receiver. The LR-88 is the 100-Watt kit brother to Scott's finest factory-wired beauties. It includes the famous Scott silverplated Field Effect Transistor front end, Integrated Circuit IF strip, all-silicon output circuitry . . . in fact, all the goodies that would cost you over a hundred dollars more if Scott did all the assembling. Performance? Just check the specs below . . . and you'll be amazed at how great a receiver sounds after you've built it yourself. Treat yourself to a weekend of fun and years of enjoyment . . . see the Scott LR-88 at your dealer's today.

LR-88 Control Features: Dual Bass and Treble; Loudness; Balance; Volume compensation; Tape monitor; Mono/stereo control; Noise filter; Interstation muting; Dual speaker switches; Stereo microphone inputs; Front panel headphone output; Input selector; Signal strength meter; Zero-center meter; Stereo threshold control; Remote speaker mono/stereo control; Tuning control; Stereo indicator light.

LR-88 Specifications: Music Power rating (IHF), 100 Watts @ 4 Ohms; Usable sensitivity, 2.0 μ V; Harmonic distortion, 0.6%; Frequency response, 15-25,000 Hz \pm 1.5 dB; Cross modulation rejection, 80 dB; Selectivity, 45 dB; Capture ratio, 2.5 dB; Signal/noise ratio, 65 dB; Price, \$334.95.

Circle 100 on reader's service card

You'll swear by it



SCOTT®

Write for complete information on the new Scott components and kits.

H.H. Scott, Inc., Dept. 570-10,
Maynard, Mass. 01754

Export: Scott International,
P.O. Box 277, Maynard, Mass. 01754

Walnut case optional extra © 1968, H.H. Scott, Inc.

color



The **RCA WT-509A** Picture Tube Tester is a precision instrument in the famous RCA tradition. It tests both color and black and white picture tubes for emission quality, interelectrode leakage, and shorted elements. It's all solid-state AND IT'S ONLY \$118.00.*



The **RCA WR-64B** Color-Bar/Dot/Crosshatch Generator has for years been the finest instrument of its type. Exceptionally stable, portable, it's a precision instrument designed for use in the laboratory and factory as well as for servicing on-the-bench and in-the-home. AND IT'S ONLY \$129.00.*



The **RCA WR-502A** "CHRO-BAR" color-bar generator has even more features than the famous WR-64B. It's all solid-state, battery operated. It provides color bars, dots, crosshatch, vertical lines, horizontal lines, blank raster. It has rock-solid stability. All new circuit design. THE "CHRO-BAR" IS ONLY \$168.00.*

*Optional Distributor resale price.

For a complete catalog of descriptions and specifications for all RCA test equipment see your RCA Test Equipment distributor or write RCA Electronic Components, Commercial Engineering, Department No. L-39WA, Harrison, N.J. 07029.

LOOK TO RCA FOR INSTRUMENTS TO TEST/MEASURE/VIEW/MONITOR/GENERATE

RCA


generate




The RCA WR-50B RF Signal Generator with sweep features is versatile, portable, and exceptionally well suited for alignment and signal tracing of AM, FM, hi-fi and citizen's band receivers and trouble-shooting in nearly all sections of TV receivers. IT'S ONLY \$65.00.* Also available in an easy to assemble kit, WR-50B(K).



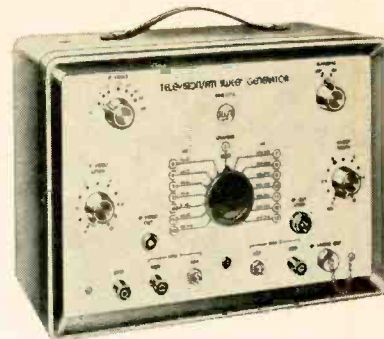The RCA WA-504A Transistorized Sine/Square Wave Audio Signal Generator covers a frequency range from 20 Hz to 200,000 Hz with exceptional frequency stability. For use in audio, hi-fi and general electronics applications, as well as in electronics training, demonstrations and lab work. ONLY \$95.00.*



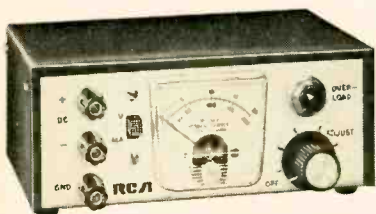The RCA WR-69A Television/FM Sweep Generator is designed for lab, service, and production applications for sweep-frequency alignment of color and black and white TV receivers and broadcast FM receivers. It's also used to align VHF tuners, picture-and-sound IF amplifiers, video amplifiers and chrominance circuitry in color TV receivers. AND IT'S ONLY \$295.00.*



The RCA WP-700A and WP-702A Power Supplies are extremely reliable, solid-state, constant voltage DC power supplies that provide 0 to 20 volts dc at current levels up to 200mA. WP-702A is actually identical to WP-700A, except it is a dual unit with two complete power supply sections. WP-700A IS ONLY \$40.00* in quantities over five, and WP-702A IS ONLY \$73.00* in quantities over five. Prices on less than five units are \$48.00* and \$87.00* respectively.



The RCA WR-70A RF/IF/VF Marker Adder is designed for use with conventional markers and sweep generators such as the RCA WR-39, WR-89 and WR-99 series calibrators and the WR-59 and WR-69 series sweep generators to produce clean, narrow markers on the sweep-response curve on an oscilloscope. AND IT'S ONLY \$96.00.*



The RCA WR-99A Crystal-Calibrated Marker Generator combines in one compact, accurate, and stable instrument the functions of a multiple-marker generator, crystal calibrator and a heterodyne frequency meter. Ideal for servicing and aligning color and black and white TV receivers, communications and other equipment in the frequency range of 19 to 260 MHz. ONLY \$256.50.*

*Optional Distributor resale price.



For a complete catalog of descriptions and specifications for all RCA test equipment see your RCA Test Equipment distributor or write RCA Electronic Components, Commercial Engineering, Department No. L-39WB, Harrison, N. J. 07029.

LOOK TO RCA FOR INSTRUMENTS TO TEST/MEASURE/VIEW/MONITOR/GENERATE



NEW DELTA DESIGN!

MODEL 3000 FET VOM

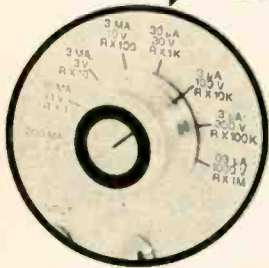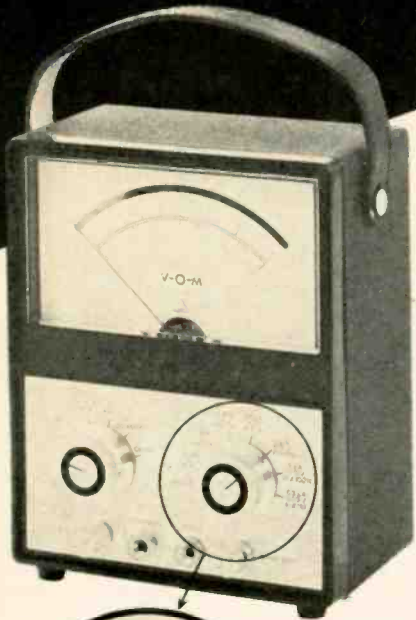

*A unique
and efficient
instrument
bridging the gap
between a
multimeter and a
digital voltmeter!*

Delta, pioneer of the famous Mark Ten® CD System, now offers a compact, versatile, and extremely sensitive VOM which combines FETs and ICs for extreme accuracy. Compact (6½" W x 8" H x 3½" D), portable, wt. 3¾ lbs. In full production at only

\$74.95
ppd.

Would you believe:

1. Mirror scale 200µ A D'Arsonval meter
2. Integrated circuit (IC) operational amplifier for extreme accuracy
3. FET input stage with current regulator
4. Two stage transistor current regulator and Zener diode on OHMS for absolute stability and accuracy
5. Voltage clippers for protection of input stage
6. Fully temperature compensated for low low zero drift
7. Ten turns ZERO and OHMS adjust potentiometers
8. Epoxy glass circuit boards and metal case
9. Enclosed switches
10. Uses readily available type AA cells
11. Uses standard test leads for maximum flexibility and ease of measurement
12. 10 Megohms input impedance

Available in Kit form:
Feedback network with pre-selected components to eliminate all final calibration. Ready to use when assembled!

Kit:
Only **\$59.95**
ppd.



DELTA PRODUCTS, INC.

P. O. Box 1147, Grand Junction, Colorado 81501

I enclose \$_____ Please send postpaid:

_____ Model 3000 FET VOMs @ \$74.95 assembled

_____ Model 3000 FET VOMs @ \$59.95 kit form

Name _____

Address _____

City/State _____ Zip _____

DP 8-7

the grid and 130 volts p-p on the plate, for a gain of 10. In a RCA CTC19, 10 volts grid, 100 volts plate, p-p, and so on.

The blue will show about the same gain as the red. The green, however, will show the lowest p-p voltages of them all—usually about half the voltage of the other two. The relationship between grid and plate waveforms are the same.

What does this tell you? Well, if you think one color is weak, check the p-p amplitude of the bar signals in and out of the amplifier stage for that color. In circuits which do not use the separate red-, green-, blue-amplifier tubes, check the demodulator stages.

Phasing of color and burst signals is supposed to be very difficult. Why? If the "high bar" isn't in the right place for any given plate, then the phasing is off. If the No. 3 bar on the red plate is not "on top" or the No. 7 bar is high, this shows you the trouble.

You can correct it by retuning the reactance coil or making whatever adjustment is recommended in the service data for the particular circuit, while watching the waveform on the plate. The PHASING control makes the high bar "walk" along the waveform. So does the TINT control.

Here's a handy tint control test. Set the control in the center of its rotation, and check any of the plates for proper positioning of the high bar. If it's off, retune the phasing just a wee bit until it's right. Then check to see that the tint control will walk the high bar back and forth along the waveform. Normal movement ought to be at least one bar on either side of the correct position.

The COLOR control will vary the amplitude of the bars. Make sure that it is set at the specified position before making any p-p voltage readings in this circuit. You can also tell whether the color control is working as it should—just move it and watch bar height.

There you have it. If you use the right equipment in the right way, and interpret your results correctly, it's just as easy to follow the signal through these stages as it is in an audio amplifier. More on other circuits in this section next month. R-E

COMING NEXT MONTH

In January, Service Editor Jack Darr looks at some peculiar problems caused by faulty bandpass amplifier and burst circuits. What happens to scope patterns and color bars with weak burst or sync? How do you check interaction between the horizontal hold control and color sync?

NEW

FINCO®

COLOR SPECTRUM™ ANTENNAS

are "signal customized"
for better color reception...



"the ANTENNA that captures the RAINBOW"

FINCO has developed the Color Spectrum Series of antennas — "Signal Customized" — to exactly fit the requirements of any given area.

There is a model scientifically designed and engineered for your area.

Check this chart for the FINCO "Signal Customized" Antenna best suited for your area.

STRENGTH OF UHF SIGNAL AT RECEIVING ANTENNA LOCATION	Strength of VHF Signal at Receiving Antenna Location						
	NO VHF	VHF SIGNAL STRONG	VHF SIGNAL MODERATE	VHF SIGNAL WEAK	VHF SIGNAL VERY WEAK		
NO UHF →→→		 CS-V3 \$11.50	 CS-V5 \$18.50	 CS-V7 \$25.95	 CS-V10 \$37.95	 CS-V15 \$50.95	 CS-V18 \$59.50
UHF SIGNAL STRONG →→→	 CS-U1 \$10.50	 CS-A1 \$19.95	 CS-B1 \$31.50	 CS-C1 \$45.95	 CS-C1 \$45.95		
UHF SIGNAL WEAK →→→	 CS-U2 \$15.95	 CS-A2 \$23.95	 CS-B2 \$41.95	 CS-C2 \$54.50	 CS-D3 \$73.50		
UHF SIGNAL VERY WEAK →→→	 CS-U3 \$22.95	 CS-A3 \$32.50	 CS-B3 \$52.50	 CS-C3 \$62.95	 CS-D3 \$73.50		



NOTE: In addition to the regular 300 ohm models (above), each model is available in a 75 ohm coaxial cable downlead where this type of installation is preferable. These models, designated "XCS", each come complete with a compact behind-the-set 75 ohm to 300 ohm balun-splitter to match the antenna system to the proper set terminals.

All Prices Subject to Change

THE FINNEY COMPANY

34 West Interstate Street • Dept. RE • Bedford, Ohio 44146

**“He’s a good worker.
I’d promote him
right now if he had
more education
in electronics.”**



Could they be talking about you?

You'll miss a lot of opportunities if you try to get along in the electronics industry without an advanced education. Many doors will be closed to you, and no amount of hard work will open them.

But you can build a rewarding career if you supplement your experience with specialized knowledge of one of the key areas of electronics. As a specialist, you will enjoy security, excellent pay, and the kind of future you want for yourself and your family.

Going back to school isn't easy for a man with a

full-time job and family obligations. But CREI Home Study Programs make it possible for you to get the additional education you need without attending classes. You study at home, at your own pace, on your own schedule. You study with the assurance that what you learn can be applied to the job immediately.

CREI Programs cover all important areas of electronics including communications, radar and sonar, even missile and spacecraft guidance. You're sure to find a program that fits your career objectives.



You're eligible for a CREI Program if you work in electronics and have a high school education. Our FREE book gives complete information. Airmail postpaid card for your copy. If card is detached, use coupon at right or write: CREI, Dept. 1412G, 3224 16th St., N.W. Washington, D.C. 20010.



**CREI, Home Study Division
McGraw-Hill Book Company
Dept. 1412G, 3224 Sixteenth Street, N.W.
Washington, D.C. 20010**

Please send me FREE book describing CREI Programs. I am employed in electronics and have a high school education.

NAME _____ AGE _____

ADDRESS _____

CITY _____ STATE _____ ZIP CODE _____

EMPLOYED BY _____

TYPE OF PRESENT WORK _____ G.I. BILL

- I am interested in Electronic Engineering Technology
 Space Electronics Nuclear Engineering Technology
 Industrial Electronics for Automation
 Computer Systems Technology

APPROVED FOR TRAINING UNDER NEW G.I. BILL

Computer Lingo—Today's

By **MATTHEW MANDL**
CONTRIBUTING EDITOR

DIGITAL COMPUTERS ARE BEING USED IN EVER-INCREASING numbers in business data processing, in industrial control and in scientific laboratories. They are vital to the military as well as for the guidance systems of space explorations. With this sharp upward trend in computer use, the demand for computer programmers is at an all-time high. Estimates state that over 500,000 people are already engaged in some form of computer programming or operation, and another 250,000 will be needed within the next few years. And this is only in the United States.

A programmer tells the computer of the particular problem or data to be processed, indicates the methods to be used and debugs faulty programs. He communicates with the computer by using the "language" the computer understands or a mathematically oriented or business-type "language," which is translated into the computer's basic language.


The binary code

Digital computer circuits operate in only two states: the diodes or transistors are either on or off. This assures accuracy and reliability because changes in transistor characteristics or other solid-state devices do not affect the two states unless the component shorts or opens. The two states represent digits 1 and 0—hence *digital* computer.

The use of only 0 and 1 requires a binary-type math with a base 2 instead of base 10, as in our ordinary numbering system. This binary code is the basic language of all digital computers. The following table shows binary numbers ranging in value up to 19:

Communicating with the computer via a Video Data Terminal, a Dodge claims supervisor in Philadelphia updates 50,000-mile warranty information in Chrysler's Detroit computer.

RCA

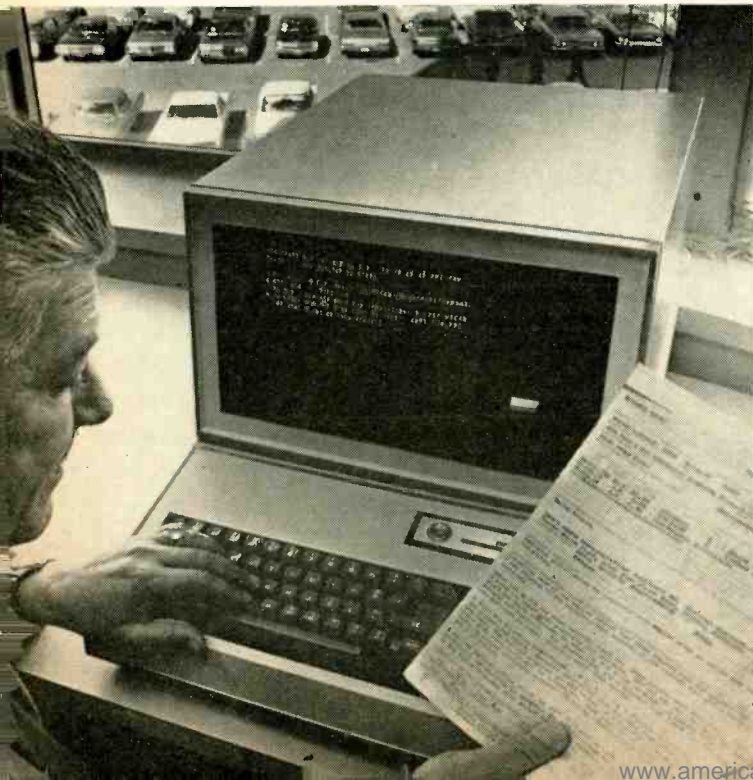

Base 10 Value	Binary Representation
0	00000
1	00001
2	00010
3	00011
4	00100
5	00101
6	00110
7	00111
8	01000
9	01001

Base 10 Value	Binary Representation
10	01010
11	01011
12	01100
13	01101
14	01110
15	01111
16	10000
17	10001
18	10010
19	10011

Note the pattern of the binary sequence. In the right-hand column (first place) the 0's and 1's alternate; in the second column from the right the 0's and 1's are paired, while in the third column from the right the sequence down the column is four 0's, four 1's, etc. Subsequent columns follow the same pattern related to the sequence 1, 2, 4, 8, 16, 32, 64, etc. Thus the fifth column from the right would have 16 0's, followed by 16 1's, etc. Knowing this principle enables you to expand the table easily.

The computer uses this binary code to identify storage locations, to identify instructions from the programmer regarding how to process data and to make computations directly. Programs consist of a sequence of instructions, each accompanied by a storage address or explanatory number. Thus, the binary numbers 000100 and 000101 might mean, "add to the accumulator the number in storage location 5." The first binary number, 000100, is the "add" instruction and the second number the address of the number to be added. Another set, such as 101010 and 001000 may indicate a shift command. Thus, the binary 101010 instructs the computer to shift a number right, while the binary 001000 indicates an 8-place number shift.

Octal code

Since the early days of digital computers, design engineers have strived to simplify the programming processes. Binary code becomes cumbersome when large numbers are involved, such as $101101 = 45$, and $1000110 = 70$. Thus, if 70 meant "subtract" we would have to convert it to its binary form. While there are various methods (including conversion tables) to find binary equivalents, much time is wasted. A simpler method is to group the binary digits into sets of three to form what is known as the *octal* code, as shown in the following examples:

$$\begin{aligned} 101\ 101 &= \text{octal } 55 \quad (\text{true value} = 45) \\ 001\ 110 &= \text{octal } 16 \quad (\text{true value} = 14) \\ 101\ 001\ 011 &= \text{octal } 513 \quad (\text{true value} = 331) \end{aligned}$$

Thus, all instructions and storage addresses can be in octal coding to expedite entries. Often the pushbuttons on the computer console are in groups of three to facilitate punching in numbers. If the computer binary address value of 331 is needed, you would be given octal 513 instead. By entering a binary 5, followed by a 1, and a 3, we have 101 001 011. The computer senses this as 101001011, which has the true value of 331.

New Machine Languages

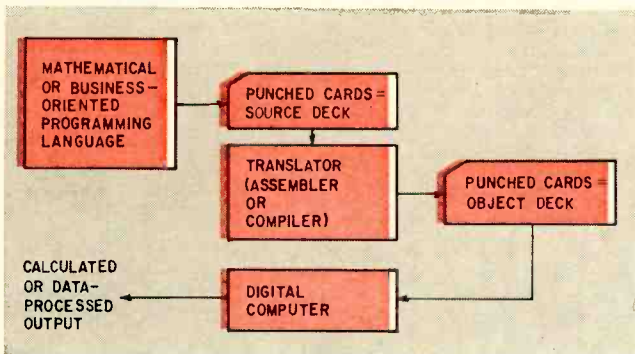


Fig. 1—Step sequence for translating mnemonic and SPS programs into binary language. Initial program is punched on cards or tape, which are read by compiler. The Computer then reads the object deck generated by the compiler.

Binary and octal codes permit us to enter programs at the computer console and examine numerical binary displays for checking the status of a program or process. It would be much more convenient, however, if we could do without the binary or octal numbers for the programming instructions.

Mnemonic or SPS language

We could save programming time if we could use the actual words *add*, *multiply* and *divide*, or abbreviations of them in our instructions to the computer. To do this we must use some sort of translating system to tell the computer that *add* means binary 100, and *shift* means binary 101010, etc. This is done by using capitalized abbreviations such as MPY for multiply, DIV for divide, etc. We could also use just A for add, S for subtract, M for multiply or D for divide. Such coding is also known as mnemonic (aid-to-memory) or SPS (symbolic program system). Thus, a simple program for adding of $5 + 3$ would be:

```

LDA 50 (Put the 5 into accumulator)
ADD 51 (Add 3 to accumulator contents)
STP 00 (Stop computation)
  
```

In this example, the 5 would have had to be placed into storage location 50 and the 3 into 51. Also, the entire program would have been stored within the computer's memory earlier. Once the data and program are loaded, the program initiating button is depressed and the program run. Thus, the addresses in which the program itself is stored must also be indicated, as shown in the following example, where a print-out instruction is also included:

Program		Data	
Address	Instruction	Address	Data
00	LDA	50	5 (Load 5)
01	ADD	51	3 (Add 3)
02	PRT		(Print answer)
03	STP		(Stop computation)

The translating of mnemonic and SPS programs into machine (binary) language is done by assembler programs, which also select storage locations automatically. The program is punched on cards or paper tape and fed into the assembler. Another deck of cards is automatically punched containing the binary-language equivalent,

and these cards are read by the computer. The initial stack of cards which contains the mnemonic program is called the *source deck*, and the resultant cards from the assembler program are called the *object deck*. These terms are also used for other language procedures, as shown in Fig. 1.

FORTRAN language

The word FORTRAN is an *acronym* formed by using the letters from the phrase: FORMULA TRANSLATOR. It is a mathematically oriented computer language that permits us to make math statements almost in the same form as the original equation. A special translator (called a *compiler*) selects appropriate storage locations and converts the FORTRAN into machine language to be processed by the computer.

Though programming math with FORTRAN is easier than with the mnemonic coding method (particularly for complex math equations), a number of rules must be observed. Among them are that all capital letters must be used, and that multiplication is expressed by an asterisk (*). Divide is shown by using the slash (/) and exponents are identified by a double asterisk (**). Thus, if we wanted to indicate the equation $(a - b)c^2$ it would appear as:

$$(A - B) * C ** 2$$

Similarly, the FORTRAN expression for the equation $y = \frac{(a + b)}{c}$ would be written as:

$$Y = (A + B) / C$$

Such statements are not, however, the complete program—but only the mathematical portion. The computer must be told what values (a, b, etc.) to read, in what manner, and what is to be printed out. The complete program would have the following:

```

READ 1, A, B, C
Y = (A+B)/C
PRINT 2, Y
STOP
1 FORMAT (3F10.4)
2 FORMAT (F12.4)
END
  
```

The READ statement tells the computer to read three variables (from cards or tape) designed as A, B and C, in the manner designed by a later FORMAT statement identified by the 1 preceding it. Thus, if we check with the FORMAT statement identified by the "1" we find that three variables are involved (the "3" in 3F10.4) and that the field width (F) is 10 characters, with four characters pointed off. The PRINT statement indicates the answer (Y) is to be printed out as identified by FORMAT 2. The latter states that 12 total characters are to be allocated, with four decimal places.

A compiler is used to translate, and the program (on the source deck) is translated into machine language on the object deck. As with the assembler, the object deck is fed into a card or tape reader and then into the computer for processing. In the FORTRAN program, STOP tells the computer when to stop computation, and END tells the compiler the program is finished.

Other statements are used in FORTRAN to permit the computer to undertake "decision" type operations, modify

the program as required and perform other manipulations. Program errors are sensed by the compiler and clues printed out so that the programmer can locate the errors or note the use of incorrect statements.

COBOL language

As with FORTRAN, the word COBOL is an acronym made up of the initial letters of the phrase: Common Business Oriented Language. Like FORTRAN, COBOL can be used with any computer if the proper compiler is used for translating it into machine language.

COBOL uses the English language directly and is made up of selected words to express the series of operations which the computer is to execute in business data processing. Hence, COBOL uses letters, numbers and punctuation marks to form descriptive or instructional sentences. However, COBOL must be written by following certain rules, just as our English language uses rules of grammar. Curiously, when a written COBOL program is examined by a nonprogrammer he can understand most of the commands and data descriptions, but could not write such a program without knowing the rules.

Verbs are used for instructional commands, and nouns for denoting the nature of the data to be processed. Capital letters are used, such as READ, WRITE, OPEN, CLOSE, DISPLAY, etc. for verbs. Nouns would include FILE, PAYROLL, INVENTORY, etc. The verbs ADD, SUBTRACT, MULTIPLY and DIVIDE can also be used, or as in FORTRAN,



IBM

Programs are constantly being developed to solve new problems.

signs such as "+", "-", "*", and "/" are valid.

COBOL programing consists of an identification division which describes the nature of the program—a configuration section, describing computer equipment to be used; a data division which identifies data sources, and a procedure division which spells out to the computer what processes are to be performed. A typical program section for the latter would appear as:

```
PROCEDURE DIVISION.
START. OPEN OUTPUT PAYROLL-FILE.
READ-IN. READ PAYROLL-FILE RECORD.
COMPUTE WITHHOLDING-TAX.
```

Hyphens and periods must be used according to COBOL rules and can't be changed arbitrarily.

Program language

The newer PL/I language was introduced early in 1966 by IBM and is intended to be a universal-type computer language. It retains some of the basic features of both FORTRAN and COBOL and can handle either mathematical or data-processing programs. A compiler, suitable

for PL/I must, of course, be used for translating this language into machine language.

In PL/I statements are written on a single line as in FORTRAN, and parenthesis are used (not brackets). Thus, $Y = a + b/a - b$ becomes:

$$Y = (A + B)/(A - B);$$

Note that a semicolon is used to indicate statement end instead of the period. As with COBOL, verbs and nouns are used to indicate instructions or descriptions. For example:

```
DECLARE (COST, PRICE, DISCOUNT);
COST = PRICE - DISCOUNT;
```

These two statements tell the computer that we are "declaring" that the program concerns cost, price and discount rates. Then we tell the computer that it determines cost by subtracting the discount from the price. Actually you could declare any name you wish and the computer will reserve a storage area for it and act accordingly when the same word is used again later in the program. Thus, you could even declare PHILODENDRON or OSHKOSH and the computer will accept them on your say-so and process them as you wish!

Also, in PL/I the programmer may insert any comments he wishes into a program and can specify that such comments are not to be acted on by the computer, but are just for the programmers information. He does this by using the symbols "/*" before the comment and ending it with "*/". Thus, anything stated within these "/*" and "*/" signs are ignored by the computer.

Other languages

The most widely used computer programing languages today are FORTRAN and COBOL. PL/I is making some inroads, but is still too new to be universally accepted or used. In certain specialized areas, however, other programing languages are used. ALGOL (algebraic-oriented language) has been popular in Europe and also used to some extent in America. FORTRAN IV, however, incorporates some aspects of ALGOL and is, of course, also a mathematically oriented computer language. Others are MAD (Michigan Algorithm Decoder) and JOVIAL (Jule's Own Version of International Algebraic Language). All have specific rules and the written program must follow them to be valid.

A mathematical programmer does not have to solve an equation (the computer does this) but he should know how to set it up in the *algorithm* (format) most suitable to computer processing. Similarly, a data-processing programmer doesn't have to know accounting, but a fundamental knowledge of business operations and basic book-keeping is certainly helpful.

Where can you learn programing? At trade schools (advertised in this magazine): at technical schools, community colleges, business colleges, and many other institutions of learning. Leading computer companies also offer courses and often give aptitude tests in logic to determine your ability and leanings toward this interesting and lucrative profession.

Numerous textbooks are available from various publishers on all aspects of programing. Many such books are of the "programed" type, which are intended for self-instruction. (Actual exposure to the operating principles of a computer is, of course, extremely helpful.) If you like checkers or chess as well as other games of logic, you might be a natural! **R-E**

See page 89 for a list of schools offering courses in computer technology and programing.



Stereo Headset Control Center

*Easy-to-build battery-powered transistor circuit costs about \$10.
Just feed in a 0.1-volt stereo signal*

By **WAYNE LEMONS**


EVER TRY TO FIND A SIMPLE, INEXPENSIVE, HIGH-fidelity, stereo headphone amplifier circuit? It isn't easy. Stabilizing diodes, specially matched transistors, unusual parts and exotic feedback circuits may be nice to have, but they aren't always needed.

It was with economy (around \$10) and simplicity in mind that this circuit was evolved. It uses

no unnecessary parts (unless you think tone and volume controls are unnecessary). The transistors are inexpensive (about 40¢ each), and there are no transformers.

It works with either low- or high-impedance phones about equally well. The frequency response is slightly better with low-impedance phones, but your ears will have to be pure gold to tell the difference.

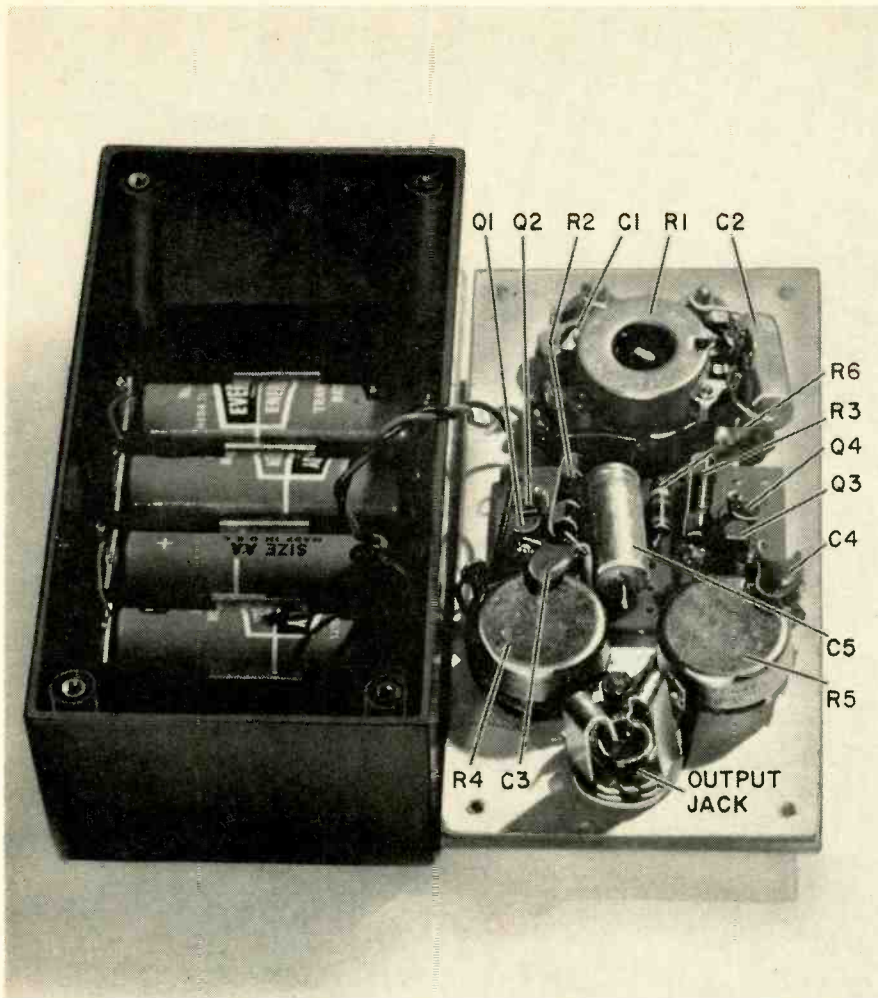Current drain is low, and lower still if the vol-



Front panel of the headphone amplifier was made from 1/8"-thick colored plastic. Lettering was placed on white cardboard, which is beneath the plastic. Flat sides of transistors face each other for one channel, away for the other as shown in Fig. 2.

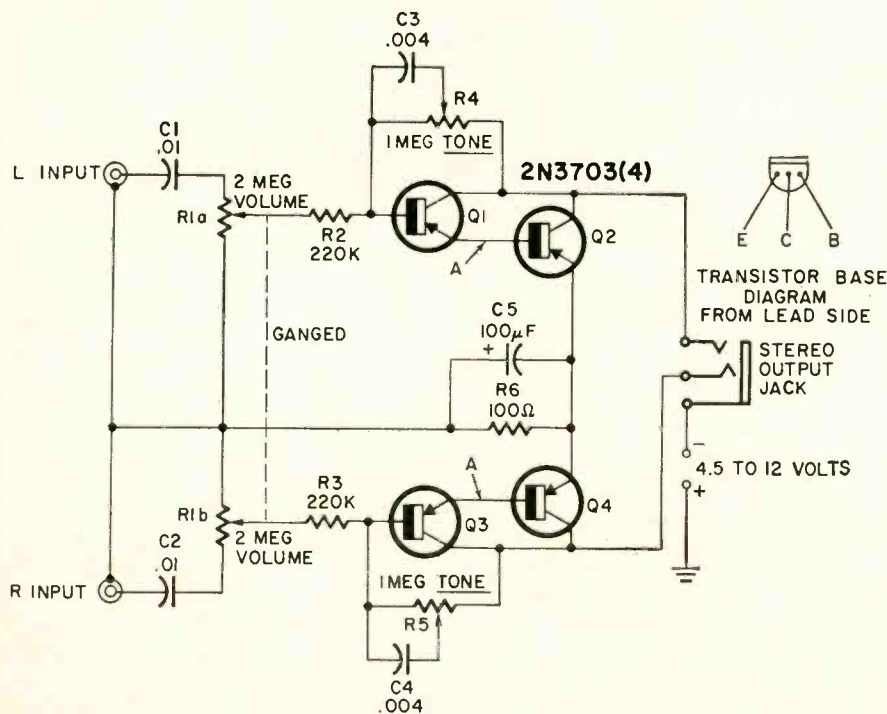


Fig. 1—Emitters of input transistors Q1 and Q3 are direct-coupled to the output transistors. Collector voltage is fed through the earphones. The setting of the tone controls determines both the amount and frequency of inverse corrective feedback.

ume control is not turned up full. Even at full volume a set of penlight cells will last 200 hours or more.

There's no on-off switch because unplugging the phones automatically disconnects the battery. Ganged volume controls are used, but they could have been separate. Individual tone controls are used, but they could have been ganged.

A 0.1-volt input produces ample headphone volume. Input may be up to about 0.5 volt at full volume before noticeable distortion occurs. For higher input voltages, turn down the volume control to remove any overload distortion in the circuit.

The 220,000-ohm base resistors prevent the bias from going to zero when the volume is turned all the way down. Depending on its position, the volume control varies the bias. This permits the circuit to draw less current at low volume and still operate with very good fidelity.

A single resistor (R6) bypassed by a 100- μ f capacitor (C5) provides protective bias for all four transistors.

PARTS LIST

- C1, C2—0.01- μ F, 400V capacitor
- C3, C4—0.004- μ F, 50V capacitor
- C5—100- μ F electrolytic capacitor, 3V or more
- R1a, R1b—ganged 2-meg-ohm linear potentiometer
- R2, R3—220,000-ohm, 1/4-watt resistor
- R4, R5—1-megohm linear potentiometer
- Q1, Q2, Q3, Q4—2N3703 silicon transistor or equivalent
- MISC—2 1/2" x 5" x 1 1/2" Bakelite utility box and cover, jacks, knobs, perforated board

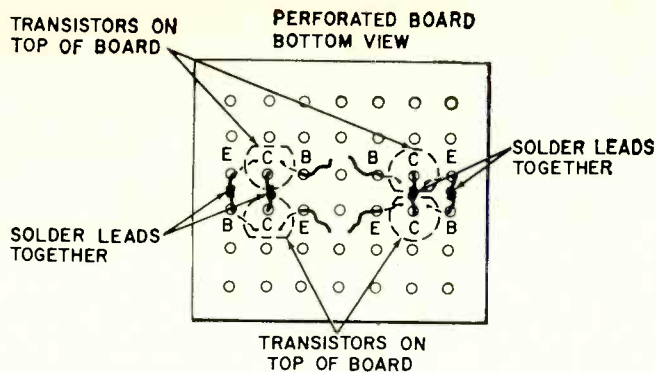


Fig. 2—Transistors are mounted directly on perforated board and the leads soldered together. Parts layout is not critical. The board used is $1\frac{3}{8}$ " x 2". A PC board can be made even smaller.

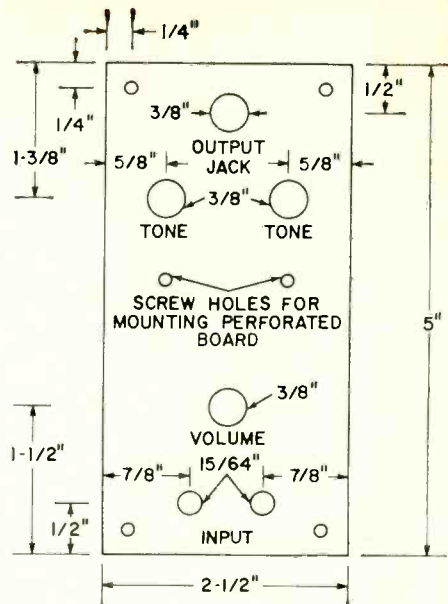


Fig. 3—Panel layout of amplifier. An ac/dc power supply can be installed.

Amplifier gain is ample for all cartridges except low-output phono types. It is an ideal amplifier for turntables with ceramic cartridges or for use with a stereo FM tuner.

Incidentally, you can use npn silicon transistors by simply reversing the battery connections. Germanium transistors will not work without modifying the circuit. Many germanium transistors will work if you will add a 1000-ohm resistor from point A in the schematic to ground.

How it works

The two amplifiers are identical, so consider only the operation of the left channel in Fig. 1. Signal is coupled into the base circuit through C1, the 0.01- μ f isolation capacitor. A 2-megohm volume control adjusts the input level to the 220,000-ohm base resistor. Transistors connected this way have a fairly high input impedance, so large input resistances can be used.

Transistor Q1's emitter is direct-coupled to the base of transistor Q2. Collectors of both transistors are tied together. Bias for the circuit is supplied through the 1-megohm tone control. The 220,000-ohm base resistor and the lower part of the volume control act as a bleeder on the bias voltage.

When the volume control is turned all the way down, R2 is grounded and bias is reduced. As the volume control is turned up, bias on Q1 increases, causing it and transistor Q2 to draw more current.

Collector voltage is fed through the earphones from the battery. The connection of the bias resistor to the collector also results in some inverse feedback. The amount of feedback and its frequency is de-

pendent on the tone control setting.

With the tone control adjusted so that C3 is at the collector end, there is maximum feedback of high frequencies. This in turn, because of the inverse feedback, reduces the amplifier gain at high frequencies and appears to improve bass response.

When the tone control is adjusted with C3 at the base end, feedback is essentially the same for all frequencies. The inverse feedback tends to provide a "leveling" action on higher-frequency signals, which are enhanced by earphone inductance so that response is essentially flat when C3 is at the base end of the control.


Construction hints

A perforated board can be used to mount the transistors (see Fig. 2). Other parts are also mounted on the board except those that can be mounted elsewhere more conveniently. Figure 3 shows dimensions of the front panel. Layout is not critical and a different arrangement can be chosen if desired. For example, by using a printed circuit and miniature controls, this amplifier could be built into a very small area.

If you want to go "electric," use any filtered 6–10-volt dc power supply with an output current of 12 mA or more. Figure 4 shows a simple supply you can build yourself, but any of the small power supplies designed for transistor radios will work. By rearranging parts you could install the power supply in the amplifier box.

Any way you do it, you'll be pleased with the performance and stability of this unpretentious little amplifier. **R-E**

Fig. 4—A power supply can be used with the amplifier. Batteries last about 200 hrs.

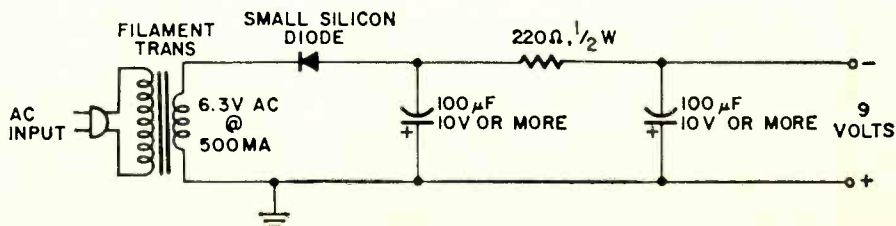

**BUILD FOR
YOUR CAR**

50-Watt Portable AC Outlet

By Jack Jaques Technical Manager
HEP Motorola Inc., Phoenix, Arizona

HERE'S AN INEXPENSIVE, EFFICIENT, convenient, compact source of 115-Vac, 60-Hz power from your car, camper or motorboat 12-Vdc battery. It offers an opportunity to eliminate the inconvenience of battery, propane and gasoline lights in boat, camp or camper. The 50-watt rating is ample to operate the HEP Guitar Amplifier (see RADIO ELECTRONICS, November 1968, p. 37) and other utilities such as a small TV set, portable hi-fi, soldering iron, electric shaver, lights, radio, etc. For example a 25-watt light, a 14-watt fan and a 3-watt radio can be used simultaneously without exceeding the 50-watt rating. Thus, by using this inverter and the battery in your vehicle, "boondock" or beach-party singouts are a lot more fun.


A pair of power transistors operated as a magnetically coupled

multivibrator are the heart of this device (Fig. 1). Transformer T1 provides the coupling. It is a standard 24-volt, 2-amp, center-tapped filament transformer. However, it is modified by adding another center-tapped secondary winding on the periphery of the existing wire bundle. The new winding consists of 12 turns of No. 22 plastic-covered hookup wire. The space between the frame and the existing wire bundle permits installing the new winding (Fig. 2).

The added winding forms the base circuit of transistors Q1 and Q2. The 12-Vdc input from the auto or boat electrical system is applied via TS1 to the secondary center taps of the transformer. The original secondary winding forms the collector circuit of Q1 and Q2. Its center tap provides the negative or return circuit to TS1, and the

dc supply. Resistor R1 establishes the turn-on bias voltage for Q1 and Q2. The value of R1 (180 ohms) assures that the transistors will begin oscillating (alternately turning on and off) under all conditions. R2 and C1-C2 set the frequency of oscillation, approximately 60 Hz. Diode D1 prevents unwanted voltage spikes from appearing at the bases of Q1 and Q2.

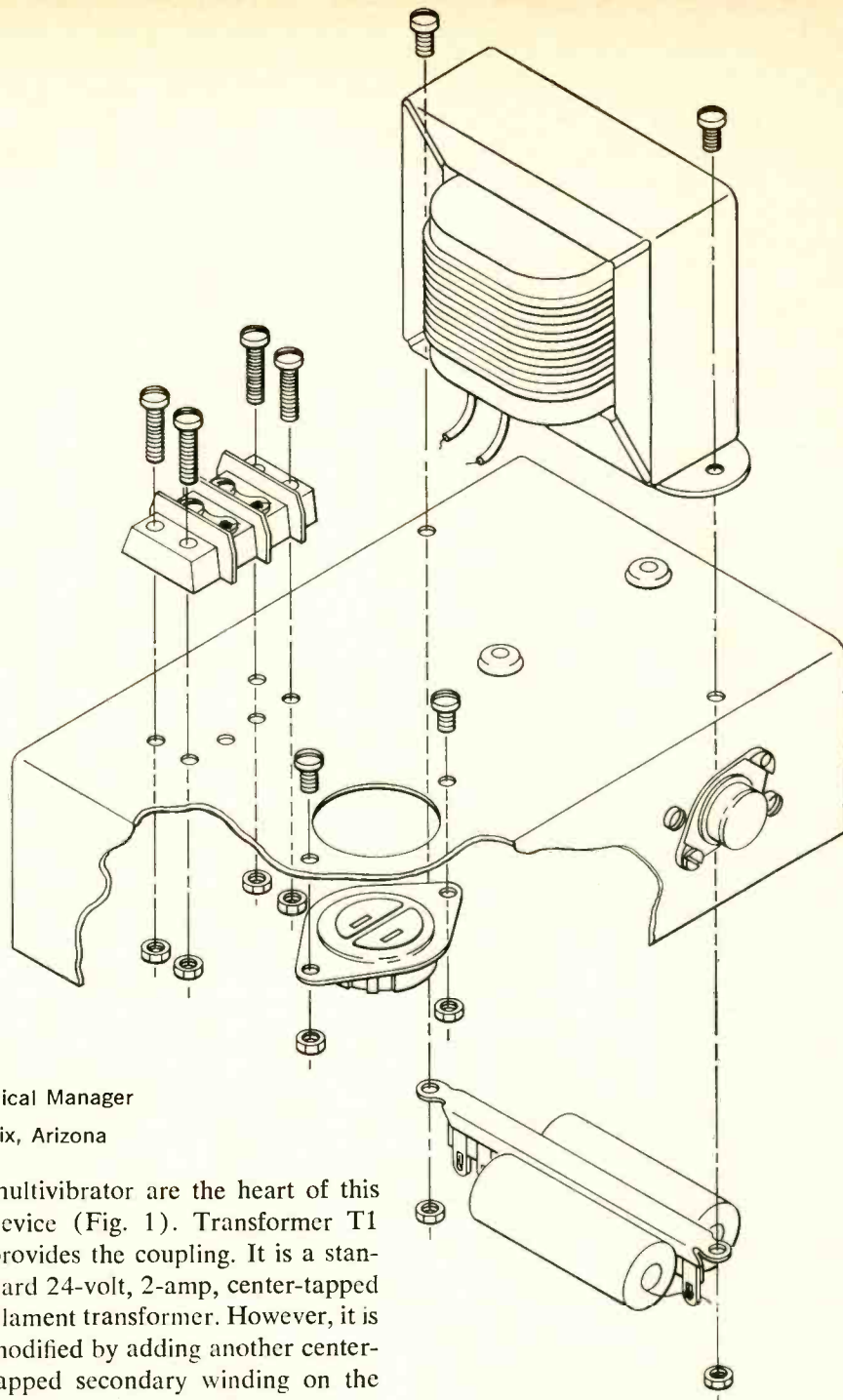When voltage is applied to T1's new 12-turn secondary, Q1 and Q2 turn on and off (oscillate) in an alternate sequence. As each



transistor conducts, current flows alternately between the extremes and the center tap of the original T1 secondary, first in one half, then in the other. This conduction causes a magnetic field to build up in the alternate halves of the winding, which collapses when the current flow ceases due to transistor turnoff. This alternating buildup and collapse of the magnetic field in the secondary causes an alternating



voltage to be induced across T1's original primary. The ratio of the number of turns in the two windings is chosen so that the transferred output is stepped up to 115 volts. The 115 volts, which is still at the same frequency as the oscillating input circuit (60 Hz), is delivered to output connector J1, where it is available for operation of the amplifier, lights or other low-wattage appliances as desired.

Using the inverter

Operating the inverter is extremely simple. There are no controls. Just connect TS-1 to a source of 12-volt dc. Then plug the 115-Vac appliance into J1.

CAUTION

Correct polarity of the 12-Vdc input must be maintained. The inverter cannot be used in a car with the positive post of the battery connected to the body (ground). Check foreign cars in particular if the cigarette lighter adapter is used.

A cable with a plug that mates with the cigarette lighter receptacle is available and is recommended as one convenient way to connect the unit to the dc source. Be sure the auto battery is in good condition. Do not overload the inverter with appliances requiring more than 50 watts of power. Do not use excessively long power cords since this added resistance will reduce the power available for operating appliances. **R-E**

CAUTION

Do not attach the inverter directly to the auto body. For rigid mounting to the auto, use insulating sleeves and isolate the inverter chassis with a mat of foam rubber $\frac{3}{16}$ " thick.

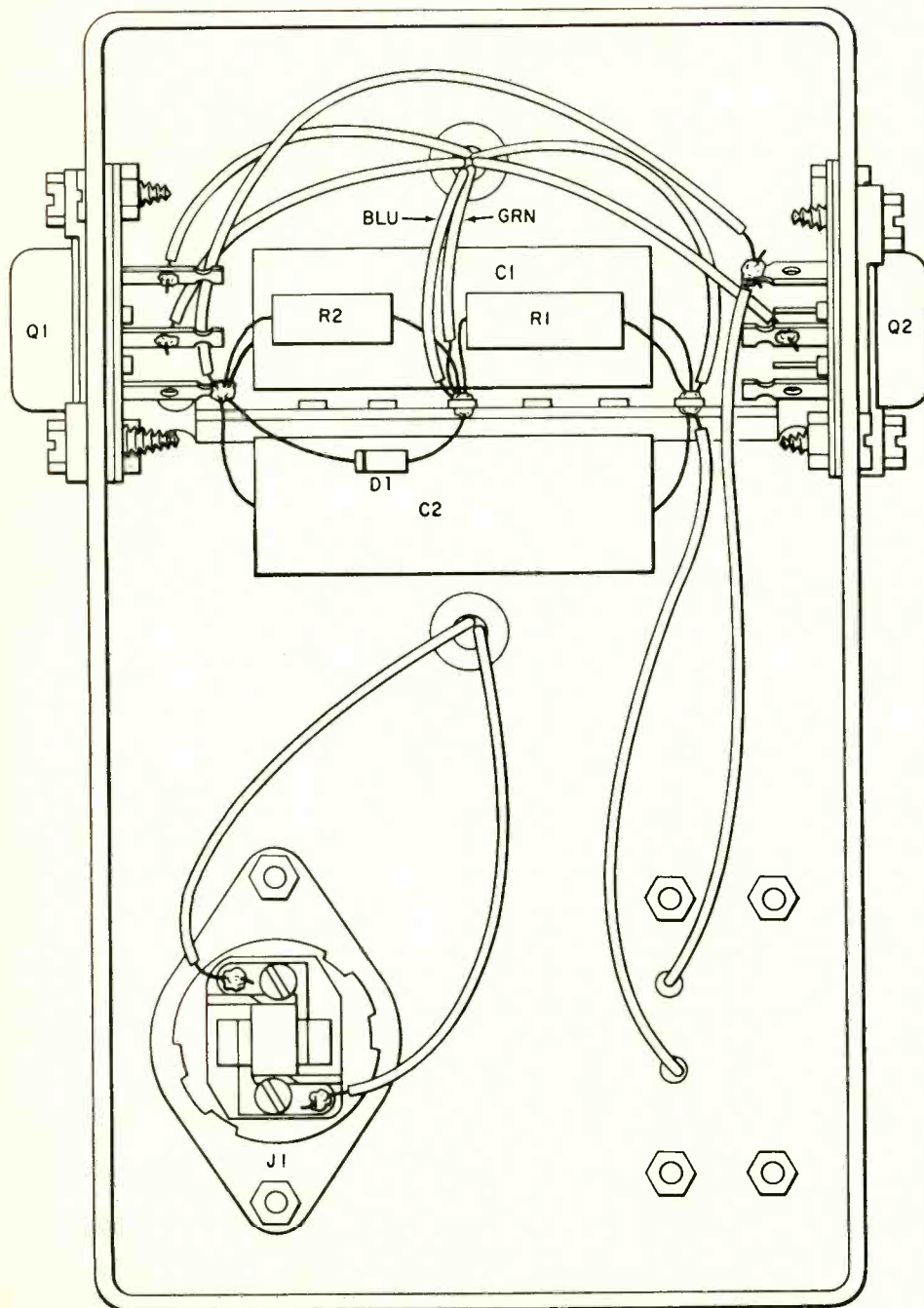


Fig. 3—Pictorial diagram shows what's going on under the chassis. Note details of parts placement and connecting lead layout. Follow this arrangement as closely as possible and you should have no difficulty in building this unit.

It's Easy To Fix Solid-State TV

The circuits may be different but they do tend to be simpler

By **MATTHEW MANDL**
CONTRIBUTING EDITOR

TRANSISTOR TVS ARE NOT FAILURE-proof. They operate at lower voltages than tube types, but component ratings are correspondingly lower, and failures do occur. We still run into sweep faults, mistuned circuitry and an occasional transistor failure.

Often, when low-gain transistors are used, extra stages are needed to get maximum performance. As a result, additional trouble possibilities exist. So we still have average run-of-the-mill faults, some troublesome intermittents and even the occasional multiple-trouble conditions of tube TV. Basic circuit knowledge always expedites servicing, as the following case histories emphatically indicate.

An even half-dozen

A good example of visual multiple troubles is shown in Fig. 1. Here, five faults are easily recognized. At the upper right we have corner shadow, at the center screen we have ghosts, at the left we have dark vertical bars, throughout the screen we have adjacent-channel interference (changing diagonal line segments) and poor focus. When the brightness control was turned up, the picture bloomed, making a total of a half-dozen faults at once.

Even though six faults are in evidence, circuit knowledge would indicate only two defective areas are contributing to the symptoms. The ghosts and dark vertical bars could be antenna troubles, as could the adjacent-channel interference lines. The blooming, focus and corner shadows could be caused by troubles in the high-voltage system.

A high-voltage check showed only 15 kV at the second anode of the pix tube, instead of the 20 kV specified for this Zenith 1Y21B55 receiver. Using a scope and working back toward the horizontal oscillator we tried to localize the bad stage.

The horizontal sweep system for this set is shown in Fig. 2. Note how much simpler these transistor circuits



Fig. 1—Five faults show up in this TV picture. They include corner shadow, ghosts, dark vertical bars, adjacent-channel interference and poor focus. A sixth problem, blooming, became apparent when the brightness was turned up. A simple repair?

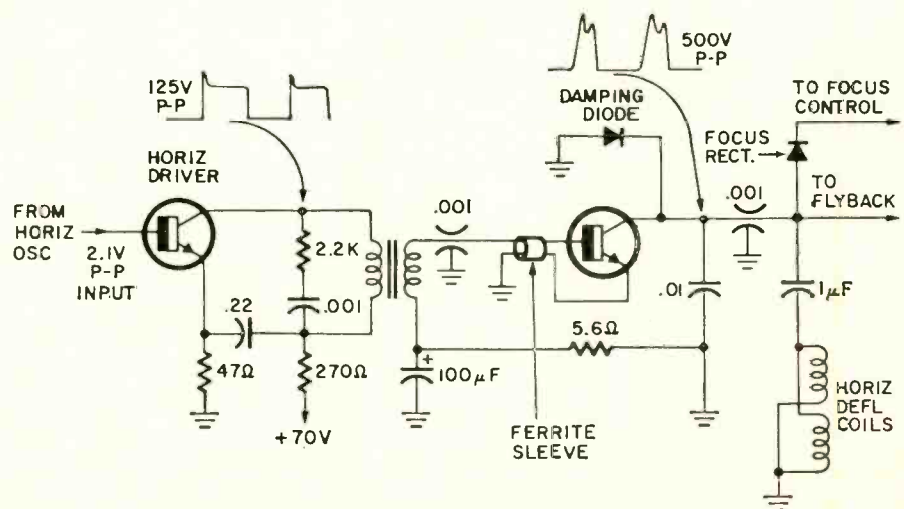


Fig. 2—Horizontal sweep system used in the Zenith 1Y21B55 chassis. A new transistor restored normal high voltage and focus voltage, eliminating the blooming and corner shadow. Interference lines, bars and ghosts remained; their cause not yet known.

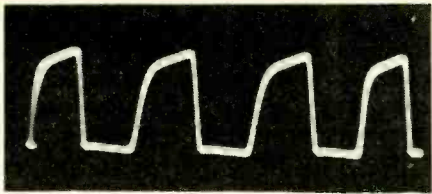


Fig. 3—A distorted horizontal-driver scope trace pinpointed the bad stage.

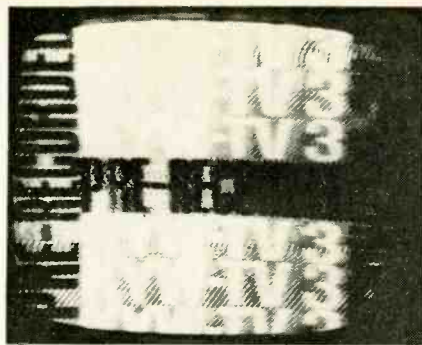


Fig. 4—Agc and focus troubles in an Admiral 2H5 resulted in distorted picture.

are than tube types. Because of the output transistor's low output impedance no transformer is needed between it and the deflection coils. Both the damping and focus rectifier diodes connect directly to the output transistor's collector.

To develop enough drive, however, a horizontal driver stage follows the horizontal oscillator. Note the ferrite sleeve around both the base and emitter leads of the output transistor. It is an inductive-type shield for stabilizing sweep function.

The scope pattern at the collector of the output transistor was some 100 V below normal. While this might indicate a defective transistor, before changing it, the scope was attached to the collector of the driver transistor. Here, the waveform was not only low in amplitude but differed from the normal waveshape. Distortion appeared at the flat-top section (see Fig. 3). A check at the horizontal driver input base, however, showed normal drive signals (2.1 V peak-to-

peak). Thus, the trouble was localized to the driver stage.

Resistors and capacitors were checked and found good, but an in-circuit check of the transistor showed poor emitter-collector conduction and reduced gain. A new transistor returned normal high voltage and focus voltage and eliminated the blooming and corner shadow. The interference lines, left vertical bars and ghosts were still there.

A check of the antenna system revealed that the antenna did not turn when the antenna-rotator control-box bar was depressed. The trouble was a defective 80- μ F ac type capacitor in the control box. (Always check this item first before deciding that the rotator motor is defective.)

Now, with the antenna free to rotate, the ghosts and vertical left bars disappeared. Remaining, however, were the wiggling adjacent-channel interference lines, though only on channel 10. A slight readjustment of the lower adjacent-channel trap

(47.25 MHz) eliminated this interference.

An Admiral 2H5 receiver had the symptoms shown in Fig. 4. While the general appearance is similar to Fig. 1, the trouble indications are not all the same. Again, some interference lines are present as is some defocusing. The overly dark areas indicate video signal overload, possibly agc troubles. If so, this could also contribute to the poor focus.

Adjusting the agc control had no effect. Voltage readings were taken at the age gate circuit shown in Fig. 5 next. Base and collector voltages were ok, but the emitter voltage was several volts above normal. A component check in the emitter circuit showed, not only an open 0.47- μ F bypass capacitor, but a increased-value resistor. Instead of 220 ohms, it read several thousand ohms. Such a large change in resistance in a low-voltage, low-current circuit is not common. It is more likely for a resistor worked near its wattage rating continuously to develop such a change.

New components in the agc circuit cleared up most of the trouble. In this receiver there are three terminal settings for focus—A, B and C. Changing from B to C improved focus. With normal age function and no video overload, the faint interfering lines also disappeared.

In the early production runs for this receiver, some parasitic oscillations would occur on occasion when component values in the third video i.f. amplifier were off far enough to affect critical circuit operation. Later production receivers incorporated a 100-pF capacitor across the 1000-ohm base resistor shown in Fig. 6. When servicing such sets, this capacitor should be added, even though no symptoms of picture instability or cut-off appear.

Intermittent sound and sync

In a Magnavox T921 9" portable, both sound and sync were intermittent. The sound would fade for a few seconds, then return for several minutes. Both vertical and horizontal sync would be lost for several minutes, then return to normal for a half-hour or more.

In this receiver a sync amplifier and phase splitter npn transistor follows the sync separator, as shown in Fig. 7. The sync amplifier feeds the horizontal phase detector diodes (connected across emitter and collector). The vertical oscillator is fed from the collector. All voltages and components checked ok in both the sync separator and the amplifier, as did the transistors with an in-circuit tester.


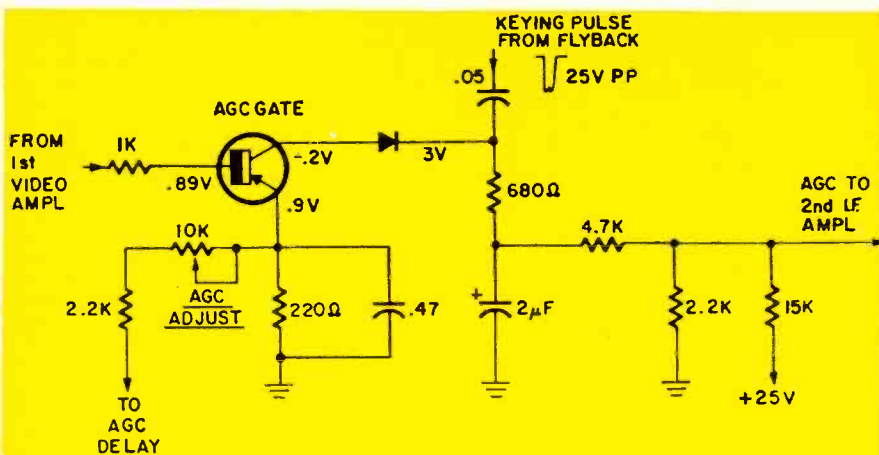


Fig. 5—Open bypass capacitor plus a higher-than-normal value resistor had to be replaced for normal circuit operation.

Fig. 6—Early models of the Admiral 2H5 did not include the 100-pF capacitor. If you service one of these sets, add one.

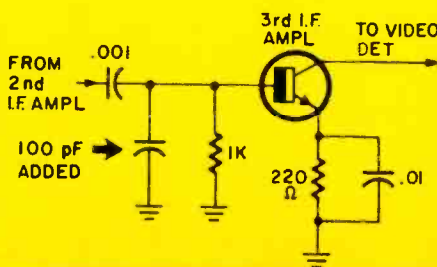

ABC's of Transistors

Here's how they work

TRANSISTORS HAVE PUZZLED TECHNICIANS FOR NEARLY A decade and there appears to be no sign of easing the strain. Each year more transistorized equipment is introduced in both television and hi-fi equipment. To keep up to date we must learn efficient transistor servicing procedures.

Many articles have been devoted to transistor troubleshooting and all of them have leaned heavily on theory. But many successful technicians working on vacuum-tube circuits do not have a solid foundation in vacuum-tube theory, so perhaps the solid-state troubleshooter does not necessarily need theory. Let's look at transistors from a troubleshooter's standpoint and minimize the theory.

For those of you with experience with tubes here is a comparison of transistors and tubes: A transistor is somewhat like a tube: Corresponding elements are:

Tube—Transistor
Cathode—Emitter
Grid—Base
Plate—Collector

There are two important differences:

1. The tube is a voltage amplifier.
2. The transistor is a current amplifier.

The grid of a tube usually has an opposite potential to the cathode and plate of a tube, but the transistor base potential is between the emitter and collector potentials.

Just two diodes

Transistors are further complicated as there are two types which operate with opposite bias and supply voltage polarities.

Yet it is easy to determine proper polarities for bias and supply voltages and what voltages we can expect in standard circuit configurations for each type.

The two basic types are, of course, pnp and npn. Physical and electrical characteristics of pnp and npn transistors are shown in Fig. 1. Both transistors are shown electrically as two diodes wired back to back. In the pnp type the cathodes are tied together; in the npn type the anodes are connected. The junction represents the base connection with the emitter or collector at either end.

Two common symbols for both pnp and npn transistors are in Fig. 2. Note that the arrows in both the diodes and the transistor symbol point in the same direction. Remember this and you cannot go wrong.

Normal circuit parameters

In conventional circuits a small forward bias, normally 0.2 to 0.7 volt, is applied to the emitter junction. An easy way to remember which polarity is required to forward-bias a junction is to note that, when a negative voltage is applied to an n-element and a positive voltage to a p-element of a pn junction, it is forward-biased. This is shown in Fig. 3. The letters tell you the crystal type in each element. That is, pnp stands for p-type (crystal) emitter, n-type base and p-type collector. Npn stands for n-type emitter, p-type base and n-type collector.

In other words, for a forward-biased emitter junction, a pnp transistor requires a negative voltage on the base with respect to the emitter. To forward-bias an npn transistor emitter junction a positive voltage on the base, with respect to the emitter, is required.

The collector circuit, on the other hand, requires a back-bias or reverse bias. So in a pnp transistor, a negative voltage

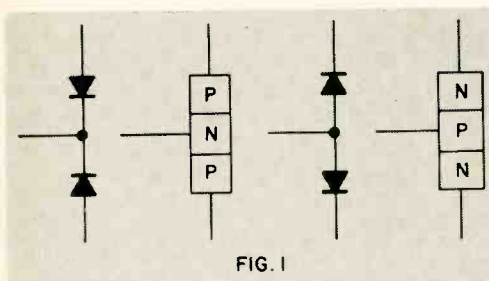


FIG. 1

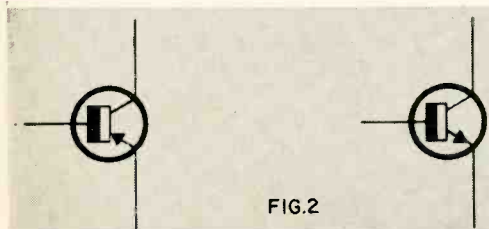


FIG. 2

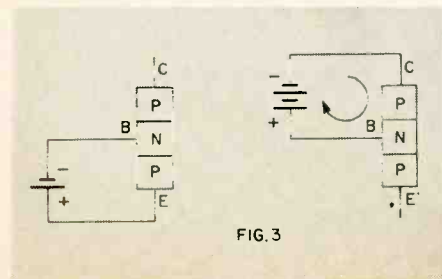


FIG. 3

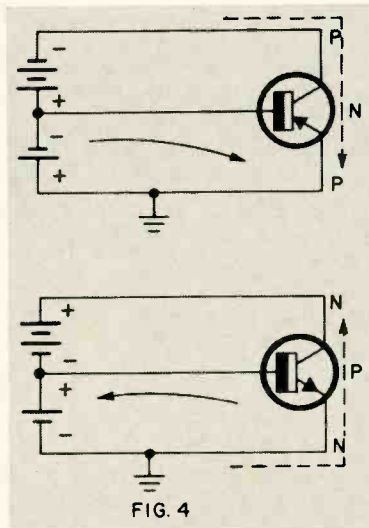


FIG. 4

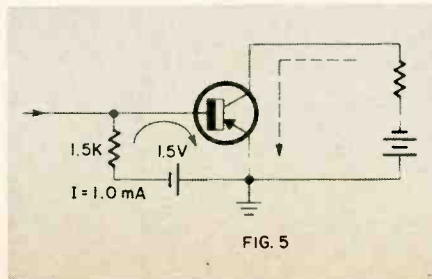


FIG. 5

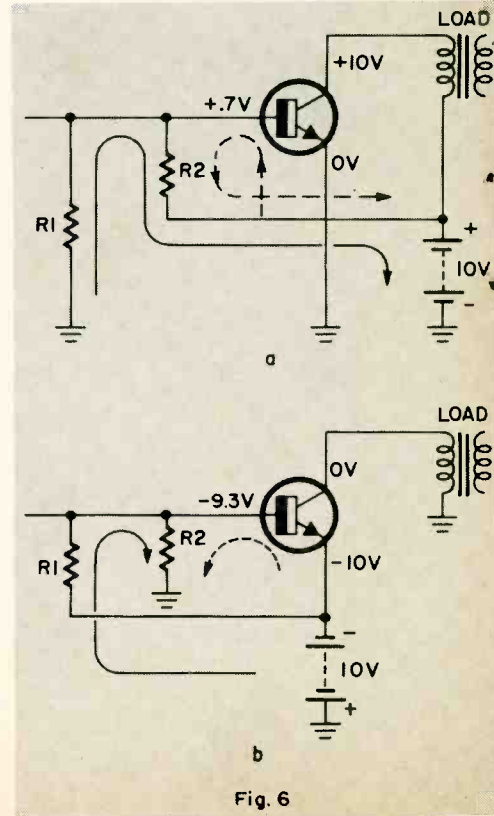


Fig. 6

is required on the collector with respect to the base and the opposite for an npn transistor. Circuits with these typical configurations are shown in Fig. 4. Note that the bias batteries are connected so they aid one another.

The need for biasing

Biasing is used in transistor circuits for the same reason that it is used in tube circuits—to set up a static operating point. Without proper bias, what was intended to be a class-A amplifier might operate class-B.

The simplest bias is accomplished with a single-resistor network. A common-emitter amplifier with a single bias resistor is shown in Fig. 5. Since the emitter-junction resistance is quite low, the base bias current can be calculated by dividing the bias voltage by base bias resistor. The base resistance is ignored because it is very small compared to the base bias resistor.

In Fig. 6-a, the negative terminal of the power supply is grounded. In Fig. 6-b, the positive terminal of the power supply is grounded. Each circuit's operation is identical. The resistors form a voltage divider network and selection of various values can result in any voltage between the supply and zero volts to appear at the base of the transistor. If there is a 0.7-volt difference between base and emitter, the transistor is turned on and emitter/collector current flows. If this voltage difference is reduced, less collector/emitter current flows. Conversely if this voltage difference is increased, collector/emitter current increases.

In Fig. 6-a, if a 10-volt supply is used, R2 will be approximately 9 times as large as R1 and +0.7-volt appears at the base. In Fig. 6-b, the values of R1 and R2 stay the same, but their relative positions are reversed to effect a +9.3-volt potential on the base. Either way, the base is +0.7-volt with respect to the emitter. The voltages shown are typical for a silicon transistor. Note that the base voltage is closest to the emitter voltage and between collector-emitter voltage.


An important consideration is the polarity and magnitude of voltage that must be applied to the base/emitter junction to turn the transistor "on" and cause electron flow between emitter and collector. While a tube requires bias voltage to reduce electron flow, the transistor requires bias current to cause electrons to flow. A tube with zero bias between grid and cathode generally has heavy current flow while a transistor

with zero bias between base and emitter is shut off and no current flows between collector and emitter.


To forward-bias or "turn on" a transistor, a small voltage is applied between the base and emitter elements. When measured from the emitter, the polarity of this bias voltage is the same as the collector voltage but its value is much lower.

Remember, as the voltage on the base element changes in the direction of the collector potential, the emitter/collector current increases. If the voltage on the base element moves in the direction of the emitter potential, the emitter/collector current decreases. This is true regardless of whether the transistor is silicon or germanium and npn or pnp.


In Fig. 7, resistor R3 is in series with the emitter. It stabilizes collector current and is referred to as a stabilizing resistor. As collector current flows through emitter resistor R3, a voltage is developed which opposes the forward-bias voltage. The effect of R3 is to oppose any change in current flow since the voltage across it is in series with the forward-bias voltage. For example, if collector current increases, the voltage drop across R3 increases and reduces the effective forward bias which, in turn, reduces collector current.

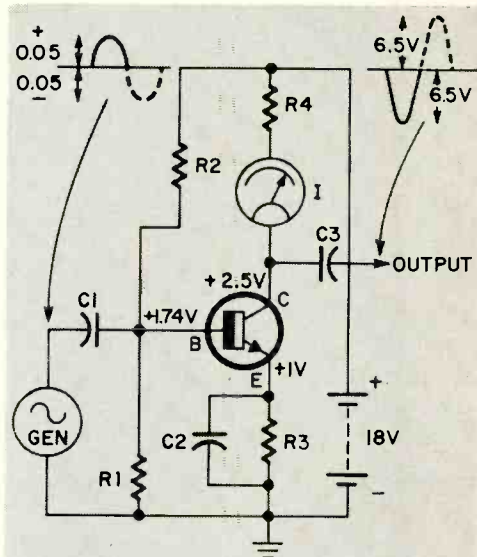

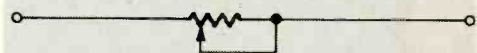
INSTANTANEOUS BIAS +0.74V
COLLECTOR I MAX
VOLTAGE ACROSS TRANSISTOR LOW
TRANSISTOR IMPEDANCE LOW



EQUIVALENT Z OF TRANSISTOR

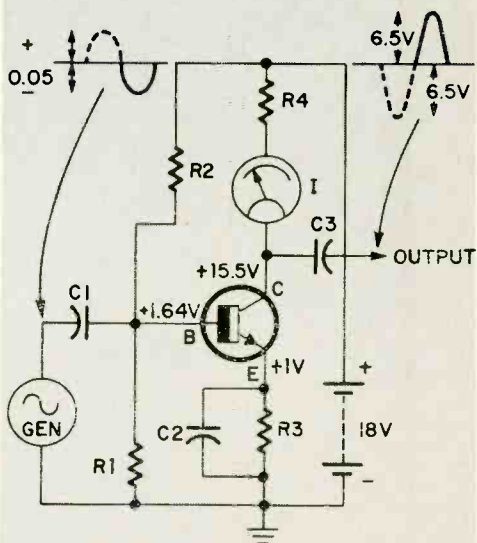

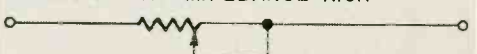INSTANTANEOUS BIAS +0.64V
COLLECTOR I MAX
VOLTAGE ACROSS TRANSISTOR HIGH
TRANSISTOR IMPEDANCE HIGH



EQUIVALENT Z OF TRANSISTOR

FIG. 9

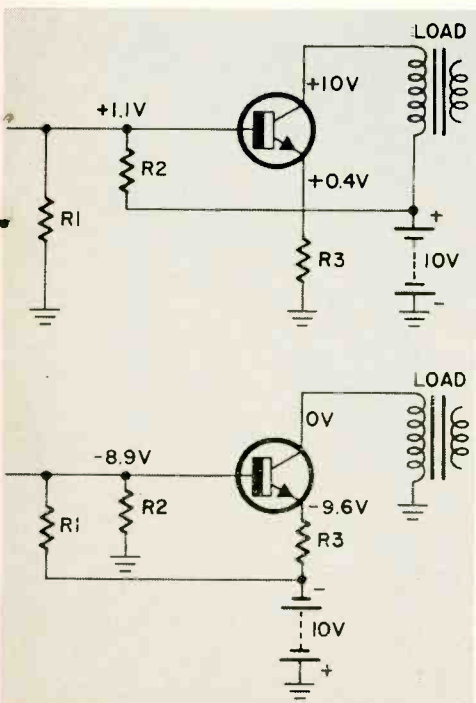


FIG. 7

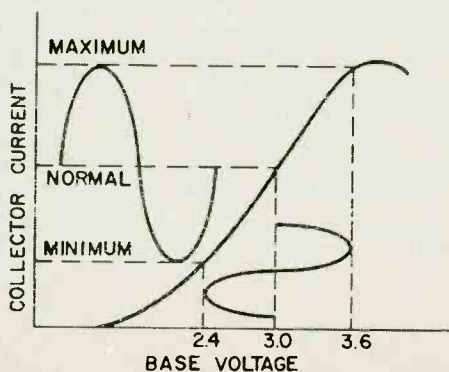
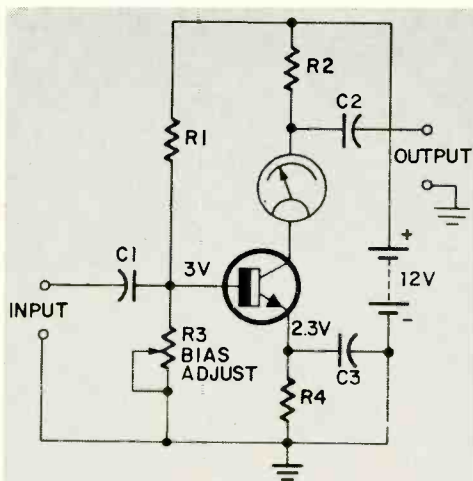


FIG. 8

Conversely, if collector current decreases, less voltage is developed across R3 and the effective forward bias increases. This, in turn, increases collector current. Adding an emitter resistor stabilizes a transistor with respect to collector-current variations which occur for a variety of reasons. The most common cause is an increase in collector current as a result of temperature increase.

When troubleshooting, the voltage drop across the emitter resistor is an important test point for checking circuit operation. A higher than normal emitter voltage generally indicates excessive collector current. This can be caused by a shorted transistor or a bias defect. A lower than normal emitter resistor voltage would indicate an open transistor or bias defect.

Class-A amplifier

A transistor stage set up for class-A or linear operation is shown in Fig. 8. In this stage, bias resistor R3 is shown as an adjustable unit, so some desired collector current will flow. This control can be used to show how the transistor amplifies the input signal.

The base voltage-collector current curve in Fig. 8 shows the collector current for several bias voltages. The horizontal line shows bias voltages developed across bias resistor R3. The vertical line shows values of collector current for each value of bias and we will neglect the effect of emitter resistor R4.

Note the mark on the bottom line indicating 2.4 V. This actually means 0.1 V between the base and emitter since the emitter is at +2.3 V. This mark corresponds with a line on the vertical column marked "minimum" as indicated by the dotted lines. This means that, with 0.1 V forward bias, only a small amount of collector current will flow.

If R3 is adjusted to make the base voltage become 3 V (0.7 V between base and emitter), the collector current increases. Referring again to the curve, we see that the collector current has increased to the mark on the vertical column marked "normal".

If R3 is adjusted to make the base voltage become +3.6 V (1.3 between base and emitter), there will be an increase in collector current. The collector current has increased to the "maximum" level.

From this we can see that by varying the base voltage, we can produce any desired value of collector current. In practice, the emitter voltage would not remain constant with different values of collector current. This action is similar to cathode-voltage variation in a tube.

An ac signal fed to the base element can also cause collector-current changes. Referring again to Fig. 8, we adjust R3 to make the base voltage become +3 V. This causes a collector current that corresponds to "normal" on the curve. The collector current through R2 causes a voltage drop so about half the supply voltage appears at the collector. These are the necessary conditions for a linear stage (amplification without distortion).

An ac generator supplies a signal between the base of the transistor and chassis ground in Fig. 9. This signal at any instant will add or subtract from the dc bias supplied by bias resistors R1 and R2. Capacitor C2 provides an ac bypass across R3 at the signal frequency.

In Fig. 9-a the generator is passing through its maximum positive excursion and is producing a peak +0.05 V. This voltage will add to the +1.69 Vdc bias voltage and cause a total in-

stantaneous voltage between base and ground of +1.74 V. From the curve in Fig. 8, we see that this corresponds to maximum current through the transistor. This is indicated by the current meter connected in series with the collector of the transistor.

The increased current through R4 causes a larger voltage drop, so that for an instant the collector voltage drops to approximately 2.5.

The result of the negative half-cycle of the generator is shown in Fig. 9-b. This negative 0.05-V excursion subtracts from the 1.69-V bias, so that for an instant the voltage between base and ground is 1.64 V. The curve in Fig. 8 shows that this corresponds to minimum collector current. The reduced current causes a smaller voltage drop across R4 and allows the collector voltage to rise to approximately +15.5.

From this we can see that an input signal of 0.1 V peak-to-peak can cause a collector or output signal of 13 V peak-to-peak. Also, phase inversion occurs. The dc and ac voltage excursions shown demonstrate amplification of the transistor. Capacitor C2 is large enough to bypass R3, so that no ac signal is lost across this resistor. The voltage at the emitter will reflect any average current change through the transistor. Emitter voltage is a good indicator of transistor conduction. If this voltage is too high, the transistor current is too high. If it is low, the current is too low.

Diode stabilization

Some amplifiers require a different type of bias stabilization since their primary purpose is to increase power. The circuits discussed are designed to maintain constant current. This would defeat the purpose of the push-pull amplifier, so another method is used.

The most common stabilization method used for these amplifiers is to use bias elements which are temperature-sensitive. One method, shown in Fig. 10, is to use a diode made from the same material as the transistor.



The diode is fed with a constant current through R1. The voltage drop across the diode biases the transistor and is inversely proportional to its temperature. In other words, as the temperature of the transistor and diode increases, the resistance of the diode decreases and the voltage drop across the diode decreases lowering the bias voltage the necessary amount.

Push-pull stabilization

Thermistors are frequently used to stabilize push-pull output stages. Thermistors have a negative temperature coefficient of resistance. A circuit using a thermistor for bias stabilization is shown in Fig. 11. The current through the thermistor is held relatively constant by the high series resistance. The voltage drop across the thermistor supplies the actual transistor bias. Since the compensation in this circuit is often greater than desired, a parallel resistor is sometimes added to the circuit to decrease its sensitivity.

Note that the purpose of the temperature sensing element is, not to compensate for ambient temperature, but to compensate for the junction temperature of the transistor. Consequently, whether the sensing element is a diode or a thermistor it should be located intimately with the transistor or transistors that it controls.

R-E

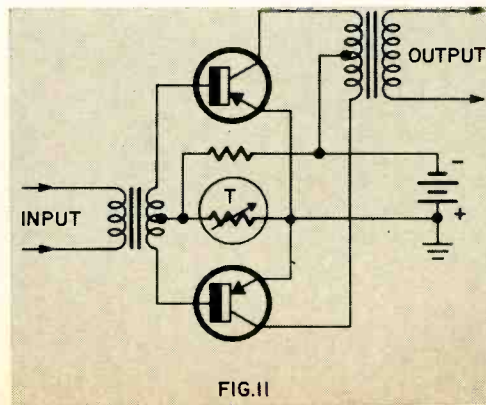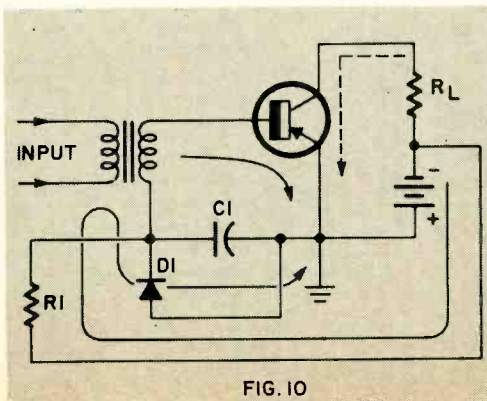

Build—Stereo Tape/Slide Controller

Solid-state control module lets you program stereo slide shows. Inaudible signals change slides automatically

By **EARL T. HANSEN**

WHY NOT RELAX WHILE YOU'RE showing slides? Let your tape machine provide stereo background music, narrate the show and change the slides.

You can do this by linking your tape playback equipment and automatic slide projector together with this controller.

An inaudible signal on the tape actuates the controller, but does not interfere with recorded audio. Using readily available components—including 5 inexpensive transistors—the controller can be built for about \$20. It has a high input impedance and relatively low output impedance.

A low-level 15-kHz signal is added to one channel during initial recording of the tape program. During playback, a notch filter in the controller attenuates this control signal.

Circuit operation

First let's look at the **PLAYBACK CONTROL** mode selected by switch S1 (Fig. 1). Program and control signals from the tape preamplifier enter the control module at J1.

Low frequencies are passed through R1 to Q1, which has a voltage gain of about 1. High frequencies, including the control signal, pass through R2 and C2 for a higher gain in Q1.

The 15-kHz control signal is routed through C3 and C4 to T1. The control signal *does not* appear at the output (J2) because it is rejected by the parallel-tuned trap, C5 and L1, and low-pass filter R7-C6. The low-pass filter also compensates for pre-emphasis added by R2 and C2.

As a result, this part of the circuit passes the program through unchanged, while amplifying and rerouting the control signal. The control signal is fed through double-tuned transformer T1, which rejects all other frequencies. The T1 secondary feeds emitter follower Q2, which drives sensitivity control R13.

Transistor Q3 amplifies the control signal and drives a peak-to-peak rectifier (C12-D1-D2-C13). When voltage on C13 is great enough to cause base current in the Q4-Q5 Darlington pair, they conduct and energize relay RY1. Resistor R17 dis-

charges C13 when the control signal has stopped. Since C13 is a relatively large capacitor and requires some time to charge, it provides excellent noise immunity and prevents unwanted relay operation from speech consonants or music harmonics. The delay is from 0.1 to 0.5 sec, depending on the setting of sensitivity control R13.

In the **RECORD COMMAND** mode, Q1 has a flat frequency response from input to output. The high-frequency pre-emphasis network (R2 and C2) is opened and the rejection filter (L1-C5-R7-C6) bypassed. The function of Q2 is changed to a Hartley oscillator, which is inoperative until the emitter current path is completed by pressing S2.

When S2 is pressed the oscillation frequency is determined by the resonance of T1, normally 15 kHz to 17 kHz. Part of this signal is fed from the secondary tap, through S1-c, R6 and R5 to the base of Q1, where it is added to the program material. The signal from Q2 is also fed through the sensitivity adjustment, R13, and the relay amplifier to actuate the relay.

Construction

An aluminum box is used for construction. Mount the large components on the sides and front. Secure T1 with self-tapping screws in the side of the can. Remove the coil assembly before drilling the pilot holes.

A perforated circuit board and push-through terminals were used for mounting most small components. The relay specified needs an insulated mounting and should be put on the perforated board.

Test and adjustment

Adjustment is much easier with an audio oscillator and ac vtvm. A scope and dc vtvm are essential.

Apply power and check the dc voltages shown on the schematic. Measure them with no signal in and S1 to playback. A 20% variation is acceptable. Collector voltages on Q1 and Q3 can fall between 5 and 12 volts with no loss of performance.


Next, apply a 1-kHz audio signal to the input and check the gain at the output. There should be approximately a gain of 1, which is controlled by the

ratio of resistor R1 to R3.

Now select a control-signal frequency. This is nominally 15 kHz, but may be higher if your tape machine has excellent high-frequency response and you want the highest possible point for the playback rejection filter. It should be lower if the tape machine has poor high-frequency response.

Set the audio oscillator to the control frequency and feed approximately 1 volt to the input, J1. With the switch set to playback, connect a scope or ac vtvm to the output and adjust L1 for minimum output. The output should be 10% or less of the input amplitude (20 dB down).

Reduce the input to 50 mV (140

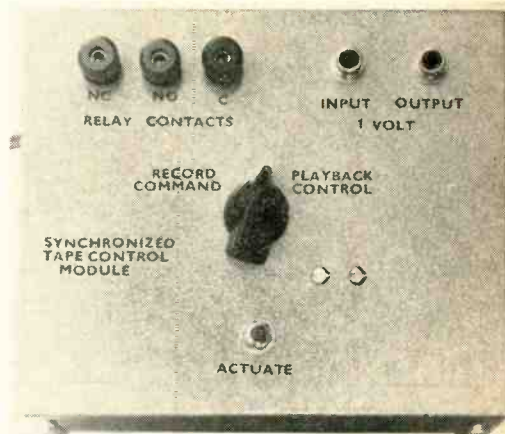

Controller has 1-volt input and output. Unit will work with monophonic recorder.

mV p-p), and connect the scope or ac vtvm to the emitter of Q2. Adjust both T1 slugs for maximum indication. This signal should be at least 50% greater than the input signal amplitude. Adjust sensitivity control R13 so the relay just closes.

Remove the audio oscillator and connect the scope or ac vtvm to the output. Press the **ACTUATE** button and adjust R6 for an output signal of 100 mV rms (240 mV p-p). This puts the control signal 20 dB below a program signal of 1 volt, as recorded, and the rejection filter gives an additional 20 dB attenuation during playback.

If an audio oscillator is not available, set the adjustment of R6, L1 and T1 about mid-range. Set S1 to the **RECORD** mode, and connect the output

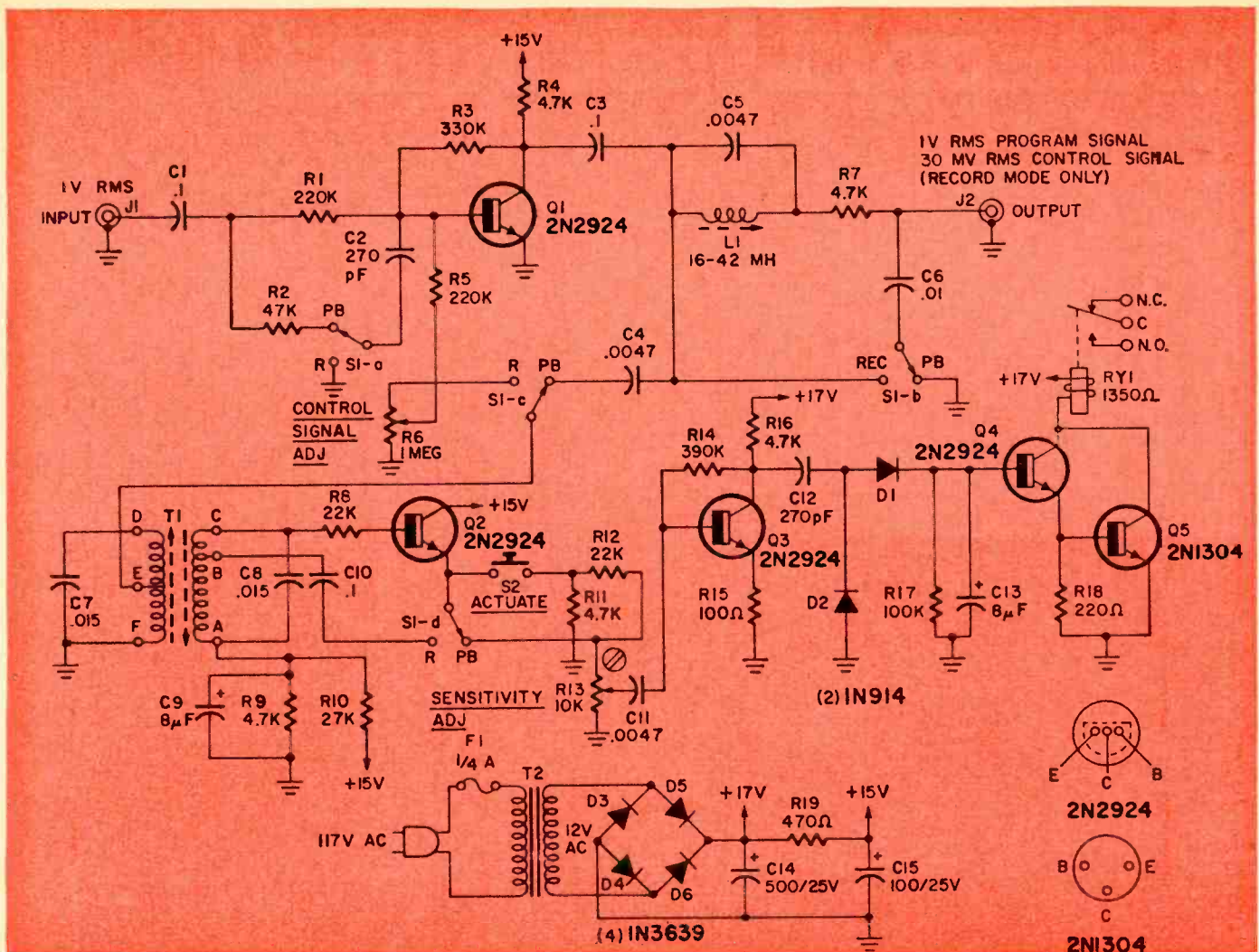


Fig. 1—Control signals are filtered from the output (J2) by parallel-tuned trap C5-L1, but amplified and routed to T1, tuned to the selected control frequency. Voltage on C13 triggers Darlington pair Q4-Q5, which energizes relay RY1 and advances slide changer or, with an extra unit, automatically shuts off the system. Q2 generates the command signal when S1 is in RECORD mode.

PARTS LIST

All capacitors 100-V paper unless noted

- C1, C3, C10—0.1- μ F
- C2, C12—270-pF, mica or ceramic
- C6—0.01- μ F
- C7, C8—0.015- μ F
- C9, C13—8- μ F, 6-V electrolytic
- C14—500- μ F, 25-V electrolytic
- C15—100- μ F, 25-V electrolytic
- All resistors $\frac{1}{2}$ -watt 10% unless noted
- R1, R5—220,000 ohms
- R2—47,000 ohms
- R3—330,000 ohms
- R4, R7, R9, R11, R16—4700 ohms

- R6—1-megohm linear potentiometer (Mallory MTC or equal)
- R8, R12—22,000 ohms
- R10—27,000 ohms
- R13—10,000 ohm linear potentiometer (Mallory MTC or equal)
- R14—390,000 ohms
- R15—100 ohms
- R17—100,000 ohms
- R18—220 ohms
- R19—470 ohms
- Q1, Q2, Q3, Q4—2N2924 transistor
- Q5—2N1304 transistor
- D1, D2—1N914 silicon diode
- D3, D4, D5, D6—1N3639 silicon rectifier

- T1—double-tuned 15-kHz transformer (Miller 6194 or equal)
- T2—12.6-V, 0.1-amp or more, filament transformer
- L1—16-42-mH adjustable inductor (Miller 6210 or equal)
- RY1—spdt, 12-15-V, 1350-2000-ohm relay (Potter Brumfield PB R 55D or equal)
- S1—4-pole, 2-position rotary switch (Centralab 1011 or equal)
- S2—spst normally open push-button switch
- Misc.—4" x 5" x 6" aluminum box, Vector type G board and T-28 terminals, RCA-type audio panel jack, hardware, ac power cord, binding posts, wire.

to your tape recorder.

Press the ACTUATE button and record several minutes of the control signal at a relatively low level. (Most tape machines will not record a 15-kHz signal at the normal record level and, therefore, frequency response runs are usually made at from 15 to 25 dB below the normal record level.)

When this recorded control signal is played back, it will be a control-signal source to make the above adjustments. You may skip the gain check using the 1-kHz signal, if the other tests look good.

Using your controller

The controller is designed for use with a tape playback deck that has a 1-volt output and an external amplifier. For playback control use, the controller is connected between one tape output channel and the amplifier.

It may be left connected at all times even though its control function is not being used. Set the switch to the RECORD COMMAND mode, and frequency response will be flat beyond 100 kHz.

If you do not have a separate

tape deck and amplifier, the controller may be connected to your all-in-one tape machine. Connect the controller in the path of the signal feeding the volume control, as shown in Fig. 2. If the same volume control is used for recording and playback, the controller will operate in both modes without changing connections.

In preparing a slide sound program I've found it easiest to record the music and commentary on a master tape, disregarding the controller. Then I borrow a second tape machine and play the master tape

through the controller to make a tape copy, adding the slide-change command signal as I go.

In the RECORD COMMAND mode, the relay is operated by the ACTUATE button as the control signal is added to the program. If the projector is connected and loaded with slides it affords a good chance to rehearse the program and keep track of the slide sequence as commands are recorded.

In the PLAYBACK CONTROL mode, it may be necessary to readjust the sensitivity control for your particular equipment. If it is set too high it will operate from "print through" from the adjacent tape. If set too low, operation will be erratic.

When recording the command signal, the recording level indicator should indicate a level about midway or less from the normal record level, even though the signal is about 20 dB down. The relatively high indication is caused by the high-frequency pre-emphasis in all tape recording equipment.

Automatic shutoff

When not being used as a slide controller, I have found the unit very useful as an automatic shutoff for all equipment at the end of a tape. This requires an extra box containing a holding relay, outlet and on button (Fig. 3).

Record the command signal at the end of each tape. The normally closed contacts are used for this function. When the signal occurs at the end of the tape, the relay opens and the ac hold relay turns the system off.


To disable the controller, operate it in the RECORD COMMAND mode. It will not affect your tapes or record anything unless your recorder is in the record mode. With a stereo system, either channel may be used for the command signal, but you should be consistent to avoid confusion. The controller can monitor only one channel at a time.

The controller inverts signal polarity 180°. If you feel phasing is critical, reverse the speaker leads on the controller channel.

Although designed for 1-volt input and output, the controller will accept signals up to 4 volts rms without distortion or clipping. Signals as low as 50 mV rms may be used without noticeable internal noise from the controller, which is down 68 dB from the 1-volt level.

When connecting the controller to your projector, locate the two leads to the regular remote pushbutton and extend these to connect to the normally open contacts on the controller.

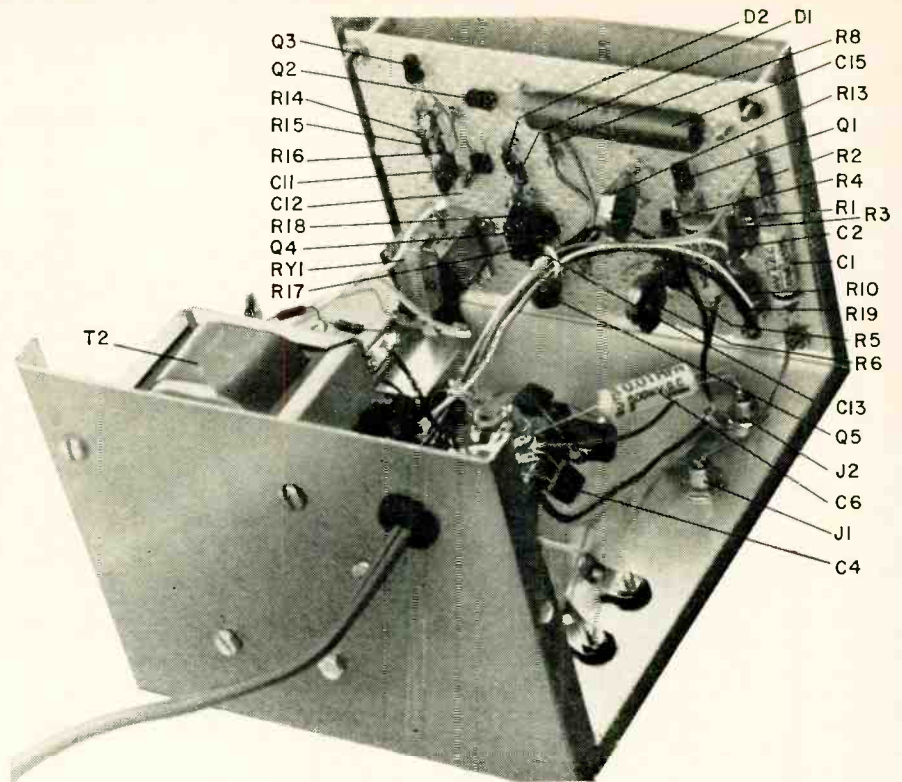You'll never cease to amaze people with this "magic" gray box. **R-E**



Transistor circuitry is mounted on perforated board with point-to-point wiring.


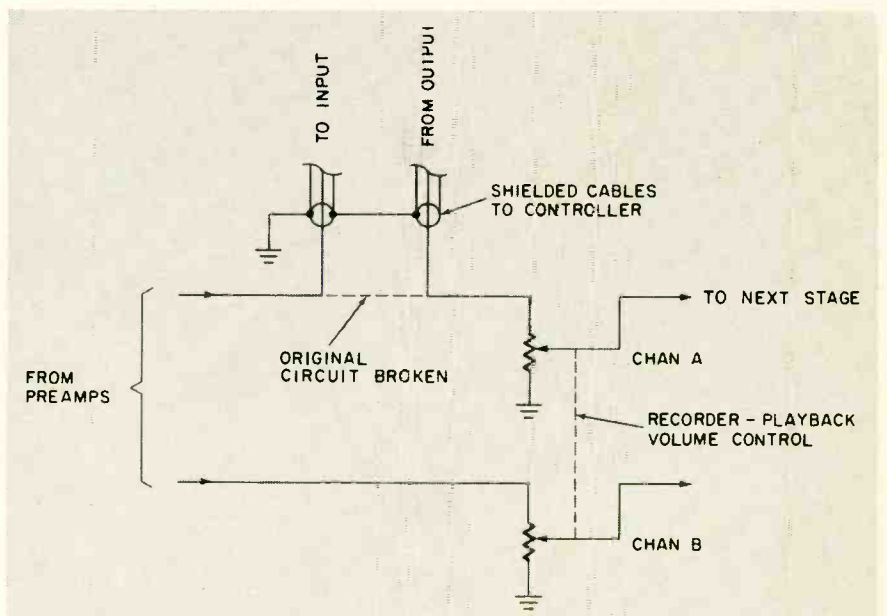


Fig. 2—Controller can be connected to tape recorders (self-contained) by wiring the controller into the signal path from the preamplifiers feeding volume control.

Fig. 3—An additional box with holding relay can be used to turn off your hi-fi system. When a control pulse occurs at end of tape, relay opens and removes power.

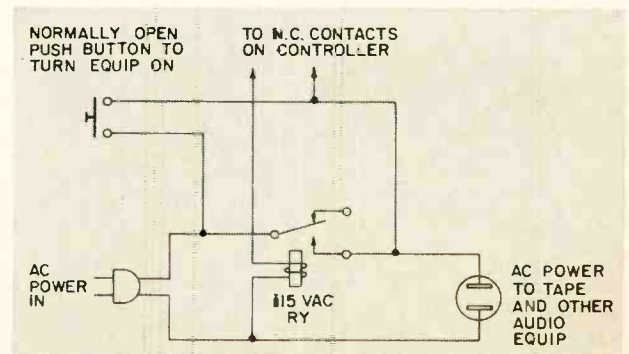

Brighten your home this season with rainbow lighting

Dancing Christmas Lights

By R. W. FOX*


REMEMBER THE COLOR WHEEL YOU bought last year, and the blinking lights from the year before? They're obsolete. Here's the color blender, the latest in special lighting for this Christmas season. No more sudden flashes; no more monotonous repetition of red, yellow, green, for hours. This year you can get every color of the rainbow with a cycle time of—well, it still hasn't been measured. All of this in a tiny box, waiting to please both family and friends.

The Color Blender consists of three identical circuits, one for blue, one for red, and one for green. Combinations of these colors will produce every color in the rainbow. Figure 1 shows graphically what is happening and, by the way, the first time you turn it on could very well be a happening! Due to the variation in component tolerances, these circuits will not be identical in performance. One may come on faster than the rest; one may stay off longer. This will give a true randomness to the colors, which is not possible with a color wheel or two, three or even fifty color wheels, since they operate similarly.

Figure 1 shows the output of the three channels as a function of time. At the start the green light is on while the others are off; the red then comes on and the color changes to yellow; then the red and green go off and the blue comes on. As this is happening the color of the display passes through a violet portion and then to pure blue. In this picture the next scene is all the lamps out or dark. Then the red comes on, followed by the green to give yellow, then the blue to give white light since all the channels are at full intensity. At the end the red lamps go out to leave a blue-green scene.

With Christmas just around the corner, the Color Blender would be the perfect addition to your home decorations, inside and out.

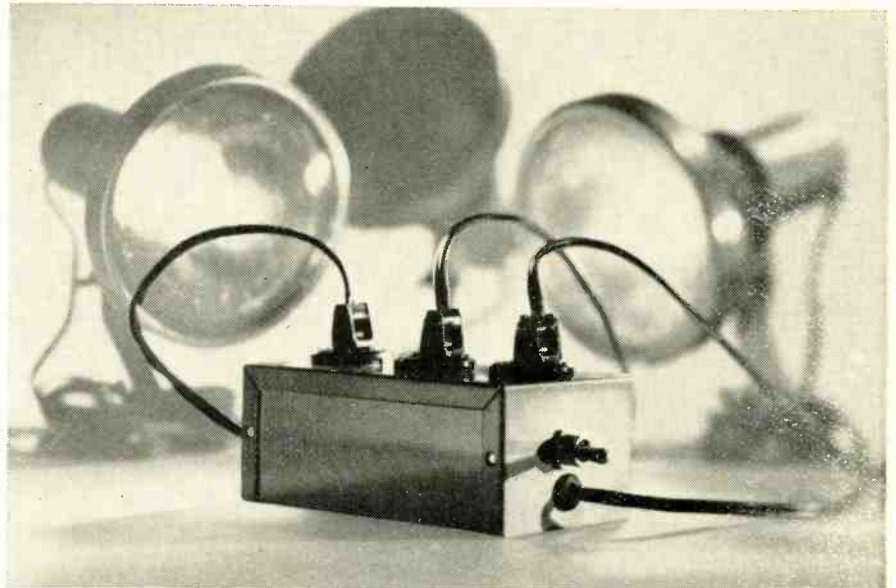Inside, the Color Blender will handle up to 25 miniature lights (6 watt) per outlet on your Christmas tree. If you intermingle three strings, one each of red, blue and green, with



balls and tinsel to reflect the light, your tree will seem to come to life. Or, as another way, you could use up to 150 watts per outlet of flood lamps with color filters shining on a metallic tree.

Outside, you could use strings of lights on a tree (be careful not to exceed the load limit on your circuit), or flood lights on the house or on a door covered with wrinkled foil. The wrinkling keeps the colors separated but allows them to blend in some areas to give a multiple color effect.

After Christmas, there is no need to put the Color Blender away. Just build a foil reflector with a large picture frame and shine floodlights on it for a great addition to your game room.

How it works

The G-E type D13T1 Programmable Unijunction Transistor, allows us to build this unique circuit. The D13T1 can be thought of as a complementary SCR. When the gate voltage drops below the anode voltage, current flows from anode to cathode. This circuit uses this feature to phase-fire the C106B1 SCR (see Fig. 2). When the Color Blender is initially turned on, both C1 and C3 have no charge. Capacitor C4 quickly charges to a voltage greater than the D13T1 gate voltage and triggers the D13T1, which in turn triggers the SCR, causing the light to come on brightly. On each succeeding cycle of operation

capacitors C1 and C3 have a higher initial charge so that C4 cannot charge to a voltage which would trigger the D13T1 until much later in the cycle. Since C3 charges at a faster rate through R7-R8 than C1 and through R5, R6, R4, the lamp dims slowly. When the lamp goes dark, C1 discharges faster than C3 and the triggering angle of Q1 is advanced and the light brightens again.

The purpose of R1 in the circuit is solely for the protection of the C106B1 SCR. This resistor keeps the peak current through the SCR within its ratings. Although it wastes a considerable amount of power, about 4 watts at full load, it is better than replacing the SCR whenever a lamp burns out.

In addition to adding to the beauty of your Christmas display, the Color Blender also increases lamp life at least 25 times. This increase in life is due to operating the lamp on half wave. An added consequence of half wave operation is lower bulb temperature, decreasing the chance of fire, hence giving greater safety.

With the board mounting, all three circuits can be built at the same time, reducing the chance for mistakes. Since one side of the line is common to many components, a single bus running the entire length of the board may well be a good way to start. To make the circuit compact, R1 should be left off the board and wired directly to the outlet. This also

* Application Engineering
Semiconductor Products Department
General Electric Company
Auburn, New York

keeps R1 far enough away from the SCR. Watch the connections of the SCR and Programmable Unijunction Transistor. Reversing the lead order could very well destroy these units. The polarities should also be observed on the electrolytic capacitors and the three diodes.

For safety's sake do not ground the box to the line, for a reversal of the plug could be dangerous. If you have a three wire system, though, by all means use that third wire as a ground for the case.

Figure 3 shows the board as it was constructed with all three circuits so that it would fit in a 5 x 2 x 3 inch box (Bud-CU-2106-A or equal). You will note in Fig. 3 that the leads and tab of the C106B1 are bent. **CAUTION:** The tab should be held by long-nosed pliers between the body and the bend while you are forming the device.

To prepare your box, punch three 1/4 inch diameter holes in the top, one small hole in one end for the line cord, one for the switch and the box is ready. Insert into the box the three outlets and fasten them in place with spring clips. The R1 resistors can be attached on one terminal and their free ends connected to the switch. Use heavy bus wire from the other outlet terminals to the board, and no other supports should be needed to hold the board in place.

Once the circuit board is mounted in the box and the final connections are made, but before you put the Color Blender to use, you may have to adjust the R8 resistors. If an associated light comes on but damps out to a level between full on and off, R8 should be decreased. If the lamp snaps on, R8 should be increased. **R-E**

References For Further Reading

1. SCR Manual, 4th Edition, General Electric Company
2. Hobby Manual, 2nd Edition, General Electric Company

PARTS LIST

Capacitors—50 volts unless noted

- C1—33 μ F, electrolytic
- C2—1 μ F, 25 V, electrolytic
- C3—10 μ F, electrolytic
- C4—0.05 μ F, paper
- D1, D2, D3—1N5059

Resistors—1/2-watt, 10%, carbon unless noted

- R1—5 ohms, 5 watts
- R2—1000 ohms
- R3—82,000 ohms
- R4—22,000 ohms
- R5—220,000 ohms
- R6, R7, R9—100,000 ohms
- R8—50,000 ohms, potentiometer
- Q1—D13T1
- SCR1—C106B1

Miscellaneous hardware—box, line cord, outlets (Amphenol 61-F1 or equiv.) circuit board, switch (Except for the box and line cord, three sets of parts will be needed to build a three-lamp controller)

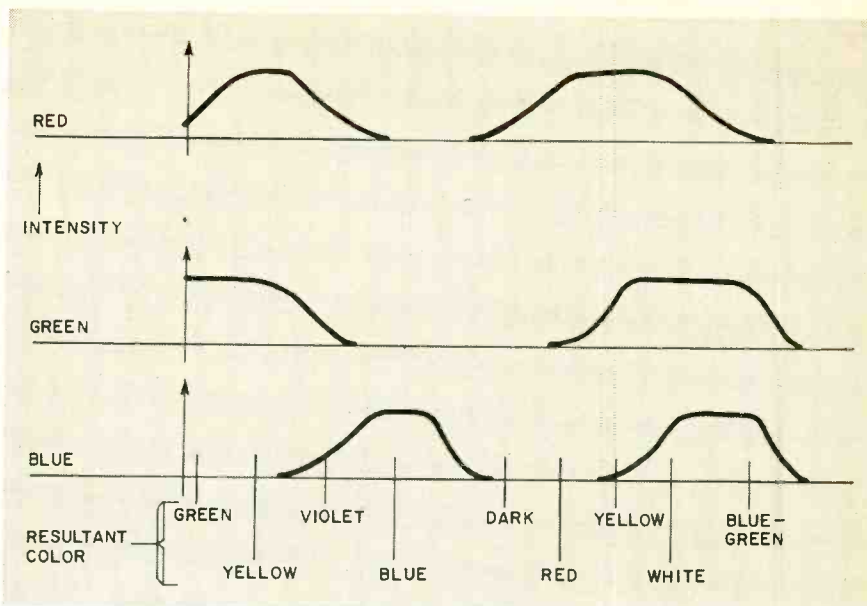


Fig. 1—Output amplitude of three light channels as a function of time. Variation in component values cause each channel to randomly vary lamp pattern and intensity.

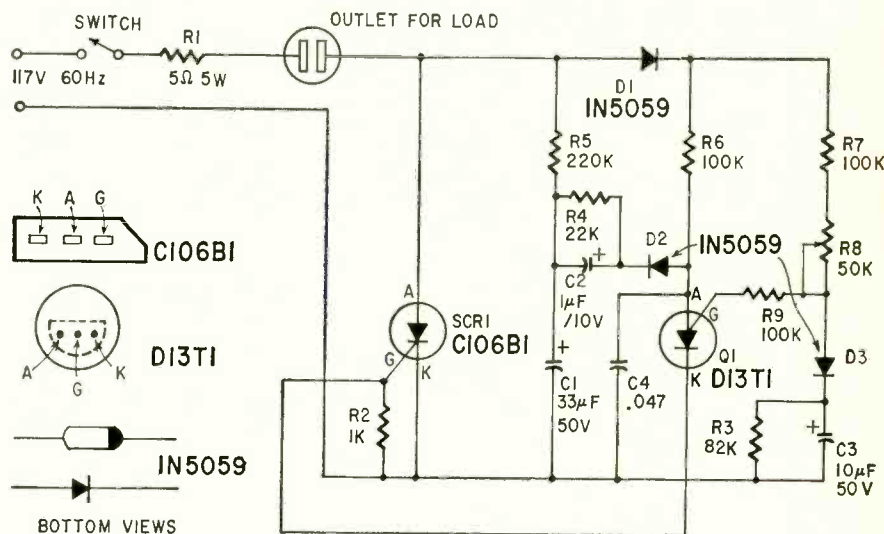


Fig. 2—Unijunction transistor Q1 is used in conjunction with the D13T1 SCR to turn the lamps on and off. The charging relationship between C1, C3 and C4 set the pattern.


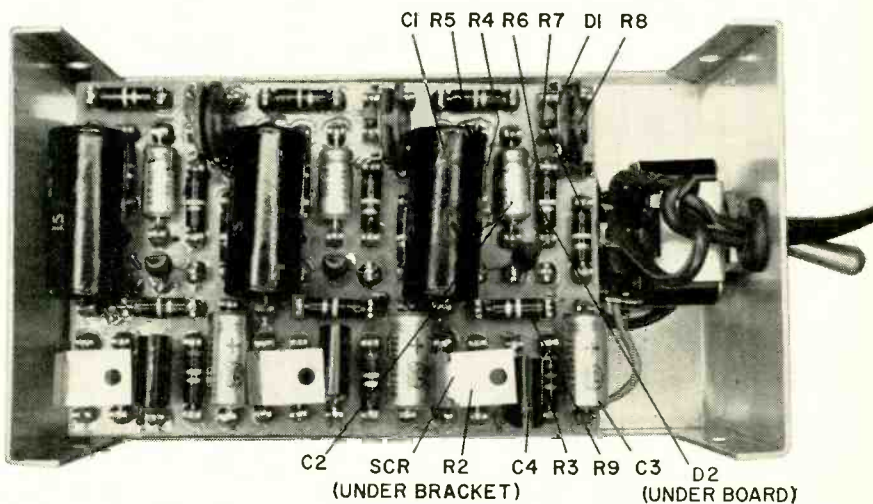


Fig. 3—Component layout for all three identical control channels. Parts are identified on one channel only. Resistor R8 is adjusted to establish proper "on" sequence.

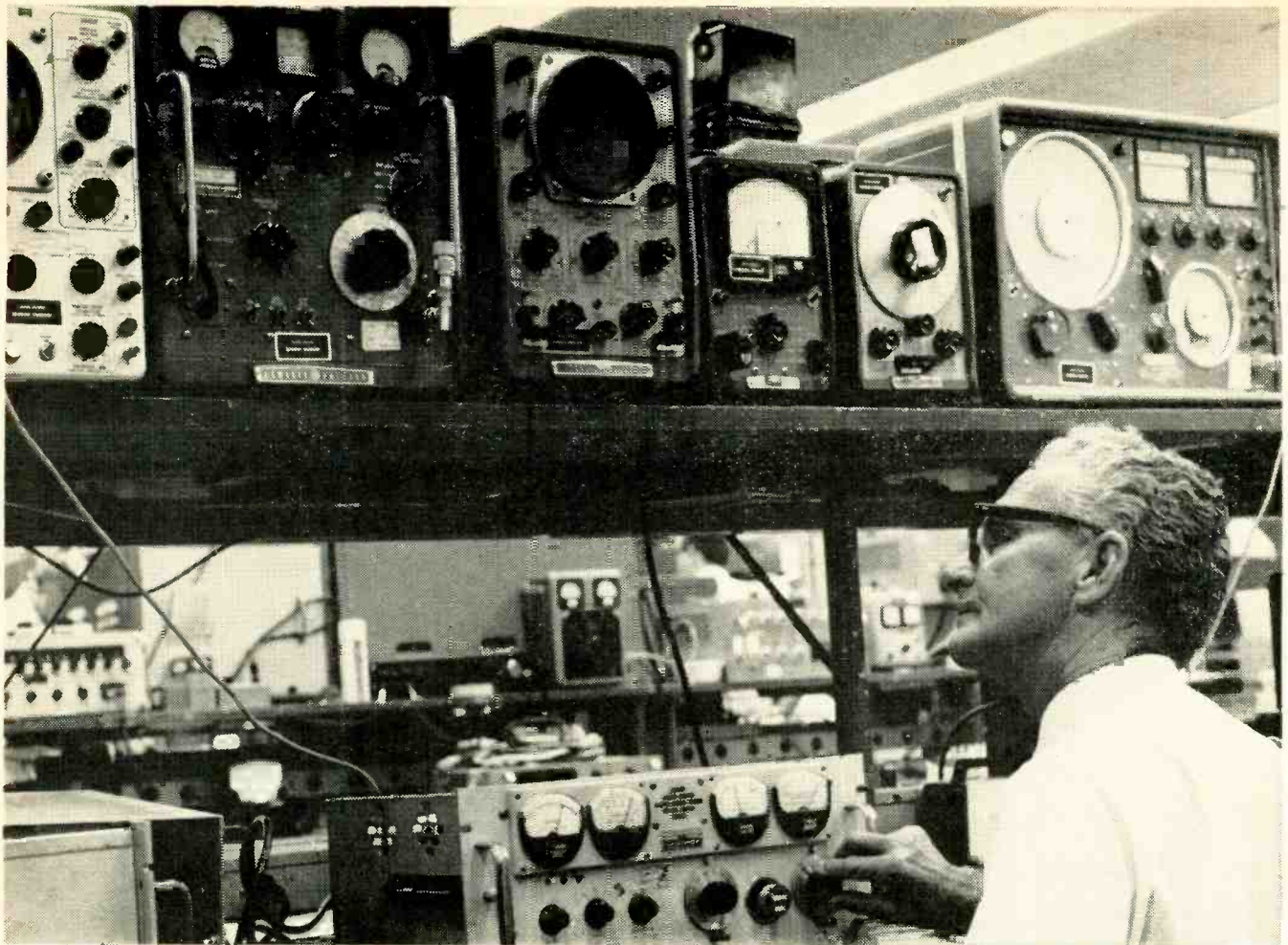

Jobs For Electronic Testers


Find out what know-how you need to start a fascinating career

By L. L. FARKAS*

WHAT SHOULD AN ELECTRONIC TESTER know to get a job in industry? The first prerequisite of course, is knowledge of basic electronic theory. This can be obtained through reputable electronic schools.

He should be familiar with the theory of transmission, reception, detection and amplification of radio signals, and with circuits used to handle audio and video frequencies. He should also know something about the different types of power supplies and various antennas.

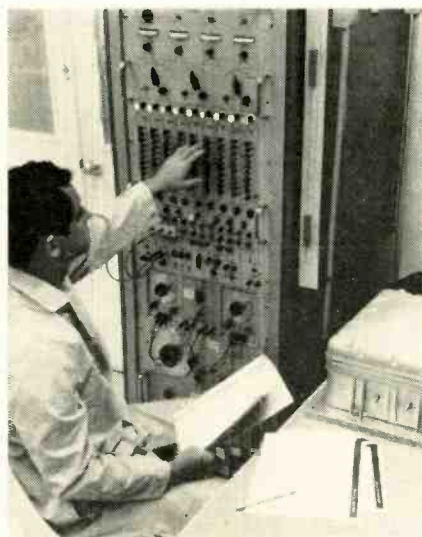Moreover, an electronic tester should be capable of calculating voltages and currents. In testing, he may have to find the value of a certain voltage-dropping resistor or determine the



Testmen must often record data from a completed unit using special equipment. Testing Saturn Control Signal Processor.

amount of current flowing through a circuit. This is particularly true when working with current-sensitive devices whose current must be limited to protect them from burnout.

The tester should be able to calculate the frequency response and impedance of a circuit, since he may need to match input and output impedances to obtain maximum energy transfer.


With the advent of solid-state technology, the tester must know something about diode and transistor characteristics, as well as the types of circuits in which they are used. In fact, by outside reading, he should bring his knowledge up to the state-of-the-art on all semiconductor devices. This is especially useful in a research and development job where, as a technician, he will have to hook up and check such devices.

As important as theory and state-

RADIO-ELECTRONICS

*Quality Division,
Martin Marietta Corp.
Orlando, Fla.

Join the rotor revolution...

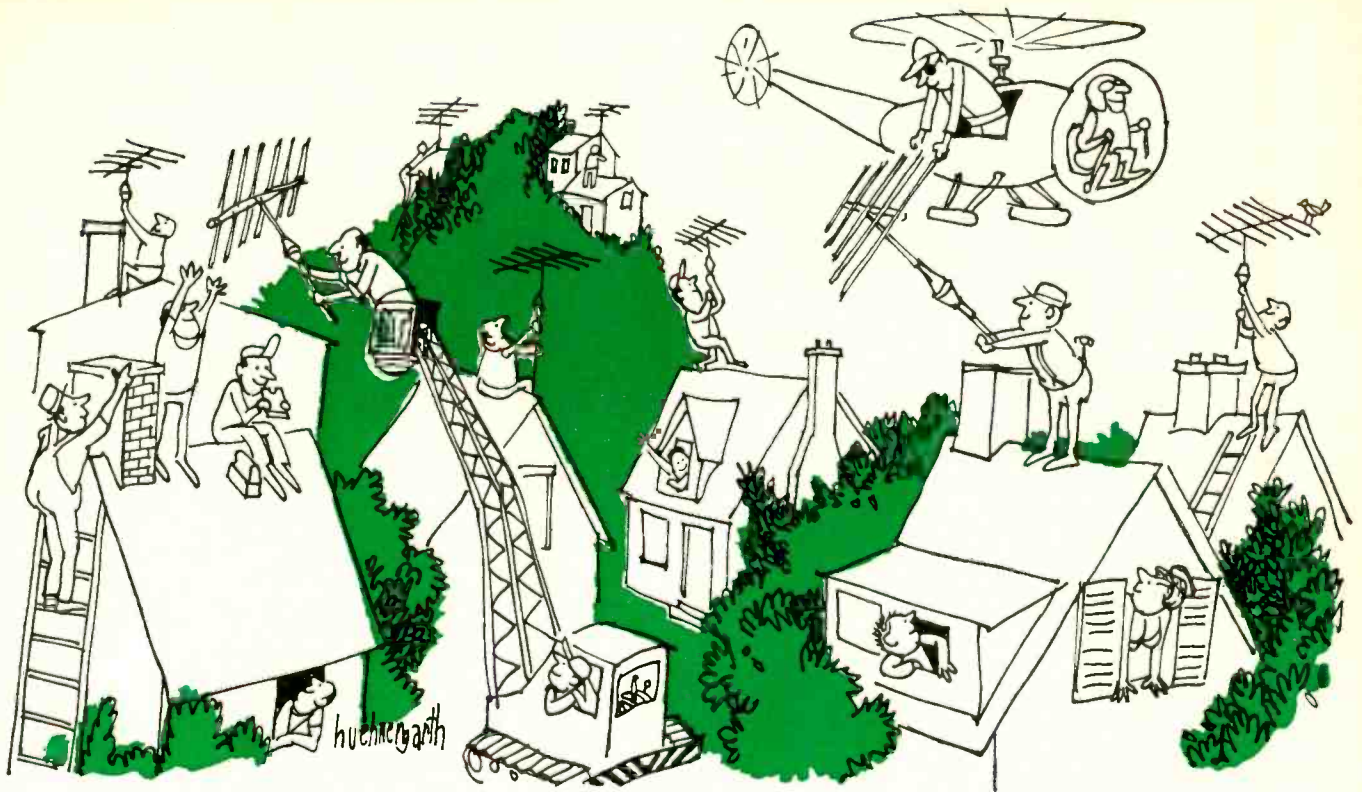

with the fast-selling new Jerrold

DYNA ROTOR™



Orders are rolling in for the new Jerrold DYNA-ROTOR—fast. We're not surprised, for here... at last... is a profit-making rotor you can rave about:

- Combines all solid-state circuitry with unique dynamic spline drive
- Fully automatic rotor moves quickly—and precisely—to the point where it is aimed by the control unit—never loses synchronization, never drifts
- High torque drives through ice, snow, and high winds
- Rotates 360° in less than 40 seconds—fastest rotor available
- Kitten-quiet solid-state control unit. No clacking. No whirring. No relays, switches, solenoids, or escapements

- No lubrication required—operates reliably at -20°F
- Lightweight, easy-to-install rotor weighs only 5 pounds
- Consumes less than 1/10th the power of other rotors
- Decorator-designed control unit
- Streamlined aluminum rotor case—in-line design

What more could you ask? Ask for the special deals now available for Jerrold DYNA-ROTOR. See your Jerrold Distributor today or write Jerrold Electronics Corporation, Distributor Sales Division, P.O. Box A, Philadelphia, Pa. 19105.



a GENERAL INSTRUMENT company


Focusing on one thing... better reception

Circle 26 on reader's service card

of-the-art familiarity is the ability to use test equipment. While technical school students get some practice in using test equipment, this function is not always stressed. Furthermore, the number and types of equipment may be limited.

Remember that a tester's or a technician's tools are the meters, bridges, generators and oscilloscopes with which he feeds signals into equipment and checks the output of the equipment.

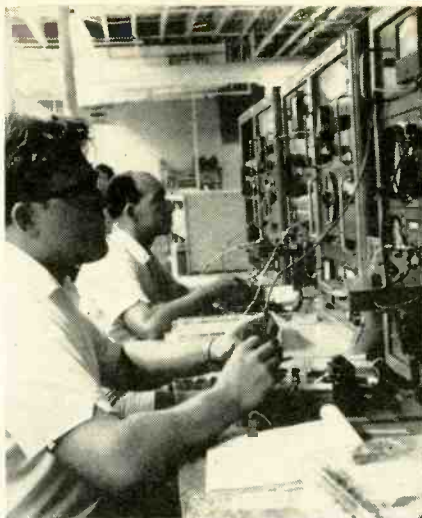Where will he use this test equipment? At a component plant, the tester must check the electrical characteris-




Completed missile modules under test.



Troubleshooting a subcarrier oscillator.

Ultra-compact Solid State

color bar pattern generator

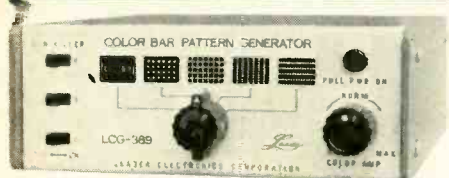

LCG-389

Pattern appears instantly when turned on, and is as stable as a station signal. Compact and sturdy construction for field use — supplied with carrying case. Only 2 1/4" x 5 7/8" x 7 3/4", weighing about 3 pounds.


- Crystal controlled oscillator.
- Flipflop and logic circuitry assure highest operating stability
- One receiver input to TV antenna
- Two selectable TV channels
- Chroma level control — 0 to 200%
- Horizontal line flickering prevented by progressive scanning
- Horizontal and vertical signal return trace blanking
- Gun killers for convergence adjustments
- Regulated DC power supply

ONLY \$99


LEADER
TEST INSTRUMENTS

24 - 20 Jackson Ave.
Long Island City, N. Y.

Circle 27 on reader's service card

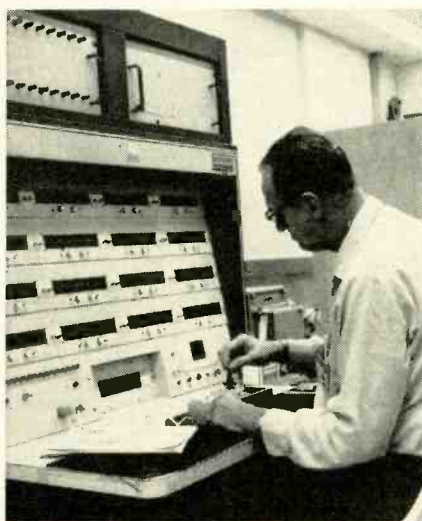

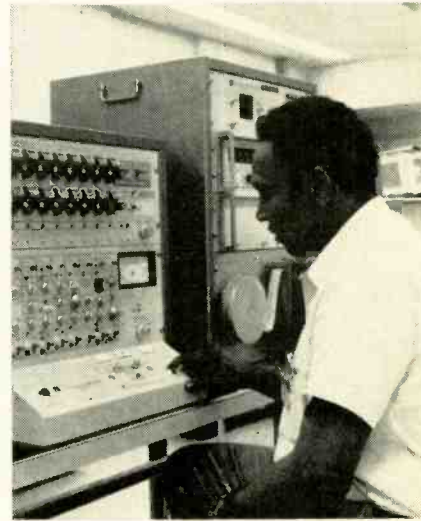Checking transistors on automatic tester.



Recording data on field effect transistors.

tics of resistors, capacitors, diodes, transistors, coils and transformers. He may have to check complete subassemblies such as i.f. or rf strips, power supplies, amplifiers, or chassis of radio or television receivers.

If he is working for a firm that buys such equipment, he may have to test components or equipment to make sure they meet purchase specifications.

On the production line, the tester will again test components, subassemblies, chassis, subsystems or complete systems. Here, not only the basic types of test equipment are used, but often the more complex digital voltmeters, frequency meters, counters, dual-beam oscilloscopes and electronic tools built specially to test hardware parameters.

Other areas where the tester uses equipment include standards and calibration laboratories, anechoic chambers, environmental test areas and various engineering laboratories where electronic equipment is developed.

To use test equipment correctly,

the tester must know its characteristics. What are the limits to which it can test hardware, parameters such as voltage, current, frequency? What is its impedance? How accurately will it measure a certain value? What are its usable scale factors?

One quality the tester must acquire is the ability to follow test procedures. On a production line, test procedures are used to insure each component or chassis is tested in the same way. Deviating from procedure might facilitate a test or make it shorter, but there is always the danger an important part of a test may be omitted or equipment may be tested to the wrong parameter. Once test procedures have been established, the tester must learn to follow them implicitly. Then, should test procedures be wrong, it is the tester's duty to point them out to his supervisor so they can be remedied.

Testers must also be able to read and record production test data. This

There's nothing wrong with the set.



You fixed the picture a week ago, now you're back repairing your repair job. And paying for it.

Replacement parts are supposed to last longer than that.

Like electrolytic capacitors. If they're wound in computer-grade, 99.99% pure aluminum foil, they'll hold up for a long time at continuous temperatures of 85 C.

Like Arcolytic capacitors do.

Even though they cost the same as any other home entertainment capacitor. And come in more than 2000 exact replacement values to maintain the set's stability.

Any Arcolytic distributor can fill you in on the whole line of

Arcolytic types—twist mounts, printed circuit twist mounts, tubular electrolytics (including very high capacitance values) and miniature tubulars in the smallest physical sizes. He can also sell you Elmenco capacitors.

Then you won't have to do repair jobs twice. If the lady in the set seems to be missing something, a week after you've done a repair job, it's her problem. Not yours.

Loral Distributor Products

A DIVISION OF LORAL CORPORATION
Pond Hill Industrial Park, Great Neck, New York 11022

Circle 28 on reader's service card

One of a series of brief discussions
by Electro-Voice engineers



While most people think of a computer as a vast mathematical machine, its advantages go beyond its ability to handle numbers. The design needs of the computer itself have created new techniques in component packaging that can be translated into design features in other products with considerable benefit to the end user.

Etched and printed circuit design has received perhaps its greatest stimulus from the needs of the computer to provide high reliability from an astronomical number of components, in as small a volume as possible.

One of the techniques developed to fulfill this need was the creation of circuit modules, composed of separate etched circuit boards with a complete sub-circuit on each board. Large numbers of modules could be combined to form a complete device of virtually any power. Initially the modules were connected by wires, but this created bulky wiring harnesses that required lengthy testing, and often were the source of poor or mis-wired connections.

In order to eliminate interconnections as a source of trouble, wiring was transferred onto a master etched circuit board, and each module plugged directly into the "wiring" board. Development of highly reliable phosphor bronze connectors simplified construction and assembly while reducing faults due to interconnection, to a minimum. Several new Electro-Voice stereo receivers (Models E-V 1181, E-V 1182, E-V 1281, and E-V 1282) are among the first to use this computer-derived assembly technique.

Male connectors are staked into the main wiring board wherever needed, then flow-soldered. Receptacles are located on each of the circuit modules, and flow-soldered along with the individual components on the module. Each module is then simply plugged into the wiring board, and locked in place with suitable mechanical fasteners.

Since wiring is identical for each receiver, the exact capacitive, inductive and resistive parameters of every production receiver can be predicted in advance. This permits optimizing circuits (especially RF and IF circuits) without the broad tolerances needed when normal lead dress variations must be taken into account in a hand wired receiver.


In addition, testing is greatly simplified. Individual modules can be tested before insertion in the receiver, then the entire unit tested as a whole. Trouble shooting is also simplified by the use of discrete circuit modules. Since virtually all circuit connections are flow-soldered, cold solder joints and mis-wiring are almost unknown in production.

Adoption of the plug-in module concept has meant that designs can more closely duplicate laboratory models, and performance is undiminished by the rigors of shipment and mishandling. A higher level of performance can be assured with no increase in cost.

For reprints of other discussions in this series,
or technical data on any E-V product, write:
ELECTRO-VOICE, INC., Dept. 1283E
613 Cecil St., Buchanan, Michigan 49107

Electro-Voice

A SUBSIDIARY OF GULTON INDUSTRIES, INC.

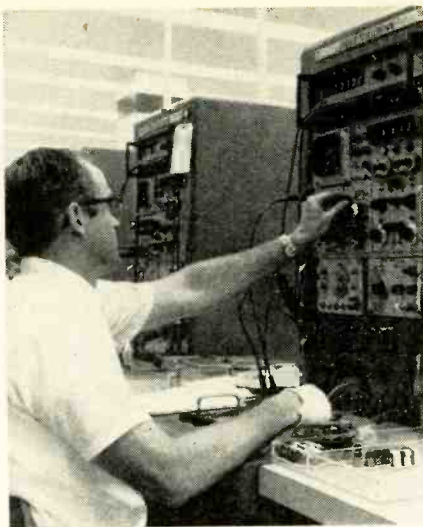

Test station for electronic modules.

may sound simple, and it is, provided the tester pays particular attention to the way he determines the data. Are the meters on the correct scale, the switches on the right setting? Are the data read directly? Are the multipliers taken into consideration? Is the right extrapolation made when the results are between calibration points? These are some of the factors that must be kept in mind when reading data.

In recording the data, the tester must also insure he does not list results erroneously. Here a little extra time checking that data are placed in the right columns, that records are legible, and that decimal points are not misplaced will prove invaluable when the time comes to refer to test results.

It also helps to write down any unusual test conditions, particularly when these affect test readings. The more information a test evaluator has about a specific test, the better he will be able to analyze problems and correctly interpret test results.

A tester must also have experience in troubleshooting hardware. Normally, troubleshooting is a fairly simple function. Faced by malfunction in equipment, the tester first plans the method he will use to isolate the defect. Then he selects the test equipment required to execute his plans.

However, to troubleshoot properly, the tester must have a good idea how the defective hardware should operate. He should know what voltages, currents or types of signal the hardware should produce. He then selects test equipment that will correctly show these characteristics.

Finally, he must determine where to connect this test equipment so it will record the desired data without affecting normal hardware operation.

Of course, troubleshooting com-



Automatically testing a module "card."

plex equipment cannot be done without training in its theory and operation. But the basic methods used for troubleshooting such items as receivers, transmitters, power supplies and displays should be part of every tester's education. As long as he knows basic troubleshooting methods, he will be able to adapt these to solving problems in more complex hardware.

Know your schematics


One basic requirement for troubleshooting is the ability to read schematics and line drawings. Only by being familiar with circuit symbols, drawing methods and print references can the tester hope to trace the operation of the circuits he's investigating.

Once he isolates the defects, he must record his findings. (There is nothing more frustrating to the corrective-action engineer than to find the record of a component replacement without an indication of the problem encountered, or with a description of the defect so garbled that he can't decipher it.)

So it is extremely important that the tester who troubleshoots does a good job of documenting his findings. Only by providing such definite and clearly understandable data can the tester help provide the required corrective action.

Thus, testers must not only know the basic theory of the equipment they are testing, but they should also be thoroughly familiar with the characteristics of their test equipment. They should be capable of following test procedures implicitly, know how to isolate defects and have the ability to record data accurately. With the capabilities, a tester should have no difficulties in obtaining and maintaining a job in industry.

R-E

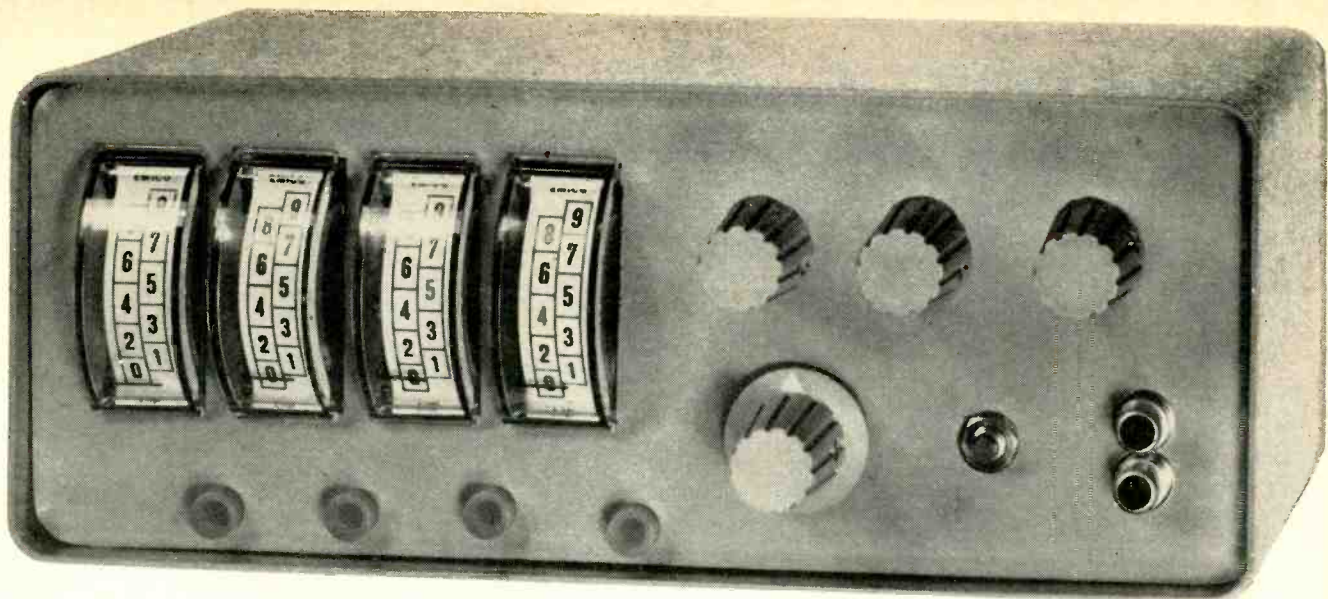

FOR THE EXPERIMENTER

9 Digital Readout IC Instruments

Start with digital readout modules, add a power supply, then try these devices.

By RALPH GENTER

WOULD YOU LIKE TO BUILD A FREQUENCY COUNTER, A digital voltmeter, an electronic piano tuner, and half a dozen other typical digital instruments? You can, and rather easily. First though you'll need some digital readout modules—complete instructions on how to build them at \$10 each appeared in November's *RADIO-ELECTRONICS*.

Powering the modules

The first order of business is a power supply. For a 4-digit readout, we'll need a regulated 40 mA at 18 V; around 0.5A at 3.6 V; and possibly a split, low current dual 6-V supply. The circuit is in Fig 1.

It is vital that the meters in the individual modules do not interact or change their readings with time. The Zener/transistor regulator insures a stable reference voltage. Low ripple is the main problem on the 3.6-V supply. We maintain it through brute-force filtering with two large electrolytics. To get by on a stock transformer, we have to drop the input dc voltage on the 3.6-V supply with the forward drops of several silicon diodes. This is better than using resistors as the voltage drop is nearly constant and independent of loading.

The final portion of the supply provides the low current +6- and -6-V supplies that will be needed if a comparator is part of the particular instrument you want to build.

Driving the modules

Now we can connect our four modules in cascade,



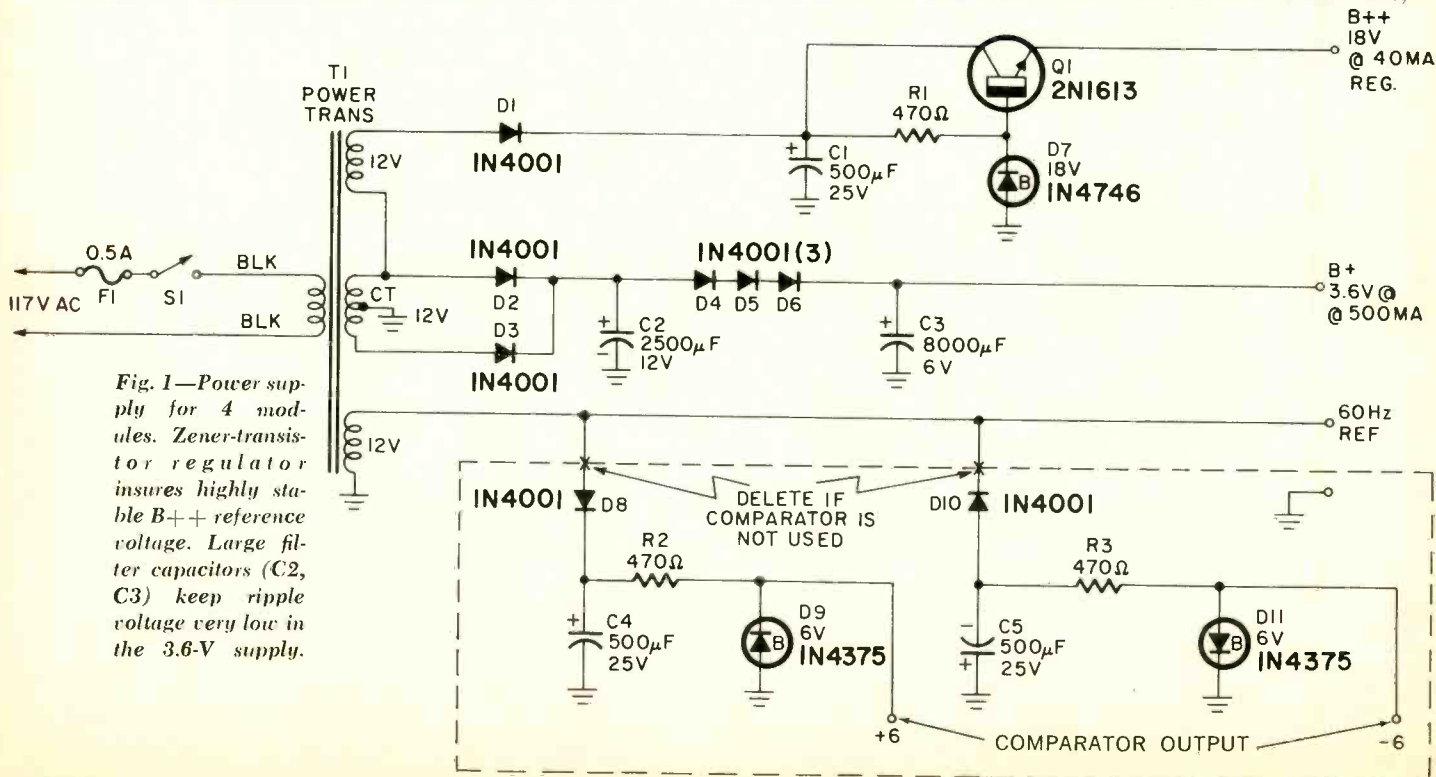


Fig. 1—Power supply for 4 modules. Zener-transistor regulator insures highly stable B++ reference voltage. Large filter capacitors (C2, C3) keep ripple voltage very low in the 3.6-V supply.

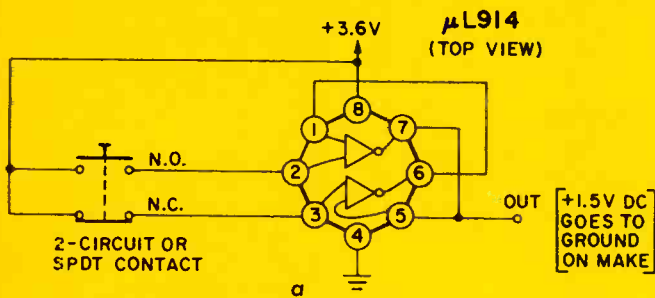


a

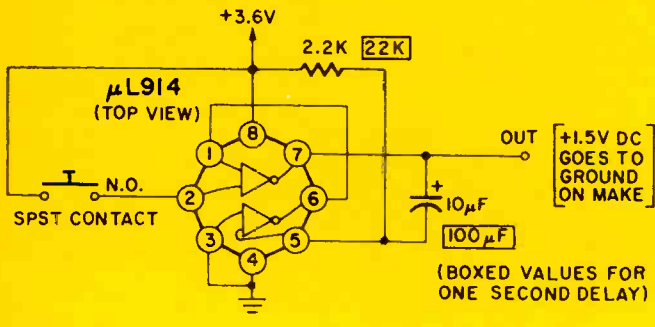


b

Fig. 5-a—A spdt switch can be made "bounceless" with a μ L914. b—External circuit connections to IC for single make contact.


Fig. 8—Scaling circuits divide input signals for easy counting. Divide by 2 circuit is a binary divider; two JK flip-flops with feedback form the divide by 3 circuit. The divide by 10 is a "Modulo ten minimum hardware circuit" without gates.

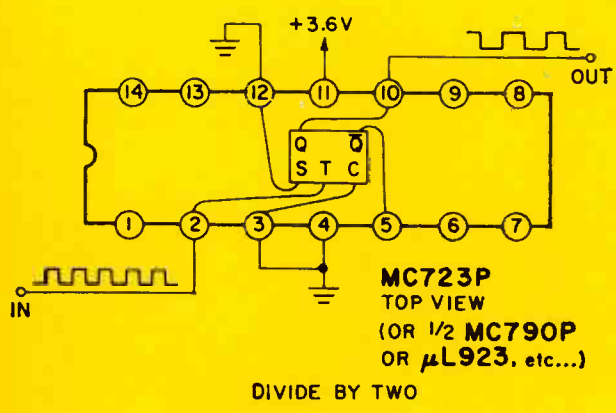

DIVIDE BY TWO

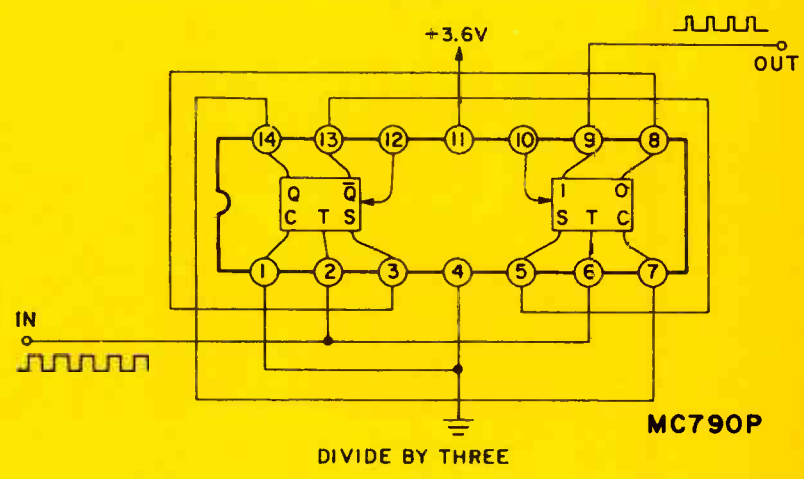

DIVIDE BY THREE

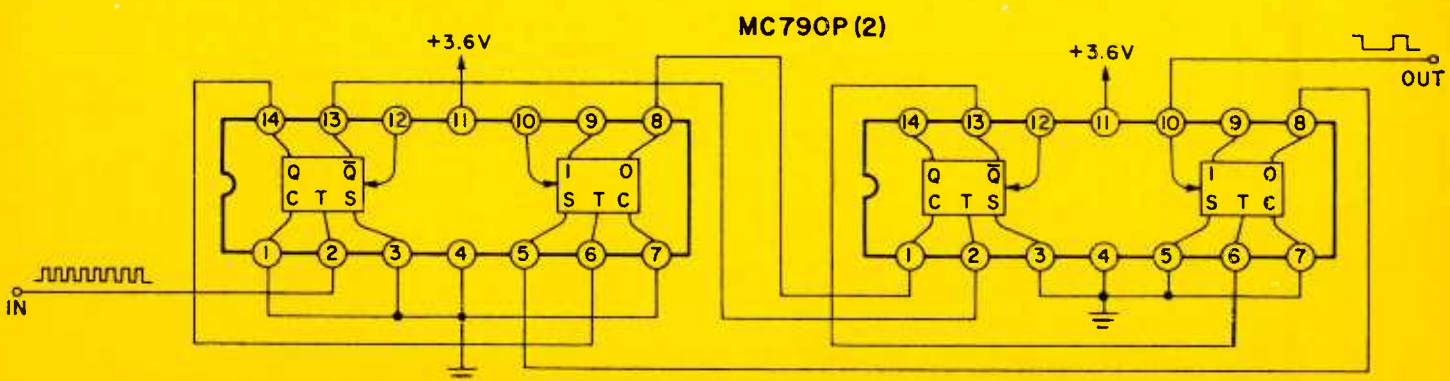

DIVIDE BY TEN

NOTE: +4 = +2, +2
 +6 = +2, +3
 +50 = +6, +10, etc.

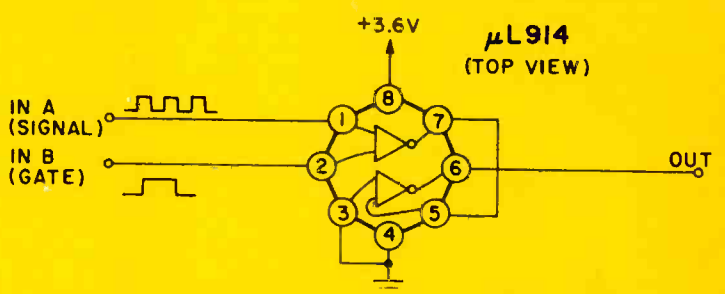


Fig. 6—Module on-off gate. If B is grounded, input A is passed. If input B is positive, output stays positive.

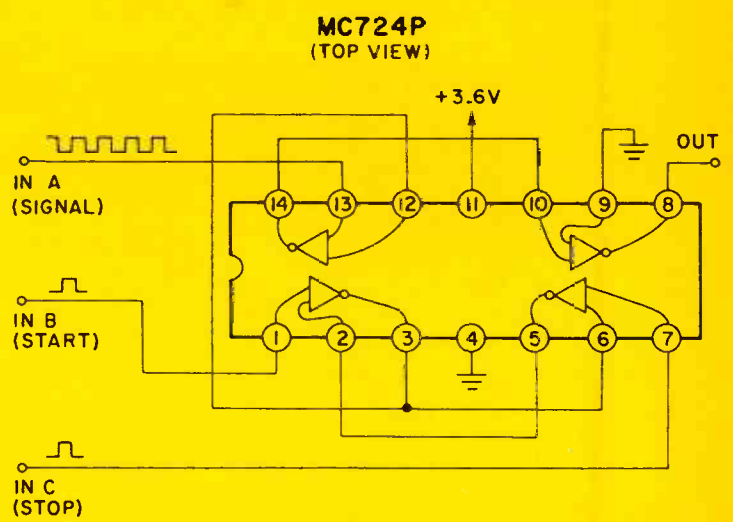


Fig. 7—Start-stop gate. Input A is passed only between pulses B and C. Input B must be off before C arrives.

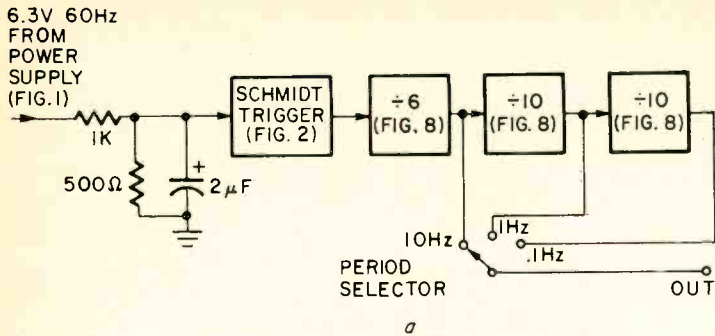


Fig. 9-a—Obtaining 10-Hz square wave from power supply. b—Crystal frequency reference.

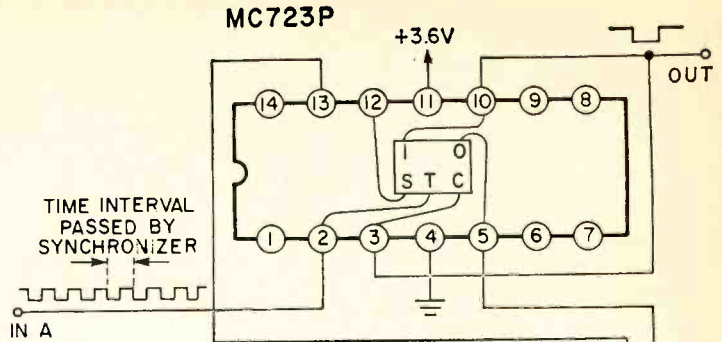
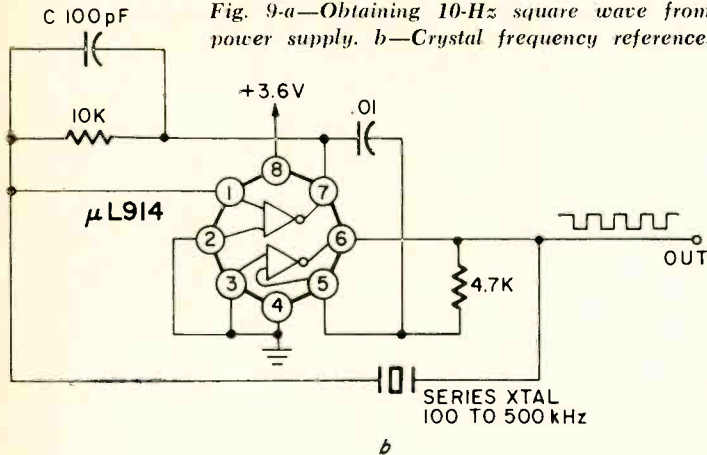


Fig. 10—Synchronizer passes one complete and precise time gate upon random command, such as from a push button.

ments that take two inputs, such as a drag-strip trap speedometer.

Scaling

We will also need a way to divide down signals, perhaps for a 10-MHz input signal that needs reduction to 100 kHz so it is easily counted, or a 60-Hz power-line signal that is divided by 6 to get 0.1-second pulses, or by 60 to get 1-second pulses. These are called scaling circuits and are easily built from the same JK flip-flops we used in the decimal counting modules. The most common factors we would like to scale by are 2, 3, 6, and 10. The required connections are shown in Fig. 8. The divide by 2 is simply a binary divider, while the divide by 3 uses two JK flip-flops and feedback to produce the division by three. A divide by 6 is nothing but a divide by three followed by a divide by two. The divide by 10 is called a "Modulo ten minimum hardware" circuit, and requires no gates to produce a division by ten.

Time and frequency bases

All but the straight counter applications of the decimal counting modules require either a source of a stable reference frequency or some gates of precisely known time widths. The accuracy of the instrument depends entirely upon the accuracy and stability of these references. A 4-decade instrument is inherently capable of 0.1 to 0.01% accuracy—if the references used exceed these figures.

The 60-Hz power line is a handy source of accurate time gates. In most parts of the country, the line is held to within 0.05% of 60 Hz, and the short-term stability is even better. This time base is good enough for most three- and four-place digital instruments, and far cheaper than starting with a high-frequency crystal and dividing down. Fig. 9-a shows how we borrow a 6.3-V ac reference off the power supply, filter it to remove noise, Schmitt trigger it, and divide it by six. This gives us a 10-Hz square wave.

Two scalings by ten will then give us 1 Hz and 0.1 Hz, with their equivalent periods of 0.1, 1 and 10 seconds.

For a frequency reference [You'll rarely need both references in a single instrument], we can turn to a crystal, possibly 100 kHz, 500 kHz, or some other frequency that is the magic number that makes the readout and the answer fit the measuring problem. This oscillator (Fig. 9-b) produces a square wave that will directly drive any of our circuits without conditioning. Capacitor C is adjusted to insure the crystal is oscillating on the proper mode and not on an unwanted overtone.

Synchronizing

This is a tricky little problem. How do we produce one precise time gate, say one second long, on the command of some totally random event, such as a pressed button? We cannot just use a gate, for we may only get a quarter second's worth of gating if we hit the button at the wrong time. And, if we stay on the button too long, we might get several 1-second gates in a row, piling up the numbers in the decimal counting modules. The required circuit is called a synchronizer, and lets one complete cycle of the input pass upon a random command. The output is a grounded signal that lasts the time between negative transitions of the input signal, and one only is produced upon command. The circuit is shown in Fig. 10. It takes two gates connected as a set-reset flip-flop that drives a synchronizing JK flip-flop.

Voltage to frequency

You'll need a voltage-to-frequency converter anytime you wish to digitally measure an input voltage, such as in a digital voltmeter, ohmmeter, or thermometer. In a digital voltmeter, for example, you scale your input voltage, convert it to a frequency, and then measure the frequency in an events-per-unit-time setup.

You'll find the 0.1% accuracy you need too tight for a conventional voltage-controlled oscillator or multivi-

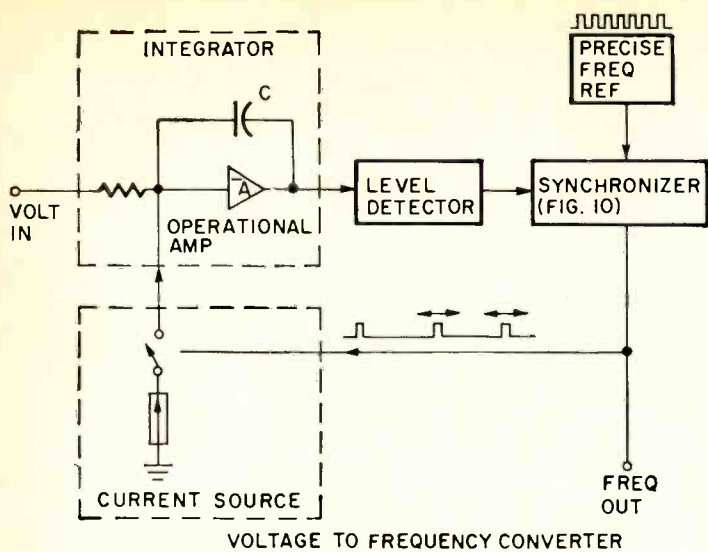


Fig. 11—This charge-integrator circuit offers 0.1% accuracy.

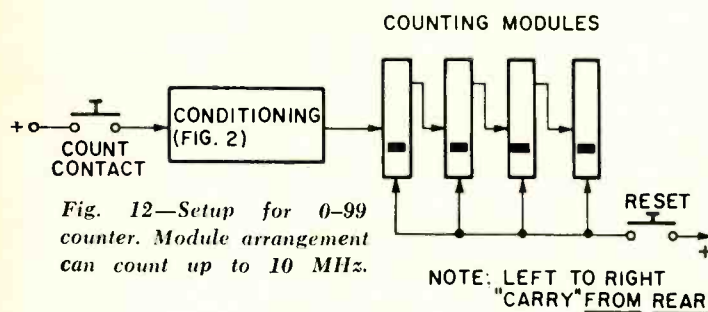


Fig. 12—Setup for 0-99 counter. Module arrangement can count up to 10 MHz.

brator setup. Instead a charge integrator circuit, like the one in Fig. 11 is needed. Operational amplifier A charges capacitor C with the input current. Everytime capacitor C swings positive, the output-level detector reaches around and removes a constant slug of charge from the capacitor. This is done with a constant current applied for a constant reference time. As charge equals current \times time, a constant amount of charge is removed each time the input manages to recharge the capacitor. The greater the input voltage, the faster the capacitor charges, and the more often constant charge has to be removed from the capacitor. The output is a series of pulses of accurate width whose frequency varies very accurately with changes in the input voltage.

Let's build some instruments

We now have all the pieces and parts we need for most any digital instrument. Now, how do we put them together? Anything we build will take three or four decimal counting modules, a power supply, and a box. You might like to try a package similar to the one shown in the photo—it's a deep drawn aluminum case about 3 x 4 x 9 in., and with some careful layout, can house almost any digital instrument you like. If you are careful, you can get by on $\frac{1}{10}$ the size, $\frac{1}{10}$ the cost, and $\frac{1}{10}$ the weight of all but the newest equivalent commercial gear!

Let's start with a straight 0-9999 counter built up like Fig. 12. With square-wave electronic input or mechanical contacts with set-reset conditioning, you can count as fast as 10 MHz. The monostable conditioning circuits are limited to a top speed of 20 counts or so per second. The reset pushbutton need not be conditioned. Resetting a counter 193 times is just as good as resetting it once.

Group your counting modules by twos, and you have a lap counter for a slot car race that not only keeps track

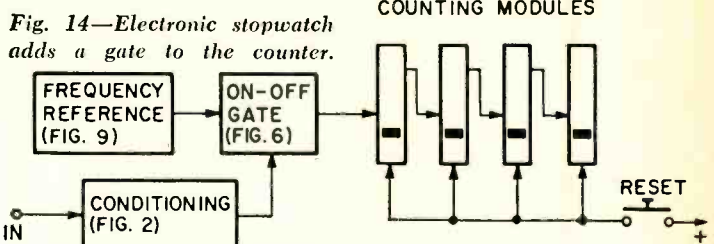
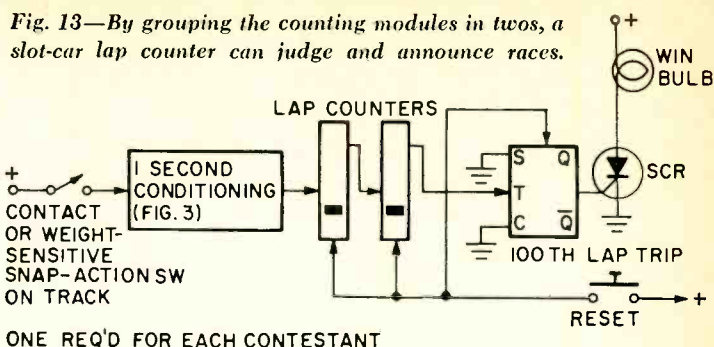


Fig. 14—Electronic stopwatch adds a gate to the counter.

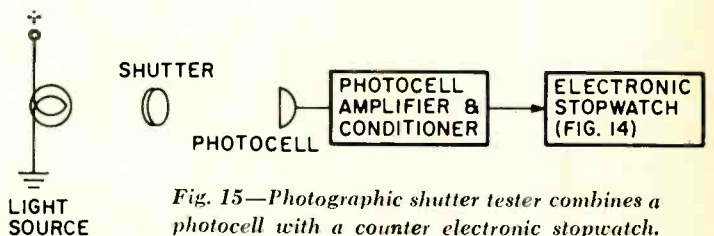


Fig. 15—Photographic shutter tester combines a photocell with a counter electronic stopwatch.


of the laps, but provides an output signal on the 100th lap. Details are in Fig. 13. You can arrange a mechanical, photoelectric, or weight sensitive track pickoff and run it through 1 second contact conditioning, just to be sure the car's bouncing does not register a false lap.

The heart of many of the instruments is an electronic stopwatch, or events-per-unit-time instrument. The simplest type is shown in Fig. 14. All we do is add a gate to the basic counter, and open and close the gate with the event we wish to measure. We obtain an input from a reference frequency source. Your choice of frequency determines the range and resolution. A 1-MHz clock gives you 1- μ sec resolution and a 10-msec range, while a 10-Hz clock gives you 0.1-second resolution and a 100-second range. Make sure your event measuring has an accuracy commensurate with your resolution. Your gating waveform must come up in less than one clock cycle and stay there without noise or breaks for the entire time. Then it must fall in less than a clock cycle. Any other response limitations must be taken into account. You're not about to measure a 10- μ sec pulse with a cadmium sulfide photocell with a 10-msec plus rise time. Nor is anything you do requiring human response on a pushbutton going to be much more accurate than 0.1 second.

Photographic shutter tester

This is a snap. We just put a good photocell in front of our counter connected as an electronic stopwatch and shine light on it only when the shutter is open. Of course you'll need a good quality silicon photocell with a 50- μ sec rise time or so. A 5-kHz clock is a good choice, as it will cover $\frac{1}{1000}$ second down to $\frac{1}{2}$ second. The $\frac{1}{1000}$ second accuracy will only be 20%. If this is not good enough, a faster clock may be switch selected. Details are in Fig. 15.

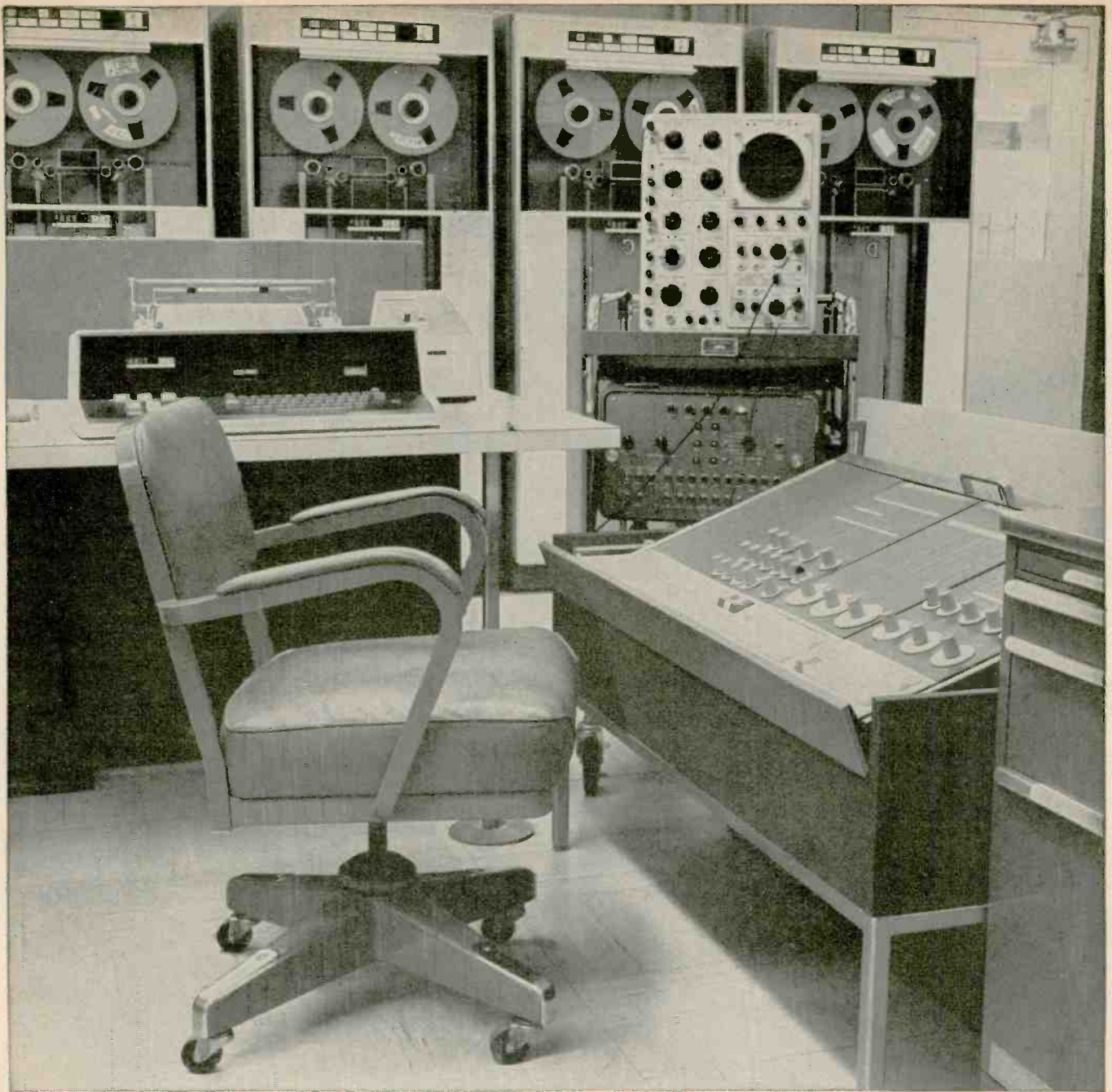A start-stop gate is needed for either the ballistic



This important job (and its big salary) is reserved for a qualified electronics technician. It can be you!

It's a fact. There are *many thousands* of jobs like this available *right now* for skilled electronics technicians. What's more, these men are going to be in even *greater* demand in the years ahead. But how about you? Where do you fit into the picture? Your opportunity will never be greater...so act *now* to take advantage of it. The first step? Learn electronics fundamentals...develop a practical understanding of transistors, troubleshooting techniques, pulse circuitry, micro-electronics, computers and many other exciting new developments in this booming field. Prepare yourself now for a job with a bright future

...unlimited opportunity...lasting security...prestige... and a steadily-increasing salary.

Thousands of ambitious men are using Cleveland Institute of Electronics Training Programs as a stepping stone to the good jobs in Electronics. Why not join them? You will learn at home, in your spare time, and tuition is remarkably low. Read the important information on the facing page. Then fill out the postage-free reply card and drop it in the mail today. Without obligation we'll send you all the details. But act now...and get *your* high-paying job just that much sooner.

How You Can Succeed In Electronics

...Select Your Future From Six Career Programs

The "right" course for your career

Cleveland Institute offers not one, but six different and up-to-date Electronics Home Study Programs. Look them over. Pick the one that is "right" for you. Then mark your selection on the bound-in reply card and send it to us. In a few days you will have complete details...without obligation.

1. Electronics Technology

A comprehensive program covering Automation, Communications, Computers, Industrial Controls, Television, Transistors, and preparation for a 1st Class FCC License.



NEW!

2. Broadcast (Radio & TV) Engineering

Here's an excellent studio engineering program which will get you a 1st Class FCC License. Now includes Video Systems, Monitors, FM Stereo Multiplex, Color Transmitter Operation, and CATV.




3. First Class FCC License

If you want a 1st Class FCC ticket quickly, this streamlined program will do the trick and enable you to maintain and service all types of transmitting equipment.



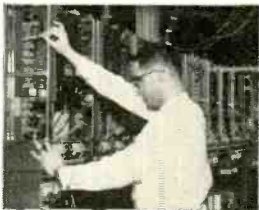4. Electronic Communications

Mobile Radio, Microwave, and 2nd Class FCC preparation are just a few of the topics covered in this "compact" program...Carrier Telephony too, if you so desire.



5. Industrial Electronics & Automation

This exciting program includes many important subjects such as Computers, Electronic Heating and Welding, Industrial Controls, Servomechanisms, and Solid State Devices.



NEW!

6. Electronics Engineering

A college-level course for men already working in Electronics... covers Steady State and Transient Network Theory, Solid State Physics and Circuitry, Pulse Techniques, Computer Logic, and Mathematics through Calculus.



ENROLL UNDER NEW G.I. BILL. All CIE courses are available under the new G.I. Bill. If you served on active duty since January 31, 1955, or are in service now, check box on reply card for G.I. Bill information.

An FCC License...or your money back!

In addition to providing you with comprehensive training in the area indicated, programs 1, 2, 3, and 4 will prepare you for a Commercial FCC License. In fact, we're so certain of their effectiveness, we make this *exclusive offer*:

The training programs described will prepare you for the FCC License specified. Should you fail to pass the FCC examination after completing the course, we will refund all tuition payments. You get an FCC License... or your money back!

CIE's AUTO-PROGRAMMED® lessons help you learn faster and easier

Cleveland Institute uses the new programmed learning approach. Our AUTO-PROGRAMMED® lessons present facts and concepts in small, easy-to-understand bits...reinforce them with clear explanations and examples. Students learn more thoroughly and faster through this modern, simplified method. You, too, will absorb...retain...advance *at your own pace*.

Lifetime job placement service for every CIE graduate...at no extra cost

Once enrolled with CIE, you will get a bi-monthly listing of the many high-paying, interesting jobs available with top companies throughout the country. Many Cleveland Institute students and graduates hold such jobs with leading companies like these: American Airlines, American Telephone & Telegraph, General Electric, General Telephone and Electronics, IBM, Motorola, North American Aviation, New York Central Railroad, Raytheon, RCA, and Westinghouse.

CIE lessons are always up-to-date

Only CIE offers new, up-to-the-minute lessons in all of these subjects: Logical Troubleshooting, Laser Theory and Application, Microminiaturization, Single Sideband Techniques, Pulse Theory and Application, Boolean Algebra.

Full accreditation...your assurance of competence and integrity

Cleveland Institute of Electronics is accredited by the Accrediting Commission of the National Home Study Council. You can be assured of competent Electronics training by a staff of skilled Electronics instructors.

CIE Cleveland Institute of Electronics
1776 East 17th Street, Cleveland, Ohio 44114

If card has been removed, mail this coupon for 2 FREE BOOKS

Cleveland Institute of Electronics
1776 East 17th Street, Cleveland, Ohio 44114

Please send me without cost or obligation:

- Your 40-page book "How To Succeed In Electronics" describing job opportunities in Electronics today, and how your courses can prepare me for them.
- Your book on "How To Get A Commercial FCC License."

I am especially interested in:

- | | | |
|--|--|--|
| <input type="checkbox"/> Electronics Technology | <input type="checkbox"/> Broadcast Engineering | <input type="checkbox"/> First Class FCC License |
| <input type="checkbox"/> Electronic Communications | <input type="checkbox"/> Industrial Electronics & Automation | <input type="checkbox"/> Electronics Engineering |

Name _____ Age _____

(PLEASE PRINT)

Address _____

City _____ State _____ Zip _____

Check here for G.I. Bill information

RE-55

Designed and manufactured in U.S.A.

NEVER A BURNOUT

IN 6 EMC DIODE-PROTECTED VOMS

NOBODY ELSE BUT EMC DESIGNS IN SO MUCH VALUE!
 • Professional quality and versatility • Lifetime protection against electrical abuse • No meter burn-out, needle damage, or fuse replacement

VOLOMETER


Model 109A Factory Wired & Tested \$28.95
 Model 109AK Easy-to-Assemble Kit \$21.15
 20,000 Ω/v DC sens. 10,000 Ω/v AC sens. $4\frac{1}{2}''$, 40 μ a meter. High impact bakelite case. 5 DC voltage ranges: 0-6-60-300-600-3000v. 5 AC voltage ranges: 0-12-120-600-1200-3000v. 3 DC current ranges: 0-6-60-600ma. 3 AC current ranges: 0-30-300ma; 0-3A. 3 resistance ranges: 0-20K, -200K, -20 megs. 5 db ranges: -4 to +67db. With carrying strap. $5\frac{1}{4}''$ W x $6\frac{3}{4}''$ H x $2\frac{7}{8}''$ D.

VOLOMETER

Model 103A Factory Wired & Tested \$20.75
 Model 103AK Easy-to-Assemble Kit \$16.80
 $4\frac{1}{2}''$, 2% accurate, 800 μ a D'Arsonval type meter. One zero adjustment for both resistance ranges. High impact bakelite case. 5 AC voltage ranges: 0-12-120-600-1200-3000v. 5 DC voltage ranges: 0-6-60-300-600-3000v. 5 db ranges: -4 to +64db. 5 AC current ranges: 0-30-150-600ma. 4 DC current ranges: 0-6-30-120ma; 0-1.2A. 2 resistance ranges: 0-1K, 0-1 meg. $5\frac{1}{4}''$ W x $6\frac{3}{4}''$ H x $2\frac{7}{8}''$ D.

POCKET SIZE VOLOMETER

Model 102A
 Factory Wired & Tested \$16.95
 Model 102AK Easy-to-Assemble Kit \$14.40
 $3\frac{1}{2}''$, 2% accurate 800 μ a D'Arsonval type meter. One zero adj. for both res. ranges. High impact bakelite case. 5 AC voltage ranges: 0-12-120-600-1200-3000v. 5 DC voltage ranges: 0-6-60-300-600-3000v. 3 AC current ranges: 0-30-150-600ma. 4 DC current ranges: 0-6-30-130ma; 0-1.2A. Resistance: 0-1K, 0-1 meg. $3\frac{3}{4}''$ W x $6\frac{1}{4}''$ H x $2''$ D.

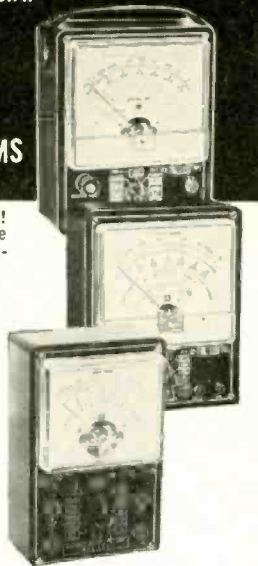

EMC, 625 Broadway, New York 12, N. Y.

Send me FREE catalog of the complete value-packed EMC line, and name of local distributor.

RE-12

NAME _____
 ADDRESS _____
 CITY _____ ZONE _____ STATE _____

EMC

ELECTRONIC MEASUREMENTS CORP.
 625 Broadway, New York 12, New York
 Export: Pan-Mar Corp., 1270 B'way, N. Y. 1

velocity meter of Fig. 16 or the drag-strip trap speedometer of Fig. 17. In the bullet meter, either photoelectric pick-offs or the usual screens may be used. By knowing the distance between the trips and the frequency of your reference clock, you can precisely calculate the time it takes for the bullet to travel through the screens, and then calculate the velocity. For instance, suppose we have a 4-ft screen separation, a 100-kHz clock, and a bullet causes a 200 reading on a three-place counter. Each clock pulse is spaced 10 μ sec from its nearest neighbor, so it apparently took 2000 μ sec or 2 msec for the bullet to travel four feet. Four feet in 2 msec is equivalent to 2000 feet per second.

The calculation is the same at the drag strip, only now we are dealing with a greater spacing and most likely, lower velocities.


Electronic piano tuner

The note is picked up with a contact microphone, and is this time to measure the time between zero crossings of the fundamental component of a piano note (Fig. 18). The note is picked up with a contact microphone, and is well filtered to pick out the fundamental frequency. It is then amplified and limited with a high-quality limiter. After the limiting, a binary divider chain octave selector reduces all the notes to square waves having a fundamental frequency between 28 and 56 Hz. A note detector [a monostable of some sort] resets the counting modules [four are needed for sufficient accuracy] and waits till the middle of the note. In the middle of the note, a synchronizer is told to produce a gate exactly two positive zero crossings wide. This routes a 250-kHz clock to the decimal counting modules, producing a number which is converted into frequency by consulting a conversion chart or table.


There are two important advantages to this method compared to conventional instruments. First, no skill at beat detection is required, and second, with a carefully calibrated chart, it is possible to "stretch" the piano tuning in exactly the manner a professional tuner does.

Frequency counters

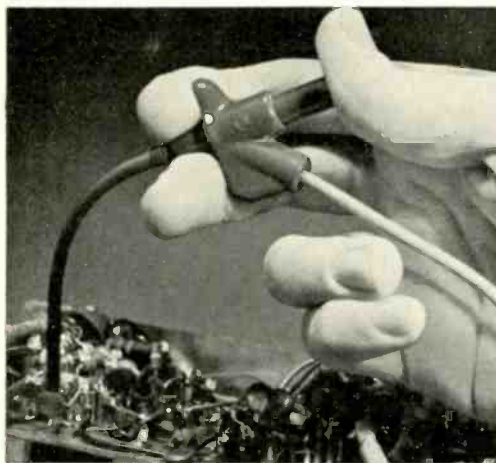it, you can measure any frequency from 10 MHz on. This is perhaps the most useful digital instrument. With



Clever Kleps 30

Push the plunger. A spring-steel forked tongue spreads out. Like this  Hang it onto a wire or terminal, let go the plunger, and Kleps 30 holds tight. Bend it, pull it, let it carry dc, sine waves, pulses to 5,000 volts peak. Not a chance of a short. The other end takes a banana plug or a bare wire test lead. Slip on a bit of shield braid to make a shielded probe. What more could you want in a test probe?

\$147



Available through your local distributor, or write to:

RYE INDUSTRIES INC.
 128 Spencer Place, Mamaroneck, N.Y. 10543

Circle 31 on reader's service card

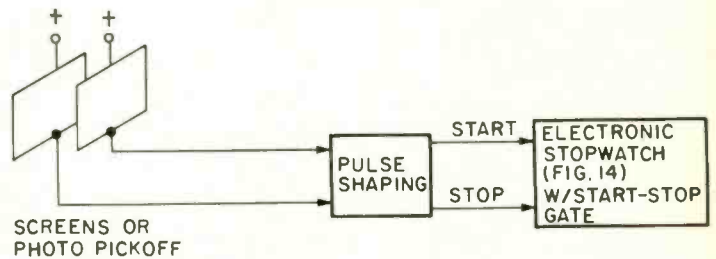


Fig. 16—Ballistic velocity meter needs a start-stop gate.



Fig. 17—Similarly, drag-strip speedometer measures time.

465



Customer Relations Specialist.

That's you. When you turn on your B & K tester / rejuvenator. A real customer pleaser (even the tough ones). At the same time, it ups your income and quickly pays for itself. This has been proved time and again:

First, by showing your customer, right in the home, the true condition of his picture tube. And how long it will last. (New picture tube sales are easier to justify when your customer is right there to see for himself.)

Second, by rejuvenating the picture tube, while your customer watches, relieved that he's been temporarily spared a major expense. You can do this as a part of your service or for an additional fee which you can offer to apply toward later purchase of a picture tube.



Third, by being able to test and repair all black & white and all color tubes, imports as well as American, in a few minutes. Without removing the picture tube from the TV set.

For shop use, of course, it's a must—for your customer's sake, or to validate your claim on an in-warranty picture tube.

Special B & K time-controlled rejuvenation-process safeguards the picture tube.

Adjustable heater voltage is metered and continuously variable from 0 to 13 volts. G-1 and G-2 voltages are completely and continuously variable.

All this enables you to pinpoint the desired voltage and make the most accurate possible tests, even on future CRT types.

Circle 35 on reader's service card


(How's that for non-obsolescence in an era of planned obsolescence?)

Color picture tubes are checked by testing each color gun separately just as the manufacturer would do it. (In fact, this CRT tester has become the commonly used diagnostic tool of the industry.)

The B & K 465 is the professional serviceman's tester.

If you would like to enlist the aid of this "customer relations specialist," see your B & K Distributor or drop us a note and ask for Catalog AP-24.

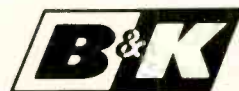**CRT Tester/Rejuvenator
Model 465 Net: \$89.95**



B & K Division of DYNASCAN CORPORATION
1801 W. Belle Plaine · Chicago, Illinois 60613
Where electronic innovation is a way of life.

DECEMBER 1968

WPEK
68-69 70 ← ALLEN FLAME

DON'T MISS... POLICE and FIRE ACTION

PERFECT FOR INDUSTRIAL, COMMERCIAL and GOVERNMENT USE



DUAL CONVERSION
SMALL SIZE • LOW POWER DRAIN
• HIGH STABILITY • CRYSTAL CONTROLLED

Specifically designed for simplicity of operation... efficiently engineered to give you years of service. Fits the smallest auto yet powerful enough to deliver a clear signal. Operates on 6 crystal controlled frequencies. Dual limiter & Foster Seeley discriminator. Quadruple tuned RF stage for greater image rejection. Noise Free squelch, PLUG IN crystals for instant frequency change. Compatible with major continuous tone systems. Operates on 117VAC and 12VDC. Size: 6 7/8" x 2 3/8" x 8 1/2". Wt. 3 lbs. 8 oz.

FR-104
(30-50 MHz) **\$140.00** Complete with AC and DC power cables, mounting bracket, less crystals.
FR-105
(150-175 MHz) Crystals \$5.00 ea.

SONAR RADIO CORPORATION
73 Wortman Ave., Bklyn, N.Y. 11207 Dept. 802
Please send me information on Model FR-104/105 FM Monitor Receivers.

Name
Address
City Zone State

LISTEN TO: POLICE, FIRE and WEATHER REPORTS!



Perfect for Industrial, Commercial, Utility and Government Use
SONAR SENTRY VHF MONITOR RECEIVERS

Designed and engineered for simplicity of operation, compact enough to fit a shirt pocket yet powerful enough to deliver a clear clean signal—it's dependable • Operates on two crystal controlled VHF channels plus broadcast band • Completely solid state for long life use • Visible battery indicator to show battery condition at all times • Built in antenna • 5 7/8" H x 2 1/2" W x 1 1/8" D. Wt. 11 oz.

FR-103
150-175 MHz
FR-106
30-50 MHz
\$39.95
With Battery, Earphone, & less Crystals
Crystals \$5.00 ea.

SONAR RADIO CORPORATION
73 Wortman Ave., Bklyn, N.Y. 11207 Dept. 802
Please send me information on Model VHF Monitor Receivers.


Name
Address
City Zone State

Circle 36 on reader's service card

EQUIPMENT REPORT

Heathkit Band Box and Playmate

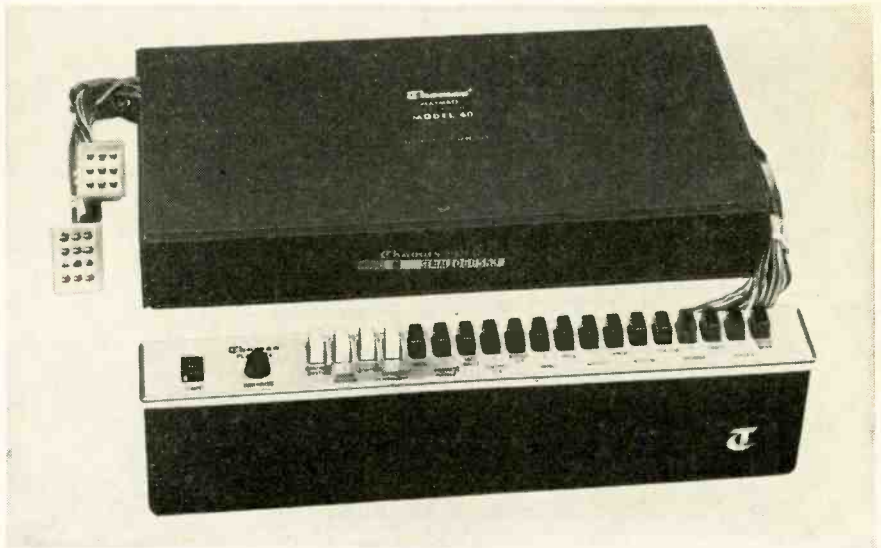For manufacturer's literature, circle No. 37 on Reader Service Card.



By FRED SHUNAMAN

WHEN THE OPPORTUNITY CAME TO add the Band Box and Playmate to the "Thomas by Heathkit" organ my daughter Ellen and I had put together two years ago, I was interested. The additions would, in effect, make it a theater organ, and I had played around a little with an ancient theater-type organ of the pre-electronic days. It must have been about 30 feet long, and it played the actual instruments (enclosed in glass-fronted compartments), pounding on the bass drum and striking cymbals together on command of a perforated paper music roll.

Ellen was enthusiastic—again. "A Viennese waltz with bongo drums!" The very incongruity appealed to her. "I'd like to play that!" But I noted carefully that her enthusiasm didn't include a promise to "do all the work," as it had when we built the organ.

What were the Band Box and Playmate I was ordering? Briefly, the Band Box is a way of adding—electronically—ten percussion instruments to the Heathkit organ. These can be played together with the regular note from either the great keyboard or the pedals.

Two of the ten percussion voices—the drum roll and castanets—sound continuously as long as the key is held down; the others sound once each time the key is pressed. Any combination of the ten (crash cymbal, brush cymbal, bass drum, snare drum, drum roll, two bongos, block, clave and castanets) may be played at the same time, on either pedals or keyboard or—in one

position of the switch—on both at the same time. Thus you can have the crash cymbal and bass drum sound when you press the pedal, while actuating one or more of the others with the keys. (Drum roll and snare drum do *not* sound at the same time.)

The Band Box has its own keyboard—a set of fingertip tabs that can be played independently of the organ. So you can use it to accompany other instruments or as part of a dance ensemble where the rock might be considered too hard for organ music.

A little drawer that slides under the knee rail of the GD-983 organ houses the Band Box, or it can be installed integrally in the newer TO-67. The electronic part consists of three circuit boards mounted in a flat frame that also mounts under the great manual shelf on the GD-983 or installed inside the newer-model organ.

Playmate

And what is the Playmate? Automation applied to the Band Box! With the Playmate installed and connected to the Band Box and organ, a supply of rhythms ranging from the Viennese waltz to the watusi can be created. Tempo can be varied with a thumb wheel on the Playmate. Pushing down the key marked ORGAN RHYTHM and not using any of the Band Box voices, you can have a simple percussive organ note repeated in the desired rhythm.

Adding any Band Box voice lets you add any of the instruments to the keyboard note. For automatic accom-

Coming in January, 1969:

PHOTOFACT[®] SET NO. 1002

When the first PHOTOFACT Folder Set appeared in May, 1946, we made this pledge to the radio servicemen of America:

"PHOTOFACT will provide complete, accurate, uniform service data, and present that data on a current and continuing basis, to keep up with the production of the industry."

We have kept that pledge. We covered all of the post-war AC-DC, AM-FM, Auto Radio, and Phonograph models. With the appearance of the first black-and-white TV, we were there with exclusive PHOTOFACT TV coverage. We kept pace as the industry introduced new types of products and poured them out in thousands of models: Automatic Record Changers, High-Fidelity Instruments and Components, Tape Recorders, Stereo Instruments, Transistor Radios, Color TV, Citizens Band Radios—right down to the introduction in 1968 of PHOTOFACT coverage of Home Cartridge Tape Players.

Today, the electronic serviceman has at his command complete PHOTOFACT service data coverage of more than 78,000 different models.

Moreover, the electronic serviceman can buy PHOTOFACT in the form which best meets his needs. Those who service all types and makes of instruments own the complete PHOTOFACT Library and stay current with a subscription to P. O. M. (Photofact-of-the-Month Club). Those who have a need for specialized service data, have the choice of subscriptions to the five Specialized PHOTOFACT Series: Auto Radio, Tape Re-

recorder, Transistor Radio, CB Radio, and Home Cartridge Tape Players.

We made a second pledge in 1946: "PHOTOFACT will be the world's finest and most complete electronic service data, providing new and exclusive features in a uniform format, to make the serviceman's work quicker, easier, and more profitable."

We have kept that pledge. PHOTOFACT introduced full photo coverage of all chassis views, keyed to the famous Standard Notation Schematic, with its wealth of vital information; disassembly instructions (including auto radio removal); tube location charts; troubleshooting charts; a superior alignment system; terminal identification; dial cord stringing; field servicing notes; alternate tuner data; complete replacement parts lists; exploded views for record changers and tape recorders; actual waveform photographs on the TV schematics, and a host of other invaluable features. With the appearance of printed circuitry, PHOTOFACT introduced CircuiTrace[®] for fast tracing of printed boards. Forthcoming PHOTOFACT Folders will feature techniques for rapid servicing of such new developments as the "Quasar" circuit TV models.

In January, 1969, PHOTOFACT Set No. 1002 will appear. It is eloquent testimony to the continuous loyalty of thousands of electronic servicemen, and solid proof of the ability of PHOTOFACT to boost their earnings day-in and day-out through faster, better repairs.

One final word: In 1946, a PHOTOFACT Set sold for \$1.50. Today, twenty-two years later, on a P. O. M. Subscription, PHOTOFACT costs only 50c more per Set. Think about it, and you'll agree that's holding the line.

PHOTOFACT is sold by more than 1800 Electronic Parts Distributors from coast-to-coast

Howard W. Sams & Co., Inc.

INDIANAPOLIS, INDIANA 46268

The Service-Minded Organization with the Service Technician in Mind

**Put your
electronic
know-how to work
in the lucrative security
business**

Dialalarm, the automatic telephone alarm, can be programmed to dial pre-selected numbers and deliver a pre-recorded emergency message. Any sensor can trigger Dialalarm. A rate-of-rise indicator can be used to call the fire department; a motion detector (microwave, ultrasonic, etc.) can trigger a message to the police department. A single alarm can be activated by two different sensors because the unit has two channels. And each channel is capable of delivering 6 different messages to 6 different numbers. There is a total of 10 minutes of message time on each channel. Other advantages: no leased lines are required, for economy; the owner can program it and change messages on the spot. There's no need to bring the unit to the dealer—a drawback of other dialing alarms.

Your electronic know-how opens the door to an excellent income in the growing security field. You can discuss the product with confidence; suggest ways of installing it for most effective protection; tie it into existing security systems. Easy to install, it has the approval of police and fire departments and local telephone companies. For details on how to put your skill in electronics to work in a lucrative field, write: **Record-O-Fone** Division of Electro-space Corp., 408 Concord Ave., Bronx, N.Y. 10454.

Patents Pending

Dialalarm
by **Record-O-Fone**

Circle 39 on reader's service card

paniment, release the **ORGAN RHYTHM** button, push down **BAND BOX RHYTHM**, and away you go . . . the rhythm continues ad infinitum, until you stop it. Any or all of the voices can be used.


If you leave **BAND BOX RHYTHM** on and push down the **TOUCH CONTROL** button, the Band Box rhythm is heard only as long as the organ key (or pedal) is held down, the organ giving forth with its own steady note meanwhile. There is a **DOWN BEAT ACCENT** button, and a down beat indicator lamp that flashes at the beginning of each measure.

The number of combinations is almost infinite and most fascinating. You can even play the great keyboard without any of the voicing stops down; thus producing no music, but controlling the Band Box rhythm with the organ keys. Other interesting effects can be produced by pressing down two rhythm buttons at the same time, like adding rock beat to waltz tempo.

Actual construction is easier than it looks. One of the three Band Box boards is already assembled. Work progresses rapidly on the others. Every time I get a new kit, there are improvements, either in the actual kit, in the instructions or in both. (So, if each job seems easier, it is not practice alone that is responsible.) **R-E**

The best TV deserves the best antenna!

Install a Zenith Quality-Engineered Antenna!

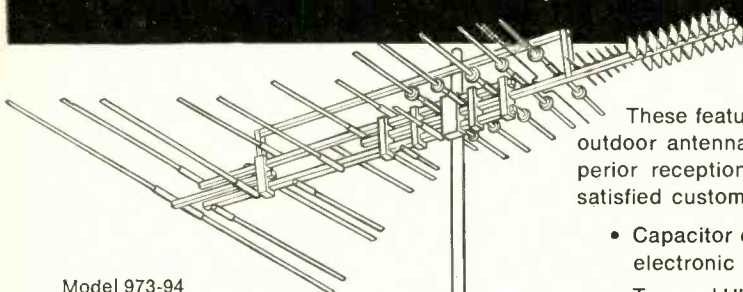

Model 973-94
designed for far fringe areas

These features help a Zenith outdoor antenna provide the superior reception that makes for satisfied customers:

- Capacitor coupled cap-electronic VHF dipoles.
- Tapered UHF grid driver.
- Staggered square UHF directors.
- Low-impedance, triple boom construction.

You can choose from 12 all-new Zenith VHF/UHF/FM or VHF/FM antennas. All are gold color alodized aluminum for better conductivity, greater corrosion resistance and longer service.

Ask your Zenith distributor for a free technical manual. He has charted the reception characteristics of your area, so he can recommend the best antenna for each installation.


Exciting Surprises
for You—
and Your Family!
Fun for all!
Get the details
at your Zenith
Distributor's
Parts Department.



BEST YEAR YET TO SELL THE BEST

ZENITH
The quality goes in
before the name goes on

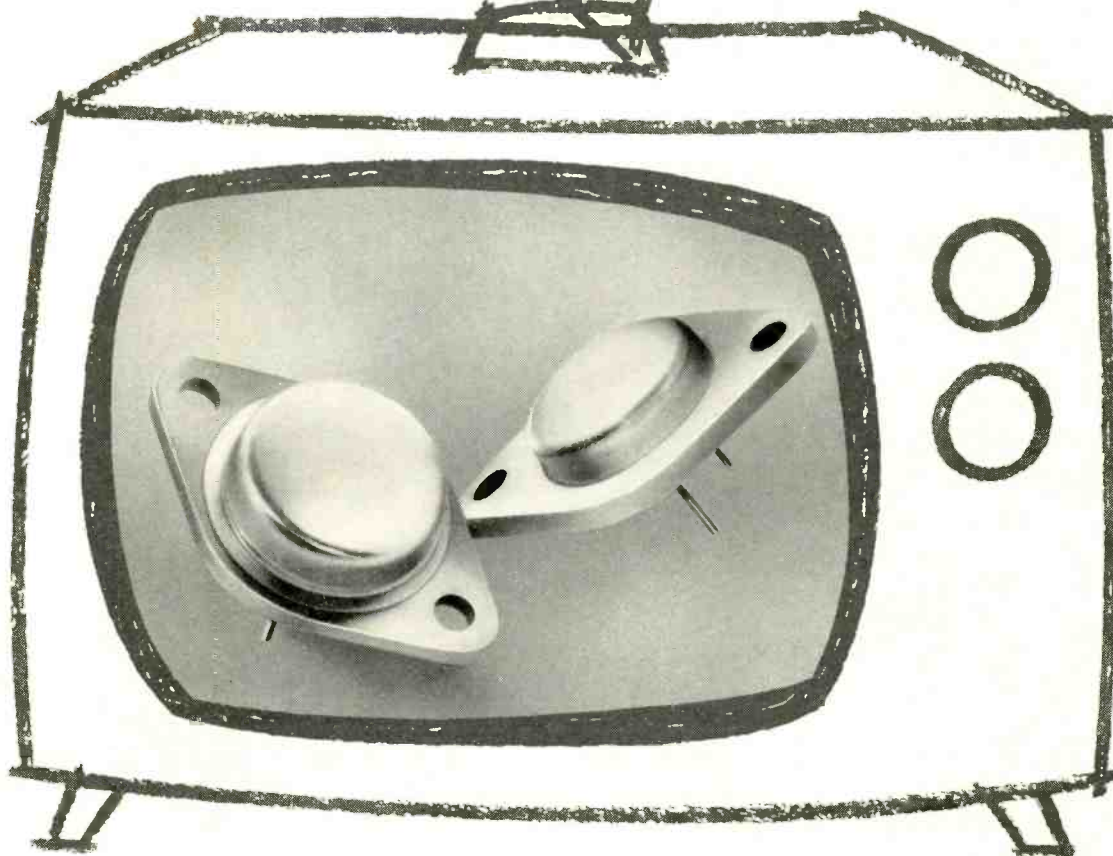Two New SK Devices Simplify Servicing of TV Deflection Circuits



More than a dozen solid-state TV sets—RCA and others—can use these two new RCA SK-Series transistors—specifically designed for replacement use in deflection circuits.

The RCA SK3034 is for replacement use in horizontal driver and in vertical-deflection-output circuits; the SK3035 is for replacement use in horizontal-deflection-output circuits.

Both units are germanium p-n-p devices in hermetically-sealed TO-3 packages, and are for use in domestic and imported TV sets with anode voltages to 18 KV and with picture tubes having deflection angles up to 114°.

Add both to your stock of RCA "Top-Of-The-Line" SK-Series replacement transistors. See your RCA Distributor today about your supply of RCA SK-Series replacements . . . 33 individual units that can replace approximately 11,800 solid-state devices.

RCA Electronic Components, Harrison, N. J. 07029.

Circle 41 on reader's service card

Now available . . . a comprehensive and accurate source of solid-state replacement information! It's RCA's Solid-State "Top-of-the-Line" Replacement Guide, SPG-202F. Cross-referencing RCA SK-Series Transistors, Silicon Rectifiers, and Integrated Circuits, the Guide provides replacements for nearly 12,000 solid-state devices—including U.S. industry standard EIA types, foreign types, and types identified only by device-manufacturers' or equipment manufacturers' parts numbers. SPG-202F is available through your RCA Distributor. Ask him about it. Today.

**Ask your participating RCA Distributor for details.*

RCA

RADIO-ELECTRONICS READER SERVICE

Here's how you can get manufacturers' literature fast:


1. Tear out the post card on the facing page. Clearly print or type your name and address. **Include zip code!**
2. Circle the number on the card that corresponds to the number appearing at the bottom of the **New Products, New Literature** or **Equipment Report** in which you are interested.
For literature on products **advertised** in this issue, circle the number on the card that corresponds to the number appearing at the bottom of the advertisement in which you are interested. Use the convenient index below to locate quickly a particular advertisement.
3. Mail the card to us (no postage required in U.S.A.)

ALLIED RADIO CORPORATION (p. 92)	Circle 128
ARCTURUS ELECTRONICS CORPORATION (p. 94)	Circle 134
B & K (Division of Dynascan Corporation) (p. 17)	Circle 19
B & K (Division of Dynascan Corporation) (p. 71)	Circle 35
BROOKS RADIO AND TV CORPORATION (p. 91)	Circle 127
BURSTEIN-APPLEBEE COMPANY (p. 70)	Circle 34
CARINGELLA ELECTRONICS, INC. (p. 92)	Circle 130
CASTLE TV TUNER SERVICE, INC. (p. 7)	Circle 11
CLEVELAND INSTITUTE OF ELECTRONICS (p. 62-65)	Circle 30
(Slide Rule) (p. 16)	Circle 17
COLETRONICS (p. 92)	Circle 131
CORNELL ELECTRONICS (p. 96)	Circle 139
DELTA PRODUCTS, INC. (p. 12)	Circle 13
DELTA PRODUCTS, INC. (p. 26)	Circle 24
EDMUND SCIENTIFIC COMPANY (p. 95)	Circle 136
FAIR RADIO SALES (p. 93)	Circle 133
FINNEY COMPANY (p. 27)	Circle 25
GAVIN INSTRUMENTS, INC. (Subsidiary of Advance Ross Corporation) (p. 93)	Circle 132
GRANTHAM SCHOOL OF ELECTRONICS (p. 1)	Circle 8
HEALD COLLEGES (p. 6)	Circle 10
HEATH COMPANY (p. 84-87)	Circle 111
INTERNATIONAL CRYSTAL MFG. COMPANY (p. 98)	Circle 149
INTERNATIONAL RESISTANCE CORPORATION (p. 88)	Circle 112

E. F. JOHNSON COMPANY (p. 81)	Circle 107
JERROLD ELECTRONICS CORPORATION (Distributor Sales Division) (p. 53)	Circle 26
JUDSON RESEARCH AND MANUFACTURING COMPANY, INC. (p. 91)	Circle 126
KARLSON RESEARCH AND MANUFACTURING (p. 89)	Circle 121
KENZAC COMPANY (p. 94)	Circle 135
LAFAYETTE RADIO ELECTRONICS (p. 80)	Circle 108
LEADER TEST INSTRUMENTS (p. 54)	Circle 27
LECTROTECH, INC. (p. 67)	Circle 32
LORAL DISTRIBUTOR PRODUCTS (Division of Loral Corp.) (p. 55)	Circle 28
MERCURY ELECTRONICS CORPORATION (p. 79)	Circle 106
MICROFLAME, INC. (p. 70)	Circle 33
MULTICORE SALES CORPORATION (p. 90)	Circle 124
MUSIC ASSOCIATED (p. 91)	Circle 125
MYRIAD PRODUCTS CORPORATION (p. 90)	Circle 123
OLSON ELECTRONICS, INC. (p. 89)	Circle 122
PACE COMMUNICATIONS (p. 14)	Circle 16
PERMA-POWER COMPANY (p. 82)	Circle 109
PIONEER ELECTRONICS U. S. A. CORPORATION (Cover III)	Circle 150
POLY PAKS (p. 97)	Circle 140
RCA ELECTRONIC COMPONENTS Semiconductors (p. 75)	Circle 41
Test Equipment (p. 24-25)	Circle 23
RECORD-O-FONE (Division of Electro Space Corporation) (p. 74)	Circle 39
RYE INDUSTRIES, INC. (p. 66)	Circle 31
SAMS & COMPANY, INC. HOWARD W. (p. 12)	Circle 14
SCHOBER ORGAN CORPORATION, INC. (p. 16)	Circle 18
SCI ELECTRONIC IGNITION (p. 92)	Circle 129
SCOTT, INC., H. H. (p. 23)	Circle 100
SENCORE (p. 83)	Circle 110
SHURE BROTHERS, INC. (p. 13)	Circle 15
SOLID STATE SALES (p. 95)	Circle 137
SONAR RADIO CORPORATION (p. 72)	Circle 36
TRIPLETT ELECTRICAL INSTRUMENT COMPANY (Cover II)	Circle 7
WARREN ELECTRONIC COMPONENTS (p. 96)	Circle 138
XCELITE, INC. (p. 22)	Circle 21
ZENITH (p. 74)	Circle 40

NEW PRODUCTS

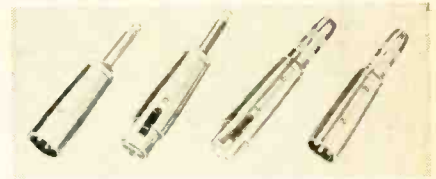More information on new products is available free from the manufacturers of items identified by a Reader's Service number. Turn to the Reader Service Card facing page 76 and circle the numbers of the new products on which you would like further information. Detach and mail the postage-paid card.



COLOR ORGAN SYSTEMS control groups of colored lamps which respond to a certain frequency band and blink in variety of brightness to the intensity of the music. Smallest, *Model 1900*, weighs 24 oz. Costs \$39.95. *Model 71,102*, 200 W, features an indicator light and brightness control for each channel as well



as a master control. Costs \$99.95. *Model 71,104*, 1000 W, has base, treble and mixer controls and features both line input and a built-in mike for \$149. Above units are all 3-channel. *Model 71,103*, 2000 W, 4-channel, includes gain controls and weighs 10 lb 11 oz. Costs \$195. Single-channel Do-It-Yourself Kit, *Model 60,759*, costs \$9.95.—Edmund Scientific Co.

Circle 46 on reader's service card

STEREO HI-FI SYSTEM, solid-state *RK-570*, combines a 12-watt FM receiver, 4-speed record player and a cassette tape recorder for recording and playing 4-track stereo or 2-track mono. Two detached, acoustically matched 2-way speaker systems, each containing a 5" woofer and 3" tweeter. FM section fea-



tures an FET front end at 2.5 μ V (IHF) sensitivity. Amplifier is rated at 12 watts output into 8 ohms with a response of 20-30,000 Hz \pm 2 dB. \$249.95. Plastic cover and mike available at \$7.95 and \$5.95, respectively.—Lafayette Radio Electronics.

Circle 47 on reader's service card

AUDIO CONNECTOR ADAPTERS, four models. Nos. 383P1 and 384P1 accept a standard 2-conductor phone plug and adapt it to a 3-contact audio connector. The former adapts phone plug

to a 3-pin receptacle, and the latter to a 3-contact connector. The other two adapters connect a standard 2-conductor jack to a 3-contact audio connector. No. 386P1 adapts the jack to a 3-pin re-

DISGRACEFUL

“Isn't it? The way Mercury shamelessly offers top quality test equipment at such low prices. Compare the features with costlier models and see how Mercury gives you top value for your dollar. It's Wonderful.”



Model 2000—MUTUAL CONDUCTANCE TUBE TRANSISTOR TESTER

Tests all tube types, old and new, plus transistors. Tests Magnovals, Nuvistors, 10-pin Decals, Compactrons, Novars, 10-pin types, foreign and hi-fi tubes, thyratrons and industrial types. Tests for true dynamic mutual conductance (GM). Spots shorts, leakage and gas. Tests Color and B/W picture tubes with use of MH-3A Multi-Head Adapter (optional). Lever switch test principal overcomes obsolescence. Automatic line voltage regulation.


\$109⁹⁵



Model 1101—DELUXE TUBE TESTER

For new Magnovals, Decals, Nuvistors, All Popular Picture Tubes and most other receiving tube types. Checks tubes for dynamic cathode emission, shorts, grid leakage and gas. Picture Tube Adapter. Exclusive 2-point test principle safeguards against obsolescence.

Kit—\$39⁹⁵ / Wired—\$69⁹⁵

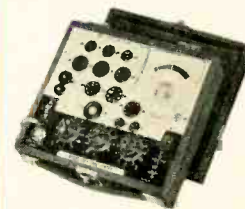

Model 1100B—TUBE TESTER

Tests more tube types than any other tester in its price range. Tests for dynamic cathode emission, shorts, grid leakage and gas. Exclusive meter bridge circuit found only in more expensive testers. Professional quality at an economical price.

Kit—\$24⁹⁵ / Wired—\$39⁹⁵

ALL MERCURY TEST EQUIPMENT GUARANTEED FOR ONE FULL YEAR!
UPDATED TUBE TEST DATA AVAILABLE ON ALL UNITS.



MERCURY ELECTRONICS CORPORATION

315 ROSLYN ROAD, MINEOLA, N. Y. 11501 • (516) 742-5400


CANADA: WILLIAM COHEN CORP., 8900 PARK AVE., MONTREAL 11

EXPORT: SINGER PRODUCTS CO., INC., 95 BROAD ST., N. Y. C. 10004, U. S. A.

ceptacle, while No. 387P1 adapts to a 3-contact receptacle. All units include a separate ground terminal and ground contactors. All completely shielded.—Switchcraft Inc.

Circle 48 on reader's service card

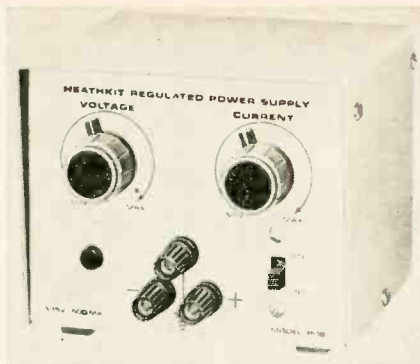
REGULATED POWER SUPPLY, Model IP-18, can be programmed for ac or dc. Voltage is regulated to a 40-mV variation; output change: less than .05%; input change: from 105–125 Vac. The unit is current-limiting and continuously variable from 10 to 500 mA. Noise distortion: under 0.1 mV; transient response time: 25 μ sec. Output impedance is 0.5 ohm or less up to 100 kHz. The all-silicon tran-



sistor power supply and circuit board construction. \$19.95.—Heath Co.

Circle 49 on reader's service card

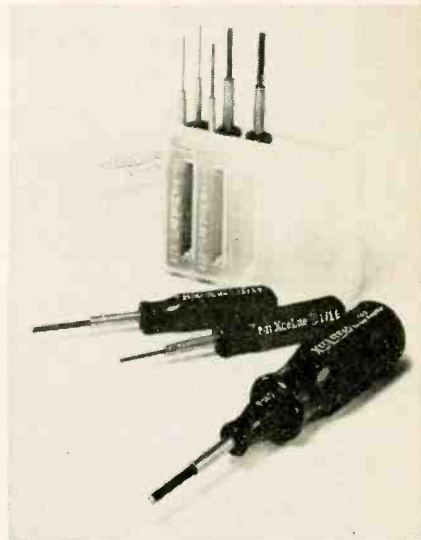SCREWDRIVER SET, No. PS-89, contains 8 midjet hex-type socket screwdrivers in sizes from 0.028" to 3/8". Included is a "piggyback" torque amplifier handle to provide larger gripping surface, extended reach and increased driving pow-



er. Useful with drivers for precision work. Housed in a sturdy, compact, see-through plastic case which can be carried in a hip pocket or used as a bench stand.—Xcelite Inc.

Circle 50 on reader's service card

FREE!



**BRAND NEW EDITION
1969 Catalog 690**

Serving The Public
Since 1920

Featuring Everything in Electronics for
● HOME ● INDUSTRY ● LABORATORY
from the "World's Hi-Fi & Electronics Center"



Over 500 Pages

- Electronic Parts...Tubes... Tools
- Citizens Band Equipment
- PA Equipment
- Test Instruments
- Closed Circuit TV
- Stereo Hi-Fi Systems & Components
- Tape Recorders
- Amateur Radio Equipment
- Radio & TV Sets & Accessories
- Cameras & Supplies
- Books

REALISTIC WALKIE-TALKIE LINE, six models: TRC-1B, 100 mW; TRC-35 (illus.), 1 W; TRC-45, 2 W. All are single-channel. TRC-25A, 100 mW, dual-channel with separate speaker and mike. TRC-99A, 3 W, 3 channels; TRC-100, 5 W, 6 channels. Prices range from \$13.95 to \$99.95. All models come with batteries, telescopic antenna and crystals for CB channel 11. 1–5-W units include a carrying case.—Radio Shack.



Circle 51 on reader's service card

LAFAYETTE RADIO ELECTRONICS

Dept. 17128

SYOSSET, L.I., N.Y. 11791

Send For **FREE**
1969 Catalog
TODAY!

Send **FREE** 1969 Catalog 690 Dept. 17128

Name.....

Address.....

City.....State.....Zip.....

Circle 108 on reader's service card




80

RADIO-ELECTRONICS

to 20,000 Hz, both channels operating. IM distortion is less than 0.2% at 120 watts or any lower power level. Noise is 85 dB below rated output from high-level inputs, 72 dB from low-level inputs. Special features include concentric bass and treble controls for optimum response from both channels and built-in stereo balancing system. \$435.—James B. Lansing Sound Inc.

Circle 52 on reader's service card

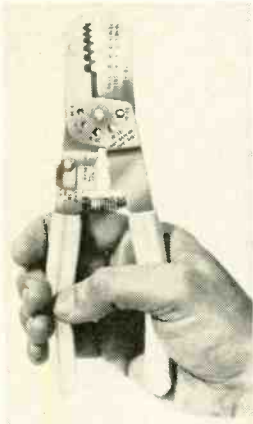


BIG-7 WIRING TOOL, made of steel, measures 8" and weighs 7 oz. Stripping holes are precision-ground to strip size No. 18 solid or stranded through No. 6 solid and No. 8 stranded wire. Blades cut aluminum and copper conductors, including UF

and Romex cable. Bolt buster cuts 4-40, 6-32, 8-32, 10-32 and 10-24 unhardened machine screws. Insulated or plain terminals and connectors from Nos. 22-10 can be crimped. Handles have large Hand-eze grips and the two halves are held by a Sta-Fast adjustable bolt. Under \$5.—Holub Industries Inc.

Circle 53 on reader's service card

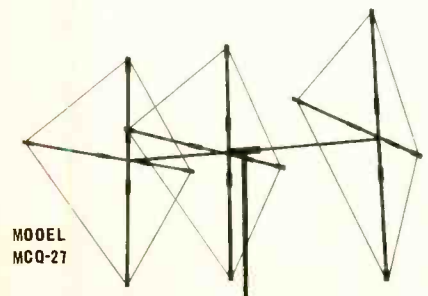ANTENNAS, two models: Model GA-3 (Gamma 232), is a 3-element Yagi, comes with all its parts preassembled and color-




coded and has a forward gain of 7.5 dB (over reference dipole); maximum length: 141" and boom length 108".

Model MCQ-27 (CB Cubical Quad) has a forward gain of 9 dB and boom length of 14'. Both units are unidirectional with a front-to-back ratio of 25 dB; SWR of 1/5/1 or better; feed-point impedance: of 52 ohms. Three elements.—Mosley Electronics Inc.

Circle 54 on reader's service card

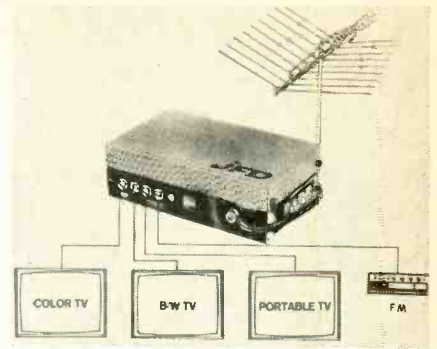PROGRAM CENTER SYSTEM, solid-state, amplifies signals from a single rooftop antenna and distributes them throughout the home. Handles up to 4 TV sets; can be expanded for 8 or more. Five models: PC4312-CD covers vhf (channels 2-13) and FM only, using twin-lead. Similar PC4712-CD uses co-



axial cable. PC4382-CD covers vhf, FM and uhf, using twin-lead. Coax version of this model is PC4782. PC4500-CD is

NEW ...a 23 channel base station offering the best of Johnson's experience!

\$199⁵⁰ \$214⁹⁵
(without mike) (with mike)

Brought to you by the same engineering team that designed the famous Messengers "I" and "Two", the Messenger 223 has the same rugged circuitry and even greater "Talk Power" capability. With at least 15 db more audio gain than the "I" and "Two", the "223" punches out a clear, penetrating signal. As with all Johnson radios, your signal will stand out compared to all others.

Ten tubes, eight diodes and six transistors form a rugged base station transceiver that can't be beat for reliable day-in, day-out performance. A built-in illuminated "S" meter /power meter measures input strength of RF signals and relative power output of the transmitter. Ready to go on all 23 channels, the Messenger 223 is FCC Type Accepted and DOT Approved.

See your Johnson dealer today for complete details!

E. F. JOHNSON COMPANY
2374 Tenth Ave. S.W., Waseca, Minnesota 56093


Providing nearly a half-century of communications leadership

Circle 107 on reader's service card

a combined twin-lead and coaxial unit. Prices range from \$30 to \$65.—JFD Electronics Co.

Circle 55 on reader's service card

KEYBOARD SWITCH, Model SB-033, suitable for test equipment, communication gear and many other applications has the following features: Rating—100 mA @ 48 V, Operating force—5 oz. Mechanical life—1,000,000 cycles; electrical life, 10,000,000 cycles. Full stroke travel 7/32", travel contact 5/32" and 3/16" high black symbols. All switch positions contain a "positive lockout" between sections and rows. An extra "decimal" button

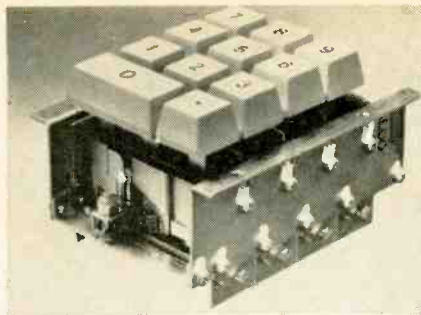

provided. \$28.50.—Alco Electronic Products Inc.

Circle 56 on reader's service card

CB TRANSCEIVER, Model CWT-10, 100 mW, 11 transistors, 3 channels. Unit puts out and pulls in clear signals. No license required. Crystals supplied for channel 9. Other features include beep-tone call-in, strong-signal limiter, separate mike and speaker, squelch control, battery-life meter, earphone jack and external power jack. Measures 10 1/4" x 1 3/8" x 2 3/4" and weighs 1 1/2 lb. \$29.95 with earphone, hand strap and shoulder strap.—Courier Communications Inc.



Circle 57 on reader's service card

easy answers to common color complaints

Perma-Power puts back Color TV Quality!



Puts back brightness

Color-Brite Picture Tube Briteners

Color-Brite brings out lost sharpness and details of fading color picture tubes. Provides increased filament voltage to boost electron emission, returns full contrast and color quality.

MODEL C-501 for round tubes
Dealer Net. \$5.85
MODEL C-511 for rectangular tubes
Dealer Net. \$5.85

Puts back black-and-white

Color-Brite Isolation Briteners

No Boost. Corrects for cathode-to-filament short causing loss of black and white video drive. Isolates the short, restores the black and white information that gives the color picture its quality.

MODEL C-502 for round tubes
Dealer Net. \$7.25
MODEL C-512 for rectangular tubes
Dealer Net. \$7.25

Puts back full voltage

Automatic Voltage Regulator

Automatically boosts voltage 10 volts when line voltage drops below 110 volts. Eliminates shrinking, loss of brightness, loss of convergence. Combats poor line voltage regulation, overloaded circuits.

MODEL D-210 for appliances rated up to 400 watts
Dealer Net. \$14.95

Put Back Profit—Use Perma-Power Briteners


Free technical literature on request

Perma-Power COMPANY
Division of Chamberlain Manufacturing Corp.

5740 North Tripp Ave. Chicago, Ill. 60646
Phone: (312) 539-7171

Circle 109 on reader's service card

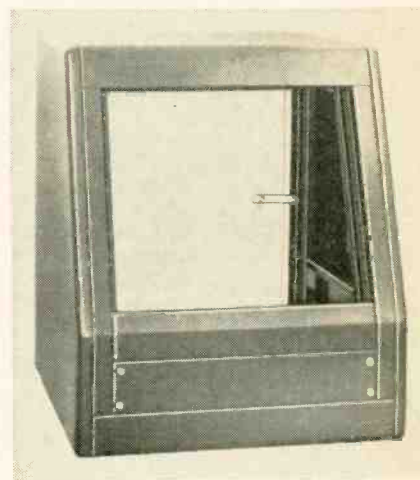CONVERTIBLE CABINET provides a rugged enclosure for delicate instruments and systems and can be placed on a table or bench or on top of a cabinet. All-welded 14-gauge steel frame has ad-



justable front and rear mounting rails tapped 10-32 with W.E. spacing. In 3 sizes with several optional construction features.—Bud Radio Inc.

Circle 58 on reader's service card

AM-FM FM-MPX RECEIVER, Model RA-999, 150 W, has a tuning range of 88-108 MHz FM/535-1605 kHz AM. Sensitivity: 1.5 μ V for 30 dB quieting. Stereo separation: more than 30 dB. Frequency response: 30-20,000 Hz \pm 3 dB.



Tone compensation: bass, 50 Hz \pm 12 dB; treble, 10 kHz \pm 10 dB. Hum and noise: -55 dB. Output impedance: 4, 8 and 16 ohms. Transistors: 25 plus 14 diodes. Size: 18 7/16" x 14 1/4" x 5 1/4". 110-120 volts ac, 50/60 Hz. \$250 with a walnut-finish wood cabinet.—Olson Electronics Inc. R-E

Circle 59 on reader's service card

END

NEW LITERATURE

All booklets, catalogs, charts, data sheets and other literature listed here with a Reader's Service number are free for the asking. Turn to the Reader's Service Card facing page 76 and circle the numbers of the items you want. Then detach and mail the card. No postage required!

LIGHTING GUIDE, LG-468, consists of four main sections, designed to aid in the selection of lamps and lamp holders best suited to particular applications or products. Sections are titled Lamp Selection Guide, Lampholder Selection Guide, Bracket Guide and a Condensed Catalog. Detailed drawing and specs provided.—**Leecraft Mfg. Co.**

Circle 60 on reader's service card

175 SEMICONDUCTORS, books and accessories in the Motorola HEP line of devices for hobbyists, experimenters and professional service techs are listed in *Catalog MHA27-4*. Of special interest to technicians is the "Equal-or-Better" replacement series.—**Motorola Semiconductor Products Inc.**

Circle 61 on reader's service card

BOOK CATALOG, 16 pages, describes over 100 current and forthcoming books covering broadcasting, basic technology, CATV, electric motors, electronic engineering, television, radio and electronics servicing, audio and hi fi, hobbies and experiments, test instruments and transistors.—**Tab Books**

Circle 62 on reader's service card

CROSS-REFERENCE GUIDE, HMA07-4, 64 pages, lists almost 18,000 semiconductors with their equivalents from the HEP line as well as tips on using replacement devices and outline drawings and dimensions. For hobbyists, experimenters and professional service technicians.—**Motorola Semiconductor Products Inc.**

Circle 63 on reader's service card

LOUDSPEAKER SYSTEMS. Three models in the Row 10 Series, *LS-10*, *LS-20* and *LS-30*, designed to reproduce music in livingrooms, not test tones in anechoic chambers, are described with frequency charts, pictures and specs in *Catalog No. 549*.—**Bogen Communications Div.**

Circle 64 on reader's service card

AUDIO CATALOG NO. 680, 20 pages, illustrated with diagrams and charts, contains technical data on magnetic heads for drum, disc or tape uses. Application form provided for information on any desired magnetic head not listed.—**Michigan Magnetics, Div. of VSI Corp.**

Circle 65 on reader's service card


Write direct to the manufacturers for information on items listed below:

ELECTRONIC COMPONENTS AND EQUIPMENT of over 500 major product lines are detailed in this 720-page 1969 catalog. Prices for all items and availabilities in industrial quantities are indicated.—**Newark Electronics Corp.**, 500 No. Pulaski Road, Chicago, Ill. 60624

VIDEO RECORDING for professional broadcasters and amateurs with techniques of TV tape production is outlined, with photographs and diagrams, in the 44-page *Producers Manual*. A glossary of terms used in video recording practice is included.—**Magnetic Products Div. of 3M Co., Marketing Services Dept.**, 3M Center, St. Paul, Minn. 55101. **R-E**

FAR SUPERIOR TO ANY VTVM OR VOM

--and for less money

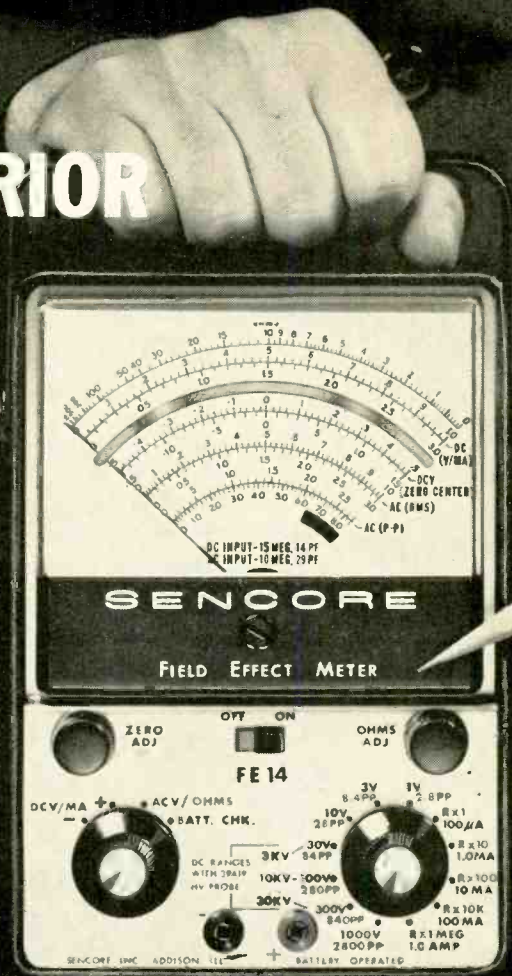

NEW FIELD EFFECT MULTIMETER

Here is the revolutionary new approach to circuit testing, the solid state Sencore FIELD EFFECT METER. This FE14 combines the advantages of a VTVM and the portability and versatility of a VOM into a single low-cost instrument. This is all made possible by the use of the new space age field effect transistor that is instant in action but operates like a vacuum tube in loading characteristics. Compare the features of the FIELD EFFECT METER to your VTVM or VOM.

Minimum circuit loading — 15 megohm input impedance on DC is better than a VTVM and up to 750 times better than a 20,000 ohm per volt VOM — 10 megohm input impedance on AC is 20 times better than a standard VTVM. The FIELD EFFECT METER is constant on all ranges, not like a VOM that changes loading with each range.

Seven AC peak-to-peak ranges with frequency response to 10MHz. Seven zero center scales down to 0.5 volt. Five ohmmeter ranges to 1000 megohms. DC current measurements to 1 ampere. Full meter and circuit protection. Mirrored scale. Low current drain on batteries — less than 2 milliamps. Built-in battery check. Unbreakable all-steel vinyl clad case. Optional Hi-Voltage probe adds 3KV, 10KV and 30KV ranges with minimum circuit loading for greatest accuracy in the industry... \$9.95.

Only Sencore offers the FIELD EFFECT METER. Ask for it by name at your distributor.

only \$69.95 (less batteries)

SENCORE

NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT

426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

Circle 110 on reader's service card




84

Make This Christmas



Kit IM-18
\$2850
Wired IMW-18
\$4795

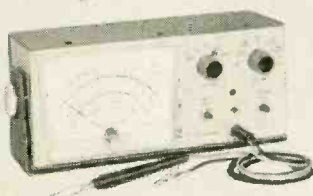

kit IM-28
\$3650
Wired IMW-28
\$5695



Kit IM-38
\$3950
Wired IMW-38
\$5495




kit IM-17
\$2195




kit IT-18
\$2495



kit IP-18
\$1995

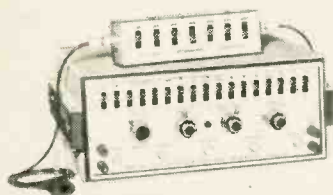

kit IG-57
\$13500
wired IGW-57
\$19900

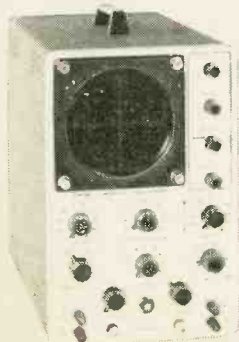

kit IO-18
\$8495
wired IOW-18
\$13995

NEW HEATHKIT IM-18 VTVM

The new IM-18 is a direct decendent of the world's most popular VTVM — the Heathkit IM-11, and continues the features that made the IM-11 famous . . . 7 AC and 7 DC voltage ranges that measure from 0-1500 volts full scale . . . 7 ohms ranges for resistance measurements from 0.1 ohm to 1000 megohms . . . single probe convenience that ends tangled leads & enables you to change from AC to DC/Ohms measurements with a flip of the switch on the probe . . . the light circuit loading of 11 megohm input impedance . . . ± 1 dB 25 Hz to 1 MHz response . . . precision 1% resistors . . . DC polarity reversing position on the function switch . . . measurement capability for RMS and Peak-To-Peak AC voltages and dB . . . precision $4\frac{1}{2}$ " 200 uA meter for extra sensitivity. In addition, the new IM-18 includes wiring options for 120V. or 240 VAC operation and a three-wire line cord for added safety. 5 lbs.

NEW HEATHKIT IM-28 "Service Bench" VTVM

The new Heathkit IM-28 bears the proud tradition of the IM-13, and it has the same performance specifications as the new IM-18 above — an unbeatable combination! But it also has a number of features that put it in a class by itself, like a large 6" meter with easy-to-read markings . . . extra 1.5 and 5 volt AC ranges for additional accuracy . . . a secure gimbal mounting that allows you to put the IM-28 above, below or in front of your most convenient mounting surface . . . "Set and Forget" calibration — all calibration controls are screwdriver adjustable from the front panel to eliminate disassembly . . . smooth ten-turn vernier control of Zero and Ohms Adjust for greater accuracy and easier setting . . . dual primary transformer for 120/240 VAC operation . . . safe 3-wire line cord as well. The new look of Heathkit instrument styling is evident too — handsome beige & brown color scheme, and new knobs that are easy to turn and fast to read. 7 lbs.

NEW HEATHKIT IM-38 Laboratory AC VTVM

For all around general service work, audio design and trouble-shooting or laboratory analysis, you couldn't find a better value than the new Heathkit IM-38 AC VTVM. Here's why — 10 voltage ranges measure from 0.01 to 300 volts RMS full scale . . . an extended frequency response of 10 Hz to 500 kHz at ± 1 dB . . . 10 megohm input on all ranges for higher accuracy and minimal circuit loading . . . wide dB range: -12 to +2 on the meter and ten switch-selected ranges from -40 to +50 in 10 dB steps . . . VU-type ballistic meter damping . . . amplifier filament voltage transformer winding that's balanced to ground for low AC noise . . . 120/240 AC wiring options and new Heathkit styling in sharp beige & brown with an easy-to-grasp, easy-to-read knob. Heathkit engineering has made assembly easy and performance tops. 5 lbs.

HEATHKIT IM-17 Solid-State Volt-Ohm Meter

Another very popular volt-ohmmeter from Heathkit engineering and it's easy to see why — all solid-state circuitry . . . high impedance FET input, 11 megohms on DC, 1 megohm on AC . . . 4 AC voltage ranges . . . 4 DC voltage ranges . . . 4 ohm ranges . . . $4\frac{1}{2}$ " 200 uA meter . . . 3 built-in test leads . . . DC polarity reversing switch . . . zero-adjust & ohms-adjust controls . . . continuous 12-position function switch. And that's not all — the IM-17 is battery powered for complete portability and comes in a rugged polypropylene case with built-in handle. Simple circuit board assembly. 4 lbs.

HEATHKIT IT-18 In-Circuit Transistor Tester

In-Circuit transistor testers don't have to be expensive, and the IT-18 is proof of that . . . tests DC Beta 2-1000, in or out-of-circuit . . . leakage I_{cbo} and I_{cco} current 0-5000 uA out-of-circuit . . . identifies NPN or PNP devices . . . tests diodes in or out-of-circuit for opens & shorts . . . identifies unknown diode leads . . . matches PNP & NPN transistors. The IT-18 is completely portable — runs on just one "D" cell. Easy to use too . . . rugged polypropylene case, attached 3' test leads, big $4\frac{1}{2}$ " 200 uA meter, all front panel controls, 10-turn calibrate control. 4 lbs.

HEATHKIT IP-18 1-15 VDC Power Supply

If you work with transistors, this is the power supply for you. All solid-state circuitry provides 1-15 VDC at up to 500 mA continuous. Features adjustable current limiting, voltage regulation, floating output for either + or - ground, AC or DC programming, circuit board construction, and small, compact size. 110 or 220 VAC. 5 lbs.

HEATHKIT IG-57 Solid-State Post Marker/Sweep Generator

The new IG-57 plus a 'scope is all you need . . . no external sweep generator required. Switch selection of any of 15 crystal-controlled marker frequencies (you can view up to six different frequencies on one 'scope trace). Select the sweep range and you are ready to instantly see the results of any changes you make. Four markers for setting color bandpass, one for TV sound, eight at 1F frequencies between 39.75 & 47.25 MHz plus picture and sound carrier markers for channels 4 & 10. Three sweep oscillators produce the 5 most-used ranges . . . color bandpass, FM IF, color & B&W IF and VHF channels 4 & 10. Save hundreds of dollars and put full alignment facilities in your shop too — order your IG-57 now. 14 lbs. Kit IG-14, same as IG-57 w/o the sweep, 11 lbs. \$99.95.

HEATHKIT IO-18 Wide-Band 5" 'Scope

The New Heathkit IO-18 is destined to be the world's most popular 'scope, just as its predecessor, the IO-12 was. Features 5 MHz bandwidth, the famous Heath patented sweep circuit — 10 Hz to 500 kHz in 5 ranges, two extra sweep positions which can be preset to often-used rates, frequency compensated vertical attenuation, built-in P-P calibration reference, Z-axis input, retrace blanking, wiring options for 120 or 240 VAC operation and new Heathkit styling in beige and brown. 24 lbs.

A Heathkit® Holiday

**Wish Your Family Merry Christmas This Year
With A New Heathkit Color TV... A Better
Buy Than Ever With New Lower Prices**

**NEW Deluxe Color TV With Automatic
Fine-Tuning—Model GR-681**

kit GR-681
\$499⁹⁵ (less cabinet)

The new Heathkit GR-681 is the most advanced color TV on the market. A strong claim, but easy to prove. Compare the "681" against every other TV — there isn't one available for any price that has all these features. Automatic Fine Tuning on all 83 channels... just push a button and the factory assembled solid-state circuit takes over to automatically tune the best color picture in the industry. Push another front-panel button and the VHF channel selector rotates until you reach the desired station, automatically. Built-in cable-type remote control that allows you to turn the "681" on and off and change VHF channels without moving from your chair. Or add the optional GRA-681-6 Wireless Remote Control described below. A bridge-type low voltage power supply for superior regulation; high & low AC taps are provided to insure that the picture transmitted exactly fits the "681" screen. Automatic degaussing, 2-speed transistor UHF tuner, hi-fi sound output, two VHF antenna inputs... plus the built-in self-servicing aids that are standard on all Heathkit color TV's but can't be bought on any other set for any price... plus all the features of the famous "295" below. Compare the "681" against the others... and be convinced.

GRA-295-4, Mediterranean cabinet shown... **\$119.50**
Other cabinets from \$62.95

Deluxe "295" Color TV... Model GR-295
now only **\$449⁹⁵**
(less cabinet)

Big, Bold, Beautiful... and packed with features. Top quality American brand color tube with 295 sq. in. viewing area... new improved phosphors and low voltage supply with boosted B+ for brighter, livelier color... automatic degaussing... exclusive Heath Magna-Shield... Automatic Color Control & Automatic Gain Control for color purity, and flutter-free pictures under all conditions... preassembled IF strip with 3 stages instead of the usual two... deluxe VHF tuner with "memory" fine tuning... three-way installation — wall, custom or any of the beautiful Heath factory assembled cabinets. Add to that the unique Heathkit self-servicing features like the built-in dot generator and full color photos in the comprehensive manual that let you set-up, converge and maintain the best color picture at all times, and can save you up to \$200 over the life of your set in service calls. For the best color picture around, order your "295" now.

GRA-295-1, Walnut cabinet shown... **\$62.95**
Other cabinets from \$99.95

Deluxe "227" Color TV... Model GR-227
now only **\$399⁹⁵**
(less cabinet)

Has same high performance features and built-in servicing facilities as the GR-295, except for 227 sq. inch viewing area. The vertical swing-out chassis makes for fast, easy servicing and installation. The dynamic convergence control board can be placed so that it is easily accessible anytime you wish to "touch-up" the picture.

GRA-227-1, Walnut cabinet shown... **\$59.95**
Mediterranean style also available at \$99.50

Deluxe "180" Color TV... Model GR-180
now only **\$349⁹⁵**
(less cabinet)

Same high performance features and exclusive self-servicing facilities as the GR-295 except for 180 sq. inch viewing area. Feature for feature the Heathkit "180" is your best buy in deluxe color TV viewing... tubes alone list for over \$245. For extra savings, extra beauty and convenience, add the table model cabinet and mobile cart.

GRS-180-5, table model cabinet and cart... **\$39.95**
Other cabinets from \$24.95

Now, Wireless Remote Control For Heathkit Color TV's

Control your Heathkit Color TV from your easy chair, turn it on and off, change VHF channels, volume, color and tint, all by sonic remote control. No cables cluttering the room... the handheld transmitter is all electronic, powered by a small 9 v. battery, housed in a small, smartly styled beige plastic case. The receiver contains an integrated circuit and a meter for adjustment ease. Installation is easy even in older Heathkit color TV's thanks to circuit board wiring harness construction. For greater TV enjoyment, order yours now.

kit GRA-681-6, 7 lbs., for Heathkit GR-681 Color TV's... **\$59.95**
kit GRA-295-6, 9 lbs., for Heathkit GR-295 & GR-25 TV's... **\$69.95**
kit GRA-227-6, 9 lbs., for Heathkit GR-227 & GR-180 TV's... **\$69.95**

**Now There Are 4 Heathkit Color TV's...
All With 2-Year Picture Tube Warranty**



kit GR-681



kit GR-295



kit GR-227



kit GR-180



**New Wireless
TV Remote Control
For GR-295, GR-227
& GR-180**

\$69⁹⁵

**New Wireless
TV Remote Control
For GR-681**

\$59⁹⁵


There's A "Just Right" Heathkit®




NEW kit AD-27
\$169⁹⁵



NEW kit AD-17
\$109⁹⁵

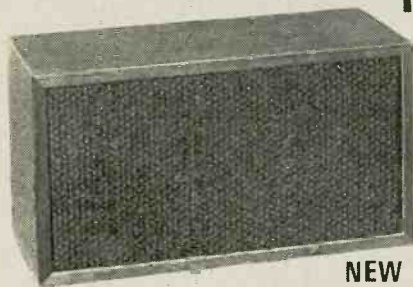

NEW kit AS-18
\$32⁹⁵

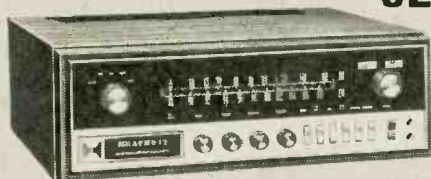

kit AR-15 **Wired ARW-15**
\$339^{95*} **\$525^{00*}**



NEW kit AJ-15
\$189^{95*}



NEW kit AA-15
\$169^{95*}

NEW HEATHKIT AD-27 FM Stereo Component-Compact

This new Heathkit AD-27 stereo compact has features not found in other units costing twice as much for one very simple reason. It wasn't engineered to meet the usual level of compact performance. Instead, Heath took one of its standard stereo/hi-fi receivers, the AR-14, and re-arranged it physically to fit a compact configuration. The result is performance that is truly high fidelity without compromise. It features 31 transistor, 10 diode circuitry with 15 watts per channel dynamic music power (enough to let you choose most any speaker system you prefer), full-range tone controls, less than 1% distortion, and 12 to 60,000 Hz response. The pre-assembled FM stereo tuner section with 4-stage IF offers 5 uV sensitivity, excellent selectivity, AFC, and the smoothest inertia tuning. The BSR McDonald "500" turntable offers features usually found only in more expensive units . . . like low mass tubular aluminum tone arm, anti-skate control, cueing and pause control, plus a Shure magnetic cartridge with diamond stylus. It's all housed in a smart oiled walnut cabinet with sliding tambour door that disappears inside the cabinet. For value and performance choose the AD-27, the new leader in stereo compacts. Shpg. wt. 41 lbs.

NEW HEATHKIT AD-17 Budget-Priced Component-Compact

Heath engineers took the stereo amplifier from the AD-27 above, matched it with the top rated BSR McDonald 400 Automatic Turntable and put both of these able performers in an attractive walnut cabinet. The result is the high performance, low cost AD-17. The all solid-state circuit delivers 15 watts music power per channel — more than enough to drive any reasonably efficient system. Wide response of 12 Hz to 60 kHz ± 1 dB and harmonic & IM distortion both less than 1% at full output are your guarantee of clean, full range sound. Stereo headphone jack, filtered tape outputs and Tuner & Auxiliary inputs too. The BSR McDonald 400 Automatic Turntable features a cueing and pause control, adjustable stylus pressure, variable anti-skate control and manual or automatic operation on all four speeds. Comes complete with a famous Shure magnetic cartridge. The Heathkit manual makes it easy to build . . . the sound makes it a pleasure to own. Order yours now. 27 lbs.

NEW HEATHKIT AS-18 Miniature Acoustic Suspension System

The new AS-18 features famous high quality Electro-Voice® speakers — 6" woofer and a 2½" tweeter. The wide frequency response of 60 Hz to 20 kHz and the clear, natural sound of these miniature systems will really amaze you. They're the ideal performance mates to the Component Compacts above and are especially suited for apartments, mobile homes, offices, etc. — anywhere that you need superior stereo sound from a small space. Handles up to 25 watts program material and has a high frequency balance control so you can adjust the sound to your liking. Order 2 for superb stereo now. 16 lbs.

HEATHKIT AR-15 Deluxe Stereo Receiver

The World's Most Sophisticated, Most Praised Stereo Receiver. And here are just a few of the reasons why leading audio critics and testing organizations, as well as thousands of owners rate the AR-15 as THE stereo receiver. The all solid-state circuit with 69 transistors, 43 diodes and two integrated circuits has many new design concepts to deliver superior performance. The amplifier section has 150 watts of music power . . . 75 watts per channel. Harmonic and IM distortion are both less than 0.5%. The special design FET FM tuner boasts sensitivity of 1.8 uV, selectivity of 70 dB and harmonic & IM distortion both less than 0.5%. The Crystal Filters provide an ideally shaped bandpass and are a Heath first in the high fidelity industry. You'll hear stations you didn't even know existed in your area, and the Noise-Operated Squelch, Adjustable Phase Control, Stereo-Only Switch, Stereo Threshold Control and FM Stereo Noise Filter Switch will let you hear them in the clearest, most natural way. Other features include two front panel stereo headphone jacks, positive circuit protection, loudness switch, speaker switch, front panel input level controls, recessed outputs, two external FM antenna connectors and one for AM, Tone Flat control, electronically filtered power supply and "Black Magic" panel lighting. Seven circuit boards and three wiring harnesses simplify assembly and you can mount your completed AR-15 in a wall, your own cabinet or the Heath assembled walnut cabinet. For the ultimate in a stereo receiver, order your AR-15 now. 34 lbs. *Optional walnut cabinet AE-16, \$24.95.

HEATHKIT AJ-15 Deluxe Stereo Tuner

For the man who already owns a fine stereo amplifier, Heath now offers the superb FM stereo tuner section of the AR-15 receiver as a separate unit. The new AJ-15 FM Stereo Tuner has the exclusive FET FM tuner for remarkable sensitivity, exclusive Crystal Filters in the IF strip for perfect response curve and no alignment; Integrated Circuits in the IF for high gain, best limiting; Noise-Operated Squelch; Stereo-Threshold Switch; Stereo-Only Switch; Adjustable Multiplex Phase, two Tuning Meters; two Stereo Phone jacks; "Black Magic" panel lighting. 18 lbs. *Walnut cabinet AE-18, \$19.95.

HEATHKIT AA-15 Deluxe Stereo Amplifier

For the man who already owns a fine stereo tuner, Heath now offers the famous amplifier section of the AR-15 receiver separately. The new AA-15 Stereo Amplifier has the same superb features: 150 watts Music Power; Ultra-Low Harmonic & IM Distortion (less than 0.5% at full output); Ultra-Wide Frequency Response (± 1 dB, 8 to 40,000 Hz at 1 watt); Front Panel Input Level Controls; Transformerless Amplifier; Capacitor Coupled Outputs; All-Silicon Transistor Circuit; Positive Circuit Protection. 26 lbs. *Walnut cabinet AE-18, \$19.95.

Gift For Everyone On Your List

Heathkit MI-18 Solid-State Tachometer

The Professional Tach. That's the new Heathkit MI-18. In Design: breaker point, "tach" lead or any inductive pickup connection; use it with any spark-type engine and any ignition system, 2 cycle 1-6 cyl. engines or 4 cycle, 2-8 cyl. engines . . . all electronics are in the tach itself. In Performance: 0-6000 & 0-9000 RPM ranges . . . 250° edge-lighted dial . . . temperature-compensated, ±4% accuracy from 0° —120° . . . adjustable red line pointer . . . 10.5 to 17.5 VDC operation. In Styling: stainless steel hardware, splash-proof black & chrome case and scratch-proof glass face for use in rugged conditions. The MI-18-1 mounts in your dash — requires only a 3/4" hole & 2 1/4" depth. The MI-18-2 comes with mounting case & hardware. Put a Professional Tach in your car, boat, dune-buggy, or bike now — the Heathkit MI-18! Shpg. wt. 3 lbs.

NEW kit MI-18-1

\$2995 Panel Mount

NEW kit MI-18-2

\$3295 With Case




Heathkit GR-17 Solid-State AM-FM Portable Radio

Here's performance the others can't match. The new Heathkit GR-17 portable has a 12 transistor, 7 diode circuit with the same front end as used in Heathkit hi-fi tuners. AM or FM at the flick of a switch and what reception! Big 1/2" ferrite rod antenna, three tuned transformers and amplified AGC pull in more AM stations. The FM section features a collapsible 34" whip antenna, three IF stages and 5 uV sensitivity for reception over greater distances than you would expect from a portable. The 4" x 6" speaker and an audio output of 350 mW provides clean sound and the GR-17 will keep you entertained for up to 300 hours on a single set of batteries. For the greatest sound everywhere, get your GR-17 today. 5 lbs.

NEW kit GR-17

\$4395

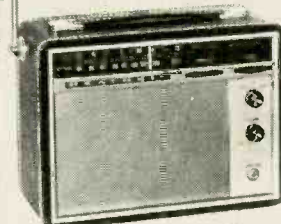


NEW kit HW-100

\$24000

NEW HEATHKIT HW-100 SSB-CW 5-Band Receiver

The new Heathkit HW-100 has all the features and performance of the competition at a money saving kit price. And here's what it delivers: the receiver portion has sensitivity of less than 0.5 uV for a 10 dB S+N/N ratio for SSB. Crystal filter selectivity is 2.1 kHz at 6 dB down, 7 kHz at 60 dB down. Image & IF rejection are better than 50 dB. The transmitter has a 180 watt input on either USB or LSB and 170 watts on CW. It operates PTT or VOX on SSB and break-in CW work is provided by operating VOX from a keyed tone, using grid-block keying. Outstanding frequency stability — less than 100 Hz per hour drift after 30 minute warmup . . . less than 100 Hz variation under a 10% line voltage variation. The HW-100 is a really loaded rig — solid-state (FET) VFO . . . 80-10 meter coverage . . . patented Harmonic Drive™ dial mechanism . . . built-in 100 kHz calibrator . . . TALC and much more. Put this hot rig in your shack — order your HW-100 today. 22 lbs.

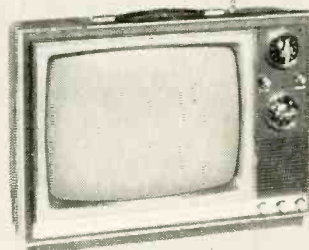

kit GR-104A

\$11995

HEATHKIT GR-104A Solid-State Portable B&W TV

The perfect portable . . . that's the GR-104. Small and light enough to carry from room to room . . . rugged enough to take it . . . and the picture is the sharpest, most realistic you've ever seen, thanks to Heathkit total engineering. 74 sq. in. viewing area . . . all solid-state circuit for extra reliability and performance . . . covers all VHF and UHF channels, 2-83 . . . 2-speed UHF tuning . . . "memory" VHF fine tuning . . . 3-stage IF for maximum gain with controlled bandwidth . . . gated AGC for steady, jitter-free pictures . . . transformer regulated power supply . . . circuit breaker protection . . . one-piece swing out chassis for easy assembly and servicing . . . runs on house current or battery power with the optional GRA-104-1 rechargeable battery pack. 27 lbs.

GRA-104-1, 9 lbs. \$39.95




kit GD-325C

\$43995

HEATHKIT GD-325C Low Cost Solid-State Organ

This money-saving kit form of the popular Thomas "Artiste" Organ can have you playing songs after just 50 hours of interesting, enjoyable assembly, thanks to the clear, easy-to-follow Heathkit manual and exclusive Thomas Color-Glo teaching method. Features 10 true organ voices . . . variable repeat percussion . . . 13 note heel and toe bass pedals . . . 2 overhanging 37 note keyboards, range C2 thru C5 each . . . 75 watt peak music power amplifier . . . 12" full response speaker . . . Vibrato . . . manual balance control . . . and the solid-state plug-in tone generators — the heart of the organ, are guaranteed for 5 years. Assembled walnut-finish cabinet included. Discover the fun and enjoyment of live music in your home . . . order your Heathkit/Thomas organ today. 172 lbs.

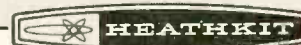

NEW

FREE 1969 CATALOG!

Now with more kits, more color. Fully describes these along with over 300 kits for stereo/hi-fi, color TV, electronic organs, electric guitar & amplifier, amateur radio, marine, educational, CB, home & hobby. Mail coupon or write Heath Company, Benton Harbor, Michigan 49022.

HEATH COMPANY, Dept. 20-12
Benton Harbor, Michigan 49022
In Canada, Daystrom Ltd.

Enclosed is \$ _____, plus shipping.

Please send model (s)

Please send FREE Heathkit Catalog.

Please send Credit Application.

Name _____

Address _____

City _____

State _____

Zip _____

Prices & specifications subject to change without notice.

CL-345

Fill 80 resistor values
with only 20

MAGIC NUMBERS OF ELECTRONICS



A practical reference guide and resistor stock all in one. It's a new IRC approach to using carbon composition resistors.

MAGIC NUMBERS BOOK—explains resistance values and how 20 values fill 80 needs. Five chapters full of helpful service information.

CHART AND RESIST-O-GRAPHS—reduce service time. 80/20 chart, dual range parallel and series indicators, and dual range power indicator for parallel or series. All in Magic Numbers book.

RESISTOR STOCK—of 20 Snap Paks. Snap Pak is the new IRC resistor package that eliminates loose parts and clutter. 1/2-watt or 1-watt stocks.

20 MAGIC VALUES ALSO IN FILE-O-PAK CABINET



Keeps Snap Pak stock neat. File by wattage, resistance, and tolerance. Workbench size.

MAGIC NUMBERS BOOKS NOW AT
YOUR IRC DISTRIBUTOR



DIVISION OF TRW INC.

401 N. Broad St., Phila., Pa. 19108

Circle 112 on reader's service card

Service Clinic

By JACK DARR
SERVICE EDITOR

Chronic sound drift; triple image

This Admiral 16R12 needs a sound realignment every couple of months. I've checked components, but no luck. Also, in a Magnavox CT-214, I get a triple image; I've checked capacitors around the horizontal circuits, including the yoke capacitor. I guess the next step would be a new yoke. What would you suggest.—J. H., Baltimore, Md.

I believe your trouble in the Admiral could be cured by replacing the discriminator transformer. This is the cause of most complaints of this kind, that is, slow drifting off alignment. It is probably due to aging of the base assembly with its tiny capacitors.

In the Magnavox, the triple image is basically due to the horizontal oscillator running away off frequency. A triple image means that the oscillator is running at one-third normal speed, or somewhere around 5,250 cycles. This could be the fault of a leaky capacitor, a resistor somewhere in the frequency-determining circuits that has drifted off value, or to a defective horizontal oscillator coil or transformer. Grid resistors are always prime suspects for this kind of trouble. This series uses a synchro-

guide oscillator circuit. Follow the standard procedure for realigning it. Short out the "waveform" coil, set the hold control in the center of its range, and tune the frequency slug for a single floating picture. If you cannot get a single picture with this procedure (and all coils, capacitors and resistors are good), then the transformer is bad and you'll have to replace it.

Sound, No Picture

I'm afraid I'm stuck. I have raster and sound but no picture on a G-E M6 chassis. Tubes and other parts check okay. If I clamp the agc, I lose the sound. What's going on here? —E. D., N. Y., N. Y.


Most likely possibility is a bad video detector diode. Note the detector is not in series but shunted from the signal path to ground (see diagram). Works just the same, of course, but can have different symptoms.

You can check this with an ohmmeter. Take a resistance reading from the last rf choke outside the detector can (point 1) to ground. Reverse the leads and you should have a "diode reading"—high resistance one way, comparatively low the other. If you get a high reading both ways the diode is open; low resistance both ways, it's shorted.

Possible reason for getting sound through bad detector stage: with a shunt detector, the signal could go on through to the video amplifier. There, it could be "grid-rectifying," thus developing a sound-i.f. signal. Incidentally, if this chassis has the small glass diode, you'll get better results by using a 1N34 or any of the older, bigger video-detector diodes. **R-E**

This column is for your service problems—TV, radio, audio or general and industrial electronics. We answer all questions individually by mail, free of charge, and the more interesting ones will be printed here.

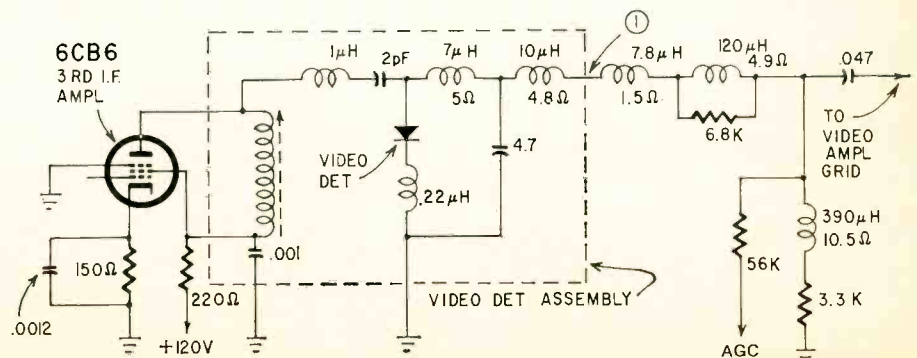If you're really stuck, write us. We'll do our best to help you. Don't forget to enclose a stamped, self-addressed envelope. Write: Service Editor, Radio-Electronics, 200 Park Ave. South, New York 10003.




U.S. GOV'T ELECTRONIC SURPLUS

• Nationally Known-World Famous SURPLUS CENTER offers finest, most expensive, Government Surplus electronic units and components at a fraction of their original acquisition cost.

ORDER DIRECT FROM AD or WRITE FOR CATALOGS

(IBM) SILICON DIODE RECTIFIERS

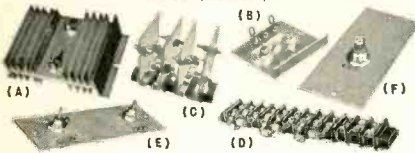• "Great Buys" in top quality, surplus, silicon diode rectifier units. (IBM Computer Units)



- (#REC-4) -- Two 12-amp., 50-V. silicon diodes on finest aluminum sinks. (1 lb.) **\$2.69**
- (#22-925) -- Twin 1 $\frac{1}{2}$ -amp., 150-V. silicon diodes on finest aluminum sinks. (1 lb.) **\$1.31**
- (#11-949) -- Eight 12-amp., 100-V. silicon diodes on heavy copper heat sinks. (1 lb.) **\$3.97**
- (#11-900) -- Six 1-amp., 100-V. silicon diodes on Kulkha strip. Very versatile. (1 lb.) **\$1.71**
- (#22-926) -- Two 25-amp., 50-V. silicon diodes on heavy copper heat sink. (1 lb.) **\$2.69**
- (#22-914) -- One 25-amp., 50-V. silicon diodes on heavy copper heat sink. (1 lb.) **\$1.81**

COMPUTER TRANSISTORS ON HEAT SINKS

IBM Computer Quality Units

• (#22-928) -- Unit consists of one 150-watt power transistor on heavy, ribbed, aluminum heat sink. Many experimental uses. (1 lb.)

Cost Gov't Over \$10.00 **\$1.99**

• (#22-915) -- Unit consists of two 150-watt power transistors, 2 pots, several diodes, capacitors, resistors, etc. on heavy, ribbed aluminum heat sinks. Ideal for use as motor speed control. (4 lbs.)

Cost Gov't Over \$35.00 **\$4.91**



COMPUTER GRADE FILTER CAPACITORS

• Latest design, high MF units. Eliminate need for expensive chokes. 2-1/16" diam. x 4-1/2". (1-1/2 lbs.)

- (#C-14-1) -- 15,500-MF @ 10-Volts **.99**
- (#C-14-2) -- 1500-MF @ 150-Volts **.98**
- (#C-14-3) -- 5000-MF @ 55-Volts **.97**
- (#C-14-7) -- 12,500-MF @ 10-Volts **\$1.19**
- (#C-14-12) -- 750-MF @ 25-Volts **.98**



RUNNING TIME METER

• (#HX-104) -- Use to record number of operating hours of electric lights and electrical devices such as refrigerators, furnaces, etc. Records total hours, months and hundredths up to 9,999.99 hours. For 115-volt, 60 cycles. Size 4 $\frac{1}{2}$ " x 3" x 2 $\frac{1}{2}$ ". Shipping weight 2 lbs.

\$5.69 Cost Over \$29.00



12 and 24-VOLT TRANSFORMER

• (#15-920) -- General Electric 115-volt, 60-cycle to 12 and 24-volts @ 750-watts. Capacity 42-amps. @ 24-volts, 64-amps. at 12-volts. Useful for battery chargers, running DC motors, etc. 7" x 5" x 5". (18 lbs.)

Cost Gov't Over \$35.00 **\$16.72**



EXPANDED SCALE 0 - 15 DCVM

• (#21-900) -- Brand new, expensive voltmeter reads 0-5 in 10-volts DC and 0 to 8-volts. Very useful for automotive and aircraft battery charge indicator, etc. D-Arsonval movement, black phenolic case. 7" x 5" x 2 $\frac{1}{2}$ ". (3 lbs.)

List \$32.50 **\$7.97**



SILICON DIODES


\$5.90

• (#RED-3) -- New, perfect, Westinghouse 2770-A, 275-amp., 50-volt. #2N4044. Fine for hi-current rectifier. (1 lb.) List Over \$15.00

DIGITAL READ-OUT UNIT

Cost Gov't \$250.00 **\$3.97**

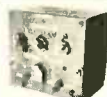• (#HE-17) -- Sophisticated electronic unit contains 5-digit "read-out" electric motor, gear train, relays, etc. 5" x 6" x 7". (10 lbs.)



TYPICAL BUYS FROM OUR 1969 CATALOGS

• Our new 1969 Catalogs (Vol. #1 and #2) contain hundreds of tremendous buys in electronic equipment, power plants, welding generators, battery wipers, mobile, electric golf carts, hydraulic gear, walkie-talkies, tape recorders, binoculars, surveying instruments, all types 12-volt power motors, blowers, relays, etc.

- \$100.00 Automatic Telephone Step Switches **\$9.95**
- \$275.00 Geared Battery Motors For Electric Cars **\$26.95**
- \$ 30.00 Standard Dial Handset Telephones **\$7.50**
- \$ 4.50 Power Transformer 115V to 25V **\$1.21**
- \$ 37.50 750-Watt Transformers 115V, to 24V **\$19.81**
- \$650.00 Power Plant 5000-Watts, 115-Volts **\$135.00**
- \$ 30.00 115-Volt AC Watt-hour Meters **\$5.95**
- \$ 42.50 115-Volt, 35-Amp. Clock Timer Switch **\$8.91**
- 15-Vol. Discontinued Correspondence Course In Electrical Engineering **\$8.79**



SEND 25¢ COIN OR STAMPS FOR CATALOGS

All Items FOB Money Back Guarantee

SURPLUS CENTER

DEPT. RE 128 LINDOLN, NEBR. 68501

COMPUTER SCHOOLS

Here is a partial listing of specialized schools that offer courses in computer technology and programming.

- American School**
Drexel Ave. at 58th St.
Chicago, Ill. 60637
- Automation Training, Inc.**
5701 Waterman Ave.
St. Louis, Mo. 63112
- Britannica Institute for Executive Development**
425 North Michigan Ave.
Chicago, Ill. 60611
- Business Electronics**
209 W. Jackson Blvd.
Chicago, Ill. 60606
- Canadian Institute of Science & Technology**
263 Adelaide St. W.
Toronto, Ont., Canada
- Capitol Radio Engineering Institute**
3224 16 St., N.W.
Washington, D.C. 20010
- Central Technical Institute**
1644 Wyandotte St.
Kansas City, Mo. 64108
- Cleveland Institute of Electronics**
1776 E. 17th St.
Cleveland, Ohio 44114
- Commercial Trades Institute**
1400 W. Greenleaf Ave.
Chicago, Ill. 60626
- Cook's Institute of Electronics Engineering**
P.O. Box 10634
Jackson, Miss. 39209
- DeVry Institute of Technology**
4141 Belmont Ave.
Chicago, Ill. 60641
- Elkins Institute**
2603 Inwood Rd.
Dallas, Texas 75235
- Grantham School of Electronics**
1505 N. Western Ave.
Hollywood, Calif. 90027
- Hill's Business University**
920 N. Robinson Ave.
Oklahoma City, Okla. 73102
- International Correspondence Schools**
Scranton, Pa. 18515
- LaSalle Extension University**
417 S. Dearborn St.
Chicago, Ill. 60605
- Massey Technical Institute, Inc.**
148 East 7th St.
Jacksonville, Fla. 32206
- Midwest Automation Training—Kansas City, Inc.**
2022 Main St.
Kansas City, Mo. 64108
- National Radio Institute**
3939 Wisconsin Ave., N.W.
Washington, D.C. 20016
- National Technical Schools**
4000 S. Figueroa St.
Los Angeles, Calif. 90037
- Northrop Institute of Technology**
1199 W. Arbor Vitae
Inglewood, Calif.
- Philco Technical Institute**
219 N. Broad St.
Philadelphia, Pa. 19107
- RCA Institutes, Inc.**
320 West 31st St.
New York, N.Y. 10001
- Sams Technical Institute, Inc.**
1720 E. 38th St.
Indianapolis, Ind. 46218
- Technical Training International, Inc.**
10447 So. Torrence Ave.
Chicago, Ill. 60617

FOR INFORMATION "too hot to handle"

Learn about the new scientific and patented miracles in sound by



**WIDE SCREEN STEREO
DEEPEST TRUE PITCH BASS
DYNAMICS WITHOUT DISTORTION
UNIFORM WIDE AREA COVERAGE
MICROWATT SENSITIVITY
AND MORE**

FREE LITERATURE

WRITE OR PHONE

KARLSON RESEARCH & MFG.
Box 117, W. Hempstead L.I., N.Y.
Tel. 516-489-3641

Circle 121 on reader's service card

Olson



FREE

Fill in coupon for a FREE One Year Subscription to OLSON ELECTRONICS' Fantastic Value Packed Catalog—Unheard of LOW, LOW PRICES on Brand Name Speakers, Changers, Tubes, Tools, Stereo Amps, Tuners, CB, Hi-Fi's, and thousands of other Electronic Values. Credit plan available.

NAME _____

ADDRESS _____

CITY _____ STATE _____

GIVE ZIP CODE _____

If you have a friend interested in electronics send his name and address for a FREE subscription also.

OLSON ELECTRONICS


289 S. Forge Street Akron, Ohio 44308

Circle 122 on reader's service card

HALF PRICE!

Yes! Half the price you would normally pay for:

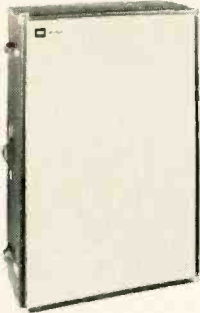- Guitar Amplifiers • Speaker Cabinets
- P. A. Amplifiers • Sound Columns
- Strobe Lights • Color Organs



How? With **MYRIAKIT**!

MYRIAKIT offers you great equipment in kit and semi-kit form, each including easy to follow step-by-step instructions to insure proper and accurate assembly.

WRITE FOR FREE CATALOG TO:

MYRIAKIT CORP.

1043 N. Main St., Akron, O. 44310

Name _____

Address _____

City _____

State _____

Zip _____

Circle 123 on reader's service card

WORLD'S FINEST
5-CORE SOLDER

ERSIN MULTICORE

NEW EASY DISPENSER PAK

ONLY 69¢


BUY IT AT RADIO-TV PARTS STORES
MULTICORE SALES CORP. WESTBURY, N.Y. 11590
Circle 124 on reader's service card

NEW TUBES AND

SEE-IN-THE-DARK TV CAMERA TUBE

A new SEC (Secondary Electron Conduction) camera tube, the WL-30691, is being produced for commercial and industrial closed-circuit TV applications. It is an outgrowth of the SEC tube originally developed for military use and noted for its ability to "see" where there is essentially no light. It can be used in vidicon camera systems with some modifications in the preamplifier.

This Westinghouse tube is charac-

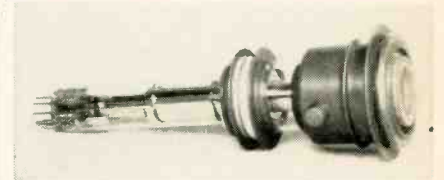

terized by high static and dynamic sensitivity, low lag and no halation or blooming. It features an all-magnetic gun, a fiber-optics faceplate, low-power operation and simple operation.

Bulletin TD-86-817, available from Westinghouse Electronic Tube Div., PO Box 284, Elmira, N.Y. 14902, includes full specifications and a suggested preamplifier design and schematic diagram.

"VALUES" THAT DEFY ALL COMPETITION

FREE \$1 BUY WITH EVERY 10 YOU ORDER

Only applies to "\$1" Buys

FREE GIFT WITH EVERY ORDER

- | | | | |
|--|---|--|--|
| <input type="checkbox"/> 100—ASST ¼ WATT RESISTORS \$1
stand. choice ohmages, some in 5% | <input type="checkbox"/> NYLON PRINTED CIRCUIT TOOL \$1
For Lead Bending & Dressing, will not scratch boards | <input type="checkbox"/> TRANSISTOR RADIO <i>asst type</i> \$1.50
good, bad, broken, as-is, potluck | <input type="checkbox"/> METER SENTRY—SOLID STATE \$9.95
Protects meter movements up to 25 amps surge |
| <input type="checkbox"/> 100—ASST ½ WATT RESISTORS \$1
stand. choice ohmages, some in 5% | <input type="checkbox"/> 50 — ASST. DISC CERAMIC CONDENSERS \$1
popular numbers | <input type="checkbox"/> TAPE RECORDER — assorted types \$4
good, bad, broken, as-is, potluck | <input type="checkbox"/> 8"—ECONOMY "OXFORD" SPEAKER \$1.69
Top quality 2.15 Mag. |
| <input type="checkbox"/> 70 — ASST 1 WATT RESISTORS \$1
stand. choice ohmages, some in 5% | <input type="checkbox"/> 100 — ASST. MICA CONDENSERS \$1
some in 5% | <input type="checkbox"/> 100 — ASST. TUBULAR CONDENSERS \$1
.001 to .47 to 600v | <input type="checkbox"/> 12" OXFORD SPEAKER, Top \$4
Quality Large Magnet |
| <input type="checkbox"/> 35 — ASST 2 WATT RESISTORS \$1
stand. choice ohmages, some in 5% | <input type="checkbox"/> 2 — POWER TRANSISTORS \$1
Replace 2N155, 2N176, 2N301, etc. | <input type="checkbox"/> TV TUNERS <i>asst.</i> all new standard makes, including Tubes \$1 | <input type="checkbox"/> MOTOROLA PWR TRANSFORM \$1
110v, CT 150/150v, 6.3v |
| <input type="checkbox"/> 50 — PRECISION RESISTORS \$1
<i>asst.</i> list-price \$50 less 98% | <input type="checkbox"/> HYTRON POWER TRANSISTOR \$1
H.V. replaces DS501, 2N173, etc. | <input type="checkbox"/> TV TUNERS <i>asst.</i> all new standard deluxe quality, including Tubes \$3 | <input type="checkbox"/> 10 — TRANSFORMERS <i>assorted</i> \$1
Audio Outputs, Chokes, I, F, 's, etc. |
| <input type="checkbox"/> 20 — ASSORTED WIREWOUND RESISTORS, 5, 10, 20 watt \$1 | <input type="checkbox"/> 70—BRASS FAHNESTOCK CLIPS \$1
popular type & size | <input type="checkbox"/> 32' — TEST PROD WIRE \$1
deluxe quality, red or black | <input type="checkbox"/> 10 — ASST. RADIO & TV TUBES \$1
Every Tube a good number |
| <input type="checkbox"/> 100—MIXED DEAL "JACKPOT" \$1
Condensers, Resistors, Surprises | <input type="checkbox"/> 10 — SPEAKER PLUG SETS \$1
deluxe type, 2 conductor | <input type="checkbox"/> HEARING AID AMPLIFIER \$1
incl. 3 Tubes, Mike, etc. (as is) | <input type="checkbox"/> 50 — ASSORTED TRANSISTORS \$1
big factory sealee, solid as-is |
| <input type="checkbox"/> 4 — TOGGLE SWITCHES \$1
SPST, SPDT, DPST, DPDT | <input type="checkbox"/> 10 SETS — DELUXE PLUGS & JACKS \$1
<i>asst.</i> for many purposes | <input type="checkbox"/> 50 — #3AG FUSES ½ AMP \$1
popular type with pigtails | <input type="checkbox"/> 20—ELECTROLYTIC CONDENSERS \$1
Fine <i>asst.</i> 100 numerous to mention |
| <input type="checkbox"/> 10—ASSORTED SLIDE SWITCHES \$1
SPST, SPDT, DPDT, etc. | <input type="checkbox"/> 10 — SETS PHONO PLUGS & PIN JACKS \$1
RCA type | <input type="checkbox"/> 10 — STANDARD TRANSISTORS \$1
NPN & PNP 2N404, 2N414, etc. | <input type="checkbox"/> 20 — ASST. VOLUME CONTROLS \$1
All desirable good types |
| <input type="checkbox"/> \$15.00 TELEVISION PARTS \$1
"JACKPOT" best buy ever | <input type="checkbox"/> 10 — SURE-GRIP ALLIGATOR CLIPS \$1
2" plated | <input type="checkbox"/> 10—ASSORTED DIODE CRYSTALS \$1
1N34, 1N48, 1N60, 1N64, etc. | <input type="checkbox"/> 100 — RADIO & TV SOCKETS \$1
<i>Asst.</i> — too numerous to mention |
| <input type="checkbox"/> 7 — TV ELECTROLYTIC CONDENSERS \$1
desirable types | <input type="checkbox"/> 50 — ASSORTED PRINTED CIRCUIT SOCKETS \$1
best types | <input type="checkbox"/> \$4 ELECTRIC FOOT SWITCH \$1
deluxe type for any equipment | <input type="checkbox"/> 100 — RADIO & TV KNOBS \$1
<i>Asst.</i> — too numerous to mention |
| <input type="checkbox"/> 15 — ASST. ROTARY SWITCHES \$1
all popular types \$20 value | <input type="checkbox"/> 100 — STRIPS ASSORTED SPAGHETTI \$1
handy sizes | <input type="checkbox"/> 6 — TRANSISTOR RADIO EARPIECES \$1
wired complete with plug | <input type="checkbox"/> 25 — 3900-OHM-7w RESISTOR \$1
10% Corning glass |
| <input type="checkbox"/> 3 — TOP BRAND 35W4 TUBES \$1 | <input type="checkbox"/> UNIVERSAL 4" PM SPEAKER \$79¢
Ainico 5 magnet, quality tone | <input type="checkbox"/> 1—SQ. YARD GRILLE CLOTH \$2
most popular brown & gold design | <input type="checkbox"/> 20 — .47-600V CONDENSERS \$1
White Ceramic C.D.-American |
| | | <input type="checkbox"/> \$20—SHURE M-7D DIAMOND NEEDLE \$3
exact replacement | |

IMMEDIATE DELIVERY . . . Scientific light packing for safe delivery at minimum cost.
HANDY WAY TO ORDER: Pencil mark or write amounts wanted in each box, place letter F in box for Free \$1 BUY. Enclose with check or money order, add extra for shipping. Tearsheets will be returned as packing slips in your order, plus lists of new offers.

Name _____ Cost of goods _____
Address _____ Shipping _____
_____ estimated _____
_____ TOTAL

Please specify refund on shipping overpayment desired: CHECK POSTAGE STAMPS MERCHANDISE (our choice) with advantage to customer

BROOKS RADIO & TV CORP., 487 Columbus Ave., New York, N. Y. 10024

212-874 5600
TELEPHONE

SEMICONDUCTORS

EPOXY TO-5 TRANSISTORS

A new epoxy TO-5 package with power dissipation equivalent to a metal can has been adapted for 13 npn and 10 pnp Fairchild transistors. The package features a molybdenum disc that seats the silicon die and removes internal heat from over a wider area. It permits power dissipation of 4 watts at case temperatures to 25°C and 500 mW at 25°C ambient temperature.

The devices are mechanically interchangeable with their metal-can counterparts. Their construction provides for a dielectrically isolated collector that greatly decreases the capacitance inherent in metal-can designs and permits external heat sinking directly to the chassis. Thus, it is possible to use larger and more efficient heat sinks without increasing capacitance.

Epoxy transistors in the series include the SE8040 and SE8050 complementary at power amplifiers. Others are equivalents of the metal-can 2N2218, 2N2219, 2N3108, 2N3722, 2N905, 2N905-A, 2N3467, 2N3468, 2N4030, -31, -32, 2N5042 and SE-7010.

Write: Fairchild Distribution Center, 313 Fairchild Drive, Mountain View, Calif. 94040. **R-E**

ENJOY THE "MUSIC ONLY" FM PROGRAMS

M. A. D.

MUSIC ASSOCIATED'S DETECTOR
NO COMMERCIALS—NO INTERRUPTIONS



It's easy! Just plug Music Associated's Sub Carrier Detector into multiplex jack of your FM tuner or easily wire into discriminator. Tune through your FM dial and hear programs of continuous commercial-free music you are now missing. The Detector, self-powered and with electronic mute for quieting between selections, permits reception of popular background music programs no longer sent by wire but transmitted as hidden programs on the FM broadcast band from coast to coast. Use with any FM tuner. Size: 5 1/2" x 9". Shipping weight approx. 7 lbs.

KIT \$4950

(with pre-tuned coils, no alignment necessary)

WIRED \$7500 (Covers extra \$4.95 ea.)

Current list of FM Broadcast stations with SCA authorization \$1.00

MUSIC ASSOCIATED

65 Glenwood Road, Upper Montclair, N. J.
Phone: (201)-744-3387 07043

Circle 125 on reader's service card


WE DON'T CLAIM
OUR ELECTRONIC
IGNITION SYSTEM
IS BEST



OUR CUSTOMERS DO!

WRITE TODAY FOR FREE LITERATURE

JUDSON

RESEARCH AND MFG. CO. 
CCNSHOHOCKEN, PA., U.S.A.

Circle 126 on reader's service card

CANADIANS: Ordering is easy — we do the paperwork — try a small order


Integrated Circuits At Prices You Can Afford

Motorola HepKit Includes

- One J-K Flip Flop
- One Dual Buffer
- One 4-Input Gate
- Two Dual 2-Input Gates

ALL FIVE JUST \$3.95

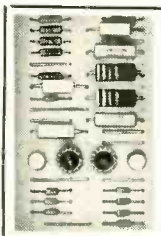ALSO Tips On Using I.C.s. Including an Integrated Circuit Cross Reference Guide & 8 I.C. Project Circuits



IBM COMPUTER SECTIONS

8 assorted Units we sell for \$1 are loaded with over 150 valuable parts.

Incl. — Transistors
Condensers, Resistors,
Heat Sinks, Diodes, Etc.
8 for \$1
100 for \$10


SHANNON MYLAR RECORDING TAPE

2 1/2" — 225' .. \$.15	7" — 2400' .. \$1.59
3" — 225' .. .17	7" — 3600' .. .2.78
3" — 300' .. .24	CASSETTE 60 minutes 1.00
3 1/4" — 600' .. .49	CASSETTE 90 minutes 1.86
5" — 600' .. .52	CASSETTE 120 minutes 2.49
5" — 900' .. .67	
5" — 1200' .. .86	2 1/2" TAPE REEL .. .04
5" — 1800' .. 1.29	3" TAPE REEL .. .05
7" — 1200' .. .69	3 1/4" TAPE REEL .. .06
7" — 1800' .. .99	5" TAPE REEL .. .12
	7" TAPE REEL .. .14

- | | | | |
|---|--|---|--|
| <input type="checkbox"/> BONANZA "JACKPOT" not gold, not oil, but a wealth of Electronic Items—Money-Back-guarantee .. \$5 | <input type="checkbox"/> ALL AMERICAN TUBE KIT 12HA6, 12BE6, 12AV6, 50C5, 35W4—total list \$9.70 .. \$2 | <input type="checkbox"/> RECORDING TAPE SPLICER \$1.49 handy, accurate, compact .. \$1.49 | <input type="checkbox"/> RCA 110° FLYBACK TRANSFORMER We scooped the Market Latest type — standard for all 110° TV's RCA's design of large Coil produces 18KV—assuring adequate width Incl Schematic Diagram application for any TV List price \$13.90 Your price .. \$3 10% off in lots of 3 |
| <input type="checkbox"/> 300 — ASSORTED HEX NUTS 2/56, 4/40, 5/40, 6/32, 8/32 .. \$1 | <input type="checkbox"/> 2—G.E. PIECES OF EQUIPMENT stacked with over 200 useful parts .. \$1 | <input type="checkbox"/> 40 — ASSORTED TV KNOBS all standard types, \$20 value .. \$1 | <input type="checkbox"/> 110° TV DEFLECTION YOKE \$3 for all types TV's incl schematic .. \$3 |
| <input type="checkbox"/> 250 — ASST. SOLDERING LUGS best types and sizes .. \$1 | <input type="checkbox"/> 15 — G.E. #NE-2 TUBES Neon Glow Lamp for 101 uses .. \$1 | <input type="checkbox"/> 25 — VERT. LINEARITY KNOBS Long shank .. best asst. .. \$1 | <input type="checkbox"/> "COMBINATION SPECIAL" RCA 110° FLYBACK plus 110° DEFLECTION YOKE .. \$5 |
| <input type="checkbox"/> 250 — ASST. WOOD SCREWS finest popular selection .. \$1 | <input type="checkbox"/> 50 — ASSORTED MYLAR CONDENSERS popular selected types .. \$1 | <input type="checkbox"/> 50 — ASST. TERMINAL STRIPS all types, 1-lug to 6-lug .. \$1 | <input type="checkbox"/> 90° FLYBACK TRANSFORMER \$2 for all type TV's incl schematic .. \$2 |
| <input type="checkbox"/> 250 — ASST. SELF TAPPING SCREWS #6, #8, etc. .. \$1 | <input type="checkbox"/> 3 — TOP BRAND SILICON RECTIFIERS 1 amp, 1000 PIV .. \$1 | <input type="checkbox"/> 25 — INSTRUMENT POINTER KNOBS selected popular types .. \$1 | <input type="checkbox"/> 90° TV DEFLECTION YOKE \$2 for all type TV's incl schematic .. \$2 |
| <input type="checkbox"/> 150 — ASST. 6/32 CREWS and 150 6/32 HEX NUTS .. \$1 | <input type="checkbox"/> 20 — ASST. PILOT LIGHTS #44, 46, 47, 51, etc. .. \$1 | <input type="checkbox"/> 1 — LB SPOOL ROSIN-CORE SOLDER 40/60 top quality .. \$1 | <input type="checkbox"/> 70° FLYBACK TRANSFORMER \$2 for all type TV's incl schematic .. \$2 |
| <input type="checkbox"/> 150 — ASST. 8/32 SCREWS and 150—8/32 HEX NUTS .. \$1 | <input type="checkbox"/> 50 — ASSORTED #3AG FUSES popular ampere ratings .. \$1 | <input type="checkbox"/> 50 — TUBULAR CONDENSERS asst. .001 to .47—400v to 1000v .. \$1 | <input type="checkbox"/> 70° TV DEFLECTION YOKE \$2 for all type TV's incl schematic .. \$2 |
| <input type="checkbox"/> 150 — ASST. 2/56 SCREWS and 150—2/56 HEX NUTS .. \$1 | <input type="checkbox"/> 4 — 50' HANKS HOOK-UP WIRE assorted colors .. \$1 | <input type="checkbox"/> 3—ELECTROLYTIC CONDENSERS most popular number 50/30—150v .. \$1 | <input type="checkbox"/> 20 — ASSORTED TV COILS I.F. video, sound, ratio, etc. \$1 |
| <input type="checkbox"/> 150 — ASST. 4/40 SCREWS and 150—4/40 HEX NUTS .. \$1 | <input type="checkbox"/> 100' — SPOOL SPEAKER WIRE 2 cond, mini zip, clear, 101 uses .. \$1 | <input type="checkbox"/> UNIVERSAL MICROPHONE regular/remote/single & dual plug .. \$2 | <input type="checkbox"/> 100° — TV TWIN LEAD-IN WIRE \$2 300 ohm, deluxe heavy duty, clear .. \$2 |
| <input type="checkbox"/> 150 — ASST. 5/40 SCREWS and 150—5/40 HEX NUTS .. \$1 | <input type="checkbox"/> 5 — I.F. COIL TRANSFORMERS 456-kc for Transistor Radios .. \$1 | <input type="checkbox"/> CRYSTAL LAPEL MICROPHONE high impedance, 200-6000 cps .. \$5.95 | |
| <input type="checkbox"/> 500 — ASSORTED RIVETS most useful selected sizes .. \$1 | <input type="checkbox"/> 5 — AUDIO OUTPUT TRANSFORM Sub-min for Trans Radios .. \$1 | <input type="checkbox"/> 25 — KNURLED RADIO KNOBS Hard to get .. best selection .. \$1 | |
| <input type="checkbox"/> 500 — ASSORTED WASHERS most useful selected sizes .. \$1 | <input type="checkbox"/> 5 — PNP TRANSISTORS general purpose, TO-5 case .. \$1 | <input type="checkbox"/> CHAPT ZU DI MITZIA "JACK POT" Double your money back if not completely satisfied .. \$1 | |
| <input type="checkbox"/> 100 — ASST. RUBBER BUMPERS for cabinet bottoms & other uses .. \$1 | <input type="checkbox"/> 5 — NPN TRANSISTORS general purpose, TO-5 case .. \$1 | <input type="checkbox"/> STEREO HEADPHONES Hi-Fi Quality .. Complete with Stereo plug .. \$5.95 | |
| <input type="checkbox"/> 100—ASSORTED RUBBER GROMMETS best sizes .. \$1 | <input type="checkbox"/> 10° PHILCO SPEAKER Top Quality .. Large Magnet .. \$2.69 | <input type="checkbox"/> 50 — TUBE CARTONS (colored) assorted sizes for Popular Tubes .. \$1 | |
| | | <input type="checkbox"/> 4 — TV ALIGNMENT TOOLS most useful assortment .. \$1 | |

Circle 127 on reader's service card

FREE!

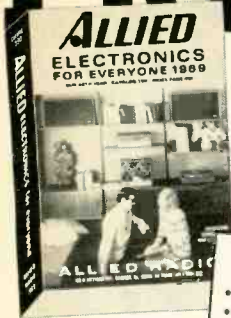

**NEW 1969
ALLIED
CATALOG**
**536
PAGES**

SAVE ON:

- Electronic & Hobby Kits
- Stereo Hi-Fi
- Tape Recorders, Tape
- CB 2-Way Radios
- Walkie-Talkies
- FM-AM & AM Radios
- Shortwave Receivers
- Portable TV
- Phonographs
- Amatec Gear
- Intercoms & PA
- Automotive Electronics
- Test Instruments
- TV Antennas & Tubes
- Power Tools, Hardware
- Tubes, Transistors
- Parts, Batteries, Books

**TOP SAVINGS ON
THE BEST IN
ELECTRONICS
FOR EVERYONE**

Shop by mail and save at Allied, world's largest electronics headquarters. Hundreds of money-saving values. NO MONEY DOWN. Up to 2 years to pay!


**MAIL COUPON
BELOW**

ALLIED RADIO, Dept. 047 Please
P.O. Box 4398, Chicago, Ill. 60680 Print

NAME _____
First Middle Last
ADDRESS _____
CITY _____
STATE _____ ZIP _____

Circle 128 on reader's service card

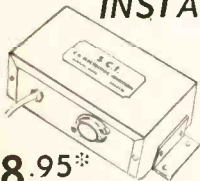**MORE POWER!
MORE GAS MILEAGE!
INSTANT START!**



—all through
SCI electronic
ignition

\$28.95*

SCI MODEL CD-101 provides 32,000 volts evenly from ignition turn-on to full power. Gas combustion is at peak efficiency always due to uniformity of spark. Voltage is constant no matter how cold your battery. Plugs and points usually last 3 times longer. You'll feel the difference both in the performance of your car and the savings in your pocket. The SCI electronic ignition is complete, contains eight high reliability semi-conductors and is hand-wired on a rugged fibreglass circuit board. Simple installation. Guaranteed for ninety days. (For negative ground vehicles only.)

SCI P.O. BOX 27 (RE)
BOSTON, MASS. 02131

Enclosed is \$28.95* (plus 75¢ shipping and mailing cost) for one SCI MODEL CD-101 electronic ignition.

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____


Circle 129 on reader's service card

NOTE- WORTHY CIRCUIT

UNUSUAL TUNABLE NOTCH FILTER

One of the unique characteristics of the FET is that it can be used as a voltage-controlled variable resistor. The diagram shows how FET's were used as variable series-leg resistors in a bridged-T notch filter in an audio spectrum analyzer described in *Electronic Engineering* (London, England).

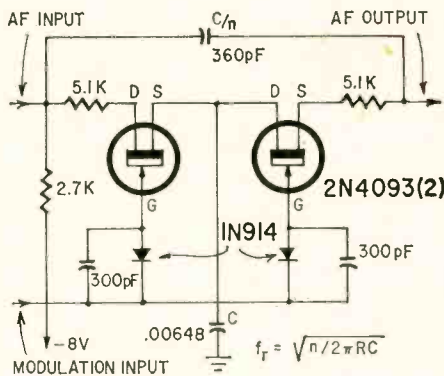The resonant frequency of the filter equals $\sqrt{n/2\pi RC}$ where R equals the sum of the fixed resistor and drain-source resistance of the FET in each series leg, C is the value of the grounded capacitor and n is the ratio of the two capacitors. The value of n is determined by the desired attenuation, the characteristics of the associated am-



plifier and other factors. The author, M. Bronzite, selected a value of 18 which yields a peak attenuation of 20 dB.

The FET's are driven to saturation and to full off by a modulating voltage in the range of 100-500 kHz. They have an impedance of around 100 ohms when on. The value of the fixed series resistors should be around fifty times the on impedance of the FET's to minimize the effects of variations in transistor characteristics. In the spectrum analyzer, the effective resistance of each series leg varied over a range of 1 to 20 with modulation. **R-E**

In January . . .

A computer expert takes the mystery out of logic circuits with a detailed explanation of JK flip-flops and other bistable digital circuits.

NEW! SOLID STATE KITS

FOR ANY
TAPE RECORDER



Automatic Recording-Level Control

Low-noise distortionless compressor — preamp easily installs in mike line. Easy-to-build kit with complete instructions.

MODEL ACP-1 KIT . . . \$18.50

Voice / Sound Actuated Controller

Voice operate any tape recorder, ham and CB transmitter. Ideal for intrusion alarms. Built-in relay switches up to 1 amp. Easy-to-build kit with complete instructions.

MODEL VOX-1 KIT . . . \$18.50

Other Kits

**Audio Amplifiers ■ Power Supplies
Test Equipment ■ Treasure Locators
and many others**

FREE Data sheets with circuit description, diagram and specifications for all kits.



CARINGELLA ELECTRONICS, Inc.
P.O. Box 327 ■ Upland, California 91786
Phone 714-985-1540

Circle 130 on reader's service card

TUBE TESTER OWNERS

WE HAVE THE
LATEST TUBE
DATA AND
ADAPTERS
FOR →

Don't let your
tube tester
become
obsolete

- EICO
- HEATH
- JACKSON
- KNIGHT
- MERCURY
- NRI-CONAR
- PRECISION
- SYLVANIA

CLIP AND MAIL COUPON TODAY

• COLETRONICS SERVICE INC.
• 1744 Rockaway Ave.,
• Hewlett, N.Y. 11557
• Please send me information on
• Model No. _____ and Make _____
• Name _____
• Address _____
• City _____ State _____ Zone _____

Circle 131 on reader's service card

NEW BOOKS

ARITHMETIC REVIEW FOR ELECTRONICS, by Nelson M. Cooke and Herbert F. R. Adams. McGraw-Hill Book Co., 330 W. 42 St., New York, N.Y. 10036. 6 1/4" x 9 1/4", 176 pp. Paperback, \$3.50

A review for those planning a systematic study of electronics. Provides tips on studying, problem-solving and taking exams. After a review of addition, subtraction and division, other chapters cover fractions, decimals, percentage, squares and square roots. Chapters have problems and solutions as well as review questions.

THE RADIO AMATEUR'S HANDBOOK, prepared by the ARRL Staff, edited by Doug DeMaw, W1CER. American Radio Relay League, Newington, Conn. 06111. 6 1/2" x 9 1/2", 704 pp. including 46 pp. amateur equipment catalog. Cloth, \$6.50 in US, its possessions and Canada; \$7.00 elsewhere.

Once again the ham's bible on communications, electronic theory, design and construction has been updated with a vast amount of new material on solid-state techniques, applications and equipment. Long used as a standard textbook for hams of all levels and a handy reference work for students and men in the communications industry, this edition is printed on no-gloss paper.

Many of the construction projects that have been standards in earlier issues have been replaced by new ones that reflect recent advances in electronic technology. Transistor and tube data charts and reference tables have been revised.—*W2PWG*

SEMICONDUCTOR AND TUBE ELECTRONICS, AN INTRODUCTION, by James G. Brazee. Holt, Rinehart & Winston, Inc., 383 Madison Ave., New York, N.Y. 10017. 6 1/4" x 9 1/4", 651 pp. Cloth, \$10.95

An introductory analysis of electronic devices and their applications in basic circuits. The book presents a graphical and numerical introduction to the analysis and utility of electronic devices. The first half of the book presents all devices in a theoretical sense while the latter half shows them in actual practical applications.

WESTINGHOUSE SILICON POWER TRANSISTOR HANDBOOK. Westinghouse Electric Corp., Semiconductor Division, Youngwood, Pa. Spiral-bound, \$2.00

Slanted toward the design engineer, but loaded with valuable power construction tips for the experimenter. Chapters cover theory, maximum ratings, cooling, power switching, inverters, linear appliances, high-frequency measurement and transistors, power transistor procurement and reliability. Data sheets included on many Westinghouse transistors. **R-E**

The First Really New INDOOR ANTENNAS!

Now, at last, your customers have a reason to get rid of their tired old droopy rabbit ears. The Gavin series of monitor antennas not only look better, they work better too.


Check these quality features:

- TOWER DESIGN GETS UP WHERE THE SIGNAL IS FOR EXTRA POWER.
- GUARANTEED TO GIVE YOUR CUSTOMERS BETTER RECEPTION OR MONEY REFUNDED.
- ROTATING SCANNER — You can aim for best pictures without turning base. No danger of scratching furniture.
- HIGH IMPACT PLASTIC CASE WITH DEEP FELT PAD.
- UHF/VHF FUNCTION SWITCH AND PHASING SWITCH.

For more details, contact your GAVIN representative today, or call:



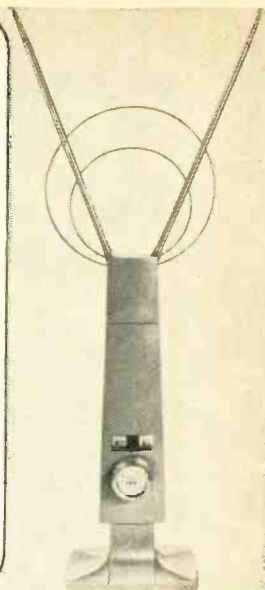GAVIN INSTRUMENTS, INC.
Subsidiary of ADVANCE ROSS CORP.
Somerville, New Jersey 08876, U.S.A.
Telephone: (201) 356-3500



Circle 132 on reader's service card

SCHOOL DIRECTORY

distinguished graduates

hold important engineering and business administration posts throughout U.S. Professionally-oriented college with outstanding placement record. Four-quarter year permits degree in three years. Fine faculty. Modern labs. Small classes. 300-acre campus. Accredited. Approved for vets. Modest costs. Enter Jan., March, June, Sept. For Catalog, write Adm. Director.
TRI-STATE COLLEGE
24128 College Avenue, Angola, Indiana 46703



GET INTO ELECTRONICS

V.T.I. training leads to success as technicians, field engineers, specialists in communications, guided missiles, computers, radar and automation. Basic & advanced courses in theory & laboratory. Electronic Engineering Technology & Electronic Technology curricula both available. Associate degree in 29 mos. B.S. also obtainable. G.I. approved. Graduates in all branches of electronics with major companies. Start Feb., Sept. Dorms, campus. High school graduate or equivalent. Catalog.

VALPARAISO TECHNICAL INSTITUTE
Dept. C, Valparaiso, Indiana 46383



A New Way To Study At Home ENGINEERING MATHEMATICS

Get all the math you need for electronic engineering from I.H.S.I. Two great new courses for the man who wants to get ahead. Created by college professors. Study at home as fast as you want. No classes to hold you back. No contract to sign. Every lesson comes with A MONEY BACK GUARANTEE. Get the information today—Free!

THE INDIANA HOME STUDY INSTITUTE
Dept. R P.O. Box 1189 Panama City, Fla. 32401

COMING IN JANUARY

What's behind hi-fi amplifier specs? A central problem with published specs for any piece of audio gear is: How well do they describe the listening quality of the component? If you're in the market for a hi-fi amplifier—or wondering about the performance of your present amplifier—don't miss this informative article next month.



FREE Catalog Of The WORLD'S FINEST GOV'T SURPLUS ELECTRONIC BARGAINS

Now **BIGGER and BETTER Than Ever!**

MAIL THIS COUPON NOW!

NAME: _____

ADDRESS: _____

CITY: _____ STATE: _____ ZIP NO.: _____

FAIR RADIO SALES • Box 1105 • Lima, Ohio 45802

Circle 133 on reader's service card

MARKET CENTER

GENERAL

MAGNETS. All types. Specials—20 disc magnets, or 2 stick magnets, or 10 small bar magnets, or 8 assorted magnets, \$1.00. **MARYLAND MAGNET COMPANY**, 5412-G Gist, Baltimore, Maryland 21215.

BACK DATE MAGAZINES! Send needs—**MID-TOWN**, Box 934-RE, Maywood, N.J. 07607.

TREASURE HUNTERS! PROSPECTORS! Relco's new instruments detect buried gold, silver, coins. Kits, assembled models. Transistorized. Weighs 3 pounds. \$19.95 up. Free catalog. **RELCO-A25**, Box 10839, Houston, Texas 77018

ELECTRONICS

CATHODIC PROTECTION INSTRUCTIONS \$1.00. **F. F. KNAPP**, P. O. Box 854, Scottsdale, Arizona 85252.

"ARCTURUS" SALE

- Tube cartons 6AU6 etc. size, \$2.15 per 100. 6SN7 etc. size, \$2.55 per 100. 5U4GB size, \$2.95 per 100. 5U4G size, .03¢ each.
 - 7" 90° TV bench test picture tube with adapter. No ion trap needed. Cat. #78P7. \$7.99.
 - Silicon rectifier, octal-based replacement for 5U4, 5V3, 5AS4, 5AW4, 5T4, 5V4, 5Z4. With diagram. Cat. #Rect 1, 99¢ each.
 - 5 transistor circuit boards containing up to 6 transistors, plus diodes, resistors, capacitors, etc. Cat. #TB10, 99¢.
 - Kit of 30 tested germanium diodes. Cat. #100, 99¢.
 - RCA-110° flyback transformer, latest type, includes schematic diagram applicable to any TV. Cat. #BR-1, \$2.99.
 - Color yokes, 70° for all round color CRT's. Cat. #XRC70, \$12.95. 90° for all rectangular 19 to 25" color CRT's. Cat. #XRC90, \$12.95.
 - Transistorized U.H.F. tuners used in 1965 to 1967 TV sets made by Admiral, RCA, Motorola, etc. Removable gearing may vary from one make to another. Need only 12 volts d.c. to function. No filament voltage needed. Easy replacement units. Cat. #U.H.F.567, \$4.95.
 - U.H.F. Tuner—original units as used in TV sets such as RCA, Admiral, etc. covering channels 14 through 82, as part #94D173-2. Complete with tube. Drive gearing is removable. Can be used in most sets. Cat. #U.H.F. 3—\$4.95.
 - F.M. tuner—Hi-Fi amplifier tuning unit. Tunes from 88 to 108 mc. Contains two 10.7 Mc. I.F. transformers, one 10.7 sound discriminator, R.F. oscillator and mixer stages and 12DT8 tube. I.F.'s are standard "K" type. Circuit diagram for building F.M. radio is included. Also plan for building F.M. tuner. Sam's photofact #620 shows 2 applications. 1 for radio, 1 for Hi-Fidelity tuner and amplifier. Cat. #FM-20, \$4.95.
- Send for our free catalog listing thousands of similar best buys in tubes, parts, kits, transistors, rectifiers, etc. Orders under \$5.00—\$1.00 handling charge. Include 4% of dollar value of order for postage. Canadian postage \$1.00 extra.

ARCTURUS ELECTRONICS CORP.
502-22nd St., Union City, N.J. 07087 Dept. MRE
Phone: 201-UN 4-5568

Circle 134 on reader's service card

7 pin miniature **TUBE TEST SOCKET ADAPTER** \$1.65 value only \$1.00. 33 VF-35V tantalum electrolytic capacitor \$4.50 value 5 for \$2.00. 120 volt NPN transistor 2N2201 \$6.90 value only \$1.00. 14" x 12" fiberglass epoxy printed circuit board, an \$8.00 value only \$3.95. Catalog 20¢. **FRANK'S SCIENTIFIC CO.**, P. O. Box 156, Martelle, Iowa 52305.

CONVERT any television to sensitive Big-Screen Oscilloscope. Only minor changes required. No electronic experience necessary. Illustrated plans \$2.00. **RELCO-A25**, Box 10563, Houston, Texas 77018


JAPANESE ELECTRONICS NEW PRODUCTS MONTHLY! Only \$1. Satisfaction/Refund. **DEE 10639-RE** Riverside, North Hollywood, Calif. 91602

FREE CATALOG of unusual electronic, scientific gadgets, parts, plans, kits. **FRANKS SCIENTIFIC CO.**, P. O. Box 156, Martelle, Iowa 52305.

SIGNATURE STAMP—\$2.80. Regular 3 or 4 line—\$1.50 (Special designs, send sketch). **Frost**, 17639—67CT, **TINLEY PARK, ILL.** 60477.

LIKE MUSIC WITHOUT COMMERCIALS?

The **SCA-2B Sub-Carrier Adapter** makes it possible for you to enjoy the background music transmitted on a 67KHz sub-carrier on many FM stations. (These programs cannot be heard on a FM set without an adapter) In the US there are approximately 400 FM stations authorized by the FCC to transmit the 67KHz programs. If you are within 50 miles of a city of 100,000 or more, it is probable that you are within the satisfactory reception range of one or more of these stations. If in doubt write for a list of such stations in your area.

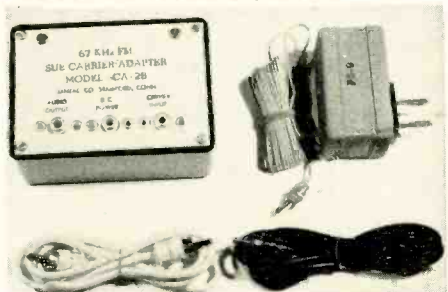

Patent Pending
Sub-Carrier Adapter, Model SCA-2B with two 36" shielded cables. Price \$39.95.
117 Volt AC Operated Power Supply, PS-9, Price \$4.95.

SCA-2B FEATURES
SIZE: 4" x 2 3/4" x 1 1/2". • Simple plug-in connections to your FM tuner/amplifier. (If your FM tuner does not have a multiplex output jack, we supply hook-up information). • No installation adjustments • All silicon transistors • Operates from our PS-9 Power Supply or 6 to 12 volts D.C.
One Year Factory Guarantee
For Custom Installations: Completely Wired SCA-2 PC card (size: 2 1/2" x 3" x 3/4") with installation instructions for \$34.95. Also available SCA-2 installed in AC operated Panasonic 7-Transistor AM-FM Radio Model RE6137 \$59.95.

Write for Dealer Quantity Discounts.
Commercial use of these units is not advised, unless the consent of the originating station is obtained.
Send order to **KENZAC Co.**
P.O. Box 66251, Houston, Texas 77006

Circle 135 on reader's service card

RADIO-ELECTRONICS does not assume responsibility for any errors which may appear in the index below.

Allied Radio Corporation	92
Arcturus Electronics Corporation	94
B & K (Division of Dynascan Corporation) 17,	71
Brooks Radio and TV Corporation	91
Burstein-Applebee Company	70
Capitol Radio Engineering Institute, The ..	28-31
Caringella Electronics, Inc.	92
Castle TV Tuner Service, Inc.	7
Cleveland Institute of Electronics	16, 62-65
Coletronics	92
Cornell Electronics Company	96
Delta Products, Inc.	12, 26
Electro-Voice, Inc.	56
EMC (Electronic Measurement Corporation).	66
Fair Radio Sales	93
Finney Company	27
Gavin Instruments, Inc. (Subsidiary of	
Advance Ross Corporation)	93
Grantham School of Electronics	1
Heald Colleges	6
Heath Company	84-87
International Crystal Mfg. Company	98
International Resistance Corporation	88
Jerrold Electronics Corporation	
(Distributor Sales Division)	53
E. F. Johnson Company	81
Judson Research and Manufacturing	
Company, Inc.	91
Karlson Research and Manufacturing	89
Kenzac Company	94
Lafayette Radio Electronics	80
Leader Test Instruments	54
Lectrotech, Inc.	67
Loral Distributor Products (Division	
of Loral Corporation)	55
Mercury Electronics Corporation	79
Microflame, Inc.	70
Multicore Sales Corporation	90
Music Associated	91
Myriad Products Corporation	90
National Radio Institute	8-11
Olson Electronics, Inc.	89
Pace Communications	14
Perma-Power Company	82
Pioneer Electronics	
U. S. A. Corporation	Cover III
Poly Paks	97
RCA Electronic Components	
Semiconductors	75
Test Equipment	24-25
Tubes	Cover IV
RCA Institutes	18-21
RCA Parts and Accessories	5
Record-O-Fone (Division of Electro	
Space Corporation)	74
Rye Industries, Inc.	66
Sams & Company, Inc. Howard W.	12, 73
Schober Organ Corporation, Inc.	16
SCI Electronic Ignition	92
Scott, Inc., H. H.	23
Sencore	83
Shure Brothers, Inc.	13
Simpson Electric Company	15
Solid State Sales	95
Sonar Radio Corporation	72
Surplus Center	89
Triplet Electrical Instrument Company. Cover II	
Xcelite, Inc.	22
Zenith	74
MARKET CENTER	94-97
Chemtronics	
Edmund Scientific Company	
McGee Radio	
United Radio Company	
Warren Electronic Components	
Wel-Dex Manufacturing Company	
SCHOOL DIRECTORY	93
Indiana Home Study Institute, The	
Tri-State College	
Valparaiso Technical Institute	
CLASSIFIED	94-97

New Sensitive TREASURE METAL DETECTORS. New low prices. Professional models from \$29.95 to \$129.50. Write for free catalog today. **JETCO ELECTRONICS**, Box 132-RE, Huntsville, Texas. 77340

NO MORE BATTERY TROUBLE for the life of your car with VX-6. Write for free brochure. **FULLER DISTRIBUTOR** 728 Hummel Lemoyne, Penna. 17043.

RECEIVING & INDUSTRIAL TUBES, TRANSISTORS, All Brands—Biggest Discounts. Technicians, Hobbyists, Experimenters—Request FREE Giant Catalog and **SAVE! ZALYTRON**, 469 Jericho Turnpike, Mineola, N.Y. 11501.

RADIO & TV TUBES 33¢ each. One year guaranteed. Plus many unusual electronic bargains. Free catalog. **CORNELL** 4217 E University, San Diego, California 92105

OSCILLOSCOPE improvement kits. High speed Triggersweep eliminates sync problems. Dual trace FET switch displays two wave-forms together. **SOLID-STATE SERVICES**, P.O. Box 901, Cupertino, California 95014

Discharge IGNITION, PHOTOFLASH. Free catalog parts, kits. **TRANSPARK**, Carlisle, Mass. 01741

SOLAR FLYING SAUCERS—(New sun powered—no motors) How to build easily for less than \$5 using styrofoam and plastic bags. Many sizes—designs. Complete descriptions, plans, drawings, \$1. Guaranteed. **SPACETRONICS** Box 31043-RE, San Francisco, Calif. 94131.

"COIL WINDING" HANDBOOK—50¢. Experimenter's catalog includes 250 exclusive items—25¢, refundable. **LABORATORIES**, 12041—B Sheridan, Garden Grove, Calif. 92640.

TELEPHONE-RECORDER ACTUATOR (TWI-007) \$22.85. Automatically turns tape recorder on when line in use. Telephone "bug" (TWI-004) \$21.95. Surveillance recorders (TWI-1000, TWI-1010). **TWILIGHT ELECTRONICS**, Box 11595-M, St. Louis, Missouri 63105.

INVENTIONS & PATENTS

MANUFACTURERS NEED NEW ITEMS! B. F. Goodrich, Black & Decker, South Bend Tackle and other million dollar corporations have authorized us to locate new products. For details regarding development, sale, licensing of your patented/unpatented invention, write: **THE RAYMOND LEE ORGANIZATION**, 230-U Park Avenue, New York City 10017

INVENTIONS WANTED. Patented; Unpatented. **GLOBAL MARKETING**, 2420-AE 77th Ave., Oakland, Calif. 94605

AUDIO — HI-FI

Tape-mates makes available to you ALL 4-TRACK STEREO TAPES. All labels—postpaid to your door—at tremendous savings. For free brochure write: **TAPEMATES CLUB**, 5280 RE West Pico Blvd., Los Angeles, Calif. 90019.

TAPE RECORDER SALE. Brand new nationally advertised brands, \$10.00 above cost. Amazing discounts on stereo components. **ARKAY ELECTRONICS**, 1028 E Commonwealth Avenue, Boston, Mass. 02215.

WRITE for highest discounts on components, recorders, tapes, from franchised distributors. Send for FREE monthly specials. **CARSTON**, 1686-R Second Ave. N.Y.C. 10028

SPEAKER REPAIR. Hi-Fi, guitar, organ speakers recond good as new at fraction of new speaker price. For details and Reconding Center in your area write **WALDOM ELECTRONICS, INC.** 9155-4, Dept. RE. 4625 W. 53rd St., Chicago, Ill. 60632

HI-FI COMPONENTS, Tape Recorders, at guaranteed "WE will not be undersold" prices. 15-day moneyback guarantee. Two-year warranty. NO Catalog. Quotations Free. **HI-FIDELITY CENTER**, 239R East 149th St., N.Y., N.Y. 10451

MAIL ORDER

SHOPPING MART

EXCELLENT for XMAS GIFTS!

A selection of products available by mail for readers of Radio Electronics. All merchandise sold on a money-back guarantee. Order direct by Stock Order No. Send check or M. O.

SEE YOUR MUSIC IN DAZZLING ACTION with



Music Vision

Dramatic Breakthrough In Audio-Visual Enjoyment

Now you can have a thrilling psychedelic "see-in" right in your own home, club, school or business—in fact—anywhere you want to add sensational "mod" effects. Colored light beams dance and prance, whirl and swirl in perfect time with the music—each individual note creating its own unique twisting, radiating shape. Adds a spectacularly wild, new dimension to the world of music and entertainment. Combines electronics, science and art with dramatic results.

Attaches in seconds to your radio, tape recorder, hi-fi or stereo with two alligator clips. Can be used on small screens, large walls, stages and whole auditoriums. Build your own Music Vision* with low-cost Do-It-Yourself KIT. Loads of fun! Fast! Easy! All you need is a light source. If you don't have one, the versatile Edmund 35mm 500 Watt Projector is a terrific bargain. All kinds of other uses in 15" x 15" x 27" Walnut Cabinet Model. Tube Unit, or 8" and 12" Sets which include encased 8" or 12" Motion-Color Wheel and set of apertures for use with our effects for commercial applications. Large 12" set provides fabulous

Order by stock number listed below. Money-back guaranteed. Complete information in new catalog. If you want additional details now, send 25¢ in coin for fully illustrated, 16-page Booklet No. 9096EH. *Introduction to Music-Vision* ■ 8" DO-IT-YOURSELF KIT, Stock No. 71,009EH, \$22.50 Ppd. ■ EDMUND 500 Watt 35mm PROJECTOR, Stock No. 71,057EH, \$24.50 Ppd. ■ 8" SET (Motionizer, color wheel, apertures) Stock No. 71,030EH, \$45.00 Ppd. ■ 12" SET (Same as above w/larger Motionizer), Stock No. 71,032EH, \$57.50 Ppd. ■ WALNUT VENEERED CABINET MODEL, Stock No. 85,184EH, \$99.50 F.O.B.

*Patent pending.



3" ASTRONOMICAL TELESCOPE

See stars, moon, phases of Venus, planets close up. 60 to 180 power—famous Mt. Palomar reflecting type. Aluminized & overcoated 3" diameter f/10 primary mirror, ventilated cell. Equipped with 60X eyepiece and mounted 3X finder scope, hardwood tripod. FREE: "STAR CHART"; 272-page "HANDBOOK OF HEAVENS"; "HOW TO USE YOUR TELESCOPE"

Stock No. 85,050EH \$29.95 Ppd.

4 1/4" REFLECTOR TELESCOPE

Stock No. 85,105EH \$64.50 FOB

6" REFLECTOR TELESCOPE

Stock No. 85,086EH \$199.50 FOB



NICKEL-CADMIUM BATTERY BARGAIN!

Terrific value—slightly used gov't surplus. Lightweight 5 cell, 6 volt, 4 Amp-hour battery with almost unlimited life. Extremely high current output. Recharges in 1 hour when left discharged. Minimum maintenance—few drops of water per year. Rugged, shock-and-vibration resistant nylon case. Delivered partially charged, filled with electrolyte. 3 1/8" x 2" x 6" 2 lb.

Stock No. 70,942EH (battery) \$15.00 Ppd.

Stock No. 70,807EH (charger kit) \$ 8.00 Ppd.

GET FREE CATALOG



148 PAGES — 1000's OF BARGAINS

Completely new 1969 edition. New items, categories, illustrations, dozens of electrical and electronic parts, accessories. Enormous selection of Astronomical Telescopes, Microscopes, Binoculars, Magnifiers, Magnets, Lenses, Prisms. Many surplus items for hobbyists, experimenters, workshops, factory. Mail coupon for catalog "EHC".

NAME.....
ADDRESS.....
CITY.....
STATE..... ZIP.....

ORDER BY STOCK NUMBER • SEND CHECK OR MONEY ORDER • MONEY-BACK GUARANTEE

EDMUND SCIENTIFIC CO. 300 EDSCORP BUILDING BARRINGTON, NEW JERSEY 08007

Circle 136 on reader's service card

YOUR SERVICE AND QUALITY LEADER

We promise to supply you with the highest quality products at the most attractive prices with the fastest service in the industry.

AVALANCHE MODE TRANSISTORS, used for TRIGGERING SCR's & TRIACS with diagrams. 3/\$1.00

ZENERS

1 Watt 6.8-68V \$.40
10 Watt 6-200V \$.75

MOUNTING HDWE KITS

These kits are used to mount our SCR's, zeners, & rectifiers etc.
6 x 32 stud 6 sets/\$1.00
1/4 x 28 stud 4 sets/\$1.00

1 AMP CONTROLLED AVA-LANCHE RECTIFIERS

PRV	AMP	(top hat & epoxy replacements)
100	.07	
200	.09	
400	.12	
600	.18	
800	.22	
1000	.35	

N-CHANNEL PLASTIC TO-18 FET'S. Low noise, low leakage, gate current, gain to 9000µ mhos. \$1.00

IN2326 voltage & temperature compensating diodes 4/\$1.00

TRIACS

TO-66
5 AMPS

PRV	
100	.90
200	1.40
300	1.75
400	2.25
500	2.60

CADMIUM SELENIDE PHOTO CONDUCTIVE CELLS. Dark resistance of 500 megohms. Sensitivity of 1.4-99 µa/ft candle with data sheet \$1.00

500 Hfe PLASTIC TRANSISTORS (NPN) TO-18, S1 unit sim to 2N3565. 4/\$1.00

HIGH-VOLTAGE NPN 150V VBCBO at 2.5A, hi gain in TO-66 pack \$.75

2N1163 a TO-3 PNP GERMANIUM TRANSISTOR rated at 35v and a gain of 50 at 25 amps. \$1.75

Silicon Power Rectifiers

PRV	3A	12A	40A
100	.09	.30	.75
200	.16	.50	1.25
400	.20	.70	1.50
600	.30	1.00	1.80
800	.40	1.25	
1000	.55	1.50	

INTEGRATED CIRCUITS



LINEAR CIRCUITS

FM IF AMPLIFIERS \$.90
702C WIDE BAND DC AMPL. \$ 3.50
709C OPERATIONAL AMP. \$ 4.50
710C HI SPEED DIFF. COMPARATOR \$ 5.00
711C DUAL COMPARATOR \$ 5.00

DIGITAL RTL CIRCUITS

2-914 QUAD 2 INPUT GATE \$1.25
901 BUFFER \$1.25
925 DUAL 2 INPUT GATE EXPANDER \$1.25
923 JK FLIP FLOP \$1.25
2-923 DUAL JK FLIP FLOPS \$1.50

NEON LIGHT OF NIXIE TUBE DRIVERS. An NPN, TO-18, Si Transistor with a V_{CEO} of 120 3/\$1.00

UNIUNCTIONS

Similar to 2N2419 Rbb of 5-7, stand off ratio of .6 and Ip of 12, with data sheet \$1.50

Silicon Control Rectifiers

PRV	3A	7A	20A	70A
50	.35	.45	.70	
100	.50	.65	1.00	4.00
200	.70	.95	1.30	8.00
300	.90	1.25	1.70	
400	1.20	1.60	2.10	12.00
500	1.50	2.00	2.50	
600	1.80	2.40	3.00	16.00
700	2.20	2.80	5.00	

Terms: FOB Cambridge, Mass. Send check or Money Order. Rate companies 30 days net. Include Postage, Average Wt. per package 1/2 lb. No COD's. Minimum Order \$3.00



POST OFFICE BOX 74D
SOMERVILLE, MASS. 02143
TELEPHONE (617)547-4005

Send For Our Latest Catalog Featuring Transistors and Rectifiers
325 Elm Street, Cambridge, Mass.

Circle 137 on reader's service card

SILICON RECTIFIER SALE

IMMEDIATE DELIVERY
FULLY GTD NEWEST TYPE
AMERICAN MADE FULLY TESTED



1 AMP TOP HAT AND EPOXIES

PIV	SALE	PIV	SALE	PIV	SALE
50	.05	800	.18	1800	.80
100	.07	1000	.27	2000	1.20
200	.08	1200	.40	3000	1.40
400	.10	1400	.52	4000	1.85
600	.14	1600	.67		

"SILICON POWER DIODE STUD MOUNT"

PIV	3A	6A	12A	50A	100A	160A
50	.06	.16	.20	.50	.85	2.25
100	.07	.21	.25	.73	1.05	2.65
200	.09	.29	.38	1.23	1.60	3.50
400	.15	.39	.49	1.45	2.50	4.25
600	.19	.53	.73	1.75	3.75	6.50
800	.29	.74	.95	2.20		
1000	.38	.85	1.10	2.60		

SPECIALS! SPECIALS! SPECIALS!
Stud Rect. 25 AMP-500 PIV—
\$1.05 Ea. or 10 for \$9.00 Special

Fil. Trans. 117V at 6.3V C.T. 10 AMP Special \$1.25

Sangamo Type DCM 10000 MFD 25 VDC \$.85 Ea.

Heat Sink 2 LBS 500 AMP
Value \$7.00 your cost \$1.40

Westinghouse 160 AMP, 500 PIV SILICON HI-POWER
STUD RECTIFIER IN1666.
Limited quantity. \$5.10 ea. 10 for \$45.00

100 Different Precision Resistors
1/2—1—2 Watt 1/2%—1% TOL \$1.25

Asst transistor Kit. P.N.P.—N.P.N.
All popular types. Unchecked
100 for \$2.95 500 for \$9.95

Computer Grade Condenser 15,500 MFD
12 VDC American Mfg. .75 ea.

NEW DIODE KIT ALL POPULAR TYPES
IN34, IN34A, IN48, IN60, IN64 etc. 100 for \$ 4.00
BEST QUALITY 500 for \$15.00

Money Back guarantee. \$2.00 min. order. Include
additional \$ for postage. Send check or money
order. C.O.D. orders 25% down.

Warren Electronic Components

230 Mercer St., N. Y., N. Y. 10012 • 212 OR 3-2620

Circle 138 on reader's service card

MARKET CENTER

RENT 4-track open reel tapes—all major labels
—3,000 different—free brochure. STEREO-
PARTI, 55 St. James Drive, Santa Rosa, Ca.
95401

Color TV TECHNICIAN. Expanding southern
California service company needs outside techni-
cians and bench technicians. Good salary,
incentive plan, paid vacations, etc. Send
resume of experience and salary requirements.
MICRO ELECTRONICS, 1903F W. Vista Way,
Vista, Calif. 92083.

WANTED

MONEY—SPARETIME OPPORTUNITY PANEL-
ISTS AT HOME WANTED BY NEW YORK RE-
SEARCHER. Leading research firm seeking peo-
ple to furnish honest opinions by mail from
home. Pays cash for all opinions rendered.
Clients' products supplied at no cost. For in-
formation write: RESEARCH 669, Mineola, N. Y.
11501, Dept. LN-24N

QUICK CASH . . . for Electronic EQUIPMENT,
COMPONENTS, unused TUBES. Send list now!
BARRY, 512 Broadway, New York, N. Y. 10012,
212 WALKER 5-7000

SERVICEMEN • EXPERIMENTERS!

IF YOU WISH TO PURCHASE BRAND NEW TUBES

RECEIVING—SPECIAL PURPOSE BC
TUBES AT OUTSTANDING MONEY SAV-
ING VALUES.

WE HAVE THE MOST UP TO DATE TUBES
LISTED PLUS THE HARD TO GET TYPES.
DON'T CONFUSE OUR TUBES WHICH
ARE NEW WITH THE PULLOUTS AND
REJECTS.

SEND FOR OUR CATALOG.

UNITED RADIO COMPANY
ESTAB. 1920

56 FERRY ST., NEWARK, N.J. 07105

ONE YEAR GUARANTEE! TUBES!

33¢

PER TUBE

100 OR
MORE TUBES

30¢

ea.

Special!

With Every \$10 Order,
25¢ PER TUBE

Your Choice
Of These Sizes

6AG5 6SN7
6W4 6B6
6AU6 6J6

CORNELL

6D6	OZ4	6AU4	6X4
6DA4	1B3	6AU5	6X8
6DE6	1H5	6AU6	7B6
6DQ6	1J3/1K3	6AV6	7C5
6EA7	1L4	6AW8	7N7
6EM5	1T4	6AX4	7Y4
6F6	1U4	6BA6	10DE7
6FQ7	1X2	6BC5	12AE6
6GH8	3BZ6	6BG6	12AT7
6H6	3DG4	6BJ6	12AU7
6J5	5U4	6BL7	12AX7
6J6	5U8	6BN4	12BA6
6K6	5V4	6BN6	12BE6
6S4	5Y3	6BN8	12BH7
6SA7	6A6	6BQ6	12C5
6SH7	6A8	6BQ7	12SN7
6SK7	6AB4	6BZ6	12W6
6SL7	6AC7	6C4	25L6
6SN7	6AF4	6C6	25Z6
6SQ7	6AG5	6CB6	35W4
6U7	6AK5	6CD6	84/6Z4
6V6	6AL5	6CG7	5687
6W4	6AN8	6CG8	6350
6W6	6AQ5	6CM7	6463
	6AT6	6CZ5	7044
	6AT8		

Tubes are New or Used and So-
Marked Lab Tested, Ind. Boxed,
Branded & Code Dated

Prestige & Success as an ELECTRONICS EXPERT!



HOME
STUDY COURSES

TV SERVICING
\$3.50

RADIO SERVICING
\$3.00

BOTH COURSES \$6.00

2 STATION INTERCOM

12⁹⁵

A.C. 110 VOLT
TRANSISTORIZED
INTERCOM!

ONE YEAR GUARANTEE! DUMONT TUBES!



Brand New Except Glass!

TUBE TYPE	DUD DEP.	TUBE PRICE
19XP4	3.00	21.95
21AMP4	1.00	14.95
21CBP4	1.00	14.95
21CEP4	3.00	18.95
23FP4	5.00	24.95
21FJP22	20.00	79.95
23EGP22	35.00	119.95
25AP22	27.50	99.95
23AHP4	5.00	24.95
24AEP4	1.00	22.95

Please remit full tube price plus
dud deposit with order. Dud de-
posit will be returned immedi-
ately upon postpaid return of dud.
No C.O.D.'s on picture tubes. All
duds returned for refund must be
under full vacuum.

FREE!
CORNELL'S
NEW
CATALOG!
WRITE FOR
YOUR COPY
TODAY!

RED & BLACK TUBE CARTONS

High Gloss, Clay Coated, Built in Diag. Partitions

SIZE	TUBE SIZE	10 CARTONS	100 CARTONS
MIN.	6AU6	.29	2.59
GT.	6SN7	.39	3.49
LG.GT	5U4GB	.59	5.29
G.	5U4G	.89	7.99

NO SUBSTITUTIONS WITHOUT YOUR PERMISSION!
YOUR ORDER FREE IF NOT SHIPPED WITHIN 24 HRS.

Terms: Orders over \$5.00: Add 3c per tube shipping. Prepay in full
and avoid C.O.D. charges. Send \$3.00 deposit on C.O.D. orders.
Orders under \$5.00: Add 3c per tube plus 50c handling. Canadian
and Foreign Orders: add approx. postage. No C.O.D. orders. Com-
bine varied orders to bring order over \$5.00.

Circle 139 on reader's service card

EXPERIENCED RADIO-TV TECHNICIANS WANTED. Salary \$125-\$150. VOICE AND VISION, West Lebanon, N. H.

EDUCATION/INSTRUCTION

ACCREDITED CANADIAN ELECTRONICS TRAINING day, night, home study courses. Free booklet. **RADIO COLLEGE OF CANADA**, 461 King St. West, Toronto 2B, Ontario Canada.

FCC First Class License in six weeks—nation's highest success rate—approved for Veterans Training. Write **ELKINS INSTITUTE**, 2603E Inwood Road, Dallas, Texas 75235

COMPUTER PROGRAMMING—the big opportunity career—new recognized correspondence course. No maths needed. Free brochure. **CANADIAN INSTITUTE OF SCIENCE AND TECHNOLOGY**, V63 Adelaide St. W., Toronto.

RADIO ANNOUNCING, learn by tape \$1.00. **JACK**, 207 King Drive, Jackson, Mississippi, 39208.



CHEMTRONICS
COLOR-LUBE
SPECIALLY FORMULATED
TUNER CLEANER FOR
COLOR TV TUNERS
Accept no substitutes

GOVERNMENT SURPLUS

JEEPS Typically From \$53.90 . . . Trucks From \$78.40 . . . Boats, Typewriters, Airplanes, Multimeters, Oscilloscopes, Transceivers, Electronics Equipment, Used. 100,000 Bid Bargains Direct From Government Nationwide. Complete Sales Directory and Surplus Catalog \$1.00 (Deductible First \$10.00 Order). **SURPLUS SERVICE**, Box 820-REL, Holland, Michigan 49423

give...
so more will live
HEART FUND



WRITE NOW FOR FREE 1969 CATALOG
McGEE RADIO COMPANY
1001 BARGAINS IN SPEAKERS—PARTS
TUBES—HIGH FIDELITY COMPONENTS
RECORD CHANGERS—TAPE RECORDERS—KITS
EVERYTHING IN ELECTRONICS.
1901 McGee St., Kansas City RE, Missouri 64108



ZIP CODE
... THE LAST WORD
JOHN JONES
300 WEST 33 ST.
NEW YORK, N.Y. 10001
MR. THOMAS GRAY
217 EAST 70 ST.
NEW YORK, N.Y. 10021
IN MAIL ADDRESSES!
YOUR POSTMASTER



HEAVY DUTY WELDER
Does work of \$85.00 welder yet costs only **1895** POST PAID
Fits ordinary 110V outlet 3 welding heats

Weld, braze, solder or cut most anything made of metal. No experience needed. Follow simple instructions. Uses standard 1/4" rods to weld iron, steel, brass, bronze, aluminum, other metals. 3 welding heats . . . not just one as with other low priced models. New **HEAVY DUTY** circuit gives higher heat . . . 4 times the heat needed to melt toughest iron. More welding power than ever before. Comes complete with welder's mask. \$2.00 pack of rods, flux, carbons, automatic arc striker, etc. **NOTHING ELSE TO BUY**. Approved for homes, garages, shops, factories. 10 day **MONEY BACK** trial. Guaranteed against burnouts. Send \$2.00 and pay \$16.95 plus small C.O.D. when delivered, or send \$18.95 cash, ck., M.O. for postpaid shipment. **WEL-DEX MFG. CO.**, Dept. W-3d, Box 10776, Houston, Texas 77018

CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services). 70¢ per word . . . minimum 10 words.
NON-COMMERCIAL RATE (for individuals who want to buy or sell personal items) 30¢ per word . . . no minimum.
Payment must accompany all ads except those placed by accredited advertising agencies. 10% discount on 12 consecutive insertions, if paid in advance. Misleading or objectionable ads not accepted. Copy for February issue must reach us before December 13.
WORD COUNT: Include name and address. Name of city (Des Moines) or state (New York) counts as one word each. Zone or Zip Code numbers not counted. (We reserve the right to omit Zip Code if space does not permit.) Count each abbreviation, initial, single figure or group of figures or letters as a word. Symbols or groups such as 8-10, COD, AC, etc., count as one word. Hyphenated words count as two words. Minor over-wordage will be edited to match advance payment.

Buy 10 **PAKS & CHOOSE 1 FREE**

NE-2 NEON BULBS **20 \$1** for **1**

★ Handles 2 Amp **2 AMP 6**
800 PIV for
 TOP HAT \$1 RECTIFIERS **1**

- \$25 SURPRISE PAK: transistors, rect. diodes, etc. . . \$1
- 6 ONE AMP 800 PIV RECTIFIERS, silicon top hat . . . \$1
- 2—CLAIREX PHOTO ELECTRIC CELL, . . . Hobby must \$1
- 50 GERMANIUM GLASS DIODES, 1N34, 1N48 no test \$1
- 40 TOP HAT SILICON RECTIFIERS, no test asst values \$1
- 25 EPOXY RECTIFIERS, silicon asst, no test . . . \$1
- 40 PRECISION RESISTORS, 1/2, 2W, 1% asst values . . \$1
- 30 TRANSISTORS, r.f. if. audio, osc, no test . . . \$1
- 60 TUBULAR CONDENSERS, to .5mf to 1KV, asst . . \$1
- 50 DISC CONDENSERS, to .05mf npo, temp coef, asst \$1
- 60 TUBE SOCKETS, receptacles, plugs, audio, etc. . . \$1
- 30 POWER RESISTORS, to 25 watts, to 24K ohms . . \$1
- 3 2N3568 NPN TRANSISTORS, 200me, 200V, 200hfe, \$1
- 3 2N3563 TRANSISTORS, npn, 600me, 100hfe, epoxy \$1
- 10 VOLUME CONTROLS, to 1 meg, switch too! . . . \$1
- 10 ELECTROLYTICS, to 100mf, tubulars too, asst . . \$1
- 50 RADIO & TV KNOBS, asst colors & styles . . . \$1
- 10 TRANSFORMER ELECTROLYTICS to 100mf, asst values \$1
- 50 COILS AND CHOKES, if, rf, ant, osc, peaking, etc \$1
- 65 HALF WATTERS, to 1 meg, 5% popular values too \$1
- 60 HI-QUALITY RESISTORS, 1/2, 1, 2W asst values . . \$1
- 10 RCA PHONO PLUGS & JACK SETS, tuners, etc. . . \$1
- 4 INTEGRATED CIRCUITS, gates, etc. no test . . . \$1
- 2-PC INFRA-RED DETECTOR & FILTER SET science prof \$1
- 2 FIELD EFFECT TRANSISTORS, n channel, hobby . . \$1
- 50 TERMINAL STRIPS, 1 to 8 lug types . . . \$1
- 3 PHOTO ELECTRIC CELLS, hi imp., schematic . . . \$1
- 3 TRANSFORMER AMPLIFIER, WIRED, 3x2x3/4" schematic \$1
- 10 PRINTED CIRCUIT BOARDS, copper clad, 100 uses \$1
- 10 TRANSISTOR SOCKETS, for npn & npn types . . . \$1
- 10 PANEL SWITCHES, toggle, slide, micro, rotary . . \$1
- 4 TRANSFORMER TRANSFORMERS, asst, worth \$25 . . . \$1
- 5 RAYTHEON CK-722 TRANSISTORS, npn, most pop \$1
- 5 G.E. 2N107 TRANSISTORS, npn, audio ekts . . . \$1
- 6 "IBM" COMPUTER BOARDS, many trans, diodes, \$1
- 40 "MICRO" CONDENSERS, for transistor circuitry \$1
- 3 1/4W. EPOXY TRANSISTORS, npn, silicon, B-5000, \$1
- 15 3 to 12 AMP STUD RECTIFIERS, up to 600 PIV . . \$1

Terms: add posttax. Rated: net 30, cod's 25%
Phone Orders: Wakefield, Mass. (617) 245-3829
Retail: 211 Albion, St., Wakefield, Mass.

GIANT 1969 CATALOG ON: Parts, Rectifiers,
 Transistors, SCRs, I.C.'s, Equipment, Etc. **10¢**

POLY PAKS P.O. BOX 942 R
Lynnfield, Mass. 01940

CLASSIFIED ADVERTISING ORDER FORM

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35

No. of Words { @ .30 Non-Commercial Rates } \$ _____
 { @ .70 Commercial Rate } \$ _____

Total Enclosed \$ _____

Insert _____ time(s)

Starting with _____ issue

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

SIGNATURE _____

MAIL TO: RADIO-ELECTRONICS, CLASSIFIED AD DEPT.,
200 PARK AVE. SOUTH, NEW YORK, N.Y. 10003

Payment must accompany order unless placed through accredited advertising agency 28

The Model 6000 Modular Frequency Meter will measure frequencies 10 KHz to 600 MHz with .000125% accuracy. Special plug-in modules allow the instrument to be used as an audio frequency meter from 500 Hz to 20 KHz full scale and in addition to be used as a dc voltmeter (10,000 ohms/volt).

The wide variety of plug-in oscillator accessories and range modules makes the Model 6000 adaptable to a number of jobs in the field and in the laboratory. Portable, battery operated with rechargeable batteries.
Model 6000 with 601A charger, less plug-in modules \$195.00

INTERNATIONAL MODEL 6000 FREQUENCY METER

measures frequencies 10 khz to 600 mhz with accuracy as close as .000125%

CHARGER



Range Modules (Mixers)
\$25.00 to \$45.00 each


Oscillator Modules
(Crystal Controlled For
Frequency Measurement)
\$30.00 to \$90.00 each

Special Modules
Audio Frequency\$45.00
DC Voltmeter..... 25.00



CRYSTAL MFG. CO., INC.
10 NO. LEE • OKLA. CITY, OKLA. 73102

where accuracy counts!

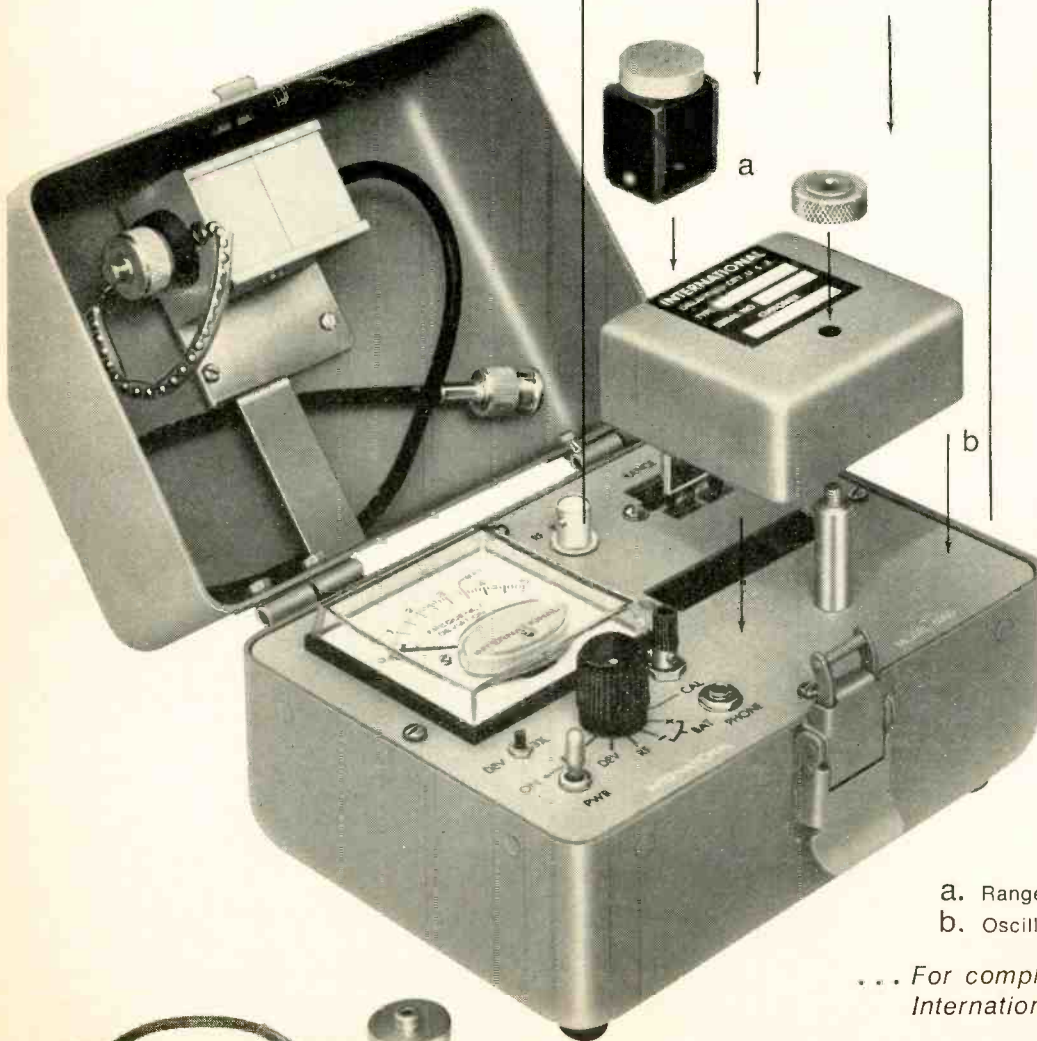


- a. Range Modules
- b. Oscillator Modules

... For complete information write
International today.

Circle 149 on reader's service card

the crowd pleaser...

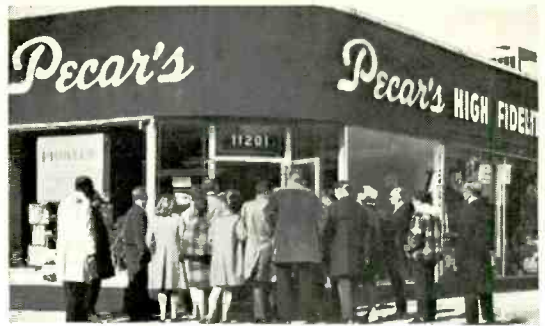

In hundreds of Pioneer franchised high fidelity dealers across the country, the SX-1500T is drawing enthusiastic attention because it is a no-compromise receiver. Its highly sensitive front end pulls in the most difficult stations . . . and is consequently pulling in the crowds. The SX-1500T was made for the thousands who wanted the finest receiver possible . . . at a reasonable price.*

The specifications and quality of the SX-1500T are substantiated by its performance and, more importantly, its sound. It boasts an output of 170 watts of music power, an extraordinary capture ratio of 1 dB, a signal-to-noise ratio of 65 dB, and harmonic distortion actually below 0.1% at half rated power (0.5% at full rated power). FM sensitivity is outstanding at 1.7 uv. Frequency response is 20 to 70,000 Hz \pm 1 dB.

If you want a better receiver, *don't be misled* — pick the one with the honest price. You owe it to yourself to compare the SX-1500T with any other receiver on the market regardless of price.

See and hear the SX-1500T now. Or write for literature and name of nearest dealer.
PIONEER ELECTRONICS U.S.A. CORP., 140 Smith Street, Farmingdale, L. I., New York 11735

PIONEER'S NEW SX-1500T AM-FM STEREO RECEIVER 170 WATTS, FET FRONT END, AND 4 IC's



* (The SX-1500T Price, only: \$360.) Shown with PIONEER CS-83 Speaker Systems at \$175. each.

PIONEER ... More Value All-Ways!



Circle 150 on reader's service card


RCA HI-LITE respects and protects ...a well-earned service reputation

A good service reputation takes time to come by. It's put together call by call, customer by customer, day after day. So why shouldn't you expect the color picture tubes you rely on every day in your business to have earned a good reputation for themselves, too.

That's what you get when you specify RCA HI-LITE. It's the replacement picture tube with OEM specs . . . the same quality . . . the same tube that goes into original equipment sets. With all-new glass, gun, the works! And such technical advancements as PERMA-CHROME and Unity Current Ratios. Plus the broadest line of types in the industry.

Insist on HI-LITE, the picture tube that respects and protects your service reputation.

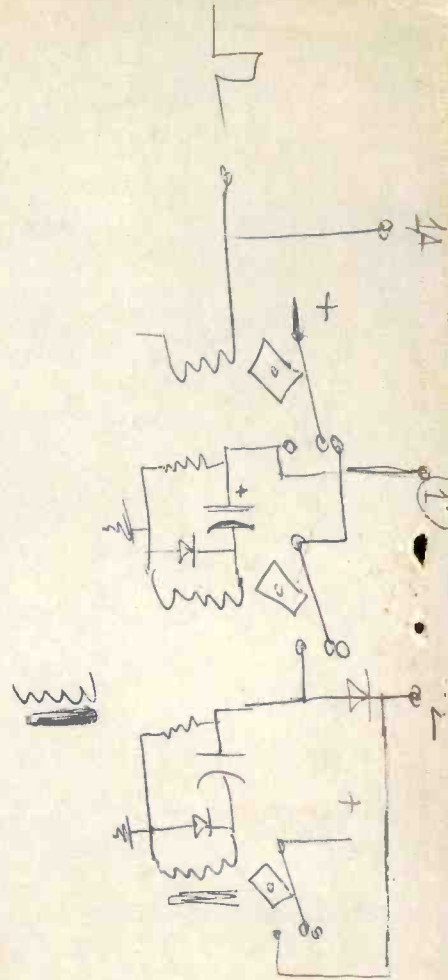RCA Electronic Components, Harrison, N. J.



RCA