

Radio-Electronics

60¢ ■ MAY 1973

FOR MEN WITH IDEAS IN ELECTRONICS

BUILD A MODULAR ELECTRONIC MUSIC SYNTHESIZER

4-CHANNEL STEREO SQ, QS, CD4
See How Systems Compare

HEATH'S DIGITAL FM TUNER
How Its 44 Computer IC's Work

SECURITY SYSTEMS
Which One Is Best

PUBLIC ADDRESS
Setting Up A System

A
EERNSBACK
PUBLICATION




PLUS

Appliance Clinic
Speed Troubleshooting
Jack Darr's Service Clinic
Lou Garner's State-Of Solid-State
Transistor Interchangeability Directory

566164 000 71TEEL96 JUL73 0 A
05
4
THE ELECTRONIC SHOP
7 1-2 4 CHURCH ST
FAIRPORT NY 14450

NEW! EICO 'DO-IT-YOURSELF' HOME SECURITY PROTECTION SYSTEM

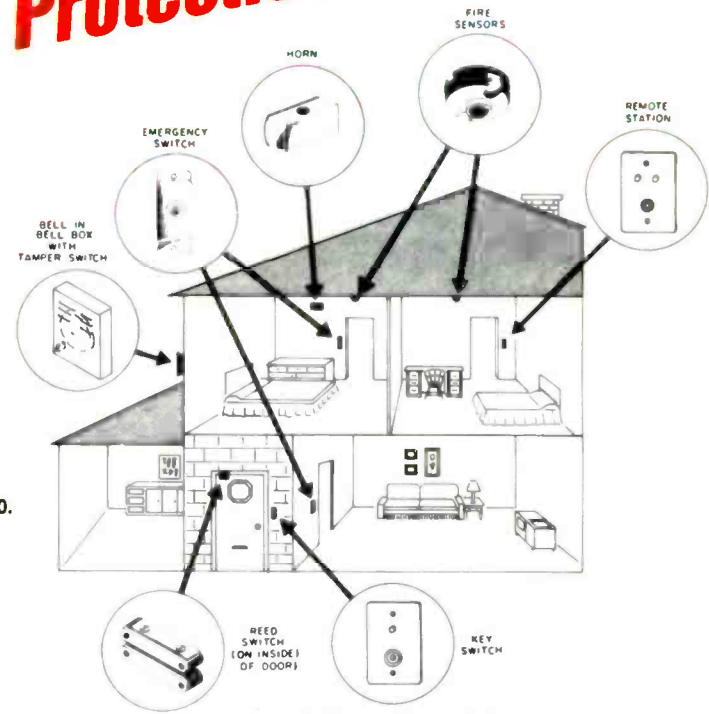The Professional Home Protection everyone can install and afford.



TYPICAL ALARM INSTALLATION

EICO FC-100 SECURITY CONTROL CENTER

- Start your custom Burglar/Hold-up/Fire Alarm System with the FC-100.
- Add on Sensors, Alarms and Accessories to suit your own needs.
- "Do-it-Yourself" Installers Handbook included.
- AC Operated-Automatic Transfer to Battery Operation in the event of Power failure
- No technical knowledge needed-No soldering.
- Ideal for Apartment, Home and certain Commercial Installations.
- 100% Professional in Design, Reliability, Performance.

The first professional Alarm Control Center designed for easy "Do-it-Yourself" installation. The FC-100 is the "heart" of the EICO home protection system.

It contains all circuits required for monitoring the burglar and fire detectors and sounding the alarm. It includes two indicator lights; a white "circuit test" light which automatically checks the status of the burglar alarm sensors in the system, and a red "alarm on" light, which indicates that the system has been activated. A built-in 117 VAC power supply supplies 6 volts DC for operating the system. In the event of power failure, the FC-100 automatically switches over to battery operation. The power supply also trickle charges the lantern battery when it is not in use. A meter and battery test switch allows you to check the condition of the battery. Each circuit in the FC-100 has its own set of screw terminals that allow easy installation.



Includes A-95 Security Handbook and A-105 warning decals.
Model FC-100 \$69.95

EICO SS-500 BURGLAR/HOLD-UP/FIRE ALARM SYSTEM

- Systems "HEART" is the EICO FC-100 Security Control Center.
- Additional Sensors, Alarms, Accessories may be added any time to meet future needs.
- "Do-it-Yourself" Installers Handbook included.

The EICO SS-500 Security System offers you the kind of professional protection you have been looking for, at a price you can afford. The System has been designed on the EICO exclusive "Expandability Concept" that enables you to "add-on" protection to meet your own special requirements. Virtually any professional security sensing device can be easily added to the EICO SS-500.

The system is supplied with the following: FC-100 Security Control Center; SA-25 8" Alarm Bell; A-45 Entrance Key-Switch with "system-on" signal light; A-65 remote station control with signal lights; SD-20 Fire Sensors; SD-10 Door/Window Contact Switches; SD-50 Tamper Switches; SD-40 Door Cords; A-35 Emergency Buttons; A-95 Installers Handbook; A-105 6 Warning Decals; A-135 (2) Alarm Circuit Hook-Up Wire and A-137 Alarm Bell Hook-Up Wire.

Model SS-500 \$129.95

"Do-it Yourself" HOME SECURITY HANDBOOK



A comprehensive 40-page Homeowners Handbook which includes a wealth of information on professional home security as well as comprehensive installation procedures in clear non-technical language.

A-95 Handbook \$2.95

EICO A-95 HOME SECURITY HANDBOOK

Save hundreds of dollars in alarm installation and monthly service charges. The EICO A-95 Home Security Handbook is a comprehensive 40 page booklet which can be easily understood by anyone. Written in clear non-technical language, it contains complete instructions not only on how a home protection system functions and how to install all EICO security devices, but also how to expand your EICO system. Before you purchase any security system for your home, we suggest you read the A-95 handbook and see how easy EICO makes it to "Do-it-Yourself."

Acclaimed by Editors and Consumers!

"The EICO SS-500 Home Protection system works as well as. If not better, than many so-called "professional" or industrial systems—at a lot less cost. Fact is, the system has more features than much "professional" equipment. And it certainly works a lot better than many do-it-yourself systems presently on the market that are supposedly intended for the average home owner."
(Test Report Summary E/E Magazine Aug. 1972)

"Wiring the Eico system is a breeze"
(Electronics Illustrated August 1972)

"We found that installing the security system is easy, and the only tools we needed were a screwdriver and a knife. We picked an arrangement from the manual, suitable to our needs, and went to work. In a matter of hours, the job was completed."
(Popular Electronics Sept. 1972)

Additional security components can be added any time, at your own pace, to suit your own needs.

EICO Electronic Instrument Co., Inc., 283 Malta Street, Brooklyn, N.Y. 11207

Circle 1 on reader service card



We taught Leonard Starr how to make money doing what he used to do for fun.

Leonard Starr's father wanted him to go to college and settle down in a "nice clean job in a brokerage office."

But Lennie had ideas of his own.

"I'd seen too many other guys serving time in jobs they couldn't stand — just as bored with their work as my father is with his. And getting soft.

"Not me. I knew what turned me on and it wasn't the brokerage business. I like action — hot cars, motorcycles, working with tools. Why, I started tearing down bicycles and rebuilding them when I was only a kid.

"So I asked myself — 'Why not do that for a living?'"

Well, why not? Lennie Starr got in touch with the school that really understands individuals — the school that makes a special point of helping people who have their own ideas about that one life they've got to live.

Today's ICS.

Now, Lennie Starr is doing just what he wants to do — as a Master Automotive Technician in the best dealership in town. He's pulling down a bigger dollar than any of his desk-bound friends — and he's having fun doing it. Which is more than a lot of people can say.

Leonard Starr is a hypothetical person — a composite of the many thousands of real individuals who are using today's ICS to change the course of their lives. But how about you?

Chances are, you're an individualist, too. Your interests are different from Lennie's, different from anybody's. And because of that, today's ICS can help you, too.

Tell us what turns you on — and we'll teach you to do it for a living!

Is electronics your bag? TV servicing? Air Conditioning? Want to earn \$7-8 an hour or more as a skilled electrician? How about a first-class FCC license? Or are you shooting for a big professional career as a full-fledged civil, mechanical or electrical engineer? You name it — and today's ICS will teach it to you.

Today's ICS is for action-minded people — people who like to learn by doing. ICS technical career programs include valuable professional tools and equipment that you learn to use in practical experiments and do-it-yourself projects — then keep for your new career . . .



a 25" (diagonally measured) Motorola Quasar II® color television chassis with the ICS TV Technician program — plus an oscilloscope, VOM, and experimental lab equipment . . .

a Philco/Ford room air conditioner with the ICS Air Conditioning and Refrigeration program — plus a whole battery of professional tools, instruments and testing equipment . . .

an electronic multimeter and top-quality electrician's tool kit (in leather case that attaches to your belt) with the ICS Electrician's program — plus a home laboratory for experiments . . .

a complete set of Proto hand tools (official tools of the Indy 500) and genuine Daytona test equipment with the Automotive Technician's program . . .

And so on. If you're an individual . . . if you have your own ideas about the kind of life you want to live . . . if you want to earn big money doing the things you do now just for fun . . . today's ICS can help.

School was never like this!

In fact, studying with ICS is like nothing you've ever done before. It's almost like taking up a fascinating new hobby — yet you wind up with a solid career skill you would probably never get otherwise.


Because you don't have to give up your job or take time away from home to do it.

Circle 2 on reader service card

You learn at home — in your spare time, at your own sweet pace. Yet your instruction is entirely personal. An instructor answers every question you ask. You can actually pick up the telephone and ask your questions out loud — toll free!

That's individualism for you. And speaking of individualism, it's pretty comforting to know that more than eight and a half million other individuals have enrolled in ICS before you.

Which is not bad for a school that specializes in helping individuals learn to do well the things they like to do best.



2,000 U.S. firms and government agencies — including Chrysler, Ford, U.S. Steel, Mobil, Motorola, Pan Am and Dupont — are using ICS training programs to upgrade their own employees.

©1973 ICS

ICS International Correspondence Schools
Scranton, Pennsylvania 18515

Tell me more about how I can make big money doing what I like to do.

Please send me free Career Guidance Booklet and a free "Demonstration Lesson" for the field I have checked below. I understand I am under no obligation.

- Air Conditioning/Refrigeration & Heating
- Automotive Mechanics
- Engineering (Civil/Electrical/Mechanical/Chemical)
- Electrician
- FCC Licensing (Electronics)
- Auto Body Rebuilding
- Communications/Broadcasting Technician
- Computer Servicing
- CATV Technician
- Diesel/Gas Mechanic
- Architecture
- Drafting
- Electronics Technician
- Engineering Technician
- TV Servicing & Repair
- Surveying & Mapping
- High School Diploma
- Check here for special information. if age 16 or under. XA625Y

Name _____ Age _____


Address _____ Apt _____

City _____

State _____ Zip _____

Approved for Veterans' Training and Accredited Member National Home Study Council

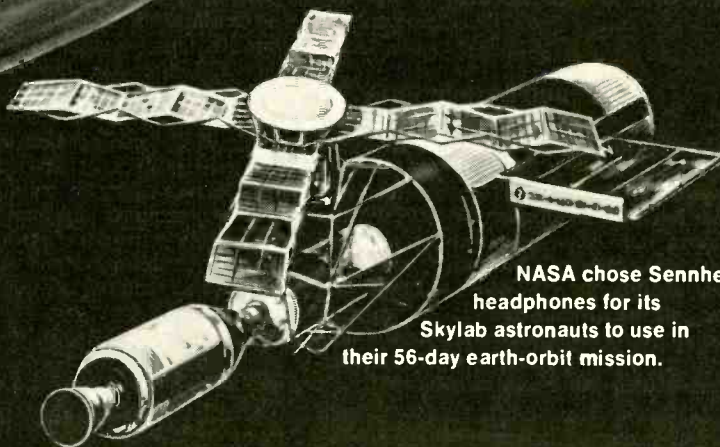When we say our headphones are out of this world ...we mean it.



NASA chose Sennheiser headphones for its Skylab astronauts to use in their 56-day earth-orbit mission.

But people prefer them for down to earth reasons.

**NASA selected us ...
but you don't have to go into
orbit for comfort**

Out in space or here on earth, the last thing you want is to be uncomfortable. Whether you're relaxing with your favorite music or communicating with a ground tracking station.

Which is one good reason so many people do their listening with our HD 414 "open-aire" headphones. Even if they weren't the lightest (which they are), they're not bulky, and don't need uncomfortable air-tight seals to get good sound.

**\$150.00 sound
under \$50.00? Ask
ELECTRONICS
WORLD!**

According to the October, 1971 issue, our HD 414 has "the best sound of any



dynamic phones" — based on factors like frequency response, transient response, sensitivity and *listening tests*. In the article's headphone comparison chart, the only really comparable headphone maker's sets were priced at \$95.00 and \$150.00 apiece! (As if that weren't enough, we were also rated most comfortable.)

Isolation or Communication?

The choice is yours. With "open-aire" headphones, you hear as much as you want of your surroundings. Or as little: a twist of the volume control and you're effectively alone!

**A "superior...natural"
headphone? Sounds
like HIGH FIDELITY
feels that way!**

They pointed out our headphones combine "the

superior close-up quality characteristic of headphone sound" with "the freedom and naturalness of loudspeaker listening." What's more, they felt that the HD 414 is cooler to use, "allowing body heat to dissipate more readily."

Hearing is believing

In this world and out, it seems more and more people rate Sennheiser "open-aire" headphones tops. But all the testimonials in the world can't tell you what your ears will. Why not visit your nearby Sennheiser dealer and put your ears in orbit. At a very down-to-earth price.



SENNHEISER
ELECTRONIC CORPORATION

10 West 37th Street, New York 10018 (212) 239-0190
Manufacturing Plant: Bissendorf, Hannover, West Germany

Circle 3 on reader service card

www.americanradiohistory.com

Radio-Electronics

FOR MEN WITH IDEAS IN ELECTRONICS

MAY 1973

SPECIAL FEATURE

- 35 **Understanding Security Systems**
There are many kinds of systems, and each one has specific advantages and disadvantages. Find out which one is best for you. *by George F. Duryea*

4-CHANNEL STEREO HI-FI AUDIO

- 42 **Inside Heath's Digital FM Tuner**
There are 55 IC's and more than 100 transistors and diodes to make it go. Much of the electronics is closely akin to that of the computer. *by David M. Thomas*
- 51 **Installing PA Speakers**
How to hook them up isn't as easy as it sounds. There's impedance matching, placement, and types to use that must be considered. *by Bogen Sound Systems*
- 54 **Unscrambling 4-Channel Sound**
An in-depth technical report including 32 scope waveforms showing how compatible the various 4-channel systems really are. *by Herb Friedman*

BUILD THIS ONE

- 38 **Electronic Music Synthesizer**
Electronic circuit modules go together to make this electronic musical instrument. *by John Simonton, Jr.*

TELEVISION

- 60 **Speed Troubleshooting Logically**
Part II: Cut it in half procedure—how it works, how to use it. *by Jon Turino*
- 71 **Service Clinic**
The trouble tree. *by Jack Darr*
- 72 **Reader Questions**
R-E's Service Editor solves reader problems.
- 80 **New Pay TV System**

GENERAL ELECTRONICS

- 4 **Looking Ahead**
Tomorrow's news today. *by David Lachenbruch*
- 26 **Equipment Report**
B & K model 281 digital multimeter

SOLID-STATE ELECTRONICS

- 62 **State Of Solid State**
Optoelectronics is the featured subject this month. *by Louis E. Garner*
- 68 **R-E's Guide For Substitution Transistors**
220 more types are listed. *compiled by Robert & Elizabeth Scott*

DEPARTMENTS

- | | |
|-------------------|-------------------------|
| 102 Books | 91 Next Month |
| 16 Letters | 111 Reader Service Card |
| 6 New & Timely | 100 Technotes |
| 90 New Literature | 101 Try This |
| 84 New Products | |



WAVEFORMS LIKE THIS ONE are the secret to unscrambling 4-channel sound. There are more than 30 different ones in this article.

... see page 54



ELECTRONIC MUSIC MACHINES can be built at home. See how you can assemble your own synthesizer. ... see page 38

Hugo Gernsback (1884-1967)
founder

M. Harvey Gernsback, editor-in-chief
and publisher

Larry Steckler, CET, editor
Robert F. Scott, W2PWG CET, technical editor

Jack Darr, CET, service editor

Louis E. Garner, Jr., semiconductor editor

I. Queen, editorial associate

Matthew Mandl, contributing editor

David Lachenbruch, contributing editor

James A. Gupton, Jr., photographic electronics

Vincent P. Cienia, production manager

Nancy Gilson, production assistant

H. Malysko, circulation

Cover photograph by Walter Herstatt

Cover design by Marius Trinque

Radio-Electronics is indexed in *Applied Science & Technology Index* and *Readers Guide to Periodical Literature*.



Radio-Electronics, May 1973, Vol. 44, No. 5. Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York City 10003. Second-class postage paid at New York, N. Y. and additional mailing offices. One-year subscription rate: U.S.A., U.S. possessions and Canada, \$7. Pan-American countries, \$8. Other countries, \$8.50. Single copies 60¢. © 1973 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

Subscription Service: Mail all subscription orders, changes, correspondence and Postmaster Notices of undelivered copies (Form 3579) to Radio-Electronics Subscription Service, Boulder, Colo. 80302.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired upon rejection. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

As a service to readers, Radio-Electronics publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, Radio-Electronics disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

looking ahead

Big numbers

Americans went on an electronics buying spree last year, according to official figures released at presstime. They bought a record 17.1 million television sets—color and monochrome—equivalent to one new set for about every fourth household in the United States. Of these, slightly more than half were color sets. They also set a record in radio purchases (more than 55 million of 'em), stereo and other phonograph system (over 7.2 million) and tape recorders and/or players (a whopping 20.7 million). That's 100 million home electronic products—not counting such odds and ends as electronic guitars, organs, hearing aids, instructional kits, individual stereo components and microwave ovens.

Videodisc compatibility

A small ray of sunshine is peeking through the clouds on the stormy videodisc compatibility scene. The European electronics giant, N. V. Philips, and California-based MCA Disco-Vision—both of which have demonstrated LP videodisc systems which use a laser readout principle—have announced they've begun discussions toward achieving compatibility.

Two other videodisc systems seem to have little chance of being brought into conformity with any Philips-MCA standards, however. The German-British Teldec system (Telefunken and Decca) uses a mechanical pressure pickup and is already scheduled for production later this year. RCA's system, long under development, but never shown publicly (at least up to the deadline for this column), works on a capacitance principle: A metallized disc is

coated with a thin layer of dielectric material and the metallic pickup stylus serves as the other side of the capacitor.

Bathometer

Rub-a-dub-dub, electronics in your tub. The latest gadget in Japan, where the bath is an important ritual, is a multi-purpose intercom and alarm. It sounds a warning if intruders break into the house, if a fire should start—or if the level or temperature of the bath water gets too high. At around \$100, it's a good way to stay out of hot water.

Videocassette recall?

Manufacturer recalls of products are becoming increasingly prevalent, particularly in the automotive field. Now there seems to be a distinct possibility of a federally mandated recall or field modification of all videotape recorders, closed-circuit cameras and other products designed to feed into the antenna terminals of standard home television receivers.

The FCC took jurisdiction over these devices to prevent excess radiation from feeding back through antennas and interfering with reception on other TV sets. During its consideration of the new radiation rules, it permitted manufacturers to make and sell devices if they agreed to abide by certain preliminary specifications and to make modifications later, if necessary, to conform with the final rules. When the final rules were issued, they contained an unexpected provision—all devices must be equipped with antenna-disconnect switches which provide 60 dB of isolation. In other words, when the recorder, player or

camera is feeding into the TV set, the antenna must be disconnected.

Manufacturers are now hurriedly developing switches designed to meet the Commission's specified 60-dB isolation for products they market in the future. They're also expected to ask to be relieved of the requirement to modify those already in use, on the ground that their signal strength is one-third of that now permitted for new devices, resulting in less interference even if a switch with under 60-dB isolation is used. If there's a recall, it would involve perhaps 35,000 videocassette machines now in use in industry, government and education. An uncounted number of older devices sold before the FCC announced its jurisdiction probably won't be affected.

New pay-TV system

With per-program or per-channel pay-TV cable operations starting up in various parts of the country, equipment manufacturers are working overtime to develop methods for distributing programs only to those who will pay for them. The latest pay-cable system was developed by Magnavox with the backing and assistance of big CATV operator TelePrompTer Corp. Designed to operate with current CATV's, it provides a method of billing customers only for the programs they watch (special programming, such as recent movies and sports not carried on regular TV).


The "Premium TV" system involves the use of a special box in the subscriber's home, enabling him to view either of two pay-TV channels or regular TV at the touch of a button. Mounted on a telephone pole is an "interactive data exchange module" (IDEM),

servicing 32 subscribers in the neighborhood. When a viewer presses a pay-TV program button, the signal is unscrambled and fed into his set on a special channel. The IDEM keeps track of his viewing, and each month a CATV employe travels through town with a low-cost battery-operated audio tape recorder, which he plugs into a special terminal connected to each IDEM. The cassette is then fed into a central billing computer (either directly or by telephone). The computer prints out a monthly bill, enumerating programs watched and the cost for each individual subscriber. The system will be tested this year in an undisclosed California city. For more details see a complete description of the system on page 80.

Comsat's first decade

Communications Satellite Corp. (Comsat), the U.S. participant in the worldwide space communications consortium Intelsat, celebrated its 10th birthday recently by releasing these statistics: Some 83 Intelsat member countries now have satellite service, with 80 ground stations in 49 countries (the others receive their communications via ground lines from the nearest station). One quarter of the earth's population is now within the range of live satellite TV broadcasts. Use of satellites for telephone service has reduced the cost of a New York-to-London phone call from \$12 to \$5.40 for three minutes. Since the start of satellite TV, the cost of a 30-minute color transmission from New York to Paris has steadily dropped from \$16,000 (for the Early Bird satellite) to \$3,870 today.

by DAVID LACHENBRUCH
CONTRIBUTING EDITOR

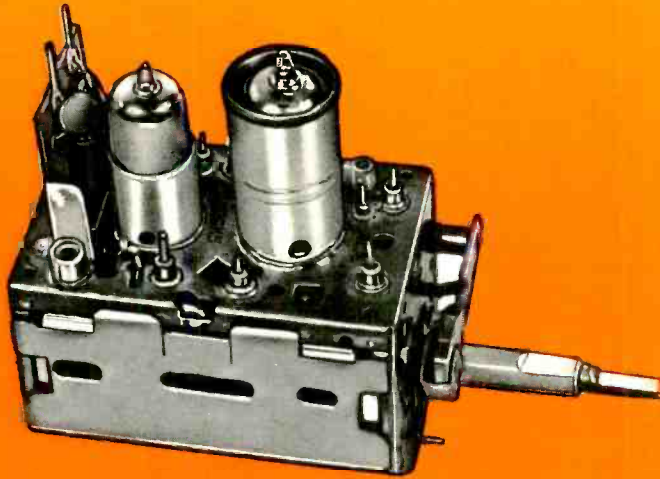

\$9.75

ALL PARTS INCLUDED

except tubes and transistors

ONE YEAR GUARANTEE

TUNER SERVICE CORPORATION

PROVIDES YOU WITH A COMPLETE SERVICE FOR ALL YOUR TELEVISION TUNER REQUIREMENTS.

REPAIR

VHF Or UHF Any Type \$9.75.
UHF/VHF Combo \$15.00.

In this price all parts are included. Tubes, transistors, diodes, and nuvistors are charged extra.

Fast efficient service at our conveniently located service centers. This price does not cover mutilated tuners.

All tuners are cleaned ultrasonically, repaired, realigned and air tested.



WATCH US GROW

REPLACE

Universal Replacement Tuner \$9.75.

This price buys you a complete new tuner built specifically by SARKES TARZIAN INC. for this purpose.

All shafts have a maximum length of 10" which can be cut to 1½".

Specify heater type parallel and series 450mA or 600mA.

CUSTOMIZE

Customized tuners are available at a cost of only \$15.95. (With trade-in \$12.95)

Send in your original tuner for comparison purposes to:

TUNER SERVICE CORPORATION FACTORY-SUPERVISED TUNER SERVICE

Backed by the largest tuner manufacturer in the U.S.—SARKES TARZIAN, Inc.

HEADQUARTERS	537 SOUTH WALNUT ST., Bloomington, Indiana 47401	TEL: 812-332-7251
ARIZONA	2629 NORTH FIRST AVE., Tucson, Arizona 85717	TEL: 602-791-9243
CALIFORNIA	SARKES TARZIAN, Inc. TUNER SERVICE DIVISION	
	10654 MAGNOLIA BLVD., North Hollywood, Calif. 91601	TEL: 213-759-2720
FLORIDA	1505 CYPRESS ST., Tampa, Florida 33606	TEL: 813-253-0324
GEORGIA	938 GORDON ST., S. W., Atlanta, Georgia 30310	TEL: 404-758-2232
INDIANA	817 N. PENNSYLVANIA ST., Indianapolis, Ind. 46204	TEL: 317-632-3493
	6833 GRAND AVE., Hammond, Indiana 46323	TEL: 219-845-2676
KENTUCKY	2920 TAYLOR BLVD., Louisville, Kentucky 40208	TEL: 502-634-3334
NEW JERSEY	547-49 TONNELE AVE., Jersey City, New Jersey 07307	TEL: 201-792-3730
	(On U. S. Highway 1 & 9)	
TENNESSEE	1215 SNAPPS FERRY RD., Greenville, Tennessee 37743	TEL: 615-639-8451
	1703 LAMAR AVE., Memphis, Tennessee 38114	TEL: 901-278-4484
TEXAS	11540 GARLAND RD., Dallas, Texas 75228	TEL: 214-327-8413
VIRGINIA	4538 PRINCESS ANN ROAD, Norfolk, Virginia 23502	TEL: 703-855-2518

Circle 4 on reader service card

new & timely

"Two-eyed" tube may improve TV color camera performance

A new two-target camera tube is expected not only to enhance the performance but to lower the cost of single-tube TV cameras. Called a BIVICON, the new 1½-inch RCA C23244 was designed originally for the RCA HoloTape system. "It is particularly well suited for generating color pictures from two-frame holographic or photographic films in which the luminance (black and white) portion of the picture is projected onto one target and the chroma (color) information, in suitable encoded form, onto the second target," according to Dr. William M. Webster, Vice President, RCA Laboratories.

The "suitable encoded form" refers to the chroma information on the HoloTape, in the color frames of which the chroma is encoded rather than appearing in actual color.

The Bivicon tube registers between the luminance and chroma information excellently without additional auxiliary coils because the beams generated by its two electron guns are controlled by a single magnetic focus and deflection system. These beams "read" out the



BIVICON CAMERA TUBE has two distinct pick-up surfaces—the dark rectangular areas.

stored picture information from the two targets and provide simultaneous output signals that can be superimposed with precision.

The tube can also be used to replace single-target vidicons in one tube color cameras that separate the luminance and chroma signals by optical filtering. It has an advantage over the vidicon in such an application because its second target can process the color signals independently. In such a camera, color filters ahead of the color target would be used to produce a point-sequential signal that could be decoded and combined with the black-and-white signal in the camera coding and control circuits, to produce an NTSC output.

The tube can also be used in other TV applications in cameras designed to produce simultaneous optical images that can be played back on separate monitors or superimposed on a single monitor. The double-beam, double-target feature provides a desirable degree of redundancy for use in unattended cameras. A TV surveillance camera with two fixed lenses might be electronically switched from one "eye" to the other to provide close-up and wide angle shots of an area under surveillance, Dr. Webster said.


A typical raster format for the Bivicon tube is 0.50 inch by 0.38 inch with center-to-center spacing of 0.41 inch. The two rasters are scanned in parallel so that two simultaneous output signals are generated. The output signals are provided for two small metal contact buttons on the tube's faceplate while mesh contact is made through a stud in the glass bulb. All other electrical connections are brought out through the tube base.

Ion implantation improves charge-coupled devices

Charge-coupled devices consist of a series of closely spaced mos capacitors in which charges are caused to step along from capacitor to capacitor by reversing the charges along the series of plates (*Radio-Electronics*, June 1971, page 6). But part of each charge finds it difficult to pass the gap between the plates—it finds a "potential threshold" hard to step over.

Siemens has introduced an implantation step in which boron ions are implanted in the gaps between the units, thus reducing the potential threshold. In

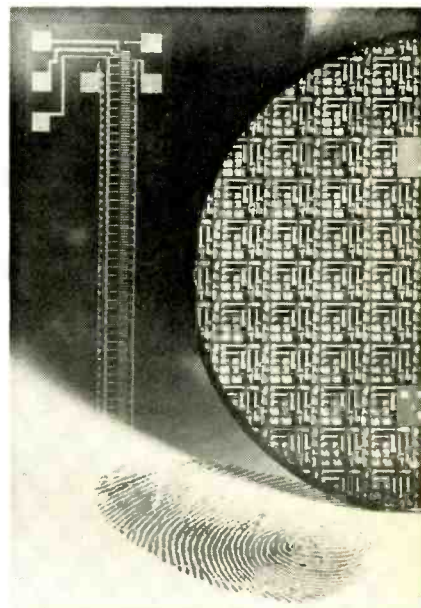older devices, gaps had to be kept to a width of 3 microns or less. With the new technique, gaps may be as wide as 7 mi-



CHARGE-COUPLED DEVICES are especially adapted to use in shift registers, but transfer losses can falsify data. Ion implantation has so reduced the losses in the Siemens IC shift register above that accuracy approaches 100%.

croons. Units with this greater gap width can be quantity-produced, thus making a wide range of applications economically possible.

Experiments with 150-electrode devices show a transfer loss of less than 0.2%, with 7-micron gaps, whereas with older devices the losses were almost 100%.

Third Annual Hugo Gernsback Scholarship Award

M. Harvey Gernsback, publisher of *Radio-Electronics*, has announced the third annual Hugo Gernsback scholarship award for 1973. The program consists of a \$125 grant to a deserving student of each of 9 technical home study schools serving in the electronics field.

The scholarships sponsored by *Radio-Electronics* were established in memory of the late Hugo Gernsback, electronic pioneer, inventor and publisher to perpetuate Mr. Gernsback's interest in developing the technological skills of young people.

(continued on page 12)

SOUTHWEST TECHNICAL PRODUCTS CORPORATION

219 W. RHAPSODY

SAN ANTONIO, TEXAS 78216

PHONE: 512 DI 4-3140

April, 1973

Dear Radio-Electronics Reader,

This will be the first of a series of "random ramblings" on "things and stuff" from the "Other" kit company. I realize that all of you are not familiar with Southwest Technical Products, or the kits we make. I hope to correct that situation in the coming months.

I started this company over 10 years ago as a source for printed circuit boards used in some of my Radio-Electronics projects. At that time circuit boards were still kind of unusual and materials to make them were not widely available. Evidently you and others who build magazine projects liked the idea, because I sold a bunch of circuit boards. Many of you requested other components for the projects too, so in Jan. of 1964 I got real brave and quit my job to go into the electronic kit business full time. Fortunately none of the first kits offered were disasters (some later ones were) and my small company began a steady growth.

Our aim then, as it still is now, was to offer kits for projects that were either a bit unusual, or kits for projects that could offer you a big saving over similar products. We have always used the best quality parts possible (short of going MIL Spec) even if they cost a bit more. All of our circuit boards are fiberglass, the resistors are deposited carbon, the transistors are new and as much as possible standard types that you can buy from local sources too in case you need one in a hurry sometime. We don't try to make our kits so easy that anyone can construct one. We assume that you know how to read a schematic, solder and strip wire. If you don't, if you simply want a nice pastime that is different from number painting, go buy a kit from Heathkit, or EICO. Most of our kits have pictorials and the instructions provided are enough for anyone fairly familiar with electronic construction. By holding down the cost of instruction manuals we are able to offer those of you who are "serious" about electronics a far better deal for your money.

I, and the other engineers who work at Southwest Technical Products, enjoy electronics. Our products are generally the result of an interest that someone had in a particular circuit, or project. We have never in our existence designed something to meet a particular price, for a market that surveys indicated was out there. Maybe we would make more money if we did, but it sure would take all the fun out of it.

If you would like to see what kind of gadgets that we make, write, phone, telegraph, or circle our number on the "Bingo" card in back. I will have our catalog in the first possible return mail to you. There is no charge. We are more than happy to get one in the hands of those "serious" electronics enthusiasts among you out there. Next month I will pick one kit to talk about. I think you might be interested in some of the circuit details and neat little features that we have put into our projects. See you then. In the meantime—send for our catalog right now.

Sincerely,



Daniel Meyer



SOUTHWEST TECHNICAL PRODUCTS CORPORATION

DEPT. RE-L

219 W. Rhapsody, San Antonio, Texas 78218

NOW train at home with NRI to be a Computer or Digital Technician—no other program is so complete in digital logic, computer operation and programming.

ANOTHER




FIRST

Your own digital computer included at no extra cost


This may very well be the most unique educational aid ever developed for home training—a *real* digital computer you build yourself and use to learn organization, operation, trouble shooting and programming. This remarkable training aid performs the same functions as bigger commercial computers. One of ten training kits you receive in the new NRI Complete Computer Electronics course.



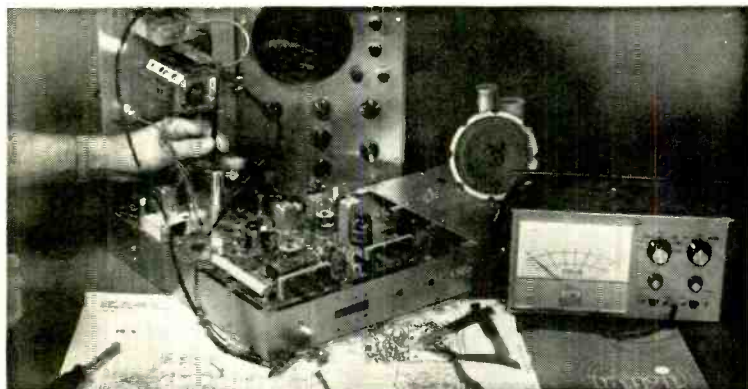NRI FIRSTS make learning Electronics fast and fascinating—give you priceless confidence



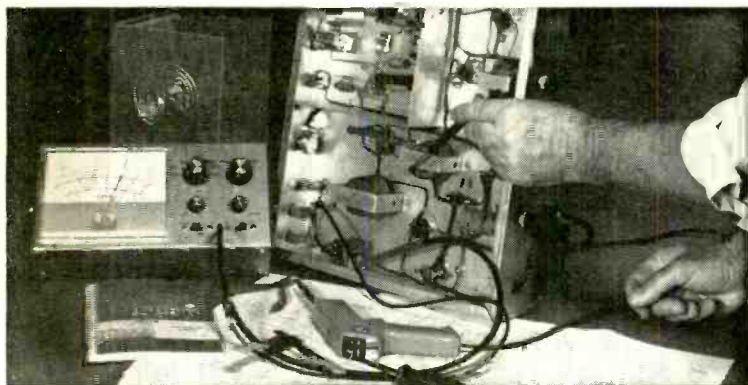FIRST to give you Color TV training equipment engineered specifically for education—built to fit NRI instructional material, not a do-it-yourself hobby kit. The end product is a superb Color TV receiver that will give you and your family years of pleasure. You “open up and explore” the functions of each color circuit as you build.



FIRST to give you true-to-life experiences as a Communications Technician. Every fascinating step you take in NRI Communications training, including circuit analysis of your own 25-watt, phone/cw transmitter, is engineered to help you prove theory and later apply it on the job. Studio equipment operation and trouble shooting become a matter of easily remembered logic.



FIRST to give you completely specialized training kits engineered for business, industrial and military Electronics Technology. Shown is your own training center in solid-state motor control and analog computer servo-mechanisms. Teletyping circuits, solid-state multivibrators and the latest types of integrated circuits are included in your course.

There is so much to tell you about this latest “first” in home training from NRI, you must fill in and mail the postage-free card today to get the full story of the Complete Computer Electronics course and the amazing digital computer you build and use as you learn.

Planned from the start to include specially designed training equipment in the pioneering NRI tradition, this exceptional new course succeeds in combining kits with NRI “bite-sized” texts to give you an easy-to-understand educational package. But, unlike other home training, this is not a general electronics course. Lessons have been specifically written to stress computer repair. You perform a hundred experiments, you build hundreds of circuits. Included are over 50 modern, dual-in-line TTL integrated circuits you use in the construction of your computer. You use professional test equipment. In addition to your digital computer, you build and use your own solid-state voltohmmeter and oscilloscope. Because you work with your hands as well as your head, your training is as much *fun* as it is education.

Train with the leader—NRI

As it has in other fields of home-study Electronics training, NRI has taken the leadership in computer training because the “Computer Age” continues to leap ahead. Qualified men are urgently needed, not only as digital technicians and field service representatives, but also for work on data acquisition systems in such fascinating fields as telemetry, meteorology and pollution control. Office equipment and test instruments also demand the skills of the digital technician. Like other NRI courses, this exciting new program can give you the priceless confidence you seek to walk into a technician’s job and know just what to do and how to do it. Mail the postage-free card for the FREE NRI Catalog. No obligation. No salesman will call. NATIONAL RADIO INSTITUTE, Washington, D.C. 20016.

GET FACTS ABOUT GI BILL

If you have served since January 31, 1955, or are in service now, check GI line on postage-free card or in coupon.

If postcard has been used, mail this coupon



NATIONAL RADIO INSTITUTE

Washington, D.C. 20016 3-053

Please send me your FREE NRI CATALOG with details about new Complete Computer Electronics training.

Name _____ Age _____

Address _____

City _____ State _____ Zip _____

Check here for facts on GI Bill

ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL

Hugo Gernsback founded **Radio-Electronics** magazine in 1929 for electronics service technicians, engineers and advanced electronics hobbyists. 1973 scholarship award winners will be announced in the magazine during the course of the year.

The 9 schools participating in the program are: Bell & Howell Schools, Career Academy, Cleveland Institute of Electronics, CREI Home Study Division of McGraw-Hill, Grantham School of Engineering, International Correspondence Schools, National Radio Institute, National Technical School and RCA Institutes.

School demonstration lasers endanger science students

Lasers "powerful enough to drill holes through diamonds" are being used in high schools and colleges without adequate safety precautions, a seven-state survey has disclosed. The survey was made by the Bureau of Radiological Health of the Food and Drug Administration, and covered the states of Florida,

Illinois, Montana, Oklahoma, Pennsylvania and Washington.

"In many cases laser beams were directed at students or areas through which students might pass," the survey states. "In a few instances high school students were exposed to direct laser beams deliberately. One instructor said he wanted the students to see a beautiful effect." Lasers were also used where beams could be reflected toward students from windows or other reflective objects. Some 72% of the lasers were operated without nearby warning signs, and 52% lacked warning labels. In more than 90% of the cases studied there were factors that could pose an unsafe situation.

The Bureau recommends that direct laser viewing be avoided, that reflective objects be removed from laser beam paths and that the beam be blocked when it is not needed. It is further recommended that preparation and testing of laser classroom demonstrations be conducted when there are no students present, that key-locked switches be

used to prevent the equipment from being operated by unauthorized persons, and that operable lasers never be left accessible and unattended.

World's slimmest calculator uses 7,000 transistors

A pocket electronic calculator only $\frac{1}{8}$ inch thick has been placed on sale in the United States by Sinclair Radionics Ltd., England, known to many of our readers through the Sinclair pulse-width-



HAND-HELD ELECTRONIC CALCULATOR only $\frac{1}{8}$ inch thick contains 7,000 transistors.

modulation amplifier (class D) described in **Radio-Electronics**, September 1967. Performing all the functions of a conventional desk unit, the new calculator is only $5\frac{1}{2}$ inches long and 2 inches wide. It weighs $2\frac{1}{2}$ ounces.

Operating on tiny hearing-aid batteries, which have a normal life of three months, the Sinclair Executive, as it is called, has a display that shows up to eight numbers, plus a fixed or floating decimal point. As the batteries age, the luminous figures become dimmer, and fade out entirely before the machine's performance is affected.

In addition to the usual addition, subtraction, multiplication and division the functions include in-calculation squaring and reciprocals, plus a "constant key" memory that permits repeated multiplication or division by a pre-determined number, a useful feature in calculating interest or discounts, or in work that requires constant conversions from one unit to another.

The Sinclair Executive is priced at \$195, and is marketed in the U.S. through Koret Inc., N.Y.C.

(continued on page 14)



HOME-SIDE "SON ET LUMIERE" light show is a hobby of Mt. Airy, Pa. science teacher and Baptist minister Hugh Cosline. He has used all surfaces of a 12 x 15 x 10-foot room, modifying a bathroom to serve as control room. The mirrored wall at rear holds some 150 light boxes, and at left is seen an ever-changing pattern of crystal slides. On the floor, Mr. Cosline, at right, discusses the production with vice president Robert Edmund of Edmund Scientific Company, from which most of the equipment was obtained.

Don't let the handy size fool you.

The Serviset E/C is a complete, self contained versatile field test instrument. A precision-built, reliable, much-used instrument to compliment your VOM, scope or other equipment, too.

The Serviset E/C is great for servicing all sorts of electronics in the field and on the bench. Whether you're a professional engineer working on communications or EDP devices. An electronics or appliance technician working in radio, television, hi-fi audio or appliance repair. Or an amateur electronics enthusiast, ham radio operator or student.

Checks you'll make with the Serviset E/C include: sync, sweep, video, audio circuits; high or low DC, RF, or pulse voltage supplies; coils, capacitors, resistors, tubes, transistors, diodes, transformers, speakers--whatever you're trouble-shooting from stage to stage, or discrete components. What's more, your Serviset E/C is safe: whatever you check, you won't blow it.

The Serviset E/C. The \$35. Electronic Test Lab (almost) that will follow you anywhere. One of an advanced line of guaranteed electronic test devices from Lee that will save you time and effort. Including our CT-1 Condenser Tester and Leakage Indicator.

*send check or money order. C.O.D., send \$2. deposit.

Serviset E/C, \$34.95 postpaid *from Lee Electronic Labs.

Available also at electronic dealers and all Olson Stores, nationwide.


The \$35. Electronic Test Lab (almost) that will follow you anywhere: Serviset E/C



Lee Electronic Labs, Inc.

BOX 78, WATERTOWN, MASS. 02172 (617) 891-8686

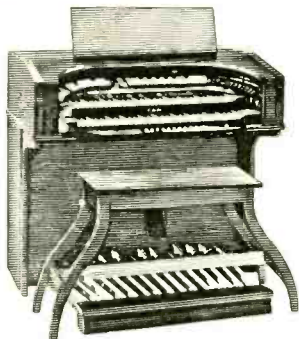**Now... the most enjoyable,
do-it-yourself project
of your life—a Schober
Electronic Organ!**



You'll never reap greater reward, more fun and proud accomplishment, more benefit for the **whole family**, than by assembling your own Schober Electronic Organ.

You need no knowledge of electronics, woodwork or music. Schober's complete kits and crystal-clear instructions show you — whoever you are, whatever your skill (or lack of it) — how to turn the hundreds of quality parts into one of the world's most beautiful, most musical organs, worth up to twice the cost of the kit.

Five superb models with kit prices from \$500 to around \$2,000, each an **authentic musical instrument actually superior to most you see in stores**, easy for any musically minded adult to learn to play, yet completely satisfying for the accomplished professional. And there are accessories you can add any time after your organ is finished — lifelike big auditorium reverberation, automatic rhythm, presets, chimes, and more.

Join the thousands of Schober Organ builder-owners who live in every state of the Union. Often starting without technical or music skills, they have the time of their lives — first assembling, then learning to play the modern King of Instruments through our superlative instructions and playing courses.

Get the full story **FREE** by mailing the coupon **TODAY** for the big Schober color catalog, with all the fascinating details!

The *Schober* Organ Corp., Dept. RE-114
43 West 61st Street, New York, N. Y. 10023

- Please send me Schober Organ Catalog.
 Enclosed please find \$1.00 for 12-inch L.P. record of Schober Organ music.

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

Circle 7 on reader service card

new & timely (continued from page 12)

First Atlantic transmission re-enacted by amateurs

To celebrate the 70th anniversary of the first transmission of a message across the Atlantic, a group of amateurs manned a special-event amateur radio station, WC1MAR, to re-enact the event, sending a duplicate of Marconi's original message. The station was set up on the original site of the Marconi station at South Wellfleet, Massachusetts, where Marconi himself tapped out the message of greeting from President (Theodore) Roosevelt to King Edward VII.

Hugo Gernsback Scholarship Winner

Cleveland Institute of Electronics has awarded its third annual Gernsback award scholarship to Peter B. Marceau of Wichita, Kansas. Peter receives \$125 from **Radio-Electronics** as an outstanding student at one of 9 home study schools of electronics. Peter is a Sergeant in the U.S. Air Force. He is 22 years of age and has served 3-1/2 years with the Air Force and has recently re-enlisted for another 6 years. Around the

middle of February, he will be transferred to England.



A student of CIE's electronics technology with laboratory program, Sgt. Marceau and his wife, Ann, are expecting their first child in February. It is interesting to note that it was while Mrs. Marceau was hospitalized with complications associated with her pregnancy in October that Sgt. Marceau wrote his award-winning essay. He actually wrote the article one night at the hospital. **R-E**

Radio-Electronics is published by Gernsback Publications, Inc. 200 Park Ave. S. New York, N.Y. 10003 (212) 777-6400
President: M. Harvey Gernsback
Secretary: Bertina Baer

ADVERTISING SALES

EAST
Stanley Levitan, Eastern Sales Mgr.
Radio-Electronics
200 Park Ave. South
New York, N.Y. 10003
(212) 777-6400

MIDWEST/Texas/Arkansas/Okla.
Ralph Bergen
The Ralph Bergen Co.
6319 N. Central Ave.
Chicago, Ill. 60646
(312) 792-3646

PACIFIC COAST/Mountain States
Jay Eisenberg
J.E. Publishers Representative Co.,
8560 Sunset Blvd.,
Suite 601,
Los Angeles, Calif. 90069
(213) 659-3810
420 Market St.,
San Francisco, Calif. 94111
(415) 981-4527

SOUTHEAST
E. Lucian Neff Associates
25 Castle Harbor Isle,
Fort Lauderdale, Florida 33308
(305) 566-5656

MOVING?

Don't miss a single copy of **Radio-Electronics**. Give us:

Six weeks' notice

Your old address and zip code

Your new address and zip code

ATTACH
LABEL
HERE

name (please print) _____

address _____

city state zip code _____

Mail to: **Radio-Electronics**
SUBSCRIPTION DEPT., BOULDER, COLO.
80302

Announcing the RCA MINI-STATE Antenna System



**The profitable new
achievement in antenna technology.**

The Mini-State is brand new from RCA. It's the first true miniaturized rotating antenna system on the market. *It works . . . and works well!*

This system is specifically made for your customers who want the quality reception of an outdoor-type antenna, in a beautifully compact unit.

Measuring just 21" across and 7" high, the Mini-State is completely enclosed in an attractive sturdy plastic case that's weatherproof and resistant to dust and dirt. It weighs just 6 pounds and can be mounted almost anywhere: rooftop, chimney, window, attic and closet.

While providing excellent reception for metropolitan and suburban areas, the RCA Mini-State's compact size makes it practical for apartments and homes. Its uni-directional pattern, VHF slotted ring and multi-element UHF design, combined with its completely integrated solid state circuitry, provides excellent reception on all channels, and helps avoid interference and ghosts.

Mini-State model 5MS440, with built-in rotator, allows your customers to zero-in for best reception on any chan-




nel. Exclusive direction indicator light on the hand held control unit tells them where the antenna is aimed.

The RCA Mini-State rotating antenna system includes: The antenna with built-in amplifier. Built-in rotator and hand held remote control unit. A 120 volt AC power supply. A VHF-UHF antenna matching transformer. An outdoor mast clamp. Legs which can be snapped into place for indoor use.

Although regular coaxial and rotator cable may be used, a unique combined coaxial and rotator cable is available in prefabricated lengths for quick, easy installation. (A fixed non-rotating model 5MS330 is also available.)

Yes, this new RCA Mini-State antenna system can mean maxi-profits for you. See your RCA Parts and Accessories distributor today, or contact RCA Parts and Accessories, P.O. Box 100, Deptford, N.J. 08096. Make sure you're in on the ground floor of this profitable new era in TV antenna systems.

RCA

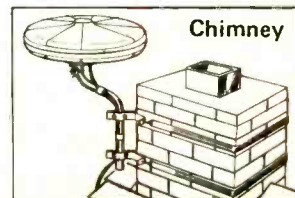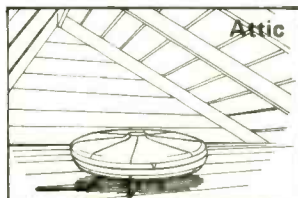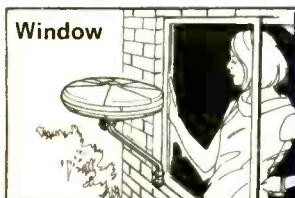

Circle 6 on reader service card



SERVICEMASTER
is
your best buy
in domestic
and
foreign
tubes.

- Discounted to provide you with a higher profit margin.
- Proven quality for better customer satisfaction.
- A complete range of domestic and foreign service types for consumer and industrial electronics.

For complete details, contact your International representative today, or International Components, 10 Daniel Street, Farmingdale, New York 11735/(516) 293-1500.

SERVICEMASTER
International ©

International Components Corp.

See us at NEWCOM Booths F-17 & 19

Circle 9 on reader service card

letters

RINGS THE BELL

Your editorial—"Serviceability—Something For Everyone"—rings the bell.

May I suggest that you invite technicians to send in their pet gripes

Mine is the way backs of portable TV sets are mounted. Sometimes it takes a great deal of fiddling to get them re-mounted. This is an unnecessary waste of time. Therefore I say . . . no antenna inputs—no speakers—no antenna rods should be mounted on the backs. Also there should be a plastic panel in the bottom of the cabinet which can be removed to get at the bottom of the chassis.

Another sore point is the lack of standardization of the hardware—in the same set. Sometimes three different self-tapping screws are used on tuners.

Plastic gears on tuners are another sore point. All uhf tuners should be separately tuned—no gearing.

JACK LANE
Los Angeles, Calif. 90046

Jack; if you and other readers want to really help yourselves, report any serviceability problems you encounter to the National Serviceability Committee of the National Electronics Association. This trade association group is responsible for collecting comments of this sort and bringing them to the direct attention of manufacturers. In fact, in the new serviceability rating forms, back removal is a specific section of the ratings and has a definite effect on the overall serviceability rating a TV receiver can earn for itself.—Editor

TELEVISION SERVICE TOMORROW

I own and operate Bell Television, a TV service shop in Chicago. When I discuss service technicians I am talking about consumer electronic service and by consumer electronic service I mean primarily television service. I mean independent television service and I mean television service for profit.

For us to try and look into the future, it is necessary that we study the past. In 1969 and 1970, J.W. Phipps of Electronic Servicing Magazine published a wealth of statistics on TV service. Those statistics pointed out problems which were very important then, but have since become critical. Some of the conclusions reached in the study of these statistics are: there are fewer shops and these fewer shops are using

more people. They are doing a larger volume of business at a smaller percentage of profit.

The reason they are making a smaller percentage of profit is that the cost of doing business has increased at a very high rate while the consumer cost of TV service has actually decreased. This decrease in profit margin makes it very hard to obtain a fair return on investments or build up a reserve for new equipment. It also makes it necessary to skimp and cut corners wherever possible.

Of course the obvious answer is to increase profits. However, I think that we will soon, if we haven't already, reach the point where the consumer may not be willing to pay what good service will cost.

To repair today's sets requires a man with a high degree of technical ability. He must be resourceful, industrious, neat and a passable amateur psychologist. The problem is that that type of man may not care to fix television sets. He can too easily find a job that is less demanding and pays more money.

With the present proliferation of basic designs, it is necessary that an effective technician be practically an engineer. We have tube chassis, plugged in and soldered in transistors in hybrid and solid state chassis. We have big boards, small boards, single-sided and double-sided boards. There are over 1200 different tube types in current use and God only knows how many different transistors.

What I am driving at is this. The public will not pay engineering prices for a service technician and we cannot sell them engineers at technician prices. This leaves open two avenues for the electronic service technician of the future. He can become a highly specialized person such as a product specialist (a man who knows very much about very little). However, to use product specialists requires a large operation and even the large operation must be specialized. A factory service operation is a perfect example. It is extremely hard for even a very large operation to effectively repair all makes and all models and make a profit doing so. The other course is for the technician to regress into a repairman. However, if this were to happen it would require that sets be easier to fix.

The present trend toward modu-
(continued on page 22)

Introducing the expensive curve tracer that doesn't cost a lot.

The B&K Model 501A.

It's a lab-quality instrument that provides fast analysis of all semiconductors including J-FET's, MOS-FET's, signal and power bipolar transistors, SCR's, UJT's and diodes.

You can test transistors in circuit for GO/NO GO condition. Badly distorted curves will indicate the stage where a defective transistor or other faulty component exists.

The 501A is complete—with scope graticule and FP-3 probe for fast, one-handed in-circuit testing. It generates true current and voltage steps, with 3% accuracy, for measuring beta at all current levels. And it has a sweep up to 100 volts and 100 milliamperes.

With the 501A, curves are displayed on an auxiliary scope screen. And you can hook it up to any scope—old or new.


All three controls can be set in quick-test positions to test and evaluate 90% of all solid-state devices without manufacturer's data sheets.

The 501A won't burn out either the semiconductors or itself.

With all these features, you'd think the 501A was an expensive curve tracer. But look at the price.

For complete technical data, call your B&K distributor. Or write Dynascan Corporation.

\$129.95

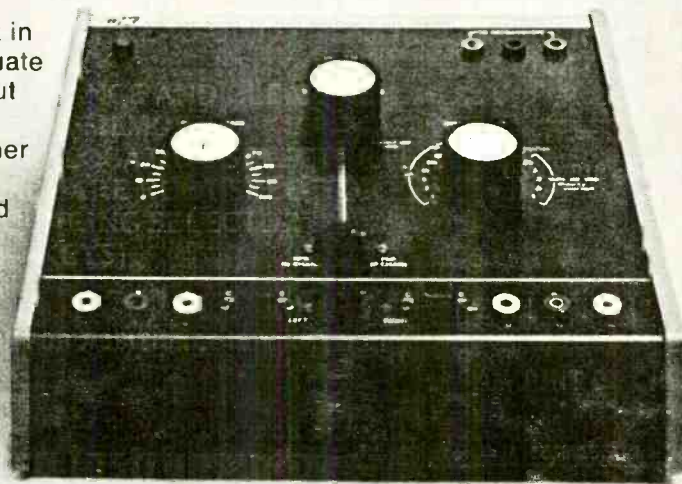


Very good equipment
at a very good price. **B&K**

Product of Dynascan Corporation
1801 West Belle Plaine Avenue, Chicago, Illinois 60613

Circle 10 on reader service card

MAY 1973 • RADIO-ELECTRONICS 17

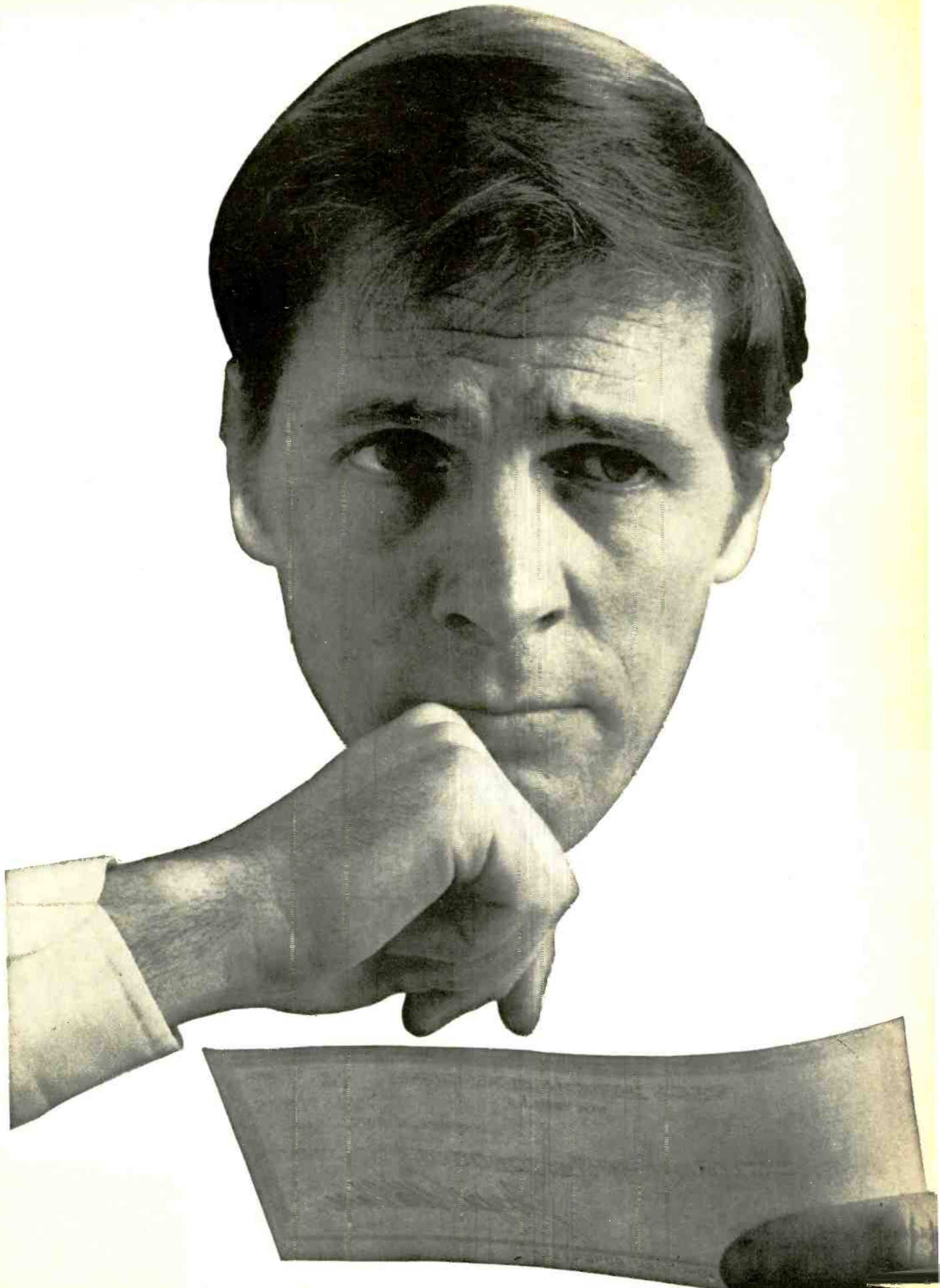

Your paycheck says a lot about you

It tells you more than how much you make. It tells you how far you've come. And if your paycheck looks very much the same as it did last year, or the year before, it simply means that you look very much the same as you did last year and the year before.

But times change, and you should be changing with them. Old dull jobs are disappearing. New exciting ones are being created. There are challenging fields such as computer technology, automation, television, space electronics where the work is interesting and the earnings are good.

RCA Institutes can give you the technical training you need, even if you've had no previous training or experience. RCA Institutes has a faster easy way for you to gain the technical skills and the knowledge required for an electronics career. And you don't have to quit work and go back to school. With RCA Institutes Home Study Plan you can work and study within reasonable limits. You set your own pace depending on your schedule.

Check over these RCA Institutes benefits:

- You get Hands-On Training—as many as 21 kits in RCA's Master TV/Radio Servicing Program.
- You get RCA's unique "Autotext" method of learning — individual programmed instruction, the easy, fast, simplified way to learn!
- You get a wide choice of electronics courses and programs—everything from Basic Electronics right up to Communications and Digital Electronics..
- You get a choice of low-cost tuition plans!

Sounds great, and it is. For complete information, without obligation, send in the attached postage paid card . . . or return the coupon below. That will say a lot about you.

Veterans: Train under new GI Bill. Accredited Member National Home Study Council. Licensed by N. Y. State Education Dep't — courses of study and instructional facilities approved by the State Education Department. "Eligible Institution" under the Federally insured Student Loan Program.

RCA Institutes, Inc. is a Subsidiary of RCA Corporation

RCA Institutes

Home Study Dept. 758-305-0
320 West 31st Street, New York, N.Y. 10001

Please rush me FREE illustrated catalog.
I understand that I am under no obligation.

Name _____ Age _____
(please print)

Address _____

City _____ State _____ Zip _____

Veterans: Check here

If reply card
is detached—
send this
coupon today

HOW DOES GEORGE DO IT?

*3 IN A SERIES



IN EVERY GROUP OF TECHNICIANS, THERE'S A "GEORGE" WHO ALWAYS SEEMS TO EARN A LITTLE MORE THAN THE REST OF US--SOMETIMES EVEN WITH SHORTER HOURS TO HELP EVERY TECHNICIAN MAKE THE MOST OF HIS TIME, HERE'S "HOW GEORGE DOES IT!"




HOW ABOUT TAKING THE WIVES TO DINNER TONIGHT?



WISH I COULD, BUT I'VE GOT A RAFT OF CALL-BACKS I'VE BEEN PUTTING OFF.

ANY KIND IN PARTICULAR?

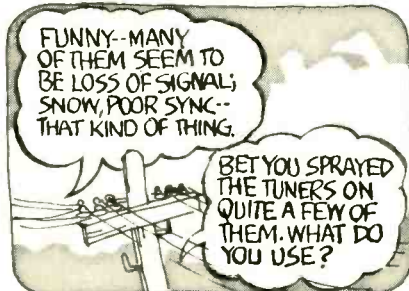


FUNNY--MANY OF THEM SEEM TO BE LOSS OF SIGNAL; SNOW, POOR SYNC-- THAT KIND OF THING.

BET YOU SPRAYED THE TUNERS ON QUITE A FEW OF THEM. WHAT DO YOU USE?



OH ONE OF THE "SPECIAL" TUNER SPRAYS JOE CARRIES--YOU KNOW.

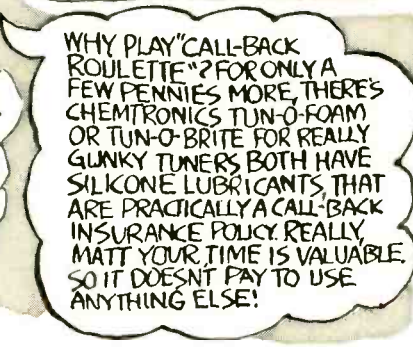THERE'S YOUR PROBLEM. MOST LOW-PRICED SPRAYS ARE NO "BARGAIN" AT ALL. IN A SET, THE LUBRICANTS ARE LIKE AXLE GREASE--THEY SOMETIMES DRY UP IN A MONTH!



WHY PLAY "CALL-BACK ROULETTE"? FOR ONLY A FEW PENNIES MORE, THERE'S CHEMTRONICS TUN-O-FOAM OR TUN-O-BRITE FOR REALLY GLUNKY TUNERS BOTH HAVE SILKONE LUBRICANTS, THAT ARE PRACTICALLY A CALL-BACK INSURANCE POLICY. REALLY, MATT YOUR TIME IS VALUABLE, SO IT DOESN'T PAY TO USE ANYTHING ELSE!

WHY LET GEORGE DO IT? DO IT YOURSELF WITH TUN-O-FOAM TUN-O-BRITE TWO CHEMTRONICS CHEMICAL PROBLEM-SOLVERS THAT SAVE YOU TIME AND MONEY.

SEND FOR OUR FREE PROBLEM-SOLVING BROCHURE AND CATALOG.

CHEMTRONICS INCORPORATED
1260 RALPH AVENUE, BROOKLYN, NEW YORK, 11236, OUR BUSINESS IS IMPROVING YOURS

Circle 11 on reader service card

LETTERS

(continued from page 16)

larization is a long step in that direction. Virtually all major American manufacturers are either now producing or have on the drawing boards, chassis using the modular concept. Using some of the troubleshooting guides is so simple that the less conventional electronics a man knows, the faster he will adjust to using the go-no go charts.

This does not mean that the highly skilled men now employed in our profession must take a crash course in stupidity. It simply means that they will be used in higher levels of service for we will always need someone to fix the set when the troubleshooting manual cannot.

It would be difficult to discuss the future of the TV service technician without bringing up the subject of licensing. Many, if not a majority, of service technicians have a deep fear of licensing, but most service association leaders are committed in favor of licensing. They qualify that, however, by saying that the license bill must be a "good" one. A "good" license bill provides for a license board which has as a majority of its members people who are actually "in the business". Also a good bill is one which pays for its own administration but does not provide too much surplus revenue for the State. A good bill should set minimum standards of equipment needed for shop licenses. It must provide for prompt judicial appeal of license revocations. A good license bill must not restrain new people from coming into the business but merely make sure they satisfy minimum requirements of conducting a TV repair business.

Another item for consideration is the impact of unions. The one possible good that could come from unionization is that it would standardize labor costs and thereby cut down the spread of service rates from shop to shop.

If we had licensed shops and union service technicians it is possible that we could someday earn as much as plumbers.

I think that the average shop in five years will be three to five men instead of one and will be subject to some type of government controls or registration. It will have to be much more efficient in the paperwork department. It will not serve all makes and models but will limit itself to servicing three or four major brands and three or four minor brands. These shops will be tight shops, compared to today's standards, and will enjoy a better public image and will be more rewarding in every sense of the word.

R-E


GEORGE WEISS
Bell Television, Inc.
4605 North Kedzie Avenue
Chicago, Ill. 60625

Leader outduals them all!

LBO-505 DUAL CHANNEL/ DUAL TRACE SOLID STATE OSCILLOSCOPE

MODEL LBO-505 \$669.95

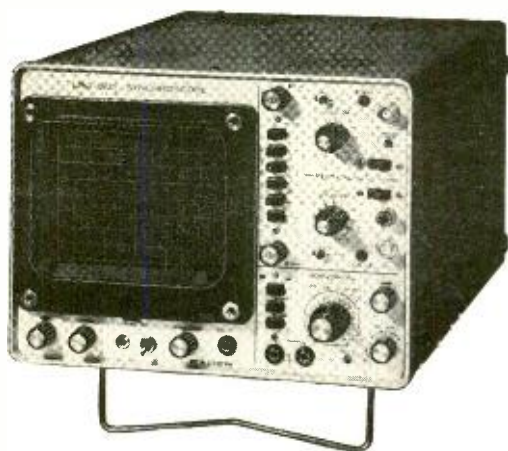Price Includes:
2 LPB-8X Direct Lo/Cap Probes
2 Terminal Adapters — BPX
1 Set of Test Leads



The more you see... the more you believe.

Accuracy! Performance! Exclusive, Leader-developed features! That's what makes the LBO-505 the Number One Dual Channel/Dual Trace Scope. You get triggered and automatic sweep. AC or DC coupling per channel. 15MHz bandwidth. Maximum horizontal speed of 0.1 microseconds/cm (10X magnification). 10MVp-p/cm vertical sensitivity. Separate or simultaneous display in sweep mode of channels 1 and 2, alternating, chopped, added algebraically and vector (X-Y). The triggered sweep range extends from 1 μ s/cm to 0.5s/cm, calibrated in 17 steps. Scale illumination is continuous with front panel control.

How can you use the LBO-505 most efficiently? You'll find more ways than you can think of... at first. It makes troubleshooting a breeze! Compare 2 signals simultaneously — input and output, for color, monochrome, audio and much more. Check gain, loss, distortion, phase shift, frequency... you name it. Do your own thing. The LBO-505 belongs on every bench and in every lab. Feature-for-feature, price-for-price, job-for-job... it outduals them all!

Send for new catalog. See your distributor.

Leader

INSTRUMENTS CORP.

37-27 Twenty-Seventh Street
Long Island City, New York 11101
(212) 729-7410

Circle 12 on reader service card

MAY 1973 • RADIO-ELECTRONICS 23



You get more "security" And it's all do-it-yourself.

The Mallory line of security products is not only the most complete line you can get anywhere, it's also just about the easiest to hook up. It's genuinely a do-it-yourself line.

Especially the complete systems. From complete home intrusion alarm systems (plug-in or wire-in) to smoke alarms and car alarms.

And we have all the accessories you need to expand and adapt any of these systems to your specific security needs.

Look for our security systems and accessories on display in their bright, new packages (with installation directions printed right on each package). It's all at your Mallory distributor's now.

In the meantime, look at the table on the right. It's everything we have in security products to date. A complete selection for one-stop security shopping.



from Mallory.

THE MALLORY SECURITY LINE

WIRE-IN

COMPLETE ALARM SYSTEMS

Closed-Circuit Alarm System

Complete alarm system containing batteries, switches, wire, etc.

Crime Alert Ultrasonic Intrusion Alarm

Battery-operated, self-contained alarm. Also operates on AC.

Car Alarm

Alarm system containing siren, six switches, wiring, etc.

ACCESSORIES

DC Weatherproof Siren
 DC Vibrating Bell
 Magnetic Switches
 Heat Sensors 135°F or 200°F
 Panic Switch
 Alarm Hook-Up Wire
 Lockswitch Round or Flat Key
 Mallory Batteries
 Auto Headlight or
 Turn Signal Alarm
 Warning Decals

PERSONAL ALARMS

Bloc Alarm
 Blocks doorways and warns if door is forced.

Handy Blast
 Loud, piercing sound scares molesters away.

Handy Blast Refill

PLUG-IN

COMPLETE ALARM SYSTEMS

Smoke Alarm

Self-contained alarm to warn against smoke and fire.

Crime Alert Ultrasonic Intrusion Alarm

Self-contained alarm which detects intruders moving in an area of approximately 300 sq. ft.

Crime Alert Alarm System

Ultrasonically detects intruder. Transmits alarm signal over house wiring to signal activated bell. Simple plug-in installation.

Manual Alarm Pack

Manually summons help instantly by transmitting alarm signal over house wiring to signal activated bell when you push the button.

ACCESSORIES

Wood Cabinet for Crime Alert
 Alarm Duration Timer for Crime Alert
 Easy-Time 24-Hour Timer
 Lockswitch Round or Flat Key
 Power Failure Alarm
 Mallory Batteries
 AC Vibrating Bell
 AC Weatherproof Horn
 AC Weatherproof Siren
 AC Rotating Red Light

SIGNAL ACTIVATED COMPONENTS

Transmit and receive alarm signal through house wiring.

Alarm Trigger—Transmits signal to:

Alarm bell	Weatherproof horn
Weatherproof siren	Outlet
Sonalert	



Send for our new Security Systems Catalog 9-654.
 It describes every item listed here, explains how to use them.



MALLORY DISTRIBUTOR PRODUCTS COMPANY
 a division of P. R. MALLORY & CO. INC.
 Box 1284, Indianapolis, Indiana 46206; Telephone: 317-636-5353



Circle 13 on reader service card

now 9 midget driver sets



for double duty on dozens
of popular screws and nuts



Three new assortments have joined Xcelite's family of "Compact Convertibles." Each an Xcelite "original." Nowhere will you find such a variety of sizes and types in a midget set, for driving slotted, Phillips, Allen, Scrulox®, hex, and clutch head screws. And hex nuts.

All of professional quality, precision made of finest materials. All doing "double duty" with torque amplifier handle that slips over color-coded midget tools for longer reach, greater driving power. Each easily identifiable on the bench or in the service kit thru Xcelite's exclusive, optically clear, plastic "show case" that closes securely with positive snap-lock.

nationwide availability through local distributors

NEW!

PS130
3 slot tip, 2 Phillips
screwdrivers, 5 nutdrivers

PS140
4 slot tip, 3 Phillips screwdrivers, 3 nutdrivers

PS6
3 slot tip, 3 Phillips screwdrivers

PLUS PS88, PS120, PS7, PS89, PS44
and PS-TR-1 with varying selections
of screwdrivers and nutdrivers.

REQUEST
FREE CATALOG.



XCELITE, INC., 10 Bank St., Orchard Park, N. Y. 14127
In Canada contact Charles W. Pointon, Ltd.

Circle 14 on reader service card

26 RADIO-ELECTRONICS • MAY 1973

equipment report

B&K Model 281 Digital Multimeter



Circle 27 on reader service card

EVERYTHING LATELY IS GOING "DIGITAL indicators". B & K-Precision has a new digital multimeter (DMM), the model 281. We gave one a good workout on the bench and were impressed with it. It's compact, easy to read (which is the main thing with digital instruments anyway!) and very handy.

The model 281 has 5 voltage ranges for ac and dc voltage; 0-100 mV, 0-1.0 V, 10 V, 100 V and 1,000 V. The dc voltage range has a positive and negative selector. Both dc and ac current can also be read, using the same fundamental 0-1 scale. For resistance, you can read 0-10 ohms (full-scale!) 100, 1,000, 10,000, 100,000, 1.0 megohm and 10.0 megohms. (There are two extra ohms ranges, for very low and very high resistances.)

This instrument has some cute features that make it very handy. For example, each range has a 100% "over-range" capability. This means that the 0 to 1-volt scale, for example, will read voltages up to 1.99 volts, accurately, and display the reading in that way. Even on the 0 to 1000-volt range, you can read voltages up to 1,990.

The selector switch lets you read positive or negative dc voltages. If you get the probes reversed, the 281 tells you! The "1" digit stays on, and the other two go out. This means; Reverse the probes or flip the selector switch.

If the voltage (ac or dc) goes over the 100% overrange, say above 200 volts on the 100-volt range, the "1" digit goes out, and the other two flash off and on, together.

You get the same error indication if the probes are reversed when reading dc currents. The "1" goes out and the other two blink.

The decimal point moves automatically, as the RANGE switch is turned. There's a very handy table in the instruction book, to tell you how to set each switch, and how to read the display for each range, including the maximum overrange reading. Basically, each one will come out 0 to 1.99, whether in volts or hundreds of volts.

The model 281 uses the standard IC drivers and decade counters for the digital readouts. FET's are used in several places. The dc power supplies are very closely regulated, to avoid inaccuracy caused by ac line voltage variations. Accuracy of calibration, by the way, is very good, $\pm 1\%$ of full range, or ± 1 digit.

The digital readout of the 281 uses two neon number-display tubes, similar to Nixies, and a neon lamp for the left-hand or "one" digit. This is known as a two-and-a-half digit readout.

The cabinet is compact and sturdy. It has a metal handle with detents, that can be used for carrying, or locked in place as a tilt leg to raise the front for better viewing. You can read this instrument all the way across the shop.

A handy test-probe is provided. It has a selector switch, for inserting a 100,000-ohm series isolation resistor. It reduces capacitive loading of the circuits by the probe. Because of the very high input impedance, 10 megohms on all ranges, the effect of this resistor on calibration is very small. In fact, it's only -1% of full-range reading. If you want to be nasty-nice, you can add a correction factor.

All in all, the 281 is a very handy instrument for all-around service work. We gave it a pretty good going-over on several different service jobs, and it performed very well. **R-E**

NEXT MONTH

Bob Middleton shows how you can test IC's 11 different ways, using your vtvm. Don't miss this timely article.

1440



**up-date
YOUR
ABACUS!**

4½ POUNDS 8" X 12" X 4"

TRADE THE BEADS FOR KEYS...THE MITS 1440 SPACE AGE CALCULATOR!

- 14 DIGIT LED DISPLAY READ-OUT
- + MOS-LSI CIRCUITRY
- MEMORY CLEARANCE AND CLEAR KEY
- x CONSTANT DATA MEMORY
- ÷ DECIMAL POINT LOCATION SELECTOR
- √ AUTOMATIC SQUARE ROOT SELECTOR
- AUTOMATIC² SQUARING SELECTOR
(MEMORY + OR - KEYS)

- 1440 KIT \$199.95
- 1440 ASSEMBLED \$249.95


USE YOUR MASTER CHARGE OR BANKAMERICARD

WRITE OR MAIL COUPON FOR ADDITIONAL INFORMATION:

mits[®] Micro Instrumentation & Telemetry Systems, Inc.
5404 Coal Ave., S. E., Albuquerque, New Mexico 87108
505/265-7553

ENCLOSED IS CHECK	<input type="checkbox"/> KIT
FOR MODEL # _____	<input type="checkbox"/> ASSEMBLED
AMOUNT OF CHECK \$ _____	R-5-73
Include \$5.00 for postage and handling.	
<input type="checkbox"/> Please send information on entire MITS line.	
NAME _____	
ADDRESS _____	
CITY _____	
STATE & ZIP _____	

Circle 15 on reader service card

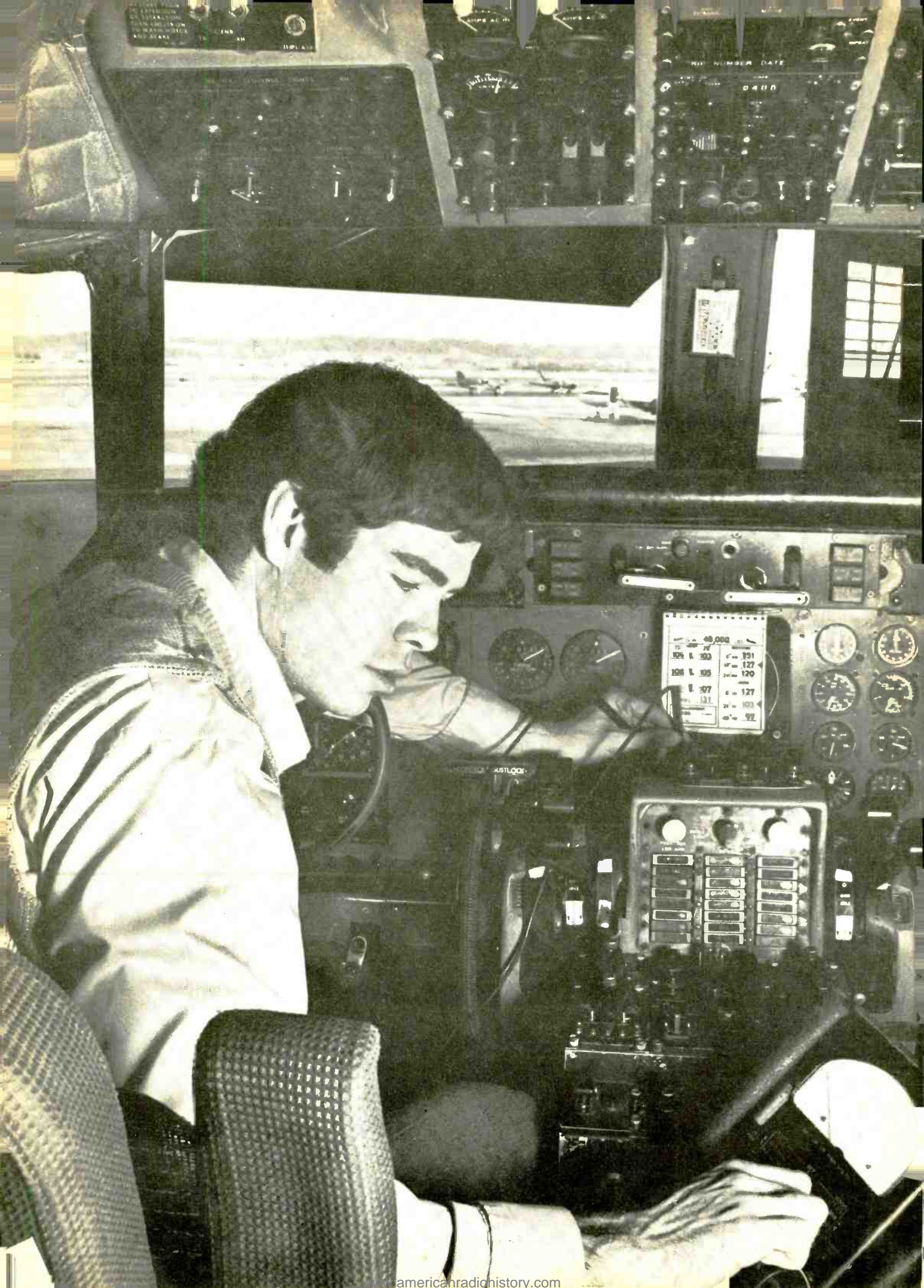

1191.4

NO. NUMBER DATE
P 400

MEMO	
15	40,000
100	151
100	127
100	120
100	127
100	103
100	92

Modern aircraft are loaded with vital electronic equipment. There is equipment for communications, direction finding, instrument landing and for many other functions to insure safe operation of the aircraft.

The man who checks out this equipment has to be an expert. Many lives depend on his specialized knowledge as an engineering technician. His work is interesting and exciting and he enjoys top pay in his field.

Consider a career In advanced electronics

Aeronautical and Navigational Electronics is just *one* of the advanced electronics programs CREI offers. There are *seventeen* others. All of the programs, except a brief introductory course, are college-level. The programs cover every major field of electronics today.

If you want to qualify for the highest paying level of technical employment in electronics, we invite you to consider the unique home study programs of CREI. Here is a list of just some of the CREI programs: *Communications Engineering • Computer Engineering • Missile & Spacecraft Guidance • Radar & Sonar • Television Engineering • Nuclear Instrumentation & Control • Digital Communications • Industrial Electronics • Electronic Systems Engineering • Microwave Communications • Satellite Communications • Cable Television Engineering*

For over 45 years, CREI programs have been recognized by industry and government as effective home study training in advanced electronics.

Qualifications to enroll. To qualify for enrollment in a CREI program, you must be a high school graduate (or equivalent). You should also be working in electronics or have previous training in this field.

Send for FREE book. If you are qualified, send for CREI's newly published book describing your career opportunities in advanced electronics. This full color book is filled with facts about career opportunities for you.

Capitol Radio Engineering Institute
A Division of McGraw-Hill Continuing Education Co.
3939 Wisconsin Avenue, Washington, D. C. 20016



Accredited Member, National Home Study Council

CREI, Dept. E1405D
3939 Wisconsin Avenue
Washington, D.C. 20016

Rush me your FREE book describing my opportunities in advanced electronics. I am a high school graduate.

Name _____ Age _____

Address _____

City _____ State _____ ZIP _____

If you have previous training in electronics, check here

Employed by _____

Type of Present Work _____

Veterans and servicemen, check here for G. I. Bill information

CREI
**CAPITOL
RADIO
ENGINEERING
INSTITUTE**

WASHINGTON, D.C.

Get the whole kit and caboodle from RCA



Now available from RCA is a wide variety of solid-state components in convenient kit form to build interesting and useful projects. Each one gives you the essentials for getting the most out of your project in enjoyment, knowledge and performance.

And with RCA's popular hobby and experimenter's manuals, you can expand your solid-state experience. For example, the 368-page RCA Solid State Hobby Circuits Manual (HM-91) has over 60 interesting circuits you can build, and the 136-page RCA Silicon Controlled Rectifier Experimenter's Manual (KM-71) has 24 more! See your RCA Distributor to buy the RCA Kits and Manuals of your choice.

RCA | Electronic Components | Harrison, N.J. 07029.

RCA IC Project Kits, Experimenter Kits, and Devices

Type	Description	Type	Description
KC4000	1 C. Microphone Pre-Amplifier Kit	KD2100	Silicon Control Rectifier Assembly
KC4001	1 C. Two-Channel Mixer Kit	KD2105	SCR Experimenter Kit
KC4002	1 C. Audio Oscillator Kit	KD2106	Add on Light Sensor Kit
KC4003	1 C. Power Amplifier and Oscillator Kit	KD2110	Add on Heat Sensor Kit
KC4004	1 C. Regulated Power Supply Kit	KD2117	1 C. Experimenter Package Basic Kit Contains: 2-KD2114, 1-KD2115, 2-KD2116
KC4005	1 C. Intruder Alarm Kit	KD2118	NPN Silicon Variety Pack (5 Units)
KC4006	1 C. Fire Alarm Kit	KD2120	PNP Silicon Variety Pack (5 Units)
KC4007A	1 C. Converter Kit: 118-136MHz Aircraft Band	KD2123	PNP Germanium Variety Pack (5 Units)
KC4008A	1 C. Converter Kit: 134-150MHz Ham, Government, Space Research Band	KD2124	NPN Germanium Variety Pack (5 Units)
KC4009A	1 C. Converter Kit: 148-164MHz Maritime Mobile, Police, Fire Band	KD2131	70-Watt IC Power Module
KC4010A	1 C. Converter Kit: 160-174MHz Police, Fire Band	3N128DP	MOS/FET Device in Display (Blister) Pack
KC4011	Digital/Readout IC Kit	40214DP	18 Amp. 1/4 in. Stud Silicon Rectifier Device in Display (Blister) Pack
KC4012	Digital/Counter IC Kit		
KC4500	Kit Enclosure for use with KC4000, KC4001, KC4002, includes Input & Output Jacks, On-Off Switch and Hardware		

RCA Electronic Components

These companies have RCA kits and manuals on sale now.

ALABAMA

Birmingham
R.P. McDavid Co., Inc.
1430 2nd Avenue South
Mobile
Specialty Distributing Co. of Ala., Inc.
1276 Bertline Highway, South

ALASKA

Anchorage
Yukon Radio Supply
3222 Commercial Drive
Fairbanks
Yukon Radio Supply
1112 Cushman Street

ARIZONA

Nogales
Guarantee Electronic Corp.
301 Marley Avenue

ARKANSAS

Fort Smith
Wise Wholesale Electronics, Inc.
1001 Towson Avenue

CALIFORNIA

Canoga Park
Sandy's Electronic Supply
21305 Satucov Street
Fresno
Dunlap Electronics
1750 McKinley
Harbor City
Buff's Electronics
25828 South Western Avenue
Hollywood
Yale Radio Electric Company
6815 Sunset Boulevard
San Francisco
Hauer Electronic Supply
1185 Mission Street

COLORADO

Boulder
Burstin Applebee Company
2626 Base Line Road
Colorado Springs
D & M Electronic Supply
P.O. Box 1777 715 N. Welser Street
Denver
Burstin Applebee Company
800 Lincoln

CONNECTICUT

Waterbury
Harty of Waterbury
480 Waterdown Avenue

DELAWARE

Dover
Standard Electronics of Delaware
1277 South Governor's Avenue
Wilmington
RESCO Electronics of Delaware
3601 North Market Street

FLORIDA

Tampa
Lykes Electronics Corporation
121 South Ashley Drive

GEORGIA

Albany
Specialty Distributing Co.
428 Roosevelt Avenue
Athens
Specialty Distributing Co.
230 Epps Bridge Road
Atlanta
Specialty Distributing Co.
3787 N.E. Expressway
Specialty Distributing Co.
763 Juniper Street, N.E.
Augusta
Specialty Distributing Co.
1251 Gordon Park Road
Brunswick
Specialty Distributing Co.
2817 Curie Street
Columbus
Specialty Distributing Co.
1112 Brookhaven Boulevard
Nation
Specialty Distributing Co.
538 Arch Street
Marietta
Specialty Distributing Co.
105 White Avenue
Savannah
Electronics 21, Inc.
21 East DeRenne
Specialty Distributing Co.
612 East Broad Street
Valdosta
Specialty Distributing Co.
916 Marion Street

ILLINOIS

Champaign
Klaus Radio, Inc.
905 South Neil Street
Chicago
Alford Electronics
2400 West Washington Boulevard
Heathkit Electronics Center
3462 West Devon Avenue
Howard Electronics
4573 South Archer Avenue
Joseph Electronics, Inc.
1733 North Harlem Avenue
North Central Electronics Supply Co.
3412 W. Bryn Avenue
Danville
Radio Shack
806A East Main Street
Des Plaines
RCA Distributing Corp.
424 East Howard Avenue
Downers Grove
Heathkit Electronics Center
224 Queen Avenue
Glenview
Playback, Inc.
Talisman Shopping Center
2654 Golf Road
Jacksonville
Baird Electronics
419 South Main Street
Jones
Mantle Supply Company
804 Theodor Street
Kankakee
Playback, Inc.
256 Court Street
Niles
Joseph Electronics, Inc.
8024 North Milwaukee Avenue
Peoria
Klaus Radio, Inc.
8400 N. Pioneer Parkway
Rockford
J & M Electronics, Inc.
7001 9th Street

INDIANA

Waukegan
Balger Electronics, Inc.
1105 Washington Street
Wilmette
Playback, Inc.
Furness Plaza Shopping Center
1346 Lake Street
Columbus
H. A. Williams Company
1003 Washington Street
Evansville
Ohio Valley Sound, Inc.
20 E. Sycamore Street
Indianapolis
Associated Distributors, Inc.
210 S. Meridian Street P.O. Box 372
Graham Electronics Supply, Inc.
133 S. Pennsylvania Street
Meurer Electronic Supply, Inc.
3409 E. Washington Street
South Bend
Radio Distributing Company
1212 High Street
Vincennes
Ohio Valley Sound, Inc.
902 Main Street

IOWA

Des Moines
Radio Trade Supply Company
1013 1017 High Street
Siles Distributing Company
2205 Bell Avenue

KANSAS

Lenexa
RCA Distributing Corp.
Old Santa Fe Trail & 102nd Street
Overland Park
Burstin Applebee Company
9629 Metcalf Avenue
Pittsburg
Pittsburg Radio Supply
212 S. Broadway
Wichita
Amateur Radio Equip. Co., Inc.
1203 E. Douglas

KENTUCKY

Louisville
Peerless Electronic Equipment Co.
1815 South 7th Street
Owensboro
Ohio Valley Sound, Inc.
500 W. Third Street

MARYLAND

Hagerstown
Alleghe Electronics, Inc.
1301 Potomac Avenue
Hyattsville
Mark Electronics, Inc.
3003 Hamilton Street
Salisbury
Standard Electronics
701 Snow Hill Road

MICHIGAN

Detroit
RS Electronics, Inc.
12775 Lyndon Avenue
Ferndale
Midway Electronic Supply
990 W. 8 Mile Road
Flint
Shand Electronics, Inc.
2401 S. Dort Highway
Grand Rapids
RS Electronics - Grand Rapids, Inc.
505 Jefferson S. E.
Kalamazoo
RS Electronics - Kalamazoo, Inc.
3219 E. Kilgore Road
Lansing
Fulton Radio Supply Co.
7207 Alpha Street
Wedenmeyer Electronic Supply Co.
800 Merrill Avenue
Muskegon
Electronic Distributors, Inc.
1960 Peck Street
Roseville
RS Electronics, Inc.
27852 Grant
Saginaw
Morley Brothers
525 Morley Drive
Traverse City
RS Electronics - Traverse City, Inc.
425 S. Airport Road
Wyandotte
RS Electronics - Wyandotte, Inc.
3450 Biddle Avenue

MISSOURI

Columbia
Missouri Cable Company
107 North 7th Street
Kansas City
Burstin Applebee Company
73 Blue Ridge Mall
Burstin Applebee Company
3199 Mercier
Rolla
Show Me Electronics
Highway 72 East P.O. Box 639
Sedalia
Radio & Television Supply, Inc.
321 East Main Street
St. Louis
Radonics Electronics, Inc.
4445 Gustine Avenue
Van Sickle Radio Electronics, Inc.
1915-1917 Washington Avenue
Springfield
Reed Radio & Supply Co., Inc.
805-809 Bonville Avenue

NEW JERSEY

Burlington
Rein Distributors, Inc.
Rt. 130 and Wood Street
Camden
General Radio Supply Co.
800 Penn Street
Cherry Hill
RESCO Electronics, Inc.
Cherry Hill Mall Drive Rt. 38
Hackensack
Midisco, Inc.
55 State Street
Hammonton
Maco Electronics
300 South Egg Harbor Road
Jersey City
Nidisco, Inc.
713 Newark Avenue
Passaic
Nidisco, Inc.
294 Passaic Street

NEW MEXICO

Albuquerque
Sterling Electronics
1712 Lomas Boulevard N.E.
Walker Radio Co., Inc.
102 West Granite Avenue N.W.
Trenton
Nidisco, Inc.
985 Princeton Avenue
Union City
Nidisco, Inc.
2812 Kennedy Boulevard

NEW YORK

Brooklyn
Mill Electronics Supply
2480 65th Street
Buffalo
Summit Distributing, Inc.
916 Main Street
Hempstead
Lafayette Radio Electronics Corp.
120 N. Franklin Street
Jamaica
Lafayette Radio Electronics Corp.
92-35 Merrick Blvd.
Lackawanna
Crossdown Electronics
Abbott & Ridge Road
Lake Grove
Lafayette Radio Electronics Corp.
2848 Middle Country Road
Lynbrook
Lafayette Radio Electronics Corp.
381 Sunrise Highway
Massapequa
Lafayette Radio Electronics Corp.
M. S. Shopping Center
5288 Sunrise Highway
New Rochelle
Lafayette Radio Electronics Corp.
218 North Avenue
New York
Lafayette Radio Electronics Corp.
49 West 45th Street
Lafayette Radio Electronics Corp.
17 Union Square West
Lafayette Radio Electronics Corp.
45 Warren Street
Reno Park
Lafayette Radio Electronics Corp.
95 20 Queens Boulevard
Scarsdale
Lafayette Radio Electronics Corp.
691 Central Avenue
Syosset
Lafayette Radio Electronics Corp.
111 Jericho Turnpike
Westbury
Lafayette Radio Electronics Corp.
541 Old Country Road

NORTH CAROLINA

Asheville
Freck Radio & Supply Co., Inc.
3840 Biltmore Avenue
Jacksonville
Southeastern Radio Supply Co.
1009 Lejeune Boulevard
Wilmington
Southeastern Radio Supply Co.
1002 South College

OHIO

Akron
Fox Radio Parts Company
300 Akron Square Shopping Center
1615 South Arlington Street
Cincinnati
United Radio, Inc.
Summit & Reinhold
Cleveland
Fox Audio Center
3736 Rocky River Drive
Fox Radio Parts, Inc.
4314 Lee Road
Main Line, Inc.
1260 East 38th Street
Columbus
Hughes Peters, Inc.
481 East 11th Avenue
Whitehead Radio Company
124 North Grant Avenue
Dayton
The Stotts-Friedman Company
108 North Jefferson Street
Elyria
EL A CO Electronics, Inc.
235 Lodi Street
Mansfield
Fox Radio Parts Company
1225 Park Avenue, West
Springfield
Becker Electronics Div.
522 West Main Street
Toledo
Burstin Applebee Company
2040 South Reynolds Road
Main Line, Inc.
Willis Day Industrial Park
RS Electronics-Toledo, Inc.
4665 West Bancroft
Zanesville
Thompson Radio Supplies
110 South Sixth Street

OKLAHOMA

Oklahoma City
Dajavian's, Inc.
100 North West 44th Street
Radio Supply, Inc.
724 North Hudson Street
Tulsa
S. S. Radio Supply Company
537 South Kenosha

OREGON

Eugene
United Radio Supply
974 West 6th Avenue
Pendleton
Round-up Electronics
2921 Riverside Avenue
Portland
H. R. Radio Supply
1812 NE 43rd Avenue
United Radio Supply, Inc.
123 NE 7th Avenue

PENNSYLVANIA

Allentown
Radio Electric Service Co.
of Lehigh Valley, Inc.
425 Handover Avenue
Drexel Hill
Kass Electronics Distributors, Inc.
2502 Township Line Road
Easton
Radio Electric Service Co.
of Lehigh Valley, Inc.
1700 Northampton Street
Elysas Park
A. G. Radio Parts Co.
939 Township Line Road
Lancaster
Barbey Electronics, Inc.
622 Columbia Avenue
Lebanon
Barbey Electronics, Inc.
821 Quentin Road
Norristown
Phila. Electronics, Inc.
624 West Ary Street
Philadelphia
Herbach & Rademan, Inc.
401 East Erie Avenue
RESCO Electronics, Inc.
6587 Roosevelt Boulevard
Raymond Rosen Parts & Service
Parkside Avenue at 51st Street
Eugene B. Wue Electronic Components
218 220 South 11th Street
Pottstown
Barbey Electronics, Inc.
157 North York Street
Pottsville
Moyer Electronic Supply Co., Inc.
300 East Norwegan Street
Reading
Barbey Electronics, Inc.
333 North 4th Street
Wittow Grove
RESCO Electronics, Inc.
29 York Drive

SOUTH CAROLINA

Charleston
Wholesale Radio Supply Company
515 East Bay Street
Charleston Heights
Wholesale Radio Supply Company
3301 Rivers Avenue
Columbia
Oxie Radio Supply Co., Inc.
1900 Barnwell Street

TENNESSEE

Bristol
Lafayette Radio Electronics
Associate Store
1275 Volunteer Parkway
Chattanooga
Specialty Distributing Company
1313 Central Avenue
Kingsport
Radio Electric Supply Company
961 East Sullivan Street

TEXAS

Austin
Electrotex-Austin
914 West 12th Street
Beaumont
Electrotex-Beaumont
1275 South 11th Street
Brownsville
Electronics Suppliers, Inc.
757 East St. Charles
Corpus Christi
Electrotex-Corpus Christi
4019 Brett
Dallas
Auliera Electronics Company
1907 McKinney Avenue
El Paso
Midland Specialty
2235 Wyoming
Harlingen
Electronic Suppliers, Inc.
217 East Monroe
Houston
Art Jones & Co.
1415 West Loop North
Electrotex-Houston
2300 Richmond Avenue
Electrotex-East
8540 Winkler Drive
Electrotex-North
512 Crosstimbers
Sterling Electronics
4201 Southwest Freeway
Irving
Electrotex
3417 E. Carpenter Freeway
Le Marque
Electrotex-LaMarque
216 Byrd Street
Lufkin
Electrotex-Lufkin
408 Atkinson Drive
McAllen
Electronics Suppliers, Inc.
408 South Broadway
San Antonio
Electrotex-San Antonio
910 West Laurel
Victoria
Electrotex-Victoria
1007 North Williams
Waco
Hargis Company
1205 Washington

UTAH

Salt Lake City
Standard Supply Company
225 East 6th Street

VIRGINIA

Norfolk
Priest Electronics, Inc.
6431 Tidewater Drive
WASHINGTON
Mt. Vernon
Skegitt Whalomco Electronics
620 West Division Street
Seattle
Robert Fraze Company
2211 Fifth Avenue
Tacoma
Wible Electronics
3723 South Lawrence
WISCONSIN
Fond du Lac
Wisconsin Electronic Supply
223 Seymour
Milwaukee
Amateur Electronic Supply
4828 West Fond du Lac Avenue
Racine
United Radio Parts Company
1244 State Street

Circle 16 on reader service card

www.americanradiohistory.com



As you can see, your Sylvania distributor has 200 picture tubes in stock.

And they're all in just five Sylvania cartons.

Because our line of five color bright 85XR® OEM-quality tubes gives maximum coverage of 19V, 21V, and 25V diagonal sets with a minimum of stock.*

It also means faster service because these Sylvania picture tubes are direct replacements. You replace a kimcode with a kimcode, a bonded with a bonded.

And then, there is the biggest advantage of all: You can count all your large-screen color tube needs on the fingers of one hand.

See your local GTE Sylvania distributor for a complete replacement list. With needs that you

can count on one hand, you can bet he has the tube you want in his hands.

Sylvania Electronic Components, 100 First Ave., Waltham, Mass. 02154.

*XR23VANP22/

SRE25BGP22 Replaces 53 types

XR23VAQP22/

SRE25BHP22 Replaces 27 types

XR19VABP22 Replaces 22 types

XR18VAHP22 Replaces 82 types

XR18VADP22 Replaces 16 types

GTE SYLVANIA



On-Guard Security Center

EiCC Fail Safe Security




by GEORGE F. DURYEY*

THE BURGLAR ALARM IS, UNFORTUNATELY, rapidly becoming a necessity of modern living. But the chore of selecting a unit is staggering. There are so many different types available that it is just about impossible for anyone not knowledgeable in this field to make a sensible choice.


This article describes the many categories of alarm devices, it also explains how they work, where they work best and what their drawbacks can be.

The sooner you catch—or better, deter—a thief, the safer you are. The best way to do this is with perimeter protection—installing detectors on exterior doors, windows, gates, fences and sometimes walls and ceilings. Businesses, schools and the like which are closed at night with no

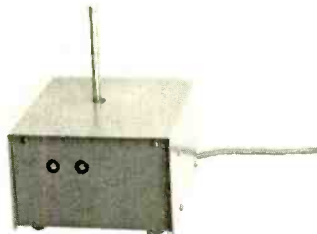*Director, Security Systems Management School, 1500 Cardinal Drive, Little Falls, N.J.




Mountain West Space Switch

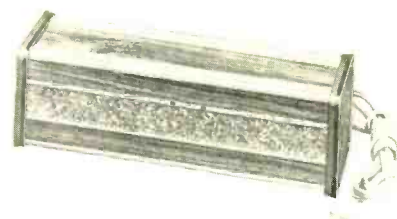

Delta Products DeltAlert

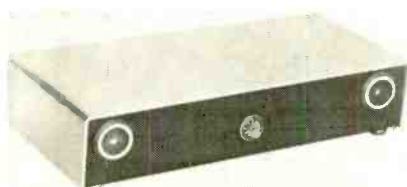how to pick the **“RIGHT”** security system



Alarm Device Motion Detector



Detectron Doppler Detectors



Crismar Challenger System

There are many ways of stopping a burglar. Use the one that offers you the best protection

watchman require this type of protection. Conversely, businesses that are open 24 hours or areas where people may wander with no intent or temptation to steal, have little use for such protection.

Perimeter protection is confined to the entry points of an area and is, therefore, ineffective against “stay-behinds,” burglars who enter legitimately during business hours and hide somewhere until the place is closed. By the time they trip a perimeter alarm, they have already done their dirty work and are on their way out.

Space or specific-area protection

This is a fast-growing segment of the security field. The equipment used here detects the presence or movement of an intruder in a certain defined area. This type of protection is often used as a back-up for a perimeter system in particularly sensitive areas which need extra protection. It is an excellent defense against the “stay-behind”

and is often used where perimeter protection is impractical.

Space alarms usually operate by filling a certain area with sound or radio waves. When these waves are disturbed by movement within the protected “space,” the alarm is set off.

Spot or point protection

A spot protection device confines itself to one or more specific objects such as a safe, file cabinet, or jewelry case. The alarm system is set into operation whenever anyone touches—or in some cases comes close to—the protected object. This type of protection is usually used in conjunction with other types, since the object it is protecting is ordinarily very valuable. At night, the point protection backs up a perimeter system, and during the day it can still be used to warn when someone is too close to the area containing the valuables. You might consider it an “extra guard.”

Perimeter protection equipment

This section will describe in some detail those electronic security devices which are best suited for *perimeter* or *point-of-entry* protection. Perimeter protection, once again, refers to the type of protection which is intended to deter a burglar from entering the premises. By one method or another, it erects an electronic "wall" around the protected premises. Perimeter protection covers only points of entry. If and when the thief gets beyond that point, he is safe, so the equipment should be used in conjunction with other types of protection—space and/or spot—where valuable property is to be safeguarded.

The types of equipment described here are also referred to as "premise" or "intrusion" alarms.

Electro-mechanical alarms

This is probably the most common form of electronic security protection and, although its chief flaw is that it is rather easily compromised by a knowledgeable thief, its advantages should not be underestimated. The system is readily visible to a prospective burglar, and this is a double-edged sword. It warns the professional and allows him to use his skill to overcome it, but the same visibility may be just the thing to scare off amateurs and vandals.

The equipment consists of a closed electric circuit around the area to be protected. Doors, windows, transoms, skylights, etc. are wired with metallic tapes, switches, contact devices, screens and other electrical equipment which will set off an alarm when an intruder breaks the circuit.

Actually, this type of protection can be expanded to more than point-of-entry protection. Pressure-sensitive doormats, for example, can be placed in front of valuable objects such as safes or paintings. These will also break the circuit if stepped on by a thief, setting off the alarm. A burglar may have skillfully cut a window around the metallic foil tape, crossed wires to nullify the system, then step on a doormat and set off the alarm anyway.

Another variation of the electro-mechanical alarm is a simple taut wire stretched around the protected area. So small it is nearly invisible, the wire is connected to a snap-action switch which is activated whenever the tension is either too tight or too loose. Thus, the alarm is sounded whenever some intruder either brushes against it or cuts it. Since such a setup is subject to false alarms because of expansion and contraction due to weather, commercial units are available which automatically compensate for temperature changes.

Photoelectric detectors

A simple photoelectric cell, or electric eye, is a device that is ordinarily used with other forms of alarm equipment. Normally, a light beam is focused on a photocell which in turn generates a small voltage that is amplified and used to supply power to an alarm circuit. When the electric beam is shining on the light-sensitive receiver, the alarm contacts are held open. As soon as an object or intruder intercepts the light beam, the photo-cell goes dark and the output voltage drops. The drop in voltage de-energizes the circuit and the alarm contacts close.

The limitations of this simple equipment are easily recognized. If something happens to the power source—a power failure, for example—the system is dead. This can be overcome by having a separate battery for the alarm circuit, which will "fail-safe" or sound the alarm if something happens to the light.

Even more serious is the visibility of an ordinary light beam. The burglar can easily detect it and slide under it. Or he can use a flashlight beam to "fool" the photocell.



PHOTOELECTRIC ALARM system has range of up to 1000 feet. Made by Ademco.

More advanced systems use infrared or ultraviolet light, which is not visible to the naked eye. Some of these installations may still have a faint red glow which can be detected by the burglar and compromised by a flashlight beam.

The best photoelectric equipment forestalls even this possibility by introducing a pulsating beam which must correspond with the receiver. If the synchronized beam is interrupted or a different source of light introduced, the alarm will sound.

By its nature, a light beam will travel only in a straight line. This makes the equipment well suited for protecting open spaces and similar areas, while at the same time making it unsatisfactory for many-angled, winding or curved perimeters.

To more effectively use photoelectric equipment, mirrors are often used to deflect the light beam in different directions. With enough mirrors and strong enough beams, an entire area can be crisscrossed with one or more beams of light, providing space as well as perimeter protection.

One of the main advantages of this type of equipment is its capability to cover open portals, aircraft runways, driveways and other exterior applications where physical obstructions would be dangerous.

On the minus side, the light beams are narrow and can be detected and avoided by the observant intruder. When the equipment is used outdoors, it is susceptible to damage, misalignment and being compromised by dust, smoke, fog, snow or soot. Also, only straight lines (or mirrored angles) are possible. On a curved building, this equipment is usually impractical.


Space-protection gear

Perhaps the greatest advances in elec-

tronic security have taken place in the field of *space protection*. Virtually unknown a few decades ago, this type of equipment has proliferated within the past few years.

Space protection is, in fact, an excellent compromise, offsetting the disadvantages of both spot and perimeter protection. It is an even better tool used as a supplement to one or both other systems (perimeter and spot). Space protection can concentrate on an *area* which is likely to be attacked. Not only is the edge (or perimeter) of the area protected, but any movement whatever inside the specific area is detected by space protectors.

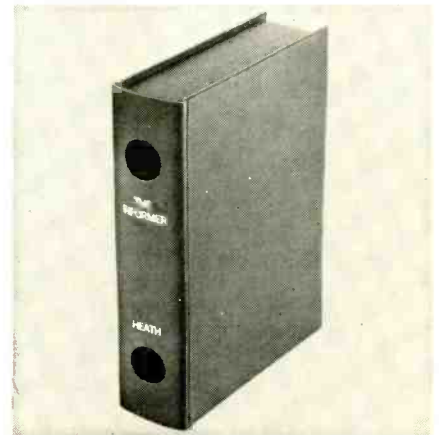One obvious advantage of this type of equipment is its defense against "stay-behinds." As soon as the stay-behind moves out of hiding, his presence sets off an alarm. If an intruder should get beyond a perimeter alarm, he is unlikely to escape the space alarm.




ULTRASONIC INTRUSION SENSOR by Heathkit looks just like a book.

Space alarms are easy to hide, or to disguise as some other object. They can be made to look like books, stereo speakers, etc.

Ultrasonic equipment

"Ultrasonic" is a slight misnomer, since the word means "beyond sound" and high frequency sound waves which are generated are just within the upper limits of the audible spectrum. For all practical purposes, however the sound is inaudible to the human ear, so the term is used.

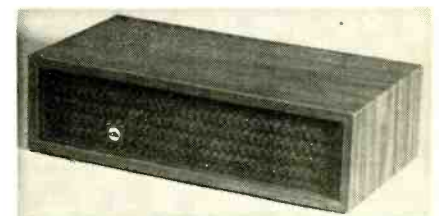Ultrasonic equipment is designed to protect an enclosed area. It operates by generating a chain of high frequency sound waves which fill the protected area with a continuous pattern. A sensitive receiver,



ULTRASONIC INTRUSION DETECTOR is a Doppler-type unit made by Detection Systems.

connected to an electronic amplifier, picks up the waves. If they are of the same frequency as the sound emitted by the transmitter, the system is neutral.

But any motion which comes from

within the protected area will send back a reflected wave of a different frequency than that generated by the transmitter. This change in frequency will be picked up and amplified in the control unit, setting off the alarm.


Some of the advantages of ultrasonic alarms are their comparative invisibility—devices are easy to hide or disguise as something else—and the excellent protection against all types of intruders, including the elusive “stay-behind.” Ultrasonic alarms are quite flexible, and the protective pattern can be altered to suit the shape of the room. The equipment can be moved when required—in many cases it may simply be picked up and carried to another location. The devices may also be used to detect fire, which can result in large savings by eliminating the need for special additional fire-detection equipment.

Although ultrasonic equipment is generally very good for area protection, it has its drawbacks—like all other devices. For one thing, if an intruder suspects that an ultrasonic detector is present, he can take extremely slow steps—about one per second—and not be picked up by the alarm. The device is also sensitive to loud noises from outside sources or building vibrations. Either of these may trigger the alarm unnecessarily. A furrier's vault or other high sound-absorbing area cannot use this equipment because the waves are “soaked up” by the clothing. A thief who is aware of the presence of an ultrasonic detector can penetrate a wall behind a large object (which would deflect the sound waves).

Audio space equipment

A simple audio system may be thought of as just the opposite of an ultrasonic installation. Whereas the ultrasonic transmitter fills a room with sound waves, the audio space device only “listens” for sound. It reacts to *any* sound and is neutral only when the room is comparatively soundless.

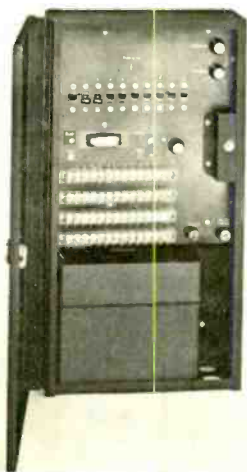An analogy can be drawn with a swimming pool full of water. In an ultrasonic system, the water would represent the ultrasonic waves. If the water were disturbed by a swimmer, an alarm would sound. A pool protected by an audio system, on the other hand, would be completely dry. The only time an alarm would sound would be when a drop of water was added to the empty pool.



SOUND DISCRIMINATOR type of intrusion detector made by Scientific Security Systems.

Unlike ultrasonic equipment, audio detectors are not disturbed by movement of air or other types of motion. What sets off an audio alarm is noise, so where loud machinery, fans or other noise-producers are a problem, audio equipment is probably not the best choice. There are, however, “cancellation” microphones available which are able to nullify specific noises.

These systems are extremely sensitive and can be programmed to pick up the sound of a dropped pin. Unfortunately, such delicate sensitivity will result in many nuisance alarms with most installations.

There are several additional limitations to audio devices. They cannot, for example, be used around heavy equipment or noisy machinery. Nor should they be used in a room with heavy drapes and carpeting which will muffle sounds.

Simple audio equipment can be put to very good use in a building which has a proprietary system. A guard who is monitoring the system can turn up the receiver and listen carefully to whatever sound comes over the wires. The guard should be able to differentiate between machine noise, wind rattling a window, and other natural sounds, and the intrusive sounds of someone attempting to burglarize the building.

There are also filters which can be used to allow an alarm to discriminate between sound that is “okay” and sound which signals intrusion. Dual microphone setups can also “cancel” sound coming from an exterior source such as a passing truck. If the noise on the outside microphone is louder than the one inside, the alarm is not sounded.

Simple audio systems are best suited for large areas and can use sound equipment (such as intercoms) which has already been installed.



MICROWAVE RADAR detection system operates in 400-MHz range. It's made by DBX Inc.

On the minus side is the fact that no perimeter protection is provided, nor can the equipment be used where sound-absorbing materials inhibit its effectiveness. Unless expensive cancellation microphones are used to drown out noise, the equipment may be too sensitive to ordinary noises to be of much benefit.


Radar equipment

This class of equipment is very similar to the ultrasonic. Ultrasonic waves depend on movement within an area filled with high frequency *sound* waves. Radar equip-

ment picks up movement in an area filled with high-frequency *radio* waves. In each, the movement of an object is reflected and causes a disturbance in the normal wave motion. Picture the swimming pool again—filled this time—and a swimmer diving into the water causing a series of waves.



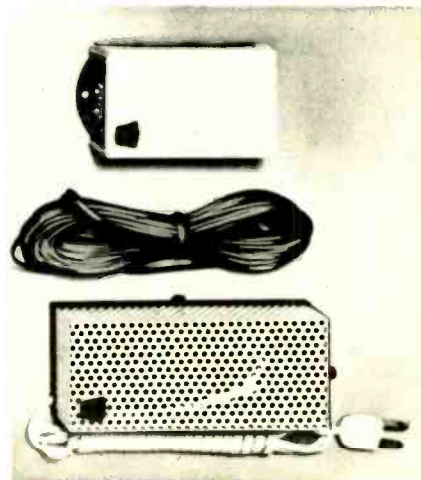HOME PROTECTION SYSTEM for do-it-yourselfers is made by EICO.





ADD A SMOKE DETECTOR like this one from Edmund Scientific for wider protection.

At the present time, radar-type equipment is in a state of flux. Although its potential is great, there are many problems and the solutions have not been entirely successful. The principal problem is that the radio waves cannot be contained within a specified area as well as ultrasonic waves. Radio waves travel easily through most materials, and the alarm can be tripped by a person walking by the window of a protected area.

Expert planning is vital for a successful installation. Properly engineered and maintained, this type of equipment can be top-flight. Poorly planned, it will lead to numerous false alarms and/or will be very easy to compromise.

Although these high-frequency radio waves are highly penetrating and will go through most materials, they bounce off metal objects. The location of radar antennas is of primary importance. Unless they are properly positioned, intruders could crawl behind a row of file cabinets, metal desks, etc., and their presence would not be picked up by the equipment. For the same reason, objects such as moving metal fans will set off nuisance alarms unless they are covered by metal screens. Elevators are another problem, but the equip-

(continued on page 98)

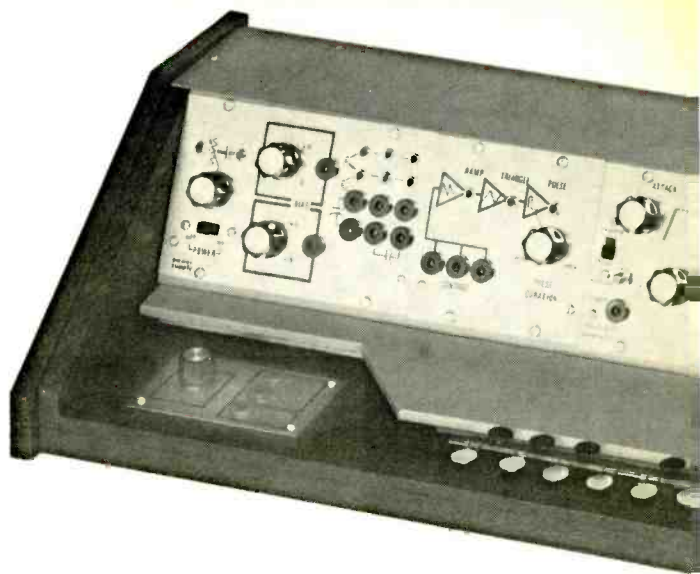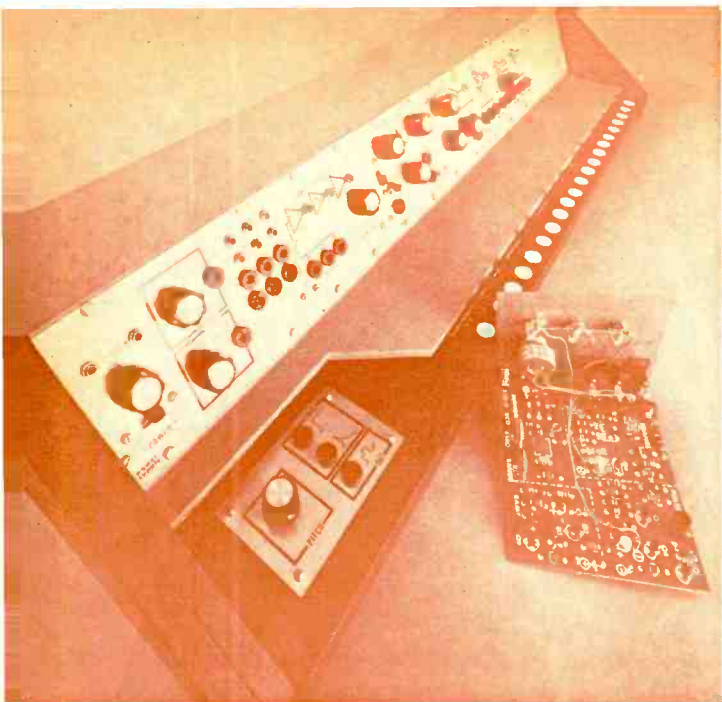

BUILD A MODULAR ELECTRONIC

*Developing music by synthesizing the tones electron-
Now it can be yours. This synthesizer is simple,*

THERE IS NOT MUCH DOUBT THAT ELECTRONIC music synthesizers are the favorite toys of the music industry; hardly a record or TV commercial is produced these days without some sort of synthesizer "gimmick." Yet despite the ubiquitous nature of these devices (or perhaps because of it) there is no other collection of electronic equipment so thoroughly misunderstood not only by the layman but by a great many musicians as well.

This article will help clear the fog surrounding electronic music by going beyond the "How They Work" material that has appeared in the past. Here we will present full details of the construction of a fully compatible set of voltage-controlled synthesizer modules.

The synthesizer that is described here has been specifically designed for construction by the electronics experimenter. While some compromises have been made in the interest of improving the price/performance ratio of professionally available equipment, you will find that the equipment described is in most ways a little brother to the studio gear selling for ten times the price. There is a power supply, voltage-controlled oscillator and controller, voltage-controlled amplifier, two voltage-controlled filters, a function (envelope) generator and control oscillator/noise source. When the first three modules are completed you will have a playable, though limited, instrument.

Power supply

As you can tell from the photographs, the power supply does a little more than just act as a source of voltage for the rest of the modules. It also includes a patch

panel, attenuator and two sources of bias voltage that will be used to set constant filter or amplifier parameters.

The schematic for the power supply is in Fig. 1. The actual power supply portion of the circuit consists of two separate full-wave rectifiers. One section (T1, D1-D4, C1, C2) provides the +18 and +9-volt supplies while the other (T2, D5, D6, C3) supplies the -9-volt side. Regulation is not included because the only module that requires a regulated supply (the VCO) has on-board regulation.

The series string of R2, R3 and potentiometer R5 provides a front panel voltage source that is variable from -5 to +5 volts while the combination of R1 and potentiometer R4 supplies a variable 0 to 5 volt source.

With the exception of the "conditional" jumpers between rows of jacks the patch panel is a straight-forward design. Referring to the schematic again we see that the switch contacts of the miniature phone jacks are arranged so that when a plug is inserted into J1 it isolates the top row of jacks from all jacks below it. Similarly, a plug inserted in J4 isolates the second row of jacks from the pin jacks below it (but not from the top row). Two sets of capacitor isolated jacks are provided at J11, J14 and J12, J13. The purpose of these jacks will become clear in a later article on using the synthesizer.

Potentiometer R6 provides a variable attenuator that can be used as a master volume control or in mixing applications.

Put it together

There is nothing at all critical in the power supply circuit and any construction

method may be used, but an etched circuit board is desirable in the interest of ease of assembly and professional appearance. The foil pattern is in Fig. 2. Circuit boards may either be etched at home or purchased from the source mentioned in the parts list.

Assembly should begin with mounting the parts on the circuit board. Form and install the two wire jumpers, then the resistors, capacitors and diodes. Bolt the two transformers and the fuse holder to the circuit board with 4-40 hardware. When they are properly installed, the transformers will be "back to back" with the primary windings facing each other (see Fig. 3).



Connect the solder lugs of the fuseholder to the circuit board with short pieces of bare wire, and before putting the circuit board aside solder in place lengths of No. 22 wire to points A through F on the circuit board. Be sure to make these wires long enough to reach from the circuit board to the front panel when the two are bolted together.

From the front panel from any flat material such as aluminum, steel or even scrap copper-clad and drill or punch the required holes before painting the panel and applying markings as desired. Install the pots, jacks and switch S1 as shown in the photos and wire the front panel before fastening the circuit board to the front panel using small "L" brackets and 4-40 hardware. Note that capacitors C4, C5 and C6 are wired in place on the front panel.

Make the final connections from the front panel controls to the circuit board and solder the line cord into the circuit board points marked ac Snap a ½-amp fuse into the fuse holder and fasten the knobs to the potentiometer shafts.

* President, PAIA Electronics

COVER STORY

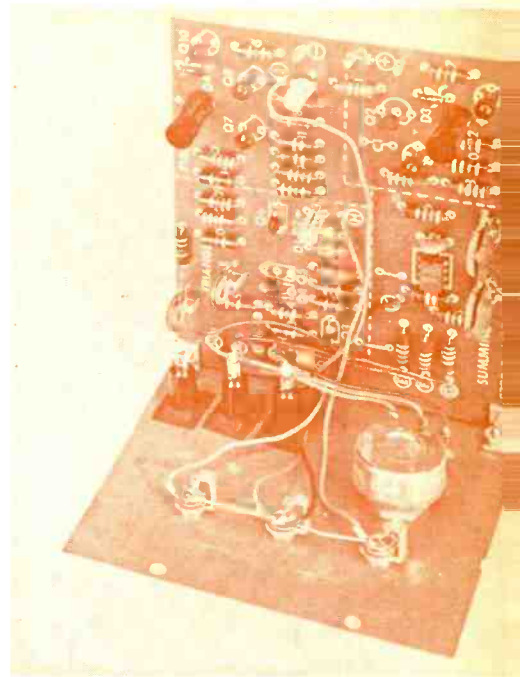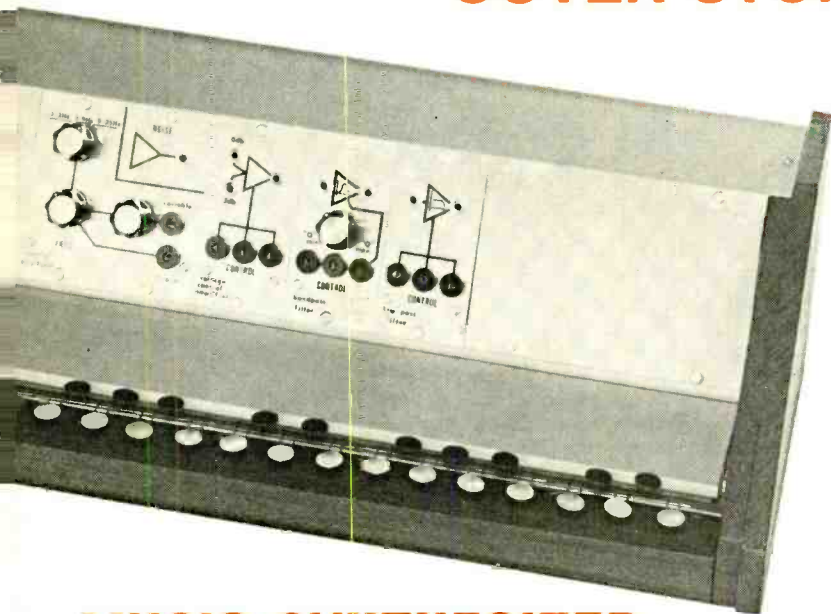

MUSIC SYNTHESIZER

by JOHN S. SIMONTON, JR.*

ically is not new but has just started gaining momentum.
inexpensive and designed for the experimenter.

Testing your work

There is really not much to test on the power supply, plug it in and use a vom to make sure that there is 18 volts between the ground and “+” points on the circuit board. Similarly check the “+” point for 9 volts to ground. Reverse the vom leads and check for -9 volts, between “-” and ground. Check the voltage output of the 0 to 5-volt and -5 to +5-volt bias supplies as the controls are rotated (all of these voltages are $\pm 20\%$). Plug a miniature phone plug into J3 and check continuity between the hot side of this jack and all the other phone jacks in the group as well as the top row of pin jacks. Plug a phone plug into J1 and observe that it isolates the top row of phone jacks from the rest of the jacks. Test the switching on the second row of jacks to make sure that it isolated J4 through J6 from the row of pin jacks directly below it but not from J1 through J3.

Voltage-controlled oscillator

Unlike electronic organs—which for the most part generate a specific sound by adding together sine waves of the desired frequency, magnitude and phase—synthesizers employ “formant synthesis” in which a desired signal is formed by dropping out selected frequencies in a harmonic rich waveform.

Our VCO generates three waveforms that are particularly rich in harmonics; ramp, triangle and variable duration pulse. Frequency range of the oscillator is almost 6 octaves from 40 Hz to 2500 Hz, in a single voltage controllable range and the frequency of the oscillator is directly proportional to the sum of the voltages at three control voltage inputs. The implica-

tions of voltage control will be fully covered in another article, but for now it will suffice to say that without it you don't have a synthesizer, you have an organ.

How the VCO works

In a synthesizer the VCO is the one module that doesn't offer many design compromises. The human ear is more sensitive to variations in pitch than to any other musical parameter so even small amounts of drift and shift are objectionable.

As can be seen in Fig. 4, two precautions keep VCO drift to a minimum. First, power supply regulation is directly on the circuit board (Zener diodes D3 and D4 plus series-pass transistors Q9 and Q10). Second, control voltage is summed by the active network built around IC1.

The ramp portion of the VCO is a standard configuration consisting of a UJT relaxation oscillator (Q2, C1). The capacitor is charged by constant current source Q1. The output of the op-amp summing network is scaled by setting the gain (R7, RANGE) and offset (R4, ZERO) of the amplifier and is used to set the amount of current delivered by the current source.

The voltage ramp that appears across capacitor C1 is isolated by emitter follower Q3 and appears at the front panel jack as the ramp output. The ramp is also used to generate the other two waveforms.




The triangle waveform is shaped by the differential pair Q4 and Q5. The voltage at the collector of Q5 is in phase with the input ramp and the voltage at the collector of Q4 is 180° out of phase (inverted from the input). Diodes D1 and D2 “select” the higher of these two collector voltages and apply it to the base of emitter fol-

lower Q6. During the lower half of the input ramp, Q4's collector voltage is higher because of the phase inversion and that section of the ramp is presented in an inverted form to the base of Q6. During the second half of the ramp the collector of Q5 is higher and this portion of the ramp is applied to the base of Q6 without an inversion. The net result is a triangular wave from the emitter of Q6. Trimmer potentiometer R19 is used to balance the gains of the transistors so that the last of the wave from Q5 and the first of the wave from Q4 occur at the same dc level.

A variable-duration pulse output is derived from the ramp by applying it to the input of the Schmitt trigger (Q7 and Q8). At some point on the ramp the triggering threshold of the circuit is exceeded and the output changes from some low voltage to almost positive supply and stays in that condition until the ramp re-sets. By using R25 to vary the amplitude of the ramp, the pulse duration, as a percentage or the total period can be varied. As the amplitude is increased the duration of the pulse is also increased. Trimmer R26 provides a fine adjustment of the ramp amplitude and is set so that when the pulse duration control is fully counter-clockwise the narrowest possible pulse is produced.

Build the VCO

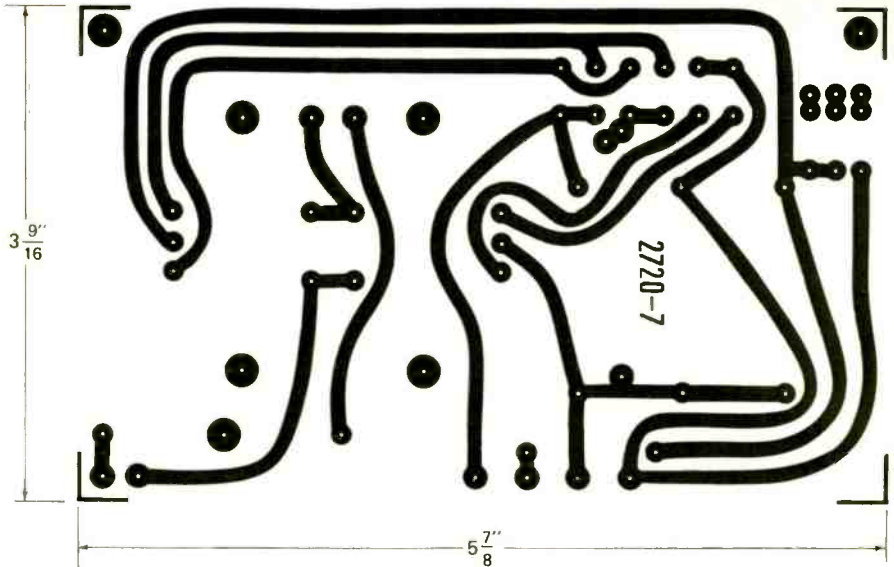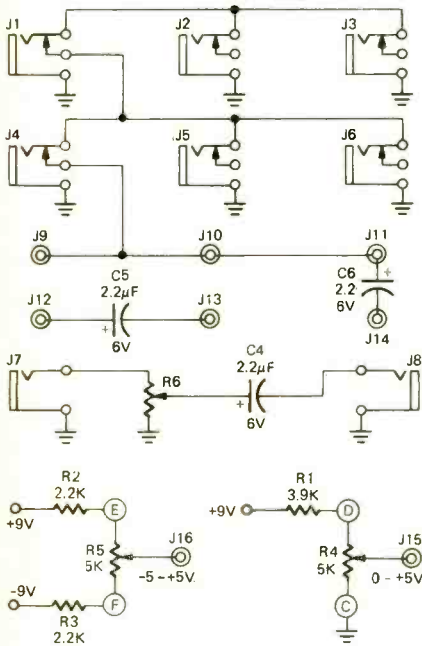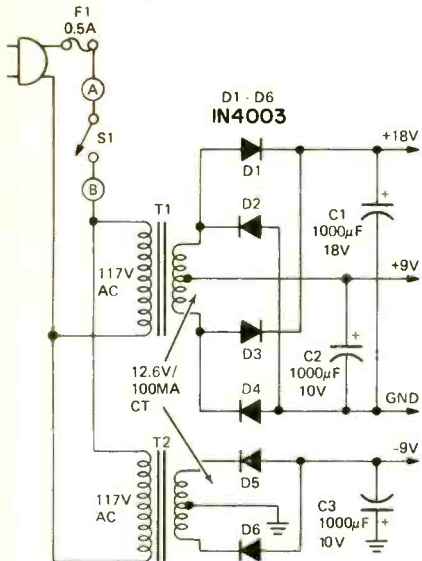The VCO circuit can be assembled using any common construction technique, but an etched circuit board (Fig. 5) is recommended. Figure 6 shows parts placement on the circuit board. When all components have been mounted, solder wires to points A through K. Make sure they are long enough to reach from the board to the



**PARTS LIST
(Power Supply)**

- C1—1000-µF 18V electrolytic
 - C2, C3—1000-µF 10V electrolytic
 - C4, C5, C6—2.2-µF, 6V electrolytic
 - D1 thru D6—1N4003
 - F1—0.5-amp fuse
 - R1—3900 ohms ½W 10%
 - R2, R3—2200 ohms, ½W, 10%
 - R4, R5, R6—5000 ohms linear taper potentiometer
 - S1—spsst slide switch
 - T1, T2—12.6V 100 MA C.T. transformer
- MISC:** Fuse holder, line cord, (8) miniature phone jacks, (8) tip jacks, (3) knobs, hardware, wire, solder, circuit board, etc.
- The following items are available from, PAIA Electronics, Inc., P.O. Box 14359, Okla. City, OK 73114

No. 2720-7—Complete kit of parts for duplicating the prototype shown including circuit board and front panel. \$22.00 plus postage for 2 lb. and insurance.

No. 2720-7pc—Circuit board only \$4.00 postpaid.

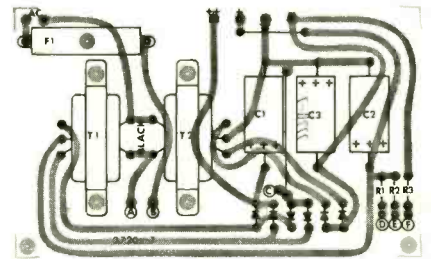


FIG. 1—(far left) COMPLETE SCHEMATIC of the power supply. FIG. 2—(top of page) FOIL PATTERN for the power supply circuit board. FIG. 3—(above) PARTS PLACEMENT on the board.

front panel controls and jacks (notice that there is no point I).

Form the front panel in the same manner as for the power supply and finish and label it before installing R25 and the input and output jacks.

Fasten the circuit board to the front panel using 4-40 screws and small "L" brackets and make the final connections between the circuit board and front panel.

Calibration and testing

Apply power to the rear connections of the circuit board; +9 volts to "+", ground to ground and -9 volts to "-". The VCO pulls a hefty 25 mA because of the regulation, so batteries are not acceptable. Give the unit about 30 minutes to stabilize before calibration.

The primary adjustment sets up the summing network so the oscillator produces a specified output frequency for a given input control voltage. This can be done using either an audio signal generator or a tuned musical instrument as the pitch reference.

If you decide to use the signal generator method, the oscillator will be tuned us-

ing Lissajous figures. Connect the output of a test oscillator set to 260 Hz to the horizontal input of an oscilloscope and the triangle output of the VCO to the vertical input. Apply power to the VCO and jumper the 0 to 5-volt bias output of the power supply to the left hand control voltage input jack. (The input summing resistors can not be trimmed so unless matched resistors are used only one of the three inputs can be precisely calibrated.) Monitor this control voltage with a vom set to 2.5 or 5 volts dc full scale. Adjust the bias output for 0.625 volts as indicated by the vom (errors caused by inaccuracies in the vom movement will cancel when the keyboard is calibrated to the VCO.) Use VCO ZERO trimmer R4 to produce a Lissajous figure on the scope that indicates that the frequency of the signal generator is exactly twice the frequency of the VCO. Do not be overly concerned with a slow rotation of the pattern at this point.

Adjust the bias supply until the scope shows the sideways 8 pattern that indicates that the output of the signal generator is half the frequency of the VCO. Read the vom. If the reading is Less than 2.5 volts, rotate RANGE trimmer R7 about 1/10 of a turn clockwise. If the reading is

greater than 2.5 volts, rotate the trimmer about 1/10 of a turn counter-clockwise. Reset the bias output for 0.625 volts on the vom and once again adjust the "zero" trimmer to produce the Lissajous figure.

Repeat the previous adjustment for the sideways 8 pattern and adjust the RANGE trimmer accordingly. After several passes through this procedure the vom should read exactly 2.5 volts when the Lissajous pattern indicates that the frequency of the VCO is twice that of the signal generator. At this point summing network calibration is complete.

A second method for calibrating the VCO is approximately the same as the first except that the ramp output is jumpered to the high level input of a hi-fi or musical instrument amplifier and the tone is "zero beat" against the C below middle C for an input voltage of 0.0625 volts; and C above middle C for an input of 2.5 volts. The same technique of successive approximations that was used with the signal generator still applies with the ZERO adjusted for zero beat with C below middle C with a control voltage of 0.625 volts. The bias supply is then adjusted so the oscillator is zero beat with C above middle C and if the vom reads more than 2.5 volts the "range" control is rotated 1/10 turn counter-clockwise. Go back and forth through these two steps until the vom reads exactly 2.5 volts when the VCO is zero beat with C above middle C.

When the linearity of the summing network has been calibrated you can set the

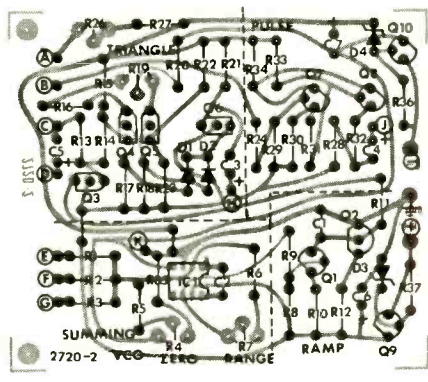
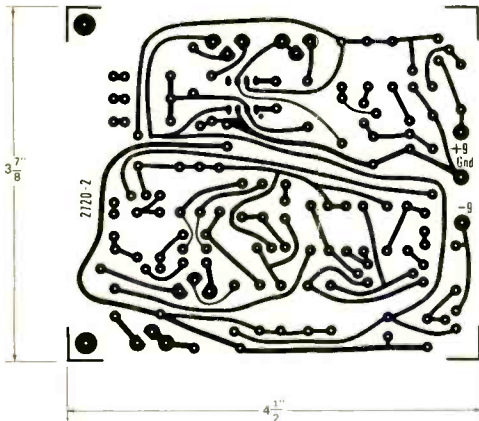
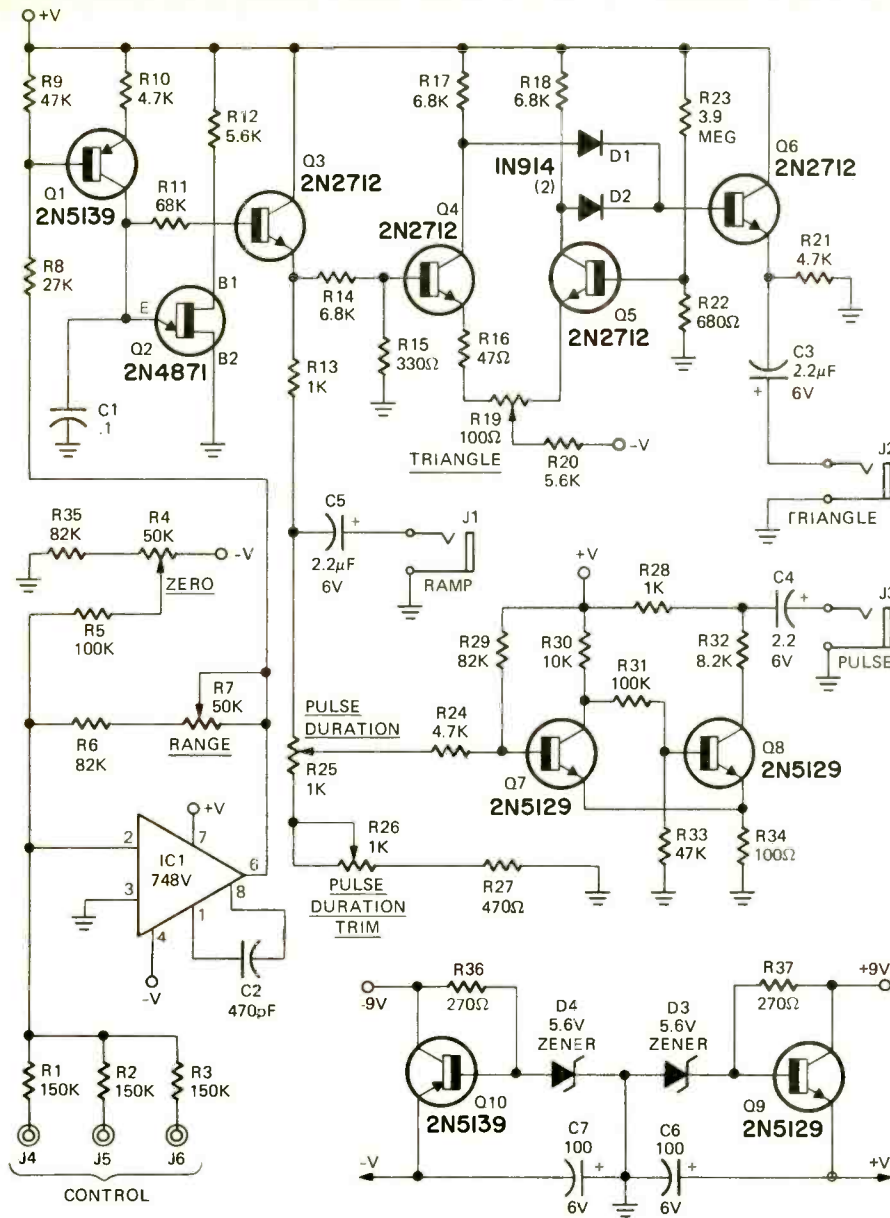


FIG. 4—(top) SCHEMATIC of the voltage-controlled oscillator. FIG. 5—(above left) FOIL PATTERN for the VCO. FIG. 6—(above right) PARTS PLACEMENT on the VCO board.

spectral purity of the triangle wave. If only an amplifier is available this adjustment can be made by jumpering the triangle output to the input of the amplifier and adjusting TRIANGLE trimmer R19 for the mellowest sound. If a scope is available you can look at the triangle output and adjust R19 so the two sides of the triangle meet at the top of the waveform.

The PULSE DURATION trimmer can also be adjusted using either an amplifier or an oscilloscope. If a scope is used rotate PULSE DURATION control R25 fully counterclockwise and adjust internal trimmer R26 so that the narrowest possible pulse appears on the screen. If an amplifier is used, adjust the trimmer so you can just barely hear the buzz of the pulse.

PARTS LIST (Controller Electronics)

- C1, C7—.01- μ F disc
 - C2—.001- μ F disc
 - C3, C11—2.2- μ F 6V electrolytic
 - C4—100-pF disc
 - C5, C6—.1- μ F mylar
 - C8, C9, C10—33- μ F 6V electrolytic
 - D1 thru D5—1N914
 - IC1, IC2—748 op-amp
 - Q1, Q6—2N5139
 - Q2, Q5—2N5129
 - Q3, Q4—MPF-102
 - All resistors— $\frac{1}{2}$ W 10%
 - R1—470 ohms
 - R2—10,000 ohms
 - R3, R17, R18, R19—680 ohms
 - R4—15,000 ohms
 - R5—100,000 ohms
 - R6—68,000 ohms
 - R7—82,000 ohms
 - R8—1 megohm
 - R9, R16, R22—3.9 megohms
 - R10—150,000 ohms
 - R11—22,000 ohms
 - R12—4700 ohms
 - R13—6800 ohms
 - R14, R15—33,000 ohms
 - R20—linear taper potentiometer, 1000 ohms
 - R21—1K pc mounting trimmer pot, 1000 ohms
 - MISC: Case, circuit board, hardware, control panel, wire, solder, etc.
- The following items are available from, PAIA Electronics, Inc., P.O. Box 14359, Okla. City, OK 73114
- No. 2720-6—Complete kit of all parts for duplicating the prototype shown including case, preformed springs, front panel, circuit board electronics, vinyl strip. \$37.00 plus postage for 12 lbs. and insurance.
 - No. 2720-6pc—Circuit board only. \$3.50 ppd.
 - No. 2720-6v—Pre-cut conductive vinyl strip. \$2.50 ppd.
- A controller kit featuring a professional 3 octave organ keyboard is also available. Details available on request.

That's about all we have room for in this issue. Next month we will present details of the third module for the synthesizer and you can then start using your unit. We would appreciate your comments on the types of additional modules you would like to see for this instrument. We'll pass them on to the author and he may be able to provide them at a later date. See you again next month.

R-E

KIT SUMMARY

- No. 2720—Kit of all parts for duplicating the complete synthesizer. Includes all parts, panels, circuit boards and detailed instructions. \$139.00 plus postage for 18 lbs and insurance
 - No. 2720-2—VCO kit including circuit board. \$24.95 ppd.
 - No. 2720-2pc—VCO circuit board only. \$4.00 ppd
 - No. 2720-6—Controller/case kit. \$37.00 + 18 lbs. postage
 - No. 2720-6pc—Sample/Hold circuit board. \$3.50 ppd.
 - No. 2720-7—Power Supply kit. \$22.00 + 2 lbs. postage
 - No. 2720-7pc—Power Supply circuit board. \$4.00 ppd.
- A controller kit featuring a professional 3 octave organ keyboard is also available. Details available on request.



HEATH'S DIGITAL FM TUNER

The Heathkit AJ-1510 FM receiver is one of the world's most sophisticated and surely the most advanced consumer model. Take a look at how it works

by DAVID M. THOMAS*

VARIABLE-CAPACITANCE DIODES, DIGITAL tuning, programmable dividers, phase-locked loops, digital discriminator and frequency synthesizer are all terms that define established engineering techniques. New and exciting is the "Where and How" these are used. Ways of applying these techniques in commercial AM and FM receivers has long been talked about, but until recently was economically prohibitive for consumer oriented products. MSI and LSI (medium and large scale integration) technology has developed to such an extent in the last few years that these sophisticated sounding terms are now appearing in the consumer market.

The Heathkit AJ-1510 FM/FM Stereo Digital Tuner is a state-of-the-art design that uses the purest digital philosophies consistent with consumer products. Some of the tuner's special features include a sophisticated digital frequency synthesizer employing a phase-locked loop to achieve channel accuracy of better than 0.005%, an inductorless digital frequency discriminator, the very latest phase-locked multiplex demodulator, a pre-assembled varactor FM rf tuning unit (front end), and a four-digit, seven-segment channel-frequency readout (instead of a scale and pointer).

Also high on this list of special features are the three different modes of tuning. First, an exclusive keyboard where the user taps out the three or four-digit frequency of the FM station desired. Second, sweep/scan tuning

which at the touch of a button, scans the entire FM spectrum at an adjustable rate, stopping at stereo only stations or at all stations with the quality of signal chosen by the listener through adjustable noise and agc controls. Third, preprogrammed card memory tuning.

A single front-panel meter indicates relative rf signal strength and with the flip of a switch it becomes a multipath indicator. There is no center channel "tweaking" since the frequency synthesizer sets it "right on."

Last, but by no means least, is the computer-like performance of the squelch control circuitry which eliminates any stations with noise levels above a presettable level. In addition, should a fault occur within the tuner prohibiting proper phase-locking, the squelch circuitry will lock out the audio and a fault indicator will light.

Most of the 55 integrated circuits, in addition to the more than 50 discrete transistors and 50 signal diodes, are mounted on ten computer-type printed circuit boards. Seven of these boards conveniently plug into a master board in modular form. Edgeboard connectors and cable connectors are used throughout, which means that circuit boards can be removed without having to unsolder or unwire a single connection. A system block diagram is shown in Fig. 1.

FM varicap tuner

The FM front-end is pre-assembled and factory aligned. Field-effect transistors (FET's) are used to get both high sensitivity and low

cross-modulation with no overload on strong-signal local stations. The familiar mechanically ganged, variable capacitor has been replaced by Varicaps (voltage-variable-capacitance diodes) in each stage to provide complete electronic tuning. The dc tuning voltage is fed to the tuner from the loop filter output of the synthesizer which is discussed later.

An important note is the *extra* output from this particular tuner; the VCO (voltage-controlled oscillator) buffer output. A sample of the tuner VCO signal is extracted by an internal buffer amplifier which provides isolation and an output signal strong enough to drive the ECL gates of the VCO frequency scaler. The frequency range of this signal is 98.8 MHz (88.1 + 10.7) to 118.6 MHz (107.9 + 10.7).

I.F. and FM digital discriminator

Technological advances have finally eliminated all i.f. and discriminator adjustments while delivering near-perfect response characteristics. The 10.7 MHz i.f. circuitry consists of an input rf amplifier and two broadband amplifier-limiters. Together, these three IC's provide more than 120 dB of i.f. gain. Two fixed-tuned five-pole L-C filters separate the three amplifier stages and shape the "ideal" frequency response with true phase linearity.

The conventional L-C frequency discriminator using balanced diodes has been replaced by an inductorless and diodeless digital frequency discriminator of the pulse counting (averaging) type usually found in only the

*Senior Design Engineer, Heath Company, on the AJ-1510 project. Presently Chief Engineer, Heath Ltd., Gloucester, England.

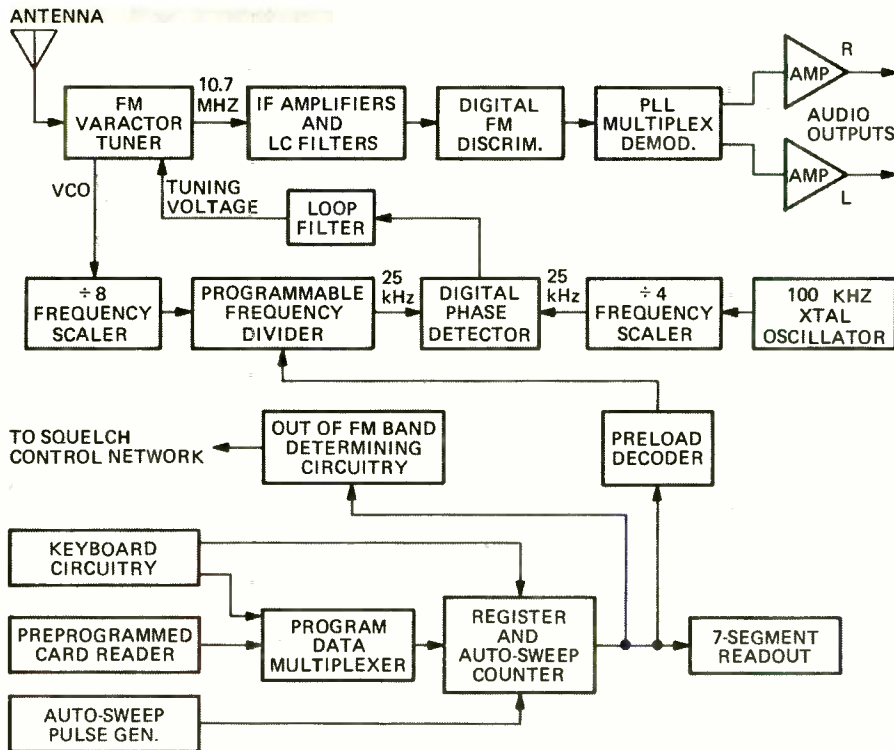


FIG. 1—A BASIC BLOCK DIAGRAM OF THE RECEIVER. Some sections will be broken down into further blocks and basic circuit diagrams as the discussion of the AJ-1510 FM receiver progresses.

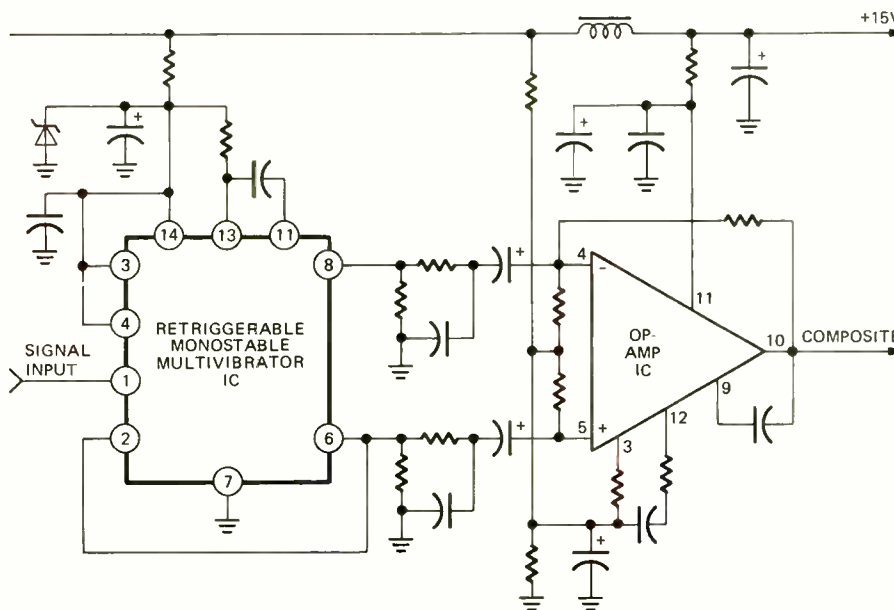


FIG. 2—BASIC CIRCUIT OF THE PULSE-COUNTING FM DETECTOR. Heretofore its use has been restricted to a few experimental receivers using very low i.f.'s.

most exotic instrumentation. This particular digital detector circuit contains two integrated circuits. One of them is a retriggerable monostable multivibrator and the other is an operational amplifier (see Fig. 2).

A signal at the input of the monostable makes it change states for a fixed period of time. The amount of time is determined by the value (time constant) of a simple RC network. However, to guarantee a high degree of pulse-width stability and thus low distortion, the monostable configuration is designed to cycle at half of the

i.f.'s frequency. A digital output pulse, that has constant width and amplitude is obtained at a 5.35-MHz rate. (The FM information is contained in the slight deviations from this rate). The inverse (Q) of this output waveform is also available from the monostable integrated circuit.

Both the Q and \bar{Q} outputs are independently coupled to the inputs of the operational amplifier through simple RC networks. Because these signals are out of phase and applied to the amplifier (+) and (-) inputs, they are added together before they

are amplified. Any in-phase noise appearing at both the (+) and (-) inputs is cancelled. This results in an improved signal-to-noise ratio of the monostable multivibrator. The operational amplifier's output is then fed to the multiplex demodulator circuit.

PLL multiplex demodulator

The very latest state-of-the-art integrated circuit phase-lock loop (PLL) multiplex demodulator is built into the tuner to deliver superior stereo performance while providing long-term circuit and alignment stability (see Fig. 3-a). This multiplex demodulator phase locks to the 19-kHz pilot of the received stereo transmission. Alignment is a simple resistance adjustment as compared to the tediously complex procedures of the past. This single adjustment "peaks" the phase-lock performance for greatest stereo separation and minimum audio distortion.

The PLL IC also has the ability to minimize the ultrasonic components (SCA) that would otherwise appear at the audio output. Previously, elaborate filters were used to do this, but there was a tendency to sacrifice high-frequency audio separation. A prealigned 19-kHz and 38-kHz L-C low-pass filter is used in both the *left* and *right* outputs to remove all unwanted signals above 15 kHz.

Frequency synthesizer

The heart of the tuner is its FREQUENCY SYNTHESIZER which includes the PROGRAMMER, the numeric readouts and an elaborate squelch control system. Each of the functional blocks in Fig. 3-b which make up this synthesizer will be discussed individually. Here we go.

Reference oscillator

Two circuits make up the reference oscillator; a 100-kHz crystal oscillator and a reference scaler (+4). The oscillator section uses a highly accurate ($\pm 0.005\%$) 100-kHz series fundamental crystal and the four gates of a quad 2-input NAND IC. Discrete resistors bias the gates near their switching threshold for reliable self-starting, and discrete capacitors provide proper capacitive loading of the crystal to insure good frequency stability. This circuit provides a highly accurate 100-kHz square wave, or a variable trimmer capacitor is not needed to set the frequency.

A dual JK flip-flop IC serves as the reference scaler. The two flip-flops are externally connected in series (+2+2) and divide the 100-kHz reference frequency by four. The resulting 25-kHz signal is used as the reference signal for the digital phase detector.

VCO frequency scaler (+8)

The VCO frequency scaler divides the 98.8 to 118.6-MHz VCO frequency from the front end by eight to provide a 12.350 to 14.825-MHz square wave to the programmable divider circuit. One gate of an ECL (Emitter Coupled Logic) dual OR/NOR gate is used at the input as a buffer amplifier while the other gate is used as a driver to run a high-speed ECL type-D flip-flop, the first divide-by-two circuit. The output of the type-D then drives an ECL integrated circuit containing two J-K flip-flops externally connected in series to form a divide by four (+2+2). The series combination of these three flip-flops provides a scale factor of eight ($VCO \div 2 \div 2 \div 2 = \frac{VCO}{8}$). The output from the final flip-flop is coupled to two

available TTL NAND gates that form an output interface to the programmable divider circuitry.

Programmable frequency divider

The programmable frequency divider divides the frequency from the VCO frequency scaler down to 25 kHz. As the front end is tuned to receive different FM channels, the frequency of its internal VCO also changes since it must remain 10.7 MHz above the received channel frequency. A different divide ratio is required for each channel to get the 25-kHz output signal. A convenient range of operation for the programmable frequency divider is one where for each adjacent channel the divide ratio is changed in steps of one. Refer to Fig. 4 for the following two examples.

Suppose we want to listen to an

FM station broadcasting on 89.3 MHz. The VCO output will be 100.0 MHz ($89.3 + 10.7$) and the VCO scaler output will be 12.50 MHz ($100.0 \div 8$). The divide ratio of the programmable frequency divider will have to be 500 ($12.50 \text{ MHz} \div 500 = 25\text{kHz}$). If we next wish to tune in a station two channels above at 89.7 MHz, the divide ratio of the programmable frequency divider must be changed to 502; ($89.7 + 10.7$) $\div 8 \div 502 = 25$ kHz.

The programmable frequency divider circuit consists of three programmable down counters (decade) and a recycle logic network. When several programmable divider stages are cascaded and a high toggle frequency is required, the terminal count output may be too slow, due to propagation delay, to simultaneously reload all the stages. Thus several counts may be lost. In the AJ-1510 application the terminal count is avoided and a recycle logic network is used to "anticipate"

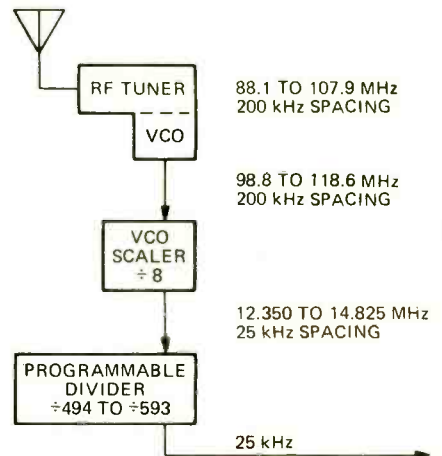
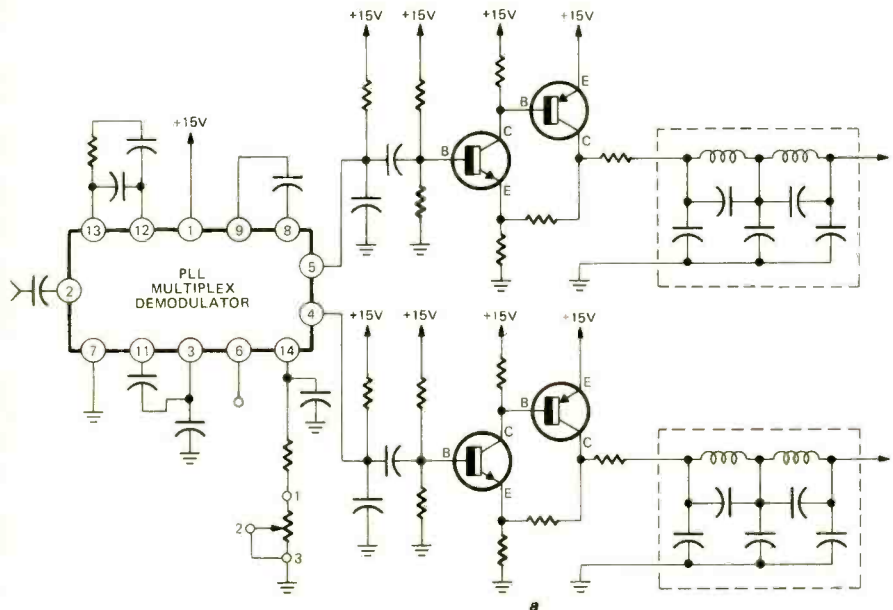


FIG. 4—FREQUENCY SCALER and programmable divider process VCO reference signal.

part" a particular count and provide a reload pulse within an acceptable gate delay time.

Digital phase detector and loop filter

The digital phase detector compares the output signal from the programmable divider (frequency scaled VCO) with the 25-kHz reference signal. When these signals differ in frequency the tuner tuning voltage is corrected, changing the rf tuning and VCO frequency so the output from the programmable divider is 25 kHz and in constant phase (but not zero) with the 25-kHz reference.

The digital phase-detector IC is commercially available and incorporates two different phase detectors with common inputs, a charge pump circuit and a high-gain amplifier. The duty cycles of the two inputs are not important since negative transitions control the operation.

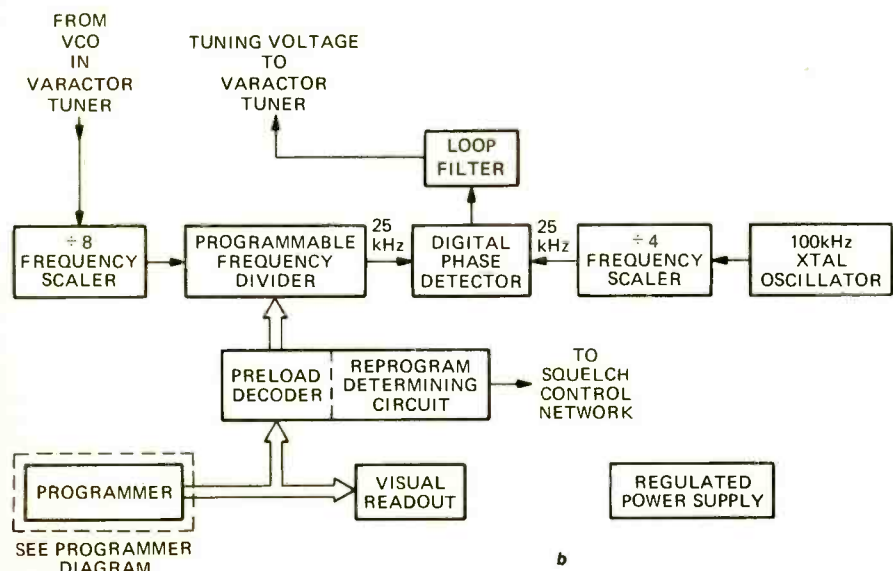


FIG. 3-a (top)—PHASE-LOCK LOOP IC is the heart of the FM multiplex system. Tuning is inductanceless. FIG. 3-b—FREQUENCY SYNTHESIZER operation is illustrated by block diagram.

The loop filter is an active integrator circuit that provides a dc tuning voltage for the tuner and establishes a control loop bandwidth. This bandwidth determines the amount of filtering on the tuner tuning voltage and also the time required to establish a stable phase-locked condition. The high-gain amplifier in the phase-detector IC along with a two-transistor dc amplifier form the active portion of this filter.

Programmer section

The programmer is the block of circuits that provides the programmable frequency divider with the required data inputs for the station frequency that has been "programmed." It provides three distinctly different modes of tuning; keyboard, pre-programmed data cards and automatic sweep/scan (Fig. 5).

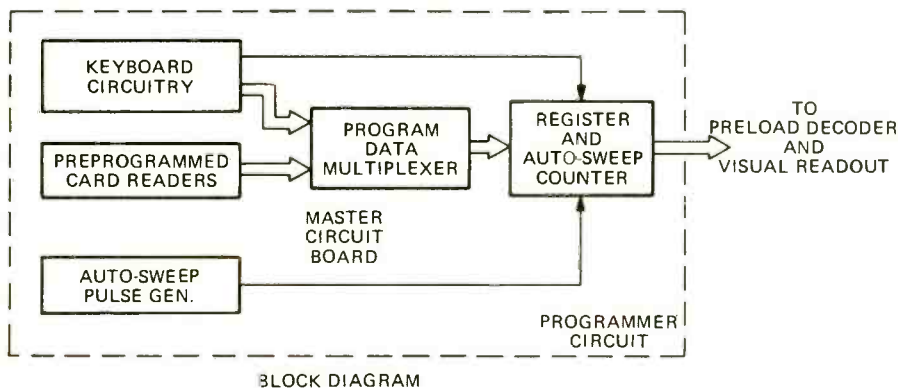


FIG. 5—PROGRAMMER SECTION handles the automatic scanning, keyboard and programmed data card inputs; processing them for the preload decoder and readouts.

Preload decoder

We need a preload decoder because the programmer is programmed with logic data that correspond to the FM channel frequencies, while the logic inputs required by the programmable divider are an entirely different set of values. Therefore, a "translator" is required. Using logic redundancies and sequential states greatly reduced this circuit complexity. Nonetheless, ten IC's were required to perform this job.

Register and auto-sweep counter

The "memory" unit of the programmer is a register consisting of four low-frequency programmable decade down-counters. The desired channel information in BCD (Binary-Coded-Decimal) form is parallel-loaded directly from the data multiplexer. During KEYBOARD programming each stage of the register is parallel-loaded individually. The completely loaded register retains this data until the RESET button is pressed to clear the register, or until a different mode of programming is selected.

Selecting AUTO-SWEEP operation

changes the memory register into a serial down counter, and a reset pulse automatically loads in the highest channel frequency, 107.9 MHz. An auto-sweep count-down pulse is supplied by a pulse generator that continues the count-down sequence until the squelch control system gives a STOP signal.

The BY-PASS key on the keyboard provides a zero voltage logic level to the "stop sweep" logic network that tells the tuner to resume or continue channel scanning. Holding this key depressed overrides any STOP signals and the tuner will continuously sweep from 107.9 to 88.1 MHz and reset to recycle until the key is released. The BY-PASS key functions only in AUTO-SWEEP.

Auto-sweep pulse generator

The auto-sweep pulse generator is

an astable multivibrator that produces a 50- μ s positive pulse at a rate that varies from one pulse per second to six pulses per second. These pulses are applied to the auto-sweep counter in the AUTO-SWEEP mode. The pulse rate is the channel sweep speed and is adjusted by a potentiometer located on the tuner front panel behind the hinged door. Once a good listenable station has been found, the pulse generator is automatically turned off, stopping the sweep. It is disabled in the other programming modes.

Program data multiplexer

The data multiplexer is located on the master circuit board and directs the BCD information from the three FM station selection inputs to the programmer circuit. The desired FM station selection scheme is activated when the appropriate front panel switch is depressed. Both negative and positive logic are used to minimize circuit complexity. Even so, eight IC's were required for a total of 25 logic gates.

The output of the data multiplexer is internally fixed when in AUTO-SWEEP with the BCD equivalent

of 107.9 MHz. This data is the "re-load" information for the auto-sweep counter circuit as it counts down to 88.1 MHz and recycles, thus providing automatic FM station scanning.

The keyboard

Keyboard tuning is the third mode. Tap out the frequency on the keys to tune in your favorite station, instantly. Touch the RESET button and you're ready to program another station.

Mounted on the keyboard circuit board are twelve spst-normally open reed keyboard switches. Ten of the keys are numbered "1" through "0" and their outputs are coupled to a simple diode matrix that provides the corresponding BCD outputs. The two remaining keys, RESET and BYPASS, provide control signals to the auto-sweep counter register. The RESET key performs a "clear" when the tuner is in the KEYBOARD mode, and the register is cleared to be programmed with another FM channel frequency.

Preprogrammed card reader

The three preprogram card readers are activated when the tuner is set to the PREPROGRAM mode. One of the three card reader switches (A, B, or C) is pressed to select the desired pre-programmed station. A simple schematic of the card reader is in Fig. 6. The corresponding outputs of the

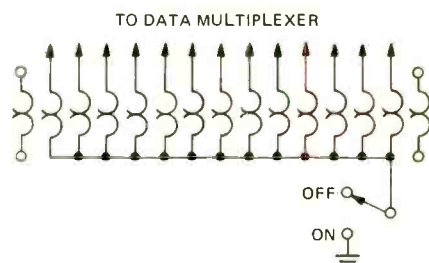


FIG. 6—CARD READER CIRCUIT. Notched card breaks unwanted circuit connections.


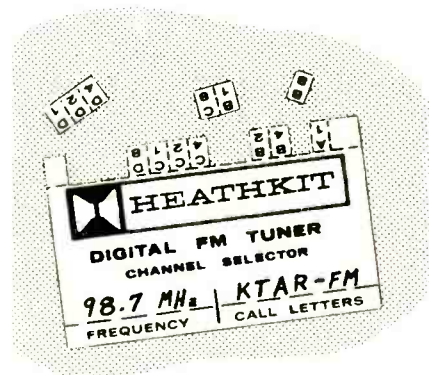


FIG. 7—CHANNEL-SELECTOR CARD. This one has been programmed for 98.7 MHz.

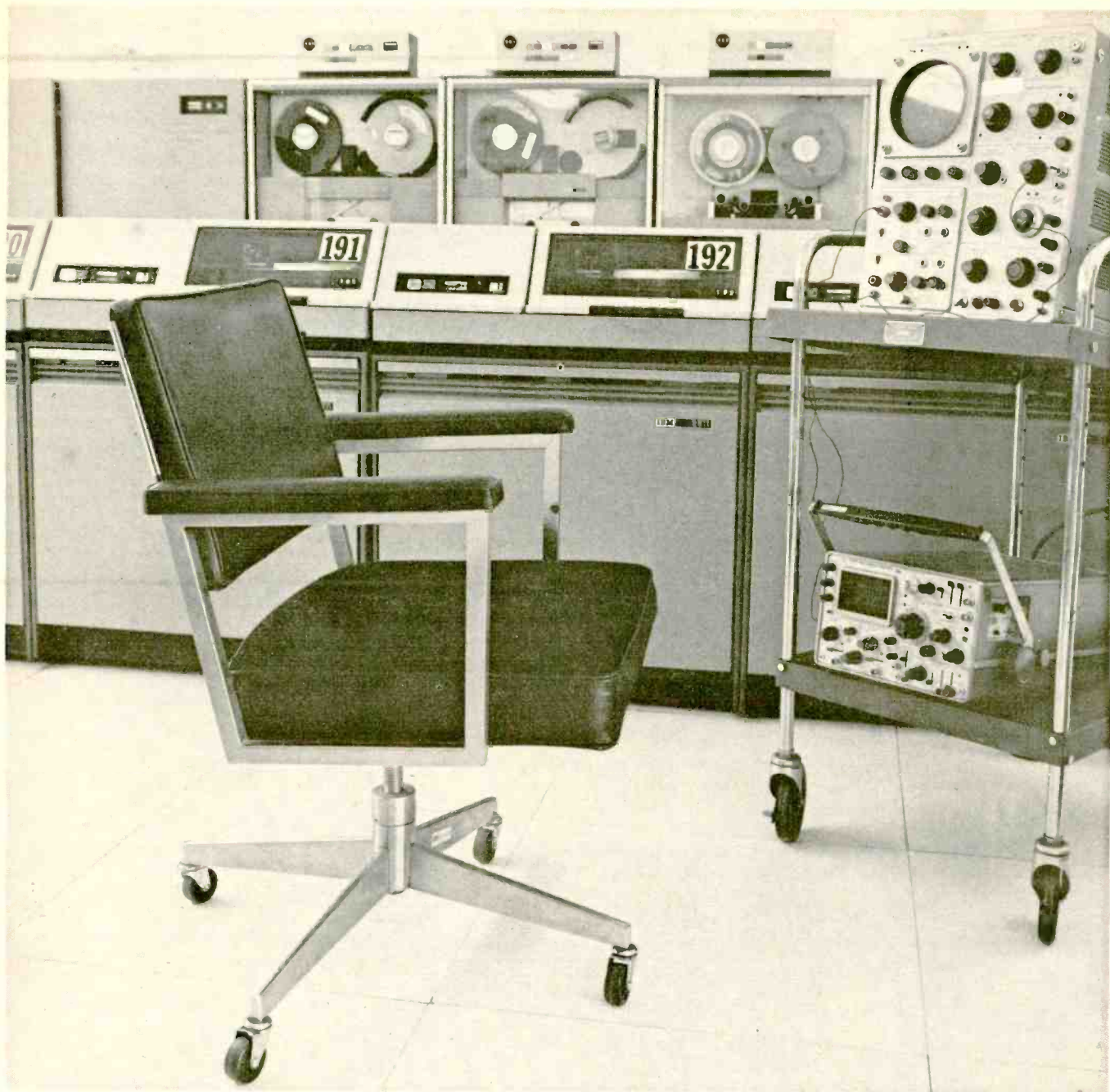three circuits are connected to the input AND gates of the data multiplexer. The card reader hardware consists of three independent 15-line edge-board
(continued on page 50)



This important job (and its big income) is reserved for a qualified electronics technician. It can be you!

It's a fact. There are *thousands* of jobs like this one available *right now* for skilled electronics technicians. What's more, these men are going to be in even *greater* demand in the years ahead. But how about you? Where do you fit into the picture? Your opportunity will never be greater . . . so act *now* to take advantage of it. The first step? Learn electronics fundamentals . . . develop a practical understanding of transistors, trouble-shooting techniques, pulse circuitry, micro-electronics, computers and many other exciting new developments in this growth field. Prepare yourself now for a job with a

bright future . . . unlimited opportunity with lasting security . . . prestige and a steadily growing paycheck.

Cleveland Institute of Electronics courses have been stepping stones to good jobs in electronics for thousands of ambitious men. Why not join them? You can learn at home, in your spare time, and tuition is remarkably low. Read the important information on the facing page. Then fill out and mail the reply card or coupon today. We'll send you all the details and for your convenience, we will try to have a representative call. Act now . . . and get your high-paying job just that much sooner.

How You Can Succeed In Electronics ... Select Your Future From Seven Career Programs

The "right" course for your career

Cleveland Institute offers not one, but seven different and up-to-date Electronics Home-Study Programs. Look them over. Pick the one that is "right" for you. Then mark your selection on the reply card or coupon and mail today. In a few days, you will have the complete details.

1A. Electronics Technology

A comprehensive program covering Automation, Communications, Computers, Industrial Controls, Solid-State Devices, and preparation for a 1st Class FCC License.



1B. Electronics Technology with Laboratory

Includes all areas of Course 1A including 1st Class FCC License preparation. In addition, student receives 161-piece Electronics Laboratory and 17 "lab" lessons for "hands-on" experience.



2. Broadcast Engineering

Here's an excellent studio engineering program which will get you a 1st Class FCC License. Now includes Video Systems, Monitors, FM Stereo Multiplex, Color Transmitter Operation and Remote Control.



3. First Class FCC License

If a 1st Class FCC ticket is your goal, this streamlined program will do the trick and enable you to maintain and service all types of transmitting equipment.



4. Electronic Communications

Mobile Radio, Microwave and 2nd Class FCC preparation are just a few of the topics covered in this "compact" program. Highly recommended for jobs with telephone companies.



5. Industrial Electronics & Automation

This exciting program includes many important subjects such as Instrumentation, Solid-State Devices used in Pulse, Digital and power controls.



6. Electronics Engineering

A college-level course for men already working in Electronics... covers Steady-State and Transient Network Theory, Solid-State Physics and Circuitry, Pulse Techniques, Computer Logic and Mathematics through Calculus.



An FCC License... or your money back!

The CIE courses described here will prepare you for the FCC License specified. In fact, we are so certain of their effectiveness we offer this Money-Back Warranty: when you complete any CIE licensing course, you'll be able to pass your FCC exam or be entitled to a full refund of all tuition paid. This warranty is valid during the completion time allowed for your course. You get your FCC License — or your money back.

CIE's **AUTO-PROGRAMMED**® Lessons help you learn faster and easier

Cleveland Institute uses the new programmed learning approach. Our Auto-Programmed Lessons present facts and concepts in small, easy-to-understand bits... reinforce them with clear explanations and examples. Students learn more thoroughly and faster through this modern, simplified method. You, too, will absorb... retain... advance at your own pace.

Employment Assistance available for all CIE students... at no extra cost

Once enrolled with CIE, you will get a bimonthly listing of high-paying, interesting jobs available with top companies throughout the country. Many CIE graduates hold such jobs with leading companies like American Airlines, AT&T, General Electric, General Telephone and Electronics, IBM, Motorola, Penn Central Railroad, Raytheon, RCA, Westinghouse and Xerox... to name a few.

CIE Lessons are continually up-dated

All lesson books and materials from CIE are continually revised or replaced according to the current needs of industry and the rapidly advancing and changing state of the art.

Approved Under G.I. Bill

All CIE career courses are approved for educational benefits under the G.I. Bill. If you are a Veteran or in service now, check box for G.I. Bill information.

CIE Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114
Accredited Member National Home Study Council

Mail coupon for 2 FREE BOOKS

Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114

Please send me your two FREE books:

1. Your school catalog, "Succeed in Electronics."
2. Your book on "How To Get a Commercial FCC License."

I am especially interested in:

- | | | |
|---|--|--|
| <input type="checkbox"/> Electronics Technology | <input type="checkbox"/> Broadcast Engineering | <input type="checkbox"/> Electronic Communications |
| <input type="checkbox"/> Electronics Technology with Laboratory | <input type="checkbox"/> First Class FCC License | <input type="checkbox"/> Industrial Electronics & Automation |
| | <input type="checkbox"/> Electronics Engineering | |

Name _____ Age _____
(please print)

Address _____

City _____ State _____ Zip _____

Veterans and Servicemen:

Check here for G.I. Bill information

RE-17

Circle 17 on reader service card

connectors mounted on the tuner front panel behind the lower hinged door. The contacts of these connectors have been designed to remain closed (short circuit) when in a normal state. A notched plastic channel selector card is inserted into the connector to "open" the unwanted connections. The notches (cutouts) therefore permit certain connections to remain closed which correspond to the desired channel frequency in BCD (binary coded decimal) form. A channel selector card is shown in Fig. 7 programmed for 98.7 MHz.

"Unlocked" detector

Outputs from both phase detectors of the digital phase detector IC are used as inputs to the lock detector. This detector consists of two 2-input NAND gates connected in an R-S type flip-flop configuration that is followed by an integrator and driver transistor. When the rf tuner VCO is phase-locked to the reference oscillator, the R-S flip-flop remains in a steady state which keeps the driver transistor cut off. However, if the VCO becomes unlocked from the reference oscillator, the R-S flip-flop produces a series of pulses. The first one turns on the driver transistor, and thus the "UNLOCKED" light, while at the same time supplying a signal to the squelch circuit to squelch off the audio.

"Re-program"

The United States FM broadcast band spans from 88.1 MHz to 107.9

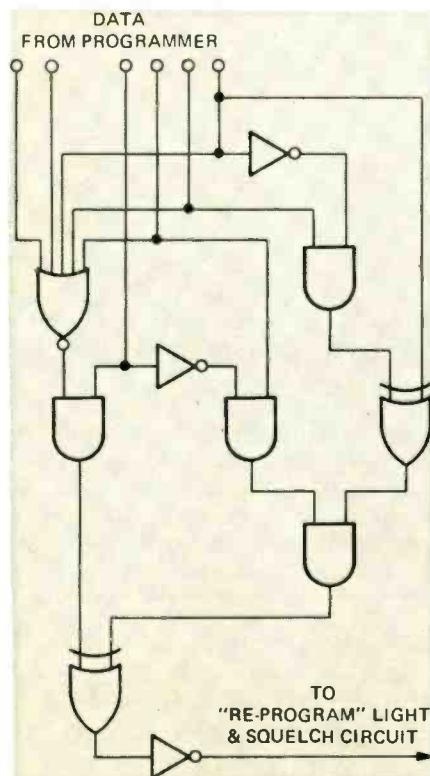


FIG. 8—RE-PROGRAM LOGIC detects when out-of-band input has been selected.

MHz with 200-kHz channel spacing. The re-program circuitry detects when a channel frequency outside of this FM band is programmed into the Tuner (usually this occurs only in the KEYBOARD mode). Should an out-of-band frequency be entered, that frequency will appear on the front panel numerical readout, but the "RE-PROGRAM" indicator will light and the audio will remain squelched. Fig. 8 is the re-program logic diagram. Should a frequency ending in an even number, i.e. 103.4, 104.6 etc. be programmed, the tuner will automatically go to the next highest odd number, i.e. 103.5, 104.7 instead of calling for a "RE-PROGRAM".

Squelch control

The AJ-1510 squelch control circuit accepts inputs from various sources within the tuner and then determine from these inputs what the state of the audio squelch control volt-

age should be (audio on or audio off). Here are eight conditions, all weighted equally, which contribute to the logic decision making of the squelch circuit:

1. Is the noise level from the i.f./FM discriminator above or below the acceptable limit?
 2. Is the tuner rf input signal above or below the desired sensitivity setting?
 3. Is the i.f. signal precisely center tuned?
 4. Is the tuner receiving a stereo transmission? (This can be switched off.)
 5. If the tuner is in the KEYBOARD mode, has the keyboard programming been completed?
 6. Is the VOC properly phase-locked to the reference oscillator?
 7. Is the SQUELCH DEFEAT switch ON?
 8. Is the tuner properly programmed or is a "re-program" signal present?
- (continued on page 98)*

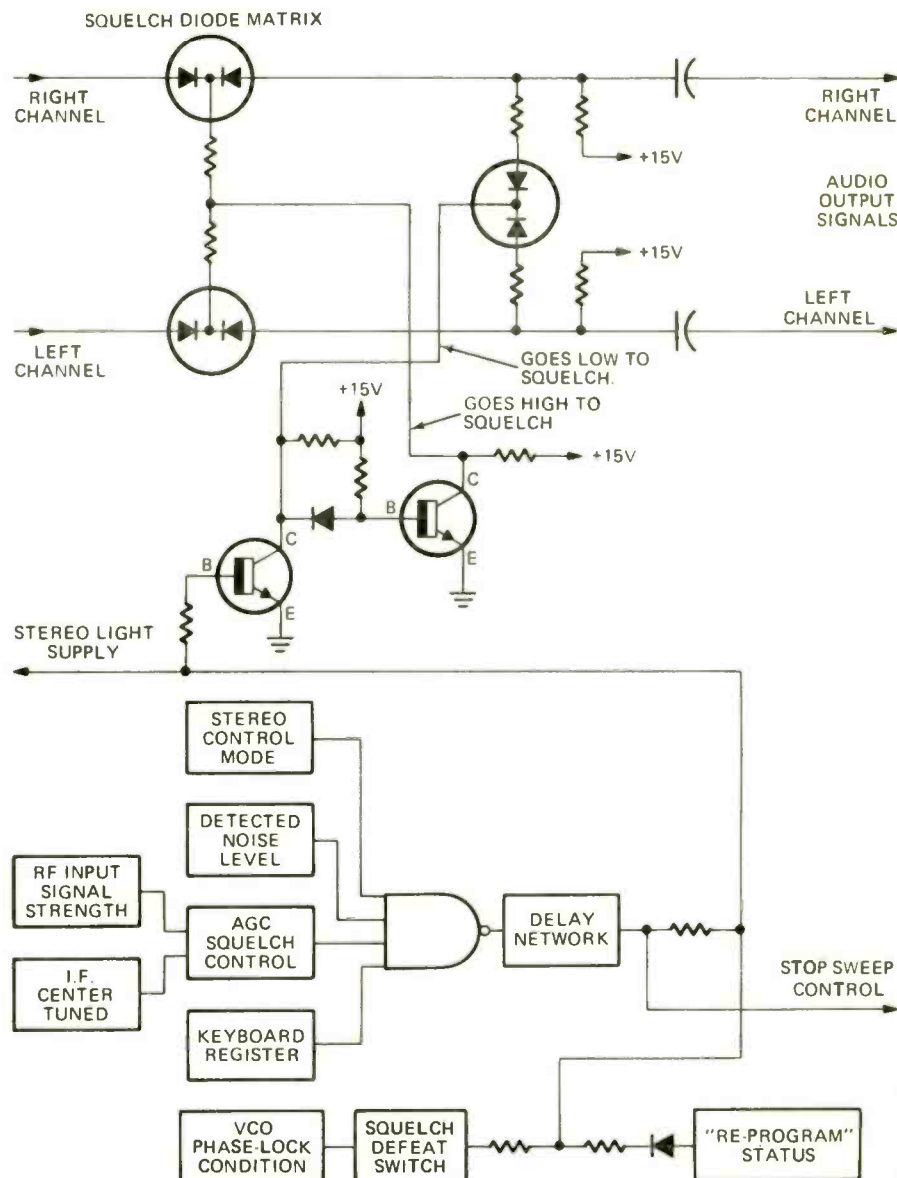


FIG. 9—SQUELCH CONTROL AND LOCK-OUT operation is illustrated by this schematic and block diagram. The logic circuits check eight important operating criteria.

How to Set Up a Public Address Speaker System

The choice, placement and layout of a speaker system can make or break a PA system. Do it this way and be sure

by **BOGEN DIVISION, L.S.I.***

THERE ARE FOUR PRIMARY CONSIDERATIONS when using cone or horn speakers as a part of a PA system. These are the power available to the speakers. The number of speakers. The type of speakers. The placement and connection of speakers.

The first step is to survey the proposed installation and carefully determine how many and what type of speakers are needed. The following table may be of aid in this respect.

4. **Fidelity and intelligibility** requirements.

5. **Economic** factors.

Speaker placement

The most complex step in speaker installation is their placement and hookup. Conditions under which each system must operate vary so widely with each installation that only the primary steps are given when considering speaker placement. For indoor systems, two kinds of placements can be used. The speakers may be posi-

reverberations or blanking by obstacles.

For outdoor systems, the main considerations are direction of sound and the area to be covered. Here, brute-force is generally used by employing highly-directive trumpets. Bear in mind that sound pressure drops approximately 75% below the previous level each time the distance from the speaker is doubled. Also, directivity (amount of power concentrated along the speaker axis) increases with the size of the speaker horn.

Speaker connections

When connecting the speakers together, impedance matching and phase relation must be considered. Since these factors are somewhat involved, an extended discussion of impedance matching and speaker phasing follows.

Efficient transfer of power from the amplifier to the speakers is the prime consideration in a sound system. The two methods of transfer of power are connection from the amplifier directly to the speaker voice coils and connection from the amplifier to the speaker voice coils through a transformer. The first method is used when short runs of wire not over 200 feet in length and simple speaker arrangements involving low impedances are used.

The second method is used when the wire runs are over 200 feet, when

AMPLIFIER POWER

6 to 8 w
15 to 18 w
25 to 30 w
45 to 50 w
60 to 70 w

SPEAKERS NEEDED FOR INDOOR INSTALLATION

Two 8-in. speakers
Two 12-in. speakers
Four 12-in. speakers
Six 12-in. speakers
Eight 12-in. speakers

SPEAKERS NEEDED FOR OUTDOOR INSTALLATION

One 12-in. speaker
One trumpet
Two trumpets
Three trumpets
Four trumpets

There are several types of speakers available, and the choice of speakers depends upon five main factors:

1. **Geometry and acoustical** characteristics of the area to be covered.

2. **Ambient sound level** in which the speakers must operate.

3. **Fundamental use** of the system (i.e.—speech or music reproduction.)

tioned flat against the walls, and the axis of the speakers rotated so that they radiate energy at an angle from the wall. The speakers may also be positioned in the corners of a room. Variations from these two arrangements must be considered where there are alcoves, balconies, booths, dividing walls, and side rooms. In such cases, extra speakers must be set up to prevent dead spots resulting from unusual

*A Division of Lear Siegler Inc., Paramus, N.J.

there are complex speaker arrangements, and when it is desired to have less than 15% power loss in the transmission lines. The use of transformers also simplifies impedance calculations and facilitates changes in complex speaker arrangements.

Impedance matching without transformers

For the most efficient transfer of power, it is important that the total speaker impedances match the output impedance of the amplifier. Single speakers should be matched as shown in Fig. 1.

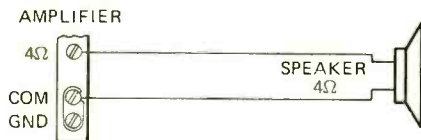


FIG. 1—SINGLE PA SPEAKER is connected like this. Just match the two impedances.

When there is more than one speaker in a sound system, calculations of total speaker impedance are based upon two formulas:

(a) For series connection of speakers, add the individual speaker impedances together to obtain the total matching impedance (see Fig. 2).

$$Z_T = Z_1 + Z_2 + \dots + Z_n$$

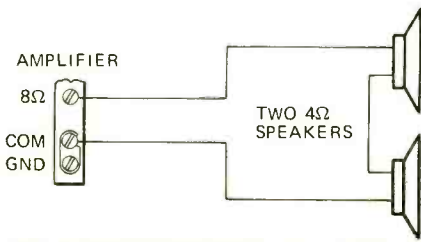


FIG. 2—SERIES SPEAKERS are selected so the sum of impedances matches amplifier.

(b) For parallel connection, add the reciprocal of the individual speaker impedances together to obtain the reciprocal of the total matching impedance (see Fig. 3).

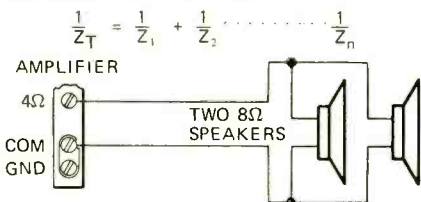


FIG. 3—PARALLEL SPEAKER connections tend to cause excessive line losses.

It is generally not advisable to use more than two speakers in parallel. Operation with less than 4 ohms impedance will result in excessive line losses.

(c) For series/parallel connections, combine the two formulas as the speaker connections indicate. For example, in Fig. 4, apply the series

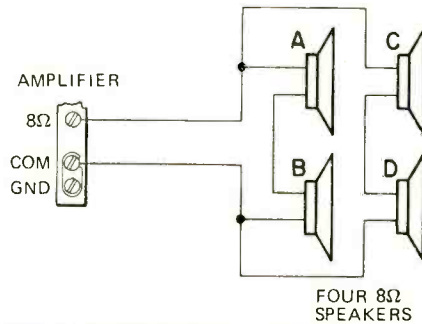


FIG. 4—SERIES-PARALLEL connections may be used to gain desired power distribution.

formula for A and B, then for C and D. Take the results of this and apply the parallel formula to obtain the final matching impedance:

$$A + B = X \quad (1)$$

$$C + D = Y \quad (2)$$

$$\frac{1}{Z_T} = \frac{1}{X} + \frac{1}{Y} \quad (3)$$

$$Z_T = \frac{XY}{X+Y} \quad (4)$$

Power distribution with transformers

In a series system of speakers, all with the same voice coil impedances, equal power distribution will occur. However, if one speaker has 4 ohms impedance and another 8 ohms, the power consumed by the 8 ohm speaker will be twice that of the 4 ohm speaker.

In parallel systems of speakers, all with the same voice coil impedances, equal power consumption will result. When speakers of different impedances are connected in parallel, the smaller impedance speaker will receive the greater power. If one speaker is 8 ohms and one is 16 ohms, the 8-ohm speaker will consume twice as much power as the 16-ohm speaker.

When operating speakers on voice coil impedance (without transformer), use as heavy a wire as possible. Speaker cable runs of 100 feet or over should be at least No. 16 wire. Runs from 50-100 feet should be No. 18 wire or larger.

Impedance matching with transformers

The proper use of transformers with speakers far from the amplifier prevents comparatively large power losses in the transmission lines. In complex installations having large numbers of speakers, the use of transformers simplifies power distribution.

Constant-voltage transformers are most commonly used for this purpose, though impedance-matching transformers may be used in some sound installations. The constant-voltage transformer has its secondary tapped for different values of power (watts) for the speaker. The primary matches the constant voltage line, which is either 25 volts or 70 volts.

Constant voltage system

The constant-voltage system was developed particularly for use in large multi-speaker installations, but that does not prevent smaller installations from enjoying its advantages.

The constant-voltage method greatly reduces the amount of computation necessary to determine the proper transformer taps when varying sound levels are required. It also permits the addition to, or changing of, an existing system without recalculation of the total impedances and the power required.

A favorable load condition exists if the total power consumed by the loudspeakers is always less than or equal to the amplifier rating.

When the constant voltage transformer taps are marked in watts:

1. Choose the transformer with a matching secondary (8-ohm secondary for an 8-ohm speaker).

2. Select the power tap desired, and connect to speaker.

3. Connect the constant-voltage line to the primary.

If the transformer is marked in impedances, the required power can be determined by applying the formula:

$$Z = E^2/P$$

Where Z = Required transformer impedance in ohms E = Amplifier output voltage (25 or 70 volts) and P = Desired power at the speaker in watts

Mismatching speaker to amplifier

Mismatching upward (connecting an 8-ohm speaker to the 4-ohm output of an amplifier) will decrease the power delivered to the speaker. Power loss will be about proportional to the upward impedance mismatch (50% when connecting an 8-ohm speaker to a 4-ohm amplifier tap). Mismatching cannot ordinarily damage a well-designed amplifier.

As a general rule, no serious frequency response deficiency will be noted if upward mismatches up to about five-to-one ratio are used.

Downward mismatching (connecting a 4-ohm speaker to an 8-ohm amplifier tap) should always be avoided. It will reduce the amplifier power output and overload the output tubes or transistors, seriously affecting their life and performance.

Phasing speakers

When more than one speaker is used in a sound system installation, it is advisable to phase the speakers to reduce the cancellation effect. Speakers out of phase lose up to one-half of their normal volume and operate with degraded tone quality and increased distortion.

For speakers facing in the same general direction, the speakers are in

phase when their respective diaphragms move outward and inward at the same time. With two speakers facing each other, proper phasing is achieved when the diaphragm of one speaker moves outward as the diaphragm of the other speaker moves inward.

Phasing is done by checking the polarity of the speaker terminals with respect to the movement of the speaker diaphragm, and connecting the speakers to produce the diaphragm movement or phasing desired. With loudspeakers of the same make and model, the respective diaphragms should move in the same direction when the terminals are connected in the same manner, but it is safer to check the polarity.

Where different speakers are used, carry out the following procedure to determine the diaphragm movement with respect to the speaker terminals for speakers connected in parallel:

1. Connect one lead from a 1.5-volt dry-cell to one voice coil terminal of the speaker.
2. Momentarily touch the other lead from the dry cell to the other speaker terminal.
3. Observe direction of cone or diaphragm movement (either inward or outward) when the circuit is closed.
4. Note this direction of the movement on a slip of paper.
5. Mark the terminal connected to the positive pole of the dry cell if the movement is outward, mark the terminal connected to the negative pole if the movement is inward.
6. Repeat steps 1 through 5 for other speaker or speakers to be checked.
7. Connect the marked and unmarked terminals according to the manner of electrical arrangement shown in Fig. 5 if the speakers are facing in the same direction. If the speakers face each other, make connections as shown in Fig. 6.

In simple sound systems, it may be easier to check phasing by listening to a low audio frequency while alternating the speaker leads. The human ear can usually detect when the low frequency sound is at the higher volume, indicating that the speakers are properly phased.

Balanced line connections
In most sound installations, unbalanced speaker lines will provide satisfactory performance. A typical unbalanced line installation for a 25-volt system is shown in Fig. 7. Two-conductor unshielded cable is normally employed in such installations. One conductor is connected to the 25-volt terminal on the amplifier output strip. The other wire goes to the common

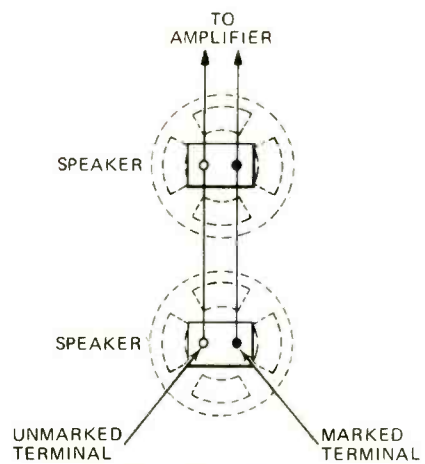


FIG. 5—PA SPEAKERS facing same way are phased with like terminals wired together.

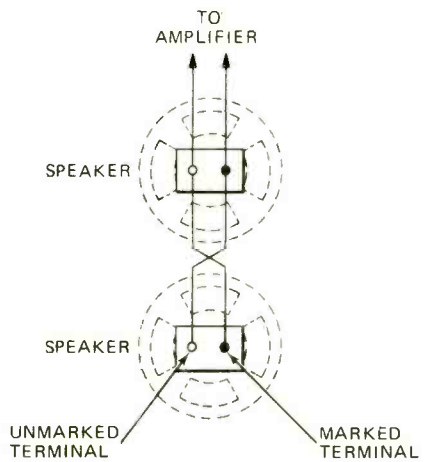


FIG. 6—SPEAKERS FACING EACH OTHER have line transposed for in-phase operation.

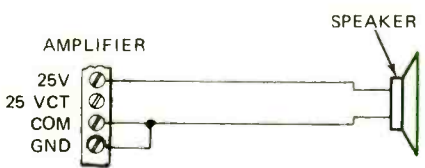


FIG. 7—A 25-VOLT UNBALANCED line is typical. Balanced lines are for special cases.

terminal, which is then connected to ground.

However, in more elaborate systems where input lines are run in close proximity to the speaker lines for extended distances, currents in the speaker lines may be picked up by the input lines. When these stray currents are fed back to the amplifier, hum and crosstalk will be introduced into the system, or the amplifier may oscillate.

For this reason, balanced line connections are recommended for installations in which long input and speaker lines are run close together. A balanced line is obtained by under-grounding the common terminal, leaving the outputs floating. In a balanced line, any current which is developed in one side of the line is offset by an equal and opposite current in the other side. This greatly reduces the

possibility of inducing stray currents in nearby input lines.

In some balanced line installations, it may also be necessary to connect the appropriate center-tap terminal to ground, and to ground the amplifier chassis.

If hum or other pickup is encountered with a balanced line as described above, it may be necessary to run a shielded two-conductor cable to the speakers and to ground the shield at the amplifier end.

Sound column speakers

Sound columns are designed for sound reinforcement in theatres, auditoriums and arenas where it is necessary to cover a large area with a minimum number of speakers. A sound column consists of six or more cone loudspeakers enclosed in a rectangular cabinet lined with acoustic material. Depending on the size and type of cone speakers employed, the output rating of a sound column may range from 25 to 200 watts. The terminal strip and sometimes a plate for mounting a line-matching transformer are located on the rear panel.

The arrangement of the speakers in the column is such that their acoustic output adds up in the forward direction, so that the effective throw of the sound column far exceeds that of the individual cone speakers. The effective throw or maximum distance at which sound from the column is distinctly audible is usually between 100 and 200 feet.

Because of its configuration, the sound column produces a highly directional beam pattern, which permits the sound to be aimed over a well-defined area of the installation site. Since about 90% of the acoustic output of the column is confined to this pattern, there is virtually no random sound available to cause reverberation or reflection. Consequently, a sound column can be properly directed to cover a hall or section of a hall most effectively and to keep harmful reflections away from the floor and ceiling.

In addition, the geometrical configuration of the speakers in the column produces a sound dispersion pattern which is quite broad in the horizontal plane but much narrower in the vertical plane. In the Bogen sound columns, the horizontal dispersion pattern is 120°, which is a great deal more than that of the individual speakers. However, the cumulative effect of the in-line speakers produces a vertical dispersion pattern of approximately 25° as shown in Fig. 8.

Placing sound columns

A typical sound column installation is shown in Fig. 9. The sound

(continued on page 99)

SQ?
 LOGIC?
 RM?
 QS?
 DISCRETE?
 MATRIX?
 CD-4?

unscrambling

The pages of contemporary publications and newspaper
An expert uses the best in 4-channel equipment and a

"THE PAGES OF HISTORY ARE LITTERED with the dried bones of those who at the dawn of a new idea sat down to think it over . . . and thinking it over, died." You could not find a better description concerning the present situation in 4-channel sound.

On the one hand we have the consumer publications with their endless articles on the differences between matrix systems . . . how they aren't compatible . . . how the consumer should sit it out until the "matrix war" is resolved in favor of one system or another.

On the same side of the coin there are the originators of the various matrix systems, each of whom can conclusively prove that only their system is technically and musically viable; yet these are the same people breaking their backs to increase separation while abandoning their original designs.

Of course, we all have read—and by now accept the fact—of the many "bugs" that plague the discrete CD-4 record system, and we all *know* it will be a long time before the CD-4 system is suitable for use in this country. In fact, at the time this article is being prepared I have just read an editorial to this effect in a leading consumer magazine . . . and all the while I'm listening to outstanding CD-4 sound from a production model JVC 4DD-5 CD-4 demodulator. (My other equipment should be so bug-free.) The only "bug" is the sparcity of records to play through the system. And the lack of equipment to play the few available records.

On the other side of the coin we have the hi-fi retailers who actually believe the articles being written every month. They are not going out of their way to inform their customers about 4-channel "until the industry settles on one standard system."

Except for Lafayette Radio and some local firms, 4-channel sound just isn't getting the push it deserves. And while we are on the flip side of the coin let us not overlook the record producers; with very few exceptions their 4-channel attempts are at best, feeble. Even if a hi-fi salesman attempted to demonstrate 4-channel, the customer's reaction to most recordings would be: "So What! For this I should spend an extra hundred or so dollars?"

In actual fact, all existing 4-channel systems *sound good, far, far better than stan-*

dard 2-channel stereo; and do not miss the emphasis on *sound good*. Theoretically, one system might be superior to another, but in practice they are all a new and exciting experience in sound even when intermixed. For example, A QS recording played through an SQ decoder can be just as exciting as when played through its matching QS decoder, and the same goes for an SQ recording played through a QS decoder, or a "universal decoder," or even an ambient sound decoder—also known as a Dyna or synthesizer.

The real determination of whether the surround-sound effect is a new experience in listening or just another gimmick is the application of the 4-channel potential. For example, the Enoch Light Project 3 4-channel recordings are outstanding, even through basic QS and SQ decoders with their limited separation.

The performers can actually be detected in corner or center locations and the overall effect is a walk-through sound field that can be enjoyed from any location. It is not necessary to be positioned dead-center between the speakers with head locked facing the "front" speakers. By simply arranging the instrumentation specifically for the capabilities and potential of the qua-

drasound systems Enoch Light attains a true three-dimensional sound field regardless of the encoding or decoding equipment. This in contrast to some of the Columbia SQ library which cannot always justify the added expense of 4-channel. (Listen for yourself.)

By what is best described as an unplanned, fortunate chain of events we are now able to show you precisely what takes place with *production 4-channel equipments*—in contrast to the negative theories usually advanced. A little background so you will better understand what we shall illustrate. First, Enoch Light issued almost identical matrix recordings, the only difference being one version was recorded SQ, the other QS. Second, when Radio-Electronics obtained a JVC 4DD-5 CD-4 demodulator, one of the demonstration records was supplied in a plain white envelope with neither the record nor envelope carrying any identification. This turned out to be a JVC (not RCA) CD-4 mix-down from the original tapes that RCA used to make the stereo release of the show "Hair," and it was now possible to compare a CD-4 and stereo version of the same program material. Note that the sound quality of the JVC record in terms of distortion, clarity of

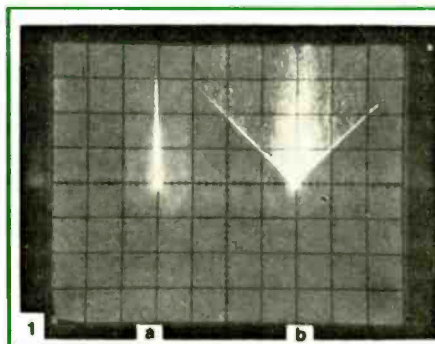


FIG. 1-a (far left)—MONO RECORD played in mono mode to produce equal-level in-phase signals at the right and left outputs of a stereo system. Vertical line indicates center-front mono image. FIG. 1-b (left)—STEREO-LIKE OUTPUT with pronounced center-front orientation is developed when mono record is played back in the stereo mode.

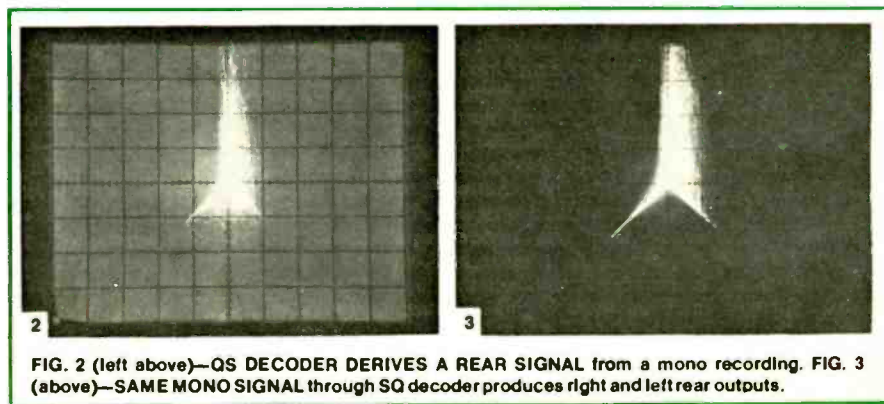


FIG. 2 (left above)—QS DECODER DERIVES A REAR SIGNAL from a mono recording. FIG. 3 (above)—SAME MONO SIGNAL through SQ decoder produces right and left rear outputs.

4-channel stereo

ads are filled with the pros and cons of 4-channel sound. vectorscope to demonstrate how the systems compare.

by HERB FRIEDMAN

sound and use of the 4-channel potential, so far outclassed the commercial releases supplied as demonstration CD-4 recordings that one could understand why CD-4 has not been as impressive as it should be—the recordings are plain rotten. (The best thing that could happen is for JVC to release their "private" recording of "Hair," destroy the presently available RCA releases and take it from there.)

Finally, JVC was willing to allow us to use their private CD-4 test records, which we added to the existing collection of 4-channel test records from CBS and United Recording Company. Between the JVC and standard Bruël & Kjaer frequency-run records we were able to check any phono pickup up to 50,000 Hz, as well as check matrix operation.

Since the important thing about any 4-channel system, or its performance, is only how it will sound in the typical home we chose as the reference equipment some of the best presently available. For SQ we used the Lafayette LR-4000 receiver which features an SQ decoder, a full logic (with wave-matching) SQ decoder and a derived ambient decoder. For both the QS and discreet 4-channel a JVC 4VN-770 amplifier was used.

For matrix tests all results are those which can be duplicated by using Shure V15 II and Empire 1000Z/E pickups. The CD-4 pickup was the JVC 4MD-20X with Shibata stylus. To avoid mistracking that could possibly mask CD-4 performance, a Garrard Zero 100 turntable was used.

Interpreting the Illustrations

Both the 2-channel and 4-channel sound fields consist of virtual and imaginary sound images. A signal fed to the left and right speakers (or left back and right back) creates a virtual sound image in the corners, for that is where the sound appears from the speaker. In the scope photographs, this virtual sound image is represented by the diagonal lines, which also indicate the relative sound power fed to the corner speakers.


A mono sound image, however, must be created from the corner signals. If the signals to the two front speakers are identical in level and phase the sound will *appear* to the listener to be coming from a center position between the two speakers: hence, the center or derived mono signal is an imaginary sound image as it really doesn't exist—it is created by phase and balance relationships between the corner signals.

In a similar manner, if the left front and left back signals are equal and in phase the listener will perceive an imaginary mono sound image between the two speakers. In the oscilloscope illustrations the imaginary mono sound image is shown as a vertical line pointing towards the center front, center back or center sides. In short, the scope traces indicate what the listener perceives, not the electrical power distribution.

The scope equipment shows only the in-phase information that tends to form an imaginary image. For example, if the left and right channels are fed equal levels that are out of phase the scope indicates the power fed to the corner speakers, and the pattern will be a "V" indicating an out of phase condition: one that cannot create a mono image.

The scope illustrations represent the sound field as it would appear to someone looking into the listening room from the floor above: upper left is LF (left front), upper right is RF, lower left is LB (left back), lower right is RB. Center positions are center positions, such as CF (center front) and CB.

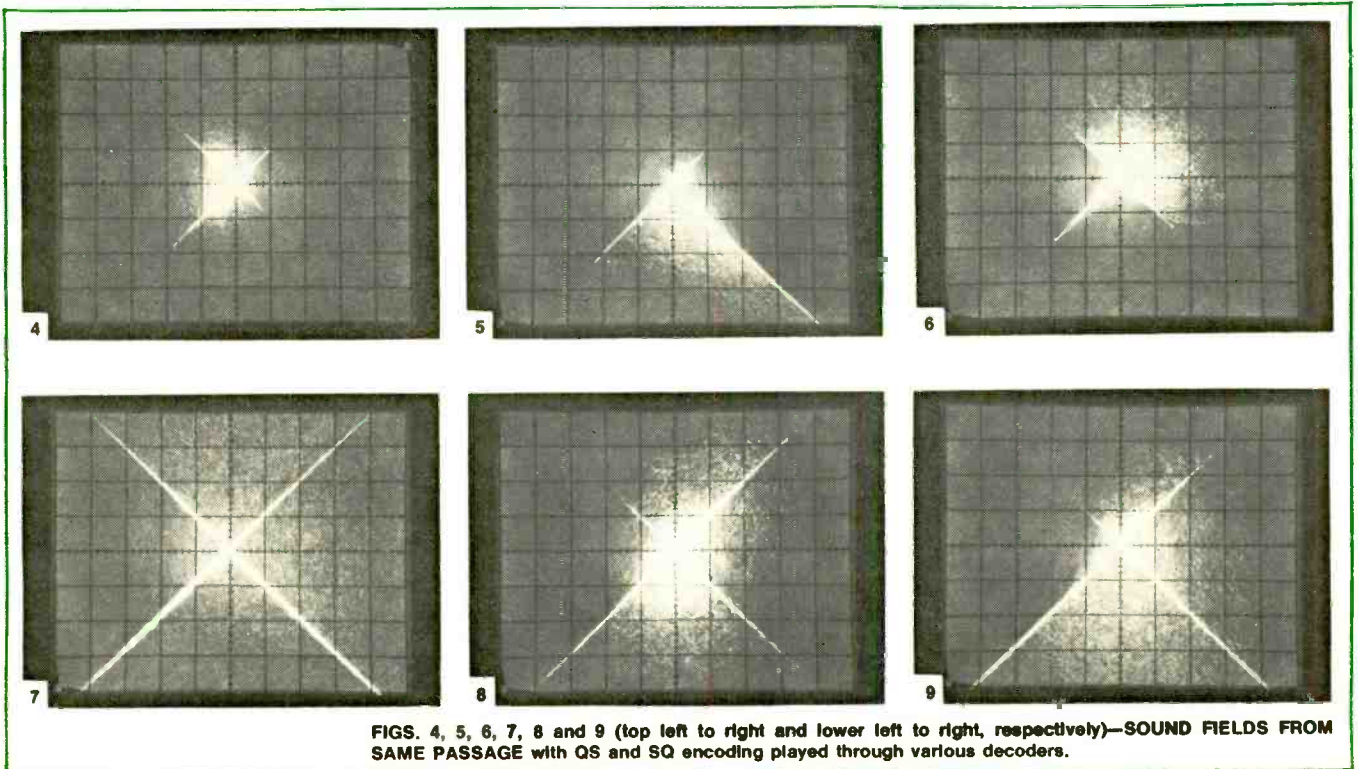In each series of illustrations the amplifiers have been balanced for optimum



FIGS. 4, 5, 6, 7, 8 and 9 (top left to right and lower left to right, respectively)—SOUND FIELDS FROM SAME PASSAGE with QS and SQ encoding played through various decoders.

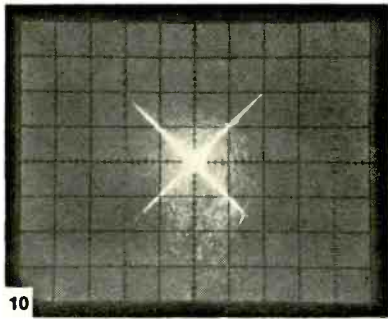


FIG. 10—STARPATTERN produced when SQ-encoded signals are applied to SQ decoder.

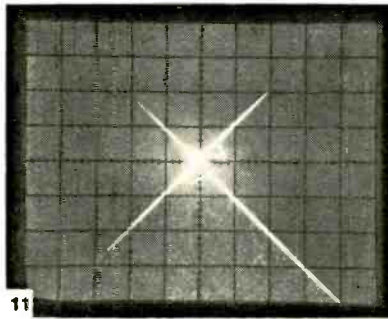


FIG. 11 (top right)—RIGHT REAR SIGNAL is pronounced when SQ-encoded signal is fed to a particular full-logic SQ decoder.

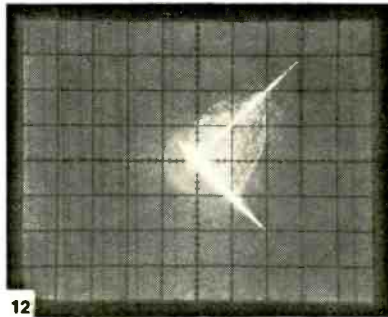


FIG. 12 (right)—QS-ENCODED signal fed through an SQ decoder produces extreme right orientation with predominant in-phase signal from right-back to center-front.

matched condition as determined by a calibration recording: the gains and/or balance was not disturbed during the series of checks and tests so that the scope illustrated what would be actually heard by the listener. If switching in a matrix decoder caused a balance shift, well that's the way it is for the listener and that's the way it's shown.

The matrix systems

All the viable matrix systems depend on a precise match of phase and amplitude

relationships. During the recording process the front and rear signals are level- and phase-oriented so that inverse orientation during playback will extract the individual corner signals. Naturally, because of bandwidth limitations there is only so much—and not much to begin with—separation possible, and each individual corner signal will appear as side signals in at least two of the other corners. Depending on the particular matrix system the undesired side signals can range from -3 dB to infinite attenuation.

If the decoding equipment was precise, the playback could be an accurate reproduction of what the record's producer intended. Unfortunately, it is virtually impossible to hold phase and amplitude relationships to a precise value(s) in consumer equipment. Resistor tolerances of 10% (standard) can produce almost 20° phase variation, while an ordinary gain shift of 3 dB—unheard in stereo listening—can shift the sound orientation from a matrix playback.

To correct many deficiencies in the matrix systems CBS developed the full-logic decoder for their SQ matrix. Basically, the full-logic decoder senses whether the predominant program information is CF (center front) or CR (center rear) and varies the gain to favor the predominant information. In a similar manner the wave-matching senses the corner information and varies the gain to enhance the discrete effect. At the time this article is being prepared the full logic decoder and lesser variations of it are the only means for enhancing the matrix sound field available to the consumer. It is rumored that CBS has an even more effective system for their SQ enhancement, while Sansui claims they have also come up with an enhancement for their QS system (Radio-Electronics, March 1973). To keep the record straight, we have heard these rumors for almost a year, but there is still no equipment. Fact is, the full-logic SQ decoder is the fifth generation of what was supposed to be a "perfect" matrix system the first time around.

But let us get back to the heart of the problem, what the user obtains when he puts down his hard earned dollars for 4-channel sound. His problems start when he places the matrix record on the turntable, as illustrated in Fig. 1. The left illustration

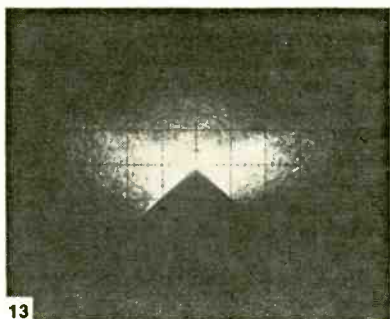


FIG. 13—SQ-ENCODED MATERIAL through an ambient-sound decoder. Program material is the same as for Figs. 4 through 9. Note similarity to QS pattern below.


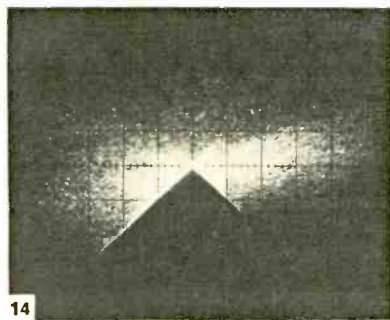


FIG. 14—QS-ENCODED single frequency through ambient (Dyna) decoder. Note the pattern is almost identical to that from SQ encoding in Fig. 13.

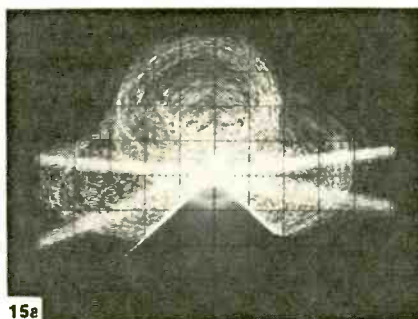

15a



16a

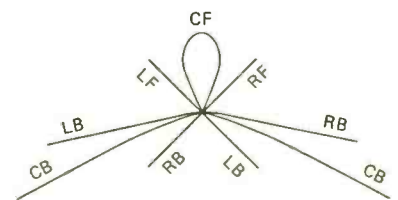
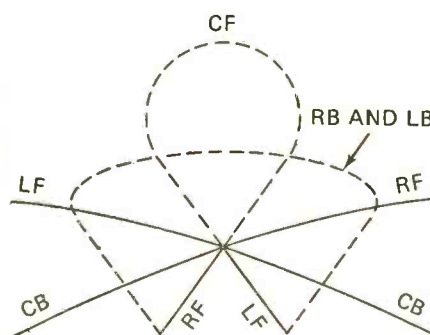


FIG. 15-a (top left)—DERIVED AMBIENT SOUND FIELD with decoder driven one channel at a time. FIG. 15-b (left above)—DIAGRAM of the derived pattern. FIGS. 16-a and -b (right top and bottom)—FIELD PATTERN AND DIAGRAM from QS encoding through ambient-sound decoder.

(Fig. 1-a) is made from a *mono* recording played with a stereo pickup with the amplifier set to *electrical mono*—both channels shorted together. The scope display is vertical, indicating *mono*, and this is what it should be even if the amplifier short was eliminated. But what really takes place is shown on the right side (Fig. 1-b with gain increased 2X for clarity). Because of phase mismatch within the pickup the one-second of mono program material is actually reproduced with a decided left-right orientation having a pronounced center or mono orientation. Now that we have a “stereo” image from a mono sound source some strange things happen. If we feed the mono-played-stereo through an SQ decoder, in addition to the front output we get a predominantly in-phase rear output as shown in Fig. 2. If we play the signal through a logic SQ decoder (Fig. 3) the rear output is out of phase. Why? Who knows, it shouldn't be, *but it does still sound good*.

Now that we understand that from pickup through decoder we do not have the most precise conditions, let us look at the final results from matrix records. Each illustration represents one second of identical program information, only the decoder or matrix recording system is changed. In Figs. 4, 5 and 6 the program comes from an SQ record and is played through SQ, full-logic SQ and QS decoders. Note that the SQ decoder output is oriented predominantly LF and CL (center left), just as perceived by the listener. Through the full-logic decoder the output level is directed towards the CR and RR. Through the QS decoder the sound is predominately CF/RF/CL. Theoretically it shouldn't happen, and doesn't happen when single-frequency test tones are used; but with program material it did take place. Sound bad? No! It sounds good. After all, maybe the logic decoder output is the correct one; perhaps the straight SQ decoder output is incorrect. The listener doesn't know which is correct so both sound good. It is even possible that neither sound distribution represents what the producer had in mind, but so what, it does sound good, and it does sound three-dimensional. As another example take a look at what happens when you feed SQ through a QS decoder (Fig. 6).

Are you still fussy about the SQ sound field not being a precise representation of the producer's thoughts. Okay, look at Figs. 7, 8 and 9. The exact same program material encoded QS, and decoded by QS, SQ and logic SQ decoders. In Fig. 7 we see that QS from QS has produced what is essentially an equalized sound field from all corners. The SQ decoder in Fig. 8 has produced a minor shift in the sound field to the RB, while the logic SQ decoder in Fig. 9 has produced a decided shift RR and CR. Now we have six possible sound fields, all of which sound good to the listener.

Which one is correct? Even the mixing engineer who controlled the sound field might not have any idea. The only thing that is important is that whether the systems are matched or intermixed there is a decided enhancement of the sound field, with the full-logic SQ providing the most enhancement in front-to-rear separation. While any condition might make a shambles of a symphony recording, if the capability inherent in each system is used

by the record producer for “pop” and light programs the overall sound field must come out pleasing to most listeners. This is easily checked for yourself by comparing the Enoch Light arrangements on Project 3 records with the attempts by other record companies. The finalized sound from Project 3 records might not be exactly what the producer had in mind, but it is to a major extent, spectacular.

Just for your amusement, now that you have observed the effect of different decoders on program material, observe what takes place when we used a steady-state tone. Figures 10, 11 and 12 represent the sound fields from SQ and QS encoding all channels driven, through SQ decoders. The SQ from SQ shown in Fig. 10 is what we should get. In Fig. 11 the logic has locked onto the RR signal, probably caused by the production tolerances described previously. Figure 12 is the result of QS encoding and SQ decoding. Note the RF orientation which compares with the RF program orientation in Fig. 6.

No illustrations are shown for equal level in all four channels through QS decoders because I have yet to find two QS decoders that will produce similar results, or any results that can be meaningful. Although the actual sound quality from program material is good, simultaneous four-

channel test-tone drive produces a scrambled scope trace from which little reliable information can be extracted. Again, the problem might simply be one of manufacturing tolerances. I do not doubt there is a QS decoder that will illustrate four-channel drive, I just haven't run across one yet.

It has been claimed that the Dyna or derived ambient decoder closely matches QS encoding. This decoding system, which originated with David Haffler when he was head of Dyna, is based on the principle that sound reflections from the recording location get mixed into the stereo (front) signal, and these signals being out of phase with the primary direct signal can be easily extracted as a differential signal from the stereo output. Of course, at any given instant the reflections might be in phase with the program material, just as the direct stereo signal might be out of phase. In a listening test you can hear in the rear speakers what appears to be the ambient sound of the recording location as well as direct stereo information. In particular, a recording made at a live concert in Carnegie Hall does recreate in the rear speakers the noise of the audience—shouts and claps—which cannot be discerned in a straight stereo playback.

But as for “matching” the QS matrix, that is another story. Figures 13 and 14 show the 4-channel output of SQ and QS recordings. (The program material is exactly the same as in Figs. 4 through 9. Both the SQ and QS produce essentially similar 4-channel sound fields; the difference in size being the level from the disc as the amplifier and scope controls were not changed. Note that in both instances the rear channels are totally out of phase, and the sound field in no way resembles that of Figs. 4 through 9. Obviously, the differential decoder does not match either SQ or QS.

Figure 15-a shows the derived ambient (Dyna) 4-channel sound field with the decoder driven equal level all four channels, but one channel at a time to avoid obscuring the pattern with hash. The en-

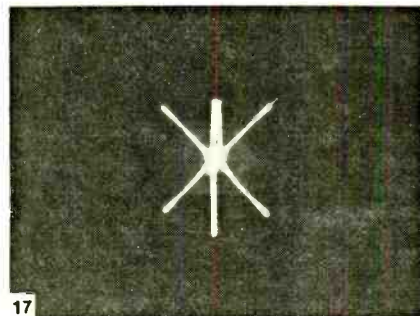


FIG. 17—FULL-LOGIC SQ DECODING is closest to full discrete. Note the “star”.

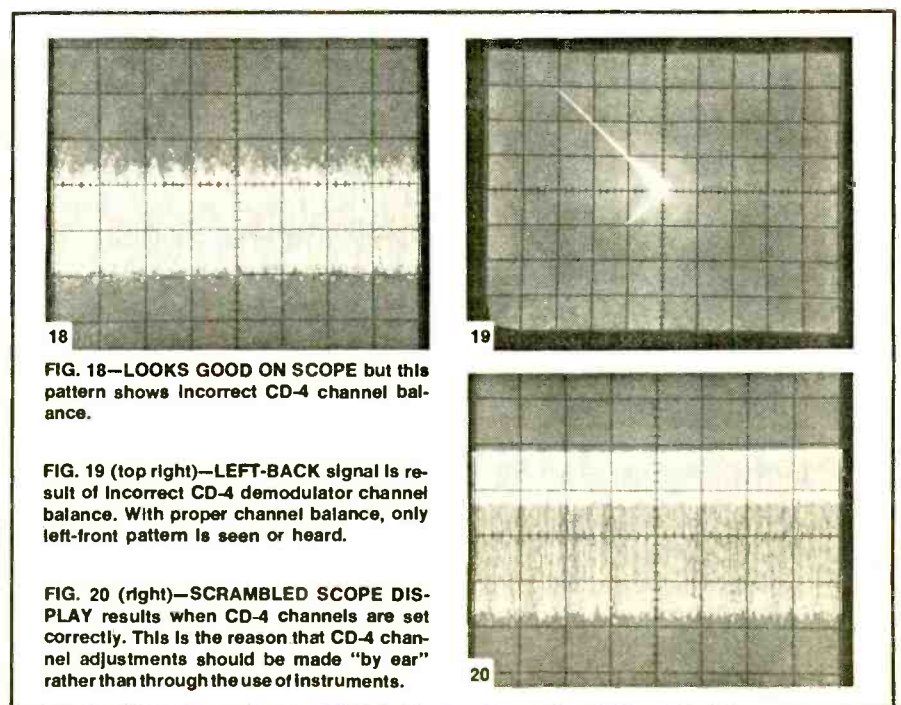


FIG. 18—LOOKS GOOD ON SCOPE but this pattern shows incorrect CD-4 channel balance.

FIG. 19 (top right)—LEFT-BACK signal is result of incorrect CD-4 demodulator channel balance. With proper channel balance, only left-front pattern is seen or heard.

FIG. 20 (right)—SCRAMBLED SCOPE DISPLAY results when CD-4 channels are set correctly. This is the reason that CD-4 channel adjustments should be made “by ear” rather than through the use of instruments.

coding is SQ. The small diagram, Fig. 15-b, shows what each pattern represents. The same idea is shown in Fig. 16 for QS encoding: by stretching the imagination this might be interpreted as "matching" or "approaching" QS decoding, providing one ignores the interchange of RB and LB, and the appearance of these signals out at the sides.

Finally, for those who wonder what takes place when full SQ logic is applied to individual signals we present Fig. 17, the SQ "star" with comers and CF and CR single-frequency test tone. Note the almost complete absence of spill over. Presently, the full-logic SQ decoder is the matrix that comes closest to discrete 4-channel.

It should be obvious that even when matrix decoders are matched to encoders the sound field is not what is claimed by the proponents of each system, at least in production equipment. And intermixing the encoder/decoder is not the horror claimed by some. Sure the sound field and specific performer orientation is changed with matrix intermix, but it can also be changed when the matrices are matched. Is this bad? Is it important for the orientation to be correct? In most instances the answer is *no*. The listener does not know the intended sound field orientation, what the producer intended, hence, what the listener hears will be a pleasurable, dramatic effect. If the record's producer has used the full capabilities of matrix 4-channel his final product is so spectacular compared to standard stereo that variations in performer orientation can only *slightly* diminish or enhance what the producer intended, it cannot destroy the three-dimensional illusion.

In fact, modern records are the results of mix-down, where 8, 16 or more tracks are blended together for a total effect as desired by the producer; it is not natural sound to start with, so why should variations introduced by matrixing make it worse (see *Radio-Electronics*, October 1972, "How 4-Channel Records Are Made"). In short, the limitations of the matrix systems are not those of the system or systems but of the record production itself—the artistry involved in blending the multiple program tracks into a single sound source. This idea is not something to be taken at face value. Try it for yourself. Ask your hi-fi dealer to demonstrate matrix 4-channel with a Project 3 record, and with an open mind, with no preconceived ideas, simply ask yourself: "Is this good?" Most will find it is good.

Compatible, discrete—4 channel, CD-4

In the context of least side-channel signal spill and faithful reproduction of the original sound field the ideal 4-channel system for records is the discrete CD-4.

In very basic terms CD-4 works this way: The LF and LB signals are summed (added together) into a left signal which is recorded in the left groove. The RF and RB signals are similarly summed and recorded in the right groove. The result is a basic stereo recording. But along with each

summed signal there is recorded a 30,000 Hz high-frequency carrier that is frequency and phase modulated with the difference frequencies, LF-LB and RF-RB. In short, each groove closely resembles a stereo FM broadcast in which the main channel carries the sum or mono program while the subcarrier carries the difference information used for converting the signal into stereo.

When a CD-4 record is played with a standard stereo pickup the output is standard stereo—at least according to its proponents. Only when the entire signal, including the high-frequency carriers, is processed through a special demodulator is the stereo signal converted to four independent signal outputs.

Since the high-frequency carriers are modulated +15/-10 kHz the total CD-4 record bandwidth is 30 Hz to 45 kHz, a formidable bandwidth for any pickup to handle. As you can imagine the foremost "bug" in the system was a pickup that could do the job. Another "bug" was record life. The minute high-frequency groove undulations are extremely sensitive to wear, and eventually required a special stylus called a Shibata stylus. This stylus, combined with high compliance, resulted in a pickup capable of tracing the undulations without causing unusually excessive wear. (As of this writing I have cycled a single inner diameter cut 57 times with no noticeable loss in signal quality.)

The CD-4 had many other bugs, most of which were in the recording process and outside the scope of this article. Suffice it to say that based on the sound quality of a CD-4 record now playing in the background these recording bugs have been overcome.

The JVC CD-4 system consists of a model 4MD-20X pickup and a model 4DD-5 demodulator. A pair of special low-capacitance pickup connecting leads are provided which must replace the existing turntable leads. Most all quality turntables—and I say *most* because there must be one somewhere that's an exception to the rule—have plug-in connecting cables. You might have to open the base to get at the plugs

and sockets, but the cables do plug into phono jacks. Empire turntables have their own special plug-in cable and there is an optional adapter available from JVC. An alignment record is also provided.





The demodulator has input jacks for the pickup and four line-level output jacks. There is also a pair of direct-output jacks which provides a direct connection from the pickup. The front panel contains the power switch, a 4-channel indicator called a RADAR and a selector knob with two positions labeled 4CH AUTO and 2CH. When the selector is in the 4CH AUTO position the demodulator automatically senses the 30-kHz carrier and provides 4-channel decoding; the RADAR light is simultaneously turned on to indicate 4-channel output. When a stereo or matrix stereo record is played there is no 30-kHz carrier to turn the demodulator on and the output at the rear connections is standard stereo.

If the selector switch is set to the 2CH position the output is always stereo, even if a CD-4 record is being played. The 2CH selector position is controlled by an ON-OFF switch adjacent to the direct output jacks. When the ON-OFF switch is set to the ON position and the front panel switch is set to 2CH, the pickup's output appears only at the direct-output jacks and can be connected to an amplifier's normal magnetic phono input.

Only three user adjustments are provided: Two on the rear apron labeled L and R and one on the underside labeled 30KHZ LEVEL. The L and R controls determine the front-rear separation, the 30KHZ LEVEL control sets the carrier level into a PLL (phase-locked loop) demodulator and determines the distortion, among other characteristics.

Total user alignment takes about two minutes after the unit is connected and installed, and as far as I can determine the alignment holds, without drift or need for realignment.

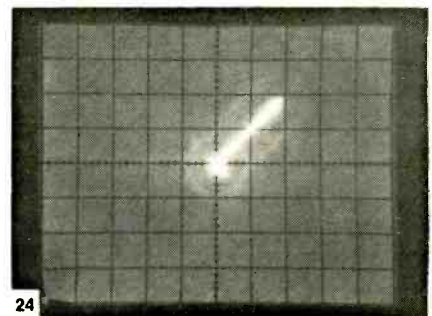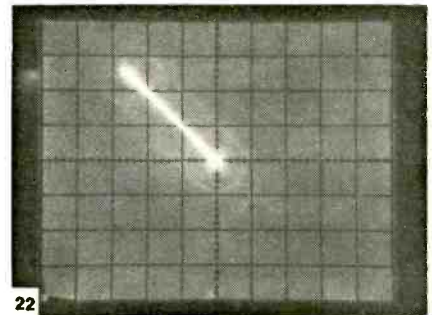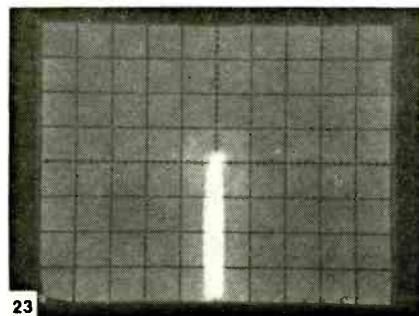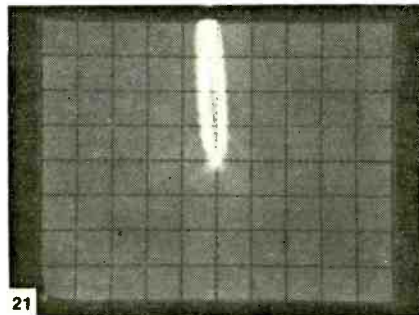The alignment procedure is rather easy. The supplied alignment record has four bands: 1. A warble tone for left channels adjustment; 2. A warble tone for right channels adjustment; 3. Channel identi-



FIGS. 21, 22, 23, 24 (top left to right and bottom left to right, respectively)—INDIVIDUAL QUADRANT CD-4 INPUT SIGNALS show no side-signal spill. Even with 2X gain on center signals, the output is full discrete.

fication (voice) and balancing signal; 4. 400-Hz single tone for carrier-level adjustment. Each band feeds through to the next.

To align the demodulator the user turns down the front-channels' volume controls on the main amplifier or receiver and starts the record. When the left-channels' adjustment tone is heard he adjusts the demodulator's L control for minimum rear signal. Similarly, when the right-channels' tone is heard he adjusts the R control for minimum rear signal. Turning up the amplifier's front volume control allows hearing of the channel identification and balancing signals, which seem a little too fast for me. Finally, when the 400-Hz carrier level tone is heard the detented 30KHZ LEVEL adjustment is set for minimum distortion; and there's really no problem setting for minimum distortion because it snaps rather than fades in and out. One instant there is considerable distortion, the next instant there's little distortion.

I absolutely suggest the adjustments be made "by ear" as specified by JVC, an instrument adjustment can go completely awry as scope indications for CD-4 are the reverse of what one would expect. For example, the "clean" L scope pattern shown in Fig. 18 is incorrect and produces the LB side signal output shown in Fig. 19. The "hash" scope pattern shown in Fig. 20 is the correct L adjustment. The best advice is to follow JVC's instructions as they correlate identically with the results taken from a lab-standard test record.

The test-record scope patterns are shown in Figs. 21 through 24. Even with 2X gain applied to the CF and CB test signals there is virtually no evidence of side-signal spill into adjacent channels; the system is truly discrete.

Figures 25 and 26 show program material sound distribution for proper and improper alignment. Figure 25 is proper alignment, the sound field is predominately LF/RB with considerable in phase LF-CF information. Figure 26, which looks like what many consider a "proper" matrix display (heaven forbid) indicates almost a mono front and imaged mono rear, cause by improper L and R channels adjustment.

Overall CD-4 performance

For proper operation the JVC CD-4 system must be installed and used exactly as specified. The pickup must work into a 100,000-ohm-100-pF load for optimum high-frequency performance. You cannot use extension cables from the pickup other than those available as an option, nor can you use any run-of-the-mill booster amplifier. The pickup's frequency response when operating into its recommended load is shown in the frequency plot, an actual measurement, not figures supplied by the manufacturer. When the pickup is connected to a standard magnetic phono input the performance rolls off 2 dB at 15 kHz, as shown (again measured). As a side note, the pickup's performance on standard stereo records is excellent, comparing favorably with the finest stereo pickups, though it's necessary stylus force of 1.5 to 2 grams is somewhat higher than normally used by top-of-the-line stereo pickups. The higher tracking force is required for CD-4 records.

Had I heard this system with the commercial record releases usually supplied for demonstration I would have been some-

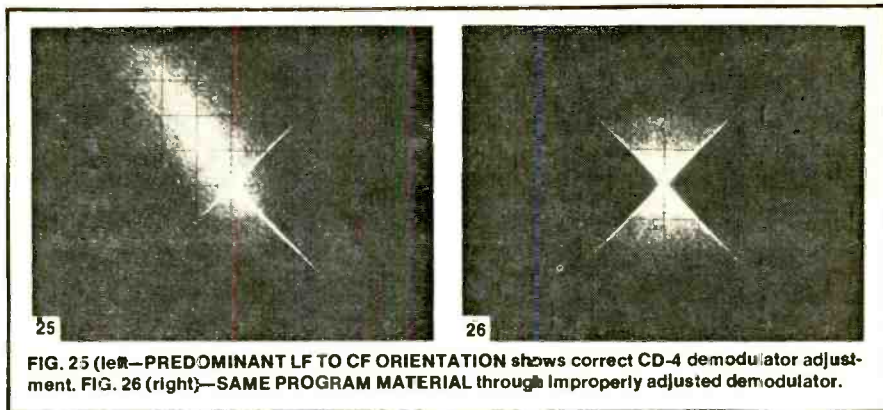


FIG. 25 (left)—PREDOMINANT LF TO CF ORIENTATION shows correct CD-4 demodulator adjustment. FIG. 26 (right)—SAME PROGRAM MATERIAL through improperly adjusted demodulator.

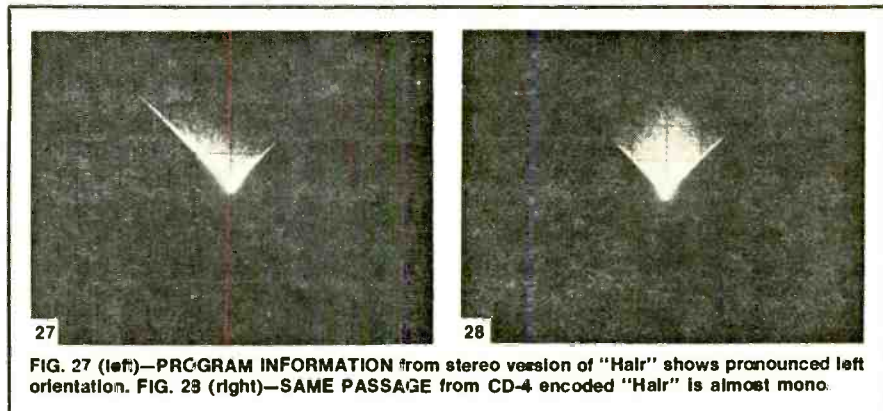


FIG. 27 (left)—PROGRAM INFORMATION from stereo version of "Hair" shows pronounced left orientation. FIG. 28 (right)—SAME PASSAGE from CD-4 encoded "Hair" is almost mono.

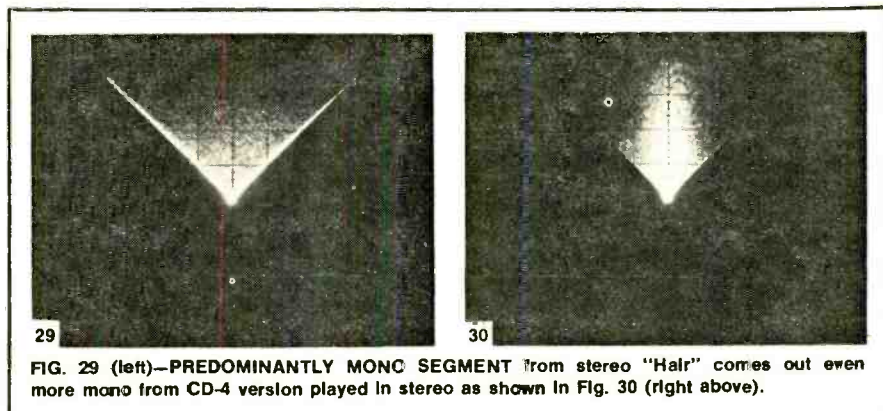


FIG. 29 (left)—PREDOMINANTLY MONO SEGMENT from stereo "Hair" comes out even more mono from CD-4 version played in stereo as shown in Fig. 30 (right above).

what impressed but not necessarily enthused; some of the classical CD-4 releases sound as if they were made 20 years ago when we argued whether we should use one mike 10 feet above the conductor's head or 20 feet above his head and 10 feet back (that sort of nonsense filled endless articles).

Fortunately, as I mentioned way back at the beginning of this discourse on 4-channel, there was this "white box" unlabeled record which turned out to be JVC's private version of the musical show "Hair." Wow, what a recording! Sound so clean it cut like a knife. Total utilization of the available surround-sound possibilities; when "Age of Aquarius" came on it was like the whole sky opened up with sound. A most spectacular and exciting musical adventure. Almost beyond description.

But as with all things, there are always clinkers. Supposedly, the CD-4 records are available with 25 minutes recording time, yet the "Hair" recording had at least two numbers missing, though it is possible they were missing because the record was made

from a master supplied for Q8 4-channel cartridges; the selections might not have been on the cartridge program. No one seems to know.

The second clinker appears to be the "stereo compatibility." If you refer back to Fig. 25 you will note the decided LF sound orientation. Figure 27 is the exact same program information from the RCA stereo version of "Hair," again, note the decided LF orientation. But Fig. 28 shows the same program material from the CD-4 version played back in stereo—the sound orientation is primarily CF, it is not the equal of the stereo version.

Now it is quite possible that JVC mixed down the tracks for optimum surround-sound effects, and there is no question they succeeded in turning out a superlative recording, but does utilization of the total 4-channel capacity preclude optimum of even good stereo reproduction? Presently, there is no way to tackle this question because there is virtually nothing to work with, only in the "Hair" recordings
(continued on page 82)

SPEED TROUBLESHOOTING

Every service technician uses some that ranges from a scatter-brained system of signal tracing or inject-

by JONATHAN L. TURINO

LAST MONTH, IN THE FIRST ARTICLE of this troubleshooting series, we talked about the first steps in fixing anything. The hardware (test equipment) was discussed, the software was defined, and the admonition to "check the simple things first" was presented.

We have checked all of the usual "simple" things (including the power supply) and find that we still have a non-operating piece of equipment facing us. How do we troubleshoot it?

There are as many troubleshooting techniques as there are people who troubleshoot. The only

one that should be avoided at all costs is the "shotgun" technique. It is time consuming and component consuming, and will not be discussed any further.

Of the reasonably efficient methods of troubleshooting, the one in most widespread use is probably stage-by-stage signal tracing (or signal injecting). You start at one end of the equipment and check each stage, in order, to isolate the defective "block" of the equipment. This method is logical and effective, but it can be improved upon. The improvement leads to what we described as the best troubleshooting method in existence—"cut it in half."

Look at the sample block diagram in Fig. 1. If we use the usual troubleshooting method, and our first two steps are the verification of the input and output devices, it can take a total of seven steps to isolate the non-functioning stage, whether we check from input to output or output to input, assuming that the last stage we check is the defective one. If, however, we apply cut-it-in-half troubleshooting, the maximum number of steps we need (including the verification of input and output) is five. Here is how the cut-it-in-half method works:

We have a known good input to Stage 1 (Fig. 1) and no output from Stage 6. The next measurement should be made *in the middle*, between stages 3 and 4. This immediately eliminates half of the stages. Suppose we find a normal signal at that point. Next, measure half way between Stage 4 and Stage 6. In this example we would measure at the input or output of Stage 5 (since the middle of three


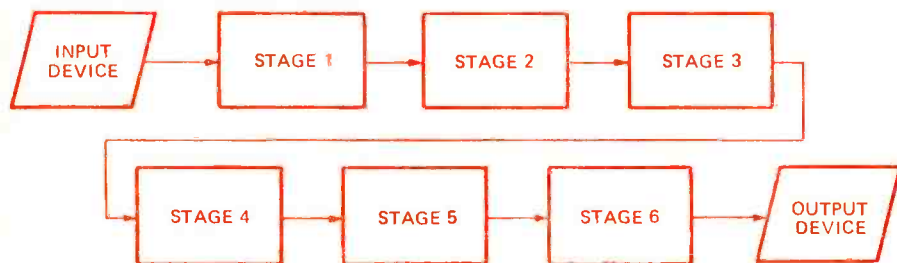
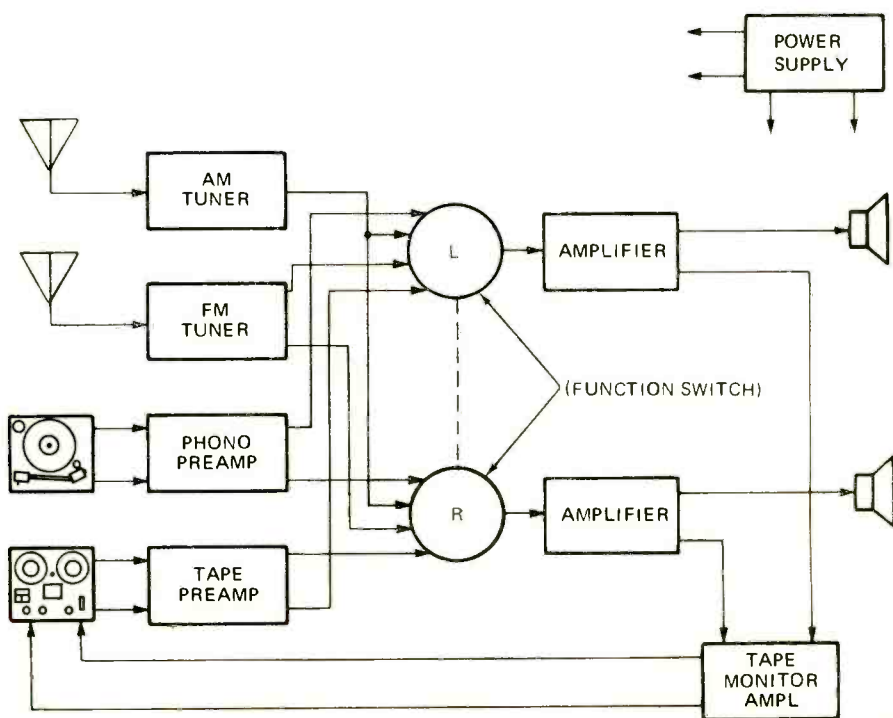


FIG. 1 (above)—SIMPLE BLOCK DIAGRAM that can be applied when servicing any type of electronic device ranging from audio, video and rf amplifiers to receivers, computers and various types of test instruments.

FIG. 2 (below)—EFFICIENCY of cut-it-in-half troubleshooting is illustrated by comparing its curve with that of step-by-step method.

FIG. 3—(right)—TYPICAL AM-FM STEREO RECEIVER is illustrated in this block diagram. Cut-it-in-half troubleshooting leads you to the seat of the trouble in record time.

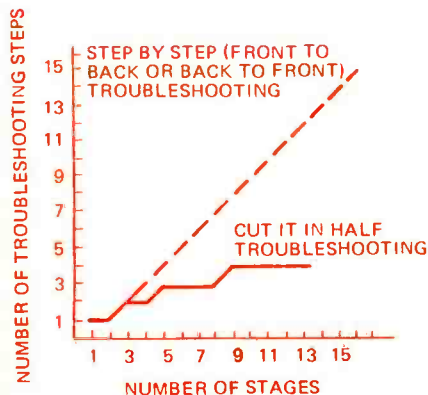

With A Logical Approach

form of troubleshooting procedure
hit-or-miss scheme to a methodical
ion. Won't you try the ultimate method?

stages is a little difficult to find). Regardless of the outcome of this measurement there remains only one measurement to completely pinpoint the defective stage. The cut-it-in-half troubleshooting method eliminated two steps in this simple example. Just to prove that is is *the* most efficient way to troubleshoot, look at the graphs in Fig. 2. The number of measurements is plotted against the number of stages in a device. The outcome is obvious—the more complex the piece of equipment to be repaired, the more efficient cut-it-in-half troubleshooting is.

Now that this point has been made (and even a little belabored!) let's apply the cut-it-in-half technique to the repair of an AM-FM stereo receiver. Using just a block diagram (see Fig. 3), a set of symptoms, and the front panel indications (sound from the speakers in this case), we can do a lot of fault isolation without even removing the back of the instrument.

Let's start with the obvious one—completely dead on all functions. Where do we check first? The power supply, of course. How about no sound from the left channel on all

functions? The left amplifier is the obvious answer, but before jumping to that conclusion, it would be better to see if both channels use a common power supply or whether there is a separate one for each channel (and maybe a third section for the low level stages!) There are a host of other possible symptoms and faulty sections in the receiver shown in Fig. 3, but with the block diagram, your eyes and ears, and a logical approach you can isolate down to a section without even taking an electrical measurement. The three examples that follow should serve to illustrate the kind of approach we are talking about.

Example 1—The left channel is dead on all functions. Check the speaker connections. Check the power supply (as was discussed previously). If both are all right, the problem is in the left amplifier.

Example 2—The FM tuner is dead on both channels. A little obvious, maybe, but check the antenna, the selector switch and the power supply before digging into the tuner (which is the most likely trouble.)

Example 3—Everything works

except that one channel will not record on the tape recorder unless microphones are used. Check the cabling between the receiver and the tape deck. If that is all right, the problem is probably in the tape monitor amplifier. (If it was the recorder it probably would not work with the microphones.)

You can see now why a block diagram approach has been stressed as the only way to avoid being buried in complex circuitry before you isolate the defective stage in a piece of equipment. Checking the simple things first, taking everything into account, proceeding logically, and being ready to abandon a wrong guess is a sure-fire troubleshooting approach. When the defective section has been determined, go to cut-it-in-half troubleshooting to find the defective stage in the shortest possible time.

There are some things that make troubleshooting something like a stereo receiver a little easier. If the symptom is common to one channel, you can interchange connectors (and even components, in some cases) when you think you have found a bad one, to quickly determine what things are and are not at fault. When you get down to the circuitry part of the troubleshooting you can compare the readings in the non-operating channel with the readings in the operating channel to verify your diagnosis. (This is particularly helpful when the schematic does not give voltage readings for normal operation.)

By now you should be well on your way to being an expert logical troubleshooter (no "shotgunning"). To test your knowledge there is a quiz for the block diagram shown in Fig. 4. Just mark your answers in the blanks and mark the number that identifies the step you would perform next in the blank for "your next step."

The answers to the quiz, some troubleshooting of a digital counter and an electronic organ, and an explanation of how the logical troubleshooting method applies to circuitry (tube and transistor) will appear next month.

R-E

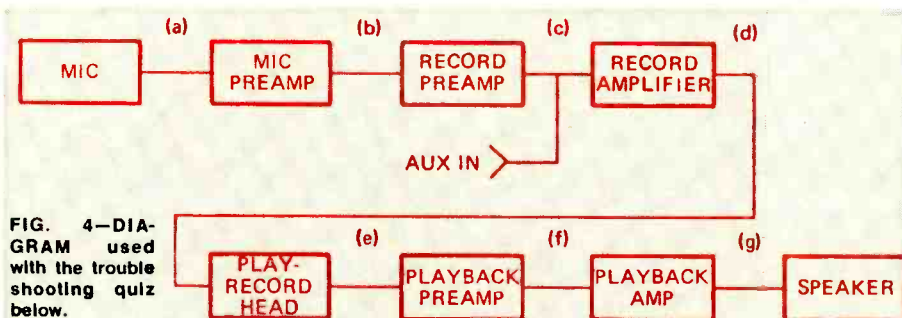


FIG. 4—DIAGRAM used with the troubleshooting quiz below.

The block diagram above shows one half of a stereo tape recorder (both channels the same). The recorder plays pre-recorded tapes properly, but one channel sounds very garbled when recording.

After switching microphones to eliminate the obvious possibility, applying cut-it-in-half troubleshooting, you would first inject a signal at point _____. The symptom with a signal injected at the above point is the same as the original symptom. Your first measurement (using

a scope or signal tracer) should be at point _____.

Assume that this measurement shows a defective signal. Your next step would be to _____:

- (1) Replace the tape head.
- (2) Use cut-it-in-half troubleshooting in the mic preamp.
- (3) Use cut-it-in-half troubleshooting in the record amp.
- (4) Troubleshoot playback preamp.
- (5) Check the recorder power supply fuse.

the state of

SOLID STATE

Optoelectronic technology is growing and new devices are announced almost daily. Many of these spearhead this month's column

by LOU GARNER
SEMICONDUCTOR EDITOR

WILL OPTOELECTRONICS EVER BECOME a household word? Perhaps not in the near future, but solid-state optoelectronic devices are being used in ever-larger numbers in test instruments, calculators, consumer products, automotive applications, medical equipment and communications gear, as well as in computers, aircraft and military equipment. Long life, relatively low cost, low power requirements, and amazing versatility are among the many factors contributing to the increasing popularity of these interesting devices.

The solid-state optoelectronic family includes light-emitting diodes (LED's), injection-diode lasers, photosensors (such as photodiodes, phototransistors, and IC devices comprising photodetectors and integral amplifiers), numeric and alphanumeric displays, and photo-couplers.

Long life? You'd better believe it! Although not enough time has passed since these devices were first developed to accumulate factual life data, accelerated tests by major semiconductor manufacturers indicate that a LED used within its ratings should have a useful operating life of 300,000 hours, or more, to its half-brightness point. Playing it safe, some manufacturers claim a life of only 100,000 hours.

If we accept the lower figure, a LED used in a piece of equipment operated 8 hours a day, 5 days a week, 50 weeks a year, would provide 50 years of operation before a replacement would be needed. While, with the higher figure, one would have a 150-year life expectancy. Even if the equipment were operated 24 hours a day continuously, 365 days each year, the life expectancy would still be over 34 years!

Low cost? Cost, of course, is a relative term—what is considered expensive in one application may be dirt cheap in another. But optoelectronic device prices have dropped considerably since they were first introduced. Within the last few months, for example, Hewlett Packard (1501 Page Mill Road, Palo Alto, Calif. 94304) introduced two new LED's; types 5082-4850 and 5082-4484. They are available for only 17 cents each in production quantities (100,000 up).

Intended for high-volume applications in appliances, automobile instrument panels and similar commercial equipment, the two new HP devices require only 20 mA at 1.6 volts for operation and furnish visible red light.

Low power? Absolutely! Actual power requirements vary with individual devices and applications, naturally, but average values may range from microwatts for photodetectors with integral IC amplifiers to the upper milliwatt levels for LED's, numeric displays, and photo-couplers. HP's 5082-7400 family of numeric indicators, typically, can provide excellent readability at power levels of only 7 mW per digit.

Versatility? Unfortunately, space limitations prohibit a detailed listing of all possible optoelectronic equipment applications, but LED's, alone, may be used as pilot lamps, polarity and logic-level indicators, on-board circuit monitors, warning signals; and, with turn-on and turn-off times in the nanosecond region, as modulated-light communication transmitters.

At a recent optoelectronic seminar, one firm's engineers described an experimental light communications system using a 5-MHz modulated carrier. Conventional LED's (not lasers) were used in the transmitters, and standard photodiodes and high-gain IC amplifiers in the receivers, with six-inch diameter lenses for light focusing and beam concentration. According to the report, excellent results were obtained at ranges of up to two miles in full daylight and even during rainy periods.

Several exciting new optoelectronic devices have been introduced by major semiconductor manufacturers within recent weeks, including two visible red light LED's, an unusual pnpn switch/LED, green LED's and readouts, a pair of medium voltage LED's, a family of intriguing dual LED's, and an inexpensive two-digit numeric display.

Designated types RL-4403 and RL-4440, the new full-flood red LED's, Fig. 1, are offered by Litronix, Inc. (19000 Homestead Road, Cupertino, Calif. 95014). Intended for control panel and instrument

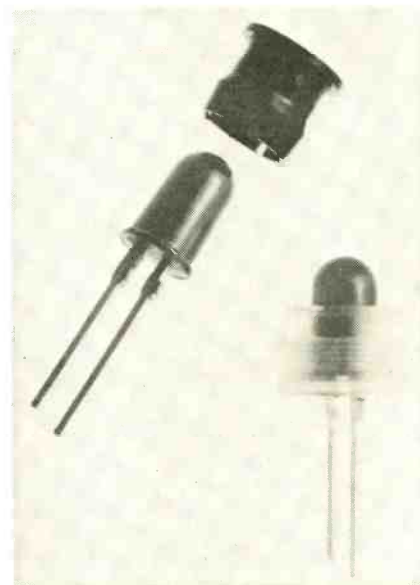


FIG. 1—FULL FLOOD LED LAMPS available from Litronix, Inc.

applications, both devices use gallium-arsenide-phosphide diodes assembled in specially designed red-diffusive molded plastic packages and require 20 mA at 1.7 volts for operation. The two units differ only in average brightness and cost, with the brighter RL-4403 somewhat more expensive than the lower rated RL-4440. Both, however, are priced at less than a dollar each in moderate production quantities. (Full-flood LED's are those in which a lens spreads the tiny spot of light from the chip over the entire viewing surface of the device.)

An interesting LED introduced by Japan's Sharp Corporation uses a four-layer pnpn structure that gives it thyristor-like fast switching properties, a comparatively high reverse breakdown voltage, and a negative resistance slope in its characteristics curve, as illustrated in Fig. 2. The new device, type GND-50G, emits infrared light that is converted into visible green light by a fluorescent phosphor coating. Sharp's

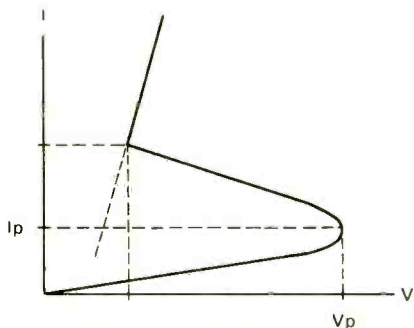


FIG. 2—NEGATIVE RESISTANCE characteristic of new Sharp GND-50G pnpn LED.

U.S. distributor is Shigoto Industries, Ltd. (Empire State Building, New York, N.Y. 10001).

Green LED's as well as numeric displays also are being offered by Opcoa (330 Talmadge Road, Edison, N.J. 08817). As predicted in our January column, prices are roughly competitive with conventional red LED's, with the green light devices priced at less than a dollar each in medium large quantities (100 up).

Designed to operate on less than 2 volts (typically, 1.5 to 1.7 volts), conventional LED's require external voltage dropping resistors when used in higher voltage applications. Recognizing this limitation, Hewlett-Packard has developed a pair of red LED's with integral IC-type resistors to permit direct operation on 5-volt dc sources, thus making the devices fully compatible with standard TTL circuitry. The new LED's, types 5082-4860 and 5082-4468, are offered in T-1 $\frac{1}{4}$ and T-1 size cases, respectively, and require a nominal 16 mA for operation.

Monsanto (Electronic Special Products, 10131 Bubb Road, Cupertino, Calif. 95014) has fulfilled another of our January predictions with their introduction of a device that emits red light at one voltage and green light at a higher voltage (with reversed polarity).

The new Monsanto device, type MV 5491, actually consists of two parallel anode-to-cathode LED's in a single package, one emitting red light, the other green light (see Fig. 3). The red LED is a gallium-arsenide-phosphide diode, the green

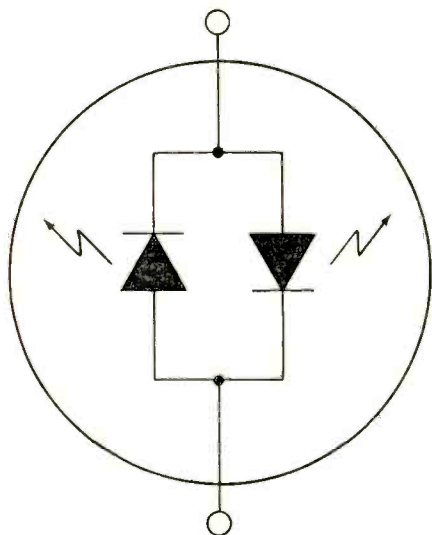


FIG. 3—SCHEMATIC OF MONSANTO'S new dual LED devices.

LED is a gallium-phosphide unit. The MV 5491 is one of a family of dual LED devices; other types are: the MV 5094, comprising two red LED's and intended for ac or dc operation, the MV 5591, a red/yellow pair, the MV 5691, a yellow/green pair, the MV 5291, a dual green pair for ac, and the MV 5391, a dual yellow pair for ac applications. In operation, the basic red/green type, MV 5491, requires 1.65 volts at 20 mA to activate the red LED, 2.3 volts at 20 mA with reversed polarity to activate the green LED.

Illustrated in Fig. 4, is a new two-digit solid-state numeric readout announced by Litronix, Inc. Designated type DL-44, the

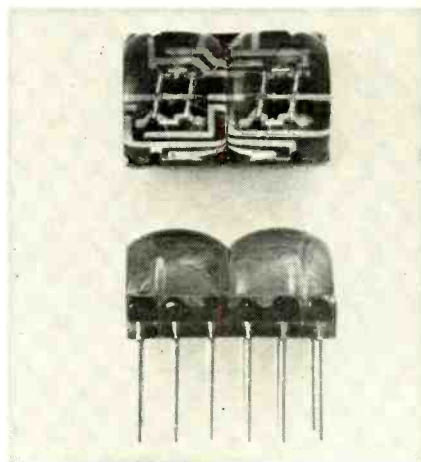


FIG. 4—LITRONIX TWO DIGIT LED module with integral magnifying lens.

new device has 0.19 inch high characters and is equipped with an integral plastic magnifying lens. Exhibiting a brightness of 250 ft-L at a current of only 5 mA per segment, the DL-44 is assembled in a standard 12-pin dual-inline package and nets for just \$4.25 per digit in unit quantities. It is designed primarily for applications in low-cost equipment using multiplex drive systems.

Optical couplers

Known, variously, as opto-couplers, opto isolators, photon-couplers, light couplers, and perhaps, by a few other names, depending on each manufacturer's individual preference, optical couplers are a comparatively new class of optoelectronic devices.

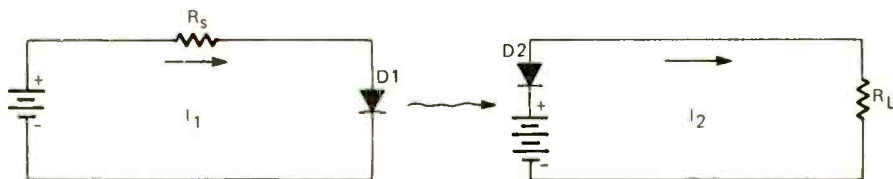


FIG. 5—BASIC ARRANGEMENT OF AN OPTICAL coupler—a LED (D1) and a photodiode (D2) coupled by a light beam.

Used primarily for interface applications between circuits, lines and sub-systems where maximum isolation is needed, they provide many times the isolation that is possible with capacitive or transformer coupling, and are used extensively in digital and analog computers, in data communications equipment, and in control systems.

As shown in Fig. 5, the basic optical coupler consists of an electrical light source, such as LED D1, and a light sensor, such as photodiode D2, arranged so that light

from the source falls on the sensor and, usually, so that external light is excluded. Variations in the signal power applied to the source cause changes in its emitted light and, therefore, corresponding changes in the signal developed by the sensor. The only coupling between the source and the sensor, other than an extremely small capacitance (typically, less than 5 pF and, often, a fraction of a pF), is through the light beam or, more precisely, through the photons of energy making up the light (hence one of the names for the device).

Physically, the LED and its corresponding sensor generally are mounted in a standard TO or DIP type case with a thin film of special plastic between them, as in Fig. 6. This plastic film serves both to furnish a light path and to provide high voltage electrical insulation. A number of


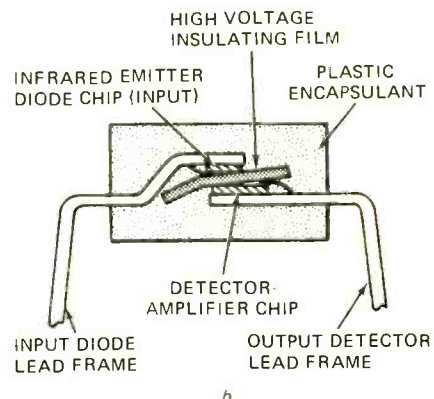
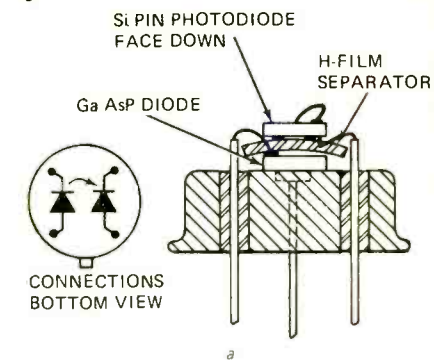


FIG. 6—CROSS-SECTION SKETCHES showing the internal construction of TO-type (a) and DIP-type (b) optical couplers.

variations of the basic design are found in commercially available devices.

A phototransistor or photo-Darlington may be used in place of the photodiode, for example, or, if only a simple switching action is desired, a light sensitive SCR may be used as the output device. In other commercial designs, a photodiode may be used in conjunction with an integral transistor, a Darlington pair, or even an integrated circuit amplifier chip.

(continued on page 68)

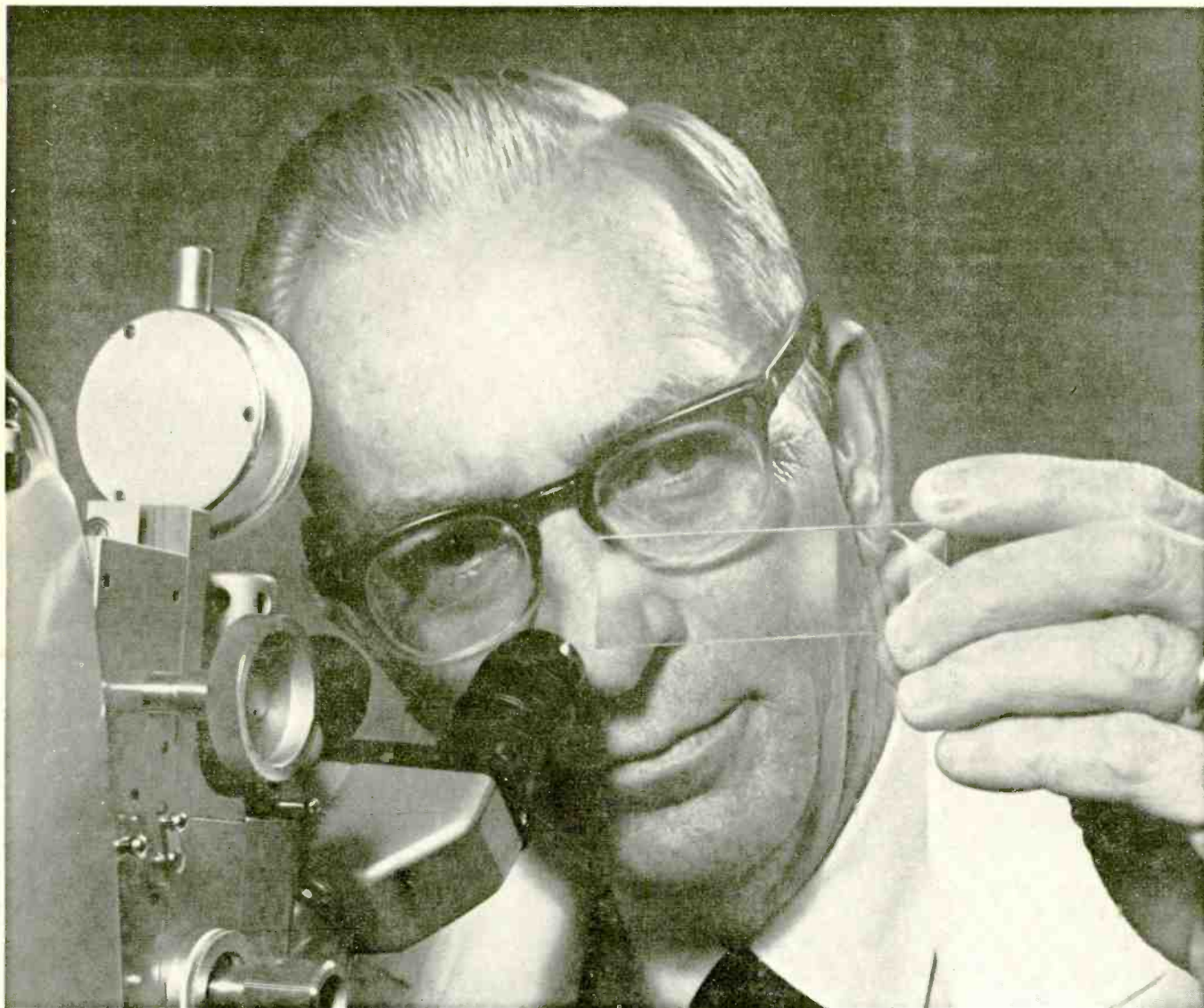

NTS Home-Training in Electronics was the start of something big for James Gupton

An NTS Graduate

James A. Gupton Jr. graduated from National Technical Schools with a diploma in TV & Radio Servicing. Today, he's a mighty important man in the world of Electronics!

Research associate with a major electronics corporation; author of numerous articles in electronics magazines; an inventor with five patent applications to his credit. In the field of electro-optics, he has perfected a revolutionary phosphor deposition technique for cathode ray tubes.

Quite a list of accomplish-

ments for a man who began his career with an NTS diploma and a job in TV & Radio servicing.

Any student can succeed

James Gupton is certainly an exceptional NTS graduate. He proves there's nothing to keep a determined man from becoming a success in Electronics. As he himself says, "Any student, properly motivated, can succeed in Electronics through home-training."

Every NTS Electronics Course is specially designed to keep you motivated from the time you

start building your first test instrument until you're ready to plug-in your solid-state Color TV or other advanced electronics equipment.

Exciting "Project Method" Training

NTS Project Method Training is the best way to learn electronics.

You build advanced equipment while you learn Electronics principles and applications.

Each week brings new excitement when you actually see the progress you've made.

NTS builds self-confidence.

For a man to become successful, like James Gupton, he must have confidence in himself.

As an NTS graduate you have this confidence. Your training is practical and thorough. You know Electronics from the bottom up. You enter a world of Electronics you're familiar with.

And if you have the drive and determination of a man like James Gupton, there are no limits on your success!

(James Gupton's address available upon request).

NTS COLOR TV SERVICING




Solid-state
315 sq. in.
Heath Color TV

Build and keep the largest, most advanced color TV made! Over-all solid-state design, ultra-rectangular screen, matrix picture tube, built-in self-servicing features, "Instant On," A.F.T., solid-state, 24-channel detent UHF/VHF power tuning, and much more! Also build and keep AM-SW Radio, solid-state Radio, FET Volt-Ohmmeter, and Electronic Tube Tester. Learn trouble-shooting, hi-fi, stereo, multiplex systems, radio, color and B&W TV servicing.

NTS B&W TV SERVICING

Learn sophisticated solid-state circuitry as you build this B&W TV Receiver, Lo-Silho "Superhet" Radio, FET Volt-Ohmmeter, solid-state Radio, Electronic Tube

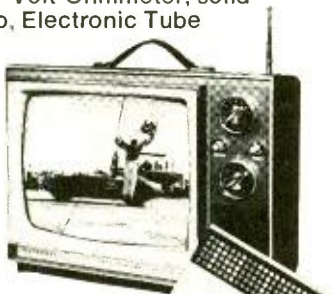Solid-state
B&W TV,
74 sq. in.
picture
cabinet
included



Checker, and Signal Generator. TV and all other equipment are yours to keep.

NTS ELECTRONIC & COMPUTER TECHNOLOGY

Solid-state Compu-Trainer 14 integrated circuits replace 198 Transistors!



Build and keep this exclusive NTS Compu-Trainer. It teaches you the same principles used in million-dollar systems. Contains 14 integrated circuits! All solid-state! You perform all wiring and patchcording. No shortcuts. No pre-wired circuit boards. Your training is complete! Also receive a FET Volt-Ohmmeter and a 5" wide-band solid-state Oscilloscope.

NTS ELECTRONIC COMMUNICATIONS

Gain the prestige and earning power of owning and F.C.C. First Class Radio-Telephone license. Two comprehensive NTS Courses cover the big opportunity field of transmitting and receiving.



5-watt AM
Transmitter/
Receiver

You build and keep 14 kits, including this amateur phone 6-meter VHF Transceiver, NTS's exclusive 6-transistor solid-state Radio, and a fully transistorized Volt-Ohmmeter. Also, learn 2-way radio, Citizens Band Microwaves, and radar.

NTS INDUSTRIAL & AUTOMATION ELECTRONICS

Automation is the future of industry, and you can play an important part! Learn industrial controls by training on the NTS Electro-Lab (a complete workshop). You also build and operate this 5" solid-state


oscilloscope. And you perform experiments that involve regulating motor speeds, temperature, pressure, liquid level, and much more. All equipment is yours to keep.



All solid-state!

NTS AUDIO ELECTRONICS SERVICING

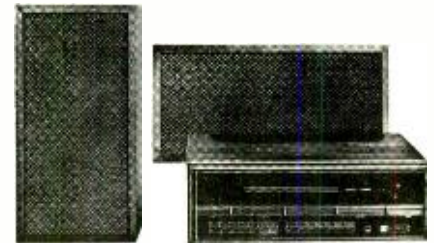Learn sound theory — how it works in home radio, car tape decks, stereo multiplex component systems, and more! Set up a spectacular music system. Learn about sound distortion, amplification and control, loud-speaker baffles, problems of system installation, etc.



Build and keep this famous Heath Stereo Receiver and Speakers

Included is Volt-Ohmmeter, In-Circuit Transistor Tester and solid-state Radio. Prepare yourself for great opportunities in the Home Entertainment Industry!

CLASSROOM TRAINING AT LOS ANGELES

You can take classroom training at Los Angeles in sunny Southern California. NTS occupies a city block with over a million dollars in technical facilities. Check box in coupon below.

APPROVED FOR VETERAN TRAINING

Accredited Member: National Association of Trade and Technical Schools; National Home Study Council.

NATIONAL TECHNICAL SCHOOLS

World-Wide Training Since 1905
Resident & Home Study Schools
4000 S. Figueroa St., Los Angeles, Ca. 90037

Dept. 206-053

Big, Colorful NTS Guide to new opportunities in Electronics. Yours FREE!

NATIONAL TECHNICAL SCHOOLS
4000 S. Figueroa Street
Los Angeles, California 90037

Please rush me FREE Color NTS Electronics Guide & FREE lesson, plus information on course checked at right. No obligation. No salesman will call.

- MASTER COURSE IN COLOR TV SERVICING
- COLOR TV SERVICING (FOR ADVANCED TECHNICIANS)
- MASTER COURSE IN B&W TV & RADIO SERVICING
- MASTER COURSE IN ELECTRONIC COMMUNICATIONS
- PRACTICAL RADIO SERVICING
- FCC LICENSE COURSE
- MASTER COURSE IN ELECTRONICS TECHNOLOGY
- AUTOMATION & INDUSTRIAL ELECTRONICS
- COMPUTER ELECTRONICS
- BASIC ELECTRONICS
- AUDIO ELECTRONICS SERVICING

NAME _____ AGE _____

ADDRESS _____

CITY _____

STATE _____ ZIP _____

- Check if interested in Veterans Training under new G.I. Bill.
- Check if interested ONLY in Classroom Training at Los Angeles

Three 8-input digital multiplexers featuring Schottky-diode-clamped TTL structures are now available from Signetics (811 East Arques Ave., Sunnyvale, Calif. 94086). The 8-input digital multiplexer is the logical equivalent of a single-pole, 8-position switch whose position is specified by a 3-bit input address.

Type numbers for the new devices are 82S30, 82S31 and 82S32. The three devices are similar except for their exact output configuration and/or the effect of their INHIBIT inputs on output. Requiring a 5-volt dc power source, all three are furnished in plastic dual-in-line packages and all are fully compatible with standard TTL circuits, including devices in the various 54/74 series.

Texas Instruments, Inc. (P.O. Box 5012, M/S 308, Dallas, Tex. 75222) has announced a number of new devices, including three npn/pnp Darlington power transistor complementary pairs and seven npn high-voltage power transistors.

Illustrated in Fig. 7, the new power

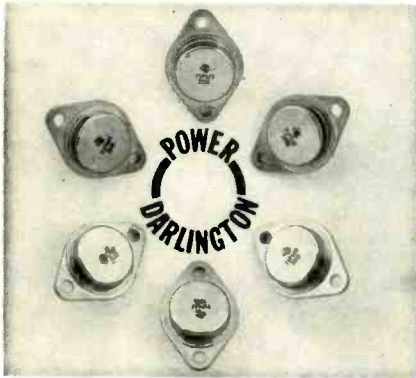


FIG. 7—NEW SERIES of complementary power Darlington.

Darlington transistors include npn types TIP620, TIP621, and TIP622, while the complementary pnp types are designated the TIP625, TIP626, and TIP627. The collector-emitter breakdown voltages for the TIP620 and TIP625 is 60 volts, for the TIP621 and the TIP625, 80 volts, and for the TIP622 and TIP627, 100 volts. Collector current for each is 5 amperes, with a rated gain of 1000 at a V_{CE} of 3 volts and a I_C of 3 amperes. All have a specified power dissipation of 100 watts at 25°C and all are furnished in standard TO-3 metal packages.

TI's new family of npn high-voltage transistors is identified as types TIP55 through TIP58 and types TIP554 through

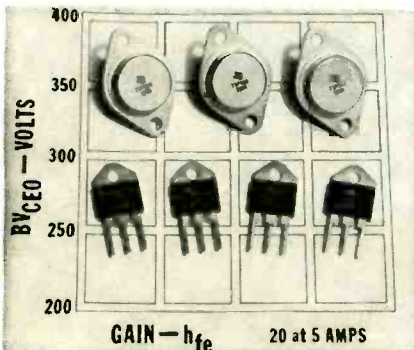


FIG. 8—HIGH-VOLTAGE power transistors now available from Texas Instruments, Inc.

TIP556. The first four are supplied in economical plastic packages, the last three in standard TO-3 metal cans, as shown in Fig. 8. Minimum collector-emitter breakdown voltages for the TIP55, 56, 57 and 58 are 250, 300, 350, and 400 volts, respectively, while for the TIP554, 555, and 556, they are 200, 300, and 400 volts. All have rated power dissipation of 125 watts at 25°C. Maximum collector currents are 7.5 amperes for types TIP55 through 58 and 5.0 amperes for types TIP554 through 556. For all, f_T is 10 MHz minimum at 10 volts and 0.2 amperes.

IC Multiplier-divider

A new self-contained IC multiplier/divider has been introduced by the Burr-Brown Research Corporation (International Airport Industrial Park, Tucson, Ariz. 85706). Hermetically sealed and internally laser trimmed in a TO-100 package, the device, type 4203K, requires no external components to deliver a guaranteed accuracy of 1%. In addition to division and four-quadrant multiplication, square-rooting also may be performed.

Illustrated in Fig. 9, the 4203 has a 1-

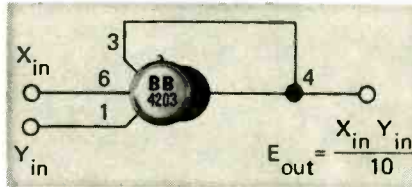


FIG. 9—BURR-BROWN'S MODEL 4203 self-contained IC multiplier/divider.

MHz bandwidth and a slew rate of 25 V/ μ sec. As a companion unit, Burr-Brown also is offering the less expensive type 4201J. This model handles all the functions of the basic unit, but requires four external trim-pots for adjustment of offset voltage and gain (i.e., scale factor). With external trim, the 4201J provides 2% accuracy.

Both units contain their own Zener-regulated references to reduce sensitivity to supply voltage variations, and both feature the same slew rate and bandwidth. Rated output of both is $\pm 10V$ at ± 5 mA. Output impedance is 1 ohm and output noise, from 10 KHz to 10 MHz, is a low 3 mV, rms. A supply voltage of from $\pm 12V$ dc to $\pm 18V$ dc is required, with the quiescent current for the 4201J a low ± 4 mA, and ± 9 mA for the 4203K. The rated temperature range for the units is 0° to +70°C. Single quantity prices are \$22.50 for the 4201J and \$39.00 for the 4203K.

Six 10-ampere commercial npn Darlington transistors and their developmental pnp complements have been announced by RCA's Solid State Division (Route 202, Somerville, N.J. 08876). Designated types 2N6383, 2N6384, and 2N6385, and rated at 40, 60 and 80 volts V_{CE0} respectively, with 100 watts dissipation, the first device family is supplied in a JEDEC TO-3 package.

Types 2N6386, 2N6387 and 2N6388 all offer similar voltage ratings and performance, but only 40 watts dissipation and come in the RCA Versawatt package. The developmental pnp complements are designated types TA8351, TA8488, and TA8350 for the 40, 60 and 80-volt devices in the TO-3 package and types TA8204, TA-8487,

and TA8203 in the Versawatt package. All devices feature a minimum gain of 1000 at 5 A, except for types 2N6386 and TA8204, which have a minimum gain of 1000 at 3 A.

Motorola has recently announced two significant advances—the introduction of economical plastic-packaged devices to their previous all ceramic-package CMOS line and the addition of nine new functional devices. The plastic-packaged devices will be priced 10% or more lower than the ceramics. The new CMOS devices are the MC14034 8-bit universal bus register, the MC14511 BCD-to-seven segment latch/decoder/driver, the MC14517 dual 64-bit static shift register, the MC14528 dual retriggerable/resettable monostable multivibrator, the MC14529 dual 4-channel analog switch or 8-channel analog data selector, the MC14530 dual 5-input majority logic gate, the MC14531 12-bit parity tree, the MC14581 4-bit arithmetic logic unit, and the MC14582 look-ahead carry block.

National Semiconductor has added five new 54C/74C devices and two new CD4000/MM4600 parts to its CMOS line, bringing to 20 the number of devices in its 54C/74C line and to 11 the items offered in its CD4000/MM4600 series. The new devices are the 74C42N BCD-to-decimal decoder, the 74C95N four-bit shift register (parallel), the 74C151N eight-bit data selector (MUX), the 74C173N quad latch with Tri-State outputs, the 74C900 quad bi-lateral switch, the CD4016/MM4616 quad bi-lateral switch, and the CD4035/MM4635 four-bit shift register (parallel). R-E

R-E's substitution guide for replacement transistors

Part III

compiled by ROBERT & ELIZABETH SCOTT

R-E's Transistor Substitution Guide is a compilation of material abstracted from the substitution guides of eight leading semiconductor manufacturers and distributors. These are:

- ARCH—Indicates the Archer brand of semiconductors sold only by Radio Shack and Allied Radio stores. Allied Radio Shack, 2725 W. 7th St., Ft. Worth, Texas 76107
- G-E—General Electric Co., Tube Product Div., Owensboro, Ky. 42301
- IR—International Rectifier, Semiconductor Div., 233 Kansas St., El Segundo, Calif. 90245
- MAL—Mallory Distributor Products Co., 101 S. Parker, Indianapolis, Ind. 46201
- MOT—Motorola Semiconductors, Box 2963, Phoenix, Ariz. 85036
- RCA—RCA Electronic Components, Harrison, N.J. 07029
- SPR—Sprague Products Co., 65 Marshall St., North Adams, Mass. 01247
- SYL—Sylvania Electric Corp., 100 1st Ave., Waltham, Mass. 02154

Radio-Electronics has done its utmost to insure that the listings in this directory are as accurate and reliable as possible; however, no responsibility is assumed by Radio-Electronics for its use. We have used the latest manufacturers material available to us and have asked each manufacturer covered in the listing to check its accuracy. Where we have been supplied with corrections, we have updated the listing to include them. The first part of this Guide appeared in March 1973.

ARCH G-E IR MAL MOT RCA SPR SYL

ARCH	G-E	IR	MAL	MOT	RCA	SPR	SYL	
2N447	RS276-2001	GE-5	TR-08	PTC 108	HEP-641	SK 3011	RT-119	ECG 101
2N448	RS276-2001	GE-7	TR-08	PTC 108	HEP-641	SK 3011	RT-119	ECG 101
2N449	RS276-2001	GE-7	TR-08	PTC 108	HEP-641	SK 3011	RT-119	ECG 101
2N450	RS276-2005	GE-1	IRTR-85	PTC 109	HEP-2	SK 3006	RT-118	ECG 100
2N451	NA	NA	NA	NA	HEP-S5003	NA	NA	NA
2N452	NA	NA	NA	NA	HEP-S5003	NA	NA	NA
2N453	NA	NA	NA	NA	HEP-701	NA	NA	NA
2N454	NA	NA	NA	NA	HEP-S5003	NA	NA	NA
2N455	RS276-2006	GE-16	TR-01	PTC 122	HEP-2307232	SK 3009	RT-124	ECG 104
2N456	RS276-2006	GE-16	TR-01	PTC 122	HEP-232	SK 3009	RT-124	ECG 104
2N458	RS276-2006	GE-16	TR-01	PTC 122	HEP-232	SK 3009	RT-124	ECG 104
2N459	RS276-2006	GE-76	TR-01	PTC 105	HEP-232	SK 3012	RT-127	ECG 121
2N460	RS276-2004	GE-2	IRTR-85	PTC 135	HEP-253	SK 3004	RT-120	ECG 102
2N461	RS276-2004	GE-1	IRTR-85	PTC 135	HEP-253	SK 3004	RT-120	ECG 102
2N462	RS276-2005	GE-2	IRTR-85	PTC 109	HEP-254	SK 3004	RT-120	ECG 102
2N463	NA	NA	NA	NA	NA	SK 3012	NA	NA
2N464	RS276-2004	GE-2	IRTR-85	PTC 135	HEP-253	SK 3004	RT-120	ECG 102
2N465	RS276-2004	GE-2	IRTR-85	PTC 135	HEP-253	SK 3004	RT-120	ECG 102
2N466	RS276-2005	GE-53	IRTR-85	PTC 109	HEP-254	SK 3003	RT-120	ECG 102
2N467	RS276-2005	GE-53	IRTR-85	PTC 135	HEP-254	SK 3003	RT-120	ECG 102
2N468	RS276-2005	GE-52	IRTR-85	PTC 102	HEP-254	SK 3004	RT-120	ECG 102
2N469	NA	GE-53	NA	NA	NA	NA	NA	NA
2N470	RS276-2009	GE-60	TR-21	PTC 115	HEP-53	SK 3124	RT-100	ECG 123
2N471	RS276-2009	GE-60	TR-21	PTC 121	HEP-53	SK 3124	RT-100	ECG 123
2N472	RS276-2009	GE-60	TR-21	PTC 121	HEP-53	SK 3122	RT-102	ECG 123A
2N473	RS276-2009	GE-60	TR-21	PTC 121	HEP-53	SK 3124	RT-100	ECG 123
2N474	RS276-2009	GE-60	TR-21	PTC 121	HEP-53	SK 3122	RT-102	ECG 123A
2N475	RS276-2009	GE-61	TR-21	PTC 121	HEP-53	SK 3122	RT-102	ECG 123A
2N476	RS276-2009	GE-60	TR-21	PTC 115	HEP-53	SK 3124	RT-100	ECG 123
2N477	RS276-2009	GE-60	TR-21	PTC 121	HEP-53	SK 3124	RT-100	ECG 123
2N478	RS276-2009	GE-60	TR-21	PTC 126	HEP-53	SK 3124	RT-100	ECG 123
2N479	RS276-2009	GE-60	TR-21	PTC 121	HEP-53	SK 3124	RT-100	ECG 123
2N480	RS276-2009	GE-61	TR-21	PTC 121	HEP-53	SK 3124	RT-100	ECG 123
2N481	RS276-2009	GE-52	IRTR-85	PTC 109	HEP-253	SK 3005	RT-118	ECG 100
2N482	RS276-2004	GE-52	IRTR-85	PTC 109	HEP-250	SK 3005	RT-118	ECG 100
2N483	RS276-2004	GE-52	IRTR-85	PTC 109	HEP-250	SK 3005	RT-118	ECG 100
2N484	RS276-2005	GE-1	IRTR-85	PTC 109	HEP-2	SK 3005	RT-118	ECG 100
2N485	RS276-2004	GE-1	IRTR-85	PTC 109	HEP-250	SK 3005	RT-118	ECG 100
2N486	RS276-2003	GE-2	IRTR-85	PTC 102	HEP-635	SK 3024	RT-110	ECG 120
2N487	NA	GE-1	IRTR-85	PTC 107	HEP-635	SK 3006	NA	NA
2N488	RS276-2023	GE-22	IRTR-88	PTC 131	HEP-52	SK 3114	RT-126	ECG 106
2N489	RS276-2023	GE-22	IRTR-88	PTC 131	HEP-52	SK 3114	RT-126	ECG 106
2N490	RS276-2018	GE-18	TR-25	PTC 143	HEP-243	SK 3024	RT-114	ECG 128
2N498	RS276-2009	GE-27	IRTR-87	NA	HEP-53	SK 3024	RT-114	ECG 128
2N499	RS276-2003	GE-9	IRTR-89	PTC 107	HEP-639	SK 3008	NA	ECG 126
2N500	RS276-2003	GE-9	IRTR-89	PTC 107	HEP-639	SK 3008	NA	ECG 126
2N501	RS276-2005	GE-9	IRTR-89	PTC 107	HEP-3	SK 3006	NA	ECG 126
2N502	RS276-2005	GE-9	IRTR-89	NA	HEP-638	SK 3006	NA	ECG 126
2N503	RS276-2003	GE-9	IRTR-85	PTC 107	HEP-2	SK 3005	RT-118	ECG 100
2N504	RS276-2003	GE-1	IRTR-89	PTC 107	HEP-3	SK 3008	NA	ECG 126
2N505	RS276-2005	GE-2	IRTR-85	PTC 102	HEP-2	SK 3005	RT-118	ECG 100
2N506	RS276-2004	GE-2	IRTR-85	PTC 109	HEP-253	SK 3004	RT-121	ECG 102A
2N507	RS276-2001	GE-8	TR-08	PTC 108	HEP-641	SK 3010	RT-122	ECG 103A
2N508	RS276-2005	GE-53	IRTR-85	PTC 135	HEP-254	SK 3003	RT-120	ECG 102
2N509	NA	GE-51	IRTR-85	PTC 107	NA	NA	NA	ECG 160
2N511	NA	GE-3	TR-01B	PTC 105	NA	SK 3009	RT-124	ECG 104
2N512	NA	GE-3	TR-01	PTC 105	NA	SK 3009	RT-124	ECG 104
2N513	NA	GE-3	TR-01	PTC 105	NA	SK 3009	RT-127	ECG 104
2N514	NA	GE-3	TR-01	PTC 105	NA	SK 3009	RT-127	ECG 121
2N515	RS276-2002	GE-5	TR-08	PTC 108	HEP-641	SK 3011	RT-122	ECG 103A
2N516	RS276-2002	GE-5	TR-08	PTC 109	HEP-641	SK 3010	RT-122	ECG 103A
2N517	RS276-2002	GE-5	TR-08	PTC 134	HEP-641	SK 3011	RT-122	ECG 103A
2N518	RS276-2005	GE-5	IRTR-85	PTC 105	HEP-2	SK 3005	RT-118	ECG 100
2N519	RS276-2004	GE-2	IRTR-85	PTC 114	HEP-253	SK 3005	RT-118	ECG 100
2N520	RS276-2005	GE-2	IRTR-85	PTC 105	HEP-254	SK 3005	RT-118	ECG 100
2N521	RS276-2005	GE-1	IRTR-85	PTC 135	HEP-254	SK 3005	RT-118	ECG 100
2N522	RS276-2005	GE-2	IRTR-85	PTC 109	HEP-2	SK 3003	RT-118	ECG 100
2N523	RS276-2005	GE-2	IRTR-85	PTC 109	HEP-2	SK 3003	RT-118	ECG 100
2N524	RS276-2004	GE-2	IRTR-85	PTC 135	HEP-253	SK 3004	RT-120	ECG 102
2N525	RS276-2004	GE-2	IRTR-85	PTC 135	HEP-253	SK 3004	RT-120	ECG 102
2N526	RS276-2005	GE-2	IRTR-85	PTC 135	HEP-254	SK 3004	RT-120	ECG 102
2N527	RS276-2005	GE-2	IRTR-85	PTC 135	HEP-254	SK 3004	RT-120	ECG 102
2N529	RS276-2004	GE-2	IRTR-85	PTC 108	HEP-253	SK 3005	RT-118	ECG 100
2N530	RS276-2004	GE-2	IRTR-85	PTC 108	HEP-253	SK 3005	RT-118	ECG 100
2N531	RS276-2004	GE-1	IRTR-85	PTC 108	HEP-250	SK 3005	RT-118	ECG 100
2N532	RS276-2004	GE-1	IRTR-85	PTC 108	HEP-253	SK 3005	RT-118	ECG 100
2N533	RS276-2004	GE-1	IRTR-85	PTC 108	HEP-253	SK 3005	RT-118	ECG 100
2N534	RS276-2005	GE-4	IRTR-85	PTC 109	HEP-3	SK 3123	RT-121	ECG 102A
2N535	RS276-2005	GE-52	IRTR-85	PTC 107	HEP-254	SK 3003	RT-121	ECG 102A
2N536	RS276-2005	GE-52	IRTR-85	PTC 135	HEP-254	SK 3003	RT-121	ECG 102A
2N537	RS276-2003	GE-2	NA	PTC 102	HEP-3	NA	NA	ECG 160
2N538	NA	GE-3	TR-01	PTC 105	NA	SK 3009	RT-127	ECG 121
2N539	RS276-2006	GE-3	TR-01	PTC 105	HEP-233	SK 3009	RT-124	ECG 104
2N540	NA	NA	TR-01	PTC 105	NA	SK 3009	RT-124	ECG 104
2N541	RS276-2009	GE-60	TR-21	PTC 121	HEP-53	SK 3122	RT-102	ECG 123A
2N542	RS276-2009	GE-60	TR-21	PTC 121	HEP-53	SK 3122	RT-102	ECG 123A
2N543	RS276-2009	GE-61	TR-21	PTC 121	HEP-53	SK 3122	RT-100	ECG 123A
2N544	RS276-2003	GE-50	IRTR-89	PTC 107	HEP-3	SK 3008	NA	ECG 126
2N545	NA	NA	IRTR-87	PTC 123	NA	SK 3024	NA	NA
2N546	RS276-2009	GE-63	TR-21	PTC 123	HEP-53	SK 3124	RT-100	ECG 123
2N547	RS276-2009	GE-63	TR-21	PTC 123	HEP-53	SK 3124	RT-100	ECG 123
2N548	RS276-2009	GE-63	TR-21	PTC 123	HEP-53	SK 3124	RT-100	ECG 123
2N549	RS276-2009	GE-63	TR-21	PTC 123	HEP-53	SK 3124	RT-100	ECG 123
2N550	RS276-2009	GE-63	TR-21	PTC 123	HEP-53	SK 3124	RT-100	ECG 123
2N551	RS276-2009	GE-18	TR-21	PTC 125	HEP-53	SK 3124	RT-100	ECG 123
2N552	RS276-2009	GE-18	TR-21	PTC 125	HEP-53	SK 3124	RT-100	ECG 123
2N553	RS276-2006	GE-3	TR-01	PTC 105	HEP-232	SK 3009	RT-127	ECG 121
2N554	RS276-2006	GE-16	TR-01	PTC 105	HEP-230	SK 3009	RT-127	ECG 121
2N555	RS276-2009	GE-76	TR-01	PTC 114	HEP-230	SK 3009	RT-127	ECG 121
2N556	RS276-2001	GE-8	TR-08	PTC 108	HEP-641	SK 3011	RT-119	ECG 101
2N557	RS276-2001	GE-6	TR-08	PTC 108	HEP-641	SK 3011	RT-119	ECG 101
2N558	RS276-2001	GE-6	TR-08	PTC 108	HEP-641	SK 3011	RT-119	ECG 101
2N559	RS276-2003	GE-51	IRTR-89	PTC 107	HEP-3	NA	NA	ECG 160
2N560	RS276-2009	GE-18	TR-21	PTC 125	HEP-53	SK 3024	RT-100	ECG 121
2N561	RS276-2006	GE-16	TR-01B	PTC 122	HEP-232	SK 3009	RT-127	ECG 121
2N562	RS276-2004	GE-53	IRTR-85	PTC 102	HEP-253	SK 3004	RT-120	ECG 102
2N563	RS276-2004	GE-53	IRTR-85	PTC 102	HEP-254	SK 3004	RT-120	ECG 102
2N564	RS276-2005	GE-53	IRTR-85	PTC 102	HEP-254	SK 3004	RT-120	ECG 102
2N565	NA	NA	IRTR-85	PTC 102	HEP-629	SK 3004	RT-120	ECG 102
2N566	NA	NA	IRTR-85	PTC 102	HEP-641	SK 3004	RT-122	ECG 103A
2N567	RS276-2002	GE-53	IRTR-85	PTC 102	HEP-641	SK 3004	RT-122	ECG 103A

ARCH G-E IR MAL MOT RCA SPR SYL

2N568	RS276-2005	GE-53	IRTR-85	PTC 102	HEP-254	SK 3004	RT-120	ECG 102
2N569	RS276-2005	GE-53	IRTR-85	PTC 102	HEP-254	SK 3003	RT-120	ECG 102
2N570	RS276-2005	GE-53	IRTR-85	PTC 102	HEP-254	SK 3003	RT-120	ECG 102
2N571	RS276-2005	GE-52	IRTR-85	PTC 135	HEP-254	SK 3003	RT-118	ECG 100
2N572	RS276-2005	GE-53	IRTR-85	PTC 102	HEP-254	SK 3003	RT-118	ECG 100
2N573	RS276-2003	GE-2	IRTR-85	PTC 102	HEP-633	SK 3004	RT-120	ECG 102
2N574	NA	GE-4	TR-03	PTC 106	HEP-233	SK 3004	NA	ECG 105
2N575	NA	GE-4	TR-03	PTC 106	NA	SK 3012	NA	ECG 105
2N576	RS276-2002	GE-5	TR-08	PTC 108	HEP-641	SK 3011	RT-119	ECG 101
2N578	RS276-2004	GE-1	IRTR-85	PTC 135	HEP-253	SK 3005	RT-118	ECG 100
2N579	RS276-2004	GE-1	IRTR-85	PTC 135	HEP-253	SK 3005	RT-118	ECG 100
2N580	RS276-2004	GE-1	IRTR-85	PTC 135	HEP-253	SK 3005	RT-118	ECG 100
2N581	RS276-2004	GE-1	IRTR-85	PTC 109	HEP-253	SK 3003	RT-118	ECG 100
2N582	RS276-2005	GE-2	IRTR-85	PTC 102	HEP-2	SK 3003	RT-118	ECG 100
2N583	RS276-2004	GE-1	IRTR-89	PTC 109	HEP-253	SK 3005	NA	ECG 126
2N584	RS276-2005	GE-2	IRTR-89	PTC 102	HEP-2	SK 3003	NA	ECG 126
2N585	RS276-2001	GE-8	TR-08	PTC 108	HEP-641	SK 3011	RT-119	ECG 101
2N586	RS276-2005	GE-1	IRTR-85	PTC 135	HEP-254	SK 3005	RT-118	ECG 100
2N587	RS276-2002	GE-5	TR-08	PTC 108	HEP-641	SK 3011	RT-119	ECG 101
2N588	RS276-2003	GE-9	IRTR-89	PTC 107	HEP-639	SK 3006	RT-119	ECG 101
2N589	RS276-2006	GE-3	TR-01	PTC 105	HEP-232	SK 3009	RT-127	ECG 126
2N590	NA	NA	IRTR-85	PTC 135	NA	NA	NA	ECG 102A
2N591	RS276-2005	GE-50	IRTR-85	PTC 109	HEP-638	SK 3004	RT-121	ECG 100
2N592	NA	NA	IRTR-85	PTC 109	NA	SK 3005	RT-118	ECG 100
2N593	NA	NA	IRTR-85	PTC 109	NA	SK 3005	RT-118	ECG 101
2N594	NA	GE-5	TR-08	PTC 108	NA	SK 3011	RT-119	ECG 101
2N595	NA	GE-5	TR-08	PTC 108	NA	SK 3011	RT-119	ECG 101
2N596	NA	GE-5	TR-08	PTC 108	NA	SK 3011	RT-119	ECG 101
2N597	RS276-2005	GE-1	IRTR-85	PTC 135	HEP-254	SK 3005	RT-118	ECG 100
2N598	RS276-2005	GE-1	IRTR-85	PTC 135	HEP-254	SK 3005	RT-118	ECG 100
2N599	RS276-2005	GE-1	IRTR-85	PTC 135	HEP-254	SK 3005	RT-118	ECG 100
2N600	NA	GE-51	IRTR-85	NA	NA	SK 3005	RT-118	ECG 100
2N601	NA	GE-51	IRTR-85	NA	NA	SK 3008	NA	ECG 126
2N602	RS276-2004	GE-50	IRTR-89	PTC 109	HEP-2	SK 3008	NA	ECG 126
2N603	RS276-2005	GE-9	IRTR-89	PTC 109	HEP-2	SK 3008	NA	ECG 126
2N604	RS276-2005	GE-5	IRTR-89	PTC 109	HEP-2	SK 3008	NA	ECG 126
2N605	RS276-2005	GE-50	IRTR-89	PTC 109	HEP-2	SK 3008	NA	ECG 126
2N606	RS276-2005	GE-50	IRTR-89	PTC 109	HEP-2	SK 3008	NA	ECG 126
2N607	RS276-2005	GE-50	IRTR-89	PTC 109	HEP-2	SK 3008	NA	ECG 126
2N608	RS276-2005	GE-50	IRTR-89	PTC 109	HEP-2	SK 3008	NA	ECG 126
2N609	RS276-2005	GE-53	IRTR-85	PTC 102	HEP-254	SK 3004	RT-120	ECG 102
2N610	RS276-2005	GE-53	IRTR-85	PTC 102	HEP-254	SK 3004	RT-120	ECG 102
2N611	RS276-2004	GE-53	IRTR-85	PTC 102	HEP-253	SK 3004	RT-120	ECG 102
2N612	RS276-2004	GE-53	IRTR-85	PTC 102	HEP-253	SK 3004	RT-120	ECG 102
2N613	RS276-2004	GE-53	IRTR-85	PTC 102	HEP-253	SK 3004	RT-120	ECG 102
2N614	RS276-2004	GE-52	IRTR-85	PTC 109	HEP-253	SK 3005	RT-118	ECG 100
2N615	RS276-2004	GE-52	IRTR-85	PTC 109	HEP-253	SK 3005	RT-118	ECG 100
2N616	RS276-2004	GE-1	IRTR-85	PTC 135	HEP-253	SK 3004	RT-118	ECG 100
2N617	RS276-2004	GE-1	IRTR-85	PTC 135	HEP-253	SK 3005	RT-118	ECG 100
2N618	RS276-2006	NA	TR-01	PTC 138	HEP-232	SK 3009	RT-127	ECG 121
2N619	NA	GE-61	IRTR-95	PTC 115	NA	SK 3039	RT-113	ECG 108
2N620	NA	GE-61	IRTR-95	PTC 115	NA	SK 3039	RT-113	ECG 108
2N621	NA	GE-61	IRTR-95	PTC 121	NA	SK 3039	RT-113	ECG 108
2N622	NA	GE-61	TR-21	PTC 132	NA	NA	RT-100	ECG 123
2N623	NA	GE-20	IRTR-89	PTC 107	NA	NA	NA	ECG 126

*These devices are silicon controlled rectifiers. (continued next month)

R-E's Service Clinic

The Trouble Tree

*Causes are many,
symptoms are few*

by JACK DARR
SERVICE EDITOR

I'VE BEEN OVER THIS BEFORE, AND I'LL probably go back over it again—and again and again. Not only for the benefit of the new men who come into our bewildering profession each year, but for the benefit of a few forgetful old goats like myself.

It deals with the most important thing in any electronics repair job—the diagnosis. Test equipment does not make diagnoses—your brain does. All the test equipment does is give you a set of facts. *You* make the diagnosis from interpreting these.

The first thing you need to keep in mind is that in a complex device like a TV set, or even a radio, there are as many potential causes for trouble as there are parts. In multiple-function devices such as color TV, this is even more important. So when we see a given symptom, we must make up a mental Trouble Tree, like Fig. 1. At the bottom is the major symptom, and the branches are all of the things which could possibly cause it.

A single, simple symptom can have multiple causes—for example, “No High Voltage.” A complaint of “No Vertical Sweep” is only a little less complex. Even “No Sound” can have quite a few possible causes.

Try growing one yourself. Sit down with a piece of paper, pick a symptom and then make up a Trouble Tree that names all of the possible causes. ALL, I said! Now, to make a useful diagnosis, start eliminating things one at a time, by testing.

To make things go faster, put the most likely or most common things first. This is easiest, and has the greatest statistical chance of success. For example, in a tube or hybrid set, experience has taught us that tubes are the most likely cause. They also plug-in. So the logical choice for the first one would be replacement of the tube.

Next would be the dc voltage supply, and so on down the line. Now, having gone this far, get out the schematic of a set, and look at it. See if you can find something you've overlooked. Remember, every part is sus-

pect until proven innocent! (How many of you put down “crack in PC board conductor” as a possibility? See what I mean?)

With a good knowledge of how the basic circuit action works, you can take shortcuts. For example, take “Blank Screen; No Sound.” Here, you have the whole signal-path of the set as a possibility. Since this is a long circuit, break it in the middle. Take a scope reading at the output of the video detector. If you see a normal video signal at this point, you've eliminated all of the stages “to the left” of this point; tuner, i.f.'s agc, etc. The trouble lies in the video amplifier, picture tube, etc.

If you find no signal at the video detector output, you know that the trouble is ahead of this point. Either the tuner, the i.f.'s, or the control circuits. For another shortcut, clamp the agc with a bias-box. It sets the control

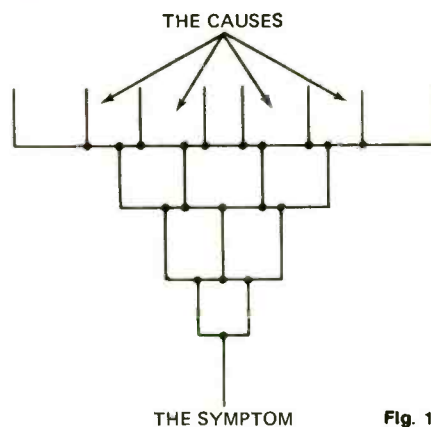


Fig. 1

voltage at maximum gain (use the no-signal agc voltage shown on the schematic). If this produces a picture, you've cleared the signal-path stages and can proceed to the agc circuitry.

If the agc clamp does not produce a picture, leave it there. Start signal tracing through the i.f.'s, to find out how far the signal goes before it stops. By feeding in a high-level, fixed pattern signal, you can read its amplitude with a crystal-detector probe on the scope. The color-bar output from a

This column is for your service problems—TV, radio, audio or general and industrial electronics. We answer all questions individually by mail, free of charge, and the more interesting ones will be printed here.

If you're really stuck, write us. We'll do our best to help you. Don't forget to enclose a stamped, self-addressed envelope. Write: Service Editor, Radio-Electronics, 200 Park Ave. South, New York 10003.

bar-dot generator is very good for this, in color or black and white. In most sets, you can even see the small i.f. signal output from the tuner, on the i.f. input. This clears or confirms the tuner as a suspect.

A lot of technicians place too much reliance on dc voltage readings. They're essential, of course, but *should never be used as the only diagnostic tool*. From a lot of experience and troubles, I believe that the fastest way is a combination of tests; first for the presence or absence of signals at a given point, and second for the dc voltage readings at key points in the suspected stage. In other words, if you

get a signal through the first i.f. stage, you don't *have* to take dc voltage readings; they're good. Find the stage which doesn't pass the signal, and read dc voltages there.

Frinstance No. 2: No Vertical Sweep. Touch the scope probe to the grid of the vertical output tube. If you get the normal sawtooth signal there, the oscillator is running. Now; you've established that the oscillator is working, yet there is no vertical sweep. Having eliminated the most likely suspects, go to the yoke tap of the output transformer. If you see the normal spike signal there, the output transformer is cleared.

Now you have one suspect, or do you? Open yoke, yes. Also! Broken wire in yoke cable, bad contact in yoke socket, bad contact in yoke plug! Don't overlook the little things.

The key point I hope I made in all of this is that each test must be made for a purpose. Don't just "sit there and poke at it;" a fault which we are all guilty of at times. When you pick up the probe of a test instrument, know what you want to test and go to a test-point that will tell you. **R-E**

reader questions

FINDING SHORTS IN PC SET

I've got a Magnavox 1-T-109, with PC boards; it had a short in the B+. I've changed the rectifier and filter capacitor, both shorted. Now, I read 20,000 ohms to ground on the B-plus. I think this is too low. How do I get into this type of circuitry to separate the loads?—T.P., Brooklyn, N.Y.

Actually, 20,000 ohms to ground isn't too bad on a +145 volt supply. Try reversing your ohmmeter prods and see if it isn't higher the other way. If so, OK. Try this; install the new filter capacitor and rectifier, but leave the cathode lead of the diode open. Connect an 0-500 dc milliammeter in this lead, between diode and filter.

Now, turn the set on and check for excessive current. Normal should be about 300 mA. There's a sneaky you can pull; just tack a 300-mA pilot light in series instead of the meter. If the bulb lights to full brightness, OK; if there's a short, it'll blow out.

BRIGHTNESS CONTROL WORKS BACKWARD


From a cold start, the picture on this RCA CTC-38 comes in fine. Brightness and contrast controls work normally. After about 3 minutes the picture pops out of focus, stretches vertically and pulls in on the sides; retrace lines show up.

Now, the brightness control works backward. If I turn it up, the raster goes dark. If I turn it down, I can find a place where the picture gets very bright, with good focus. However, it's much too bright, and the retrace lines are still there.

Picture tube good, high-voltage regulator tube good, yoke OK, flyback OK. Now where do I go?—A.M., Morgan Hill, Calif.

I'd say "To the video output stage." Monitor the plate voltage of the 12HG7 tube. See if it suddenly

LEARN THE BURGLAR ALARM BUSINESS!!!

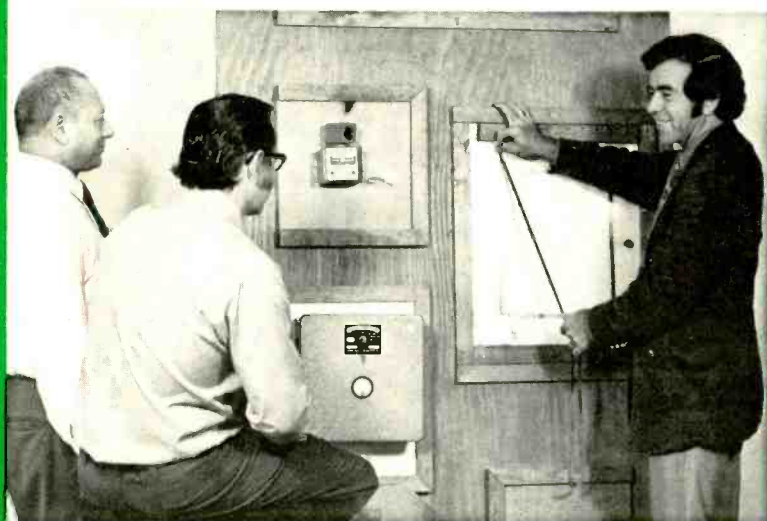

Burglar alarm installation is one of the most rapidly growing industries today. The tremendous publicity associated with security systems has created a widespread demand for installation of alarm systems.

A formal program has not been previously available to an individual seeking training in this profitable field. Now Ademco, the world's leading manufacturer of burglar alarm equipment offers you an opportunity to learn alarm installation techniques even if you have little or no experience in the alarm field. In just two short days you can be ready to install your first alarm!

Seminars are held throughout the year at Ademco's plant in Syosset, New York and at various locations throughout the country. All sessions are limited in attendance, so reservations should be made well in advance.

**FOR FURTHER INFORMATION CONTACT:
ALARM DEVICE MANUFACTURING CO.**

A DIVISION OF PITTSWAY CORPORATION

165 Eileen Way, Syosset, N.Y. 11791

Area Code 516-921-6700



drops (goes less positive) when the trouble shows up. If so, this will make the cathode voltage of the picture tube "go negative," which is the same as making the picture tube grids *more positive*. Thus, the tube tries to draw far more than its normal beam-current and the raster flares. This overloads the high-voltage supply, and the horizontal sweep is reduced; at the same time, the reduced high voltage lets the vertical sweep push the beam farther, so you get vertical stretch.

If the video output tube is OK, you can get the same effect if something happens to make the color-difference amplifier plates go more positive. This makes the picture-tube grids more positive. With the circuitry used here, one of two things could be happening. The color-difference amplifier tubes *heaters* could be going out, due to a bad solder joint, or the single cathode resistor could be opening up; same cause.

HOT CHASSIS WITH POWER TRANSFORMER

This Sylvania 580-1 color TV is definitely a "hot chassis" type now, after being hit by lightning! Works on rabbit-ears, but kicks the breaker when the external antenna is connected. The den where the set's located has a tile floor, and the customer gets free shock-treat-

ments, which he doesn't enjoy!—C.I., Montgomery, Ala.

Most likely cause; a short to core in the primary of the power transformer. It might even be a leakage of ac from one of the secondaries, since this set uses a half-wave doubler circuit, with a big electrolytic capacitor to chassis as the lower part of the doubler circuitry.

In any case, I'd check the primary first, then disconnect and check the secondaries for leakage to the core. New power transformer will probably clear it up.

SLOW COLOR WARMUP

It takes about 20 minutes for the color to come on in this Zenith 14A9C50 chassis. I'm enclosing a list of the dc voltages around the color stages. Any ideas?—L.T., Winnipeg, Man.

One at least. You show a -0.5 volt on the color amplifier grid (pin 7, 6KT8) which is normal with no signal, or B/W signal. However, when a color signal is received, this should *change* to a +6.0 volts. It doesn't. So, your color killer circuit isn't working, or isn't starting up as it should. The color amplifier state is being cut off, at all times (or for far too long).

Check the acc/killer diodes. The dc voltages on these should be equal and *opposite*, and should change when

a color signal is received. This will run about -50 volts on the anode of CR213, and +50 v. on the cathode of CR214.

Also, check for the presence of the 3.58-MHz oscillator signal. In a few sets, this oscillator is slow starting; weak tube, bad crystal, etc. This will do the same thing.

INTERMITTENT LOSS OF RED

The reader wrote: "I am getting an intermittent loss of red on a Zenith 14A9C19 chassis, with the "chip" demodulator." I replied: "Check the signal-in vs the signal-out of the demodulator chip. If it is only on the one color, and the rest work, then I'd suspect a bad chip. Be sure that external parts are definitely good."

He replied: "It was a defective demodulator. For your information, the Zenith distributor says that the recommended replacement for this chip is the "silver" type, Part No. 221-39, to replace the original "black" unit, Part No. 221-37."

For which many thanks to Peter Hartnett, Rahway, N.J.

AGC TOO HIGH

When I turn this Sears 9168 color set on, the picture comes on for a second, and then it whites-out. I read a (continued on page 78)



Trophy Year

Thanks. Every year that goes by proves we have the best competitive team going. You, the independent serviceman, and Raytheon, the largest independent tube supplier. In 1972, we put together the best tube year in a lot

of years. It didn't just happen. Raytheon worked hard to give you more dependability. You worked hard to stay ahead of the competition. Teamwork like that makes trophy years, every year. For both of us.

Circle 19 on reader service card

USE IT ALL AS YOU GET READY FOR A NEW CAREER...

\$1,500.00 worth of two-way radio electronic communications equipment!

Bell & Howell Schools announces a new learn-at-home program that gives you "hands on" experience with commercial-grade equipment—as you prepare for a business of your own in two-way radio electronic communications servicing.

You need "hands on" experience with a real, commercial-band FM transceiver and actual commercial-grade test equipment—to take full advantage of growing opportunities in electronic communications.

Two-way radio communications is a healthy growth area in electronics. And it's lucrative. Almost two million commercial two-way radio systems now serve as vital communications links for trucks, planes, boats and taxis. And the FCC requires each system to have its equipment serviced regularly by a licensed technician. That's where you come in. But you need career-oriented training—plus your FCC license.

Knowing how to put an amateur radio kit together won't help when you're "on the job"—servicing two-way radio systems for aircraft or advising trucking companies about their land-mobile communications system. For that, you need "hands on" experience with the real thing. This unique new Bell & Howell Schools learn-at-home program that gives you just that. You can work with the equipment by attending one of our special "help sessions" or by dropping by one of the Bell & Howell resident schools. If neither of these plans

is convenient, you can have the equipment shipped to your home in return for a \$100 deposit, which is refundable when you return the equipment.

Find out more about this exciting new Bell & Howell Schools program. There's no obligation.



For free facts, mail attached card today!

Let Bell & Howell Schools help you get ready for an exciting career or business of your own in two-way radio electronic communications!

Bell & Howell Schools has helped thousands of people prepare for careers—and businesses of their own—in electronics. You can have absolute confidence in the thorough training you get.

Expert instructors at Bell & Howell Schools plan each program to answer a single question: "What qualifications will you need to take advantage of *actual career opportunities* in electronics?" They then build each program to give you those exact qualifications.

To get ready for a business of your own in two-way radio, you need: 1) career-oriented training; 2) FCC License; 3) "hands on" experience with commercial-grade equipment. Bell & Howell Schools now offers this new at-home training program that gives you all three. (See FCC License Warranty on attached card.)

JUST LOOK AT ALL THE EQUIPMENT YOU'LL WORK WITH DURING YOUR TRAINING PROGRAM WITH BELL & HOWELL SCHOOLS!

Commercial-Band FM Transceiver . . . exactly the kind of two-way radio you'll service throughout your career

FCC REGULATIONS GIVE YOU THE OPPORTUNITY TO START YOUR OWN BUSINESS!

The Federal Communications Commission requires that all commercial two-way communications systems be checked and serviced by a licensed technician at regular intervals.

As a Bell & Howell Schools graduate, you'll have the technical know-how you need. With your FCC license, you can go out and eventually build your own business—signing contracts with companies that use two-way radio. FCC regulations could mean security and regular income for you!

BELL & HOWELL SCHOOLS OFFERS YOU THESE SPECIAL ADVANTAGES:

Help Sessions Scheduled regularly every few Saturdays at the Bell & Howell Schools and in many other cities throughout the U.S. and Canada. Top instructors give you personal help and guidance.

Transfer Privileges After completion, you can transfer to any of the resident schools for more advanced study, if you wish.

Lifetime National Placement Assistance Helps you locate a job where you want to anytime after you complete program.

Veterans' Benefits We are approved by the state approval agency for Veterans' Benefits.

Student Financial Aid We are an eligible institution under the Federally Insured Student Loan Program.

EXCLUSIVE ELECTRO-LAB®—YOURS TO KEEP!

To make sure you get practical experience with instruments used daily by professionals, we've integrated into your program three precision instruments you assemble yourself and keep:

Design Console Use this to rapidly "breadboard" circuits without soldering.

Oscilloscope Offers bright, sharp screen images, 3-way jacks for leads, plugs.

Transistorized Meter Registers current, voltage and resistance.

FOR FULL INFORMATION, MAIL THE ATTACHED CARD TODAY! OR WRITE:

An Electronics Home Study School
DeVRY INSTITUTE OF TECHNOLOGY



ONE OF THE
BELL & HOWELL SCHOOLS
4141 Belmont, Chicago, Illinois 60641

406R3

Deviation Meter
... model favored by many working technicians to check modulation of transmitted signal.

Frequency Meter . . . highly sensitive instrument used to check signal frequency within precise tolerances established by government standards.

Power Output Meter . . . meter used almost universally by trained and licensed technicians to check power output—or wattage—of signal.

Alignment Generator
... a custom-designed unit you use to generate test signals for transceiver alignment.



READER QUESTIONS

(continued from page 73)

very high negative voltage, -60 volts, on the 12AV6 agc tube plate. Where's this coming from?—G.S., Highland, Calif.

You're in the right place! This very high agc voltage is cutting off the i.f. Check to see that you do have the proper keying pulse on the plate of this tube. Should be 200 volts p-p. Also, check the 33-megohm resistor from agc to +125 volts. Could be open.

However, I believe I'd be more apt to suspect an open agc bypass ca-

pacitor somewhere in there. This would let the agc go into oscillation, and build up that excessive negative voltage on the plate. Check the cathode voltages, through that voltage-divider and the agc control. The 47,000-ohm resistor to ground may be open, or increased in value.

HIGH VOLTAGE SUPPLY

I replaced the high-voltage rectifier heater winding on this RCA CTC-25. Original was shorted. Now, I can't get the set to work properly! If I turn the brightness down to where I can barely see the picture, OK. If I try to turn it up, I get thin white streaks across the

raster. I can get the same thing by turning up the pix tube screen controls. All tubes good.—G.S., Highland, Calif.

It sounds as if the heater of the 3A3 isn't getting hot enough. This would account for the big drop in the high voltage when you increase the brightness (raise the pix tube beam current.) Recheck the new heater winding; be sure that you put on exactly the same number of turns around the core that the original had! If you're one short, your heater voltage will be low, and the cathode of the tube will be too cool.

While you're in there, look for signs of arcing across the 3A3 socket. Arcs, or a bad contact, can cause the "thin white lines" symptom. Check the 3A3 plate lead for corrosion, too.

CHECKLISTS FOR DIM RASTER

The raster on this Magnavox 904 is very dim. What should I check to find out what's causing it?—W.B., Philadelphia, Pa.

OK, here's your checklist:

1. High voltage—23-25 kV minimum.
2. Focus voltage—20% of high voltage.
3. Pix tube cathode voltage.
4. Pix Tube grid(s) voltage. (The difference between these is the actual bias on the pix tube.)
5. The pix tube itself, for emission. Must have a minimum emission of 500- μ A per gun for good brightness.

If the video output tube's plate voltage is low, or the color-difference amplifier tubes plate voltage is high, this will change the pix-tube bias to the point where the pic tube cannot conduct enough beam current. Faults in these little tubes can cut off the pix tube.

RASTER BREATHING

As soon as this set is turned on, the bottom of the raster moves slowly up and down for about an inch. It's a Setchell-Carlson ECL-66. I can also see thick horizontal lines about 2 inches wide moving slowly up the picture. What causes this?—G.S., Highland, Calif.

This is sometimes called "breathing." Most frequent cause is a little excess ripple on the B+ supply to the vertical output stage or oscillator. Check this line with a scope. If the ripple is higher than normal, look for a bad filter capacitor. Ripple here shouldn't be more than 0.5 volt p-p at the worst.

Don't forget to check the 6GF7 tube for heater-to-cathode leakage, too! Substitution is the quickest way.

NO VERTICAL SWEEP

This Zenith 24NC31Z came in with no raster or sound. I found a bad resistor in the B+, changed it, and it

CHANNELLOCK

Gives You More In Hand Tools Including
Handcrafted...High Polished
PRECISION PLIERS
(wonderful for fine work)


Beautiful? They'd grace a jeweler's window.

Practical? Thousands of precision work craftsmen—professionals and hobbyists alike—buy them every year and swear by them.

Precision made of high grade drop forged steel. Beautiful polished finish. Blue dipped plastic comfort grips.

Ask for CHANNELLOCK Little Champ precision pliers. You'll like 'em.

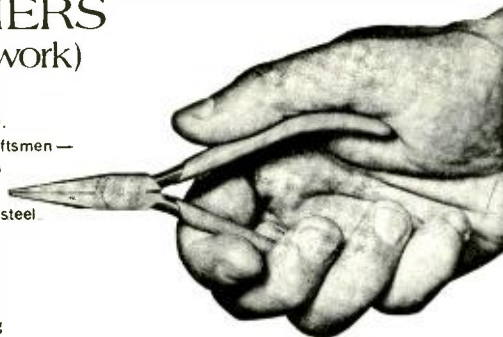LET US SEND YOU OUR CATALOG showing Little Champs and their equally fine big cousins.



TOOLS BY
CHAN NEL LOCK

MEADVILLE, PA. 16335

Circle 20 on reader service card

worked. When I took it back, all I could get in the home was a horizontal bar about an inch high! Checked the service switch, tube, and so on. No help.—A.S., St. Paul, Minn.

I did the same thing not long ago! Set working perfectly on bench, on extension cables; back in cabinet, no vertical sweep. So, do what I did—check to see what isn't hooked up! There has to be something.

Crystal-ball diagnosis: check the convergence yoke, plug and socket. If this isn't plugged in, or has a bad contact on one certain pin, you'll get exactly this symptom. The vertical output tube cathode circuit returns to ground through the convergence circuitry. So, without this plug in properly, you have far too much resistance in this cathode, and lose practically all your height, due to excessive bias.

"SQUAWK" IN HV

Turn the brightness full up on this Motorola TS-915, and it's fine. Good pix, good focus, etc. But, if you turn the brightness down, it makes a loud squawk in the speaker, and the picture goes out. Raster has fuzzy horizontal bars, about 2-inches wide.—R.McK., De Queen, Ariz.

Turn the sound off, make it squawk, and listen around the high-voltage compartment to see if you can

hear an arc. Check the high voltage. I think you'll find that it stays up, but that the focus voltage drops drastically, to 2-3 kV.

This could be in the big dropping resistor for the focus voltage, but in this chassis, it's more apt to be a breakdown in that little 2-conductor socket which carries the focus voltage to the pix-tube base. Pull this plug, and look at it. It's a light colored plastic. If you can see a tiny brown spot, replace it; the plug is breaking down and allowing the focus voltage to arc to chassis.

TOO MUCH GREEN

The screen of this RCA CTC-16 is green all the time; color and B/W. The dc voltage readings on the G-Y amplifier are OK. B-Y and R-Y plates read +80 volts. The pix tube is good. Resistors and capacitors in the color-difference amplifier circuits all check.—T.C., Cicero, Ill.

You've found the problem; that low plate voltage on the color-diff amplifiers. Since this determines the conduction of the pix-tube guns, by controlling the grid voltages, the "less-positive" voltage here shows that these two grids are almost cut off (in other words, the picture-tube grids are "too far negative," which reduces the conduction of any tube).

Most likely cause for this; a bad solder joint on the printed-circuit board, at the B+ supply point for the two 27,000-ohm plate resistors of the B-Y and R-Y amplifier stages. These are the 2-watt, light blue resistors just behind the 6GU7's. The G-Y plate resistor goes to a different connection.


LOSES COLOR PURITY

I've got an odd problem in a Motorola TS-914 chassis. It loses purity as it runs. After it's been on about 2 or 3 hours, I get blobs of color on the screen. These are hard to get out even with an external degausser. The degauss circuit seems to be OK; I read 25 ohms on the coils. Where do I go from here?—C.C. Dix Hills, N.Y.

This sounds as if it is a problem in the set's auto-degausser. This set has an unusual degausser circuit, operated from the focus voltage; when the DEGAUSS button is pushed, a charge is sent through the coil, from a capacitor.

If you read 25 ohms on that coil, look out. The factory schematic shows a normal resistance of only 1.1 ohms. This could indicate a bad degausser coil. Check the switch and capacitor for leakage. Incidentally, you can not run this set if the degausser coil isn't hooked up, it upsets the focus. Let's hear how you make out. R-E

INTERNATIONAL Frequency meter FM-2400CH

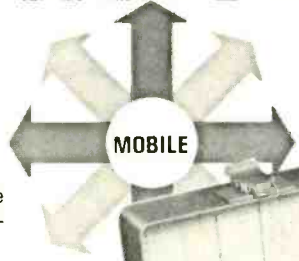

The FM-2400CH provides an accurate frequency standard for testing and adjustment of mobile transmitters and receivers at predetermined frequencies.

The FM-2400CH with its extended range covers 25 to 1000 MHz. The frequencies can be those of the radio frequency channels of operation and/or the intermediate frequencies of the receiver between 5 MHz and 40 MHz.

Frequency Stability: $\pm .0005\%$ from $+50^\circ$ to $+104^\circ\text{F}$.

Frequency stability with built-in thermometer and temperature corrected charts: $\pm .00025\%$ from $+25^\circ$ to $+125^\circ$ (.000125% special 450 MHz crystals available).

Self-contained in small portable case. Complete solid state circuitry. Rechargeable batteries.

WRITE FOR CATALOG!

- Tests Predetermined Frequencies 25 to 1000 MHz
- Extended Range Covers 950 MHz Band
- Pin Diode Attenuator for Full Range Coverage as Signal Generator
- Measures FM Deviation



FM-2400CH (meter only)	\$595.00
RF crystals (with temperature correction)	24.00 ea.
RF crystals (less temperature correction)	18.00 ea.
IF crystals	catalog price

INTERNATIONAL
CRYSTAL MFG. CO., INC.
10 NO. LEE • OKLA. CITY, OKLA. 73102

Circle 21 on reader service card

new pay tv system


Pay-for-program system provides two separate premium channels for first-run movies or special sports events

A NEW SYSTEM THAT CAN OFFER INDIVIDUAL CATV television subscribers special cultural programs, sports events, recent movies, live plays and other special programs for a fee has been developed jointly by Magnavox and TelePrompTer. The system has been labelled *Premium Television*—the old term "Pay-TV" has been abandoned. (Pay-TV would be inappropriate in any case—the CATV subscriber pays for all his programs.) The new system will include two special or "premium" channels in addition to the regular ones of the CATV system.

The old pay-TV problems of ordering programs by phone, using special plastic cards and the like are overcome, as is that of billing for services. The subscriber has a compact Home Terminal with switches for the special channels. In most cases, he can see a short preview of the program on the premium channel he selects, after which the program becomes scrambled. If the viewer likes what has already been seen, he pushes an "accept" button and the program continues in unscrambled form.

A neighborhood unit known as an IDEM routes the programs from the CATV distribution system or "head end" to the viewer, handles the requests for previews and the "accept" orders and makes up the accounts. Each IDEM can serve up to 32 home terminals. The billing information is stored in the

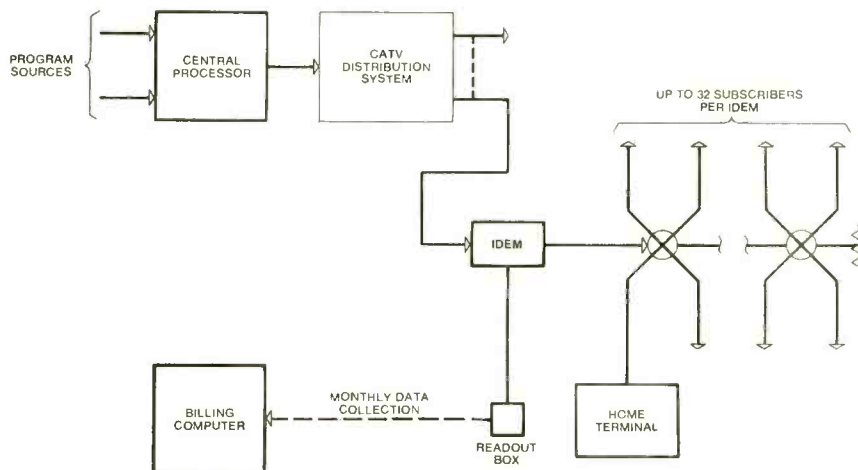
IDEM, and collected regularly through its read-out on an ordinary cassette tape, which is sent to the system's computer for monthly billing. In a two-way system, the accounts are transmitted direct from the IDEM to the billing computer. The same can be done with a one-way system if a re-




THE PREMIUM TV SYSTEM IS made up of a processor, a CATV head end, the neighborhood units called IDEM's, and numbers of home terminals, with arrangements for billing. This block diagram shows how these elements are interconnected.

The "Country Boys" Have it!

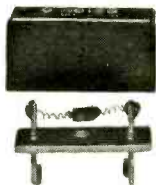Isn't an absolutely safe
BEL Chemical FUSE
worth a nickel more?



Bel Chemical Fuse

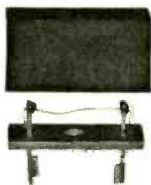

Wire Type Competitive Fuse

If there's any doubt about which replacement fuse to install in your customer's TV set... install the only fuses used in original television sets... BEL-FUSES. It's what's inside that makes BEL-FUSES safe for expensive sets... a chemical. Never substitute a wire type fuse. Here's why. Break open an Oneida BEL-FUSE. Now do the same with the one that looks like ours. Light a match to each. Result? The chemical in the BEL-FUSE blows *instantly*. And you'll burn your fingers before the other one blows. This same safety protects the circuitry in TV sets. So specify Oneida BEL-FUSES.

We even have handy Oneida Caddy Kits with a complete range of BEL-FUSES... for all major TV sets. See your Oneida Distributor or Dealer TODAY

The "Country Boys" Appreciate Your Business



ONEIDA ELECTRONIC MFG. INC.
MEADVILLE, PA. 16335



George Dalton

ELECTRONIC
MFG. INC.



HOME TERMINAL CONTAINS CHANNEL switches and an "accept" button. Pushing either premium channel switch gives a preview of its program. The third switch is for ordinary CATV.

turn line is provided, or if telephone lines are used.

Basically, the system (see diagram) consists of:

1. A Central Processor. This accepts the programs from their sources, adds the scrambling codes and controls the sequence of programs throughout the day. It can be operator-attended, or operated with a program on punched or magnetic tape that can be set up for a whole day's programming.

2. The CATV distribution system, or head end, a normal amplification

Circle 22 on reader service card


and distribution system, taking its program from the Central Processor and supplying the subscribers through the cable system.

3. **The IDEM's** (Interactive Data Exchange Modules). These handle the communications between the subscriber and the system, accepting orders and supplying desired programs. They also store the accounting information until it is collected via the read-out box. Since one IDEM will accommodate up to 32 subscribers, the cost of such circuitry—which in some older proposed systems was required in each subscriber's home—is much reduced.

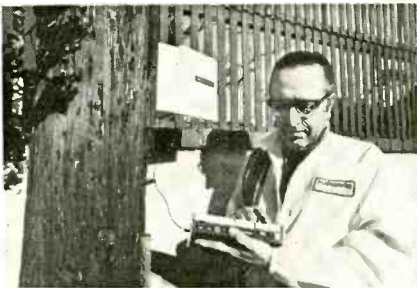4. **The Home Terminal.** It contains equipment for communicating with the IDEM, and converts the audio-video signal from it to a vhf channel on the subscriber's TV receiver. It



IDEM, NERVE CENTER OF THE SYSTEM, is the liaison between subscriber and head end.



ELECTRONIC METER READER just plugs in his cassette to record the month's bill on tape.

has pushbuttons to switch the TV to normal CATV viewing or to either of the two "premium" channels—which permit a short preview of the premium program—and an "accept" button, which gives the viewer a de-scrambled picture and signals the IDEM to make the appropriate charge for the service. The premium channels have key-lock switches, preventing unauthorized access to the pay channels by teen-agers or others.

Magnavox is supplying Tele-Prompter with systems this spring, when a complete set of field trials will be initiated, with each subscriber initially supplied with two channels of premium programming. If tests justify it, later systems may be equipped with more than two premium channels. R-E

Checklist of Books for the Libraries of Technicians, Hobbyists & Students

AUDIO, HI-FI & TAPE RECORDERS

- 4-Channel Stereo—From Source to Sound 176p., 98 illus. \$3.95
- Selecting & Improving Your Hi-Fi System 224p., 122 illus. \$4.95
- Pictorial Guide to Tape Recorder Repairs 256p., 320 illus. \$4.95
- How to Repair Musical Instrument Amplifiers. 288p., 110 illus. \$4.95
- Hi-Fi for the Enthusiast 176p., 51 illus. \$3.95
- Servicing Electronic Organs 196p., 8 1/2 x 11, 184 illus. \$7.95
- Electronic Musical Instruments 192p., 121 illus. \$4.95
- Servicing Modern Hi-Fi Stereo Systems 248p., 125 illus. \$4.95
- Handbook of Magnetic Recording. 224p., 90 illus. \$4.95
- Installing & Servicing Home Audio Systems 256p., 150 illus. \$4.95
- Tape Recording for Fun & Profit. 224p., 200 illus. \$4.95
- Audio Systems Handbook 192p., 125 illus. \$4.95

ELECTRONIC SERVICING

- Troubleshooting Solid-State Amplifiers 256p., 95 illus. \$4.95
- How to Solve Solid-State Circuit Troubles 304p., 161 illus. \$5.95
- Troubleshooting Solid-State Electronic Power Supplies. 208p., 85 illus. \$4.95
- Solid-State Circuit Troubleshooting Guide 224p., 150 illus. \$4.95
- Jack Darr's Service Clinic No. 2 176p., 165 illus. \$3.95
- Practical Electronic Servicing Techniques 256p., 127 ill. \$4.95

REFERENCE & GENERAL ELECTRONICS

- Dictionary of Electronics 420p., 487 illus. \$3.95
- 1972 Popular Tube-Transistor Substitution Guide. 256p. \$2.95
- Marine Electronics Handbook 192p., 106 illus. \$4.95
- Handbook of Electronic Tables—2nd Ed. 224p., 224 illus. \$4.95
- Electronics Data Handbook: 2nd Ed. 256p., fully illus. \$4.95
- Pulse & Switching Circuits 256p., 184 illus. \$4.95
- Electronics Reference Databook 232p., 100 ill., 45 tables \$4.95
- Modern Radar: Theory Operation & Maintenance. 480p., 367 ill. \$7.95
- Industrial Electronics: Principles & Practice. 416p., 380 illus. \$5.95

"LEARN-IT-YOURSELF" BEGINNER'S BOOKS

- Basic Electricity & Beginning Electronics 256p., 191 illus. \$4.95
- Basic Electronic Circuits Simplified. 352p., 170 illus. \$5.95
- How to Read Electronic Circuit Diagrams 256p., 140 ill. \$3.95
- Understanding & Using Radio Communications Receivers. 192p., 56 illus. \$3.95
- Basic Electronics Course 384p., 275 illus. \$5.95
- The Fascinating World of Radio Communications. 176p., 80 illus. \$3.95
- Beginner's Guide to TV Repair 176p., 80 illus. \$3.95
- How to Become a Radio Disc Jockey 256p., 25 lessons plus text. \$7.95
- Electronics Self-Taught With Experiments & Projects. 288p., 191 ill. \$4.95
- Model Car Racing by Radio Control 224p., 250 illus. \$3.95

RADIO & TV SERVICING

- Simplified TV Trouble Diagnosis 320p., 229 illus. \$5.95
- Kwik-Fix® TV Service Manual 384p., fully illus. \$5.95
- All-in-One TV Alignment Handbook 304p., 145 illus. \$5.95
- Basic Color Television Course. 420p., 300 illus. \$6.95
- Modern Radio Repair Techniques 260p., incl. 36p. foldout \$4.95
- TV Troubleshooter's Handbook 2nd Ed. 288p., 150 illus. \$2.95
- Home-Call TV Repair Guide 144p., numerous charts \$2.95

HOBBY PROJECTS & PLANS

- Handbook of IC Circuit Projects 224p., 136 illus. \$4.95
- How to Build Solid-State Audio Circuits. 320p., 190 illus. \$5.95
- New IC FET Principles & Projects. 160p., 60 illus. \$3.95
- VHF Projects for Amateur & Experimenter 224p., 271 illus. \$4.95
- Solid-State Projects for the Experimenter 224p., 228 illus. \$3.95
- Practical Solid-State Principles & Projects 176p., 127 illus. \$3.95
- Digital Electronics: Principles & Practice 288p., 191 illus. \$5.95
- Radio Electronics Hobby Projects 192p., 214 illus. \$3.95
- IC Projects for Amateur & Experimenter. 192p., 252 illus. \$3.95
- Transistor Projects for Hobbyists & Students. 192p., 153 ill. \$4.95
- 125 One-Transistor Projects 192p., 125 illus. \$3.95
- 104 Easy Projects for the Electronics Gadgeteer. 160p., 105 ill. \$3.95

COMMUNICATIONS & HAM RADIO

- Commercial FCC License Study Guide. 432p., 150 illus. \$5.95
 - The 2-Meter FM Handbook 312p., 182 illus. \$5.95
 - RTTY Handbook. 320p., 230 illus. \$5.95
 - You're On the Air! 224p., 49 illus. \$7.95
 - Designing & Maintaining the CATV & Small TV Studio. 256p., 102 ill. \$12.95
 - Citizens Band Radio Service Manual. 228p., 96 illus. \$4.95
 - CB Radio Operator's Guide 224p., 246 illus. \$3.95
 - Video Tape Production & Communication Techniques. 256p., 100 ill. \$12.95
- AMATEUR RADIO STUDY GUIDES**
- Novice \$3.95
 - General \$5.95
 - Advanced \$3.95
 - Extra \$4.95
 - Incentive \$3.95

COMPUTER TECHNOLOGY

- Beginner's Guide to Computer Programming. 480p., 364 illus. \$6.95
- Computer Technician's Handbook 480p., 400 illus. \$7.95
- Beginner's Guide to Computer Logic. 192p., 100 illus. \$4.95
- Computer Circuits & How They Work. 192p., 136 illus. \$4.95

AUTO, ENGINE & APPLIANCE REPAIR

- How to Repair Small Gasoline Engines 288p., 124 illus. \$4.95
- Using Electronic Testers for Automotive Tuneup. 256p., 226 illus. \$4.95
- Major Appliance Repair Guide 260p., illus. \$5.95
- Small Appliance Repair Guide 224p., 100 illus. \$4.95
- How to Repair Home & Auto Air Conditioners. 208p., 100 illus. \$4.95
- Refrigeration. 160p., 53 illus. \$2.95

ELECTRONIC TEST EQUIPMENT

- Basic Electronic Test Procedures 416p., 178 illus. \$6.95
- How to Interpret TV Waveforms 256p., 270 illus. \$4.95
- 199 Electronic Test & Alignment Techniques 224p., 130 ill. \$4.95
- How to Use Color TV Test Instruments. 256p., 230 illus. \$4.95
- How to Use Vectorscope-Oscilloscopes & Sweep Marker Gen's. 256p., illus. \$4.95
- Electronic Test & Measurement Handbook. 224p., 100 ill. \$4.95
- The Oscilloscope: Third Edition 256p., 160 illus. \$4.95
- Advanced Techniques for Troubleshooting with the Oscilloscope. 256p., 222 illus. \$4.95

See these helpful books at your parts distributor or clip this ad and order on FREE 10-DAY TRIAL!

NO-RISK COUPON—MAIL ENTIRE AD

TAB BOOKS, Blue Ridge Summit, Pa. 17214
Please send me books checked above.

- I enclose \$
- Please invoice on 10-day FREE trial.
- Send FREE 28-page catalog.

Name _____ Phone _____

Company _____

Address _____

City _____ State _____ Zip _____

SAVE POSTAGE by remitting with order. Foreign add 10%. Pa. residents add 6%. RE-53

Circle 23 on reader service card

UNSCRAMBLE 4-CHANNEL
(continued from page 59)

do we have what appears to be an optimized CD-4 recording which can be compared with a standard stereo release. Even comparing different program segments from "Hair" tells us little, as illustrated in Figs. 29 and 30. Figure 29, program material from the stereo "Hair" with pronounced CF information is reproduced from the CD-4 version in stereo with predominant CF orientation; whether working with corner or front signals the CD-4 to stereo conversion shifts the orientation to the front.

Based on my own listening experiences I feel that optimum discrete 4-channel is

not coincident with optimum stereo, and somewhere along the line the powers in charge will have to make a firm decision. It will, however, be unfortunate if the capacity of CD-4 is compromised for stereo performance. My feeling, based I must admit on my experience with only the JVC "Hair" recording, is that CD-4 is to stereo as stereo is to mono.

Summing up

As far as creating a three-dimensional sound field is concerned, all the various matrix systems and CD-4 work; with CD-4 far and away the winner in creating vast spacial perspectives, though full-logic SQ very closely approximates the discrete system in spacial perspective.

As far as the listener is concerned there is no good reason why there cannot be two distinct incompatible systems, though it is technically feasible to combine both the matrix and CD-4 systems on a single record—and most probably, this is the wave of the future, the not-too-distant future if the various system proponents are willing to share the pie.

But while the giants of industry hassle over who will control the rights to the most popular, income-producing system, what of the consumer who is told to "sit it out," who is warned against purchasing equipment that might be obsolete if something called the "matrix war" is won by a new, yet unannounced matrix system? The truth of the matter is that the consumer is being conned, both by dealers who might want to unload their stock of stereo equipment, and by the system originators who see much in the way of license and royalty fees. The one who can't lose anything is the consumer, he is really sitting on top of the heap and can upgrade to 4-channel now with little possibility of obsolescence.

PTS ELECTRONICS, INC. is proud to announce the **GRAND OPENING** of our new Service Center in **PHILADELPHIA, PA.**

now you too...
...get Fast 8 hr. Service!

\$995

1 YEAR GUARANTEE

Come and see us. PTS Branches are all company owned—No Franchises—we care for our customers. For a **TUNER PART** or **COMPLETE TUNER REBUILT**, come to us, we will take care of your tuner problems like no one else can. **WE'RE PROFESSIONALS—18 years experience made us what we are!**

You owe it to yourself

to try P.T.S. We are the fastest growing, oldest and now the largest tuner service company in the world. Here is what you get:

1. Fastest Service—8 hour—in and out the same day. Overnight transit to one of our plants.
2. Fine Quality! Your customers are satisfied and you are not bothered with returning tuners for rework!
3. Lower Cost! Up to \$5.50 less than other tuners for rework!
4. Friendly, helpful service! We help you do more business—that way we will do more, too. We want your business and we try to deserve it!

Color—Black & White—Transistor—Tubes
—Varactor—Detent UHF

VHF or UHF \$9.95
UV-Comb. \$16.95

Major parts, tubes, transistors—shipping—
charged at net cost
(Dealer net!)

for finer, faster,
... Precision
Tuner Service


FREE JOB CARDS · FREE SHIPPING LABELS
send faulty unit with tubes, shields and all broken parts to:

PTS ELECTRONICS, INC.
P. O. BOX 16855
1921 S. 70TH ST.
PHILADELPHIA, PA. 19142


... Or to any of these strategically located Service Centers:

- | | | | | | | |
|---|---|--|--|--|--|--|
| HOME OFFICE—BOSTON:
PTS ELECTRONICS, INC.
P. O. BOX 272
BLOOMINGTON, IND. 47401
TEL. 812, 824-9331 | EAST:
PTS ELECTRONICS, INC.
P. O. BOX 12955
PHILADELPHIA, PA. 19142
TEL. 215, 724-0999 | NORTHEAST:
PTS ELECTRONICS, INC.
P. O. BOX 3399
SPRINGFIELD, MASS. 01103
TEL. 617, 734-2737 | SOUTHEAST:
PTS ELECTRONICS, INC.
P. O. BOX 3481
JACKSONVILLE, FLA. 32205
TEL. 904, 385-9952 | WEST COAST:
PTS ELECTRONICS, INC.
P. O. BOX 41356
SACRAMENTO, CALIF. 95841
TEL. 916, 482-6220 | SOUTHWEST:
PTS ELECTRONICS, INC.
P. O. BOX 7332
LONGVIEW, TEX. 75601
TEL. 214, 753-4334 | MOUNTAIN:
PTS ELECTRONICS, INC.
P. O. BOX 4245
DENVER, COLO. 80204
TEL. 303, 744-7018 |
|---|---|--|--|--|--|--|

Circle 24 on reader service card

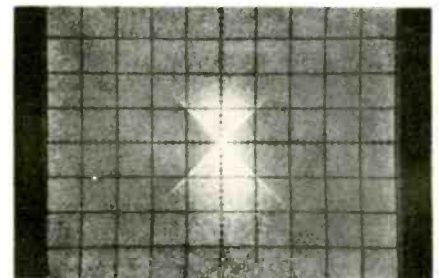

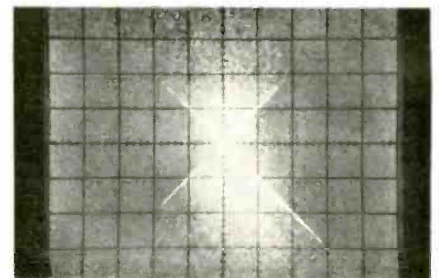
QS RECORD DECODED using Sansul QS-500 decoder/rear amplifier.



ANOTHER BAND of QS record played back through Sansul QS-500 unit.

To explain: The basic additional expense of 4-channel equipments is an extra pair of amplifiers for the rear channels, a two-speaker system and a decoder. With the full-logic SQ decoder now available on an IC chip the decoder expense is a minute part of the price of a new 4-channel amplifier or receiver. Even if a completely different matrix system is declared "the winner" of the so-called matrix war the user will still get a three-dimensional sound field from the full-logic SQ decoder, and someone, somewhere, will produce a decoder for the new matrix system that plugs into an amplifier's tape monitor or auxiliary jacks. Should CD-4 eventually become the prevailing 4-channel system all the user need do is plug in a CD-4 demodulator, and get a new, wide-frequency-range cartridge.

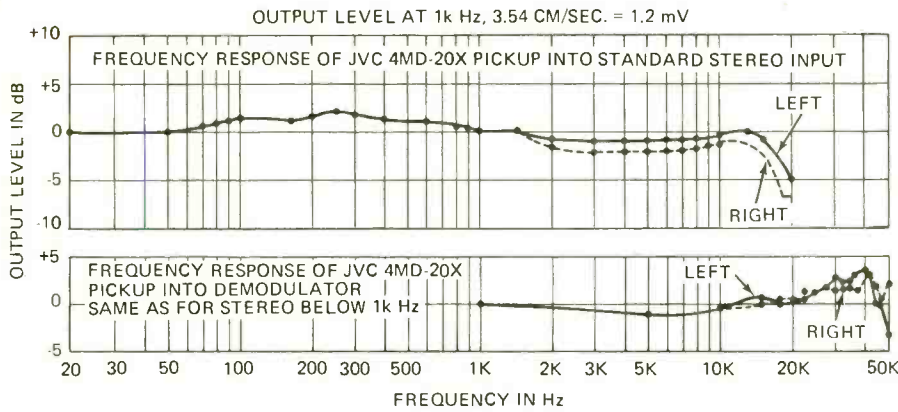On the other hand, suppose our audiophile favors CD-4 and purchases a 4-channel amplifier with built-in demodulator. Later, he decides there are matrix recordings he'd like to hear; again, he need only



JVC 4MD-20X PICKUP EASILY PROVIDED wide frequency response needed for optimum CD-4 performance. Note how lower load resistance and higher capacitance of standard phono input limits high-frequency response.

purchase an add-on matrix decoder.

As long as the consumer has equipment with four amplifiers for front and rear and the usual multitude of input and output "line level" connections, he can accommodate any 4-channel system at minimal extra expense. Even if he uses a stereo amplifier with one of the rock-bottom priced Dynaco-type passive ambient-sound decoders he will get a three-dimensional sound field from any stereo or matrix record.

This idea of add-on equipment is not really so far out as it might appear. Pioneer already offers 4-channel equipment with both SQ and RM decoders—RM meaning Regular Matrix, the term used in Japan for the QS system, and discrete 4-channel inputs for tape and/or demodulators.

Marantz has equipment with a compartment prewired for add-on decoders; you buy the amplifier or receiver now and the decoder if and when needed. Panasonic, one of the CD-4 proponents, has equipment with three different rear-signal phase decoders as well as discrete 4-channel inputs. Most manufacturers of name-brand equipment do the same thing as Lafayette, Fisher, Harman-Kardon and Heathkit, just to name a few, who provide a jam-packed rear apron loaded from end to end with matrix and discrete 4-channel inputs.

So take your choice: any 4-channel system falls into the good-better-best category, and if you're not completely satisfied you can always upgrade to the latest technology with reasonably priced add-ons. **R-E**

ELECTRONIC TECHNICIANS!

Raise your professional standing and prepare for promotion! Win your diploma in

ENGINEERING MATHEMATICS

from the Indiana Home Study Institute

We are proud to announce two great new courses in Engineering Mathematics for the electronic industry.

These unusual courses are the result of many years of study and thought by the President of Indiana Home Study, who has personally lectured in the classroom to thousands of men, from all walks of life, on mathematics, and electrical and electronic engineering.

You will have to see the lessons to appreciate them!

NOW you can master engineering mathematics and actually enjoy doing it!

WE ARE THIS SURE: you sign no contracts—you order your lessons on a money-back guarantee.

In plain language, if you aren't satisfied you don't pay, and there are no strings attached.

Write today for more information and your outline of courses.

You have nothing to lose, and everything to gain!

The INDIANA HOME STUDY INSTITUTE

Dept. RE-5, P.O. Box 1189, Panama City, Fla. 32401

Circle 25 on reader service card

Fastest gun tester of them all... for only \$169*

It's the new RCA WT-333A Television Picture Tube Tester that:

- Tests red, blue and green color guns simultaneously with RCA's unique CR III "SIMUL-TEST" 3-meter system.
- Provides new, more effective 3-step rejuvenation function and newly-designed "no-delay" G1 shorts removal function.
- Reveals H-K leakage other testers may miss, with special high-voltage surge circuit.
- Performs "brightness," "life" and other evaluation-type tests.
- Tests over 1800 TV picture tubes — including RCA's new "Precision In-Line," Sony's "Trinitron" and other in-line types.
- Includes built-in socket plus four socket adapters at no extra charge to cover most of today's picture tubes.

See your RCA Distributor now for more information on the WT-333A. Or write RCA Electronic Instruments Headquarters, Harrison, N.J. 07029.

*Optional Distributor Resale Price



RCA Electronic Instruments

Circle 26 on reader service card

new products

More information on new products is available from the manufacturers of items identified by a Reader Service number. Use the Reader Service Card inside the back cover.

STEREO HEADPHONES model OA-1. Dynamic open-air phones weigh only 10.9 oz. Impedance; 8 ohms. Maximum input power; 300 mW. Sensitivity; 100 dB at 600 Hz. Frequency response; 30 to



19,000 Hz. Distortion: less than 1%. Unit comes with a 7-foot cord and is priced at \$19.95.—**Pickering & Company Inc.**, Sunnyside Blvd., Plainview, N.Y. 11803.

Circle 31 on reader service card

INTRUSION DETECTORS will detect the motion of any mass in three dimensional space using Doppler techniques and both ultrasonic and microwave frequencies. Detection range is as much as 30 feet and several detectors can be combined to cover larger areas. Also available is a stress intrusion detection




system that uses a small solid-state sensor glued to a structural member likely to flex when someone walks across it. These detectors must be used in conjunction with a security controller to process the information from the detectors.—**Defectron Security Systems Inc.**, Bay Street, Sag Harbor, N.Y. 11963.

Circle 32 on reader service card

TELEPHONE ANSWERER, designed for use in the home, answers the phone

when you are not there and records up to 30 messages. All functions are push-button-activated and a message-waiting indicator light indicates when a call has been taped.

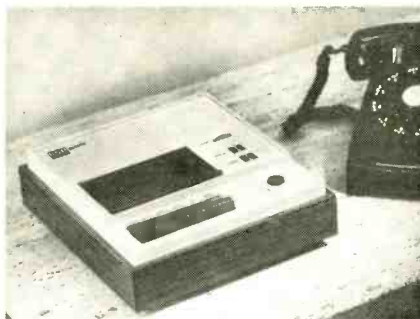
Unit is factory-set to answer after three rings, but can be adjusted to answer af-



ter as many as five rings. Unit is 9" x 10" x 2 3/4". \$99.95.—**BSR-Metrotec**, Blauvelt, N.Y. 10913.

Circle 33 on reader service card

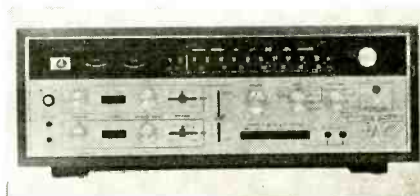4-CHANNEL RECEIVER, QEX-6500 has Variomatrix, an improved version of the Sansui QS regular matrix. Unit automatically accommodates all present 4-channel modes as well as conventional 2-channel stereo and 1-channel mono sources. The new matrix is claimed to offer drastic improvements in front-to-rear separation, greatly enhancing the 4-channel effect.




The amplifier delivers 280 watts of total IHF music power (50 watts at 4 ohms per channel). Frequency response is 20 to 30,000 Hz ± 1 dB. Distortion is less than 0.5% at rated output. IHF sensitivity of the FM tuner is 1.8 mV. \$699.95 complete with walnut-finished cabinet.—**Sansui Electronics Corporation**, 55-11 Queens Blvd., Woodside, N.Y. 11377.

Circle 34 on reader service card

MULTITESTERS. Complete line ranging from compact 1,000 ohms-per-volt experimenters' unit to 100,000 ohms-per-

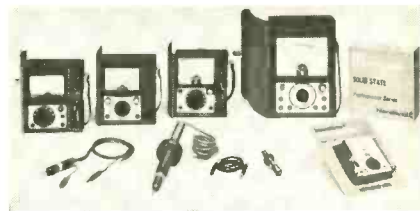
volt professional unit, plus FET professional model with a 10-megohm dc input. Mini-tester model IC-100 is \$7.95. Model IC-200—the 20,000 ohms per volt unit—is \$18.95, has 17 ranges and two color scales. Model IC-300, at \$38.95, has 22 ranges and measures both ac and dc voltages. It is a 30,000 ohms-per-volt unit. Model IC-400 is a 100,000



ohms-per-volt unit, priced at \$49.95, and has 43 ranges. What may be the smallest FET multimeter—the IC-500—provides 17 ranges, has a center zero feature and can measure resistance as high as 1,000 megohms. Its price is \$54.95.—**International Components Corporation** 10 Daniel Street, Farmingdale, N.Y. 11735.

Circle 35 on reader service card

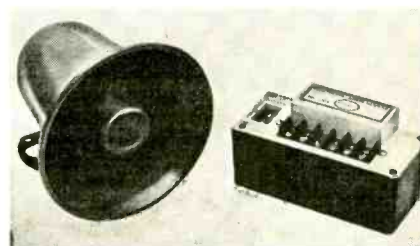ELECTRONIC SIREN, No. 700 Howler. A solid-state sounding device that produces two distinctively different and very loud alarm signals. Unit generates a loud howling (by pulsating) sound similar to that of police and fire sirens as well as a steady-tone alarm signal. The two-channel capability enables the installer to



provide separate signals for burglary and fire.


The Howler draws 700 mA and can be used only with a 6-volt system. It may be powered from batteries, rechargeable battery packs.—**Alarm Device Manufacturing Co.**, 165 Eileen Way, Syosset, N.Y. 11791.

Circle 36 on reader service card

MINI-MOUNTS, LSI-42 pad provides a quick and easy way to breadboard LSI packages with up to 42 pins. Without drilling holes, you can assemble the circuit prototype on any flat surface. Pressure-sensitive adhesive on the back holds it in place while interconnecting wires are installed. Mounts can be

moved or exchanged as the circuit develops yet will remain firmly in place in the finished assembly.

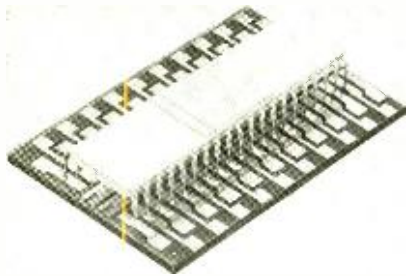
Provides a fast and flexible method of assembling high-performance electronic circuits, including analog, digital, and rf circuits from dc to the GHz re-



gion. Comes in different configurations to fit 14- and 16-pin dip's, 6-12 pin to -5 style cans, transistors, inductors, resistors and other components.—**Christiansen Radio, Inc.**, 3034 Nestall, Laguna Beach, Calif. 92651.

Circle 37 on reader service card

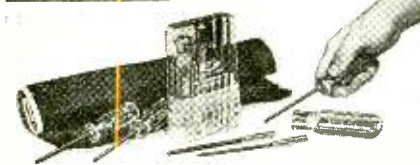SCREWDRIVERS AND BLADES, Series 99 work at any angle and handle hex socket screws which, because of obstructions, cannot be reached straight-on. Has ballpoint tip design that achieves a speed and ease in engaging and turning that is unattainable with



other drivers.

Nine sizes from .050" through 3/16", fixed handle types singly or complete kit that includes regular detachable handle, 4" extension and standup transparent plastic case.—**Xcellite Incorporated**, Orchard Park, N.Y. 14127.

Circle 38 on reader service card

TV TUNER SUBBER, model Mark IV. Improved version of the original subber, this unit not only substitutes for the tuner but also substitutes the 40-MHz i.f. signal at any point in the i.f. chain up to the final i.f. stage. By substituting the signal after the agc stages, the technician can

analyze the agc system without confusion. The receiver will operate normally without overriding the agc line with a fixed bias supply. Now tests can be made on the defective agc system without masking any of the defects with false biasing from the bias box.


Low-impedance output circuit matches older bandpass coupling i.f. inputs, late model link coupled inputs and



any input in the i.f. chain to the final i.f. stage. Not only is output level high, but output bandwidth is maintained so it is virtually impossible to lose the color due to mismatching. Unit is housed in a molded case and is completely self contained and battery powered, \$45.95.—**Castle Television Tuner Service Inc.**, 5710 North Western Avenue, Chicago, Ill. 60645.

Circle 39 on reader service card

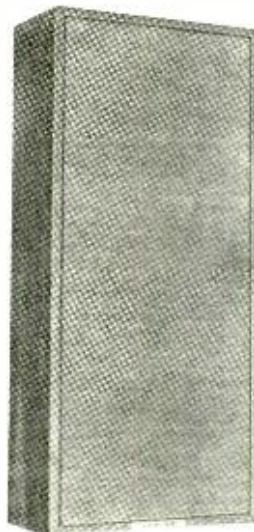SOUND COLUMNS, 10/150 & No. 10/151 for sound reinforcement applications in auditoriums, churches,




schools, etc.

Directional sound dispersion pattern model 10/150—120° horizontal and 40° vertical, frequency response 80-15,000 Hz, program material 24 watts, peak 40

Reduce Car Maintenance Increase Engine Performance.

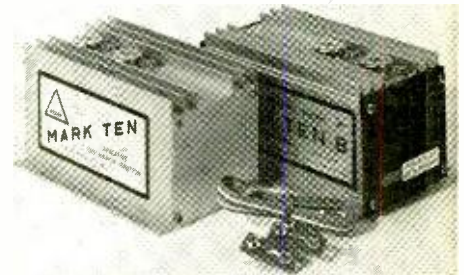Put a Mark Ten Capacitive Discharge Ignition (CDI) System On Your Car.



Even Detroit finally recognizes that electronic ignition systems dramatically increase engine performance. Chrysler is now putting them on their new models. The Mark Ten CDI, the original electronic ignition system, has been giving increased performance with lower maintenance to hundreds of thousands of satisfied customers for over eight years. Install a Mark Ten CDI on your car, boat or truck and eliminate 3 out of 4 tune-ups. Increase gasoline mileage up to 20%. Enjoy improved engine performance. Or put a Mark Ten B on your car. It was especially designed for engines with smog control devices. By reducing combustion contaminants, the Mark Ten B restores power losses caused by these devices. Equipped with a convenient switch for instant return to standard ignition, the Mark Ten B is applicable to ANY 12 volt negative ground engine. Both systems install in 10 minutes with no rewiring. Order a Mark Ten or Mark Ten B CDI today.

Mark Ten (Assembled)	\$44.95 ppd.
Mark Ten (DeltaKit)	\$29.95 ppd.
<small>(Kit available in 12 volt only, positive or negative ground.)</small>	
Mark Ten B	\$59.95 ppd.
<small>(12 volt negative ground only)</small>	


Superior Products at Sensible Prices
Mfg. in U.S.A.

Dept. RE
DELTA PRODUCTS, INC.
P.O. Box 1147 / Grand Junction, Colo. 81501
(303) 242-9000

Please send me free literature.
Enclosed is \$ _____ Ship ppd. Ship C.O.D.
Please send:
____ Mark Ten B @ \$59.95 ppd.
____ Standard Mark Ten (Assembled) @ \$44.95 ppd.
____ 6 Volt: Neg. Ground Only
____ 12 Volt: Specify _____
____ Positive Ground _____ Negative Ground
____ Standard Mark Ten (DeltaKit) @ \$29.95 ppd.
(12 Volt Positive Or Negative Ground Only)
Car Year _____ Make _____
Name _____
Address _____
City/State _____ Zip _____

Circle 61 on reader service card

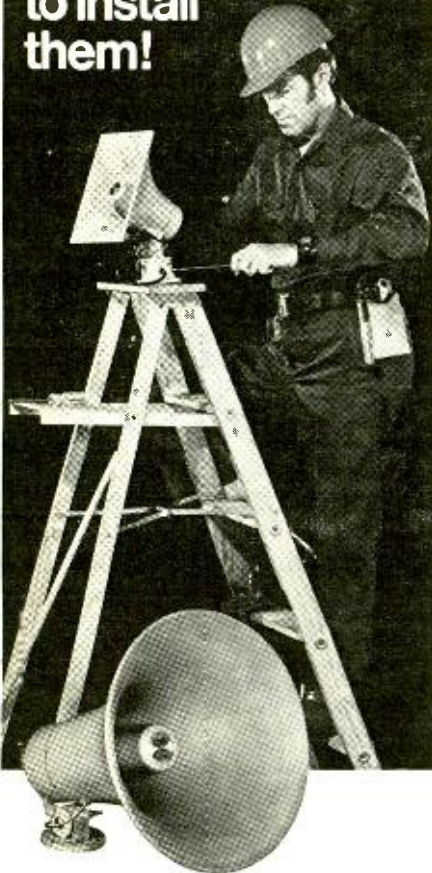If paging speakers all seem about alike to you...wait 'til you get to the top of the ladder to install them!



Electro-Voice Paging Speakers...
If you pay less it may cost you more!

How many trips up the ladder does it take you to finally install a paging speaker? (Be honest and include the times you drop hardware, and the extra trips to change level or positioning). Good news! E-V has made paging speaker installation easier and faster.

Now you need fewer tools and less time to get better sound. Speaker base removes for easy mounting, and it won't fall apart in your hands in the process. There are no screw terminals to short out, pigtailed are already attached, no transformer cover plates to unscrew, and final speaker positioning is simple and positive.

All this and great sound in the bargain. Plus competitive prices on every model. More than a dozen from which to choose. Write today for our catalog or see your nearby Electro-Voice sound merchant.

ELECTRO-VOICE, INC., Dept. 536E
613 Cecil Street, Buchanan, Michigan 49107
In Europe: Electro-Voice, S. A., Rorerstrasse 49, 2560 Nidau, Switzerland
In Canada: EV of Canada, Ltd., Ontario

ElectroVoice[®]

a Gulton
COMPANY

Circle 63 on reader service card


watts; model 10/151—120° horizontal and 30° vertical. Frequency response 60-18,000 Hz, program material 40 watts, peak 80 watts. Model 10/150—24"H x 10½"W x 5¼"D, 15 lbs. Model 10/151—47"H x 10½"W x 5¼"D, 34 lbs.

Oiled walnut veneer finish. Supplied with wall and mounting brackets. Provisions for plug-in line transformer modules.—American Geloso Electronics Inc., 251 Park Avenue South, New York, N.Y. 10010.

Circle 40 on reader service card

BURGLAR ALARM SYSTEMS, Minutemen are a series of radio frequency, radar-type, space alarm systems which emit invisible rays that detect the slightest movement instantly.

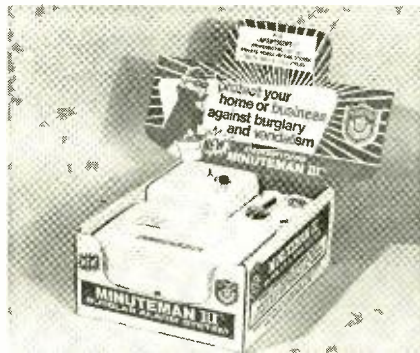Minuteman II can cover more than one room or area with one antenna as its protective pattern can penetrate most building materials.



Space alarms protect against burglaries perpetrated by entering the premises through walls, floor or ceiling.

Contains burglar and fire alarm contacts, remote key switch, automatic resetting, central station capability and tamper-proof cables. \$279.50—GBC Closed Circuit TV Corp., 74 Fifth Avenue, New York, New York.

Circle 41 on reader service card

ULTRASONIC INTRUSION SENSOR, GD-39 is valuable addition to any bookcase because this "book" keeps a vigilant watch on home and belongings.



Between the bogus covers of "The Informer" is a solid-state ultrasonic sensor that can be used to trigger an alarm, turn on a light, or both should it detect movement in the area under surveil-

lance. To install, plug unit into an ac wall outlet, then plug the alarm and light into the receptacles provided. Unit has adjustable sensitivity, automatic and manual reset and a built-in 30-second delay circuit.

Device can be assembled in approximately two evenings and can be positioned to survey an entire room or entranceway. \$49.95.—Heath Company, Benton Harbor, Mich. 49022.

Circle 100 on reader service card

MICROPHONE FLOOR STAND, MS-50 is triangular-based and features wearproof grip-action clutch and scuff-resistant steel base with protective pads and anti-tip provisions for stability.



Adjustable height 35" to 63"; base size 14½"; 6½ lbs.; \$8.75.—Atlas Sound, 10 Pomeroy Road, Parsippany, N.J. 07054.

Circle 42 on reader service card

SOLID STATE AUTOMOTIVE BURGLAR ALARMS, MBA-335 & MBA-335R is contained in a small plastic case with an on/off switch integral with the case and is easily concealed behind the dashboard. Senses any current change in the




car's electrical system. After a 6 to 8-second delay, the alarm triggers, blowing the car's horn in pulsating blasts. An optional siren and parking-light flasher may be connected instead.

The sensing system eliminates the need for an external key switch and separate door trip switches. Quickly and easily connected with a single wire connection to the horn button switch wire and a wire to ground. MBA-335, \$18.95.

for AMC, Chrysler and GM cars; **MBA-335R**, \$20.95, for Ford-made cars and foreign cars that do not have a horn relay.—**Metra Electronics Corp.** 660 McDonald Ave., Brooklyn, N.Y. 11218.
Circle 43 on reader service card

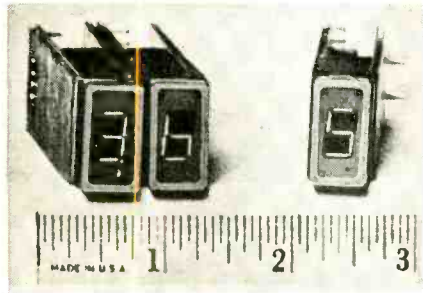MINIATURE DECADE COUNTERS, DEC-100 offers small size (0.5 x 0.88" in viewing plane), operation from a single 5V power supply and a side-by-side plug-in feature that allows fast assembly of any number of digits with no unit-to-unit wiring for main-sequence operations. Uses 7-segment incandescent readouts. Up-down counter has preset capability, frequency response to 32



MHz, and mutual Vcc, ground, load, re-set, strobe, lamp test, up-clock and down-clock signal lines. A simple plug-in adapter is available for use with systems that require a single clock line with independent up-down control logic. Single-unit price \$29.50 (includes readouts).—**Compton Electronics**, P.O. Box 5326, Compton, Calif. 90224.
Circle 44 on reader service card

FIRE DETECTOR/ALARM, Fireguard TBE800 is an all solid state, self-contained flame, smoke and heat detector and alarm. Operates on house current, automatically switches to standby batteries if line power fails.

In high sensitivity position, unit will detect the flame of a striking match up



to 10 feet distance, fire in a waste paper basket up to 30 feet distance. In low sensitivity position, a flame from a waste-paper basket 10 feet away; in total darkness, fire up to 100 feet away. Smoke detector sensitivity: average below 4%; adjustable to 1%. Heat sensitivity: fixed temperature 135°F. (200° F.).

120 Vac at 6A, delayed by about 60 seconds, is provided for turning on a sprinkler system, fire department tele-

RANGE 73

Optional "Portafolio style" carrier. Besides carrying "Range 73" parts or tools, uniquely unfolds flat to four times its own size (from 6"x16" to 24"x16") and converts into a good protector for TV cabinet top when on service calls.—Net \$4.95

bench or flash lights and standard or polarized cheater cords. Also includes a built-in AC outlet for any auxiliary feeding or extension. As the entire unit is made of high voltage insulating materials, it allows close-ups of "hot" areas of a TV chassis. When not plugged into a chassis it can be used conveniently by placing in any position or twisted, looped, hung or inserted in almost any place by the special head, neck or body. Its compactness and safety designs allow seeing and inspecting among transistorized and IC components, or even "X Raying" Solid State Printed Circuit Boards. Price — \$9.95 Net

A useful unit for field or bench servicing. Includes a powerful and flexible spotlight mounted on a rigid Poly Sources Body, with Standard and polarized interlocks. When plugged into a TV or any other chassis it provides AC power to them and automatically supports itself, allowing illumination to any part of the chassis being repaired. It eliminates

Spotlight ext. to 21 in. • Head dia. 1.4 in. • Bulb: 115V. (SP)
 • Power cord: 7 ft. • Weight: 7 oz. • Color: black.

Please mail check or money order "RANGE 73" — Net \$9.95. Optional carrier Net \$4.95. (Add \$1.00 for shipping) (Calif. resident 5% tax) OR: Mail Only \$5.95 with order, balance plus shipping on C.O.D.

Made in USA under National and International PATENT RIGHTS EXCLUSIVELY FOR:
MICHELIN INTERNATIONAL
 P.O. BOX 6743, Los Angeles, California 90022

Circle 64 on reader service card

Why pay an answering service when you can own your own?



Dictaphone has a machine to make sure you never lose another cent through a missed phone call or a garbled message. In fact, we have a whole line of them.

They're called Ansafones. You can buy one outright or possibly lease it for about what you're paying your answering service now. And it works for you 24 hours a day, 7 days a week.

For a free brochure describing how much an Ansafone can help you, mail this coupon now.

▶ Dictaphone

Box L-5-34, 120 Old Post Road, Rye, New York 10580
 Please send me full details of the Ansafone line.

Name _____

Company _____ Phone _____

Address _____

City _____ State _____ Zip Code _____

Ansafone and Dictaphone are registered trademarks of Dictaphone Corp.

Circle 65 on reader service card

FREE ALARM SYSTEMS CATALOG



Full line of professional burglar and fire alarm systems and supplies. 80 pages, 400 items. Off-the shelf delivery, quantity prices.



mountain west alarm
4215 n. 16th st.
phoenix, az. 85016

Circle 66 on reader service card

A LITTLE SQUIRT stops all the noise.

A squirt of Quietrole from the handy Spray Pack silences any moving T.V. part. Cleans as it lubricates, too. Guarantees quiet, trouble-free operation. Absolutely safe for any black and white or color set. Try it and see why it's preferred by top servicemen everywhere.

Also available in bottles, and the new silicone—"Silitron."



Product of

QUIETROLE

COMPANY

Spartanburg, South Carolina

Circle 67 on reader service card

phone dialer, police type sirens, bells or lights.—**Three • B • Electronics Inc.**, 5404 Eighth Avenue, Brooklyn, N.Y. 11220.

Circle 45 on reader service card

TAPE-RECORDER SPEED CHECKER, LFM-30 will check tape recorder speeds using 1, 2, 3, 4, 5, 6, 7, 8 and 9 kHz test tones. Has test range of -3% to +3% with an input level of 100 mV to 10 mV rms. Input impedance is 150,000 ohms. Has an accuracy of $\pm 5\%$ of end scale.



Is effective for tape cassette, tape cartridge and reel-to-reel recorders. Comes with standard 4-kHz test tape and carrying case. 11"H x 3"W x 2 1/2"D; 2 lbs., \$129.95.—**Leader Instruments Corp.**, 37-27 27th Street, Long Island City, N.Y. 11101.

Circle 46 on reader service card

FIRE/INTRUDER ALARM SYSTEM, Challenger contains magnetic door/window guards that trigger alarm when door or window is moved. Fire sensors trigger alarm when temperature reaches 130°F.

System contains: 6 door/window guards, 4 fire sensors, alarm, electronic



control unit, master panel, 12 push-in wire connectors, 250 feet of insulated, shock-proof, ultra-fine, high-strength steel wire and illustrated step-by-step instructions. \$95.00.—**Crismar Corporation**, Johnson Avenue, Plainville, Conn.

Circle 47 on reader service card

BOOKSHELF SPEAKER, Project 100 uses an air-suspension type enclosure housing a 10-inch woofer and a 1 1/2 inch hemispherical dome combination mid-range and tweeter. Maximum input power of 35 watts. With frequency response down to 30 Hz.

Pix-Mate™ the crt tester you can afford to take along

only... \$34.95



- A quality CRT tester with individual test for each gun.
- Compare guns for emission.
 - Test for leakage and shorts.
 - Legible 3 color scale.
 - Compact, portable, rugged.
 - Avoid recalls, check the CRT on every call.

WRITE US!

TeleMatic



take along the time savers

- PIX-MATE • CRY-S-MATE • GEN-MATE
- SOUND-MATE • TRACE-MATE

The Caddy-Mate Line.

2245 PITKIN AVE., BROOKLYN, N. Y. 11207


Circle 68 on reader service card

Fixed L-C network has a crossover at 1,000 Hz. Voice coil impedance is 8



ohms. 13"W x 23"H x 10 1/2"D; 40 lbs., \$99.95.—U.S. Pioneer Electronics Corp., 178 Commerce Road, Carlstadt, N.J. Circle 48 on reader service card

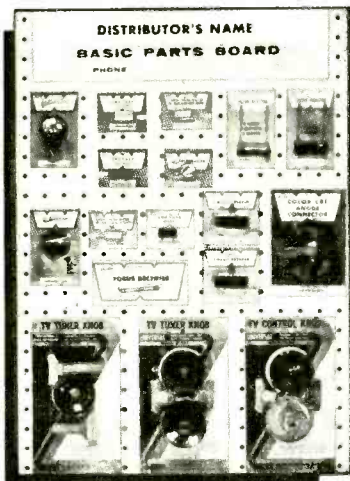BASIC PARTS BOARD, BP contains 62 pieces of the most frequently needed replacement parts used by the TV/radio service industry. Merchandise is displayed on a 17" x 24" white pegboard consisting of fuses, fused resistors, focus rectifiers, circuit breakers, pix-tube an-



ode connectors, current limiting resistors and the completely universal TV channel selector, fine tuning and control knobs.—Workman Electronic Products Inc., P.O. Box 3828, Sarasota, Fla. 33578. R-E

Circle 49 on reader service card

There's only one thing worse than finding out you have cancer.

Not finding out.

We want to wipe out cancer in your lifetime.

Give to the American Cancer Society



12 REASONS YOUR CAR NEEDS A TIGER 500

Instant starting in any weather - Eliminates tune-ups - Increases gas mileage - Increases horsepower 15% - Improves acceleration & performance - Spark plugs and points last up to 70,000 miles - Reduces engine maintenance expense - Amplifies spark plug voltage to 45,000 volts - Maintains spark plug voltage to 10,000 RPM - Reduces exhaust emissions - Dual ignition switch - Unconditional guarantee for original owner - Installs in 10 minutes on any car with 12 volt negative ground - No rewiring - Most powerful, efficient and reliable Solid State Ignition made.

SATISFACTION GUARANTEED or money back.

Assembled \$49.95
Post Paid in U.S.A.

Send check or money order with order to:

Tri-Star Corporation

Dept. R, P. O. Box 1946
Grand Junction, Colorado 81501

DEALER INQUIRIES INVITED
Circle 69 on reader service card

why pay retail?

Buy from us, save money on

hifi

Choose from over 100 name brands, and save on time and freight charges by ordering from the location nearest you!

Midwest Hifi

WHOLESALE & MAIL ORDER DIVISION

Send for our free catalog!
2455b Wisconsin Ave.,
Downers Grove, Ill. 60515
(Attn Ralph Edwards)
3309 E. J W Carpenter Frwy.,
Irving, Tex. 75060
(Attn Ron Elkins)

Circle 70 on reader service card

What do you think of a guy who bought a \$150 turntable to go with a \$75 amplifier and a pair of \$40 speakers?

Smart. Audio "accountants" have formulas for appropriating funds to the various components in a stereo system. Usually they recommend about 20% of the total to take care of the turntable and cartridge, which is OK if your total is \$500 or more.

But what do you do if you really love music, and have a 10-LP-per-month habit that leaves you with peanuts to spend for hardware.

If you followed the accountants' advice you might end up with a \$5 or \$10 cartridge in a \$30 changer. It would be arithmetically compatible, and might even sound OK. But later on, when you can afford that monster system

you've had your eyes on, you might find that your records sound worse than they did on your old cheapie system —because the inexpensive changer, with heavy stylus pressure and unbalanced skating force, was grinding up the grooves. And your cheap amp and speakers wouldn't let you hear the damage.

And now that you've spent a pile on high power, low distortion electronics, and wide-range speakers, you have to spend another pile replacing your records.

So, if you think you will want the best amplifier and speakers later, be smart and get the best turntable now... the BSR 810. Send for detailed specifications. BSR (USA) Ltd., Blauvelt, N.Y. 10913.



Circle 71 on reader service card

SPECIAL OF THE MONTH MEMORIES

E	1101	256 Bit RAM MOS	\$2.45	Ea.
U	8223	Field Programmable Rom	\$5.95	Ea.
	7400	7401 7402 7403 7404 7405	\$.20	Ea.
	7408	7410 7420 7430 7440 7460	\$.20	
	74L00	\$.40 74L71 \$.50	Ea. 7491	\$1.05 Ea.
	74L02	\$.40 74L72 \$.50	7492	.85
	74L04	\$.40 74L73 .75	7495	.85
	74L20	\$.40 74L74 .75	74123	.99
	74L30	\$.40 7474 .30	74154	1.75
	7413	.95 7475 .69	74160	1.65
	7441	1.10 7476 .45	74161	1.65
	7442	1.10 7483 1.20	74165	1.65
	7443	1.10 7485 1.20	74181	4.50
	7446	1.40 7486 .45	74192	1.65
	7447	.95 7489 3.25	74193	1.65
	7448	1.25 7490 .69		

LINEAR SPECIALS

LM300	Positive Volt Reg.	Ea.	\$.95
LM301	Hi Performance Amp	Ea.	.45
LM302	Voltage Follower	Ea.	.95
LM308	Micro Power Op. Amp.	Ea.	1.50
LM309H	(T05) 5 Volt 200Ma V Reg		.95
LM309K	(T03) 5 Volt 1 Amp Reg	Ea.	1.95
LM311	(T05) Comparator	Ea.	1.50
LM320	(T03) -5.2V Neg. Reg.	Ea.	3.95
LM320	(T03) -15V Neg. Reg.	Ea.	3.95
LM380	(Dip) 2 Watt Audio Amp.	Ea.	1.45
NE565	Phase Lock Loop	Ea.	2.95
NE566	Function Generator	Ea.	2.95
NE567	Tone Decoder	Ea.	2.95
707	Op Amp	\$.35 Ea. or 10 for	3.00
723	Volt Reg.	.95 Ea. or 5 for	4.00
741	Freq. Comp	.45 Ea. or 10 for	4.00
747	Dual 741	.95 Ea. or 5 for	4.00

EXTRA SPECIAL
5001 LSI Calculator Chip
with complete info Each \$7.95

LED SPECIALS

Man III	Type Readouts	Ea.	2.95
Man IV	Type 2/10 character	Ea.	3.25
MV50	Type height	.29 Ea. or 4/	1.00
MV5040	Type large Visable Red	.40 Ea. or 3/	1.00

Min. Order \$4.00 Prepaid in U.S.
Orders filled within 3 days after receipt
Note: add .50 per spec sheet for item priced at less than \$1.00 each.

INTERNATIONAL ELECTRONICS UNLIMITED
P.O. Box 2238
Walnut Creek, Calif. 94595

Circle 72 on reader service card

TUNE-IN

on these TOP-RATED "NO-NOISE" PRODUCTS

PROVEN PERFORMANCE FOR COLOR AND B/W

FIRST, simply spray parts with **SUPER SPRAY BATH**.
Dissolve and flush away grease, dirt, oil and oxidation—penetrative action cleans and restores all component parts.

THEN, follow with **VOLUME CONTROL AND CONTACT RESTORER**
for special attention to volume controls, push button assemblies, band switches, relays and other electrical contacts.

"NO-NOISE" products are guaranteed non-flammable, no carbon tet, non-toxic -- safe for plastics.

For Tuners (Incl. wafer type) use **TUNER TONIC With Perma Film OR SUPER LUBE** for further cleaning and lubrication — economical, a little does a lot.

Other Famous "NO-NOISE" Products
• EC-44 • Frigid-Air • Tape-Recd Head Cleaner

Often imitated but never duplicated

ELECTRONIC CHEMICAL CORP.
813 Communipaw Avenue Jersey City, N. J. 07304

Circle 73 on reader service card

new lit

All booklets, catalogs, charts, data sheets and other literature listed here with a Reader Service number are free. Use the Reader Service Card inside the back cover.

ALARM EQUIPMENT CATALOG, M-73 is an 80-page catalog that describes over 400 intrusion and fire alarm products. Many are UL listed.

The alarm equipment ranges from relatively simple kits with instructions to the latest ultrasonic, radar and infrared intrusion detectors. Products are described in some detail regarding application, principle of operation and specifications.

A general alarm system discussion is followed by 8 pages of applications notes on how to use the many detector options. Some basic installation procedures are presented. For custom installations, several diagrams are presented to permit design and fabrication of basic systems.—**Mountain West Alarm Supply Co.**, 4215 North 16th Street, Phoenix, Ariz. 85016.

Circle 50 on reader service card

LOW-VOLTAGE LOW-CURRENT LAMP CATALOG includes photos, diagrams and complete specifications for such Muralites as standard lamp assemblies, Bi-Pin assemblies, lens caps, fuse type, pigtail type, neon and high brightness lamps.—**Mura Corporation**, 50 South Service Road, Jericho, N.Y. 11753.

Circle 51 on reader service card

INTEGRATED-CIRCUITS CATALOG, WR-125F. 36-page catalog gives salient information on the broad line of linear integrated circuits, Hall effect integrated circuits, functional electronic circuits, thin-film resistor arrays, thin-film hybrid circuits and digital integrated circuits.—**Sprague Electric Co.**, 81 Marshall Street, North Adams, Mass. 01247.

Circle 52 on reader service card

BURGLAR ALARM CATALOG. 6-page booklet contains sensors, alarms, accessories, control center/systems, automotive security, auto alarms, demonstrators and complete price list.—**EICO Electronic Instrument Co. Inc.**, 283 Malta Street, Brooklyn, N.Y. 11207.

Circle 53 on reader service card

Write direct to the manufacturers for information on items listed below:

TUNER REPLACEMENT GUIDE & PARTS CATALOG No. III. 80-page book enables reader to pinpoint the tuner problem quickly and easily find the right replacement part. Includes uhf tuner parts, tuner chemicals and tools, blow-ups for vhf and uhf tuners, replacement guide for antenna coils and shafts. 2,000 available exact-replacement tuners are listed under original manufacturer number for easy exchange. \$1.00 (redeemable on first minimum parts order).—**PTS Electronics, Inc.**, P.O. Box 272, 5233 Hwy. 37 S., Bloomington, Ind. 47401.

R-E

South River's New Improved EAVE MOUNTS

FOR SUPPORTED MAST INSTALLATION
SLOTTED WASHER HEAD LAG SCREW SIMPLIFIES INSTALLATION

FOR GROUND-UP TELESCOPING MAST INSTALLATIONS UP TO AND INCLUDING 50 FT. MASTS
Available in Hot-Dip Galvanized Steel or Aluminum

TEARDROP SCREW HOLES FOR MOUNTING EASE

RIVETED CONSTRUCTION

SERRATED TEETH HOLD MAST

EXCLUSIVE SWIVEL MAST SUPPORT (Back View)

WRITE FOR FULL DETAILS.

Choice of: 30", 48" or 60" models (size indicates spread of lower bracket).

SOUTH RIVER METAL PRODUCTS CO., INC.
SOUTH RIVER, NEW JERSEY 08882

Circle 74 on reader service card

For faster service

USE ZIP CODE

on all mail

next month

JUNE 1973

■ Build A Phone Sentry

\$30 gadget is used with one cassette tape player to answer your phone with a pre-recorded message. Use it with two cassette machines to take messages from callers.

■ 4-Channel Matrix Logic Systems

Leonard Feldman, R-E's new Contributing Hi-Fi Editor reports on the latest developments in matrix logic systems that enhance front-to-rear separation. If you want to know how and what logic does for 4-channel stereo, mark this story *must reading*.

■ VTR's; Where They Stand

Popularity and use of video tape recorders is soaring. Here's an overview of what's happening in this exciting field and how it will affect you.

■ Test IC's With A Vtm

Bob Middleton shows how you can accurately check out an IC using everyday test gear you already own.

PLUS

**R-E's Guide For Replacement Transistors
Step-by-Step Troubleshooting
Jack Darr's Service Clinic
Technical Topics**

MOVE AHEAD from Technician to ENGINEER

Advance beyond the technician level

Become an electronics engineer


Your technical experience can be a valuable asset in advancing your electronics career to the *engineering* level. By adding engineering training and a college degree to your experience, you can *move up* to greater opportunities.

After three years of reduced demand, electronics engineering is now beginning to BOOM! It is predicted that there will be twice as many engineering jobs available by 1976 as there will be graduates to fill them.

Grantham School of Engineering is a college-level institution, specializing in teaching electronics, computer science, and supporting subjects, mainly

BY CORRESPONDENCE

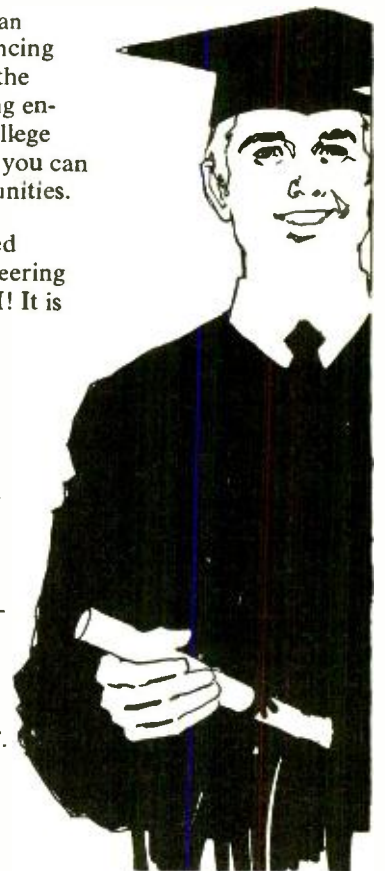You may earn your A.S.E.T. degree by correspondence, and then earn your B.S.E.E. degree thru additional training in residence.



Grantham School of Engineering

1505 N. Western Ave.

Hollywood, Calif. 90027

Mail the coupon below for our free Bulletin

Grantham School of Engineering RE-5-73

1505 N. Western Ave., Hollywood, Calif. 90027

Please mail me your free Bulletin, which explains how the Grantham educational program can prepare me for my Degree in Electronics Engineering.

Name _____

Address _____

City _____ State _____ Zip _____

I have been in electronics for _____ years.

Circle 75 on reader service card


MAY 1973 • RADIO-ELECTRONICS 91

It's fun to build quality. Heathkit Electronics

For full spectrum color, black & white



GR-900 **599^{95*}**
(LESS CABINET)

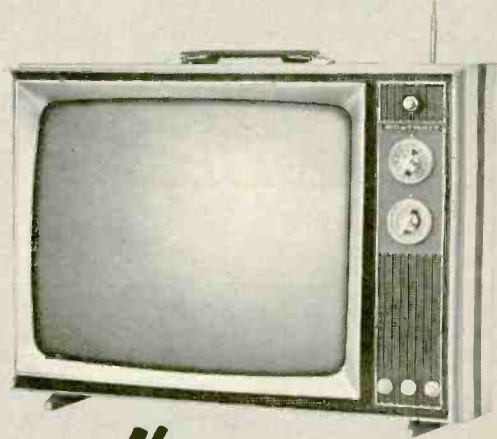

New
GR-1900 **179^{95*}**
(INCLUDES CABINET)

...and staying out of the red.



New
IC-2108
79^{95*}



New
IC-2009
92^{50*}

(INCLUDES CHARGER)

See them all at your Heathkit Electronic Center . . . or send for Free '73 Heathkit Catalog.

HEATHKIT ELECTRONIC CENTERS

ARIZ.: Phoenix, 2727 W. Indian School Rd.; CALIF.: Anaheim, 330 E. Ball Rd.; El Cerrito, 6000 Potrero Ave.; Los Angeles, 2309 S. Flower St.; Pomona, 1555 Orange Grove Ave. N.; Redwood City, 2001 Middlefield Rd.; San Diego (La Mesa), 8363 Center Dr.; Woodland Hills, 22504 Ventura Blvd.; COLO.: Denver, 5940 W. 38th Ave.; CONN.: Hartford (Avon), 395 W. Main St. (Rte. 44); FLA.: Miami (Hialeah), 4705 W. 16th Ave.; GA.: Atlanta, 5285 Roswell Rd.; ILL.: Chicago, 3462-66 W. Devon Ave.; Downers Grove, 224 Ogden Ave.; IND.: Indianapolis, 2112 E. 62nd Ave.; KANSAS: Kansas City (Mission), 59 J Lamar Ave.; MD.: Baltimore, 1713 E. Joppa Rd.; Rockville, 5542 Nicholson Lane; MASS.: Boston (Wellesley), 165 Worcester St.; MICH.: Detroit, 18645 W. Eight Mile Rd. & 18149 E. Eight Mile Rd.; MINN.: Minneapolis (Hopkins), 101 Shady Oak Rd.; MO.: St. Louis, 9296 Gravois Ave.; N.J.: Fair Lawn, 35-07 Broadway (Rte. 4); N.Y.: Buffalo (Amherst), 3476 Sheridan Dr.; New York City, 35 W. 45th St.; JERICO, L.I., 15 Jericho Turnpike; ROCHESTER, Long Ridge Plaza; OHIO: Cincinnati (Woodlawn), 10133 Springfield Pike; CLEVELAND, 5444 Pearl Rd.; PA.: Philadelphia, 6318 Roosevelt Blvd.; Pittsburgh, 3482 Wm. Penn Hwy.; TEXAS: Dallas, 2715 Ross Ave.; Houston, 3705 Westheimer; WASH.: Seattle, 221 Third Ave.; WIS.: Milwaukee, 5215 Fond du Lac.

Heathkit GR-900 25V Color TV with total-tuning convenience.

It's the most advanced TV circuitry you can build. Yet everything goes together with traditional Heathkit simplicity. And the built-in convergence board and test meter for at-home maintenance and self-service add further savings over the life of the set. With the GR-900 you pre-set any 12 UHF stations for positive pushbutton power tuning, and you can scan both UHF and VHF channels in either direction. An ultra-rectangular black matrix tube, voltage controlled varactor UHF tuner, MOSFET VHF tuner and an exclusive angular tint control for consistently better flesh tones combine to produce an absolutely brilliant color picture. There are four preassembled and finished cabinets to choose from, plus the Heathkit Wall Mount and wireless remote control option. Any way you look at it, the Heathkit GR-900 is one of the most rewarding kits you can build. Mailing weight, 125 lbs.

New Heathkit Solid-State B&W 19V Portable TV — a truly extraordinary set

The new Heathkit GR-1900 is like no other B&W portable! With advanced solid-state "modular" design — most circuitry mounts on just four plug-in boards. Dependable solid-state circuitry, including 23 transistors, 13 diodes, 2 ICs, and just 2 tubes; picture & high voltage. Total detent tuning on all 70 UHF channels as well as VHF. "Instant-On" for sound and pictures at a touch — plus other "big-set" front panel control features such as VHF/UHF fine tuning; brightness; contrast; master on/off; vertical hold; AGC; and height. New Ultrarectangular picture tube for a full 184 sq. in. viewing area. Automatic Vertical Linearity for rock-steady pictures — a feature usually found only on expensive color sets. Dual-Controlled AGC for improved picture/noise ratio — another "big-set" bonus feature. Extra-wide Video Bandwidth for theater-quality black-and-white pictures. Four circuits (most sets have only 3) in the grounded base VHF tuner for superior cross modulation in dense station areas. With all this, the GR-1900 is a kit even the novice can build. Both tuners come preassembled and aligned, transistors & ICs plug into sockets, and all chassis wiring is color coded. For truly extraordinary performance in B&W TV, you've got it all in the GR-1900. Mailing weight, 56 lbs.

New Heathkit Desk-top Calculator — an outstanding kit-form value.

The Heathkit IC-2108 features a sleek, low-profile case with bright 1/2" readout tubes in an 8-digit display — one of the largest, most legible in the industry. The color-coded keyboard is human engineered to slope down to the desk so you can rest your arm while using. And the IC-2108 is loaded with features: Four arithmetic functions. Floating and fixed decimal. Constant key. Chain calculation capability. Clear display key. Entry and result overflow indicators. Negative number indicator. 120/240 VAC operation. In addition, the IC-2108 is amazingly simple to build. Two spare evenings will do it. Kit IC-2108, 4 lbs.

New Heathkit "Pocketable" Calculator — you can service it yourself

The Heathkit IC-2009 is first a self-contained portable, weighing in at 11 oz. and small enough to fit in your coat pocket, but it's a desk-top calculator too. The internal Nickel-Cadmium battery gives five to eight hours use between charges. Or, the IC-2009 can be left connected to its charger for indefinite operation. And unlike other pocket calculators, the Heathkit IC-2009 is designed to be maintained by you. Plug-in keyboard and display boards, plus a complete troubleshooting section in the manual, make it easy — and economical. Add up the features for yourself: 8-digit capacity. Four arithmetic functions. Full floating decimal. Constant key. Chain calculation capability. Clear entry key. Entry and total overflow indicators. Negative answer indicator. Battery-saver circuitry. Low battery indicator. Tactile-feedback keyboard for positive entry indication. Order your IC-2009 now. You'll have it built in two or three evenings. Mailing weight, 3 lbs.



Heathkit 4-Channel Amplifier with Universal Decoder... 359.95*
(less cabinet)

You select discrete 4-channel, or switch-in the "Universal" decoder for reproduction of all the matrixed 4-channel discs now on the market, plus "derived" 4-channel from conventional stereo. Four solid-state amplifiers produce 200 watts (4x50 IHF) into 8 ohms, with power bandwidth on all channels from less than 5 Hz to greater than 45 kHz at 0.25% distortion. Kit AA2010, 37 lbs. AAA-2004-1, pecan cabinet, 7 lbs. 24.95*




Heathkit Universal Decoder for 4-channel conversion... 39.95*

Reproduces all matrixed discs, plus "derived" 4-channel from conventional stereo materials. Plug it into your receiver's tape matrix circuit, add a second stereo amp and speakers and you're set. Kit AD-2C22, 4 lbs.



New Heathkit Ultrasonic Intrusion Alarm looks like a book... 49.95*

Disguised as an ordinary library book, this novel device fits unobtrusively anywhere in the home. Transmitter disperses a 41 kHz signal which bounces off walls and returns to the receiver where it's monitored for any change in amplitude. Triggers lights and any conventional alarm device — just plug them into AC outlets on the rear panel. Can be installed anywhere there's a 120 VAC outlet. An enjoyable 2-evening kit. Kit GC-39, 4 lbs.

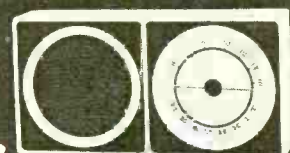

New Heathkit GR-1008 AM Radio can be built in one evening... 14.95*

A smartly styled, great sounding solid-state radio that makes a great introduction to Heathkit building. Eight-transistor circuitry mounts on one printed board, big 3 1/2" speaker mounts in high impact plastic case. If you've never built a kit before you can probably have this one together in one fun evening. Uses 9-volt battery (not supplied). Order the Heathkit GR-1008 for yourself or the kids. Kit GR-1008, 2 lbs.

HEATH
Schlumberger

SEND FOR YOUR FREE 1973 HEATHKIT CATALOG — it describes more than 350 Heathkit projects

HEATH COMPANY, Dept. 20-5
Benton Harbor, Michigan 49022

Please send FREE Heathkit Catalog.
Enclosed is \$ _____, plus shipping.

Please send model(s) _____

Name _____

Address _____

City _____ State _____ Zip _____


*Mail order prices; F.O.B. factory CL-464

Circle 100 on reader service card

WANTED... BURGLAR & FIRE PROTECTION


by

audiotex

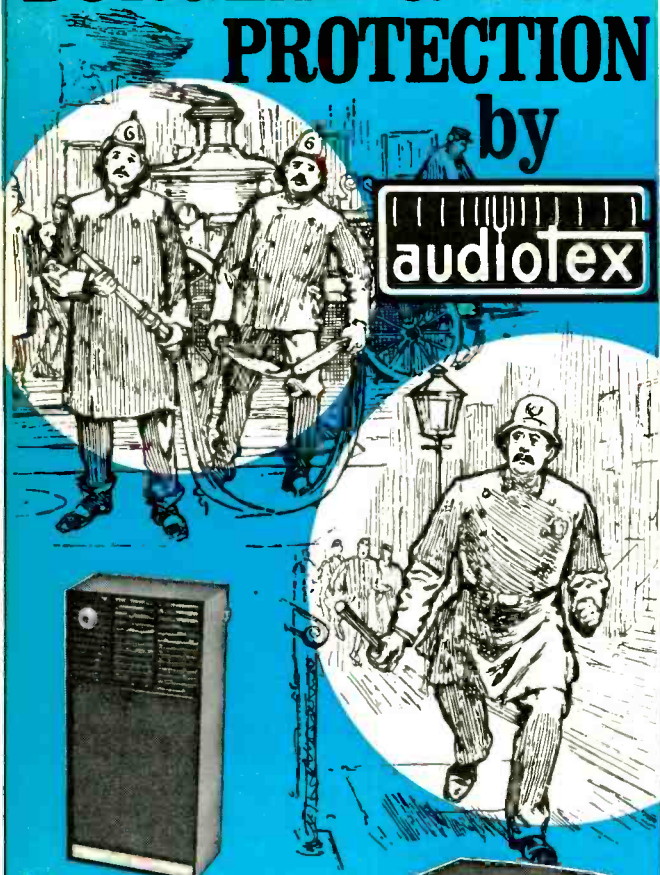

Magna-Sentry
BURGLAR & FIRE ALARM
Low cost protection for you
and your valuables.

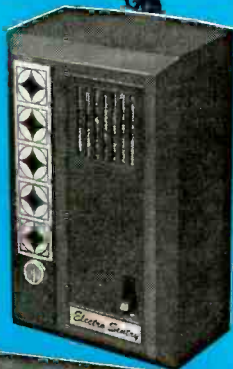Electro-Sentry
BURGLAR ALARM
Professional type
Do-It-Yourself protection
for your home and business



Ultrasonic-Sentry
BURGLAR ALARM
Protects you with harmless invisible ultrasonic waves.

Take this ad to your electronic supplier for your copy
of "SECURITY AND YOU" for only 50¢.

GC ELECTRONICS
ELECTRONICS DIVISION OF HYDROMETALS, INC.
ROCKFORD, ILLINOIS 61101 U.S.A.


MAGNAVOX T952 CHASSIS

Elimination of 3.58-MHz beat pattern: Later versions of this chassis have a 33-pF capacitor across L19 in the delay line circuit. This capacitor identified as C75 (Part number 250508-33050) can be added to earlier versions of the chassis to reduce beat pattern.

High-voltage rectifier lead dress: In some cases of flyback transformer failure in this chassis, there were indications of improper lead dress. You should check to see that the high-voltage rectifier leads are dressed away from the flyback high-voltage (tertiary) winding. Also, the anode lead must be dressed away from the tertiary winding and the anode cap of the 3DB3 tube.—*Magnavox Service News*

TAPE CASSETTE SERVICE HINT

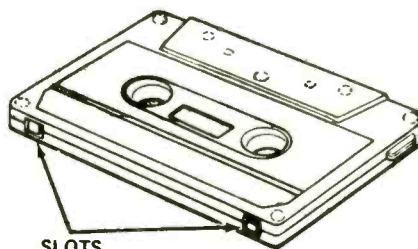Tape cassettes have tabs in small slots (see drawing) that can be removed by the user to prevent accidental erasure or re-recording on the tape.



SLOTS

Some tape recorders are showing up in service shops with a complaint of "Will not erase or record" because the user removed the tabs and has forgotten about it.

If you get one of these complaints, look for the tabs on the user's cassettes. If none were supplied by the user, try a known good cassette before looking for fault in the set.—*Admiral Service News Letter*

OUR GANG-

QUALITY SILICON RETRO-FIT RECTIFIERS



ELECTRICAL RATINGS

RCC TYPE No.	I_o $T_a = 55^\circ\text{C}$ Aav	PRV KVpk	MINIMUM BVR 25°C KVpk	Isurge 1~ Apk	PRICING 1-4 QUANTITIES \$
HVK1143/250R	0.2	60.0	65.0	50	86.50
HVK1130/371	0.25	25.0	30.0	50	33.50
HVK1115/575	1.5	15.0	18.0	50	18.00
HVK1144/575	1.5	15.0	18.0	125	60.00
HVK1145/576	0.5	25.0	30.0	50	27.25
HVK1126/673	1.5	15.0	18.0	125	60.00
HVK1109/866	0.5	10.0	12.0	50	7.00
HVK1139/866	0.5	10.0	17.0	50	13.00
HVK1110/872	1.25	10.0	12.0	60	13.10
HVK1138/872	1.25	10.0	17.0	60	17.80
HVK1117/869	2.5	20.0	28.0	125	96.00
HVK1121/8008	1.25	10.0	12.0	60	13.10
HVK1146/8008	1.25	10.0	17.0	60	17.80
HVK1129/8020	0.10	40.0	42.0	50	38.50

RECTIFIER COMPONENTS corp.
1112 LOUSONS ROAD UNION, NEW JERSEY 07083

Circle 77 on reader service card

SECURITY SYSTEMS

(continued from page 37)

ment can be adjusted to not "see" a moving elevator. Venetian blinds must not be allowed to wave back and forth because of breezes. These and similar problems can be avoided by expert planning.

A likely area for this type of equipment is where there is a great deal of machine or background noise. Since the radio waves are not affected by sound, this type of equipment will work when ultrasonic will not.

The radiation field is difficult to detect and an intruder may not even realize that he has tripped such an alarm. The equipment is compact and can be installed in much less time than many other types of equipment. Coverage is good when the equipment is properly installed, and it is unaffected by light or air currents. Equipment is easily moved when necessary.

The chief fault is that the waves go through walls into areas not intended for protection. People or vehicles going by outside the protected area can unknowingly cause frequent nuisance alarms.

Spot protection devices

In conjunction with perimeter protection and space protection, spot protection is important where a specific valuable object is to be safeguarded. While there is a bewildering array of electronic security devices on the market, a certain few are best suited to provide this sort of protection.

Capacitance alarms

One of the most successful applications of electronic security is typified by the class of equipment known as "proximity" or "capacitance" alarms. With this type of alarm, the protected object (safe, cabinet, etc.) acts as a unit of the tuned circuit. If an intruder wanders into the region of the protected object, the circuit will be thrown "out of kilter" and an alarm will sound.



CAPACITANCE ALARM can provide spot protection for a safe or other single item.

This type of equipment is very flexible and may be used to connect several safes or files in the same area to a single system. Unlike space alarm systems, the protective field on the object is kept down to a range

of not more than a few inches from the surface of the object. Very close proximity will set off the alarm, but there is a minimum chance of accidental alarms caused by authorized persons passing within a few feet of the protected object with no intention of intrusion.

When used as intended, this type of equipment offers many advantages. It is simple to install and is extremely flexible. Almost any ungrounded metallic object can be so protected, including windows and doors. The protection so provided is invis-



MINUTEMAN RADIO-FREQUENCY system by GBC for complete area protection.

ible so that the thief never knows which object is safeguarded and which isn't. The equipment can easily be transferred from one object or location to another.

The major problem with this equipment is sensitivity to nuisance alarms. **R-E**



Think of it as the best tester in your bag. Only \$299

Now you can get a high performance Model 8000A Digital V.O.M. from Fluke, America's foremost maker of quality digital multimeters, especially designed for TV, radio, stereo and audio service. No other digital V.O.M. gives you the resistance range to check breakers and switches, the high resolution voltage to look at emitter base and other transistor voltages, excellent ac accuracy and full accuracy with a 30 second warm-up.

Measures in 26 ranges 100 μ V to 1200 V, 0.1 μ A to 2A, and 100 milli Ω to 20 meg Ω with a basic dc accuracy of 0.1%. Full year guarantee. Low cost options include rechargeable battery pack, printer output, deluxe test leads, HV, RF & 600-amp ac current probes, carrying case, and rack mount. Unique self zero eliminates offset uncertainty. Electronics securely mounted in high-impact case. Service centers throughout U.S., Canada, Europe and Far East for 48-hour turnaround repair.

FLUKE P. O. Box 7428,
Seattle, Washington 98133.

Get all the details from your nearest Fluke sales office. Dial toll-free 800-426-0361 for address of office nearest you.

Circle 79 on reader service card
98 RADIO-ELECTRONICS • MAY 1973



**NEXT
MONTH
IN R-E**

*Build the
Phone
Sentry
It answers
your phone
while you're
away.*

**JUNE
ISSUE
ON SALE
MAY 17**

HEATH DIGITAL TUNER

(continued from page 50)

Fig. 9 shows these logic inputs and the squelch diode matrix circuit. When a squelch signal is present, the supply voltage is removed from the stereo indicator lamp to assure that it does not light. The SQUELCH DEFEAT switch prevents any of the squelch control inputs, with the exception of the re-program squelch input, from turning off the audio signals. Any time an incorrect frequency is selected, the re-program squelch input will override the squelch defeat control and cause the audio to squelch.

The readout circuit, mounted directly behind the tuner front panel window, consists of three incandescent 7-segment numerical display tubes and three BCD-to-seven-segment decoder driver IC's. A fourth display tube (the most significant figure) contains two segments that can only display the numeral 1. When frequencies below 100.1 MHz are displayed, the numerical 1 tube remains unlighted. The three integrated circuits decode the BCD information from the twelve output lines of the programmer. Pressing the L/T (light test) switch located behind the front panel hinged door lights all the display tube segments to insure that they are operative. **R-E**

PA SPEAKER SYSTEMS
(continued from page 53)

column is placed in the general vicinity of the original sound source (singer, speaker), as close as practicable to the source. Having the loud-speaker sound originate near the original source provides a more natural effect for the audience, and avoids confusion of the performer.

The column is placed so that the microphone is below and slightly behind the sound column, to minimize feedback. The sound column is oriented so that its vertical distribution will deliver nearly equal loudness to all listeners, from front to back, except

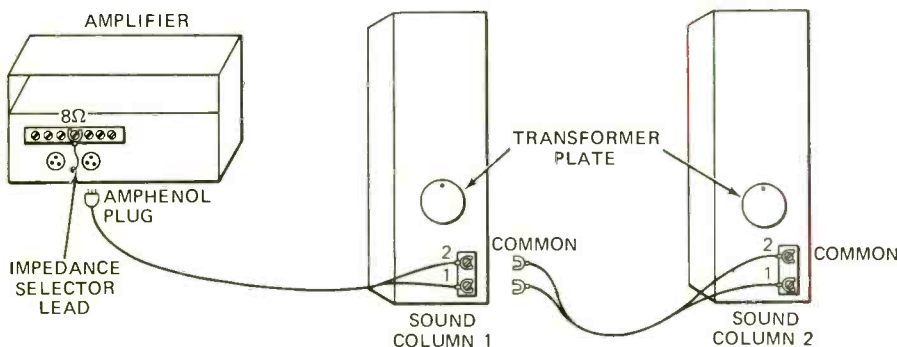


FIG. 10—ONE WAY to connect sound columns to PA amplifier system. Here two 16-ohm columns are in parallel across the amplifier output adjusted for an 8-ohm load impedance.

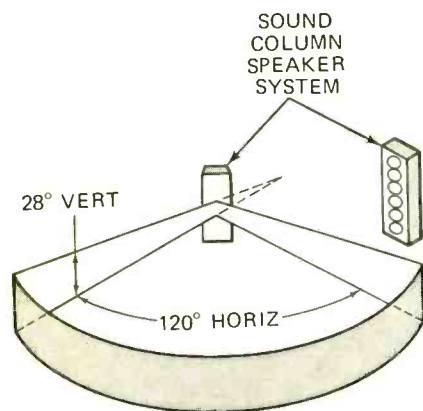


FIG. 8—RADIATION PATTERN from a vertically oriented sound column is horizontal.

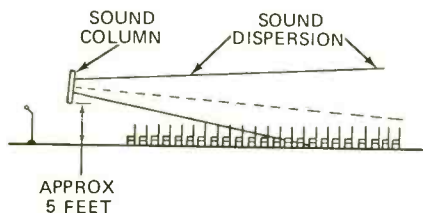


FIG. 9—HOW SOUND COLUMN IS PLACED for most effective coverage of an audience.

those who are within the effective range of the speaker's voice.

A sound column can be aimed quite accurately at this point by the light reflection method. Attach a small mirror to the face of the column center. Standing at the aiming point with a light directed at the sound column,

have the column adjusted for maximum light reflection from the mirror.

Connecting sound columns

One or more sound columns may be connected to an amplifier in a sound system. The columns are normally connected in parallel as shown in Fig. 10.

Sound columns normally have an impedance rating of 16 ohms. If only one sound column is used, connect the amplifier leads to the 16-ohm output terminal. For two sound columns in parallel, connect the leads to the 8-ohm terminal.

There you have it, a quick guide to PA speaker installation—use it to simplify your next PA job. **R-E**

SPRING SALE

RAYTHEON

- | | | | |
|---------------------------------------|--------|--|--------|
| <input type="checkbox"/> 5-3HQ5 | \$6.20 | <input type="checkbox"/> 5-6BA11 | \$5.35 |
| <input type="checkbox"/> 5-6AW8 | \$4.90 | <input type="checkbox"/> 5-6KT8 | \$5.90 |
| <input type="checkbox"/> 5-6GU7 | \$4.65 | <input type="checkbox"/> 5-6GH8 | \$3.45 |
| <input type="checkbox"/> 5-6HA5 | \$4.20 | <input type="checkbox"/> 5-12AU7 | \$3.30 |
| <input type="checkbox"/> 5-6JC6 | \$4.90 | <input type="checkbox"/> 5-8FQ7 | \$3.25 |
-
- | | |
|--|---------------|
| <input type="checkbox"/> Circuit Breakers 1.25 Amp. | 10 for \$1.00 |
| <input type="checkbox"/> 10 Asst'd Aligning Tools | \$1.98 |
| <input type="checkbox"/> 100 Asst'd Mica Cond. | \$1.19 |
| <input type="checkbox"/> 300 Asst'd 1 & 2 Watt Res. | \$4.95 |
| <input type="checkbox"/> HV Anode Leads B/W Sets | 10 for \$1.00 |
| <input type="checkbox"/> RF Cables Tinned Ends | 6 for \$.89 |
| <input type="checkbox"/> DELAY LINES | 2 for \$1.19 |
| <input type="checkbox"/> Knife Switches DPDT | 4 for \$1.00 |
| <input type="checkbox"/> Spaghetti Asst'd | 75 Pcs. \$.59 |

DIODES SEMI CONDUCTORS

- | | |
|---|---------------|
| <input type="checkbox"/> HEP 170 2.5 Amp. | |
| <input type="checkbox"/> 1000 PIV | 25 for \$4.95 |
| <input type="checkbox"/> 6500 PIV Focus Rect. | 4 for \$2.00 |
| <input type="checkbox"/> 13.5 KV Focus Rect. | 5 for \$3.00 |
| <input type="checkbox"/> 18.5 KV Focus Rect. | 3 for \$2.49 |
| <input type="checkbox"/> Sel. Boost Rect. | 5 for \$2.00 |
| <input type="checkbox"/> Crystal Diodes 1N34A | 25 for \$2.00 |

CONDENSERS—(CANS)

- | | |
|--|--------------|
| <input type="checkbox"/> 300 Mfd.—200 Volts | 4 for \$2.00 |
| <input type="checkbox"/> 500 Mfd.—200 Volts | 3 for \$2.00 |
| <input type="checkbox"/> 160-100-60 Mfd.—350 V. | 6 for \$2.49 |
| <input type="checkbox"/> 500 Mfd.—50 Volts | 3 for \$1.49 |
| <input type="checkbox"/> 1500 Mfd.—50 Volts | 3 for \$1.98 |
| <input type="checkbox"/> 25 Assorted Cans | \$4.95 |

CONDENSERS (AXIAL LEADS)

- | | |
|---|---------------|
| <input type="checkbox"/> 100 Mfd.—150 Volts | 12 for \$1.98 |
| <input type="checkbox"/> 50 Mfd.—25 Volts | 5 for \$1.00 |
| <input type="checkbox"/> 16 Mfd.—450 Volts | 4 for \$1.19 |
| <input type="checkbox"/> 500 Mfd.—75 Volts | 3 for \$1.49 |
| <input type="checkbox"/> 1000 Mfd.—50 Volts | 6 for \$2.49 |
| <input type="checkbox"/> .01 Mfd.—1KV (Spark Gap) | 20 for \$2.00 |
| <input type="checkbox"/> 25 Asst'd Disc Cond. | \$1.39 |
| <input type="checkbox"/> 25 Asst'd Cond Axial | \$4.95 |

SPEAKERS

- | | | | |
|---|-------|---|--------|
| <input type="checkbox"/> 3" Round | \$.49 | <input type="checkbox"/> 6" Round | \$1.39 |
| <input type="checkbox"/> 3½" Sq. | \$.69 | <input type="checkbox"/> 5X7 | \$1.99 |
| <input type="checkbox"/> 4" Sq. | \$.79 | <input type="checkbox"/> 6X9 | \$2.59 |
| <input type="checkbox"/> 2X6 | \$.99 | <input type="checkbox"/> 4X10 | \$2.79 |
| <input type="checkbox"/> 4X6 | \$.99 | | |

MINIMUM ORDER \$15.00
SEND FOR FREE CATALOG
TUBES UP TO 80% OFF

SEND CHECK OR MONEY ORDER

TV TECH SPECIALS

P.O. BOX 603
Kings Park, L.I.,
New York 11754

FREE catalog
over 1000
unique tools, handy kits, precision instruments, technical supplies.

Our 20th year of service to the World's finest craftsmen and technicians.


National Camera
2000 West Union Ave. Dept. G88
Englewood, Colorado, 80110

Send a **FREE** copy of the nc Flasher

name _____
address _____
city _____
state _____ zip _____

National Camera
2000 West Union Ave. Dept. G88
Englewood, Colorado, 80110

Circle 80 on reader service card

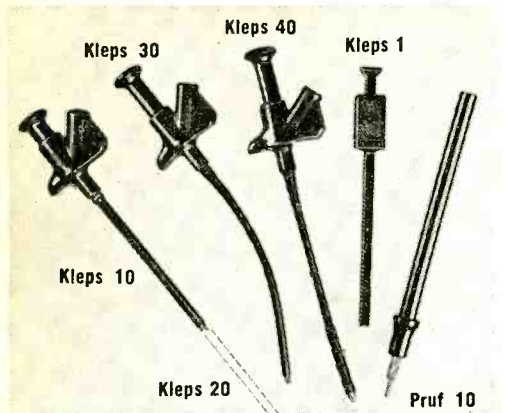

Clever Kleps

Test probes designed by your needs — Push to seize, push to release (all Kleps spring loaded).
Kleps 10. Boathook clamp grips wires, lugs, terminals. Accepts banana plug or bare wire lead. 4¾" long. **\$1.19**
Kleps 20. Same, but 7" long. **\$1.39**
Kleps 30. Completely flexible. Forked-tongue gripper. Accepts banana plug or bare lead. 6" long. **\$1.47**
Kleps 40. Completely flexible. 3-segment automatic collet firmly grips wire ends, PC-board terminals, connector pins. Accepts banana plug or plain wire. 6¾" long. **\$2.39**
Kleps 1. Economy Kleps for light line work (not lab quality). Meshing claws. 4½" long. **\$.99**
Pruf 10. Versatile test prod. Solder connection. Molded phenolic. Doubles as scribing tool. "Bunch" pin fits banana jack. Phone tip. 5½" long. **\$.79**
 All in red or black - specify. (Add 50¢ postage and handling). Write for complete catalog of - test probes, plugs, sockets, connectors, earphones, headsets, miniature components.



Available through your local distributor, or write to:
RYE INDUSTRIES INC.
 130 Spencer Place, Mamaroneck, N.Y. 10543
 In Canada: Rye Industries (Canada) Ltd.
 Circle 62 on reader service card



technotes

MAGNAVOX SPEAKER SYSTEMS

Speaker systems such as models 1S8757 through 1S8759 and 1S8762 through 1S8766 have a fusible resistor in series with the positive lead to the speakers. This resistor is rated at 0.225 ohms, 2 watts. The unusual and protective characteristics of this resistor make it necessary for you to use an exact replacement (part number 240104-3). Use the full length of resistor leads and use a heat sink while soldering them in place.—*Magnavox Service News Letter*

AUTOMATIC RADIO FNP -4052

This auto radio was dead when brought in. Its audio system was working and the trouble seemed to be in the front-end.
 The trouble was traced to the second i.f. transformer. The ground lug that was soldered to the chassis had broken loose. Resoldering the lug to the chassis restored the radio to normal operation.—*David Murphy*

DEGAUSSING CAUTION

Several current color TV models have a built-in 8-track tape player. When you use a degaussing coil to degauss these sets, be *very sure* that there are no recorded tapes in the player or within several feet of the set. Built-in automatic degaussing coils are adequately shielded from the built-in tape player, but an external degaussing coil can do a good job of erasing tapes!
 This precaution will also apply when the customer has an accessory tape player or recorder on or near his TV set.—*Admiral Service News Letter*

CRACKED OSCILLATOR TUBE

A follow-up on reports of cracked 5JW8 horizontal oscillator tubes in the Admiral K19 chassis has traced this trouble to a small metal prong between pins 1 and 9 on the socket. This prong, by contacting the glass envelope of the tube, causes a temperature difference which results in a crack in the glass.
 The prong was originally added to the socket to ground a shield but was not used for this purpose on the K19 chassis. It should be bent back so it does not contact the tube.—*Admiral Service News Letter*

MAGNAVOX T936/956/957 COLOR TV

Snivets on the left side of the screen on uhf channels may be caused by a leaky diode, D102. This diode is located in the horizontal output section and is in series with the center arm of the high-voltage adjustment control. Replacement with Magnavox Part No. 530088-1004 diode will correct this condition.—*Magnavox Service News Letter*

MAGNAVOX UHF TUNER FAILURE

If the transistor in the uhf tuner fails in the 1T5052 and 1T5054 models, check to see if there is a ground strap from the upper right side of the tuner mounting assembly to the picture-tube shield. This strap is used in only a small number of these models and you should remove it from the models that you service.
 It is suspected that a momentary arcing in the picture tube could result in sufficient conduction through this strap to damage the transistor.—*Magnavox Service News Letter* **R-E**

Amazing!

THE QUARTZ SOLID STATE WATCH

with liquid crystal display.



This precision timepiece with no moving parts will show you the time of your life... The quartz crystal oscillates 32,768 times per second. A tiny CMOS chip with over 1200 transistors translates this oscillation into an equally precise digital display of time. Exact hour and minute is shown; colon oscillates once per second. Accuracy: 5 sec/month. Uses 1.5V battery. Guaranteed.




Order direct from: **\$149.00**
EEP CORPORATION
 10180 W. JEFFERSON BLVD.
 CULVER CITY, CA. 90230 213/838-1912

try this

THIRD HAND SOLDERING AID

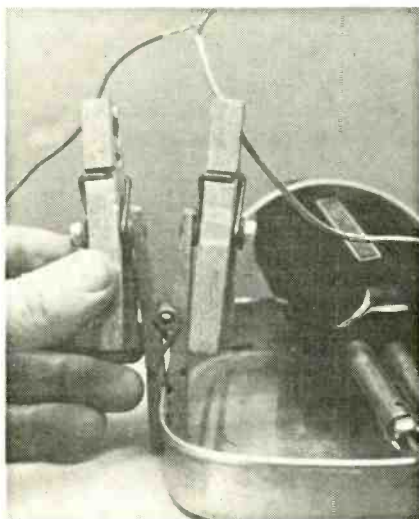A third or even fourth hand for delicate soldering can be quickly devised using three spring-type clothespins. To the handle of one clothespin fasten two others by small bolts through the spring "eyes" and holes drilled in the handle end of the first clothespin. The latter serves as a



THREE CLOTHESPINS form the basis for a handy soldering clamp. A coat of spray paint improves appearances.

clamp for use on any suitable projection, rim or flange to support the other two clothespins in a flexible working position. The jaw ends will hold wire ends or solder without cooling it to make soldering easy without burning your fingers.—Glen F. Stillwell

CONTAINER SERVES DUAL PURPOSE

Many instruments and delicate parts are now shipped or packed in shaped, white plastic foam containers. Don't discard them because they make excellent holders for small parts such as screws, nuts, washers, etc. Small parts show



TWO HANDY BENCH AIDS made from foam plastic packing material used when shipping appliances and electronic devices.

up clearly on the white plastic and are easily located. In addition half of the container can be used as a drill-bit rack with sizes appropriately noted directly on the holder. Holes of the proper size are readily punched in this lightweight compressed plastic.—Glen F. Stillwell **R-E**

INTERESTED IN OPTOELECTRONICS? Turn back to page 62, and read Lou Garner's State-of-Solid-State. It's all about optoelectronics devices.

NEW ...for the sound buff
HYBRID POWER AMPLIFIERS

With the addition of a few off-the-shelf components, you can easily build your own quality amplifier for record player, tape deck, tuner, P.A. (musical instruments) or intercom system.

USED BY LEADING MANUFACTURERS • 2 YEAR WARRANTY

AVAILABLE IN 3 MODELS:		CHARACTERISTICS:
Power	RMS IHF	
1. SI-1010Y	10W 25W	• Harmonic Distortion < .05%
2. SI-1025E	25W 65W	• Bandwidth 20 Hz — 100K Hz
3. SI-1050E	50W 120W	• Flat response within 1.2dB
		• Input sensitivity 500 mV

Contact your local electronic component distributor!

AIRPAX™ INTERNATIONAL DIVISION
P.O. Box 8488
Ft. Lauderdale, Fla. 33310
Circle 88 on reader service card

**Accuracy like a VTVM...
Convenience like a VOM...**

**NEW BATTERY-OPERATED FET
SOLID-STATE VOLT-OHMMETER #116**

Easy-to-build KIT

\$30.90 =116K

Factory-Wired & Tested


\$42.90 =116W

Now you can get all the benefits of a VTVM (laboratory accuracy, stability and wide range) but with its drawbacks gone: no plugging into an AC outlet, no waiting for warm-up, no bulkiness. New Field Effect Transistor (FET) design makes possible low loading, instant-on battery-operation and small size. Excellent for both bench and field work.

Compare these valuable features:

- High impedance low loading: 11 megohms input on DC, 1 megohm on AC
- 500-times more sensitive than a standard 20,000 ohms-per-volt VOM
- Wide-range versatility: 4 P-P AC voltage ranges: 0-3.3, 33, 330, 1200V; 4 RMS AC voltage ranges: 0-1.2, 12, 120, 1200V; 4 DC voltage ranges: 0-1.2, 12, 120, 1200V; 4 Resistance ranges: 0-1K, 0-100K, 0-10 meg., 0-1000 meg.; 4dB ranges: -24 to +56dB.

Sensitive easy-to read 4 1/2" 200 micro-amp meter. Zero center position available. Comprises FET transistor, 4 silicon transistors, 2 diodes. Meter and transistors protected against burnout. Etched panel for durability. High-impact bakelite case with handle useable as instrument stand. Kit has simplified step-by-step assembly instructions. Both kit and factory-wired versions shipped complete with batteries and test leads. 5 1/4"H x 6 3/4"W x 2 7/8"D. 3 lbs.

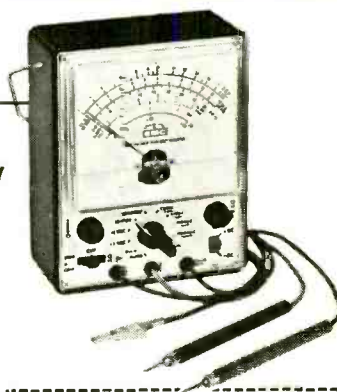

Send FREE catalog of complete EMC line and name of nearest distributor. RE-5

Name _____
Address _____
City _____
State _____ Zip _____

EMC

ELECTRONIC MEASUREMENTS CORP.
625 Broadway, New York, N.Y. 10012

POWER SUPPLY PC BOARD



This board contains everything you need for a power supply up to 40 volts, 2 amps. You add the transformer for the voltage you want. Reg-

ulator, filter, protective resistors and fuse holder, all on fiberglass board.

STOCK NO. F9483 \$2.75 2/5.00

VERSATILE AUTO TRANSFORMER



This autotransformer can supply 50 different voltages, from 10 volts to over 250 volts, at currents from 15 to 25 amps. Ideal for laboratories, experimental work, development work, or can be built into

equipment. Made by General Electric, for use in computers. We supply data sheet showing all details. Original cost, \$78.50. In factory boxed cartons.

STOCK NO. F9467 \$12.50 ea. 2/22.00

COMPUTER GRADE CAPACITORS

J2062 40,000 mfd. 10 volts 3 1/4" x 4 1/4" 1.25 ea. 6/7.00
 J2118 70,000 mfd. 10 volts 3 1/4" x 4 1/4" 1.75 ea. 6/9.00
 J2220 32,000 mfd. 40 volts 2 3/4" x 5 1/2" 2.00 ea. 5/9.00
 J2116 3.750 mfd. 75 volts 2 1/2" x 4 1/4" 1.75 ea. 6/9.00
 All above are brand new and include terminal hardware.

Include sufficient postage, excess will be refunded. Send for new 48 page catalog loaded with other items. Minimum order \$3.00.

DELTA ELECTRONICS CO.
 BOX 1, LYNN, MASSACHUSETTS 01903
 Phone (617) 388-4705
 Circle 83 on reader service card

DISCOUNT PRICES TEST EQUIPMENT

B&K
SENCORE Leader

I.E.C./Mullard Tube Specials
Telematic Test Jigs & Accessories

Catalog & Prices on Request

FORDHAM Radio Supply Company, Inc.
 558 Morris Ave. Bronx, N.Y. Tel: (212) 585-0330 **RCA**

DISTRIBUTORS OF ELECTRONIC SUPPLIES

Circle 84 on reader service card

books

MODERN RADAR: THEORY, OPERATION & MAINTENANCE, by Edward L. Stafford, Jr. TAB Books, Blue Ridge Summit, Pa. 17214. 480 pp. 5 1/2" x 8 1/2". Hardcover, \$9.95; Softcover, \$6.95.

Informative handbook covers all types of systems—land-based, aircraft, shipboard, police-car, earth to satellite, weather surveillance, etc., containing much of the information needed by technicians interested in the field of radar and radar communications. The development of radar is traced from its earliest stages, explaining the various types of systems and how each works and with schematics and photographs shows how they are put together, prescribed tests and troubleshooting procedures.

FUNDAMENTALS OF ELECTRONIC CIRCUITS by Arthur L. Pike, Prentice-Hall Inc., Englewood Cliffs, N.J. 07632. x 7 9/8 in. 700 pp. Hardcover \$15.50.

Those just beginning a serious study of electronics should find this a valuable text. Because electronic devices work in electric circuits, some previous knowledge of ac circuits is assumed. However, the opening chapter reviews the ac theory needed. Starting with such basic topics as Signal Flow and Efficiency for dc and ac signals the book goes on through diode devices and circuits, two-ports, triodes, basic amplifier circuits, feedback and pulse and ramp signals.

BATTERIES AND ENERGY SYSTEMS, by Charles L. Mantell. McGraw-Hill Book Co., 330 W. 42nd St., New York, NY 10036. 6 1/2 x 9 1/4 in., 221 pp. Hardcover, \$14.00.

Guide to primary and secondary batteries and energy systems, detailing military and civilian uses with special emphasis on engineering applications. Subjects include the zinc-alkali-manganese dioxide systems, silver batteries, water activated systems, nickel-cadmium system, conversion of sunlight. Detailed tables, illustrations and formulas in text, along with bibliographical references.

PRACTICAL INSTRUMENTATION TRANSDUCERS by Frank J. Oliver. Hayden Book Co. Inc., 116 W. 14 St., New York, NY 10011. 7 1/4 x 10 in. 340 pp. Hardcover \$20.00.


A survey of physical-to-electrical transducers. Over 400 diagrams highlight the text discussion of basic operating principles and limits of accuracy of an amazing number of electrical transducers. Detailed chapters treat the specifics of selecting instruments for measuring strain, force, load, angular position, rotary speed, pressure, flow, etc.

HOME-CALL TV REPAIR GUIDE by Jay Shane. TAB Books, Blue Ridge Summit, PA 17214. 144 pp. 5 1/4 x 8 1/4 in. Hardcover, \$6.95, Softcover, \$2.95.

An on-the-spot repair guide with quick reference charts. Specifically designed as a troubleshooting guide for the technician working in the field. The book is arranged in logical reference sections, covering raster, video, chrominance, and other circuit troubles. By comparing the symptoms with the charts, the technician is guided through quick checks for the most logical causes of any malfunction. Separate chapters are devoted to antenna and reception troubles, portable color sets, and TV-radio combination. **R-E**

You worked hard for that "B" in algebra.

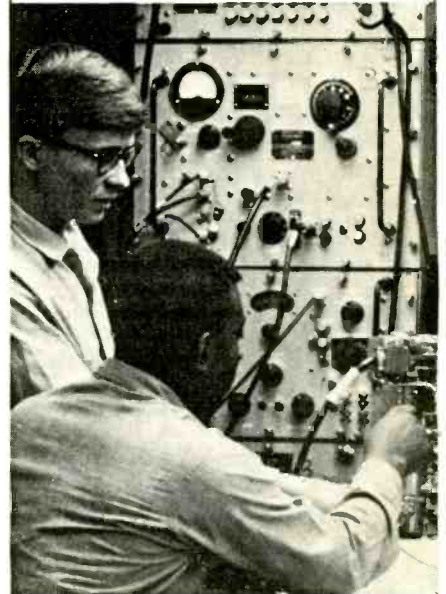We know how to make it work hard for you.



A "B" is too tough to win to let it just sit there . . . especially when you can turn it into a career that the 1970's are only now discovering.

And it's being discovered in the Navy. We'll take your "B" in algebra, put it through our special process, and change it into a challenging responsibility working with the most sophisticated electronics hardware yet developed . . . doing things with electronics that were undreamed when you got your "B."

We'll pay for every dime of your training in electronics theory and systems. And we'll give you a salary to boot . . . like going to college and getting paid for it.

It's a tough school, but when you're through, there will be very little you can't do in electronics . . . in the Navy . . . or in civilian industry.

If you're over 17 and have a high school diploma, let us turn your interest in algebra into something special.

If you're going to be something, why not be something special?

THE NAVY

RE

For further information write to:
 Building 157-4
 Washington Navy Yard
 Washington, D.C. 20390

It sounds good to me and I'd like the full rundown on the Navy's Electronics Program.

Name _____

Address _____

City _____

State _____

Zip _____

market center

WANTED

QUICK cash . . . for electronic equipment, components, unused tubes. Send list now! **BARRY**, 512 Broadway, New York, N.Y. 10012, 212 Walker 5-7000

PLANS & KITS

COLOR organ—Complete schematic, details, parts sources: only \$2.00. Kits, 3-channel 460 W/per only \$14.95 less cabinet & lights. Send check or M.O. to: **JOHN BOSTICK**, 19230 Erwin Street, Reseda, Calif. 91335

ANTIGRAVITY device. Brochure rushed free. **AGD**. Box 3062-RE, Bartlesville, Okla. 74003

BUILD digital freq. counter PC boards and plans \$15.00 plans only \$4.00 **MIKRA-D**, Box 403, Holliston, Mass. 01746

WHY not jam unwanted noise with relaxing pink noise? Kit \$4.95, assembled \$6.95. **Flyer MINDLIGHT**, POB 2846RE, Van Nuys, Calif. 91404.

IC color pattern generator P.C. board again available by popular demand. Originally described in January 1970 issue. Undrilled glass epoxy board postpaid \$3.95. **TECHNIQUES INC.**, Englewood, N.J. 07631

BUILD 32-FUNCTION DIGITAL COMPUTER 24-PIN IC, 12 TRANSISTORS, COMPLETE INSTRUCTIONS, \$15.25. **ELECTRONETICS**, Box 278, Cranbury, N.J. 08512

ELECTRONIC ORGAN KITS, KEYBOARDS and many components. Independent and divider tone generators. All diode keying. I.C. circuitry. With our kits you can build any type or size organ desired. 25¢ for catalog. **DEVTRONIX ORGAN PRODUCTS**, Dept. B, 5872 Amapola Dr., San Jose, Calif. 95129

CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services). \$1.00 per word . . . minimum 10 words.

NONCOMMERCIAL RATE (for individuals who want to buy or sell personal items) 70¢ per word . . . no minimum.

FIRST WORD and NAME set in bold caps at no extra charge. Additional bold face at 10¢ per word. Payment must accompany all ads except those placed by accredited advertising agencies. 10% discount on 12 consecutive insertions, if paid in advance. Misleading or objectionable ads not accepted. Copy for July issue must reach us before May 1.

CLASSIFIED ADVERTISING ORDER FORM

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35

No. of Words { @ .70 Non-Commercial Rates } = \$
 { @ \$1.00 Commercial Rate } = \$
 No. of Words in bold face @ .10 = \$

Total Enclosed \$

Insert _____ time(s)

Starting with _____ issue

Payment must accompany order unless placed through accredited advertising agency 28

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____


SIGNATURE _____

MAIL TO: RADIO-ELECTRONICS, CLASSIFIED AD DEPT., 200 PARK AVE. SOUTH, NEW YORK, N.Y. 10003

IC PRICES SLASHED

FACTORY FIRSTS

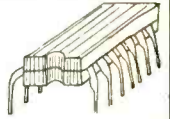NATIONALLY KNOWN BRANDS SATISFACTION GUARANTEED



DIGITAL TTL			
7400N	32¢	7454N	32¢
7401N	32¢	7472N	39¢
7402N	32¢	7473N	48¢
7403N	32¢	7474N	48¢
7404N	35¢	7475N	72¢
7410N	32¢	7476N	53¢
7420N	32¢	7486N	53¢
7430N	32¢	7490N	72¢
7440N	32¢	7492N	72¢
7441N	\$1.50	7493N	72¢
7442N	\$1.20	7495N	\$1.20
7447N	\$1.15	74107N	54¢
7451N	32¢	74121N	56¢
7453N	32¢		

LINEAR INTEGRATED CIRCUITS

709C MINIDIP	40¢	10	\$3.50	100	\$29
723C TO-5	90¢	10	\$8.25	100	\$78
741C MINIDIP	50¢	10	\$4.05	100	\$36
748C MINIDIP	55¢	10	\$4.50	100	\$40
558 MINIDIP	88¢	10	\$6.90	100	\$61
LM301 MINIDIP	45¢	10	\$3.70	100	\$31
LM309K TO-3			\$2.50	5	\$11.25

The above full specification first line devices are also available with "relaxed specs", fully functional at discounts up to 50%. Mail reader service card for flyer.

GENERAL PURPOSE SILICON TRANSISTORS

2N3638	PNP	20¢	10	\$1.65	100	\$15.00
2N3638A	PNP	22¢	10	\$1.80	100	\$16.50
2N3641	NPN	23¢	10	\$2.00	100	\$17.50
2N3643	NPN	23¢	10	\$2.00	100	\$17.50
2N5133	NPN	15¢	10	\$1.25	100	\$10.00
2N5134	NPN	15¢	10	\$1.25	100	\$10.00
2N5137	NPN	18¢	10	\$1.50	100	\$13.65
2N5138	PNP	15¢	10	\$1.25	100	\$10.00
2N5139	PNP	15¢	10	\$1.25	100	\$10.00
2N3055	NPN	\$1	10	\$9.50	100	\$86.25

1 AMP SILICON RECTIFIERS

1N4003	200PIV	12¢	100	\$6	1M	\$45
1N4005	600PIV	10¢	100	\$7	1M	\$55
1N4007	1000PIV	7¢	100	\$9	1M	\$75

DTL INTEGRATED CIRCUITS DIP PACKAGE

930, 936, 945, 946 and 962 . . . Specify number of each type . . . 20¢ 10/\$1.75 100/\$16.00

SILICON SIGNAL DIODES

1N4148 (1N914 equiv.) 20¢ \$1 100/\$4 1M/\$30

RTL INTEGRATED CIRCUITS TO-5 EPOXY PACKAGE

uL900, uL914 and uL923 . . . Specify number of each type . . . 5/\$1.00 100/\$15.00

MOLEX IC SOCKET PINS

100/\$1.00 200/\$1.80 300/\$2.60 500/\$4.20 700/\$5.80 1000/\$8.20 ea addn 1000/\$7.50

READOUT TUBES

5 Volt 7 Segment Readout Tube \$3.75. Counting and Display Kit (Readout Tube +7490+7475+7447) \$5.75, 3 Kits for \$16.50

1/4 & 1/2 WATT 10% RESISTORS

1/4W 5¢ 30/\$1.20, 100/\$3.00, 500/\$13.75 as low as 1.7¢ ea in quantity-see catalog
 1/2W 4¢ 30/90¢, 100/\$2.50, 500/\$11.25 as low as 1¢ ea in quantity-see catalog

COD orders accepted for same day shipment. Call 218 681 6674.

Free Catalog—Large Quantity Discounts—Orders Less Than \$10.00 Add 25¢—Others Postpaid

DIGI-KEY PRICE PAGESetter FOR QUALITY IC'S
 BOX 126H THIEF RIVER FALLS, MN56701

D.C. POWER UNIT \$3.50
TRANSFORMER & RECTIFIER
 IN A WALL PLUG
 U.L. LABELED
 8V DC - 4 WATT

ADD AN LM309H REGULATOR \$.90
 & A 1000 MFD-12V CAPACITOR \$1.10
 FOR A 5V-100 MA
 POWER SUPPLY TOTAL \$5.50

THE MONSANTO MAN-1 \$3.90
7 SEGMENT LED DISPLAY

MONSANTO MAN-3 LED 7 BY 5 ARRAY. \$8.95
 COMPLETE DATA FOR ASCII
 ALPHANUMERIC CIRCUITRY INCLUDED

8224 FIELD PROGRAMMABLE ROM \$7.50
 256 BIT 2 2 BIT WORDS
 CUSTOM PROGRAMMING \$5.00

PHASE LOCKED LOOPS 565 566 567 \$2.95
 555 TIMER—WITH ALL DATA \$1.05
 LM309K REGULATOR \$1.90

YOU WON'T BELIEVE THE SPECS ON THESE!

LM 311 SUPER COMPARATOR \$2.50
 LM 308 ULTRA HI IMPED OP-AMP \$1.95
 LM 302 1000 MEGOHM OP-AMP
 VOLTAGE FOLLOWER \$1.20

LM/303 DUAL STEREO PREAMPLIFIER \$1.95
 LM 380 2-WATT AUDIO AMPLIFIER \$1.75
 CALCULATOR CHIP SPECIAL \$9.75
 40 PIN - 4 FUNCTION - 12 DIGIT - CHAIN CALC.
 AUTO-OVERFLOW - ZERO SUPPRESSION
 WITH COMPLETE DATA

NATIONAL "DM" SERIES

8090, 8091, 8092, 8093, 8094 \$.85 8210,
 8220 \$1.00 8601, 8820, 8830 \$.95 8280 8281
 \$1.10 8200, 8211, 8520, 8551 \$1.50 8570,
 8590, 8880 \$1.75 8123, 8810, 8812 \$2.00

LO-POWER TTL

74L00, 74L02, 74L04, 74L10, 74L30, 74L51 \$3.35
 74L72, 74L73, 74L74 \$7.75 74L90, 74L93 \$2.00


7400, 7401, 7402, 7403, 7404, 7405, 7408,
 7410, 7420, 7430, 7432, 7440, 7450, 7453,
 7454, 7460 \$2.20
 7447, 7448, 7483, 7496 \$1.10 7475, 7490,
 7493, 7495 74153 \$1.25 74154 \$1.50 74192,
 74193 \$1.65

I.C.s SENT FIRST CLASS MAIL—WE PAY!
JTM ASSOCIATES
 P. O. BOX 843 MANCHESTER, MO. 63011
 Circle 90 on reader service card



COMPUTER KEYBOARD W/ENCODER \$35
 Another shipment just received. Alpha-numeric
 keyboard excellent condition. Once again we expect
 an early sellout. Price of \$35 includes prepaid ship-
 ment in the US and shipment made within 24 hours
 of receipt of order.

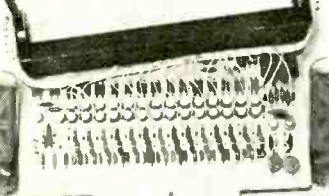GIANT B-7971 NIXIES (2) with 2 sockets and driver
 board containing hi voltage transistors. Complete
 plug-in board as removed from operational equip-
 ment. Schematics included. Unbelievable but true
 . . . just \$2.50 for the complete package.
 #72S-10 \$2.50




15 IC BONANZA
 Brand new DTL dual inline (DIP) package, factory
 marked ceramic type. The price is too good to be
 true. Fully guaranteed and with specs.

930 Dual 4 input NAND gate similar to	7420
931 Clocked flip flop	74110
932 Dual 4 input Expand Buff	7440
933 Dual 4 input expander	7460
936 Hex Inverter	7405
945 JK Flip Flop	74110
946 Quad 2 input gate	7400
962 Triple 3 input gate	7410

Please add postage for above.
JOHN MESHNA JR.
 PO Box 62, E. LYNN, MASS. 01904
 Circle 91 on reader service card

The XR205 monolithic WAVEFORM GENERATOR KIT

Only \$28.00

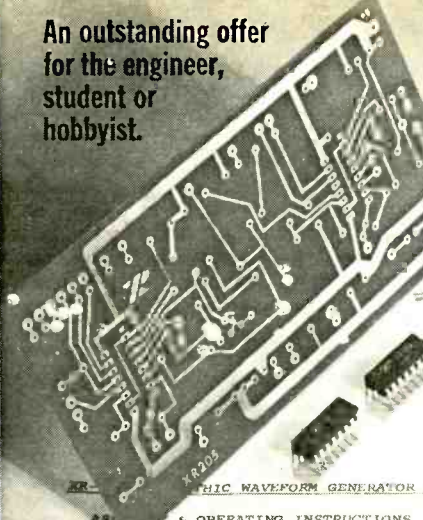

An outstanding offer for the engineer, student or hobbyist.

Here's a highly versatile laboratory instrument for waveform generation at a fraction of the cost of conventional waveform or function generators.

The Kit contains:

- 1) Two XR205 waveform generator IC's
- 2) Data sheet and applications notes
- 3) PC board (etched and drilled, ready for assembly)
- 4) Detailed assembly and hook-up instructions with parts list, schematic and layout diagram.

Immediate delivery.
 Order direct from:
EEP CORPORATION
 10180 W. JEFFERSON BLVD.
 CULVER CITY, CA. 90230 213/838-1912
 Circle 92 on reader service card

MOST VERSATILE Stereo Theatre TRUCK DEVELOPED!

FURNITURE PADS \$5.00 Each \$69.95 per dozen

CONSOLE TV COVER \$24.95

YEATS PLATFORM DOLLY \$24.95

STAIR CLIMBING DOLLY

STANDARD MODEL No. 7 \$89.50

FREE illustrated brochure

YEATS dollies
 1324 W. FOND DU LAC AVE.
 MILWAUKEE, WIS. 53205

BUILD A "SPACE-AGE" TV CAMERA!

ONLY KNOWN SOLID-STATE CAMERA KIT FORM!
 Also available factory assembled. Ideal for
 experiments, industry, education, etc. High
 quality performance backed by over seven years of
 lab and field testing. Fully Guaranteed. A
 Complete self-contained kit. Connects to any TV
 set without modification. Expedient
 assembly manual. Model TV-A Series D com-
 plete kit. (includes 3100.00 PIP anywhere in USA &
 Canada (less vidicon tube \$116.95)). Many other
 kits, parts and plans also available.

PHONE or WRITE for CATALOG... DIAL 402-987-3771
BOX 433-88 ATV Research DAKOTA CITY, NEBR. 68731

REBUILD YOUR OWN PICTURE TUBES?

With Lakeside Industries precision equipment, you can rebuild any picture tube!

For complete details, send name, address, zip code to:
LAKESIDE INDUSTRIES
 3520 W. Fullerton Ave.
 Chicago, Ill. 60647
 Phone: 312-342-3399

F.C.C. EXAM MANUAL

PASS FCC EXAMS! Memorize, study—"1973 Tests-Answers" for FCC First and Second Class Radio-telephone licenses. Newly revised multiple-choice questions and diagrams cover all areas tested in FCC exams—plus—"Self-Study Ability Test." \$9.95 postpaid.

Tests-Answers for FCC First and Second Class Commercial License

COMMAND PRODUCTIONS P.O. BOX 26348 E
 RADIO ENGINEERING DIVISION • SAN FRANCISCO, CALIF. 94126

HIGHLY PROFITABLE ONE-MAN ELECTRONIC FACTORY

Investment unnecessary, knowledge not required, sales handled by professionals. Ideal home business. Write today for facts! Postcard will do. Barta-DRC, Box 248, Walnut Creek, CA 94597.

DIGITAL alarm clock kit, consisting of MOSTEK MK 5017AA MOS/LSI DIP, four 1/2 inch readouts, PC Board, and instructions. Send \$29.95. **DIGI-TEL ELECTRONICS**, Box 6585, Toledo, Ohio 43612

BUILD digital clock, PC boards and plans \$15.00. Plans only \$4.00 **MIKRA-D**, Box 403, Holliston, Mass. 01746

CONVERT any television to sensitive big-screen oscilloscope. Only minor changes required. No electronic experience necessary. Illustrated plans \$2.00. **RELCO-A25**, Box 10563, Houston, Tex. 77018

ELECTRONIC KITS for PHOTOGRAPHERS. Free catalog. **P.C.B.C.**, Box 11012, Palo Alto, Calif. 94306

FREE catalog. Most unusual electronic kits available. Music accessories, Surf, Wind Synthesizers, Wind Chimes, many others. **PAIA ELECTRONICS**, Box B14359, Oklahoma City, Okla. 73114.

INVENTIONS & PATENTS

CASH-ROYALTIES for patented, unpatented inventions. **GLOBAL MARKETING SERVICE**, 2420-AF 77th, Oakland, Calif. 94605

FOR SALE

1973 HOBBY ELECTRONICS DIRECTORY. Hundreds of companies, products and services. Parts, test equipment, surplus, plans, kits, and more. \$1.50. **NEWCAL ENTERPRISES**, Box 323-C, El Segundo, Calif. 90245.

FREE diodes with free catalog. **BDJ ELECTRONICS**, 11 Revere, Tappan, New York 10983

SYLVANIA black light bulbs 475 \$3.00 or 4/\$10.00 ppd. S.A.S.E. for list of surplus and test equipment. **PENINSULAR ELECTRONICS**, 5625 Balfrey Drive, West Palm Beach, Fla. 33406

DIGITAL IC MANUAL—1973 EDITION—1500 TYPES. DOUBLE LISTING BY TYPE AND WIRING DIAGRAM NUMBER. MANY CROSS-REFERENCED. \$3.95. **ELECTRONETICS**, Box 278, Cranbury, N.J. 08512.

DIGITAL ELECTRONICS! Complete schematics, parts lists, theories—Discrete Component Digital Clock, \$3.00—Sound Sensitive Switch, \$1.50. Increase technical competence, hobby skills—Complete course in Digital Electronics is highly effective, \$10.00. Free literature. **DY-NASIGN**, Box 60R2, Wayland, Mass. 01778

B & K, SENCORE TEST EQUIPMENT, DISCOUNT PRICES. FREE CATALOG AND PRICE SHEET. FORDHAM RADIO, 558 MORRIS AVENUE, BRONX, N.Y. 10451

PHOTO Timer L.E.D. readout Digiswitch programmable, Six Digit L.E.D. clock guaranteed **ASTRO LABS**, Box 524, Mesa, Ariz.

MANUALS for Govt. surplus radios, test sets, scopes, teletype. List 50¢. **BOOKS**, 7218 Roanne Drive, Washington, D.C. 20021

GUARANTEED metal detectors. Catalog. **DETECTOR**, Room 275-T, 102 W. Arrellaga, Santa Barbara, Calif. 93101

BEAUTIFUL catalog. Free! Professional Line of Guaranteed Metal Detectors. Find Coins, Jewelry, Relics. **FISHER**, Room 527-Q, Box 490, Belmont, Calif. 94002

LOGIC power supply. Lab quality floating output bench supply. 5V-2.5A. 95-125VAC input. \$59. 0.1% regulation. Foldback current limiting. Other voltages also available. Overvoltage protection \$18. **RONLIN INSTRUMENTS**, Box 6162, San Jose, Calif. 95150

SUPREME sixteen different Radio-Television Diagram manuals, \$40.00 value, only \$14.95 **SUPREME PUBLICATIONS**, 1760 Balsam, Highland Park, Ill. 60035

WESTON 1250 Digital Frequency Counter, new, \$200. Weston 4440 Digital Multimeter, used, \$135. **RICHARD TRIPLETT**, 1304 15th, Huntsville, Tex. 77340

PRINTED board design, fabrication, plain and sensitized boards. **PCDS**, 1610 Melville, Fairfield, Conn. 06430

TUNER service UHF or VHF \$9. 5, combo \$15.00. Includes all parts except tubes, transistors, diodes, nuvistors. Tuners repaired, realigned and neutralized by expert technicians. Send to **RAINBOW TUNER LABS**, 4158 Greeby St., Philadelphia, Pa. 19135

LOGIC Probe with LED display \$20.00 post-paid U.S. Order from **UTI** POB 252 Waldwick, N.J. 07463

SEMICONDUCTOR and parts catalog. **J. & J. ELECTRONICS**, Box 1437, Winnipeg, Manitoba, Canada

IC APPLICATIONS Newsletter. Construction and circuits. Sample copy \$1.00. **ESTRADA**, 17 Slate Lane, Central Islip, N.Y. 11722

FREE catalog lists resistors, tubes, transistors, rectifiers, condensers, tools, tuners, etc. etc. **HYTRON HUDSON**, Dept. RE 2201 Bergenline Ave., Union City, N.J. 07087

CANADIAN surplus catalog \$1.00. **ETCO ELECTRONICS**, 464B McGill, Montreal, Canada


ELECTRONICS ENGINEERING & INSTRUCTION

SHORTCUTS to success! Highly effective, profitable short courses. (75 choices). Study at home. Diploma awarded. Our 27th year. Free literature. **CIEE-E**, Box 10634, Jackson, Miss. 39209

MOD-KIT

LOW COST POWER SUPPLIES

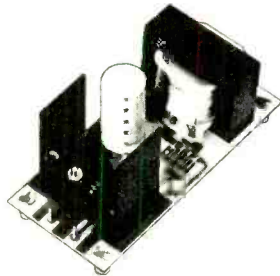
New series of power supplies are completely self-contained with transformer and solid state regulator. Outputs are short circuit proof. No calibration required. Either negative or positive output. May be placed in series or parallel.



Line Voltage	110-125 VAC	DPS-5	5V	1A	.. \$12.95
Line Frequency	50-400 Hz	DPS-52	5V	2A	.. \$18.95
Line Regulation	0.1% typ	DPS-12	12V	.6A	.. \$12.95
Load Regulation	0.2% typ	DPS-15	15V	.5A	.. \$12.95
Ripple & Noise	10mV max				
Temp Coefficient	-2mV/°C				

COUNTER/DISPLAY MODULE

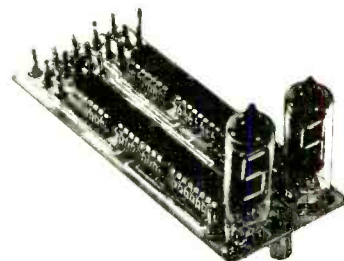
These versatile modules will count and display any number from 0-99. Each stage has a 20 MHz decade counter, latch, decoder/driver and bright seven segment display. Great for bread-boarding frequency meters DVM's etc. Sockets included for IC's and display. Double-sided, plated through PC board has solderless Connections. Operates from single 5 volt supply.



CDM-100 Dual Counter/Display Module \$17.95

LED COUNTER/DISPLAY

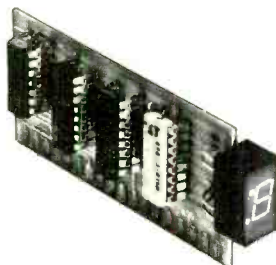Easily the fastest selling counter display modules on the market. These micro-units offer the largest TTL circuitry and a large LED display. All conceivable circuit functions have been brought out to plated contact fingers. Mounts in dual 18 pin connector. Requires 5 volt supply.




LR-100	...	Latch only and Display	\$13.95
LR-110	...	Counter/Latch/Display	32 MHz	.. \$15.95
LR-110H	..	Counter/Latch/Display	70 MHz	.. \$15.95
LR-110UD	..	Up/Dn Cntr/Ltch/Dsply	32 MHz	.. \$16.95

HEATER/COOLER

No. 801

Thermo-electric Module

\$15.95

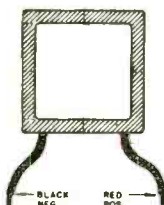

This solid state unit can develop more than 150 F across its plates. Original cost \$60. With specs and suggested power supply.

30 MHz FREQUENCY METER PREAMP

The PR-30 will operate with any TTL frequency meter circuit up to 30 MHz. The MOSFET input stage is followed by a wide band amp with gain controls. The input is protected against transients and overloads.

SENSITIVITY


250 mV 50 Hz-100 MHz
250 mV 20 MHz-30 MHz

MAX INPUT

100 V DC-1 MHz
50 V 1 MHz-30 MHz
20 V 10 MHz-30 MHz

INPUT IMPEDANCE

1 Megohm 10 pF

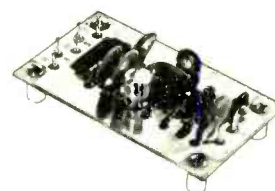

PR-30 Frequency Meter Preamplifier Kit \$15.95

*BANKAMERICARD
*MASTER CHARGE

Send us your order giving all information that is RAISED on your card. Phone orders on BankAmericard and Master Charge accepted.



TERMS:

Please allow for postage
Rated firms NET 30 days
Color residents add 3%
tax. 48 page catalog 50¢
refundable with order.



ENVIRONMENTAL PRODUCTS

BOX 1014 Glenwood Springs, CO 81601

Circle 93 on reader service card

LOGIC NEWSLETTER, design and construction. Sample copy \$1.00. LOGIC NEWSLETTER, Box 252, Waldwick, N.J. 07463

TV TUNER repairs—Complete course details. 12 repair tricks. Many plans. Two lessons, all for \$1. Refundable. FRANK BOCEK, Box 3236 (Enterprise), Redding, Calif. 96001

AVIATION ELECTRONICS TECHNICIAN—Prepare for exciting career in new field of "Avionics". Train at nation's largest aeronautical school. Indicate if eligible for G. I. Benefits. SPARTAN AIRSCHOOL, International Airport, MNW, Tulsa, Okla. 74151

TUBES

SAVE money on parts and transmitting-receiving tubes, foreign-domestic. Send 25¢ for giant catalog. Refunded first order. UNITED RADIO COMPANY, 56-R Ferry Street, Newark, N.J. 07105

RECEIVING & industrial tubes, transistors. All brands—Biggest discounts. Technicians, hobbyists, experimenters—Request free giant catalog and save! ZALYTRON, 469 Jericho Turnpike, Mineola, N.Y. 11501

Technical Excellence in Electronics.

On our small, friendly campus the emphasis is on Living as well as Learning. Extra-curricular social activities, student clubs, a student operated radio station, student government, new dormitory and a full sports program help provide a world of your own in which to prepare for tomorrow. Associate Degree in Engineering Electronics. B.S. obtainable. G.I. approved.



VALPARAISO TECHNICAL INSTITUTE
Dept. C, Yellowstone Trail, Valparaiso, Indiana 46383

STAR-TRONICS

INDUSTRIAL AND GOVERNMENT ELECTRONIC SURPLUS
PARTS & PIECES FOR SCHOOLS, SHOPS, HAMS & HOBBYISTS
SEND FOR OUR LATEST ALL DIFFERENT MONTHLY PICTURE CATALOG. NOW!
Box 17127, Portland, Ore. 97217



NOW build your own Capacitor Discharge Ignition System for as little as \$11.45! Circuit diagram included with special ignition transformer.

TR-200 transformer
6 or 12 volts 11.45

Complete COMPAC KIT
6 or 12 volts 25.95

(as described in
POPULAR ELECTRONICS—Nov. 1966)

FREE LITERATURE on all SYDMUR "CD" Systems.

SYDMUR—1268 E. 12 St.,
Brooklyn, N.Y. 11230



AN/GRR-5 RECEIVER
1.5 to 18 MHz in 4 Bands. AM, CW and MCW, continuous tuning & 10 pre-set frequency, 200 KHz crystal calibrator, 4" P.M. speaker, 12 tubes, with power supply for 115 V. 50/60 cyc., 6, 12, or 24 V. DC—Also dry cells 90 & 1.5 VDC. Size, 13 1/2 x 8 1/2 x 12 1/2". Shpg. Wt. 75 lbs. USED, repairable... \$49.50
CHECKED \$59.50
Power Plug \$2.00
Manual \$7.50

R-392 RECEIVER—500 KHZ to 32 MHz. 32 Bands. 25 Tubes, 24/28 VDC. Size: 11 1/2 x 14 x 11". 70 lbs. USED, repairable: \$295 CHECKED \$350. Manual: \$8.50
All prices F.O.B., Lima, Ohio - Dept. RE
SEND FOR OUR BIG NEW CATALOG!

FAIR RADIO SALES
1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

Opto Electronics Sale


LIGHT EMITTING DIODE GaAs INDICATORS



- 1-MV2*, TO-18, Dome, green, visible \$1.19
 - 1-MV4*, stud, high power, red, 2-watts 3.95
 - 1-MV4H*, stud, high power, hi-dome, red, 2-watts 3.95
 - 2-MV10*, TO-18, clear, diffused dome, red 1.00
 - 2-MV50*, axial leads, micro-mini dome, clear, red 1.00
 - 2-MV5022*, jumbo red dome, TO-18, visible 1.19
 - 2-MV5020*, jumbo clear dome, TO-18, visible, red 1.19
 - 2-MV5040*, 4-LED red array, with 6-lead pak 1.49
 - 2-MV5060*, TO-18, micro-mini, clear dome, red 1.00
 - 1-MV5222*, jumbo dome, green, panel snap-in 1.98
 - 1-MV5322*, jumbo dome, GaAsP, panel snap-in 1.98
 - 1-MV9000*, cartridge panel lamp, sealed, red, clear lens 1.49
 - 1-ME-1*, infra-red, parabolic lens, pin type 1.19
 - 2-ME-4*, infra-red, "invisible", TO-18, diff. dome 1.19
 - 2-ME60*, infra-red, "invisible", axial, micro-mini 1.00
 - 5-LED HOBBY SPECIAL, asst. types, axial, TO-18, etc. 1.00
 - 1-LED MAN-4*, hobby special, readout, 14-pin 1.49
 - 1-LED MAN-3*, hobby special, readout, "the claw" 1.19
- * Monsanto LED equivalents.

LED MITY DIGIT 'DCM'S'

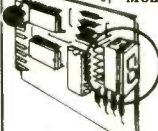Will outperform any other DCM on the market today, not gaseous, not incandescent, but a device that will READ almost for life. MAN-4, Monsanto equal.



Digital Counting Modules by Scientific Devices

9.99

Only Poly Paks can do it!

Kit includes: 3 x 2' printed ckt board, with fingers tool Slide-mounting MAN-4 socket, resistors, 7448, 7475, 7490, booklet.

NEW! BURROUGHS 8-DIGIT "UNIVERSAL" NEON READOUTS

PC Board Included
Only \$19.95
WORTH \$50.00
1ST Time

- Designed for use with LSI, digital clocks, calculators, frequency counters, DVM's, & precision chronometers, tool
- Eight individual Burroughs B5750's Nixie tubes mounted on a universal 4 1/2 x 1 1/2" MUX board with pin outs for digit drivers & segment.

Use all 8 readouts or any number of readouts from 1 to 8 SIMPLY, EASILY. Electrical characteristics: 170 VDC. 2 decimal points, 2 anode pins. We include schematics & instructions. • Characters 9/16" high!
 POWER TRANSFORMER FOR ABOVE
110 to 170 VAC with 6.3V tap on secondary
Only \$1.95
for TTL's

LED 7-SEGMENT READOUTS

0-9 plus letters, for SN-7448. Snaps in 14-pin DIP socket. 3/4" x 1/2" x 3/8". 5V 10ma. with decimal point. Like MAN-1
 Socket for above, 50c



Only \$3.95
 3 for \$10.

LED READOUTS

Buy 3 — \$2.95
Take 10%

This display is excellent for small portable electronics, such as DVM's, calculators, etc. Equivalent to Monsanto MAN-3A. Operates from 5V to 20 milliamperes, with 47 ohm dropping resistor.

COUNTING SYSTEM

Includes SN7490, decade counter, SN7475 latch, SN7441 BCD decoder driver. 0-10-9 Nixie tube, instructions.



Only \$5.50
3 for \$15.00

PHILCO 11 TRANSISTOR AM RADIO CHASSIS

Use as:
• Mike amplifier
• Phono amplifier
• Tape amplifier
• Covers 555 Kcs to 1500 Kcs Broadcast band

One of the most versatile AM Radio and multi-purpose amplifiers we have seen at Poly Paks famous "Economy" price. Measures only 4 1/2" x 8 1/2" x 2 1/2" high. With tuning capacitor, IF circuit, loopstick, auto. volume control with switch. AC and phono-mike jacks. Separate switch for changing from AM radio to amplifier. Uses either 110V plug-in adapter (not with unit) and a 9-volt battery power. Exceptional sensitivity and power. Feeds into 16 ohm speaker. Complete with spec sheets, diagrams, and hookup ideas.

FIBER OPTICS WHALE LAMP

MYRIAD OF SPARKLETS OF LIGHT" from 200 plastic optical fibers — either continuously or intermittently. A "whale" of a method of tying together a black ceramic whale and the marvelous optical science of fiber optics. SELF-POWER! Lights up in color too. Supplied with 2 bulbs, for continuous or flashing light, and a magic multi-colored disc that provides colorful effects. Overall size: 9 x 9 x 7" high. Shpg. wt. 1 1/2 lbs.

Retail: 16-18 Del Carmine St., Wakefield, Mass.
Terms: add postage, cod's 25%. Rated net 30
Phone Orders: Wakefield, Mass. (617) 245-3829
C.O.D.'S MAY BE PHONED IN
P.O. BOX 942R
Lynnfield, Mass. 01940

POLY PAKS


OPTO COUPLER PHOTO DARLINGTON RELAY

\$1.98

RCA NUMITRON 7-SEGMENT TUBES

RCA DR2110 NUMITRON TUBES

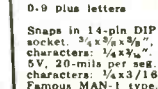0-9 Plus letters
Snaps in 14-pin DIP socket. 3/4 x 1/2 x 3/8". Characters: 1/4 x 3/8". 5V, 20-mils per seg. Characters: 1/4 x 3/16". Famous MAN-1 type. Sockets .50 ea.



LED READOUTS

\$4.50
3 for \$12.

MAN-2* ALPHA-NUMERIC

\$9.99

MAN-5* GREEN

\$8.88

MAN-8* YELLOW

\$12.50

6-DIGIT MAN-3A MUX'D PC BOARD

\$2.95

8 TRANSISTOR AMPLIFIER CHASSIS

Only \$3.95

AC-DC CHARGER CONVERTER

Only \$1.98

PLUGS INTO 110 VAC

Only \$13.95

MCA-30. 1500 volt isolation. 6-pin mini dip. Replaces all types of relays, etc. 100's of opto applications. Infra-red emitter optically coupled to photo darlington amplifier.

DR2000. Character height 0.6" x .235". 5V @ 24 mils per seg. Fit standard 9-pin tube socket. 0-to-9 numerals. **\$3.99**

7-Segment. 10-pins, fits TO5 socket. Character size: 0.40" x .230". 5V @ 24 mils per seg. With left decimal. 0-to-9 **\$3.99**

5x7 dot matrix (35 LEDs). 0 to 9 and A to Z. Displays 64 characters ASCII code. Requires 2513 character generator. Each diode 3V @ 20 mils. Snaps in 14-pin dip socket.

0-9 Numerals, 9 letters, left decimal. Snaps in 14-pin dip socket. Size equal to MAN-1. Compatible with ICs. 3V @ 40 mils per seg. 7-segment.

0-9 Numerals, 0 letters, left dec. pt. Snaps in 14-pin dip socket. Size equal to MAN-1. Compatible with TTL ICs. 5V @ 40 mils. 7-Seg.

Same as above, except no AM radio section. Completely wired! With built-in preamp, mike, phono and tape inputs. Color-coded wires with diagram and hookups. Works off 9VDC transistor battery. Excellent fidelity. Shpg. wt. 1-lb.

Converts above 11-and-8-transistor chassis from 9VDC to 110VAC. Easy to hook in. Use as "NICAD" battery charger too (with instructions). Size: 2' x 1 1/2" x 1 1/4". 1-lb. 5-IN. "HI-FI" PM SPEAKER — Only \$1.98

5-ounce ceramic, cylindrical magnet. Twin voice coil. 4 and 8 ohms. 50-16,000 cycles. Shpg. wt. 3 lbs.

Not a kit!

PLUGS INTO 110 VAC
Only \$13.95



Only \$11.95

Only \$13.95

MANEM
 0-127° HIGH LED 7-SEGMENT
 DISPLAYS ALL NUMBERS AND NINE LETTERS
 COMPACT SPACING - 5 PER INCH
 BRIGHT RED 400FT-L AT 10 MA PER SEGMENT
 EACH \$7.00
 TEN OR MORE FOR .. 7.50

LED's
 MV-50 RED LMITTING 10-40MA @2V40
 MV-5020 RED LED60
 MV-100 VISIBLE RED 5-70MA @2V75

RCA 2010
 NUMITRON DIGITAL DISPLAY TUBE, INCANDESCENT FIVE VOLT SEVEN SEGMENT
 .6" HIGH NUMERAL VISIBLE FROM 30 FEET
 STANDARD NINE PIN BASE (SOLDERABLE)
 LEFT HAND DECIMAL POINT
 \$4.00 EACH

CT5005
 A SINGLE MOS CHIP WITH ALL THE LOGIC NECESSARY FOR A - TWELVE DIGIT - FOUR FUNCTION CALCULATOR WITH AN EXTRA STORAGE REGISTER FOR CONSTANT OR MEMORY APPLICATION
 .28 LEAD DIL PACKAGE
 CAPABILITIES(+, -, x, /)
 CHAIN CALCULATIONS
 TRUE CREDIT BALANCE SIGN DISPLAY
 AUTOMATIC KEYBOARD DEBOUNCE
 SINGLE VOLTAGE SUPPLY IS POSSIBLE
 COMPLETE WITH DATA \$12.75
 DATA ONLY 1.00 (REFUNDABLE WITH PURCHASE OF CHIP)

SINGLE CHIP 40 PIN
 ADD, SUBTRACT, MULTIPLY, AND DIVIDE
 12 DIGIT DISPLAY AND CALCULATE
 CHAIN CALCULATIONS
 TRUE CREDIT BALANCE SIGN OUTPUT
 AUTOMATIC OVERFLOW INDICATION
 FIXED DECIMAL POINT AT 0, 2, 3, OR 4
 LEADING ZERO SUPPRESSION
 DATA ONLY 1.00 (REFUNDABLE WITH PURCHASE OF CHIP)
 COMPLETE WITH DATA 9.75

3 CHIP SET
 EIGHT DIGIT
 FLOATING DECIMAL
 LEFT HAND ENTRY
 WILL +, -, x, /
 OVERFLOW SIGNALS
 COMPLETE WITH DATA \$ 6.95
 DATA ONLY 1.00 (REFUNDABLE WITH PURCHASE OF CHIP)

NATIONAL/MOS
 DYNAMIC SHIFT REGISTERS TO-5
 MMS02 DUAL 50 BIT .75
 MMS06 DUAL 100 BIT 1.00
 MMS06 DUAL 100 BIT 1.00
 MMS03 DUAL 100 BIT 1.00
 MMS013 1024 BIT 1.50
 MMS017 DUAL 512 BIT 1.50
 MMS016 512 DIL 1.00
 STATIC SHIFT REGISTERS
 MMS04 DUAL 16 BIT 1.00
 MMS05 DUAL 32 BIT 1.25
 MMS50 DUAL DIFFERENTIAL ANALOG SWITCH 2.00

7400dip

7400	.25
74000 TTL	.35
7401	.25
74001	.75
7402	.25
7403	.25
7404	.25
74004	.75
7405	.25
74005	.35
7406	1.00
740A	.40
7410	.25
7420	.25
74L20	.35
74H20	.75
74H22	.50
7430	.25
74L30	.35
7440	.25
74H40	.40
7441	1.30
7442	1.00
7446	1.50
7447	1.50
7448	1.25
7450	.25
7451	.25
74H51	.35
7453	.25
74H53	.40
7454	.30
74L54	.15
7460	.25
74L71	.50
7472	.40
74L72	.50
7473	.55
7474	.80
7474	.40
74L74	.80
7475	1.15
7476	.55
7480	.50
7483	1.15
7486	.65
7487	1.00
7490	1.00
7491	1.15
7492	.90
7493	.90
7495	1.15
74L95	2.00
74107	.55
74153	1.75
74181	3.50
74193	2.00
74195	1.00

CMOS
 CD4001 .75
 CD4002 .75
 CD4011 .75
 CD4012 .75
 CD4023 .75

LINEARS
 LM100 \$.80
 LM309H 1.00
 LM309K 2.50
 NE555B .75
 NE555A 1.00
 747 1.00
 709 .30
 710 .40
 711 .40
 723 1.00
 555(TIMER) .75

LINEAR SPECIAL
 TEN 741 FULLY COMPENSATED OP AMPS WITH DATA SHEETS 8-PIN DIP ONLY
 TEN FOR \$2.75 EACH35

T. I. H38 PHOTO DIODE \$1.50

ZENER DIODES
 1W
 IN4651 3.9V
 IN4735 6.2V
 IN4740 10.0V
 EACH \$.50

SEND FOR FREE FLYER!!

ALL IC'S-NEW AND FULLY TESTED. LEADS PLATED WITH GOLD OR SOLDER. ORDERS FOR \$5.00 OR MORE ARE SHIPPED PREPAID. SMALLER ORDERS---ADD \$5. CALIFORNIA RESIDENTS ADD SALES TAX. IC'S SHIPPED WITHIN 24 HOURS
BABYLON ELECTRONICS P.O. BOX J CARMICHAEL, CA. (916) 966-2111
 Circle 95 on reader service card

Semiconductor Supermart


FREE CATALOG

**MOTOROLA
RCA
FAIRCHILD
NATIONAL
HEP
PRIME QUALITY
IC's
TRANSISTORS
Other Parts & Equipment**

**CIRCUIT SPECIALISTS CO
BOX 3047 SCOTTSDALE AZ 85257**

Circle 96 on reader service card

the SYSTEM ONE



low cost Computer Kit

The SYSTEM ONE is a complete digital computer in kit form. Originally designed as a teaching aid for university and technical school labs, it is now available to the serious experimenter.

The SYSTEM ONE features:

- * Single buss architecture
- * 8 Bit CPU
- * 1024 Bit Core Memory
- * Fast Parallel Operation
- * Display and Control Console
- * Micro-programmable
- * Solderless intraboard connections
- * 91 TTL Packages

For complete information circle the number below or write Brian Taylor.

epd ELECTRONICS
 BOX 1014 Glenwood Springs, CO 81601

Circle 97 on reader service card

ADVERTISING INDEX


RADIO-ELECTRONICS does not assume responsibility for any errors which may appear in the index below.

READER SERVICE NUMBER		PAGE
88	Airpax Electronics.....	101
18	Alarm Device Mfg. Co.....	72
	Bell & Howell Schools.....	74-77
10	B & K, Division of Dynascan Corp.....	17
78	Brooks Radio & TV Corp.....	97
71	BSR USA Ltd.....	89
87	Castle TV Tuner Service, Inc.....	Cover IV
20	Channellock, Inc.....	78
11	Chemtronics, Inc.....	22
17	Cleveland Institute of Electronics.....	46-49
	CREI, Division of the McGraw-Hill Continuing Education Co.....	28-31
83	Delta Electronics.....	102
61	Delta Products, Inc.....	85
65	Dictaphone Corp.....	87
85	Edmund Scientific Co.....	110
82	EFP Corp.....	100
73	Electronic Chemical Corp.....	90
1	EICO, Electronic Instrument Co.....	Cover II
	EMC, Electronic Measurements Corp.....	101
63	Electro-Voice, Inc.....	86
79	John Fluke Mfg. Co., Inc.....	98
84	Fordham Radio Supply Co.....	102
76	GC Electronics.....	96
75	Grantham School of Engineering.....	91
	GTE Sylvania.....	34
100	Heath Co.....	92-95
2	ICS School of Electronics.....	1
25	Indiana Home Study Institute.....	83
9	International Components Corp.....	16
21	International Crystal Mfg. Co.....	79
72	International Electronics Unlimited.....	90
86	Jerrold Electronics.....	Cover III
12	Leader Instruments.....	23
8	Lee Electronic Labs.....	15
13	Mallory Distributor Products Co.....	24-25
64	Michelin International.....	87
70	Midwest Hifi.....	89
15	MITS.....	27
66	Mountain West Alarm.....	88
80	National Camera Co.....	99
	National Radio Institute.....	8-11
	National Technical Schools.....	64-67
22	Oneida Electronic Mfg. Co., Inc.....	80
24	PTS Electronics, Inc.....	82
67	Quietrol.....	88
19	Raytheon Co.....	73
	RCA Electronic Components Semiconductors.....	32-33
26	Test Equipment.....	83
	RCA Institutes.....	18-21
6	RCA Parts & Accessories.....	13
77	Rectifier Components Corp.....	96
62	Rye Industries, Inc.....	100
7	Schober Organ.....	14
3	Sennheiser Electronics.....	2
74	South River Metal Products Co., Inc.....	90
5	Southwest Technical Products.....	7
23	Tab Books.....	81
68	Telematic.....	88
69	Tri-Star Corp.....	89
4	Tuner Service Corp.....	5
81	TV Tech Aids.....	99
14	Xcelite.....	26
	MARKET CENTER.....	103-109
	ATV Research Corp.....	104
95	Babylon Electronics.....	108
	Barta.....	104
96	Circuit Specialists.....	108
	Command Productions.....	104
89	Digi-Key.....	103
92	EFP Corp.....	104
93	EPD Electronics.....	105
97	EPD Electronics.....	108
	Fair Radio Sales.....	106
90	JTM Associates.....	104
	Lakeside Industries.....	104
91	Meshna Electronics, John Jr.....	104
94	Polypaks.....	106-107
98	Solid State Sales.....	109
	Startronics.....	106
	Sydmar Electronics.....	106
	Yeats Appliance Dolly Sales Co.....	104
	SCHOOL DIRECTORY.....	106
	Valparaiso Technical Institute.....	106

NOVEL SPEAKER ENCLOSURE


I enjoy experimenting with loudspeakers and enclosures. The drawings show the details of an enclosure that gives me very satisfactory performance. It is essentially a simple box with a smaller one inserted in it. The smaller box is divided into small compartments or pigeon-holes by corrugated cardboard separators like those used in shipping cartons for bottles and fragile glassware.

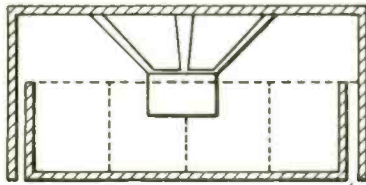This arrangement minimizes the "boom" and reverberation within the enclosure and appears to reinforce the sound and there seems to be a better




3/4 INCH SPACE FOR LARGE CABINETS LESS FOR SMALLER

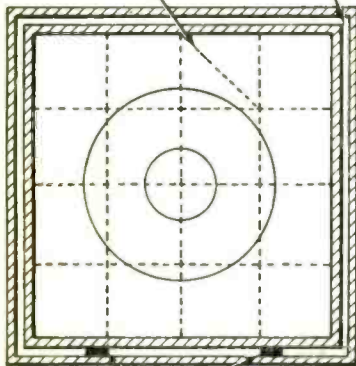IF NECESSARY THE PARTITIONS CAN BE REDUCED BY INSERTING PIECES OF CARDBOARD DIAGONALLY



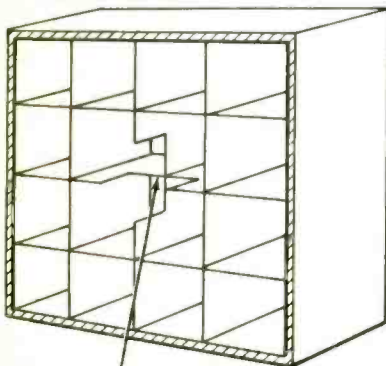LONG BLOCKS FOR RESTS TIES OR FASTENERS AT OTHER POINTS



SEPARATORS CUT OUT TO ACCOMMODATE SPEAKERPOT



SUGGESTED INSULATION FOR LARGE ENCLOSURES

separation between all instruments.

I line large multi-speaker enclosures with one thickness of insulation—I use old carpeting—layered over with panels of thin sheet metal stapled to two thicknesses of corrugated cardboard. The hard surface and the deadness of the interior appear to contribute to the overall performance of the speaker system.

The depth that the inner unit is inserted into the outer can best be determined by experimenting. The space between the two sections is roughly equal to a ducted port in a bass reflex enclosure and can be blocked off at several points for tuning.—Joseph Kriz R-E

RADIO and TV tubes 36¢ each. One year guaranteed. Plus many unusual electronic bargains. Free catalog. CORNELL 4217-E University, San Diego, Calif. 92105

BUSINESS OPPORTUNITIES

START SMALL HIGHLY PROFITABLE ELECTRONIC PRODUCTION IN YOUR BASEMENT. Investment, knowledge unnecessary. Postcard brings facts. BARTA-REI, Box 248, Walnut Creek, Calif. 94597

Give Happiness The United Way

8000 series IC's

8230—1.75	8284—1.95
8233—1.75	8T13—1.75
8242—1.00	8T14—1.75
8250—1.95	8T16—1.95
8252—1.95	8T22—1.75
8262—1.95	8T23—1.75
8270—1.95	8T24—1.75
8271—1.95	8T26—1.75
8275—.90	8T80—1.10
8280—1.75	8T90—1.10

TRANSISTOR SPECIALS

2N965	PNP	6E	TO-18	.15W	7V	.1A	300MHZ	40Hte	5/\$1.00
2N1605	NPN	6E	TO-5	.15W	24V	.1A	14MHZ	125	5/\$1.00
2N2360	PNP	6E	TO-33	.06W	20V	.05A		980	32 \$.50
2N5324	PNP	6E	TO-3	60W	250V	10A		20	35 \$1.50
2N1015D	NPN	SI	TO-82	150W	200V	7.5A		.025	10 \$1.45
2N2015	NPN	SI	TO-36	150W	50V	10A		.012	26 \$.90
2N3584	NPN	SI	TO-66	35W	250V	2A		10	100 \$1.50
2N3055	NPN	SI	TO-3	115W	100V	15A		.01	50 \$1.00
2N3772	NPN	SI	TO-3	150W	60V	30A		.2	30 \$1.25
2N5296	NPN	SI	TO-220	36W	40V	4A		.8	60 \$.50
2N6109	PNP	SI	TO-220	36W	40V	4A		.8	60 \$.55
2N4898	PNP	SI	TO-66	25W	40V	4A		4	46 \$.60
MJ2251	NPN	SI	TO-66	10W	225V	.5A		10	40 \$.70

PRINTED CIRCUIT BOARD

4 1/2"x6 1/2" double sided fiberglass board, 1/16" thick, unetched \$6.60 ea. 5/\$2.50

NIXIE TUBES

Similar to Raytheon 8754 tubes, with socket & data sheet \$2.25 3/\$6.00

2N3819 FET	\$.50
TIS43 UJT	\$.50

VERIPAX PC BOARD

This board is a 1/16" single sided paper epoxy board, 4 1/2"x6 1/2" (standard veripax), DRILLED and ETCHED which will hold up to 21 single 14 pin IC's or 8, 16 or LSI DIP IC's with busses for power supply connections. It is also etched for a 22 pin connector. \$5.25 3/14.50

ER900 TRIGGER DIODES

These bidirectional trigger diodes are one of the best and cheapest methods to trigger SCR's and triacs. 4/\$1.00

FLV 100 Visible LED	\$.65
ME-4 IR LED	\$.65
MRD 14B photo darlington	\$.65
MV 5026 Vis. LED	\$.65
MT-2 PHOTO TRAS.	\$.90
MCT-2 OPTO-ISOL.	\$ 1.49
MCD-2 OPTO-ISOL.	\$ 1.49
3/4" reed switch	6/\$1.00
1N4886 25-40W Power varactor	\$ 4.95

TRIACS

PRV	1A	10A	15A	20A
100	.30	.60	.85	1.05
200	.65	.85	1.25	1.45
300	.75	1.10	1.45	1.65
400	.90	1.35	1.75	1.90
500	1.20	1.50	2.50	2.20

*Press fit

Terms: FOB Cambridge, Mass. Send check or Money Order. Include Postage. Average Wt. per package 1/2 lb. No. C.O.D.'s. Minimum Order \$3.00

5V 1 Amp regulated power supplies. These units are similar to Analog Devices encapsulated SE 905 power supplies. \$34.95

MAN-3 LED READOUT 3/\$5.50

MAN-4 LED 5 Volt READOUTS \$4.50 3/\$12.00

Full Wave Bridges

PRV	2A	6A
200	.95	1.25
400	1.15	1.50
600	1.35	1.75

8223 field prog. ROM	\$8.00
1101 256 bit RAM	\$4.00
8225 64 bit read-write RAM	\$3.95

DECADE COUNTER KIT

CONSISTING OF:
1—NIXIE TUBE and SOCKET
1—7490 1—7475 1—7441
Special priced at \$5.50

TTL IC SERIES

7400—.25	7480—.65
7401—.25	7481—1.25
7402—.25	7483—1.25
7403—.25	7486—.60
7404—.28	7490—1.00
7408—.25	7492—.79
7410—.25	7493—.79
7411—.28	7494—1.20
7420—.25	7495—.90
7430—.25	74107—.60
7440—.25	74121—.70
7441—1.30	74123—1.20
7442—1.50	74141—1.35
7446—1.50	74154—1.95
7447—1.50	74161—1.79
7448—1.25	74192—1.75
7450—.25	74193—1.75
7460—.25	74194—2.35
7472—.40	8570—1.90
7473—.75	8590—1.90
7474—.50	9309—1.95
7475—1.00	9312—1.95
7476—.60	9322—1.95
14 Pin DIP sockets	3/\$1.00
16 Pin DIP sockets	.60

PRECISION TRIM POTS

500ohm, 10K, 20K, 25K 50K \$.75 3/\$2.00

Silicon Power Rectifiers

PRV	1A	3A	12A	50A
100	.06	.09	.24	.90
200	.07	.12	.20	1.25
400	.09	.16	.35	1.50
600	.11	.20	.50	1.80
800	.15	.28	.70	2.30
1000	.20	.35	.90	2.75

LINEAR CIRCUITS

PA234 1W audio ampl.	\$1.25
PA264—5 Watt regulator	\$1.25
LM309K 5V 1A regulator	\$2.25
531 High slew oper amp	\$2.50
536 FET input oper amp	\$3.25
537 Precision 741	\$2.50
540 70W Power driver	\$2.04
555 2 us to 1 hour timer	\$1.19
560 phase lock loop	\$3.25
561 phase lock loop	\$3.25
565 phase lock loop	\$3.35
566 Function gen	\$3.25
567 Tone decoder	\$3.25
703 RF-IF amplifier	\$.80
Dual 709	\$.95
709C operational Amp	\$.39
723 Regulator	\$.75
741 operational Amp	\$.50
747 Dual 741	\$1.25
TVR 2002 high power 723	\$1.00
CA3065 FM/TV amp	\$1.35
5558 dual 741	\$.88
LM 308 oper amp	\$2.95
5556 oper amp	\$.75
101 oper amp	\$.75
741 CV oper amp	\$.55
320—5V reg.	\$1.75
320—15V reg.	\$1.75
424 Zero volt switch	\$1.25

Silicon Control Rectifiers

PRV	6A	10A	20A	70A
50	.25	.32		
100	.30	.45	1.00	3.50
200	.50	.75	1.25	6.50
300	.60	.90	1.50	
400	.70	1.10	1.75	9.50
500	.80	1.25	2.00	
600	.90	1.40	2.25	11.00

Send 20¢ for our Spring catalog featuring Transistors and Rectifiers; 325 Elm St., Cambridge, Mass.

SOLID

TATE

SALES

Post Office Box 74D

Somerville, Mass. 02143

Tel. (617) 547-4005

Circle 98 on reader service card

LIVE IN THE WORLD OF TOMORROW...TODAY!

A BETTER LIFE STARTS HERE


3-CHANNEL COLOR ORGAN KIT

Easy to build low-cost kit needs no technical knowledge. Completed unit has 3 bands of audio frequencies to modulate 3 independent strings of colored lamps (i.e. "lows"-reds, "middles"-greens, "highs"-blues. Just connect hi-fi, radio, power lamp etc. & plug ea. lamp string into own channel (max. 300w ea.). Kit features 3 neon indicators, color intensity controls, controlled individ SCR circuits; isolation transformer; custom plastic housing; instr.



Stock No. 41,831EH \$15.75 Ppd.

TERRIFIC BUY IN HE-NE LASERS

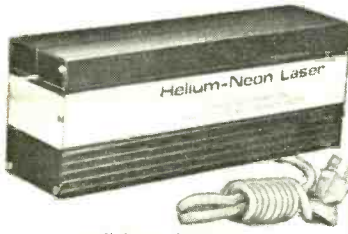

Low price on 0.5mW Laser (random mode); 0.9mm beam dia. (at 10M-, 16mm) belies its quality. New cold aluminum cathode tube for more life stability (hi beam: 9000-hr tube life under normal cond.) Ready to plug in, turn on. Starts instantly. Safe, easy for holography, interferometry, alignment. Metal case, 2.8 x 3.8 x 10", 110v AC, 633nm wavelength,


small beam divergence.

Stock No. 79,020EH \$88.50 Ppd.

0.7mW (SINGLE TEM₀₀MODE), 0.8mm BEAM DIA.

Stock No. 79,024EH \$99.50 Ppd.

130 EXPERIMENTS IN OPTICS

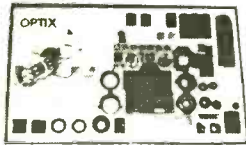

and photography! Optix® Experiments Kit is a complete optical & photography lab for 130 exciting experiments. Lets you recreate the periscope, telescope, microscope, kaleidoscope! Build a 35mm reflex camera with interchangeable lens system! Make, develop photographic film! Enjoy the fun and fascination of having your own optics lab. Fully illustrated 112-pg. manual, 8 1/2" x 11", clearly explains usage of this stimulating kit's 114 precision engineered components.


Stock No. 71,646EH \$21.00 Ppd.

(And our FREE CATALOG is packed with exciting and unusual ecological & physical science items—plus 4,000 finds for fun, study or profit . . . for every member of the family.)


NEW! ELECTRONIC DIGITAL COMPUTER KIT

Solve problems, play games, predict weather, even play miniature chess, with this actual working model of giant electronic brains. Amazing new fun way to learn all about computer programming . . . logic, decimal, binary systems, Laws of Sets. Even do your own programming after completing the simplified, 116-page instruction booklet. Circuits are easily changed, readout is from an illuminated control panel. Requires 2 "D" batteries (not incl.)

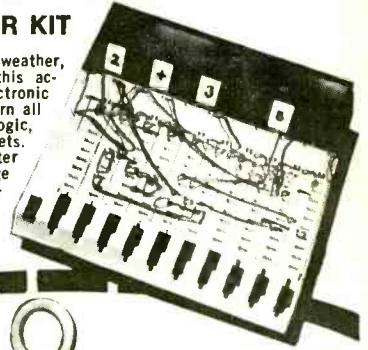Stock No. 71,434EH . . . \$31.50 Ppd. (11 x 12 1/2 x 4")



FEATHERWEIGHT TREASURE FINDER

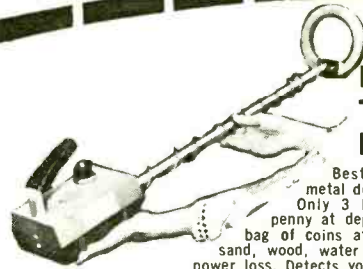

Best, easiest to use solid state metal detector at its price. U.S. made! Only 3 lbs. 6" search head detects penny at depth of 5", silver dollar at 8", bag of coins at 18". Easily works thru dirt, sand, wood, water (30" deep) and rock with no power loss. Detects your "find" sharply with "sound-off" loudspeaker. Comes ready to go. One tuner control; all transistor; adjust. stem; perfect balance. Includes 9v battery, FREE TREASURE GUIDE To 101 Treasure Sites.

Stock No. 80-175EH \$39.95 Ppd.

10-Transistor Treasurer Finder

Stock No. 80,181EH \$71.00 Ppd.

KNOW YOUR ALPHA FROM THETA!

Learn to control your Alpha-Theta brainwaves for relaxation, improved memory, concentration. Electrode headband (w/o messy creams, etc.) atchd to amplifier filters brainwaves, signals beep for ea. Alpha or Theta wave passed. Splcl monitoring button to simulate Alpha sound; audio & visual (L.E.D.) feedback. Reliable, easy-to-use trainer unit has features comparable to many costlier modes. Completely safe. Most people can learn in 8-12 hrs w/ incl instr.

No. 1635EH (8x3x4"; 24 oz.) \$124.50 Ppd.



MAIL COUPON FOR GIANT FREE CATALOG!

164 PAGES • MORE THAN 4000 UNUSUAL BARGAINS!

Completely new Catalog. Packed with huge selection of telescopes, microscopes, binoculars, magnets, magnifiers, prisms, photo components, ecology and Unique Lighting items, parts, kits, accessories — many hard-to-get surplus bargains. 100's of charts, illustrations. For hobbyists, experimenters, schools, industry

EDMUND SCIENTIFIC CO.

300 Edscorp Building, Barrington, N. J. 08007

Please rush Free Giant Catalog "EH"

Name _____

Address _____

City _____

State _____ Zip _____

COMPLETE & MAIL WITH CHECK OR M.O.

EDMUND SCIENTIFIC COMPANY

300 Edscorp Building, Barrington, N.J. 08007

How Many	Stock No.	Description	Price Each	Total

PLEASE SEND GIANT FREE CATALOG "EH"

MERCHANDISE TOTAL \$

HANDLING CHARGE \$1.00*

TOTAL \$

*50¢ ON ORDERS OVER \$5.00



I enclose check

money order for \$ _____

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

Every time you sell an antenna for one set, you're losing money

by Bert Wolf
Manager, Jerrold DSD Division

EVERY CUSTOMER WHO BUYS AN ANTENNA FOR A NEW COLOR SET ALREADY OWNS ONE OR TWO BLACK AND WHITE TV SETS.

Chances are, he's been getting along with an indoor antenna for his old black and white set. He decided to invest in an outdoor antenna because he realized he needed more signal power and more directivity for top-notch color reception.

What your customer probably doesn't know is that he can connect two or more TV sets to a single antenna, using a 2-set antenna amplifier.

Essentially, color reception is not very different from black and white reception. Ghosts, snow and other types of interference look a lot worse in color, but they are easily discernible on a black and white set, too.

Therefore, you are doing your customer a real favor when you recommend that he hook a second set up to his new antenna. Only in this way can he get maximum value from his investment. For you, of course, the sale of a 2-set antenna amplifier represents extra profit.

COLORCASTER II IS A BREAKTHRU IN QUALITY AND PRICE

Figure 1 shows how easy it is to add a second set to an antenna system. The Jerrold Colorcaster II is an important breakthrough in quality and price. Never before has it been so inexpensive to connect two or more sets to a single antenna --- even in poor signal areas --- without deteriorating picture quality.

The Colorcaster II lists for only \$21.50. Yet, it amplifies all UHF and VHF TV channels, plus all FM stations. It provides more signal voltage to each TV set than the antenna would provide if connected directly to one set. Thus, it more than overcomes the splitting losses caused by ordinary passive multi-set couplers.

TWO TV SETS PLUS FM RADIO

What if the home includes not only two TV sets, but an FM stereo receiver, as well? FM stereo is a lot like color TV. FM stereo receivers require stronger signals than monophonic radios. What's more, they are subject to multi-path distortion, which is the equivalent of a "ghost" in TV reception.

Therefore, a good outdoor antenna can do wonders for FM stereo reception. However, your customer doesn't have to invest in a separate outdoor FM antenna. Many TV antennas, such as the Jerrold




Super VU-Finder series, provide excellent pick-up of FM signals.

The system in Figure 2 shows how easy it is to connect an FM stereo receiver to the color TV antenna. Using the Colorcaster II and a Jerrold FS-1314-FM frequency splitter as shown, you can provide superb pictures to two TV sets, plus outstanding stereo signals to the FM receiver. What's more, there is absolutely no interaction between receivers.

FOUR TV SETS PLUS FM RADIO

No, the home with three or four TV sets is no longer unusual. Black and white portables are now so inexpensive that they are frequently given to teenagers as gifts.

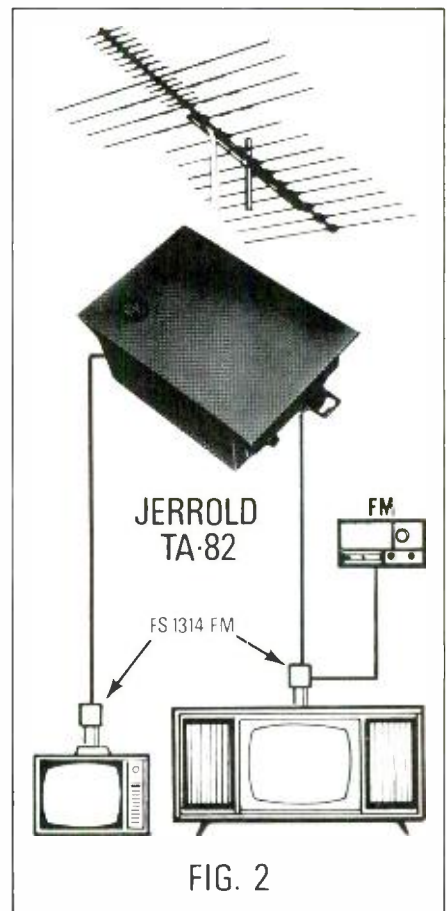You can easily use a Colorcaster II to serve three or four TV sets, plus an FM stereo receiver. All you have to do is split the outputs of the Colorcaster II with Jerrold MF-82 couplers. The high gain of the Colorcaster II is sufficient to overcome the coupler.



An easier way of installing a 4-set home system would be to use a 4-output Colorcaster Plus, such as the Jerrold TA-84.

This brings us to another point. Jerrold has a complete line of Colorcaster Plus models, including 75 ohm models and VHF/FM only models. Thus, you can offer your customers a very wide choice for any reception area.

Jerrold also makes a full range of outdoor Powermate Plus preamplifiers for fringe and deep fringe areas. These preamps are ideal for bringing in distant channels and eliminating snow.

Finally, Jerrold offers the industry's most complete line of reception aids, including filters and traps to eliminate all kinds of interference.

When you need to improve TV or FM reception, Jerrold has the products to do it. And you should be suggesting the appropriate Jerrold reception aids with every antenna you sell. Your customers will love you for it and you'll make a lot more money.

Circle 86 on reader service card

The all NEW


TV TUNER SUBBER™

Mark IV



Latest, all solid state version of the sensational signal circuit analyzing timesaver originated by Castle.

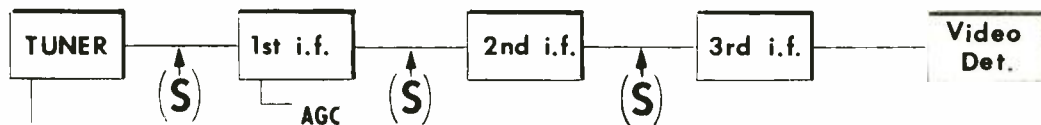Invaluable for locating the break in the tuner and i.f. signal chain or analyzing agc system defects in tube TV receivers . . . essential for speedy location of signal circuit defects in modular IC, solid state and hybrid TV receivers.



Subber Mk. IV permits injection of substitute 40MHz signal at points (S) in signal amplifier chain. Permits signal injection after the agc controlled stages to simplify testing for agc defects.

- Works with any 40MHz receiver . . . color or black and white . . . solid state, tube or hybrid.
- High level, low impedance output furnishes signal usable at input of final i.f. stage.
- Special output circuit works equally well into first i.f. input of late model, link coupled systems and older, low "C" bandpass coupled systems.
- Antenna input and i.f. output electrically isolated; no "hot" chassis hazards.
- No need to disconnect supply leads from suspected tuner being tested. Substitutes the VHF tuner and tests the UHF tuner.
- Tunes all 12 VHF channels, has preset (memory) fine tuning on all channels.
- Higher overall gain than previous models with wide range gain reduction control of 60db.
- Completely self contained and battery operated, uses popular batteries available everywhere. Simple battery replacement; battery compartment in rear of custom molded case.
- Reduced current consumption extends battery life to as much as double that of previous models. Bright LED indicator warns when unit is ON.
- Use on the bench or in the home . . . anywhere.
- Comes complete with extension cables, batteries and instructions.

TV TUNER SUBBER™ Mark IV net \$45.95 Contact your distributor.

Include \$1.50 shipping and handling on prepaid mail orders: we will ship C.O.D.



CASTLE TV TUNER SERVICE, INC.

5715 N. Western Ave., Chicago, Illinois 60645 • Phone: (312) - 561-6354

Circle 87 on reader service card