
IC UPDATE-OPERATIONAL AMPLIFIERS -**Electronics** THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS **NEW LAB POWER SUPPLIES BIAS & TAPE EQUALIZATION 8 Kits From Heath How To Get** Them Straight **BURGLAR ALARM CIRCUITS Build Them Now** With COSMOS IC's **MORE WAYS TO USE Your Curve Tracer** MEASURE dB's With Your Scope SERVICING MATY

It's Easy

And Profitable

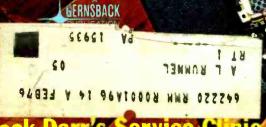

PTS ELECTRONICS

Precision Tuner Service



now available near you

ALABAMA:

52- 32nd ST SOUTH BIRMINGHAM ALA 35222 TEL 205 323-2657

CALIFORNIA-4611 AUBURN BLVD

SACRAMENTO CALIF 9584 TEL 916 182-6220 CALIFORNIA-SOUTH:

5111 UNIVERSITY AVE SAN DIEGO CALIF 92105 TEL 714 280-7070

NEW PTS PRODUCTS... STOP... PTS 4001...
PORTA-ANALYST... STOP... NOT JUST A SUBBER.
THE CADILLAC OF ALL ANALYZERS... STOP... PT
82 CHANNELS OF HIGH GAIN RECEPTION... STOP...
THE AND VHE... STOP... USE AS AN ANALYST
OR PORT V-TUNER... STOP... COMPLETELY
SAFE... STOP... ELECTRICALLY ISOLATED...
115V AC 18V DC... STOP...

PTS ELEX

.. \$59.95...

WRITE THE PTS SERVICE CENTER NEAR YOU FOR MORE INFORMATION

STOP

SEE YOUR DISTRIBUTOR OR

COLORADO:

1958 ALLISON ST ARVADA COLO 80001 TEL 303 423-7080 FLORIDA-NORTH:

1918 BLANDING BLVD ACKSONVILLE FLA 32210 904 389-9952

PTS 4001 GIVES

FLORIDA-SOUTH:

12934 N.W. "TH AVE MIAMI FLA 33168 TEL 305 685-9811

HOME OFFICE-

5233 S HWY 3

KANSAS

"16 MERRIAM LANE KANSAS CITY KANSAS 66100

TEXAS-FAST

4324-26 TELEPHONE RD HOUSTON TEX 77032 TEL 713 644-6793

TEXAS-NORTH

MOPAC LANE LONGVIEW TEX 75601 TEL 214 753-4334

TENNESSEE:

3614 LAMAR AVENUE MEMPHIS TENNESSEE 38118 TEL 901 365-1918

PENNSYLVANIA-WEST:

257 RIVERVIEW AVE W PITTSBURGH PA 15202 TEL 412 761-7648

PENNSYLVANIA-EAST:

1921 S. 70TH ST PHILADELPHIA PA 19142 TEL 215, 724-0999

OREGON:

5220 E SANDY BLVD PORTLAND OREGON 97213 TEL 503 282-9636

OKLAHOMA:

3007 N MAY OKLAHOMA CITY OKLA 73106 TEL 405, 947-2013

US TUNER SERVICE CINCINNATI OHIO 45215 TEL: 513 821-2298

OHIO-SOUTH:

682 STATE RD

OHIO-NORTH:

CLEVELAND, OHIO 44134 TEL 216 845-4480

NORTH CAROLINA

CHARLOTTE, N.C. 28205 TEL. 704. 332-8007

NEW JERSEY-NEW YORK CITY

158 MARKET ST E PATERSON NJ 07407 TEL 201 791-6380

BLOOMINGION INDIANA 3730 TEL 812 824 9331

LOUISIANA:

2914 WYTCHWOOD DRIVE METAIRIE 504 885 2349

MARYLAND:

1105 SPRING ST SILVER SPRING MD 20910 TEL 301 565-0025

MASSACHUSETTS

191 CHESTNUT ST MASS 01103 TEL 413 734-2737

MICHIGAN:

13709 W 8 MILE RD DETROIT MICH. 48235 TEL 313 862-1783

MINNESOTA:

815 LAKE ST. MINNEAPOLIS MINN. 55408 TEL. 613 824-2333

NEW YORK: MISSOURI:

> 8456 PAGE BLVD ST LOUIS MO 63130 TEL 314 428-1299

NOTE TWO NEW LOCATIONS:

ARIZONA: 2412 West Indian School Road, Phoenix, Arizona 85061 TEL. 602-279-8718 WISCONSIN: 3509 West National Milwaukee, Wisconsin 53215 TEL. 414-643-8800

.THIS IS THE SERVICE WE OFFER:

- 1. Fastest Service—8 hour—in and out the same day. Overnight transit to one of our strategically located
- 2. Best Quality—Your customers are satisfied and you are not bothered with returning tuners for rework.
- 3. PTS uses only ORtGINAL PARTS! No homemade or make-do, inferior merchandise (this is why we charge for major parts!). You get your tuner back in ORIGINAL EQUIPMENT condition.
- 4. PTS is recommended by more TV Manufacturers than any other tuner company
- 5. PTS is overhauling more tuners than all other tuner services combined.

Fast 8 hr. Service! We offer you finer, faster...

uner Service

1 YEAR GUARANTEE IF-SUBCHASSIS Major part

VHF. UHF UV-COMBO

993 SYCAMORE ST

TEL 716 891-4935

BUFFALO N Y 14212

\$10.95 17.95 12.50

Major parts and shipping charged at cost. (Dealer net!)


Over 4000 exact tuner replacements available for \$14.95 up (new or rebuilt).

ELECTRONICS, INC....

... Number ONE and still trying harder!

(Not a Franchise Company)

Circle 1 on reader service card

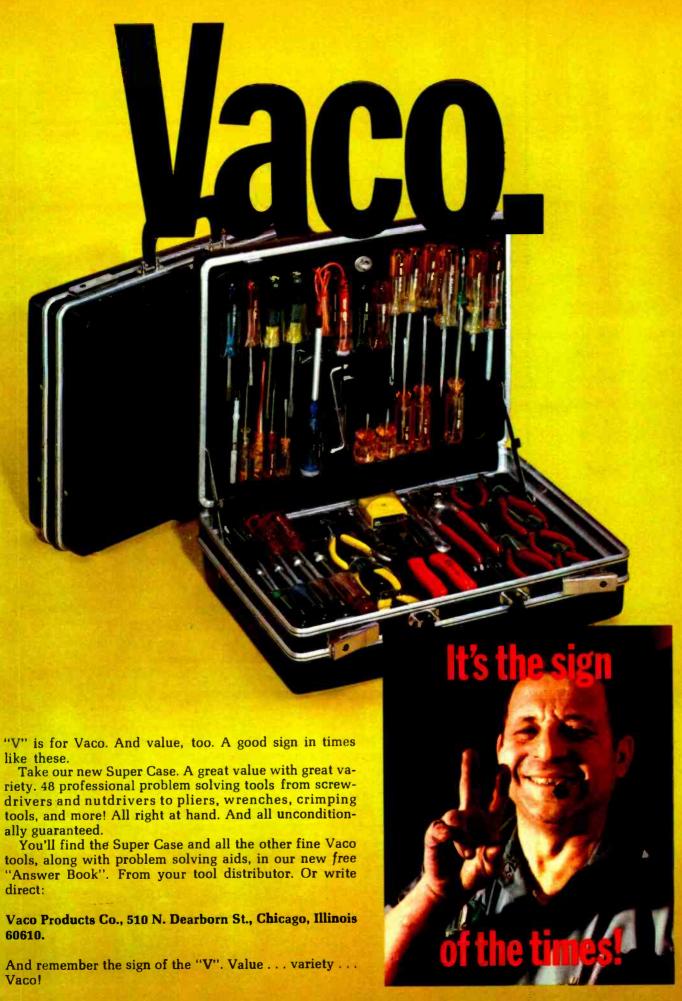

Avoid serious trouble in color TV sets by using the <u>right</u> replacement capacitor!



This capacitor is GREAT for 90% of your film capacitor replacements. But . . . it's NOT designed for certain critical applications.

SPRAGUE
TYPE PP
polypropylene film

SPRAGUE
TYPE PM
polycarhenete film

These capacitors are a MUST for critical commutating and S-shaping applications.

The next time you replace a dipped tubular in one of the newer color TV sets, don't automatically assume you're replacing an ordinary every-day film or paper capacitor. If it happens to be a deflection capacitor used for commutating or S-shaping, you need a polypropylene or polycarbonate film replacement with (1) high a-c current-carrying capability; (2) close capacitance tolerance; (3) good capacitance stability. The standard replacement

capacitors used in the industry, even our superior Type PS dipped tubulars, just won't do the job . . . and they could cause the set to become inoperative again.

Play it safe . . . dipped tubulars may look alike on the surface, but there can be a big difference in the film dielectric. Keep a supply of Sprague Type PP and PM capacitors on hand for those critical situations where ordinary replacements won't work.

SPRAGUE TYPE PP POLYPROPYLENE FILM CAPACITORS

μF @ WVDC	Cap. Tol.	D. x L.	Cat. No.	μF @ WVDC	Cap. Tol.	D. x L.	Cat. No.
1.75 @ 100	±5%	.900 x 1.000	PM1-M1.75	.0039 @ 600	±5%	.400 x .800	PP6-D39S
1.5 @ 150	±5%	.800 x .937	PM15-M1.5	.01 @ 600 .066 @ 600	±5% ±5%	.500 x 1.250 .800 x 1.250	PP6-S10S PP6-S66S
.01 @ 400	±5%	.400 x .750	PP4-S10	.075 @ 600	±5%	$.750 \times 1.250$	PPS-S75S
.015 @ 400 .033 @ 400	±5%	.450 x .750	PP4-S15	.022 @ 800	±3%	.600 x 1.300	PP8-S22S
.033 @ 400 .06 @ 400 .081 @ 400	±5% ±5% ±2%	.500 x .750 .800 x 1.250	PP4-S33S PP4-S60S	.047 @ 800 .051 @ 800	±5% ±5%	.700 x 1.250 .800 x 1.250	PP8-S47S PP8-S51S
.2 @ 400	±5%	.600 x 1.300 .700 x 1.700	PP4-S81S PP4-P20	.0018 @ 1600 .002 @ 1600	±5% ±5%	.500 x 1.300 .500 x 1.300	PP16-D18 PP16-D20
.0018 @ 600 .0022 @ 600	±5% ±5%	.400 x .750 .400 x .750	PP6-D18S PP6-D22S	.0033 @ 1600 .0039 @ 1600	±5% ±5%	.550 x 1.300 .600 x 1.300	PP16-D33 PP16-D39

For cross-reference information on close-tolerance polypropylene and polycarbonate film capacitors, showing original part numbers with correct Sprague replacements, ask your Sprague distributor for Cross-Reference Guide C-873, or write to: Sprague Products Company, 81 Marshall Street, North Adams, Mass. 01247.

THE BROAD-LINE PRODUCER OF ELECTRONIC PARTS



in-Electronics

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

More than 65 years of electronics publishing

MAY 1975 Vol. 46 No. 5

TEST EQUIPMENT

- 20 Equipment Report Lectrotech TO-60 dual-trace oscilloscope
- 8 Great Lab Power Supplies A complete family of power supplies for the bench. There's one that's right for you. by Larry Steckler
- All About Curve Tracers Concluding article wraps-up curve-tracer applications. by Charles Gilmore

HI-FI **AUDIO STEREO**

Bias And Tape Equalization R-E's contributing high-fidelity editor tells it like it is. by Len Feldman

GENERAL ELECTRONICS

- 4 Looking Ahead Tomorrow's news today. by David Lachenbruch
- **Equipment Report** Tri-Star Tiger electronic ignition system.
- Inside Op-Amps A detailed look at the how and why behind how they work. by Don Lancaster
- Measure dB's With Your Scope Easy once you know how. by John D. Gabbert
- **Buck Or Boost** Combine transformers to produce higher or lower voltages, by Lyman E. Greenlee
- 72 R-E's Replacement Transistor Directory One more page for your growing directory. compiled by Elizabeth & Robert F. Scott

BUILD THIS ONE


20 COSMOS ALARM CIRCUITS More IC alarm circuits that are easy to build and work effectively. by R. M. Marston

TELEVISION

- 30 Equipment Report G-E MOV Varistor
- 41 Servicing MATV Systems Any competent technician can do it after he's learned the guidelines. by Bert Wolf
- 62 Sherlock Ohms And The Case Of The Substitute Sync Detective work solves a TV problem. by Jack Darr
- Service Clinic Those HEW Circuits. by Jack Darr
- Reader Questions R-E's service editor solves reader problems.

DEPARTMENTS

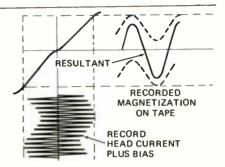- 106 **Advertising Index**
 - Letters
 - 6 New & Timely
- **New Literature** 92
- **New Products** 87
- **Next Month**
- **Reader Service Card** 109
- 93, 95 **Service Questions**
 - 93 Try This









AUDIO

BIAS MIXED

TAPE BIAS is combined with audio signal. For full details see page 70.

Hugo Gernsback (1884-1967) founder M. Harvey Gernsback editor-in-chief and publisher

Larry Steckler, CET, editor Robert F. Scott, W2PWG, CET, technical editor

Arthur Kleiman, associate editor Jack Darr, CET service editor Leonard Feldman

contributing high-fidelity editor David Lachenbruch, contributing editor Karl Savon, semiconductor editor Barbara Schwartz, editorial assistant Vincent P. Cicenia, production manager Sarah Martin, production assistant Harriet I. Matysko, circulation director Arline R. Bailey, advertising coordinator Advertising Sales Offices, see page 106

Cover photo courtesy Heath Company Cover design by Louis G. Rubsamen

Radio Electronics is a member of the Institute of High Fidelity and is indexed in Applied Science & Technology Index and Readers Guide to Periodical Literature.

in U.S.A.

Radio-Electronics, Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Phone: 212-777-6400. Second-class postage paid at New York, NY and additional mailing offices. One-year subscription rate: U.S.A., U.S. possessions and Canada, \$8.75. Pan-American countries, \$10.25. Other countries, \$10.75. Single copies 75c. © 1975 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

Subscription Service: Mail all subscription orders, changes, correspondence and Postmaster Notices of undelivered copies (Form 3579) to Radio-Electronics Subscription Service, Boulder, CO 80302.

A stamped self-addressed envelope must ac-company all submitted manuscripts and/or art-work or photographs if their return is desired should they be rejected. We disclaim any re-sponsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

As a service to readers, Radio-Electronics publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, Radio-Electronics disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

looking ahead

New watch readout

Digital wristwatches may well be the wave of the future, but many watchmakers feel that readouts leave something to be desired. Of the two types currently used, the LED is easier to read, but requires the use of two hands, because the free hand must be used to push the button to turn on the display. This makes it difficult to take a surreptitious look at your watch without letting others know about it. Liquid-crystal displays can be read onehanded, but they're often hard to read in low light conditions because of insufficient contrast.

A new type of display is attracting attention now. It is the electrochromic readout, employing metallic chemicals that change to a dark color when a voltage is applied, and keep their color until the voltage is reversed. The numbers are conventional sevensegment figures that stand out clearly against the background and can be designed to show up in any of a large number of colors and shades. The price of the new display is said to be competitive with both LED and LCD devices and the power drain is claimed to be less. American Cyanamid, who holds several electrochromic patents, is understood to be the leader in the field. An experimental watch program is under way in Switzerland using the displays now. But don't expect to see them in calculatorstheir response time is too slow, at least for the time being.

Back to 90 days

As expected—and forecast here two months ago—Zenith has decided to go along with the trend to reduce labor warranties on solid-state color TV sets from one year to 90 days, starting with the 1976

models, to be introduced in May and June. RCA and Sylvania had already announced their intentions to reduce warranties. The cutbacks represent an attempt to reduce costs and, the manufacturers say, avoid the necessity for large price increases-although there are expected to be some price hikes in the new sets, anyway. The financial reports of TV manufacturers indicate that most of them lost money on the production of television sets last

G-E quits audio

Another mass-market manufacturer is curtailing its product lines. General Electric, believed to be the largest marketer of phonographs in the United States with sales of more than a million units annually, has decided to discontinue manufacturing and eventually the marketing of phonographs, including compact stereo systems. G-E will continue to sell radios, tape recorders and players, and, of course, television. Last year, RCA discontinued all audio products, including

The big British recordchanger manufacturer BSR, meanwhile, has reached an agreement to buy the second biggest mass-market changer maker, Glenburn. Both firms were formed by Danial Mc-Donald, whose name is used on BSR's audiophile turntable.

TV saves energy

Television probably is the only product which has already met its government-established energy conservation goal for 1980. The Commerce Department is assigning each major product a target for energy saving by 1980. The TV industry was charged with reducing the average power consumption of its products

by 25% between January 1972 and December 1980. The EIA estimates that the average set made in 1974 consumed 147 watts as compared with 225 watts for 1973 sets-a decrease of about 35%. Most of the decrease is the result of the increasing proportion of solid-state sets in television's mix, but the rise in the number of smallscreen sets and the increasing use of slot-mask picture tubes has probably been another factor. There will be further energy savings as the industry shifts completely to solid-state. (In 1974, 72.6% of the color sets produced or imported into the U.S. were solid-state, up from 51.1% in 1973. All-solid-state circuitry was featured in 39.1% of monochrome sets last year, up from 20.3% in 1973.) The government isn't asking for an energy reduction for audio products.

Troubled calculators

The turbulent calculator industry has incurred a major casualty. Bowmar Instruments, one of the pioneer manufacturers and still one of the top four producers, has filed a petition for voluntary bankruptcy because of inability to pay its debts. The company is being reorganized. Earlier, Bowmar had filed a \$240-million patent and anti-trust suit against its major chip supplier Texas Instruments.

The fierce competition in the calculator field has driven prices steadily downward. It's estimated that some 15 million were produced last year. And already this year, handheld four-function calculators—which sold for \$100 and up as recently as 1972—have been sold as low as \$9.95.

'Emergency radio'

Those low-cost radios capable of tuning to the rapidly

increasing number of government weather radio channels are going to become more indispensible as the result of a new ruling by the President's Office of Telecommunications Policy. After years of experimenting with various emergency warning systems, the government has decided that the weather channels will constitute the sole federally operated radio system for communicating attack or disaster warnings directly to the public. The system will incorporate a tone-alert signal designed to activate special home radios automatically. The OTP said consumer use of the system will be completely voluntary and there's no intent to "legislate a warning receiver into the private home.'

Tubeless TV camera

The first television camera to provide a standard 525line video signal without a pickup tube is being placed on the market by RCA in sample developmental quantities. The pickup element is a postage-stamp sized charge-coupled device, with 512 elements horizontally by 320 vertically. Other CCD cameras are currently on the market, but none of them approach the high-resolution capabilities of the RCA unit or are capable of being used with an unmodified standard TV set as monitor.

The CCD chips are still highly expensive — RCA is selling them at \$1500 and \$2300, depending on quality —but an RCA official forecast they'd be selling for about \$30 in the early 1980's or possibly sooner. The CCD principle is seen as most likely to make possible the low-cost home color cameras required by upcoming generations of consumer color videotape recorders.

by DAVID LACHENBRUCH CONTRIBUTING EDITOR

Your sure-fire smoke detector is here...the Mallory SDA3 Alarm.

Automatically, 'round the clock, when hazardous smoke fumes threaten, it sounds a life-saving intermittent blast—so loud it can break through the deepest sleep.

The Mallory Smoke Detector Alarm is completely self-contained, battery-powered. It installs easily on ceilings—in hallways, bedrooms, wherever warning for escape from lethal combustion products (visible or invisible) is needed.

And the 12.6-volt Mallory battery is specially designed for added security. It changes characteristics after a life of approximately one year and the Alarm then emits a burst of sound at one-minute intervals, signaling that a fresh battery is needed.

All for a price so affordable, every home, apartment, trailer, office can have sure-fire smoke-alarm protection.

For details, see your Mallory distributor.





MALLORY DISTRIBUTOR PRODUCTS COMPANY

a division of P. R. MALLORY & CO. INC. Box 1284, Indianapolis, Indiana 46206; Telephone: 317-856-3731

Batteries • Capacitors • Controls • Security Products • OURATAPE® • Resistors • Semiconductors • SONALERT® • Switches • Timing Devices and Motors

DURACELL®, DURATAPE® and SONALERT® are registered trademarks of P. R. Mallory & Co. Inc.

new & timely

Cinemascope-like color TV is now possible with new system

A new projection-TV system, recently demonstrated in New York by General Electric, transmits wide-screen pictures with standard equipment. It may make network wide-screen theater television practical.

The color TV camera is equipped with a cinemascope-type (anamorphic) lens to compress an 8×3 view into the standard 4×3 television format, which is then handled as an ordinary TV signal. At the receiving end, another anamorphic lens broadens the picture out again into the wide-screen 8×3 aspect. The process of compression and re-expansion is optical rather than electronic. Pictures can be up to 20 feet wide.



SPECIAL ULTRA-WIDE-SCREEN LENS being adjusted by Dr. William Good, manager of G-E's Video Display Operation in Syracuse, NY, makes a Cinemascope-like screen display available to projection television theaters.

To get the light necessary for largescreen projection, G-E's single-gun light valve system is used. Illumination from a 650-watt sealed-beam xenon tube is modulated by passing it through a deformable membrane composed of an oily substance. The membrance is scanned by three electron beams that pass through three diffraction gratings, each of which transmits one of the color television signals. Deformation of the membrane in accordance with the electrical signal causes it to transmit more or less of the light from the xenon tube. The optical image thus produced is focused on the projection lens, which spreads it out to the large-screen aspect.

The single-gun light valve is already being used in a number of industrial aplications. Its single gun needs no convergence adjustments, and it is free of the problems of adjusting the image for picture and color registration that is practically insurmountable in the widescreen format for any system using three optical paths. These advantages may hasten the day of the wide-screen "teevie" house.

Veteran Wireless Operators celebrate golden anniversary

Fifty years ago, a new radio organization was introduced dramatically by Radio WRNY, the broadcast station owned jointly by Hugo and Sydney Gernsback, and situated in the Hotel Roosevelt in New York City.

"This is Radio News Station, WRNY. You are about to hear one of the most extraordinary broadcasts in the history of wireless communication. We are broadcasting the first official meeting of a group of wireless men who are about to form a society or an organization."

Thus, in 1925, the Veteran Wireless Operators Association was founded. Dedicated to fostering a fraternal spirit among wireless operators and to recognize meritorious services by them, it conducts an annual memorial service at the Wireless Operators Monument, erected in New York City's Battery Park in memory of operators who lost their lives in performance of their duty. It adds bronze plaques as other names are added to the list of radio officers who have gone down with their ships.

The Association also presents awards to deserving figures in the communications field at annual awards banquets held each February. Marconi, de Forest, Sarnoff, Barry Goldwater (K7UGA-K3UIG) and Zworykin have been among those so honored. The Golden Anniversary Banquet was held February 22, 1975.

The address of the Association is: Box 35, Church Street Station, New York, NY 10008.

Optoelectronic system frees headphones from cords

A cord-free headphone system just developed by Siemens uses modulated infrared light as a medium, with a photodiode as the receiver and a number of luminescent diodes in parallel as the transmitter. Infrared is particularly suitable for transmitting purposes. The radiation cannot be absorbed nor distorted by dark or rough areas, and pro-

truding edges of furniture have no effect on the quality of reproduction. The signal-carrying "light" is evenly diffused throughout the room, and the headphones do not have to be trained in any particular direction.

The new silicon optodiode receiver element (Siemens BPW 34) was developed with special attention to achieving the smallest possible capacitance, despite its rather large area of 9 mm². It is covered with a filter to prevent other than infrared light from producing signals in the diode. The transmitter elements are Siemens LD 241 luminescent diodes. An array of smaller diodes rather than one large one makes impedance matching easier. Four such diodes produce a peak output of 60 mW, which is adequate for a



SIEMENS BPW 34's on a musical background.

medium-size room. Four diodes, doubling the power, will cover a small hall.

The system was originally intended for home entertainment devices designed for headphone reception, but would be suitable for studio use where it would not create nor be affected by electromagnetic interference. It could also be used for multichannel remote control systems.

Yankee technician maintains Tonga communications network

William P. Bowden, former RCA technician from Sherman Oaks, CA, is fast becoming an important figure in South

(continued on page 12)

TUNER SERVICE CORPORATION





FEATURES

- A UHF Tuner with 70 channels which are detented and indicated just like VHF channels.
- A VHF Hi Gain Solid State Tuner.
- AC Powered.
- 90 Day Warranty.

Demonstrate the **SUESTITUMER** to your customers and show improved reception with their TV sets.

You may place your order through any of the Centers listed below.

PROVIDES YOU WITH A COMPLETE SERVICE FOR ALL YOUR TELEVISION TUNER REQUIREMENTS.

REPAIR

VHF OR UHF ANY TYPE (U.S.A. ONLY) \$ 9.95 UHF/VHF COMBINATION (U.S.A. ONLY) \$15.00

- IN THIS PRICE ALL PARTS ARE INCLUDED.

 Tubes, transistors, diodes, and nuvistors are charged extra. This price does not include mutilated tuners.
- Fast, efficient service at our conveniently located Service Centers.
- All tuners are ultrasonically cleaned, repaired, realigned, and air tested.



UNIVERSAL REPLACEMENT TUNER \$12.95 (U.S.A. ONLY)

- This price buys you a complete new tuner built specifically by Sarkes Tarzian Inc. for this purpose.
- All shafts have a maximum length of 10 $\frac{1}{2}$ " which can be cut to 1 $\frac{1}{2}$ ".
- Specify heater type parallel and series 450 mA.

CUSTOMIZE

- Customized tuners are available at a cost of only \$15.95. With trade-in \$13.95. (U.S.A. ONLY)
- Send in your original tuner for comparison purposes to Franchises listed below.



WATCH US GROW

HEADQUARTERS	BLOOMINGTON, INDIANA 47401	537 South Walnut Street	Tel. 812-334-0411
ARIZONA	TUCSON, ARIZONA 85713		Tel. 602-791-9243
CALIFORNIA	NORTH HOLLYWOOD, CALIF. 91601		
CAEIFORNIA	BURLINGAME, CALIF. 94010	1324 Marsten Road	Tel. 415-347 5728
11 0	MODESTO, CALIF 95351	123 Phoenix Avenue	Tel 209-521-8051
FLORIDA	TAMPA FLORIDA 33606	1505 Cypress Street	Tel. 813-253-0324
TEOMIDA		906 East 25th Street	Tel. 305-836-7078
GEORGIA	ATLANTA, GEORGIA 30310	CONTRACTOR OF THE PROPERTY OF	Tel. 404-758-2232
ILLINOIS		405 East University Street	. Tel. 217-356-6400
122110	CHICAGO ILLINOIS 60621	737 West 55th Street	Tel. 312-873-5556-7
A STATE OF THE PARTY OF THE PAR	SKOKIE, IULINOIS 60076		Tel. 312-675-0230
INDIANA		6833 Grand Avenue	el 219-845-2676
	INDIANAPOLIS, INDIANA 46204	112 West St. Clair Street	7-632-3493
KENTUCKY	LOUISVILLE KENTUCKY 40208	2920 Taylor Boulevard	Tel 602-634-3334
LOUISIANA	SHREVEPORT, LOUISIANA 71104	3025 Highland Avanue	Tel 318-221-3027
MARYLAND	BASTIMORE, MARYLAND 21215	. 5505 Reisterstown Rd. Box 2005	
MISSOURI	ST. LOUIS, MISSOURI 63132	10530 Page Avenue	Tel, 314-429-0633
NEVADA	LAS VEGAS, NEVADA 89102	1412 Western Avenue No. 1	702-384-4235
NEW JERSEY	TRENTON NEW JERSEY 08638	do. marin black stronge	Tel. 609-393-0999
	JERSEY CITY, NEW JERSEY 07307	547-49-Fonnele Ale., Hwy.1 & 9	Tel. 201-792-3730
OHIO	CINCINNATI, OHIO 45216	7450 Vine Street	//. Tel. 513-821-5080
	CLEVELAND, OHIO 44109	4525 Pearl Road J	Tel. 216-741-2314
OREGON		1732 N.W. 25th Avenue	Tel. 503-222-9059
TENNESSEE	GREENEVILLE TENNESSEE 37743	1215 Snapps Feety Rend	el. 615-639-8451
	MEMPHIS TENNESSEE 38111	3158 Bargon Avenue	. Tel. 901-458-2355
TEXAS			Tel. 214-327-8413
VIRGINIA		3295 Santos Street	
WISCONSIN	MILWAUKEE, WISCONSIN 53216	4722 West Fond Du Lac Avenue	Tel. 414-871-7655
CANADA			
	CALGARY, ALBERTA		

IF YOU WANT TO BRANCH OUT INTO THE TV TUNER REPAIR BUSINESS, WRITE TO THE BLOOMINGTON HEADQUARTERS ABOUT A FRANCHISE.

The real way to learn digital electronics!



NRI is the only school to train you at home on a real digital computer.



Learn computer design, construction, maintenance and programming techniques on your own digital computer using a professional digital multimeter!

Qualified technicians are urgently needed for careers in the exciting new field of digital and computer electronics . . . and the best way to learn digital logic and operations is now available to you in NRI's Complete Computer Electronics Course.

This exclusive course trains you at home on your own digital computer! This is no beginner's "logic trainer", but a complete programmable digital computer that contains a memory and is fully automatic. You build it yourself and use it to define and flow-chart a program, code your program, store your program and data in the memory bank. Press the start button and the computer solves your

NOW...
YOUR OWN DIGITAL (3½ DIGITS)
MULTIMETER INCLUDED
AT NO EXTRA COST!

The latest in digital testing equipment . . . along with valuable training experiments in digital techniques.

problem and displays the result instantly.

The NRI digital computer is one of 10 kits you receive in the NRI Complete Computer Electronics Course. You build and use your own 3½ digit digital multimeter... while you perform hundreds of experiments, building hundreds of circuits, learning organization, operation, troubleshooting and programming.

Only NRI offers you five TV/Audio Servicing Courses



Color TV repair is another big opportunity field right now and NRI can train you at home to service and repair any color or black white TV, hi-fi equipment, AM-FM radios, and sound systems. You can choose from

5 courses, starting with a basic servicing course with 65 lessons...up to a Master Color TV course, complete with 25" diagonal solid state color TV in handsome woodgrain cabinet. No other school offers so many choices or so much value.

All courses are available with low down payment and convenient monthly payments to fit your budget. And all courses provide professional tools and equipment along with NRI-designed kits for handson training. With the Master Course, for instance, you receive your own 5" wide-band triggered sweep solid state oscilloscope, TV pattern generator, 3½ digit digital multimeter and a NRI 25" diagonal solid state television receiver expressly designed for color TV training.

YOU PAY LESS WITH NRI TRAINING AND YOU GET MORE FOR YOUR MONEY.

NRI employs no salesmen, pays no commissions. We pass the savings on to you in reduced tuitions and extras in the way of professional equipment, testing instruments, etc. You can pay more, but you can't get better training.

NRI's complete communication course includes your own CB Training Transceiver





NRI prepares you for a career in the rapidly expanding field of communications . . . a field destined to double in the next decade! NRI can train you at home for one of the thousands of service and

maintenance jobs opening in AM and FM Transmission and Reception, TV Broadcasting, Microwave Systems, Teletype, Radar, Marine Electronics, Mobile Communications and Aircraft Electronics. You train on your own 23-channel Johnson Transceiver and AC power supply; a digital multimeter, for digital experiments and precise testing; bitesize lessons leading to your FCC license and the communications field of your choice.

NEARLY ONE MILLION STUDENTS IN 60 YEARS HAVE LEARNED AT HOME THE NRI WAY.

Mail the insert card and discover for yourself why NRI is the recognized leader in home study training. No salesman will call. Do it today and get started on that new career.

APPROVED UNDER GI BILL

For the career minded, we are approved for veterans benefits. Check box on card for detalls.

MAIL THE INSERT CARD FOR YOUR FREE NRI CATALOG

No salesman will call



NRI SCHOOLS

McGraw-Hill Continuing Education Center 3939 Wisconsin Avenue, Washington, D.C. 20016 3-055



RADIO-ELECTRONICS

YOU'LL **NEVER NEED ANOTHER** TUBE TESTER.



The Hickok Model 230 Solid State Dynamic Emission Tube Tester is a rugged performer, built for a lifetime of day-in day-out service. In addition to the best warranty in the business, the 230 offers easily replaced sockets and components for lifetime serviceability.

The Model 230 has all the critical tests you need, including:

- Opens test for all elements (a Hickok exclusive).
- A directly metered H-K leakage test.
- True tests for shorts, and for all new and old tubes.

Ask to see the Hickok Model 230 at your Hickok distributor or contact us for more information.

\$155⁰⁰ HICKOK


the value innovator

INSTRUMENTATION & CONTROLS DIVISION THE HICKOK ELECTRICAL INSTRUMENT CO. 10514 Oupont Avenue • Cleveland. Ohio 44108 (216) 541-8060 • TWX: 810-421-8286

new & timely (continued from page 6)

volunteer, he is working as a radio repair technician in the Telephone and Telegraph department of the kingdom of Tonga (once known as the Friendly Islands), a country of 150 islands and 96,000 people east of Fiji.

work, Bowden says, is not

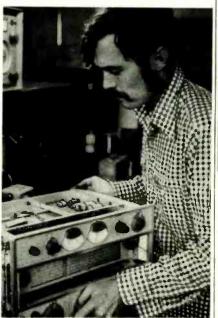

PEACE CORPS VOLUNTEER TECHNICIAN William Bowden checks a signal generator in the Tonga Telephone & Telegraph Dept. workshop.

monotonous. The department handles overseas communications, radio and telegraph between the islands, the nonautomated telephone exchange, airport communications, ships radars, ship-toshore and even mobile police radios.

Bowden is also training young Tongans in electronics, working with three radio repair apprentices and supplying lesson materials to the instructors in charge of the department's electronic training course.


Fish signal their passage through dangerous waters

Radio-Electronics readers are familiar with the use of miniature radio transmitters to check the movements and habits of small wild animals. Now fish have adopted the technique and signal to Fish and Game researchers how well they are able to overcome hazards while ascending rivers to spawn.

The Division of Fishery Services in Laconia, NH, is "tagging" sea run sal- one over the Indian Ocean.

Pacific communications. A Peace Corps mon and shad with tiny radio transmitters to determine how well they can get through a pump storage reservoir, and how many don't make it.

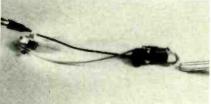The transmitter-about the size of a peanut-is placed inside the fish, since externally attached tags have been found to hamper their swimming ability and would reduce its chances of getting through difficult places. The fish is anesthetized and the transmitter inserted through the throat into the stomach. A small protrusion on the



transmitter prevents it from leaving the stomach and being expelled by the fish. After a time, stomach juices dissolve the protrusion and the fish is able to eliminate the transmitter.

By that time, the biologists have the information they need and know whether the fish does, in fact, pass into and out of a pump storage unit, and if so, what are the effects and the percentage of



SWITCHBOARD-IN-THE-SKY, completed with the sixth Intelsat IV satellite, launched over the Pacific, 22,000 miles high and one degree from the International date line. It surrounds the earth with a ring of communication stations. The new satellite, built by Hughes Aircraft Co., backs up and adds capacity to the original Pacific satellite, launched in January 1972. They serve the 1.3 billion people of the Pacific basin through 19 earth stations scattered from the USA to Singapore. There are six satellites altogether, three over the Atlantic and



Microphones matter most.



Never have so few words said so much about sound system installations. The truth is that a carefully chosen, top-quality microphone makes a measurable difference in sound system quality—regardless of the other components in the system. It is false economy at its worst to be a microphone miser. Install Shure Unidyne or Unisphere microphones—for installations with a marked superiority in voice intelligibility (and fewer service calls due to microphone problems).

Shure Brothers Inc.
222 Hartrey Ave., Evanston, Illinois 60204
In Canada: A. C. Simmonds & Sons Ltd.







Kit or Assembled, they out-feature any others for the price.

Analog models from \$169.95

Digital models from \$219.95

Heath sets a new benchmark for lab-grade power supplies with the new "2700" series. Their precision, stability, and ease of operation make them ideal for laboratories, yet their prices put them in reach of hobbyists and technicians alike.

Wide model choice. Choose from 4 DC voltage ranges; 0-7.5V. @ 10A., 0-15V. @ 5A., 0-30V. @ 3A., 0-60V. @ 1.5A. Choose 3½ digit readout or 3½" analog meter readout. Choose kit or assembled models. All kit analog models are 169.95; kit digital models 219.95; assembled analog models 255.00; assembled digital models 340.00.

More features, more versatility. Constant voltage and constant current (not simple current limiting, but fully specifed constant current operation), each independent of the other. Complete voltage and current programmability with rear panel connectors for external control. Remote sensing at the load compensates for lead and connector voltage drop. Any of the supplies can be connected in auto-series or auto-parallel to deliver specific voltages or currents beyond that of single units. When two supplies of the same rating are connected in series, internal circuitry insures proper voltage sharing to maintain regulation. Supplies of different ratings can be connected in series with external circuitry. Units operate in master-slave configuration. Two or more supplies can be connected in parallel for greater current capacity. They will deliver 80% of current rating with no loss of regulation, regardless of load. Full protection against indefinite short-circuit operation, accidentally applied voltages, and open remote-sensing leads. For full information including the superb specifications of this new series, see the new Heathkit catalog.



15, 17 & 19" (diagonal) Color TVs with On-Screen Digital Readout

Advanced Heath engineering and outstanding picture quality. All feature on-screen channel readout & optional plug-in clock modules. In-line picture tubes with slotted shadow masks provide exceptionally bright, sharp pictures. In the GR-400 and 500, black matrix tubes improve contrast. And here's something new — static toroid yoke & magnet assemblies never require convergence & fixed LC filters eliminate instrument IF alignment. GR-300 & 400 come with walnut veneer cabinets; cabinets for the GR-500 start at \$39.95.*

Kit	GR-300 (15	" diag.), w	vith cabinet		449.95*
Kit	GR-400 (17	" diag.), w	ith cabinet		489.95*
Kit	GR-500 (19	" diag.), le	ess cabinet		499.95*
Kit	GRA-2000-	1. Digital C	lock Module	e	. 29.95*



Highly Acclaimed GR-2000 Digital-Design Color TV

The set that brought TV into the digital age — and still one of the finest made. Tuning is totally digital solid-state & the channel number appears right on the big, 25" (diagonal) screen. The optional clock module also displays the time on the screen. For the ultimate in convenience, add the optional wireless remote control. Can be custom mounted; optional cabinets start at \$119.95*.

Kit GR-2000, less cabinet	669.95*
Kit GRA-2000-1, Digital Clock Module	29.95*

YOUR FREE HEATHKIT CATALOG



NEW Heathkit Stereo "Super-Amp"

200 watts, minimum RMS, per channel into 8 ohms with less than 0.1% total harmonic distortion from 20-20,000 Hz.

AA-1640 \$439.95, less meters

Specifications don't say it all, but they do indicate the quality of this exceptional amplifier. Take the power statement above, for example; if you are familiar with Heath's conservative stance in specifications, you will know that there's no question that this amplifier will do at least that well. The same holds true for the exceptionally low distortion figures. Other impressive figures are: hum and noise 100 dB below full output; damping factor greater than 50; channel separation 50 dB minimum.

The features behind the specifications. The super power comes from the super power supply . . . a 25 lb. transformer that will maintain full output under the most demanding program material. Two 6 lb. die-cast heatsinks cool the 16 output transistors . . . no noisy fans are needed. Even when used as a PA amplifier, it needs only normal ventilation. Automatic circuitry helps protect your speakers; a 10-second delay protects your speakers from turn-on "thumps" and disconnects them instantly when power is turned off. The delay circuit also disconnects the speakers if it detects DC or extremely low-frequency AC at the outputs. Automatic thermal shut-down helps prevent damage from overheating. And speaker fuses are located within the

primary feedback loop...an exclusive Heath design which maintains a high damping factor for high-definition bass response.

Optional peak-responding meters continuously monitor the output. The back-lighted meters have linear calibrations from -30 to +3 dB and can also be read directly in watts from 0.2 to 200 watts into 8 ohms. So fast they even respond to record "clicks", they are useful as overload indicators. And if you buy the meters at the same time as the amp., you save \$20.

Front panel controls include pushbutton on/off, left and right channel gain controls, and LED power and high temperature indicators.

To hear music as you've never heard it before . . . build the AA-1640. For sheer power and exceptionally low distortion, we believe it is one of the finest amplifiers ever made. Super-amp . . . super-sound.

Kit AA-1640, less meters, 69 lbs., Exp/Frt	439.95
Kit AAA-1640-1, meters only, 4 lbs., mailable	. 69.95
Kit AA-1640 & Kit AAA-1640-1, 73 lbs., Exp/Frt	489.95



For fine home recording facilities and elaborate PA and sound reinforcement systems. Wide response (40-20,000 Hz, +1 dB) and low distortion (0.5%) with unusual versatility. Each of the two outputs has its own master control and meter and switchable for stereo or mono modes. Six inputs: two high-level for disc or tape, four low-level for microphones (switchable to high impedance, unbalanced, or low impedance, balanced). The fourth mic. input has a "pan" control to adjust its apparent location anywhere from left to right. All inputs can be individually switched to left, off, or right channel. Mixing bus access permits paralleling added mixers for extra inputs and outputs. Two lighted dual-range meters plus adjustable LED peak indicators. Slider controls and switches.



AM/FM Stereo Receiver...139.95

Proof that good sound can cost less. The preassembled AM/FM tuner section has 5 μv sensitivity for distant station reception. Ceramic filters offer 60 dB selectivity to remove alternate channel interference. AFC. Integrated circuit FM IF. Phase-locked toop integrated circuit multiplex. Direct-coupled amplifier design with an honest 4.5 watts, min. RMS, per channel into 8 ohms from 50-15,000 Hz with less than 1% total harmonic distortion. Slider vol. and balance controls; ganged rotary bass and treble controls. Inputs for ceramic cart. changer and tape. Handsome walnut-grained vinyl-clad plastic and metal enclosure included. It's one of Heath's new Valu-Component line; see them all in the Heathkit catalog.

Kit AC-1118, receiver, 15 lbs., mailable	9.95
Kit AS-1140, pair of speakers, 15 lbs	4.95
Order with speakers and save 5%	

HEATHKIT ELECTRONIC CENTERS — Units of Schlumberger Products Corporation Retail prices slightly higher.

Retail prices slightly higher.

ARIZ.: Phoenix; CALIF.: Ananeim, El Cerrito, Los Angeles, Pomona, Redwood City, San Diego (La Mesa), Woodland Hills; COLO.: Denver; CONN.: Hartford (Avon); FLA.: Miámi (Hialeah), Tampa; GA.: Atlanta; ILL: Chicago, Downers Grove; IND.: Indianapolis; KANSAS: Kansas City (Mission); KY.: Louisville; LA.: New Orleans (Kenner); MD.: Baltimore, Rockville; MASS.: Boston (Wellesley); MICH.: Detroit; MINN.: Minneapolis (Hopkins); MO.: St. Louis (Bridgeton); NEB.: Omaha; N.J.: Fair Lawn; N.Y.: Buffalo (Amherst), New York City, Jericho (L.I.), Rochester, White Plains; OHIO: Cincinnati (Woodlawn), Cleveland, Columbus, Toledo; PA.: Philadelphia, Pittsburgh; R.I.: Providence (Warwick); TEXAS: Daltas, Houston; VA.: Norfolk (Va. Beach); WASH.: Seattle; WIS.: Milwaukee.



New Heathkit Catalog shows these and 350 other easy-to-build kits including Color TV, Stereo, Test, Marine, Amateur Radio, etc. Send today.

Send for FREE Catalog

Hoath Compa	ny, Dept. 20-05		EATH
Benton Harbo		Schlu	mberger
() Enclosed is	Free Heathkit Catalog. \$; please ship mo	dels	
NAME			
ADDRESS			
CITY	STATE	ZIP	
	S SUBJEC? TO CHANGE WITHOUT NOTICE.		CL-564

RADIO-ELECTRONICS

FIEE ECO CAMPOS

346 Ways To Save On Instruments, Burglar Alarms, Automotive & Hobby Electronics!

The more you know about electronics, the more you'll appreciate EICO. We have a wide range of products for you to choose from, each designed to provide you with the most pleasure and quality performance for your money. The fact that more than 3 million EICO products are in use attests to their quality and performance.

"Build-it-Yourself" and save up to 50% with our famous electronic kits.

For latest EICO Catalog on Test
Instruments, Automotive and Hobby
Electronics, Eicocraft Project kits,
Burglar-Fire Alarm Systems and name
of nearest EICO Distributor, check reader
service card or send 50 c for fast first
class mail service.

EICO—283 Malta Street, Brooklyn, N.Y. 11207

Leadership in creative electronics since 1945.

FICO

letters

ME, OH MY. ME AND MY SINEWAVES!

In the Service Clinic for November 1974, I showed the results I got from playing with a function generator and an R-C network. (I wasn't kidding; I really was playing!) I wrote it up mostly as a sort of "Well, well! Look what happens here!" thing. Didn't expect it to be printed.

I have received a surprising amount of mail from readers on this. Most of them, quite correctly, took me to task for saying that a sinewave wasn't changed by passing through the integrating and differentiating networks. (One of my books did give me an explanation something like that. Needless to say, I can't find it now!)

Here is the correct explanation: what looks like a sine wave is really a cosine wave; practically the same as the original sinewave but shifted in phase by 90 degrees! Since I was using a single-trace scope, this was not apparent; a dual-trace will show it.

For one more, the "change a triangular wave to a sine wave" is not precisely correct, either. This is actually a parabolic waveform. To the Uncalibrated Eyeball, it does look like a sine wave. In fact (and here I was right for a change!) quite a few function generators actually make a very good sine wave from a triangle. However, they do it with a good sized network of diodes and resistors, etc. Thanks very much to the many readers who took the time to write about it, especially Ken Holet of G-E Applications Engineering. He spotted the parabolic wave!

JACK DARR Service Editor

UART TO TVT

In the article "Add This UART To Your TV Typewriter" (Radio Electronics, Feb. 1975), a diagram was omitted from step 3 of the "Changes To TV Typewriter." This diagram (Fig. 1) shows connections to IC6 and IC1. Connect IC1 pins 8, 9 and 10 as shown. Also, the correct equation should be $CR = A6 \cdot A7 \cdot A3$

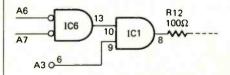


Fig. 1

Several readers have asked about my statement in the article that mentions adding a 74123 and relay for automatic

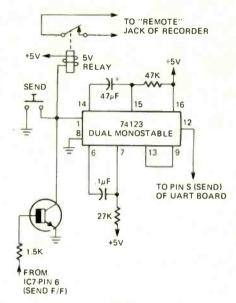


Fig. 2

START and STOP of the tape recorder. The accompanying diagram (Fig. 2) should explain how. The idea is to delay the SEND signal to the UART for a second or so until the recorder reaches speed. Depress SEND pushbutton and hold until characters start to be transmitted

ROGER SMITH Phoenix, AZ

OOOPS!

I read your "New & Timely" article (page 12) in the November Radio-Electronics with great interest. Unfortunately, the statement that the color TV camera is manufactured by Motorola is *incorrect*. It is actually designed and manufactured by Magnavox.

The camera used at Mount Sinai is the Magnavox Chromavue 400 and we have been shipping it for the last 1½ years.

We also offer a battery-powered version called the Chromavue 440. Suggested price for this unit is \$2750. And . . . it is designed to match up with the new color battery-powered video table recorders.

I would appreciate it if you print a correction in your next issue. The camera is, in fact, a Magnavox Chromavue 400. And . . . Magnavox is, in fact, the first manufacturer to offer a color TV camera at such a low price. Plus . . . it is built in Magnavox plants in the U.S.A.

JOHN C. COPE Magnavox Video Systems Ft. Wayne, IN

410 to 1 you'll find devices you need

Over 103,200 devices can be replaced by 250 RCA SK Series types. That's 410 to 1! Best ratio in the industry. Which means the odds are, SK is your best, fastest way to get what you need. With

minimum inventory.
And RCA provides the top quality you'd expect from a top manufacturer of OEM devices.
Same strict AQL standards, same strict Directorof Quality Assurance.
Get SK devices and your free 1975 SK
Series Replacement Guide from your local RCA distributor.





RADIO-ELECTRONICS

More chances to be right



Thousands more cross references



Transistor kit for foreign sets



Replacement amplifier modules



All the help you need at your authorized distributor

Tube Products Department General Electric Company Owensboro, Kentucky 42301

GENERAL 8 ELECTRIC

equipment reports

Tri-Star Tiger Capacitive-Discharge Ignition Simpli-Kit



Circle 101 on reader service card

AS THE COSTS OF DRIVING AND MAINTAINing a car continue to rise, many people are turning to the field of automotive electronics for help. One area of recent interest in this slightly ignored field is the electronic ignition system. Until this year, there have been only two ways to obtain the benefits of better performance offered by the electronic system. You could either buy a car with the electronic ignition system installed by the factory or find an automotive center that would install the system in your present car. Both of these alternatives presented a cost that was more than most motorists cared to pay. Now, with the advent of kits for electronic ignitions, there is a third and less expensive alternative.

Recently, I was considering installing such a system in my car. Faced with the costs of the three alternatives and my "college-student" budget, I chose to assemble and install the system myself. I chose a kit that is called the Tiger Capacitive Discharge Ignition Simpli-Kit. It is distributed by the Tri-Star Corporation of Grand Junction, Colorado. The kit consisted of all parts, equipment and instructions necessary to assemble and install the system. The only equipment that is needed is a soldering iron, a pair of wire cutters and a pair of screw-drivers. It is essential that you have some knowledge of soldering, but very little knowledge of electronics is necessary. Still, you will learn in the course of assembly a little about the difference between a diode and a transistor. The parts are pictured in the instruction book and the parts are color-coded so that people with a lack of electronics knowledge (like me) can not only tell a resistor from the solder but also a 270-ohm resistor from a 33-ohm resistor. The time for the assembly totalled about three hours. In other words, you could assemble the kit on a Sunday afternoon, I had very little trouble assembling the system due to the fact that the instructions and the kit were as the manufacturer said—simple.

As for installation in the car, it took about an hour to completely put the system to work. Although the kit includes hardware, a drill or punch is needed to install the ignition housing. There are easy-to-follow diagrams to help with the placing and wiring of the system in the car. In addition, there are instructions for trouble shooting and adjustments for cars with tachometers. When I finished the installation of the system, I was afraid to start the car for fear that my car would blow up or burn just like my cooking projects have done in the past. To my amazement, it did not burn but started better than ever. I decided to keep track of my gas mileage over a period of two weeks. I found that at the end of the period, my mileage increased by 3-4 miles per gallon. Although it was not a very scientific mileage report, it is a fact that the system delivered more miles per gallon of gasoline in my particular car.

As for the kit, its type is recognized as the most desirable for today's cars; a capacitive-discharge ignition system or CDI. It is favored because of its low current drain, constant output over various speed ranges and it allows the engine to remain in tune longer due to reduction of contact breaker wear. The kit also has a switch on the housing which allows the driver to change from CDI to the standard ignition in case of failure of the CDI. As said before, the kit sincludes all circuit boards, diodes, transformers and housing. The extra tools can be found in most homes or borrowed from a neighbor. Perhaps one of the best things about the kit is the fact that there is a guarantee for components to be free from defects in workmanship and material for ninety days. The guarantee does not cover mistakes in assembly methods and techniques.

I can honestly say that working with the kit helped me learn a little about electronics and my car. If you have an electronics amateur or professional in the house as I did, there are many things that can be learned in the course of assembling the kit about electronics such as the use of a voltmeter and the purpose of a transistor. I would recommend this kit for anyone that owns a car without a CDI.

(continued on page 20)

Power-play-mates



SANSUI's power playmates – the TU-7700 tuner and the AU-7700

amplifier are made for each other - by design.

The TU-7700AM/FM stereo tuner, a breakthrough in tuner development, has far less distortion and wider stereo sound separation than comparable tuners.

Selectivity and sensitivity figures are so good as to be almost unbelievable. And this is a fitting component companion for SANSUI's AU-7700, a star at the top of the line of SANSUI's integrated amplifiers.

55 Watts per channel minimum RMS into 8 Ohm load from 20Hz to 20KHz with no more than 0.1% total harmonic distortion.

Separate or together-power houses both of them. Hear either the TU-7700 and/or the AU-7700 at your nearest SANSUI franchised dealer and be sure to pick up your free copy of "The Sounds of SANSUI" or write directly to us.

SANSUI ELECTRONICS CORP.

Woodside, New York 11377 • Gardenia, California 90247 • SANSUI ELECTRIC CO. LTD. Tokyo, Japan SANSUI AUDIO EUROPE S.A. Antwerp, Belgium • ELECTRONIC DISTRIBUTORS (Canada) B.C.



Lectrotech TO-60 Dual-Trace Oscilloscope

THE WIDEBAND, DUAL-TRACE, TRIGGERED sweep oscilloscope is fast becoming THE instrument in the service industry. Lectrotech's new TO-60 is a very good example of this kind of instrument. It's a 5-inch, all solid-state scope, with a bandwidth of DC to 15 MHz on both channels. It has all of the desirable features such as independent triggering of either channel. You can trigger the displays on the channel-A or channel-B input signal. You can also select channel-A trigger



Circle 102 on reader service card

displaying channel-A and channel-B chopped, up to 100 kHz or channel-A and channel-B alternate sweep above 100

kHz. "A and B added," displaying the sum of the two signals, is available too.

Both vertical amplifiers are DC coupled. You can select either AC or DC coupling, or ground the input of the unused channel to prevent interference. In the ground position of the channel-A switch, the sweep becomes free-running so that you can check the operation.

The triggering is solid. You can use automatic trigger on many waveforms. The trigger operates on the highest average point in the pattern. For TV work, switch in the TV Sync selector. This must be used with the amplitude or triglevel control. This gives you triggering on the vertical sync at the lower frequencies, switching automatically to the horizontal sync on the higher ones. A slope selector allows triggering on either positive or negative peaks. To get the best results from this, it must be set to match the polarity of the sync in the TV signal being viewed. The horizontal sweep switch is calibrated from 0.2 second-perdivision up to 0.5 microsecond-per-div. The speed can be varied with the center knob, if desired. For calibrated sweep, it's turned full clockwise. Pulling out on this knob gives you a 5-times multiplication of the sweep, equal to a speed of 0.1 microsecond-per-division on the highest frequency.

With the growing use of digital circuitry in entertainment electronics, we'll need scopes with a very fast rise-time, to read the sharp pulses used in frequency-dividers, etc. Here is one place where the (continued on page 24)



Here's the ONLY plier/wrench you can work with one hand. Finger-squeeze the handles to lock the jaws onto the work. With the same hand, finger-trip the release lever to open the jaws. Simple, fast, efficient. Only TOG-L-LOK has the release lever where it belongs: OUTSIDE the lower handle. Easy to get at. No chance of pinched fingers. No snap sting when you trip the lever (it's plastic cushion-coated). Ask your tool supplier for TOG-L-LOK, straight or curved jaws. Meet the Family. Send for our free Catalog.

CHANNELLOCK, INC. . Meadville, Pennsylvania 16335



No. 950 Tog-L-Lok Plier/Wrench





The latest improvement in picture tubes.

Our labels.



If you can say what you want, you've got it. That's our simple new labeling system.

The labels tell you what's inside, in simple, everyday language.

We've kept our standard color coding: red for all-new; blue for new screen and gun; green for new gun.

And inside, there's the same great tubes you've always had from Sylvania.

Trust Sylvania to make life easier. See your Sylvania distributor.

We're helping you make it.

GIE SYLVANIA

Electronics servicing is no mystery when

The 20 books offered on these two pages are representative of the vast amount of clear and authoritative electronic servicing help available from Sams. They can help you understand and efficiently service almost every electronic application. Look them over-and use the coupon to broaden your skills.

TELEVISION **E**

Here are the first three of an all-new series of specialized service guides by Stan Prentiss.

Developed by the Audel® Division of Howard W. Sams & Co., Inc., they are comprehensive directories of detailed servicing data and information for all 1974-75 models of the leading home-entertainment manufacturers. Each covers troubleshooting, schematics, replacement parts lists, and service tips, and includes specific circuit write-ups and identification of all integrated circuits used.




COLOR-TV SERVICING **GUIDE** (2nd Edition) by Robert G. Middleton

This guide uses color photos to show symptoms of circuit defects as they appear on the picture-tube screen. If the picture-tube screen. If the serviceman follows these pic-ture clues and uses proper troubleshooting methods, he can service sets correctly and in less time. Covers both tube and solid-state circuits. 112 pages, softbound.

No. 20990



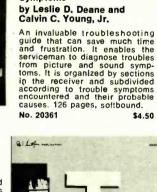

TV SERVICING GUIDE

Arranged by Trouble

Symptoms



COLOR-TV SERVICING MADE EASY (Volume 3) by Wayne Lemons and Carl Babcoke

This service guide is designed to help you service all makes and models of color tv. It covers general circuit descriptions; troubleshooting; high voltage regulators, including "tail-safe" circuits; and universal setup procedures; and has separate chapters devoted to specific manufacturers. 288 pages, softbound.

No. 20875



101 WAYS TO USE YOUR OSCILLOSCOPE by Robert G. Middleton

This book is an eyeopener to television servicemen and elec-tronics techniclans who have gotten in the habit of using an oscilloscope on only a limited number of tasks. It describes potential oscilloscope uses, from basic to involved and complex; includes demonstration photos of wavefarms and

demonstration photos of waveforms, and discusses likely defects when the waveform is abnormal. 192 pages, softbound. No. 20416

PHOTOFACT® GUIDE TO TV TROUBLES (2nd Edition) by the Howard W

Shows just what hapshows just what hap-pens to the picture-tube display when any com-ponent in the receiver becomes defective. All of the Guide's many pictures are actual phopictures are actual photos taken under simulated-defect conditions. By comparing them to the picture produced by a defective set, the components most likely to cause the trouble can be readily determined. 192 pages, softbound.

Sams Editorial Staff

No. 20521





you follow these informative guides.

HI-FI, TAPE & AMPLIFIER

TAPE RECORDER SERVICING GUIDE — by Robert G. Middleton.
Brings the technician up to date in serv-Brings the technician up to date in servicing a fast-growing field of home and auto tape cartridges, tape cassettes, and stereo tape players. While the basic electronic circuitry may be familiar to the radio and television serviceman, this guide also explains and shows how to service such unique tape recorder features as magnetic circuits and bias oscillators. 96 pages, softbound.

No. 20748

\$4.50

No. 20748

HI-FI STEREO HANDBOOK (4th Edition)—by William F. Boyce. A most valuable handbook on all kinds of sound equipment. It provides full coverage of the three major stages in hi-fi reproduction—the program-source equipment, preamplifier and amplifier sections, and the speaker system. Completely updated with information on the latest equipment, and technology. 400 circuits, systems, and technology. 400 pages, softbound. No. 20918 \$6.95

HI-FI STEREO SERVICING GUIDE (2nd Edition)-by Robert G. Middleton. Anyone servicing a-m tuners, fm tuners, stereo-multiplex units, and audio amplifiers can gain valuable service direction and assistance from this guide. It also covers hi-fi speaker installations, system evaluation, troubleshooting, and methods of verifying test equipment performance, 104 pages, softbound.

UNDERSTANDING IC OPERATION-AL AMPLIFIERS — by Roger Melen and Harry Garland, With the advent of semiconductor and microminiature elec-tronics, complete op amps on a single troncis, compete op arps on a single tiny chip of silicon now have many ap-plications. This book cavers the IC op amp exclusively, explaining how it works, how it is fabricated, how practical cir-cuits can be designed by using them, and how complete electronic circuits can be formed around op amp circuits. 128 pages, softbound. No. 20855 \$3.95

ELECTRIC GUITAR AMPLIFIER HANDBOOK (3rd Edition)—by Jack Darr. You no longer need hesitate to service an electric guitar amplifier. This informative guide relates the functions of all parts of the guitar to familiar electronic circuitry, and shows how to cor-rect all electronic malfunctions. The latest types of amplifier schematics, solidstate amplifiers, replacement transistors, and integrated circuits are all covered. 240 pages, softbound. No. 20848 \$7.95



SOLID STATE

SOLID-STATE SERVICING-by William Sloot. Explains semiconductor theory as it applies to servicing solid-state electronics, and covers the function of circuits used in home-entertainment electronic products. By enabling the reader to think of circuits in terms of the functions they perform, it promotes the development of service techniques applicable to all solid-state electronic functions, 160 pages, softbound. No. 20888

TTL COOKBOOK - by Donald E. Lancaster. Transistor-Transistor Logic has opened up a fantastic number of aphas opened up a fantastic number of applications for digital circuitry. It is not only better than traditional analog circuits, it is often cheaper. This timely book, by the author of the famous RTL Cookbook, explains what TTL is, how it works, and how to use it. 336 pages softbound. No. 21035

RTL COOKBOOK - by Donald E. RTL COORBOOK — by Donald E. Lancaster. The family of digital-logic integrated circuits called Resistor-Transistor Logic, or RTL, is used in applications ranging from simple switching through digital measuring circuits. This book explains how RTL ICs are used, how they work, and how to adapt them for the complex electronic systems in use

today. 240 pages, softbound. No. 20715

LINEAR IC PRINCIPLES, EXPERI-MENTS, AND PROJECTS—by Edward M. Noll. Introduces the principle of operation of the integrated circuit or operation or the integrated circuit. Reviews semiconductor theory and practical devices, and discusses common internal circuit arrangements and basic external circuitry. Covers differential and operational amplifiers; multipurpose and digital ICs; and linear IC use in commercial, Industrial, home, and test applica-tions. 384 pages, softbound. No. 21019 \$8.95

TRANSISTOR-TRANSISTOR LOGIC THANSISTOR-THANSISTOR LOGIC
—by George Flynn. An invaluable aid
to understanding the function and circuit
construction of logic devices. The book
discusses the digital families of which
TTL is a part, and covers the basic units
—the gate, the various basic circuits,
and the voltage and current requirements. Also covered are: flip-flops,
decoders, multiplexers, shift registers,
counters, TTL math, methods for determining Information priority and storage. counters, TTL math, methods for determining Information priority and storage, and how TTL, the dominant form of semi-conductor logic, works with other types of circuits and logic families. 176 pages, softbound. No. 20967



AUTOMOTIVE ELECTRONICS

AUTOMOTIVE ELECTRONICS
by Rudolf F. Graf and
George J. Whalen
This book divides the automobile electronic system into starting system, sensor instruments, and indicators. It then explains the operating characteristics of each system in great detail. Troubleshooting is covered in detail, along with the test instruments used. 320 nages softhound ELECTRONICS the automobile elecinstruments used. 320 pages, softbound

> STUDY GUIDE FOR CET EXAMINATIONS

EXAMINATIONS
by J. A. Wilson, CET and
Dick Glass, CET
You must pass a demanding 12-section
test and have at least four years of experience in electronic servicing before you
can become a Certified Electronics Technician (CET). This book presents a comprehensive review of the material covered
by the CET examination, and also serves
to help the reader pass a state or local
licensing exam. 282 pages, softbound.
No. 20834

	i
-	
Guide	
IONS	ĺ

8 4300 West Szild Street, India	napons, maia	110 40200
Order from your Electronics Parts I Howard W. Sams & Co., Inc.	Distributor, or	mail to
Send books checked at right. \$	Cod	de:
enclosed. Please include sales tax	21155	□ 21075
where applicable. Canadian prices	21165	□ 20855
slightly higher.	□ 21199	□ 20848
Send FREE 1975 Sams Catalog.	□ 20990	20888
	20361	21035
Name	□ 20416	□ 20715
Address	20875	21019
	□ 20521	20967
City	□ 20748	□ 20856
StateZip	□ 20918	□ 20834

HOWARD W. SAMS & CO., INC.

BUILD&TEST CIRCUITS AS FAST AS YOU THINK!

- POWER FOR THE PROFESSIONAL
- ECONOMY KITS FOR THE HOBBYIST
 A MODEL AND A PRICE FOR EVERYONE



PROTO BOARD 203

Breadboard Prototesting with 5 Volt,

1 AMP Regulated Power Supply included!

A total ready-to-use power breadboard prototest device with a built-in regulated, short-proof power supply. Just plug-in and start building! 2 extra floating 5-way binding posts for external signals. Self-contained with power switch indicator lamp and power fuse. 24-14 pin DIP capacity. Attractive two-tone quality case. All metal construction. 934"L x

6½"W x 2¾"H. 5 lbs. Order today!

Add \$2.50 shipping/handling

A modestly priced kit for the economy-minded experimenter . .

PROTO BOARD 100

A low cost, big 10 IC capacity breadboard kit with all the quality of QT sockets and the best of the Proto Board series . . . complete down to the last nut, boit and screw. Includes 2 QT-35\$ Sockets; 1 QT-358 Bus Strip; 2 5-way binding posts; 4 rubber feet; screws, nuts, bolts; and easy assembly instructions.

1995
Add \$1.50
shipping/handling.

PROTO-CLIP for Power-On, Hands-Off Signal Tracing. No more shorting leads. Costs less than . . .

^{\$}5

Bring tC leads from pc board for fast signal tracing and troubleshooting. Inject signals. Wire unused circuits into boards. Scope probes and test leads lock onto Dynagrip inset (see circle) for hands-off testing. Plastic construction eliminates springs, pivots. Non-corrosive nickel/silver contacts for simultaneous low resistance connections.

PC-14. 14-pin Proto Clip. \$4.50 ea.

PC-14, 14-pin Proto Clip, \$4.50 ea. PC-16, 16-pin Proto Clip, \$4.75 ea. Add 75¢ shipping/handling.

Order today off-the-shelf from CSC or local distributor. Charge: BAC, MC, AX. Write for free catalog. Free English/Metric Slide Rule with each order. Dealer inquiries invited.

Foreign Orders add 15%.

Patents Pending Made in USA
Prices subject to change

Box 1942, New Haven, CT 06509 • 203/624-3103

W. Coast Off.: Box 7809, S. Francisco, CA 94119 • 415/383-4207 Canada: Available thru Len Finkler Ltd., Ontarlo

Circle 14 on reader service card

EQUIPMENT REPORTS

(continued from page 20)

dual-trace scope is essential; the input and output signals can be displayed simultaneously, and the divider action checked with ease. In a divide-by-six stage, for example, you'll see one output pulse and 6 input pulses, and you know it's working properly. The TO-60 vertical amplifiers have a rise-time of only 23 nanoseconds, which is fine.

Two PR-10 probes are used with the TO-60. These are compact, rugged, and have a handy thumb-switch on the case. With this, you can change instantly from direct to low-capacitance without taking the probe off the test point. They're equipped with needle-point tips, to penetrate insulating coatings on PC boards, go through the insulation of wires, etc.

A PR-12 wideband demodulator probe is also available. Since the instrument I got was a pilot model, the final instruction manual wasn't ready yet. So, I don't know the exact spec's on the PR-12. I do know what it can do. For one thing, you can pull the IF cable from a tuner and read the demodulated TV signal right off the end of it! This must be at least a voltage-doubler type probe, for I got a reading indicating a level of 4 volts P-P on a horizontal-frequency signal! On the IF output of a Tuner-Subber, I got a display indicating 2 volts P-P. The waveforms were clean as a whistle; fine sharp (continued on page 30)

SHOCK spotter



RCA's WT-540A tells you fast how much AC leakage there is in appliances, power tools. TV sets and more. For safety's sake, order one today for only \$33.00' from any one of the more than 1,000 RCA Distributors worldwide. Or write: RCA Electronic Instruments Headquarters, Harrison, N.J. 07029.

Optional price

REAL Electronic Instruments

Circle 15 on reader service card

MITS

BUILDING YOUR OWN COMPUTER WON'T BE A PIECE OF CAKE.

(But, we'll make it a rewarding experience.)

Chances are you won't be able to assemble the Altair 8800 Computer in an hour or two. But, that's only because the Altair is a real, full-blown computer. It's not a demonstration kit.

The Altair Computer is fast, powerful, and flexible. Its basic instruction cycle time is 2 microseconds. It can directly address 256 input and 256 output devices and up to 65,000 words of memory.

Thanks to buss orientation and wide selection of interface cards the *Altair 8800* requires almost no design changes to connect with most external devices. Up to 15 additional cards can be added inside the main case.

The Altair Computer kit is about as difficult to assemble as a desktop calculator. If you can handle a soldering iron and follow simple instructions, you can build a computer.

You see, at MITS, we want your experience with our kits to be rewarding. That's why we take such pains to write an accurate, straight-forward assembly manual. One that you follow step-by-step. (We leave nothing to the imagination.)

Some electronic kit companies are experts at cutting the corners. They promise you the sky and deliver a box full of surplus parts and a few pages of faded instructions run off on their copying machine.

We're experts at **not** cutting the corners. Our *Altair Computer* has been designed for both the hobby and the industrial market. It has to be constructed of the finest, quality parts. And it is.

That's why we give you double-sided boards, gold-plated connectors, a 10 Amp power supply (enough to power 15 additional cards), toggle switches and an all aluminum case complete with sub-panel and detachable dress panel.

That's why we give you three manuals (Assembly, Operator's and Trouble-shooting) in a hard-cover, 3 ring binder plus an Assembly Hints manual.

Buy our computer and we'll automatically make you a member of the Altair User's Group. You'll have access to a whole range of custom software designed exclusively for the Altair 8800.

We're quite serious about making computer power available to you at a price you can afford.

BASIC ALTAIR AND OPTIONS

The basic Altair 8800 Computer includes the CPU, front panel control board, front panel lights and switches, power supply and expander board (with room for 3 extra cards) all enclosed in a handsome, aluminum case.

Options now available include 4K dynamic memory cards, 1K static memory cards, parallel I/O cards, three serial I/O cards (TTL, RS232, and TTY), octal to binary computer terminal, 32 character alpha-numeric display terminal, ASCII keyboard, audio tape interface, floppy disc system, and expander cards.



PRICES: Altair Computer Kit with complete assembly instructions \$439.00
Assembled Altair Computer \$621.00
1,000 word static memory cards \$176.00 kit
& \$209.00 assembled.
4,000 word dynamic memory card \$264.00 kit
& \$338.00 assembled.

NOTE: Altair Computers come with complete documentation and operating instructions. Altair customers receive software and general computer information through free membership to the Altair User's Club. Software now available includes a resident assembler. System monitor, text editor, and Basic compiler.

Prices and specifications subject to change without notice. Warranty: 90 days on parts for kits and 90 days on parts and labor for assembled units.


MITS/6328 Linn N.E., Albuquerque, N.M., 87108, 505/265-7553

MAIL T	HIS COUPON TODAY!
☐ Enclosed is a Check for	or \$
□ or Bank Americard #	
□ or Master Charge	#
Credit Card Expiration D	ate
□ ALTAIR 8800 □ Kit	□ Assembled
Include \$8.00 for Postage and	Handling
NAME	
ADDRESS	
City	State & Zip
	Albuquerque, New Mexico 87108

From CIE — Cleveland Institute of Electronics

learn by doing!

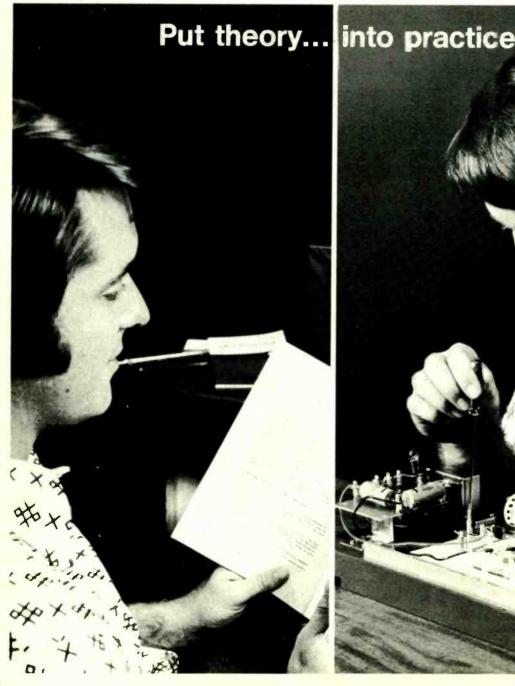Perform more than 200 exciting experiments with CIE's fascinating ELECTRONICS LABORATORY PROGRAM!





² Free

If you want more money... and an exciting career... send for these Free Books about opportunities in Electronics. **Just mail** attached postcard.

Books

YES! Send me your FREE books TODAY.

- I am especially interested in the following career(s): Industrial Electronics
- ☐ Electronics Technician FCC License Preparation
- T Electronics Engineering
- ☐ Color TV Maintenance Mobile Communications
- Other

PRINT NAME

ADDRESS

APT.

CITY STATE

AGE

Check box for G.I. Bill information.

ZIP

RE-54

☐ Serviceman ∀eteran

Cleveland Institute of Electronics, inc.

1776 East 17th Street, Cleveland, Ohio 44114 Accredited Member National Home Study Council

Job opportunities in Electronics. The value of an FCC License. Beginning, intermediate and advanced course outlines. Free.

electronics No obligation to you.

BADIO BLUCTROWICS

Cleveland, Ohio 44114 1776 East 17th Street Sleveland Institute Electronics, Inc.

BUSINE No postage stamp necessary if mailed in the United States S S D EP LY MAIL

Cleveland, Ohio Permit No. 8685 FIRST CLASS

Postage will be paid by-

Attention Veterans and Servicemen:

All CIE career courses are approved under the G.I. Bill for


educationa benefits




Fill in the postpaid reply card and mail ... TODAY. If card he been removed, send your narr and address to: Cleveland Institute of Electronics, Inc., 1776 East 17th Street. Cleveland, Ohio 44114.



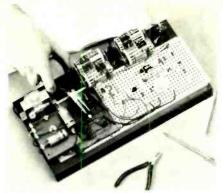
You get your own Experimental Electronics Laboratory... work with components comparable to those used by industry!



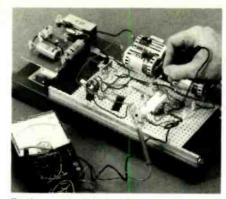With CIE's Experimental Electronics Laboratory, you'll perform actual experiments and become adept at handing components. This valuable "hands on" experience helps you learn the "how" as well as the "why."



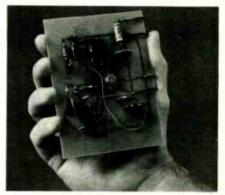Testing and troubleshooting are an important part of your learning experience. Included in your laboratory is a precision "multimeter" to diagnose electrical and electronic troubles quickly and accurately.



Modern space-age components like this IC (integrated circuit) are professional quality and can be used again and again in many of your projects. Lesson by lesson, piece by piece your knowledge grows!

Prepare now for a rewarding career in Electronics . . . the Science of the Seventies.

Electronics miracles are changing today's world with breathtaking speed.

This growth in electronics technology has generated a need for electronics technicians trained in theory and practice to build the products, maintain them, and troubleshoot them during the Seventies and beyond.

Don't just wait for something to "happen" in your present job. Get ready now for a career you'll really enjoy . . . with the opportunity for a good income and the chance for advancement.

Practical experience with experiments

"Hands on" experience helps to reinforce basic theory. When you learn by doing, you discover the "how" as well as the "why." You'll find out for yourself the right way as well as the wrong way to use electronic components. How to construct your own circuits, to discover trouble spots and learn how to fix them.

CIE offers a number of laboratory courses where you learn Electronics by "doing it yourself." You work with your own hands on electronics components and lab equipment. This combination of "head and hands" learning locks in your understanding of the crucial principles you'll use on the job in your new career.

And you do it all at home, in your spare, time, at your best study pace. CIE's outstanding lessons allow you to progress step by step. An instructional technique time-tested for over 40 years of specialized electronics independent home-study training.

Importance of an FCC License and our Warranty

If you want to work in commercial broadcasting . . . television or AM or FM broadcasting . . . as a broadcast engineer, federal law requires you to have a First Class Radiotelephone License. Or if you plan to operate or to maintain mobile two-way communications systems, microwave relay stations or radar and signaling devices, a Second Class FCC License is required.

Even if you aren't planning a career which involves radio transmission of any kind, an FCC License is valuable to have as Government certification of certain technical skills. It's a job credential recognized by some employers as evidence that you really know your stuff.

To get an FCC License, you must pass a licensing exam administered by the government. And we are confident you can successfully earn your license, if you're willing to put forth an effort, because the vast majority of CIE students have. In fact, based on continuing surveys, close to 9 out of 10 CIE graduates passed their FCC exams!

That's why we can offer this Warranty: when you successfully complete any CIE career course which includes FCC License preparation, you will be able to pass the Government FCC Examination for the License for which the course prepared you or you will be entitled to a full refund of an amount equal to the cash price of tuition for CIE's Course No. 3, "First Class FCC License," in effect at the time you enrolled. This warranty is good from the date you enroll until the last date allowed for completion of your course.

That's it! We warrant that you will get the License you trained for.

You'll have attractive job opportunities

There have already been many exciting developments and breakthroughs in Electronics and some people might assume there will be no new frontiers...no new worlds to conquer. Not so.

Electronics is still growing. In nearly every one of the new and exciting fields of the Seventies you find electronics

skills and knowledge in demand. Computers and data processing. Air traffic control. Medical technology. Pollution control. Broadcasting and communications. Once you have the solid technical background you need, you can go after the career field you want ... work for a big corporation, a small company, or even go into business for yourself.

Yes, Electronics can be the door to a whole new world of career opportunities for you. And CIE training can be your key.

Send for FREE school catalog

Discover the opportunities open to people with electronics training. Learn how CIE career courses can help you build new skills and knowledge and prepare you for a meaningful, rewarding career. We have courses for the beginner, for the hobbyist, for the electronics technician, and for the electronics engineer. Whether you are just starting out in Electronics or are a college-trained engineer in need of updating (or anywhere in between), CIE has a course designed to fit your background. experience, and future goals.

Send today for our FREE school catalog and complete career information. For your convenience, we will try to have a representative call to assist in course selection. Mail reply card or coupon to CIE . . . or write: Cleveland Institute of Electronics, Inc., 1776 East 17th Street, Cleveland, Ohio 44114. Do it TODAY.

All CIE career courses are approved for educational benefits under the G.I. Bill. If you are a veteran or in service now, check box for G.I. Bill information.

CIE Cleveland Inst	Street, Cleveland, (ober National Home Study Co	Ohio 44114
Please send me your FREE school cata	log and career informa	ation package
I am especially interested in:		
☐ Electronics Technician	☐ Industrial Elec	tronics
FCC License Preparation	☐ Electronics Eng	gineering
□ Color TV Maintenance	Other	
☐ Mobile Communications		
Print Name	A	ge
Address	A	pt.
City	State Z	ip
Check box for G.I. Bill information. Vet	eran 🔲 On Active Duty	RE-5

(continued from page 24)


horizontal sync, etc. This could be a fast and easy way of checking tuners or for signal-tracing through the IF stages in either tube or solid-state sets.

The TO-60 can also be used for sweepalignment work. It has an additional horizontal amplifier that is switched on when the time-per-division switch is in the external position. This additional amplifier is necessary for vectorscope applications. It has a sensitivity of 0.5 volt-per-division, and a bandwidth of 0.5-MHz. This can be controlled by the variable control on the time-per-division switch. Vectorscope tests can be made

from the front panel, using either channel-A or channel-B and the external input to the horizontal amplifier. Z-axis modulation can also be used from a front panel jack. If external trigger signals are needed, there is a jack for this. Sync can be chosen from internal, external or line frequencies by a 3-position switch. A 1.0 volt P-P square wave test jack is provided, for checking compensation of the low-capacitance probes, or for quick-checking the voltage calibration of the vertical amplifiers. Incident-ally, the TV selector can be used with other types of signals, for better triggering; it acts as a low-pass filter to keep out undesired components. The triggering is solid; the TO-60 will lock in on a waveform that is only one division high.

The TO-60 is a solidly-built instrument, in a very compact case. It's only 13 inches deep, so it takes up very little room on the bench. Controls are arranged for easy operation. It should find application in almost any area of electronics work, from entertainment to industrial. It sells for \$489.50.

General Electric "GE-MOV" Varistor

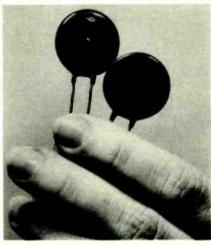

TRANSIENTS HAVE NEVER BEEN POPULAR with electronics men. Now, with everything full of solid-state devices, they are even less popular. Transistors and IC's hate voltage transients with a purple pas-(continued on page 32)



- Eliminates trial and error lead bending.
- · Fast, exact, thumbwheel adjusted spacing hetween hends.
- "Breezes" through special units and short production runs.
- Increases production 50%. Pays for itself within a week.

Ask for MODEL N-300 for 1/4 watt and larger components; MODEL N-400 for micro-components.







Immediate delivery from . . .

HARWIL COMPANY

903 Colorado Avenue, Santa Monica phone: 213 / 394-4710 California 90401

INTERNATIONAL FREQUENCY FM 2400CH METER for testing mobile transmitters and receivers ■ Tests Predetermined Frequencies 25 to 1000 MHz

- Extended Range Covers 950 MHz Band
- Pin Diode Attenuator for Full Range Coverage as Signal Generator
- Measures FM Deviation



The FM-2400CH with its extended

MHz. The range covers 25 to 1000 frequencies can be those of the radio frequency channels of operation and/or the intermediate frequencies of the receiver between 5 MHz and 40 MHz.

Frequency Stability: ± .0005% from +50° to +104°F. Frequency stability with built-in thermometer and temperature corrected charts: ± .00025% from +25° to +125° (.000125% special

450 MHz crystals available). Self-contained in small portable case. Complete solid state circuitry. Rechargeable batteries.

....\$595.00 FM-2400CH (meter only) RF crystals (with temperature correction) ... 24.00 ea. RF crystals (less temperature correction).catalog price IF crystals

Write for catalog!



This automatic transistor tester works in-circuit when others can't.



520 Dynapeak (TM) \$150.00

Now you can avoid wasting time unsoldering good transistors that test bad in-circuit and good out-of-circuit because of erroneous testing. With B&K-Precision Dynapeak^(TM) Transistor Tester you can quickly determine whether a transistor is good or bad in circuits where automatic transistor testers have never worked before. Low impedance circuits are becoming more and more common in TV, audio and industrial controls—and the Dynapeak^(TM) pulse testing system will let you test transistors in these circuits which have shunt impedances as low as 10 ohms or 50 mfd!

COMPLETE TEST IN 9 SECONDS:


You connect the leads any way, turn the switch and the rest is automatic: Pulsating audio tone and a light automatically indicate a good device. PNP or NPN determination and Germanium or Silicon identification are automatically indicated by LED's. Leakage tests require no charts, because leakage current limits are shown on the meter face for the different kinds of devices.

Actual transistor action is determined in-circuit not just junction or diode characteristics; you know you're making a valid test.

Write for our full color brochure explaining why the Dynapeak^(TM) transistor testing system will stop time-wasting diagnostic errors and speed solid state servicing.

EVEN WORKS IN CIRCUITS LIKE THIS!

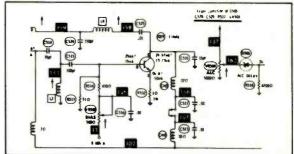If you don't have a 520 Dynapeak(TM), you'll have to unsolder the transistor to test it in this circuit.





1801 W. Belle Plaine Avenue • Chicago, IL 60613

CUT WIRE & CABLE INSTALLATION COSTS

... without cutting into insulation!

SAFE! Grooved Guide positions wire for proper staple envelopment! Grooved Driving Blade stops staple at right depth of penetration to prevent cutting into wire or cable insulation!





3/8", 7/16" and 9/16" leg lengths.

T-18 and T-25 staples also available in Monel and with beige, brown and ivory finish at extra cost.



Arrow Automatic Staple Guns save 70% in time and effort on every type of wire or cable fastening job. Arrow staples are specially designed with divergent-pointed legs for easier driving and rosin-coated for greater holding power! All-steel working parts are your assurance of maximum long-life service and trouble-free performance.

Ask your Electrical Supply Dealer or write for further details.

Saddle Brook, New Jersey 07663

"Pioneers and Pacesetters
For Almost A Half Century"

EQUIPMENT REPORTS

(continued from page 30)

sion. It only takes 50 milliseconds or so to damage them badly. So, a fast-acting transient suppressor is a welcome thing.

G-E has come up with a new version. This is a specially compounded varistor, made with metal oxide and a new method, using "grain boundaries" in the polycrystalline material. (A varistor, Clyde, is a special resistor; its resistance drops when the voltage increases.) These new devices are called GE-MOV® varistors. They're made in many different sizes and voltage ratings, but the most commonly used operates on standard 120 VAC and is readily available from authorized distributors of G-E replacement semiconductors.

GE-MOV varistors are described as symmetrical voltage-dependent resistors which act like back-to-back Zener diodes. They can be used to replace previous types such as Zeners, silicon-carbide varistors, selenium thyrectors, and the old original R-C networks; the first suppressor used.

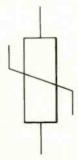


Fig. 1

The basic action of these things is like an open set of relay contacts, connected right across the circuit to be protected. When a transient comes along, they "close" very rapidly. This is a "crowbar" effect that shorts out the transient spike, Then, after the transient passes, the "relay" opens again. This is possible because of the very high resistance of the devices when not conducting. They also have very low capacitance, 300-400 pF. So, you may find them used in the circuitry of amplifier stages, etc., in the same place as bypass capacitors.


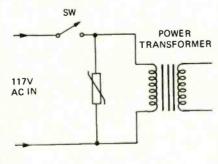


Fig. 2

Figure 1 shows the symbol adopted for the MOV. Figure 2 shows a common use for it; right across the AC line input, to a TV, stereo, etc. Here, it will absorb sharp line transients, from lightning or (continued on page 34)

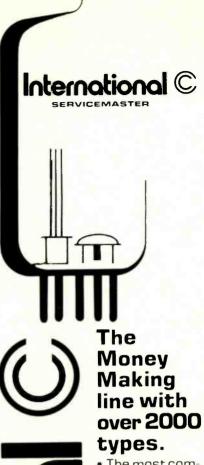

- The most complete range of domestic and foreign consumer and industrial receiving tubes in the world. Classic and antique, too.
 - Complete range of replacement Semiconductors.
 - Discounted to give you higher profit margins
 - Quality your customers can depend on.

For the name of your local distributor call (516) 293-1500 Or write,

International Components Corporation

105 Maxess Road, Melville, New York 11746 See us at NewCombooths #D20 & D22 May 5-8

Circle 22 on reader service card

EMA

Talk about **Microwave Tube Replacements** and whose name comes up first?

Amperex.


What gave Amperex such leadership in Microwaves?

Radar Magnetrons and Klystrons, Microwave Oven Magnetrons,

UHF Klystrons, Industrial Magnetrons, Silicon Rectifier Stacks, TR Tubes,

Pulse Modulator Tetrodes.

Thyratrons and SCR's,

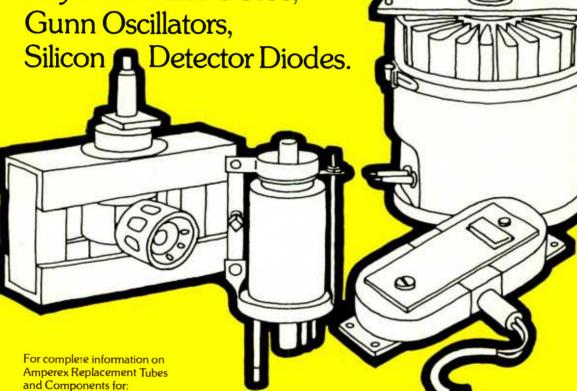

- Microwave Ovens & Commercial Radar Equipment
- Radio & TV Broadcast Equipment
- Industrial Power Supplies & Oscillators
- RF Communications Transmitters
- · Scientific Instruments...

contact Bob Norris. Distributor Sales Operation. Amperex Electronic Corporation, Hicksville, New York 11802 Telephone: 516-931-6210.

A NORTH AMERICAN PHILIPS COMPANY

□ AUTD ELECTRONICS SIMPLIFIED — Complete Guide to Service/Repair of Automotive Electronic Systems. Extremely thorough coverage of auto electronics includes EVER yis circuit to be found in a car including circuit descriptions and servicing procedures for ignition and charging, safety and security systems, radios/tape players, antiskid systems, emission control and performance devices, on-board computers, test Instruments, etc. 256 p. 207 ill. \$5,55 paper; \$8,95 hard. ☐ THE COMPLETE AUTO ELECTRIC HANDROOK — A Practical Guide to

☐ THE COMPLETE AUTO ELECTRIC MANUBUUM — A Practical Guide to Diagnosis & Repair. A self-teaching course that tells how the car's electrical system works and how to repair it when it doesn't. Begins where factory manuals leave off. Covers all the electrical theory you will ever need to know. A large number of time-saving analysis and servicing techniques are included in the coverage on lest instruments. AC and DC charging systems, suto accessories, and electrical repair. 210 p. 139 iil. \$5.95 paper; \$8.95

USING ELECTRONIC TESTERS FOR AUTOMOTIVE TUNE-UP. Provides complete info and operating instructions on all electronic devices for auto tune-up. Completely covers the subject from basics through sophisticated devices. Stresses interpretation of test results and shows how to save time by using electronic devices for auto tuneup. 252 p. 226 iil \$4.95 pager. \$7.95 hard.

THE COMPLETE HANDBOOK OF AUTOMOTIVE ENGINES & SYSTEMS.

THE COMPLETE HANDBOOK OF AUTOMOTIVE ENGINES & SYSTEMS.
Perhaps the most understandable book ever published on the subject.
It's a practical, profusely illustrated guide to what happens under the
hood of the modern auto. Crystal clear discussions unravel the mysteries of all types of engines, fuel systems, electrical fundamentals,
ignition systems, batteries, starters, afternators, lights, emission control systems, test equipment, air conditioning, etc. 252 p. 239 Ill. \$5.95
nater. \$8.85 hard.

paper; 30.39 and 0.

MOCENT QUIDE TO AUTO TUNEUP & EMISSION CONTROL SERVICING. This comprehensive guide to tuneup and emission-control servicing will pave the way to top performance of any late model car and will
help owners get the best gas mileage of which any car is capable. A
must for drivers concerned about gas shortages. 240 p. 135 ill. \$5.95

THE COMPLETE FM 2-WAY RADIO HANOBOOK. Covers police and fireman's radio, taxicab and business radio, boaters' radio, and activens band. Explains all types of systems and stations. FCC technical terms, types of emissions and lechnical standards. Covers every lacet of the field including the technical aspects of radio theory and 2-way servicing 294 p. 111 iil. \$6,95 paper, \$9,95 hard. ■ AUTO STEREO SERVICE & INSTALLATION, Indispensable one-stop source of Into (including how to get rid of interference) for all types of auto stereo equipment ... plus detalled installation procedures for FM radios, 8-track cartridge units and cassette players. Also covers the mechanical aspects — dial cord and lamp replacement, replacing controls, demagnetizing tape splicing, etc. 252 p., 245 iil. \$5.95 paper; \$8.85 hard.

36.35 indiv. REPAIR HOME & AUTO AIR CONDITIONERS. Clearly explains how air conditioners work, emphasizing the practical knowledge necessary to competently maintain and repair all types of units used in homes, offices, and modern cars. 208 p., 100 iii. \$4.95 paper; \$7.95 hard.

DMOBILE RADIO MANOBOOK. All the fine points of the two-way business, from estimating communications range to maintaining modern equipment — in a single volume. 192 p., 175 ill. \$4.95 paper; \$7.95

TRIOUGH CONTROL OF THE CONTROL OF TH

COMMERCIAL FCC LICENSE MANDBOOK. Unique study guide and reference manual, combining theory and applications with up-to-date questions and answers for 1st, 2nd, and 3rd Class Radiotelephone license exams plus broadcast and radar endorsements. Detailed answers to questions on any subject you may be asked when you take your exam, plus sample questions on each element (with answers). 444. p., 150 ill. \$5.95 paper. \$9.95 had.

PICTORIAL GUIDE TO CB RADIO INSTALLATION: & REPAIR. Step-by-

PICTORIAL GUIDE TO CR RADIO INSTALLATION & REPAIR. Step-bystep approach to setting up a 2-way radio in home or car — the simple techniques outlined are equally applicable to commercial and ham systems. Complete guide to the proper installation, checkout, and maintenance of all types of modern transceivers and antenans, both mobile and fixed. Also covers mobile equipment mounting and tuneup. 256 p. ill 54.95 paper: \$7.35 hard.

SENTICING CASETTE AND CARRINGE TAPENTERS. THE CHEST STITLE AND THE CHES

NO-RISK COUPON - MAIL ENTIRE AD

TAB BOOKS, Blue Ridge Summit, Pa. 17214

Send me book paper).	s checked a	bove (specif	y hard or
☐ I enclose \$_☐ Please invoi ☐ Send FREE 4	ce on 10-day	FREE trial.	
Name		Phone _	
Company			
Address			
City	State	Zi	p
SAVE POSTAGE	by remittin	g with order.	RF-55

EQUIPMENT REPORTS

(continued from page 32)

sudden switching on or off of heavy loads. If a direct hit from lightning gets it, that's it. Nothing will stop that. The type used for this purpose is listed as GE 750. G-E makes a wide variety of MOV varistors in addition to the type 750. These range from 26 to 1,000 volts. Their numbering system is different. Take the V130LA 10A. The "130" in the type number stands for the operating voltage; it can be connected directly across an AC line at not more than 130 volts rms. The "10" farther along means that it can absorb 10 joules of energy without damage.

For other uses, they might be connected to the bottom of the load on a transistor amplifier stage, as in Fig. 3.

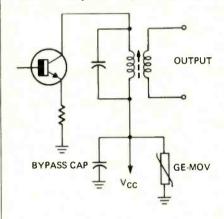


Fig. 3

If the collector voltage used was 30 volts, a Type V33ZA5 would do. This goes into conduction at 33 volts DC, and will handle a 5-joule transient. These low-voltage types have a very fast reaction, less than one nanosecond! There will be quite a few other, similar places where the protective characteristics would be very handy indeed.

In industrial electronics and control work, one of these will do wonders in suppressing arcs across relay contacts, as in Fig. 4. A copy of an actual oscillogram of unprotected and protected relay contact arcing is seen in Fig. 5. The arcing (shaded area to the left) looks like about 2-3 kV peak! In the second picture, you can see that there is no arcing at all! All you have to know for this is the energy absorbed per pulse, and the maximum supply voltage. This can be calculated from the formula $E = \frac{1}{2} \times$ $L \times I^2$ Where L is the coil inductance and I is the peak coil current. This will give you the voltage rating and the energy in joules for the last significant figure in the type number. These are available in many voltages from the 33volt series up to 1,000 volts at 160 joules.

For the present these are sold only to original equipment manufacturers and industrial users in bulk quantities.

Application and installation data is packaged with the GE-750 device. This is the one intended for use by service technicians in the home entertainment

(continued on page 61)

... here Today!

"IGNITION OF THE FUTURE" ALLISON "OPTO-ELECTRIC"

☆ The BEST...the ULTIMATE...
of ALL the Ignition Systems!




Never wears out or needs any Maintenance!



GAS SAVINGS

...it gives you Maximum Power with continuous PEAK PERFORMANCE

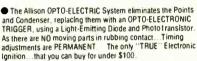...while reducing Maintenance and Operating Costs!



● Gives 40-Times more Timing Accuracy than ANY system using "Mechanical" Breaker-Points! UNLIMITED RPM! "Electronically-Controlled" DWELL automatically supplies HIGHEST Performance at both Low and High speeds. Spark strength does not fall off at high RPM. POSITIVE SPARK helps eliminate "Misfire" for faster acceleration and improved Engine Performance! Smoother running (No timing fluctuation as with Magnetic Units). Easier Starting under any condition! Sparkplugs LAST 3 to 10-Times LONGER.

All SOLID-STATE Components. UNAFFECTED By Temperature Moisture, or Vibration! Highest grade materials Guarantee you solid, Dependable Performance.

★ Perfect Timing and Dwell never change.

Pays for itself! Eliminates ignition Tune-Ups forever! "INFINITE LIFE"... Once installed... Never needs replacing.

● PERFECT TIMING INCREASES Engine Efficiency and Gas Mileage. SAVES Precious Fuel! Allison gives you MAXIMUM Engine Efficiency 100% of the time... and that's the name of the game for BETTER Gas Mileage and Economy.



QUICK AND EASY INSTALLATION

If you want the BEST, and SAVE! This is IT!

ORDER with CONFIDENCE...
 SATISFACTION GUARANTEED!
 1-YEAR FACTORY WARRANTY.

Only \$4995 COMPLETE.

As you can see, you're not laking any chances at all...Send your Order Today.

State Make, Year, Engine Size. (Calif. Res. add Tax).

(So New...It's Sold ONLY FROM FACTORY DIRECT).

You may use your MASTER CHARGE or BANKAMERICARD.
Send us (1) Your Number. (2) Interbank No., (3) Exp. Date.

Before buying any other Type Ignition system...

Send Postcard for our FREE BROCHURE.

★ If you have already installed a C-D Ignition system, Modernize and Increase Its Efficiency... CONVERT YOUR "C-D" UNIT TO BREAKERLESS! Opto-Electric "TRIGGER UNIT"...Only '34.95



 Our BEST Salesmen are the owners and users of our ALLISON System!

ALLISON
AUTOMOTIVE COMPANY
1269- L. East EDNA PL., COVINA, CAL, 91722

61)

Circle 24 on reader service card







TeleMatic Sub-Tuners save hours of guesswork by rapidly pinpointing trouble in the antenna, UHF or VHF Tuners, or I.F. Stages. Powered by popular transistor batteries.

COMBO-DEAL STD 440

Send literature and name of my distributor.

Telematic 2245 Pitkin Ave., Brooklyn, N.Y. 11207

SPECIAL ONLY	\$49.95	CITYSTATEZIP
SAVE (On deal)	12.00	O.T.V
REGULAR PRICE	\$61.95	ADDRESS
KTU-745 UHF/SUB	16.95	NAME
KT-730 VHF/SUB	\$45.00	


A ac wa	40 KV DUAL RANGE Probe Current & Voltage Reading For Today And Tomorrow! MODEL \$2995 651 RANGE NO. 1: 40,000 VOLTS DC
4	Ser d literature and name of my distributor. Polaris New York 2862 FULTON STREET BROOKLYN, N.Y. 11207 Name Address City State
	ZipState



The Hottest New Product Since The Calculator...

- Makes every set on your floor a remote control model
- Universal— Attaches to any set in minutes
- ☐ Changes channel instantly and fine tunes
- ☐ Turns set on/off

 - ☐ Silent push-button varactor— diode tuning— 12 channels
- Amplifies signal and eliminates direct pick up ghosts
- ☐ For homes, apartments, bars, hotels/motels, schools, hospitals and nursing homes.





a GENERAL INSTRUMENT company

HEADQUARTERS & EASTERN OFFICE 200 Witmer Rd., Horsham, Penna. 19044, (215) 674-4800 SOUTHERN OFFICE 1 Perimeter Place, Suite 101, Atlanta, Georgia 30339, (404) 432-3102 WESTERN OFFICE 1255 Veterans Blvd., Redwood City, Calif. 94063, (415) 365-5050 MIDWESTERN OFFICE 1334 Atlantic Street, North Kansas City, Mc. 64116, (816) 842-1555



A new family of laboratory power supplies from the

Heath Company. They offer a variety of voltage ranges, automatic
output monitoring and adjustment of output. There's one for every bench

by LARRY STECKLER EDITOR

FOR MANY YEARS BENCH POWER SUPPLIES WERE NOT VERY important to the technicians, experimenters and hobbyists that used them. Just about anything that would deliver 6 or 12 volts DC with enough amperage to power a car radio would meet most needs. But today it's a very different world. The modern power supply must provide precise voltages, be well regulated, offer constant currents and provide accurate monitoring and metering of the voltages and currents that it delivers.

The reason for this "revolution" is the semiconductor—the transistor, integrated circuit, or other solid-state device that is not very tolerant of extreme voltage and current changes. As we well know, even a small change in a DC supply voltage can play havoc with a solid-state circuit.

To fill the needs of the modern electronics bench, the Heath Company has introduced eight great new power

supply kits. There are four pairs of fraternal twins, and are shown in the photo at the top of this page and on this month's front cover.

When we at Radio-Electronics previewed these kits, just a few months ago, we learned that they included several rather special features. They provide either constant current or constant voltage. A remote-sensing connection permits precise compensation for voltage drop at the load when the power supplies are used with long leads. The digital readout units have a two-decade auto-ranging to provide high resolution for low voltage and current settings. And the units are fully protected against shorted outputs or even the chance of open remote sensing leads.

A bit further on we'll take a closer look at each of these features, but for now, lets stop for just a moment and scan the specifications listed in Tables I, II and III.

Now that we've taken a moment to look at the specifications of this family of power supplies, let's take a quick run-down on how they work. All eight power supplies are pretty much alike, except for their output ratings. So we can talk about one unit and, in effect, be describing all of them at the same time.

The Heathkit Laboratory Power Supplies all consist of six basic circuits—a power source (the power transformer block in Fig. 1), the output amplifier current source (Q101 in Fig. 2), the output amplifier (Q1, Q2, Q3, Q4 in Fig. 1), the voltage regulator, and the display circuit (a block diagram of the digital display circuit is shown in Fig. 2).

Because of its size and complexity

TABLE I — SPECIFICATIONS (TYPICAL FOR MODEL IP2731)

LOAD REGULATION

Voltage $\pm 0.05\% + 1$ mV Current $\pm 0.10\% + 1$ mA

LINE REGULATION

Voltage ±0.05% + 1mV Current ±0.10% + 1mA

RIPPLE & NOISE

Voltage — 1mV RMS, 0.03% of rated output, peak-to-peak.

READOUT ACCURACY

Voltage: Analog — ±3% of rated output.

Digital — ±0.5% of reading ±1 count using lab standard. ±1% of reading ±1 count using built-in calibrator.

Current: Analog — ±3% of rated output.

Digital — ±1% of reading +4 counts using lab standard.
±1.5% of reading +4 counts

STABILITY AT OUTPUT

Voltage $\pm (0.01\% + 1 \text{mV/hr} \\ \text{Current} \\ \pm (0.05\% + 1 \text{mA})/\text{hr}$

LOAD TRANSIENT RECOVERY

using built-in calibrator.

Output voltage within 0.05% + 1mV within 50 μ s for rated output current change or 5A, whichever is less.

OUTPUT VOLTAGE OVERSHOOT

None, using power switch only.

OPERATING MODES

Constant voltage, constant current, auto-series, auto-parallel.

PROGRAMMING MODE

Voltage — A—Zero to rated output with 0 to 5.0V applied; B-Zero to rated output with 0 to 5000-ohm external resistor.

Current—Zero to rated output with applied voltage to 1.0 volt/amp.

Frequency response — DC to 100 Hz, 2 dB.

Transient response — 0.1 ms for low current to high current change. 1.0 ms for high current to low current change.

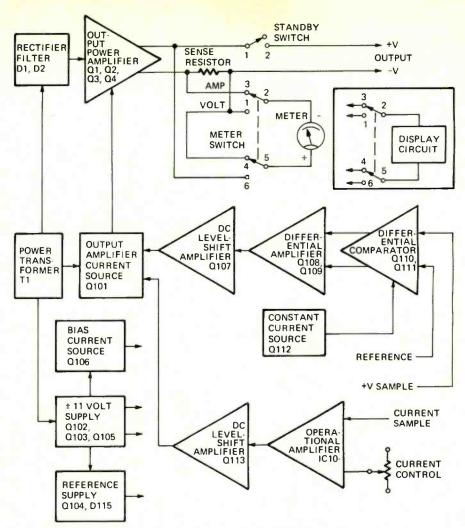


FIG. 1—BLOCK DIAGRAM OF THE COMPLETE power supply. When shown in this way it doesn't appear as elaborate as it really is.

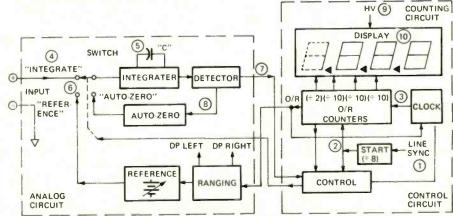


FIG. 2—BLOCK DIAGRAM OF THE DIGITAL READOUT CIRCUIT. Follow this diagram along with Fig. 3 when looking at how it works.

we are unable to present the full schematic of the power supply here, so for the purposes of this discussion we will use the block diagrams of Fig. 1 and Fig. 2.

The power source

The power transformer (T1) has a dual primary that can be switch selected to permit 120 VAC or 240 VAC, 50/60 Hz operation. The secondaries, of course, supply the AC

voltages to power the various circuits in the unit.

One secondary is connected to the output amplifier current source. In addition, it supplies voltage to the meter lamps. Another secondary feeds a rectifier filter network to produce a 75 VAC output (for the 60-volt supply). Still another secondary is used to produce +20 and -20 VDC sources for the +11 VDC and -11 VDC supplies. This voltage is fed through a



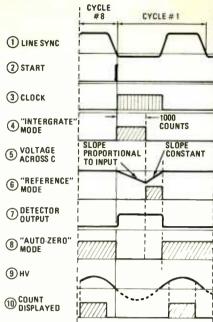


FIG. 3—WAVEFORMS IN THE digital readout circuit. Use along with Fig. 2.

constant-current network so the regulated 11 volts is available for use in the current and voltage regulators.

Output amplifier current source

This circuit supplies drive current to the output amplifier. Its constantcurrent output is controlled by the current and voltage regulators to maintain the desired power supply output level.

Output amplifier

The output amplifier supplies the output power. The power transistors in this circuit are connected in parallel. Power from the output amplifier current source is amplified and coupled to the base of the power transistors. This current determines the voltage as well as the maximum current passed by the power transistors.

WITH ITS COVER REMOVED you can take a look inside the power supply.

The output amplifier current source operates at a higher DC voltage level than the output amplifier. This insures that up to six power supplies can operate in parallel with complete voltage and current control.

Voltage regulator

The voltage regulator maintains the output voltage level and consists of three primary circuits — a differential comparator that compares a sample of the output voltage to a reference voltage, a differential amplifier to amplify the error signal from the comparator, and a DC level-shift amplifier to sink current from the output amplifier current source.

Current regulator


Current limiting is controlled by two basic circuits—an operational amplifier that compares a reference voltage to the voltage drop across the current sense resistor, and a DC level-shift amplifier to sink current from the output amplifier current source.

As the output current exceeds the level set by the current control, the comparator generates a positive voltage that is coupled to the base of the

DC level shift amplifier (Q113). This increases the base current, which in turn increases the collector current and sinks current from the output amplifier current source. A lower current level to the output amplifier will limit the current the output amplifier can supply.

Display circuit

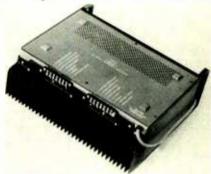As we mentioned earlier there are two display options—an analog meter or a digital readout. In either case the



MASSIVE HEAT SINKS cover the entire rear panel of the power supply.

meter switch is used to read either voltage or current as desired. The analog circuit uses a conventional meter. The digital circuit is a bit more elaborate. A block diagram of this circuit is in Fig. 2. In the description that follows you will want to refer to this block diagram along with Fig. 3, which shows the functional waveforms.

The line sync signal (waveform 1) is derived from the line voltage frequency ot 50 or 60 Hz and is applied to the start circuit, a divide-by-8 counter. After 8 cycles, the start circuit generates a 1-\(\mu\)s pulse (waveform 2). This pulse resets the display counters to 9000, and resets the control circuit for a measurement cycle. When reset, the control circuit starts the clock (waveform 3) and switches the analog circuit to the "integrate" mode (waveform 4).

As the counters count the clock pulses, the integrator output develops a voltage on timing capacitor C (waveform 5), at a rate that is proportional to the positive input voltage (that is the charge voltage versus time increases with higher input voltage levels).

Integration continues as the counters count from 9000 to 9999. The next clock pulse "sets" the counters to 0000, which tells the control circuit to switch the analog circuit to the "reference" mode (waveform 6).

While the counters continue to count up from 0000, a negative reference voltage causes the voltage across timing capacitor C to ramp back toward zero. The ramp slope is constant, because of the fixed reference voltage.

TABLE II — ANALOG POWER SUPPLIES

	Max. Rat	ed Output	Readout Range		
Model	Voltage	Current	Voltage	Current	
IP/SP-2700	60 V	1.5 A	0 to 60	0 to 1.5	
IP/SP-2710	30 V	3.0 A	0 to 30	0 to 3.0	
IP/SP-2720	15 V	5.0 A	0 to 15	0 to 5.0	
IP/SP-2730	7.5 V	10.0 A	0 to 7.5	0 to 10.0	

TABLE III — DIGITAL POWER SUPPLIES

	Max. Rat	ed Output	Readout R	ange
Model	Voltage	Current	Voltage	Current
			0.00 to 19.99)	
IP/SP-2701	60 V	1.5 A	20.0 to 60.00 *	.000 to 1.500
			0.00 to 19.99)	.000 to 1.999)
IP/SP-2711	30 V	3.0 A	20.0 to 30.0 } *	2.00 to 3.00
				.000 to 1.999)
IP/SP-2721	15 V	5.0 A	0.00 to 15.00	2.00 to 5.00 }
				.000 to 1.999)
IP/SP-2731	7.5 V	10.0 A	0.00 to 7.50	2.00 to 10.00
				* 4 4

*Autoranged

When the detector senses a zero voltage across C, its output goes low (waveform 7) and signals the control circuit to turn off the clock. The count stored in the counters represents the input voltage. When the control circuit turns off the clock, it also switches the analog circuit to the "auto zero" mode (waveform 8). This lets the integrator and detector stabilize to prepare for a new measurement cycle.

During the preceding operations, the high voltage to the display tubes was low, as represented by the dotted portion of waveform 9, and the display was not lit. As the high voltage goes more positive, a level is reached where the gas in the tubes ionizes waveform 10) and the seven-segment digits display the count stored in the counters. Each of the next seven positive portions of the high voltage signal relight the display tubes.

If, during the "reference" mode of operation, the count exceeds 1999, the overrange (O/R) output of the counters turns the clock off and triggers the ranging circuit. This increased the reference voltage level by a factor of 10, and shifts the decimal point (DP) position. Thus, on the next measurement cycle, the timing capacitor will discharge 10 times more quickly and the count will be displayed with one decade less resolution.

Figure 4 shows a front panel diagram of one of the digital power supplies. Note that all front-panel control functions are clearly illustrated. These are the same for all four digital readout units.

Figure 5 shows the rear panel of the power supply. Each output terminal is identified to give you a better idea of the capabilities of these units.

Summary

There is little doubt that if you have been looking for a first-rate power supply for your bench at a practical price these new Heath units are what you have been looking for.

The manuals for assembly are just as easy to follow and as complete in detail as we have grown to expect from Heath. And while I haven't built one of these power supplies yet, I'm confident it will be as straightforward a job as all of the previous Heathkits.

Finally, all major circuitry is on individual circuit boards and wiring harnesses are provided to reduce complicated point-to-point wiring to a minimum.

Prices for all four analog units are \$169.95 and the digital units are \$219.95 in kit form. All eight are also available completely assembled at somewhat higher prices. I'm sure you'll be wanting to add one of these power supplies to your bench. R-E

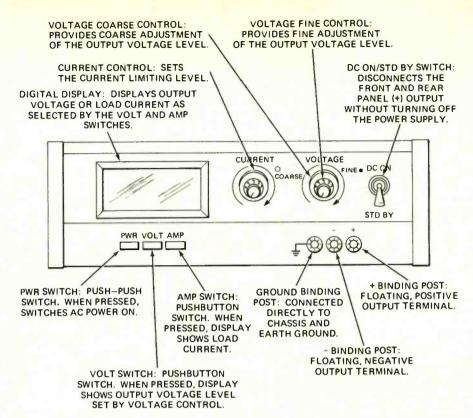


FIG. 4—FRONT PANEL CONTROLS ARE IDENTIFIED in this diagram and their functions are detailed. The units are easy to use yet versatile.

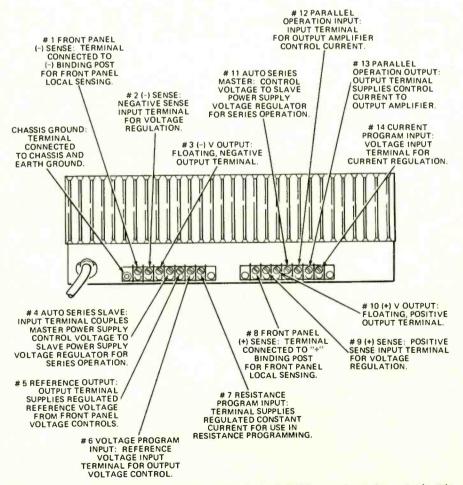


FIG. 5—OUTPUT TERMINALS OF THE LAB POWER SUPPLY are shown here. Again this helps give a picture of what the units can do.



by BERT WOLF*

AUTHOR shown using a field-strength meter.

HIGH INTEREST RATES AND GALLOPING inflation are beginning to put single family houses out of reach of most Americans. Therefore, more and more Americans are turning to apartment houses, condominiums and trailer parks, all of which require Master Antenna TV (MATV) systems. MATV systems are also used in hotels, motels, schools, hospitals, municipal buildings, broadcast studios, public buildings and even private homes. Based on growth in all of these areas, the MATV business is expected to increase considerably.

All of these new and old MATV systems require servicing. Most MATV systems are sold with service for the first year included in the price. After that, the building owner either takes out a service policy or takes his chances with system failure.

Many MATV system contractors are too busy to pay much attention to system servicing. Thus, there is a void which independent technicians can fill.

Servicing MATV systems is a lot easier than servicing color TV sets. It does require some specialized equipment, a working knowledge of MATV system theory and some legwork, but MATV service can be very lucrative.

Required tools

Aside from hand tools, you need

*Manager, Jerrold DSD Division

only four pieces of equipment to service MATV systems successfully:

- 1. Field strength meter.
- 2. Portable TV set
- 3. Variable attenuator
- 4. Ohmmeter

The field strength meter should be battery operated, compact and portable. It should read directly in dBmV as well as microvolts and cover the entire VHF, FM and UHF spectrum. Accuracy should be ±3 dB or better.

The TV set should also be compact, portable and battery operated. The ohmmeter need not be particularly accurate, but it too should be portable.

The attenuator should be a switch type, with type F connectors for fast connect/disconnect.

Troubleshooting new systems

Troubleshooting MATV systems can be divided into two distinct kinds of problems: new systems and old systems.

Let's look at new systems first. Assume that the system has been designed in accordance with good MATV practice. It's still quite possible that you will encounter some difficulties in getting good picture quality on every channel throughout the system. Here

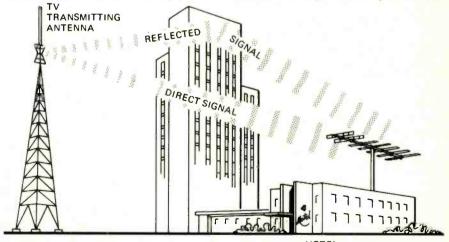


FIG. 1—GHOSTS are usually caused by an antenna simultaneously receiving a direct signal and a reflected signal.

are some of the problems you are most likely to encounter.

Ghosts and smears

The most common cause of ghosts is reflected signals, as shown in Fig. 1. Many people feel that ghosts are usually caused by mountains or tall structures many miles away, but the trouble is usually a lot closer to home. For example, a water tower 400 feet behind an antenna can cause a ghost displaced about 1/4 inch to the right on a 21-inch screen. (Reflected path is actually 800 feet longer than direct path.) However, a mountain 5 miles to the side of the antenna would cause a ghost displaced 8 inches to the right on a 21-inch screen. Ghosts displaced more than an inch to the right are not as noticeable as closely spaced ghosts.

In large cities, it is possible for the reflected signal to reach the set stronger than the direct signal. This relatively rare occurrence produces a ghost displaced to the left, known as a leading ghost.

Multiple ghosts and smears are generally caused by standing waves within the MATV system. When a TV signal sees a mismatch, part of the signal is reflected back into the line. Reflected signals bouncing around in the system usually arrive at the set in evenly spaced waves. If the signals travel through a lot of coaxial cable before they reach the set, they are displaced significantly to the right of the main image. If they travel less than 200 feet extra, they are seen as smears rather than separate images.

If you did a signal survey before installing the system, you should have detected the problem of ghosts picked up by the antenna. The solution to this problem is usually bigger, better antennas, carefully oriented. In severe cases, you may have to use horizontally stacked antennas, as shown in Fig. 2. Horizontal stacking results in signal cancellation of specific angles, depending on the distance between the two antennas. You have to find a distance

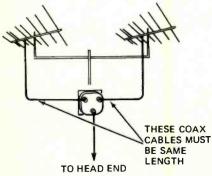


FIG. 2—HORIZONTAL STACKING of two antennas, both directed at the transmitting antenna, can reduce the reception of reflected signals. The horizontal spacing between the two antennas is important.

that will cancel signals from the direction of the ghost. This is best done by trial and error. Use a compass and a map to aim both antennas directly at the TV transmitter. Connect a TV set directly to the combined signal from the two antennas and watch it while the antennas are moved closer and further apart. The spacing is right when the ghost disappears.

Multiple ghosts in a new system are generally caused by poor installation, which in turn causes a mismatch. A single strand of cable shield at a connector can cause a short. A loose connector or a center conductor that was knicked and broken can cause an open. A fast way to isolate this kind of problem is to insert a 6 dB attenuator into different parts of the system. The attenuator will improve the match, thus making the trouble diminish or disappear. Once you've located the problem, it is generally easy to correct.

increase the signal level to each tapoff by using a more powerful headend amplifier.

Interference

Low-frequency transmission such as Citizens band at 27 MHz, amateur radio (Ham) at 28 MHz or 50 MHz, Police or Fire at 29 to 50 MHz, can cause severe problems in MATV systems—anything from weak beats to wiggly lines that make the pictures on one or more channels impossible to view.

Since these interference sources are intermittent, it is easy to overlook them at the time of the signal survey. To identify the offending signal, tune your field strength meter for a maximum reading on the interferring frequency and then plug in the earphone. What you hear should enable you to pinpoint the source of the problem.

To eliminate the interference, use a sub-channel/TV splitter between the

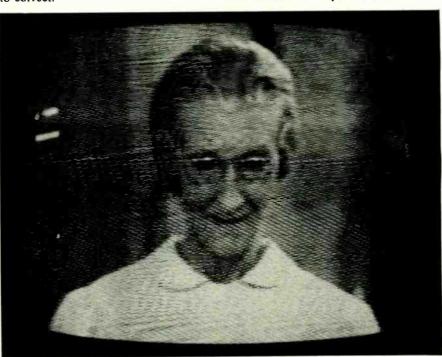


FIG. 3—HERRINGBONE PATTERN usually caused by FM interference.

Some systems use wall tap-offs with 300 ohm outputs. This eliminates the need for set-matching transformers, but it means that there is a length of twinlead between the wall and the TV set. This twinlead acts as an antenna, picking up signals direct from the transmitter and causing ghosts. In weak signal areas, direct pick-up is no problem, but within about 20 miles of a transmitter, ghosting can be severe. The best way to solve this problem is to avoid it by using 75ohm output taps if you have the slightest qualms about direct pickup. If you encounter this problem in an existing system, the only solution is to antenna and the first amplifier in the system. The splitter siphons off all frequencies below 54 MHz, keeping them out of the amplifier.

FM interference

FM interference is a problem in many areas. It usually cause a herringbone pattern such as that shown in Fig. 3. If the head-end uses single-channel amplifiers, FM interference will usually be confiined to Channel 6, though once in a while it can also affect Channel 5. In a broadband system, FM interference can cause interference on Channel 6, but it may also show up on some other low-band

channel, a high-band channel or several channels

To eliminate FM interference, you can use either a single frequency tunable trap or an FM band rejection filter. Tunable traps can give you up to 40 dB or more of signal attenuation, but they tend to drift. Band rejection filters give you only about 20 dB of attenuation, but they are drift free. Generally, it's best to use a band rejection filter if it will do the job. If not, use an FM trap, but detune it slightly to reduce attenuation to about 30 dB. This will give you a wider notch to compensate for drift. Whether you use a trap or a filter, be sure to insert it before the first amplifier in the system.

Electrical interference

Electrical interference usually shows up on the TV screen as thin bands of noise ("snow") across the picture. The bands may roll up or down or stay in place.

Electrical interference is caused by defective equipment which arcs, generating interference across the entire RF frequency spectrum. You are more likely to see the interference on low-band antennas, however, because the signal strength of electrical interference decreases with frequency. UHF, in fact, is seldom bothered by this type of interference.

If the interference is continuous, the problem probably lies with the power company. Somewhere in the vicinity there is a loose C-clamp or Kearney connector, a cracked insulator, an arcing transformer or some other type of poor connection.

These problems are not easy to solve. Try calling the power company. Sometimes they are very cooperative and locate the fault quickly. If they are not, you'll have to try to pinpoint the trouble source for them. Use a high-gain antenna and a fieldstrength meter to get an idea of the direction of the interference. Rotate the antenna till you get a maximum reading on the interfering signal. Relay this information to the power company. As a last resort, try driving toward the interference with your AM radio tuned to the noise between stations. If you can narrow the area down to a block or two, the power company will probably do the rest.

Intermittent electrical interference is usually caused by defective brushes on some electrical motor. If the interference occurs at regular time intervals, it's probably some unit that turns itself on and off periodically, like a furnace or an air conditioner. An irregular time pattern indicates a machine that requires an operator, such as a vacuum cleaner or an electrical


drill.

Using the clues at hand and a little detective work, you should be able to track the culprit down eventually. Once you do, the owner of the machine is usually glad to replace the worn motor brushes.

Ignition noise

Automobile and truck ignition noise generally shows up on the TV screen as bright, broken streaks across the picture. Ignition noise is usually more a problem on home systems using twinlead than MATV systems using coaxial cable. However, ignition interference can show up on some sets in some MATV systems.

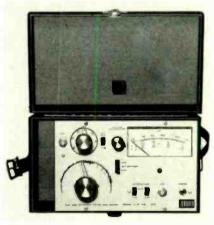The key to eliminating ignition problems is to increase the signal-tonoise ratio. There is no way you can
decrease the amount of noise generated by passing vehicles or to increase the amount of signal transmitted from the TV station. But you
can increase signal pickup by using
high gain antennas—vertically stacked,
if necessary. Vertical stacking gives



JERROLD MODEL AIM-719 signal-strength meter.

you almost 3 dB of gain and decreases noise pick-up by increasing directivity.

You can maintain a high signal-tonoise ratio by designing for more than 0 dBmV per outlet. In the case of an existing system with heavy ignition interference, try substituting an amplifier with more output and more gain.

Ribbon lead-in (300-ohm) between wall tap-offs and sets can pick up ignition noise as well as direct signals. It may be necessary to replace the tap with a 75-ohm output unit and take coax directly to the back of the set. This solution is not practical for a whole system, but if only a few tenants at the ends of the trunk lines complain, the tap-offs in their apartments can be replaced.

Converter interference

In many MATV systems, UHF

channels are converted to unused VHF channels. The advantage is lower distribution system losses, especially important in very large systems. However, converters can cause interference that looks a lot like HAM, CB or FM interference. The heart of every converter is a local oscillator. The oscillator frequency is set to beat with the incoming UHF signal so the difference is the desired VHF signal. For example, a channel 14 (470 MHz) to Channel 6 (82 MHz) converter generates a local oscillator frequency of 388 MHz (470 -82 = 388).

The best UHF to VHF converters are crystal-controlled for stability, but some are not. Even a crystal-controlled converter can cause problems. The output of the converter is usually a multiple of the fundamental oscillator frequency. Intermediate frequencies can beat with other frequencies in the system and cause interference. It's very hard to calculate all possible beat combinations, especially if more than one converter is involved. Your best bet is to get the recommendations of the manufacturer before you order specific converters. This will avoid most problems.

If you suspect converter interference in an existing system, it is easy to isolate. Simply unplug the converter and look at the pictures on the other channels. Once you know a converter is causing problems, try physically isolating it and putting it into a separate radiation proof housing. Also, reduce output levels if necessary to balance signals. This may do the trick.

Beats similar to converter interference can also be caused by modulators. The cure is the same—balance signals and isolate the modulator.

Overload

Too much signal can cause as many problems as too little signal. Overload problems occur only in active equipment such as preamplifiers, amplifiers and TV sets.

Broadband amplifiers and preamplifier overload usually results in cross-modulation. This appears on the screen as "windshield wiper" effect—bars sweeping across the picture.

Single-channel amplifiers, on the other hand, go into sync compression. Sync signals are carried on the blackerthan-black portion of the TV signal—the points of highest power. Nonlinearity in amplifier gain affects the highest power points first, compressing them somewhat. Sync compression starts with tearing, usually at the top of the TV picture. It causes the vertical hold controls to be very critical. In extreme cases of sync compression, the picture may break up completely.

(continued on page 69)



As an NTS student you'll acquire the know-how that comes with first-hand training on NTS professional equipment. Equipment you'll build and keep. Our courses include equipment like the NTS/Heath Digital GR-2000 Solid State color TV with first-ever features like silent varactor diode tuning; digital channel selection, (with optional digital clock), and big 315 sq. in. ultra-rectangular screen.

Also pictured above are other units — 5" solid state oscilloscope, vector monitor scope, solid-state stereo AM-FM receiver with twin speakers, digital multimeter, and more. It's the kind of better equipment that gets you better equipped for the electronics industry.

This electronic gear is not only designed for training; it's field-type — like you'll meet on the job, or when you're making service calls. And with NTS easy-to-read, profusely illustrated lessons you learn the theory behind these tools of the trade.

Choose from 12 NTS courses covering a wide range of fields in electronics, each complete with equipment, lessons, and manuals to make your training more practical and interesting.

Compare our training; compare our lower tuition. We employ no salesmen, pay no commissions. You receive all home-study information by mail only. All Kits, lessons, and experiments are described in tull color. Most liberal refund policy and cancella-



5" OSCILLOSCOPE

clip coupon if card is missing.

MULTIMETER TRANSCEIVER & POWER SUPPLY tion privileges spelled out. Make your own comparisons, your own decision. Mail card today, or

SOLID-STATE 2-METER FM

NO OBLIGATION. NO SALESMAN WILL CALL

DIGITAL

APPROVED FOR VETERAN TRAINING

Get facts on new 2-year extension

TECHNICAL SCHOOLS

TECHNICAL-TRADE TRAINING SINCE 1905 Resident and Home-Study Schools 4000 So. Figueroa St., Los Angeles, Calif. 90037

NATIONAL TECHNICAL SCHOOLS 4000 South Figueroa St., Los Angele Please send FREE Color Catalog an NO OBLIGATION. NO SALESMAN V	d Sample Lesson.
Color TV Servicing B & W TV and Radio Servicing Electronic Communications FCC License Course	Electronics Technology Computer Electronics Basic Electronics Audio Electronics Servicing
NAME	AGE
ADDRESS	APT #
CITY	STATE
Please fill in Zip Code for fast servic Check if interested in G.I. B Check if interested ONLY in	

SOLID-STATE POCKET RADIO

SIGNAL GENERATOR

20 easy-to-build COSMOS burglar alarms - part 2

Here are a few accessories that can be added to the basic alarm circuits presented last month. The options you add are entirely up to you.

by R. M. MARSTON

IN PART ONE OF THIS SERIES, FIVE basic burglar alarm projects were presented. Those basic alarm circuits were built around COSMOS logic and are very effective. This month we describe several options that can be added to the basic alarm circuits to make them even more effective.

The three circuits of Projects 3 to 5 act as excellent burglar alarm systems in their own rights. Their capabilities can be considerably expanded, however, by adding on a few simple electronic accessories, as shown in the following section.

Alarm system accessories

A problem with all burglar alarm systems is that of leaving or entering the house via a protected door once the system has been set into the STANDBY mode. A simple way around the problem is to fit a key-operated bypass switch to the outside of the door, so that the doors sensor switch can be temporarily disabled by the authorized key holder.

In this case, the proceedure for leavthe house is to first open the door and disable its sensor via the key switch, then re-enter the house and set the alarm to STANDBY, then leave the house again and close the door and re-enable its sensor via the key switch. The proceedure for re-entering the house without sounding the alarm is to simply disable the door sensor via the key-switch, then enter the house and turn the alarm system off.

Most of the tedium of this proceedure can be eliminated by equipping the alarm system with an exit-delay facility, which automatically disables the door sensor for a pre-set period after the main alarm system is switched to STANDBY. This facility enables the owner to simply switch the alarm system to STANDBY and then leave the house without sounding the alarm, but it is still necessary for the owner to manually disable the door sensor switch on re-entry if entry is to be made without sounding the

If required, even this re-entry proceedure can be eliminated by equipping the alarm system with a combined exit-delay and entry-delay facility. This facility ensures that the alarm will not sound until a pre-set time after the door sensor is initially activated by the entry action, thus giving the owner time to enter the house and turn off or reset the alarm system before the alarm actually sounds.

Practical exit-delay facility and exitand-entry-delay facility circuits are shown in Projects 6 and 7. These facilities can readily be added to any of the main alarm system circuits shown in

Projects 3 through 5.


The exit-delay facility of Project 6 uses three gates of a CD4001AE IC. Door sensor switch S7 can be of either the n.o. or n.c. types, and is connected in such a way that the input to pin 1 of gate A is at the positive supply voltage when the door is closed, and is at ground potential when the door is open. Gate A is wired as a simple NOR gate, which gives a low output when either input is high, and timedelay network C1-R3 is connected to the pin 2 input of the gate via R4. When power is first applied to the circuit, capacitor C1 is fully discharged, so pin 2 is effectively shorted to the positive supply line via R4, and the output of the gate is at ground potential, independent of the state of the door sensor switch. After a delay determined by C1 and R3 (roughly 0.5 seconds per #F of C1) the pin 2 voltage decays to such a value that the gate is influenced by the state of the door sensor switch. If the door is closed at this point, the gate output remains low, but if the door is open the output goes high.

The output of gate A is taken directly to pin 8 of gate B, which is also connected as a NOR gate. The main section of the alarm system sensor circuitry is taken to pin 9 of gate B in such a way that this pin is effectively grounded under normal conditions. The output of gate B is inverted by gate C, which thus gives an output that is normally low. This output is passed on directly to pin 2 of IC1 in the main alarm circuit.


Thus, the action of the Project 6 circuit is such that all sensor switches except S7 are enabled as soon as S1 is set to the STANDBY position, and S7 is disabled for a pre-set period. At the end of this period S7 is automatically enabled, and the alarm is able to respond to the actions of S7.

The combined exit-and-entry-delay facility circuit of Project 7 is similar to that of Project 6, except that R1 is increased to 10K, gate A is converted into a self-latching switch with the aid of D1 and gate D, and the output of gate A is fed to the input of gate B via time-delay network C2-R7 and R8. The circuit works as follows.

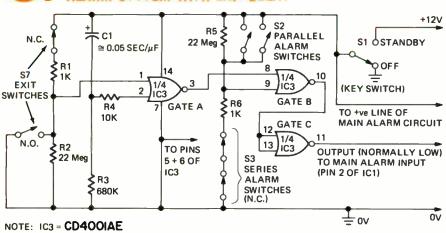When power is first applied to the circuit, all sensor switches are enabled except S7, which is disabled for a preset period via time-delay network C1-R3. The output of gate A is held in the low state under this condition. At the end of this pre-set period, S7 is auto-




ALARM SYSTEM WITH EXIT-AND-ENTRY DELAY

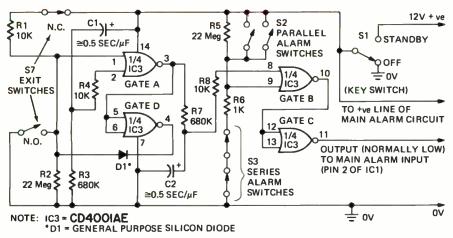

TRANSIENT SUPPRESSOR FOR SENSORS

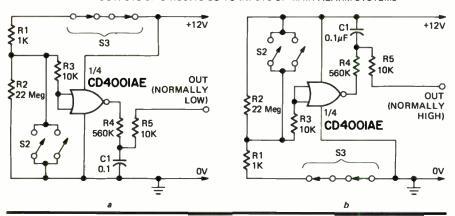NOTES: S2 = N.O. ALARM SWITCHES, IN PARALLEL
S3 = N.C. ALARM SWITCHES, IN SERIES
OUTPUTS OF CIRCUITS GO TO INPUTS OF MAIN ALARM SYSTEMS



matically enabled. If S7 is activated after the end of this pre-set period, the output of gate A immediately goes high, and is locked in this state by the action of diode D1 and gate D. This

high output voltage is applied to the input of gate B via time-delay network C2-R7, and after a pre-set delay (approximately equal to 0.5 seconds per μ F of C2) the voltage applied to gate

B rises to such a value that the alarm is activated.

The exit-delay facility or exit-andentry-delay facility circuit of Projects 6 or 7 can be added to the main alarm circuits of Projects 3 through 5 by simply removing the existing connections to pin 2 of IC1, by rewiring the existing alarm sensors into the Project 6 or 7 circuits, and by connecting the outputs of the Projects 6 or 7 circuits to pin 2 of IC1. Note that it is also necessary to wire the OFF pin of key-switch S1 to ground if these facilities are used, so as to provide a discharge path for the timing capacitors of these circuits.

All the burglar alarm circuits that we have looked at give reliable performance and are not prone to giving false alarms under normal circumstances. One exceptional circumstance which may initiate false alarms in any type of alarm system is that of the thunderstorm, where heavy electrical discharges may induce such large energy pulses into the alarm sensor wiring that the alarm is made to trigger falsely. In COS/MOS alarm systems, this possibility can be eliminated by simply interposing sensor-transientsuppressor circuits between the outputs of the main sensor networks and the inputs of the main alarm systems. Project 8 shows practical circuits of this type.


In the Project 8 circuit, a spare gate of a CD4001AE IC is wired as a simple inverter. The input of this gate is connected to the output of the main sensor network via limiting resistor R3. The output of the gate is connected to the input of the main alarm via R5 and a time-constant network formed by C1-R4. This network only passes signals that are applied to the gate input for periods greater than 50 ms. Consequently, the circuti rejects short-duration spurious pulses that are induced into the sensor wiring, but passes longer-duration signals that are generated by the activation of the sensor switches.

The Project 8-a circuit is intended for application where the sensor input to the main alarm system is required to be normally low, and the Project 8-b circuit is intended for use where the sensor input needs to be normally high. It should be noted that in practice these transient suppressor circuits are only likely to be needed in cases where the lengths of alarm sensor wiring exceeds fifty meters or so, since all the COS/MOS alarm circuits shown in this article have relatively low input impedances (1K or 10K ohms) when the sensor switches are in their normal states, and are thus not unduly sensitive to induced signals.


One final accessory that can be added to a burglar alarm system is an

intrusion recorder. This gadget is intended for use in auto-turn-off alarm systems only, and consists simply of a low-power sound generator that turns on and self-latches if an intrusion occurs, thus giving a continuous indication of the intrusion. The device can tell the owner that an intrusion has occurred during his absence from the house even though the main alarm has turned off and no signs of the intrusion are visible. A practical intrusion-recorder circuit is shown in Project 9.

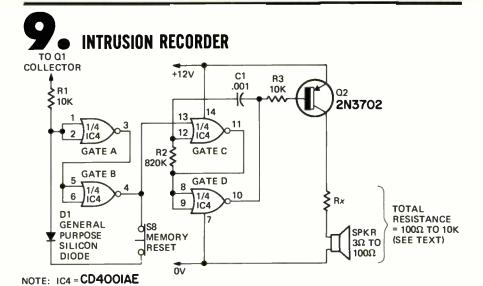The Project 9 circuit is permanently wired across the supply lines and its operation is quite simple. Gates C and D are connected as a gated 800-Hz oscillator which drives a speaker via Q2 and Rx. This oscillator is activated



COMPREHENSIVE ALARM SYSTEM

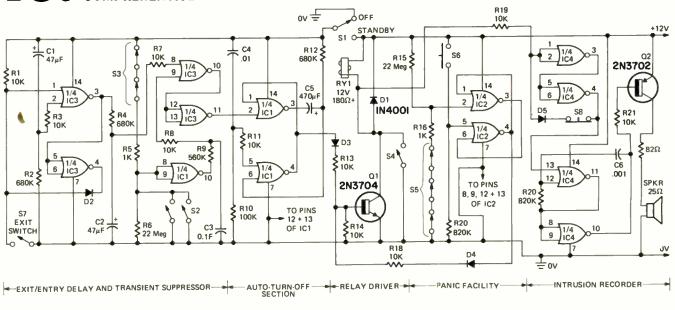

S1 = KEY SWITCH

S2 = N.O. ALARM SWITCHES, IN PARALLEL

S3 = N.C. ALARM SWITCHES, IN SERIES S4 = N.O. FIRE-SENSOR SWITCHES, IN PARALLEL

S5 = N.C. 'PANIC' BUTTONS, IN SERIES

S6 = N.O. 'RESET' BUTTON FOR PANIC ALARM

S7 = N.O. EXIT SWITCH S8 = N.C. MEMORY 'RESET' BUTTON, FOR RECORDER D2 - D5 = GENERAL-PURPOSE SILICON DIODES

IC1 - IC4 = CD400IAE

from the collector of transistor Q1 of the main alarm system via the selflatching switch formed by gates A and B. Normally, the collector voltage of transistor Q1 is high and the alarm relay is de-activated. Under this condition, the 800-Hz oscillator is inoperative and the recorder circuit consumes a quiescent current of only 1μA. If the main alarm system is activated, the relay is energized for a pre-set period and the collector of Q1 goes high. When this occurs, gates A and B of the recorder turn on and self-latch, activating the 800-Hz oscillator, thus causing an audible signal to be generated in the speaker. Once this audible signal has been initiated, it can

only be stopped by operating RESET switch S8.

The Project 9 circuit can be added to the auto-turn-off circuit of Project 4 or 5 by simply wiring it across the supply lines and connecting R1 to the collector of Q1. The speaker used in the circuit can have any impedance in the range 3-ohms to 100-ohms. The combined series value of Rx and the speaker impedance can be varied from a minimum value of 100-ohms up to about 10K-ohms, depending on the sound intensity that is required from the speaker. The maximum power output of the circuit is about 250-mW when R, has a value of zero and a 100-ohm speaker is used, and in this

case the circuit consumes roughly 50mA of current. Proportionately lower currents are consumed at lower power

A comprehensive alarm system

The alarm system accessory circuits of Projects 6 through 9 can be added to the basic alarm circuits of Projects 3 through 5 in any combination, depending on the requirements of the individual reader. The final alarm system can be as simple or as complex as the reader desires.

The comprehensive alarm system of Project 10 is shown as an example of how a number of different circuits can (continued on page 96)

IC UPDATE

ing CP the CMP

This article presents the basic rules and explains how to properly design around the operational amplifier.

by DON LANCASTER

BY NOW. EVERYONE SHOULD BE MORE OR less familiar with the "741," a low cost, internally compensated operational amplifier that has an incredible variety of DC and audio uses. But, very often, the 741 won't seem to work at all in the circuit, or perhaps not as well as you expected. This often happens when some use rule of the 741 is broken, or you make some basic assumption about the device that either isn't true or, at best, isn't very true.

For instance, what is the upper -3 dB cutoff frequency of a 741? Would you believe 3 hertz? Is the 741 as good as a plain old transistor as an amplifier at, say, 80 kHz? No, it isn't-but some op-amps are. Why do we have two inputs on an op-amp with apparently identical input circuitry, one marked + and one marked -, and yet the — one acts like a dead short and the + one acts like a very high input impedance? Because the feedback you are supposed to use creates a virtual ground. And why, sometimes, does the output of the op-amp sit at the positive or negative supply, and apparently refuse to budge no matter what you do? Probably because you forgot to use feedback or forgot to properly DC bias the inputs.

Yet, if you follow the simple rules, the 741 and its improved offspring are extremely well behaved, low cost, easy-to-use devices, good for a wide variety of DC and AC amplification problems, integrators, ramp generators, electronic music circuits, active filters, and very much more. So, let's take a rather basic look at the operational amplifier, and build up a set of rules of the game, particularly seeing what the 741 can and can't do. From there, we'll look at some devices and manufacturers, and then we'll end up with some applications.

What is an operational amplifier?

The name operational amplifier came from the theory of feedback amplifiers. If you build a DC coupled amplifier with very much more gain than you could possibly want, and then use very heavy negative feedback around the amplifier, the

performance of your circuit will depend almost entirely on what is doing the feeding back and what is doing the feeding in. Use resistors, and you have a simple and stable gain DC amplifier. The gain is determined by the resistor ratio only and is independent of the amplifier gain and power supply variations, provided that the op-amp has very much more gain than you need compared to the resistor ratio. For instance, with a 100K feedback resistor and a 10K input resistor, you can build a gain-of-ten amplifier, and if the frequency of operation gives you an opamp gain of at least 1000, the most gain error you can get from the amplifier or power supply is only around 1%, and progressively less with higher gains.

If you use a capacitor for feedback, the capacitor has to charge and discharge in response to input currents. This gives you an integrator, or a ramp generator. You can use it for waveform generation, triangles, sawtooth, etc., or to mathematically find the area-under-a-curve of a time waveform. It's also a low-pass filter. Add more rseistors and capacitors to your feedback and input networks, and you can build other high performance active filters—highpass. bandpass, band reject, equalizers, etc.

So, if we have enough excess gain in our op-amp, we end up performing an operation based on the ratio of feedback to input impedance. If the op-amp has enough extra gain at the frequency of operation, the operation you are trying to do depends only on stable resistors and capacitors. So, we start our rules:

- 1. An operational amplifier is almost always used with heavy feedback. If the feedback is negative, the ratio of the feedback impedance to the input impedance decides what the circuit is to do. and ...
- If an operational amplifier is going to work properly, it has to have much more open loop gain at the frequencies of interest than the circuit calls for.

We'll take a closer look at the 741 and its improved offspring in just a bit, but for now, the DC gain of a 741 is around 200,000. Now this is a bunch of gain. But the frequency response starts falling off immediately. For instance, you are already three decibels down from your DC value (the - 3 dB "cutoff frequency") at 3 hertz. Still, a gain of 140,000 or so is rather respectable, so we can use the beast at higher frequencies. Gain drops by 6 dB per octave (20 dB per decade) of frequency, so by 10 kHz you only have a gain of 100 left over, and by 100 kHz, only a gain of ten. So the 741 will be hard pressed to provide the excess gain we need for proper operation in the upper audio range. We'll find out about a much better (and somewhat more expensive) beast called the LM318 later on, that easily handles any audio problem. The point is that any operational amplifier falls off with frequency and you have a limit beyond which you can't get enough excess gain to keep the circuit working properly. The minimum excess gain you should ever work with is ten times the circuit needs at the maximum frequency of interest:

3. For non-precision applications, at least ten times the circuit gain must be available from the op-amp at the highest frequency of interest. Circuit gain limits for the 741 in a non-precision circuit is ten at 10 kHz and one at 100 kHz.


By "non-precision," we mean that a five or ten percent performance error won't hurt anything. For one percent precision, use one hundred times the gain, and so on. As long as you are *lower* in frequency than these limits, you get lots of *extra* gain and proportionately more precision.

An inside look

Figure 1 shows us how we can look at the operational amplifier as three distinct gain blocks, a differential input stage, a high gain intermediate stage, and a relatively high power, low impedance output stage. The differential input stage accepts input signals at very high impedances and with light loading. It also provides a way to take the difference between two input signals. This is the most critical stage of the

op-amp. The intermediate stage only has to provide lots of gain. The output stage has to provide drive power for the outside world, very important if circuit loading isn't going to change what gets fed back.

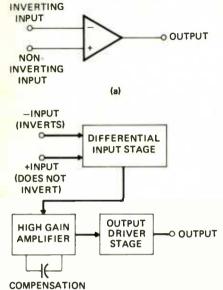There are two inputs to the differential input stage. One is called the *inverting* input and is normally shown as a (–). One is called the *non-inverting* input and is normally



(b)
FIG. 1—SCHEMATIC SYMBOL of the operational amplifier is shown in a. The three stages of the OP-AMP is shown in b.

mally shown as a (+). Note that this + and - has nothing to do with the supply lines. The positive supply is usually called V+; V = is the normal pin callout for the negative supply. There is no ground connection for the op-amp, and the circuit works best with split supplies of equal value, ranging from +5, -5 to +20, -20, with +15, -15 being the most common. Input signals must be limited to something halfway between the two supply levels, a specification called the common mode range. Thus a grounded signal reference is in the middle of the common mode range for a split supply amplifier. Another rule:

4. Operational amplifiers often work with a split power supply. With a split supply, input signals should be restricted to a range that is significantly less than the positive supply and significantly more than the negative supply. The common mode range for a 741 with ±15-volt supplies is ±12 volts maximum. Thus, you cannot normally ground the negative supply and apply a grounded input.

Back to those inputs. If we apply a very small positive voltage step to the + input, it drives the output positive, since it is not (or non) inverting the step. If we apply the same small positive step to the - input, the output gets driven in the negative direction since this is the inverting input.

Remember that there is no ground connection on the op-amp. Ground for the circuit is simply "a stake driven in the ground" that tells us where halfway between the two supply limits happens to be, and the point where we get the most common mode swing in either direction. Our circuit always amplifies the difference between the two inputs and ignores any common signal that both inputs identically share, provided, of course, that that common signal is within the proper commonmode operating range of the amplifier.

If we use both inputs, we are operating in a differential mode. If we ground one input, or tie it to some other reference within the allowable limits, we are working in the single-ended mode. Thus, the inputs are referenced only to each other, unless you "stake one down" to some reference voltage such as ground.

Feedback

We apparently have a choice of where we put our feedback. Usually, we apply feedback to only the (-) or inverting input. Rarely, we can apply positive feedback to the (+) or non-inverting input, but you essentially never do both at once in simple circuits.

If the feedback network goes from the output to the + input, a small positive input gets amplified, turns around and drives the input further positive, and builds up avalanche style. This would be positive feedback and is inherently unstable. You normally can use positive feedback only where a snap-action or speedup is desired. With positive feedback, the output usually sits as close as it can get to either the positive or the negative supply. The output is then essentially two-valued or digital.

Normally, we are more interested in having the amplifier behave linearly instead of flipping from stop to stop, digitallogic style. To do this, we use negative feedback from the output to the (—) input. Negative feedback always tries to correct any changes forced on the amplifier by the input signals. Negative feedback always tries to force the difference between the two inputs to zero.

If we make the + input ground for single-ended operation, the negative feedback will always force the input to ground continuously. For if it wasn't at ground, the high gain of the amplifier would immediately amplify the error signal and feed it back for correction.

If the (-) input is never allowed to go away from ground by anything but a tiny amount, we can think of it as being the same as ground as far as the feedback networks are concerned. The name for this is a virtual ground, and in a properly connected and fedback operational amplifier, the (-) input behaves as a dead short to ground, as far as the rest of the circuit can tell. Since there is no feedback taking place at the (+) input, it remains as a very high impedance. So, with negative feedback, the (-) input looks like a short and the (+) input looks like an open, despite apparently identical internal circuitry. Some more rules:

5. If the feedback on an operational amplifier goes from the output to the + input, you will get a snap-action and a digital-logic style output. This is useful only for comparators and other snap-action circuits.

6. If the feedback on an operational amplifier goes from the output to the — input, you will get a linear operation useful for amplifiers, integrators and filters.

The output will exactly follow the ratio of the input to output impedances, provided there is enough excess gain at the operating frequency.

7. When negative feedback is used, the input impedance on the + input is normally very high. The input impedance on the — input is normally extremely low and is called a virtual ground.

Now, this virtual ground thing is extremely useful. It means you can *sum* input signals without crosstalk or interaction. It means that the input and feedback networks don't interact with signal levels or each other. And it vastly simplifies the math behind whatever you are trying to do.

Offsets

Figure 2 shows a typical differential amplifier stage from the input circuit of

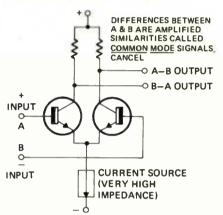


FIG. 2—THE DIFFERENTIAL INPUT STAGE provides an output signal proportional to the difference between the two input signals.

an operational amplifier. The + input goes through the first transistor as an emitter follower and through the second transistor as a grounded base stage to arrive at the A-B output. Neither stage inverts and the amplified signal stays the same polarity as it went in. On the other hand, the — input goes to the A—B output as a common emitter stage, which inverts the sense of the signal, so that at the output, identical polarity signals on both inputs are cancelled, while differential polarity signals on both inputs are amplified. We've already seen that these identical polarity signals are common-mode signals. If the op-amp is good enough, commonmode signals are essentially totally eliminated. Since power supply hum and voltage variations are one form of common-mode signal, this is extremely handy.

If you look at the mirror image of the inputs, you'll find that the — input ends up uninverted and amplified on the left output and the + input gets inverted by a common emitter stage. The pair of outputs will be an amplified version of only the difference between the two inputs, and common-mode signals will be ignored as they exactly cancel.


Now the inputs go to the bases of two NPN transistors. Where does this base current come from to run them? Well, ah, er..., You better have a good answer to this or your circuit won't work. The base current can come from your input circuit through a low-impedance DC path, from

a resistor to ground, from a special current source, or from the output via a feedback resistor, but it MUST be provided. The most important rule and the cause of most op-amp problems:

8. DC base bias current MUST be provided for both the + and — input to an operational amplifier. This is usually done as resistors or coils to ground, back through the input, from the output, or from another reference voltage. In a 741 style amplifier, around 100 nA of current must be provided for both + and — inputs.

The input transistors are very nearly identical, being integrated and all on the same chip at essentially the same temperature. They also track very well with temperature. However; even with the best of matching, there will be a slight voltage difference (a millivolt or two) between the inputs. This is called the *input offset voltage*. The rest of the amplifier has no way of telling the difference between this offset and a legitimate input signal.

Figure 3 shows some tricks we can pull

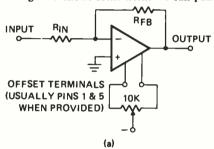

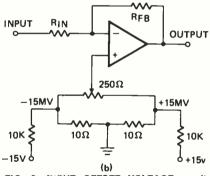


FIG. 3—INPUT OFFSET VOLTAGE results from a mismatch in the differential input stage. Two methods for reducing the voltage is shown.

to reduce the input offset. A pot can be added if pins are available for this (usually omitted on dual and quad devices), or input currents can be balanced by unbalancing impedances, or special bias sources can be added. Correction of offset will only be perfect at one temperature, but a 10:1 reduction in input offset is usually easy to do over a reasonable temperature range.

The importance of the offset depends on what you are trying to do with the operational amplifier. If you set your amplifier to a gain of 100 with feedback resistors, a 2-mV input offset becomes a 0.2-volt output offset. AC couple your output and there is no problem at all. But for DC outputs and high gain, the amplifier input offset must be allowed for. Another rule:

9. An operational amplifier such as the 741 has an input offset of one or

TABLE OF OP-AMP MANUFACTURERS

ADVANCED MICRO DEVICES 901 Thompson Place Sunnyvale, California 94086

FAIRCHILD SEMICONDUCTOR 313 Fairchild Drive Mountain View, California 94040

MOTOROLA SEMICONDUCTOR Box 20912 Phoenix, Arizona 85036

NATIONAL SEMICONDUCTOR 2900 Semiconductor Drive Santa Clara, California 95015 RCA SOLID STATE Box 3200 Somerville, New Jersey 08876

RAYTHEON SEMICONDUCTOR 350 Ellis Street Mountain View, California 94040

SIGNETICS 811 E. Arques Avenue Sunnyvale, California 94086

SILICON GENERAL 7382 Bolsa Avenue ... Westminster, California 92683

See Radio-Electronics back-of-the-book ads for surplus availability and prices.

more millivolts. This offset voltage is amplified and treated as a legitimate input signal. Input offset can be externally bucked out at one temperature if it is a problem. The remaining offset defines the minimum acceptable value for the DC input signals.

10. The output offset in DC volts will equal the input offset times the in-circuit gain of the operational amplifier.


So we have to provide a source of base current for both the + and — inputs, and we get a DC offset voltage "free" that we have to minimize somehow.

Besides the voltage offset, we have another problem to worry about — current offset. Whatever resistance is doing the biasing for our inputs will produce a voltage drop across it caused by the biasing current. This biasing current is typically 100 nA, but a difference of as much as 20 nA typically might be exhibited by both inputs under identical conditions.

A current of 100 nA is the same as 0.1 μ A. A 0.1- μ A current through a 10K resistor gives you a 1-mV drop, not really very much. But a 100K resistor gives you a 10-mV drop which can get important, and a 1-megohm one gives you a full tenth of a volt, which is hard to ignore, particularly in high-gain applications. For instance. Ground the + input and use a 1-megohm input resistor and a 20-megohm feedback resistor to try to get high input impedance in an inverting gain-of-20 amplifier. The output offset will be a very hard-to-ignore 2 volts!

How do we get rid of it? Simply provide a 1-megohm resistor in the + lead as well. Now, the input bias currents provide the same drop on both sides and everything cancels out. Everything that is, but the differential offset current, and you can get a one temperature cancellation of this by making the two source impedances slightly different. Figure 4 shows how we can go about cancelling offset currents. Another rule:

11. The impedances doing the DC biasing of the op-amp inputs should be approximately the same value particularly at high gains or at high impedance levels. Input offset current can be adjusted by trimming one impedance level with respect to the other. Impedance levels above 100K on a 741 will introduce major offset problems.

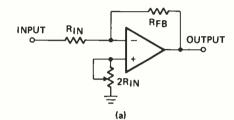

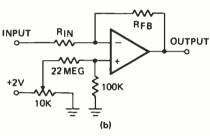


FIG. 4—INPUT OFFSET CURRENT results from a mismatch in the input stage. Two methods for reducing the current is shown.

At very low impedance levels, say 1K or so, you usually can ignore the input currents and input offset currents. As the impedance level goes up, the offset currents become more important. So, at low impedance levels, only worry about the offset voltages, At higher levels, consider both the offset voltages and currents.

Compensation

At some very high frequency of operation, the internal capacitance, delays, and storage times of any amplifier will begin adding delay or phase shift to the signal being amplified. If we ever reach a frequency that shifts the phase by 180° and still have gain, a negative feedback connection will give us two 180° inversions, or it will put us back in phase with the input. If the loop gain is high enough, we end up with an oscillator rather than an amplifier, because the added phase shift converts what is supposed to be negative feedback into positive feedback, reinforcing its own input.

This is true of any feedback amplifier. Depending on the design, the circuit can be stable, conditionally stable, or inherently unstable. One of the surprising things that turns up is that the lower the in-circuit gain of the amplifier, the more likely it is to oscillate! This is caused by a greater percentage of the input being

Get inside digital electronics!

Bell & Howell Schools now offers you two fascinating learn-at-home programs that can equip you with professional know-how in the expanding field of digital technology!

The world of electronics is an astounding place-a world that, in the short span of 70 years, has taken us from a simple mechanical age into an age where electronic sophistication has actually helped man set foot on the lunar

One area of this space-age technology that has been successfully harnassed for consumer and industrial use is digital electronics. It is this breakthrough that has given us such remarkable new products as tiny pocket calculators and digital-display wristwatches. And now, you can learn about some of the many extraordinary applications of digital electronics in two special learn-at-home programs from Bell & Howell Schools.

Start your exploration of electronics at home!

With these exciting home learning adventures from Bell & Howell Schools you'll experience the true thrill of discovery as did such electronic pioneers as Thomas Edison and Dr. Lee DeForest. And think about this ... they didn't discover electronics in a classroom, and you don't have to either!

Whichever program you choose, test new electronic theories as you build and experiment with the exclusive Electro-Lab® electronics training system!

With your very first lesson you'll receive a special Lab Starter Kit, so you'll be able to see how basic electron-Lab Starter Nit, so you il be able to see now basic electronic principles actually work in practice. Then, step by step, as your understanding of electronics increases, you'll actually be able to perform your own experiments and work on fascinating projects from "scratch"—like building the exclusive Electro-Lab® electronics training system. This important project helps you learn electronic skills through "hands on" experience with professional testing equipment. The Electro-Lab® system consists of a design console to help you learn how to hookup circuits—a digital multimeter for measuring electrical voltage, current and resistance. And a solid-state "triggered sweep" oscilloscope that, among other things, you'll use to analyze the operation of tiny integrated circuits. The "triggered sweep" feature locks in signals for easier reading.

I. HOME ENTERTAINMENT ELECTRONICS

Learn how digital technology is being applied to home entertainment products—build and experiment with the new generation 25" diagonal color TV with digital features!

To learn the most advanced electronics technology you must work with up-to-date training tools. That's why

****** you'll build Bell & Howell Schools' 25" diagonal color TV with digital features as part of your training. Step by step you'll learn about the many exciting applications of the most up-to-the-minute electronics technology. And you'll have the confidence in knowing that the advanced skills you're learning will be valuable for years to come. "Hands on" training will help you

2:39:03 S

understand advanced applications of digital technology!

Your "hands on" training will give you a professional's understanding of how this advanced technology works. How features such as on-screen, digital display channel numbers and a digital time readout in hours, minutes and seconds are possible. You'll learn to program an automatic channel selector so that it skips over dead channels and "homes-in" on the channels of your choice. And, how "state-of-the-art" integrated circuitry and the 100% solid-state chassis add immensely to your understanding of circuit theory and TV servicing techniques. You'll also become thoroughly familiar with the technology behind features such as digitally-automated tuning, and the outstanding color clarity of the Black Matrix picture tube.

By actually building and experimenting with this exceptional equipment, you'll gain the occupational skills, specialized knowledge—and

skills, specialized knowledge—and the self-confidence that could open up exciting new directions for you!


II. DIGITAL INDUSTRIAL ELECTRONICS

Our exclusive digital trainer will help you discover today's exciting applications of digital electronics in industry.

Industry is constantly finding new applications for digital technology. Today, this technology is helping to set new standards of accuracy and provid-

new standards of accuracy and providing a more precise method of control in refining, food processing, transportation and in manufacturing plants.

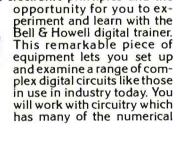Now Bell & Howell Schools has a learn-at-home program that could get you involved in the industrial uses of this challenging technology. The program provides a solid background in basic electronic principles and the



and process control applications used in a number of today's most sophisticated manufacturing operations.

Bell & Howell Schools is with you every step of the way!

You'll be pleased to know that, throughout all of these dynamic Bell & Howell Schools' programs, you're just a toll-free phone call away from expert assistance should you need it.

For even more personal attention...Bell & Howell Schools has a truly unique idea—

You can attend in-person help sessions scheduled in over 50 major cities at various times throughout the year, where you can meet and talk with fellow students and receive additional assistance from an instructor.

Once you've completed this program, your skills in electronic troubleshooting could lead you in exciting new directions. While we cannot offer assurance of income opportunities you can use your training: to seek out a job in the electronics industry, to upgrade

your current job, or as a foundation for advanced programs in electronics.

Now...audio/quadraphonics...first home program of its kind!

It's another first from a leader in home learning. Bell & Howell Schools proudly introduces America's first learn-at-home program in audio electronics featuring the exploration of quadraphonics. It's the 4-channel "wraparound" sound system that has opened a new era in audio technology! You'll actually build Bell & Howell's 4-channel audio center including amplifier and FM-FM Stereo receiver as a part of the development of professional knowhow in this exciting and promising new field. Get more details now...check the appropriate box on card and mail today!+

Why not aim yourself in an exciting new direction today—just check the Bell & Howell Schools' program you're interested in and...

Mail the postage-free card right away!

We'll see that you get more details! Taken for vocational purposes, these programs are approved by the state approval agency for Veterans' Benefits.

†Cabinet and speakers available at extra cost.

Simulated TV picture/test pattern.

"Electro-Lab*" is a registered trademark of the Bell & Howell Company.

If card has been removed, write:

An Electronics Home Study School
DEVRY INSTITUTE OF TECHNOLOGY



4141 Belmont, Chicago, Illinois 60641

RADIO-ELECTRONICS

fed back in lower gain situations. Unity gain of a feedback amplifier is much more likely to oscillate than say a gain of 100 or some other high value.

The process of stabilizing an amplifier is called compensation. The basic rule of compensation says that for any gain (open loop) above one, your amplitude versus frequency slope must always be less than -12 dB-per-octave. Hit -12 dB-peroctave, and if you do it at a frequency where the open loop gain equals one or more, you've got yourself an oscillator, not an amplifier. One obvious way to compensate is to hang a very large capacitor in the middle of the circuit. So large that it completely dominates the amplitude versus frequency response, giving you a simple and safe 6-dB-per-octave slope. This is called a dominant pole, and while it certainly stabilizes the amplifier, it also drastically reduces the frequency re-


The dominant pole capacitor is used in the 741. This gives you an unconditionally stable amplifier (unless you go out of your way to try to make an oscillator out of it on purpose), and results in simple and easy circuits. The price paid is the frequency response. The dominant pole breaks at 3 hertz, dropping at 6 decibels per octave eventually to reach unity gain at 1 megahertz.

Another rule:

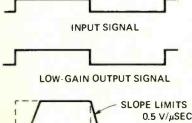12. Frequency compensation must be provided for any operational amplifier using negative feedback. The 741 is internally compensated at the price of a relatively poor frequency response. The LM318 offers either internal or external compensation.

Slew rate

When we are done with our compensation, we end up with another problem, called the slew rate problem. At small signal levels and small output swings, our normal frequency versus amplitude response curves apply. But, if we try to swing the output through larger amplitudes, the output goes into a currentlimited ramp mode and, as Fig. 5 shows us, considerable distortion.



0.5 V/μSEC 741 50 V/μSEC 318

HIGH-GAIN OUTPUT SIGNAL

FIG. 5—THE SLEW RATE of an operational amplifier limits large output, high-frequency sinnals

What this means is that you can't have high-frequency operation and large output swings at the same time. The fastest you normally can change the output of a 741 is 0.5 volt/µs. You can estimate how bad the slew-rate problem is by substituting a triangle wave of one and one half times the normal amplitude of your highest frequency sinewave and see what happens.

For instance, suppose you have a 4-volt peak-to-peak, 10-kHz sinewave. Approximate it with a 6-volt peak-to-peak triangle wave. The period of the waveform will be $100~\mu\text{s}$. The half period will be $50~\mu\text{s}$. We have to change 6 volts in $50~\mu\text{s}$, or around an eighth of a volt per microsecond. Since the 741 can only handle $0.5~\text{volt}~\mu\text{s}$ maximum, you're pretty near the reasonable limit of operation.

Note that slew rate is determined both by frequency and amplitude. Eight volts peak-to-peak at 5 kHz will have about the same needed slew rate as 2 volts peak-topeak at 20 kHz, and so on.

If you need larger signal swings in the upper audio region, the 741 simply won't do the job. Consider the more expensive LM318 that has a 50-volt \(\mu\)s slew rate, or one hundred times as much for these applications. For our next rule:

13. The slew rate limits the large signal output swing to a maximum slope ramp at higher frequency. The slew rate is 0.5 V/ μ s for the 741 and 50 V/ μ s for the LM 318.

Besides these slew rate limits, there are obviously drive limits at the output stage that apply to any operataing frequency. If possible, you should keep your external output and feedback loads above 1000 ohms, although you can reduce this to several hundred ohms with lower output swings. The maximum output current you can possibly get in a limiting (clipping) mode is around 25 mA. This is beyond the normal range of linear operation.

Noise

A final limit to an operational amplifier is the input noise level which gets amplified along with the signal. All amplifiers produce some noise, and the worst of it is usually involved with the first stage. The 741 is not particularly a low-noise device, but it is useful for many small-signal amplification problems. Typical noise for a 741 referred to the input is $10~\mu V$. Thus if you have a gain of ten, you get $100~\mu V$ of noise out. At a gain of 100, you get 1~mV out, assuming you are using the full bandwidth of the device.

If you reduce your bandwidth, the noise goes down, but only very slowly, for noise is proportional to the square root of the bandwidth. So, to get only 1 μ V of noise, you have to cut your bandwidth by 100, from a rominal 100 kHz to only 1000 Hz. Regardless of your application, the final noise sets your overall signal-to-noise ratio. For instance, with a gain-of-ten circuit, you can amplify a 10- μ V signal with unity signal-to-noise ratio (essentially worthless), a $100-\mu$ V one with 20 dB signal-to-noise (possibly useful) or a 1-mV one with a 40-dB signal-to-noise ratio (pretty good.)

The LM318 generally has better noise performance than the 741, although at high impedances and wide bandwidths (remember it has 100 times the bandwidth), the noise can get up to 200 μ V at the input. With a 1000-ohm source on the

inputs, the equivalent noise to the 741 is around 3 μ V, 12 dB better than the 741, provided that you limit the bandwidth suitably. A final rule:

14. The first stage noise level of any operational amplifier sets the minimum possible signal level for a given signal-to-noise ratio. Referred to the input at a 100-kHz bandwidth, this noise is 10 μ V for the 741 and 3 μ V for the LM318. Noise is normally proportional to the square root of bandwidth.

(to be continued)

Virginia electronic technicians take strong stand on warranties

The Board of Directors of the Virginia Electronics Association adopted the following resolution unanimously at its meeting in Chester, VA.

"WHEREAS: The Virginia Electronics Association recognizes that warranties extended beyond a period of 90 days

- have no bearing on the quality, serviceability or anticipated life of a product;
- 2. are frequently used to mask inferior product quality and/or perfor-
- 3. are a deceptive sales tool used by some manufacturers and retailers to create a captive repair market with the customer's own money, and
- actually hamper consumer satisfaction by frequently foisting inadequate compensation upon the servicer or less than quality service on the buyer, and

WHEREAS: the Virginia Electronics Association feels that the manufacturer, the servicer and the customer are best served by devoting more time and money to improving product performance and safety and less of the consumer's purchasing dollar on extended warranty/insurance schemes, and

WHEREAS: one major manufacturer, in the face of rising consumerist pressures, has decided to reduce its labor warranties to a more realistic 90-day period, therefore:

BE IT RESOLVED: that the Virginia Electronics Association hereby commends GTE-Sylvania for its wise and courageous decision in taking the lead to restore sanity to the field of consumer-electronics product warranties, and


BE IT FURTHER RESOLVED: that the Virginia Electronics Association implores all such manufacturers to review their present costly, deceptive frustrating and self-defeating extended warranty programs and take similar steps to redesign and reduce those warranties to better serve the consumer and the electronics service industry."

Copies of the resolution were mailed to nearly 500 manufacturers and importers, 50 association, trade and technical publications, three national electronics associations, and to all persons who might be concerned.

measure dB's with your scope

With the simple method described in this article, you can use your oscilloscope to measure dB's quickly and accurately.

by JOHN D. GABBERT

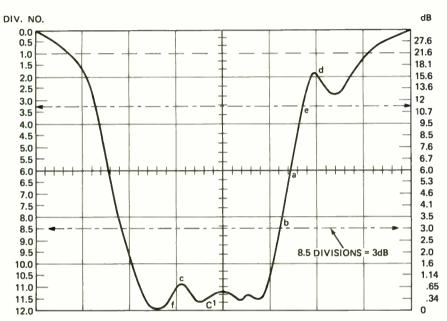

DECIBELS MAY BE MEASURED QUICKLY and with reasonable accuracy by using an oscilloscope with the simple scale shown. No calculation is necessary. Each vertical graduation on the figure, which normally represents one centimeter, has been subdivided into four divisions. On the left side are the division numbers and on the right the corresponding value of each division in decibels.

The graticule illustrated is a standard laboratory scope scale with six vertical and eight horizontal centimeter graduations on which decibel values are calculated using the formula:

$$dB = log \frac{V_1}{V_2}.$$

To use the scale: Set the oscilloscope controls so that the display exactly fills the graticule, with the peak amplitude of the waveform resting on the bottom graduation. Count the number of divisions to the point on the waveform that you want to measure and read from left to right on the scale to find out how many decibels of attenuation that point represents: For example, point a at 6 divisions equals -6 dB, point b at 8.5 divisions equals

-3 dB, point f at 12 divisions is equal to 0 dB or peak amplitude.

Some interpolation is necessary at point **d**, which is between 1.5 and 2 divisions and is equal to 16.7 dB and also at point **e** at 3.25 divisions and equal to 11.3 dB.

Points c and c' represent the peakto-peak value of the first cycle of a ripple or damped oscillation.

As the oscilloscope response is linear, the actual voltages need not be considered—only the ratio of V₁ to V₂. If the value of V₁ is considered to be 12 at peak amplitude, V₂ will be some value less than 12. For instance, at point d, V₁ equals 12, V₂ equals 1.75. From the formula.

$$dB = 20 \log \frac{12}{1.75}$$

 $dB = 20 \log 6.86$

 $dB = 20 \times 0.8363$


dB = 16.7 dB

In most cases the 24 divisions, each representing 1/4 centimeter, will supply the required degree of accuracy.

Keep input voltage to the scope low so that the amplifiers will not overload and flatten the trace—this could result in inaccurate measurements.

EQUIPMENT REPORTS

(continued from page 34)

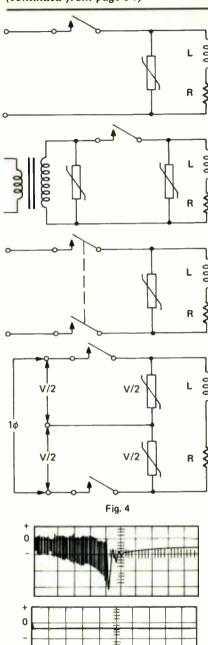

HORIZONTAL: t, 500 μsec/cm VERTICAL: V, 1.0 kV/cm

Fig. 5

field. Requests for data on the other GE-MOV varistors should be addressed to distributors of G-E industrial semi-conductors, Ask for G-E application notes 200.60, 220.71 or 200.72 or for spec sheets.

NEXT MONTH IN R-E

Tape recorders contain more than just record and playback electronics. Many modern tape transports also have a heap of electronics to direct the mechanical operations. Len Feldman explores these special electronics features of modern tape decks next month. Be sure you don't miss the June issue of Radio-Electronics.



l about curve tracers

This article tells what to look for when purchasing a curve tracer; how to test different solid-state devices, and how to interpret the resulting waveforms

by CHARLES GILMORE*

LAST MONTH WE DISCUSSED THE TESTing of diodes and bipolar transistors. We also started discussing field-effect transistors

This month we will complete our look at field-effect transistors and conclude the article with SCR's and triacs.

One of the most important measurements that can be made for field-effect devices is gain. The gain of an FET is referred to as transconductance (gm)—ratio of the change in drain current caused by a change in gate voltage, expressed in µmhos. Figure 16 is a display of an n-channel junction FET. (2N4416). To measure trans-

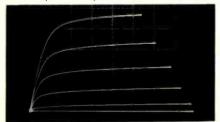


FIG. 16—A FAMILY OF CURVES for the 2N4416 n-channel JFET. The uppermost curve is the curve for step-generator output of zero volts. Succeeding downward curves represent increased voltage output from the step generator. Settings are: step generator, —0.5 volt/step; drain limiting resistance, 500 ohms; horizontal sensitivity, 2 volts/cm; vertical sensitivity, 2 mA/cm.

conductance, a change in drain (sweep) current, is read from the curve tracer. Since the step value causing this current change is known, the change in drain current can be divided by the change in gate (step) voltage, yielding transconductance.

Note that the transconductance is not uniform from curve to curve. Therefore, transconductance must be measured at or about the normal operating current. The next most important characteristic is voltage breakdown.

*Design Engineer Heath Company, Benton Harbor, Mich.

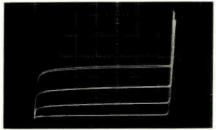


FIG. 17—BREAKDOWN CHARACTERISTICS OF A 2N4416 n-channel JFET. Settings are: step generator, —0.5 volts/step; drain limiting resistance, 500 ohms; horizontal sensitivity, 10 volts/cm; vertical sensitivity, 2 mA/cm. The drain to source breakdown of the 2N4416 is specified at 30 volts.

Figure 17 shows the breakdown characteristics of the 2N4416. These characteristic curves are quite similar to those of the bipolar transistor.

When FET's are used in digital applications or for switching analog signals the "on" resistance expressed as $R_{\rm on}$ is important.

For an n-channel JFET, $R_{\rm ox}$ is the resistance from drain to source with the gate-to-source voltage at zero. The value of $R_{\rm ox}$ can be determined by increasing the horizontal sensitivity of the curve tracer until the resistance of the "ON" portion of the curve can be measured. (Fig. 18).

Special precautions that should be taken when testing field-effect transistors include taking extreme care with MOS devices, especially those that are unprotected, to make sure that the terminals are not exposed to static electricity. One way to do this is to wrap a fine wire around the leads of the transistor before removing it. Unwrap this wire only when the device is securely mounted in the curve tracer. If the FET is a dual-gate MOS FET, return the unused gate to the source terminal of the device. If the characteristics are specified with a certain gate-to-source voltage on the un-



FIG. 18—THE "ON" RESISTANCE of a TI TIS-73 n-channel JFET. This device is specially designed for switching applications. Settings are: step generator,—1 volt/step; drain series limiting resistance, 10,000 ohms; horizontal sensitivity, 0.02 volts/cm (0.1 volt/cm with a X5 magnifier); vertical sensitivity, 0.5 mA/cm. The steepest curve (the first) has a slope of 24 ohms. This curve is generated by a drain sweep with the gate to source at zero. Specifications for the TIS-73 call for 25 ohms maximum resistance.

used gate, this voltage should be supplied from an external source. Never test MOS devices with the gates unconnected.

SCR's and triac's

The characteristics of silicon controlled rectifiers (SCR) and the dual version of the SCR, the triac, can be easily examined on the curve tracer. Figure 19 shows the curves of an SCR. We can use these to measure forward



FIG. 19—THE FORWARD CHARACTERISTICS OF A TIC-44 SCR. Settings are: anode series limiting resistance, 50,000 ohms; horizontal sensitivity, 40 volts/cm (20 volts/cm with a X0.5 magnifier); vertical sensitivity, 0.5 mA/cm. The forward blocking voltage of this device is 230 volts, and the holding current is 0.5 mA.

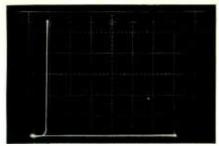


FIG. 20—"ON" RESISTANCE OF THE TIC-44 SCR. Settings are: anode series limiting resistance, 1000 ohms; horizontal sensitivity, 1 volt/cm; vertical sensitivity, 1 mA/cm.

blocking voltage and holding current. As with the diac, forward blocking voltage is the maximum collector voltage that can be reached. The holding current is the lowest forward current that can be maintained. When making these measurements, the step generator is set for zero current output.

Figure 20 shows a display used to measure gate trigger current and "ON" resistance of the SCR. To measure gate trigger current, reduce collector sweep voltage to a point below the forward blocking voltage of the SCR. Adjust the steps-per-family control for a known number of steps - if necessary this is the maximum number of steps available from the curve tracer. Then advance the step range control from the smallest step current to the first position at which the vertical line appears. This tells us that gate sensitivity falls between the position just prior to this and the position which caused the vertical line.

Once we see a vertical line, the onresistance of the SCR is measured by expanding the horizontal sensitivity and computing the resistance the vertical line represents.

With the SCR, the reverse blocking voltage is essentially the reverse voltage of the main diode portion of the SCR. This is measured in exactly the same manner as the reverse breakdown voltage of a diode.

Make forward measurements on a triac in the same way as for an SCR. Reverse measurements will produce curves identical to the forward set, but inverted; as the triac acts like two SCR's in parallel, with one reversed.

Figure 21 is the characteristics of a unijunction transistor (UJT), connected as indicated on the set-up chart. The slope of this curve shows the inter-base resistance of the device.

Wrap-up

The number of devices that can be analyzed with curve tracer are limitless. All measurements that have been discussed can be applied in one form or another as in-circuit measurements as well as measurements on devices. When making in-circuit measurements, the power supplies should be turned


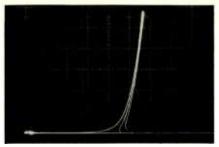



FIG. 21 — INTER-BASE RESISTANCE OF THE 2N2646 unijunction transistor. The unijunction is connected to the curve tracer terminals as follows; B1 to E, B2 to B, and E to C. Settings are: step generator, O mA/step; emitter series limiting resistance, 500 ohms; horizontal sensitivity 0.2 volts/cm; vertical sensitivity, 0.5 mA/cm.

off, and if possible disconnected from the device under test. Remember, resistances in the circuit, in addition to those of the device, can affect the characteristic curves.

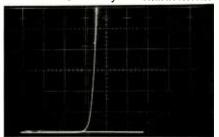Virtually any device can be measured with a curve tracer. Neon lamps, tungsten lamps, LED's, vacuum tubes and even IC's can yield characteristic



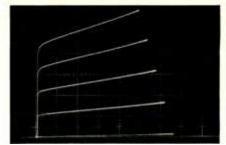BREAKDOWN AND HOLDING VOLTAGE of an NE-2H neon lamp. Settings are: series limiting resistance, 10,000 ohms; horizontal sensitivity, 20 volts/cm; vertical sensitivity, 1 mA/cm. For this particular lamp, breakdown occurs at 130 volts and holding voltage is 65 volts at 1 mA.



FAMILY OF CURVES FOR A H1GH-GAIN silicon pnp transistor (MPS-6522). Curve tracer settings are: step generator, 0.005 mA/step; collector series limiting resistance, 1000 ohms; horizontal sensitivity, 4 volts/cm; vertical sensitivity, 1 mA/cm. At 8 volts Vcs and an average collector current of 3.5 mA, beta is calculated to be 1.45 mA/0.005 mA, or 290.

traces that may tell a great deal about their function.

Once you feel that you have a solid grasp of the fundamentals of curve tracer measurements, and a good knowledge of the limitations of your curve tracer, a great number of measurements can be made. These are bound only by the specifications of your curve tracer.


Because of its fundamental measuring concepts, the curve tracer will probably be directly applicable to new devices as they are developed. Applying fundamental curve tracer measurement principles to the new device will produce a set of characteristic curves that may be used for comparing devices and measuring their varied parameters.

NEXT ISSUE SCOPES

SET-UP TABLE

Table describes the setup of the curve tracer for each particular device.

			•		
Device	Terminals	Sweep	Step Generator	Initial Spot Position	
NPN	СВЕ	+	+ Current	Lower left	
PNP	СВЕ		Current	Upper Right	
N-CHANNEL JFET	DGS	+	Volts	Lower Left	
P-CHANNEL JFET	DGS	_	+ Volts	Upper Right	
N-CHANNEL MOS FET (depletion)	DGS	+	Volts	Lower Left	
P-CHANNEL MOS FET (depletion)	DGS	_	+ Volts	Upper Right	
N-CHANNEL MOS FET (enhancement)	DGS	+	+ Volts	Lower Left	
P-CHANNEL MOS FET (enhancement)	DGS	_	 Volts	Upper Right	
Forward Diode	A Nc C	+	None	Lower Left	small-signal diode rectifier
Reverse Diode	A Nc C	_	None	Upper Right	Zener diode or checking reverse breakdown
SCR Forward	AGC	+	Current	Lower Left	½ of Triac
SCR Reverse	AGC	+	Current	Upper Right	½ of Triac

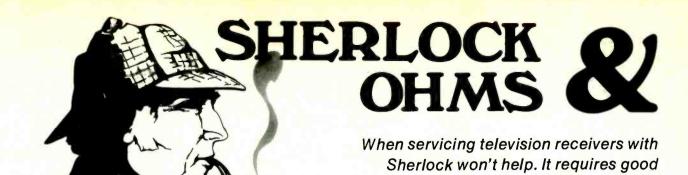

THE OLD-TIMER SAT IN THE MIDDLE OF a spider web of extension cables and scowled at the underside of the big Magnavox chassis on the bench. The cabinet sat on a bench-high cart. Peering around the end of it, he checked the picture in the mirror. Yes, it was still going up and down with that queer jerky motion that he'd been trying to dig out for quite a while. He frowned at the screen of the scope; this showed a very peculiar pattern. The probe was clipped to the open end of a resistor.

He growled a few choice words that were answered by a not-too-muffled snort from the doorway. He looked up. "Hi. Henry! Didn't hear you come

"Hi, Henry! Didn't hear you come in"

in."

"I heard you," said Henry, grinning.
"What did you tell us about calling them names when you were lecturing us the other night? That's not supposed to be the way to do it, remember?"

"Yeah, yeah," said the Old-Timer, reluctantly. "Actually, I was really calling myself names! It looks like I'm going to start another one of my Stupid Days. I can tell by the way this chassis is acting, that it's gonna turn out to be something so simple that I'll really feel foolish! They always do. And no matter how I try to hide, there's always some snoop like you that comes in and catches me!"

"Actually, all I wanted was to borrow a 6JE6 tube; I'm out," said Henry. "Anyway, let me prescribe a dose of your favorite remedy for you; a good cuppa cawfee!"

"What a salesman," said the Old-Timer, unwinding himself from the extension cables and getting up. "You got a deal".

Settled over their coffee cups, Henry laughed at the sour look on the older man's face. "OK, tell me the sad story. I have a dry shoulder for you to cry on."

"Well, you asked for it," said the Old-Timer. "That thing has no vertical sync at all. The darn picture jumps

and jiggles up and down, but won't lock. Oscillator's OK, rolls up or down with the hold control. BUT! I have the screwiest symptom I can ever remember seeing. There is absolutely NO vertical sync in the composite-sync waveform out of the sync-separator!"

"Huh?" said Henry, puzzled. "How is the peak-to-peak amplitude?"

"Just right!" said the Old-Timer. Makes a good bar pattern on the scope, just like it should. And the horizontal sync is steady as a rock! Perfect sawtooth, plenty of hold, color, and everything else. With the scope on the integrator input, all I can see is a smooth bar. There isn't a single vertical sync spike in it!" (Fig. 1.)



FIG. 1—COMPOSITE-SYNC WAVEFORM at the integrater input shows a complete lack of any vertical sync spikes.

"How in the world could that happen?" asked Henry, bewildered. "It looks like anything that took out the vertical sync would get the whole composite sync waveform."

"That's what I've been trying to find out for an hour," said the Old-Timer, gulping the last of his coffee. "And I had the scope on the open end of the vertical integrator; not a sign of any vertical sync, or anything else for that matter. It just isn't there. All of the integrator components check out good. Also, did you notice how the picture was acting when you came in? Sort of jumping and jerking at two points on the screen, looked almost like it did have some kind of sync. Well, it did not, at least not from the set; I had one end of the integrator completely open!"

Henry tut-tutted sympathetically as

they walked back across the alley, and into the shop. The Old-Timer turned the set on again, and they watched the picture jumping and jerking as it rolled slowly downward.

circuit analysis to find the solution.

"Makes my head ache," said the Old-Timer. "What's worse, I know it's going to be something that is so blasted simple that I should be kicked for not being able to see it."

The Old-Timer poked the scope here and there in the chassis, showing Henry the waveforms. Henry studied the jerking picture intently. Suddenly he cried "Hey! Your picture just turned bright blue!" and it had.

"Oh, that," said the Old-Timer wearily. "It just does that now and then to annoy me", and he slapped the rear apron of the chassis smartly with his fingers. The picture went back to normal. "I'll dig that out just as soon as I find out what's cancelling the sync—HEY! I think I just said the secret word. That's the only thing that could be happening! Somehow or other, I'm gittin' an opposite-polarity pulse into that circuit and it's cancelling-out the vertical sync!"

"Well, it's gotta be something like that," agreed Henry. "You sure couldn't filter it out. There isn't a filter anywhere that's sharp enough to—what are you doing?" The Old-Timer had gotten up from his stool, walked around and bent over in front of Henry.

"I said I'd kick myself, didn't I?" he said. "Well, I'm tired! Will you do the honors?" Henry gave him a carefully adjusted kick, then looked inquiringly at him. The Old-Timer sat down again. "I knew it! I knew it! After all the time I've spent lecturing you guys about it, and then I blow it. Now look here," and he reached over the set to flip the Service switch to the RASTER position.

The picture disappeared, leaving a smooth blank raster, with shading on it. "See there! Look! If those aren't 120-Hz hum-bars I'll eat my hat!" They weren't too plain, but they were

The Case of the Substitute Sync

problems like this one, even the real troubleshooting procedures and solid Here's how the Old-Timer did it.

by JACK DARR SERVICE EDITOR

unmistakably hum-bars. Two of them showed on the screen, rolling slowly and jerkily. "I noticed that when it was having a spell of flashing blue a while ago, but it didn't get through my thick skul! How many times have I said it? If you find a lot of unexplained symptoms all over the set, go and look at the FILTERS! You just said it! Filters. You want to kick me again?" Henry shook his head, grinning. The Old-Timer picked up the scope probe again, then sat there.

"Let's try analyzing it; it'll be quite a novelty, but I'll try. Let's just see how close we can get before we check. Now; we're obviously getting a very sharp vertical-frequency spike into that circuit somewhere. Since the normal sync is about 30-40 volts and negativegoing, we're getting enough positivegoing spikes in there to cancel it. Now, where could these spikes come from? That's right," he said as Henry opened his mouth. "From the vertical output! There's a perfectly normal, very high voltage spike in that circuit. So, where's a likely path for this to get back to somewhere that it isn't wanted? Right again."

Henry closed his mouth again. "Back through the power supply. If one of the filters opens up, It leaves such a high impedance that you can get all kinds of frightfulness all the way back to the front end!"

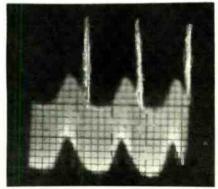


FIG. 2—VERTICAL SPIKES appear among hash at the terminal of one of the filter capacitors in the power supply.

He bent over the schematic diagram. "Let's see. That would be either this" and he touched the scope-probe to the terminal of a large multiple electrolytic capacitor. A straight line showed up on the scope screen. "Nope. Well, then, how about this one?" touching another terminal in the same can. The straight line disappeared, leaving the scope full of blurs. The Old-Timer beamed at it, and cut the vertical gain until the pattern appeared; See Fig. 2.

"Hoo, hoo, hee hee!" he crowed. "Look at that! Look at all those big fat vertical *spikes* in there with all of the rest of the hash. Hand me the electrolytic capacitor sub box. It's right behind you. Let's see. Halfmoon capacitor in C107, which is—80 microfarads. OK! We set the box to 80 microfarads, and now we push the switch! Wait a minute. Let's see something." He clipped the scope-probe to the open end of the vertical integrator resistor; nothing showed at that point.

"Now we push the switch." He did. The scope pattern suddenly jumped; a thick baseline appeared, with long, clean spikes coming down from it. See Fig. 3. The Old-Timer crowed hap-

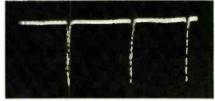


FIG. 3—NORMAL WAVEFORM appears at the output of the vertical integrater when a substitute filter capacitor is used.

pily. He released the switch, unhooked the probe, and soldered the integrator resistor back in place. Pushing the sub-box switch again, the picture suddenly locked tightly into place.

"Just a minute," said the Old-Timer.
"Before we sew up the patient, I want to show you something. I didn't believe it the first time I saw it, and I want you for a witness. I have never

seen exactly this symptom before. He connected the scope probe to the composite-sync output, adjusted the sweep, and said "There! There's your composite sync without a bit of vertical sync; same one you saw before. (Fig. 1) Now, we put in the good capacitor and boom. Plenty of vertical sync. (Fig. 4) BUT! When we take out the

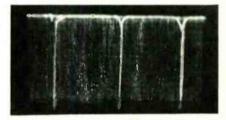


FIG. 4—NORMAL COMPOSITE-SYNC waveform shows plenty of vertical sync when a substitute filter capacitor is used.


capacitor, out goes the normal vertical sync, and the picture is trying to lock in on the spikes leaking through into the oscillator circuit! Notice that the picture jerks and tries to lock at two points as it rolls? One for each peak in the 120-Hz spike from the power supply!"

"Well, that's a new one," said Henry. "First time I ever saw that."

"True, true," said the Old-Timer, checking the schematic to find the sizes of the capacitors in the bad unit. "You think you've seen them all, and then they run another one in on you. Beats all what these things can do when they really try, doesn't it?" and he went to his stock cabinet to look up a replacement capacitor.

*In case you're still wondering about the blue flashing of the picture tube screen, this was due to an intermittent solder-joint on the socket of the 6MD8 color-difference amplifier! Pin I, the "blue plate", was opening up. This cut off all plate-current and the plate voltage rose to the supply value of about +350 volts. This, of course, being directly coupled to the blue grid of the CRT, caused it to bias the blue gun on very hard. Brightness controls, etc. had no effect.

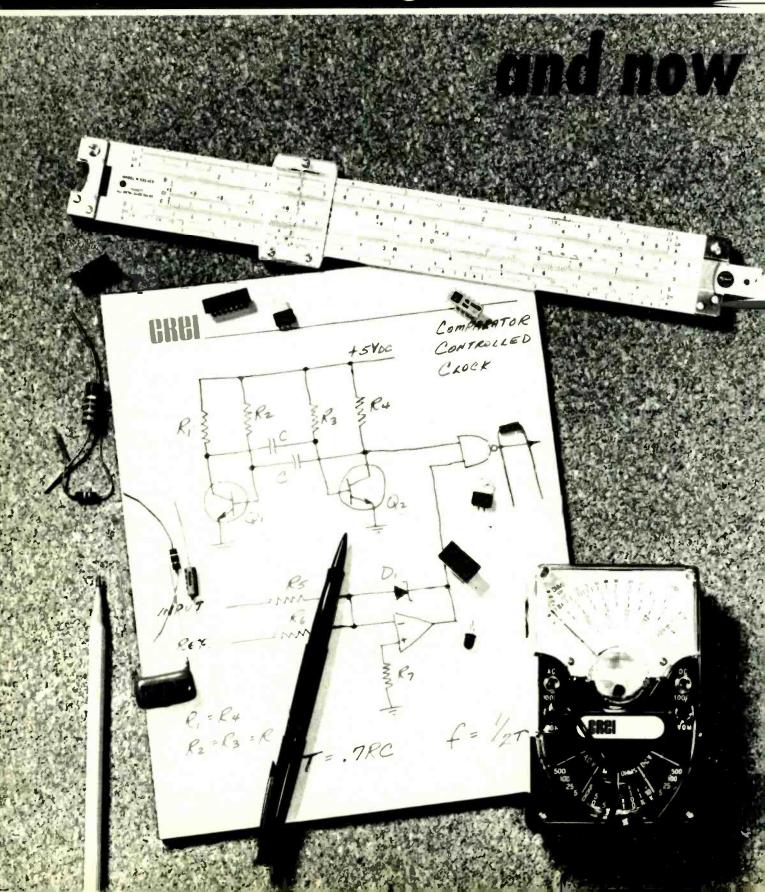CMET the uny numer study college-level training



in electronic circuit design

only CREI offers you a complete college-level Electronic Design Laboratory to speed your learning

Electronic circuit design—source of all new development in the application of electronics to new products and services. Without this skill, we would be unable to monitor the heartbeat of men in space. Without it, the computer revolution would never have occurred. And we would have yet to see our first TV show. Yet, only CREI teaches electronic circuit design at home.

ELECTRONIC CIRCUIT DESIGN

A key skill which paces our nation's progress in countless fields—from pollution control to satellite tracking to modern medicine to exploring the ocean's depths. And beyond. A skill which you must have to move to the top in advanced electronics.

CREI programs open up new worlds of opportunity for you.

In addition to electronic circuit design, CREI provides you with a full advanced electronics education in any of thirteen fields of specialization you choose. Communications, computers, space operations, television, nuclear power, industrial electronics—to mention just a few of the career fields for which CREI training is qualifying. With such preparation, you will have the background for a career which can take you to the frontiers of the nation's most exciting new developments. And around the world.

This free book can change your life. Send for it.

If you are a high-school graduate (or equivalent) and have previous training or experience in electronics, then you are qualified to enroll in a CREI program to move you ahead in advanced electronics.



Send now for our full-color, eighty page book on careers in advanced electronics. In it, you will find full facts on the exciting kinds of work which CREI programs open up to you. And full facts on the comprehensive courses of instruction, the strong personal help, and the professional laboratory equipment which CREI makes available to you. All at a surprisingly low tuition cost.

And when you have it, talk with your employer about it.

Tell him you're considering enrolling with CREI. He'll undoubtedly be happy to know you are planning to increase your value to him. And he may offer to pay all or part of your tuition cost. Hundreds of employers and government agencies do. Large and small. Including some of the giants in electronics. If they are willing to pay for CREI training for their employees, you know it must be good.

Send for Advanced Electronics today. You'll be glad you did.



CREI Dept. E-1405F 3939 Wisconsin Avenue Washington, D.C. 20016

Rush me your FREE book describing my opportunities in advanced electronics. I am a high school graduate.

Veterans and servicemen, check here for G. I. Bill information [7]

CREI

CAPITOL RADIO ENGINEERING INSTITUTE

WASHINGTON, D.C. 20016

RADIO-ELECTRONICS

TRANSFORMERS

BUCKing or BOOSTing Voltages

Don't throw those old transformers away.

Put them to work. Here's how to do it.

by LYMAN E. GREENLEE

TRANFORMERS FOR TUBE EQUIPMENT are cheap, but the newly designed ones for solid-state circuitry can be expensive, and a special transformer is not always available at any price unless we want to make one.

Suppose we need a 36-volt transformer for that new hi-fi amplifier. Easy does it . . . just hook up a 12-volt filament transformer and a 24-volt power transformer with primaries in parallel and secondaries in series. The result is shown in Fig. 1. If we use a 12-volt center-tapped transformer, we have a choice of 24-volt, 30-volt, or 36-volt outputs. Both trans-

36V 30V 24V 71 – 12 VAC, 1 AMP T2 – 24 VAC, 1 AMP


FIG. 1—THIS BOOST CONNECTION gives 24, 30, or 36 volts with a 24-volt and center-tapped 12-volt transformer. The switch will not be needed in most cases.

formers should have the same ampere rating. If they do not have the same rating, the smaller rating will apply to both secondaries when used in series. Example: If one transformer is rated at 12 volts and 2 amps., and the other one at 24 volts and 1 amp., the rating of the series combination will be 36 volts AT ONE AMPERE.

Hook the primaries in parallel and connect to the power lines. Now connect the secondaries in SERIES and measure the ac voltage. If it is 36, we have a BOOST connection. If it is only 12, we have a BUCKING connection.

One of the windings should be reversed to get 36 volts.

If the load carrying ability of any surplus transformer is not known, let it run at no load on the bench for an hour and check the operating temperature. A hand "feel" test is usually sufficient, but in case of doubt. use a thermometer. Now, connect the maximum load and allow it to run an hour or so and check the operating temperature again. Use a power resistor for the load. Make this check for overheating before you put the transformers to work in equipment, and you will have no overheating troubles after the equipment is put to use, assuming of course that you have calcu-

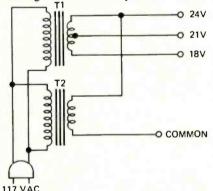

T1 – 6 VOLT FILAMENT TRANSFORMER T2 – 24 VOLT POWER TRANSFORMER

FIG. 2—THE FIG. 1 TRANSFORMERS can also be hooked up to give 18, 21 and 24 volts, simply by using a bucking connection.

lated your maximum load and have checked out the transformer at that load or a slightly greater one just to make sure it will not be overheated. (In a typical transformer, the case or core temperature should not rise more than 20—30°C above ambient at full load. Large transformers have a tendency to run hotter than small ones. —Editor)

The bucking connection

Suppose we need 18 volts and all

we can find is a 24-volt and a 6-volt transformer. Fig. 2 shows a BUCK-ING connection that will give the required 18-volt output. If the 6-volt transformer is center-tapped, we will also have 21 volts available. Now we have 18, 21, and 24 volts.

Fig. 3 shows how we can get 3, 6, 9, and 12 volts from two 6-volt center-tapped filament transformers with their primaries in parallel and secondaries in series. This combination is very useful for low-voltage solid-state

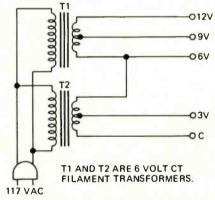


FIG. 3—ADJUSTABLE-VOLTAGE UNIT, using two center-tapped 6-volt transformers.

power supplies, and nobody has much use for a 6-volt filament transformer. You usually need at least 9 volts for transistorized equipment.

Fig. 4 shows two transformers connected in parallel for double the current (VA) output rating. Normally, if both transformers are identical, this parallel connection gives no trouble, but always check for overheating by allowing the transformers to run for an hour or so with no load, and be sure windings are properly phased—you can tell in a hurry—if they are not, fire will fly!

Identifying unknown transformers

Most transformer leads are coded according to EIA standards, as shown in the table. To check them, simply

TRANSFORMER LEAD IDENTIFICATION

(EIA code for power transformers)

Black, Black
Red, Red
High Voltage
Red with tracer
Yellow
Green, Green
Green with tracer

Black, Black
High Voltage
Center tap
5-volt rectifier
Filament winding
Center tap

(Where there is more than one filament winding, the second one may be brown, the third gray. Center taps are same color as winding, with yellow tracer. Rectifier filament center tap is yellow with green tracer.)

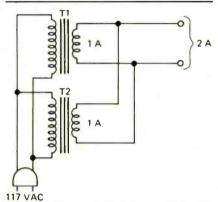


FIG. 4—A CURRENT-BOOSTING HOOKUP. Identical transformers give the best results.

connect the power line and measure the voltages. Some prefer to hook the line to the high-voltage first, to avoid fireworks if a winding (other than the high-voltage) is shorted.

For transformers that do not use a standard color code: You can usually identify windings by making a careful resistance check. The high-voltage windings will have the highest resistance. The reading to the center tap should be approximately the same on both sides. It should not be exactly the same because as the winding progresses it takes more wire to complete each turn and outer layers will contain more wire but the same number of turns. This means more resistance on the outer side of the winding and can be used to identify inner and outer winding layers.

The ac primary winding will measure out at some intermediate value. The heater and rectifier windings have very little resistance and are best identified by actual measurement with an ac voltmeter, after connecting the primary to the power line.

In case of doubt, and as a safety precaution, always connect the highest resistance winding to the power line first. Check the voltages across all other windings before trying another primary connection. THIS IS IMPORTANT. Connecting a 6.3-volt heater winding to the power line CAN BE HAZARDOUS—VERY HIGH VOLTAGE will be generated in the transformer primary.

SERVICING MATV


(continued from page 43)

The cure of overload on a singlechannel amplifier is to use a pad to decrease signal input and/or adjust the gain control for reduced output. For a broadband amplifier, careful balancing of each sound and picture carrier is called for. You may have to use a frequency splitter in front of the amplifier to adjust input channels individually.

If an individual TV receiver connected to an MATV system gets too much signal, it can be overloaded. Sets with tube-type front ends are quite tolerant of strong signals, but solid-state TV sets may overload with 10,000 µV (20 dBmV) or less. The answer to this problem is to increase tap-off isolation.

Dynamic window

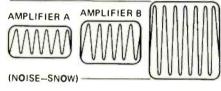Every piece of active MATV equipment can be thought of as having a "dynamic window," as illustrated in Fig. 4. The bottom of the window is (OVERLOAD-DISTORTION) AMPLIFIER C



V: 80X V: 100X V: 200X U: 25X U: 50X U: 125X FIG. 4—THE DYNAMIC WINDOW of three different amplifiers is shown. A wide dynamic window is an important consideration in purchasing an amplifier.

the least amount of signal the device can accept and still deliver a reasonably good picture. We define "reasonably good as a 30-dB signal-to-noise ratio, which is equivalent to a passable picture by the Television Allocation Study Organization (TASO) standards. The top of the window is the maximum signal the unit can accept before it produces perceptible cross modulation.

The concept of dynamic window is especially important in home MATV amplifiers and amplified couplers. Units meant for large systems usually have a large dynamic window, but the window in many home units is pitifully small. The only cure for this type of problem is to replace the amplifier with a unit that can accept a larger range of input signals.

Troubleshooting older systems

Troubleshooting an MATV system is analogous to troubleshooting a TV set. You have to isolate the problem and then solve it. Isolating MATV problems is a lot easier than isolating TV troubles, however. For one thing, the circuits are less complicated and

don't interact. For another, you can easily disconnect parts of the system without affecting the operation of the other part. This enables you to divide and conquer—to isolate the problem quickly by the process of elimination.

Every good MATV installer should make "as built" drawings. These drawings should show the entire system, with input and output signal levels at all channels noted for each piece of equipment. This is a tremendous servicing tool. If you have good "as built" drawings, all you have to do is compare the levels with what you read on your field-strength meter. Any discrepencies will pinpoint the trouble.

If you don't have "as built" drawings, troubleshooting is still not difficult. Start at the antennas, checking signals on the field-strength meter as well as the portable TV set. A good picture going into an amplifier and a poor picture coming out leaves little doubt as to the cause of the trouble.

Distribution system troubles are a little harder to track down. For one thing, you have to disturb tenants or guests to get at the tap-offs. For another, checking many tap-offs takes a lot of time and legwork. Therefore, you should try to narrow the trouble down to as small an area as possible before you leave the head end. Suppose you have eight trunklines and trouble is reported on only one of the lines. Disconnect the line from the splitter at the head end. Then, use your ohmmeter to measure from the center conductor to the shield of the troublesome trunkline.

Before you can evaluate your readings, you have to know something about the tap-offs and splitters used in the system. Use your ohmmeter to check one unit of each type. Splitters and directional couplers usually appear to be shorted to ground, as far as the ohmmeter is concerned. If this type of unit is in your system, it can set you off on a wild short chase unless you are aware of it. In most systems, you should read about 75 to 100 ohms between the center conductor and the shield of the trunk cable. If you read a short or an open, you know you have spotted a trouble.

If you read an open, split the branch in half. Go to a tap-off in the middle of the line. Remove the tap-off and disconnect the output cable. Check again for proper resistance between center conductor and ground. If you get in the neighborhood of 100 ohms, your trouble is between the splitter and the tap-off you are checking. If not, it is between the tap-off and the terminator at the end of the line. Continue to split the trunkline in half until you find the trouble.

(continued on page 90)

What does it really mean?

You can't get the most out of your tape recorder without optimizing the equalization and bias level.

This article explains bias and equalization

by LEN FELDMAN
CONTRIBUTING HIGH FIDELITY
EDITOR

THE INCREASING POPULARITY OF TAPE recorders as a high-fidelity program source is not difficult to understand. Unlike other program sources, such as FM radio and phonograph records, tape offers the audio enthusiast the sense of involvement that makes the hobby all the more worthwhile. In addition, today's open-reel tape decks offer performance which is often indistinguishable from that afforded by professional studio tape recorders, and the once looked down upon cassette deck has been transformed from a portable "dictating machine" to an acceptable high-fidelity component. With such a wide interest in tape and tape recording, it is surprising how little most users of these products know regarding their operation. Unlike purely electronic products, such as amplifiers, tuners or receivers, tape decks involve an interrelation of mechanical, magnetic and electronic sys-

Today, most audiophiles have a fairly clear understanding of what phonograph equalization is all about. The amplifier or preamplifier spec sheet has drummed home the idea that the closer a phono preamp adheres to the RIAA playback curve, (shown in Fig. 1) the better the product. These

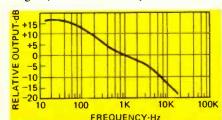


FIG. 1—STANDARD RIAA PLAYBACK CURVE used for phono disc reproduction.

reached where the tape itself begins same people often ask me why the tape industry cannot "get together on a single, standard equalization" for tape recording and playback. Why, in fact, are better recorders (both openreel and cassette) equipped with multiple equalization settings? And what about those multiple bias settings on some of those same recorders?

Equalization

To begin with, a tape recorder does not reproduce signals with a flat frequency response. A tape playback head, being sensitive to the rate of change of a magnetic field, produces a greater output as frequencies increase since at higher frequencies, alternations of magnetic field become more rapid. Thus the output voltage increases with frequency as illustrated in Fig. 2. Eventually, the level ceases

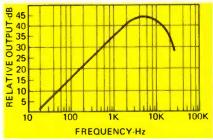


FIG. 2—TYPICAL TAPE PLAYBACK HEAD OUTPUT with constant-level signal recorded on tape.

to increase with frequency and, in fact, begins to drop off fairly rapidly. Two factors are responsible for this drop off. As the frequency to be recorded increases, the wavelength decreases. In addition, as magnetic variations increase in intensity, a point is

to be saturated—it cannot accept greater and greater amounts of magnetization—and level begins to drop. The second of these factors is, to some degree, governed by the formulation of the tape itself, while the first is governed primarily by tape speed and the gap length of the tape head. Fig. 3 illustrates how the linearly increasing voltage output varies with

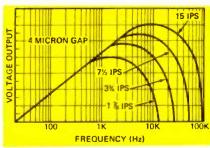


FIG. 3—LINEAR INCREASE IN OUTPUT VOLTAGE extends to higher frequencies at increased tape speed.


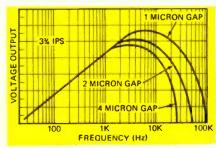


FIG. 4—REDUCING PLAYBACK HEAD GAP while maintaining constant tape speed will extend the high-frequency response.

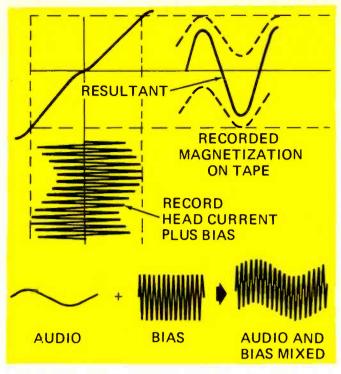popular tape speeds for a given tape head gap (4 microns) while Fig. 4 shows how linear output can be extended to higher frequencies at a given tape speed by decreasing the tape head gap.





Obviously, none of the curves of Figs. 2, 3 or 4 would be acceptable for high-fidelity reproduction. The process used to restore "flat" response in tape recording and playback is called *equalization*. Equalization can be applied both during the record operation and during playback. Referring again to Fig. 2, if during playback the response curve of Fig. 5 is used, the resulting overall record/playback response will be as shown in Fig. 6.

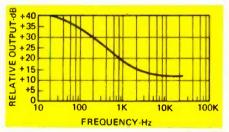


FIG. 5—TYPICAL PLAYBACK EQUALIZATION in tape deck preamp circuitry.

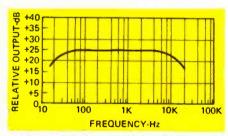


FIG. 6—COMBINING RECORDING RE-SPONSE (Fig. 2) with equalized playback response (Fig. 5) results in overall record/ play response shown.

Note that there is still some roll-off at low and high frequencies.

Record equalization

In order to realize optimum highfrequency response, equalization is used in the record process, too. Record equalization can offset high-frequency roll-off to some degree, but if too much high-frequency pre-emphasis is used, the tape will become saturated at lower nominal recording levels and distortion and roll-off will occur anyway. Playback equalization can in theory, be used to extend high-frequency response but if highs are boosted too much during playback, increased tape hiss will be heard. The record and playback curves must therefore strike a balance to minimize problems of each.

In professional recording work, standards of record and playback equalization were developed by the NAB (National Association of Broadcasters), and the German standards organization known as DIN. These standardized curves are plotted in Fig. 7. The DIN or CCIR curves tend to

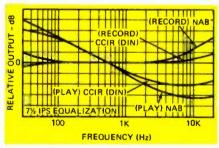


FIG. 7—RECORD AND PLAYBACK equalization standards adopted by the NAB and European standards organizations.

strive for higher frequency response. By using a bit less record equalization, tape saturation is not reached as soon. But this requires more playback equalization which results in higher tape hiss. In the consumer audio field, manufacturers often change their equalization curves to offer "extended response" which seems to be the sole criterion by which many audiophiles judge tape deck performance. With a given tape speed and a given head gap, however, such "improvements" are invariably accompanied by either reduced level of recordings or increased tape hiss or combinations of both.

In general, frequency response curves for tape equipment are plotted not at 0 db level on the record level meters but at a level of -10 db or even -20 dB in the case of open-reel machines and at -20 dB or even -30 dB in the case of slower-speed cassette decks (which require greater high-frequency boosting during recording to compensate for reduced tape speed.)

Some years ago, the industry introduced Chromium Dioxide tape. It delivers somewhat higher frequency before saturation drop-off occurs. This characteristic produces a slight increase in high-frequency response or for improved signal-to-noise ratio (reduced tape hiss) or a combination of both.

Today, there are a great many different tape formulations, each of which requires a different record and playback equalization. Multiple switch positions are provided on many openreel and cassette decks which adjust equalization to suit the various popular formulations. Actually, professional machines used in recording studios are often adjusted to work best with one and only one brand and type of recording tape. Conscientious studio engineers may even re-calibrate or adjust equalization when different pro-

duction batches of the same brand and type of tape are used. The very least that a home user can do to ensure optimum results with an openreel recorder or better cassette unit is to follow the manufacturer's recommended equalization settings for the type of tape being used. Most owner's manuals list a variety of tapes and their appropriate settings for machines equipped with more than one equalization switch position.

Bias

Assuming that both recording and playback equalization have been optimized with respect to each other in a given recorder, one would expect that the magnetic pattern recorded on the tape will now correspond exactly to the strength of magnetic fields generated by the record head. Unfortunately, magnetic tape is basically a nonlinear medium. The magnetic pattern left on the tape is not always proportional to the instantaneous current in the recording head. The greatest amount of non-linearity occurs as the audio waveform passes through the zero axis, as shown diagramatically in

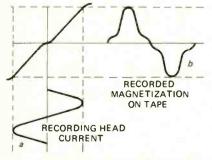


FIG. 8—DISTORTION caused by non-linear magnetization characteristics of tape is similar to crossover distortion encountered in improperly biased Class B audio amplifiers.

Fig. 8. Hysteresis effect, a sort of magnetic inertia, acts upon the particle as magnetization begins. After this initial reaction, the particle responds linearly to the applied field. If nothing were done to offset this effect, a sine wave recorded onto tape as shown in Fig. 8-a would take on the appearance of Fig. 8-b when played back. Obviously, this is a form of distortion and, what is worse, it is a very annoying form of distortion containing high order harmonics. Furthermore, it is a form of distortion that actually is more disturbing at low recording levels than at high signal levels, since the distortion components remain constant and therefore constitute a higher percentage of the total signal at lower recording levels.

High-frequency bias current is used in all modern recorders to overcome this problem. Generally, this superaudible frequency should be at least four times the frequency of the highest audio signal to be recorded, but open-reel recorders will often employ bias frequencies of the order of 100 kHz to 125 kHz while modern high-quality cassette units use frequencies in the range from about 80 kHz to 105 kHz.

The combined action of the desired audio signal and inaudible bias signal can best be understood by referring to Fig. 9. The bias current magnetizes

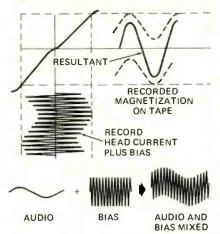


FIG. 9—COMBINING high-frequency bias with desired audio signals during recording shifts audio magnetization of tape to its linear undistorted region.

the oxide particles through the nonlinear segment of the curve. Then the audio signal actually demagnetizes the particles to a level which is proportional to the signal.

Bias level changes will affect distortion level. Generally, as bias level is increased (starting from no bias) distortion will decrease rapidly at first. With further increase of bias level, distortion decreases more slowly. If bias is increased much beyond this desired point, high-frequency response will get poorer. Ideally, bias should be set as high as possible without causing severe high-frequency losses in the recorded tape. The action of bias in relation to distortion and high frequency response is shown in the gen-

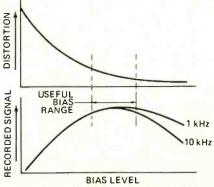


FIG. 10—INCREASING BIAS LEVEL reduces distortion, but overbiasing will reduce high-frequency response.

eral curves of Fig. 10.

Audiophiles who learn of bias for the first time often wonder why the high-frequency bias signal is not recovered as part of the playback signal. In fact, the bias signal does record a series of magnetic fields of its own, but their wavelength is so short that no playback head, however narrow its gap, can significantly respond to these high frequencies. Some small high-frequency energy is picked up by the playback head (however many dB down it may be compared to desired audio signals) and is one of the reasons why higher than necessary frequencies are now used for bias.

Much home recording is done of stereo FM programs and stereo composite signals contain varying amounts of 38-kHz signals in their output. If, for example, 45 kHz were used as a bias frequency in tape decks, a distinct 7-kHz "whistle" might be heard when playing back such recorded stereo FM programs, resulting from the beat or difference between the two otherwise inaudible high-frequency signals.

Since oxide formulations vary greatly from one tape type to another, each requires a different bias level. For this (continued on page 81)

R-E's Substitution guide for replacement transistors

PART XXV by ROBERT & ELIZABETH SCOTT

ARCH—Indicates the Archer brand of semiconductors sold only by Radio Shack and Allied Radio stores. Allied Radio Shack, 2725 W. 7th St., Ft. Worth, Texas 76107

DM—D. M. Semiconductor Co., P.O. Box 131, Melrose, Mass. 02176

G-E—General Electric Co., Tube Product Div., Owensboro, Ky. 42301

ICC—International Components, 10 Daniel
Street, Farmingdale, N.Y. 11735
IR—International Rectifier. Semiconductor

IR—International Rectifier, Semiconductor Div., 233 Kansas St., El Segundo, Calif. 90245

MAL—Mallory Distributor Products Co., 4760 Kentucky Ave., Indianapolis, Ind. 46241

MOT—Motorola Semiconductors, Box 2963, Phoenix, Ariz. 85036

RCA—RCA Electronic Components, Harrison, N.J. 07029

SPR—Sprague Products Co., 65 Marshall St., North Adams, Mass. 01247

SYL—Sylvania Electric Corp., 100 1st Ave., Waltham, Mass. 02154

WOR—Workman Electronic Products, Inc., Box 3828, Sarasota, Fla. 33578

ZEN—Zenith Sales Co., 5600 W. Jarvis Ave., Chicago, III. 60648

Radio-Electronics has done its utmost to insure that the listings in this directory are as accurate and reliable as possible; however, no responsibility is assumed by Radio-Electronics for its use. We have used the latest manufacturers material available to us and have asked each manufacturer covered in the listing to check its accuracy. Where we have been supplied with corrections, we have updated the listing to include them. The first part of this Guide appeared in March 1973.

	ARCH	DM	G-E	ICC	IR	MAL	MOT	RCA	SPR	SYL	WOR	ZEN
2N6012	NA	TS-3001 TS-3031	NA	ICC-S3001	NA	PTC 136 NA	HEP-S3001 HEP-S3031	NA	NA RT-115	ECG 153 NA	NA NA	NA NA
2N6013 2N6014	NA NA	TS-3031	GE-63	ICC-S3031 ICC-S3020	NA NA	NA	HEP-S3020	NA NA	NA	NA	NA	NA
2N6015 2N6016	NA NA	TS-3031 TS-3001	GE-67 NA	ICC-S3031 ICC-S3001	NA NA	PTC 127 NA	HEP-S3031 HEP-S3001	NA NA	RT-115 NA	na NA	NA:	na NA
2N6017	NA	TS-3031	NA	ICC-S3031	NA		HEP-S3031	NA	RT-115	NA	NA	NA
2N6021	NA	TS-5006	NA	ICC-S5006	TR-77	NA	HEP-S5006	NA	RT-149	ECG 153	WEP-246 WEP-246	NA NA
2N6022 2N6023	NA NA	TS-5006 TS-5007	NA GE-69	ICC-S5006 ICC-S5007	TR-77	NA PTC 157	HEP-S5006 HEP-S5007	NA NA	RT-149 NA	ECG 153 ECG 153	WEP-246	ZEN 211
2N6024	NA	TS-5007	GE-69	ICC-S5007	TR-77	PTC 157		NA	RT-153	ECG 153	WEP-246	ZEN 211
2N6025 2N6026	NA NA	TS-5006 TS-5006	GE-69 GE-69	ICC-S5006 ICC-S5006	NA TR-77		HEP-S5006 HEP-S5006	NA NA	RT-149 RT-149	ECG 180 ECG 153	NA WEP-246	ZEN 211 NA
2N6027	NA	NA	GE-X17	ICC-52	NA	NA	HEP-52	NA	NA	ECG 6402	NA	NA
2N6067 2N6068	NA NA	T-52 SR-1721	NA NA	NA ICC-R1721	NA NA	PTC 103 NA	NA HEP-R1721	NA NA	NA NA	NA ECG 5600	NA NA	NA NA
2N6069	NA	SR-1721	NA	ICC-R1721	NA	NA	HEP-R1721	NA	NA	ECG 5601	NA	NA
2N6070 2n6071	NA NA	SR-1722 SR-1723	NA NA	ICC-R1722 ICC-R1723	NA NA	NA NA	HEP-R1722 HEP-R1723	NA NA	NA NA	ECG 5602 ECG 5603	NA NA	NA NA
2N6072	NA	SR-1725	NA	ICC-R1725	NA	NA	HEP-R1725	NA	NA	ECG 5604	NA	NA
2N6073	NA	SR-1725	NA	ICC-R1725	NA	NA	HEP-R1725	NA	NA	ECG 5605 ECG 5606	NA NA	NA NA
2N6074 2N6075	NA NA	NA NA	NA NA	NA NA	NA NA	NA NA	NA NA	NA NA	NA NA	ECG 5607	NA	NA
2N6076 2N6080	NA NA	T-723 NA	GE-67 NA	ICC-723 ICC-S3005	NA NA	PTC 121 NA	HEP-723 HEP-S3005	NA NA	NA NA	NA NA	NA NA	ZEN 111 NA
2N6081	NA	NA	NA	ICC-S3005	NA	NA	HEP-S3006	NA	NA	NA	NA	NA
2N6082	NA	NA	NA	ICC-S3007	NA	NA	HEP-S3007	NA	NA	NA	NA	NA
2N6083 2N6084	NA NA	NA NA	NA NA	ICC-S3007 ICC-S3009	NA NA	NA NA	HEP-S3007 HEP-S3009	NA NA	NA NA	NA NA	NA NA	NA NA
2N6085* 2N6086*	NA NA	T-729 T-728	NA	ICC-729	NA	NA	HEP-729	NA NA	NA RT-109	NA NA	NA NA	ZEN 115 ZEN 114
2N6087*	NA NA	T-729	NA NA	ICC-728 ICC-729	NA NA	NA PTC 139	HEP-728 HEP-729	NA NA	RT-109	NA NA	NA NA	ZEN 115
2N6088*	NA	T-728	NA	ICC-728	NA	PTC 139	HEP-728	NA	RT-109	NA	NA	ZEN 114
2N6089°	NA NA	T-729 T-728	NA NA	ICC-729 ICC-728	NA NA	PTC 139 PTC 139	HEP-729 HEP-728	NA NA	RT-109 RT-109	NA NA	NA NA	ZEN 115 ZEN 114
2N6091°	NA	T-729	NA	ICC-729	NA	PTC 139	HEP-729	NA	RT-109	NA	NA	ZEN 115
2N6092* 2N6099	NA NA	TS-0007 TS-5001	NA NA	ICC-S0007 ICC-S5001	NA NA	NA NA	HEP-S0007 HEP-S5001	NA SK 3534	RT-109 NA	NA NA	NA NA	NA ZEN 209
2N6101	NA	TS-5004	NA	ICC-S5004	NA	NA	HEP-S5004	SK 3534	NA	NA	NA	NA
2N6105 2N6106	NA NA	NA TS-5005	NA NA	ICC-S0007 ICC-S5005	NA NA	NA NA	HEP-S0007 HEP-S5005	NA SK 3083	NA RT-153	NA ECG 197	NA WEP-246	NA NA
2N6107	NA	TS-5005	NA	ICC-S5005	NA	NA	HEP-5005	SK 3083	RT-153	ECG 197	WEP-246	NA
2N6108 2N6109	NA NA	TS-5002 TS-5002	NA NA	ICC-S5002 ICC-S5002	NA NA	NA NA	HEP-S5002 HEP-S5002	SK 3083 SK 3083	RT-153 RT-153	ECG 197 ECG 197	WEP-246 WEP-246	NA NA
2N6110	NA	TS-5002	NA	ICC-S5002	NA	PTC 157	HEP-S5002	SK 3084	RT-153	ECG 197	WEP-246	NA
2N6111 2N6112	NA NA	TS-5002 T-736	NA GE-62	ICC-S5002	NA NA	PTC 157 PTC 121	HEP-S5002 HEP-736	SK 3084 NA	RT-153 RT-109	ECG 197 NA	WEP-246 WEP-245	NA ZEN 120
2N6121	NA	T-701	NA	ICC-701	TR-76	NA	HEP-701	NA	NA	ECG 152	WEP-245	NA
2N6122 2N6123	NA NA	TS-5003 TS-5000	NA NA	ICC-S5003 ICC-S5000	TR-76 NA		HEP-S5003 HEP-S5000	NA NA	RT-154 RT-150	ECG 152 NA	WEP-245 WEP-245	ZEN 210 NA
2N6124	NA	T-700	NA	ICC-700	TR-77	NA	HEP-700	NA	RT-155	ECG 153	WEP-246	NA
2N6125 2N6126	NA NA	TS-5007 TS-5006	NA NA	ICC-S5007 ICC-S5006	TR-77 TR-77	NA NA	HEP-S5007 HEP-S5006	NA NA	RT-155 RT-155	ECG 153 ECG 153	WEP-246 WEP-246	ZEN 211 NA
2N6129	NA	TS-5001	NA	ICC-S5001	NA	PTC 137	HEP-S5001	NA	NA	NA	NA	ZEN 209
2N6130 2N6131	. NA NA	TS-5001 TS-5004	NA NA	ICC-S5001 ICC-S5004	NA NA	PTC 154 PTC 154	HEP-S5001 HEP-S5004	NA NA	NA NA	NA NA	NA NA	ZEN 209 NA
2N6132	NA	TS-5008	NA	ICC-S5008	NA	NA	HEP-S5008	NA	RT-153	ECG 197	WEP-246	NA
2N6133 2N6134	NA NA	TS-5002 TS-5005	NA NA	ICC-S5002 ICC-S5005	NA NA	NA PTC 143	HEP-S5002 HEP-S5005	NA NA	RT-153 RT-153	ECG 197 ECG 197	WEP-246 WEP-246	NA NA
2N6139	NA	SR-1751	NA	ICC-R1751	NA	NA	HEP-R1751	NA	NA	ECG 5663	NA	NA
2N6140 2N6141	NA NA	NA NA	NA NA	NA NA	NA NA	NA NA	NA NA	NA NA	NA NA	ECG 5665 ECG 5667	NA NA	NA NA
2N6146	NA	NA	NA	NA	NA	NA	NA	NA	NA	ECG 5675	NA	NA
2N6151 2N6152	NA NA	NA NA	NA NA	NA NA	NA NA	NA NA	NA NA	NA NA	NA NA	ECG 5614 ECG 5616	NA NA	NA NA
2N6153	NA	NA	NA	NA	NA	NA NA	NA	NA	NA	ECG 5618	NA	NA
2N6154	NA	NA NA	NA	NA	NA	NA	NA	NA	NA	ECG 5624	NA	NA
2N6155 2N6156	NA NA	NA NA	NA NA	NA NA	NA NA	NA NA	NA NA	NA NA	NA NA	ECG 5624 ECG 5628	NA NA	NA NA
2N6160 2N6161	NA NA	SR-1783 SR-1785	NA NA	ICC-R1783 ICC-R1785	NA NA	NA NA	HEP-R1783 HEP-R1785	NA NA	NA NA	ECG 5693 ECG 5682	NA NA	NA NA
2N6162	NA	NA	NA	NA NA	NA	NA.	NA NA	NA	NA	ECG 5697	NA	NA
2N6165 2N6167	NA	NA	NA	NA	NA	NA	NA	NA ·	NA	ECG 5697	NA	NA
2N6169	NA NA	NA NA	NA NA	NA NA	NA NA	NA NA	NA NA	NA NA	NA NA	ECG 5673 ECG 5675	NA NA	NA NA
2N6175	NA	T-244	NA	ICC-244	NA	NA	HEP-244	SK 3104	RT-135	NA	NA	ZEN 201
2N6176 2N6177	NA NA	T-244 NA	NA NA	ICC-244 NA	NA NA	NA NA	HEP-244 NA	SK 3103 SK 3103	RT-135 RT-131	NA NA	NA NA	ZEN 201 NA
2N6178	NA	TS-5000	NA	ICC-S5000	NA	NA	HEP-S5000	SK 3024	RT-150	NA	NA	NA
2N6179 2N6180	NA NA	TS-5000 TS-5006	NA NA	ICC-S5000 ICC-S5006	NA NA	NA NA	HEP-S5000 HEP-S5006	SK 3024 SK 3025	RT-150 RT-149	NA NA	NA NA	NA NA
											/to be	oontinued)

LEADER Automatic Dual Channel/Dual Trace 5" Scope/Vectorscope



- Automatic Trigger Automatic Horizontal Sweep
 - Automatic Vertical Input

Automatic operation is the key and virtually error free accuracy is your bonus with this unique 5" Dual Trace Scope. The advanced design even lets you read between the ranges in any position, as easily as you can with analog VTVM's or VOM's. High reliability PC boards assure long term dependability while a high intensity CRT delivers excellent contrast. It features: separate or simultaneous sweep display, Ch 1 & 2 - alternate, chopped, auto/norm trigger; 10MHz b'width;

10mVp-p/cm to 20Vp-p/cm vert'l sensitivity in 11 calib. steps; 0.5μ S/cm to 0.2S/cm sweep range, 18 steps calib.; X5 mag.; XY and vectorscope displays. Compact, lightweight, economical.

\$569 95 MODEL LBO-506

Complete with probes, terminal adapters, test leads.

LEADER "Put Us To The Test"

Instruments Corp. 151 Dupont St., Plainview, L.I., N.Y. 11803 (516) 822-9300

RE's Service Clinic

Those new HEW circuits

Redundancy in the high-voltage supply

by JACK DARR SERVICE EDITOR

This column is for your service problems—TV, radio, audio or general and industrial electronics. We answer all questions individually by mail, free of charge and the more interesting ones will be printed here.

If you're really stuck, write us. We'll do our best to help you. Don't forget to enclose a stamped, self-addressed envelope. If return postage is not included, we cannot process your question. Write: Service Editor, Radio-Electronics, 200 Park Ave. South, N.Y. 10003.

IF WE WANT TO ANALYZE TROUBLE IN A circuit, we've got to know what's in it! If "something new has been added" that we don't know about, we're in deep trouble. This is specially true if the added circuits duplicate the functions of circuits that are already in there.

In quite a few color TV sets, we're already in that shape. Any set built in 1971 or later may have extra circuits that many of us don't know about. These were added to comply with HEW (Department of Health, Education and Welfare) regulations. The idea is to control the high voltage, so that it cannot rise above the rated level.

I don't know what these will do for our health, the effect on our welfare is yet to be determined, but if you don't know they're in there, they can be highly educational! (Voice of Experience!)

Practically all color TV sets use some kind of high-voltage regulator. However, the new circuits are added to existing ones, They're in the form of "redundant regulators" (which translates into "two circuits doing the same thing" or a sort of belt-and-suspenders action.) In some, you'll find as many as three separate regulator or control circuits, all doing, in effect, the same work.

The operation of these circuits isn't complicated, any more than the original high-voltage regulators. However, if you don't know they're there, they can lead you far from the correct conclusions when trying to diagnose troubles! So, let's look at a few typical redundant-


regulator circuits and see how they work.

All of them are basically "hold-down". If he high voltage rises above the correct level, they go into action. Some are simple clamp types; some are designed to kill the high voltage entirely, if it goes up. Still others are designed to disable some other circuit, to prevent the set from operating; the video, sync, and in one case the horizontal oscillator.

How the circuits work

The Sylvania D-12 chassis would be a good one to start with. At first glance, this looks like our old friend the 6BK4 shunt regulator; it is, but with differences. Figure 1 shows the important parts. Note the diode in the cathode circuit of the 6BK4. This is called the "Regulator Limiter" SC-410. In normal operation, the 6BK4 conducts through this diode. So, the 6BK4 cathode, and the diode anode, will be about +340 volts. This is fed back to the 6LR6 control-grid circuit, through R416, 5.6 megohms, and R436, 1.0 megohms. This positive voltage would tend to turn on the 6LR6.

However, there is additional circuitry: Diode SC-404, and R412 are also connected to the bottom of the grid resistor R436. A high pulse voltage from the flyback is fed to the diode anode. This develops a very high negative voltage, to buck out the positive voltage. So, the 6LR6 grid develops its normal bias by grid-leak action, from the drive signal. The result of all this is a grid voltage of about -45 volts.

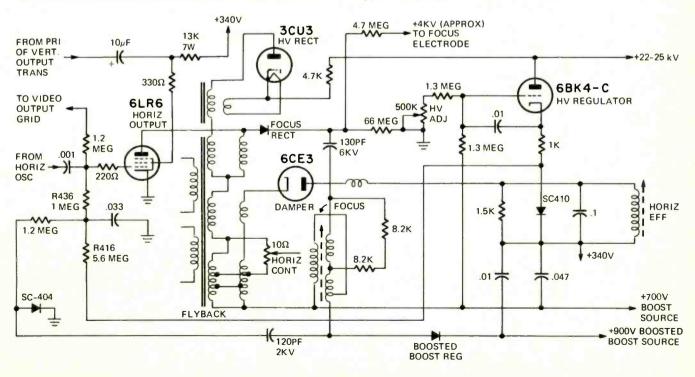

EXAR

IC'S AND KITS
NOW AVAILABLE FROM:
JAMES ELECTRONICS

FUNCTION GENERATOR KIT

Introductory Offer



The Function Generator...Kit features sine, triangle and square wave; THD 0.5% typ.; AM/FM capability.

XR-2206KA

Includes monolithic function generator IC, PC board, and assembly instruction manual.

\$19.95

XR-2206KB

Same as XR-2206KA above and includes external components for PC board.

\$29.95


MONOLITHIC IC'S

TIMERS	
XR-555CP Monolithic Timer \$	1.10
XR-320P Precision Timer	1.55
XR-556CP Dual-555 Timer	1.85
XR-2556CP Dual Timing Circuit	3.20
XR-2240CP Programmable Counter/	
Timer	4.80
PHASE LOCKED LOOPS	
XR-210 FSK Demodulator !	5.20
XR-215 High Frequency PLL	6.60
	1.95
XR-567CT Tone Decoder (TO-5)	1.70
STEREO DECODERS	
XR-1310P PLL Stereo Decoder :	3.20
XR-1310EP PLL Stereo Decoder	3.20
XR-1800P PLL Stereo Decoder	3.20
WAVEFORM GENERATORS	
XR-205 Waveform Generator 8	8.40
XR-2206CP Monolithic Function	
Generator	5.50
XR-2207CP Voltage-Controlled	
Oscillator	3.85
OTHER EXAR IC'S	
XR-T468CN Dual ±15V Tracking	
	3.85
XR-1488N Quad Line Driver	5.80
XR-1489AN Quad Line Receiver	4.80
XR-2208CP Operational Multiplier	5.20

Satisfaction Guaranteed. \$5.00 Min. Order—1st Class Mail No Charge/ California Residents Add 6% Sales Tax

JAMES

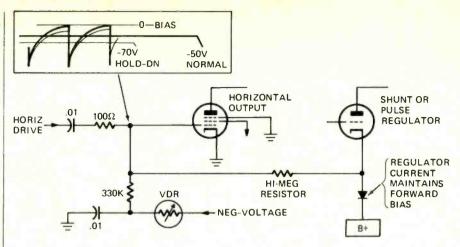P.O. BOX 822, BELMONT, CA. 94002 PHONE ORDERS — (415) 592-8097



Now what happens if the 6BK4 tube fails? It stops conducting. (I love those nice obvious statements. Nobody can contradict me). No current flow, SC-410 becomes reversed-biased and the 6BK4 cathode goes far more negative. This negative shift is fed to the 6LR6 through the resistor network, cutting down the output, high voltage, etc. In the original circuit, of course, a dead 6BK4 would let the high voltage jump to about 32-33 kV. The belt and suspenders action of the other negative voltage, from SC-404, is also shoved in there to make sure that the tube is cut off.

The negative voltage from SC-404 is also fed to the grid of the video amplifier tube. It cuts *this* tube off as well. Its plate voltage rises, the picture-tube

cathodes go far more positive (same as negative grid voltage) and the beam current is held down, reducing brightness.

The end result of all these actions is an old symptom—narrow raster, about an inch short on each side, and a severe loss of brightness. If you run into one of these, you'll probably try a new horizontal output tube first, just as I did. If this doesnt help, even though all of the symptoms seem to be pointing to it, don't pull the chassis—not yet.

Step 1: Read the grid voltage on the 6LR6. If this is up to about -95 volts, try a new 6BK4 tube. High-voltage will drop to about 17 kV, by the way. If the new regulator tube doesn't help, check both diodes, SC-410 and SC-404. Failure of either one of these (short or open!) will cause the trouble. SC-410, if it's open, will cause the same symptoms as a dead 6BK4, and so on.

RCA uses a very similar circuit in their CTC 38 chassis and others. Figure 2 shows the basic circuit. The bucking voltage from the high-voltage regulator cathode (either the shunt, as with 6BK4, or "pulse", with 6HS5 etc.). Once again, this voltage goes to the grid return of the horizontal output tube.

The positive voltage is again bucked out by a negative voltage developed from a flyback pulse. This time, a VDR is used instead of a diode. In this set, the symptoms are the same as before. Narrow, dim raster, and high negative bias on the horizontal output tube.

HYBRID SEMICONDUCTORS & ELECTRONICS INC.

P.O. Box 103 Fresh Meadows, N.Y. 11365

A new dynamic company offering two important features to electronic technicians, radio amateurs, experimenters, and hobbyists.

- 1. A source for replacement semiconductor components.
- 2. Free application assistance in replacing semiconductor components. (Describe problem clearly and enclose stamped, self-addressed envelope.)

Send for our catalog listing semi-conductor cross references with application tips and notes relating to common problems in semiconductor component selection.

reader questions


DOUBLE DOTS

I get two dots, or two lines, on my PACO S-50 scope, with no signal input. What's wrong? — A.D., Harvey, La.

You're obviously getting some vertical deflection that you should not be getting. This could be due to an unbalance in the vertical output tubes; perhaps a bad peaking coil in one of them. Check these tubes for any sign of heater-cathode leakage.

(continued on page 78)

CT-1024 TERMINAL SYSTEM

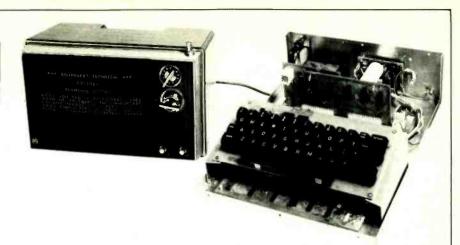

When we designed the CT-1024 we knew that there were many applications for an inexpensive TV display terminal system. Even so, we have been surprised at the many additional uses that have been suggested by our customer in the last four months since we introduced this kit.

The basic kit, consisting of the character generator, sync and timing circuits, cursor and 1024 byte memory gives you everything you need to put a sixteen line message on the screen of any TV monitor, or standard set with a video input jack added to it. Input information to the CT-1024 may be any ASCII coded source having TTL logic levels. Two pages of memory for a total of up to one thousand and twenty four characters may be stored at a time. The CT-1024 automatically switches from page one to page two and back when you reach the bottom of the screen. A manual page selector switch is also provided. The main board is 9½ x 12 inches. It has space provided to allow up to four accessory circuits to be plugged in. If you want a display for advertising, a teaching aid, or a communication system then our basis kit and a suitable power supply is all you will need.

CT-1 TERMINAL SYSTEM with

MEMORY KIT \$175.00 ppd Power supply kit to provide + 5 Volts @ 2.0 Amps and - 5 Volts, -12 Volts @ 100 Ma. required by the CT-1 basic display system.

CT-P POWER SUPPLY KIT\$15.50 ppd

A very nice convenience feature at a very reasonable cost is our manual cursor control plug-in circuit. The basic kit allows you to erase a frame and to bring the cursor to the upper left corner (home up). By adding this plug-in, you can get Up. Down, Left, Right, Erase to End of Line and Erase to End of Frame functions. These may be operated by pushbutton switches, or uncommitted keyswitches on your keyboard. Although not essential to terminal operation, these features can be very helpful in some applications.

CT-M MANUAL CURSOR CONTROL KIT.....\$11.50 ppd

If you plan to use your terminal with a telephone line modem, or any other system that requries a serial data output; you will need our serial interface (UART) plug-in circuit. This circuit converts the ASCII code from a parallel to a serial form and adds "Start" and "Stop" bits to each character. The standard transmission rate for this circuit is 110 Baud, but optional rates of 150, 300, 600 and 1200 Baud may be obtained by adding additional parts to the board. The output of this circuit is an RS-232 type interface and may be used to drive any type modem, or coupler system using this standard interface.

CT-S SERIAL INTERFACE (UART) KIT.....\$39.95 ppd

If you are using the CT-1024 as an 10 (input - output) device on your own computer system, you will probably want to connect it to the computer with a parallel interface system. A direct parallel interface allows for much faster data transmission and reception and is basically a simpler device than a serial interface system. Our parallel interface circuit contains the necessary tristate buffers to drive either a separate transmitt and receive bus system, or a bidirectional data bus system. TTL logic levels are standard on this interface. Switch selection of either full, or half duplex operation is provided. The terminal may write directly to the screen, or the computer may "echo" the message and write to the screen.

CT-L PARALLEL INTERFACE KIT.....\$22.95 ppd

We would be happy to send you a complete data package describing the CT-1024 and a achematic. If you want this additional information, circle our number shown below on your reader information service card. The CT-1024 kit has complete assembly instructions with parts location diagrams and stepby-step wiring instructions. If you would like to check the instruction manual before you purchase the kit, please return the coupon with \$1.00 and we will rush you the manual and the additional data mentioned above.

MAIL	THIS	COUPON	TODAY

_____ or Master Charge #__ ☐ Enclosed is \$____ or Bank Americard # _____ Card Expiration Date ___ ☐ CT-1024 Kit CT-M Cursor Control Kit ☐ CT-L Parallel Interface Kit ☐ CT-S Serial Interface Kit NAME ADDRESS_____ _STATE____ZIP__ CITY__


S1.00 Enclosed send manual and data package

Southwest Technical Products Corp., Box 32040, San Antonio, Texas 78284

77

RADIO-ELECTRONICS

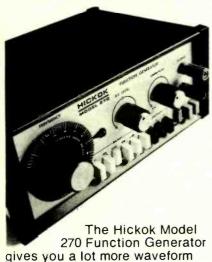A PRECISION WAVEFORM **GENERATOR** AT A **PRICE YOU** CAN AFFORD.



generating capability than you'd expect for its price. Puts stable, calibrated, high quality sine, square and triangle waveforms from 1 Hz

to 500 kHz at your fingertips.

- With external connections you can produce logic pulses, sweeps and ramps, AM and FM outputs, phase and frequency shift keying signals, tone bursts and more.
- Its an audio generator and much more.

Before you buy another function generator, check out the Hickok Model 270. Ask your Hickok distributor for full details or write us for our 4-page technical brochure.

\$166⁰⁰ HICKOK

the value innovator

INSTRUMENTATION & CONTROLS DIVISION THE HICKOK ELECTRICAL INSTRUMENT CO. 10514 Dupont Avenue • Cleveland, Ohio 44108 (216) 541-8060 • TWX: 810-421-8286

READER QUESTIONS

(continued from page 76)


Also. In this scope, you have "links" on the back of the chassis, which can be opened to get directly to the crt vertical deflection plates. In some scopes, these links have caused trouble by getting loose, corroded or dirty. Take them off, clean them, and retighten the screws securely.

PURPLE PICTURE

After replacing a bad picture tube in a Sears 7185, I have setup problems. I get a purple picture, mostly reddish, with all of the screen and drive controls turned off. Only way I can get anything near normal is to turn up only the green screen. I checked it on a test-jig, and got the same symptoms; they showed up in the old tube, too.

I'm enclosing a table of the dc voltages I found on the picture tube base. Any help will be appreciated. – J.S., Dallas, Tex.

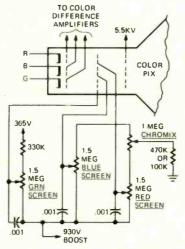I think I see the difficulty. Note that your screens are all far too high -950 to 1000 volts, with the control turned all the way off. With screen voltages this far above normal (about 740 to 800 volts) your picture tube cutoff will be away up, and you will lose control of the raster.



The diagram shows the screen control circuit of this one, which is a voltage divider between B+400 volts and B++950 volts. You obviously have the boost-boost voltage on these controls; it looks very much as if the circuit to B+ 400 volts is open. Check; you should be able to get those screen voltages down to around +400 volts. If you can't, find out why.

There is another possibility. Check that 470K resistor from the CHROMIX controls to ground. If it is open, it would let the red and blue screens go higher than they should; this, of course would give you a purple (red + blue)



Circle 61 on reader service card



Our 23rd year of service to the World's finest craftsmen and technicians.

A carefully selected and tested assortment of unique, hard-to-find tools, clever gadgets, precision instruments, bargain kits. One-stop shopping for the technician, craftsman, hobbyist, lab specialist, production supervisor. Many tools and measuring instruments available nowhere else. One of the most unusual and complete tool catalogs anywhere. Get your copy of the NC FLASHER today.



NO BRAND NEW TV IS A STRANGER TO PHOTOFACT OF THE MONTH CLUB MEMBERS

Photofact-of-the-Month Club members are never at a loss in servicing a model that's so new they're seeing it for the first time.

Because Photofact is the most factually accurate and trustworthy guide a serviceman can use ... and P.O.M. Club members receive seven new Photofact Sets every month.

Sets contain detailed circuit data on over 150 of the latest TV, radio, stereo and record player models. In addition, their monthly P.O.M. package contains "advance" color schematics, a standard size file folder for each set, a Photofact Servicer with helpful service hints, and coupons good towards permanent metal Photofact Set file cabinets.

The coupon below is your invitation to membership in the Club. The dues—just \$18 a month—are a genuine bargain. You'll save \$10.00 a month (\$120.00 a year) over what you'd pay for the sets if you bought them singly!

Use that coupon now. Sub-

scribe to P.O.M. for 12 months and you'll also receive, FREE, a new member bonus gift of a de-

luxe 10-piece Xcelite PS-120 Nutdriver set.

P.S. Our T.I.P. Trade-in Program for exchanging old model Photofact sets and our Easy-Buy payment plan give you two more money-saving ways to update and fill out your Photofact library. Ask about them.




Howard W. Sams		RE 055
4300 West 62nd S	Street, Indianapoli	s, Indiana 46206
Please enroll me as a new membe to pay \$18.00 a month for my sub and I agree to maintain this sub receive, as a free bonus, the Xceli	oscription, which will loscription for at least	begin 12 months. I will also
Send full information on T.I.P.	and Easy Buy.	
Name		
Company name		
Company name		
Address	State	Zip

LIGHT BARS MOVING THROUGH RASTER

I've got light, horizontal bars moving slowly through the raster on an Olympic CT-910. They're not humbars, for these are darker than the rest of the picture. There's a little bluish shading at one end.

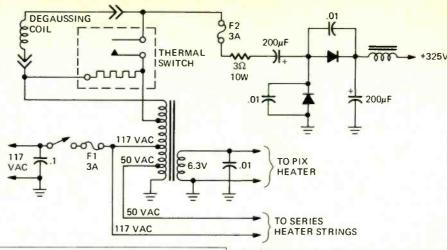Couple of notes first; "hum-bars" can be either light or dark. They're caused by ripple in the dc power supply; in other words, a "pulse" of voltage on what should be a nice smooth



BARGAIN BONANZA

EDLE

KITS ONLY NEW

(B128) 13 MINIATURE ELECTROLYTIC CONDENSERS \$1.00
Axial & upright, popular values.

PRODUCTS

- (B150) 15 HI-FI KNOBS \$1.00 Every one superb! Purchased from Harmon Kardon, Fisher, etc.
- (B127) 20 ASST. VOLUME CONTROLS \$1.00 Assorted ohmages, some with switches.
- (B153) CHASSIS
 MYSTERY \$1.19
 Take a chance! Could be a tape recorder, radio, walkie talkie, etc.
- ☐ (B156) 60 DISC
 CAPACITORS \$1.00
 Asst. capacitances from .0001
 to .1, most 600v, Z5U, NPO, N750, etc.
- ☐ (B147) 4 lb. GRAB BAG SPECIAL \$1.00 Full of exotic and exciting electronics parts.
- (B140) TAPE RECORDER
 SPARE PARTS KIT
 Parts for repairing most tape
 recorders: capacitors, meter,
 pilot lamp, jacks, and MUCH
 MORE.
- (B155) TUBE BONANZA! \$1.00 20 asst. popular tubes, untested.



(B223) 10 ASST. LED's \$1.00 guaranteed.

guaranteed.

(B178) 2 BATTERY

MOTORS Misc.

MOTORS Misc. \$1.00

☐ (B242) 3 LED's
Yellow or green (specify) guar.

(B001) 5 RED LED's guaranteed \$1.00

(BLSS32) 10 ZENER DIODES

DIODES \$1.19
1w, 3-30v, under 1v forward characteristic.



OBS (B253) 7 AMP POWER TRANSISTOR \$1.49 Si NPN. Similar to SK3054. 9v, 90w.

☐ (BLSS24) 25 ZENER
DIODES \$1.19
400mw, 4-20v. Under 1v forward characteristic.

☐ (BLSS23) 25 POWER
TRANSISTORS
Outstanding value! Asst. cases
and types, up to 15w, RF to
2 mHz.

(B167) 10 MINIATURE POTENTIOMETERS \$1.00 For transistor applications.

(B175) 70 ½ w CARBON RESISTORS \$1.00 All Std. makes & EIA values. Some 5%.

(B154) 150 CUT LEAD
RESISTORS \$1.00
Carbon, all leads long enough
for soldering.

(B149) 20 POLYSTYRENE TOP GRADE CAPACITORS \$1.00 Popular sizes.

(B132) 20 DUAL
POTENTIOMETERS \$1.00
Asst. ohmages.

(B131) 13 ELECTROLYTIC
CONDENSERS \$1.00
FP types, tubulars, some multiple sections.

(B138) 10 SLIDE
SWITCHES \$1.00

SWITCHES \$1.00
All types: DPDT, SPST, etc.

☐ (B134) 8 ROTARY
SWITCHES
Some multiple gang.
\$1.00

(B145) 50 TIE LUGS \$1.00 From 2 lugs up.

(B125) 4 TRANS-FORMERS \$1.00 Some power, filament, worth up to \$10 each.

(B144) TRANSISTOR
REPAIR KIT \$1.19
Various and sundry parts used to repair all transistorized devices.

(B137) 10 INSTRUMENT KNOBS Made by Ratheon, etc. \$1.00

MONEY BACK GUARANTEE Terms: Minimum order \$4.00. Include postage. Either full payment with order or 20% deposit, bal-

WRITE FOR FREE
VALUE PACKED CATALOG

BONUS
FREE CAPACITOR KIT
With Every \$5 Purchase



SURPLUS TUBES
All guaranteed for
1 full year.

ANY 3 FOR \$1.25

Acquired from U.S. Defense depots or removed from equipment (new and used). These are laboratory tested and guaranteed for one full year. Most are of such standard makers as RCA, GE, etc.

3A3	6AQ5	6DE4	6X4
3AF4	6AQ7	6DR7	10EW7
3BN6	6AT6	6DW4	12AE7
3DG4	6AU6	6EA8	12AL5
3F17	6AV6	6EB8	12AL11
3KT6	6AV11	6EJ7	12AT7
304	6AX4	6EM7	12AU7
4BC5	6AX5	6ER5	12AV6
4BN6	6AY3	6EY6	12BE6
4BU8	6AY11	6GF7	12BH7
4BZ7	6BA6	6GH8	1208
4CY5	6BG6	6GN8	17JZ8
4HA5	6BJ8	6GU7	18FW6
5V6	6BQ6	6K6	21KQ6
5Y3	6BZ6	6K11	25L6
6AC7	6CB6	6LB6	35EH5
6AF4	6CG7	6SN7	3525
6AG5	6CL6	6T8	36AM3
6AG7	6CM7	6V6	50A5
6AL5	6DA4	6W4	50L6
CALT			

- (B143) 20 RUBBER FEET \$1.00 For bottom of cabinets.
- ☐ (B164) 4 ROLLS OF WIRE \$1.00
 Approx. 25 ft, per roll, 20-28ga.
 ☐ (B148) 4 ROCKER SWITCHES
 Assorted. \$1.00

Assorted. \$1.00

(B141) 6 RCA JACK
STRIPS \$1.00

From 2-6 per strip.

(B142) 50 PRECISION
RESISTORS \$1.00

RESISTORS \$1.00
All 1%, ½w and 1w, low and high ohmages.

(B161) 50 CERAMIC AND

MICA CONDENSERS \$1.00

(B162) 25 CORNING GLASS
RESISTORS \$1.00
10% tolerance, 2-7 watts.

(B170) 4 RELAYS \$1.00
Asst. types, 6-110v, some worth up to \$10.

(B171) 5 CRYSTALS \$1.00
Asst. holders and bands.

(B182) 2 TUNING
METERS \$1.00
Misc., miniature.

☐ (B427) 12" HEAVY DUTY WOOFER \$17.95 20 oz. ceramic magnet, 75W RMS

(B124) 3 TRANSISTOR EARPIECES With plug. \$1.00

(B102) CALCULATOR
KEYBOARD \$4.95
Wild Rover C-1380. Made for
use with C75001. 4 function,
clear, clear entry and constant.

(B222) 20 DIODES 1A 50PIV. Epoxy, guar.

☐ (B417) 4" X-air SPEAKER \$6.95 15 watts, high compliance, response 35-16,000Hz. dc. If this pulse is of a polarity that will make the raster brighter, you get a light bar. If it's opposite, (tending to turn the beam off) you get dark bars.

Cause is the same; something in the dc power supply which is putting too much ripple on the B+ lines. Check that thermal switch in the degausser circuit. In some cases, it has been known to stick, and keep the degausser turned on at all times. Since this chassis has a half-wave voltage-doubler rectifier circuit, your ripple will have a slightly different waveform than the more common full-wave bridge rectifier. This is probably the cause of the two-bar symptom.

THE MEAN LITTLE KIT



New compact 24-piece kit of electronic tools for engineers, scientists, technicians, students, executives. Includes 7 sizes screwdrivers, adjustable wrench, 2 pair pliers, wire stripper, knife, 2 alignment tools, stainless rule, hex-key set, scissors, 2 flexible files, burnisher, miniature soldering iron, solder aid, coil of solder and desoldering braid. Highest quality padded zipper case, 6 x 9 x 1¾'' inside. Satisfaction guaranteed. Send check, company purchase order or charge BankAmericard or Mastercharge. We pay the shipping charges.

JTK-6 TOOL KIT......\$49.00

FREE CATALOG

112 pages of hard-to-find precision tools. Also contains 10 pages of useful "Tool Tips" to aid in tool selection. Send for your free copy today!



JENSEN TOOLS and ALLOYS
4117 N. 44TH STREET, PHOENIX, ARIZONA 85018

EOLIE ELECTRONICS, INC., 2700-B HEMPSTEAD TPKE., LEVITTOWN, N.Y. 11756



TAPE BIAS

(continued from page 72)

reason, home tape recorders now come equipped with separate bias switches to match the various bias requirements of different tapes. In the case of professional machines, bias adjustment is usually continuously variable and professionals will often apply a slight amount of excess bias. This practice can reduce recording drop outs that sometimes occur because of poor or non-uniform dispersion of oxide particles on the tape surface. Again, the professional recording engineer will often choose a slight reduction of highfrequency response if that choice means reduced overall distortion and the elimination of other bias related problems.

In a subsequent article, we will explore some of the ambiguities and confusion that exist in the tape field in specifying signal-to-noise ratios. We'll see how one tape deck's 55-db S/N spec may well give quieter performance than another deck's published 60-dB S/N specification.

NEXT MONTH IN R-E

Len Feldman explores the special electronic features of modern tape deck transports next month. Be sure you don't miss the June issue of Radio-Electronics.

MATHEMATICS ELECTRONICS

We are proud to announce two great new courses for the electronic industry.

These unusual courses are the result of many years of study and thought by the President of Indiana Home Study, who has personally lectured in the classroom to thousands of men, from all walks of life, on mathematics, and electrical and electronic engineering.

You will have to see the lessons to appreciate them!

NOW you can master mathematics and electronics and actually *enjoy* doing in

WE ARE THIS SURE: you sign no contracts—you order your lessons on a money-back guarantee.

In plain language, if you aren't satisfied you don't pay, and there are no strings attached.

Write today for more information and your outline of courses.

You have nothing to lose, and everything to gain!

The INDIANA HOME STUDY INSTITUTE

DEPT. RE-575, P.O. BOX 1189 PANAMA CITY, FLA 32401


Circle 67 on reader service card

You don't have to buy a new car to get an electronic ignition.



Most of you know the evaluation of automotive electrical systems . . . an evaluation characterized only occasionally by efficiency and performance. I know that, and that's why I use the Delta Mark Ten B CDI on all my cars, new and old. And believe me, you don't have to have a new car to appreciate the best electronic ignition available today. Study these features and you'll know what I mean.

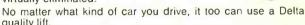- 1. Mark Ten and Mark Ten B Capacitive Discharge Ignition Systems are manufactured by Delta Products, Inc., a company with a conscience, and with a proven record of reliability both in product and in customer relations.
- 2. The Mark Ten CDI's really do save money by eliminating the need for 2 out of 3 tune-ups. Figure it out for yourself. The first tune-up or two saved pays for the unit, the rest is money in your pocket. No bunk!
- 3. Because the Mark Ten CDI's keep your car in better tune, you actually can save on expensive gasoline.
- 4. With a Mark Ten, spark plugs stay clean and last longer . . . fouling is virtually eliminated.



Name		
Address		
City	State	Zip

Mark Ten B, assembled Mark Ten B, kit

\$64.95 ppd \$49.95 ppd Standard Mark Ten, assembled \$ Deltakit® \$

\$49.95 ppd \$34.95 ppd

Circle 68 on reader service card



How to start making it early in life.

(A TRUE STORY)

Since he got out of the Navy, John Muirhead of Gales Ferry, Conn., has provided well for his family.

Two cars. A new house going up alongside a wooded lake. Even a handsome Great Dane named Sherman.

But John has bigger ambitions.

"I want my own air-conditioning business doing installations and repairs. For homes, office buildings, restaurants, small factories, motels.

"That's no dream. With the training I'm getting from ICS, I know I can do it.

"In fact, my ICS training helped me get the first job I ever applied for. I won out over two guys with college degrees, even though I had no experience.

"Naturally, I was nervous at first. So I took my lesson diagrams with me on the job. And I found I could lick any problem.

"Pretty soon, they asked me to head up the air-conditioning department. I also picked up some repair and installation business of my own on the side. That's what's helping to pay for the new house."

The right combination for success

John has the right combination for success. He's in a growing field. And he has good training for it. You could, too.

Especially if you're interested in one of the fast-growing careers where ICS concentrates its training. Like accounting. Engineering. Auto repair. Electrician. Air conditioning, etc. (Check your choice on card or coupon.)

Ideal way to learn

As an ICS student, you study at home, on your own schedule. You waste no time traveling to and from class. And you never have to miss a paycheck.

But you're never alone. Skilled instructors are always ready to help you.

If you ever have any doubts or problems or just want to talk to your instructor, you can even call ICS from anywhere, at any hour. Toll-free.

ICS training works

Since 1890 more than 8,500,000 men and women have turned to ICS for career training.

Some of the top American corporations (including Ford, U.S. Steel, Mobil, Alcoa, Pan Am, GE, Motorola and RCA) use ICS courses in their own training programs. Government agencies and unions have also approved ICS training.

Free demonstration lesson

If you want your job to give you more, (more money, more day-to-day satisfaction, and more future) send for our career guide booklet and free demonstration lesson.

Remember, it's your life. You might as well make the most of it.

ICS

We'll show you a better way to earn a living.

	1	G
ICS International Correspor Scranton, Pennsylvania		ols XA806D
Please send me the Free Caree and Free Demonstration Lesso checked below. I understand I	on for the fie	ld I have
 □ Engineering □ Airline-Travel Training □ Data Processing Mgt. □ Motel/Hotel Management □ Surveying & Mapping □ Business Management □ ICS High School Diploma Program □ Check here for special inform 	☐ TV Serv ☐ Electron ☐ Automo	ation an ting ricing tics otive
Name	Age	
City		
State	Zip_	
Telephone No.		
anadian residents use Scranton, Pa. add d. In Hawaii: 931 University Ave., Hon	ress for service olulu, Hawaii 9	from ICS Canad 06814.
APPROVED FOR VETERANS TRAINING		

Soon, a new home built on a wooded lake site will give John and Cheryl Muirhead lots of room for their growing family. (Photo: Frank Cowan)


9 new ways to improve tv reception and your profit-picture.

Whether it's a 1000-set installation at the International Hotel in Las Vegas...or a basic 4-set home TV system, there's a Blonder-Tongue MATV product that will deliver better TV reception.

Here are 9 new products backed by 25 years of experience in improving TV reception

AB-300, 25dB gain C h 2-13, FM. Dual voltage power for short or long 25dB loss runs of 75 ohm or 3000 ohm downlead.

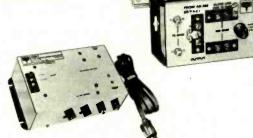DA8-T—famous DA8B fully transistorized.
13dB gain. Lower noise. 1 input/8 outputs.
VHF/FM. Universal 300 ohm/75 ohm.



DA-21—21dB gain, 75 ohm. VHF/FM and all CATV channels to 300 MHz.

Homer 375 Amplified Splitter—VHF/FM and all CATV channels to 300 MHz. 3 sets 300 ohms and one set at 75 ohms from a CATV cable input.



Vamp T-75 Mast-Mounted Preamp—17dB gain. Patented ICEF overload protection circuit. 6dB noise figure 75 ohm downlead 2-13.

6 CR-4—Deluxe compound, parallel-jaw crimping plier.



Model 4994—75 ohm 2-way antenna switch. Video, VHF, FM and all CATV channels to 300 MHz.

4946 U/V/FM—An economical band separator for TV sets and an FM takeoff connection.



SA-1000 Semi-automatic Rotor. Computer-age LED tuning indicator. 360° rotation. Economical two-wire installation.



These new BLONDER-TONGUE products are now at your distributor.

Blonder-Tongue Laboratories, Inc., One Jake Brown Road, Old Bridge, New Jersey 08857

new products

More information on new products is available from the manufacturers of items identified by a Reader Service number. Use the Reader Service Card inside the back cover.

PHOTOELECTRIC BEAM RELAY KIT, model GD-1021 is used around home, office, stores, factories, warehouses and garages as an alarm against instruders, for activating door openers, turning on lights, counting people entering or leaving an area, counting units on production lines, etc.


Consists of a light source, mirror assembly and a photocell-controlled relay that is ac-



tivated when reflected light beam is broken, energizing the AC socket. When beam again becomes unobstructed, relay turns off power to alarm or other devices. Unit will activate any external 120-volt alarm or lamps up to 150 watts. Built-in light source operates at distances of up to 25 feet from reflecting mirror. \$14.95.—Heath Co., Benton Harbor, MI 49022.

Circle 100 on reader service card

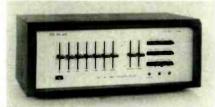STEREO PREAMPLIFIER EQUALIZER, model IXB. This 7-band graphic equalizer uses professional-type slidepots and pushbuttons instead of conventional rotary-type controls. Center frequency of each band is 40 Hz, 120 Hz, 320 Hz, 960 Hz, 2500 Hz, 7500 Hz and 15,000 Hz respectively. Torroidal LC bandpass filters with 12 dB/octave slopes




are used. Each slidepot has a dual range; variable to ±16 dB or ±8 dB. Equalizer defeat switch is provided to electrically remove equalizer from circuit. Tape copy facility is provided to eliminate patching to rear of chassis.

Frequency response: high level inputs is ±0.25-dB 10-Hz to 100-kHz and low level inputs is ±1-dB 20-Hz to 20-kHz. RMS harmonic distortion is less than 0.02% between 20 Hz and 20 kHz at the rated output of 2.5

volts, IM distortion is less than 0.02% at rated output, S/N level: low-level is 75-dB below a 10-mV input and high-level is 90-dB below rated output. Maximum output is 18V into high impedance, 5.75 × 17 × 7 in. — Scientific Audio Electronic, Inc., 701 Macy Street, Los Angeles, CA 90012.

Circle 31 on reader service card

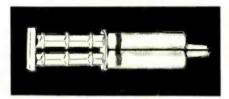DOUBLE BARREL EPOXY, model 33-104. Epoxy glue has always been supplied in two tubes requiring the exact mixture of both tubes. Now, double barrel epoxy is contained in a double-nozzled, self-meas-



uring dispenser. Easy-to-use, all that is required is to push the piston to meter equal parts of hardener and resin. Cap is replaced and product is stored until needed.
—Workman Electronic Products, Inc., Box 3828, Sarasota, FL 33578.

Circle 32 on reader service card

MASTER RIG, model MJ-195 is a complete test rig for both tube and solid-state chassis. Features include: built-in hi-voltage meter, speaker, front panel connections and metal cabinet. When equipped with the proper CRT, they are capable of operating with late model



chassis that delivers over 30 kV. Comes complete with all components for the deflection circuit hookup and four solid-state yoke adapters, \$149.95, less 19-in. picture tube.—TeleMatic, 2245 Pitkin Avenue, Brooklyn, NY 11207.

Circle 33 on reader service card

CB RADIOTELEPHONE, Messenger 132 extends radiotelephone operating concept to base station use. Offers all advantages of the handset design including option of private listening. If user selects, the speaker is automatically silenced when he lifts the




VISUAL APPLICATIONS OF THE World'S
Most Practical Solder HANDLING TOOLS



NEW.,, 144 PAGE TRAINING MANUAL
OVER 1,000 ILLUSTRATIONS

manual designer	raphic motion in a training I to stimulate the mind to he line. Avaitable at \$7.9	FAMOVESTON
Send FR	PATING DISTRIBUTORS EE Information on NOVISIONManua	EDSYN. Products
chase of \$7.	OVISION Manual will be 195 (or more) of any E ANUAL to a customer.	e sent FREE with pur- IDSYN Products. Limit
Name		
Address		
Address City	State	Zip

Circle 70 on reader service card

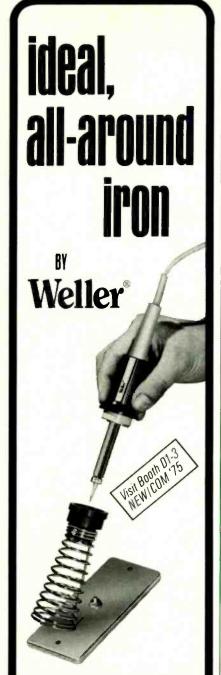


FOR ELECTRONIC SOLDERING

Model WP-25. Popular 25-watt, penciltype iron for general purpose work. Handy size: 71/8" long. Lightweight: 13/4 oz. Comfortable to hold. Perfect for crowded areas. Easily stored. Longlife, double-coated, 1/6" screwdriver tip quickly changed to other available styles and sizes. Rugged stainless steel barrel. Use with or without optional, mounted or free-standing bench stand PH-25.

Ask your local distributor or write...

Weller-Xcelite **Electronics Division**

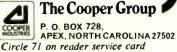

handset to permit listening without disturbing others. Handset also provides increased clarity under noisy conditions. When group listening is desired, a switch on the front panel provides simultaneous handset and loudspeaker operation.

Also featured is an illuminated meter that indicates received signal strength as well as



relative RF power output. A PA function allows paging when radio is used with a remote speaker. With the PA switch in the on position, radio can also be used for remote listening of incoming radio calls. Unit is equipped with all 23 CB channels and has a back-lighted channel selector that changes from white to red when radio is in transmit mode.-E. F. Johnson Co., Waseca, MN 56093

Circle 34 on reader service card

THERMISTORS, No. GB-205 is a fast response, instant-on degaussing thermistor for use in most late model sets. Other additions include exact replacements for RCA and



other TV brands. Company makes available over 360 different semiconductors capable of replacing 90% of the industry.-Oneida Electronic Mfg., Inc., 843 North Cottage Street, Meadville, PA 16335.

Circle 35 on reader service card

FUNCTION GENERATOR, model 10 provides simultaneous outputs of sine, square and triangle waveforms. Features include: TTL



compatible output, four volt P-P triangle output and a selectable function output with the amplitude adjustable from 0V to 20V P-P into 600 ohms. Frequency range is 1 Hz to 1 MHz; sinewave distortion is less than

FREE ALARM SYSTEM **CATALOG**



Circle 72 on reader service card

RGS ELECTRONICS

(602) 263-8831

008A MICROCOMPUTER KIT

8008 CPU, 1024 × 8 memory; memory is expandable. Kit includes manual with schematic, programming instructions and suggestions; all ICs and parts supplied except cabinet, fuses and hardware. Includes p.c. boards

MANUAL ONLY, \$25.00 (No Discount on Manual)

008A-C AUDIO CASSETTE ADAPTER KIT

Kit includes all ICs, p.c. board, schematic and instructions. Will interface most audio cassette recorders to the 008A Micro-computer. NOT intended to interface with any other computer. *\$50.00 computer.

008A-K ASCII KEYBOARD INPUT ATT
Kit includes keys, p.c. board, ICs, schematic
and instructions. This kit is intended to interface ONLY with the RGS Electronics 008A
\$75.00

TRANSISTORS

NPN General purpose TO-92 \$.08; \$5.95/100 PNP General purpose TO-92 \$.08; \$5,95/100 Other transistors and JFETS available at our usual low prices; all are tested, good units. Specs available in our flyer.

RGS ELECTRONICS, 3650 Charles St. Ste K, Santa Clara, CA 95050 (408) 247-0158 (408) 247-0158

We sell many ICs and components not listed in this ad, included most of the 7400 series; send a stamp for our free flyer.

TERMS OF SALE: All orders prepaid; we pay postage on all U.S. orders. Handling charge of \$1.00 on U.S. orders under \$10.00, foreign orders under \$25.00. California residents please include sales tax. Please include name, address, and zip code on all orders and their requests. and flyer requests.

*DISCOUNTS: 10% OFF ORDERS OVER \$25.00 - 20% OFF ORDERS OVER \$250.

PRICES SBIECT TO CHANGE WITHOUT NOTICE.

Circle 73 on reader service card

2% (1 Hz to 100 kHz); input power is 105-125 VAC 60 Hz at 10 watts. $6 \times 4 \times 3$ in.; 1 lb.; \$89.95.—Advanced Electronics, P.O. Box 63, 63 Lincoln Street, Newton, MA 02161.

Circle 36 on reader service card

AUDIO SWEEP GENERATOR/FREQUENCY METER, 140B is three instruments in one—audio oscillator, audio sweep generator and frequency meter. Operates manually as conventional oscillator or swept automatically as voltage controlled generator. Generator sweeps over two ranges—high range from



1 kHz to 20 kHz and extended low range from 40 Hz to 1 kHz.

Frequency may be used independently. However, when connected to output of sweep generator, the frequency reading is continuously displayed. May be used to monitor changing frequency of sweep generator or any other external frequency source. Unit is source for testing amplifier frequency response, speaker enclosures, tape recorder head alignment. Provides sinewave output that is variable from 0 to 2.5 Vp-p. Once set, amplitude remains flat over entire frequency range. Sinewave distortion is less than 1.5%; square wave output is fixed at 8 volts. \$78.95.—Production Devices, 7857 Raytheon Road, San Diego, CA 92111.

Circle 37 on reader service card

LOOK FOR

THE

JUNE

ISSUE OF

RADIO-

ELECTRONICS

AT YOUR

NEWSDEALER

MAY 20

Autoranging multi-function counter

\$349

Indicate the state of the st

If You Work In Electronics:

GRANTHAM OFFERS YOU College-Level Training

Electronic Circuit Design,
Engineering Analysis (including mathematics thru calculus),
Classical and Solid-State
Physics, Engineering Design,
etc., etc., are all part of
the Grantham home-study degree program in Electronics
Engineering.

PUT PROFESSIONAL RECOGNITION IN YOUR CAREER.

and a college degree.

By adding collegelevel home training and a college degree to your experience, you can *move up* to greater opportunities in electronics.

Grantham offers the A.S.E.T. degree by correspondence. After earning this degree, you may continue with additional correspondence plus a 3-day

residential seminar and certain transfer credits, to earn the B.S.E.T. degree. Then, the B.S.E.E. is available through further study.

GRANTHAM SCHOOL OF ENGINEERING

2000 Stoner Ave., Los Angeles CA 90025

• Telephone (213) 477-1901

Worldwide Career Training thru Home Study
Mail the coupon below for free bulletin.

Grantham School of Engineering RE 5-75

2000 Stoner Ave., Los Angeles, CA 90025
I have been in electronics foryears. Please mail me your free bulletin which gives details concerning your electronics degree programs.
Name Age

Address _____

ity____State___Zip__

Circle 74 on reader service card

COUNTER DIVISION

John Fluke Mfg. Co., Ltd.

P.O. Box 1094, Station "D" Buffalo, N.Y. 14210 Phone (716) 842-0311 TWX 610-492-3214

INSTRUMENTS Out-of-Circuit

- - Transistor Analyzer
 - Dynamic In-Circuit Transistor & Radio Tester
 - Signal Generator
 - Signal Tracer Voltmeter
 - Milliammeter
 - Battery Tester
 - Diode Checker

Transistor Analyzer Model 212

Factory Wired & Tested-\$26.95 Easy-to-Assemble Kit-\$17.95

YOU DON'T NEED A BENCH FULL OF EQUIPMENT TO TEST TRANSISTOR RADIOS! All the facilities you need to check the transistors themselves — and the radios or other circuits in which they are used — have been ingeniously engineered into the compact, 6-inch high case of the Model 212. It's the transistor radio troubleshooter with all the features found only in more expensive units. Find defective transistors and circuit troubles speedily with a single, streamlined instrument instead of an elaborate

Features:

Checks all transistor types — high or low power. Checks DC current gain (beta) to 200 in 3 ranges. Checks leakage. Uni-versal test socket accepts different base configurations. Identifies unknown tran-sistors as NPN or PNP.

Dynamic test for all transistors as signal amplifiers (oscillator check), in or out of circuit. Develops test signal for AF, IF, or RF circuits. Signal traces all circuits. Checks condition of diodes. Measures battery or other transistor-circuit power-supply voltages on 12-volt scale. No external power source needed. Measures circuit drain or other DC currents to 80 milliamperes. Supplied with three external leads for in-circuit testing and a pair of test leads for measuring voltage and current. Comes complete with instruction manual and translator listing.

CITY	ZONE	STATE
ADDRESS		
NAME		RE-5
Send me FRE value-packed local distribut	EMC line.	the complete and name of
EMC, 625 Bro	adway, New	York 12, N. Y.

ELECTRONIC MEASUREMENTS CORP 625 Broadway, New York, N Y

Makes circuits THREE WAYS

1 FULL SCALE ARTWORK MASTER			
2 MAGAZINE ART POSITIVE NEGATIVE	DEVELOPED PHOTO RESIST IMAGE ON COPPER CLAD CINCUIT BOARD	•	ETCHEI CIRCUI BOARD
•	_		

DIRECT ETCH DRY TRANSFERS APPLIED TO COPPER CLAD BOARD

USES DATAK'S POS-NEG PROCESS The revolutionary photographic way that makes PERFECT printed circuits from original art or a printed page.

ER-4 COMPLETE PHOTO ETCH SET \$	24.95
ER-2 PC patterns and tapes — refill	3.39
ER-3 ¼ pound dry etchant – refill	
ER-5 6 sheets photocopy film — refill	
ER-6 Film process chemicals — refill	
ER-7 Photo resist spray, 2.5 oz. — refill	
ER-8 Resist developer, 16 oz. can – refill	2.95

AT YOUR DISTRIBUTOR OR DIRECT

the DATAK corp. 65 71st St. • Guttenberg, N. J. 07093

You'll never know how much good you can do until you do it.

You can help people.

In fact, there's a crying need for you. Your talents. Your training. Your concerns. They make you valuable to your business. They can make you priceless to your community.

If you can spare even a few hours a week, call the Voluntary Action Center in your town. Or write: "Volunteer," Washington, D.C. 20013.

It'll do you good to see how much good you can do.



The National Center for Voluntary Action.

A Public Service of This Magazine & The Advertising Council

For faster service

USE CODE

mail

SERVICING MATV

(continued from page 69)

Shorts are easier to track with your field-strength meter. If you read a short, re-connect the trunkline to the splitter and fire the system up again. Then, use the field-strength meter to check the signal out of each tap-off in the line. As you approach the short, the signal level will decrease markedly. The advantage of using the fieldstrength meter for this routine is that it is much faster and easier. You don't have to remove any tap-offs from the wall or disconnect input or output cables.

Frequent troubles

You don't always have to go through an entire troubleshooting procedure to pinpoint MATV troubles. A knowledge of what is most likely to happen as a system is used can help you to take very effective shortcuts. Here are the most common causes of MATV troubles in older systems:

Ac hum. Appears on screen as one or two stationary or rolling dark bars. One bar indicates 60 Hz hum, halfwave power supply. Two bars indicate 120 Hz hum, full-wave power supply.

Use your portable TV set to make sure the hum isn't originating from a defective filter in the tenant's set. If hum appears on all sets, the hum is probably caused by a filter in the MATV amplifier.

Picture rolling: on one channel only. Usually caused by sync compression in single-channel amplifier. As amplifier ages, tuning shifts and AGC increases gain. If you encounter this problem, use the manufacturers recommended procedure to reset the AGC tuning and reduce the gain of the amplifier.

Cross modulation in broadband system. Levels may have been set right initially, but the maintenance man or some tenant may have taken it upon himself to turn up the amplifier gain.

Ghosts. Some tenants try to compensate for aging tuners on their TV sets by getting more signal out of the MATV system. They simply short out the isolation in the tap-off. This tenant's pictures will be very good, but others along his trunkline will be bothered by ghosts.

Another common cause of ghosts is that someone has extended the line, adding a few extra outlets. This causes no problem if done properly, but most people forget to terminate the line when they add outlets. No termination means standing waves which equal ghosts.

If the ghosts are seen in only one or two apartments, it's a good bet that (continued on page 97)

ROOKS VALUE S

FREE \$1 BUY WITH EVERY 10 YOU ORDER Only applies to "\$1" Buys

FREE GIFT WITH EVERY ORDER

CANADIANS: Ordering is easy—we do the paperwork—try a small order

RCA 110° FLYBACK TRANSFORMER We scooped the Mar-ket. Latest type — standard for all 110° TV's (BIK. & Wht.). TV's (Blk. & Wht.). RCA's design of large Coll produces 18KV— assuring adequate width Incl. Schematic Diagram application for any TV. List price \$13.90 395 Your price

WESTINGHOUSE ALL TRANSISTOR HOME/OFFICE MESSAGE CENTER

Leaves messages for other for replay . . . Built in speaker/microphone for talk-into convenience . . . Records up to 3 minutes of messages . . . Illuminated signal shows when a message is waiting. Control adjusts playback volume without affecting recording volume . . . Capstan Drive: 795 BRAND NEW SOLD AS IS

	SHANNON MYLA	R RECORDING TAPE
31/4" 5" 5" 5" 5"	- 600'	CASSETTE C-9019 CASSETTE C-901.9 CASSETTE C-1201.9 8-Track — 64 Min29 8-Track — 80 Min1.59 8-Track — Cleaner1.49
7" 7" 7"	— 1200'	3" TAPE REEL .09 3¼" TAPE REEL .12 5" TAPE REEL .29 7" TAPE REEL .35

10% off in lo	ts of
or all types TV's incl schematic	495
"COMBINATION SPECIAL" RCA 10° FLYBACK plus 110° DEFLECTION YOKE	6 ⁹⁵
90° FLYBACK TRANSFORMER	295
for all type TV's (Blk. & Wht.)	
90° TV DEFLECTION YOKE	395
for all type TV's (Blk. & Wht.)	
70° FLYBACK TRANSFORMER for all type TV's (Blk. & Wht.)	200
70° TV DEFLECTION YOKE	
for all type TV's (Blk, & Wht.)	200
OLYMPIC & SHARP FLY.	_
BACK Part #8FT592 Equiv.	
Stancor #HO-408-	395
Thordarson #Fly339	J
90° COLOR YDKE For all	
Rectangular 19 to 25"	795
Color CRT's	
70 COLORE YDKE	895
For all round color CRT's	_
DELMONICO NIVICO COLOR	795
FLYBACK Part # A20411-B	
SARKES TARZIAN TUNE 41mc	R
Latest Compa	ct

2 COLOR-TV CRT SOCKETS
Wired leads, for all color TV's
3-RCA 110° CRT SOCKETS
Wired leads, for all TV's
RMS-9 ELEMENT COLOR
OUTDOOR ANTENNA
Model HA-9 VHF/UHF
4-Polarized CHEATER CORD

2—Colorburst Quartz-Crystal
For most color TV sets 3579.545 KC 1
5 ASST GLOBAR VARISTOR
Popular replacements for 100

most COLOR TV
UHF or VHF Matching Trans.
Simple Fool-proof installation

Grey
Grey
70° COLOR TUBE
BRIGHTNER
90° COLOR TUBE
BRIGHTNER
Colorburst Quarti

Model good for all 41 mc TV's.

BRAND NEW -

100 895 100

395 495

100

TELMATIC Tuner-Mate KT-73 Portable "Substi-Tuner"— Instant Tuner Check	4250
TELEMATIC Test Jig Model— EJ-190—Master Rigs— Combo Rigs—Econo Rigs	4995
KLEPS "CLEVER" TEST PRO	DS
"Third-hand" test prods, reach out of way places - Insulated - c slip - accommodates hare wir banana plug—no soldering.	annot
PRUF 10— Versatile Test Probe	89°
KLEPS 10- Boathook Clamp 434" long	139
KLEPS 20— Boathook Clamp 7" long	149
KLEPS 30— flexible-forked Tongue 6" long	179
Board Terminals 61/4" long	259
KLEPS L.ECONOMY	OO6

Test Equip. Special Discount Prices

SENCORE MERCURY COMPACT TUBE TESTER Model #990 Ministure-sized Speca Saver Full sized

74100

BILL

in performance

	most useful assortment #1	1
Best TUNER "SARKES TARZIAN"	For Color TV #2	149
ever made — last word for stability,	6 - TV COLOR ALIGNMENT	279
definition & smoothness of operation.	TOOLS Most popular type	2
An opportunity—to improve and bring	TV TWIN LEAD-IN	100
your TV Receiver up-to-date. 795	300 ohm 500'-\$7 100'-\$1.50, 50'	1
Complete with Tubes	CO-AX CABLE RG59U (Black)	269
	250'-\$10, 100'-\$4.50, 50'	_
WESTINGHOUSE FM TUNER 399	5-DUAL DIODE-MOST	
# 110 1 GIOISO I II MISINGI	POPULAR TYPES Common	250
WESTINGHOUSE FM TUNER 100	cathode or Series connected	_
(12DT8 Tube)	CONVERGENCE RECTIFIER-	
UHF TUNER—Transistor Type 395	For COLOR TV 4 Cell-	100
Card in all I v sets	Used In ItCA—Phileo, etc.	•
G.E. UHF TUNER-TRANSIS- 395		2.29
TOR TYPE Model #85X4 J		3.95
	COLOR POWER TRANS.	3.33
Model #94C393-1 (2HA5-4LJ8) 795	-Good for most sets 26R150	C95
Model #T94C441-3 (Transistor) WELLS GARDNER TUNER Part 795	List Price \$36.75	0,
#7A 120-1 (4G87-2HA7 Tubes)	6-Top Brand Silicon RECT.	1 00
G.ETV TUNER (2GK5-4LJ8) 795	1 amp., 1000 PIV	1
Model #ED 90-11		100
PHILCO UHF/VHF TUNER 995	general purpose, TO-5 case	L
	5-NPN TRANSISTORS	100
GE TV TUNER 595	general purpose, TO-5 case	I
ET 86x196, (6GK5-6BL8)	25-ASSORTED TRANSISTORS	1 00
UNIVERSAL TV Antenna Back of 999	big factory scoop—sold as-is	100
set mounting 5 section rods	5-9 VOLT MOTORS	100
BLUE LATERAL Magnet Assy. 179	Excellent for hobbyist	100
Replacement for most color TV's	2-ELECTROLYTIC CON-	100
5-10K-2 WATT BIAS POTS 100	DENSERS Axial leads-500-25V	100
Used in solid state application	ELECTROLYTIC CONDENSER	1 00
Universal type—good for most sets 249	300 mfd.—200V	1
COLOR-TV RECTIFIER—Used 195	2-ELECTROLYTIC CONDENS-	1 00
In most color sets—6500 kv 3 for	ERS 80/100/60 MFD-160V	T
2 COLOR-TV CRT SOCKETS 100	2-ELECTROLYTIC COND	1 00
Wired leads, for all color TV's	200/30/4-mfd-350V	T
The second second at a second	3_FI FCTROLYTIC COND	400

L	Kleps for Light Work	9"
	4 - TV ALIGNMENT TOOLS	100
	most useful assortment #1 4 — TV ALIGNMENT TOOLS	40
\sqcup	4 - TV ALIGNMENT TOOLS For Color TV #2	149
	6 - TV COLOR ALIGNMENT	279
\Box	TOOLS Most popular type	2
	TV TWIN LEAD-IN 300 ohm 500'—\$7 100'—\$1.50, 50'	100
\equiv	CO-AX CABLE RG59U (Black)	269
	250'-\$10, 100'-\$4.50, 50'	2
	5-DUAL DIODE-MOST	
	POPULAR TYPES Common cathode or Series connected	250
	CONVERGENCE RECTIFIER-	
\Box	For COLOR TV 4 Cell-	100
	Used in RCA-Philco, etc. TV DAMPER DIODE Single-	•
ш	Replace RCA part # 120818	\$2.29
	Dual-RCA part # 135932 COLOR POWER TRANS.	\$3.95
	-Good for most sets 26R150	695
	List Price-\$36.75	0
	6-Top Brand Silicon RECT.	100
	1 amp., 1000 PIV	-
	5—PNP TRANSISTOR general purpose, TO-5 case	100
	5-NPN TRANSISTORS	100
\sqcup	general purpose, TO-5 case	I.
	25-ASSORTED TRANSISTORS	1 00
\Box	blg factory scoop—sold as-is	A
	5—9 VOLT MOTORS Excellent for hobbyist	100
$\overline{\Box}$	2-ELECTROLYTIC CON-	100
\Box	DENSERS Axial leads-500-25V	•
П	ELECTROLYTIC CONDENSER 300 mfd.—200V	100
\equiv	2-ELECTROLYTIC CONDENS-	1 00
\Box	ERS 80/100/60 MFD-160V	1
	2-ELECTROLYTIC COND	100
7	200/30/4-mfd-350V 3-ELECTROLYTIC COND	100
\Box	100 mfd100V. 50 mfd75V	1
	2-ELECTROLYTIC COND	100
=	40 mfd-500V, 40 mfd-400V 5-AC LINE CORDS	100
\square	Approved 6'	I
\Box	4-50' HANKS Hook-Up Wire	100
\Box	assorted colors	1
	PIN JACKS RCA type	100
\equiv	8-MINI PILOT BULBS With	100
\sqcup	8" Leads-6.3V 30MA (5000 Hrs)	1
	8-MINI PILOT BULBS With 12"	100
	Leads—6.3V, 150MA (5000 Hrs.) 32'—TEST PROD WIRE	100
Ш	DELUXE QUALITY red & black	
	10-MINI ELECTROLYTIC Cond	100
\Box	For Transistor & miniature work	

d signal shows when a	7" — 1200'			•	_
layback volume without	7" — 1800'	1.32		EEL	.12
on Drive: 795	7" — 2400' 7" — 3600'	3.49	5" TAPE RI		.29
Vuon onto			KET SCOOF		_
KNOB SPEC	IO KNOBS 100				•
All standard types :	\$20 value		& Etch your		995
POPULAR TYPES	Tuning 100	easy (o use instructio	ns	
Mostly Selector & F	THE YOURS -		nd IC3 Integra in Scott-Fishe		100
Long shank F		15-A	SSORTED IC"		10
assortment 20—Vertical Linear	IN KNOBS 100	Silico	ixperimenters	ANSISTOR	
Side mount Sta		RCA-	-SK-3021-Her -SK-3026Her	5-240	100
Hard to get. Bes	t selection	Trans	istor Specials-	Your Choice	-
Hard to get, Bes	KNOBS 100		06, 8K3018, 8K 22, 8K3124	3020	100
most popular types ANY 6 KITS F	ACT COMMISSION	Trans	istor Specials-		19
TRANSISTOR RADI	0		09, SK3024, SF 10meter 21/41		
asst type good, bad, hi			1-VDC, full esistance 0-6000		20
as-is, potluck	Change on	coli r	esistance 0-6000 ASSETTE type	dynamic Mik	
assorted types good, b	ad 400	with	universal plugs-	-200 Ohms -	_
broken, as-is, potiuck	SISTORS		" PANEL ME'	IER	12
Top Brands, Short Let	ads, 100	100'	GREY SPEAK		20
Excellent Selection	RESISTORS 100	2 Cor	id mini zip, 10 L-CORDLESS	SOLDER	
stand, choice ohmages,	some in 5%	☐ IRON	Complete with	Auto	1995
stand, choice ohmages,	RESISTORS 100	5—Ai	er - Fast Heating	ANSFORM	10
stand, choice ohmages,	RESISTORS 100	Sub-r	nin for Trans I	Radios	1
stand, choice ohmages,	RESISTORS 100	456-k	c for Transistor	Radios	10
stand, choice ohmages	, some in 5%		uality Special b		159
asst. list-price \$50 les	8 98%	12" U	NIVERSAL SE	PEAKER	58
RESISTORS, 5, 10, 2	REWOUND 100	Top C	uality Lar	ge Magnet	39
I ID-ASST SLIDE S	WITCHES 100	Top (Quality Lar	ge Magnet	
SPST, SPDT, DPDT	TSINKS 100	Large	NIVERSAL SI Magnet—Spec	EAKER—	29
For Transistors		3" 11	VIVERSAL TW	EETER	129
20—ASSORTED TV I.F. VIDEO, sound I—ELECTROLYTIC	COILS 100	21/2")	Magnet 4" SPEAKER		_
I-ELECTROLYTIC	COND. 100	Speci	al Buy 10 for \$ "QUAM" 16	5EA	69
200/300/100/100 MFI	COND 100	Large	magnet Sp		179
3-ELECTROLYTIC		(10 f	or \$15.00) H 8" HEAVY		
20/20 MFD-450V		SPE/	KER Ceramic	Type-8 Ohn	4
Most popular types		Ceran	x9"Heavy Duty nic Type 8	Ohm Speake	45
2—ELECTROLYTIC 300 mfd-200V,	Condensers	I5"	x7" UNIVERSA	AL SPK.	29
300/60 mfd-150V	100	3 SPI	0-40 OHM Imp EAKER—7 WA	Y SELECTO	R 100
T5/30mfd—150V	COND 100	SWIT	CH Wall Mous	nt	
ELECTROLYTIC CO	NDENSERS 100	- FL 19	79/01 Made in		r 6⁵
200/200 mfd.—200V	COND 100	TRAI	NCOR POWER		
1500 mfd.—35V	*****************	117 V-	-50-60 Cycle-	-Pri.	32
best types and sizes		POW	2.6 Cent. Tan 2 ER TRANSFO	RMER	-
250—ASST WOOD S		Used	48)—110V Pri in many transis	-12V Sec.	229
250-Asst Self Tappi	SCREWS 100	Power	supplys	£7989	2
#6, #8, etc.		ASSY	LINC. Yoke. I	Soard &	
and 100-6/32 HEX		to mo	Conn. Adaptable st 90° sets	2	39
100—ASST 8/32 SCF		COLC	R DELAY LIN	E—Used	169
and 100—8/32 HEX I		7-A	STORTED VOL	UME	100
and 100-2/56 HEX I	1010	- 10-A	ROLS with swi	LUME	100
and 100-4/40 HEX I		CONT	SST. ROTARY	ch	
and 100-5/40 HEX	NUTS	All be	mular types-\$2	0 value	100
most useful selected	VETS 100		DINE PILLOW S plug & volume of		249
300 ASSORTED WAS	HERS 100	2-12	BH7 RCA	OHITOI	100
most useful selected :		TUBE	SST DIODE C	RYSTALS	
for cabinet bottoms-		IN34,	1N48, 1N60, 11	N64, etc.	100
best sizes		TUBE	& CONTINUI	TY CKR.	- 0
15-DIPPED MYLA		(Tests	fuses, heaters,		19
15-DIPPED MYLA	R CAP. 100		co Stereo Carti		001
.033-600V		needle	,		
15-DIPPED MYLAI		RONI	TTE Steres C dual sapphire Headphones H	flipover type	200
15-DIPPED MYLAI	R CAP. 100				595
15-Molded Tubular 0			Complete with STANDARD TR		
.056-400 V	-	NPN	& PNP 2N404	, 2N414, etc.	
15-DIPPED MYLEI	R Condensers 100	Grey	ielded MIKE C 25/1	ABLE	189
-777		4.0)			


MAY 1975

IMMEDIATE DELIVERY Scientific light packing for safe delivery at minimum cost.

HANDY WAY TO ORDER . . . Send check or money order, add extra for shipping. Lists of new offers will be returned in your order.

Please specify refund on shipping overpayment desired:

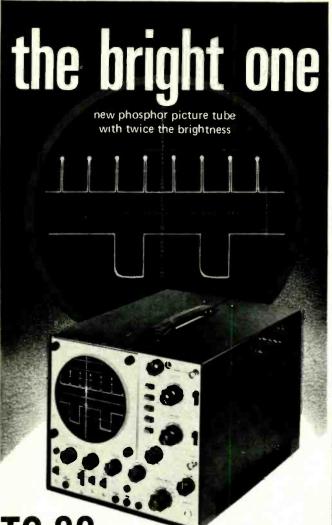CHECK POSTAGE STAMPS MERCHANDISE (our choice) with advantage to customer BROOKS RADIO & TV CORP., 487 Columbus Ave., New York, N.Y. 10024 TELEPHONE 212-874 5600



T0-60 automatic dual-trace triggered-sweep oscilloscope

P-31 phosphor CRT has double the brightness for bright displays even in high speed dual-trace modes. Bandwidth: DC to 15 mhz. Unique features for the industry's greatest value are: • Automatic Triggering • Automatic Astigmation • Automatic Horizontal Sweep • Automatic Horiz/Vert. TV Triggering provides positive display on composite video signals. Vertical sensitivity: .01 volts/cm to 20 volts/cm in 1-2-5 step sequence. Horizontal Sweep Speeds: .2 sec/cm to .5μ sec/cm in 1-2-5 step sequence. Has 5X magnifier at all sweep speeds. External Horiz. Amp. Bandwidth: DC to .5 mhz; Sensitivity: .5 volts/cm. Calibrated Test Signal: 1 volt P-P square wave. Power: 105-125 volts, 60 cycles, 65 watts

Model TO-60 Less Probes. Net \$489.50

For the "bright one," see your distributor, or write:



Circle 78 on reader service card

new lit


All booklets, catalogs, charts, data sheets and other literature listed here with a Reader Service number are free. Use the Reader Service Card inside the back cover.

HARDWARE & SOFTWARE APPLICATIONS CATALOG, Tekgraphics. Quarterly publication delves into several scientific fields and explains how the company's computer graphics terminals and programmable calculators have liberated searchers from time-consuming chores. Major articles in October's 16-page issue includes a story on how NASA optimizes aircraft design testing with interactive computer graphics, a story on how a programmable calculator speeded up the engineering of a telescopic wing for a physician's amphibian airplane and much more.—Tektronix, Inc., P.O. Box 500, Beaverton, OR 97005.

Circle 38 on reader service card

SPEAKERS BROCHURE, 8-page catalog offers a choice of ten preengineered Starrsond speaker systems—complete with speakers, crossover components, wiring schematic and suggsted enclosure dimensions that allow the buyer to build his own system in the cabinet of his choice. Features hi-fi speakers, automotive, extension and public address speakers, aircraft speakers, musical instrument speakers and Starrsond systems.—CTS of Paducah, Inc., 1565 North 8th Street, Paducah, KY 42001.

Circle 39 on reader service card

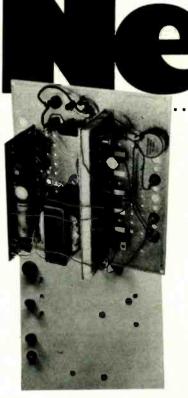

CIRCUIT DESIGN, INC.

Div. of E&L Instruments P.O. Box 24 Shelton, Conn. 06484

. UNIVERSAL ELECTRONIC INSTRUMENT DESIGN AND BUILD YOUR OWN ELECTRONIC INSTRUMENT IN HOURS, NOT DAYS!

Think of it. No circuit board to assemble or solder; just push your electronic components into the SK-10; no panels to lay out and machine — simply mount your parts . . . combine your design with the self-contained power supplies and you've got a finished instrument.

Available in 3 kit versions to meet your unique requirements it combines the SK-10

Available in 3 kit versions to meet your unique requirements, it combines the SK-10 socket with the UMP-01 universal panel and gives the designer an instrument In 1/10th the time it would take with custom instruments.


From \$50.00 to \$85.00 depending on the power supplies you want. Write for free literature.

service questions

RESISTOR SMOKES: NO SHORTS!

This Magnavox 920 has a really weird symptom. R146, 68K 1/2 watt, in the pulse-feed circuit to the blanker grid, and other circuits keeps burning up. I finally got it to hold by using a 1-watt resistor. It runs pretty hot, but stays. There are no short-circuits on the load side of the resistor; blanker tube replaced, etc. I don't understand this. What makes it burn up?—L.F., Altus, Okla.

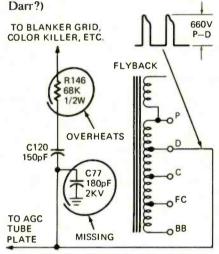This kind of thing can be puzzling (puzzled me no end the first time I ran over it). If you do not have a dc short, causing excess current to be drawn through this resistor, there's only one logical explanation left. (Who says that TV circuits have to react logically,



In circuits with high pulse voltages, an open bypass can cause this. The bypass capacitor reduces the amplitude of the pulse, so that the resistor can hold. Good suspect would be C77, 180 pF, which is right on the flyback terminal board. You might overlook this, because it's drawn on the schematic away up on the age tube plate!

(Field feedback; this was right. Another victory for the Crystal Ball!)

REPLACEMENT TRANSISTORS

I have an old stereo amplifier to fix. Transistors out, and some modifications on the PC boards. It's a TEC S15. Where can I get a schematic, and what's a "B-1215" transistor?—B.A., Livingston Manor, N.Y.


You're in luck. Sams Photofacts lists exactly *one* Tec, and it's a model S-15. Company out of business, but looks fairly stock.


B-1215 transistor finally run to earth in one of my Transistor Guides. Germanium, TO-3 case, 50 volts breakdown, 7A max Ic. An SK-3009 should be a good replacement.

After you get it fixed, plug it into a

variable-voltage transformer, with a current meter in the collector supply, and bring the line voltage up from zero very slowly. This will tell you if there's anything else wrong before the smoke starts to rise.

Get free luggage ...on the QT

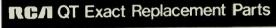

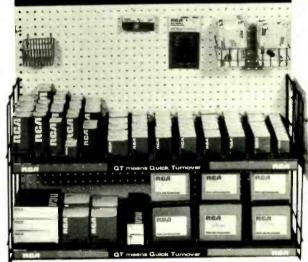

Buy any RCA replacements parts QT package now and we'll give you a bonus — free luggage. With our DP175 package of most needed "Quick Turnover" parts, for example, you'll get a piece of Biscayne soft luggage valued at \$42.50 manufacturer's suggested retail price. Free.

Chances are you'd order our QT package anyway. It puts the most frequently used parts right at your fingertips. And combined with the QT rack that's also available, you can streamline your inventory control. Cut reordering time. Give faster customer service.

And eliminate inventory risk.


Get in touch with your nearest participating RCA Parts Distributor and he'll show you which free luggage goes with which QT package. Or contact RCA Parts and Accessories, P.O. Box 100, Deptford, N.J. 08096.

'Offer expires June 30, 1975



Circle 80 on reader service card



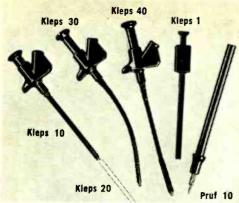


Clever Kleps

Test probes designed by your needs - Push to seize, push

All in red or black - specify. (Add 50¢ postage and handling). Write for complete catalog of - test probes, plugs, sockets, connectors, earphones, headsets, miniature components.

 Available through your local distributor, or write to:



129 Spencer Place, Mamaroneck, N.Y. 10543 In Canada: Rye Industries (Canada) Ltd.

Circle 106 on reader service card

ENJOY OLD RADIO-T

A FLICK OF THE SWITCH your new 1930-1950 book

A FLICK OF THE SWITCH is your time trip through the golden days of radio broadcasting and into the dawn of television.

Revisit "cathedral" radios, old Ham days and many more. Discover the rewards of collecting. Over 1,000 pictures make this book the 1930-1950 collector's reference. Order your copy of



next month

JUNE 1975

■ Digital Memory For Your Scope

4-channel add-on storage unit costs less than \$150 to build. It displays digital pulse chains for checking digital logic circuits.

■ Video Disc 1975

Where does it stand today? Where will it go tomorrow? Get an expert's view.

■ How R-E Lab Tests Hi-Fi Gear

Yes, we will be doing laboratory tests to measure the performance of today's hifi equipment. We'll be presenting at least two test reports in each issue. But first, we would like to explain how our tests are performed.

■ Phono Cartridges for CD-4

There are many different ones now. See how they work.

■ Using Your Scope

Practical ways you can do more with your scope. Proven techniques that you may already know, plus many that you may not have even thought of before.

PLUS

State-Of-Solid-State Jack Darr's Service Clinic Radio-Electronics' Replacement **Transistor Directory**


June issue goes on sale May 20, 1975

service questions

SPEAKER HOOKUP, OLD RCA RADIO

I'm working on an old RCA radio, a T62. Speaker's gone. I see three wires that might have gone to it; one to pin 4 of the 6F6 tube, one to pin 5, and one to a 10-4F electrolytic capacitor. How do these connect to the speaker?-K.O., Syracuse, NY.

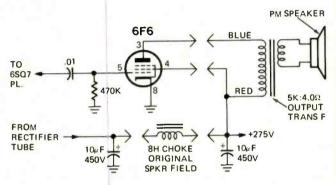Two things here; one, to hook up the output transformer, connect the primary (red and blue wires) to the plate,



pin 3, and screen-grid, pin 4, of the 6F6. That 10-µF electrolytic capacitor should also go to the screen.

The original speaker was an electrodynamic with a 1000-ohm field. This was the choke in the B+ power supply. Replace this with about an 8-henry choke, as shown in the diagram.

POWER TRANSFORMER?

The tubes all light in this Motorola TS-908Y, but that's all. No sound, practically no de voltages. Could this be a power transformer problem?-R.B., Toledo, OH.

Not likely; your tube heaters are fed from the power transformer. Most likely cause, a defective circuit-breaker, diode rectifier, electrolytic capacitor, etc. For quick checking, hook a dc voltmeter to the dc power supply output, then put a jumper across the circuit breaker. We have had some problems with these. (Field Feedback: it was a bad circuit breaker.)

CONVERGENCE: LINE? LINES?

The problem I have is in color temperature adjustments with the screen controls. When I set up the horizontal line, the red and green are perfect. But I can't get the blue line down; it's about 1/8 of an inch above. Where can I look for this problem?-L.B., Edison, NJ.

It depends on whether you mean "line" or "lines"! If this is singular, meaning the one line you see in SERVICE position, ignore it! When you set the switch to SERVICE, you kill the vertical output; also, you change the convergence waveforms. So it makes no difference whether the three (single) lines are overlapped or not.

However, if you mean "lines", as in a crosshatch pattern, this is misconvergence (NOT color-temperature). If the blue lines are straight, and won't come down to cover the yellow (R+G) lines, move them down with the static magnets. You can move the blue in any direction with these.







The All-New, Quick & Easy Way to Reproduce Printed Circuits. Get Your Kit From Your Favorite CALECTRO Electronics



Distributor Today!





DIVISION OF HYDROMETALS, INC.

ROCKFORD, ILLINOIS 61101 U.S.A.



12 REASONS YOUR CAR NEEDS TIGER CDI

Instant starting in any weather - Eliminates tune-ups - Increases gas mileage - Increases horsepower 15% - Improves acceleration and performance - Spark plugs last up to and performance - Spark plugs last up to 70,000 miles - Reduces engine maintenance expense - Amplifies spark plug voltage to 45,000 volts - Maintains spark plug voltage to 10,000 RPM - Reduces exhaust emissions - Dual ignition switch - An Unconditional LIFETIME GUARANTEE Installs in 10 minutes on any car with 12 volt negative ground - No rewiring - Most powerful, efficient and reliable Solid State powerful, efficient and reliable Solid State gnition made.

SATISFACTION GUARANTEED or money

TIGER 500 assembled \$53.95 TIGER SST assembled \$42.95 Post Paid in U.S.A.

Send check or money order with order to:

Tri-Star Corporation

P.O. Box 1727 Grand Junction, Colorado 81501

DEALER INQUIRIES INVITED

Circle 82 on reader service card

COSMOS BURGLER ALARMS

(continued from page 50)

be wired together to meet a specific alarm system requirement. In this case, the alarm is of the auto-turn-off type, and has a 'panic' facility and an intrusion recorder. The system is intended for use with a n.o. exit/entry switch, and the system incorporates an exitand-entry-delay facility, giving delays of approximately 25 seconds in each mode, and has transient suppression applied to the main sensor network. The system has provision for nonlatch activation via n.o. heat-sensing switches, and thus also functions as an automatic fire alarm.

The 'panic' facility is designed around IC2, and the intrusion-recorder is designed around IC4. Both of these sections of the circuit are permanently wired across the supply lines. The autoturn-off operation is obtained via IC1, and one of the spare gates of this IC is used to provide transient-suppression for the main-sensor network. Finally, IC3 provides the exit-andentry-delay facility. All four of the IC's used in the system are CD4001AE types. Note that the OFF terminal of key-switch S1 is connected directly to ground, to provide a discharge path for the systems timing capacitors.

(to be continued)

Now...the most enjoyable do-it-yourself project of your life-a Schober **Electronic Organ!**

You'll never reap greater reward, more fun and proud accomplishment, more benefit for the

whole family, than by assembling your own Schober Electronic Organ.
You need no knowledge of electronics, woodwork or music. Schober's complete kits and crystal-clear instructions show you - whoever you are, whatever your skill (or lack of it) how to turn the hundreds of quality parts into one of the world's most beautiful, most musical organs, worth up to twice the cost of the kit.



Five superb models with kit prices from \$575 to around \$2,300, each an authentic musical instrument actually superior to most you see in stores, easy for any musically minded adult to learn to play, yet completely satisfying for the accomplished professional. And there are accessories you can add any time after your organ is finished - lifelike big auditorium reverberation, automatic rhythm, presets, chimes, and more.

Join the thousands of Schober Organ builder-owners who live in every state of the Union. Often starting without technical or music skills, they have the time of their lives - first assem-bling, then learning to play the modern King of Instruments through our superlative instructions and playing courses.

Get the full story FREE by mailing the coupon

TODAY for the big Schober color catalog, with all the fascinating details!

The Schober Organ Corp., Dept. RE-138 43 West 61st Street, New York, N. Y. 10023

Please send me Schober Organ Catalog. ☐ Enclosed please find \$1.00 for 12-inch L.P. record of Schober Organ music.

NAME.

ADDRESS CITY_

STATE

ZIP_

SUPER BUYS!

FAMOUS MAKE, NEW JOBBER-BOXED TUBES

	80% OF	F LIST	
1 B3 1 1V2 1 2AV2 3 3AT2 3 3GK5 3 3HA5 3 3HM5 4 BZ6 6 6AX4 6 6AX4 6 6CG3 6 6CG3 6 6CG3 6 6CG3 6 6CG4 6 6CG4 6 6CG4 6 6CG7 6 6CG7	80% OF 5 for \$5.00 5 for \$3.00 5 for \$3.95 5 for \$4.90 5 for \$4.80 5 for \$4.80 5 for \$4.80 5 for \$4.80 5 for \$4.70 5 for \$5.05 5 for \$5.05 5 for \$5.05 5 for \$5.05 5 for \$4.70 5 for \$5.49 5 for \$4.70 5 for \$4.70 5 for \$5.49 5 for \$4.70 5 for \$5.55 5 for \$4.70 5 for \$5.55 5 for \$5.25 5 for \$5.25 5 for \$5.25 5 for \$5.25 5 for \$5.25 5 for \$4.35	6HA5 6HB7 6HD5 6HV5 6JC6 6JC6 6JC6 6JC8 6KB8 6KM6 6KK8 6KK8 6KK6 6LQ6 6LQ6 8FQ7 12BY7 12GN7 12GN7 33GYC 33GYC 33GYC 33GYC 33HE7 36MC6 38HE7 36MC6 38HE7 42KNG	5 for \$4.80 5 for \$4.85 5 for \$6.35 5 for \$11.80 5 for \$5.65 5 for \$11.15 5 for \$9.30 5 for \$5.55 5 for \$6.15 5 for \$7.65 5 for \$11.25 5 for \$1.25 5 for \$10.75 5 for \$11.5 5 for \$10.75 5
100-2.5 Am RCA DAMPE 4-6500 PIV 5-13.5 KV I 25-1N34A	D. 1000 PIV (ID). 100	(IR) 0818	\$11.95 .Ea. \$1.50 \$2.00 \$3.00
10 RCA PHO 5 Asst'd ST BSR-SC5MD SONOTONE	DNO EQUIP. DNO PLUGS FEREO CART. EV5540D-Cart 8-T—Cart. (E -Cart.	. (Bulk) Bulk)	\$5.95 \$1.50 \$1.25
RCA—1366	BACKS 361461-2L 40 45		\$7.95 \$6.95 \$6.95
MAGNAVUX	(ES 361340 361380-4 95AC-Y109 (U		\$6.95

EQUIV. DY 95AC-Y109 (Univ.) SILVERTONE 80-56-4G JAP YOKE 70%—(21" CRT)

BLACK & WHITE YOKES THORDARDSON—Y-105 (UNIVERSAL) ...\$7.95 THORDARDSON—Y-130 ZENITH\$7.95 ANTENNA EQUIPMENT

 2-Set Coupler
 Each ONLY \$1.49

 4-Set Coupler
 Each ONLY \$1.89

 6-ANT. CLOTHESPINS
 \$1.00

CONTROLS RESISTORS 50 Asst'd MALLORY CONTROLS\$2.59 50 Assorted W.W. Res. \$2.69 100 Assorted Carbon Resistors \$1.69

CONDENSERS CANS 200-80-Mfd. 350V ... 3 for \$1.79
200 Mfd. 80 Mfd.—350 Volts ... 3 for \$1.79
500 Mfd. 25 Volts (P.C.) ... 5 for \$1.00
90% COLOR CRT BOOSTERS ... 3 for \$11.50

SEND FOR FREE CATALOG

TUBES UP TO 80% OFF MINIMUM ORDER \$15.00

SEND CHECK OR M.O.

TV TECH SPECIALS

P.O. BOX 603 KINGS PARK, L.I., NEW YORK 11754 PHONE 516-269-0805

Circle 84 on reader service card

INVENTORY DISCOUNT SALE

RCA COLOR BAR GENERATOR

- with basic patterns
- with AC and battery power supply

Reg. Price \$89.90 Our Price \$69.50



☐ CASTLE MEZZER
Field Strength Meter

Reg. Price \$119.95 Our Price \$102.00



CASTLE TUNER SUBBER MARK IV
Reg. Price \$45.95 Our Price \$36.50

SOLDERING IRON 30 WATTS
Pencil type \$1.95

LARGE DISCOUNTS ON ALL TEST EQUIPMENT

Free Catalog of Each Manufacturer

HICKOK

FICO

Lesder

BI

SENCORE

ПСЛ

TUBES ICC/International Servicemaster

1B310 for \$11.00 1K310 for \$11.00	☐ 6EH710 for \$10.50 ☐ 6EJ710 for \$10.00
1V210 for \$ 6.50	GJC610 for \$12.50
2AV210 for \$ 9.00	6JE610 for \$25.00
3AT210 for \$11.00	8CG710 for \$ 8.50
6BK410 for \$20.00	17BF1110 for \$17.00
6CG310 for \$11.00	7 17JZ810 for \$10.00
6CG710 for \$ 8.50	23Z910 for \$13.00
6DW410 for \$10.00	33GY710 for \$18.00
6EA810 for \$11.00	38HE710 for \$20.00
☐ 6GH82	5 for \$20.00

Complete line of RCA and Raytheon tubes also available.

PARTS

Replacement Rods, 4 Sections, Extending to 38"12 for \$9.00
☐ Varco Cartridge; CN75, TN4Beach \$1.95
☐ BSR Cartridge; SX1H, 5X5Heach \$1.75
☐ Electrical Tape, ¾" x 66'10 rolls for \$4.99
Telematic CR 250 90° Color Booster5 for \$20.00
☐ Thordarson Y94, Y105, Y130each \$9.00
25 ft. Speaker Cable
RCA Plug to RCA Plug4 for \$3.90
Speaker; 6x9, 10 oz., Cloth Rolleach \$4.95
☐ 6x8 Grilleeach \$.69
AC Adapter: 6, 7, 5, 9V, 300maeach \$3,95

FREE CATALOG

Minimum order \$50.00. Send check or money order.
Add \$1.00 for shipping and insurance.

FORDHAM

RADIO SUPPLY CO., INC. 558 Morris Ave., Bronx, N.Y. 10451 Tel: (212) 585-0330

SERVICING MATV

(continued from page 90)

someone has connected sets directly to coax without benefit of a matching transformer.

Snow. If the snow is throughout the whole system, suspect the amplifier immediately. Snow in a given branch can be caused by water in a splitter or tap-off.

Snow can also be caused by anything from a new building which blocks the antenna, to a defective cable, a bad coax connector, or a TV receiver with a poor front end. You should be able to isolate snow problems with your field-strength meter.

Repairing squipment

Don't waste too much time repairing MATV equipment. Passive devices should generally be discarded rather than repaired, unless the trouble is readily apparent and easy to correct.

Of course, you can't throw away amplifiers, converters and other expensive equipment. You can, however, send them to the manufacturer's repair department.

If you want to repair amplifiers yourself and have the equipment to do it, be careful. To check the frequency response of a single-channel strip, you need a sweep-frequency generator, an RF marker generator, a good scope, and an RF detector. In some cases you may even need an impedance bridge.

Broadband amplifiers are not as tricky, since they are not as frequency sensitive. However, you still have to be careful about moving wires and coils. At TV frequencies, a short piece of wire acts as an inductance and a wire parallel to the chassis acts as a capacitor. Further, parts are sometimes very specialized. You can not substitute a standard transistor for one of the same type in most MATV amplifiers. You have to order a selected transistor directly from the MATV manufacturer.

All in all, today's well designed, properly installed MATV systems require a minimum of service. Most troubles are caused by tenant or guest abuse of the system. Since tracking down MATV troubles is relatively easy, servicing MATV systems can be quite lucrative.



THE NEW DIGITAL VOLKSMETER

World's lowest priced digital multimeter. Designed to be a more accurate replacement of delicate pointer-type meters.

MES

LM-3



\$119.95

With rechargeable batteries and charger unit

Features Include:

- Rugged Ideal for field service use
- Auto polarity no more lead reversing or switching
- Three digits with 1% accuracy on all functions
- 13 ranges: 4 vac, 4 vdc & 5 resistance
- 1 millivolt resolution with 500 volts and 10 megohms full scale
 - Small Size: 1.9"H x 2.7"W x 3.9"D

Options Include:

- Leather case \$16
- High voltage probe \$30
- Current shunts \$6 each

For immediate delivery, fill in below and mail direct to NLS.

NON-LINEAR SYSTEMS, INC. Box N, Del Mar CA 92014 PH (714) 755-1139 - TWX 910-322-1132

☐ Special offer of \$119.95 with your check and coupon. ☐ Single unit price of \$125.00 C.O.D. or valid purchase order.

One year guarantee.

Name

Company

Address

City

Zip

California Residents Add 6% Sales Tax
Offer expires in 90 days
1234 6789101112 ★ 23456789101112

market center

CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services). **\$1.40 per word** . . . minimum 15 words.

NONCOMMERCIAL RATE (for individuals who want to buy or sell personal items) 85c per word . . . no minimum.

FIRST WORD AND NAME set in bold caps at no extra charge. Additional bold face at 10c per word. Payment must accompany all ads except those placed by accredited advertising agencies. 10% discount on 12 consecutive insertions, if paid in advance. All copy subject to publisher's approval. Advertisements using P.O. Box address will not be accepted until advertiser supplies publisher with permanent address and phone number. Copy to be in our hands on the 26th of the third month preceding the date of the issue (i.e. August issue closes May 26). When normal closing date falls on Saturday, Sunday or a holiday, issue closes on preceding working day.

WANTED

QUICK cash . . . for electronic equipment, components, unused tubes. Send list now! BARRY, 512 Broadway, New York, NY 10012, 212 Walker 5-7000

COMPUTER printed circuit boards and equipment. Send list now! FLATIRON ENTERPRIZES, 4654 Harwich St., Boulder, CO 80301

EDUCATION & INSTRUCTION

ELECTRONICS book discounts. Save! Free selected, reviewed list. T/DOC, Box 340, Centerville, VA 22020

LEARN design techniques. Electronics monthly newsletter. Digital, linear construction projects, design theory and procedures. Sample copy \$1.00. VALLEY WEST, Box 2119-A, Sunnyvale, CA 94087

US converting to metric. Everyone must learn. Simplified university mini course. Tuition \$5.00 to: MIT, Science Dept. 302, 8002 Downing Circle, Tampa, FL 33610

TELEPHONE bugged? Don't be Watergated! Countermeasures brochure \$1.00. NEGEYE LABORATORIES, Box 547-RE, Pennsboro, WV 26415

MANUALS for Govt. surplus radios, test sets, scopes, list 50c (coin). BOOKS, 7218 Roanne Drive, Washington, DC 20021

TV tuner repairs—Complete course details, 12 repair tricks. Many plans. Two lessons, all for \$2. Refundable, FRANK BOCEK, Box 3236 (Enterprise), Redding, CA 96001.

PLANS & KITS

BRAND new! Six-digit alarm clock IC — Mostek MK60250 — Full feature, snooze, dimming, with schematics plus data sheets, \$5.95 — Kit of six 0.6" LED's, like DL-747 \$11.70! All new, guaranteed parts. Catalog 25c, redeemable. DIAMONDBACK ENGINEERING, P.O. Box 194, Spring Valley, IL 61362

CONVERT any television to sensitive, bigscreen oscilloscope. Only minor changes required. No electronic experience necessary. Illustrated plans \$2.00. SANDERS, Dept. A-25, Box 92102, Houston, TX 77010

PASS FCC EXAMS MEmorite, study—Tests. Answers for FCC 1st and 2nd class Redictelephone licenses. Newly revised multiple choice questions and diagrams cover all occess tested in FCC enam. plus Self-Study Ability Test. 59-95 postpaid. Money-bock gworantee. COMMAND PRODUCTIONS P.O. BOX 76348 E RADID ENGINEERING DIV SAN FRANCISCO. CAL 94176

FREE catalog. Most unusual electronic kits available. Music accessories, surf, wind synthesizers, wind chimes, many others. PAIA ELECTRONICS, Box B14359, Oklahoma City, OK 73114

FUNCTION and pulse generator. Laboratory features and specifications. Plans \$3.00 each, both \$5.00. Send dime for complete specifications. INSTRUMEX, Box 284, Ambler, PA 19002

NEW organ kit builders manual \$3.00. Circuits, block diagrams, details on diode keyed IC divider and independent oscillator designs. Many new kits and models. Keyboards also for synthesizers. Manual cost refundable with purchase. DEVTRONIX ORGAN PRODUCTS, Dept. B, 5872 Amapola Dr., San Jose, CA 95129

EM synthesizer concept-features universal compatibility, modular construction. For complete information send SASE or 25c to: CFR ASSOCIATES, POB F, Newton, NH 03858

SS.95 ppd CMOS SAMPLER

NOW YOU CAN EXPERIMENT WITH THIS POPULAR LOGIC FAMILY AT SUBSTANTIAL SAVINGS. WE SEND YOU 2 EACH 4001, 4009, 4010, 4018, 4025, AND 1 EACH 4016 AND 4116. PINOUT CHART AND DATA SUPPLIED.

HOBBYIST WIREWRAP **GUN**

Everyone needs a wire wrap gun; now you can afford it. Comes complete and ready to go with charger, rechargeable batteries, and bit. Cut your project time to shreds for

41.95 ppd

GIVE US YOUR ADDRESS & A STAMP AND WE'LL SEND YOU THE STORY ON OUR TIL, OTHER CMOS, LINEARS, LEDS, MUSICIAN'S KITS, POWER SUPPLIES, READOUTS, COM-PONENTS, AND MORE. OUR FLYER TELLS ALL. SEND FOR IT! BE SURPRISED.



5 function (+ - x ÷ %) plus separate memory and constant registers. Floating point, 8 digit, timed display turnoff, low battery indicator. Kit complete with instructions, all parts, and handsome gray case, but less batteries.

\$17.95

CALCULATOR KIT

MEMORY

Here is the ideal memory for the minicomputer hobbyist, for half-a-cent a bit. Compatible with the MK 8 and other 8008-8080 minicomputers. Comes complete with double-sided, plated through PC board, 32-2102 NMOS static 1K memories, 2-7442, 2-7404, and 1-7400. SOCKETS FOR ALL ICS INCLUDED. Runs on standard +5 VDC. All this

\$163.84_B



TERMS: INCLUDE POSTAGE
ON TITEMS WHEN INDICATED;
ALL OTHER ITEMS SHIPPED
POSTPAID. CALIFORNIA
RESIDENTS ADD TAX. FOR
MASTERCHARGE OR BANKAMERICARD ORDERS, CALL
(415) 357-7007. SORRY,
NO COD.

MOVING?

Don't miss a single copy of Radio-Electronics. Give us:

Six weeks' notice

Your old address and zip code

Your new address and zip code

name

address

(please print)

ATTACH

LABEL

HERE

city state

zip code

Mail to: Radio-Electronics
SUBSCRIPTION DEPT., BOULDER, COLO.
80302

by Poly Pal





MONSANTO TYPE	CHAR. HT.	SALE EACH	Quantity Discounts
MAN-1	.27	\$3.50	3 for \$ 9.
MAN-2	.32*	4.95	3 for \$14.
MAN-3	.12	1.00	3 for \$2.50

Epox	YSIL	.ICC	ON BE	RIDG	E RE	CTIFI	ERS
Full Wave	PIN		Amp	6 Am		AMP	2
wave	100		5 .69		99	\$1.49	m
1	200		.95	1.	25 🗆	1.89	W
20	600		1.19		75	2.09	W
1111	800		1.59	1.	95 C	ode: 2 a	
1111	1000		1.79		25 T		



\$24.50

MM5203 Eraceable ultra-violet PROMS! Quartz lid. 2048 static, Specs

☐ MM5202 (1702) like above — \$24.50

DKit of a IC'S \$99. 8008 Microprocessor with 8-2102/2602 n channel "STATIC" 1000 BIT RAM'S, Requires single 5 VDC power supply, Specs.



уре М300

Usually called "Microprocessor" — It is a p Channel Si gate MOS 8-bit Parallel Central Processor A CPU Central Processor Internation of the Contral Processor A CPU Only 16K x 8 bits of memory (RAM, ROM, SR). Build a micro-computer system when interfacing with other chips, such as 1101, 1103, 2102 (RAMS), etc. With spec sheets, 16-pin dip package, \$59,95

2102 1000-bit 'static" Ram for above.

16-BIT MICRO PROCESSOR BASIC The lowest-priced 18-bit system! Quiperforms the 8008. SYSTEM

8

The lowest-priced 18-bit system! Outperforms the 8008. The CPU (Central Processing Unit) includes 4-MM5750's, called RALU's, and one MM6751 CROM. RALU — called Register and Arithmetic Logic Unit — is a 4-bit control bus, and the CROM is a Control-and-Read-Only Memory. The four RALU's in parallel form a 16-bit unit. The RALU's are controlled by micro-lastructions, stored in the CROM. With spec sheets.

"GIANT DIGIT" READOUTS

3 for \$12.

□ \$4.50 each



RAYTHEON-RCA Buy 3 — Take 10 % NATIONAL CODE SIGNETICS

State 1st, 2nd, 3rd Choices of Case Styles LINEAR *State Voltages 5 thru 24 (D) = Duals; (Q) = Qua IC'S

WRISTWATCH LIQUID CRYSTAL DISPLAY



INDUSTRIAL SPEED CONTROL - \$4.95

\$9.95 3½ digit, 7-segment only 1 1/16 x 11/16 x 1/1/6 x 1/1/6





8.88 707 and 704, Opcos's S ter heights of 0.33 at cludes 3x2" p.c board (the la Cuttes 352" p.c board with fingers for a FREE economic try, side-mounting dip socket, LED readout MARIA 139 h. Monanto your choice, resistors, 3 ICh, and Molex connect 700". 335 h. Utrosic bioshiet. INCLUDES P.C. EDCC CONNECTOR — FREE STATE 335 h. Cutter of the second of the second



D555 OR 558 2 for \$1 Sale good till XENON FLASH STROBE \$1.95



June 15,1975

BIGGEST THAT'S RIGHT! MAN-7's at the rendout sale of the rendout sale of the gentury! The MAN-7' at the rendout sale of the gentury! The MAN-7' at the rendout sale of the gentury! The MAN-7' on 1N4000 SECTIFIER PRICES like, the MAN-1. Pin connections same, Wide angle viewing. 0.27" character height, color red.

| Type | PiV | Sale | 1N4001 | 50 10 for 45c | 1N4002 | 100 11 for 55c | 1N4003 | 200 10 for 65c | 1N4003 | 400 10 for 75c | 1N4004 | 400 10 for 75

"PROFESSIONAL" 60 WATT AM-FM MUX TUNER AMP

MAN-5 as MAN-7 except green 1.49 MAN-8 as MAN-7 except yellow 1.49

Туре	PIV	Sale
1N4001	50 10	for 45c
☐ 1N4002	100 10	for 55c
☐ 1N4003	200 10	for 65c
☐ 1N4004	400 10	for 75c
☐ 1N4005		for 85c
☐ 1N4006	800 10	for 99c
☐ 1N4007	1000 10	for 1.29

Size 0.7 0.7 o 7-SEGMENT 0.6 e Reflective bar 0.6 25 mila per seg 0.6 *TIL compatible nocket* DCMs. etc. NATIONAL GAS DISCHARGE NUMERICAL DISPLAY POWER SUPPLIES DISPLAY PANEL \$3.95 22236859 CODMINA \$5.95 3 for \$15 Type NDP1252 cold cath-

Type NDP1252 cold cathode gas discharge. 7-seg-ment/8-digit symbols minus, overflow and dot. Properly multiplexed. Like Burroughs Panaplex-Two. Color: OR-ANGE. Used in calculators cauping the color of the color of

Same as the 9-digit Pan-aplex Two and the Na-tional unit, but 11 digits with socket\$6.95



a x 3" pc board power sup-ply with brightness control for the NDP or any gas dis-charge tubes. Completely wired. As extra feature has calculator clock circuit. The calculator clock circuit. The transformer is the new Toroidal transformer itself worth our asking price. Only $\frac{1}{2} \times \frac{1}{2}$ ". Electrical specs 110 vac input, output. With sheet. LM566 2
LM567 2
LM703
LM703
LM703
LM709
LM710
LM711
LM723
LM733 1
LM741
LM741CV
LM747(D)
LM741CV
LM748
LM1004
LM1800 1
LM1800
LM1800 LM380-8 LM380 LM381 LM382 LM531 LM532 LM533 LM536 LM540 LM555 LM558 LM560 LM560 LM561

8 WATT STEREO AUDIO AMP The factory "snipped" most of the cables to this compact 8 watt stereo unit
marked ready to use. With power supply. 115vac. 3
controls. LEFT and RIGHT VOLUME Controls for two
speakers for balancing and center TONE control. With
knobs. 7 x 3/y x 3/2, 1 lookup speakets.

\$3.98 - 2 for \$7 0 0 5 WATT AUDIO 35 WATT AUDIO

For Class AB use. Basic includes: Signetic 840.30 transistor high power driver TO-5 "IC", with a pair of complimentary 35-watt plastic transistors, i.e. 2N5296 npn and 2N6109 ppp. With schematics, printed circuit and parts board layouts.

BUY 10 IC'S TAKE 15% - BUY 100 TAKE 25%

Inflation-Fighting ECONOMY IC PRICES



Type	Sale	Maria in tale indi	under Ste	be, russing our radio	dest ON	L) · Pacto	ry Mark	ed .	
☐ SN740		☐ 5N7438	.49	☐ SN7481	1.25	SN74141	1.19	☐ SN74191 1.	4
SN740		☐ SN7440	.19	□ SN7482	.99	SN74145	1.19	SN74192 1.	
SN740	2 .22	☐ SN7441	1.00	☐ SN7483	1.19	SN74148	2.95	SN74193 1.	
☐ 5N740			1.00	SN7486	.49	☐ SN74150	1.19		
☐ SN740		SN7 443	1.00	SN7489	2.95	SN74151		SN74195 1.	
☐ SN740		SN7444	1.00	SN7490	1.81		.99	SN74197 1.	
☐ SN740		SN7445			1.35	SN74153	1.39	SN74198 2.	
SN740			1.00	SN7491		U SN74154	1.69	SN74199 2.4	4
☐ SN740			1.10	SN7493	.99	SN74155	1.29	☐ SN74200 7.5	5(
		SN7447	1.10	☐ SN7495	.99	☐ SN74156	1.45		
SN741		☐ SN7448	1.45	SN7496	.99	SN74157	1.45		
U 5N741		SN7450	.27	SN74100	1.55	SN74158	1.45	1	_
☐ SN741		SN7451	.28	SN74104	1.25	SN74161	1.59	02 3	
SN741		SN7453	.28	SN74105	.95	SN74163	1.75	1 1 2	
☐ SN741		SN7455	.28	SN74106	.95	SN74164	2.85	1)	
SN741		☐ SN7462	.39	☐ SN74107	.49	SN74165	2.85	11000	
SN741		☐ SN7464	.39	SN74108	.95	☐ 5N74166	1.85	11	
SN742		☐ SN7465	.39	☐ SN74112	.95	☐ SN74173	1.85		į.
SN742	.29	☐ SN7471	.55	SN74113	.95	☐ 5N74174	2.25	19 6401	1
☐ SN742	.32	☐ SN7472	.42	□ SN74114	.95	☐ SN74175	1.99	POR ELP	
☐ SN7425		☐ SN7473	.52	SN74121	.49	□SN74176	1.25	- 000	3
☐ SN7426		☐ SN7474	.39	SN74122	.55	SN74177	1.25	Money-Back	
☐ SN7427		☐ SN7475	.91					Coney-Back	П
SN7430		□ SN7476	.52		1.09	SN74180	1.10	GUARANTEE	
☐ SN743		SN7478	.79		.65	U 5N74181	3.95	on all items	ч
SN743				SN74126	.89	☐ SN74182	1.05		J
U 3R/43	.45	☐ SN7480	.59	☐ SN74140	2.50	☐ 5N74190	1.49		

The finest built 60 watt tuner amp we've had for years. We call it THE AUDIOPHILE BUY OF THE YEAR! It compares to Fisher and II H Scott quality. Crisp hi's, organ type quality for the lows. Fine linear response using a pair of 35 watt style matched hower tab transistors for each channel. Built-in preamp for using magnetic cartridges, black and chrome-silver look molded panel with glass already attached to tuner. It's made to JUST SLIDE INTO CABINET. Push-hutton features for phono, am. fm. fm stereo, tape. Red "FM and TAPE" show on glass. You can't see dial plate behind glass it! you press any of the above push buttons, and then the scale Illuminates. Two separate rocker switches for POWER ON-OFF and AFC Controls. Modern slide volume, balance, bass and treble control. Worldern slide volume, balance, bass and treble control would be sufficiently and the sufficient speakers. Jack on panel for standard stereo head-phones. Built-in AM and FM antennas. REAR CONNECTIONS: has two separate cables to plus into stereo, hono system. AC cable for interconnect power to turn-table, cable to connect to phono system for automatic shut-off. Separate bakelite panel that you can add an additional FM antenna for "souping up" signals, stereo jacks for Playback and record for external tape decks. 4-WAY SPEAKER SYSTEM with switch to any channel individually for testing. Wt. 5 lbs.

3 for \$6. 5 7-SEGMENT OPCOA SLA-1 \$2.50 TREFLECTIVE Litronix 704 LED READOUT itronix □ Red □ Yellow □ Green

Terms: add postage Rated: net 30 Phone Orders: Wakefield, Mass. (617) 245-3829 Retail: 16-18 Del Carmine St., Wakefield, Mass. (off Water Street) C.O.D.'S MAY BE PHONED ☐ 20c CATALOG Fiber Optics, 'ICs', Semi's, Parts

MINIMUM ORDER - \$4.00 POLY PAKS P.O. BOX 942R. LYNNFIELD. MASS. 01940



Circle 91 on reader service card

CONSTRUCTION plans telephone surveil-lance others, catalog free circuits, \$1.00. ALLEY SERVICE, 233 Laurelton, Rochester, NY 14609

FOR SALE

FREE bargain catalog. Ultrasonic devices, LED's, transistors, IC's, keyboards, Xtals, unique components. CHANEY'S, Box 15431, Lakewood, CO 80215



RECONDITIONED test equipment. \$0.50 for catalog. WALTER, 2697 Nickel, San Pablo,

\$5.25

\$.40 \$.60 \$.40 \$.30 \$.40 \$.50

.80

ME-4 IR LED MT-2 PHOTO TRANS

16 PIN DIP SOCKETS

10 WATT ZENERS 3.9, 4.7 OR 18V 1. WATT ZENERS 5.6,

.11 600

100 .06 .14

200 .07

400 .09 .25 .30

10. 12, 15, 18, OR 22V\$.40 EA.

Silicon Power Rectifiers 1A 3A

.20

.30

.50

.35 1.15

.70 1.80

GREEN GAP OSL-16 LED RED GAP OSL-3 LED 14 FIN DIP SOCKETS

DELTA Mark Ten-B, 12V negative ground, \$37.50 ppd. BERCOM ELECTRONICS, P.O. Box 237, Bergenfield, NJ 07621

DIODES, Mallory 2½A, 1000V. 10/\$2.00, 50/\$8.00, 100/\$15.00, 1000/\$120.00. BECO, INC., Box 686RE, Salem, VA 24153

PC boards, from magazine page; original; magic marker; art ½:1, 1:1, 2:1 scale size. \$3.30 up. BECO, INC., Box 686RE, Salem,

WHOLESALE electronics components. Catalog of bargains, 25c refundable W/order. ATLANTIS, P.O. Box 12654R, Tucson, AZ

ELECTRONIC Ignition: Capacitor, transistor, pointless. Auburn sparkplugs. Information 10c. ANDERSON ENGINEERING, Epsom, NH

COMPONENTS, new and surplus. 10c stamp for latest flyer jammed with bargains in new and industrial surplus components. TRI-TEK, Box 14206, Phoenix, AZ 85063

DIGITAL logic lab kit. Everything needed to design, build logic circuits. Manual teaches design build logic circuits. Manual teaches theory, TTL design techniques. Build clock generator, gate circuits, counters, seven segment display, etc. LED's indicate logic states. Electrical parts, sockets, perfboard, manual, \$19.95 postpaid. With +5V logic supply kit, \$39.95. VALLEY WEST, Box 2119-X, Sunnyvale, CA 94087

SYNTHESIZER circuit handbook, keyboards, modules, kits, Write for free information to: SYNECTIC MUSIC SYSTEMS, P.O. Box 30531, Seattle, WA 98103

FREE flexible magnetic strip with, 20 dics, or 10 bar, or 2 stick, or 8 assorted magnets, \$1.00. Any 5 sets, \$4.50. MAGNETS, Box 192-FF, Randallstown, MD 21133

MM5314N clock chip 4.50, DL747 readouts \$2.50. LECTRONIX, Box 47, Madison Heights, MI 48071

HOLD-IT! A new precision electronic product. Details free. INNOVATIVE CONCEPTS, 4018 Clarke, Ft. Worth, TX 76107

SURPRISE! Build inexpensively, the most unusual test instruments, futuristic gadgets using numerical readouts! Catalogue free! GBS, Box 100B, Greenbank, WV 24944

MiniMicroMart

Supermaket of Microprocessor Values

8008's - 8080's Memories
Microprocessor Kits & IC's-also for Mark 8Allair 8800-Scelbl. Write for detalls.

1618 James St., Syracuse, N.Y. 13203 315/422-4467

NEW Canadian Magazine, "Electronics Workshop", \$5.00 yearly, sample \$1.00. ETHCO, Box 741 "A", Montreal

ETHCO, Box 741 "A", Montreal

MF8008R, 8bit CPU: \$55.00; 8038, VCO: \$4.95; MM5203Q-1. 2048 RE-PROM: \$16.50; CT7001: \$8.95; NEC6003, 2048 RAM: \$9.00; MF2102, 1K RAM: \$9.00; 1103A-2, 1K RAM: \$3.95; MCM7001, 1K RAM: \$8.95; 8111, 1K RAM: \$12.25; 8T97, hex inv: \$3.50; 3106, 256 RAM: \$2.25; NE526 volt. compar: \$1.55; AY5-1008, TTY RX: \$6.00; AY5-1010, TTY TX: \$6.00; AY5-1010, TTY TX: \$6.00; AY5-1010, TTY TX: \$6.00; AY5-1010, TTY DEMOD: \$6.00; XF2240, prog. timer: \$5.95; SPDT, CTROFF, moment. mini toggle: \$1.95; (same function, slide sw: \$1.00); ribbon (same function, slide sw: \$1.00); ribbon cable, 13 twisted pair: 7FT/\$4.00, ELECTRONIC DISCOUNT SALES, 138 N. 81st ST., Mesa, AZ 85207

FREE giant bargain electronic catalog listing thousands of components, tubes, transistors, IC's, kits, test equipment. EDLIE'S 2700-RA Hempstead Tpke., Levittown, NY 11756



DIGITAL/analog multimeters, logic probes-guaranteed lowest prices. Free catalog. guaranteed lowest prices. Free catalog. ELECTRO INDUSTRIES, 4201 Irving Park, Chicago, IL 60641

DIGITAL electronics! Complete schematics, parts lists, theories—Discrete Component Digital Clock, \$3.00. Increase technical competence, hobby skills—Complete course in Digital Electronics is highly effective, \$10.00. Free literature. **DYNASIGN**, Box 60R2, Wayland, MA 01778

JAPANESE transistors, wholesale prices, free catalog. WEST PACIFIC ELECTRONICS, Box 25837, W. Los Angeles, CA 90025.

WANTED Heathkit IM-25 voltmeter. Write: JAMES WIESE, Prairie Village, Booneville, IA 50038

S1883 UART. \$11.95 postpaid. DATRON-R5, Box 26456, Denver, CO 80226

FREE catalog. IC's, Semi's. CORONET ELECTRONICS, 649A Notre Dame W., Montreal, Que., Canada, H3C-1H8 US Inquiries.

INTEL 8008 8 BIT MICRO PROCESS- ING CHIP (with data book)\$64.50 2102A-1024 BIT RAM\$ 6.95 1702A UV PROM\$24.00	TRANSISTOR SPECIALS 2N4898 PNP TO-66 \$.60 2N404 PNP GE TO-5	C/MOS (DIODE CLAMPED) 74C 02 \$.55 CD 4022 \$2.10 74C 165 \$3.50 CD 4023 \$.53 CD 4001 \$.53 CD 4024 \$2.15
MINIATURE TRIM POTS 5K, 10K, 25K, 50K, 100K \$.75 ea. 3/\$2.00	MPSA13 NPN Si TO-92	CD 4002 \$.53 CD 4025 \$.50 CD 4006 \$3.60 CD 4026 \$5.00 CD 4007 \$.60 CD 4027 \$1.20
MULTI-TURN TRIM POTS Similar to Bourns 3010 style, 3/4" x 1/4"; 50, 100, 500, 2000, 5000, 10,000 ohms. \$1.50	2N3055 NPN SI TO-3 \$1.00 2N3904 NPN SI TO-92 4/\$1.00 2N3906 PNP SI TO-92 4/\$1.00 2N5296 NPN SI TO-220 \$.50 2N6109 PNP SI TO-220 \$.55	CD 4009 \$.80 CD 4028 \$2.75 CD 4010 \$.53 CD 4029 \$4.80 CD 4011 \$.53 CD 4030 \$.53 CD 4012 \$.53 CD 4035 \$2.30 CD 4013 \$1.00 CD 4042 \$2.75
LIGHT ACTIVATED SCR'S TO-18, 200V 1A \$1.75	2N3866 NPN Si TO-5 Si RF PDWER \$.75 MJ2252 NPN Si TO-66	CD 4015 \$3.35 CD 4046 \$3.75 CD 4016 \$1.05 CD 4047 \$3.60 CD 4017 \$2.70 CD 4050 \$1.05
PRINTED CIRCUIT BOARD 4½" x 6½" single sided epoxy board, ¼" thick, unetched \$.50 ea. 5/\$2.20	200V 4.7 uf ELECT\$.30 LED RÉAD 200V 4.7 uf ELECT\$.30 MAN-3 RE	CD 4019 \$1.20 CD 4055 \$3.20 ed or Yellow Full Wave Bridges OUT\$2.50 PRV 2A 6A 25A ADOUT \$1.75 200 .95 1.25 4.00 ADOUT \$2.00 400 1.15 1.50 5.00\$4.50 600 1.35 1.75 6.00
MC14435 & MC1405L A two piece 3½ digit A/D converter system for panel meters and DUM's \$39.95	NEC 6003 2048 bit RAM, \$9.50 HOLI 1101 256 bit RAM \$1.75 5314 8225 64 bit-write RAM\$2.75 COU	1 — CLOCK CHIP 6 DIGIT BCD D COUNT, OUTPUT STROBE \$6.75 1 — CLOCK CHIP 6 DIGIT HOLD NT, OUTPUT STROBE\$6.75 6 — ALARM CLOCK CHIP\$6.75

2513 — 64x7x5 CHARACTER GEN

Si 1050 E 50 WATTS

4 WATT IR LASER DIODE

- 64x6x8 STATIC CHARACTER GEN.

SANKEN AUDIO POWER AMPS

LINEAR CIRCUITS

\$9.95

\$ 6.40

2N4891 UJT \$.50 ER900 TRIGGER DIODES 4/\$1.00 2N6028 PROG. UJT \$.75	solid state cameras with appli cations \$249.00 8223-PROM \$4.75			
VERIPAX PC BOARD This board is a 1/14" single sided	MM5203-2048 BiT ERASABLE PROM\$24.00			
paper epoxy board, 4½"84½", DRILLED and ETCHED which will hold up to 21 single 14 pin IC's or 8, 16 or LSI DIP IC's with busses for power supply connections. Is also etched for 22 pin connector.	Conductive Elastometer low profile calculator keyboard. 234" × 314" × 12" flex key 19SK-6 keyboard having 0-9, • +, -, ×, +, -, K+C button with off, on switch\$6.00			

CT5005 12 DIGIT CALCULATOR CHIPS

TTL IC	SERIES
74L0030	747645
740017	748061
740117	7483— .99
740217	7485-1.30
740317	748648
740421	749071
740521	7491-1.10
740637	7492— .75
740737	7493— .71
740823	749585
741017	749685
741127	8267-1.95
741245	74107— .45
7413— .73	7412155
7416— .37	7412391
7417— .37	74125— .65
742017	7412670
7425— .37	7415099
7426— .27	74151— .85
7427— .31	74153-1.05
743017	74154—1.49
743227	741 55 —1.05
7437— .41	74157—1.19
743835	74163—1.49
7440— .17	74164-1.79
744195	74165—1.79
7442— .95	74173—1.55
7445—1.05	74175—1.80
7446-1.10	74177—1.50
7447-1.10	74181—3.50
7448—1.10	74192-1.45
7472 33	7/1031 30

, on switch\$6.00	LINEAR CIRCUITS	
10 01017	LM 309K 5V 1A REGULATOR	\$1.50
12 DIGIT ATOR CHIPS\$7.95	723 —40 +40V REGULATOR 301/748-Hi Per. Op. Amp. LM 320 —5 or —15 V REG	\$.58
TOR CHIPS\$7.95	301/748-Hi Per. Op. Amp	\$.30
TTL IC SERIES	LM 320 -5 or -15 V REG	\$1.75
LLF IC SEKIE?	LM 376 —V to 37V POS REG. 741A or 741C OP. AMP.	\$.58
— .30	741A or 741C OP. AMP	\$.31
— .17 7480 — .61	709C OPER. AMP.	\$.25
— .17	340T-5, 12, 15, 18, 24V POS. REG. TO-220	
17 7485—1.30	POS. REG. TO-220	\$1.75
— .17	101 OPER, AMP, HI PERFORM	\$.75
21 749071	LM 308 Oper. Amp., Low Power	\$1.05
— .21 7491—1.10	747—DUAL 741	\$.75
— .37	747—DUAL 741. 537—PRECISION OP. AMP	\$2.60
— .37 7493 — .71	LM 3900-QUAD OP. AMP	\$.49
− .23 7495 − .85	LM 324-QUAD 741	\$2.20
7476 45 - 30 7476 45 - 17 7483 99 - 17 7485 130 - 17 7485 - 130 - 17 7486 48 - 21 7490 - 71 - 21 7490 - 71 - 21 7491 - 110 - 37 7492 - 75 - 37 7493 - 71 - 23 7495 85 - 27 8267 - 195 - 45 74107 45	560-PHASE LOCK LOOP	\$2.50
27 <u>8267</u> —1.95	561-PHASE LOCK LOOP	\$2.50
	565-PHASE LOCK LOOP	\$2.50
— .73 74121— .55	567—TONE DECODER	\$2.85
— .37 74123— .91	703—RF-IF AMP	\$.41
37 74125— .65 17 74126— .70	LM370-AGC SQUELCH AMP	\$1.15
17 74126 — .70	555-2 μs - 2 HR. TIMER	\$.88
— .37 74150— .99	1456 OP. AMP	\$.95
27 74151— .85	CA 3054 TRANSISTOR ARRAY	\$.75
31 741 5 3-1.05	LM 380-2W AUDIO AMP	\$1.39
17 74154—1.49	LM 377-2W Stereo Audio Amp.	\$2.50
27 74155—1.05	LM 381-STEREO PREAMP	\$1.69
41 74157—1.19	LM 382-DUAL AUDIO PREAMP	\$1.69
35 74163—1.49	LM 311-HI PER. COMPARATOR	\$.95
17 74164-1.79	LM 319-Dual Hi Speed Comp.	\$1.15
95 74165—1.79 95 74173—1.55	LM 339-JUAD COMPARATOR	\$1.45
1.05 74175 1.00		
-1.05 74175—1.80 -1.10 74177 1.50	TRIACS SCR'S PRV 1A 10A 25A 1.5A 6A	
-1.10 74181-3.50	PRV 1A 10A 25A 1.5A 6A	35A
-1.10 74177—1.50 -1.10 74181—3.50 -1.10 74192—1.45	100 .40 .70 1.30 .40 .50	1.20
22 74102 1.45		-

200 .15 .35 90 1000 .20 .45 1.10 REGULATED MODULAR POWER SUPPLIES 15VDC AT 100ma 115VAC INPUT \$24.95 5VDC AT 1A, 115VAC INPUT \$19.95 IN 4148 (IN914) 14/\$1.00 8038C IC VOLTAGE CONTROLLED OSCILLATOR\$4.95 74193—1.30 74195— .89 75324—1.75 75491—1.10 7472— .33 7473— .41 7474— .41 7475— .71 Terms: FOB Cambridge, Mass. Send Check or Money Order. Include Postage. Minimum Order \$5.00.

SOLID STATE SALES

WE SHIP OVER 95% OF OUR ORDERS THE DAY WE RECEIVE THEM

200 .70 1.10 1.75 .60 .70 1.60 400 1.10 1.60 2.60 1.00 1.20 2.20

600 1.70 2.30 3.00

TUNER TORNADO = 9,95 for A



AM TUNER WITH BUILT-IN AMP

- Slide-Rule Dial Covers (10-watts Peak Power)
- ALL SOLID STATE!!!

For the Audiophiles who are seeking an economy hisf AM only at our give-away price! Never advertises before. Same quality and construction as our 20W to 60W units. Features: 4 controls; Tuning, Tone, ON/OF! Volume, Circuit Switch (AM-phono), 2-Speaker steree effect system, 6-ft, power cord, Phono cables, with hookups, 115 VAC, 60 cycles. No escutcheon, Size: $10\frac{9}{26} \times 5\frac{3}{8} \times 3\frac{1}{2}''$ deep, Wt, 3 lbs.

AM - FM **\$19.95** Never before have we ever seen such a combination of AM and FM with bullt-in high quality at such a low price. A "natural" for the economy-minded Audionhile Features: Tuning Tone, ON/OFF Volume, Balance, Circuit Switch (AM, FM, FM, AFC, phono). 2-Speaker stereo effect system. 6-ft, power cord, Phono cables, with hook-ups, 115 VAC, 60 cycles. No escutcheon. Size: 13 x 7 x 3½" deep, Wt. 3 lbs.

GIANT SALE ON LED'S

LIGHT EMITTING DIODE GAAS INDICATORS



COUPLERS 2- MCT2, 1500V Isolation photo transistor ...

SEMI-KON Dollar Stretcher

10-1N82 GERMANIUM UMF diode, clip-in type*

2-EPOXY 2-AMP SILICON BRIDGE RECT. 1000 V "comb. type"

10-MOS FETS, 3N187, 3N200, 3N128, TO-18, Fairchiid*

5-SCR5 & TRIACS up to 25 amps. 6-12-24 prv. studs too

2-2N3819, Tevas, N channel, 6500 umbn TO-18

2-2N3648 UNIJUNCTIONS, plastic transistors, Texas

50-SILICON, glass rectifiers, capituler, axial leads*

50-SILICON, glass rectifiers, capituler, axial leads*

6-1-MP 1000 PIV, epoxy, aubmini, silicon rectifiers

50-1-W ZENERS, axial 4, 6, 9, 10, 12V rectifiers, et

4-2N3055, HOBBY, 40W npn silicon transistors, TO-3

30-3-AMP RECTIFIERS, silicon. epoxy, assorted V, axial*

2-ZM529 35-WATT NPN PLASTIC TRANSISTORS, for NE-540 2 - 2N5296 35-WATT NPN PLASTIC TRANSISTORS, for NE-540 S1. 2 - 2N6109 40-WATT PNP PLASTIC TRANSISTORS, for NE540 S1.

1 — PHOTO TRANSISTOR, with darlington amp filter, \$1 2 — PHOTO TRANSISTORS, with darlington amp. 2N5777, GE. . \$1

2 — PMOTO TRANSISTORS, with darlington amp. 2N5777. GE. 81

5 — EN900 TRIGGER DIODES for SCR& & Triacs.
2 - FET'S 2N5457 N channel 5000 umbos, TO-92 plastic.
10 — 1N914 fast switch diodes, silicon. 4 manoseconds.
2-Sylvanis 18,000V Matchstik TV rectifier, 4"x ½, with leads.
50 — ITT MICRO MINI RECTIFIERS silicon porcelain to 1KV'.
50 — WORDLO'S SMALLEST RECT. & zeners, 1W, assorted volts'.
10 - 6000 PIV 50 mil epoxy rectifiers, axial leads'.
10 - BENDIX 25 WAST ''pellet''. power transistors, silicon'.
3-DARLINGTON, powers, plastic. IIFE up to 60K, 6W, 30V...
10 - POWER TABS, plastic includes Darlingtons, HI AMP, HI VS.
1 - 2N5036 HI.PWR plastic trans 100 vceo, 7 amp 85 watts.
4 - 2N5036 HOBBY, 35 watts, plastic powers, NPN.
4 - 2N5108 HOBBY, 40 watts, plastic powers, PNP.
5 - PLASTIC 35W powers, pnp., silicon, hobby 2N6121.
5 - PLASTIC 35W powers, pnp., silicon, hobby 2N6121.
5 - PLASTIC 35W powers, pnp., silicon, hobby 2N6121.
5 - MOS FETS, N channel 10K umon 3N12R, TO-18, RCA.
2 - MOS FETS, DUAL GATE, N chan, 3N187, TO-18, RCA.
2 - MOS FETS, DUAL GATE, N chan, 3N187, TO-18, RCA.
4 - RCA 2N3600 NPN, UHF transistors, tv-fm, TO-18, 1000mc.
2 - 2N5655 200 her, 250 vceo. power tab. 1-5316 CLOCK CHIP, hobby 2-5005 MEMORY CALCULATOR CHIPS, 28-pin HOBBY 5-555 TIMERS, mini DIP, hobby 10-741 OP AMPS, mini DIP HOBBY

I.C. & LED HOBBY-ONICS

UNTESTED GUARANTEED SATISFACTION



THE SIMPLEST! FINEST! SMALLEST!

6-FUNCTION AC-DC \$24.50 CALCULATOR KIT!

· Lightweight, pocket size

Extra large display • Simplified Indexing
6 functions plus, minus, • Mark up and Mark down
times, percentage, constant • Constant multiplication

• Floating decimal and division
• Chain and Mix calculations • AC adaptor jack

and division
and Mix calculations

AC adaptor jack

Designed specifically for Poly Paks under the Daltone
80 brand IMAGINE! only 2½ x 1 x 4½". Slides ensily
into your vest pocket, brief case, or handbag, We
hunted severywhere to find a calculator kit that can
be small, do the many functions, with fine engineering
design and SIMPLE TO BUILD! Willy? Because it has
the fewest parts in a kit, Imagine the pc board only
has the chip, 4 realstors, two triver
ic's with the 9 digit readout. SIMPLE! You bet it is.
The entire kit is even packed in a multicolor attractively designed box that in itself tells the min calculafilter; Flex key (type 20SK-66) 18 key keyboard that
measures only 2½ x 2" with 2 switches, one for ONOFF, one for K constant: MAIN pc board; readout
board; famous Cal Tech 5030 26-pin calculator chip;
two 75491 is drivers;
ac jack; 9 Volt battery connector resistors; two transiators; back protective plate; necessary wire plugs;
easy instructions. (Less 9 volt standard battery and
AC adapter) EASIEST KIT TO BUILD



BASIC KIT #1 — includes case, all-function Flex Key Keyboard, Cal Tech CT5002 calculator chip, 9-digit LED display with built-on individual magnifiers, plus sheets. 8-Digits.

\$ 516.95 BASIC KIT #2 — same as Basic #1 except calculator chip is National 8-digit MM5725. BASIC KIT #3 — same as Basic #1 except calculator chip is National 6-digit MM5736 and 75492. 316.95

12 DIGIT BASIC #4 — Key parts include: CT6001 chip, 4-3 digit rendouts, factory etched PC board, case, carrying case, 2-resistor networks, decimal switch. Wild Rover Keyboard with ON-OFF switch diagrams. Sale \$13.95 []

8-DIGIT "TEXAS INSTRUMENT" BASIC KIT 27—includes Texaskeyboard, 1KS149, standard 4-function. With T-I calculator chip TMS-0128, p.c. board, case, lens. Microswitch (on-off). 9-digit array: includes diagram. \$16.95.

6 & 8 DIGIT MINI CALCULATOR BASICS

4 5 6 2 "The key parts kits" So small fits in 'ur paim! Easiest basics around! Requires approx. 6 more parts 0 - 2 +3

KIT NO. 5030 — 6 functions. Includes mini case, with lens, HP nine digit readouts with multiplex pe board, main pe board, mini keyboard (with two switches, percent and constant), ac adapter jack, 2-SNT6491 drivers, CT8030 calculator chip with diagram. 8-Digits,
KIT NO. 5031 — 4 function, same as 5030 except uses CT8031 chip. 8-Digits,
KIT NO. 5736 — 4 function, like 5031. Uses National MM5736 6-Digits.



94.98 GIANT VENTILATING FAN

28530535

1 1 CC C

Heavy-iluy powerful hitorque motor, ruggedly constructed, Permanently lubricated type bearings,
Thermalloy protected, Motor
size: 3 x 3 x 2.5/2, Rigged
60 hz. 0.70 arms, William
TORIN fan blade, 1500 rbm.
For all types of ham & industrial equipment.

"MEMORY LANE"

THITTIN | 1101 | 256 Bit RAM MOS | 1.50 | 1103 | 1024 Bit RAM MOS | 1.50 | 1024 Bit RAM TL | 2.99 | 1024 Bit RAM TL | 2.99 | 1024 Bit RAM TL | 2.99 | 1024 Bit RAM | 2.99 | 1024 Bit RAM | 2.99 | 1024 Bit RAM | 6.50 | 1024 Bit RAM | 10 Buy Any 3

NATIONAL LM-340T VR's * TO-220 Case * 1 Amp * POSITIVE VOLTAGE

Buy 3 - Take 10 70 Type Volts
LM:340:087 5 v
LM:340:087 6 v
LM:340:087 8 v
LM:340:12712 v
LM:340:12715 v
LM:340:18718 v
LM:340:24724 v

Low Prices CT 5001
On National CT 5005
Calculator
CHIPS CT 5031 CT 5030 CT 5031 00000

WITH DATA SHEETS

CLOCK CHIPS

MM5311 6-digit 28-Pin MM5312 4-digit 24-Pin MM5313 6-digit 28-Pin MM5314 6-digit 24-Pin MM5316 4-digit 40-Pin, alarm

'BEEPER" AND "DATER' CLOCK ON THE CHIPS

Imagine a chip (MK50250)
Imagine a chip (MK502

Sanken Watts
Si-1010G 10
S 8.88
Si-1020G 20
Si-1030G 30
Si-1030G 50
Si-1030G 50
Si-1030G 50
Si-1080G 5



Type Sale CD4011AE .51
CD4000AE .53 CD4012AE .53
CD4001AE .53 CD4012AE .53
CD4001AE .53 CD4012AE .53
CD4001AE .53 CD4014AE 3.50
CD4006AE .53 CD4014AE 3.50
CD4006AE .3.50 CD4019AE 1.10
CD4007AE .61 C04020AE 2.10
CD4009AE .75 CD4022AE .53
CD4010AE .55 CD4022AE .53
CD4010AE .55 CD4023AE .53 CD4009AE CD4010AE

\$4.95 6-VOLT NICAD POWER PAK Includes 4 "A" cell nicad hatteries hooked up to give Your Choice of VOLTS! TU

Includes 4 "A" cell nicad batteries hooked up to give you 6-volts for all types of energy uses. The best bat-teries made. Rechargeable. AC ADAPTERS & CHARGERS

6 VDC @ 100 ma. \$2.95

110 vac | 7.5 v @ 200 ma. 1.50

110 vac | 12 VDC @ 275 mils. 3.50

9 VDC @ 100 ma. \$3.50 9 VDC @ 100 ma. *Not illustrated

Forms: add posture Rated: net 30 Phone Orders: Wakefield, Mass. (617) 245-38 Retait: 16-18 bel Carmine St., Wakefield, Mass (off Water Street) C.O.D.'S MAY BE PHONED

☐ 20c CATALOG on Fiber Optics, 'ICs', Semi's, Parts
MINIMUM ORDER — \$4,00

POLY PAKS

FULLY DECODED STATIC RANDOM ACCESS MEMORY DIRECTLY TTL COMPATIBLE INPUTS AND OUTPUT SINGLE SV SUPPLY - - NO CLOCKS OR REFRESH

\$695 EA. (DIP) & FOA \$4999

Numeric Display 1/4" Single Digit GaAsP LED

COMMON CATHODE WITH RH DECIMAL

Compact—10 digits in 3" panel width ACTUAL SIZE Highly legible- bright red 1/4" character easily read within 10 feet over a wide viewing angle 125 mW per digit at typical brightness SUPER SPECIAL \$.75 \$5.95 TEN for

SPECIAL 8553 PROM

8 BIT 32 WORD MEMORY #3.00 EA 10 - \$29 WE PROGRAM

7413 .75 7417 .40 7420 .20 74L20 .30 FOR \$5 EACH .30 74H20 74H22 .30

TTL DIP

.20

.25

.20

.25

.25

.25

.25

.30

.30

.40

.30

.20

.20

.20

.30

.30

.20

.30

1.00

1.50

.20

.30

.20

.25

.20

.20

.25

.25

.16

.25

.40

.60 .35

.75

.45

.75

.80

.55

.70

.50

.70

3.00

1.00

1.00

.65

.65

.50

.80

7400

7401

74H01

7402

7403

7404

74H04

7405

7406

7408

7400

7410

7430

74H30

74L30

74H40

7442

7447

7450

7451

74H51

7453

7454

74L54

74L55

7460

7472

74L71

74L72

7473

74L73

7474

74H74

7475

7476

7480

7483

7489

7490

7492

7493

7495

74107

74195

74L95 1.00

74145 1.25

74180 1.00

74193 1.50

74L78


74H50

7440

74H00

CD-2 COUNTER KIT

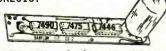Unit includes board, 7490, 7475, quad latch, 7447 seven-segment driver, and RCA DR2010.



COMPLETE KIT only \$11.95; FULLY-ASSEM-BLED \$15.00; boards can be supplied separately at \$2.50 per digit.

RCA 2010

Numitron Digital Display Tube, incandescent 5-volt 7-segment:

.6" High numeral visible from 30 ft Standard 9-pin base (solderable) Left-hand decimal point 5 FOR \$20.00 EACH \$5.00

CM	ΠS	004016		TRANSISTOR
		CD4016	1.00	SPECIAL
CD4000	\$.55	CD4019	1.00	PLECTAL
CD4001	. 45	CD4023	.45	2N3568-HEP736
CD4002	.45	CD4024	1.60	TO92 PLASTIC
CD4007	1.00	CD4025	.45	NPN 300MW
CD4008	3.25	CD4027	1.00	POA 40-7508
CD4009	.75	CD4030	1.00	EACH \$.15
CD4010	. 75	74C20	.65	TEN 1.00
				100 9.00
CD4011	.45	74C42	2.00	1000 80.00
CD4012	.45	74C157	2.50	2000 00.00
CD4013	1.00	74C161	3.00	NEW-TELEDYNE
CD4015	3.00	74C195	2.00	MARKED T3568



POTTER BRUMFIELD

Type KHP Relay 4 PDT 3A Contacts

24 VDC (650 coil) \$1.50 EA.

120 VAC (10.5 MA coil) \$1.75 EA.

FREE FLYER!

C.O.D. PHONE ORDERS ACCEPTED--\$10 MINIMUM

All IC's new and fully tested, leads plated with gold or solder. Orders for \$5.00 or more are shipped prepaid, smaller orders--add 55c. California residents add Sales Tax.....IC's shipped within 24 hours. P.O. BOX 41727


SACRAMENTO, CA 95841 . .

916 334 2161

LIQUID CRYSTAL CALCULATOR \$10.00

Rejects and require repairs but most easily repaired. Desk top models. We furnish 32 page instruction and trouble shooting. 8 digit 4 function. Two models available.

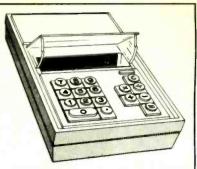AC model #SP102A \$10 each; 3 for \$26.50 Btry, model #SP102B \$11 each; 3 for \$30.00



PANAPLEX 12 DIGIT DISPLAY

12 digit neon (180 volts) display. Genuine Burroughs Panaplex II cold cathode gas discharge 7 segments. Unused and we include the special socket. Measures 3% x % (pic shown is full size). Data sheet included. Good for clocks, timers, counters, any type of digital readout use. Readability at 15 feet. #PANAPLEX \$6.00

HI-VOLTAGE (NEON) DRIVER PACKAGE

Package of 3 IC units for interfacing of high voltage neon type displays with low voltage calculator chips. This set of three IC's consists of Cathode Driver IC, Anode Driver IC, and Level Shifter IC. We include data for use. Good with Planaplex displays, Sperry displays, Anaplex displays, etc. From what we can see, no one seems to have them and this is the first time offered at surplus prices. They are first

ave them and this is the first time offered at surplus prices. The devices, surplus due to a manufacturer of keyboard displays going out #DION \$6.00 of business.

MOS ASCII ENCODER CHIP

With all the interest in keyboard encoders, TV readouts, etc. this single chip ASCII encoder should be welcome news. And the price ... unbelievable at \$9.95. 40 pin DIP, made by MOS Technology. Data sheets enclosed with each order.

#SP-105 \$9.95; 3 for \$25

SURPLUS ELECTRONIC MATERIAL

P.O. BOX 62, E. LYNN, MASS, 01904

Circle 93 on reader service card

BURROUGHS DIGITAL COUNTERS

Also available without Nixie tubes; write for information.

BURROUGHS Series C2506 decade counters with memory. Available with 4,5,6 or 7 digits. NIXIE tube readouts. Complete 25 Mhz counter, all you need is a power supply, 200 Vdc

and 5.0 Vdc (Vcc). This a basic unit for digital instruments such as frequency counters, clocks, thermometers, DVMs etc. With 6 pages of data.

STOCK NO.F5134 4 digits (C2506-4) 29 50 STOCK NO.F5135 5 digits (C2506-5) 36.00 6 digits (C2506-6) 42.50 STOCK NO.F5136 49.50 STOCK NO.F5137 7 digits (C2506-7)

THREE 0.1% 15 VOLT REGULATORS ON ONE BOARD



2 regulators rated @ 3.0 amps. Other rated @ 6.0 amps. 2 regulators have electronic crowbar overvoltage protection, and all 3 are short circuit proof. Output current can be doubled in all 3 regulators, and regulation becomes 0.5%. Pass transistors are 5 2N5878 NPN TO-3 power. 4 used, and 1 spare. 6"x6" 3 lbs.

STOCK NO.R5169 \$11.95 ea. 2/21.00

Ideal transformer for REGULATOR BOARO or TRANSISTOR ASSEMBLY above, 28 volts, @ 5.0 amp. shielded. STOCK NO.R9860 24"x34"x3" 6 lbs. \$6.50, 2/12.00

HIGH POWER TRANSFORMER 35 Volts @ 6.0 Amps. ct. and 10 volts @ 10 amps. STOCK NO.R9906 \$8.95 ea.

Include sufficient postage. Excess refunded. Send for new Catalog 13, just out, with many electronic bargains.



BOX 1, LYNN, MASSACHUSETTS 01903 Phone (617) 388-4705

INTERNATIONAL ELECTRONICS UNLIMITED

10% OFF

ON ORDERS OVER \$25.00

	1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1	
TTL	S 4444000	T .
	111111111	Ea.
Ea.	Ea.	74141 \$1.23
7400 \$.19	7447 \$1.15	74145 1.15
7401 .19	7448 1.15	74150 1.09
7402 .19	7450 .24	74151 .89
7403 .19	7451 .27	74153 1.29 74154 1.59
7404 .22	7453 .27	74155 1.19
7405 .22	7454 .39	74156 1.29
7406 .39 7407 .39	7460 .19 7464 .39	74157 1.29
7407 .39 7408 .25	7465 .39	74161 1.39
7409 .25	7472 .36	74163 1.59
7410 .19	7473 .43	74164 1.89
7411 .29	7474 .43	74165 1.89
7413 .79	7475 .75	74166 1.65
7415 .39	7476 .47	74173 1.65
7416 .39	7483 1.11	74175 1.89
7417 .39	7485 1.39 7486 .44	74176 1.65 74177 .99
7420 .19 7422 .29	7489 275	74177 .99 74180 1.09
7423 .35	7490 .76	74181 3.65
7425 .39	/491 1.49	74182 .89
7426 .29	7492 .79	74184 2.69
7427 .35	7493 .79	74185 2.19
7430 .22	7494 .89	74190 1.59
7432 .29	7495 .89	74191 1.59
7437 .45 7438 .39	7496 .89 74100 1.65	74192 1.49 74193 1.39
7440 .19	74105 .49	74194 1.39
7441 1.09	74107 .49	74195 .99
7442 .99	74121 .57	74196 1.85
7443 .99	74122 .53	74197 .99
7444 1.10		74198 2.19
7445 1.10	74125 .69	74199 2.19
7446 1.15	74126 .79	74200 7.95
LOW POW		
74L00 .33	74L51 .33	74L90 1.69
74L02 .33 74L03 .33	74L55 .33 74L71 .33	74L91 1.45 74L93 1.69
74L03 .33	74L72 .49	74L95 1.69
74106 .33	74173 .69	74L98 2.79
74L10 .33	74L74 .69	74L164 2.79
74L20 .33	74L78 .79	74L165 2.79
74L30 .33	74L85 1.25	
74L42 1.69	74L86 .69	Į.
HIGH SPEEL		
74H00 .33	74H21 .33 74H22 .33	74H55 .39 74H60 .39
74H01 .33 74H04 .33	74H22 .33 74H30 .33	74H60 .39 74H61 .39
74H08 .33	74H40 .33	74H62 .39
74H10 .33	74H50 .33	74H72 .49
74H11 .33	74H52 .33	74H74 .59
74H20 .33	74H53 .39	74H76 .59
8000 SERIES	TTL	
8091 .59	8214 1.69	8811 .69
8092 .59	8220 1.69	8812 1.10
8095 1.39	8230 2.59	8822 2.59
8121 .89	8520 1.29	8830 2.59
8123 1.59 8130 2.19	8551 1.65 8552 2.49	8831 2.59 8836 .49
8200 2.59	8554 2.49	8880 1.33
8210 3.49	8810 .79	1.33
9000 SERIES		
9002 .39	9309 .89	9601 .99
9301 1.14	9312 .89	9602 .89

CMOS

74C00	.39	74C74 1.15	74C162 3.25
74C02	.55	74C76 1.70	74C163 3.25
74C04	.75	74C107 1.50	74C164 3.50
74C08	.75	74C151 2.90	74C173 2.90
74C10	.65	74C154 3.50	74C195 3.00
74C20	.65	74C157 2.19	80C95 1.50
74C42	2.15	74C160 3.25	80C97 1.50
74C73	1.55	74C161 3.25	

Data sheets supplied on request Add \$.50 ea. for items less than \$1.00

MAY SPECIALS

	8008	CPU	\$59.50	MAN 1	\$1.50
	2102-	1024 bit	6.95	MAN 5	1.95
	1702A	2048 bit	21.95	MAN 6	3.95
١.	5203	UV eras.	17.95	MAN 8	1.95
	5261	1024 bit	2.95	MAN 66	2.95
	5262	2048 bit	7.95	HP 5082	
	5316	alarm clock	4.95	7414 (4 DIG)	2.75
	7001	alarm clock	7.95	HP 5082	
	8038	V cont. osc.	5.95	7405 (5 DIG)	2.95
ı	7441		.69	5020 RED LED	5/\$1.00
ı	7445		.79	MCT 2	.59
ı	7475		.49		
ı	7490		.59	COSMETIC R	EJECTS
ı	74123		.59	FUNCTIONALLY P	ERFECT
ı	340T 5v	(7805)	1.35	5001	\$1.95
ı	340T 15V		1.35	5002	2.50

POCKET CALCULATOR KIT

5 function plus constant addressable memory with individual recall — 8 digit display plus overflow battery saver — uses standard or rechargeable batteries — all necessary parts in ready to assemble form — instructions included. 3" x 51/4".....

18 PIN CALCULATOR KIT

- MM 5736 18 PIN Calc. Chip four function 6 Digit
- A pair of 3-In-1 PAKS (6 digit) LED NSN 33
- One 75492 HEX Digit driver Schematic and Instructions included. You supply switches, keyboard and battery for complete calculator

MEMORIES w/data

1101	256 bit RAM MOS	\$1.75
1103	1024 bit RAM MOS	3.95
5203	2048 bit eras, PROM	24.95
5260	1024 bit RAM low power	3.95
7489	64 bit RAM TTL	2.75
8223	Programmable ROM	3.95

CALCULATOR & CLOCK CHIPS w/data

5001	12 DIG 4 funct fix dec	2.95
5002	Same as 5001 exc btry pwr	3.95
5005	12 DIG 4 funct w/mem	5.95
MM5725	8 DIG 4 funct chain & dec	2.79
MM5736	18 pin 6 DIG 4 funct	4.95
MM5738	8 DIG 5 funct K & Mem	7.95
MM5739	9 DIG 4 funct (btry sur)	6.95
MM 5311	28 pin BCD 6 dig mux	4.95
MM 5312	24 pin 1 pps BCD 4 dig mux	6.95
MM 5313	28 pin 1 pps BCD 6 dig mux	4.95
MM 5314	24 pin 6 dig mux	4.95
MM 5316	40 pm alarm 4 dig	8.95

LED & OPTO ISOLATORS

MV10B	Red TD 18	S .25 ea.
MV50	Axial leads	.20
MV5020	Jumbo Vis. Red (Red Dome)	.25
	Jumbo Vis. Red (Clear Dome)	.25
ME4	Infra red diff. dome	.60
MAN1	Red 7 seg270"	2.50
MAN2	Red alpha num .32"	4.95
MAN4	Red 7 seg190"	2.15
MAN5	Green 7 seg270"	2.95
MAN6	.6" high solid seg	4.95
MAN7	Red 7 seg270"	1.35
MAN8	Yellow 7 seg270"	3.95
MAN64	.4" high solid seg	3.50
MAN66	.6" high spaced seg	4.65
DL707	Red 7 seq3"	2.15
MCD2	Opto-iso diodes	1.09
MCT2	Opto-iso transistor	.69

DTI

930 \$.17	937 \$.17	949 \$.17
932 .17	944 .17	962 .17
936 17	946 .17	963 .17

4000 SERIES -RCA EQUIVALENT

CD4001	55	CD4013	1.20	CD4023	.55	
CD4009	.85	CD4016	1.25	CD4025	.55	
CD4010	85	CD4017	2.95	CD4027	1.35	
CD4011	55	CD4019	1.35	CD4030	.95	
CD4012	.55	CD4022	2.75	CD4035	2.85	

LINEAR CIRCUITS





\$24.95

300	Pos V Reg (super 723)	TO-5	\$.7
301	Hi Perf Op Amp	mDIP TO-5	.3
302	Volt follower	TO-5	.5
304	Neg V Reg	TO-5	.8
305	Pos V Reg	TO-5	.7
307	Op AMP (super 741)	mDIP TO-5	.2
308	Micro Pwr Op Amp	mDIP TO-5	.9
309K	5V 1A regulator	TO-3	1.5
310	V Follower Op Amp	TO-5 mDIP	1.1
311	Hi perf V Comp	mDIP TO-5	1.0
319	Hi Speed Dual Comp	DIP	1.2
320	Neg Reg 5.2, 12, 15	TO-3	1.2
322	Precision Timer	DIP	1.1
324	Quad Op Amp	DIP	1.8
339	Quad Comparator	DIP	1.6
340T	Pos Volt Reg		
	(5V-6V-8V-12V-15V-18V-24	IVITO-220	1.7
370	AGC/Squetch AMPL	TO-5 or DIP	1.1
372	AF-IF Strip detector	DIP	.7
373	AM/FM/SSB Strlp	DIP	3.2
376	Pos. V Reg	mDIP	.5
377	2w Stereo amp	DIP	2.6
380	2w Audio Amp	DIP	1.2
380-8	.6w Audio amp	mDIP	1.2
381	Lo Noise Dual preamp	DIP	1.6
382	Lo Noise Dual preamp	DIP	1.6
550	Prec V Reg	DIP	.7
555	Timer	mDIP	.9
560	Phase Locked Loop	DIP	2.7
562	Phase Locked Loop	DIP	2.7
565	Phase Locked Loop	DIP TD-5	2.6
566	Function Gen	mDIP TD-5	2.5
567	Tone Decoder	mDIP	2.9
709	Operational AMPL	TD-5 or DIP	.2
710	Hi Speed Volt Comp	DIP	.39
711	Dual Difference Compar	DIP	.29
723	V Reg	DIP	.69
739	Dual Hi Pert Dp Amp	DIP	1.15
741	Comp Dp AMP	mDIP TD-5	.39
747	Dual 741 Dp Amp	DIP or TD-5	.79
748	Freq Adj 741	mDIP	.3
1304	FM Mulpx Stereo Demod	DIP	1.1
1307	FM Mulpx Stereo Demod	DIP	.8:
1458	Dual Comp Dp Amp	mDIP	.6
1800	Stereo multiplexer	DIP	2.7
LH2111	Dual LM 211 V Comp	DIP	1.89
3065	TV-FM Sound System	DIP	.69
3075	FM Det-LMTR &		
	Audio preamp	DIP	.79
3900	Quad Amplifier	DIP	.39
7524	Core Mem Sense AMPL	DIP	.79
7534	Core Mem Sense Amp	DIP	.79
3864	9 DIG Led Cath Dryr	DIP	2.5
75451	Dual Perepheral Driver	mDIP	.39
5452	Dual Peripheral Driver	mDIP	.39
5453	(351) Dual Perlph. Driver	mDIP	.39
5491	Quad Seg Driver for LED	DIP	. 7
5492	Hex Digit Driver	DIP	.8
	-		

SHIFT REGISTERS

MM 5013	1024 bit accum, dynamic	mDIP	\$1.95
MM 5016	500/512 bit dynamic	mDIP	1.75
MM 5058	1024 bit static	DIP	3.95
SL-5-4025	Dual 64 bit static	DIP	1.50



Shipment will be made via first class mail - postage paid in U.S., Canada and Mexico - within three days from receipt of order. Minimum order -\$5.00. California residents add sales tax.

INTERNATIONAL ELECTRONICS UNLIMITED P.O. BOX 1708 MONTEREY, CA. 93940 USA PHONE (408) 659-3171



PC board, resistor, capacitors and all semiconductors are furnished. Plus for a limited time only we will furnish the power supply transformer FREE.

All you need to add to complete the kit are the cabinet, switches, jacks and potentiometers. All of these can be purchased for less than \$20.00 from your local electronics supply store.

All parts not furnished are specified.

Curve Tracer adapts to any scope with horizontal and vertical inputs.

To order send check or money order in the amount of \$35.00 plus \$1.50 shipping and handling to: **EFI UNIT #7**

8100 REMMET AVE. CANOGA PARK, CA 91304

1.00 .95 .95 .97 .95

1.50 .47 .55 .47

1.15 .95 1.20

1.50 1.25 1.30

1.30 1.55 1.65 1.65 2.50 2.50 2.50

3.00 1.75 1.85 1.85

1.00

1.00 2.30 2.30 7.00

1.50 1.50 1.25

1.25 1.05 2.25 2.75 7.00

5.00

CMOS

CD4002 .48 CD4006 3.75 CD4007 .55 CD4009 .89 CD4010 .69 CD4011 .48 CD4012 .48 CD4013 1.00 CD4016 1.00 CD4017 2.65 CD4019 1.15 CD4020 1.50 CD4022 1.50 CD4023 .48 CD4024 1.95 CD4025 .48

CD4024 1.95 CD4025 .48 CD4027 1.15 CD4028 2.65 CD4029 3.95 CD40403 1.00 CD4035 2.65 CD4044 2.75 CD4044 2.75 CD4044 2.75 CD4044 1.00 CD4050 1.00 CD4050 1.00 CD4050 3.00 74C00 3.00 74C160 3.00

(Zener) DIODES (Rectifier) IN456 6/ IN458 6/

1N458 6/\$1 IN485A 5/\$1 IN746 4/\$1 IN752 4/\$1

| N | 183 | 1.60 | N | 1184 | 1.70 | N | 1186 | 1.80 | N | 3600 | 6/\$1 | N | 4001 | .09 | N | 4002 | .10 | N | 4004 | .10 |

IN4148 15/\$1 IN4154 12/\$1 IN4734 .28c IN4735 .28c IN5232 .28c IN5234 .28c

4.00 CD4000\$.48 2.25ea CD4001 .48 .69ea CD4002 .48

California residents add 6% sales tax to the purchase price. Allow 2 to 3 weeks for delivery.

Circle 96 on reader service card

TTL

7400*6/\$1.00 7488 7401 .23 7489* 7402 .23 7490* 7403 6/1.00 7491* 7404 .25 7492

7405 7406 7407

7408

7442 7443 7444

7450 7451 7453

7486

.40 .50 1.75 1.15

1.10

20% Discount for 100 pcs. Combined 7400's (Except Specials)

74197 74198 74199

74200 74250

RADIO & TV tubes 36c each. One-year guarantee. Plus many unusual electronic gains. Free catalog. CORNELL, 4217-E University, San Diego, CA 92105

NEW INSTRUMENT TO USE WITH MULTITRACER



\$19.95--CHECK DR MONEY ORDER

BOX 14. LESCO ELECTRONICS. SKOKIE, ILL. 60076

LOW-noise resistors—¼ W, 5% carbon film from 10 — 3.3 megohms for 3½c each. Fifty of one value for \$1.25. 1N4148 diodes for 6c. 75c postage. Free samples/specifications. COMPONENTS CENTER—RE, Box 134, New York, NY 10038

PRINTED CIRCUIT

EPOXY GLASS CIRCUIT BOARD STOCK; CARBIDE DRILL BITS; TAPE RESIST; ARTWORK; BUBBLE ETCHERS SEND S.A.S.E. FOR FLYER TRUMBULL 833 BALRA DR., EL ŒRRITO,CA. 94530



LISTEN TO

Spectacular **4-Channel Sound!**

Latest High-Quality Quadraphonic Performance with the Vista SQ-3 Decoder

EXCLUSIVE CBS LICENSED CIRCUITY, SUPERB RESPONSE AND CHANNEL SEPARATION FULL LOGIC, WAVE MATCHING AND VARIABLE BLEND

KIT SQ-3

ALL NECESSARY PARTS EXCEPT CASE AND +20V 75mA POWER SUPPLY

Shipped prepaid in USA NY State add Tax \$2.00 additional for CANADA

PHOTOLUME CORPORATION

118 East 28th STREET, New York, N.Y. 10016

Circle 97 on reader service card

* MAY SPECIALS *

8008 Processor \$49.95 | AY5.1013 UART 1101 256 x 1 RAM 2.25 | RC4194 TK 2102 1024 RAM 7.95 | RC4195 TK \$9.95 5.95 3.25 1101 256 × 1 RAI 2102 1024 RAM 50 VOLT CERAMIC DISC CAPACITORS
1-9 10-49 50-100
.001mf. 5c 3.5c 3c .0047mf. 6c 4c 3.5c .0047mf. 6c 4c 3.5c .01mf. 5c 3.5c 3c .022mf. 6c 4c 3.5c .022mf. 6c 4c 3.5c .022mf. 6c 4c 3.5c .022mf. 6c 4c 3.5c .022mf. 6c 4c 3.5c

100 Volt Mylar Film Capacitors .09 .07 .05 .022UFD .09 .07 .05 .047UFD .09 .07 .05 .1UFD .10 .08 .06 .22UFD .10 .08 .06 .12 .09 .07 .15 .12 .10 .21 .18 .15 .0022UFD .0047UFD .01UFD

1C-Skts 8 P \$.2 14 P .2 16 P .2 18 P .2 24 P .6 28 P .8 36 P 1... 40 P 1... Cal. & Clk.Chips WALL or T.V. DIGITAL CLOCK 25' VIEWING DISTANCE Ca1. & CIR. Chips 5001 \$3.95 5005 5.95 5030 7.95 MM5311 4.95 MM5312 4.95 MM5313 4.95 MM5314 4.95 MM5316 6.95 Walnut Case-6"x3"x1" Hr. & Min.-.6" High Seconds-.3" High .68 Seconds-.3" High KIT - All Comp.& Case \$39.95 Wired & Assembled \$44.95

Satisfaction Guaranteed. \$5.00 Min. Order. U.S. Funds. California Residents — Add 6% Sales Tax Write for FREE 1975 Catalog — Data Sheets .25¢ each

PHONE ORDERS - (415) 592-8097

Circle 98 on reader service card

LINEAR

.31° .69 .35 .79 \$.69 .29* .69 .79 .89 .35 1.05 1.25* 1.19 .95 LM300H LM301H/N LM302H LM304H LM747N LM748N LM1303N LM1307N LM1307N LM1310P LM1458N LM1469N LM1556V LM305H/N LM307H/N LM308H/N LM309K 3.25* .69 LM310H/N LM311H/N LM318N LM319 1.85 1.70 2.15 2.25 1.35 1.15 2.46 LM1556V CA3013 CA3023 CA3035 CA30359 CA3060 CA30650 CA30650 CA3060 CA3083 CA3086 CA3089 CA3089 CA3089 CA3089 CA3089 CA3089 CA3089 CA3080 CA308 LM320K* 1.50 LM324 1.85 LM339N 1.95 LM340K 1.89 LM340T 1.75 LM370N 1.05 LM373N 2.05 LM380-8 1.00 LM380-8 1.00 NE5536T 3.00 NE555N 79 NE555N 79 NE555N 1.85 NE561 2.50 NE561 2.50 NE562 2.50 LM320K* 1.50 3.25 8.25 1.85 1.75 .55 .55* 1.75 3.95* .55 .75 .49 .39 .39 .39 .79 NE556N NE560 NE562 NE565H/N NE566 NE5667H/N LM703H/N LM710H/N 2.50 2.00* 2.00* .50 .00* 8038B LM711H/N LM723H/N LM733H/N

1/4 W 5% CARBON COMP RESISTORS 5-25 30-95 100-495 500-995 1000 UP .0275 .04 .03

All Std. Values - 5 Ea. Min. Add 5∉ per value if sorting is required

8000 Series PROJECTS LEDS MV 10 5/1 8090-98 .55 MV 50 6/1 8123 1.50 MV 50245/1 8223 * 3.00 MAN-1 1.95 8263 7.00 MAN-3 .95 8267 4.00 MAN-4 1.95 8280 .75 MAN-7 1.50 8281 .85 DL 33 1.95 8288 1.15 DL 747 2.50 8880 1.35 8263 \$ 7.00 8267 4.00 2513* 11.00 2518 7.00 2519 4.00 4.00 3.95 7.00

BUILD YOUR OWN MINICOMPUTER

Thousands of Radio-Electronics readers have already built their own minicomputer. You can still build yours. To get started, order our 52-page book — COMPUTER! It contains complete construction information including full-size circuit board patterns, data on how it works, a group of eight experiments you can perform with the computer and other important information.

Use the coupon below to order. Print! The Coupon will be used as the shipping label. Then check off the way you want it shipped; this determines the price. Payment must be in U.S. currency.

Radio-Electronics Computer Book 45 E. 17 St., New York, NY 10003 MUST PRINT Address Zip Book price includes postage. U.S., Canada, First-class Mail \$5.50* U.S., Canada, Air Mail \$5.65 Foreign, Surface \$5.90 \$7.30 Foreign, Air Mail Only these four methods of shipment can be provided. *New York State residents must include 7% sales tax—39c additional. New York City residents must include 8% sales tax—44c

COMPUTER! will be mailed within three weeks

of receipt of your order.

BUILD YOUR OWN TV TYPEWRITER

As you type, the letters appear on the screen of your TV set. Use it as a computer terminal. You can still build yours. To get started, order our 16-page brochure—TV TYPEWRITER. It contains complete construction information, fullsize circuit board patterns, data on how it works, troubleshooting tables, connections and other important information. The cost is \$3.00, postpaid, plus tax where applicable.

Use the coupon below to order your personal copy. Print! The coupon will be used as the shipping label. Payment must be in U.S. currency.

	ctronics TV Ty St., New York, NY	
	MUST PRINT	
Name		
Address		
City	State	Zip
Brochure price tax where appl	is \$3.00, postpa icable.	id, plus sales
First Class	Mail (U.S. & Fore	eign) \$3.00
NY State F	lesidents	\$3.21*
NY City Re	sidents	\$3.24*
	s 7% state sales is s 8% city sales ta	
Only first class \$1.25 additional	mall available. Fo	oreign air mai
	will be mailed of of your order.	within three

MEMORY SYSTEM \$125.00

1024 core memory system, 1024 words memory 8, 9, or 1C bits word. Random access, with all logic, register timing control, core select with 60 page book.et includes schematics. Measures only \$x4x1 inches. Good start for mini-computer

TONE GEN. BOARD

3 Octave tone gan board from Magnus Organ Unused, as is, with instructions & amp. \$9.55 two for \$18.00.

PIANO KEYBOARD \$9.95

For use with above organ or synthesizer, etc.

MULTI-USE XFMR \$8.95

Output 18 V @ 6 amp. 17 V @ 6 amps. 10 V 10 amp Brard new \$8.95 ea. 2 for \$15 10 for \$50

PHOTO-STROBE

Made for Instamatic but useful on any Camera with instructions provided. Info also on trick uses automotive strope, slave strope, auto-mctive strope. Esychadelic repetitive strope. etc. Complete with charger & Nickel Cadmium

\$9.00 or 3 for \$24.00

Please add shipping cost on above FREE

Meshna SURPLUS ELECTRONIC MATERIAL

P.O. BOX 62 E. LYNN MASS. 01904

Circle 99 on reader service card

.25 3.00 3.20 10.50 4.80 .70 .30 .25 7.00 1.10

.80 3.50 4.80 .90 5.50 2.70 3.20 1.60

2N3789 2N3793 2N3796 2N3799 2N3805 2N3807 2N3819 2N3823 2N3843 2N3856 2N3866

2N3866 2N3903 2N3904

2N3904 2N3905 2N3906 2N3909 2N3924 2N3925 2N3945

2N3954 2N3954A 2N3956

2N3955A 2N3957

1.00		
	2N1204 2N1234	1.50
.60	2N1302	15.00
		.35
		1.50
		.50
1.00		.60
1.25		50
9.00		1.20
2.70		1.60
1.00		5.00
.20		1.00
.50	2N 1540	1.10
1.20	2N1543	3.50
9.00	2N 1544	.90
1.00	2N1549	1.35
1.15	2N1551	4.00
1.30		4.00
		2.00
		1.70
		3.30
2.90		1.50
		1.60
1.00		2.20
1.50		2.00
		2.30
		.45
		2.00
2.50	201093	15.00
2.70		.50
4.00		.70 5.00
7.00		69.00
		5.00
4.00		3.00
60		1.30
20		9,40
		.80
.40	2N2060	2.10
.60	2N2065A	1.80
.30	2N2080	5.00
.50	2N2081A	2.50
1.50		3.00
.35		.50
1.00		.70
		.66
.50	2N2193	.45
.70		.90
3.00		.26
.35	2N2218A	.30
2.50		.30
		.25
40		.26
		.30
50		1.10
50		.40
2.00		3.70
1.00		6.00
		1.00
18.00	2N2322	1.80
1.50		1.90
2.00	2N2324	2.40
	2N2325	2.60
1.50		
1.50 2.00	2N2325	
	2N2326 2N2326 2N2327 2N2328	3.40 4.60
	.50 1.40 1.40 1.25 9.00 2.70 1.00 1.20 9.00 1.10 1.50 1.40 1.50 1.50 1.00 1.50 1.00 1.50 1.00 1.50 1.5	.50 2N1307 1.40 2N1307 1.40 2N1408 1.00 2N1408 1.25 2N1420 9.00 2N1483 2.70 2N1485 1.00 2N153 .50 2N1530 .50 2N1540 1.20 2N1544 1.00 2N1544 1.00 2N1544 1.00 2N1544 1.00 2N1555 1.40 2N1556 1.40 2N1556 1.40 2N1556 1.40 2N1556 1.40 2N1556 1.40 2N1556 2.90 2N1596 1.00 2N1596 1.00 2N1597 1.50 2N1598 3.50 2N1598 3.50 2N1599 3.50 2N1596 1.00 2N1605 5.50 2N1596 1.00 2N1607 1.50 2N1598 3.50 2N1599 3.50 2N1599 3.50 2N1599 3.50 2N1599 3.50 2N1599 3.50 2N1691 3.40 2N1720 2N1605 5.50 2N1671 2.50 2N1691 3.40 2N1721 3.40 2N1721 3.40 2N1721 3.40 2N1721 3.40 2N1720 3.00 2N1691 3.00 2N1693 3.00 2N1691 3.00 2N1693 3.0

2N2329	7.00	2N2905A	.34	2N3502	1.40
2N2356	6.00	2N2906	.18	2N3503	1.60
2N2356A	7.00	2N2906A	.20	2N3506	7.50
2N2359	16.00	2N2907	.20	2N3544	4.00
2N2368	.30	2N2907A	.30	2N3548	2.80
2N2369	.20	2N2913	.90	2N3549	3.00
2N2382	4.50	2N2914	1.40	2N3553	1.80
2N2440	3.50	2N2916A	4.05	2N3563	.15
2N2453	3.00	2N2925	.20	2N3564	.14
2N2465	7.50	2N2926	.15	2N3565	.18
2N2475	.60	2N2947	14.50	2N3567	.19
2N2476	.80	2N2949	6.00	2N3568	.30
2N2484	.25	2N2950	6.50	2N3569	.17
2N2511	1.50	2N2969	31.00	2N3584	1.80
				•	

PREMIUM QUALITY TRANSISTORS

We've been buying and selling top quality components, including transistors, for nearly ten years. Our annual volume exceeds \$3 million. We handle only original parts, from the world's leading manufacturers and our customers include some of the largest and most quality-conscious companies.

We invite you to take advantage of our component buying skills. Select the transistors you need from the Ancrona line. For your other component needs, see our full page advertisement in this edition.

2N2518	6.00	2N3019	1.50	2N3599	38.00
2N2526	4.50	2N3022	18.00	2N3614	1.10
2N2527	5.50	2N3053	.35	2N3616	1.25
2N2537	1,30	2N3054	.80	2N3617	2.50
2N2538	2.50	2N3055	.95	2N3634	8.00
2N2600	7.10	2N3060	3.00	2N3638	.18
2N2604	1.80	2N3066A	1.20	2N3642	.19
2N2605	.50	2N3070	1.30	2N3643	.14
2N2646	.70	2N3107	.80	2N3645	.15
2N2648	4.00	2N3109	.75	2N3646	.10
2N2658	7.00	2N3117	1.00	2N3656	8.60
2N2708	.25	2N3130	5.00	2N3657	9.00
2N2712	.30	2N3133	.80	2N3680	6.00
2N2713	.15	2N3202	16.00	2N3684	1.25
2N2715	.18	2N3209	.90	2N3685A	1.50
2N2716	.18	2N3227	2.40	2N3692	.20
2N2754	95.00	2N3239	3.00	2N3693	.21
2N2802	9.80	2N3247	3.90	2N3694	.22
2N2808	9.00	2N3250	.50	2N3702	.18
2N2833	4.00	2N3371	4.00	2N3705	.25
2N2880	11.00	2N3375	5.50	2N3707	.17
2N2890	4.60	2N3390	.50	2N3710	.20
2N2892	6.70	2N3393	.20	2N3711	.18
2N2893	9.80	2N3398	.25	2N3725	.36
2N2894	.50	2N3442	2.20	2N3730	1.50
2N2895	1.00	2N3445	5.00	2N3731	2.00
2N2903	4.00	2N3467	1.50	2N3740	1.20
2N2904	.30	2N3468	1,90	2N3763	5.00
2N2904A	.36	2N3500	4.00	2N3771	2.20
2N 29 05	.32	2N3501	6.50	2N3772	2.30

MINIMUM ORDER: \$10.00
Add \$1.00 to cover postage and handling
SEND CHECK OR MONEY ORDER (NO C.O.D.) TO:



California residents add 6% sales tax. P.O. BOX 2208R, Culver City, CA 90230

1	2N3958	1.40	2N5198
	2N3964	1.10	2N5202
38.00	2N3971	1.00	2N5294
1.10	2N3972	1.40	2N5306
1.25	2N4012	10.50	2N5354
2.50	2N4037	.70	2N5369
8.00	2N4045	1.95	2N5397
.18	2N4093	1.05	2N5407
.19	2N4120	3.90	2N5409
.14	2N4124	.20	2N5414
.15	2N4126	.26	2N5449
.10	2N4141	.26	2N5453
8.60	2N4142	. 17	2N5457
9.00	2N4143	.16	2N5458
6.00	2N4208	2.05	2N5467
1.25	2N4220A	1.00	2N5562
1.50	2N4225	3.80	2N5563
.20	2N4226	3.95	2N5636
.21	2N4227	.35	2N5637
.22	2N4228	.50	2N5655
.18	2N4234	1.50	2N5657
.25	2N4235	1.90	2N5679
.17	2N4248	.17	2N5742
.20	2N4249	.18	2N5778
.18	2N4250	.22	2N5923
.36	2N425B	.34	2N6027
1.50	2N4291	.35	2N602B
2.00	2N4293	.50	2N6076
1.20	2N4303	.30	2N6099
5.00	2N4341	1.35	2N6101
2.20	2N4347	1.60	2N6103
2.30	2N4348	2.00	2N6155
17	2N4352	2.00	FRE
	2N4356	.30	
(Final)	2N4395	1.30	"Store Opening
PHOST	2N4399	6.40	IC AUDIO AME
TTI	2N4400	.30	LM354A 12.
7	2N4401	.32	Bring this coupo
	2N 4402	.34	new electronic p
	2N4403	.40	let for your Fre
	2N4416	.90	Amplifier, Limit
	2N4429	6.00	coupon. (Not red
	2N4430	8.60	by mail) Offer go 7/1/75. Ancro
	2N4441	.95	11080 Jefferson
			yard, Culver City

LIFIER

1.10 1.40 .80 1.10 1.20 5.50 .60 3.90 .90 1.10 2.00 1.00

.85 1.20 1.40 41.00 .55 12.80 .65 .20 .95 .85

2N4442 2N4453 2N4858 2N4859 2N4863 2N4870 2N4878 2N4890 2N4898 2N4905 2N4922

2N5016 2N5036 2N5061 2N5064 2N5086

BOW)

105

Quality Electronic Components SPECIAL SAVINGS DISCOUNT ON LINEAR AND DIGITAL INTEGRATED CIRCUITS but 4% from the total of your S.C. order if it exceeds \$25.00 based on single lat prices, 7% \$50.00 or more, 10% for \$100.00 or more. Additional large quantity discounts offered. TTL & CMOS INTEGRATED CIRCUITS 25: 7445N, 81: 7495N, 90: 74158N 3117 407745. 676 25: 7445N, 81: 7495N, 81: 7495N, 91: 7495N, 3273 403645. 51: 07 25: 7445N, 81: 7495N, 81: 7495N, 91: 7495N, 3273 403645. 51: 07 25: 7447N, 81: 74107N, 31: 74107N, 32: 74197N, 32: 7419N, 32: TTL & CMOS INTEGRATED CIRCUITS 7418N 7420N 7421N 7423N 7426N 7430N LINEAR INTEGRATED CIRCUITS MINIATURE ALUMINUM ELECTROLYTIC CAPACITORS 1 AMP SILICON RECTIFIERS 1N4001 50 PIV 12/51 100/56 1000/548 1N4005 600 PIV 8/51 100/59 1000/570 1N4007 1000 PIV 6/51 100/511 1000/588 SILICON SIGNAL & SWITCHING DIODE MOLEX SOLDERCON IC TERMINALS 500/\$4.20 1000/\$8.20 5000/\$38.20 50.00 LED 7 SEGMENT DISPLAYS DATALIT-704 . . \$1.00 DATALIT-707 . . \$1.50 MACHINE SCREWS, NUTS & LOCKWASHERS REED RELAYS 2-56 ¼ Screw - 90c/c 2-56 ½ Screw - 90c/c 4-40 ¼ Screw - 90c/c 4-40 ½ Screw - 90c/c 6-32 ½ Screw - 90c/c 6-32 ½ Screw - 80c/c 8-32 ¾ Screw - 80c/c 8-32 ¾ Screw - 80c/c 2-26 Hes Nut. \$1.45/c 2 Lock Wosher - 45c/c 4-40 Hes Nut. \$1.45/c 6 Lock Wosher - 45c/c 8-32 Hes Nut. \$1.50/c 8 Lock Wosher - 45c/c 8-32 Hes Nut. \$1.50/c 8 Lock Wosher - 45c/c 6 AMP SPST N.O. Coll Vehage 1 10 5V . \$2.00 \$1.50 6V . \$2.00 \$1.50 12V \$2.00 \$1.50 24V \$2.00 \$1.50 DISC CAPACITORS I.C. SOCKETS 8 pin Solder . 27c 210 100 pf/500V . . . 3.6c 14 pin Solder. 27c 3.6c 14 pin Solder. 29c 3.6c 16 pin Solder. 32c 3.6c 18 pin Solder. 34c 3.6c 24 pin Solder. 54c 3.6c 24 pin Solder. 54c 3.6c 14 pin W.W. 38c 100 pf/500V. 220 pf/500V. 470 pf/500V. 001/500V. 0022/500V. 5.5c 5.5c 5.5c 5.5c 5.5c 7.5c 3.5c 4.0c 6.0c 9.0c 4.5c 4.5c 4.5c 4.5c 4.5c 6.3c 3.0c 26c 42c . 10c . 5c . 6c . 9c .01/500V01/25V. 14 pin W.W. . 50c 390 .022/25V ... 6c .047/25V ... 9c .1/25V ... 12c 3,5c 5.3c 7.5c 2.7€ 16 pin W.W. . 54c 18 pin W.W. . 88c 24 pin W.W. . 99c 1/2 & 1/4 WATT CARBON COMP. RESISTORS 5 eoch of the 85 stondard 10% values (2.2-22M) ½ W Resistors (425 pcs.) Sorted by value \$12/ser 2-4 are \$11/set 5-9 are \$10/ser. 5 each of the 70 stondard 10% values (10-5.6M) ¼ W Resistors (350 pcs.) Sorted by value \$12/ser 2-4 are \$11/set 5-9 are \$10/ser. SILICON TRANSISTORS | 18 | 16-7 | 16 | 16.5 | 10-105 | 20.5 | 17.5 | 18.5 | 16.5 | 10-105 | 20.5 | 17.5 | 19.6 | 10.5 | 10.5 | 10.5 | 10.5 | EN930 EN222 EN2369A EN2907 EN27192 2N3391A 2N3392 2N3393 2N3593 2N3565 2N3638 2N3640 2N3640 2N3640 2N3643 FIELD EFFECT TRANSISTORS MPF102 . TO- 92 ,44 380 350 2N5457 . TO- 92 .47 .420 .375 NPN DARLINGTON TRANSISTOR MPS-A13. TO- 92 "Min. DC Current Gain of 5,000 at 10mA. Send for Free Catalog or Mail Readers Service Card COD ORDERS ACCEPTED FOR SAME DAY SHIPMENT CALL 218-681-6674

ADVERTISING INDEX

RADIO-ELECTRONICS does not assume responsibility for any errors which may appear in the index below.

ingex	below.
READE	R SERVICE CARD NO. PAGE
24	Allison Automotive 34
21	Amperex
20	B & K Division of
	Dynascan Corp
69	Blonder-Tongue 86
77	Brooks Radio & TV Corp 91
89	Castle TV Tuner Service CorpCover IV
11	Channellock 20
17	CIE, Cleveland Institute of Electronics26-29
14	Continental Specialties Corp. 24
	CREI, Division of the
	McGraw-Hill Continuing Education Center64-67
75	Datak Corp 90
68 79	Delta Products Corp. 81 E&L Instruments, Inc. 92
64	E&L Instruments, Inc. 92 Edlie Electronics 80
87	Edmund Scientific Co108
70	Edsyn, Inc
8	Instrument, Inc
	EMC, Electronics
27	Measurement Corp. 90 Exar. Division of James 76
76	Exar, Division of James 76 Fluke 90
85	Fordham Radio Supply Co 97
	GC Electronics
	Tube Div 18
74	Grantham School of
	Electronics 89
	GET Sylvania Electronic Components
19	Harwil Co 30
100	Heath Co14-15
6,30	Hickok Electrical Co12, 78
28	Hybrid Semiconductors 76 ICS, International
	Correspondence Schools 82-85
67	Indiana Home Study Institute 81
22	International Components Corp 32
18	International Crystal Mfg. Co. 30
65	Jensen Tool & Alloy 80
26	Jerrold Electronics
12	Judson Research 20
90 78	Leader
4	Mallory Distributor Corp 5
16	MITS, Micro-Instrumentation
	Telemetry Systems, Inc 25
72	Mountain West Alarm Supply Co 88
62	National Camera Co 78
	National Technical Schools 44-47
86	Non-Linear Systems, Inc 97
61	NRI Training8-11 PAIA Electronics78
1	PTS ElectronicsCover II
88	Radio ShackCover III
15	RCA Electronics Components,
80	Test Equipment
9	RCA Solid State Division 17
73	RGS Electronics
106	Rye Industries 94
63,13	Sams & Co. Howard W79, 22, 23
10	Howard W79, 22, 23 Sansui
	Canadi mining

READE	ER SERVICE CARD NO. PAGE
83	Schober Organ 96
7	Shure Bros
29	Southwest Technical Products 77
3	Sprague Products Corp 2
23	Tab Books 34
25	Telematic
66	Teletronics Company
82	of America
5	Tri-Star 96 Tuner Service Corp 7
84	TV Tech Special
2	Vaco Products Co 1
	Vintage Radio 94
71	Weller-Xcelite
	Electronics Division 88
	MARKET CENTER
102 105	Ancrona Corp105, 107
103,103	ATV Research100
92	Babylon Electronics102
92	Command Productions 98
	Cornell Electronics
0.4	Delta Electronics102
94 104	Digi-Key106
	E.F.I. Associates104
96	Bill Godbout Electronics 98
0.5	
95	International Electronics Unlimited103
98	James Electronics103
98	Lesco Electronics104
93,99	Meshna Electronics.
73,77	John Jr102, 105
	Mini Micro Mart100
97	Photolume Corp104
91	Poly Paks99, 101
71	Solid State Sales100
	Trumbull104
	Trumoun104
back P	Electronics is published by Gerns- ublications, Inc. 200 Park Ave. S. ork, NY 10003 (212) 777-6400
Preside	ent: M. Harvey Gernsback
Secreta	ary: Bertina Baer
	ADVERTISING SALES
EAST	
Radio-I 200 Pa New Yo	r Levitan, Sales Manager Electronics rk Ave. South ork, NY 10003 77-6400
MIDWE	ST/Toyas/Arkaneas/Okla

MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen The Ralph Bergen Co. 6319 N. Central Ave. Chicago, IL 60646 (312) 792-3646

PACIFIC COAST/Mountain States

Jay Eisenberg
J.E. Publishers Representative Co.,
8732 Sunset Blvd.,
4th Floor,
Los Angeles, CA 90069
(213) 659-3810

Sales Mart Building 1485 Bayshore Blvd., Box 140 San Francisco, CA 94124 (415) 467-0125

Orders Loss than \$10.00 add 50c Service Charge - Others Postpaid

"Only Quality Components Sold!"

DIGI-KEY CORPORATION

Thief River Falls, MN 56701

P.O. Box 126

7400N TTL

7400N 7401N \$.14 .17

7401N 7402N 7403N 7404N 7405N 7406N 7407N 7408N 7409N 7410N 7411N

7412N 7413N 7414N 7415N 7416N 7417N 7420N 7421N 7422N 7423N 7425N

7426N 7426N 7428N 7430N 7432N 7433N 7437N 7438N 7439N 7440N 7441N 7442N

4021AE 2.20 1.90 4022AE 1.80 1.60 4023AE .48 .45 4024AE 1.60 1.40 4025AE .45 .32 4026AE 8.40 7.90 4027AE .90 .80 4028AE 1.70 1.50 4029AE 2.20 2.00 4030AE .340 2.90 4035AE 2.00 1.80 4040AE 2.20 2.00 4040AE 2.20 2.00 4041AE 1.20 9.00

7444N \$1.05 7445N 1.04 7446N 1.10 7447N 1.00 7448N 1.00

.15 .23 .20 .26 .37 .25 .37 .37 .30 .49 .33 .38 .35 .60 .45 .55 .60

7444N 7445N 7446N 7447N 7448N 7450N 7451N 7453N 7454N 7456N

7460N 7462N 7464N 7465N 7470N 7471N 7472N 7473N 7474N 7475N 7476N 7476N 7478N 7480N 7481N

7482N 7483N

7483N 7484N 7485N 7486N 7489N 7490N 7491N 7492N 7493N 7494N .80 3.02 2.50 .40 2.40 .60 1.00 .84 .60

WAVEFORM GENERATOR XR205K KIT Only \$28.00

Here's a highly versatile lab in-strument at a fraction of the cost of conventional unit. Kit includes two XR205 iC's, data & applica-tions, PC board (etched & drilled, ready for assembly) and detailed instructions.

7496N \$.85 74100N 1.30 74104N 1.25 74105N .45 74107N .40 74109N .92 74110N .72 74111N .92 74115N .92 74115N .92 74118N 1.51 74121N .50

74121N .50 74122N .50 74123N .60 74125N .60 74125N .60 74126N .64 74128N 1.32 74132N 2.06 74136N .92 74140N 2.50 74141N 1.19 74147N 2.90 74145N 1.08 74147N 2.90 74151N .84 74152N 1.50 74154N 1.48 74155N 1.48 74155N 1.48 74155N 1.48

Туре

DUAL LOW NOISE OP AMP

V_{io} = 6mV I_{ie} = 1000 nA I_b= 2000 nA Noise = 1.5dB \$2.20

74161N 1.28
74162N 1.48
74162N 1.48
74164N 1.70
74165N 1.78
74165N 1.78
74166N 1.70
74165N 1.78
74160N 1.20
74173N 1.20
74173N 1.20
74175N 1.30
74175N 1.30
74175N 1.30
74180N 1.02
74181N 2.90
74185N 2.90
74185N 2.90
74193N 1.20



E : ce ... 7 B 0 6 0 0 1 B 2

0

CALCULATORS (Limited Qty.)

\$19.00

1024-BIT

N-Channel

RAM

DISPLAYS OPCOA SLA1 Red SLA11 Green SLA21 Yellow SLA7 Red LITRONIX DLSO Rec DL81 DL10 DL10A DL 101 DL57 DL61 DL33 DL44 DL44 DL402 DL701 DL704 DL707 DL747

74LS -

74LS00 74LS01 74LS02 74LS03 74LS04 74LS05 74LS06

74LS09 74LS10 74LS11 74LS15 74LS20 74LS21 74LS22 74LS30 74LS30 74LS51 74LS54 74LS54 74LS53 74LS73

· 88888888

1.60 6.00 6.00 6.00 4.00 4.90 9.90 12.00 4.00 6.00 4.00 3.40 2.25 2.35 2.50

Red XCITON XAN72 Red XAN52 Green 2.00

defendalmode EP 9125 9-DIGIT DISPLAY 1/8" character height
 compact, thin PC
 package
 wide viewing angle

OPTOISOLATORS MONSANTO

MCT2 1.35 LITRONIX IL1 1.30 IL12 1.40 IL16 1.80 IL74 1.35 ILD74 1.76 ILQ74 3.40

9300 SERIES 74LS76 92
74LS78 92
74LS107 92
74LS109 92
74LS112 92
74LS114 92
74LS113 2.38
74LS13 2.38
74LS15 2.30
74LS15 2.30
74LS15 2.30
74LS15 2.30
74LS15 2.30
74LS16 2.70
74LS17 3.92
74LS16 2.70
74LS17 3.92
74LS18 2.50
74LS16 3.97

9300PC 1.00 9301PC 1.20 9304PC 1.20 9304PC 6.90 9308PC 2.69 9308PC 1.60 9311PC 2.30 9311PC 2.30 9312PC 1.30 9314PC 1.30 9321PC 1.30 9321PC 2.50 9321PC 2.50 9321PC 2.50 9321PC 3.50 9321PC 2.50 9321PC 2.50 9321PC 2.50 9321PC 2.50 9321PC 3.50 9334PC 3.50 9334PC 3.50 934PC 3.50 934P

MV50 Red \$.3 1-AMP RECTIFIERS 10 100

10 100 1000 1.00 7.00 60.00 1.10 8.00 70.00 1.20 9.00 80.00 1.30 10.00 90.00 1.40 11.00 100.00 1.50 12.00 110.00 1.60 13.00 120.00 1N4001 1N4002 1N4003 1N4004 1N4005 1N4006 1N4007

LEDs

.125" dia.

209 Red 209 Yellow 209 Green

.160" dia.

216 Red 216 Yellow 216 Green

.200" dia.

220 Red 220 Yellow 220 Green

LOW PROFILE

226 Red \$.25 226 Yellow .30 226 Green .30 226 Orange .30

5053 Red .35 5053 Yellow .40 5053 Green .40 5053 Orange .40

216 = MV5024 5053 = MV5053

1000

119.00

.30

.30

PHASE-LOCKED LOOPS

LM567CM Mini-dip 2.10

DECODED READ/WRITE RAM

P1103 \$6.20

4056AE 3.45 4.40 4060AE 3.30 3.00 4060AE 1.20 1.00 4069AE 80 76 4076AE 1.70 1.50 4081AE 2.90 2.80 4518AE 3.30 3.00 4520AE 1.90 1.70 4901AE 45 3.8 4911AE 45 3.8 74S158N 2.40 74S160N 4.70 74S161N 4.70 74S174N 3.30 74S181N10.20 74S189N 5.10 74S199N 3.30 74S195N 3.30 74S195N 3.30 SCHOTTKY TTL 74S74N 1.30 74S85N 6.10 74S86N 2.70 74S112N 2.20 74S112N 3.60 74S133N 9.0 74S133N 2.40 74S139N 2.40 74S151N 2.40 74S157N 2.40 74S157N 2.40 4500N 4502N .45 .80 .75 .75 .80 .75 .65 .80 .80 .80 74S03N 74S04N 74S08N 74S10N 74S11N 74511N 74520N 74530N 74532N 74540N 74S251N 74S253N 745251N 2.40 745253N 2.40 745257N 2.40 745258N 2.40 745260N .90 745280N 5.70

LOW POWER HIGH SPEED TTL TTL 74H00N

74H53N 74H54N 74H55N 74H61N 74H61N 74H62N 74H71N 74H72N 74H73N 74H74N 74H76N 74H101N 74H102N 74H103N 74H103N 74L00N 74L02N 74L03N 74L04N 74L10N 74H00N 74H01N 74H04N 74H08N 74H10N 74H11N 74H21N 74H21N 74H22N 74H30N 74H30N 74H50N 74H51N .36 .36 .36 .36 .36 .36 .80 .74 .90 .87 .34 .38 .37 .40 .36 .36 .36 .36 .36 .36 .36 .36 74L20N 74L42N 1.62 74L42N 74L51N 74L73N 74L74N 74L90N 74L93N 74L95N 93L00 93L01 93L08 .74 .89 1.62 1.74 1.62 1.50 1.60 3.20 1.80 2.80 93L08 93L09 93L10 93L11 93L12 93L14 93L16 93L18 93L21 93L21

BIPOLAR MEMORY

C3101 P3101 C3101A P3101A IM5501CDE IM5501CPE MM5560D MM5560N 6.50 4.90 7.30 5.80 7.30 5.80 7.30 5.80 5.80 DM8599N 93403PC

P1101A P1101A1 1402AN 1403AH 1403AN 1404AH 1405A 1506 1507 1602 1702 C2102 P2102 C2102-1 P2102-1

TWO-PHASE MOS CLOCK DRIVER MH0026CN \$5.50

INTERFACE DM8820N DM8820AN DM8820AN DM8831N DM8831N DM8831N DM8832N N8T26B 9600PC 9601PC 9601PC 9615PC 9615PC 9615PC 9615PC 5.20 6.00 4.40 1.30 1.20 2.10 2.30 2.40 5.00 3.50 4.00

4.20 1.80 1.70 3.20 3.50 1.50 1.80 2.80 3.70 4.00 4.20 6.50 3.00 2.70

93L22 93L24 93L28 93L34 93L38 93L40 93L41 93L60 93L60

9617PC 9620PC 9621PC

COMPUTER

A PORTABLE 4% DIGIT MULTIMETER FOR \$299 A 10 MHZ

PULSE GENERATOR

Interdesign 1101: 0.1Hz-2MHz, 0-5V Output, var. width, line or battery operation. \$159.00



We've been buying and selling top quality components for nearly ten years, Our annual volume exceeds \$3 million. We handle only original parts, from the world's FIRST

companies. Now you can take advantage of our component buying skills and power and select

from a broad range of advanced circuits.

leading manufacturers and our customers include DUALITY some of the largest and most quality-conscious ONLY **AUDIO AMPS**

K SOCKETS

V W Ω Price SOLDER - TIN B pln DIL .22 14 pin DIL .26 16 pin DIL .29 24 pin DIL .75 28 pin DIL 1.10 36 pin DIL 1.70 40 pin DIL 1.90 Type V W II S B LM352 A 6-15 1.15 8 LM354A 6-15 1.15 8 LM354A 6-27 2.80 8 TAA611812 6-15 1.15 8 TAA621A12 6-27 1.40 8 TBA8610AS 420 2.50 4 TBA800 5-30 4.70 8 TBA810AS 420 2.50 4 TBA8030 5-20 2.00 4 TCA940 6-24 6.50 8 1.60 1.60 2.00 3.00 2.20 3.00 1.70 2.20 4.40 WIRE WRAP-GOLD 14 pin DIL .45 SOLDER - GOLD 14 pin DIL .35 16 pin DIL .40

TEFLON
3 pin TO-5 .55
4 pin TO-5 .65
6 pin TO-5 .90
8 pin TO-5 1.10
10 pin TO-5 1.40 2524V Recirculating 512 Bit Dynamic Shift Register 1-24: \$3.90 25 up: \$3.80 FM STEREO DEMODULATOR

MOS-LSI C2102-2 P2102-2 2505K 2512K 2512K 2521V 2524V 2525V 2533V 3341PC MM5025N MM5025N MM5055N MM5055N MM5055N MM5055N 8.00 6.00 3.30 5.50 4.00 3.90 5.30 8.50 8.20 20.00 20.00 20.00 5.50 5.50 5.50 5.40 8.00 6.40 4.10 4.00 33.00 33.00 8.00 6.00 8.00 6.00

INTERSIL 8038 PRECISION WAVEFORM

GENERATOR & VCO For simultaneous sine, square and triangular waveforms <.001 Hz to 1MHz. Part No. 1-9 8038CCPD \$4.50 10 up \$3.70 MM404H 12.00 MM405H 23.00 MM407H 6.50 MM407H 6.50 MM451H 11.40 MM500H 2.00 MM500H 3.20 MM507H 3.20 MM550H 5.60 MM555H 5.60

XB1310 \$3.90

MM

XR-215 PHASE-LOCKED LOOP For FM or FSK demodulation, freq. synthesis and tracking filter applications. 5 to 26V from 0.5Hz to 35MHz. Accepts analog signals 300mV to 3V. Interfaces with DTL, TTL & ECL

1-24 \$15.00

MINIMUM ORDER: \$10.00
Add \$1.00 to cover postage and handling SEND CHECK OR MONEY ORDER (NO C.O.D.) TO:

California residents add 6% sales tax.

P.O. BOX 2208R, Culver City, CA 90230

INTERFACE MODULES

Instr. Amp., Bipolar Input Instr. Amp., Bipolar Input Instr. Amp., FET Input DAC, 12 Bit, Low Drift DAC, 12 Bit, Low Drift DAC, 12 Bit, Low Drift DAC, 4 Dialt BCD, Low Cost ADC, 8 Bit, Sect. Counting, Low Cost CY1010 CY1011A 29.00 49.00 CY1010 CY1011A CY1020 CY1021 CY1021A CY2137 CY2218 CY2237 CY2735 CY3035 89.00 ADC, 3 Digit BCD, Sect. Count, Low Cost CY3635

LINEAR KS

H=TO5 N=DIP M=MINI-DIP D=CER-DIP K=TO3

LM114H LM300H LM300N LM301AH LM301AN LM301M LM301H LM302D LM302N LM302N LM304H LM305H LM711CN LM715CH LM715CD LM723CH LM723CN LM725CH LM725CH LM725CD LM311H LM311D LM311M LM311N LM312H LM312H LM322H LM329N LM320-5T LM320-12T LM320-12T LM340-06K LM340-06K LM340-06K LM340-12K LM340-15K LM340-15K LM340-15K LM340-15K LM340-15K LM340-15K LM340-15K LM340-15K LM340-15K LM311H 75107 1.20 751078N 2.60 751088N 2.30 75109N 2.20 1.10 .90 .90 3.50 1.30 1.50 75109 N 75110 N 75115 N 75138 N 75150 N 75154 N 75208 N 75234 N 75450 N 75451 N 75452 N 75453 N LM725CD LM733CH LM733CD LM733CN LM741CH LM741CD LM741CM LM741CN LM747CH 2.20 2.25 2.25 2.95 3.10 4.10 2.70 2.50 1.25 1.00 1.00 LM305H LM305AH LM305AH LM305N LM306H LM307H LM307M LM307N LM747CN LM747CD .95 .75 .95 1.50 1.20 5.00 2.00 1.75 1.95 1.60 1.80 7520 SERIES LM748CM LM748CN LM777CH LM777CM LM3046CN LM3054CN SG4501T SG4501N LM307N LM308H LM308AH LM308A LM308M LM309H LM309K LM310H LM310M SENSE AMPS LM340-24 LM555CM LM556CN LM709CH LM709CN LM710CH LM710CN LM711CH 4.00 2.00 4.25 1.75 2.00 4.50 7520N 7521N

HYBRID Power **AMPLIFIERS**

SI-1010G 10W \$6.90 SI-1020G 20W 9.90 SI-1030G 30W 18.70 SI-1050G 50W 25.90

POWER TRANSISTORS

BU204 3A 1300V \$4.14 BU205 3A 1500V 4.95 BU206 3A 1700V 5.94 BU207 6A 1300V 5.93 BU208 6A 1500V 6.93 BU209 6A 1700V 8.64

K POWER REGULATORS

LM335K: 5V, 600mA 2.40 LM336K: 12V, 500mA 2.90 LM337K: 15V, 450mA 2.90 15000 COMPACE 700

USRT UNIVERSAL SYNCHRONOUS RECEIVER/TRANSMITTER from Standard Microsystems

STR, SSC, bi-sync and interleaved bi-sync modes of operation of fully programmable of full or half duplex operation of fully double buffered offerctly TTL compatible on the fully double buffered offerctly TTL compatible on the full of 1·9 10 up \$30.00 \$24.00

DEN 7938 7943

COM2502 UART

UNIVERSAL ASYNCHRONOUS RECEIVER/TRANSMITTER from Standard Microsystems

Direct TTL compatibility e full or half duplex operation • fully double buffered • fully programmable • high speed operation • fri-state outputs

PRICE: 1-9 10 up

\$13.20 \$10.60

SPECIFICATION SHEETS: \$.25 ea

107

LIVE IN THE WORLD OF TOMORROW ... TODAY!

And our FREE 180 PAGE CATALOG is packed with exciting and unusual values in electronic, hobby and science items - plus 4.500 finds for fun. study or profit . . . for every member of the family



A BETTER LIFE STARTS HERE

3.CHANNEL COLOR ORGAN KIT

Easy to build low-cost kit needs no technical knowledge. Completed unit



technical knowledge. Completed unit has 3 bands of audio frequencies to modulate 3 independent strings of colored lamps (i.e. "lows"-reds, "middles"-greens, "highs"-blues. Just connect hi-fi, radio, power lamp etc. & plug ea. lamp string into own channel (max. 300w ea.) Kit features 3 neon indicators, color intensity controls, controlled individ SCR circuits: isolation transformer; custom plastic housing; instructions.

Stock No. 41,831 EH

\$18.95 Ppd.

AM RADID FITS IN/ON YOUR EAR!

Wear it inconspicuously everywhere,
Listen as you work (lawn, yard, office), watch (game, beach) or wait.
Instant music, news, sports. No
gimmick, our 6/10 oz. Technological
wonder has integrated circuit, 11
transistors, patented ferrite antenna/
tuner/volume dial. Uses normal silver
oxide hearing aid batt. (incl) for approx. 100 hrs. playing.
New batt. to slip in avail. at drug stores (about 50c). No
lengthy wires, bulky cases, or power-packs!



Stock No. 42,275 EH

\$14.95 Ppd.

GET A CHARGE FROM THE SUN!

Our 12V Solar Battery Charger allows direct conversion of light-to-electricity. Compact panel put on a boat can automatically charge its 12V battery over entire daylite period. Use anywhere for a trickle charge. Big value, it comprises 30 2V silicon solar cells in series w/diode



\$89.95 Ppd.

No. 71,971 EH (AB. 30 W-HRS./WK.) 9x18" HI CURRENT MODEL (6W, 12V, 500 mA) No. 72,010 EH (AB. 150 W-HRS./WK.) \$420.00 Ppd

Ex6" LO VOLTAGE MODEL (1.5V, .38W, 250 mA) No. 42.172 EH

\$49.95 Ppd.

WHICH ARE YOUR CRITICAL DAYS?

Can Bio-rhythm tell you? We're not sure, but we're told that vast mood shifts are caused by your body's Internal Time Clock whose rhythms can be charted ahead to possibly warn you of "critical" days. Some are great, some blah. Maybe it's your physical, emotional & intellectual at the right or wrong time. Compute your cycles with our Bio-rhythm kit and judge for yourself. Incls Charting kit, metal Dialgraft Calc. instrs.



\$11.50 Ppd.

Stock No. 71,949
1 YR. PERSONALIZED REPORT — BY COMPUTER
Stock No. 19,200 (Send Birthdate)

\$15.95 Ppd.



He-Ne LASERS . . . \$115.00 up!

Top quality lasers feature TEMoo mode, internal mirror plasma tubes w/10,000 hr. life, self-starting cold aluminum cathodes, low noise & ripple, guaranteed output power stability and more for demanding lab work. 18-mo. mfr. wty. 115v AC

(A) 0.5mW . . . 0.88 Beam Dia., 1 mRad Diverg. = 79,070 EH (2.6x8.5x14.8")
(B) 1.0mW . . . (as above) = 79,073 EH
(C) 4.0mW . . . 0.8 Beam Dia., 1.1 mRad Diverg. = 79,079 EH (3.9x5.5x15.6")

\$150.00 Ppd.

.\$485.00 Ppd.

TEST YOUR DEGREE OF ESP!

Which light comes on when you push the button — Star. Square, Triangle or Circle? If you've got ESP you or your subject will guess right, significantly. Solid state ESP Tester has guaranteed random circuit for accuracy — you can't beat the ability, telepathy experiments. Portable. Reg. 4 "D" batt.

.

No. 72,090 EH (61/4x33/4x2")

\$29.95 Ppd.

EXTRA PADS TO RECORD 250 EXPERIMENTS Stock No. 72,092 EH

\$3.50 Ppd.



. LOW COST 7X INFRA-RED VIEWER

For Infra-red crime detection surveillance, security system alignment, I.R. Detection, laser checking, nite wildlife study, any work req. I.R. detection & conv. to visible spectrum. Self cont. scope w/everything incl. I.R. light source. 6v adjust. triplet eyepiece. Focuses from 10' to infinity.

8275.00 Pnd.

No. 1659 EH (11x141/4x3") WITHOUT LIGHT SOURCE No. 1648 EH

\$275.00 Ppd.

\$225,00 Ppd.



NEW! KIRLIAN PHOTOGRAPHY KIT!

Experiment in the fascinating new field of "Kirlian electrophotography"—images obtained on film without camera or lens by direct recording of electric charge transmitted by animate & inanimate objects. Each "aura" differs—animate aura said to changes. Kit incls portable darkroom, double transformer isolated from power source: instructions.

No. 71,938 EH

"HIGH VOLTAGE PHOTOGRAPHY" by H. S. Dakin No. 9129 EH (60-PG.) PPBK BK.)

\$5.00 Ppd.

DELUXE KIRLIAN PHOTOGRAPHY SET NO. 72.053 EH

\$399.00 Ppd.



KNOW YOUR ALPHA FROM THETA!

For greater relaxation, concentration, listen to your Alpha-Theta brain-waves. Ultra-sensitive electrode headband slips on/off in seconds—elimi-

nates need for messy creams, etc.
Atch'd to amplifier, filters brainwaves, signals beep for ea. Alpha
or Theta wave passed. Monitoring
button simulates Alpha sound; audio & visual (L.E.D.) feedback.
Reliable, easy-to-use unit—comparable to costiler models. Completely safe. Comprehensive instruction booklet.

No. 1635 EH (8x3x4"; 24 oz.) LOW COST "STARTER" UNIT No. 71,809 EH

\$55.00 Ppd.

DELUXE "ON" TIME MONITOR MEASURES & RECORDS %
No. 1652 EH \$349.50 Ppd.



MAIL COUPON FOR CATALOG:

180 PAGES . MORE THAN 4500 UNUSUAL BARGAINS

Completely new 1975 edition. New items, categories, Illustrations. Dozens of electrical and electromagnetic parts, accessories. Enormous selection of Astronomical Telescopes, Unique lighting and ecological items. Microscopes, Binoculars, Magnifiers, Magnets, Lenses, Prisms. Hard-to-get surplus bargains. Ingenious scientific tools. 1000's of components.

EDMUND SCIENTIFIC CO.
300 Edscorp Building, Barrington, N.J. 08007
Please rush Free Giant Catalog "EH".

Address _

State



COMPLETE AND MAIL WITH CHECK, M.O. OR CHARGE NO.

EDMUND SCIENTIFIC CO.		CO. 300 Edscorp Buil	ding, Barrington, I	N.J. 0800
Ho	w Many Stock No.	Description	Price Each	Total
PLEASE SEND GIANT FREE CATALOG "EH"				_
Charge my BankAmericard *				
		00, Orders Under \$5.00, 50¢,		
Interbank No.	AMERICAN Master charge	i enclose Check money	order for TOTAL \$	

My C

ard No. Is		. 4.	3

Card Expiration Date. 30-DAY MONEY-BACK GUARANTEE. You must be satisfied or return any purchase in 30 days for full refund. *\$15.00 minimum refund.

NameAddress		
City	State	Zip

Circle 87 on reader service card

ı

Radio Shack announces new heights in Archer antennas!

New FCC rules allow your omnidirectional CB antenna to be 60 feet above ground—triple the old limit! Take advantage of the amended rules to upgrade your antenna (Part 95, Sections 95.3 & 95.37C).

Deluxe Colinear. Outstanding 4 dB gain and low radiation angle—this is the one for maximum omnidirectional CB range. 19-ft., 10-in. 5/8-wave radiator. Static dissipator. Fits masts to 1-5/8" dia. #21-1133.

"Super Maxim." More gain (3.75 dB) than many high-priced omni's. 5-section seamless aluminum half-wave radiator, 52" radials, static dissipating hex loops, 1.25-to-1 VSWR. Fits masts to 1-5/8" dia. #21-902.

Ground Plane. The low-priced "omni with the mostest." All tubular aluminum elements, quarter wave radiator, three 108" quarter wave radials, static discharge protector. Fits masts to 1-5/8" dia. #21-901.

FREE New 1975 Radio Shack Catalog

OVER 2000 PRODUCTS EXCLUSIVES ON EVERY PAGE BEAUTIFUL FULL COLOR


Stereo • Quadraphonic • Phonographs
TV Antennas • Radios • Citizens Band
Kits • Recorders • Tape • Tools
Auto Tune-Up • Electronic Parts
Test Instruments • More!



164 pages of the finest in home and hobby electronics Respected brand names like Realistic, Micronta. Archer. Science Fair — and they're available only at Radio Shack stores and dealers nationwide! See what's really new in electronics by getting this catalog now.

SEND FOR YOURS TODAY! FILL OUT COUPON BELOW

1975 Catalog	Mail to Radio Shack, P. O. Box 1052, Ft. Worth, Texas 76101. (Please print.)
Name_	Apt. No
Street_	
City	
State	ZIP

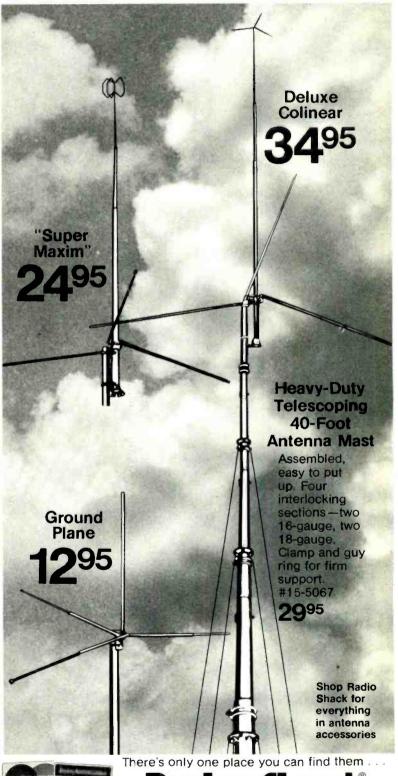

3000 STORES • 50 STATES • 7 COUNTRIES

Retail prices may vary at individual stores

Bank Americard at participating stores

Circle 88 on reader service card

Mastercharge or

Proved in the lab! ... approved in the field!



The NEW MEZZER

TELEVISION FIELD STRENGTH METERS

Invaluable for

Antenna installation

Antenna evaluation

Output calibration of TV signal generators and similar signal sources

The instruments use two 9v alkaline transistor batteries for field use, plus inbuilt power supply with wall plug-in transformer for 120vac operation.

VHF Model FSM - V net \$119.95

Range: 20 microvolts to 100 millivolts

Meter: Scale calibrated in microvolts (linear) and dB (log.). Ref: 0dB =

l millivolt. Full scale basic range l millivolt Attenuator: X 1 (+ 0dB); X 10 (+ 20dB); X 100 (+ 40dB)

All 12 VHF channels Tuning:

75 ohms - "F" connector; 300 ohms - screw terminals ± 3dB typ. Inputs:

Accuracy:

Model FSM - U UHF net \$99.95

Range: 20 microvolts to 10 millivolts

Scale calibrated in microvolts (linear) and dB (log.) Meter:

Attenuator: X 1 (+ 0dB) and X 10 (+ 20dB) Tuning: Full UHF band. Ch. 14 - 83

Inputs: 75 ohms - "F" connector; 300 ohms - screw terminals

Accuracy:

These instruments boast the extra features of all Castle products-advanced technology-modern styling-and they work!

Ask your electronic distributor for them . . . or write for more details.



CASTLE TV TUNER SERVICE. INC.

5715 N. Western Ave., Chicago, III. 60645 • Ph. 312-561-6354

In Canada: Len Finkler Ltd., Ontario