

RADIO ENGINEERING

*A Magazine of Technical Accuracy
for the Radio Engineer, Dealer, and Manufacturer*

Edited by M.B. SLEEPER

NO-LOSS REGENERATIVE SET

ELIMINATION OF LOSSES AND THE USE OF A SPECIAL CIRCUIT MAKE THIS OUTFIT OF INTEREST TO DX OPERATORS.

DATA ON THE R-A-R REFLEX CIRCUIT, GIVING AMPLIFICATION AT AUDIO AND RADIO FREQUENCIES AND FROM REGENERATION.

DESIGN OF THE BOONTON LIGHT FOUR PORTABLE RECEIVER.

20c a Copy—In England, 1/-

AUGUST, 1924

Vol. 4 No. 7

"THE AIR IS FULL OF THINGS YOU SHOULDN'T MISS"



Eveready "B" Battery No. 772 for detector and amplifier. Connections at 22½ and 45 volts. Three Fahnestock Clips. Approximate over-all dimensions, 8¼ in. x 3¼ in. x 7¾ in.

Sustained power!

WHERE table or cabinet space is limited, use this new vertical 45-volt Eveready "B" Battery No. 772. It has the same long life, the same steady high power as the horizontal Eveready 45-volt "B" Battery, but because it stands upright it takes less than half the table space.

Tables and most battery cabinets have more headroom than floor space. This battery is built in recognition of that fact. It fits the Radiola Super-Heterodyne cabinet perfectly.

Many multi-tube receiving sets use a "hard" detector tube which does not require fine adjustment of "B" voltage, so the new Eveready Vertical 45-volt "B" has but three plainly marked terminals, negative, plus 22½ and plus 45 volts.

Standing upright to save space, made of large, powerful cells to last longer, here is the battery you've been looking for.

Manufactured and guaranteed by
NATIONAL CARBON COMPANY, Inc.
New York San Francisco
Headquarters for Radio Battery Information

Canadian National Carbon Co., Limited, Toronto, Ontario
If you have any battery problem, write G. C. Furness, Manager, Radio Division, National Carbon Co., Inc., 130 Thompson Ave., Long Island City, N. Y.

EVEREADY

Radio Batteries

-they last longer

Eveready 6-volt Storage "A" Battery



No. 767
"B" Battery, 45
volts. Variable
taps. Fahnestock
Clips



No. 766
Eveready "B"
22½ volts.
Six Fahnestock
Spring Clip
Connectors




No. 771
Eveready "C"
Battery.
Clarifies tone
and prolongs
"B" Battery
life



No. 764
The Space
Saver.
Vertical
22½-volt
"B" Battery



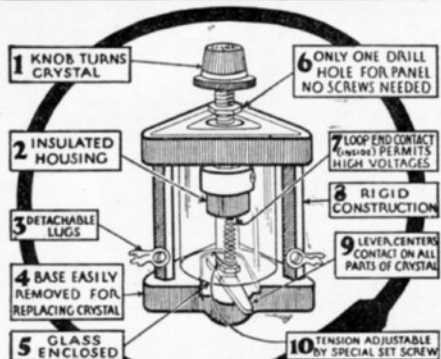No. 7111
Eveready Radio
"A" Dry Cell.
Specially manu-
factured for use
with dry cell
tubes



Best Crystal Ever Designed!

FRESHMAN

Double Adjustable Crystal Detector

At last the experimenter who has searched for the ideal crystal can now depend upon a perfect detector. The new Freshman Double Adjustable Crystal Detector has met every requirement of the ideal unit. It affords uninterrupted, noiseless, distortionless reception, yielding extraordinary volume with entire absence of squeals and howls often introduced by vacuum tube detectors.

The World's Best for Crystal or Reflex Sets

No more searching for the sensitive spot—merely turn the knob as you would a dial.

Freshman Double Adjustable Crystal Detector for panel or base use, complete **\$1.50**

Freshman Super-Crystal with Non-Metallic Housing. Fits any standard detector unit... **50c**


At your dealer's, or send purchase price and you will be supplied postpaid.

FREE! Write for building plans and hook-ups of Super-Heterodyne, Reflex and other popular circuits.

Chas. Freshman Co. Inc.
Radio & Condenser Products
106 Seventh Ave., New York

FRESHMAN

Noiseless Tested Mica Condensers

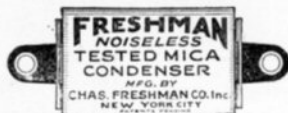

maintain their fixed capacity due to scientific design and construction in which constant equal pressure is exerted on the condenser plates over the entire area, making the Freshman condensers the only ones that avoid noises due to variable pressure on the plates. A metal casing protects the plates and reduces hysteresis losses to a minimum.


Capacity	Each	Capacity	Each
.00005 \$0.35	.0025 \$0.50
.000135	.00360
.0001535	.003570
.000235	.00475
.0002535	.00575
.000335	.00675
.0003535	.0075 1.00
.0003535	.008 1.00
.000640	.009 1.00
.000840	.01 1.00
.00140	.015 1.50
.001540	.02 2.00
.00240	.025 2.50

Exclusive Features of Freshman Noiseless Tested Mica Condensers

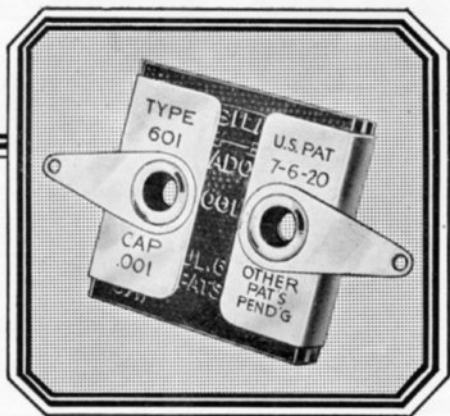1. No losses through di-electric hysteresis of fibre covers.
2. No insulating binder to melt at the application of heat and by releasing pressure, change the capacity.
3. Capacity fixed and invariable.
4. Metal case protects against accidental injury.
5. Direct connection to copper plates avoids losses through inefficient eyelet contact.
6. Application of soldering iron does not affect condenser.

At your dealers—otherwise send purchase price and you will be supplied postpaid.

Chas. Freshman Co. Inc.
Radio & Condenser Products
106 Seventh Ave., New York



MICADONS

Condensers of Fixed and Permanent Capacity

You will have condensers that maintain their fixed capacity if you buy Micadons.

These accurate Dubilier Micadons are found in over ninety per cent of the sets made by amateurs and manufacturers throughout the country. The experts specify Micadons.


The name Dubilier on a condenser has the same meaning as the name Sterling on silverware—highest quality.

There is a Micadon for every circuit—different types are made for different requirements.

For free booklet showing methods of soldering Micadons in radio circuits address 45-49 West Fourth street, New York.

Dubilier

CONDENSER AND RADIO CORPORATION

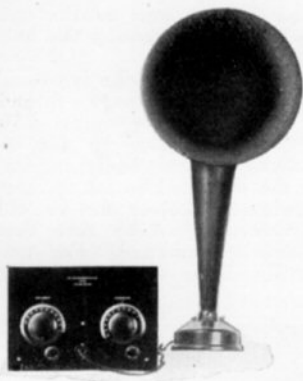

No-Loss Regenerative Set

The condenser-tickler feed back circuit, giving a perfect control of the regeneration, is used with a mechanical design in which losses are at a minimum, making the selectivity and sensitivity unusually high

IN spite of the popularity of reflex and tuned radio frequency receivers there is still a persistent demand for improvements in regenerative receivers, and particularly, judging from requests, for 2-tube outfits, capable of giving loud speaker volume from stations within a moderate radius and telephone reception over an almost unlimited range.

With these ideas in mind, we have worked for some time to develop an outfit meeting those requirements plus several refinements which most regenerative receivers lack. The two-variometer outfit is much too large for convenience, and rather expensive to build. The one-variometer and coupler, with condenser tuning for the secondary, is good altho it, too, requires a fairly large panel, and too often trouble is experienced in making the set regenerate properly over the entire wavelength range. It is not practical to use the single circuit receiver in congested areas. More than that, it has two defects which appear in the operation, that is, the wavelength is altered when the tickler is rotated and the circuit breaks quite sharply into oscillation.

Description of The Type 6300 Receiver

In the type 6300 receiver we believe that the three-circuit regenerative outfit has been made up into a set embodying practically all of the refinements brought out so far in appearance, operation, and efficiency.

The circuit, shown in Fig. 6, is one which has never been used in any manufactured equipment, probably because it is known to very few radio men. You will see that an untuned primary is used coupled to a secondary coil controlled by a variable condenser. The fixed tickler, also coupled to the secondary, is in series with another variable condenser which runs to the filament of the detector tube. From the plate a radio frequency choke coil is

connected to the telephones and on to the detector plate battery.

Because of the radio frequency choke coil, no R. F. currents pass in the telephone circuit but, instead, flow through the tickler coil and the condenser to the filament. When the regeneration condenser is at minimum capacity, the impedance is so high that the tickler does not feed back sufficient energy to make the circuit regenerate or oscillate, but regeneration and oscillation take place when the impedance is reduced by increasing the capacity. A fixed condenser of 0.00025 mfd. is shunted around the variable because the working capacity range from no regeneration to full oscillation is 0.00025 to 0.00075 mfd. A larger variable condenser could have been used but the addition of a Micadon served the purpose just as well.

By this arrangement, a perfectly smooth regeneration control is obtained, without any tendency for the set to jump into oscillation as the regenerative action is increased. Therefore, the adjustment can be brought right up to the point of maximum regeneration without distortion.

A pickle bottle coil is used for the inductance unit. This form of wiring practically eliminates the losses in the secondary and not only makes the tuning sharper but gives a slight increase in the signal strength.

As for the mechanical arrangement, it worked out so as to give a symmetrical arrangement, thoroughly workmanlike in appearance.

Standard Parts Required

A Formica sheet 7 by 10 ins., serves as the front panel, while two panels 3½ by 9 ins. are used for the sub and tube panels. All are 3/16 in. thick.

The instruments themselves comprise two 0.0005 mfd. vernier variable condensers from the General Instrument Company, two Marshall-Gerken sockets, two

type 1A Amperites, a Carter 3-spring filament control jack, 1 to $4\frac{1}{2}$ ratio Thordarson A. F. transformer, six Eby binding posts, two 0.00025 mfd. Micadons, and two 3-in. Kurz-Kasch knobs and dials.

In addition, there is the inductance unit to make up as well as the R. F. choke coil. For hardware, three panel support pillars, $\frac{3}{4}$ ins. long by $\frac{3}{8}$ -in. diameter, threaded for 6-32 screws at each end, two left hand and two right hand angle brackets, and four coil support pillars, $\frac{11}{16}$ -in. long by $\frac{5}{16}$ in. diameter, threaded

minimal indications on the tops so that no errors will be made in connecting the batteries.

Winding the
Choke and Coil
Unit

The R. F. choke is wound on an ordinary thread spool, with about 250 turns of No. 38 silk or enameled wire. The exact size is not important so that the wire can be taken from a 75-ohm telephone receiver or an old spark coil secondary. Just be sure that the insulation is not damaged. For terminals, we simply drove short pieces of

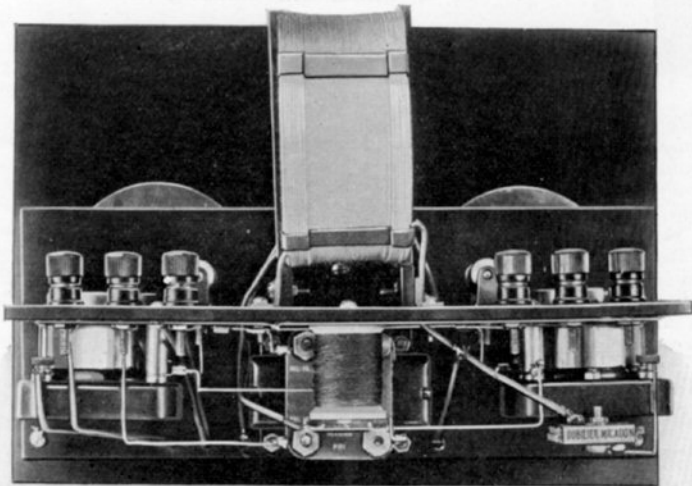


Fig. 1. A rear view of the No-loss receiver. The choke coil is directly underneath the inductance unit and in front of the audio transformer

clear through for 6-32 screws, are necessary.

Drilling The Panels

Since the drawings of the panel layouts in Figs. 4 and 6 are at one-half scale, each dimension must be doubled when it is transferred to the panel. When you lay out the holes, work entirely from the bottom edge of the panel and of the drawing, measuring upward from the bottom and to the right and to the left of the center line. This is the most accurate way because no errors will be introduced if the panel is not cut perfectly.


The holes for the socket tubes are made with a $\frac{1}{2}$ -in. Stevens panel cutter. A $\frac{3}{16}$ -in. center hole, to start the panel cutter, must be made first. Then the large hole can be cut out very quickly. This is far more satisfactory than drilling a circle of small holes.

It improves the appearance of the set to have the panels engraved. If, however, you do not have this work done, it is advisable to use binding posts with the ter-

Wirit into the end of the wooden spool and soldered the leads to these wires.

If you have wound any pickle bottle coils already you will have no trouble with these units. Be sure, however, that you understand how the extra turns are put on which serve as leads.

The coil should be wound on a bottle $2\frac{3}{4}$ to 3 ins. in diameter. Twelve strips of gummed paper tape are required, measuring $\frac{3}{8}$ by 4 ins. The secondary, of 45 turns of No. 20 D. C. C. wire, is put on first, and the ends of the tape bent over on to the coil and stuck down in the usual manner. This completed, two turns are put around the bottle a little distance from the end of the secondary winding, and the wire brought back on to the coil again at a point directly opposite that at which the secondary was started. Then, turning the bottle in the same direction, eight turns are wound on top of the secondary. Paper strips should be put under this coil, directly on top of the strips which already hold the secondary. After eight turns have been

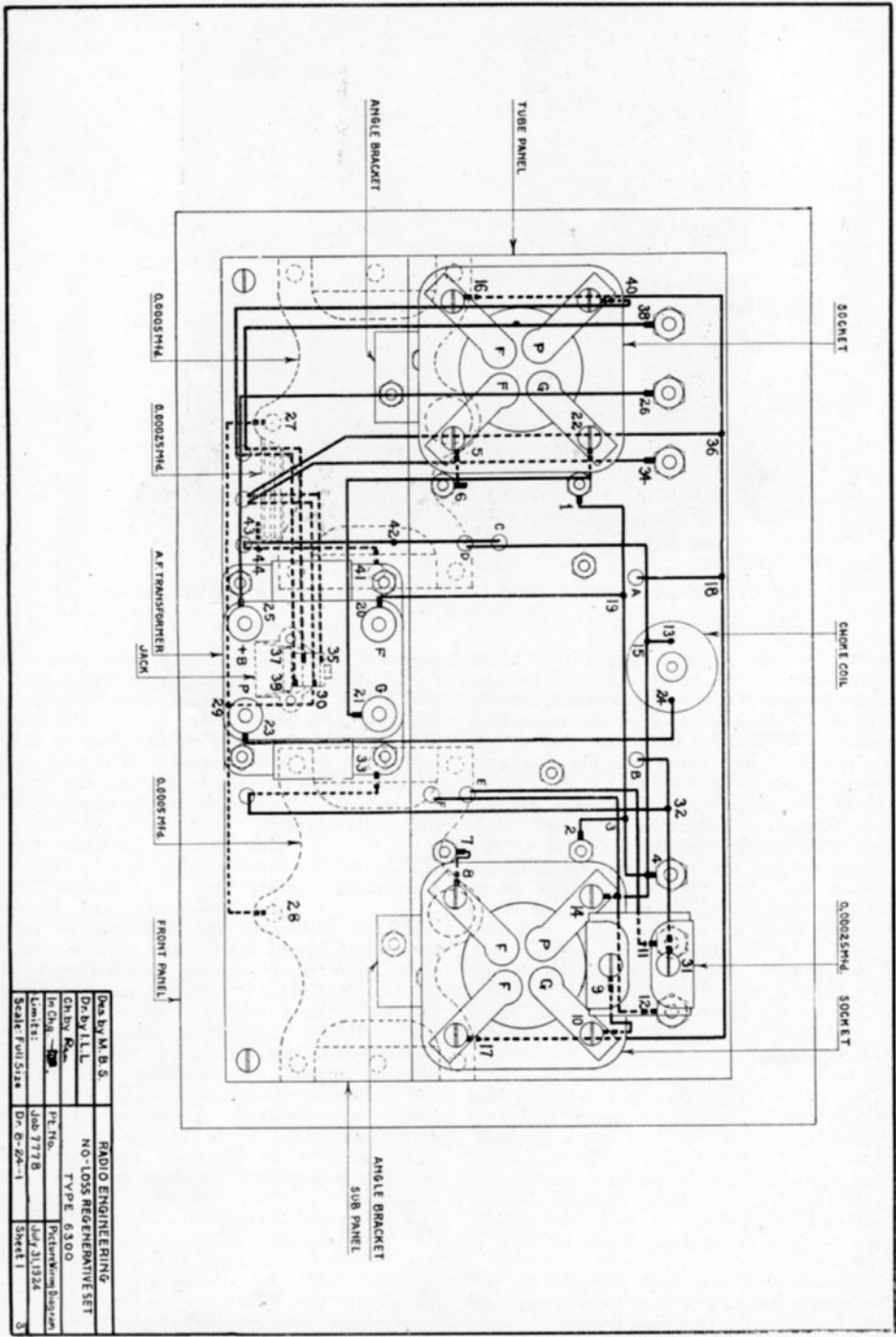

Des. by	M. B. S.	RADIO ENGINEERING
Dr. by	L. L.	NO-LOSS REGENERATIVE SET
Ch. by	R. S.	TYPE 6300
In Chrg.	W. S.	
Number	Job 777 B	Printed Wiring Diagram
Scale	Full Size	July 31, 1924
	Dr. 6-26-1	Sheet 1
		3

Fig. 2 Picture wiring diagram of the set. The tube panel has been turned upward to show the wiring as it appears underneath

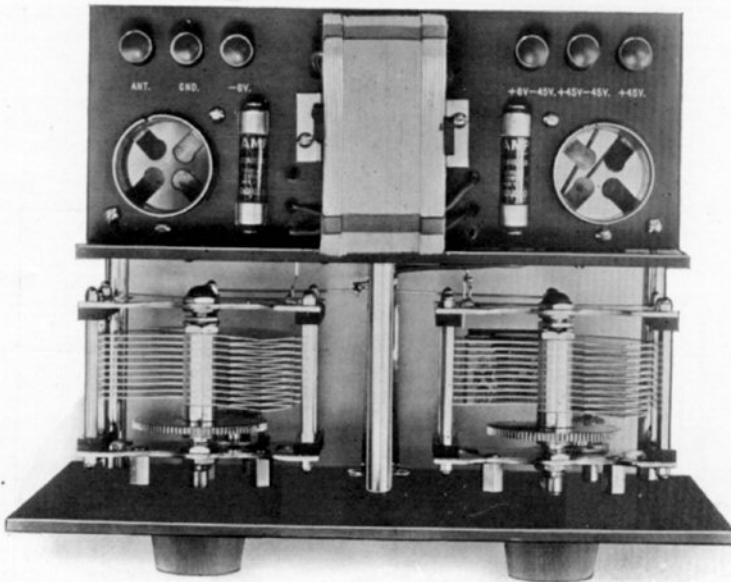


Fig. 3. No arrangement could be more attractive than the interior of the No-loss receiver

put on for the plate coil put two turns around the center of the secondary and bring the wire over to within one-fourth of an inch of the beginning of the secondary winding. With strips under the coil as before, wind on six turns for the primary. That completes the winding.

Only the work of cutting and sticking down the strips remains. Cut off each outer strip at the tickler coil and at the antenna coil so that they are not quite as long as the coils are wide. Bend them over and stick them down. At this stage the bottle must be broken out from inside the coil. Do it carefully or you will cut the insulation. Finally, bend the inside strips toward the outside of the coil and around to the inside. This sounds hard but you will see just how it works out when you are actually making the inductance unit.

The two extra turns put around the bottle at the end of the secondary coil provide leads from the end of the secondary and the start of the tickler. The two turns at the center of the secondary are for the end of the tickler and the start of the antenna coil. Cut these turns in the middle so as to leave fairly long leads, at least 8 or 10 ins.

No binder of any sort is used on the wire, partly because it is not necessary and partly because it introduces losses.

The coil supports, shown in Fig. 6, are arranged so as to have as little insulating

material as possible within the magnetic field. When you cut out these strips, make two pieces 1 in. by 4 ins. Then saw down the long sides before you cut in at the base. Do not make the coil slots too deep or they will make the strips crack. It is also important to be careful in drilling the holes for the screws which hold the supports to the angle brackets.

Notes
On the
Condensers

The vernier variable condensers illustrated are of very efficient design and give extremely low losses.

This set, however, was arranged to take the new General Instrument condensers, a very interesting design development in which Pyrex glass is used for the insulation. Instead of hard rubber strips, metal strips are used, but each metal strip carries a thimble into which a short rod of Pyrex glass is forced. At the other end of the rod is another thimble to which the fixed plates are secured. This new type is recommended in place of the condensers shown altho when this outfit was assembled the Pyrex-insulated condensers were not available.

Two special features are incorporated in the new design. Mechanically the construction is far stronger and is not effected in any way by temperature changes. Moreover, the losses are so low that the condensers are equivalent to the very elaborate quartz-insulated types used by the Bureau of Standards.

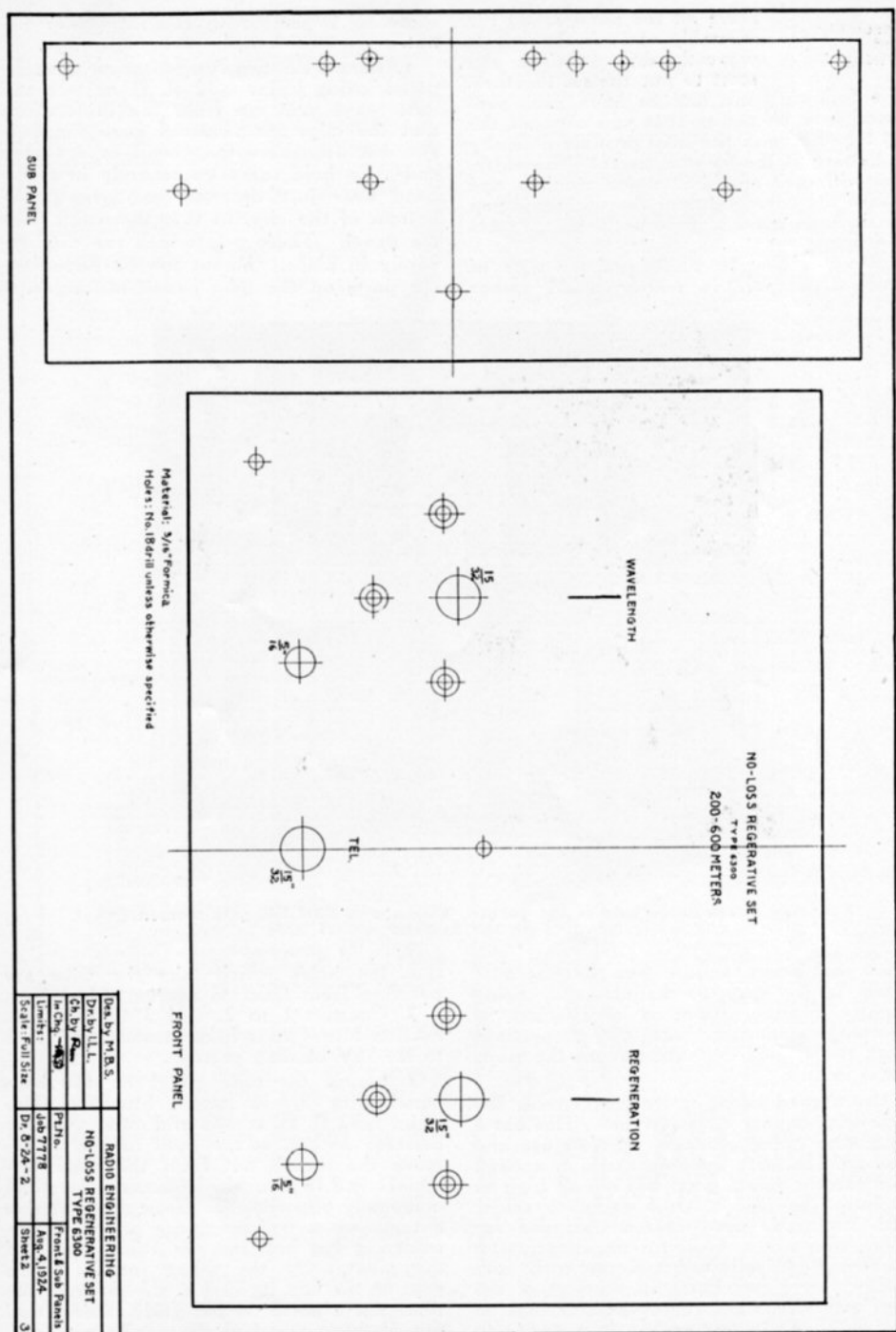


Fig. 4. One-half scale drawing of the front panel and sub panel. Concentric circles indicate counter sinking for flat head screws

Assembly and Wiring

Have all the parts ready for assembly and all the panels correctly drilled before you start to put the set together.

The following instructions have been prepared in such a way that you can put the set together with the least possible difficulty in getting at the various parts. Therefore, you will save much time and trouble, and assure the correctness of the wiring, if you go through these steps exactly as they are laid out.

Wirit, a No. 18 tinned copper wire of medium temper, is recommended rather

soldering is done with the lug under the nut.

1. Mount the two Amperites on the tube panel, using $\frac{1}{2}$ -in. 6-32 R. H. screws and nuts. You will see from the illustrations that the clips are removed from the base and cut off where they bend over at the end. To hold the clips securely in place, bend over just the very corners of the bottom of the clip, so that they stick into the panel. These points lock the clips securely in place. Mount the six Eby binding posts on the tube panel, making sure

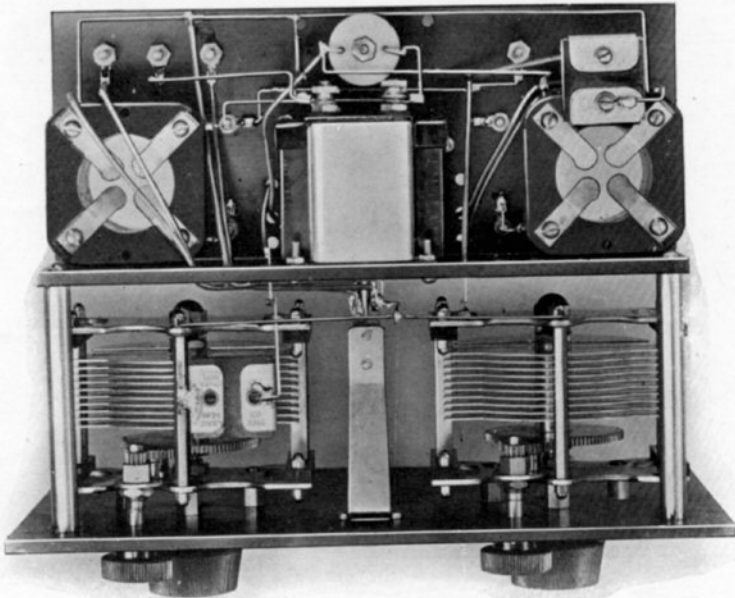


Fig. 5. The underside of the outfit. This shows how the grid condenser is mounted on the detector socket base

than the heavy square bus bar because Wirit is so easy to handle and, being slightly flexible, there is no danger of breaking soldering lugs or connections from the strains that are put on the parts while in use.

Use a good soldering iron, preferably the American Beauty electric type. This has a long slim point which is easy to use and maintains an even temperature high enough to make the joints good but not so high as to burn the iron. Altho ordinary solder with Nokorode paste is recommended for those who are not skillful at soldering, it is better electrically to use Kester rosin core solder. In either case, fill the lips of the lugs with solder before you put the lugs on the nuts. For some reason it is easier to make the solder take hold when this is done and less heat is required than when the

that the holes which take the wire are pointing from front to rear.

2. Connect 1 to 2, and 3 to 4. Connection 3 to 4 runs from connection 1 to 2 to the -6V binding post.

3. Mount the tube panel on the base panel with $\frac{3}{8}$ -in. angle brackets. Use $\frac{1}{2}$ -in. 6-32 R. H. screws and nuts. On the detector socket, at the right in Fig. 2, remove the thumb nut from the plate terminal and from the filament terminal diagonally opposite. In place of the thumb nut put on a coil mounting pillar, with a soldering lug between the round nut and the pillar. On the other socket, which goes on the left, looking at the set from the rear, put a pillar on the grid terminal and the filament terminal diagonally opposite. Mount the sockets under the base panel, putting $\frac{1}{2}$ -in. 6-32 R. H. screws through

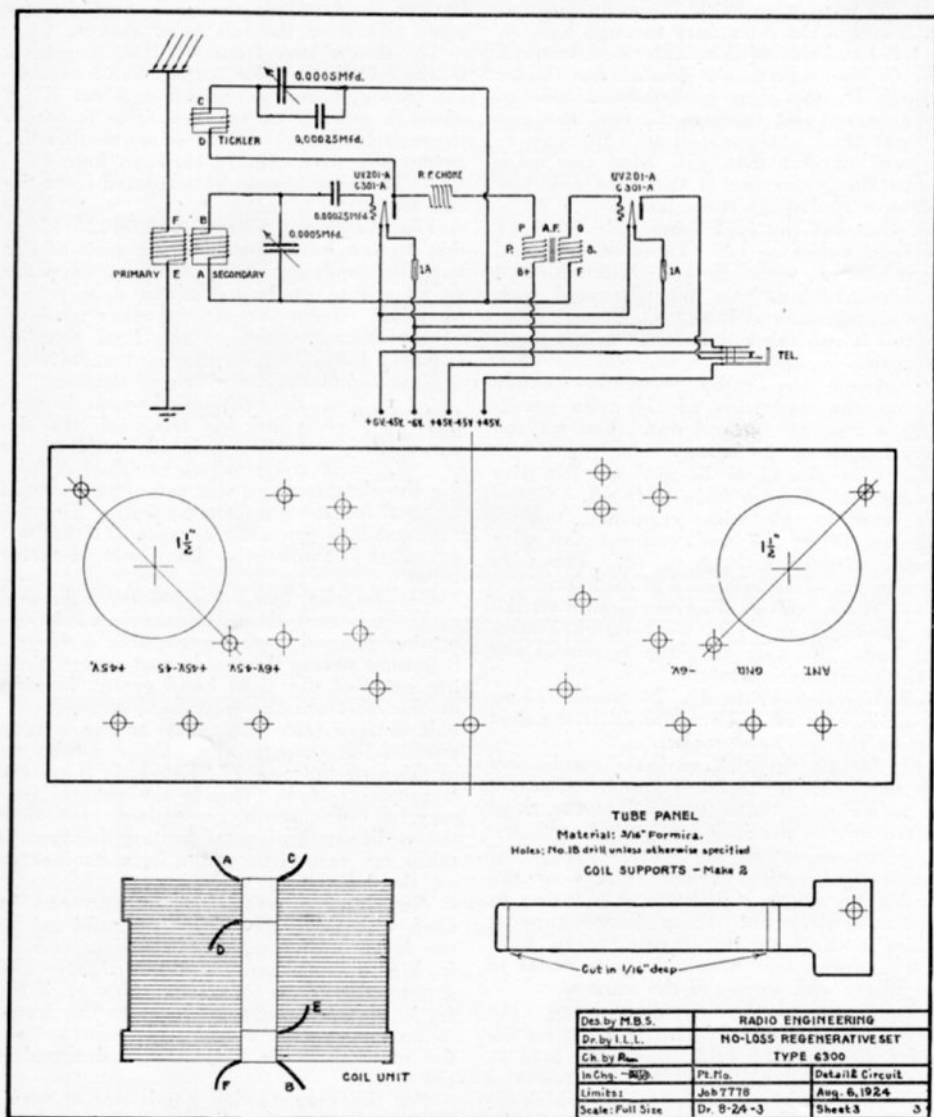


Fig. 6. One-half scale drawings of the tube panel, coil unit, and coil supports, as well as a schematic wiring diagram illustrating the circuit system

the panel and into the upper ends of the pillars.

4. Connect 5 to 6, and 7 to 8.

5. Mount the 0.00025 Micadon on the detector socket base, putting a 1-in. 6-32 R. H. screw through one terminal of the Micadon and the mounting hole in the socket.

6. Connect 9 to 10. 10 is the grid binding post on the socket.

7. Fasten angle brackets to the upright

strips which hold the tuning inductance, using 1/2-in. 6-32 R. H. screws and nuts. Then fasten the angle brackets to the tube panel with the same size screws, and put the coil in position between the uprights. Put the leads from the inductance unit through the holes in the tube panel, but do not put varnished tubing on the leads until later. You will see that the start of the secondary, on the right looking at the set

from the rear, goes to the hole indicated as B, the end of the secondary through hole A, the left-hand side of the tickler coil through hole C, the right-hand side of the tickler through D, the start or left-hand side of the antenna coil through E, and the end or right-hand antenna coil lead through F. Be very careful that you have the leads in just this order for, if they are not, you will have to change them later.

8. Connect the lead from hole E to 11 and from hole F to 12. These leads should be insulated with No. 7 Mitchell-Rand varnished tubing. No Wirit is used with these connections as the D. C. C. wire from the coil is run the full distance to the binding posts.

9. Mount the radio frequency choke coil on the underside of the tube panel, using a 2-in. screw and nut. Cut off the extra length of the screw.

10. Connect 13 to 14 and run the wire coming out through hole D to 15. Cover this lead to 15 with varnished tubing. Connect 16 to 17 and connect the wire coming through hole A to 18. The wire running to 18 is insulated with tubing.

11. Mount the A. F. transformer on the sub panel, using $\frac{1}{2}$ -in. 6-32 R. H. screws and nuts. Be sure that the terminals are in the positions indicated.

12. Connect 19 to 20, 21 to 22, 23 to 24, and 25 to 26. Terminal 22 is the grid post on the left hand socket.

13. Mount the two variable condensers and the jack on the front panel. Connect 27 to 28 and 29 to 30. 30 is the third contact up on the jack.

14. Be sure that the soldering lugs for connection to the variable plates of the condensers are in position and pointing as shown. Fasten the three panel support pillars to the front panel, using $\frac{1}{2}$ -in. 6-32 R. H. screws and fasten the sub panel to the pillars with screws of the same size.

15. Connect the wire coming out through hole B to 31. This is a lug on the under side of the grid condenser held in place by a $\frac{1}{2}$ -inch. 6-32 R. H. screw and nut. Make a break in the tubing which insulates this lead so that joint 32 can be made. Connect 32 to 33. 33 is the terminal for the fixed plates on the right hand condenser. This lead was insulated with tubing from 32 as far as the rear of the sub panel, altho that is not necessary. Connect 30 to 34, insulating the wire with tubing. Be careful not to melt off the lead 29 to 30. Connect 35 to 36. This lead should be insulated. Terminal 35 is the top contact on the jack. Connect 37 to 38. This lead should be insulated. Terminal 37 is the second contact up on the jack. Connect 39 to 40. This lead should be insulated. Terminal 39 is the

bottom contact on the jack and 40 the plate circuit of the left hand socket.

16. Run a wire from 41, the connection to the fixed plates on the left-hand condenser, through the sub panel and cut it off about a quarter of an inch after it passes through the panel. This is connection 42. Solder the wire coming through hole C 42. The wire should be insulated from the coil to 42.

17. Solder one side of a 0.00025 Micadon to the bottom supporting post of the variable condenser. Do this very carefully so as not to apply too much heat to Micadon. Then connect the other terminal of the Micadon, 43, to the lead running from 41 to 42 making the joint at 44.

This completes the wiring of the set.

Installation and Operation Because no rheostat is provided for adjusting the detector, it is advisable to use a UV201-A or C301-A tube for the detector and the same type should be used for the amplifier as well. This arrangement is generally accepted as the best except by those who have pet detector tubes.

Put on the 6-volt A battery first and make sure that the filament circuit is operating properly. Then connect a 45-volt B battery across the inside and center binding posts of the right hand group, looking at the set from the front, and another 45-volt battery from the center to the outside post of the same group. On a 2-tube set of this sort the new 772 Eveready B battery is recommended. This is the vertical battery, a much more convenient type than the ordinary horizontal battery because it takes up very little space in a cabinet or on the laboratory table.

Any kind of receiving antenna can be used with this outfit altho it should not be too large. One wire 100 ft. long and 20 ft. high at each end is about right. The ground should go to a water pipe or, if the set is used for portable work, to the frame of an automobile, a large spike driven into the roots of a tree, or to a cam dropped in the water.

Put the regeneration condenser at maximum and see if the circuit oscillates, as indicated by a double plucking sound when the grid terminal of the tube is touched. If your finger is dry, moisten it slightly. In case you are not able to make the set oscillate, reverse the leads from the tickler coil.

When signals have been brought in by adjusting the wavelength condenser, reduce the capacity of the regeneration condenser until oscillations cease. Then get a close adjustment of the wavelength and increase the capacity of the regeneration condenser until the signals are at maximum volume without distortion.

RADIO ENGINEERING

M. B. SLEEPER, Editor

F. A. SKELTON, Managing Editor

Published monthly by

M. B. SLEEPER, Inc.

Editorial and General Offices

A-52 Vanderbilt Ave., New York, N. Y.

Twenty cents per copy in the United States and Canada; in foreign countries one shilling. Two dollars per year, twelve numbers in the United States and Canada; ten shillings in foreign countries.

Copyright 1924 by M. B. Sleeper, Inc.

Vol. IV AUGUST, 1924 No. 7

EDITORIAL

WITH this issue the name RADIO and MODEL ENGINEERING which, during the last three years has become so well known to radio men, is changed to RADIO ENGINEERING. This change, important in itself, indicates another step in the steady advance which has been maintained in developing the usefulness of the Magazine. There is a real surprise in store for you—the September issue in which the plans on which we have been working all summer will be realized. I won't tell you about it now, but you'll see for yourself and, I think, you'll be very much pleased.

Last month, while the final work was being done on the type 6200 resistance coupled amplifier, we had an experience which answered one of the most frequent of radio questions in a most convincing way. The question, if you haven't guessed it, is, "What is wrong with my set? Everything is exactly right, but I can't get good reception." The easiest answer is that everything can't be exactly right or the set would work, but the average man can't be convinced when he has already made up his mind that the fault is not his.

However, a set made right works right—as was the case with our amplifier. The circuit was drawn correctly, the constants were worked out accurately, and the set was wired in accordance with the diagram. But it didn't work. Because of the limited time before publication, photographs were taken, for we knew that there was just

some little bug that would be found. Yet we couldn't locate it. The picture wiring diagram had to be drawn. Still, we hardly dared to make it up from a set that wasn't working. As a matter of fact, the signals were louder at the first step than at the fourth step—with everything exactly correct, just the kind of situation that is so frequently encountered in radio experimenting.

At last, because no time was left, it seemed as if we would not have to assume that the poor results were due to some peculiarity of this particular unit, and would not be encountered in another duplicate amplifier. Our job, tho, isn't to side-step troubles; we're here to straighten them out. It seemed like a hopeless situation, everything O. K. except the results, wiring tested thru, no opens, no shorts, no errors, and—no amplification. And then it occurred to us wonder about the first jack. We thought that adjacent terminals were connected together when the plug was removed, but, as we discovered on testing it, opposite terminals worked together.

When this change was made, or when the set really was wired correctly, the results were even better than we expected. All of which proves that it is only safe to say that a set is right only when it works. This explains also the difference between the wiring of the first jack as shown in the rear view of the set and in the picture wiring diagram, and illustrates the thoroughness with which articles are prepared for Radio Engineering.

A very practical comment is often made now-a-days concerning low-loss condensers. They don't seem to affect the tuning or the signal strength when they are substituted for the cheaply made types. As usual, there is a good reason. If there is a leak around the packing in a steam engine, it won't help much to clean the boiler tubes. The losses in a tuning circuit are not limited to the tuning condenser. Frequently, the losses in the inductance are many times greater. Consequently, if only ten per cent of the circuit losses are in the condenser, a perfect condenser will not help much.

The value of a low-loss condenser can be realized only when it is used with low-loss inductances, an inductance of the lowest possible high frequency resistance. For this purpose the pickle-bottle coil, first shown in the March 1924 issue of this publication, is not only the most efficient type of winding but the only type which shows up, in actual operation, the real worth of well-designed condensers.

M. B. SLEEPER, Editor.

Commercial Type Sets and Circuits

The Boonton Light Four

An unusually well designed portable receiver employing two steps of R. F. amplification with Ballantine Variotransformers. The weight of the complete outfit, with batteries, is only nineteen pounds.



THE design of a portable receiver is largely a question of good judgment on the part of the engineer in charge of the work, for a portable set may range from a pocket outfit to something that is carried on a truck. Some outfits sacrifice genuine usefulness for light weight, while others, however well they may perform, are of no value to the man who wants a radio outfit as an incidental part of the luggage that has to be taken on an automobile or camping trip.

In the matter of electrical design, the Boonton Light Four is planned to do just about anything that is required of a radio set, to bring in distant stations on the telephones and from transmitters within 50 to 500 miles on a loud speaker. In other words, it is a useful and interesting adjunct to the camping outfit. This is as it should be for people take radio sets so that they can enjoy the broadcast entertainment while they are camping rather than to go camping so that they can listen to radio in the woods.

Mechanically the outfit is equally good. As the illustrations show, the installation is divided into two parts which can be carried separately and then set up together. Of course, the entire outfit can be carried in one hand since, with the batteries and telephones, the total weight is less than 20 lbs., but it is easier to carry a section in each hand so as to make a balanced load.


Each section measures $4\frac{1}{2}$ ins. high, 8 ins. deep, and $12\frac{3}{4}$ ins. long. You will note that the front of the receiver cabinet turns upward. This gets it out of the way while the outfit is in operation. The battery case, however, has a cover hinged at the side, but this is never opened except for removing the phones or changing the batteries.

The receiving circuit, shown in the wiring diagram opposite, is of a type designed to give the best results with the Ballantine variotransformers, two of which are used to give two steps of radio frequency amplification, followed by a detector and one step of audio amplification. This makes a most efficient type of receiver for bringing in transmitters operating on 250 to 550 meters.

A special adjustment is provided on the primary of the fixed coupler, particularly to adapt the set for home use where, usually, sharper tuning is required than off in the woods at some distance from the nearest broadcasting station. The antenna and ground are connected to binding posts A and G. With the antenna lead connected to the binding post marked X on the coil, the full primary is in the circuit. This gives maximum signal strength with slightly broad tuning. When sharper tuning is necessary, the connection should be made to Y. Then only a part of the primary is in the antenna circuit.

Current and voltage are supplied to the UV199 tubes by means of three 6-in. Eveready dry cells type 7111. The two B batteries are of the small $22\frac{1}{2}$ -volt size, type 763. These batteries provide sufficient energy for operating the outfit over a considerable period of time, much longer than is usually spent on most camping trips. At the same time the weight is very small, making the power unit easy to carry.

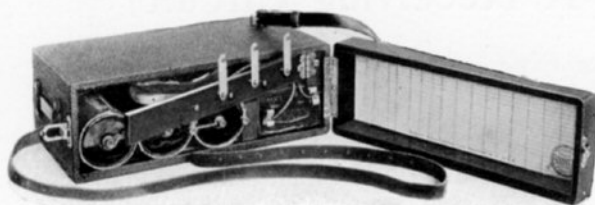For fairly long distance reception the antenna wire should be about 100 ft. long, of bare wire or annunciator wire. The latter is a little easier to handle since it is less liable to become tangled. The height at each end need not be more than 15 ft. above the ground. Any good receiving antenna can be employed for home operation. Out in the country the ground con-




Left: The battery case. It holds three 6-in. Eveready dry cells and two 22 1/2-volt B batteries. Phones are kept in the upper part of the A battery compartment. This is a complete power plant for the four UV199 tubes.

Right: A second case, of the same dimension as that for the batteries, houses the receiving equipment. Notice how the panel swings out to make the sockets accessible. The tube socket unit is mounted on shock absorbing springs to eliminate microphonic noises.



nection can be made to a metal plate or can be dropped into the water or the frame of an automobile can be employed. In that

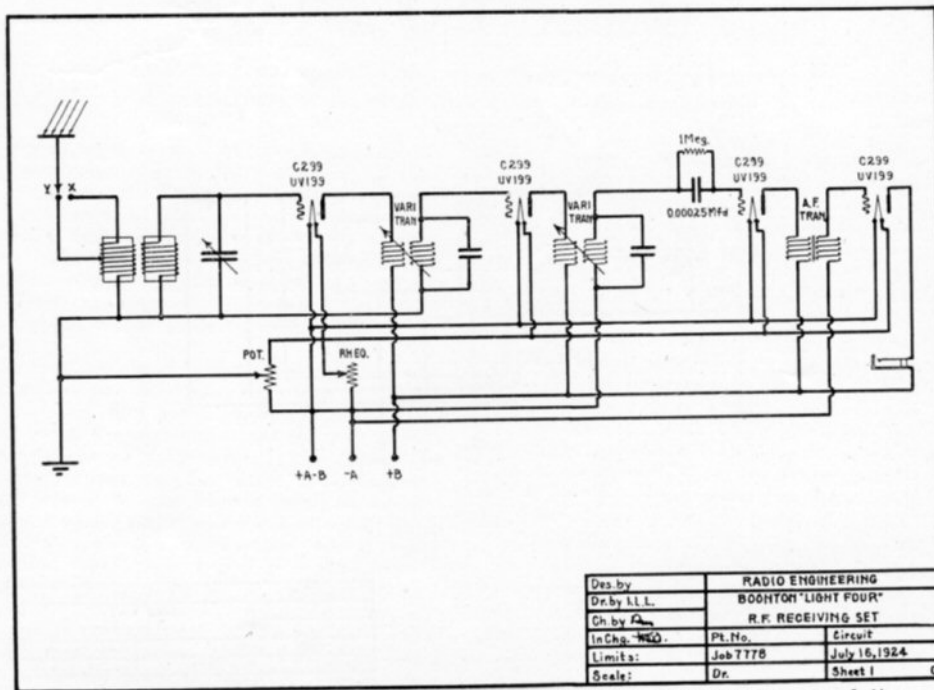case, it is well to stretch the antenna above the car, for then the latter acts as a counterpoise ground.



Des. by	RADIO ENGINEERING		
Dr. by	BOONTON "LIGHT FOUR"		
Ch. by	R.F. RECEIVING SET		
In Chg. WEO.	Pt. No.	Circuit	
Limits:	Job 7778	July 16, 1924	
Scale:	Dr.	Sheet 1 C	

Complete wiring diagram of the Boonton Light Four, showing the use of the variotransformers

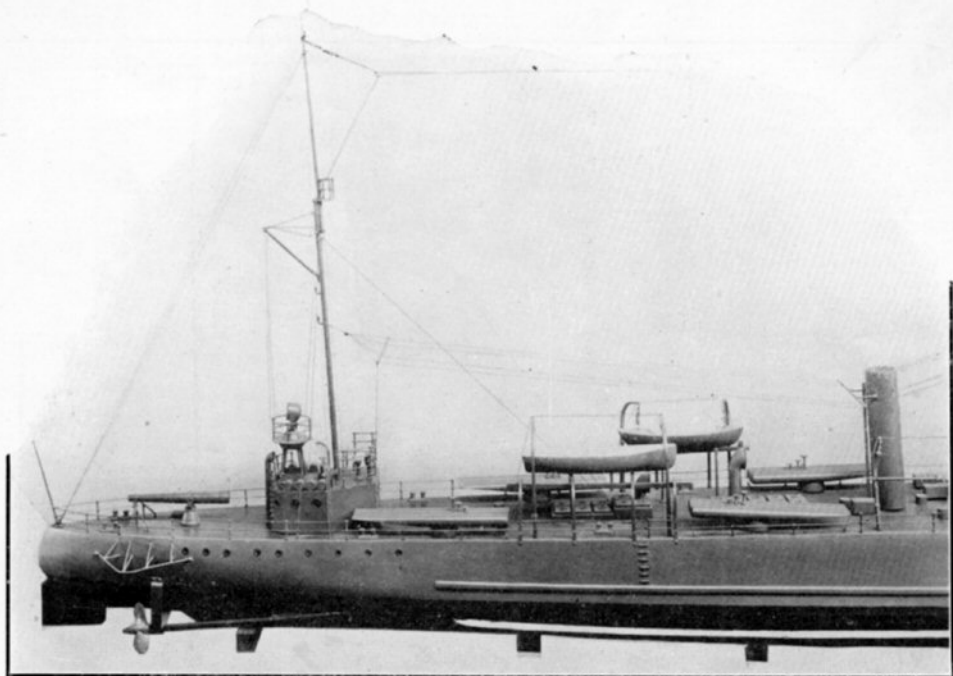


Fig. 12. This illustration is most helpful in interpreting the scale drawings

Construction of a One-Eighth-Inch Scale Model 310-Foot U.S. Destroyer

Part 6. Final installment, describing special features
of construction on the after part of the destroyer.

IF you have carried out the construction work on the model destroyer in the order in which the data has been given, the last part of the work is fitting and finishing the parts on the after half of the deck. To make this as clear as possible, the accompanying photographs are given to show the exact appearance of the original model as built by H. E. Boucher, Inc.

Comparing Fig. 11, the scale drawing of this part of the destroyer with Figs. 12 and 13, you will find some slight discrepancies although these are not important as they only affect details of arrangement, the essential features remaining the same. The deck house should be cut from a small block of pattern-makers' pine and finished up in accordance with the dimensions which can be scaled from Figs. 4 and 11. The overall height is 1 in. and the greatest width 1-7/8 ins. by 2 1/4 ins. long. The center line for the port holes is 3/4 in. up from the deck. The holes should be drilled out very carefully and fitted with eyelets or with regular scale port holes which can be

bought ready made. The staunchions should be purchased unless you have the facilities for handling the very fine work of turning them out. On the starboard side you will see the depth bombs. These are 3/16-in. in diameter by 1/4-in. long, just little pieces of wood which can be glued or fastened down with very fine wire brads.

For the search light mounting, four lengths of brass rod, 1/16-in. in diameter and 1-1/8 ins. long should be used. This allows an extra 3/8-in. so that the rods can be forced into the deck house and into the search light platform. The platform itself is 3/4-in. in diameter, turned from a small piece of wood. Dimensions for the search light have been given already.

The torpedo tubes are 3 1/4 ins. long over all by 1/4-in. in diameter. They are mounted on a wooden disc 1/2-in. in diameter and 7/32-in. thick.

The main mast stands 6 1/8 ins. above the deck house and is 3/32-in. in diameter. An additional length should be allowed for it to set into a hole drilled in the deck

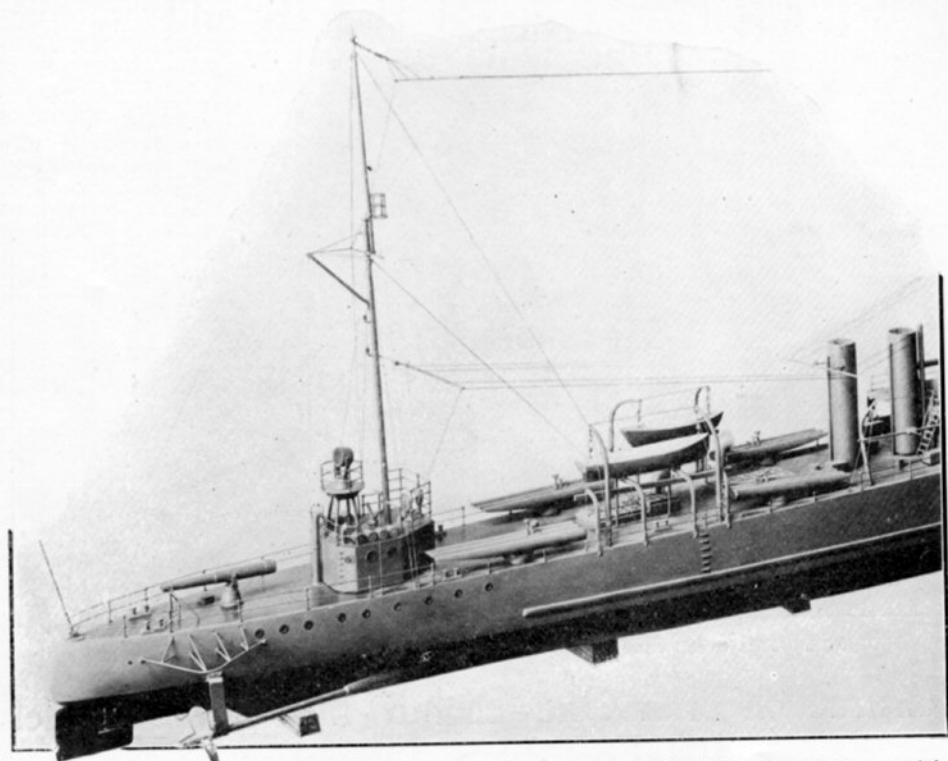


Fig. 13. So perfect is this scale reproduction that you could not recognize it as a model if it had been photographed in the water

house. Another rod 1/8-in. in diameter by $3\frac{3}{4}$ ins. long is required for the top mast. An overlap of $\frac{3}{4}$ -in. is taken care of in these dimensions for fastening the two masts together.

A brass tube 5/16-in. in diameter and $\frac{3}{4}$ -in. long, cut down at an angle at the top, will serve as a crow's nest. Because of the ease with which these parts can be soldered together, it is much better to use brass rod and sheet or tubing than to use wood, for even the slightest strains of the halyards will cause the wooden mast to warp out of shape.

The engine room hatches can be seen in Figs. 11 and 12, and dimensions for them are shown in Fig. 4. To save work, you can use plain, solid pieces of wood although a more realistic appearance will be produced if the solid pieces are grooved to correspond to the construction as shown. Another illustration of these hatches is given in Fig. 3.

Other details, such as the controls on the torpedo tubes, the signal lights, antenna insulators, and similar fittings can be put on or left off according to your skill and your desire to include all the special items.

What Kind of a Super Have You?

The new book, Super-heterodyne Hook-ups, is now being mailed out. This book gives the very latest circuit data on super-heterodyne sets as worked out by engineers from Acme Apparatus, Branston, Brooklyn Metal Stamping Co., Haynes-Griffin, Phenix, and Radio Receptor. In addition, there is much valuable data of interest to experimenters building super-heterodyne sets of

any type. There are 25 photos and 8 diagrams.

None of this material has appeared before and you will find many valuable ideas given which will help greatly in your work.

The price of Super-heterodyne Hook-ups is fifty cents post paid. If your dealer cannot supply you, send your order to M. B. Sleeper, Inc., A-52 Vanderbilt Avenue, New York City, N. Y.

And Now
for **ROUND** nuts-
Spintite

Now you can tighten all the nuts on your set—Spintites for round nuts are ready.

Go over your set with Spintites and make connections as solid as if soldered—then you will get greater distance and volume and cut out noises.

Set of 3 Spintites, for either round or hex nuts, \$1.00.


Set of 9 Spintites, for all hex nuts, \$3.50.

If not at your dealer's, send us your order with his name. Write for Booklet No. 23 of Special Radio Tools.

STEVENS & COMPANY

375 Broadway,

New York, N. Y.

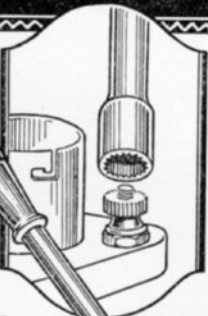

Resistance Coupled Amplification

The DAVEN Resisto-Coupler illustrated above greatly simplifies the construction of these distortionless amplifiers. They are included in the **DAVEN KITS**. Ask your dealer to explain.

Complete Kits	Kits Without Sockets and Condensers
3-stage \$13.50	3-stage \$8.50
4-stage \$17.00	4-stage \$11.00

Also read "The How and Why of Resistance Coupled Amplification." Price 10c

These booklets may be obtained from your dealer.
DAVEN RADIO CORP.
"Resistor Specialists"
11 Campbell Street
Newark, N. J.

THE PACE SETTER

1924—1925

NOLOSS

Registered U.S. Patent Office

A VARIABLE CONDENSER

manufactured by

GENERAL INSTRUMENT CORPORATION

423 Broome Street, New York City

AMPLEX
GRID-DENSER

ANY set can be improved by replacing fixed condensers with GRID-DENSERS. Distance just naturally follows GRID-DENSER.

GRID-DENSER, with its microscopic variations of capacity, makes for stability by controlling oscillation and regeneration perfectly.

The .0005 type or the .001 type (with or without the gridleak clips shown) at your dealer or direct from us for \$1.25. Write for booklet MR FREE.

AMPLEX INSTRUMENT LABS.
88 W. Broadway, New York



**Better than,
a Fixed
Condenser**



Easily Equipped for Accurate Tuning

Two minutes and a screw driver replaces ordinary dials with Accuratune Micrometer Tuning Controls.

Accuratune Micrometer Controls actually eliminate need for vernier condensers, built-in verniers and all vernier devices. Endorsed by Super-Heterodyne Engineers. Designed to give infinite tuning precision, operating ratio of 80-1. Mount flush with panel and fit all standard condenser shafts.

Accuratune Dials cost more than ordinary dials and are worth their price of \$3.50 in unsurpassed tuning efficiency. Try them, you'll pull in stations you never got before.

Write for descriptive circular.

MYDAR RADIO COMPANY

Pioneer Manufacturers of Quality Vernier Condensers
9-E Campbell St. Newark, N. J.

ACCURATUNE

80-1

MICROMETER CONTROLS

Radio, Ltd., Montreal, Canadian Representatives

Ready for Delivery

SUPER TRIODYNE

(IMPROVED SUPER-HETERODYNE)

*Eight tubes with five-tube
B battery consumption*

The SUPER-TRIODYNE is the first practical type of super-heterodyne, for it consumes no more B battery current than a five-tube neutrodyne. It does away with the necessity of buying B batteries every two or three weeks.

The SUPER-TRIODYNE uses no B battery on the three intermediate amplifiers, yet the volume and clarity are superior to any other Super set. UV-201-A tubes are recommended, altho others can be used. Parts required can be obtained from your local dealer—nothing difficult about the construction.

SET OF BLUEPRINTS AND PANEL PATTERNS, rolled in mailing tube, \$2.00

Technical Book Shop
52 Vanderbilt Ave., New York City

Reflex Experts Built These!

Write for the Rasla Reflex Construction Bulletins with full size layouts. They're FREE!

THE RASLA Fixed Detector and the RASLA CR Transformer are the result of thorough research work by reflex experts. Use these two essentials in your reflex for results.



RASLA Type CR Transformer is a radio frequency transformer designed especially to link a vacuum tube and a crystal detector. Therein lies the reason for its efficiency.



RASLA Fixed Detector is all that its name implies. It is a permanently fixed supersensitive crystal. RASLA Fixed Detectors are as uniform as peas in a pod! Everyone is a good one.

DAVIDSON RADIO CORP.
720 Atlantic Ave., Brooklyn, N. Y.


RASLA

TRANSFORMER ~ FIXED DETECTOR

The Improved

RASLA REFLEX

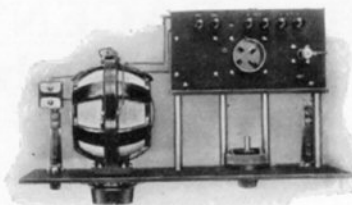If you want a good set, sharply tuned, sensitive to weak signals, using only one tube, build a RASLA



IMPROVED RASLA REFLEX

The DURRANT construction set for the Rasla includes all the standard parts listed in the May issue of R. and M. Rasla and Modern transformers, S. R. C. variometer, etc., with the Formica panels drilled, ready for assembly. This is an ideal outfit for portable use as it works best on a 50 to 75 ft. antenna.

Complete set of parts as described \$25.00

DURRANT can supply promptly all items listed in the Standard Parts Lists in R and M, at the prices shown. DURRANT is not a cut rate mail order house, but an established organization of men who can handle your orders quickly, courteously, and intelligently. DURRANT always ships exactly what is ordered, without substitution. Quality and workmanship are absolutely guaranteed. Parts will be shipped C. O. D. if one-fourth of the amount is sent with the order. 10 cents must be added for registration to insure safe delivery.

DURRANT RADIO, Ltd.

C-52 Vanderbilt Avenue,

New York City

POSTER'S PERFECT PANELS

THE RECOGNIZED STANDARD

ENGRAVING-MACHINING

FORMICA
RADIO PANELS

POSTER—that name on a radio panel is a guarantee of perfection. Always look for it and insist upon getting it!

POSTER Panels, engraved and drilled and polished, can be obtained for any of the circuits described in Radio & Model Engineering. For the panel for any set from super-heterodyne down, specify POSTER Panels.

POSTER & CO. INC.

26-28 BARCLAY ST., N.Y. TEL. CORT. 4965-6
(WHOLESALE ONLY)

Write for a copy
today



A new twenty-four page booklet will be sent, gratis, to those interested in building their own receiving sets.

A simplified method of construction is described. Illustrations and diagrams.

On Request

EISEMANN MAGNETO CORPN.

William N. Shaw, *President*

Dept. N

165 BROADWAY, NEW YORK

What PACENT leadership should mean to you

Pacent Radio Essentials

Adapters
Audioformers
Coil Plug
Coil Plug Receptacle
Condensers, variable
Detector Stand
Duojack
Duoplug
Duo Lateral Coils
Headsets, Everytone
Jacks
Jack Set
Loop Plug.
Loop Jack
Multijack
Plugs
Potentiometers
Rheostats
Resistances, Cartridge
Sockets
Super Audioformers
Twin Adapter, etc., etc.

TRADE MARK

See our exhibit at the FIRST
RADIO WORLD'S FAIR
Madison Square Garden, Sep-
tember 22-28th 1924.

WITH the fact that over thirty of the leading and most widely known radio set manufacturers equip their sets with Pacent Radio Essentials is proof conclusive of Pacent quality.

Only after meeting high Electrical and Mechanical Standards are Pacent Radio Essentials worthy of bearing the Pacent Trade Mark.

By following the judgment of these set manufacturers in your selection of radio parts you will minimize the possibility of disappointment in results in your home-made set.

Insist on Pacent Radio Essentials. Your favorite dealer carries them or can get them for you. Write for Complete Pacent Catalog No. P-8.

PACENT ELECTRIC COMPANY, INC.
22 Park Place New York, N. Y.

Pacent

RADIO ESSENTIALS

AMPERITE

The "SELF-ADJUSTING" Rheostat

For Every Amplifying Circuit—
Radio and Audio Frequency.

Perfect for resistance coupled
amplification.

- Eliminates hand Rheo-
stats.
- Simplifies wiring.
- Prolongs life of tubes.



\$1.10

From
your dealer

Write Dept. M-3 for Free Hook-Ups

—MANUFACTURERS—

RADIALL COMPANY

320 W. 42nd Street, New York

Kellogg Radio Kit



Everything complete for assembling two
stages of audio frequency amplification.
The panel is drilled for three tuning
units, which together with this No. 501
Kit will complete a radio set using your
favorite hook-up, or most any other that
you may desire to try.

"Build your own" with this Kel-
logg 501 Radio Kit.



AT YOUR DEALERS FOR \$43.00

Use — Is The Test

**KELLOGG SWITCHBOARD
& SUPPLY COMPANY**

1065 W. Adams St. Chicago, Ill.

New!

Scientifically correct
and guaranteed!



—its calibrated

Resistances can be read in terms
of the megohm through panel
peep-hole. (Also equipped for
table mounting.) Set
it for specified resist-
ance—adjust it for
best results. Accu-
racy assured. Each
Fil-ko-leak hand calibrated (1/4
to 5 meg.—the oper-
ating range for all
tubes) and doubly
checked.



2.00

Terminal posts
space to fit
the standard grid
condensers.

You cannot get
all that your set
can give unless
your grid leak res-
istance is pre-
cisely correct.

FIL-KO-LEAK
SCIENTIFICALLY CORRECT
VARIABLE GRID LEAK

—with battery switch



2.00

And at no extra cost! Fil-ko-
stat gives perfect control of any
type tube in any hook-up—
maximum signal strength—longer
tube life and battery life. Stops
tube noise. Brings in DX sta-
tions you never heard before.
Switch attaches to regular "Stat"
mounting screws.

FIL-KO-STAT
SCIENTIFICALLY CORRECT
RADIO RHEOSTAT

—with \$100 guarantee



1.50

Protects your set from light-
ning or we pay you \$100 or
repair the set. That's our
guarantee. "Umbrella"
shield keeps dust, moisture,
etc., from the hermetically
sealed Bakelite insulation.
Maximum reception assured,
because all radio impulses
reaching antenna reach your
set. No leakage losses.

FIL-KO-LIGHTNING
SCIENTIFICALLY CORRECT
RADIO LIGHTNING ARRESTER




If dealer has
none send his
name and your
remittance to
Dept. RES24

MADE AND GUARANTEED BY
DX INSTRUMENT CO.

HARRISBURG, PA.

New York Office, 220 W. 34th Street
FOREIGN REPRESENTATIVES
Radio Stores Corp., New York

"The Knobs Can't Come Off"

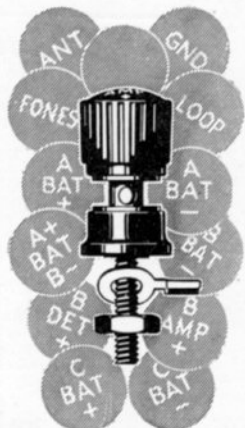

New
Improved
Model

13
Styles
Engraved

"Read'em"

(Copyrighted)

Manufacturers of radio sets are invited to write for a sample of this new model of the "Read'em" Binding Post, considered to be the finest post made, both in quality and appearance. Retail at 15c.

THE MARSHALL-GERKEN CO.,

Dept. 184

Toledo, Ohio



The Aristocrat of Amplifiers

Quality in Radio is No Less Marked Than Quality in People. The Resistance Coupled Amplifier is a quality product.

DAVEN Type 3-C AMPLIFIER KIT as illustrated contains all the necessary parts to build a three stage Resistance Coupled Amplifier that cannot distort.

Price Complete\$13.50

Read "RESISTORS, THEIR PRACTICAL APPLICATION IN RADIO RECEPTION," by Zeki Boucek.

Price 15c

Also read, "THE HOW AND WHY OF RESISTANCE COUPLED AMPLIFICATION"

Price 10c

These booklets may be obtained from your dealer.

DAVEN RADIO CORP.

"Resistor Specialists"

11 Campbell Street, Newark, N. J.

BLUEPRINTS

During the past three years, Radio Engineering has developed a system of making panel patterns and picture wiring diagrams which, as success insurance to the radio set builder, are superior to all others. Below is a selection of blueprints giving the designs of the finest sets which have been shown in Radio Engineering. Each is one hundred per cent good in its class.

1. DX receiver, a four-tube non-oscillating tuned R. F. set which has an unlimited range, coupled with sharp tuning, making it an ideal outfit for the man who wants the best for loud speaker reception. Set of six blueprints, type 5300.....\$1.50
2. Portable tuned R. F. set, using four UV199 tubes. This is similar to the type 5300, but smaller and less expensive. It also operates a loud speaker, with perfect quality, up to several hundred miles. Set of three blueprints, 5800.....\$.75
3. Circuits come and go, but the famous X-1900 three-circuit regenerative set is as popular as ever. Equipped with one tube, this is a splendid outfit for those who play radio golf and want a record score. Set of three prints, type X-1900.....\$.75
4. T. C. Circuit set—Twenty-five cities for twenty-five dollars—it is a one tube UV199 outfit that runs rings around any other outfit at the same cost. With an amplifier it brings in everything that's on the air. Set of three blueprints, type X-4000.....\$.75
5. Rasla Reflex is the choice for one-tube reflex sets, for it is sharp, has only one tuning control, and works with a UV201-A, making a storage battery unnecessary. The crystal is of the fixed Rasla type. Set of three blueprints, type 5900.....\$.75
6. Two-step amplifier, a unit which can be added to any receiving set. Takes any type of vacuum tubes. Jacks permit plugging in at each step. This is the most popular and practical amplifier to use. Set of three prints, type 3100.....\$.75
7. Resistance coupled amplifier, the perfect, distortionless amplifier for any receiving set. Uses one step of transformer coupling followed by three steps of resistance coupling. Set of three blue prints, type 6200\$.75
8. Regenerative set with one step of A. F. amplification. This is the easiest of all sets to handle, for there are only two controls. It uses the new tickler-condenser regulation. Set of three blue prints, type 6300.....\$.75

Complete assembly instructions, fully illustrated, with parts list for any of these sets..... 20c extra

M. B. SLEEPER, Inc.
B-52 VANDERBILT AVE.
NEW YORK CITY

TRI-JACK



90c

Two B.M.S. Winners

TRI-JACK is a revelation in radio jacks. Dustproof, solderless, super-compact, and of practically zero capacity, TRI-JACK is the biggest improvement so far made in jacks. TRI-JACK will improve any set.

TRI-COIL Radio Frequency Transformers are wonderful performers when it comes to distance and volume in the one tube reflex circuit. Write for the TRI-COIL Construction booklet FREE.

BROOKLYN METAL STAMPING Corp.
718 Atlantic Ave., Brooklyn N.Y.

TRI-COIL

\$2



LARK

An accurate reproduction of the Cape Cod boats, 18 ins. overall, 6 in. beam, 200 sq. in. sail area.

Price complete.....\$10.00



LARK

CURLEW

Racing sloop, 30 ins. overall, 7½ in. beam, 590 sq. ins. sail area. The most popular model among model racing enthusiasts.

Price complete.....\$25.00



CURLEW

Boucher Boats

Are perfect reproductions of the larger craft, not only in appearance but in sailing qualities. In no sense ordinary "toy boats," they are real sport to sail because they can be handled just like the big ones.

The Boucher line includes both sail and power boats, sold complete or as construction sets. They are described in catalog 507, a copy of which will be sent without charge upon request.

BOUCHER, INC.,

Retail Store and Show Room,
415 Madison Ave., New York

Standardized Parts List

The materials used to make up the set described in this issue were supplied by the following companies. The manufacturers whose names appear below will be glad to send you bulletins describing other products which they make. Please mention RADIO ENGINEERING when you write them.

PARTS FOR THE TYPE 6300 NO-LOSS RECEIVER

Type	Name	Price
	Carter Radio Co., G-209 So. State St., Chicago, Ill.	
103	1—3-spring filament control jack	\$0.90
	Cornish Wire Co., R-30 Church St., New York City, N. Y.	
1	1/4-lb. spool No. 20 D. C. C. Wire40
	Dubilier Condenser & Radio Corp., A-48 West 4th St., New York City, N. Y.	
601	2—0.0005 mfd. Micadons70
	H. H. Eby Mfg. Co., X-40 So. 7th St., Philadelphia, Pa.	
Ensign	6—Ensign binding posts	1.20
	General Instrument Co., 423 Broome St., New York City, N. Y.	
47D	1—.0005 mfd. Low-loss condenser with gear vernier...	8.00
	James Goldmark Co., B-83 Warren St., New York City, N. Y.	
W	1—100 ft. spool of Wirit92
	Kurz-Kasch Co., South Broadway, Dayton, Ohio	
A213	2—3-in. knobs and dials	1.50
	Marshall-Gerken Co., Toledo, Ohio	
MG	2—201-A sockets	1.50
	Poster & Co., 26 Barclay St., New York City, N. Y.	
153	1—7 by 10 by 3/16 in. Formica panel	1.81
98	1-3 1/2 by 2 1/2 by 3/16 in. Formica panel	2.75
	Radiall Co., 320 West 42nd St., New York City, N. Y.	
1A	2—Amperites for 201-A tubes.	2.20

Miscellaneous Parts		
58	2 Pkgs. of 25 tinned soldering lugs40
22	2—right-hand nicked angle brackets20
185	2—left-hand nicked angle brackets20
14	4 coil support pillars32
151	3—nicked panel supports90
63	2 Pkgs. of 10 1/2-in. 6-32 R. H. nicked screws12
49	1 Pkg. of 10 6-32 nicked nuts08
178	1 Pkg. of 10 1 1/2-in. 6-32 R. H. nicked screws18

COMPLETE SET OF PARTS.. \$24.29

BLUE PRINTS		
6300	Set of three full-size blue prints for the 6300 receiver.	\$ 7.50
AUXILIARY PARTS		
Chas. Freshman Co., Inc. 106 Seventh Ave., New York City, N. Y.		
DA	Double adjustable crystal detector	1.50
National Carbon Co. Long Island City, N. Y.		
763	Small 22 1/2-volt B battery	1.50
766	Large 22 1/2-volt variable B battery	2.00
772	Large 45-volt vertical B battery	3.75
771	4 1/2-volt variable battery60
6810	50-amp. storage battery 6-volts	15.00
Stanley Patterson West and Hubert Sts., New York City		
843	Deveau Gold Seal Phones, 2200 ohms	6.00
	Deveau Gold Seal Phones, 3200 ohms	8.00
Dictograph Products Corp. A-220 West 42nd St., New York City		
R6	Dictogrand loud speaker	15.00
Clark & Tilson, Inc. 1-A East 42nd St., New York City		
W	Automatic drilling template..	1.00
Pacent Electric Co. A-22 Park Pl., New York City		
40	Universal phone plug50
51	Twinadapter for two plugs...	1.00
Stevens & Co. 395 Broadway, New York City		
T-71	Set of 3 Spintite wrenches for hexnuts	1.00
T-825	Set of 3 Spintite wrenches for round nuts	1.00
T-580	Reamer for 1/8 to 1/2 in. holes..	1.50

Back Issues of R & M

If you have missed any issues of RADIO and MODEL ENGINEERING for this year, check over the following list and order those that you did not get so as to make your file complete. Until September 1st a special price of 10c. a copy will be allowed for these back numbers.

January—Tuska Superdyne, 4-tube Monotrol, oscillating wavemeter.

February—7-tube super-heterodyne set, Cockaday Receiver.

March-April—Portable tuned R. F. set

using UV199 tubes, Harkness circuit for Diode or crystal detector.


May—Improved Rasla reflex, the most successful I-tube receiver ever built, 100-meter Sodian receiver.

June—Sodian reflex set using UV201—A amplifier, the Bestone V-60, tuning filter for cutting out interference.

July—Resistance coupled amplifier, Tools for the radio model shop, Crystals that oscillate.

These copies will be sent promptly upon receipt of your order accompanied by a money order or postage stamps.

CARTER JACK SWITCHES

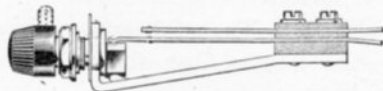

MADE IN FOUR DIFFERENT SPRING COMBINATIONS

Quarter turn snap switch with "On and Off" name-plate. Used to control "A" battery circuit. Adopted by exacting manufacturers who demand only the best in their sets.

Insist on the Original

Write for
Complete
Catalogue

Carter Radio Co.
209 S. STATE STREET
CHICAGO

Any Dealer
Can
Supply



A Manufacturers' International Exposition
Under the Direction of James F. Kerr
A MAMMOTH SPECTACLE OF SCIENTIFIC ACHIEVEMENT

The FIRST
RADIO WORLD'S FAIR
Madison Square Garden
SEPT. 22 to 28 Monday to Sunday Night
INCLUSIVE
1 P.M. UNTIL 11 P.M.

Extraordinary Features Daily!

A Manufacturers Exposition which will be attended by the Principal Radio Jobbers and Dealers of the Universe

De Luxe Exhibits by Nationally Known American Manufacturers

Representative Displays by the Famous Manufacturers of ENGLAND, FRANCE, BELGIUM, ITALY, SWITZERLAND & AUSTRIA

Business Office
HOTEL PRINCE GEORGE, N. Y. C.


Direction of
U. J. HERRMANN and JAMES F. KERR

Amplify the MODERN way!

NOT until you listen to an amplifier built around MODERN Transformers can you experience that joy that radio brings when it is properly reproduced.

Insist upon MODERN Transformers. They are made in three types—the Ten to One, the Push-Pull, and the Four to One.

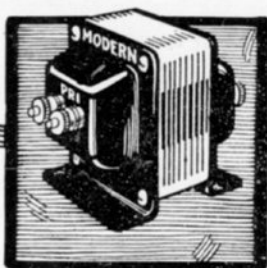*Send for the Book of MODERN Hook-ups.
We will gladly mail it to you FREE!*



B.L. SALES CO.
35 Warren St.
New York

A MESSAGE TO OUR FRIENDS!

We have created a demand for scientifically designed and beautifully finished binding posts by consistently advertising the advantages of quality posts with engraved tops which don't come off.

By carefully studying production methods we are in a position to manufacture a superior product to meet this demand and sell it at a close margin.

EBY Service is Swift and Reliable

These two posts are standard equipment on the sets of most of America's leading manufacturers. They can't be duplicated.




EN SIGN
Plain



EN SIGN
Engraved

Insist on Genuine EBY Posts

H. H. EBY MFG. CO. : PHILADELPHIA, PA.

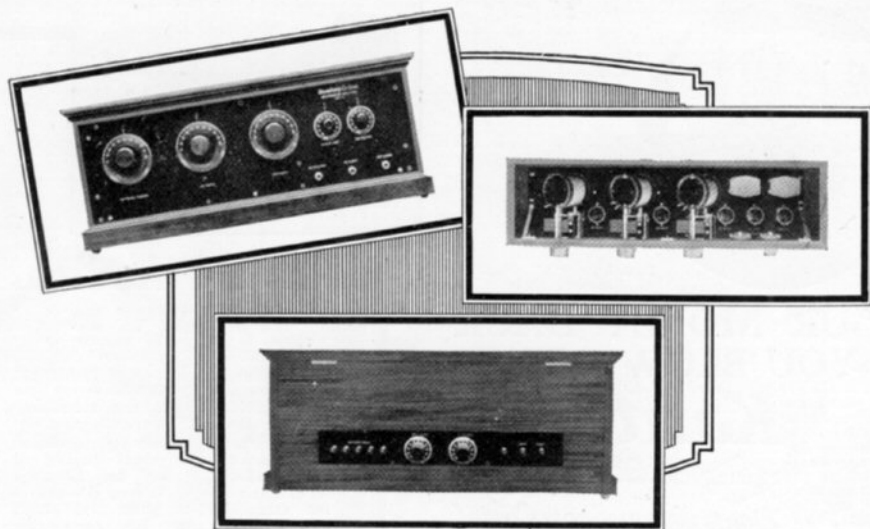

The photographs show the Formica front panel, Formica base panel and Formica back panel used in the Stromberg-Carlson Neutrodyne set

For more distance and more volume, Use more Formica!

DESIGNERS and builders of sets incorporating radio frequency amplification—neutrodyne, super-heterodyne, and reflex—have found that the best possible parts will give far less than maximum results unless the greatest care is taken to prevent current leakages.

They are using Formica front panels, Formica baseboards for mounting the instruments, and in some cases Formica back panels for the battery terminals. The remarkable new Stromberg-Carlson Neutrodyne set is an example of what can be accomplished in this way.

There is often a difference that means loud speaker volume on stations that would otherwise come in only on the phones; it means logging new DX stations that would have been impossible before.

Insist on Formica. It won't warp. Binding posts won't loosen up because the material cold flows. The insulating quality is certain and uniform—and the finish the best there is.

Dealers who wish to give real service to their customers are urging the use of Formica base panels in these sets.

THE FORMICA INSULATION COMPANY

4653 Spring Grove Avenue, Cincinnati, Ohio

SALES OFFICES


50 Church St., New York, N. Y.
422 First Ave., Pittsburgh, Pa.
1142 Granite Bldg., Rochester, N. Y.
419 Ohio Bldg., Toledo, Ohio

1210 Arch St., Philadelphia, Pa.
1026 Second Ave., S. Minneapolis, Minn.
585 Mission St., San Francisco, Calif.
Whitney Central Bldg., New Orleans, La.

516 Caxton Bldg., Cleveland, Ohio
9 S. Clinton St., Chicago, Ill.
708 Title Bldg., Baltimore, Md.
47 King St., Toronto, Ontario

FORMICA

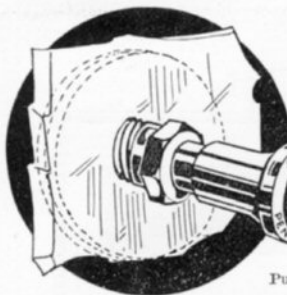
Made from Anhydrous Bakelite Resins
SHEETS TUBES RODS



"The Kant-Blo Switch on our Super-Heterodyne does all that you claim for it. If we had installed this signal long ago it would have paid for itself hundreds of times."

(Copy of letter on request.)

Push-Pull "A" Battery Switch Style

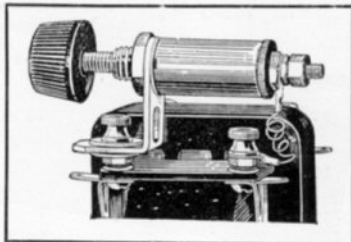

YOUR MONEY BACK IF YOU BLOW A TUBE

When your radio set is equipped with a Kant-Blo

Kant-Blo

Only one Kant-Blo needed to protect any number of any kind of radio tubes,

SWITCH SIGNAL BINDING POST
Lights on any Short Circuit

The Kant-Blo Signal is easily installed. Simply takes the place of either the ordinary push-pull "A" Battery Switch or one "B" Battery Binding Post now on set.

Kant-Blo Signals—both Binding Post Style and Switch Style—are at all the best radio stores. If your dealer is out of stock send us \$2 for a Kant-Blo Binding Post Style, or \$3 for the Switch Style, and we will ship any number of KANT-BLOS direct to you, charges prepaid.

Sole Distributors

APEX RADIO COMPANY

Suite 208 503 Fifth Ave. New York, N. Y.

Manufactured by Ganto Kramer Co., Inc., New York

Electrad Audiohm

C. P. HILDEBRAND said:—
 "This is certainly the Missing Link in Radio—To Express it Mildly, it is Marvelous."

Mr. Hildebrand is one of thousands who have placed this wonderful new radio device across the secondary of their first audio transformer.

If you want to eliminate distortion and improve the tonal quality of your radio set buy an Electrad Audiohm today. Place it across the secondary of your first audio transformer and be convinced. Price, \$1.50. If your dealer cannot supply you order direct, advising us of the name of your local dealer.


ELECTRAD Inc.

Dept. 3F

428 BROADWAY, N. Y.



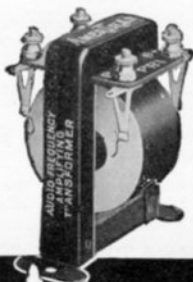Improve your set with an AmerTran and enjoy radio this summer as never before



STANDARD of EXCELLENCE for audio amplification

AMERTRAN

TRADE MARK REG. U.S. PAT. OFF.

The AmerTran is now made in two types: AmerTran AF-6 (turn ratio 5), is for use in the first stage; AmerTran AF-7 (turn ratio 3½) is the

companion transformer for use in further stages of amplification. Ask your Electrical Dealer; or sent carriage charges collect. Price, each type, \$7.

American Transformer Co., 173 Emmet St., Newark, N. J.

Designers and builders of radio transformers for over 23 years



No matter what the circuit

Acme Transformers make it better

NO MATTER what the circuit, its efficiency depends on the apparatus used. Low losses and amplification go hand in hand.

Acme low loss condenser. It remained for the Acme Apparatus Company to make the lowest loss condenser, with a mechanical structure which has no equal. Silver plated, logarithmic, brass plates, cast metal heads, smooth noiseless vernier, brass to steel cone bearings, pigtailed bearing connection, enclosed to keep the dust out.


Acme 30 KC transformer. As transformer and amplifying specialists we produced the Acme 30 KC

transformer for efficient long wave amplification. No interstage howling, and no shielding necessary.

Acme A-2 audio frequency transformer. Known to everyone and used by the majority, for Amplification without Distortion.

Acme pot rheo. The Acme pot rheo combines in a small space a well made 300 ohm potentiometer and either 6 or 30 ohm rheostat. With this instrument gaseous detector tubes can be operated at their most efficient point.

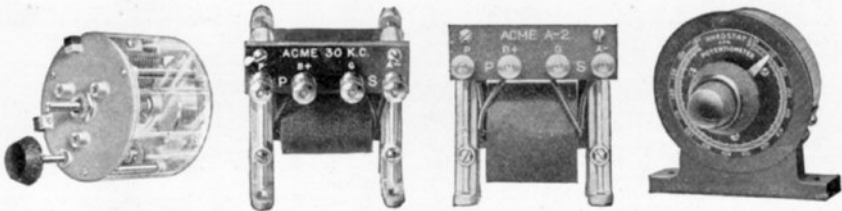Acme guarantee. All Acme Apparatus bears a guarantee tag and those who have used it will testify to its sincerity.



ACME for amplification

ACME APPARATUS COMPANY

Dept. R. M. 8 : : : Cambridge, Mass.

Transformer and Radio Engineers and Manufacturers

"The Best That Money Can Buy"



"Gold Seal" Head Sets

2200 Ohms

\$8.00

3200 Ohms

\$10.50

"DEVEAU GOLD SEAL" HEAD SETS are electrically and mechanically,—as well as from a radio standpoint,—as perfect as the highest-priced Head Set on the market,—yet, with all their perfection, they retail at only \$8.00 for 2200 Ohm and \$10.50 for 3200 Ohm.

The trade mark "DEVEAU" has stood for the highest quality in telephone apparatus for thirty years,—a guarantee that every known advantage in design and manufacturing has been taken into careful consideration.

Magnets are extra-heavy one-piece units; cups are of aluminum to keep down the weight but unlike other Head Sets, every exposed metal part of the set is finished in genuine 24-karat gold,—under a protective lacquer so that the finish will last for years; the terminals of each unit are concealed,—no contact possible with users' hands.

"DEVEAU GOLD SEAL" HEAD SETS are like a piece of fine jewelry in appearance, but with all the radio niceties that the most advanced radio enthusiast can desire. DEVEAU Units exactly match each other in tone,—each has maximum sensitivity and perfection of tone quality.

The patented design of headgear is far ahead of any Head Set on the market,—affording as it does, instant fitting to ears and head without "re-harnessing" and without binding or pressure,—the latter an admitted nuisance with all other makes of Head Sets.

Cups are of genuine Bakelite,—of scientific design, and comfortable to the ear; the bakelite never loses its jet-black lustre or highly polished surface.

"DEVEAU GOLD SEAL" HEAD SETS are never found in the cut-rate market,—they are only sold to Jobbers who appreciate their value.

"DEVEAU GOLD SEAL" HEAD SETS are guaranteed to be electrically and mechanically perfect,—our Guarantee protects every purchaser.

Order through your regular Jobber or write direct for the names of authorized Distributors throughout the country.

Send for descriptive Bulletin of Deveau Radio Apparatus and Micrometer Adjustable Air-Gap Radio Loud-Speakers.

STANLEY & PATTERSON

250 WEST STREET

Downtown Stores { 27 WARREN ST.
23 MURRAY ST.

NEW YORK, U. S. A.