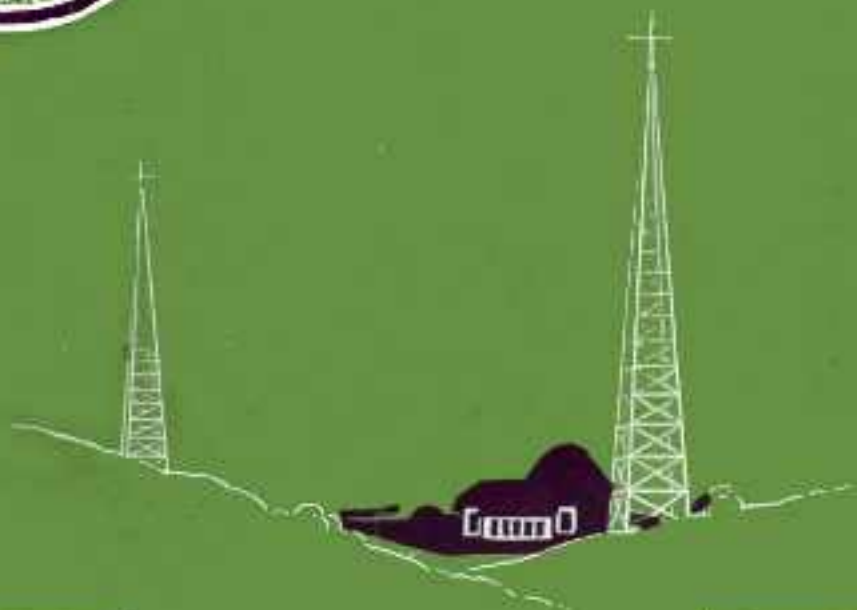


RADIO Engineering

A Magazine of Technical Accuracy for the
Radio Set Builder, Engineer and Manufacturer



Edited by
M.B.SLEEPER



AUGUST 1925

VOL. V NO. 8

**EVEREADY HOUR
EVERY TUESDAY
AT 8 P. M.**

Dates Observed Free

For real radio enjoyment, tune in the "Eveready Group."

Broadcast Through

WEAF	New York
WJAB	Providence
WEEI	Boston
WFI	Philadelphia
WGB	Buffalo
WCAX	Philadelphia
WEAR	Cleveland
WSAI	Cincinnati
WWJ	Detroit
WOOB	Indianapolis
WOC	Des Moines

*Eveready
Columbia
Ignitor
"A" Battery
You
cannot
dry cell
for all
radio
dry cell
needs
135
volts*



PREFERRED

It is no accident that more Eveready Radio Batteries are purchased by the radio public than any other radio batteries.

Such complete and voluntary endorsement can lead to but one conclusion—for best reception and longest life, Eveready Radio Batteries lead the field.

You can prove this for yourself by hooking Eveready Radio Batteries to your set. You will find that they deliver a steady, vigorous stream of power that lasts longer. It is Eveready economy that has created such an overwhelming preference for Evereadys. There is an Eveready dealer nearby.

Manufactured and guaranteed by

NATIONAL CARBON COMPANY, Inc.
New York San Francisco

Canadian National Carbon Co., Limited
Toronto, Ontario

EVEREADY Radio Batteries

-they last longer



*No. 772
45-volt
Large
Vertical
Price
\$5.75*



*No. 767
45-volt
Large
Horizontal
Price
\$5.75
If 66
variable
size*



The familiar names
WD-11, WD-12,
UV-199, UV-200
and UV-201-A
rightfully belong
to Radiotrons
only. To be sure of
quality, it is im-
portant to look care-
fully at the base of
every tube you buy
to see that it carries
the name Radio-
tron and the RCA
mark as proof that
it is a genuine
Radiotron.

It isn't a
genuine
UV-199
unless
it's a
Radiotron



Radio Corporation of America

Chicago

New York

San Francisco



Radiotron

AN RCA PRODUCT

RADIO ENGINEERING

Edited by M. B. SLEEPER

Associate Editor, Alfred A. Ghirardi

Fifth Year

Vol. V, No. 8

Contents — August, 1925

	Page
Building the Samson T. C. Receiver	383
Selenium and Photo Electric Cells	390
Editorial	393
Tuning an R. F. Set by Inductance	394
How to Connect Jacks for All Circuits	396
Some Angles on A. F. Circuits	399
With the Manufacturers	402
Directory of Manufacturers of Materials	412

Radio Engineering, August, 1925, Vol. 5, No. 8. Published monthly by M. B. Sleeper, Inc., Publication office, Lyon Block, Albany, New York. Editorial and General office, 52 Vanderbilt Ave., New York, N. Y. Printed in U. S. A. Yearly subscription \$7.00 in U. S. and Canada; ten shillings in foreign countries. Entered as second class matter at the postoffice at Albany, New York, January 9, 1925, under the act of March 3, 1879.

ULTRA-LOWLOSS CONDENSER



CAP. 0005 mfd.

\$5.00



Quick, positive tuning

SPEED—ability to turn directly to any station, to tune-in instantly and get your station without interference from broadcasting on similar wavelengths—is the outstanding feature of the Ultra-Lowloss Condenser.

With one station of known wavelength located on the dial, all others can be found instantly. Special design of Cutlass stator plates distributes stations evenly over the dial—each degree on a 100 degree dial represents approximately $3\frac{1}{2}$ meters difference in wavelength.

In addition, losses common in other condensers are reduced in the Ultra-Lowloss to a minimum by use of only one small strip of insulation, by the small amount of high resistance metal in the field and frame, and by a special monoblock mounting of fixed and movable plates. Designed by R. E. Lacault E. E., originator of the famous Ultralyne receiver and Ultra-Verdier tuning controls.

At your dealer's; otherwise send purchase price and you will be supplied postpaid.

ULTRA-LOWLOSS CONDENSER



Cutlass Stator Plate includes is an Ultra-Lowloss feature

A guarantee of resistance and Lacault design



ULTRA-VERDIER TUNING CONTROL

Simple radio tuning. Press metal station on the dial—observer, directly sees the indicator beam pencil mark and you get that station instantly! Easy—quick to use in U.S. Ultralyne tuning systems. A single control controls two sets 25 to 1. Finished complete or sub-components in gold or silver finish.

Silver, \$2.50 Gold, \$3.50

PHENIX RADIO CORPORATION

116-D E. 25th Street, New York City

You Want Business

YOUR new equipment, new sales plan, new advertising campaign—what are they worth if they don't bring business, if you can't get the acceptance of the jobber and dealer?

Sell your policy to the president, sell your campaign to the sales manager—but remember that the final O. K. that closes the jobber contract comes from the trained radio expert who passes on the technical merits of your line.

Sell your discounts to the manager, sell your advertising to the salesmen—but remember that that quiet fellow at the back of the dealer's store will be called in to pass judgment on the technical merits of your line.

The radio expert and engineer is the man who accepts or rejects your line. To gain his confidence, talk to him in the language he understands best, reach him in his own magazine, *Radio Engineering*. 8,176 of these men are paid subscribers to *Radio Engineering*, more than the total paid circulation of any other radio trade paper.

Radio Engineering readers absolutely control the buying power of the Radio Industry

This is the first of a series of six advertisements published to show frankly and truthfully, the exact status of *Radio Engineering* as a publication—its circulation, range of influence, editorial policy, class of readers, position as an advertising medium, and why it has been accepted as the leading technical magazine of the Radio Industry.

1



Special for Set Manufacturers

Thirty-eight Set Manufacturers are using Dongan Quality Radio Parts. No matter what your requirements in audio transformers and voltmeters Dongan will assure the best performance.

Dongan Type B—A. C. Tube Transformers for A. C. Tube Receivers were the first on the market and are standard. Get complete data for building A. C. Sets.

Transformers and Chokes for B- Eliminators

DONGAN ELECTRIC MANUFACTURING CO.

2995 Franklin St., Detroit, Michigan

**Type 5
Audio Transformer**

Special quality in this handsome mounted transformer. Attractive price.



**Type CSB
Audio Transformer**

One of 35 types exclusively for set mfgs. Performance equal to any.




**Type N
Voltmeter**

One of 5 types. Range 0-7, 0-50, 0-100 volts. A guaranteed, high grade instrument.



"Transformers of Merit for 15 Years."

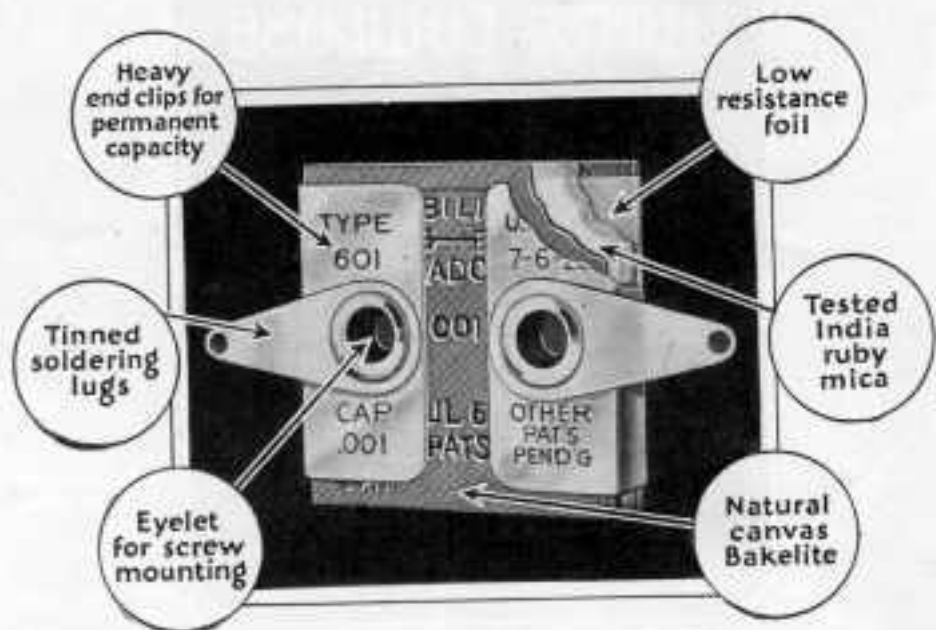

What makes for Efficiency in Fixed Condensers?

This diagram indicates the efficient details of construction that have made Micadons the standard* fixed condensers of radio.

Dubilier engineers have developed these standard condensers of accurate and permanent capacity. Micadons are known the world over—and are used in 90% of all radio sets.

**Standard—anything recognized as correct by common consent of a high degree of excellence.*
—Webster

Dubilier

CONDENSER AND RADIO CORPORATION



Fig. 1. The T. C. set at the Darien laboratory, operating from a Timmons B-Liminator. Note the double-range Jewell voltmeter, used to get the correct rheostat settings

Building and Operating the Samson T. C. Receiver

Presenting the complete construction data on the Samson outfit, the first new kit brought out this fall

Editor's Note: This article introduces an entirely new method of presenting assembly and wiring instructions. Altho Radio Engineering introduced the picture wiring diagram system in 1922, none of the other publications which have used it subsequently have been able to improve upon it.

We believe, however, that we ourselves have increased its usefulness greatly by the changes incorporated in this article. There have been two weaknesses in the past — the difficulty of locating numbers on the drawings, and the lack of adequate means for checking connections.

With the new system, any connection can be found in a second because each

connection is identified with the instrument on which it is located. No wire can be omitted by mistake, because it will show up in the terminal checking list. Each instrument can be checked with the schematic, which also gives the constants and the manufacturer's name as well.

We shall be interested in having your comments on the new schematic and picture wiring diagrams.

MOST everyone has heard rumors and rumblings from Boston, portending interesting results of things which Prof. Bowles, in his quiet way, has been doing. "A construction kit," we heard. "New system of neutralizing," and a word or two about an R. F. choke

which actually performed the service implied by the name.

And now that the set has made its initial appearance, if you know Prof. Bowles, you have an idea of the product so long anticipated—a finished job in every sense of the word, operating in a way to combine with full power and range.

The Samson T. C. Receiver The T. C. receiver, developed by Prof. Bowles, is being produced by the Samson Electric

which are very poor above 375 meters. The R. F. transformer is mounted at the center of the panel. The main tube carries the secondary winding, with the primary mounted at the bottom, and the plate coil, regulating the volume, at the top. Making the primary coupling adjustable is a new stunt, and a good one, because it allows a range of control from full power with slightly broad tuning to moderate power with extreme selectivity. The advantages of this design are ob-

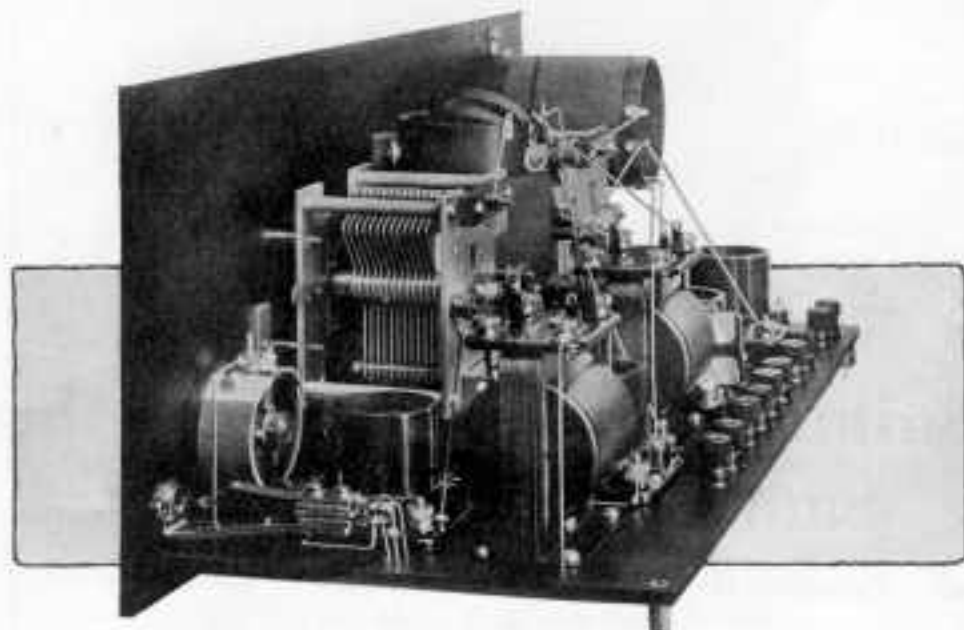


Fig. 2. The A. F. amplifying end of the T. C. receiving set

Company in the form of a construction kit, differing from the usual kits, however, in that it is assembled at the factory, but the wiring is left for the set builder. Thus the cost is greatly reduced over the expense of a finished outfit, yet most of the errors ordinarily made in putting together an unassembled kit are eliminated, since there is very little opportunity to go wrong on the wiring.

The various views of the T. C. set show the new features which have been incorporated. It is interesting to designers to note the increasing tendency to use one step of high efficiency R. F. amplification, capable of amplifying the higher wavelengths, instead of two stages

vious when the set is being adjusted, tho the two controls do not complicate the tuning since the primary coupling is left at maximum unless there is interference, while the volume control requires resetting only when the wavelength is changed considerably.

Fig. 6, the schematic diagram, shows the wiring of the neutralizing circuit. It includes the neutralizing condenser *Q*, R. F. choke *R*, and by-pass condenser *S*. The neutralizing condenser, Fig. 8, is mounted between the R. F. and detector sockets, while the choke and condenser can be seen in the end view, Fig. 3. It is an easy matter to neutralize the set, since the little knob on the condenser

gives a wide range of control.

Contrary to general practice, both A.F. transformers are of the low ratio type, 1 to 3, for the amplification is so high that it was not considered necessary to take a chance of overloading the tubes on heavy, local reception.

Any tubes can be used on this set, tho it is built to operate UV201-A's or C301-A's from a 6-volt storage battery. Reducing the A battery to 4 volts, 199's can be substituted, with adapters to hold them, or the WD-12 tubes work without adapters from 1½ volts.

lighted unless the loud speaker is plugged in at the last jack. All the other instruments are mounted on the base panel.

Holes are already drilled in the base panel where leads from the binding posts are run along the under side. This leaves no drilling or assembly work to be done by the constructor.

Wiring In the preparation of the the T. C. schematic and picture wiring Receiver diagrams, every precaution was taken to guard against mistakes, and at the same time they were arranged as simply as possible, so as not to be con-

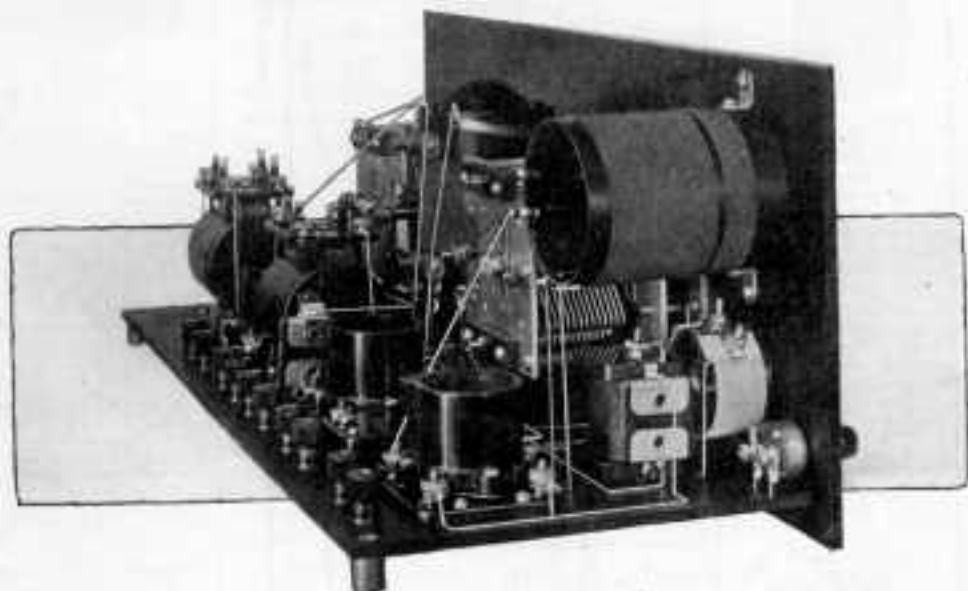


Fig. 3. R. F. amplifying end. Note the choke and fixed condenser


Description The front panel is of Formica, measuring 7 by 18 by 3/16-in., while the base panel, also of Formica, is 7 by 17 by 3/16-in. Lettering is engraved on the front panel to indicate the purpose of the various controls, while the Eby binding posts are identified by lettering also. A Carter Imp switch for filament control is mounted in the lower left hand corner, with a 30-ohm General Radio rheostat, for the detector tube, at the side, and the antenna coupling coil just above. Then come the R.F. tuning condenser, R.F. transformer, first stage jack, tuning condenser, 10-ohm amplifier rheostat, and second stage jack. The last tube is not

fusing to those who lack experience.

Fig. 4 shows the wiring between instruments on the front panel and the wires running from instruments on the front panel to those on the base panel. Fig. 5 illustrates the connections for parts on the base panel.

Each instrument is marked by a capital letter within a circle; each terminal is numbered, starting from 1. For example, the last stage jack is marked A, while the terminals are numbered 1, 2, 3, and 4. The combination A1, therefore, refers to the upper left hand lug of the jack.

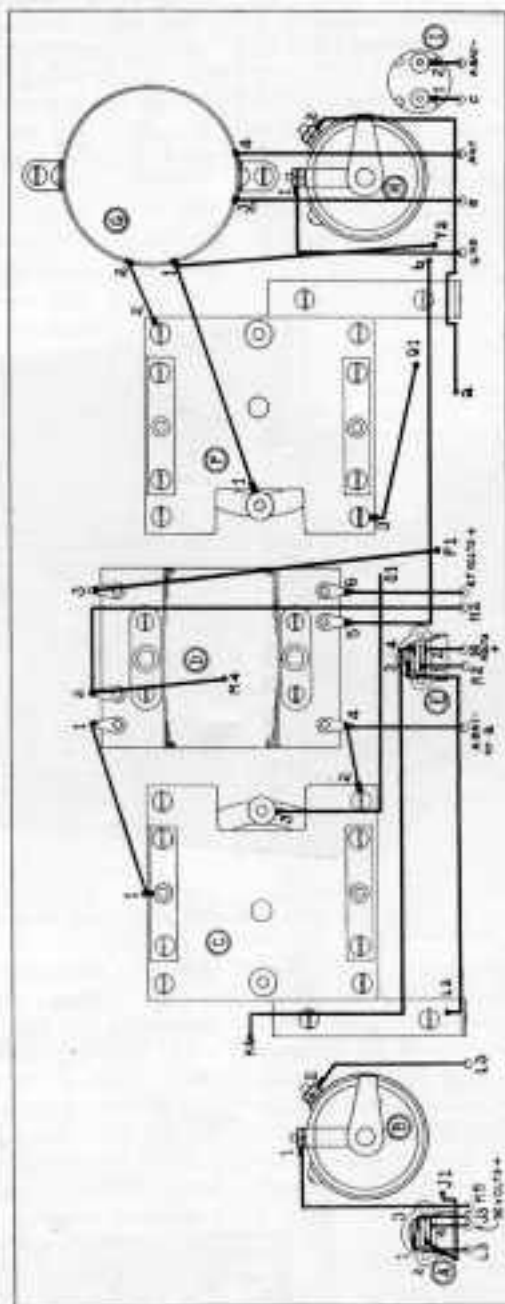If wires from the instruments in Fig. 4 end in small circles, they are run down into holes in the base panel. The wire



DEFINITION	20	21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40	41	42	43	44	45	46	47	48	49	50	51	52	53	54	55	56	57	58	59	60	61	62	63	64	65	66	67	68	69	70	71	72	73	74	75	76	77	78	79	80	81	82	83	84	85	86	87	88	89	90	91	92	93	94	95	96	97	98	99	100
------------	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	-----

W1	W2	W3	W4	W5	W6	W7	W8	W9	W10	W11	W12	W13	W14	W15	W16	W17	W18	W19	W20	W21	W22	W23	W24	W25	W26	W27	W28	W29	W30	W31	W32	W33	W34	W35	W36	W37	W38	W39	W40	W41	W42	W43	W44	W45	W46	W47	W48	W49	W50	W51	W52	W53	W54	W55	W56	W57	W58	W59	W60	W61	W62	W63	W64	W65	W66	W67	W68	W69	W70	W71	W72	W73	W74	W75	W76	W77	W78	W79	W80	W81	W82	W83	W84	W85	W86	W87	W88	W89	W90	W91	W92	W93	W94	W95	W96	W97	W98	W99	W100
----	----	----	----	----	----	----	----	----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	------

W1	W2	W3	W4	W5	W6	W7	W8	W9	W10	W11	W12	W13	W14	W15	W16	W17	W18	W19	W20	W21	W22	W23	W24	W25	W26	W27	W28	W29	W30	W31	W32	W33	W34	W35	W36	W37	W38	W39	W40	W41	W42	W43	W44	W45	W46	W47	W48	W49	W50	W51	W52	W53	W54	W55	W56	W57	W58	W59	W60	W61	W62	W63	W64	W65	W66	W67	W68	W69	W70	W71	W72	W73	W74	W75	W76	W77	W78	W79	W80	W81	W82	W83	W84	W85	W86	W87	W88	W89	W90	W91	W92	W93	W94	W95	W96	W97	W98	W99	W100
----	----	----	----	----	----	----	----	----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	------

W1	W2	W3	W4	W5	W6	W7	W8	W9	W10	W11	W12	W13	W14	W15	W16	W17	W18	W19	W20	W21	W22	W23	W24	W25	W26	W27	W28	W29	W30	W31	W32	W33	W34	W35	W36	W37	W38	W39	W40	W41	W42	W43	W44	W45	W46	W47	W48	W49	W50	W51	W52	W53	W54	W55	W56	W57	W58	W59	W60	W61	W62	W63	W64	W65	W66	W67	W68	W69	W70	W71	W72	W73	W74	W75	W76	W77	W78	W79	W80	W81	W82	W83	W84	W85	W86	W87	W88	W89	W90	W91	W92	W93	W94	W95	W96	W97	W98	W99	W100
----	----	----	----	----	----	----	----	----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	------


W1	W2	W3	W4	W5	W6	W7	W8	W9	W10	W11	W12	W13	W14	W15	W16	W17	W18	W19	W20	W21	W22	W23	W24	W25	W26	W27	W28	W29	W30	W31	W32	W33	W34	W35	W36	W37	W38	W39	W40	W41	W42	W43	W44	W45	W46	W47	W48	W49	W50	W51	W52	W53	W54	W55	W56	W57	W58	W59	W60	W61	W62	W63	W64	W65	W66	W67	W68	W69	W70	W71	W72	W73	W74	W75	W76	W77	W78	W79	W80	W81	W82	W83	W84	W85	W86	W87	W88	W89	W90	W91	W92	W93	W94	W95	W96	W97	W98	W99	W100
----	----	----	----	----	----	----	----	----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	------

W1	W2	W3	W4	W5	W6	W7	W8	W9	W10	W11	W12	W13	W14	W15	W16	W17	W18	W19	W20	W21	W22	W23	W24	W25	W26	W27	W28	W29	W30	W31	W32	W33	W34	W35	W36	W37	W38	W39	W40	W41	W42	W43	W44	W45	W46	W47	W48	W49	W50	W51	W52	W53	W54	W55	W56	W57	W58	W59	W60	W61	W62	W63	W64	W65	W66	W67	W68	W69	W70	W71	W72	W73	W74	W75	W76	W77	W78	W79	W80	W81	W82	W83	W84	W85	W86	W87	W88	W89	W90	W91	W92	W93	W94	W95	W96	W97	W98	W99	W100
----	----	----	----	----	----	----	----	----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	------

W1	W2	W3	W4	W5	W6	W7	W8	W9	W10	W11	W12	W13	W14	W15	W16	W17	W18	W19	W20	W21	W22	W23	W24	W25	W26	W27	W28	W29	W30	W31	W32	W33	W34	W35	W36	W37	W38	W39	W40	W41	W42	W43	W44	W45	W46	W47	W48	W49	W50	W51	W52	W53	W54	W55	W56	W57	W58	W59	W60	W61	W62	W63	W64	W65	W66	W67	W68	W69	W70	W71	W72	W73	W74	W75	W76	W77	W78	W79	W80	W81	W82	W83	W84	W85	W86	W87	W88	W89	W90	W91	W92	W93	W94	W95	W96	W97	W98	W99	W100
----	----	----	----	----	----	----	----	----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	------

Drawn by	RADIO ENGINEERING
Checked by	EMERSON T.C. RECEIVING
Scale	C-2-B
Location	Production Shop
Date	Feb. 2, 1938
Sheet No.	2 of 2
Sheet	1 of 1

Fig. 4. Picture wiring diagram of the front panel, and the checking list of connections

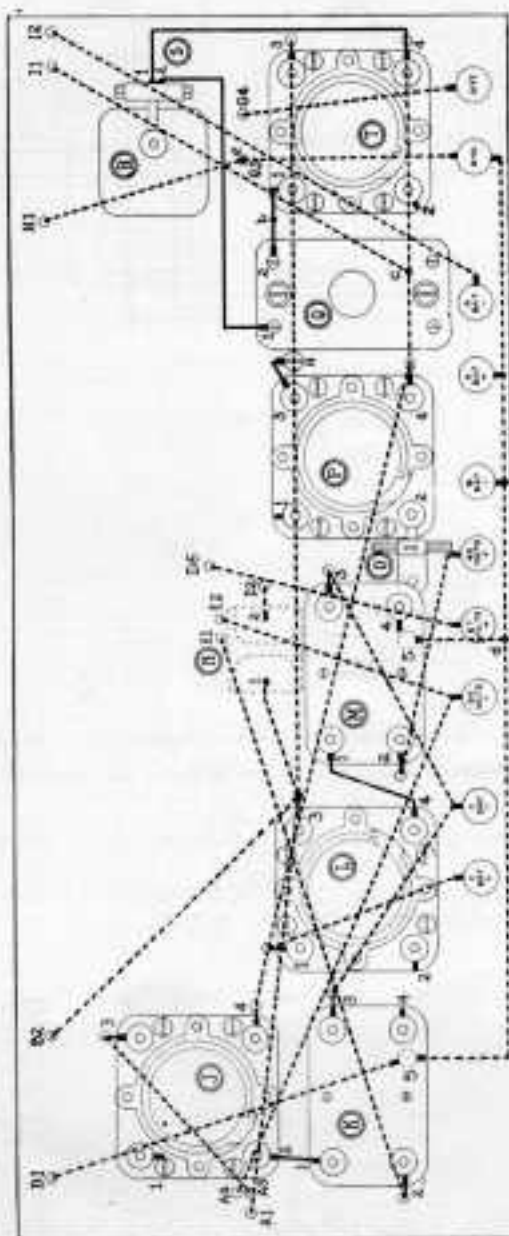

WIRE CONNECTIONS	
ANTENNA	ANTENNA
GRID	GRID
PLATE	PLATE
SCREEN	SCREEN
SHIELD	SHIELD
...	...

Designed by	SAMSON T. C. SET
Checked by	J. H. W. M.
Drawn by	J. H. W. M.
Printed by	J. H. W. M.
Sheet No.	Sheet 1

Fig. 5. The base panel. Dotted lines show wires beneath the panel. They must be covered with tubing

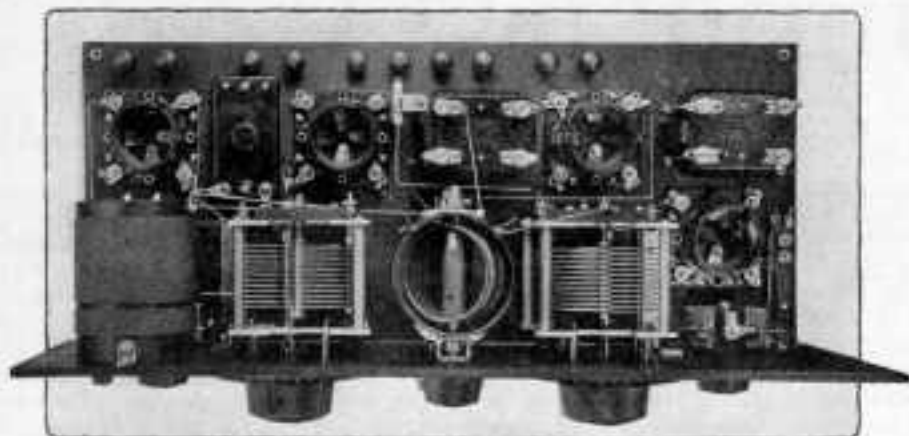


Fig. 8. Looking down on the set. The neutralizing condenser is at the left of the right hand socket

To trace the wire, therefore, start at A1, in Fig. 4, and locate the other end of the wire, L3, in Fig. 5. Then find out thru what hole on the base panel the wire goes up to A1. These drawings are exactly to scale, so that you can find the corresponding holes in the panel without any trouble.

Connection D5 to b presents a different story. Connections made to wires, not binding posts, are given small letters. Look straight down from point b, in Fig. 4, and you will find b in Fig. 5, marked on the wire running from Q2 to T1.

If there is any question about the meaning of the letters in Figs. 4 and 5, look them up on the schematic diagram and parts list in Fig. 6.

Now, for the wiring. The steps are given in Fig. 5, with the reference notes in the following paragraphs. After removing M, to permit access to the jack terminals, connect E2 to 90 VOLTS+. Terminal E2 is the right hand lower contact on the jack, Fig. 4. The wire runs down thru a hole in the tube panel, and along the under side to a lug on binding post 90 VOLTS+. All wiring under the panel must be covered with varnished tubing. As soon as you have completed this wire, put a mark beside E2 and 90 VOLTS+ in the checking list, Fig. 4. Do this with every wire: when you have finished, if any letters in the checking list are not marked, you have omitted a con-

nection. If two wires go to the same terminal, it appears twice in the checking list.

Note 1: Remove transformer M from the tube panel, first noting the locations of the terminals.

Note 2: This lead from D4 must be long enough to reach either the screw on the A BAT—post or screw a. If a D-21 Sodiion detector is to be used, the lead should be fastened to A BAT—, or to a, for a UV201-A detector.

Note 3: Be sure to put two lugs on K5; the rear right hand screw fastening the transformer to the panel.

Note 4: Solder the lugs on the R.F. choke, R, to the terminal of the 0.00025 mfd. Micadon.

Note 5: S2 is the lower lug on the Micadon.

Note 6: Solder a long wire to T4, run it under the hole next to P4, and solder a short wire from P4 to the long lead. Run the wire under L1, and make a similar connection to L1. Finally, run the wire up thru the tube panel to J4.

Note 7: S1 is the upper lug on the Micadon.

Note 8: Put a lug on P2 and solder it to the lower side of the grid leak condenser. Put a 5-megohm leak in the clips.

Note 9: K5 and M5 are screws holding the transformers to the tube panel.

Note 10: Terminal a is a $\frac{1}{2}$ -in. 6-32
(Continued on page 398)

Selenium and Photo Electric Cells

Chapter II. Essentials of Selenium cell construction and forms discussed—by Samuel Wein

The Selenium Cell Defined. The specific electrical resistance of selenium is said by Bidwell¹⁰ to be in the neighborhood of 2,500 megohms per cubic centimeter. Therefore, in order to facilitate experimentation, it is necessary to apply the selenium in such a way that only a short path of a comparatively large cross section is traversed by the current. A further condition is that the selenium must be spread out in a thin layer, so that a comparatively large surface, with respect to its volume, will be affected by the light. This is necessary because the thinner the film of selenium, the less inertia the cell possesses, for the light appears to act only on the surface of the selenium. A device employing selenium so as to fulfill the foregoing conditions is called a selenium cell, bridge, unit, or element. Since the term "selenium cell" is used universally amongst those who have occasion to work with these devices, that term will be used hereafter.

A selenium cell consists of two electrically conducting substances, between which is deposited the selenium, and thereafter annealed, so that the selenium cell will exhibit the greatest light sensitive characteristics.

There are a number of various types of selenium cells in use. Of the various types, there are only three distinct forms in constructional details, viz: (1) in which the selenium is deposited between two electrically conducting mediums in the form of wires, tapes, or plates; (2) deposited on a metal plate on which is applied a transparent or translucent conductor, such as metallic foil; (3) a very fine cell construction consisting of a metal film divided into two parts between which the selenium is applied, filling the dividing lines.

The Conducting Materials. Use has been made of copper, iron, nickel, platinum, German silver, brass, various alloys, graphite, and carbon.

These various metals, excepting platinum and nickel, oxidize very freely, especially during the process of annealing the selenium cell. Metallic selenides—reaction product between the selenium and the metal plate used—are also formed during the annealing process. This oxidation and the formation of selenides produce poor grades of completed cells. For ideal purposes, although the cost is somewhat higher, the use of platinum is always advocated, or if this is prohibitive, nickel should be used. Any wire on which platinum has been electrolytically deposited can be used with ideal results.

The Non-Conducting Materials. Slate, free from metallic veins, mica, unglazed porcelain, roughened glass—sand blasted or etched with hydrofluoric acid—soap stone, and various compositions can be used as the non-conductor.

Applying The Selenium. The various forms or types of selenium cells have their advantages as well as disadvantages, depending greatly on the specific manner in which the cell has been made, as well as the layer or film of selenium itself. The temperature of annealing the cell has much to do with its characteristics. To show each phase of cell construction, we shall review the specific methods of applying the selenium to the embryo cell form.

Some investigators prefer to heat the cell and rub a rod of selenium over it, spreading the selenium evenly over the surface with a steel spatula. Others prefer to sprinkle a little of the powdered selenium over the hot cell form and after it has melted, spread it over the surface. A simple form is to melt a little of the selenium in a spoon and allow a few drops of it to fall on the embryo cell, spreading it over the surface afterwards. The former methods produce thick and uneven films of selenium. Keeping this fact in mind, several investigators produced thinner and more even films by

means of cathode disintegration. This process necessitates considerable apparatus and time to produce such a film. The condensing of selenium vapors, made by boiling the element, has produced very fine cells.

It is well to mention the fact that the literature of the subject is very confusing with respect to credit for originality. Several experimenters have already



Fig. 1. Circular type of Siemens cell. The wires are covered with selenium.

claimed priority on certain constructional forms. The author will not attempt to pass judgment on these claims, but will merely cite such cell forms as are identical to those described in earlier references in the technical literature and for those on which patents have been granted.

The details of the cell construction are those given by the original constructors, tho changes can be made to suit individual conveniences and requirements.

Group 1, Type A.

Siemens.¹¹ The first high efficiency selenium cells were made by Siemens. These he built by winding two separate lengths of No. 40 B. & S. gauge wire, side by side and equidistant throughout



Fig. 2. Another arrangement of the Siemens cell.

their entire length, on a non-conducting substance about 1/8 in. thick, and about 1 1/2 in. wide. Two typical cells are shown in the Figs. 1 and 2.

Bell and Tainter.¹² During their experiments, Bell and Tainter found that

they required the use of cells which could be placed in the focal plane of a parabolic reflector. To this end they devised the cell shown in Figs. 3 and 4. Two No. 40 B. & S. gauge wires 1/32 in. apart were wound throughout the entire length of a glass rod or tube about 2 1/2 ins. long and 3/4 in. in diameter. Fig. 3

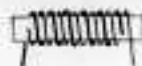


Fig. 3. A single cell made by winding two wires on a glass rod.

shows the completed cell as used in their famous photophonic experiments, and Fig. 4, the cell fixed in the focal plane of a parabolic reflector.

Bidwell.¹³ Simplified construction of the former types of cell construction developed by Bidwell, are used almost universally to-day.

This cell is made by winding on a piece of non-conducting material 2 1/2 ins. long and 3/4 in. wide, beginning at 1/4 of an inch from one end, a flat spiral of No. 40 B. & S. gauge wire. The pitch of each turn of the spiral is 1/16 in. The winding is brought to 1/4 in. from the other end. The ends of the wire are fixed by passing them through holes drilled in the slab. Then a second wire is wound beside the other, forming a



Fig. 4. The Bell-Tainter cell mounted in a parabolic reflector.

second spiral, the turn of which are midway between those of the original one. The method is shown in Fig. 5.

Ruhmer.¹⁴ In making the so-called Bidwell type cells, difficulties are always experienced in the short circuiting of the two wires, due to the expansion and contraction of the wires during the process of annealing and cooling the cell. To eliminate this difficulty, Ruhmer cuts the slab of non-conducting material in half, so that the wires will fit snugly in it. The expansion of the wires during the

annealing process is taken up by separating the slabs a little.

Pfund.¹³ Many experimenters find difficulty to wind the slab of non-conducting material with the two wires evenly spaced throughout its entire length. A convenient manner of accomplishing this is suggested by Pfund. He ground one side of a piece of glass plate 1 by 3 by 0.1 with emery, or etched the glass with hydrofluoric acid. Then he spread selen-



Fig. 5. A flat cell, with two spiral wires coated with a thin layer of selenium

ium over the ground glass surface by means of a hot glass rod. The thickness of the layer was such that in transmitted light the film of selenium, in its thinner portions, appeared deep ruby red. Next, he wound four strands of No. 30 B. & S.



Ruhmer mounted his cell in an evacuated tube to protect it against moisture and temperature changes

gauge bare copper wires around the glass plate in such a manner that the entire selenium surface was covered. After binding the loose ends of the wires to the glass plate, he removed the second and fourth wires, leaving the first and third separated by a distance equal to the diameter of the wire.

Ruhmer.¹⁴ The selenium cell used by Ruhmer was mounted in an evacuated glass bulb to eliminate the probabilities of

errors in the change in ohmic value due to atmospheric pressure, humidity, and other physical conditions. Such a cell is more stable, and readily adapted into electrical circuits. Two forms are shown in Figs. 6 and 7.

These cells are made on a double thread cut into a soapstone or unglazed tubing. A convenient size for construction purposes is $\frac{1}{2}$ in. in diameter and 2 ins. long. Into these grooves are wound, while hot, two No. 40 B. & S. gauge wires. These are secured to the base of a standard Edison incandescent lamp. The selenium is applied over the surface of the wires and properly annealed, then enclosed in an evacuated glass bulb.



Fig. 7. This Ruhmer cell is mounted in an evacuated tube which is silvered on the sides to reflect light on the cell

The glass bulb of the cell shown in Fig. 7 is silvered on the bottom, to reflect the light on the selenium around the entire surface.

These were first used in connection with the photophone.

REFERENCES

- ¹ Bidwell, *Philos. Mag.* (5) vol. 31, page 251, 1891.
- ² Siemens, *Berl. Sitz. Ber.* vol. —, page 280, 1875.
- ³ Bell and Tainter, United States Pat. No. 225,497 Dec. 14, 1880.
- ⁴ Bidwell, *Nature*, vol. 23, page 58, 1860.
- ⁵ Ruhmer, *Electrotech. Zeit.* vol. 25, page 1021, 1904.
- ⁶ Pfund, *Phys. Rev.* vol. 28, page 325, 1909. *Phys. Zeit.* vol. 10, page 349, 1909.

BAKELITE MOLDING

With the cooperation of the Hydraulic Press Manufacturing Company, we are preparing an article of special interest to radio manufacturers. It deals with the installations, operation, and maintenance of a typical moulding department, detailing the costs, space requirements, personnel, and other factors. This article will appear in the September or October issue.

RADIO ENGINEERING

M. B. SLEEPER, Editor

F. A. SKELTON, Managing Editor

Published monthly by

M. B. SLEEPER, Inc.

Publication Office, Lyon Block, Albany, N. Y.

Editorial and General Offices

A-52 Vanderbilt Ave., New York, N. Y.

Chicago Advertising Office

E. H. Moran, Bell Building

307 North Michigan Ave., Chicago

Twenty cents per copy in the United States and Canada; in foreign countries one shilling. Two dollars per year, twelve numbers in the United States and Canada; ten shillings in foreign countries.

Copyright 1925 by M. B. Sleeper, Inc.

Vol. V AUGUST, 1925 No. 8

EDITORIAL

EVERY radio magazine naturally aspires to bring out a set which will be the big success among radio set builders and which, in turn, will be taken up by the manufacturers.

This summer we decided that Radio Engineering would introduce not only the outstanding set for this winter but a design which will set a precedent for future developments.

Because we always tackle our construction and design articles as laboratory problems, we had an advantage at the start. So it was as a laboratory problem that we set to work on this task. There are always plenty of set builders who make any new set, and of that number some are always conceited enough, or ignorant enough, to think the results are wonderful, no matter how they would show up against a good outfit.

Unfortunately radio sets won't give unusual results just to be ob'iging. They require reasons. So we knew we couldn't shake up a lot of parts and roll them out until they turned up in the right combination. Reviewing past experience, we remembered that the easiest set to operate, and the finest of all sets for quality, was the old crystal receiver. And we decided that if we could add sharpness of tuning and volume of tone to crystal set operation and quality, we would have the design which would dominate all others.

Three months ago we completed the RX-1 receiver at the Darien laboratory—

produced the results we had sought—and did it with a non-regenerative circuit, a circuit so old that most of the men in the radio business to-day don't know there is such a thing as a set, unless there's something wrong with it, that isn't operated in a regenerating condition, just under the point of oscillation.

Put your finger on any part of the circuit, mention any feature of the operation and there's a reason for it or for what happens. Why is it non-regenerative, why is the tuning sharp, why the particular selection of tubes, the high R. F. amplification, the resistance coupled amplifier before the transformer stage, the almost uncanny quality of reproduction, the elimination of rheostat adjustments without which no tuned R. F. or neutrodyne set can be operated to full volume?

There is a plain answer to each of these questions, no camouflage or mystery, but ordinary facts which any novice can understand. That's why the RX-1 receiver, developed entirely in the Darien Laboratory, will be the most popular outfit among set builders this winter, and will set a new standard for radio manufacturers who now think a radio set that isn't tuned R. F. or straight regenerative must be a super-heterodyne.

You may wonder why, since the set was completed three months ago, we waited until now to talk about it. You'll understand if you have had experience in manufacturing radio equipment. To produce a laboratory model means nothing until the set has been in operation over a period of months, and has been tried out under all sorts of conditions, operated by all kinds of people. We have run the RX-1 for days at a time, exposed it to the weather, tried it on different antennas, worked with dozens of different tubes, operated it in the woods, and at the sea shore, working by the illumination from motor car head-lights.

We put it to every test we could devise, yet the greater the task, the more splendid the response until now, as we are preparing the complete construction article for the September issue, we are thoroughly confident that it will win your respect as it has won ours, that on a scale of points it will score above any other set as an example of radio engineering skill and judgment.

M. B. SLEEPER,
Editor.

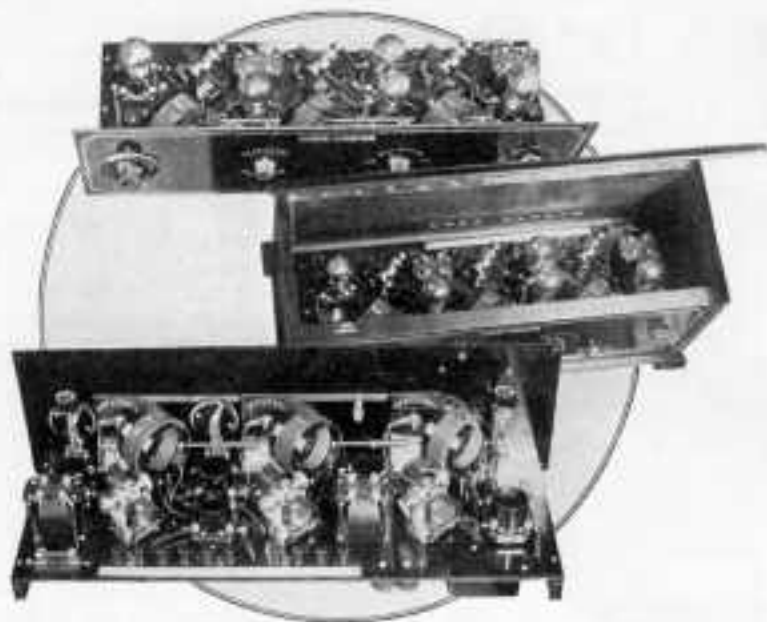


Fig. 1. Three views which show the mechanism of the Kellogg set

Tuning an R.F. Set by Inductance

Examine the design of the Kellogg Wave Master and you will discover a number of new ideas you have not seen before.

THE first original development in single control receivers, so far this fall, is that of the Kellogg Wave Master. Detailed illustrations of the set are given in Figs. 1 and 2, with the complete wiring diagram in Fig. 3. Some of us will be rather surprised to see tapped coils on this set but, after all, when theory and practice disagree, we must be guided by practical results.

The new Kellogg set has two stages of tuned R.F., detector, and two stages of audio amplification. There are three tuned circuits, in this new type of receiver, but the control of the wavelength is obtained by a switch on each R.F. transformer secondary and a variometer control for fine tuning, with fixed air condensers to provide the capacity in each circuit.

In Fig. 1 you can see the three switches, controlled by a single knob at the front,

and the common shafting for the variometer rotors, turned by a knob and dial connected through beveled gears.

Aside from the single control feature for tuning, this design was worked out to give extremely sharp tuning. In the ordinary Neutrodyne receiver, each circuit is adjusted over its full range by rotating a dial through 180 degrees. On the Kellogg set, there are nine wavelength ranges obtainable by a 9-point switch, each covering approximately 40 meters, with an overlap at the upper and lower ends of the scale. 60 degrees rotation are required for the 40-meter range which is equivalent to 540 degrees of rotation for the full range of the set. Therefore, the tuning is three times sharper than on the regular Neutrodyne receiver.

The primaries of the transformers are fixed, with the secondaries wound partly

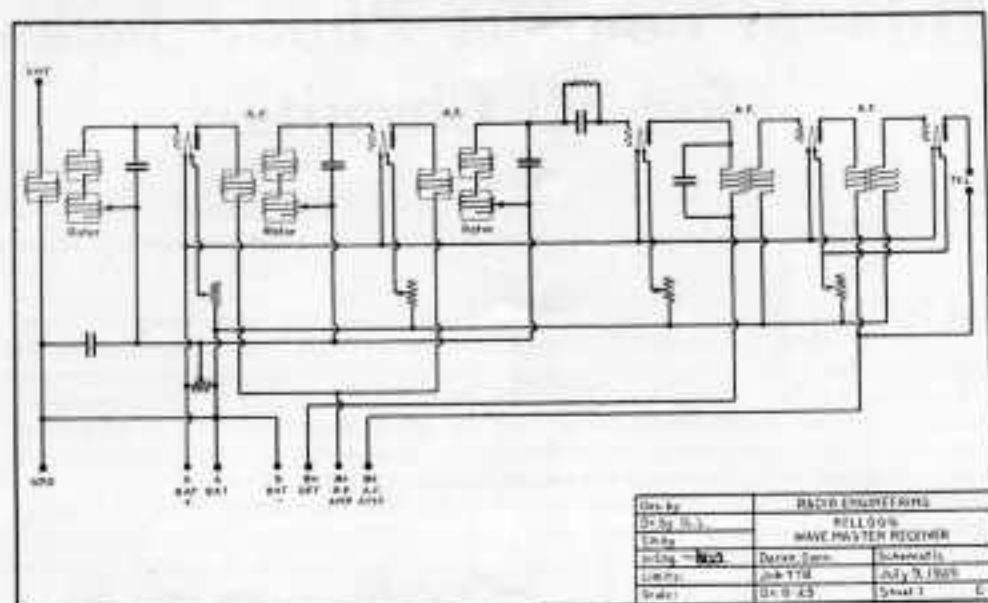


Fig. 3. Schematic circuit of the receiver. All three secondary inductance switches operate from one knob

on the stationary tube and partly on the rotating tube. This is somewhat on the order of the Danziger-Jones transformers, except that they cover the full range at one rotation of the movable coils.

The capacities of the variable condensers, mounted at the rear of the tube panel, are set at the factory when the outfit is given the final test. When the adjustments are being made, not only are the variable condensers regulated to their proper positions but the correct relation between the three rotors is also determined, in order that the circuit will be in tune at the longest wavelengths as well as the shortest.

By the use of variometers for tuning, as the design works out in practice, particularly close regulation can be obtained since the variation of inductance at the center of the scale is comparatively slow, increasing rapidly at the upper and lower ends. Since only 60 degrees are used at each setting of the inductance switches, those 60 degrees come at the center of the scale, right where the inductance is varied at the lowest rate.

Tests indicate that it is practical to use a fairly long antenna with this outfit, and still maintain the extreme selectivity. It will operate on a short single wire but for best results one wire about 80 ft. long is recommended.



Fig. 2. The outward appearance is simple and attractive enough for anyone

How to Connect Phone Jacks for All Circuits

By reducing telephone and filament control jack circuits to their elements, they can be applied easily to any type of hook-up

WHEN Mr. Engelson, of the Brooklyn Metal Stamping Company, suggested that a set of diagrams showing various ways to connect jacks in different kinds of circuits would help to clear up the confusion and misunderstanding about their use, we agreed with him, and started forthwith to determine what hook-ups would present the most information. But we discovered a few diagrams would not show enough, and even a great many would not cover all circuits.

Which accounts for the peculiar set of sketches opposite. Since we couldn't possibly show all the receiving set circuits using jacks, we decided to show all the jack circuits used in receiving sets.

Just because these diagrams look different, don't assume that they are complicated, for if you think about them enough to get the idea, you'll be able to use them as simply as a footrule.

Examine a filament control jack and you will see that it has two sections—on top, the two or three springs for the filament circuit, and one, two, or four springs below for the plate circuit. Accordingly, we divided the diagrams into those which concern the filament, and those connected to the plate. If you don't want filament control, pay no attention to sketches E to J. Simply pick what you want from A to D. Or, in case you want filament control, get the combination from E to J and add it to the suitable diagrams from A to D.

A: Ordinary method for an A.F. amplifier except the last stage. This is often used, but is not recommended because it does not cut out the transformer when the phones are plugged in.

B: Most common arrangement for all stages except the last. A simple way to disconnect one side of the transformer when the plug is inserted.

C: Here the transformer is disconnected entirely when the phones are plugged in. Many designers prefer this method altho, so far as the operation of the set is concerned, it is no better than B. This is for all except the last A.F. stage.

D: The last stage of an A.F. amplifier, or the detector, if no A.F. amplification is employed, is always connected this way.

Notes: Only the transformer primary is shown, as the wiring of the secondary is not affected by the use of jacks. The +B lead goes to +22V. if the jack is in the detector or, in an amplifier circuit to +45V. or whatever is used for the amplifier voltage.

A set without an A.F. amplifier should use D in the detector plate. With a detector and one stage of A.F. use B in the detector plate, and D in the amplifier plate circuit. When there are two stages of A.F., use B in the detector and first stage, and D in the second.

E: When you have a detector and two stages of A.F., if you want to plug in at each tube, you must use this circuit, with three rheostats, for filament control.


F: Both A.F. tubes can be controlled by one rheostat if you do not want to plug in at the first A.F. stage.

G: Four-tube set with three jacks, using a separate rheostat for each tube.

H: Four-tube set with two jacks, one rheostat controlling both A.F. tubes.

I: This is for a five-tube set, arranged with filament control jacks at the detector, first stage, and second stage. Both R.F. tubes are on one rheostat, but separate rheostats are required for the A.F. tubes.

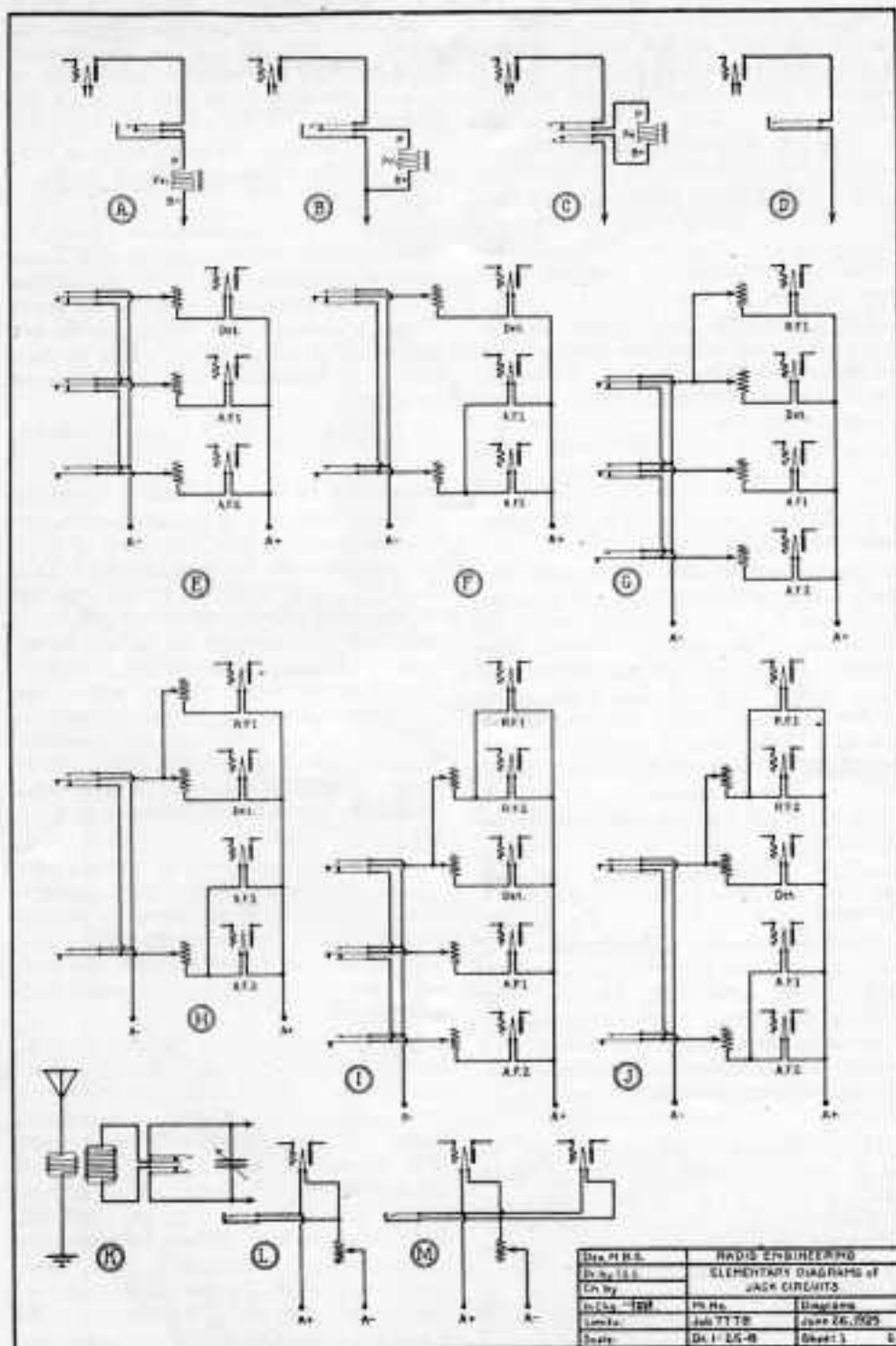J: The same sort of set as at G, except that both A.F. tubes work on one rheostat. No jack is used at the first stage.



Thirteen different elements of circuits using telephone jacks

Notes: To obtain a positive bias on the grid of any tube, connect the filament side of the transformer to the + lead, as shown in the sketches, or for a negative bias, to the - lead. Where rheostats are shown, Amperites, Brachstats, or Daven balast resistors can be substituted.

K: This diagram gives the connections for a set to operate on an antenna and ground or on a loop. Normally the coupler is connected, but plugging in the loop cuts out the coupler.

L: If you want to measure the voltage across your tubes, and don't want to mount a meter on the panel, you can use jacks for plugging in the voltmeter.

You must use an open circuit jack, and connect it on one side to the common filament lead and on the other side to a wire running from the tubes to the rheostat.

M: Two or more tubes must be connected to the voltmeter jack as shown in this diagram.

Note: It is important to remember that soldering paste must be kept away from the insulation. This is particularly true on the amplifier jacks, for the paste forms a leakage path which causes the insulation to break down. For safety's sake it is advisable to use rosin core solder.

(Continued from page 389)

machine screw put thru the tube panel, and held by a nut.

While you are wiring the set, bear these points in mind: Have the soldering iron clean and hot enough to make the solder run smoothly—use rosin core solder—if the lugs are not bright and clean, scrape them off with a file or the solder will not stick—for the wiring use Wirit, the No. 18 special-tempered tinned copper wire which you can stretch and straighten yourself—use Spintite wrenches to get the nuts and thumbscrews tight.

Testing and Operating When the wiring has been completed, connect the A battery as shown in Fig. 6. Put in the tubes, turn the rheostats about half way on, and put the filament switch at ON. If the tubes light, disconnect the positive lead from the storage battery and connect it to each of the +B binding posts. The tubes should not light then. If they do, there is a short circuit in the wiring.

If the filament circuit is O.K., put on the B and C batteries, Fig. 6. The only exact way to tell about the correct adjustments of the rheostats is to have a voltmeter by which the voltage can be measured across each tube. In Fig. 1, showing the outfit set up for test at the Darien laboratory you will see a Jewell double-range voltmeter mounted above the bench. Leads are provided so that the

voltage can be measured across the tubes. It is also used to test B battery voltages, since it has one scale for 0 to 12 volts and another scale for 0 to 120 volts. This takes the guess work out of the rheostat settings and assures maximum life from the tubes. To measure the voltage across a tube, connect a low-reading voltmeter directly to the socket binding posts. Do not measure the voltage of the A battery, since that does not show the potential actually applied to the tubes. With 201-A tubes the voltage measured at the socket should not be over 5, or 3 volts with UV-199 tubes.

As for the C battery, on the Crosley Musicone we had only 1½ volts negative C taken from a small Eveready biasing battery, for a Western Electric Cone speaker we used 4½ volts, while the Kellogg and N & K speakers worked best with 3 volts.

It took a little study to find out just how to get the best results from the T.C. set. Accordingly, a few suggestions are given below. The T.C. set is extremely sharp, much more so than the usual tuned R.F. set, so that the dials must be turned slowly and carefully or a station may be passed over. In our tests we used the D-21 standard base Sodian detector with a negative grid return, as it gave louder signals and made the set much easier to handle than with the 201-A detector with a positive bias. On all dial settings above

(Continued on page 413)



Fig. 1. We didn't count stations, in the RX-1 tests, unless the Musicone would bring them in clearly. This photograph was taken at 2.00 A. M. on the shore at Southport, Conn.

Some Angles On A. F. Circuits

Explaining the line of reasoning followed in planning the audio frequency amplifying end of the RX-1 non-regenerative receiver.

FIGS. 2 and 3 show the detector and audio frequency amplifier of the RX-1 receiver. The first striking thing about these illustrations is the extreme simplicity of the arrangement, the short leads, and the small number of wires required.

But simplicity is only useful when it serves a practical end. It is largely a matter of good fortune that the RX-1 amplifying system is so simple.

The reason that the RX-1 gives the impression of having big reserve power lies in the D21 Sodian. This tube also supplies the answer to the question that has already been raised, "Why doesn't the detector circuit oscillate?" There are other questions which will be answered but let us take them up, with their answers, in the sequence in which they appear in the circuit.

The detector circuit doesn't oscillate because of the extremely high impedance in the plate circuit of the Sodian detector. It is several times higher than the

impedance of the 201-A tube. Some experimenters use a high variable resistance in the detector plate of a 201-A to stop oscillations. That is not an efficient method, although it is effective in stopping oscillations. The same result is obtained efficiently in the Sodian, for the construction which is employed to make the tube extremely sensitive turns out, happily, to produce a high impedance in the plate.

If the Sodian is followed by a transformer coupled amplifier, and a tickler coil is provided, the detector can be made to oscillate at short wavelengths. However, in the RX-1 no tickler was used, nor it is necessary to produce maximum efficiency either at the high or low wavelengths.

Because of the high impedance of the Sodian, there is no need to use a transformer. In fact, the Acme Apparatus Company, in their Cabot Circuit Receiver, use only the secondary of an A. F. transformer, connecting it as an

impedance coupled amplifier. Our tests show that as great or greater amplification can be obtained with resistance coupling. This effects a saving in expense, assures distortionless amplification, and, without sacrificing efficiency, allows the addition of 100,000-ohms in the plate circuit of the Sodian as a further prevention of regeneration or oscillation. Resistances up to 1.0 megohm have been used in the resistance coupled amplifier without cutting down the signal strength. A very definite sav-

with the 1 to 6 type, but the 1 to 3 transformer has a slightly better amplification curve, and sufficient kick is delivered to the primary of the transformer so that there is no necessity for forcing the last tube.

Several people who have seen the original model of the RX-1 have remarked on the fact that four-tube sets do not give quite enough pep, and that one stage of radio frequency amplification is not enough to bring in distance.

The obvious answer to arguments of

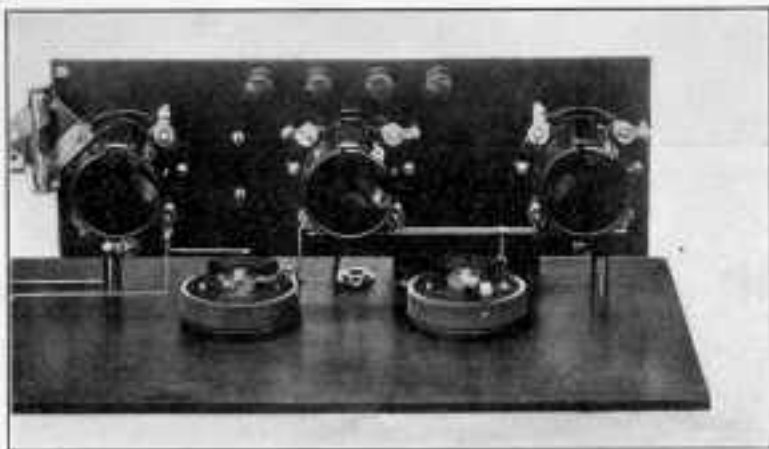


Fig. 2. Efficiency usually means simplicity. That is the case with the RX-1 receiver.

ing in B battery consumption is effected since the detector plate current is only 0.25 milliamperes, against 3 to 5 milliamperes with a UV201-A detector.

The first impression of the circuit arrangement, using resistance coupling first and then transformer coupling, is that it is exactly opposite to the customary method in amplifiers which have both resistance and transformer coupling. In the ordinary amplifier the transformer coupling is used first to get extra amplification at the start for the resistance stages to work on. In the RX-1 circuit, on the other hand, no useful purpose would be served by having a transformer stage following the detector since the amplification would not be increased at all.

In the second A. F. stage we used a 1 to 3 Samson transformer. A little greater amplification can be obtained

that sort is given by the results produced. If you think that a five tube tuned R. F. receiver requires two stages of R. F. for its range, try putting the antenna and ground on to the primary of the first R. F. transformer, eliminating the first R. F. tube altogether. You will probably find that the range will not be affected appreciably. Most five-tube sets have two stages of R. F. for reasons of convention only.

If you think that a set must be operated just under oscillation to have real kick in the loudspeaker, try the RX-1 and you will get the answer from the set itself. Over a period of ten days in a series of final tests, the RX-1, set up at the Durien laboratory using a single wire antenna sixty feet long and eighteen feet high at each end, has brought in sixty-seven stations, ranging from New Orleans to Montreal, Miami,

Fla. comes in as loud as many of the New York stations. After midnight, WSB, WTAM, WJJD, WREO, operate a Crosley Musicone with sufficient volume to dance by. These tests were made from July 3rd to July 12th, a time at which in New England, the worst static of the year is experienced.

During the last four months, we have tried the RX-1 set under all kinds of

wants a lot of knobs on his set, so that the RX-1 would not appeal to him for that reason alone. The outstanding features of this set are the simplicity of tuning, lack of hairsplitting adjustments, freedom from howling, and the quality of reproduction of which only a non-regenerative receiver is capable, together with volume equal to that obtained from circuits which depend for signal strength

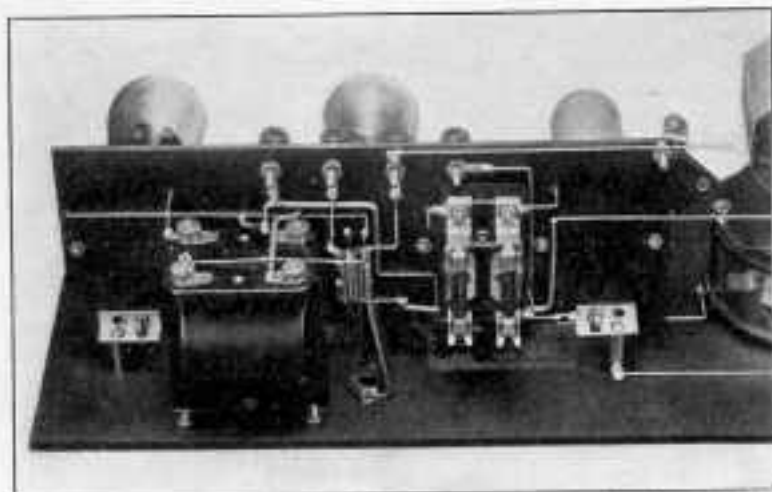


Fig. 3. The same general design was followed in the final model, but improvements were incorporated here and there.

circumstances, using it right in New York City, to test the selectivity, operating it in the woods and at points on Long Island Sound to see how it would respond away from the more or less ideal conditions at the laboratory. Fig. 1 is reproduced from a photograph taken at night by the illumination from the motor car headlights. The set was put up on the shore at Southport, Conn. The ground connection was a sparkplug wrench, fastened to the ground lead and dropped into the water. The antenna was a thirty-foot length of wire two feet high at one end and seven feet high at the other end. On this occasion we heard WREO, WJJD, WMBF, WBZ, WPG, WGN, KDKA and a number of other stations less distant, in addition to those in New York City.

However, these results are not given to indicate that the RX-1 receiver is primarily a long distance outfit. As a rule, the DX hound is the sort of man who

upon operation just below the oscillating point.

The set shown in the accompanying illustrations, and in the illustrations in the previous article on the RX-1 tuning circuit, is the original experimental model. This has been changed considerably in working out the mechanical design for the final set. The electrical constants and characteristics have not been altered but the appearance is quite different. Complete photographs with picture wiring diagrams and step-by-step instructions for the final RX-1 design will be given in the September issue of RADIO ENGINEERING.

Dataprints are already available, giving full-size panel patterns, picture wiring diagrams, parts list, and all other details necessary, including the winding data for the pickle bottle coils. The construction of the set is extremely simple, no kinks or tricks, and the parts required are all of standard makes which you can obtain easily.



Silver-Marshall SLW variable condenser

A SPECIAL exhibition of German precision instruments and radio equipment is a feature of the Leipzig Technical Fair which will be held from August 30th to September 9th, 1925 and from February 28th to March 10th, 1926.

The Alden Manufacturing Company has announced a new series of sockets and adapters to take the new R. C. A. tubes, UX199, UX11, UX12, and UX201-A. The Na-Ald socket for these tubes bears the type number 481X, while the adapter is designated as type 419X. These new R. C. A. tubes have contacts similar to those on the WD-11, but of different dimensions.

Glass panels and cabinets are being featured by the A. W. Hornig Company of Chicago. They are designed for home use or for special display purposes in dealers' stores. Each hole in the glass is protected by a safety bushing, so that screws can be tightened without fear of breaking the glass. This is an important point, making the use of glass panels and cabinets thoroughly practical.

No tube is too critical in the adjustment of the filament for the "Three E" rheostats, a new development recently introduced by the Electrical Engineers Equipment Company of Chicago. These rheostats accomplish in a very simple way what a number of designers have tried to do unsuccessfully. The resis-

tance wire unwinds from a threaded spool of insulating material on to a threaded metal spool, as the controlling knob is rotated. In this way the contact is made with every fraction of an inch of the resistance wire, giving the finest variation that can be obtained. A clever arrangement of the mechanism prevents the spools from being turned so far that the wire would be broken off at the minimum and maximum settings. The rheostat has been worked out mechanically in a very attractive way.

The Heliotron power tube, manufactured at a price of \$5.00 by the Helios Electric Company at West New York, New Jersey, operates at 5 volts with a filament current of 0.5 ampere. The plate voltage can be varied from 45 to 135. The voltage amplification is 7.5 to 8.5, plate impedance 4000 to 5000 ohms, and mutual inductance but 500 to 1,700 Micromhos.

Silver-Marshall is now making deliveries on their new S. L. W. condenser, a very small and neat single bearing type with an unusually clever tension adjustment which holds the plates securely. Only one strip of insulating material is used on this condenser. The plates are silver plated.

Philco is announcing A and B battery supply devices, operating from 110 volts A. C. It was recently demonstrated at Philadelphia for the first time.

The Samson Electric Company will feature an S. L. F. condenser which is very different from any of the other designs. Recognizing the importance of keeping dust from the insulation, they will enclose it in an attractive metal case.

EBY PATENTED BINDING POSTS

After you have put time money and labor into the building of your set, don't jeopardize its efficiency with doubtful binding posts.

Ask your dealer to show you why EBY Quality Posts are the choice of over 150 radio manufacturers.

6 types—25 different markings—and the tops don't come off!

The H. H. EBY MFG. CO.
Philadelphia, Pa.



Ensign Enclosed



15c
each

20 Microfarad

Mershon Condensers

Just the thing for battery eliminator circuits—can't be burned out. Small in size, to fit nicely in cabinets.

SPECIAL BARGAIN

While they last, \$4.00 postpaid for the 20 mf. size; \$4.50 for the 40 mf. size. Brand new, guaranteed. Manufactured by the Amrad Company under the Mershon patents.

C. J. BROWN & CO.

Room 213, Vanderbilt Concourse Bldg.
New York City



No. 55
WITH SELF-CONTAINED
MULTIPLE SWITCH

Pat. Feb. 24, 1925.

MEASURE—

Your batteries from the panel of your set.

¶ The Jewell No. 55 Instrument has a self-contained multiple switch. We originated this type Instrument for receiving sets and have applied for patent.

¶ Super-Heterodyne Sets with their large number of tubes should have a constant control of "A" and "B" Batteries from panel of set.

Buy from your dealer.—Ask for our 15-B Catalog.

Jewell Electrical Instrument Co.

1650 Walnut St. - - Chicago



3-Stage Resistance Coupled Amplifier Kit No. 1-C

Price \$6.75

Contains 3 "Electrad" Resistor Couplers, 1-00625, 1-005 and 2-006 "Electrad" Certified Mica Condensers, 1 condenser mounting, 2 "Electrad" Certified Grid Leaks, 4 "Electrad" Certified Resistors. Only other parts needed are sockets, one rheostat, binding posts and bus-bar.

ELECTRAD INC

428 Broadway, New York City

LAST
A
S
T
I
T
E

the
centered
terminal

Lastite
is Radio's only
perfect, permanent
Contact.

This fact is of the utmost interest to all Manufacturers, and all set builders, who seek to eliminate a prevailing fault of radio circuits—the common nut-and-lug connection that after a time works loose.

If your intention is to permanently sustain the precise functions of your apparatus, by having it in dependable circuits, you will find the Lastite is preeminently necessary.



Manufacturers and Distributors, write or telegraph for samples
William Stevens Co.,
27 Hammatt Road, Roslindale, Mass.

PATENT APPLIED FOR

A Revelation in Tone—Volume—Clarity

The Kellogg Symphony Reproducer brings the broadcasting studio into your very room, so realistic is its reproduction.

Piano music, the most difficult to reproduce, sounds so natural that you are completely carried away by its beauty.

Vocal selections retain all of the tone colorings of the artist.

Orchestra music is indeed a recreation, every instrument can be heard, clear and full.

Magnetic diaphragm control—used exclusively in the Kellogg unit is the new principle that performs wonders in radio reproduction.

Nothing like it at twice the price—\$25.00 each


At your dealers—Hear one today.



KELLOGG SWITCHBOARD & SUPPLY COMPANY
Chicago, Ill.

Back of Each Instrument

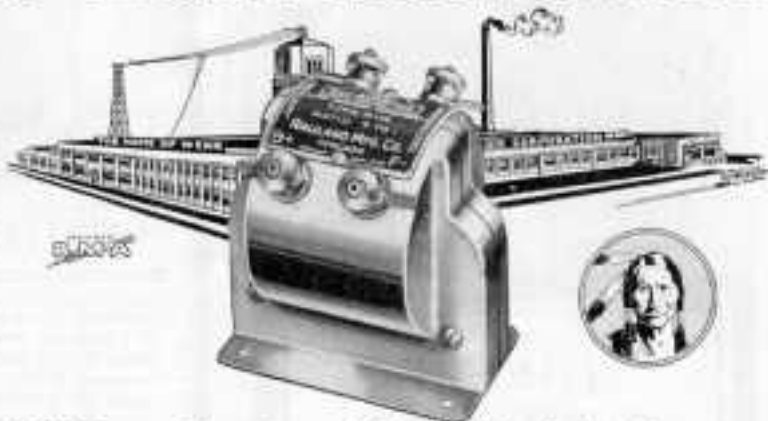The assurance of reliable performance, which you have always felt when buying an ALL-AMERICAN Transformer, is now increased by a knowledge that it is the product of one of the largest and most completely equipped factories in America devoted exclusively to radio products.



The RADIO KEY BOOK—new edition—is a practical handbook for all who wish to enjoy modern radio at its best. Send 10 cents—coin or stamps—for the KEY BOOK.

ALL-AMERICAN RADIO CORP., E. N. RAULAND, Pres., 4217 Belmont Ave., Chicago

ALL-AMERICAN

Largest Selling Transformers in the World

The Great
Manufacturers'
Exposition
Attended by
Leading
Jobbers and
Dealers

The Official ¹⁹²⁵ RMA Show
THE SECOND
RADIO WORLD'S FAIR
NEW YORK CITY

U. J. HERRMANN, MANAGING DIRECTOR
SEPTEMBER 14th to 19th
MONDAY NOON TO SATURDAY MIDNIGHT
ENTIRE EXHIBITION ON GROUND FLOOR
IN THE LARGEST HALL IN THE WORLD
258th Field Artillery Armory

NEW YORK OFFICE:
230 FIFTH AVENUE
NEW YORK CITY





THEY'RE PERMANENT

AmerTrans govern the quality of speech or music—in a capable and permanent manner. Once tried in a set, you know they will stay there—they must if you want all that is to be had in quality reception.

Regardless of new apparatus and low priced parts, AmerTrans continue to be recognized as one of the *best* transformers because they are efficient and permanent.


*AmerTrans are sold only through Authorized Amer-
Tran Dealers. Buy them by
the Pair!*

AmerTran is made in two types—A F 6, ratio 5:1, and A F 7, ratio 3½:1. Price either model \$7.00.

AMERICAN TRANSFORMER
COMPANY

173 Emmet Street, Newark, N. J.

AMERTRAN



Patent
April
21-41
Other
Patents
Pending

Geared 80 to 1

Adaptable to coarse or fine tuning, the infinite precision of the Accuratune brings in all stations within the scope of your set clearly, strongly, and with little effort on your part. Easily substituted in a few minutes for ordinary dials without alteration of your set. An essential accessory.

Write for descriptive folder

MYDAR RADIO CO.
11 CAMPBELL ST., NEWARK, N. J.

ACCURATUNE



Pat. Pending

The Crowning Refinement

No matter how good a set you have designed, the Chelten Midget can make it better—by permitting finer tuning. Shunted across terminals of main condenser, it gives hair-line adjustment. No redesigning—just mount it anywhere on panel. No additional losses introduced. Requires only 1½" space.

Bridge meas. max esp.	00045 MID. Frequency	
meas. max esp.		\$150
00007 MID.		150

CHELTEN

Low Loss Midget Vernier

Remember, the Chelten is the ORIGINAL Midget variable condenser. All others are imitations. Useful also as a STABILIZER in most circuits.

Write for full information

CHELTEN ELECTRIC COMPANY
Stanton Ave. & Rockland Street
PHILADELPHIA

Why set manufacturers should use Radion Panels

Appearance Radion Panels have a high-polished, satin-like finish that enhances the attractiveness of any set. They come in two colors, standard black and Mahoganite; the Mahoganite panels with their beautiful coloring and graining give an effect that is especially distinctive. Radion takes engraving beautifully.

Efficiency. Built to order exclusively for radio purposes, Radion meets the most exacting tests for high insulating qualities. Surface leakage and dielectric absorption have been proved to be exceptionally low. This is an aid in getting distance and volume.

Convenience Another feature that recommends Radio Panels to the manufacturer is the ease with which they can be cut, sawed and drilled. Edges are smooth and even; holes are trim and clean-cut. Radion does not chip as do other panel materials.

We invite manufacturers' inquiries

WE ARE always glad to co-operate with manufacturers in meeting their requirements. We invite them to send us samples or specifications of panels and other insulated parts of radio instruments or radio sets. Radion is used on the leading makes of condensers.

AMERICAN HARD RUBBER COMPANY
Dept. M N 4, 11 Mercer St., New York City

RADION


The Supreme Insulation

Compensated Multiple



Variable Condenser

PROVEN!

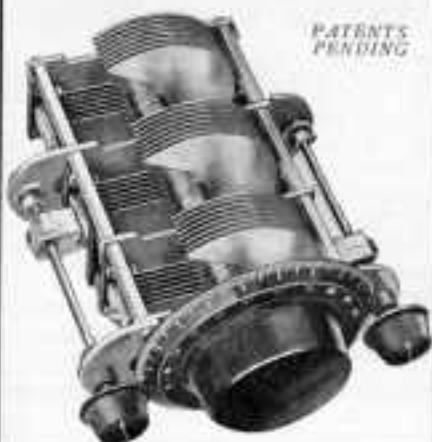

ONLY REAL AND PRACTICAL ONE DIAL CONTROL UNIT

SINCE our announcement of this new Multiple Condenser, they have been given the most thorough and impartial tests throughout the country and reports confirm our statement that it is the only practical one dial control unit. Evenly matched and balanced; 100% perfect electrically and mechanically. Can be built into any T.R.F. circuit, saves space and cost of making any set. It is a straight line, low loss unit, making the sharpest tuning quick and easy.

Capacity .00035 mfd. Per Unit

\$13.50 Including Bakelite Dial and Two Knobs

Order a Sample To-Day

MANUFACTURERS

Submit us your specifications and get our prices before placing your parts contracts for the coming season.

United Scientific Laboratories, Inc.
82 Fourth Ave., New York

More Amplification Per Stage
 Sharper Tuning---Delicate Sensitivity
 Rugged Construction



95%
 AIR
 DIELECTRIC

The amazing performance of the Aero Coil as a V.I.F. Transformer is due to its latest patented construction. Aero Coil has much lower distributed capacity, much lower high frequency resistance, and its exact, ideal electrical coefficients cannot be duplicated by any other type of inductive construction.

Try a set of Aero Coils. Note how they tune into stations not a "hazy" signal! How delicately sensitive they are to the weakest signals! Low transmission in the amplification as compared with other inductances which you have used! \$3.00 each, or \$15.00 complete set of three with brackets, screw, chassis and full constructional instructions.

AERO PRODUCTS, INC.
 SUCCESSORS TO
HENNINGER RADIO MFG. CO.
 217 N. Desplaines St., Chicago
 MANUFACTURERS: Write for a sample set of AERO Coils and for prices.

The New "Better Tuning" Control

Write for Complete Information
 Different Better



Fully
 Protected by
 Patent Pending

\$2.50

Bremer-Tully MFG. CO.
 532 S. Canal St., Chicago

NEW
CARTER
"IMP" LOCK SWITCH
 Pat. 1-30-33

Quarter turn filament switch with "Off and On" Name Plate



Locks and protects your set

3 keys furnished with each switch

75c

In Canada: Carter Radio Co., Limited, Toronto

Write for catalogue of other CARTER Products

Carter Radio Co.
 300 S. MICHIGAN AVENUE
 CHICAGO, ILL., U.S.A.

Any Dealer can supply

Mold Bakelite At Lower Cost—

—with the new H-P-M HIGH PRESSURE HYDRAULIC AUTOMATIC PRESS. The most important development for the plastic molding industry!

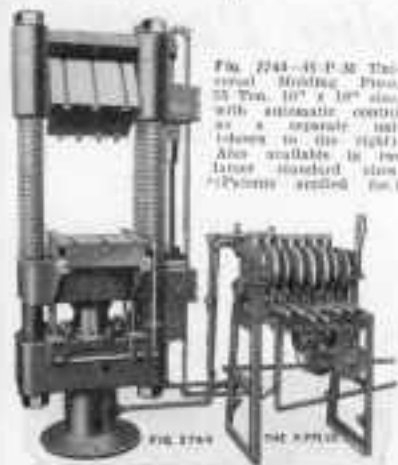


FIG. 1744—H-P-M Thermal Molding Press, 25 Tons, 10" x 10" die, with automatic control as a separate unit (shown to the right). Also available in two sizes—standard size. *Polymers applied (see.)

CONSIDER THESE FEATURES:

1. The timing of every portion of the molding cycle automatically controlled.
2. Labor costs are reduced—one inexperienced operator serves a group of these H-P-M Presses.
3. Rejects due to faulty timing are eliminated—with the "human element" removed.
4. Idle time between operations reduced—the revolving head and sliding table place both halves of the die in the most convenient position for cleaning, reloading, placing of inserts, etc.
5. Molded parts are ejected automatically—of course.


Send for complete data.

THE HYDRAULIC PRESS MFG. CO.

251 Lincoln Ave., Mount Gilead, Ohio

H-P-M HIGH PRESSURE HYDRAULIC PRESSES

"FOR YOUR PRESSING NEEDS"

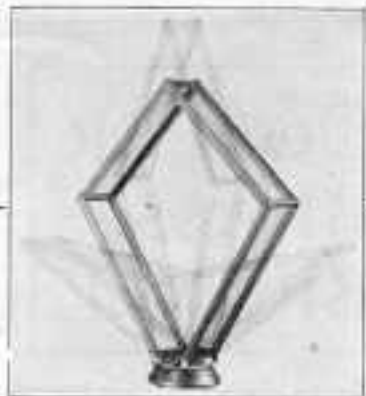

Reg. U. S. Pat. Off. Infringements Thereof
Prohibited.

THE AALCO LOOP

The latest addition to the line of quality radio accessories. All parts metal, hand-crafted finished with all metal parts highly polished—the artistic appearance of the Aalco Loop is easily matched by its superior design and exceptional performance. Length 24 in., Normal Height 30 in., Wavelength Range 170-600 meters.

IT'S DIFFERENT. Different both in appearance and operation. Adjustable in any position with wire always taut—You will find the new Aalco Loop greatly adds to the performance of your set. If your Dealer cannot supply you send Money Order and we will ship direct. Price \$11.

JOBBERS Write for Discount
AALCO RADIO LABS.
6338 Cottage Grove Ave., CHICAGO.

RADIO PANELS

Decorated, Drilled,
Engraved

Poster & Co. is Bakelite headquarters. Specialization for years in Panel work has built up a national reputation. Many of the largest radio manufacturers are now using Poster's Perfect Panels.

Improved Equipment for
Machining

All the latest developments in machining are now available to you through "The Oldest and Largest Complete Panel Service House in America."
Phone or write nearest office.



Poster & Co. Inc.
26-B BARCLAY ST., NEW YORK CITY
721 FULTON STREET CHICAGO


COPPER BRASS BRONZE

Indispensable for Radio Parts

Data concerning the application of Copper, Brass and Bronze to radio manufacture, and information about sources of supply furnished by

**COPPER & BRASS
RESEARCH ASSOCIATION**
25-Broadway - New York

Compact and Efficient

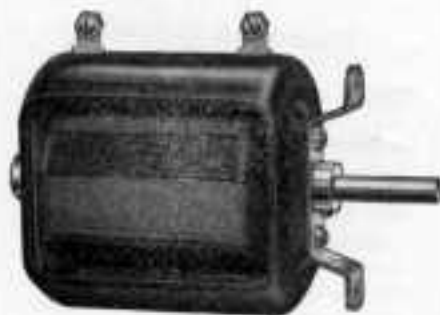

General Radio Type 269 Variometer

Price \$5.00

The outstanding features of the type 269 variometer are its size and its efficiency of operation.

It is much smaller than the average variometer which gives it a decided advantage where compactness and portability of the set are considerations.

Terminals are very accessible and a soldering lug is provided for using split variometer connections.

Stator and rotor forms are of genuine moulded bakelite, wound with green silk covered copper wire. Bearings are accurate and smooth running.

The ratio of maximum to minimum inductance is 10 to 1.

GENERAL RADIO Co
CAMBRIDGE, MASS.

RX-1 Dataprints

Save \$1.25—Get a set of RX-1 dataprints FREE by subscribing to Radio Engineering Magazine for one year. The cost of the Dataprints plus a year's subscription, is \$3.25. Send in \$2.00 for a year's subscription and the RX-1 Dataprints will be mailed to you without charge.

**ONLY
DATA-
PRINTS
ARE
SO
COMPLETE**

1. Parts list
2. All constants
3. Battery connections
4. Picture wiring diagram
5. Schematic wiring diagram
6. Terminal checking list
7. Step-by-step instructions
8. Names of manufacturers
9. Full-size panel patterns
10. Accuracy in every detail

RX-1 results can be obtained only with RX-1 design, results never before considered even possible with a non-regenerative circuit, results which cannot be equalled with a set which oscillates. Be the first in your city to have the complete information given in the RX-1 Dataprints.

No special equipment except the coils and Sudion, no complicated wiring, no expensive parts—but RESULTS.

COMPLETE SET OF FIVE FULL-SIZE DATAPRINTS..... \$1.25

BLUEPRINTS for STANDARD SETS

- REINARTZ RECEIVER, one of the most popular models ever described in Radio Engineering. A splendid set for all around broadcast work. Type 3300, 4 sheets..... \$1.00
- HAYNES TUNER, known as the "One Thousand Miles for Fifteen Dollars" set. 2 sheets..... .50
- BROWNING-DRAKE 199, the standard B-D design, built for dry cell operation. It is equipped with four UV-99 or C-299 types. Type 2000, 3 sheets..... 1.25
- BROWNING-DRAKE 201-A, using one UV-199 and three 201-A tubes, arranged to operate on a 6-volt storage battery. Type 6600, 6 sheets... 1.25
- BROWNING-DRAKE FIVE, equipped with a 3-step resistance coupled amplifier. Uses one UV-199 and four 201-A's. The finest of all the B-D receivers. Type 7500, 5 sheets..... 1.25
- COTTON SUPER, peer of long distance receivers, and the simplest of all eight-tube supers in design and construction. Type 7200, 7 sheets.... 1.75
- 2-STEP AF AMPLIFIER, designed for use with any type of receiving set where additional amplification is required. Type 3100, 3 sheets..... .75

M. B. SLEEPER, Inc. Technical
Publisher

A-52 Vanderbilt Avenue

New York City

DIRECTORY

OF CONCERNS MANUFACTURING MATERIALS EMPLOYED IN RADIO EQUIPMENT

BRASS AND COPPER

- American Brass Co., The., Waterbury, Conn.
American Smelting & Refining Co., 120 Broadway, New York, N. Y.
Anaconda Copper Mining Co., 21 Broadway, New York, N. Y.
Bridgport Brass Co., East Main St., Bridgport, Conn.
Chase Metal Works, Waterbury, Conn.
Cooklin, T. E., Brass & Copper Co., Inc., 54 Lafayette St., New York, N. Y.
Dallat Brass & Copper Co., 820 Orleans St., Chicago, Ill.
Hungerford, U. T., Brass & Copper Co., 80 Lafayette St., New York, N. Y.
Hussey, C. G., & Company, 2530 Second Ave., Pittsburgh, Pa.
Merchant & Evans Co., Washington Ave., at 21st St., Philadelphia, Pa.
Michigan Copper & Brass Co., Detroit, Mich.
National Brass & Copper Co., The, Lisbon, Ohio.
New England Brass Co., Park St., Taunton, Mass.
New Jersey Wire Cloth Co., The, Trenton, N. J.
Osborn Co., J. M. & L. A., The, 1541-51 E. 20th St., Cleveland, Ohio.
Paper and Textile Machinery Co., The, Sandusky, Ohio.
Richards & Co., Inc., Battery Wharf, Boston, Mass.
Rinne Brass & Copper Co., Dominick & Busch Sts., Rome, N. Y.
Scruff Manufacturing Co., Waterbury, Conn.
Taunton New Bedford Copper Co., 267 West Water St., Taunton, Mass.

DIE CASTINGS

- Bazehart Bros. & Spindler, 1300 W. Mason St., Chicago, Ill.
Duehler Die-Casting Co., Court & 9th Sts., Brooklyn, N. Y.
Krone-Schek Die Cast & Mfg. Co., 686 W. Austin, Chicago, Ill.
Republic Die-Casting Co., 128 Mott St., New York, N. Y.
Sael Co., H. G., 1800 Montrose, Chicago, Ill.
Stewart Mfg. Corp., 4533 Fullerton, Chicago, Ill.

LACQUER

- Arizona Lacquer Mfg. Co., 7 1/2th St., Brooklyn, N. Y.
Bakelite Corp., 247 Park Ave., New York, N. Y.
Celluloid Zapon Co., 200 Fifth Ave., New York, N. Y.
Casper & Co., Charles, 194 Worth St., New York, N. Y.
DuPont Chemical Wks., Wilmington, Del.
Durable Products Co., East Liverpool, Ohio.
Eastman Kodak Co., Rochester, N. Y.
Ergman Lacquer Mfg. Co., Brooklyn, N. Y.
Hls. Varnish Corp., Brooklyn, N. Y.
Kallbein Corp., 250 Fifth Ave., New York, N. Y.
Little Falls Chemical Co., Little Falls, N. Y.
Maxx & Waltham, 45 John St., New York, N. Y.
Nikolas & Co., G. J., 1235 Van Buren St., Chicago, Ill.
O'Brien Varnish Co., South Bend, Ind.
Waukegan Chemical Co., Waukegan, Ill.
Zeller Lacquer Mfg. Co., 342 Madison Ave., New York, N. Y.

MICA

- American Mica Wks., 6 Hammer St., New York, N. Y.
Ashville Mica Co., Biltmore, N. C.
Blake, Edward, New Dale, N. C.
Brand & Co., Wm., 27 E. 25th St., New York, N. Y.
Carolina Mineral Co., Peshaw, N. C.
Chicago Mica Co., Valparaiso, Ind.
Consolidated Mica Co., So. Bend, Ind.
Deberet Mfg. Co., Vandewater & Duncan Aves., St. Louis, Mo.

- Fillion, S. O., 98 Murray St., New York, N. Y.
Frig & Co., L. L., 325 W. Ohio St., Chicago, Ill.
Ford Mica Co., New York, N. Y.
Hirsch Mica Co., 1067 Blushing Ave., Brooklyn, N. Y.
Fuse-Liberty Mica Co., 73 Long Wharf, Boston, Mass.
Keene Mica Products Co., Keene, N. H.
Macalloy Co., Boston, Mass.
Meinowsky, Inc., Jersey City, N. J.
Mica Co. of Canada (N. Y.) Inc., Masena, N. Y.
Mica Insulator Co., 68 Church St., New York, N. Y.
Mica Mfg. Co., 134 Johnson St., Brooklyn, N. Y.
Murrel & Co., Eugene, 58 Church St., New York, N. Y.
New England Mica Co., Waltham, Mass.
New England Minerals Co., Boston, Mass.
New York Mica & Mfg. Co., Ashburn, N. Y.
Proctor Mica Co., Bubb, K., 204 Monmouth Bldg., Chicago, Ill.
Radio Mica Products Co., 155 E. 43rd St., New York, N. Y.
Rogers-Pryatt Shellac Co., 41 Water St., New York, N. Y.
Schonemaker Insulation Co., A. O., 30 University Place, New York, N. Y.
Storrs Mica Co., Orange, N. Y.
U. S. Mica Mfg. Co., Oak Park (Forest Park), Ill.
Watson Bros., Boston, Mass.

MOLDED INSULATION

- Alden Mfg. Co., Springfield, Mass.
American Elec. Co., Inc., 22 Prospect St., Newark, N. J.
American Insulator Corp., New Freedom, Pa.
Bakelite Corp., 247 Park Ave., New York, N. Y.
Ballston Insulating & Composition Co., Ballston Spa, N. Y.
Belden Mfg. Co., 23108 S. Western Ave., Chicago, Ill.
Bell Mfg. Co., 11 Elkins St., Boston, Mass.
Bennington Radio & Electric Co., Bennington, Vt.
Boston Molding Co., Boston, N. J.
Boston Rubber Mfg. Co., Boston, N. J.
Colasta Co., Housick Falls, N. Y.
Compo-Site, Inc., Newark, N. J.
Commercial Tube & Elec. Co., Meriden, Conn.
Cutter-Hammer Mfg. Co., Milwaukee, Wis.
Durrand Mfg. Co., 213 Chestnut St., Newark, N. J.
Electrose Mfg. Co., 40 Washington St., Brooklyn, N. Y.
Formica Insulation Co., 4614 Spring Grove Ave., Cincinnati, Ohio.
Garfield Mfg. Co., Garfield, N. J.
General Insulate Co., 1600 Atlantic Ave., Brooklyn, N. Y.
Hopewell Insulation & Mfg. Co., Hopewell, Va.
Insulation Products Co., Pittsburgh, Pa.
International Insulating Corp., Elyria, O.
Inaway Insulation Co., New Brunswick, N. J.
Johns-Pratt Co., Hartford, Conn.
Kurz-Kasch Co., Dayton, O.
Mack Molding Co., Little Falls, N. Y.
National Lead Co., 111 Broadway, New York, N. Y.
Niagara Insul-Bak-Societies Co., Albany, N. Y.
Northern Industrial Chemical Co., 11 Elkins St., South Boston, Mass.
Proven Composition Products Corp., Milford, Conn.
Radio Products Mfg. Co., 301 S. Jefferson St., Chicago, Ill.
Rayson Moulding Co., 5 Beacon St., Boston, Mass.
Reynolds Spring Co., Jackson, Mich.
Ridgely Trimmer Co., Springfield, O.
Scranton Button Co., Scranton, Pa.
Shaw Insulator Co., Irvington, N. J.
Sizem Co., Bridgeport, Conn.
Specialty Insulation Mfg. Co., Housick Falls, N. Y.
Sphibrot Elec. Co., 192 High St., Newark, N. J.
Sou-Rubber Co., Harborton, O.
Telendurco Co., Ambler, Pa.
Waterbury Button Co., Waterbury, Conn.
Watertown Mfg. Co., Watertown, Conn.
Westinghouse Elec. & Mfg. Co., East Pittsburgh, Pa.

PANEL MATERIAL

American Hard Rubber Co., 11 Marner St., New York, N. Y.
Diamond State Fibre Co., Bridgeport, Pa.
Fibroc Insulation Co., Valparaiso, Ind.
Furnica Insulation Co., Cincinnati, Ohio.
Goodrich, B. F. Co., Akron, Ohio.
Hood Rubber Co., Watertown, Mass.
National Vulcanized Fibre Co., Wilmington, Del.
Spaulding Fibre Co., North Tonawanda, N. Y.
United States Rubber Co., 58th St. and Broadway, New York, N. Y.
Westinghouse Elec. Mfg. Co., Pittsburgh, Pa.

SCREW MACHINE PRODUCTS

American Metal Works, Stenton Ave. & Rockland St., Philadelphia, Pa.
Blake & Johnson Co., Waterbury, Conn.
Chapman Machine Co., Terryville, Conn.
Chicago Screw Co., Chicago, Ill.
Cincinnati Automatic Mach. Co., Cincinnati, O.
Columbia Metal Prod. Co., 361 E. Ohio St., Chicago, Ill.
Darton Auto Specialty Co., Dayton, O.
Eby Mfg. Co., H. H., Philadelphia, Pa.
Economy Screw Corp., 5215 Ravenswood Ave., Chicago, Ill.
Golde Mfg. Co., Inc., 100 S. Third St., Brooklyn, N. Y.
Habbell, Inc., Harvey, Bridgeport, Conn.
New England Screw Co., 44 Farnsworth St., Boston, Mass.
Olson Mfg. Co., 56 Commercial St., Worcester, Mass.
Pawtucket Screw Co., Pawtucket, R. I.
Perry-Fay Co., Elyria, O.
Phell Mfg. Co., 5705 Roosevelt Rd., Chicago, Ill.
Progressive Mfg. Co., Torrington, Conn.
Screw Machine Products Corp., 1011 Eddy St., Providence, R. I.
Sovell Mfg. Co., Waterbury, Conn.
Stein & Co., 297 Washington St., Newark, N. J.
Thomaston Mfg. Co., Thomaston, Conn.
Trumbull Elec. Mfg. Co., Plainville, Conn.
Waterbury Mfg. Co., Waterbury, Conn.

SOLDER

American Solder & Flux Co., Philadelphia, Pa.
Belden Mfg. Co., 23108 S. Western Ave., Chicago, Ill.
Chicago Solder Co., 4212 Wrightwood Ave., Chicago, Ill.
Dielectric Mfg. Co., Vandeventer & Duncan Aves., St. Louis, Mo.
National Lead Co., 111 Broadway, New York, N. Y.
Solderall Co., 129 Sussex Ave., Newark, N. J.

WIRE, MAGNET

Aame Wire Co., New Haven, Conn.
Allied Magnet Wire Corp., Indianapolis, Ind.
American Brass Co., 21 Broadway, New York, N. Y.
American Electrical Works, Phillipsdale, R. I.
American Enamelled Magnet Wire Co., Muskegon, Mich.
American Insulated Wire & Cable Co., Chicago, Ill.
American Steel & Wire Co., Chicago, Ill.
Ansonia Electrical Co., Ansonia, Conn.
Atlantic Insulated Wire & Cable Co., Rome, N. Y.
Belden Mfg. Co., 4695 W. Van Buren St., Chicago, Ill.
Bradford Kyle & Co., Plymouth, Mass.
Chicago Insulated Wire & Mfg. Co., Chicago, Ill.
Crescent Ins. Wire & Cable Co., Trenton, N. J.
Dudley Mfg. Co., Fort Wayne, Ind.
General Elec. Co., Schenectady, N. Y.
Goldmark Co., James, 83 Warren St., New York, N. Y.
Harvey Wire Co., 277 Sherman Ave., Newark, N. J.
Kelllogg Switchboard & Supply Co., Chicago, Ill.
Maring Wire Co., Muskegon, Mich.
Marion Insulated Wire & Rubber Co., Marion, Ind.
Massachusetts Elec. Mfg. Co., West Lynn, Mass.
Philmore Mfg. Co., 105 Chambers St., New York, N. Y.
Providence Insulated Wire Co., Providence, R. I.
Rockbestos Products Co., New Haven, Conn.
Ro-Ming's Sons, Co., John A., Trenton, N. J.
Rome Electrical Co., Rome, N. Y.
Rome Wire Co., Rome, N. Y.
Standard Alloy Wire Co., Elizabeth, N. J.
Strand & Sweet Mfg. Co., Winsted, Conn.
Super-Insulated Wire Co., Plymouth, Mass.
Whetzel Insulated Wire Co., Bridgeport, Conn.
York Insulated Wire Works, 1737 Broadway, New York, N. Y.

(Continued from page 398)

50 we put the upper coil of the R.F. transformer at maximum coupling and adjusted the lower coil to stop oscillations. The lower coil, when turned to increase the coupling, stops oscillating. Below 50 degrees on the dials we reduced the coupling at the upper coil, and set the lower one at an angle of 45 degrees.

The volume from the set is tremendous. Altho the set has only four tubes, there is no reason for adding another tube since, even on stations several hundred miles away, the Musicone is given as great a load as it can handle.

This set, while simple enough to be operated by the ordinary B.C.L., will appeal strongly to the more experienced set builders as a splendid outfit for long distance reception. While the set was under test, we tried the experiment of receiving as many stations as possible out of those listed in the New York Sun's daily radio program. In 45 minutes we heard and verified by the station call twenty-four of the broadcasters listed in the program, ranging from New York to Chicago on wavelengths from 276 to 526 meters.

Do S. L. F. Condensers Eliminate Squeals?

FROM some source or other many radio men seem to have the idea that the use of S. L. F. condensers will eliminate heterodyne squeals. The S. L. F. condenser serves several important and useful purposes but it cannot affect squeals caused by regenerative receivers, either to make the effect less pronounced or more so.

Heterodyne squeals come from three sources, beat notes set up between your station and the broadcast transmitter, when your own set is adjusted to an oscillating condition, beat notes set up between an outside receiver in an oscillating condition, and your own when it is also oscillating, and between an outside receiver and the broadcasting station, even tho your own set is not oscillating. The last is the most common cause of whistling or heterodyning interference and has nothing to do with your own set.

SM SUPER PARTS



Entirely silver-plated! And a new standard has been set for low-loss condensers! It is only logical that the new Silver-Marshall S-L-W Condensers should be the first to be so built. Their losses are lower than many laboratory standards—their mechanical design unique and original. The S-L-W plates mean *real* selectivity and station separation.

No. 205 .0005	\$6.00
No. 206 .00035	1.75
No. 207 .00025	2.50

S-M Type 210 and 211 Trans- formers



S-M 210 and 211 transformers are known as the finest intermediate transformers ever made. They were an important feature of the receiver built entirely of S-M parts, that took the grand sweepstake prize at the recent Los Angeles Radio Show.

Price, each \$8.00

Send 4c in stamps for Free Circulars of S-M Products, and reprints of article from Radio Engineering describing the remarkable new Super-Autodyne Receiver.

Silver-Marshall, Inc.

108 S. Wabash Avenue
CHICAGO, ILL.

DURHAM *Metallized* High Resistors



for special Work

Leaping into popularity on account of its accuracy and permanence, the DURHAM Metallized filament has been in great demand for all high resistance purposes—couplers, by-passes, and B power units. Special designs have been worked out to meet special conditions. Above is shown a pig tailed unit. No doubt our engineers can help you, too—if you'll just write!

INTERNATIONAL RESISTANCE Co.

728 Sansom St., Philadelphia

Oh boy
KESTER
Rosin Core
Radio SOLDER

Save in Size and Simple
APPROVED BY RADIO ENGINEERS
A LANTANA BRAND
CHICAGO SOLDER COMPANY

4224 Wrigleywood Ave., Chicago, U.S.A.

Organized and Healthful Learning System
Approved by Federal Education Board
YOUR DEALER CAN SUPPLY YOU

Announcing the Balkite Trickle Charger at \$10 and the new Balkite "B" at \$35

A



Balkite Trickle Charger

Charges both 4 and 6 volt radio "A" batteries at about .5 amperes. Usable in 3 ways: (1) As a regular charger with a low capacity storage battery for sets now using dry cells. (2) With storage battery sets of few tubes. (3) As a "trickle" or continuous charger for storage battery sets of as many as 8 tubes. See 5 1/2 in. long, 2 3/4 in. wide, 5 in. high. Operates from 110-120 AC 60 cycle current.

Manufacturers are offering switches which turn on Balkite "B" and turn off the charger when you turn on your set. This makes the current supply for both circuits automatic.

Price \$10

West of Rockies, \$10.30
Slightly higher in Canada



Balkite Battery Charger

The most popular battery charger on the market. It can be used while the radio set is in operation. Charging rate 2.5 amperes. Operates from 110-120 AC 60 cycle current. Special model for 50 cycles.

Price \$19.50

West of Rockies, \$20
Slightly higher in Canada

The Balkite Battery Charger is today the most popular charger on the market. It is the only charger commonly used while the set is in operation. Balkite "B" II is also well known. It replaces "B" batteries entirely and supplies plate current from the light socket.

We now announce the Balkite Trickle Charger at \$10. This low-rate charger is especially adapted to use with sets of relatively low "A" current requirements—any dry cell set and storage battery sets with few tubes. Owners of dry cell sets can now make a very compact and economical installation with a Balkite Trickle Charger and a low capacity storage battery of the type offered by battery manufacturers this fall.

We also announce the new Balkite "B" at \$35. This new model will serve sets of five tubes and less. It fits in your present "B" battery compartment.

Noiseless—No bulbs—Permanent

All Balkite Radio Power Units are entirely noiseless in operation. They have no moving parts, no bulbs, and nothing to adjust, break or get out of order. Each is a permanent piece of equipment with nothing to replace. They require no other attention than the infrequent addition of water. They require no changes or additions to your set. They are guaranteed to give satisfaction.

Manufactured by
FANSTEEL PRODUCTS COMPANY, Inc.
North Chicago, Illinois

FANSTEEL
Balkite
Radio Power Units

B



Balkite "B"

Eliminates "B" batteries. Supplies plate current from the light socket. Operates with either storage battery or dry cell tubes. Keeps "B" circuit always operating at maximum efficiency. Requires no attention other than adding water about once a year.

Will serve any set of 5 tubes or less. Occupies about same space as 45 volt dry "B" battery. Operates from 110-120 AC 60 cycle current.

Price \$35

Slightly higher in Canada



Balkite "B" II

Same as the new Balkite "B" but will fit any set including those of 10 tubes or more. Operates from 110-120 AC 60 cycle current. Special model for 50 cycles.

Price \$55

Slightly higher in Canada

The Gould Unitpower is equipped with a special Balkite Radio Power Unit


Who designed the first jack?

The first jack built exclusively for radio was designed by Louis G. Pacent, for the past eighteen years an outstanding figure among radio engineers.

Today, ten different models of Pacent jacks and twenty five other Pacent radio units are used by forty leading set manufacturers. Investigate Pacent Radio Essentials for yourself. You can soon prove their superiority.

Ask your dealer to show you the complete line of Pacent Parts.

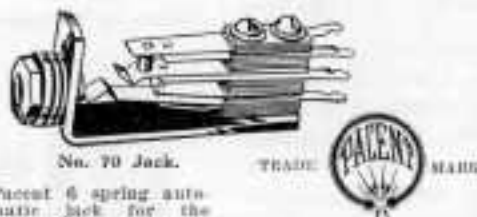You'll find our illustrated catalog helpful in making your selections. Write for it today.



No. 70 Jack. Pacent's spring automatic jack for the latest R. F. circuits.

PACENT ELECTRIC COMPANY, Inc.

91 Seventh Ave., New York City.

Washington	Birmingham	Detroit
Chicago	Jacksonville	San Francisco
Buffalo	Boston	St. Louis
Minneapolis	Philadelphia	Pittsburgh


Canadian Licensee: White Radio, Limited, Hamilton, Ont.

Pacent

RADIO ESSENTIALS

MANUFACTURERS!

New Design

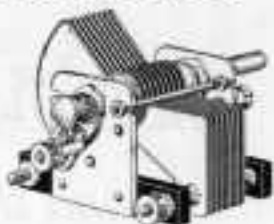

Stops Trouble with Condensers

At last, set manufacturers can obtain a condenser that can be relied on to perform exactly as the circuit designer calculated. Our new model fulfills every requirement of the latest ideas in radio engineering. Minimum losses consistent with good construction. Permits open tuning on low waves. Sturdy. Compact. Will stand the most critical tests for either electrical or mechanical soundness. Capacities guaranteed.

Manufacturers: Write for sample and price

RADIO CONDENSER CO.
CAMDEN, N. J.

World's Largest Exclusive Radio Condenser Plant

EASTERN Pickle Bottle COILS



EASTERN Pickle Bottle Coils represent the greatest advance in low loss coil design.

All tests have proven them to be unequalled in efficiency. No matter what circuit they are used in, the quality and purity of tone is at once noticeable—and their sheer beauty of design adds distinction to any radio set.

Designed for perfect performance in the following circuits: ROBERTS' circuit (\$4.50), SUPERDYNE (\$6), BROWNING-DRAKE (\$8), THREE CIRCUIT (\$6), TUNED R. F. (\$2 each).

At your dealer's or direct, Postpaid.

EASTERN COIL CORP.

22 Warren St. Dept. R. E. New York

RX-1 Durrant offers you the big development of the year

Puzzle 'em?

Well, you'll be just as much perplexed yourself when you first operate the RX-1 as your friends will be when you show them the set—Because the RX-1 not only does things which no set in radio history ever did, but it does things which engineers have so long assumed couldn't be done that they forgot to try it.

A Pioneer Radio Development Although the RX-1 circuit has been available to the public for only two months, it is already making radio history as the first high-power non-regenerative receiver ever produced, a pioneer development in methods and results.

When you tune in the RX-1 you'll go back to the hook-up to find out how, with such simple parts, it is possible to achieve such extraordinary characteristics in tuning, volume, and quality.

Sounds like old stuff? It does when you read the words, but not when you hear the results, because there's a reason for each of these three factors. Take the tuning—just like a crystal set, and it's done with only two dials. It tunes that

No Mystery About RX-1 Results way because it's non-regenerative. You set the dials and stop. No wiggling a rheostat, no breaking into oscillations, no squeals and distortion. Those things just can't happen in a non-regenerative set.

Volume? Of course you can't help gauging volume by the number of tubes, but the RX-1 will fool you

The RX-1 is the only successful non-regenerative set ever developed in the history of radio, the set which accomplishes the things until now thought impossible.

there. Don't try to bet against this set for you'll lose. A quick turn of the dials and it will reach right out and bring in the station you want with volume that will make five tubes turn

blue with shame. Reasons? Here you are—While tuned R.F. sets use 6 turns at most, for the primary of the R.F. transformers, RX-1 has a 20-turn primary giving an efficiency which two stages of the ordinary type cannot equal. Add to that the sensitivity of the D-21 Sodian and you have the answer to RX-1 volume.

And the quality—A non-regenerative R.F. amplifier and detector cannot distort. A stage of resistance coupled amplification first delivers perfect quality to a high-pep transformer coupled circuit which cannot be over-loaded by the strongest station, and which brings up weak ones in a way that will astound you.


Simplest of All Designs Now about building the RX-1. There are only three special items required, the two RX-1 transformers and a Sodian tube. These Durrant can supply; the rest of the parts you have already, or can get them easily. A complete wiring diagram is furnished with each set of transformers.

Set of RX-1 transformers, \$7.50 postpaid. Type D-21 Sodian detector tube, \$5.00 postpaid. Add 10c for registry to insure safe delivery.

DURRANT RADIO, Ltd.

C-52 Vanderbilt Avenue
New York City New York

They All Need Union Radio Tip Jacks

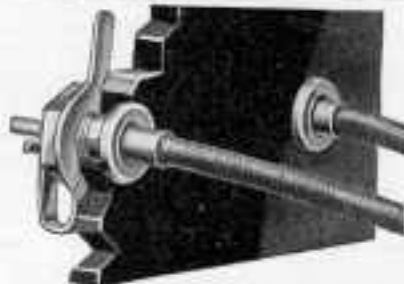

It's Profitable to Sell Them
at **25c** a Pair

The hook-up man and the amateur and professional set builders, now use Union Radio TIP JACKS to replace binding posts. They are regular equipment in many of the best sets on the market. Handy for temporary connections, ideal for permanent mountings. Nickel plated—nothing to chip, break or get lost. Firmly grip all wires from No. 11 to No. 24, B. & S. gauge.

Three Sizes for all Mountings

Packed in "self-sealing" counter capsules of 1/12, 1/8 and 1 gross pairs. Type A for panels 3/16" to 1/4" thick. Type B for panels, cabinet walls and partitions 5/16" to 3/8" thick. Type C for panels up to 1/2" thick.



IDENTIFICATION TAGS—Black red blue caps with various designations as "H" and many others. Threaded on brass wire they tell which is which and save time of tracing-up. A valuable safeguard. Two sizes, 1/2" diameter, will take any wire up to 1/4". Packed 100 to a box of one designation only. Retail price \$1.00.

TUBE SOCKETS—Bladed, acoustically shielded, bakelite. Provision for air exhaust openings. Bakelite-based bakelite die. Fits standard tubes. Retail price 75c.

DIAL ADJUSTERS—Precision ultimate adjustment of dials. Very necessary for fine tuning. Retail price 50c.

RETAILERS WHOLESALE
SET MANUFACTURERS

Write for samples, literature and price lists.
Ask for illustrated catalogue N.



Makes Any Set Better

No matter what kind of a radio set you operate, the addition of Stasco Rheostats is bound to improve your tuning efficiency.

Get rid of that annoying flickering of tubes that injures clear reception. The exclusive feature of a spring contact plate, makes possible permanent contact. That means greater distance and more volume. It's a sure winner.

Stasco Rheostats

are made of bakelite only. All styles. All ohmages.

Made chiefly for the man who wants a highly efficient part at the lowest possible cost.

Manufacturers: Add Stasco Rheostats to your sets and watch your orders increase. It improves tuning efficiency and is backed by a guarantee.

Write for further particulars.

SHEFFIELD TRIMMING & STAMPING CORP.


211 Centre St. New York City

Also manufacturers of Vernier Dials, Beels, Potentiometers, Gold Leaf Mountings, Battery Clips, etc.

UNION-RADIO-CORPORATION
124 W. SUSSEX AVENUE, NEWARK, N.J.
NEW YORK OFFICE: 116 WEST 32nd STREET.
8888

Samson T&A Assembly

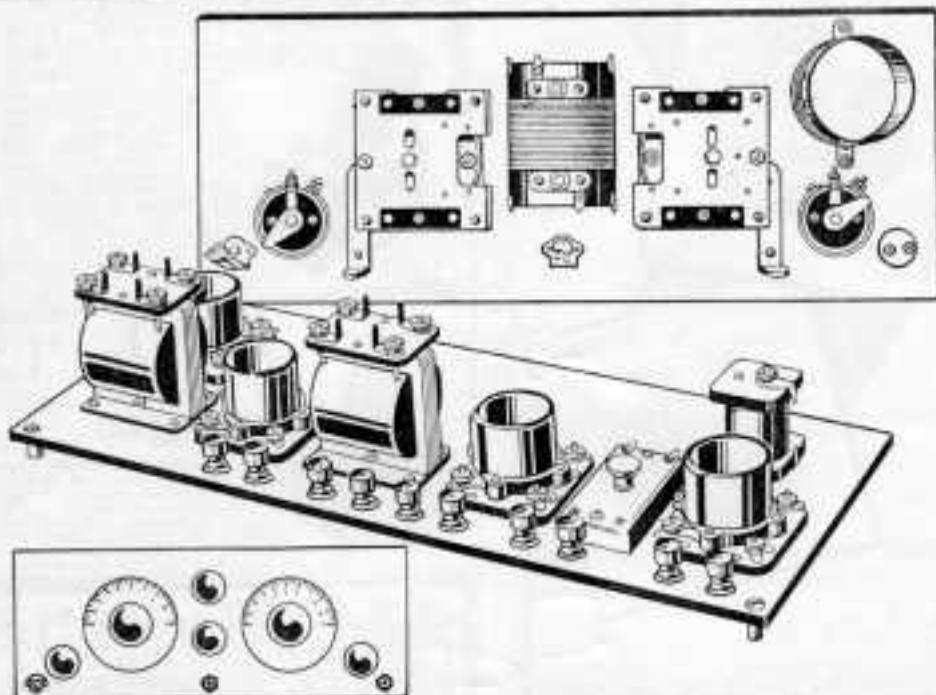AN engineered assembly of quality parts designed for fidelity of reproduction, utmost selectivity, simplicity of operation and nerve like sensitivity, offering to the dealer and constructor a custom made set which will meet the most exacting requirements.




Samson Radio products are sold through Authorized Dealers and Distributors

Write for information to

SAMSON ELECTRIC COMPANY

CANTON, MASS.

Manufacturers since 1882

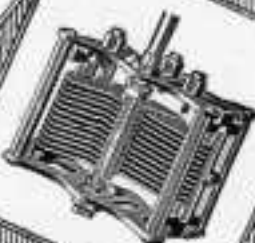

Amsco Quality Parts

The standard of excellence by which all others are judged. Used by many of the leading set manufacturers as well as by foremost radio engineers. They are laboratory instruments.

At dealers everywhere.
Free literature on request.

AMSCO PRODUCTS, Inc.
416 Broome Street New York

FIL-KO-LEAK

SCIENTIFICALLY CORRECT
VARIABLE GRID LEAK

\$1.75

\$2.60

in
Canada

its calibrated



Fil
Standard
Component

See your FIL-KO-LEAK just as you do your other tuning units. Get station and power heard before clear up distortion and increase volume. You need FIL-KO-LEAK resistance to exact terms of the coupling (A to 2 megohms through a two-hole in the panel. It's also calibrated for base-board mounting.) Resistance, elements, contacts, assembly, not affected by atmospheric conditions, wear or aging. Unconditionally Guaranteed.

FIL-KO-STAT

SCIENTIFICALLY CORRECT RADIO RHEOSTAT

\$1.50

\$2.10

in
Canada

with Battery Switch



Turn your tube circuit with FIL-KO-STAT and volume stays just as you heard before. Get greater distance, louder signals, sharper tuning, freedom from hiss and noise. It is the only rheostat that enables you to set maximum audibility with any type of tube in any knob-up (full resistance, 50 ohms). The new and improved model is fitted with battery switch that attaches to the regular mounting screws. Unconditionally Guaranteed.

FIL-KO VARIABLE RESISTOR

SCIENTIFICALLY CORRECT
INDIVIDUALLY CALIBRATED TO ORDER

\$1.50

\$2.10

in
Canada



Stop distortion and increase volume when connected across the secondary of audio frequency transformer. Also for use in resistance coupled amplification. Individually calibrated from 1,000 to 250,000 ohms. Comes with brackets for base board or transformer mounting. Unconditionally Guaranteed.

FIL-KO-ARRESTER

SCIENTIFICALLY CORRECT
RADIO LIGHTNING ARRESTER

\$1.50

\$2.10

in
Canada

with the 100% Guarantee



Eliminate distortion or prevent your set from burning, with a guarantee in any case \$1.00 or to repair your set, should it be damaged through faulty operation of the arrester.
The "Inchella" shield keeps dust, moisture, etc., from the Bakelite insulator, preventing leakage losses from aerial to ground. This makes certain that all radio impulses reaching the antenna pass through your set, avoiding maximum distortion.

Listed as Standard under the re-examination service of the National Board of Fire Underwriters' Laboratories.

Send 2c stamp to Dept. RE 325 for descriptive literature on Improved Reception.

D. X. INSTRUMENT CO., Harrisburg, Pa.

The Tide Has Turned!

Today, wherever you go—to set manufacturers, radio engineers, dealers, experimenters, or amateur set builders—you hear the praises sung of Daven Resistance Coupled Amplifiers. Why?

Because years of research, experimentation, and investigation have conclusively proven that Resistance Coupled Amplification is the best known method of procuring **AMPLIFICATION WITHOUT DISTORTION**.

Recognizing the *shortcomings* of the average present day vacuum tube, Daven has created a special tube for specific use in Daven Resistance Coupled Amplifiers—the **DAVEN HIGH MU VACUUM TUBE**. This tube is recommended solely for use with Daven amplifiers. It is not a "Jack of all trades" tube.

Folder descriptive of Daven High Mu and Daven Power Tubes may be obtained from your dealer or we will mail one direct.

Daven Super
Amplifier
\$15.00

High Mu Tubes
Mu-20 84.00
Mu-6 3.00

Daven 3-Stage
Amplifier Kit
\$9.00


Daven Products are sold only by good dealers.

For valuable information on Resistance Coupled Amplification, read the **RESISTOR MANUAL**.
From Your Dealer 25c or postpaid 35c.

The Slave of Music

DAVEN RADIO CORPORATION

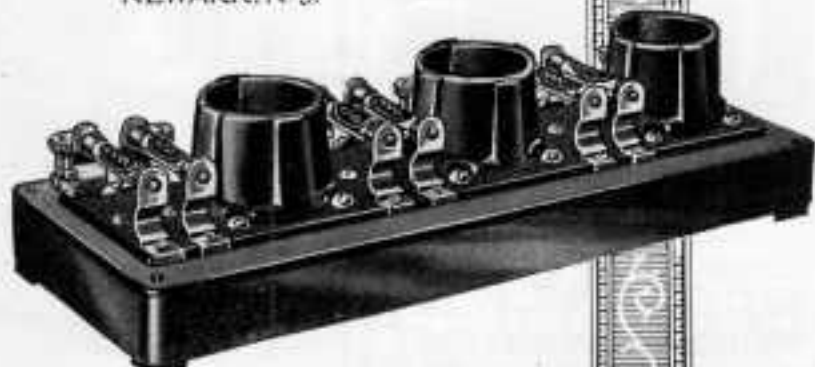TRADE MARK "Resistor Specialists" INC. U.S. PAT. OFF.
NEWARK, N. J.



Why


Set Manufacturers are Standardizing on DXL Condensers --- the New Single End Plate Model C

When the engineers of many set manufacturers from all parts of the country specify DXL Condensers for the new Sets --- when they select DXL from the hundreds offered them --- it means they are satisfied with the sound, sensible principles of design upon which DXL Condensers are built.

Light, yet sturdy and rigid --- Simple, yet a marvel of precise workmanship --- Instant admiration is won for Model C --- just one end plate, yet any engineer will vouch for its absolute rigidity. Like all DXL Straight Line Condensers Model C is guaranteed to run true to specifications and careful workmanship in every single shipment. Buy DXL with perfect confidence.

Samples to reputable manufacturers shipped instantly.

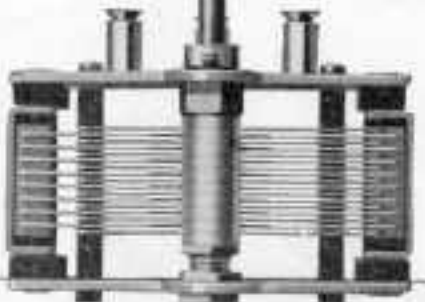Deliveries throughout our season guaranteed with acceptance of order.



Individual Set Builders

DXL Condensers will make your set perform at maximum. Ideal for low wave lengths. Details and prices on request.

TRADE **DXL** MARK

RADIO CORPORATION

5777 Stanton Ave., Detroit, Mich.

Obsolete



Take the **"GUESS"** Out of Tube Control

\$1.10 Everywhere

with

Amperite automatically controls tube current, eliminates hand rheostats, filament meters, guessing and all tube worry. Simplifies wiring, tuning and operation. Permits the use of any type of tube or any combination of tubes. Tested and used by more than 50 set manufacturers and in every popular construction set.

RADIALL COMPANY
Dept. R.E.-2, 50 Franklin St., New York City



Write for **FREE** Hook-ups

AMPERITE

The "SELF-ADJUSTING" Rheostat

At your dealer **\$1.25**



WALBERT made it first!

TUNE-IN More Stations!

GET those far-away ones quickly, easily, clearly --- just replace your dial with

WALBERT

WUNIVERNIER

WALBERT MFG. CO., CHICAGO

Iⁿd M REGISTRY

The men whose names are listed below are prepared to handle all emergency work, take care of batteries, and replace tubes. Their charge is \$1.50 per hour, not including travelling time except to unusual distances.

The charge for listing in this section is 50c. for one month, \$2.00 for six months, \$3.00 for twelve months, payable in advance. The * indicates that we have received letters from six set owners stating that the man after whose name the * appears has handled their I and M work satisfactorily.

A REGISTRY OF RADIO INSTALLATION and MAINTENANCE SERVICE MEN WHO INSTALL, MAINTAIN, and REPAIR RADIO EQUIPMENT

Conn., South Norwalk—A. GHIRARDI*
Rowayton. Tel. Noz. 2724

D. C., Washington—A. C. BURG
U. S. Soldiers' Home. Tel. Col. 750 Br. 41

Ill., Chicago—WEILAND & CO.
6711 Stewart Ave. Tel. 1124 Normal

Mass., Boston—H. A. NICKERSON
201 Devonshire St. Tel. Cong. 5156

Mich., Detroit—J. E. JOHNSON
91 Gladstone Ave., Tel. Empire 8581J

Minn., Minneapolis—GEO. A. BECKER
4709 Wentworth Ave. Tel. Locust 6291

N. Y., New York—APEX RADIO CO.
123 Liberty St. Tel. Rector 3176

N. Y., New York—HERBERT MULLER
954 Lexington Ave. Tel. Rhldr. 3905
154 Nassau St. Beek. 8040

N. Y., New York—RADIO CONST. LABS.*
71 W. B'way. Tel. Walker 2143

O., Kent—KLADAG RADIO LABS.*
Kline Bldg. Tel. 127

SCREW MACHINE PRODUCTS & SPRINGS

Wm. STEINEN & CO.

297 Washington St.

NEWARK - - - N. J.

TEL. MARKET 9077

We have five 1924 Bound Volumes of RADIO ENGINEERING in stock available for those who are interested in keeping a complete file of our publication. The price for two weeks only is \$2.00 each.

M. B. SLEEPER, INC.,
52 Vanderbilt Ave.,
New York, N. Y.

MADE IN ALL STATES



B.M.S.
FAN-TAIL-JACK

NOT APPLICABLE FOR

Connections cupped and spread apart

For Easy Soldering
Mfg. by BROOKLYN METAL STAMPING CO. INC.
718 Atlantic Ave., Brooklyn, N.Y.

AT ALL GOOD DEALERS



Your Trade Deserves the Best

NO Panel Marks
No Inks
No Vibration

GENUINE IMPREGNATED ELEMENT

TRIPOT

Your own name or trade-mark if desired

Registered Trade-Mark
ELECTRIC CO., INC.
16 HUDSON ST., NEW YORK CITY

Another tribute to
New England's Radio Craftsmen



The
product
←
The
tribute
←

"I am very well pleased with my NATIONALS and their fine Velvet Vernier Dials," writes Mr. Surber.



Write for
Bulletin 106 R.E.

National Company
Engineers and Manufacturers
110 Brookline Street
Cambridge • • Mass.

Sole manufacturers of the genuine and justly famous Brooking-Drake Transformers. Patents pending.

SURBER'S HARDWARE

DEALER
HARDWARE - FURNITURE - IMPLEMENTS
STONE - LINOLEUM - PAINT

FRANKLIN SQUARE
CAMBRIDGE 15, MASS.

The
National Company, Inc.,
Cambridge, Mass.

Dear Sirs:

I have at hand ten December V.S.'s, and note the National's arrangement of components. The points shown are indeed remarkable but I believe that you would be interested in knowing of my use.

I use a 2-tube live-line tuner, with two National receivers. With this receiver I have heard better on both the Decade and vernier dials, savings out of \$10.00. I have carried on the day communication with 3K4, 3K4B, 3K4C and 4K4B. I have also heard 3K4F and the other variations. These stations run close to 5,000 miles.


I am very well pleased with my Nationals and their fine Velvet Vernier Dials.

Having the National Company the best built and continued success, I am

Very truly yours,

Stanley Surber
Stanley Surber, S-207

The ACME condenser has these advantages

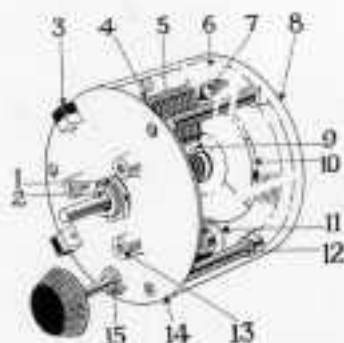

All parts are of non-rusting metal, except steel bearing, which is covered with nickel-plated protective surface. End plate capacity is .002010 m.f., full capacity is .0095 m.f.

Price \$6.50

Distinctive Points

1. Bezel to brass cone bearings adjustable.
2. Lock nut for bearing.
3. Highest grade hard rubber Dielectric in that part of the field to prevent losses.
4. Brass separator to which both rotary and stationary plates are soldered, making continuous circuit for each.
5. Brass silver-plated plates; rotary plates logarithmic.
6. Dust-proof covering.
7. Stops at extreme end of movements.
8. Coiled connections between shaft and heads allowing lubrication of bearings.
9. Brass separator to which both rotary and stationary plates are soldered, making continuous circuit for each.
10. Counterweight which balances rotary plates.
11. Noiseless friction Vernier control seven to one ratio.
12. Brass separators, to prevent twisting and to take strain off Dielectric.
13. Panel mounting holds for 120 degree spacing.
14. Metal heads.
15. Steel bushing to prevent wear on Vernier shaft.

Low loss, sharp tuning --- practically all currents on antenna can now be used

IT remained for Acme—manufacturers of the famous Acme transformers—to perfect the “lowest loss” Condenser. The Acme Engineers have been working for two years to bring out a condenser which would give to Radio Experimenters sharp tuning and minimum losses.

The new Acme Condenser has these fundamental advantages and also has many new improvements in structure and equipment. See the illustration with explanation, and, for more information, write to us for booklet—“Amplification without Distortion,” which contains many diagrams and helpful hints on how to build and get the most out of a set. Enclose 10 cents in stamps.

ACME APPARATUS COMPANY
Dept. H-7 Cambridge, Mass.

ACME ~for amplification

SCREW MACHINE PRODUCTS

WITH

UNIFORM PRECISION



Fifty years of experience plus the latest obtainable equipment together with an efficient organization and a sincere desire to give our customers quality and service we feel places us in a position to offer you a satisfactory source of supply on screw machine products.

Steadfast standards maintained by rigid inspection assures you a clean cut product that you can have complete confidence in for quick and accurate assembly.

Brass parts acid dipped clean and bright. Send us samples or blue prints for quotation.

CHICAGO SCREW COMPANY

1026 So. Homari Avenue

Chicago, Ill.