

RADIO & TELEVISION NEWS

AUGUST
1953
35 CENTS
In Canada 40¢

IN THIS ISSUE

FILM FOR TV

BUILDING THE E-V REGENCY

KNOW YOUR 1953 EMERSON
TV RECEIVERS

A SIMPLE
ANTI-FLUTTER CIRCUIT

SIX-METER EMERGENCY
TRANSCEIVER


ELECTRONIC
"BUTLER AND BABYSITTER"

CHOOSE THE PROBE
TO FIT THE TEST

HOME SECURITY RADIO

ELECTRONICS FOR THE
YACHTSMAN

(See Page 67)

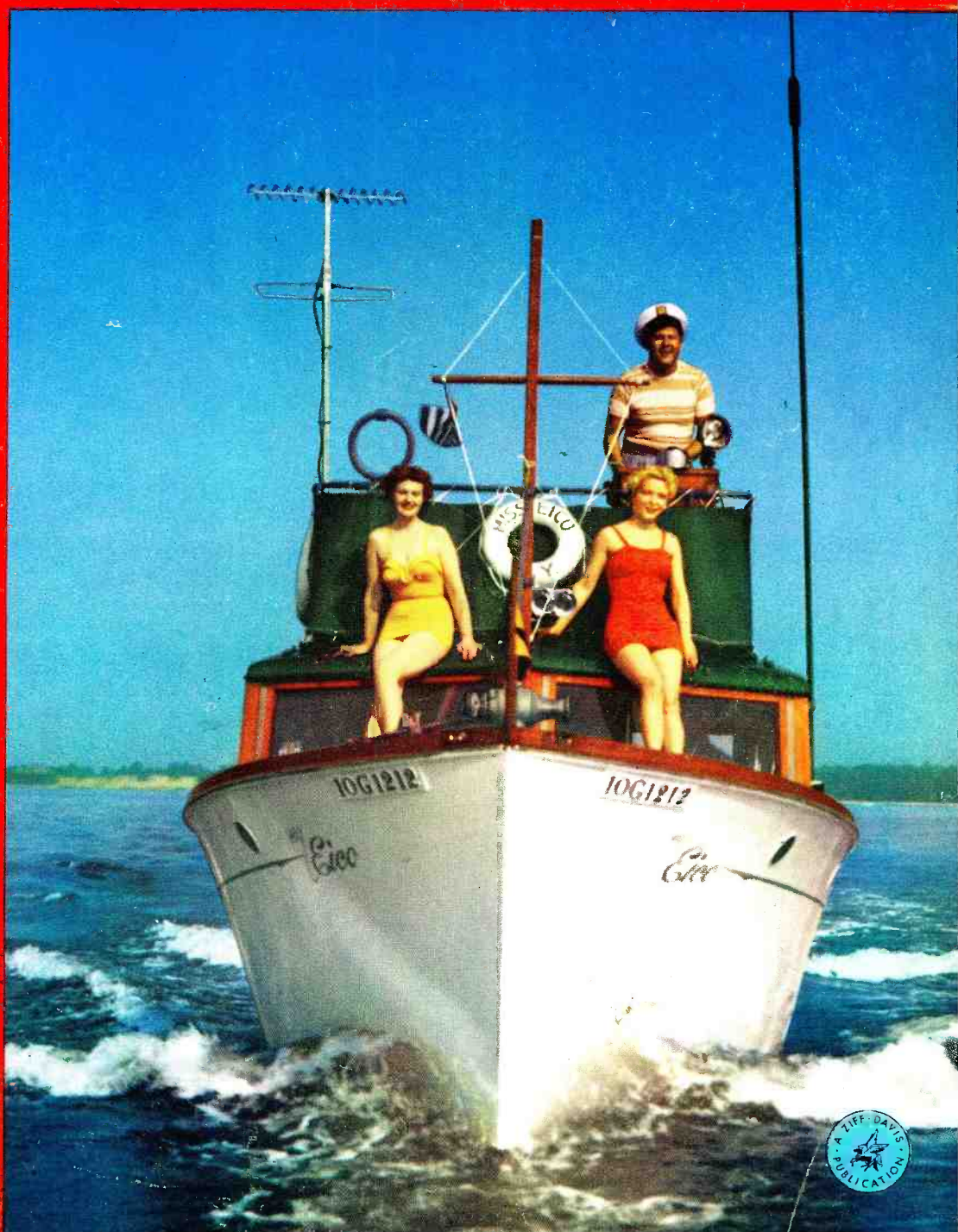

A serviceman's

"best friend" is an RCA Tube

An RCA Tube starts working for you from the instant the customer first sees the familiar red, black, and white carton. You have her confidence from the start, because she knows and respects the RCA trademark.

But the big payoff to you begins when the tube goes to work. For, experience has proven that the superior quality of RCA Receiving Tubes and Kinescopes is your best measure of protection against premature tube failures. With RCA Tubes, you can be sure the job is well done.

Helping you to safeguard your reputation is a vital, everyday service of RCA Tubes. And that protection is yours at no extra cost.



**UNLOCK
THE DOOR TO
BIGGER
PROFITS**


Here's *your* key to better business... RCA's dynamic Dealer Identification Program. Ask your **RCA Tube Distributor** for your copy of the colorful, 16-page booklet "A Magic Pass-Key to Customer Confidence." It tells you how you can become a Registered Dealer... and get *extra* sales benefits.



RADIO CORPORATION of AMERICA
ELECTRON TUBES


HARRISON, N. J.

NEW

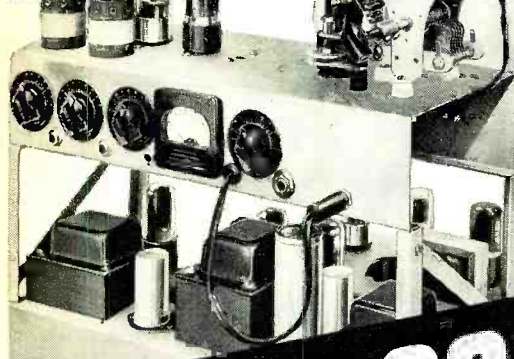

I'LL TRAIN YOU FOR YOUR FCC LICENSE

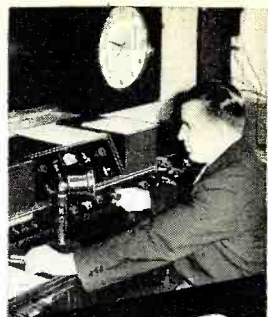A Federal Communications Commission Commercial Operator's License puts you in line for a good job in Radio or Television Broadcasting, Police, Marine, Aviation, Two-way, Mobile or Micro-wave Relay Radio. Mail coupon below for 64-page book FREE. It will give you complete facts about my NEW Communications course.



YOU BUILD THIS TRANSMITTER

with parts I send. With this Transmitter you practice how to put a station "on the air." You perform procedures demanded of Broadcast Station Operators, conduct many experiments, make many practical tests.


LEARN COMMUNICATIONS by PRACTICING at Home in Spare Time




YOU BUILD this Transmitter Power Supply used in the basic experiments in RF and AF amplifiers, frequency multipliers, buffers, etc.



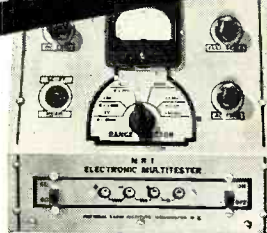YOU PRACTICE setting up code, amplitude and frequency modulation circuits (put voice, music, etc., on "carrier signals" you produce). You learn how to get best performance.



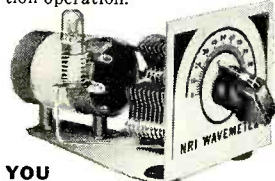YOU MEASURE current, voltage (AC, DC and RF), resistance and impedance in circuits with Electronic Multimeter you build. Shows how basic transmitter circuits behave; needed to maintain station operation.



YOU BUILD this Wavemeter and use it to determine frequency of operation, make other tests on transmitter currents.

Get Practical Experience on Circuits Common to Radio & TV

Ever think HOW FAST Radio-Television Communications is changing, developing, growing? Have you considered what this amazing progress can mean to you? Even without Television the industry is bigger than ever before. 105 million home and auto radios, 2900 Radio Broadcasting Stations, 108 TV Stations with 1800 more now authorized. Expanding use of Aviation and Police Radio, Micro-Wave Relay, Two-Way Radio for buses, taxis, etc. makes opportunities for Communications Technicians and FCC Licensed Operators. New jobs, more jobs for beginners! Better jobs, better pay for experienced men!

Television Is Today's Good Job Maker

In 1952, over 18,000,000 homes had TV sets. More are being sold every day. The "freeze" on building new TV stations has been lifted. The time to act is NOW! Start learning Radio-TV communications. America's fast growing industry offers good pay, a bright future, security. If you are a beginner, my course can help you get FCC License, prepare for the job you

J. E. SMITH, President National Radio Institute Washington, D. C.

For 38 years, the leader in training men for Radio-Television.



MY COURSE INCLUDES TELEVISION

want. If you've had some training in Radio or Radar, or as a Licensed Operator, my course modernizes, increases the value of your knowledge.

Includes New Developments

Mail coupon now for facts about my practical course in Radio-Television Communications. Let me send you my FREE book. See the nine big Kits of Parts I send that "bring to life" theory you learn. You get practical experience by working on circuits common to both Radio and Television; also lessons on TV principles. Read about the Transmitter you build and operate, about the Electronic Multimeter you get. All equipment is yours to keep.

My graduates are filling jobs, making good money in both Radio and Television. Remember, the way to a successful career in Television is through experience in Radio.

Mail Coupon for Book FREE

Send today! See what my Communications course is like. Find out how I get you ready for a brighter future, better earnings, more security in Radio-Television. Send coupon now in envelope or paste on postal. NO OBLIGATION, NO SALESMAN WILL CALL! My book, sent to you FREE, tells the full story. J. E. SMITH, President, Dept. 3HE, National Radio Institute, Washington 9, D. C. Our 39th year.

Training Leads to Jobs Like These

- | | | |
|---|--|---|
| BROADCASTING
Chief Technician
Chief Operator
Power Monitor
Recording Operator
Remote Control Operator | GOVERNMENT RADIO
Operator in Army,
Navy, Marine Corps,
Coast Guard
Forestry Service
Dispatcher
Airways Radio Operator | AVIATION RADIO
Plane Radio Operator
Airport Transmitter Operator |
| SHIP AND HARBOR RADIO
Chief Operator
Assistant Operator
Radiotelephone Operator | POLICE RADIO
Transmitter Operator
Service Technician | TELEVISION
Pick-Up Operator
Voice Transmitter Operator
TV Technician
Remote Control Operator |

TRAINED THESE MEN



"My position with WNBT is video control engineer on the RCA color project. I owe a lot of my success to your textbooks."—Warren Deem, Malverne, N. Y.



"I am a technician at WTOP in Washington and I like it very much. Most of my radio knowledge was from N.R.I."—John Britto, Hyattsville, Md.



"A former employer recommended N.R.I. training. Now employed as transmitter operator at WKBO."—Albert Herr, New Cumberland, Pa.

AVAILABLE TO VETERANS UNDER G.I. BILLS

MAIL NOW-BOOK FREE

MR. J. E. SMITH, President, Dept. 3HE National Radio Institute, Washington 9, D. C.


Mail me Sample Lesson and 64-page Book, FREE. (No salesman will call. Please write plainly.)

Name Age

Address

City Zone State

VETS write in date of discharge

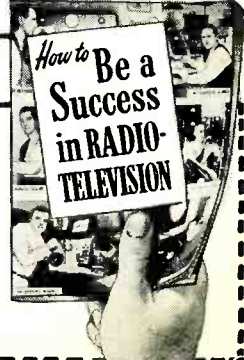

RADIO & TELEVISION NEWS is published monthly by the Ziff-Davis Publishing Company at 64 E. Lake St., Chicago 1, Ill. Entered as second-class matter, July 21, 1948, at the Post Office, Chicago, Ill., under the act of March 3, 1879. Authorized by Post Office Department, Ottawa, Canada, as second-class matter. SUBSCRIPTION RATES: Radio & Television News—one year, U. S. and Possessions, Pan-American countries, and Canada \$4.00; all other foreign countries \$5.00; Radio-Electronic Engineering Edition—one year, U. S. and Possessions, Pan-American countries, and Canada \$6.00; all other foreign countries \$7.00. Postmaster—Please return undelivered copies under form 3589 to 64 E. Lake St., Chicago 1, Ill.

Editor and Asst. Publisher
OLIVER READ, D.Sc., WIETI

Managing Editor
WM. A. STOCKLIN, B.S.

Technical Editor
H. S. RENNE, M.S.

Service Editor
CHARLES TEPFER

Amateur Radio Editor
N. ROSA, WINOA

Assistant Editors
P. B. HOEFER
M. C. MAGNA

Television Consultant
WALTER H. BUCHSBAUM

Short-Wave Editor
KENNETH R. BOORD

Staff Artist
FRANK SAYLES

Draftsmen
A. A. GANS, W2TSP
J. A. GOLANEK

Advertising Manager
L. L. OSTEN

Midwest Adv. Manager
JOHN A. RONAN, JR.

Western Adv. Manager
JOHN E. PAYNE

RADIO & TELEVISION NEWS

Reg. U.S. Pat. Off.

First in
radio-television-electronics

Average Paid Circulation over 200,000

Radio News Trademark Reg. U. S. Pat. Office • Television News Trademark Reg. U. S. Pat. Office.

CONTENTS

AUGUST, 1953

New TV Grants Since Freeze Lift.....	16
Film for TV.....	Henry J. Seitz 35
A Simple Anti-Flutter Circuit.....	John K. Frieborn 38
Choose the Probe to Fit the Test.....	Art Liebscher 40
Electronic "Butler and Babysitter".....	Sidney Lipman 43
Transistor Physics Simplified (Part 2).....	S. P. Gentile & P. J. Barotta 46
Troubleshooting TV High-Voltage Supplies.....	Milton H. Lowe 48
Building the E-V Regency.....	Howard Souther 50
Know Your 1953 Emerson TV Receivers.....	Bron Kutny 52
Six-Meter Emergency Transceiver.....	Robert L. Hankey, W3OBC, & Maurice P. Johnson, W3TRR 56
Adapting V.O.M. as a Field Strength Meter.....	Elbert Robberson 59
A Home Security Radio.....	H. G. Bourne & E. J. Cordier 60
A Low-Cost Crystal Calibrator.....	G. L. Countryman, W3HH 63
High-Quality Record Reproduction at Low Cost.....	Francis H. Yonker 64
Mac's Radio Service Shop.....	John T. Frye 66
Electronics for the Yachtsman.....	Harry R. Ashley 67
Modernize Your AM-FM Tuner.....	Lt. Col. Byron E. Hargrove 80
Hints and Kinks for Mobileers.....	Jack Najork, W2HNN 84
New "Pay-as-You-Watch" System.....	93
New TV Stations on the Air.....	112
Radio-TV Service Industry News.....	120
Service Hints on Emerson TV Sets.....	126



COVER PHOTO: The "Miss Eico", a 31-ft. motor launch carrying an extensive array of radio gear. The boat offers remote control of its radiotelephone system on the flying bridge. (Ektachrome by Jay Seymour)

ZIFF-DAVIS PUBLISHING COMPANY

Chairman of the Board and Publisher
WILLIAM B. ZIFF

President
B. G. DAVIS

Secretary-Treasurer
G. E. CARNEY

Vice-Presidents
H. J. MORGANROTH

Production Director
LYNN PHILLIPS, JR.

Advertising Director
H. G. STRONG

Circulation Director

BRANCH OFFICES

CHICAGO (1)

64 E. Lake St., AN 3-5200

LOS ANGELES (14)

StatterCenter, 900 Wilshire Blvd., Mich. 9856

DEPARTMENTS

For The Record.....	The Editor 8	Short-Wave.....	K. R. Boord 68
Spot Radio News.....	16	Technical Books.....	70
Within the Industry.....	24	Manufacturers' Literature.....	94
What's New in Radio.....	99		



COPYRIGHT 1953

(All Rights Reserved)

ZIFF-DAVIS PUBLISHING COMPANY

Editorial and Executive Offices

366 Madison Ave., New York 17, N. Y.

VOLUME 50 • NUMBER 2



Member
 Audit Bureau of
 Circulations

SUBSCRIPTION SERVICE: All communications concerning subscriptions should be addressed to Circulation Dept., 64 E. Lake St., Chicago 1, Ill. Subscribers should allow at least four weeks for change of address.

CONTRIBUTIONS: Contributors are advised to retain a copy of their manuscripts and illustrations. Contributions should be mailed to the New York Editorial Office and must be accompanied by return postage. Contributions will be handled with reasonable care, but this magazine assumes no responsibility for their safety. Any copy accepted is subject to whatever adaptations and revisions are necessary to meet the requirements of this publication. Payment covers all author's, contributor's, and contestant's rights, title, and interest in and to the material accepted and will be made at our current rates upon acceptance. All photos and drawings will be considered as part of the material purchased.

NOW...from D.T.I.'s MILLION DOLLAR TRAINING CENTER



Learn to master **TELEVISION**

RADIO - ELECTRONICS
by getting **EVERYTHING YOU NEED!**

**NOW—
get training
to suit your NEEDS**

**TAKE YOUR
CHOICE**

Come to
D.T.I.'s
great **CHICAGO
LABORATORIES**

...one of the Nation's FINEST!

Now, in the heart of the nation's TV Center, you can get all of your preparation in D.T.I.'s big, modern, wonderfully equipped training laboratories. Loads of commercial equipment and ample, well qualified instructors help you get a thorough, practical preparation in the **SHORTEST POSSIBLE TIME**. Part time student Employment assistance can help you pay your way while in training.

EMPLOYMENT SERVICE

As soon as you complete either the Chicago Laboratory or Home Training, you'll find D.T.I.'s grand Employment Service ready to help you start earning real money. Get full facts. Mail coupon today.

MILITARY SERVICE: If subject to military service, the training information we have for you should prove very helpful. Mail coupon today.

**89 WAYS TO
EARN MONEY
IN TELEVISION
RADIO ELECTRONICS**


ACT NOW! MAIL COUPON TODAY
Get this publication FREE!

DeFOREST'S TRAINING INC. RN-8-J
2533 N. ASHLAND AVE., CHICAGO 14, ILL.
I would like your Opportunity News Bulletin showing "89 Ways to Earn Money In Television-Radio-Electronics"; also, complete facts about the training opportunity made possible by your organization.

Name _____ Age _____
Address _____ Apt. _____
City _____ Zone _____ State _____

America's amazing multi-billion dollar Television field now offers you a chance of a lifetime to get started toward a grand job or your own business. With TV station limit now raised from over 100 to 2053, Television is headed for almost every community. Mail coupon today. See how you may prepare to cash in on the coming TV BOOM.

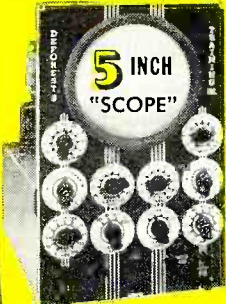**Get ALL of your training
AT HOME!...including setting
up your own HOME LABORATORY**



ABOVE: You build and keep this big 5 INCH commercial-type oscilloscope — one of the most useful test units used in TV today.



21 INCH

Build and keep this BIG DTI engineered TV set—easily converted to U.H.F.



Use 16 mm. MOVIES Only D.T.I. provides you with the loan of visual training movies at home to help you master important basic points faster... easier... better!

"ONE OF AMERICA'S FOREMOST TELEVISION TRAINING CENTERS"
— Established 1931 —




DeFOREST'S TRAINING, INC.
AFFILIATED WITH
DeVRY Technical INSTITUTE
CHICAGO 14, ILLINOIS

PICKERING

PROFESSIONAL AUDIO EQUIPMENT

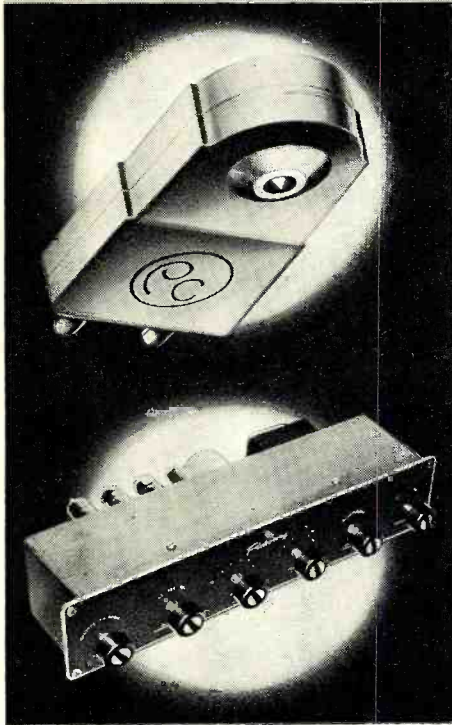BALANCED COMPONENTS / MAXIMIZE PLAYBACK PERFORMANCE



PICKERING CARTRIDGES . . .

are the choice of audio engineers throughout the world. They are universally acclaimed because of their high output, wide range performance and low distortion. They are used wherever a fine cartridge is required in radio stations, recording studios and for purposes of quality control by leading record manufacturers.


MODEL 410 AUDIO INPUT SYSTEM . . .

is designed to provide a complete audio control center. Model 410 may be used in any high quality playback system. Three input channels are provided—one for magnetic cartridges and 2 "flat" channels for other audio circuits. A 3-position equalizer network is built into the magnetic cartridge channel and provides accurate equalization for LP, AES and 78 rpm recording characteristics. Separate bass and treble controls are also provided. These are of the step-type and permit bass and treble adjustments in 2 db increments. The tone control circuits are intended to compensate for record characteristics and for listener-environment acoustical conditions. They are not intended to compensate for amplifier and/or loudspeaker deficiencies. Model 410 is intended for use with the highest quality professional type playback equipment. The output of the Model 410 is fed from a cathode-follower circuit and will work into any high quality audio or line amplifier having a high impedance input. It may also be used with a transformer for the purpose of feeding a 500 ohm line. Because of its flexibility, low noise and low distortion level, it is ideally suited for bridging and monitoring purposes and for critical listening applications.



THE MODEL 190 ARM . . .

is designed primarily for use with microgroove records. Its design has been recognized by leading audio engineers as that which incorporates all of the desirable tracking characteristics. Analysis has shown that for maximum performance with LP records the vertical mass of the moving arm element must be held to a minimum and further, that the arm must be counterbalanced about the vertical axis. This permits minimum stylus or tracking force and provides maximum record life. The Model 190 Arm embodies these all important features necessary for proper microgroove record playback.

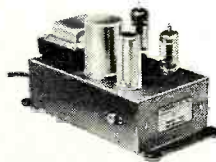

MODEL 230H EQUALIZER-PREAMPLIFIER . . .

is unique in its accuracy of equalization and frequency response. The intermodulation distortion is .2 per cent at normal output level. It is intended for use with high quality amplifiers having gain and tone controls. When used with the Pickering Model 132E Record Compensator the 230H is ideal for radio station and recording studio use and for applications requiring accurate low noise and distortion free playback.



MODEL 132E RECORD COMPENSATOR . . .

is designed to be used in conjunction with a magnetic cartridge preamplifier such as the Pickering 230H or any preamplifier which provides 6 db per octave bass boost. Six playback positions are incorporated:

- 1—European 78 rpm Records
- 2—Victor 45 rpm and Decca 78 rpm Records
- 3—No high frequency roll-off, 500 cycle turnover
- 4—All Capitol Records, new Victor 33 1/3, Audio Engineering Society Curve
- 5—Columbia, London and most LP Records
- 6—To remove the hiss from old noisy records

Precision elements are used in its construction to give accurate compensation. The 132E is inherently a low distortion R-C device.

PICKERING PROFESSIONAL AUDIO EQUIPMENT

"For those who can hear the difference"

...Demonstrated and sold by Leading Radio Parts Distributors everywhere.
For the one nearest you and for detailed literature, write Dept. C-2



PICKERING and company incorporated • Oceanside, L. I., New York

Check the specs...

Check performance...

Then, They'll Choose Hallicrafters




Model S-76

Double conversion receiver. Broadcast Band 538-1580 kc plus three short-wave bands covering 1720 kc-34 Mc.


Calibrated electrical bandspread for easy tuning. Double superhet with 50 kc second i-f and giant 4-inch "S" meter. Five position selectivity, one r-f, two conversion, two i-f stages, temperature compensated. 3.2 or 500 ohm outputs.

Satin black steel cabinet. 18½" x 8⅞" x 9½" deep. Nine tubes, voltage regulator, and rectifier. For 105/125 V. 50/60 cycle AC. Use R-46 speaker. . . **\$17950**

SELECTIVITY CURVES, S-76

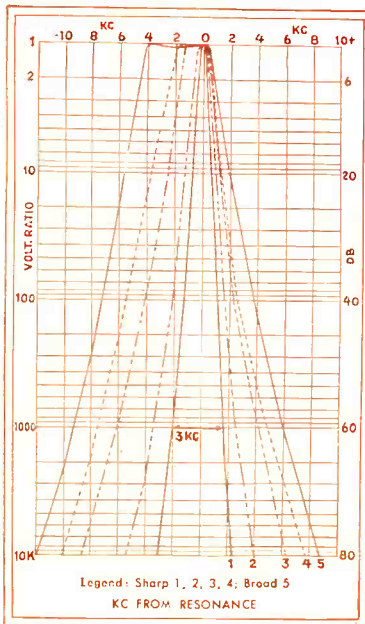

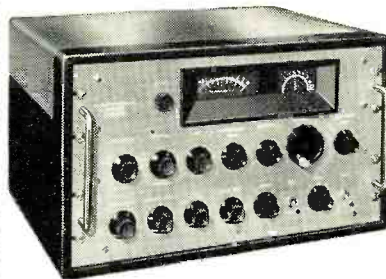Do you know any better way, any other way, to judge SW equipment than to check the specifications and the performance? Frankly that's the only valid way we can think of to make sure you get your money's worth. Check these specs. Take a look at the selectivity curve for the S-76. It is typical of the outstanding value Hallicrafters offers in every price class.



Model HT-20. T.V.I. suppressed 100 watt AM-CW transmitter with all spurious outputs above 40 Mc at least 90 db. below full rated output.

All stages metered; single meter with eight position meter switch; output tuning indication. Frequency range of 1.7 Mc to 31 Mc continuous on front panel control. Seven tubes plus five rectifiers.

For 105/125 V. 50/60 cycle **\$44950**

Model SX-71. Covers Broadcast Band 535-1650 kc plus four short-wave bands covering 1650 kc-34 Mc. and 46-56 Mc.


Narrow Band FM one r-f, two conversion, and three i-f stages. Temperature compensated, voltage regulated. Three watt output (terminals for 500 and 3.2 ohms).

Satin black steel cabinet. 18½" x 8⅞" x 12" deep. 11 tubes plus regulator, rectifier. For 105/125 V. 50/60 cycle AC. Use R-46 speaker. . . **\$22450**



Model R-46. Matching 10" PM speaker for use with Hallicrafters communications receivers SX-71, SX-76, SX-73 or SX-62. 80 to 5000 cycle range. Matching transformer with 500-ohm input. Speaker voice coil impedance, 3.2 ohms.

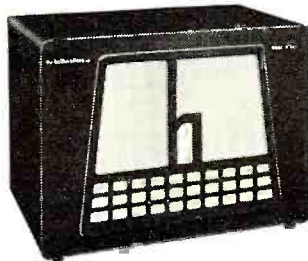Satin black steel cabinet matches all Hallicrafters receivers. Cloth covered metal grille. 15" x 10⅞" x 10⅞" deep. Ship. wt. 17 lbs. . . **\$1995**



hallicrafters

World's Leading Exclusive Manufacturer of Communications and High Fidelity Equipment, Radio and Television

4401 West Fifth Avenue, Chicago 24, Illinois
Hallicrafters Ltd., 51 Camden Street, Toronto, Canada

**NEW SMALL VERSATILE
P.A. Lavalier
DYNAMIC MICROPHONE**
For Chest, Desk or Hand Use



MODEL 647



**FIRST EVER IN
SUCH SMALL SIZE
FOR PUBLIC ADDRESS**

Unlike any lapel microphone, the "647" offers full-range E-V dynamic microphone quality, ruggedness and performance characteristics for indoor and outdoor use. Response 60-13,000 cps, specially compensated for chest resonance. Output -57 db.

Only 4" x 1", the "647" can be worn around the neck, or used in the hand, on a desk or on a boom. When suspended from the neck, a unique clip provides secure support—frees the user's hands for gestures and demonstrations, permits him to move around.



Exclusive E-V Acoustalloy diaphragm is virtually indestructible. Acoustically-treated grille minimizes effects of wind and breath blasts. Supplied complete with combination neck cord and tie clip for microphone, belt clip for cable, rubber desk stand and 18 ft. cable. Available in Low or Hi-Z.

Model 647. List Price, \$80.00
Net, \$48.00

See your E-V Distributor
or Send for Bulletin 201

Electro-Voice

410 CARROL ST. • BUCHANAN, MICHIGAN
Export: 13 E. 40th St., New York 16, U. S. A. Cables: Arlab

For the **RECORD.**

BY THE EDITOR

ENGINEERING AND THE FUTURE

THE engineering profession, particularly in the electronics field, is riding at an all-time high. According to an analysis in a recent issue of the magazine "U. S. News & World Report," college graduates in general and engineering graduates in particular were never in greater demand. Students and young people would do well to analyze their aptitudes and talents in the light of this demand and seriously consider entering the field.

A year ago, the Survey Committee of Engineers Joint Council indicated a shortage of about 80,000 engineers. This shortage is gradually being reduced but there is still a demand for about 42,000 engineers a year, and the total number of engineering graduates this year will probably not exceed 21,000. A similar situation holds true for scientists.

The present salary scales for graduate engineers would make the old-timers who graduated during the depression really drool. The starting scale runs roughly \$350 a month, with extremes of as much as \$500 being reported. This is for men with very little or no experience, just getting out of school.

These factors make engineering a very attractive and promising field. The long-term trend still favors the engineer and with the rapid developments in electronics and other fields, this trend may even be accelerated.

There are many other factors that make the engineering field attractive. Here is a chance to get in on the ground floor of some of the most startling developments of modern times. Here is a chance to satisfy one's inherent thirst for knowledge regarding the "why's" and "wherefore's" of scientific knowledge. Here is a chance to do something really constructive—increase the standard of living, develop something "new" that gives a feeling of accomplishment.

One of the questions asked of our readers in a recent survey dealt with the "special interests," including those readers attending classes in college and in trade school. We found as a result that a total of 61,673 were presently studying subjects in electronics. Nearly 24,000 of these readers were going to a trade school and another 20,000 were attending college. The survey showed that more than 24,000 were currently studying engineering and nearly 17,000 were studying communications. It has been most gratifying to the editors that ever since World War II there has been an ever-increasing number of high school grad-

uates entering the field of engineering as a profession.

In addition to these men, we find that over 25,000 of our readers are studying servicing. While the total of the above is but a drop in the bucket compared to the requirements of the electronics industry, it does show that these students are greatly augmenting the entire engineering profession in our electronic industry.

Our high schools are doing an excellent job of training students to enter engineering colleges but still more must be done to cut down on the mortality rate. The analysis mentioned above reveals that many students are deficient in math. Others have not been taught to work and to think. These factors are of supreme importance to the engineer, and must be recognized early by engineering students. Probably the major reason for this is the shortage of good high school teachers who are able to inspire their students to think and work.

Another factor which is rapidly entering into the engineering field is that of executive ability and training. More and more of the larger companies are drawing from their engineering staffs to fill executive positions. This means even greater opportunities for engineers in the years to come. It also means greater responsibilities, more intensive training, and the development of aptitudes not ordinarily required in engineering as such. These aptitudes come under the broad heading of executive ability. It used to be the common impression that executive ability, or lack of it, was born in a person. However, it has been proved time and again that this ability can be developed to a remarkable degree.

What does all this add up to? It means that more and more of our students in high school and college should seriously consider entering one of the various engineering fields. It means further that these students must learn to discipline themselves to work and to think. They must learn how to get along with other people—how to organize and direct various activities—how to get the utmost in cooperation from associates—how to handle problems in human relations. More attention to the humanities can perhaps assist in this direction.

This might appear to be a difficult road to travel, but the rewards more than justify the difficulties. The feeling of satisfaction resulting from a job well done is worth many a tedious hour of study and preparation... O. R.

always in stock
at **ALLIED**

TRIPLITT
test instruments

**exceptional
quality and value**

Choose this reliable equipment for your service or lab bench—and save! Order Triplitt test instruments from ALLIED—for top value and continuously dependable service.

OUTSTANDING VALUES IN DEPENDABLE VOLT-OHM-MILLIAMMETERS



Model 630: 33 Ranges

Completely enclosed single selector switch; 5 1/2" meter with 4 3/4" scale. Uses 1% resistors. Provides direct connections without cabling. Ranges: DC and AC volts, 0-3-12-60-300-1200-6000, DC at 20,000 ohms/v., AC at 5000 ohms/v.; DC current 0-60 microamps, 0-1-2-12-120 ma. and 0-12 amps; res. 0-1000-10,000 ohms and 0-1-100 megs; db. -30 to +70 in 6 ranges; output v., 0-3-12-60-300-1200-6000. 20-

position switch selects both circuit and range. Black molded case, 3 1/2 x 5 1/2 x 7 1/2". With batteries and 50" test leads. Shpg. wt., 4 1/2 lbs.
84-568. Only..... \$38.71



Model 630A: 1/2% Resistors

Overall accuracy: 1 1/2% on ohms and 0-1200 DC volts; 4% on 6000 DC volts and all AC ranges. Features mirror scale to eliminate errors in reading due to parallax; uses 1/2% resistors. Ranges: DC and AC volts 0-3-12-60-300-1200-6000 (DC at 20,000 ohms per volt, AC at 5000 ohms per volt); DC current, 0-60 microamps, 0-1-2-12-120 milliamps, and 0-12 amps; resistance, 0-1000-10,000 ohms, and 0-1-100 meg-

ohms; db. -30 to +70 in 6 ranges; output volts, 0-3-12-60-300-1200-6000. Single knob selects both circuit and range. 5 1/2" meter with 4 3/4" scale. 7 1/2 x 5 1/2 x 3 1/2". With batteries and 50" test leads. Shpg. wt., 6 lbs. Here's the compactly built unit—constructed VOM—ideal for all applications requiring top accuracy. 84-574. Only..... \$48.51

Model 650: Single Switch

Single selector switch for all ranges. Complete frequency coverage from 15 cps to over 110 mc with one probe. Ranges: DC v., 0-1-5-10-50-100-500-1000; AC-RF v., 0-1-5-10-50-100-500; peak-to-peak volts, 0-2.8-14-28-140-280; ohms, 0-1000-10,000-100,000-1 meg.-100 meg.-1000 meg. Large 5 1/2" meter with 4 3/4" scale. 3 3/4 x 5 1/2 x 7 1/2"; complete with power cord, DC v. and ohms lead, AC-RF volt tube probe, battery Shpg. wt., 6 lbs.

84-558. Only..... \$68.11
84-564. HV Probe. Only..... \$14.21



Model 666R: 1000 ohms/volt

Economical pocket-size VOM with handy single selector switch. Only 2 controls—the range switch and the ohms adjust control. 1000 ohms/volt sensitivity on AC and DC volt ranges. Red Dot 3" 0-200 microammeter movement with 250 millivolt sensitivity. Ranges: DC and AC volts, 0-10-50-250-1000-5000; DC ma, 0-10-100; DC amps, 0-1; ohms, 0-3000-300,000; megs. Size: 3 1/2 x 5 1/2 x 2 3/8". Complete with batteries, 50" test leads with banana plugs and alligator clips. Shpg. wt., 3 lbs.

84-557. Only..... \$25.97
Model 666RL. Same as above, but in camera-type black leather case. Shpg. wt., 4 lbs.
84-538. Only..... \$31.85



Model 3441 TV-FM Oscilloscope

Vertical deflection sensitivity .01 rms v./inch. Vertical response 4 mc. Horizontal, 20 cps to 150 kc; deflection sensitivity, .1 rms v./inch. Vertical input impedance, 2 megs, 20 mmf (with probe). Reads peak-to-peak volts direct on meter. 0-1000 in 8 ranges. Linear sweep: 10 cps to 60 kc/second. Phased 60 cycle horizontal sweep and return trace eliminator for use with sweep generators. Synchronizing and horizontal sweep selector combined in one simple control. Has phone jack for hearing wave-form under observation; simplifies audio circuit tracing. Uses 5" cathode-ray tube (5U1). Fully shielded and fused. Complete with tubes, 2 coaxial cables, rubber-covered test leads, low capacity probe and instructions. Size: 15 1/2" x 16 x 11 1/2". For 105-115 volts, 50-60 cycles AC. Shpg. wt., 65 lbs.


84-530. Only..... \$195.51



Model 3434A TV-FM Sweep Generator

High output on VHF and sufficient harmonics for UHF. Continuous tuning to 240 mc covers all TV, FM and IF ranges with no gaps. Sweep center frequency: 0-60-120 and 120-240 mc. Sweep width: 0-12 mc, continuously variable. Marker frequencies: 3.5-4.9, 19.5-29.3, 29-48.6 (fundamentals); harmonics to 240 mc. Crystal frequency: to 20 mc on fundamentals; harmonics to 216 (crystals not supplied). Modulation: 600 cycles. Output 1 to 1.5 volts. Two built-in markers: absorption and pip and crystal. Ladder type attenuator. Horizontal bar generator for vertical alignment. Large mirror scale for precise marker adjustment. 15 1/2" x 11 1/2" x 8 3/4". With 2 coaxial cables, ground straps, test leads and instructions. For 105-115 v., 50-60 cycles AC. 45 lbs.

84-534. Only..... \$195.51

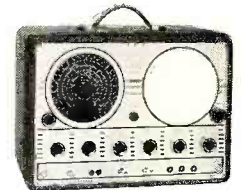


ALLIED STOCKS ALL TRIPLITT TEST INSTRUMENTS

We can supply promptly any test instrument made by Triplitt, including the following models:
84-537. Model 660 Load-Chek. Only..... \$28.91
84-592. Model 3432 Signal Generator. Only... 77.91
84-575. Model 625 NA V-O-M. Only..... 48.51

All Triplitt instruments over \$45 available on Easy Terms—write for details

3413A Tube Tester

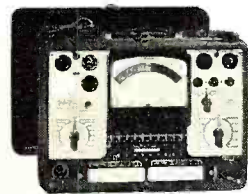Tops for flexibility and simplicity. Tests all modern tubes (including 9-pin noval) pilot lamps, ballast tubes, resistors, etc. 6" Red Dot lifetime guaranteed meter gives quick, accurate BAD—?—GOOD tests. Checks emission.




shorted and open elements. Built-in Speed-Roll chart. Counter-portable case. 15 1/2" x 11 1/2" x 6 1/2". Shpg. wt., 28 lbs.
84-591. Only..... \$77.91

TYPE BV ADAPTOR, T2247-BV. Checks TV picture tubes with 3413A. Shpg. wt., 1 lb.
84-539. Only..... \$7.74

3423 Tube-Tester


New Proportional Mutual Conductance type for all TV and Radio tube tests. Gives mutual conductance readings in micromhos. Six plate voltages for tube tests, including 0-10 AC variable for low voltage tubes. 4 KC used to make mutual conductance tests. Also has GOOD—?—BAD scale. Checks for shorts, leakage, gas, noise. Tests all tube types speedily and accurately. Built-in Speed-Roll chart. Lined-oak case, 14 3/4" x 18 3/4" x 6 1/2". Shpg. wt., 21 lbs. With accessories and instructions. For extremely accurate and completely dependable testing of all tube types—this is the instrument to own.

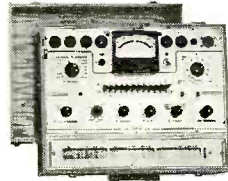

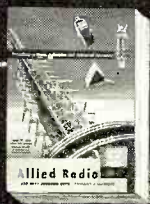84-541. Only..... \$195.51

FREE 236-PAGE BUYING GUIDE

Make your selections from the world's largest stocks of tubes, parts, test instruments, audio equipment, amateur gear, industrial components—everything in electronics at lowest prices. Get your FREE catalog now.



ALLIED RADIO

ALLIED RADIO CORP., Dept. 1-H-3
833 W. Jackson Blvd., Chicago 7, Ill.

- Send FREE 1953 Allied Catalog.
- Please ship the following Triplitt instruments.....

.....\$.....enclosed

Name.....

Address.....

City.....Zone.....State.....

*Quality
conscious dealers
want the
Nepco Line*

Experience is a great teacher. And experience has taught more and more TV installers and service men they can't afford to risk their reputations on inferior materials.

That's why so many demand the NEPCO LINE—television's "Master of the Elements." They've found that National Electric's complete line of TV Antennas, Mounting Accessories, and Wire provides built-in ruggedness . . . meets the test of time and weather—and assures their reputation in both the new and replacement markets.



EXAMINE THE NEPCO LINE—

**Quality materials
with the strength to
stay on the job . . .**

- * Extra heavy zinc galvanizing on all parts.
- * Baked on "Shera-solution" for extra corrosion protection.
- * Rigid heavy gauge steel used in all mounts (1 $\frac{3}{4}$ "x1 $\frac{1}{8}$ ").
- * Two 15' stainless steel chimney bands, $\frac{5}{16}$ " eye bolts, and 4 heavy gauge banding clips with patented imbedding screws available with each chimney mount.
- * All hardware corrosion-protected in the same complete manner as the mounts.


* Every item in the NEPCO Line is engineered, tested and field proved to assure long service on the job.

**Plus features
for fast, easy installation
and handling**


- * Unique adjustable mast clamp with one bolt mounting.
- * Exclusive antenna mast clamp with positive alignment in all planes.
- * Patented imbedding type screw for positive electrical and mechanical locking.
- * Versatile mounts that accommodate all types of installations.

National

RADIO & TELEVISION NEWS

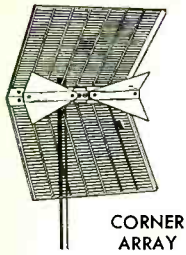

CORNER ARRAY

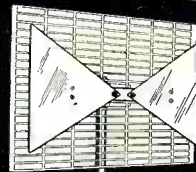

BOW TIE REFLECTOR

ANTENNAS—UHF

- DOUBLE DIPOLE REFLECTOR
- STACKED DIPOLE REFLECTOR
- YAGI TYPE
- BOW TIE
- CONICAL TYPE




YAGI TYPE

ANTENNAS—VHF


CONICAL TYPE

THE COMPLETE LINE
FOR A FAST
PERMANENT INSTALLATION

MASTING

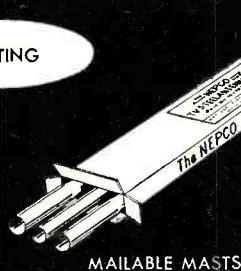

MAILABLE MASTS

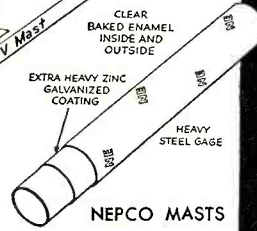

CLEAR BAKED ENAMEL INSIDE AND OUTSIDE


EXTRA HEAVY ZINC GALVANIZED COATING

HEAVY STEEL GAGE

NEPCO MASTS


TELESCOPING MASTS

MOUNTS

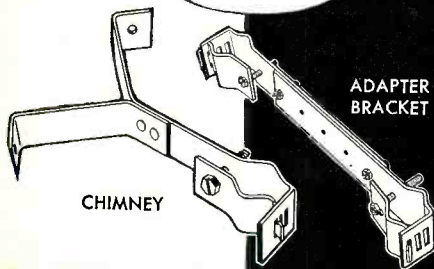


CHIMNEY


ADAPTER BRACKET

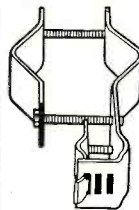

VENT

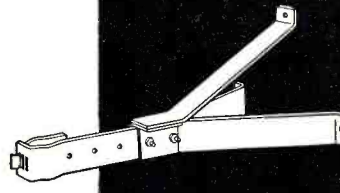

ADJUSTABLE WALL

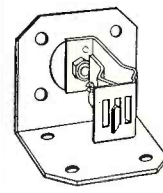


ROOF

WIRES



ZEE LINE

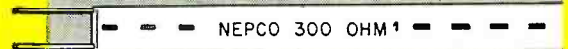

POLYON 300 OHM TWIN LEAD WIRE

YOU'LL FIND...

- * A line designed with your handling problems in mind . . . strong compact boxes easy to move and stack.
- * Large easy-to-read illustrated package labels.

In addition . . .

Brand recognition has been gained for the NEPCO Line through superior service on the job, and a national advertising and promotional program has created acceptance for this quality line.

The NEPCO Line is priced right for your customers.

Write, wire or phone for the name of your nearest representative today

Plus


- Wall Brackets
- Guy Rings
- Chimney Banding
- Banding and Mast Clamps

THE
NEPCO
LINE


Electric Products

Radio & Television Department, Pittsburgh, Pa.

In a Class
by Itself

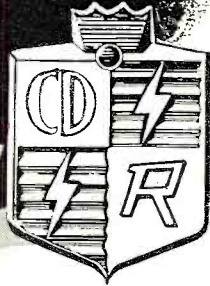

the
CDR Rotor

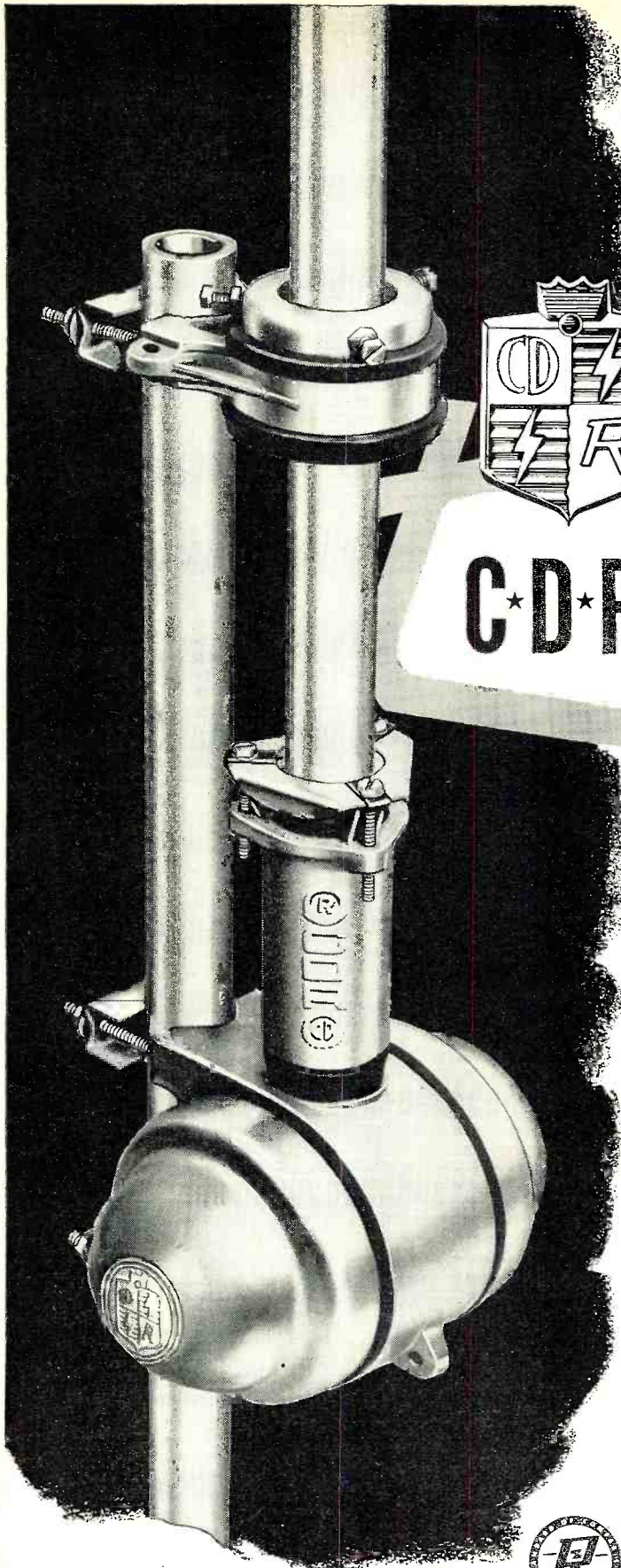

Speedy Installation ... the servicemen's dream come true! No loose parts to assemble... no kits with loose washers, nuts and bolts... quick mounting antenna mast collet plus four wire cable hookups!

Dependable ... experience has proven that once a CDR ROTOR is up... it's THERE TO STAY! No costly call-backs! Completely weather-sealed and streamlined... it's the outstanding value in the field!

Powerful ... sturdy in design to support and TURN ANY TV ANTENNA array... never a worry about the CDR rotor working! Locking instantly it will not drift! Instantly reversible... makes a complete revolution in 45 seconds!

MODEL TR-12 A special combination value consisting of complete rotor including thrust bearing... handsome modern design plastic cabinet with meter control dial, only..... **\$47.95**

MODEL TA-6 Thrust bearing accessory, separately.... **\$4.95**

MODEL TR-11 Same as TR-12 without thrust bearing.. **\$44.95**



SUBSIDIARY OF




THE **RADIART** CORPORATION
CLEVELAND 13, OHIO

CORNELL-DUBILIER
SOUTH PLAINFIELD, NEW JERSEY
RADIO & TELEVISION NEWS


Let me send you FREE
the entire story

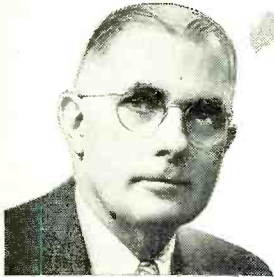Just fill out the coupon and mail it. I will send you, free of charge, a copy of "How to Pass FCC License Exams," plus a sample FCC-type Exam, and the amazing new booklet, "Money-Making FCC License Information."



EDW. H. GUILFORD
Vice President

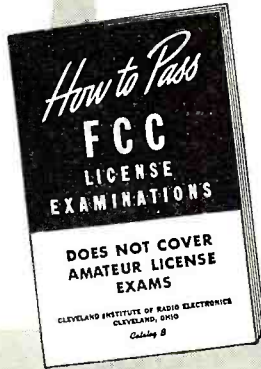I can train you to pass your FCC License Exams in a minimum of time if you've had any practical radio experience—amateur, Army, Navy, radio servicing, or other. My time-proven plan can help put you, too, on the road to success.



How to Pass FCC COMMERCIAL Radio Operator License Exams

FREE

Tells where to apply and take FCC examinations, location of examining office, scope of knowledge required, approved way to prepare for FCC examinations, positive method of checking your knowledge before taking the examination.

GET YOUR FCC TICKET IN A MINIMUM OF TIME

Get this Amazing Booklet FREE

TELLS HOW

HERE IS YOUR GUARANTEE

If you fail to pass your Commercial License exam after completing our course, we guarantee to continue your training without additional cost of any kind, until you successfully obtain your Commercial license, provided you first sit for this examination within 90 days after completing our course.

TELLS HOW

WE GUARANTEE

TO TRAIN AND COACH YOU AT HOME IN SPARE TIME UNTIL YOU GET

YOUR FCC LICENSE

If you have had any practical experience—Amateur, Army, Navy, radio repair, or experimenting

Employers make

JOB OFFERS Like These to Our Graduates Every Month

Letter from nationally-known Airlines, "We would also appreciate if you would place the following additional advertisement in your bulletin—Wanted—Superintendent of Communications . . . Salary \$666.66 per month."

Letter from nationally-known airplane manufacturer, "We need men with electronic training or experience in radar maintenance to perform operational check-out of radar and other electronics systems . . . starting salary . . . amounting to \$329.33 per month."

These are just a few examples of the job offers that come to our office periodically. Some licensed radiomen filled each of these jobs . . . it might have been you!

HERE'S PROOF FCC LICENSES Are OFTEN SECURED IN A FEW HOURS OF STUDY WITH OUR COACHING at HOME in SPARE TIME

Name and Address	License	Lessons
Lee Worthy 2210 1/2 Wilshire St., Bakersfield, Calif.	2nd Phone	16
Clyford E. Vogt Box 1016, Dania, Fla.	1st Phone	20
Francis X. Foerfel 38 Beucier Pl., Bergenfield, N. J.	1st Phone	38
S/Sgt. Ben H. Davis 317 North Roosevelt, Lebanon, Ill.	1st Phone	28
Albert Schoell 110 West 11th St., Escondido, Calif.	2nd Phone	23

CLEVELAND INSTITUTE OF RADIO ELECTRONICS

CARL E. SMITH, E. E., Consulting Engineer, President
Desk RN-55—4900 Euclid Bldg., Cleveland 3, Ohio

TELLS HOW

Our Amazingly Effective JOB-FINDING SERVICE

Helps GIRE Students Get Better Jobs

Here are a few recent examples of Job-Finding results

GETS FIVE JOB-OFFERS FROM BROADCAST STATIONS
"Your 'Chief Engineer's Bulletin' is a grand way of obtaining employment for your graduates who have obtained their 1st class license. Since my name has been on the list I have received calls or letters from five stations in the southern states, and am now employed as Transmitting Engineer at WMMT."
Elmer Powell, Box 274, Sparta, Tenn.

GETS CIVIL SERVICE JOB
"I have obtained a position at Wright-Patterson Air Force Base, Dayton, Ohio, as Junior Electronic Equipment Repairman. The Employment Application you prepared for me had a lot to do with my landing this desirable position."
Charles E. Loomis, 4516 Genesee Ave., Dayton 6, Ohio.

OURS IS THE ONLY HOME STUDY COURSE WHICH SUPPLIES FCC-TYPE EXAMINATIONS WITH ALL LESSONS AND FINAL TESTS.

GETS AIRLINES JOB
"Due to your Job-Finding Service, I have been getting many offers from all over the country, and have taken a job with Capital Airlines in Chicago, as Radio Mechanic."
Harry Clare, 4537 S. Drexel Blvd., Chicago, Ill.

Your FCC Ticket is recognized in all radio fields as proof of your technical ability.

Get All 3 FREE

MAIL COUPON NOW

CLEVELAND INSTITUTE OF RADIO ELECTRONICS

Desk RN-55
4900 Euclid Bldg., Cleveland 3, Ohio
(Address to Desk No. to avoid delay)

I want to know how I can get my FCC ticket in a minimum of time. Send me your FREE booklet, "How to Pass FCC License Examinations" (does not cover exams for Amateur License), as well as a Sample FCC-type exam and the amazing new booklet, "Money-Making FCC License Information."

Tell me how I can get a TV Engineering Course without additional charge.

NAME

ADDRESS


CITY..... ZONE..... STATE.....

Paste on 2-cent post card or send air mail

To help you boost your sales
and make more money



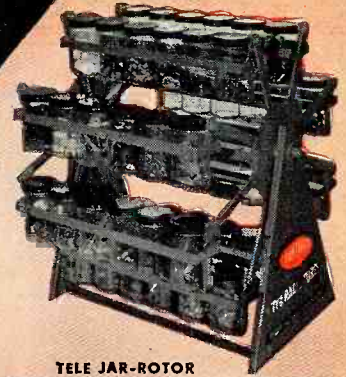makes these
SALES AND SHOP AIDS
available to you




TELE JAR-ROTOR
A perfect small parts storage unit. Only 17" x 15" x 13".
Has 48 transparent plastic jars.



ILLUMINATED OUTDOOR SIGN
Double sided, formed plastic sign. 36" x 24" UL approved.



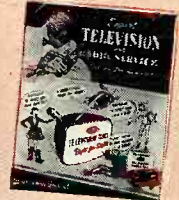THREE DIMENSIONAL PLASTIC ILLUMINATED SIGN
A colorful "3-D" rather illuminated formed plastic beauty.



DISPLAYS
Six color displays that sell your service.



REFLECTORIZED OUTDOOR METAL SIGN
Two sided metal sign to catch the eye of passers-by.



TUBE AND TOOL CARRYING CASE
Holds 137 tubes — plus all regular tools.



TRANSPARENT PLASTIC WINDOW STREAMER



PLASTIC "WILL RETURN" DIAL SIGN



SHOP JACKETS AND COATS
Full length or jacket style.



ILLUMINATED TEST PATTERN CLOCK
A Telechron Motored beauty.

Write
for
FREE BOOKLET!



Pictured are only a few of the many useful shop aids and sales promotion items that Raytheon has made available to you. There are many others — job tags and record cards, imprinted stationery, post cards, ad mats, shipping labels, decals, paper bags, giant outdoor thermometers, etc. — all designed with your needs in mind. Many items are free, the rest available at very low cost. Ask your Raytheon Tube Distributor about them or write for free Booklet. Address your request to Department A, Raytheon Manufacturing Company, Receiving Tube Division, 55 Chapel Street, Newton 58, Mass.



Excellence in Electronics

RAYTHEON MANUFACTURING COMPANY

Receiving Tube Division
Newton, Mass., Chicago, Ill., Atlanta, Ga., Los Angeles, Calif.

RAYTHEON MAKES ALL THESE:

RECEIVING AND PICTURE TUBES • RELIABLE SUBMINIATURE AND MINIATURE TUBES • GERMANIUM DIODES AND TRANSISTORS • NUCLEONIC TUBES • MICROWAVE TUBES

Leonard C. Lane, B.S., M.A.
President of Radio-Television
Training Association. Exec. Dir.
of Pierce School of Radio and
Television.



**I GIVE YOU
MORE EQUIPMENT
TO TRAIN YOU BETTER**

Set up your own home laboratory with the 15 BIG TV-Radio kits we send you. You build AND KEEP your own complete BIG SCREEN TV RECEIVER, Super-Het Radio Receiver, R.F. Signal Generator, Combination Voltmeter-Ammeter-Ohmmeter, C-W Telephone Receiver, AC-DC Power Supply. Everything is furnished complete, including all tubes, plus big TV picture tube.



GET MORE!

LEARN MORE!

EARN MORE!

I PREPARE YOU AT HOME IN YOUR SPARE TIME

**THOUSANDS OF NEW JOBS IN
TELEVISION**

MORE

**TRAINING TO FIT YOU
FOR THE BETTER PAY JOBS**

Thousands of new jobs will open up right in your own state, now that the government has lifted restrictions on new TV stations. My simple, successful methods have helped hundreds of men — most of them with NO PREVIOUS TRAINING — find places in America's booming TELEVISION and Electronics industries. You too can get the success and happiness you always wanted out of life within months... studying at home... as I train you to become a full-fledged TV TECHNICIAN. Many of my students make as much as \$25.00 a week repairing Radio-TV sets in their spare time while learning... pay their entire training almost from the very beginning from spare time earnings... start their own profitable service business.

But I don't stop after I qualify you as a TV Technician... although right there you can choose from among dozens of fascinating careers! I continue to train you — AT NO EXTRA COST — to qualify for even better pay in the BETTER JOBS that demand FCC licenses, with my...

FREE FCC COACHING COURSE

PREPARES YOU AT HOME FOR YOUR FCC LICENSE. THE BEST JOBS IN TV AND RADIO REQUIRE AN FCC LICENSE. Given at NO EXTRA COST after TV Theory and Practice is completed.

NOW! ADVANCED FM-TV TRAINING

If you have previous Armed Forces or civilian radio experience—my ADVANCED COURSE can save you months of training. Full theory and practical training... complete with kits, including BIG SCREEN TV RECEIVER and FREE FCC License Coaching Course.

FREE EMPLOYMENT ASSISTANCE

My vocational adviser will help you obtain a good-paying job in the locality of your choice.

RADIO-TELEVISION TRAINING ASSOCIATION

1629 Broadway, Radio City Station, New York City 19, N. Y.
LICENSED BY THE STATE OF NEW YORK

MORE VALUE!

**YOU GET A ROUND TRIP TO
NEW YORK CITY
AT NO EXTRA COST**

FROM ANYWHERE IN THE U.S. OR CANADA — I pay your way to New York and return, PLUS 2 FREE weeks, 50 hours of advanced instruction and shop training at the PIERCE SCHOOL OF RADIO & TELEVISION. You use modern electronics equipment, including student-operated TV and Radio stations. You go behind the scenes of New York's big Radio-TV centers, to study first hand. And I give you all this AT NO EXTRA COST! (Applies to complete Radio-TV course only.)

Only RTTA makes this amazing offer.

I GET MY

GRADUATES GOOD PAYING JOBS

"Thanks to your training, I qualified for a good job as a Receiver Tester at Federal Telephone and Radio."
— Paul Frank Seier



"I'm making good money in my own business, repairing and installing radio and TV sets — thanks to your training."
— Irwin Polansky



"Your excellent instruction helped me get my present job as an airport radio mechanic for American Airlines."
— Eugene E. Basko



"I'll always be grateful to your training which helped me get my present fine position as Assistant Parts Manager."
— Norman Weston



Many others working at NBC, RCA, CBS, DuMont, Philco, Emerson, Admiral and other leading firms.

VETERANS!




MY SCHOOLS FULLY APPROVED TO TRAIN VETERANS UNDER NEW G.I. BILL! If discharged after June 27, 1950 — CHECK COUPON BELOW!

Also approved for RESIDENT TRAINING in New York City... qualifies you for full subsistence allowance up to \$160 per month.

MAIL COUPON TODAY!

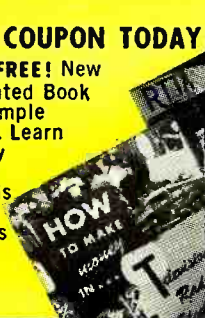BOTH FREE! New Illustrated Book and Sample Lesson. Learn How My Simple Methods Make Success Easy!



NO SALESMAN WILL CALL!

Mr. Leonard C. Lane, President
RADIO-TELEVISION TRAINING ASSOCIATION
1629 Broadway, Radio City Station
New York 19, N. Y. Dept. T-8


Dear Mr. Lane: Mail me your NEW FREE BOOK and SAMPLE LESSON that will show me how I can make BIG MONEY in TELEVISION. I understand I am under no obligation and no salesman will call.

(PLEASE PRINT PLAINLY)

Name _____ Age _____
Address _____
City _____ Zone _____ State _____

I am interested in: Radio-TV Advanced FM-TV.
VETERANS: If qualified under new G.I. Bill, check your choice: Home Study Resident Study.

are you
**BURNED
UP?**

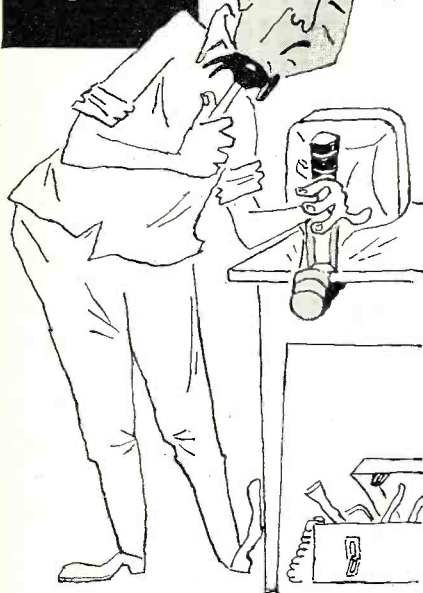

**TRIAD
DEFLECTION
YOKES**

*will cool
you off*



If you are tired of blasting cooked yokes off of picture tubes—then switch to Triad Deflection Yokes. They have a molded high-temperature plastic insulation between vertical and horizontal coils, reducing chances of cooking and simplifying servicing. Triad's new 1953 Catalog features 18 new items which have been added to an extensive line of TV replacements—every item designed for long trouble-free service, and to ease and speed the serviceman's job.

Write for Catalogs TR-53A and TV-53A



4055 Redwood Ave. • Venice, Calif.

Spot Radio News

★ Presenting latest information on the Radio Industry.

By RADIO & TELEVISION NEWS'
WASHINGTON EDITOR

COMPATIBLE COLOR, which dazzled members of Congress during that striking Princeton show, at this writing is being readied for a grandstand appearance before the seven guardians of the airlines, the Commission, by the folks who staged the demonstration in New Jersey, *RCA*. Originally, the industry committee studying color was scheduled to file a petition as a body. Now, according to company spokesmen, two petitions may be filed, with the NTSC delaying its presentation until the late Fall.

The early prospects for color have so excited broadcasters, that over thirty affiliates of *RCA's NBC* net have signed affiliation contract supplements allowing them to carry colorcasts when the reds, greens, and blues begin coming over the coax. Among those who said yes, were *WBRE-TV*, Wilkes-Barre; *WSYR-TV*, Syracuse; *WJAC-TV*, Johnstown; *WLWD*, Dayton; *WLWC*, Columbus; *WLWT*, Cincinnati; *WSAZ-TV*, Huntington; *WDSU-TV*, New Orleans; *KSTP-TV*, St. Paul-Minneapolis; *WKY-TV*, Ok-

lahoma City; *KCBD-TV*, Lubbock; *WBAP-TV*, Fort Worth; *KPRC-TV*, Houston, and *KPTV*, Portland.

According to the company's production experts, setmaking should begin about nine months after government approval is received; thus sets *might* be available *next* Spring. However, many have indicated, and quite strongly, that the Winter of '54, probably around Thanksgiving or Christmas looks like a more realistic date-line for color-chassis deliveries.

In the meantime, NTSC task groups are pushing ahead with their exhaustive tests. Particularly active are the field panels which have members in New York, Chicago, Syracuse, Philadelphia, and Washington constantly probing and conducting actual observation tests. Not only are they concerned with the effectiveness of color reception, but the compatibility of chassis for viewing and listening, too. According to the test procedures of one sub-committee, task groups are responsible for official tests in strong signal, intermediate strength signal,

NEW TV GRANTS SINCE FREEZE LIFT

Continuing the listing of construction permits granted by FCC since lifting of freeze. Additional stations will be carried next month.

STATE	CITY	CALL**	CHANNEL	FREQUENCY (mc.)	POWER* (Video)
Idaho	Meridian	2	54-60	16.5
Illinois	Rockford	13	210-216	195
Ohio	Cincinnati	WCIN-TV	54	710-716	89
Oregon	Eugene	13	210-216	56
Pennsylvania	Lancaster	21	512-518	18
Texas	Harlingen	4	66-72	13
"	Lubbock	KFYO-TV	5	76-82	100
Wyoming	Casper	KSPR-TV	2	54-60	1.2
Hawaii	Honolulu	4	66-72	58

REVISED CALL LETTER LISTING

(Since the publication of the listings last month, the following final TV call letters have been assigned to new stations by the Commission.)

STATE	CITY	CALL	CHANNEL	FREQUENCY
California	Fresno	KJEO	47	668-674
"	San Francisco	KSAN-TV	32	578-584
Florida	Lakeland	WO-TV	16	482-488
Louisiana	Alexandria	KSPJ	62	758-764
Minnesota	Minneapolis	WTCN-TV	11	198-204
Michigan	Cadillac	WWTV	13	210-216
Missouri	Cape Girardeau	KGMO-TV	18	494-500
New Hampshire	Keene	WKNE-TV	45	656-662
Pennsylvania	Lancaster	WWLA	21	512-518
Tennessee	Knoxville	WCEE-TV	26	542-548
Texas	Victoria	KNAL-TV	19	500-506

*ERP = (effective radiated power, kw.). **Call letters without TV suffix from application files and subject to change; except where included in calls such as KKTU or WTVT. . . = Call letters to be announced

WE BELIEVE Norman Foster's recent advertisement in the Chicago "TV Guide" is of interest to the entire television and radio industry. Consequently, with Mr. Foster's permission, we are reprinting it here as a public service for every television and radio service technician in America.

Harry Kalker
(HARRY KALKER, President)

SPRAGUE PRODUCTS COMPANY
(Distributors' Division of the Sprague Electric Company)
North Adams, Massachusetts



NORMAN FOSTER

UNFORTUNATELY

Because of the Greed of a Few,

THE ENTIRE TV SERVICE INDUSTRY MUST SUFFER

HERE IS WHAT I HAVE DONE TO GUARANTEE YOU HONEST TV SERVICE

1. The name, Foster Television is not taken from a street, a deck of cards, or a country, and it is not an adjective. It comes from the name of its sole owner, Norman Foster. I have spent 22 years in the Radio, Electronics and Television service business, and in these years I have worked for just about every type of Operator, good, bad and indifferent. When the time came that I could open my own business, I decided that because of the reputation that the Radio and Television repair business has always had, a company operating so honestly that they could invite their customers into the shop to watch their work being done could be a success. The volume of business we did last year proves I was right.

2. The reason that a service man would attempt to sell you something you do not need is because he had something to gain personally. Many Television service operators hire men, driving their own cars, on a percentage basis. This is advantageous because the service company can be in business with practically no investment. Under these conditions if this man needs money, it's only human nature that he is going to want to do the thing to your television set that will make him the most money—whether it be 5 tubes or haul it to the shop.

3. Every man that I have, works by the hour and punches a time clock. He drives a company owned new truck bearing my name and his equipment and uniforms are furnished to him without charge. He has orders to repair your set in your home whenever possible. He receives the same amount of money whether he repairs 1 set or 10, and whether he charges \$1 or \$10. His rate of pay and his advancement are based on the number of sets he can repair in the home.

4. Our service call price is a flat \$3 and covers all labor necessary to make any repair possible in your home except cleaning a screen, for which we charge \$1 extra. It is evident that on this basis we do not make money on every job, but with the large volume of business we do, it has averaged out to a modest profit at the end of the year. You can bring your set into our shop and not only save this service charge, but also see it repaired while you wait. There is no minimum charge on this service. You pay only for the actual time spent on your set.


5. How fast can service be? I have a large fleet of trucks operating throughout Chicago from 9:30 A.M. to 11:00 P.M. I do not advertise one hour service and I do not believe that anything but a coincidence could give such fast service. Because it is impossible to predict in advance how long each job will take a man, the best we can do is to offer same day service. Occasionally at this time of the year, bad weather causing slow driving, makes it necessary to postpone calls received late, until the next day.

6. Quality of parts. I use only nationally advertised tubes and parts. Every tube I sell is new, fresh and cartoned, bearing a name and a date, and is coded by the manufacturer to indicate that it is a tube manufactured and guaranteed for replacement use. I do not use bulk or surplus tubes. Every picture tube I sell bears a serial number and has a factory registration certificate to guarantee that it is a new first quality tube. I do not sell rebuilt or rejuvenated picture tubes. I use only Sprague plastic sealed condensers, which are far superior to the parts used in many TV sets.

7. I guarantee every part I replace for 90 days. If a part or tube I have replaced fails, it is replaced at absolutely no charge to you. Our guarantee is further underwritten by the American Mutual Liability Insurance Co. by arrangement with the Raytheon Manufacturing Co.

8. I have not satisfied everybody and I do not claim to. I cannot repair a set that needs a new picture tube for \$3 and I cannot give a \$60 service contract with each call. Nothing less would satisfy certain people. However, if you hear a complaint against Foster Television, that same person will generally have one against the plumber, the auto mechanic, the dentist and nearly everyone else who is unfortunate enough to do business with him. I need and value your patronage and I will sincerely respect it.

Norman Foster

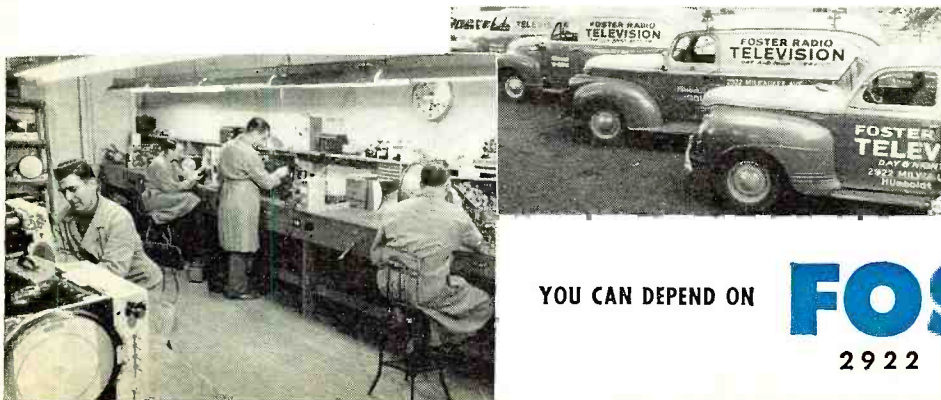

Open 9:30 am-8:30 pm


- Home Service to 11 pm
- Sundays 11 am-3 pm
- H U M B O L D T 9-0911

YOU CAN DEPEND ON

FOSTER TV


2922 MILWAUKEE AVENUE
CHICAGO

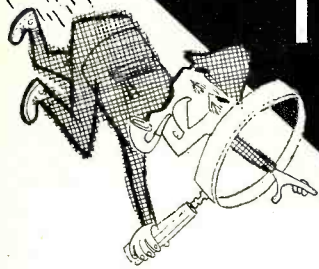LOOKING for the RIGHT TV REPLACEMENT TRANSFORMER?



you'll find it in

STANCOR'S NEW TV REPLACEMENT GUIDE

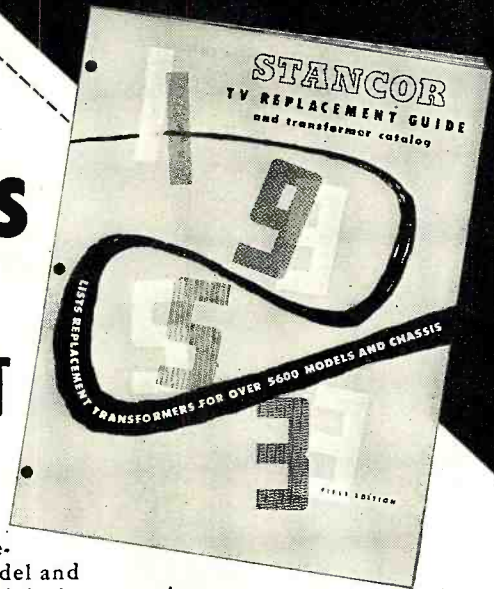

Easier to use . . . lists replacements by manufacturer's model and chassis number and also by original part number.

Up-to-date . . . over 5600 models and chassis are covered, including virtually all sets built prior to 1953 as well as most 1953 models.

You'll save time and trouble when you use this valuable Stancor reference. Get it now from your Stancor distributor, or write us directly for your free copy.

Five new Stancor exact replacement flyback transformers. Many of these units are the result of recommendations of the Stancor Servicemen Advisory board, composed of the top TV servicemen throughout the country.

PLUS A-8126, Universal vertical blocking-oscillator transformer for all Philco sets, including 1953 models.

Stancor Part No.	Exact Replacement For	No. of Models Using Flyback
A-8137	Hoffman #5035	29
A-8220	Philco #32-8555	24
A-8221	Philco #32-8565	18
A-8222	Philco #32-8533 & #32-8534	38
A-8223	Philco #32-8572	15



CHICAGO STANDARD TRANSFORMER CORPORATION


3584 ELSTON AVENUE • CHICAGO 18, ILLINOIS

EXPORT SALES—Roburn Agencies, Inc., 39 Warren St., New York 7, N. Y.

MOSLEY 3-WAY TV ANTENNA SWITCH

for Multiple

UHF and VHF ANTENNA INSTALLATIONS

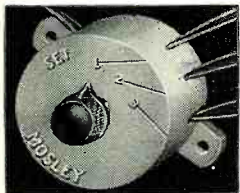


Cat. No. F-20 — MOSLEY
3-Way TV Antenna Switch
List Price \$3.75

- Install anywhere. Extension rod supplied for back of set mounting.
- Constant impedance—Low loss—Solderless.
- Sturdy rotary switch making silver-to-silver contact.
- In brown or ivory polystyrene case.
- Also available in Flush Wall Plate style.

At Radio Parts Jobbers

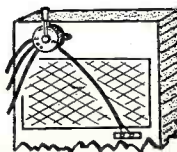8622 St. Charles Rock Road
St. Louis 14, Missouri



MOSLEY Electronics, Inc.

and fringe signal areas. For the intermediate signal-strength tests, signals between 3000 and 10,000 microvolts are required.

In studying the signals, eight tests are made for resolution, over-all picture quality, flicker, brightness, contrast, picture texture, adequacy of sync, and sound quality. The over-all picture quality report, it is said, reveals the general impression a picture makes on the observer, and also if such defects as poor focus, streaking, beats, or noise, appear. In scrutinizing picture texture, observers are required to look for dot structure, dot crawl, moire, or beat patterns in the picture. Viewers are warned that they must look carefully to see if they recognize any limitations in subject matter. They are also obliged to look for evidence of brightening of the horizontal retrace lines due to presence of color sync signals, and make a record of such observations for several possible settings of the horizontal hold control, with brightness control set for best monochrome picture.

A novel scoring technique has been prepared to permit an evaluation of observed results. Two scales are provided, and a series of numbers from one to six to simplify identification. To illustrate, not perceptible represents condition 1; just perceptible, 2; definitely perceptible, but not objectionable, 3; somewhat objectionable, 4; definitely objectionable, 5; and not usable, 6. In the second scale, which is complementary, 1 means excellent; 2, good; 3, passable; 4, not quite passable; 5, poor; and 6, not usable.

The comprehensive tests also involve detailed studies of such problems as susceptibility to co-channel and adjacent-channel interference. In the former test, a lab signal generator is modulated with a signal from a scanner or other pickup equipment in accordance with the NTSC proposed signal, and applied to a color set. Then an interfering signal is applied to the set at a -40 db level. Signals are non-sync, co-channel type and the receiver picture is evaluated for the effects of this interference. A performance comparison is also made with operation of a black and white signal, under similar conditions. The tests are repeated with offset carrier operations at a -28 db level.

Everyone in industry and Washington is well aware of the thoroughness of the work of these task groups, and certainly their efforts will play a major role in producing better color-casting and viewing.

GLOBAL TV, a doodling idea for years, which last Spring captured the fancy of Washington legislators and prompted the evolution of a blueprint for a North Atlantic Treaty TV plan, plus the introduction of a bill in the Senate to establish a Commission on Cooperative International Relations, which would encourage existing agencies . . . "to design . . . and
(Continued on page 111)

CREI prepares you quickly for success in

The handwriting is on the wall.

The signs are plain as to the future of the trained men in the electronics industry. It is a tremendous industry, and—at the *present time* there are more jobs than there are trained men to fill them. But—when there's a choice between a trained and untrained applicant, the trained man will get the job. Your biggest problem is to decide on—and begin the best possible training program.

CREI Home Study . . . The Quick Way to Get There.



Since 1927, CREI has given thousands of ambitious young men the technical knowledge that leads to more money and security. The time-tested CREI procedure can help *you*, too—if you really want to be helped. CREI lessons are prepared by experts in easy-to-understand form. There is a course of instruction geared to the field in which you want to specialize. You study at *your* convenience, at *your* rate of speed. Your CREI instructors guide you carefully through the material, and grade your written work personally (not by machine).

Industry Recognizes CREI Training.

CREI courses are prepared, and taught with an eye to the needs and demands of industry, so your CREI diploma can open many doors for you. Countless CREI graduates now enjoy important,

good-paying positions with America's most important companies. Many famous organizations have arranged CREI group training for their radio-electronics-television personnel. To name a few: All America Cables and Radio, Inc.; Canadian Aviation Electronics, Ltd.; Canadian Broadcasting Corporation; Columbia Broadcasting System; Canadian Marconi Company; Hoffman Radio Corporation; Machlett Laboratories; Glenn L. Martin Company; Magnavox Company; Pan American Airways, Atlantic Division; Radio Corporation of America, RCA Victor Division; Technical Appliance Corporation; Trans-Canada Air Lines; United Air Lines. Their choice for training of their own personnel is a good cue for *your* choice of a school.



Benefits Felt Right Away.

Almost immediately, you feel the benefits of CREI training. Your employer, when informed of your step toward advancement (only at your request), is certain to take new interest in you and in your future. What you learn in CREI Home Study can start helping you do a better job immediately.

- BROADCASTING
- TELEVISION
- MANUFACTURING
- COMMUNICATIONS
- SERVICING
- AERONAUTICAL ELECTRONICS



CREI also offers Resident Instruction

at the same high technical level—day or night, in Washington, D. C. New classes start once a month. If this instruction meets your requirements, check the coupon for Residence School catalog.

INFORMATION FOR VETERANS

If you were discharged after June 27, 1950—let the new G. I. Bill of Rights help you obtain resident instruction. Check the coupon for full information.

Get this fact-packed booklet today. It's free.

Called "Your Future in the New World of Electronics," this free illustrated booklet gives you the latest picture of the growth and future of the gigantic electronics world. It includes a complete outline of the courses CREI offers (except Television and FM Servicing) together with all the facts you need to judge and compare. Take 2 minutes to send for this booklet right now. We'll promptly send your copy. The rest—your future—is up to you.



CAPITOL RADIO ENGINEERING INSTITUTE

An Accredited Technical Institute • Founded in 1927

3224 16th Street, N.W.

Washington 10, D. C.

MAIL COUPON TODAY

CAPITOL RADIO ENGINEERING INSTITUTE

Dept. 118 3224 16th St., N.W., Washington 10, D. C.

Send booklet "Your Future in the New World of Electronics" and course outline.

CHECK FIELD OF GREATEST INTEREST TV, FM & Advanced AM Servicing Practical Radio Engineering Broadcast Radio Engineering (AM, FM, TV) Practical Television Engineering Aeronautical Radio Engineering

Name.....

Street.....

City..... Zone..... State.....

Check— Residence School Veteran

WALSCO

HAS THE ONLY UHF ANTENNAS WITH AMAZING

X-77

INSULATOR


Hollow, unbreakable X-77
Insulator used exclusively on
Walsco Corner Reflector and
Reflecto-Fan.

X-77 insulator makes Walsco the most efficient, all-band UHF antennas in America. Nothing compares with it!

X-77 is hollow, allowing lead-in wire to pass through the center. Wire is kept completely out of field pattern. It eliminates broken wires caused by strain of wire on antenna terminals.

X-77 can't break . . . ever! It's 5 times stronger than polystyrene. Silicone treated to shed dust and moisture . . . not affected by extreme heat, cold or wind.

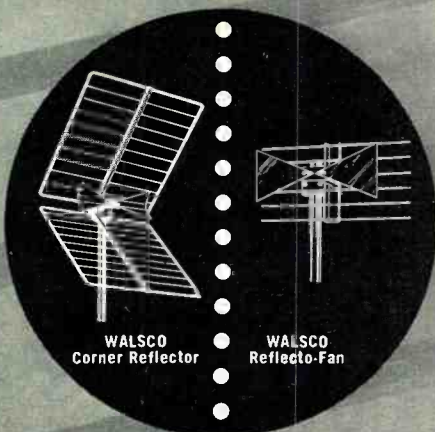X-77 is non-hygroscopic. Outstanding insulating qualities will last indefinitely.



Largest in demand everywhere

	Catalog No.	Description	Avg. Gain (db)	List Price
Reflecto-Fan	4400	Single Bay	7.0	\$ 6.75
	*4402	Dual Stack	11.0	14.25
	*4404	4 Bay Stack	14.5	35.00
Corner Reflector	4450	Single Bay	11.2	14.50
	*4452	Dual Stack	16.4	32.00

*Supplied with complete stacking kit.
Most not included in prices.

WALSCO

Walter L. Schott Co.

Los Angeles 18, Calif.
Chicago 6, Ill.

Overseas Representative: Ad Auriema, Inc., 89 Broad St., New York 4, N.Y.

ADVANCE! Raise your earning power—learn RADIO-TELEVISION-ELECTRONICS by SHOP-METHOD HOME TRAINING


GOOD JOBS AWAIT THE TRAINED RADIO-TV TECHNICIAN

There is a place for *you* in the great Radio-Television-Electronics industry when you are trained as National Schools will train you at home!


Trained technicians are in growing demand at good pay—in manufacturing, broadcasting, television, communications, radar, research laboratories, home Radio-TV service, and other branches of the field. National Schools Master Shop-Method Home Training, with newly added lessons and equipment, trains you in your spare time, right in your own home, for these fascinating opportunities. **OUR METHOD IS PROVED BY THE SUCCESS OF NATIONAL SCHOOLS TRAINED MEN, ALL OVER THE WORLD, SINCE 1905.**

EARN WHILE YOU LEARN

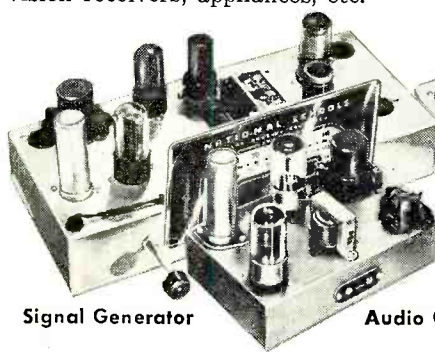Many National students pay for all or part of their training with spare time earnings. We'll show you how you can do the same! Early in your training, you receive "Spare-time Work" Lessons which will enable you to earn extra money servicing neighbors' and friends' Radio and Television receivers, appliances, etc.



Signal Generator

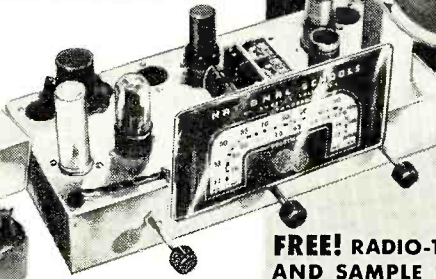


T. R. F. Receiver

Audio Oscillator

MASTER ALL PHASES!
Get Master Shop-Method Home Training from an Established Practical Resident School with its own Training Studios — almost 50 Years of Successful Experience in Training Ambitious Men.
We Bring National Schools To You!



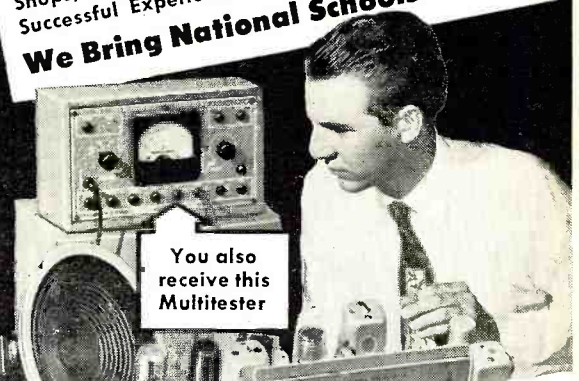Shops, Laboratories, Studios — almost 50 Years of Successful Experience in Training Ambitious Men.



You also receive this Multitester



Superheterodyne Receiver

LEARN BY DOING

You receive and keep all the modern equipment shown above, including tubes and valuable, professional quality Multitester. *No extra charges.*

FREE! RADIO-TV BOOK AND SAMPLE LESSON!


Send today for National Schools' new, illustrated Book of Opportunity in Radio-Television-

Electronics, and an actual Sample Lesson. No cost—

no obligation. Use the coupon now—we'll answer by return airmail.

APPROVED FOR VETERANS AND NON-VETERANS
Check coupon below

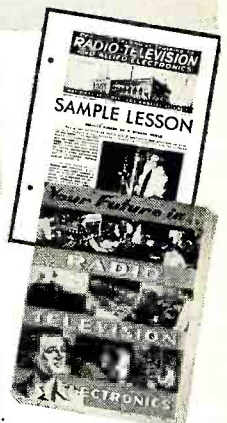Both Resident and Home Study Courses Offered!



National Schools Training is All-Embracing

National Schools prepares you for your choice of many job opportunities. Thousands of home, portable, and auto radios are being sold daily—more than ever before. Television is sweeping the country, too. Co-axial cables are now bringing Television to more cities, towns, and farms every day! National Schools' *complete* training program qualifies you in all fields. Read this partial list of opportunities for trained technicians:

- Business of Your Own • Broadcasting
- Radio Manufacturing, Sales, Service • Telecasting
- Television Manufacturing, Sales, Service
- Laboratories: Installation, Maintenance of Electronic Equipment
- Electrolysis, Call Systems
- Garages: Auto Radio Sales, Service
- Sound Systems and Telephone Companies, Engineering Firms
- Theatre Sound Systems, Police Radio
- And scores of other good jobs in many related fields.

TELEVISION TRAINING

You get a complete series of up-to-the-minute lessons covering all phases of repairing, servicing and construction. The same lesson texts used by resident students in our modern and complete Television broadcast studios, laboratories and classrooms!



NATIONAL SCHOOLS

LOS ANGELES 37, CALIFORNIA • ESTABLISHED 1905
IN CANADA: 193 E. HASTINGS STREET, VANCOUVER, B.C.

FIND OUT NOW—MAIL COUPON TODAY!



NATIONAL SCHOOLS, Dept. RH-83
4000 South Figueroa Street
Los Angeles 37, California

Mail in envelope or paste on postal card.

Send FREE Radio-TV Electronics book and FREE sample lesson. I understand no salesman will call on me.

NAME _____ AGE _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____
 Check here if released from service less than 4 years ago.
 Check here if interested in Resident Training at Los Angeles.

Specifically DESIGNED FOR

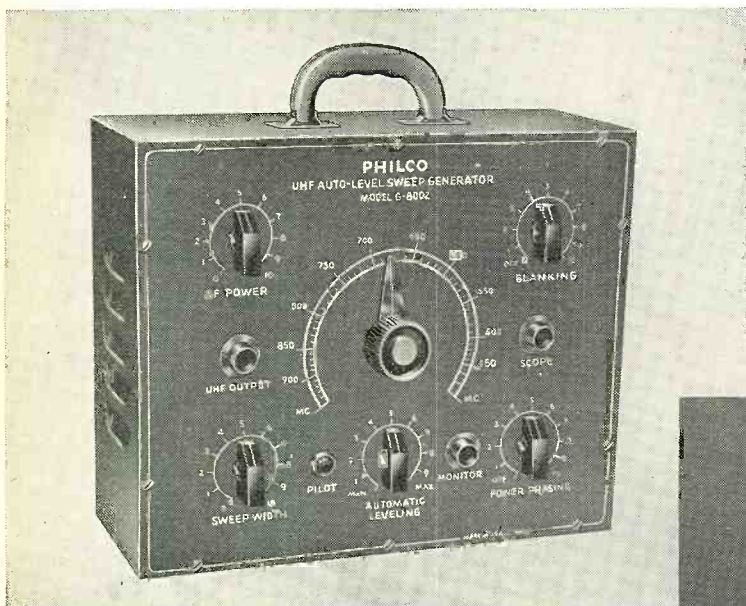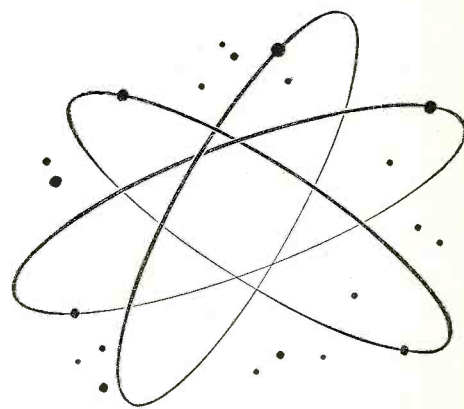

UHF Auto-Level Sweep Generator

Model G-8002. The newest, most modern, most inexpensive UHF sweep generator on the market. Checks sweep alignment with *any* test oscilloscope. Its output is controllable . . . makes possible overall trouble shooting and testing of low level units such as UHF tuners, boosters, converters, etc.

PHILCO
Test
Equipment



Field Strength Meter

Model M-8104. More features than any other unit at this popular price. Reads signal strength directly from the dial from 10 to 100,000 microvolts. A serviceman's time saver to measure actual TV picture signal strength.

NOW YOURS
ON NEW
EASY PAYMENT
PLAN




3-inch TV Oscilloscope

Model S-8200. The most practical portable unit available for bench or field servicing. Preset horizontal and vertical sweep rates take the guesswork out of trouble shooting. Ideal for television because of its high sensitivity and wide response.



Cathode Ray Tube Checker

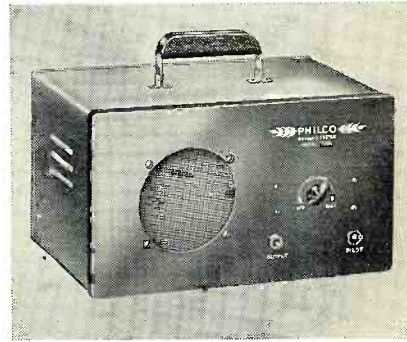Model 7053. Tests *all* picture tubes used in home TV receivers. Special cathode-ray tubes are easily checked by using plug-in adapters. Eliminates trouble shooting guesswork. Neon lamp indicates shorts and open elements in the electrodes of the gun.




Dynamic Signal Tracer

Model 7031. An extremely versatile instrument . . . this unit is designed for fast diagnosis of radio trouble by audibly monitoring RF and AF circuits. Can be used to accurately check P.A. systems, microphones and phonograph pick-up circuits.


THE SERVICEMAN

The Philco test equipment line is new! New circuits, new styling, new ruggedness, new versatility, new accuracy! Each piece of equipment is precision-built and now brings new features specifically designed *with your needs and your problems in mind!* Look over the individual instruments shown on these pages, and then mail the coupon below or get in touch with your Philco distributor to find out how easy it is to own a complete Philco Test Equipment Service Laboratory.

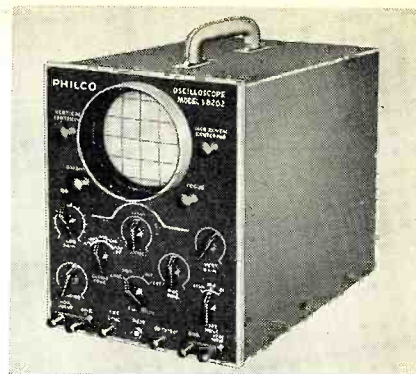

5-inch High Gain Oscilloscope

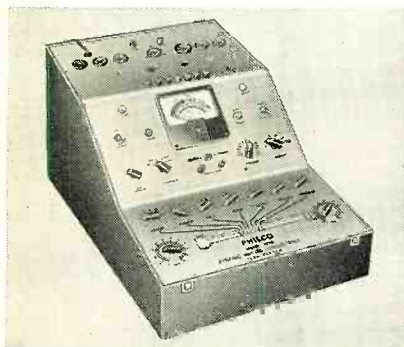Model 5-8202. This outstanding scope is built to the highest standards of test instruments... It features the highest gain 10 millivolts/inch, and widest frequency range at its popular price. Wide sweep ranges allow flexibility in sweep circuit trouble shooting.




Mutual Conductance Tube Checker

Model 7052. Tests more different type tubes than any unit on the market, from subminiature to acorn low power transmitting tubes... Forecasts tube life... employs roll chart instead of cards... for use as a portable or counter top unit.




Model M-8100

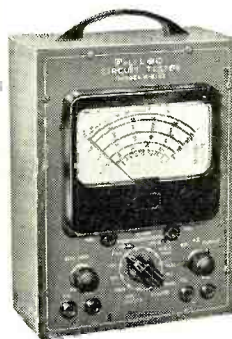

Model M-8102

Model M-8100. The rugged PHILCO CIRCUIT MASTER is one of the finest vacuum tube voltmeters ever designed. With its companion unit the famous...

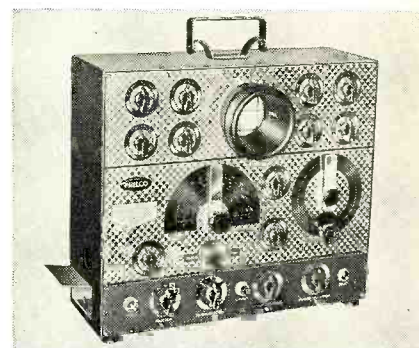Model M-8102. PHILCO CIRCUIT TESTER you have a combination engineered to meet the most rigid specifications for reliability, durability and accuracy of design.



Visual Alignment Generator

Model 7008. Combines in one economical instrument functions that can be approached only in a cumbersome collection of costly devices. No special scope connections are required for the most accurate visual alignment that is possible to achieve.


For new FREE BOOKLET fill out and mail this coupon
OR SEE YOUR PHILCO DISTRIBUTOR



VHF to UHF Signal Generator Adapter

Model G-8000. The most economical system yet designed to produce UHF signals for TV receiver tests. Through a conversion process this unit produces from an input VHF signal, UHF signals having the same characteristics as the VHF signal.

August, 1953

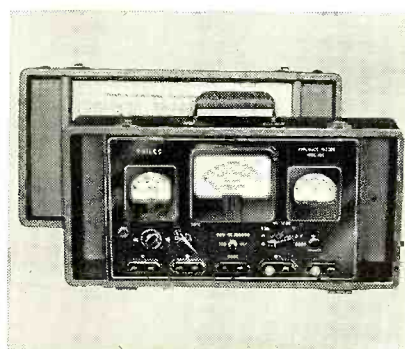

Appliance Tester

Model 5007. The ultimate in versatility. A one package, all purpose, portable appliance service unit. Permits over-all analysis of refrigerators, ranges, air conditioners and household appliances. With "pick-up" elements to determine temperature.

PHILCO CORPORATION
Accessory Division
Allegheny Ave. & "A" St.
Philadelphia 34, Pa.

I am interested in the Philco Test Equipment shown here. Please send me details of your SPECIAL PURCHASE PLAN for obtaining these units.

Please send FREE copy of your new booklet on Philco Test Equipment.

NAME

ADDRESS

CITY STATE





PREAMPLIFIER-EQUALIZER • MODEL 50-CM


"Of the very best!"

—HIGH FIDELITY MAGAZINE

The Fisher
"50" SERIES

Master Audio Control

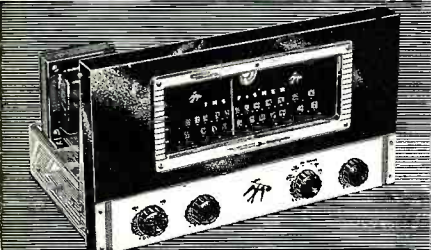■ Can be used with any amplifier. Inter-modulation distortion virtually unmeasurable. Complete, professional phonograph equalization settings and tone controls; genuine F-M loudness control; 5 inputs and 5 independent input level controls; 2 cathode follower outputs. Equipped with finest phono preamplifier. Self-powered. Chassis, \$89.50 • With cabinet, \$97.50



FM-AM Tuner MODEL 50-R

■ Features extreme sensitivity (1.5 mv for 20 db of quieting,) low distortion (less than 0.04% for 1 volt output,) low hum (more than 100 db below 2 volts output.) Armstrong system, AFC with switch, adjustable AM selectivity, separate FM and AM front ends, fully shock-mounted, cathode follower output, fully shielded, etched aluminum chassis. Self-powered. \$159.50


50-Watt Amplifier

■ Truly the world's finest all-triode amplifier, yet moderately priced. A man's size unit, with less than 1% distortion at 50 watts (.08% at 10 watts.) Intermodulation distortion below 2% at 50 watts. Uniform response within .1 db, 20-20,000 cycles; 1 db, 5 to 100,000 cycles. Hum and noise more than 96 db below full output. Quality components throughout. \$159.50

Write for complete specifications

FISHER RADIO CORPORATION
39 EAST 47th STREET • NEW YORK

ALL-TRIODE AMPLIFIER • MODEL 50-A

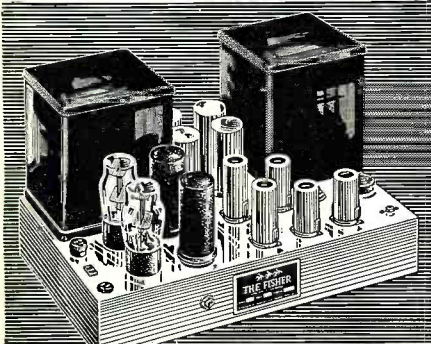

Within the
INDUSTRY

JAMES L. BYROM has been named to the new position of director of engineering for *General Dry Batteries, Inc.* of Cleveland.



The position was created as part of the company's broad program to strengthen its functional organization and to expand all phases of engineering activities in producing a full line of dry-cell batteries for radios, hearing aids, etc.

Mr. Byrom was formerly vice-president and general manager of the *Chandler-Evans Division* of *Niles-Bement-Pond Co.* and prior to that served *Underwood Corp.* and *National Carbon Co.* in engineering capacities.

DR. W. R. G. BAKER, *General Electric Company* vice-president and general manager of its Electronics Division, has been awarded the Medal of Freedom by the Honorable Earl D. Johnson, under-secretary of the Army.

Dr. Baker was awarded the medal for accelerating the application of electronics to the solution of Army research and development problems. He led a mission of leading scientists and industrialists to Korea in the summer of 1952, to study the problem of utilizing electronic devices and principles to the maximum extent in modern war, thereby increasing the effectiveness of the individual soldier and reducing the cost of human life.

LEO G. SANDS has been appointed to the post of sales manager of *Langevin Manufacturing Corporation* of New York.



Mr. Sands recently resigned as president of *Bogue Railway Equipment Division*, manufacturer of railway electrical and communications equipment. He had also served *Bogue Electric Manufacturing Company* as general sales manager.

In his new position, Mr. Sands will make his headquarters at the company's main offices at 37 West 65th Street, New York City.

RUSS DIERTH of the Chicagoland Chapter was unanimously elected national president of "The Representatives" at the organization's annual delegates' meeting held recently in Chicago. Norman B. Neely of the Los Angeles Chapter was the retiring president.

Wally B. Swank of the Empire State Chapter was named first vice-president, Dean A. Lewis of the California Chapter was elected second vice-president, and Ross Merchant of the Wolverine Chapter, third vice-president.

Ronald G. Bowen of the Rocky Mountain Chapter was elected national secretary while George Pettitt of the Chicago Chapter was named national treasurer.

Mose S. Branum of the Southwestern Chapter was elected to serve on the board of governors for a three-year term.

EDWARD L. NUNG, formerly manager of the Long Island City parts division plant of *Sylvania*, has been named manager of the tuner division of *P. R. Mallory & Co., Inc.* of Indianapolis . . .

DONALD H. KUNSMAN is the new vice-president of the *RCA Service Company*. He will be in charge of the consumer products service division . . .

CBS-Columbia Inc. has appointed **LOUIS HAUSMAN** to the post of vice-president. The firm is the television and radio receiver manufacturing subsidiary of the *Columbia Broadcasting System, Inc.* . . .

C. J. HARRISON has been named to the newly-created post of marketing manager for the television transmitter division of *Allen B. Du Mont Laboratories, Inc.* He will supervise field sales activity, order administration, the division's advertising and publicity program, as well as coordinate all contract processing . . .

EDWIN I. GUTHMAN, head of one of the largest independent coil manufacturing companies in the country, died recently of a heart attack. He was 49 years old at the time of his death. He was the president and founder of the *Edwin I. Guthman Co.* of Chicago . . .

General Electric Company's tube department has named **GRADY L. ROARK** to the post of manager of marketing with headquarters in Schenectady . . .

LEONARD L. ROSENFELD has been named production manager of *Jerrold Electronic Corporation*. He was formerly chief industrial engineer in the Joliet, Ill., plant of the *F. W. Sickles Division* of *General Instrument Corp.* . . .

WEBSTER E. BARTH has been appointed general sales manager of *La-Pointe Electronics Inc.* In his new post he will coordinate the sales efforts of all of the company's divisions.


THE MAGNETIC RECORDING INDUSTRY ASSN. has been recently formed by a majority group of the leading tape recording manufacturers in the U. S. The meeting to discuss the forma-

ONLY TELCO UHF ANTENNAS HAVE THE "WISHBONE"

TELCO

UHF

"WISHBONE" HIGH DI-ELECTRIC INSULATOR

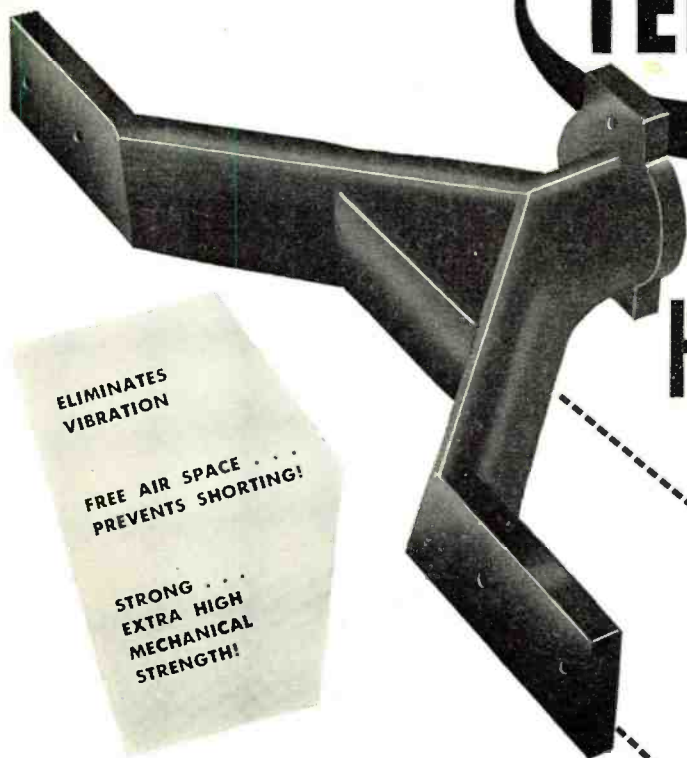


ELIMINATES
VIBRATION

FREE AIR SPACE . . .
PREVENTS SHORTING!


STRONG . . .
EXTRA HIGH
MECHANICAL
STRENGTH!

- EASY TO INSTALL
- ELIMINATES GHOSTS
- VERY HIGH GAIN

THAT'S RIGHT . . . Only TELCO'S got this remarkable new free air insulator . . . the "Wishbone" . . . that absolutely prevents shorting out under any conditions. Sturdy vibration-proof reflector and rugged aircraft aluminum elements are fastened to the "Wishbone" to prevent vibration and shaky pictures. Antenna performance is proved by actual UHF field testing . . . assures high gain on all channels. Better buy TELCO . . . your all-ways best UHF Antennas!

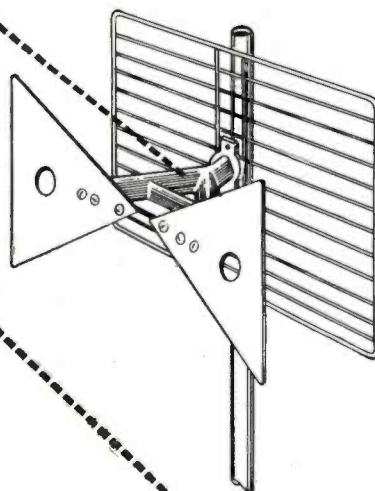

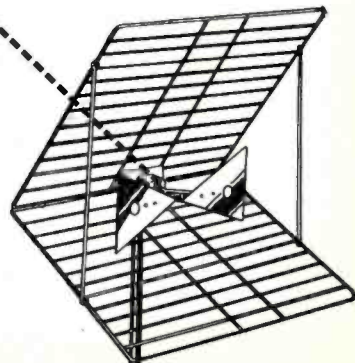No. 8965—Butterfly
Wishbone Antenna,
complete with
stacking bar.
List \$7.50



No. 8984 Wishbone
Corner Reflector.
List \$14.50




FREE! WRITE TODAY for all-new 32-page
TELCO Catalog. Send Postcard.

TELEVISION HARDWARE MFG. CO.

DIVISION OF GENERAL CEMENT MFG. CO.
904 TAYLOR AVENUE • ROCKFORD, ILLINOIS

A new concept
of recorded music

THE HEATHKIT *Dual* RECORD PLAYER KIT

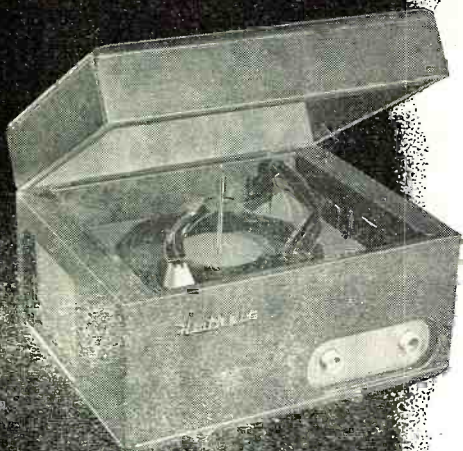

- Dual matched speakers for room filled perimeter sound
- Plays all record sizes, all speeds
- Newly developed ceramic cartridge
- Automatic shut off for changer and amplifier

MODEL RP-1

\$59.50

SHIPPING
WT. 30 LBS.

Shipped
Express
Only

Here is a *new* introduction to quality record reproduction. A simple to operate compact table top model with none of the specialized custom installation problems usually associated with high fidelity systems. Two matched speakers mounted in an acoustically correct enclosure reproduce *all* of the music on the record. Reproduction with the unique sensation of being in a halo of glorious sound.

production with the unique sensation of being in a halo of glorious sound.

The world famous VM Tri-O-Matic record changer plays all three record sizes at all three speeds. Automatic shut off for both changer and

amplifier after the last record is played. A wide range ceramic cartridge features an ingenious "turn-under" twin sapphire stylus for LP or 78 records without turning the cartridge. Simplified easy to assemble four tube amplifier featuring compensated volume control and separate tone control. Proxylin impregnated fabric covered cabinet supplied completely assembled. You build only the amplifier from simple step-by-step instructions. No specialized tools or knowledge required.

The Heathkit Dual Kit includes cabinet, VM player, speakers, tubes, and all circuit components required for amplifier construction. If a kit project has ever tempted you, here is the perfect introduction to an interesting and exciting pastime. Build the Heathkit Dual and enjoy unusually realistic room filling reproduction of fine recorded music.

OTHER *Famous*
HEATHKIT AMPLIFIERS

THE HEATHKIT 6 WATT AMPLIFIER KIT

Model A-7B

\$14.50

Ship. Wt. 10 lbs.
The Heathkit Model A-7B Amplifier features separate bass and treble tone

controls — two compensated inputs — three output impedances 4, 8, and 16 ohms — frequency response $\pm 1\frac{1}{2}$ db from 20 to 20,000 cycles — push pull beam power output at full 6 watts.

Heathkit Model A-7C with preamplifier stage..... **\$16.50**

HEATHKIT *High* FIDELITY AMPLIFIER KIT

\$35.50

Model A-9A
Ship. Wt. 17 lbs.

A 20 watt high fidelity amplifier especially designed for custom installations. Low hum and noise level 9 pin miniature dual triodes in pre-amplifier and tone control circuits. Four switch selected inputs. Frequency response ± 1 db 20 to 20,000 cycles. Output impedances of 4, 8, and 16 ohms.

tion of this new trade association was called by Joseph F. Hards, vice-president of *A-V Tape Libraries Inc.* Tape manufacturers and firms manufacturing related tape recording equipment voted unanimously to form the new association.

Tape recording manufacturers attending the initial meeting included *Ampex Electric Corp., Audio Devices, Inc., Bell Sound Systems, Brush Electronics Co., Crestwood Recorder Division of the Daystrom Electric Corp., Dukane Corporation, Fidelitone, Inc., Magnecord Corp., Minnesota Mining and Manufacturing Co., ORRadio Industries, Inc., The Pentron Corporation, Webster-Chicago Corp., and Webster Electric Co.*

Mr. Hards was elected president *pro-tem.* An organizing committee has been appointed to outline the purposes and functions, and to draw up the by-laws of the association.

* * *

EUGENE F. PETERSON has been appointed manager of marketing for *General Electric Company's* radio and television department.



He was formerly manager of marketing for the company's tube department with headquarters in Schenectady. He will now be located at the Electronics Park plant in Syracuse.

Upon graduation from college, and after serving a year as a professor of physics at Sterling College, Mr. Peterson joined the *G-E* test engineering program in 1933. He joined the Tube Department in 1934 and completed the company's advanced course in engineering in 1936.

He has served in various engineering and supervisory capacities at the company's Schenectady and Owensboro, Ky. plants. He was named manager of marketing for the tube department in 1951.

* * *

MILWAUKEE SCHOOL OF ENGINEERING recently celebrated its 50th anniversary with a banquet attended by state and civic dignitaries.

Founded in 1903 by Oscar Werwath, the school has grown until today it has an annual enrollment of 1500 full-time and 350 evening students. Nearly 50,000 students have received training at the school since 1903.

Karl Werwath, son of the founder, assumed the presidency upon his father's death in 1948. Another son, Heinz M. is controller and treasurer.

* * *

MOTOROLA, INC. of Chicago is currently celebrating its 25th year in the electronics field.

Founded in 1928 as *Galvin Manufacturing Company* by Paul V. Galvin, the firm had six employees and a capital fund of \$565. The company, now *Motorola, Inc.*, has since grown

(Continued on page 105)


HEATH COMPANY

BENTON HARBOR 15
MICHIGAN

Write For Free
CATALOG

New 32 page 1953 Catalog lists all kits, specifications, schematics and latest price information.

YOU SAVE BY ORDERING DIRECT FROM FACTORY

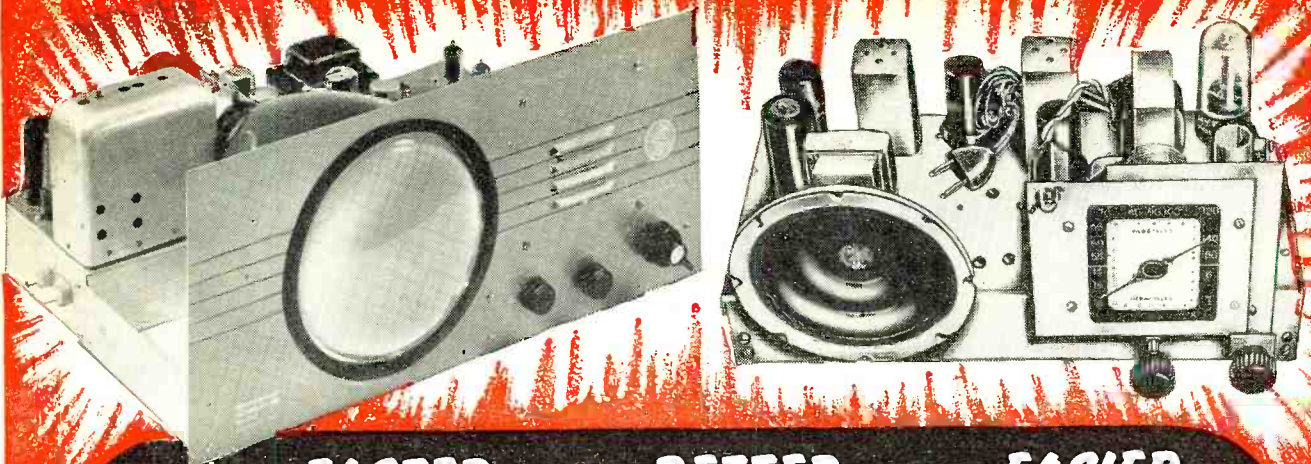

**TRAIN FASTER—TRAIN BETTER—TRAIN EASIER
 IN 10 MONTHS—OR LESS—FOR
RADIO-TELEVISION**


Our 21st Year Training Men for Greater Incomes and Security in Radio-Television

**I SEND YOU
 18 BIG KITS**

of Radio Television parts and equipment. Much of your training will be actual construction and experimentation . . . the kind of truly PRACTICAL instruction that prepares you for your Radio-Television career.



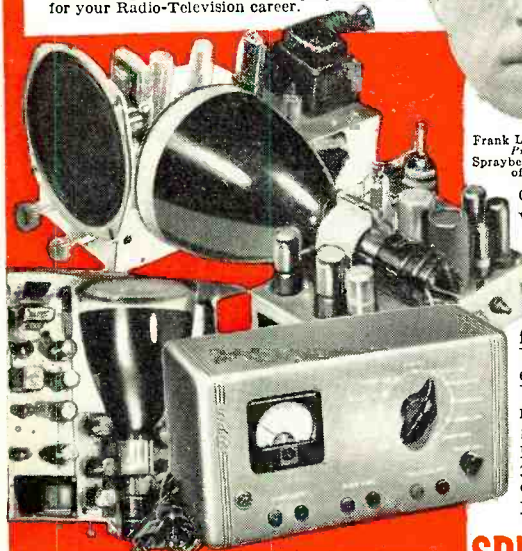Frank L. Sprayberry
 President
 Sprayberry Academy
 of Radio



YOU BUILD

the Television set and the powerful superhet radio receiver shown above. IN ADDITION to the other test units shown here (many are not shown because of lack of space). All equipment I send you is YOURS TO KEEP.

Approved for Veterans under the G. I. Bill



I invite you to get all the facts—

FREE TO YOU 3 BIG RADIO-TELEVISION BOOKS

I want you to have ALL the facts about my new 10-MONTH Radio-Television Training—without cost! Rush coupon for my three big Radio-Television books: "How to Make Money in Radio-Television" PLUS my new Illustrated Television Bulletin PLUS an actual sample Sprayberry Lesson—ALL FREE. No obligation and no salesman will call. Mail coupon NOW!

NEW! NO OBLIGATION PLA

You Have No Monthly Payment Contract to Sign Pay For Your Training as You Earn and Learn

You can get into Radio-Television, today's fastest growing big money opportunity field, in *months* instead of years! My completely new "package unit" training plan prepares you in as little as 10 months or even less! *No monthly payment contract to sign—thus NO RISK to you!* This is America's finest, most complete, practical training—gets you ready to handle any practical job in the booming Radio-Television industry. Start your own profitable Radio-Television shop . . . or accept a good paying job. I have trained hundreds of successful Radio-Television technicians during the past 21 years—and stand ready to train you, even if you have no previous experience! Mail coupon and get all the facts—FREE!

Valuable Equipment Included With Training

The new Sprayberry "package" plan includes many big kits of genuine, professional Radio-Television equipment. You perform over 300 demonstrations, experiments and construction projects. You build a powerful 6-tube 2-band radio set, multi-range test meter, signal generator, signal tracer, many other projects. All equipment and lessons are yours to keep . . . you have practically everything you need to set up your own profitable Radio-Television service shop.

Earn Extra Money While You Learn!

All your 10 months of training is IN YOUR HOME in spare hours. Keep on with your present job and income while learning. With each training "package" unit, you receive extra plans and "Business Builder" ideas for spare time Radio-Television jobs. New television stations everywhere, open vast new opportunities for trained Radio-Television Technicians—and those in training. If you expect to be in the armed forces later, there is no better preparation than practical Sprayberry Radio-Television training.

SPRAYBERRY ACADEMY OF RADIO 111 NORTH CANAL ST. Dept. 25-Z, Chicago 6, Ill.

MAIL COUPON TODAY! NO OBLIGATION

SPRAYBERRY ACADEMY OF RADIO, Dept. 25-Z 111 North Canal St., Chicago 6, Ill.

Please rush to me all information on your 10-MONTH Radio-Television Training Plan. I understand this does not obligate me and that no salesman will call upon me. Be sure to include 3 books FREE.

Name..... Age.....

Address.....

City..... Zone..... State.....

R_x for UHF's fringe areas!

CHANNEL MASTER'S all-UHF TWIN CORNER REFLECTOR

the most sensitive fringe area antenna ever developed for UHF!

- Two dipoles—actually two antennas in one.
- Provides twice the gain of any standard-type UHF Corner Reflector.
- Instantly installed in just three steps.
- Furnishes far better picture quality — at far greater distances.


Eliminates UHF's TWIN TERRORS. Features vibration-proof construction; and "free-space" terminals.




model no. 406

up to
16 DB gain!

gain above tuned
reference dipole

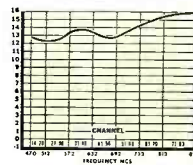

horizontal
polar pattern
(relative voltage)

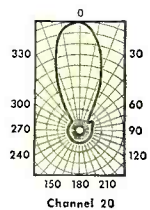


Channel 20



practically
no
assembly
necessary

CHANNEL MASTER'S 10-ELEMENT DELTA-WELD YAGI

custom-designed for your specific area!

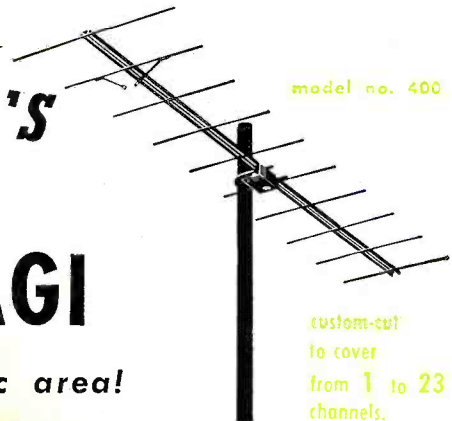

model no. 400

custom-cut
to cover
from 1 to 23
channels.

CHANNEL MASTER
engineering
pays off on **UHF!**

- Elements permanently **WELDED IN POSITION** on crossarm.
- Custom construction — designed for almost any UHF area.
- Delta-matched dipole for excellent impedance match.
- Brilliant performance. Average gain: over 11 DB, single bay; over 14 DB, stacked. Even higher on some models.
- Eliminates UHF's TWIN TERRORS.



CHANNEL MASTER CORP.
ELLENVILLE, N. Y.

Write for complete technical literature.



This man can save you service-time, work and money


YOUR Centralab Distributor has Custom Controls for 277 major manufacturer's listing in his Centralab Control Guide. Each is cataloged for quick reference so he can fill your orders accurately and systematically.

These controls are factory-specified type equipment on practically all major radio and TV sets on the market today. They're *exact* duplicates of the original part — some even closer tolerance than specified by the original set manufacturer — produced with the same modern, precision equipment and *carrying the same Centralab guarantee.*


To give you an idea of the wide usage, these 277 major manufacturers use these same controls in 50,552 different applications. That's a mighty strong tribute to the performance of Centralab controls!

Remember, when you use genuine Centralab replacements, you have assurance of a lasting repair job. Because they are custom-designed, you work faster . . . make a cleaner installation . . . insure greater customer satisfaction. That's why it's a good idea to see your Centralab Distributor *first* for genuine control replacements.


HERE ARE JUST 4 EXAMPLES OF THE WIDE USAGE OF CENTRALAB CONTROLS

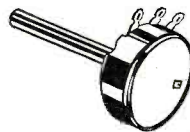

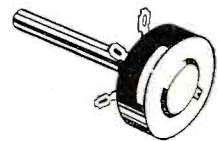
SV5-926 — Focus Control — used as original equipment by 6 manufacturers in 120 applications.



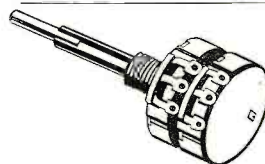S-119 — Volume Control — installed as original equipment on sets of 5 manufacturers in 12 applications.



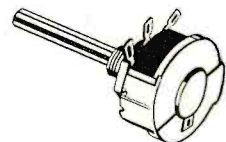SBB-505 — Vertical and Horizontal Hold Control — included as original equipment in 38 applications by 4 manufacturers.



F-122 — Volume Control — 6 manufacturers use this control as original equipment in 9 applications.

Centralab

A Division of Globe-Union Inc.

910-H E. Keefe Ave., Milwaukee 1, Wisconsin

In Canada, Box 208, Ajax, Ontario

August, 1953

29

*Now a new
synthetic
helps
dial telephone
service*



In a large, modern telephone office, two million relay contacts await the orders of your dial to clear a path for your voice. They open and close a billion times a day.



Unrolled view (one-third size) of capacitor unit wound with "Mylar." The transparent film is only 0.0005" thick yet stands handling without breaking.

AMONG the elements that guard your dial telephone service are electrical capacitors. They help prevent the formation of arcs that pit and may eventually destroy relay contacts. But millions more of these capacitors are needed each year. How could they be made less costly?

Bell Laboratories engineers, on the lookout for new materials, became alert to the possibilities of the new "Mylar" polyester film. A product of the Du Pont Company, "Mylar" is chemically the same as Du Pont's "Dacron" polyester fiber used to make fabrics. Bell engineers discovered that it also had remarkable dielectric properties—of just the right kind to help their capacitor problem.

The film takes the place of impregnated paper formerly used to separate the metal foil electrodes. It is tougher, stands more voltage and needs no impregnation. The new capacitors require no protective housing and are much smaller and less costly.

Here is another example of the way America's technology advances through the sharing of knowledge. Just as Bell Telephone Laboratories makes many of its discoveries—the Transistor, for example—available to other companies, so does it adapt the inventiveness of others when it can help your telephone service.



BELL TELEPHONE LABORATORIES

Improving telephone service for America provides careers for creative men in scientific and technical fields

RADIO & TELEVISION NEWS

FAR BETTER RECEPTION


IN EVERY LOCATION

with Sensational New

TRIO ZIG-ZAG


Patent Pending

TV ANTENNAS

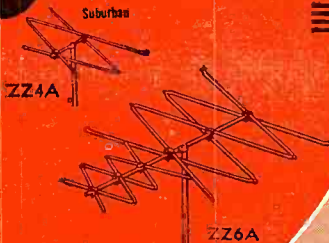


SUBURBAN MODELS

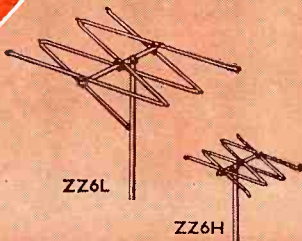Models ZZ4A and ZZ6A give you all-channel (2 thru 13) reception in ONE SINGLE BAY ANTENNA. The Model ZZ4A has excellent gain and is designed for suburban areas. Model ZZ6A has even greater gain and provides excellent all-channel reception in near fringe areas.




NEAR FRINGE MODELS

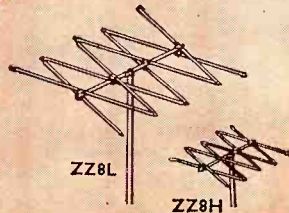For near fringe area reception, the Models ZZ6L and ZZ6H are recommended. Model ZZ6L covers Channels 2 thru 6, Model ZZ6H is for Channels 7 thru 13. Both antennas offer high gain with patterns and front-to-back ratios similar to cut-to-channel yagis.




FRINGE MODELS

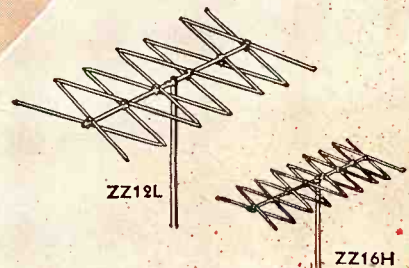Models ZZ8L and ZZ8H were designed for normal fringe area reception and provide clear, snow-free pictures. Forward lobe patterns and front-to-back ratios are similar to a good single channel, multi-element yagi.




ULTRA FRINGE MODELS

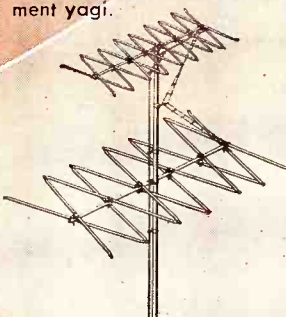The extremely high gains of the ZZ12L and the ZZ16H models provide unequalled reception in ultra-fringe areas. Model ZZ12L covers Channels 2 thru 6 and Model ZZ16H, Channels 7 thru 13. These two models when stacked, are fed with only one 300 ohm line and provide ALL VHF CHANNEL RECEPTION. Line match is excellent and front-to-back ratios are unusually high.



ZZ12L and ZZ16H are stacked for all VHF Channel Reception

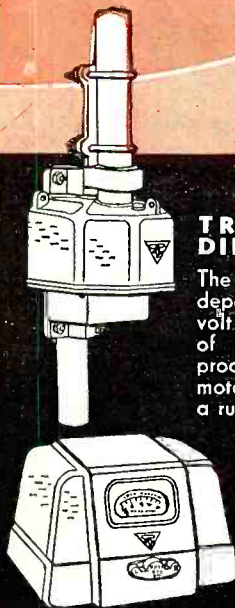* To provide even greater strength, TRIO Antennas now have stamped steel element clamps.



TRIO ROTATOR AND DIRECTION INDICATOR

The TRIO Rotator is America's most dependable — has two powerful 24 volt motors — one for each direction of rotation. Absolutely weather-proof, permanently lubricated. All motors, shafts and gears mounted on a rugged, one-piece casting for true alignment, strength and longer life. Every TRIO Rotator fully guaranteed for two years! Beautiful Direction Indicator has "finger tip" control — no need to hold knob for rotation. A touch of the finger starts it — a touch stops it!



TRIO

TRIO MANUFACTURING COMPANY

GRIGGSVILLE, ILLINOIS

Sweeping the Country!

**BUY DIRECT
AND SAVE**


'PRE-FAB'

COLLINS TUNERS and RECEIVERS

AUDIO PRODUCTS CO.

Collins Audio Products Co. is in no way affiliated with Collins Radio Co.

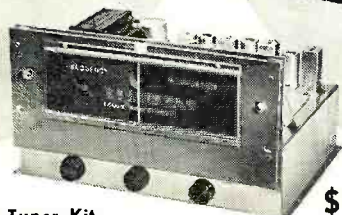Two ALL NEW Complete Kits for
Every High-Fidelity Need




FM Tuner Kit

\$55

The FM-11 tuner is available in kit form with the IF Amplifier mounted in the chassis wired and tested by us. You mount the completed RF Tuning Unit and power supply, then after some simple wiring, it's all set to operate. 11 tubes: 6J6 RF amp, 6AG5 converter, 6C4 oscillator, 6BA6 1st IF, (2) 6AU6 2nd and 3rd IF, (2) 6AU6 limiters, 6AL5 discriminator, 6AL7-GT double tuning eye, 5Y3-GT rectifier. Sensitivity 6 to 10 microvolts, less than 1/2 of 1% distortion, 20 to 20,000 cycle response with 2DB variation. Chassis dimensions: 12 1/2" wide, 8" deep, 7" high. Illustrated manual supplied. Shipping weight 14 lbs.

Each Collins Tuner Kit is complete with punched chassis, tubes, power transformer, power supply components, hardware, dial assembly, tuning eye, knobs, wire, etc., as well as the completed sub-assemblies: FM tuning units, AM tuning units, IF amplifiers, etc., where applicable. Since all these sub-assemblies are wired, tested and aligned at the factory, Collins Pre-Fab Kits are easily assembled even without technical knowledge. The end result is a fine, high quality, high fidelity instrument at often less than half the cost — because you helped make it and bought it direct from the factory. Bring your present reproducing system up to date with a new Collins Tuner.

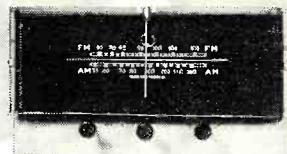


FM/AM Tuner Kit

\$77⁵⁰

The original 15 tube deluxe FM/AM pre-fab kit redesigned on a smaller chassis. The tuner now measures 14" wide by 12" deep by 7 1/2" high. This attractive new front and dial assembly opens up new applications where space is at a premium. Kit includes everything necessary to put it into operation — punched chassis, tubes, wired and aligned components, power supply, hardware, etc. Kit comprises FMF-3 tuning unit, IF-6 amplifier, AM-4 AM tuning unit, magic eye assembly and complete instructions. All tubes included. Shipping weight 19 lbs.

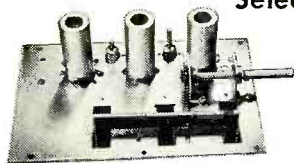Selected Basic Components For Special Applications



FMF-3 Tuning Unit

\$15²⁵


The best for FM. The most sensitive and most selective type of "front end" on the market. 6 to 10 microvolts sensitivity. Image ratio 500 to 1. 6J6 tuned RF stage, 6AG5 converter, 6C4 oscillator. Permeability tuned, stable and drift-free. Chassis plate measures 6 1/2" x 4 1/2". In combination with the IF-6 amplifier, the highest order of sensitivity on FM can be attained. Tubes included as well as schematic and instructions. Draws 30 ma. Shipping weight FMF-3: 2 1/2 lbs. Dial available @ \$3.85



IF-6 Amplifier

\$19⁷⁵

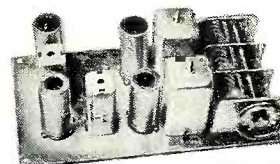
A remarkable value! 6 tubes are used in the IF amplifier: 6BA6 1st IF, (2) 6AU6 2nd and 3rd IF's, (2) 6AU6 limiters and 6AL5 discriminator. High gain, wide-band response (200 KC) for highest fidelity. 20 to 20,000 cycles. Distortion less than 1/2 of 1%. Draws 40 ma @ 220 volts. Chassis plate dimensions: 11-5/16" x 2 1/2" Shipping weight: 3 lbs.



AM-4 Tuning Unit

\$24⁵⁰

Tops in AM superhet performance! A 3-gang tuning condenser gives 3 tuned stages with high sensitivity and selectivity. Assembly is completely wired, tested and aligned ready for immediate use. Frequency coverage 540 KC to 1650 KC at a sensitivity of 5 microvolts. Tubes 6BA6 RF amplifier, 6BE6 converter, 6BA6 IF amplifier and 6AT6 detector. Draws 30 ma @ 220 volts. Mounts on a chassis plate measuring 4" x 7 3/8". Shipping weight 2 1/2 lbs. Dial available at \$3.85.

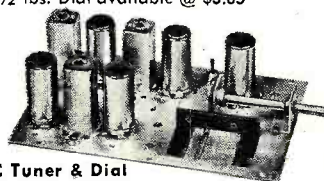

RD-1C Tuner & Dial

\$28⁵⁰

The COLLINS RD-1C FM tuner chassis is unique in the field. A whole, compact FM tuner and dial that fits in the palm of your hand. Convert AM sets to FM/AM receivers for only a few dollars! Unlimited applications where space is at a premium. Use in conjunction with your phonograph amplifier. Full frequency response to 20,000 cycles. Sensitivity 20 microvolts, permeability tuned. Tuning unit and IF amplifier on the same chassis plate. Draws 40 ma @ 100 volts. Tubes: 6AG5 converter, 6C4 oscillator, (2) 6AU6 IF amplifiers, 6AL5 in new ratio detector circuit. Shipping weight tuner and dial 5 lbs.

**MAIL
COUPON
TODAY**

To: Collins Audio Products Co. Inc.
P.O. Box 368, Westfield, N. J.
Tel. Westfield 2-4390

- FM Tuner Kit FM/AM Tuner Kit Slide Rule Dial Assembly
 FMF-3 Tuning Unit IF-6 Amplifier RD-1C Tuner and Dial
 AM-4 Tuning Unit

NAME.....

ADDRESS.....

CITY..... STATE.....

Amount for Kit \$..... See weights, add shipping cost \$.....

Total amount enclosed \$..... Check Money Order

WHEN YOU THINK OF TUNERS, THINK OF COLLINS AUDIO PRODUCTS

RADIO & TELEVISION NEWS

START ON THE ROAD TO SUCCESS

Study the RCA TV Servicing Course in your spare time

ARE YOU SATISFIED with the position you now hold? Do you feel you're worth more money? Are you pleased with yourself, your work, your associates . . . and your future? What does the next year hold for you . . . and the year after that?

Are you content merely to plod along through the best years of your life . . . or do you want to get into more pleasant work . . . hold a well-paid job . . . perhaps establish your own business?

If you are looking for a REAL opportunity . . . If you want to GROW with a GROWING INDUSTRY . . . If you want to grasp the success that should be yours, *then we say to you, study TV Servicing.*

Everyone knows that Television is the fastest growing industry today. Opportunities are going begging for men who have the training and ability to grasp them. *Now is the time to start on the road to success in TV Servicing.*

Study at Home in your spare time

The RCA Institutes Home Study Course in TV Servicing is easy to learn. You progress rapidly, step by step, as you learn the procedure of servicing and trouble-shooting TV receivers and installing TV antennas. Hundreds of pictures and diagrams help you understand the how-it-works information and the how-to-do-it techniques.


A Service of Radio Corporation of America

The RCA Institutes TV Servicing course was written and planned by instructors with years of specialized experience in training men. You get up-to-the-minute information, too, because you study right at the source of the latest developments in Television. Your lessons are carefully examined and accurately graded by competent teachers who are interested in helping YOU to succeed.

RCA Institutes is licensed by the University of the State of New York . . . an affiliate member of the American Society for Engineering Education . . . approved by leading Radio-Television Service Organizations.

It costs so little to gain so much

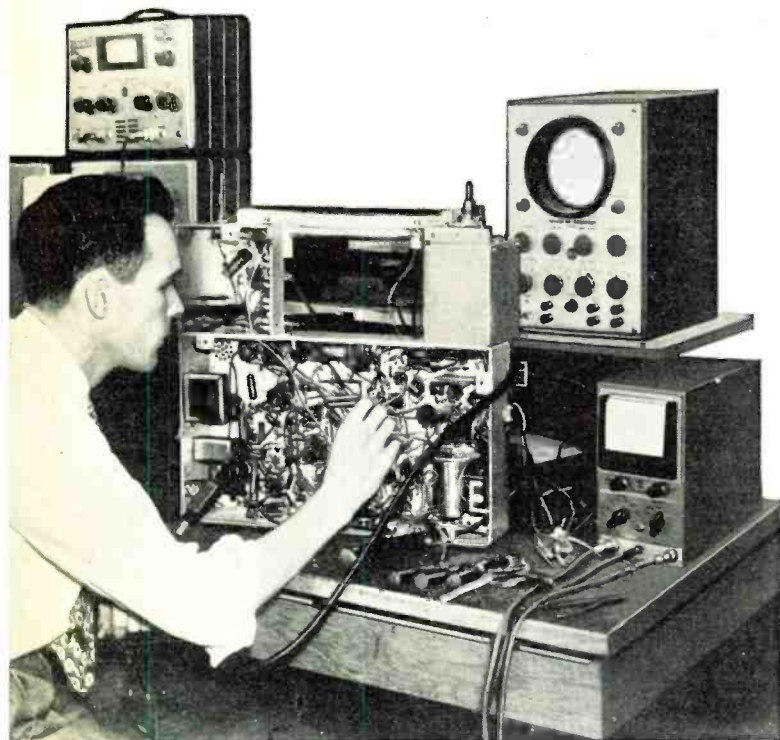RCA Institutes makes it easy for you to take advantage of the big opportunities in TV Servicing. The cost of the TV Servicing Home Study Course has been cut to a minimum. You pay for the course on a pay-as-you-learn unit lesson basis. *No other home study course in TV Servicing offers so much for so little cost to you.*



RCA Institutes conducts a resident school in New York City offering day and evening courses in Radio and TV Servicing, Radio Code and Radio Operating, Radio Broadcasting, Advanced Technology. *Write for free catalog on resident courses.*



RCA INSTITUTES, INC.
A SERVICE OF RADIO CORPORATION OF AMERICA
350 WEST FOURTH STREET, NEW YORK 14, N.Y.

SEND FOR FREE BOOKLET—Mail the coupon—today. Get complete information on the RCA INSTITUTES Home Study Course in Television Servicing. Booklet gives you a general outline of the course by units. See how this practical home study course trains you quickly, easily. Mail coupon in envelope or paste on postal card.



MAIL COUPON NOW!

RCA INSTITUTES, INC., Home Study Dept. RN853
350 West Fourth Street, New York 14, N. Y.

Without obligation on my part, please send me copy of booklet "RCA INSTITUTES Home Study Course in TELEVISION SERVICING." (No salesman will call.)


Name _____ (please print)

Address _____

City _____ Zone _____ State _____




320K SIG. GEN.
KIT \$19.95 WIRED \$29.95

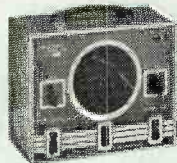


145K SIG. TRACER
KIT \$19.95 WIRED \$28.95



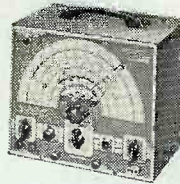
950K R-C BRIDGE &
R-C-L COMP. KIT \$19.95
WIRED \$29.95



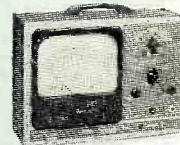
360K SWEEP GEN.
KIT \$34.95 WIRED \$49.95



New 214K VTVM KIT
\$34.95 WIRED \$54.95

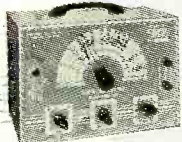

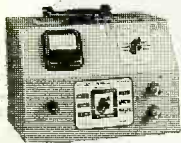
New 377K SINE & SQUARE
WAVE AUDIO GEN. KIT \$31.95
WIRED \$49.95



1040K BATTERY ELIM.
KIT \$25.95 WIRED \$34.95



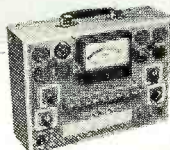1171K RES. DECADE BOX
KIT \$19.95 WIRED \$24.95




625K TUBE TESTER
KIT \$34.95 WIRED \$49.95



CRA PIX TUBE ADAPTOR
for Tube Tester \$4.50



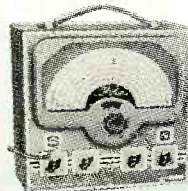New 565K MULTIMETER
KIT \$24.95 WIRED \$29.95
20,000 Ω/v ; 31 ranges




315K DELUXE SIG. GEN.
KIT \$39.95 WIRED \$59.95




HIGH VOLTAGE
PROBE \$6.95



221K VTVM KIT \$25.95
WIRED \$49.95

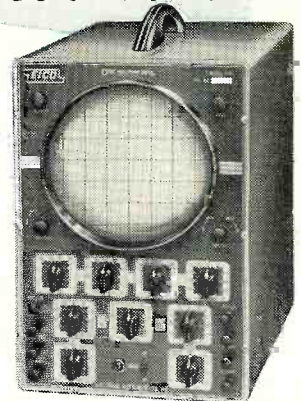

470K KIT \$79.95 WIRED \$129.50

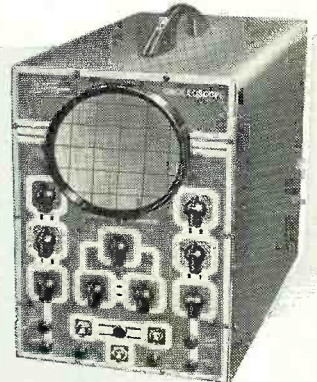

425K 5" PUSH-PULL SCOPE
KIT \$44.95 WIRED \$79.95



NEW!

MODEL 495-K SCOPE VOLTAGE
CALIBRATOR
KIT \$12.95 WIRED \$17.95

OVER 1/4 MILLION

EICO INSTRUMENTS

in use the world over!

EICO new modern facilities for research,
development and production—your greater
assurance of . . .

LABORATORY PRECISION AT LOWEST COST

NEW 7" Push-Pull OSCILLOSCOPE

- V Ampl: Resp. 10 cps — 1 mc \pm 2 db; Sens. 10 mv rms/in.
- H Ampl: Resp. 10 cps — 200 kc flat, —4 db at 500 kc; Sens. 0.3 volts rms/in. • V Input: 3-step freq.-compensated attenuator plus cathode follower; 3 meg Z. • H Input: Cathode follower; 1 meg Z.
- Both V & H Amps: push-pull output. • Sweep Range: 15 cps — 100 kc. • Sync: +INT., —INT., EXT., & 60 cps. • Distortionless V & H Trace Expansion & Centering to 1.5 X full screen. • Features: Return trace blanking; int. volt. calibrator; phasing control; direct connection to V plates of CRT. • At Front Panel: sawtooth, 60 cps outputs; intensity mod. & ext. sync inputs. • 10 tubes (6 dual-purpose) & 7JP1 CRT.

You Build EICO Kits in One Evening, but . . . They last a Lifetime! and You SAVE OVER 50%

YOU be the judge. See the famous EICO line TODAY — in stock at your local jobber — and SAVE!

Write NOW for FREE newest Catalog R-8.

America's greatest instrument values bear the name—



ELECTRONIC INSTRUMENT CO., Inc., 84 Withers Street, Brooklyn 11, N. Y.

FILM FOR TV

By
HENRY J. SEITZ, S.M.P.T.E.

As production costs continue to spiral, more and more of your favorite TV programs will come to you on film.

Fig. 1. Over-all view of the 16 mm television film projector designed and built by Radio Corp. of America.

IT IS an obvious conclusion that motion picture films are destined to play an increasingly important role in the future of television. To effectively demonstrate their products at lower cost and at the same time maintain standards comparable to live studio pick-up, alert business executives are turning towards the medium of film advertisement.

An ever increasing footage of commercial film flows daily out of processing laboratories. Kinescope recordings in New York City alone, according to a well-known trade publication, reach 2,000,000 feet per week. The techniques of laboratory quality control are most rigid wherever television is directly concerned.

Today phrases like "gamma," "print density" and "tonal gradation" appear in conversation with TV broadcast engineers. It would seem that a creeping technical revolution is slowly taking place, wherein tomorrow's technician must not only be well versed in electronics but in the art of photography as well. Some of the larger advertising agencies, as a matter of fact, employ skilled consultants whose job is to integrate the medium of film to that of television.


In lieu of moving pictures, advertisers will often employ pictorial stills or "telops" as they are sometimes called. (Fig. 2) These may be similar to standard 4x5 photo reproductions. In other cases a slide transparency may be used. Various effects such as dissolves, superimpositions, and even

emergency transmission of the TV station's test pattern can be achieved by using either of these devices. A dissolve-to-black, for instance, may be obtained by slowly cutting off the 500-watt lamp filament supply. (See Fig. 2)

Kinescope recording or the filming of moving pictures from the face of a special CRT offers unlimited horizons. In effect it conveniently satisfies the U.S. time zone differences. A hit show that begins at 8:00 p.m. New York time will hardly be acceptable to Californians, where it is only five o'clock in the afternoon. By kinescoping the live show and presenting it over the station's film facilities later in the evening, the sponsor's product is thereby advertised to a West Coast audience.

As an effective transducer for converting film images into their electrical equivalent, the iconoscope (Fig. 3) is presently among the most popular. Its grey scale response has a curve that closely approximates that of the average home television receiver. Furthermore film camera control operators favor the "Ike" because video gain riding is reduced to two major operating controls, namely, gain and pedestal. (Fig. 9)

Fig. 2. How the "telop" device is used to transmit static images in television work.

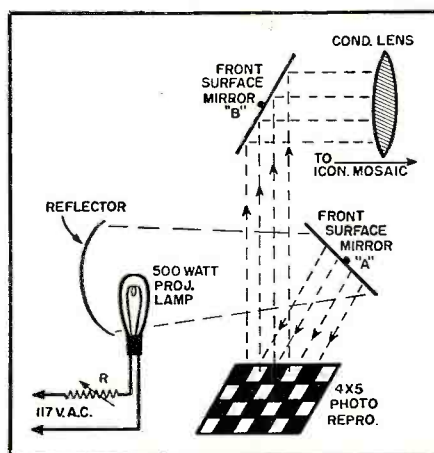

In this fashion shading problems are reduced to a minimum and necessary critical adjustments can be performed quickly and effectively. Except for ordinary routine maintenance, the iconoscope requires little attention once it has been correctly aligned.

Modern innovations like edge- and back-lighting, have reduced to a minimum certain drawbacks that were prevalent when iconoscopes were first employed. Many old time viewers will undoubtedly recall the anguish experienced whenever their celluloid hero disappeared into the flare at the viewing tube's edge, only to emerge later showered by secondary electrons. In those days the "Ghost Rider" really lived up to his name.

Before proceeding any further, certain basic characteristics of film might well be investigated. For example, an outdoor scene may register a brightness contrast (the ratio between the brightest and darkest values) of 150 to 1 or higher between the bluish light of the sky and the darkest of shadows. The human optical mechanism accounts for an adaptation of about 100 to 1. A theater-type motion picture projector is capable of yielding a screen brightness of 40 to 1. With home TV receivers approximating only 25 to 1, it can readily be seen that film quality is of paramount importance.

To effectively reproduce a good grey scale or tonal gradation between the highlights and shadows, print density should conform to certain basic standards. This, in turn, depends upon a sequence of factors that may well include (a) the photographic negative original; (b) laboratory processing, and (c) the final printing. Whether 16 or 35 mm, if the release or final print is able to reproduce many delicate shades of grey, it is called "low contrast" film.

On the other hand, films of "high contrast" (contrasty) are extremely black and white. Having little or no grey scale, the end result is a rather harsh picture and one lacking in fine detail. The measure of contrast is in-

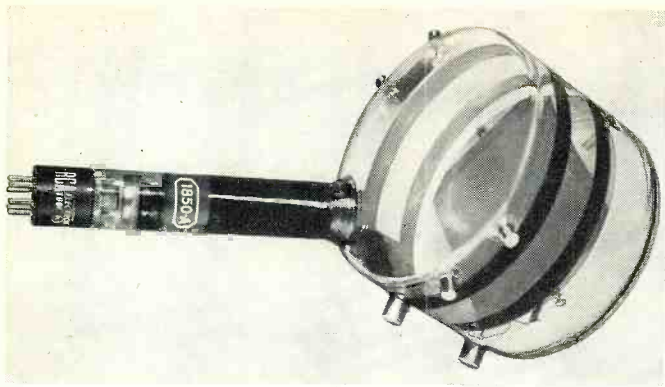


Fig. 3. Over-all view of RCA's Type 1850A iconoscope tube.



Fig. 4. RCA's 5WP11 transcriber kinescope for TV film work.

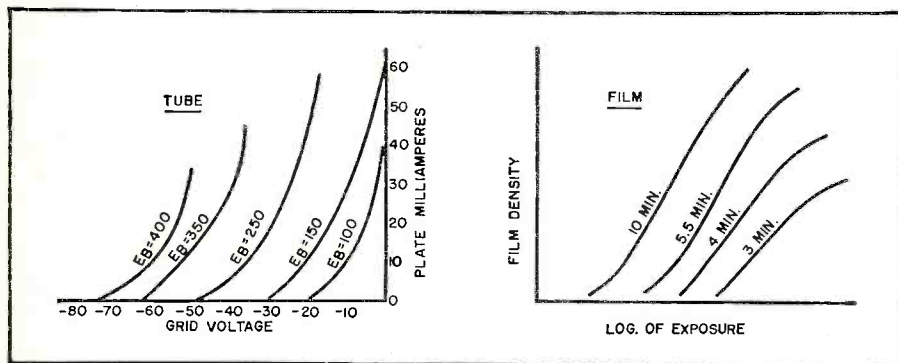


Fig. 5. Demonstrating the similarity between tube and film characteristic curves.

indicated by the letter γ (gamma) of the Greek alphabet.

Film also possesses its own series of characteristic curves remarkably similar to those of vacuum tubes with which we are all familiar. (Fig. 5) However, instead of E_p , E_s being the determinant factors, sensitometry makes use of the relationship between the two variables, exposure and density. Since tubes fall into specialized

groups (sharp cut-off, high μ , etc.) it conveniently follows that many types of film stock having countless variations (coarse grain, fine grain, slow speed) are also obtainable.

It can readily be seen that any decrease in light transmission caused by dense or contrasty film, will tend to limit iconoscope action to the lower portion of its own characteristic curve. (Fig. 11) Consequently flare, graini-

ness, and noise have a tendency to be accentuated. Noise acts to prevent the transmission of higher frequencies, so necessary to a sharp, snappy picture.

Obviously the best means of overcoming noise is to maintain a high signal-to-noise ratio. In the RCA unit preamplifier special attention is given to the critical film camera input stage. A Western Electric 417A dual miniature triode is used. The transconductance (G_m) of this amazing little tube is about 25,000. If we remember our musty classroom texts, ordinary run-of-the-mill triodes fall within a range of only 200 to 5000 micromhos!

This tube, when used as a cascode-type input feeding a 6J6 output (Fig. 8), vastly enhances iconoscope performance. The over-all gain is about three times that of the earlier 6AK5 which was 8. The heater operation is d.c. In addition, low inductance bypass condensers are inserted in the filament circuits. Sixty-cycle problems are thereby eliminated.


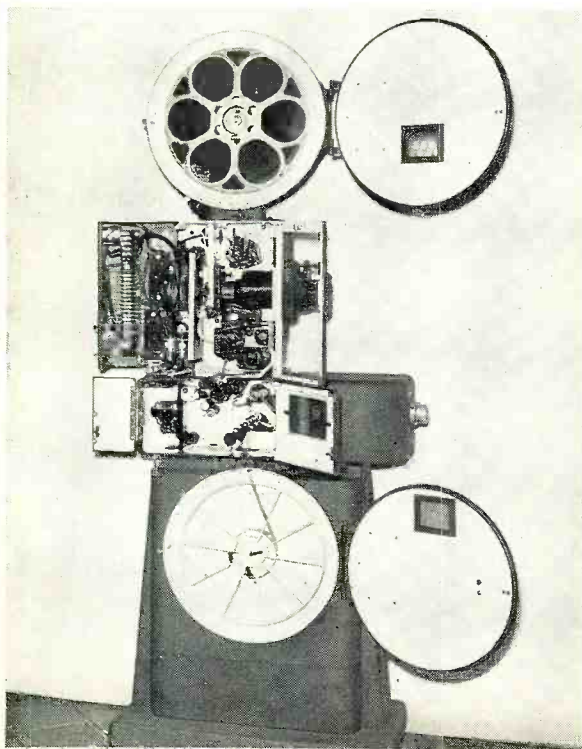


Fig. 6. Radio Corporation of America's TP-35B 35 mm television film projector unit. The intermittent is a three-sided Geneva movement driven by a specially-designed synchronous motor.

Fig. 7. One of the newer type pulsed light film projectors made by RCA. This machine eliminates the need for a shutter and is available in both 16 and 35 mm sizes for television film work.

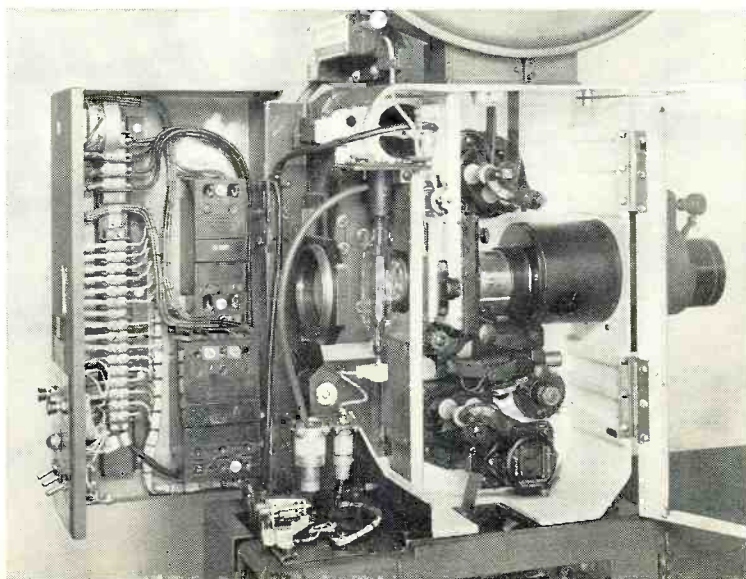


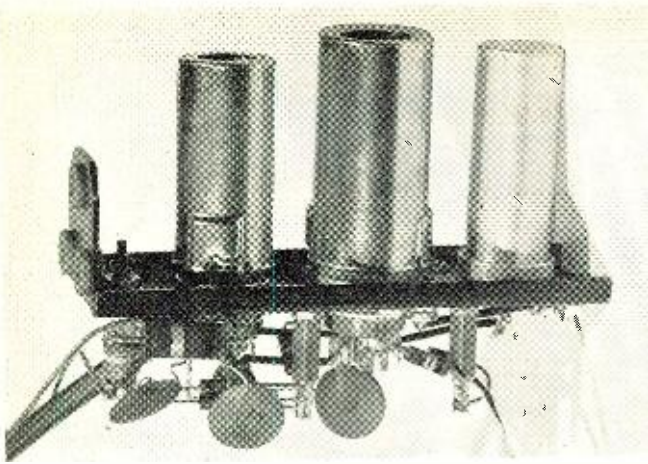


Fig. 8. Cascade preamp using the W.E. 417A (the middle tube).

Fig. 9. RCA's new TK-20A film camera control which consists of a console desk section with a control chassis mounted in lower compartment and camera monitor mounted in upper part. A picture amplifier fed by the preamp in the camera, pulse line amplifiers which feed driving signals from the studio sync generator to the camera and monitor, shading signal generators, and several associated camera controls are included in chassis.

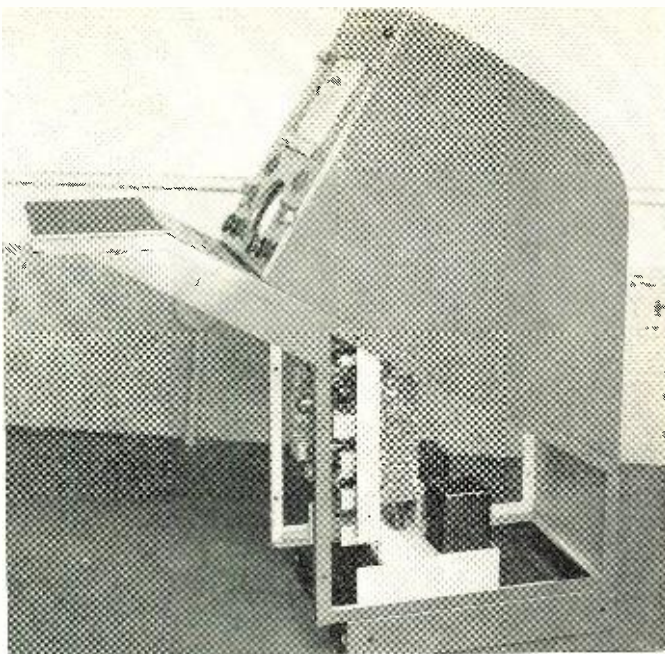

Since no subject is more frequently misunderstood, the conversion of moving picture film rate to conform to television standards requires some explanation. Fortunately a standardized projection rate of 24 frames or pictures-per-second holds for both the 16 and 35 mm systems.

In most 16 mm systems (Fig. 10), the projected light illuminating the film is momentarily interrupted by a notched rotary disc called the shutter. This permits the projector's film pull-down mechanism to operate while the screen is dark. Since the next successive film frame now rests in the film aperture, the intense light beam will easily pass through it whenever the notch and beam coincide.

In effect, each frame is projected either two or three times. However, since the entire action takes place in such a rapid sequence, (7.2 inches-per-second for 16 mm) the eye is tricked into believing that it sees a continuous motion of fast moving images.

Since the frame rate for television is 60 fields interlaced to produce 30 complete pictures-per-second, some means must be utilized to compensate for existing frame differences. Standard projection rates, as it was previously mentioned, consist of 24 frames-per-second. We have, therefore, a ratio of 5 to 4 to satisfy. In other words two frames of motion picture film will require the same amount of time as five TV fields or 2.5 TV frames. Therefore by flashing and scanning one film frame twice and the other three times, the difference in frame rate is conveniently satisfied.

Moving pictures consist of a series taken at a 24 frame-per-second rate. Each frame pauses a fraction of a second while being exposed. Conversely, the same principle applies in projection. Television film projectors, on the other hand, employ an intermit-

tent movement. Film advancing mechanisms in the latter type are categorized as 2 to 3 intermittents.

In the RCA TP-35B (Fig. 6) the intermittent is a three-sided Geneva movement driven by a synchronous motor. This pulls the film down at unequal time intervals (2:3). Thus a combination of mechanical motion plus iconoscope storage and scanning synthesizes to produce television moving pictures—a tribute to engineering ingenuity.

In a typical TV 16 mm system, (Fig. 1), a rotary shutter synchronized at 3600 rpm interrupts the projected light 60 times per second. The shutter is so designed that each flash lasts 1/1200th of a second. By accurately timing these flashes and causing them to fall within the system's vertical blanking period of 1270 microseconds, we impress upon the iconoscope's mosaic information which is then scanned and converted into a video signal.

As will be seen from Fig. 12 these intense bursts of light occur only before or after pull-down. In effect this prevents "travel ghost," a most unpleasant phenomenon, caused by non-synchronous action in the projector's shutter operation. The newer type of pulsed-light machine eliminates the need for a shutter and is available in both the 16 and 35 mm sizes (Fig. 7).

These light flashes coming from the projection lamp must at all times coincide or "lock-in" with the system's vertical blanking interval. Accurate synchronism is maintained by using a common source of a.c. for both the TV station's sync generator and the film projector motors. In addition synchronous type motors are used throughout.

Television recording or the transcribing of images by photographic means sounds complex, however when reduced to its basic fundamentals it

practically amounts to no more than a reversal of preceding film techniques. Instead of 24 film frames being converted to 30 pictures-per-second we now work backwards to convert 30 TV pictures to 24 film frames.

The cathode-ray tube, a 5WP11, from which the pictures are taken is one of high resolution and short persistence (Fig. 4). In comparison
(Continued on page 130)


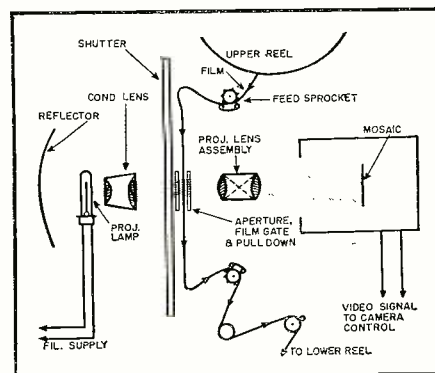



Fig. 10. Typical 16 mm TV-type film projector.

Fig. 11. Iconoscope characteristic curve (1850A).

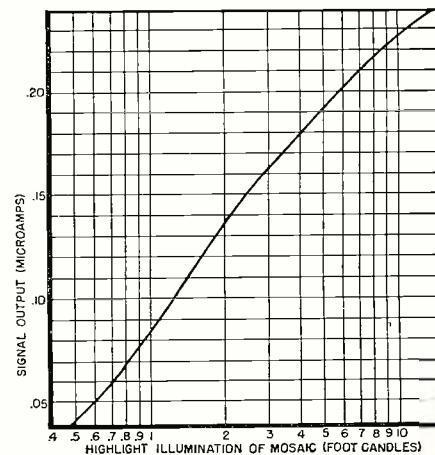

A SIMPLE ANTI-FLUTTER CIRCUIT

By JOHN K. FRIEBORN

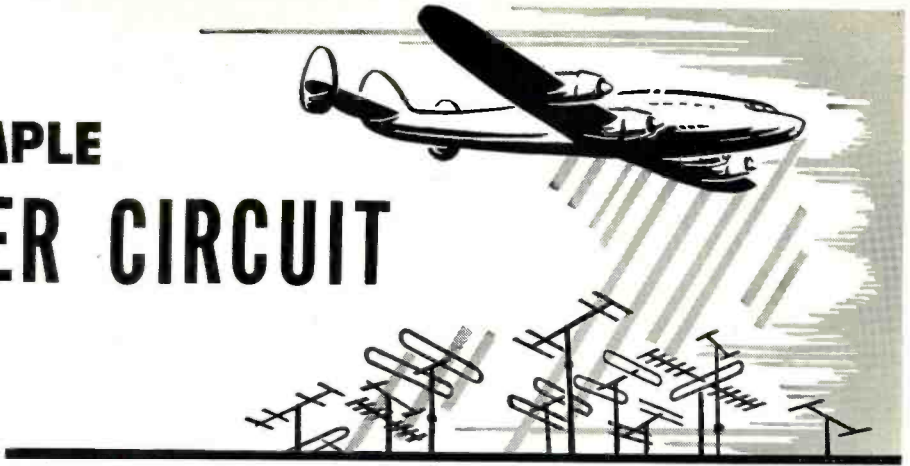

This simple British TV circuit may be used in U.S. receivers to eliminate airplane picture flutter.

MANY television set-owners have no idea what the effects of airplane flutter look like. A few, who live near airports, hardly know what a television picture would look like without these effects—unless their receivers contain some circuit to reduce them. Most recent American television receivers incorporate automatic gain control circuits which are “keyed” specifically to reduce one of the effects of airplane flutter. Keyed a.g.c. circuits are relatively complex; they require the addition of one tube and several other components to the receiver. Recent 21-inch *HMV* (British) television receivers use a simpler circuit which accomplishes about the same thing.¹ The fact that the circuit and several related ones are covered by a 1951 British patent² may or may not account for the fact that nothing of the sort seems to have been used by any American manufacturer in place of a keyed a.g.c. circuit.

Airplane flutter is the name given to the combination of effects on the television picture when a signal reflected from a moving aircraft is combined in the receiver with the direct signal from the station. There are two main effects: first, a “ghost” picture is produced and second, there is a fluctuation in the over-all average brightness of the screen. By using an extremely directional antenna, both effects can be reduced, unless the aircraft is nearly the same direction from the receiver as the transmitter. If a sufficiently directional antenna is impractical, appropriate receiver circuits can at least reduce the amount of brightness fluctuation.

A reflected signal may be in-phase with the direct signal and add to it or out-of-phase and subtract from it. The exact phase relation will depend upon the difference between the times taken by the signal to travel over the direct and reflected paths. If the time difference is exactly enough to allow the r.f. signal to complete a whole number of cycles, the two signals will be in-phase, although they may have slightly different instantaneous modulations. The modulation of the reflected signal, which travels for the longer time, corresponds to an earlier part of each line in the original

picture. Therefore, the modulation corresponding to a certain point on the original scene appears later (that is, farther to the right) in the ghost image than in the direct signal image. If the time difference between the two paths is exactly enough to allow a whole number of cycles of the r.f. signal and one-half cycle more, then the signals are out-of-phase and the resultant is generally (neglecting difference in modulation) less than the amplitude of the direct signal alone.


If the signal is reflected from a moving object, such as an airplane, the combined amplitude is increased, decreased, and then increased again, possibly several times. This variation in signal strength results in a variation in the brightness of the reproduced picture on any receiver which can follow these changes in the d.c. component of the video signal. The frequency of the brightness fluctuations depends upon the speed of the aircraft, its position and direction of flight with respect to the transmitter and receiver, and the frequency of the r.f. carrier. A typical range of frequencies under

different conditions and on different v.h.f. television channels is from 0.1 to 40 cycles-per-second. The most rapid variations are masked by the persistence of the picture tube phosphor and persistence of vision of the eye, while the slowest variations are not particularly objectionable. The frequency range of objectionable fluctuations may be from approximately 0.5 to 10 cycles-per-second.

Since the fluctuations in brightness are caused by variations in signal strength, one obvious solution to the problem is to keep the signal strength constant by means of an automatic gain control circuit. It should be noted that it is the peak amplitude of the signal which is kept constant by an ideal a.g.c. circuit, so that variations in the average signal strength due to variations in the average brightness of the original scene are reproduced at the receiver. Compensation for such rapid variations in signal strength as those caused by airplane flutter requires a short time constant in the automatic gain control circuit. However, the shorter the time constant in the a.g.c. circuit, other things being equal, the more the circuit is affected by noise. One method of reducing the effect of noise while retaining the short time constant is to key the a.g.c. circuit on for short periods of time and key it off for long periods in between. A keyed a.g.c. circuit is, of course, affected only by the noise which occurs during the small fraction of the total time when it is keyed-on. Keyed a.g.c. is an effective solution to the problem of airplane flutter (or at least to the brightness-fluctuation part of the problem), but it is complicated.

A different approach to the problem is based on the fact that the fluctuations in brightness are, in effect, spurious video signals of very low fre-

Fig. 1. Partial schematic of the British *HMV* 21-inch receiver showing the anti-flutter circuit described in the text.

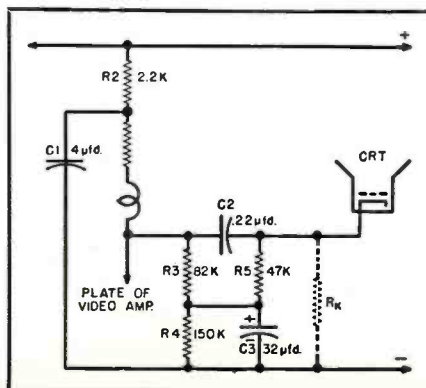

quencies. One simple way to eliminate these very low video frequencies is by using capacitive coupling in the video amplifier and omitting d.c. restoration. This method has two related disadvantages: first, the average brightness is the same for every scene, regardless of what it was originally and second, with the average brightness constant, the blanking level varies, so that additional blanking circuits are necessary to keep the retrace lines from becoming visible occasionally.

The method used in the HMV receiver mentioned at the beginning of this article reduces the d.c. component about 50%, but it reduces the amplitude of the most objectionable flutter frequencies much more. A partial schematic diagram of the receiver is shown in Fig. 1. This circuit provides a boost of extremely low-frequency and d.c. components of the video signal in the plate circuit of the video amplifier, by means of R_2 and C_1 , then two separate paths for the video signal from the video amplifier plate to the picture tube cathode. The a.c. components of the signal (frequencies from 50 cycles up, under the British standards) are transmitted through C_2 without much loss. The d.c. component is boosted almost 50% by R_2 , then applied through R_3 , R_4 , and R_5 , the cathode input resistance of the picture tube. The net transmission is said to be about 55%, which would mean a value for R_2 of about 140,000 ohms. At one cycle-per-second, the transmission via both paths is reduced so that the combined transmission is only about 9%. The overall transmission characteristic is approximately as shown in Fig. 2. This graph shows that the attenuation is considerable over the entire band of frequencies involved in airplane flutter.

A theoretical disadvantage of the circuit of Fig. 1 is that very rapid changes in the average brightness of the original scene would not be realistically reproduced, but such rapid changes hardly ever occur. Probably most people living near airports would be willing to sacrifice perfect reproduction of an occasional lightning flash on a television program in order to have a simple method of reducing airplane flutter.

Many American television receivers which do not have keyed a.g.c. could be modified to incorporate anti-flutter circuits of this type. Several observations can be made which would save some "cut-and-try" time for experimenters wishing to make such modifications.

First, since the circuit is basically a bandstop filter, it may be thought that circuits such as the Wien bridge, the bridged-T, or the parallel-T would be better, since they give almost no output at all at their null frequencies, whereas the original circuit does transmit 9%. The greater attenuation might be desirable, but these circuits have bandwidths less

than the one in Fig. 1, so that they may not be effective over as wide a range of flutter frequencies. Also, they require more components.

Second, the original circuit was found to be satisfactory in a receiver tuned to the London television channel, a frequency of less than 50 megacycles. The highest American v.h.f. channel being more than four times as high in frequency, American receivers could be subject to flutter frequencies more than four times as high as those for which the original circuit was found to be effective. The best compromise for all of our channels probably would be obtained with a time constant approximately twice as high as the original, that is, a frequency of maximum attenuation of about two cycles-per-second, instead of one.

Third, it may be desirable to transmit the d.c. component without the 45% loss. This can be done by increasing the values of R_2 and R_4 in Fig. 1. The limit of increasing R_4 would be to make it infinite (that is, an open circuit—omit it altogether). We would still have some resistance effectively in parallel with C_3 , the leakage resistance of the condenser, which would reduce the d.c. component of the video signal slightly.

Fourth, if the anti-flutter circuit is used in a receiver which has d.c. reinsertion, it must follow the d.c. reinsertion; otherwise, the d.c. reinsertion will cancel out the effect of the anti-flutter circuit. This fact makes it a bit difficult to use the circuit in receivers which have any type of d.c. reinsertion except that based on video amplifier grid-leak bias.

Fifth, the effects of the resistors in the network on the d.c. potentials on the picture tube must be taken into account and compensated for if necessary.

Sixth, the values of the components must be suitable to the impedance level at the point in the receiver where the circuit is to be inserted.

Seventh, the wiring must be carefully done in such a way as to add a minimum of shunt capacitance to the video circuit, as excessive added capacitance would disturb the original high-frequency compensation.

Two typical examples of receivers which can be modified to include this

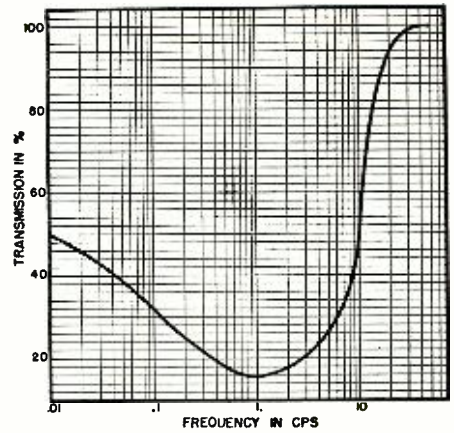


Fig. 2. Low-frequency transmission characteristic of the circuit in Fig. 1.

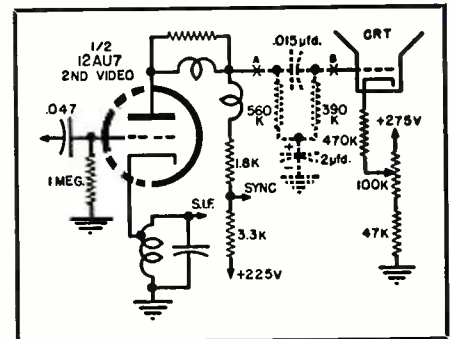



Fig. 3. Partial schematic of the Majestic Series 106 TV receiver showing (dotted) the modification to eliminate flutter.

anti-flutter circuit without too much difficulty are shown in Figs. 3 and 4. The component values given in the modified circuits are tentative and may have to be adjusted in a particular receiver to restore the original picture tube potentials or to give maximum reduction of the flutter frequency which is found most troublesome in a particular location.

The Majestic Series 106 TV receivers use a diode a.g.c. circuit, grid-leak bias d.c. reinsertion, and grid drive to the picture tube. Modification of this circuit consists simply of inserting the new components between the peaking coils and the grid of the picture tube, see Fig. 3, paying attention to the caution about wiring capacitance given previously.


Fada TV receiver Model S7C20 uses
(Continued on page 78)

Fig. 4. (A) Original video circuit of the Fada Model S7C20 TV receiver. (B) Anti-flutter modified circuit showing additions required to maintain circuit voltages.

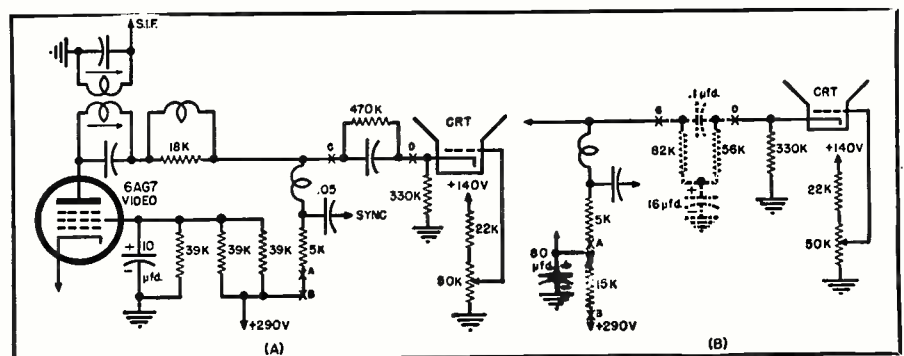

CHOOSE THE PROBE TO FIT THE TEST

By
ART LIEBSCHER *

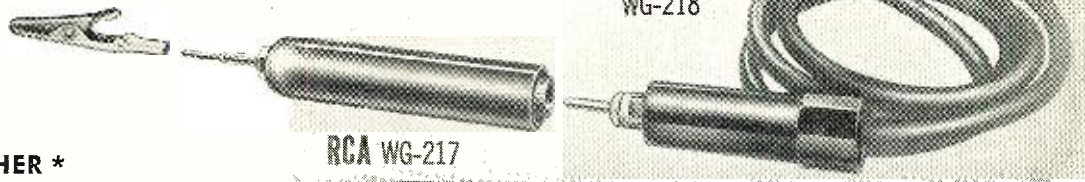

(Left) The RCA WG-217 isolating probe for d.c. voltage measurements. (Right) Direct WG-218 unit which is used for low-frequency a.c. voltage measurement.

IN THE servicing of modern electronic devices, accuracy of measurement is the prime requisite for fast, positive analysis of circuit performance.

Under ideal circumstances, a test instrument would measure the full voltage in any electronic circuit. The instrument would have infinite input resistance and zero shunt capacitance; therefore, it would not cause any detuning, produce any alteration of waveform, nor develop any other detriment to normal operation of the circuit being tested.

From a practical viewpoint, however, it is well recognized that the contact of any measuring device has its immediate effects on the operation of an electronic circuit. Depending on the type of circuit being tested, the actual degree of this effect may vary from negligible shunting to susceptibility to the very approach of a test prod.

While some small amount of power from the circuit must be shared with the resistive input of the testing facilities, those facilities which hold power-sampling requirements to a minimum consistent with stability and accuracy most nearly approach the "ideal." Where high-frequency circuits are concerned, the detuning caused by test prod and cable capacitance is often more serious than the resistive loading problem. Together, these problems so complicate the measurement of electronic circuits as to require complete departure from the use of low-impedance, unshielded test instruments with open-wire test leads. Coping with any one problem leads to a train of problems, each of which must be fully solved to insure accurate and stable readings.

Resistive loading can be minimized by the use of high-impedance electronic measuring instruments. The circuits in such instruments, however, are not normally designed to discriminate between all of the desired and undesired potentials to which they are subjected. Therefore, they must be shielded from extraneous electrostatic and electromagnetic fields which would introduce hum, noise, and other unwanted interference. For this reason, the majority of vacuum-tube volt-

The scope or v.t.v.m. probe you select will affect the test results obtained. Here are pointers on choosing the right one.

meters and oscilloscopes are equipped with metal cases. But the problem of shielding does not end with the case alone, for there must be an electrical link between the point of circuit measurement and the test instrument. This link, in the form of a test lead, must also be shielded. If the test lead is viewed as an extension of the electronic measuring circuit contained in a shielded test-instrument case, the logic of shielding the test lead right up to the tip of the test prod becomes obvious.

Unshielded test leads are sometimes responsible for obscure effects which hinder measurement accuracy. A test lead often acts as an antenna in picking up the signal from one circuit and re-radiating it to another circuit in the device being tested. In this way cross-coupling is established between normally shielded sections of a receiver or other electronic device, even to the extent that regeneration or oscillation occurs.

Although test-lead shielding serves to exclude interference, it increases circuit loading at high frequencies because the capacitance of the shielded wire lowers the effective input impedance of the measuring instrument. However, the capacitance added by the shielded lead is fixed and remains unchanged irrespective of the position or movement of the lead.

The effect of added capacitance can be removed and the smaller loading effect characteristic of open-wire test leads restored through the use of a low-capacitance test probe in conjunction with the shielded lead. The reduction in capacitance, however, is accompanied by a loss in signal voltage entering the test instrument. Low-capacitance probes, therefore, are designed to increase the input resist-

ance of the test instrument. When the signal loss in the probe is regained by amplification in the test instrument, the desired qualities of high input impedance, freedom from interference, and minimum circuit loading are obtained.

Probes, originally used as test prods and intended for convenience in handling the ends of flexible test leads, have now become housings for various circuit components. These components are often required at the point of test contact for least disturbance to the circuit and for maximum efficiency in supplying measurable currents through the test cable to the instrument. Input specifications for test instruments should, therefore, be specified *at the probe*, if they are to represent the true conditions of test application. Panel input terminal specifications are meaningless where test cables must be added to make use of an instrument, for it is as impractical to do without the cable as it is to hold the entire instrument against the circuit being tested.

While many electronic test instruments are now equipped with shielded cables, only a few have input cables which are designed for use with a number of different probes. The RCA WG-218 direct probe and cable accommodates four varieties of slip-on probes which are now available. Having assorted and quickly interchangeable probes is like acquiring additional instruments.




In order to become familiar with the application of various types of probes now commercially available, it is well to consider them first by functional classification. The major classifications are: direct probes, low-capacitance probes, isolating probes, rectifying probes, and multiplying probes.

Direct Probes

The RCA WG-218 direct probe and

RADIO & TELEVISION NEWS

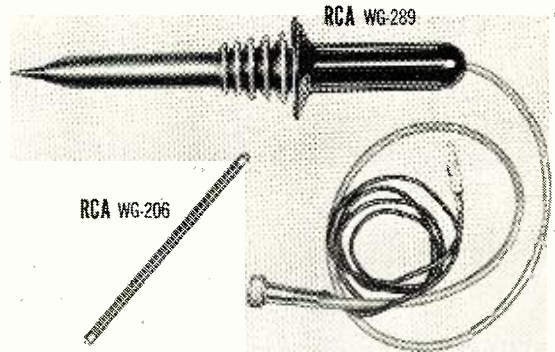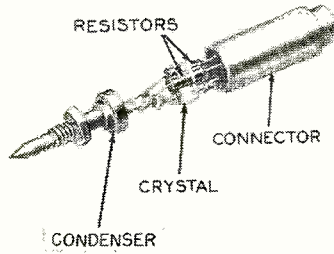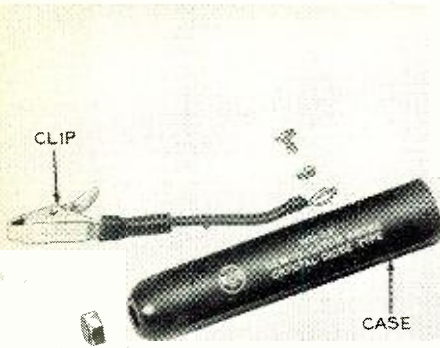* Formerly Test Equipment Specialist, Tube Dept., Radio Corporation of America, Camden, New Jersey



The RCA Model WG-291 demodulator probe of the crystal diode type. See text for details on the various circuit applications for this probe.

WG-289 high-voltage probe with auxiliary WG-206 unit. Latter unit is added to probe to provide required voltage division.


cable is a "straight-through" connection-type test probe attached to a single-lead shielded cable. It possesses the normal electrical characteristics of the cable itself. This probe and associated cable have been standardized for use with RCA oscilloscopes and "VoltOhmysts," their principal application being for the transfer of electrical information from a circuit (or slip-on probe) to the input connector on the instrument. When used with RCA "VoltOhmysts" and oscilloscopes, this cable provides an over-all input capacitance of approximately 80 $\mu\mu\text{fd}$. Because the maximum frequency range of the cable-and-instrument combination varies inversely with the impedance of the voltage source, it is impractical to state one maximum frequency limit. In general, all low-frequency voltages, even those with complex waveforms, can be measured in both low-impedance and high-impedance circuits. Accurate measurement at higher frequencies is limited to lower-impedance circuits.

The direct probe and cable cannot be used in the accurate measurement of voltages of complex waves or pulses having considerable high-frequency content because cable-capacitance loading acts to reduce those voltages. Means for reducing or eliminating the effects of this input capacitance will be discussed in connection with the following probes, most of which are designed for use in conjunction with the WG-218 direct probe and cable.

Low-Capacitance Probes

The use of a small condenser in an oscilloscope probe, connected in series with the capacitance of the shielded test lead, provides a voltage divider having very small input capacitance. This is typified by adding an RCA WG-216B low-capacitance probe to the direct probe and cable.

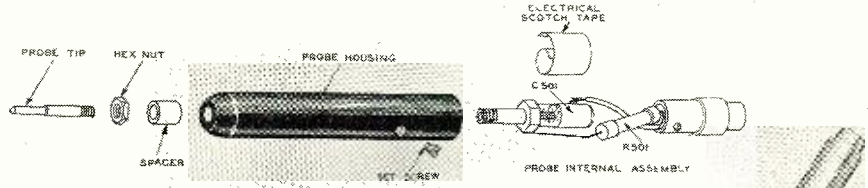
The normal capacitance of a direct probe and cable may be about 70 to 100 $\mu\mu\text{fd}$. With selected resistance and capacitance combinations the input capacitance of a low-capacitance probe can be held to a value below 10 $\mu\mu\text{fd}$. Low-capacitance input, however, is not obtained without some sacrifice of input signal level, because this type of



"Exploded" view of RCA WG-216B probe showing the various component parts.

probe is a voltage divider. The inherent loss in the WG-216B probe is fixed at a factor of 10 for convenience in calculating the attenuating effect when the probe is used with a calibrated instrument. Because the attenuation factor must be applied at low frequencies as well as high, the probe must be frequency-compensated for a wide response range.

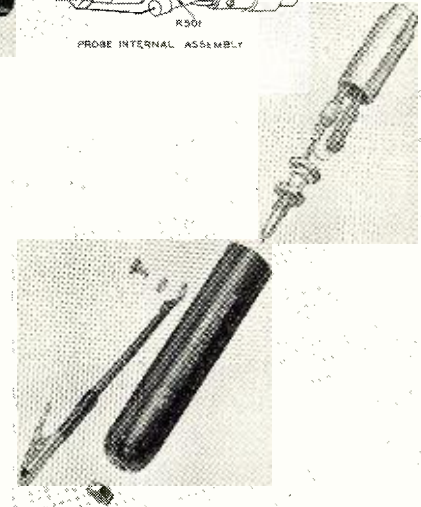Where the normal resistance of an oscilloscope is on the order of one megohm, and the small input condenser in a low-capacitance probe is shunted by a high value of resistance, the total series input resistance can be raised to 10 megohms. The combined resist-



WG-264 rectifying probe disassembled to show the various component parts.

Table 1. Quick reference chart for selecting proper probe for the job at hand.

MEASUREMENT	CLASSIFICATION	RCA TYPE	LOADING FACTOR	VOLTAGE LIMITATIONS
D.C. Voltage (V.T.V.M.)	Isolating	WG-217	11 megohms*	1500 v. d.c. max.
High-Voltage D.C.	Multiplying	WG-289	1100 megohms*	50 kv. d.c. max.
Low-Frequency A.C.	Direct	WG-218	70 $\mu\mu\text{fd}$., 1 megohm*	1500 v. r.m.s.; 4200 v. peak-to-peak sine wave*
High-Frequency A.C. or Complex Wave	Low-Capacitance	WG-216B	9 $\mu\mu\text{fd}$., 10 megohms	2000 v. peak-to-peak; 500 v. d.c.*
Rectified R.F. or A.C.	Rectifying	WG-264	1.75 $\mu\mu\text{fd}$., 6000 ohms at 200 mc.**	20 v. r.m.s., 28 v. peak; 250 v. d.c.
Modulated R.F.	Rectifying and Demodulating	WG-291	2.25 $\mu\mu\text{fd}$., 2500 ohms at 200 mc.**	20 v. r.m.s., 28 v. peak; 250 v. d.c.

* Approximate values which vary with instrument

** Approximate values which vary with frequency

ance divider and capacitance divider form an RC divider having both flat frequency response and minimum circuit-loading characteristics.

The WG-216B probe input condenser is adjustable and it is made accessible by unscrewing the contact tip. This condenser is adjusted by the manufacturer to obtain best square-wave response.

The WG-216B probe is designed for use with RCA WO-56, WO-57, and WO-88 series oscilloscopes. Its voltage input ratings are consistent with the input ratings of these instruments.

The two-fold purpose of a low-capacitance probe is to reduce the capacitive and resistive loading effect on the circuit being tested and to pass all frequency components in the circuit to the test instrument. The use of such a probe can in no way extend the frequency response of the test instrument. Some distorted waveforms seen on an oscilloscope, therefore, are unimproved by the addition of a low-capacitance probe. The full value of the probe can only be realized when the response of the instrument is not the limiting factor.

The low-capacitance probe used in conjunction with an oscilloscope gives that instrument a marked advantage which is readily observed when it is desired to examine the waveform in a sensitive circuit as, for example, a television horizontal oscillator. With a probe that does not have low capacitance, the waveform will change its slope and the picture will usually tear out when the oscillator is detuned by application of the probe. With the low-capacitance probe, the waveform will have a straight horizontal appearance between start and finish peaks and the TV picture is not likely to tear out during probe contact.

Isolating Probes

The RCA WG-217 d.c. probe is fitted with a one-megohm resistor in its housing to isolate the circuit under test from the test instrument and cable and to keep high-frequency a.c. out of the vacuum-tube voltmeter with which it is used.

When this probe is applied to the

grid of an i.f. amplifier, for example, the distributed capacitance across the one-megohm isolating resistor is the only path for high-frequency loss. Because that capacitance is negligible, no discernible detuning problem exists. Although the value of the resistor is too high to pass any appreciable high frequency, it results in perfect combination with the high internal 10-megohm input resistance of the "Volt-Ohmyst" for indication of the d.c. grid bias. The total resistance of 11 megohms is great enough to allow bias reading without serious loading error.

When it is desired to read a.c. from a source which also contains d.c., a blocking condenser is necessary. This condenser may be located either in the probe or in the test instrument. Good low-frequency response requires the use of a fairly large condenser and it is normally found in the instrument simply because it would be too cumbersome to house in a probe.

Rectifying Probes

The primary function of a rectifying probe is to extend the high-frequency range of a test instrument. Used at the point of test contact, such a probe performs the function of a detector and delivers rectified output voltage proportional to the r.f. input voltage being detected. Because of the usual sine-wave composition of high-frequency voltages, rectifying probes are generally of the half-wave type capable of developing either r.m.s. voltages for vacuum tube voltmeter measurements or peak voltages for oscilloscope indication.

Depending upon whether the probe is to be used with a voltmeter or oscilloscope, its output circuit has a long or short time constant. A probe designed for use with a vacuum tube voltmeter delivers filtered d.c. output proportional to the amplitude of the r.f. wave. A probe designed for use with an oscilloscope delivers d.c. output which fluctuates according to the amplitude modulation of the r.f. wave.

Because the circuitry differs with the output requirements of rectifying probes, it is necessary to have special probes for particular applications. The

two most popular types, therefore, are described separately in the following paragraphs.

Crystal Diode Probes

The RCA WG-264 crystal diode probe contains a germanium crystal diode which, by proximity to the point of test, produces rectified output with a minimum of signal loss. It is a half-wave rectifier of the peak-reading type and develops a d.c. output which is indicated as a negative d.c. voltage across the input resistance of a "Volt-Ohmyst." The probe is calibrated for use with "VoltOhmysts" so that the measured d.c. output is equivalent to the r.m.s. value of the sine-wave voltage at the input of the probe.

When intermediate-frequency to v.h.f. signals are measured, r.m.s. voltage readings are normally sufficient. The measurement of video and sync signals in peak-to-peak values is not a function of the WG-264 type of probe. These values are better measured with a direct probe and a peak-to-peak reading vacuum tube voltmeter such as the RCA WV-97A "Senior Volt-Ohmyst."

The WG-264 crystal diode probe has an input frequency range from 50 kc. to 250 mc. and an input capacitance of 1.75 μmfd . Its input voltage ratings are sufficient for applications in the r.f. and i.f. sections of TV sets and other low-level electronic devices.


When quantitative measurement of r.f. (and i.f.) is the sole consideration, the crystal diode probe is excellent for checking stage gain, tracing signals, locating spurious oscillations, and detecting and measuring r.f. output from oscillators and signal generators.

Demodulator Probes


Another in the family of crystal-diode rectifier probes, the demodulator probe RCA WG-291 serves to perform certain functions beyond the basic requirement of furnishing d.c. output. Although the demodulator probe will rectify r.f. input and produce d.c. equivalent to the peak value of the input voltage, it differs from the WG-264 in that it is not calibrated and

(Continued on page 132)

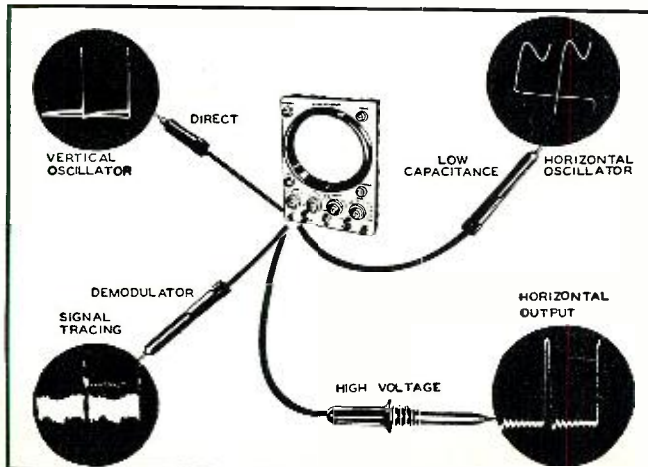Applications of probes used in conjunction with oscilloscope.




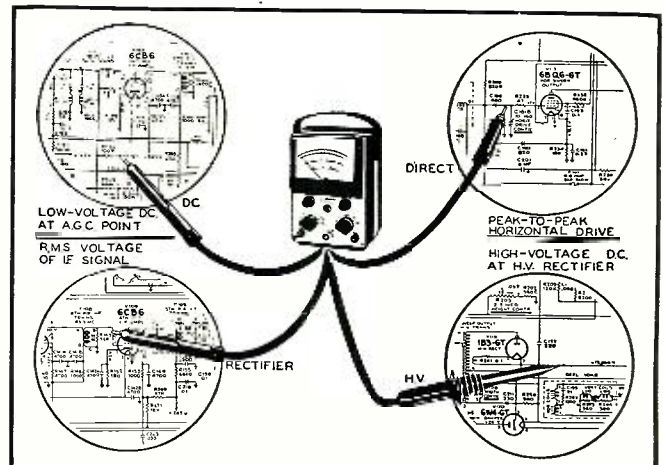Circuit testing with a v.t.v.m. and various types of probes.



ELECTRONIC "BUTLER AND BABYSITTER"

By SIDNEY LIPMAN

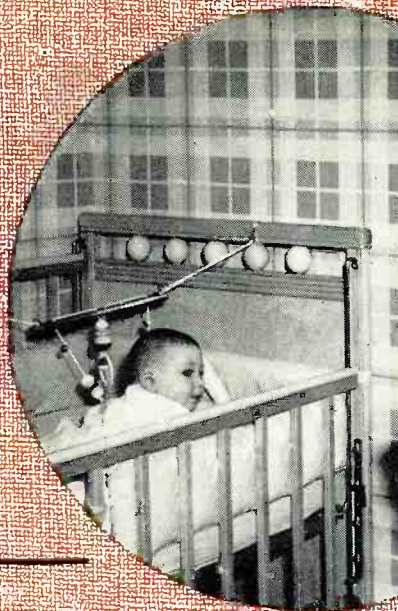

The nursery can be monitored or front door answered from the kitchen or basement with intercom.



A few cents a month for power and a well-stocked junk box are the only requirements for building this home intercom system.

ANY intercom for the home must be inexpensive to build and to operate and must be useful enough to warrant the cost. As the name implies, the two most important functions of the system to be described are answering the door and keeping in touch with the "King" or "Queen" in the nursery. Initial cost, if every item is bought new, and the junk box can not provide any help, will be about fifty dollars and the running costs are about as much as running an electric clock—a few cents a month.

The installation described consists of three master stations and one slave station, all powered from the same amplifier. Additional stations may be added or some of the stations eliminated, depending upon the requirements of the individual home, without altering the efficiency of the system. Because of the very low power requirements, the author runs the amplifier continuously day and night and after a number of months of operation not a single component, including tubes and rectifier, has overheated.

The amplifier is a high-gain, three-stage unit built on a standard 5 x 7 x 2 inch deep aluminum chassis. The tubes selected require less than three watts for heater power and the selenium rectifier power supply requires about the same wattage. To prevent shocks from the amplifier chassis, a polarized plug was used to insure that the chassis is always at ground potential. If a polarized plug and socket are not available, only the hot side of the line should be connected to one prong of the plug and the chassis connected to a water pipe

ground by a single wire. In the event the plug is not inserted properly the heaters will not light up when the switch is turned on and it will only be necessary to turn the plug over to obtain proper operation.

In the amplifier shown in the photographs a number of the resistors pictured are of greater wattage than those specified in the diagram. This is because the unit was built from junk box parts. All values shown on the diagram are for minimum wattages but no harm can be done by using a resistor of a higher wattage rating if it is more readily available. The electrolytic condensers, in some cases, are of a larger capacity and higher voltage rating than those called for in the diagram. Again the diagram values should be taken as minimum values and higher capacity or voltage ratings may be substituted if more readily available.


The biggest problem to overcome is hum pickup. The amplifier pictured uses the point-to-point wiring technique to minimize hum, with a single row of tie points to support the ground and voltage supply ends of the resistors. The decoupling and screen dropping resistors are mounted on the tie point strip. The power supply components are all arranged at one end of the chassis and the signal components at the other. On top of the chassis are placed the filament transformer and the output transformer. The heater pins of the tubes (pins 3 and 4 in all cases) face the power end of the chassis. Two leads are run to the heaters and the center tap of the transformer is grounded, to

minimize hum. The transformer mounted on the edge of the chassis is the input transformer and was mounted in this spot to—you guessed it—reduce hum. It is a standard output transformer.

The input to the amplifier uses a shielded lead with the hot wire connecting to one end of the input transformer voice coil winding at the two-terminal board and the shield connecting to the other voice coil lead. The output from the amplifier is handled in the same manner. No connection is made to the chassis and the shields are connected together only at the central terminal board mounted centrally in the cellar on a ceiling beam. The amplifier is located on a storage shelf a few inches away from the terminal board.

Each station is wired to a barrier strip connection block, and crimp-on lugs are used on all leads. This eliminates the necessity for chasing all over the house with a soldering iron and simplifies troubleshooting or the addition of more stations. Provision was made for a fifth station which will probably remain unused until a garage is built.

The station in the nursery is located between the crib and the bathinette and the pickup is sensitive enough to allow the smallest whimper to be heard. If someone rings the doorbell while baby is being bathed, the controls are within easy reach of Mother to tell the visitor to "return later" or "wait a moment" or "we do not want any." After interviewing half a dozen storm window salesmen, Mother found it gratifying to be

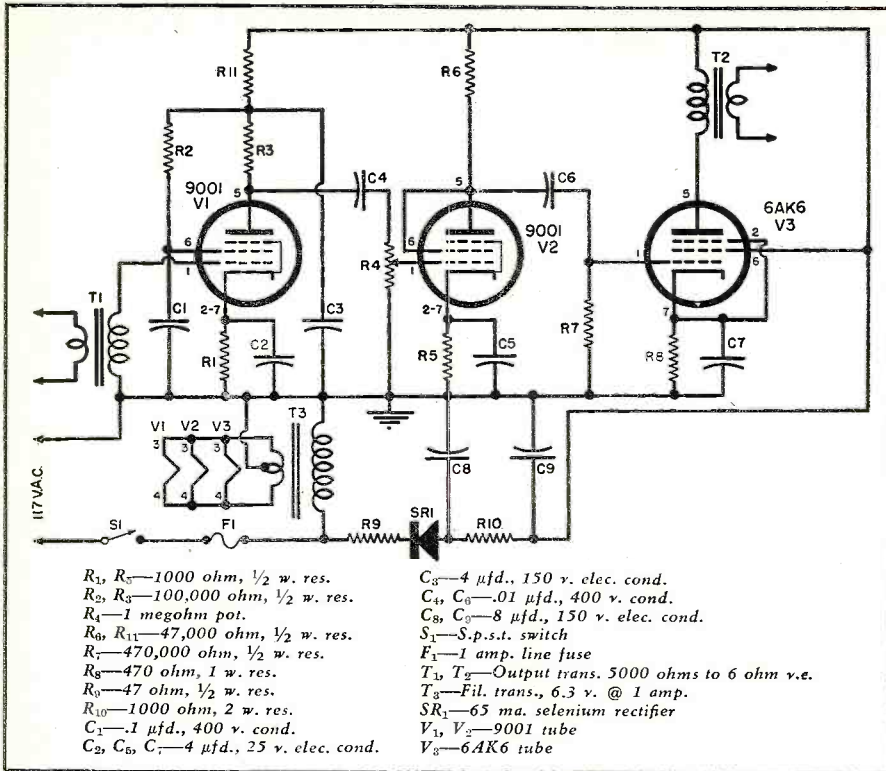


Complete schematic of intercom station. Any number of units can be used in system.

able to send the others away without subjecting baby to a draught in the middle of her bath.

The master stations are equipped with a separate double-pole, double-throw, center-off switch for each other station. The switches of all stations are normally left in the cen-

ter-off position. When a call is to be initiated, the switch for the station being called is put in the "up" position and the message delivered from any distance away from the speaker, up to four feet or more. The switch is then pushed to the "down" position to hear the answer. When the con-

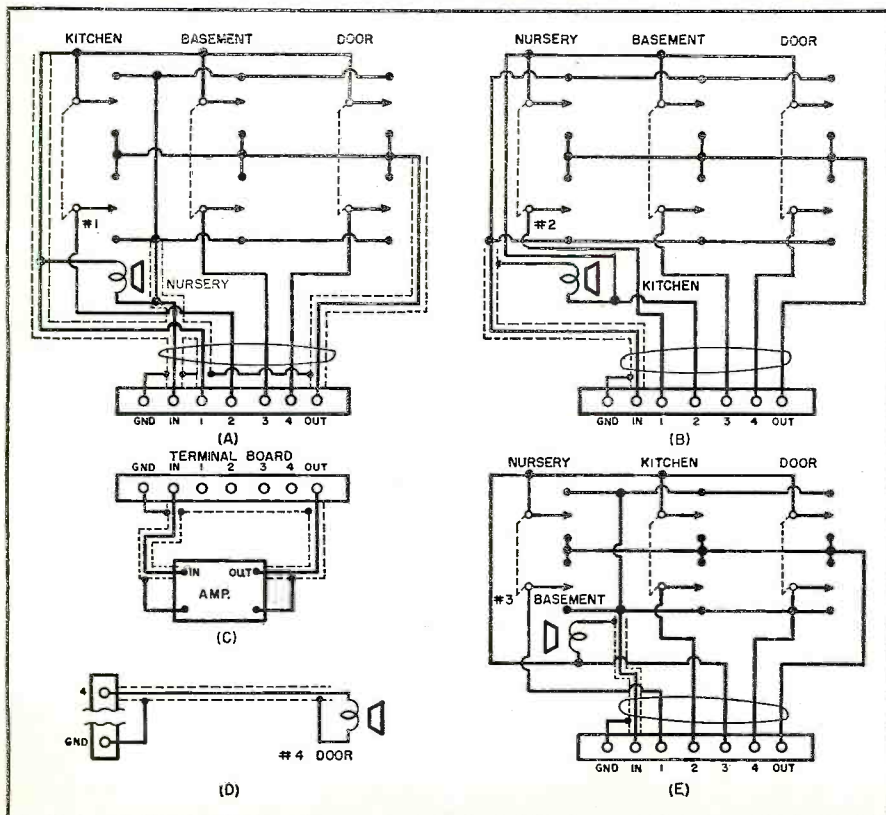Different methods for hooking up intercom system. See text for complete details.



versation is over the switch is returned to the middle position. The person at the station being called need do nothing more than answer the question put to him from any point in the room being called.

When the lady of the house is busy in the kitchen, which is a good part of the day, she is but a step away from the baby's room at the far end of the house via the speaker mounted over her work space. When supper is ready it requires only a softly spoken word with the basement switch in the "up" position to bring Father up from his various hobbies. A special dish need not be spoiled by having to be left alone at a critical moment in order to answer the front door when a few well chosen words into the "Butler" will keep the Fuller Brush salesman on the front porch until the crisis is past.

The kitchen station is mounted under the metal cabinets with self-tapping screws. There is a double bottom to the cabinets so the screws do not extend through. The leads run inconspicuously along the bottom of the cabinets, down the edge of the tile and through a small hole in the floor behind the refrigerator. The station in the nursery is mounted against the wall with wood screws that go through screw eyes screwed along the top and bottom of the cabinet. The cable runs down the wall and along the baseboard until it snakes its way down a hole in the corner of the room under the crib. Standard insulated staples are used for holding the cable.

The front door speaker was treated with *Walltex* before being installed in the cabinet. This is a material that waterproofs the cone and is designed for treating wall paper to make it washable. It has a wax base. All the speaker cabinets were home-made of $\frac{3}{16}$ " plywood and painted to match the walls upon which they are mounted. The front door and kitchen units are painted white and the nursery unit is a cream color. After the paint is dry a thick coat of paste wax, such as *Johnson's* floor wax, is applied. This makes the cabinets easy to clean as well as making them waterproof.

All speakers are protected by a piece of copper window screen with a piece of an old sheet in front of it. The holes for the speakers were cut in the plywood with a fly cutter before the cabinets were assembled. By cutting half way through from each side, a neat hole is produced. The cabinets are butt joined and glued with *Stanley* glue. In addition a few small nails, similar to those found in cigar boxes, were used to hold the pieces together until the glue dried.


The cables running from the various stations to the central terminal board are run along the rafters. A small hole through the wood shingles where they meet the concrete foundation was used to bring the single shielded lead into the cellar from the front

door station. The wires were strung one at a time and were held in place by finishing nails crossed with about a quarter-inch spacing between the two nails. Wires can be installed by twisting them at right angles to their normal position, putting them between the heads of the nails and then taking up the slack, which puts the wire under both nails. This system allows more wires to be added any time.

The shields of the cable going to the nursery are grounded to a water pipe at a convenient spot. There should be only one ground in the cable of all the stations. If a ground wire is used for a return of the amplifier chassis it should be separate and go to the nearest cold water pipe. The basement station, which is not illustrated, is built slightly differently. The switches for calling other stations were mounted on an inch and a half strip of aluminum which is screwed along the edge of the work bench. The speaker has a three foot wire on it so it can be set at any convenient spot on the bench, or on the floor when a big job is undertaken. There were no walls convenient to hang the speaker on. The first installation was a direct line from the nursery to the basement and was responsible for the author having a chance to complete the other stations while Mother was out. The slightest whimper brought Father up armed with bottle, safety pins, and so on. Another labor saving convenience is the ability to tell the door-to-door salesman "we do not want any" without running up the stairs and halfway through the house to open the door.

Some trouble may be encountered if any of the cables exceed twenty feet in length. Oscillation may occur due to coupling between input and output circuits. If the wires in the cable can be spaced an inch or more from each other, this will not occur. Simpler, but more expensive is shielded wire. The author found it necessary to shield only one cable, that going to the nursery. Three wires are all that must be shielded: The input, output, and the wire that is connected directly to the speaker of the distant station. The author found it convenient to run a single shielded lead to all stations for the input circuit in order to minimize hum pickup from those stations not used during a particular conversation. The shield is also used as a return, saving wire. If possible, color coded wire should be used to simplify servicing. If this is not convenient, tag the leads so that, at a later date, you will know which is which.

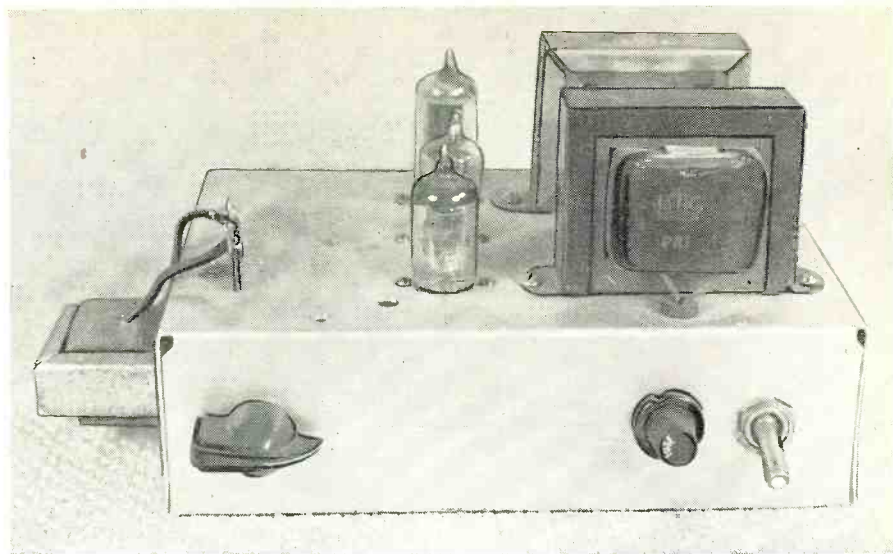As in a railroad telegraph system, the worst offense an operator can commit is to leave a switch in the wrong position. However; with this system all is not lost as is the case with the telegraph. If, for instance, Mother has left her switch for the basement station in the "down" or "listen" position and Father puts his




A station unit. Any cabinet appropriate to decorative scheme may be employed.

switch in the basement to the kitchen "talk" position, oscillations will be reproduced at the two stations. This will indicate to Mother that she left her switch in the wrong position and that it should be returned to its neutral position since someone is trying to call her. It also indicates to Father in the basement that his message was not received.


While the author claims no startling innovations for this set-up, this intercom system works well, is virtually foolproof, costs little to build, and even less to operate—all desirable features for any home intercom installation to have. In addition, it is easy to build and install.

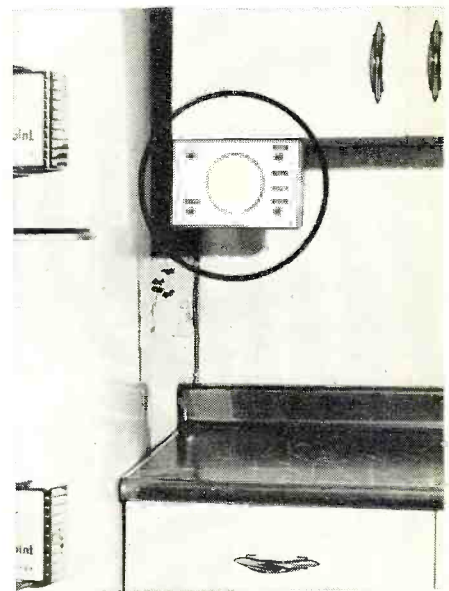In the few months that the electronic "Butler and Babysitter" have been working for the family, untold numbers of steps have been saved. It has also been gratifying to know that Mother need not answer the door when alone in the house without first knowing "Who's calling please?" —30—



Kitchen intercom mounted on metal cabinet.

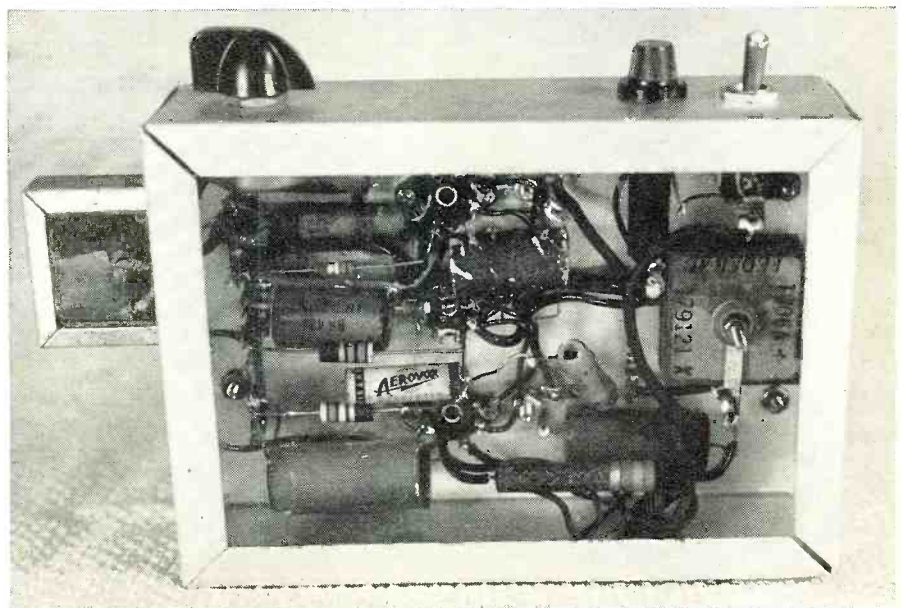Under chassis view of station. This layout prevents overheating of components.






TRANSISTOR

PHYSICS

Simplified

IT WAS pointed out in the previous article (July) that in a junction transistor the emitter, base, and collector connections to the crystal are low-resistance (large area) connections. In the point-contact transistor the emitter and the collector connections to the crystal are point-contact (relatively high-resistance, small area) connections. Fig 10 is a line drawing cut-away view of the transistor. The base connection, however, is a low-resistance (large area) connection. It was mentioned in previous paragraphs that the emitter current is slightly larger than the collector current in the junction transistor and that the base current is extremely small. It has been found by experiment that in the point-contact transistor the collector current (unlike the collector current of the junction transistor) is substantially larger than the emitter current, and that the base current is relatively large. In the following paragraphs an attempt will be made to explain these differences between the junction transistor and the point-contact transistor.

Although the point-contact transistor employs what is considered to be either an *n*-type germanium crystal or a *p*-type germanium only, experimental investigation has shown that in the *n*-type point-contact transistor, *p*-type layers occur, and that in the *p*-type contact transistor, *n*-type layers occur. Fig. 11A shows an *n*-type point-contact transistor. It is seen that under the emitter point is a very thin layer of *p*-type germanium (P_1), and under the collector point is a thin layer of *n*-type germanium (N_2), followed by a thin layer of *p*-type germanium (P_2). By observation it can be seen that the emitter-base section is biased in the forward direction. Current flow consisting mainly of holes in the P_1 -type germanium and mainly of electrons in the N_1 -type germanium will occur. However, an increase in emitter current causes a large increase in collector current and a decrease in emitter current causes a large decrease in collector current. The following paragraph will attempt to explain the current amplification of the transistor. Fig. 11B is an enlarged view of the

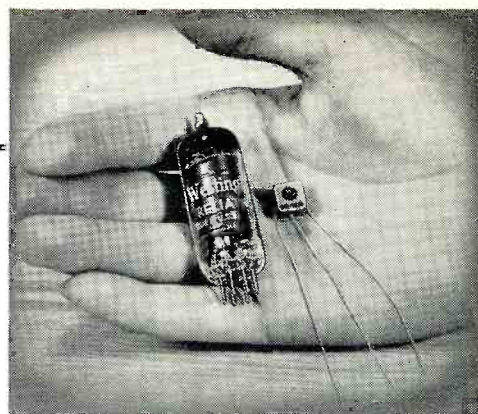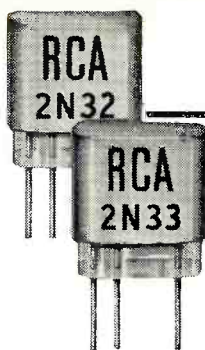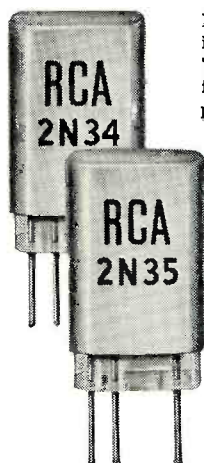

RCA's 2N32 point-contact type designed for large-signal pulse or switching operations. The 2N33 for oscillator applications in 50 mc. region. The 2N34, a "p-n-p" junction type audio amplifier for low-power, low-frequency applications. RCA's 2N35, an "n-p-n" junction type audio amplifier for low-power, low-frequency use. (Above) Westinghouse's WX-4813.

By

S. P. GENTILE and P. J. BAROTTA

Sig. Corps Pub. Agency
Fort Monmouth, N. J.

Dir., Hudson Tech. Inst.
Union City, N. J.

Part 2. Concluding article covers point contact type transistors, their design, construction, and circuit applications.


collector-base circuit. The potential energy diagram for electrons in the crystal portion of this circuit is shown in Fig. 11C. Under steady-state conditions (no signal applied), very few electrons climb the potential energy hill between N_2 and P_2 . However, those that do climb the hill do not combine with the holes in the P_2 region because it is a thin region. These electrons fall quickly down the potential hill between P_2 and N_1 . When the emitter-base region conducts, some of the holes which leave the P_1 region of the emitter, drift into the P_2 region of the collector. With holes in the P_2 region from the emitter, the potential energy diagram for electrons between the collector and base conforms to that in Fig. 11D. Note that the potential energy hill between N_2 and P_2 has been substantially reduced, and electrons in the N_2 region can climb readily into the P_2 region. Most of these electrons do not combine with holes

in this region, but fall very rapidly into the N_2 (base) region. For every hole that enters the P_2 region from the P_1 region, many electrons flow from the N_2 region through the P_2 region down into the N_1 region. Thus, it is seen that large current amplification may be effected. This amplification of current is expressed as α (alpha) and is equivalent to μ (the voltage amplification factor of a vacuum tube). Mathematically, $\alpha = \Delta I_c / \Delta I_e$, where ΔI_c equals a small change in collector current, and ΔI_e a small change in emitter current.

Point-contact transistors have been made with *p*-type germanium as the main body. The theory explaining the operation of this type point-contact transistor is similar to that explaining the operation of the *n*-type point-contact transistor. The difference, of course, is that the main current carrier consists of holes instead of electrons. The explanation in the previous paragraph coupled with the information in Fig. 12 will enable the reader to understand the theory of operation of *p*-type point-contact transistors. Note that the polarities for the emitter with respect to the base, and the collector with respect to the base have, of necessity, been changed.

The operation of a point-contact transistor can be compared to the operation of a triode vacuum tube. The emitter is equivalent to the grid, the base to the cathode, and the collector to the plate. The base current is relatively large, and the major por-

Fig. 10. Line drawing of a cutaway view of a transistor of the point-contact type.

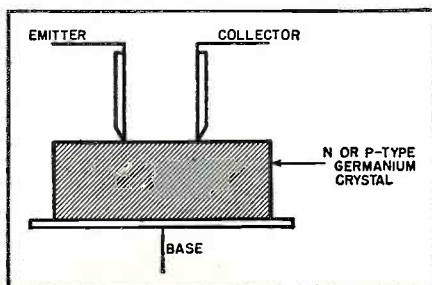

tion of it goes to the collector. Unlike the grid of a vacuum tube, the emitter draws a continuous current. The input (emitter) impedance is low and the output (collector) impedance is high. In a vacuum tube the input (grid) impedance is high and the output (plate) impedance is low. For a comparison of transistors and vacuum tubes see Tables 1 and 2.

Bias Voltages

In a vacuum tube the grid is usually biased negatively with respect to the cathode, and the plate is made positive with respect to the cathode. With the transistor the collector may be positive or negative with respect to the base, and the emitter may be positive or negative with respect to the base. These are illustrated in Fig. 13. The bias polarities depend on whether the transistor is an *n-p-n* or *p-n-p* junction type, or a *p* or *n* point-contact type. To simplify the problem for the technician, the diagrams of Fig. 13 have been prepared, which indicate bias polarities required for the various types of transistors. If one remembers that the *n*-type point-contact transistor is, by stretching the imagination a bit, actually, a *p-n-p* type transistor, and the *p*-type transistor, is an *n-p-n* transistor, bias polarities can be remembered easily by the following simple rule. The emitter is biased in a forward direction with respect to the base and the collector is biased in the reverse direction with respect to the base, in any transistor.

Conclusion

These articles have presented in purely descriptive, non-mathematical terms the fairly complicated physics of transistors. Although this type of treatment is inadequate for those interested in a quantitative presentation, it is hoped that the average radio-television technician will have a greater understanding and appreciation of those circuits employing transistors in the place of vacuum tubes. It may be mentioned here briefly that major differences occur in transistor circuits compared with the corresponding vacuum tube circuits. This is a study in itself and since this article was designed to be merely an introduction to the large number of transistor circuits which will make their appearance on the radio-television horizon, no attempt has been made to discuss specific circuitry.

Many articles have been written about the theory of transistor physics; however, these articles explained mainly the mathematical concepts, and as a result, to coin a phrase, "did not hit home" as far as the technician or engineer who is not directly concerned with transistor application. In this article the authors have attempted to provide the theoretical justification for a different method of practical transistor physics presentation.

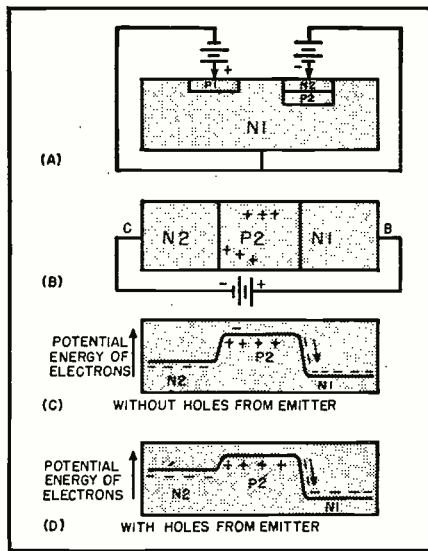


Fig. 11. An "n" type point-contact type of transistor. See text for complete details.

VACUUM TUBE	TRANSISTOR
Cathode	Emitter
Plate	Collector
Grid	Base
$\mu = \Delta E_p / \Delta E_g$	$\alpha = \Delta I_c / \Delta I_e$
Voltage Amp.	Current Amp.
High Input Imp.	High Input Imp.
(grounded cathode)	(grounded emitter)
Low Output Imp.	Low Output Imp.
High Power Consumption	Low Power Consumption
Fragile	Rugged
Large in Size	Small in Size

Table 1. Comparison of characteristics between vacuum tube and a junction transistor.

Although the transistor is only five years old, much is expected of it in the near future. Many electronic units will be freed from the vacuum tube's limitations, namely, fragility, bulkiness, and short life. To think that in such a short time since its inception, the combined production of transistor makers has resulted in an output of 50,000 units a month. Before the end of 1953, output is expected to exceed 250,000 units a month. Is it any wonder that they call transistors the miracle of the Twentieth Century?

From the outset of radio it has been known that semiconductors, such as galena, have the ability to rectify alternating current signals. In fact, the "cat whisker" galena crystal was a standard part of the early radio set. But the fundamental reason why some substances conduct and others do not had to be investigated by some of our leading physicists before the transistor became a reality.

Transistors have been introduced successfully in such units as the phono amplifier, radio and television receiver, hearing aid, "walkie-talkie" set, radar spotting device, computer, and other devices which employ, at present, vacuum tubes. No theoretical limitations are placed on transistor applications. The experts are optimistic about the possibility of overcoming present transistor limitations, *i.e.*, the higher noise level and the effects of heat and humidity upon its operation. Because the transistor is still in its infancy, it is undoubtedly just a mat-

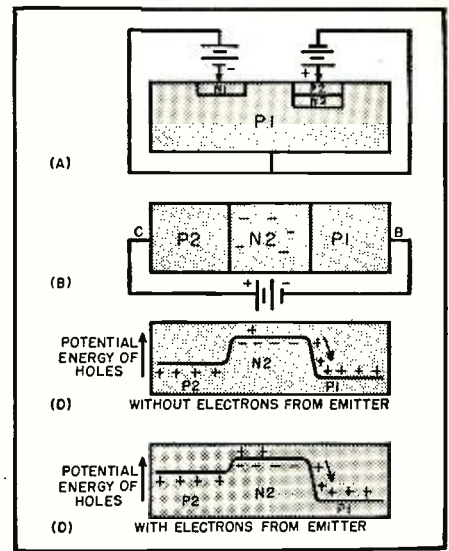


Fig. 12. A "p" type point-contact transistor. Note differences from Fig. 11, left.

VACUUM TUBE	TRANSISTOR
Cathode	Base
Plate	Emitter
Grid	Collector
Voltage Amp.	Current Amp.
$\mu = \Delta E_p / \Delta E_g$	$\alpha = \Delta I_c / \Delta I_e$
High Input Imp.	Low Input Imp.
Low Output Imp.	High Output Imp.
I_p	E_c
E_p	I_c
I_g	E_e
E_g	I_e
Constant E Supply	Constant I Supply
Capacitance	Inductance
Large in Size	Small in Size
High Power Consumption	Low Power Consumption
Fragile to Shock	Rugged
Reverse Bias	Forward Bias


Table 2. Comparison between point-contact type transistor and standard vacuum tube.

ter of time until these problems are ironed out.

BIBLIOGRAPHY

- Shockley, W.: "Theory of *p-n* Junctions in Semiconductors and *p-n* Junction Transistors", *Bell System Technical Journal*, July, 1949
 ; *Proceedings of the IRE*, November 1952.

Fig. 13. Emitter and collector bias voltages for different types of transistors.

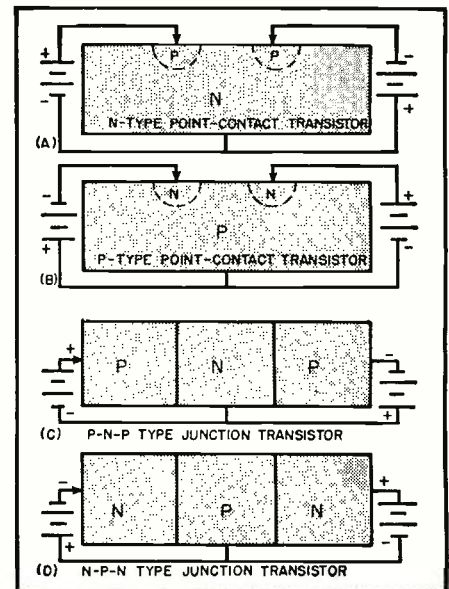

T.V. TROUBLESHOOTING

HIGH-VOLTAGE SUPPLIES

By
MILTON H. LOWE

Flyback type high-voltage circuits: how they operate, and hints for time-saving receiver troubleshooting.

A FEW years ago, before 19 and 21 inch picture tubes made their appearance, 9 or 10 kilovolts were all that were required to operate the average "kine." Nowadays, 15 kilovolts is quite common, and the high voltage required increases as picture tubes get larger. You have probably noticed that the physical size of components, such as the flyback transformer and high-voltage rectifier tube, have not kept pace with the demands placed upon them. If anything, the tendency is towards smaller and smaller parts whose values must be calculated critically in order to obtain the desired results. Replacing these parts without regard to tolerances and characteristics may cause troubles that did not exist before the repair was made. The best way to avoid these additional bugs is by being careful while troubleshooting, and by using correct replacement parts.

In an effort to improve the performance of the high voltage power supply, some 1953 television receivers utilize a flyback transformer of new design. It has a number of extra primary taps to which the damping diode is connected, in contrast to the older types where the damper is connected across the secondary. The principal advantage of this design is the reduction of transformer leakage inductance and distributed capacity, thus extending the high frequency response of the transformer. This results in a lower horizontal retrace time and, ultimately, reduces the problem of horizontal foldover due to lack of transformer response.

Typical varieties of the newest types of high-voltage supplies are shown in

Figs. 1 and 2. Fig. 1 is the partial schematic diagram of the parts that comprise the high-voltage supply of *Admiral* chassis 19H1. The operation of this type flyback circuit is similar to the older types. The output of the horizontal oscillator is applied to the 6BQ6 horizontal output tube where it is amplified. The "Horizontal Drive" condenser and the 680 μ fd. coupling condenser comprise a voltage divider for the grid input signal. For proper operation of the circuit, the "Horizontal Drive" control is adjusted so that the saw-tooth shaped grid signal has a peak-to-peak amplitude of 65 volts. The 68-ohm grid loading resistor minimizes the tendency toward Barkhausen-type parasitic oscillations. A negative grid potential of approximately 24 volts is developed across the grid-leak network consisting of the 1-megohm grid return and the "Horizontal Drive" condenser (in series with the 68-ohm resistor). This potential, in conjunction with 5 volts of self bias developed across the 47-ohm cathode resistor, results in a total of approximately 30 volts of grid bias. This is a convenient number to remember when troubleshooting most horizontal output grid circuits, because one measurement from *grid-to-cathode* will indicate if the drive and bias are approximately correct. The amplified plate signal is applied to the horizontal deflection coils; stepped-down to produce the 1.5-volt filament potential for the 1B3; and stepped-up to produce the high voltage pulse, which is rectified and filtered to produce the high voltage output.

During the horizontal retrace, or

flyback time, the horizontal output tube stops conducting, and a large pulse of voltage is developed across the flyback transformer due to the rapidly collapsing flux lines. This pulse would induce transient oscillations in the yoke were it not for the damping diode, which is driven into conduction at this time, reducing the magnitude of the voltage across the coils and causing the oscillations to decay quickly. The "pi" network, consisting of the linearity coil and the two .047 μ fd. condensers, filter this rectified pulse to produce the "B+" boost voltage (approximately 470 volts). A good point to remember about "pi" networks is that the input leg has the greatest effect on the amplitude of the network's output voltage, whereas the output leg has the greatest effect on the phase shift through the network. Thus, the .047 μ fd. input condenser should be suspected if the boost voltage is too low, and the output .047 μ fd. condenser should be suspected if the linearity of the picture is unsatisfactory.

The linearity and width coils are both tunable to provide for shaping the horizontal deflection current by shifting its phase with respect to the applied voltage. These controls are interacting and must be adjusted alternately to obtain the desired picture width and shape. The width coil is split into two parts so that a given minimum of inductance shorts the lower portion of the flyback transformer irrespective of the setting of the width control.

Defects in the grid and screen circuits of the output tube produce symptoms similar to those obtained in any grid-leak biased audio amplifier. For example, if the 1-megohm grid return should increase in value, there is a strong possibility that the high voltage would be intermittent in a fashion that would be the visual counterpart of the aural motorboating effect. If the .047 μ fd. screen bypass should become slightly leaky, the width would be reduced somewhat. If this condenser should become very leaky, the brightness and/or width would be noticeably affected.

Fig. 2 is a simplified schematic of a flyback circuit that is a modified version of the type shown in Fig. 1. This circuit is used in the *Crosley* chassis 387, *Motorola* chassis TS-410A, and many other receivers, and is a beautiful example of simplified design. Its principal difference, compared to the circuit of Fig. 1, is the noncontinuous flyback primary. A 50-ohm potentiometer, used for horizontal centering, separates the upper and lower portions of the flyback primary. Notice that a portion of the upper half of the primary is tunable by means of an adjustable slug. This provides a means for adjusting picture width by changing the high voltage by a small amount (the picture width is a function of two variables, namely the sweep and high voltage, with the high voltage having the greater effect).








RECEIVER CHASSIS No.	OUTPUT TUBE GRID	GRID TO CATHODE BIAS
EMERSON 120168-D 120166-D	 120V.	-20V.
MOTOROLA TS-395 TS-400 TS-410	 70V.	-25V.
SYLVANIA 1-437-3 1-507-1	 105V.	-30V.
DUMONT RA-147	 60V.	-28V.
ADMIRAL 22C2 23A1	 90V.	-36V.
CBS-COLUMBIA 817 820	 100V.	-35V.
OLYMPIC 217	 75V.	-35V.

Table 1. Signal wavelshape and the bias at the grid of the horizontal output tubes of some commercial TV receivers.

The apparent brightness is not affected, because the change in high voltage is very small, about 30 volts. Yet with a change of this order, the width is visibly affected. Notice, also, that the grid-leak bias is 27 volts, a value close to that of the circuit in Fig. 1. The boost potential, approximately +490 volts, is applied through the horizontal centering control and the output transformer to the plate circuit of the horizontal output tube. A parallel LC network is used to decouple the horizontal deflection coils from the damping circuit. The 2.2-ohm high-voltage current limiting resistor is used instead of a 4.7-ohm resistor to change the load that the filament winding presents to the primary.

An older type flyback circuit using a high efficiency ferrite core in the transformer is shown in the simplified schematic of Fig. 3. The 500 μ fd. condenser connected from the 1B3 filament winding to the high side of the secondary is the principal factor that permits a 14-kilovolt output to be obtained from this type of circuit. It applies a 3-kilovolt negative pulse, that is developed at the high side of the secondary at the same instant that the positive high-voltage pulse is developed across the primary, to the 1B3, and thus boosts the over-all potential across the high-voltage rectifier. The 550-volt boost voltage developed across the .22 μ fd. damper-cathode filter is applied to the horizontal output plate circuit and to the CRT first anode. The deflection coil is connected across the output transformer secondary to obtain an optimum impedance match between the 6BQ6 and the yoke, so as to minimize the tendency towards high-frequency ringing, which would appear as alternate light and dark vertical lines or bars on the raster. The potentials developed in this circuit are much the same as those in the previous two.

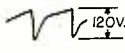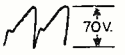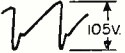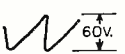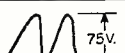A word of caution is necessary be-

fore discussing the troubleshooting procedures. The most dangerous stages to troubleshoot are the horizontal output, damper, and high-voltage rectifier. Especially dangerous is the plate circuit of the horizontal output tube. This is due to the fact that the plate cap of this stage has a "B+" potential of from 400 to 600 volts in addition to an r.f. pulse of some 3 to 5 kilovolts. Thus, you have the combined dangers of the very lethal "B+" supply, and the possibilities of a "burn" from the r.f. Many technicians can attest to the fact that the plate cap of the output tube is far more "shocking" than the plate cap of the rectifier. Also, most test equipment is not designed to handle the high potentials found in these circuits. Therefore, specially insulated test leads, high voltage probes, and voltage dividers should be resorted to in order to obtain a proportional indication of the voltages and waveshapes present.

Troubleshooting

Assume that the trouble symptom is a black CRT (sound normal). Only two possible troubles exist: either the CRT is dead or the high voltage is missing. A quick, though inconclusive, check of the CRT is to see if the heater is lit. If so, the trouble is probably in the high-voltage circuit, unless the customer has described symptoms that may lead you to believe that the CRT has gone. To check the high-voltage circuits, turn off the power and disconnect the lead to the CRT high-voltage button. Place the lead within $\frac{1}{4}$ " of the chassis and turn the power on again. An arc should be drawn if the high-voltage circuits are operating. If the arc is drawn, either the CRT is defective, or the CRT biasing circuits, including the brightness control, should be checked for a condition that would prevent the CRT beam current from flowing. Do not allow the arc to be drawn for more than a few moments as the current-limiting resistor in the rectifier filament circuit may be damaged.

If the arc is not drawn, use a well insulated screwdriver to pull an arc from the plate cap of the rectifier. It should be about $\frac{3}{8}$ " long for a 15-

Fig. 3. Capehart TV chassis CX-37 high voltage circuit furnishing 14 kilovolts.

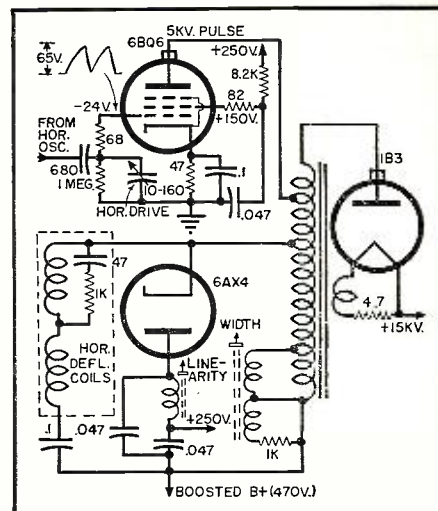
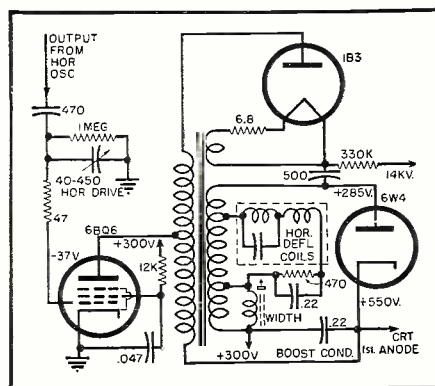


Fig. 1. Partial schematic of the high voltage circuits of Admiral 19H1 TV chassis.

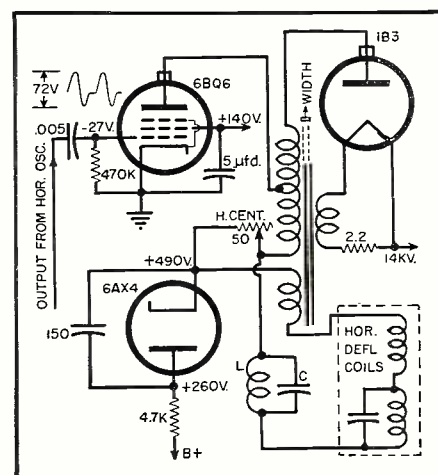


Fig. 2. Flyback transformer circuit of the Motorola TS-410A and Crosley 387.

kilovolt potential. If an arc is obtained at this point, but not at the end of the high-voltage lead, the high-voltage rectifier tube is probably defective. Also, check the high-voltage filter condenser, if a physical one is used. If the arc is appreciably less than $\frac{1}{4}$ ", the high voltage is too low and the CRT may not be bright for this reason. This point is discussed more in detail a little later. If an arc is obtained, touch the screwdriver to the plate cap of the horizontal output tube. Listen for a "click" in the speaker, and look for a very small spark at the point of contact. If both are obtained, the chances are that the output stage is OK. In this case, check the flyback transformer. (When the power is on, do not short the plate of the output tube to the chassis as this will cause either the low voltage fuse or low voltage rectifier tube to blow.)

A crude indication of the relative condition of the flyback can be obtained with an ohmmeter. The resistance from the plate cap of the output tube to the plate cap of the rectifier will range from 200 to 600 ohms, depending upon the type of flyback used.


(Continued on page 118)

BUILDING THE

E·V

Regency

By
HOWARD SOUTHER
Electro-Voice, Inc.

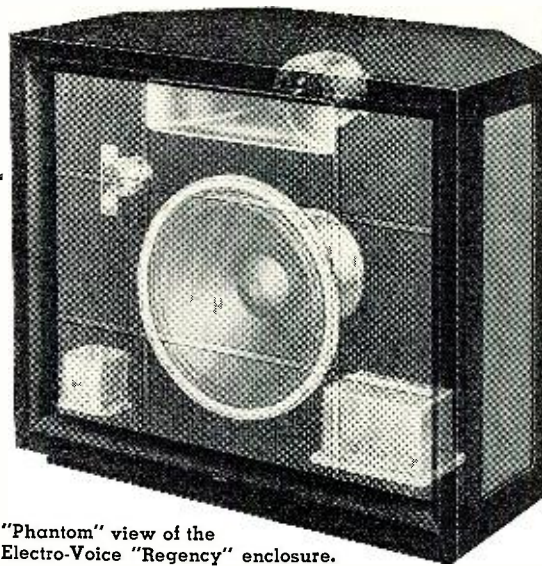

"Phantom" view of the Electro-Voice "Regency" enclosure.

Design details on a commercial folded horn enclosure which can be used with any high-quality 15" loudspeaker system.

THE SEARCH for better bass response in loudspeaker systems proceeds apace. In the design of an enclosure for promoting superior reproduction in the lower octaves, certain practical considerations often enter into the choice of construction.

For instance, a room corner is not always available. This design includes an operational as well as functional styling which allows wall or corner placement. The height of the unit is sometimes important, because a window sill, picture, or series of shelves may intrude. Accordingly, the unit described is designed to standard lowboy height of approximately 29 inches, just missing the usual window

sill and matching the height of other contemporary furnishings.

For the widest choice of driver complement, the acoustic loading permits a higher, more economical crossover point by allowing front radiation from the large driver cone. Thus, a high-frequency horn of small dimensions (the *E-V* Model 8-HD) can be housed within the structure with ease.

A horn is conceded to be the very best coupling medium for a high quality system. When this horn uses the corner of the room to extend the mouth opening, we have what is called a *folded corner horn*. These horns call for a very low crossover and the use of multiple components when they are of the indirect radiator type, such as the *Klipsch* "K" design. A more compact and economical system with 800 cps crossover must include front radiation from the driver cone for the frequencies above 300 cps. This is because the higher frequencies experience difficulty in following the circuitous path of the folds.

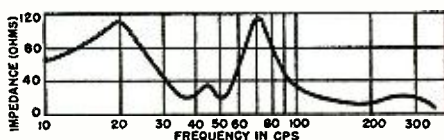


Fig. 1. Impedance curve of the "Regency" with E-V 15-inch driver of 37 cps free-space resonance. See text for details.

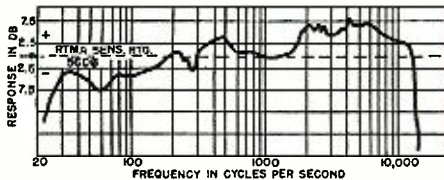


Fig. 2. "Regency" frequency response with 114-A 800 cps separate two-way system.

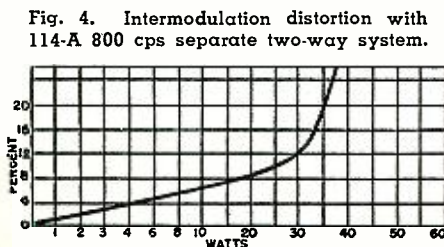


Fig. 4. Intermodulation distortion with 114-A 800 cps separate two-way system.

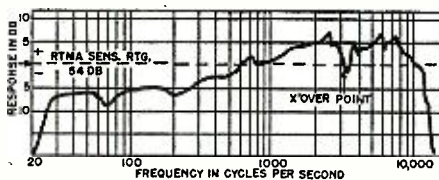


Fig. 3. Frequency response of the "Regency" with the SP15 "Radax" coaxial driver.

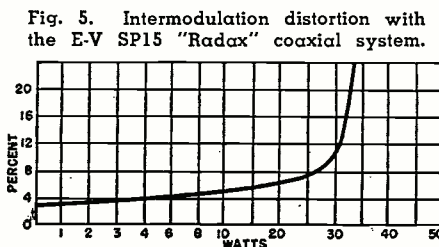


Fig. 5. Intermodulation distortion with the E-V SP15 "Radax" coaxial system.

The "Regency" is an acoustic system of the latter type, permitting direct radiation of the frequencies above 225 cps and efficiently horn loading the back of the cone for the tones below this point.

Because the "Regency" has its own integrally "built-in" corner with a low taper-rate, it may also be employed against a flat wall. In this case, the extended bass range is preserved, but at a slightly lower efficiency than when used in a corner. The two sides of the cabinet, along with the floor and adjacent wall, form a complete horn, only the cabinet side of which is slightly compromised. Thus, very satisfactory extended bass is achieved at good levels. The listening results are supported by the impedance characteristic (Fig. 1), showing a very high reactive component in the 10-30 cps region.




Performance

Performance with the *Electro-Voice* 114-A and 114-B two- and three-way systems using the 15W-1 15" cone driver, indicates unusual efficiency in the 30 cps region (Fig. 2). Harmonic distortion at the usual low room-playing levels is on the order of 2%.

A 15" coaxial driver (the *E-V* SP15) shows no less than 3% distortion at low levels. Remarkably enough, at the higher levels around 10-15 watts input, this driver shows less distortion than the multiple-way 114 series systems. This is true because the 114 systems are more sensitive, or efficient, and are being driven harder by the same power input. At the same listening levels they have appreciably less distortion than the coaxial unit.

Where extended high-frequency response is desired as a pleasing balance to the bass efficiency, the *E-V* T-35 "Super-Sonax" very-high frequency driver may be added as shown on the facing page. This is the equivalent of the 114-B three-way system, and requires the supplementary X-36, 3500 cps network and AT-37 high-frequency level control.

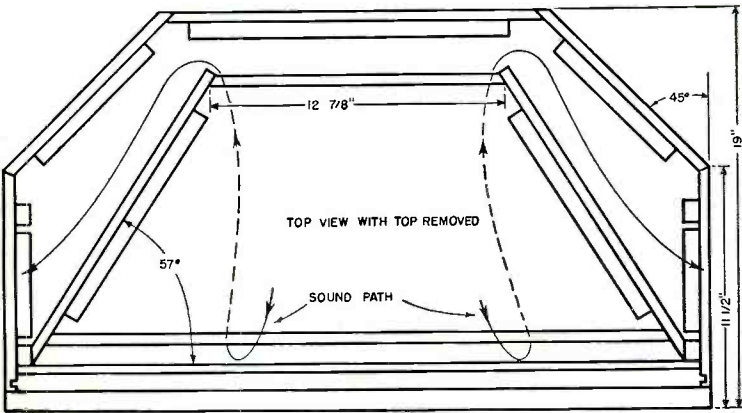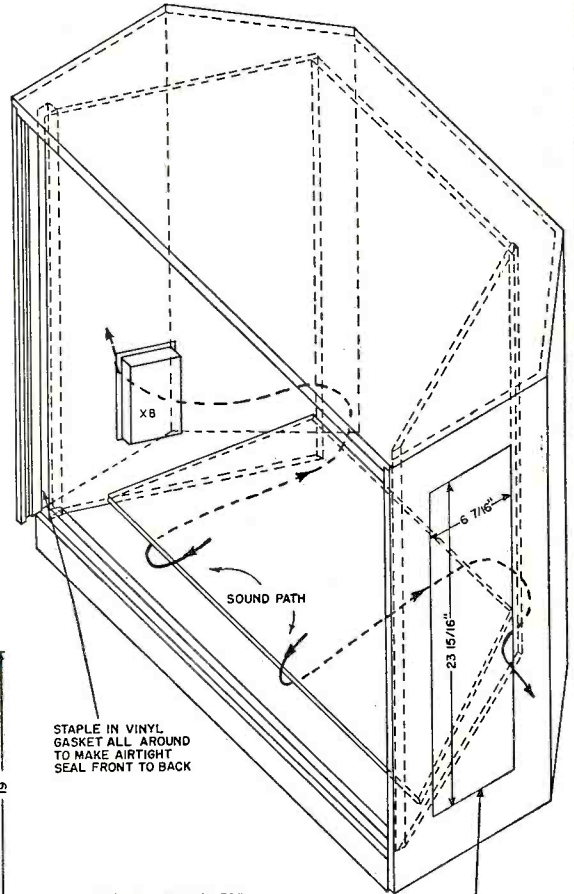
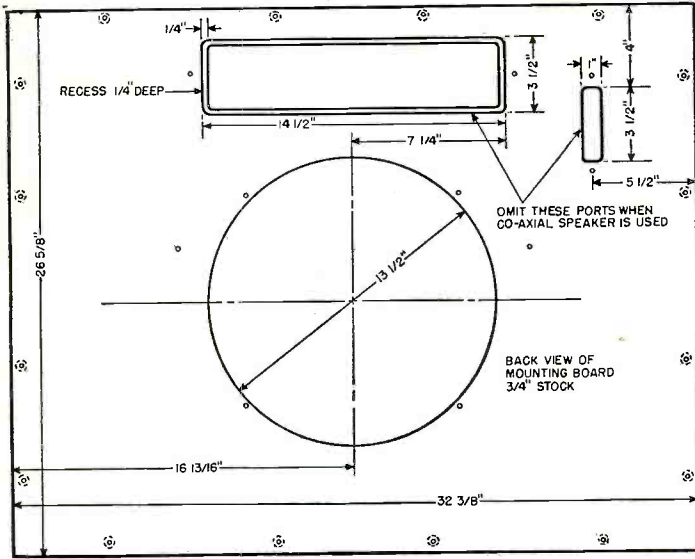
Mechanical details for constructing the Electro-Voice "Regency" loudspeaker enclosure. This housing is designed to accommodate a single 15" speaker, a 15" coaxial unit, or two- or three-way systems. For a two-way system it is necessary to add a high-frequency diffraction horn and with a three-way system a very high frequency tweeter is used.



USE IN A CORNER FOR AUGMENTED BASS AGAINST A FLAT WALL FOR NORMAL BASS

USE SAME SIZE PORT OPENING ON OPPOSITE SIDE


VIEW WITH FRONT MOUNTING BOARD REMOVED

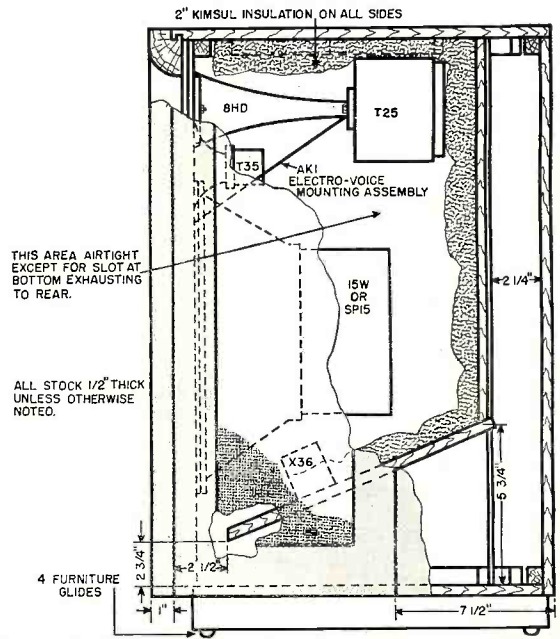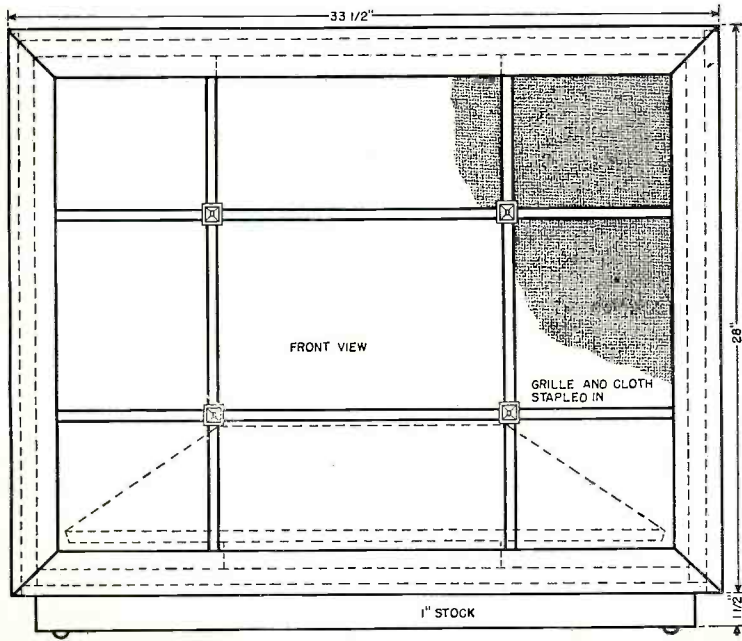

KNOW YOUR 1953 EMERSON TV RECEIVERS

By
BRON KUTNY
Educational Director
Emerson Radio & Phonograph Corp.

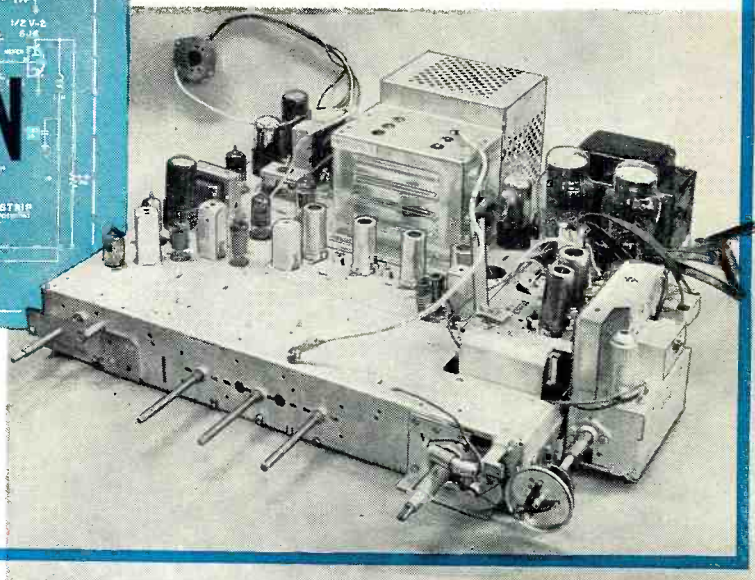Front view of the Emerson chassis 120174B showing the u.h.f. tuner at the lower right.



WITH more television stations going on the air daily, and with more communities being served by u.h.f. or v.h.f. stations, or both, Emerson's new line of TV receivers contains models suitable for all types of reception.

Ultra-High Frequency Tuner

In the all-channel chassis 120174B, a continuous tuner is used in order to receive Channels 14 to 83. For the v.h.f. Channels 2 to 13, a cascode amplifier turret tuner is used. Tuning is accomplished by means of a two-part concentric control for both v.h.f. and u.h.f. so as to reduce the number of knobs necessary for the customer to handle, and also to simplify the appearance of the receiver. With this

Complete circuit explanation of the new Emerson u.h.f. tuner and u.h.f.-v.h.f. receiver with servicing data.

arrangement, the customer uses the channel selector and fine tuning controls for v.h.f., and only a single control, the v.h.f. fine tuner, for u.h.f. The fine tuning control is connected through a gear and dial cord arrangement to the u.h.f. tuner control shaft (Fig. 1).


Conventional balanced-to-ground 300-ohm input is provided for the u.h.f. tuner by two loops of wire fed through the tuner housing and fastened to the tuner chassis. (See Fig. 2.)

The v.h.f. tuner uses the standard input coil arrangement.

The u.h.f. tuner consists of two r.f. preselector tuned circuits which are equivalent to shorted-end resonant lines. These lines are shorter than a quarter wavelength for all u.h.f. channels and, therefore, appear as inductances whose electrical length can be varied by the variable condenser at the open end. The plates of this variable condenser are sometimes bent and may seem to be out of shape. *Absolutely no attempt should be made to straighten these plates.* They are bent to maintain proper tracking over the entire tuning range. The r.f. resonant lines are coupled through their respective shields, either by loops fed through openings, or by slots in the shields.

A 6J6, operating as a push-pull oscillator using lumped constants, oscillates at one-half the desired frequency. This push-pull arrangement and its operation at a lower frequency contributes to stable operation. To obtain the second harmonic frequency which is needed in the mixing action, the tank of the oscillator is coupled to a harmonic generator G7B or G7C crystal. The second harmonic frequency output from the crystal is coupled to a harmonic selector tuned line. The signals from this harmonic selector line, and the second r.f. preselector, are fed through coils L_5 and L_6 to a 1N82 mixer crystal (D_1 in Fig. 2). The 40-mc. output is then applied to the 13-position v.h.f. turret tuner, where the 6BK7 r.f. amplifier is now used as a low-noise 40-mc. i.f. ampli-

Fig. 1. Combination of u.h.f. and v.h.f. tuners showing the tuning mechanism.

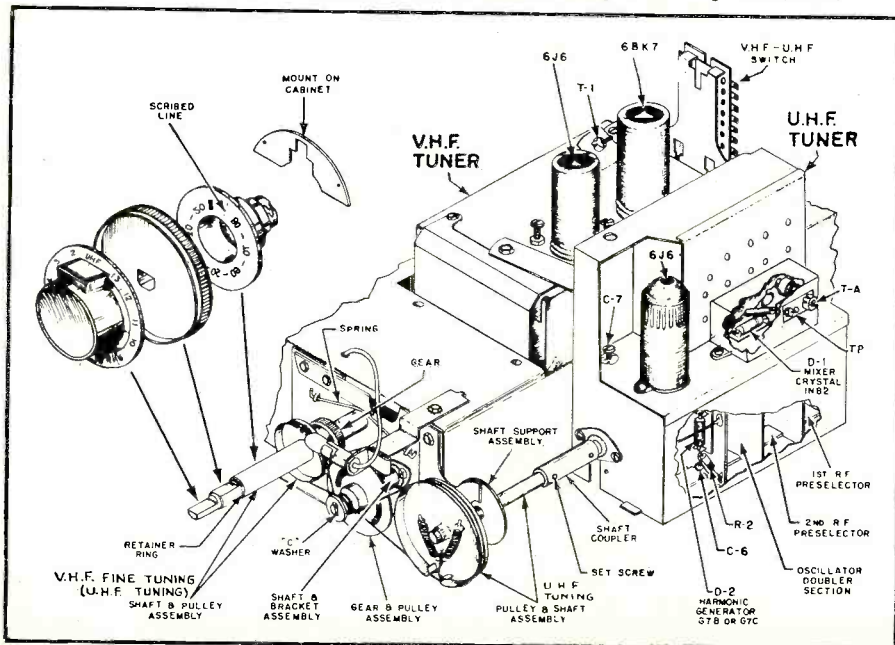

fier. (See Fig. 3.) The 6J6, V_2 , which is the v.h.f. mixer and local oscillator, receives no oscillator plate voltage in the u.h.f. position and, therefore, the oscillator section is completely inoperative during u.h.f. reception. The mixer portion of the 6J6 has a negative voltage applied to its grid from a negative tap on the power supply through the u.h.f.-v.h.f. switch and v.h.f. tuner test point, and it becomes another low-noise triode i.f. amplifier. The output from the i.f. preamplifier is then fed to the standard 40-mc. i.f. amplifier on the main chassis. In the v.h.f. position, when u.h.f. oscillator operation is not required, the plate voltage is reduced but not eliminated. This is done to prevent cathode poisoning.

All u.h.f. tuners are pre-aligned at the factory and will not normally require adjustment in the field. However, if the 6J6 u.h.f. local oscillator is replaced, the tracking on the u.h.f. band may be off slightly. Under these conditions, it would be best to try several 6J6's until one with similar characteristics to the original is found. If another tube is not available, it may be necessary to compensate for the minor difference by adjusting C_7 (see Fig. 1) slightly for the highest channel received.

A combined u.h.f.-v.h.f. antenna can be connected to the receiver through a common 300-ohm lead-in, or separate u.h.f. and v.h.f. antennas can be connected through independent lead-ins. An internal connector is provided for use with the common lead-in, and connects the antenna into the u.h.f. or v.h.f. tuner when the channel selector is rotated to the desired position. If separate antennas are used, this connector can be removed from the outside of the cabinet and requires no internal adjustments.

The u.h.f.-v.h.f. switch, shown in the upper left of Fig. 4, is automatically operated by a cam located on the v.h.f. tuner shaft. This cam changes the switch from its v.h.f. position (as in Fig. 4) to its u.h.f. position (slides one step down) whenever the v.h.f. tuner is set for u.h.f. operation. In the v.h.f. position, the antenna is connected through switch contacts 8-9 and 17-18 to the high-pass filter L_{15} , and thence through switch contacts 2-3 and 11-12 to the v.h.f. tuner. "B+" is supplied to the u.h.f. tuner through the 100,000-ohm resistor R_6 , preventing the 6J6 in the tuner from oscillating but allowing some current flow through the tube to prevent its cathode from being poisoned during long periods of v.h.f. reception when it is inoperative.

With the switch in the u.h.f. position, the v.h.f. antenna, or combination u.h.f.-v.h.f. antenna, is disconnected from the v.h.f. tuner and connected through switch contacts 7-8 and 16-17 to the input of the u.h.f. tuner (terminals 3 and 4 on the connector TS-1 in Fig. 4). If a separate lead-in is used for u.h.f., it should be connected directly to the u.h.f. tuner

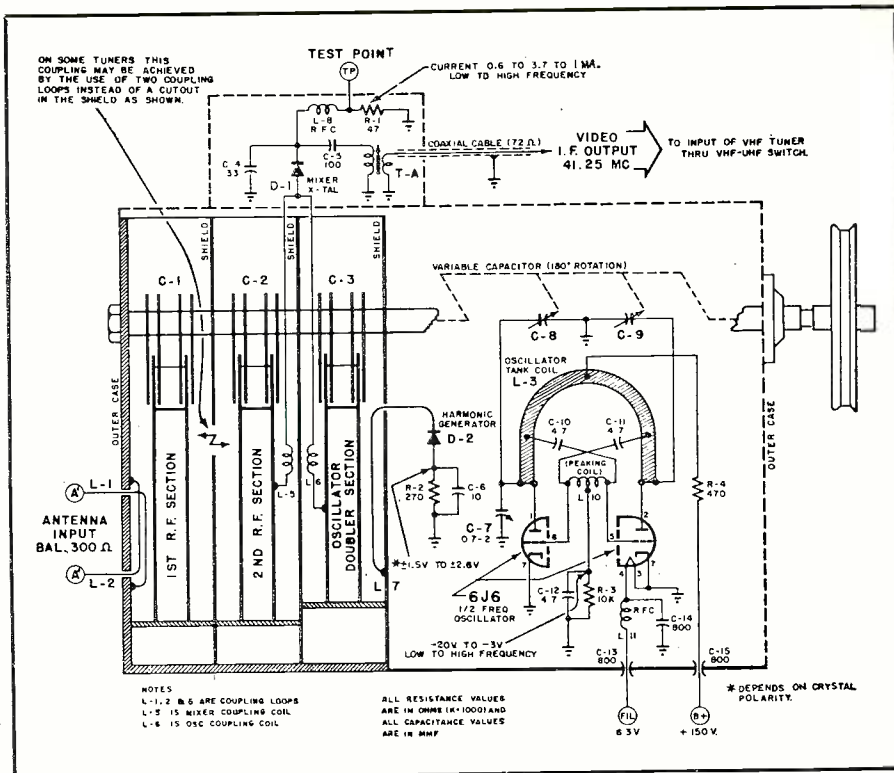


Fig. 2. Schematic diagram of the Emerson u.h.f. tuner showing test points.

antenna terminal; terminals 3 and 4 on the connector strip should be disconnected. The single-ended output of the u.h.f. tuner is fed through switch contacts 1 and 2 to the input of the v.h.f. tuner. The 100,000-ohm resistor, R_6 , is shorted out by the switch through contacts 14 and 15, so that full "B+" (150 volts) is applied to the u.h.f. tuner. To enable the v.h.f. mixer tube to function as a 40-mc. amplifier when tuned to u.h.f., fixed grid bias is applied to the mixer through switch contacts 5 and 6 and the v.h.f. test point. Of course, the high-pass filter is switched completely out of the circuit for u.h.f. operation.


The i.f. amplifier is of conventional design, using three 6CB6's in three stagger-tuned stages. (See Table 2 for

alignment of the i.f. amplifiers.) The first and second i.f. amplifiers are controlled by an a.g.c. line that is independent of the r.f. a.g.c. For this intercarrier receiver, the sound is taken from a 4.5-mc. take-off in the second detector output circuit and fed to the sound i.f. amplifier. The signal is limited by a 6AU6, detected by a Foster-Seeley discriminator, and then fed to a conventional audio output circuit. Table 2 contains alignment instructions for the sound section of the receiver.

Delay in Tuner A. G. C.

A subject worth going into is the a.g.c. because of its deviation from the common types of a.g.c. found in most receivers. To appreciate the

Fig. 3. Schematic diagram of the Emerson v.h.f. tuner described in the text.

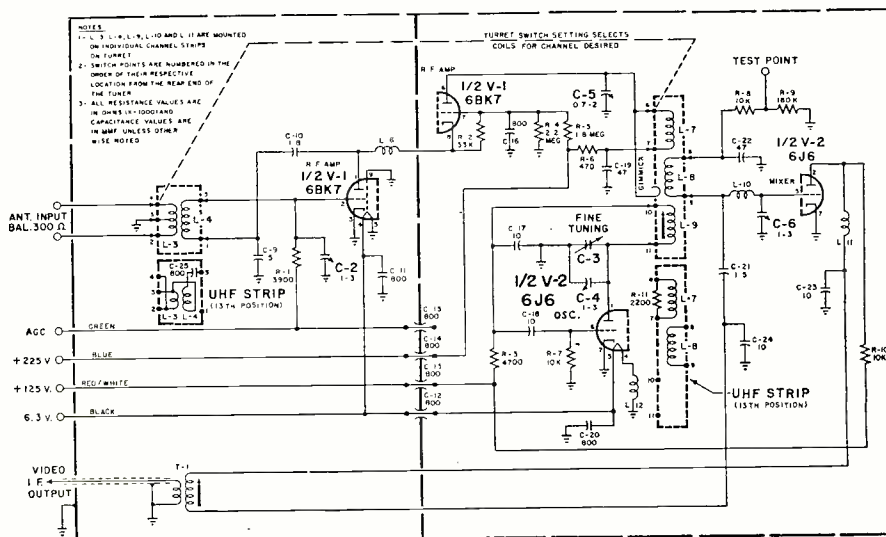

variation, the need for it must be understood.

Early television receiver a.g.c. systems fell into one of three general categories:

1. No a.g.c.
2. Simple a.g.c., where the control voltage is obtained from the negative d.c. component developed across the video detector load resistor. (Fig. 5A.)
3. Voltage-doubler a.g.c., using a separate diode to rectify the composite video signal at the output of the i.f. amplifier, and adding it in series with the simple a.g.c. developed by method 2. (Fig. 5B.)

The requirements for a good a.g.c. has, no doubt, been seen by many

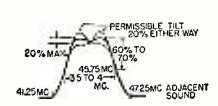
COMPONENT	CHECK POINT	VARIATIONS LOW TO HIGH FREQUENCY	POSSIBLE TROUBLE (If voltage readings are not normal)
6J6	"B+"	+150 v.	C ₁₀ , C ₁₃ , C ₁₁ shorted, the v.h.f.-u.h.f. switch.
	Filament	6.3 v.a.c.	L ₁₁ open, C ₁₄ , C ₁₃ shorted.
	R ₃	-20 v. to -3 v.	R ₃ open, C ₁₂ shorted, L ₁₀ open or shorted.
D ₂ Harmonic Gen. Crystal	R ₄	±1.5 v. to ±2.6 v.	Crystal defective, L ₇ shorted to chassis, C ₇ shorted. Voltage polarity depends upon crystal polarity.
D ₁ Mixer Crystal	Current through R ₁ . Insert milliammeter	0.6 through 3.7 to 1 ma.	D ₁ defective, C ₄ shorted, L ₈ open.

Table 1. Troubleshooting data for the Emerson u.h.f. tuner.

television technicians but, more often than not, not understood. To give examples of two extremes, when a technician installed a receiver in a strong

signal area, the picture would become extremely contrasty and, on some receivers, there would be a complete loss
(Continued on page 114)

Table 2. Alignment procedure for the video i.f. and sound circuits of the Emerson 120174B chassis.

VIDEO I. F. ALIGNMENT						
STEP	SIGNAL GENERATOR FREQUENCY	CONNECT TO	OUTPUT INDICATOR	CONNECT TO	ADJUST	REMARKS
1	45.75 mc. unmodulated	Floating shield of converter tube V ₂₃ (6J6)	V.T.V.M.	Video test point D	T ₄ for maximum reading	Adjust output of signal generator so that maximum response does not produce more than -2 v. d.c. on V.T.V.M.
2	43.2 mc. unmodulated	Same as above	Same as above	Same as above	T ₃ for maximum reading	
3	42.0 mc. unmodulated	Same as above	Same as above	Same as above	T ₂ for maximum reading	
4	45.0 mc. unmodulated	Same as above	Same as above	Same as above	L ₈ , T ₁ for maximum reading	
5	41.25 mc. unmodulated	Same as above	Same as above	Same as above	L ₂ for minimum reading	Increase output of signal generator
6	47.25 mc. 400 cycles amplitude modulated	Same as above	Oscilloscope gain near maximum; horizontal sweep at 400 cycles	Same as above	L ₁ for minimum vertical deflection	Set signal generator at maximum output
7	44 mc. center frequency. 10 mc. sweep. Marker generator at 45.75 mc.	See Fig. 8	Oscilloscope	Same as above	T ₄ for waveform below	Set signal generator output as low as possible
						
SOUND ALIGNMENT						
8	4.5 mc. unmodulated or tune to on-the-air TV channel	Pin 7 of V ₄ (through .01 μfd. condenser)	V.T.V.M. (through 10,000-ohm resistor)	Junction of C ₃₀ , R ₃₅ , and R ₃₆	T ₅ top or bottom for maximum reading. T ₆ top and bottom for maximum reading	Adjust signal generator output (or antenna coupling) to produce a 1-volt d.c. rise on meter. If using signal generator short pin 1 of V ₃ to chassis T ₇ secondary adjustment is on top for part #708018, #708151; on bottom for part #708017
9	Same as above	Same as above	Same as above	Junction of R ₄₄ and C ₃₄	T ₇ secondary for maximum negative reading	
10	Same as above	Same as above	Same as above	Same as above	T ₇ primary for maximum negative reading	
11	Same as above	Same as above	Same as above	Same as above	T ₇ secondary for zero d.c. reading	
4.5 MC. VIDEO TRAP						
12	4.5 mc. unmodulated	Pin 2 of V ₅ (through .01 μfd. condenser)	V.T.V.M. (negative scale)	Junction of R ₃₄ , T ₆ , and C ₂₉	L ₈ for minimum negative reading	Short pin 1 of V ₃ to chassis. Set contrast control completely counterclockwise. Repeak T ₅

SIX-METER EMERGENCY TRANSCEIVER

By

ROBERT L. HANKEY, W30BC

and

MAURICE P. JOHNSON, W3TRR

WAAM (TV) Engineering Dept.

THE DESIGN of most emergency amateur equipment, portable gear intended to be carried by hand in particular, is necessarily a compromise dictated by the unyielding demands for lightweight, small size, and low battery drain. Naturally this results in simple receivers and low power transmitters. To obtain any degree of reliable communication between such units, the choice of operating frequency warrants careful consideration.

Persons aware of current trends in emergency equipment probably already realize that the six-meter band is being favored as the band best suited to this type operation. Six meters gives satisfactory coverage, yet is not cluttered with the QRM so typical of the more active lower frequencies. Reasonably efficient designs for six-meter gear are possible with conventional components and without complex circuitry, since the band is within the frequency ratings of most miniature tubes. Another point of amateur interest is the antenna efficiency which can be obtained with reasonable antenna lengths.

For these and other reasons the FCDA prefers six meters for *RACES* (Radio Amateur Civil Emergency Service) use rather than the more popular ten-meter band. Local coverage is likely to be more reliable because "six" is less frequently bothered by DX interference, which can be a serious factor. The FCDA's plan for "matching funds" to supplement community expenditures for CD radio does not allow for the setting up of new ten-meter systems, although it does allow for replacement and growth in existing systems. A community about to set up a *RACES* system, or an existing system wishing to add a network of hand-carried portables, would do well to consider six meters.

The six-meter, hand-held transceiver discussed here is the first of several equipment designs being un-



Above, the six-meter transceiver with its antenna. Controls are "tone-voice" switch, regeneration, and battery "on-off." Small hole is for receiver tuning. At right, one of the transceivers is shown in operation.

The six-meter amateur band has advantages in equipment and performance over both "ten" and "two" for CD and other portable-emergency work.

dertaken to provide a complete portable and emergency service, and is thus well suited to Civilian Defense needs. This transceiver meets the demands for a compact, lightweight, battery-powered unit, entirely self-contained, intended for use at locations that would be inaccessible to mobile or other equipment.

As six meters had been selected as the most promising band for the equipment, considerable effort was directed toward an efficient transceiver design. Previously published material was carefully perused, and several worthwhile ideas gleaned, but no design was encountered which completely met our requirements. It was therefore decided to establish our own design criteria, and make trial constructions and tests to check the various circuits examined.

Ordinary modulated oscillators and superregenerative receivers were combined in some of the simplest transceiver designs and a test of such a circuit was made. A two-tube set was constructed, one tube for the oscillator and detector, the other as modulator and audio amplifier. The circuit adapted itself to extremely compact construction and low battery drain, but the faults inherent in its simplicity did not permit the unit to meet our specifications. The transmitter proved to be much too unstable for dependable fixed-frequency reception, and the superregenerative detector produced excessive radiation. Body-capacity effects on the antenna affected stability to a great degree, which was considered especially undesirable in a hand-held transceiver.


These tests of the simplest transceiver circuits indicated that somewhat more refined circuitry would be necessary if any degree of reliability was to be obtained.

The circuit which finally evolved after considerable study, test, and discussion is a carefully balanced choice of the features needed to provide the desired stability and dependability without undue weight or battery drain. As the design of the prototype units progressed, every effort was made to avoid special, subminiature, or surplus parts, so that duplication could be more easily accomplished.

Our contemplated six-meter project is based upon single-frequency network-type operation, with transceivers intermingled with other mobile-portable and fixed station equipment, and with the majority of receivers intended for fixed-frequency operation. Therefore, crystal control of the transmitter became almost mandatory in the interest of frequency stability. Harmonic-type oscillator circuits were rejected in favor of a conventional triode oscillator with multiplier stages, since the latter was considered somewhat less difficult to adjust and tune.

Four stages in the r.f. lineup make use of two dual-triode tubes, multiplying the crystal frequency eight times to produce the six-meter carrier. The oscillator plate circuit tunes to the crystal frequency, with each following stage functioning as a doubler. Operating the final amplifier as a doubler admittedly reduces the efficiency, but this slight sacrifice avoids the necessity of neutralization.

A receiver of comparable perform-

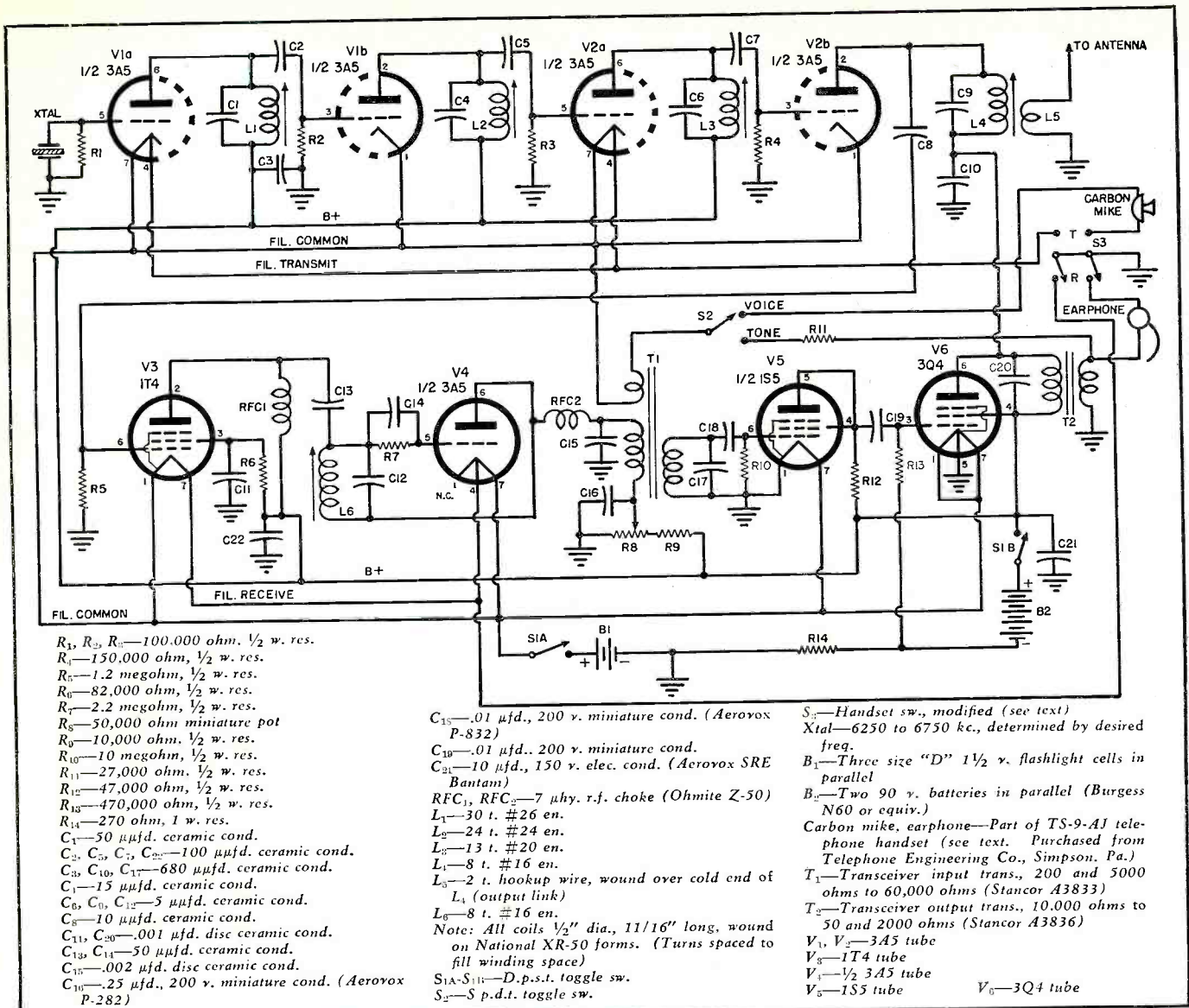



Schematic of the six-meter CD and emergency portable transceiver. The two audio tubes are shared by transmitter and receiver; the transmitter output tank coil doubles as an input coil for the receiver r.f. stage, thus eliminating antenna switching. Otherwise the transmitter is distinct from the receiver, unlike the usual tube-sharing "transceiver" circuit.

ance was the next objective. Examination of the superheterodyne circuit indicated that the inherent complexity for even moderate sensitivity would not be justified in this application. The excellent sensitivity of the superregenerative detector makes it worthy of consideration. It possesses a degree of a.v.c. action in itself, and its slightly broad bandpass characteristic is not particularly objectionable for a fixed-tuned receiver on an uncrowded band. Furthermore, its simplicity lends itself admirably to a compact construction such as this.


A triode circuit was found to produce the smoothest performance in this particular unit. One-half of a 3A5 was finally used as about the only tube available. Control R_8 is the regeneration control, made variable to allow adjustment for battery voltage changes, and to permit optimum detector operating adjustments. The values of C_{11} , R_{11} , and C_{15} all affect the operation and the listed values were those which gave best results in this circuit.

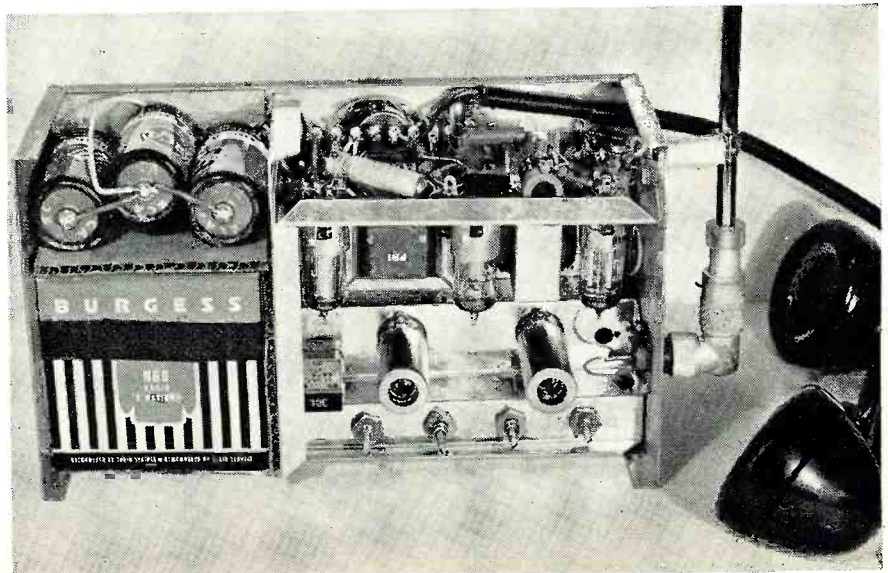A view of the transceiver with the cover removed and antenna attached. The transmitter and receiver occupy separate chassis, simplifying construction. The receiver is intended for fixed-frequency use and is slug-tuned through a hole in the case.



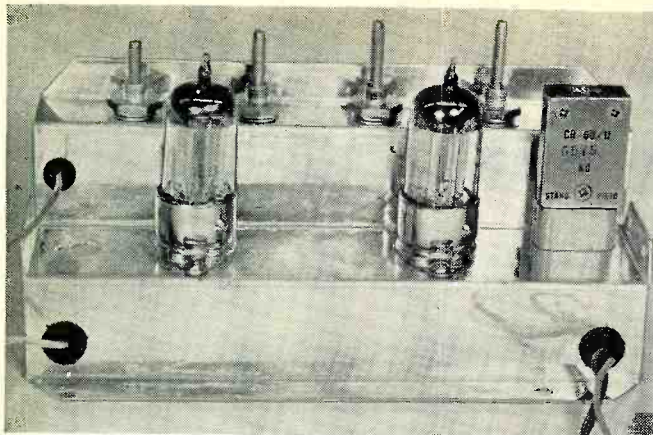

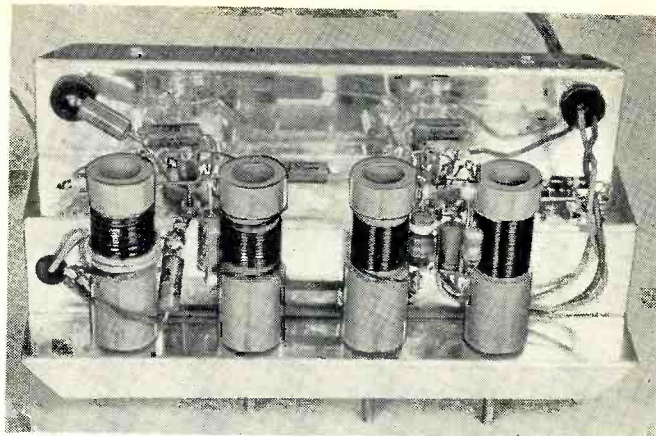The transmitter chassis, showing small size and simplicity of the unit. Grommet at upper left carries the antenna lead; the other is for receiver input. Modulator is on receiver chassis.



Under-chassis view. Oscillator at right operates on crystal fundamental; all other stages, including final, are doublers. Parts are standard. Chassis is cut from a transcription disc.

The primary objections to the super-regenerative detector, namely oscillator radiation and antenna loading effects, were remedied in this receiver by incorporating an r.f. stage to isolate the detector from the antenna. A pentode amplifier is used which helps to increase the sensitivity of the receiver.

The use of an antenna changeover relay or switch was avoided in a practical and convenient manner. Coil L_a , together with C_a , serves the dual role of tank circuit for the transmitter final and also tuned input for the receiver. Condenser C_s and R_s form the receiver coupling, and by proper choice of values very little energy is lost when transmitting.

The requirements of the modulator and receiver audio amplifier were easily combined in a common circuit using two tubes. One winding of a dual-purpose input transformer couples the detector to a pentode voltage amplifier. The other primary introduces the single-button carbon mike when transmitting. The button current is drawn from the filament string. Contact bias on the voltage amplifier produces excellent gain in the stage, which is RC-coupled to the power output tube. The output transformer secondary matches the tube to the

receiving earphone, and the primary is used for the Heising modulator.

The selector switch S_2 injects a side-tone which makes a very convenient modulating signal for alerting or tuning the receiving station. Proper phasing of the windings in the feedback loop is essential to generate the tone.

The power changeover for "transmit-receive" switching is accomplished by S_3 . Half of this d.p.t. switch completes the ground path for the filaments of each section as required, while the other half completes the mike or earphone circuit, depending upon the use. The dual-purpose audio section operates continuously as it functions during both reception and transmission.

The advantages of having this push-to-talk changeover incorporated as a switch in the handset were obvious. Several TS-9-AJ handsets with butterfly switches were available, and these were carefully rebuilt as d.p.t. switches by using thinner insulating spacers and adding two switch leaves. The "receive" contacts were adjusted to be normally closed. A length of four-wire cable with a shield for the ground return was connected from the handset to the transceiver proper.

Should this handset revamping be

considered too laborious to the constructor, the same electrical results can be accomplished by mounting a spring-return switch on the transceiver within easy reach of the carrying handle.

The handset clips into the carrying handle when not in use. This handle is a U-shaped bracket which was folded from $\frac{1}{16}$ -inch aluminum stock in such a manner as to grip the handset snugly.



The controls on the front panel are the regeneration control, the "tone-voice" switch, the battery "on-off" switch, and an access hole for tuning the receiver slug. The antenna mounts on the front end of the cabinet and, if desired, a terminal strip can be included for external battery connections.

It is suggested that a careful study of the schematic, photographs, and sketches be made before duplication of the transceiver is undertaken. The parts layout and method of construction will be evident from the photos. Careful adherence to the layout and listed parts is suggested to circumvent unnecessary complications in assembly.

The entire rig is fitted into a Bud CU-2110 "Minibox," measuring 6"x10"
(Continued on page 77)

Top view of the receiver and audio section. The transceiver transformer is at left; output/modulation transformer at right. The tubes, left to right, are the 1T4, 3A5, 1S5, and the 3Q4.

Receiver and audio section under-chassis view. Ceramic sockets are used for the r.f. amplifier and detector tubes. Note the coil-mounting bracket. Potentiometer is regeneration control.

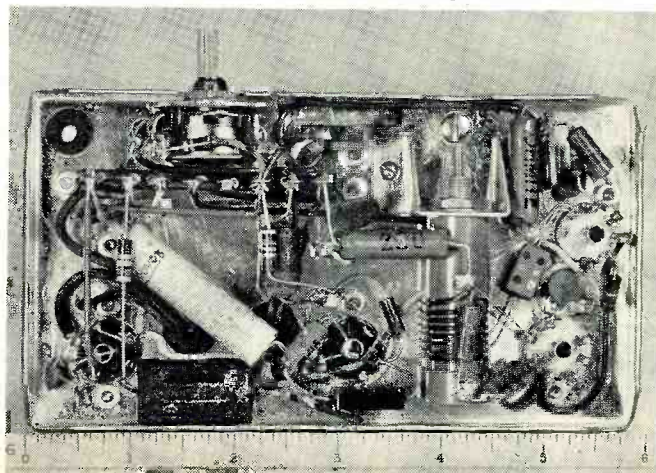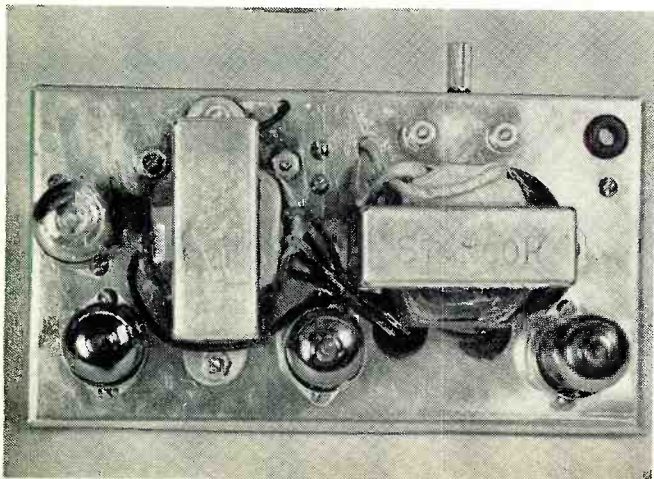

ADAPTING V.O.M. AS A FIELD STRENGTH METER

TRANSMITTER workers, both amateur and professional, have long known that the *field strength meter* is better for tuning up output and antenna circuits than antenna ammeters, plate milliammeters, or any other single instrument. All too often, however, it is not used—either because one is unavailable for some reason, or because it would represent just one more bulky object to be added to the already heavy load of instruments and tools to be carried to the field.

The photograph at right above shows an adapter which will convert the conventional volt-ohm-milliammeter normally carried by a technician, into a sensitive field strength meter which will give accurate relative measurements of actual radiated power on any frequency up to thousands of megacycles.

The sensitivity may be judged from the fact that the pointer of the instrument in the photograph is being deflected $\frac{2}{3}$ of full scale, or about 68 microamperes, by the relatively feeble amount of power being generated (in this case on 50 megacycles) by a grid-dip oscillator in the same room.



The adapter requires no power source, weighs only one-half ounce, can be tucked away in the meter-lead compartment of the instrument, and, best of all, it can be made in minutes from surplus and scrap.

Its general aspect is shown in the photo above (left). The heart of the adapter is a 1N21 radar crystal, used as a detector. The mechanical design of the adapter connects the crystal across the meter input, in parallel with the normal leads, which are used as a pickup dipole antenna. Since the length of the leads determines the resonant frequency of the detector, a special pair may be used for any particularly important frequency, or they may be tuned by rolling them up, or clipping onto other nearby metallic objects to add length to the antenna.

The simplest mounting base is one of the Bakelite fuse strips found in about every major surplus equipment item. One of the pairs is sawed off, leaving enough Bakelite on one side so that it will cover the input jacks.

Two strips of thin brass stock (photo right) are cut to the approximate shape shown, and fastened under the fuse clips. Two holes *one size smaller* than the exact diameter of the meter-lead plugs are drilled through the brass and the Bakelite, and the brass pieces slit as shown so they form

By **ELBERT ROBERSON**

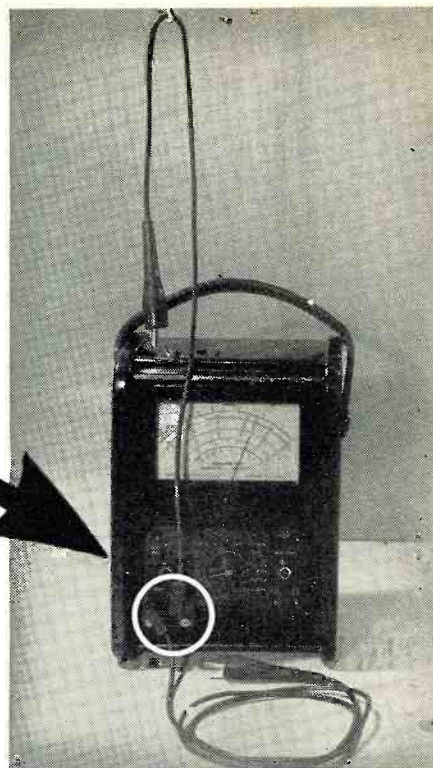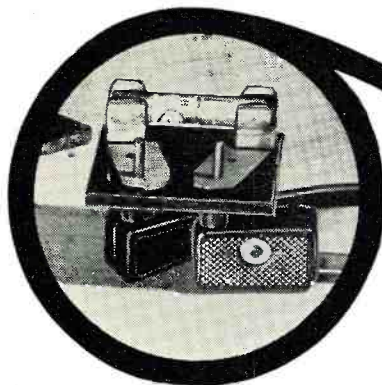

A common volt-ohm-milliammeter is quickly converted to a sensitive field-strength meter by connecting a crystal diode across the input terminals by a simple adapter. Meter leads plug through the adapter, securing it and providing an antenna.

This simple adapter converts a transmitter technician's v.o.m. into a field-strength meter for on-the-spot checks.


spring contacts. The holes in the Bakelite are reamed slightly so the plugs fit snugly. The hole spacing should be exactly the same as that in the meter, so the plugs will fit through the adapter holes and into the meter jacks.

The cartridge-like rim on the end of the surplus crystal is then filed off, and a piece of $\frac{1}{4}$ " rod, either brass or aluminum, is then cut to make up the length between the fuse clips, and is drilled in the end to take the crystal tip. The extension is slipped onto the tip, and the assembly is clipped into the holder, just like a fuse.

Of course the crystal must be clipped in with the correct polarity to make the meter read properly.

If it is desired to make use of the later model crystals with pigtail leads,

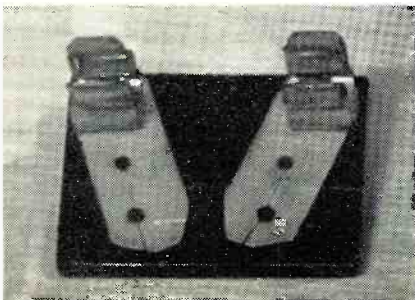The fuse clips and brass contact strips are mounted as shown. Strips are slit for "spring" effect for positive contact.




solder lugs may be substituted for the fuse clips, and the crystal mounted between them.

In the field, the test leads and the adapter are plugged into the meter, the selector switch set on the microampere position, care being taken, if transmitter power is high, not to "pin" the meter. If pickup is too great for safety to the meter, the leads may be shortened or rolled up. If insufficient pickup is obtained, the leads may be connected to other metal objects.

The meter should be placed as far away as working area and vision permit so that movements of the operator will not affect the indications and in order that direct pickup from the transmitter is minimized. An example of correct placement would be the case of tuning a small boat transmitter, with the meter placed in sight of the operator on the stern of the boat or preferably, on the dock. With transmitters located on dry land the possibilities for placement of the meter are virtually unlimited, and fences, automobiles, trees, etc., may be used to support or augment the antenna.

With correct placement and a proper pickup circuit, excellent comparisons may be made for tuning transmitters of as little as five watts' output. The adapter can be used with any instrument having a microampere or sensitive low-voltage scale.

Fig. 1. External view of the security radio showing large dial for accurately logging stations, combined "on" and "off" switch and volume control, the interlock battery switch, and accessories compartment for battery, headphone, and the hank antenna.

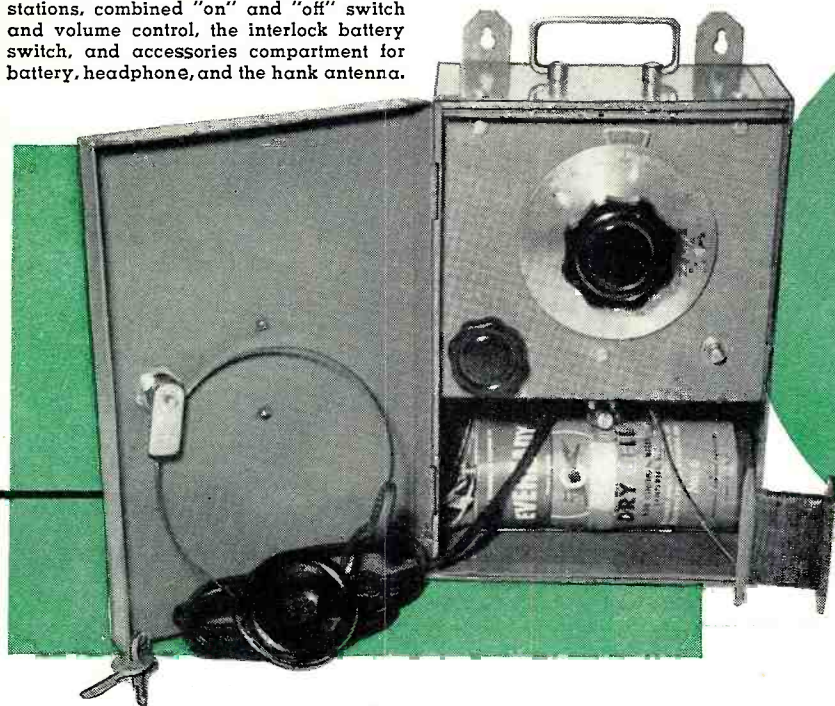

A HOME SECURITY RADIO

By
H. G. BOURNE and E. J. CORDIER
Ohio Department of Health

A rugged, four-tube superhet which combines good sensitivity with long battery life—insuring reliable emergency service.

THE fear reaction of military personnel who were not acquainted with the technical details, atomic bomb, was appalling at Bikini and Eniwetok. The fear reaction of the uninitiated civilian is ever evident. It is of such magnitude that it could well interfere with an important military mission in time of war." So states the Army Medical Department in the publication "What You Should Know About the Atomic Bomb."

One of the major causes of panic is fear. Terror of the unknown promotes disorganized behavior. By predisaster education and training, the threat of unknown or fantastic dangers may be diminished. During the emergency or danger situation itself, and for several hours to a day or more thereafter, other factors such as rumor, suggestibility in contrast to critical judgment, imitative behavior (people run when others run), and tension and insecurity will continue to operate to produce panic.

Civil defense authorities may inform the individual, stimulate leadership, dispel fear, and explain the procedure one must follow to satisfy basic needs such as hunger and safety if a means is available for communication with each household. How can this panic-decreasing information be conveyed

to the individual in the absence of telephone service and failure of conventional broadcast receivers subject to community electric service?

There are those who have counseled that aircraft, taxis, and police cars already equipped with radio receivers be provided with a public address system to soundcast information and instruction. Such a procedure limits the broadcast information to short disconnected phrases such as "Boil water!" "Stay indoors!" "Keep off the roads!" Such brief pronouncements containing a modicum of truth in the absence of explanation may be elaborated, distorted, misinterpreted, mangled, and constantly magnified with each retelling until they contribute to hysteria.

Moreover, loud noise as from a public address system may, in conjunction with other sounds, directly contribute to panic. Caldwell *et al*¹ state "In a disaster people may hear the loud noise, smell objects burning, and see people running. These sensory stimuli heighten excitement and contribute to panic behavior." Schmidberg² in describing British experience has stated "Auditory impressions in war exercise the strongest effect of all on nerves. The whistling of falling bombs, the sounds of their explosions, and the boom of the anti-aircraft guns

mingle in the inferno of noise with shattering effects on the nerves."

Others have recommended battery-operated portable broadcast-band receivers of the vacation type or automobile radios as a means of communicating with householders. In each household, however, unless leadership is maintained, the collective behavior of the group will be panic in type. To maintain leadership, civil defense communications affecting the family unit should be directed exclusively to the family head. This privacy of communication is defeated by a speaker-equipped vacation or automobile receiver. Moreover, World War II recollections suggest in the event of future conflicts the majority of vacation receivers will be inoperative because batteries are unobtainable. An automobile receiver is a heavy drain on the car storage battery. And, a dead battery is poor preparation for flight if evacuation is ordered. If the car engine is run to maintain the battery charge, the usual caution to avoid running internal combustion engines in closed garages is likely to be disregarded in time of mental stress and more deaths can be anticipated from carbon monoxide poisoning than lives saved by radio-acquired information. Hence neither personal-type, battery-operated radios nor the automobile receiver provide a satisfactory solution.

A special-purpose, home-security radio of improved sensitivity and powered by a universally available battery is proposed by the authors. One receiver believed to be suitable is described in the hope it may stimulate further development and eventual commercial manufacture for public service.

There are now available to the public portable radios that are inexpensive and of simple operation; such features pose no special problem. Reli-

ability may be secured through the use of quality components adequately protected from the destructive forces of man and nature. Two features of the emergency home receiver, however, require special study, i.e., source of power and sensitivity.

Energy Source

The ideal source of energy for a home-security receiver would be a single battery of sufficient capacity and infinite shelf life which could be energized by the addition of tap water or urine. Furthermore it should be of convenient size and weight, commercially available everywhere, low priced, and nonpillable. Since no such battery was known to the authors a single No. 6 dry cell was selected as a compromise. The standard No. 6 dry cell will deliver 80-90 per-cent of its original power when placed in use at the end of one year and 50 per-cent even at the end of two years. It may be replaced for less than \$1.00 and otherwise appears to satisfy the requirements of an ideal battery.

The useful life of a No. 6 dry cell would obviously be too brief to operate any radio expected by the public to provide entertainment; however, in the event of disaster, a receiver would give emergency service if it was capable of maintaining a schedule of 10 minutes "on," 20 minutes "off" for 8 hours (daylight) and then after an overnight rest the same schedule repeated for a total of three days. The power pack was therefore designed to adapt the energy from a single No. 6 dry cell to the operation of a receiver for three days on this timetable. It remained to construct a receiver to combine minimum battery drain with high sensitivity.

The circuit and components of a vibrator power supply which proved satisfactory are shown as part of Fig. 2. Although commercially available parts were utilized wherever possible, it was necessary to make special chokes and to readjust the standard 2-volt vibrator driver contacts to secure dependable starting and maximum output voltage and current when operating on 1.5 volts. If the vibrator fails to start on 1.5 volts or the "B" voltage is too low due to poor vibrator action, open the vibrator by carefully sawing around the can about $\frac{1}{2}$ " above the base. Turn the driving contact adjustment screw until optimum operation is obtained. Replace the can and hold in place with plastic vinyl tape.

The audio frequency choke, CH₁, deserves special attention. The core was that of a standard output transformer similar to that used as the vibrator output transformer (Knight 8000/3 ohms—Allied No. 62-093). Any small transformer core will do. It is only necessary to remove the "I" section of the core which opens the "E" section. The winding will then slip off easily. First wrap one or two layers of vinyl plastic tape on the core, then wind No. 24 d.c.c. enameled wire about the cen-


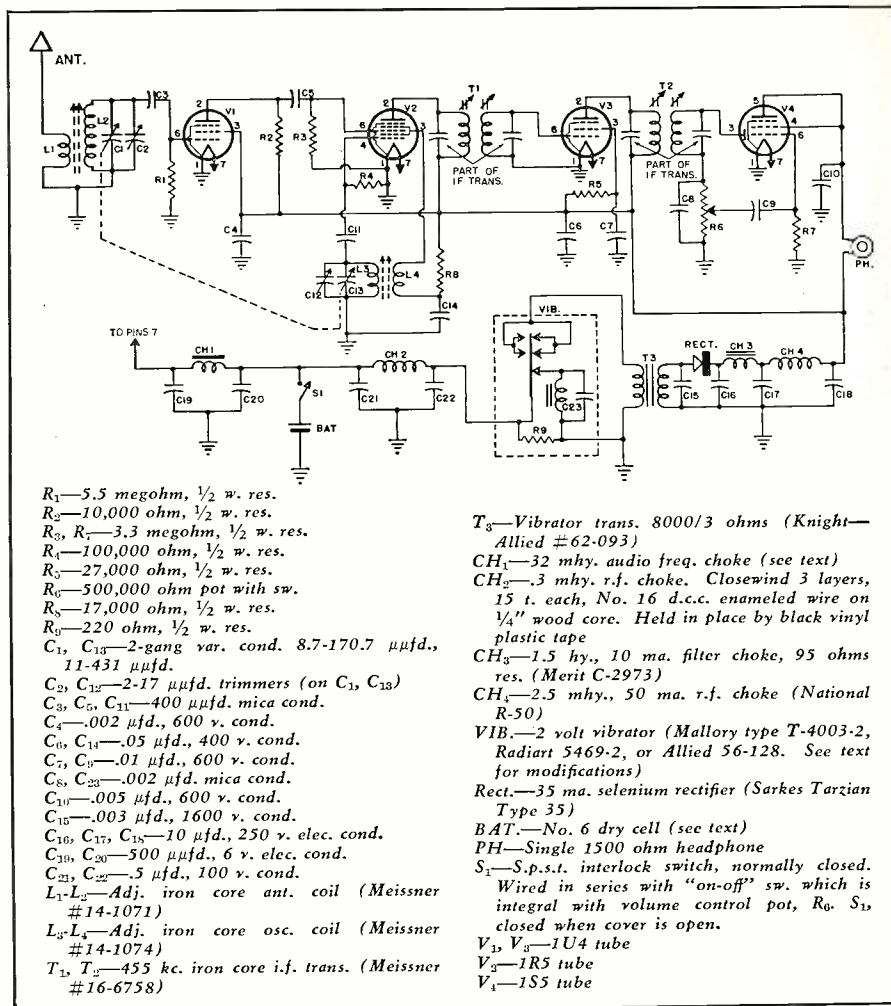


Fig. 2. Complete schematic diagram of the battery-operated "security" radio receiver.

Fig. 3. Internal view showing vibrator power supply mounted on the vertical chassis and receiver proper located on the horizontal chassis. See text for details.

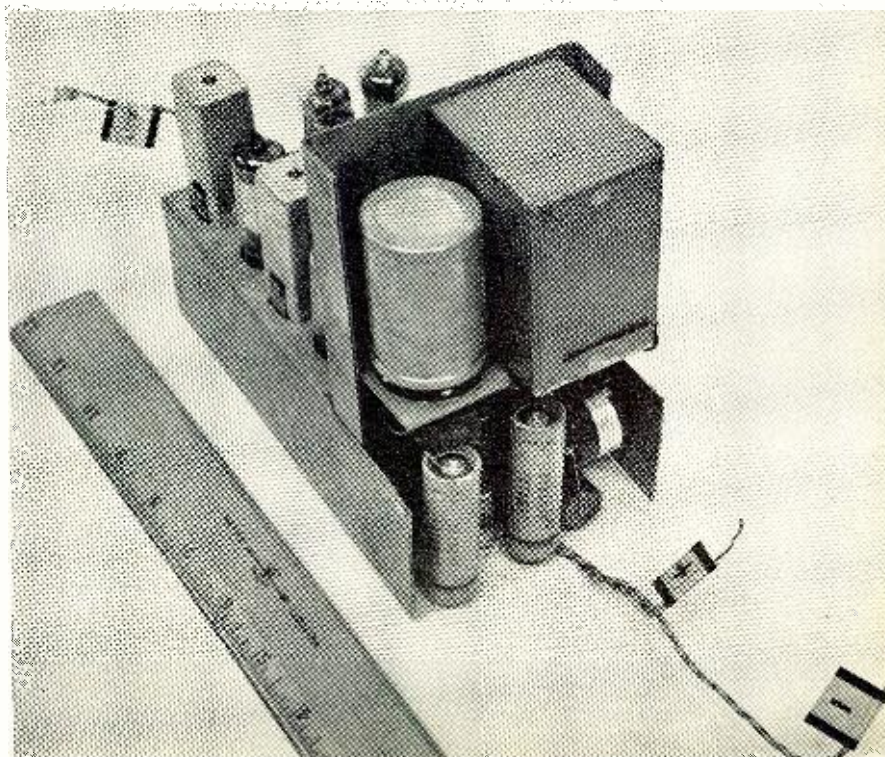

ter leg until the "window" area is full. Replace the "I" section, being careful to make good contact with the "E" section. One must also exercise caution against shorting the wire to the core. The "I" and "E" sections are then held firmly in place by bending the mounting bracket lugs into their former position.

Upon completion of the receiver and its included power pack, trial runs were made to determine the plate potential and current as well as the battery terminal potential as the 10 minutes "on," 20 minutes "off" schedule progressed. After four days of operation the terminal potential of the No. 6 dry cell dropped to approximately 1.2 volts and the vibrator ceased to start.

Sensitivity

The home security radio was designed upon the premise that it must receive, during daylight hours, stations 25 miles or more distant having 1000 watts or less power. Furthermore, the reception must be accomplished with no more antenna than could be located in a cellar or bomb shelter. These specifications are based upon the assumption that metropolitan and suburban transmitters will be silent following an attack for one or more of the following reasons: station destroyed, no power, personnel dead. Elsewhere, silence will be imposed for security reasons except for previously designated transmitters located in the nearest supporting communities. The power output of these outlying stations will be restricted to the minimum necessary to reach the devastated area effectively. Transmissions will proceed during daylight hours in order that the information broadcast can be converted by the family head into appropriate action.

A four-tube superheterodyne utilizing one stage of untuned r.f. amplification was found to be most capable of achieving high sensitivity with low battery drain, portability, operational simplicity, and moderate cost. A similar conclusion was arrived at by Pasow³ who also had the problem of obtaining more sensitivity from loop-operated receivers so that they could be used in isolated communities throughout the country rather than only in metropolitan areas.

Portability and Cost

Sufficient portability to permit the receiver being easily moved from the owner's house to a neighbor's, to the automobile, bomb shelter, or garage is desirable. "Pocket size" is considered unnecessary since the family which may be required to evacuate its home will wisely choose to burden itself with no more than food, extra clothing, money, and valuable papers.

The total net retail cost of the components of the single receiver constructed was \$42.50. Quantity buying, construction simplification, and manufacturing "know how" could be ex-

pected to reduce the cost very considerably. However, it is believed that it is far better that many foresighted families make a financial sacrifice to purchase an adequately built unit rather than to have every household be induced by cheapness to buy a worthless product.

General Description

The receiver circuit is a standard superheterodyne employing a 1U4 in an untuned r.f. stage, a 1R5 as oscillator-mixer, another 1U4 in the i.f. stage and a 1S5 as diode-detector and audio-amplifier. Automatic volume control has been omitted and audio-amplification is limited to that of the 1S5 triode since its output is sufficient to operate the headphone. The untuned r.f. stage represents a compromise between the greater sensitivity of a tuned r.f. stage and the necessity of a large 3-gang condenser and other components which would have increased the size, weight, and cost of the receiver.

The chassis consists of two sections as may be seen in Fig. 3. The horizontal receiver member contains on the topside tubes, i.f. cans, and variable condenser while directly beneath are located the usual fixed condensers, resistors, tube sockets, volume control, safety switch, etc. The vertical power supply chassis is inset into and attached to the receiver unit. On the upper portion of the vertical chassis

is mounted the vibrator and a mini-can containing the high voltage transformer, rectifier, choke, and filter condensers. Underneath are placed the low voltage filtering chokes and high capacity condensers needed to remove r.f. hash and audio-hum produced by the vibrator. This construction and the use of steel chassis material was found necessary to reduce internal noises to an acceptable level.

An external view of the complete receiver is shown in Fig. 1. The sturdy metal box housing the receiver is 10 $\frac{5}{16}$ inches high, 7 $\frac{1}{8}$ inches wide, 4 $\frac{1}{2}$ inches deep and is provided with two mounting ears and a carrying handle. The cover when closed and locked insures against unwarranted use of the radio by inquisitive members of the family. The weight of the entire receiver and accessories is 10 pounds, 6 ounces.


Certain other external features merit special mention. An interlock switch is provided which automatically shuts off the battery when the cover is closed. The battery is intentionally conspicuous to remind the set owner that it must be replaced periodically and to facilitate its change. Moreover since one instinctively associates a limited output with a single battery, its prominent location tends to temper the receiver's use. A hank antenna is provided in place of the more usual built-in loop to add a certain inconvenience to operation, thereby discouraging the radio's use as a casual "plaything." The large dial with vernier enables one to log stations accurately in advance, thereby obviating the necessity of station hunting during an emergency.

Performance

In the absence of suitable laboratory equipment to measure absolute sensitivity, it was necessary to resort to a comparison method in order to evaluate the emergency receiver's performance. In the first test the security receiver (A-2), with 25-foot hank antenna placed in a horizontal position six feet above ground, was compared for sensitivity with a commercial communications receiver (C.R.) employing a suitable outside double antenna and with a commercial four-tube personal portable radio (E.M.) provided with the usual built-in loop. To make this comparison, every broadcast station within a 100 mile radius of the test location was noted and placed in one of four power groups: 250, 500, 1000, and 5000 watts. The number of stations in each power group which each of the three receivers was able to "bring in" during the daytime was recorded and the percent of the total in each power group calculated. The results are presented in Fig. 4A. This bar graph shows that the A-2 radio could receive considerably more stations than a commercial four-tube vacation portable but less than a commercial communications receiver having a sensitivity of ap-


(Continued on page 107)

Fig. 4. (A) Comparative performance of a communications receiver (C.R.), the home security radio (A-2), and a commercial four-tube personal portable (E.M.). "Percent stations" represents the percent of b.c. stations within 100-mile radius of test locations which were received in each of four power classifications: 250, 500, 1000, and 5000 watts. (B) Similar comparison with b.c. stations of 1000 watts power or less made at three sites as indicated on graph.

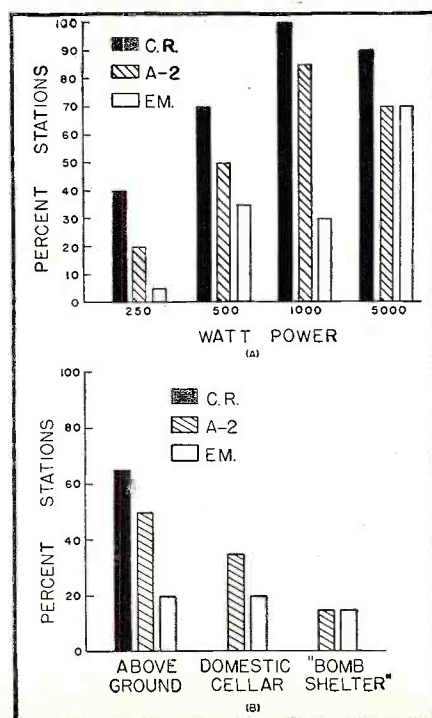

A LOW-COST CRYSTAL CALIBRATOR

By G. L. COUNTRYMAN, W3HH

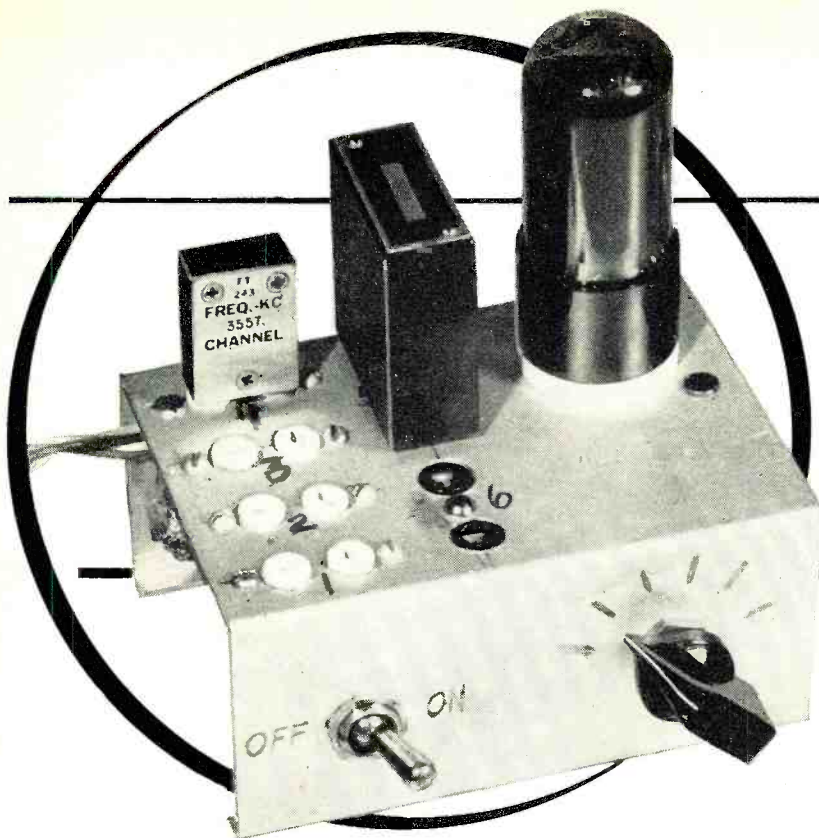

Six-frequency crystal marker assembled from junk-box parts. The circuit will oscillate at almost any frequency. Over-all cost is low.

Crystal calibrators can be expensive, but versatile junior models can be put together at surprisingly little expense.

CRYSTAL calibrators for modern receivers are a "must," especially for operation on net frequencies, but at 25 dollars a copy, they become a luxury item. Their use is even more important if older or more moderately priced receivers are used, as the calibration of these sets is seldom too accurate and varies as the components "age." Most receivers will drift several kilocycles in the first 20 or 30 minutes and, if a schedule is to be kept on a spot frequency, it is nice to be able to come up "on the nose" even if you have forgotten to warm up the receiver in advance.

One "calibrator" or marker unit built by the author is constructed on a small aluminum open-end chassis 4½" long x 3½" wide x 2" high and contains six crystal sockets, four small ones for ½" holders and two for ¾" holders. The tube is a 6V6, but any pentode or beam power tube, regular or miniature, will be equally satisfactory. No power supply is included as there is invariably a source of power in the shack, and any receiver can supply the low heater current and the few ma. of high voltage required.

If the calibrator is to be used with an HRO, a unit with one crystal can be built into a Vector C12-M #3 miniature plug-in turret, using a 6AG5, 6AQ5, or 6AK5 tube, and the turret plugged into the calibrator socket of the HRO. One such unit is shown in the photograph on this page. With this type of construction, turning the HRO switch to either the 100- or 1000- kc. position will operate the marker, as the HRO switch is in the high volt-

age lead. The heater supply and high voltage come from the HRO. Many receivers have an accessory socket from which power is available.

A simple, foolproof circuit is utilized, one that will oscillate with a crystal of any frequency. Your old friend, the modified Pierce with unnecessary "trills" removed, is shown in the schematic. If only one crystal is used, the socket can be wired in place and the selector switch eliminated. It is not too much trouble to plug in different crystals for different frequencies, anyway. A 100-kc. crystal makes it a true calibrator; other crystals provide calibrated marker points.


The cost is very close to the zero point. Most amateurs will have no difficulty in finding the required parts in their junk boxes: a small chassis, any convenient size; a pentode and socket; one or more crystals and sockets; two 50,000-ohm, ½-watt re-

sistors; three mica or ceramic condensers, .01 and .001 μfd., and .0001 μfd.; a 2.5 mhy. r.f. choke; and a toggle switch are all the parts required. A 2-circuit, 6-position selector switch may be added for extra crystals. A one-watt dropping resistor may be needed if the "B-plus" supply is much higher than 150 volts.


That's all it takes! The high voltage lead in the author's copy was brought to a 2-terminal tie point so that the terminals could either be jumpered, or an appropriate series resistor added, depending on the high-voltage source to be used. With the present high voltage source (a 275-volt supply that operates the monitor) a 30,000 ohm, 1 watt resistor is used to keep the voltage down to the minimum required to insure stable oscillation of the crystal.

It is easy to begin. First look over your crystals, the lower the frequency (Continued on page 133)

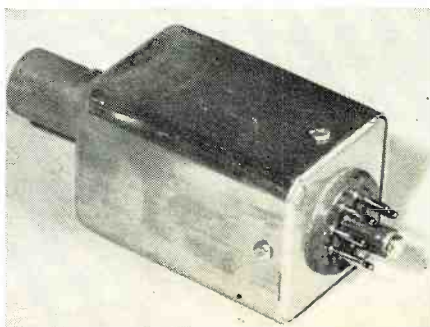A one-crystal version, using same circuit but eliminating selector switch, was built using a miniature tube and turret socket.



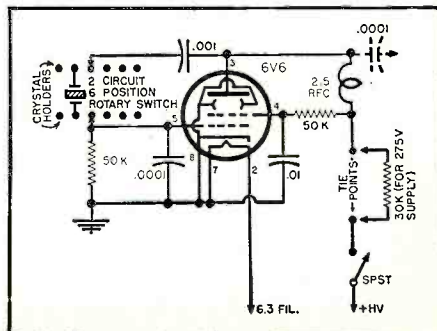Schematic of the low-cost calibrator. It will work with any common pentode, although 6V6 is shown. Receiver supplies the power.



HIGH-QUALITY RECORD REPRODUCTION

AT LOW COST

By FRANCIS H. YONKER

Electronics Lab., Pennsylvania State College

Construction data on a low-cost amplifier that will match variable reluctance, crystal, and Brush PL-20 type pickups.

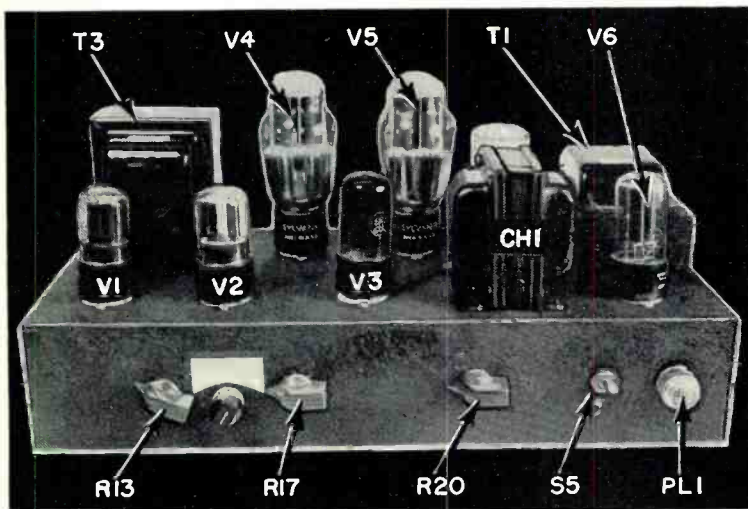


Fig. 1. Over-all view of the home-built amplifier which was especially designed to handle various type phono pickups.

THE components sold for use in today's new high-fidelity circuits cost so much that the average experimenter or music lover can't afford the parts to build the equipment he has read about or seen. The twenty-to thirty-dollar output transformers and the one-hundred-dollar loudspeakers shoo the builder right back to his old equipment.

Fig. 2 is the schematic diagram of an audio amplifier that will match the hi-fi enthusiast's phono pickup whether it be the magnetic reluctance, regular crystal, or the old favorite Brush PL-20, which the author uses for 33½ rpm broadcast transcriptions.

The magnetic pickup preamplifier consists of V_1 , the 6SL7 tube, and its component parts which form a circuit almost identical to the *General Electric* preamplifier. The required compensation for record equalization is built into this circuit but by varying the 6800 ohm input resistor to higher or lower values the frequency response will change.

The next input, "Crystal Pickup," is for those regular phono-arms found on the typical record player. By experimentation and curves obtained using the RCA constant tone record #84522-A, the equalizer consisting of a 5 megohm resistor and 67 μ fd. condenser was employed.

The final input, "Brush PL-20," was added because so many music lovers have proven in the past that this pickup and the 16-inch broadcast transcriptions equalized by the Brush filter cartridge, afford much enjoyment in the way of varied programs of radio broadcast recordings.

Each of these inputs is switched to the amplifier by the rotary switch S_1 - S_2 - S_3 . The first half of V_2 , 6SL7,

is necessary for amplification of inputs except for the reluctance pickup, whose preamplifier output is sufficient to drive the second half of V_2 directly via the tone control circuit. The treble control, 100,000 ohms, and bass control, 200,000 ohms, with their associated condensers, introduce considerable loss but the preamplifiers have sufficient gain to overcome this attenuation.

The second half of V_2 is an ordinary amplifier with negative feedback incorporated by omitting the cathode by-pass condenser.

V_3 , a 6N7, is a straight-through amplifier and phase inverter which also contains negative feedback of the same form described previously. The 6N7 tube characteristics allow a greater voltage swing output without distortion than other smaller tubes such as the 6SN7, and also allows operation on the more linear portion of its characteristic curve.

The push-pull output stage, consisting of two 6B4 tubes, gives that preferred triode low plate resistance with less distortion and smaller transformation ratio to the low loudspeaker impedance. The output transformer is a low-cost Thorndarson 25-watt T-22S70 unit. The transformer does not have a flat response curve up to 20,000 cycles but why care too much about its high-frequency efficiency when adjustment of the tone controls will allow greater signal input to the output transformer at the "fall off" frequency to make up for the transformer loss.

The beauty of this amplifier lies in the availability of bass and treble tone control. Reference to Fig. 3A shows the actual frequency response when the controls are set as indicated.

It's possible to make the recording sound like accentuation of high or low frequencies, complete loss of one or the other, or a combination near the middle range of controls allows a small adjustment to satisfy the individual ear. Any way, the next fellow to hear your "set-up" is going to like some other combination of tone controls. Pointer knobs and dial plates will aid in setting controls for exact reproduction of the many different phonograph record characteristics.


It's true one can make much more elaborate amplifiers with switch-equalizers for every type record on the market but since each individual likes music to suit his own taste, it can be adjusted by this tone-control combination to satisfy the conditions.

Switch S_4 is added for those who like to experiment with feedback voltage direct from the loudspeaker winding. The frequency response curves of Fig. 3A and 3B were obtained with this feedback switch in the "Off" position. By adjusting R_{21} throughout its range, where oscillation or motor-boating does not occur one will find much in the way of hi-fi entertainment by listening to the tone combinations that are produced.

The builder used a 25-watt, 12-inch speaker as a woofer and installed a separate 5-inch tweeter directly above it. The speaker combination was mounted in a bass reflex cabinet built to specifications given in "Data-Print 2" in the June 1952 issue of RADIO & TELEVISION NEWS.

EDITOR'S NOTE: In order to keep the cost of this unit low, the author has built a preamp, amplifier, and power supply on a single chassis. Where cost is no object, readers are referred to "The RADIO & TELEVISION NEWS Preamp" (Nov. 1952) and "Improving the Williamson Amplifier" (Feb. 1953) for circuits capable of excellent performance.

- R₁—6800 ohm, 1/2 w. res.
- R₂, R₈—3.3 megohm, 1/2 w. res.
- R₃, R₄—68,000 ohm, 1 w. res.
- R₅, R₆—33,000 ohm, 1 w. res.
- R₇—68,000 ohm, 1/2 w. res.
- R₉, R₁₁—180,000 ohm, 1/2 w. res.
- R₁₀—27,000 ohm, 1/2 w. res.
- R₁₂—5 megohm, 1/2 w. res.
- R₁₃—2 megohm pot. ("Volume Control")
- R₁₄, R₂₇—1500 ohm, 1 w. res.
- R₁₅, R₂₁—22,000 ohm, 1 w. res.
- R₁₆, R₂₂—56,000 ohm, 1 w. res.
- R₁₇—100,000 ohm pot. ("Tone Control")
- R₁₈—100,000 ohm, 1/2 w. res.
- R₁₉—4700 ohm, 1/2 w. res.
- R₂₀—200,000 ohm pot. ("Tone Control")
- R₂₃—1800 ohm, 1 w. res.
- R₂₄—270,000 ohm, 1/2 w. res.
- R₂₅, R₂₆—130,000 ohm, 1 w. res.
- R₂₈, R₃₀—240,000 ohm, 1/2 w. res.
- R₂₉—10,000 ohm, 1/2 w. res.
- R₃₁—50,000 ohm pot. ("Feedback Control")
- R₃₂—750 ohm, 10 w. wirewound res.
- C₁, C₃—.05 μfd., 400 v. cond.
- C₂, C₉—.2 μfd., 600 v. cond.
- C₄—.02 μfd., 400 v. cond.
- C₅—.01 μfd., 400 v. cond.
- C₆—67 μfd. ceramic cond.
- C₇—20 μfd., 25 v. elec. cond. (used only if feedback is eliminated)
- C₈, C₁₀, C₁₂, C₁₃, C₁₄, C₁₅, C₁₆—.06 μfd., 600 v. cond.
- C₁₁—124 μfd. ceramic cond.
- C₁₇—.25 μfd., 400 v. paper cond.
- C₁₈, C₁₉—40 μfd., 450 v. elec. cond.
- C₂₀—30 μfd., 150 v. elec. cond.
- T₁—Power trans. 350-0-350 v. @ 200 ma.; 5 v. @ 3 amps.; 6.3 v. c.t. @ 6 amps. (Thordarson T-22R07 or equiv.)

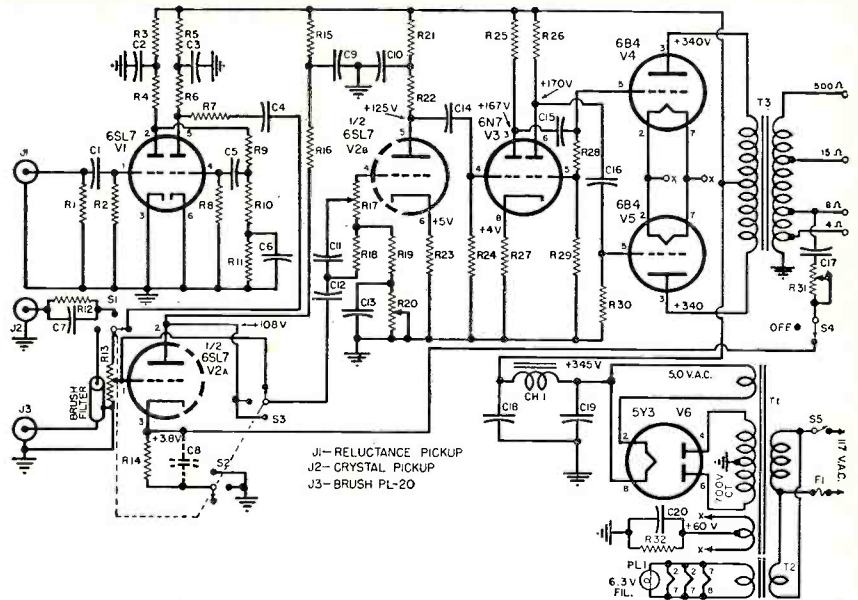

- T₂—Fil. trans. 6.3 v. c.t. @ 3 amps. (Thordarson T-21F10 or equiv.) Ground one side of secondary.
- T₃—Output trans. 5000 ohms plate-to-plate (Thordarson T-22S70 or equiv.)
- CH₁—12 hy., 100 ma. filter choke (Thordarson T-20C53 or equiv.)
- F₁—Line fuse
- S₁-S₂-S₃—3-pole, 3-pos. rotary wafer switch
- S₄—S.p.d.t. switch ("Feedback")
- S₅—S.p.s.t. switch ("Power")
- PL₁—6.3 v. pilot lamp
- I—Brush filter unit (for Brush PL-20 pickup)
- J₁, J₂, J₃—Closed circuit phono jack
- V₁, V₂—6SL7 tube
- V₃—6N7 tube
- V₄, V₅—6B4 tube
- V₆—5Y3 tube

Fig. 2. Circuit diagram and parts list covering a low-cost audio amplifier which uses standard, easily-available components.



Fig. 3. (A) Amplifier response with various positions of tone controls. Note particularly that where "maximum" and "minimum" is shown reference is made to the physical position of tone controls and not to response. In operation there is an interaction between bass and treble circuits. (B) Over-all amplifier response with tone control circuit out. Input is at the crystal phono jack. Power output is 9.3 watts.


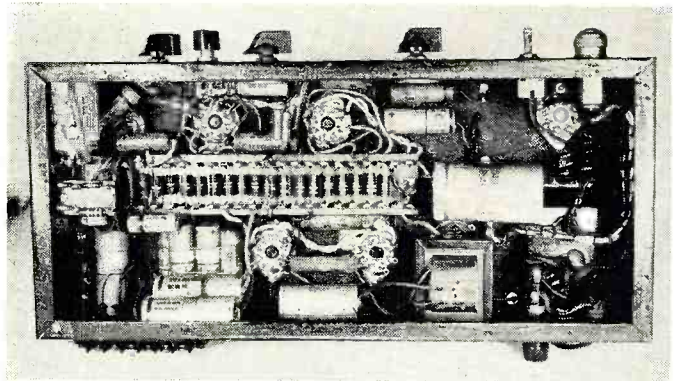
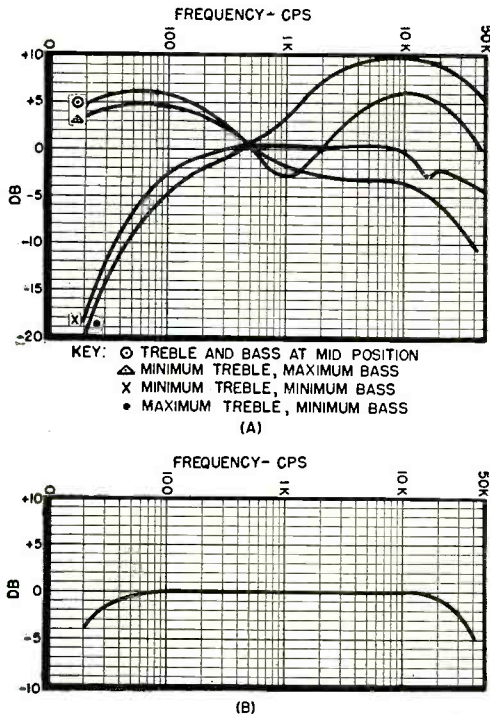



Fig. 4. Under chassis view shows terminal-board construction of unit.

Fig. 5. Side view of amplifier showing location of phono pickup jacks.

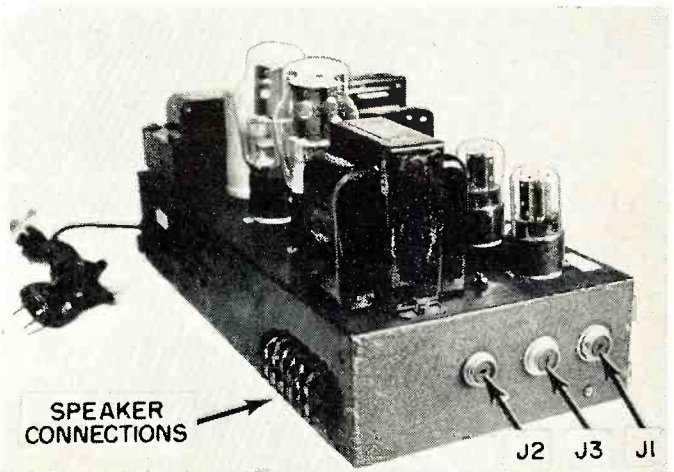

Mac's RADIO SERVICE SHOP

By JOHN T. FRYE

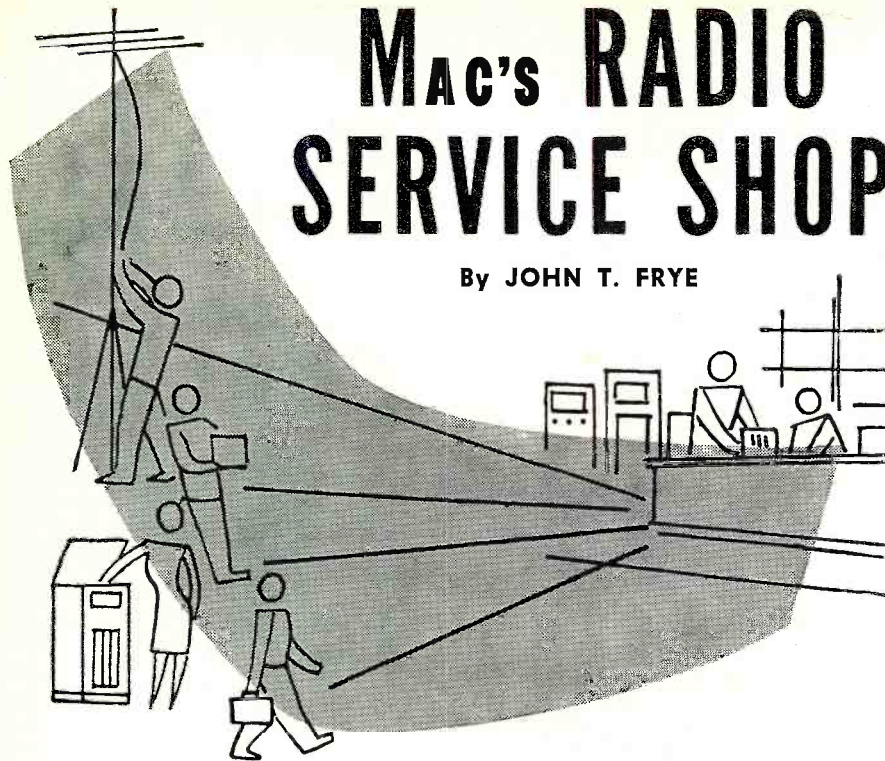

THE FIELD STRENGTH METER

THAT DOES IT!" Barney suddenly snapped as he threw down the tools he had been using in an attempt to adjust the linearity of a TV set. "I'm going to find what's causing that interference or know the reason why!"

Mac, his boss, cocked a sympathetic eye at the face of the picture tube. The test pattern on it was moving steadily downward. By adjusting the vertical hold control the boy could make the picture frame correctly for a few seconds at a time, and then a dark, inch-wide band of interference could be seen moving slowly from the bottom to the top of the pattern. When this line reached the top, however, it replaced the blanking bar there, and then the picture started sliding down again.

"It'll be a good trick—if you can do it," Mac commented skeptically. "That thing has been hanging around for two days now."

"Just watch Uncle Barney; he's got it all planned," the youth boasted.

He was already connecting a hot-shot battery to the inverter normally used in the service truck to supply small amounts of 117 volt a.c. from the car battery when needed. This combination went into a knapsack on his back. The leather shoulder strap of the shop's *Simpson* field strength meter was plugged into the inverter, and a folded dipole fashioned from twin-lead and supported on a T-frame made of plaster lath was connected to the meter's 300-ohm binding posts. A pair of phones on the boy's head was plugged into the jack of the field strength meter.

He switched on the instrument, carefully manipulated its fine-tuning control, and swished the probe antenna about as he listened intently.

"Contact!" he shouted triumphantly. "I can hear it fine, and it reads thirty microvolts on the meter. Open the back door and let old bring-em-back-alive-Barney out. If you don't hear from me in a couple of days you'd better send out a search party."

"I'll not wait that long," Mac shouted back so Barney could hear him with the phones on. "Neither your legs nor that hot-shot battery will last very long with the load they are carrying."

Barney sallied forth into the alley and Mac, still chuckling at the ludicrous figure his assistant made with all the paraphernalia, went back to the bench and picked up what Barney termed "Mac's idea of a thrilling whodunit book." It was Milton Kiver's "TV Servicing Shortcuts" and really was as fascinating to Mac as any collection of detective stories; for it was not made up of just rare service problems but was composed of actual cases encountered in routine servicing of a wide variety of sets. He became so engrossed in reading about the symptoms and then trying to guess the trouble before reading ahead to see if he was right or wrong that he did not note the passage of time. When he did look up it was to see the test pattern standing perfectly still with no sign of interference. At the same time there was a lusty kicking at the back door to indicate the interference sleuth had returned.

"Mission accomplished!" Barney announced triumphantly as soon as Mac opened the door. He lumbered inside

and waved an old-fashioned sharp-pointed light globe under Mac's nose. "I just watched the meter and kept moving toward where the antenna's directional pattern and the changing meter reading pointed, and I walked right up to this relic in a socket over a loading platform down the alley. When I told the store owner about it and offered to buy him a new bulb for this one, he said I was welcome to it for it had been fouling up a TV set in the store for a couple of days, too. Said he couldn't imagine where the maintenance man ever found the thing in the first place. Anyway, it puts out a mean 5000 microvolts on Channel 6 when you put the antenna right up against it."

"Anyone comment on your appearance?" Mac asked with a grin as he helped Barney out of his rigging.

"No, but a gang of little boys gave me a hard time. They called me 'Flash' and kept wanting to hear me talk to my space ship. Finally I had to tell them that if they didn't scam I was going to melt them down with my atomic disintegrator pistol."

"Guess we've got to rack up another victory for the good old field strength meter," Mac commented as he fondly patted the gray enamel case of the instrument. "This thing has more uses than a piece of twine."

"Yet quite a few technicians try to get along without one," Barney pointed out. "They argue that all a field strength meter is good for is to tell if a signal is coming down the feed line and to help point the antenna at the station when you install it. They say they can tell all this just by watching the set itself."

"Then they've got a better eye than I have. We found out from experience with the meter that as soon as you get past 200 microvolts of signal it takes a tremendous increase to show much effect on the picture. The a.g.c. circuit does its best to hold the signal delivered to the picture tube at the same value no matter how the signal at the antenna terminals changes. If you line up an antenna with just a picture for an indicator, you get the impression the main receiving lobe is much, much wider than it really is. With the meter, since it responds to the slightest change in signal strength, you can point the antenna right on the button. However, I'll not argue a signal strength meter will do a lot of jobs that cannot be done by any other means; I'm simply convinced it does these jobs quicker, easier, and more accurately."


"Know what you mean," Barney agreed. "When I run up against a set with a normal raster but with weak picture and sound or none at all, my first move is to hook the field strength meter to the antenna. If a good signal is coming in, I know I can concentrate on the set; if not, I know I'm in for some roof scampering. A funny thing, too, is how much that meter impresses the average customer." (Continued on page 124)

RADIO & TELEVISION NEWS

ELECTRONICS FOR THE YACHTSMAN

By **HARRY R. ASHLEY**

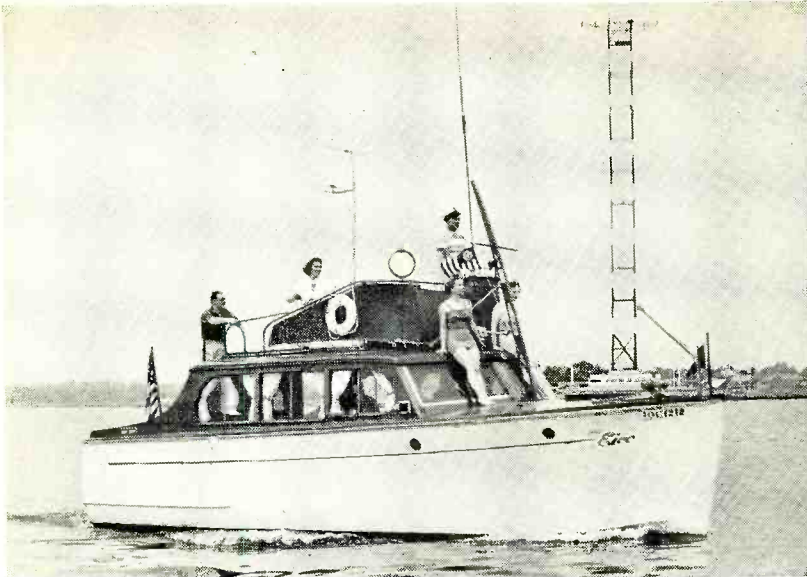Pres., Electronic Instrument Co., Inc. (Eico)



Over-all view of the motor yacht "Miss Eico" showing radio and TV antennas and direction finder loop. Station WCBS' transmitting tower at New Rochelle, N. Y. may be seen at right rear.

*Add to the pleasure and safety of your cruises
by using modern marine electronic equipment.*

THE longing which prompted Masfield to declaim "I must go down to the sea again", has obviously gripped large segments of the American populace as literally thousands are joining the ranks of small boat owners each year. Whether the "sea" is the Atlantic Ocean, Lake Michigan, or some quiet inland lake or riverway, the lure is proving irresistible to many a weekday "landlubber".


The questions foremost in the minds of the average present or prospective boat owners are what electronic equipment should I have and what will it cost? Since the War, many marine electronic items have been made available to the small boat owner through simplification, miniaturization, and price reduction. Today even the most modestly priced bottom can boast of a radio receiver capable of tuning the marine bands. From such minimal equipment the electronic gear a boat may carry will range all the way up to an elaborate installation worthy of an ocean-going liner.

Should the boat be a small one which is to be operated exclusively in charted channels or within sight of land, electronic equipment is not essential. Any gear which is installed, however, adds to the operating convenience of the craft but falls more or less into the "luxury" category.

For craft operating in open waters out of sight of land, a two-way radiotelephone is virtually a "must" for the safety of those aboard. Radiotelephone can be readily used from any near-shore location and, should an emergency arise, the Coast Guard can be summoned. This same equipment may be used for ship-to-ship contacts for the friendly exchange of information ranging all the way from navigational tips to the latest dope on where the fish are running. Because of the shared enthusiasm for boating, many friendships have been formed as a result of such informal ship-to-ship radio contacts—reminiscent of the friendships begun on the ham bands.

If you are a good seaman, one that can navigate with confidence by compass alone, perhaps you will not require the second piece of "must" equipment for the deep-water sailor. If, however, you are dubious about your seamanship or will be navigating in totally unfamiliar waters, a radio direction finder is a handy item to have aboard. Needless to say when the fog rolls in the direction finder becomes the yachtsman's "best friend".


(Continued on page 108)

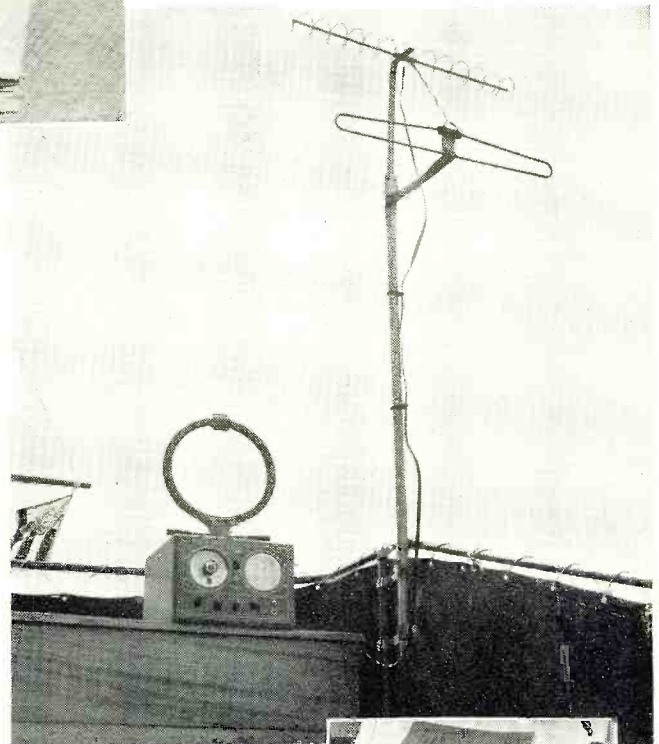

The Bludworth Marine direction finder which covers beacon, broadcast, and marine bands for widest protection and surest results.


Bendix recording depth finder aboard the "Miss Eico."

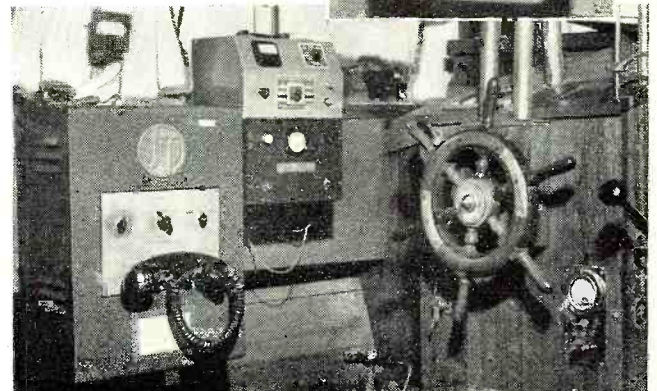Jefferson Travis radiotelephone, Surrette battery charger, Eico battery eliminator and charger, transmitter output meter, and the charge indicator (on panel).





International SHORT-WAVE

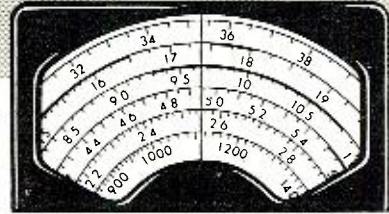

Compiled by KENNETH R. BOORD

THE Japanese Standard Frequency Station, JJY, can be heard on 4.000 (error: 5×10^{-8}) daily 1900-0900 and on 8.000 (error: 5×10^{-8}) at 1600-0600; QSL's by card; QRA is Radio Regulatory Commission, Standard Frequency Section, Engineering and Monitoring Division, Minato-ku, Aoyama, Tokyo, Japan. (Ishikawa, Takemi, Japan)

This Month's Schedules

Albania—Radio Tirana now operates on *announced* 6.570, 7.853 with *English* 1415, *French* 1330, *German* 1400, *Italian* 1315, 1500. (WRH)

Anglo-Egyptian Sudan—Radio Omdurman noted near 7.655 at 1330 with call, then talk or news in Arabic, followed by Arabic music. (Pearce, England)

Angola—Luanda, 9.472A, noted with music 1505; Portuguese announcements; weak to fair. (Cox, Dela.)

Argentina—LRYL, 9.760, Buenos Aires, noted mixing with TGWA, Guatemala, around 2350. (Cox, Dela.) Strong in Tokyo around 0600. (Ishikawa) **Radio El Mundo**, 6.120, heard 2000-2030, fair level; all-Spanish. (Borne, Sweden) **LRA**, 15.345, noted with news to North America 1815, strong. (Zerosh, Pa.)

Australia—Radio Australia has been moving around in its 0700-0845 beam to Eastern North America, due to QRM; by this time may be using 11.840 or may have moved to the 31-m. band (try 9.540 or 9.615). Dexter, Iowa, notes VLA15, 15.200, very good around 2200.

Bolivia—CP38, 9.497, La Paz, noted opening 2030 at good level. (Ferguson, N. C.) Heard opening 1756 with "Onward, Christian Soldiers." (Pearce, England)

Borneo (USI)—The Home Service of Radio Republic Indonesia is heard on 5.030 from Bandjermasin, with 1 kw., until 1030 closedown. (Japanese Short-Wave Club)

Brazil—Radio Relogio Federal, 4.905, Rio de Janeiro, noted 1730 relaying "A Voz do Brasil." (de Mesquita e Sousa, Portugal) **ZYK2**, 15.145, Recife, noted in Sweden 0930-1010 with **QRK4** signal. (Borne) **Radio Tamoio**, **ZYC8**, 9.610, good level 1915-1930. (Oestreich, Wash. State)

British Honduras—Radio Belize, 4.950, noted with news 1800; identifying 2130, followed by commercials, then light music; has trouble with **Radio Dakar**, Fr. West Africa, prior to 1800. (Cox, Dela.)

British New Guinea—VLT6, 6.130, now used *exclusively* by Port Moresby, noted 0600 with ABC news relay. (Ferguson, N. C., others)

Bulgaria—Radio Sofia, 9.700, lately has had *English* 1800-1815. (Zerosh, Pa., others) Now has news for Europe 1500 and 1615 on 6.070, 7.671A. (Pearce, England)

Cape Verde Islands—Praia, 5.890A, noted daily 1530-1700. (de Mesquita e Sousa, Portugal)

Ceylon—Commercial Service, 15.120, noted opening 2030; BBC news relay 2100. (Ferguson, N. C., others) Good on 11.975 at 0830. (Riggs, Calif.) Noted parallel on 9.520 at 1000-1230 closedown. (Gay, Calif.)

Chile—CE766, Radio Yungay, Santiago, noted on 7.660 fair level 1550 with music. (Cox, Dela.) Schedule is 0630-0130. (WRH) **Radio Sociedad Nacional de Minería** has been varying lately around 11.945-11.957; noted to around 2200. (Stark, Texas) Schedule is 0630-2300 and outlets are listed CE622, 6.220, 5 kw., and CE1198, 11.985, 2.5 kw. (WRH)

Colombia—A new station of Radio Cadena Nacional has been heard on *announced* 4.935 signing off between 2230-2300; **HJFV, Radio Neiva**, 4.855, is now on the air until 2300 weekdays, to after 0100 Sun. (Radio Sweden) **HJFK**, 6.098, Pereira, fair level 2010; slight QRM. (Norman, N. C.)

Costa Rica—TIHV, San Jose, is a new station heard on 6.008A; announces "Radio Cristal;" strong after 2230 when is in clear; suffers QRM earlier from **HJCH**, 6.009, and **CJCX**, Rome, and **YSS** on 6.010. (Robbins, Ind.)

Cuba—COCQ, Havana, is now using 9.675 on an irregular schedule (moved from 8.825). (Robbins, Ind.)

Cyprus—Sharq-al-Adna sent schedule of 2225-0130 daily, 0130-0330 Fri. and Sun., 0330-1500 daily on 635 kc., 6.120, 6.170, 6.790, 9.650, 11.720. (Scheiner, N. J.)

Czechoslovakia—Prague, 9.95, heard with *English* to North America 2300-2330A. (Hyson, Md., others)

Denmark—OZF, 9.52, Copenhagen, noted with improved signal in North

American beams 2030-2130, 2200-2300. (Jim Smith, Mich.; Saylor, Va., others)

Dominican Republic—HI2A, Santiago de los Caballeros, has moved from 9.680 to 4.840; signal peaks in Ind. around 2000, then fades to a lower level and mixes badly with **YVOX**, Venezuela, same channel. (Robbins)

Dutch New Guinea—Radio New Guinea soon is to be returned to Biak from Hollandia; will have a new studio, a 5 kw. transmitter. (NNRC, others)

Ecuador—Summer schedule of HCJB, Quito, includes *English* to North America 2100-2400, 9.745, 11.915, 15.115, and 2300-2400 also on 6.05; *English* to North and South America 0630-0730 on 9.745, 11.915; *English* to Europe 1600-1700, 17.89, 15.115, 11.915, and 1700-1730, 17.89, 15.115; *English* to Pacific 0130-0500 on 15.115, 11.915, 9.745; *off the air Mon.* (Matherly, Ohio)

Egypt—Current schedule of Cairo, 11.815, is 1320-1600 (Sat., Sun. to 1700); news 1330. (Bellington, N. Y., others) Noted on 9.750 lately as early as 1035 with call in Arabic. (Pearce, England) Heard on this channel 2345 with Arabic Service in news and Western music. (Sanderson, Australia, and others.)

Ethiopia—Radio Addis Ababa, 15-040A, noted 1330 in *English*. (Mast, N. Y.)

Fiji—Some months ago, the Posts and Telegraphs Department experimented on 6.100 parallel with regular 5.995 at Suva; latter has ABC news relay 0400; operates around 0030-0500. (Cushen, N. Z., others) More recently has *tested* on 3.980. (Radio Australia)

Finland—Helsinki, 15.19, noted in *English* around 1430-1440. (Golden, Mass., others)

France—Paris noted opening in French on 15.24 at 0730, excellent level. (Golden, Mass.) Heard parallel on 9.55, 6.200 at 1745 tune-in with *Paris-Inter* session in French. (Bellington, N. Y.) The *English Service* to Great Britain now is daily 0145 on 7.240, French Lesson; daily 1345 on 11.970, French Lesson; daily 1500-1600 on 6.050 with varied programs; answers to listeners' letters Wed., Sun. (Catch, England) Noted in French 1830-2000 on 9.680, 11.700. (Dexter, Iowa)

French Equatorial Africa—Brazzaville, 9.44, 11.970, noted with news (Continued on page 86)

(Note: Unless otherwise indicated, all time is expressed in American EST; add 5 hours for GCT. "News" refers to newscasts in the English language. In order to avoid confusion, the 24 hour clock has been used in designating the times of broadcasts. The hours from midnight until noon are shown as 0000 to 1200 while from 1 p.m. to midnight are shown as 1300 to 2400.) The symbol "w." following a listed frequency indicates "varying." The station may operate either above or below the frequency given. "A" means frequency is approximate.

TAKE YOUR PICK

EITHER OF THESE VALUABLE SERVICING ITEMS...YOURS AT NO EXTRA COST...with purchases of Federal Picture Tubes!

1

THIS TOOL and TUBE CADDY or...



CADDY FACTS: An attractive convenience — for tools and tubes — you'll be proud to carry on all service calls.

Sturdy wood construction . . . covered with simulated alligator leather (blue). Over-all size: 18 3/4 inches long, 13 1/4 inches high, 9 inches wide.

Brass-finished lach, hinges, catches and corner guards. Compartments hold approximately 75 receiving tubes of various sizes. Opens into three separate, easily-accessible sections. \$9.50 value! (A \$14.95 list value).

2

THIS 135-WATT WELLER SOLDERING GUN



GUN FACTS: Weller Model WD-135 (135 watts). Ideal for all types of soldering and dozens of household jobs. Instant heating. Dual heat increases tip life. High or low heat as desired. Exclusive tip-fastening feature — full, constant heat. Low-cost, replaceable tips. Pre-focused spotlight. Longer reach — perfect balance. Shatter-proof plastic housing. \$10.95 value! (A \$14.90 list value).

We want you to know the Quality, Long-Life Performance and Replacement Profits in

Federal PICTURE TUBES



How to get your choice —

With every purchase of a Federal "Best-in-Sight" Picture Tube, your participating Federal Distributor gives you one Federal Certificate. There are no restrictions on type of tube. You may buy one tube at a time, or as many as you need.

As soon as you have accumulated 10 certificates, deliver them to the distributor from whom you purchased your Federal Picture Tubes and he will exchange them for the Combination Tool and Tube Servicing Caddy OR the Weller Soldering Gun. (If you wish, both Caddy and Soldering Gun will be given in exchange for 20 Federal Certificates.)



See your Federal DISTRIBUTOR For Federal Tubes and Certificates!

This offer is void wherever prohibited or wherever any tax, license or other restriction is imposed.

(This offer expires August 31, 1953)

TV SET MANUFACTURER TEST SHOWS OVER

99% HIT THE BULL'S-EYE FOR QUALITY!

Here's proof that it pays to replace with Federal. Here's assurance of customer satisfaction . . . of less time wasted on call-backs . . . of more dollars of profit.

Join the trend to Federal "Best-in-Sight" Picture Tubes . . . outstanding for *quality*, because they are made by a world leader in broadcast tubes.

Federal's line of popular-size tubes will take care of over 90% of all TV replacements!



Start Ordering Federal Picture Tubes — Start Saving Federal Certificates!

Federal Telephone and Radio Corporation

VACUUM TUBE DIVISION • 100 KINGSLAND ROAD, CLIFTON, N. J.

In Canada: Federal Electric Manufacturing Company Ltd., Montreal, P. Q.
Export Distributors: International Standard Electric Corp., 67 Broad St., N. Y.

BARGAINS · BARGAINS · BARGAINS

BARGAINS · BARGAINS · BARGAINS

Famous
STEVE-EL
BRANDED

TUBES

All Brand New
Individually Boxed
FAR BELOW WHOLESALE COST!

1A7	\$.59	6AT6	.37	6SA7	.52	12AT6	.48	25L6	.48
1B3	.63	6AX4	.52	6SC7	.49	12A7	.68	25Z6	.42
1P5	.54	6BB8	.52	6SK7	.49	12AU6	.48	35C5	.47
1R5	.56	6BA6	.45	6SL7	.52	12AU7	.56	35L6	.48
1S5	.48	6BC5	.58	6SN7	.54	12AV6	.52	35W4	.37
1U4	.48	6BC7	.86	6SQ7	.42	12AX7	.94	35Z5	.33
1U5	.48	6BE6	.48	6SR7	.44	12AZ7	.74	50B5	.48
1X2	.63	6BG6	1.21	6T8	.74	12BA6	.46	50L6	.47
3V4	.47	6BH6	.53	6U8	.78	12BA7	.59	50P5	.48
5U4	.47	6BJ6	.53	6V8	.46	12BE6	.46	117Z3	.36
5W4	.46	6BN6	.74	6V6GT	.46	12SA7	.52		
6A7	.51	6C4	.48	6V8	.83	12SK7	.49		
6A8	.62	6CB6	.48	6W4	.45	12SL7	.57		
6A95	.62	6CD6	1.21	6W6	.52	12SR7	.54		
6AK5	1.14	6F6	.49	6X4	.34	12SQ7	.42		
6AL5	.41	6J5	.37	6X5	.37	14AF7	.59		
6AU6	.43	6J6	.79	6U5	.42	14N7	.64		
6AV6	.37	6K6	.41	7N7	.52	19T8	.78		
6AS5	.49	6L6G	.89	7X7	.62	25BQ6	.77		
6AQ5	.39	6S4	.44	12A6	.48	25W4	.48		

Technical BOOKS

"RADIOTRON DESIGNER'S HANDBOOK" edited by F. Langford-Smith. Reproduced and distributed by the RCA Victor Division of Radio Corporation of America. 1423 pages. Price \$7.00. Fourth Edition.

Those who are familiar with the earlier editions of this handbook will be both surprised and pleased by the encyclopedic proportions it has assumed in this newest and most complete version.

This well-known "bible" of the industry is four times larger than the Third Edition published in 1940, reflecting the great strides made by the electronics industry in the past decade or so.

The text material is prepared with the engineer, student, and experimenter in mind and covers thoroughly the design of radio and audio circuits and equipment. The information on circuit design and application is presented not only mathematically but practically so that those with limited engineering experience can profit from the exposition. For the engineer who wants to know "why" and "how" such circuits function—that information is also provided.

The book itself is divided into seven major sections and covers such topics as radio tubes; general theory and components; audio frequencies; radio frequencies; rectification, regulation, filtering, and hum; complete receivers; and an impressive array of tables, graphs, charts, bibliographies, references, etc.

For a compact and ready-reference source of a veritable gold mine of pertinent information, this book will be hard to beat.

* * *

"TV MANUFACTURERS' RECEIVER TROUBLE CURES" edited by Milton S. Snitzer, Published by John F. Rider Publisher, Inc., New York. 113 pages. Price \$1.80. Paper bound. Volume 3.

This is the third in the current Rider series covering troubleshooting procedures as developed by the set manufacturers themselves.

Service notes for receivers manufactured by Kaye-Halbert, Kent, Magnavox, Majestic, Meck, Mercury, Midwest, Montgomery Ward, Motorola, Muntz, National, North American Philips, Olympic, Pacific Mercury, Packard-Bell, and Philco have been included in this volume.

The book is completely indexed by model numbers to permit the rapid location of the desired data. Subsequent volumes will cover receivers of other companies.

* * *

"TV SWEEP ALIGNMENT TECHNIQUES" by Art Liebscher. Published by John F. Rider Publisher, Inc., New York. 120 pages. Price \$2.10. Paper bound.

INTERCOM SPECIAL



Now you can own an intercom that has a thousand uses at a price you would normally pay for a kit. This intercom comes housed in wooden cabinets completely wired and ready to operate. Outfit consists of one master, one substation and fifty feet of two-wire cable. Ideal for home as baby sitter. Perfect for office or factory. Order now as quantities are limited.

YOUR COST COMPLETE only.....\$15.95
Minimum order \$5.00

Another NEW
STEVE-EL STORE!

166 Washington Street, New York City
Come in and get acquainted.

STEVE-EL ELECTRONICS CORP.

Dept. N-8 61 Reade St., New York 7, N. Y. COrtland 7-0086

630 CHASSIS



Latest model. Complete with all tubes, Cascode tuner and 12" speaker. Less C. R. T. and mounting brackets.

\$146⁵⁰

G. I. RECORD CHANGERS


Special while they last. Single \$10.95
Speed 78 rpm.....\$10.95

3 Speed 78, 45, 33 rpm single needle.....\$16.99

3 Speed with twist cartridge.....\$18.99

Minimum order \$5.00

SAVE MONEY ON INSTRUMENTS!

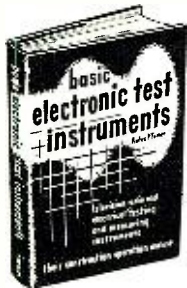

How to test with fewer instruments . . .

How to use old instruments in new ways . . .

How to select the instruments you need . . .

How to evaluate instrument readings and put them to practical use.

BASIC ELECTRONIC TEST INSTRUMENTS

by Rufus P. Turner
254 pages, 171 illus. Price \$4.00

Written especially for servicemen, amateurs and experimenters, this new book is a complete training course in instruments. Over 60 instruments—from the most modern TV pattern generators to grid-dip oscillators and special-purpose bridges—are fully explained. Work-saving short cuts are outlined. You learn how to put your old instruments to new uses and thus avoid buying costly new ones. Tells all about current & voltage meters; ohmmeters and V-O-M's; V-T voltmeters; power meters; oscilloscopes; r-f test oscillators; signal tracers; tube testers; TV linearity pattern generators and dozens more.

READ IT 10 DAYS . . . at Our Risk

Dept. RN-83, Rinehart Books, Inc.,
Technical Division,
232 Madison Ave., New York 16, N. Y.

Send Turner's BASIC ELECTRONIC TEST INSTRUMENTS for 10-day examination. If I decide to keep book, I will then remit \$4.00 plus postage in full payment. Otherwise, I will return book postpaid and owe you nothing.

Name

Address

City, Zone, State.....

The NEW JSC Tubular Twin Lead...



The best low loss, low cost 300 ohm lead-in for UHF and VHF television.


Rain, snow, dirt or salt deposits do not materially affect impedance and electrical efficiency.

JSC tubular construction contains and protects the concentrated field of energy and reduces to a minimum high ratio signal losses.



Manufactured under
license of Amphenol
Pat. 2543696

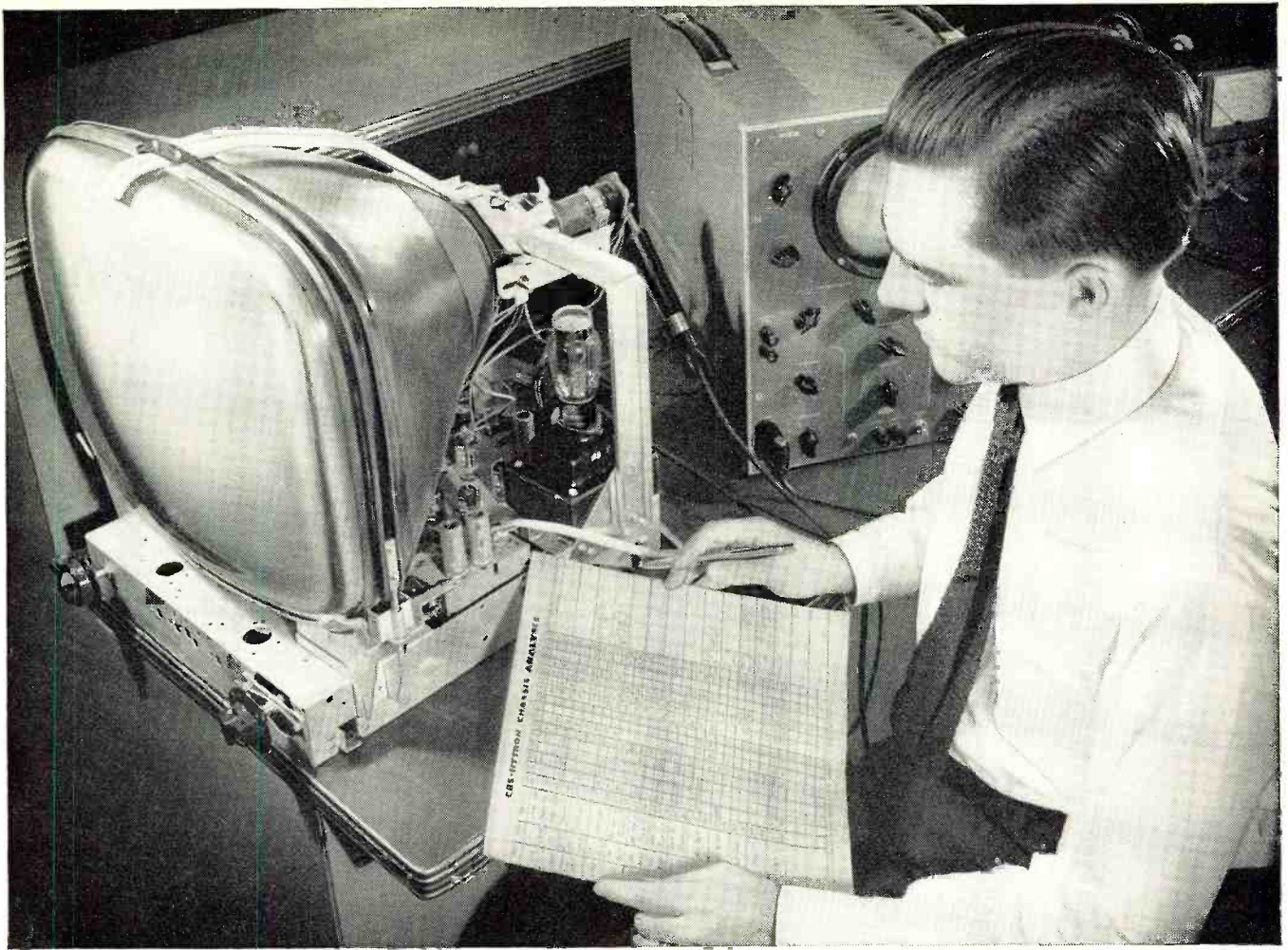Always Look for the Orange and Blue Disc of Quality



Bring back that New-Set Sparkle with **Performance-Tested Tubes**


Meet John Cunningham, a CBS-Hytron Commercial Engineer. John is beginning at the beginning for you. Socket by socket, he is analyzing the tube requirements of a brand-new TV set design.

John knows the superior performance demanded. He concentrates his know-how on insuring top tube operation within standard specification limits. He tests sample tubes . . . checks analysis data. Working hand-in-glove with the set designer . . . and with CBS-Hytron engineers . . . he assures control of the characteristics of all tubes for this new chassis. Finally he achieves . . . from rectifiers to picture tube . . . the perfect performance all of this engineering team (and you) seek.

Constantly CBS-Hytron carries on teamwork like this. Socket by socket analysis. Day in, day out — with 9 out of 10

leading TV set makers. Both tube and set engineers pool their specialized skills. Scores of the nation's foremost TV set engineers help make endless CBS-Hytron improvements. Help assure you of unsurpassed performance in virtually *all* leading TV sets.

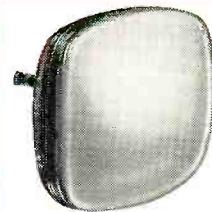Small wonder that your CBS-Hytron replacement tubes recapture that new-set sparkle. Please *your* customers. Cut *your* call-backs. Profit more. Take advantage of CBS-Hytron engineering. Demand CBS-Hytron . . . your logical replacement tube, because it is performance-tested all the way . . . from original to replacement.



Now
**CBS-
HYTRON**
MIRROR-BACK

ALUMINIZED PICTURE TUBES
27EP4 and 24TP4 . . . both
mirror-backed, spherical, elec-
tromagnetic types.

Leading TV set makers demanded maximum brightness from their large-screen sets. Without strain on component parts. For them, CBS-Hytron introduced its *Mirror-Back* picture tubes. Mirror-like effect of their aluminumized backing steps up light output. Adds sparkling brilliance to the picture. Gives greater contrast and freedom from screen discoloration. You, too, will want CBS-Hytron *Mirror-Back* tubes for replacement. Because your customers can *see* them recapture that bright, new-set sparkle. Order the performance-tested 27EP4 and 24TP4 from your CBS-Hytron distributor.



CBS-HYTRON Main Office: Danvers, Mass.

A Division of Columbia Broadcasting System, Inc.

Manufacturers of
Receiving Tubes Since 1921

RECEIVING . . . TRANSMITTING . . . SPECIAL-PURPOSE AND TV PICTURE TUBES • GERMANIUM DIODES AND TRANSISTORS

August, 1953

71

BECOME AN ELECTRICAL ENGINEER



**Bachelor of Science Degree
in 36 months.**

Major in Electronics or Power.
Now, prepare for a career in
these rapidly expanding fields.

This school will prepare you to become an engineer, technician or service man. Previous military, academic or practical training may be evaluated for advanced credit.

Enter Both Radio and Television

In 12 months you can attain the *Radio-Technician's* certificate. An added 6 months course qualifies you for the *Radio-TV Technician's* certificate and the Degree of "Associate in Applied Science." The Technician's course is the first third of the program leading to a Bachelor of Science Degree in Electrical Engineering with a major in Electronics.

Also offered: 12-month Radio-TV service course; 12-month Electronics or Electro Technician Courses; 6-month Electrical Service Course and 3-month refresher and general preparatory classes.

Terms Open April, July, Oct., Jan.

Famous for its Concentric Curriculum. Faculty of specialists. 50,000 former students. Annual enrolment from 48 states and 23 overseas countries. *Non-profit. 50th year.* Courses approved for Veterans. Resident courses only.



MILWAUKEE SCHOOL OF ENGINEERING

MILWAUKEE SCHOOL OF ENGINEERING
Dept RA853, 1025 N. Milwaukee
Milwaukee 1, Wisconsin

Send: Free 45-page "Your Career" booklet;
 Booklet on Careers in Radio-TV.

I am interested in.....
name of course

Name.....Age.....

Address.....

City.....Zone.....State.....

If veteran, indicate date of discharge.....

This is a practical handbook for the television technician which is characterized by the common-sense approach which marks all of Mr. Liebscher's writings.

The book is divided into eleven main chapters and includes discussions of modern sweep alignment, sweep alignment techniques, markers, "supermark," sweep curves, tuner curve formation, i.f. alignment, i.f. curve adjustment, sound i.f. and sound detector alignment, video amplifier response testing, and u.h.f. sweep alignment.

The text material is lavishly illustrated with oscilloscope patterns showing the various circuit conditions encountered in television service work.

Both the practicing service technician and the student will find this little book a worthwhile adjunct to the servicing library.

* * *

**"UHF ANTENNAS, CONVERTERS,
AND TUNERS"** by Milton S. Kiver,
Published by *Howard W. Sams & Co.,
Inc.*, Indianapolis, Ind. 134 pages.
Price \$1.50. Paper bound.

As more and more television stations take to the air in the u.h.f. band, more and more service technicians are encountering problems heretofore unheard of in their experience.

To cope with these new and unfamiliar problems, Mr. Kiver has written this down-to-earth book to answer just such questions. The book is divided into five sections and deals in detail with such subjects as u.h.f. antennas, transmission lines and match-

ing networks, u.h.f. installation practices, u.h.f. converters, and u.h.f. tuners.

The material presented is specific and to the point. Similarities and differences between v.h.f. and u.h.f. systems are pointed out where such comparisons serve to advance an understanding of circuit operation. Photographs, drawings, graphs, and sketches have been used lavishly to amplify the text material.

Mr. Kiver's style is familiar to all readers of this magazine so it will come as no surprise to them to hear that this book is in the same concise, clear-cut form as his articles, and should provide the technician with a lot of much-needed and authentic data on u.h.f.


-30-

AMATEUR EXTRA CLASS

FCC has announced that radio "old-timers" applying for the Extra Class amateur radio license may submit, for waiver of some of the requirements, a "Certificate of Skill" issued by the old Department of Commerce and Labor before June 30, 1913. Heretofore it has been necessary for an applicant seeking a waiver to show evidence of possession of an actual amateur license before April, 1917. It is necessary, when submitting a "Certificate of Skill" for this purpose, to supply evidence of either ownership or operation of an actual amateur station before June 30, 1913. Details are in the Commission's Safety and Special Radio Services Bureau Bulletin No. 2, available from FCC, Washington 25, D. C.

-30-


Stromberg-Carlson Company's Sound Division at Rochester, N. Y. has placed in operation a new 2½ ton magnetizing unit on its loudspeaker assembly line. The new electromagnet was designed especially for magnetizing the 10½ pound piece of Alnico V that serves as the permanent magnet in the company's 15 inch high-fidelity speakers. The magnetizing unit consists of a steel yoke, supporting the two pole pieces, each one foot in diameter. Each of the pole pieces is wound with three coils. There are approximately 700 pounds of copper in the coils. The complete assembly weighs slightly over 5000 pounds. The photoelectric cell which controls the magnetizer is activated by the loudspeaker passing through the light beam on the slowly moving belt.

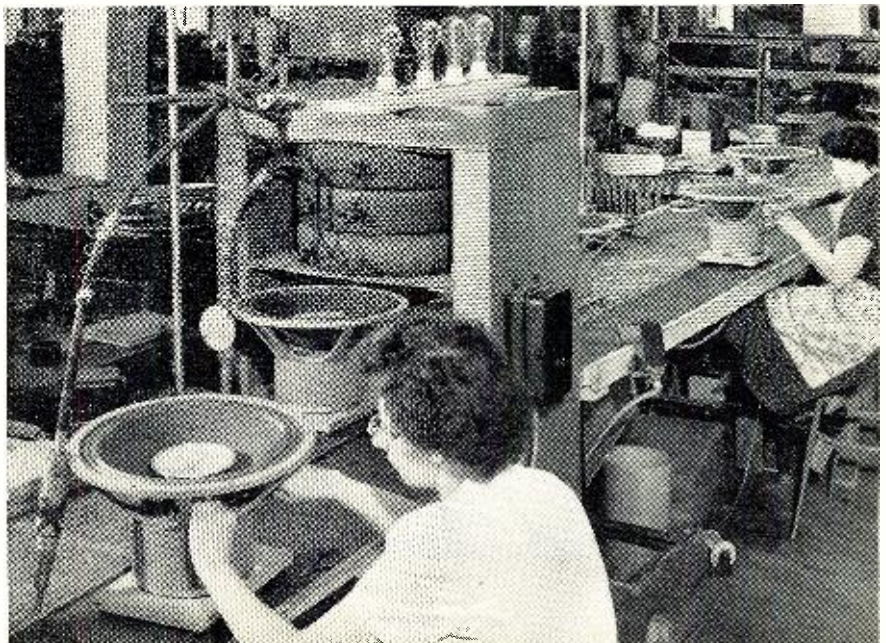


BUILD YOUR OWN Heathkits

- TEST INSTRUMENTS
- AMPLIFIERS
- RECEIVERS, etc.

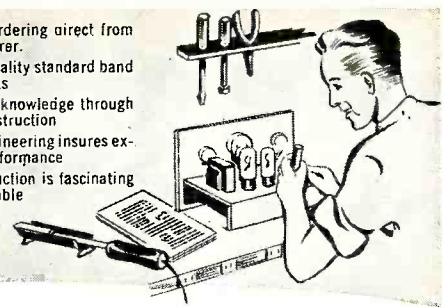- 1 Save by ordering direct from manufacturer.
- 2 All high quality standard band components
- 3 Increased knowledge through actual construction
- 4 Sound engineering insures excellent performance
- 5 Kit construction is fascinating and enjoyable



Heathkit MODEL O-8 OSCILLOSCOPE KIT

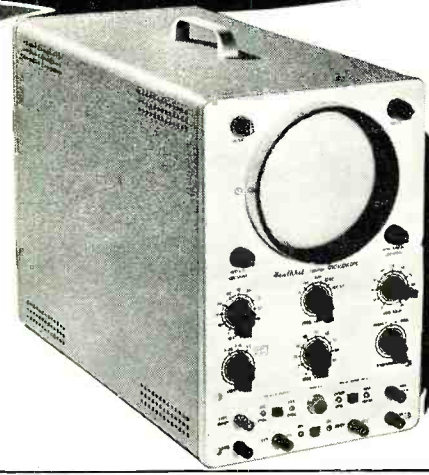

\$4350.
Shipping
Wt. 26 lbs.

The outstanding new 1953 model O-8 Heathkit Oscilloscope features the finest performance ever offered in this extremely popular kit instrument. Primarily intended as a general purpose oscilloscope for the faithful reproduction of actual wave forms and other electrical phenomena, it's vastly improved band width, good 100 KC square wave reproduction, three step vertical input attenuator, .025 volts per inch vertical sensitivity, etc., admirably qualify this instrument for TV and radio servicing, laboratory use, ham application and all general electronic development work. Improved vertical band width is obtained through the use of shunt peaking chokes with proper cathode compensation in the push-pull output stage. For additional flexibility of operation, provisions have been made for direct connections to the deflection plates, a Z axis input and a spot shape control for really fine focusing.

This beautiful kit is complete with all 10 tubes, including a 5" cathode ray tube, calibrated graph screen and flexible test leads. All necessary construction components, such as hardware, chassis, transformer, etc., and a detailed step by step construction manual, greatly simplify the assembly of this instrument.

Heathkit VOLTAGE CALIBRATOR KIT


The use of a Voltage Calibrator will greatly increase oscilloscope usefulness. Provides a convenient method of making peak to peak voltage measurements by establishing a relationship between the unknown wave shape and the Voltage Calibrator. Voltage ranges .01-100 volts peak to peak. The Voltage Calibrator features direct reading scales and a regulated power supply system.



MODEL VC-2
\$1150.
Shipping Wt. 4 lbs.

Heathkit ELECTRONIC SWITCH KIT

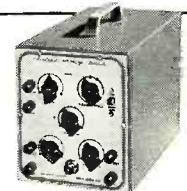The Heathkit Electronic Switch Kit will further extend scope usefulness by permitting simultaneous observation of two individually controlled traces. Continuously variable switching rates 10 cps to 2,000 cps in three ranges. Will also serve as a square wave generator over the range of switching frequencies.



MODEL S-2
\$1950.
Shipping Wt. 11 lbs.

Heathkit VACUUM TUBE VOLTMETER KIT

The beautiful new 1953 Heathkit Model V-6 VTVM, the world's most popular kit instrument, now offers many outstanding new features in addition to retaining all of the refinements developed and proven through the production of over 70,000 VTVM kits. The Heathkit VTVM now features extended voltage ranges with 50% greater coverage on the DC range. New 1 1/2 volt low scale provides well over 2 1/2 inches of scale length per volt permitting faster measurements with greater accuracy. AC and DC ranges are 0-1.5-5-15-50-150-500-1500 volts (1,000 volts maximum on AC). Ohmmeter ranges are X1, X10, X100, X1,000, X10K, X100K X1 meg. Measures .1 ohm to 1,000 megohms. Other features are dB scale, center scale zero adjust and polarity reversal switch. High 11 megohm input resistance virtually eliminates circuit loading.

The low anti-inflation price of this tremendously popular kit includes all tubes, necessary constructional material, test leads and the construction manual.

MODEL V-6
\$2450.
Shipping
Wt. 6 lbs.



Heathkit AC VACUUM TUBE VOLTMETER KIT

MODEL AV-2
\$2950.
Shipping
Wt. 5 lbs.

A new amplifier type AC VTVM that makes possible those sensitive measurements so essential in laboratory or audio work. Ten voltage ranges covering from .01 RMS full scale to 300 volts RMS full scale. Input impedance 1 megohm with frequency response 20-50,000 cycles. Ten DB ranges from -52 to +52 DB. Four diodes in meter bridge circuit for maximum linearity.



Heathkit HANDITESTER KIT

MODEL M-1
\$1350.
Shipping
Wt. 3 lbs.

The ever popular Handitester is now supplied with a Simpson 400 microampere meter movement. Provides AC and DC voltage ranges 0-10-30-300-1,000-5,000 volts. Ohmmeter ranges 0-3,000 and 0-300,000 ohms. DC current measurements 0-10 and 0-100 milliamperes. A completely self contained portable instrument.



HEATH COMPANY • Benton Harbor 15, Mich.

HEATHKITS for the ENGINEER

Heathkit VISUAL AURAL SIGNAL TRACER KIT



MODEL T-3
\$22.50
 Shipping
 Wt. 10 lbs.

Designed especially for service applications in AM-SW-FM-TV repair work. RF and audio two channel input. More than adequate sensitivity—new noise locator circuit—calibrated wattmeter—substitution speaker—visual signal indication. Can be used with scope and VTVM, checks phono cartridges, phono mechanisms, microphones, tuners, etc. Let the Heathkit Visual Aural Signal Tracer help you.

Heathkit RESISTANCE SUBSTITUTION BOX KIT



Choice of 36 switch selected resistance values 15 ohms to 10 megohms. All standard RTMA 1 watt 10% resistors. Buy several for those lab and service applications.

MODEL RS-1
 Ship. Wt. **\$5.50**
 2 lbs.

Heathkit AMATEUR TRANSMITTER KIT



MODEL AT-1
\$29.50
 Shipping Wt. 15 lbs.

Here is the long awaited Heathkit entry into the amateur radio field. The Heathkit AT-1 Transmitter kit is a well designed basic transmitter incorporating many desirable features and providing maximum overall performance.

Convenient band switching eliminates the bother and annoyance of plug in coils. It is merely necessary to switch to the desired frequency and plug in your favorite crystal or VFO. This transmitter features a self-contained power supply mounted on the same chassis and cabinet enclosed to minimize TVI. AC line by-passed to reduce radiation.

The coils supplied with the Heathkit AT-1 are pre-wound and adjusted for the necessary frequency coverage of 80-40-20-10 meters. The entire kit is supplied complete with all tubes, coils, punched and formed chassis and cabinet, as well as all constructional material required. A detailed assembly and operation manual is also furnished.

Heathkit CONDENSER CHECKER KIT



An instrument designed solely for its particular job. Not a "sideline" of a multiple function instrument. Measures value and quality of unknown condensers and resistors. Capacity range .00001 mfd to 1,000 mfd. Resistance range 100 ohms to 5 megohms. Sensitive electron beam indicator—five polarizing test voltages—safety spring return leakage test switch. An amazingly accurate instrument at this low price.

MODEL C-3
\$19.50 Shipping
 Wt. 8 lbs.

Heathkit SIGNAL GENERATOR KIT



MODEL SG-7
\$19.50
 Ship. Wt. 8 Lbs.

A service "must" is a reliable source of modulated (400 cycles) or unmodulated RF output. Frequency range 150 KC to 150 MC. Step attenuated and variable output—internal or external modulation. High output level and performance with low cost.


Heathkit GRID DIP METER KIT



World's largest selling Grid Dip Meter. Five pre-wound coils—frequency coverage 2-250 mc. Simplified construction and operation

MODEL GD-1A
\$19.50
 Ship. Wt. 4 Lbs.

Heathkit TUBE CHECKER KIT

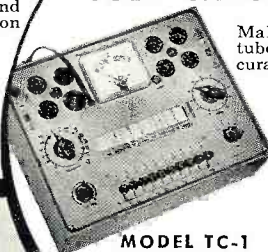

MODEL TC-1
\$29.50
 Shipping Wt. 12 lbs.

Make those all important tube tests quickly and accurately. Checks all tube types encountered in radio and TV work. Simplified setup and switching system provides fast checks for shorts, opens, individual elements and over-all quality. Portable cabinet available at slight additional cost. TV picture tube adapter also available. See order blank.

Revised Roll Chart .50

Heathkit LABORATORY REGULATED POWER SUPPLY KIT



MODEL PS-2
\$29.50
 Ship. Wt. 17 Lbs.

A regulated variable 160-450 volt DC output power supply for the lab or service shop. Accurate voltage and current measurements with large Simpson meter. AC supply 6.3 volts at 4 amperes—standby switch eliminates warmup time. Low hum content—5 tube circuit. AC and DC output voltages isolated from panel for maximum operational flexibility.

Heathkit VIBRATOR TESTER KIT



MODEL VT-1
\$14.50
 Shipping Wt. 6 lbs.

Checks for starting and quality of interrupter and self rectifier type vibrators. Five sockets—checks hundreds of types. Operates from continuously variable type battery eliminator.

Heathkit SQUARE WAVE GENERATOR KIT



MODEL SQ-1
\$29.50 Ship. Wt. 12 lbs.

True square wave output with frequency range 10 cycles to 100 KC. High variable output voltage level 0-20 volts at 600 ohms output impedance. Provisions for external synchronization. The ideal instrument for TV service work and wide band amplifier circuit development.


HEATH COMPANY • Benton Harbor 15, Mich.

SERVICEMAN • AMATEUR • STUDENT

Heathkit IMPEDANCE BRIDGE KIT

Provides choice of Wheatstone, Capacitance Comparison, Maxwell or Hay bridge circuits. Measurement of resistance-capacitance-inductance-dissipation factor-storage factor. 1% precision silver mica capacitance standard 1/2% precision resistors.

MODEL IB-18
\$69.50
Shipping Wt. 15 lbs.

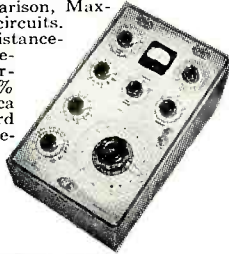

Heathkit INTERMODULATION ANALYZER KIT

Intermodulation distortion analysis is one of the most satisfactory methods of checking audio equipment. The IM-1 features two self contained high frequency generators (3,000 and 7,000 cycles) a 60 cycle low frequency source, intermodulation section, AC VTVM, and power supply all in one complete unit. Direct reading IM percentages on 3 calibrated scales 30%—10%—3%.


MODEL IM-1
Shipping Wt. 17 lbs. **\$39.50**



Heathkit AUDIO OSCILLATOR KIT

MODEL AO-1
\$24.50
Ship. Wt. 11 lbs.

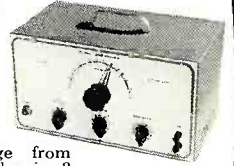Features sine or square wave coverage from 20-20,000 cycles in 3 ranges. Variable 10 volt output level at 600 ohms impedance. Thermistor controlled linearity—precision multiplier resistors—distortion less than .6%. An outstanding instrument value at this amazing low price.




Heathkit DECADE RESISTANCE KIT

MODEL DR-1
\$19.50

Ship. Wt. 4 lbs.

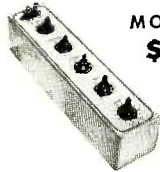
Individual switch selection of twenty 1% precision resistors in 1 ohm steps from 1 to 99,999 ohms. Sturdy ceramic wafer switches featuring silver plated contacts and smooth positive detent action.



Heathkit Q METER KIT

A typical Heathkit in vasion of the laborator instrument field. Her is the first successful low priced Q meter ever offered in kit form. Oscillator supplies RF in the range of 150 KC to 18 mc. Reads Q directly on calibrated meter scales. Measures Q of condensers, RF resistance and distributed capacity of coils. Calibrate capacitor with range of 40 mmf to 450 mmf with vernier ± 3 mmf. All measurements made at the operating frequency.


MODEL QM-1
\$39.50 Ship. Wt. 14 lbs.

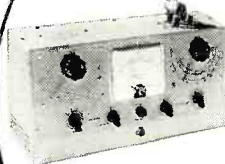

Heathkit AUDIO FREQUENCY METER KIT

Indicates audio frequency on large 4 1/2" Simpson meter. Ranges 10 cycles to 100 kc at input voltage level of 3-300 volts RMS. The input wave shape is not at all critical. Useful in production line testing—indicating square wave frequency—determining generator output. Operation entirely electronic, no vibrating reeds.

MODEL AF-1
\$34.50
Ship. Wt. 12 lbs.

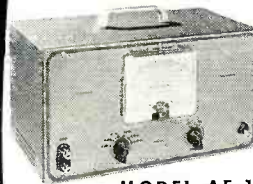

Heathkit BAR GENERATOR KIT

MODEL BG-1
\$14.50
Ship. Wt. 6 lbs.



The Heathkit BG-1 Bar Generator represents another welcome addition to the fast growing line of popular Heathkits. The station transmitted test pattern is rapidly disappearing and the Bar Generator is the logical answer to the TV serviceman's problem in obtaining quick accurate adjustment information.

The Bar Generator produces a series of horizontal or vertical bars on the TV screen. These bars are equally spaced and will quickly indicate picture linearity of the receiver under test. Since picture linearity is independent of transmitting frequency, it is unnecessary to provide coverage throughout the VHF range, thereby holding down instrument cost.

The Heathkit Bar generator is simple to use and is extremely portable, providing a quick means of checking the television receiver either in your workshop or in the customer's home.

Heathkit DECADE CONDENSER KIT

Switch selected 1% silver mica precision condensers providing capacity range of 100 mmf. to 0.111 mfd. in steps of 100 mmf.

MODEL DC-1
\$16.50

Shipping Wt. 4 lbs.



Heathkit AUDIO GENERATOR KIT

A new extended range 18 cycles—1 megacycle audio instrument at a remarkably low price. Five continuously variable output ranges—600 ohm output impedance—low distortion figure, less than 4% from 100 cps through audible range.


MODEL AG-8
\$29.50
Ship. Wt. 11 lbs.



Heathkit TELEVISION SWEEP GENERATOR KIT

Frequency coverage 10-90 mc and 150-230 mc. Variable sweep width 0-12 mc, built in absorption type marker, step and continuously variable output and blanking circuit.

MODEL TS-2
Ship. Wt. 20 lbs. **\$39.50**

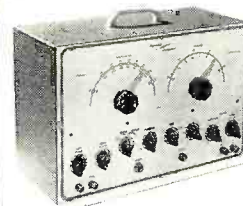

Heathkit BATTERY ELIMINATOR KIT

A variable 0-8 volt DC supply source rated at 10 amperes continuously and up to 15 amperes intermittently. Voltmeter, ammeter, automatic overload relay, fuse protection—heavy duty Mallory 17 disc rectifier.

MODEL BE-3
Ship. Wt. 17 lbs. **\$24.50**



WRITE FOR *Free* CATALOG

New 32 page 1953 Catalog lists all kits, specifications, schematics and latest price information.

HEATH COMPANY • Benton Harbor 15, Mich.

Heathkit SUPERHETERODYNE RECEIVER KITS



Broadcast Model BR-1 5 Tube-Broadcast Band 550 to 1600 KC coverage. Shipping Weight 11 lbs.
\$19.50



Three Band Model AR-1 6 Tube all wave circuit 3 Ranges, continuous coverage 550 KC to over 20 MC. Shipping Weight 11 lbs.
\$23.50

NEW HEATHKIT WILLIAMSON TYPE AMPLIFIER KIT

The ideal amplifier for custom high fidelity audio installations. Tops in performance, value, and flexibility of operation. Either Altec Lansing Peerless or Acrosound output transformers available. First Williamson type amplifier supplied with a matching preamplifier.

PRICES OF VARIOUS COMBINATIONS

W-2 Amplifier Kit (Incl. Main Amplifier with Peerless Output Transformer, Power Supply and WA-P1 Preamplifier Kit) Shipping Weight 37 lbs. Shipped express only **\$69.50**

W-2M Amplifier Kit (Incl. Main Amplifier with Peerless Output Transformer and Power Supply) Shipping Weight 29 lbs. Shipped express only **\$49.75**

W-3 Amplifier Kit (Incl. Main Amplifier with Acrosound Output Transformer, Power Supply and WA-P1 Preamplifier Kit) Shipping Weight 37 lbs. Shipped express only **\$69.50**

W-3M Amplifier Kit (Incl. Main Amplifier with Acrosound Output Transformer and Power Supply) Shipping Weight 29 lbs. Shipped express only **\$49.75**

WA-P1 Preamplifier Kit only. Shipping Weight 6 lbs. Shipped express or parcel post. **\$19.75**



Heathkit ECONOMY 6 WATT AMPLIFIER KIT

MODEL A-7

\$14.50

Dual inputs—separate bass and treble tone controls—output impedances 4-8-15 ohms.

Ship. Wt. 10 LBS.

A-7A

Amplifier with pre-amplifier stage for low level inputs... **\$16.50**

Heathkit HIGH FIDELITY 20 WATT AMPLIFIER KIT

MODEL A-8

\$33.50

Shipping Wt. 16 lbs.



A high fidelity full 20 watt general purpose amplifier. Dual inputs and separate tone controls for maximum flexibility. Peerless output transformer 4, 8 and 16 ohms.

A-8A with additional preamplifier stage for low level cartridge, microphone, etc. **\$35.50**

Heathkit FM TUNER KIT

MODEL FM-2

\$22.50

Shipping Wt. 9 lbs.

Sensitive transformer operated 8 tube circuit. Frequency coverage 88-108 mc. Pre-assembled and tuned "front end." Vernier tuning with slide rule type dial.

HEATH COMPANY • Benton Harbor 15, Mich.

ORDER BLANK

MAIL YOUR ORDER
TODAY TO THE
HEATH COMPANY
BENTON HARBOR 15,
MICHIGAN

From

SHIP VIA

- Parcel Post
 Express
 Freight
 Best Way

(PLEASE PRINT)

QUANTITY	ITEM	PRICE	QUANTITY	ITEM	PRICE
	Heathkit Oscilloscope Kit—Model O-8 (26 lbs.)	\$43.50		Heathkit Square Wave Generator—Model SQ-1 (12 lbs.)	29.50
	Heathkit Amateur Transmitter Kit—Model AT-1 (15 lbs.)	29.50		Heathkit AC VTVM Kit—Model AV-2 (5 lbs.)	29.50
	Heathkit Bar Generator Kit—Model BG-1 (6 lbs.)	14.50		Heathkit Intermodulation Analyzer Kit—Model IM-1 (17 lbs.)	39.50
	Heathkit Voltage Calibrator Kit Model VC-2 (4 lbs.)	11.50		Heathkit Regulated Power Supply Kit—Model PS-2 (17 lbs.)	29.50
	Heathkit Electronic Switch Kit—Model S-2 (11 lbs.)	19.50		Heathkit Handitester Kit—Model M-1 (3 lbs.)	13.50
	Heathkit TV Alignment Generator Kit—Model TS-2 (20 lbs.)	39.50		Heathkit Decade Resistance Kit—Model DR-1 (4 lbs.)	19.50
	Heathkit Q Meter Kit—Model QM-1 (14 lbs.)	39.50		Heathkit Decade Condenser Kit—Model DC-1 (4 lbs.)	16.50
	Heathkit Grid Dip Meter Kit—Model GD-1A (4 lbs.)	19.50		Heathkit Impedance Bridge Kit—Model IB-1B (15 lbs.)	69.50
	Heathkit VTVM Kit—Model V-6 (6 lbs.)	24.50		Heathkit Resistance Substitution Box Kit—Model RS-1 (2 lbs.)	5.50
	Heathkit Visual-Aural Signal Tracer Kit—Model T-3 (10 lbs.)	22.50		Heathkit F.M. Tuner Kit—Model FM-2 (9 lbs.)	22.50
	Heathkit Condenser Checker Kit—Model C-3 (8 lbs.)	19.50		Heathkit Broadcast Receiver Kit—Model BR-1 (11 lbs.)	19.50
	Heathkit RF Signal Generator Kit—Model SG-7 (8 lbs.)	19.50		Heathkit Three Band Receiver Kit—Model AR-1 (11 lbs.)	23.50
	Heathkit Tube Checker Kit—Model TC-1 (12 lbs.)	29.50		Heathkit Amplifier Kit—Model A-7 (10 lbs.)	14.50
	Heathkit Portable Tube Checker Kit—Model TC-1P (15 lbs.)	34.50		Heathkit Amplifier Kit—Model A-7A (10 lbs.)	16.50
	Heathkit Portable Tube Checker Cab. only No. 365 (8 lbs.)	7.50		Heathkit Amplifier Kit—Model A-8 (16 lbs.)	33.50
	Heathkit TV Tube Adapter No. 355 (1 lb.)	4.50		Heathkit Amplifier Kit—Model A-8A (16 lbs.)	35.50
	Heathkit Battery Eliminator Kit—Model BE-3 (17 lbs.)	24.50		Williamson Type Amplifier Kit (Type:)	
	Heathkit Vibrator Tester Kit—Model VT-1 (6 lbs.)	14.50		Shipped express only	
	Heathkit Audio Generator Kit—Model AG-8 (11 lbs.)	29.50		WA-P1 Preamplifier Kit (6 lbs.) (Shipped exp. or p.p.)	
	Heathkit Audio Oscillator Kit—Model AO-1 (11 lbs.)	24.50			
	Heathkit Audio Frequency Meter Kit—Model AF-1 (12 lbs.)	34.50			

Enclosed find () check () money order for _____ pounds.
Please ship C.O.D. () postage enclosed for _____

On Express orders do not include transportation charges—they will be collected by the express agency at time of delivery.

ON PARCEL POST ORDERS include postage for weight shown..... ORDERS FROM CANADA must include full remittance for merchandise.

Six-Meter Transceiver

(Continued from page 58)


by 3½" over-all, which contributes much to a neat finished appearance. The transceiver is built as two small subassemblies which are completely wired before mounting within the "Minibox." Aluminum sheet salvaged from old transcriptions was folded to form the two chassis bases. A flat mounting plate with lips serves for the receiver and audio section, with the tubes and audio transformers mounted below the plate. The transmitter r.f. section required a step-shaped chassis to position the tubes and coil forms properly. The layout of components for these two units has to be carefully correlated so that the sections will interlace when fitted into the "Minibox."

The control switches should be mounted on the "Minibox" panel with suitable lengths of wire soldered to them before the two subassemblies are bolted in place in one corner of the box. The interconnecting wiring can then be completed, and the end support plate attached to form the battery compartment. This space measures just under 4" x 6" to provide room for two 90-volt "B" batteries in parallel, together with three 1½-volt flashlight cells which are connected in parallel for the "A" supply.

Operation and Adjustment

The initial tune-up of the transmitter is most easily done with the aid of a grid-dip meter. The oscillator

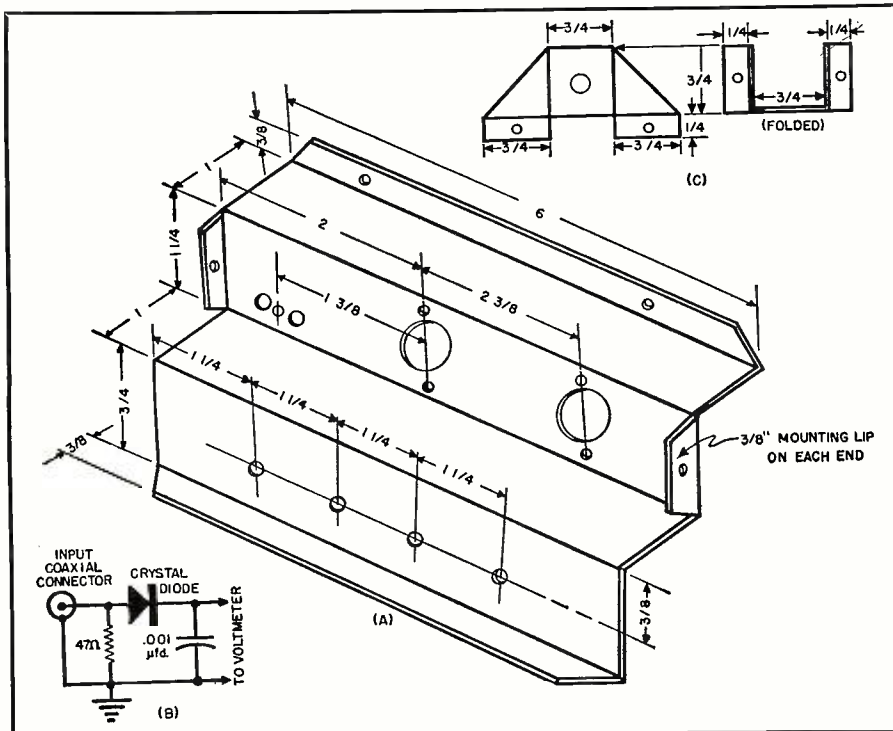(A) Details of the transmitter chassis, bent up from sheet aluminum. (B) A dummy load for tuning the transmitter. (C) Details of the receiver coil mounting bracket. Its position can be seen in receiver bottom-view photograph. Receiver chassis is a flat mounting plate, 3¼" x 6", with ⅜" lips. See photos for parts layout.



slug should be detuned slightly from resonance so that the circuit will be sure to oscillate whenever power is applied. The multiplier tanks are tuned for peak output. The "Minibox" cover has some detuning effect on the coils, so optimum adjustments are best made with this cover in place. Small ¼" holes drilled in the cover to give access to the slugs from outside can be neatly covered by hole plugs when not in use.

A communications receiver "S" meter, or a voltmeter connected to the suggested dummy load will make a handy output indicator for the tuning adjustments.

The detector slug, accessible through the front panel hole, can be adjusted by listening to a received signal. Since the operation is on a fixed frequency, the tuning adjustment will hold for long periods.

As would be expected, the useful range of the transceiver is limited by the signal-to-noise ratio of the receiver, so antenna efficiency plays a major part in the performance. Center- and top-loaded verticals were found to be less satisfactory than a quarter-wave whip for portable operation. A three-section collapsible auto radio whip fitted to a coax connector has proved to be a very serviceable antenna.

Any simulated ground plane or counterpoise will increase the antenna effectiveness. The range can, therefore, be increased by placing the transceiver on top of a car or other metal surface. In some applications a low-channel TV antenna can be used with excellent results. When used in a car, the regular 55" broad-

Electrical Appliance Repairs MADE EASY

Great Repair Manual Covers EVERY Repair on ALL Home Appliances

FREE 10-Day Trial

NO repair job is too tough with the help of this big new Guide. TELLS and SHOWS how to service ALL home appliances.

SAVE MONEY keeping your own appliances like new.

MAKE MONEY with a home repair shop of your own . . . full or spare time. OVER 850 "how-to-do-it" pages, packed with pictures, drawings, diagrams. Sectional charts locate "trouble spots" in a jiffy . . . make it easy to dismantle and reassemble appliances correctly. A-B-C directions tell "why" as well as "how." Book covers fundamentals of electricity for beginners. Over 150 manufacturers supplied the servicing and repair data.

Try! Constructions! Trouble-Shooting! Remedies!

- on:
- electric heaters
 - broilers
 - wafflebakers
 - washing machines
 - water pumps
 - food mixers
 - irons
 - toasters
 - ironers
 - sewing machines
 - ranges
 - clothes dryers
 - garbage disposers
 - lawn mowers
 - floor waxers
 - water heaters
 - clocks
 - dishwashers
 - coffee makers
 - air conditioning units
 - electric fans
 - vacuum cleaners
 - refrigerators

"WHAT A BOOK"

"What a book! Just crammed full of useful information, it deals with everything from electric irons and toasters to electric dishwashers and washing machines. Written in practical and everyday language and profusely illustrated throughout, the work will enable the serviceman to determine trouble spots in the quickest possible time and will provide him with the know-how to tackle the problem and solve it."

—Canadian Industrial Equipment News

BEST INVESTMENT FOR RADIO SERVICEMEN

"Here is the year's best investment for radio servicemen who want to increase their incomes . . . If you aren't a first-class handyman after reading Electrical Appliance Servicing this reviewer will be very much amazed."—Radiofile

MAIL THIS COUPON NOW FOR FREE 10-DAY EXAMINATION

McGraw-Hill Book Co., Dept. RTN-8
330 W. 42nd St., N. Y. C. 36

Send Crouse's Electrical Appliance Servicing for 10-DAY FREE EXAMINATION. I will send only \$3.00 (plus small delivery charge) in 10 days—and \$3.00 a month for 2 months to complete payment. Otherwise I will return the book postpaid.

Name

Address

City..... Zone..... State.....

Company

Position..... RTN-8

WE'll pay delivery if you enclose \$9.00 (check or M.O.) with coupon. Same 10-day Return Privilege for full refund.


(This offer applies to U. S. only)

Concertone

"Just like being there"

THE ONLY TAPE RECORDER UNDER \$1000 WITH ALL THESE FEATURES

- Designed for Custom, Console, or Portable installation ★
- 50-15,000 CPS frequency response with negligible distortion ★
- 3 Heads — Monitor from the tape while recording ★
- 3 Motors for superb tape motion and fast forward and rewind operation ★
- Instantaneous selection of 7½ or 15 ips with automatic equalization ★
- "Straight line" tape threading ★
- Plays up to 10½ inch reels without extension arms ★
- Interchangeable heads for single or dual track ★

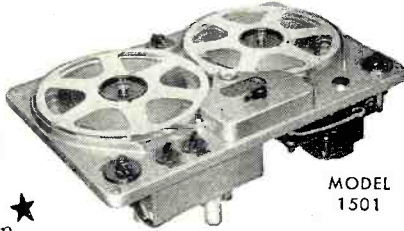

MODEL 1501

Professional Users
Net \$345.00

WRITE FOR BULLETIN 201

Manufactured by

Berlant Associates

4917 W. Jefferson Boulevard Los Angeles 16, California



cast receiver antenna gives a fine account of itself.

The range between transceivers is naturally affected by intervening terrain. Transmissions of a mile or so can be expected over good paths when the units are hand-held, with correspondingly greater coverage when better antenna systems are used. —30—

Anti-Flutter Circuit

(Continued from page 39)

a diode a.g.c. circuit, direct-coupled video amplifier, and cathode drive to the picture tube. Its modification is more complicated. See Fig. 4. The 470k resistor and parallel condenser are removed and replaced by the anti-flutter network shown in Fig. 4B. The resistance values in the network are modified as one of the steps to restore the picture tube cathode potential to its original value and the condensers are changed to maintain the proper time constants with the new resistance values. A resistance-capacitance low-frequency compensation network is added in the plate circuit as the second step in restoring the picture tube cathode potential and also to boost the transmission of the video signal d.c. component to approximately 100%, assuming a picture tube cathode input resistance of 50,000 ohms.

REFERENCES

1. Billin, J. J.: "Anti-Flutter Circuit," *Journal of the Television Society*, October-December 1952.
2. British Patent 648,537.

—30—

INTERNATIONAL CONTACTS

UNITED STATES radio amateurs are reminded that communication between amateur stations licensed by the Federal Communications Commission and foreign amateur stations is permissible subject to the limitations of Section 1 of Article 42 of the Radio Regulations annexed to the International Telecommunications Convention (Atlantic City 1947). Section 1 of this Article provides as follows:

"Radiocommunications between amateur stations of different countries shall be forbidden if the Administration of one of the countries concerned has notified that it objects to such radiocommunications."

Information available through April 16, 1953, indicates that the following countries have forbidden radio communication between their amateur stations and amateur stations of other countries: Austria, Cambodia, Indonesia, Iran (all amateur operation forbidden), Korea, Laos, Thailand, and Viet Nam.

Amateur stations in Australia are authorized to conduct radiocommunication for purely experimental purposes with amateur stations in other countries, the administrations of which permit such radiocommunication.

Amateur service has not yet been organized in Jordan and Rumania.

This information does not modify the handling of third-party communications by amateurs as outlined in the Commission's Public Notice of April 15, 1952.

—30—

COMPARISON PROVES

EICO OFFERS

GREATEST V-O-M values!



GET the MOST for your money — Before you buy, see chart below!

World-renowned **EICO**
VOLT-OHM-MILLIAMMETERS

- * #536 KIT \$12.90. Wired \$14.90
- #526 KIT (with 1% multipliers) only \$13.90. Wired \$16.90

VERIFY AT YOUR DEALER'S	EICO	Co. A	Co. B	Co. C	Co. D.	
	\$12.90 up (KIT)	All Over \$24.00				EICO price range
31 ranges?	YES	No	No	No	No	
Full-size 3-inch meter?	YES	Yes	Yes	Yes	No	
400 ua sensitivity?	YES	Yes	Yes	Yes	No	
Zero to 1 v. range on both AC and DC?	YES	No	No	No	No	
5000 v. range on both AC and DC?	YES	Yes	No	Yes	No	
AC/DC sens: 1000 Ω /v.?	YES	Yes	Yes	Yes	No	
DC and AC Current Ranges?	YES	No	No	No	No	
In KIT and Wired Form?	YES	Wired Only	Wired Only	Wired Only	Wired Only	
Lowest cost in the Industry?	YES *See Above	No	No	No	No	
		All over \$24.00				EICO price range

Write for FREE Catalog MR-8 & name of local dealer. Prices 3% higher on West Coast.

ELECTRONIC INSTRUMENT CO., Inc.
84 WITHERS STREET, BROOKLYN 11, N. Y.

(Advertisement)




"I'm not complaining. Just wanted to compliment you on the quality of the music since you got the **JENSEN NEEDLE!**"



\$24⁹⁵
VALUE
 for only **\$5.00**
 and 30 Sylvania
 Premium Tokens . . .

Between Aug. 1st and Nov. 15th

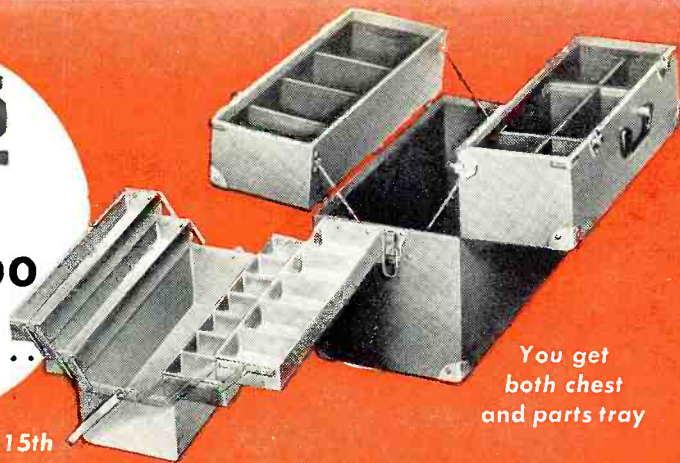


You get
 both chest
 and parts tray

Servicemen! Here's Your Sylvania

T-N-T CHEST

(TUBE AND TOOL)

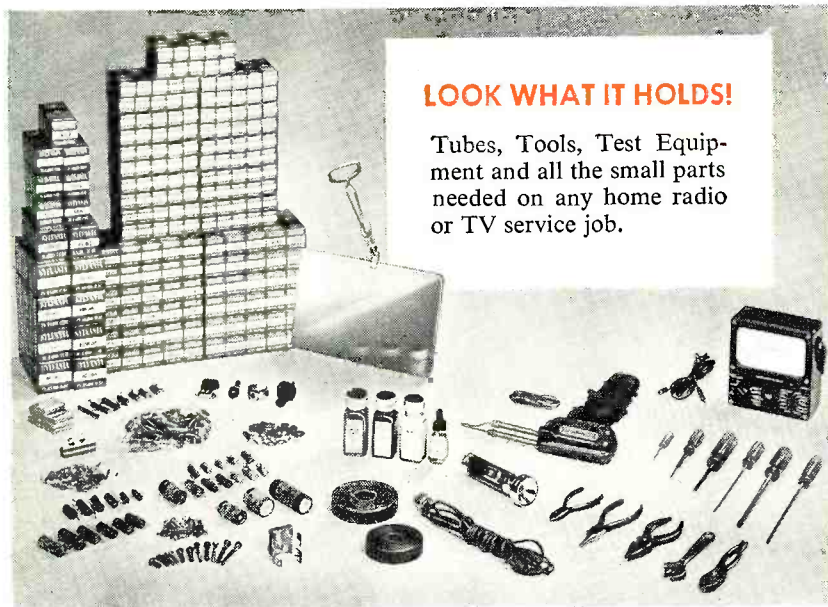The Most Valuable Service Aid You've Ever Seen!



LOOK WHAT IT HOLDS!

Tubes, Tools, Test Equipment and all the small parts needed on any home radio or TV service job.

Talk about a useful servicing aid . . . this Sylvania T-N-T (Tube and Tool) Chest is really it! Carries more tubes, tools and parts than any chest on the market!

LOOK AT THESE FEATURES:

- Bass and fir plywood case
- Waterproof Du Pont Fabrikoid cover
- Holds 187 receiving tubes
- Lightweight folding aluminum tool and parts tray
- Unbreakable plastic handle
- Brass-plated hardware
- Room for mirror and ohmmeter
- It's a complete, portable service shop!

ACT NOW . . . Offer Limited!

This chest is now yours for only \$5.00 and 30 Sylvania Premium Tokens. Offer good only between August 1st and November 15th. See your Sylvania Distributor who has these kits now.

SYLVANIA

Sylvania Electric Products Inc., 1740 Broadway, New York 19, N. Y.

LIGHTING • RADIO • ELECTRONICS • TELEVISION

In Canada: Sylvania Electric (Canada) Ltd.
 University Tower Building, St. Catherine St., Montreal, P. Q.

Remember, you get 1 Sylvania Premium Token with every 25 receiving tubes or with every picture tube you buy.



**OWN THIS GREAT LIBRARY
for complete authoritative
analyses of all important
AUDIO AMPLIFIERS**

Only data of its kind available on hundreds of important audio amplifiers. Complete, uniform, detailed analysis of each unit, based on actual laboratory study of the equipment. Includes circuit diagrams, chassis photo views, parts data, full technical coverage. Available in four profusely illustrated volumes—absolutely indispensable to audiophiles, engineers and students.

VOL. 4. Covers 75 audio amplifiers and important tuners produced during 1951 and 1952. Never before available in a single compilation. 352 pages, 8½ x 11".

ORDER AA-4. Only \$3.95

VOL. 3. Covers 50 audio amplifiers and 22 FM and AM tuners made during 1950. Detailed data on design and servicing. 352 pages, 8½ x 11".

ORDER AA-3. Only \$3.95

VOL. 2. Covers 104 amplifiers and 12 tuners produced in 1949. 368 pages, 8½ x 11".

ORDER AA-2. Only \$3.95

VOL. 1. Covers 102 post-war amplifiers and tuners produced through 1948. 352p, 8½ x 11".

ORDER AA-1. Only \$3.95

BEST-SELLER ON AUDIO!



"The Recording and Reproduction of Sound"

Only complete reference on AUDIO! New second edition—over 800 pages. Chapters on sound wave behavior; recording methods; the decibel; phono reproducers; cutting styli; microphones; loudspeakers;

dividing networks; attenuators; mixers; amplifiers; tuners; home music systems—hundreds of other subjects. The great Audio book by Oliver Read—largest-selling in its field.

ORDER RR-2. Only \$7.95

HOWARD W. SAMS & CO., INC.

Order from your Parts Jobber today, or write direct to Howard W. Sams & Co., Inc. 2203 East 46th St., Indianapolis 5, Ind.

\$ enclosed. Send following books:
 AA-1 (\$3.95) AA-3 (\$3.95) RR-2 (\$7.95)
 AA-2 (\$3.95) AA-4 (\$3.95)

Name
 Address
 City Zone State

MODERNIZE YOUR AM-FM TUNER

By **LT. COL. BYRON E. HARGROVE**

Signal Liaison Officer
 TRADS. Fort Eustis, Va.

Pep up those older model AM/FM tuners by making a few easy circuit changes and substituting newer and hotter tubes.

MANY FM-AM enthusiasts purchased sets as soon as they were available after World War II. Although many have given excellent service through the years, almost all of them are performing considerably below what could be expected of them.


The modernization of a *Meissner* Model 2961 is described. Some, or all, of the changes described can be applied profitably to most FM-AM receivers.

The *Meissner* Model 2961 is a 29 tube FM-AM-phono combination with completely independent FM and AM tuners, but a common power supply and audio system. It was equipped with a phono unit having a crystal pickup and compensating preamplifier.

The audio system uses four 6L6 tubes, triode connected, in push-pull parallel as output tubes. Original specifications called for substantially flat response between 60 and 20,000 cps. Since the speaker with which this unit is equipped is capable of good reproduction of considerably lower frequencies, all audio coupling condensers in the main audio unit were replaced with .1 µfd., 600 volt units. Low frequency response was considerably improved by this change.

To obtain better record reproduction, the crystal pickup was replaced with a *G-E* reluctance unit. This necessitated replacement of the original preamp stage using a 9002 triode, with a 6SC7 preamp stage. The 6SC7 tube was mounted in the same position as the original preamplifier by removing the miniature socket, reaming the hole, and mounting an octal socket. See diagram Fig. 1.

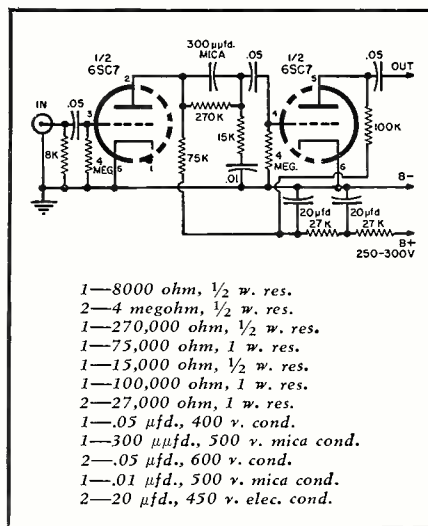In the FM unit, the 6AG5 r.f. tube and the three 6AG5 i.f. tubes are replaced by 6CB6 tubes, a newer, hotter



- 1—8000 ohm, ½ w. res.
- 2—4 megohm, ½ w. res.
- 1—270,000 ohm, ½ w. res.
- 1—75,000 ohm, 1 w. res.
- 1—15,000 ohm, ½ w. res.
- 1—100,000 ohm, 1 w. res.
- 2—27,000 ohm, 1 w. res.
- 1—.05 µfd., 400 v. cond.
- 1—300 µµfd., 500 v. mica cond.
- 2—.05 µfd., 600 v. cond.
- 1—.01 µfd., 500 v. mica cond.
- 2—20 µfd., 450 v. elec. cond.


Fig. 1. Preamp circuit added to permit use of the *G-E* variable reluctance pickup unit.

type. No circuit changes are required except to connect pins 2 and 7 together at each tube socket concerned.

Re-alignment of the set will be required. While the use of a sweep generator and oscilloscope is preferred, a thoroughly satisfactory job can be done with nothing more than a good FM station within comparatively short range.

Tune the set to the high frequency portion of the FM band to a point where no station is being received. Beginning with the i.f. transformer nearest the discriminator (not the discriminator transformer), and progressing toward the "front end", adjust all i.f. transformers for maximum noise output. (Better relations with the wife and other members of the family will be maintained if this is done when you

Rear view of the author's "modernized" FM tuner. At the extreme left is the Drake 300-ohm hi-pass filter. The glass tube above the "UL" stamp on the chassis is the 6SC7 preamplifier with aluminum foil wrapped around it. This is not necessary if a metal tube is used. To the rear of the 6SC7 and above it is the 6AB4 grounded-grid r.f. stage mounted on aluminum bracket. Behind this is the original FM tuner. To the right of the tuner is the AM r.f. mixer and oscillator tubes. In front of the AM tuning condenser is the new "Ferri-Loop" antenna. The 300-ohm ribbon to this antenna connects one side of the original loop antenna to top of "Ferri-Loop." The two hook-up wires from top of cabinet are built-in antennas, one for push-button tuner and the other for reception on the shortwave bands.

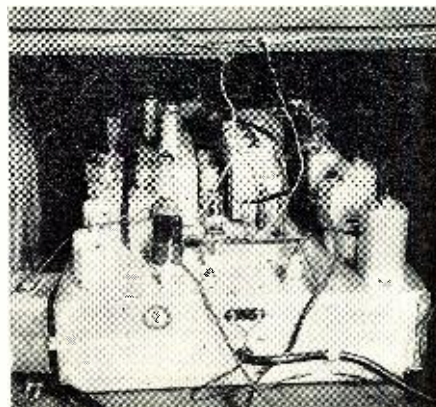

NO INTEREST!!

Buy on our radically new Time Payment Plan

NO CARRYING CHARGES!!

— OUR POLICY —

All merchandise offered on a "try-before-you-buy" basis. If the item you order does not meet with your approval, you may return it, no explanation necessary.

All merchandise offered on easy terms at the net cash price with no interest charges added!

Superior's New
Model 770



Model 770 is an accurate pocket-size V.O.M. Measures only 3 1/8" x 5 1/2" x 2 1/4".

VOLT-OHM MILLIAMMETER

Sensitivity—1000 ohms per volt


Uses latest design 2% accurate 1 Mil. D'Arsonval type meter. • Same zero adjustment holds for both resistance ranges. It is not necessary to readjust when switching from one resistance range to another. This is an important time-saving feature never before included in a V.O.M. in this price range. • Housed in round-cornered, molded case. • Beautiful black etched panel. Depressed letters filled with permanent white. Insures long-life even with constant use.

- SPECIFICATIONS:**
- 6 A.C. VOLTAGE RANGES: 0-15/30/150/300/1500/3000 Volts.
 - 6 D.C. VOLTAGE RANGES: 0-7.5/15/75/150/750/1500 Volts.
 - 4 D.C. CURRENT RANGES: 0-1.5/15/150 MA. 0-1.5 Amps.
 - 2 RESISTANCE RANGES: 0-500 Ohms. 0-1 Megohm.

The Model 770 comes complete with self-contained batteries, test leads and all operating instructions.

\$14.90
NET

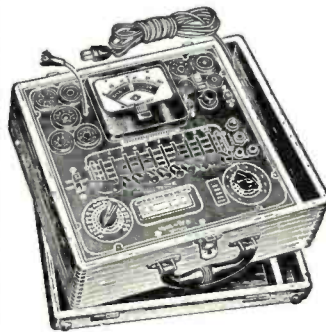Superior's New
Model TV-11 **TUBE TESTER**



Operates on 105-130 Volt 60 Cycles A.C. Hand-rubbed oak cabinet complete with portable cover **\$47.50** NET

• Uses the new self-cleaning Lever Action Switches for individual element testing. Because all elements are numbered according to pin number in the RMA base numbering system, the user can instantly identify which element is under test. Tubes having tapped filaments and tubes with filaments terminating in more than one pin are truly tested with the Model TV-11 as any of the pins may be placed in the neutral position when necessary. • Uses no combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible to damage a tube by inserting it in the wrong socket. • Free-moving built-in roll chart provides complete data for all tubes. • Phono jack on front panel for plugging in either phones or external amplifier detects microphonic tubes or noise due to faulty elements and loose external connections.

Superior's New
Model 670-A

SUPER-METER

A COMBINATION VOLT-OHM MILLIAMMETER PLUS CAPACITY REACTANCE INDUCTANCE AND DECIBEL MEASUREMENTS

- SPECIFICATIONS:**
- D.C. VOLTS: 0 to 7.5/15/75/150/750/1,500/7,500 Volts.
 - A.C. VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
 - OUTPUT VOLTS: 0 to 15/30/160/300/1,500/3,000 Volts
 - D.C. CURRENT: 0 to 1.5/15/150 Ma. 0 to 1.5/15 Amperes
 - RESISTANCE: 0 to 1,000/100,000 Ohms 0 to 10 Megohms
 - CAPACITY: .001 to 1 Mfd. 1 to 50 Mfd. (Quality test for electrolytics)
 - REACTANCE: 5 to 2,500 Ohms, 2,500 Ohms to 2.5 Megohms
 - INDUCTANCE: .15 to 7 Henries 7 to 7,000 Henries
 - DECIBELS: -6 to +18 +14 to +38 +34 to +58



Comes housed in rugged, crackle-finished steel cabinet complete with test leads and operating instructions. Size 6 1/4" x 9 1/2" x 1 1/2".

\$28.40
NET

ADDED FEATURE:
The Model 670-A includes a special GOOD-BAD scale for checking the quality of electrolytic condensers at a test potential of 150 Volts.

Superior's New
TV BAR GENERATOR

THROWS AN ACTUAL BAR PATTERN ON ANY TV RECEIVER SCREEN!!



TV Bar Generator comes complete with shielded leads and detailed operating instructions. Only **\$39.95** NET

CONNECTS DIRECT TO ANTENNA POST
NO CONNECTION INSIDE RECEIVER

Features.—Can be used when no stations are on the air. • Provides linear patterns to adjust vertical and horizontal linearity • Provides vertical and horizontal sweep signals • Provides signal for testing video amplifiers.

Superior's Model 660-A—A NEW A.C. OPERATED

SIGNAL GENERATOR

Provides Complete Coverage for A.M.—F.M. and TV Alignment



• Tubes used: 1-6BE6 as R. F. Oscillator, mixer and amplifier. 1-6BE6 as Audio Oscillator. 1-6HG as Power Rectifier. The Model 660-A comes complete with coaxial cable test lead and instructions **\$42.95** NET

• Generates Radio Frequencies from 100 Kilocycles to 50 Megacycles on fundamentals and from 60 Megacycles to 220 Megacycles on powerful harmonics. • Accuracy and stability are assured by the use of permeability trimmed Hi-Q coils. • R. F. available separately or modulated by the internal audio oscillator. • Built in 400 cycle sine wave audio oscillator used to modulate the R. F. signal also available separately for audio testing of receivers, amplifiers, hard of hearing aids, etc. • R. F. Oscillator Circuit: A high transconductance heptode is used as an R. F. oscillator, mixer and amplifier. Modulation is effected by electron coupling in the mixer section thus isolating the oscillator from load changes and affording high stability. • A. F. Oscillator Circuit: A high transconductance heptode connected as a high-mu triode is used as an audio oscillator in a high-Coupled Circuit. The output (over 1 Volt) is nearly pure sine wave. • Attenuator: A 5 step ladder type of attenuator is used.

NEW TIME PAYMENT PLAN

ORDER BLANK

MOSS ELECTRONIC DISTRIBUTING CO., INC.
Dept. B-65, 38 Murray Street, New York 7, N. Y.

Please send me the units checked below. I am enclosing the down payment with order and agree to pay the monthly balance as shown. It is understood there will be no carrying interest or any other charges, provided I send my monthly payments when due. It is further understood that should I fail to make payment when due, the full unpaid balance shall become immediately due and payable.

- MODEL 770 Total Price \$14.90
\$2.90 down payment. Balance \$2.00 monthly for 6 months.
- MODEL TV-11 Total Price \$47.50
\$11.50 down payment. Balance \$6.00 monthly for 6 months.
- MODEL 670-A Total Price \$28.40
\$7.40 down payment. Balance \$3.50 monthly for 6 months.
- TELEVISION BAR GENERATOR Total Price \$39.95
\$9.95 down payment. Balance \$5.00 monthly for 6 months.
- MODEL 660-A Total Price \$42.95
\$12.95 down payment. Balance \$5.00 monthly for 6 months.
- I enclose \$..... as down payment.
- Ship C.O.D. for the down payment.

Signature.....

Name.....

Address.....

City..... Zone..... State.....

to the

E. E. or

PHYSICS GRADUATE

with an interest
or experience in

RADAR or

ELECTRONICS

Hughes Research and Development Laboratories, one of the nation's large electronic organizations, are now creating a number of new openings in an important phase of operations.

Here is
what one of
these
positions offers
you

OUR COMPANY

located in Southern California, is presently engaged in the development of advanced radar devices, electronic computers and guided missiles.

THESE NEW POSITIONS

are for men who will serve as technical advisors to the companies and government agencies purchasing Hughes equipment.

YOU WILL BE TRAINED

(at full pay) in our Laboratories for several months until you are thoroughly familiar with the equipment that you will later help the Services to understand and properly employ.

AFTER TRAINING

you may (1) remain with the Laboratories in Southern California in an instruction or administrative capacity, (2) become the Hughes representative at a company where our equipment is being installed, or (3) be the Hughes representative at a military base in this country—or overseas (single men only). Adequate traveling allowances are given, and married men keep their families with them at all times.

YOUR FUTURE

in the expanding electronics field will be enhanced by the all-around experience gained. As the employment of commercial electronic systems increases, you will find this training in the most advanced techniques extremely valuable.

How
to
apply

If you are under 35 years of age
and have an E.E. or Physics
degree and an interest or
experience in radar or electronics,

write
to

HUGHES

RESEARCH AND DEVELOPMENT
LABORATORIES

Scientific and Engineering Staff
Culver City,
Los Angeles County, California

Assurance is required that the relocation of the applicant will not cause the disruption of an urgent military project.

are the sole occupant of the house.)

After completing the i.f. alignment, align the 1st detector or converter stage and the r.f. stage in that order, again tuning for maximum noise. The FM antenna to be used should be connected before aligning the r.f. stage.

Now tune in an FM station. Identify it and check the frequency. Adjust the oscillator trimmer, if necessary, to bring it on frequency. If you are lucky, the quality should be OK. However, if distortion is present, adjust the discriminator transformer for best audio quality.

It should be possible now to obtain considerably improved FM reception. Further worthwhile improvement can be obtained by adding a grounded-grid triode r.f. amplifier. This stage is broadly tuned to the FM band and no additional controls are required. The r.f. stage should be mounted on a bracket as close as practicable to the existing r.f. stage. No shielding is necessary and if the set has been free from amateur radio and other interference previously, none should be present after the stage is installed.

"B+" for the 6AB4 grounded-grid r.f. amplifier should be taken from the "B+" lead for the r.f. or i.f. tubes in the original receiver. This will insure a well filtered, correct voltage for this stage. Heater voltage (for pins 3 and 4) may be obtained from any i.f. or r.f. socket.

The output from the r.f. amplifier is fed through a 22 μ fd. condenser directly to the "hot" end of the original antenna coil by means of the shortest lead possible. Use insulated hook-up wire, not shielded wire.

Now turn on the set and re-align the original r.f. amplifier for maximum noise output. The noise output will be increased slightly, since a grounded-grid triode amplifier introduces little noise, but the receiver sensitivity should be up materially.

With the completion of the above changes, the number of usable FM stations should be vastly increased.

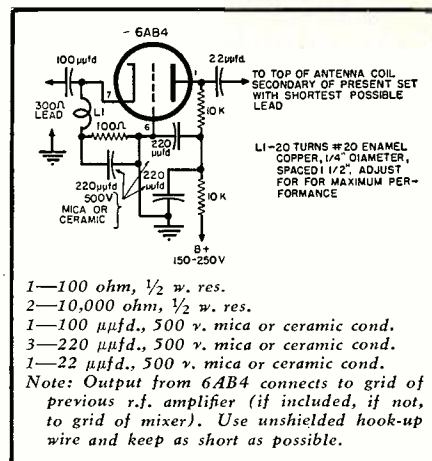


Fig. 2. Adding a grounded-grid triode r.f. amplifier to Meissner Model 2961 radio.


Now to tackle the AM portion of the set. Disconnect the lead from the antenna coil to the tuning condenser. Mount a "Ferri-Loop" (one of the new compact antennas) above the chassis and close to the tuning condenser. Ground one side of the "Ferri-Loop" and connect the other lead to the variable condenser. Remove the small wire attached to the "Ferri-Loop" and connect one side of the original loop antenna to the point where this small wire was attached. Leave the other lead from the loop antenna disconnected.

Now tune the set to about 1000 kc. and adjust the "Ferri-Loop" for maximum signal response. The Meissner uses 9003 tubes as the r.f. amplifier and in the two i.f. stages. Replacing these with 6BJ6 tubes will raise the performance considerably. No circuit changes are required other than connecting together pins 2 and 7 on the sockets concerned.

After installing the new tubes, re-align the set. Performance on AM, FM, and phono should be much better now than when the set was new. Total cost, if all parts are purchased new, should be approximately \$25.00

-30-

Visitors to Electronic Wholesalers, Inc.'s recent "High Fidelity Music Festival" were able to see and compare a wide variety of audio equipment at this Sound Sales Salon set up in the Emerald Room of the Hotel Burlington in downtown Washington. The 45-day event drew thousands of interested spectators, attesting to the ever-increasing popularity of high quality home sound systems. Because of this widespread interest, the company has recently opened a new downtown Sound Sales Salon.

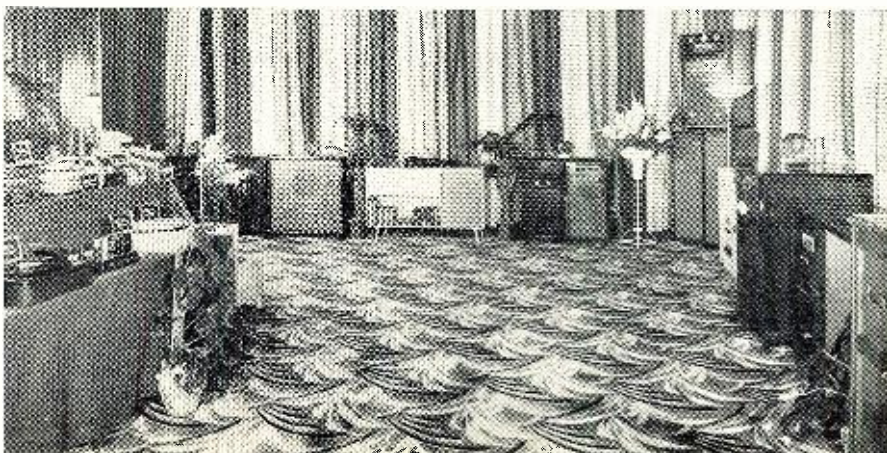



KEEP YOUR EYE ON THE "Surprise" TRADE-IN EVENT OF THE YEAR



HALLICRAFTERS SX-71.
Less Speaker. Shpg. wt. 51 lbs.
Net \$224.50

Don't be distracted by claims of "just as good." Nothing, but absolutely nothing beats a Walter Ashe "Surprise" Trade-In on your used test and communication equipment. Allowances were never better than now. So get your trade-in deal working today. Wire, write, phone or use the handy coupon below.



COLLINS 75A-3 with 3 KC Mechanical Filter. Less speaker.
Net \$530.00



ELMAC Model A-54. Wired for 10, 11, 20, 40 and 75 meters. Net \$143.00
Model A-54H. Same as above but for crystal or dynamic mike. Net \$153.00



ELMAC MOBILE Receiver. Model PMR-6-A. Net \$134.50



JOHNSON VIKING II Transmitter Kit. Shpg. wt. 85 lbs. Net \$279.50
JOHNSON VIKING II. Wired and Tested. Net \$319.50

All prices f. o. b. St. Louis • Phone Chestnut 1125

Walter Ashe
RADIO CO.
1125 PINE ST. • ST. LOUIS 1, MO.

FREE CATALOG!

WALTER ASHE RADIO COMPANY
1125 Pine Street, St. Louis 1, Missouri

Rush "Surprise" Trade-in Offer on my _____

for _____ (show make and model number of new equipment desired)

Send new 1953 Catalog.

Name _____

Address _____

City _____ Zone _____ State _____

R-53-8

Send
for
your
copy
today

HINTS and KINKS for MOBILEERS

By JACK NAJORK, W2HNN

These simple antenna tricks and a painless addition to the receiver will add greatly to the enjoyment of mobile QSO's.

MANY articles on center- and base-loaded mobile antennas have pointed out that an antenna of this type must be accurately pruned to resonance at the operating frequency if it is to accept power and do a good job of radiating. If the ham is fortunate enough to own a grid-dip meter, finding the resonant frequency of the antenna is a simple matter.

Without such an instrument, determination of antenna frequency can become quite a problem, especially if a loading coil of unknown inductance is used with a whip whose capacity is also a matter of speculation. Starting with such a combination, it is often found that the resonant frequency of the system may be a half megacycle or more removed from the desired frequency.

The approximate resonant frequency of a new or experimental antenna of this type can be found very easily (and inexpensively) by a method filched from the broadcast antenna engineers*, which makes use of an ordinary buzzer and a calibrated receiver. The whip is grounded and the buzzer is loosely coupled to it, as shown in Fig. 1A. The resulting shock excitation of the system radiates a signal which peaks up sharply at the resonant frequency of the antenna. The station receiver is used to find this frequency and the system can then be pruned to the desired channel.

This method really works very well, the buzzer radiation showing a peak about 30 kc. wide which can be detected at a distance of twenty to thirty feet from the antenna with the average communications receiver. The higher the "Q" of the antenna being excited, the sharper will be the noise peak.

It is best to make the test at a

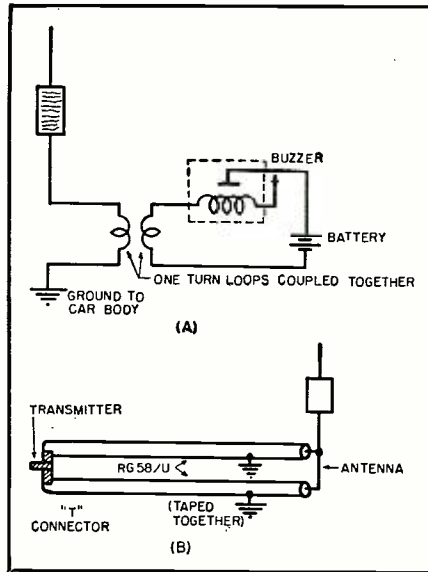


Fig. 1. (A) Method of using a buzzer to determine resonant frequency of a mobile antenna. (B) The use of paralleled 52-ohm coax cables to improve impedance match.


time when the frequencies involved are relatively quiet, otherwise strong QRM may mask the noise peak. To prevent detuning, short leads should be used at the base of the antenna. An extra two inches in the form of a single-turn loop will provide sufficient coupling.

Feeding the Loaded Whip

Antennascope measurements on a number of base- and centerloaded 75 meter whips show that the base impedance of these systems is very close to 25 ohms. Although 52-ohm coax can be used as a feed line, a much

* Henney, Keith: "Radio Engineering Handbook" (4th Rev. Ed.), chap. 14, p. 613.

Fig. 2. Circuit diagram of an additional i.f. stage for the car's broadcast receiver to improve over-all selectivity. Unmarked condensers are in the i.f. cans.

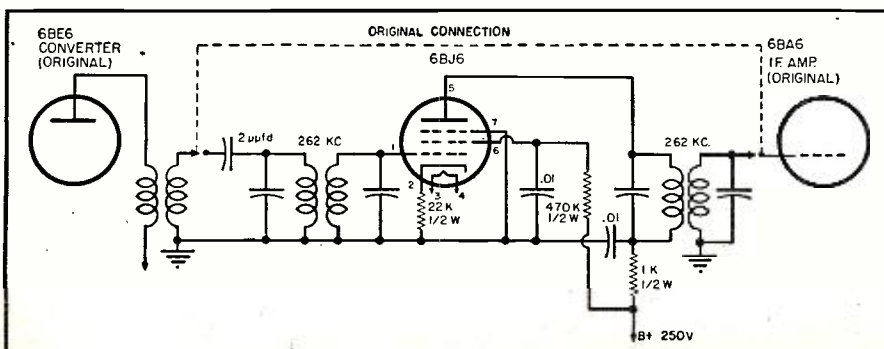

better match can be obtained by using two sections of small diameter RG-58/U (53.5 ohms) in parallel.

A neat job can be done by taping the two sections of line together and using a "T" coax fitting at the transmitter end, as shown in Fig. 1B.

Improving Receiver Selectivity

The usual converter-car receiver combination used for mobile reception leaves much to be desired from the standpoint of selectivity, especially on the lower frequency bands where considerable activity is encountered. Aside from the common deficiency of poor station separation, the poor selectivity causes loss of gain on weaker signals, because a.v.c. action on a strong adjacent carrier decreases the sensitivity of the receiver over a relatively broad spectrum. Since adjacent-channel attenuation is primarily a function of the i.f. bandwidth in the car receiver, considerable improvement can be made by sharpening the skirt selectivity in the i.f. amplifier in "Q-5'er" fashion by the insertion of additional tuned circuits.

Such a modification is not nearly as complicated as it sounds or looks, and it will be found that quite a few of the modern automobile receivers now have ample room for the additional components required.

Fig. 2 shows the circuit added to a 1950 Philco receiver in the author's Studebaker. Two additional midget i.f. cans (four tuned circuits) were added between the mixer and i.f. amplifier tubes, together with a 6BJ6 amplifier tube. There was sufficient room inside the set to mount these components alongside the i.f. amplifier stage without crowding.

With the circuit values shown (265 kc. i.f.) the gain of the 6BJ6 stage is held down to 1.5 times because all that is desired here is sufficient amplification to make up for the insertion loss of the additional transformers. It is necessary that the suppressor of the 6BJ6 be grounded rather than being connected in usual fashion to the cathode. With the high value of cathode resistance used, the tube cut off completely until this change was made. Total cathode current of the 6BJ6 is less than two milliamperes, and the heater current was gotten "for free" by disconnecting one of the two dial lamps.

You will have to take the usual precautions in installing the extra stage to avoid oscillation in the i.f. system of the set.

After the modification is made, a complete i.f. alignment (preferably visual alignment with a sweep generator and scope) should be carried out. When you put the set back in operation you will find that you can sneak up a lot closer to the strong ones to copy those "S3" signals that were formerly "snowed under." The additional stage gives a healthy improvement with practically no increase in power consumption.

McGEE OFFERS YOU TERRIFIC VALUES IN T.V. BOOSTERS—AMP'S AND KITS

GENUINE STANDARD COIL T.V. BOOSTER \$10.95

Not Surplus, But Right From the Factory

Latest Model B-51 Standard Coil Television Booster. McGee makes another lucky purchase and as a result passes the saving on to you. The famous Model B-51, 12 Channel Standard Coil TV booster, which lists for \$35.00, is offered to you for only \$10.95 each. Brand new, factory cartoned and fully guaranteed by McGee. This top quality single stage booster utilizes printed high frequency circuits, for improved performance on all channels. Uses 6AK5 tube. Average gain, 6 to 10 volts on low channels and 5 or 6 on high channels. No distortion of picture or sound. Has extremely low noise factor. Continuous one-knob tuning and channel selector control switch for on-off and by-passing 300 ohm lead-in to set. Modern design. dark plastic cabinet. net. \$8.44 1/2. Sale price, \$10.95 each, or buy 2 for only \$20.00.

14-Inch Conversion Kit \$25.95 WITH G.E. TUBE

14-inch conversion kit. You get a 14-inch black face, 1 year guarantee G.E. 14CP4 picture tube, a 70" deflection yoke with matching 14,000 volt G.E. flyback and a 14 plexiglas gold trim safety mask, plus conversion instructions. Stock No. 14CC-G. Sale price, \$25.95.

20-Inch Conversion Kit \$29.95

Our 20" conversion kit includes a 6-month guarantee G.E. 20HP4, 20" rectangular blackface picture tube, plus a 14,000 volt G.E. built high voltage fly-back transformer, plus a 20" rectangular gold trimmed plexiglas mask and suggested diagram. The picture tube is the latest electrostatic focus type that requires no focus coil. Shipped via express or truck only. Ship. weight 40 lbs. Stock No. 20HP-G, net price, \$29.95. Price with Raytheon or GE 1 year guarantee picture tube, \$10.00 extra.

17-INCH CONVERSION KIT \$25.95

17-inch conversion kit with a 17BP4A, 17" rectangular blackface electro-magnetic focus picture tube with 6 months' guarantee, plus a matched 70" cosine yoke, a G.E. built 14,000 volt flyback and a 17" rectangular gold trimmed plexiglas mask and safety shield. Suggested diagram furnished. Shipping weight, 30 lbs. via Express or Truck only. Stock No. 17-4XL, 17" conversion kit. Sale price, \$25.95. Kit with GE or Raytheon 1 year guarantee picture tube, \$5.00 extra.

SPEAKER AND BAFFLE SALE 8" SPEAKER AND BAFFLE \$4.95

Stock No. 818, Tan leatherette covered, plywood slant type baffle; plus an 8" Oxford, 2.15 oz. Alnico 5 magnet PM speaker. A red hot McGee special for only \$4.95 each, or \$4.70 each in lots of 3 or more.


12" SPEAKER AND BAFFLE \$7.95

Stock No. CA-12. Tan leatherette covered plywood slant type wall baffle; plus a 12" Quam, 4.64 oz. Alnico 3 magnet PM speaker. (Popular Adjastune model.) A terrific McGee value for only \$7.95 each, or \$7.50 each in lots of 3 or more.

10" SPEAKER AND BAFFLE \$6.95


Stock No. CA-10, Tan leatherette covered plywood slant type wall baffle; plus a 10" Permaturex, 3.16 oz. Alnico V PM speaker. Only a few hundred to sell at \$6.50 each, or \$6.25 each in lots of 3 or more.

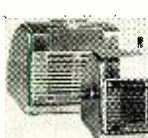3 STATION INTERCOM MASTER \$16.95 SUB STATION \$3.95



3-station intercom master housed in chrome plated metal cabinet 7 1/2"x8"x5" sloping front. Full 3-tube amplifier for 110 volt AC-DC operation. Press-to-talk switch is on top of the cabinet and volume control with on-off switch and station selector switch are on either side. May be used with from one to 3 sub-stations. (See matching cabinet chrome plated sub-station No. PM-A5. Master is quiet at all times except when press-to-talk switch is pressed at the master or call-back switch is pressed at the sub. Uses 3-wire intercom cable. 3-station intercom master, MP-A-A, shipping weight 10 lbs. net price, \$16.95. Price with sub-stations extra. 3-wire plastic intercom cable, 100 ft. for \$1.95, 500 ft. for \$8.95.

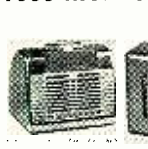1000 INTERCOM SUB-STATIONS TO SELL AT \$3.95 EACH



Chrome plated, with call back switch for a 3-wire intercom master. Size, 7 1/2"x5"x5" sloping front. 5" Alnico V PM spkr. Intercom dealers buy at less than present production costs. Limited quantity. Stock each of 3 for \$10.00. Special 3-wire plastic intercom cable, 100 ft. \$1.95, 500 ft. for \$8.95. Brown leatherette covered intercom sub-station with call back switch for use with 3-wire intercom masters. 5" square and 2 1/2" deep. Has new plastic grill cloth, Alnico V PM speaker. A true McGee value. Stock No. NE-3, shipping weight, 1 1/2 lbs. Sale price \$3.95 each or 2 for \$10.00. 3-wire plastic intercom cable, 100 ft. for \$1.95, 500 ft. for \$8.95.

FRINGE AREA TV RECEPTION IS BETTER WITH OUR McMURDO SILVER TV BOOSTER \$10.95—TWO FOR \$20.00

Read the article on pages 32 and 33 of the December "Radio & TV News." You will see how a booster like the McMurdo Silver Super Sonic was used for fringe area TV reception. We can't guarantee this unusual reception, but we will guarantee this booster to be a sensational value. Continuous inductance type tuner from channel 1 including the FM band through channel 13. Self-powered for 110 volts AC operation. It incorporates a 6J6 tube. Input for 300 ohm TV line and 300 ohm output to TV set. Single knob tuning. Attractive plastic case. McMurdo Silver Super Sonic TV-FM booster, Stock No. GB-6B, shipping weight 5 lbs. Sale price, \$10.95 each or two for \$20.00.

3-TUBE SARKES-TARZIAN T.V. TUNER \$9.95

This popular Sarkes-Tarzian Type 3 tuner is widely used. 13 channel rotary type switch with individually tuned coils. Gives 30 watts of audio. Complete with diagram and the tubes: 6C4 osc., 6BH6 R.F. and 6AG5 mixer. Regular factory cost is twice our price. Each tuner is wired ready to hook up to a video and sound IF strip. The two variable controls, for remote control or separate sound IF circuits. Has built-on converter coil, built in fine frequency control. Sarkes-Tarzian TV tuner, with 3 tubes. Net price, \$9.95 each. Specify shaft length, either 2 3/4" or 4 3/4".

50-WATT BOOSTER AMPLIFIER \$39.95



50-WATT BOOSTER AMPLIFIER. 2-Mike Pre-Amp \$12.95 Extra. Not a Kit, but a Manufactured Amp. 50-WATT BOOSTER A sensational value. 50 watt booster amplifier with push-pull parallel 6L6 output tubes. Connect to your present amplifier as a booster or use with the PR-2X Pre-amp to add the use of 2 mikes and gives 30 watts of audio. Booster has a 6 lb. potted case high fidelity output transformer, matches speaker with 4-8-16 ohm voice coil, also 60 ohm and 250 ohm line. Booster has a 225 mill power supply with 5U4 rectifier. Price includes tubes: 4 6L6, 7N7 and 5U4, 8 x 6 1/2 x 14 1/2. Stock No. PA-55N. Shipping weight 26 lbs. Sale price \$39.95 ea.

2-MIKE PRE-AMP. \$12.95

Pre-amplifier plugs in directly to the PA-55N Booster amplifier. It enables use of Crystal or Dynamic Mikes plus one low level input. Furnished with 4 foot cables and plugs for remote control of the 55 watt Booster Amplifier. Small chassis size 5 x 3 1/4 x 4". Stock No. PR-2X, with tubes 7F7 and 7N7. Net price \$12.95 ea.

McGEE'S \$62.50 LIST 15" COAXIAL SPEAKER, \$23.95



New 1953 Model—21 Oz. Alnico V Magnet—5" Tweeter. This is the finest 15" coaxial PM speaker ever offered. New 1953 production, of a famous manufacturer of fine speakers. The 15" speaker has a 2 1/2 oz. Alnico V magnet, equal to 68 oz. of the Alnico 3 type magnet, the cone is free floating, one piece construction, will reproduce low frequencies down to 20 cps. The 5" tweeter is coaxially suspended and has a ridged cone to reproduce only the high frequencies. It will respond up to 17,500 cps. The high-pass filter is concealed under the pot cover, leaving only two wires to connect both the tweeter and woofer to any 8 ohm output transformer of a radio, or high fidelity music lover's amplifier. Stock No. R-136C, shipping weight 13 lbs. Net price, \$23.95.

12" JENSEN PM, \$15.95



Another McGee Scoop! Jensen Co. 12" Alnico V magnet PM speaker. 8 ohm voice coil. Will take 25 watt audio. You save dollars on this speaker. Just 100 to sell. Shipping weight 8 lbs. Stock No. P-12P. Sale price \$15.95; 2 for \$30.00.

G.I. 3-SPEED CHANGER WITH G.E. \$22.95



VARIABLE RELUCTANCE TURN-ABOUT CARTRIDGE. Another tremendous McGee Scoop! Brand New General Instrument chassis for use with 45. Complete with RPX-050 G.E. variable reluctance changer with turn-about stylus. Plays all 3 speeds automatically: 7 1/2, 15 or 30 cps. Has reject button. Repeats last record. Base size 12" x 12 1/2". Shipping weight 14 lbs. Stock No. 700-G. Scoop price, \$22.95.

GI 3-speed changer same as above, but with Webster flip-over twin needle cartridge. Stock No. GI-700. Sale price, \$21.95 each.

COMPLETE RADIO, TELEVISION AND AMPLIFIER KITS AT McGEE

3-WAY PORTABLE KIT \$15.95



New 1952 Model 3-way personal portable radio kit. Operates on 110 Volts AC-DC or 67 1/2 B conventional 2-gang superhet circuit with 450 KC iron core IP's. Incorporates the new super gain slide loop antenna. All plated chassis. Price includes all parts, tubes, diagram, Alnico V PM speaker, factory quality kit. Stock No. PN-4T. Shipping weight 7 lbs. The complete kit, less batteries, \$15.95. 67 1/2 V, B, \$1.59; 1 1/2 V, A, 29c extra.

8-Tube Hi-Fi Amplifier Kit \$29.95



A complete kit, including tubes 6X4, 6X5, 12AX7, 2-triode plus rectifier diagram and photos. Inputs for radio tuner and any kind of phono pickup or G.E. variable reluctance and either crystal or dynamic mike. Output matches 8 ohm voice coil. Selects treble and treble tone controls with range selector switch for either juke box quality with heavy bass response or brilliant symphonic range. Response 18 to 20,000 cps. 8 tube all triode amplifier kit, complete with tubes. Shipping weight 25 lbs. Model TX5. Net \$29.95.

10-TUBE RADIO KIT \$29.95



10 tube broadcast radio chassis for use with complete kit with tubes: 6-6SK7, 6-6SN7, 1-6SL7, 2-6V6 plus 5Y3 rectifier, diagram and instructions, 3 gang superhet with 8" slide rule dial. Chassis size, 12 1/2"x10"x6 1/2" high. Features matches 3 to 8 ohm voice coil speakers. Inputs for G.E. variable reluctance or crystal or dynamic mike. Heavy duty power transformer. Model BK-10 kit less speaker, shipping weight 18 lbs. Net \$29.95.

6-TUBE 2-BAND KIT \$14.95



Popular with schools and amateurs for training. 6 tube AC-DC, 2 band radio kit with plastic cabinet. Receives broadcast and 6 to 18 mc shortwave. Full 2 gang superhet with 5" speaker and a slide rule dial. Complete kit with tubes: 12SK7, 12K8, 12SK7, 12SQ7, 50L6 and 3Z5, diagram and instructions. Factory quality. Cabinet size 13"x8 3/4"x6 1/4". Shipping weight 12 lbs. Model MB-2. Net \$14.95.

5-TUBE AC-DC KIT \$12.95

Model RS-5. A 5 tube AC-DC straight broadcast kit, housed in the same cabinet as Model 2 above. Complete kit with tubes. Shipping weight 10 lbs.. Net \$12.95.

AG POWERED BROADCAST TUNER KIT \$12.95



A self-powered, 3-gang superhet tuner kit with R.F. stage. This complete kit is furnished with a diagram, photos and tubes. 6BA6 R.F., 6BE6 oscillator, R.F., 6BA6 LP detector, 6AL5 diode, AVC, plus rectifier. Connect to any audio amplifier. Ideal for use with our S-2020 or 7x5 amplifier kits. Chassis size 9 3/4"x4 1/4" high. Shipping weight, 7 lbs. Broadcast tuner kit Model BT-38X. Net price, \$12.95.

17, 20" T.V. Kit \$59.95 Less Tubes

A complete kit of parts to build an AC transformer operated television chassis for use with a 16", 17" or 20" rectangular picture tube. The 12 channel Sarkes-Tarzian tuner is ready wired. Includes the 4 tube video IF strip. Circuit is of the conventional design. Do not buy this unless you understand television. It is difficult to wire. We furnish schematic. Kit model with 20" ship. wt. 40 lbs. less 21 tubes. Net \$59.95. Cascode tuner \$10.00 extra! 12" speaker \$2.95 extra. Kit of 22 tubes and picture tube \$16.95. 17 1/2 BP4A, \$19.95. 20HP4, \$25.00.

Build Your Own Phono-Mike Broadcaster \$7.95



Kit Model DE-6R. With this simple kit, you can build a 3-tube phono oscillator that also has a mike input. Will broadcast over any radio, within your home, (about 75 feet) from 1000 to 1500 kc. Inputs for crystal mike or crystal phono pickup. Folder control, feeds from mike to record. Ideal for a home P.A. system, baby listener and home entertainment. A complete kit of parts including tubes. Kit Model DE-6R. Net price, \$7.95. DE-6RWT, wired and tested. Net price, \$9.95. Crystal mike and desk stand, \$4.95 extra. Concealed microphone unit, only 1" in diameter and 1 1/4" thick. Specify hidden mike when ordering. Stock No. T-001. Net, \$3.95 extra.

WRITE FOR McGEE'S 1953 CATALOGUE


56 PAGES OF BARGAINS—EVERYTHING FOR THE TELEVISION AND RADIO SERVICE MAN. UP TO DATE UHF TELEVISION MATERIAL. WRITE FOR YOUR COPY TODAY.

McGEE RADIO COMPANY

TELEPHONE VICTOR 9045. WRITE FOR FLYER 1422 GRAND AVE., KANSAS CITY, MISSOURI

August, 1953

South River ★★ NEWS ★★

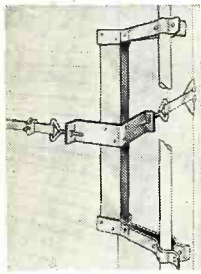

CHIMNEY UNI-MOUNT Model UM-1


Riveted, heavy-gauge, galv. steel with wide, flared-lip, snap-in mast holders. 18" spacing be-

tween mast holders for firm support. Available with one heavy-gauge stainless steel strap, Kwik-Klip banding closure and Chimney Corner Guards. Model UM-2 . . . same as UM-1 with 2 heavy-gauge stainless steel straps.

Write for our new 1953 catalog
In Canada—A.T.R. Armstrong Co., Toronto

**SOUTH RIVER METAL
PRODUCTS CO., INC.**
SOUTH RIVER, N. J.

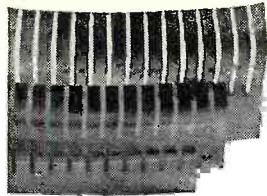PIONEER AND OUTSTANDING PRODUCER
OF FINEST LINE OF ANTENNA MOUNTS



FINGER STOCK

**Electrical Weather-Stripping
by Eimac —
Now Available!**

Silver-plated, spring alloy, pre-formed finger stock especially suited for electrical "weather-stripping" for TVI-proofing cabinet access doors, etc. Also ideal for making coaxially constructed tube connections and many other uses. Available in 17/32", 31/32", and 1 7/8" widths.

- Write for new Eimac Catalogue Summary showing Eimac tubes and other accessories.

Eimac

EITEL-McCULLOUGH, INC.
San Bruno, California

International Short-Wave

(Continued from page 68)

1745-1800 closing. (Roberts, Conn., others) Good with news on these channels. (MacIndoe, N. J.)

Germany—Overseas Service from Cologne noted on 11.795 at 1400 to Africa; signed off with German, *English* announcements 1547. (Pearce, England) Heard on 6.270 at 0045 to North Africa. (Sanderson) Surprisingly good signal heard on 7.290 around 2130; news in German 0015-0025. (Lerch, Mass.) Has Mailbag Program Mon. 1400, 1800 on 11.795; 2130 on 6.270, 7.290; Tue. 0630 on 15.275, 1030 on 11.795. Correct reports will be verified by new card. The "Staatliches Rundunkomitee" in the Russian Zone operates Berlin I, 6.115, at 2330-1930; Berlin II, 7.150, at 2230-1930, and Berlin III, 9.730, at 2230-1900. (Radio Sweden) AFN, 5.740, Beyreuth, noted in Sweden 1200 with jazz music. (Malmo DX-aren, Sweden)

Gold Coast—ZOY, 4.915, Accra, shortly will increase power to 20 kw. (Fox, N. Z., via Radio Australia)

Greece—Radio Athens, 11.718, noted around 1240 in *English*. (Mast, N. Y., others) Central Forces Radio Station, 6.33, Athens, seems nearer 6.34 lately, noted 1330 with call in Greek, then Greek music; also heard 0100 with Greek songs. Larissa, 6.745, noted 0115 with popular music. (Pearce, England)

Guadeloupe—FG8HA, 9.430V, Basse-Terre noted 1810 in French; closes 2000 with "La Marseillaise." (Cox, Dela.) Heard also erratically 0600-0630 closedown. (Stark, Texas, others)

Guam—KIJ39, 9.490, noted *testing irregularly* around 0250. (Hooker, Alberta)

Guatemala—TGWA noted opening 0730 on 9.760 (rather than old 15.17 outlet.) (Ferguson, N. C.) If not found on 9.760, try 15.17.

TGCQ, 9.702, noted around 2315 at weak level. (Cox, Dela., Stark, Texas) TGNA lists frequencies of 720 kc., 5.9525, 9.668, 11.850, 15.100 (*inactive*), 17.870 (*inactive*). (Carroll, Me.)

Haiti—4VEH, Cap Haitien, noted 0600-0900 on 9.69A, mostly *English*. (Middleton, Ohio) 4VCP, Cap Haitien, is now back on 6.993, modulation is still poor. (Robbins, Ind.) Radio Haiti noted recently parallel on 10.06A, 5.84 with *English* in progress at 2146 tune-in; continued with U. S. popular music until 2221 closedown. (Gay, Calif.)

Holland—Hilversum, 11.730, noted with music 1700-1725, then short newscast prior to 1730 closedown. (Wade, Fla.)

Honduras—HRP1, San Pedro Sula, has moved from 6.351 to 6.360 where it mixes badly with Lisbon around 1800. (Robbins, Ind.)

Hungary—Budapest, 11.910, noted in *English* 1800-1815. (Zerosh, Pa.)

Iceland—TFJ, 12.175, noted Sundays *only* in its 1115-1130 session in Icelandic; CWQRM, QSB. (Cox, Dela.)

BARGAIN! RCA 15" HI-FI SPEAKER



**REGULAR LIST \$82.50,
DESIGN BY DR. OLSON!**

Biggest buy in a quality 15" coax we've ever seen!
40-12,000 cps, 25 watts, 2 lb. magnet, 16 ohms,
x-over 2000 cycles, duo-cone. Order No. R-5108RN.
Ship. wt. 16 lbs.

\$29⁵⁰

CLOCK-TIMER 29% OFF!

Famous-make \$5.50 switch-timer clock, all knobs on front. Turns radios etc. on up to 12 hrs., tells time. New! Complete! Order No. R-5105RN Ship. 1 1/2 lbs.

\$3⁹⁵



Reg. \$12.50 DIAMOND-TIP 3-SPEED NEEDLE, \$4.98!


Fits ANY thumb-screw or set-screw cartridge! Guaranteed! Order No. R-5097RN.

Going, Going, GONE

Just a few left! Stancor ST-203-A mobile transmitter kits, reg. \$47.50 net less tubes. Sale price \$36.50, Order No. R-5107RN. Hurry! Wt. 10 lbs. Kit of 5 tubes: order no. R-5096RN, only \$6.15.



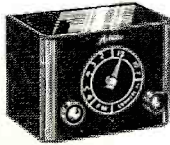\$29.95-LIST ASTATIC TV/FM BOOSTER, \$9.95!



Also makes hot R9er-type pre-selector on 2 meters! Built-in AC supply. Continuous 52-216 mc range! New, guar. model BT-1. Order No. 36-601RN. Wt. 5 lbs. Limited quantity!

OUR 225-PAGE 1954 CATALOG IS READY!

Rush copy to:

NAME _____

ADDRESS _____

STATE _____

FREE WITH ORDER of any item sold in this ad, a reg. \$1 child's unbreakable 10" record, 78 rpm. Must be requested in writing on your order. NOTE: include est. postage with orders; COD's must include 25% deposit.

RADIO SHACK

CORPORATION

167 Washington St., Boston 8, Mass.

Here's how to increase your Auto Radio Repair Business!



There's one sure way to get ahead in the car radio repair business, and that's to be in a position to tap the vast market of Delco Radio-equipped cars and trucks that daily passes your door! To do this you need only sign up with Delco Radio, through your United Motors Electronics Distributor. Then, automatically, you have a reliable source for Delco Radio original equipment replacement parts, and for universal replacement parts. You will regularly receive monthly issues of "Testing Tips," a bulletin giving the very latest factory information on testing and repairing Delco car radios. So if you want to increase your business—permanently—get on the Delco Radio team. Don't delay . . . contact your United Motors Electronics Distributor right away!

DISTRIBUTED BY
ELECTRONICS
WHOLESALEERS
EVERYWHERE

DELCO RADIO
DIVISION OF GENERAL MOTORS CORPORATION, KOKOMO, INDIANA

A GENERAL MOTORS PRODUCT   A UNITED MOTORS LINE




MOST POWERFUL FRINGE AREA CHASSIS THE NEW AIREX CO-CHANNEL "630 FA-2*" With Genuine Armstrong FM Sound System

The CHASSIS That Television Engineers and Servicemen Are Buying

FREE DELIVERY DURING AUGUST ON CHASSIS, CR TUBES & CABINETS

CHECK THESE EXCLUSIVE FEATURES

• 10 WATT push-pull audio output. Frequency range from 40 to 12,000 cycles • Standard Coil Cascade Tuner prevents radiation • Retrace Blanking Circuit allows you to raise the brightness without the annoying vertical retrace lines • Heavy duty front focus control • Automatic gain control potentiometer allows you to adjust the threshold sensitivity as low as 4 microvolts & still keep the full 4MC band width • Improved sync amplifier • Improved automatic brightness control • Set aligned for 21.9 MC. New Ham band will not interfere • Improved fused high voltage power supply gives full 14.5 KV under load. Will handle all picture tubes up to 24 inch with full sweep • Improved video amplifier has a gain of 40 • All moulded plastic condensers give long life & trouble-free operation • Easily adapted to new UHF stations in 2 minutes by just changing a strip in the tuner • Extra heavy duty power transformer with large safety factor • 6CB6 tubes in Video IF to give full gain • Extra filtering in power supply for hum & ripple-free operation • Phono Connection & switch on chassis allows you to play your phonograph or tuner through the built-in 10 watt hi-fidelity amplifier • Extra heavy duty focus coil, which runs cool • Full focus cosine yoke. Send for New FREE TV Parts & Hi-Fi Catalog

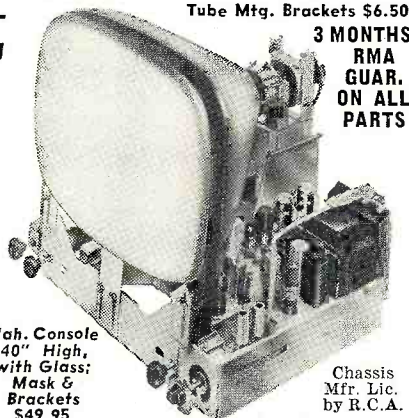

Mah. Console 40" High, with Glass; Mask & Brackets \$49.95

Tube Mtg. Brackets \$6.50
3 MONTHS RMA GUAR. ON ALL PARTS

Chassis Mfr. Lic. by R.C.A.

THE ONLY CHASSIS WITH PUSH-PULL AUDIO OUTPUT AT

\$169⁹⁵

Less C.R. Tube and Brackets

Complete with 12" ROLA Hi-Fi Speaker (Fed. Tax Incl.) Detailed Service Manual & Schematic—\$1

TV PICTURE TUBE SALE

Standard Brands • Factory New GUARANTEED 1 FULL YEAR

- 16" Tube. \$19.95
- 17" Tube. \$27.95
- Ring and Sleeve for 24" . . . \$7.50
- 20" Tube. \$34.95
- 21" Tube. \$39.95
- 24" Tube. \$79.95

TV GOLD PLASTIC MASKS

- 16" and 17" . . . \$ 4.95
- 20" and 21" . . . \$ 7.95
- 24" \$14.95

OVER 100 BARGAIN-PRICED CABINETS FOR TV & AUDIO INSTALLATIONS. Send for FREE folder and price list. Full line table models, consoles, consolettes and TV-Radio Phono combinations. Many styles, Mahogany, blonde, etc.

All merchandise is brand new, factory fresh & fully guaranteed. Mail & phone orders filled upon receipt of certified check or money order for \$25 as deposit on TV chassis. 20% on other items. Balance C.O.D., F.O.B. N. Y. Prices & specifications subject to change without notice. No Fed. taxes to pay. Prices lower than O.F.S. SHOWROOM: 171 Washington St., N.Y. 7, N.Y. Grammercy 7-9245 MAIL ORDER DEPT.: 400 Lafayette St., N. Y. 3

AIREX RADIO CORP.

MEASURE ALL

3!

- ★ FLUTTER
- ★ WOW
- ★ DRIFT



New, Sensitive FLUTTER METER

First Aid for the sound engineer — the ACA Flutter Meter! Accurate, sensitive instrument designed for rapid visual indication of flutter, wow, and drift content of discs (all speeds), sound film mechanisms, film recorders, and magnetic wire and tape recorders.

Three distinct and simultaneous readings may be made of flutter, wow, and drift. Large, sensitive 4" meter has three scales: 0.3%, 1.0%, and 3.0%, calibrated for flutter, wow, and drift readings. Accuracy within 2% of full scale value, independent of wave-form, amplitude variation, hum, noise, etc.

Flutter Meter complies with tentative standards set by Society of Motion Picture Engineers. Recommended for schools, labs, broadcast stations, recording equipment manufacturers, and studios.

Write today for circular 5036

AMPLIFIER CORP. of AMERICA
398 BROADWAY • NEW YORK 13, N. Y.

Electron

Tube

Technicians

We now have openings for work in the fabrication and processing of experimental electron tubes.

Applicants should be high school graduates with a natural aptitude for making small parts. Experience in electronics, precision machine work and experimental tube work is desirable.

Address resume of experience and training to

Hughes

RESEARCH AND DEVELOPMENT LABORATORIES

Technical Personnel Department
Culver City, Los Angeles County,
California

Indo-China (Vietnam) — Radio France-Asie, 6.116A, Saigon, noted 0600 with news in French; on 11.975 with news 2030. Hanoi, 7.405, noted 0630 with French program; is *Radio Hirondelle*. (Sanderson, Australia) Saigon, 9.750A, noted opening 0600 with "La Marseillaise;" heard on 11.935A at 1000-1115 at strong level. (Ishikawa, Japan) *Radio Laos* is heard at fair strength on 7.215 around 0830 to closedown 0923 with "La Marseillaise." "Voice of Vietnam," Saigon, closes down around 0958-1001 and then announces use of 9.620, 7.288, 4.969; however, latter is heard on 4.960A. (Japanese Short-Wave Club)

Iraq—Radio Baghdad, 11.725, noted around 2308 in Arabic. (Bellington, N. Y., others)

Israel—Tel Aviv, 9.010A, noted with "Voice of Zion" relay from Jerusalem 1515-1600 closedown; asks for reports to Box 754, Jerusalem, Israel. (Mast, N. Y.; Bjornert, Sweden, others)

Jamaica—Radio Jamaica verified 3.360 with QSL card in two colors—green and black. (Klein, Va., others)

Japan — The Far East Network (AFRS), Tokyo, is scheduled 1600-0645, JKL2, 9.605, JK16, 11.825; 0500-1000, JKL, 4.860, JK13, 6.080. (Scheiner, N. J.) JOA6, 15.135, JOA4, 11.705, noted opening in *English* to Western North America 0000. (Hooker, Alberta) JOA3, 9.675, heard 0600 with news. (Sanderson, Australia)

Luxembourg — Radio Luxembourg by now should have its *new* 50 kw. transmitter on the air on 6.090 at 0040-0930, 1045-1700 in French. (ISWC, London, others)

Madagascar — Radio Tananarive, 9.515, noted with interval signal 2229; signed on 2231 with "La Marseillaise."

Malaya—Forces Broadcasting Service, 5.010, Singapore, 7.5 kw., is scheduled 0645-0659 with tone; 0700-0730 Swahili, Chinyanja; 0730-0800 Fijian; 0800-0900 Gurka; *English* is to be added shortly. (WRH, others)

Mexico—XEHH, 11.880, very strong 1745 with call in Spanish. (Norman, N. C.)

Monaco — Radio Monte Carlo, 7.349A, noted closing 1800 (some days earlier). (Cox, Dela.)

Mozambique—CR7BJ, 9.768A, Lourenco Marques, still noted with *English* from 2300 opening (from 0000 Sun.). (Littlefield, Mass., others) Heard on 4.920AV at 1750 with popular music and *English* announcements; ended with Ted Lewis' "Goodnight Waltz" at 1800. (Cox, Dela.) Lourenco Marques, 4.872, noted with news in Portuguese 1500, then music, closing announcements after chimes and call, played "A Portuguesa" and signed off 1514. (Pearce, England) Heard signing on in Portuguese on 11.952A at 0000, weak level in Ind. (Niblack)

Nepal—Still uses 7.10 with *English* 0845-0900. (Etersvop, Sweden)

New Zealand—Heard closing 0625 on 9.540. (Middleton, Ohio)

Nigeria—Radio Nigeria is to increase power to 20 kw. shortly. (Fox, N. Z., via Radio Australia)

Norway—LLG, 9.61, Oslo, noted 2300-2400 (Sun. to 0020 Mon. with "Norway This Week" in *English*) to West Coast, excellent level. (Riggs, Balbi, Calif.) Channels that may be used during the year are LLQ, 21.730; LLP, 21.670; LLN, 17.825; LKW, 17.755; LLM, 15.175; LKV, 15.170; LLK, 11.850; LKQ, 11.735; LLH, 9.645; LLG, 9.610; LLD, 9.550; LKJ2, 9.540; LLR, 7.240; LLS, 7.210; LLI, 6.185; LKJ, 6.130; LKF, 1578 kc. (Hornstein, Mich.)

Pakistan—Radio Pakistan noted on 17.770 with news 0200-0210; in *English* 0515-0530 on 17.835. (Fernell, Sweden) Noted with news 0330 and Western music 0400 on 17.710; news 0730 near 17.750 now. (Pearce, England) Heard on 9.645A with *English* for Turkey 1430-1530 and to Britain 1530-1615. (Pearce, England, Bellington, N. Y.) Noted parallel on 11.885, 15.335 at 2035 tune-in with Hindu music for Southeast Asia. (Bellington, N. Y.) Heard opening 0630 on 15.27, 17.770, much native music. (Takemi, Japan)

Panama—HOLA, 9.505, Colon, noted recently 2200-2400 closedown. (Gay, Calif.) Heard in *English* 2130. (Hornstein, Mich.)

Peru—OAX4H, 6.307, Radio Mundial, Lima, noted with call in Spanish 2130. (McPhadden, Calif.)

Philippines—DZH3, 9.500, heard around 0700; uses commercials. (Stark, Texas) The Far East Broadcasting Co., Manila, reports that the two new 10 kw. transmitters—for use on 9.730, 11.855—are on order; one will be ready by this fall, the other several months later; a new transmitter on 21.475 is expected to be in operation within a year; higher power will be given all transmitters gradually. (Scheiner, N. J.) DZH9, 11.855, heard best in Alberta 1100-1200; noted closing 1203. (Hooker) DZ16, 17.804, noted 0130 with religious program in progress. (Sander-son, Australia) DZH2, 9.640, Manila, noted 0600 at good level in Tokyo with news. (Ishikawa, Takemi)

Poland—Radio Warsaw, 9.57, noted in *English* 1715-1800, strong signal. (Wade, Fla.)

Portugal—Emissora Nacional, Lisbon, is reported on three new channels in the 25-m. band—11.797, 11.760,



V-M 935HF Record Changer
\$59.95**
**all the music is all you hear!

triomatic® HIGH FIDELITY RECORD CHANGER

All the music is all you hear, with this superb instrument in your high fidelity music system. Every part of the handsome gold and burgundy V-M 935HF is produced with meticulous care to give you faithful, wide-range tonal reproduction, record protection and luxurious convenience.

IMPORTANT 935HF FEATURES

include: Exclusive aluminum die cast tone arm that is absolutely resonance-free! Two precision-made tone arm heads adaptable to most cartridges.* Laminated turntable and exclusive 4-pole, 4-COIL motor assure constant-speed operation . . . wow, hum and rumble are eliminated! Muting switch provides silent change cycle. Gentle tri-o-matic spindle eliminates record holders that grip the grooves. It lowers records to spindle shelf, holds them flat for silent, air-cushion drop to turntable. The automatic V-M 45 Spindle is included.

*Pre-amplification stage required

**Slightly higher in west

PLEASE MAIL THIS COUPON for complete, illustrated details of the magnificent 935HF high fidelity record changer.


V-M Corporation, Benton Harbor 4, Mich.
Please send me illustrated folder, "Bring Concert Halls Within Your Walls."

Name _____

Address _____

City _____ State _____

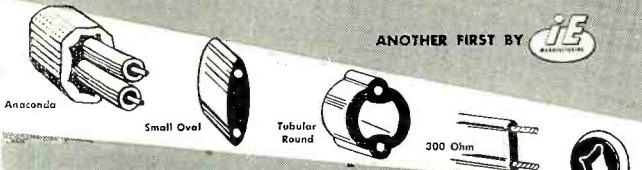REVOLUTIONARY NEW "UNIVERSAL-UHF-VHF" INSERT



ANOTHER FIRST BY **IE**

FITS 'EM ALL!

CUTS INVENTORY . . . SIMPLIFIES HANDLING!

Now, a new "4-in-1" polyethylene standoff insert that outperforms anything on the market! It's the versatile "UNIVERSAL-UHF-VHF" insert . . . product of **IE** "look ahead" planning and precision engineering. Functionally designed to carry the tubular cable, small oval, large oval and 300 ohm line. Available on all **IE** standoffs . . . will cut down your inventory and reduce your shipping problems!

OTHER OUTSTANDING **IE** STANDOFF INSERTS

UNIVERSAL
Designed for all VHF installations and the new open line.

LARGE CO-AX
Made specifically to carry the large round lead-in.



325 NORTH HOYNE AVE., CHICAGO 12, ILL.

ANTENNAS • MOUNTS • ACCESSORIES

Music Lovers and Professionals

RECOGNIZE THE INIMITABLE

MODEL 12A4
10 WATT



MODEL 10C4
30 WATT

Naturalness
IN SOUND REPRODUCTION



MODEL 7
SELF-POWERED PRE-AMP

AFFORDED ONLY

BY

BROOK

HIGH QUALITY
AUDIO AMPLIFIERS

Write today for complete technical data;
also name of nearest dealer. Dept. RI-3

BROOK ELECTRONICS, INC.

First in the High-Quality Audio Field Since 1934
34 DeHART PLACE, ELIZABETH, N. J.

11.835. (WRH) The 11.835 channel noted in Indiana at 1430. (Niblack) Signs on 1230. (Pearce, England)

Reunion—Radio St. Denis is heard in Sweden on 7.170 around 1625. (Radioklubben Universal, Sweden)

Saudi-Arabia—Djeddah now broadcasts on 725 kc., 3.960, 3.980, 5.975, 6.175, 7.245 at 2305-2335, 1045-1135, 1215-1335, and on 725 kc., 3.950, 5.975, 7.245, 11.850, 11.950 at 0605-0635. (WRH) (The 41-m. channel more recently has been heard around 7.300A instead of 7.245.) Noted by Pearce, England, opening with interval signal 1030 on 11.850A.

South Africa—Cape Town, 5.892A, noted 0110-0125 with morning produce market quotations in *English*. (Gay, Calif.)

South Korea—Radio Korea informs Scheiner, N. J., that the new 10 kw. short-wave and medium-wave trans-

mitters to operate as *Radio Seoul* are still under construction; the 9.555 outlet in Seoul is still 300 watts, and there is another outlet there—HLKA, 3.8925, 1 kw.

Spain—Madrid, 9.363, noted in *English* for North America 1800-1840. (Middleton, Ohio, others) Measured 9.359 recently. (Roberts, Conn.)

Switzerland—HED5, 15.120, Berne, noted 1145 with *English*. (Mast, N. Y.)

Tahiti—In verifying, *Radio Tahiti*, Papeete, listed FO8AA, 6.980, 200 w.; FZPS, 6.135, 1 kw. Both use half-wave antennas. (Kary, Pa.)

Thailand—Bangkok, 6.240, heard with news by man 0515; 7.105 heard 0700 when identified in *English*.

Trinidad—Radio Trinidad, 6.085, noted 0515 when identified. (Stark, Texas) Heard closing 2202 with "God Save the Queen" on 3.275; good level, slight heterodyne. (Cox, Dela.)

RCA'S PRINTED-CIRCUIT COMPONENTS

THE tube department of Radio Corporation of America has announced the development of a series of printed-circuit components which is expected to stimulate the production of more compact and efficient radios, TV sets, and communications gear.

These new components—six 40 mc. i.f. transformers, coils, and traps—are produced by a special photo-etching process which makes possible virtually limitless production of identical electronic circuits from a single photographic negative.

Conventional inductors depend upon coils of handwound or machinewound copper wire to provide the desired inductance values—the exact values are largely determined by the number of turns of wire, its spacing, and the diameter of the coil form. With the printed circuit method, both the copper wire and the wire-winding operations are


eliminated. Inductances are provided by flat inductors having rectangular windings which are photographically printed on copper-clad plastic strips.

Although these RCA printed-circuit components are intended for applications in home television receivers, the same photo-etching process can be used to print circuits for components used in a wide range of radio and communications equipment.

The new components are i.f. types designed for television sets utilizing intercarrier sound systems and incorporating picture i.f. and sound i.f. carriers of 45.75 mc. and 41.25 mc., respectively. The presently-available components include a first video i.f. grid-circuit coil and trap; a first video i.f. plate-circuit coil; a second video i.f. grid-circuit coil; first and second video i.f. filter traps; second video i.f. transformer; and third video i.f. transformer.

-30-

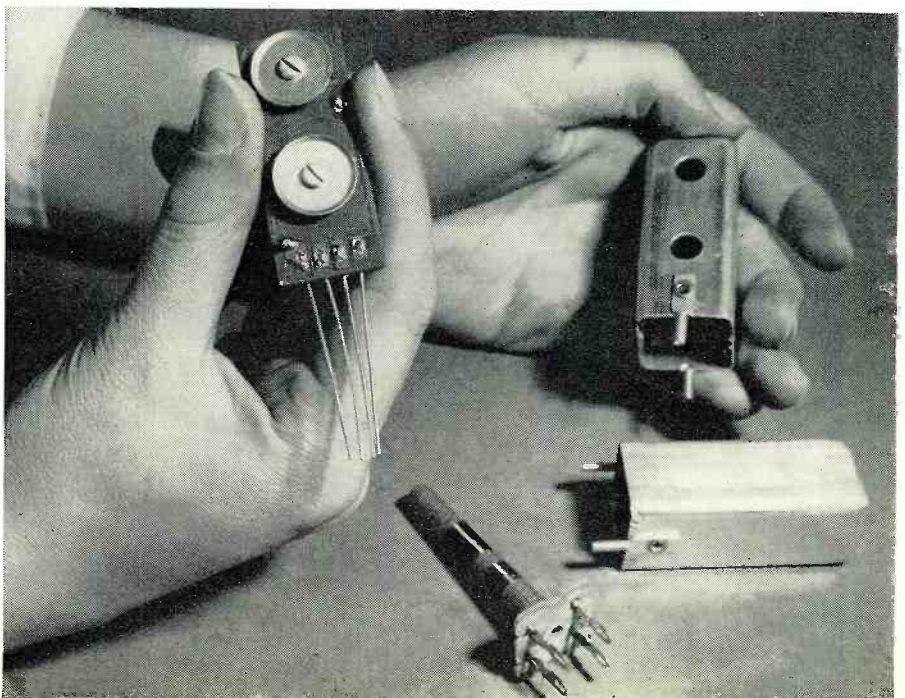RCA'S "Tandem" 40 mc. printed-circuit i.f. transformer used in home TV sets. A standard wirewound transformer is shown on table to permit a comparison of size.



TUBES & PARTS

Barga Catalog

ALL TUBES are guaranteed for one year . . . individually boxed. Very BEST BRANDS available for immediate delivery!

024	59c	246	89c	6AH6	1.89	6BH6	69c	6K5GT	69	6SQ7	59c	7C5	89	12AU7	79	12SN7GT	99	26	59c	57	79c
024C	79	2A7	89c	6AK5	1.08	6B16	69c	6K6GT	59	6SP7GT	59c	7C6	89	12AV6	59	12SQ7	99	27	59c	58	79c
1A5GT	79	2B3	89c	6AK6	1.08	6B17	69c	6K7GT	59	6SP7GT	59c	7C7	89	12AV7	59	12SQ7GT	99	28	59c	59	79c
1A7	69	2B7	89c	6AL5	1.08	6B18	69c	6K8GT	1.19	6SS7	79c	7E6	89	12AX4	69	1223	95	35C5	69c	71A	87
1A7GT	79	2C34	89c	6A16	1.19	6B19	69c	6K9GT	1.19	6S1G	95	7E7	89	12AX7	69	14A7	1.05	35L6	69c	71A	79
1B3GT	95	2E5	89c	6A16	1.19	6B19	69c	6K9GT	1.19	6S1G	95	7F7	89	12AY7	1.95	14A7	1.05	35W4	59	77	69
1B5	29	2X2/879	74	6A7Q	1.19	6B0GGT	1.19	6L6G	95c	6U5	69c	7F8	1.47	12BA6	59	14B6	1.05	35Y4	99c	78/6D6	1.10
1B5GT	59	3L4	1.25	6AR5	79	6B0T	69c	6L7	1.19	6U6GT	69c	7G7	1.19	12BA7	1.19	14B8	1.05	35Z3	99c	79	69
1B6GT	304		69	6AT6	59	6B27	1.29	6L7	1.19	6U7G	69c	7G8	1.19	12BE6	69c	14C5	1.25	35Z5	75	80	69
114	69c	305GT	89	6AS5	90	6C4	59	6N7GT	1.19	6U8	69c	7H7	1.05	12BF6	69c	14C5	1.25	35Z5	75	83	1.45
116	1.19	354	69	6AUSGT	1.29	6C5GT	69c	6P5GT	89	6V3	1.29	7I7	1.19	12B7	69c	14C7	1.12	35Z5	75	84/6Z4	.72
11A4	1.19	3V4	45	6A16	1.19	6D6	69c	6Q7GT	59	6V6GT	69c	7J7	1.19	12B7	69c	14F7	1.05	35/51	79	85	.79
11C5	69	5U4G	59	6AV6	59	6C8	1.29	6S4	59	6W6	69c	7Q7	79	12B7	69c	14F8	1.45	36	1.06	85	.79
11C6	59	5V4G	87	6AX4	59	6C0D6	2.49	6S7GT	1.15	6X4	59c	7Q7	79	12C5GT	65	14Q7	1.12	37	93	VR90	
11D5	1.19	5W4	59	6AX5	79	6C0D6G	1.69	6S8GT	1.25	6X5GT	69c	7R7	1.19	12H6	89	14Q7	1.19	39/44	72	VR105	\$1.19
11E3	1.19	5W4GT	45	6AV5GT	89	6D6/78	1.10	6S7GT	69c	6X6	69c	7R7	1.19	12J5GT	71	14K7	1.19	41	69	VR150	
11M4	1.19	5Y3GT	45	6AV5GT	89	6D8G	1.15	6S7GT	69c	6V6G	69	7V7	1.19	12K7GT	69	19B6G	99	42	72	VT51	
1R5	1.19	5Y4G	54	6B4G	1.44	6E5	69	6S07GT	99	6Z4/84	72	7W7	1.19	12K8	89	19B6GG	1.89	43	72c	117L7	1.40
1N5LT		5X4G	69	6B8GT	1.15	6F5GT	59c	6S7GT	69	6Z5GT	59	7A4	59	12S7GT	89	19T8	89	45	69	117N7	1.95
1P5GT	79c	5Z3	69	6BA6	59	6F6GT	59c	6S7GT	69	6Z5GT	59	7A5	1.19	12S8	89	20A	1.40	45Z5	69	117P7	1.95
1Q6GT	69c	6A3	1.68	6BA7	89	6F7	1.59	6S7GT	69	6Z5GT	59	7A6	89	12S8	89	20A	1.40	45Z5	69	117Z6	1.95
1S4	69c	6A7	1.21	6B05	69	6F8G	1.51	6S7GT	69	6Z5GT	59	7A7	89	12S8	89	20A	1.40	45Z5	69	117Z6	1.95
1S5	99	6A8GT	69c	6B07	1.05	6G6G	95	6S7GT	69	6Z5GT	59	7A8	1.59	12S7GT	69	25B0G	1.19	50A5	1.05	117Z6	1.19
1S5	69c	6B07	1.05	6B05GT	89	6G6G	95	6S7GT	69	6Z5GT	59	7A8	1.59	12S7GT	69	25B0G	1.19	50A5	1.05	117Z6	1.19
1T4	69c	6B7	1.15	6B65	59	6H6GT	89	6S7GT	69	6Z5GT	59	7A8	1.59	12S7GT	69	25B0G	1.19	50A5	1.05	117Z6	1.19
1U4	69c	6AC5GT	89	6B75	69	6I5GT	59	6S7GT	69	6Z5GT	59	7A8	1.59	12S7GT	69	25B0G	1.19	50A5	1.05	117Z6	1.19
1U5	59	6AC7	1.45	6B76	69c	6J6	79	6S7GT	69	6Z5GT	59	7A8	1.59	12S7GT	69	25B0G	1.19	50A5	1.05	117Z6	1.19
1V	69c	6AG5	1.05	6B66	1.89	6J7G	69	6S7GT	69	6Z5GT	59	7A8	1.59	12S7GT	69	25B0G	1.19	50A5	1.05	117Z6	1.19
1X2A	89c	6AG7	1.49	6B66G	1.89	6J8G	1.15	6S7GT	69	6Z5GT	59	7A8	1.59	12S7GT	69	25B0G	1.19	50A5	1.05	117Z6	1.19

SPECIAL
For August only

Ask abo
Free elect
sign de

10% DISCOUNT
on orders of 100
tubes or more,
5% DISCOUNT
on orders of 50
to 99 tubes.

FREE

5 small screw-
drivers with
rotating handle
and handy case
with purchase of
\$20.00 or more.



Outdo
UHF anten
\$5.

TELEVISION PICTURE TUBES

SEND US YOUR ORDER AND WE WILL SHIP FROM STOCK IMMEDIATELY	SIZE	PRICE
	7 inch	\$17.95
	8 inch	\$19.95
	10 inch	\$21.95
	12 inch	\$23.95
	14 inch	\$25.95
	15 inch	\$27.95

METAL TUBES \$1.50 extra per tube
Electrostatic Tubes \$1.50 extra per tube

SIZE	PRICE
16 inch	\$19.95
17 inch	\$20.95
19 inch	\$23.95
20 inch	\$24.95
21 inch	\$26.95
24 inch	\$49.95
27 inch	\$69.95

These allowances apply when you purchase the same size picture tube and dud is shipped prepaid.

WE PAY FOR YOUR DUD

Your worn out picture tube is worth money if it is not broken.

Size	We Pay	Size	We Pay	Size	We Pay
7"	\$1.00	14"	\$3.00	19"	\$4.00
8"	1.00	15"	4.00	20"	4.00
10"	2.00	16"	3.00	21"	5.00
12"	3.00	17"	3.00	24"	9.50
		17"	3.00	27"	10.00

RADAR TYPE TV ANTENNA

For UHF and VHF RECEIVES ALL CHANNELS WE FINALLY DID IT

You ordered so many thousands of these radar type TV Antennas, that the cost has come down through the savings of mass production.

WE ARE PASSING THESE SAVINGS ON TO YOU!

The only TV antenna with the money-back guarantee with the new Electronic Dipole Separators. Unbeatable for fringe area and DX at this low, low price we cannot mention manufacturer's name.

\$18.75

5' ALUMINUM MAST heavy gauge 1 1/4" diam. with interlocking end. Slip two sections together for a ten-footer. **\$1.00**

TV Antennas

10 Element conical . . . rugged throughout. **\$3.95**

Double bay array, with stacking bars. **\$7.75**

4 Bay array, with harness and stacking bars . . . **\$14.95**

6 Element Conical. Only . . . **\$2.95**

JFD BOW TIE REFLECTOR

UHF Antenna
Bowtie Reflector
Ultra-high Gain

Completely assembled—ready to mount. For All Channels—easy to stack for two or four-bay.

Single Bay . . . **\$4.50**
Two Bay, complete. **\$8.45**



VTMV PRECISION

Vacuum Tube Volt-Meter, 1% accuracy precision resistors; Coax DC connector; FM zero alignment scale; burn-out proof circuit, rugged oversized 4 1/2" factory Model 909, factory wired \$44.98. 909K—Kit. **\$25.98**



Model 300
Precise Oscilloscope

Here Is the Buy

7" tube size, Sweep magnifier, complete push-pull input through output. Vertical sensitivity better than 10 milliVolts. Bandpass +0 —3db., 0 to FIVE mc, complete with phasing control, blanking control, intensity mod. and self-measurement peak to peak feature, with DC amplifiers throughout as found only in scopes selling for over \$950.00. Exclusive, easy maintenance feature.

In kit form ONLY **\$94.95**

Pictu
to
brighter
\$1.69

R
convert
All U
chann
\$29



12-COAXIAL PM SPEAKERS—High Fidelity
with crossover filter attached. 20 watts, 40,000 cps.
8 ohm Voice-Coil. ea. **\$12.95**

15-COAXIAL SPEAKER.
20-7,500 cps., ea. **\$19.95**
Very best quality—NATIONAL BRANDS.
Individually Packed.
5 . . . ea. \$1.39 10 . . . ea. \$3.22
5 . . . ea. \$1.59 10 . . . ea. \$1.10
5 . . . ea. \$1.59 12 . . . ea. \$1.95
6 SPECIAL PRICE . . . ea. \$1.79



TV CONVERSION KITS

Consisting of rectangular tube, 70 DEGREE YOKE, Beautiful Mask and FLY-BACK TRANSFORMER.

21" TV Conversion Kit, as above, complete. **\$31.95**
20" TV Conversion Kit, as above, complete. **28.95**
17" TV Conversion Kit, as above, complete. **23.95**
24" TV Conversion Kit, as above, complete. **69.95**
27" Conversion Kit, as above, complete. **89.95**

MISCELLANEOUS BUYS

I.F. TRANSFORMER—45 Kc 29c
PILOT LIGHTS, Type No. 47 10 for 99c; 100 for \$2.95
VOLUME CONTROLS with SWITCH.
2" shaft, 1 meg, 1/2 meg, 1/4 meg . . . 34c
SINGLE ION TRAPS . . . ea. 19c
DOUBLE ION TRAPS . . . ea. 28c
OUTPUT TRANSFORMER—for 50L6 for 6V6. . . 39c
CHIMNEY MOUNT for TV ant. . . \$1.29
6-foot LINE CORD UL . . . 10 for \$1.95
TV-INTERLOCK CORDS . . . ea. 49c

T
set anten
coupl
\$1.17

TUBE KITS

BEST BRANDS AT BEST PRICES

3V4, 1T4, 1R5, 1S5 **\$2.19**
3Q4, 1T4, 1R5, 1S5, List Value \$9.00. Tube Kit only **\$1.98**
354, 1T4, 1S5, 1R5, List Value \$7.80. 4-Tube Kit. **\$1.98**
1U4, 354, 1S5, 1R5, List Value \$7.60. **\$1.98**

All Four Tubes for
117Z3, 1U5, 354, 1R5, 1T4, AC-DC Portable Kit. All for **\$2.49**
12AT6, 12BA6, 12BE6, 35W4, 50B5. 5 Tubes for **\$2.59**
12S0GT, 35Z5GT, 12SK7G, 12SA7C. 5 Tubes for **\$3.22**



REGENCY UHF CONVERTER

UNIVERSAL-CONVERTERS ALL SETS—the only converter recommended for the 5,000,000 split sound and video TV sets now in use as well as all intercarrier TV sets. **\$37.46**

RESISTOR KITS

Insulated 1/2, 1 and 2-watt assortment of most used values, I.R.C. Ohmite, Stackpole, Speer, etc., 100 for **\$2.95**

300 OHM TWIN LEAD

55 Mil, 100 ft. \$1.59
1,000 ft. **\$3.95**
20 Ga, 80 Mil, 100 ft. **1.89**
1,000 ft. **16.95**

UNF TUBULAR 300 OHM LINE
1,000 ft. **\$34.50**
100 ft. **\$4.95**

Selenium Rectifiers
75 mil 79c
100 mil 89c
150 \$1.10
200 \$1.48
250 \$1.59
300 \$1.79
350 \$1.98
450 \$2.45

Flyb
Transfor
TV Horiz
output, univ
sal replacem
\$14,500
\$2.49

Telerin TV Wave Trap

For VHF Channels 2 through 13. Clears VHF picture, stops interference at once, 30 seconds to attach. ea. net **\$1.75**

"SERVICE SHORT-CUTS"

One highly successful executive once said that he spends an hour each day with his feet up on the desk doing nothing but thinking. While you don't have to go quite to this extreme, you can profitably spend an hour a day reading one of the many well-written books available that not only tell you how television sets operate but also what goes wrong with them and how they can be fixed. Why sweat out the same mistakes others have made when a little time spent reading can save you lots of time on difficult service jobs?

We have prepared a list of recommended books both for the beginner and the advanced technician. If you drop us a card, we will be happy to send you a copy free and without obligation.

70 deg
cosine y
with 4 le
and netw
\$2.95

TERMS: 20% DEPOSIT with order, balance C.O.D. ALL shipments F.O.B. Chicago. ORDERS LESS THAN \$5.00—\$1.00 SERVICE CHARGE. CABLE ADDRESS: CONTULAB. These prices supersede all previously advertised prices, subject to change without notice.



PREMIER RADIO-TV SUPPLY, division of CONTINENTAL CORPORATION
3239 West North Avenue, Chicago 47, Illinois • ARmitage 6-5550


Ind
UHF anten
\$7

UHF or VHF


Whatever the location, whatever the reception problems, the variety of types in the expanded AMPHENOL line insures top reception.

There is an **AMPHENOL**


antenna
for every
area

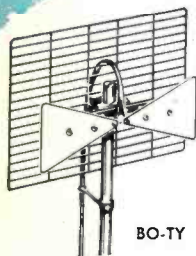

BO-TY

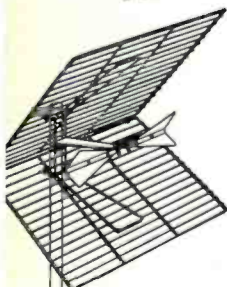

CORNER REFLECTOR

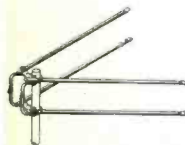


STACKED-V



YAGI



RHOMBIC

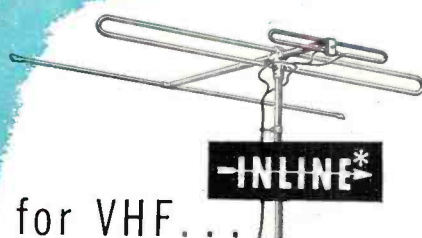

—INLINE*

for VHF...
For over four years the dependable INLINE has provided top viewing satisfaction to its users. With excellent gain and directional response, the INLINE is also available in a Stacked Array for additional gain in fringe areas.

for UHF...

BO-TY and Reflector. With its rejection of unwanted signals off the back and sides, the BO-TY is excellent for major signal areas. Where additional gain is desired in fringe areas, two BO-TYs can be easily stacked.

CORNER REFLECTOR. The high ascending gain and strong forward radiation pattern of the new CORNER REFLECTOR make this AMPHENOL antenna ideal for fringe areas. Of exceptionally sturdy construction, the CORNER REFLECTOR also has the advantage of being mounted in front of the mast to insure no signal interference from the mast or accessories.

STACKED-V. Reception of all television channels, 2 to 83 is provided by the STACKED-V. It can be adjusted to three angles: 70° for UHF/VHF, 50° for UHF and 90° for VHF. Gain is good to excellent at all three.

RHOMBIC. Another AMPHENOL antenna built to give the high gain needed for UHF in outlying districts. It also features rejection of ground reflections, an important consideration in UHF.

YAGI. There are 11 custom models of the YAGI for top reception across the entire UHF band. Each features extremely high gain on its assigned channels as well as a strong forward radiation pattern.

Turkey—Radio Ankara noted in *English* 1600-1645 now on 15.160 to Western Europe, Britain. (Golden, Mass., others) Still has powerful signal in *English* to North America daily 1815-1700 over TAT, 9.515. (Wade, Fla.; Oestreich, Wash. State, others)

Uruguay—CXA19, 11.835, Montevideo, noted 1715 at good level with music. (Cox, Dela.) CXA10, 11.909, Montevideo, is good level daily around 2100. (Norman, Ferguson, N. C.)

USI (Indonesia)—Djakarta, 9.710, strong with news 0900, 0945. (Hooker, Alberta) Heard opening 1400 after chimes on 11.785 to Europe-New Zealand; announces 9.710 parallel in this beam which closes 1500. (Pearce, England)

Western Samoa—By this time, Apia should have tested on 6.040 and (later) 3.241; probably will settle down on one of these channels and may follow the m.w. schedule of 1700-1900 Sun.-Wed.; 2200-2300 Sun.-Wed.; 0230-0600 Mon., Wed., Sat., 0230-0530 Fri.; 0330-0430 Sun. (Scheiner, N. J.)

Zanzibar—The Information Officer, Box 344, Zanzibar, informs Scheiner, N. J., there is one station operating in that country—"Sauti ya Unguja," 4.795, 250 w., 1000-1100 in Swahili only.

* * *

Press Time Flashes

Radio Somali, 7.125, Brt. Somaliland, is on the air 0815-0930; all-Somali language; transmitter is RCA type ET-4331 with nominal output of 1 kw.; uses half-wave dipole antenna. (Radioklubben Universal, Sweden)

Forces Broadcasting Service, Tripoli, has been noted around 1845 on 4.785; closes 1600A with "God Save the Queen." (Pearce, England)

More recently, **Radio Africa**, Tangier, has been using 7.193 again instead of 7.126; noted 1030 with popular music. (Pearce, England)

Damascus, Syria, has been noted recently on 11.725A around 1900-2100 closedown (parallel 11.913A), evidently to Latin America. (Niblack, Ind., Bellington, N. Y.)

HS8JS, Thai Army Radio, Thailand (Siam) is heard at fair strength 0630-0700 on 4.870; programs in Thai. (Cushen, N. Z.) ALF, 9.915A, Juneau, of the Alaskan Communications System, noted testing 2230 at excellent level. (Niblack, Ind.)

Ishikawa and Takemi, Japan, say **Radio Free Japan** is Red-Chinese operated, heard on 11.896 and 10.180 at 0800-0830 in Japanese; location is North Korea; strong level in Tokyo.

Radio Pakistan, 11.884A, lately has had news 2035A. (Ferguson, N. C.)

The new s.w. VOA relay station at Salonika, Greece, is scheduled on 6.040 at 1215-1645 to Europe; 7.270 at 0900-1645, 1730-0130 to Europe; 11.735 at 0900-1230 to USSR-Middle East. URDXC says is 35 kw.

Cairo, Egypt, noted on measured 11.966 around 1928-2046 closedown; seems parallel 6.085 (Ferguson, N. C.; Niblack, Ind.; Bellington, N. Y.)

At press time, Balbi, Calif., reported Peking, 6.20A, weak 0400 with news; 7.50 fair, 10.26 weak, 11.67A fair; 6.200 good level 0500 with Home Service. USSR heard to China from 0230 on 15.11, 11.72, 11.75, 9.725, 9.66, 9.545, 6.11, 6.055; signing off 0900.

Catch, England, flashed he had noted Lisbon, 9.742, opening to Brazil, Cape Verde Islands, Portuguese Guinea at 1600, excellent level; ZPA5, 11.950, Encarnacion, Paraguay, fair level 1645; ZYP23, 5.045, Petropolis, Brazil, fair 1725; a station, probably the *Yugoslav Emigrant Station*, noted opening with march 1720 on 6.283, and clandestine *Radio Espana de Independiente*, noted on 10.280 around 1730. And Niblack, Ind., noted CE1173, Santiago, Chile, at 1940-2030 on 11.945AV one day, next on 11.965A.

* * *

Acknowledgement

Thanks for FB reports! ISW DEPARTMENT monitor's certificates for 1953-54 are now available—*gratis* to all reporters to the Department. Send reports and requests for monitor's certificates to Kenneth R. Boord, 948 Stewartstown Road, Morgantown, West Virginia, USA. K.R.B.

AMPHENOL
AMERICAN
PHENOLIC
CORPORATION
Chicago 50, Illinois

NEW "PAY-AS-YOU-WATCH" SYSTEM

Boxoffice Television's new closed-circuit transmitter for TV makes possible retransmissions on Channels 2 through 13.

THE ever-mounting cost of television program sponsorship is causing more and more companies to cast a tentative eye at the various "TV-for-pay" systems which have been developed in the past few years.

Although not as yet sanctioned by the FCC, several companies are proceeding with the development of equipment to handle this type of transmission.

Among the new items on the market is *Boxoffice Television's* "Picturecaster", a unique closed-circuit transmitter for television pictures and sound.

The unit accepts video and audio from any source—a receiver, camera chain, coaxial line, generator, etc. and transmits them into any type of transmission line on any v.h.f. channel, 2 through 13. The transmitter frequency is crystal-controlled, with the sound and video carriers automatically maintained 4.5 mc. apart for best results with intercarrier receivers. AM pictures and FM sound are receivable on all standard TV sets.

The system as it operates now, in conjunction with master antenna systems, is inexpensive and easily installed and operated.

The audio and video are piped by a

Max Genodman, president of United Elco (a contracting firm specializing in hotel master antenna system installation), inserts the decoding key in the rear of a television set equipped to receive *Boxoffice Television's* closed-circuit TV.


Lee Bunting, treasurer of Bell Television, Inc. (a master antenna TV system operating firm), is shown with a demonstration set-up incorporating the new "Picturecaster" and the TV set with which it is employed.

common carrier (such as telephone company lines) to each master antenna system which is part of the network. These normal signals are then fed into the "Picturecaster" which scrambles the picture so that while it can be tuned in in the normal way it cannot be viewed.


The special decoder with which the receiving set is equipped consists of an inexpensive tube circuit, which is installed in one of the receiver's existing tube sockets, and a box with a keyhole.

To view an unscrambled picture, the user inserts the key in the keyhole and the picture comes in clear. Keys can be rented for various periods of time, the rental depending on the program material to be received. The key rental is the fee for watching the program. Removing the key scrambles the picture again so that a single key cannot be used to operate several receivers.

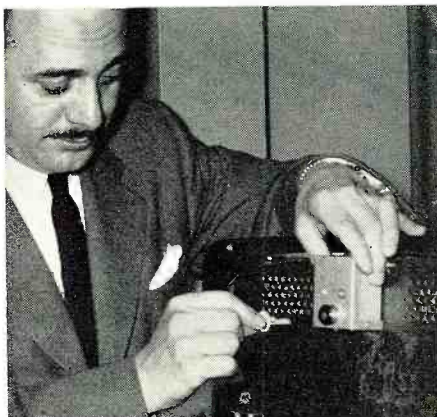The equipment is undergoing extensive testing at the present time in anticipation of an FCC OK on "Pay-As-You-Watch" programming. —50—



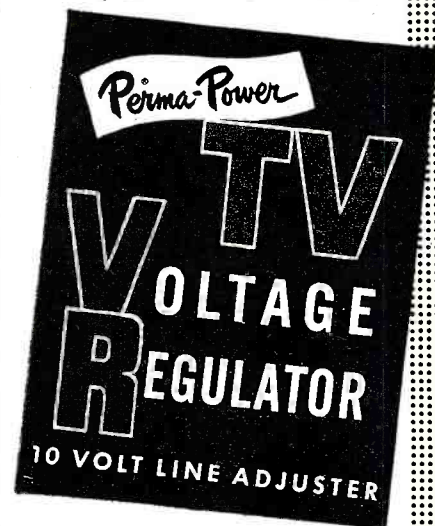there's always
something
new
being developed
by *Perma-Power*



- NORMAL LINE VOLTS
 - 10 VOLTS INCREASE
 - 10 VOLTS DECREASE
- 300 WATTS**

List Price
\$6.75

Sold Through
Better Jobbers

manufactured by
Perma-Power COMPANY
Chicago 25, Ill.
Manufacturers of Electronic Equipment Since 1928


"In music, listening quality is everything . . ."

1 It is the No. 1 MUST. Without it everything else becomes meaningless. The AUDAX CHROMATIC has that quality to a degree not equalled by any other pickup" . . . so says violinist David Sarsar, of MUSICIAN'S amplifier fame (Toscanini's NBC Symphony).

2 Be it diamond or sapphire, every stylus has a limited life-span; the diamond lasts the longer. Obviously, then, replaceability of the stylus—at home—is of the greatest importance.

3 But . . . only YOU can decide what sounds best to you. Therefore, See and Hear the Audax CHROMATIC and—You be the judge . . . yet Audax costs no more than ordinary magnetic pickups.

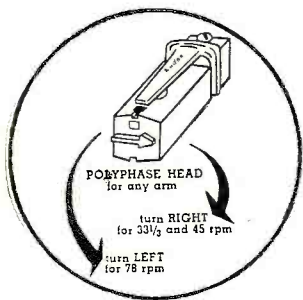ONLY AUDAX PROVIDES HOME REPLACEABILITY OF EITHER STYLUS, INDEPENDENTLY OF THE OTHER.



One single magnetic unit plays all home records

Available with the New Compass-Pivoted Audax arms and to fit the high quality record changers.

Ask for 1953 ELECTRONIC PHONO FACTS at your dealer

AUDAX COMPANY
500 Fifth Avenue New York 36

Creators of Fine Audio-Electronic apparatus for over 25 years

"The Standard by Which Others Are Judged and Valued"

MANUFACTURERS' LITERATURE

Readers are asked to write directly to the manufacturer for the literature. By mentioning RADIO & TELEVISION NEWS, the issue and page, and enclosing the proper amount, when indicated, delay will be prevented.

INDICATOR LIGHTS

Dialight Corporation, 58 Stewart Ave., Brooklyn 37, N. Y. is currently offering a copy of its new brochure, L-153.

This four-page publication describes and illustrates the company's line of subminiature indicator lights for various applications. Units described fall into five general categories: for plastic plate edge lighting, indicator lights, dimmer types, light shield, and indicator lights with "press-to-test" feature.

When writing for a copy of this brochure, address your requests to Mr. E. Greene of the company.

REPLACEMENT GUIDE

Standard Transformer Corporation of Chicago has prepared a "Tape-Wire Recorder Replacement Guide" which lists sixty-three models by twenty-two companies manufacturing tape and wire recorders.

The Guide has been published to meet the need for authoritative information on power transformer, filter choke, and audio output transformer replacements, according to the company.

Manufacturer and model number, manufacturer's part number and *Stancor* part numbers are listed for all models included in the Guide.

Distributors and service technicians may secure a copy of this guide by writing the company at 3580 Elston Avenue, Chicago 18, Ill.

CONVERTER AND BOOSTERS

Electro-Voice, Inc. of Buchanan, Michigan has issued a new bulletin covering its u.h.f. converter and v.h.f. booster line.

Features, specifications, and other details on these products are covered in Bulletin No. 182. Information on the company's 3300 u.h.f. converter, "Tune-O-Matic" and "Tenna-Top" boosters is given in detail.

U.H.F. BOOKLET

How its signal generators can be adapted for u.h.f. applications is the subject of a new booklet, "How to Use the *Simpson* 478-480 for U.H.F. Alignment", currently available from *Simpson Electric Company*, 5200 W. Kinzie Street, Chicago 44, Ill.

The booklet describes how the company's v.h.f. test equipment can be adapted for use in u.h.f. service work. By following the instructions given in the publication the technician can obtain signals of the type, accuracy, and strength necessary to identify the nature of troubles in u.h.f. circuits.

Copies of this booklet are available without charge from the company.

TRIAD TRANSFORMERS

The new catalogue just released by *Triad Transformer Corporation* of 4055 Redwood Avenue, Venice, California lists more than 500 items of interest to technicians.

The publication features an expanded line of TV components and industrial transformers including toroids, pulse transformers, transistor transformers, and additional miniatures. The catalogue also contains a geophysical section.

Copies of Catalogue TR-53 may be obtained by writing the company direct.

DISTRIBUTOR CATALOGUE

Dealers and technicians, in addition to the company's distributors, are currently receiving copies of the new 1953 *Mallory* distributor Catalogue No. 553, according to the company.

The new publication lists and describes more than 2200 items, mostly replacement components which are handled through the company's distributor system. For the first time the catalogue also includes list prices for the items covered.

A copy of this new catalogue may be obtained by writing to *P. R. Mallory & Co. Inc.*, 3029 E. Washington St., Indianapolis 6, Ind.

ANTENNAS AND ACCESSORIES

A 36-page catalogue of television antennas and accessories has been issued by *Radio Merchandise Sales, Inc.* of 2016 Bronxdale Ave., New York 60, N. Y.

The new publication covers all items necessary for receiver installation from the rooftop to the set itself. The catalogue contains a general alphabetical index which provides a logical breakdown of accessory categories which helps speed the location of the desired parts.

As a further aid to the technician for whom the catalogue is intended, *RMS* has included a technical data section. Copies of this publication are available from the company's distributors or from the company itself.

"GLASSEAL" CATALOGUE

A new 20-page catalogue covering its line of "Glasseal" condensers has been issued by *Pyramid Electric Company*, 1445 Hudson Boulevard, North Bergen, N. J.

Designated as Catalogue PG-3, the new publication contains complete en-

gineering data, performance curves, construction styles, sizes, capacitance, and voltage listings for the subminiature units.

Copies of this two-color catalogue are available without charge upon letterhead request direct to the manufacturer.

TUBE CHARACTERISTICS

The Receiving Tube and TV Picture Tube Divisions of *Sylvania Electric Products Inc.*, 1100 Main Street, Buffalo, N. Y. has released new versions of its characteristic booklets. The two booklets, revised and brought up-to-date, are available without charge and can be obtained through the company's distributors or the company's Advertising Distribution Department at the above address.

The "Television Picture Tube and General Purpose Cathode Ray Tube" characteristic chart has been revised to include the latest modifications, type changes, etc. Over 30 tube types have been added, which brings the total types listed in the booklet to over 250. There are 56 different basing diagrams accompanying these tube types.

The revised "Radio and Television Receiving Tubes" booklet includes, in addition to previously listed types, the latest television receiver and subminiature tubes. Over 750 different receiving tube types are listed in the chart along with their basing diagrams.

NEEDLE REPLACEMENTS

The *Recoton Corporation*, 147 West 22nd Street, New York, N. Y. has issued a 1953-54 edition of its "Simplified Reference Guide to Replacement Needles."

Designed to assist dealers in selecting the correct replacement part, the guide is thoroughly cross-indexed for fast reference.

Copies are available without charge from the company on request.

DEALER AID


A new thermometer designed to attract the attention of customers of radio and television dealers is now available from parts distributors of *Sprague Products Co.*, 51 Marshall Street, North Adams, Mass.

Twelve inches in diameter, the easily-visible face is finished in characteristic *Sprague* orange and blue. Weather-sealed in an aluminum case for outdoor as well as indoor use, this thermometer is available to radio and television service technicians through all *Sprague* jobbers or may be obtained postpaid by sending a \$4.00 check or money order to the company. Ask for Thermometer D-114.

U.H.F. ACCESSORIES

Mosley Electronics, Inc. of 8622 St. Charles Rock Road, St. Louis 14, Missouri is currently offering a copy of its new catalogue which lists and describes the company's line of television installation accessories.

Catalogue 53-54 offers several of

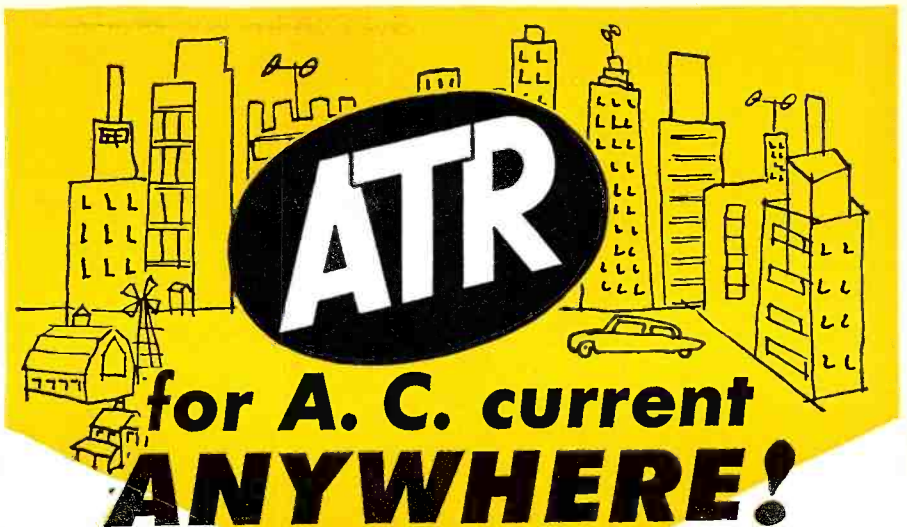


AT NEW
LOW COST

\$25⁵⁵
And Up
Retail Price

INVERTERS

For Inverting D.C. to A.C. . . . Specially Designed for operating A.C. Radios, Tape Recorders, Wire Recorders, Record Changers, Television Sets, Amplifiers, Address Systems, Radio Test Equipment and most small electrical and electronic devices from D. C. Voltages in Vehicles, Ships, Trains, Planes and in D. C. Districts.

Type	Input DC Volts	A.C. Output 60 Cycles	Output Int.	Wattage Cont.	Consumer Net Price
6-LIF	6	110 volts	40	35	\$25.55
12-LIF	12	110	50	35	25.55
* 6-RSD	6	110	85	75	39.25
*12-RSD	12	110	125	100	39.25
32-RSD	32	110	150	100	39.25
110-RSD	110	110	250	150	39.25
*12T-HSG	12	110	250	200	96.45
110AT-RHE	110	110	325	250	56.95

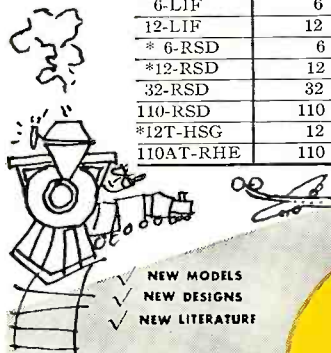

See your jobber
or write factory

There is an ATR model for most any application.
* Available with leather carrying handle at \$1.00 additional—optional.



"A" Battery Eliminators, DC-AC Inverters, Auto Radio Vibrators

AMERICAN TELEVISION & RADIO Co.

Quality Products Since 1931

SAINT PAUL 1, MINNESOTA—U. S. A.

BIG VALUE at a Low Price



Model M-G 18

You'll look long and hard before you'll find an 18-watt amplifier with mike and phono inputs, bass and treble controls, output impedances from 4 to 500 ohms, and two speaker outlet sockets, that will outperform this M-G unit. You'll pay *much more* for one of equal performance.


Compare its value . . . or that of any of the six other M-G models . . . with amplifiers of other makes. You'll say it's the biggest value on the market for the money.

FREE Catalog

Catalog 200 shows the entire line of M-G Sound Equipment. Get your copy today!



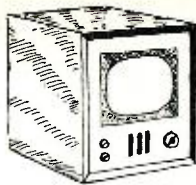DON McGOHAN, INC.
3700 W. ROOSEVELT RD., CHICAGO 24, ILL.



10" TV REMOTE AUXILIARY SET—BUY OF A LIFETIME FOR THAT EXTRA SET IN THE HOME, BAR or OFFICE!!! Operates with any standard TV receiver. **FEATURES:**
* 19 TUBES incl. 10BP4—all 90 day warr'd. * H.V. O.S.C. POWER SUPPLY detachable unit. * MAJOR STANDARD PARTS INCLUDED: Defl. Yoke, Focus Coil, Hor. & Vert. Outputs, two 10h-100ma Chokes, 150ma Sel. Rectifier, electrolytics, controls, etc. **FANTASOME WALNUT VENEER-LEATHERETTE CABINET. COMPLETE SCHEMATIC & HOOK-UP DATA SUPPLIED.** Operates on 110VDC. All conversion data supplied. **PARTS ALONE WORTH SEVERAL TIMES THE PRICE OF . . .**
(Overall: 20 1/2" x 17" x 14 1/2") Shpg. \$23.95

PERFECT CONDITION—USED
STEP-BY-STEP MOTOR (Bendix CAL-14810, Mkt. Mod. O) 70VDC input. Brand new. \$6.95
1 1/2 H.P. G-E MOTOR (Type 325) 115 V. 7 amp. Dble. 3/8" shaft, 110VDC. 434" X \$3.95
5 1/2" Shpg. wt. 13 lbs.
115VAC PLUNGER SOLENOID (1 1/2" sq. x 1 1/2") . . . 1 1/2" stroke. 30 sec. duty. ea. \$1.49; 4/\$5.00
RADIO HARDWARE TREASURE . . . FULL LB. CAN of Nuts, Screws, LugS, Washers. 89c; 3 lbs. 2.49
CRYSTAL MIKE cartridge (Brush, 1" sq. x 3/16") . . . Sensitive, hi-impedance. . . . ea. 1.98
(Other mike cartridges in stock. Write needs.)
HEARING AID AMPLIFIER CHASSIS (2 tube) . . . MAKE A REAL VEST POCKET RADIO or AMPLIFIER adding only simple tuner & phone. Ready-wire WITH SCHEMATICS FOR 2 or 3 TUBE SET. Less tubes, case. 2.49
SET OF 2 SUB-MIN. TUBES for above. 2.98
HEAR. AID BONE CONDUCTION RCVR. 1 1/2" x 3/4" x 1 1/2". Exc. for MUSICAL CONTACT MIKE, DETECTOPHONE. Lo-impedance, magnetic type NOW ONLY 1.98
STOCK UP ON TUBES!! . . . LOW, LOW PRICES!! 90-DAY GUARANTEED, STD. BRANDS, unsealed cartons.
= 24, 26, 27, 34, 41, 42, 53, 56, 89 or 6K7 . . . each 29c
= 1H4, 1H6, 1J6, 5Y3, 5Y4, 6BT, 6C3, 6F3, 6G5, 6A5, 6K8, 6SD7, 6SQ7, 6R7, 7S or 80 . . . each 39c
= 1L4, 6U4, 6AR, 6A3, 6AU6, 6BE6, 6CG6, 6P6, 6H6, 6J6, 6SA7, 6SK7, 6SN7, 6W4, 7A4, 12SN7, 45 or 77 each 49c
= 1A7, 1LC6, 1LH4, 2A5, 2A6, 6A3, 6A6, 6B8, 6B04, 6SC7, 6SP3, 6SH7, 6SR3, 6UT, 7A67, 7B6, 7A7, 7C5, 7C7, 7G7, 7Y4, 12A6, 12AU7, 12AT7, 47, 50, 58 or 81 each 69c
"BUY OF THE MONTH" . . . NEW "JUMBO RADIO PARTS KIT" . . . A BIG, BIG assortment of inventory odds & ends: Resistors, Condensers, Coils, Wire, Sockets, Controls, Etc., Etc. Shpg. wt. 20 lbs. ALL FOR \$3.95

"DIRECT FACTORY SPEAKER REPAIRS SINCE 1927"
Min. order \$3.00. 20% deposit req. on all C.O.D.'s. Please add sufficient postage—excess refunded.
LEOTONE RADIO CORP.
67 Day Street
New York 7, N. Y.

the company's new products which have been designed for the particular requirements of u.h.f. as well as v.h.f. television installations.
Copies of this publication are currently available from radio and television parts jobbers or from the company direct.

VIBRATOR GUIDE

A completely revised "1953 Vibrator Guide" is now available from P. R. Mallory & Co. Inc. of Indianapolis 6, Ind.

The new guide is a complete vibrator handbook for the auto radio technician. Containing nine sections of valuable information, it includes reference sections prepared according to the Mallory replacement number, original equipment number, vibrator type and application, and manufacturer's replacement number.

Sections are included which show the company's vibrator specifications and base diagrams, installation notes and circuit diagrams, buffer condenser reference circuits, auto battery ground chart, and auto radio service notes.

The "Vibrator Guide" contains 50 pages and sells for 15 cents.

STANDBY POWER

D. W. Onan & Sons Inc., Minneapolis, Minnesota has issued a two-color folder which describes and illustrates its line of standby power units for communications systems.

The folder shows examples of portable and mobile electric plants on the job providing primary electric power for mobile TV studios, radio remote broadcasting units, television maintenance trucks, and mobile CD centers.

A copy of Communications Folder, Form A-307, is available on request.

PRE-RECORDED TAPE

The A-V Tape Libraries, Inc. of 730 Fifth Avenue, New York, N. Y. has published a new catalogue of pre-recorded tapes for home, office, and classroom use.

The handy, pocket-size publication lists many new semiclassical compositions, "pops", vocal varieties, as well as a lecture series on English literature and Bible readings.

A copy of this new catalogue is available on request from the company.

COMPONENT PARTS

A new two-color catalogue covering TV and radio components is now available from Heppner Manufacturing Company, Round Lake, Illinois.

Illustrations and detailed descriptions are given on slip-on ion traps, snap-on ion traps, centering devices, correcting magnets, PM speakers, ED speakers, ferrite rod antennas, flyback transformers, and PM "Focomags".

RCA TRANSISTORS

The Commercial Engineering Department of the RCA Tube Department, Harrison, N. J. has issued an 8-page booklet describing its new transistors.

Let MILTON S. KIVER Help You Prepare For U.H.F.-TV And...



Easy to TRAIN AT HOME This Practical Way!

Men with the right training in Television Servicing are in big demand . . . pull down big pay. T.C.I. TRAINS YOU RIGHT with easy-to-follow technical training designed by servicemen, for servicemen! You learn practical, professional type Television Servicing without leaving your present job. Included are money-making extras such as set conversion, master antenna installation, U.H.F.-TV and field servicing short cuts. You can start earning Television money after the first few lessons. You learn to test, trouble shoot and repair all types of TV sets the proven, practical way!


HERE'S HOW YOU GET EXPERIENCE!

You train on your own large screen modern television receiver, furnished as part of your course. This set is yours to keep! As an optional feature you can get two weeks of actual field experience out on service jobs and on the repair bench for Chicago's largest independent servicing organization. You learn Television Servicing by actually doing Television Servicing . . . you get the practical know-how you need to qualify for BIG MONEY in this fast-growing field! Age is no barrier. Many TCI students are over 40!

VETERANS! T.C.I. is approved for G.I. training under Public Law 550. Check coupon.

ACT NOW! Mail coupon for FREE Catalog and SAMPLE LESSON. Write TODAY!

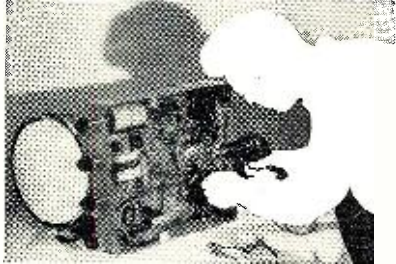TELEVISION COMMUNICATIONS INSTITUTE
205 W. Wacker Dr., Dept. LAO Chicago 6, Ill.



YOU GET and keep modern large screen Television receiver.
YOU DO actual testing, servicing, trouble shooting and repairing

TV BROADCASTING COURSE READY NOW!
Train at home for these big pay studio jobs! Video engineers, cameramen, microwave engineers, etc. Easy non-mathematical training covers all phases. Write!

MAIL NOW FOR FREE BOOKLET

MILTON S. KIVER, President
TELEVISION COMMUNICATIONS INSTITUTE
205 W. Wacker Dr., Dept. LAO, Chicago 6, Ill.
Rush full facts on the course checked below. I am not obligated. Salesman will not call.
 TV Servicing TV Broadcasting
Name _____
Address _____
City _____ Zone _____ State _____
 VETERANS: check here
 BEGINNERS check here for information on Pre-Tel Radio Course.

Included in the booklet is information on the company's Type 2N32 point-contact transistor for use in pulse or switching applications where an operating frequency for voltage-gain cut-off of .9 mc., an operating frequency for current-gain cut-off of 2.7 mc., and a high current amplification factor are important design considerations.

The Type 2N33 point-contact unit for use in oscillator service at frequencies up to 50 mc. is also described.

The types 2N34 and 2N35 junction transistors of the p-n-p and n-p-n type respectively are covered in some detail.

Each of the four types has a base with three small pins in line and spaced to provide mechanical indexing for socket insertion.

HOW MUCH IS YOUR LABOR WORTH?

AN INFORMATIVE little booklet is now available to all radio and television service technicians at the Howard W. Sams Co., 2201 E. 46th St., Indianapolis, Ind. The publication offers an intelligent approach to the setting up of labor costs for service establishments of varied requirements.

Written by Donald B. Shaw, vice-president and treasurer of the company, the booklet is a "must" for all service shop operators. It contains information on the simplest possible ways of estimating labor and assuring compensation for time and business expenses in the operation of a one-man shop. It also explains "productive labor" (the labor performed on a repair job for which you can charge a customer at a given rate). These examples are also based on a one-man shop.


Mr. Shaw demonstrates how these same general principles may be applied when an owner adds personnel. The booklet concludes with a discussion of the allocation of overhead expenses to all profitable departments of the business.

The meteoric rise of the Heath Company of Benton Harbor, Michigan continues unabated as the firm announces the opening of a new addition which more than doubles its facilities for the design and production of all types of test equipment in kit form. The new building houses enlarged laboratory facilities, assembly lines, and office space for the expanded staff of clerical workers necessitated by increased business.



August, 1953

ARC 5 EQUIPMENT:

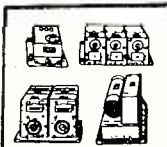

TRANSMITTERS

4 to 5.3 MCS. . . \$8.95
5.3 to 7 MCS. . . 7.95
All above complete with tubes and crystal. In excellent condition.
R-4/ARC-2 RECEIVER—5.3-2.55 MCS.
Complete with all tubes and dynamotor. Excellent condition. . . **\$19.95**

COMPONENTS

MOUNTING RACKS
Single Trans. . . \$1.00 Ea.
Double Trans. . . 1.75 Ea.
Triple Rec. . . 2.25 Ea.
RE-2ARC-5 ANTENNA RELAY UNIT
Comp. with Meter and 50 MMFD vac. . . **\$4.50**
WD-7/ARC-5 PUSHER PULL MODULATOR UNIT
Comp. w/ tubes and dynamotor. Exc. . . **\$11.50**

RECEIVERS

190 to 550 KC \$16.95
6 to 9 MCS. 9.95
All above Receivers complete with all tubes and dynamotor. In excellent condition.

MIDGET SELVENS

AY6 type operates from 6-12 Volts 60 Cycle. Use as both transmitter and receiver. These compact little units draw almost no current and work fine for all remote position indicating applications. OD 2 1/4 x 2 1/4 x 2 1/4. Has spring return shaft. All New (Appr. wt. . . . **\$2.50**
1 lb. **\$4.95**
AY-2 Type, same as above, has continuous rotating shaft. These compact units are all new. . . . **\$4.95**

ARMY AMMUNITION CANS

Type M-3 50 Cal. M3 12" Long x 6" Wide x 7 1/2" Deep. . . **\$1.50**
Type M-1 12.7mm 18 1/2" Long x 3 1/2" Wide x 6 1/2" Deep. . . **\$1.50**
All aluminum with Leather Handle and Hinged Top with hasp. Use for all your small parts or tools. O.D. Color, clean them and buff or paint. **\$1.50**

BK-22 RELAY UNIT

Part of Radio Compass Equipment. Contains 1-12 V. D.P.S.T. Leach Relay and 10 contact 10 pole double throw switch. Terminal mountings on back of unit. All enclosed aluminum housing. . . . **\$5.95**
Brand New

CRYSTALS

FT-341 54th Harmonic Type. Fundamental Frequencies listed below in KC.

370	390	410	430	449	469	486	508
372	392	412	432	451	470	488	510
374	394	414	434	453	471	490	512
376	396	416	436	454	472	491	513
378	398	418	438	456	475	494	516
380	399	420	440	458	477	496	518
382	400	422	442	460	479	498	520
384	402	424	444	462	480	502	
386	404	426	446	464	482	504	
388	406	428	447	466	484	506	

Each Frequency 59c Ea.; 3 for \$1.50; 6 for \$2.70; 10 for \$4.00
500 KC. 1.25

12 VOLT BLOWER MOTOR

The famous Trade Winds Blower for use on Trucks, Boats, Etc. Ideal for Engine Room use as motor is completely enclosed and Sparkproof. 4" outlet. . . **\$9.95**
All Brand New Each

ARC-4 TRANSCEIVER

140-144 MC. Ideal for 2 meters. Complete with 20 tubes and control box. . . **\$29.95**
BRAND NEW

WILLARD 2 VOLT RADIO BATTERY

NEW. Uncharged (Appr. wt. . . **\$2.50**
4 lbs.) TYPE 20-2 Ea.
Complete set of three with Box and Connections to make a 6 volt. 2.0 Amp. Hrs. Battery Uncharged (Appr. wt. 15 lbs.) Set **\$8.95**

2 VOLT VIBRATORS. VB8A Synchronous Type. Used in all portable radios having 2 volt wet cell supply. All new. **\$1.00**

AIRCRAFT HEATERS Stewart-Warner Gasoline Heater with 24 Volt Blower Motor attached S.M.B.T.U. Per Hour. . . **\$4.95**
All in Excellent Condition. Each

12 VOLT GENERATOR

Same generator as used in Trucks and Tractor Units. 12 Volt 25 Amp. with V-Pulley for connection to motor or engine. **\$12.50**

USE SAME WAY AS HAND SET HEAD AND CHEST SET
Use same way as Hand Set head you have freedom of hands. No Batteries or power source required for operation. Excellent Condition. Per Pair **\$11.95**

HOBBY MOTORS

Operates from 110 Volts. 30 Cy. AC. Geared Motors: 3 Speeds: 4,000 RPM., 200 RPM., 5 RPM. These motors can be used for Bar-B-Que pits, Home Work shops or any low speed application. Each speed on a separate shaft. Can be used separately or at the same time. All New. . . **\$12.95**

CAPACITORS • FIXED • OIL FILLED

2 MFD. 50 V. \$1.00	1 MFD. 100 V. 1.25
3X3 MFD. 400 V. 1.95	2 MFD. 1000 V. 3.95
10 MFD. 400 V. 2.95	8 MFD. 1000 V. 4.95
1 MFD. 600 V. 1.95	1 MFD. 1500 V. 1.50
4 MFD. 600 V. 1.95	1 MFD. 1500 V. 2.25
5 MFD. 600 V. 1.95	4 MFD. 1500 V. 2.95
6 MFD. 600 V. 1.95	6 MFD. 1500 V. 2.95
7 MFD. 600 V. 1.95	1 MFD. 2000 V. 1.95
8 MFD. 600 V. 1.95	2 MFD. 2000 V. 1.95
8X8 MFD. 600 V. 2.25	3 MFD. 2000 V. 3.50
10 MFD. 600 V. 2.25	1 MFD. 3000 V. 3.95
15 MFD. 600 V. 2.95	1 MFD. 5000 V. 5.95
20 MFD. 600 V. 2.95	

12 VOLT GENERATOR

Famous "Jeep Generator," 12 Volt, D.C. at 55 Amp. Complete with charging ammeter and 55 Amp. Voltage Regulator. All in enclosed housing. Use for Boats, Trucks, Tractors or Mobile Radio. In excellent condition **\$55.00**



REVERSIBLE MOTOR

1/40 H.P. Ball-bearing 3450 R.P.M. in Blast-proof case. Needs only a capacitor for starting. All Brand New. 110 V. 60 **\$4.95**
Cy. Special Low Price. Starting Capacitor \$0.69 Ea.

DRY BATTERIES

New shipment of recent Expiration Date Surplus Batteries. All Checked.

TYPE	VOLTAGE	WEIGHT	TEN
BA-51	67 1/2 V. Portable Batt.	\$.75	\$6.50
BA-37	1 1/2 V. Handy Talkie Batt.	.25	2.00
BA-38	103 1/2 V. Handy Talkie Batt.	.75	7.00
BA-56	4 1/2 V. Portable Batt.	.60	5.00

PROP PITCH MOTORS

For Your Beam Antenna: 20 Volt to 32 Volt. A.C. or D.C. 1/4 H.P. Motor: 1 1/4 RPM Gear Reduction, 9000 to 1. **\$16.95**
ALL BRAND NEW. Each

MODEL GO-9 TRANSMITTER

ONLY A FEW LEFT
All brand New. 100 Watts CW. or MCW. emission. Operates from 110 V. 60 Cycle, easily converted to 80 Cycle operation. Low frequency range, 300 KC. to 600 KC. High frequency, 3,000 KC. to 20,000 KC. using an E.C.O. We furnish complete conversion data with each transmitter. **\$59.95**
Complete with schematics.

NEW 12 VOLT BATTERIES

For Mobile or light Airplanes. In original factory boxes. Weight . . . 37 Lbs.
Size: 5 1/2" wide x 10" long x 10" high. Signal Corps Type BB-53, 12 Volt, 34 AH. **\$9.95**
A real terrific surplus value while they last, all new. Ea.

HYDRAULIC TRANSMISSION

Variable speed for use in Lathe, Pumps, Drills, Milling Machines, etc. Can be varied from 0 R.P.M. to 650 R.P.M. forward or reverse. At 1/4 H.P. to 1 1/2 H.P. input. Unit must be converted to bring reversing switch and speed control outside case. Has 5/8 H.P. 115 V. Motor mounted on unit. Complete. . . **\$47.50**
in excellent condition.

SOUND POWER PHONES

These are the old style telephone magnetic earpiece which now can be used as sound power phones. Will work up to a few hundred feet without any external voltage source. Sound power phones never before at this low price. **\$1.50 PAIR**

12 or 24 VOLT VIBRATOR INVERTER

Use for Mobile Radio, Trucks, Boats, etc., where 110 Volt 60 Cycle is desired. Can be used on 12 Volts or 24 Volts D.C. Input 110 V. 60 cycle, 240 watt maximum output. Uses separate vibrator for each input. voltage. In enclosed case. **\$27.50**
excellent condition.

MICA CAPACITORS

MFD.	Ea.	MFD	2500 V.	Ea.	MFD.	Ea.
.1	1000 V.	.025	2500 V.	2.25	.00005	.95
.07	.95	.0075	1.50	.0005	5000 V.	.95
.062	.90	.006	1.25	.004	3.50	.95
.05	.85	.005	1.25	.0035	3.25	.95
1500 V.			3000 V.	.003	3.25	.95
.075	1.25	.006	1.50	.0025	2.75	.95
.05	1.10	.004	1.50	.002	2.75	.95
.039	1.10	.003	1.50	.0015	2.75	.95
.03	1.00	.002	1.50	.001	2.35	.95
2000 V.			3000 V.	.0002	1.75	.95
.03	2.25	.001	1.35	.0001	1.75	.95
.01	2.00	.000625	1.35	.00008	7500 V.	.95
.006	1.50	.0005	1.25	.0005	3.95	.95
.005	1.50	.0004	1.25	.0004	8000 V.	.95
.003	1.25	.00025	1.15	.001	5.95	.95
.00275	1.25	.00025	1.10	.0006	4.50	.95
.0025	1.25	.00025	1.00	.0005	4.50	.95
.00125	1.00	.00025	1.00	.00025	3.95	.95
.000625	1.00	.00025	1.00			

FIG. B. SCREW TERMINAL

MFD.	Ea.	1200 V.	Ea.	2500 V.	Ea.	
.05	500 V.	1.00	.85	.015	1.60	
.04	.85	.02	.85	.01	1.50	
.02	.75	.01	.75	.0035	1.25	
600 V.			.005	.50	.003	1.25
.01	.65	.01	.75	.0018	1.00	.95
.04	.85	.02	.75	.0015	1.00	.95
.03	.75	.03	.95	.0015	1.00	.95
.0375	.75	.025	.85	.0016	.90	.95
.0005	.45	.01	.80	.0005	.90	.95
.00015	.35	.004	.60	.00025	.85	.95
.00005	.35	.004	.60	.00015	.85	.95
1000 V.			2000 V.	.0005	.85	.95
.01	.75	.0004	.75	.005	3000 V.	.95
.00005	.50	.00027	.75	.005	1.50	.95


FIG. C. SOLDER LUG TYPE

MFD.	Ea.	500 V.	Ea.	.02 <th>1250 V.</th> <th>Ea.</th>	1250 V.	Ea.
.02	.75	.005	.65	.02	.85	.95
.01	.75	.00004	.50	.02	1.50	.95
.006	.65	.03	1.00	.00005	.50	.95

All Mail Orders Promptly Filled, F.O.B., San Francisco . . . All California Orders—Add 3% Sales Tax . . . Do not send postage stamps. Write for new 1953 free booklet listing our stock and prices on Radio, Electronics, Tools, Hardware, Motors, Wire, Meters, Batteries, Aluminum Sheets, etc. 20% Dep. on all C.O.D. orders. All items subject to prior sale and prices subject to change without notice. On purchases under \$5.00, send full amount.

STANDARD SURPLUS 1230 Market St., San Francisco 3, Cal. Telephone HEMlock 1-3106

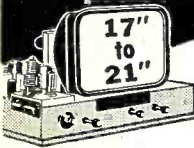Let me show you how EASY it is to
LEARN TV
the practical way--



**ASSEMBLE A
TRANSVISION
TV KIT**

Pay as You Wire \$**39**
Down Payment

I WILL HELP YOU to start learning TV the practical way -- by assembling a TRANSVISION TV KIT in EASY STAGES. For only \$39 you get PACKAGE #1 (standard first pkg. for all of our kits). This package gives you the BASIC CHASSIS and over 450 TV COMPONENTS with complete Instructions, Drawings, Photos, Service Booklet, and a year's subscription to my "TV and Electronics Notes". When ready, you order the next stage (pkg. #2), etc. Low prices make your complete kit a terrific buy!



FREE CATALOG
Shows 6 Great TV Kits:
EXCLUSIVE: Only Transvision TV Kits are adaptable to UHF. Ideal for FRINGE AREAS. No Previous Technical Knowledge required. Write now!
TRANSVISION, INC., Dept. RN8
NEW ROCHELLE, N. Y.


--- MAIL THIS COUPON TODAY ---
Mr. D. Gnessin, Educational Director
TRANSVISION, INC., NEW ROCHELLE, N. Y. Dept. RN8
 I'm enclosing \$_____ deposit. Send standard kit PACKAGE #1, with all Instruction Material. Balance C.O.D.
 Send FREE copy of your new TV Kit Catalog.
Name _____
Address _____
City _____ State _____

Tremendous Opportunities in
COIN TV
and COMMERCIAL TV

TRANSVISION offers the only specially designed line of Coin-Operated and Commercial TV with the
FREEVIEWER* ATTACHMENT
(Pat. Pend.)

This field offers rich rewards to enterprising servicemen or dealers -- on part time or full time basis.
*The Electronic Freeviewer is a patented device which makes coin operation really pay off in a big way. Boosts revenue by "sampling" -- by giving a short freeview of TV programs to prospective customers. Works like magic in enticing sales.

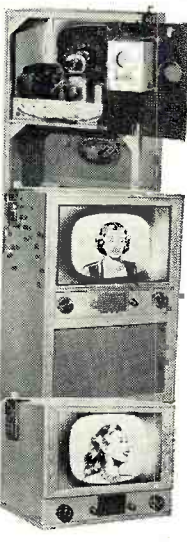Get details now.
TRANSVISION, INC.
NEW ROCHELLE, N. Y.



--- MAIL THIS COUPON TODAY ---
TRANSVISION, INC., NEW ROCHELLE, N. Y. Dept. RN8
 Rush full details on COIN OPERATED TV.
Name _____
Address _____
City _____ State _____

RECTIFIERS AGAIN

By THOMAS R. HUGHES

THIS is a further commentary on my article, "Unrecognized Hazards in Electronics," which was published in the April issue of this magazine. Since this article appeared, I have received some objections from the manufacturers of rectifiers who feel that it may have placed the use of selenium rectifiers in a bad light.

I want to assure you that I had no such intention, in fact—if anything—I meant to accomplish the opposite. Being a safety engineer and, at the same time, an experimenter in sound equipment and electronics, I was somewhat concerned over a previous article on the subject, in another publication, that included misinformation and exaggerations.

My article was aimed at electronics designers, maintenance men in factories and plants, and radio or television technicians in repair and service shops. It was not expected to apply to users of electronic equipment in the office or home, nor to workers in selenium rectifier manufacturing plants (where suitable precautions are observed).

Selenium rectifiers have provided the means for valuable progress in many fields where direct current is required. Though they are used extensively in the electronics and aircraft industries in California, we apparently have no record of serious injury as a result.

My article was not intended to cause alarm in the mind of any reader but it was my wish to call to the attention of those who deal with large rectifiers that the existence of toxic fumes is possible.

While there is little in past experience to base opinions on, I left the implication that one could dismiss the normal use of small rectifiers (in radios, television, etc.) as a source of serious hazard. However, since the uses of electronic circuits and their supply from rectifiers are invading more fields every day and we have no means of anticipating their applications or misuse, we cannot let possible hazards go unrecognized.

Thus, I went to some pains to outline the precautions that one could observe if he felt any concern over his application of a rectifier. I used the word "should" in some places and was careful not to imply that any of the precautions recommended were absolutely required.

One more point that I feel should be cleared up is what I meant by a "burn-out." I used the word "arc-over" as electricians use it—to indicate that damage was caused by electricity passing over the surface of a dielectric or insulator rather than through an internal short circuit. I find that my use of the term was misinterpreted as referring to the momentary flashes frequently occurring during the first energizing of the cells in manufacture.

By a "burn-out," I was referring to the breakdown of a group of cells and the burning, by prolonged arcing or conduction of current, to chemical compounds differing from those required for normal operation. In other words, its destruction as a rectifier.

I hope this will be of value in removing any discredit my article may have brought to selenium rectifiers. In their present state of perfection they merit our high regard as simple, foolproof servants.

CRYSTALS!
LOWEST PRICES!
ONLY 79¢ E.A.
ACT NOW

In FT 241-A Holders—1/2 in. Pin SPC. These are designated 54th Harmonic MC freq. Listed by fundamental freq. with fractions omitted.

370	392	414	437	494	477	505
372	394	416	439	496	479	507
374	396	418	440	499	481	509
375	398	420	442	461	483	511
377	400	422	444	462	485	512
379	401	424	446	464	487	514
381	403	425	448	466	488	516
383	405	427	450	468	490	518
385	407	429	451	470	492	520
387	409	431	453	472	494	522
388	411	433	455	474	496	524
390	412	435	457	475	497	525

5 CRYSTALS. Assorted ONLY \$2.75
10 for \$4.50, 20 for \$8.50

COMPLETE SET!!!!—80 crystals covering above basic freq. including a 500 Kc. crystal. Lowest Price in United States! Write in for terrific buy!

SUPREME TUBE 600
Illuminated TUBE & SET TESTER
Tests all latest tubes. Seven in. multi-tester tests DC 0-2,500 V. in 7 ranges. AC 0-2,500 V. in 6 ranges. DC current 7 ranges: 0-1,000 microamps, 0-1,000 ma., and 0-10 amps. Ohmmeter 3 ranges: 0-20 megohms. Output meter and battery tester which tests radio batteries under load. Comes with test leads and gray metal Hammerlock case. Size: 11x15x8 1/2 in. Factory guarantee includes 1 year of free tube setting service. BRAND NEW IN ORIGINAL BOXES. You know this set is designed to net for \$117.50. While they last, our \$69.95 price—the country's lowest. Only . . . \$69.95

SPECIAL 500 Kc. Crystal \$1.25
1000 Kc. Crystal 2.25
All above crystals sent postpaid in U. S. only. Also available in complete sets for SCR-608, SCR-528, SCR-628 and TRC-2. Foreign orders at dealer. Inquiries invited. Write for LARGE QUANTITY DISCOUNTS.

MARINE EQUIPMENT
COLUMBIA'S NEWEST HI-POWERED 1953 MARINE TRANSMITTER. Puts out max. power allowed by F.C.C. Contains all latest improvements & meets newest F.C.C. specs. Specify whether 12 or 24 V., frequency desired, and positive or negative ground. Full 90-day, unconditional guarantee. Pre-tuned ready to install. \$349.50
BC-223 25 W. MARINE TRANSMITTER & ARB RECEIVER. For 24 V. installation. Complete with PLETE! Ready to go. \$185.00
JEFFERSON-TRAVIS MARINE 5 W. RADIO-TELEPHONE. Made by Emerson Radio Corp. 2-channel, crystal controlled receiver & transmitter. F.B. for small boats with 6 V. system or sail boat. Will run 48 hrs. on standard 6V. car battery. Complete with tubes, instructions, but less crystals and battery. N.W. \$89.50
Above unit with 110 V. charger for 60 day battery. NEW \$95.00
CRYSTALS FOR ABOVE: Specify freq. Set of 4 needed. Per Set \$22.50

AIRCRAFT, HAMS & MARINE MEN!
SCR-183 12 V. RECEIVER & TRANSMITTER! Covers aircraft, marine and ham bands! Complete with 2 coils, control boxes, tuning head, flex cable, rack and shock mount! Plus 12 V. dynamotor! Individual parts worth \$25.35. EXCEL COND. COMPLETE! Never before sold at this sensationally low price. \$15.95

ARC-5 OR 274-N TRANSMITTERS
2.1-3 mcs. Brand new. \$19.95
3-4 mcs. With tubes. 25.00
4-5.3 mcs. With tubes. 8.95
5-3.7 mcs. With tubes. 6.95
7-9.1 With tubes. 14.50

ARC-5 OR 274-N RECEIVERS
Equipped with tuning knobs
.19-.55 kc. \$19.95
1.3-3 mcs. Brand new. 24.50
3-6 mcs. Brand new. 22.50
3-6 mcs. With tubes. 10.95
6-9.1 mcs. With tubes. Used. 7.95
New 22.50
6-9.1 mcs. Used. Less tubes. 6.50
cond.
MD-7 ARC-5 PLATE MODULATOR. Excel. cond. 17.95
BC-456 274-N Modulator. Less dynamotor. Excel. cond. 3.95
12 V. COMMAND RECEIVER DYNAMOTOR. New. 12.95
Plus All Accessories Needed for Above.

LOW? Is your vacation dough LOW? Sell your new or used radio gear NOW! Tell us how much you want.
Write Today—and ask for FREE CATALOGUE!
All orders F.O.B. Los Angeles. 25% deposit required. All items subject to prior sale.
COLUMBIA ELECTRONIC SALES
522 South San Pedro St. Los Angeles 13, Calif.


CASH FOR SELSYNS
Navy or Army Ordnance type 60 cycle types as follows: \$35.00 for 1DG, 1D, 1F, 1G, 1DF, 1CT; \$20.00 for 5DG, 5G, 5F, 5CT, 5D, 6DG, 6G, 6CT; \$25.00 for 7G, 7F, 7CT, 7DG. ALSO NEEDED: GE Selsyns Models 2J5HA1, 2J5HA1, 2J5LA1; Autosyns AY100 or 200 series; Diehl Control Motors 49-7, 25-11, etc.; Delco and GE PM Motors, Inverters, Tubes, and other Electronic Components. All Merchandise Subject to Inspection. Send Lists—Will advise Price.
ELECTRO SALES CO., INC.
Dept. RN 58 Eastern Ave. Boston, 13

WHAT'S

For additional information on any of the items described herein, readers are asked to write direct to the manufacturer. By mentioning RADIO & TELEVISION NEWS, the page and the issue number, delay will be avoided.

PORTABLE RECORDER

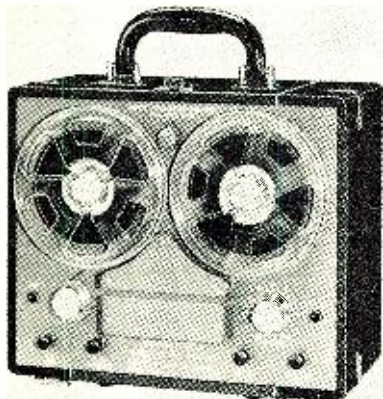The Magnematic Division of *Amplifier Corp. of America*, 398 Broadway, New York 13, N. Y. is now offering a



new 117 volt, a.c. portable tape recorder which weighs 19 pounds and attains a frequency response of 50 to 15,000 cps at 7½ inches-per-second.


Completely operated by push-button control, the new unit features a solenoid-operated, clutch-controlled capstan drive to start and stop tape travel within 1/20th of a second.

The "Magnematic" is designed for extreme simplicity of operation; it is ruggedly constructed to withstand the rigors of portability, and provide maximum stability and dependability of performance.

For complete technical specifications and prices write the company direct.

BASS REFLEX ENCLOSURE

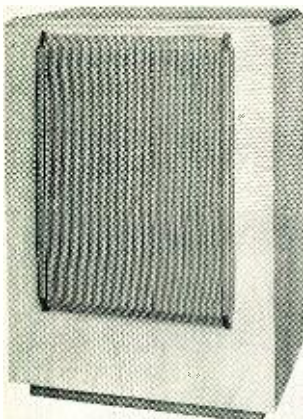Beam Instruments Corporation, 350 Fifth Avenue, New York 1. New York has added two new wall and corner type bass reflex loudspeaker enclosures to its line of "Tannoy" housings.



While designed to be used with the company's dual-concentric speakers, the new enclosures can be used with


other makes of 12- and 15-inch loudspeakers. They are constructed of ¾" lumber with all joints close battened, screwed and glued. Interiors are completely insulated to absorb internal standing waves and sound reflections.

The wall-type enclosure is designated as the "Westminster," the corner-type has been named the "Parliament." The "Westminster" is 39½" high, 28" wide, and 19¼" deep. The "Parliament" is 42¾" high, 30" wide, and 20½" deep. Both styles are available on a custom basis.

TURNOVER CARTRIDGE

Sonotone Corporation of Elmsford, New York is now offering a new phonograph pickup design, the "Titone Turnover."

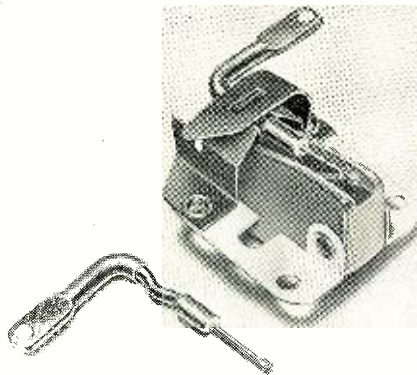Using a high-compliance, high-sensitivity ceramic element and a unique turnover method, the new cartridge provides some interesting characteristics. Requiring no equalizers or preamplifiers, the cartridge has an out-



put of one volt and is unaffected by moisture or temperature.

The jewel needle tips (either diamonds or sapphires) are mounted back-to-back on a single shank, the entire assembly rotating for needle change. When replacement is required, the complete needle assembly, including the lever handle, is removable as a unit.

NEW UTAH BAFFLES

Utah Radio Products Co., Inc. of Huntington, Indiana has added a series of wall baffles to its line of products.

The new baffles have been trademarked "Utone" and are designed and engineered to give a maximum of clean, life-like tone. The baffles are built without a single nail, all joints being mortised and secured with waterproof glue. They are self-mounting, needing no metal brackets for installation.

They are available in four sizes for 6, 8, 10, and 12 inch speakers and



L. Veltri, busy service-dealer of Westchester, N. Y., reports:

I SAVED \$940*
by making a \$59 INVESTMENT
in a Transvision
FIELD STRENGTH METER

* Says Mr. Veltri: "... The way I figure, in the last 6 months I saved that much money in installation time alone ..."



FIELD STRENGTH METER
Saves 50% of Installation Cost
Pays for itself on 3 or 4 jobs


NO TV SET NEEDED

Works from antenna . . . Measures actual picture signal strength directly from antenna. Shows antenna orientation maxima. Compares gain of antenna systems. Measures TVI on all channels. Checks receiver re-radiation (local oscillator). Permits one man antenna installation.



Eliminate variables, insure accuracy with direct meter readings on the FSM.

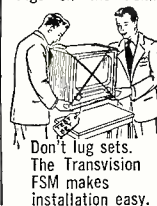PREVENT WASTE OF SERVICING TIME! By checking antenna performance with the *Field Strength Meter*, the serviceman can determine whether the TV set or antenna, or both, are the source of trouble. Call backs are eliminated.



Don't lug sets. The Transvision FSM makes installation easy.

Wide range: Measures field strength from 10-50,000 microvolts. Has *Fringe Area Switch* for weak signal areas. 13 channel selector. Individually calibrated on every channel.

ADAPTABLE for UHF

Model **FSM-2**, for 110V AC only. Complete with tubes. Wt. 13 lbs. net \$59.

Model **FSM-3B**, for 110V AC and Battery Operation (all batteries and cables included). Wt. 22 lbs. net \$79.

Order direct from factory:
TRANSVISION INC., NEW ROCHELLE, N. Y.

FREE: Sample copy of "TV and Electronics Notes". Or send 50¢ for year's subscription.



10 DAY TRIAL

Buy and try this fine instrument for 10 DAYS. Then, if you wish, you may return it. Your purchase price less 10% (our cost of handling and re-packaging) will be promptly refunded.

TRANSVISION, INC.
DEPT. RN-8 F NEW ROCHELLE, N. Y.

() Send me _____ Model FSM-2; _____ FSM-3B
() Enclosed find \$ _____ deposit. Balance C.O.D.
() Enclosed find \$ _____ in full.
I accept your 10 Day Trial terms.

Name _____
Address _____
City _____ State _____

WHEN YOU ORDER WELLS COMPONENTS...



HERE'S WHAT
YOU GET

- 1 IMMEDIATE DELIVERY FROM STOCK
(in any quantity)
- 2 FINEST QUALITY OF FAMOUS BRANDS
- 3 GENERALLY LOWER PRICES
- 4 RETURN PRIVILEGE FOR FULL
CREDIT IF NOT SUITED TO YOUR
REQUIREMENTS

The valuable service Wells provides to the industry is being used by many of our greatest manufacturers as a matter of course.

Our vast stock (the world's largest) may contain just the components you need to fill urgent orders — at a substantial savings in time and cost.

ADEL CLAMPS • ANTENNAS, Insulators, Mast Sections • BINDING POSTS • BLOWERS • CABLE ASSEMBLIES • CHOKES • COILS • CONDENSERS Oil Filled, Bathtub, Hearing Aid, Transmitting Mic, Silver Mic, Ceramic, Variable, Trimmer • CRYSTALS • FILTERS • FUSES & MOUNTINGS • GENERATORS • GROUND RODS • HEADSETS • I.F. COILS • JACKS • JACK BOXES • KEYS, Telegraph KNOBS • LAMPS • LORD MOUNTS • LUGS MOTORS & BRUSHES • PLUGS • RECTIFIERS Selenium, Copper Oxide, Meter, Diode • RESISTORS—All Types • SELSYNS • SOCKETS • SWITCHES Aircraft, Micro, Switchettes, Toggle • TIMERS • TUBING—Flexible • TUNING SHAFTS • TRANSFORMERS All Types • VIBRATORS • WALKIE TALKIES

DYNAMOTORS

OVER 100,000
NEW DYNAMOTORS
IN STOCK!

DM 32A — DM 53A — PE 86 — PE 101C
DM 33A — D 101 — PE 94, etc.

Large quantities of brushes for all types of dynamotors and motors.

Write us for quotations. Advise us your requirements.

A complete Signal Corps stock number listing of items in our stock. Write for listing No. SG-200. (For government agencies and contractors only.)

Manufacturers and distributors—write for new Condenser Catalog C-10 now available.

Write, Wire, Phone Your Requirements
all phones: **SEEley 8-4143**


WELLS SALES, INC.

33 W. Chicago Ave., Dept. R, Chicago 22, Illinois

come in three finishes—red or brown mahogany finish and futuristic blonde finish. All sizes are also available in natural, unfinished wood.

STANCOR "TINYTRANS"
Standard Transformer Corporation,
3580 Elston Ave., Chicago 18, Ill. is now marketing a new line of miniature high-fidelity audio transformers, known as "Stancor Tinytrans."

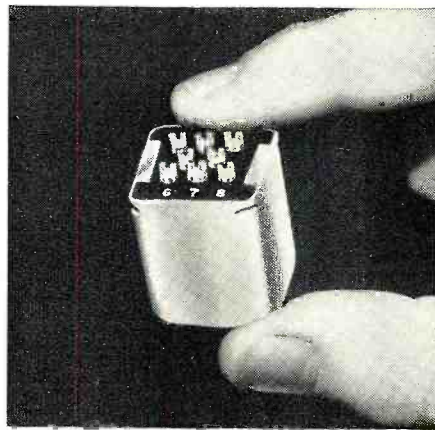The miniature units are made with nickel steel laminations, with a fre-



quency response of ± 1 db, 30-15,000 cps, maximum level 0 db. They are sealed and potted in $\frac{7}{8}$ " square, anodized aluminum cases with phenolic terminal boards. Total height, including terminals, is only $1\frac{1}{4}$ ". The case has two 2-56 threaded inserts, $1\frac{1}{16}$ " centers, for easy chassis mounting. It weighs only 1.3 ounces.

A bulletin on these units is available on request.

REGULATED SUPPLY
Kepco Laboratories, 131-38 Sanford Ave., Flushing 55, N. Y. has introduced the Model #400 voltage regulated power supply which features one regulated "B" supply, one regulated "C" supply, and one unregulated filament supply.

The "B" supply is continuously variable from 0-400 volts and delivers from 0-150 ma. Ripple voltage is less than 5 millivolts. The "C" supply is continuously variable from 0-150 volts and delivers from 0-5 ma. The filament supply delivers 6.3 volts at 10 amperes and is unregulated, center-tapped, and ungrounded.

The power supply is designed for relay rack mounting or bench use. The cabinet is 7" high, 19" wide, and 11" deep. The weight is 40 pounds.

SUPPORT CHANNELS
The Lowell Manufacturing Company of 3030 Laclede Station Road, St. Louis, Mo. has announced the availability of a line of steel support channels which simplify the installation of sound system speakers in suspended ceilings.

These channels are available for 24" and 48" spans and are easily installed in any standard type of suspended ceiling construction. They can be used in either new or existing ceilings.

CRYSTALS

FOR ALL PURPOSES

LOW FREQ.—FT 241A for SSB, lattice filter, $\frac{1}{2}$ " spc. 54th or 72nd harm channels listed by fund. Fractions omitted.	SCR. 522 $\frac{1}{2}$ " p $\frac{1}{2}$ " sp	BC-610 2 banana plugs $\frac{3}{4}$ " spc.
370 392 412 433 494 515	400 459 5520	2030 2390
372 393 413 434 495 516	440 461 5910	2032 2415
374 394 414 435 496 518	441 462 6370	2045 2435
375 395 415 436 497 519	442 463 6450	2052 2442 5
376 396 416 437 498 520	444 465 6470	2065 2532 5
377 397 418 438 501 522	445 466 6497 9	2105 2545
379 398 419 481 502 523	446 466 6522 9	2125 2557 5
380 401 420 483 503 525	447 468 6547 9	2131 3202 5
381 402 422 484 504 526	448 469 6610	2145 3215
383 403 423 485 505 527	450 470 7380	2155 3237 5
384 404 424 486 506 529	451 472 7390	2220 3250
385 405 425 487 507 530	452 473 7480	2258 3322 5
386 406 426 488 508 531	453 474 7580	2260 3510
387 407 427 490 509 533	454 475 7810	2280 3520
388 408 429 491 511 534	455 476 7930	2282 2 3550
390 409 430 492 512 536	456 477 8290	2290 3570
391 411 431 493 513 537	457 479 EA.	2300 3580
	458 480 EA.	2305 3945
	200 or 500 KC IN FT HOLDER $\frac{1}{2}$ " SPC.	2320 3955
	99¢ each	2360 3995
	10 for \$9.00	
	49¢ EA—10 for \$4.50	\$1.29 EA.

FT 243— $\frac{1}{2}$ " P IN SPC.

4190 6175 7806	1015 5760 5873 6340 6573 6740 7650
5030 6206 7840	3735 5773 5906 6373 6575 7440 7673
5485 6773 7873	5305 5800 5940 6406 6600 7506 7706
6040 6873 7906	5677 5806 5973 6450 6606 7540 7973
6073 7740 7940	5706 5825 6273 6473 6640 7573 8240
6140 7773	5725 5840 6306 6506 6673 7606 8273
	5740 5850 6325 6540 6706 7640
	49¢ EA—10 for \$4.50

Special Purchase! FM RADIO CHASSIS
88-108 MC—complete with 6 tubes, built-in antenna and speaker. Product of famous radio and TV maker whose name we promised not to mention... **\$16.95**
Maroon plastic cabinet for above \$5.95.

TWO-STATION INTERCOM SYSTEM
Consists of master and remote station, 20-ft. of 3 wire cable, 115 V operation, AC or DC. Extra wire .05 per ft... **\$16.97**

NOTICE TO ALL HAMS
TRADE-IN your used communications gear on new Hallicrafters, National, RME, Hammarlund, Sonar, Elmac, Gonset, Etc. equipment. Write for FREE ESTIMATE, attention "Pick"—W3PPP.

FREE QUOTATIONS on hi-fi equipment yours on request. All famous brands of amplifiers, tuners, chargers, pick-ups, speakers, etc. Just tell us how much you want to spend and we'll recommend the best matched system your budget will allow!

Sun

PARTS DISTRIBUTORS, LTD.

520 TENTH ST., N.W. - WASHINGTON, D.C.

SPEAKER RECONING

Complete line Cones, Spiders, Rings and Voice Coils. Custom Built Voice Coils. Low prices. Write for Parts List and Reconing information.

WESTERN ELECTRONICS CO.
3164 West Colfax Denver 4, Colo.

BARGAIN HUNTING?

RADIO SERVICEMEN!

Write for SENSATIONAL CATALOG
HENSHAW RADIO SUPPLY
3619 TROOST KANSAS CITY, MO.

Specifications and information on these steel support channels are available from the company on request.

PRINTED-CIRCUIT SWITCH

The Daven Company, 191 Central Avenue, Newark, N. J., now has available a new printed circuit rotary switch Type PCF-1 with 60 position, shorting-type action.

Eyelets are provided for solder connections at every position. The Type



PCF-2, having non-shortening positions, is also available. The switch segments are silver-alloy bonded to the phenolic contact panel. The rotor arm is the company's "knee-action" type rotor which provides uniform contact pressure and very low contact resistance throughout switch life.

Contact resistance is approximately .003 to .004 ohm and does not vary more than .0003 ohm over the life of the unit. The diameter is 3" and the depth is 2 1/16".

Additional information is available from Dept. PCS of the company.

GERMANIUM DIODES

A line of nineteen point-contact germanium diodes has been announced by the transistor division of National Union Radio Corp. of Hatboro, Pa.

The encasing cartridge is composed of a plastic material impervious to moisture and having good electrical characteristics and mechanical stability at high temperatures. The stiff terminal pins permit clipping of the unit into spring terminals either for test or circuit application and the flexible leads permit soldering or other suitable connection means.

An engineering bulletin, No. 1001, gives electrical specifications on the nineteen new units. It is available on request.

GENERATOR ADAPTER

The Accessory Division of Philco Corporation, Allegheny & "A" St., Philadelphia, Pa. is in production on its Model G8000 v.h.f.-to-u.h.f. signal generator adapter.

The company's u.h.f. tuner is the heart of the new adapter. It permits measurements to be made at u.h.f. while controls, markers, and attenuators are operated with the usual convenience at the common v.h.f. frequencies.

As the output from any v.h.f. signal generator at 60 mc. is fed into the

August, 1953



FOLLOW ARROW FOR BIGGEST STOCK AT LOWEST PRICES

- RADAR—TRANSMITTERS
- RECEIVERS — TUBES — PARTS



234-258 MC RECEIVER

11-tube UHF tunable receiver with schematic. Like new.

\$17.95

Rack\$3.50
Control Box.. 1.50

RADAR TEST EQUIPMENT


TS-3, TS-19, TS-13, TS-15, TS-33, TS-34, TS-35, TS-36, TS-45A/PA3.

FOLLOW ARROW TO GET HIGHEST PRICES FOR YOUR NEW AND USED RADIO GEAR! What have you to sell? WRITE TODAY!



UHF 420 MC TRANSCEIVER. Complete transmitter-receiver unit with 5 stages of 30 MC. 1F amplifier. This unit is the famous APS-13 Radar Set. Less tubes and dynamotor. With schematic. Excel. cond. **\$12.95**

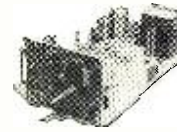BC-604 30 W. FM TRANSMITTER. For 20-27 MC. band. Ideal for 10-11 meters. Complete with tubes, temperature controlled crystal oven and technical manual with all instructions for BC-603 and BC-604. Less dynamotor and crystals. Excel. cond. **\$12.95**



UHF Transmitter

450-710 MC. Tunable Transmitter. 10 W. output. Two 368-type tubes as push-pull oscillators. Wide band video amplifier. Less tubes, with schematic. Excellent condition. **\$8.95**



R.F. Modulator

Complete Tunable 205 MC. Test Set. With 110 V. 60 cps. power supply. 3-stage audio amplifier. Terrific chassis for experimentation. With schematic. Like new. **\$9.95**



INTERPHONE AMPLIFIER BC-709-B

A 2-position single stage audio amplifier. Uses 1 tube and operates from self-contained batteries. With Instruction Manual and Schematic. **\$3.95**
NEW (less batteries).....

ARC-4 TRANSCEIVER

140-144 MC. Complete with control box, tubes. 12/24 VDC dynamotor with schematic. This is a special reduction for this month only. **\$32.50**
Like new
MT 101 ARC-4. Rack..... **\$6.00**

COMMAND EQUIPMENT (SCR-274N)

	Used	New		Used	New
BC-442 ANTENNA RELAY. Less cond.	\$1.95		BC-453 With tubes	\$19.95	\$0.95
BC-451 TRANSMITTER CONTROL BOX		5 3.95	MC-211 90° ANGLE COUPLING UNIT.		\$19.95
BC-450 3-RECEIVER REMOTE CONTROL BOX		1.50	FT-234 MOUNTING RACK for single transmitter	2.95	3.50
MC-215 MECHANICAL DRIVE SHAFT. Per length		2.95	FT-226 MOUNTING RACK for 2 Command Amps.		3.95
BC-496 2-POSITION RECEIVER CONTROL BOX		2.95	FT-221 MOUNTING PLATE for FT-220		1.50
BC-455 6-9 MC RECEIVER. With tubes	9.95	14.95	FT-220 MOUNTING RACK for 3 receivers		2.25
BC-454 (3-6 MC) With tubes	9.95		FT-225 MOUNTING PLATE for BC-456		2.25
			BC-456 MODULATOR. For SCR-274.		4.50
			Complete set of 4 tubes for transmitter		1.25

C.A.P. SPECIAL BC-625 VHF TRANSMITTER

Freq. range 100-156 MC. With modulation section. Less tubes & crystals, with conversion dope. **\$9.95**
Used, good condition



H-16 V HEADSET. 8,000 ohms.	\$3.95	PE-125 POWER SUPPLY: Operates on 12 or 24 v. battery. NEW	\$17.95
HS-18 HEADSET. New	2.45	CD-307 EXTENSION CORD. For HS-23-33.	NEW .95
HS-23 HEADSET. High imp. New	4.95	RS-38 MIKE. NEW	4.95
HS-30 HEADSET. Featherweight type. Low imp. NEW.	\$2.49 USED..... 1.49	SCR-625 MINE DETECTOR. New	\$9.50
HS-33 HEADSET. Low imp. New	6.95	BC-605 INTERPHONE AMPLIFIER. With dual mike input circuit. NEW	5.95
HS-38 HEADSET. USED. excel. cond	1.49	TELEPHONE REPEATER AMPLIFIERS:	
NEW	3.50	EE-89, New, with tubes	17.95
T-32 DESK STAND MIKE. New	5.95	EE-89, New	12.95
LIP MIKE. Navy type. New	.98	FL-8 RANGE FILTER	1.95

TUBES!	TUBES!	TUBES!	TUBES!	TUBES!	
161P4\$19.95	304TH\$8.95	5CP1\$4.95	3P17\$2.25	9002\$1.65	
16AP424.95	304TL8.95	5CP24.95	4AP101.49	90011.65	
16BP412.95	830-B2.75	5BP42.25	211D69	90031.65	
MP-22 MOBILE ANTENNA. MOUNTING RACK. Comp. with hardware. Per Pair \$4.95. Ea.	\$2.95	IN-4A L/R TUNING METER. Used	\$ 3.95	FL-5 RANGE FILTER	1.25
TU-17 TUNING UNIT. (2-3 MC.) For BC-223	2.95	FL-5 RANGE POWERED HAND SET—Used. excel.	14.50	cond. Per Pair	
I-70 "S" TUNING METER. NEW	2.50	PE-55 DYNAMOTOR 12 V input. 500 VDC @ 200 mls output. New	\$24.50	FIELD TELEPHONE. EE-8. Complete BAND NEW. SPECIAL. ONLY	27.50
WOBLATOR. See p. 43 Dec. '51 RADIO NEWS	5.95				
BC-1023 75 MC. MARKER BEACON RECEIVER. Complete with tubes. Mfg. rack. NEW	10.95				
TU-25 TUNING UNIT. (3.5-5.2 MC.) For BC-223 Xmtr. Used	2.95				

250 TL TUBES—Limited Quantity!
Only \$9.50 each
Save \$2.00! Order 2 for only \$17.00

\$5.00 MINIMUM ORDER ACCEPTED. All items subject to prior sale. All shipments F.O.B. warehouse, Calif. Residents add tax with remittance. 20% deposit required. Please specify shipping instructions with order. EQUIPMENT WANTED! Highest prices paid for all types of Electronic Gear!

ARROW SALES, INC.

Cable Address: ARROWSALES POPlar 5-1818

Mailing Address:
P. O. Box 3872-R, N. Hollywood, Calif.
Office-Warehouse:
7440 Yarn Ave., N. Hollywood, Calif.

4 for 53 NEW Trav-Electric CONVERTERS

CHANGE 6 OR 12 VOLT D.C. TO
110 VOLT A.C. 60 CYCLE
Just plug into Cigar Lighter on Dash.



**Trav-Electric
Super**
Model 6-71160
60 cycle
60-75 Watts
\$37⁹⁵
LIST

Size
4"x5"x6"

Operates

- Wire Recorders
- Amplifiers
- Soldering Iron
- Dictating Machines
- Turntables
- Small Electric Drill



**Trav-Electric
Master**
Model 6-51160
60 cycle
40-50 Watts
\$24⁹⁵
LIST

Size
4"x5"x6"

Operates

- Curling Irons
- Radios
- Turntables
- Small Dictating Machines
- Test Equipment, etc.
- Portable Phonographs



**Trav-Electric
Senior**
Model 6-1160
60 cycle
35-40 Watts
\$15⁹⁵
LIST

Size 2 1/2"x2 1/2"x4 1/2"

Operates

- Test Equipment
- Turntables
- Lights
- Short, Long Wave Radios
- Portable Phonographs
- Electric Shavers, etc.



**Trav-Electric
Midget**
Model 6-11160
60 cycle
10-15 Watts
\$11⁹⁵
LIST

Size 2"x2"x3 1/2"

Operates Test Equipment, All Electric Shavers

Fully Guaranteed

See Your Jobber or Dealer

TERADO COMPANY

MFRS. OF PRECISION EQUIPMENT

1068 RAYMOND AVE. • ST. PAUL 14, MINN.

In Canada write: Atlas Radio Corp., Ltd.
560 King St. West, Toronto 28, Ont.

Export Sales Division: Scheel International, Inc.,
4237 N. Lincoln Ave., Chicago 18, Ill., U. S. A.

Cable Address—Horscheel


adapter, the v.h.f. sweep or marker signal beats against the u.h.f. oscillator of the unit, producing u.h.f. signals having the same characteristics as the v.h.f. input signal.

The company will supply full details on this and other units in its test equipment line on request.

TV BOOSTER

Electro-Voice, Inc. of Buchanan, Michigan is now offering a new, improved Model 3012-A, 3-tube automatic, all-channel television booster, for v.h.f. applications.

A new low-noise, broadband circuit

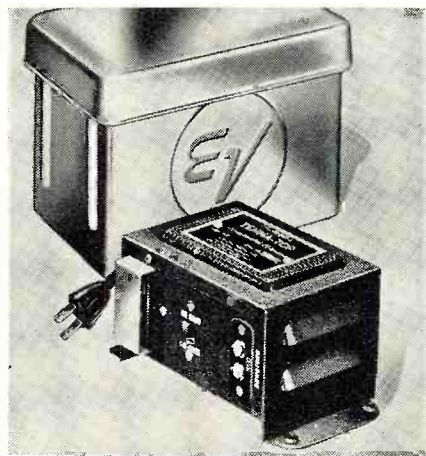

multiplies the signal at the antenna. Three tubes in balanced stages, including a power multiplier stage, are used to provide adequate gain for producing clear, sharp signals.

The booster unit is housed in a weather-resistant case which mounts on the antenna mast. The junction box plugs in between the receiver and an a.c. outlet. Input and output are to 300-ohm balanced line.

Bulletin No. 182, available from the company, describes the Model 3012-A in detail.

LEAD-IN WALL PLATE

A new television lead-in wall plate socket that requires no wall opening or outlet box has been announced by *Mosley Electronics, Inc.* of 8622 St. Charles Rock Road, St. Louis 14, Mo.

The new socket mounts flush on the wall or baseboard and may be installed in seconds with a screwdriver. Designated as the F-2, the new unit was designed to meet the need for plug-in convenience. The socket is available in brown or ivory molded polystyrene and is supplied with mounting wood screws. It is also available packaged with one mating constant-impedance solderless plug.

Write the company direct for additional information.

TUBE SALVAGE

Kahle Engineering Co. of 1307 Seventh Ave., North Bergen, N. J. has developed and is manufacturing a combination neck cutting and neck splicing machine that will salvage larger size cathode-ray picture tubes. Rejected tubes in 24", 27", 30", 33",

and larger sizes can be easily and rapidly returned to the assembly-line as all operations are performed with one handling of the bulb.

The Model 2185 is a single head machine that takes all standard sizes and shapes of tubes. The neck cutting operation is performed by the hot-chill method, producing a clean, square cut. The cut-off mechanism is adjustable up and down. Neck tubing can also be cut.

The company will supply complete specifications and performance data on this unit to manufacturers writing the firm direct.

TUBULAR TWIN-LEAD

A new tubular twin-lead for u.h.f., designed so that attenuation is negligible under all weather conditions, has been announced by *Plastoid Corporation* of 42-61 24th St., Long Island City 1, New York.


Known as "Synkote Ultratube", the new transmission line has the leads spaced several millimeters within the tube, equidistant from the outer insulation. Thus the magnetic field between them is unaffected by any moisture or salt which may condense on the outer covering and the signal strength is maintained at a maximum all the way down to the receiver.

The new twin-lead can be used not only for u.h.f. but for peak transmission of v.h.f. signals in stormy weather, in fringe areas, and in sea-coast areas where moisture and salt spray are factors.

NON-CORNER HORN

A non-corner horn, tradenamed "The Purest", has been recently introduced by *Gately Development Laboratory*, Barrington, N. J.

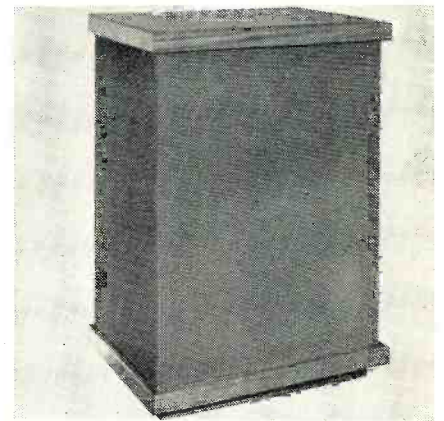The unit is a new type baffle employing a horn load on the back side of the speaker it encloses for improved low-frequency response, at the same time permitting direct radiation of high frequencies. The enclosure is designed for use along any wall and does not rely on the walls of the room to act as an extension of the horn. The unit gains adequate horn mouth



area by exhausting on three sides of the enclosure. Total fold of the horn is 180 degrees.

"The Purest" is available for 12 or

15 inch speaker systems. Standard finishes are dark mahogany, blonde, and natural mahogany. It is also available unfinished for those who desire to do their own finishing. Over-all dimensions are 38" high, 28" wide, and 18" deep. Technical literature is available on request.

"CUSTOM SOUND ENSEMBLE"

The General Electric Company has announced additions to its line of audio products which will be marketed under the name "Custom Sound Ensemble".

The ensemble consists of a pre-amplifier control unit, a 10-watt ampli-



fier, and a dualcoaxial speaker. A three-speed record changer equipped with the company's variable reluctance cartridge is used with the system for demonstration purposes.

All units are so designed as to make them adaptable to either custom installation or as separate furniture pieces.

Full details on all of the units comprising the new line are available from G-E dealers and distributors.

24-INCH TUBE

CBS-Hytron of Salem, Massachusetts has recently added the Type 24TP4 to its line of television picture tubes.

This 24-inch rectangular, 90 degree, all-glass, magnetically-focused picture tube provides an effective screen area of over 370 square inches. It features an aluminized screen for increased brightness, spherical filter-glass face plate, single ion-trap gun design, and an external conductive coating which serves as a filter condenser.

Performance and engineering data on the Type 24TP4 are available on request.

HI-FI COMPONENT LINE

The Engineering Products Department of Radio Corporation of America recently introduced its initial line of matched high-fidelity sound reproduction system components.

Although the new components will be marketed individually to preserve the flexibility and freedom of choice demanded by most hi-fi enthusiasts, characteristics are carefully matched to insure maximum performance in any system.

Built around the "Olson speaker", the line will include a deluxe three-speed automatic record changer, two AM-FM tuners (one a deluxe instru-

SEE LEO FIRST FOR . . .

hallicrafters

I can SAVE you money . . . Liberal Trade-ins



LEO I. MEYERSON WØGQ

SEE US FIRST FOR THE NEW SX-88 RECEIVER!



\$179.50

S-76 RECEIVER

Extra selectivity with double superhetrodyne circuit. One RF, two conversion and 3 IF stages. Range 550-1550 Kc, 1.7-34 Mc in four bands. 8 tubes plus voltage regulator and rectifier. Complete with tubes, less speaker.



\$224.50

SX-71 RECEIVER

Double Conversion sharp selectivity, plus built-in NBFM at moderate cost. 11 tubes plus voltage regulator and rectifier. Low down payment.

NAME YOUR TERMS • LOW DOWN PAYMENTS • PERSONALIZED SERVICE

HALLICRAFTERS RECEIVERS AVAILABLE FOR IMMEDIATE SHIPMENT

S-81	\$49.50	S-40B	\$119.95	ST-83	\$129.95
S-82	\$49.50	S-53A	\$ 89.95	S-78A	\$ 89.50
A-84	\$99.50	S-72L	\$119.95	SX-62	\$299.50
S-38C	\$49.50	S-77A	\$119.95	S-72 Portable	\$109.95

R-46 Speaker \$19.95

NEW 100 WATT HT-20 XMTR—\$449.50

Famous WRL RADIO REFERENCE MAP 25c



CU on 10-20 & 75 Meters

NEW LOG BOOK 25c

For mobile or fixed station. Spiral binding. Full column log listing all FCC required info. Will accommodate 1,525 stations. "Q" signals, phonetic alphabet, amateur international prefixes.

PHONE 7795


WRITE—WIRE



IT'S NEW! IT'S FREE!

WRL 1953 CATALOG

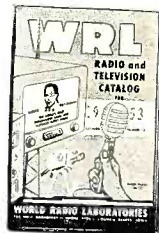Send for your copy today. Contains everything new in radio and television. Jam-packed with bargains. Leo I. Meyerson, WØGQ



Send For FREE Copy

WORLD RADIO LABORATORIES
744 West Broadway
Council Bluffs, Iowa

R-8

Please send me:

- Radio Map 25¢
- New Catalog
- Used Equipment List
- SX-71 Info
- S-76 Info
- New Log Book 25¢

Name

Address

City

State

SAVE UP TO 60% ON PICTURE TUBES

Add To Your Profit By Letting NATIONAL Rebuild Your Duds

LOOK AT THESE LOW PRICES

Exchange old tubes direct with the factory and double your profits on tube replacements. Our new process gives you a tube with a new phosphor screen, new inside-dag, new electron gun. Exhausted to highest standards. All tubes meter and set tested.

EVERY TUBE CARRIES A 1-YEAR NEW TUBE WARRANTY.

How To Order

Send old tubes direct to National, together with check or money order for quantity desired at prices quoted here. We ship you new tubes immediately. All tubes sold F.O.B. Blue Springs, Mo., but we pay incoming freight on tubes shipped to us in quantities of 5 or more.

Over 17-inch to 21-INCH TUBES
18.85
Plus 10% Fed. Excise Tax
Up to and Including 17-INCH TUBES
14.85
Plus 10% Fed. Excise Tax

National Picture Tube, Inc., Blue Springs, Mo.

BC-645 TRANSMITTER-RECEIVER

15 Tubes 435 To 500 MC
Set can be modified to use for 2-way communications, voice or code on following bands; ham band 420-450 mc., citizens radio 460-470 mc., fixed and mobile 450-460 mc., television experimental 470-500 mc. 15 tubes (tubes alone worth more than sale price!); 4-7F7, 4-7H7, 2-7E6, 2-6F6, 2-9X5 and 1-WE316A. Now covers 460 to 490 mc. Brand new BC-645 with tubes, less power supply in factory carton. Shipping weight 25 lbs.

BRAND NEW

\$4950

each

CONVERSION DIAGRAM INCLUDED!

PE-101C DYNAMOTOR for above BC-645..... **\$4.85**UHF ANTENNA ASSY, for above BC-645..... **\$2.45****SCR-274N COMMAND & ARC-5 EQUIPMENT**

Type	Excellent USED	BRAND NEW
BC-453 Rcvr. 190-550 Kc.	\$28.50	\$44.50
BC-454 Rcvr. 3-6 Mc.	12.50	24.95
BC-455 Rcvr. 6-9 Mc.	12.95	17.95
Rcvr. 1-5-3 Mcs.		34.95
BC-456 Modulator	2.75	5.75
BC-457 Xmtr. 4-5.3 Mc.	18.50	29.50
BC-458 Xmtr. 5-3.7 Mc.	9.75	37.50
BC-459 Xmtr. 7-9.1 Mc.	13.95	24.45
BC-450 3 Rcvr. control box	1.49	2.45
BC-451 Xmtr. control box	1.25	1.95
3 Receiver rack	1.79	3.25
2 Transmitter rack	1.59	3.25
Single Transmitter rack		3.25

ARC-5/R28 RECEIVER. 10 tube superhet. 100-156 Mc. Incl. tubes..... **\$27.95**ARC-5/T23 TRANSMITTER. Companion for above. Brand new..... **\$59.50****SELSYN 2J1G1**

Operates from 57½ V.
100 Cycles. Suggested wiring for 100 V. 60 cycle included.
New, tested
Price each..... **\$4.50**

BEACON RECEIVER BC-1206C

Receives A-N beam signals. Tunes 195 to 420 Kc. 4x4x6½" Wt. 4 Lbs. Complete with 9 tubes. Brand new..... **\$13.50**
Same as above. Used excellent..... **\$8.95**

HEADSETS

Model	Excellent USED	BRAND NEW
HS-23 high impedance	\$2.95	\$4.75
HS-33 low impedance	2.45	5.75
HS-30 low imp (featherwt)	1.49	2.45
H-16 U high imp (2 units)		4.95
CD-307A cords, with PL55 plug and JK26 jack, 8' long		1.19

DYNAMOTORS

TYPE	INPUT Volts	OUTPUT V	Excellent USED	BRAND NEW
PE-86	28	224 @ .06	5.27	9.50
DM-28	28	224 @ .07	3.50	5.95
PE-101C	12/24	400 @ .13	2.75	4.85
PE-103	6/12	500 @ .16	22.50	34.50
PE-94	28	300 @ .2	4.35	7.95
DM-32	28	250 @ .06	2.50	6.50
DW-21	23	1000 @ .09		16.50
DW-77	12	1000 @ .35		29.50

MICROPHONES

Model	Excellent USED	BRAND NEW
T-45 Lip Mike, navy type	\$0.49	\$1.45
T-30 Thread Mike	.49	.85
T-32 Desk Stand Mike		4.95

MODULATED BC-221-AK FREQUENCY METER

BRAND NEW..... **\$210.00**
BC-221 (Non-modulated) Reconditioned, PERFECT! Complete with tubes and crystal..... **\$129.50**


WILLARD 6-VOLT MIDGET STORAGE BATTERY

3 amp hr. Brand New. 3½" x 1-13/16" x 2¾". Uses standard electrolyte..... **\$2.85**

WILLARD 2-VOLT STORAGE BATTERY

20 Amp Hr. BRAND NEW..... **\$2.69**

1 Qt. electrolyte for above (fills 2 cells)..... **\$1.49**

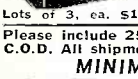NATIONAL TURRET TV BOOSTER

BRAND NEW..... **\$1000**
FACTORY PACKED..... **\$11.95**

Lots of 3, ea. \$10.95. Single lots..... **\$11.95**

Please include 25% deposit with order—balance C.O.D. All shipments F.O.B. our warehouse N.Y.C.

MINIMUM ORDER \$3.00

G & G RADIO SUPPLY COMPANY

51 VESEY STREET • NEW YORK 7, N. Y.
Branch: 7123 Bryn Mawr Ave., Chicago, Ill.

ment with built-in preamp), four different high-fidelity amplifiers, three hi-fi speakers (8", 12", and 15") and separate speaker and equipment enclosures.

The line will be marketed through RCA electronic parts distributors and is expected to be available in September.

SX-88 RECEIVER

The Hallicrafters Company of Chicago has recently introduced its SX-88 communications receiver which has been designed to replace the company's SX-28.

The new receiver is said to offer an exceptionally high degree of usable



selectivity, incorporate a new audio system which provides for standard broadcast reception with near high-fidelity quality, and features a reduction of selective fading in short-wave reception.

The unit uses 17 tubes, plus voltage and current regulator and a rectifier. Six tuning bands cover a range from 535 kc. to 33 mc. Over-all dimensions are 20" long, 10¾" high, and 18¼" deep. It weighs 65 pounds.

The SX-88 is currently available at dealers.

TRANSMISSION LINES

Fenton Company, 15 Moore St., New York 4, New York is featuring two new products, "Fentube-Airspaced" and "Twistube" which are designed to give better reception on u.h.f. and v.h.f. by reducing interference pickup.

The "Fentube-Airspaced" uses one common covering tube which surrounds and is fused to the spiral cords to the extent of from about 180 to 270 degrees of a circuit. There is practically no dielectric between the conductors.

"Twistube," besides being air-spaced, incorporates the added feature of being transposed to equalize the average proximity, and thus the capacity, of both conductors in relation to the mast and other grounded objects. The twin conductors are uniformly transposed which drastically reduces interference pickup. —30—

TRANSISTOR PRICE CUT

Raytheon Mfg. Co. of Newton, Mass., has announced a new low user price of \$4.50 for its CK722 junction-type transistors.

The price reduction, according to a company spokesman, was made possible by the greatly increased production of these units.

SUMMER CLEARANCE PRICES SLASHED**T.V. TUBES—ROCK BOTTOM PRICES**

In lots of 6 each No. only

6BG6	89c	6CB6	39c	6AG5	38c
19BG6	89c	6AK5	69c	6CP6	\$1.05
12AX7	60c	6BQ6	57c	6S4	49c

Tube Special—Broken Keys—Electrically Perfect
12A6... 29c; 4 for \$1.00

Tube Sale—2A7-55-27-85-31-56. No Mixed Ass't. 6 of Any Type \$2.25

Heavy Duty Shielded P.P. Input Trans..... \$1.00
H.D. Silver Contact Trans. Keys..... 1.00
Bat Handle S.P.S.T. or D.P.S.T. Toggle Switch..... 25c
Insulante Octal Panel Clamp Sockets..... 3c ea.
100 Assorted Resistors..... \$1.95

1 Mfd., 1,000V Oil Filled Cond..... 75c
2 Gang Var. Cond. 456 K.C. with Osc. Section. 234 in. Pulley on 3/8" Shaft..... 49c

Westinghouse Kuprox Rectifier 0.64 Amp. 28 Volts. Reg. \$11.00 ea. Special..... \$1.95

BRAND NEW 10" PHONO RECORDS—Ass't. Jazz—Popular. Rhythm—Blues. Rhyth. Specif. 12 for \$1.79 or 24 for \$3.00

Single Pole—10 Pos. 2 Gang Switch..... 29c

Grind your own Crystals. Pure Brazilian Quartz. Various sizes and thicknesses. ¼ lb. pkg..... \$1.00

4 Tube Drilled Chassis. 4 1/2"x6 1/2"x1 1/2". 29c each

Signal Corps Phones—2 M. Ohms (8 M. Ohms Imp.)..... \$1.25

2 Ft. Ext. Cord (and Plug)..... 40c

TOBE TUBULAR ELECTROLYTICS

20-20 MFD. 150 V..... 49c 30-30 MFD. 150 V..... 57c
40-40 MFD. 150 V..... 59c

Low-Loss Short Wave Lock Type Air Trimmer Variable Condensers

5 Pl.—20Mmf. 14c

7 Pl.—25-30 Mmf. 15c

8 Pl.—30-35 Mmf. 16c

14 Pl.—56 Mmf. 24c

1,000 OHM WIRE WOUND POTENTIOMETER..... 15c
30 HY-FILTER CHOKE SHIELDED 3 for \$1.25

PIEZO CRYSTAL HOLDERS... 12 for \$1.00—\$6.00 per C

RCA Band Switches—3 gang, 3 pos. 3 band. 30c 6 gang, 4 pos. 4-5 band. 40c

Trimmer-Padder Ass't.—all isolante—singles, dual: triplex—100 ass't. \$2.25

ATTENTION: Prospectors, Explorers for Hidden Treasures! Construct a U.S. Army Type of Metallic Mine Detector Amplifier. Amplifier unit only (less tubes and batteries) with cables, headphones, cord, and jack. Army wiring diagram. Type AN/PRS-1..... \$1.95

Phileco push button Rotary Switch Double Pole..... 35c

8 or 9 Gang Push button Switch..... 49c

DRILLED CHASSIS FOR 5-6 tubes 5"x10"x1 1/2". 25c

PHONO JACKS—OPEN & CLOSED AUTO..... 15c

156-1 RATIO VERNIER DIALS—4 in. 9/16 in. Hub. 35c

SALE—PHONO RECORD ALBUMS—12" 3 comp.—15c; 10" 3 comp.—15c; 4 comp.—20c; 12 comp.—69c

VULCAN HEAVY DUTY 100 WATT SOLDERING IRON. Built for U.S.N.—Brand New—Compl. set for \$8.50..... OUR PRICE \$2.99

MINIMUM ORDER \$3.00—NO C.O.D.

SHIPMENTS—PLEASE INCLUDE POSTAGE

NEWARK SURPLUS MATERIALS CO.

324 Plane Street, Dept. A, NEWARK 1, N. J.

Selected Surplus Components

For INDUSTRY • AMATEUR • SERVICEMEN
Completely Guaranteed

Special #1 1000,000 KC Crystal—CR-48/U—GRV—Hermetic Seal 1/2" Spacing..... Ea. \$3.95 10 for \$35.00 Lots of 50— 2.95 ea.

Special #2 0-30 Micamps DC—Weston 301—(See July issue for foto) MFD—for Test TS 62—No. KS9490..... Ea. \$9.95

Special #3 Telex Pillow Speaker—LIKE NEW..... Ea. \$1.95

Special #4 RG59/U—72 Ohm Coax—Approx. 150'/300' lengths. \$3.00 per Ft.

Special #5 TV Power Xformer—300-0-300 @ 225 MA; 6.3V-9A; 6.3V-1A; 5.0V-3A. NEW..... \$3.95

Special #6 VFO Assembly—Tank. Variable, Dial Calibrated 40-50 MC—Complete..... 2 for \$1.00

Special #7 ARC-3 Quartz Assembly—Ant. Osc. RF, 190-550 KC—Plug-In Unit—NEW..... Complete \$1.00

Special #8 Metal—GH6—Surplus..... 3 for \$1.00 Dozen \$3.00 Quantity Available

Special #9 Rheostat—80 Ohm—25 Watt—Screwdriver Adjust—Famous Makes—2 for \$1.00 Dozen \$4.50—Quantity Disc. Large Lot—Inquire—Many Sizes Available—NEW.

25% with order. Balance C.O.D. unless well rated.

GREENWICH SALES CO.

59 Cortlandt St., New York 7, N. Y., Digby 9-3813

GET INTO TV SERVICING

Send for free 24-page illustrated booklet which tells you how to become a successful TV technician. America's leading TV servicing school offers you a specialized training program that omits non-essential math & design theory. You concentrate on radio & TV servicing only. You get professional training & experience right in our full-equipment shops & laboratories. Send for this booklet today. Write Dept. R-83. No obligation—no salesman will call. Approved for Veterans

WESTERN TELEVISION INSTITUTE

341 W. 18th St. Los Angeles 15, Calif.

Within the Industry
(Continued from page 26)

until its net worth in 1953 was \$41,750,000 and its original six employees had increased to 10,000. Sales increased from \$63,000 in 1928 to \$168,730,000 in 1952. The company operates plants in Chicago, Quincy, Phoenix, New York, Philadelphia, Detroit, and Toronto for an aggregate of 1,500,000 square feet of space.

* * *

RALPH R. SHIELDS has been named to the newly-created post of product sales manager of television picture tubes for *Sylvania Electric Products Inc.*



He joined the commercial engineering department of the company's radio tube division at Emporium in 1948 as a senior engineer. He joined the merchandising department in 1950, assuming supervision of test equipment products. In the following year he was given an additional responsibility as supervisor of distributor sales engineering, which included a nationwide program of special projects and meetings. In October 1951, he was appointed merchandising supervisor, television picture tubes, with headquarters at Seneca Falls, N. Y.

* * *

CBS-HYTRON has purchased a 42,000 square foot plant in Lowell, Mass. which will be used to manufacture transistors and germanium diodes. Present plans call for the employment of up to 1000 people, but the company has taken an option on adjoining property for future expansion . . . **SPIRLING PRODUCTS CO., INC.** has built a new plant at Hicksville, Long Island which will enable the firm to increase production of its line of indoor and outdoor TV antennas. The new address is P. O. Box 411, Hicksville . . . **TRI-POINT MANUFACTURING AND DEVELOPING CO.** has moved into a new and modern plant at 401 Grand St. in Brooklyn, N. Y. The company specializes in the machining of plastics for the electronic, electrical, aircraft, etc. industries . . . The Statistical Department of **RADIO-TELEVISION MANUFACTURERS ASSOCIATION** has moved to new and enlarged quarters in Room 201, Bond Building, 1404 New York Avenue, N. W., Washington 5, D. C. . . . **ERIE RESISTOR CORPORATION** of Erie, Pa. is building a new plant for the manufacture of electronic and plastic products at Holly Springs, Mississippi, 40 miles south of Memphis, Tenn. . . . **HARRISON RADIO CORPORATION** has removed its Jamaica Branch from 172-31 to 144-24 Hillside Avenue in Jamaica to provide larger warehouse and sales facilities for its Queens and Long Island customers. The new location features convenient drive-in shipping



"Boy... Have I Got the Lines!"

You, too, can have the lines—that meet your exact leadline conditions — whether you are a TV Set Dealer or Service Organization making the finest television reception installations, or a TV fan that demands sharp, "SNOW-FREE" pictures.

We specialize in the manufacture of television transmission lines — built with only one idea in mind: "THE FINEST TELEVISION RECEPTION!"

For UHF and VHF

"SHEATH-LEED" — the all-weather leadline for the toughest conditions: Salt spray in coastal areas; hot, humid weather, or for frosty, icy, wintry wind-whipping conditions which impose a severe tax . . . Pure Polyethylene Tubing encasing Standard GOODLINE AIRLEAD.



"GOODLINE" AIRLEAD—standard of leadline excellence —with 80% of the loss producing web removed. Correct impedance for sharp, "snow-free" pictures. Of pure polyethylene with flexible stranded copper-clad conductors. MANY IMPORTANT FEATURES.

NEW FULL-WEB "SHEATH-LEED" — the pure polyethylene of "SHEATH-LEED" and full characteristics of GOODLINE AIRLEAD — but **NO PERFORATED WEB**. No 20 (7 strand 28) copper-weld wire in pure electronic golden clear polyethylene — with a pure silver-gray polyethylene sheath overall — for *Maximum Weather Protection*.

Don Good, INC.

SOLD BY LEADING JOBBERS & DEALERS

Send coupon NOW!
Get samples "in your hands"
—you'll realize why
Don Good Products make
the finest television
reception possible.

DON GOOD, INC. 1-7
1014 Fair Oaks Ave., So. Pasadena, Calif.
Please rush Samples and Complete Information covering Don Good Products.
Name _____
Street _____
City _____ State _____

CODE SENDING RECEIVING SPEED

Be a "key" man. Learn how to send and receive messages in code by telegraph and radio. Commerce needs thousands of men for jobs. Good pay; adventure, interesting work. Learn at home quickly through famous Candler System. Quality for Amateur or Commercial License. Write for FREE BOOK.
CANDLER SYSTEM CO.
Dept. 2-J, Box 928, Denver 1, Colo., U.S.A.

ARKAY
world's finest radio kits
Write for free Brochure
RADIO KITS, INC., 120 Cedar St., N. Y. 6

TUBES 60% OFF LIST
Original distributors boxed tubes, late code dates, full RMA guaranteed.
Only—RCA—Sylvania—G.E.


RCA Type No. 208T2 Vertical Blocking OSC 4.2:1 Potted, each **\$1.20** Lots of 3, **99c**
RCA 70° Yoke 209D1, Wired, **\$2.95**
RCA 44:1 Vertical Output XFormer, **\$1.99**

TERMS: 25% check or money order, balance C.O.D.

STUART ELECTRONIC DISTRIBUTORS, Inc.
Dept. A
149-09 Union Turnpike, Flushing 67, New York
Phone OL 8-3553

**SAVE
AT
NEWARK**

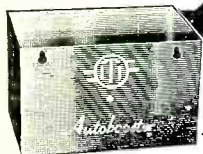★ **BARGAINS**
★ **SPECIAL
VALUES**
★ **SAVINGS**



**INDUSTRIAL TELEVISION
AUTOBOOSTER**
★ **only \$8.95**

Model IT-75A. Originally sold for \$26.43. Now available, while quantities last, at less than manufacturer's cost. Completely automatic operation—turns on or off and is tuned by the TV receiver. For all sets drawing up to 450 watts. With 1-6AK5 and 1-6CB6 tubes. Brown hammettone case. Shpg wt., 6 lbs.
90G171. Special Price..... **8.95**

BRUSH MICROPHONE

While They Last! \$5.95

Originally sold for \$8.61! Response, 50 to 6,000 cycles. Output level, —53 db. High impedance. Has 3/8" x 27 thread. Brown. Wt., 1 1/2 lbs.
54G350. Special Price..... **5.95**



**FAMOUS NAME
MIDGET CONTROLS**
10 of one type.. ONLY \$1.75

Save while quantities last! Flat 2" shaft with all fittings and hardware. All are linear taper except *audio and *series or cathode. Wt., per 10, 1 lb.

No.	Ohms	No.	Ohms	No.	Ohms
U-12	5,000*	U-33	50,000*	U-46	250,000*
U-14	5,000	U-34	50,000†	U-48	500,000*
U-18	10,000*	U-35	50,000	U-50	500,000*
U-19	10,000†	U-36	75,000*	U-51	750,000*
U-20	10,000	U-39	100,000*	U-53	1 Meg*
U-21	15,000*	U-40	100,000†	U-54	1 Meg*
U-22	15,000†	U-41	100,000	U-55	2 Meg*
U-24	20,000*	U-42	150,000*	U-56	2 Meg*
U-26	20,000	U-43	200,000*	U-57	3 Meg*
U-28	25,000†	U-44	250,000*	U-59	3 Meg*
U-29	25,000	U-45	250,000†	U-65	5 Meg*

TAPPED MIDGET CONTROLS

No.	Ohms	Tap	No.	Ohms	Tap
UT-420	250,000	50,000	UT-443	1 Meg	450,000
UT-425	350,000	70,000	UT-448	2 Meg	250,000
UT-427	500,000	100,000	UT-450	2 Meg	125,000
UT-429	500,000	50,000	UT-451	2 Meg	900,000
UT-431	500,000	225,000	UT-454	2 Meg	400,000

★ **Newark Specials** ★



2 Mfd. 600 VDC. General Electric Pyranol-filled capacitor. Flange type mounting. Ceramic pillar terminals, 10/32" studs. Size, 2x2 3/4 x 1". Wt., 1 lb
54G006. 10 for 3.00..... **Each 39c**

5 Mfd. 1000 VDC. Type BAR. Oil filled. Solder terminals. Size, 3 3/8 x 3 3/4 x 1 3/4". Wt., 1 lb
54G400. 10 for 7.50..... **Each 98c**

1 Mfd. 5000 VDC. General Electric Pyranol-filled filter capacitor. Large ceramic terminals. With mtg clamps. Size, 4 1/2 x 3 3/4 x 4 1/8". Wt., 3 lbs.
54G004. Special Price..... **4.95**

35 ohm, 50-watt Pot. Ohmite Type "J" wire-wound pot. Heavy ceramic form. 1/4" shaft for 3/8" mtg hole. 1 lb
54G587. 10 for 5.50..... **Each 69c**

Thordarson T-45166 Output Transformer. Single 6L6 to 2-4-8-500 ohms voice coil. Case size 2 1/2 x 2 1/2 x 3" high. Shpg. wt., 5 lbs.
54G581. 10 for 12.00..... **Each 1.50**

Driver Transformer. P.P. 2A3's to grids. Case size, 3 1/4 x 2 1/2 x 3" high. Shpg. wt., 5 lbs.
54G111. 10 for 15.00..... **Each 1.95**

Order from Dept. R-8

Send for **FREE Catalog**

NEWARK
ELECTRIC COMPANY

223 W. MADISON ST. CHICAGO 6, ILL.

and receiving platforms and 5000 square feet of service area on a single floor . . . **GATES RADIO COMPANY** of Quincy, Illinois has opened a new and larger office in New York City at 51 E. 42nd Street, across the street from the Airlines Terminal Building . . . **CBS-COLUMBIA INC.** has moved its administrative offices from its Brooklyn plant to its new Long Island City plant at 3400 47th Avenue . . . A second plant has been opened by **HEPPNER MANUFACTURING CO.**, Round Lake, Ill. manufacturer of television components. The new plant at Mendota, Ill. will be devoted exclusively to the manufacture of ferrite rod antennas and flyback transformers . . . **GENERAL ELECTRIC COMPANY** has opened a new tube warehouse at 3800 N. Milwaukee Ave. in Chicago. The structure provides almost 100,000 square feet of floor space and will serve as headquarters for the company's central regional sales organization for electronic tubes . . . **PHILCO CORPORATION OF CANADA** is erecting a modern, 80,000 square foot plant at Don's Mills, a Toronto suburb, which will be devoted to the manufacture of television receivers, radios, and other electronic equipment. The plant is expected to be ready for occupancy early in 1954. The company is currently operating in rented quarters in Toronto . . . **RAYTHEON MANUFACTURING COMPANY** has started a \$1,750,000 modernization program at the former Lowell (Mass.) Ordnance plant. The plant was occupied last November by the company and the modernization program is being carried out while the plant is in production . . . **SYLVANIA ELECTRIC PRODUCTS INC.** has announced plans for a new 416,000 square foot television set manufacturing plant to be built in Batavia, N. Y. The plant is expected to be completed by Feb. 1, 1954.

RAYMOND C. COSGROVE has been elected to the post of chairman of the board of the *National Company*, succeeding William A. Ready who retired recently.



Mr. Cosgrove was formerly executive vice - president of *Avco Manufacturing Corp.* and president of *Radio Television Manufacturers Association.*

Mr. Ready is the oldest official of an electronic manufacturing firm still active in the ARRL. He has been an official of the company for 38 years and until March of this year served as president and chairman of the board.

E. F. JOHNSON COMPANY of Waseca, Minn. has purchased the inventory, tools, dies, and rights to manufacture the *Signal* line of telegraph instruments and keys. The line was formerly manufactured by **SIGNAL ELECTRIC MANUFACTURING COMPANY** of Menominee, Mich. . . . A new organiza-

tion for the development and manufacture of electronic equipment has been formed under the name of **AMPLITRONIX INC.** at 280 Ninth Ave., New York 1, N. Y. Products include multi-waveform generators, projection scopes, electronic timers, and oscilloscope calibrators.

THE WESTERN ELECTRONIC SHOW'S ninth annual meet will open August 19th at the Civic Auditorium in San Francisco for a three-day run.

Almost 80 per-cent of the electronic manufacturers of this country will occupy 327 booths to display products used in broadcasting, communications, telemetry, servicing and installation accessories, etc.

The trade show is closed to the general public and no home receivers or other strictly consumer items will be displayed.

Four technical sessions daily will be sponsored by the (7th Region) Institute of Radio Engineers.

ATLANTA HAMFEST

THE Atlanta Radio Club, Inc., will hold its annual Hamfest on August 30th at Robinson's Tropical Gardens near Atlanta, Georgia. The menu will include fried chicken and free drinks, and the program features games and activities for YL's and XYL's as well as contests and a transmitter hunt for the men.

Admission will be \$3.00 for adults, \$1.75 for children. Reservations and further information can be had from R. R. Warren, W4RVH, 490 Angier Ave., N.E. (Apt. #3), Atlanta, Georgia.

MARS CD PLANS

BY JOINT agreement the Department of Army and the Department of Air Force have issued the policy indicated below to military commanders in the interest of providing guidance relative to civil defense planning.

"Within the scope and mission of the MARS program as approved and published, the use of MARS facilities as a military communications asset in support of Civil Defense will be governed by these policies. Within the current availability of personnel and equipment MARS may:

a. Make available communications services between the military forces in support of civil defense and the civil defense agencies.

b. Make available communications services for civil defense forces on a temporary or emergency basis when such services are not otherwise available.

c. Make available radio terminal facilities at designated military installations for civil defense tie-in as required.

d. Make these services available on military frequencies assigned to established MARS networks."

The military requirement for MARS and the availability of personnel, equipment, and frequencies during periods of national emergency will govern the extent to which MARS services can be made available to Civil Defense agencies.

A survey will be conducted by MARS in order to determine those civilian members who will be qualified and willing to participate in this communications support mission.

Home Security Radio

(Continued from page 62)

proximately 10 microvolts-per-meter.

A second series of trials was next made to compare the sensitivity of the receivers when situated in unfavorable reception locations. In this test all 1000 watt and less stations in a 100 mile radius were recorded without grouping according to power. The number of these stations which could be logged by each of the three sets was determined and the per-cent received was calculated. This pattern was followed for three locations: an above the ground site, a householder's cellar, and a "bomb shelter."

The A-2 receiver, when set up in the cellar, was provided with 20 feet of horizontal antenna one and one-half feet below grade. The "bomb shelter" was a culvert 33 feet long, 18 feet wide, and 7½ feet high, open at each end and overlaid by reinforced concrete and a secondary roadbed. The 17-foot horizontal antenna of the emergency receiver was positioned in the center of the culvert and perpendicular to its long axis. The three sites were geographically less than one-half mile apart.

The comparative sensitivity of two of the receivers in the three locations is shown in Fig. 4B. The security receiver is superior to the commercial four-tube portable at two sites but at

the third, the "bomb shelter," they appear as equal. Lack of apparent superiority of the A-2 receiver in the shelter site may be explained by the fact that there was no signal of intermediate strength. The culvert attenuated weak surface signals to a nondetectable level while strong original signals penetrated the culvert sufficiently to be heard by both receivers.

Immediately following an enemy attack on a large metropolitan area, each surviving household would require vital information and instruction to forestall panic. Instruction could be broadcast, lacking telephone and metropolitan broadcast service, by utilizing a sensitive battery-operated receiver tuned to a transmitter located in a neighboring community. A home security receiver designed for this purpose and operating from a single No. 6 dry cell is described. The sensitivity of this receiver assayed at ground level, in a cellar, and in a simulated bomb shelter was superior to a commercial four-tube portable vacation radio but less than that of a commercial communications receiver.


REFERENCES

¹ Caldwell, John M.; Ranson, Stephen W.; Sacks, Jerome G.: "Group Panic and Other Mass Disruptive Reactions," U. S. Armed Forces Medical Journal, April 1951.

² Schmidberg, W.: "Treatment of panic in casualty area and clearing station," Life and Letters Today, Autumn 1939.

³ Passow, E. E.: "Preselection in Inexpensive Broadcast Receivers," Electronics, September 1941.

-50-

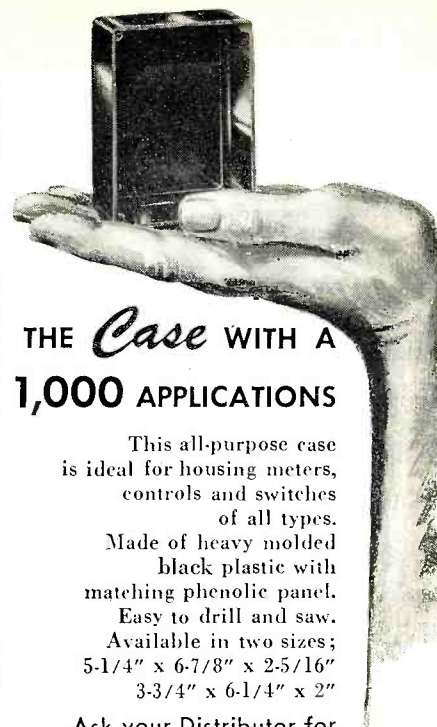

THE Case WITH A 1,000 APPLICATIONS

This all-purpose case is ideal for housing meters, controls and switches of all types.

Made of heavy molded black plastic with matching phenolic panel.

Easy to drill and saw. Available in two sizes; 5-1/4" x 6-7/8" x 2-5/16" 3-3/4" x 6-1/4" x 2"

Ask your Distributor for Waldom's Plastic Case.

**WALDOM
ELECTRONICS INC.**

911 Larrabee St., Chicago 10, Ill.

Presenting . . . at most moderate cost . . .

ESPEY

25th Anniversary "Trophy" Models

AM-FM CHASSIS • TUNERS • AMPLIFIERS



In commemoration of twenty-five years' experience in the manufacture and development of high-fidelity audio equipment, Espey is proud to present its distinguished "Trophy" models. Renowned for beauty of styling and excellence of performance, the new Espey models are so reasonably priced that for the first time magnificent listening pleasure is within the means of all lovers of fine audio reproduction.

Descriptive literature on the new Espey AM-FM chassis, tuners and amplifiers is now available . . . your inquiry is invited.

SYLVAN A. WOLIN & ASSOCIATES SALES CORP., 409 GRAND AVENUE, ENGLEWOOD, N. J.

WORLD'S LARGEST MANUFACTURER
OF CUSTOM BUILT TELEVISION

MATTISON


SILVER ROCKET 630 CHASSIS
• with TUNEABLE •

**BUILT-IN BOOSTER
for Better DX Reception**

Featuring NEW CASCODE TUNER
made for UHF interchangeable
tuning strips and 70° COSINE YOKE

Tube
Complement:
28 tubes
3 rectifiers
1 CRT

32

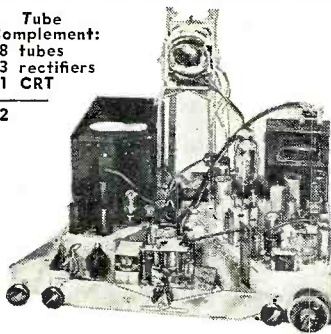

All Channel Booster

• Broad band single knob control pre-amplifier built in to eliminate long leads which may cause regeneration and attenuation of signal.

• ONLY THE MATTISON 630 CHASSIS HAS AN ALL CHANNEL TUNEABLE BUILT-IN BOOSTER THAT INCREASES SIGNAL STRENGTH UP TO 10 TIMES. THE SILVER ROCKET WILL OUT-PERFORM ANY CHASSIS MADE AND IS PRICED RIGHT TO SELL FAST WITH

AN EXTRAORDINARY MARGIN OF PROFIT FOR YOU. WRITE FOR CONFIDENTIAL PRICE SCHEDULE.

ALL CABINETS MADE IN MATTISON'S OWN CABINET FACTORY!

ANNOUNCING
the New
AMBASSADOR
for 1953

The only open face console made in every expensive decorator finish . . . on guaranteed genuine mahogany, walnut, oak and other rare woods!



The AMBASSADOR 17" and 21"
Best Looking . . . Best Value, Too!

Full size console for eye level television. Available in every expensive decorator finish. Featuring removable safety glass. Dimensions height 42 inches, width 26 inches, depth 23 inches.

DEALERS! SERVICE DEALERS! Here is your opportunity to become the "important" TV Dealer in your area for THE FINEST CUSTOM-BUILT LINE OF TV RECEIVERS. FREE!! Write for Mattison's merchandising portfolio explaining the "UNASSEMBLED PLAN" and "\$1,000,000 FLOOR PLAN."



Manufactured with integrity

When you buy from Mattison you need only one source of supply! You can buy a Mattison Chassis, a Mattison Cabinet or a complete Mattison TV Set!

Mattison Television & Radio Corp.

10 West 181st St., Dept. RN, N.Y. 53, N.Y.

Electronics for Yachtsmen

(Continued from page 67)

The radio direction finder has begun to find acceptance among small boat owners in recent years. Basically, it is a sensitive radio receiver with a very directional loop antenna which can be rotated on a compass-calibrated base. When beamed on known signal sources, generally RDF (radio direction finder) stations or charted broadcast stations, the boat's position can be established. Once this point is known, it is plotted on the chart and the new compass bearing determined. From there on it is a simple matter to hit the destination "on the nose."

While these are the only really important items needed aboard small craft, there are other pieces of electronic gear that contribute to the safety of the boat and the peace of mind of the captain. Moderate cost radio depth finders (fathometers) are now available and are being enthusiastically accepted by yachtsmen who cruise outside of charted areas. The instrument gives an indication of the depth of the water based on half the time it takes the signal to be transmitted from the boat to the bottom and return, with some allowance being made for mud penetration. In addition to preventing accidental grounding of the boat on hidden reefs, the fathometer is being used extensively to locate schools of fish whose massed bodies reflect the sound waves in the same way that the sea bottom does. Like the direction finder, the depth finder can be used to advantage in fogs and other closed-down conditions. By comparing depth readings from the graph with depth readings on the navigation charts, a fairly educated "guess" as to location can be made.

Since many small boats do not have the battery capacity to operate all this equipment for any extended period of time, extra generators (run from the motors), extra batteries (if possible), and shoreline battery chargers and eliminators are essential. Batteries can be recharged either at the boat's destination or in its home port. Power lines are run to the boat when in port and the charging handled there.

In addition to the safety radio equipment aboard a boat, many owners are adding such purely pleasure gear as television receivers and small portable radios. Television lends itself particularly well to use in close quarters and provides ready-made entertainment when in strange ports. Because of the load, it isn't practical to run the television receiver from the boat's battery supply but in port where it can be operated from power lines it is a real addition to the basic equipment. The requisite a.c. is available at most commercial and yacht club piers.

The boat, "Miss Eico", shown on

RADIO & TV TUBES

70 to 90% Off List

Write today for complete price list

YOUR INQUIRIES INVITED ON SPECIAL PURPOSE AND TRANSMITTING TYPES.

CONDENSERS

20-20—150V10 for \$2.95
40-40—150V10 for \$3.24
50-30—150V10 for \$3.24

HEAD PHONES

5 ft. moisture proof cord and phone tip terminals. 600 OHMS. Now only \$2.98 each per set.

TUBE REJUVENATORS

Increases the life of fading picture tubes. \$1.63 each.

RESISTORS

Sold only in assorted lots of 200 for the low, low price of \$1.98. Not insulated.

Hi-Lite Electronic Sales Co.

Dept. RN 837 18th Ave.
Irvington 11, New Jersey



RCA INSTITUTES, INC.


A service of Radio Corporation of America
350 West 4th St., New York 14, N.Y.

OFFERS COURSES IN
ALL TECHNICAL PHASES OF
RADIO, TELEVISION, ELECTRONICS

Approved for Veterans
Write Dept. RN-53 for Catalog

AUDELS TV-RADIO SERVICE LIBRARY

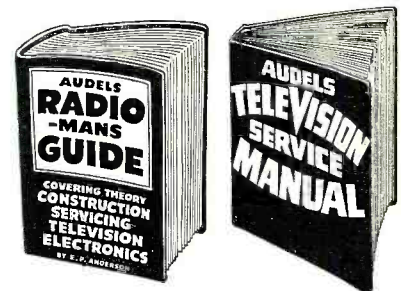HERE IS LATE INFORMATION IN A HANDY FORM FOR RADIO & TELEVISION REPAIRMEN, SERVICEMEN & STUDENTS



2 VOLS. \$6 COMPLETE \$1.00
PAY ONLY 1 MO.
IT PAYS TO KNOW!

AUDELS T.V.-RADIO SERVICE LIBRARY presents the important subjects of Modern Radio, Television, Industrial Electronics, F.M. Public Address Systems, Auto, Marine & Aircraft Radio, Phonograph Pick-Ups, etc. Covers Basic Principles—Construction—Installation—Operation—Repairs—Trouble Shooting. Shows How to get Sharp, Clear T.V. Pictures. Install Aerials—How to Test. Explains Color Systems & Methods of Conversion. 1001 Facts—Over 1260 Pages—625 Illustrations—Parts & Diagrams—Valuable for Quick Ready Reference & Home Study. Tells How to Solve T.V. & Radio Troubles—Answers T.V. & Radio Questions.

Get this information for Yourself.
7 DAY TEST—ASK TO SEE IT!

MAIL ORDER

AUDELS, Publishers, 49 W. 23 St., N.Y. 10
Mail AUDELS T.V. RADIO SERVICE LIBRARY 2 Vols. \$6 on 7 days free trial. If O.K., I will remit \$1 in 7 days and \$1 monthly until \$6 is paid. Otherwise I will return them.

Name _____
Address _____
Occupation _____
Employed by _____ RN

this month's cover is a 31-foot cabin cruiser which carries a full complement of electronic devices including a *Jefferson Travis (Emerson)* 35-watt radiotelephone. The unit covers four bands and a spare (two ship-to-ship; one Coast Guard emergency; one marine—*Bell System*—telephone channel; and the spare). Calls may be made to any telephone by contacting the nearest marine telephone operator. The cost of the call is the regular toll charge plus an additional fee of \$1.00. There is no monthly carrying or minimum charge.

The boat also carries a *Bludworth Marine* radio direction finder, the Model DF1029A. This unit covers three bands (one of which is the broadcast band) and has a range of 125 miles. It will operate on 6, 12, or 32 volts d.c.

The depth finder aboard the craft is a *Bendix* recording model which is capable of measuring depths from 0 to 100 fathoms (0 to 600 feet). It has a single range and may be operated from either 12 or 32 volt power sources.

Other units include a *Surette* battery charger (12 volts) and an *Eico* Model 1040 battery charger for 6 and 12 volts. This latter unit can be used to provide the requisite 6 volts needed to operate small appliances aboard the boat, the major pieces of electronic gear being operated by either 12 volts d.c. or 117 volts a.c. The a.c. is available in ports and is fed into the boat by means of an outlet in the rear cockpit. The boat carries dual wiring which permits the lights, battery charger, small appliances, the television set, etc., to be run from the a.c. power lines when the boat is docked. The Model 1040 battery charger also provides power for the regular 6 volt gear when in port.

A meter to measure transmitter output is an extremely useful item as it tells at a glance whether or not your signal is getting out. A "Chargicator" which indicates the charge on any of the boat's four batteries by a flip of the switch completes the operating gear aboard. In addition, a television receiver and a radio receiver are provided for the entertainment of guests.

While all of the equipment aboard is standard, it may be a little more elaborate than that desired by the average boat owner. Radiotelephone units (*RCA, Pearce-Simpson, Hudson-American, Fisher*, etc.) range in price from around \$230 to \$760. They may be obtained with as few as two channels or as many as six and provide coverage from a minimum of 20 to 200 miles. Installation charges are extra. Crystals for the various bands run about \$15.00 a pair. Antennas for use with such equipment range in price from a modest \$25.00 for a home-built unit comprising a bamboo pole, some wire, and a swivel socket to a commercial unit in the \$80 price class. Incidentally, the swivel socket is a "must" for sailing under stationary bridges or up tree-lined inlets, etc.

THIS **NEWEST** WELLER GUN INVITES COMPARISON

NOW 275 WATTS

COMPARE It To The Soldering Tool You Now Use

COMPARE It To Any Soldering Tool On The Market

Here's the professional tool with all the features you've wanted for fast, dependable soldering.

- **COMPARE the soldering capacity.** This newest Weller Gun handles up to 275 watts. Four new models from 100 to 275 watts give full coverage of heavy or light soldering.
- **COMPARE the performance.** 5 second heat saves time and current. Dual heat gives extra soldering capacity. Thermostatic control instantly and automatically regulates tip temperature.
- **COMPARE the comfort.** This newest Weller Gun floats in your hand. Perfect wrist-action balance and streamlined design, with pistol grip centered under housing, provide easier operation.
- **COMPARE the versatility.** There are 4 new Weller models—heavy duty, light duty, single heat and dual heat. And 2 new accessory tips are available for all models. A hot knife-blade cutting tip and a trowel-shape smoothing tip add to the practical uses of a Weller Gun.
- **COMPARE the reputation.** This newest Weller gun is backed by the *first* name in the soldering gun field. Over a half-million Weller Guns are used by professional servicemen and craftsmen. See this *newest* Weller Gun at your Distributor or write for Bulletin direct.

Weller
SOLDERING GUNS

Better from Grip to Tip!

810 Packer Street
Easton, Pa

**JUST SEND \$1
for YOUR CHOICE**

OF THESE BARGAINS!

CRYSTAL HEARING AID MIKE..... only \$1
40 MICA CONDENSERS (Assorted)..... only \$1
45 CERAMIC CONDENSERS (Assorted)..... only \$1
75 RESISTORS (Assorted)..... only \$1


Send check or money order—WE PAY POSTAGE

PHILIP GLICK & CO.
256 Greenwich St. New York 7, N. Y.

Unlimited Opportunities in
RADIO ENGINEERING

DEGREE IN 27 MONTHS

Complete Radio Engineering course, including Telev., U.H.F. and E.M. Bachelor of Science Degree also in Mech., Civil, Elect., Chem., and Aero. Eng.; Bus. Adm., Acct. Extensive campus, modern buildings, well equipped labs. Low cost. Prep courses. Personalized, practical instruction. Founded 1884. Placement service. Growing shortage of engineers. Prepare now for unlimited opportunities ahead. Approved for Korean vets. Enter September, January, March, June. Write for catalog.

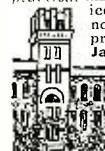

TRI-STATE COLLEGE

1683 College Avenue, ANGOLA, INDIANA

Direction finders fall in the \$200 to \$400 price class and range from units which operate from four self-contained batteries and cover 100 miles to units which operate from the boat's 6, 12, or 32 volt power supply, cover three bands, and are effective for distances up to 125-200 miles. One recently announced unit which has been especially designed for small boats and lean pocketbooks is being offered at a price in the neighborhood of \$85.00. This simple device consists of a receiver capable of tuning the marine, aircraft, and local broadcast bands, an earphone, and an antenna.

Depth finders, as produced by *Bendix* and *Raytheon*, are priced from \$350 to around \$1000 depending on the features incorporated. One modestly priced unit features a rotating disc and indicator light. It reads from 1 foot to 160 feet. Another model has two ranges, one for 1-100 fathoms and the other for 1-200 fathoms, while a still more elaborate version keeps a permanent record of the bottom over which the boat is traveling.

Needless to say, there are any number of other devices which can be included should the size of the boat and the wishes of the owner so dictate. *Radiomarine Corp.* is now offering a compact 3.2 cm radar unit which has been designed for small craft while a photoelectric-type automatic pilot which operates on the gyro principle is being made available to yachtsmen who do a lot of open-water cruising over long distances.

While many of the items described herein may appear to be unduly elaborate for a small craft, in reality none of the items could be considered "luxuries" since, in conditions of fog or bad weather, every single piece of electronic gear becomes a "life-line" which may be responsible for saving the crew and/or the boat itself—a point well worth considering.

No matter how few or how many

pieces of electronic equipment you have aboard, take the word of an experienced "skipper" when he advises that the more protective devices available the more comfortable and trouble-free the cruise. Being ready for any emergency is one of the marks of an "old hand". Electronic gear helps you to anticipate such emergencies and handle them smoothly should they be unavoidable. —30—

DELTA CONVENTION

AMATEURS of the Delta District will hold a convention in New Orleans on September 5-6 at the Jung Hotel on Canal Street.

Sponsored by the Greater New Orleans Amateur Radio Club and by the West-side Radio Club of New Orleans, a full program of sightseeing, convention sessions, and displays has been planned for amateurs and their wives.

Contact A. L. Powell, W5MXQ, at 224 Hollywood, New Orleans 20, La., for further information. —30—

HAM CLUB ACTIVITIES

THE Baltimore Amateur Radio Club, Inc. has scheduled its Sixth Annual Hamfest-Picnic for Sunday, August 9th at Triton Beach, Mayo, Maryland. Tickets are \$1.00 per person (children half price) and include the use of the bathing facilities, bath-house, locker, use of picnic tables, and pavilion.

An interesting program has been planned and there will be awards for the best mobile installations. The festivities are scheduled to start at 10 a.m. W3PSG will be on hand to guide visiting mobiles.

For further information write Chairman Ernie Dobos, W3JCL, 2208 North Fulton Avenue, Baltimore 17, Maryland. * * *

THE Seventh Annual Ham Outing of the Buckeye Shortwave Radio Association will be held August 30th at Happy Days Camp, Virginia Kendall Park, located just north of Akron, Ohio on Route 303, .8 mile west of Route 8.

Registration is set for 2 p.m. with a fee of \$2.00 per family. Prizes for young and old have been provided. For further details contact R. J. Nuss, W8KDW. —30—

CUT HOLES 1/2" to 3 1/2" IN RADIO CHASSIS



WITH A GREENLEE RADIO CHASSIS PUNCH

● Save hours of work... no reaming or tedious filing. Punch cuts through chassis quickly... makes accurate, clean holes for sockets, plugs, and other receptacles. Just turn with an ordinary wrench. There's a GREENLEE Punch in each of these sizes: 1/2"; 5/8"; 3/4"; 7/8"; 1"; 1 1/8"; 1 1/4"; 1 1/2"; 1 3/4"; 1 7/8"; 2"; 2 1/4". Write for complete facts. Also get information on Knockout Punches and Cutters for conduit and meter holes up to 3 1/2". Greenlee Tool Co. 1888 Columbia Avenue, Rockford, Illinois.


TOOLS FOR CRAFTSMEN

GREENLEE



END BATTERY TROUBLE!!

WITH THE AMAZING NEW AND PROVEN **SELECT-A-CHARGE — WATTAGE REGULATOR**
 Revolutionary New Invention In Voltage Regulation
SENSATIONAL NEW DASHBOARD CHARGE-LEVEL CONTROL
 Greatest Feat In Auto-Electric Since The Self-Starter
 UNCONDITIONALLY GUARANTEED — LUCRATIVE TERRITORIAL OPPORTUNITIES. CLEARLY ILLUSTRATED CATALOG ON THIS AMAZING DISCOVERY FREE — WRITE...
 SCIENTIFIC ELECTRIC CO. • BOX 2162G CLEVELAND 8, O.

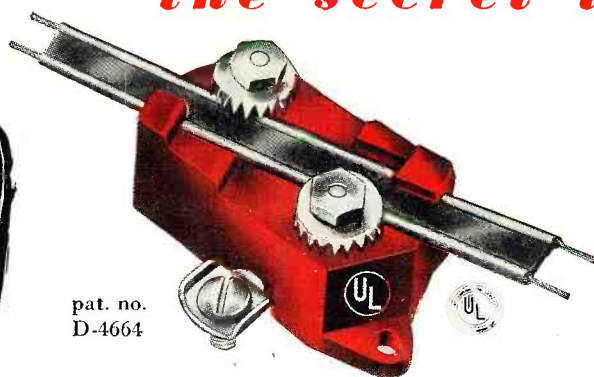

pat. no. D-4664

the only lightning arresters with the strain relief lips are made by JFD. A patent is its proof!

JFD MANUFACTURING CO., INC. BROOKLYN 4, N.Y.

World's largest manufacturer of TV antennas and accessories

the secret is in the LIPS!



"Little Giant" LIGHTNING ARRESTER

for flat and oval jumbo twin lead
 No. AT105 (with hardware for wall or window sill mounting) \$1.25 list
 No. AT105S (with stainless steel strap for universal mounting) \$1.50 list

Spot Radio News
(Continued from page 18)

install . . . new communication techniques and facilities . . ." is back in officialdom once again with another transoceanic telecasting proposal. Under consideration now is a "Narcom" or North Atlantic Relay Communications, system, which calls for relays from this country to London, by way of Canada, Greenland, Iceland, and so on.

In the earlier plan which revolved about Near East operations about twenty relay stations were envisioned. It was estimated that the network equipment alone would cost up to \$15 million, while annual network operation would involve a budget well over a quarter of a million dollars. Cost of operating each of the relay stations would be about \$25,000, and programming could run up a figure of \$10 million. Then there would be the technical problem and cost of servicing and maintenance not only the transmitters and associated gear, but projection receivers, also included in the project. According to Senator Mundt who sponsored the measure, only \$3 to \$4 million would be required at the beginning and only about 5000 receivers would suffice.

In its present form, the global plan would be included within a "Voice of America" program and probably supplement or supplant audio transmissions to certain countries.

EDUCATIONAL TV, which reached a climactic stage a short time ago, as the deadline for reserved channels passed, with little reaction from commercial interests, recently received strong support from the headman of the Senate Interstate and Foreign Commerce Committee, Senator Charles W. Tobey.

Reviewing FCC's position on school television, the Senator said: "I shall keep a watchful eye on each and every one of these 242 channels for education, and upon the slightest evidence that the FCC is about to weaken and to delete one of them or substitute a substantially less valuable channel for one of them, I shall call for a full-scale investigation."

Others supported the Senator. Congressman Heller pointed out that few are aware of the . . . "importance of the action taken by the FCC or of the great significance of the gift it has presented to the American people." He felt that reservations of the educational channels should continue indefinitely, regardless of pressure from the commercial world, or the statement included within the freeze-lift order.

Approval of a move to delay cancelling of the special channels, was also voiced during the nomination hearings of Commissioner John C. Doerfer. Senator John Bricker noted that educational television offers great


**ORDER BY MAIL FROM
WHOLESALE RADIO**
Low Prices • Complete Stocks • Fast Shipments

**Equal to \$50 Aerial Systems
All Directional TV AERIAL**

360° DIRECTRONIC SYSTEM

Exclusive Snyder Engineering and designs cut cost to

COMPLETE with three 3 1/2 ft. masts, 75 ft. 3 cond. cable, beam selector sw., guy rings and mtg. base. Electronically beams complete 360° rotation to give clear pic on all channels. You choose direction with directronic selector sw. mounted on or near TV set. Complete double stacked array with 18 bi-tensil double alloy aluminum elements. AX-595 same as TX-599 less masts, guy ring & mtg. base . . . \$16.95

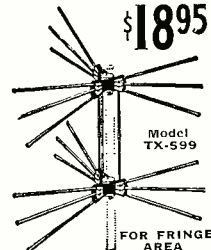

Model TX-599


FOR FRINGE AREA

AX-548 4 BAY SUPER DIRECTRONIC
Complete with 48 elements, 6 pos. beam selector sw., 130' tubular tri-x cable, universal U clamps. \$44.95
For ultra fringe

**Cover All VHF Channels with 2 Arrays
SNYDER BROAD BAND YAGIS**

- Higher Gain Than Conventional Yagis
- For Fringe and Ultra Fringe


High signal level for sharp, bright pictures. H-tensil 3% aluminum elements: 7 on low band; 9 on high band. Complete with universal U clamps. Easy to assemble. Space-saver design.

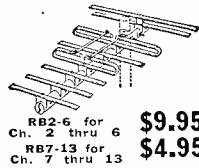

RB2-6 for Ch. 2 thru 6 \$9.95
RB7-13 for Ch. 7 thru 13 \$4.95

**Amazing New Broadband Hi-Gain
UHF YAGIS**

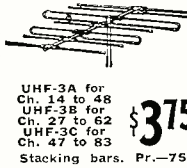Get clearest, brightest picture in fringe and ultra fringe with new Snyder Broadband UHF Yagis. Completely pre-assembled. 8 aluminum elements; 2 reflectors, 2 dipoles; 4 directors. Sturdy aluminum cross-arm. Universal "U" clamp. Three models cover all UHF channels. Designed for stacking in fringe areas.



UHF-3A for Ch. 14 to 48 \$375
UHF-3B for Ch. 27 to 52
UHF-3C for Ch. 47 to 83
Stacking bars. Pr.—75c

RESISTOR & CONDENSER BARGAINS
100 ASS'T RESISTORS. 1/2-1.2 W. \$1.95
50 ASS'T MICA COND. 5mmf to .001 mf 1.95

FREE! Write for new value-packed "FYI" bulletin #110. Write for our big audio guide, "Hi-fidelity Magic."

WHOLESALE RADIO PARTS CO., Inc.
311 W. BALTIMORE ST., BALTIMORE 1, MD.

**BLONDER-TONGUE All Channel
MASTER ANTENNA SYSTEMS**

Antennifiers & TV Distribution Amplifiers
HA-3 POWERFUL HOME BOOSTER

Fully automatic, broadband. 3 stage push-pull cascade circuit. Boosts signal greater than 16 db. No knobs, no tuning, no switching. Plug set into booster & booster in wall outlet. Turns on and off with set. \$23.70
Matches 300 ohm line. 105-120 V. AC.
CA-1-M COMMERCIAL TV ANTENSIFIER. Fully automatic. All channel amplifier. 30 times gain. \$46.50
DA2-1M DISTRIBUTION AMPLIFIER. 2 TV set outlets for multiple distribution systems. Full isolation. \$23.70
DAB-1-M DISTRIBUTION AMPLIFIER. 8 TV set outlets for multiple distribution system. \$52.50
MA-4-1 MIXER AMPLIFIER. Mixes and feeds signals of up to five ants. to 1 recvr. or distribution system. (Loss channel strip) \$31.50
CS-1 CHANNEL STRIP. \$11.70
UC-1 CONVERTER STRIP. Specify channel. \$25.88

**SUTCO UHF CONVERTER &
VHF BOOSTER IN 1 UNIT**

Enables any TV now being made to receive UHF and also boost VHF in fringe area. Has own power supply, a crystal mixer, a 6AF6 and a 6J6. Booster has 75-300 ohm input and output. Operates on 110-125 V AC. Terminals for UHF & VHF antennas. \$35.70
Model 21A.



CLOSEOUT! Price Slashed!
Reg. \$17.57 NATIONAL VHF BOOSTER

The famous National TVB-2B at this unheard of low price. Channels 2 to 13. Order now while stocks last. \$11.95

**SPECIAL
NEW "UTAH"
AUTO SPEAKERS**
Dynamic 4 ohm field. 5" model SE-5YG; mtr. hole ctr. 3 5/16 x 3 5/16". 5 1/2" model SE-5SG; mtr. hole ctr. 4 x 4". 95c ea.

**REAR DECK
AUTO SPEAKER
KIT WITH
SPEAKER**
Easy to install. You get Clifton 5" x 5" PM speaker, wire harness, grille, 3 pos. sw. for use of front, back, or both speakers. Instructions. Model 10 \$5.37

**SANGAMO MOLDED PLASTIC
600V. TUBULAR CONDENSERS**

.0005-10	.004-10	.025-12	.06-18
.001-10	.0047-10	.03-15	.068-18
.002-10	.005-10	.035-15	1-18
.0022-10	.006-10	.04-15	.25-25
.003-10	.01-12	.047-15	.5-32
.0033-10	.02-12	.05-15	

USED RECORDING TAPE (PLASTIC BASE)

\$1.99 for 7"—1200 foot
1.09 for 5"—600 foot
.59 for 4"—300 foot
.29 for 3"—150 foot
Plastic reels included with all above sizes.

Money cheerfully refunded if you do not find this tape cleanly erased and as good as new. (If you are skeptical and from Missouri send us 12c in stamps and we'll roll you a sample.)

New empty plastic reels in boxes for easy labeling, 3"—10c; 4"—22c; 5"—24c; 7"—30c ea. EMPTY BOXES: 3"—3c; 4"—5c; 5"—5c; 7"—10c ea.

We carry new recorders, recording blanks, tape recorders, etc. at large savings. PLEASE INCLUDE SUFFICIENT POSTAGE.

COMMISSIONED ELECTRONICS CO.
2503 Champlain St. N. W., Washington 9, D. C.

EASY TO LEARN CODE

It is easy to learn or increase speed with an Instructograph Code Teacher. Affords the quickest and most practical method yet developed. For beginners or advanced students. Available tapes from beginner's alphabet to typical messages on all subjects. Speed range 5 to 40 WPM. Always ready—no QRM.

ENDORSED BY THOUSANDS!

The Instructograph Code Teacher literally takes the place of an operator-instructor and enables anyone to learn and master code without further assistance. Thousands of successful operators have "acquired the code" with the Instructograph System. Write today for convenient rental and purchase plans.

INSTRUCTOGRAPH COMPANY
4711 SHERIDAN ROAD, CHICAGO 40, ILLINOIS

MOTOROLA-DETROIT CO.

one of the country's largest distributors of television sets and appliances

SAYS




IS A PROFITABLE ITEM TO STOCK FOR 2 REASONS

1. TV SERVICEMEN BUY IT



"Our customers use Krylon and plenty of it," reports Motorola-Detroit parts manager, Paul Wallace. "The spray nozzle makes it easy to insulate the complete chassis in a matter of minutes." Because of its high dielectric strength, Krylon helps prevent corona.

2. WE USE IT OURSELVES

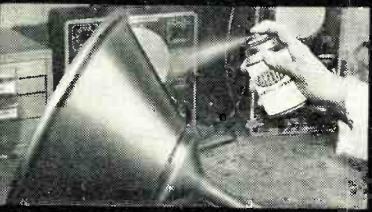

Indoor service chief, John Workman, reports, "We use Krylon clear plastic coating to spray the bell part of metal picture tubes. Krylon stops dust from adhering to the tube and prevents arcing. We find Krylon is a must in television service operations."

ALSO

"Our appliance division uses White Krylon to touch up any white goods that become chipped. We're sold on White Krylon for one big reason — it won't turn yellow."

Charles J. Weyoff
Service Manager
Motorola-Detroit Co.



In U.S.A. and CANADA
SEE YOUR JOBBER
Or Write For Information
Department 2708

KRYLON, Inc.

2038 Washington Ave., Philadelphia 46, Pa.

possibilities and educators should be given every chance to put up their own stations. He declared that while it would not be wise to have educational institutions take over TV, we would be . . . "passing up one of the great opportunities in the educational field, if we don't reserve channels for them."

When the reservation deadline passed, technically the Commission was in a position to change a channel from reserve for education to commercial, or even the reverse; change commercial to a reserved state. In addition, the government could add a new channel to any city, whether it presently has channels allocated to it or not, and could also remove a channel from any city and assign it to another. It also became possible to substitute or exchange channels among cities, whether they were on the very-high or ultra-high bands. A change in the minimum mileage separation required between a channel in one city and a co-channel or adjacent channel in another city now also can be entertained.

In some quarters, educational interests have been very active. In New Jersey, for instance, a commission report to the governor proposed the erection of a six-station network and allotment of \$190,000 to continue research in programming, already under way at New Brunswick, and \$425,350 for construction of station and allied facilities.

Suggested was the building of a station with a studio on the campus of Rutgers University, using a 5-kilowatt transmitter and antenna at Washington Rock State Park, Watchung. Other stations, it was reported, would be built in the vicinity of Montclair, and another with a studio in the Camden area with the transmitter and antenna in the Mount Holly vicinity. Still others would be erected in the vicinities of Freehold, Hammononton, and Andover. Local boards of education would be responsible for

providing receiving facilities, the report continued.

Among those who served on the report commission were Drs. Elmer W. Engstrom of RCA and Allen B. DuMont. Engstrom served as chairman.

MICROWAVES, often described as the eventual home of many, many services, was recently the subject of one of the most searching analyses ever offered by a spokesman of the Commission; Edwin L. White, chief of the Safety and Special Radio Services Bureau.

Speaking before the Petroleum Industry Electrical Association in Houston, Texas, he said that the one outstanding characteristic of microwave systems is the ease with which the radiations of the transmitters and angle of acceptance of receivers can be restricted. In view of this feature, the same frequency can be and is being used in the same geographical area by two independent point-to-point systems, without noticeable interference, it was pointed out. If this engineering can be carried to the ultimate, White said it might well be that, as a matter of policy, the Commission could assign identical frequencies to a number of systems in the same area without harmful mutual interference resulting.

Exploring some of the benefits and some of the possible drawbacks of such a procedure, the Commission's expert said that if such a procedure is practicable, the number of potential channels in any one area could become so large that some of the means of frequency economy applied to individual systems might become unnecessary. For example, he pointed out, it may not make too great a difference if passive reflectors are used, and frequency requirements for any point-to-point system doubled thereby. The bandwidth required for multiplexing might not be of great importance, it was revealed. Under such an ideal

NEW TV STATIONS ON THE AIR

(As of July 25, 1953)

The following new stations brings the lists published in previous issues up to date.

STATE, CITY	STATION	CHANNEL	FREQUENCY RANGE (IN MC.)	VIDEO WAVELENGTH (IN FT.)	VIDEO POWER* (IN KW.)
Kansas Hutchinson	KTVH	12	204-210	4.79	115
Minnesota Rochester	KROC-TV	10	192-198	5.08	105
Missouri Kansas City	KCTY	25	536-542	1.83	93
Nebraska Lincoln	KFOR-TV	10	192-198	5.08	59
Ohio Akron	WAKR-TV	49	680-686	1.44	145
Ohio Ashtabula	WICA-TV	15	476-482	2.06	20
Texas San Angelo	KTXL-TV	8	180-186	5.43	11
Texas Texarkana	KCMC-TV	6	82-88	11.8	18.5
Wisconsin Madison	WMTV	33	584-590	1.68	16.5
Wisconsin Milwaukee	WCAN-TV	25	536-542	1.83	105

*From Station CP application.

The frequency of the video carrier = 1.25 + channel lower freq. limit.

Total number of television stations now on the air: 207 (49 of which are u.h.f.)

plan, the report added, the Commission could allow each system to be as the applicant might desire, both as to choice of equipment and as to ultimate capacity, and there would be no need to inquire into the plans of the applicants for future growth. Thus, the Commission might assign a channel of from 8 to 10-mc. width to each microwave system, leaving it to the licensee to make his choice of modulation system, and use as much of the channel as his needs dictate, provided, of course, that the techniques used did not result in occupancy of frequencies outside the channel or produce radiation outside of the geographic area provided for the system.

Unfortunately, White said, for some there were a few problems that could disturb the bright prospects. For the mobile and broadcast systems, the frequencies above 800 or 900 mc. are not too attractive. And, information also indicates that above approximately 8000 or 10,000 mc., atmospheric absorption is also serious. Because of these conditions, the report noted, it may well be that at some future time we may find that because of requirements for mobile uses we cannot afford to use the frequencies below 800 mc. for point-to-point communications. If this should happen, White declared, point-to-point systems designed to operate in the lower portion of the spectrum would be forced to vacate and move up to those frequencies suitable for point-to-point, but unsuitable for mobile work. Notwithstanding the interference situation above 10,000 mc., extremely high powers can be used to overcome this atmospheric problem, as radar operation has proved. Under these circumstances, the petroleum specialists were told, the fixed frequencies between 800 and 10,000 mc. might be reserved for intercity point-to-point systems and the fixed frequencies above 10,000 mc. could be reserved for intracity networks and to connect the suburban

terminals of intercity networks with central urban terminals.

Noting that the number of microwave systems is growing, White disclosed that there are approximately 60 fixed microwave communication systems which are over 50 miles in length, in addition to possibly 75 to 80 other systems which consist of one or two hops only.

FACED WITH mounting hearing problems, examiners have found it impossible to maintain the early post-freeze pace and grants have begun to trickle instead of pour as they did in the first few months.

As the table on page 16 reveals, the number of approvals for station construction has dropped substantially; over 50 per-cent in this instance as can be readily seen.

It is believed that this situation will be alleviated soon by Congress by means of an appropriation to permit the hiring of more examiner teams. It is expected that about \$300,000 will be appropriated for the cause, and at least seven more teams of examiners will be retained. Since one team can handle about 15 applications yearly, the present ten and additional seven would be able to process 255 applications a year. Senator Ed Johnson has been arguing for even more money so that more lawyers and assistants can be hired to expedite further the processing of applications. He warned his colleagues that actually Congress would be continuing the freeze if they did not approve funds for more examiner teams. He would like to see a total of 40 teams in action at the Commission's offices. Such a force, he felt, would enable more stations to begin telecasting and set in motion a chain reaction which very quickly would create billions of dollars in business. Everyone is grateful to the driving Senator for his earthy plea for these urgently needed dollars. It is to be hoped that Congress concurs...L.W.

STAN-BURN E-D-A-R-K-E

CATHODE RAY TUBE SPECIALS			
One Year Guarantee			
G. E.		STAN-BURN	
5TP4\$44.95	10BP4A\$11.00
7JP417.10	12LP4A14.20
10BP4A19.25	14CP417.00
10FP4A24.00	15DP419.50
12KP4A27.10	16AP421.60
12LP4A21.70	16FP419.60
12UP4B28.25	16GP421.60
14CP424.50	16HP4A22.60
16AP4A30.95	16DP/HP419.60
16DP4A28.20	16DP/HP4A20.60
16GP431.25	16KP418.50
16KP4/16RP428.20	16LP420.60
17BP4A23.90	16LP4A21.60
17CP423.90	17BP418.50
19AP4A39.45	17CP421.60
20CP424.75	19AP423.90
20LP437.50	19AP4A25.90
21EP4A37.35	20CP429.50
24AP4A78.50	21EP432.50

ANTENNAE SPECIALS			
RED DOUBLE "V" Antenna1-5	6 or more\$1.98
10 ELEMENT CONICAL DOWELED INSERTS2.98	2.79
Folded Hi Straight Low Quick Rig 1/2" elements4.25	3.25
WINDOW CONICAL MASTS		3.75
5 FOOT SWEDGED79	69
10 FOOT PLAIN1.29	1.29
NEPCO MASTS1.69	1.49
42 Mil. TV WIRE\$ 9.95	50 Ft.\$ 9.95
55 Mil. 300 OHM11.95	50 Ft.11.95
72 OHM COAXIAL35.00	50 Ft.35.00
12" Heavy Slug SpeakerSpecial	\$3.98
CHASSIS 630 REGAL with Cascode Tuner\$149.50		
OPEN FACE CABINET42.00		
WIRE RECORDERS IN STOCK			
PENTRON - Model ST3C - 2-speed Tape RecorderWrite for Price		
RADIO CRAFTSMAN			
Model C400 - Hi-Fi AmplifierNet	42.90	
Model C10 - AM-FM TunerNet	131.50	
Model C500 - Williamson AmplifierNet	99.50	
We also carry MASCQ-BOGEN-PILOT, etc., Amplifiers, Pre-Amps, FM Tuners and WEBSTER Tape Recorders.			
6x9 PM Speaker\$ 3.98	630 Vert. output potted1.29
7" PM Speaker3.98	630 Vert. Blocking89
77J1 G.E. Flyback1.98	OSC. XForm1.95
70" Yoke1.98	Cascode Tuners17.95
630 Vert. output Upright1.98	Standard Tuners21.25
		Dumont14.95

AUTHORIZED DISTRIBUTORS for General Electric, Kenrad, Tung-Sol, National Union, De Wald, Regal, Automatic and General Motors.

Automatic Custom-Built Radios for Plymouth, Ford, Chevrolet and many others, always in stock.

We carry a Complete Line of HI-FIDELITY and sound equipment. Send us your requests.

We also carry a complete line of popular makes of Radio Tubes at 50/10 discount. Also many other special purpose and transmitting tubes, and all electronic parts and equipment at lowest prices. Send us a list of your requirements for prompt quotations.

Terms: 20% with order. Balance C.O.D. All prices F.O.B. NEW YORK Warehouse. Minimum order \$5.00. Write for our latest price list and Hi-Fi catalog to Dept. RN-8.


STAN-BURN RADIO and ELECTRONICS CO.
(C.B.S. THEATRE BLDG.)
1697 BROADWAY • NEW YORK 19, N.Y.

Regency

UHF

the quarter million dollar convert


CONVERTED
MODEL RC-60

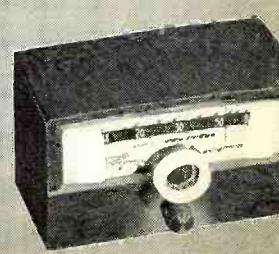


\$49.95 list

the New McIntosh

30 WATT AMPLIFIER

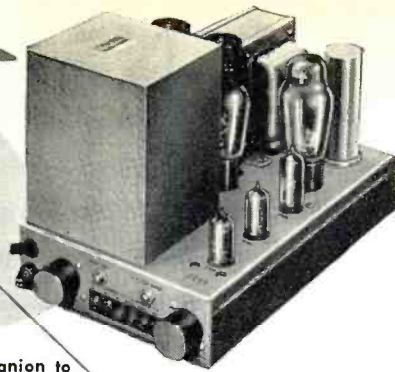

Companion to
the McIntosh 50

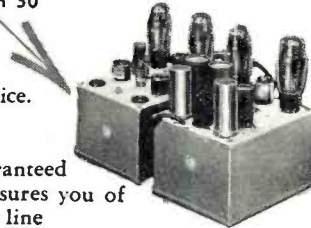

For you who expect the finest. Designed to satisfy a demand for professional performance in home sound systems at reasonable price. The new McIntosh 30 watt amplifier features the same patented output transformer circuit used in its widely acclaimed companion, the 50 watt model. Guaranteed less than 0.5% harmonic distortion at full 30 watts assures you of complete listening pleasure. Any tuner or zero VU line will drive to full output. Hear it perform at your high fidelity dealer's showroom soon!

Write today for LOST INSTRUMENTS a free 32 page booklet explaining the fundamentals of high fidelity sound enjoyment.



McIntosh

LABORATORY, INC.

322 WATER ST., BINGHAMTON, N. Y. • PHONE 3-3566
EXPORT DIVISION: 25 WARREN ST., NEW YORK 7, N. Y.

1953 Emerson TV Sets (Continued from page 55)


of horizontal and vertical sync. This was remedied by attenuating the signal, or by simply removing the first r.f. amplifier, usually a 6J6 or a 6CB6 tube. On the other hand, when a set was installed in a fringe or weak-signal area, the contrast, or signal strength, could be improved by shorting out the a.g.c. line completely, permitting the receiver to run "wide open," always in the maximum gain condition.

Upon close examination, it will be noticed that the "trick" of obtaining good reception in all signal areas depends upon the amount of amplification the receiver obtains from the r.f. amplifier. In strong-signal areas the r.f. amplifier is not really necessary and, if its amplification were eliminated, there would be enough signal leaking through the tube and wiring capacities to give a very satisfactory picture. This can be done by increasing the bias on the control grid to the point where the tube amplifies very slightly, if at all; likewise, in the weak areas, the tube will have maximum gain if the a.g.c. is shorted out.

Another important consideration is the signal-to-noise ratio of the receiver. This, too, is determined by the r.f. amplifier since, in weak-signal areas, the r.f. amplifier must amplify the signal above the noise level of the receiver in order to have a snow-free picture. To accomplish all this, the r.f. amplifier must have an a.g.c. curve like that shown in Fig. 5C. The a.g.c. for the i.f. stages must also vary with the signal strength, but not as severely as the r.f. a.g.c.

All this is accomplished by utilizing a two-part a.g.c. system. The negative

Fig. 5. (A) Simple a.g.c. circuit with its operating curve. (B) Voltage doubler type a.g.c. and curve. (C) Curve showing ideal a.g.c. for r.f. and i.f. stages.

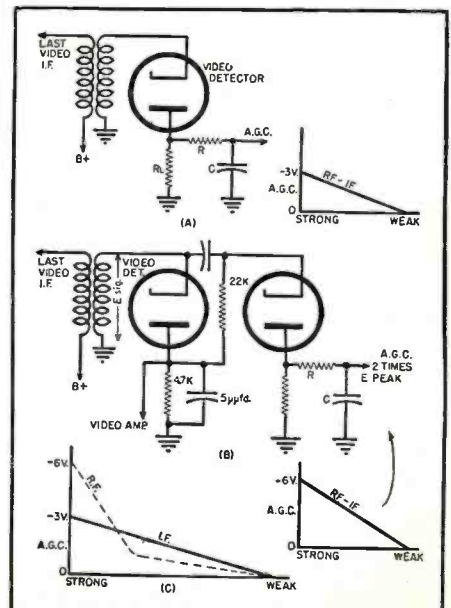

V. E. C. TUBES AT WHOLESALE

MINIMUM ORDER \$10.00 OR 25 TUBES

BRAND NEW • BOXED • BRANDED • 100% GUARANTEED •

1A7GT ... \$.55	6BE6 ... \$.48	12AT6 ... \$.39
183GT64	6BG6G ... 1.20	12AT773
1H5GT53	6BH653	12AU645
1L453	6BJ653	12AU760
1L653	6BK780	12AV635
1N5GT53	6BL7GT80	12AV775
1R553	6BQ6GT85	12AX763
1S545	6BQ787	12BA648
1T453	6BZ789	12BA755
1U453	6C443	12BE648
1U545	6CB653	12BH767
1X267	6CD6G ... 1.65	12SA7GT47
3Q5GT55	6F6GT42	12SK7GT47
3Q5GT63	6J663	12SL7GT63
3S450	6K6GT40	12SM7GT58
3V450	6L680	12SQ7GT40
5U4G45	6S443	198GGG ... 1.50
5Y334	6S8GT67	19T873
5Z344	6SA7GT47	25BQ6GT84
6AB445	6SD7GT73	25L6GT43
6AC554	6SK7GT47	25WAGT45
6AJ598	6SL7GT62	25Z6GT38
6AK598	6S7GT62	35B550
6AL545	6SQ7GT40	35C550
6AQ550	6T873	35L6GT43
6AT639	6U878	35W435
6AV645	6V6GT50	35Z5GT35
6B639	6WAGT45	50B550
6BA658	6W6GT55	50C550
6BA760	6X439	50L6GT52
6BC550	6X5GT39	117L7GT ... 1.06
6BD5GT60	12AL545	117Z335

UNBEATABLE TUBE KIT VALUES

KIT	KIT CONTAINS	LIST PRICE	NET PRICE
1	3Q4, 1T4, 1R5, 1S5	8.00	
2	3S4, 1T4, 1S5, 1R5	7.80	
3	1U4, 3S4, 1S5, 1R5	7.80	1.85
4	3V4, 1R5, 1S5, 1T4	7.80	
5	117Z3, 1U5, 3V4, 1R5, 1T4	9.75	
6	12AT6, 12BA6, 12BE6, 35W4, 50C5	8.70	
7	12SA7, 12SK7, 12SQ7, 35Z5, 50L6	8.40	2.10

SAVE C.O.D. FEES. All orders accompanied by full remittance will be shipped POST PAID anywhere within continental U.S.A.

PRICES are guaranteed to remain as advertised until SEPT. 1 or until stock is exhausted.

25% DEPOSIT on all C.O.D. orders. NO OPEN ACCOUNTS.

VIDEO ELECTRIC CO.
P. O. BOX 911 NEWARK, N. J.

POLYSTYRENE

ROD — 12" or 48" lengths.

Dia.	12"	48"	Dia.	12"	48"
1/8"	\$.03	\$.12	3/4"	\$.80	\$ 3.20
3/16"	.06	.24	1"	1.55	6.20
1/4"	.10	.40	1-1/8"	2.00	8.00
5/16"	.16	.64	1-1/4"	2.30	9.20
3/8"	.21	.84	1-3/8"	3.00	12.00
7/16"	.30	1.20	1-1/2"	3.30	13.20
1/2"	.40	1.60	1-3/4"	4.50	18.00
5/8"	.57	2.28	2"	5.90	23.60

SHEET — masking paper both sides.

Thickness	Size	Price
1/16"	12" x 12"	\$ 2.50
3/32"	12" x 12"	2.75
1/8"	12" x 12"	3.00
3/16"	12" x 12"	3.75
1/4"	12" x 12"	4.60
1/16"	12" x 24"	4.90
3/32"	12" x 24"	5.25
1/8"	12" x 24"	5.90
3/16"	12" x 24"	7.25
1/4"	12" x 24"	8.25
1/16"	20" x 20"	7.75
1/16"	24" x 24"	9.50
3/32"	24" x 24"	10.25
1/8"	24" x 24"	11.75
3/16"	24" x 24"	14.00
1/4"	24" x 24"	16.00
5/16"	20" x 20"	14.50
3/8"	20" x 20"	16.00
3/8"	24" x 24"	23.75
1/2"	20" x 20"	21.50
1/2"	24" x 24"	31.88
5/8"	20" x 20"	34.50
3/4"	20" x 20"	41.00
1"	20" x 20"	55.50

TUBING — 12" or 48" lengths.

O.D.	I.D.	12" lgth.	48" lgth.
1/4"	1/8"	\$.07	\$.28
5/16"	3/16"	.10	.40
3/8"	1/4"	.13	.52
1/2"	3/8"	.18	.72
5/8"	1/2"	.23	.92
3/4"	5/8"	.29	1.16
1"	7/8"	.38	1.52
1-1/2"	1-1/4"	1.13	4.52
2"	1-3/4"	1.50	6.00

All prices F.O.B. our warehouse New York

LEEDS RADIO CO.

75 Vesey St. Dept. A New York City 7

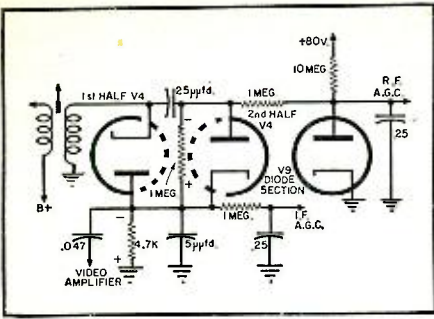


Fig. 6. Simplified schematic diagram of delay type a.g.c. circuit used by Emerson.

d.c. voltage developed across the video detector load resistor serves as the a.g.c. source for the i.f. stages only. (See Fig. 6.) Since in the strong signal areas the r.f. amplifier must effectively be cut off, or close to it, the higher a.g.c. potential is developed by the modified voltage-doubling action of the second-section diode of V_1 . This peak d.c. voltage will then add to the average voltage across the 4.7K resistor, giving the total voltage for the r.f. a.g.c., reducing the r.f. gain in the high-signal area. For weak signals, the action of the modified voltage doubler is reduced by applying a positive voltage through the 10-megohm resistor from a positive 80-volt source, reducing the r.f. a.g.c. to some value close to zero. If the diode section of V_1 were removed from the circuit while receiving a weak signal, the r.f. a.g.c. line would go positive. The a.g.c. clamper diode prevents this from occurring by conducting whenever there is a tendency for a positive voltage to exist on the r.f. a.g.c. line. Actually, this a.g.c. line will never become positive, due to the contact potentials of the diodes, and will always be approximately -0.5 volt with no signal received.

A low value of negative voltage will be present on the r.f. a.g.c. line until the signal is strong enough to develop a large enough bias in the a.g.c. diode circuit to overcome the positive delay voltage from the 80-volt source. From that point on, the a.g.c. voltage will rise very rapidly as the signal increases, crossing over the i.f. a.g.c. bias point (see Fig. 5C) and, for very strong signals, cutting off the r.f. amplifier.

The vertical oscillator frequency is controlled directly by the vertical sync pulse after it is integrated by an improved integrator network. This improved integrator is made up of two sections of a low-pass network, R_{34} , R_{35} , R_{36} , C_{71} , and C_{72} , rather than the customary three sections. Also, the input impedance is lower which makes its operation more successful, since any noise or horizontal pulses that may induce currents into the vertical circuit will develop a negligible voltage across the low resistance of the integrator. Another important factor is that, with the two-section integrator, the time constant is shorter, therefore permitting the vertical sync pulse to discharge fully after the ver-

SPECIAL BUYS!



Radars Indicator unit for conversion to test scope or for use as a modulation monitor. Complete with tubes. But, less 58P1.
New **\$9.95**



BC-454, used, exc. condition..... \$11.95
BC-455, exc. condition..... 9.95
BC-459, used, exc. cond..... 14.95
BC-459, used, as is; Less Tubes..... 7.95

SCR-625—Mine Detector—New..... \$59.50
BC-357—Exc. L/T..... 5.95
BC-709—Inter. Amo. New..... 3.95

	EXC. USED	AS IS	NEW
	(with tubes)		
BC-456, Modulator.....	\$2.95	\$4.95	\$7.95
BC-457, Transmitter.....	4.95		
BC-458, Transmitter.....	4.95		
BC-455 Receiver, 6 to 9 mc (as is, less tubes and crystals) only.....	4.95 each		

Control boxes, racks, receivers to move in stock—write.

WHILE THEY LAST!

350 ft. of 50 ohm coaxial cable..... \$ 9.95
Attenuator—one cavity type..... 7.95
TS13 Hand Sets, excellent condition..... 5.95
TS Type, exc., less cord..... 2.95
EES Portable Telephone exc. cond..... ea. 18.95
2 for..... 35.00

CRYSTALS

Low Freq.—FT 241 A for SSB, lattice filler, 1/2" spc.	374	386	396	409	420
	375	387	397	411	422
	377	388	398	412	423
	379	390	401	413	424
	381	391	402	414	425
	382	392	404	415	426
	383	393	405	416	427
	384	394	407	418	431
	385	395	408	419	433

54th harm channels listed by fund. Fractions omitted.
435 491 504
436 492 506
481 493 507
483 494 508
484 495 509
485 496 511
487 497 514
488 498 515
490 503 516

304TL }
58P1 }
SCP1 } **\$5.95 ea. TUBES**

100 assorted for \$3.00
954, 955, CK1095, 1625, 1626, 1613,
1615, 32, 33, 34, 9002, 9004, 9006,
627G, 1N5CT, 6J5G.

MONTHLY SPECIAL! Brand New

R-1 ARR-1—220 mc converter with minor alterations becomes a high gain converter with two stages of R. F. amplification—(see "Radio & TV News," Jan. 1949)..... \$4.95
TS-1—Test Set for above..... 4.95

DYNAMOTORS: The best dynamotor for conversion to 6v. Multiple windings! After conversion you get choice of 190 or 350 v, at 50 MA or 250 v, at 100 MA. Complete dope sheet furnished.
BRAND NEW (See "CQ" Aug. issue)..... **\$4.65**

AR2 Receiver—234 to 258 mc, less tubes..... \$10.95

MISCELLANEOUS EQUIPMENT

FL-8 used, exc..... \$1.19 | BC-347 each..... used 95c
BC-906 each..... 9.95

RT7 APN-1 TRANSCEIVER UNIT—Used as an altimeter, it may be converted for signaling control circuits, etc. Complete with 14 tubes and dynamotor they are in good used condition at the amazing low price of..... **\$29.95**
Used, less tubes, as is..... 4.95

BROADCAST BAND & AERO Ideal for Use in Boats, etc.

MN-26-C Remote Controlled Navigational Direction finder and communications receiver. Manual DF in any one of three freq. bands, 150 to 1500 KC, 24 V. Self contained dynamotor supply. Complete installation including receiver, control box, loop, azimuth control. Left-Right Indicator, plugs, loop transmission line and flex. shafts.
BRAND NEW..... \$89.50
LIKE NEW..... 69.50
MN-26-Y 150 to 325 KC, 325 to 695 KC, 3.4 to 7 megacycles, comp. installation..... 69.50
Receiver alone..... 35.95
MN-26-C alone, like new..... 39.50
MN-26-C or MN-26-Y as is less tubes..... 13.95
With tubes, Used good..... 24.95
MN-20-E Loop, Brand New..... 6.95
MN-52 Crank drive, New..... 2.50

MIKES and HEADSETS: HS-33 Low Impedance Headset..... exc. \$2.95 new \$5.95
HS-23 Headset..... used 2.95 new 4.95
CO-307 Ext. cord for HS-23-33..... like new .79
Throat Mike-7-20..... new .98
Lip Mike—Navy Type..... new .98
CW-49505 High Impedance headset complete with headband..... used..... 98c
HB-7 Headband..... used..... \$1.29
HS-18 Headset..... used 1.29 new \$1.98
HS-38..... exc. 1.95 new 2.29
HS-30, miniature headset..... used 1.49 new 2.49
Shipments F.O.B. warehouse. 20% Deposit on orders. Retail sales tax to remittance.

WANTED! All TS, APR, APS, ARC, ARN, ART, SCR, R8) and BC equipment..... write today!
Quote lowest prices in your first letter

RT 34 APS 12 Transceiver used as a full warning radar on 415 MC, containing a 30MC IF Strip and various other parts, these units have been stripped of RF sections and all tubes, but are an excellent buy if only for parts and IF Strip..... used \$ 4.95
BC-624 receiver (SCR 522), less tubes, 100-136MC..... used \$14.95

TRANSCEIVER—140-144 mc, 2 meter, used, excellent condition, less dynamotor, less tubes, only \$17.95

WOBLATOR

BUILD TV-FM-AM SWEEP GENERATOR
You can build "Versatile Sweep Frequency Generator" with APN-1 magnetic units..... \$ 6.95
BC-1206 Beacon Receiver..... 200-400KC..... 9.95
MN-26LB Receiver exc..... 59.50
RCA Sound Powered Phones..... brand new, 12.95 two for 24.95
TS-184/AP Test Set..... 69.50
APR-2 Radar Search Receiver, 85-1000MC..... 195.00
APR-4 Radar Search Receiver, 38-4000MC..... 399.00
TS100 Oscilloscope..... 113.00
19A-SCR52 Test Unit..... 295.00
MG-153 Inverter..... Used 69.50
I-229-Signal Generator..... Used, exc. 125.00
R-11B-APRS..... Like new 350.00
AN/APTS Transmitter..... Like new 189.50
SURPRISE PACKAGE, 15 lbs. of assorted good radio parts..... **\$1.95**
A real value at.....

SELSYN TRANSMITTER: Autosyn Transmitter Assembly for matching to I-82 Indicator. Used, excellent condition.
ONLY \$7.95, Complete with Indicator..... \$14.95
RL-42 Reversible Motor with antenna reel and clutch, used..... \$ 2.95
BC-432 RADIO COMPASS RECEIVER, 200 to 1700 KC, used, excellent condition, with tubes..... 39.95
as is, less tubes..... 24.95
used, as is, less tubes and cover, exc. for parts..... 8.95
Minimum order \$5.00. Illinois residents, add regular prices subject to change without notice.

R W ELECTRONICS Dept. N, 1712-14 S. Michigan Ave., Chicago 16, Ill.
PHONE: HARRISON 7-9374

MORE CASH

Att.: Schools, Labs, Hams!

Cash in on your surplus Radio Parts & Equipment! We pay more—or trade for something you really need. TV Sets, Mobile Equipment. Available for Trade. Write Now!

HARJO SALES CO.
4109 Burbank Blvd.
Burbank, Calif. Cable HARJO

ON THE BATTERY RECORDER

WALKIE-RECORDALL 8 lb. miniature BATTERY RECORDER-PLAYBACK
Continuous, permanent, accurate, indexed recording at only 5c per hr. Instantaneous permanent. Picks up sound up to 60 ft. Records conferences, lectures, dictation, 2-way phone & sales talks; while walking, riding or flying. Records in closed briefcase with "hidden mike"! Write for detailed literature.

MILES REPRODUCER CO., INC.
812 BROADWAY Dept. RN-8, NEW YORK 3, N. Y.

RADIO ENGINEERING 27 MONTHS DEGREE IN 27 MONTHS

Radio engineering is a big field. There's room for you in it—if you're good. Get first-class training at Indiana Tech. Intensive, specialized course, including strong basis in mathematics and electrical engineering, advanced radio theory and design, television, electronics, Modern Laboratories. Low rate. Also B.S. DEGREE IN 27 MONTHS in Aeronautical, Chemical, Civil, Electrical and Mechanical Engineering. G.I. Government approval. Enter September, December, March, June. You can earn part of your expenses right here in Fort Wayne while you are studying.

INDIANA TECHNICAL COLLEGE


983 E. Washington Blvd., Fort Wayne 2, Indiana
Please send me free information on B.S. Engineering Degree in 27 months as checked.

Radio-Television Aeronautical
 Civil Mechanical Electrical

Name.....
Address.....

NEW

POWER BOOSTER

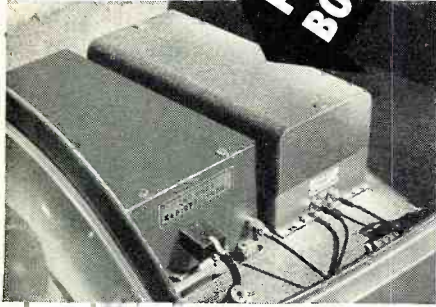


NEW POWER BOOSTER Boosts Power instantly!

Stronger signals and greater transmission range even in hilly country are now possible through use of the new Kaar Power Booster, which increases by six times the power output of any 8 to 10 watt mobile transmitter, without adding to standby battery needs—a recent, outstanding engineering achievement of the Kaar research laboratories.

**DEPENDABLE
MOBILE
COMMUNICATION**

RADIOPAK

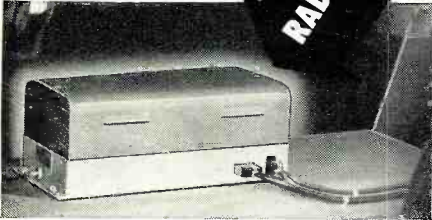

Rugged construction... simplicity of design... lowest possible battery drain... exceptional voice quality—these are the features that make the Radiopak the most dependable single unit mobile radiotelephone available today. Furnished for both the 25 to 50 mc band and the 152 to 174 mc band, the Radiopak is ideally suited for use in police cars, taxis, fire department vehicles, trucks, and three-wheeled motorcycles.

DEALERS!

Kaar is the only major radiotelephone manufacturer selling through authorized dealers. Write for complete information.

● WRITE FOR SUMMARY CATALOG ON ALL KAAR MOBILE EQUIPMENT

KAAR
ENGINEERING CORP.
MIDDLEFIELD ROAD • PALO ALTO, CALIF.

tical pulses are removed, within the time interval of the equalizing pulses. This arrangement permits improved interlace, allowing the receiver to have its maximum resolution and resulting in better picture quality.

The horizontal sync circuit uses the latest type of horizontal phase-detector circuit as an automatic frequency control. As seen from the schematic diagram in Fig. 4, the horizontal multivibrator (V_{13}) frequency is not controlled by pulses, as is the vertical circuit; instead, a d.c. control voltage is applied to its grid from the output of the phase detector. This voltage is negative or positive, depending upon the relation of the multivibrator frequency to the horizontal sync pulse. Increasing the horizontal frequency, or to be more correct, its phase, is accomplished by making the grid of the first half of V_{13} more negative, decreasing its gain, but resulting in an increase in horizontal phase. To decrease the horizontal phase, a positive voltage is applied to the grid.

Noise Inverter Circuit

To improve the noise immunity of the circuits, early receivers used a noise clipper diode. The noise was clipped by the diode action down to the level of the sync peaks, at best, if the circuit was adjusted properly. The remaining noise pulse below the sync level, however, could still cause unstable sync. Also, under continuously heavy noise bursts, the noise clipper tended to build up a bias across it equal to the noise peaks and, therefore, was not effective for the elimination of such noise.


The Emerson noise inverter circuit, Fig. 7, not only prevents the noise

from exceeding the sync peaks, but also reverses the polarity of the noise pulses into the negative region, where they have absolutely no detrimental effects on the sync circuits. It should be noted that the noise inverter circuit will function on noise in the sync circuit only, and not in the video circuit. Noise appearing at the output of the video detector will appear on the picture tube.

The normal path of the sync pulses, with the noise inverter inoperative, would be from the video detector through the sync amplifier, through an RC noise-immunity circuit to the sync separator and, finally, to the horizontal or vertical sync circuits. In operation, one-third of the output voltage of the sync amplifier is taken off from the junction of resistors R_{53} and R_{54} , and is applied to the grid of the noise inverter. The variable resistance, R_{90} , which is part of a voltage divider in the cathode of the noise inverter, is adjusted so that the bias of the tube is just at cut-off when no signal is received. The total bias on the grid of the noise inverter must always be equal to the cut-off bias of the tube, plus the peak voltage of the sync pulses. The latter varies from scene to scene, and is coupled to the noise inverter grid. A varying bias voltage that will follow the sync amplitude variations is developed on the grid, due to the action of the sync clamper in the following manner.

Pulse voltages, which are a function of the horizontal frequency, are obtained from the horizontal output transformer and are applied to the grid of the sync clamper at the same instant that a horizontal sync pulse is applied to the plate of the clamper.

Fig. 7. Noise inverter circuit showing the waveforms at essential points.

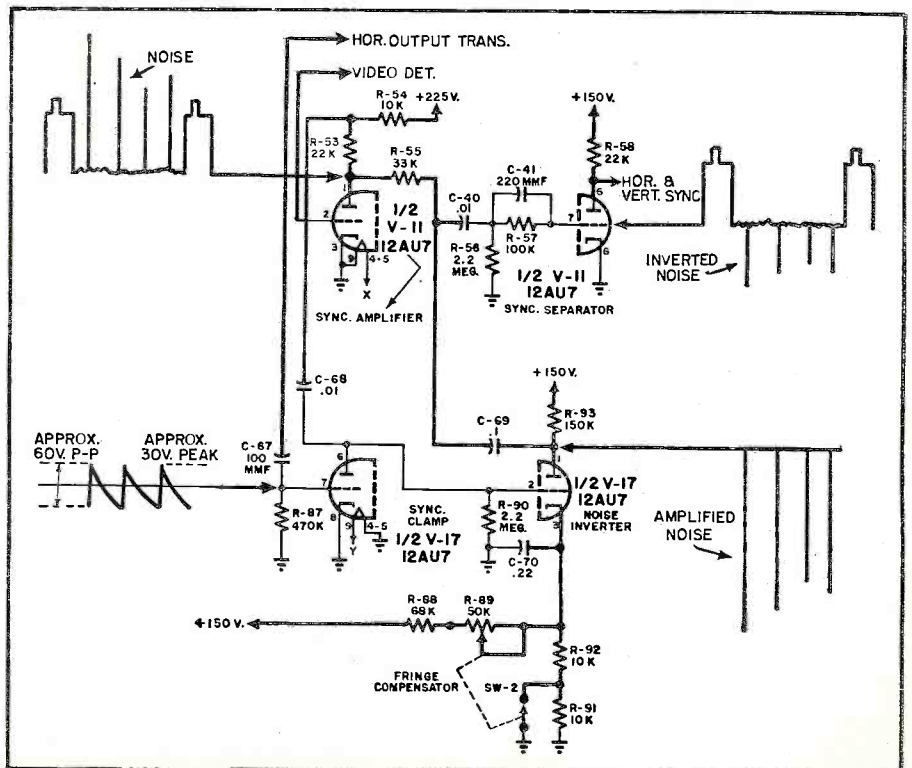


A grid-leak bias will develop on the sync clamper from the grid pulses which will keep it cut off between horizontal pulses. When the clamper tube does conduct, it charges C_{ss} up to the peak voltage of the sync pulses applied, and its discharge through R_{90} develops a bias voltage equal to the peak of the sync pulse. Adding the voltage developed across R_{90} , and the voltage in the cathode circuit of the noise inverter, results in the total bias on the tube, maintaining it at the proper cut-off potential.

When the clamper does not conduct, it appears as a high impedance permitting the noise pulses to overcome the bias on the noise inverter, driving it into conduction. These noise pulses are amplified and appear across the 33,000-ohm resistor, R_{55} , with an opposite polarity and greater amplitude than the same noise coming from the plate of the sync amplifier. The latter noise pulse is therefore cancelled completely, and appears as a negative-going noise pulse having no harmful effects anywhere in the sync.

Although the setting of R_{55} is not too critical, care must be taken so as not to develop excessive or insufficient bias. With excessive bias, not all of the noise will cause the tube to conduct and this will result in inadequate cancellation. With insufficient bias, there is the possibility that the sync pulse will be cancelled, adding to sync instability. This variable resistor is called the "fringe compensator control," and its adjustment is simple since it is rotated until noise does not cause any sync instability of the picture on the screen. If the fringe compensator operation is not desired, the control is rotated fully counterclockwise until SW_2 is opened, removing the short across R_{55} . The increased voltage drop across the additional 10,000-ohm resistor biases the tube well beyond cut-off.

Alignment Data

To aid the service technician in aligning the horizontal oscillator, leads from the multivibrator phase coil (L_{11}), and from the grid of the horizontal oscillator are brought up to a dummy lug on the top rear of the chassis. Since the multivibrator control grid must be at zero voltage for operation at 15,750 cycles, the lug connected to the grid is simply shorted by a jumper to the chassis of the receiver. Another jumper is used to short out the other two closely-wired lugs from the phase coil to each other. Now all controlling elements of the oscillator are removed, leaving the normal RC time constant. The horizontal hold control, R_{13} , located on the front of the chassis behind the hinged Emerson name plate, is adjusted so that it is in the center of its mechanical range. With the set tuned to a signal, the horizontal balance control, R_{11} , located on the rear of the chassis, is adjusted so that the picture does not tear. Next, the jumper shorting the lugs connected to the phase coil is



Same Day Service!

TOP TUBE BUYS

70% to 90% off list!

All Tubes Individually Boxed! Check this list for Fully One-Year Guaranteed Tubes

Another RAD-TEL Extra!

200 ASSORTED RESISTORS \$ 39

Carbon, Wire Wound, Carbon Film, Standard RMA Color Code or Value Printed. Uninsulated Type. 1/2 Watt, 1 Watt, 2 Watt and Some 10 Watt. Very Few Duplications or Odd Values!

Type	Price	Type	Price	Type	Price
1A5GT	.46	6B46	.46	12A7	.38
1A6G	.30	6B6	.39	12BA7	.60
1A7GT	.47	6B7	.59	12BD6	.45
1A85	.30	6B8	.39	12BE6	.39
1B3	.65	6B96GT	.59	12BF6	.39
1B5	.30	6B07	.95	12BH7	.63
1B7GT	.30	6B27	.95	12C8	.34
1C5GT	.43	6C4	.37	12C8	.34
1E7	.29	6C5GT	.39	12F5GT	.34
1C4GT	.24	6C6	.58	12G5GT	.42
1G5	.30	6C8	.24	12J7GT	.34
1H4G	.30	6C86	.44	12K7GT	.34
1H5GT	.24	6D6	1.11	12L7GT	.70
1H5	.24	6D6	.45	12SA7GT	.44
1J6	.24	6E5	.48	12SF5	.50
1LA	.46	6F5GT	.37	12SL7GT	.52
1L5	.24	6H7	.37	12S7	.44
1N5	.46	6F8G	.24	12SK7GT	.48
1P5	.57	6G8G	.52	12SL7GT	.47
1Q5	.53	6H5GT	.37	12N7GT	.52
1R5	.45	6J5GT	.37	12SQ7	.44
1S5	.39	6J6	.52	12SR7	.49
1T5	.45	6J7G	.43	12S7	.39
1U4	.45	6J8	.30	14W7	.30
1V5	.39	6K5	.47	19BGG	.95
1X2	.63	6K7	.44	19T8	.79
1Y5	.70	6L5	.24	19V8	.89
2A4G	.24	6M7	.44	19W8	.89
2X2	1.50	6O7	.45	25AV5	.83
3A4	.46	6S4	.38	25B06GT	.62
3A5	.46	6S4	.43	25C7GT	.39
3Q4	.48	6SA7GT	.43	25W4	.56
3Q5GT	.46	6SD7GT	.41	25Z5	.40
3S3	.49	6S7GT	.41	25Z6GT	.40
3V4	.47	6S7GT	.41	26	.45
5U4G	.47	6SH7	.73	27	.39
5V4	.73	6S17GT	.41	32L7	.39
5W4	.50	6SK7GT	.41	35B5	.40
5X4	.40	6SL7GT	.48	35C5	.39
5Y4	.32	6SN7GT	.40	35L6GT	.41
5Y3GT	.32	6S07GT	.37	35W4	.37
5Y4G	.35	6SR7GT	.45	35Z4	.39
5Z5	.46	6S57	.42	3Z5GT	.39
6A7	.59	6T5	.56	37	.60
6A8	.62	6U4	.60	41	.42
6A85	.44	6U5	.44	44	.42
6A95	.43	6U6	.63	43	.55
6A15	.90	6UR	.61	45	.55
6A25	.75	6VACT	.39	45Z5	.49
6A35	.38	6W4GT	.44	50B5	.39
6A05	.39	6W6GT	.44	50C5	.39
6A05	.37	6X4	.37	50C6	.59
6A05	.37	6X5GT	.37	50C6GT	.41
6A05	.50	6X8	.61	50Y7	.50
6A15	.37	6Y6G	.48	53	.24
6A15	.38	7A4	.47	53	.39
6A15	.38	7A7	.53	57	.58
6A15	.83	7B4	.44	58	.60
6A15	.37	7C6	.40	7L7GT	1.19
6A15	.53	7E6	.30	75	.41
6A15	.64	7X7	.70	76	.44
6A15	.64	12A8	.61	77	.61
6A15	.39	12A5	.37	78	.47
6A15	.57	12A6	.37	80	.35
6A15	.44	12A7	.58	80	.52
6A15	.34	12A6	.38	85	.59
6A15	.59	12A7	.43	117L7	.99
6A15	.45	12A6	.39	117Z3	.99
6A15	.39	12A7	.43	205	1.15
6A15	.41	12AX4	.48	1274	.99
6A15	.27	12AX7	.43	205	1.45
6A15	1.25	12AX7	.69	613	1.00

TERMS: A 25% deposit must accompany all orders—balance C.O.D. All shipments F.O.B. Irvington warehouse. Orders under \$10—\$1.00 Handling Charge. Subject to prior sale. Don't Delay . . . Order Today!

RAD-TEL TUBE CO.

"Integrity Is Our Chief Asset"

Phone: Essex 5-2947 115 Coit Street
Dept. RN8 IRVINGTON 11, N. J.

FREE!

U.H.F. and "THE VERSATILE CRYSTAL PROBE"

Solve your U. H. F. ANTENNA PLACEMENT and ORIENTATION problems the easy way!

★

Get maximum picture strength - eliminate ghosts - no more roof-top shouting - no expensive field strength meters needed!

ONE MAN CAN DO IT!

★

Write for FREE bulletin today and other information about KLIPZON products.

UNITED TECHNICAL LABORATORIES
203 LITTLETON RD. ★ MORRISTOWN, N. J.

TRAIN FOR A SUPERVISORY POSITION IN
ELECTRONICS

Through 2-year course covers electrical circuits and machinery, basic electronics and industrial electronics. Franklin Technical Institute graduates are in demand as junior engineers for research and test work, sales engineering, supervisory work on production lines and drafting room design work. Other engineering and technical courses. Coed. Day, evening, 45th year. Write for catalog.

FRANKLIN TECHNICAL INSTITUTE
46 Berkeley Street Boston 16, Mass.

THE NEW TV
DYNATRACER



TRACES TV SIGNALS and VOLTAGES

LOCATES DEFECTIVE COMPONENTS INSTANTLY

REQUIRES NO ADDITIONAL EQUIPMENT

\$495

Ppd. or C.O.D. + Chgs.

Makes Television Servicing Easier, Faster and More Accurate—AT LOW COST

Ideal for trouble-shooting television in the field or on the bench. Used under actual operating conditions. Will out-perform more expensive testers. A must for every alert TV technician!

SPECIFICATIONS:
The "DYNATRACER" is a self-powered quality instrument designed to trace TV signals through any Video, Sound, Sync, APC or Sweep Circuit, and will isolate trouble to a stage or component.
With a flick-of-the-switch, "DYNATRACER" will also trace all voltages in any section. All components (Condensers, Resistors, Coils, Transformers, Speakers, etc.) can be checked for either open, shorted or intermittent condition, locating defective components.
Complete 10-Page Instruction and Trouble-shooting Book Enclosed.

10-DAY MONEY-BACK GUARANTEE
Send Check or Money Order to

Century ELECTRONICS CO.
8509-21st Ave., Dept. 203, Brooklyn 14, N. Y.

BUILD 15 RADIOS

AT HOME ONLY

With the New Improved 1953 \$19.95
Progressive Radio "EDU-KIT"

NOW INCLUDES
SIGNAL TRACER
and
CODE OSCILLATOR

- FREE TOOLS WITH KIT
- ABSOLUTELY NO KNOWLEDGE OF RADIO NECESSARY
- NO ADDITIONAL PARTS NEEDED
- EXCELLENT BACKGROUND FOR TELEVISION
- 10-DAY MONEY-BACK GUARANTEE



WHAT THE PROGRESSIVE RADIO "EDU-KIT" OFFERS YOU

The Progressive Radio "Edu-Kit" offers you a home study course at a rock bottom price. Our Kit is designed to train Radio Technicians, with the basic facts of Radio Theory and Construction. Practice expressed simply and clearly. You will gain a knowledge of basic Radio Principles involved in Radio Reception, Radio Transmission and Audio Amplification.

You will learn how to identify Radio Symbols and Diagrams; how to build radios, using regular radio circuit schematics; how to mount various radio parts; how to wire and solder in a professional manner. You will learn how to operate Receivers, Transmitters, and Audio Amplifiers. You will learn how to service and trouble-shoot radios.

You will learn code. You will receive training for F.C.C. license. In brief, you will receive a basic education in Radio exactly like the kind you would expect to receive in a Radio Course costing several hundreds of dollars.

THE KIT FOR EVERYONE

The Progressive Radio "Edu-Kit" was specifically prepared for any person who has a desire to learn Radio. The Kit has been used successfully by young and old in all parts of the world. It is not necessary that you have even the slightest background in science or radio.

The Progressive Radio "Edu-Kit" is used by many Radio Schools and Clubs in this country and abroad. It is used by the Veterans Administration for Vocational Guidance and Training.

The Progressive Radio "Edu-Kit" requires no instructor. All instructions are included. All parts are individually boxed, and identified by photograph and diagram. Every step involved in building these sets is carefully explained. You cannot make a mistake.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" comes complete with instructions. These instructions are arranged in a clear, simple and progressive manner. The theory of Radio Reception, Radio Transmission, Radio Amplification and Audio Amplification, servicing by Signal Tracing is clearly explained. Every part is identified by photograph and diagram. You will learn the function and theory of every part used.

The Progressive Radio "Edu-Kit" uses the principle of "Learn by Doing." Therefore you will build radios to illustrate the principles which you learn. These radios are designed in a modern manner, according to the best principles of present-day educational practice. You begin by building a simple radio. The next set that you build is slightly more advanced. Gradually, in a progressive manner, you will find yourself constructing still more advanced radio sets, and doing work like a professional Radio Technician. Altogether you will build fifteen radios, including Receivers, Transmitters, Amplifiers, Code Oscillator and Signal Tracer. These sets operate on 105-125 V. AC/DC.

The Progressive Radio "EDU-KIT" Is Complete

You will receive every part necessary to build 15 different radio sets. Our kits contain tubes, tube sockets, chassis, variable condensers, electrolytic condensers, mica condensers, paper condensers, resistors, line cords, selenium rectifiers, tie strips, coils, hardware, tubing, hook-up wire, solder, etc.

Every part that you need is included. These parts are individually packaged, so that you can easily identify every item. Tools are included, as well as an Electrical and Radio Tester. Complete, easy-to-follow instructions are provided.

In addition, the "Edu-Kit" now contains lessons for servicing with the Progressive Signal Tracer, F.C.C. instructions, quizzes. The "Edu-Kit" is a complete radio course, down to the smallest detail.

TROUBLE-SHOOTING LESSONS

Trouble-shooting and servicing are included. You will be taught to recognize and repair troubles. You will build and learn to operate a professional Signal Tracer. You receive an Electrical and Radio Tester, and learn to use it for radio repairs. While you are learning in this practical way, you will be able to do many a repair job for your neighbors and friends, and charge fees which will far exceed the cost of the "Edu-Kit." Here is your opportunity to learn radio quickly and easily, and have others pay for it. Our Consultation Service will help you with any technical problems which you may have.

FREE EXTRAS IN 1953

- Electrical and Radio Tester • Electric Soldering Iron • Book on Television • Radio Trouble-Shooting Guide • Membership in Radio-Television Club • Consultation Service • Quizzes • Training for F.C.C. License.

The Progressive Radio "Edu-Kit" is sold with a 10-day money-back guarantee. Order your Progressive Radio "EDU-KIT" Today, or send for further information. We pay shipping charges all over the world. If you send check or money order for \$19.95 with your order. On C.O.D. orders, you pay cost of delivery.

PROGRESSIVE ELECTRONICS CO.
497 UNION AVE., RN-21, Brooklyn 11, N. Y.

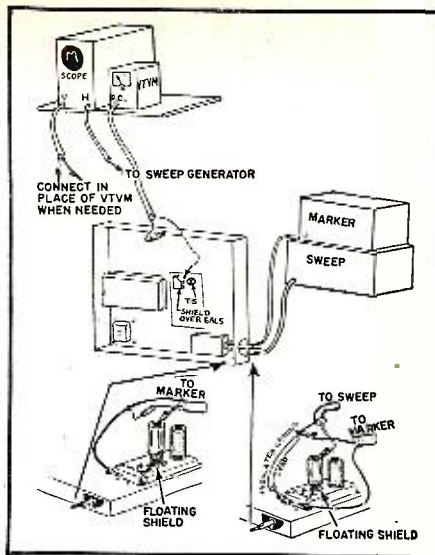


Fig. 8. Test equipment setup for video i.f. alignment outlined in Table 2.

removed, and the phase coil is adjusted so that the picture does not tear.

Note: Since no a.f.c. voltage is being applied to the multivibrator during the above adjustments, the horizontal blanking bar may move back and forth across the face of the picture tube.

To complete the adjustment, the jumper shorting the grid of the multivibrator is removed. The horizontal hold control should hold over the entire range if it is rotated slowly. If the horizontal should tear at only one end of the control, it is still within engineering specifications.

Before aligning the video i.f. stages of the receiver, do the following:

a. Tune the receiver to unused Channels 10 or 12.

b. Connect the negative terminal of a 3-volt bias battery to the i.f. a.g.c. This connection should be made at the junction of R_{10} , C_8 , and R_{16} (see Fig. 4). Connect the positive terminal of the bias battery to the chassis.

c. Raise the shield of the 6J6 converter tube, V_{23} , slightly so that it does not make contact with the chassis. (See Fig. 8).

d. The output cable of the sweep and marker generators should be properly terminated in their characteristic impedance (usually 50 to 75 ohms). If this termination has not been built into the end of the cable, connect a resistor of the same value as this characteristic impedance across the output of each generator cable, as shown in Fig. 8.

e. Proceed to step 1 on Table 2. ~~30~~

HAM CLUB ELECTS

MILWAUKEE Radio Amateurs' Club has named K. W. Eggert, W9MOT, president; Dr. C. P. Lawrence, W9RZJ, first vice-president; C. W. Thomas, W9WK, second vice-president; W. E. Herzog, W9LSK, secretary; and E. J. Belanger, W9MDG, treasurer for the year 1953-1954. Four directors were also elected. ~~30~~

TV High-Voltage Supplies

(Continued from page 49)

The resistance from the plate cap of the output tube to the low end of the flyback transformer will probably range from 15 to 60 ohms.

If the click and spark are not obtained, the output stage is either defective, the boost voltage is absent, or the output stage is not being driven by the horizontal oscillator circuits. This now requires the use of test equipment to locate the trouble.

Use a vacuum-tube voltmeter to measure the bias between grid and cathode pins on the output tube. Anything less than 20 volts is indicative of insufficient drive. If approximately 30 or more volts is obtained, check the damper by measuring the boost voltage at its cathode. If the boost voltage, which is usually a little less than twice the "B+" voltage, is not obtained, the damper stage or the flyback transformer may be defective. Make sure, of course, that the high voltage fuse (if there is one) is not blown. If the aforementioned tests fail to locate the defective part, use a scope to check the waveshape at the grid of the output tube. Since this is a qualitative analysis and the waveshapes differ from receiver to receiver, it is difficult to give a hard and fast rule as to what to look for. However, Table 1 contains the grid waveshapes and potentials obtained for a number of representative receivers. Failure to obtain these waveshapes and/or potentials indicates that the trouble lies between the grid circuit of the output stage and the horizontal oscillator circuits.

There are many troubles that do not cause the complete loss of high voltage, or which affect the width, linearity, etc. Among the most common troubles of this type are the following:

Picture Blooming: Due to a gassy high-voltage rectifier tube. Replace the tube, and if a doubler circuit is used, replace both rectifier tubes.

Insufficient Width: Caused by weak low-voltage rectifiers, or a weak output tube. Check the output tube cathode bypass if one is used. Also, check the screen grid components. If the linearity on the left side of the screen is affected more than on the right, check the damper tube and associated components. Check the boost voltage and the boost filter, such as the .22 μ f. condenser connected to the damper cathode (see Fig. 3).

Output Tube Requires Frequent Replacement (more than once a year): Check the grid coupling condenser. It may be leaky, causing excessive grid current to be drawn. Also, check the grid waveform to make sure that the tube is not being overdriven. In either case, a check of the bias will reveal if the tube is drawing excessive grid current.

In cases where the trouble has been traced to a defective flyback trans-

former it is very important that an exact replacement be made if additional troubles are to be avoided. Even a direct replacement sometimes may not work properly due to the fact that aging of components, or a previous incorrect substitution of parts may have produced operating conditions which are so far off tolerance that the rear apron controls can no longer reset the circuit for the desired results. Some of the more common troubles resulting from such mismatches, and the cures for them, are described below.

If, after replacing a flyback, insufficient width results, try shunting the width coil with a condenser whose value is between .025 to .05 μ fd. Another method is to increase the output tube coupling condenser in increments no higher than 10%, or to decrease the value of the screen dropping resistor in steps no higher than 10%, or combinations of both. If the high voltage is too low, reduce the capacitance across the width coil in decrements of 20%, or increase the drive and/or screen voltage as described for insufficient width. If excessive high voltage is obtained, reduce the drive to the output-tube grid by decreasing the size of the coupling condenser, or increasing the size of the screen-dropping resistor. If this fails, insert a 1000 ohm, 10 watt potentiometer in series with the low side of the flyback and the "B+" supply. Adjust the pot until the high voltage is reduced a sufficient amount. Remove the pot and substitute a 10-watt fixed resistor of a value determined experimentally.

If alternate light and dark vertical bars modulate the raster, check the damper stage and the drive to the grid of the output tube. If parasitic oscillations develop, insert a 47- to 68-ohm loading resistor in the grid circuit of the output tube, and a 68- to 82-ohm resistor in the screen circuit. Parasitics can also be suppressed by means of a magnet clamped to the output tube, or by redressing the leads connected to the flyback transformer. If a horizontal foldover develops, first check the horizontal a.f.c. circuits for correct adjustment, and then check the width and linearity components. Also, try substituting a number of different output tubes to obtain the one that matches best.

HAMFESTERS' PICNIC


THE Hamfesters Radio Club of Chicago will hold its annual picnic and automobile meet on August 9th at Mance Park, 1/4 mile east of Route 45 and 1/4 mile south of Route 66 (Stinson Airport). Free parking of planes at Stinson airport will be available but pilots must bring their own tie-downs.

Food, ice cream, and beverages will be available at the picnic grounds. A full program has been planned for the whole family.

Tickets are available from John J. Ruth, W9GVO, 4460 Oakenwald Ave., Chicago 15, Ill. A donation of \$1.50 is requested from those planning to attend the affair.

**NOW... PROFESSIONAL QUALITY SOUND REPRODUCTION
RIGHT IN YOUR OWN HOME!**

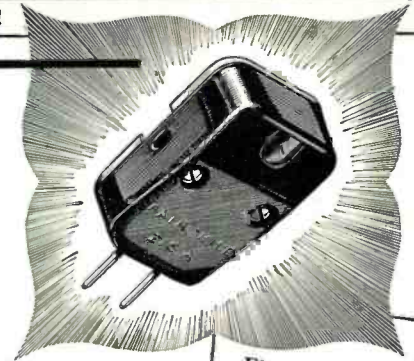THE AMAZING NEW **FAIRCHILD** SERIES 215 **DIAMOND CARTRIDGE**



Replace any modern pickup with this new cartridge, and enjoy recorded music as never before! **High compliance**—freedom of stylus to yield to rapid lateral deflections—provides these exciting improvements:

- New shades of tone color from fine recordings!
- New clear timbre in high volume piano chords!
- Rich low-frequency tones never previously heard!
- Arm resonance, "needle talk," rendered inaudible!
- Stylus wear greatly reduced, record quality preserved!
- And above all—**TRACKING DISTORTION ELIMINATED!**

High compliance, low-mass stylus assembly and smooth linearity of extended range are exclusive features of the new Fairchild 215.

First to achieve near-perfect lateral compliance for optimum Hi-Fi performance...

With finest diamond stylus for 33, 45 or 78 rpm records

Now Only
\$37.50

ORDER FROM YOUR AUDIO DEALER—or write direct to:

FAIRCHILD RECORDING EQUIPMENT

8th Ave. & 154th St., Whitestone, N.Y.
Manufacturers of the World's Finest Professional Sound Equipment

Watch for the

PHOTOGRAPHY ANNUAL

Everybody likes good pictures, and this big value is a treasurehouse of them. . . . Contains the best work of today's photographers in every field. . . . Concise notes in the back of the book tell the technical story behind each striking photograph.

ON SALE AUGUST 21

Reserve your copy now



L. A. HAM SHACK SELLS FOR LESS

METERS—WESTON • SANGAMO
ALL NEW • ALL D. C. • 2" SQUARE

0-5 Ma	} \$3.29 EACH or 3 for \$9.00
0-15 Ma	
0-50 Ma	
0-100 Ma	
0-200 Ma	
0-300 Ma	
0-500 Ma	

Mfg's inquiries: lots over 100

Voltmeter, 2" sq.—0 to 20 Volts	\$3.29
DC Voltmeter, 2" sq.—0 to 300 Volts w/Ext. resistance. Complete	\$3.95 3 for \$9.95
RF Ampmeter, 2" sq.—0 to .5 Amp.	\$3.95
Ampmeter, 2" rd.—0 to 50 Amps.	\$3.29
Ampmeter, 2" sq.—0 to 50 Amps.	\$3.29 3 for \$9.00

3" Round Meters, DC, All New, 0-15, 0-30, 0-300 Mills.	\$4.95 Each, 3 for \$11.95
Milliammeters, 2 1/2" rd., 0-30 Mills.	Each \$3.95
Milliammeters, 2" rd., 0-50 Ma, 0 to 5 Ma. movement.	Each \$3.29 3 for \$9.00
Thermocouple, 2" rd., 350 Milliamp. HF.	\$3.29
"S" METER, Illuminated face, Full scale reading of 5 ma. A standard value for most "S" Meter Circuits, 2 3/8". Black face, New.	\$2.49
Amp. Meter, No. 60-0-60, New.	\$1.29

COMMAND AND/OR ARCS TRANSMITTERS AND RECEIVERS	
3-6 MC Receiver	Used \$17.95 New 12.95
6-9.1 Receiver	Used 7.95—New 12.95
Triple Receiver Rack	1.95
V.H.F. ARCS Transmitter or Receiver, Complete w/tubes	Used 24.95
ARC-4 w/tubes, Good	Used 22.95
4-5.3 MC Transmitter with tubes	Used 8.95 New
5.3-7 MC Transmitter with tubes	8.95
7-9.1 MC Transmitter with tubes	10.95
3-4 MC Transmitter with tubes	18.95

TUBES:		
832A—\$7.95	815—\$3.95	866A—\$1.59
VP127A—\$2.95	872A—\$4.95	6AK5—\$.79
751L—\$3.95	304TL—\$4.95	717A—\$.97

1625—3 for \$1.00	W/Order of \$2 or more.
Trans. & Choke Combination	\$5.95
PRI: 115V. 60 cy.	SEC: 5.0V 2.0A
SEC: 5.0V 3.0A	412/710 VCT
6.4V 1.2A	225 MA. 6.4V 10.4A

Code Tapes for TG-10, 15 rolls: New. \$7.95
Cash with order. California orders please include 3 1/2% Sales Tax. Please include approximate postage—excess will be refunded. What have you in surplus? Submit.
L.A. HAM SHACK
1306 Bond Street, at Pico, Los Angeles 15, Calif.

Sensational TV BARGAINS!

NEW HIGH GAIN UHF YAGI

Good UHF reception in fringe areas now assured with new Rocket Broad band UHF Yagis. Compact, easy to stack for all the gain required anywhere. Three models cover all UHF channels. Rocket UHF Yagis are completely pre-assembled—just simply tighten mast clamp. Serviceman's array includes two reflectors, 2 dipoles, 4 directors and Universal mast clamp.



- Model UHF-2A—Ch. 14 thru 48
- Model UHF-2B—Ch. 27 thru 62
- Model UHF-2C—Ch. 47 thru 83

Single \$4.25 ea.
Lots of 6 3.75 ea.
Matched stacking bars—1/2 wave 75 pr.
UHF tubular twin lead—100' Coil 4.95

UHF TELEVISION CONVERTER

Suteo UHF television converter with built-in booster. Continuously variable for channels 12 thru 83. Built-in wide band VHF booster for channels 2 thru 13. Self-powered for 110 volt, 60 cycle AC operation. Selector switch gives choice of VHF or UHF antenna. VHF antenna may be fed thru the broad band booster or direct to the TV set. Stock No. 21A, shipping weight 7 lbs.



\$34.95

FAMOUS ROCKET ZOOM-UP TOWERS

Sturdy • Reliable • Easiest Installation
Economize with Rocket Zoom-up Towers. Offers quickest, easiest way to make an installation up to 50'. Each section telescopes inside the other—to erect, simply slide out each section in reverse—tighten to keep mast from turning. Each tower complete with guy rings, bolts, and mounting base suitable for flat roof. Handsome and sturdy. Rocket Zoom-ups offer you economy and long life. Order by size.



20' \$ 9.95 30' \$16.95
40' 21.95 50' 32.95
(Deduct 10% discount in lots of 3)

Sensational NEW ROCKET BROAD BAND YAGIS


- SENSATIONAL GAIN
- SENSATIONAL PICTURES IN FRINGE AND ULTRA FRINGE AREAS



Switch to Yagi Broad Band Hi-Gain antennas! These new Yagis give you Yagi reception on the 5 low-band and 7 hi-band channels—no restriction to one single channel. A tiny array will outperform even a 10 or 12-element single channel Yagi. Price is sensationally low. Complete serviceman's array includes 1 double reflector, 3 folded dipoles, 3 directors, universal mast clamp. Easy-to-assemble quick rig construction.

Model RB-26 Ch. 2 thru 6 \$10.95 Ea.
Model RB-713 Ch. 7 thru 13 5.95 Ea.
Matched stacking bars 1.25 Pr.

Fringe Master MOTORLESS DIRECTRONIC

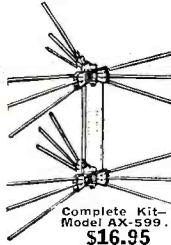

Clear Sharp Pictures—All Channels in All Directions.

- NO GHOSTS
- ELECTRONICALLY BEAMED
- NO INTERFERENCE
- NO MOTORS NEEDED

With new transmitters coming on the air, only the Motorless Directronic offers "round the compass" reception without motors. The Model AX-599 18-element stacked array provides sparkling reception in city or fringe—in all directions. Serviceman's kit provides 18 hi-tensil aluminum elements, 6-position Directronic Beam Selector, 1 set matched stacking bars, 75' TRI-X Cable, Universal U-Clamp.

Complete Kit—Model AX-599
\$16.95

Lowest Prices on Antenna Accessories

Mast Steel (Dualcoated 5' crimped) 1 1/4" O.D. \$1.05
Mast Steel (Dualcoated 10') 1 1/4" O.D. 1.95
Mast Connectors for 1 1/4" O.D. Mast59
Chimney Mount. Complete with Staps 1.19
Peak Roof Saddle (will take up to 1 1/2" O.D.) 1.59
Lightning Arrestor59
Galvanized Steel Guy Wire—6/20 3/4ct.
Rocket Twin-Lead—7/28 stranded 2ct.
Mast Stand-off Insulators—3"10
Screw Type Stand-off Insulators—3"02

NEW FALL AND WINTER CATALOG AVAILABLE

ALL PRICES F.O.B. CLEVELAND, OHIO
Do not remit more than complete purchase price. Pay shipping charges on receipt of goods. 25% deposit on all C.O.D. orders, please. Money-back guarantee. Prices Subject to Change Without Notice.

National Electronics
OF CLEVELAND
THE HOUSE OF TV VALUES
108 Delco Building Cleveland 3, Ohio

RADIO-TV Service Industry News

AS REPORTED BY THE TELEVISION TECHNICIANS LECTURE BUREAU

TO MANY of those who attended the annual electronic parts and equipment trade show in Chicago last May, the most significant development in new products introduced was the RCA "TV-Eye" and the Radio Corporation's new plan for distributing it.

The "TV-Eye" is a new camera for closed-circuit applications. Its significance as a new product stems from its price of less than one thousand dollars. The special importance of RCA's plan of distributing is that the "TV-Eye" will be sold through regular parts distributing channels. Installation, maintenance, and service will be handled by the selling organizations or independent service companies.

"You may logically ask—"Why is this development especially significant?"

To answer that question for you we would like to first review what David Sarnoff, chairman of the board of the Radio Corporation of America, said about industrial television in his speech before the IRE convention in New York City last March:

Industrial Television

"In a few short years we have seen television develop into a major factor in American life. Its extraordinary potentialities for political education, cultural instruction, and entertainment have been amply demonstrated. However, many other applications of television's basic function—extension of human sight—are ready for practical use.

"Thus far, the phenomenal growth of broadcast television has overshadowed these other applications which operate over closed-circuit systems and constitute the growing field of industrial television. The opportunities for expansion of television in this field are wide.

"Wherever danger, remoteness, or discomfort preclude the presence of a human observer, the industrial television camera can take his place. Handling of explosives, pouring of castings, watching the operations of furnaces, and remote power sub-stations are examples of television's usefulness to industry.

"As yet only a negligible fraction of

the potential of industrial television has been tapped. The major obstacle has been cost. That obstacle is being overcome by lightweight equipment. *The dimensions of industrial television may surpass the growth in broadcast television we are now witnessing.*" (Editor's note: italics ours.)

"Tomorrow we will demonstrate a much simplified closed-circuit television system, which provides a Vidicon camera attachment for a standard home television receiver. The simple attachment is connected as easily to a television receiver as a record-player and does not affect the normal use of the receiver in any way. With the addition of this camera unit every one of the 23,000,000 television receivers now in use becomes potentially a closed-circuit system for schools, the home, and other places.

TV in Schools

"Schools, in which television sets are becoming more and more a standard classroom fixture, may employ their TV sets to bring talks and demonstrations to the entire school or to selected classes, without the loss of time or the confusion attendant upon a call to assembly. On college campuses the linking of the lecture halls by television will permit exchange of instruction between departments, adding to the variety and interest of the courses. In biological research and technical education, this form of television has proved a valuable tool.

"The availability of a simple closed circuit system will put the television microscope as a new instrument for instruction within reach of every high school and college in the country.

"Until now industrial television has been utilized mainly by larger business and industrial organizations, but the reduction in cost brings it within reach of thousands of small businesses.

"Many uses are also foreseen for closed-circuit TV in hotels, department stores, and other business establishments.

Closed-Circuit TV in Homes

"One of the largest fields ahead for the use of closed-circuit television is the home itself. Closed-circuit sound

It's
"Capitol" for Values!

VARIABLE TUNING CONDENSER

Three-section gang condenser, with a worm gear drive. Which has a turn ratio of 1.5 to 180 degrees rotation. Tracking section has a capacity of 162 MMFD. The other two sections have a capacity of 388 MMFD. each. Trimmers mounted on the base. **\$1.49**

DUAL BRIDGE RECTIFIERS

Bradley Labs. copper oxide rectifiers with the Current and Temperature Characteristics balance to less than 1%. 10.5 Volts Input max. D.C. Center leg current 15 M.A. Discs have vaporized gold contact surfaces. These units are used as balance Modulators and Bridges. **\$2.25**

FILAMENT TRANSFORMER

MIL-T-27

Phi. 107.5, 112.5, 117.5, 122.5, 215, 255 and 245 Volts 50/60 Cycles. Secondary 6.3 Volts @ 0.32 Amps. and 6.3 Volts @ 3 Amps. Ceramic bushings with solder lug terminals. Rated for continuous duty under MIL-T-27, Class A Grade 1 Spec. Hermetically Sealed. **\$3.50**

WEBSTER CHICAGO CHANGER

Model 121

Automatically plays all records, all sizes, 12", 10", 7", all speeds—78, 45, and 33 1/3 RPM. Simple to operate. Automatically shuts off and tone arm returns to rest after last record has been played. Minimum mounting space required, 14 1/2" W., 13 1/2" D., 8 1/4" H., with 6 1/4" above mounting board. Wt. 14 lbs. **\$29.95**

GARRARD MODEL RC-80 RECORD CHANGER

Completely automatic, plays all records, 78, 33 1/3, or 45 r.p.m. regardless of size, 7", 10", and 12". Pusher type platform handles all records gently and positively. Has a special spindle to accommodate the large hole 45 r.p.m. records. Tone arm comes to rest when the last record is played. Comes with two interchangeable plug-in heads which will accommodate most crystal or magnetic cartridges, including the G. E. Variable Reliance Cartridge. Minimum mounting space 15 1/2" long x 13 1/2" wide with 2" above and 3 1/2" below motor board. Wt. 20 lbs. Operates on 105-120 volts, 60 cycles. Priced at a **\$37.50** new low.

HIGH FIDELITY TRIODE AMPLIFIER

Grommes model 215BA all triode basic amplifier. When the 215BA is used with the finest program sources such as F.M. tuners or transcription type phonographs and coupled to the best multiple speaker systems the result is reproduction of music as near to the original as is electronically possible. Frequency response of .5 db. 10 to 100,000 CPS (8 watt level). Power Response -1 db. 20 to 20,000 CPS (15 watt level). Output impedance 8 to 16 ohms (with a 50% mismatch permissible). Finished in chrome; also has 2 AC outlets. 105-120 volts, 60 cycles. Size 13"x7 1/2"x8" **\$89.50** Wt. 22 lbs. Price, each.

GROMMES MODEL 50PG AMPLIFIER

A 10 Watt high fidelity single unit amplifier, with unusual performance. The output essentially free of harmonics and intermodulation distortion as well as transient and high frequency oscillation. Frequency response 20 to 20,000 CPS ± 1 db. The built-in pre-amp is equalized for use of G. E. Pickering and similar type magnetic pick-ups. Output impedances, 3-4, 8 to 16 ohms. Attractive brown hammerloid finish. Size 11"x6 3/4"x7". Wt. 12 lbs. for 105-120 volts, 60 cycles. **\$49.50** Price, each.

IS YOUR TUBE DARK?

RE-VITALIZE THAT WORN OUT PICTURE TUBE WITH A CRT BRITENER.

Get months more service out of that old picture tube. No tools required, just plug it in, and watch that old brilliance restored. Used on any AC conventional parallel circuit. **\$1.65** Special price.....each

CAPITOL COMMODITIES CO., INC.
1229 W. WASHINGTON BLVD.
CHICAGO 7, ILLINOIS
TEL. TAYLOR 9-7393

systems are familiar to Americans. We think nothing of voice communication between rooms in the same house, between offices in the same building, between upstairs and downstairs. We are destined, I believe, to become equally familiar with closed-circuit systems of sight transmission.

"When the cost of the camera attachments is sufficiently low to permit their use in the average home they may make the television receiver truly the control center of the home. The snap of a switch will turn the receiver from the broadcast program to view the children asleep in the nursery or at play in the yard, or the cooking on the kitchen range. The housewife will not only hear but see the caller at the door before she opens it."

Up until last Fall the cheapest "camera chain" available for closed circuit TV sold for more than four-thousand dollars. These units were sold directly by their manufacturers and were installed and maintained by factory service people.

Last Fall the *Dage Electronic Corporation* introduced a TV camera that carries a list price of \$2850.00. When this camera was announced the *Dage Company* was literally swamped with inquiries about it, clearly demonstrating the tremendous interest already existing in the field of closed-circuit television.

In the span of less than a year's time closed-circuit TV camera systems have dropped in price from more than five-thousand dollars to less than one-thousand dollars. The most important factor in the cost of a TV camera is the price of the camera tube. The present list price of the Vidicon tube is around \$400. RCA is said to be stepping up production of this tube and it is possible that production efficiencies and economies will result in a steady lowering of the price of this popular tube.

It is obvious that *Radio Corporation of America* visualizes closed-circuit television as a potentially immense business in its own right perhaps, as Mr. Sarnoff said, "even surpassing the growth in broadcast television we are now witnessing."

Last Fall, speaking before the NEDA convention in Atlantic City, Hal Bershe, renewal sales manager for the RCA tube department, told parts distributors assembled there, "Today, now, ITV is practical for millions of applications. Do you realize that in this statement we are suggesting that millions of television cameras may someday be placed in service? Have you considered the possibility of stocking Vidicon camera tubes, as you now do with 6L6's?"

Importance to Service Industry

Many men operating TV service businesses have weathered the vicissitudes of the early "boom and bust" and subsequent periods of thoughtless service price cutting and user indifference to build stable business operations. Many of these men have ex-

get out
ahead in **uhf**

THESE PRACTICAL BOOKS
GIVE YOU THE "KNOW-HOW"

"UHF ANTENNAS, CONVERTERS AND TUNERS"



Milton S. Kiver gives you
all the answers on:

UHF Antennas: Full analysis of each UHF type—design, operation, directional characteristics, input impedance, gain—tells you type best suited for any given location and conditions.

Transmission Lines, Matching Networks: tells how to select proper line to deliver maximum signal to receiver.

Installation Practices: Practical advice on proper antenna location and routing of line to set; tells how to check for antenna mismatch, how to determine whether system is properly installed.

UHF Converters: Full analysis of all existing self-contained types, including turret tuner strips.

UHF Tuners: Covers tuner design and operation, ranging from parallel-wire to "butterfly" types—tells how they work.

This book keeps you ahead in TV, makes you a UHF expert, for extra profits. Get your copy today.

ORDER UHF-1 Only **\$1.50**

"UHF CONVERTERS"

Covers 21 Models

Be among the first to understand the design and operation of the new UHF converters and tuners. This book describes all the popular units and tells how they work with present VHF sets. Covers the following makes:

Arvin, Crosley, Dumont, G.E., Mallory, Motorola, RCA, Raytheon, Regency, Sarnes-Tarzan, Standard Coil, Stromberg, Sutco, Sylvania. To stay ahead in TV, you'll want this essential book.

ORDER UC-1. Only **\$1.00**



ORDER THESE BOOKS TODAY!

HOWARD W. SAMS & CO., INC.

Order from your Parts Jobber today, or write direct to Howard W. Sams & Co., Inc. 2203 E. 46th Street, Indianapolis 5, Ind.

My (check) (money order) for \$..... enclosed. Send the following books.

UHF-1 (\$1.50) UC-1 (\$1.00)

Name.....

Address.....

City..... Zone.... State.....

SPECIAL OF THE MONTH

GENERAL ELECTRIC 2" METER \$3.49 Ea.
0-500 Ma. Dc., Flush Bakelite Case...

NON-INDUCTIVE RESISTORS **59¢**
Ohmite, 250 Ohm, 100 Watt.
Special, 5 for \$2.50

SOLA CONSTANT VOLT. TRANSFORMER
Pri. 95-125 volts, 60 cy. Sec. Regulated
at 115 volts..... 30 VA. \$ 9.95
60 VA.\$14.95 120 VA.\$22.50

OIL CONDENSER SALE
2 MFD-2500 VDC. \$2.95 3.75 mfd 660VAC. \$2.45
4 MFD-2500 VDC. 5.95 .1 mfd 7500VDC. 1.75
2 MFD-3000 VDC. 3.95 .1 12KV DC. 2.95
3 MFD-4000 VDC. 5.95 .01x .01 12KV DC. 2.95
1 MFD-5000 VDC. 2.95 5 mfd 660 VAC. 2.95

6 HY, 400 MA FILTER CHOKE
Made by Acme. Only 30 Ohms DC Res. \$2.50
3000 Volt INS. ALL BRAND NEW.
Priced at a fraction of cost. 3 for \$6.50

0-150 MICROAMP METER
G.E., 2" flush Bakelite case. Scale 0-150
Microamps. BRAND NEW. A Terrific Value. \$4.95

FILAMENT TRANSFORMER \$1.95
10 Volts @ 6 Amps. Center tapped, 115
V., 60 cy. Primary..... ONLY
2 for \$3.50

G.E. PLATE TRANSFORMER
Pri. 120 V., 60 cy. Sec. 1140 Volts Ct. @ 1 amp.
Ideal for Bridge Rect. Fully Cased, Herm.
Sealed. In original cartons. ONLY...ea. \$16.95

MOBILE DYNAMOTORS
MADE BY PIONEER AND EIGOR
6 Volts Input, 425 Volts at 375
MA Output, 6 3/4" Long, 4" Di-
ameter. Weight 10 lbs. List
Price Approx. \$70.00.
BRAND NEW, ONLY. **\$24.95**

CARTER SUPER DYNAMOTOR
12 Volts Input, 400 V. Output @ 200 MA
Continuous or 3 MA Intermittent duty. Model B420.
Designed for Police, Aircraft and Ma-
rine Use. Small, rugged and effi-
cient. \$24.95 Each
BRAND NEW, ONLY.....

G. E. RELAY CONTROL
(Ideal for Model Controls, Etc.)
Contains a sigma midget 8,000 ohm, relay (trips
at less than 2 MA), high impedance choke, bi-
metal strip, neon pilot and many useful parts.
The sensitive relay alone is worth more
than the total low price of... \$1.25 Each 10 for \$9.90

Panel Meters **METER BUY**
NEW GOV'T SURPLUS **OF THE YEAR!**
STANDARD BRANDS 2" Simpson Meters
3" METERS Round Bakelite Case
0-10 MA AC.....\$2.95 Brand New—
Original Cartons
0-50 Microamps...\$8.95
0-100 Microamps... 7.95
0-200 Microamps... 6.95
0-400 Microamps... 5.95
0-500 Microamps... 5.95
0-10 Milliamp... 4.50
0-150 Milliamp... 4.50
0-200 Milliamp... 4.50
0-300 Milliamp... 4.50
0-500 Milliamp... 4.50
0-1000 Milliamp... 4.50
0-50 Volt DC (1 MA) 4.95
0-150 V. DC (1 MA) 4.95
0-1.5 Volts AC... 4.95
0-3 Volts AC... 4.95
0-150 Volts AC... 7.50
4" METERS
0-200 Microamps...\$8.95

WIRE WOUND RESISTORS
Stock too long to list. We can supply most sizes,
so order what you need.
5 Watts. From 1 Ohm to 40K Ohms. Ea. \$.09
10 Watts. From 1 Ohm to 70K Ohms. Ea. .15
20 Watts. From 4 Ohms to 50K Ohms. Ea. .20
25 Watts. From 1 Ohm to 100K Ohms. Ea. .30
50 Watts. From 5 Ohms to 100K Ohms. Ea. .40
100 Watts. From 50 Ohms to 100K Ohms. Ea. .50
ADJUSTABLE SLIDER, WIRE WOUND
10 Watts from 1 Ohm to 10K..... \$.25
25 Watts from 20 Ohms to 2.5K..... .35

VACUUM CONDENSERS
50 mmf. 5 KV, General Electric..... \$ 5.95
50 mmf. 20 KV, Jennings..... 7.95
100 mmf. 20 KV, Jennings..... 12.95
150 mmf. 20 KV, Jennings..... 16.95

1 MEGOHM, 1% W.W. PRECISION RESISTORS, SHALLCROSS.
ONLY..... 97c ea.; 10 for \$8.95

BAKELITE CASED MICAS
MFD VDC Price MFD VDC Price MFD VDC Price
.001 600 \$.18 .01 1 KV \$.45 .02 2 KV \$.90
.002 600 .24 .002 1200 .35 .005 2500 .55
.01 600 .26 .02 1500 .65 .002 2500 .45
.02 600 .26 .033 1500 .75 .004 2500 .50

Min. Order \$3.00—25% with Order

PEAK ELECTRONICS CO.

66 West Broadway, New York 7, N. Y.
Phone WOrth 2-5439

panded the scope of their activities to handle other facets of service in the electronics field like AM-FM radios, auto radios, and mobile 2-way communications systems. In some cases, to level off seasonal fluctuations, these service executives have gone into home air conditioning, low voltage house wiring, and major appliance installation and maintenance.

It is for these businesses that closed-circuit television holds the greatest immediate opportunities. In most of our discussions of ITV we have dealt with monochrome systems. Substantial progress has been made in perfecting color TV equipment for closed-circuit work. Color TV has an especial appeal in medical applications and it is reported that one company is now in production on color TV cameras and monitors with the idea of aggressively exploiting the ready markets for this type of equipment. It is the plan of this organization to arrange for the installation, maintenance, and service of its systems by competent, independent TV service companies.

However, it is imperative that any TV service organization that wants to share substantially in the growth of closed circuit television must start now to prepare its personnel in both camera circuitry and application idiosyncrasies of this type of electronic equipment. Where it was possible to learn a lot about TV service and installation through 'cut and try' in the early days, closed circuit installation and maintenance will require expert technical 'know-how' right from the start.

Hi-Fi Future

One of the most interesting developments in recent months is the announcement by such primarily radio and television firms as RCA, General Electric, Admiral, Philco, and I.D.E.A. ("Regency") that they are entering the high-fidelity audio equipment field. These and other companies are finding out, just as Stromberg-Carlson did almost a year ago, that there is a strong and ever-growing market for "packaged" high-fidelity systems or individual units which have been engineered to work together to produce the best results. These "matched" sets, which can be purchased at one time or added as the customer wishes, are gaining an enthusiastic acceptance among audiophiles.

The tremendous interest in high-fidelity reproduction that music lovers have shown during the past two years through their attendance at audio equipment shows in various parts of the country, indicates an ever-widening interest in custom-installed sound equipment in the home.

The bottleneck in the exploitation of the high-fidelity market has been brought about by the wide variety of methods employed in distributing the equipment which is of interest to the mass market of home owners. Service businessmen have not been interested in promoting custom-installed sound

equipment because after they have spent the money and time getting a customer interested in high fidelity equipment the customer will discover where he can buy the units at dealer prices and either buy them himself or drop the idea with the feeling that the service dealer is profiteering at his expense.

In numerous instances service operators have shown your editors where, after they had spent considerable time in detailing an installation of sound equipment for a church or a commercial organization, the principals involved bypassed them and bought the necessary units from a local parts distributor. In selling custom-installed sound equipment it is necessary to give the customer a layout of where the units will be placed, how the wiring will be accomplished, and details of the units that will be used in the installation.

A novice to the hi-fi field, figuring on an investment in custom-installed equipment, quickly finds other hi-fi enthusiasts who know all the answers—particularly about where you can buy the elements for a high-fidelity system at the lowest cost. When that happens the retail dealer who developed the interest is out of luck. He doesn't have a chance to close the sale or to get any return on the time and knowledge he has given in developing the consumer's interest.

This situation has brought aggressive selling of high fidelity equipment to a standstill at the consumer level.

The unfortunate part of this situation is that the tremendous mass market for custom-installed hi-fi equipment will remain unexploited because of the lack of aggressive promotional activity at local levels. The present hi-fi market is largely comprised of the audio enthusiasts in the half million segment of our population who are familiar with the elements of electronic circuitry.

This impasse may be broken some day by some manufacturer or combination of manufacturers who set up sales programs for package sound that will be available only through authorized dealers capable of installing and maintaining it. A "package" of quality equipment aggressively merchandised to home owners would find a receptive market among the many thousands who would appreciate the pleasures of high fidelity sound without the bother of trying to understand how it is accomplished.

Service Business Categories

When you speak of an electronic service business, the average man will visualize a one-man shop with the owner busy plying a soldering iron to the innards of an up-turned radio or television receiver. But while industry attention has been directed largely to the expanding base provided by new products and the extension of manufacturing and distributing facilities, a great many changes have been taking place in

the businesses devoted to the servicing of electronics products. We felt it would be of interest to our readers in the service business to know the many categories into which the activity has expanded:

1. Television (installation and service)
 - (a) TV Service—dealer operated
 - (b) TV Service—wholesale — for non-servicing dealers
 - (c) TV Service—consumer only —complete service home and shop
 - (d) TV Service—installations only—for dealers
 - (e) TV Service—drive-in — customer brings set in —picks it up after service is completed.
2. AM-FM radio service
3. Phono service—automatic changer specialists
4. Auto radio specialists
5. Wire and tape recorders
6. Audio equipment — (industrial and commercial) — sales and service
7. Mobile 2-way communications equipment
8. Industrial electronics maintenance
9. Community and apartment house TV systems.

In their travels about the country your editors have found several thriving businesses that specialize in the servicing of wire and tape recorders. This type of equipment, now widely used in businesses and by professional people, has been passed up by most service operators. On the other hand, one typewriter sales store that went into selling wire and tape dictating machines soon found the adjustment and servicing of recorders to be a profitable avenue that supplies a consistent volume of business.

TTLB Bulletins Available

From time to time we have offered bulletins to our readers which cover various subjects of interest to people

engaged in the service business. From time to time we get letters from readers asking for bulletins that were offered several years ago. Unfortunately, most of these bulletins are out of print.

At the present time we have the following bulletins available to those who would like to have them:

1. Financing a TV Service Business
2. Standard TV Labor Pricing Schedule
3. Your Market — Replacement phono needles, cartridges and changers
4. Closed Circuit TV—Opportunities for Independent Service Businesses.

In requesting bulletins address your letter to: TTLB Information Service, P. O. Box 1321, Indianapolis 6, Ind., and include an addressed, stamped envelope. Twelve cents in postage is required for all four bulletins listed above. —30—

AMATEUR TELETYPE

THE Southern California Radio Teletype Society, an amateur group, has been publishing a highly informative and professionally laid out bulletin called "RTTY" since January of this year. "RTTY" carries articles on amateur teletype equipment and techniques, reports on station and network activities, and supplies information on the availability of equipment, etc.


A page called "Tape off the Floor" gives interesting gleanings from conversations between amateur teletype stations all over this country and Canada. The SCRTS and "RTTY" plan to make an "Amateur Radio Teletype Handbook" available late in September.

Subscription to "RTTY," which is non-commercial and non-profit, is not restricted to SCRTS members and may be had by anyone for \$1.80 a year, which covers the cost of printing and mailing. Further information may be obtained from Merrill Swann, W6AEE, at 3769 East Green Street, Pasadena 10, California, the address of the Society. —30—

Over-all view of the manufacturing area of Allen B. Du Mont Laboratories' new Instrument Division plant in Clifton, N. J. The new facility contains 118,000 square feet of space for the development and manufacture of cathode-ray instruments.



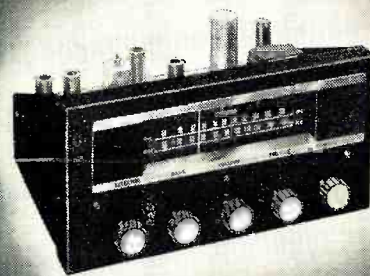The C-800 is here
to bring you new
record performance!



the new
craftsmen 800

FM-AM TUNER

with built-in phono
preamplifier and
record equalizer

Now—Craftsmen brings you a tuner that matches all your finest records... is setting new records for versatility, too. The C-800 is further evidence that Craftsman leadership in high fidelity is something you can put your finger on, something you can hear.

- Front-panel-selected equalization for AES, LP or European recording characteristics. Inverse feedback compensated dual-triode phono preamp for correct turnover and roll-off characteristics.
- Improved AM reception. Wider bandwidth for better fidelity, and sharper IF bandwidth "skirts" for greater selectivity.
- Double-shadow tuning eye and AFC (no drift) on FM simplifies tuning. Front-panel AFC cut-out for tuning weak stations.
- Efficient new layout. Bottom plate, completely shielded chassis minimize oscillator radiation, assure tuner isolation.
- Cathode follower audio output for remote installations; 2 volts at less than 1/2% dist. Detector output also has cathode follower for recording applications.
- Bass and treble controls continuously variable from attenuation to boost—flat position clearly marked. Selector positions: FM, FM with AFC, AM, TV, LP, AES, EUR, and SPare.
- Mahogany-finish wood cabinet available.

HIGH FIDELITY — LOW COST! C-400 audio amplifier offers 10 watts ± 1 db., 15—20,000 cps., less than 1% distortion. New streamlined chassis design.

Write
today for
information

THE RADIO[®]
craftsmen INC.

Dept. R-8, 4401 N. Ravenswood Ave.
Chicago 40, Ill.



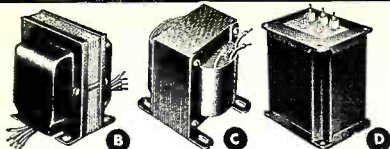


PLATE TRANSFORMERS

(All primaries are 110 v. 60 cps, single phase)
DC ratings are approximate values obtained at output of a 2-section choke input filter using MV rect. tubes.

TYPE	VOLTS AC. R.M.S.	D.C. VOLTS	D.C. MA.	FIG.	PRICE
PT 401	550-550	400	150	B	\$ 6.43
PT 157	660-660*	500	250	B	8.42
	550-550	400			
PT 158	1080-1080	1000	125	B	10.00
	500-500	400	150		
PT 159	900-900	750	225	B	9.70
	800-800				
PT 167	1400-1400	1200	300	C	24.10
	1175-1175				
PT 168	2100-2100	1750	300	C	30.58
	1800-1800	1500			
PT 062	2900-2900	2500	300	D	47.04
	2385-2385	2000			

*Simultaneous rating

FILTER CHOKES

(Smoothing)

TYPE	IND. HYS.	CUR. MA.	DCR (OHMS)	TEST VOLTS	FIG.	PRICE
181	10	200	140	3000	B	\$4.70
182	10	250	125	3000	B	6.47
183	8	300	80	3000	B	6.76
Swinging input choke						
187	4-16	150	210	3000	B	3.82
189	4-16	250	125	3000	B	6.47
190	3-14	300	80	3000	B	6.76

DYNAMOTORS

ALL BRAND NEW—ORIGINAL PACKING

TYPE	INPUT VOLTS	INPUT AMPS	OUTPUT VOLTS	OUTPUT AMPS	PRICE
PE 86	28	1.25	250	.060	\$4.25
DM 416	14	6.2	330	.170	6.75
DM 33A	28	7	540	.250	3.95
BD AR 93	28	3.25	375	.150	7.50
23350	27	1.75	285	.075	3.95
B-19 Pack	12	9.4	275	.110	8.95
			500	.050	
DA-3A*	28	10	300	.260	6.95
			150	.010	
			14.5	5.	
5053	28	14	250	.060	3.95
PE 73 CM**	14	1.8	1000	.350	**
337	14	8	425	.160	7.95

* Replacement for PE 94.
** Price sent on request.

INVERTERS

PE-218-H: Input: 25/28 vdc, 92 amp. Output: 115 v. 350/500 cy 1500 volt-amperes. New. . . . \$44.50
PE-206: Input: 28 vdc, 38 amps. Output: 80 v 800 cy, 500 volt-amps. Dim: 13"x5 1/2"x10 1/2". New. . . . \$22.50
NAVY QCR-211095: Input 22-30 VDC/75-80A. OUTPUT: 115V/400 CY. 1 KVA/8.7A. RPM: 4800. With coupling provision for motor. Brand New. Original packing \$150.00

TELEVISION TEST GEAR

KAY MEGASWEEP, T.V. Align. Gen. . . . \$215.00
KAY MEGAPIPPER T.V. Mark. Gen. . . . 85.00
KAY MEGAMARKER SR. Chan. 2-13. Marker Gen. . . . 95.00
*All equipment is used, but excellent. Guaranteed to be in A-1 shape.

RCA TV TEST PANEL

Complete RCA TV Service and Test Laboratory comprising the WV-55A Master Voltohmmeter, WA-54A Beat Frequency Oscillator, WO-55A Oscilloscope, WR-67A Test Oscillator, WR-59A TV Sweep Generator, WR-39A Calibrator on a sturdy metal display rack. A complete TV service bench. \$597.00 Used, but A-1 cond.

APN-3 SPARE PARTS

K-901684-501: SCS #229632-306, Trans. . . . \$2.49
K-901689-501: SCS #229631-238, Trans. . . . 2.25
K-901692-503: SCS #229617-70, Xfmr, Fil. . . . 2.49
K-901699-501: SCS #229617-68, Fil. Xfmr. . . . 3.45
K-901698-501: SCS #229618-38, Plate Xfmr. . . . 4.29
K-901695-501: SCS #229627-10, Pulse Xfmr. . . . 3.50

AUDIO TRANSFORMERS

AT SUB Subcoupler, Multimatch, 200 ohms to 15 K ohm C.T. and 100 K ohm Grids. . . . \$ 69
AT731 H.F. Plate (1500 ohm C.T.) to V.C. (16/4 ohms) 20-15KC \$3.29
AT501 Hi-Fi Special: PRI: 3000 ohms P-P/Sec: 4/16/12/30/200 ohms 60-10,000 CY. -I db 50W \$3.49
AT152 Hi-Fi Driver PRI: 10,000 ohms Sec: 40,000 ohms P.P. Grids 30-15 K/1 db. . . . \$1.49
AT602 Output to H.S. or line PRI: 14,200 Ohms SEC: 8000/600 ohms \$1.10
AT449 Hi-Fi Driver (5000 ohms) to P.P. output grids (4,000 ohms) 100-10,000 CY, 10 W 6V6 to PP 805's \$2.39
AT666 Intercon Input: Spkr (-4.8 ohms) to grid (250,000 ohms) \$0.69
AT415 Plate (18,000 ohms C.T.) to line (125 ohms) 175 w.-500-600 CY. . . . \$1.95
AT858 Plate (10,000 ohms C.T.) to line (125 ohms) 125130 ohms HI-FI-50 W \$6.95

Send M.O. or Check. Shipping Chgs. C.O.D.
COMMUNICATIONS EQUIPMENT CO.
131 Liberty St. Dept. N-8 New York City 7, N. Y.

Mac's Service Shop (Continued from page 66)

"It's not so strange. People are pretty meter-minded. The gas man measures the pressure delivered to the house with a meter. The electrician uses a similar gadget on the mains. The garageman checks their car battery with a meter, and the local police may even, on occasion, use a meter to tell how many beers they have had. It only seems natural and businesslike to them that the TV service technician should have a device to measure the amount of signal delivered to the set."

"That meter does a fine job of checking set accessories, too," Barney remarked. "With it I can tell in a matter of seconds if a booster is boosting or not and how much. In the same way I can put it across the output of a u.h.f. converter and tell in a minute if the cause of poor u.h.f. reception lies in the converter or in the set. Along with this, of course, I employ the meter to measure the u.h.f. antenna voltage. Since we installed those u.h.f. strips in the meter's turret tuner, the gadget is just as useful on u.h.f. signals as it is on v.h.f. measurements. Some of those u.h.f. antennas have mighty sharp lobes, and you need the meter to line them up exactly."

"I was just thinking," Mac mused, "that we use the field strength meter around the shop for a lot of things besides the ones we've mentioned. For instance, I ran the signal generator into that two-set coupler we bought and then measured the output across the two receiver connections and found that one leg had twice as much output as the other. I used the meter again when I was building up that ladder-type attenuator so we might have as weak a u.h.f. signal as we want for checking fringe-area sets. The field strength meter tells me exactly how many sections to cut in or out to get just the signal strength required."

"It is also just what the doctor ordered for checking the output and attenuators of our sweep and marker generators. You will recall that we found our sweep generator could not be reduced to a very low level of output until probing around with a piece of twin-lead connected to the field strength meter showed that the r.f. was coming out on the line cord. After we put a line filter inside the case, that put an end to the leakage, and the attenuator worked as it should."

"Yeah, and that gave me an idea," Barney exclaimed. "I put a highpass filter on the input terminals of the meter and took it home with me to help track down some harmonic leakage in my ham rig that was causing TVI. With a short length of twin-lead terminating in a two- or three-turn coil for a probe, that field strength meter makes the most sensi-

CRYSTALS

LARGEST STOCK

IN THE WORLD



In FT 241-A Holders—1/2 in. Pin SPC. These are designated 54th

or 72nd Harmonic MC freq. Listed by fundamental freq. with fractions omitted.

370	396	419	443	466	491	513
372	397	420	444	468	492	514
374	398	422	445	469	493	515
375	400	423	446	470	494	516
376	401	424	447	472	495	518
377	402	425	448	473	496	519
379	403	426	449	474	497	520
380	404	427	451	475	498	522
381	405	429	452	476	500	523
383	406	430	453	477	501	525
384	407	431	454	479	502	526
385	408	433	455	480	503	527
386	409	434	456	481	504	529
388	411	435	457	483	505	530
390	412	436	458	484	506	531
391	413	437	459	485	507	534
392	414	438	461	486	508	536
393	415	440	462	487	509	537
394	416	441	464	488	511	538
395	418	442	465	490	512	540

All above crystals sent postpaid. Also available in complete sets for SCR-608, SCR-528, SCR-628, and TRC, Foreign, wholesale, and dealer inquiries invited. Write for LARGE QUANTITY DISCOUNTS.


COMPLETE SET—80 CRYSTALS

In above gradations, INCLUDING 500 Kc. & 455 Kc. crystals. . . . Per set \$12.50
Only

COMPLETE SET—120 CRYSTALS

In above gradations. PLUS 500 Kc. & 455 Kc. crystals. . . . Per set \$16.95
Only
200 KC. CRYSTAL. . . . Ea. \$2.25
1,000 KC. CRYSTAL. . . . Ea. \$2.25

All crystals sold as is.

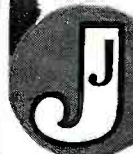

J. J. GLASS ELECTRONICS CO.
1615 S. MAIN STREET
LOS ANGELES 15, CALIF.

GET INTO ELECTRONICS



You can enter this uncrowded, interesting field. Defense expansion, new developments demand trained specialists. Study all phases radio & electronics theory and practice: TV; FM; broadcasting; servicing; aviation, marine, police radio. 18-month course. Graduates in demand by major companies. H.S. or equivalent required. Begin Jan., March, June, Sept. Campus life. Write for catalog.

VALPARAISO TECHNICAL INSTITUTE
Dept. RD Valparaiso, Indiana

ANOTHER OUTSTANDING JOBBER RADIO PRODUCTS SALES CO.

1237 - 16th St.
Denver 2, Colorado

HAS THE SENSATIONAL NEW
EICO 470-K 7"
SCOPE KIT
IN STOCK!



\$79.95

SCHEMATICS—CONVERSIONS FOR SURPLUS GEAR

NEW LIST! MANY ADDITIONS!

Send stamped, self addressed envelope for List C. Add 25c for chart explaining AN nomenclature.

R. E. BOX 1220
GOODHEART BEVERLY HILLS, CAL.

tive harmonic indicator you could hope for. Later I learned that Phil Rand in the June, 1952 issue of "QST" tells how this very meter can be modified especially for running down TVI by installing a coax connector and a couple of filters and by drilling a hole in the panel so the oscillator coils may be adjusted to cover an extended range either side of the video carriers. I was able to track down my trouble, though, without doing this."

"I am glad," Mac remarked dryly as he turned the channel selector knob to make sure no holes had been drilled in the panel.

"Don't forget the tests we made on u.h.f. antennas and lead-ins," Barney said, "You had me up on the cold, cold roof connecting identical lengths of various kinds of lead line to the antenna and pouring water down along them while you sat here in the nice warm shop tabulating relative field strength readings."

"Well, you were the one who wouldn't trust the attenuation figures given in the books," Mac retorted; "and then our findings were almost identical with the published ones. One thing worthwhile we did find out, though, was which of the various brands of matching transformers used for connecting a v.h.f. and a u.h.f. antenna to a single lead-in were the best. By connecting the lead first to the u.h.f. antenna and then to the v.h.f. antenna and noting the relative signal strength received, and then by using the various types of matching transformers one at a time and taking new u.h.f. and v.h.f. readings, we got a clear picture of the effect each transformer had on the two signals."

"The thing I like about using a field strength meter is that it teaches you what kind of performance to expect out of each brand of receiver," Barney said. "That is important in this area that is ultra-fringe v.h.f. but primary u.h.f. since we got our new station. While I realize this meter is not intended to measure received signal strength in absolute microvolts—such a job would cost several thousands of dollars—it is a very dependable indicator of relative signal strength. Using it, we have learned that we must have a reading of ten to fifteen microvolts to make some sets hold sync, while others will hang right in there down to two or three indicated microvolts. Certain models will be snow-free when our meter shows 100 microvolts; others take two or three times this amount. Knowing what to expect out of a set is dog-gone important, but first you have to know what goes into it."

"That's right," Mac agreed. "The signal is what the technician has to work with, and with a good field strength meter he can trace it beyond the antenna terminals right up to the antenna itself. Considering the important part that the antenna plays in TV reception, I should say that was essential."

PAY LESS FOR TUBES

INDIVIDUALLY BOXED - FULLY TESTED - EACH TUBE GUARANTEED FOR SIX MONTHS

Type	Price	Type	Price	Type	Price	Type	Price
1B3GT	\$.69	6A55	\$.50	6K6GT	\$.41	12A27	\$.70
1H5GT	.46	6AT6	.38	6L6G	.80	12BA6	.45
1L4	.57	6AU6	.43	6L6GA	.80	12BE6	.47
1N5GT	.57	6AV6	.36	6S4	.46	12BH7	.63
1R5	.56	6B4G	.96	6SA7GT	.52	12BZ7	.75
1S5	.47	6BA6	.48	6S17GT	.47	12SA7GT	.52
1T4	.56	6BC5	.53	6SK7GT	.50	12SK7GT	.50
1T5GT	.71	6BD5GT	.89	6SL7GT	.62	12SL7GT	.61
1X2	.67	6BF6	.47	6SN7GT	.54	12SN7GT	.54
3Q5GT	.65	6BF5	.60	6S07GT	.42	12S07GT	.44
354	.58	6BG2	1.34	6T8	.78	19G6	1.33
3V4	.58	6BH6	.57	6U8	.85	19C8	.74
5U4G	.43	6BJ6	.48	6V6GT	.48	19TR	.59
5V4G	.73	6BK7	1.10	6W4GT	.45	2100G	.80
5Y3G	.34	6BL7	.83	6W6GT	.57	2110GT	.48
5Y3GT	.30	6B0G	.89	6X4	.31	2326GT	.42
6AB4	.46	6BQ7	1.10	6X5GT	.33	33A5	.48
6AF4	1.40	6BZ7	1.10	6Y6G	.59	33B5	.47
6AG5	.54	6C4	.31	7AT	.42	35C5	.47
6AK5	.95	6C6	.53	12AT6	.38	35L6GT	.47
6AK6	.63	6CD6	1.85	12AT7	.68	35W4	.31
6AL5	.40	6CGT	.45	12A06	.43	35Z5GT	.30
6AN4	1.30	6H6GT	.49	12AU7	.55	60B5	.47
6A05	.46	6H8GT	.45	12AV6	.38	50C5	.47
6A06	.42	6J5GT	.40	12AV7	.80	50L6	.39
6AR5	.38	6J6	.62	12AX7	.61	11Z3	.68
						11Z6	.68

Motorola Ballast Tube #17A48545930
 Each tube is performance-proven. 25% deposit must accompany all orders. Balance C.O.D. All prices F.O.B., N.Y.C. If remittance is made with order, you can deduct 2%. \$1.00 handling charge for orders under \$10.00. Subject to Prior Sale. Importer inquiries invited.

PHILLIPS TUBE COMPANY

2281 Nostrand Ave.
 BROOKLYN 10, N. Y.
 CLOVERDALE 3-8010-1-2

IT'S HERE!

The NEW IMPROVED DAVIS SUPER-VISION


**ALL-CHANNEL TELEVISION ANTENNA
 For FRINGE AREA and DX**

**Brings in the Signals STRONG
 and CLEAR up to 125 Miles and
 More Away from the Station**

**The NEW DAVIS
 SUPER-VISION**

**has been
 WIND-TESTED
 and
 WEATHERIZED**

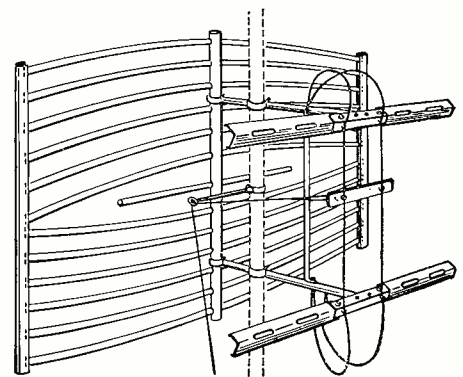**...STURDY BUILT and
 STRENGTH-INCREASED
 so it will stand the gaff in
 any part of the country**



"The Original Antenna Sold With A
 Money-Back Guarantee"

**Built By America's Fastest Growing
 Antenna Manufacturer**

AT YOUR JOBBERS, or MAIL COUPON TO:

DAVIS ELECTRONICS
 BOX 1247, Burbank, California

SIRS: RUSH INFORMATION TO ME AS CHECKED:

Send Complete Information and Technical Data on New SUPER-VISION ANTENNA.

Send Name and Address of NEAREST JOBBER.

Name _____


Street _____

City _____ State _____



THE Original

WRENCH
WITH THE
SCREWDRIVER ACTION!

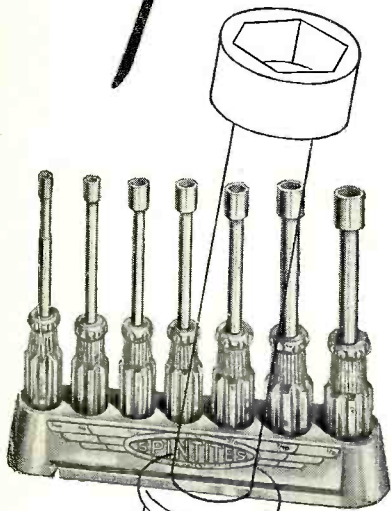

SPINTITE

REG. U. S. PAT. OFFICE

120 STYLES and SIZES

for

- ASSEMBLY WORK
- REPAIR WORK
- RADIO
- TELEVISION
- INDUSTRIAL
- AIRCRAFT



STEVENS WALDEN, Inc.
WORCESTER 4, MASS.

SERVICE HINTS ON EMERSON TV SETS

CHASSIS 120094A

60-cycle buzz.

To eliminate such buzz from the audio when it is present even at low settings of the volume control, do the following:

1. Dress all leads to the picture-tube socket as far from the 6T8 tube as possible. This can be done by securing the green grid lead wire to the side of the cabinet.
2. If the buzz persists, realign the sound circuits and sound traps.

CHASSIS 120095

Bright noise streaks.

To eliminate such disturbances from the picture, remove the 22-ohm resistor connected between the tuner frame and "B—", and replace with a jumper wire.

CHASSIS 120095B


Audio buzz.

Change condenser C_{15} (1500 $\mu\text{fd.}$) to a 220- $\mu\text{fd.}$ unit. This is the cathode bypass condenser of the sound mixer tube (V_4 , 12AT7).

CHASSIS 120109 & 120120

Replacement of the 2-megohm high-voltage resistor.

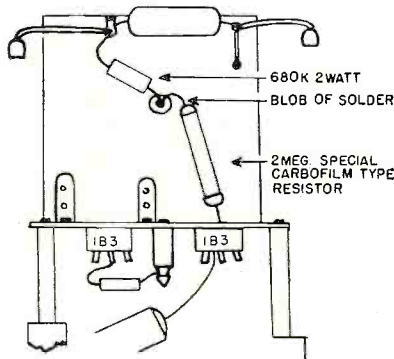This resistor is R_{30} in the 120109 chassis, and R_{16} in the 120120 chassis. When replacement of these resistors becomes necessary, a 680,000-ohm, 2-watt Allen Bradley resistor should be placed in series with the new 2-megohm unit. No substitutes should be used for either one of these resistors. The



method of mounting is shown in the accompanying diagram.

The junction of the two resistors should be looped, and a large blob of solder should cover any points or sharp ends. This prevents ionization of the air, or arcing.

CHASSIS 120118B

Loss of horizontal sync.

1. Replace the horizontal oscil-

lator and control tube (V_{13} , 12SN7GT).

2. Replace C_{37} (.002 $\mu\text{fd.}$, 400 volt) condenser with a 600-volt unit of the same value.


Bad arcing in raster, small irregular raster. Replace T_1 horizontal oscillator and phasing coils.

CHASSIS 120123B

Inter-carrier buzz.

To eliminate this condition, do the following:

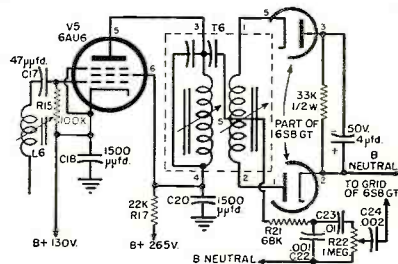1. Remove the following components from the circuit:
 - a. C_{21} (110 $\mu\text{fd.}$) connected



between pin 5 and pin 2 of V_6 (6S8).

- b. Resistors R_{29} and R_{20} (100,000 ohms) from lug 5 of T_6 , the discriminator transformer. (Lug 1 has a green dot, lug 3 has a blue dot. Numbers run counterclockwise.)
- c. R_{16} (8200 ohms) and C_{19} (1500 $\mu\text{fd.}$) from pin 6 of V_5 (6AU6).
- d. R_{18} (2200 ohms) from the "B—" point on the terminal strip to lug 4 of T_6 .
2. Reconnect the following components:
 - a. Remove pigtail of R_{21} (68,000 ohms) going to pin 5 of 6S8, and connect to lug 5 of T_6 .
 - b. Remove lead from pin 3 of 6S8, and connect to pin 5.
 - c. Add a jumper wire from lug 4 of T_6 to pin 6 of the 6AU6.
 3. Add the following components:
 - a. A 33,000-ohm, $\frac{1}{2}$ -watt resistor in parallel with a 4- $\mu\text{fd.}$, 50-volt electrolytic condenser, from pin 3 of the 6S8 to "B neutral" on the nearby terminal board (second lug from tuner), with the negative side of electrolytic to pin 3 of 6S8.
 - b. Add a .001- $\mu\text{fd.}$, 400-volt condenser from pin 6 of the 6S8 to "B neutral."

The accompanying diagram above shows the new circuit.

4. Align the sound circuits as follows:

- Place a d.c. v.t.v.m. (negative scale) across the 4- μ fd. electrolytic, ground terminal to "B neutral" (plus side of electrolytic).
- Tune in a good television station.
- Adjust L_6 and primary of T_6 for maximum meter deflection.
- Remove meter and adjust secondary of T_6 for maximum sound with minimum buzz. (The secondary of T_6 is on top for Part No. 708018; on bottom for Part No. 708017.)

CHASSIS 120124

Interference on AM radio sets in vicinity.
Construct a filter as follows: Connect a .05- μ fd., 400-volt condenser in parallel with a 100,000-ohm, 1-watt resistor from the line switch side of the a.c. input plug to ground.
Unstable sync due to internal radiation.
To eliminate the effect of internal radiation on synchronization circuits of the receiver, do the following:

- Add a 1500- μ fd. condenser from the "B+" side of fuse, F_1 , to chassis. (Keep the leads about $\frac{1}{4}$ " long.)
- Add a metal shield 4" long, 2" wide, along the side of the i.f. dummy lug strip.
- Change condenser, C_{73} , from 50 μ fd. (mica) to 42 μ fd. (ceramic, 2000 volts).
- Change condenser C_{51} (18- μ fd., 6000-volt mica) between the plate of the 6BG6 tube and chassis, to an 18- μ fd., 6000-volt ceramic unit.

CHASSIS 120127B & 120128B

Neck shadows.
If a shadow on the right-hand side of the picture tube persists after the beam bender focus coil and the deflection yoke have been properly adjusted, do the following:

- Reverse the electrical connections to the focus coil.
- Magnetize the molded iron core in the deflection yoke as follows:
 - Remove V_{15} (6BG6), V_{17} (1B3), and V_{16} (6W4) from their sockets.
 - Remove the white lead from the horizontal deflection yoke at the width coil (junction of L_{11} and R_{21} , 750-ohm resistor), and connect to a "B+" 230-volt point (red lead on electrolytic condenser).
 - Connect the negative terminal of a spare 40- μ fd., 450-volt electrolytic condenser to the chassis.
 - With the set operating momentarily, touch the posi-

COAXIAL CABLES:

RG-8/U (SPECIAL) 51.5 ohms. Same size RG-8/U. Prices: 1 to 100 ft. @ 50¢ per ft.—100 to 500 ft. @ 7½¢ per ft.—500 ft. and over @ 7¢ per ft. **\$15.00**
RG-34/U—71 ohms, 145 ft. length..... **\$15.00**

RECEIVER AND TRANSMITTER

RECEIVER BC-229 or 429—TRF Receiver with 3 Plug-in Coils to cover Freq. Range 201 to 398, 2500—4700, 4150—7700 KC. With 6 Tubes: 1/37—1/38—3/39. Power Supply required, 6 or 12 Volt & 250 Volts. Size: 16"x8"x7". Schematic included.....USED: **\$8.95**

TRANSMITTER BC-230—Voice modulated Trans. with 5 Plug-in Coils to cover Freq. Range 2500 to 7700 KC. With 4 Tubes: 2/10y—2/45 & RF Meter 0-1.5 Amps. Power Supply required, 6 or 12 Volt & 350 Volts. Size: 13"x8"x7". Schematic included.....USED: **\$8.95**

SPECIAL BUY—BOTH RECEIVER AND TRANSMITTER.....**\$75.00**

BLOWERS—115 VAC 60 CYCLE

SINGLE TYPE: (Illustrated at left) 100 CFM. 2¼" intake; 2" outlet. Complete size: 5" x 6". Order No. IC939.....**\$8.95**

DUAL TYPE: 100 CFM. 4" intake; 2" Dis. Each Side. Complete Size: 8" x 6". Order No. IC880.....**\$13.95**

COMPACT TYPE: 108 CFM. Motor built inside squirrel cage. 4½" intake; 3¾" x 3" Dis. Complete size: 4¼" W x 8¾" H x 8½" D. Order No. 2C067.....**\$14.50**

FLANGE TYPE: 140 CFM. 3½" intake; 2½" Dis. Complete size: 7½" W x 7¼" H x 6¾" D. Order No. IC807.....**\$13.95**

FLANGE TWIN: 275 CFM. 4½" intake; 3¼" x 3" Dis. Complete size: 11¾" W x 8¾" H x 8-1/16" D. Order No. 2C069.....**\$21.95**

DYNAMOTORS

DYNAMOTOR and BLOWER: 9 Volts DC input; output 450 Volts 60 MA. 4500 RPM. At 6 Volts DC input; output 260 Volts 65 MA. 3000 RPM. **\$4.95**

INPUT:	OUTPUT:	STOCK No.:	PRICE:
14 V.D.C.	330 V. 135 MA.	DM-330	\$7.95
12 V.D.C.	250 V. 50 MA.	DM-25	8.95
12 or 24 V.D.C.	500 V. 50 MA.	USA/0515	4.95

Address Dept. RN • Minimum Order \$5.00 • Prices F.O.B., Lima, O. • 25% Deposit on C.O.D. Orders

FAIR RADIO SALES 132 SOUTH MAIN ST. LIMA, OHIO

PE-103 DYNAMOTOR

6 or 12 Volt input; output 500 Volts 160 MA. Complete with battery cables, circuit breakers, and filter base. Prices: NEW: \$39.95 USED: \$29.95 OUTPUT CABLE 1/PE-103—8 ft. CD-501.....\$2.95

PE-101C DYNAMOTOR

6 or 12 Volt



(Reprints of original CQ conversion articles—Oct. and Dec., 1952 issues, furnished.)

This is the Dynamotor the Hams have been talking about! Easily adapted to supply 625 V. @ 150 MA. and 325 V. 125 MA. at 12 Volts—or 300 V. 90 MA. and 160 V. 110 MA. at 6 Volts. (Illustration shows modified.) NEW: **\$19.95**

BATTERY SWITCHING UNIT and METER

Used to switch load from one battery to another—or 6 to 12 Volts. Contains Weston 2" Meter —0-15 Volt DC Scale for reading battery voltage. 20 Amp DPDT Switch and Indicator. Case size: 4" x 6¼" x 2¾".....NEW: **\$2.95**

ANTENNA EQUIPMENT

MAST BASES—INSULATED:

MP-132 BASE—Illustrated at left—1" heavy coil spring, 2" insulator. Overall length: 11½" Weight: 2¾ lbs. Price.....**\$3.95**

MP-S-33 BASE—Insulated type with heavy coil spring and 5" dia. insulator. Requires 2" hole for mounting. Weight: 9 lbs.**\$5.95**

MAST SECTIONS FOR ABOVE BASES

Tubular steel, copper coated, painted, in 3 ft. sections, screw-in type. MS-53 can be taper. Any section.....50¢ Each Larger Diameter Section: MS-54.....**\$1.25**

TRANSFORMERS—110 V. 60 CYCLE PRIMARIES: 5 Volt CT-25A—10,000 V. Ins. OPEN FRAME—6" x 5" x 4½".....**\$7.95**
6.3 V. 1 Amp.....1.25 24 V. 1 Amp.....1.95
24 V. ½ Amp.....1.50 24 V. 6.5 Amp.....5.95
6-24—or 30 Volt 8 Amp.....5.95



Nationally Famous T.V. SETS

17" Table \$122⁶⁸ Pl. \$12.27 Fed. Excise Tax	Check these luxury features: Ultra sensitivity, dynamic range control, UHF adaptability, Duo power supply, Acoustic-clear Sound system... all in a beautiful Mahogany finish cabinet.	20" Console \$149⁹⁵ Pl. \$15.00 Fed. Excise Tax
20" Table \$134⁵⁰ Pl. \$13.45 Fed. Excise Tax		21" Console \$164⁹⁵ Pl. \$16.50 Fed. Excise Tax

ALSO AVAILABLE TV CHASSIS
All sets have full 1-yr. factory picture tube warranty, and standard 90-day RTMA parts warranty. Mail and Phone Orders Filled. \$25 deposit, balance C.O.D., Shipping Charges Additional.

STEPHEN SALES CORP.
45 Crosby St., N.Y. 12, N.Y. Phone: WO4-8233
Dealer Inquiries Invited

TELEPHONE EQUIPMENT & PARTS

New TS9 handsets for EER telephone.....	Each	\$7.00
Reconditioned & tested TS9 handsets.....	Each	4.95
New WECO F1W handsets less cord.....	Each	6.50
Reconditioned F1W handsets with 3 cond. cord.....	Each	4.95
EES field telephones reconditioned & tested. Ea.		19.50
New ATR Inverter-Input 110V.D.C.—O.P.115V. A.C.....	Each	40.00
New Raytheon Rectifiers. Input 115V.A.C.—Output 24V.D.C.—1.0 Amp.....	Each	50.00
New PL68 plugs.....	Each	1.00
New PL58 plugs.....	Each	.50
New PL-7104 plugs.....	Each	.75
New PL47 plugs with 4¼ foot cord.....	Each	.75
New CD 494 cords less plugs for TS13-15-11 handsets.....	Each	1.50
New WECO B3A telephone ringers.....	Each	2.50
20-line WECO jack strips.....	Each	7.00
10-line lamp jacks.....	Each	4.00
New R.C.A. 90 Watt Amplifiers 50-60 cycles 115V.A.C.....	Each	50.00
Upright desk telephones for Extensions, Intertons, etc.....	Each	1.40
NEW WECO P1 & H41 elements for handset. Ea.		1.25
New CC-333-3 cond. cords.....	Each	.40
New WECO T30Q throat mikes.....	Each	.90
EE2 units less cord for BD72 switchboards, complete.....	Each	1.00
New RM29A remote control units w/bag, export packed.....	Each	16.00
EES Army field telephone PARTS.....	Each	35.00
New EE65G wire chief test sets.....	Each	2.00
Sound power receiver & transmitter units. Each		5.00
Lineman's pole safety belts.....	Each	2.50
Diats WECO 4H.....	Each	1.75
Diats Conn. Tel.....	Each	5.00
Batteries Burgess, BA 70 Taps—4 & ½ V.—60V.—90V.....	Each	3.00
Batteries BA 40-Taps 1.5V. & 90V.....	Each	3.00
Batteries BA 205U—Tap—30V.....	Each	3.00
Batteries BA 39—Taps—7.5V. & 150V.....	Each	2.00
Batteries BA 206U—Taps—9V.....	Each	2.00
New RAK-7 Filter reactors, D.C. res. 210 ohms.....	Each	5.00


TERMS: Check with order F.O.B. Brooklyn, N. Y.
EASTERN TELEPHONE CO.
323 Vanderbilt Avenue Brooklyn 5, N. Y.

HARVEY

WHERE YOU
FIND the FINEST



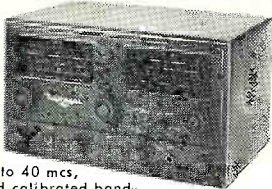Presenting
The NEW
NATIONAL
NC-88
Receiver



Covers 540 kcs to 40 mcs, with illuminated calibrated band-spread scales for 80, 40, 20, and 10 meter bands. Has tuned RF stage, two IF stages, and two high fidelity audio stages, with phono input and tone control provided with built-in speaker, antenna trimmer, separate high frequency oscillator, gain control, noise limiter, AVC, headphone jack, and send-receiver switch.

Complete with tubes \$11995

GONSET "COMMUNICATOR"

A complete two-way station for 2 meter band operation. Suitable for mobile or fixed location use. Receiver is a sensitive superheterodyne with built-in noise clipper circuit and 6BQ7 Cascode rf stage. Transmitter uses 2E26 in final 15 watts input. Employs 8 mc. crystals for stability, and has a range of over 100 miles. Operates on either 110 volts AC or 6 volts DC. Weight approx. 16 pounds.



Complete with Tubes (less crystal and microphone) \$19950
Also available for commercial or airport Unicom applications. With crystal \$299.50

THE ORIGINAL WILLIAMSON HR-15 AMPLIFIER KIT



The famous, original Williamson HR-15... still acclaimed the leader... in kit form, with the original Partridge output Transformer. Assemble this kit, and in 3 hours or less, enjoy the finest sound you ever heard. Operates from a tuner, phono-preamp, crystal pick-up, or other signal source. Absolute gain is 70.8 db with 20 db of feedback. Frequency response: ± 5 db, from 10 to 100,000 cps. Output impedances to match all speakers from 1.7 to 109 ohms. Kit is complete with 5 tubes (1-5V4, 2-6SN7, and 2-5881 (or 807 if requested), 2-Punched Chassis, 2-Resistor Mounting Strips, Sockets, Partridge WWFB Output Transformer, Assembly Instructions, and All Other Necessary Parts for Amplifier and Power Supply. \$76.50

HR-15 as above, but with Partridge CFB Output Transformers (hermetically sealed). \$90.00

PARTRIDGE OUTPUT TRANSFORMERS available separately. WWFB \$26.00 CFB \$40.00

NOTE: HR-15 Kits may be had with British KT-66 Output tubes for \$3.00 additional.

Generous Trade-in Allowance
Made for All Equipment

Visit the Harvey AUDIotorium
See, hear, and compare sound equipment from the largest selection available anywhere.

NOTE: Prices Net, F.O.B., N.Y.C.
Subject to change without notice.



Harvey
RADIO COMPANY, INC.

103-W. 43rd St., N.Y. 36, N.Y. • JU 2-1500


tive side of this electrolytic to pin 3 of the V_{10} (6W4, damper tube) socket.

- e. Remove the 40- μ fd. electrolytic making sure to first discharge the positive terminal to the chassis to avoid a shock.
- f. Replace tubes and reconnect yoke.

Black vertical line at left of picture.

This is generally caused by Barkhausen oscillations. After normal means (adjusting the horizontal drive condenser or changing the 6BG6) to eliminate this interference have been tried, and if the oscillation persists, do the following:

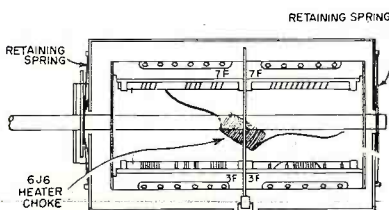Break the cement which glues the 6J6 heater choke to the underside of the tuner chassis, and press this choke away from the chassis (toward turret). See the



accompanying diagram. This can be accomplished by removing both sets of coils for Channels 4, 5, 6, 11, 12, and 13, and then gently prying the choke loose with a screwdriver. Be careful not to damage or change the shape of the coil.

CHASSIS 120142B, 120143B

Horizontal foldover.

This condition is characterized by white hash within the left quarter of the picture which varies with the setting of the horizontal hold control.

To cure this, do the following:

1. Replace resistor R_{13} (220,000 ohms) connected through condenser C_{52} (82 μ fd.) to pin 1 of V_{15} (6SN7 horizontal control tube) with two 100,000-ohm, $\frac{1}{2}$ -watt resistors in series.
2. Connect a 25 μ fd. ceramic condenser from the junction of the two 100,000-ohm resistors to chassis ground.

Raster comes on after sound (more than one minute later).

This usually is the result of a slow-starting horizontal oscillator, and may be cured by the following:

1. Check the 6AX5 low-voltage rectifier tubes (V_{19} and V_{20}). These may have low emission causing a low "B+" voltage.
2. Change the 6BQ6 horizontal output tube (V_{16}). It may be necessary to try a few tubes since some of these may have slow heaters.
3. Check C_{60} , the 10 μ fd. "B+" boost filter condenser, and replace if leaky.
4. Check all solder connections

in the 6SN7 horizontal oscillator and control circuits (V_{13} and V_{10}).

5. In low line voltage areas, change the value of R_{86} (at pin 10 of the CRT) from 22,000 ohms to 15,000 ohms.
6. Try a new horizontal phase coil L_T and oscillator transformer T_{10} . These may have shorted turns or may be opening intermittently.

CHASSIS 120166D

Vertical roll.

When this occurs with the reception of noise interference, it may be corrected by replacing the 150-ohm resistor, R_{86} (grid resistor from pin 4 of 6SN7 vertical oscillator, V_{18} , to ground) with a 100-ohm unit.

Hiss in fringe areas

To increase the signal-to-noise ratio and reduce hiss in fringe areas, change the value of C_{33} (from volume control to ground) from .001 μ fd. to .002 μ fd.

CHASSIS 120166D, 120168D, and 120169B, F, & D

Picture wiggle.

This may be caused by incorrect lead dress of the picture tube leads.


To correct this, do the following:

1. Dress the yellow lead to the cathode of the picture tube (pin 11) away from the horizontal oscillator tube (V_{13} , 6SN7) to prevent stray pickup of video information by the oscillator tube. The yellow picture tube lead can be secured to the deflection yoke support bracket.
2. Dress the white lead to the fringe compensator "on-off" switch away from the horizontal phase coil (L_{11}) and the grid of the 6SN7 horizontal oscillator tube (pin 4 of V_{13}).

CHASSIS 120168D

Popping sound in audio.

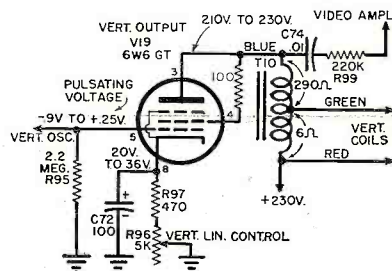When this condition occurs at the same time that the picture starts to roll vertically or when the vertical hold control is adjusted, it may be cured by installing a 100-ohm, $\frac{1}{2}$ -watt resistor between the



screen and plate of the vertical output tube (V_{19} , 6W6), as shown in the diagram.

Hiss noise in fringe areas.

To reduce the amount of hiss, add a decoupling condenser to the

SENSITROL RELAY

WESTON SENSITROL coil sensitivity only 10 microamps! Built like meter. At 10ua, needle swings over into permanent magnet which grips it to close contacts rated 1 ampere. Perfectly damped; vibration will not close contacts. Built-in reset relay unlatches contacts when 12 to 24 volts AC or DC is momentarily applied to reset leads. The Sensitrol works directly from photocells, thermocouples, or any source of minute current. No electronic amplifier needed! **\$12.95**
A \$69.50 precision device for only...

SENSITIVE POLARIZED RELAY

This is the device that the services use to replace solenoids. Now offered to the public for the first time! SP/DT, both contacts normally open. The POLARITY of an applied 1/2 VDC, 5 MA current determines which contact closes. Use for micro-positioning, remote control, model control, etc. Our free data sheet shows you just how to use it. In metal box with two 600 Ohm heavier duty relays. NEW, slightly dirty. **\$6.95**
(Shipping weight, 4 lbs.)

SUPER SENSITIVE RELAY BK-7-B

Single pole, double throw. Coil 4000 ohms. Sensitivity accurately adjustable on calibrated scale. At 5 on scale sensitivity is 1/2 milliamper (1 milliwatt, 2 volts) and from 5 to 40 on scale the sensitivity decreases linearly to 1.5 ma (9 milliwatts, 6 volts). Thousands of uses: telemetering, voice-operated or capably operated or thermocouple operated circuits, sequence circuits, etc. Fully enclosed, 1 1/2" x 3 1/2" x 1 1/4" deep. Weight, 6 oz. With hinged contact-inspection door and screwdriver adjustable stationary contacts. BRAND NEW, Only \$1.95 each for **\$17.50**
(Shipping Weight, each, 1 lb.)

A SENSITIVE RELAY!

Closes at 4 to 5 ma. (Extra set of SP/ST contacts for additional service, closed at 6.5 ma, 6000 ohms. Sensitivity easily altered by bending limit arm or changing spring. Only 1 1/2" x 2 1/4" x 1 5/8" overall; dozens of applications, and offered at a "stock up" price. Removed from clean equipment.
ONLY 98c each, 3 for \$2.75

PRECISION CALIBRATING CRYSTAL

200 KC. Same as used in late model Collins Automatic Xmitters. In FT-241-A holder (1/2" pin spacing). Use in Pierce untuned oscillator circuits to retune points very close together all the way up the spectrum. **BRAND NEW** ... **\$2.95**

12 CHANNEL T-V TUNER

Complete front end, famous make "Silver Circle." Furnished with original factory insulations, less tubes. Dozens of uses: receivers, converters, etc. The TV bargain of the year for builders, amateurs, students. These are factory perfect and offered at a "stock up" price. **ONLY \$1.95 each, 3 for \$5.00**
(Shipping Weight, each, 3 lbs.)

OIL FILLED FILTER CONDENSERS

(All famous makes)

10 mfd, 600 vdc, 3" x 1 1/2" x 5 3/8" O.A. ht. **BRAND NEW \$2.25**
6-6 mfd, 600 vdc, 2 1/2" x 2 1/2" x 1 1/4" high, bolt mounting, lugs under. **BRAND NEW 2.25**
8-8 mfd, 600 vdc, 2 1/2" x 2 1/2" x 1 1/4" high, bolt mounting, lugs under. **BRAND NEW 2.95**
2" PM SPEAKERS, heavy magnets. **BRAND NEW \$1.25**

12 VOLT RECEIVER DYNAMOTORS. Deliver 250 vdc, 60 ma. Shipping weight, 1 lb. **EXCELLENT USED \$7.95**

274N PLUG. 7-prong male plug to fit back of command revars. and xmtrs. This is the same plug as used in the racks. **NEW, each 21c; five for \$1.00**
Local Control Adapter Parts for 274N or ARC-crvr. Exact part, switch, knobs, etched plate, and instruction data. Ready to mount. **ONLY \$1.29**

MOBILE VHF ANTENNA KIT

Famous make, designed for two-way police and taxi operation. Complete with chrome plated detachable rod, base fitting, 10' coax, dope sheet. **BRAND NEW, Only 98c**
(Shipping weight, 2 lbs.)

PE-101-C DYNAMOTOR. Brand new. **\$4.95**
(Shipping weight, 13 lbs.)

OUTPUT TRANSFORMER. 5000 ohms input to TWO outputs, 800 ohms or 3.5 ohm output for 12A6, 6V6, etc., or to match speaker or headset. **NEW, potted, shielded. .79c**

ANTENNA MAST SECTIONS, MS-49, 50, 51, 52, **39c**
NEW, original packing. ... Each

CRYSTAL MICROPHONE GIVEAWAY!

Sensitive hearing aid capsule sealed in neat, compact, flat container with tinned terminals. Crisp, clear, high-level output. Ideal for lapels, ties, tuck-aways. Individually tested and guaranteed. **ONLY 98c**

CERAMIC COIL FORM ASSORTMENT

Contains 12 BRAND NEW ceramic coil forms, 98c various diameters and spacings. **ONLY 98c**
(Shipping wt.—10 lbs.)

BROADCAST BAND & AERO

MN-26-C Remote Controlled navigational direction finder and communications receiver. Manual DF in any one of three freq. bands, 150 to 1500 KC. 24 V. Self-contained dynamotor supply. Complete installation, including receiver, control box, loop, azimuth control, Left-Right indicator, plugs, loop transmission line, and flex. shafts. **\$69.50**
BRAND NEW, ORIG. PACK.
(Shipping Wt. 75 lbs. Express Collect.)

HI-FI HEADSET

Uses annular grooved plastic fibre cones with voice coils as in speakers, and padded diaphragm ear muffs to obtain spacing for correct acoustic load. Gives finest music reproduction, flat far beyond upper and lower limits of auditory perception. Pat. in series has measured response of 600 cycles to 10,000 cycles, obtained with built-in high quality transformers. Checked out with freshly latined ear pads. **\$7.95**
(Shipping weight, 3 lbs.)

6 V VIBRATOR KIT. Vibrator plus non-syne transformer, two outputs: 750 VGT, 145 ma for plates; 15 V for bias. Can deliver 320 V at 130 ma. (Shipping wt. 6 lbs.) **NEW \$2.89**

EASY MONEY!

We're still buying surplus gear. Tell us what you've got, its condition, and your price. If we like it you'll get our check quick.

G. L. ELECTRONICS


905 S. Vermont Ave., Los Angeles 6, Calif.
All Prices F.O.B. Los Angeles Calif. Buyers Add Sales Tax
GET ON OUR MAILING LIST

plate circuit of the 1st audio amplifier. This condenser should be .001 μ fd., and should be connected from pin 7 of V_5 (6AV6) to chassis.

Black horizontal streaks when tuned to Channel 6.

This condition is usually only apparent in fringe areas, and is caused by harmonics of the picture i.f. generated in the video detector coupling to the front end, causing regeneration of certain frequencies. In many cases it may be tuned out with fine tuning, and can sometimes affect Channels 5 or 7.

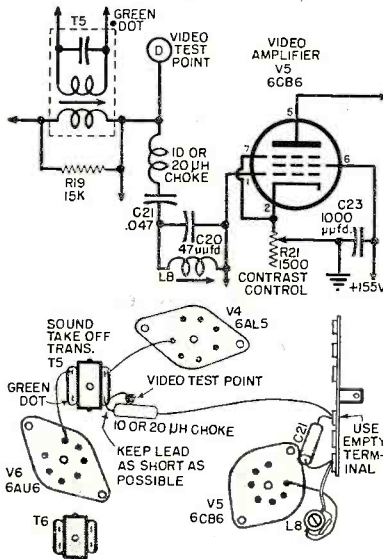These streaks may be eliminated by connecting a 10- or 20- μ hy. r.f. choke in series with the .047 μ fd. condenser (C_{21}) connected to the grid of the 6CB6 video amplifier tube (V_5). This choke should



be connected and dressed as shown in the diagram.

In some chassis, the 4.5-mc. trap (C_{20} - L_5) has been eliminated. This serves to improve the sound in fringe areas.

CHASSIS 120168D, AND CHASSIS 120169B, F, & D

Repeated fuse failure.

This can be caused by momentary arcs in tubes or components which occur intermittently and soon heal themselves.

To cure such fuse failure, replace the burnt-out fuse with a 6-amp. slow-blowing type.

CHASSIS 120169B & F

Yoke ringing.

This condition is characterized by a rippling of the horizontal raster lines at the left third of the picture.

To cure this effect, check condenser C_{62} which is across part of the horizontal deflection yoke coil. If this condenser is bad, it should be replaced with a new 2000-volt unit between 38 μ fd. and 62 μ fd. (Try values between these limits for the best ringing elimination.)

For sound trucks • parades
carnivals • resorts • busses
outdoor meetings

ECONOMICAL MOBILE AMPLIFIERS

by
Newcomb





Newcomb mobile amplifiers are carefully built for the rugged conditions of mobile use and to deliver consistently the top quality performance you expect from any Newcomb amplifier. Dollar for dollar they give you more good service, more convenient operational features and more all around, long-time satisfaction.

MODEL E-25MP delivers 25 watts from either 6 volt battery or 117 A.C. It has a standby switch, separate power and phono switches and inputs for 2 mikes and 1 phono. Heavy duty plugs. 2000 volt hermetically sealed buffer condenser. Phase correction capacitor for phono motor.

MODEL E-25M is the same amplifier without phono top.


MODEL E-10M is a rugged, low cost, 10 watt unit also for either battery or A.C. power. Has standby switch, inputs for 1 mike, 1 phono. Special mounting simplifies installation and removal.

Send for full
information
today!

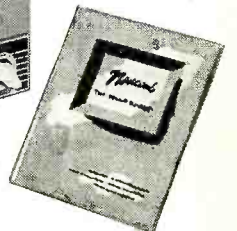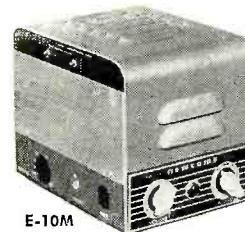

NEWCOMB AUDIO PRODUCTS CO.

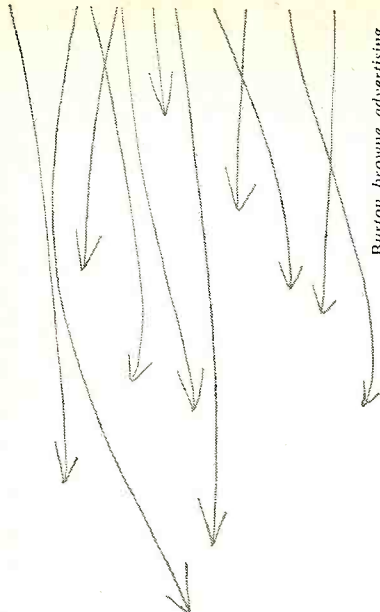Dent. F, 6824 Lexington Ave., Hollywood 38, Calif.



Film for TV
(Continued from page 37)

with a white light of equal intensity, the latter gives off a highly actinic blue radiation. Photographically speaking, this fits the bill since it cuts down on the all important film exposure time.

Early TV film recording utilized a shutter that opened 170°, resulting in an exposure time of about 1/30th second. By accurately synchronizing the camera motor it was then possible to make the shutter open and close during vertical blanking. With this experimental device, kinescopes were recorded at a 15 frame-per-second rate.

Currently in use, a 16 mm TV recording camera is phased to the system's synchronizing generator. Its shutter, driven by a 60-cycle synchronous motor through a set of precision gears, has a closing angle of 72°. At a 24 cps rate this is equal to a single TV frame. Thus, two and one-half fields occupy one-twenty-fourth of a second which is the equivalent of one frame of 16 mm film.

Since the top portion of field 3 is unexposed during the film pull-down period, it is made up later by exposing the upper portion of field 5, before the shutter again commences its action. Two fields are therefore fully exposed since the continuity of action is at such a rapid rate.

Accurate synchronization must exist at all times. Any change, however slight, in the speed of the shutter inevitably results in banding. TV recording engineers call this "shutter bar." This may sometimes occupy a space of some ten or twelve horizontal lines running through the center portion of the picture. They may be overexposed or underexposed and exist as an unpleasant pulsating optical phenomenon.

In order to insure an extremely high degree of shutter accuracy, to-

day's drives are designed with the care and precision of a Swiss watch. The all-electronic shutter is, however, slowly gaining prominence in certain installations. The adjustments required with mechanical shutters present no problem in this system since no shutter is used.

Due primarily to economic considerations, the great majority of kinescope recordings will undoubtedly continue to be made on 16 mm film. Furthermore, fire regulations covering the use of 35 mm film are most rigorous. Consequently 16 mm technique in both kinescoping and film projection is undergoing vast improvement.

As to the future development of films and television, several noteworthy investigations are taking place simultaneously in Hollywood and Great Britain. Technically very little is known at this time regarding the video tape recording process of the Hollywood Crosby laboratories. Presumably pictures have already been produced from a rapidly moving spool of special tape!

Engineers in England are well on the way towards perfecting a method that eventually will replace existing movie making techniques. In the filming of a movie, no one but the camera operator can have a true picture of what is actually taking place on the stage. His eyes see what the film sees. Consequently two, three, or even four different shots may be taken of the same scene. It remains for the director to integrate these.

After processing hundreds of these, assembled clips are projected on a screen in the screening room. Within these confines the director selects, chooses, and rejects. This rather crude, though accurate, presentation is rather costly. Now if the director had an instantaneous prevue of several camera shots on location, similar to those on TV broadcast monitors, his problems would be simplified.

Let us have a "preview" of what might occur.

Once a director's decision is made

Bob Henry
to all radio hams and hobbyists—
Over!

Yes—you're at the controls when you do business with Bob Henry! As one radio fan to another, Bob knows what equipment and services you want—and he's made both his stores to-the-order of the radio ham or hobbyist. Dealing with Bob, you get 90 days FREE service—really liberal trade-ins—and a payment plan that just can't be matched! Write, wire, phone or visit either store today. Find out all the "extras" you get with Bob Henry—the world's largest distributor of short wave receivers.

Bob Henry has

a complete line of new Hallicrafter receivers and transmitters.





MODEL SX-71... Double superheterodyne circuit plus built-in Narrow Band FM reception. Temperature compensated, voltage regulated. 5 position band selector for 538-1650 Kc, 1600-4800 Kc, 4.6-13.5 Kc, 12.5-35 Mc, 46-56 Mc. 11 tubes plus voltage regulator and rectifier, \$224.50.

Also available — Hallicrafters Model HT-20, \$449.50 • Model S-76, \$179.50 • Model SX-62, \$299.50 • And all other models.

HENRY RADIO STORES
LARGEST DISTRIBUTORS OF SHORT WAVE RECEIVERS
LOS ANGELES OFFICE: 11240 Olympic Blvd.,
Los Angeles 64. BRadshaw 2-2917
BUTLER OFFICE: Butler 1, Missouri. Phone: 395

Fig. 12. 16 mm film conversion using 2 to 3 intermittent. See text for explanation.

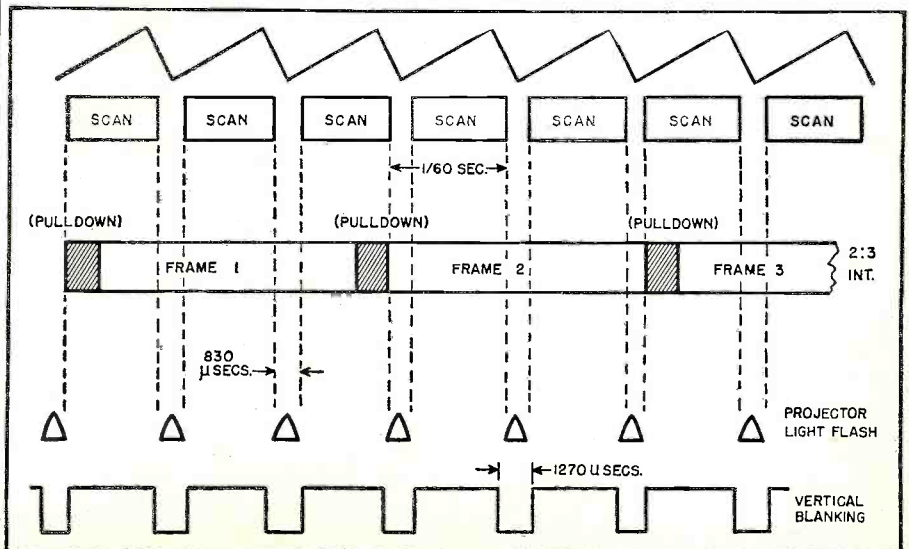

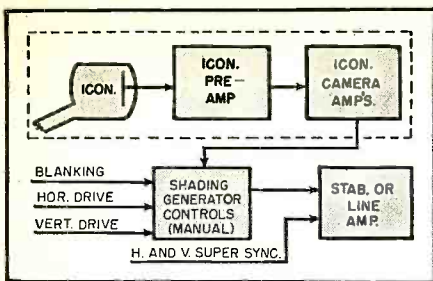

A television film camera control chain.

as to a particular shot it is communicated verbally to the technical supervisor, "Take Four." Camera #4 is punched up on the intricate dissolve-switching console and its picture travels over a closed circuit to the recording (kinescope) studio. Here it is recorded on fine grain high quality 35 mm stock.

Special effects such as "wipes," "dissolves" and superimpositions present no problem. Modern TV techniques make use of the latter two, hundreds of times throughout a single evening of transmission. As a matter of fact, London bridge was once "moved" into a rather small TV studio via the method of rear screen projection!

Probably the last technical hurdle lies in overcoming the limiting resolution of present-day camera tubes and recording kinescopes. In the writer's opinion an idealized experimental approach would be a closed circuit system capable of passing an over-all bandwidth of some 960 lines (12 mc.). Intermediate video amplifiers are today commercially available with up to ten, twelve, and even fifteen megacycle response.

In view of the fact that most of the film transmission problems have been solved with ingenuity, it is only a matter of time until all the "bugs" have been eliminated.

It seems hardly fair to the already staggering movie industry that television has been elected to deal the final death blow. The film capital's latest comeback is the three dimensional (3D) medium. TV's answer may well be as follows: "Not only are we today experimenting with three dimensional color television, but we propose to have our pictures broadcast on an international scale." Truly it has been said, "In anticipation of tomorrow's miracles lies the inspiration of today's engineer!"

BIBLIOGRAPHY

- Fink, Donald G.: "Principles of Television Engineering," McGraw-Hill Book Co.
- Spottiswoode, Raymond: "Film and its Techniques," University of California Press.
- Fraser, Robert M.: "Motion Picture Photography of Television Images," NBC Department of Engineering.
- "The Use of Motion Picture Films in Television," Eastman Kodak Co., Motion Picture Film Dept.
- "Films in Television," Society of Motion Picture & Television Engineers.
- Collins, Norman and Macnamara, T.V.: "High Definition Films," British Kinematography, August 1952.
- Kozanowski, H.N.: "Improved TV Picture Performance," Broadcast News, Jan.-Feb. 1952.

PERFORMANCE

Guaranteed

TO LAST A LIFETIME!

UNIVERSITY COBREFLEX-2 WIDE-ANGLE TRUMPET



Lifetime Performance has been built into each Cobreflex-2. Nothing yet produced compares in construction and design efficiency. Once installed, the Cobreflex-2 can be forgotten. The Cobreflex-2 is Breakdown-Proof... truly performance guaranteed to last a lifetime.

Compared! Tested! Proven Superior!

Write for technical literature



When used with University Driver Units—
Frequency Response
Power Capacity
Meets Any Impedance Requirement
Mounting Application

Model T-30 Driver Unit Cont. Power: 20 Watts over 250 CPS Response: 250-15,000 CPS Impedance: 8 Ohms	Model SA-HF Driver Unit Cont. Power: 25 Watts Response: 90-10,000 CPS Impedance: 16 Ohms	Model MA-25 Driver Unit Cont. Power: 25 Watts Response: 90-6000 CPS Impedance: 16 Ohms	Model PA-30 Driver Unit Cont. Power: 30 Watts Response: 80-10,000 CPS Impedance: 16/165/250/500 1000/2000 ohms Power Taps (70%): 30/20/10/5/2 1/2 Watts	Model SA-30 Driver Unit Cont. Power: 30 Watts Response: 90-10,000 CPS Impedance: 16/45/165/250 500/1000/2000 ohms Power Taps (70%): 30/20/10/5/2 1/2 Watts

UNIVERSITY LOUDSPEAKERS • INC. 80 SOUTH KENSICO AVENUE, WHITE PLAINS, N. Y.

Editors and Engineers PUBLICATIONS

ANTENNA MANUAL

OVER 300 PAGES OF PRACTICAL INFORMATION FOR EVERY RADIO MAN

One of the most comprehensive practical antenna books ever published. Gives the "why" and "how" of radio-wave propagation in the HF, VHF and UHF ranges, plus a comprehensive coverage of antennas and transmission lines for all frequency ranges.



\$3.50*
per copy
(clothbound)

Book No. E&E-AM1

RADIOTELEPHONE LICENSE MANUAL. Typical study questions with concise answers for any commercial U.S.A. radiotelephone operators license. Book No. E&E-RL1.....\$3.75*

BETTER TV RECEPTION (in fringe and low-signal areas). NEW SECOND EDITION. The standard guide for installation technicians. A popular text for TV enthusiasts. Book No. E&E-TR2.....\$2.50*

RADIO HANDBOOK. GIANT 13TH EDITION. A one-volume library of radio information with extensive, simplified theory. Detailed how-to-build-it data on dozens of items of practical radio equipment. Book No. E&E-RH13...\$6.00*

SURPLUS RADIO CONVERSION MANUAL. VOL. 1. Practical conversions. Write for list of contents. Book No. E&E-SM1.....\$2.50*

SURPLUS RADIO CONVERSION MANUAL. VOL. 2. Companion to Volume 1. Book No. E&E-SM2.....\$2.50*

*Plus any tax.

BUY FROM YOUR DISTRIBUTOR
ADD 10% ON DIRECT MAIL ORDERS TO
EDITORS and ENGINEERS, LTD.
BOX 689A SANTA BARBARA, CALIF.
Bookstores order from BAKER & TAYLOR, Hillside, N. J.

Windsor TUBES

TESTED and GUARANTEED for PEAK PERFORMANCE

TO MERIT your confidence—to insure your satisfaction—every tube we ship has been tested in a radio or TV set for PEAK PERFORMANCE. Each tube is attractively packaged in individual carton—and, EACH WINDSOR Tube carries full RTMA GUARANTEE!

Type	Price	Type	Price	Type	Price
1B3GT	\$0.63	6BH6	\$0.57	12AT6	\$0.48
1R5	.56	6BQ6GT	.89	12AT7	.68
1S5	.47	6BQ7	.84	12AU7	.53
1T4	.56	6C4	.37	12AV7	.79
1U4	.55	6CB6	.53	12AX7	.61
1U5	.46	6CD6G	1.85	12BA6	.45
1X2A	.67	6J5GT	.40	12BE6	.47
3V4	.56	6J6	.62	12BH7	.63
5R4GY	.91	6K6GT	.41	12SA7GT	.52
5U4G	.40	6S4	.46	12SK7GT	.50
6AB4	.46	6SH7GT	.47	12SQ7GT	.42
6AG5	.54	6SK7GT	.50	25BQ6GT	.89
6AK5	.95	6SL7GT	.62	25L6GT	.48
6AL5	.40	6SN7GT	.54	35B5	.48
6AQ5	.46	6SQ7GT	.42	35C5	.48
6AU6	.43	6T8	.77	35Z5GT	.30
6BA6	.45	6V6GT	.46	50B5	.47
6BC5	.53	6W4GT	.45	50C5	.47
6BE6	.46	6W6GT	.57	50L6GT	.47
6BG6G	1.34	6X4	.34	117Z3GT	.39
		6X5GT	.33		

WRITE FOR ADDITIONAL TUBE TYPES AND PRICES. We also stock Special Purpose and Transmitting Tubes at similar savings! 25% Deposit with Order. All merchandise F.O.B., N.Y.C. For orders less than \$10, add \$1 handling cost. Deduct 2% if full remittance accompanies order. All merchandise subject to prior sale and price change without notice. Dept. N-8.

Windsor ELECTRONIC TUBE CO.
1515-N SHEEPSHEAD BAY ROAD, BROOKLYN 35, N. Y.

Choosing a Probe

(Continued from page 42)

that the time constant of its output is short enough to pass audio frequencies.

The demodulator probe is primarily intended for observation of sweep curves and audio waveforms. In responding to the modulation envelope of an r.f. carrier, this probe is capable of accurately following the complex waveforms conveyed by modulation. The demodulated output of the probe can be measured as an a.c. voltage on a "VoltOhmyst" or it can be observed as an audio waveform on an oscilloscope. The output range of the WG-291 is flat from d.c. to 5000 cycles and, therefore, includes both the high-frequency and low-frequency components of a 60-cycle square wave, making this particular probe especially good for the observation of sweep curve response.

The input frequency response of this probe is flat from 500 kc. to 250 mc., enabling it to demodulate any video, i.f., and TV channel sweep frequencies or audio amplitude-modulated carriers within that range.

Because of its low input capacitance of 2.25 $\mu\text{fd.}$, the WG-291 demodulator probe can be used to observe video sweep curves or to observe i.f. amplifier curves at any stage. It is very handy for signal tracing and troubleshooting whenever modulated carriers are present, and it is particularly helpful in locating causes of hum modulation.

When the demodulator probe is used with an oscilloscope equipped with a d.c. blocking condenser, a demodulated waveform will appear at the normal vertical centering location. When used with an oscilloscope having a direct-coupled amplifier and direct-coupled input, the demodulated waveform is displaced in a positive direction by an amount proportional to the r.f. carrier level. When an unmodulated carrier is applied to the probe and its rectified output is applied to a d.c. scope, the trace is displaced in the positive direction by an amount equivalent to the peak value of the carrier.

The WG-291 demodulator probe is a peak-rectifying type which produces right-side-up video curves on any oscilloscope which is correctly polarized for upward deflection from a positive voltage.

Multiplying Probes

Safety is the prime consideration in the design of the RCA WG-289 high-voltage probe. The probe itself is a housing for a high-resistance multiplier and is shaped to minimize leakage and corona.

A 1090-megohm multiplier in a WG-289 high-voltage probe used in conjunction with a "VoltOhmyst" having 10 megohms internal resistance provides a convenient 100-to-1 voltage reduction for all d.c. ranges. The ex-

tremely high resistance causes negligible loading on TV high-voltage supplies.

If it is desired to measure 19 kilovolts with a high-voltage probe, the "VoltOhmyst" should be set on the 500-volt range to read 1.9 on the 5 scale. The meter reading is then 1.9 times 100 or 190 volts. This, in turn, is multiplied by the probe factor of 100 to indicate a total of 19,000 volts.

In a unique application of the high-voltage probe, the waveforms of 15.75 kc. television horizontal-output and high-voltage circuits can be viewed on an oscilloscope provided that the scope has a d.c. path to ground of approximately one megohm in series with the probe resistance. Signal tracing and waveform analysis in high-voltage circuits are thereby made practical. This type of probe is not recommended for exact a.c. measurement because of stray capacitance pickup. It is not advisable to shield the multiplier resistor because shielding would reduce the safety factor.

-30-

NEW DIODE FOR U.H.F. TELEVISION

CBS-Hytron has introduced a new germanium diode which has been especially designed and tested for mixer applications in the u.h.f. television spectrum from 470 to 890 megacycles.


The new Type 1N133 is housed in a glass-filled phenolic case and is especially impregnated to insure optimum performance under adverse humidity conditions.

Maximum ratings at 25° C. include a d.c. inverse voltage of 5 volts, a maximum (average) d.c. current of 50 ma.; a maximum d.c. peak current of 150 ma.; surge current (1 sec. duration) of 500 ma. Typical characteristics at 25° C. include: maximum reverse current (at -6 volt) of .3 ma.; minimum forward current (at +.5 volt) of 3 ma.; average shunt capacitance of .8 $\mu\text{fd.}$; and peak inverse voltage of 6 volts.

The germanium diode's mixer characteristics in the u.h.f. television circuit shown include oscillator injection of 1 ma., frequency of 850 mc., average conversion gain of .5, and an average noise figure of 16 db.

-30-

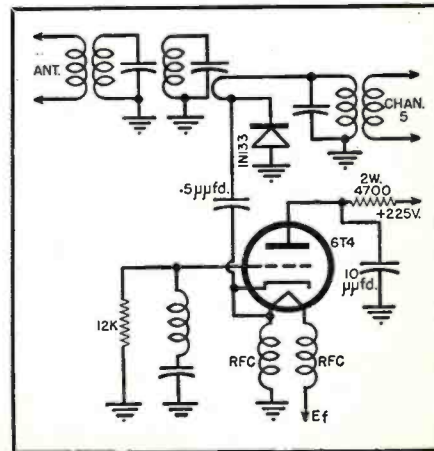The new CBS-Hytron Type 1N133 germanium diode used as a u.h.f. television mixer.



RADIO & TELEVISION NEWS




TUNG-SOL statistical quality control methods produce the industry's most reliable tubes for all uses.

Tung-Sol makes: All-Glass Sealed Beam Lamps, Miniature Lamps, Signal Flashers, Picture Tubes, Radio, TV and Special Purpose Electron Tubes.


TUNG-SOL ELECTRIC INC.
Newark 4, N. J.

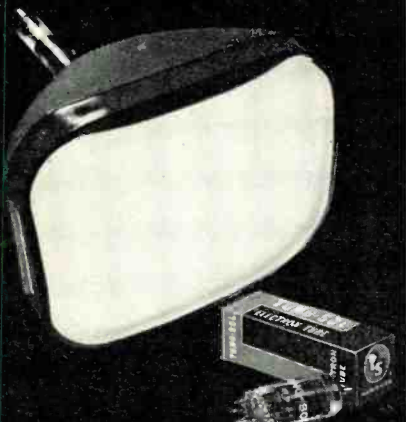Sales Offices: Atlanta, Chicago, Culver City (Los Angeles), Dallas, Denver, Detroit, Newark



TUNG-SOL
RADIO, TV TUBES, DIAL LAMPS

**Last
Chance
to buy at this price!**

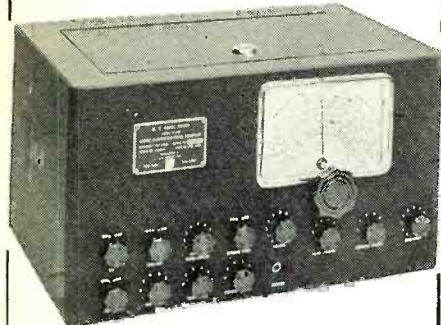

**COMMUNICATIONS
RECEIVERS**

Contains All Components

**Front Panel
Controls**

- Tuning
- R.F. Gain
- Audio Gain
- BFO-AVC Switch
- BFO Pitch
- Power On-Off
- Stand-by
- Noise Limiter
- On-Off and Control
- Antenna Trimmer
- Crystal Filter
- On-Off
- Crystal Phasing
- Selectivity
- Band Change Switch
- Calibrated Dial Face

Special

\$59.50
KIT PRICE EACH

Wired and Tested

\$89.50

Features:

- 2 Watt P.P. Audio
- Amplified AVC
- Voltage Regulated
- Oscillator Supply
- Noise Limiter
- Beat Oscillator
- Air Tuned R.F. Trimmers
- 2 Stage Permeability Tuned 455 KC I.F. Plus Crystal Filter
- Phone Jack—Built-in Stand-by Relay
- Operates on 105 to 125 Volts AC or DC
- Power Source
- Frequency Range 200 KC to 400 KC and 490 KC to 19 MC in Six Bands
- 40:1 Geared Ratio Dial Drive
- 11 Tubes Plus Selenium Rectifier
- 6SG7 RF AMP.
- 6SB7Y Mixer
- 2-6SG7 I.F.
- 6H6 2nd Det & N. L.
- 6SF7 AVC AMP.
- 6SL7 BFO & 1st Audio
- 6SL7 Phase Inverter
- P.P. 25L6GT Audio
- VR-75 Voltage Regulator
- Full Vision Calibrated Dial
- Cabinet 19 1/2" long x 10 1/2" high x 12 1/2" deep
- Finished in fine grain black wrinkle
- Front panel silk screened to identify each control
- Shipping weight 45 lbs.
- Shipped Express Only

This kit is complete with every part necessary to assemble into a finished receiver, including tubes and cabinet. Chassis is punched and marked. Mount the parts, wire it, align it and you have a fine receiver of commercial appearance, that can't be beat for 3 or 4 times the price. Parts layout, schematic diagram and alignment instructions are supplied.

ORDER TODAY!

TERMS: 25% Deposit with order. Balance C.O.D. Include postage with parcel post orders. All prices F.O.B. Chicago and subject to change without notice. All merchandise subject to prior sale.

BOULEVARD ELECTRONICS, INC.
Radio and Television Supplies
808 W. Jackson Boulevard, Chicago 7, Ill.
Phone DEarborn 2-4458

Crystal Calibrator
(Continued from page 63)

band the better, as the beat note in the receiver is S-9 on the fundamental. An 80-meter crystal gives strong beats from 160 to 10 meters and is also usable on the higher bands. Decide how many crystals you want to use in this application, and with an appropriate switch, if more than one crystal is used, wire up the unit in 30 minutes. Note that the tube terminals shown in the schematic are for a 6V6.

A crystal with its fundamental frequency in any amateur band can be used for checking purposes on all of the ham bands since the circuit is rich in harmonics and subharmonics.


No r.f. connection to the receiver is necessary. Merely place the unit in a convenient location anywhere in the shack, or inside your receiver, if desired, and when you snap the switch "on," there is your checking signal.

The author usually operates near 7100 kc., and the crystal generally used is 3560 kc., giving a fine marker at 7120 kc.

Most modern crystals are accurately calibrated and reasonably drift-free in this application. Some of the surplus crystals available at bargain prices may be of a slightly different frequency from that stamped on the holder. It would be wise to check their frequencies before depending on their accuracy. If your receiver is equipped with a vernier on the h.f. oscillator (like the modern HRO series) or an adjustable dial (like the Collins), setting it on frequency is easy and accurate. With other receivers, it is easy to interpolate mentally. If the calibrator gives a 7150 kc. signal, and zero beat on the crystal shows 7145 kc. on the receiver dial, it is obvious that within the range of 100 kc. or so, your receiver calibration is 5 kc. low.

Be sure and check the calibration every 10 or 15 minutes for the first half hour warm-up, as most receivers drift and they all vary somewhat from day to day due to differences of temperature and humidity in the shack and due to "aging" of components, as previously mentioned.

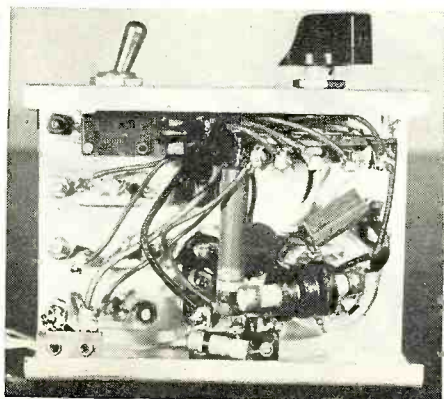Underchassis view of the junk-box calibrator shows easy wiring of the few parts.




**You can do MORE
with an RCP "DO-ALL"**

for **UHF**
and
VHF

SIGNAL GENERATOR

MARKER GENERATOR

PATTERN GENERATOR

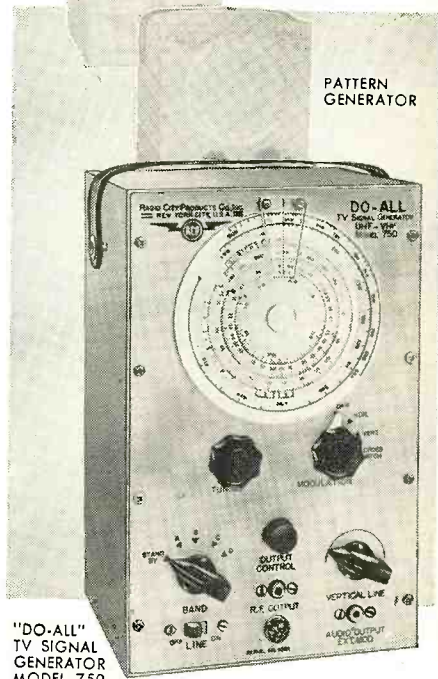

"DO-ALL"
TV SIGNAL GENERATOR
MODEL 750

ONE

**RCP "DO-ALL"
SIGNAL GENERATOR**

for all **THREE**

- SIGNAL GENERATOR
- MARKER GENERATOR
- PATTERN GENERATOR

Designed for portable or bench use, the 750 reflects the finest in construction and appearance. It is handsomely finished in an attractive brushed aluminum panel with a steel carrying case.

- Inductuner insures accuracy of within 1/2 of 1% over the entire range of 9 Mc to 900 Mc.
- All VHF frequencies are on fundamentals.
- RF's and IF's are clearly calibrated on a large etched aluminum dial.
- Steady horizontal bars, vertical bars and crosshatch pattern individually produced on all channels.

PRICE \$79.50

See Model 750 At Your Local Parts Distributor. Write For Complete Catalog RN-8.


RADIO CITY PRODUCTS CO., INC.

52 West 25th Street **RCP** New York 1, N. Y.

The **XL** series
—available

**CANNON
PLUGS**


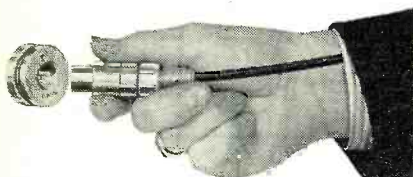
through
radio parts
distributors
and electrical
wholesalers
everywhere



Cannon's famous XL Connector Series for audio applications is available in 14 shell designs through Radio Parts Distributors and Electrical Wholesalers. These lightweight, compact connectors embody many desirable features: adaptable either to cord end or wall mounting applications...convenient latchlock coupling device...cable entry with compression gland and relief spring or integral clamp...tapped metal for insert retaining screw...provision for special grounding contact or grounding to shell. Accessories include dust caps and adapter shunts, receptacles for integral mounting on microphones and other audio components. Watch for the colorful Cannon counter display carton at your Radio Parts Distributor.

NOTE TO JOBBERS AND WHOLESALERS:

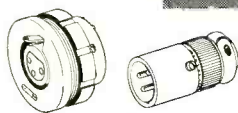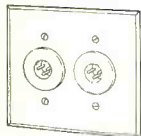Be sure the name "Cannon" is on every plug you buy...it's your customers' guarantee of satisfaction. For complete details send for Bulletin RJC-6.



XL Connectors are available in 14 shell designs shown here.

Watch for this Cannon XL counter display carton.



CANNON ELECTRIC

Since 1915



Cannon Electric Co., Los Angeles 31, Cal.
Factories in Los Angeles, Toronto, New Haven.
Representatives in principal cities. Address inquiries to Cannon Electric Co., Dept. H-145, Los Angeles 31, California.

FCC rules provide that some method external to the transmitter be provided to insure that operation is within the assigned bands. This unit is a "natural" for this job. Establishing your receiver frequency and then zero-beating the transmitter with the receiver insures operation within the law.

The unit will be found valuable for other purposes around the shack. Adding a .0001 μ fd. condenser as shown in dotted lines on the circuit diagram gives you an exciter and keeps you on the air while you rebuild your v.f.o. and you have a choice of six frequencies at the turn of a switch, if your

unit is constructed similar to the author's. If you have a crystal of the proper frequency the 455 or 453 kc. subharmonic or any other desired subharmonic can be used for alignment of the receiver i.f. By itself, the unit is a fine low-powered transmitter for emergency use, with a key in the negative high-voltage lead. Power can be supplied by batteries if necessary and the antenna may be connected at the dotted line point in the diagram. Dozens of other uses will come to mind. All in all, it will turn out to be a handy gadget around the shack. It will be well worth the time and money involved in its construction. —30—

COMPACT FILAMENT AND SHORT CHECKER

By ROBERT BAXTER

THIS checker can be built with a minimum of time and expense and will test filament continuity on all types of 7-pin miniature, 9-pin miniature, octal, and loctal tubes.

Shorts may be checked between any two elements of any of the above-mentioned tube types.


Two pin jacks have been provided for test leads which may be used to check continuity externally. When using test leads, a condenser, C_1 , is used to prevent direct contact between the a.c. line and the user's body.

All socket pins of the same number are wired together. These pins are then wired to the corresponding number on both selector switches. This combination makes it possible to select any two elements for checking.

Modifications may be made which will effect some economy including the use of wafer-type tube sockets, a less expensive



pilot light socket, etc. A small wood cabinet could be used in lieu of the metal unit.

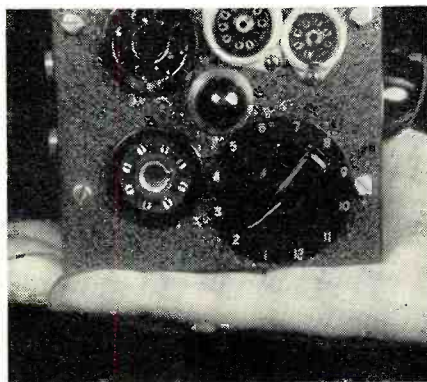The selector switches have twelve positions, of which only nine are used. It is necessary to remember that when testing for continuity externally, the selector switches must be switched to different numbers. —30—



Over-all view of filament and short checker.

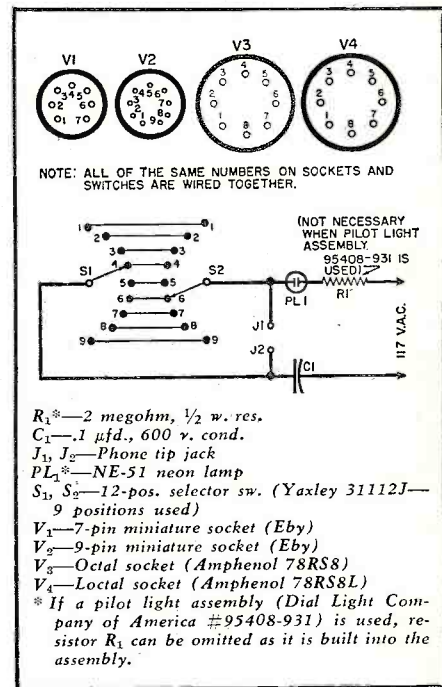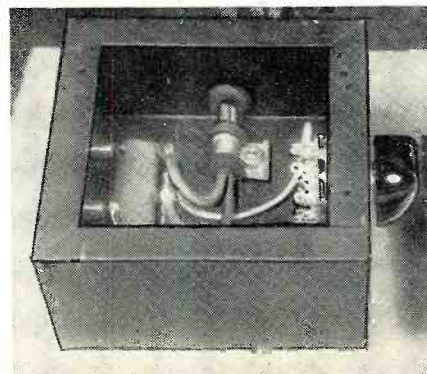
Rear view of the compact and handy tester.



- R_1 —2 megohm, $\frac{1}{2}$ w. res.
 - C_1 —.1 μ fd., 600 v. cond.
 - J_1, J_2 —Phone tip jack
 - PL_1 —NE-51 neon lamp
 - S_1, S_2 —12-pos. selector sw. (Yaxley 31112J—9 positions used)
 - V_1 —7-pin miniature socket (Eby)
 - V_2 —9-pin miniature socket (Eby)
 - V_3 —Octal socket (Amphenol 78RS8)
 - V_4 —Loctal socket (Amphenol 78RS8L)
- * If a pilot light assembly (Dial Light Company of America #95408-931) is used, resistor R_1 can be omitted as it is built into the assembly.

Schematic and parts list for test unit.

Under chassis view showing the wiring.

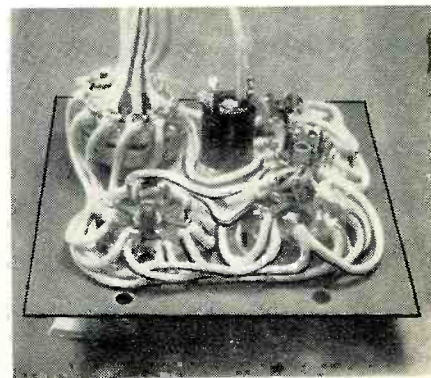



**SCR-274N
COMMAND
and
ARC-5
EQUIPMENT**

RECEIVERS		USED	EXCELLENT	NEW
BC-453-190 to 550 KC		\$29.95		\$49.95
BC-454-3 to 6 MC				24.95
BC-455-6 to 9 MC		\$13.95		19.95
1.5 to 3				34.95
TRANSMITTERS				
A-958-2.1 to 3 MC				29.95
BC-457-4 to 5.3 MC			14.95	29.95
BC-458-5.3 to 7 MC			29.95	34.95
ARC5-T-19-3 to 4 MC			24.95	24.95
BC-459-7 to 9.1 MC				29.95
T-15 ARC 5-500 to 800 KC				
ADDITIONAL EQUIPMENT				
BC-456 Modulator				7.29
BC-450 Control Box (3 Receiver)	1.49	1.95		2.75
BC-451 Control Box (Transmitter)	1.29	1.79		2.35
BC-442 Relay Unit (ANT)				5.69
Plugs: PL-147, 148, 151, 152, 153, 154, 156-EACH		1.25		
Flexible Shafting with gear to fit receivers				2.69
3 Receiver Rack	1.79	2.29		2.95
2 Transmitter Rack	1.69	2.39		3.97
Single Transmitter Rack				3.95
DM-33 Dynamotor for Command Set		2.95		1.95
Mounts for Above Racks				

TUBES	BRAND NEW! JAN! BOXED!	TUBES		
1B22	69c	39/44	29c	826
1B23	\$3.75	100R	49c	811
2B22	51c	114B	29c	843
2C26	99c	915A	99c	864
2C26A	99c	921A	29c	1926
3B22	\$1.19	316A	29c	7193
3D6	39c	388A	59c	9002
7C4	39c	471A	\$1.19	E1148
6Y	19c	82A	\$1.19	RK34
12K8Y	39c	722A	99c	VI92
15R	39c	801A	19c	VT127

TURBO AMPLIFIER
4 tube Amplifier used by U. S. Air Force. 115 V. input at 400 cycles. Without tubes—EXCELLENT! **\$1.19**
SPECIAL

HEADSETS
HS-23 high impedance. BRAND NEW with ear pads. \$5.95
HS-33 low impedance. BRAND NEW with ear pads, cord and PL34 plug. 6.45
HS-33—BRAND NEW—Western Electric
CD-307A Cords. 6 ft. NEW. \$1.49
H-16/U high impedance. Includes two receiving units. 3.95
HS-16 high impedance—used. .98

ARC-5/R-28 2 MTR RCVR
\$25.95
Here is the 2-meter superhet you have been looking for! Absolutely one of the BEST available today! Tunes from 100 to 156 Mcs. in four crystal channels. (Easily converted to continuous tuning.) Tube lineup is as follows:
717A—R.F. 717A—Mixer. 2-12SH7—1st and 2nd I.F. 12SL7—1st audio-spueltu amplifier.
12AV—2nd audio, 12SH7—R.F. Osc.—4th Harmonic Gen.
717A—Trip. 12th Harmonic Gen. 717A—Dbr.—12th Harmonic.
Excellent. used. **\$25.95**

ARMY TEST UNIT 1-236
Meter is contained in a metal box 5 1/2" long x 3 3/4" wide x 3 1/4" deep. Comes complete with test leads and instruction book. Can be used for testing between AC and DC measuring resistance of circuits, checking fuses and testing capacitors. **\$4.19**
SPECIAL

FIELD TELEPHONES
Army surplus, completely reconditioned and electrically tested, using 2 flashlight cells and a pair of interconnecting wires. GUARANTEED. New **\$28.95**. LIKE NEW **\$22.95**

20 POUNDS OF ASSORTED RADIO PARTS
A TERRIFIC BUY AT ONLY... **\$2.79**

BE SURE TO VISIT PLATT'S BRANCH STORE at 159 GREENWICH ST., N.Y.C. (just off Cortland St.). You'll find many bargains that space does not allow us to list here.

MINIMUM ORDER \$2.00
Immediate Delivery—Send 25% deposit on C.O.D. orders. All shipments F.O.B., N.Y.C. (N.Y.C. residents add sales tax to your remittance.)

PLATT ELECTRONICS CORP.
Dept. A. 489 Broome St., N. Y. 13, N. Y.
PHONES: WO 4-0827 and WO 4-0828
BRANCH STORE: 159 Greenwich St., N.Y.C.

PHOTO CREDITS

Page	Credit
35, 36, 37, 40, 41, 42, 46 (center & left)	Radio Corporation of America
46 (right)	Westinghouse Electric Corp.
50, 51	Electro-Voice, Inc.
52, 67	Jay Seymour
72	Stromberg-Carlson Co.
82	Electronic Wholesalers, Inc.
83	Boxoffice Television
87	The Health Company
123	Allan B. Du Mont Laboratories, Inc.
135	Skiatron Electronics & Television Corp.

ADDENDUM
The American Recording Society of New York has advised that its records are cut according to AES-RCA Victor characteristics. This information is intended to supplement the data provided in the equalizer table accompanying Charles P. Boegli's article "New Developments in Phono Equalizers" (April 1953 issue).

SANTA CLARA BARBECUE
THE annual Central California barbecue will be held this year at Cedarbrook Park in San Jose on August 8th.

Sponsored by the Santa Clara County Amateur Radio Association, the event is scheduled for 3 p.m. A full program and plenty of prizes have been planned by the committee in charge.

Reservations may be made by writing the club, P. O. Box 6, San Jose, California. **-30-**

"SUBSCRIBER-VISION"
SKIATRON Electronics & Television Corp. of New York City recently previewed its new "Subscriber-Vision" television system before a group of invited guests.

The new system consists of a "coder," three portable units which are installed at transmitting locations to scramble the video and audio signals and a "decoder" for the home. Only TV set owners who have decoders attached to their receivers can unscramble the jumbled sound and video carriers.

Each decoder, a small unit which can be attached to any standard TV set, has a slot at the top where subscribers insert subscription program cards that are sent to them periodically and are the key to control of the decoder. These cards make it possible for subscribers to pay only for the programs they order.

This system, like other "pay-as-you-see" television units currently being tried out, is subject to FCC approval.

-30-
The Skiatron "Subscriber-Vision" decoder unit with the electronic program card being inserted. With the card fitted into the slot, the TV viewer can then order the program being offered, simply by pushing a button. System was previewed recently.



Train IN Great COYNE shops for big pay jobs

IN Television - Radio

OR Electricity - ELECTRONICS

Learn on REAL EQUIPMENT! in Best Equipped School of its kind in U. S.

Prepare for your future NOW! Come to the Great Shops of Coyne. Get practical training in opportunity fields—TELEVISION-RADIO—ELECTRICITY—ELECTRONICS. Prepare for a better job in industry or better service rating if drafted.

WE TRAIN YOU IN CHICAGO
At Coyne you learn on real, full-size equipment. Trained instructors show you how, then you do shop jobs yourself. No previous experience or advanced education needed.

Approved for Veterans
Finance Plan—Enroll now, pay most of tuition later. If you need part-time work to help out with living expenses while at Coyne, we'll help you get it. Special tuition plan for men of draft age.

FREE BOOK Clip coupon for Big Free Illustrated Book. No salesman will call. Act NOW.

COYNE SCHOOL
Established 1899
510 S. Paulina St., Dept. C3-85H
APPROVED for VETERANS

B. W. COOKE, Pres.
COYNE School
510 S. Paulina St., Chicago 12, Ill., Dept. C3-85H
Send FREE BOOK and full details on:
 TELEVISION-RADIO ELECTRICITY

NAME
ADDRESS
CITY STATE

Here's the new **SHURE** **SLIM-X**

All-Purpose Crystal MICROPHONE



MODEL 777
List Price \$18.95
MODEL 777s
(with switch)
List Price \$20.95
(Price includes
cradle
for mounting
on stand)

Its Versatility and
"Hand-a-Bility" make it
an ideal low-cost
all-purpose microphone



LIGHT! The new "777" Slim-X Microphones are rugged little microphones weighing only 6 ounces! They are designed for good-quality voice and music reproduction. Their versatility and "hand-a-bility" make them ideal for use by lecturers, announcers, instructors, and Hams; for audience participation shows; carnivals; panel and quiz shows; and use with home-recorders. When mounted on either cradle or swivel, the "777" can be removed in a flash (no tools necessary)—simply by lifting it out of the holder. This makes it an ideal "walk-around" hand-held microphone.

TECHNICAL INFORMATION: Smooth frequency response—60 to 10,000 c.p.s.; special-sealed crystal element—for long operating life; high impedance; 7' single-conductor cable, disconnect type. Dimensions: (Microphone only) Length, 4½"; Diameter 1". *Finish:* Rich satin chrome overall.

NOTE: Lavalier cord for suspension of Microphone around neck is available. (optional).

ACCESSORIES FOR "777"

MODEL S38 STAND is a heavy die-cast base. Includes metal screw machine stud for connecting microphone adaptor to stand base.

List Price: \$3.00

MODEL A25 SWIVEL ADAPTOR features a long-life, high-quality swivel connector. Is lined with a long-life nylon sleeve—for noise-free and scratch-free insertion and removal of microphone.

List Price: \$5.00



With Lavalier

On S38 Desk Stand

On Floor Stand

On S38 Desk Stand (With A25 Swivel)

SHURE BROTHERS, Inc.
MICROPHONES and ACOUSTIC DEVICES

225 W. Huron St., Chicago 10, Ill., Cable: SHUREMICRO

INDEX OF Advertisers

AUGUST
1953

While every precaution is taken to insure accuracy, we cannot guarantee against the possibility of an occasional change or omission in the preparation of this index.

ADVERTISER	PAGE	ADVERTISER	PAGE
Airex Radio Corp.	88	McGraw Hill Book Co., Inc.	77
Allied Radio Corp.	99	McIntosh Engineering Laboratories, Inc.	114
American Phenolic Corporation	92	Mallory & Company, P. R.	4th Cover
American Television & Radio Co.	95	Mattison Television & Radio Corp.	108
Amplifier Corp. of America	88	Miles Reproducer Co., Inc.	115
Arka Radio Kits	105	Milwaukee School of Engineering	72
Arrow Sales, Inc.	101	Mosley Electronics, Inc.	18
Ashe Radio Company, Walter	83	Moss Electronics Distributing Co., Inc.	81
Audak Company, Inc.	94	National Electric Products	10, 11
Audel, Publishers	108	National Electronics of Cleveland	120
Bell Telephone Laboratories	30	National Picture Tube Co.	103
Berlant Associates	78	National Radio Institute	3
Boulevard Electronics, Inc.	133	National Schools	21
Brook Electronics, Inc.	90	Newark Electric Company	106
C B S Hyrton	81	Newark Surplus Material Co.	104
Candler System Co.	105	Newcomb Audio Products Co.	129
Cannon Electric Company	134	Peak Electronics Co.	122
Capitol Commodities Co., Inc.	121	Perma Power Company	93
Capitol Radio Engineering Institute	19	Phileo Corporation	22, 23
Centralab	29	Phillips Tube Company, Incorporated	125
Century Electronics Co.	117	Photocon Sales	137
Channel Master Corporation	28	Pickering & Company	6
Cleveland Institute of Radio Electronics	13	Platt Electronics	135
Collins Audio Products Co., Inc.	32	Premier T.V. Radio Supply	91
Columbia Electronics Sales	98	Progressive Electronics Co.	136
Commissioned Electronics Co.	111	RCA Institute, Inc.	33, 108
Communication Equipment Co.	124	R. W. Electronics	115
Concord Radio	137	Radiart Corporation	12
Coyne Electrical School	135	Radio City Products, Inc.	133
Davis Electronics	125	Radio Corporation of America	2nd Cover
DeForest's Training, Inc.	5	Radio Craftsmen, Inc.	123
Delco Radio Corporation	87	Radio Product Sales Co.	124
Eastern Telephone Co.	127	Radio Shack Corporation	86
Editors & Engineers Limited	131	Radio-Television Training Association	15
Eitel-McCullough, Inc.	86	Rad-Tel Tube Co.	117
Electro Sales	98	Rauland Corporation	3rd Cover
Electro Voice	8	Raytheon Mfg. Company	14
Electronic Instrument Co., Inc.	34, 78	Regency	113
Espey Manufacturing Co., Inc.	107	Rinehart Books, Inc.	70
Fair Radio Sales	127	Sams & Co., Inc., Howard W.	80, 121
Fairchild Recording Equipment	119	Schott Company, Walter L.	20
Federal Telephone & Radio Corporation	69	Scientific Electric Company	140
Fisher Radio	24	Shure Brothers, Inc.	136
Franklin Technical Institute	117	South River Metal Products Co., Inc.	86
G & G Radio Supply Company	104	Sprague Electric Products Company	17
G. L. Electronics	129	Sprayberry Academy of Radio	27
Glick & Company, Phillip	109	Stan Burn Radio & Electronics Co.	113
General Cement Manufacturing Co.	25	Standard Surplus	97
Good, Inc., Don	105	Standard Transformer Corporation	18
Goodheart, R. E.	124	Stephan Sales Corp.	129
Greenlee Tool Co.	110	Steve-El Electronics Corp.	70
Greenwich Sales Company	104	Stevens Walden, Inc.	126
Hallcrafters	7	Stuart Electronic Distributors Co.	105
Harjo Sales Co.	115	Sun Parts Distributors, Ltd.	100
Harvey Radio Company	128	Sylvania Electric Products, Inc.	79
Heath Company	26, 73/76	TAB	138
Henry Radio Stores	130	Television Communication Institute	96
Henshaw Radio Supply	100	Terado Company	102
Hi-Lite Electronic Sales Co.	108	Transvision, Inc.	98, 99
Hughes Research & Development Laboratories	82, 87	Triad Transformer Corp.	16
I. E. Manufacturing Co.	89	Tri-State College	109
Indiana Technical College	115	Trio Manufacturing Company	31
Instructograph Company	111	Tung-Sol Electric Co.	132
J F D Mfg. Co.	110	United Technical Laboratories	117
J. J. Electronics	124	University Loudspeaker, Inc.	131
J S H Sales Co.	137	V-M Corp	89
Jensen Industries	78	Valparaiso Technical Institute	124
Jersey Specialty Co.	70	Video Electric Co.	114
Kaar Engineering Company	116	Waldom Electronics, Inc.	107
Krylon, Inc.	112	Weller Electric Corporation	109
L A Ham Shack	119	Wells Sales, Inc.	100
Leeds Radio Co.	114	Western Electronics Co.	100
Leotone Radio Corp.	96	Western Television Institute	104
McGee Radio Company	85	Windsor Electronics Tube Co.	131
McGohan, Inc., Don	96	World Radio Laboratories	103
		Wholesale Radio Parts Co., Inc.	111

Classified

Rate 50c per word. Minimum 10 words

RADIO ENGINEERING

COMPLETE radio, electronics theory & practice: television; broadcasting; servicing; aviation, marine, police radio. 12 or 18 months. Catalog. Valparaiso Technical Institute, Dept. N, Valparaiso, Ind.

FOR SALE

TAPE Recorders, Tapes, Accessories. Unusual Values. Dressner, 624-R East 20th St., N.Y.C. 9.

TUBES and equipment bought, sold, and exchanged. For action and a fair deal, write B. N. Gensler, W2LNI, 136 Liberty, New York 6, N. Y.

NEW RCA 3AP1A original cartons, \$8.75 each. Tubes, surplus—bought, sold. Free list. Write, Mark, Box 14, New York City 72.

DIAGRAMS Radio, 75c; Record Changers, Recorders, \$1.25; Television with Service Data, \$2.00. Where model unknown give part numbers. Kramer's Radio Service, Dept. J53, 36 Columbus Ave., New York 23, N. Y.

ISOLATION transformer 35w 117v sec 117 or 135 plus 6.3v.45a 2 1/2 x 2 1/2 x 3, tap, \$2.45; include postage 3 lbs. Send for flyer. Empire Electronics Company, 409a Avenue L, Brooklyn 30, N. Y.

RECONDITIONED TV sets \$30.00. Jones, 1115 Rambler Ave., Pottstown, Penna. 20" TV set slightly used, \$175.00. 75 assorted tubes, \$50. Clyde E. Bisbee, Ossipee, N. H.

USED Televisions, \$30 up. W4API, 1420 South Randolph, Arlington, Virginia.

BROOK 10 C 3 amplifier, perfect condition, \$180. Gray 106SP arm (never used), \$22. S. Leen, Hyannis, Mass.

TV-PM antennas. All types including UHF. Mounts, accessories. Lowest prices. Wholesale Supply Co., Dept. H, Lunenburg, Mass.

SURPLUS, electric time-switch clocks. Ideal for controlling fans, motors, lights, etc. High quality, money-back guarantee. Mechanism only, no case, \$2.95 plus postage. Deluxe model has additional mechanical clock which keeps mechanism on correct time if power fails, \$3.95 without case. Shipping weight, 5 lbs. C. G. Gray, 3224 Montgall, Kansas City, Mo.

WANTED

AN/APR-1, other "APR-," "ARR-," "TS-," "DE-," ARC-1, ARC-3, ART-13, everything surplus; Tubes, Manuals, Laboratory equipment. Describe, price in first letter. For Sale: Reconditioned Watthour Meters, four for \$10.00. Engineering Associates, 434 Patterson Rd., Dayton 9, Ohio.

WILL buy all ART-13/type T-47A \$200.00; ART-13/type T-47, \$150.00; BC-348 unmodified \$65.00. BC-348 modified \$50.00; APN-9 \$200.00; ARC-3 complete \$600.00; R77 Receivers \$300.00; ARC-1 \$300.00; BC-312 \$60.00; BC-342 \$60.00. Ship via Express C.O.D., subject to inspection to: H. Finnegan, 49 Washington Avenue, Little Ferry, N. J.

CORRESPONDENCE COURSES

USED correspondence Courses and Books sold and rented. Money back guarantee. Catalog free. (Courses bought.) Lee Mountain, Pisgah, Alabama.

SITUATIONS WANTED

DO you need a communications technician in your FM or TV studio? If a holder of an F.C.C. Radiotelephone 2nd Class License (a graduate of Delehanty School of Radio & TV, New York City) can be of service to your organization, why not contact me? E. J. Fahey, 1054 81st Street, Brooklyn 28, New York.

MISCELLANEOUS

TAPE recording Exchange for education, amusement. Foreign members. World Tape Pals, Box 9211, Dallas, Texas.

SPEAKERS repaired, wholesale prices, guaranteed workmanship. Anpreite Speaker Service, 70 Vesey St., New York City 7.

BC348, \$75. BC221, \$50. 12" Stevens 22FR, \$18. Federal Disc Recorder, \$100. Take camera. Sherzer's Photos, Temple, Texas.

!!WANTED!!

In order to supply government and industrial requirements, we are paying top dollar for all types of radio and electronic surplus. We specialize in test equipment and complete radios, such as:

APA, APN, APQ, APR, APS, APT, ARB, ARC, ARN, ART, ATC, BC, DY, I, IE, LM, MG, PE, PU, SCR, TCS, TN, TS, and many others.

WE ESPECIALLY NEED: APA10, APN9, APR4, APS4, ARC1, ARC3, ART13, ATC, BC221, BC342, BC348, BC611, BC721, DY12, DY17, I100, LM10 to LM18, MG149F, MG149H, PUI4, R5/ARN7, R5A/ARN7, SCR718C, TCS, TNI6, TN17, TN18, TN19, TN54, TS3, TS13/AP, TS33, TS35, TS45, TS75, TS76, TS102, TS147/UP, TS148/UP, TS173, TS174, TS175, TS250, TS251, TS323, (ICT, IF, IG, SCT, 5DG, 5F, 5G, 6DG, 6G 115V. 60 c.p.s. Selsyns), and all types of Hewlett Packard, General Radio Co., Measurements Corp., Boonton Radio, Ferris, Leeds & Northrup, and other test equipment.

Please state accurate description, condition, and your lowest price. Explain modifications, if any. We pay freight charges.

PURCHASING AGENTS, ENGINEERS, EXPORTERS, INDUSTRIAL BUYERS, DEALERS, AND INDIVIDUALS. Please send us your requirements.

New Catalog Now Available

PHOTOCON SALES

417 N. Foothill Blvd. Pasadena 8, California Sycamore 2-4131 RYan 1-6751

New Guaranteed		TUBES		Standard Brands	
0A2 51.00	5D21 18.50	803 3.95
0A3 /VR75 1.10	5FP7 1.95	804 10.95
0B2 1.40	5R4GY 1.25	807 1.65
0C3 /VR105 1.00	6AL5W 1.75	807W 9.95
0C3 /VR15090	6AN5 2.30	809 2.95
1A3 1.00	6AS6 2.30	811 2.90
1B23 8.95	6BL6 69.50	813 10.95
1B24 9.50	6BM6 69.50	814 2.95
1B27 12.50	6F4 4.50	828 9.95
1N21B 2.50			829 8.95
1N22 1.25			829B 9.95
1N23 1.25			830 2.75
1N23A 1.25			832A 9.50
1N23B 3.25			836 3.45
1N34A 1.79			837 3.45
1N38 1.25			849 29.50
1N58A 1.25			852 19.95
1N63 2.15			860 4.50
1N69 2.59			861 1.35
IN70 4.25	614 5.25	866A 1.50
2A515 19.95	6K4 3.50	872A 3.25
2C40 1.95	15E 1.75	931A 5.50
2C42 19.95	15R 1.89	95433
2C43 14.95	FG17 3.95	95549
2C44 19.95	FG32 1.95	958A69
2C46 19.95	FG57 14.95	959 2.45
2C51 4.50	FG95 22.00	96045
2C53 2.50	FG104 2.50	100569
2D21 1.35	VT-127A 2.95	161690
2D21W 2.49	100TH 9.50	1625 1.45
2E22 11.00	250TH 1.50	162539
2K22 32.50	304TH 7.95	162639
2K25 28.50	304TL 7.95	2050 1.40
2K26 75.00	307A/RK75 4.25	2051 1.10
2K28 27.50	310A 4.95	5635 8.95
2K34 125.00	350R 3.95	5637 6.50
3B26 3.50	353A 8.95	5638 8.50
3B28 6.50	354A 3.95	5645 8.95
3C22 72.50	417A 8.50	5646 8.95
3C23 9.95	446A 1.19	5651 4.75
3C24 1.50	446A 1.19	5654 2.00
3C33 9.95	703A 1.50	5670 4.30
3C45 12.50	705A 1.50	5672 1.20
3C46 11.95	707B 14.95	5676 1.65
3FP7 1.95	 8.95	5686 4.25
3GP1 3.95	715C 18.00	5687 2.75
3MP7 3.95	717A90	5702 2.95
3K30 299.50	722A 1.95	5703 1.15
4B24 6.95	723A/B 16.95	5704 2.25
4C5 22.00	724A 2.95	5718 8.95
4-6SA 15.00	724B 2.75	5719 8.95
4-12SA 22.50	726A 12.50	5726 2.00
4X150A 22.50	726B 45.00	5744 1.95
4X500A 75.00	801A39	5749 2.25
5BP1 4.50	802 2.95	5814 2.50
5C22 42.00			5814 2.50

WE PAY HIGHEST PRICES FOR YOUR SURPLUS!

Vacuum Capacitors

50-15 \$5.95
50-32 12.50
12-32 10.00
100-20 14.50

Jsh ELECTRONICS
Dept. R-24
7552 Melrose Ave.
Los Angeles 46, California

IT'S READY NOW!

SEND FOR YOUR GIANT NEW Concord Catalog

FALL 1953 EDITION

IT'S GOT **EVERYTHING!**

- Standard Lines
- Special Buys

and **IT'S FREE!**

IMPOSSIBLE BUT TRUE!

SINGLE CHANNEL 5 ELEMENT DELTA-MATCH YAGIS

only \$2.00 ea. Lots of 5

These beautifully fabricated Yagis usually sell for 3 to 5 times our price! Now available for channels 2, 3, 4, 5 and 6, together with detailed instructions for cutting to channels 7, 8, 9, 10, 11, 12 or 13. Sorry, no less than 5 antennas of one channel. SPECIFY CHANNEL WHEN ORDERING.

Free with each order of 5 antennas 1 all-purpose hack-saw with blade and complete instructions for simple conversion of lower frequency Yagis to high frequency Yagis

Stock No. YDM5—Packages of 5 Yagis
Wt. 40 lbs.....Net \$10.00

CONCORD RADIO, 55 Vesey St., New York 7, N. Y. Dept. N-8
Send Giant New FREE Concord Catalog at once to:

Name _____
Address _____
City _____ Zone _____ State _____

Concord Radio
55 Vesey Street, New York 7, N. Y.
Phone DIgby 9-1132



this TV set IMPROVES WITH AGE

Five years old next week—and now better than ever. When the original tube wore out it was replaced with a Rauland. Now pictures are brighter, sharper, clearer. Another Rauland success story—your cue to sell *improvement* through *replacement* with Rauland—and chalk up plus business.

THE RAULAND CORPORATION 4245 NORTH KNOX AVENUE
CHICAGO 41, ILLINOIS · MULBERRY 5-5000
ZENITH SUBSIOIARY

RN-3-19-53-33-24
LLOYD W BREGARD
2722. VICENTE ST
SAN FRANCISCO 16 CALIF


Approved Precision Quality



“Better Than Ever”

“I put a Mallory Vibrator in it. Used 'em for years on all my service work and haven't had a call-back yet.”

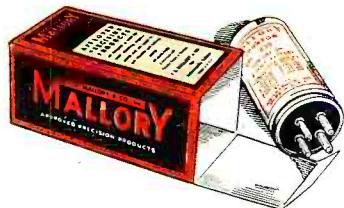That is the main reason you'll find 5 out of 6 service men using Mallory Vibrators for all their service work. When you put a Mallory Vibrator in a set, the job stays sold . . . no call-backs . . . no wasted time to run up costs.



The patented, tuned mechanism in Mallory Vibrators is the secret of their dependability and long life . . . the reason they are more widely used as original equipment than all other makes combined.

These exclusive performance features give you better vibrators, available in a complete line, meeting or exceeding original equipment specifications . . .

Slow contact make . . . for less wear

High contact pressure . . . for low resistance

Fast clean break . . . for reduced arcing

Next time you order vibrators . . . ask for Mallory. It is a sure way to beat the call-back problem . . . be sure all your service jobs stay “sold”.

P. R. MALLORY & CO. Inc.
MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
RECTIFIERS • POWER SUPPLIES • FILTERS • MERCURY BATTERIES

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA